

2 | Power

Power Amplifiers

- Amplifiers that produce voltage amplification or current amplification also produce power amplification
- However, the term **power amplifier** is normally reserved for circuits whose main function is to deliver large amounts of power
- These can be produced using FETs or bipolar transistors, or using special purpose devices such as **thyristors**.


BIPOLAR TRANSISTOR POWER AMPLIFIERS

When designing a power amplifier we normally require a low output resistance so that the circuit can deliver a high output current

- we often use an **emitter-follower** (i.e. buffer amplifier)
- this does not produce voltage gain but has a **low output resistance**, $r_o \approx r_e \approx 25\Omega$
- in many cases the load applied to a power amplifier is not simply **resistive** but also has an **inductive** or **capacitive** element

CURRENT SOURCES AND LOADS

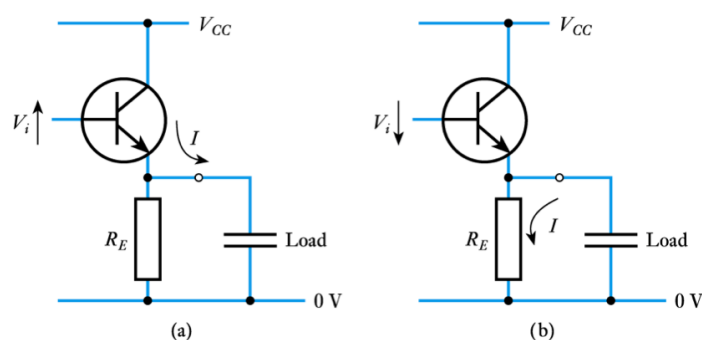- When driving a reactive load, we need to supply current at some times (the output acts as a **current source**)
- At other times we need to absorb current (the output acts as a **current sink**)




sourcing current (good) sinking current (poor)

This circuit is a **good current source** but, the one on the right has a **poor current sink** (since the stored charge must be removed by R_E).


Resistors need to be avoided as they consume a lot of power and take up a lot of space.

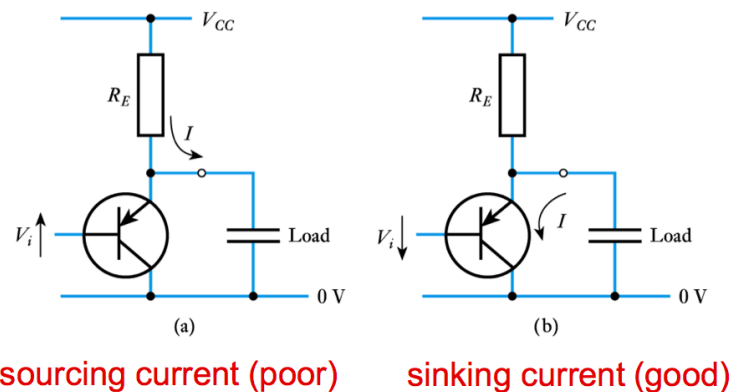An alternative circuit using **pnp** transistors is a **good current sink**, but a **poor current source**, as it uses R_E . The gain is about 1.




Push-Pull Amplifiers

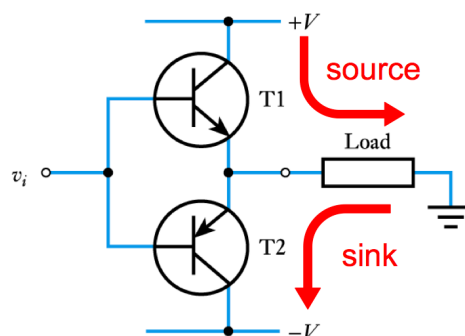- Combining these circuits can produce an arrangement that is both a good current source and a good current sink. This is called a **push-pull amplifier**.
- This has a low output resistance when both sourcing and sinking current
- Only one transistor is turned-on at a time.




PUSH-PULL STAGE

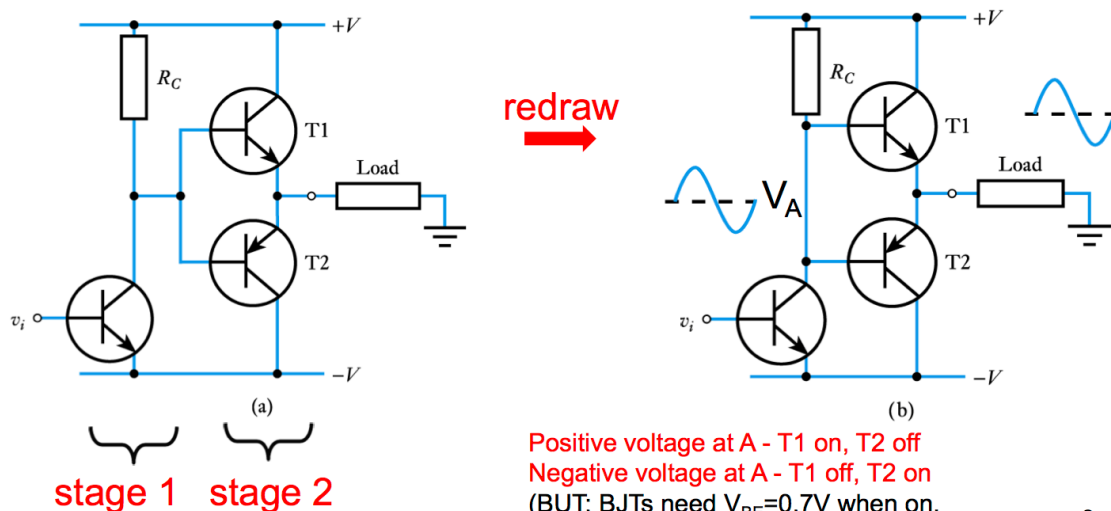

Positive voltage at A - T1 on, T2 off
 Negative voltage at A - T1 off, T2 on
 (BUT: BJTs need $V_{BE}=0.7V$ when on,
 so for signal values $-0.7 < V_A < 0.7V$, none is ON)


Distortion in push-pull amplifiers

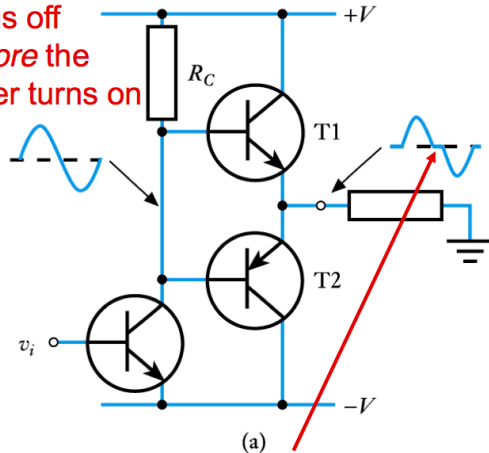One transistor turns off before the other turns on



Therefore this simple circuit produces **cross over distortion**

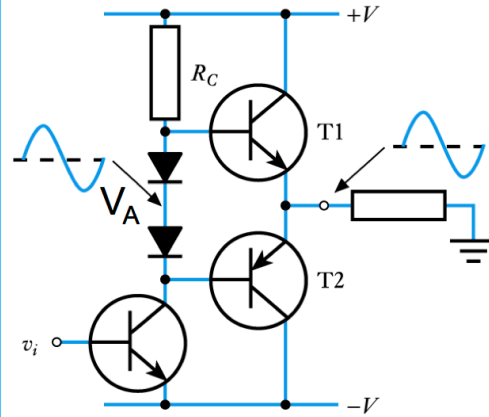This improved circuit produces less distortion




Sets $V_{B(T2)} 2V_{on}$ below $V_{B(T1)}$

$$V_{B(T1)} = V_A + V_{on}, \quad V_{B(T2)} = V_A - V_{on}$$

9

- Although the inclusion of diodes **reduces the distortion**, it does not remove it all together.
- The current through the transistors is greater than that through the diodes, and therefore the turn-on voltage across each diode is slightly less than the V_{BE} of each transistor.
- Therefore, some distortion still remains.

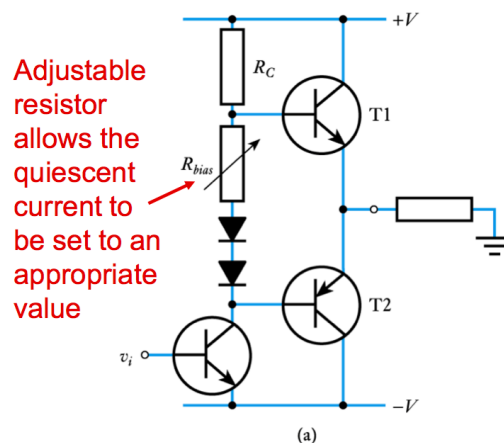Improved push-pull output stage arrangements



AMPLIFIER EFFICIENCY

An important consideration in the design of power amplifiers is efficiency




$$\text{Efficiency} = \frac{\text{Power Dissipated in the Load}}{\text{Power Absorbed from the Supply}}$$

Efficiency determines the power dissipated in the amplifier itself.

Power dissipation is important because it determines the amount of waste heat produced. (Excess heat may require heat sinks, cooling fans etc.).


Classes of Amplifiers

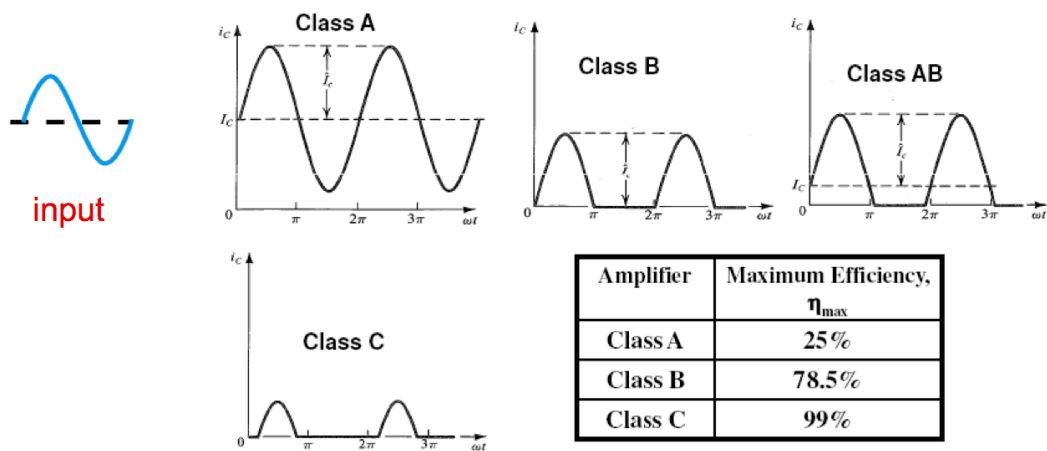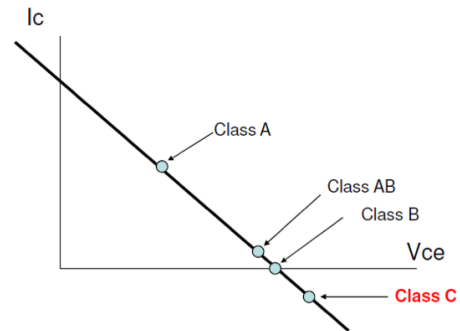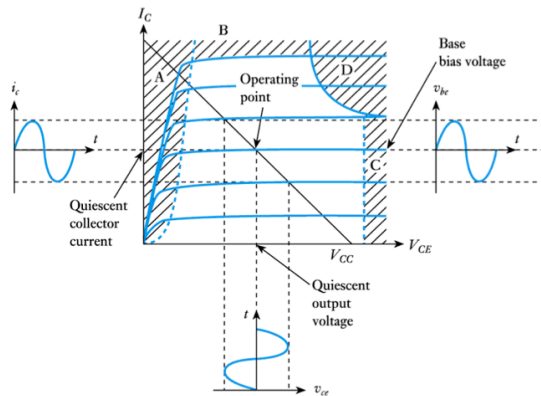Operating point on load line for various output stages




CLASS A

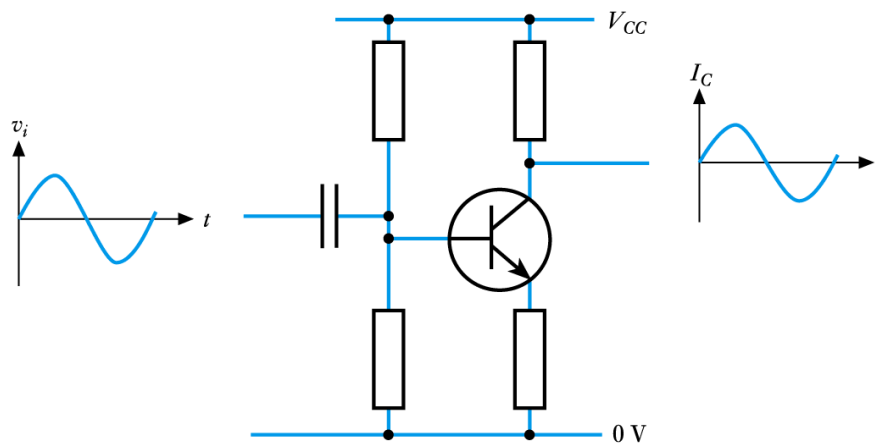- Active device conducts for complete cycle of input signal
- Example shown here with input stage
- Poor efficiency (normally less than 25%)
- Low distortion




CLASS B

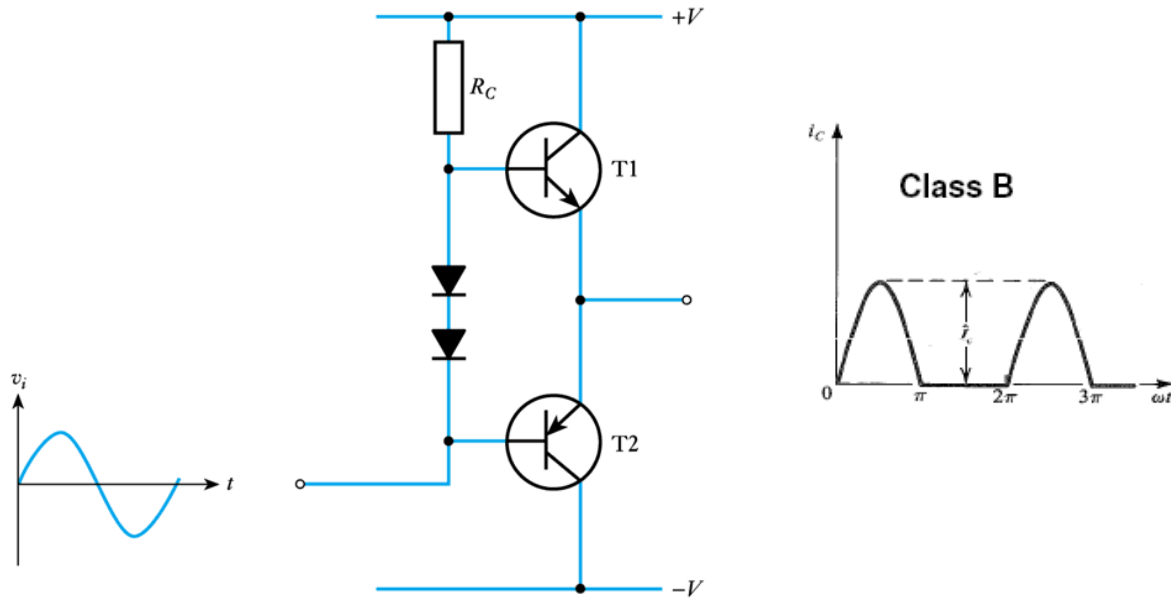- Active devices conduct for half of the complete cycle of input signal (operating point is at the edge)
- Good efficiency (up to 78%)
- Quiescent current is zero
- Considerable distortion




CLASS AB

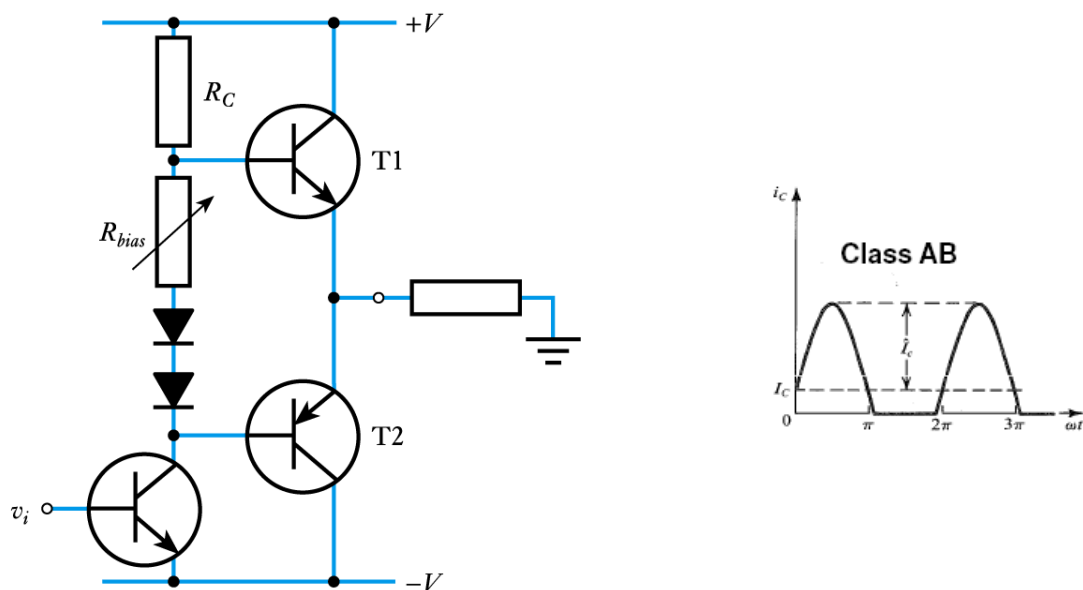- Active devices conduct for more than half but less than the complete cycle of input signal.
- Example shown here (with appropriate R_{bias})
- Efficiency depends on bias
- Distortion depends on bias



CLASS C

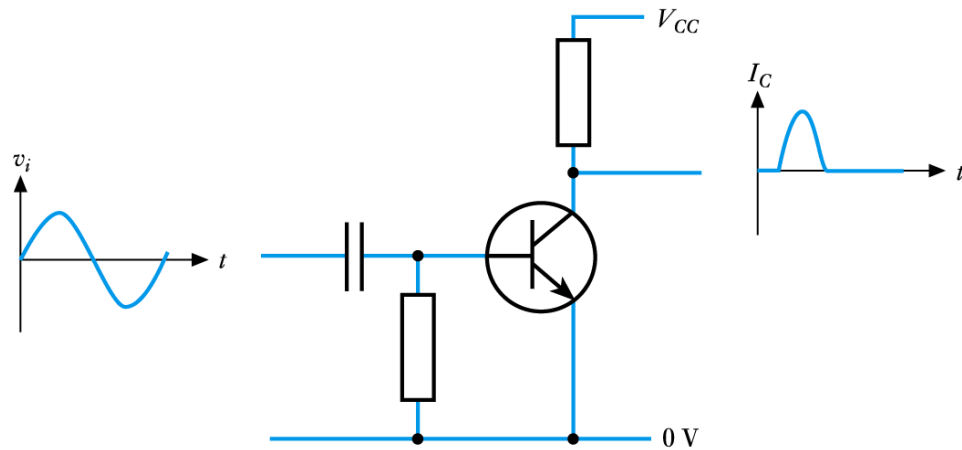- Active devices conducts for less than half the complete cycle of input signal
- Operating point is adjusted accordingly
- Example shown here
- High efficiency (approaching 100%)
- Gross distortion




Design Techniques

OUT STAGE TECHNIQUES

Back to our amplifier:

■ Insert feedback resistors


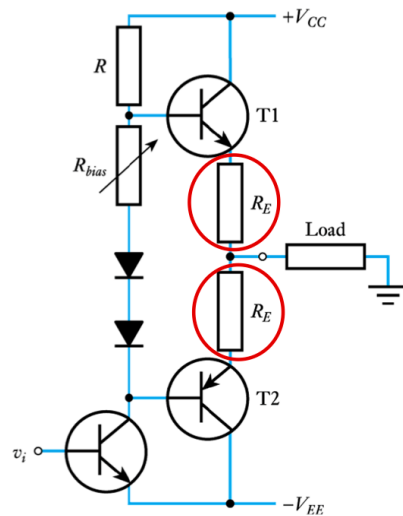
- The stability of the earlier circuit can be improved by adding small emitter resistors
 - These provide negative feedback
 - Stabilises the quiescent current
 - R_{bias} is adjusted to compensate



DARLINGTON TRANSISTORS

Current gain of first transistor is multiplied by that of the second

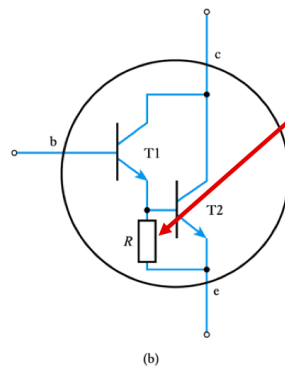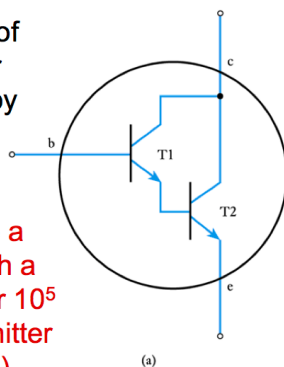Can produce a transistor with a gain of 10^4 or 10^5 (common-emitter configuration)



Often a resistor R is added to improve the turn-off time – typically this is a few kilo-ohms and does not affect the basic operation of the circuit

Base-emitter voltage is about 1.4 V

- A high input resistance buffer amplifier
- **Example:** For the circuit indicated:

Quiescent output voltage

$$V_B \approx V_{CC} \frac{R_2}{R_1 + R_2} = 10 \times \frac{18 \text{ M}\Omega}{10 \text{ M}\Omega + 18 \text{ M}\Omega} = 6.4 \text{ V}$$


$$V_{o(\text{quiescent})} = V_E = V_B - V_{BE} = 6.4 - 1.4 = 5.0 \text{ V}$$

Small signal voltage gain

Small signal voltage gain ≈ 1 (Common Collector)

Small signal input resistance
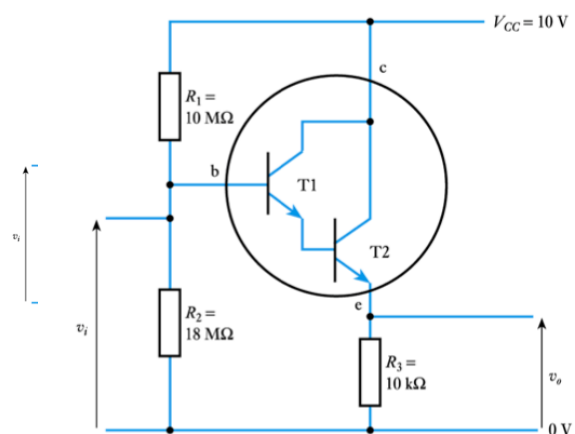
$$R_i \approx R_1 \parallel R_2 = 10 \text{ M}\Omega \parallel 18 \text{ M}\Omega = 6.4 \text{ M}\Omega$$




- A common application of Darlington and complementary Darlington transistors is in the production of power transistors.
- Conventional high-power transistors have a relatively low gain, perhaps 10 - 60
- A typical Darlington power transistor would have a much higher gain – Perhaps a minimum gain of 1000 at 10 A


OUTPUT STAGE TECHNIQUES

■ Insert Darlington transistors

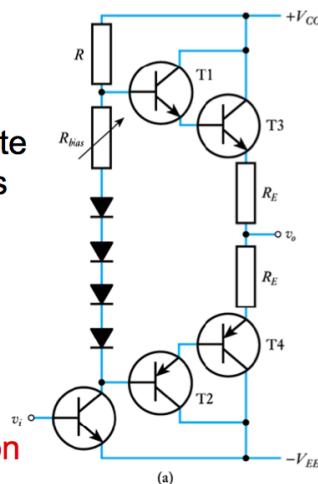- Since the gain of power transistors is normally quite low, Darlington transistors are sometimes used
- The offset between the bases is adjusted to suit
- Darlington pairs provide high input impedance
- Complementary Darlington pairs provide even larger input impedance and almost 100% negative feedback




Use of Darlington pairs

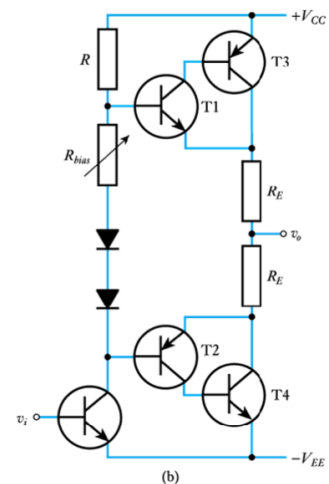


Use of complementary Darlington pairs 25

■ V_{BE} multiplier

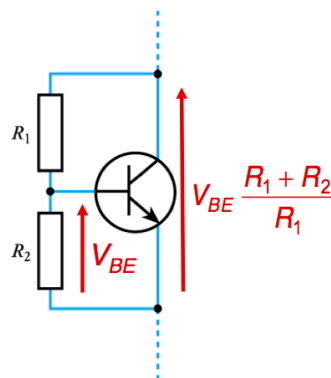- A V_{BE} multiplier arrangement allows the offset voltage between the bases to be set using a single transistor and two resistors




(a) A V_{BE} multiplier

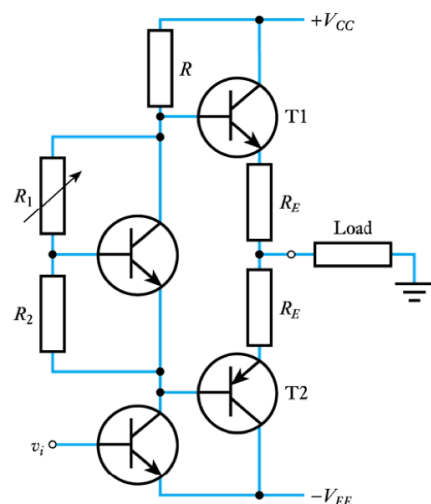


(b) An output stage using a V_{BE} multiplier


Power Amplifier Design Stages

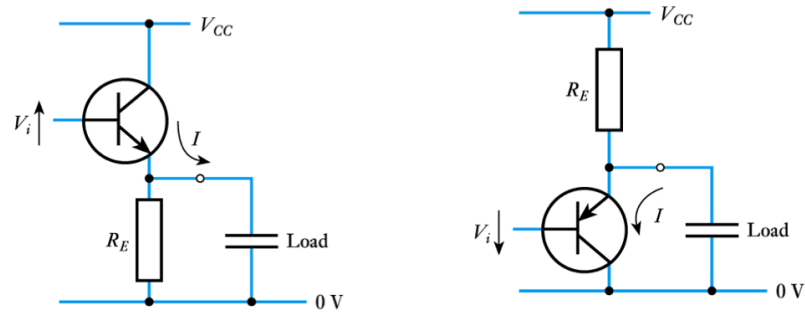

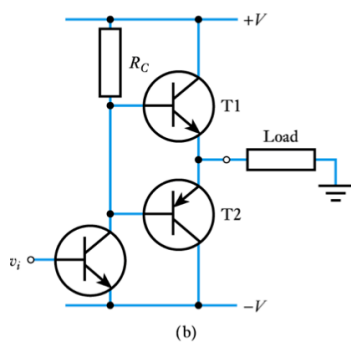
Started with the good current source/sink configurations




(1) Simple push-pull amplifier

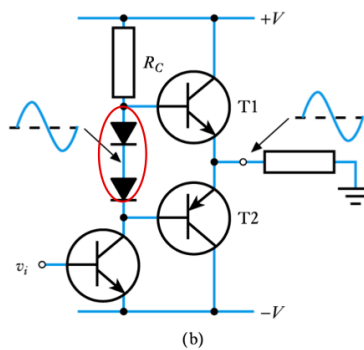


(2) Add diodes to eliminate distortion

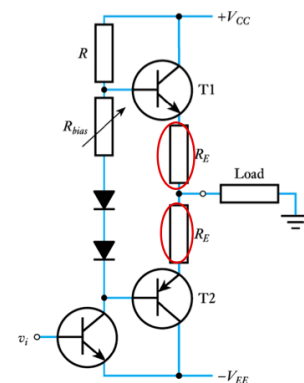

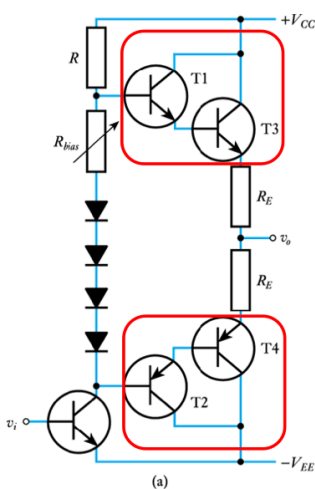
(3) Add resistances for negative feedback



(4a) Add Darlington transistors

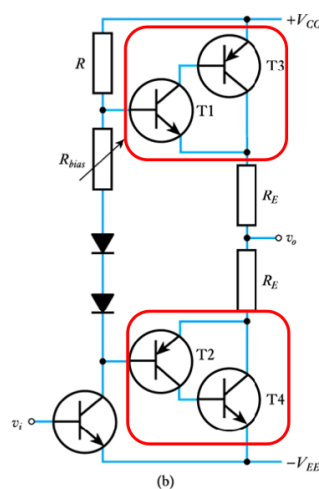

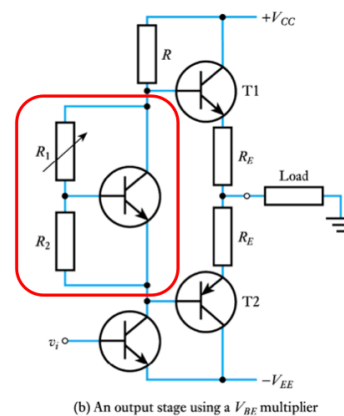(4b) Complementary Darlington transistors




(5) Replace diodes with V_{BE} multiplier


Another example on how to remove resistances

- When producing integrated circuits, resistors are to be avoided
- A range of **active load** arrangements are used

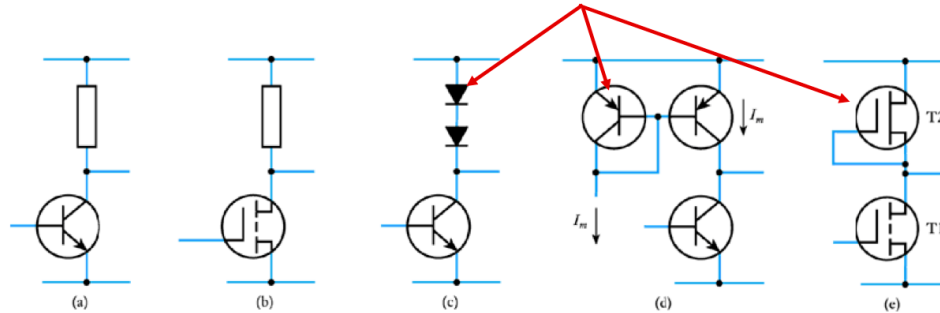These devices are smaller than resistors within ICs




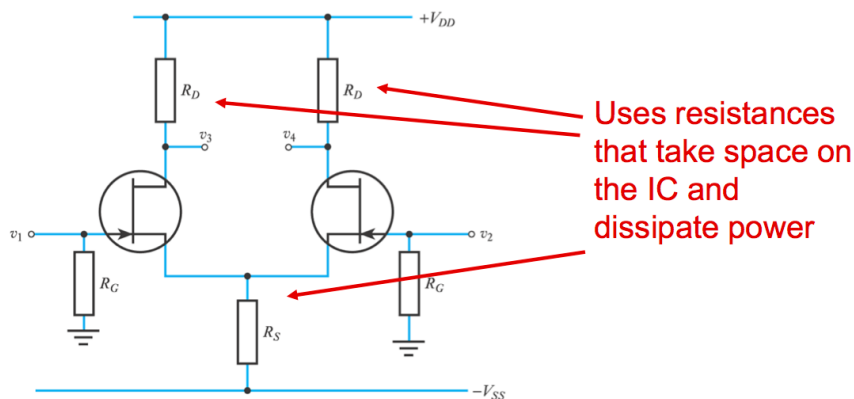- Earlier we studied the differential amplifier



- a long-tailed pair amplifier with a current-mirror load

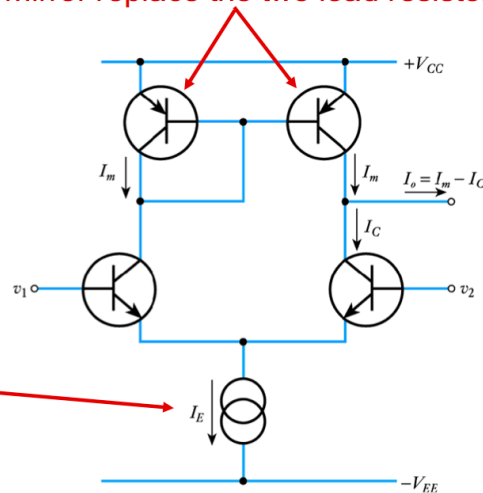
Here the two halves of the current mirror replace the two load resistors



We noted earlier that a current mirror could also be used here as a constant current source

Power Supply Basics


■ Unregulated DC power supplies

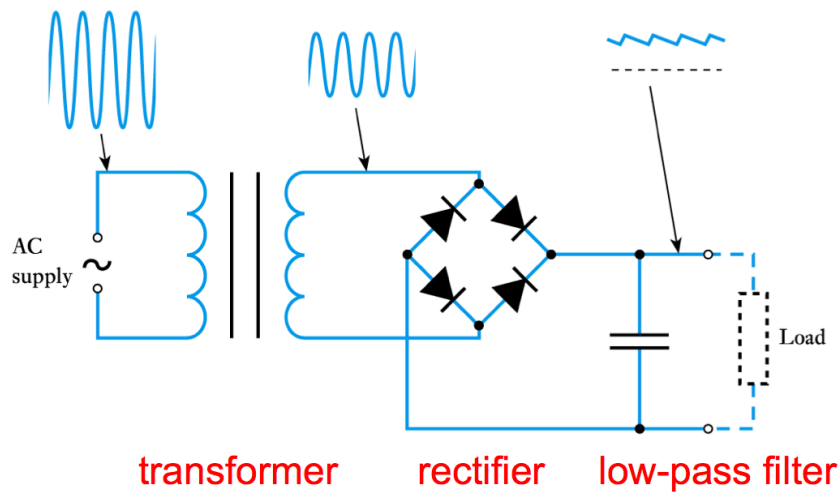


NEED FOR REGULATORS

- A simple power supply consisting of only transformer, rectifier, reservoir and low pass filter however, does have some drawbacks.
- The output voltage of the power supply unit (PSU) tends to fall as more current is drawn from the output. This is due to:
 - The reservoir capacitor being discharged more on each cycle.
 - Greater voltage drop across the resistor.
- These problems can be largely overcome by **including a regulator stage** at the power supply output. The regulator transforms the voltage and takes away any ripple.
- The basic power supply circuits described here are commonly used in DC adaptors supplied with many electronics products.

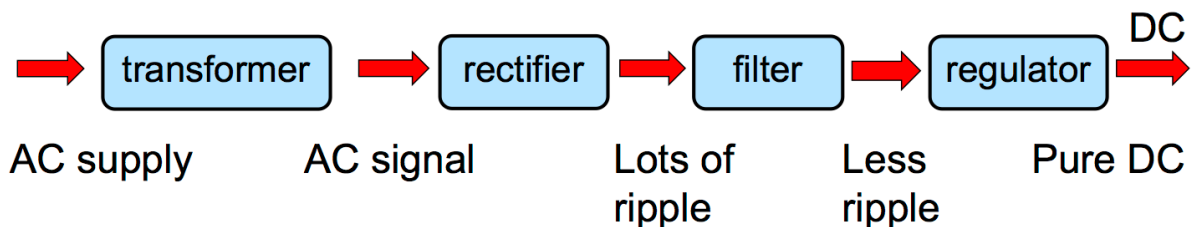DC POWER SUPPLY DESIGN - MAIN STAGES OF SIGNAL CONVERSION




REGULATED DC POWER SUPPLIES

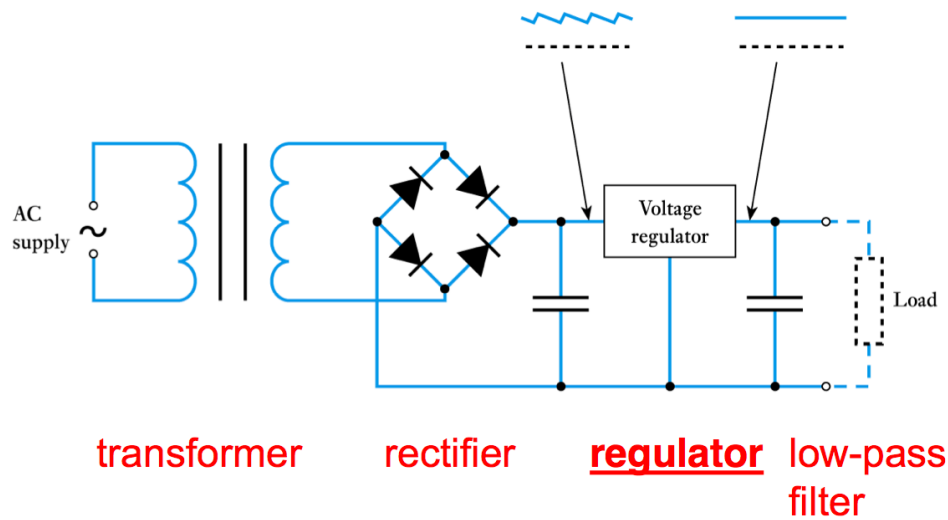

ROLE OF CAPACITORS IN REGULATORS


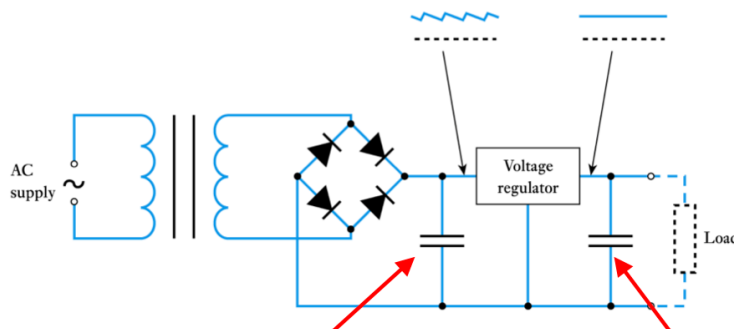
- **Modern day regulators require two capacitors (may/may-not be integrated within the regulator)**





- Decoupling capacitor, to remove high-frequency noise that may be present on the input, (or smooth the ac signal after the bridge)
- Internally the regulator uses a feedback loop to stabilize the output voltage. The second capacitor ensures that the feedback loop is stable

Full Wave Rectifier – Bridge

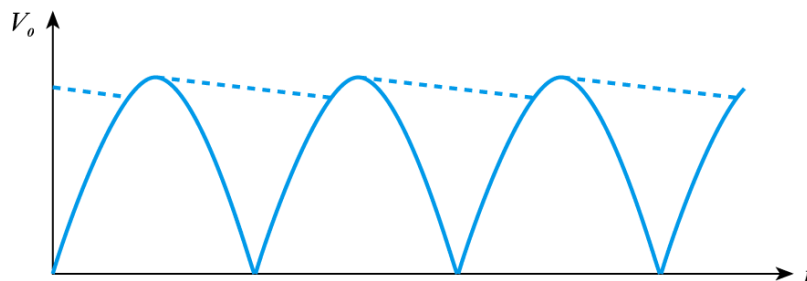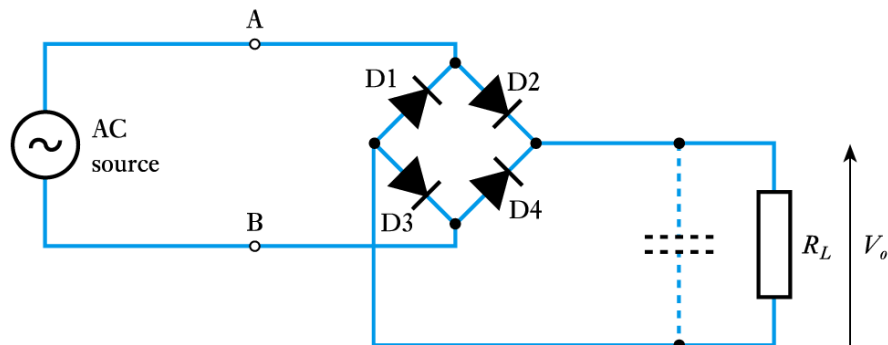
Use of a diode bridge reduces the time for which the capacitor has to maintain the output voltage and thus reduces the ripple voltage;



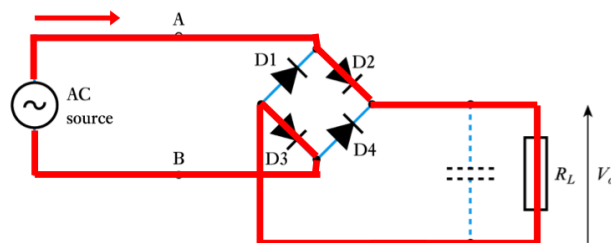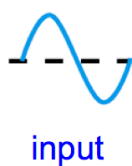- Positive half cycle
- D2, D3 conducting



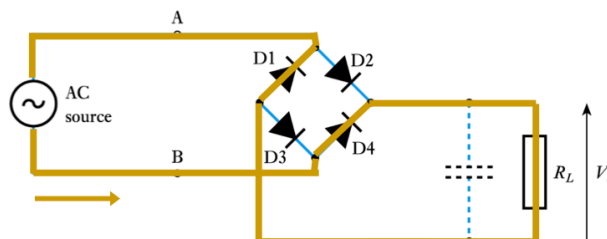
- Negative half cycle
- D1, D4 conducting



Example: Assume a power supply using a bridge rectifier connected to a 60Hz input. The output should be $V_{out} = 13.8V$ across a load resistance of 0.276Ω . A voltage regulator is in series with the bridge, and requires a minimum of $1.2V$.

a) Determine the value of the filter capacitor C which produces a maximum voltage ripple at the input of the regulator of $5V$.

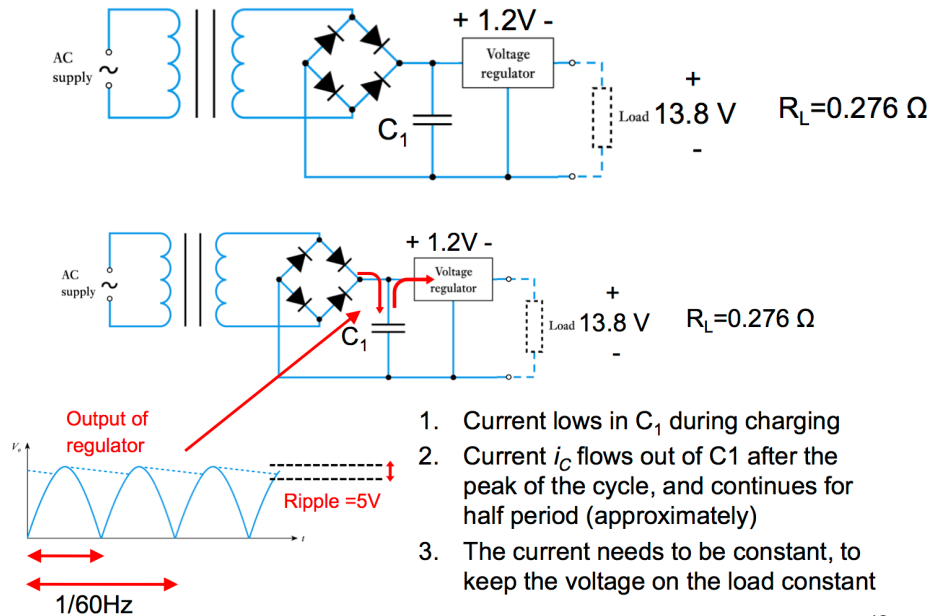b) Determine the rms voltage of the secondary winding of the transformer



▪ **Solution (part a):** The capacitor supplies current into the load for half period to keep its voltage constant. Only $5V$ drop in the C_1 voltage is allowed

The current needed in the load is: $i_c = i_R = \frac{V_R}{R} = \frac{13.8V}{0.276} = 50A$
(supplied by C_1)

The current in/out of the capacitor is: $i_c \approx -C \frac{\Delta v_C}{\Delta t}$ thus $C \approx -i_c \frac{\Delta t}{\Delta v_C}$

The period of the signal out of the bridge is: $\Delta t = \frac{1}{2 \times 60Hz} = 8.33ms$

Since $\Delta v_C = 5V$ $C \approx i_c \frac{\Delta t}{\Delta v_C} = 50A \frac{8.33 \times 10^{-3}s}{5V} = 83.3mF$

▪ **Solution (part b):**

Need to identify the peak voltage, so add all voltage drops:

Remember: The on-voltage for each diode is $V_{on} \sim 0.7V$


The bridge has two diodes switched on at a time

$$\begin{aligned} \text{Therefore } V_p &= V_{out} + V_{reg.} + V_{ripple} + V_{D1} + V_{D2} \\ &= 13.8 + 1.2 + 5 + 0.7 + 0.7 = 21.4V \end{aligned}$$

and

$$V_{rms} = \frac{V_p}{\sqrt{2}} = 15.13V$$


Shunt Regulator (Voltage Reference)

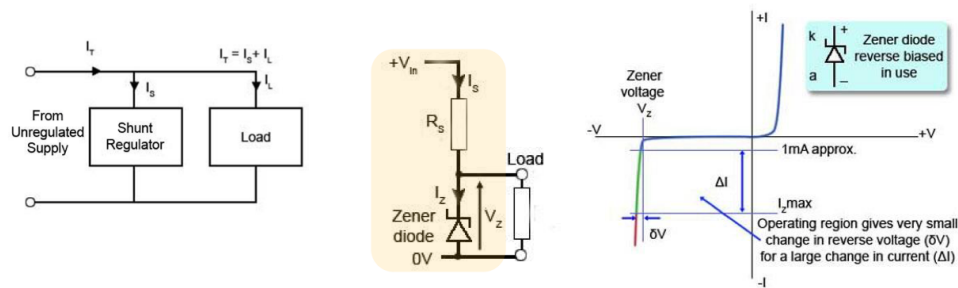

- **Shunt regulator**
 - Ensures a stable voltage across the load at all times.
 - Achieved by regulating the current.
- **Zener diode in reverse breakdown**
 - The extra current goes through the diode, rather than the load.
 - Limitations: small currents/voltages, as much as the diode can handle.

- **Example:** Consider the output of a bridge rectifier. Assume the ac voltage supplying the bridge rectifier has a peak voltage $V_p=17V$ and a 60Hz frequency. Design the rest of the power supply using a Zener diode in the regulator section. The output should be $V_{out}=12V$ and the maximum output current should be 50mA. Assume the Zener diode can handle 1.2W and that the minimum current flow required through the Zener is appr. $\sim 1mA$.
 - What is the maximum current that the Zener can handle?
 - Determine the value of C such that the voltage does not drop below 14V
 - Determine the value of the series resistance
 - Determine the maximum power dissipation in the resistance

Explain the problem:

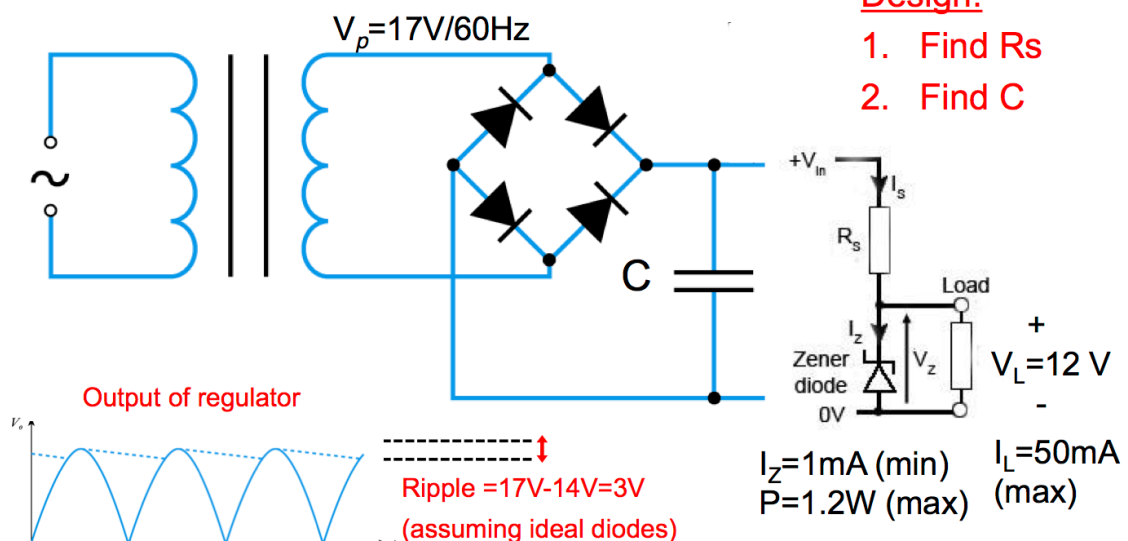

Design:

- Find R_S
- Find C

▪ **Solution (assuming ideal diodes):**

a) $P = v \times i$ and therefore $i_{\max} = \frac{P}{v} = \frac{1.2W}{12} = 0.1A = 100mA$

b) Assuming the diodes are ideal:

$$C \approx -i_c \frac{\Delta t}{\Delta v_c} = 0.05 \frac{1/(2 \times 60Hz)}{17V - 14V} = \frac{0.00833s}{3V} = 139\mu F$$

For C pick something larger (even 5x) to ensure more current can be supplied (Zener current is not constant)

c) Series resistance: $R_s = \frac{\Delta V_{Rs}}{i} = \frac{14V - 12V}{0.05A} = 40\Omega$

For Rs pick something a bit smaller to ensure always at least 12V on output

Design for lowest voltage (14V) – worst case scenario

d) $P_{\max} = \Delta V_{\max}^2 / R_s = (V_{\max}^{in} - V_{out})^2 / R_s = (17V - 12V) / 40\Omega = 0.625W$

▪ **Solution (assuming non-ideal diodes):**

b) Assuming non-ideal, the capacitance will be larger:



$$C \approx -i_c \frac{\Delta t}{\Delta v_c} = 0.05 \frac{1/(2 \times 60Hz)}{(17V - 2 \times 0.7V) - 14V} = \frac{0.00833s}{1.6V} = 260\mu F$$

c) Series resistance: $R = \frac{\Delta V}{i} = \frac{14V - 12V}{0.05A} = 40\Omega$

d) $P_{\max} = \Delta V_{\max}^2 / R = (V_{\max}^{in} - 2 \times V_{on} - V_{out})^2 / R$
 $= (17V - 2 \times 0.7V - 12V)^2 / 40\Omega = 0.324W$

Note: Now the rest of the power is dissipated in the bridge diodes

Series Regulator

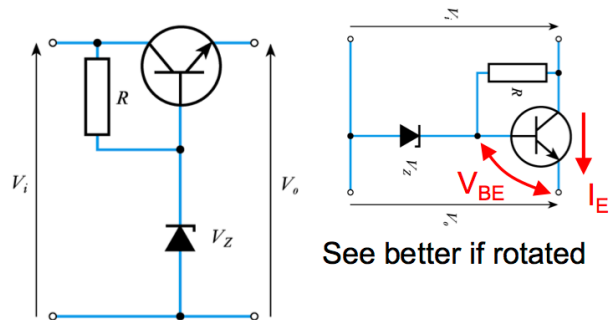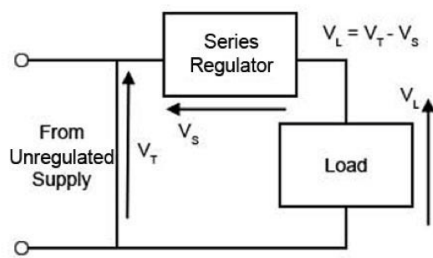



Series regulator

- Ensures a stable voltage across the load at all times.
- Achieved by regulating the voltage drop across it using a negative feedback system.

Stable voltage reference at the base of the power transistor TR by V_Z

- $V_{out} + V_{BE} = V_Z$ therefore $V_{out} = V_Z - V_{BE}$
- If $V_{out} = V_E$ drops, V_{BE} increases, I_E increases, and V_{out} increases again.
- If $V_{out} = V_E$ increases, V_{BE} drops, I_E decreases, and V_{out} decreases again


Voltage regulators

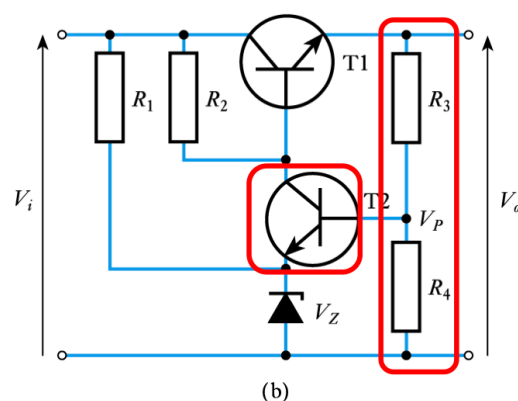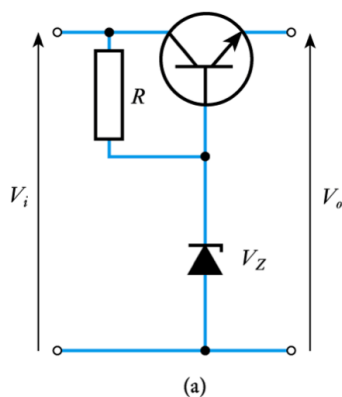

Feedback using T2

If V_{out} drops:

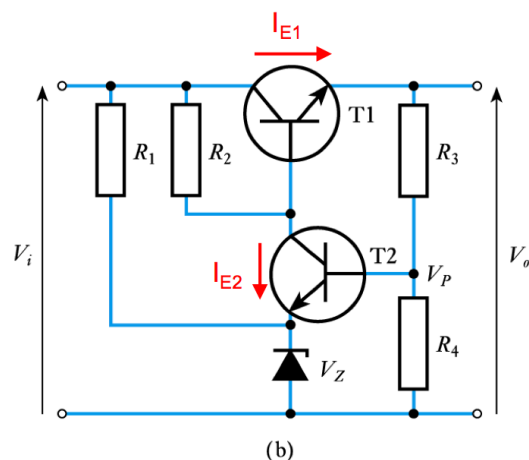
- V_P drops,
- V_{BE2} drops (since V_Z is const.
- I_{E2} drops,
- current through R_2 drops
- the potential difference across R_2 drops,
- $V_{C2} = V_{B1}$ increases (since V_i remains the same),
- V_{BE1} increases,
- I_{E1} increases, and
- V_{out} increases again.



Feedback using T2


If V_{out} increases:

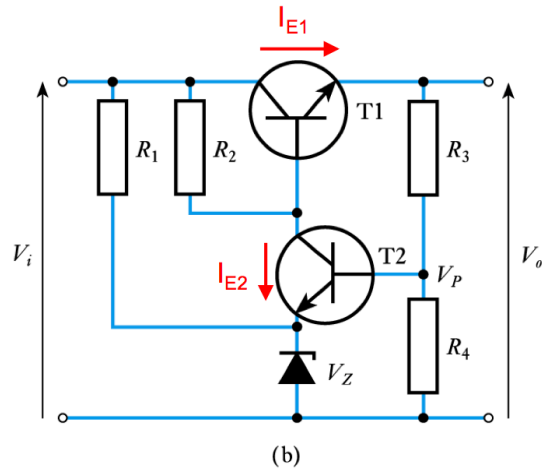- V_P increases,
- V_{BE2} increases (V_Z is const.)
- I_{E2} increases,
- current through R_2 increases
- the potential difference across R_2 increases,
- $V_{C2} = V_{B1}$ drops,
- V_{BE1} drops,
- I_{E1} drops, and
- V_{out} drops again.




The role of the Zener diode

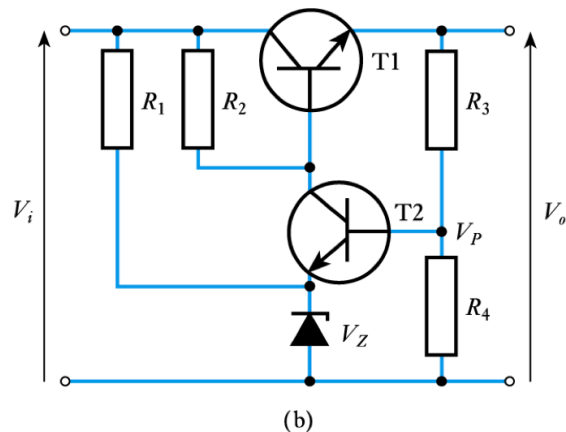- The emitter voltage is held constant by the Zener diode
- Thus the circuit stabilises at a point where the voltage at the midpoint of the potential divider (V_P) is approximately equal to $+0.7V$



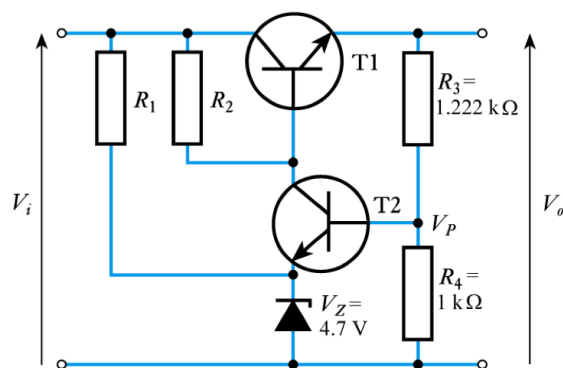- **Example:** Determine the output voltage of the following regulator (assuming that the input voltage is sufficiently high to allow normal operation).




$V_P = V_Z + 0.7V$, therefore;

$$V_o = (V_Z + 0.7V) \frac{R_3 + R_4}{R_4} = (4.7 + 0.7V) \frac{1.222 \text{ k}\Omega + 1 \text{ k}\Omega}{1 \text{ k}\Omega}$$


$$v_o = 12.0 \text{ V}$$

Switch Mode Power Supplies

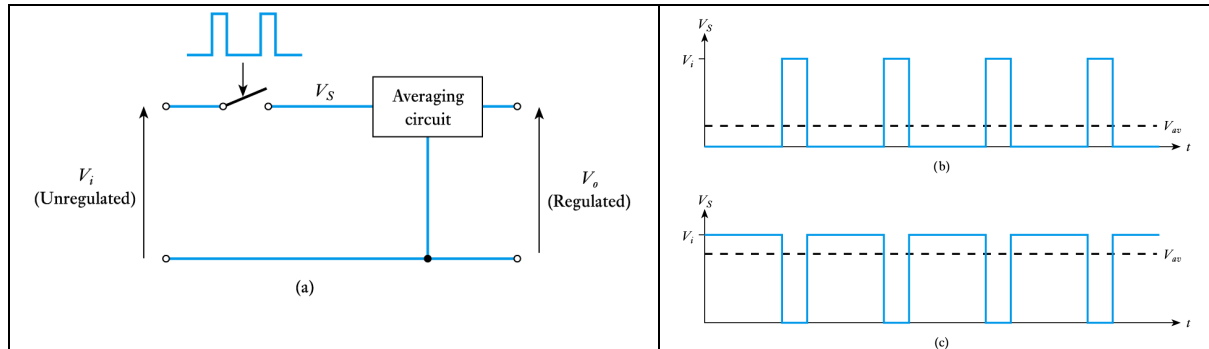- Uses a switching regulator
- Output voltage is controlled by the duty-cycle of the switch
- Uses an averaging circuit to 'smooth' output



AN LC AVERAGING CIRCUIT

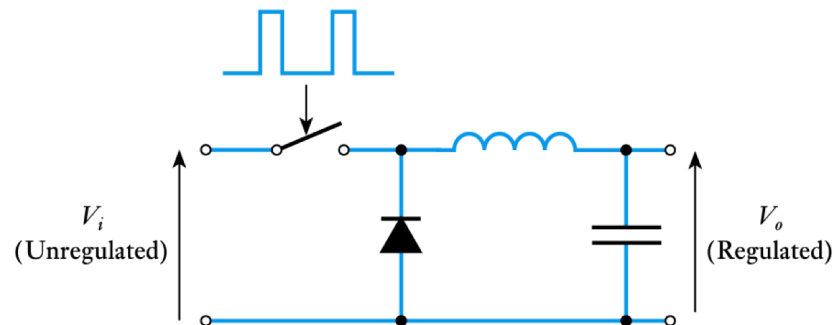


- When switch closed current flows through the inductor and into the capacitor (diode passes no current)
- Although, time current is stored in the inductor
- When switch opens, current is supplied by the inductor
- This forward biases the diode
- Current is taken from the capacitor by the load and the voltage drops (ripple)

Using feedback in a switching regulator

Comparator:

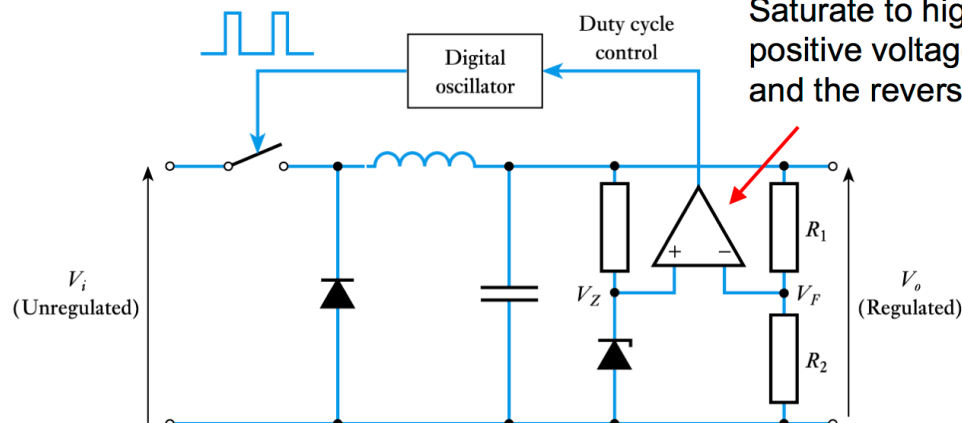When $V_+ > V_-$,
Saturate to highest
positive voltage,
and the reverse



- The voltage V_F is formed from R_1 and R_2 .
- This is compared to the Zener output (V_Z)
- The output from the comparator is used to vary the duty cycle.
- Thus the output is maintained that V_F equals V_Z

$$V_F = V_o \frac{R_2}{R_1 + R_2} = V_Z$$

therefore;

$$V_o = V_Z \frac{R_1 + R_2}{R_2}$$