

THE No.1 MAGAZINE FOR ELECTRONICS TECHNOLOGY & COMPUTER PROJECTS

EVERYDAY

JUNE 2004

PRACTICAL ELECTRONICS

£3.10

MIDI SYNCHRONOME
An audio/visual metronome

**CRAFTY
COOLING**
Peltier cooler

QUICKSTEP
Versatile stepper
motor driver

PLUS
CLINICAL THERAPY
Electronics in medicine

TEACH-IN - PART 8
Movement detection

BUY EPE
ON THE WEB
www.epemag.com



<http://www.epemag.wimborne.co.uk>



Colour CCTV camera. 8mm lens, 12V d.c. 200mA 582x628 Resolution 380 lines Automatic aperture lens Mirror function PAL Back Light Compensation MLR, 100x40x40mm. Ref EE2 £75.90

Built-in Audio .15lux CCD camera 12V d.c. 200mA 480 lines s/n ratio >48db 1V-P-P output 110mm x 60mm x 50mm. Ref EE1 £108.90



Metal CCTV camera housings for internal or external use. Made from aluminium and plastic they are suitable for mounting body cameras in. Available in two sizes 1 - 100 x 70 x 170mm and 2 - 100 x 70 x 280mm. Ref EE6 £24.20 EE7 £28.60 multi-position brackets. Ref EE8 £8.80

Excellent quality multi-purpose TV/TFT screen, works as just a LCD colour monitor with any of our CCTV cameras or as a conventional TV. Ideal for use in boats and caravans 49.7MHz-91.75MHz VHF channels 1-5, 168-25MHz-222.75MHz VHF channels 6-12, 471.25MHz-869.75MHz, Cable channels 112-325MHz-166.75MHz Z1-Z7, Cable channels 224-25MHz-446.75MHz Z8-Z35 5" colour screen. Audio output 150mW. Connections, external aerial, earphone jack, audio/video input, 12V d.c. or mains, Accessories supplied Power supply, Remote control, Cigar lead power supply, Headphone Stand/bracket. 5" model £152.90 Ref EE9, 6" model £163.90 Ref EE10



Self-cocking pistol p1cr002 crossbow with metal body. Self-cocking for precise string alignment Aluminium alloy construction High tec fibre glass limbs Automatic safety catch Supplied with three bolts Track style for greater accuracy. Adjustable rear sight 50lb drawweight 150ft sec velocity Break action 17" string 30m range £23.84 Ref PLCR002

Fully cased IR light source suitable for CCTV applications. The unit measures 10 x 10 x 150mm, is 12V d.c. operated and contains 54 infra-red LEDs. Designed to mount on a standard CCTV camera bracket. The unit also contains a daylight sensor that will only activate the infra-red lamp when the light level drops below a preset level. The infra-red lamp is suitable for indoor or exterior use, typical useage would be to provide additional IR illumination for CCTV cameras. £53.90. Ref EE11



Mains operated and designed to be used with any CCTV camera causing it to scan. The clips can be moved to adjust the scan angle, the motor reversing when it detects a clip. With the clips removed the scanner will rotate constantly at approx 2-3rpm. 75 x 75 x 80mm £25.30. Ref EE12

Colour CCTV Camera measures 60x45mm and has a built-in light level detector and 12 IR LEDs 0.2 lux 12 IR LEDs 12V d.c. Bracket Easy connect leads £75.90. Ref EE15



A high quality external colour CCTV camera with built-in infrared LEDs measuring 60 x 60 x 60mm Easy connect leads colour Waterproof PAL 1/4in. CCD 542 x 588 pixels 420 lines 0.05 lux 3.6mm F2.78 deg lens 12V d.c. 400mA Built-in light level sensor. £108.90. Ref EE13

Colour pinhole CCTV camera module with audio. Compact, just 20x20x20mm, built-in audio and easy connect leads PAL CMOS sensor 6-9V d.c. Effective Pixels 628x582 Illumination 2 lux Definition >240 Signal/noise ratio >40db Power consumption 200mW £38.50. Ref EE21



A small colour CCTV camera measuring just 35 x 28 x 36mm. Supplied complete with bracket, microphone and easy connect leads. Built-in audio. Colour 380 line resolution PAL 0.2 lux +18db sensitivity. Effective pixels 628 x 582 Power source 6-12V d.c. Power consumption 200mW £39.60. Ref EE16

Complete wireless CCTV system with video. Kit comprises pinhole colour camera with simple battery connection and a receiver with video output. 380 lines colour 2.4GHz 3 lux 6-12V d.c. manual tuning Available in two versions, pinhole and standard. £86.90 (pinhole) Ref EE17, £86.90 (standard). Ref EE18



Small transmitter designed to transmit audio and video signals on 2.4GHz. Unit measures 45 x 35 x 10mm. Ideal for assembly into covert CCTV systems Easy connect leads Audio and video input 12V d.c. Complete with aerial Selectable channel switch £33. Ref EE19




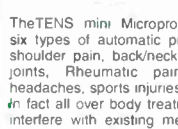2.4GHz wireless receiver Fully cased audio and video 2.4GHz wireless receiver 190x140x30mm, metal case, 4 channel, 12V d.c. Adjustable time delay, 4s, 8s, 12s, 16s. £49.50. Ref EE20

The smallest PMR446 radios currently available (54x87x37mm). These tiny handheld PMR radios not only look great, but they are user friendly & packed with features including VOX, Scan & Dual Watch. Priced at £64.90 PER PAIR they are excellent value for money. Our new favourite PMR radios! Standby: - 35 hours Includes: - 2 x Radios, 2 x Belt Clips & 2 x Carry Strap £64.90 Ref ALAN1 Or supplied with 2 sets of rechargeable batteries and two mains chargers £93.49. Ref Alan2



Beltronics BEL550 Euro radar and GATSO detector Claimed Detection Range: GATSO up to 400m. Radar & Laser guns up to 3 miles. Detects GATSO speed cameras at least 200 metres away, plenty of time to adjust your speed £350.90. Ref BEL550



TheTENS mini Microprocessors offer six types of automatic programme for shoulder pain, back/neck pain, aching joints, Rheumatic pain, migraines headaches, sports injuries, period pain. In fact all over body treatment. Will not interfere with existing medication. Not suitable for anyone with a heart pacemaker. Batteries supplied £21.95 Ref TEN327 Spare pack of electrodes £6.59. Ref TEN327X



Dummy CCTV cameras These motorised cameras will work either on 2 AA batteries or with a standard DC adapter (not supplied) They have a built-in movement detector that will activate the camera if movement is detected causing the camera to pan! Good deterrent. Camera measures 20cm high, supplied with fixing screws. Camera also has a flashing red l.e.d. built in. £10.95. Ref CAMERAB

INFRA-RED FILM 6" square piece of flexible infra-red film that will only allow IR light through. Perfect for converting ordinary torches, lights, headlights etc to infra-red output only using standard light bulbs Easily cut to shape 6" square £16.50. Ref IRF2 or a 12" sq for £34.07 IRF2A



GASTON SEALED LEAD-ACID BATTERIES


1.3AH 12V @ £5.50 REF GT1213
3.4AH 12V @ £8.80 REF GT1234
7AH 12V @ £8.80 REF GT127
17AH 12V @ £19.80 REF GT1217



All new and boxed, bargain prices. Good quality sealed lead-acid batteries

SOLAR PANEL 10 watt silicon solar panel, at least 10 year life. 365 x 25mm, waterproof, ideal for fixing to caravans, boat, motorhomes etc. Nicely made unit with fixing holes for secure fittings. Complete with leads and connectors. Anodised frame. Supplied with two leads, one 3M lead is used for the op with two croc clips, the other lead is used to connect extra panels. Panels do NOT require a blocking diode, they can be left connected at all times without discharging the battery. £43.49. REF PAN

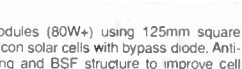8A solar regulator 12V, 96 watt, 150mm x 100mm x 25mm, £30 REF SOLREG2



High-power modules (80W+) using 125mm square multi-crystal silicon solar cells with bypass diode. Anti-reflection coating and BSF structure to improve cell conversion efficiency: 14%. Using white tempered glass, EVA resin, and a weatherproof film along with an aluminium frame for extended outdoor use. system Lead wire with waterproof connector. Four sizes, 80W 12V dc, 1200 x 530 x 35mm. £315.17. REF NER80. 123W 12V d.c., 1499 x 662 x 46mm, £482.90. REF NDL3 125W 24V, 1190 x 792 x 46mm, £482.90. REF NEL5 and 165W 24V, 157 x 826 x 46mm, £652.30



BULL GROUP LTD
UNIT D, HENFIELD BUSINESS PARK,
HENFIELD, SUSSEX BN5 9SL
TERMS: CASH, PO, CHEQUE PRICES + VAT
WITH ORDER PLUS £5.50 P&P (UK) PLUS VAT.
24 HOUR SERVICE £7.50 (UK) PLUS VAT.
OVERSEAS ORDERS AT COST PLUS £3.50
Tel: 0870 7707520 Fax 01273 491813
Sales@bullnet.co.uk
www.bullnet.co.uk


THE TIDE CLOCK. These clocks indicate the state of the tide. Most areas in the world have two high tides and two low tides a day, so the tide clock has been specially designed to rotate twice each lunar day (every 12 hours and 25 minutes) giving you a quick and easy indication of high and low water. The Quartz tide clock will always stay calibrated to the moon. £23.10 REF TIDEC



LINEAR ACTUATORS 12-36V D.C. BUILT-IN ADJUSTABLE LIMIT SWITCHES. POWER COATED 18in. THROW UP TO 1,000lb. THRUST (400lb. RECOMMENDED LOAD). SUPPLIED WITH MOUNTING BRACKETS DESIGNED FOR OUTDOOR USE. These brackets originally made for moving very large satellite dishes are possibly more suitable for closing gates, mechanical machinery, robot wars etc. Our first sale was to a company building solar panels that track the sun! Two sizes available, 12in. and 18in. throw. £32.95. REF ACT12. £38.45 REF ACT18



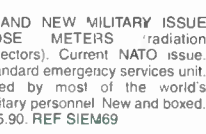
POWERSAFE DEEP CYCLE BATTERIES
12V 51AH. NOW ONLY £29.95 EACH
YUASA 6V 100AH NOW ONLY £25 + £5 POSTAGE EACH



NIGHT VISION SYSTEM. Superb hunting rifle sight to fit most rifles, grooved for a telescopic sight. Complete with infra-red illuminator. Magnification 2.7x. Complete with rubber eye shield and case. Opens up a whole new world! Russian made. Can be used as a hand-held or mounted on a rifle. £108.90. REF PN1



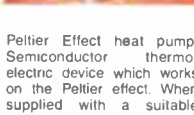These Samarium magnets measure 57mm x 20mm and have a threaded hole (5/16th UNF) in the centre and magnetic strength of 2.2 gauss. We have tested these on a steel beam running through the offices and found that they will take more than 170lb (77kg) in weight before being pulled off. With keeper £21.95. REF MAG77.




Peltier Effect heat pump. Semiconductor thermoelectric device which works on the Peltier effect. When supplied with a suitable electric current, can either cool or heat. Also when subject to an externally applied temperature gradient can produce an electric current. Ideal for cooling or controlling the temperature of sub assemblies. Each module is supplied with a comprehensive 18-page Peltier design manual featuring circuit designs, design information etc. etc. The Peltier manual is also available separately. Maximum watts 56 2 40 x 40mm Imax, 5.5A Vmax, 16.7 Tmax (c-dry N2), 72. £32.95 (inc. manual. REF PELT1. Just manual £4.40 REF PE-T2



New transmitter, receiver and camera kit. £75.90. Kit contains four channel switchable camera with built-in audio, six IR l.e.d.s and transmitter, four channel switchable receiver, 2 power supplies, cables, connectors and mounting bracket. £75.90. Wireless Transmitter, Black and white camera (75 x 50 x 55mm). Built-in 4 channel transmitter (switchable).

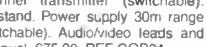Audio built-in 6 IR l.e.d.s. Bracket/stand. Power supply 30m range Wireless Receiver 4 channel (switchable). Audio/video leads and scart adapter. Power supply and manual. £75.90. REF COP24.



This miniature Stirling Cycle Engine measures 7in. x 4in. and comes complete with built-in alcohol burner. Red flywheels and chassis mounted on a green base, these all-metal beauties silently running at speeds in excess of 1,000 r.p.m. attract attention and create awe wherever displayed. This model comes completely assembled and ready to run. £106.70. REF SOL1



SHOP ONLINE
WWW.BULLNET.CO.UK

ISSN 0262 3617

PROJECTS ... THEORY ... NEWS ...
COMMENTS ... POPULAR FEATURES ...

VOL. 33. No. 6 JUNE 2004

Cover illustration by jgr22



EVERYDAY

PRACTICAL ELECTRONICS

INCORPORATING ELECTRONICS TODAY INTERNATIONAL

www.epemag.wimborne.co.uk

EPE Online: www.epemag.com

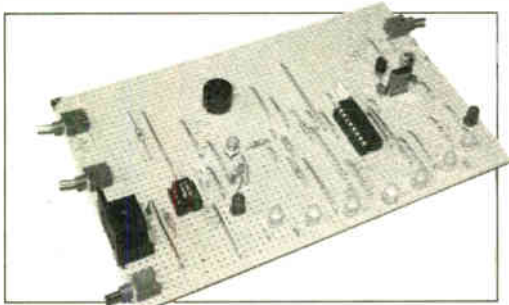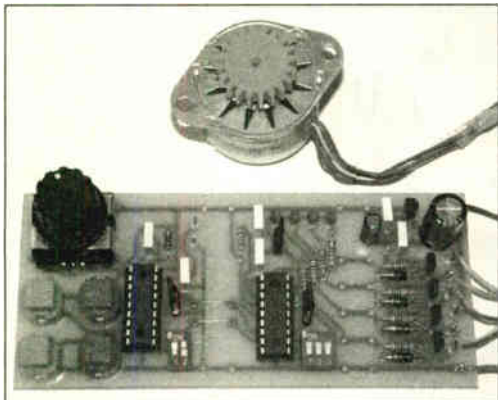

© Wimborne Publishing Ltd 2004. Copyright in all drawings, photographs and articles published in EVERYDAY PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or in part are expressly forbidden.

Projects and Circuits

- PIC QUICKSTEP** by Andy Flind 376
A simple and versatile stepper motor driver and controller
- INGENUITY UNLIMITED - Sharing your Ideas with others** 382
White Noise Generator; Pressure Pad; Dual-Mode Charger; Simple Siren
- CRAFTY COOLING** by Terry de Vaux-Balbirnie 392
Make a drink can cooler and learn about Peltier and Seebeck effects
- BODY DETECTOR Mk2** by Thomas Scarborough 398
Create your own invisible defence shield!
- MIDI SYNCHRONOME** by David Clark 408
Improve your musical time-keeping when recording MIDI instruments

Series and Features

- CLINICAL ELECTROTHERAPY** by Ed Bye 386
Electrotherapy developments through the ages, and some possible future progress
- TECHNO TALK** by Andy Emmerson 396
Not surprisingly, self-destructing electronic products are a mixed blessing!
- INTERFACE** by Robert Penfold 406
More practical suggestions for case-modding your PC
- PIC N' MIX** by Andrew Jarvis 414
A potted history of *EPE Toolkit* and an overview of other low-cost PIC programmers
- NET WORK - THE INTERNET PAGE** surfed by Alan Winstanley 419
Google, Alta Vista, MSN and Yahoo! web search engines
- TEACH-IN 2004 - 8. Movement Detection** by Max Horsey 420
Continuing our 10-part tutorial and practical series - how to apply electronics meaningfully
- CIRCUIT SURGERY** by Alan Winstanley and Ian Bell 426
Power Op.Amps; Servo Controller; Brazen Terminology; Current Flow and Outputs

Regulars and Services

- PIC PROJECTS VOL 1 CD-ROM** Invaluable to all PICKers! 370
A plethora of 20 "hand-PICKed" *EPE* past projects
- EDITORIAL** 375
- NEWS** - Barry Fox highlights technology's leading edge 384
Plus everyday news from the world of electronics
- READOUT** John Becker addresses general points arising 403
- BACK ISSUE CD-ROMS** Single-source shopping for issues you've missed 404
- SHOPTALK** with David Barrington 415
The *essential* guide to component buying for *EPE* projects
- PLEASE TAKE NOTE** 415
Toolkit TK3 software update
- CD-ROMS FOR ELECTRONICS** 416
A wide range of CD-ROMs for hobbyists, students and engineers
- DIRECT BOOK SERVICE** 428
A wide range of technical books available by mail order, plus more CD-ROMs
- PRINTED CIRCUIT BOARD AND SOFTWARE SERVICE** 431
PCBs for *EPE* projects. Plus *EPE* project software
- ELECTRONICS MANUALS** 432
Essential CD-ROM reference works for hobbyists, students and service engineers
- ADVERTISERS INDEX** 436

Our July 2004 issue will be published on Thursday, 10 June 2004. See page 367 for details

Readers Services • Editorial and Advertisement Departments 375

Visit our website
www.distel.co.uk

THE ORIGINAL SURPLUS WONDERLAND!

THIS MONTH'S SELECTION FROM OUR VAST EVER CHANGING STOCKS

Surplus always
wanted for cash!

GIANT 10" 7-SEGMENT DISPLAYS

A bulk purchase enables us to bring to you these GIANT 7-segment digital displays at a now affordable price!! The 10" character size gives exceptional readability at long distances and enables a host of applications including, score boards, digital clocks, counters, event timers etc. As the units are a simple electro-mechanical device and operate from 12V DC, simple switching via switches, relays, PIC or PC may be used to control single or multiple digits. Units feature integral Zero Power memory which greatly simplifies design. For an excellent DIY practical article, see the May issue of 'Everyday Practical Electronics' magazine. Ideal School / College construction project. Supplied in good RFE condition, complete with data sheet.



Less than 30% of makers price **Only £29.95(B) or 4 x £99.00(D)**
Order RW44 Order PH26

THE AMAZING TELEBOX



TV SOUND &
VIDEO TUNER
CABLE COMPATIBLE

Converts your colour monitor into a QUALITY COLOUR TV!!

The TELEBOX is an attractive fully cased mains powered unit, containing all electronics ready to plug into a host of video monitors or AV equipment which are fitted with a composite video or SCART input. The composite video output will also plug directly into most video recorders, allowing reception of TV channels not normally receivable on most television receivers (TELEBOX MB). Push button controls on the front panel allow reception of 8 fully tuneable 'off air' UHF colour television channels. TELEBOX MB covers virtually all television frequencies VHF and UHF including the HYPERBAND as used by most cable TV operators. Ideal for desktop computer video systems & PIP (picture in picture) setups. For complete compatibility - even for monitors without sound - an integral 4 watt audio amplifier and low level Hi Fi audio output are provided as standard. Brand new - fully guaranteed.

TELEBOX ST for composite video input type monitors £36.95
TELEBOX STL as ST but fitted with integral speaker £39.50
TELEBOX MB Multiband VHF/UHF/Cable/Hyperband tuner £69.95
For overseas PAL versions state 5.5 or 6 MHz sound specification.
*For cable / hyperband signal reception Telebox MB should be connected to a cable type service. Shipping on all Telebox's, code (B)

NEW State of the art PAL (UK spec) UHF TV tuner module with composite 1V pp video & NICAM hi fi stereo sound outputs. Micro electronics all on one small PCB only 73 x 160 x 52 mm enable full tuning control via a simple 3 wire link to an IBM pc type computer. Supplied complete with simple working program and documentation. Requires +12V & +5V DC to operate. **BRAND NEW - Order as MY00. Only £39.95 code (B)**
See www.distel.co.uk/data_my00.htm for picture & full details

HARD DISK DRIVES 2 1/2" - 14"

2 1/2" TOSHIBA MK1002MAV 1.1Gb laptop (12.5 mm H) **New £59.95**
2 1/2" TOSHIBA MK4313MAT 4.3Gb laptop (8.2 mm H) **New £105.00**
2 1/2" TOSHIBA MK6409MAV 6.1Gb laptop (12.7 mm H) **New £98.00**
2 1/2" TOSHIBA MK1614GAV 18 Gb laptop (12 mm H) **New £149.95**
2 1/2" to 3 1/2" conversion kit for PC's, complete with connectors £15.95
3 1/2" COMPAQ 313706-B21 (IBM) 9 gb ULT/SCSI3 **New £199.00**
3 1/2" FUJII FK-309-26 20mb MFM I/F RFE **£59.95**
3 1/2" CONNER CP3024 20 mb IDE I/F (or equiv.) RFE **£59.95**
3 1/2" CONNER CP3044 40 mb IDE I/F (or equiv.) RFE **£69.00**
3 1/2" QUANTUM 40S Prodriv 4e 42mb SCSI I/F, New RFE **£49.00**
5 1/4" MINISCRIBE 3425 20mb MFM I/F (or equiv.) RFE **£49.95**
5 1/4" SEAGATE ST-238R 30 mb RLL I/F RFE **£69.95**
5 1/4" CDC 94205-51 40mb HH MFM I/F Refur tested **£69.95**
5 1/4" HP 97548 850 Mb SCSI RFE tested **£99.00**
5 1/4" HP C3010 2 Gbyte SCSI differential RFE tested **£195.00**
8" NEC D2246 85 Mb SMD interface. **New £99.00**
8" FUJITSU M2322K 160Mb SMD I/F RFE tested **£195.00**
8" FUJITSU M2392K 2 Gb SMD I/F RFE tested **£345.00**
Many other floppy & H drives, IDE, SCSI, ESDI etc from stock, see website for full stock list. Shipping on all drives is code

TEST EQUIPMENT & SPECIAL INTEREST ITEMS

MITSUBISHI FA3445ETKL 14" Ind. spec SVGA monitors £245
FARNELL 0-60V DC @ 50 Amps, bench Power Supplies £995
FARNELL AP3080 0-30V DC @ 80 Amps, bench Supply £1850
KINGSHILL CZ403/1 0-50V @ DC 200 Amps - NEW £3950
1kW to 400 kW - 400 Hz 3 phase power sources - ex stock EPOA
IBM 8230 Type 1, Token ring base unit driver £760
Wayne Kerr RA200 Audio frequency response analyser £2500
INFODEC 1U, 24 port, RJ45 network patchpanels. #TH93 £49
3COM 16670 12 Port Ethernet hub - RJ45 connectors #LD97 £69
3COM 16671 24 Port Ethernet hub - RJ45 connectors £89
3COM 16700 8 Port Ethernet hub - RJ45 connectors-NEW £39
IBM 53F5501 Token Ring ICS 20 port lobe modules EPOA
IBM MAU Token ring distribution panel 8228-23-505DN £45
AIM 501 Low distortion Oscillator 9Hz to 330KHz, IEEE I/O £55
ALLGON 8360.11805-1880 MHz hybrid power combiners £250
Trend DSA 274 Data Analyser with G703(2M) 64 i/c EPOA
Marconi 6310 Programmable 2 to 22 GHz sweep generator £4500
Marconi 2022C 10KHz-1GHz RF signal generator £1550
HP1650B Logic Analyser £3750
HP3781A Pattern generator & HP3782A Error Detector £1800
HP6621A Dual Programmable GPIB PSU 0-7 V 160 watts £1800
HP6264 Rack mount variable 0-20V @ 20A metered PSU £475
HP54121A DC to 22 GHz four channel test set EPOA
HP8130A opt 020 300 MHz pulse generator, GPIB etc £7900
HP A1, A0 8 pen HPGL high speed drum plotters - from HP DRAFTMASTER 1 8 pen high speed plotter £550
EG+G Brookdecal 95035C Precision lock in amp £750
Keithley 590 CV capacitor / voltage analyser £1800
Racal ICR40 dual 40 channel video recorder system £3750
Fiskers 45KVA 3 ph On Line UPS - New batteries £4500
Emerson AP130 2.5KVA industrial spec UPS £1499
Mann Tally MT645 High speed line printer £2200
Intel SBC 486/133SE Multibus 486 system. 8Mb Ram £945

IC's - TRANSISTORS - DIODES

OBSOLETE - SHORT SUPPLY - BULK
10,000,000 items EX STOCK
For MAJOR SAVINGS
CALL or see web site www.distel.co.uk

COMPUTER MONITOR SPECIALS

Legacy products
High spec genuine multisync.
CGA, EGA, VGA, SVGA

Mitsubishi FA3115ETKL 14" SVGA Multisync colour monitor with fine 0.28 dot pitch tube and resolution of 1024 x 768. A variety of inputs allows connection to a host of computers including IBM PC's in CGA, EGA, VGA & SVGA modes, BBC COMMODORE (including Amiga 1200), ARCHIMEDES and APPLE. Many features: Etched faceplate, text switching and LOW RADIATION MPR specification. Fully guaranteed, in EXCELLENT little used condition. Tilt & Swivel Base £4.75

VGA cable for IBM PC included. **Only £129 (E)** Order as CG73

External cables for other types of computers available - CALL

Generic LOW COST SVGA Monitors

We choose the make, which includes Compaq, Mitsubishi, IBM, etc. Supplied ready to run with all cables, Standard RTB 90 day guarantee.

14" £59.00 15" £69.00 17" £79.00
Supplied in good used condition. Shipping code (D)

VIDEO MONITORS

PHILIPS HCS35 (same style as CM8833) attractively styled 14" colour monitor with both RGB and standard composite 15.625 KHz video inputs via SCART socket and separate phono jacks. Integral audio power amp and speaker for all audio visual uses. Will connect direct to Amiga and Atari BBC computers. Ideal for all video monitoring / security applications with direct connection to most colour cameras. High quality with many features such as front concealed flap controls, VCR correction button etc. Good used condition - fully tested - guaranteed
Dimensions: W14" x H12 3/4" x 1 1/2" D. **Only £99.00 (E)**

PHILIPS HCS31 Ultra compact 9" colour video monitor with standard composite 15.625 KHz video input via SCART socket. Ideal for all monitoring / security applications. High quality, ex-equipment fully tested & guaranteed (possible minor screen burns). In attractive square black plastic case measuring W10" x H10" x 1 1/2" D. 240 V AC mains powered. **Only £79.00 (D)**

INDUSTRIAL COMPUTERS

Tiny shoebox sized industrial 40 Mhz 386 PC system measuring only (mm) 266 w X 88 h X 272 d. Ideal for dedicated control applications running DOS, Linux or even Windows! Steel case contains 8 to 265 V AC 50 / 60 Hz 70 Watt PSU, a 3 slot ISA passive backplane and a Rocky 318 (PC104) standard, single board computer with 8 MByte NON VOLATILE solid state 'Disk On Chip' RAMDISK. System comprises: Rocky 318 (PC104) SBC ISA card with 40MHz ALI 386SX CPU, 72 pin SIMM slot with 16 Mbyte SIMM, AMI BIOS, battery backed up real time clock, 2 x 9 pin D 16550 serial ports. EPP/ECP printer port, mini DIN keyboard connector, floppy port, IDE port for hard drives up to 528 MByte capacity, watchdog timer and PC/104 bus socket. The 8 MByte solid state 'disk on a chip' has its own BIOS, and can be formatted, formatted & booted. Supplied BRAND NEW fully tested and guaranteed. For full data see featured item on website. Order as **Only £99.00 (D)**

100's of applications inc: firewall, routers, robotics etc

19" RACK CABINETS

Europe's Largest Stocks of quality rack cabinets, enclosures and accessories. Over 1000 Racks from stock

Save £££'s

This month's special
33 / 42 / 47 U - High Quality
All steel Rack Cabinets

BIG £ SAVER

Made by Eurocraft Enclosures Ltd to the highest possible spec, rack features all steel construction with removable side, front and back doors. Front and back doors are hinged for easy access and all lockable with five secure 5 lever barrel locks. The front door is constructed of double walled steel with a 'designer style' smoked acrylic front panel to enable status indicators to be seen through the panel, yet remain unobtrusive. Internally the rack features fully slotted reinforced vertical fixing members to take the heaviest of 19" rack equipment. The two movable vertical fixing struts (extras available) are pre-punched for standard 'cage nuts'. A mains distribution panel internally mounted to the bottom rear, provides 8 x IEC 3 pin Euro sockets and 1 x 13 amp 3 pin switched utility socket. Overall ventilation is provided by fully louvered back door and double skinned top section with top and side louvers. The top panel may be removed for fitting of integral fans to the sub plate etc. Other features include: fitted castors and floor levelers, pre-punched utility panel at lower rear for cable / connector access etc. Supplied in excellent, slightly used condition with keys. Colour Royal blue. some grey available - CALL - Can be supplied in many other configurations.



33U Order as BC44 External dimensions mm=1825H x 635D x 603 W. (64" H x 25" D x 23 3/4" W) Only £245	42U Order as DT20 External dimensions mm=2019H x 635D x 603 W. (79.5" H x 25" D x 23 3/4" W) Only £345	47U Order as RV36 External dimensions mm=2019H x 635D x 603 W. (88" H x 25" D x 23 3/4" W) Only £410
--	--	--

Call for shipping quotation

COLOUR CCD CAMERAS

Undoubtedly a miracle of modern technology & our special buying power! A quality product featuring a fully cased COLOUR CCD camera at a give away price! Unit features full autolight sensing for use in low light & high light applications. A 10 mm fixed focus wide angle lens gives excellent focus and resolution from close up to long range. The composite video output will connect to any composite monitor or TV (via SCART socket) and most video recorders. Unit runs from 12V DC so ideal for security & portable applications where mains power not available. Overall dimensions 66 mm wide x 117 deep x 43 high. Supplied BRAND NEW & fully guaranteed with user data, 100's of applications including Security, Home Video, Web TV, Web Cams etc, etc.



Order as LK33 **ONLY £79.00 or 2 for £149.00 (B)**

SOFTWARE SPECIALS

NT4 WorkStation, complete with service pack 3 and licence - OEM packaged. **ONLY £89.00 (B)**
ENCARTA 95 - CDROM, Not the latest - but at this price! £7.95
DOS 5.0 on 3 1/2" disks with concise books c/w QBasic. £14.95
Windows for Workgroups 3.11+ Dos 6.22 on 3.5" disks £55.00
Windows 95 CDROM Only - No Licence - £19.95

Wordperfect 6 for DOS supplied on 3 1/2" disks with manual £24.95

SOLID STATE LASERS

Visible red, 670nm laser diode assembly. Unit runs from 5 V DC at approx 50 mA. Originally made for continuous use in industrial barcode scanners, the laser is mounted in a removable solid aluminium block, which functions as a heatsink and rigid optical mount. Dims of block are 50 w x 50 d x 15 h mm. Integral features include over temperature shutdown, current control, laser OK output, and gated TTL ON / OFF. Many uses for experimental optics, comms & lightshows etc. Supplied complete with data sheet.
Order as TD91 **ONLY £24.95 (A)**

DC POWER SUPPLIES

Virtually every type of power supply you can imagine. Over 10,000 Power Supplies Ex Stock - Call or see our web site.

RELAYS - 200,000 FROM STOCK

Save £££'s by choosing your next relay from our Massive Stocks covering types such as Military, Octal, Cradle, Hermetically Sealed, Continental, Contactors, Time Delay, Reed, Mercury Wetted, Solid State, Printed Circuit Mounting etc., CALL or see our web site www.distel.co.uk for more information. Many obsolete types from stock. Save £££'s

Display

ELECTRONICS

ALL MAIL TO
Dept PE, 29 / 35 Osborne Rd
Thornton Heath
Surrey CR7 8PD
Open Mon - Fri 9.00 - 5:30

18 Million Items On Line Now!
Secure ordering, Pictures, Information
www.distel.co.uk
email = admin@distel.co.uk


ALL ENQUIRIES
0208 653 3333
FAX 0208 653 8888

All prices for UK Mainland, UK customers add 17.5% VAT to TOTAL order amount. Minimum order £10. Bona Fide account orders accepted from Government, Schools, Universities and Local Authorities - minimum account order £50. Cheques over £100 are subject to 7 working days clearance. Carriage charges (A)=£3.50, (B)=£6.50, (D)=£15.00, (E)=£18.00 (F)=CALL. Allow approx 3 days for shipping - faster CALL. All goods supplied to our Standard Conditions of Sale which can be viewed at our website and unless stated guaranteed for 90 days. All guarantees on a return to base basis. All rights reserved to change prices / specifications without prior notice. Orders subject to stock. Discounts for volume. Top CASH prices paid for surplus goods. All trademarks, tradenames etc acknowledged. © Display Electronics 2002. E & O E.

NEXT MONTH

EPE PIC MAGNETOMETRY LOGGER

Magnetometers are instruments for measuring the direction and/or intensity of magnetic fields. Such fields are created by electrical current flow and also exist naturally in ferromagnetic substances, such as iron and nickel. It is the latter fields that this magnetometer has been designed to detect, particularly those associated with man's activities. This design is PIC-controlled and uses two FGM-3 fluxgate sensors from Speake & Co who describe them as "very high sensitivity magnetic field sensors operating in the ± 50 microtesla range", which covers the Earth's magnetic field. Their applications include conventional magnetometry, ferrous metal detectors, magnetic material measurement and archaeological artifact assessment. Data is recorded by the PIC to on-board memory, from where it can later be downloaded to a Windows-based PC for visual analysis.

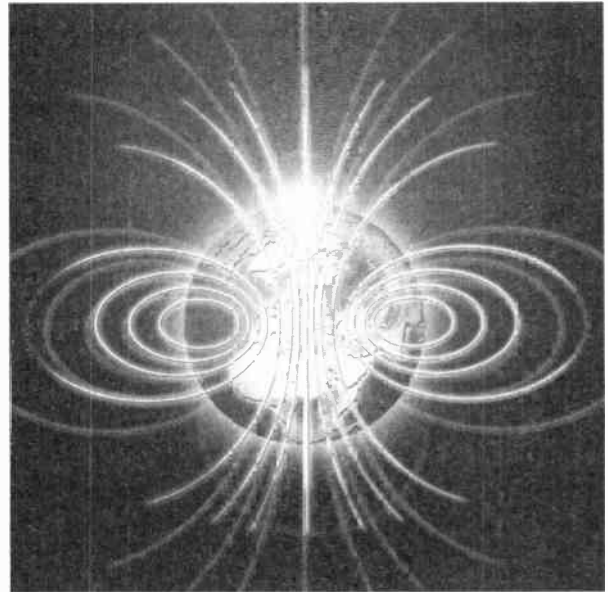

PORTABLE MINI ALARM

This is a unit that should find many applications within home and business security. Battery-powered and about the size of a small brick, it can be simply placed at the area to be protected, switched on and left. Intruders entering the area will trigger a siren that is loud enough to alert anyone nearby. The circuit features "pulse counting" that enables it to distinguish between passers-by and someone loitering, perhaps with "intent", in the protected area. The count can be adjusted by the user for the desired degree of immunity from false alarms. The battery life will depend upon the number of detections and alarms, but the circuit is a micro-power design and is capable of remaining "on guard" for periods well in excess of a year.

FRONT PANEL FINISHING

Adding the finishing touches to your project can be a time-consuming and laborious task, and the results may not be as professional as you would have liked! However, with the use of a home PC, professional looking front panel overlays can be quickly and easily produced. This article shows you how.

BONGO BOX

The Bongo Box is for budding drummers everywhere who like to tap out a rhythm with their fingertips on any available surface. This project is guaranteed to make such individuals even more annoying to any partner, parent or pet in the vicinity! In fact, the Bongo Box could be of serious use to anyone involved in playing or recording music using MIDI (Musical Instrument Digital Interface) controlled instruments. Any box or enclosure can be turned into an electronic drum by placing this design inside it and linking it to a PC. The response of the device is rapid, and drumming your fingers on the box causes a series of drum sounds to be played in quick succession.

This a great improvement over the usual situation where a MIDI keyboard is used to trigger sounds – normally it is not possible with a keyboard to mimic the quick "rolls" that drummers play. The Bongo Box makes this technique possible, without having to go to the expense of buying an electronic drum kit!

PLUS TEACH-IN 2004 – PART 9 LOCK AND ALARM SYSTEMS

NO ONE DOES IT BETTER

EVERYDAY
PRACTICAL
ELECTRONICS

**DON'T MISS AN
ISSUE – PLACE YOUR
ORDER NOW!**
Demand is bound to be high



Quasar Electronics Limited
PO Box 6935, Bishops Stortford,
CM23 4WP
Tel: 0870 246 1826
Fax: 0870 460 1045
E-mail: sales@quasarelectronics.com

Add £3.00 P&P to all UK orders or 1st Class Recorded – £5.
Next day (Insured £250) – £8. Europe – £6. Rest of World – £10
(order online for reduced price UK Postage).
We accept all major credit/debit cards. Make cheques/POs
payable to Quasar Electronics Limited.
Prices include 17.5% VAT. MAIL ORDER ONLY.
Call now for our FREE CATALOGUE with details of over 300
high quality kits, projects, modules and publications.



QUASAR 0871 CREDIT CARD SALES 717 7168

Helping you make the right connections!

PIC & ATMEL Programmers

We have a wide range of low cost PIC and ATMEL Programmers. Complete range and documentation available from our web site.

Programmer Accessories:

40-pin Wide ZIF socket (ZIF40W) £15.00
18VDC Power supply (PSU020) £5.95
Leads: Parallel (LEAD108) £4.95 / Serial (LEAD76) £4.95 / USB (LEADUAA) £2.95

NEW! USB 'All-Flash' PIC Programmer

USB PIC programmer for all 'Flash' devices. No external power supply making it truly portable. Supplied with box and Windows Software. ZIF Socket and USB Plug A-A lead not incl.



Kit Order Code: 3128KT – £39.95

Assembled Order Code: AS3128 – £49.95

Enhanced "PICALL" ISP PIC Programmer

Will program virtually ALL 8 to 40 pin PICs plus certain ATMEL AVR, SCENIX SX and EEPROM 24C devices. Also supports In System Programming (ISP) for PIC and ATMEL AVR's. Free software. Blank chip auto detect for super fast bulk programming. Requires a 40-pin wide ZIF socket (not included)

Assembled Order Code: AS3144 – £59.95

ATMEL 89xxx Programmer

Uses serial port and any standard terminal comms program. 4 LEDs display the status. ZIF sockets not included. Supply: 16VDC.

Kit Order Code: 3123KT – £29.95

Assembled Order Code: AS3123 – £34.95

NEW! USB & Serial Port PIC Programmer

USB/Serial connection. Header cable for ICSP. Free Windows software. See website for PICs supported. ZIF Socket and USB Plug A-A lead extra. 18VDC.

Kit Order Code: 3149KT – £39.95

Assembled Order Code: AS3149 – £54.95

Introduction to PIC Programming

Go from a complete PIC beginner to burning your first PIC and writing your own code in no time!

Includes a 49-page step-by-step Tutorial Manual,

Programming Hardware (with LED bench testing section), Win 3.11-XP Programming Software (will Program, Read, Verify & Erase), and a rewritable PIC16F84A that you can use with different code (4 detailed examples provided for you to learn from). Connects to PC parallel port.

Kit Order Code: 3081KT – £14.95

Assembled Order Code: AS3081 – £24.95

ABC Maxi AVR Development Board

The ABC Maxi board has an open architecture design based on Atmel's AVR AT90S8535 RISC microcontroller and is ideal for developing new designs.



Features:

8Kb of In-System Programmable Flash (1000 write/erase cycles) • 512 bytes internal SRAM • 512 bytes EEPROM
• 8 analogue inputs (range 0-5V)
• 4 Opto-isolated Inputs (I/Os are bi-directional with internal pull-up resistors)
• Output buffers can sink 20mA current (direct i.e.d. drive) • 4 x 12A open drain MOSFET outputs • RS485 network connector • 2-16 LCD Connector
• 3.5mm Speaker Phone Jack
• Supply: 9-12VDC.

The ABC Maxi STARTER PACK includes one assembled Maxi Board, parallel and serial cables, and Windows software CD-ROM featuring an Assembler, BASIC compiler and in-system programmer.

Order Code ABCMAXISP – £79.95

The ABC Maxi boards only can also be purchased separately at £59.95 each.

Controllers & Loggers

Here are just a few of the controller and data acquisition and control units we have. See website for full details. Suitable PSU for all units: Order Code PSU345 – £9.95

Rolling Code 4-Channel UHF Remote

State-of-the-Art. High security. 4 channels. Momentary or latching relay output. Range up to 40m. Up to 15 TXs can be learned by one Rx (kit includes one Tx but more available separately). 4 indicator LEDs.

Rx: PCB 77x85mm, 12VDC/6mA (standby).

Two & Ten Channel versions also available.

Kit Order Code: 3180KIT – £41.95

Assembled Order Code: AS3180 – £49.95



Computer Temperature Data Logger

Serial port 4-channel temperature logger. °C or °F. Continuously logs up to 4 separate sensors located 200m+ from board. Wide range of free software applications for storing/using data. PCB just 38x38mm. Powered

by PC. Includes one DS1820 sensor and four header cables.

Kit Order Code: 3145KT – £19.95

Assembled Order Code: AS3145 – £26.95

Additional DS1820 Sensors – £3.95 each



Most items are available in kit form (KT suffix) or pre-assembled and ready for use (AS prefix).

NEW! DTMF Telephone Relay Switcher

Call your phone number using a DTMF phone from anywhere in the world and remotely turn on/off any of the 4 relays as desired. User settable Security Password, Anti-Tamper, Rings to Answer, Auto Hang-up and Lockout. Includes plastic case. 130 x 110 x 30mm. Power: 12VDC.



Kit Order Code: 3140KT – £39.95

Assembled Order Code: AS3140 – £49.95

Serial Port Isolated I/O Module

Computer controlled 8-channel relay board. 5A mains rated relay outputs and 4 opto-isolated digital inputs (for monitoring switch states, etc). Useful in a variety of control and sensing applications. Programmed via serial port (use our new Windows interface, terminal emulator or batch files). Serial cable can be up to 35m long. Includes plastic case 130 x 100 x 30mm. Power: 12VDC/500mA.

Kit Order Code: 3108KT – £54.95

Assembled Order Code: AS3108 – £64.95

Infra-red RC 12-Channel Relay Board

Control 12 on-board relays with included infra-red remote control unit. Toggle or momentary. 15m+ range. 112 x 122mm.

Supply: 12VDC/0.5A.

Kit Order Code: 3142KT – £41.95

Assembled Order Code: AS3142 – £51.95

PC Data Acquisition & Control Unit

Monitor and log a mixture of analogue and digital inputs and control external devices via the analogue and digital outputs. Monitor pressure, temperature, light intensity, weight, switch state, movement, relays, etc. with the appropriate sensors (not supplied). Data can be processed, stored and the results used to control devices such as motors, sirens, relays, servo motors (up to 11) and two stepper motors.

Features

- 11 Analogue Inputs – 0-5V, 10 bit (5mV/step)
- 16 Digital Inputs – 20V max. Protection 1K in series, 5-1V Zener
- 1 Analogue Output – 0-2.5V or 0-10V. 8 bit (20mV/step)
- 8 Digital Outputs – Open collector, 500mA, 3V max
- Custom box (140 x 110 x 35mm) with printed front & rear panels
- Windows software utilities (3-1 to XP) and programming examples
- Supply: 12V DC (Order Code PSU203)


Kit Order Code: 3093KT – £69.95

Assembled Order Code: AS3093 – £99.95

Cool New Kits This Winter!

Here are a few of the most recent kits added to our range. See website or join our email Newsletter for all the latest news.

NEW! EPE Ultrasonic Wind Speed Meter

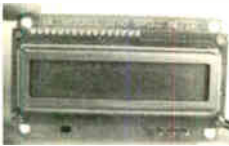

Solid-state design wind speed meter (anemometer) that uses ultrasonic techniques and has no moving parts and does not need

calibrating. It is intended for sports-type activities, such as track events, sailing, hang-gliding, kites and model aircraft flying, to name but a few. It can even be used to monitor conditions in your garden. The probe is pointed in the direction from which the wind is blowing and the speed is displayed on an LCD display.

Specifications


- Units of display: metres per second, feet per second, kilometres per hour and miles per hour
- Resolution: Nearest tenth of a metre
- Range: Zero to 50mph approx.

Based on the project published in Everyday Practical Electronics, Jan 2003. We have made a few minor design changes (see web site for full details). Power: 9VDC (PP3 battery or Order Code PSU345).

Main PCB: 50 x 83mm.

Kit Order Code: 3168KT – £34.95

NEW! Audio DTMF Decoder and Display

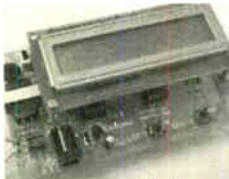

Detects DTMF tones via an on-board electret microphone or direct from the phone lines through an audio transformer. The

numbers are displayed on a 16-character, single line display as they are received. Up to 32 numbers can be displayed by scrolling the display left and right. There is also a serial output for sending the detected tones to a PC via the serial port. The unit will not detect numbers dialled using pulse dialling. Circuit is microcontroller based.

Supply: 9-12V DC (Order Code PSU345).

Main PCB: 55 x 95mm.

Kit Order Code: 3153KT – £17.95

Assembled Order Code: AS3153 – £29.95

NEW! EPE PIC Controlled LED Flasher



This versatile PIC-based LED or filament bulb flasher can be used to flash from 1 to 160

LEDs. The user arranges the LEDs in any pattern they wish. The kit comes with 8 superbright red LEDs and 8 green LEDs. Based on the Versatile PIC Flasher by Steve Challinor, *EPE Magazine* Dec '02. See website for full details. Board Supply: 9-12V DC. LED supply: 9-45V DC (depending on number of LED used). PCB: 43 x 54mm. Kit Order Code: 3169KT – £10.95

Most items are available in kit form (KT suffix) or assembled and ready for use (AS prefix)

FM Bugs & Transmitters

Our extensive range goes from discreet surveillance bugs to powerful FM broadcast transmitters. Here are a few examples. All can be received on a standard FM radio and have adjustable transmitting frequency.

MMTX' Micro-Miniature 9V FM Room Bug



Our best selling bug! Good performance. Just 25 x 15mm. Sold to detective agencies worldwide. Small enough to hide just about anywhere.

Operates at the 'less busy' part end of the commercial FM waveband and also up into the more private Air band. Range: 500m. Supply: PP3 battery. Kit Order Code: 3051KT – £8.95
Assembled Order Code: AS3051 – £14.95

HPTX' High Power FM Room Bug

Our most powerful room bug.

Very Impressive



performance. Clear and stable output signal thanks to the extra circuitry employed. Range: 1000m @ 9V. Supply: 6-12V DC (9V PP3 battery clip supplied). 70 x 15mm. Kit Order Code: 3032KT – £9.95
Assembled Order Code: AS3032 – £17.95

MTTX' Miniature Telephone Transmitter



Attach anywhere along phone line. Tune a radio into the signal and hear

exactly what both parties are saying. Transmits only when phone is used. Clear, stable signal. Powered from phone line so completely maintenance free once installed. Requires no aerial wire – uses phone line as antenna. Suitable for any phone system worldwide. Range: 300m. 20 x 45mm. Kit Order Code: 3016KT – £7.95
Assembled Order Code: AS3016 – £13.95

3 Watt FM Transmitter



Small, powerful FM transmitter. Audio preamp stage and three RF stages deliver 3 watts of RF power. Can be used with the electret

microphone supplied or any line level audio source (e.g. CD or tape OUT, mixer, sound card, etc). Aerial can be an open dipole or Ground Plane. Ideal project for the novice wishing to get started in the fascinating world of FM broadcasting. 45 x 145mm. Kit Order Code: 1028KT – £22.95
Assembled Order Code: AS1028 – £34.95

25 Watt FM Transmitter

Four transistor based stages with a Philips BLY89 (or equivalent) in the final stage. Delivers a mighty 25 Watts of RF power. Accepts any line level audio source (input sensitivity is adjustable). Antenna can be an open dipole, ground plane, 5/8, J, or YAGI configuration. Supply 12-14V DC, 5A. Supplied fully assembled and aligned – just connect the aerial, power and audio input. 70 x 220mm.

Order Code: 1031M – £124.95



QUASAR
electronics

Helping you make the right connections!

**CREDIT
CARD
SALES**
0871
717
7168

Electronic Project Labs

Great introduction to the world of electronics. Ideal gift for budding electronics expert!

500-in-1 Electronic Project Lab

This is the top of the range and is a complete electronics course taking you from beginner to 'A' level standard and beyond! It contains all the parts and instructions to assemble 500 projects. You get three comprehensive course books (total 368 pages) – *Hardware Entry Course*, *Hardware Advanced Course* and a micro-computer based *Software Programming Course*. Each book has individual circuit explanations, schematic and assembly diagrams. Suitable for age 12 and above. Order Code EPL500 – £149.95

30, 130, 200 and 300-in-1 project labs also available – see website for details.



Number 1 for Kits!

With over 300 projects in our range we are the UK's number 1 electronic kit specialist. Here are a few other kits from our range.

- 1046KT – 25W Stereo Car Booster £26.95
- 3087KT – 1W Stereo Amplifier £4.95
- 3105KT – 18W BTL mono Amplifier £9.95
- 3106KT – 50W Mono Hi-fi Amplifier £19.95
- 3143KT – 10W Stereo Amplifier £9.95
- 1011KT – Motorbike Alarm £11.95
- 1019KT – Car Alarm System £10.95
- 1048KT – Electronic Thermostat £9.95
- 1080KT – Liquid Level Sensor £5.95
- 3005KT – LED Dice with Box £7.95
- 3006KT – LED Roulette Wheel £8.95
- 3074KT – 8-Ch PC Relay Board £29.95
- 3082KT – 2-Ch UHF Relay £26.95
- 3126KT – Sound-Activated Relay £7.95
- 3063KT – One Chip AM Radio £10.95
- 3102KT – 4-Ch Servo Motor Driver £15.95
- 3160KT – PIC16F62x Experimenter £8.95
- 1096KT – 3-30V, 5A Stabilised PSU £30.95
- 3029KT – Combination Lock £6.95
- 3049KT – Ultrasonic Detector £13.95
- 3130KT – Infra-red Security Beam £12.95
- SG01MKT – Train Sounds £6.95
- SG10 MKT – Animal Sounds £5.95
- 1131KT – Robot Voice Effect £8.95
- 3007KT – 3V FM Room Bug £6.95
- 3028KT – Voice-Activated FM Bug £12.95
- 3033KT – Telephone Recording Adpt £9.95
- 3112KT – PC Data Logger/Sampler £18.95
- 3118KT – 12-bit Data Acquisition Unit £52.95
- 3101KT – 20MHz Function Generator £69.95

www.quasarelectronics.com

Secure Online Ordering Facilities ● Full Product Listing, Descriptions & Photos ● Kit Documentation & Software Downloads



EPE PIC PROJECTS VOLUME 1 MINI CD-ROM

NEW



A plethora of 20 "hand-PICked" PIC Projects from selected past issues of EPE

Together with the PIC programming software for each project plus bonus articles

The projects are:

PIC-Based Ultrasonic Tape Measure

You've got it taped if you PIC this ultrasonic distance measuring calculator

EPE Mind PICKler

Want seven ways to relax? Try our PIC-controlled mind machine!

PIC MIDI Sustain Pedal

Add sustain and glissando to your MIDI line-up with this inexpensive PIC-controlled effects unit

PIC-based MIDI Handbells

Ring out thy bells with merry tolling – plus a MIDI PIC-up, of course!

EPE Mood PICKer

Oh for a good night's sleep! Insomniacs rejoice – your wakeful nights could soon be over with this mini-micro under the pillow!

PIC Micro-Probe

A hardware tool to help debug your PIC software

PIC Video Cleaner

Improving video viewing on poorly maintained TVs and VCRs

PIC Graphics LCD Scope

A PIC and graphics LCD signal monitor for your workshop

PIC to Printer Interface

How to use dot-matrix printers as data loggers with PIC microcontrollers

PIC Polywhatsit

A novel compendium of musical effects to delight the creative musician

PIC Magick Musick

Conjure music from thin air at the mere untouching gesture of a fingertip

PIC Mini-Enigma

Share encrypted messages with your friends — true spymaster entertainment

PIC Virus Zapper

Can disease be cured electronically? Investigate this controversial subject for yourself

PIC Controlled Intruder Alarm

A sophisticated multi-zone intruder detection system that offers a variety of monitoring facilities

PIC Big-Digit Display

Control the giant ex-British Rail platform clock 7-segment digits that are now available on the surplus market

PIC Freezer Alarm

How to prevent your food from defrosting unexpectedly

PIC World Clock

Graphically displays world map, calendar, clock and global time-zone data

PICAXE Projects

A 3-part series using PICAXE devices – PIC microcontrollers that do not need specialist knowledge or programming equipment

PIC-based Tuning Fork and Metronome

Thrill everyone by at long last getting your instrument properly tuned!

Versatile PIC Flasher

An attractive display to enhance your Christmas decorations or your child's ceiling

**ONLY
£14.45
INCLUDING
VAT and P&P**

Order on-line from

www.epemag.wimborne.co.uk/shopdoor.htm

or www.epemag.com (USA \$ prices)

or by Phone, Fax, Email or Post.

NOTE: The PDF files on this CD-ROM are suitable to use on any PC with a CD-ROM drive. They require Adobe Acrobat Reader.

EPE PIC PROJECTS CD-ROM ORDER FORM

Please send me (quantity) EPE PIC PROJECTS VOL 1 CD-ROM

Price £14.45 each – includes postage to anywhere in the world.

Name

Address

.....

.....

..... Post Code

I enclose cheque/P.O./bank draft to the value of £

Please charge my Visa/Mastercard/Amex/Diners Club/Switch

£

Card No.

Card Security Code (The last 3 digits on or just under the signature strip)

Start Date Expiry Date Switch Issue No.

**SEND TO: Everyday Practical Electronics,
Wimborne Publishing Ltd.,**

408 Wimborne Road East, Ferndown, Dorset BH22 9ND.

Tel: 01202 873872. Fax: 01202 874562.

Email: orders@epemag.wimborne.co.uk


Payments must be by card or in £ Sterling – cheque or bank draft drawn on a UK bank.

Normally supplied within seven days of receipt of order.

Send a copy of this form, or order by letter if you do not wish to cut your issue.

BECOME A PIC PROJECT BUILDER WITH THE HELP OF EPE!

Learn About Microcontrollers

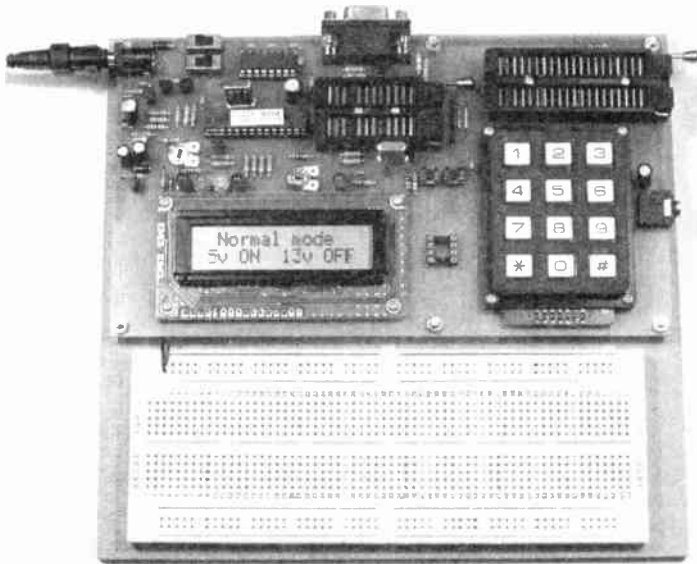

PIC Training & Development System

The best place to start learning about microcontrollers is the PIC16F84. This is easy to understand and very popular with construct on projects. Then continue on using the more sophisticated PIC16F877 family.

The heart of our system is two real books which lie open on your desk while you use your computer to type in the programme and control the hardware. Start with four very simple programmes. Run the simulator to see how they work. Test them with real hardware. Follow on with a little theory....

Our complete PIC training and development system consists of our universal mid range PIC programmer, a 306 page book covering the PIC16F84, a 262 page book introducing the PIC16F877 family, and a suite of programmes to run on a PC. The module is an advanced design using a 28 pin PIC16F870 to handle the timing, programming and voltage switching requirements. The module has two ZIF sockets and an 8 pin socket which between them allow most mid range 8, 18, 28 and 40 pin PICs to be programmed. The plugboard is wired with a 5 volt supply. The software is an integrated system comprising a text editor, assembler disassembler, simulator and programming software. The programming is performed at 5 volts, verified with 2 volts or 3 volts applied and verified again with 5.5 volts applied to ensure that the PIC is programmed correctly over its full operating voltage. DC version for UK, battery version for overseas. UK orders include a plugtop power supply.

- Universal mid range PIC programmer module
 - + Book Experimenting with PIC Microcontrollers
 - + Book Experimenting with the PIC16F877 (2nd edition)
 - + Universal mid range PIC software suite
 - + PIC16F84 and PIC16F870 test PICs. £159.00
- (Postage & insurance UK £10, Europe £15, Rest of world £25)

Experimenting with PIC Microcontrollers

This book introduces the PIC16F84 and PIC16C711, and is the easy way to get started for anyone who is new to PIC programming. We begin with four simple experiments, the first of which is explained over ten and half a pages assuming no starting knowledge except the ability to operate a PC. Then having gained some practical experience we study the basic principles of PIC programming, learn about the 8 bit timer, how to drive the liquid crystal display, create a real time clock, experiment with the watchdog timer, sleep mode, beeps and music, including a rendition of Beethoven's *Für Elise*. Finally there are two projects to work through, using the PIC16F84 to create a sinewave generator and investigating the power taken by domestic appliances. In the space of 24 experiments, two projects and 56 exercises the book works through from absolute beginner to experienced engineer level.

Hardware & Ordering Information

Our latest programmer module connects to the serial port of your PC (COM1 or COM2), which enables our PIC software to operate directly within Windows 98, XP, NT, 2000 etc.

Telephone with Visa, Mastercard or Switch, or send cheque/PO for immediate despatch. All prices include VAT if applicable.

Web site:- www.brunningsoftware.co.uk

NEW 32 bit PC Assembler

Experimenting with PC Computers with its kit is the easiest way ever to learn assembly language programming. If you have enough intelligence to understand the English language and you can operate a PC computer then you have all the necessary background knowledge. Flashing LEDs, digital to analogue converters, simple oscilloscope, charging curves, temperature graphs and audio digitising.

Kit now supplied with our 32 bit assembler with 84 page supplement detailing the new features and including 7 experiments PC to PIC communication. Flashing LEDs, writing to LCD and two way data using 3 wires from PC's parallel port to PIC16F84.

- Book + made up kit 1a + software..... £73.50
 - Book + unmade kit 1u + software..... £66.50
- (PP UK £4, Europe £10, Rest of world £14)

C & C++ for the PC

Experimenting with C & C++ Programmes teaches us to programme by using C to drive the simple hardware circuits built using the materials supplied in the kit. The circuits build up to a storage oscilloscope using relatively simple C techniques to construct a programme that is by no means simple. When approached in this way C is only marginally more difficult than BASIC and infinitely more powerful. C programmers are always in demand. Ideal for absolute beginners and experienced programmers.


- Book + made up kit 2a + software £57.50
 - Book + unmade kit 2u + software £51.50
 - Book + top up kit 2t + software £37.98
- (PP UK £4, Europe £10, Rest of world £14)

The Kits

The assembler and C & C++ kits contain the prototyping board, lead assemblies, components and programming software to do all the experiments. The 'made up' kits are supplied ready to start. The 'top up' kit is for readers who have already purchased kit 1a or 1u.

Assembler and C & C++

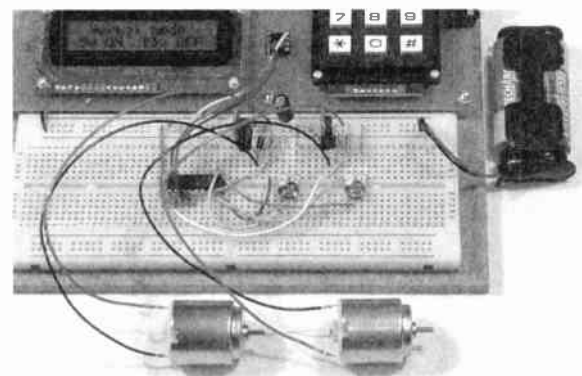Click on 'Special Offers' on our website for details of how to save by buying a combined kit for assembler and C & C++.



Experimenting with the PIC16F877

The second PIC book starts with the simplest of experiments to give us a basic understanding of the PIC16F877 family. Then we look at the 16 bit timer, efficient storage and display of text messages, simple frequency counter, use a keypad for numbers, letters and security codes, and examine the 10 bit A/D converter.

The PIC16F627 is then introduced as a low cost PIC16F84. We use the PIC16F627 as a step up switching regulator, and to control the speed of a DC motor with maximum torque still available. We study how to use a PIC to switch mains power using an optoisolated triac driving a high current triac. Finally we study how to use the PICs USART for serial communication to a PC.

Mail order address:

Brunning Software 138 The Street, Little Clacton, Clacton-on-sea, Essex, CO16 9LS. Tel 01255 862308

MAIL ORDER ONLY • CALLERS BY APPOINTMENT

EPE PROJECT PICS

Programmed PICs for *EPE Projects

12C508/9 - £3.90; 16F627/8 - £4.90

16C84/16F84/16C71 - £5.90

16F876/877 - £10.00

All inc. VAT and Postage

(*Some projects are copyright)

EPE MICROCONTROLLER P.I. TREASURE HUNTER

The latest MAGENTA DESIGN - highly stable & sensitive - with I.C. control of all timing functions and advanced pulse separation techniques.

- High stability drift cancelling
- Easy to build & use
- No ground effect, works in seawater



- Detects gold, silver, ferrous & non-ferrous metals

- Efficient quartz controlled microcontroller pulse generation.
- Full kit with headphones & all hardware

KIT 847£63.95

PIC PIPE DESCALER

- SIMPLE TO BUILD
- HIGH POWER OUTPUT
- AUDIO & VISUAL MONITORING
- SWEPT FREQUENCY

An affordable circuit which sweeps the incoming water supply with variable frequency electromagnetic signals. May reduce scale formation, dissolve existing scale and improve lathering ability by altering the way salts in the water behave.

Kit includes case, P.C.B., coupling coil and all components. High coil current ensures maximum effect. L.E.D. monitor.



KIT 868 £22.95 POWER UNIT.....£3.99

MICRO PEST SCARER

Our latest design - The ultimate scarer for the garden. Uses special microchip to give random delay and pulse time. Easy to build reliable circuit. Keeps pets/pests away from newly sown areas, play areas, etc. uses power source from 9 to 24 volts.

- RANDOM PULSES
- HIGH POWER
- DUAL OPTION



Plug-in power supply £4.99

KIT 867.....£19.99

KIT + SLAVE UNIT.....£32.50

WINDICATOR

A novel wind speed indicator with LED readout. Kit comes complete with sensor cups, and weatherproof sensing head. Mains power unit £5.99 extra.

KIT 856.....£28.00

★ TENS UNIT ★

DUAL OUTPUT TENS UNIT

As featured in March '97 issue.

Magenta have prepared a FULL KIT for this excellent new project. All components, PCB, hardware and electrodes are included. Designed for simple assembly and testing and providing high level dual output drive.

KIT 866. . Full kit including four electrodes £32.90

Set of 4 spare electrodes £6.50

1000V & 500V INSULATION TESTER



Superb new design. Regulated output, efficient circuit. Dual-scale meter, compact case. Reads up to 200 Megohms.

Kit includes wound coil, cut-out case, meter scale, PCB & ALL components.

KIT 848.....£32.95

EPE TEACH-IN 2000

Full set of top quality NEW components for this educational series. All parts as specified by EPE. Kit includes breadboard, wire, croc clips, pins and all components for experiments, as listed in introduction to Part 1.

*Batteries and tools not included.

TEACH-IN 2000 -

KIT 879 £44.95

MULTIMETER £14.45

SPACEWRITER

An innovative and exciting project. Wave the wand through the air and your message appears. Programmable to hold any message up to 16 digits long. Comes pre-loaded with "MERRY XMAS". Kit includes PCB, all components & tube plus instructions for message loading.

KIT 849£16.99



12V EPROM ERASER

A safe low cost eraser for up to 4 EPROMS at a time in less than 20 minutes. Operates from a 12V supply (400mA). Used extensively for mobile work - updating equipment in the field etc. Also in educational situations where mains supplies are not allowed. Safety interlock prevents contact with UV.

KIT 790£29.90

SUPER BAT DETECTOR

1 WATT O/P, BUILT IN SPEAKER, COMPACT CASE 20kHz-140kHz NEW DESIGN WITH 40kHz MIC.

A new circuit using a 'full-bridge' audio amplifier i.c., internal speaker, and headphone/tape socket. The latest sensitive transducer, and 'double balanced mixer' give a stable, high performance superheterodyne design.

KIT 861£27.99

ALSO AVAILABLE Built & Tested... £42.99




68000 DEVELOPMENT TRAINING KIT

- NEW PCB DESIGN
- 8MHz 68000 16-BIT BUS
- MANUAL AND SOFTWARE
- 2 SERIAL PORTS
- PIT AND I/O PORT OPTIONS
- 12C PORT OPTIONS

KIT 621

£99.95

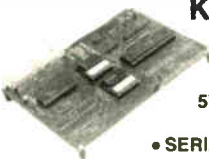- ON BOARD 5V REGULATOR
- PSU £6.99
- SERIAL LEAD £3.99



Stepping Motors

MD100...Std 100 step...£9.99

MD200...200 step...£12.99

MD24...Large 200 step...£22.95



MOSFET MKII VARIABLE BENCH POWER SUPPLY 0-25V 2.5A

Based on our Mk1 design and preserving all the features, but now with switching pre-regulator for much higher efficiency. Panel meters indicate Volts and Amps. Fully variable down to zero. Toroidal mains transformer. Kit includes punched and printed case and all parts. As featured in April 1994 EPE. An essential piece of equipment.



Kit No. 845£64.95

ULTRASONIC PEST SCARER

Keep pets/pests away from newly sown areas, fruit, vegetable and flower beds, children's play areas, patios etc. This project produces intense pulses of ultrasound which deter visiting animals.

- KIT INCLUDES ALL COMPONENTS, PCB & CASE
- EFFICIENT 100V TRANSDUCER OUTPUT
- COMPLETELY INAUDIBLE TO HUMANS



- UP TO 4 METRES RANGE
- LOW CURRENT DRAIN

KIT 812.....£15.00

SIMPLE PIC PROGRAMMER

KIT 857... £12.99


Includes PIC16F84 chip disk, lead, plug, p.c.b., all components and instructions

Extra 16F84 chips £3.84 Power Supply £3.99

MAGENTA BRAINIBOT I & II

- Full kit with ALL hardware and electronics
- As featured in *EPE* Feb '03 – KIT 910
- Seeks light, beeps, avoids obstacles
- Spins and reverses when 'cornered'
- Uses 8-pin PIC
- ALSO KIT 911 – As 910 PLUS programmable from PC serial port – leads and software CD provided

NEW

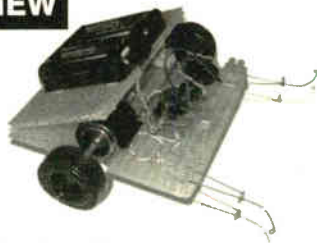

KIT 910 £16.99 KIT 911 £24.99

PIC 16F84 MAINS POWER 4-CHANNEL CONTROLLER & LIGHT CHASER

- ZERO VOLT SWITCHING
- OPTO ISOLATED 5 Amp
- 12 KEYPAD CONTROL
- HARD-FIRED TRIACS
- WITH SOURCE CODE
- SPEED & DIMMING POT.
- EASILY PROGRAMMED

Kit 855 £39.95

PIC 16F84 LCD DISPLAY DRIVER

INCLUDES 1-PIC16F84 WITH DEMO PROGRAM SOFTWARE DISK, PCB, INSTRUCTIONS AND 16-CHARACTER 2-LINE

LCD DISPLAY

Kit 860 £19.99

Power Supply £3.99

FULL PROGRAM SOURCE CODE SUPPLIED – DEVELOP YOUR OWN APPLICATION!


Another super PIC project from Magenta. Supplied with PCB, industry standard 2-LINE x 16-character display, data, all components, and software to include in your own programs. Ideal development base for meters, terminals, calculators, counters, timers – Just waiting for your application!

8-CHANNEL DATA LOGGER

As featured in Aug./Sept. '99 *EPE*. Full kit with Magenta redesigned PCB – LCD fits directly on board. Use as Data Logger or as a test bed for many other 16F877 projects. Kit includes programmed chip, 8 EEPROMs. PCB, case and all components.

KIT 877 £49.95 inc. 8 x 256K EEPROMS

ICEBREAKER

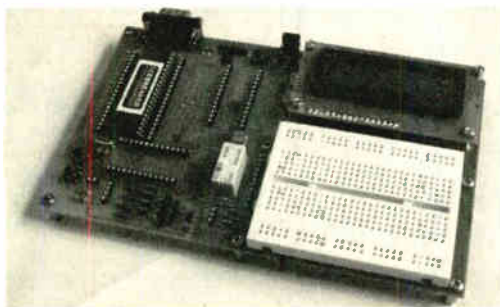

PIC Real Time In-Circuit Emulator

- Icebreaker uses PIC16F877 in circuit debugger
- Links to Standard PC Serial Port (lead supplied)
- Windows™ (95+) Software included
- Works with MPASM and MPLAB Microchip software
- 16 x 2 L.C.D., Breadboard, Relay, I/O devices and patch leads supplied

As featured in March '00 *EPE*. Ideal for beginners AND advanced users. Programs can be written, assembled, downloaded into the microcontroller and run at full speed (up to 20MHz), or one step at a time.

Full emulation means that all I/O ports respond exactly and immediately, reading and driving external hardware.

Features include: Reset; Halt on external pulse; Set Breakpoint; Examine and Change registers EEPROM and program memory; Load program, Single Step with display of Status, W register, Program counter, and user selected 'Watch Window' registers.

KIT 900 . . . £34.99

POWER SUPPLY £3.99 STEPPING MOTOR 100 STEP £9.99

EPE TEACH-IN 2004

THE LATEST SERIES – STARTED NOV '03
ALL PARTS INCLUDING PROTOTYPE BREADBOARD AND WIRE – AS LISTED ON p752 NOV. ISSUE (EXCL MISC.)
"A BRILLIANT NEW ELECTRONICS COURSE"

KIT 920 . . . £29.99

ADDITIONAL PARTS – AS LISTED UNDER MISCELLANEOUS – BUT LESS RADIO MODULES, SOLENOID LOCK AND MOTOR/ GEARBOX.

KIT 921 . . . £12.99

EPE PIC Tutorial V2

EPE APR/MAY/JUNE '03 and PIC RESOURCES CD

FOLLOW THIS SERIES WITH EPE PIC TOOLKIT 3

- THE LATEST TOOLKIT BOARD – 8, 18, 28 AND 40-PIN CHIPS
- MAGENTA DESIGNED P.C.B. WITH COMPONENT LAYOUT AND EXTRAS
- L.C.D. BREADBOARD AND PIC CHIP INCLUDED
- ALL TOP QUALITY COMPONENTS AND SOFTWARE SUPPLIED

KIT 880 . . . £34.99 WITH 16F84

PIC TUTOR 1 MARCH - APRIL - MAY '98

EPE SERIES 16F84

PIC TUTOR BOARD KIT

Includes: PIC16F84 Chip, TOP Quality PCB printed with Component Layout and all components* (*not ZIF Socket or Displays). Included with the Magenta Kit is a disk with Test and Demonstration routines.

KIT 870 £27.95, Built & Tested £42.95

Optional: Power Supply – £3.99, ZIF Socket – £9.99

LCD Display £7.99 LED Display £6.99

Reprints Mar/Apr/May 98 – £3.00 set 3

SUPER PIC PROGRAMMER

- READS, PROGRAMS, AND VERIFIES
- WINDOWS® SOFTWARE
- PIC16C AND 16F – 6X, 7X, AND 8X
- USES ANY PC PARALLEL PORT
- USES STANDARD MICROCHIP • HEX FILES
- DISASSEMBLER SOFTWARE
- PCB, LEAD, ALL COMPONENTS, TURNED-PIN SOCKETS FOR 18, 28, AND 40 PIN ICs

• SEND FOR DETAILED INFORMATION – A SUPERB PRODUCT AT AN UNBEATABLE LOW PRICE.

Kit 862 £29.99

Power Supply £3.99

PIC STEPPING MOTOR DRIVER

INCLUDES PCB, PIC16F84 WITH DEMO PROGRAM, SOFTWARE DISC, INSTRUCTIONS AND MOTOR.

Kit 863 £18.99

FULL SOURCE CODE SUPPLIED ALSO USE FOR DRIVING OTHER POWER DEVICES e.g. SOLENOIDS

Another Magenta PIC project. Drives any 4-phase unipolar motor – up to 24V and 1A. Kit includes all components and 48 step motor. Chip is pre-programmed with demo software, then write your own, and re-program the same chip! Circuit accepts inputs from switches etc and drives motor in response. Also runs standard demo sequence from memory.

MAGENTA

All prices include VAT. Add £3.00 p&p. Next day £6.99

Tel: 01283 565435 Fax: 01283 546932 E-mail: sales@magenta2000.co.uk

Everyday Practical Electronics, June 2004

373



Station Road, Cullercoats, Tyne & Wear, NE30 4PQ

Prices Exclude Vat @ 17.5%, UK Carriage £2.50 (less than 1kg) £5.50 greater than 1kg Cheques / Postal orders payable to ESR Electronic Components

See Next / Last Months Ad. for ELECTRONIC COMPONENTS

Prices Exclude Vat @ 17.5%, UK Carriage £2.50 (less than 1kg) £5.50 greater than 1kg Cheques / Postal orders payable to ESR Electronic Components

See Next / Last Months Ad. for ELECTRONIC COMPONENTS

Prices Exclude Vat @ 17.5%, UK Carriage £2.50 (less than 1kg) £5.50 greater than 1kg Cheques / Postal orders payable to ESR Electronic Components

See Next / Last Months Ad. for ELECTRONIC COMPONENTS

Prices Exclude Vat @ 17.5%, UK Carriage £2.50 (less than 1kg) £5.50 greater than 1kg Cheques / Postal orders payable to ESR Electronic Components

See Next / Last Months Ad. for ELECTRONIC COMPONENTS

Prices Exclude Vat @ 17.5%, UK Carriage £2.50 (less than 1kg) £5.50 greater than 1kg Cheques / Postal orders payable to ESR Electronic Components

RF Connectors	Push Switches	Boxes & Cases	3.579545MHz £0.41
BNC Plug 50Ω Solder £0.99	Miniature Round	Many more sizes available	3.6864MHz £0.41
BNC Plug 50Ω Crimp £0.68	250mA 125V 28 x 10mm		4.0MHz £0.45
BNC Plug 75Ω Solder £1.08	7mm Ø Mounting Hole		4.194304MHz £0.37
BNC Plug 75Ω Crimp £0.69	Non Latching Push to Make		4.33619MHz £0.31
BNC Chassis Socket £0.76	Black, Red, Yellow, Green,		4.9152MHz £0.41
F Plug - Twist £0.20	Blue or White £0.23		6.0MHz £0.34
F Plug - Crimp £0.20	Non Latching Push to Break		6.144MHz £0.41
TNC Plug 50Ω Solder £1.08	Black PTFE £0.24		7.3728MHz £0.53
TNC Plug 50Ω Crimp £1.04	Standard Square		8.0MHz £0.49
TNC Plug 75Ω Solder £1.17			8.667238MHz £0.39
TNC Plug 75Ω Crimp £0.96			11.1 x 57 x 22mm £1.12
UHF Plug 5mm Cable £0.63			11 x 57 x 22mm £1.12
UHF Plug 11mm Cable £0.72			79 x 61 x 40mm £1.70
UHF Chassis Skt - Sar £0.54			100 x 76 x 41mm £1.39
UHF Chassis Skt - Rnd £0.75			118 x 98 x 45mm £2.08
			150 x 100 x 60mm £2.77
			150 x 80 x 50mm £2.72
			Diecast Aluminium
			50 x 50 x 31mm £2.67
			100 x 50 x 25mm £3.50
			112 x 62 x 31mm £4.18
			120 x 65 x 40mm £4.61
			150 x 80 x 50mm £6.56
			121 x 95 x 61mm £7.06
			Low Profile Crystals, 2 & 3 Pin Ceramic Resonators
			Details on our web site
			Opto Electronics
			LEDs
			3mm White 900mcd £2.13
			3mm Red Led £0.07
			3mm Green Led £0.09
			3mm Yellow Led £0.09
			3mm Orange Led £0.10
			3mm Blue 40mcd £0.78
			3mm Blue 60mcd £0.78
			3mm Blue 550mcd £0.96
			5mm White 300mcd £0.69
			5mm White 3000mcd £0.65
			5mm Blue 3200mcd £0.94
			3mm Bi-Colour £0.15
			3mm Tri-Colour £0.24
			5mm Red Led £0.07
			5mm Green Led £0.08
			5mm Yellow Led £0.08
			5mm Orange Led £0.10
			5mm Blue 60mcd £0.78
			5mm BlueC 100mcd £0.78
			5mm Blue 100mcd £1.12
			5mm Blue 450mcd £1.12
			5mm Blue 1000mcd £1.12
			5mm Blue 1400mcd £1.02
			5mm Blue 2200mcd £1.02
			5mm Red Flashing £0.37
			5mm Green Flashing £0.37
			5mm Yellow Flashing £0.37
			5mm Bi-Colour Led £0.15
			5mm Tri-Colour Led £0.15
			7 Segment Displays
			0.56" Red Cathode £0.65
			0.56" Red C Anode £0.65
			0.3" Red C Cathode £0.65
			0.3" Red C Anode £0.65
			Infra Red Devices
			3mm IR Emitter £0.15
			5mm IR Emitter £0.30
			3mm Photo-Transistor £0.15
			5mm Photo Diode £0.76
			6PW4 Pin Diode £0.58
			4N25 Opto-Coupler £0.25
			4N26 Opto-Coupler £0.36
			4N32 Opto-Coupler £0.36
			6N135 Opto-Coupler £0.96
			6N136 Opto-Coupler £0.85
			6N137 Opto-Coupler £0.85
			6N138 Opto-Coupler £0.84
			6N139 Opto-Coupler £0.90
			CNY17-1 O-Coupler £0.38
			CNY17-2 O-Coupler £0.32
			CNY17-3 O-Coupler £0.48
			IS-74 Opto-Coupler £0.40
			ISD-74 Opto-Coupler £1.02
			ISQ-74 Opto-Coupler £1.41
			MOC3020 Opto-Triac £0.58
			MOC3041 Opto-Triac £0.49
			Mini LDR £0.45
			ORP12 LDR £0.10
			Technical Books & CD ROMs
			Data Table & Equivalent charts from ECA
			Characteristics, pin outs, equivalents & selector tables for semiconductors. Demo version of the CD ROMs & full details of the complete range are available from our web site
			Semiconductors Equivalents & Reference
			Covering Transistors, Diodes, Thyristors, Triacs & ICs. These reference books series covers more than 115,000 types with more than 200,000 equivalent types. Each type is provided with information as to device family, short form description and the salient electrical data, along with the dimensioned outline drawing and pin assignments. Split into two paper volumes or available on one CDROM.
			vrt volume 1 A - Z Device Codes £13.34
			ISBN 9397469001, 1184 Pages, 2004 Version
			vrt volume 2 1N, 60,000... Device Codes £13.34
			ISBN 939746901X, 720 Pages, 2004 Version
			These books are zero vat rated, carriage for one OR both £5.50+vat
			vrt-disk 2004 CD ROM £29.88+vat
			ISBN 939746908 Windows 95/98/NT/2000/XP
			The software version of the two vrt books. In addition to pin assignments of all discrete semiconductors this CD-ROM version contains the pin assignments for all standard CMOS 4000/7400, TTL 7400 circuits, many operational amplifiers and some Audio- and Video IC's. Extensive search facility, Manufacturers Details, a "Note-Function" to add your own data for each device. Carriage for CD only £2.50+vat
			Full details of UK, European or Worldwide Order Information on our web site.

Tel: 0191 2514363 Fax: 0191 2522296 Email: sales@esr.co.uk http://www.esr.co.uk

EVERYDAY PRACTICAL ELECTRONICS

THE No.1 MAGAZINE FOR ELECTRONICS TECHNOLOGY & COMPUTER PROJECTS

VOL. 33 No. 6

JUNE 2004

HOW DO THEY DO IT ?

How can they make a solar powered l.e.d. light with a light-sensitive switch, charging circuit, rechargeable batteries and a stylish plastic housing for just £3.99? This is what our local garage is selling as garden lights, and very good they are too. In fact, the staff of Wimborne Publishing must have nearly wiped out their entire stock. It would not surprise me if a plane does not land in someone's back garden soon!

If we cost up the components, the l.e.d., solar cell and two rechargeable AA batteries would be about £6.00, without a little circuit to turn it on at dusk etc. and the injection moulded housing. The same thing applies to basic digital clocks and calculators these days, and it makes one wonder if it is worth building anything yourself anymore.


Of course you only have to look at this month's and next month's contents to see the reason why our hobby continues to be popular – can you buy a MIDI Synchronome, or a Body Detector, or maybe an inexpensive Magnetometer (coming next month). There are plenty of projects like test gear, amplifiers, radios, alarms, timers, light flashers etc. that you can buy off the shelf, but where is the fun, satisfaction and "hobby" in that? As one reader put it, I cannot play golf as good as Tiger Woods but that does not mean I will not play and just watch him!

FIRST

We have also been able to introduce ideas that have later become available as commercial items – things like meters to measure the cost of electricity used by appliances, guitar tuners, l.e.d. torches, and possibly the Wart Zapper we have lined up for a future issue. Electronics continues to be a fascinating and ever changing subject, one with many facets.

We know that not every reader will be interested in building every project, but plenty of readers tell us of the knowledge they gain from reading about how the circuits work and seeing how each author solved the various problems. Or maybe they borrow a section of circuitry or a chunk of PIC software to use in their own pet designs.

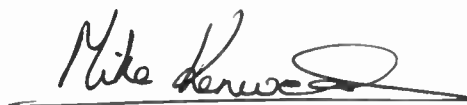The interaction between the magazine and the readers, and between readers, is great to see – our *Readout* page and the *Chat Zone* on the website are always lively forums. (Although we have only been able to fit in one page of Letters this month due to lack of space.) We are always interested in your views and ideas, so please keep them coming.



AVAILABILITY

Copies of *EPE* are available on subscription anywhere in the world (see opposite), from all UK newsgroups (distributed by COMAG) and from the following electronic component retailers: Omni Electronics and Yebo Electronics (S. Africa) *EPE* can also be purchased from retail magazine outlets around the world. An Internet on-line version can be purchased and downloaded for just \$10.99US (approx £7) per year available from www.epemag.com

SUBSCRIPTIONS

Subscriptions for delivery direct to any address in the UK: 6 months £16.50, 12 months £31, two years £57; Overseas: 6 months £19.50 standard air service or £28.50 express airmail, 12 months £37 standard air service or £55 express airmail, 24 months £69 standard air service or £105 express airmail. To subscribe from the USA or Canada see the last magazine page. Online subscriptions, for downloading the magazine via the Internet, \$10.99US (approx £7) for one year available from www.epemag.com.

Cheques or bank drafts (in £ sterling only) payable to *Everyday Practical Electronics* and sent to EPE Subs. Dept., Wimborne Publishing Ltd, 408 Wimborne Road East, Ferndown, Dorset BH22 9ND. Tel: 01202 873872. Fax: 01202 874562. Email: subs@epemag.wimborne.co.uk. Also via the Web at: <http://www.epemag.wimborne.co.uk>. Subscriptions start with the next available issue. We accept MasterCard, Amex, Diners Club, Switch or Visa. (For past issues see the *Back Issues* page.)

BINDERS

Binders to hold one volume (12 issues) are available from the above address. These are finished in blue p.v.c., printed with the magazine logo in gold on the spine. Price £6.95 plus £3.50 p&p (for overseas readers the postage is £6.00 to everywhere except Australia and Papua New Guinea which cost £10.50). Normally sent within seven days but please allow 28 days for delivery – more for overseas.

Payment in £ sterling only please. Visa, Amex, Diners Club, Switch and MasterCard accepted. Send, fax or phone your card number, card expiry date and card security code (the last 3 digits on or just under the signature strip), with your name, address etc. Or order on our secure server via our UK web site. Overseas customers – your credit card will be charged by the card provider in your local currency at the existing exchange rate.

Editorial Offices:

EVERYDAY PRACTICAL ELECTRONICS EDITORIAL
WIMBORNE PUBLISHING LTD., 408 WIMBORNE ROAD EAST,
FERNDOWN, DORSET BH22 9ND
Phone: (01202) 873872. Fax: (01202) 874562.

Email: enquiries@epemag.wimborne.co.uk

Web Site: www.epemag.wimborne.co.uk

EPE Online (downloadable version of *EPE*): www.epemag.com

EPE Online Shop: www.epemag.wimborne.co.uk/shopdoor.htm

See notes on Readers' Technical Enquiries below – we regret lengthy technical enquiries cannot be answered over the telephone.

Advertisement Offices:

EVERYDAY PRACTICAL ELECTRONICS ADVERTISEMENTS
MILL LODGE, MILL LANE,
THORPE-LE-SOKEN, ESSEX CO16 0ED
Phone/Fax: (01255) 861161 Email: epeads@aol.com

Editor: MIKE KENWARD

Deputy Editor: DAVID BARRINGTON

Technical Editor: JOHN BECKER

Business Manager: DAVID J. LEAVER

Subscriptions: MARILYN GOLDBERG

Administration: FAY KENWARD

Editorial/Admin: (01202) 873872

Advertisement Manager:

PETER J. MEW, (01255) 861161

Advertisement Copy Controller:

PETER SHERIDAN, (01202) 873872

On-Line Editor: ALAN WINSTANLEY

EPE Online (Internet version) Editors:

CLIVE (MAX) MAXFIELD and ALVIN BROWN

READERS' TECHNICAL ENQUIRIES

E-mail: techdept@epemag.wimborne.co.uk

We are unable to offer any advice on the use, purchase, repair or modification of commercial equipment or the incorporation or modification of designs published in the magazine. We regret that we cannot provide data or answer queries on articles or projects that are more than five years old. Letters requiring a personal reply *must* be accompanied by a stamped self-addressed envelope or a self-addressed envelope and international reply coupons.

PROJECTS AND CIRCUITS

All reasonable precautions are taken to ensure that the advice and data given to readers is reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it.

A number of projects and circuits published in *EPE* employ voltages that can be lethal. You should not build, test, modify or renovate any item of mains powered equipment unless you fully understand the safety aspects involved and you use an RCD adaptor.

COMPONENT SUPPLIES

We do not supply electronic components or kits for building the projects featured, these can be supplied by advertisers (see *Shoptalk*). We advise readers to check that all parts are still available before commencing any project in a back-dated issue.

ADVERTISEMENTS

Although the proprietors and staff of EVERYDAY PRACTICAL ELECTRONICS take reasonable precautions to protect the interests of readers by ensuring as far as practicable that advertisements are *bona fide*, the magazine and its Publishers cannot give any undertakings in respect of statements or claims made by advertisers, whether these advertisements are printed as part of the magazine, or in inserts.

The Publishers regret that under no circumstances will the magazine accept liability for non-receipt of goods ordered, or for late delivery, or for faults in manufacture.

TRANSMITTERS/BUGS/TELEPHONE EQUIPMENT

We advise readers that certain items of radio transmitting and telephone equipment which may be advertised in our pages cannot be legally used in the UK. Readers should check the law before buying any transmitting or telephone equipment as a fine, confiscation of equipment and/or imprisonment can result from illegal use or ownership. The laws vary from country to country; readers should check local laws.



PIC QUICKSTEP

ANDY FLIND

A simple and versatile stepper motor driver and controller

FOR mechanical applications requiring precise control, stepper motors offer many advantages over simple d.c. types. They can start and stop virtually instantly and move in tiny, precise increments. Forward and reverse operation is simple. Accurate speed control is easy to achieve through step rate, and shaft position may be tracked simply by counting the steps.

There is a downside though, since electronic circuitry is required to generate the coil drive sequence needed for operating these motors. Special stepper driving i.c.s are available but these usually offer only one out of several possible drive methods, and they often draw too much supply current for battery applications.

Additional circuitry is usually required to generate step and direction inputs so it is often a better idea to use a custom programmed PIC microcontroller for complete step sequence control, and perhaps also the controlling system.

For the experimenter who has acquired a stepper motor, the priorities will usually be to check out its speed, torque and the effects of different types of drive sequence. It might also be desired to bolt it into a prototype design and rotate it back and forth in a controlled manner to check whether the project is likely to work. The PIC QuickStep allows rapid testing of this kind with many options that can be tried out to see their effects.

MOTOR CHOICE

There are various types of stepper motor. This article is concerned only with the four-phase unipolar type. This is the most common and may be bought new from suppliers or salvaged from old computer equipment such as printers and scanners. It will usually have either 48 or 200 steps per revolution and is likely to have either five or six connecting wires, four of which connect to four internal stator coils whilst the other(s) are "common" connections to the coils.

Sometimes the coils will be arranged as two pairs with a common lead each, sometimes all four will share a single common lead. Fig.1 shows the basic arrangement.

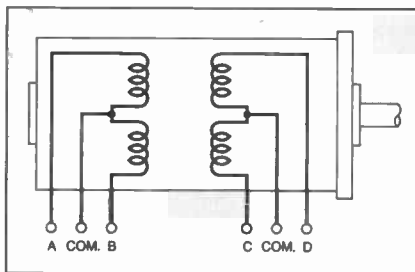



Fig.1. Connections for a 4-phase unipolar stepper motor.

The rotor of one of these motors is permanently magnetised so when its shaft is turned a "cogging" effect can be felt as its poles pass the poles of the stator. Fig.2 is a greatly simplified diagram showing the connections to a 4-phase unipolar stepper motor.

The rotor poles are facing stator coil A. If coil B is energised the rotor will turn one step to face it. If C is energised it will turn to face C, and then D, then A again. So by energising each coil in the sequence A, B, C, D, A... clockwise rotation is achieved. Powering the coils with the opposite sequence, A, D, C, B, A... would produce anti-clockwise operation.

WAVES AND STEPS

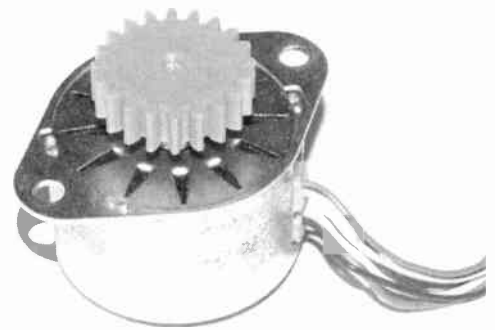Powering one coil at a time is known as wave operation and has the advantage of



low supply current and, if the supply is turned off, the motor is likely to stay where it is due to the attraction of the permanent magnet rotor to the last energised pole.


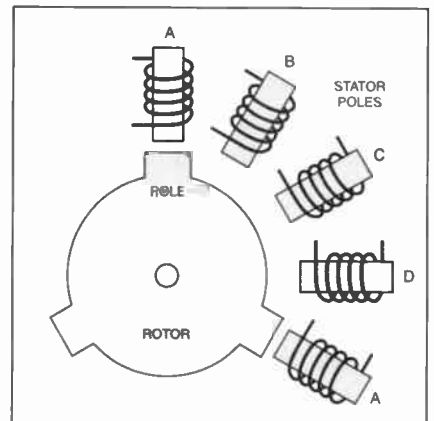


Fig.2. Stepper motor operation basics.

The drive method used by most stepper driver i.c.s is called *full step*. The coils are energised two at a time, A+B, B+C, C+D, D+A, A+B... This gives nearly twice the torque but also draws twice the supply current, and if the power is turned off the rotor may move slightly since it has been left halfway between two stator poles. For these reasons wave stepping may be preferable for some designs.

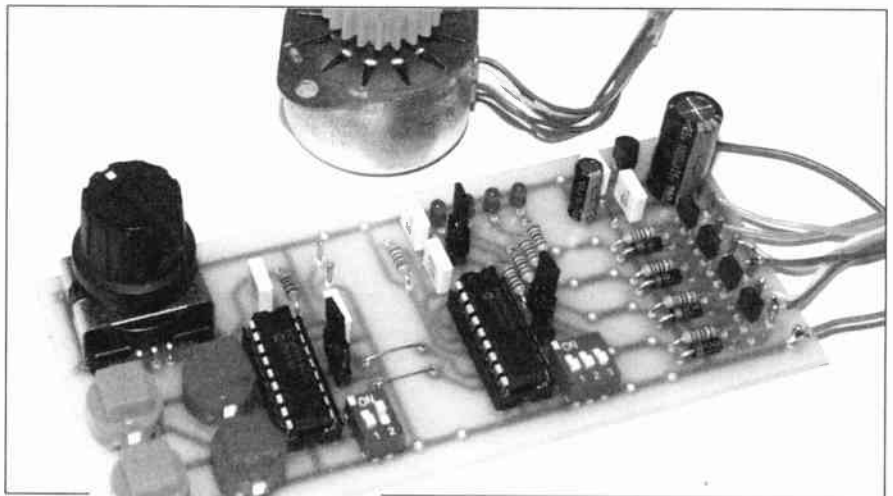Finally, where greater precision or smoother rotation is required, half stepping may be employed. This is a hybrid



of full and wave stepping where the energising sequence takes the form of A, A+B, B, B+C, C . . . , the picture should be clear enough. For a given step rate the motor will rotate at half the speed given by the other two methods, but the increased precision and smoothness is instantly apparent.

It normally takes less than a couple of milliseconds for the motor to move. If the power stays on it will take considerable torque to move the motor from its static position, which can be useful. However, if the torque applied to the motor shaft is minimal it may be better to turn off the power between steps. This brings large power savings and may be the only practical solution for long-term battery operation. A "power-down" feature in QuickStep can be used to try this out.

CIRCUIT DIAGRAM

In the full circuit diagram of Fig.3 it can be seen that the QuickStep project is split into three sections. The first is the controller, based around IC1, a PIC16F628. Four pushbutton switches provide basic control, S5 for single step forward, S4 for single step reverse, S6 continuous stepping forward, and S3 continuous reverse. These four buttons are all "debounced" in software.

During continuous operation the speed may be controlled by variable resistor VR1 over a range slightly greater than ten to one, nominally from one step per second to 10 steps per second. The action of VR1 is non-linear, but adequate for testing.

Two switches, S1 and S2, multiply the speed range by ten or a hundred. S1 gives 10 to 100 steps per second and S2 gives 100 to 1000 steps per second. If both switches are "on", S2 takes precedence. The output from this part of the circuit consists of "forward step" commands from RA0 and "reverse step" commands from RB6.

Many dedicated stepper controller: i.c.s do not use this method, instead they have "direction" and "step" inputs. To allow the QuickStep controller to be used with such i.c.s this method of operation is also available and may be selected by fitting link LK1. When this is done S5 controls direction through RA0, and S4 and S3 provide single and continuous steps respectively from RB6. In this mode "direction" switch S5 is not debounced, but S4 and S3 are, whilst S6 is not used.

During continuous stepping, RA1 provides output from test point TP1 for a frequency counter so that the precise step rate can be measured. There's little point in showing flowcharts for this project. Because of the many options available they are complex and space probably would not allow their inclusion. Basically both PICs check through the switches to locate the required action and then execute it.

The timer operation using VR1 may be of interest though; it works as follows. RA4 is made an output, taken low, and a few microseconds are allowed for C1 to discharge. It is then made an input again so C1 charges through VR1 and R1. As an input RA4 has a Schmitt trigger characteristic, ideal for this purpose. For timing, it is now only necessary to check occasionally to see if it has gone high.

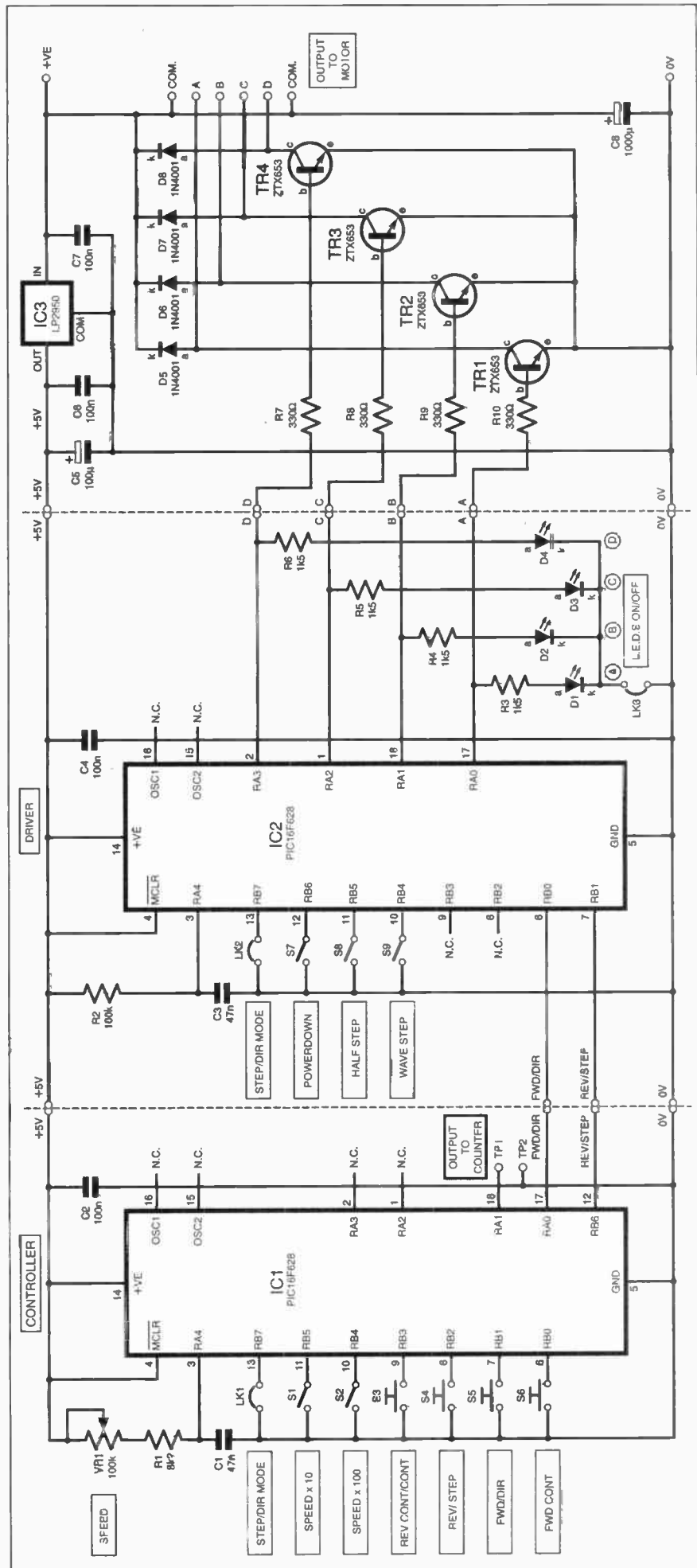


Fig.3. Complete circuit diagram for the PIC QuickStep stepper motor controller and driver.

PIC devotees will notice that there are no oscillator components in this circuit. The PIC16F628 has an internal 4MHz oscillator for use where timing is non-critical, thus saving the bother of including the usual oscillator components.

All the inputs and outputs of this circuit are "active low" since this allows use of the internal weak pull-ups of Port B, removing the need to use external resistors with the switches and buttons. If the circuit is used to test a commercial stepper driver i.c. it may need reversal of the outputs to "active high", as discussed later.

STEPPER DRIVER

The second part of the circuit, around IC2, another PIC16F628, is the stepper driver. It has two inputs, "step forward" and "step reverse" through RB1 and RB0 respectively. As with the controller section, fitting link LK2 changes these inputs to "direction" and "step" so that it can be used with a circuit designed for this type of input.


If switches S8 and S9 are both open the output will be full step, otherwise S8 selects half step and S9 wave step. If both are closed, half step takes priority.

The "powerdown" feature can be selected with S7; this causes all outputs to be turned off after about 5ms of inactivity. The timing for this is set by resistor R2 and capacitor C3 so it may be altered to some extent if desired.

Active outputs are indicated by low-current l.e.d.s D1 to D3, so at slow speeds the output sequence can be clearly seen. These diodes can be turned off by removing link LK3. Once again, the inputs are all "active low" to allow use of Port B's weak pull-ups option. It would have been possible to have the two links between IC1 and IC2 operate in "active high" mode, but this would have led to both inputs to IC2 being seen as "active" if open circuit, so this option was not taken.

Again, the flow chart is complex and would probably not be very helpful, so instead here are some guidelines on driving a stepper motor with PIC software. The method used by the author is to have a table containing the required step patterns, four of them for full and wave step, eight for half step, see Listing 1.

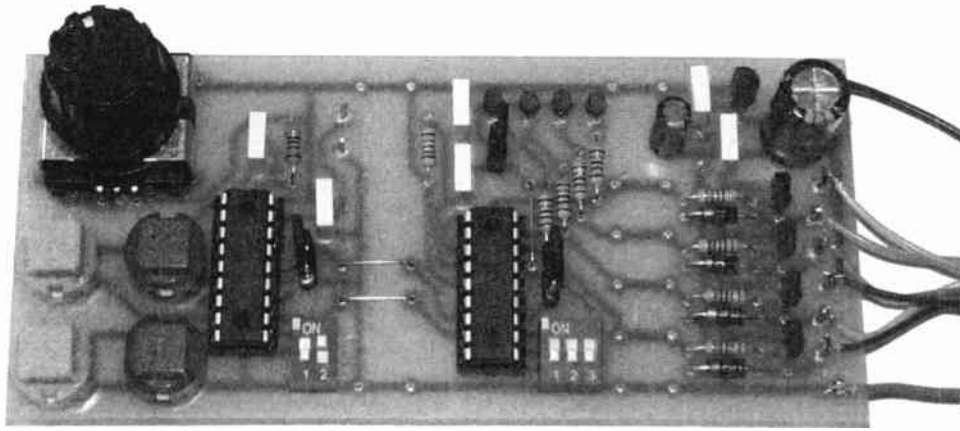The register called STEPS is incremented or decremented for forward or reverse. The least significant two bits (or three bits



Component layout on the completed circuit board.

for half step) of this register always contains the required step number, the values of its other bits do not matter.

When a call is made to the table, the value of STEPS is loaded into the working register W, ANDed with binary 00000011 or 00000110 (3 or 6) to get rid of the unwanted bits, then added to the program counter for a "return with literal in W" operation. A call to the table thus comes back with the required pattern in the W register, all ready to be copied into an output port, in this case Port A. This makes stepper driving a cinch. Alter the value of STEPS, call the table, output the value, job done.

Note that if this part of the circuit is constructed with just IC2, decoupling capacitor C4 and a wire link in place of LK2, it will perform the job of most dedicated stepper driver i.c.s by providing full-step operation from "direction" and "step" inputs. All the other components can be simply omitted for this.

OUTPUT DRIVER

The output stage consists of four ZTX653 transistors to power the motor coils. Despite their tiny E-line packages, these are 2A transistors, though the amount of bias provided by this circuit only safely allows for 1A or so per coil. This should be more than enough for most steppers, many of which take a couple of hundred milliamps or less. Diodes D5 to D8 protect against back-e.m.f. surges as the coils are turned off.

A 5V regulated supply is included in this section to provide power for the two PICs. Regulator IC3 is a low-dropout micropower type, suitable for battery operation. If the supply voltage falls below 5V it will follow it down with little further drop, so the circuit can either be used as it is with a 5V motor, or IC3 can be replaced with a link from input to output.

Additionally, this supply could feed other sections of control circuitry in the user's application. The main supply will be chosen to suit the motor, often 5V or 12V, though a maximum of 25V can be accommodated.

LISTING 1: Driving a Stepper Motor with a PIC Microcontroller

```

; TABLE FOR FULL STEPS
TABFULL    MOVF STEPS,W
            ANDLW B'00000011'
            ADDWF PCL,F
            RETLW B'00000011'
            RETLW B'00000110'
            RETLW B'00001100'
            RETLW B'00001001'

; STEP CLOCKWISE
CW STEP    INCF STEPS,F
            CALL TABFULL
            MOVWF PORTA
    
```

COMPONENTS

Resistors

R1	8k2
R2	100k
R3 to R6	1k5 (4 off)
R7 to R10	330Ω (4 off)

All resistors 0.6W 1%.

See
**SHOP
TALK**
page

Potentiometer

VR1	100k rotary carbon, p.c.b. mounting, lin.
-----	---

Capacitors

C1, C3	47n polyester layer, 5mm pitch (2 off)
C2, C4, C6, C7	100n polyester layer, 5mm pitch (4 off)
C5	100μ radial elect. 10V
C8	1000μ radial elect. 25V

Semiconductors

D1 to D4	3mm red l.e.d., low current (2mA), (4 off)
D5 to D8	1N4001 rectifier diode (4 off)
TR1 to TR4	ZTX653 npn transistor (4 off)
IC1, IC2	PIC16F628 pre-programmed (see text) (2 off)
IC3	LP2950CZ-5 micropower +5V regulator

Miscellaneous

S1, S2	2-way 4-pin d.i.l. switch (2 off)
S3, S6	push-to-make keyboard switch, p.c.b. mounting, red (2 off)
S4, S5	push-to-make keyboard switch, p.c.b. mounting, green (2 off)
S7 to S9	3-way 6-pin d.i.l. switch (3 off)
LK1 to LK3	2-way single row 2.54mm p.c.b. header plug plus jumper link (3 off)

Printed circuit board, available from the EPE PCB Service, code 448; 18-pin d.i.l. sockets (2 off); knob; terminal pins; connecting wire; solder, etc.

Approx. Cost
Guidance Only

£21

excl. servo, case & p.s.u.

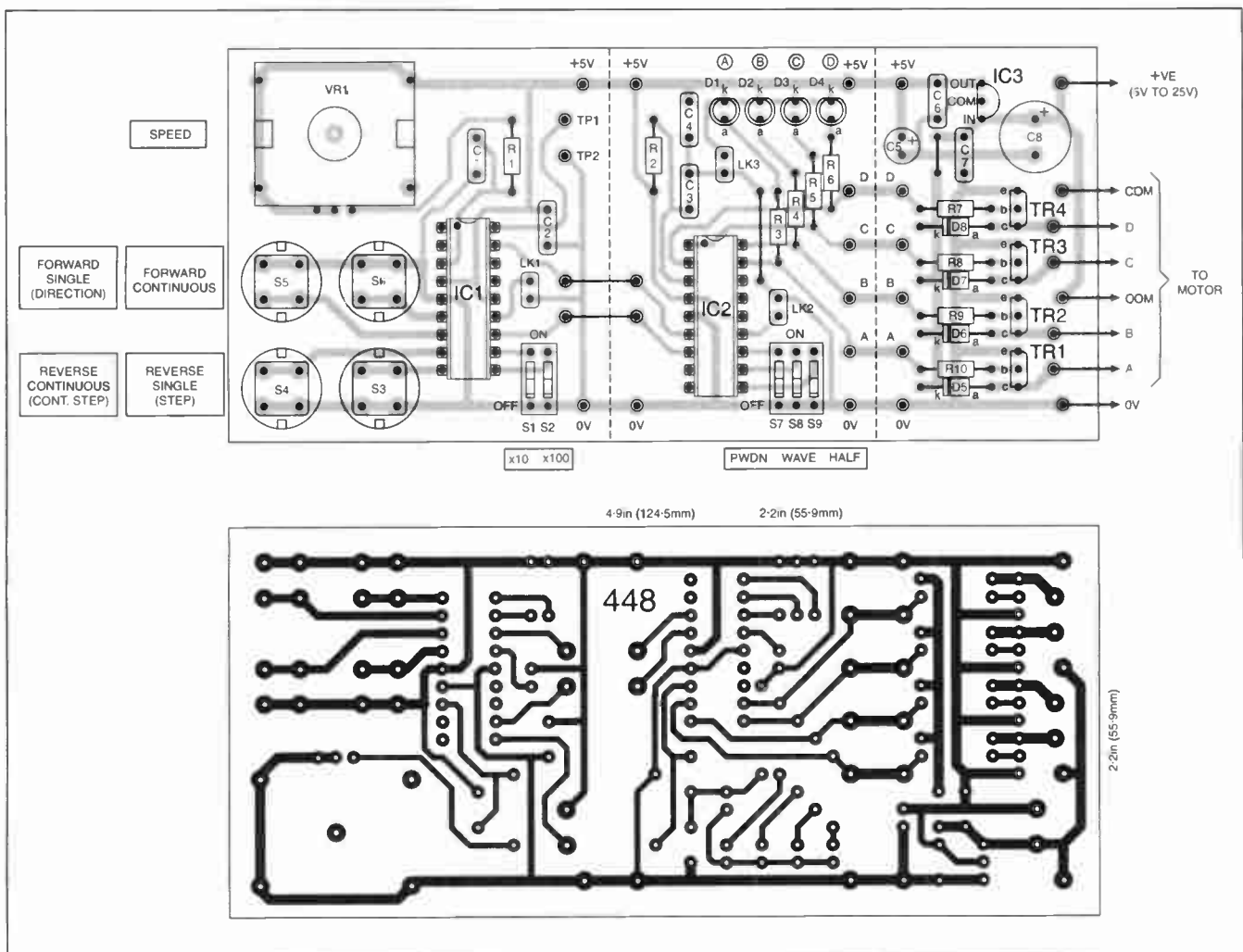


Fig.4. PIC QuickStep printed circuit board component layout and full-size copper foil master. Refer to Fig.1 for motor wiring.

CONSTRUCTION

The layout of components on the printed circuit board is shown in Fig.4. This board is available from the *EPE PCB Service*, code 448. It has been designed so that it can be literally cut into three sections if some of the functions are not required. On the left is the controller, which can drive a dedicated i.c. if needed. In the centre is the driver, and on the right the power output stage.

Positions for pins to give access to the inputs and outputs of each section are provided, but there is no need to fit these unless they are likely to be needed. The prototype has just the supply and output pins fitted, plus the two for frequency counter connection.

Dual-in-line (d.i.l.) sockets should be used for both PICs. All the other components are soldered directly to the board. Potentiometer VR1 is a type designed to fit to the component side of the board with a built-in mounting bracket, but where this is not available there is sufficient room to fit a standard pot to the board with its mounting bush and nut, and connect it with short leads.

All the components except IC1 and IC2 should be fitted. Thoroughly check the accuracy of your assembly and soldering before applying power.

OPERATIONAL CHECKS

The first check is to power up with a supply of 6V or more, and check that the 5V


output from IC3 is present and correct. After this IC1 can be inserted. Link LK1 should be omitted and switches S1 and S2 should be off. The two outputs, the wire links to the right, should be high (+5V). If S5 is pressed, the upper output link should go low (0V). If S6 is pressed, the upper output link should alternate between high and low at a rate adjustable with VR1.

Switches S4 and S3 should have a similar effect on the lower output link. If this works, this part of the circuit should be fully functional, but feel free to try "direction and step" mode with link LK1 fitted, and to check out the counter output from TP1 if desired.

IC2 can be fitted next, with LK2 omitted and LK3 in place. Incidentally, LK1 and LK2 should always be fitted or removed as a pair so that the modes of IC1 and IC2 are the same, so LK1 should also be omitted at this point in testing.

If S9 (Wave) is on and S7 and S8 are off, repeatedly pressing S5 (Forward Single Step) should result in the l.e.d.s lighting sequentially, one at a time from left to right. S4 (Reverse Single Step) should have them lighting from right to left. Switching off S9 will show the full-step sequence, and switching on S8 will show the half steps. Switching on S7 (Powerdown) should show brief l.e.d. flashes as pushswitches S3 to S6 are pressed.

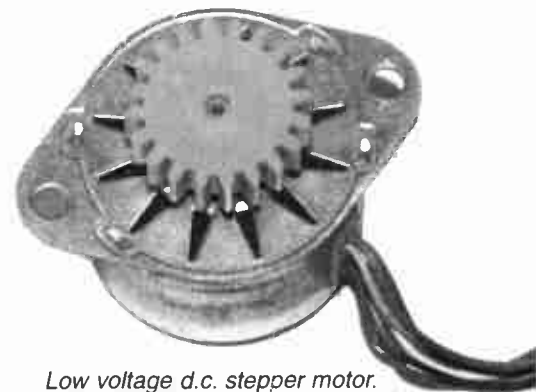If LK1 and LK2 are now fitted, S4 should cause the stepping and S5 should set the direction.



Low voltage d.c. stepper motor.

MOTOR CONNECTIONS

The unit can now be tested with a motor! If this came with connection data there should be no problem connecting it up to this project. If it didn't, or it was salvaged from scrap equipment, the connections will have to be identified.

The "common" leads can be located with a meter. Where a resistance can be measured across any two leads, it will be found that it will be either the value for a coil lead to a common, or twice that value, i.e. two coils in series via a common. So, the common(s) will be the lead(s) having the lower resistance value compared to two or more of the others. Fig.1 shows how this comes about.

Having identified the common(s), connect them to the positive output of a

atlas LCR

£79

Passive Component Analyser


(Model LCR40)

fully inclusive UK price

Just clip on the test leads and press test. The Atlas LCR will automatically identify the type of component, apply the appropriate test level and frequency, display the component's value and more!

Probes are detachable too, so you can use the optional SMD tweezers for your tiny unmarked passives - fantastic.

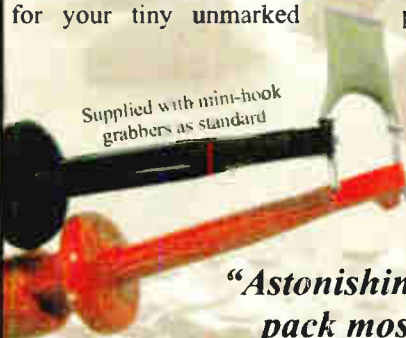- Automatic component identification (Inductor, Capacitor or Resistor)
- Component value measurement
- Auto frequency (DC, 1kHz, 15kHz, 200kHz)
- Inductor DC resistance measurement
- Non-volatile probe compensation memory
- Detachable probes allowing use of optional test prods. SMD tweezers, etc...
- Hands free mode with value hold



Supplied with mini-hook grabbers as standard

Inductance range: 1µH to 10H
 Capacitance range: 1pF to 10,000µF
 Resistance range: 1Ω to 2MΩ
 Basic accuracy: 1%
 Test signals: 1V, 3mA max

"Astonishingly, this little unit seems to pack most of the punch of a large and very expensive automated LCR bridge into its tiny case."

Andy Flind - EPE Magazine March 2003

See the full review on our website!



features high contrast green-mode LCD

Accessories:

- Carry case
 - Tweezer Probes
 - Crocodile Probe Set
 - Large Grabber Probes
- (more available soon)

atlas DCA

£60

Semiconductor Analyser

(Model DCA55)

full inclusive UK price

NOW MEASURES TRANSISTOR LEAKAGE!



enclosure colours may vary

Check and identify your semi's

- Bipolar transistors,
- Darlington transistors,
- Diode protected transistors,
- Resistor shunted transistors,
- Enhancement mode MOSFETs,
- Depletion mode MOSFETs,
- Junction FETs,
- Low power triacs and thyristors,
- Diodes and diode networks,
- LEDs (+bicolours)

- Automatic component identification
- Pinout identification
- Transistor gain measurement
- MOSFET gate threshold measurement
- PN junction characteristics measurement
- Shorted Junction identification
- Transistor leakage measurement
- Just connect the part anyway round and press the button!
- Auto power on/off

"It's the kind of instrument that should be on every engineers and enthusiasts bench."

EPE Magazine March 2000

NPN bipolar Darlington
 Diode protection between C-E
 Resistor shunt between B-E
 Current gain Hfe=126
 Enhancement mode N-Ch MOSFET
 Gate Threshold Vgs=3.42V
 RFD 6.1 BLUE
 B... ..mit
lta
77U
 P... ..
 ka
 =0.2

atlas PACK £129!

LCR40 and DCA55 Pack

fully inclusive UK price

Why not order both analysers at the same time and take advantage of our special offer, saving you £10!



Visit www.peakelec.co.uk to download the data sheets, user guides and copies of independent reviews. You can pay using a cheque, postal order, credit or debit card and even pay securely online. Please contact us for your volume requirements.

Also available from Farnell, Maplin, Rapid and CPC (prices vary)




Atlas House, Kiln Lane
Harpur Ind. Est., Buxton
Derbyshire, SK17 9JL, UK

www.peakelec.co.uk
sales@peakelec.co.uk

Tel. 01298 70012 Fax. 01298 70046



INGENUITY UNLIMITED

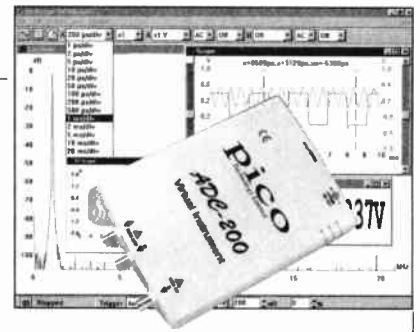


WIN A PICO PC BASED OSCILLOSCOPE WORTH £586

- 100MS/s Dual Channel Storage Oscilloscope
- 50MHz Spectrum Analyser
- Multimeter • Frequency Meter
- Signal Generator

If you have a novel circuit idea which would be of use to other readers then a Pico Technology PC based oscilloscope could be yours.

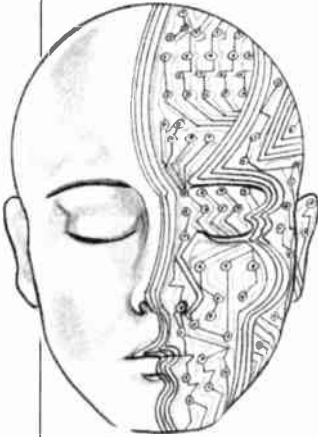Every 12 months, Pico Technology will be awarding an ADC200-100 digital storage oscilloscope for the best IU submission. In addition, a DrDAQ Data Logger/Scope worth £69 will be presented to the runner up.



Our regular round-up of readers' own circuits. We pay between £10 and £50 for all material published, depending on length and technical merit. We're looking for novel applications and circuit designs, not simply mechanical, electrical or software ideas. Ideas *must be the reader's own work* and **must not have been published or submitted for publication elsewhere**. The circuits shown have NOT been proven by us. *Ingenuity Unlimited* is open to ALL abilities, but items for consideration in this column should be typed or word-processed, with a brief circuit description (between 100 and 500 words maximum) and full circuit diagram showing all component values. **Please draw all circuit schematics as clearly as possible.**

Send your circuit ideas to: *Ingenuity Unlimited*, Wimborne Publishing Ltd., 408 Wimborne Road East, Ferndown Dorset BH22 9ND. (We do not accept submissions for *IU* via E-mail.) Your ideas could earn you some cash and a prize!

White Noise Generator – Sound Check

HAVING a need to align the centre frequency and bandwidth of an 8MHz filter in a radio set, it was decided to find an alternative to using an expensive Spectrum Analyser. This is not a common item of test gear for your average experimenter and is not something the writer owns.

A cheaper alternative, although not as accurate, is to feed the output of a noise generator into the filter and adjust the filter for maximum output. A "white noise" generator is a useful piece of inexpensive test gear and it was decided to explore this further.

Investigating the existing literature suggests that a Zener diode was a good noise source. Some tests with a few "spares box" Zeners were disappointing, providing quite a low output even after amplification.

A very useful alternative to the Zener, using an "inverted" transistor, is shown in the White Noise Generator circuit diagram Fig. 1. The noise source itself is the BC549 transistor followed by two 2N3904 transistors, used for amplification of the noise.

The interesting characteristic of this circuit is that TR1 is connected the wrong way round. Usually, an npn transistor's collector (c) is positive with respect to its emitter (e). It was found that by connecting it in this way results in a great rush of "white noise". I do not recommend this treatment for an npn transistor under normal conditions, but as an experiment it worked very well.

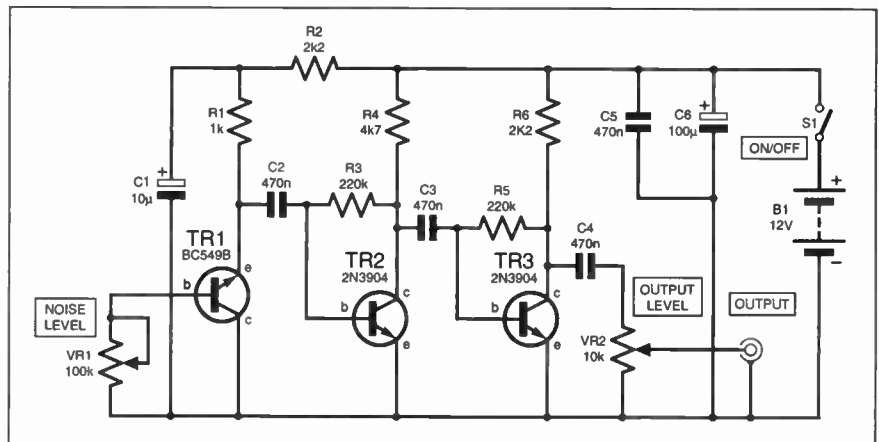


Fig. 1. Circuit diagram for a White Noise Generator.

Potentiometer VR1 needs to be adjusted for maximum output, as measured at the collector of TR3, or simply take a length of wire from your receiver antenna socket and place it a few centimetres away from the generator's noise output. Tune the receiver to any frequency up to 30MHz and the noise should be apparent.

The output level can be adjusted by potentiometer VR2. This measured about 5V peak-to-peak output up to 30MHz, so I expect it could be used in the v.h.f. region.

Also, the high output could prove useful in driving passive r.f. bridges for measurement of circuit impedance or antenna characteristics.

Using a BC549 is not critical and other types could work as well or even better in this circuit. This is a matter for experiment. Potentiometer VR1 can be replaced with a fixed resistor once you are satisfied with the output.

Alan Lippett,
Stafford

Pressure Pad – Step On It!

TRADITIONAL pressure mats (or pads) may be useful in a variety of applications, particularly for security. A smaller sized pressure pad may be especially useful in soft toys, to trigger a sound or an action.

However, pressure mats (or pads) of any kind tend to be pricy, even without the electronics. They also tend to be tailored to specific applications, and this may limit their uses. While one could resort to a simple pressure switch, such switches often pose problems with mounting.

The design in Fig. 2 uses a sandwich made of conductive foam as the pressure pad. Conductive foam sheets are widely and inexpensively available, being used in particular for the safe storage of static sensitive devices. A small piece, say 2cm x 2cm, can be sandwiched between two similar sized pieces of copper-clad board, with the copper making contact with the conductive foam on each side. If the conductive foam is a little brittle to begin with, it may be softened up by squeezing it. The "sandwich" may be held together with sticky-back tape.

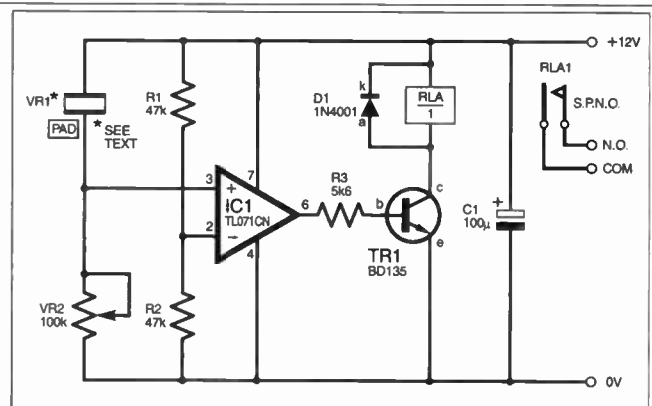


Fig. 2. Versatile Pressure Pad circuit diagram.

Dual-mode Charger – Powerful Advantage

THERE are two main types of battery charger – constant voltage and constant current. Both have their advantages and disadvantages. For constant voltage, the battery cannot be overcharged but the charging rate is slow. Constant current mode can charge batteries more swiftly, but there is the danger of overcharging them.

The circuit in Fig.3 was designed to combine both modes, but without their disadvantages, for use with a 6V sealed lead-acid battery. The main players of the circuit are voltage regulator IC1, which is used for constant current mode, and precision adjustable shunt regulator IC2, which is used for constant voltage mode.

In constant current mode, resistor R4 sets the current at 370mA, according to the equation:

$$R4 = (1.25/I) \times 1000$$

where I = the constant current required, in milliamps.

Diode D3 prevents the battery from discharging back into IC1 if the input supply is disconnected. Resistor R3 provides current to switch on transistor TR1 when the input supply is present.

Shunt regulator IC2, resistors R6, R7 and preset potentiometer VR1 form the network which determines whether or not the battery has reached its required voltage. When the voltage at IC2's reference input reaches 2.5V, IC2 switches on its internal transistor, connecting IC1's ADJ (adjust) pin to 0V. In this condition, IC1 holds IC1 in constant current supply mode. Capacitor C3 helps to stabilise the switching of IC2.

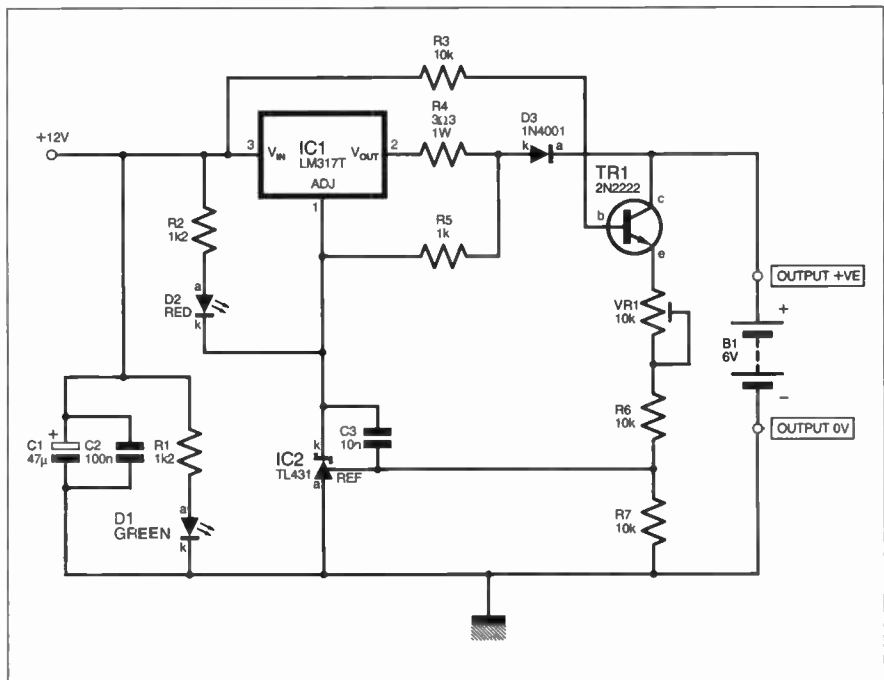


Fig.3. Circuit diagram for a Dual-mode Charger.

Capacitors C1 and C2 decouple the d.c. input supply voltage. Light emitting diode D1 is a power-on indicator, and i.e.d. D2 is turned on when constant voltage mode is activated. A heatsink may be needed with IC1.

In use, adjust preset VR1 so that the voltage at the output suits the peak voltage required by the sealed lead-acid battery,

which is usually printed on its body. Once adjusted correctly, it should not need further adjustment.

The author used a 12V 600mA d.c. adapter for powering the circuit. The battery with which it is used has a peak voltage range of 6.9V to 7.12V.

Myo Min, Yangon, Myanmar

Simple Siren – Cacophony Unleashed!

THE circuit shown in Fig.4 provides a smooth, piercing, wailing siren with a minimum of components. Not only this, but three spare gates of hex inverter IC1 remain, which means that a true cacophony could be created by running two sirens off the same i.c.

Gate IC1a is configured as a slow oscillator which repeatedly charges and discharges capacitor C1. The charge on C1 is used to control the conductance of power MOSFET TR1, which in turn modifies the frequency of the audio oscillator formed around IC1b. IC1c serves as a buffer. The period of the siren is determined by C1 and resistor R1, and its frequency by C2 and R2.

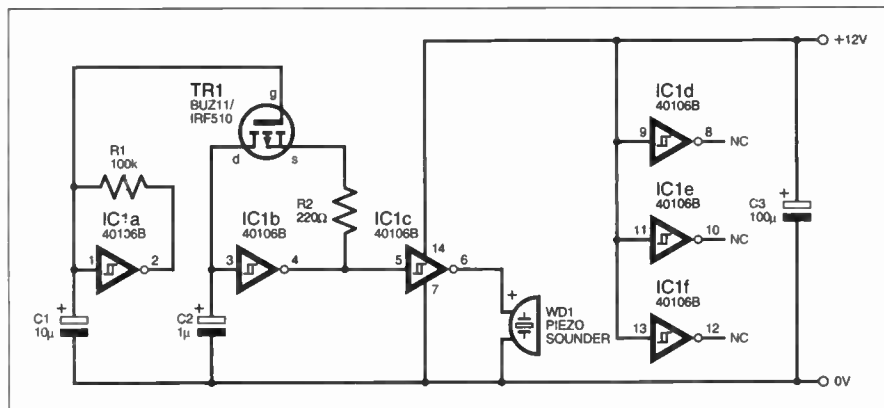


Fig.4. Circuit diagram for a Simple Siren.

Ideally, C2 and R2 will be selected to find the resonant frequency of the piezo sounder for maximum volume. If a piezo tweeter is used, the Simple Siren will produce an impressive volume. An inductive sounder (e.g. a speaker) may be used if a capacitor (e.g. 100μF) is wired in series with it.

Thomas Scarborough,
Cape Town, South Africa

This is then wired to the simple circuit as shown in Fig.2, which is a common j.f.e.t. op.amp wired as a non-inverting comparator. Supply voltage may vary within wide margins (3.5V to 18V). Although a 12V relay is shown here (RLA), the output (pin 6) may be used to switch any logic circuit of corresponding supply voltage.

When minimal pressure is applied to the "sandwich", the resistance of the foam may represent around half a megohm. When pressure is applied, resistance drops dramatically. It will easily drop to 10kΩ, and with heavy pressure may drop below 1kΩ. Depending on the application, VR1 adjusts the circuit to respond to the appropriate amount of pressure.

Different sizes of pressure pad may be built, and in this case one only needs to ensure that potentiometer VR1 is suitably chosen and adjusted to the resistance of the pressure pad, with the voltage at pin 3 rising above that of pin 2 (half supply voltage) when pressure is applied.

More innovative uses are possible, e.g. switching off the light when getting into bed, or monitoring the amount of time someone spends in a seat.

Thomas Scarborough, Cape Town, South Africa

INGENUITY UNLIMITED BE INTERACTIVE

IU is *your* forum where you can offer other readers the benefit of your Ingenuity. Share those ideas, earn some cash and possibly a prize!



HI-FI GETS HIGHER!

BARRY FOX

TAG McLaren Audio - the top end hi-fi spin-off from the F1 motor car racing company - looks like starting a new trend in home cinema. New AV amps from TAG add a "height" channel to make helicopters and aeroplanes "fly overhead". Owners of existing AV32R or AV192R amps can download new control software which adds the feature.

An extra speaker is fitted to the ceiling and connected to the wires normally used to drive a rear right surround speaker. The existing rear right speaker shares the feed to the rear left.

Any movie sound which moves from front to rear, or rear to front, is detected and fed to the ceiling speaker. So planes appear to be moving overhead.

An on/off switch stops F1 racing cars flying overhead as well!

THE CAT FROM OZ!

"ELECTRONICS - from Australia?! You have to be joking?" is the exclamatory opening line statement on the press release from Jaycar Electronics! It goes on to say: "No not all! The hobby electronics market in Australia has been historically very strong with large numbers of enthusiasts serviced by dynamic electronic magazines and vigorous commercial suppliers."

Jaycar Electronics is "the most dominant company in this Down Under market" and is now in a position to offer its great range of products to a wider audience, thanks to the internet, through which they have been doing business for over 10 years, using 128-bit secure-online ordering.

Their brand new 2004 catalogue is priced in UK pounds and is crammed with over 6000 "exciting products". You can get one free by logging on to www.jaycar-electronics.co.uk/catalogue. Jaycar tell us that they stock a huge range of exciting kits, a great range of robotics and electronics components, plus a large range of gadgets. They also stock security, surveillance, audio/video, lighting, computer and telecom parts etc.

For more information contact Jaycar Electronics, Dept EPE, 100 Silverwater Road, Silverwater, NSW 2128, Sydney, Australia. The Australian website address is www.jarcar.com.au.

RADIO PROPAGATION

IAN POOLE, whose *New Technology Updates* until recently graced our pages for many years, has had a new book published, *Radio Propagation - Principles and Practice*. The book gives clear introductions to various aspects of the title subject, covering the ways in which radio waves travel at frequencies beyond the Medium Wave broadcast band right up to the microwave region of the frequency spectrum. Readers are given a sound grounding in the subject to enable them to understand why radio signals are heard and how best to hear them.

The book is priced at £14.99, ISBN 1872309976, and is published by the Radio Society of Great Britain, Lambda House, Cranborne Road, Potters Bar, Herts EN6 3EJ. Tel: 0870 904 7373. Fax: 0870 904 7374. Email: sales@rsgb.org.uk. Ian Poole can be contacted via ian.poole@radio-communications.co. Web: www.radio-electronics.com.

SCOPE TRAINING

FLUKE, the world leader in compact, professional electronic tools, is offering a free interactive oscilloscope training CD. Designed to operate on a standard PC, the guide provides illustrated lessons regarding standard analogue and digital scopes and their use.

For more information contact Fluke (UK) Ltd, Dept EPE, 52 Hurricane Way, Norwich, Norfolk NR6 6JB. Tel: 0207 942 0700. Fax: 0207 942 0701. Email: industrial@uk.fluke.nl. Web: www.fluke.co.uk.

John Linsley Hood


We regret to report the death of John Linsley Hood on 11 March 2004, aged 79.

Born on 9 February 1925, JLH became renowned for the quality of his audio designs. He published numerous technical feature articles in the leading electronics-related journals, from *Hi-Fi News* and *Short Wave Magazine* to *Wireless World* and *Electronics World*, and twice he also wrote for us.

He was the author of several well-respected books, including *Audio Electronics* and *The Art of Linear Electronics*. A list of his books and published articles is at www.tcaas.btinternet.co.uk/jlharticles.htm.

Our thanks to reader John North for advising us of JLH's death.

ELECTRICKERY

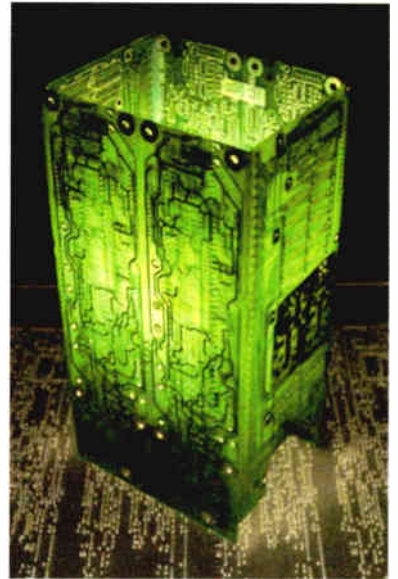

Now here's an intriguing story told in one press release received here at HQ - David Wright, an architect and founder of the design company Electricravery, has struck upon the innovative idea of using printed circuit boards in the construction of lights. He has discovered that passing light through translucent circuit boards can create amazing effects. He has just received a patent to cover this.

So what's new, you may be wondering - anyone who makes their own boards will know that when they hold their boards to the light to check that all the holes have been drilled that they are translucent in the non-track areas. What David has found, though, is that there is an infinite variety of colours and designs of circuit boards, and that many thousands of them are discarded each year by the electronics industry. He is now exploiting this resource to good effect.

What started as simple four-sided pendant lamps has turned into intricate multi-dimension installations and commissions. Electricravery have participated in a number of exhibitions and installed numerous private commissions.

David says that if anyone has a domestic or business space that could do with some exciting lighting, he can design "something ideal" for it. "We are always being inspired by our customers and their ideas to design and build totally new forms of lighting", he comments enthusiastically.


For more information contact David Wright at Electricravery.

Tel: 020 7610 9877.


Email: david.j.wright@freeuk.com.

Web: www.electrickery.uk.com.

Mention *EPE* when you contact him!

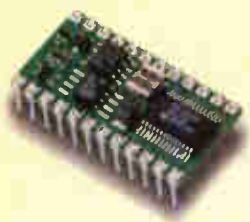


BS2-1C

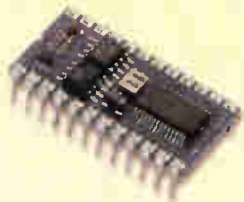

BS2-SX



BS2E-1C

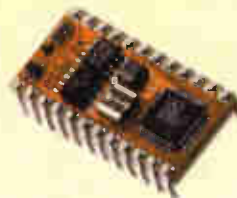


BS2P/24



BS2P/40

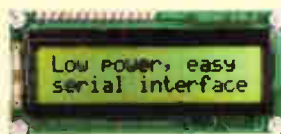Parallax BASIC Stamps - still the easy way to get your project up and running!



**Serial Alphanumeric and Graphic Displays,
Mini-Terminals and Bezel kits**

www.milinst.com



Animated Head



3-Axis Machine



Six-Legged Walkers



Robotic Arms




Bipeds

Robotic models for both the beginner and the advanced hobbyist



Servo Drivers

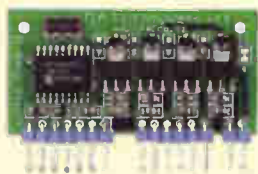


Motor Drivers



On-Screen Displays



DMX Protocol

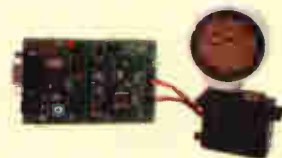

U/Sound Ranging

Animatronics and Specialist Interface-Control Modules



Quadravox
MP3 & Speech Systems



SensoryInc
Voice Recognition



Parallax
Ubicom Tool Kits



Tech-Tools
PIC & Rom Emulators




BASICMicro
PIC BASIC Compilers

Development Tools

Milford Instruments Limited Tel 01977 683665, Fax 01977 681465, sales@milinst.com

CLINICAL ELECTROTHERAPY

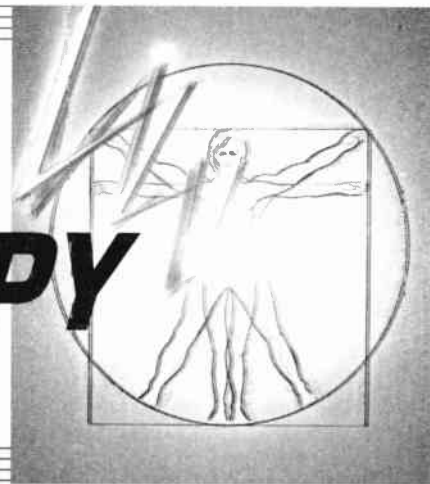

ED BYE

The application of clinical electrotherapy covers just about the full spectrum of electricity and magnetism, from direct currents through to light waves. Here we take a very brief look at developments through the ages and highlight some of its possible future progress.

THIS article starts by looking at some early developments in medical electricity and goes on to look at some current day clinical applications across the whole spectrum, including some areas of research and pioneering technology as well as other related topics.

HISTORY OF ELECTROTHERAPY

Man's interest in electrotherapy probably extends several thousand years before the birth of Christ. At that time only natural forms of magnetism and electricity existed. Many bracelets, necklaces and other items of jewellery made from loadstone have been found. Fishermen were certainly aware of the electrical discharge effect obtainable from certain types of fish; the electric torpedo fish is capable of delivering a very painful shock.

The first recorded clinical application of electric shock therapy is attributed to Roman physician Scribonius Largus in 46AD, using the electric power of a torpedo fish as a cure for headache and gout. Galen (131 – 201AD) also advocated the use of the electric torpedo fish for all types of disease and ailments. He is perhaps the first to try muscle stimulation by electricity from a fish in his cure for anal prolapse (the mind boggles).

The practice of using the electric discharge of this type of fish for clinical reasons continued until about the mid 1800s with ever increasing applications being found. The development of man-made electricity from electrostatic generators eventually took over from the natural source of electricity from fish. Also with the development of the Leyden jar (an early capacitor) it was found that stronger electrical shocks could be obtained.

Perhaps an unexpected contributor in this transformative time is the Rev. John Wesley (1702-1791), better known maybe as the founder of the Methodist Church movement. Part of his mission was to help the poor and sick people of London. In the UK at this time physician's bills were unaffordable by the poor, Wesley sought to bring cheap medical treatment to the poor and often found himself at odds with the medical profession. Not only did Wesley experiment with electricity and documented for what ailments and conditions he found it useful, he also took as much care over investigating various other medicinal and herbal treatments.

He wrote several medical books in which he extolled the virtues of electricity as a cure.

By 1768 the Middlesex hospital in London was the first to have installed an electrical shock machine; many other hospitals followed this lead over the next decade. It seems almost every medical practitioner was using electricity and the diseases, illnesses, conditions etc curable or treatable by this means were unlimited. Pretty soon some very questionable cures were being offered by frauds and fakes, and over the years there have been many. One notable early quack practitioner was James Graham who in 1780 was offering a night's sleep for £50 in his electric "celestial bed" to promote fertility.

For over 100 years electricity was dispensed liberally for virtually everything presented to the doctor and of course there was also an ever increasing number of quack's. These factors contributed heavily to its decline in the early 1900s, electricity had fallen out of fashion and new ideas were not viewed with very high regard in main stream science. It was not until about the 1960s that electricity in medical circles began to make a comeback as being an effective form of pain relief, and its ability to activate muscles.

That provides a very brief history of electrotherapy; there are many gaps and considerably more developments than space here permits. For anyone interested in its fascinating past we would direct you to the website of Dr Gordon Gadsby <http://freespace.virgin.net/joseph.gadsby/>. You will find a lot of useful information on electrotherapy along with a very detailed account of its history, especially concerning Rev. John Wesley.

CLINICAL ELECTROTHERAPY TODAY

The term electrotherapy covers the application of just about the full spectrum of electricity and magnetism from direct currents, through electromagnetic radiation right up to light waves, stopping short of ionising radiation. Electric currents of all descriptions, along with electromagnetic waves, ultrasound, infra red and UV phototherapy as well as lasers, are all common place and in regular clinical use for eliciting thermal and non-thermal effects in the

BACKGROUND

This work is inspired by the writings of Stan Hood in the December 2003 issue of *EPE*. Stan provided a very brief overview of many areas which are not widely accepted in main stream science and touched on a few areas that are. The previous article did not cover the impact of electrotherapy in clinical practice, nor the world-wide research of this technology in mainstream science. Therefore the aim of this article is to complement Stan's, to educate and provide interest in an exciting branch of electronics.

The author has worked professionally for a number of years as a medical electronics engineer and is currently employed as part of a team of doctors and scientists researching movement and movement disorders. He has also had more general experience in other aspects of electronics in medicine as well as holding an interest in this area outside of work.

body for an extremely wide variety of conditions and dysfunctions, including wound healing and, of course, pain relief.

Electrotherapy in clinical use can be regarded as another form of medicine, dispensed on prescription for a particular diagnosis or ailment. Just like medicines there is often a range of options available to the doctor. Not all will be effective for a particular case and patient. Electrotherapy is seen as another treatment option, which may not be the first or preferred choice. You are likely to see electrotherapy techniques in use in some hospitals more than others and in certain departments rather than others.

As an example; for pain management there are various options for treatment using electrical stimulation techniques and equipment. Heat inducing apparatus that employs shortwave or microwave radiation (diathermy apparatus) might be used in pain management. So might infrared sources, ultrasound or lasers be used for treating pain. Also there is a considerable variety of non-electrical treatment options available.

PHOTOTHERAPY

Phototherapy is a very effective treatment for the common disorder of neonatal hyperbilirubinaemia or newborn jaundice, a yellowish appearance of the skin and whites of the eyes. It is due to immaturity of the liver which causes an increased level of bilirubin in the blood. By exposing the baby to blue light (400 to 550nm) the bilirubin is broken down and excreted. Typically special fluorescent lights that emit in the blue part of the spectrum are placed above the baby (eyes are covered for protection) for a controlled period of time.

Phototherapy is also used regularly to treat a variety of skin conditions such as psoriasis and eczema. Ultra-violet light UVA (320 to 400nm) is delivered to the body in whole body cubicles or bed/canopy arrangement like those encountered in tanning salons for a set period of time. Depending on the condition being treated, often the exposure is made in conjunction with photochemicals applied topically to the skin or as ingested pharmaceuticals to improve the outcome.

There are dangers and risks associated with UV exposure; skin damage, skin aging, skin cancer and eye damage – so care must be taken to limit these effects. UV exposure also has some beneficial effects in thickening the skin and producing vitamin D.

Like all lamps their output diminishes with age, meaning longer exposure times and/or ineffective treatment. The intensity must be regularly monitored to ensure the correct dosage is delivered. This is especially important with new lamps because of the risk of an overdose, which could cause skin damage. UV phototherapy has also been used in wound healing although it is not yet a popular or recommended form of treatment in clinical practice in the UK.

Phototherapy using pulsating l.e.d.s with peak spectral output at 645nm has been used to treat migraine and PMS. A mask over the eyes blocks out all light. A pair of l.e.d.s are fitted to the mask, one on the left, the other on the right. A control box permits intensity and frequency to be adjusted in the range 10mcd to 45mcd and 0.5Hz to 50Hz respectively; a timer limits treatment time to a maximum of 15 minutes. The l.e.d.s flash alternately with a 50% duty cycle. Forty-four per cent of migraine sufferers that took part in the study (not a rigorous scientific study) claimed some benefit. Considerably more women with PMS claimed benefit. For further details see <http://www.lightmask.com/science.htm>.

Note: If anyone considers trying this for themselves, there are dangers at certain frequencies of triggering an epileptic attack, especially in those with epilepsy. More detailed information should be sought and you should of course discuss the matter with your doctor before starting any self-treatment plan.

RADIO WAVES

Electromagnetic waves in the radio spectrum have a very long standing medical history and are in regular clinical use by physiotherapists, primarily to deliver heat deep to tissue within the body. Broadly speaking two bands are used, shortwave and microwave. The medical term for this type of treatment and apparatus is known as “diathermy”.

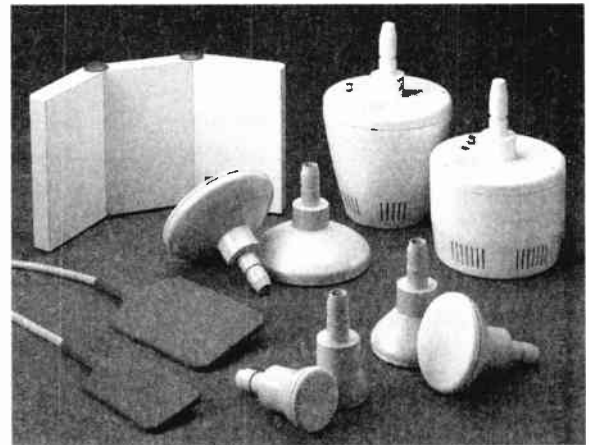
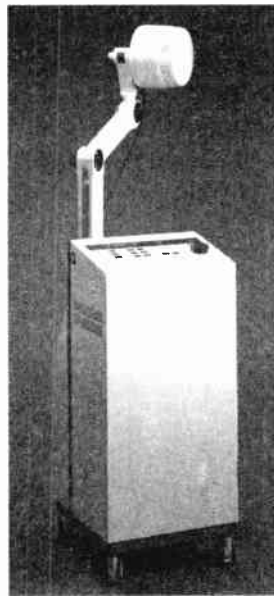


Fig.1 (left). A shortwave diathermy machine.

Fig.2 (above). A selection of accessory couplers (inductive and capacitive) for the diathermy machine. (Photos courtesy Mettler Electronics Corp.).

Shortwave diathermy operates in the range 10MHz to 100MHz and the RF energy (around 27MHz in UK) is either inductively coupled to the body by means of a coil or capacitively coupled by way of insulated electrode plates. The RF output may be continuous or pulsed. Typically the average power for high dosage is about 80W with peak pulse power as much as 1kW. The heat produced can be very effective for treating joint stiffness, relieving muscle pain and spasm, as well as reducing swelling. Fig.1 and Fig.2 (courtesy Mettler Electronics Corp. <http://www.mettler-electronics.com/>) shows an Auto*Therm 395 diathermy set with a selection of accessory couplers (inductive and capacitive). This particular model provides continuous or pulsed output up to 400W peak.

Microwave diathermy operates at much higher frequencies, up to 300GHz (UK has standardised on 2.45GHz). Because of the much shorter wavelengths, heat penetration into the body is less than that from shortwave equipment. Microwave energy is absorbed more by structures with a high water content (blood vessels, muscle, skin, internal organs but not fat). The energy is delivered to the body by means of “directors” (antennas).

ULTRASOUND

In therapeutic clinical terms ultrasound (US) covers the range of frequencies between 1MHz to 3MHz (diagnostic US extends to 20MHz or beyond). Sometimes low frequency ultrasound (~44kHz) is used. Principally, US is used for wound healing and has been in use for this purpose for a number of years. A UK survey in 1985 showed 20% of all NHS physiotherapy treatments involved US; this figure rose to 54% in private treatments (Haar G., Dyson M., Oakley E. M., *The use of ultrasound by physiotherapists in Britain, 1985, Ultrasound Med Biol.* 1987 Oct;13(10): 659-63).

Both thermal effects and non-thermal effects are utilised. An advantage of US thermal effects is that the depth of effective penetration in soft tissue can be controlled easily by altering the frequency (~4mm at 3MHz, ~11mm at 1MHz) see Fig.3 (courtesy of Mettler Electronics Corp).

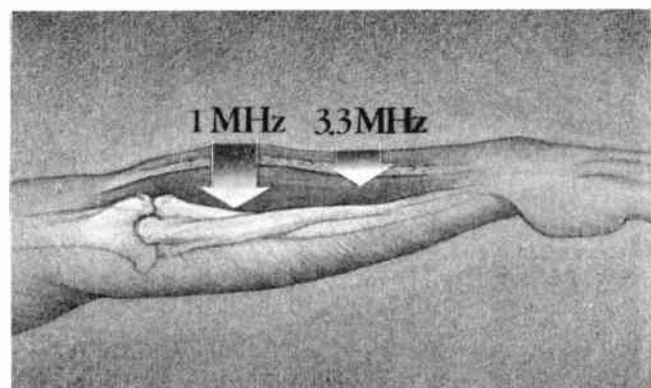


Fig.3. Ultrasound penetration at different frequencies. (Courtesy Mettler Electronics Corp.).

A sophisticated therapeutic ultrasound system 'Sonicator 730' is shown in Fig.4 (courtesy of Mettler Electronics Corp). It is microprocessor controlled and has interchangeable applicator heads. Membrane key pads and digital displays allow mode and timing selection and the device includes a feature to warn of poor patient contact. Like all US devices, the output transducer is formed from piezo-electric elements.

SIMPLISTIC VIEW OF WOUND HEALING

There are three phases of tissue repair; inflammation, proliferation and remodelling. Inflammation is characterised by the formation of a clot; this serves as a temporary seal. Clotting also releases many active substances known as "wound factors" that are used in subsequent phases and also "cleaner" agents that break down and dispose of tissue debris, foreign matter and bacteria. The proliferation phase is where deposits of new tissue(s) are formed and new skin layer is created; the process can be monitored by observing the decrease in wound size. The last phase, remodelling, takes place over months or years. The wound has fully healed, but we are left with a scar.

EFFECTS OF ULTRASOUND ON WOUND HEALING

Ultrasound can modulate the chemical processes of the inflammatory phase in various ways that accelerate tissue repair. A single US treatment, if given early enough after injury (early inflammatory period), can be very effective. There is also evidence that wound contraction can be accelerated by the application of US during the proliferation phase. Commencing treatment at the early inflammatory phase and continuing treatment three times a week for two weeks has been shown to have a beneficial effect on scar formation.

An interesting recent development using ultrasound concerns delivering drugs into the body. Ultrasound has been shown to be able to "push" certain drugs through the skin into the body; this process is known as "phonophoresis". More research is needed to clarify parameters and limitations. For further detail on this application see <http://www.eng.utah.edu/~holzer/ultrasound.htm>.

Whilst on the subject of vibrating waves, there is the allegedly true story concerning Tesla's vibrating platform and his intrigued friend Mark Twain who overdosed on it and discovered its power as a laxative, apparently an effect known to many of the laboratory staff. <http://www.nuc.berkeley.edu/dept/Courses/E-24/E-24Projects/Krumme1.pdf>. It is claimed that very low frequency sound and vibrations in the range 10-5Hz to 16Hz cause an urge to defecate. <http://www.rhfweb.com/hweb/shared2/Newrad.html>. Maybe someone would like to design a project based on this principle to relieve constipation. Annually in the UK some 10 million prescriptions are written for laxatives. If anyone is interested in other physiological effects of infrasound or infrasonics, then there is a range of material on the web, including "death rays" from giant whistles.

ELECTRICAL CURRENTS IN CLINICAL THERAPY

Electrotherapy has been used clinically for a few centuries for numerous and countless conditions, diseases etc. Current modern day regular practice and application can be broadly classified into muscular control, pain relief, and neuromodulation. Wound healing is a relatively new application of electric current and is not in widespread practice here in the UK.

Electric currents for pain relief have been covered in *EPE* in the past. The *Simple Dual Output TENS Unit* constructional project in the March '97 issue covered in depth the theory or principle(s) by which it is claimed to work, at least by what is currently understood in scientific circles. Therefore the subject will not be covered here.

Many electrical stimulators for whatever function are essentially the same – a repetitive rectangular pulse generator that switches a high-voltage stage on and off. The difference perhaps is the frequency of repetition, pulse width and amplitude which is usually a constant current or constant voltage output. Other refinements are frequently added such as "ramp-up" – "ramp-down" that



Fig.4. Therapeutic ultrasound set. (Courtesy Mettler Electronics Corp.)

slowly increases and decreases the amplitude to make the device's use more comfortable. Often a timer will also be incorporated to deliver the stimulation for a set period of time.

Electrical stimulators are often used for muscle strengthening in conjunction with some form of biofeedback, for example in toning up pelvic floor muscles for some forms of incontinence. They are also used for other muscle toning. The sports industry uses them for this purpose.

Anyone reading this who is overweight might be tempted to try such a device to aid slimming; they are commonly advertised as muscle toning devices. This to a large extent is a myth. Yes they can and do tone muscles but fat is a poor conductor of electricity, so to be effective in obese people the intensity would need to be so high that it would be a painful experience and people that have tried it discontinue with the program very rapidly.

In summarising the general state of electrical stimulators, it is fair to say that there is an immense variety of devices producing different output waveforms and patterns. There is also just as much variety, if not more, in the manner in which they are used. One may not be surprised therefore that for a particular form of electro-stimulation there are advocates and adversaries. Certainly further controlled and well documented studies are needed to separate the wheat from the chaff.

FUNCTIONAL ELECTRICAL STIMULATION

Functional electrical stimulation (FES) can play a significant role in patients with spinal cord injury (SCI) and may be the only way for some of exercising muscles artificially. Such exercise helps prevent muscle wastage and pressure sores and can even assist in whole-body exercise plans, for example aiding a paraplegic or quadriplegic to ride a trike, either in exercise mode or out and about. See <http://fesnet.eng.gla.ac.uk/CRE/overview5.html> and <http://www.mpi-magdeburg.mpg.de/people/negaard/HunSchNeg02.pdf> for further information.

A "Windcheater" tricycle is shown in Fig.5, courtesy of Tim Perkins UCLH. (T. A. Perkins, N. de N. Donaldson, R. Fitzwater, G. F. Phillips, D. E. Wood, *Leg Powered Paraplegic Cycling System Using Surface Functional Electrical Stimulation, Proceedings of the 7th Vienna International Workshop on Functional Electrical Stimulation*, Vienna, Sept 12-15, 2001, ISBN 3-900928-05-3, Pages 36-39, Fig.1). Research and development continues on the trike.

More often than not the electrical output of a stimulator is applied via electrodes to the surface of the skin (transcutaneous). This, as mentioned above, can cause some discomfort or even pain. There may well be other effects also. In clinical settings

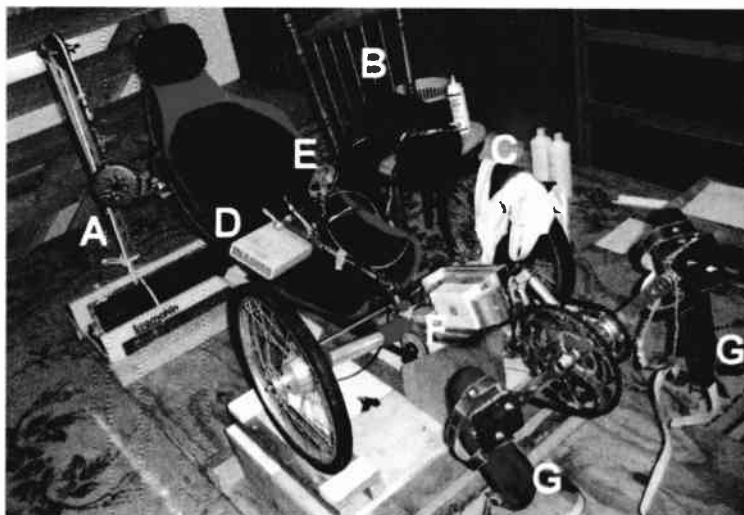


Fig.5. Windcheater functional electrical stimulation tricycle – A: Trainer. B: Electrode shorts. C: Tights to retain cables and electrodes. D: Stimulator. E: Throttle and switches. F: Shaft encoder. G: foot-plates. (Courtesy Tim Perkins, UCLH.)

sometimes the electrical signal is applied through the skin (percutaneous) by means of needle electrodes and also on occasions (heart pacemaker for example) a package and electrodes are surgically implanted to the body.

BIONS

An up and coming development is that which has been termed "BIONS". BIONS are microminiaturized electro-stimulators that are inserted by way of a large bore needle directly into a muscle. The device measures about 2mm diameter by 15mm long. Power and commands are sent to it by means of an external radio signal from a coil. See <http://www.vard.org/jour/02/39/3/sup/Loeb.htm>. These devices are currently undergoing clinical trials in aiding people recovering movement after a stroke, see <http://www.techtv.com/news/scitech/story/0,24195,3383097,00.html>. A second generation of BIONS is under development that will also transmit data via a radio telemetry link out of the body to some control equipment that can be used in a feedback control loop.

One issue that these devices may be able to address is that of giving fine control over a particular muscle. A muscle is made up of smaller muscle units; our normal nerve signals fire up only the units of a muscle needed for a particular task. With current day electro-stimulation technology we invariably fire up all the units simultaneously; it is difficult to get a fine graded response. By using much smaller and more localised stimulators, implanted directly at strategic points in a muscle, it might be possible to obtain a finer response.

NEUROMODULATION

Electrical stimulators are used effectively to modulate the impulses travelling along the nerve fibres to effect muscular control. A typical example is an aid for continence. An electrode is surgically wrapped around a nerve exiting the lower spinal column and an implanted electrical stimulator controls the current which travels along the nerve to the target muscle or muscle groups. Research is also in progress with less invasive methods of neuro-modulation such as percutaneous and transcutaneous application in various regions such as the tibial nerve in the leg, which has been reported as having a beneficial effect in control of continence.

Neuro-implants are also successfully used for pain control. Like all treatments these devices are not without complications of surgery and side effects, many unwanted. A very desirable side-effect has been noted by some and commercial exploitation for an "orgasm generator" is being considered. See <http://www.wired.com/news/technology/0,1282,41682,00.html> for more detail.

DEEP BRAIN STIMULATION (DBS)

Several years ago surgeons were removing specific parts of the brain to treat some cases of Parkinson's Disease. They located the precise region to excise using an electrical stimulator and an electrode slowly inserted to deep within the brain. Once the tremor had stopped, they knew they had identified the target region and they removed it. Someone had the brilliant idea that perhaps excision of part of the brain wasn't necessary; it appeared that electrical stimulation would somehow counteract the symptoms of Parkinson's Disease. Further research took place and the result is what is called DBS.

In some ways DBS is to the brain what a "pacemaker" is to the heart. The pacemaker is an implanted device that controls the heart muscle's electrical activity by means of connected electrodes. Note that Charles Kite first used electricity to "jump start" the heart (defibrillation) in 1788, see <http://www.thebakken.org/artifacts/Kite-Charles.htm>, he received an inscribed medal for his electrical resuscitations, the translation reads "*Possibly a little spark may yet lie hid*". Not of significant electrical content, but in part interesting reading is an overview of resuscitation. http://www.aap.org/nrp/DOCS/historical_overview_nrp.doc. It mentions a novel way of smoking, no longer practiced – medically (if it were a social requirement, then I'm sure the number of smokers would be reduced). This document also shows the colourful developmental path resuscitation has taken over history, with some quaint ideas and what is now widespread practice starting off very slowly or not widely accepted, in some respects similar to certain notions and practices in electrotherapy.

In DBS a similar sized and implanted package in the chest cavity is wired internally, by a process called tunnelling, to electrodes that have been implanted to deep within the brain. The DBS stimulator modulates neural activity in a certain part of the brain. As the brain comprises two hemispheres (left and right), often two

sets of stimulators and electrodes are installed (bilateral stimulation). Fig.6 depicts a Kinetra® implantable pulse generator (IPG) that allows independent dual channel stimulation to both sides of the brain (except frequency).

Reproduced with kind permission of Medtronic Inc.

In Fig.6 you will see implanted in the chest the dual-channel stimulator (pulse generator) package with wires under the skin leading up the neck to the top of the head and connected to two electrode sets that have been inserted deep within the brain.

The region frequently targeted is called the Sub-Thalamic Nucleus (STN) and has been found very effective in treatment of some cases of Parkinson's Disease as well as other tremor based disorders including dystonia. There are other areas of the brain that have also been found to be effective targets. Not all patients are eligible on medical grounds for this form of therapy, but it is very effective and an utterly amazing transformation takes place when stimulation is switched on. To see some video footage visit the Medtronic website http://www.medtronic.com/activa/physician/video_downloads.html.

Technically the pulse generator delivers a pulse about 100µs wide and 3V amplitude at a frequency of just over 100Hz. These parameters can be altered and the pulse generator can be turned on and off via a radio telemetry link. The implant is battery powered with a life expectancy of five years.

If anyone wants to read more about this topic, there is plenty of material available on the internet, for example <http://www.southshorenurologic.com/clinical/move-dis/dbis-overview.html>.

There are also other conditions that are being researched that appear to respond to this form of electrical stimulation.

GALVANIC STIMULATION

Galvanic, d.c. or pulsed d.c. stimulation is used for several therapeutic purposes and may be high or low voltage. Areas of application include pain relief, drug delivery and wound healing.

Many drugs have an electric (ionic) charge. If placed on electrodes connected to the body and a current passed between the electrodes, then the substance can be transported through the skin into the body; the process is called iontophoresis. Crudely speaking it is rather like the process of electroplating where certain metals in an electrolyte can be deposited on other conductive objects by the passage of an electric current. See <http://physicaltherapy.about.com/gi/dynamic/offsite.htm?site=http%3A%2F%2Fwww.life-tech.com%2Fpmp%2Fwhatis.html>.

It is also possible to extract small quantities of substances out of the body, a process called strangely enough "reverse iontophoresis". This extraction process is used commercially for glucose monitoring of diabetics in a product called the "Glucowatch", a wristwatch-sized device that uses electrical current to drive out a small sample of the extra cellular fluid (ECF). This fluid is present in our bodies surrounding the cells, it is the fluid found in blisters. From the ECF the level of glucose in the body can be determined by the machine and the results displayed. Although not therapy, it is an application of electric currents in medicine and one that makes a painful finger pricking exercise non-invasive. See <http://care.diabetesjournals.org/cgi/content/full/24/5/881> for more detail on the Glucowatch.

WOUND HEALING

Wound healing using electric currents is an area that appears to be gaining popularity. The latest edition of Clayton's

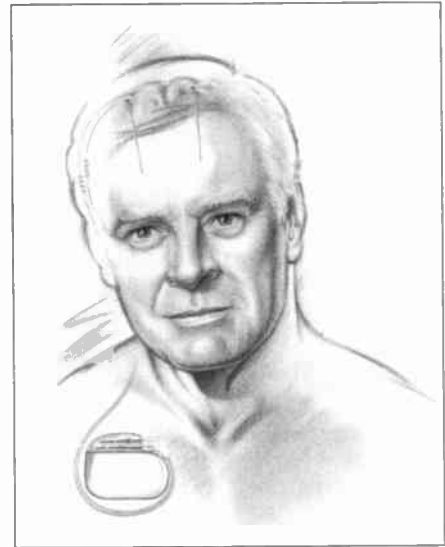


Fig.6. Dual-channel deep brain stimulation using the Kinetra implantable pulse generator (IPG). (Courtesy Medtronic Inc.)

Electrotherapy (now called *Electrotherapy: Evidence-based practice*, edited by Sheila Kitchen, published 2002, ISBN 0 443 07216 7) includes a good deal on wound healing by electrical currents. If you want to learn more about therapeutic clinical applications across the broad spectrum of electricity from d.c. to light waves this book deals with theory and effects of a number of modalities in current clinical practice and is aimed primarily at student physiotherapists but covers very well the electrical basis. It is quite technical and deep.

Some people have been involved with research into electromagnetic radiations for bone healing and found a degree of success in improving healing times of certain fractures. In terms of galvanic currents there appear to be many options, low voltage, high voltage, simple waveform, complex waveform, all claiming to offer improvements in soft and hard (bone) tissue wound healing. Perhaps, based on Dr Beker's work, setting up an electric field enhances healing times by promoting increased blood flow and for other reasons. It is interesting to note that electricity in the form of charged gold leaf was first used to treat wounds (prevention of smallpox scars) over 300 years ago.

GALVANIC VESTIBULAR STIMULATION (GVS)

The passage of a small direct current between electrodes placed just behind the ears can influence the vestibular apparatus, the principle organ that gives us a sense of balance and is often disrupted in motion sickness, and can cause the body to sway or lean to one side. The direction can be changed by reversing the current.

At the moment interest seems to be focused on establishing the effect and control on posture and balance. There might at a later date be some therapeutic benefit to this research.

CRANIAL ELECTRICAL STIMULATION (CES)

Time varying d.c. or a.c. at low amperage (microcurrents) is applied via electrodes typically clipped to the ear lobes or fixed just behind the ears to provide, it is claimed, relaxation and relief from depression, anxiety, stress and insomnia. There are some claims that also mental alertness and performance can be improved using this technique.

The basic idea is that currents in the microamp range with frequencies of certain brainwaves can be used to promote production of specific neurotransmitters (chemicals) in the brain. Depending on the frequency, and maybe waveform, specific effects may be induced. For further detail on the whole subject of "microcurrents" see http://alpha-stim.com/Information/Products/Educational/CES_Intro/Old_CES_Intro/old_ces_intro.html.

MAGNETIC STIMULATION

In the ever increasing quest for less invasive and non-invasive clinical methods and procedures, the body's magnetic properties can and have been exploited to provide a "non-contact" means of stimulation. The tissues of the body are not particularly magnetic and therefore a vast amount of energy is required to elicit an effect. Current commercial equipment can generate in a brief period of time enough energy to lift a person weighing 50kg, one metre. Essentially this type of apparatus charges a bank of capacitors to a high voltage and then rapidly discharges them into a coil which generates an electromagnetic pulse.

Because of practical limitations on re-charging, the achievable repetition rate is very slow using a single magnetic stimulator. Where faster repetition rates are needed, then several stimulators are coupled to the same coil and fired in succession. As the power generated is very high, care must be taken to avoid overheating.

A typical selection of magnetic stimulators and coils is shown in Fig.7. This photograph, reproduced with thanks to Peter Assleman, Institute of Neurology, is a small example of apparatus used in one of the research labs. Several different types of magnetic stimulator can be seen on the rack and two typical coils rest on the pillow. At the back you can see a selection of coils. Note the thickness of the cable to the coils, required to reduce heating effects of the very high currents. The coils are temperature monitored and if overheating occurs, the equipment automatically shuts down to prevent injury and damage.

By placing the coil over a neuromuscular junction, the interface between muscle and excitatory nerve, a muscle twitch can be elicited in response to a magnetic pulse from the coil. The coil can also be situated over the spinal column and muscles can be influenced

by magnetic stimulation of the nerve roots. It can also be sited over one hemisphere of the brain in the motor cortex region and indirect non-invasive stimulation of muscles can be made by stimulating the brain (trans-cranial magnetic stimulation or TMS). Note if the coil is placed over the visual cortex at the back of the head then flashes of light (phosphenes) can be seen in response to the stimulation.

The large coils used means the beam is not particularly focal and quite a large area gets excited by the stimulation pulse. Also some care and adjustment is needed to ensure the desired structure is stimulated. Apart from muscle control, magnetic stimulation has also been used to treat other disorders such as depression. It provides the researcher a means to non-invasively stimulate the brain, which is good for volunteers knowing that they don't need to have their head cut open, whilst helping to advance medical science. For anyone wishing to find out more a good starting point is <http://www.biomag.hus.fi/tms/>.

TEMPORAL LOBE EPILEPSY (TLE)

From the extensive research of Dr Michael Persinger on TLE and religious and ecstatic experiences it has been observed that weak electromagnetic stimulation of the front part of the brain can cause spiritual responses in some people. Persinger uses a special helmet in which several coils are placed and these are excited in specific sequence in an attempt to elicit a response and has found a variety of responses can be obtained from physical type arousal of emotions through to states of religious ecstasy and also the feelings of hauntings. He has also found that similar responses can be obtained in some from long exposure to electronic equipment such as computers.

The UK BBC TV *Horizon* science series carried a program on his work in 2003 <http://www.bbc.co.uk/science/horizon/2003/godonbrainqa.shtml>. More detail on the topic can be found at <http://www.angelfire.com/tx5/randysresume/termpaper.html>.

ELECTRODIAGNOSIS

In the main the preceding information only addresses therapeutic applications of electricity. There is also a great deal of interest in main stream science on diagnostic techniques using the body's electricity and related properties.

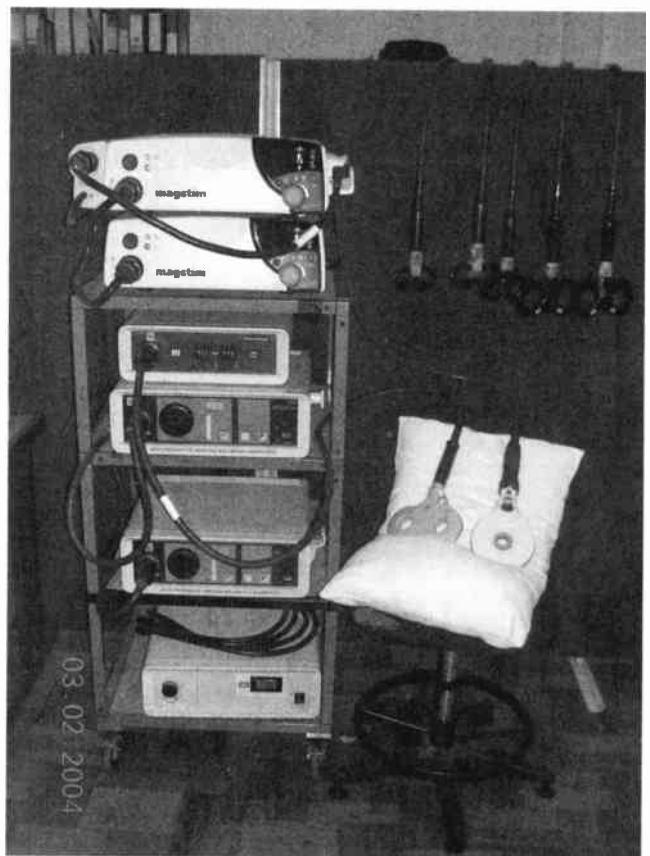


Fig.7. A rack of typical magnetic stimulators and coils. The coils are temperature monitored and if overheating occurs, the equipment automatically shuts down. (Photo courtesy of Peter Assleman, Institute of Neurology.)

For numerous decades measurement of electrical activity of the heart (electrocardiogram e.c.g.), that of the brain (electroencephalogram e.e.g.) and the electrical activity associated with muscle movement (electromyogram e.m.g.) have formed regular and routine clinical diagnostic tools for certain disorders. Several of the stimulations described above are used in diagnosis to attempt to evoke a response from the body that can be electronically measured.

BIO-IMPEDANCE ANALYSIS AND ELECTRICAL IMPEDANCE TOMOGRAPHY

Disease and illness is known to alter the electrical impedance of tissue and other biological substances and there is investigative work trying to establish the usefulness of this technique for diagnostic purposes. A novel application of this is the electronic bra to detect breast cancer <http://www.bra-n-bras.com/8592-electronic-bra.html>. Impedance analysis is also the principle used in the devices available in the high street shops as electronic body fat analysers, fatty and non-fatty tissue have different impedances at different frequencies.

An extension of bio-impedance techniques is electro-impedance tomography or EIT for short. This is essentially an impedance imaging system that uses electrical currents delivered between multiple electrodes. A computer running a reconstruction algorithm creates a visual image, see <http://www.geocities.com/CapeCanaveral/9710/html/eit.html> as just one sample of some of the work undertaken, there are many more.

KIRLIAN PHOTOGRAPHY

The work of Kirlian is a curiosity which is said to produce photographs of the human aura or life force. There is certainly an effect. The Kirlian effect stems from corona discharge, much the same as the infamous "St. Elmo's fire" witnessed by mariners since the dawn of time. A high voltage charge say during or just after a thunderstorm on an object like a ship's mast under the right conditions gives rise to an eerie white/bluish glow. A good short synopsis and history can be found at <http://lkm.fri.uni-lj.si/xaigor/eng/kirlian.htm>.

In Kirlian photography, the high voltage is electronically generated by an amplified oscillator that drives a very high voltage transformer, typically a car ignition coil, TV line output transformer (LOPT) or a transformer for a neon sign is used.

Kirlian coupled the high voltage to what is effectively a capacitive circuit that included the object to be studied and a photographic plate in series. When energised the high voltage breaks down (ionises) the surrounding air and maybe the dielectric. The result is a weak glow that can be detected by the photographic paper. There is some debate if detection is a result of light by the photosensitive paper or by direct electro-chemical action to the photographic emulsion(s) on the paper. Corona discharge is predominantly in the ultraviolet (UV) region for which our eyes and photographic papers are not particularly sensitive. Such "contact" means of producing "Kirlian photographs", especially using colour film, are prone to process errors and distortions, artefacts that over the years have fuelled the debate on the claims made over this effect relating to "human energy fields". For further information see http://www.geocities.com/lemagicien_2000/kfpage/kf.html.

Non-contact methods that use cameras to photograph this phenomenon have been developed; these eliminate many of the artefacts of the "in-contact" method. Usually some transparent electrode arrangement is used. Fashioned from two glass or clear acrylic sheets a slim-line sealed tank is formed, rather like a double-glazed window. The gap is filled with conductive liquid (water) and an inserted wire electrode that connects to the outside world. The high voltage generator connects to this external terminal and to the object of interest which then touches one side of the transparent plate. The camera is used to take a picture from the other side of the plate.

Kirlian photography appears to be regaining a much wider appeal under the more general title of gas discharge visualisation (GDV) or electrophotography. CCDs have been used to produce videos of this phenomenon. See <http://www.gdvusa.org/index.html> for more information.

GALVANIC SKIN RESISTANCE (GSR)

The "psycho-galvanometer", is a device popularised by Carl Gustav Jung, back in 1906, for use in psychoanalysis. Today we would say this device measures the galvanic skin resistance (GSR). It formed a significant role in the development of the polygraph or lie detector. Basically the principle by which this works can be

AUTHOR'S SUMMARY

I began this journey by exploring some of the early history of electrotherapy, looking at the clinical uses of natural electricity and how it has developed over the centuries. There has over its history been many strange and sometimes "quack" ideas and devices produced. I have endeavoured to stay away from the fringe of science and focus on aspects that are well accepted in mainstream science and also have tried to show that the level, interest and application is very well accepted within the main core of medical science with many branches in regular clinical practice as a treatment option. I have ended up looking at a few current areas of scientific exploration and some considered to be on the fringe in diagnostic applications.

described as a psychological state giving rise to a physiological response – in this case a change in resistance of the skin. With what amounts to little more than an ohmmeter (usually a bridge circuit is used and "peak" detectors and other refinements are added) changes in skin resistance can be detected. Much more information is available on the web, especially concerning the interpretation.

Back in the 70s Christian Scientologists used this principle and a similar meter for "spiritual divination" and a healing process they called "clearing". Much the same techniques are still used today but by a much wider audience, and without religion being involved for dealing with psychological issues and in promoting spiritual growth by either a practitioner or as some form of self-help/development program. For further information see <http://www.trans4mind.com/psychotechnics/gsr.html>.

THE AURAMETER

Side-tracking away from GSR for the moment. Professor Valerie Hunt of UCLA noticed during studies of electrical muscle activity there was a high frequency noise. For more than 20 years she has studied this phenomenon and has developed a system for detecting these signals. See <http://www.spiritofmaat.com/archive/nov1/vh.htm> for more information. Dr Hunt believes these signals relate to a non-physical energy field surrounding the body and has related these signals to the colours of the human aurora as seen by "sensitives". Essentially she performs a spectrum analysis of the high frequency noise signal; the results show non-random peaks which over the years she has classified.

SPECTRUM ANALYSIS OF GSR SIGNAL

Similar effects by spectrum analysis have been observed in the GSR response, see <http://www.trans4mind.com/psychotechnics/energyfield.html>. So, anyone up for the challenge of designing a safe project to experiment with this? Not so long ago in *EPE* (Feb 2002) there was a PIC based spectrum analyser and it is not too difficult to design a bridge circuit to acquire the GSR signal. There have in the past been published designs in some electronics magazines, maybe it's time for a new design.

Although man's interest in electrotherapy has been around for millennia, very little of how it works and what works when is understood. We know certain things work some of the time for some people. We should also realise that our bodies are essentially electrochemical and therefore expect electricity to influence it. A very large industry has grown up focusing on chemical (pharmaceutical) effects and remedies, nowadays there are still many "tweaks" to medicines to improve their potencies or reduce side-effects and even new chemical options appear. Why should there not be a similar multitude of electrical treatments?

On the highly controversial issue of harmful effects of electromagnetic radiation, it is possible that there could be some ill-effects. Many medicines taken in the right amount for the right condition are highly effective. If they are overdosed on there could be serious and even fatal consequences, some have an accumulative effect. Maybe the same is true of EM radiation. We are just scratching the surface on the very wide range of electrotherapy topics, those with a strong scientific background and those with a less general acceptance by the scientific community.

Perhaps from dubious beginnings and false assumptions we are beginning to see that such things work, at least in modified form, and understand more what makes it work and its limitations. In some respects what was once, and maybe still is, considered fringe or pseudo-science is beginning to take a place in main stream science and become respected. Much more research is required to establish what techniques will be more useful as therapeutic and diagnostic tools. □

CRAFTY COOLING

TERRY de VAUX-BALBIRNIE

Make a drink can cooler and learn about Peltier and Seebeck effects at the same time!



MANY recent inventions depend on principles that were discovered years ago. Modern applications of well-established ideas may come about because a new need arises. At the same time, modern materials and techniques that allow devices to operate more efficiently or to be made more cheaply create commercial opportunities.

THAT'S COOL!

To give an example, many readers will have seen the small portable refrigerators that are now widely available. These may be advertised as "wine chillers" or being "large enough to hold four drink cans". There may be some confusion because they are often said to be suitable for either *cooling* or *heating* the contents!

These little fridges rely on the *Peltier Effect*. If you look through advertisements in *EPE*, or in the pages of electronic suppliers' catalogues, you will find Peltier modules for sale and one, or more, of these forms the basis of such a fridge. You may have seen similar devices used in sophisticated microprocessor coolers, in night

vision equipment or for cooling laser diodes. They are also found in certain medical and scientific instruments.

WATCHMAKER'S FINDING

Far from being new, the Peltier Effect was discovered long ago – in 1834 – by the French watchmaker, Jean Charles Athanase Peltier (1785 – 1845). The background to his discovery is that some years previously, Thomas Johann Seebeck (1770 – 1832) had demonstrated a phenomenon which we now know as the *Seebeck Effect*.

Seebeck had connected together three pieces of wire made from two different metals to provide a pair of junctions (see Fig. 1a). He heated one junction and found that a small current flowed when a circuit was completed (he showed this by a compass needle moving but the diagram shows a microammeter).



Peltier tried the converse effect. He found that when current was passed through a similar arrangement of wires, the temperature of one junction fell while that of the other rose (see Fig. 1b). Which one

heated up and which one cooled down depended on the direction of current flow.

Before looking at the Peltier Effect in more detail, it would help to look more closely at Seebeck's discovery.

The Seebeck Effect is easily demonstrated by twisting a piece of bare iron wire (say, thin garden wire) with two pieces of constantan wire in the manner shown in Fig. 1a and the photo below. Constantan wire (an alloy of copper and nickel) may be obtained from electronics suppliers and is used as a type of resistance wire. A microammeter may be used to measure the current. Alternatively, you could use a digital voltmeter because it is a *difference in voltage* between the free ends of the wires that causes the current to flow. When one junction is heated, current flows or a voltage is indicated. Even warming the junction between the fingers or placing it in warm water will be sufficient if the meter is sufficiently sensitive.

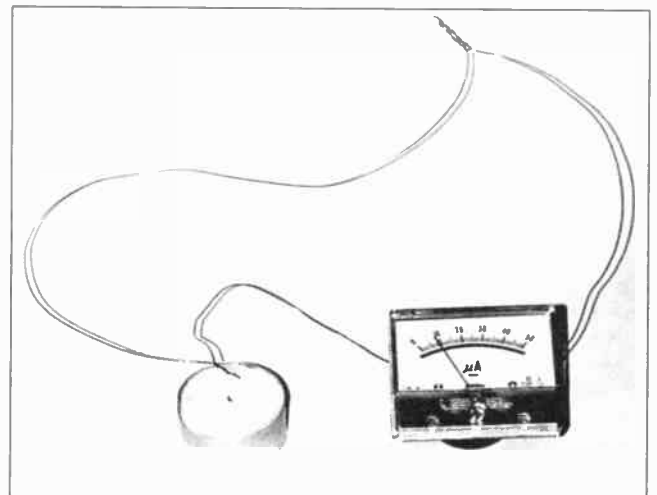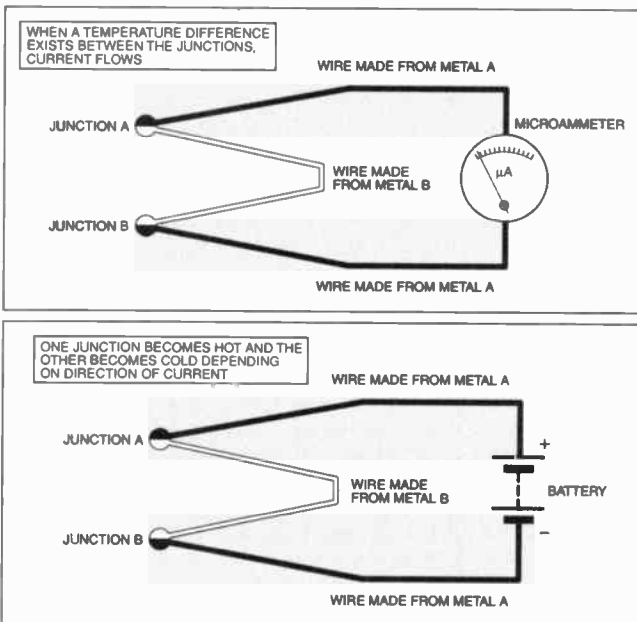This could not be explained during Seebeck's lifetime because the electron had yet to be discovered (in 1897 by the initial experiments of J. J. Thomson). We now



Demonstrating the Seebeck Effect with a candle, wire and meter. See also Fig. 1a above left.

Fig. 1b (left). The Peltier Effect, one junction becomes hot, the other cold.

know that the Seebeck Effect is a consequence of the different electron densities in the materials used. Dissimilar (unlike) metals have differing numbers of free electrons in a given volume and these wander around randomly inside the structure. The higher the temperature, the faster they move.

PARTY PROPULSION

If wires made from different conducting materials are connected together, there will be a tendency for electrons to move from the region of high to that of low density (see Fig.2). This is because they spread out. This situation is similar to a party where there are already too many people in a

high, so variations in the "cold" junction's temperature are insignificant. However, for accurate work, the "cold" junction will be maintained at a fixed temperature (by placing it in a thermostatically-controlled water bath, for example).

THERMOELECTRIC TABLE

A chart known as the Thermoelectric Table lists the chemical elements in thermoelectric EMF order. The further apart are the materials comprising the junctions, the greater will be the EMF. Table 1 shows some of the more common elements, in high to low EMF order.

Some alloys (mixtures of metals) or an alloy in combination with a single metal show more marked thermoelectric properties than elements alone. Constantan (an

Table 1. Thermoelectric Table

Silicon	Gold
Bismuth	Silver
Nickel	Aluminium
Cobalt	Zinc
Platinum	Tungsten
Copper	Cadmium
Manganese	Iron
Lead	Antimony
Tin	Germanium
Chromium	


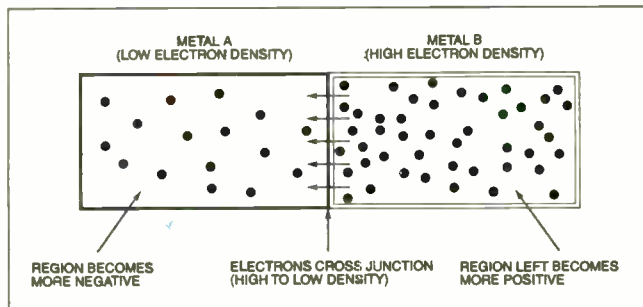


Fig.2 (left). The movement of electrons from a high density region to a low density one.

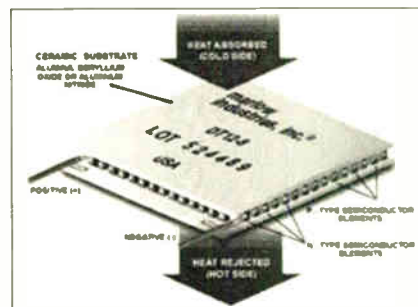(Right) Structure of a practical TEC (thermoelectric cooler). Courtesy Marlow Industries Inc.



room (a region of high people-density). They tend to wander into another place which is less crowded.

However, when electrons (which are negatively-charged particles) do this they tend to be drawn back by the region they came from and be repelled by the one they travel to. This is because the place from where negative charge has been removed will be left more positive and the one it travels to, more negative. The forces will rapidly balance and the process stops – just like the party, the place to where people go becomes just as bad as the room they left and overall movement stops.

There will, however, still be an equal to-and-fro trickle of people just as with the electrons. Fig.3 represents the situation shown in Fig.1a, but now in terms of electron density. Here, the left-hand side of Junction A becomes negative (to where some electrons have travelled) while the right-hand side becomes positive (where they have left). There is therefore a voltage across it, known as the *thermoelectric EMF* (electromotive force).

The same happens at Junction B, but here the left-hand side will be positive and the right-hand side negative. The voltages produced at the two junctions are equal and opposite so they cancel to give zero overall effect at the free ends of the wires.

ENERGETIC ELECTRONS

If one junction is heated, the electrons move faster and more easily cross the junction. This increases the voltage across it. There is now a voltage difference between the junctions and hence at the ends of the wires. This is the EMF that drives current through the microammeter or is indicated by the voltmeter in the experiment above.

The arrangement of wires shown in Fig.1a is called a thermocouple. This device is often used in industry for measuring a temperature so that it may be displayed on a remote meter. Sometimes it is good enough for one junction to remain at ambient temperature. This will be the case when the temperature of the "hot" junction is very

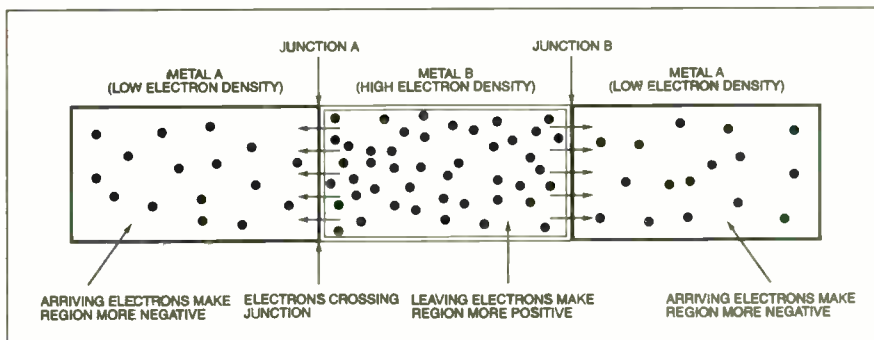


Fig.3. The effects of "arriving" and "leaving" electrons on region density.

You Will Need . . .

- Peltier Module – 36W 14V (nominal) 40mm square
- Aluminium beaker – 250ml 67mm internal diameter
- Heatsink (finned) – 1°C/W or better
- Fan(s) – 12V cooling fan (see text)
- Heatsink thermal transfer compound; plastic case; 5A connecting lead; 5A screw terminal block; strain-relief grommet; bubble-wrap (see text); nuts and bolts etc.



alloy of copper and nickel) in conjunction with iron gives a particularly high thermoelectric voltage, so wires made from these materials are often used to make practical thermocouples.

Antimony and bismuth have a very marked effect and have been widely used for scientific purposes. However, the highest thermoelectric voltages of all are obtained using semiconductor materials, whereby junctions are established between pieces of the *p*-type and *n*-type doped material.

PRACTICAL MODULES

Commercial Peltier modules are often called "thermoelectric coolers" (TECs). A typical unit has 127 junctions formed between *p*-type and *n*-type bismuth telluride (a semiconductor material which has been found to be particularly effective). The precise degree of doping is controlled at manufacture to maximise its thermoelectric properties. The junctions are soldered together in series and grouped so that the "cold" ones appear at one face and the

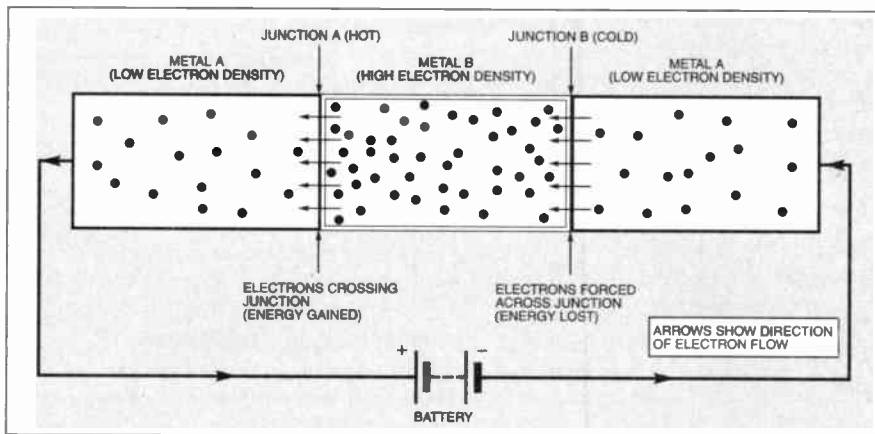


Fig.4. Peltier Effect. Movement of electrons from low density to high produces a cold junction, movement from high to low produces a hot junction.

CHILL OUT

Returning to the Peltier Effect and referring to Fig.4, the negative battery terminal will force electrons across Junction B in the direction right to left – that is, from a region of low density to one of high density. To do this against the natural repulsive force, they must do work and give up energy – they slow down and the junction becomes cold.

At Junction A, the electrons move from a region of high density to low density and acquire energy – they speed up and the junction becomes hot. The electrons then return to the positive terminal of the battery and start another trip.

Think of a roller coaster. When the car rises against the force of gravity, it gives up kinetic energy and slows down. On a downward slope, it increases its kinetic energy and speeds up.

Before reaching for your pieces of wire to try out the Peltier Effect, remember that current flowing through the resistance of any wire causes a rise in temperature (*Joule Heating*). This will dwarf the Peltier Effect if common materials are used. This is especially so because Joule Heating is proportional to the square of the current (doubling it multiplies the heating effect by four) whereas Peltier phenomena are proportional to the current alone.

Note that Joule Heating occurs whichever direction the current flows – it never causes a fall in temperature as does the Peltier Effect. Another important difference is that the Peltier Effect only takes place at junctions, whereas Joule Heating occurs throughout the entire circuit. If you were to use bismuth and antimony for the materials, the Peltier effect would be large enough to observe using simple equipment. However, this is not very practical and it is much easier and better to use a commercial device.

"hot" ones at the other. Which surface becomes hot and which ends up cold will depend on the direction of the current.

Although the junctions as connected electrically in series, they may be regarded as being connected thermally in parallel (to multiply the effect of one junction). The device is fitted with faceplates made of a ceramic material (an electrical insulator but a good thermal conductor). Short circuits are therefore avoided between the junctions and any external metalwork, while allowing the free flow of heat.

A TEC is just a type of heat pump. Its purpose is to transfer heat (thermal energy) from one face to the other. A conventional refrigerator is also a heat pump but uses the latent heat of evaporation (liquid to gas where heat is absorbed) and condensation (gas to liquid where heat is liberated) as the working medium. It becomes cold inside of the fridge cabinet but the fins outside become hot.

A TEC can develop a temperature difference of several tens of degrees Celsius. In fact, the cold face may fall well below 0°C if heat is removed efficiently from the hot one and the ambient temperature is not too high. Peltier devices are limited in their physical dimensions (at the moment to some 50mm square). The reason is thermal expansion. In operation, the cold side of the device will contract while the hot one will expand. This can be tolerated by the design up to a point. However, beyond a certain size internal stresses would destroy it. For greater power transfer, multiple units are therefore used.

EFFICIENCY

With a conventional machine, such as an electric motor, there is a definite notion of "power in" (electricity) being converted into "power out" in the form of work done. The ratio of power in to power out

expressed as a percentage then gives a measure of the efficiency – that is, how well the machine performs. With a Peltier device, its "goodness" is measured by comparing the electrical power entering with the power transferred between its faces.

A typical TEC might be described as 36 watts. This means that, working "flat out", it can transfer 36 watts or 36 joules of thermal energy per second. Suppose its maximum current and voltage ratings are 4.4A and 13.5V respectively. Since amps multiplied by volts gives watts, the power drawn from the supply will be almost 60 watts. The "goodness" of the device is therefore 36/60 or 60 percent. 40 percent of the incoming electrical energy is converted into heat by Joule Heating.

Due to its arrangement of many thermoelectric junctions, a Peltier module may also be used to generate a useful amount of electricity (using the Seebeck Effect) if its faces are subjected to a temperature difference. Such a system could be used to turn waste heat into electricity. In fact, a similar low-tech method has been in use for many years to make inexpensive generators. These use a large number of thermocouple junctions connected together in series and heated by an oil lamp or fire. They have been used in remote areas to charge batteries or to operate a small radio.

In deep space exploration, sunlight is insufficient to provide an adequate amount of electricity using solar panels. To overcome this problem, heat developed naturally by the radioactive isotope plutonium-238 is utilised. Into this is buried an arrangement of thermoelectric junctions. The electricity produced is sufficient to power the transmitting equipment that sends data back to the base station.

CONSIDERATIONS

Peltier modules are fairly expensive and easily damaged through misuse. However, if used correctly they are robust and reliable. Sure ways of ruining one are failing to remove heat effectively from the hot surface or passing a current greater than the rated value through it (both of which cause it to overheat). It will also be destroyed by putting it under mechanical stress.

The removal of heat is extremely important, so never connect a Peltier module as it stands to a supply to see if it works! You must use a substantial heatsink (possibly assisted by a fan) placed in good thermal contact with its hot side. The temperature here should rise as little as possible above that of the surroundings, but up to 15°C is acceptable.

BATTERY SUPPLY

A practical Peltier device needs a high current, low voltage supply. If this is derived from the mains, a substantial transformer and rectifier would be needed. Also, a high-value smoothing capacitor would be required because these devices work best with smooth d.c. – their ability to pump heat falls with any ripple present (although, in practice, up to 10% would be tolerated).

A cost-effective power supply which avoids these components would be a car battery (but check that the TEC is rated at 14V minimum). Remember, a well-charged "12V" car battery can develop considerably more than the nominal voltage and this must be allowed for.


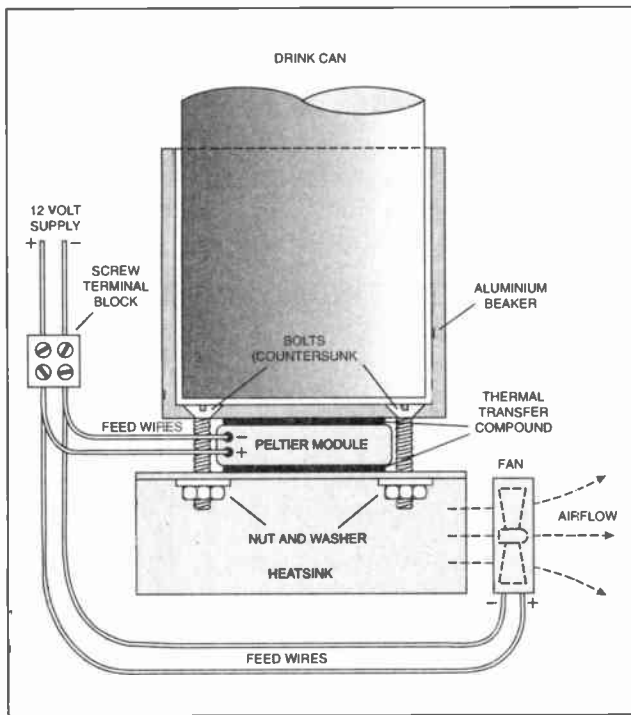


Fig.5. Experimental Drinks Cooler construction details.

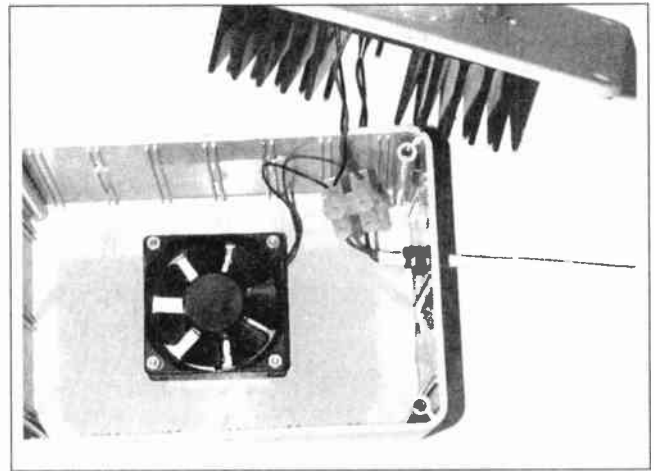

Cooling fan mounted in the base of the case and the finned heatsink on the rear of the lid.

If a Peltier module were to be connected to a supply developing a higher voltage than the rated value, a larger current than it was designed to carry would flow. Its pumping ability would be exceeded by Joule Heating and the device would heat up the system that it was supposed to cool. After that, it would probably be destroyed.

When a nominal 14V module is connected to a 12V supply, the current will be less than the rated value. Calculation shows that only about 26W will be available from a nominal 36W TEC and this will result in longer cooling times.

COOL IT YOURSELF!

We now show you a drink can cooling design you can construct for yourself, using a 12V car battery as a power source. It will be found handy for cooling a drink while in the car. A 40mm square 14V 36W (nominal) TEC was used in the prototype unit and was found to be adequate.

It is impossible to say with any accuracy how quickly it will cool the drink. This depends on the required final temperature, the ambient temperature, the efficiency of insulation and thermal contact, how well heat is removed from the heatsink and the supply voltage. To give an idea, the prototype provides adequate cooling in less than one hour.

However, unless you are desperate for a drink, the cooling time does not usually matter and the unit may just be left operating for as long as required. It is important for the cold side of the TEC to make efficient thermal contact with the can to be cooled. The better the coupling, the quicker the cooling will be. The specified 250ml aluminium beaker has an internal diameter of 67mm and provides a good fit for many drinks cans. It was found that some supermarket "own brand" cola cans gave a tighter, and therefore better, fit than some "famous make" ones.

By attaching the bottom surface of the beaker to the cold side of the Peltier device, a drink can placed in the beaker is cooled effectively. At the end of construction, insulation

("bubble-wrap") will be placed around the beaker so that cooling is confined as much as possible to the can and the drink inside it, rather than reducing the temperature of the surrounding air!

MOISTURE SEALED

It is best to choose a TEC which has been factory sealed against the entry of moisture. This is because the cold surface will make the temperature of the surrounding air fall below the dew point and condensation will form. Without sealing, water will enter the module and eventually damage it. An unsealed module would need to be protected by applying some flexible, waterproof material around the periphery.

Arranging for the TEC to be vertical would help because it would allow any condensation to drip off. However, for ease of construction, the device was placed horizontally in the prototype unit. It is vital to choose a heatsink that will remove heat from the hot surface of the TEC as well as possible. This should be rated at 1°C/watt (or better) and a small 12V fan, or fans, should be used to assist the removal of hot air. A suitable fan would be a 12V unit designed for cooling a microprocessor.

Referring to Fig.5, drill holes in the heatsink and beaker to allow the Peltier device to be sandwiched between them. These parts must make very good thermal contact with the TEC's faces and thermal transfer paste should be applied to the surfaces to assist the flow of heat. If the bottom of the beaker is not absolutely flat around the area of contact, it should be rubbed on a sheet of abrasive paper, which is itself placed on a flat surface, until it is. Similarly with the heatsink.

Countersink the fixing bolts so that the heads are flush with the inside surface of the beaker. **Important: when tightening the bolts, use only sufficient force to hold the module securely without slipping. Any more will destroy it.**

TESTING

Make up a connecting lead of 5A rating (or use a ready-made lead) having a cigar lighter plug on one end. This should be no longer than necessary to avoid an excessive voltage drop. Taking care over the polarity,

connect the other ends of the wires to the TEC and the fan using a two-section piece of 5A screw terminal block. The TEC will probably have its polarity marked (say, a red wire used to indicate the positive). If the fan is of the microprocessor type, only the red and black wires are used – the red one being connected to supply positive.

If there is a yellow wire, it should be cut off short and ignored – this would normally be connected to the computer motherboard to monitor the fan's performance. It will not be necessary to actually use the fan during short tests. Just leave it free but out of the way for the moment. Connect the supply and check that the "cold" side of the TEC (and hence the beaker) becomes cold. If it becomes hot, reverse the current. Also check operation of the fan. Allow the unit to operate for a minute or two but do not allow the heatsink to become hot.

BOXING UP

The finished assembly is housed in a plastic box (see photograph). This has a hole cut in the top a little larger than the can. The heatsink, and therefore the whole assembly, is bolted to the underside of the lid. Make a large hole in the base of the box and mount the fan over it on the inside (see photograph) making sure that, in operation, air will be extracted from the box rather than the opposite.

Drill a few holes in the sides of the box to allow air to enter and flow between the heatsink fins. Drill a hole in the side of the box for the connecting wire to pass through. Fit a rubber grommet and use a tight cable tie on the wire inside the box to provide strain relief (or use a strain relief bush). Leave a little slack in the wire inside the case.

Plastic blocks should be attached to the base of the box to hold it 10mm minimum above the surface on which it stands. This must allow the free flow of air out of the box. Always make sure that, in operation, this hole is not obstructed and the fan is not fouled. Wrap several layers of insulation, "bubble wrap" for example, around the beaker and place a drink can in position.

Make certain the fan is not obstructed by stray wires and route them as necessary so that this can never happen. Allow the unit to operate for increasing times up to one hour, checking that the box remains quite cool and the heatsink does not become excessively hot. When satisfied, attach the lid.

Happy cooling! □

Limited Life Cycle

Electronic products that destroy themselves sound like a mixed blessing and Andy Emmerson confirms this.

CONSUMER electronics that self-destruct are nothing new. Twenty years ago certain brands of colour TV were notorious for catching fire, whilst the switch-mode power supplies in another mass-market manufacturer's satellite receivers and home fax machines invariably suffered an early demise.

Of course these effects were unintentional, unless you consider lousy design and penny pinching (sorry – value engineering!) a deliberate policy. But today's novelty is products intentionally designed to self-destruct after a period of use.

The stated and obvious reason for these is to assist recycling and thus protect the environment, although a secondary objective is limiting what manufacturers and rights holders would consider misuse. We'll touch on waste recycling in a moment but let's look first at self-destructing DVDs.

IMPECCABLE VIEWING

This time last year an American company, Flexplay Technologies Inc., announced what it called "a breakthrough in the DVD manufacturing process" and "a major technological achievement for the industry". The industry breathed a sigh of relief, although savvy consumers were not so ecstatic, since Flexplay DVDs self-destruct after 48 hours. Branded "EZ-D", these discs start to deteriorate as soon as they are removed from their packaging.

Consumers can enjoy their movie as many times as they wish during this time frame. After 48 hours of impeccable play, the DVDs are no longer readable by the DVD player and can then be recycled (or more likely thrown away as general rubbish). The makers say a Flexplay-enabled DVD works in all players, DVD drives and gaming systems designed to accept a standard DVD. GE Plastics, a division of (American) General Electric, developed a new patented Lexan resin co-polymer essential to the flexible play design.

EZ-D's goal is to expand the overall home entertainment market by appealing to consumers who find the current rental process tedious. With EZ-D they no longer have to return their choice to the shop, nor need they worry about late fees or scratched discs. The Buena Vista Home Entertainment Division of the Walt Disney Company certainly likes the idea and started test-marketing this technology last summer.

Hollywood studios are enthusiastic too and are planning to use self-destructing DVD for the "screeners" (viewing copies) they send out for judges of the Oscar awards. Voters for France's César awards, the French equivalent of the Oscars, have

already received DVDs that become unplayable after two days. In both cases the idea is to defeat bootleggers who bribe voters and then sell pirate copies of the brand-new movies. Whether the move will succeed is debatable, since 48 hours is plenty long enough to copy a DVD.

SPOILSPORT SONY

One of Sony's subsidiaries has devised a spoiler for downloadable movie files, making these self-destruct after a given time. There's big money to be made offering video entertainment over the Internet but in the process the door is opened to illegal copying as well. The movie provider Sonnet has incorporated into its service a digital rights management (DRM) technology from software maker Japan Wave that makes copying impossible.

Instead of saving a video to a single file and location, Japan Wave's technology splits the data into numerous directories on a hard disk. People need to download special software to play back the various pieces as a continuous movie. A second layer of protection embedded in the file then ensures that it self-destructs after a given time.

How successful this technique will be is debatable. There are plenty of computer programs that capture the video and audio bitstreams before they are saved or processed, and if you can see material, you must be able to capture the bitstreams.

SMART MATERIALS

If you think saving the planet is more important than saving movies for watching a second time, then you'll be interested in moves to make recycling simpler. The pressure to limit waste when electronic products come to the end of their life cycle is exercising the minds of activists and technologists alike. It's also spawning some mighty ingenious new ideas involving "smart materials" and one of these is plastic screws that self-extract when heated.

Active Fasteners Ltd, a spin-off company of Brunel University, has spent three and a half years perfecting a product that self-disassembles for recycling. The plastic screws use special "shape memory polymers" that lose their mechanical strength when heated and can be used as releasable fasteners. The development project involved manufacturers such as Nokia, Motorola and Sony, all of whom have a keen interest in minimising their exposure to the new pan-European recycling regulations that come into force in 2006.

Known as the Waste Electrical and Electronic Equipment Directive (WEEE), the rules apply to a huge spectrum of products and aim to minimise the impacts of

electrical and electronic equipment on the environment during their life times and when they become waste. Critically, the new regulations make producers responsible for financing most of these recycling activities, with private householders being allowed to return products covered by WEEE without charge.

Manufacturers will need to ensure that their products – and their components – comply in order to stay on the Single Market. If they do not, they will need to redesign products.

BIG BANG THEORY

Some kinds of electronics self-destruct with explosive force. Researchers at the University of California in San Diego (UCSD) have developed silicon chips that explode. Two years ago professor Michael Sailor, head of the project, stated: "We're making a silicon nanocrystal which has such a high surface area that it burns very quickly. The faster the burn, the bigger the bang."

The explosive effects were discovered accidentally when a researcher working on porous silicon wafers substituted potassium nitrate with gadolinium nitrate. The effect has two potential applications, for performing rapid chemical analysis of elements in the field and as a propulsion source for micro-electrical mechanical systems (nanobots).

Some electronics hobbyists are already familiar with the explosive capabilities of electronic components. I myself have created a miniature Mount Vesuvius after accidentally applying 24V d.c. to a memory chip (impressive . . . and expensive). And electrolytic capacitors are not called "smoothing bombs" for nothing. Big ones can cover an entire ceiling with their mess when provoked.

EXPLOSIVE CHARGES

Most spectacular of all are the detonators hidden in some Allied and German WW2 military surplus radio equipment. At least one collector has seen his garden shed go up with a bang (spontaneous detonation) and another, to his horror, had an innocent-looking "component" identified as a charge. Frequently these detonators look extremely similar in shape and size to electrolytic capacitors, as a photo feature in the German historical wireless society's magazine, *Funkgeschichte*, showed. It also quoted a newspaper report of 1949 in which a domestic radio technician testing war-surplus radio components for re-use lost his sight when one of these "capacitors" blew up in his face.

Next month I'd better bring more cheerful news!

Electronics – from Australia??!!

You have to be joking?

No, not at all!

The hobby electronics market in Australia has been historically very strong with large numbers of enthusiasts serviced by dynamic electronic magazines and vigorous commercial suppliers.

The most dominant company in this "Down Under" market, Jaycar Electronics, is now in a position to offer its great range of products to a wider audience, thanks to the Internet.



Moreinfo?
www.jaycarelectronics.co.uk

Concerned about dealing on the Internet?

Well, you should be. At the same time, the amount of legitimate internet trade exceeds the fraudulent trade by millions and millions to one. World internet trade today easily exceeds the Gross National Product of many large countries!

Jaycar has been doing business on the Internet now for over 10 years. The thousands of happy repeat customers on our files is a testimony to how safe it can be when you deal with a reliable supplier like us. Worried about freight costs? NO NEED with our great rates.

New 2004 Catalogue - all 424 pages

We have a brand new catalogue priced in UK Pounds crammed with over 6000 exciting products. You can get one FREE by logging on to our website and filling out the catalogue request form at www.jaycarelectronics.co.uk/catalogue (Offer valid till October 2004).

FREE
424 page
Catalogue

We Stock:

- A huge range of exciting kits
- A great range of robotic components
- The best range of electronic components
- The largest single-source range of gadgets
- Security, Surveillance, Audio/Video, Lighting, Computer & Telecoms Parts etc.

Check our website!

- Entire Jaycar 2004 Catalogue on-line – over 6000 products.
- 128-bit Secure on-line ordering – safe & secure.
- Express ordering.
- Search by category, keyword or catalogue number, & advanced search.
- Over 3500 product datasheets & application notes available on-line.



This is a built up Theremin from a Jaycar kit. The Theremin is a weird musical instrument that was invented early last century but is still used today. The Beach Boys hit: "Good Vibrations" featured the Theremin. You can have one of these kits (cat no. KC-5295) for £12.95. All kits have first class instructions written in clear English text with plenty of illustrations and component identification.



www.jaycarelectronics.co.uk

0800 032 7241

(Monday - Friday 09.00 to 17.30 GMT + 10 hours only)

For those that want to write:

100 Silverwater Rd Silverwater NSW 2128 Sydney Australia

Jaycar
Electronics

BODY DETECTOR MkII

THOMAS SCARBOROUGH



Create your own invisible defence shield

EVERY living human body is surrounded by an electric field, which may potentially be detected at a few metres' distance. Even if this can only be detected at a distance of a few centimetres (as opposed to millimetres), the applications are legion.

Consider now that the phenomenon of capacitance is entirely dependent on the existence of electric fields. If, therefore, a human body should approach the positive plate of a capacitor, the body's electric field will cause the value of the capacitor to rise.

In the Body Detector circuit described here, this is detected by means of an RC (resistance-capacitance) oscillator. As the value of *C* rises, so the frequency of the oscillator drops. All that remains is to detect this drop in frequency to obtain some very interesting results.

APPLICATIONS

Some of the possible applications for the Body Detector MkII are outlined in the "Modes" panel, together with operation diagrams (Fig.1a to Fig.1g).

While in theory its operation is dependent on the electric field which surrounds the human body, in effect it would seem that an invisible field surrounds the sensor – somewhat like the "invisible" defence shields seen in the *Star Wars* movies. It would appear, therefore, that as a human hand (for instance) enters this invisible field, an alarm is triggered.

DESIGN PRINCIPLES

Modern proximity sensors will seldom detect a human body at more than a few millimetres' distance (for example, the touch switch on a bedside lamp, or the button of a lift). Besides the fact that some applications don't need a greater range, this is because it is difficult to achieve greater sensitivity with any reliability.

In order to achieve a greater range, two challenges in particular need to be overcome:

The first is environmental variations which affect the stability of the circuit, as well as variations within the circuit itself (such as warming).

The body's electric field may be described as extremely weak, and the

body's capacitance at a small distance from a sensor is typically measured in fractions of a picofarad. Therefore the circuit needs to be exceedingly sensitive.

This, however, greatly increases its sensitivity to variations in voltage, temperature, humidity, and so on, and means that special measures need to be taken to protect it from such variations, or to eliminate them.

The second important challenge is to find a means of reliably picking up small shifts in frequency as a body approaches, and (if possible) to incorporate these in the circuit in a user-friendly way.

The author's original *Body Detector* (EPE March 2001) used five "building blocks" in its detection section, while the new Body Detector MkII circuit (Fig.3) uses only two. The new version also requires no special optimisation for the sensor, as did the original design, and may be easily adjusted to almost any sensor of one's choosing.

In brief, the new design is based on an astable oscillator (IC1a) and a non-retriggerable monostable (IC1b) operating in tandem – see Fig.3. Notice that these use


somewhat similar component values, as well as similar physical components, so that any environmental influences on IC1a are duplicated in IC1b. Most importantly, nearly all of the components surrounding IC1 have the same temperature coefficients.

Also, notice that both the astable oscillator and the non-retriggerable monostable are housed in the same package (IC1), which means that any warming or cooling of the device affects both sub-circuits more or less equally. Thus environmental variations are largely cancelled out.

SENSITIVITY

It is hard to quantify the circuit's sensitivity and stability, since this depends on a number of factors, particularly the range it is adjusted to, and the surface area of the sensor.

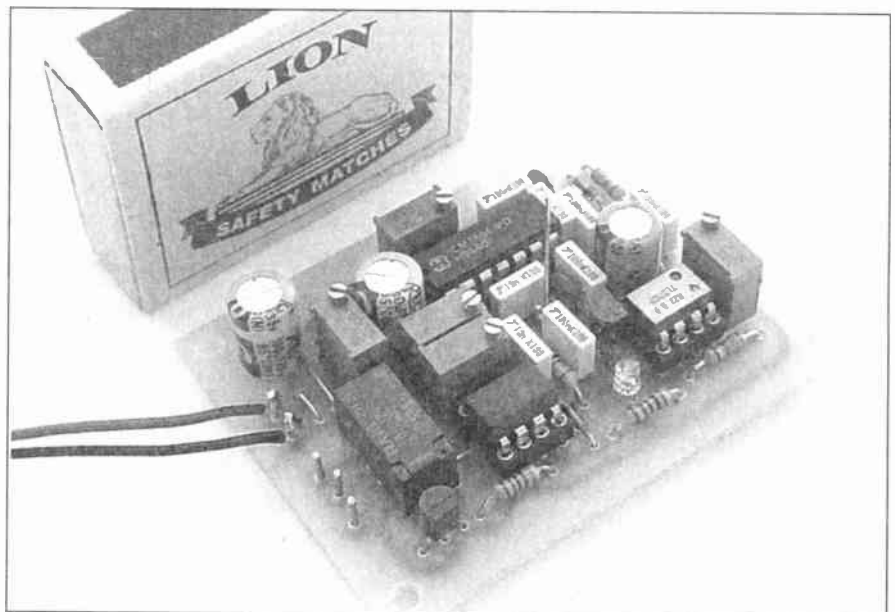During tests, at 100mm range, using a 300mm × 300mm sheet of tin foil as the sensor, the prototype showed just over 1.5% shift in sensitivity per 1°C temperature variation. This means that in most situations the circuit is "solid" at 100mm range, which is more than adequate for protecting a bicycle, or valuables on a shelf.



However, at 250mm range, and using the same sensor, temperature becomes a significant problem (it triggers the circuit) if temperature *increases* by more than about 10°C. The maximum range of the circuit will lie around 600mm.

CHERRY PICKING

The output of IC1a (at pin 5) is fed to the trigger input of IC1b. Therefore astable IC1a triggers monostable IC1b. However, it is the way in which IC1b is triggered that is important.

Suppose that monostable timer IC1b goes "high" for a duration fractionally longer than the period of astable IC1a (with IC1b being triggered by the trailing edges of pulses from IC1a). Therefore IC1b will miss the next trailing edge from IC1a, and will only be triggered by the following trailing edge. The result is a square wave as seen at the top of Fig.2a.


If then a body comes near, the frequency of IC1a will drop, therefore monostable timer IC1b will go "high" for a duration

fractionally *shorter* than the period of astable IC1a. Therefore, IC1b is almost instantly triggered again as it "runs smack into" the next trailing edge from the oscillator. The result is the sharp negative-going pulses seen at the top of Fig.2b.

It need hardly be said that these two very different waveforms will have a significantly different effect on a standard charge pump. Therefore a minute variation in frequency at IC1a pin 5 results in a very significant difference at IC1b output pin 9. In effect, a great amplification takes place. A variation amounting to a fraction of a picofarad at C1 results in a voltage swing of about 1V at IC2 input pin 2.

To explain this by means of analogy, imagine that a worker at a conveyor belt needs to place cherries on passing cakes. The worker is barely able to do this fast enough, yet manages to give each cake a cherry.

Fig.2 (right). Body Detector trigger waveforms: a) before and b) when triggering.

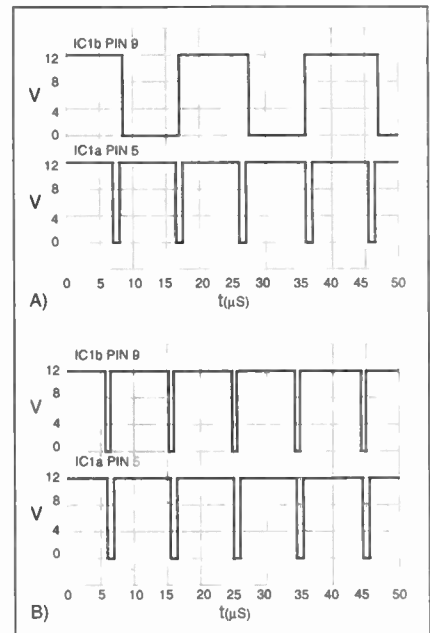

MODES OF OPERATION

If the positive plate of the timing capacitor *C* is attached to a metal sensor, this makes it more receptive to the body's electric field. This sensor may have several "modes of operation", as illustrated by Fig.1:

- As a simple metal sensor plate, Fig.1a, for example the button of a lift. This may be as small as desired – even the size of a pinhead. Or the sensor plate may be replaced with another metal object – e.g. a set of burglar bars as shown in Fig.1b. This may weigh as much as tens of kilos.

Up to a point, a larger sensor increases the Detector's sensitivity, until the mass of the sensor begins to "swamp" the electric field of the human body approaching it.

Note that the Body Detector may be used either with or without an earth wire (or a "proxy" earth through a d.c. power supply), and this will make a significant difference to its performance (see article).

With an earth wire, the author's prototype had no difficulty protecting his large and heavy single-cylinder motorbike. When clipped to the exhaust pipe at the rear, a finger touching a spoke on the front wheel triggered the circuit.

Without an earth wire, sensitivity is much reduced. Even so, without an earth, the prototype was easily capable of protecting a bicycle. It was stretched to the limit, however, with a 6-metre aluminium ladder.

The author also tested the Detector on a cat, which triggered the circuit every time it climbed through a set of burglar bars.

- Place a conductive object on top of a sensor plate (e.g. a drink tin) as shown in Fig.1c. This object then becomes an *extension* of the sensor. This could be useful to protect a valuable or dangerous object.

- More interesting still, place some insulating material between a sensor plate and the conductive object. A book is shown in Fig.1d, since paper serves as a good insulator. (Plastic, rubber, glass, ceramics, wood, and even air serve as good insulators.) If the circuit is suitably adjusted, the object on top of the insulator will serve as an extension of the sensor, even though it is not physically connected to it.

Now consider that the book is replaced with a tablecloth, or even a tabletop, and a silver dinner service is placed on top. The dinner service is now protected by the Detector, without the need for any wired connections, and without any "electronics" being evident.

This could be useful, among other things, for protecting items on shop shelves, or at a hospital bedside. It could detect feet passing over a carpet – even a hand placed over an invisible "panic plate" hidden in concrete.

- Conversely, if a metal object which is in contact with a human body approaches the sensor plate, Fig.1e, the circuit will detect this object as though it were the body itself. As far as the Detector is concerned, such an object becomes indistinguishable from the human body.

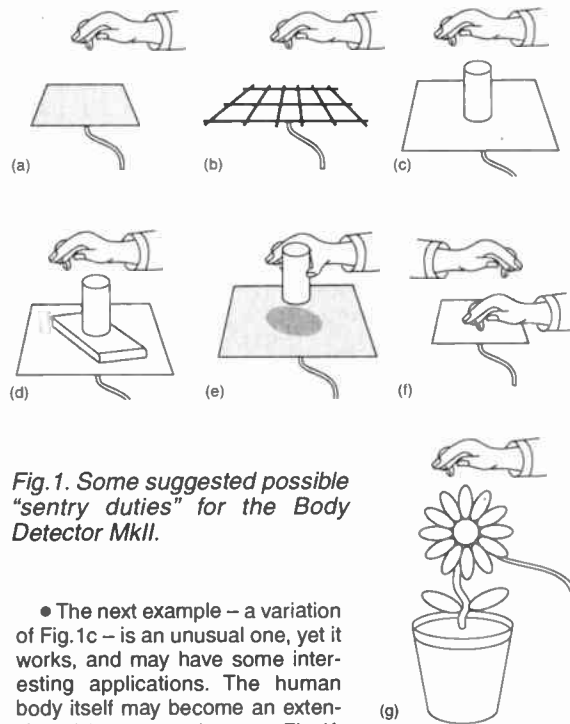


Fig.1. Some suggested possible "sentry duties" for the Body Detector MkII.

- The next example – a variation of Fig.1c – is an unusual one, yet it works, and may have some interesting applications. The human body itself may become an extension of the sensor plate, see Fig.1f. In this case, a second human body which approaches the first will trigger the circuit.

If, as an example, a metal sensor were strapped to the ankle of an infant, the circuit would detect a person touching the infant – even with the tip of a finger. This works better when a larger person is touching a smaller person. We might call it an "Anti-Kidnap Alarm".

The circuit is also able, to a point, to detect how *large* a body is, and whether two or more bodies are in physical contact with each other when they touch the sensor. In fact if the Body Detector were capable of a little more accuracy, it would indicate someone's weight by shaking their hand!

- Since plants are conductive, as well as having a high degree of electrical isolation from the ground, these may also serve as the sensor, Fig.1g, with the contact to the circuit being made, for example, through a pin stuck into the stem. This could serve to protect valuable flora, or ripening fruit.

In one experiment, the author detected bare feet walking on grass. Since this was buffalo grass, the grass "sensor" covered an area of about 1m x 1m.

Consider then that the conveyor belt slightly speeds up. The worker is unable to keep up any more, and is too late for every second cake. A slight increase in the speed of the conveyor belt thus results in a 50% change to the appearance of the cakes.

Needless to say, this same filter arrangement may be used in various applications where a frequency remains within known parameters (that is, comfortably within $2f$, where f is the frequency threshold to be detected). This will work at frequencies from tens of hertz to a few hundred kilohertz, assuming that the component values in the charge pump are suitably adjusted.

CIRCUIT DETAIL

The full circuit diagram for the Body Detector MkII is shown in Fig.3. The functions of IC1a and IC1b have just been described. A dual CMOS 7556 timer is used for IC1, and this should not be replaced with a standard 556 timer i.e. – it will not work!

The frequency of oscillator IC1a is calculated by the formula:

$$f = 1.46 / ((VR1 + VR2) \times C1) \text{ Hz}$$

while the period time of monostable IC1b is calculated by the formula:

$$t = 0.69 \times (VR3 + R1) \times C3 \text{ seconds.}$$

IC1a oscillates at around 100kHz, although its frequency is dependent to a large degree on the mass of the sensor.

A very small value timing capacitor (C1) is employed for IC1a, in particular so that the oscillator will readily respond to the body's electric field. Capacitor C3, as used with IC1b, is the same value as C1. If possible, both C1 and C3 should have a zero temperature coefficient or NPO. Control voltage decoupling (C2 and C4) has been included on both IC1a and IC1b for added stability, along with supply decoupling capacitors C12 and C13.

All the timing components of IC1a and IC1b have identical temperature coefficients. This is why variable resistors (trimmer potentiometers) are used throughout – with the one exception of R1. Resistor R1 amounts to just one kilohm (1k), and will only have a small effect on the stability of the circuit. Perfectionists might, however, wish to replace this with a link wire (or with another variable resistor). In this case, VR1 should never be reduced below about 1k, otherwise IC1 is sure to self-destruct!

The output of the non-retriggerable monostable timer (IC1b) is fed to a standard diode charge pump. Charging is both limited and controlled by resistors R2 and R3, so that the charge on capacitor C6 will vary between about 5.5V and 6.5V as a body comes near the sensor.

The values of resistors R2, R3, and C6 are chosen to be large enough to damp mains transients and electromagnetic pulses (e.g. a nearby fluorescent light switching on or off) for greater reliability. This may be appreciated by tapping the sensor very rapidly. If it is tapped rapidly enough (thus

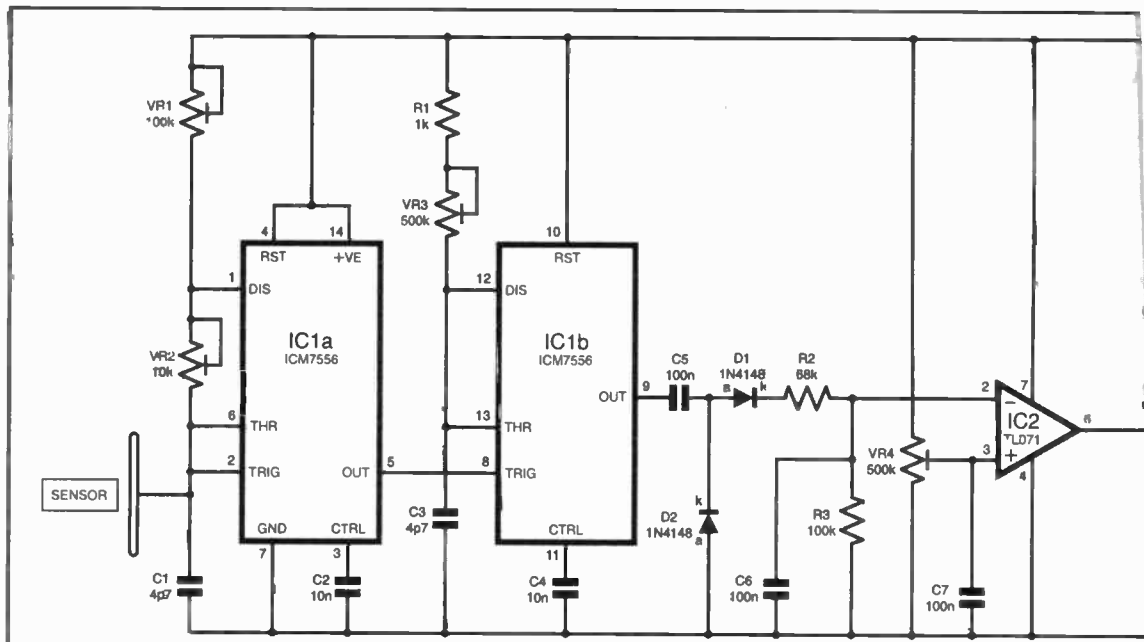


Fig.3. Complete circuit diagram for the Body Detector MkII.

mimicking a transient), the Body Detector will fail to trigger. The value of capacitor C6 may be increased if there is any problem in this department.

A simple inverting comparator is formed around IC2 and associated components. The "threshold voltage" is set by preset VR4, so that the output, at IC2 pin 1, swings "high" or "low" as the inverting input crosses the threshold. It will swing "low" as a body approaches the sensor – assuming that VR4 is suitably adjusted.

BLANKING OUT

Resistor R4, together with field-effect transistor TR1, R5, C8, and D3, represent a "blanking" circuit, which for a brief moment (about 200ms) blanks the action of relay RLA after it has been activated. This ensures that the relay's back-e.m.f. does not destabilise the very finely balanced circuit.

The effect of these components may be appreciated by holding one's hand to the sensor continually. As IC3's timing period comes to an end, and i.e.d. D4 extinguishes, a fraction of a second's delay is noticed before it illuminates again.


A simple monostable timer, IC3, triggers the relay for a period determined by preset VR5 and resistor R8. Its period time is calculated by the formula: $t = 0.69 \times (VR5 + R6) \times C9$ seconds, so that it may be adjusted between about 70ms and 35 seconds with the component values shown. If different timing periods are required, the value of capacitor C9 may be increased for longer time periods, and vice versa. The output of monostable

timer IC3 (pin 3) provides current for transistor TR2, which in turn switches relay RLA.

The arrangement at IC3 reset pin 4 delays the circuit's "coming alive" at switch-on by about seven seconds, so that one has time to stand back from the circuit after switching on. Failing this, body capacitance could trigger the circuit at switch-on.

Although, in circuit diagram Fig.3, there is no direct provision for a delay before the circuit is triggered (e.g. when returning to a bicycle which is protected by the Body Detector), this could be arranged by wiring a large value capacitor (say 47μF) in parallel with C6, then reducing preset VR4 as far as possible (this means turning it *clockwise!*) without disabling IC2's output (see further notes under "Setting Up").

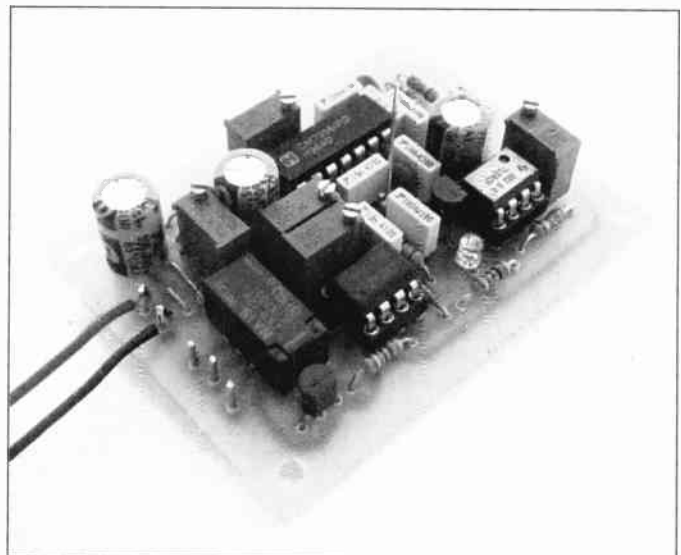Relay RLA is a miniature Telecom type with integral diode to reduce back-e.m.f. It has two sets of changeover contacts, which are rated 60W (2A/30V d.c.) maximum.



Completed Detector circuit board showing the d.i.l. relay and the three contact pins on the edge of the p.c.b.

CONSTRUCTION


The Body Detector MkII is built up on a small printed circuit board (p.c.b.) measuring about 65mm x 50mm. Details of the topside component layout, together with the full-size underside copper foil master, are shown in Fig.4 (note that these differ slightly from the photographs). This board is available from the *EPE PCB Service*, code 449.

All the components should fit into place without too much difficulty. However, a fine-tipped soldering iron would help, since this is a compact circuit board.

Before soldering and commencing construction work, adjust preset VR1 to about 50k, VR2 to 5k, VR3 to 10k, VR4 to 250k, and VR5 to 10k.

Turning to the circuit board, solder the eleven link wires and six solder pins, and the three dual-in-line (d.i.l.) sockets in position. Since the printed circuit board is so densely populated, the author abandoned the usual soldering sequence, and built up the board by filling the holes from one side to the other, including the presets.

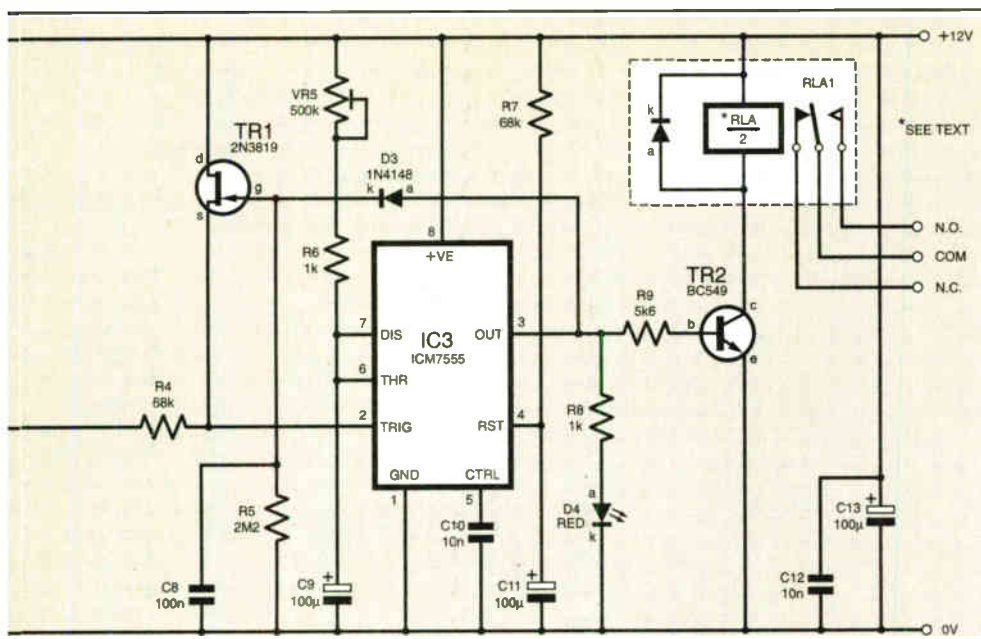Take special note of the orientation of electrolytic capacitors C9, C11 and C13. All other orientations are clear from the layout diagram Fig.4. The electrolytic capacitors must also be suitably rated, namely 16V or higher.



POWER SOURCE

No reverse polarity protection is included in the Body Detector circuit, so that it may be run off both 12V and 9V (up to about three days and nights off a small 9V alkaline PP3 battery). Note, therefore, that special care needs to be taken that the power is connected the correct way round.

The circuit is unusually stable, therefore no voltage regulation is included. However, a clean, regulated supply is sure to improve performance.

The circuit is virtually immune to static, and to e.m.f.-induced eddy currents in

the body. The Body Detector MkII is designed to detect the electric field surrounding the human body, and has a high degree of immunity to a.c. fields, as well as being able (unlike some proximity detectors) to function well out of range of such fields.

COMPONENTS

Resistors

R1, R6, R8	1k (3 off)
R2, R4, R7	68k (3 off)
R3	100k
R5	2M2
R9	5k6

All 0.25W 5% carbon film

Potentiometers

VR1	100k 25-turn cermet preset, top adjust
VR2	10k 25-turn cermet preset, top adjust
VR3 to VR5	500k 25-turn cermet preset, top adjust (3 off)

Capacitors

C1, C3	4p7 ceramic (2 off)
C2, C4, C10	10n polyester (3 off)
C5 to C8 C12	100n polyester (5 off)
C9, C11, C13	100µ radial elect. 16V (3 off)

Semiconductors

D1 to D3	1N4148 signal diode (3 off)
D4	3mm ultrabright l.e.d. red
TR1	2N3819 field-effect transistor (f.e.t.)
TR2	BC549 npn small signal transistor
IC1	7556 CMOS dual timer
IC2	TL071CN j.f.e.t. op.amp
IC3	7555 CMOS timer

Miscellaneous

RLA	12V d.c. coil, Telecom TX series, relay with 2A 30V d.c. d.p.c.o. contacts
-----	--

Printed circuit board available from the *EPE PCB Service*, code 449; plastic case, size and type to choice; 8-pin d.i.l. socket (2 off); 16-pin d.i.l. socket; plastic self-adhesive p.c.b. stand-off pillars (4 off); battery clip, with leads, or power socket (see text); link wire; solder pins; solder etc.

Approx. Cost
Guidance Only

£17
excl. case & batt.

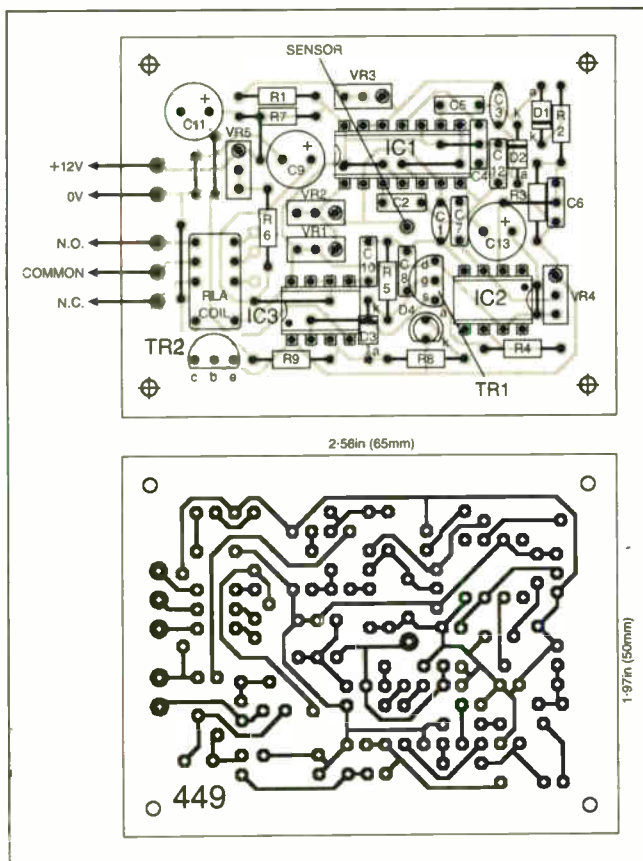


Fig.4. Printed circuit board topside component layout, wiring and full-size underside copper master for the Body Detector MkII. Note, some of the link wires pass under some components.

Any lead which is taken from the board to a sensor should be *soldered* to the solder pin at the centre of the p.c.b., and the "free" end *bolted* to the sensor to ensure good electrical contact.

Finally, insert the i.c.s in the d.i.l. sockets, noting their correct orientation. Observe anti-static precautions with IC1 and IC3, which are CMOS devices, albeit relatively tough ones. The most important precaution is to touch your body to ground immediately before handling these devices. Take care also with f.e.t. TR1, since this is also a more sensitive device.

RELAY

One set of relay contacts is routed to three solder pins on the edge of the p.c.b., and these may be used to wire up an external load. Another three holes are provided on the p.c.b. in case the spare set of relay terminals is required.

Since the relay is rated 60W (2A/30V d.c.) maximum, a powerful siren may be wired to the contacts. The Body Detector may also be wired to the input of a standard alarm system.

Finally, check that there are no solder bridges on the board, and connect the power (9V or 12V, but preferably 12V), again being very careful not to confuse these wires!

A mains to 12V power supply would usually provide a "proxy" earth for the circuit – or a separate earth wire may be taken from 0V on the p.c.b. to ground, which may be a metal stake driven into the ground, or the household metal plumbing in particular.

SETTING UP

Setting up may require a little patience, but should not be difficult. Do not further adjust preset VR1 or VR2, which only serve the purpose of matching temperature coefficients.

The best way to adjust the circuit is to use an oscilloscope. First touch the probe to IC1 pin 8 and glance at the period on the screen, which will eventually more or less

match the period time of IC1b. This waveform should show short negative-going pulses as seen at the bottom of Fig.2.

Then touch the probe to IC1 pin 9, and start turning up preset VR3 (clockwise). The positive-going pulses will gradually widen, until they turn into very narrow negative-going pulses (see the top of Fig.2b). Then suddenly a more or less balanced square wave will bounce onto the screen (see the top of Fig.2a). Touch the sensor, and the narrow negative-going pulses will reappear.

Now adjust preset VR4 so that i.e.d. D4 illuminates and the relay clicks when the narrow negative-going pulses appear. Note that if VR4 is turned up too high (too far *anticlockwise*), the circuit will be needlessly susceptible to transients.

Adjustment with a multimeter is equally straightforward. Monitor the voltage at the positive plate of capacitor C6, and slowly turn up VR3. The voltage should gradually rise to above 6V, then suddenly plunge to somewhere over 5V. This "plunge" amounts to about 1V or a little more.

Measure the voltage at IC2 pin 3, and adjust it (via VR4) to about 0.3V higher than the voltage measured after the "plunge" referred to above. When the sensor is now touched, i.e.d. D4 should illuminate.

If a different sized sensor is used, or if a sensor is moved about, preset VR3 will likely require readjustment. If there is a significant difference in the mass of sensors used, VR4 might need readjusting also.

If the Body Detector is attached to a new sensor, and the set-up above has already been completed, VR3 may be turned right back (anticlockwise), then turned up (clockwise) until i.e.d. D4 illuminates, continuing until D4 just goes out again. The rest is fine-tuning.

Bear in mind that the circuit might be affected by your own body capacitance during adjustment, so that you might need to stand back between adjustments to check how it is going. Ideally, you would use a screwdriver with an insulated shaft. Also bear in mind that the circuit might need to settle after initial adjustment. Come back to it ten minutes later to re-check the adjustment.

SUMMARY

All in all, it is sensible to adjust the Body Detector so that it is sensitive enough to safely trigger, yet not so sensitive that it comes too close to its trigger threshold, which may lead to false triggering, particularly with temperature variations. A distance of 100mm (4in.) represents a dependable range for a lightweight sensor such as a sheet of tin foil or a small set of burglar bars.

Finally, adjust preset VR5 (turning this clockwise) to set the monostable timer and relay to the desired time period.

You can now go to the "Modes of Operation" panel listed earlier (see Fig.1), to test any of the options which are of interest to you, as well as testing the outer limits of the circuit. □



IT'S AN ATTRACTIVE ISSUE NEXT MONTH – ORDER YOUR COPY NOW!

★ EPE MAGNETOMETER – Pt 1 ★

★ BONGO BOX ★

PLUS

TEACH-IN 2004 Part 9

Annual subscription rates:

6 Months: UK £16.50, Overseas £19.50 (standard air service),
£28.50 (express airmail)

1 Year: UK £31.00, Overseas £37.00 (standard air service),
£55 (express airmail)

2 Years: UK £57.00, Overseas £69.00 (standard air service),
£105 (express airmail)

To: Everyday Practical Electronics,
Wimborne Publishing Ltd., 408 Wimborne Road East, Ferndown, Dorset
BH22 9ND

Tel: 01202 873872 Fax: 01202 874562

E-mail: subs@epemag.wimborne.co.uk

Order from our online shop at:

www.epemag.wimborne.co.uk/shopdoor.htm

EVERYDAY
**PRACTICAL
ELECTRONICS**

TAKE ADVANTAGE NOW!

SUBSCRIPTION ORDER FORM

To subscribe from the USA or Canada
see the last magazine page

I enclose payment of £
(cheque/PO in £ sterling only),

payable to Everyday Practical Electronics



My card number is:

Please print clearly, and check that you have the number correct

Signature

Card Security Code (The last 3 digits on or just under
the signature strip)

Card Valid From Date Ex. Date Switch Issue No.

Subscriptions can only start with the next available issue.
For back numbers see the *Back Issues* page.

06/04

Name

Address

Post code Tel.

If you do not wish to cut your issue, send a letter or copy of this form.

READOUT

WIN AN ATLAS LCR ANALYSER WORTH £79

Email: john.becker@wimborne.co.uk

John Becker addresses some of the general points readers have raised. Have you anything interesting to say? Drop us a line!

All letters quoted here have previously been replied to directly.

An Atlas LCR Passive Component Analyser, kindly donated by Peak Electronic Design Ltd., will be awarded to the author of the *Letter Of The Month* each month.

The Atlas LCR automatically measures inductance from 1 μ H to 10H, capacitance from 1pF to 10,000 μ F and resistance from 1 Ω to 2M Ω with a basic accuracy of 1%.



★ LETTER OF THE MONTH ★

ONLINE P.C.B. SIZING

Dear EPE,

In response to Harry Wellborne's letter (Mar '04) outlining the sizing problem of p.c.b. track layouts from the *EPE Online* editions, I would like to share my three-step method which produces fairly good quality images.

Step 1: Open up the *EPE Online* (Adobe Acrobat) document on the desired page and reduce the size of the bookmark section to as small as possible. Then use the Zoom In function (CTRL++) on the View menu to increase the copper foil master to the maximum size that still just fits on the screen (use the horizontal and vertical sliders to position it properly). Now put the image on the clipboard by pressing and holding the Alt key, while pressing the PrintScr key.

Step 2: Open up Microsoft Paint and paste the image into it from the clipboard. Use the Select tool in Paint to select the complete copper foil master with its border only. Once done,

copy it to the clipboard. Now open up a new Paint window, and paste the image into it. It happens occasionally, especially with larger images, that unwanted "noise" ends up between the tracks. Simply zoom in by selecting Large or Custom Size, then use the Eraser tool to delete the unwanted "noise".

Ensure that the image is saved as a 24-bit bitmap, as the higher the quality, the better the end product will be.

Step 3: The final step is to scale the image to the exact size. I use Adobe Photoshop 4.0, but most image editing software packages have a resize function. Open the saved file, select Image Size on the Image menu, and specify either the print size width or height as printed on the copper foil master. Ensure that the Constrain Proportions option is selected.

Anton Fouche, via email

Thanks Anton, that seems to be advice that will be useful to quite a few readers.

MISSING THE POINT

Dear EPE,

I read the *Jazzy Necklace* letter (April '04) with dismay. I realise that you always publish a fair and balanced selection from your mailbag, good or bad, but feel that this particular letter was indicative of missing the point of having such a magazine as *EPE*.

I have taken your magazine from 1964 (when it was *Practical Electronics*) and have thoroughly enjoyed looking at all of the projects, obviously some more than others. Whilst I may not necessarily build them due to me designing and building my own in the process of my work, I always enjoy "reading" the diagrams and especially the explanations so as to see how the author has solved a particular problem. Indeed the classic to me was the one John Becker did, which was an altimeter using a 6502 microcontroller, because it also included a good background on the subject of air pressure.

I noted the first batch of Rev Thomas Scarborough's *Ingenuity Unlimited* some time back and would like to say how impressed I have been with his practical and simple approach to solving a problem – I would like to "take my hat off" to him and applaud his creativity. He displays a depth of talent. Unfortunately, the writer of the said April letter appears to have totally missed the point about Rev Scarborough's *Necklace* project. I do not, in any way intend to be critical of the writer's view or cause offence. However, it should be that projects do not always have to be practical, long lasting, earth shattering... they can also be there to stimulate thought on certain principles.

Long may Rev Scarborough continue to be inventive and please do not let such a negative criticism dissuade him. I look forward to his next one.

Dr Stephen Alsop, via email

It is rare to get negative views on what we publish, Stephen, but I'm just as content to publish criticism if it arises as I am praise (although, frankly, publicising too much praise gets tedious!)

Like you, I took PE since 1964 (although I was in another career at the time, but electronics eventually got the better of that!). I have long maintained that EPE is not just about building as published, but about illustrating techniques of problem solving and discovering how others find solutions.

And yes, we very much appreciate Thomas's ingenuity, and its simplicity of implementation.

PRAISING MILFORD

Dear EPE,

I recently acquired a 3-Axis Machine, which was in need of some repair. I contacted the manufacturers, Milford Instruments (a regular advertiser in *EPE*), to quote for the item needed to repair this machine. Not only did they reply straight away, they also agreed to supply F.O.C. the item needed.

A public thank you to Milford Instruments, for their generosity, superb customer service and for excellent customer-relations. A rare thing today!

D. J. Lacey, via email

That's so refreshing! Thanks for telling us.

TEACH-IN CAPS

Dear EPE,

I have been reading Max Horsey's *Teach-in 2004 Part 4* about the coffee machine controller. Why does the circuit in Fig.4.10 have two capacitors in parallel, C1 1000 μ F and C2 100nF, across the power supply? Also, does a capacitor have to be in the physical position that the circuit diagram indicates, i.e. close to the battery, to smooth out power supply voltage fluctuations, or could it be soldered anywhere across the power supply rails?

Len Doel, via email

Max Horsey replies:

A large capacitor is required to smooth out fluctuations in the power supply. Fluctuations occur particularly when an output device switches on e.g. a large bulb, solenoid or motor. Large value capacitors have to be electrolytic (non-electrolytic large-value capacitors are not readily available). The physical position of a large capacitor is not normally critical.

A small value capacitor (e.g. 100nF) is also required as large electrolytic capacitors are not able to remove brief voltage "spikes". These come from many sources including electro-magnetic induction. The small capacitor should ideally be physically close to any sensitive component, e.g. logic i.c., radio receiver module, regulator i.c., etc. Several such capacitors may be required in large circuits.

Max Horsey, via email

RADIO CONSTRUCTOR

Dear EPE,

I've just read Roger Parker reminiscing (Apr '04) about *Radio Constructor*. I too enjoyed the same column of "In your Workshop". I'm reminded of a very interesting article in this mag sometime during the mid to late '50s. It

concerned a record player amplifier which required no external power supply. It employed an electron multiplier valve. This valve had a number of anodes and the principle of operation was that an electron arriving at A1 would dislodge two electrons which would migrate to A2 and each dislodge two more electrons and so on, the number of electrons increasing as they progressed up the anode chain.

In the amp a radioactive source took the place of the heater/cathode, the radiation then passed through a grid to which was applied the output of a crystal or similar high output pick-up. Amplification then took place as described above. The output from this device was then suitably coupled to a loudspeaker. I can't for the life of me remember which year in the '50s that this article appeared but I do remember quite clearly the month... it was April!

By the way, did you know that before the condenser, capacitance was measured in jars? As described in the *Admiralty Handbook*. Keep up the good quality of *EPE*, all the best to you all.

Peter Mitchell, via email

Before my time Peter! It was not till the late '50s I first got an interest in electronics (having blown up my father's hi-fi by making an ill-considered link between it and another bit of gear – I forget what).

But, yes, an April edition was I'm sure well-suited to the design you mention! Even today, though, the occasional reader on our ChatZone (access via www.epemag.wimborne.co.uk) asserts his total conviction that perpetual motion does exist and requires no energy input!


No, I didn't know the other term, but I assume it has to do with Leyden jars, which if I recall correctly were the method through which electricity was first stored, and invented in Leyden (now Leiden, Holland).

STORE YOUR BACK ISSUES ON MINI CD-ROMS



**VOL 10
NOW AVAILABLE**

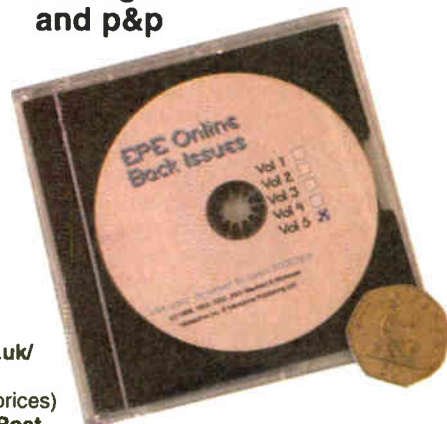**ONLY
£14.45** each
including VAT
and p&p



A great way to buy *EPE* Back Issues – our mini CD-ROMs contain back issues from our *EPE Online* website plus bonus articles, all the relevant PIC software and web links. Note: no free gifts are included. All this for just £14.45 each including postage and packing.

VOL 1: BACK ISSUES – January 1999 to June 1999
Plus bonus material from November and December 1998

VOL 2: BACK ISSUES – July 1999 to December 1999

VOL 3: BACK ISSUES – January 2000 to June 2000

VOL 4: BACK ISSUES – July 2000 to December 2000

VOL 5: BACK ISSUES – January 2001 to June 2001

VOL 6: BACK ISSUES – July 2001 to December 2001

VOL 7: BACK ISSUES – January 2002 to June 2002

VOL 8: BACK ISSUES – July 2002 to December 2002

VOL 9: BACK ISSUES – January 2003 to June 2003

VOL 10: BACK ISSUES – July 2003 to December 2003

NOTE: These mini CD-ROMs are suitable for use on any PC with a CD-ROM drive. They require Adobe Acrobat Reader (available free from the Internet – www.adobe.com/acrobat)

WHAT IS INCLUDED

All volumes include the *EPE Online* editorial content of every listed issue, plus all the available PIC Project Codes for the PIC projects published in those issues.

Note: Some supplements etc. can be downloaded free from the Library on the *EPE Online* website at www.epemag.com. No advertisements are included in Volumes 1 and 2; from Volume 5 onwards the available relevant software for *Interface* articles is also included.

EXTRA ARTICLES – ON ALL VOLUMES

BASIC SOLDERING GUIDE – Alan Winstanley's internationally acclaimed fully illustrated guide. **UNDERSTANDING PASSIVE COMPONENTS** – Introduction to the basic principles of passive components. **HOW TO USE INTELLIGENT L.C.D.s**, by Julian Ilett – An utterly practical guide to interfacing and programming intelligent liquid crystal display modules. **Phyzyb COMPUTERS BONUS ARTICLE 1** – Signed and Unsigned Binary Numbers. By Clive "Max" Maxfield and Alvin Brown. **Phyzyb COMPUTERS BONUS ARTICLE 2** – Creating an Event Counter. By Clive "Max" Maxfield and Alvin Brown. **INTERGRAPH COMPUTER SYSTEMS 3D GRAPHICS** – A chapter from Intergraph's book that explains computer graphics technology. **FROM RUSSIA WITH LOVE**, by Barry Fox – Russian rockets launching American Satellites. **PC ENGINES**, by Ernest Flint – The evolution of Intel's microprocessors. **THE END TO ALL DISEASE**, by Aubrey Scoon – The original work of Rife. **COLLECTING AND RESTORING VINTAGE RADIOS**, by Paul Stenning. **THE LIFE & WORKS OF KONRAD ZUSE** – a brilliant pioneer in the evolution of computers. A bonus article on his life and work written by his eldest son, including many previously unpublished photographs.

Note: Some of the EXTRA ARTICLES require WinZip to unzip them.

Order on-line from
www.epemag.wimborne.co.uk/shopdoor.htm
or www.epemag.com (USA \$ prices)
or by phone, Fax, E-mail or Post

BACK ISSUES MINI CD-ROM ORDER FORM

Please send me (quantity) BACK ISSUES CD-ROM VOL 1
Please send me (quantity) BACK ISSUES CD-ROM VOL 2
Please send me (quantity) BACK ISSUES CD-ROM VOL 3
Please send me (quantity) BACK ISSUES CD-ROM VOL 4
Please send me (quantity) BACK ISSUES CD-ROM VOL 5
Please send me (quantity) BACK ISSUES CD-ROM VOL 6
Please send me (quantity) BACK ISSUES CD-ROM VOL 7
Please send me (quantity) BACK ISSUES CD-ROM VOL 8
Please send me (quantity) BACK ISSUES CD-ROM VOL 9
Please send me (quantity) BACK ISSUES CD-ROM VOL 9
Please send me (quantity) BACK ISSUES CD-ROM VOL 10
Price £14.45 each – includes postage to anywhere in the world.

Name

Address

..... Post Code

I enclose cheque/P.O./bank draft to the value of £

Please charge my Visa/Mastercard/Amex/Diners Club/Switch

£

Card No.

Card Security Code (The last 3 digits on or just under the signature strip)

Valid From Expiry Date

Switch Issue No.

SEND TO: **Everyday Practical Electronics,
Wimborne Publishing Ltd.,**

408 Wimborne Road East, Ferndown, Dorset BH22 9ND.

Tel: 01202 873872. Fax: 01202 874562.

E-mail: orders@epemag.wimborne.co.uk

Payments must be by card or in £ Sterling – cheque or bank draft drawn on a UK bank.

Normally supplied within seven days of receipt of order.

Send a copy of this form, or order by letter if you do not wish to cut your issue.

solutions for learning electronics

PICmicro(R) microcontroller training days



We can help you learn PICmicro programming and also help you teach PICmicro programming to others. We provide a number of training days each term in:

Introduction to PICmicro and flowchart programming

Programming PICmicros in Assembly

Programming PICmicros in C

Each day includes 7 hands-on hours of training and full support materials to allow you to continue learning at home

CPLD/FPGA training resources



£99
-VAT

This low cost development board is suitable for both learning how to program CPLDs as well as for developing CPLD based projects

Suitable for programming and developing CPLD projects

Free development software from Altera*

Includes an Altera 7000 series device

Includes sample projects

*requires broadband internet connection

FLOWLOG electronics workbench



**Multi-channel scope
Power supply
Proto board**

£149
+VAT

Flowlog electronics workbench is the perfect platform to allow you to develop electronic projects and learn electronics. When connected to your PC it will provide you with:

5V power supply (500mA)

2 channel analogue 'scope

4 channel digital 'scope

Software for datalogging and control

Prototype board and metal backplane

please see our web site for full details of all products and training days and for free resources



next time you are online take a quick look at:

www.matrixmultimedia.co.uk

Matrix Multimedia Limited
sales@matrixmultimedia.co.uk
t. 0870 700 1831 f. 0870 700 1832



A COMPLETE RANGE OF INVERTERS 150W TO 2500W - 12V & 24V

A Complete range of regulated inverters to power 220V and 240V AC equipment via a car, lorry or boat battery. Due to their high performance (>90%) the inverters generate very little heat. The high stability of the output frequency (+/-1%) makes them equally suitable to power sensitive devices.



These inverters generate a modified sine wave, which are considerably superior to the square waves which are produced by most other inverters. Due to this superior feature they are capable of powering electrical equipment such as TV's, videos, desktop & notepad computers, microwave ovens, electrical lamps, pumps, battery chargers, etc.

Low Battery Alarm

The inverters give an audible warning signal when the battery voltage is lower than 10.5V (21V for the 24V version). The inverter automatically shuts off when the battery voltage drops below 10V (20V for the 24V version). Fuse protected input circuitry.

Order Code	Power	Voltage	Was	Price
651.581	150W Continuous	12V	£36.39	£29.72
651.578	150W Continuous	24V	£36.39	£29.72
651.582	300W Continuous	12V	£50.64	£41.93
651.585	300W Continuous	24V	£50.64	£41.93
651.583	600W Continuous	12V	£101.59	£83.76
651.593	600W Continuous	24V	£101.59	£83.76
651.587	1000W Continuous	12V	£177.18	£147.52
651.597	1000W Continuous	24V	£177.18	£147.52
651.602	1500W Continuous	12V	£314.52	£261.18
651.605	1500W Continuous	24V	£314.52	£261.18
651.589	2500W Continuous	12V	£490.54	£416.27
651.599	2500W Continuous	24V	£490.54	£416.27



ILLUSTRATION SHOWN IS 651.583 600W VERSION.

All prices are inclusive of VAT

Many uses include:- . Fetes . Fairgrounds . Airshows . Picnics . Camping . Caravans . Boats . Carnivals . Field Research and . Amateur Radio field days * Powering Desktop & Notepad Computers.



B.K. ELECTRONICS



UNIT 1, COMET WAY, SOUTHBEND-ON-SEA, ESSEX. SS2 6TR
TEL.: +44(0)1702-527572 FAX.:+44(0)1702-420243

DELIVERY CHARGES ARE £6.00 PER ORDER. OFFICIAL ORDERS FROM SCHOOLS, COLLEGES, GOVT. BODIES, PLC,S ETC. PRICES ARE INCLUSIVE OF V.A.T. SALES COUNTER. VISA AND ACCESS ACCEPTED BY POST, PHONE OR FAX, OR EMAIL US AT SALES@BKELEC.COM ALTERNATIVELY SEND CHEQUE OR POSTAL ORDERS MADE PAYABLE TO BK ELECTRONICS.

For Full Specifications View our web site at:-

WWW.BKELEC.COM/INVERTERS.HTM

INTERFACE

Robert Penfold



SOME MORE PRACTICAL IDEAS FOR CASE MODDING YOUR PC

IN the previous *Interface* article some ideas for improved PC case modding were put forward. Things continue along the same lines this month before returning to weightier matters next time.

A big advantage for case modding electronics enthusiasts is that you can "do your own thing", rather than being limited to what is available from the computer stores and fairs. You can also produce what might be termed "value added" versions of commercial units.

The circuits featured here were inspired by a young computer enthusiast who was not totally impressed with one or two EL (electroluminescent) panels he had purchased. A gadget of this type consists of a small inverter unit plus the panel itself. The panels have various designs, such as the classic "alien" type shown in Fig.1. Long EL strips are also available.

In use the EL material lights up, and various colours are used. For example, blue and green are the colours used for the "alien" design. The voltage needed to drive an EL display is higher than the maximum (12V) that can be provided by a PC. A simple inverter is therefore used to provide the necessary voltage step-up, and a suitable unit is normally supplied with the display.

Alien Flasher

This is fine as far as it goes, but the display would clearly be more dynamic and interesting if it did a bit more than light up continuously. The obvious improvement is to have it flash on or off or vary in intensity.

The amount of current drawn by one of these devices is surprisingly low, and is typically about 10mA to 15mA. In common with l.e.d.s, EL displays are quite efficient and produce very little heat.

Also, in common with l.e.d.s, the actual light output is not that huge. Even with a large EL panel or long strip, and with losses through the inverter taken into account, the power consumption is only a fraction of a watt.

The low power consumption makes it easy to pulse one of these devices. Something as basic as the 555 oscillator circuit of Fig.2 will do the job perfectly well. A standard 555 timer was used in the prototype circuit, and represents the safest option. The output stages of some low-power 555 timers have inferior ratings and could produce unacceptable voltage drops in this application.

Timer device IC1 is used in the standard 555 oscillator configuration, which has timing capacitor C1 repeatedly charging via resistors R4 and R5, but discharging through R5 alone. The output at pin 3 is high while C1 is charging and low while it is discharging. The inverter is switched on while the output of IC1 is low.

Tinkering

Using the specified values for the timing components this means that it is briefly switched on every second or so. This gives quite a good effect with most EL displays, but different effects can be obtained by tinkering with the values of the timing components.

The "on" time can be increased by using a higher value for resistor R5, and it is proportional to R4's value. If approximately equal on and off times are required, make the value of R5 high in relation to that of R4. For example, using a value of 4M7 for R5 and 47k for R4 gives "on" and "off" times that are both a little over one second. The "on" and "off" times are both proportional to the value of C1, and can easily be extended or shortened

by making its value higher and lower respectively.

Resistors R1 to R3 and transistor TR1 are optional, and enable the display to be switched off via any standard digital output. A flashing display is more interesting than a continuous type, but it is potentially more of an irritation as well.

Accordingly, it is a good idea to have some means of switching it off. Transistor TR1 is switched off when there is a logic 0 level at the Control Input of the circuit, and the unit is then able to function normally. A logic 1 input level switches on TR1, which then holds capacitor C1 in a discharged state. This in turn keeps the output at IC1 pin 3 high and the display switched off.

Making Connections

Power for an EL display is usually obtained from the PC's +12V supply via a simple adaptor. If there is a spare drive power lead, the socket on this lead is connected to the plug on the display unit's adaptor.

Power can still be obtained if there is no spare power lead, and it is just a matter of connecting the display unit's adaptor in-line with the power lead to a CD-ROM or hard disc drive. Two leads run from the adaptor to the inverter, and the one that connects to the yellow lead on the adaptor carries the 12V supply. The other lead connects to one of the black leads on the adaptor and is the 0V or ground connection.

These two leads must be cut so that the flasher circuit can be connected between the adaptor and the inverter. Make sure that the supply is connected to the flasher circuit with the correct polarity and that the inverter is also connected to the output of the flasher unit with the right polarity.

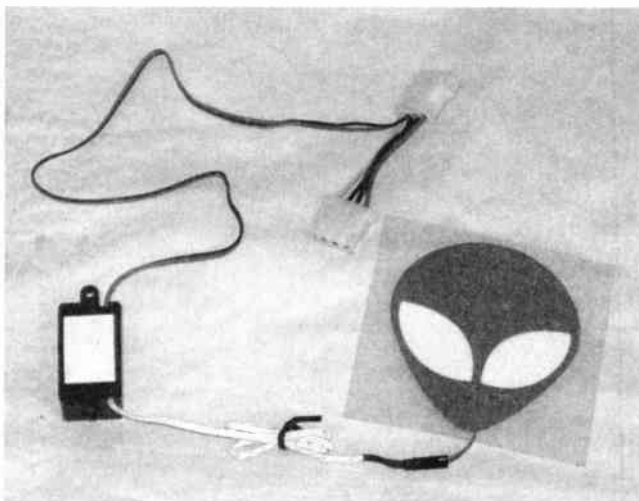


Fig.1. A typical EL (electroluminescent) panel with matching inverter and power adaptor.

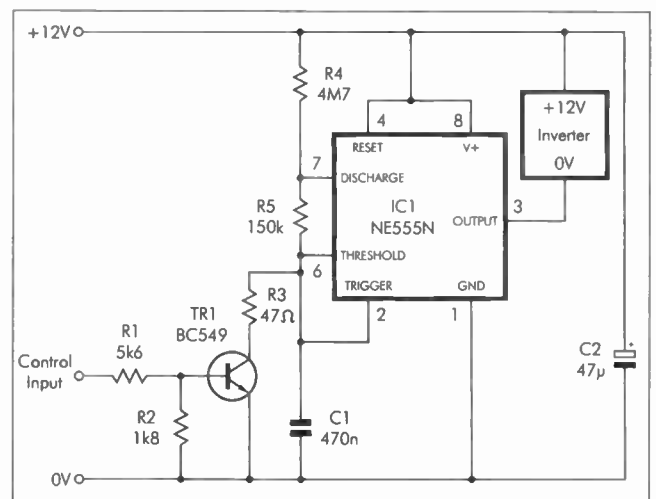


Fig.2. Basic flasher circuit diagram using a standard 555 timer i.c. A high level on the control input switches off the EL display.

Of course, cutting the power leads will certainly invalidate the guarantee, but EL display units are very cheap so you are not risking much. However, it would be prudent to check that the inverter and display are functioning correctly before cutting the wires.

Fading

The flasher circuit diagram of Fig.3 provides a slightly more sophisticated effect that has the display faded in and out rather than switching abruptly on and off. Op.amp IC1 is used in a standard oscillator configuration that provides a triangular output signal at pin 1 and a squarewave signal at pin 7. In this case it is the triangular signal that is required, and it is amplified slightly by the inverting mode amplifier based on IC2. A slightly clipped triangular output signal is provided by IC2, and this is used to drive the inverter via a common emitter buffer stage (TR2). Note, TR2 is a *pnp* device.

The display is switched on for a second or two, switched off for a second or two, and so on. However, the slow transitions at the output of IC2 (pin 6) give the required gradual change from one state to the other. There is a potential problem with this method, which is that the display might not vary in intensity as the supply voltage is varied. The inverter could have a stabilised output voltage, or it could simply cut off when the supply voltage is reduced slightly.

Tests on a few EL displays always provided good results, and the inverters seem to be extremely basic. Changes in the input potential were matched by proportionate changes in the output voltage. Nevertheless, it would be a good idea to try the unit with a variable voltage power supply before building this circuit. The display should work well with this circuit if varying its supply voltage from about 5V to 12V gives a smooth increase in its brightness.

Going Digital

Resistors R6, R7 and transistor TR1 are optional, and enable the display to be controlled via a standard digital output. Applying a logic 0 input level leaves TR1 switched off and the circuit then functions normally. A logic 1 input level switches on TR1 and pulls the inverting input (pin 2) of IC2 down to little more than 0V. The non-inverting input (pin 3) is biased to half the supply voltage, and will therefore be at the higher potential. Consequently, the output of IC2 goes high and cuts off the supply to the inverter.

Note that the CA3140E used for IC2 has a PMOS input stage and that the usual anti-static handling precautions are therefore required when dealing with this device. The "on" and "off" times are proportional to the value of capacitor C3, and can therefore be altered by changing the value of this component. A fairly high value has to be used in order to obtain a good fade-up and fade-down effect, so it is advisable not to use a value much lower than the one specified in Fig.3.

Audio Controlled

The circuit diagram shown in Fig.4 responds to the audio input level. The stronger the input signal, the brighter the display. Left and right hand channel input signals are provided by the audio output of the sound card. A line or headphone output will do.

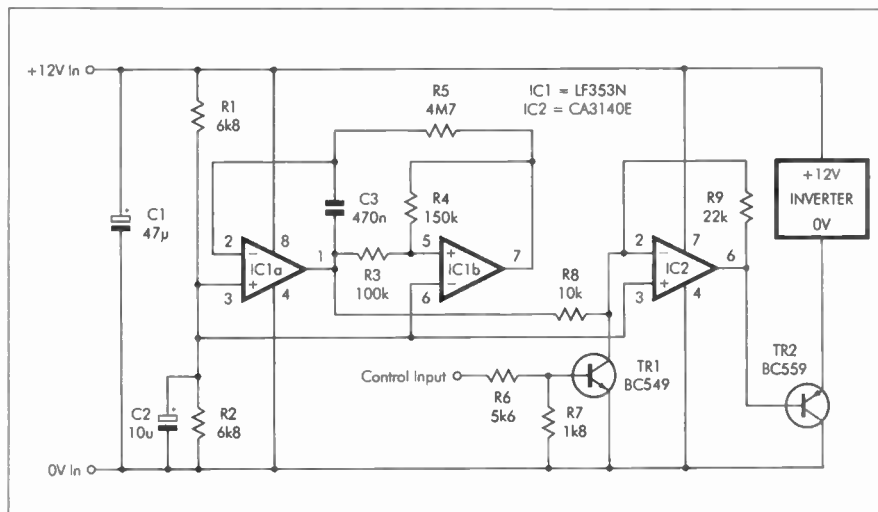


Fig.3. Circuit diagram to provide a gentle fade-up and fade-down display effect.

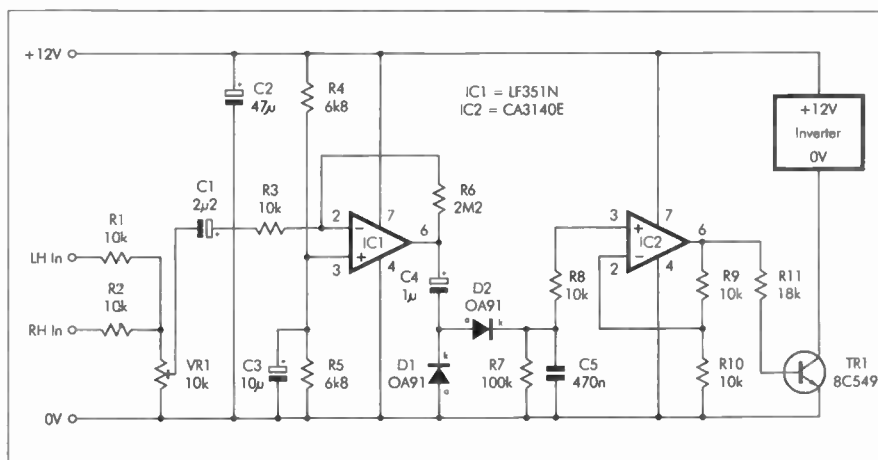


Fig.4. Circuit diagram for a sound-controlled display. The stronger the audio input signal, the brighter the display.

Preset potentiometer VR1 enables the sensitivity of the circuit to be adjusted, and in practice it is given the setting that provides the best effect. IC1 is an inverting mode amplifier that provides a voltage gain of 220 times, which should give more than adequate sensitivity using any soundcard.

Diodes D1 and D2 rectify the output from IC1 to produce a positive d.c. signal that is roughly proportional to the amplitude of the input signal. D1 and D2 can be any general-purpose germanium diodes.

The values of smoothing components R7 and C5 provide the circuit with a fast

attack but a much slower decay time. This enables the circuit to respond to brief high level signals. Op.amp IC2 operates as a low gain d.c. amplifier which drives output transistor TR1. This operates as a simple common emitter output stage.

Try adding a capacitor of about 470pF in parallel with resistor R6 if you would rather have the circuit respond primarily to low frequency signals. Remember to observe the standard anti-static handling precautions when dealing with the CA3140E used for IC2.

Radio Bygones

The leading magazine
for vintage radio
enthusiasts

ARTICLES on restoration and repair, history, circuit techniques, personalities, reminiscences and just plain nostalgia – you'll find them all. Plus features on museums and private collections and a full-colour photo-feature in every issue. It's MOSTLY about valves, of course, but 'solid-state' – whether of the coherer and spark-gap variety or early transistors – also has a place.

FROM THE DAYS of Maxwell, Hertz, Lodge and Marconi to what was the state-of-the-art just a few short years ago... THERE IS ALSO a selection of free readers' For Sale and Wanted advertisements in every issue.

Radio Bygones covers it all!


THE MAGAZINE is published six times a year, and is only available by postal subscription. It is not available at newsagents.

TO TAKE OUT a subscription, or to order a sample copy, please contact:
RADIO BYGONES, Wimborne Publishing Ltd.,
 408 Wimborne Road East, Ferndown, Dorset BH22 9ND.
 Tel: 01202 873872. Fax 01202 874562.
 Web sites: www.radiobygones.co.uk
www.radiobygones.com

Now Also
Available to
BUY ONLINE
www.radiobygones.com
 Log on, pay by credit card
 and download the magazine
 to your PC
ONLY \$9.99 (US dollars)
FOR 6 ISSUES
 A free issue is
 available

MIDI SYNCHRONOME

DAVID CLARK

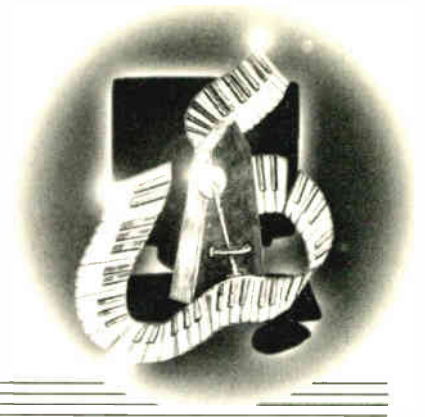

Need help to improve your musical time-keeping when recording with MIDI instruments? This project could help!

THIS article describes a novel metronome that will automatically synchronise to the clock messages output by most MIDI (Musical Instrument Digital Interface) instruments and computer sequencers. Furthermore, this design not only provides the usual time-keeping click but also simulates the swinging arm of a mechanical metronome with nine light-emitting diodes (l.e.d.s).

ON THE BEAT

Many modern music recording sessions, and live performances that involve a combination of live performance integrated with pre-recorded backing music and/or pre-programmed lighting and effects, involve the musicians synchronising their playing to a click-track. This click-track usually takes the form of a series of short percussive sounds transmitted to the performer's ear-piece, and it allows time-keeping to be much more accurate than would otherwise be likely.

For the home studio user recording with a computer-based sequencer, a click-track is usually available, and takes the form of a MIDI output that is normally converted to a percussive sound by a sound card or MIDI module. The options for the home studio musician who does not have or even want a computer-based system are more limited.

One channel of a multi-track recorder can be dedicated for use as a click-track, which would, of course, have to be recorded manually before recording proper was started. This, however, is an inconvenient and inflexible solution – one track is lost, and for a home user, tracks are at a premium, often being limited to four in an analogue system. The beats per minute (b.p.m.) rate cannot be altered either once the click-track has been recorded.

Owners of digital multi-tracker recorders often fare little better. Some do have a Metronome Output option, but many do not. And none of these options offer the visible time markers that a mechanical metronome offers, namely the sight of the arm swinging from side-to-side.

This project overcomes these limitations; it connects to the MIDI output of a multi-track recorder or sequencer that offers MIDI clock timing information, and the recorder or sequencer controls the swinging arm l.e.d. display and triggers an audible click at appropriate points. Straight or triple-time feel can be selected, and the device automatically calculates the b.p.m. rate and adds off-beat clicks between beats as appropriate.

This not only gives the straight or triple-time feel, but also fills in the gaps at low b.p.m. rates, making it easier to keep on the beat. The device also detects song pointer messages so that the metronome stays in synchronisation with the recorder or sequencer even when the controlling device is stopped, started or restarted within a song. There is also a reset button so that when used with a device that only outputs clock messages the swinging arm and beat click can be set to begin on the beat.

BASIC IDEAS

A very important aspect of the metronome is, of course, the audible click given for each beat. This allows the musician to concentrate on reading music, or perhaps on some aspect of playing the instrument itself. However, the subtle aspects of the swinging arm of the

metronome should not be overlooked. The speed of the swing of the moving arm, perhaps only caught out of the corner of the eye, and maybe only registered subconsciously, nevertheless gives the musician a sense of the rate of (musical) time passing.

Its position unconsciously prepares the musician for the actual occurrence of the beat. This is something that is missing from the type of electronic metronome that provides only a beep and/or a single l.e.d. that flashes with the beat.

This MIDI Synchronome provides not only the click and a simulation of the swinging arm of the mechanical metronome, but also off-beat clicks at a lower volume, something that a mechanical metronome does not supply. This gives better timing guidance, particularly for blues and jazz-influenced styles where a shuffle or swing feel is all-important.


GETTING THE MESSAGE

The complete circuit diagram for the MIDI Synchronome is shown in Fig.1.

The input section is a standard MIDI input based on a 5-pin DIN socket and an optoisolator, IC2, in this case a type 6N139. This provides electrical isolation, thus reducing the chance of multiple-earth problems, and converts the 5mA current loop used to convey MIDI messages and data into 5V logic signals for processing by the PIC16F627 microcontroller, IC3.

The USART (Universal Synchronous/Asynchronous Receiver/Transmitter) module of the PIC is used to extract the MIDI information from the logic signals, which are input on Port B pin RB1.

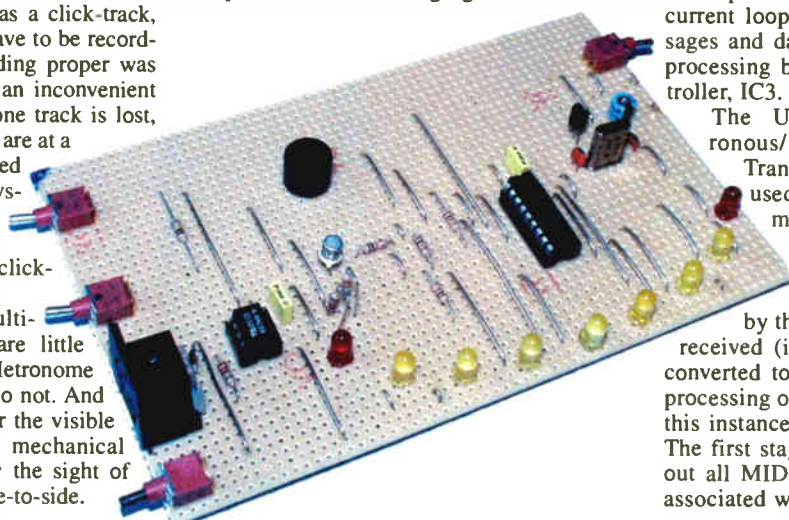The interrupt generated by this module when valid data is received (i.e. when the single bits are converted to an 8-bit word) triggers the processing of this data, processing that in this instance is all done by the software. The first stage of this process is to filter out all MIDI messages other than those associated with time keeping.



be configured as inputs in order to use the USART. These therefore are by-passed as I.e.d. drivers.

This could be overcome by using further software procedures to alter the configuration of Port B between reading MIDI data in, but this increases processing overhead, which is at a premium in real-time applications and raises the chance of a clock message being missed while other processing is occurring.

Six lines of Port B and three lines of Port A are therefore used to drive the I.e.d.s. A further two lines of Port A are used, one as an input to read the state of the Straight/Triplet Feel switch S2, and one as an output to drive the sounder that makes the MIDI Synchronome tick.

CLICK SOUNDER

The sounder chosen (WD1) generates its own frequency and so it is not necessary to use software to cause the PIC to create an output waveform; a change of level simply switches the sounder on and off. This again saves processing overhead. (The loudness is determined by how long the sounder is held on.)

The specified sounder needs 30mA to drive it. Unfortunately, the maximum output that any PIC16F627 output pin can sink or source is 25mA. The Port A driver output is therefore connected to the sounder via a general-purpose driver transistor, TR1. Fitting the sounder directly to the stripboard on which this circuit is assembled makes the click sound louder, as well as being a neater option since the metronome is not housed in an enclosure.

HARDWARE

The rest of the hardware for the circuit is straightforward. Voltage regulator IC1 provides the 5V needed to power the circuit from a 9V battery, and the timing of the PIC is determined by the usual quartz crystal arrangement (X1 plus C2 and C3) for accuracy, operating at 4MHz. The Restart switch, S3, although connected to the PIC's MCLR pin to provide a standard reset function, actually has a special function that will be described later.

To provide a further visual marker, the I.e.d.s at both extremes of the swinging arm arc are red (D2 and D10). Finally, since only one I.e.d. is lit at any one moment, a single common-cathode resistor, R6, is used to limit the current through the I.e.d.s.

SONG POSITION

Although timing the interval at which the clock messages are received enables the b.p.m. rate to be determined, it gives no information as to when the actual beat occurs. To overcome this, many MIDI instruments and sequencers also transmit a song position pointer message – see Song Position panel.

The MIDI Synchronome will detect this message and use it to calculate where the beat is. The appropriate entry in the look-up tables is then selected so that the appropriate I.e.d. lights and the click sounds at the correct time.

Some MIDI instruments, such as digital multi-track recorders and computer sequencers, allow a song recording to be stopped and re-started at any point. These usually send a fresh song position pointer message at the time of stopping and

re-starting. These systems present no problem for the MIDI Synchronome. Some types of equipment, however, do not transmit a song position pointer because in most cases this is inappropriate, for example when playing a synthesiser.

Clock messages might be needed to synchronise the tempo of a delay unit perhaps, but there is no meaningful start or stop point. In these cases, it might be necessary to re-start the MIDI Synchronome at an arbitrary point, and to this end it has been given a Restart button (S3). This resets the PIC via its MCLR reset pin.

However, the software has been written so that on receiving the first clock message in the absence of a song position pointer message, the MIDI Synchronome starts on the beat with a click and with the swinging arm at its extreme position.

CONSTRUCTION

The MIDI Synchronome is assembled on stripboard. The component layout and track cutting details are shown in Fig.2.

Begin assembly by enlarging slightly the stripboard holes needed to accommodate the p.c.b.-mounting DIN connector, SK1. Next make the track cuts, 52 in total. Ensure that the tracks are cut cleanly, removing any debris or burrs that might cause a short-circuit across the cut or between tracks. There is a relatively large number of track cuts, so ensuring each is of good quality at this stage could ease any fault-finding that might be necessary later.

The components should then be fitted in the usual order of increasing height for ease of soldering, apart from the transistor and the i.c.s, beginning with the wire links, 33 in all. Carefully observe the orientation of any polarity-conscious components.

Special note should be made of fitting the I.e.d.s. In order to maintain the sense of a swinging arm display, I.e.d. D6 needs to be offset slightly. This can be achieved by soldering one lead of the I.e.d. in position so that its base is a millimetre or two above the surface of the stripboard. The body of the I.e.d. can then be pushed towards the top of the stripboard, which will bend both of the I.e.d. leads. When the I.e.d. is suitably positioned, its second lead can be soldered in place.

For a consistent appearance, all the I.e.d.s could be positioned at the same height above the stripboard, but in practice

COMPONENTS

Resistors

R1	220Ω
R2	100k
R3	2k
R4	330Ω
R5, R6	1k (2 off)
R7, R8	10k (2 off)

All 0.25W 5% carbon film or better.

Capacitors

C1	47μ radial elect. 16V
C2, C3	22p ceramic disc, 2.5mm pitch (2 off)
C4, C5	100n polyester 63V, 5mm pitch (2 off)

Semiconductors

D1	1N4148 signal diode
D2, D10	5mm red I.e.d., low current, (2 off)
D3 to D9	5mm yellow I.e.d., low current, (7 off)
TR1	BC108C npn transistor
IC1	78L05 +5V 100mA voltage regulator
IC2	6N139 optoisolator
IC3	PIC16F627 microcontroller, preprogrammed (see text)


Miscellaneous

WD1	piezo sounder, 30mA
SK1	5-pin 180 degree DIN socket, p.c.b. mounting
S1, S2, S4	min. s.p.s.t. toggle switch, p.c.b. mounting (3 off)
S3	min. s.p.s.t. momentary toggle switch, p.c.b. mounting
X1	4MHz crystal

Stripboard, 39 strips x 62 holes; 8-pin d.i.l. socket; 18-pin d.i.l. socket; PP3 battery clip; tinned copper wire, 22s.w.g. or similar, for link wires; solder, etc.

Approx. Cost
Guidance Only

£15
excl. case

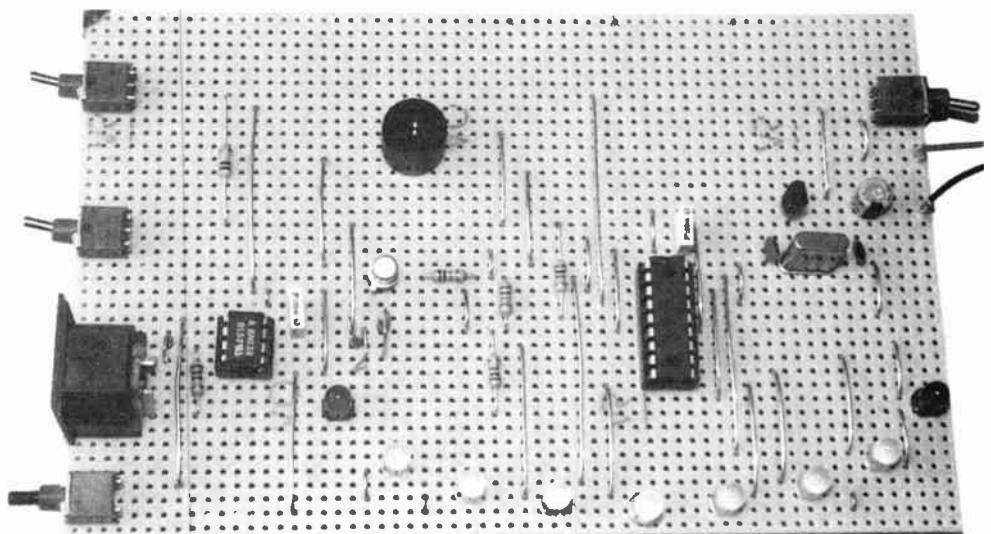

this does not affect the illusion of the swinging arm.

After all the passive components and the i.e.d.s have been fitted, transistor TR1 can be soldered in place. Voltage regulator IC1 should be soldered into position last. The pre-programmed PIC and optoisolator should only be inserted into their sockets

when construction is complete, noting that they face downwards.

Care needs to be taken when fitting the sounder. This entails some cautious bending of the sounder terminals before fitting in place as their spacing does not exactly match the stripboard hole pitch. Note that this device has polarised connections – the

positive terminal should be marked on its case.

SOFTWARE

The heart of the software lies in the tables that define the outputs to Port A and Port B and hence the lighting of the i.e.d.s and the sounding of the click. The main

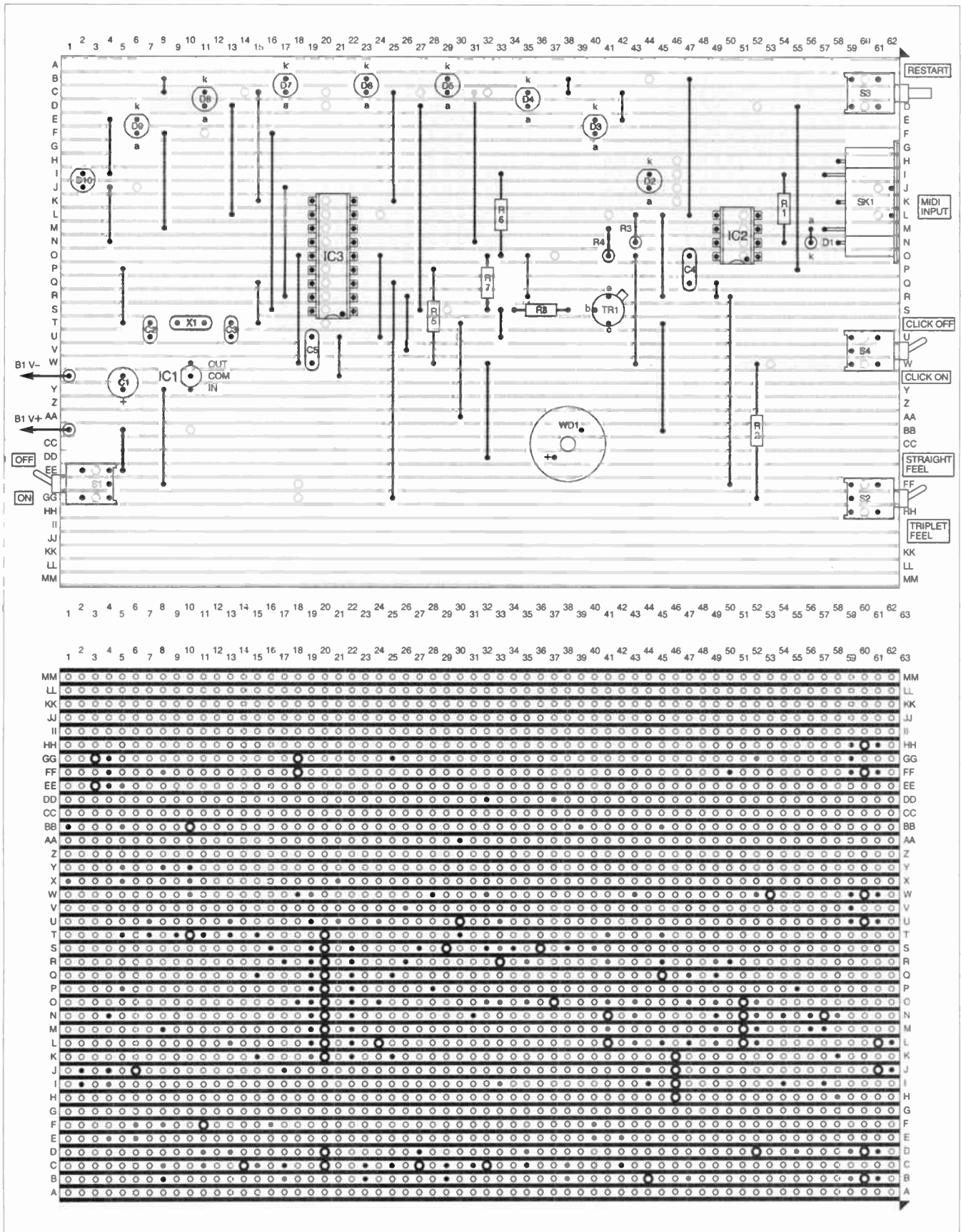


Fig.2. MIDI Synchronome stripboard component layout and details of breaks required in the underside copper tracks.

section of the program consists of a two-line loop that resets the USART and waits for the next interrupt, which occurs when a MIDI message is received.

All the processing of the messages received is done in the interrupt service routine (ISR), and this must be completed in the minimum time allowed before another MIDI message could conceivably be received. This is around a third of a millisecond (0.33ms), though as most MIDI messages need three bytes there is usually longer.

However, the software does not have the luxury of using this extra time, since, if a clock message were to be missed, the proper (musical) timing would be lost. Nevertheless, 0.33ms allows a lot of processing to be done at a clock rate of 4MHz, and there is plenty of time for the relatively simple requirements of this application.

The ISR firstly checks to see if the current message is needed for determining song position. If so, this procedure is followed. Otherwise, having ignored any messages not relevant to the Synchronome, the ISR calculates the b.p.m. rate from the time elapsed since the last clock message was received and checks whether the Feel switch (S2) is set to Straight or Triplet.

From this information the appropriate entries in the look-up tables for Ports A and B are selected and output to the ports at appropriate intervals, giving an electronic impression of a mechanical metronome.

Determining the Song Position

A MIDI system that transmits MIDI clock timing information sends out 24 messages for every quarter note. The look-up tables used by the MIDI Synchronome each contain 48 entries to correspond to the clock messages that drive the l.e.d. display through a complete cycle, i.e. from one extreme to the other and then back to its original state.

Although the MIDI Synchronome uses only eight l.e.d.s per quarter note beat (the ninth is the beginning of the next series of eight) 24 entries are needed for each beat, or half-cycle. This is to accommodate the triplet feel, since the click falls between lit l.e.d.s in this situation. The MIDI clock message is the basic timing information. For a b.p.m. rate of 85, one clock message will be sent every 29.4ms. For a b.p.m. rate of 120, one clock message will be sent every 20.8ms. Thus a simple timer will determine b.p.m. rate, as shown earlier in Musical Terms panel.

Further information is needed to determine where the main beats fall. This information can be provided from the Song Position Pointer (SPP). The SPP is a count of the number of MIDI Beats that have occurred since the beginning of a song, and a MIDI Beat is defined as six MIDI clocks. The data sent with an SPP consists of the least significant byte of the SPP count followed by the most significant byte.

To determine where in the 48-step cycle the MIDI Synchronome needs to be, the Interrupt Service Routine (ISR) first takes the three least significant bits of the SPP least significant byte. The most significant byte is ignored. This value cycles from zero to seven (i.e. eight counts, equivalent to two quarter-note beats) and then restarts from zero. Each increment of this value corresponds to six clock messages, so multiplying this value by six will give the table offset number corresponding to that point in the cycle.

By designing the table values to be on the beat at the first and twenty-fifth entries (offsets of zero and 24) the MIDI Synchronome will always be synchronised to the SPP.

switch it on, select Straight or Triplet feel as required and leave the rest to the master device. The click sounder can be switched off if the unit is to be used while recording with a microphone, rather than by using a direct electrical input to the recording device.

To restart the unit on the beat when using it in conjunction with a device that does not output song position messages, simply press Restart switch S3 when required.

This relatively simple project highlights once more how powerful PIC microcontrollers are. Most of the software code for the project consists of the look-up tables, yet the result is a remarkably useful device. It should prove ideal for the home-studio musician wanting a timing indicator that is a great improvement over the limited options usually available.

RESOURCES

The software for the MIDI Synchronome is available from the *EPE PCB Service* on 3.5in disk (for which a nominal handling charge applies). It is also available for free download from the *EPE* website, accessible via the Downloads click-link on our home page at www.epemag.wimborne.co.uk (folder path PICs/MIDI

synchronome).

Read this month's *Shoptalk* page for information on component buying for the MIDI Synchronome.

THE BEAT GOES ON

Using the MIDI Synchronome could not be more straightforward. Connect it to the MIDI output of the controlling instrument,

FRUSTRATED!

Looking for ICs TRANSISTORS?

A phone call to us could get a result. We offer an extensive range and with a world-wide database at our fingertips, we are able to source even more. We specialise in devices with the following prefix (to name but a few).



2N 2SA 2SB 2SC 2SD 2P 2SJ 2SK 3N 3SK 4N 6N 17 40 AD ADC AN AM AY BA BC BD BDT BDV BDW BDX BF BFR BFS BFT BFX BFY BLY BLX BS BR BRX BRY BS BSS BSV BSW BSX BT BTA BTB BRW BU BUK BUT BUV BUW BUX BUY BUZ CA CD CX CXA DAC DG DM DS DTA DTC GL GM HA HCF HD HEF ICL ICM IRF J KA KIA L LA LB LC LD LF LM M M5M MA MAB MAX MB MC MDAJ MJE MJF MM MN MPS MPSA MP5H MPSU MRF NJM NE OM OP PA PAL PIC PN RC S SAA SAB SAD SAJ SAS SDA SG SI SL SN SO STA STK STR STRD STRM STRS SVI T TA TAA TAG TBA TC TCA TDA TDB TEA TIC TIP TIPL TEA TL TLC TMP TMS TPU U UA UAA UC UDN ULN UM UPA UPC UPD VN X XR Z ZN ZTX + many others

PLEASE ASK FOR OUR FREE CD-ROM
(in Excel) STOCK LIST

We Stock a Massive Range of Components

Mail, phone, Fax Credit Card orders and callers welcome



Connect

Cricklewood Electronics Ltd

40-42 Cricklewood Broadway London NW2 3ET

Tel: 020 8452 0161 Fax: 020 8208 1441

Kit
Radio
Company

Unit 11, Marlborough Court, Westerham, Kent.
TN16 1EU

Mail Order Direct
Credit Cards, Cheques and
Postal Orders Welcome
P&P £4.00

TEL 01959 563023



KRC-1. A four-band superhet receiver built in five easy stages. Each completed stage works, as a receiver in its own right. The kit is supplied with pre punched and labeled case, hardware, coil pack, even batteries. Frequency coverage MW, 160, 80 and 40 meters. AM/CW and SSB.

£59.99 + P&P

KRC-2. Regeneration with a difference. Unlike most regenerative designs this regeneration is virtually unaffected by the receiver tuning or the antenna. Simple to build. Covers 1 to 30 MHz in three bands, with bandspread tuning. Kit includes care all hardware and batteries.

£59.99 + P&P



KRC-A-2 Restore that cherished valve portable with this solid-state replacement HT battery. Powered by six AAA cells it outputs 90 volts at up to 10mA. The inverter goes into 'sleep mode' when the receiver is turned off. The Eveready look-alike case and batteries are supplied as part of the kit.

£29.99 + P&P

KRC-C-1 Granddads crystal set. Re-creating the past. This kit employs a galena crystal and cats whisker, variometer for the tuning and high impedance earphone. Relive those early days of wireless construction with this kit.



Basic kit £39.99 + P&P

Cabinet top £9.99

Send SAE or visit our web site for full details of all our kits. <http://hometown.aol.co.uk/kitradioco/uk.htm>



DrDAQ Data Logger

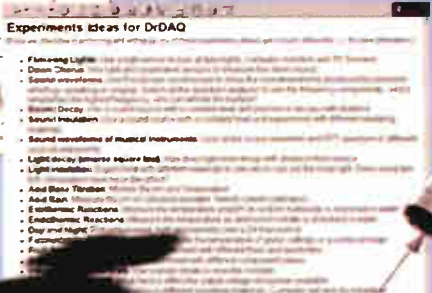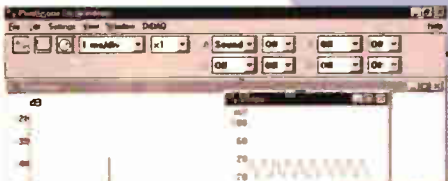


- Output
- Resistance
- Voltage
- Light level
- Temperature
- External sensors: Humidity
- Temperature
- O2 In Air
- Reed Switch

- Low cost - under £60
- Built in sensors for light, temperature and sound (level and waveforms)
- Use DrDAQ to capture fast signals
- Outputs for control experiments
- Supplied with both PicoScope (oscilloscope) and PicoLog (data logging) software

For more information on DrDAQ, please visit:

www.picotech.com/drdaq93

PC Oscilloscopes

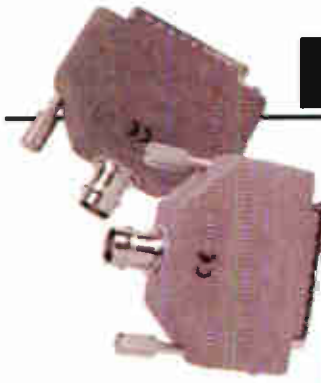

- Scope and spectrum analyser functions
- A fraction of the cost of benchtop scope
- Save multiple setups, for ease of use
- Save, print and e-mail your traces
- FREE technical support for life
- FREE software and upgrades
- Automated measurements

For more information on our scopes, please visit:

www.picotech.com/scope164

Tel: 01480 396395 Fax: 01480 396296 E-mail: sales@picotech.com

PICO
Technology Limited

PIC N' MIX ANDREW JARVIS

Our periodic column for your PIC programming enlightenment

A potted history of EPE Toolkit and an overview of other low cost programmers

EVERYBODY seems to be programming these days. Not too long ago it was largely professors and engineers who were the most active in the field, but times change. With all this Internet activity it's no surprise that Visual Basic is so popular, being a natural progression from HTML and scripting, and it's great that so many people are willing to attempt PIC programming despite it being perceived as a little further up the learning curve.

If you're one of them, then know that embedded development is certainly different to the PC world you might be used to, but not much harder. It just requires a slightly different approach and a little more patience with the tools and the debugging. All you need to get started is a low cost programmer and some software to drive it. Before you know it you'll be quoting your age in hexadecimal and laughing at binary jokes.

GREAT HEXPECTATIONS

A low cost programmer in this context isn't somebody who will write your application code for you on the cheap, it's the tool you need to put the PIC into programming mode and get your code out of the PC and down onto the device. There are various ways to do this, but most solutions usually boil down to two important parts – the hardware that you plug your PIC into, and the software that you run on your computer to move the code around and view the result.

Hardware can range from "zero parts" (but usually at least a single resistor) to feature rich development boards; software from the full IDE (integrated development environment) with integrated compiler/assembler to simple download utilities. In many cases the software and hardware component parts are interchangeable, something we'll demonstrate with the EPE Toolkit TK3 programming system in the coming months. Over time, you will come to love your chosen arrangement like a favourite pair of slippers, and find it equally comforting as the midnight oil burns away.

If you ever Google the net on this subject, it's difficult to avoid reference to what are popularly known as "Tait" style programmers. This has become a catch-all phrase for simple parallel port designs like the early EPE projects, named after the internet publication of David Tait's classic 16C84 programmer with associated FAQ/links pages. Definitely worth reading. (Unfortunately, they are no longer updated and have been removed from their original home, but they are still possible to locate quite easily – try the *piclist* www.piclist.com for starters).

STARTER FOR 1010

It was Derren Crome who introduced the first PIC programmer to EPE (*Simple PIC16C84 Programmer*) in February '96. Based on DOS, it required only a few components (in addition to a PSU) and used shareware assembly language and programming software. John Becker then created the original EPE PIC Tutorial, published between March and May '98, and later what would become the Toolkit series of programmers, in response to the thousands of queries asking how to program PICs.

was the result, published in October and November 2001 and with several updates since then. The rest, as they say, is history.


Of course, there are lots of other DIY programmers out there – each with their own set of passionate enthusiasts. If you want to build your own you should certainly consider them, but remember to compare like with like when you look around. Cost, support and quality vary enormously.

Something to bear in mind if you decide to build a "Tait" style programmer is the ultimate disappearance of the PC parallel port in favour of USB and Firewire. You might find your pride and joy sidelined when you next upgrade the PC! There are other issues as well with software that writes directly to the parallel port being unsupported by some Windows versions (notably 2000 and XP) – but workarounds for this are well publicised.

WOULD YOU LIKE THAT WRAPPED?

Despite the hobbyist in you no doubt suggesting that there is no alternative to building a DIY programmer, you might reasonably ask yourself if you have time to be bothered with the maintenance they sometimes bring – particularly if it is just a means to an end and all you really want is the programmed PIC in your circuit with little regard for how it gets there. Perhaps you just want to be able to send it back if it goes wrong, or be sure that if your code isn't working, you don't spend hours debugging the debugger. If you don't want to customise the hardware or tinker with the software, there are some good shrink-wrapped alternatives.

Microchip's entry-level programmer is the affordable PICkit 1. This is a particularly interesting example because you can read all about it from application note AN258, including how it was designed and put together around the USB enabled PIC16C745. In addition, you can download the firmware for this PIC and the Visual Basic source code for the GUI. If you get the user's guide (40051c.pdf) as well, you'll even get the circuit diagram, which doesn't leave

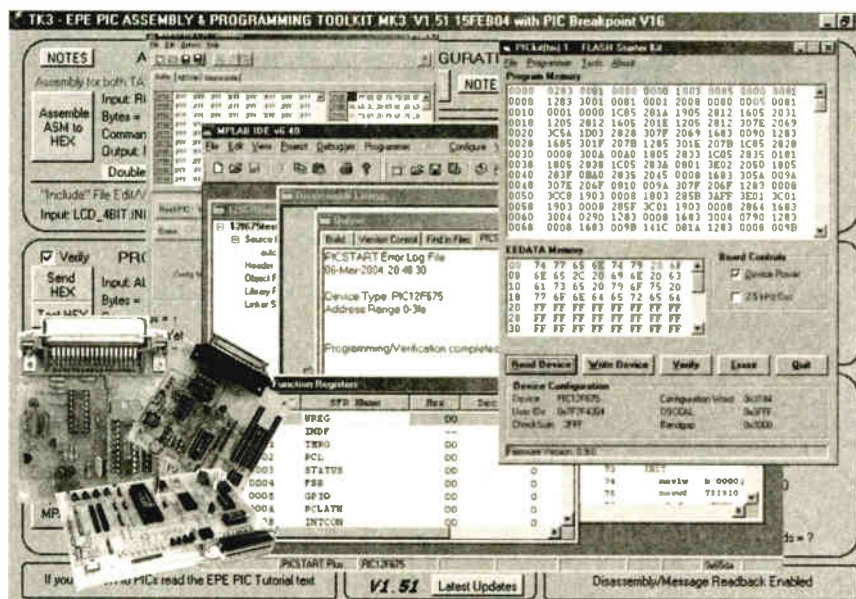

Toolkit Mk1 appeared in July '98, with its own assembly and programming software. Toolkit Mk2 was published in May and June of '99 following the introduction of PIC16F87x devices, which it could handle in addition to the PIC16x84. Also in this release were disassembly, verification and the ability to read/write the PIC's EEPROM. Visual Basic then created an opportunity to add lots of new features not possible with Mk2, and the popular TK3

level programmer is the affordable PICkit 1. This is a particularly interesting example because you can read all about it from application note AN258, including how it was designed and put together around the USB enabled PIC16C745. In addition, you can download the firmware for this PIC and the Visual Basic source code for the GUI. If you get the user's guide (40051c.pdf) as well, you'll even get the circuit diagram, which doesn't leave

much else left to understand about it. The only down side is that PICKit 1 is very limited, supporting just the 8-pin and 14-pin flash families.

If you think that you and PICs will become inseparable, then your choice should be flexible enough to grow with you as new devices become available. Although certainly not "low cost", Microchip's PICSTART Plus development programmer sets the pace here, supporting most DIP packaged devices as they become available. The firmware for it is flash upgradeable and reprogrammed directly from the MPLAB IDE at no extra cost (but you need hardware revision R20 or later for this feature – if you're thinking of buying a new one be sure to ask).

Interestingly, some third party programmers claim compatibility with PICSTART Plus, and therefore MPLAB for a much-reduced price. The Warp-13 from Newfound Electronics is one example I found listed that you can apparently use from the Microchip IDE or its own proprietary GUI. You might find others – search

through the third party developer tools (www.microchip.com/1010/pline/tools/tparty/index.htm).

I'm curious to know how these are kept in sync with the firmware versions and/or protocol revisions expected by the IDE. Unlike the PICKit 1, I could find no "official" source for the PICSTART Plus protocol. Other programmers that crop up regularly include the PICALL and P16PRO from Quasar Electronics and the EPIC from RF Solutions, but there are hundreds more, like those from Forest Electronic Developments – have a good look around.

KICKSTART DEVELOPMENT

Some PICs can program themselves, with the help of a bootloader (a small program already resident on the chip that the PC talks to). This is what the PICAXE system does. If you can't make a decision about a programmer, or you're not sure if PICs are for you, then consider this a gentler introduction and one that eliminates the problem while you decide.

PICAXE microcontrollers receive your code using a direct serial link from the PC. All the software you need to create the program is free so it's easy to get started, but note that your choice of PIC is limited and some pins or features that you need may be unavailable. You can get them from the Revolution Education website www.rev-ed.co.uk, and they featured in a series of projects presented in *EPE* Nov '02 to Jan '03. They are also featuring in the current *Teach In 2004* series.

PIC RESOURCES

The published texts and software for the *EPE PIC Tutorial V2* and *EPE PIC Toolkit TK3* programmer, are available on the *PIC Resources V2* CD-ROM, available from the Editorial address for £14.95 inclusive.

NEXT TIME

In the next issue Andrew examines "Hello World" for PICs – how to flash an i.e.d. using timing loops, analysing instruction cycles and their timing with respect to delays – a subject dear to many reader's inquisitive appetites!

SHOP TALK

with David Barrington

Body Detector

Regarding components for the *Body Detector* project, the author advises us that, "if possible, capacitors C1 and C3 should have a zero temperature coefficient or NPO (0 ppm/°C)". In other words – you need low loss, close tolerance and high stability types, as used for temperature compensation in tuned circuits.

A miniature zero-rated temperature coefficient capacitor of the required 4-7pF value is currently listed by **Rapid Electronics** (☎ 01206 751166 or www.rapidelectronics.co.uk) under their low-k ceramic plate range, code 08-1206, and by **Squires** (☎ 01243 842424 or www.squirestools.com), code 540-025. We also notice that **RS Components** (☎ 01536 444079 or rswww.com – credit card only) list a 10pF sub-min., zero rated, ceramic plate capacitor, code 126-809. Although this is double the value specified, the author indicates this would be OK in this circuit. Alternatively, two could be wired in series to give the required value of 5pF. However, we would point out that RS have a minimum order quantity on this range of 10.

The 12V d.c. coil, d.i.l. relay used in the model is a miniature Telecom TX series type with integral diode to reduce back-e.m.f. It has two sets of changeover contacts, which are rated 60W (2A/30V d.c.) maximum. This relay was purchased from RS, code 178-1924. You can, of course, use a different relay, with contact ratings to suit your application, but you will need to check its pinout against the p.c.b. arrangement.

The small printed circuit board is available from the *EPE PCB Service*, code 449 (see page 431).

MIDI Synchronome

Nearly all of the components to construct the *MIDI Synchronome* project should be widely available. The 6N139 Darlington opto-isolator is listed by **Cricklewood Electronics** (☎ 0208 452 0161), code as type number, and **Squires** (☎ 01243 842424 or www.squirestools.com), code 622-075.

The software is available on a 3.5in. PC-compatible disk (Disk 7) from the *EPE Editorial Office* for the sum of £3 each (UK), to cover admin costs (for overseas charges see page 431). It is also available for *Free* download from the *EPE* website, accessible via the Downloads click-link on our home page at www.epemag.wimborne.co.uk (path **PICs/MIDIsynchronome**).

For those readers unable to program their own PICs, a ready-programmed PIC16F627 microcontroller can be purchased directly from the author for the sum of £5.00 each inclusive (add £1 for overseas). Orders should be sent to **David Clark, PO Box 3103, Sheffield, South Yorks, S11 7WW**. Payments should be made out to *David Clark*, in £ sterling only and drawn on a British bank, UK postal orders are also accepted.

You will need to purchase a fairly large "expensive" piece of stripboard and cut it down to size. However, looking at the component layout diagram, there appears to be plenty of "space-saving" room to reduce its size and cost quite considerably.

PIC QuickStep

The low-profile conductive plastic type potentiometer used in the *QuickStep* project is one listed for p.c.b. mounting, via a mounting bracket, and came from **Rapid Electronics** (☎ 01206 751166 or www.rapidelectronics.co.uk), code 68-1504. You can, of course, use a standard miniature, p.c.b. mounting, rotary carbon type in its place. They also supplied the single row 2.54mm jumper links and p.c.b. header plugs.

Some readers may experience difficulties in finding the Zetec ZTX653 2A npn transistor. It is certainly listed by **Cricklewood** (☎ 0208 452 0161), code as type number, and **Squires** (☎ 01243 842424 or www.squirestools.com), code 710-540.

For those readers unable to program their own PICs, preprogrammed PIC16F628 microcontrollers (two separately programmed – as a pair) can be purchased from **Magenta Electronics** (☎ 01283 565435 or www.magenta2000.co.uk) for the inclusive price of £9.80 each pair (overseas add £1 p&p). The software is available on a 3.5in. PC-compatible disk (Disk 7) from the *EPE Editorial Office* for the sum of £3 each (UK), to cover admin costs (for overseas charges see page 431). It is also available *Free* via the Downloads click-link option on the *EPE* home page when you enter our main web site at www.epemag.wimborne.co.uk (take path **PICs/QuickStep**).

The printed circuit board is available from the *EPE PCB Service*, code 448 (see page 431). Incidentally, if you are looking for a low-voltage stepper motor you might like to investigate the ones stocked by **Magenta** (see above and their advertisement).

Crafty Cooling

During our search for possible parts for the "experimental" *Crafty Cooling* project, we were pleased to find the following information regarding the supply of Peltier modules. Before you purchase a module, check that it is a "factory" sealed unit – see text.

Our regular advertiser **Bull Group** (☎ 0870 7707520 or www.bullnet.co.uk) has an interesting picture and details, including a manual, for a Peltier module – see inside front cover. Likewise, **Greenweld Ltd** (☎ 01277 811042 or www.greenweld.co.uk) currently stock two types: a 17W device, code CDT0098, and a 33W module, code CDT0255. They are listed on their new web site at: www.sciencestore.co.uk. They are also able to supply heatsinks and cooling fans.

No doubt readers should be able to select a suitable 12V fan from the many sold for cooling computer power supplies or microprocessor i.c.s.

Finally, it is impossible to say how quickly the "cooler" will cool the drink, but, unless you are desperate for a drink, time will not be a major factor. To give an idea, the prototype takes less than an hour.

Teach-In '04 – Part 8

Readers wishing to experiment with the PIC-controlled *Movement Detector* (Fig.8.11), part of this month's *Teach-In '04* instalment, a pre-programmed PIC microcontroller can be obtained from **Max Horsey, Electronics Dept., Radley College, Abingdon, Oxon OX14 2HR**, for the sum of £5 per PIC, including postage. Specify that the PIC is for *Teach-In 2004 Part 8, Fig.8.11*. Enclose a cheque payable to **Radley College**.

The software for the PIC program (except for the PICAXE programming software) is available on a 3.5in. disk (Disk 7) from the *EPE Editorial Office* for the sum of £3 each (UK), see page 431 for overseas charges. It is also available for *Free* download via the click-link option on the *EPE* home page at www.epemag.wimborne.co.uk; enter the PIC microcontroller source codes folder and select *Teach-In 2004*.

PICAXE programming software can be obtained from: **Revolution Education, Dept. EPE, 4 Old Dairy Business Centre, Melcombe Road, Bath BA2 3LR** (☎ 01225 340563 or www.rev-ed.co.uk).


PLEASE TAKE NOTE

Toolkit TK3 Software Update

The latest version, in which minor changes have been made to the "PIC Breakpoint" facility, has been placed on the Downloads site.

EPE IS PLEASED TO BE ABLE TO OFFER YOU THESE ELECTRONICS CD-ROMS


ELECTRONICS PROJECTS

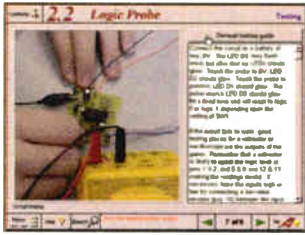

Logic Probe testing

Electronic Projects is split into two main sections: **Building Electronic Projects** contains comprehensive information about the components, tools and techniques used in developing projects from initial concept through to final circuit board production. Extensive use is made of video presentations showing soldering and construction techniques. The second section contains a set of ten projects for students to build, ranging from the simple sensor circuits through to power amplifiers. A shareware version of Matrix's CADPACK schematic capture, circuit simulation and p.c.b. design software is included. The projects on the CD-ROM are: Logic Probe; Light, Heat and Moisture Sensor; NE555 Timer; Egg Timer; Dice Machine; Bike Alarm; Stereo Mixer; Power Amplifier; Sound Activated Switch; Reaction Tester. Full parts lists, schematics and p.c.b. layouts are included on the CD-ROM.


ELECTRONICS CAD PACK

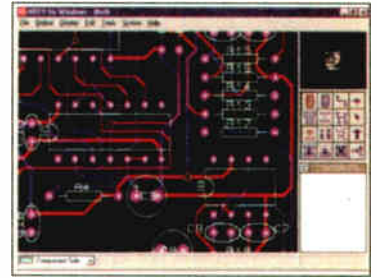

PCB Layout

Electronics CADPACK allows users to design complex circuit schematics, to view circuit animations using a unique SPICE-based simulation tool, and to design printed circuit boards. CADPACK is made up of three separate software modules. (These are restricted versions of the full Labcenter software.) **ISIS Lite** which provides full schematic drawing features including full control of drawing appearance, automatic wire routing, and over 6,000 parts. **PROSPICE Lite** (integrated into ISIS Lite) which uses unique animation to show the operation of any circuit with mouse-operated switches, pots, etc. The animation is compiled using a full mixed mode SPICE simulator. **ARES Lite** PCB layout software allows professional quality PCBs to be designed and includes advanced features such as 16-layer boards, SMT components, and an autorouter operating on user generated Net Lists.


ELECTRONIC CIRCUITS & COMPONENTS V2.0

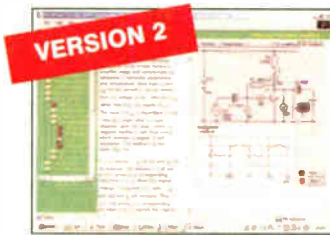

Circuit simulation screen

Provides an introduction to the principles and application of the most common types of electronic components and shows how they are used to form complete circuits. The virtual laboratories, worked examples and pre-designed circuits allow students to learn, experiment and check their understanding. Version 2 has been considerably expanded in almost every area following a review of major syllabuses (GCSE, GNVQ, A level and HNC). It also contains both European and American circuit symbols. Sections include: **Fundamentals**: units & multiples, electricity, electric circuits, alternating circuits. **Passive Components**: resistors, capacitors, inductors, transformers. **Semiconductors**: diodes, transistors, op.amps, logic gates. **Passive Circuits**. **Active Circuits**. **The Parts Gallery** will help students to recognise common electronic components and their corresponding symbols in circuit diagrams. Included in the Institutional Versions are multiple choice questions, exam style questions, fault finding virtual laboratories and investigations/worksheets.

ANALOGUE ELECTRONICS

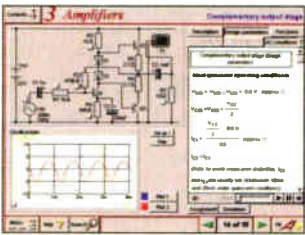

Complimentary output stage

Analogue Electronics is a complete learning resource for this most difficult branch of electronics. The CD-ROM includes a host of virtual laboratories, animations, diagrams, photographs and text as well as a SPICE electronic circuit simulator with over 50 pre-designed circuits. Sections on the CD-ROM include: **Fundamentals** – Analogue Signals (5 sections), Transistors (4 sections), Waveshaping Circuits (6 sections), **Op.Amps** – 17 sections covering everything from Symbols and Signal Connections to Differentiators. **Amplifiers** – Single Stage Amplifiers (8 sections), Multi-stage Amplifiers (3 sections), **Filters** – Passive Filters (10 sections), Phase Shifting Networks (4 sections), Active Filters (6 sections), **Oscillators** – 6 sections from Positive Feedback to Crystal Oscillators. **Systems** – 12 sections from Audio Pre-Amplifiers to 8-Bit ADC plus a gallery showing representative p.c.b. photos.

ROBOTICS & MECHATRONICS




Case study of the Milford Instruments Spider

Robotics and Mechatronics is designed to enable hobbyists/students with little previous experience of electronics to design and build electromechanical systems. The CD-ROM deals with all aspects of robotics from the control systems used, the transducers available, motors/actuators and the circuits to drive them. Case study material (including the NASA Mars Rover, the Milford Spider and the Furby) is used to show how practical robotic systems are designed. The result is a highly stimulating resource that will make learning, and building robotics and mechatronic systems easier. The Institutional versions have additional worksheets and multiple choice questions.

- Interactive Virtual Laboratories
- Little previous knowledge required
- Mathematics is kept to a minimum and all calculations are explained
- Clear circuit simulations


DIGITAL ELECTRONICS V2.0

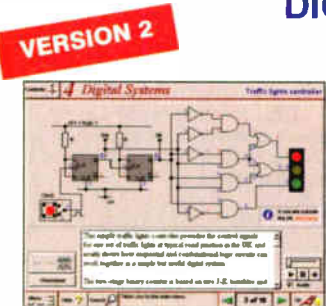

Virtual laboratory – Traffic Lights

Digital Electronics builds on the knowledge of logic gates covered in *Electronic Circuits & Components* (opposite), and takes users through the subject of digital electronics up to the operation and architecture of microprocessors. The virtual laboratories allow users to operate many circuits on screen. Covers binary and hexadecimal numbering systems, ASCII, basic logic gates, monostable action and circuits, and bistables – including JK and D-type flip-flops. Multiple gate circuits, equivalent logic functions and specialised logic functions. Introduces sequential logic including clocks and clock circuitry, counters, binary coded decimal and shift registers. A/D and D/A converters, traffic light controllers, memories and microprocessors – architecture, bus systems and their arithmetic logic units. Sections on Boolean Logic and Venn diagrams, displays and chip types have been expanded in Version 2 and new sections include shift registers, digital fault finding, programmable logic controllers, and microcontrollers and microprocessors. The Institutional versions now also include several types of assessment for supervisors, including worksheets, multiple choice tests, fault finding exercises and examination questions.

FILTERS

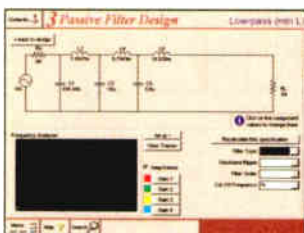

Filter synthesis

Filters is a complete course in designing active and passive filters that makes use of highly interactive virtual laboratories and simulations to explain how filters are designed. It is split into five chapters: **Revision** which provides underpinning knowledge required for those who need to design filters. **Filter Basics** which is a course in terminology and filter characterization, important classes of filter, filter order, filter impedance and impedance matching, and effects of different filter types. **Advanced Theory** which covers the use of filter tables, mathematics behind filter design, and an explanation of the design of active filters. **Passive Filter Design** which includes an expert system and filter synthesis tool for the design of low-pass, high-pass, band-pass, and band-stop Bessel, Butterworth and Chebyshev ladder filters. **Active Filter Design** which includes an expert system and filter synthesis tool for the design of low-pass, high-pass, band-pass, and band-stop Bessel, Butterworth and Chebyshev op.amp filters.

PRICES

Prices for each of the CD-ROMs above are:

(Order form on third page)

(UK and EU customers add VAT at 17.5% to "plus VAT" prices)

Hobbyist/Student£45 inc VAT
 Institutional (Schools/HE/FE/Industry).....£99 plus VAT
 Institutional 10 user (Network Licence)£199 plus VAT
 Site Licence.....£499 plus VAT

PICmicro TUTORIALS AND PROGRAMMING


HARDWARE

VERSION 2 PICmicro MCU DEVELOPMENT BOARD

Suitable for use with the three software packages listed below.

This flexible development board allows students to learn both how to program PICmicro microcontrollers as well as program a range of 8, 18, 28 and 40-pin devices. For experienced programmers all programming software is included in the PPP utility that comes with the development board. For those who want to learn, choose one or all of the packages below to use with the Development Board.

- Makes it easier to develop PICmicro projects
- Supports low cost Flash-programmable PICmicro devices
- Fully featured integrated displays – 13 individual I.e.d.s, quad 7-segment display and alphanumeric I.c.d. display
- Supports PICmicro microcontrollers with A/D converters
- Fully protected expansion bus for project work
- All inputs and outputs available on screw terminal connectors for easy connection

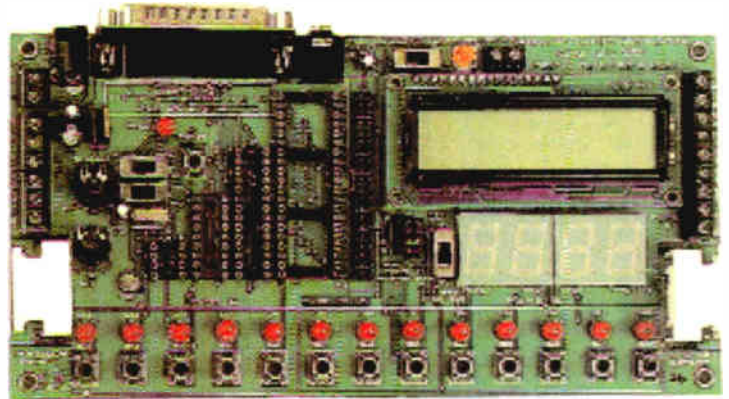

£145 including VAT and postage

12V 500mA plug-top PSU (UK plug) £7

25-way 'D' type connecting cable £5


SOFTWARE

Suitable for use with the Development Board shown above.

ASSEMBLY FOR PICmicro V2 (Formerly PICtutor)

Assembly for PICmicro microcontrollers V2.0 (previously known as PICtutor) by John Becker contains a complete course in programming the PIC16F84 PICmicro microcontroller from Arizona Microchip. It starts with fundamental concepts and extends up to complex programs including watchdog timers, interrupts and sleep modes. The CD makes use of the latest simulation techniques which provide a superb tool for learning: the Virtual PICmicro microcontroller. This is a simulation tool that allows users to write and execute MPASM assembler code for the PIC16F84 microcontroller on-screen. Using this you can actually see what happens inside the PICmicro MCU as each instruction is executed which enhances understanding.

- Comprehensive instruction through 39 tutorial sections
- Includes Vlab, a Virtual PICmicro microcontroller: a fully functioning simulator
- Tests, exercises and projects covering a wide range of PICmicro MCU applications
- Includes MPLAB assembler
- Visual representation of a PICmicro showing architecture and functions
- Expert system for code entry helps first time users
- Shows data flow and fetch execute cycle and has challenges (washing machine, lift, crossroads etc.)
- Imports MPASM files.

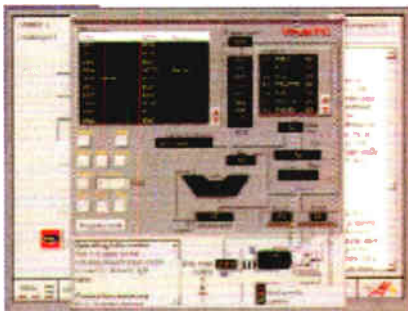


Virtual PICmicro

'C' FOR PICmicro VERSION 2

The C for PICmicro microcontrollers CD-ROM is designed for students and professionals who need to learn how to program embedded microcontrollers in C. The CD contains a course as well as all the software tools needed to create Hex code for a wide range of PICmicro devices – including a full C compiler for a wide range of PICmicro devices.

Although the course focuses on the use of the PICmicro microcontrollers, this CD-ROM will provide a good grounding in C programming for any microcontroller.

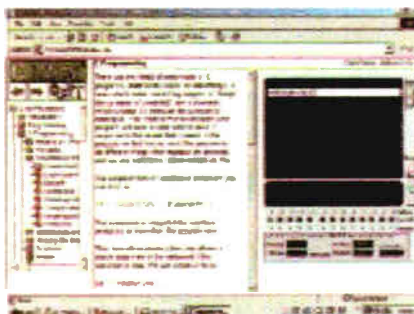- Complete course in C as well as C programming for PICmicro microcontrollers
- Highly interactive course
- Virtual C PICmicro improves understanding
- Includes a C compiler for a wide range of PICmicro devices
- Includes full Integrated Development Environment
- Includes MPLAB software
- Compatible with most PICmicro programmers
- Includes a compiler for all the PICmicro devices.



Minimum system requirements for these items: Pentium PC running Windows 98, NT, 2000, ME, XP; CD-ROM drive; 64MB RAM; 10MB hard disk space.

FLOWCODE FOR PICmicro

Flowcode is a very high level language programming system for PICmicro microcontrollers based on flowcharts. Flowcode allows you to design and simulate complex robotics and control systems in a matter of minutes.

Flowcode is a powerful language that uses macros to facilitate the control of complex devices like 7-segment displays, motor controllers and I.c.d. displays. The use of macros allows you to control these electronic devices without getting bogged down in understanding the programming involved.

Flowcode produces MPASM code which is compatible with virtually all PICmicro programmers. When used in conjunction with the Version 2 development board this provides a seamless solution that allows you to program chips in minutes.

- Requires no programming experience
- Allows complex PICmicro applications to be designed quickly
- Uses international standard flow chart symbols (ISO5807)
- Full on-screen simulation allows debugging and speeds up the development process
- Facilitates learning via a full suite of demonstration tutorials
- Produces ASM code for a range of 8, 18, 28 and 40-pin devices
- Institutional versions include virtual systems (burglar alarms, car parks etc.).



Burglar Alarm Simulation

PRICES

Prices for each of the CD-ROMs above are:

(Order form on next page)


(UK and EU customers add VAT at 17.5% to "plus VAT" prices)

Hobbyist/Student
Institutional (Schools/HE/FE/Industry)
Flowcode Institutional
Institutional 10 user (Network Licence)
Site Licence

£45 Inc VAT
£99 plus VAT
£70 plus VAT
£249 plus VAT
£599 plus VAT


TEACH-IN 2000 – LEARN ELECTRONICS WITH EPE

EPE's own *Teach-In* CD-ROM, contains the full 12-part *Teach-In* series by John Becker in PDF form plus the *Teach-In* interactive software (Win 95, 98, ME and above) covering all aspects of the series. We have also added Alan Winstanley's highly acclaimed *Basic Soldering Guide* which is fully illustrated and which also includes *Desoldering*. The *Teach-In* series covers: Colour Codes and Resistors, Capacitors, Potentiometers, Sensor Resistors, Ohm's Law, Diodes and L.E.D.s, Waveforms, Frequency and Time, Logic Gates, Binary and Hex Logic, Op.amps, Comparators, Mixers, Audio and Sensor Amplifiers, Transistors, Transformers and Rectifiers, Voltage Regulation, Integration, Differentiation, 7-segment Displays, L.C.D.s, Digital-to-Analogue. Each part has an associated practical section and the series includes a simple PC interface (Win 95, 98, ME ONLY) so you can use your PC as a basic oscilloscope with the various circuits.

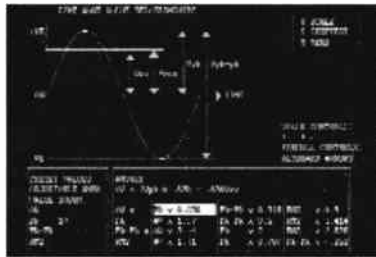

Sine wave relationship values


FREE BOOK WITH TEACH-IN 2000 CD-ROM

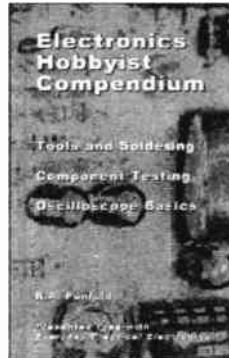

A hands-on approach to electronics with numerous breadboard circuits to try out. £12.45 including VAT and postage. Requires Adobe Acrobat (available free from the Internet – www.adobe.com/acrobat).

FREE WITH EACH TEACH-IN CD-ROM – Electronics Hobbyist Compendium 80-page book by Robert Penfold. Covers Tools For The Job; Component Testing; Oscilloscope Basics.

DIGITAL WORKS 3.0

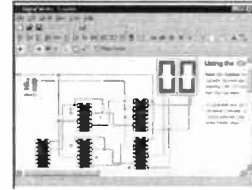

Counter project

Digital Works Version 3.0 is a graphical design tool that enables you to construct digital logic circuits and analyze their behaviour. It is so simple to use that it will take you less than 10 minutes to make your first digital design. It is so powerful that you will never outgrow its capability ● Software for simulating digital logic circuits ● Create your own macros – highly scalable ● Create your own circuits, components, and i.c.s ● Easy-to-use digital interface ● Animation brings circuits to life ● Vast library of logic macros and 74 series i.c.s with data sheets ● Powerful tool for designing and learning. **Hobbyist/Student £45 inc. VAT. Institutional £99 plus VAT. Institutional 10 user £199 plus VAT. Site Licence £499 plus VAT.**

ELECTRONICS IN CONTROL

Two colourful animated courses for students on one CD-ROM. These cover Key Stage 3 and GCSE syllabuses. **Key Stage 3:** A pictorial look at the Electronics section featuring animations and video clips. Provides an ideal introduction or revision guide, including multi-choice questions with feedback. **GCSE:** Aimed at the Electronics in many Design & Technology courses, it covers many sections of GCSE Electronics. Provides an ideal revision guide with Homework Questions on each chapter. Worked answers with an access code are provided on a special website.

Single User £29 inc. VAT. Multiple User £39 plus VAT
Student copies (available only with a multiple user copy) £6 plus VAT
 (UK and EU customers add VAT at 17.5% to "plus VAT" prices)

MODULAR CIRCUIT DESIGN

Contains a range of tried and tested analogue and digital circuit modules, together with the knowledge to use and interface them. Thus allowing anyone with a basic understanding of circuit symbols to design and build their own projects. **Version 3** includes data and circuit modules for a range of popular PICs; includes PICAXE circuits, the system which enables a PIC to be programmed without a programmer, and without removing it from the circuit. Shows where to obtain free software downloads to enable BASIC programming. Essential information for anyone undertaking GCSE or "A" level electronics or technology and for hobbyists who want to get to grips with project design. Over seventy different Input, Processor and Output modules are illustrated and fully described, together with detailed information on construction, fault finding and components, including circuit symbols, pinouts, power supplies, decoupling etc.

Single User £19.95 inc. VAT. Multiple User £34 plus VAT
 (UK and EU customers add VAT at 17.5% to "plus VAT" prices)

ELECTRONIC COMPONENTS PHOTOS

A high quality selection of over 200 JPG images of electronic components. This selection of high resolution photos can be used to enhance projects and presentations or to help with training and educational material. They are royalty free for use in commercial or personal printed projects, and can also be used royalty free in books, catalogues, magazine articles as well as worldwide web pages (subject to restrictions – see licence for full details). Also contains a **FREE** 30-day evaluation of Paint Shop Pro 6 – Paint Shop Pro image editing tips and on-line help included!



Price £19.95 inc. VAT

Minimum system requirements for these CD-ROMs: Pentium PC, CD-ROM drive, 32MB RAM, 10MB hard disk space. Windows 95/98/NT/2000/ME/XP, mouse, sound card, web browser.

Please send me:

CD-ROM ORDER FORM

- Electronic Projects
- Electronic Circuits & Components V2.0
- Analogue Electronics
- Digital Electronics V2.0
- Filters
- Electronics CAD Pack
- Robotics & Mechatronics
- Assembler for PICmicro
- 'C' for PICmicro
- Flowcode for PICmicro
- Digital Works 3.0

- Version required:
- Hobbyist/Student
 - Institutional
 - Institutional 10 user
 - Site licence



- PICmicro Development Board (hardware)
- Development Board UK plugtop power supply
- Development Board 25-way connecting lead

- Teach-In 2000 + FREE BOOK
- Electronic Components Photos
- Electronics In Control – Single User
- Electronics In Control – Multiple User
- Modular Circuit Design – Single User
- Modular Circuit Design – Multiple User

Note: The software on each version is the same, only the licence for use varies.

Full name:

Address:

.....Post code:Tel. No:

Signature:

I enclose cheque/PO in £ sterling payable to WIMBORNE PUBLISHING LTD for £

Please charge my Visa/Mastercard/Amex/Diners Club/Switch: £

Valid From:Card expiry date:

Card No:Switch Issue No.

Card Security Code (The last 3 digits on or just under the signature strip)

ORDERING

ALL PRICES INCLUDE UK POSTAGE

Student/Single User/Standard Version price includes postage to most countries in the world
EU residents outside the UK add £5 for airmail postage per order

Institutional, Multiple User and Deluxe Versions – overseas readers add £5 to the basic price of each order for airmail postage (do not add VAT unless you live in an EU (European Union) country, then add 17½% VAT or provide your official VAT registration number).

Send your order to:

**Direct Book Service
 Wimborne Publishing Ltd
 408 Wimborne Road East
 Ferndown, Dorset BH22 9ND**

To order by phone ring

01202 873872. Fax: 01202 874562

Goods are normally sent within seven days

E-mail: orders@wimborne.co.uk


Online shop:

www.epemag.wimborne.co.uk/shopdoor.htm

SURFING THE INTERNET

NET WORK

ALAN WINSTANLEY

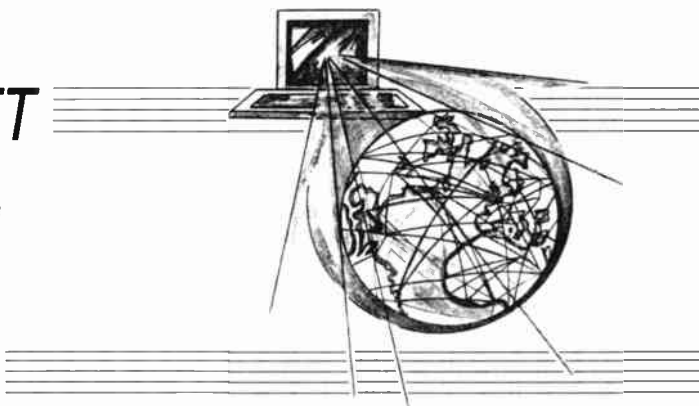

MOST internet users have a favourite search engine to help pinpoint information of some sort or other: when we wanted to know about the National LM12 power op.amp, all we needed to do was "google" directly to the PDF data sheet, an action performed with Google's usual speed (< 1 second) and efficiency (no. 1 link). Much better than agonising over the accuracy of data and pinouts drawn in mail order catalogues!

Alta Vista

When Google was just a minor beta product and the web was many magnitudes smaller, many 'net enthusiasts cut their search engine teeth on Yahoo! (www.yahoo.com) or Alta Vista (www.altavista.com). The latter started life as Digital Equipment Corporation's fabulous demonstration of DEC computing power, before being hived off to Compaq: Alta Vista is now owned by Yahoo! Its results are very different from those shown by Google: Alta Vista's new slimmed-down interface failed our LM12 data sheet test completely. After floating the idea of free 0800 dial up access in the UK, a disaster that ended with the departure of Managing Director Andy Mitchell in 2000, it is a pity that Alta Vista seems to have all but disappeared from the UK mainstream user's search engine toolbox: most folks google instead.

Google (www.google.co.uk and other countries) is the ubiquitous engine that started life as a mathematical exercise intended to index the data available on a burgeoning world wide web. Google's clean bloat-free non-portal style proved popular and it became the largest "true" search engine in the world. It was even awarded the accolade of having a verb created in its honour (guilty, see above). Following a radical (and some say near-disastrous) re-indexing exercise earlier this year (known in the trade as doing the "Google Dance"), Google is going through a phase when many web sites that had previously featured well in its database have lowered or lost their rankings altogether.

For reasons that dismayed many web site owners, Google suddenly displayed search requests based on new criteria. A number of analytical web sites sprang up that highlighted the dramatic "before and after" (good and bad, respectively) effect that was seen after the rebuild. For the first quarter of 2004 there was near panic in many quarters, because many web site owners who relied on Google for trade suddenly found that they were invisible to inquisitive web users: only now are web site rankings and relevance improving again.

At one time, Google could do no wrong, but its most recent suggestion of free web-based email (dubbed *Gmail*) to rival Hotmail has been widely criticised, not least because of the suggestion that the contents of Gmails might be scanned by Google in search of keywords, which could then trigger some corresponding advertising mails. The fact that it may not be possible to delete ones' personal Gmail from the Google servers has also alarmed privacy groups considerably.

Google plays its financial cards close to its chest. With a widely-spectulated share-offering looming larger, the danger is that they may talk up its value and move away from its roots by adopting an altogether more commercial approach, so watch out for headline-grabbing announcements from Google in coming months.

MSN and Yahoo

MSN (www.msn.co.uk and other countries) is also one of the big three search engines and is often overlooked; it's the magnifying glass icon in the MSIE toolbar. It has some attractive features, including an interesting preview thumbnail image of web site home-pages. Just like Alta Vista, a search on MSN for "LM12" failed to deliver any links to National Semiconductor, not surprisingly as both

engines currently get their search engine results via Yahoo!'s Overture.com and Inktomi.com, yet another Yahoo! acquisition.

It has been all-change at Yahoo! and "Yahoogle" is no more: there can be no doubt that Yahoo! is now gunning for Google. Yahoo! has previously traded on its own directory of web sites and used Google to provide its "other results" – so that if a search for an LM12 drew a blank in Yahoo!'s directory, then there was at least a chance that Google could provide alternative links. Yahoo! has now dumped Google and is focusing on competing head-to-head with it instead. Yahoo! owns Alta Vista, Overture, FAST and Inktomi so there is a heavy focus on pay-per-click advertising services.

In summary, the top three search engines continue to be Google, Yahoo! and MSN. Google looks set to become more commercialised (watch out for an IPO – initial public offering – announcement, and more headline-grabbing news as Google's corporate machine swings into action). For general mainstream searching, the emphasis is shifting towards Yahoo! which is evidently gearing up to compete for the top slot. Third place goes to MSN, the default search engine found in MSIE.

Next month I'll be suggesting a fourth search engine that powers some other well-know search sites, and asking the question: did it pass our LM12 test? You can email comments to alan@epemag.demon.co.uk.



The Yahoo! portal web site offers plenty to do for everyday surfers.



The MSN search engine has a preview option to display small images of web pages.

TEACH-IN 2004

Part Eight – Movement Detection

MAX HORSEY



How to apply electronics meaningfully – the aim of this 10-part series is to show, experimentally, how electronic components function as part of circuits and systems, demonstrating how each part of a circuit can be understood and tested, and offering advice about choosing components

MOVEMENT detection is the general heading for this month's *Teach-In*. It is a term which has many interpretations. Here we shall first place the emphasis on detecting whether or not a specific signal is being generated. We touched on this last month when briefly examining the concept of missing pulse detection.

In the example given, the pulse was that output periodically by a radio transmitter as an indication that it was working. If the signal was picked up by the receiver, this confirmed that the receiver was also working. If neither was true, i.e. the required pulse was missing, then a fault condition was signalled.

The classic use of a missing pulse detector is in heart beat monitoring. If the time between two consecutive heart beats is longer than permitted by the circuit, an alarm sounds.

There are many other applications. For example, you may have an alarm system in a shed or garage linked to your house via a pair of radio modules (discussed in Part 7). If you send a continuous radio message to indicate that all is well, you will be jamming all other devices on the same radio frequency. If you send a radio signal only when the alarm is triggered, you will have no way of knowing that the radio link is actually working.

The solution, as we outlined last month, is to send a short radio signal at intervals. Your receiving circuit is then programmed to look for the regular signal, and if no signal is received, the alarm is sounded.

Systems such as heart beat monitors, or the DVT (Deep Vein Thrombosis) warning system we discuss later, rely on pulses generated by your body, or generated by movement. But some systems (e.g. radio linked alarms) need an electronically generated pulse, and so we will begin by examining circuits designed to generate regular pulses.

ASTABLES

We first examined astables in Part 4 when discussing logic gates. Last month we illustrated a practical use for a logic

gate astable, employing it as the transmitter control device. Astables can also be constructed using a pair of transistors as shown in Fig.8.1.

If two bulbs, LP1 and LP2, are employed (e.g. 6V torch bulbs) then the transistors should be *npn* Darlington types, such as the TIP122. If i.e.d.s (with series resistors of say 330Ω) are employed then any pair of high-gain *npn* transistors may be used.

A good starting point for the resistor/capacitor values is: $R1 = R2 = 10k\Omega$, and $C1 = C2 = 470\mu F$. Note that the capacitors are electrolytic and so the positive side of each must be the way round indicated. The supply voltage should match the bulbs used, so a 6V supply is ideal with the bulbs suggested. A photograph of the test circuit is shown in Photo 8.1

At power-on one transistor will turn-on faster than the other. We will assume it is TR1, and so bulb LP1 lights up. Hence point X will be at 0V. Any sudden change of voltage is transferred across a capacitor, C1 in this case, and so the base (b) of TR2 will be at 0V, keeping TR2 switched off. Hence the voltage at point Y will be at 6V, and the base of TR1 will remain positive enough to keep it switched on.

Since the upper side of resistor R1 is at 6V, and its lower side is at 0V, current will flow through it and into capacitor C1, which

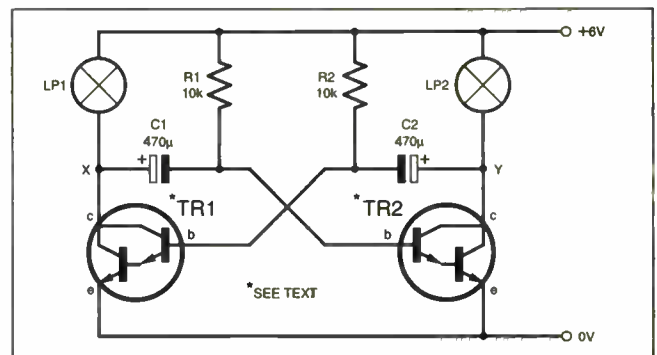


Fig.8.1. An astable (oscillator) formed around two Darlington transistors.

will charge up accordingly. (You may notice that C1 will become charged with its polarity the wrong way round, but it will only be for a short time, with a maximum reverse differential of only about 1.4V, the turn-on voltage at the base of transistor TR1.)

After an interval, the base of TR2 will become positive enough for this transistor to switch on. Now bulb LP2 will light, and point Y will fall to 0V. This sudden change will transfer across to capacitor C2, hence switching off TR1 and its bulb, LP1.

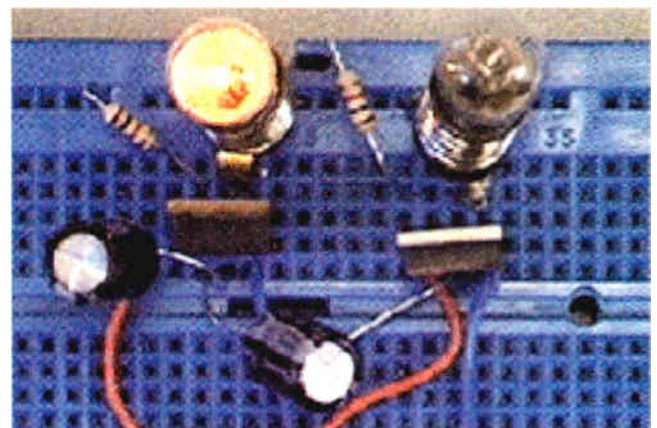


Photo 8.1. Breadboard layout of the circuit in Fig.8.1.

Current will now flow through resistor R2, slowly charging C2 until the circuit reverts to its original state. Note that the values of R1 and C1 determine the time for which lamp LP1 is lit, and R2 and C2 control the time for which LP2 is lit.

MARK/SPACE RATIO

Using the values indicated earlier, the mark/space ratio will be equal. The concept of mark/space ratio was explained last month in Part 7. Fig.8.2a illustrates the voltage at point Y with the component values suggested earlier. The voltage at point X will be similar but the exact opposite of that at point Y.

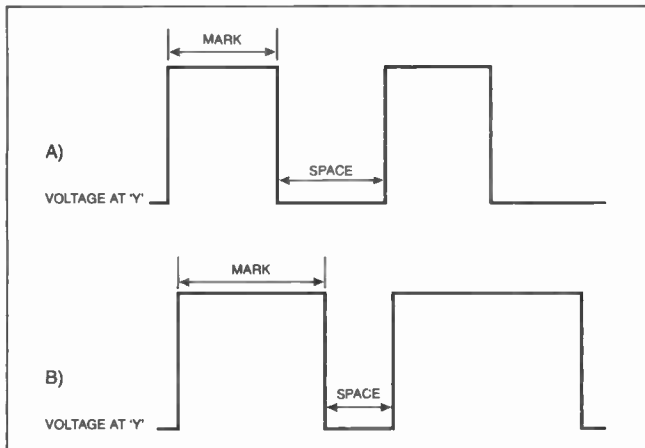


Fig.8.2. Illustrating the waveforms generated by the circuit in Fig.8.1.

Now if resistor R2 is reduced in value to, say, 4.7kΩ then LP2 will be lit for a shorter time than LP1, and so the voltage at Y will remain positive for longer, as shown in Fig.8.2b. The mark/space ratio is about 2:1.

WARNING: Do not reduce the value of either resistor to less than 1kΩ or you may damage the transistor. If you use values greater than 10kΩ, you may find that the transistors fail to switch on. It may be safer to experiment with the values of the capacitors since a wide range of values may be safely employed.

The circuit is simple, though crude. Even if the bulbs are replaced with resistors, it is quite current-hungry, and points X and Y do not switch cleanly between positive and 0V. But it illustrates the point, and can be fun, particularly if a loudspeaker or headphone (impedance 64Ω or more) is connected in place of one of the lamps. You should hear a clicking sound. Try reducing both capacitors to, say, 100nF in order to speed up the frequency by over 1000 times. You should hear a musical note, or at least the sound of a motor bike!

555 TIMER

Another very popular astable is that based on an i.c. known as a 555 Timer. Although other timers are available,

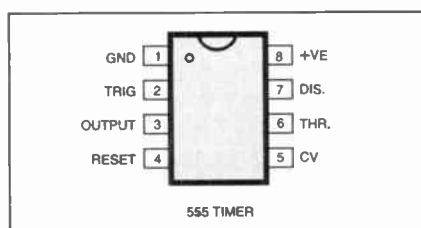


Fig.8.3. Pinouts for the 555 timer.

including the CMOS 7555 timer, the 555 remains common in project work, and still features in many electronics examination syllabuses. The pinouts for the 555 (and 7555) timer are shown in Fig.8.3.

The pin functions are:

1. GND. Power supply ground (0V)
2. TRIG. Triggers timing cycle when connected briefly to 0V
3. OUTPUT. Goes high during timing cycle
4. RESET. Resets the timer when connected to 0V
5. CV. Control voltage. Can be used to modulate the timer, but is normally connected via a small value capacitor to the 0V line, although it is often left unconnected
6. THR. Sets the threshold voltage at which the timer is reset
7. DIS. The pin through which the external timing capacitor is discharged
8. +VE. The positive power supply pin, with a voltage range of typically 4.5V to 16V

The output current that can be sunk or sourced is typically 100mA, but some variants can handle 200mA.

The 555 is manufactured by a number of companies and the type number will be prefixed by that manufacturer's code, e.g. NE555, LM555, TS555. A full datasheet for the National Semiconductor LM555 is available from www.national.com/DS/LM/LM555.pdf. This datasheet also gives application examples of how the 555 can be used in a variety of modes.

Pin 4 (reset) is negative-triggered. In other words, if pin 4 is made positive, it has no effect on the timer, but if pin 4 is briefly connected to 0V, the timer is reset. Pin 2 (trigger) is also triggered by a negative signal.

ASTABLE CIRCUIT

An example of how a 555 timer is employed in astable mode is shown in Fig.8.4. The purpose of the circuit is to make l.e.d. D1 flash on and off at a rate determined by the values of resistors R1, R2 and capacitor C1.

The control voltage (CV) input, pin 5, is not required and is left unconnected. Pin 4

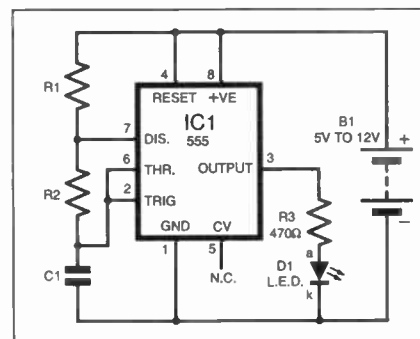


Fig.8.4. A 555 timer used in astable mode.

(reset) is connected to the positive line to allow the timer to operate (the opposite of reset mode).

At power-on, the voltage across capacitor C1 is at 0V, so holding low pins 6 and 7 (threshold and discharge). This causes the timer to start its timing cycle, during which output pin 3 is held high, causing l.e.d. D1 to turn on, buffered by resistor R3. Pin 7 (discharge) is internally disconnected by the i.c.

Current flows through resistors R1 and R2, charging up capacitor C1. Pin 6 monitors the voltage on C1 and when this reaches two-thirds of the supply voltage, the i.c. simultaneously resets output pin 3 low, and internally connects pin 7 to 0V. Current now flows back through R2, discharging the capacitor via pin 7. Pin 2 monitors this voltage, and at one-third of the supply voltage, output pin 3 switches high again, pin 7 disconnects internally, and the cycle repeats.

On a 12V supply, for example, capacitor C1 charges to 8V and discharges to 4V, oscillating between these levels. The capacitor charges via R1 and R2, but discharges via R2 alone. So for a given value of C1, the time for which pin 3 is high is determined by the total resistance of R1 + R2, but the time for which output pin 3 is low is determined only by R2. By changing the relative values of resistors R1 and R2, the mark/space ratio can be adjusted.

The oscilloscope waveforms in Photo 8.2 illustrate the behaviour of the timer during a timing cycle. The lower waveform is that at the junction of capacitor C1 and pins 2 and 6, and the upper is the output at pin 3.

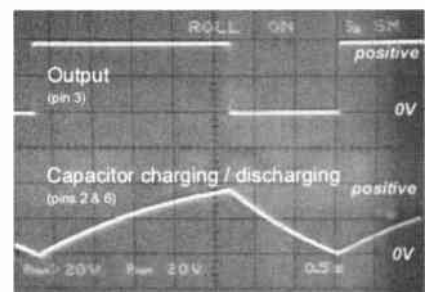


Photo 8.2. Waveforms for the circuit shown in Fig.8.4.

The time, T1, for which the output is high is given by:

$$T1 = 0.7 \times (R1 + R2) \times C1$$

The time, T2, for which the output is low is given by:

$$T2 = 0.7 \times R2 \times C1$$

Units must be in seconds, ohms and farads, or in seconds, MΩ and μF.

Notice that resistor R2 appears in both formulae; hence if you wish to obtain an almost equal mark/space ratio, make R2 large (e.g. 1MΩ) and R1 small (e.g. 1kΩ).

The circuit is ideal if you wish to obtain an unequal mark/space ratio, as is often required in "missing pulse" circuits. But note that in this simple arrangement, T1 (output high) is always longer than T2 (output low). If R1 and R2 are equal, then T1 will be twice T2 (look at the two equations to confirm this). If R1 is nine times the

value of R2 then the mark/space ratio will be 10:1.

CONSTRAINTS

For reliable operation, resistor values should be between $1k\Omega$ and $1M\Omega$. The capacitor value can be as small as necessary, but in this application values of $1\mu F$ and above will probably be needed to make the astable rate slow enough for the flashing of l.e.d. D1 to be obvious. If an electrolytic capacitor is used, ensure that it is the correct way round with its positive lead joined to resistor R2.

Electrolytic capacitors are quite inaccurate in value, and so do not expect your actual results to agree perfectly with your calculations. If accuracy is important, R2 could be a variable resistor, to allow precise setting. Also note that electrolytic capacitors tend to be "leaky" (i.e. not good insulators) and this will increase the actual timing period. In fact, with values of over $1000\mu F$, predictable results are quite difficult to achieve.

Longer and more accurate delays are generally achieved by employing an astable with a fairly high frequency, which allows the use of non-electrolytic (and hence more stable and reliable) capacitors to be used. The pulses from the astable are then output to a dividing circuit. The result can be a very accurately timed output.

555 MONOSTABLE

If a short pulse followed by a long gap is required, a monostable can be employed together with an astable. The mark/space ratio of the monostable is unimportant, and this simplifies the circuit design. Whenever the output of the astable switches from, say, 0V to positive, the monostable is triggered, and can be set to produce a single very short pulse.

Monostable circuits were looked at in Part 4, in which logic gates were used. The basic monostable arrangement using a 555 timer is shown in Fig.8.5. Resistor R1 can be any value from $1k\Omega$ to $1M\Omega$, its purpose is simply to keep pin 2 positive unless the switch (S1) is pressed. Resistor R2 (value R) together with capacitor C1 (value C) sets the period (T) for which the output is high, according to the formula:

$$T \text{ in seconds} = 1.1 \times R \times C$$

Again, R is in ohms and C in farads, although, as before, a useful shortcut is to measure R in $M\Omega$ and C in μF .

As in the astable circuit, an l.e.d., D1, shows the state of the output, and is buffered by resistor R3.

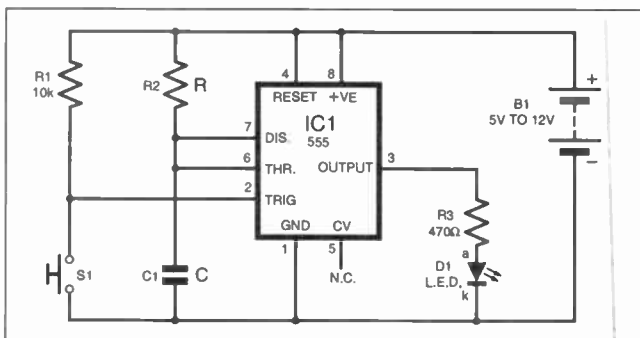


Fig.8.5. A 555 timer used in monostable mode.

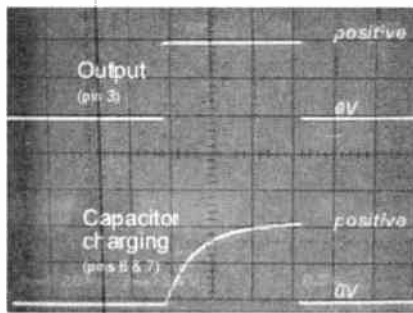


Photo 8.3. Waveforms for the circuit shown in Fig.8.5.

The oscilloscope photograph in Photo 8.3 shows the results obtained with the circuit in Fig.8.5. When the circuit is stable, output pin 3 is at 0V, and discharge pin 7 is internally connected to 0V. When trigger pin 2 is connected to 0V for a moment (e.g. by pressing switch S1), output pin 3 goes high, and the discharge pin internally disconnects itself. Hence current flows through resistor R2 and charges capacitor C1, as shown in the lower waveform. Threshold pin 6 monitors this rising voltage, and at two-thirds of the supply voltage, pin 3 switches back to 0V and pin 7 internally connects to 0V again.

CONSTRAINTS

As before, resistor values should be between $1k\Omega$ and $1M\Omega$, and rather unpredictable results will be obtained with capacitors greater than $1000\mu F$. Remember that if an electrolytic capacitor is used, its positive side should be connected to R2. In theory, the i.c. is capable of timings up to one hour, but in practice you will be lucky to achieve this, though you will at least win a gold-star for patience!

However, in our application, the monostable is required to provide a short pulse, and so testing should not be tedious. We will now show how to join the monostable and astable together.

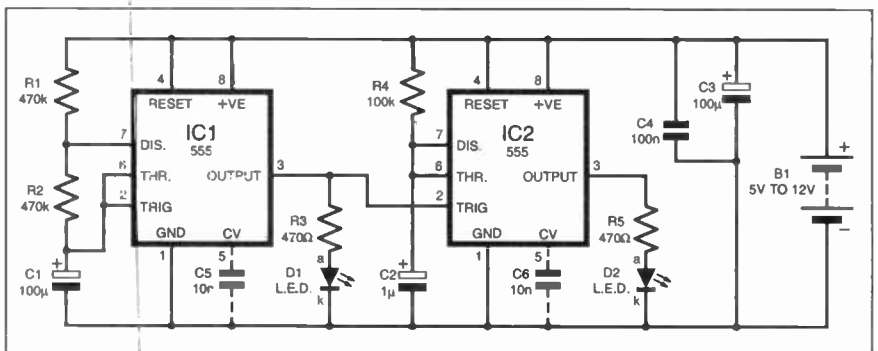


Fig.8.6. Combined astable and monostable circuit.

TIMED PULSES

As said before, the 555 timer requires a negative-going (0V) pulse at pin 2. Since the astable will be switching continuously between 0V and high and back to 0V, this is not a problem.

The combined astable-monostable

circuit is shown in Fig.8.6. We have retained the l.e.d.s, D1 and D2, to show that the circuit is working, but in practice they may not be required, in which case their series resistors (R3, R5) are also redundant. The values of resistors R1 and R2, and capacitor C1 will provide the following timings at IC1 pin 3:

$$\text{High} = 0.7 \times (0.47M\Omega + 0.47M\Omega) \times 100\mu F = 65.8 \text{ secs}$$

$$\text{Low} = 0.7 \times 0.47M\Omega \times 100\mu F = 32.9 \text{ secs}$$

$$\text{Hence total period (full cycle)} = 98.7 \text{ secs}$$

In other words, IC1 will supply a rising pulse (or falling pulse) approximately every 100 seconds. The rising pulse will be ignored by IC2, but the falling pulse will trigger the input (pin 2) of IC2. The values of R4 and C2 are chosen to provide the following time for a high pulse at IC2 pin 3:

$$\text{High} = 1.1 \times 0.1M\Omega \times 1\mu F = 0.11 \text{ secs}$$

So l.e.d. D2 will flash for about one-tenth of a second every 100 seconds, approximately.

POSSIBLE PROBLEMS

The 555 timer is very popular, but has some deficiencies, such as rather high current consumption (about 10mA) and the tendency to cause voltage spikes on the power lines every time its output switches high or low. These spikes can upset other devices. So, without preventative measures, you could find that IC2 might be triggered at the wrong times.

However, capacitors C3 and C4 across the power lines in Fig.8.6 help to provide a stable supply for the system. Pin 5 (CV) of each timer can also be decoupled beneficially by connecting 10nF capacitors (C5 and C6) between them and 0V.


If all else fails, the CMOS versions of the 555, such as the TLC555CP or

ICM7555, are much less troublesome in this respect, and can be directly substituted in this circuit. Also, consider using a dual-timer such as the NE556 (or the CMOS version ICM7556), which houses two timers in a single package, at virtually the same price.

A breadboarded test assembly of the circuit in Fig.8.6 is shown in Photo 8.4 (but excludes capacitors C4, C5 and C6).

DETECTING MISSING PULSES

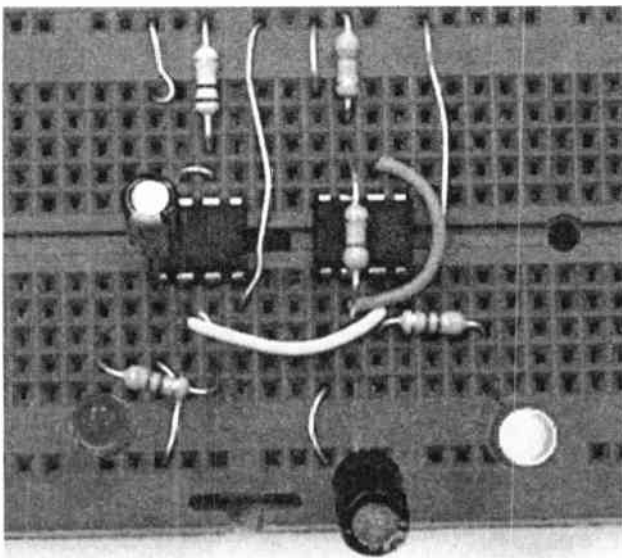We examined a basic missing pulse detector last month, but we will now



consider more elegant ways of achieving the same end. The principle is simple: make a timing circuit, but allow the pulse to reset the circuit before the timing cycle is complete.

A simple timer can be made using a single transistor, as shown in Fig.8.7. The transistor, TR1, can be any high gain *nnp* type, a Darlington-pair such as a TIP122 will offer slightly longer timings since its turn-on voltage is 1.4V rather than 0.7V for a "normal" bipolar transistor.

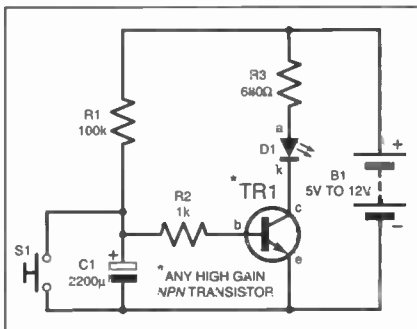


Fig.8.7. Single-transistor timing circuit.

When switch S1 is pressed, the voltage at the junction of resistors R1, R2 and capacitor C1 is pulled to 0V. Hence TR1 is turned off, and so too is l.e.d. D1. When the switch is released, current flowing through R1 will cause C1 to charge. This rising voltage will make TR1 turn on once it reaches the threshold of about 0.7V. The delay between releasing the switch and l.e.d. D1 lighting up will depend upon the values of R1 and C1.

If the switch is pressed at regular intervals, capacitor C1 will never charge sufficiently to turn on the transistor, and so l.e.d. D1 will never be turned on. When you stop pressing the switch, the circuit will then "time out", causing D1 to light.

This is the principle of classic heart-beat monitoring. Imagine your heart triggering a sensor just like pressing a switch; if your heart stops, the l.e.d., or a warning buzzer, will switch on.

DEFICIENCIES

Transistor TR1 turns on at about 0.7V, and even a large capacitor will quickly charge to this level. Hence the timed period will be quite short. If you try to increase the

value of resistor R1, there will come a point when insufficient current is available to switch on the transistor properly.

Using an *nnp* Darlington transistor instead of a normal bipolar type will help, because of its higher turn-on threshold of about 1.4V, but the method just described is presented to illustrate the principle, rather than provide a useful circuit. We could improve the circuit by adding more transistors, but there are other much better methods waiting in the wings.

RE-ENTER THE 555

The 555 in its monostable mode is ideally suited to this application, and the CMOS 7555 equivalent mentioned earlier will offer low current consumption as well. A possible arrangement is shown in Fig.8.8.


Transistor TR1 is a normal high-gain *pnp* type. This means that if the voltage on its base (b) is more positive than the voltage at its emitter (e) minus 0.7V, it will be turned off. In other words, for a 9V power supply, and with TR1's emitter held at 9V via resistor R3 and potentiometer VR1 (capacitor C1 fully charged), TR1 will only turn on if its base is at $9V - 0.7V = 8.3V$ approximately. If the base voltage is greater than 8.3V, TR1 will be turned off.

In Fig.8.8, TR1's base is normally held at 9V via resistors R1 and R2, and so it is turned off. If the signal input is briefly connected to 0V, the transistor will turn on and discharge capacitor C1. The 555 will also be triggered and will start the timing cycle.

Assuming that the input returns high almost immediately following it being taken low (i.e. just a short trigger pulse), the timing cycle will finish at the end of the set period, unless further 0V pulses are received at the input. Hence the output will remain high, indicating that "all is well", but if the pulses stop, the output will go low.

The values of capacitor C1, resistor R3 and potentiometer VR1, set the timing period, after which the alarm is raised. The purpose of using a variable resistor is so that the timing period can be adjusted; you could use a single resistor in place of R3/VR1 if preferred, as in previous circuits. However, a 1MΩ pot or preset for VR1 will provide a wide range of timings.

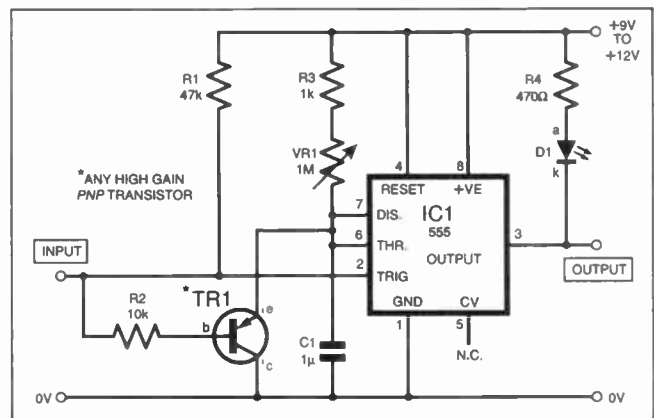Resistor R3 is needed in case VR1 is reduced to zero resistance, a condition that would cause a short-circuit via TR1.



Above: Fig.8.8. A missing pulse detector based on a 555 timer.

Left: Photo 8.4. Breadboard layout of the circuit in Fig.8.6.

Whilst in this area, some readers may wonder at the wisdom of discharging C1 directly through TR1. If in doubt, a resistor (say 100Ω) could be connected in series with the emitter of TR1, but this should not be necessary with smaller value capacitors e.g. 100µF or lower. For larger values of capacitance, the buffering resistor may be more essential to reduce the current flow, as was done in the circuit of Fig.7.12 last month (R5). The value of this resistor, though, will affect the rate at which C1 discharges.

NEGATIVE LOGIC

Note that "negative logic" applies in this circuit. In other words, the input looks for negative-going (0V) pulses, and the output is normally positive (high), but switches to 0V to signal an alarm condition (i.e. missing pulses). In this circuit, l.e.d. D1 indicates the alarm condition, turning on when IC1 output pin 3 goes low.

As mentioned earlier, the 555 timer tends to be upset by stray pulses in a circuit, and is rather prone to generating its own stray pulses. The CMOS version is much better in this respect, and if you wish to employ a buzzer at the output, you may have to use the CMOS version, or add capacitors (say 100nF) across the power lines to "soak up" the interference. The next missing pulse detector is far less prone to this type of interference.

DIGITALLY DETECTING PULSES

The circuit shown in Fig.8.9 employs four 2-input NOR gates as a missing pulse detector. The pin numbers are for a CMOS 4001B, and the circuit can be powered from a 5V to 12V supply. Gates from the CMOS 74HC series (i.e. 74HC02) will also work, but note that the pin numbers are different, and the supply must be between 4V and 6V.

At the heart of the circuit is a monostable, comprised of gates IC1a and IC1b. This type of monostable was described in detail in Part 4. The timing period is set by the values of capacitor C1 and resistor R2, according to the formula:

$$\text{Time in seconds} = 0.7 \times R \times C$$

By employing the usual shortcut of measuring R in MΩ and C in µF, the period set by the values shown in Fig.8.9 is

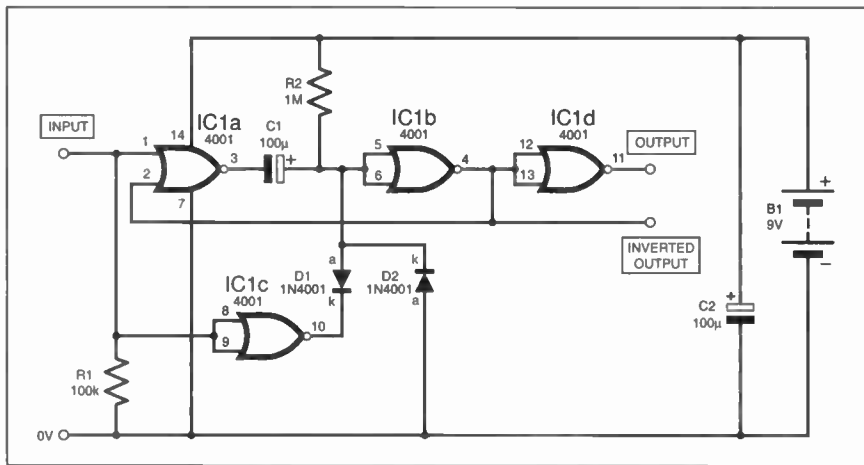


Fig.8.9. A missing pulse detector based on NOR gates.

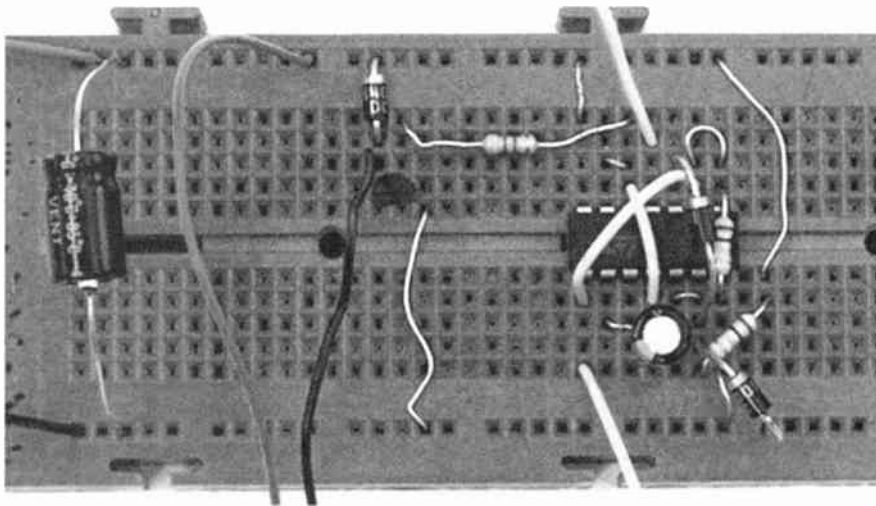


Photo 8.5. Breadboard layout of the circuit in Fig.8.9.

70 seconds. In practice, the timing is affected by the tolerance (accuracy) of the component values, and your electrolytic capacitor may well have a tolerance of 50%.

If a shorter period is required, the value of C1 (or R2) can be reduced, and if longer periods are needed, C1 can be increased. Note that it is unwise to use values greater than 1000µF and 1MΩ since electrical leakage through the capacitor will become a factor. If you require a variable period, a potentiometer can be used as a variable resistor. In this case it is wise to include a low-value (e.g. 1kΩ) fixed resistor in series with it as shown previously (Fig.8.8).

DETECTING PULSES

The pulse input at IC1a pin 1 is held at 0V by resistor R1, and so the output from IC1b pin 4 will also be at 0V (full details of the monostable are in Part 4), hence IC1d pin 11 will be high.

As described in Part 4, a positive-going pulse received at IC1a input pin 1 will cause IC1b pin 4 to go high, so setting IC1d pin 11 low. If another pulse is received in say 30 seconds, IC1c output pin 10 will go low, and current will flow via D1, discharging C1 in the process. Hence if the input is pulsed high, or remains high, IC1d output pin 11 will remain low.

If a pulse is *not* received at the input, then after 70 seconds (in this case) the output from pin 11 will go high again, indicating an alarm condition.

Diode D1 is needed to prevent IC1c pin 10 charging up the capacitor, and D2 is to prevent the input pins 5 and 6 going negative (i.e. below 0V) if pin 10 (or pin 3) switches to 0V when pins 5 and 6 are already at 0V. Although logic gates include built-in input protection diodes, D2 is there to reinforce the protection, just in case!

The output at IC1d pin 11 goes high to indicate an alarm condition. The "inverted output" at IC1b pin 4 goes *low* to indicate an alarm condition. This may be useful in some applications.

It is possible to drive a low-current l.e.d. directly from IC1d pin 11 via a suitable ballast resistor. There is insufficient current available to satisfactorily drive a normal l.e.d. Do not attempt to drive an l.e.d. directly from the inverted output since it may disrupt the voltage fed back to pin 2.

If you wish to use a buzzer or bright l.e.d. etc., a single transistor interface should be employed, in the manner shown

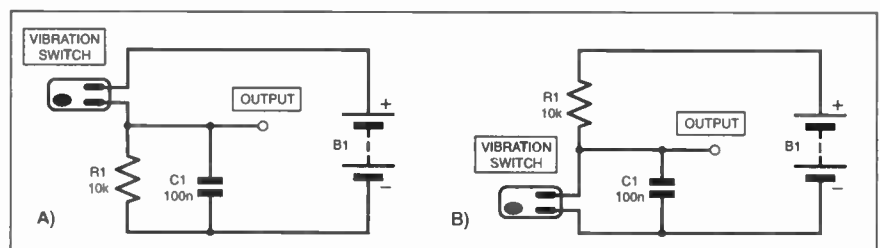


Fig.8.10. Two methods for "conditioning" the pulses from a vibration switch.

in Part 7 Fig.7.4, for example. Photo 8.5 shows a breadboard assembly of Fig.8.9 plus the components for a buzzer driving interface.

MOVEMENT DETECTION

The medical condition Deep Vein Thrombosis (DVT) is caused by a lack of movement, when sitting for long periods on an aircraft for example. When the legs are inactive for a long period, potentially fatal blood clots can form in the vein. We shall now describe a simple system which can give a warning if limbs are motionless for too long.

There are many techniques for monitoring movement. We shall first show how a vibration switch can be used in this context, providing output signals which can be monitored by the missing pulse detector circuits already described.

One form of vibration switch is shown inset in Fig.8.11. Two types are available, one with mercury inside, the other without. As mercury is a toxic substance, only the non-mercury type must be used.

In the photo there appears to be only one connection on the device, but the other connection is the metal casing – to which a wire can be soldered with care. Some vibration switches already have a wire fixed to the casing. A vibration switch differs from a tilt switch in that it can be in any position and will still detect movement. Hence it is ideal in this application.

The contacts of a vibration switch are normally open (unconnected) and close briefly when the switch is moved. So in the DVT application, the switch generates the pulses, a detection circuit monitors them, and sounds a warning if movement stops for too long a period.

The two circuits in Fig.8.10 show alternative ways of "conditioning" the vibration sensor's output prior to applying it to the main detector circuit. The arrangement Fig.8.10a produces positive-going (from low to high) pulses when the switch is vibrated. Resistor R1 ensures that the output is at 0V unless the switch is moved. Capacitor C1 removes any interference which is induced into the system, particularly if long wires are employed to link the switch to the circuit.

In Fig.8.10b the resistor holds the output high, unless the switch is vibrated, at which point the output pulses to 0V. This is useful for circuits or devices which require negative-going (from high to low) trigger pulses, such as the 555 timer. Note that some circuits may already have an internal resistor to bias the input high or low, in which case resistor R1 may be omitted.

PIC SOLUTION

Any of the missing pulse detectors previously described could be employed with one or other of the vibration switch circuits in

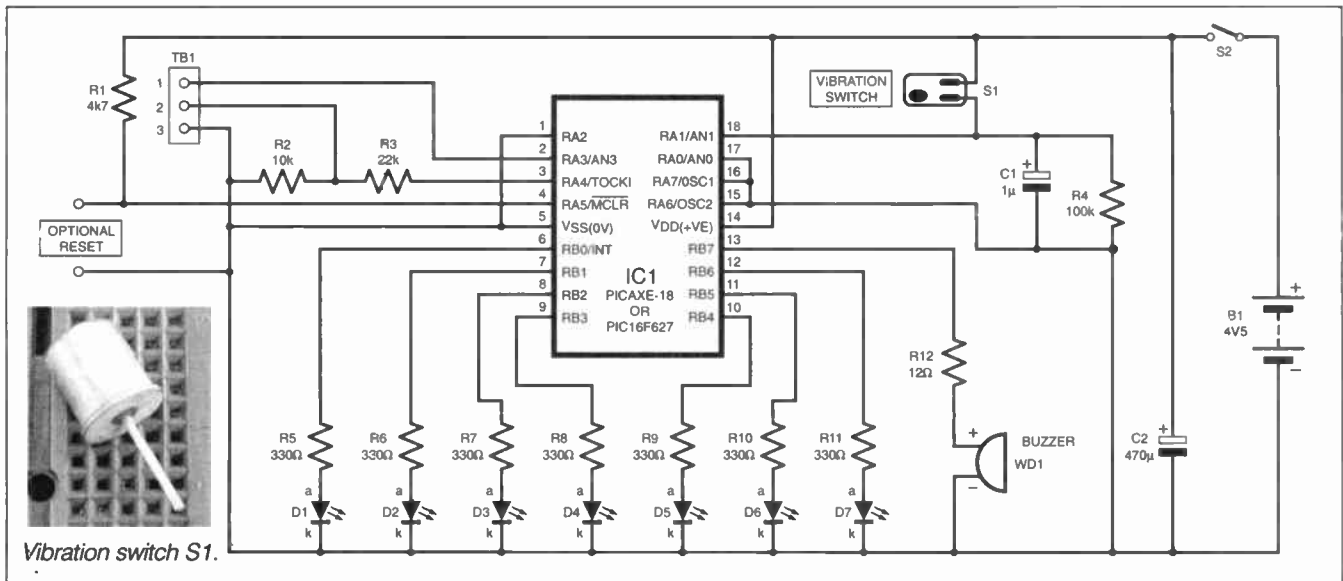


Fig.8.11. Circuit diagram for a PIC-controlled movement detection circuit.

Fig.8.10. However, PIC microcontrollers can provide a more sophisticated method. This allows the easy provision of a "count-down", i.e. a set of l.e.d.s which indicate the period of time before sounding the alarm. Whilst it is possible to design a non-PIC circuit with a set of l.e.d.s, the PIC provides the simplest and most flexible method.

The arrangement described now is based on the PIC variant known as the PICAXE-18, but a PIC16F627 (or PIC16F628) can be used if preferred. Details of the PICAXE-18 were discussed in Part 5, but in brief, these devices allow a program to be written in a form of BASIC, then downloaded directly into them via a serial lead from a PC.

This provides immense flexibility since the program can be modified and downloaded repeatedly, without the user having to worry about more conventional PIC programming techniques. For those who have such PIC programming facilities, however, a HEX file suitable for PIC16F627 devices is also available. For both options see later.

PIC CIRCUIT

The circuit schematic is shown in Fig.8.11. The pin notations used here are those for the PIC16F627/8. The PIC, IC1, includes a built-in clocking oscillator.

Terminal block TB1 is the PICAXE-18 serial programming connector. It may be omitted if programming is to be done with a standard PIC programmer and a PIC16F627, or if the chip is purchased ready-programmed. However, it is necessary to retain R2 and R3 since these hold pin RA4 at 0V when not in use.

Resistor R1 biases the MCLR pin high, for normal running mode. If required, resetting can be achieved by bridging the Optional Reset connections briefly with a metal object, such as a screwdriver blade.

Vibration switch S1 is connected to pin RA1, which is configured as an input. Its pull-down resistor R4 has been increased to 100kΩ (compared with Fig.8.10), and capacitor C1 has been increased to 1μF. The purpose of both changes is to lengthen the time for which input pin RA1 is held high after the vibration switch has been triggered,

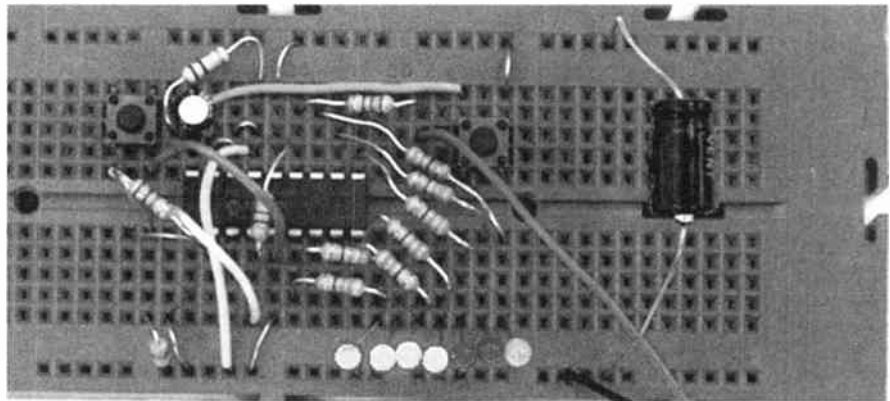


Photo 8.6. Breadboard layout of the circuit in Fig.8.11.

since the state of RA1 is checked by the program periodically rather than continuously.

Pins RB0 to RB6 are used as outputs to drive the set of l.e.d.s, D1 to D7. Note that D7 (a green l.e.d. in the prototype) indicates that the vibration sensor has been detected, and D1 to D6 (red) indicate the "countdown". The final output, RB7, is reserved for the buzzer or other warning device, WD1. Resistors R5 to R11 limit the flow of current through the l.e.d.s. R12 prevents a surge of current through the buzzer, which might upset the working of the PIC. In practice R12 is probably unnecessary, and could be bridged by a wire link.

The circuit may be powered at between 4.5V and 6V. The latter value must not be exceeded. Capacitor C2 provides power line decoupling (smoothing) for the circuit.

At switch-on, l.e.d.s D1 to D6 are all turned on, indicating that the maximum timing period is allowed. The program then checks the vibration switch repeatedly during a timing loop. The total time allowed before the alarm is sounded is six minutes. This may seem rather short, but readers with programming facilities can increase it if preferred by adding more steps in the timing loop. The l.e.d.s indicate the countdown progress, successively turning off at about one minute intervals.

RESOURCES

Pre-programmed PIC microcontrollers for the circuit in Fig.8.11 can be obtained

from: M. P. Horsey, Electronics Dept., Radley College, Abingdon, Oxon OX14 2HR. The price is £5 per PIC, including postage. Specify that the PIC is for *Teach-In 2004* Part 8. Enclose a cheque payable to Radley College.

The software for the PIC program (except for the PICAXE programming software) is available on 3.5in disk (*EPE* Disk 7), for which a nominal handling charge applies, from the Editorial Office, see the *EPE PCB Service* page. It is also available for free download via the click-link on the *EPE* home page at www.epemag.wimborne.co.uk.

PICAXE programming software can be obtained from: Revolution Education, Dept. *EPE*, 4 Old Dairy Business Centre, Melcombe Road, Bath BA2 3LR.

The telephone number is: 01225 340563, and their website is at www.rev-ed.co.uk.


PART 7 CORRECTION

The p.c.b. in Fig.7.16 was designed for a BC184L transistor (TR1) and its pin notations should read *e, c, b* from top to bottom.

NEXT MONTH

In Part 9 next month we examine hard-wired and logic gate control of lock and alarm systems, including the use of thyristors and matrix keypads, and how to use a PIC to decode keypad signals.

CIRCUIT SURGERY

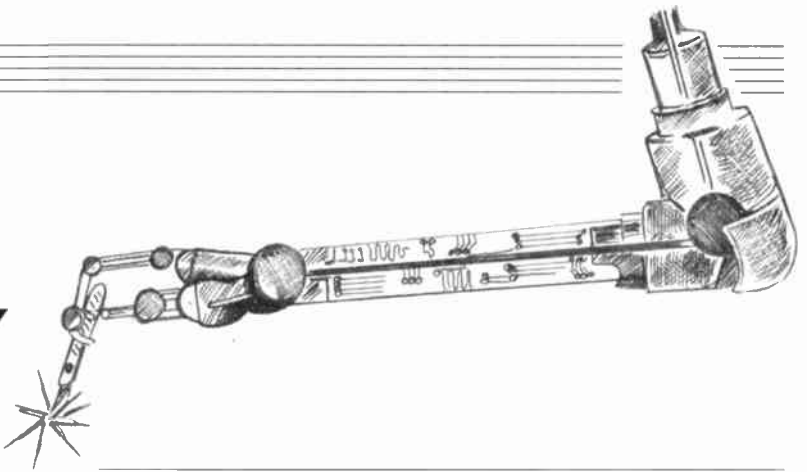

**ALAN WINSTANLEY
and IAN BELL**

This month, our intrepid surgeons look at some options for motor control using power op.amps, some brazen terminology and a current flow mystery

Power Op.Amps

Robert Penfold used the now obsolete L165D power op.amp for motor control in a number of his books and articles and I need a modern replacement. Could the low cost, readily available TDA2006V audio amp i.c. be used as an op.amp? For an H-bridge single rail 12V supply, the TDA2005M twin op.amp looks like being able to drive a motor at, say 3A.

I have in mind both PWM and d.c. servo feedback control. Would they work, and if so how? Or am I pipe-dreaming? Dave McCloy. P.S. Many thanks for the excellent articles!

The TDA2006 is an audio power amplifier i.c. delivering 12W into 4 ohms and 8W into 8 ohms from a 12V supply. Two TDA2006s can be used in a bridge configuration to deliver 24W.

Although the internal circuitry of the TDA2006 is similar to that of a basic op.amp, the device is optimised for use as

an audio power amplifier. It is not meant for general-purpose use and the TDA2006 datasheet provides three specific circuits for split supply, single supply and bridge amplifiers that the manufacturers recommend. The datasheet also provides a p.c.b. layout and details of the effect of changing component values in the circuits provided. The split supply TDA2006 circuit is shown in Fig.1 (courtesy ST Microelectronics).

One could experiment using the device as an op.amp, but problems such as instability and poor common mode input range may be experienced. It is possible that the TDA2006 would not perform well at d.c. as it is not intended for this purpose, whereas op.amps are usually designed for good d.c. performance.

In Comparison

For applications other than audio – such as the motor controller you have in mind – it would be better to use a power op.amp such as the LM12 or LM675 from National

Semiconductor. Both these devices are suitable for circuits such as servos and motor speed controllers.

The LM12 can deliver up to 80W, up to $\pm 10A$ and operates from a total supply of 15V to 60V ($\pm 30V$) and can be used in circuits with a closed loop voltage gain down to unity ($\times 1$). The LM675 is a lower power device delivering up to 20W, up to $\pm 3A$ and operating from a total supply of 16V to 60V. It is designed for use with closed loop voltage gains down to $\times 10$; the use of gains below this value may cause oscillation to occur.

In comparison, the TDA2006 is like an op.amp in that it is a high open-loop gain amplifier operated with negative feedback to set a much lower circuit gain. The TDA2006 is usually operated with a voltage gain of $\times 32$ and can be used with minimum gain of about $\times 16$.

The minimum gain of a high open-loop gain amplifier with negative feedback is set by the point at which the amplifier becomes unstable. At high frequencies, phase shifts in the circuit convert this negative feedback into positive feedback. More negative feedback means lower circuit gain, but also


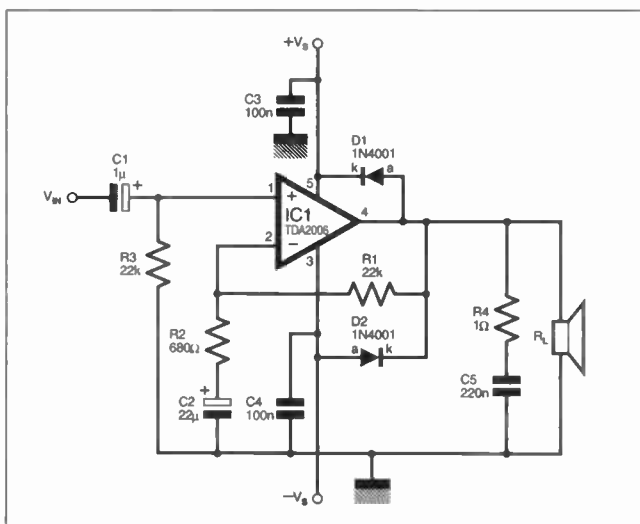


Fig.1. A TDA2006 split supply amplifier circuit from the i.c. datasheet. (Courtesy ST Microelectronics.)

Fig.2 (right). A typical LM12 power op.amp motor control circuit. This is a servo with motor speed proportional to input voltage. A good common earth/ground return point must be provided to avoid introducing "earth loops". (Courtesy National Semi.)

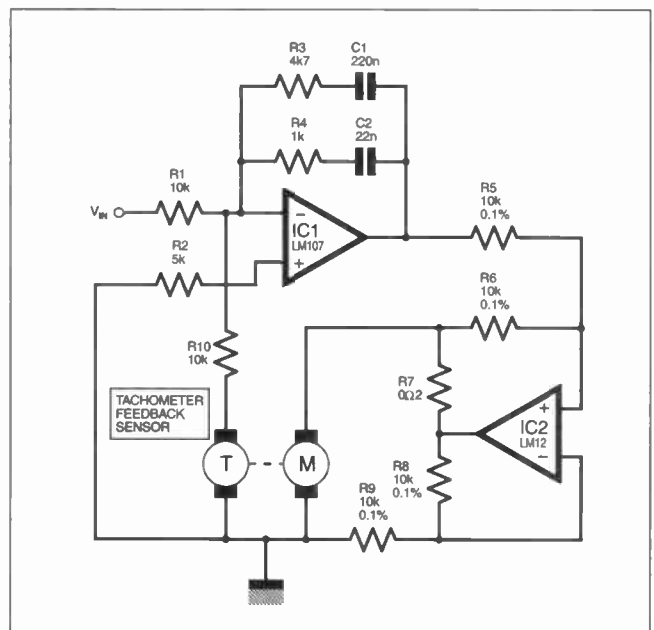

means more positive feedback at the frequencies at which the phase shift is sufficient. Thus, the lower the gain, the more unstable the circuit is likely to be.

The minimum gain is determined by the level of compensation built into the amplifier. This makes sure that the gain falls off at high frequencies before the phase shift is sufficient to cause problems. More compensation means that a greater range of low gain circuits can be built, but reduces bandwidth at any given gain.

Servo Controller

The circuit diagram shown in Fig.2 is for a servo circuit using the LM12 power op.amp taken from the National Semiconductor datasheet: a number of products are available for this purpose, often classified under the sub-heading of "motion control". The motor speed is proportional to the input voltage: note that the motor (the "M" symbol) has a tachometer (the "T" symbol) that provides a feedback signal to the controller.

The power op.amps are happy to drive resistive and inductive loads such as loudspeakers and motors, and the LM12 TO3 package would handle reactive loads of 800 watts peak without the need to de-rate; however, they have difficulty with capacitive loads. Capacitive loads interact with the feedback in such a way as to cause potential instability.

Again, the lower the gain, and the greater the level of feedback in use, then the more problematical capacitive loads become. For unity gain, the LM12 can handle 0.01 μ F and both op.amps can handle 1 μ F in circuits with a gain of 10. To drive large capacitive loads, connect a low value resistor (typically 5 ohms to 10 ohms) in series with an inductor (typically 4 μ H or 5 μ H) between the amplifier output and the load.

All power circuits require great care to be taken with power supply design and standards of construction. Supply leads for all these devices should be bypassed by low inductance capacitors (e.g. C3 and C4 in Fig.1 – not shown in Fig.2). The LM12 may need capacitors as large as 470 μ F or more close to the device for high quality operation. At least 20 μ F should be used. Good ground returns to a common point must be provided if the accidental introduction of earth loops is to be avoided.

Clamp Down

For all three devices, output clamp diodes should be included when driving inductive loads such as motors, solenoids and loudspeakers (e.g. D1 and D2 in Fig. 1, not shown in Fig. 2). For some motor-driving applications it also helps to put a diode in series with the negative supply lead. This diode must be able to dissipate continuous power depending on the supply current and may need to be on a heatsink. The clamp diodes only dissipate transient power and so they should not require heatsinking, but they need to be able to withstand high transient currents.

As with all power circuits good thermal design is also required when using any of the three devices discussed here. All the devices feature internal thermal shutdown protection circuits so they should survive situations which cause them to overheat, but the circuit will not be operating when the i.c. is shut down.

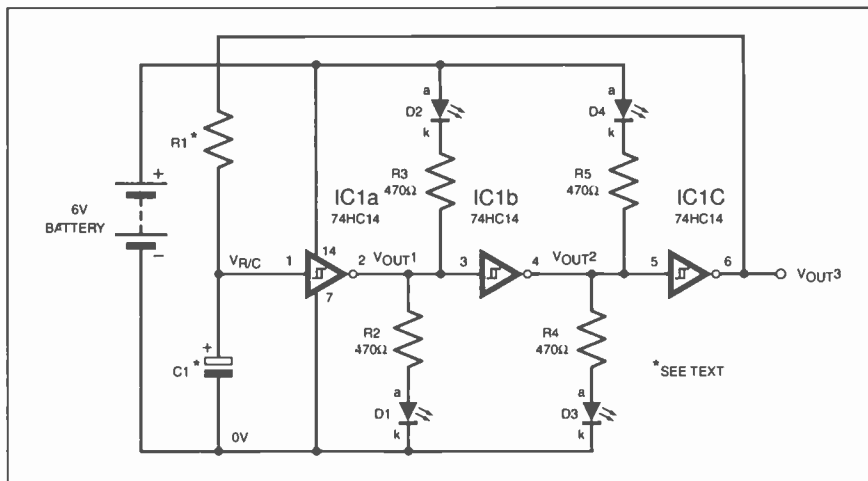


Fig.3. Original Schmitt trigger-based circuit diagram (Fig.2.15) from the EPE Teach-In 2000 (Part 2) series. The complete series (plus the interactive software) is available on a single CD-ROM – see CD-ROMs for Electronics or Direct Book Service pages.

The datasheet provides more details and can be fetched from the National web site (www.national.com) – or type "LM12" into Google. I.M.B.

Brazen Terminology

Thank you very much for the notes on "soldering" and I hope the material will help my civil engineering students to learn the basics. I would be thankful if you could kindly mail sketches of the soldering "set up" and some similar explanations on "brazing" and incidentally the glossary of terms including "solidus" and "liquidus". Thank you for providing the learning material. Prof. V.R. Vivekanandan, Periyar Maniammai College of Technology for Women, Thanjavur, India.

The Basic Soldering Guide on our web site (www.epemag.wimbborne.co.uk – go to Resources) continues to provide beginners everywhere with a very fundamental introduction to electronics soldering: it rates as being the most popular resource of its type on the internet. I'm afraid that no sketches are available to send you but hopefully the online step-by-step photos will explain the use of a soldering iron and desoldering pump.

The terms *solidus* and *liquidus* in this electronics context relate to the melting or solidifying points of solder: solidus is the highest temperature at which the solder is completely solid, before it starts to flow. Liquidus is the coolest temperature at which it is completely liquid, before it starts to harden.

I have been asked a number of times by readers and internet users to explain what exactly "brazing" is. Brazing uses higher temperatures than can be achieved with a soldering iron, and is a technique used in metal fabrication work, using suitable gas torches and adding non-ferrous alloy wire as a filler, to bond metals together. This is less aggressive than welding and is suited to more precise work.

If you have a mini gas torch of the type supplied with e.g. soldering tips or hot air blowers, note that the hottest part of a butane flame is the inner blue tip, where the gas is being burnt. Because the temperature needed is typically >425 degrees Celsius, ordinary solder cannot be used, and specialist alloy wire should be used instead. (I did however witness a car

mechanic brazing a small steel plate onto a car body repair, using some coat hanger wire as the "alloy".) A.R.W.

Current Flow

Reader Pete Barber (in the EPE Chat Zone) recently asked:

I am learning electronics and am currently up to the Capacitors section of EPE Teach-In 2000. I am building the Schmitt trigger-based oscillator (Fig. 2.15 on page 922, EPE Dec '99), see Fig.3. Looking at the ancillary circuitry, my Schmitt trigger has an l.e.d. in series with a 470 ohm resistor connected between the positive rail and the output pin.

My question is, given that an output pin is used, how can the current flow into it to make the l.e.d. light?

This relates to the subject of "sourcing" and "sinking" current, which was dealt with in more detail in the Jan '04 issue of *Circuit Surgery*. To recap, some (but not all!) integrated circuits are capable of sinking current to 0V via their output pins. Indeed, some devices are optimised to sink current rather than source it from a "high" output. In your experiment, current can sink into the Schmitt trigger and illuminates the l.e.d. along the way.

Apart from having a logic "high" or logic "low" state when the output will either source or sink current respectively, another class of driver has a third state equivalent to an "open circuit" where the output is disconnected completely. These are termed "tri-state" devices and they can be used for controlling the flow of data on a data bus. An example is the 74HCT574 i.c. which has eight tri-state latches. A.R.W.

Circuit Surgery will wherever possible offer advice or pointers to readers, but we cannot guarantee to do so, and the ease with which queries can be sent by email does nothing to help! It is not always possible to offer either quick "snap" or considered answers to every circuit, especially if it would be necessary to build or simulate the circuit, but we do read every letter, reply where we can and we publish a selection of your queries every month. You can send your emails to alan@epemag.demon.co.uk.

DIRECT BOOK SERVICE

NOTE: ALL PRICES INCLUDE UK POSTAGE

FREE *Electronics Hobbyist Compendium* book with Teach-In 2000 CD-ROM



EPE TEACH-IN 2000 CD-ROM

The whole of the 12-part *Teach-In 2000* series by John Becker (published in *EPE* Nov '99 to Oct 2000) is now available on CD-ROM. Plus the *Teach-In 2000* interactive software (Win 95, 98, ME and above) covering all aspects of the series and Alan Winstanley's *Basic Soldering Guide* (including illustrations and Desoldering).

Teach-In 2000 covers all the basic principles of electronics from Ohm's Law to Displays, including Op.Amps, Logic Gates etc. Each part has its own section on the interactive software where you can also change component values in the various on-screen demonstration circuits.

The series gives a hands-on approach to electronics with numerous breadboard circuits to try out, plus a simple computer interface (Win 95, 98, ME only) which allows a PC to be used as a basic oscilloscope.

ONLY **£12.45** including VAT and p&p

Order code Teach-In CD-ROM

Circuits and Design

DISCOVERING ELECTRONIC CLOCKS

W. D. Phillips

This is a whole book about designing and making electronic clocks. You start by connecting HIGH and LOW logic signals to logic gates. You find out about and then build and test bistables, crystal-controlled astables, counters, decoders and displays. All of these subsystems are carefully explained, with practical work supported by easy to follow prototype board layouts.

Full constructional details, including circuit diagrams and a printed circuit board pattern, are given for a digital electronic clock. The circuit for the First Clock is modified and developed to produce additional designs which include a Big Digit Clock, Binary Clock, Linear Clock, Andrew's Clock (with a semi-analogue display), and a Circles Clock. All of these designs are unusual and distinctive.

This is an ideal resource for project work in GCSE *Design and Technology: Electronics Product*, and for project work in AS-Level and A-Level *Electronics and Technology*.

194 pages, A4 spiral bound Order code DEP1 £17.50

DOMESTIC SECURITY SYSTEMS

A. L. Brown

This book shows you how, with common sense and basic do-it-yourself skills, you can protect your home. It also gives tips and ideas which will help you to maintain and improve your home security, even if you already have an alarm. Every circuit in this book is clearly described and illustrated, and contains components that are easy to source. Advice and guidance are based on the real experience of the author who is an alarm installer, and the designs themselves have been rigorously put to use on some of the most crime-ridden streets in the world.

The designs include all elements, including sensors, detectors, alarms, controls, lights, video and door entry systems. Chapters cover installation, testing, maintenance and upgrading.

192 pages

Order code NE25

£20.99

MICROCONTROLLER COOKBOOK

Mike James

The practical solutions to real problems shown in this cookbook provide the basis to make PIC and 8051 devices really work. Capabilities of the variants are examined, and ways to enhance these are shown. A survey of common interface devices, and a description of programming models, lead on to a section on development techniques. The cookbook offers an introduction that will allow any user, novice or experienced, to make the most of microcontrollers.

240 pages

Order code NE26

£23.99

A BEGINNER'S GUIDE TO TTL DIGITAL ICs

R. A. Penfold

This book first covers the basics of simple logic circuits in general, and then progresses to specific TTL logic integrated circuits. The devices covered include gates, oscillators, timers, flip/flops, dividers, and decoder circuits. Some practical circuits are used to illustrate the use of TTL devices in the "real world".

142 pages

Order code BP332

£5.45

PRACTICAL ELECTRONICS CALCULATIONS AND FORMULAE

F. A. Wilson, C.G.I.A., C.Eng., F.I.E.E., F.I.E.R.E., F.B.I.M.

Bridges the gap between complicated technical theory, and "cut-and-try" methods which may bring success in design but leave the experimenter unfulfilled. A strong practical bias – tedious and higher mathematics have been avoided where possible and many tables have been included.

The book is divided into six basic sections: Units and Constants, Direct-Current Circuits, Passive Components, Alternating-Current Circuits, Networks and Theorems, Measurements.

256 pages

Order code BP53

£5.49

Computing & Robotics

WINDOWS XP EXPLAINED

N. Kantaris and P. R. M. Oliver

If you want to know what to do next when confronted with Microsoft's Windows XP screen, then this book is for you. It applies to both the Professional and Home editions.

The book was written with the non-expert, busy person in mind. It explains what hardware requirements you need in order to run Windows XP successfully, and gives an overview of the Windows XP environment.

The book explains: How to manipulate Windows, and how to use the Control Panel to add or change your printer, and control your display; How to control information using WordPad, Notepad and Paint, and how to use the Clipboard facility to transfer information between Windows applications; How to be in control of your filing system using Windows Explorer and My Computer; How to control printers, fonts, characters, multimedia and images, and how to add hardware and software to your system; How to configure your system to communicate with the outside world, and use Outlook Express for all your email requirements; How to use the Windows Media Player 8 to play your CDs, burn CDs with your favourite tracks, use the Radio Tuner, transfer your videos to your PC, and how to use the Sound Recorder and Movie Maker; How to use the System Tools to restore your system to a previously working state, using Microsoft's Website to update your Windows set-up, how to clean up, defragment and scan your hard disk, and how to backup and restore your data; How to successfully transfer text from those old but cherished MS-DOS programs.

268 pages

Order code BP514

£7.99

INTRODUCING ROBOTICS WITH LEGO MINDSTORMS

Robert Penfold

Shows the reader how to build a variety of increasingly sophisticated computer controlled robots using the brilliant Lego Mindstorms Robotic Invention System (RIS). Initially covers fundamental building techniques and mechanics needed to construct strong and efficient robots using the various "click-together" components supplied in the basic RIS kit. Explains in simple terms how the "brain" of the robot may be programmed on screen using a PC and "zapped" to the robot over an infra-red link. Also, shows how a more sophisticated Windows programming language such as Visual BASIC may be used to control the robots.

Detailed building and programming instructions provided, including numerous step-by-step photographs.

288 pages – large format

Order code BP901

£14.99

MORE ADVANCED ROBOTICS WITH LEGO MINDSTORMS – Robert Penfold

Covers the Vision Command System

Shows the reader how to extend the capabilities of the brilliant Lego Mindstorms Robotic Invention System (RIS) by using Lego's own accessories and some simple home constructed units. You will be able to build robots that can provide you with "waiter service" when you clap your hands, perform tricks, "see" and avoid objects by using "bats radar", or accurately follow a line marked on

the floor. Learn to use additional types of sensors including rotation, light, temperature, sound and ultrasonic and also explore the possibilities provided by using an additional (third) motor. For the less experienced, RCX code programs accompany most of the featured robots. However, the more adventurous reader is also shown how to write programs using Microsoft's VisualBASIC running with the ActiveX control (Spirit.OCX) that is provided with the RIS kit.

Detailed building instructions are provided for the featured robots, including numerous step-by-step photographs. The designs include rover vehicles, a virtual pet, a robot arm, an "intelligent" sweet dispenser and a colour conscious robot that will try to grab objects of a specific colour.

298 pages

Order code BP902

£14.99

PIC YOUR PERSONAL INTRODUCTORY COURSE

SECOND EDITION John Morton

Discover the potential of the PIC microcontroller through graded projects – this book could revolutionise your electronics construction work!

A uniquely concise and practical guide to getting up and running with the PIC Microcontroller. The PIC is one of the most popular of the microcontrollers that are transforming electronic project work and product design.

Assuming no prior knowledge of microcontrollers and introducing the PICs capabilities through simple projects, this book is ideal for use in schools and colleges. It is the ideal introduction for students, teachers, technicians and electronics enthusiasts. The step-by-step explanations make it ideal for self-study too: this is not a reference book – you start work with the PIC straight away.

The revised second edition covers the popular reprogrammable EEPROM PICs: P16C84/16F84 as well as the P54 and P71 families.

270 pages

Order code NE36

£15.99

INTRODUCTION TO MICROPROCESSORS

John Crisp

If you are, or soon will be, involved in the use of microprocessors, this practical introduction is essential reading. This book provides a thoroughly readable introduction to microprocessors, assuming no previous knowledge of the subject, nor a technical or mathematical background. It is suitable for students, technicians, engineers and hobbyists, and covers the full range of modern microprocessors.

After a thorough introduction to the subject, ideas are developed progressively in a well-structured format. All technical terms are carefully introduced and subjects which have proved difficult, for example 2's complement, are clearly explained. John Crisp covers the complete range of microprocessors from the popular 4-bit and 8-bit designs to today's super-fast 32-bit and 64-bit versions that power PCs and engine management systems etc.

222 pages

Order code NE31

£19.99

The books listed have been selected by *Everyday Practical Electronics* editorial staff as being of special interest to everyone involved in electronics and computing. They are supplied by mail order direct to your door. Full ordering details are given on the last book page.

FOR A FURTHER SELECTION OF BOOKS SEE THE NEXT TWO ISSUES OF *EPE*

All prices include UK postage

NEWNES INTERFACING COMPANION

Tony Fischer-Cripps

A uniquely concise and practical guide to the hardware, applications and design issues involved in computer interfacing and the use of transducers and instrumentation.

Newnes Interfacing Companion presents the essential information needed to design a PC-based interfacing system from the selection of suitable transducers, to collection of data, and the appropriate signal processing and conditioning.

Contents: Part 1 – Transducers; Measurement systems; Temperature; Light; Position and motion; Force, pressure and flow. Part 2 – Interfacing; Number systems; Computer architecture; Assembly language; Interfacing; A to D and D to A conversions; Data communications; Programmable logic controllers; Data acquisition project. Part 3 – Signal processing; Transfer function; Active filters; Instrumentation amplifier; Noise; Digital signal processing.

320 pages

Order code NE38

£26.99

Testing, Theory and Reference

THE AMATEUR SCIENTIST CD-ROM

The complete collection of The Amateur Scientist articles from *Scientific American* magazine. Over 1,000 classic science projects from a renowned source of winning projects. All projects are rated for cost, difficulty and possible hazards.

Plus over 1,000 pages of helpful science techniques that never appeared in *Scientific American*.

Exciting science projects in: Astronomy; Earth Science; Biology; Physics; Chemistry; Weather... and much more! The most complete resource ever assembled for hobbyists, and professionals looking for novel solutions to research problems. Includes extensive Science Software Library with even more science tools.

Suitable for Mac, Windows, Linux or UNIX. 32MB RAM minimum, Netscape 4.0 or higher or Internet Explorer 4.0 or higher. Over 1,000 projects

Order code AS1 CD-ROM

£19.95



BEBOP BYTES BACK (and the Beboputer Computer Simulator) CD-ROM

Clive (Max) Maxfield and Alvin Brown

This follow-on to *Bebop to the Boolean Boogie* is a multimedia extravaganza of information about how computers work. It picks up where "Bebop I" left off, guiding you through the fascinating world of computer design... and you'll have a few chuckles, if not belly laughs, along the way. In addition to over 200 megabytes of mega-cool multimedia, the CD-ROM contains a virtual microcomputer, simulating the motherboard and standard computer peripherals in an extremely realistic manner. In addition to a wealth of technical information, myriad nuggets of trivia, and hundreds of carefully drawn illustrations, the CD-ROM contains a set of lab experiments for the virtual microcomputer that let you recreate the experiences of early computer pioneers. If you're the slightest bit interested in the inner workings of computers, then don't dare to miss this!

Over 800 pages in Adobe Acrobat format

Order code BEB2 CD-ROM £21.95



DIGITAL ELECTRONICS - A PRACTICAL APPROACH With FREE Software: Number One Systems - EASY-PC Professional XM and Pulsar (Limited Functionality)

Richard Monk

Covers binary arithmetic, Boolean algebra and logic gates, combination logic, sequential logic including the design and construction of asynchronous and synchronous circuits and register circuits. Together with a considerable practical content plus the additional attraction of its close association with computer-aided design including the FREE software.

There is a 'blow-by-blow' guide to the use of EASY-PC Professional XM (a schematic drawing and printed circuit board design computer package). The guide also conducts the reader through logic circuit simulation using Pulsar software. Chapters on p.c.b. physics and p.c.b. production techniques make the book unique, and with its host of project ideas make it an ideal companion for the integrative assignment and common skills components required by BTEC and the key skills demanded by GNVQ. The principal aim of the book is to provide a straightforward approach to the understanding of digital electronics.

Those who prefer the 'Teach-In' approach or would rather experiment with some simple circuits should find the book's final chapters on printed circuit board production and project ideas especially useful.

250 pages

Order code NE28

£21.99

FREE SOFTWARE

OSCILLOSCOPES - FIFTH EDITION

Ian Hickman

Oscilloscopes are essential tools for checking circuit operation and diagnosing faults, and an enormous range of models are available.

This handy guide to oscilloscopes is essential reading for anyone who has to use a 'scope for their work or hobby; electronics designers, technicians, anyone in industry involved in test and measurement, electronics enthusiasts... Ian Hickman's review of all the latest types of 'scope currently available will prove especially useful for anyone planning to buy - or even build - an oscilloscope.

The contents include a description of the basic oscilloscope; Advanced real-time oscilloscope; Accessories; Using oscilloscopes; Sampling oscilloscopes; Digital storage oscilloscopes; Oscilloscopes for special purposes; How oscilloscopes work (1): the CRT; How oscilloscopes work (2): circuitry; How oscilloscopes work (3): storage CRTs; plus a listing of Oscilloscope manufacturers and suppliers.

288 pages

Order code NE37

£22.99

EDA - WHERE ELECTRONICS BEGINS

Clive "Max" Maxfield and Kuhoo Goyal Edson

ON SALE 50% OFF

"Did you ever wonder how the circuit boards and silicon chips inside your personal computer or cell phone were designed? This book walks you through the process of designing a city on an alien planet and compares it to designing an electronic system. The result is a fun, light-hearted and entertaining way to learn about one of the most important - and least understood - industries on this planet."

EDA, which stands for *electronic design automation*, refers to the software tools (computer programs) used to design electronic products. EDA actually encompasses a tremendous variety of tools and concepts. The aim of this book is to take a 30,000-foot view of the EDA world. To paint a "big picture" that introduces some of the most important EDA tools and describes how they are used to create integrated circuits, circuit boards and electronic systems. To show you how everything fits together without making you want to bang your head against the nearest wall.

Specially imported by EPE - Excellent value £29.95

98 pages - Large format

Order code EDA1

£14.95 while stocks last

PRACTICAL ELECTRONIC FAULT FINDING AND TROUBLESHOOTING

Robin Pain

To be a real fault finder, you must be able to get a feel for what is going on in the circuit you are examining. In this book Robin Pain explains the basic techniques needed to be a fault finder.

Simple circuit examples are used to illustrate principles and concepts fundamental to the process of fault finding. This is not a book of theory, it is a book of practical tips, hints and rules of thumb, all of which will equip the reader to tackle any job. You may be an engineer or technician in search of information and guidance, a college student, a hobbyist building a project from a magazine, or simply a keen self-taught amateur who is interested in electronic fault finding but finds books on the subject too mathematical or specialised.

The fundamental principles of analogue and digital fault finding are described (although, of course, there is no such thing as a "digital fault" - all faults are by nature analogue). This book is written entirely for a fault finder using only the basic fault-finding equipment: a digital multimeter and an oscilloscope. The treatment is non-mathematical (apart from Ohm's law) and all jargon is strictly avoided.

274 pages

Order code NE22

£25.99

ELECTRONIC TEST EQUIPMENT HANDBOOK

Steve Money

In most applications of electronics, test instruments are essential for checking the performance of a system or for diagnosing faults in operation, and so it is important for engineers, technicians, students and hobbyists to understand how the basic test instruments work and how they can be used.

The principles of operation of the various types of test instrument are explained in simple terms with a minimum of mathematical analysis. The book covers analogue and digital meters, bridges, oscilloscopes, signal generators, counters, timers and frequency measurement. The practical uses of these instruments are also examined.

206 pages

Order code PC109

£9.95

DIGITAL GATES AND FLIP-FLOPS

Ian R. Sinclair

This book, intended for enthusiasts, students and technicians, seeks to establish a firm foundation in digital electronics by treating the topics of gates and flip-flops thoroughly and from the beginning.

Topics such as Boolean algebra and Karnaugh mapping are explained, demonstrated and used extensively, and more attention is paid to the subject of synchronous counters than to the simple but less important ripple counters.

No background other than a basic knowledge of electronics is assumed, and the more theoretical topics are explained from the beginning, as also are many working practices. The book concludes with an explanation of micro-processor techniques as applied to digital logic.

200 pages

Order code PC106

£9.95

UNDERSTANDING ELECTRONIC CONTROL SYSTEMS

Owen Bishop

Owen Bishop has produced a concise, readable text to introduce a wide range of students, technicians and professionals to an important area of electronics. Control is a highly mathematical subject, but here maths is kept to a minimum, with flow charts to illustrate principles and techniques instead of equations.

Cutting edge topics such as microcontrollers, neural networks and fuzzy control are all here, making this an ideal refresher course for those working in industry. Basic principles, control algorithms and hardwired control systems are also fully covered so the resulting book is a comprehensive text and well suited to college courses or background reading for university students.

The text is supported by questions under the headings Keeping Up and Test Your Knowledge so that the reader can develop a sound understanding and the ability to apply the techniques they are learning.

228 pages

Order code NE35

£20.99

HOW ELECTRONIC THINGS WORK - AND WHAT TO DO WHEN THEY DON'T

Robert Goodman

You never again have to be flummoxed, flustered or taken for a ride by a piece of electronics equipment. With this fully illustrated, simple-to-use guide, you will get a grasp on the workings of the electronic world that surrounds you - and even learn to make your own repairs.

You don't need any technical experience. This book gives you: Clear explanations of how things work, written in everyday language. Easy-to-follow, illustrated instructions on using test equipment to diagnose problems. Guidelines to help you decide for or against professional repair. Tips on protecting your expensive equipment from lightning and other electrical damage. Lubrication and maintenance suggestions.

Covers: colour TVs, VCRs, radios, PCs, CD players, printers, telephones, monitors, camcorders, satellite dishes, and much more!

394 pages

Order code MGH3

£21.99

VINTAGE RADIOS - COLLECTING • SERVICING • RESTORING

Tony Thompson

The essential guide to collecting, repairing and restoring vintage valve radios. These receivers are becoming ever more popular as collectibles, this is a good thing because it means that a very large piece of technological history is being reclaimed when at one time many thought it lost forever. If you look around, you will find plenty of valve radio sets just waiting for a loving restoration. They may not yet be the most highly prized, and they are unlikely to be in top condition, but they can be yours and, if you develop the skills outlined in this book, you will possess radio receivers to be proud of.

The book covers radio history, styling, faultfinding, chassis and cabinet restoration, types of set.

124 pages spiral bound

Order code TT1

£12.95



All prices include UK P&P



Theory and Reference

ELECTRONICS MADE SIMPLE

Ian Sinclair

Assuming no prior knowledge, *Electronics Made Simple* presents an outline of modern electronics with an emphasis on understanding how systems work rather than on details of circuit diagrams and calculations. It is ideal for students on a range of courses in electronics, including GCSE, C&G and GNVQ, and for students of other subjects who will be using electronic instruments and methods.

Contents: waves and pulses, passive components, active components and ICs, linear circuits, block and circuit diagrams, how radio works, disc and tape recording, elements of TV and radar, digital signals, gating and logic circuits, counting and correcting, micro-processors, calculators and computers, miscellaneous systems.

199 pages

Order code NE23

£13.99

SCROGGIE'S FOUNDATIONS OF WIRELESS AND ELECTRONICS - ELEVENTH EDITION

S. W. Amos and Roger Amos

Scroggie's Foundations is a classic text for anyone working with electronics, who needs to know the art and craft of the subject. It covers both the theory and practical aspects of a huge range of topics from valve and tube technology, and the application of cathode ray tubes to radar, to digital tape systems and optical recording techniques.

Since *Foundations of Wireless* was first published over 60 years ago, it has helped many thousands of readers to become familiar with the principles of radio and electronics. The original author Sowerby was succeeded by Scroggie in the 1940s, whose name became synonymous with this classic primer for practitioners and students alike. Stan Amos, one of the fathers of modern electronics and the author of many well-known books in the area, took over the revision of this book in the 1980s and it is he, with his son, who have produced this latest version.

400 pages

Order code NE27

£23.99

GETTING THE MOST FROM YOUR MULTIMETER

R. A. Penfold

This book is primarily aimed at beginners and those of limited experience of electronics. Chapter 1 covers the basics of analogue and digital multimeters, discussing the relative merits and the limitations of the two types. In Chapter 2 various methods of component checking are described, including tests for transistors, thyristors, resistors, capacitors and diodes. Circuit testing is covered in Chapter 3, with subjects such as voltage, current and continuity checks being discussed.

In the main little or no previous knowledge or experience is assumed. Using these simple component and circuit testing techniques the reader should be able to confidently tackle servicing of most electronic projects.

96 pages

Order code BP239

£5.49

PRACTICAL ELECTRONIC FILTERS

Owen Bishop

This book deals with the subject in a non-mathematical way. It reviews the main types of filter, explaining in simple terms how each type works and how it is used.

The book also presents a dozen filter-based projects with applications in and around the home or in the constructor's workshop. These include a number of audio projects such as a rhythm sequencer and a multi-voiced electronic organ.

Concluding the book is a practical step-by-step guide to designing simple filters for a wide range of purposes, with circuit diagrams and worked examples.

188 pages

Order code BP299

£5.49

PREAMPLIFIER AND FILTER CIRCUITS

R. A. Penfold

This book provides circuits and background information for a range of preamplifiers, plus tone controls, filters, mixers, etc. The use of modern low noise operational amplifiers and a specialist high performance audio preamplifier i.c. results in circuits that have excellent performance, but which are still quite simple. All the circuits featured can be built at quite low cost (just a few pounds in most cases). The preamplifier circuits featured include: Microphone preamplifiers (low impedance, high impedance, and crystal). Magnetic cartridge pick-up preamplifiers with R.I.A.A. equalisation. Crystal/ceramic pick-up preamplifier. Guitar pick-up preamplifier. Tape head preamplifier (for use with compact cassette systems).

Other circuits include: Audio limiter to prevent overloading of power amplifiers. Passive tone controls. Active tone controls. PA filters (highpass and lowpass). Scratch and rumble filters. Loudness filter. Mixers. Volume and balance controls.

92 pages

Order code BP309

£4.49

Project Building

ELECTRONIC PROJECTS FOR EXPERIMENTERS

R. A. Penfold

Many electronic hobbyists who have been pursuing their hobby for a number of years seem to suffer from the dreaded "seen it all before" syndrome. This book is fairly and squarely aimed at sufferers of this complaint, plus any other electronics enthusiasts who yearn to try something a bit different.

The subjects covered include:- Magnetic field detector, Basic Hall effect compass, Hall effect audio isolator, Voice scrambler/descrambler, Bat detector, Bat style echo location, Noise cancelling, LED stroboscope, Infra-red "torch", Electronic breeze detector, Class D power amplifier, Strain gauge amplifier, Super hearing aid.

138 pages

Order code BP371

£5.45

PRACTICAL FIBRE-OPTIC PROJECTS

R. A. Penfold

While fibre-optic cables may have potential advantages over ordinary electric cables, for the electronics enthusiast it is probably their novelty value that makes them worthy of exploration. Fibre-optic cables provide an innovative interesting alternative to electric cables, but in most cases they also represent a practical approach to the problem. This book provides a number of tried and tested circuits for projects that utilize fibre-optic cables.

The projects include:- Simple audio links, F.M. audio link, P.W.M. audio links, Simple d.c. links, P.W.M. d.c. link, P.W.M. motor speed control, RS232C data links, MIDI link, Loop alarms, R.P.M. meter.

All the components used in these designs are readily available, none of them require the constructor to take out a second mortgage.

132 pages

Order code BP374

£5.45

ELECTRONIC MUSIC AND MIDI PROJECTS

R. A. Penfold

Whether you wish to save money, boldly go where no musician has gone before, rekindle the pioneering spirit,

or simply have fun building some electronic music gadgets, the designs featured in this book should suit your needs. The projects are all easy to build, and some are so simple that even complete beginners at electronic project construction can tackle them with ease. Stripboard layouts are provided for every project, together with a wiring diagram. The mechanical side of construction has largely been left to the individual constructors to sort out, simply because the vast majority of project builders prefer to do their own thing.

None of the designs requires the use of any test equipment in order to get them set up properly. Where any setting up is required, the procedures are very straightforward, and they are described in detail.

Projects covered: Simple MIDI tester, Message grabber, Byte grabber, THRU box, MIDI auto switcher, Auto/manual switcher, Manual switcher, MIDI patchbay, MIDI controlled switcher, MIDI lead tester, Program change pedal, Improved program change pedal, Basic mixer, Stereo mixer, Electronic swell pedal, Metronome, Analogue echo unit.

138 pages

Order code PC116

£5.45

VIDEO PROJECTS FOR THE ELECTRONICS CONSTRUCTOR

R. A. Penfold

Written by highly respected author R. A. Penfold, this book contains a collection of electronic projects specially designed for video enthusiasts. All the projects can be simply constructed, and most are suitable for the newcomer to project construction, as they are assembled on stripboard.

There are faders, wipers and effects units which will add sparkle and originality to your video recordings, an audio mixer and noise reducer to enhance your soundtracks and a basic computer control interface. Also, there's a useful selection on basic video production techniques to get you started.

Circuits include: video enhancer, improved video enhancer, video fader, horizontal wiper, improved video wiper, negative video unit, fade to grey unit, black and white keyer, vertical wiper, audio mixer, stereo headphone amplifier, dynamic noise reducer, automatic fader, pushbutton fader, computer control interface, 12 volt mains power supply.

124 pages

Order code PC115

£5.45

BOOK ORDERING DETAILS

All prices include UK postage. For postage to Europe (air) and the rest of the world (surface) please add £2 per book. For the rest of the world airmail add £3 per book. CD-ROM prices include VAT and/or postage to anywhere in the world. Send a PO, cheque, international money order (£ sterling only) made payable to **Direct Book Service** or card details, Visa, Mastercard, Amex, Diners Club or Switch to:

**DIRECT BOOK SERVICE, WIMBORNE PUBLISHING LTD.,
408 WIMBORNE ROAD EAST, FERNDOWN, DORSET BH22 9ND.**

Books are normally sent within seven days of receipt of order, but please allow 28 days for delivery - more for overseas orders. *Please check price and availability (see latest issue of Everyday Practical Electronics) before ordering from old lists.*

For a further selection of books see the next two issues of *EPE*.

Tel 01202 873872 Fax 01202 874562. Email: dbs@epemag.wimbome.co.uk

Order from our online shop at: www.epemag.wimbome.co.uk/shopdoor.htm

BOOK ORDER FORM

Full name:

Address:

.....

.....

..... Post code: Telephone No:

Signature:

I enclose cheque/PO payable to DIRECT BOOK SERVICE for £

Please charge my card £ Card expiry date:

Card Number Switch Issue No.

Card Security Code (the last three digits on or just under the signature strip)

Please send book order codes:

.....

Please continue on separate sheet of paper if necessary
If you do not wish to cut your magazine, send a letter or copy of this form

PCB SERVICE

Printed circuit boards for most recent *EPE* constructional projects are available from the PCB Service, see list. These are fabricated in glass fibre, and are fully drilled and roller tinned. All prices include VAT and postage and packing. Add £1 per board for airmail outside of Europe. Remittances should be sent to The PCB Service, *Everyday Practical Electronics*, Wimborne Publishing Ltd., 408 Wimborne Road East, Ferndown, Dorset BH22 9ND. Tel: 01202 873872; Fax 01202 874562; Email: orders@epemag.wimborne.co.uk. On-line Shop: www.epemag.wimborne.co.uk/shopdoor.htm. Cheques should be crossed and made payable to *Everyday Practical Electronics* (Payment in £ sterling only).

NOTE: While 95% of our boards are held in stock and are dispatched within seven days of receipt of order, please allow a maximum of 28 days for delivery – overseas readers allow extra if ordered by surface mail.

Back numbers or photostats of articles are available if required – see the *Back Issues* page for details. We do not supply kits or components for our projects.

Please check price and availability in the latest issue.

A large number of older boards are listed on our website.

Boards can only be supplied on a payment with order basis.

PROJECT TITLE	Order Code	Cost
★PIC Controlled Intruder Alarm	APR '02	339 £6.50
★PIC Big Digit Display	MAY '02	341 £6.02
★Biopic Heartbeat Monitor	JUNE '02	355 £5.71
★EPE StyloPIC	JULY '02	359 £6.50
★PIC World Clock	AUG '02	363 £5.39
Simple Audio Circuits-4 – Low Freq. Oscillator – Resonance Detector		364 £4.44 365 £4.28
Vinyl-To-CD Preamp	SEPT '02	366 £5.71
★Freebird Glider Control		367 £4.91
★Morse Code Reader		368 £5.23
Headset Communicator	OCT '02	369 £4.75
EPE Bounty Treasure Hunter		370 £4.77
★ ★ Digital I.C. Tester		371 £7.14
★PIC-Pocket Battleships – Software only		–
Transient Tracker	NOV '02	372 £4.75
★PICAXE Projects-1: Egg Timer; Dice Machine; Quiz Game Monitor (Multiboard)		373 £3.00 374 £5.39
★Tuning Fork & Metronome		375 £18.87
★ ★ EPE Hybrid Computer – Main Board } double- – Atom Board } sided		376 £11.57
★PICAXE Projects-2: Temperature Sensor; Voltage Sensor; VU Indicator (Multiboard)	DEC '02	373 £3.00 377 £5.07
★Versatile PIC Flasher		377 £5.07
★PICAXE Projects-3: Chaser Lights 6-Channel Mains Interface	JAN '03	373 £3.00 381 £5.08
EPE Minder – Transmitter – Receiver		378 £4.75 379 £5.39
★Wind Speed Monitor		380 £5.08
Tesla Transformer	FEB '03	382 £5.07
★Brainbot Buggy		383 £3.00
★Wind Tunnel		384 £6.02
200kHz Function Generator	MAR '03	385 £6.34
Wind-Up Torch Mk II		386 £4.75
★Driver Alert		387 £6.35
★Earth Resistivity Logger	APR '03	388 £6.02
★Intelligent Garden Lights Controller		389 £3.96
★PIC Tutorial V2 – Software only		–
Door Chime	MAY '03	390 £5.07
Super Motion Sensor		391 £5.55
Radio Circuits-1 MK484 TRF Receiver	JUNE '03	392 £4.44
Headphone Amp.		393 £4.28
★Fido Pedometer		394 £4.91
★PICronos L.E.D. Wall Clock		395 £14.65
EPE Mini Metal Detector	JULY '03	396 £4.28
Radio Circuits – 2 Q-Multiplier		397 £4.28
MW Reflex Radio		398 £4.60
Wave Trap		399 £4.28
Speaker Amplifier		400 £4.44
Ohmmeter Adaptor MkII		401 £4.60
Ultimate Egg Timer (Top Tenner)		403 £4.91
★EPE PIC Met Office	AUG '03	402 £10.46
Alarm System Fault Finder		404 £4.44
Radio Circuits-3 Regen. Radio		405 £5.07
Tuning Capacitor Board		406 £4.28
Master/Slave Intercom (Top Tenner)		407 £4.75
Two-Up (Top Tenner)		408 £4.91
Priority Referee (Top Tenner)	SEPT '03	410 £5.07
Vibration Alarm (Top Tenner)		411 £5.39
Radio Circuits-4 Varicap Tuner		412 £4.44
Coil Pack – General Coverage		413 £5.07
Coil Pack – Amateur Bands		414 £4.75
★PIC-A-Colour – Software only		–
Spooky Bug (Top Tenner)	OCT '03	409 £5.07
Radio Circuits-5 Crystal Marker		415 £4.44
Super Regen. Receiver		419 £5.07
Buffer Amplifier		420 £4.44
★ ★ Serial Interface for PICs and VB6		416 £5.23
★PIC Breakpoint – Software only		–
Anyone At Home – Logic Board	NOV '03	421 } Pair £6.35
– Relay Board		422 }
Radio Circuits-8 Direct Conversion SW Receiver		423 £6.02
★PIC Random L.E.D. Flasher		424 £4.60

PROJECT TITLE	Order Code	Cost
★PIC Virus Zapper Mk2	DEC '03	425 £5.72
Radio Circuits-7 SW Superhet Tuner/Mixer		426 £5.70
Christmas Cheeks (double-sided)		427 £4.44
★PIC Nim Machine – Software only		–
Bedside Nightlight (Top Tenner)	JAN '04	–
Sound Trigger		417 £4.44
Timing/Lamp		418 £4.60
Radio Circuits-8 Dual Conversion SW Receiver		–
I.F. Amp		428 £5.71
Signal-Strength Meter		429 £4.45
B.F.O./Prod. Detector		430 £4.75
★Car Computer (double-sided)		431 £7.61
★PIC Watering Timer – Software only		–
★GPS to PIC and PC Interface – Software only		–
Jazzy Necklace	FEB '04	432 pair £5.40
Sonic Ice Warning		433 £5.39
★LCF Meter		434 £5.00
★PIC Pug-of-War		435 £5.00
Bat-Band Converter	MAR '04	436 £4.76
★MIDI Health Check – Transmitter/Receiver		437 pair £7.61
Emergency Stand-by Light		438 £5.55
★PIC Mixer for RC Planes – Software only		–
★Teach-In '04 Part 5 – Software only		–
Infra-Guard	APR '04	439 £5.07
★EPE Seismograph Logger		–
Control Board		440 } pair £6.50
Sensor Amp. Board		441 }
★Moon Clock		442 £5.71
★Teach-In '04 Part 6 – Software only		–
In-Car Lap-Top PSU	MAY '04	443 £4.60
Beat Balance Metal Detector		444 £4.60
Teach-In '04 Part 7		–
Transmitter		445 £4.91
Receiver		446 £4.75
Moisture		447 £4.44
★PIC Quickstep	JUNE '04	448 £5.71
Body Detector MkII		449 £4.91
★Teach-In '04 Part 8 – Software only		–

EPE SOFTWARE

Software programs for *EPE* projects marked with a single asterisk ★ are available on 3.5 inch PC-compatible disks or free from our Internet site. The following disks are available: *PIC Tutorial V2* (Apr-June '03); *EPE Disk 3* (2000); *EPE Disk 4* (2001 – excl. PIC Toolkit TK3); *EPE Disk 5* (2002); *EPE Disk 6* (2003 – excl. Earth Resistivity and Met Office); *EPE Disk 7* (Jan 2004 to current cover date); *EPE Earth Resistivity Logger* (Apr-May '03); *EPE PIC Met Office* (Aug-Sept '03); *EPE Seismograph* (Apr-May '04); *EPE Teach-In 2000*; *EPE Spectrum*; *EPE Interface Disk 1* (October '00 issue to current cover date). *EPE Toolkit TK3* software is available on the *EPE PIC Resources* CD-ROM, £14.45. Its p.c.b. is order code 319, £8.24. ★ The software for these projects is on its own CD-ROM. The 3.5 inch disks are £3.00 each (UK), the CD-ROMs are £6.95 (UK). Add 50p each for overseas surface mail, and £1 each for airmail. All are available from the *EPE PCB Service*. All files can be downloaded free from our Internet FTP site, accessible via our home page at: www.epemag.wimborne.co.uk.

EPE PRINTED CIRCUIT BOARD SERVICE

Order Code Project Quantity Price

Name

Address

Tel. No.

I enclose payment of £..... (cheque/PO in £ sterling only) to:



**Everyday
Practical Electronics**
MasterCard, Amex, Diners
Club, Visa or Switch



Card No.

Valid From Expiry Date

Card Security Code Switch Issue No

(The last 3 digits on or just under the signature strip)


Signature

NOTE: You can also order p.c.b.s by phone, Fax, Email or via our Internet site on a secure server:

<http://www.epemag.wimborne.co.uk/shopdoor.htm>

**WHETHER ELECTRONICS IS YOUR HOBBY
OR YOUR LIVELIHOOD . . .
YOU NEED THE MODERN ELECTRONICS MANUAL
and the ELECTRONICS SERVICE MANUAL**

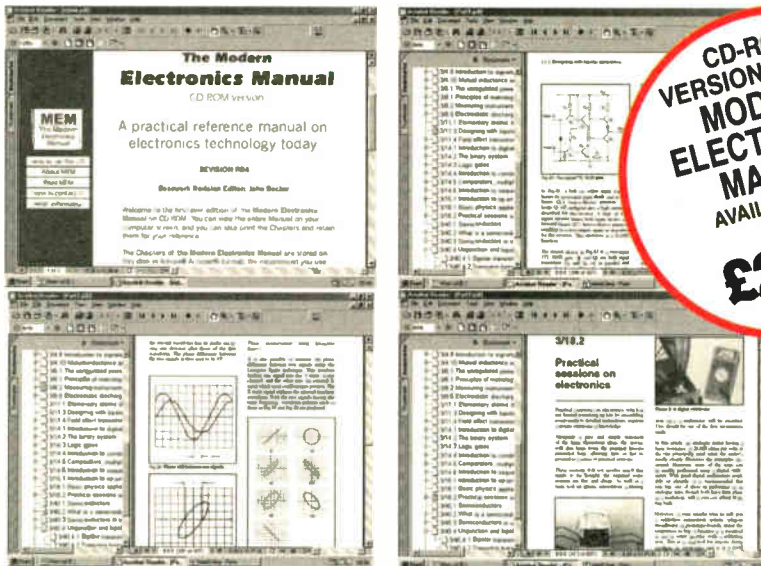THE MODERN ELECTRONICS MANUAL (CD-ROM VERSION ONLY)



**CD-ROM
VERSION OF THE
MODERN
ELECTRONICS
MANUAL
AVAILABLE NOW
ONLY
£29.95**

**The essential reference
work for everyone
studying electronics**

- Over 800 pages
- In-depth theory
- Projects to build
- Detailed assembly instructions
- Full components checklists
- Extensive data tables
- Manufacturers' web links
- Easy-to-use Adobe Acrobat format
- Clear and simple layout
- Comprehensive subject range
- Professionally written
- Supplements

**EVERYTHING YOU NEED TO GET
STARTED AND GO FURTHER IN ELECTRONICS!**

The revised CD-ROM edition of the Modern Electronics Base Manual (MEM) contains practical, easy-to-follow information on the following subjects:

BASIC PRINCIPLES: Electronic Components and their Characteristics (16 sections from Resistors and Potentiometers to Crystals, Crystal Modules and Resonators); Circuits Using Passive Components (10 sections); Power Supplies; The Amateur Electronics Workshop; The Uses of Semiconductors; Digital Electronics (6 sections); Operational Amplifiers; Introduction to Physics, including practical experiments; Semiconductors (5 sections) and Digital Instruments (3 sections).

CIRCUITS TO BUILD: There's nothing to beat the satisfaction of creating your own projects. From basic principles, like soldering and making printed circuit boards, to the tools needed for circuit-building, the Modern Electronics Manual and its Supplements describe clearly, with appropriate diagrams, how to assemble a radio, loudspeaker circuits, amplifiers, car projects,

a computer interface, measuring instruments, workshop equipment, security systems, medical and musical circuits, etc. The Base Manual describes 12 projects including a Theremin and a Simple TENS Unit.

ESSENTIAL DATA: Extensive tables on diodes, transistors, thyristors and triacs, digital and linear i.c.s.

EXTENSIVE GLOSSARY: Should you come across a technical word, phrase or abbreviation you're not familiar with, simply look up the glossary included in the Manual and you'll find a comprehensive definition in plain English.

The Manual also covers **Safety** and provides web links to component and equipment **Manufacturers and Suppliers**. The most comprehensive reference work ever produced at a price you can afford, the CD-ROM edition of **THE MODERN ELECTRONICS MANUAL** provides you with all the **essential** information you need.

THE MODERN ELECTRONICS MANUAL (MEM - CD-ROM version only)

Revised CD-ROM Edition of Basic Work: Contains over 800 pages of information in Adobe Acrobat format. Edited by John Becker.
Supplements: Additional CD-ROMs each containing approximately 500 pages of additional information on specific areas of electronics are available for £19.95 each. Information on the availability and content of each Supplement CD-ROM will be sent to you.
Presentation: CD-ROM suitable for any modern PC. Requires Adobe Acrobat Reader which is included on the MEM CD-ROM.

Price of the Basic Work: £29.95 POST FREE.

ORDER BOTH MANUALS TOGETHER AND SAVE £10

*A mass of well-organised and clearly explained information is brought to you by expert editorial teams whose combined experience ensures the widest coverage
Supplements to these unique publications, keep you abreast of the latest technology and techniques if required*

ELECTRONICS SERVICE MANUAL

(CD-ROM VERSION ONLY)

EVERYTHING YOU NEED TO KNOW TO GET STARTED IN REPAIRING AND SERVICING ELECTRONIC EQUIPMENT

SAFETY: Be knowledgeable about Safety Regulations, Electrical Safety and First Aid.

UNDERPINNING KNOWLEDGE: Specific sections enable you to Understand Electrical and Electronic Principles, Active and Passive Components, Circuit Diagrams, Circuit Measurements, Radio, Computers, Valves and Manufacturers' Data, etc.

PRACTICAL SKILLS: Learn how to identify Electronic Components, Avoid Static Hazards, Carry Out Soldering and Wiring, Remove and Replace Components.

TEST EQUIPMENT: How to Choose and Use Test Equipment, Assemble a Toolkit, Set Up a Workshop, and Get the Most from Your Multimeter and Oscilloscope, etc.

SERVICING TECHNIQUES: The Manual includes vital guidelines on how to Service Audio Amplifiers. The Supplements include similar guidelines for Radio Receivers, TV Receivers, Cassette Recorders, Video Recorders, Personal Computers, etc.

TECHNICAL NOTES: Commencing with the IBM PC, this section and the Supplements deal with a very wide range of specific types of equipment – radios, TVs, cassette recorders, amplifiers, video recorders etc..

REFERENCE DATA: Detailing vital parameters for Diodes, Small-Signal Transistors, Power Transistors, Thyristors, Triacs and Field Effect Transistors. Supplements include Operational Amplifiers, Logic Circuits, Optoelectronic Devices, etc.

ELECTRONICS SERVICE MANUAL (ESM – CD-ROM version only)

Basic Work: Contains around 900 pages of information. Edited by Mike Tooley BA

Supplements: Additional CD-ROMs each containing approximately 500 pages of additional information on specific areas of electronics are available for £19.95 each. Information on the availability and content of each Supplement CD-ROM will be sent to you.

Presentation: CD-ROM suitable for any modern PC. Requires Adobe Acrobat Reader which is included on the ESM CD-ROM.

Price of the Basic Work: £29.95 POST FREE

The essential work for servicing and repairing electronic equipment

- Around 900 pages
- Fundamental principles
- Troubleshooting techniques
- Servicing techniques
- Choosing and using test equipment
- Reference data
- Manufacturers' web links
- Easy-to-use Adobe Acrobat format
- Clear and simple layout
- Vital safety precautions
- Professionally written
- Supplements

CD-ROM VERSION OF THE ELECTRONICS SERVICE MANUAL AVAILABLE NOW ONLY **£29.95**

SPECIAL OFFER

£10 OFF Buy both Manuals together and save £10.

PLUS FREE POSTAGE TO ANYWHERE IN THE WORLD
(We use the VAT portion of the price to pay for overseas AIRMAIL postage)

Wimborne Publishing Ltd., Dept Y6, 408 Wimborne Road East, Ferndown, Dorset BH22 9ND. Tel: 01202 873872. Fax: 01202 874562.
Online shop: www.epemag.wimborne.co.uk/shopdoor.htm

PLEASE send me

THE MODERN ELECTRONICS MANUAL (CD-ROM version only)

ELECTRONICS SERVICE MANUAL (CD-ROM version only)

I enclose payment of £29.95 (for one Manual) or £49.90 for both Manuals (saving £10 by ordering both together).

FULL NAME
(PLEASE PRINT)

ADDRESS

.....POSTCODE

SIGNATURE

I enclose cheque/PO in UK pounds payable to Wimborne Publishing Ltd.

Please charge my Visa/Mastercard/Amex/Diners Club/Switch Switch Issue No

Card No

Valid From Expiry Date

Card Security Code (The last 3 digits on or just under the signature strip)

ORDER FORM

Simply complete and return the order form with your payment to the following address:

Wimborne Publishing Ltd,
Dept. Y6,
408 Wimborne Road East,
Ferndown,
Dorset BH22 9ND

Your CD-ROM(s) will be posted to you by first class mail or airmail within four working days of receipt of your order

Everyday Practical Electronics reaches twice as many UK readers as any other UK monthly hobby electronics magazine, our sales figures prove it. We have been the leading monthly magazine in this market for the last nineteen years.

If you want your advertisements to be seen by the largest readership at the most economical price our classified and semi-display pages offer the best value. The prepaid rate for semi-display space is £10 (+VAT) per single column centimetre (minimum 2.5cm). The prepaid rate for classified adverts is 40p (+VAT) per word (minimum 12 words).

All cheques, postal orders, etc., to be made payable to Everyday Practical Electronics. VAT must be added. Advertisements, together with remittance, should be sent to Everyday Practical Electronics Advertisements, Mill Lodge, Mill Lane, Thorpe-le-Soken, Essex CO16 0ED. Phone/Fax (01255) 861161.

For rates and information on display and classified advertising please contact our Advertisement Manager, Peter Mew as above.

VVT TRANSFORMERS
Transformers and Chokes for all types of circuits including specialist valve units
Custom design or standard range
High and low voltage
Variable Voltage Technology Ltd
Unit 3, Sheat Manor Farm, Chillerton, Newport, Isle of Wight, PO30 3HP
Tel: 0870 243 0414 Fax: 01983 721572
email: sales@vvt-cowes.freeserve.co.uk
www.vvttransformers.co.uk

X-10® Home Automation
We put you in control™
Why tolerate when you can automate?
An extensive range of 230V X-10 products and starter kits available. Uses proven Power Line Carrier technology, no wires required.
Products Catalogue available Online.
Worldwide delivery.
Laser Business Systems Ltd.
E-Mail: info@laser.com
<http://www.laser.com>
Tel: (020) 8441 9788
Fax: (020) 8449 0430

The Electronic WIZARDS
Apprenticeship
Invent & Inspire
www.kidstuff.co.uk
Electronic Projects
Every 2-weeks!
A fantastic inspirational Postal Course for the student inventor. Every 2 weeks a mystery 'WONDER BOX' will arrive at your door! Filled with projects to build, Tasks & Internet Forum all parts included!
Next Term 1 Starts: July 19th 2004
Apply NOW online or telephone: 01225 760629
www.kidstuff.co.uk
Just about the most exciting thing a boy or girl could do!

The Versatile, Programmable On Screen Display System
www.STV5730A.co.uk

PAL - NTSC compatible
● Fully programmable
● PIC 16F628 microcontroller
● Demo software code available
● OSD IC 28 by 11 screen
● I/O lines free to connect sensors or buttons
● Serial or PC keyboard interface versions
TEXT, GPS or DATA

PELTIER ELEMENTS HEATSINKS & COOLING FANS
WWW.GREENWELD.CO.UK
Tel: 01277 811042
New and Surplus Electrical, Mechanical and Electronic equipment for the hobbyist.
Ask for a free catalogue.

Low Cost PICs
PIC12F629-I/P - £0.75 each
PIC12F675-I/P - £0.99 each
PIC16F627A-I/P - £1.59 each
PIC16F84A-04/P - £2.99 each
PIC16F873-04SP - £3.79 each
PIC16F874-04P - £3.79 each
Pre-programmed with EPE source code £1.00 extra. All prices include VAT.
P&P £1.00 for all orders, order any qty. Fast delivery. Discount for bulk purchases.
Email orders and enquiries to: paddy@magee-electronics.co.uk
Magee Electronics, 1 Drumlamph Road, Magherafelt, N. Ireland, BT45 8LU
Tel: 02879 387090
www.magee-electronics.co.uk

BTEC ELECTRONICS TECHNICIAN TRAINING
VCE ADVANCED ENGINEERING ELECTRONICS AND ICT
HNC AND HND ELECTRONICS NVQ ENGINEERING AND IT
PLEASE APPLY TO COLLEGE FOR NEXT COURSE DATE
FULL PROSPECTUS FROM
LONDON ELECTRONICS COLLEGE (Dept EPE) 20 PENYWERN ROAD EARLS COURT, LONDON SW5 9SU
TEL: (020) 7373 8721

TRANSFORMERS
● Custom Wound ● Transformer Kits
● 1 Phase to 50kVA ● Coils up to 1m Dia.
● 3 Phase to 100kVA ● Transformer Rectifiers
● A.C. and D.C. Chokes ● Toroidals
● H.T. up to 5kV ● Motor Generators
Visit www.jemelec.com for details or request our free leaflet
Jemelec, Unit 7, Shirebrook Business Park, Mansfield, NG20 8RN
Tel: 0870 787 1769

TOTALROBOTS
ROBOTICS, CONTROL & ELECTRONICS TECHNOLOGY
High quality robot kits and components UK distributor of the OOPic microcontroller
Secure on-line ordering
Rapid delivery
Highly competitive prices
Visit www.totalrobots.com
Tel: 0208 823 9220

BOWOOD ELECTRONICS LTD
Suppliers of Electronic Components
Place a secure order on our website or call our sales line
All major credit cards accepted
Web: www.bowood-electronics.co.uk
7 Bakewell Road, Baslow, Derbyshire DE45 1RE
Sales: 01246 583777
Send 42p stamp for catalogue

PIC PROGRAMMER
USB/SERIAL KIT £24.95 + P&P
Other kits and components available
www.kitsandcomponents.co.uk
DP Developments, 68 Horden View, Blackburn BB2 5DH. Tel: 08707 442843

SWAYSCIENCE
LOW TEMPERATURE DESOLDERING (60°C-80°C)
Remove electronic components without heat damage to semiconductors or p.c.b.s.
★ Cost Effective ★ Free Details
★ Safer than most solder itself
★ Trade and Retail Enquiries Welcome
TEL: 0778 770 3785

Miscellaneous

FREE! PROTOTYPE PRINTED CIRCUIT BOARDS! Free prototype p.c.b. with quantity orders. Call Patrick on 028 9073 8897 for details. Agar Circuits, Unit 5, East Belfast Enterprise Park, 308 Albertbridge Road, Belfast BT5 4GX.

PRINTED CIRCUIT BOARDS - QUICK SERVICE. Prototype and production artwork raised from magazines or draft designs at low cost. PCBs designed from schematics. Production assembly, wiring and software programming. For details contact Patrick at Agar Circuits, Unit 5, East Belfast Enterprise Park, 308 Albertbridge Road, Belfast, BT5 4GX. Phone 028 9073 8897, Fax 028 9073 1802, Email agar@argonet.co.uk.

VALVES AND ALLIED COMPONENTS IN STOCK. Phone for free list. Valves, books and magazines wanted. Geoff Davies (Radio), tel. 01788 574774.

KITS, TOOLS, COMPONENTS. S.a.e. catalogue: Sir-Kit Electronics, 52 Severn Road, Clacton, CO15 3RB. www.geocities.com/sirkituk.

RETIREMENT SALE! All items half price with ref. to our catalogue No. 308. Credit/debit cards, cheques, POs accepted. Send your orders to: FML Electronics, Freepost NEA3627, Bedale DL8 2BR. Finally, thanks to all our customers who have supported us over the last 32 years. PS: Is there anyone interested in taking over?

PELTIER ELEMENTS, HEATSINKS AND FANS for your low-cost experiments. www.sciencestore.co.uk. Tel: 01277 811042.

Computer Software

ELECTRONICS AND ELECTRICAL V8.2 colourful highly interactive software as used in schools and colleges. Now downloadable for just £4.95, normally £120. FREE trial download www.eptsoft.com.

GCSE MATHS V8.2 colourful highly interactive software as used in schools and colleges. Now downloadable for just £4.95, normally £120. FREE trial download www.eptsoft.com.



Get your magazine "instantly" anywhere in the world - buy from the web.

TAKE A LOOK, A FREE ISSUE IS AVAILABLE

A one year subscription (12 issues) costs just \$10.99 (US)

www.epemag.com

N. R. BARDWELL LTD (Est. 1948)

100	Signal Diodes 1N4148	£1.00	80	Ass'd. capacitors 1nF to 1µF	£1.00
75	Rectifier Diodes 1N4001	£1.00	200	Ass'd. disc ceramic capacitors	£1.00
50	Rectifier Diodes 1N4007	£1.00	50	Ass'd. S&K Presets (sm, stand, cermet)	£1.00
10	W01 Bridge Rectifiers	£1.00	50	Ass'd. RF chokes (inductors)	£1.00
10	555 Timer I.C.s	£1.00	25	Ass'd. grommets	60p
4	741 Op Amps	£1.00	8	Ass'd. diode switches	£1.00
50	Assorted Zener Diodes 400mW	£1.00	8	Ass'd. push-button switches, multi-bank, multi-pole	£1.00
12	Assorted 7-segment Displays	£1.00	30	Ass'd. diode sockets up to 40 way	£1.00
35	Assorted I.e.d.s, var shapes, colours & sizes	£1.00	10	TV coast plugs, plastic	£1.00
25	5mm I.e.d.s, red or green or yellow	£1.00	40	metres very fine connecting wire, red	£1.00
25	3mm I.e.d.s, red or green or yellow	£1.00	20	1in glass reed switches	£1.00
75	5mm I.e.d.s, green, 6.5mm legs	£1.00	100	Any ons value ¼W 5% of resistors range 1R to 10M	£0.45
50	Axial I.e.d.s, 2mm red Diode Package	£1.00	10	7812 Voltage Regulators	£1.00
25	Ass'd. High Brightness I.e.d.s, var cols	£1.00	300	Ass'd. resistors, ¼W/½W, mostly on tapes	£1.00
20	BC182L Transistors	£1.00			
25	BC212L Transistors	£1.00			
30	BC237 Transistors	£1.00			
20	BC327 Transistors	£1.00			
30	BC328 Transistors	£1.00			
30	BC547 Transistors	£1.00			
20	BC547B Transistor	£1.00			
30	BC548 Transistors	£1.00			
30	BC549 Transistors	£1.00			
25	BC557 Transistors	£1.00			
30	BC558 Transistors	£1.00			
25	BC559 Transistors	£1.00			
20	2N3904 Transistors	£1.00			
100	1nF 50V wkg Axial Capacitors	£1.00			
80	Ass'd capacitors electrolytic	£1.00			

288 Abbeydale Road, Sheffield S7 1FL
Phone (local rate): 0845 166 2329
Fax: 0114 255 5039

e-mail: sales@bardwells.co.uk
web: www.bardwells.co.uk
Prices include VAT. Postage £1.85
44p stamp for lists or disk
POs, Cheques and Credit Cards accepted
SEE OUR WEB PAGES FOR MORE COMPONENTS AND SPECIAL OFFERS

CHEVET SUPPLIES

157 DICKSON ROAD, BLACKPOOL FY1 2EU.

TEL: 01253 751858 FAX 01253 302979 EMAIL chevet@globalnet.co.uk

WEB: www.chevet-supplies.co.uk

POs, cheque and credit card orders taken. P&P £2 under £12. Over FREE unless otherwise stated. Send two 1st class stamps for Vatalogue.

Digital handheld LCR meter, 2MHz-20Hz; 2,000pF-200µF; 2k to 20 Meg. Brand new with test leads and manual. £44. P&P £4.50.
Ex-RAF Bubble Sextant, ex-Canberra/Vulcan, in conical metal transit case, 18in. x 10in. x 4in., used but in good condition. £59. Carriage £13.
Ex-point-of-sale I.c.d., keyboard and magnetic card reader unit. £13.50. Carriage £7.50 2 for £35 incl. carriage.
5mm red I.e.d.s 30 for £1.00
555 timers 10 for £1.00
BC557 25 for £1.00
BC182L 25 for £1.00
BDY91 4 for £1.00
OC42 military spec. 10 for £2.50
ILD74 8-pin dual opto 2 for £1.00
40-pin gold turned pin I.c. sockets 10 for £2.00

Double-sided copper clad board,
105mm x 115mm x 1mm 2 for £1.50
B7G valve base 2 for £1.00
B9A valve base 2 for £1.00
Octal valve base 2 for £1.00
Vintage 1 watt res., mixed values 50 for £3.00
Vintage ½ watt 30 for £2.25
250V 10A d.p.s.t. toggle 2 for £1.00
954 Acorn valves 2 for £8.00
0-01µF 2000V wkg polyester caps 5 for £3.00
Wirewound resistors, 10Ω to 20k, 3W to 10W, mixed values 30 for £4.00. P&P £2.00
Fused IEC sockets 4 for £1.00
68µF 480V wkg can elect £4.50. 2 for £8.00
¼W metal/carbon film resistors 250 for £1.00
Keyswitch, 250V, 2A 2 for £3.00
Heavy duty 80W mains soldering irons £12.50
P&P £4.00

SQUIRES

MODEL & CRAFT TOOLS

A COMPREHENSIVE RANGE OF MINIATURE HAND AND POWER TOOLS AND AN EXTENSIVE RANGE OF ELECTRONIC COMPONENTS

FEATURED IN A FULLY ILLUSTRATED 656 PAGE MAIL ORDER CATALOGUE

2004 ISSUE

**SAME DAY DESPATCH
FREE POST AND PACKAGING**

Catalogues: FREE OF CHARGE to addresses in the UK. Overseas: CATALOGUE FREE, postage at cost charged to credit card

SHOP EXTENSION NOW OPEN

Squires, 100 London Road,
Bognor Regis, West Sussex, PO21 1DD



TEL: 01243 842424
FAX: 01243 842525

VISA



National College of Technology

DISTANCE LEARNING COURSES

Electronic Circuits Electronic Testing & Fault Finding
Digital Circuits Programmable Logic Controllers
Mathematics Mechanics & Mechanisms

These courses lead to a BTEC QUALIFICATION and are suitable for beginners and those with more experience, needing to update their skills.

Register NOW and learn at your own pace with tutor support available to help you succeed.

For further details telephone

08456 345 445

or visit our web site

www.oakcad.co.uk/nct.aspx



NCT is part of the OakCAD Training Group.

Watch Slides on TV.

Make videos of your slides. Digitise your slides (using a video capture card)
 "Liesgang diatv" automatic slide viewer with built in high quality colour TV camera. It has a composite video output to a phono plug (SCART & BNC adaptors are available). They are in very good condition with few signs of use. More details see www.diatv.co.uk.
 £91.91 + VAT = £108.00



Board cameras all with 512 x 582 pixels 8.5mm 1/3 inch sensor and composite video out. All need to be housed in your own enclosure and have fragile exposed surface mount parts. They all require a power supply of between 10V and 12V DC 150mA.
 47MIR size 60 x 36 x 27mm with 6 infra red LEDs (gives the same illumination as a small torch but is not visible to the human eye) £37.00 + VAT = £43.48
 30MP size 32 x 32 x 14mm spy camera with a fixed focus pin hole lens for hiding behind a very small hole £35.00 + VAT = £41.13
 40MC size 39 x 38 x 27mm camera for 'C' mount lens these give a much sharper image than with the smaller lenses £32.00 + VAT = £37.60
 Economy C mount lenses all fixed focus & fixed iris
 VSL1220F 12mm F1.6 12 x 15 degrees viewing angle £15.97 + VAT £18.76
 VSL4022F 4mm F1.22 63 x 47 degrees viewing angle £17.65 + VAT £20.74
 VSL6022F 6mm F1.22 42 x 32 degrees viewing angle £19.05 + VAT £22.38
 VSL8020F 8mm F1.22 32 x 24 degrees viewing angle £19.90 + VAT £23.38

Better quality C Mount lenses

VSL1614F 16mm F1.6 30 x 24 degrees viewing angle £26.43 + VAT £31.06
 VWL813M 8mm F1.3 with iris 56 x 42 degrees viewing angle £77.45 + VAT = £91.00
 1206 surface mount resistors E12 values 10 ohm to 1M ohm
 100 of 1 value £1.00 + VAT 1000 of 1 value £5.00 + VAT

866 battery pack originally intended to be used with an orbital mobile telephone it contains 10 1.6Ah sub C batteries (42 x 22 dia. the size usually used in cordless screwdrivers etc.) the pack is new and unused and can be broken open quite easily
 £7.46 + VAT = £8.77



Please add £1.66 + vat = £1.95 postage & packing per order

JPG Electronics

Shaws Row, Old Road, Chesterfield, S40 2RB.

Tel 01246 211202 Fax 01246 550959

Mastercard/Visa/Switch

Callers welcome 9.30 a.m. to 5.30 p.m. Monday to Saturday

SHERWOOD ELECTRONICS

FREE COMPONENTS

Buy 10 x £1 Special Packs and choose another one FREE

SP1	15 x 5mm Red LEDs	SP133	20 x 1N4004 diodes
SP2	12 x 5mm Green LEDs	SP134	15 x 1N4007 diodes
SP3	12 x 5mm Yellow LEDs	SP135	6 x Miniature slide switches
SP5	25 x 5mm 1 part LED clips	SP136	3 x BF950 transistors
SP6	15 x 3mm Red LED	SP137	4 x W005 1.5A bridge rectifiers
SP7	12 x 3mm Green LEDs	SP138	20 x 2.2/63V radial elect. caps.
SP8	10 x 3mm Yellow LEDs	SP140	3 x W04 1.5A bridge rectifiers
SP9	25 x 3mm 1 part LED clips	SP142	2 x CMOS 4017
SP10	100 x 1N4148 diodes	SP143	5 Pairs min. crocodile clips (Red & Black)
SP11	30 x 1N4001 diodes	SP146	10 x 2N3704 transistors
SP12	30 x 1N4002 diodes	SP147	5 x Stripboard 9 strips x 25 holes
SP18	20 x BC182 transistors	SP151	4 x 8mm Red LEDs
SP20	20 x BC184 transistors	SP152	4 x 8mm Green LEDs
SP23	20 x BC549 transistors	SP153	4 x 8mm Yellow LEDs
SP24	4 x CMOS 4001	SP154	15 x BC548 transistors
SP25	4 x 555 timers	SP156	3 x Stripboard, 14 strips x 27 holes
SP26	4 x 741 Op.Amps	SP160	10 x 2N3904 transistors
SP28	4 x CMOS 4011	SP161	10 x 2N3906 transistors
SP29	3 x CMOS 4013	SP165	2 x LF351 Op.Amps
SP33	4 x CMOS 4081	SP166	20 x 1N4003 diodes
SP34	20 x 1N914 diodes	SP167	5 x BC107 transistors
SP36	25 x 10/25V radial elect. caps.	SP168	5 x BC108 transistors
SP37	12 x 100/35V radial elect. caps.	SP172	4 x Standard slide switches
SP39	10 x 470/16V radial elect. caps.	SP173	10 x 220/25V radial elect. caps.
SP40	15 x BC237 transistors	SP174	20 x 22/25V radial elect. caps.
SP41	20 x Mixed transistors	SP175	20 x 1/63V radial elect. caps.
SP42	200 x Mixed 0.25W C.F. resistors	SP177	10 x 1A 20mm quick blow fuses
SP47	5 x Min. PB switches	SP178	10 x 2A 20mm quick blow fuses
SP49	4 x 5 metres stranded core wire	SP181	5 x Phono plugs - assd colours
SP102	20 x 8-pin DIL sockets	SP182	20 x 4-7/63V radial elect. caps.
SP103	15 x 14-pin DIL sockets	SP183	20 x BC547 transistors
SP104	15 x 16-pin DIL sockets	SP187	15 x BC239 transistors
SP105	4 x 74LS00	SP189	4 x 5 metres solid core wire
SP109	15 x BC557 transistors	SP192	3 x CMOS 4066
SP112	4 x CMOS 4093	SP195	3 x 10mm Yellow LEDs
SP115	3 x 10mm Red LEDs	SP197	6 x 20 pin DIL sockets
SP116	3 x 10mm Green LEDs	SP198	5 x 24 pin DIL sockets
SP118	2 x CMOS 4047	SP199	5 x 2.5mm mono jack plugs
SP124	20 x Assorted ceramic disc caps	SP200	5 x 2.5mm mono jack sockets
SP126	6 x Battery clips - 3 ea. PP3 + PP9		
SP130	100 x Mixed 0.5W C.F. resistors		
SP131	2 x TL071 Op.Amps		

RESISTOR PACKS - C.Film

RP3	5 each value - total 365 0-25W	£3.20
RP7	10 each value - total 730 0-25W	£4.45
RP10	1000 popular values 0-25W	£6.35
RP4	5 each value-total 345 0-5W	£4.10
RP8	10 each value-total 690 0-5W	£6.75
RP11	1000 popular values 0-5W	£8.60

2004 Catalogue now available £1 inc. P&P or FREE with first order. P&P £1.50 per order. NO VAT. Cheques and Postal Orders to: Sherwood Electronics, 7 Williamson St., Mansfield, Notts. NG19 6TD.

ADVERTISERS INDEX

N. R. BARDWELL	363
B.K. ELECTRONICS	Cover (iv)/316
BRUNNING SOFTWARE	299
BULL GROUP	Cover (ii)
CRICKLEWOOD ELECTRONICS	308
DISPLAY ELECTRONICS	294
ENERGISE TECHNOLOGY	363
ESR ELECTRONIC COMPONENTS	302
FOREST ELECTRONIC DEVELOPMENTS	311
JPG ELECTRONICS	364
KIT RADIO COMPANY	363
LABCENTER	Cover (iii)
MAGENTA ELECTRONICS	300/301
MATRIX MULTIMEDIA	316
MILFORD INSTRUMENTS	321
NATIONAL COLLEGE OF TECHNOLOGY	363
PEAK ELECTRONIC DESIGN	309
PICO TECHNOLOGY	324
QUASAR ELECTRONICS	296/297
SHERWOOD ELECTRONICS	364
SQUIRES	363
STEWART OF READING	353

ADVERTISEMENT MANAGER: PETER J. MEW

ADVERTISEMENT OFFICES:

EVERYDAY PRACTICAL ELECTRONICS, ADVERTISEMENTS, MILL LODGE, MILL LANE, THORPE-LE-SOKEN, ESSEX CO16 0ED.

Phone/Fax: (01255) 861161

For Editorial address and phone numbers see page 303

EPE SUBSCRIPTIONS

Subscriptions for delivery direct to any address in the UK: 6 months £16.50, 12 months £31, two years £57; Overseas: 6 months £19.50 standard air service or £28.50 express airmail, 12 months £37 standard air service or £55 express airmail, 24 months £69 standard air service or £105 express airmail.

Cheques or bank drafts (in £ sterling only) payable to *Everyday Practical Electronics* and sent to EPE Subs. Dept., Wimborne Publishing Ltd., 408 Wimborne Road East, Ferndown, Dorset BH22 9ND. Tel: 01202 873872. Fax: 01202 874562. Email: subs@epemag.wimborne.co.uk. Also via the Web at <http://www.epemag.wimborne.co.uk>. Subscriptions start with the next available issue. We accept MasterCard, Amex, Diners Club, Switch or Visa. (For past issues see the Back Issues page.)

ONLINE SUBSCRIPTIONS

Online subscriptions, for downloading the magazine via the Internet, \$10.99US (approx. £7) for one year available from www.epemag.com.

USA/CANADA SUBSCRIPTIONS

To subscribe to *EPE* from the USA or Canada please telephone Express Mag toll free on 1877 363-1310 and have your credit card details ready. Or fax (514) 355 3332 or write to Express Mag, PO Box 2769, Plattsburgh, NY 12901-0239 or Express Mag, 8155 Larney Street, Anjou, Quebec, H1J 2L5.

Email address: expmag@expressmag.com.


Web site: www.expressmag.com.

USA price \$60(US) per annum, Canada price \$97(Can) per annum - 12 issues per year.

Everyday Practical Electronics, periodicals pending, ISSN 0262 3617 is published twelve times a year by Wimborne Publishing Ltd., USA agent USACAN at 1320 Route 9, Champlain, NY 12919. Subscription price in US \$60(US) per annum. Periodicals postage paid at Champlain NY and at additional mailing offices. POSTMASTER: Send USA and Canada address changes to *Everyday Practical Electronics*, c/o Express Mag., PO Box 2769, Plattsburgh, NY, USA 12901-0239.

PROTEUS

The Complete Electronics Design System

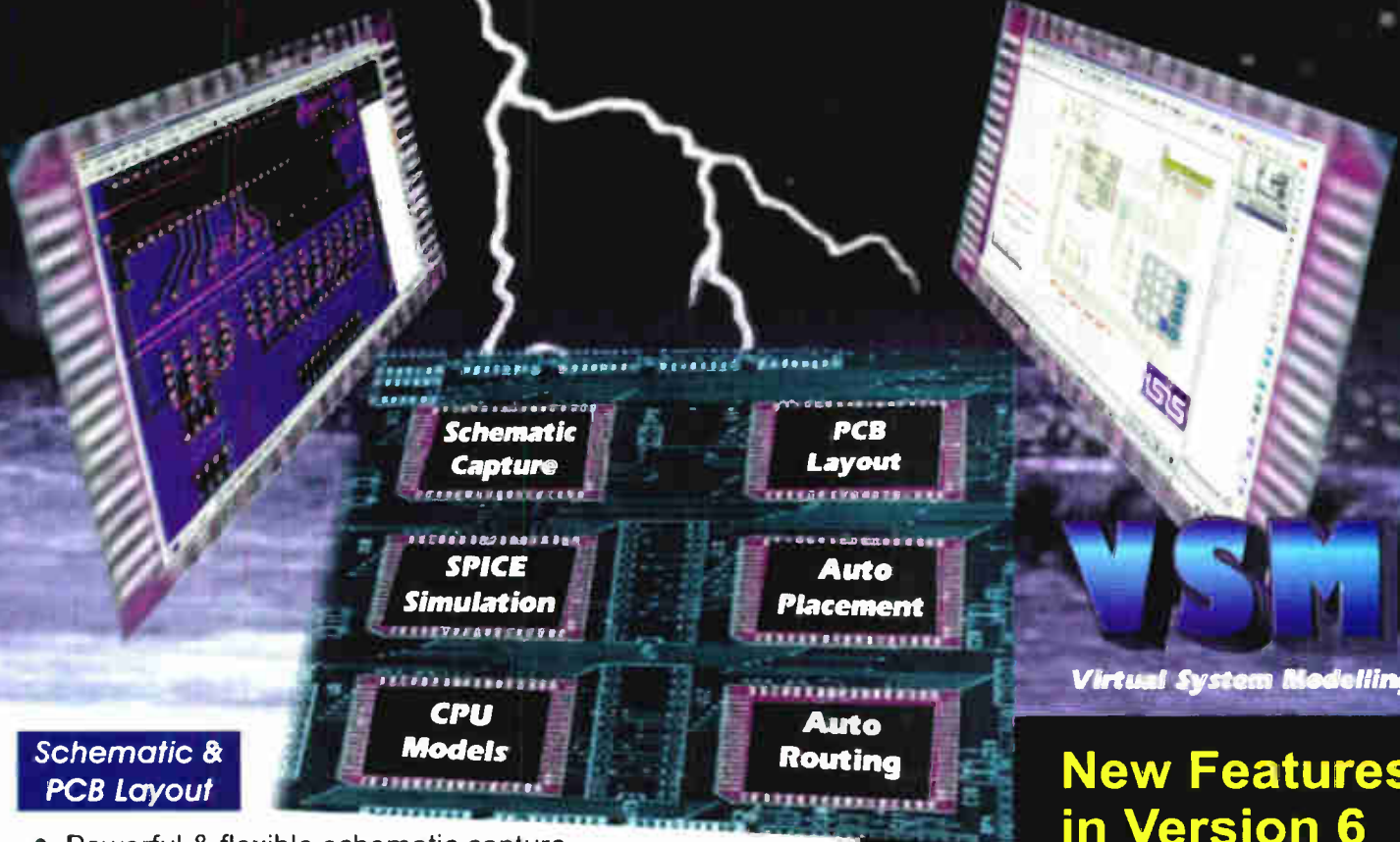

Schematic & PCB Layout

- Powerful & flexible schematic capture.
- Auto-component placement and rip-up/retry PCB routing.
- Polygonal gridless ground planes.
- Libraries of over 8000 schematic and 1000 PCB parts.
- Bill of materials, DRC reports and much more.

Mixed Mode SPICE Circuit Simulation

- Berkeley SPICE3F5 simulator with custom extensions for true mixed mode and interactive simulation.
- 6 virtual instruments and 14 graph based analysis types.
- 6000 models including TTL, CMOS and PLD digital parts.
- Fully compatible with manufacturers' SPICE models.

Proteus VSM - Co-simulation and debugging for popular Micro-controllers

- Supports PIC AVR 8051, HC11 and ARM micro controllers
- Co-simulate target firmware with your hardware design.
- Includes interactive peripheral models for LED and LCD displays, switches, keypads, virtual terminal and much, much more.
- Provides source level debugging for popular compilers and assemblers from Crownhill, IAR, Keil, and others.

New Features in Version 6

- Drag and drop toolbars.
- Visual PCB packaging tool.
- Improved route editing.
- Point and click DRC report.
- Multiple design rules (per net).
- Multiple undo/redo.

Call Now for Upgrade Pricing

**Works with
PIC Basic Plus
from Crownhill
Associates**

labcenter
Electronics
53-55 Main Street, Grassington. BD23 5AA

Tel: 01756 753440
Fax: 01756 752857
Contact us for
Free Demo CD

www.labcenter.co.uk
info@labcenter.co.uk



POWER AMPLIFIER MODULES-LOUDSPEAKERS-MIXERS 19 INCH STEREO AMPLIFIERS-ACTIVE CROSS/OVERS.

- * PRICES INCLUDE V.A.T.
- * PROMPT DELIVERY

OMP MOS-FET POWER AMPLIFIERS HIGH POWER, TWO CHANNEL 19 INCH RACK

10,000's
SOLD
TO PRO
USERS



THE RENOWNED MXF SERIES OF POWER AMPLIFIERS

FOUR MODELS:- MXF200 (100W + 100W) MXF400 (200W + 200W)
MXF600 (300W + 300W) MXF900 (450W + 450W)

ALL POWER RATINGS ARE R.M.S. INTO 4 OHMS, WITH BOTH CHANNELS DRIVEN
FEATURES:- * Independent power supplies with two toroidal transformers * Twin L.E.D. Vu Meters * Level controls * Illuminated on/off switch * Jack / XLR inputs * Speaker Outputs * Standard 775mv inputs * Open and Short circuit proof * Latest Mos-Fets for stress free delivery into virtually any load * High slew rate * Very low distortion * Aluminium cases * MXF600 & MXF900 fan cooled with D.C. Loudspeaker and thermal protection.

USED THE WORLD OVER IN CLUBS, PUBS, CINEMAS, DISCOS ETC

SIZES:-
MXF200 W19" D11" H3 1/2" (2U)
MXF400 W19" D12" H5 1/4" (3U)
MXF600 W19" D13" H5 1/4" (3U)
MXF900 W19" D14" H5 1/4" (3U)

PRICES:- MXF200 £175.00 MXF400 £233.85
MXF600 £329.00 MXF900 £449.15
SPECIALIST CARRIER DEL £12.50 Each



ABSOLUTE HIGH END CLASS D AMPLIFIER

The OMP MFD600 can be used as a stand alone monoblock amplifier or fitted into existing loudspeakers to make them active

- Compact design due to switch mode P.S.U.
- 90% Efficient high switching frequency
- Small size, fits in a 110mm x 92mm opening
- Neutrik® Combi input balanced / unbalanced
- Output fully protected
- Status LEDs - Presence / Clip / Protect
- 600W / 2 Ohm - 500W / 4 Ohm - 300W / 8 Ohm
- All powers in R.M.S.
- Volume control. Input sensitivity 775mV
- Freq. Response 2Hz-20kHz
- Light weight 3kg

**Stunning performance
Audiophile Quality**



For further information please look at our website at www.bkelec.com and click on the modules and hybrids button

Special quantity pricing and customised artwork for OEM's.

Price £281.12 Inc Vat Each or £499.00 Per Pair when quoting this advert

Carriage UK Mainland Only £8.00

100 WATT ACTIVE SUB BASS AMPLIFIER PANEL



AN ACTIVE SUB BASS AMPLIFIER WITH A TRUE 100W RMS OUTPUT SUPERB CONSTRUCTION WITH THE FACILITIES TO INTEGRATE SEAMLESSLY INTO MOST HI-FI OR HOME CINEMA SETUPS. USE THIS PANEL PLUS ONE OF OUR LOUSPEAKERS TO MAKE YOUR OWN SUB WOOFER THAT WILL MATCH OR BEAT MOST COMMERCIALY AVAILABLE SUB WOOFERS.

FEATURES:- * 100W RMS INTO 8 OHMS * HIGH AND LOW LEVEL INPUTS * TOROIDAL TRANSFORMER * SHORT CIRCUIT PROTECTION * D.C. SPEAKER PROTECTION * FREQUENCY ROLL OFF, LOWER 10Hz, UPPER 60Hz TO 240Hz (FULLY ADJUSTABLE) * AC3 COMPATIBLE FILTER CAN BE BYPASSED FOR 5-1 FORMATS. * AIRTIGHT CONSTRUCTION * TENS OF THOUSANDS OF OUR PANELS ALREADY IN USE. * COMPLETE WITH LEADS

SPECIFICATIONS:- * POWER 100W RMS @ 8 OHMS * FREQ RESP. 10Hz-15kHz -3dB * DAMPING FACTOR >200 * DISTORTION 0.05% * S/N A WEIGHTED >100dB * SUPPLY 230V A.C. * WEIGHT 2.7kg * SIZE H254 X W254 X D94mm

THERE ARE 2 VERSIONS OF THE ABOVE PANEL AVAILABLE :- **BSB100/8 8 OHM VERSION** BSB100/4 4 OHM VERSION BOTH PANELS ARE PRICED AT £117.44 + £5.00 P&P INCL. V.A.T. CHECK WEBSITE FOR PANELS UP TO 500W

FLIGHTCASED LOUSPEAKERS

A new range of quality loudspeakers, designed to take advantage of latest loudspeaker technology and enclosure designs. All models utilise high quality studio cast aluminium loudspeakers with factory fitted grilles, wide dispersion constant directivity horns, extruded aluminium corner protection and steel ball corners, complimented with heavy duty black covering. The enclosures are fitted as standard with top hats for optional loudspeaker stands. The FC15-300 incorporates a large 16 X 6 inch horn. All cabinets are fitted with the latest Speakon connectors for your convenience and safety. Five models to choose from.

WEDGE MONITOR



PLEASE NOTE:- POWER RATINGS QUOTED ARE IN WATTS R.M.S. FOR EACH INDIVIDUAL CABINET ALL ENCLOSURES ARE 8 OHMS

15" 15 Inch speaker
12" 12 Inch speaker

- ibl FC15-300 WATTS Freq Range 35Hz-20kHz, Sens 101dB, Size H695 W502 D415mm Price:- £299.00 per pair Size H600 W405 D300mm Price:- £249.00 per pair
- ibl FC12-200 WATTS Freq Range 40Hz-20kHz, Sens 97dB, Size H600 W405 D300mm Price:- £199.00 per pair
- ibl FC12-100 WATTS Freq Range 45Hz-20kHz, Sens 100dB, Size H546 W380 D300mm Price:- £179.00 per pair
- ibl WM12-200 WATTS Freq Range 40Hz-20kHz, Sens 97dB, Size H418 W600 D385mm

SPECIALIST CARRIER DEL:- £12.50 per pair, wedge monitor £7.00 each
Optional Metal Stands PRICE:- £49.00 per pair Delivery:- £6.00

OMP MOS-FET POWER AMPLIFIER MODULES

SUPPLIED READY BUILT AND TESTED

These modules now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models are available to suit the needs of the professional and hobby market i.e. Industry, Leisure, Instrumental and Hi-Fi etc. When comparing prices, NOTE that all models include toroidal power supply, integral heatsink, glass fibre P.C.B. and drive circuits to power a compatible Vu meter. All models are open and short circuit proof

THOUSANDS OF MODULES PURCHASED BY PROFESSIONAL USERS



OMP/MF 100 Mos-Fet Output Power 110 watts R.M.S. into 4 ohms, frequency response 1Hz - 100kHz -3dB, Damping Factor >300, Slew Rate 45V/uS, T.H.D. typical 0.002%, Input Sensitivity 500mV, S.N.R. 110dB, Size 300 x 123 x 60mm. Price:- £43.85 + £4.00 P&P

OMP/MF 200 Mos-Fet Output Power 200 watts R.M.S. into 4 ohms, frequency response 1Hz - 100kHz -3dB, Damping Factor >300, Slew Rate 50V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. 110dB, Size 300 x 155 x 100mm. Price:- £67.35 + £4.00 P&P

OMP/MF 300 Mos-Fet Output Power 300 watts R.M.S. into 4 ohms, frequency response 1Hz - 100kHz -3dB, Damping Factor >300, Slew Rate 60V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. 110dB, Size 330 x 175 x 100mm. Price:- £84.75 + £5.00 P&P

OMP/MF 450 Mos-Fet Output Power 450 watts R.M.S. into 4 ohms, frequency response 1Hz - 100kHz -3dB, Damping Factor >300, Slew Rate 75V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. 110dB, Fan Cooled, D.C. Loudspeaker Protection, 2 Second Anti Thump Delay, Size 385 x 210 x 105mm. Price:- £137.85 + £6.00 P&P

OMP/MF 1000 Mos-Fet Output Power 1000 watts R.M.S. into 2 ohms, frequency response 1Hz - 100kHz -3dB, Damping Factor >300, Slew Rate 75V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. 110dB, Fan Cooled, D.C. Loudspeaker Protection, 2 Second Anti Thump Delay, Size 422 x 300 x 125mm. Price:- £264.00 + £12.00 P&P

NOTE: MOS-FET MODULES ARE AVAILABLE IN TWO VERSIONS: STANDARD - INPUT SENS 500mV, BANDWIDTH 100kHz OR PEC (PROFESSIONAL EQUIPMENT COMPATIBLE) - INPUT SENS 775mV, BANDWIDTH 50kHz ORDER STANDARD OR PEC

WHARFEDALE - CHALLENGER COMPETITION SERIES CAR SUB WOOFERS

A superb range of car sub woofer loudspeakers manufactured by Wharfedale. Five models to choose from. All 4 Ohm



Challenger ProBass professional series sub woofers with cast aluminium chassis, heavy duty magnets and fitted with a steel protective grille (Not Shown)
PB-10 10 Inch 100W RMS 300W Max Price £29.37
PB-15 15 Inch 300W RMS 800W Max Price £45.82

Titan Competition series with pressed steel chassis (No Grille)
TC10-150 10 Inch 150W RMS 400W Max Price £28.20
TC12-200 12 Inch 200W RMS 600W Max Price £36.42
TC15-300 15 Inch 300W RMS 800W Max Price £43.47

Shown TC15-300

For more bargains go to www.bkelec.com and click on the bargain corner button

Carriage £8.00 any quantity

A punchy 10 Inch, a shockingly powerful 12 Inch and an awesome 15 Inch that will make your ears inform your eyes what they are missing out on ! CAR HI-FI magazine had this to say about the 10 Inch 150W sub. "This debutante needs a good shove by a punchy amplifier before it stirs, but when it does, the lion roars. There's no doubting the authority it carries, and there's a highly prominent musical element - precise and snappy!" Please note we have tried these loudspeakers for PA use with great success with our MXF range of amplifier and OMP MF mosfet modules.

B.K. ELECTRONICS

REF D8

UNIT 1 COMET WAY, SOUTHEND-ON-SEA, ESSEX. SS2 6TR.
TEL.: 01702-527572 FAX.: 01702-420243

Web:- <http://www.bkelec.com> E-Mail sales@bkelec.com



DELIVERY CHARGES:- PLEASE INCLUDE AS ABOVE TO A MAXIMUM AMOUNT £30.00. OFFICIAL ORDERS FROM SCHOOL COLLEGES, GOVT. PLCs ETC. PRICES INCLUSIVE OF V.A.T. SALES COUNTER CREDIT CARD ORDERS ACCEPTED BY POST PHONE OR FAX.

