

RADIO... ELECTRONICS... INSTRUMENTS... AUDIO...

practical WIRELESS

55p


Australia 95c
New Zealand \$1.10
South Africa 90c
Malaysia \$3.50

APRIL 1980



PULL-OUT 8-PAGE SUPPLEMENT

EXTRA

RADIO SERVICING AND ALIGNMENT PROCEDURES

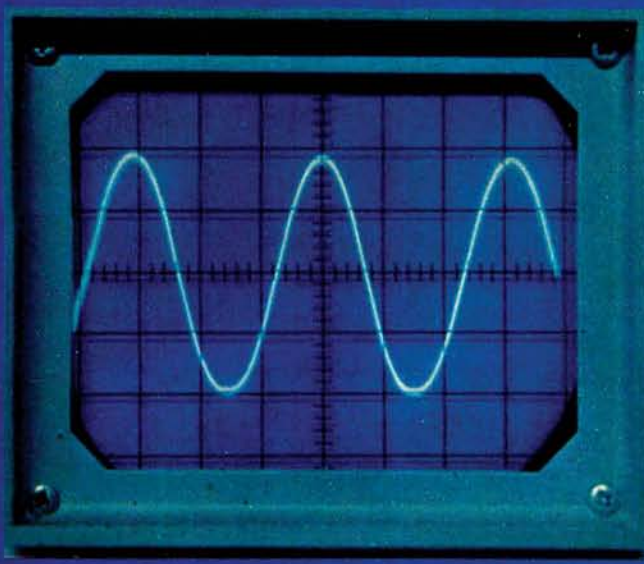

LOW FREQUENCY SIGNAL GENERATOR

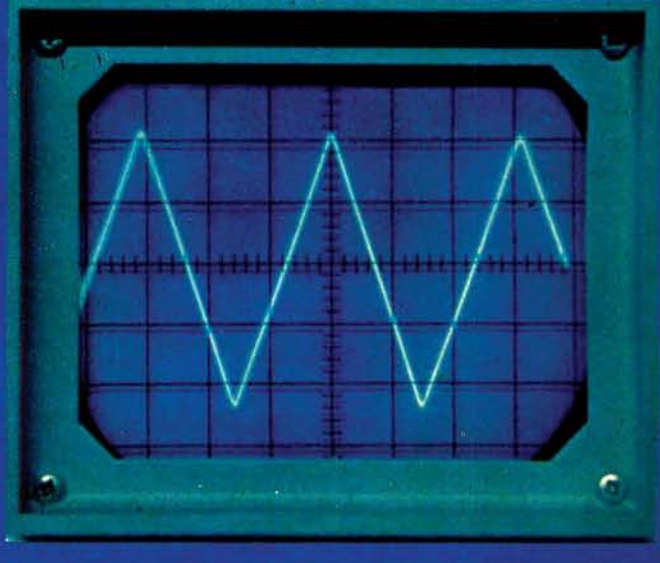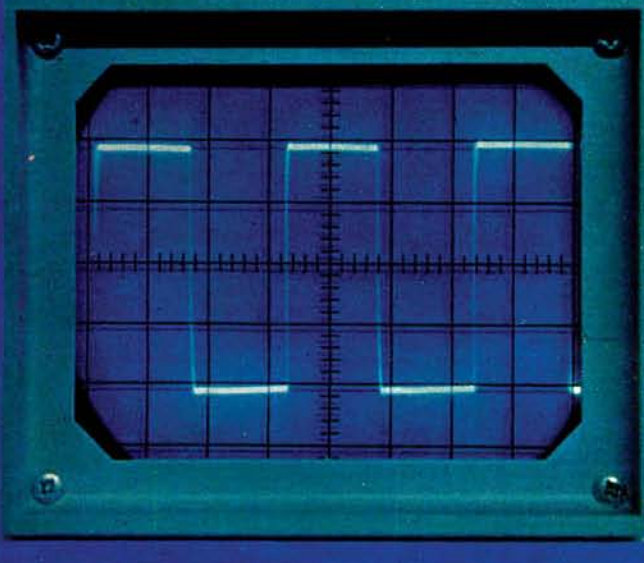

STEREO AUTOMATIC FADER

also: 'SUREFIRE' IGNITION SYSTEM KITS REVIEWED

**QUARTZ LCD
5 Function**

Hours, mins, secs., month, date, auto calender, back-light, quality metal bracelet.

£6.65

Guaranteed same day despatch.
Very slim, only 6mm thick.



M1

**SOLAR QUARTZ
LCD 5 Function**

Genuine solar panel with battery back-up. Hours, mins., secs., day, date. Fully adjustable bracelet. Back-light. Only 7mm thick.

£8.65

Guaranteed same day despatch.



M2

**QUARTZ LCD
11 Function** SLIM CHRONO

6 digit, 11 functions. Hours, mins., secs., day, date, day of week. 1/100th, 1/10th, secs., 10X secs., mins., Split and lap modes. Back-light, auto calendar. Only 8mm thick. Stainless steel bracelet and back. Adjustable bracelet. Metac Price

£10.65 Thousands sold!
Guaranteed same day despatch.



M3

**QUARTZ LCD
ALARM 7 Function**

Hours, mins., secs., month, date, day. 6 digits, 3 flags plus continuous display of day and date or seconds. Back-light. Only 9mm thick.

£9.95

Guaranteed same day despatch.



M4

**MULTI ALARM
6 Digits 10 Functions**

- Hours, mins., secs.
- Months, date, day.
- Basic alarm.
- Memory date alarm.
- Timer alarm with dual.
- Time and 10 country zone.
- Back-light.
- 8mm thick.

£18.65



M5

**FRONT-BUTTON
Alarm Chrono
Dual Time**

6 digits, 5 flags, 22 functions. Constant display of hours and mins., plus optional seconds or date display. AM/PM indication, month, date. Continuous display of day. Stop-watch to 12 hours 59.9 secs., in 1/10 second steps. Split and lap timing modes. Dual time zones. Only 8mm thick. Back-light. Fully adjustable open bracelet.

£18.95

Guaranteed same day despatch



M6

**SOLAR QUARTZ LCD
Chronograph with Alarm
Dual Time Zone Facility**

6 digits, 5 flags, 22 functions. Solar panel with battery back-up. 6 basic functions. Stop-watch to 12 hours 59.9 secs., in 1/10 sec., steps. Split and lap timing modes. Dual time zones. Alarm. 9mm thick. Back-light. Fully adjustable bracelet.

£19.95



M7

**ALARM CHRONO
with 9 world time zones**

- 6 digits, 5 flags.
- 6 basic functions.
- 8 further time zones.
- Count-down alarm.
- Stop-watch to 12 hours 59.9 secs.
- in 1/10 sec. steps.
- Split and timing modes.
- Alarm.
- 9 mm thick.
- Back-light.
- Fully adjustable bracelet.

£19.95



M8

**SOLAR QUARTZ LCD
Chronograph**

Powered from solar panel with battery back-up. 6 digit, 11 functions. Hours, mins., secs., day, date, day of week. 1/100th, 1/10th, secs., 10X secs., mins. Split and lap modes. Back-light, auto calendar. Only 8mm thick. Stainless steel bracelet and back. Adjustable bracelet. Metac Price

£13.65

Guaranteed same day despatch.



M9

SEIKO Alarm Chrono

LCD, hours, mins., secs., day of week, month, day and date, 24 hour Alarm, 12 hour chronograph, 1/10th secs., and lap time. Back light, stainless steel, HARDLEX glass.

List Price £130.00
METAC PRICE
£105.00



M10

SEIKO MEMORY BANK

Calendar watch M354. Hours, mins., secs. Month, day, date in 12 or 24 hour format all indicated continuously. Monthly calendar display month, year and all dates for any selected month over 80 year period. Memory bank function. Any desired dates up to 11 can be stored in advanced. 2 year battery life. Water resistant.

List Price £130
Metac Price **£79.50**



M11

**SEIKO-STYLE
Dual time-alarm
Chronograph**

Mineral glass face. Battery hatch for DIY battery replacement. Top quality finish with fully adjustable bracelet.

£35.00



M12

**HANIMEX
Electronic
LED Alarm Clock**



Features and Specifications:
Hour/minute display. Large LED display with p.m. and alarm indicator. 24 Hours alarm with on/off control. Display flashing for power loss indication. Repeatable 9 minute snooze. Display bright alarm modes control. Size: 5.15" x 3.93" x 2.38" (131mm x 110mm x 60mm). Weight: 1.43 lbs (10.65 kgs). AC power 220V.

£9.65 Thousands sold!
Mains operated.

Guaranteed same day despatch.

M13

**HANIMEX portable
LCD clock radio**



- Time set & alarm controls.
- Snooze & sleep controls.
- Wake to music or alarm.
- AM/PM indicator.
- Battery operated. No plug required.
- Receives all standard AM radio broadcasts.
- Drawstring carrying case included.
- Back-light.
- Batteries supplied free.
- Quartz crystal controlled.

£14.95

M14

**QUARTZ LCD
Ladies 5 Function**

Only 25 x 20mm and 6mm thick. 5 function. Hours, mins., secs., day, date and back light and auto calendar. Elegant metal bracelet in silver or gold. State preference.

£9.95

Guaranteed same day despatch.



M15

**Price breakthrough
only**

£14.50



OUTSTANDING FEATURES

- **DUAL TIME.** Local time always visible and you can set and recall any other time zone (such as GMT). Also has a light for night viewing.
- **CALENDAR FUNCTIONS** include the date and day in each time zone.
- **CHRONOGRAPH/STOPWATCH** displays up to 12 hours, 59 minutes, and 59.9 seconds.
- On command, stopwatch display freezes to show intermediate (split/lap) time while stopwatch continues to run. Can also switch to and from timekeeping and stopwatch modes without affecting either's operation.
- **ALARM** can be set to anytime within a 24 hour period. At the designated time, a pleasant, but effective buzzer sounds to remind or awaken you!

Guaranteed same day despatch. **M16**

HOW TO ORDER

Payment can be made by sending cheque, postal order, Barclay, Access or American Express card numbers. Write your name, address and the order details clearly, enclose 30p for post and packing or the amount stated. We do not wait to clear your cheque before sending the goods so this will not delay delivery. All products carry 1 year guarantee and full money back 10 day reassurance. Battery fitting service is available at our shops. All prices include VAT.

Trade enquiries: Send for a complete list of trade prices - minimum order value £100.
Telephone Orders: Credit card customers can telephone orders direct to Daventry or Edgware Rd., 24 hour phone service at both shops: 01 723 4753 03272 76545.

CALLERS WELCOME
Shops open 9.30 - 6.00.




Metac ELECTRONICS & TIME CENTRES

North & Midlands
67 High Street, DAVENTRY
Northamptonshire
Telephone: 03272 76545

South of England
327 Edgware Road
LONDON W.2
Telephone: (01) 723 4753

practical WIRELESS

APRIL 1980
VOLUME 56
NUMBER 4
ISSUE 878

BRITAINS LEADING JOURNAL FOR THE RADIO & ELECTRONIC CONSTRUCTOR

Published by IPC Magazines Ltd., Westover House, West Quay Rd., POOLE, Dorset BH15 1JG

QUERIES

While we will always try to assist readers in difficulties with a *Practical Wireless* project, we cannot offer advice on modifications to our designs, nor on commercial radio, TV or electronic equipment. Please address your letters to the Editor, *Practical Wireless*, at the above address, giving a clear description of the problem and enclosing a stamped self-addressed envelope. Only one project per letter please.

Components for our projects are usually available from advertisers. A source will be suggested for difficult items.

SUBSCRIPTIONS

Subscriptions are available to both home and overseas addresses at £10.60 per annum, from "Practical Wireless" Subscription Department, Oakfield House, Perrymount Road, Haywards Heath, West Sussex RH16 3DH.

BACK NUMBERS AND BINDERS

Limited stocks of some recent issues of *PW* are available at 85p each, including post and packing to addresses at home and overseas.

Binders are available (Price £4.10 to UK addresses and overseas, including post and packing) each accommodating one volume of *PW*. Please state the year and volume number for which the binder is required.

Send your orders to **Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF.**

All prices include VAT where appropriate. Please make cheques, postal orders, etc., payable to IPC Magazines Limited.

COPYRIGHT

© IPC Magazines Limited 1980. Copyright in all drawings, photographs and articles published in *Practical Wireless* is fully protected and reproduction or imitation in whole or in part is expressly forbidden.

All reasonable precautions are taken by *Practical Wireless* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

□ NEWS & VIEWS

- 20 **Leader:** Multiple Choice
- 21, 38, 45 **News . . . News . . . News**
- 22 **Special Product Report**
Surefire electronic ignition system kits
- 23 **Kindly Note**
Burglar Alarms, Part 2. October 1979
Car Wiper Unit, February 1980
ICF-6800W Receiver Review, February 1980
- 37 **Production Lines** Alan Martin
Information on the latest products
- 52 **Radio Special Product Report**
Yaesu FT-7B h.f. mobile transceiver—2
- 60 **RAE Reprint Announcement**

□ FOR OUR CONSTRUCTORS

- 24 **Stereo Automatic Fader** R. A. Penfold
A handy accessory for disco or tape recording
- 30 **Model Radio Control—5** J. Burchell & W. S. Poel
Basic installation in various models
- 34 **Dual Trace Unit—3** Ian Hickman
Extend the facilities of your *PW* Purbeck oscilloscope
- 39 **Low Frequency Signal Generator** P. Leah
Sine, square and triangular waves to 70kHz
- 46 **PW "Nimbus"—2** M. Tooley & D. Whitfield
A modular 2-metre transceiver system

□ GENERAL INTEREST

- 58 **A German Wartime Receiver** Ron Ham
An interesting vintage item
- 61 **On the Air**
Amateur Bands Eric Dowdeswell
Medium Wave DX Charles Molloy
Short Wave Broadcasts Charles Molloy
VHF Bands Ron Ham
VHF Personality—Roy Bannister Ron Ham

☆ FREE THIS MONTH

"RADIO SERVICING & ALIGNMENT PROCEDURES"
A special 8-page supplement

We regret that the final part of
Hi-Fi Glossary has had to be held over

Our May issue will be published on 3 April
(for details see page 33)

All these advantages...

- Instant all-weather starting
- Smoother running
- Continual peak performance
- Longer battery & plug life
- Improved fuel consumption
- Improved acceleration/top speed
- Extended energy storage

..in kit form

SPARKRITE X5 is a high performance, top quality inductive discharge electronic ignition system designed for the electronics D.I.Y. world. It has been tried, tested and proven to be utterly reliable. Assembly only takes 1-2 hours and installation even less due to the patented 'clip on' easy fitting.

The superb technical design of the Sparkrite circuit eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current by 95% of the norm.

There is also a unique extended dwell circuit which allows the coil a longer period of time to store its energy before discharging to the plugs. The unit includes built in static timing light systems function light, and security change-over switch. Will work all rev counters.



Fits all 12v negative-earth vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISES EVERY THING NEEDED. Die pressed case, Ready drilled, aluminium extruded base and heat sink, coil mounting clips and accessories. All kit components are guaranteed for a period of 2 years from date of purchase. Fully illustrated assembly and installation instructions are included.

Roger Clark the world famous rally driver says "Sparkrite electronic ignition systems are the best you can buy."



Sparkrite

HIGH PERFORMANCE ELECTRONIC IGNITION

Electronics Design Associates,
82 Bath Street, Walsall, WS1 3DE.

Electronics Design Associates, Dept. PW4
82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 614791

Name _____
Address _____

Phone your order with Access or Barclaycard
Inc. V.A.T. and P.P. QUANTITY REQ'D. I enclose cheque PO's for £
X5KIT £16.95
ACCESS OR BARCLAY CARD No. Cheque No. Send SAE if brochure only required.

Electronics GRAND SPRING SALE

10th - 29th March

SOME ITEMS HALF PRICE!

Bargains in Components, Bargains in Equipment, Bargains in FDK, Bargains in I.C.'s, Bargains in Jaybeam, Bargains in LED's, Bargains in Transistors, Bargains in Trio, Bargains in Yaesu!

MANY, MANY PRICE REDUCTIONS including 15% off CSC Breadboarding Equipment, 10% off all Jaybeam Antennas, 10% to 20% off selected Trio Equipment, 25% off Vero Boards etc, 50% off some discontinued items!

A FEW EXAMPLE BARGAINS:

Swan 500 Rx/Tx	£243.00	40W 2m PA Kit	£20.00
TR7600 2m	£222.50	TR2200GX 2m	£110.00
TR7200 2m	£160.00	FT101ZD Rx/Tx	£550.00
DL304 7 seg LED	£4 for 4	2N4440 Transistor	75p
Dipole Centre Insulators	£2.00	Matrix H Decoder	£48.00
SG402 R.F. Sig. Gen.	£61.50	FT227RB 2m	£220.00
CSC PB100	£10.03	TBA120	70p
CSC PB103	£29.30	uL914	£1.40
Snooper Radar Detector	£66.50	2N6084	£11.20
Trio R300	£170.00	74S262	£12.50
6BA6/EF93, 6GK6	75p each	1/2 wave window clip aerial	£5.00
2513/CM3021	£7.35	R512 Airband Rx	£143.50
LM3900	73p	BC143	28p ea.
SL6640	£4.50	BCY71	20p ea.
ZTX500	13p	CA3130E	80p
2N3904	17p	2N2906	21p
2N3906	17p	710	42p
		BF224	25p ea.
		LM380	92p
		MLED500	10p
		CFT455C	69p
		IN4148	3p

All prices include V.A.T., but add carriage £4.50 Securicor, Min. 50p Post.

All items are offered subject to availability and while stocks last only.

DONT DELAY - phone or write for complete list. Pay by Barclaycard, Trustcard, Visacard, Access, Eurocard, Master Charge, etc., Cash, Cheque, H.P. or the new Catronics Credit Charge.

CATRONICS LTD., COMMUNICATIONS HOUSE,
(Dept. 84) 20 WALLINGTON SQUARE,
WALLINGTON, SURREY, SM6 8RG.

Tel. 01-669 6700 (9a.m. to 5.30 p.m. Sat 1 p.m.) Closed lunch 12.45-1.45



£137.⁰⁰

SAFGAN ST-45

SINGLE TRACE OSCILLOSCOPE

- 10mv/div ● 5MHz ● BRITISH
- CHOICE OF FRONT PANEL ●

ST-45 SPECIFICATION

VERTICAL SYSTEM
Sensitivity 10mv/div 5v/div in 9 cal. steps
Bandwidth (3dB)
DC Coupled DC 5MHz
AC Coupled 5Hz-5MHz
Risetime 70µsec
Input Impedance 1MΩ + 22 PF approx. (for all ranges) 50Ω for 10mv/div 50mv/div
Input coupling AC CND DC
Input volts: 400V max.
Accuracy ± 5%

HORIZONTAL SYSTEM
Time base speeds
50ms/div 1µsec/div in 15 cal. steps with X5 Multiplier to 250msec/div and X5 Expansion to 200nsec/div
External - X sensitivity 1v/div
External - X Bandwidth 500KHz
Accuracy ± 5%

TRIGGER

Internal 0.5div (10Hz-2MHz), 1 div (2MHz-5MHz)
External 100mv (10Hz-2MHz), 200mv (2MHz-5MHz)
Bright Line Auto
Trace free runs in absence of signal
Trigger Level selects triggering point
Trigger (+)ve and (-)ve slope selection

FRONT PANEL

Black-Silver-White-ST-45-S The Silver Scope or Black-Gold-White-ST-45-G The Gold Scope

GENERAL

Power consumption 10VA approx.
Majns selection 200V-220V-240V rms (40Hz-60Hz)
Weight 10lbs 4.5kg approx.
Case aluminium with black pvc finish and black handle, front panel white with black control knobs, black feet and tilt bar.

Safgan Electronics Ltd.,
56 Bishops Wood, St. Johns,
Woking, Surrey GU1 3QB

ORDERS TO: SAFGAN ELECTRONICS LTD.

56 Bishops Wood, St. Johns, Woking
Surrey GU21 3QB or Tel: Woking 66836.

Please send me.....ST-45-S.....ST-45-G.....Probe.....Adaptor

I enclose PO/Cheque.....(Goods + 15% VAT + £3.00 p&p)

Name.....

Address.....

*Ex VAT UK

RSC

Sound Advice
Nationwide

MAGNUM 100
including PAIR DISCO 80C
SPEAKERS as illustrated
£275.00
Package Saving £50
Deposit **£55.00** and 18
monthly payments of **£16.00**
(Total Credit
Price **£343.00**)
Carr Free



NEW FOR 1980 MAGNUM 100

ANOTHER DISCO WINNER FROM THE SPECIALISTS
RSC PROUDLY PRESENT THE MAGNUM 100
FEATURES GALORE AT A PRICE
YOU CAN AFFORD

- Full 100 watts output
- Mike Input with Separate Treble/ Bass
- Full Headphone Monitor Facilities
- Autofade
- Master Volume
- 11" Turntables with Independent Illuminated Mains Switches
- Twin Speaker Sockets
- Slave and Sound to Light Outputs

SPECIAL OFFER
PAIR **£90**

MAGNUM 100 SUPER VALUE AT ONLY £225.00

OR DEPOSIT £45.00 and 18 monthly payments of £13.10 (Total Credit Price £280.80) (Carr £5)

Titan Disco 80C Speakers each unit incorporating 12" Full range 80 watt Speakers **£50.00 each**
CARR FREE


Exclusive to R.S.C.
AS-1 FOLK ACOUSTIC GUITAR Just **£17.95**

(Carriage £1)

OR £5 DEPOSIT & 8 MONTHLY PAYMENTS OF £2 (TOTAL CREDIT PRICE £21)

RSC Phantom 50 Combo Amplifier

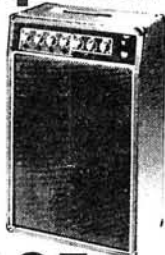- ★ Full 50 watts RMS
- ★ 12" Heavy Duty Fane Speaker
- ★ Treble, Bass and Presence Controls
- ★ 3 Separate Inputs
- ★ Master Volume Control
- ★ Full 12 Month Guarantee



TOP VALUE £99.95
AT ONLY

or Deposit **£20.00** and 12 Monthly Payments at **£8.07**
(Total Credit **£116.84**) CARR.FREE
Also available 15 watt Practice Amp
FAL Super Minstrel **£39.95**

MORE PEOPLE ARE DEMANDING TITAN SPEAKERS !!!

**MORE POWER
MORE RELIABILITY
MORE VALUE FOR MONEY**

Titan Group Disco Speakers

All Ratings RMS

Imp. 8-15 ohms Compare these prices with other makes

T12/50R	12"	50 Watts	£16.95	Deposit £4.95 & 8 Months at £2.00 (Total Credit £20.95)
T12/100A	12"	100 Watts	£26.95	Deposit £6.95 & 8 Months at £3.12 (Total Credit £31.91)
T15/70	15"	70 Watts	£24.95	Deposit £5.95 & 8 Months at £3.00 (Total Credit £29.95)
T15/85	15"	85 Watts	£28.95	Deposit £7.95 & 8 Months at £3.25 (Total Credit £31.95)
T15/100	15"	100 Watts	£35.95	Deposit £8.95 & 8 Months at £4.00 (Total Credit £40.95)
T18/100	18"	100 Watts	£47.95	Deposit £8.95 & 8 Months at £5.80 (Total Credit £55.35)



FUZZ LIGHTS

£27.95 Each

RED OR BLUE

(Post 75p or 2 FOR **£50.00**)
(Post FREE)

TERMS FOR 2
DEPOSIT **£10.00**
12 MONTHLY
PAYMENTS OF **£4.03**
(TOTAL **£58.36**)




ROOST 400S

Designed for high power public address systems, sound monitoring and discos. Two independent power amplifiers in one cabinet, each features an input socket, link socket and a gain control. The chassis is designed to be standard 19" (48.3 cm) rack mounting.

225 watts per channel into 4 ohms

£199.95

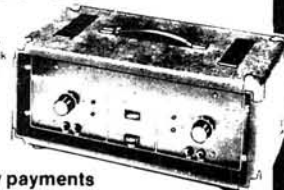Deposit **£40.00** & 18 monthly payments of **£11.20** (Total **£241.60**) (Carriage Free).



RSC Sound Advice Nationwide All Branches open all day Saturday

BRADFORD 10 North Parade (Closed Wed)
Tel 25349

BIRMINGHAM 30/31 Great Western Arcade (Closed Wed)
Tel 021-236 1279

CARLISLE 8 English Street (Closed Thurs)
Tel 38744

COVENTRY 17 Shelton Square, The Precinct (Closed Thurs)
Tel 25983

DERBY 97 St Peter's Street (Closed Wed)
Tel 41361

DEWBURY 9/11 Kingsway (Closed Tues)
Tel 468058

DONCASTER 3 Queensgate, Waterdale Centre (Closed Thurs)
Tel 63069

EDINBURGH 101 Lothian Road (Closed Wed)
Tel 229 9501

GLASGOW Unit 13, Anderston Shopping Precinct (Closed Tues)
Tel 041-248 4158

HULL 7 Whitefriargate (Closed Thurs)
Tel 20505

LEICESTER 32 High Street (Closed Thurs)
Tel 56420

LONDON 238 Edgeware Road W2 (Closed Thurs)
Tel 723-1629

★ **LEEDS** 16-18 County (Mecca) Arcade, Briggate (Closed Wed)
Tel 449609

★ **LIVERPOOL** St John's Precinct (Closed Wed)
Temporarily closed due to fire.
All enquiries to Leeds or Manchester.

★ **MANCHESTER** 60A Oldham Street (Closed Wed)
Tel 236-2778

MIDDLESBROUGH 103 Linthorpe Road (Closed Wed)
Tel 247096

★ **NEWCASTLE UPON TYNE** 59 Grainger St (Closed Wed)
Tel 21469

NOTTINGHAM 19/19A Market Street (Closed Thurs)
Tel 48068

SHEFFIELD 13 Exchange Street (Castle Mkt Blds) (Closed Thurs)
Tel 20716

★ **WOLVERHAMPTON** 6 Wulfrun Way (Closed Thurs)
Tel 26612

* **MUSICAL INSTRUMENTS & ACCESSORIES** in stock at these branches
S.A.E. for **FREE** illustrated brochures.
Please state main interest/s

DEPT. GC AUDIO HOUSE,
HENCONNER LANE, LEEDS 13
Tel: 0532 577631



Barclaycard, Access & Trustcard
Phone orders quoting card number accepted

MAIL ORDERS MUST NOT BE SENT TO SHOPS

E & OE prices correct at 28.1.80.

SUPER POWER



There's a lot of talk about SUPER POWERS in this wonderful world of ours, but in the context of Hi-Fi Amplifiers we must admit to puzzlement verging in some cases to downright mind bogglement, as perusing current advertising reveals costs ranging from about 60 pence, to as much as £6.00 per watt.

Why should this be so? and what is a Watt? It all seems to depend upon the devious state of mind of the advertising copy writer, some 'Amps giving their rated power at 1KHz only, whilst others give a "Music Power" figure, lovely term that one! Still more will only deliver the goods with only one channel driven, but the icing on the cake must surely go to the 'Amp rated at 100 watts, but with distortion figures given at the 10 watt level - nuff said.

FACTS: The WINTON will deliver 50+50 WATTS of the good old fashioned sine wave variety into an 8 Ohm load, and will do so continuously over a frequency range of 20 Hz to 20KHz, with a total harmonic distortion content of less than 0.1% - good enough?

Power at 1 KHz is 55+55 Watts.
"Music Power" (ugh) is 68+68 Watts.

At about 135 pence per Watt, the WINTON is an absolute steal, so put some Pzazz into your Jazz, and some Whack in your Bach, send us a 10p stamp for the full frontal 'spec which will reveal all, or better yet send your cheque NOW for the greatest value for money Hi-Fi kit around. POWER MOSFETS RULE! O.K.?

The Superlative WINTON is available for your convenience packed as follows:

- Pack (A) All Capacitors and Fixed Value Resistors, (Inc. 7 Amp ripple Res. Caps.) **£21.93**
- Pack (B) Switch Bank, Switches, Potentiometers, Pre-Sets & all Knobs **£15.93**
- Pack (C) Printed Circuit Board (Tinned, Drilled, & Overlay Printed) & Pins **£8.28**
- Pack (D) Hardware Pack, consisting of precision formed & punched Chassis, Black Epoxy finish Heat Sinks, Teak Veneered Cabinet, all screws, wire, fuseholders, etc., and a super Brushed Silver Aluminium Fascia Panel. **£40.25**
- Pack (E) All Semiconductors, (Including HITACHI POWER MOS-FETS) **£31.21**
- Pack (F) Special LOW HUM FIELD Toroidal Transformer **£23.55**

COMPLETE KIT, of all parts necessary to build the P.W. WINTON **£133.50**

Order with complete confidence (C.W.O. only please) from:

T. & T. ELECTRONICS

Green Hayes, Surlingham Lane, Rockland St. Mary, Norwich, NR14 7HH. Telephone 05088 632

ALL PRICES INCLUSIVE OF V.A.T. & CARRIAGE. Callers by appointment only.



Handy size Reels & Dispensers

OF THE WORLD'S FINEST CORED SOLDER TO DO A PROFESSIONAL JOB AT HOME

Ersin Multicore Solder contains 5 cores of non-corrosive flux that instantly cleans heavily oxidised surfaces and makes fast, reliable soldering easy. No extra flux is required.

SAVBIT
handy solder dispenser

Contains 2.3 metres approx. of 1.22 mm Ersin Multicore Savbit Solder. Savbit increases life of copper bits by 10 times.
Size 5 78p

For soldering fine joints

handy size reels of **SAVBIT, 40/60, 60/40 & ALU-SOL** solder alloys

These latest Multicore solder reels are ideal for the toolbox. Popular specifications cover all general and electrical applications, plus a major advance in soldering aluminium. Ask for a free copy of 'Hints on Soldering' containing clear instructions to make every job easy.

WIRE STRIPPER & CUTTER

Easily adjustable for most sizes of flex and cable. Fitted with extra strong spring for automatic opening. Easy grip handles and handle locking device.
Ref 9 **£2.21 inc. VAT.**

Two more dispensers to simplify those smaller jobs. PC115 provides 6.4 metres approx. of 0.71 mm solder for fine wires, small components and printed circuits.
PC115 92p
Or size 19A for kit wiring or radio and TV repairs. 2.1 metres approx. of 1.22 mm solder.
Size 19A 83p

Ref.	Alloy	Diam. mm.	Length metres approx.	Use	Price
Size 3	40/60 Tin/Lead	1.6	10.0	For economical general purpose repairs and electrical joints.	£3.22
Size 4	ALU-SOL	1.6	8.5	For aluminium repairs. Also solders aluminium to copper, brass etc.	£3.22
Size 10	60/40 Tin/Lead	0.7	39.6	For fine wires, small components and printed circuits.	£3.22
Size 12	SAVBIT	1.2	13.7	For radio, TV and similar work. Increases copper-bit life tenfold.	£3.22

MULTICORE WICK
for solder removal and desoldering.

Absorbs solder instantly from tags, printed circuits etc. Only needs 40-50 Watts soldering iron. Quick and easy to use. Non-corrosive.

Size AB10 £1.29

Sole UK Sales Concessionaires
Bib Hi-Fi Accessories Limited,
Kelsey House, Wood Lane End, Hemel Hempstead, Herts. HP2 4RQ

Prices shown are recommended retail inc. VAT. From Electrical and Hardware Shops. In dubio, send direct, plus 20p P&P. Prices and specifications subject to change without notice.

NEW

CONSTRUCTORS PACK 7

ALL THE PARTS TO BUILD THE PE TRAVELLER CAR RADIO



* EASY TO BUILD * 6 WATT OUTPUT * READY ETCHED & PUNCHED P.C.B. * INCORPORATES SUPPRESSION CIRCUITS

The pack contains all the electronic components to build the radio, you supply only the wire and solder as featured in the Practical Electronics March issue. The P.E. Traveller features pre-set tuning with five push button options, black illuminated tuning scale, with matching rotary control knobs, one, combining on/off volume and tone-control, the other for manual tuning, each set on wood simulated fascia. The P.E. Traveller has a 6 watts output, negative ground and incorporates an integrated circuit output stage, a Mullard IF module LP1181 ceramic filter type, pre-aligned and assembled and a Bird pre-aligned push button tuning unit. The P.E. Traveller fits easily in or under dashboards. Complete with instructions.

£10.50 p&p £1.50

CONSTRUCTORS PACK 7A Suitable stainless steel fully retractable locking aerial and speaker (approx 6" x 4") is available as a kit complete.

£1.95 Per Pack, p & p £1.00. Pack 7A may only be purchased at the same time as Pack 7.


A FEATURED PROJECT IN PRACTICAL ELECTRONICS



323 EDGWARE ROAD, LONDON W2. For Personal Shoppers Only. 21C HIGH STREET, ACTON W3 6NG. Mail Order Only. No Callers.

Mon-Sat 9.30am-5.30pm Closed Thursday

NEW 12+12 AMPLIFIER KIT

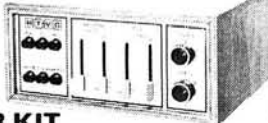


An opportunity to build your own 12 watts per channel stereo amplifier with up-to-the-minute features. To complete you just supply screws, connecting wire and solder. Features include din input sockets for ceramic cartridge, microphone, tape or tuner. Outputs—tape, speakers and headphones. By the press of a button it transforms into a 24 watt mono disco amplifier with twin deck mixing. The kit incorporates a Mullard LP1183 pre-amp module, plus 2 power amplifier assembly kits. Also featured 4 slider level controls, rotary bass and treble controls and 6 push button switches. Silver finish fascia panel with matching knobs. Easy to assemble teak simulate cabinet and ready made metal work. For further information instructions are available price 50p. Free with kit. Size 9 1/4" x 8 1/4" x 4"

NOTE: for use with 4 to 8 ohms speakers. p&p £2.55 **£13.95**

50 WATT MONO DISCO AMP £30.60 p&p £2.70



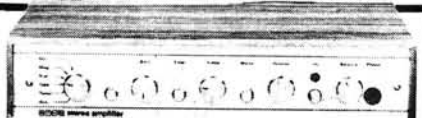Size approx. 13 1/2" x 5 1/4" x 6 1/4" 50 watts rms. 100 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and treble controls and master volume.



20 x 20 WATT STEREO AMPLIFIER Viscount IV unit in teak simulate cabinet. Silver finish rotary controls and pushbuttons with matching fascia, red mains indicator and stereo jack socket. Functions switch for mic, magnetic and crystal pickups, tape tuner and auxiliary. Rear panel features fuse holder, DIN speaker and input sockets. 20 x 20 watts RMS. 40 x 40 watts peak for use with 8 to 15 ohm speakers. Size 14 1/4" x 3" x 10" approx. **£31.90** includes a built in four channel stereo sound facility. £3.00 p&p

Mullard AUDIO MODULES IN BARGAIN PACKS

CURRENT CATALOGUE PRICE AT OVER

£25 PER PACK

SEE OUR PRICES

1 PACK 1 2 x LP1173 10w RMS output power audio amp modules, + 1 LP1182/2 Stereo pre amp for ceramic and auxiliary input. OUR PRICE **£5.00** p&p £1.00

2 PACK 2 2 x LP1173 10w RMS output power audio amp modules, + 1 LP1184/2 Stereo pre amp for magnetic, ceramic and auxiliary inputs. illus. OUR PRICE **£7.65** p&p £1.00

ACCESSORIES Suitable mains power supply parts, consisting of mains transformer, bridge rectifier, smoothing capacitor and set of rotary stereo controls for treble, bass, volume and balance. **£3.00** plus £1.50 p&p

Two Way Speaker Kit Comprising of two 8" x 5" approx. 4 ohm bass and two 3 1/2" 15 ohm mid-range tweeter with two cross-over capacitors.

AVAILABLE ALSO TO PURCHASERS OF THE 10 + 10 AMPLIFIER KIT Per stereo pair plus £1.55 p&p **£4.05**



323 EDGWARE ROAD, LONDON W2 21C HIGH STREET, ACTON W3 6NG

ACTON: Mail Order only. No callers. ALL PRICES INCLUDE VAT AT 15% All items subject to availability. Price correct at 1.2.80 and subject to change without notice. All enquires Stamped Addressed Envelope. NOTE: Persons under 16 years not served without parent's authorisation.

30x30 WATT AMPLIFIER IN KIT FORM


For the experienced constructor complete in every detail, same facilities as Viscount IV, but with 30x30 output 60x60 watts peak. For use with 4 to 15 ohms speakers. **£31.50** p&p £3.00



EMI SPEAKER BARGAIN

Stereo pair 350 kit. System consists of 13" x 8" approx. woofer with rolled surround, 3 1/2" Goodman tweeter crossover components and circuit diagram. Frequency response 20 Hz to 20 KHz. Power handling 15 watts RMS. 20 watts max. 8 ohm impedance.


£18.25 Per stereo pair **£3.65** p&p

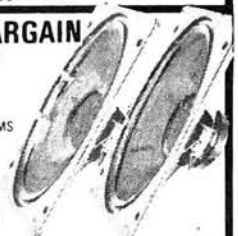

BSR P200

£25.50

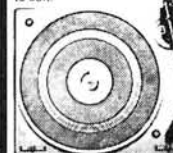Belt drive chassis turntable unit semi-automatic, cueing device p&p £2.60 Shure M75 6 Magnetic Cartridge to suit.



£7.95

BSR Manual single play record deck with auto return and cueing lever. Fitted with stereo ceramic cartridge 2 speeds with 45 r.p.m. spindle adaptor ideally suited for home or disco use. **£12.25** p&p **£2.75** OUR PRICE

PHILLIPS RECORD PLAYER DECK GC037

HiFi record player deck, belt drive complete with GP401 magnetic cartridge—LIMITED STOCK UNBEATABLE OFFER AT **£27.50** complete.



BARGAIN OFFER

Ariston pick-up arm manufactured in Japan. Complete with headshell. Listed price over **£30.00**. **OUR PRICE £11.95** p&p £2.50

Personal Shoppers EDGWARE ROAD LONDON W2 Tel: 01-723 8432. 9.30am-5.30pm. Closed all day Thursday. ACTON: Mail Order only. No callers. GOODS DESPATCHED TO MAINLAND AND N. IRELAND ONLY

CHORDGATE LTD. SWINDON

SILICON TRANSISTORS FULL SPEC.

TIP31B 25p comp. TIP32B 25p, 5 pairs £2.00 or 10 either type £2.00.
2N3707 gen. pur. NPN 10 for 50p. 2N5293 NPN 75V 4A TAB collector
20p 10 for £1.75. TIP34A PNP 60V 10A 40p 10 for £3. 1N914 25p 10 for
60p. BD525 30p comp. BD526 30p useful up to 50MHz. 5 pairs £2.50 10
either type £2.50.

2102L RAMS 75p each.

Fairchild FND10 7 seg. displays
0-15" red common cathode 60p.

Pye dynamics thick film 1MHz
clocking oscillator, 5 volt supply,
drives 1 TTL load 60p.

368-640KHz XTAL PCB MTG
HCU + 2¹⁰ = 360Hz 75p.

444-8KHz XTAL wire end £1.95.

Beehive trimmer 3-30PF 10 for 50p.
1-5-2-5PF min trimmer 5mm x
5mm HOR MTG 12p 10 for £1.

Stettner 3-15PF CER trimmer
10mm dia. vert. MTG 15p 10 for
£1.20.

Denco transistor 1FTs interstage
IFT13 60p. IFT14 Det. output 60p
470KHz.

Std air spaced trimmer capacitors
20pF, 30pF or 40pF 12p any 10 for
£1. Tubular trimmer capacitors
2pF, 18pF or 30pF 12p any 10 for
£1.

Tantalum bead capacitors 10MFD
6-3V 8p each. 10 for 70p. 2-2MFD
50V 12p each. 10 for £1.05.
6-8MFD 35V 12p each. 10 for
£1.05. Tantalum miniature axial
1MFD 15V 4mm x 1.5mm dia. 8p
each. 10 for 70p. 2-2MFD 15V
5mm x 1.5mm dia. 8p each. 10 for
70p.

Colvern 1 watt wire wound pots 25R,
100R, 1K, 2K, 2.5K, 10K, 30K,
40p. 10 for £3. State value.

4700MFD 16V 60p. 6800 MFD
10V 60p. 15000MFD 10V 60p.
6F10 stud rect. 100V P.I.V. 6A 25p.
4 for 80p.

Mullard pot cores. All supplied with
data sheet. LA1 50p. LA2 60p. LA4
70p. LA7 80p.

Waveform generator kit. PCB and all components to build 20Hz-20KHz
generator with sine square and triangle outputs. 10-30V supply, complete with
data sheet £9.95. (8038 Based).

For all above supplies add 35p post and packing. Order over £5.00 post and
packing inclusive.

Printed circuits detailed below add 35p post and packing 1-3 boards. Larger
quantities post and packing inclusive.

PCB contains 2 IP 10W wafer
switches. 2 x 7440 I/C 2 x 74141
I/C. Various logic I/Cs 1N4148s and
over 50 components 70p.

PCB with GEC G424 triac control
I/C. 2 SGS transistors. Three 9 watt
WW resistors and 12 other compo-
nents supplied now with G424
data and application sheet £1.00.

PCB with 4 x 0.1 MFD 1000V caps
2 pre-sets, 1 bridge rect., 4 x 1N4007,
9 resistors 70p.

PCB with 2 x 741. 2N4921 and over
40 other components and multirun
20K pot 70p.

PCB with 8 x BC107 8 x BCY70 4
pre-set pots and over 70 other compo-
nents 80p.

Special bargain 10 Kilo inclusive of packing parcel of PCBs, resistors,
capacitors, etc. etc. and items not listed above £6.95.

Avo in circuit transistor tester type TT169 complete in case with instructions
for testing transistors diodes and SCRs £17.50. Excellent condition fully
tested.

(Dept B.) 194 A DRIVE ROAD, SWINDON, WILTS.

ALL OUR PRICES INCLUDE VAT

28 PIN I/C holder 20p.

30 turret tags 50p.

500 OHM multi-turn PCB MTG pot
20p. 10 for £1.50.

Airflow Developments snail blower
110V 50Hz £4.50.

Citenco 48V motor with right angle
drive geared for 4 R.P.M. torque 24
oz-ins. 1/4" round or for 5/32"
square shaft £9.50.

Honeywell plastic snap panel MTG
push button DP/CO switch, latch or
non latch 15p. 10 for £1.25. State
type.

Alma push button reed switch ideal
for keyboard 30p. 10 for £2.50.

Min. glass reed switches 20mm
length 10 for 60p.

Photo diode and lamp 60p pair.

Mercury battery 1-35V 1000 MA/H
16mm dia. 16mm high 15p. 10 for
£1.20.

LM324N quad op-amp I/C 60p.

LM1303N stereo pre-amp I/C 60p.

SN76110 P.L.L. FM stereo mul-
tiplex decoder I/C 75p.

0-2" red LEDs 10p. 10 for 90p.

4-7V 400 MW zener 6p. 10 for 50p.

13V 400 MW zener 6p. 10 for 50p.

Min cermet trimmers HOR MTG
220R and 10K 15p. 10 for £1.20.
State value.

1/2W carbon resistors, 100 packed in
manufacturers cartons. 15R, 39R,
47R, 150R, 560R, 2-K, 22K, 68K,
100K, 50p per carton. State value.

Resistor pack 200 assorted 70p.

Min electrolytic pack approx. 100
assorted values, few types unmarked
75p.

NEW FROM MAGNUM

DIGITAL INDICATION of RADIO FREQUENCY using a unique com-
bination of FUTABA FLUORESCENT DISPLAY (the 'Green One')
and OKI COUNTECR/DRIVER.

Combination 1

OKI MSM 5524RS

OKI MSL 2318

FUTABA 6-LT-09

Crystal

Combination 2

OKI MSM 5525RS

OKI MSL 2318

FUTABA 6-LT-06

Crystal

Combination 3

OKI MSM 55271

OKI MSL 2318

FUTABA 7-LT-02

Crystal

Special Price Offer **£21.38**

AM, FM, SW

Pre-Scaler

5 digits + MHz, KHz

3.2768 MHz

Special Price Offer **£18.32**

AM, FM

Pre-Scaler

3 1/2 digits + MHz, KHz + AM, FM

6.5536 MHz

Special Price Offer **£24.57**

AM, FM, SW

Pre-Scaler

5 digits + MHz, KHz + AM, FM

6.5536 MHz

Send today for your Combination (suggested circuit details and
FREE I/C Socket are included) and enjoy "spot on" visual tuning.

OUR NEW CATALOGUE IS NOW READY. Send S.A.E.

MAGNUM AUDIO Ltd.

DEPT. PW1, 13 HAZELBURY CRESCENT,
LUTON, BEDS. LU1 1DF.
TEL: 0582 2887

J. H. MEARS LTD.

PRINTED CIRCUIT BOARD MANUFACTURERS

Production space now available for high quality printed
circuit boards made to your specification. We have full
facilities for component assembly work, artwork. Modifi-
cations, PCB design from your circuit diagram to PCB,
drilling, tinning, gold plating, silk screen printing on box
lids, facia's etc. No job too big or small.

J. H. MEARS LTD,

Cannon Maltings, Gateford Rd, Worksop, Notts.

Tel: Worksop 720652

CALLERS ALWAYS WELCOME

NICADS

VARTA & SAFT
Rechargeable Batteries.

14 day money back
guarantee if not
totally satisfied.

"DEAC" DKZ Button Cells

4.8v Receiver Pack

225mA..... £3.20

500mA..... £5.35

9.6v Transmitter Pack

500mA..... £10.70

Rx/Tx conversion

12 pencils, charging holders

and Rx/Tx charger..... £21.00

"VENTED" CELL (for fast charge)

0.5Ah* Pencil/HP7..... £1.30

1.2Ah RSH Electric flight. Tags only..... £1.65

1.2Ah VR Electric flight Tags only..... £1.65

1.8Ah* U11 replacement..... £2.35

4.0Ah* U2 replacement..... £3.20

*Tags available extra 10p per cell.

CONSTANT CURRENT CHARGER - ideal for all nicads - switched 25mA/50mA/
120mA/200mA/400mA output - charges up to 12 cells in series without adjust-
ment - £13.95 see for further details.

PHOTOGRAPHER'S CHARGER - Charges 1 to 4 HP7 size nicads £6.45.

FIELD CHARGER 12v input/two 50mA constant current outputs - ideal
for charging up to eight 0.5Ah nicads or two "Deacs" per output £8.30.

UK POST AND PACKING - ADD 60p PER ORDER.

V & F SMALLCRAFT (POPLAR) LTD.

38 Stoneleigh Road, Clayhall, Ilford, Essex. Tel: 01-550 6642

MORE BIG VALUE FROM YOUR TANDY STORE

1000 OHMS/VOLTS AC/DC 8 RANGES

Handy multimeter for home and work-shop. Easy-to-read two colour 5cm meter, pin jacks for all 8 ranges. Reads AC and DC volts: 0-15-150-1000 DC current; 0-150 mA. Resistance: 0-100,000 ohms. Accuracy: $\pm 3\%$ full scale on DC ranges, $\pm 4\%$ on AC ranges. Complete battery. 22-027. REG. PRICE

£6.95



6-DIGIT FREQUENCY COUNTER

Counts frequencies from 100 Hz to over 45 MHz with 100 mS gate time. Accuracy is 3 ppm at 25°C or less then ± 30 Mhz on 10 MHz! Overload-protected 1-meg input. Sensitivity, 30 mV up to 30 MHz. Reg. 9V battery. 22-351. REG. PRICE

£79.95



MULTITESTER

Dual FET input for accuracy and minimum loading. 11.5cm mirrored scale. DC volts, 0-1-3-10-30-100-300-1000. DC current 0-100 a, 0-3-30-300 milliamp. Resistance 0-30-300-3k-301C-1 megaohm. 0-100-1k-101C-100K-3 megaohms. Reg. 9V battery. 22-209.

REG. PRICE
£29.95



TRANSISTORIZED SIGNAL TRACER

Spot circuit troubles and check RF, IF and audio signals from aerial to speaker on all audio equipment. With 9V battery, instructions. 22-010.

REG. PRICE **£9.95**



DIGITAL IC LOGIC PROBE

Unique circuitry makes it a combined level detector, pulse detector and pulse stretcher. Hi-LED indicates logic "1". Lo-LED is logic "0". Pulse LED displays pulse transitions to 300 nanoseconds, blinks at 3 Hz for high frequency signals (up to 1.5 MHz). Input impedance: 300K ohms. With 36" power cables. 22-300.

REG. PRICE **£19.95**



SIGNAL INJECTOR

For RF, IF, AF circuits. Maximum accuracy. Easy pushbutton operation. Needs two "AA" batteries. 22-4033.

REG. PRICE **£2.79**

AC/DC CIRCUIT TESTER

Accuracy in 1-300 volts ranges. Safe in live/dead circuits. Needs two "AA" batteries. 22-4034.

REG. PRICE **£1.99**



REALISTIC DX 300

General coverage receiver. Quartz-synthesised tuning, digital frequency readout. 3-step RF Attenuator. 6-range preselector with LED indicators. SSB and CW demodulation. Speaker. Code oscillator. Batteries (not included) or 12V DC. 20-204.

REG. PRICE **£229.95**



DYNAMIC TRANSISTOR CHECKER

Shows current gain and electrode open and short circuit. Tests low, medium or high power PNP or NPN types. Go/no-Go test from 5-50mA on power types. 22-024.

REG. PRICE
£9.95



VARIABLE POWER SUPPLY

Power project boards. IC's, other low-voltage DC equipment. Load regulation: less than 450mV at 1 amp at 24V DC. Ripple: less than 25mV. Maximum output current: 1.25 amps. Switchable colour-coded meter reads 0-25V. DC and 0-1.25 amps. Three-way binding posts take wires, banana plugs or dual banana plugs with 0.75" centres. For 220/240V AC. 22-9123

REG. PRICE **£35.95**



You save because we design, manufacture, sell and service. Tandy has over 7,000 stores and dealerships worldwide. Over 2,500 products are made

specifically for or by Tandy at 16 factories around the world. The quality of our products has been achieved by over 60 years of continuous technological advancement.

KNOWN AS RADIO SHACK IN THE U.S.A. MAKERS OF THE WORLD'S BIGGEST SELLING MICROCOMPUTER TRS80

TANDY

The largest electronics retailer in the world.

Offers subject to availability. Instant credit available in most cases.

OVER 170 STORES AND DEALERSHIPS NATIONWIDE.



TANDY DEALER

Most items also available at Tandy Dealers. Look for this sign in your area.



Access. Barclaycard and Trustcard welcome.

Prices may vary at individual stores.

CHROMASONIC electronics

your soundest connection in the world of components

The items shown in this advert are just a small selection taken from our 1979 Catalogue containing everything from Resistors to the latest in Microprocessors. Order your copy today FREE with all orders upon request or S.A.E.

Dept PW1, 56 FORTIS GREEN ROAD, MUSWELL HILL, LONDON, N10 3HN

TEL: 01 883 3705 01 883 2289

VOLTAGE REGULATORS	DENCO COILS	QUARTZ CRYSTALS	RESISTORS	VEROBOARD	LINEAR IC's	IC SOCKETS
Positive 70L SERIES 100mA 5v, 6v, 8v, 12v & 15v. All 32p each	ROD AERIALS FRA1 L & MW (300pf) 1.17 FRA2 L & MW (500pf) 1.17	100KHz 3.85 1.0MHz 3.45 2.0MHz 3.45 2.097152MHz 3.45 2.5625MHz 3.45 3.27680MHz 3.45 4.194304MHz 3.45 4.433619MHz 1.27 5.0MHz 3.45 8.0MHz 3.45 10.0MHz 3.45 10.7MHz 3.45	1/2 Watt HI/STAB 5% 27Q-10M 1/2 Watt HI/STAB 5% 10Q-1M All 2p each 100 + £1.75	Size inches 0.1 c/dad 2.5 x 1 .12 2.5 x 3.75 .45 2.5 x 5 .52 3.75 x 3.75 .52 3.75 x 5.0 .60 17 x 2.5 1.55 17 x 3.75 2.08 17.9 x 4.7 2.68 Pin insertion tool .98 Spot face cutter .84 Veropins per 100 .42	741 8 Pin .23 748 8 Pin .38 LM301 .28 LM307 .28 LM308 .51 LM308 .76 LM324 .65 LM380 .65 LM381 1.77 LM3900 .55 MC1310 1.28 NE555 .30 18A81UAS .99 TCA940 1.76 TDA2020 3.58 ZN414 .75	TEXAS DIL 14 PIN .13 16 PIN .14 28 PIN .32 40 PIN .47 T099 10 PIN
78M SERIES 500mA 5v, 6v, 8v, 12v, 15v, 20v & 24v. All 64p	L.F. TRANSFORMERS 1FT 13.465KHz .87 1FT 14.465KHz .87 1FT 15.10.7MHz .97 1FT 16.1.6MHz .97 1FT 17.1.6MHz .97 1FT 18.465KHz 1.14 1FT 18.1.6MHz 1.14	TUNING CAPACITORS DILECON 100pf 1.94 40pf Max .25 300pf 2.29 500pf Max .38 500pf 2.52	PRESETS 0.1 Watt Carbon .07 0.5 Watt Cermet .62	VERO BOXES 2523E 8.78 1798K 5.08	TRANSISTORS BC107 .10 BC108 .10 BC109 & C .10 BC147 .08 BC148 .08 BC149 .08 BC157 .09 BC158 .09 BC159 .09 BC182L .12 BC183L .12 BC184L .12 BC212L .12 BC213L .12 BC214L .12 BC327 .12 BF194 .10 BF195 .10	
7800 SERIES 1A 5v, 6v, 12v, 15v, 18v & 24v. All 80p	TRANSISTOR RANGE 1T BLUE 2T YELLOW 3T RED 4T AND 5T WHITE £1.06	TRIMMERS C804 5pf, 10pf, 15pf, 25pf 2.23 20pf, 50pf 2.41 60pf, 75pf, 100pf 2.77	POTENTIOMETERS Log/Lin L/S .31 Log/Lin W/S .72 Dual Log Lin L/S .90 Dual Log Lin W/S 1.28	SPECIAL OFFERS 5 x 741 for 1.00 4 x 555 for 1.00 2 x ZN414 1.00 2 x CA3086 1.00 2 x MC1310 1.50 10 x TL209 1.00 10 x 2 Red LED 1.00 1.TCA730 8.50 1.TCA740 8.50	BC159 .09 BC182L .12 BC183L .12 BC184L .12 BC212L .12 BC213L .12 BC214L .12 BC327 .12 BF194 .10 BF195 .10 BF196 .18 BF197 .10 BF198 .10 BF199 .10 BF200 .23 2N1711 .22 2N2905 .23 2N2925 .10 2N2926G .12 2N3055 .51	
Negative 79M SERIES 500mA 5v, 6v, 8v, 12v, 15v, 20v & 24v. All 70p	DUAL PURPOSE RANGE DP1 BLUE DP2 YELLOW DP3 GREEN DP4 RED DP5 AND DP6 WHITE DP7 87p	TYPE 'O' 365pf 3.46 365pf + 365pf 3.97 '00' 208pf + 176pf 3.67	SLIDERS Single .41 Dual .81	PLASTIC 2514F 1.99 2516G 2.27 2518H 2.53 2520J 2.87 2522K 3.85	DIN Pin Plug Socket 2 .15 .10 3 .15 .10 4 .15 .10 5 (180°) .15 .10 5 (240°) .15 .10	
7900 SERIES 1A 5v, 6v, 12v, 15v, 18v & 24v. All 80p	ANTEX SOLDERING IRONS X25 4.25 CX 4.25 CCN 4.25	ELEMENTS AND BITS 1.80 50, 51, and 52 .57 1.80 6/1106 53p 7/1101 .86 2.10 1100, 1101, 1102, 1103 .53	CAPACITORS Polyester Silver Mica Polystyrene Mylar Ceramics All in stock send Electrolytics for catalogue S.A.E. Tantalum Bead	AUDIO AMP KITS 75B 7 Watts 3.67 75 x 10 Watts 4.60	RESISTOR NETWORKS 150Q, 270Q, 1K, 4.7K, 10K, 47K, 100K 81p each	
VARIABLES µA723 (DIL) .43 L200 1.95 LM304H 2.55 LM323K 6.86 LM325N 2.77 LM326N 2.77 LM345K 8.91	DESOLDERING GUN Gun 8.37 Spare Nozzle .98 Desolder Braid .63	REELS OF SOLDER 18 SWG Size 5 .62 22 SWG Size PC115 .74 18 SWG Size 12 .29 ST3 Soldering Iron Stand 1.70	3 1/2 DIGIT METER KITS 7106 L.C.D. 26.99 7107 L.E.D. 23.99	CASE BOX 2037C 3.93 2068B 5.21 2073K 7.08		
ZENERS BZY88 400MW Range 9p each BZX61 1.3 WATT Range 15p each						



V.A.T. Inclusive prices 15%. Export Customers deduct V.A.T. 3/23.

Postage and Packing 25p. Trade and Export Inquiries most Welcome. Hours 9.00am - 5.00pm.

Now available our ORDER RING line, just phone your order through with your Access or Barclaycard number and providing the order is received by 3.00pm the components will be despatched the same day (min tel order £5.00).



FANE

STILL TOP VALUE and

LIFETIME GUARANTEE

INTRODUCING THE 'CLASSIC 55' 12" 55 WATT MULTI-PURPOSE BASS - LEAD GUITAR - P.A. - DISCO

A HIGH PERFORMANCE SPEAKER AT A REMARKABLY LOW PRICE

FULL CLASSIC RANGE

Classic 45 12" 45 Watts
Classic 55 12" 55 Watts
Classic 80 12" 80 Watts
Classic 85 15" 85 Watts
Classic 150 15" 150 Watts
Classic 125 18" 125 Watts
Classic 175 18" 175 Watts

Impedances 8 ohms or 15 ohms as required.

£19.94

Rec. Retail Price (inc. V.A.T.)



LOOK AT THESE TYPICAL PERFORMANCE FIGURES and it's a BUDGET SPEAKER

Total distortion at rated output 3%
Sensitivity 98dB.
Frequency range 50-5000Hz

Also Available
HIGH FREQUENCY HORN UNITS
SPECIALIST RANGE SPEAKERS
CRESCENDO 'E' SERIES SPEAKERS

Available from YOUR LOCAL DEALER or if in difficulty post free direct from

BRITAINS LARGEST PRODUCERS OF HIGH POWER CHASSIS SPEAKERS
FANE ACOUSTICS LTD, HICK LANE, BATLEY, YORKS.
Telephone: (0924) 476431 Telex: 556498 FANE G

MARPLIN


ELECTRONIC SUPPLIES



PRINTED CIRCUIT DRILLS
Miniature 12V DC drills designed for drilling pcb's.
Small drill: Order as **BW03D**
Price £6.75
Large drill: Order as **BW02C**
Price £10.63



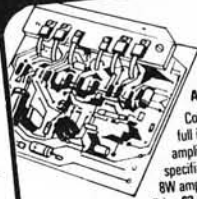ANTI-STATIC MAT & GUN
Turntable mat removes static from discs while they are playing.
Order as **LX10L** Price £2.95
Gun removes static charge from discs. After use dust no longer clings and may be easily brushed off.
Order as **LX04E** Price £4.99



AMP KITS
Complete kits of parts with full instructions to make hi-fi amplifiers with excellent specifications.
8W amp kit: Order as **LW36P**
Price £3.83
50W amp kit: Order as **LW35Q** Price £13.73
150W amp kit: Order as **LW32K** Price £14.89



HEADPHONES
High quality stereo headphone with large padded headband and slider volume controls.
Order as **WF14Q**
Price £7.99



CONDUCTIVE PAINT
Repair pcb's, car demisters, etc., with this silver paint. Phial contains 3gm.
Order as **FY27P** Price £2.59



McKENZIE POWER SPEAKERS
High quality, high power speakers.
12in. 50W 8Ω Order as **X079L**
Price £18.79
12in. 50W 16Ω Order as **X080B**
Price £18.79
12in. 80W 8Ω Order as **X081C**
Price £26.92
12in. 80W 16Ω Order as **X082D**
Price £26.92
15in. 150W 8Ω Order as **X083E**
Price £57.80
15in. 150W 16Ω Order as **X084F**
Price £57.80



MINIATURE VICE
Small modellers vice in tough plastic with metal faced jaws. Clamps to bench. Jaws width 41mm, maximum opening 30mm.
Order as **FY53H**
Price £2.78



20,000 OHM-VOLT MULTIMETER
A 20,000 ohms-per volt multimeter at an incredibly low price. DC volts 5, 25, 125, 500, 2,500; AC volts 10, 50, 250, 1,000; DC amps 0 to 0.05mA, 0 to 250mA; Resistance 0 to 50k, 0 to 5M ohms; Decibels -20 to +22dB. Complete with test leads, battery and instruction leaflet.
Order as **YB83E**
Price £13.70



ELECTRET MICROPHONES
Super quality genuine electret microphones operating on 1.5V battery (HP7-type) supplied. Cassette type with miniature jack plugs.
Order as **YB33L** Price £3.84
Omnidirectional low-cost with standard jack plug.
Order as **YB34M** Price £3.75
Unidirectional 600Ω with standard jack plug.
Order as **YB35Q** Price £9.75
Unidirectional 600Ω/50kΩ dual with standard jack plug (pictured).
Order as **WF34M** Price £16.77



WIRING TOOLS
Miniature box-jointed wiring pliers with insulated handles and return spring.
Order as **BR69A** Price £4.52
Miniature box-jointed side-cutters with insulated handles, return spring and precision cutting edges.
Order as **BR70M** Price £4.45
End action wire strippers, fully adjustable, insulated handles.
Order as **BR76H** Price £5.85



CLOCK MODULE
Module requires only transformer and two push switches to operate 4-digit, 0.7in red LED display. Alarm and radio outputs. Battery back-up when mains fail. Sleep and snooze timer. Seconds display. Just add speaker for alarm tone. Full details on page 267 of our catalogue.
Order as **XL14Q** Price £8.41



MEGAPHONE
High quality megaphone with differential microphone. Requires eight HP11 batteries (not supplied). Shoulder strap for portable operation.
Order as **X072P** Price £48.50



SWR POWER METER
SWR meter and transmitted power meter in one handy instrument. Frequency range 3.5 to 150MHz. Impedance: 50Ω.
Order as **YB02C** Price £19.89



CAR AERIAL BOOSTER
High gain car aerial booster for long, medium, short and VHF bands. Negative earth cars only. Very easy to fit - just plugs in plus one wire to +12V. We have measured gains of 200B at 90MHz!
Order as **XX37S** Price £5.95



TEACH YOURSELF ELECTRONICS
There is no better way of learning basic electronics than by practical experience and this set of books is undoubtedly the very best basic course for doing just that. Set of five Basic Electronics books.
Order as **XX10L** Price £8.30



MULTIMETER & TRANSISTOR TESTER
Superb high sensitivity multimeter and transistor tester in one. Sensitivity 100,000 ohms per volt. DC Ranges DC volts 0.5, 2.5, 10, 50, 250, 1,000; AC volts 5, 10, 50, 250, 1,000; DC current 0.01, 0.025, 0.5, 5, 50, 500mA, 10A; AC current 10A; Resistance 5k, 50k, 5M, 50M ohms; Decibels -10dB to +62dB. Complete with test leads, three leads for transistor tester batteries and instruction leaflet.
Order as **YB87U** Price £39.30



TURNTABLES
Autochanger complete with stereo ceramic cartridge and circuit to make a complete low-cost record player ideal for the young pop fan.
Order as **X000A** Price £18.48
Single-play rim-drive turntable with stereo ceramic cartridge.
Order as **XB23A** Price £24.79
Single-play belt-drive turntable 'S' shaped tone arm.
Order as **XB25C** Price £30.63



TRANSISTOR TESTER
Accurate transistor tester measures dynamic gain, identifies unknown transistors, also ideal for matching transistors into pairs.
Order as **LH05F** Price £12.28



SWR & FIELD STRENGTH METER
SWR meter and relative field strength meter for transmitter antenna alignment.
Accuracy: ±5%.
Order as **YB03D**
Price £11.89

All prices include VAT and postage and packing, but if total under £4 please add 30p handling charge. Prices guaranteed until May 8th, 1980. Export customers deduct 13% and export postage will be charged extra at cost.
Please use order code.
All items in stock at time of going to press.

FOR FULL CATALOGUE DETAILS SEE BACK COVER.


MARPLIN

ELECTRONIC SUPPLIES LIMITED

All mail to PO Box 3, Rayleigh, Essex SS6 8LR. Telephone: Southend (0702) 554155.
Shop: 284 London Road, Westcliff-on-Sea, Essex (closed on Monday). Telephone: Southend (0702) 554000.

Simply ahead . .

ILP'S NEW GENERATION OF HIGH

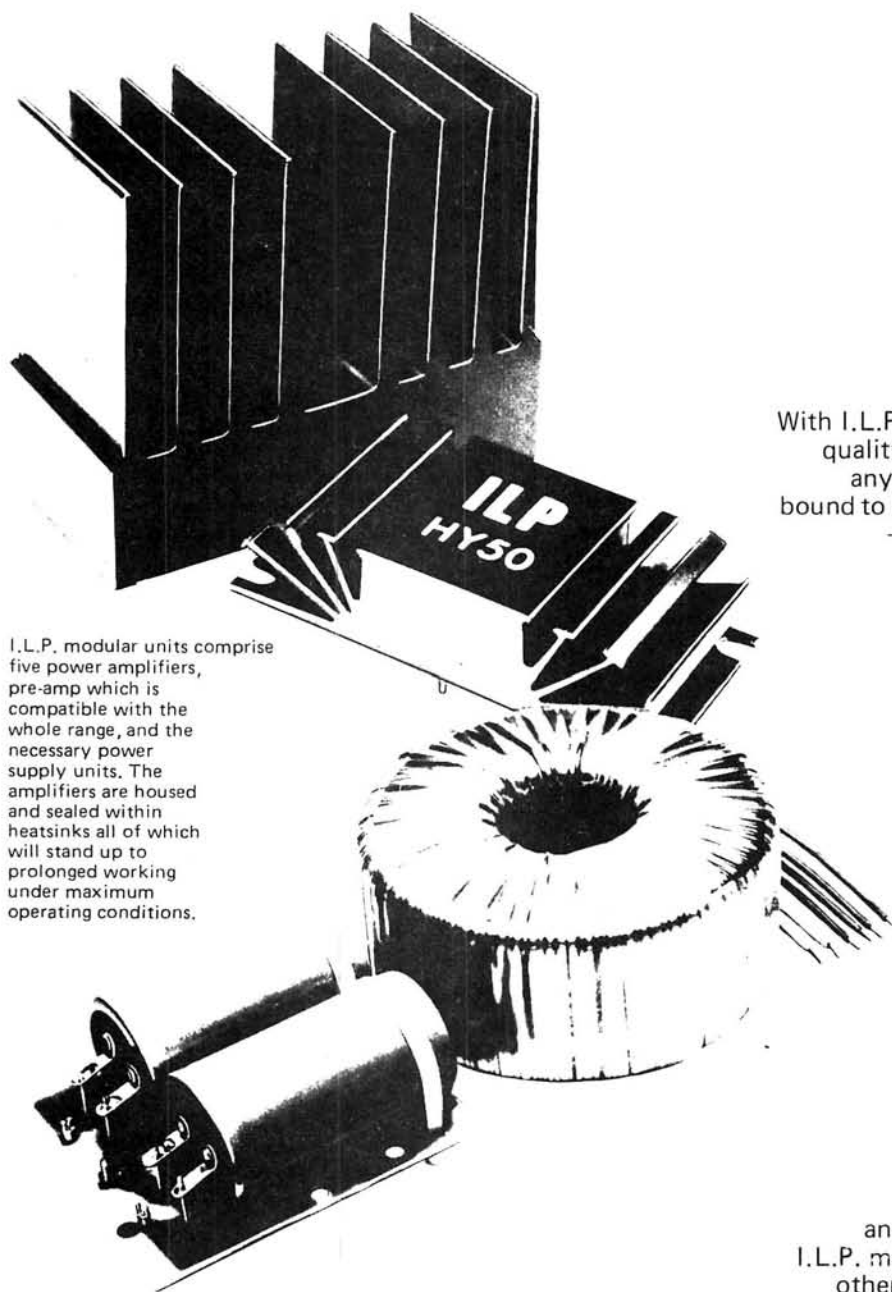

I.L.P. modular units comprise five power amplifiers, pre-amp which is compatible with the whole range, and the necessary power supply units. The amplifiers are housed and sealed within heatsinks all of which will stand up to prolonged working under maximum operating conditions.



With I.L.P. performance standards and quality already so well established, any advances in I.L.P. design are bound to be of outstanding importance – and this is exactly what we have achieved in our new generation of modular units. I.L.P. professional design principles remain – the completely adequate heatsinks, protected sealed circuitry, rugged construction and excellent performance. These have stood the test of time far longer than normally expected from ordinary commercial modules. So we have concentrated on improvements whereby our products will meet even more stringent demands such, for example, as those revealed by vastly improved pick-ups, tuners, loudspeakers, etc., all of which can prove merciless to an indifferent amplifier system. I.L.P. modules are for laboratory and other specialised applications too.

**PRODUCTS OF THE WORLD'S FOREMOST SPECIALISTS
IN ELECTRONIC MODULAR DESIGN**

and staying there

PERFORMANCE MODULAR UNITS

HY5 PRE-AMPLIFIER

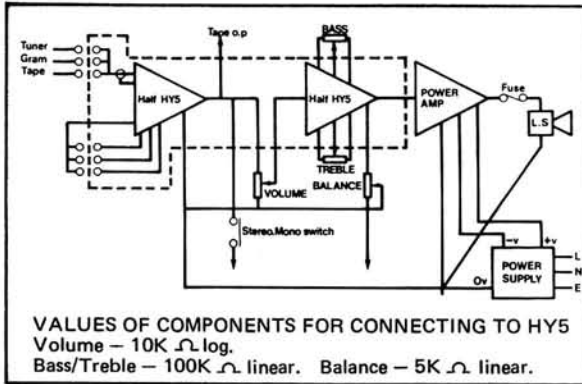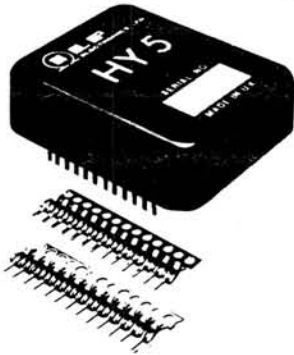


The HY5 pre-amp is compatible with all I.L.P. amplifiers and P.S.U.'s. It is contained within a single pack 50 x 40 x 15 mm. and provides multi-function equalisation for Magnetic/Ceramic/Tuner/Mic and Aux (Tape) inputs, all with high overload margins. Active tone control circuits; 500 mV out. Distortion at 1KHz—0.01%. Special strips are provided for connecting external pots and switching systems as required. Two HY5's connect easily in stereo. With easy to follow instructions.

£4.64 + 74p VAT

VALUES OF COMPONENTS FOR CONNECTING TO HY5
Volume — 10K Ω log.
Bass/Treble — 100K Ω linear. Balance — 5K Ω linear.

THE POWER AMPLIFIERS

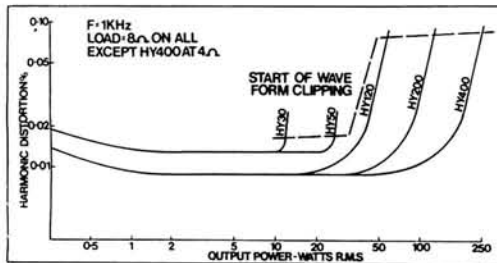

Model	Output Power R.M.S.	Distortion Typical at 1KHz	Minimum Signal/Noise Ratio	Power Supply Voltage	Size in mm	Weight in gms	Price + V.A.T.
HY30	15 W into 8 Ω	0.02%	80dB	-20 -0 +20	105x50x25	155	£6.34 + 95p
HY50	30 W into 8 Ω	0.02%	90dB	-25 -0 +25	105x50x25	155	£7.24 + £1.09
HY120	60 W into 8 Ω	0.01%	100dB	-35 -0 +35	114x50x85	575	£15.20 + £2.28
HY200	120 W into 8 Ω	0.01%	100dB	-45 -0 +45	114x50x85	575	£18.44 + £2.77
HY400	240 W into 4 Ω	0.01%	100dB	-45 -0 +45	114x100x85	1.15Kg	£27.68 + £4.15

Load impedance — all models 4 - 16 Ω
Input sensitivity — all models 500 mV
Input impedance — all models 100K Ω
Frequency response — all models 10Hz - 45Hz - 3dB

THE POWER SUPPLY UNITS



I.L.P. Power Supply Units are designed specifically for use with our power amplifiers and are in two basic forms — one with circuit panel mounted on conventionally styled transformer, the other with toroidal transformer, having half the weight and height of conventional laminated types.

PSU 30 $\pm 15V$ at 100ma to drive up to five HY5 pre-amps £4.50 + £0.68 VAT
PSU 36 for 1 or 2 HY30's £8.10 + £1.22 VAT
PSU 50 for 1 or 2 HY50's £8.10 + £1.22 VAT
PSU 70 with toroidal transformer for 1 or 2 HY120's £13.61 + £2.04 VAT
PSU 90 with toroidal transformer for 1 HY200 £13.61 + £2.04 VAT
PSU 180 with toroidal transformer for 1 HY400 or 2 x HY200 £23.02 + £3.45 VAT

NO QUIBBLE
5 YEAR GUARANTEE

7-DAY DESPATCH ON ALL ORDERS

INTEGRAL HEATSINKS

BRITISH DESIGN AND MANUFACTURE

FREEPOST SERVICE — see below

★ ALL U.K. ORDERS DESPATCHED POST PAID HOW TO ORDER, USING FREEPOST SYSTEM

Simply fill in order coupon with payment or credit card instructions. Post to address as below but do not stamp envelope — we pay postage on all letters sent to us by readers of this journal.



I.L.P. ELECTRONICS LTD.
FREEPOST 1 Graham Bell House, Roper Close,
Canterbury, Kent CT2 7EP.
Telephone (0227) 54778 Telex 965780

Please supply

..... Total purchase price £.

I enclose Cheque Postal Orders International Money Order

Please debit my Account/Barclaycard Account No.

NAME

ADDRESS

Signature

TWO REALLY GREAT ANTENNAS

THE JOYSTICK VFA (Variable Freq. Antenna)

claims un-beaten scoring over commercial and/or conventional antennae. ● Simple, rapid erection ● Not only 6-band but CONTINUOUS 0.5-30MHz., incl. BC & MARS ● Omni-directional ● Substantially Harmonic FREE ● 1,000,000 miles per watt, world record! ● Poor QTH's enhanced! CLIFF DWELLERS DREAM ANTENNA! ● QUOTE from RADIO ZS (South Africa) "A remarkable antenna with great possibilities. Its physical size makes confined space operation a practical proposition."

SYSTEM "A" 150 w.p.e.p. OR for the SWL **£48.55**
SYSTEM "J" 500 w.p.e.p. Improved "Q" receive **£54.00**

NEW JOYMASTER ANTENNA SYSTEMS Amateur Bands 3.5-30MHz

ANY amateur receiving or transmitting can benefit from PARTRIDGE JOYSTICK expertise. The JOYMASTER development adds to the efficiency of the JOYSTICK by providing tunable artificial earth elements to make your shack independent of its location problems. High-rise flat and cliff dwellers please note!

SYSTEM JM1 150 w.p.e.p. **£61.50**
SYSTEM JM2 500 w.p.e.p. **£69.00**

JOYSTICK OWNERS - PLEASE NOTE. YOU CAN CONVERT YOUR EXISTING SYSTEM "A" or "J" TO A JOYMASTER OF THE SAME RATING WITH AN ADD-ON PURCHASE (£35.50 to update "A", £43 to update "J"). ALL INSTRUCTIONS USUAL CARRIAGE, etc.

PARTRIDGE SUPER PACKAGES COMPLETE RECEIVING STATIONS FOR ANY LOCATION

All cables, matching communications, headphones, JOYSTICK System "A" Antenna. ON THE AIR IN SECONDS! SAVE £21.45!

FRG7Rx (and all accessories) (Ask for Pkg. R1) **£240.80**
(Rx. only £210.00, with FREE HEADPHONES).


FRG700Rx (and all accessories) (Ask for Pkg. R2) **£409.00**
(Rx. only £372.60, with FREE HEADPHONES).

SUPER BARGAINS IN YAESU/SWAN/PARTRIDGE PACKAGES

Quotes/Brochures on request.

BUSINESSMEN - VHF RADIO

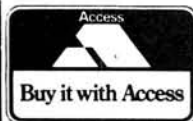Save time - petrol. Kill phone bills. Radio communication with your staff costs surprisingly little.
What is your problem?



JUST TELEPHONE YOUR CARD NUMBER

0843 62535 (ext 5) (62839 after office hours) or send 10p for FREE literature. Prices correct as at press. NOTE our prices are always INCLUSIVE OF VAT, carriage. Prompt service too, goods usually despatched WITHIN 48 HOURS!

5 Partridge House,
Prospect Road, Broadstairs, Kent CT10 1LD
(Callers by appointment).

G3CED
G3VFA



WAVEMETER Adm pattern LF wavemeter covers 10 to 30Kc in two ranges uses two plug in coils with direct calibration, absorption type with lamp ind. Also contains Tx 1100pf tuning cond this can be rebuilt for other capacities and spacings, the two coils contain large amount of silk covered copper wire all contained in polished wood case size 12x7x9 1/2" £10.50.

AMPLIFIER MODULE self contained plug in unit provides var gain up to 500 DC coupled, contains mains trans providing stab +20 & -20V supplies, good selection of 1% res, trim pots, transistors etc standard 230vI/P £5.50.

U.H.F. RX ASS single chan crystal controlled with crystal for 243Mc/s dual conversion IFs 20.5 & 2Mc/s 11 min valves low imp O/P reqs 200v HT & 6.3 size 9x4 1/2x4" new cond £16.50.

POWER UNIT INVERTOR special purpose unit for 115v I/P contains 6 pot cores FX2240/42/43 types, 2x HV TO-3 power transis, 4x 400v 3 amp diodes, 8x BC107, 2x BFY52 (types may vary) 2x Thyristors inc 4 amp type, 3x 20mm panel fuse holders, elec conds, res, swt & zener diodes etc all in screened case size 9x3 1/2x4" with circ £4.50 or 2 for £8.

RECORDING TAPE 1/4" by Ampex 3600 ft on 10 1/2" spools new £7.50.

RECEIVER UNIT small high performance Rx uses 7 min valves covers 2.5 to 20Mc/s in 3 bands as RF stage, BFO, Volt Stab. with O/P for HR or Crystal phones direct feq cal with geared drive size 5x3 3/4x3 1/2" these req ext supplies of 180v DC HT 40Ma & 6.3v AC 1 amp supplied tested with circ & notes no ext case £25.

TRANSMITTER ASS 2/8Mc/s low power contains 500Ua meter, tuning cond, coils, swts, terminals etc complete in case with circ less valves £5.50.

MAINS TRANS 200/250v Pria Sec 340-250-0-250-340v at 210Ma LTs 6.3v at 5 amps twice & 5v Ct at 5 amps size inc term 5 1/2x4 3/4x6" these will do 700v DC at 250Ma with no LT load new boxed £9.50.

RECEIVER UNIT small battery operated covers 2 to 8Mc/s in two band 4 valve superhet plus BFO in case direct feq cal O/P for low or high res phones with circ reqs 135v HT & 1.5v DC LT £13.50.

AUDIO TEST SET CT373 bench test set comprises AF Osc 17C/S to 170Kc, AF VTVM & Distortion meter new cond further spec on request £65.

CRYSTAL UNIT dual 1 Mc/s & 100Kc with suggested circ £2.80.

CRYSTALS 5/8Mc/s 10XJ type 20 for £2.20. H.F. RX R4187 & CONTROL BOX crystal controlled 24 chan Rx covers 2.8 to 18Mc/s intended for remote control dual conversion Rx with 2 RF stages, BFO, ML etc 15 miniature valves reqs ext supplies of 19 & 24v DC supplied with circs notes & suggested mods £25.

TAPE RECORDERS ex American services for 115v 50c/s supply 19" rack mounting uses 1/4" tape as 3 heads, 3 motors with servo controlled capstan drive speed 3 3/4" takes 7 1/2" spools, level meter, all controls on front panel weight about 30Kg valve amps 8 or 600 ohm O/P 600 ohm I/P £36.

HEAVY DUTY SLIDE RESISTORS 1 ohm 12 amps £5.75.

METERS 2" dia 0 to 40 amps DC with shunt £3.

AUDIBLE WARNING UNIT small warning unit for use on 12v DC size 1 1/2" dia about 800c/s new £1 ea or 2 for £1.70.

HELIPOT DIALS two types 10tr to fit 3/8th bush 1/4" shaft £1.50 also 15tr type with lock by Beckman £2.50 Helipot 100K & 30K £1 ea or 50p ea if ordered with Dials.

METERS panel mounting type all moving coil 2 & 3" types 4 different for £4.50.

IND UNIT 100 special test set contains meter 5-0-5 Ua with linear scale 3" dia in deluxe carrying case size 10x8x7 1/2" with terminals etc £8.50.

BLOWER UNITS heavy duty single ended outlet 2 1/2x3 1/2" for 240v supply req ext cond new £11.50.

MAINS TRANS general purpose type 240v pria sec tapped 0, 12, 15, 20, 24 & 30v at 1 amp £3.50 or 2 amp type £4.60. Miniature types 9+9 or 15+15 or 20+20v all 3Va per winding £2.40 ea all new.

FANS EXTRACTOR 230v 6" dia mount flange 7x8" new ex Adm £7.50.

TRANSISTOR INVERTORS 12v DC I/P O/P 180v at 40 Ma or 425v at 120Ma DC also 6.3v DC 2.5 amps in case size 5x4x3" tested with circ £10.50.

For callers Counters 1Mc/s valve type 115v £10.

Above prices include VAT & Carriage Goods ex equip unless stated new.

S.A.E. for enquiry or List 24.

A. H. SUPPLIES
122 HANDSWORTH RD,
SHEFFIELD S9 4AE
Phone 444278 (0742)

U.K. RETURN OF POST MAIL-ORDER SERVICE ALSO WORLD WIDE EXPORT SERVICE

R.C.S. LOW VOLTAGE STABILISED POWER PACK KITS

Post 45p **£2.95**
All parts and instructions with Zener diode printed circuit, rectifiers and double wound mains transformer input 200-240 a.c. Output voltages available 6 or 7.5 or 9 or 12V d.c. up to 100mA or less. Size 3 x 2½ x 1½in. Please state voltage required.

THE "INSTANT" BULK TAPE ERASER


Suitable for cassettes, and all sizes of tape reels. A.C. mains 200/249V. Leaflet S.A.E. **£7.50** Post 50p



HEAD DEMAGNETISER PROBE

£5.00

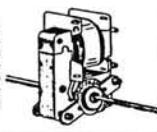A.C. ELECTRIC MOTORS
2 Pole, 240V, .2 Amp. Spindle - 1.43 x 0.212in. £1.75. 2 pole, 240V, .15 Amp. Double spindle - 1.75 x 0.16in. Each £1.50. 2 Pole, 120V, .5 Amp. Spindle - 0.75 x 0.2in. Two in series - 240V. 75p each. Brush Motor. From a Food Mixer 240V, .3 Amp. High Speed and Powerful. Spindle - 0.5 x 0.25in. £2.95



BLANK ALUMINIUM CHASSIS, 18 s.w.g. 2½in. sides, 6 x 4in. 95p; 8 x 6in. £1.40; 10 x 7in. £1.55; 14 x 9in. £1.90; 16 x 6in. £1.85; 12 x 3in. £1.20; 16 x 10in. £2.20; 12 x 8in. £1.70.

ALUMINIUM PANELS, 18 s.w.g. 6 x 4in. 24p; 8 x 6in. 38p; 10 x 7in. 54p; 12 x 5in. 44p; 12 x 8in. 70p; 16 x 6in. 70p; 14 x 9in. 94p; 12 x 12in. £1.16 x 10in. £1.16.
ALUMINIUM ANGLE BRACKET 6 x ½ x ½in. 20p.
ALUMINIUM BOXES, MANY SIZES IN STOCK.
4 x 2 x 2in. 86p; 3 x 2 x 1in. 60p; 6 x 4 x 2in. £1; 8 x 6 x 3in. £1.90; 12 x 5 x 3in. £2; 6 x 4 x 4in. £1.30; 10 x 7 x 3in. £2.20.

DE LUXE BSR HI-FI AUTOCHANGER

Plays 12in., 10in., or 7in records Auto or Manual. A high quality unit backed by BSR reliability with 12 months guarantee. A.C. 200/250V. Size 13½ x 11½in. Above motor board 3½in. Below motor board 2½in. With CERAMIC STEREO CARTRIDGE
BSR Single Record Player P207 cueing device, ceramic cartridge. Garrard Minichanger. Plays all size records. Ceramic cartridge. Stereo. **£15**
BSR. P182. Snake arm, flared Aluminium Turntable Stereo ceramic cartridge. Latest model. **£24**
BSR. Disco Single Player Cueing Device 11in. Turntable. Budget price. **£21**
RSC Disco Deck 3 speed Stereo **£9.95 or £18 pair**



BAKER 50 WATT AMPLIFIER

Post £1 **£65**
Superior quality ideal for Halls/PA systems. Disco's and Groups. Two inputs with Mixer Volume Controls. Master Bass, Treble and Gain Controls. 50 watts RMS. Three loudspeaker outlets 4, 8, 16 ohm. AC 240V (120V available). Blue wording on black cabinet.



BAKER 150 Watt AMPLIFIER 4 Inputs

Post 35p **£85**
DRILL SPEED CONTROLLER/LIGHT DIMMER KIT. Easy to build kit. Controls up to 480 watts AC mains. Printed circuit and components **£3.25**
STEREO PRE-AMP KIT. All parts to build this pre-amp. 3 inputs for high medium or low gain per channel, with volume control and P.C. Board. Can be ganged to make multi-way stereo mixers. **£2.95**

R.C.S. SOUND TO LIGHT DISPLAY MK 2

Complete kit of parts with R.C.S. printed circuit. Three channels. Up to 1,000 watts each. Will operate from 200MV to 100 watts signal source. Suitable for home Hi-Fi and all Disco Amplifiers. Cabinet extra £4.50. **£18**
200 Watt Rear Reflecting White Light Bulbs. Ideal for Disco Lights. Edison Screw 75p each or 6 for £4, or 12 for £7.50.

MAINS TRANSFORMERS Primary 240V A.C. ALL POST 75p
250-0-250V 70mA, 6-3V, 2A.....£3.45
250-0-250V 80mA, 6-3V 3.5A, 6-3V 1A.....£4.60
300-0-300V 100mA 6-3V 3.5 amp.....£5.80
300-0-300V 120mA, 2x6-3V 2A C.T.; 5V 2A.....£8.50
220V 45mA, 6-3V 2A.....£2.50
HEATER TRANSFORMER, 6-3V ½ amp £2.00 3 amp £2.20
GENERAL PURPOSE LOW VOLTAGE.

Tapped outputs available
2 amp 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 25 and 30V.....£6.00
1 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60.....£6.00
2 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60.....£9.50
3 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60.....£12.50
5 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60.....£16.00
12V, 100mA.....£1.30 20V, 40V, 60V, 1 amp.....£4.00
12V, 750mA.....£1.75 12V, 3 amp.....£3.50
10-0-10V 2 amp.....£3.00 10V, 30V, 40V, 2 amp.....£3.50
30V, 5 amp and 17V-0-17V, 40V, 2 amp.....£3.50
2 amp.....£4.00 20V, 1 amp.....£3.00
0-5, 8, 10, 16V, ½ amp.....£2.50 20-0-20V, 1 amp.....£3.50
9V, 3 amp.....£3.50 30V-0-30V, 2 amp.....£8.00
15-0-15V 2 amp.....£3.75 2 of 18V, 6 amp, each.....£11.00
30V, 2 amp.....£3.50 12-0-12V, 2 amp.....£3.50
30V, 1½ amp.....£3.30 9V, ½ amp.....£1.50
AUTO TRANSFORMERS
115V to 230V or 230V to 115V 150W.....£7.00
250W.....£8.00 400W.....£9.00 500W.....£10.00
CHARGER TRANSFORMERS
£4 4 amp.....£6.50
6 and 12V 3 amp.....£4.50
FULL WAVE BRIDGE CHARGERS RECTIFIERS.
6 or 12V outputs, 2 amp.....75p, 4 amp.....£1.75

BAKER LOUSPEAKERS "SPECIAL PRICES"

Model	Ohms	Size in.	Power Watts	Type	Our Price
Major	4, 8, 16	12	30	HI-FI	£12
Deluxe Mk II	8, 16	12	15	HI-FI	£14
Superb	8, 16	12	30	HI-FI	£22
Auditorium	8, 16	12	45	HI-FI	£20
Auditorium	8, 16	15	60	HI-FI	£30
Group 35	4, 8, 16	12	40	PA	£12
Group 45	4, 8, 16	12	45	PA	£15
Group 50	8, 16	12	60	PA	£20
Group 50	4, 8, 16	15	75	PA	£30
Group 75	8, 16	12	75	PA	£24
Group 100	8, 16	12	100	PA	£29
Group 100	8, 16	15	100	PA	£35
Disco 100	8, 16	12	100	Disco	£29
Disco 100	8, 16	15	100	Disco	£35

R.C.S. LOUSPEAKER BARGAINS

3 ohm. 6 x 4in. £1.50. 7 x 4in. £1.50. 8 x 5in. £2.50. 6½in. £1.80. 8in. £2.60. 10in. £3. 12in. £4.
8 ohm. 2½in. £1.50. 3in. £1.50. 5in. £1.50. 10in. £3. 12in. £4.
16 ohm. 6 x 4in. £1.50. 7 x 4in. £1.50. 5in. £1.50. 8in. £2.60. 10in. £3. 12in. £4. 10 x 6in. £3.50.

E.M.I. 13½ x 8in. SPEAKER SALE!

With tweeter. And crossover. **£9.95**
10W. State 3 or 8 ohm. Post 75p
Illustrated.
15W model with tweeter **£10.95**
8 ohms only. Post 75p



GOODMANS 20 Watt Woofer


Size 12 x 10in. 4 ohms. Rubber cone surround **£9.95**
Hi-Fi Bass unit. Post 65p

GOODMANS TWIN AXIOM 8-15 Watt

8in. 8 ohm Hi-Fi Twin Cone **£10.50**

R.C.S. MINI MODULE HI-FI KIT

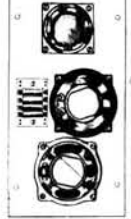15 x 8½in. 3-way Loudspeaker System, EMI 5 in. Bass 5in., Middle 3in. Tweeter with 3-way Crossover and Ready Cut Baffle. Full assembly instructions supplied.
Response = 60 to 20 000cps
12 watt RMS. 8 ohm.
£10.95 per kit. Two kits £20.
Postage £1. One or two kits.



RADIO COMPONENT SPECIALISTS 337 WHITEHORSE ROAD, CROYDON Tel. 01-684 1665

Cash price include VAT. Minimum post 30p. List 20p. Phone Access Barclay VISA. Open 9-6 Sat. 9-5 (Closed all day Wednesday)

Choose the World's finest kits.

Superb value. Building electronic kits is an enjoyable and very rewarding pastime.

And with Heathkit, it's also an easy way of making a wide range of useful electronic devices from doorbells to microcomputers, from car maintenance products to test equipment.

Top quality. Heathkit kits not only give you the pleasure of 'doing it yourself' but also the satisfaction that every kit is of the highest quality.

The step-by-step instructions, compiled by experts, make it easy for beginners and 'old hands' alike. And with Heathkit's excellent after sales service complete success is guaranteed. After all, 13 million kit builders over the last 34 years can't be wrong.

Excellent choice. To find the best kits, all you need is the Heathkit catalogue.

It contains detailed specifications of our comprehensive range to aid you in your selection.

Send for your copy today. Or if you're near our showrooms in Tottenham Court Road, London or Bristol Road, Gloucester, just call in and browse around.



To: Heath (Gloucester) Limited, Dept. (PW4), Bristol Road, Gloucester, GL2 6EE.
Please send a copy of the Heathkit catalogue. I enclose 20p in stamps.

Name _____

Address _____

Soldering Iron offer FREE


N.B. If you are already on the Heathkit mailing list you will automatically receive a copy of the latest Heathkit catalogue without having to use this coupon. When you receive your catalogue you will get details of this free offer.



STARCHASER 4000


THE NEW FOUR CHANNEL LIGHTING CONTROLLER

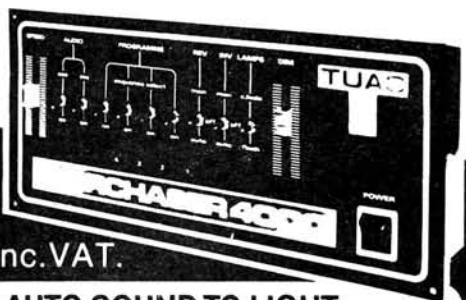- 4 channels 750W each
 - over 1000 different sequence patterns and effects
 - 3 alternative sound triggers
 - A.G.C.
 - simulated strobing
 - zero reference triac firing
 - superb TUAC quality and reliability
- £99.00 inc. VAT.



4 CHANNEL SOUND TO LIGHT SEQUENCE CHASER - 4LSM1

£22.95

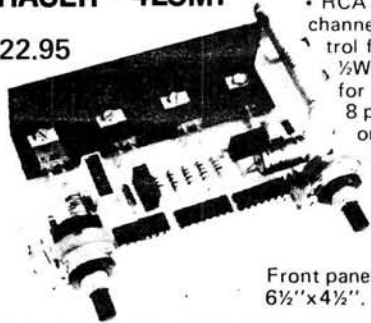

Front panel, size: 6 1/2" x 4 1/2". £7.75.

- RCA 8A Triacs • 1000W per channel
- Switched master control for sound operation from 1/2W to 125W
- Speed control for fixed rate sequence from 8 per minute to 50 per second
- Full logic integrated circuitry with optical isolation for amplifier protection.



3 CHANNEL AUTO SOUND TO LIGHT - AFL 6

£17.50



- RCA 8 amp Triacs • 500W per channel
- 2 channels flip flop, 1 channel sound to light
- Fully automatic via built in mic • No connection to amplifier necessary.

SEND FOR OUR FREE 28 PAGE CATALOGUE, PLEASE ENCLOSE A STAMP



TUAC Ltd., 119 Charlmont Road, SW17, Tel: 01-672 3137/9080
PRICE INCLUDES VAT. P+P FREE

TO ORDER BY POST. Make cheques/P.O.s payable to TUAC LTD. or quote Access/Barclaycard No. and post to TUAC LTD, 119 Charlmont Road, London SW17 9AB. We accept telephone orders from Access/Barclaycard Holders. Phone 01 672 9080.

TUAC MAIN DISTRIBUTORS (Callers Only)

- Birmingham, George Matthews, 85/87 Hurst Street, (Tel: 622 1941).
- London, Garland Bros., Deptford Broadway, (Tel: 01-692 4412).
- London, Session Music, 163 Mitcham Road, Tooting, (Tel: 01-672 3413) Mon-Sat 10am to 5.30pm. Closed Wed.
- Luton, Luton Disco Centre, 88 Wellington Street, (Tel: 411733).
- Manchester, A1 Music, 88 Oxford Street, (Tel: 236 0340).
- Middlesborough, Salcoglen, 43 Borough Road, (Tel: 242851).
- Watford, Component Centre, 7 Langley Road, (Tel: 45335)

VALVES			VAT INCLUDED		
EL81 1.20	PCF801 1.05	52.80	1R5*** 0.65	6AV6 0.60	6V6GT 0.95
EL82 0.70	PCF802 0.75	154 0.45	1S4 0.45	6AX4GT 0.95	6X4 0.70
EL84 0.90	PCF805 2.10	114 0.45	1T4 0.45	6AXSGT 1.15	6XSGT 0.65
EL86 1.05	PCF806 0.95	174 0.45	1X28 1.30	6B7 0.85	6Y6G 1.10
EL90 0.90	PCF808 2.05	184 0.45	1X28 1.30	6BA6 0.50	6Z4 0.75
EL91 3.25	PCF8200 0.95	202 0.80	1X28 1.30	6BE6 0.60	6-30L2 2.05
EL95 0.80	PCL81 0.70	202 0.80	1X28 1.30	6BG6 1.15	7B7 0.90
EL500 1.85	PCL82 0.75	202 0.80	1X28 1.30	6BH6 0.95	7V4 0.90
EL504 1.85	PCL84 0.80	202 0.80	1X28 1.30	6BJ6 1.25	902 0.70
EL822 7.50	PCL805/85	202 0.80	1X28 1.30	6BD7A 0.70	906 0.85
EM31 1.60	P0500 4.35	202 0.80	1X28 1.30	6BR7 2.70	10C2 0.70
EM80 0.70	PFL200 2.80	202 0.80	1X28 1.30	6BW6 5.18	10F18 0.70
EM81 0.70	PL36 0.95	202 0.80	1X28 1.30	6B7 1.15	10P13 1.25
EM84 0.70	PL81 0.85	202 0.80	1X28 1.30	6C4 0.70	10P14 1.25
EM87 1.15	PL82 0.65	202 0.80	1X28 1.30	6C4 0.70	10P18 1.25
EY81 0.65	PL83 0.60	202 0.80	1X28 1.30	6C6 0.70	35W4 0.80
EY86/87 0.65	PL84 0.75	202 0.80	1X28 1.30	6C6H 0.70	50C5 1.35
EY88 0.85	PL504 1.60	202 0.80	1X28 1.30	6C6H 0.70	50D66 1.45
EZ80 0.85	PL508 1.50	202 0.80	1X28 1.30	6C6H 0.70	50D66 1.45
EZ81 0.70	PL519 1.50	202 0.80	1X28 1.30	6C6H 0.70	50D66 1.45
GY501 1.05	PL509 3.85	202 0.80	1X28 1.30	6C6H 0.70	50D66 1.45
GZ32 0.75	PL802 3.15	202 0.80	1X28 1.30	6C6H 0.70	50D66 1.45
GZ33 3.95	PL810 3.45	202 0.80	1X28 1.30	6C6H 0.70	50D66 1.45
GZ34 2.30	PY33 0.70	202 0.80	1X28 1.30	6C6H 0.70	50D66 1.45
GZ37 2.80	PY80 0.70	202 0.80	1X28 1.30	6C6H 0.70	50D66 1.45
KT66 6.30	Y81/80/70	202 0.80	1X28 1.30	6C6H 0.70	50D66 1.45
KT88 8.95	Y82 0.70	202 0.80	1X28 1.30	6C6H 0.70	50D66 1.45
MH4 1.15	Y83 0.60	202 0.80	1X28 1.30	6C6H 0.70	50D66 1.45
ML6 1.15	Y84 0.60	202 0.80	1X28 1.30	6C6H 0.70	50D66 1.45
N78 10.45	Y85 0.60	202 0.80	1X28 1.30	6C6H 0.70	50D66 1.45
OZ2 0.65	Y86 0.60	202 0.80	1X28 1.30	6C6H 0.70	50D66 1.45
PC82 0.70	Y87 0.60	202 0.80	1X28 1.30	6C6H 0.70	50D66 1.45
PABCO 0.60	Y88 0.60	202 0.80	1X28 1.30	6C6H 0.70	50D66 1.45
PC85 0.60	Y89 0.60	202 0.80	1X28 1.30	6C6H 0.70	50D66 1.45
PC86 0.95	Y810 0.70	202 0.80	1X28 1.30	6C6H 0.70	50D66 1.45
PC88 0.85	Y811 0.70	202 0.80	1X28 1.30	6C6H 0.70	50D66 1.45
PC90 1.45	Y812 0.70	202 0.80	1X28 1.30	6C6H 0.70	50D66 1.45
PC92 0.75	Y813 0.70	202 0.80	1X28 1.30	6C6H 0.70	50D66 1.45
PC94 0.75	Y814 0.70	202 0.80	1X28 1.30	6C6H 0.70	50D66 1.45
PCF86 0.80	Y815 0.70	202 0.80	1X28 1.30	6C6H 0.70	50D66 1.45
PCF200 1.05	Y816 0.70	202 0.80	1X28 1.30	6C6H 0.70	50D66 1.45
PCF201 1.05	Y817 0.70	202 0.80	1X28 1.30	6C6H 0.70	50D66 1.45

POSTAGE: £1-£2 20p; £2-£3 30p; £3-£5 40p; £5-£10 60p; over £10 free, minimum order £1.
A lot of these valves are imported and prices vary for each delivery, so we reserve the right to change prices for new stock when unavoidable.

VALVES AND TRANSISTORS
Telephone enquiries for valves, transistors, etc.; retail 749 3934, trade and export 743 0899.

COLOMOR 907353/London
(ELECTRONICS) LTD.
170 Goldhawk Rd., London W.12
Tel. 01-743 0899
Open Monday to Friday
9-12.30, 1.30-5.30 p.m.

OHIO SCIENTIFIC SUPERBOARD 2	S-DECS AND D-DECS	BATTERY ELIMINATORS	BATTERY ELIMINATOR KITS	STABILIZED POWER KITS	COMPUTER GAMES	TV GAMES	MAIN TRANSFORMERS	JC12 AND JC20 AMPLIFIERS	CONTINENTAL SPECIALTIES PRODUCTS	PRINTED CIRCUIT MATERIALS	SWANLEY ELECTRONICS Dept. PW
50Hz model for UK tv sets. Full keyboard and cassette interface. Uses your tv as a vdu. 8K basic. 4K ram. Fully assembled £188 + 15% VAT, post free.	S-Dec £3.79, T-Dec £4.59, u-Dec A £4.69, u-Dec B £7.16.	3-way types with switched output and 4 way multi-tack: 3/4/6V 100ma £2.39, 6/7/9V 300ma £3.14, 100ma recorder types with press stud connectors 9V £3.57, 6V £3.57, 4.5V £3.57, 9+9V £4.79, 6+6V £4.79, 4+1.5V £4.79. Cassette recorder mains unit 7.5V 100ma with 5 pin din plug £3.57. Fully stabilized type 3/6/7/9V 400ma £5.89. Car converters 12V dc input, output 9V 300ma £1.19, output 7.5V 300ma £1.19, output 3/4/6/7/9/12V 300ma £2.66.	100ma recorder types with press-stud connectors 4.5V £1.49, 6V £1.49, 9V £1.49, 4+1.5V £1.92, 6+6V £1.92, 9+9V £1.92. Cassette type 7.5V 100ma with din plug £1.49. Heavy duty 13 way types 4+1.5V £1.19, 1/13/14/17/21/25/28/34/42V £4.95, 2A £8.20. Car converter input 12V dc, output 6/7/9V 1A stabilized £1.35.	The first price is for kit without transformer, the bracketed price includes transformer. TTL computer supply 5V 2A £2.95 (E£ 45), 5V 4A £3.95 (E£ 10.32). 8-way types 3/4/6/7/9/12/15/18V 100ma £1.74 (£2.50), 1A £3.18 (£5.30), 2A £4.17 (£8.15). Variable voltage models 2-18V 100ma £2.12 (£2.98), 1-30V A £3.18 (£6.20), 1-30V 2A £4.98 (£11.24).	Chess champion 6 £49.95. Chess challenger 7 £84. Chess challenger 2 £46. Star chess £62. Grandstand video entertainment computer £79.95. Videocarts £12.60. Philips G7000 Videopak home computer £149. Videopaks £12.95. Atari Videocomputer £147. Cartridges £14.85 (except chess £43.95 and backgammon £33.95).	Tank battles kit £8.34. AY-38500 chip £3.00, kit £4.26. Stunt cycle AY-38760 chip £13.71, kit £4.95. 10 game paddle £2. AY-38600 chip £10.25, kit £7.03. Racing car chip AY-38603 £13.63. Modified shoot kit £5.28. Rifle kit £5.27. Colour generator kit £9.05.	6-0-6V 1 1/2 £2.60, 9-0-9V 75ma 76p, 1a £2.22, 2a £3.94, 10-12-12V 100ma 92p, 1a £2.80, 15-0-15V 1a £3.15.	Integrated circuit amplifier chips with data and printed circuitries. JC12 6 Watts £2.08, JC20 10 Watts £3.14.	EXP300 £6.61, EXP350 £3.62, EXP325 £1.84, EXP650 £4.14, EXP48 £2.64, LP2 £20.70.	PC etching kits: economy £2.42, standard £4.48, 40 sq ins pcb 45p, 1 lb FeCl1 £1.30. Etch resist pens: economy 50p, delo 84p. Drill bits 1/32" or 1mm 30p. Etching dish 92p. Laminata cutter 90p.	1N4148 0.9p, 1N4002 2.9p, 1N4004 3.4p, BC109B 5.5p, 723 14 d1 33p, NE555 8 d1 24p, bc183, bc213, bc547, bc549 4.9p, bc182, bc184, bc212, bc214, bc548 5.5p, tip31c, tip32c 36p, tip41c 30p, bd131, bd132 27p, plastic equiv. bv72 5p, fuscs 20mm x 5mm cartridge -15, -25, -5, 1, 2, 3, 5 Amp quickblow 1p, anti-surge 3.6p, resistors 5amp 1/2W £12 10R to 10M 1p, 0.8p for 50+ of one value, polyester capacitors 250V -015, -068, -1mF 1.5p, -01mf 3.0p, -022, -033mf 3.3p, -047mf 3.5p, -15, -22, -33, -47mf 4.9p, polystyrene capacitors E12 63V 10 to 1000pF 3p, 1n2 to 10n 4p, ceramic capacitors 50V £22p to 47n 2p, electrolytic capacitors 50V .5, 1, 2mf 5p, 25V 5, 10mf 5p, 16V 22, 33mf 5p, 47, 68mf 3.5p, 100mf 6p, 330, 470mf 9p, 1000mf 10p, zenors 400mW E24 27V to 33V 7p, preset pots subminiature 0-1W 70p or var 100 to 4M7 7p, potentiometers 1W 4K7 to 2M2 log or lin single 2.7p, dual 7p, 1" red LEDs 9.7p, ic sockets 8 d1l 8.7p, 14 d1l 10.1p, 16 d1l 12p.

The Logic Probes

Spend Less

Test More



LP-1 Logic Probe

The LP-1 has a minimum detachable pulse width of 50 nanoseconds and maximum input frequency of 10MHz. This 100 K ohm probe is an inexpensive workhorse for any shop, lab or field service tool kit. It detects high-speed pulse trains or one-shot events and stores pulse or level transitions, replacing separate level detectors, pulse detectors, pulse stretchers and pulse memory devices.

All for less than the price of a DVM

£31.00*



LP-2 Logic Probe

The LP-2 performs the same basic functions as the LP-1, but, for slower-speed circuits and without pulse memory capability. Handling a minimum pulse width of 300 nanoseconds, this 300 K ohm probe is the economical way to test circuits up to 1.5 MHz. It detects pulse trains or single-shot events in TTL, DTL, HTL and CMOS circuits,


replacing separate pulse detectors, pulse stretchers and mode state analysers.

(Available in kit form LPK-1 £11.92)

£18.00*

The logic probes shown are all suitable for TTL, DTL, HTL and CMOS circuits.

*price excluding P.&P. and 15% VAT

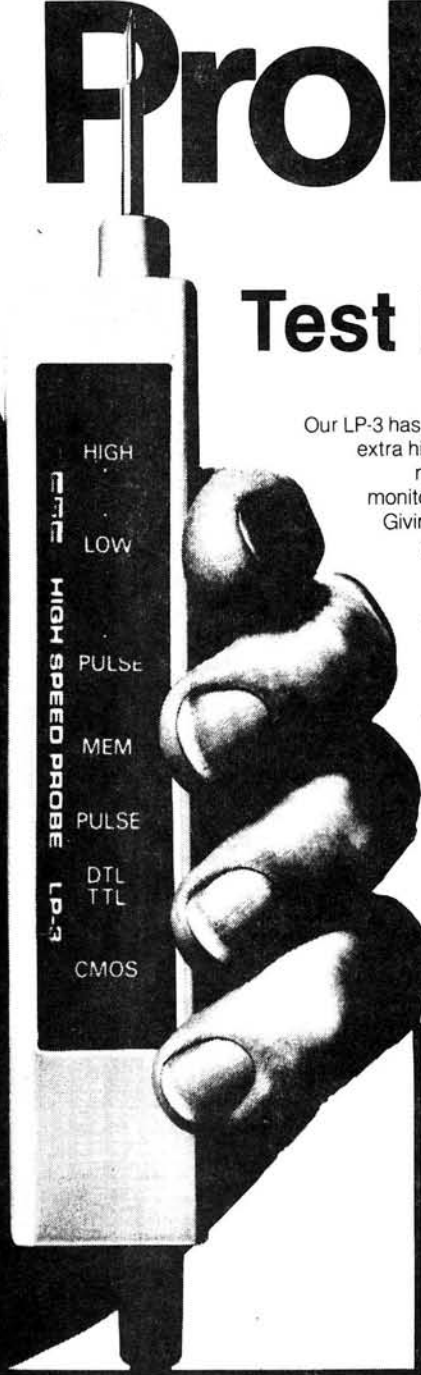

LP-3 Logic Probe

Our LP-3 has all the-features of the LP-1 plus extra high speed. It captures pulses as narrow as 10 nanoseconds, and monitors pulse trains to over 50 MHz.

Giving you the essential capabilities of a high-quality memory scope at 1/1000th the cost.

LP-3 captures one shot or low-rep-events all-but-impossible to detect any other way.

All without the weight, bulk, inconvenience and power consumption of conventional methods.

£49.00*



The New Pulser DP-1

The Digital Pulser: another new idea from C.S.C. The DP-1 registers the polarity of any pin, pad or component and then, when you touch the 'PULSE' button, delivers a single no-bounce pulse to swing the logic state the other way. Or if you hold the button down for more than a second, the DP-1 shoots out pulse after pulse at 1000 Hz.

The single LED blinks for each single pulse, or glows during a pulse train. If your circuit is a very fast one, you can open the clock line and take it through its function step by step, at single pulse rate or at 100 per second. Clever! And at a very reasonable price.

£51.00*

CONTINENTAL SPECIALTIES CORPORATION



C.S.C. (UK) Limited,
Dept.611, Unit 1, Shire Hill Industrial Estate,
Saffron Walden, Essex CB11 3AQ.
Telephone: Saffron Walden (0799) 21682
Telex: 817477

C.S.C. (UK) Ltd., Dept 611, Unit 1, Shire Hill Industrial Estate, Saffron Walden Essex CB11 3AQ
Prices include P.&P. and 15% VAT

LP-1	£37.38	Qty	LP-2	£22.14	Qty	LP-3	£58.08	Qty	DP-1	£60.38	Qty	LPK-1	£14.86	Qty
------	--------	-----	------	--------	-----	------	--------	-----	------	--------	-----	-------	--------	-----

Name _____ Address _____

I enclose Cheque/P.O. for £ _____ or debit my Barclaycard/Access/
American Express card no. _____ exp. date _____

FOR IMMEDIATE ACTION — The C.S.C. 24 hour, 5 day a week service.
Telephone (0799) 21682 and give us your Barclaycard, Access, American Express
number and your order will be in the post immediately. for FREE catalogue tick box

ELECTRO-TECH COMPONENTS LTD.


364 EDGWARE ROAD, LONDON, W.2. TEL: 01-723 5667

JVC-VICTOR HIGH FIDELITY STEREO CASSETTE TRANSPORT MECHANISM

ELECTRO-TECH COMPONENTS have secured a very large quantity of cassette transport mechanisms, equipped with all the latest improvements, as well as "SEN ALLOY" type 1.5 micron record/replay heads, and solenoid-controlled autostop action. These were manufactured by JVC/VICTOR of Japan to specification of TANDBERG OF NORWAY, for inclusion in a cassette deck costing over £250. This mechanism alone would normally cost over £50.

FEATURES:

- ★ Close-tolerance, high-quality, top loading transport
- ★ "Sen-Alloy" (SA type) R/P head
- ★ Solenoid-driven autostop circuit
- ★ Automatic head cleaning device
- ★ Air damped "soft" cassette eject
- ★ Miniature microswitches for switching
- ★ Pre-aligned heads and calibrated motor speed regulator built in
- ★ Three-digit tape position counter
- ★ Six-function keyboard controls "Record," "Rewind," "Forward," "Play," "Stop/Eject," "Pause."
- ★ PCB connectors and cables attached
- ★ High-mass balanced flywheel with permanent lubrication spindle
- ★ Full specifications for motor, heads, and switches available on request.

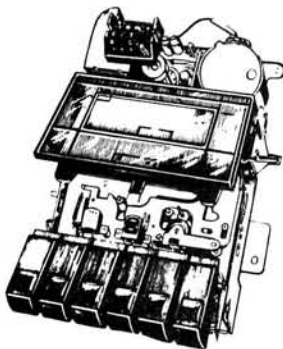

£14.95 VAT inc.

plus £1.00 P&P

★ CASSETTE DECK KIT BASED ON DESIGN OF MR. LINSLEY-HOOD ★

We have developed an outstanding stereo cassette kit with the aid of Mr. Linsley-Hood, to complement the improved specification and latest important advances in cassette electronics since the original design was published. The kit is ideal for use in conjunction with the JVC transport mechanism (left).

Included in the kit are two fibreglass PCB's, drilled and plated for immediate assembly, two VU meters, Dual LED Peak Meters, Variable Bias system, Power Supply, over 10 micro-circuit IC's for the most up-to-date performance, as well as monitoring amplifier, test and calibration cassette, etc.

Price of Kit (without transport mech.)

£35.95 VAT inc. plus £1.00 P&P

Also available. A custom-designed case for the Kit, this is a fully screened enclosure, sloping panel, satin anodised, wood end panels, professional finish.

Price of Case £9.75 VAT inc. plus £1.00 P&P

Readers will know of the original LINSLEY-HOOD CASSETTE DECK design, published in May 1976. Subsequent articles by Mr. Linsley-Hood have confirmed that the design far exceeded his original expectations, so much so that he published a number of improvements, modifications, and additional features to the original design, which are now incorporated in this Kit.

ELECTRO-TECH COMPONENTS LTD.

OFF THE SHELF DELIVERY ON THESE



DIGITAL MULTIMETERS

BRAND NEW FROM FLUKE NOW AVAILABLE THE 8024A HAND HELD DMM

This model incorporates all the features of the 8020A but in addition has:

- A peak hold switch which can be used in AC or DC for volts and current functions.
- Audible continuity testing and level detection for sensing logic levels.
- A temperature (°C) range for use with a thermocouple.

£135

Carriage and Insurance £3

The following accessories are in stock now

Y8008 Touch and Hold Probe.....	£18.00
80K-40 High Voltage Probe.....	£45.00
81RF RF Probe to 100 MHz.....	£32.00
80T-150C Temperature Probe (C).....	£55.00
801-600 Clamp-on AC Current Probe	£50.00



HERE IT IS .. THE BRAND NEW 8022A HAND-HELD DMM

Consider the following features:

- 8 resistance ranges from 200 ohm-20 ohms.
- 8 current ranges from 2mA-2A AC/DC.
- 10 voltage ranges from 200 mv-1000v DC-200 mc-750V AC.
- Pocket size - weighing only 370 gms.
- Full overload protection - will withstand 6kv spikes.
- Rugged construction - virtually indestructible.
- Meets tough military specs. - drop proof.
- In line, pushbutton operation for single-handed usage.
- Incorporates low power CMOS chip for low power consumption.
- All this plus a 2-year full guarantee.



For only £89

Carriage and Insurance £3

Soft carrying case

£7 extra

Even more sophisticated the Fluke 8020A.


Identical in most respects to the 8022A but in addition incorporates a conductance range from 2mS-200nS.

Price £112

Carriage and Insurance £3.00

A handsome soft carrying case is included (this model only)

OFF THE SHELF DELIVERY ON THESE

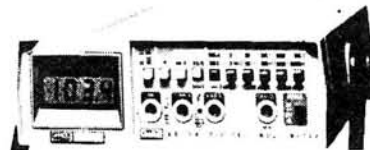

8010A AND 8012A BENCH MODEL D.M.M.s

The 8010A is a general purpose, bench/portable digital multimeter with more functions and features than ever offered for such a low price. Its companion, the 8012A, has identical characteristics except that it has two additional low resistance ranges, 2Ω and 20Ω to replace the 8010A's 10 ampere current range.

The 8010A and 8012A feature:

- 10 voltage ranges from 200mv-1000v dc, 200mv-75v ac.
- 3 conductance ranges from 2mS-200nS.
- 6 resistance ranges from 200Ω-20mΩ - the 8012A has two additional resistance ranges 2Ω and 20Ω.
- 10 current ranges from 200μA-2A AC/DC - the 8010A has two additional current ranges 10A AC and 10A DC.

8010A £159 8012A £179

Carriage and Insurance £3.

The 8010A is also available with two rechargeable Nicad size C batteries installed in option -01 a+ **£179.00.**



TMK500 MULTIMETER 30,000 OPV

A sturdy and reliable instrument. Has internal buzzer. AC volts: 0 to 2.5, 10, 25, 100, 250, 500, 1000.

DC volts: 0 to 0.25, 1, 2.5, 10, 25, 100, 250, 1000. DC current: 0 to 50 ua, 5 ma, 50 ma, 12 amp. Resistance: 0 to 6K, 6 meg, 60 meg. Decibels: -20 to +56 db. Short test: Internal buzzer. Size: 160x110x55 mm. **£20.50 P&P 75p**

IT 1/2 20,000 OPV

AC volts: 0 to 10, 50, 100, 500, 1000. DC volts: 0 to 5, 25, 50, 250, 500, 2500. DC current 0 to 50 ua. 2.5 ma, 250 ma. Resistance: 0 to 6K ohms, 6 meg ohms. Decibels: -20 to +22 db. Capacitance: 10 pf, 0.01 uF, 0.1 uF. Size: 4½x3½x1 inch. **£10.95 P&P 75p**


PLEASE ADD 15% VAT to ALL ORDERS EXCEPT WHERE ITEMS MARKED "VAT INCLUDED" CALLERS WELCOME

We are open 9 a.m.-6 p.m. Monday-Saturday. We carry a very large selection of electronic components and electro-mechanical items. Special quotations on quantities.

BENDIX MAGNETIC CLUTCH

Superb example of electro-mechanics. Main body in two sections, coil section fixed with ¾" sleeve, drive section rotating on outer perimeter. Uniting plate has ¾" ID bearing concentric with main section and 18-tooth cog wheel. Extremely powerful transmission. 24V D.C. 240 m/a.

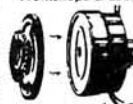Dozens of uses in Home, Farm, Workshops & Lab.



£4.75 P&P 75p

ROTARY STUD SWITCH

PLESSEY 30-way, 2 bank, Single pole. Contacts 1 amp 240v, AC/DC, 0.05Ω res. Make before break. Stop infinitely adjustable allowing for any desired arc of travel. Ideal for instrument and model switching. Size 2½" dia. overall 2½" deep plus 1½"x¼" dia. spindle. **£3.25 P&P 50p**





Multiple Choice

EDITOR

Geoffrey C. Arnold

ASSISTANT EDITOR

Dick Ganderton C. Eng., MIERE

ART EDITOR

Peter Metalli

TECHNICAL EDITOR

Malcolm Cummings G8KPN

NEWS & PRODUCTION EDITOR

Alan Martin

TECHNICAL SUB-EDITOR

Joe Bishop

TECHNICAL ARTIST

Rob Mackie

ASSISTANT ART EDITOR

Keith Woodruff

SECRETARIAL

Sylvia Barrett
Sharron Breeze

EDITORIAL OFFICES

Westover House,
West Quay Road,
POOLE, Dorset BH15 1JG
Telephone: Poole 71191

ADVERTISEMENT MANAGER

Telephone: 01-261 6636

Dennis Brough

AD. SALES EXECUTIVE

Telephone: 01-261 6807

Roger Hall G8TNT (Sam)

CLASSIFIED ADVERTISEMENTS

Telephone: 01-261 5762

Colin R. Brown

MAKE UP & COPY DEPARTMENT

Telephone: 01-261 6570

Dave Kerindi

ADVERTISEMENT OFFICES

King's Reach Tower, Stamford St.,
London, SE1 9LS
TELEX: 915748 MAGDIV-G

FOLLOWING the first of the "new format" Radio Amateurs' Examinations in May 1979, several readers wrote to us complaining that some of the questions had been misleading, and asking that we put pressure on the City and Guilds of London Institute (the examining body) to get the problems sorted out. Unfortunately, none of these readers could provide any examples, and we felt we could not pursue the matter.

When the December examination came around, several members of *PW*'s editorial team were candidates, and, if the gods smile on us, there will be more callsigns appearing on the staff list shortly. What we saw then certainly confirmed what had been said about the May exam, and prompted us to write to the CGLI at some length. The points which we made can be summarised as follows:

1. Questions in a single-answer, multiple-choice examination paper must be ones having only one answer according to established and widely published knowledge, and that answer must be included as one of the options. If not, choosing an answer becomes at best a process of elimination, and at worst a lottery. (*I will be returning to this later.*)
2. It follows from "1" above, that in questions on subjects where knowledge is incomplete, or where opinions differ, the contentious parts of the subject must be avoided at all costs. (*A question on propagation asked for the highest reflecting layer in the UK at midwinter noon. On this point, textbooks tend not to agree even with themselves, let alone each other!*)
3. The language in which the questions are phrased must be easily understood by a competent candidate and must, above all, be good English. (*One question was not a complete sentence.*)
4. Any drawings must be accurately drawn if the candidate is not to be left wondering whether some particular feature is intentional (and therefore possibly important) or accidental. (*Some of the modulation waveforms were frankly weird!*)

The above were illustrated with a number of examples which we could recall from the exam (the question papers cannot be taken away by the candidates).

It also seemed strange to us that, while some questions demanded knowledge of two or three topics to arrive at an answer, penalising a candidate who was not familiar with one topic, other questions were almost duplicates, or virtually gave the answer to each other.

The initial reaction from City and Guilds has been, to say the least, disappointing. In answer to point "2" above, they comment that because the syllabus requires only an elementary knowledge of radio-communication, such as might reasonably be gained during a one-year course, a candidate should not infer more from the questions than is intended or expressed. This seems to be saying: (a) Don't read the questions too carefully, and (b) You could be penalised if you know too much; both of which are obviously nonsense.

On the point of overlapping questions, the CGLI's answer infers that the number of questions to be asked is too great for the breadth of the syllabus, and that overlap is inevitable.

We were interested to receive from an unknown reader, shortly before Christmas, a photocopy of a document which purports to be the May 1979 RAE question papers. This reinforces a feeling that the examiners have certain pet subjects. From the question topic and frequency, one might be forgiven for thinking that the average radio amateur likes little better than to operate a temporary or mobile station, using an indoor aerial and located within half a mile of an aerodrome boundary on the Isle of Man, transmitting nothing but recordings with s.s.b. modulation, and wondering all the while who might come along to revoke his licence!

In all this, it is important to remember just what the Radio Amateurs' Examination is supposed to achieve. It is to ensure that a successful candidate can safely be let loose on the air, designing, building and operating his own equipment if he so desires, with enough knowledge to avoid the wholesale wiping out of other radio-communication services. The subject area covered by the syllabus is not over-wide, but the past two exams have not, in our opinion, covered even that adequately.

continued opposite ►

Mobile Rallies

The North Midlands Mobile Rally, organised by The Midland Amateur Radio Society and Stoke-on-Trent Amateur Radio Society, will take place on Sunday, 13 April 1980 at Drayton Manor Park near Tamworth, Staffs.

The rally opens at 11.30am and visitors will be made very welcome. There will be talk-in stations on 2m and 70cm.

Further details of the programme, car stickers etc. free on request from: *Norman Gutteridge G8BHE, 68 Max Road, Quinton, Birmingham B32 1LB. Tel: 021-422 9787.*

Simon Lloyd Hughes GW8NVN, Publicity Officer of the Barry College of Further Education Radio Society, informs me that the "Welsh Amateur Mobile Rally" will be held at the Barry Memorial Hall on Sunday, 20 April 1980.

Further details can be obtained from: *K. B. Hodge, 16 Claude Road West, Barry, South Glamorgan.*

2m Contest

Barking Radio & Electronics Society G3XBF/G8GPK, have organised a 2m contest to be held on 30 March 1980, between 1300 and 1700hrs GMT.

The contest will be divided into three sections: 1. All licensed operators residing in the county of Essex; 2. All licensed operators residing outside the county of Essex; 3. All short wave listeners.

For further details of scoring and contest rules contact: *A. Sammons G8IZN, 80 Lyndhurst Gardens, Barking, Essex IG11 9XZ. Tel: 01-594 2471.*

► We have no wish to bring the CGLI into disrepute, nor to reveal large sections of their question bank, but would quote the following, which we understand to have been included in the May 1979 examinations, as an example of a question which should never have got through the vetting and pre-test procedure.

Q Ohm's Law states that

a a current of one ampere flows in a circuit having a resistance of one ohm when one volt is applied to it

b $I = \frac{E}{R}$

c when one coulomb of electricity passes between two points there is a potential difference of one volt then one joule of work is done

d the current flowing in a circuit is directly proportional to the applied e.m.f. and inversely proportional to the resistance of the circuit.

Well, remembering that the paper clearly states that "only ONE is correct", which would **you** choose as your answer? Turn to page 44!

EDXC Conference in Paris, 1980

The 14th annual European DX Conference is to be held in Paris, between 23 and 26 May 1980. The conference is primarily aimed at short-wave broadcast band listeners as a forum for discussion.

Many well-known s.w. broadcasting stations will also be participating, creating a unique opportunity for broadcaster-listener dialogue.

Every effort has been made to keep the cost of participation as low as possible and it is estimated that the approximate cost of participation, including all meals and trips, will be 600 French Francs.

All s.w. listeners and DXers, regardless of experience, are invited. Conference registration is open now and the closing date for receipt of forms is 25 March 1980. A charter group from the UK to Paris may be organised if sufficient demand is shown.

For full conference details send a s.a.e. (or 2 IRCs outside UK) to: *EDXC, PO Box 4, St Ives, Huntingdon, England PE17 4FE.*

Television Exhibition

In March 1930, Baird's much-heralded "Televisor" was finally on sale, and the experimental 30-line transmissions from the BBC's Brookmans Park station were for the first time accompanied by sound. Television broadcasting, in fact, had arrived, and the fiftieth anniversary of this milestone is being marked by a special exhibition at the Science Museum, opening at the end of March 1980 for six months.

The title of the exhibition is "The Great Optical Illusion", and one of its aims is to reawaken the sense of wonder that is properly due to television but that our familiarity with it has inevitably dulled. An introductory exhibit will show what is involved in making a moving picture out of a single spot of light, and the "illusion" theme will be maintained with other demonstrations: "Chromakey", an electronic overlay technique, will make visitors appear to be performing a feat of aerial daring while actually just off the floor, while 'Front Axial Projection' will insert them optically into a projected scene. Nearby, visitors will be able to see each other on a reconstructed 30-line system, amidst relics of the low-definition era.

The exhibits outlining television's development since the opening of the 405-line service in 1936 will be punctuated by a series of period room-settings, in each of which it is hoped to show a montage of contemporary programmes on restored receivers of appropriate vintage; these will include a pre-war set with a five-inch tube, and a 'projection' set of the early 1950s. A display of videotape recorders will illustrate the dramatic fall in their size and price since they were first introduced, and there will be a working specimen of a type of British telecine machine that has been used with conspicuous success through three decades.

The final section of the exhibition will show how the television set is outgrowing its original function of receiving broadcast programmes, with items on TV games, teletext, viewdata, the video long-playing disc, and the domestic colour camera. This last, with the aid of two domestic videotape recorders and a tape loop, will enable visitors to make a short appearance before the camera and then, a minute or so later, see and hear themselves played back on a large-screen projection colour receiver.

The exhibition has been made possible by the collaboration and generosity of the BBC, the IBA and the ITV programme companies, and of the television industry, notably Philips Industries, Thorn Consumer Electronics, and Radio Rentals.


The exhibition (Admission Free) is open: From 10.00-17.45hrs weekdays; 14.30-17.45 Sundays, at: *Science Museum, South Kensington, London SW7 2DD. Tel: 01-589 3456.*

**SPECIAL
PRODUCT
REPORT**

**ELECTRONIC
IGNITION
SYSTEM
KITS**



SUREFIRE

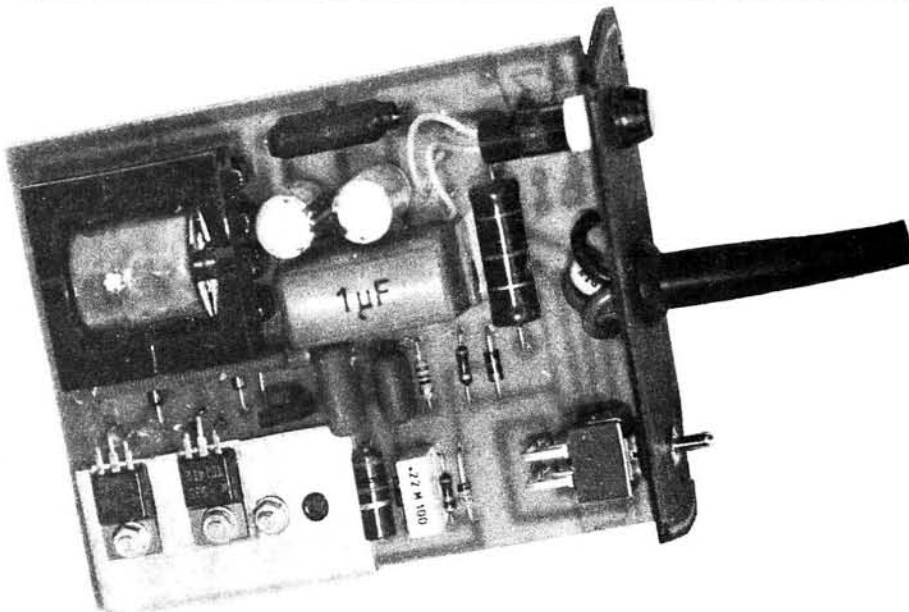

Now that petrol prices seem to go up every few weeks, motorists have become more interested than ever in any improvement in fuel economy. This is one of the benefits claimed (somewhat extravagantly by some manufacturers) for electronic ignition systems, and has undoubtedly played a large part in their rise in popularity in recent years. It is interesting to note that Suretron Systems (UK) Limited do not claim increased fuel economy for their systems, other than as a result of the reduced wear on the Contact Breaker points, allowing them to remain in correct adjustment for longer periods.

Suretron have been involved in the manufacture of electronic ignition systems for some five years, and currently produce the Surefire ES1000, ES2000 and C3000 models, the first two being inductive systems, and the last a capacitive discharge system. In 1979 Suretron decided to launch kit versions of the ES2000 and C3000, called the ES200 and C300 respectively. These are electrically similar to their ready-built brothers, but differ mechanically in some ways, principally in that the p.c.b. module is no longer unpluggable for repair. The CONVENTIONAL-OFF-ELECTRONIC switch is retained as a useful "insurance" feature.

A sample of each kit was built and fitted to a *PW* staff-member's car, with the following results.

ES200

The ES200 proved reasonably simple to construct from kit form, once one had sorted out exactly what was what. The components list in the kit assembly instructions described nine separate "packs"; in fact, the box contained five polythene bags of parts, the lengths of wire, the extruded aluminium case and the bolt-on heat shunt, with no indication as to which bit belonged to which "pack"!

It was pleasing to find that all the lead-wires had been accurately trimmed and bent to suit, but it must be admitted

that the shine was taken off by discovering that one of the resistors was missing! The lead spacing of one of the capacitors was incorrect for the p.c.b. drilling—otherwise, assembling the components onto the board was snag-free.

The assembly of the unit itself was a little more problematical, however. Persuading the four wires that connect the unit into the car's electrical system that they should fit through the sleeved grommet supplied, took several minutes, liberal applications of cable lubricant and a couple of words that you won't find in Chamber's Dictionary. At home one would, I suppose, use soap or washing-up liquid to ease things along but if a grommet of a slightly larger diameter were supplied, the task would be facilitated without making the unit any less water-resistant.

Fitting the p.c.b. into the case was frustrated by the heat shunt locating rather poorly, presumably due to inaccurate drilling. Some fairly energetic filing was necessary before a firm sliding fit could be achieved. The instructions confidently described the spade terminal-shrouds as being either clear or black when they were, in fact, all clear—the dif-



ference in dimensions between the two types was not really obvious from the drawing supplied.

Generally, though, there were no problems that anyone with even a modicum of common sense could not have rapidly sorted out. It took just on two hours to construct the unit—installing it into my ancient Austin 1300 was simplicity itself (15 minutes). Changing the contacts for a new set, and re-setting the timing and sparking plug gaps took about 45 minutes and I found the orange static-timing light, which is a feature of this unit, very handy in doing the job. This light is illuminated all the time when the engine is running on "electronic" (you do have a choice so that you are not immobilised if the unit fails) and, in view of this, it seems a pity that an l.e.d. or at least an easily replaceable lamp could not have been used. To replace the type supplied (which admittedly should last quite a time, being underrun) would involve dismantling the unit; rather a nuisance, I felt.

Certainly, the ES200 has had a marked beneficial effect on the cold starting of the car, which is kept permanently outside. Even when it has been left standing for a couple of days, it usually responds first time which was certainly *not* the case before the unit was fitted! Another immediate benefit appeared to be a marked improvement in fuel consumption but, feeling that this was probably more as a result of the timing being inaccurate *before* the unit was fitted, I decided to compare the fuel consumption and general performance during two almost identical weeks of driving, covering around 400 miles in each week. This seemed the fairest and most valid way of assessing the difference which the Surefire is making to the *economy* performance of the car while, at the same time, identifying any other effects.

My feeling that the timing was inaccurate before the unit was fitted (it was set by a garage) proved to be entirely justified, for the fuel consumption proved to be virtually identical during both weeks of the test (around 37 m.p.g.)—if anything, slightly better fuel economy was obtained with the ignition in the "conventional" mode! Each week contained a weekend round trip of 300 miles as well as the normal "drag" to and from the office and therefore my old workhorse can be considered to have run the full gamut of road conditions and usage, during the test period. In fairness, as already pointed out, the manufacturer does not claim that improved economy will result from the installation of an electronic system—the claimed advantages are those of improved and consistent cold starting, and improved contact wear leading to a reduction in maintenance.

At the conclusion of the test, I can certainly confirm both of these points with some enthusiasm; the car starts a lot better, runs well and the contacts are still very new and pristine-looking after 1000 miles or so of "electronic" motoring. The ES200 appears to be a worthwhile investment which can, as a matter of simplicity, be transferred from one vehicle to another and which should survive many miles and years of use. JB

C300

The comments on assembly of the ES200 kit apply equally to the C300, except that in this case, all components were present, but the inverter transformer, which is externally symmetrical, did not have the red dot on one corner as promised by the instruction sheet. Some 10-15 minutes detective work with test meter and circuit diagram was required to sort this one out. (*Suretron tell us that their procedures for component checking when packing the kits should have overcome this type of problem. Ours were taken from a small pilot run*).

The holes in the heatsink and p.c.b. did not correspond exactly, but by placing the two together in such a way as to distribute the errors evenly, no problems were experienced, and the completed assembly slid into the case perfectly.

The unit was fitted to an early Leyland Princess 1800 (patriotic lot, aren't we!) in about ten minutes. Regapping the sparking plugs took another ten minutes, the points were almost new so they were left alone. Starting of this car is very good in all conditions anyway (aided, no doubt, by its owner's obsessive attitude towards keeping the ignition system parts clean and coated in anti-damp compound), but the electronic system does seem to improve marginally even upon that.

There was no opportunity to carry out any extensive economy tests. Over a fairly short distance there was no noticeable difference in consumption, compared with conventional ignition. GCA

Prices

The kits are available by mail order from the manufacturers, who also offer a fault-finding and repair service for a standard charge of £5 including the cost of all parts used in the repair, VAT, carriage and insurance for the return of the unit. The prices for the kits are £13.95 for the ES200 and £17.95 for the C300, inclusive of VAT, postage and packing.

Suretron Systems (UK) Ltd., Piccadilly Place, London Road, Bath BA1 6PW. Telephone: Bath (0225) 23194.

KINDLY NOTE!

Burglar Alarms, Part 2. October 1979

It has been brought to our notice that uncorrected versions of the component layout diagrams (Figs. 4 and 9) were used in error. As a result, all diodes (with the exception of D10, which was drawn correctly) have been shown reversed. We apologise for any confusion that this may have caused.

Car Wiper Unit, February 1980

In Fig. 2, Tr3 and Tr5 have been drawn with the correct lead connections but with their case outlines reversed. The diagram shows the correct lead configuration for the BC182L, *viewed from below*. Note also that R1 and R2 are mounted on the terminals of VR1 and S2 respectively.



BC182L

WRM235

ICF-6800W Receiver Review, February 1980

In the Specification table, two items of information were omitted. The Frequency range on FM is: 87.5-108MHz. The Circuit system on FM/MW is: Single superhet.

STEREO AUTOMATIC FADER

R.A. PENFOLD

A stereo fader unit is a form of mixer which combines the signal from a microphone with a stereo music signal. However, it has an additional feature of automatically fading out the music signal to some predetermined level when there is a microphone signal of a suitably high amplitude.

The main use for this type of equipment is probably in the preparation of tapes to accompany slide or home movie shows. The unit is used to automatically fade out the background music during the commentary, and return it to its normal level during breaks in the commentary. This type of equipment can also be employed in disco systems, and there could well be other fields of application.

Block Diagram

The block diagram of Fig. 1 shows the general arrangement of the automatic fader unit. The microphone signal is fed to a high gain preamplifier which brings the signal up to a level of a few hundred millivolts r.m.s., before it is split into three parts. One part is mixed with the right hand channel music signal, and another is mixed with the left hand channel music signal. Each music channel is fed to its respective mixer stage via a v.c.a. (voltage controlled attenuator) which normally gives zero attenuation. However, in the presence of a reasonably high output from the microphone preamplifier, the third part of this signal causes the two v.c.a.s to fade out the music signals.

This is accomplished by first rectifying and smoothing some of the preamplifier's output. The d.c. bias this produces is then fed to a level detector, and if the bias is of a suitably high level the output of the level detector falls from a high level to virtually zero volts.

The voltage change is used to drive the v.c.a.s via a buffer stage, and causes the music signal to fade out. A time constant is included between the level detector and buffer stages, with a characteristic which gives a fast attack and slow decay. This ensures that the music signal quickly fades out at the commencement of the voice signal, and then the music slowly returns to full level when the microphone signal has ceased, which gives the best effect in practice. The rectifier and smoothing network ahead of the level detector has a similar characteristic, and this again ensures that the music signal level rapidly diminishes at the commencement of the voice signal. The slower decay time prevents the music signal from starting to return to normal level during the brief pauses that occur during normal speech.

Opto-Isolator

As can be seen from the circuit diagram of Fig. 2, the v.c.a.s in this unit use an opto-isolator arrangement with a light emitting diode driving a cadmium sulphide photo-resistor. D5 and PCC1 form the opto-isolator for the left hand channel, while D8 and PCC2 are the opto-isolator for the other channel. With its driving l.e.d. switched off and the photocell in total darkness, it exhibits a resistance of at least 200M Ω , but by switching on the l.e.d. this can be considerably reduced. The actual resistance with the l.e.d. fully on is about 50k Ω in this circuit.

It is obviously a quite straightforward matter to connect the photocell in an attenuator, and then control the attenuation level by varying the voltage fed to the l.e.d. and its series current limiting resistor. There are disadvantages to this system when compared to some others, and it is for instance more expensive than using a j.f.e.t. as the gain control element, and needs a far larger driving signal. It does have two important advantages over most alternative methods, the main one being the generation of negligible noise and distortion. The complete electrical isolation between the l.e.d. and the photocell makes this arrangement very convenient and versatile from the designer's point of view.

If we now consider the operation of one channel of the unit, PCC1 is connected to the negative feedback loop of an operational amplifier inverting mode circuit which utilises IC2. The closed loop voltage gain of the circuit is equal to R15 divided by the resistance between the input signal and the inverting (-) input of the operational amplifier.

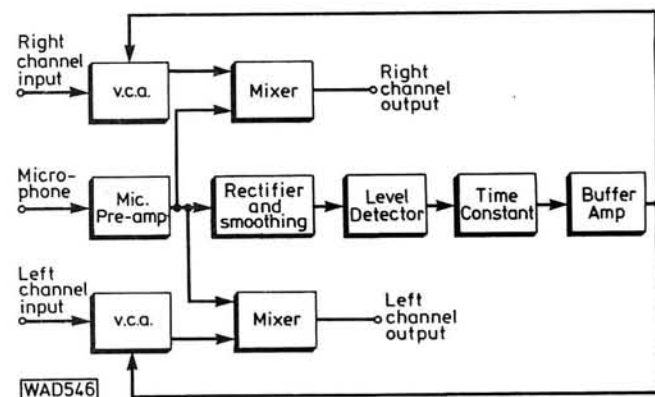


Fig. 1: Block diagram of the automatic fader

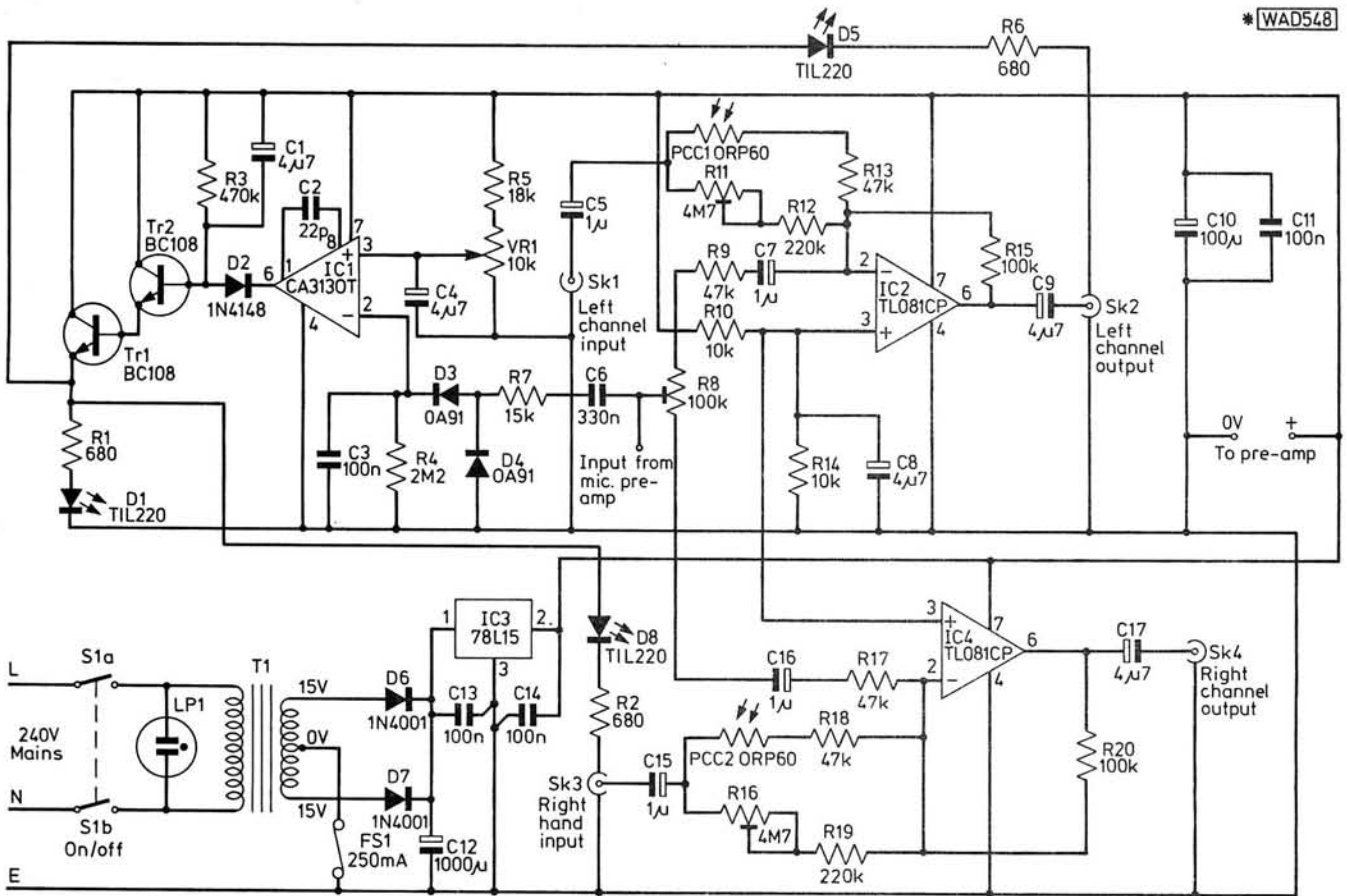



Fig. 2: Circuit diagram of the fader unit

This input resistance is comprised by the series-parallel combination of PCC1, R13, R11 and R12. Under quiescent conditions R3 will strongly forward bias the buffer amplifier formed by Tr1 and Tr2, and D5 will be switched fully on by the drive voltage from Tr1 emitter. This gives a series resistance of roughly 100kΩ through PCC1 and R13, and gives IC2 a closed loop gain of about unity. R11 and R12 have little effect on the circuit at this stage due to their relatively high resistance.

If the output of the level detector circuit (IC1 output) goes to a low voltage the base bias for Tr2 will be diverted through D2 and IC1 output, causing Tr1, Tr2 and D5 to turn off. The resistance of PCC1 then goes to a very high level, effectively cutting both it and R13 out of circuit. The voltage gain between the left hand input and output is then determined by the series resistance of R11 and R12, and varies from about -7dB, with R11 at minimum resistance, to approximately -34dB, when it is at maximum resistance. Thus the signal is faded out in the required manner, and by an amount which can be adjusted to suit individual requirements.

When the level detector's output returns to the high state the presence of D2 prevents D5 from immediately being switched fully on again. Instead it is slowly brought up to full brightness over a period of one or two seconds as C1 gradually discharges through R3, and the voltage at Tr1 emitter is increased back to maximum. This results in the music signal being smoothly brought back to its previous level.

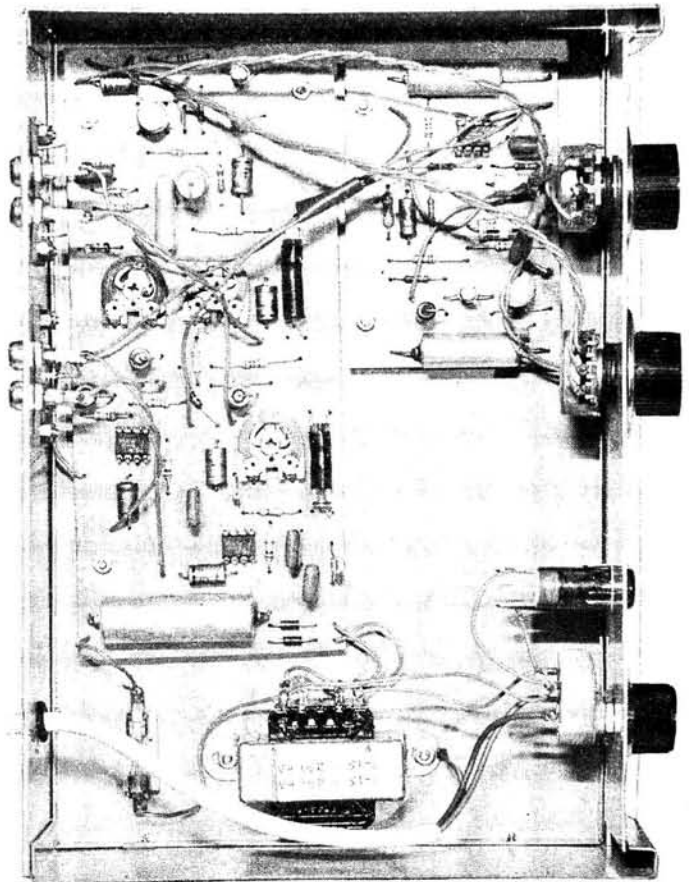The right hand channel uses IC4 in an arrangement that is identical to that employed in the left hand channel. D8 is driven in parallel with D5 from Tr1 emitter. There is a third i.e.d., D1, fitted as a panel indicator. This switches off when the music channels are faded out.



Interior view of the unit

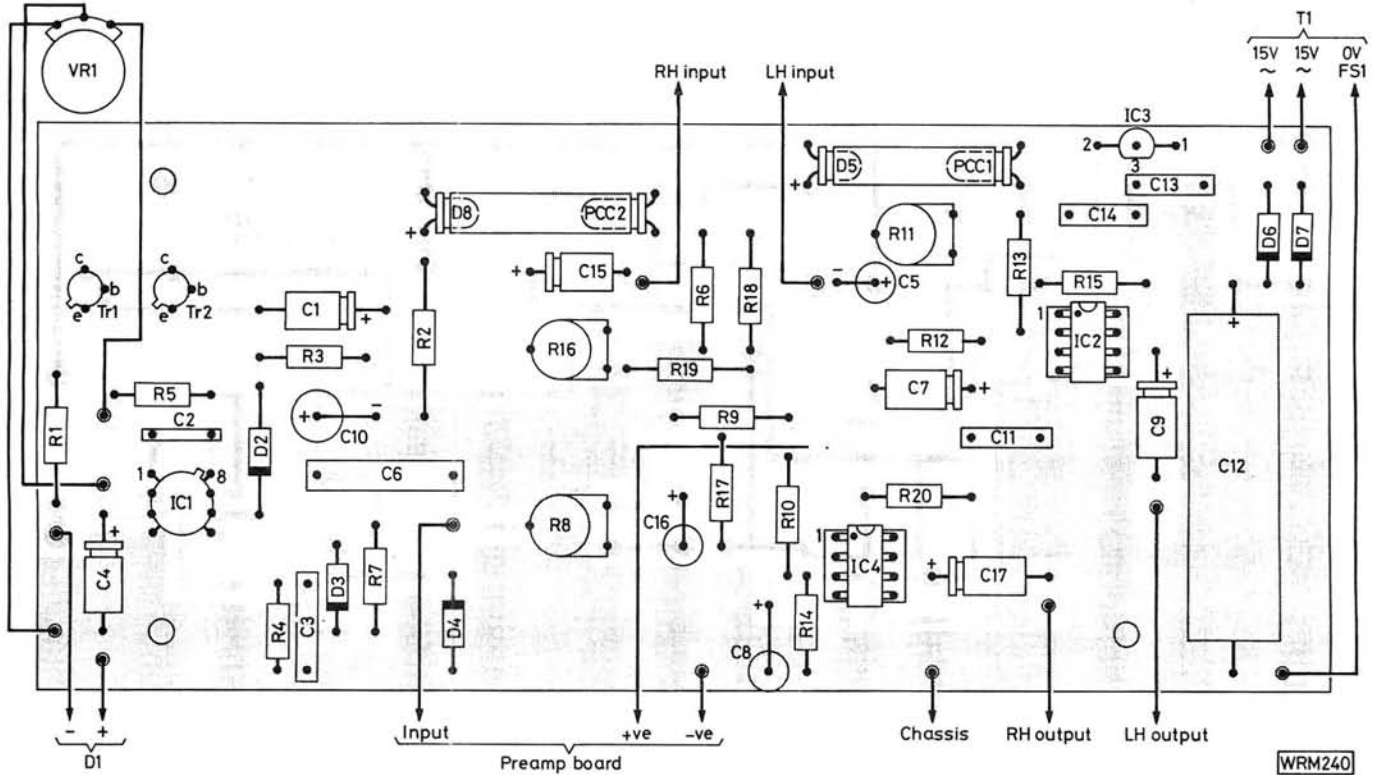
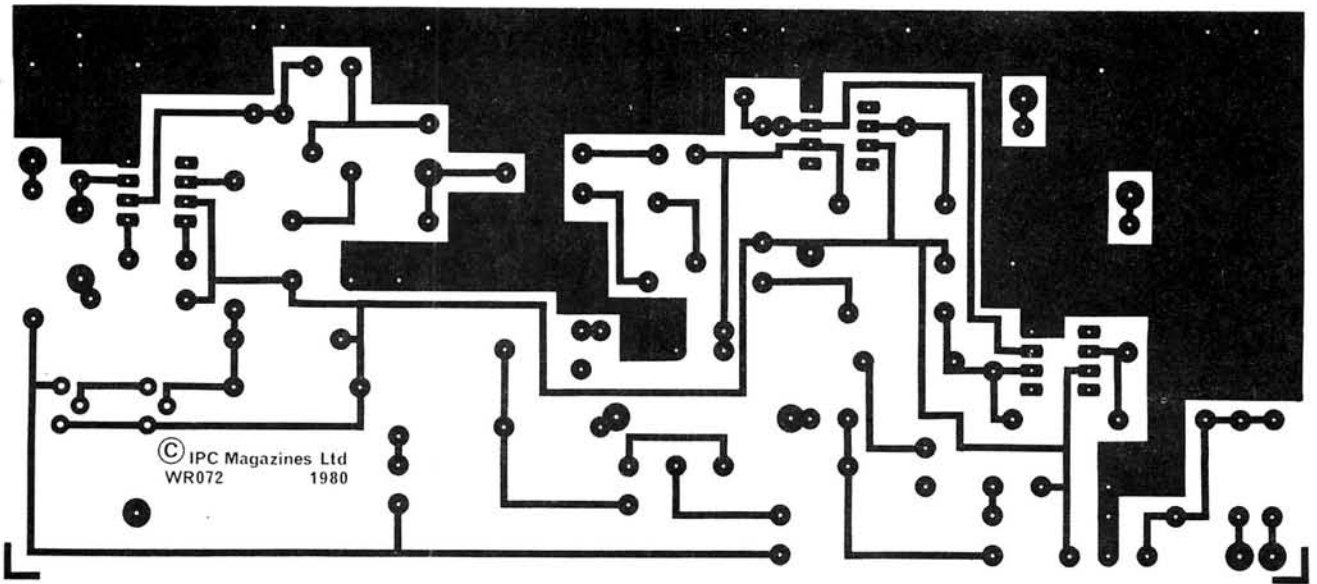


Fig. 3: (Top) copper track pattern shown full size for the main p.c.b.
Fig. 4: (Above) the component placement drawing for the main board

Level Detector

Some of the input from the microphone preamplifier is coupled via R8, R9 and C7 into the left hand channel, and IC2 acts as a conventional virtual earth mixer to combine this with the music signal. Similarly, some of the microphone signal is mixed into the right hand channel. R8 is adjusted for the correct channel balance of the microphone signal.

The rest of the microphone signal is coupled by C6 and R7 to the rectifier and smoothing network which consists of D3, D4, R4 and C3. This circuit has a fast attack time since C3 will quickly charge to virtually the peak signal level through the relatively low impedance path of R7 and

D3. The much slower decay time is obtained as the only significant discharge path for C3 is through the quite high resistance of R4.

IC1 forms the basis of the level detector, and this is used as a comparator. Under quiescent conditions the inverting input of IC1 is at earth potential, and the voltage fed to the non-inverting input produces a fully positive output. A microphone signal takes the inverting input positive, and if it goes more positive than the non-inverting input the output goes almost down to the negative supply rail voltage. VR1 controls the voltage fed to the non-inverting input, and therefore sets the threshold level which the microphone signal must exceed in order to initiate the fading action.

★ components

Resistors

$\frac{1}{4}$ W 5% carbon

680 Ω	3	R1,2,6
10k Ω	2	R10,14
15k Ω	1	R7
18k Ω	1	R5
47k Ω	4	R9,13,17,18
100k Ω	2	R15,20
220k Ω	2	R12,19
470k Ω	1	R3
2.2M Ω	1	R4

Potentiometers

Min. horizontal preset

100k Ω	1	R8
4.7M Ω	2	R11,16

$\frac{1}{4}$ inch shaft

10k Ω lin.	1	VR1
-------------------	---	-----

Capacitors

Electrolytic

1 μ F 63V	4	C5,7,15,16
4.7 μ F 63V	5	C1,4,8,9,17
100 μ F 25V	1	C10
1000 μ F 25V	1	C12

Polyester

100nF	4	C3,11,13,14
330nF	1	C6

Ceramic Plate

22pF	1	C2
------	---	----

Semiconductors

Diodes

TIL220	3	D1,5,8
IN4148	1	D2
OA91	2	D3,4
IN4001	2	D6,7

Transistors

BC108	2	Tr1,2
-------	---	-------

Integrated Circuits

CA3130T	1	IC1
TL081CP	2	IC2,4
78L15	1	IC3

Photocells

ORP60	2	PCC1,2
-------	---	--------

Switches

Rotary Mains	1	S1
--------------	---	----

Miscellaneous

Instrument Case 230 x 152 x 76mm (Harrison Bros. Type HB1); Printed circuit board; Mains Transformer 15-0-15V 200mA (T1); 20mm chassis mounting fuseholder; 20mm 250mA fuse (FS1); Mains Panel neon indicator (LP1); Double phono sockets (2); Control knobs (3).

MICROPHONE PREAMPLIFIER

Resistors

$\frac{1}{4}$ W 5%

3.9k Ω	1	R24
12k Ω	2	R22,25
18k Ω	2	R23,26
68k Ω	1	R21
120k Ω	1	R28
150k Ω	1	R27
1.8M Ω	1	R29

Potentiometers

47k Ω log.	1	VR2
-------------------	---	-----

Capacitors

Electrolytic

10 μ F 25V	4	C19,21,23
100 μ F 25V	3	C18,22,24,26

Polyester

100nF	1	C25
-------	---	-----

Ceramic Plate

2.2nF	1	C20
-------	---	-----

Semiconductors

Transistors

BC109C	1	Tr3
--------	---	-----

Integrated Circuits

TL081CP	1	IC5
---------	---	-----

Miscellaneous

Printed circuit board; 3.5mm jack socket (SK5).



The completed stereo automatic fader unit

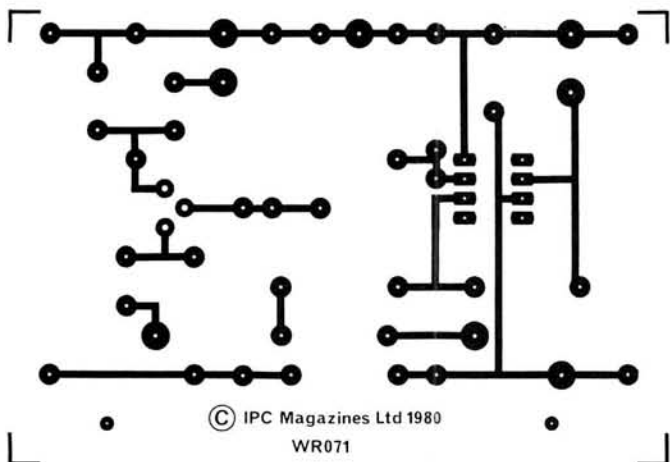
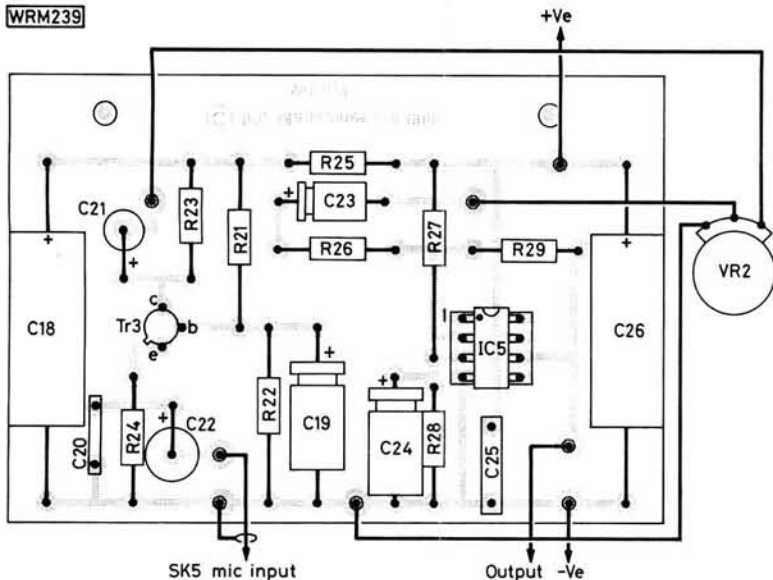


Fig. 5: (Top) the component placement drawing for the microphone preamplifier p.c.b. Fig. 6: (Above) the copper track pattern shown full size for the preamplifier board

Power for the unit is obtained from a simple mains power supply which feeds a 15 volt monolithic voltage regulator device (IC3).

Microphone Preamplifier

The circuit of Fig. 7 requires the music signals and the microphone signal to be at approximately equal levels, and since the music signals will presumably be at a few hundred millivolts r.m.s., a high gain amplifier must obviously be used ahead of the microphone. Fig. 3 shows the circuit diagram of the preamplifier used in the prototype, and this works well with 200Ω and 600Ω dynamic microphones. It should also give good results with electret types having a low impedance output, but other types of microphone will require a different preamplifier to be fitted.

A conventional common base stage is used at the input of the amplifier, and this gives the necessary low input impedance together with a reasonably high voltage gain. Good noise performance is obtained by using a low noise device run at a collector current of only about 500μA in

the Tr3 position. Breakthrough of r.f. is often a problem with high gain microphone pre-amplifiers, and C20 is included at the input to act as an r.f. filter.

The output from Tr3 is coupled to a further stage of amplification via C21 and the gain control, VR2. This final stage uses IC5 in a standard operational amplifier inverting mode, and it gives a voltage gain of 40dB. Texas b.i.f.e.t. devices are used for IC5 as well as IC2 and IC4 as the audio performance of these devices is superior to the standard 741C.

With VR2 at maximum gain the preamplifier needs an input of only about 200μV for 1V r.m.s. at the output.

Construction

It is advisable to house the unit in a metal case which should be earthed via a 3-core mains lead. The general layout of the unit can be seen from the photographs and is not especially critical, although the mains wiring should be kept as far away from sensitive audio wiring as possible.

Most of the circuitry is assembled on a printed circuit board and this is shown in Fig. 4. The opto-isolators are made by taping each l.e.d. to its associated photocell, the two being placed end to end and as close together as possible. As the two are of the same diameter this is quite easily done, and apart from keeping the two components in the correct relative positions it will also exclude extraneous light which could otherwise prevent the unit from working if the lid of the case was removed, or when testing the board prior to installing it in the case.

The preamplifier is constructed on a separate printed circuit board, and details of this are given in Fig. 5. A screened lead should be used to connect the microphone socket to the preamplifier board, but it is not essential for any other connecting wires to be screened.

continued on page 51 ▶▶▶

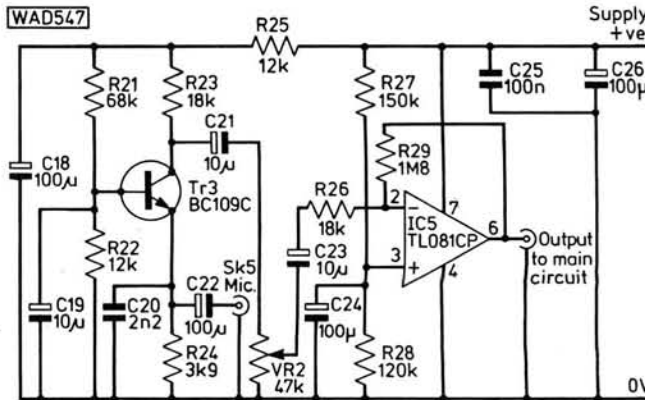


Fig. 7: Circuit diagram of the microphone preamplifier



QUARTZ CRYSTALS FOR THE NIMBUS (EX STOCK) OR FOR ANY OTHER PROJECT

2 METRE STOCK CRYSTALS. Price £1.83 for one crystal. £1.74/crystal when two or more purchased.

	HC6/U 30pF TX	HC6/U 30pF TX	HC25/U 30pF and 40pF TX	HC25/U 20pF and 20pF RX	HC25/U 25pF and 20pF TX	HC6 & 25/U SR RX
R0	4.0277	8.0555	12.0833	14.9888	18.1250	44.9666
R1	4.0284	8.0569	12.0854	14.9916	18.1281	44.9750
R2	4.0291	8.0583	12.0875	14.9944	18.1312	44.9833
R3	4.0298	8.0597	12.0895	14.9972	18.1343	44.9916
R4	4.0305	8.0611	12.0916	15.0000	18.1375	45.0000
R5	4.0312	8.0625	12.0937	15.0027	18.1406	45.0083
R6	4.0319	8.0638	12.0958	15.0055	18.1437	45.0166
R7	4.0326	8.0652	12.0979	15.0083	18.1468	45.0250
S8	—	—	12.1000	14.9444	18.1500	44.8333*
S9	—	—	12.1020	14.9472	18.1531	44.8416*
S10	—	—	12.1041	14.9500	18.1562	44.8500*
S11	—	—	12.1062	14.9527	18.1593	44.8583*
S12	—	—	12.1083	14.9555	18.1625	44.8666*
S13	—	—	12.1104	14.9583	18.1656	44.8750*
S14	—	—	12.1125	14.9611	18.1687	44.8833*
S15	—	—	12.1145	14.9638	18.1718	44.8916*
S16	—	—	12.1167	14.9667	18.1750	44.9000*
S17	—	—	12.1187	14.9694	18.1781	44.9083*
S18	—	—	12.1208	14.9722	18.1812	44.9166*
S19	—	—	12.1229	14.9750	18.1843	44.9250*
S20	4.0416	8.0833	12.1250	14.9777	18.1875	44.9333
S21	4.0423	8.0847	12.1270	14.9805	18.1906	44.9416
S22	4.0430	8.0861	12.1291	14.9833	18.1937	44.9500
S23	4.0437	8.0875	12.1312	14.9861	18.1968	44.9583

SR - Series Resonance *HC25 only

Also in stock: R0 to R7 for FT221 R0 to R7 and S8 to S23 for following: Belcom FS1007, FDK TM56, Multi 11 Quartz 16 and Multi 7, Icom IC2F, 21, 22A and 215, Ito Kenwood 2200, 7200, Uniden 2030 and Yaesu FT2FB, FT2 Auto, FT224, FT223 and FT202.

Also in stock: 4 and 8MHz TX in HC6/U for 145.8MHz. Icom crystals TX for 145.6MHz (RRO). 44MHz RX crystals in HC6 for 145.8 and 145 (RRO) and 145.475MHz (S19). All at above price.

4 METRE CRYSTALS for 70.26MHz in HC6/U at £2.25. TX 8.78250MHz. RX 6.7466 or 29.78MHz in stock.

70cm CRYSTALS in stock 8.0222 and 12.0333 in HC6 £1.85. Pye Pocketfone PF1, PF2, PF70 and Wood and Douglas £4.50 a pair or TX £2.25, RX £2.50, SUB(433.2) RBO, RB2, RB4, RB6, RB10, RB11, RB13 and RB14.

CONVERTER CRYSTALS in HC18/U at £2.85. In stock 38.666, 42.000, 70.000, 96.000, 101.000, 101.500, 105.666 and 116.000MHz.

tone BURST AND I.F. CRYSTALS in HC18/U at £2.25 in stock. 7.168MHz for 1750kHz and 10.245MHz for 10.7MHz I.F.s.

FREQUENCY STANDARDS in stock £2.75, HC6 200kHz, 455kHz, 1000kHz, 5.000MHz and 10.000MHz. HC13 100kHz, HC18 1000kHz, 7.000MHz, 10.700MHz, 48.000MHz and 100.000MHz.

PRICES ARE EX VAT. PLEASE ADD 15%.

MADE TO ORDER CRYSTALS SINGLE UNIT PRICING

Fundamentals	Price Group	Adjustment Tolerance ppm	Frequency Ranges	Price and Delivery	
				A	B
	1	200 (total)	10 to 19.999 kHz	—	£23.00
	2	200 (total)	20 to 29.999 kHz	—	£16.50
	3	200 (total)	30 to 99.999 kHz	—	£10.50
	4	200 (total)	100 to 999.999 kHz	—	£6.00
	5	50	1.00 to 1.499 MHz	£9.00	£6.00
	6	10	1.50 to 1.999 MHz	£4.75	£4.20
	7	10	2.00 to 2.999 MHz	£4.75	£4.00
	8	10	2.80 to 3.999 MHz	£4.55	£3.70
	9	10	4.00 to 20.999 MHz	£4.55	£3.60
	10	10	21.00 to 24.000 MHz	£6.00	£5.40
3rd OVT	11	10	21.00 to 59.999 MHz	£4.55	£3.60
5th OVT	12	10	60.00 to 99.999 MHz	£5.00	£4.00
	13	10	100.00 to 124.999 MHz	£6.15	£5.20
5th, 7th & 9th OVT	14	20	125.00 to 149.999 MHz	—	£6.00
	15	20	150.00 to 225.000 MHz	—	£7.50

Unless otherwise requested fundamentals will be supplied with 30pF load capacity and overtones for series resonance operation.

HOLDERS - Please specify when ordering - 10 to 200kHz HC13/U, 170kHz to 170MHz HC6 or HC33/U, 4 to 225MHz, HC18 and HC25.

DELIVERY. Column A 3 to 4 weeks, Column B 6 to 8 weeks.

DISCOUNTS. 5% mixed frequency discount for 5 or more crystals at B delivery. Price on application for 10 or more crystals to same frequency specification. Special rates for bulk purchase schemes including FREE supply of crystals used in UK repeaters.

EMERGENCY SERVICE SURCHARGES (to be added to A delivery prices). 4 working days £8, 5 working days £6, 6 working days £4, 13 working days £3 (maximum of 5 crystals on 4 day delivery).

CRYSTAL SOCKETS HC6/U and HC25/U 16p.

MINIMUM ORDER CHARGE £1.50.

COMMERCIAL USERS. Crystals can be supplied for MPU, industrial control, etc. in the range 4-21MHz fundamental and 3rd OVT 18 to 60MHz at £1.15 for 100 off. This is only a limited example of our capabilities. Please enquire about other quantities, frequency ranges, watch and sub-carrier crystals. We can supply crystals for marine and land mobile radio telephone use. Send for details.

TERMS. Cash with order, cheques and postal orders payable to QSL Ltd. All prices include postage to UK and Irish addresses. Please note Southern Irish cheques and postal orders are no longer acceptable. Please send bank draft in pounds Sterling.

OVERSEAS DISTRIBUTORS

West Germany, Austria and Benelux countries - SSB Electronic, Karl Arnold Str. 23, 5860 Iserlohn, West Germany.

Denmark - Asbjorn Jorgensen, Aabrinken 1, Tapdrup, DK806, Viborg, Denmark.

Portugal - Sorubal SARL, Rua General Fimanta de Castro, 15-81, Lisboa 5, Portugal.

(Enquiries invited from companies in other countries.)

QuartzLab

(Dept. C) MARKETING LTD. P.O. BOX 73 SUMMIT HOUSE, LONDON SE18 3LR
Telephone: 01-690 4889 24hr Ansafone: Erith (03224) 30830
Telex: 912881 CWUKTX-G (Attention QUARTSLAB). Cables: QUARTSLAB LONDON SE18

The NEW Marshall's 79/80 catalogue is just full of components

and that's not all . . .

. . . our new catalogue is bigger and better than ever. Within its 60 pages are details and prices of the complete range of components and accessories available from Marshall's.

These include Audio Amps, Connectors, Boxes, Cases, Bridge Rectifiers, Cables, Capacitors, Crystals, Diacs, Diodes, Displays, Heatsinks, I.Cs, Knobs, LEDs, Multimeters, Plugs, Sockets, Pots, Publications, Relays, Resistors, Soldering Equipment, Thyristors, Transistors, Transformers, Voltage Regulators, etc., etc.

Plus details of the NEW Marshall's 'budget' Credit Card. We are the first UK component retailer to offer our customers our own credit card facility.

Plus - Twin postage paid order forms to facilitate speedy ordering.

Plus - Many new products and data.

Plus 100s of prices cut on our popular lines including I.Cs, Transistors, Resistors and many more.

If you need components you need the new Marshall's Catalogue.

Available by post 65p post paid from **Marshall's, Kingsgate House, Kingsgate Place, London NW6 4TA**. Also available from any branch to callers 50p.




Retail Sales: London: 40 Cricklewood Broadway, NW2 3ET. Tel: 01-452 0161/2. Also 325 Edgware Road, W2. Tel: 01-723 4242. Glasgow: 85 West Regent Street, G2 2QD. Tel: 041-332 4133. And Bristol: 108A Stokes Croft, Bristol. Tel: 0272 426801/2.

Model Radio Control

Part 5

THE PW FM-80 SYSTEM

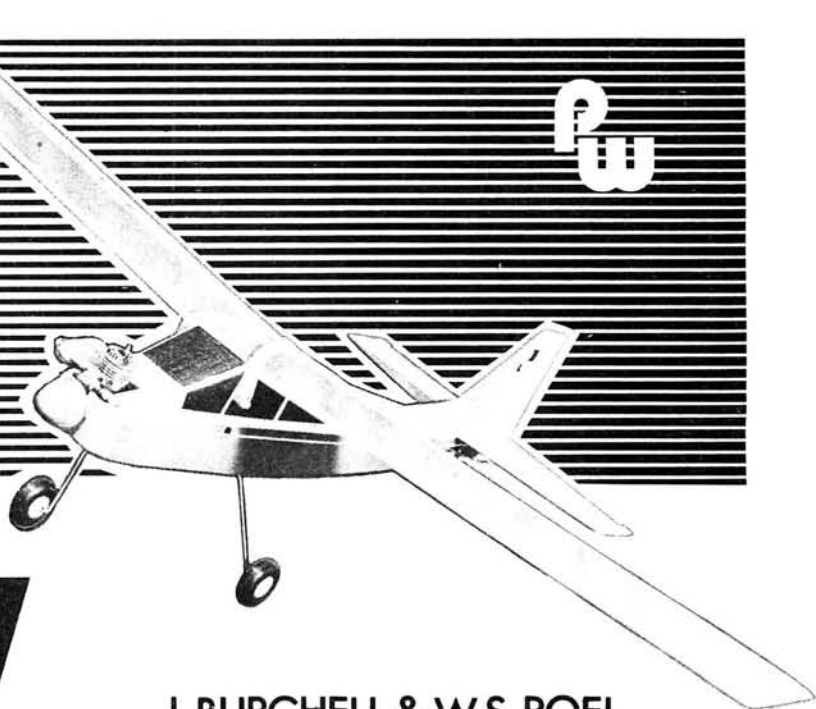


J. BURCHELL & W.S. POEL

The choice of a suitable model for radio control purposes is not so simple as most people imagine. The person attracted to radio control modelling for the first time imagines himself at the controls of a scale Spitfire performing aerobatics in the sky above his head. Unfortunately for him a lot of training on simpler models is needed before he can even think of flying such exotic models.


The beginner was kept very much in mind when designing the PW FM-80 system and in this article the installation of the system in a suitable training aircraft will be described. The boat and car enthusiasts have not been forgotten however, and simple installation hints are given for an electric powered boat and car.

Mini-Escort

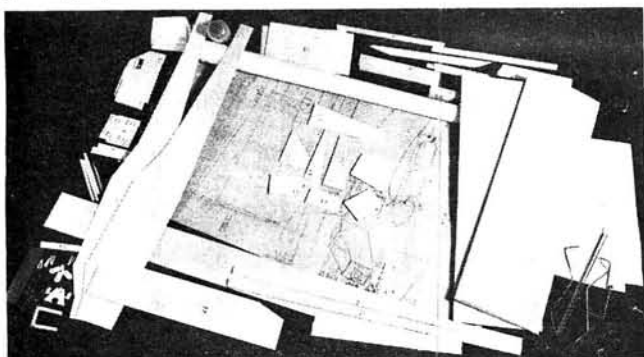The aircraft chosen to illustrate the FM-80 system is the Mini-Escort produced in kit form by Cloud Models. This is probably the least expensive model to get into the air and proved to be very simple to build, the fuselage being made from pre-cut balsa sheet and the wings from veneer covered plastic foam. No problems were encountered in putting together the model shown in the photographs.




Some hints on the installation of the radio gear are given in the instructions provided with the kit. For our model we installed the NiCad battery pack in the front fuel tank bay ensuring that it was very firmly fastened in place and could not break loose in the likely event of a heavy landing. The picture shows the installation of the receiver and two servo units. The receiver would normally be packed in soft foam to absorb vibration from the engine and cushion the unit against landing shocks. Like the battery pack the receiver should not be free to wander around

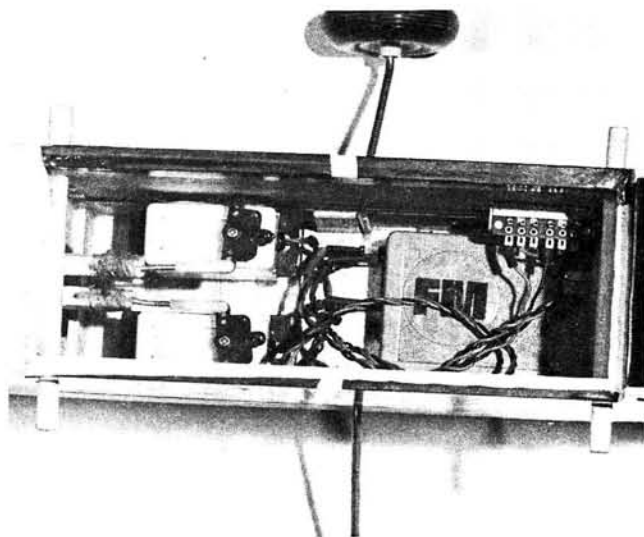

The servos operating the elevator and rudder are mounted at the rear of the cabin space using double-sided adhesive foam tape. The FM-80 receiver is positioned ahead of the servos and should, of course, be wrapped with foam rubber.

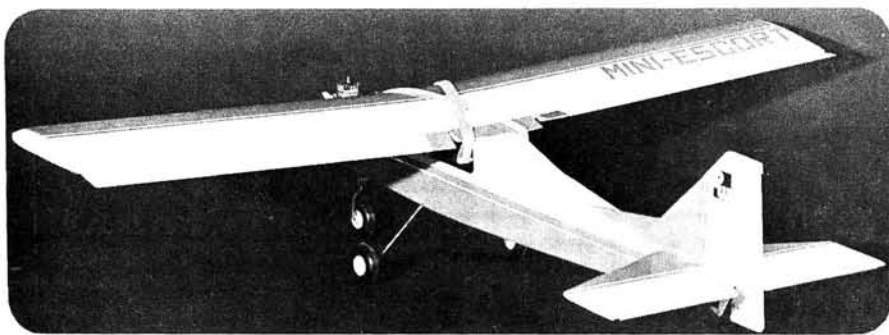The kit for the Mini-Escort trainer is shown on the left and proved very easy to build




The aileron version of the Mini-Escort trainer. The wing is interchangeable with the plain version and can be built later. The engine fitted to our model is a Flash 15 R/C glow-plug which suits the Mini-Escort perfectly

The Caribbean Coaster tramp steamer makes an ideal model for the newcomer to radio controlled boats

the aircraft. The two servos shown operate the elevator and rudder by pushrods made up from soft balsa strip supplied with the kit. The clevises and threaded wire from which the push-rod ends are made are also supplied in the kit.

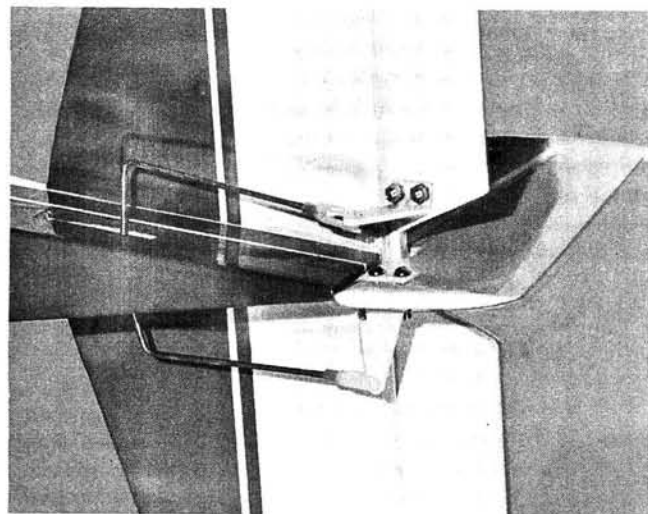The servos can be mounted in a number of different ways. Micron make special servo mounting clips which allow you to remove servos easily. This is important if you have a number of models but only a limited number of servos. We took the easy way out and used a double-sided self-adhesive rubber tape, sold by model shops especially



The push-rods are attached to the control surfaces by plastic clevises. Careful fitting is essential to give smooth frictionless movement

for fixing servos. This allows the servos to be positioned easily without the need for very accurate placing of servo mounts or wooden bearers, but does have the disadvantage of making it difficult to remove the servos from the model.


Care must be taken to ensure that the control surfaces and linkages operate smoothly with the minimum of effort. Failure to achieve this will certainly impose extra loads on the servos resulting in poor control of the model.

At a later date it is intended to fit a third servo for motor control and this will have to be fitted in such a position as to avoid the receiver and yet allow the control push-rod to pass easily through the fuel tank bay into the engine compartment.

The on-off switch is fitted in the fuselage side and if desired can be wired in such a way as to allow the battery pack to be charged via an SLM charger socket also mounted in the fuselage side.

Insurance

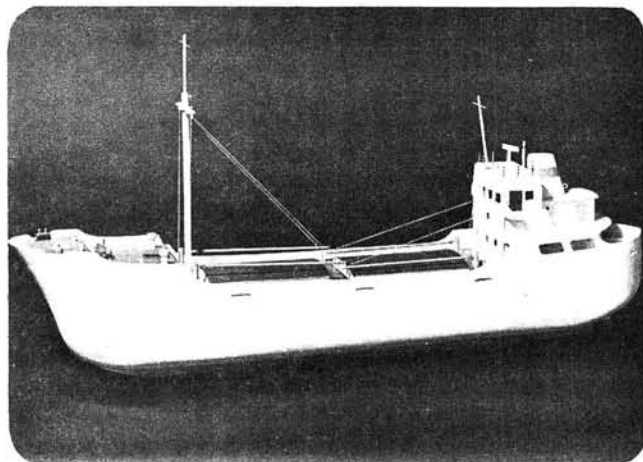
Before you launch your model into the blue sky please ensure that you are adequately insured. Even a simple trainer can wreak expensive havoc if anything goes wrong.




Caribbean Coaster

A model boat might seem to be a much simpler proposition than an aircraft but this is not necessarily the case. After all most aircraft come nowhere near water, and water, especially salt water, is the arch-enemy of anything electronic. So the first requisite when planning the installation of your FM-80 system into a boat is to ensure that it will remain dry.

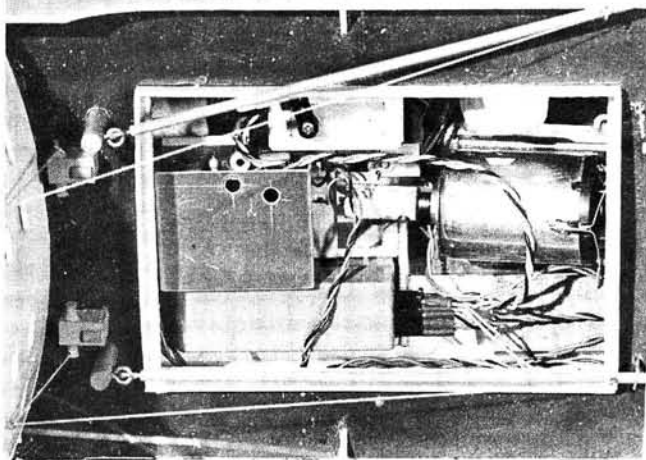We fitted our FM-80 into a Veron Caribbean Coaster using one servo unit for the rudder and the electronic speed controller for motor control. The receiver, servo and speed controller were all mounted in the aft cargo hold along with the motor and propellor shaft. Suitable plywood compartments were fabricated to hold the



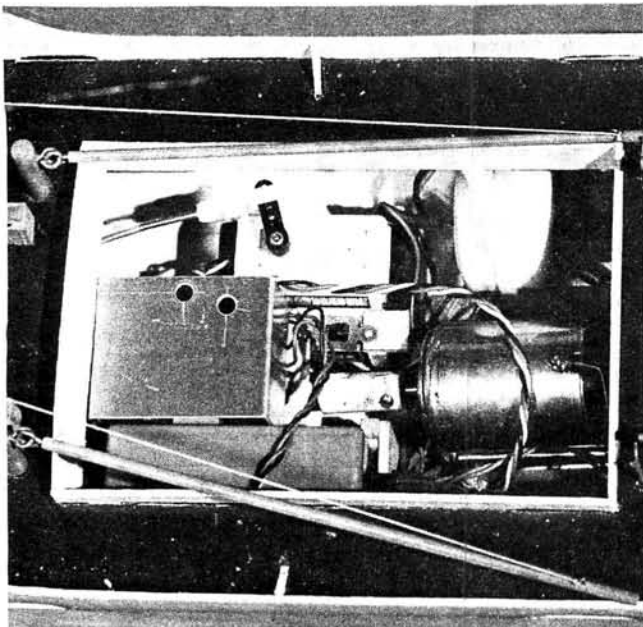The speed controller and FM-80 receiver are simply mounted in plywood boxes in the aft hold of the Caribbean Coaster




The servo used to operate the rudder is also mounted in a simple close-fitting ply box. Care must be taken to ensure smooth operation of the rudder assembly. The NiCad battery pack is fitted into a self-adhesive cable-tie attached to the side of the hold

receiver and the servo, and the speed controller was attached to a plywood cover over the propellor shaft by servo-tape.

The propulsion batteries were housed in the forward hold while the radio battery pack was held in a large cable tie attached to the hull side in the aft hold.

The model aerial, rigged in wire between the two masts, was actually used as the aerial for the receiver and this functioned very well in spite of its short length.

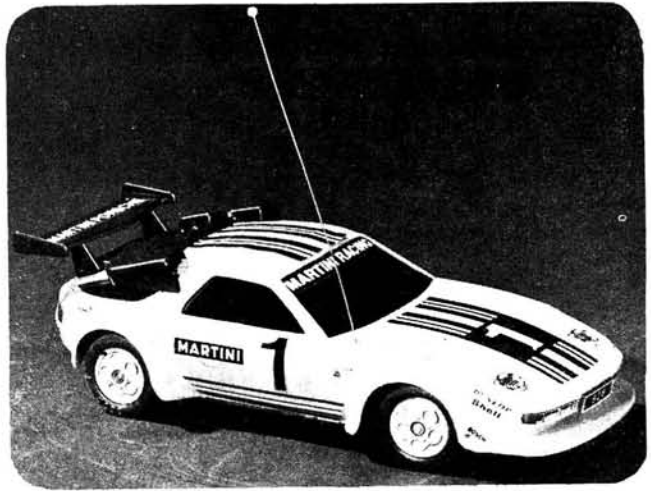


Porsche 928

The model car used was one of the cheap oriental imports which seem to have been popular as Christmas presents. The original crude radio system was removed to leave the basic model car with motor and servo mechanics for the steering.

A basic FM-80 servo amplifier is used to drive the steering motor with the feedback being obtained from the original potentiometer fitted to the steering unit.

The main motor is controlled by a speed controller unit which together with the receiver is mounted in place of the original radio equipment. The battery compartment is used to house the batteries which can be dry cells as originally intended or, with suitable modifications to the battery compartment, NiCads.

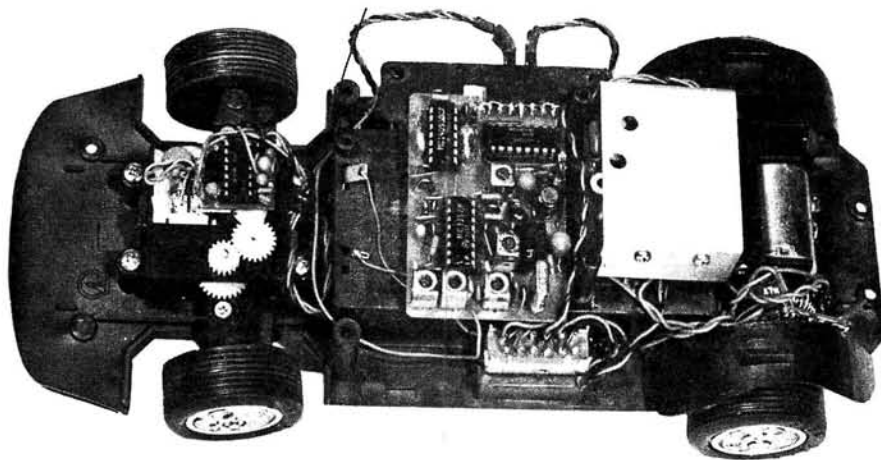The next part of this series will describe a NiCad battery charger and servo tester.



The FM-80 system is a tight fit inside the "Oriental" Porsche. The receiver is used without its plastic case and could also be arranged without the seven way output socket. Both the receiver and speed controller are secured with "servo tape" to the floor of the model. The FM-80 servo amplifier is used in conjunction with the original steering motor and feedback pot. NiCad battery packs can be fitted if desired in the built-in battery compartments

The Mini-Escort trainer was supplied by Galaxy Models, 88 Catton Grove Road, Norwich NR3 3AA; The Flash 15 motor came from Neway Models, The Walnuts, The Street, Rickingham, Diss, Norfolk; The Veron Caribbean Coaster was loaned by Mrs Marion Cottle; The Oriental Porsche came from Ambit International but could be by courtesy of Father Christmas

FM-80 Receiver

An error occurred in the component placement drawing of the receiver p.c.b., T3 was shown turned through 180°. This will prevent the local oscillator from working. T3 must therefore be turned round and an extra hole drilled in the board to take the centre tap connection. Alternatively this centre tap pin can be cut off.

A licence is required to operate radio control equipment. This costs £2.80 for five years. Application forms are available from: The Home Office, Radio Regulatory Dept., Waterloo Bridge House, Waterloo Road, London SE1 8UA

ON SALE 3RD. APRIL

NEXT MONTH IN...

practical WIRELESS

practical WIRELESS

MAY 1980

COMPONENT CALCULATOR


DATACARD

This nomograph simplifies the calculation of parallel resistors. Place a straight edge between point A on the left hand scale at a value corresponding to the value of the first resistor. The line crosses the right hand scale at a value corresponding to the combined value of the two resistors.

FREE INSIDE

The second in our series of useful reference cards, this Component Calculator enables you to work out parallel resistors and series capacitors. A handy nomograph simplifies power calculations for d.c. circuits. Other subjects covered are multipliers and the ubiquitous formula wheel

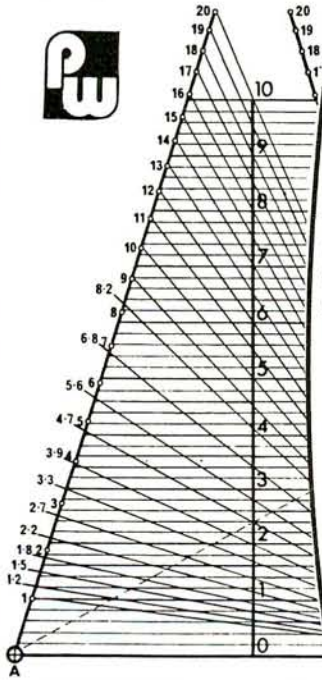For values of resistor it may be necessary to divide both values by a factor in order to bring them on to the scales. For example, 180000Ω (180kΩ) may be divided by 100 to give 1800Ω and 68Ω may be divided by 10 to give 6.8Ω. Combined value of resistors is 2.8kΩ.



A Reproduction Vintage Radio Set

The answer to our readers who are always clamouring for the return of valves. *PW* presents a real valve project which will go well with your lace tablecloth and vintage aspidistra. Your granny will be delighted with this authentic reproduction

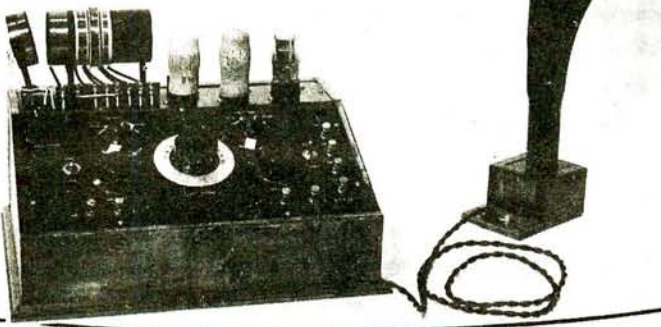


Diagram showing three values

100 SECOND PHOTOGRAPHIC CLOCK

Accurate timing is essential in photography if consistently good results are to be achieved. The circuit of a two-digit seconds counter will be described using red l.e.d. display devices with reset and brightness controls



dual trace unit

for the
PURBECK

Ian HICKMAN

Part 3

Using the Dual Trace Unit

You will of course already have used each of the two Y channels separately during the course of setting up and calibrating the instrument. Now we wish to familiarise ourselves with dual trace working in particular. As a start select as trigger source Y1 HF REJ, alternate mode, and set the Purbeck time-base controls to 5ms/div. Connect both Y inputs of the Dual Trace Unit (using two 10:1 probes if available) to the CAL output of the Purbeck. With suitable settings of the Y1 and Y2 input attenuators, VAR GAIN and SHIFT controls, two traces will appear alternately, each showing the approximately square 50Hz CAL waveform. As the repetition rate of the timebase will be 16.67Hz (each trace shows $2\frac{1}{2}$ cycles and therefore the timebase will retrigger every third cycle) each of the two traces will be repeated 8.33 times a second. This results in pronounced flicker, which will still be noticed but to a lesser extent when the time-base speed is set to 2ms/div. Now however, change the mode switch from ALT to CHOP, and the flicker will disappear. This is because instead of writing the two traces alternately the electron beam in the cathode ray tube is now writing part of one trace for 5 μ s. (about one four-hundredth of a horizontal division!) and then the other trace for the next 5 μ s. and so on.

So far so good, but of course it is rather a waste of a Dual Trace Unit to display one waveform twice over. So now let's examine two different waveforms. However, a moments reflection will make it clear that they must be of the same frequency, or an exact multiple. Otherwise, if we trigger from one, the other will "run through" unsynchronised, and vice versa. An a.f. oscillator with both sine and square-wave outputs makes a handy source, and if you don't possess one, the circuit of Fig. 16 will provide both, plus a triangular wave to boot (the 'sine wave' is an approximation with 3 $\frac{1}{2}$ % total harmonic distortion). Even simpler, use a low voltage secondary on a mains transformer to give you a 50Hz sine wave, and use the Purbeck CAL waveform for your squarewave. You will see that these are in phase (or antiphase according to which way round your secondary is connected), whereas the

squarewave of the circuit of Fig. 16 is in "quadrature" (displaced one quarter of a cycle) to the triangular wave, and in antiphase to the sine-wave.

With input waveforms of a few kHz and higher, the "granular" effect of the traces in the chopped mode may be visible. In fact frequencies up to the chopping frequency or even higher can be displayed in the chopped mode, but the display may be unsatisfactory due to a stroboscopic effect. If the input frequency is carefully adjusted, the waveform can be seen to be traced out in dashes—the missing bits corresponding to the dashes where the other trace is being drawn. The sudden transitions of the beam between traces can also just be seen with care, but are not normally noticeable as they are so fast. On early double trace scopes in the CHOP mode, these transitions were not fast enough to be invisible, and blanking pulses were therefore fed to the cathode ray tube grid or cathode to dim the trace during the transitions. However the switching speed of the BSV81 f.e.t.s used in the Dual Trace Unit is so high as to render this unnecessary.


So far we have used the unit mainly in the CHOP mode, which is most suitable for lower frequencies—say from a few kHz down (though it can also often be used at frequencies in the MHz range). When displaying low frequencies in the CHOP mode, it is best if the trig. selector is at HF REJ, whether Y1 or Y2 channel is used as a trigger source. This is because the chopping action could possibly superimpose spikes at the chopping rate on the outputs of the 733 amplifiers, albeit of very small amplitude. The HF REJ facility prevents these entering the trigger pick-off amplifier, thus they cannot interfere with the trigger function. If the HF REJ is not selected when in CHOP mode, then at low frequencies the trace may trigger on either the positive or the negative going slope of the waveform, whilst at higher frequencies the trace may tend to synchronise to the chopping frequency.

Having demonstrated both the Alternate and the Chopped modes with different waveforms of the same frequency, let's move on to something more meaty—a $\div 10$ counter. This demonstrates better the diagnostic value of the two traces, and also illustrates how it pays to give some


The set of traces shown on this page were all photographed from the screen of the author's

prototype Purbeck oscilloscope. The inputs to the PW Dual Trace Unit were via commercial 10:1

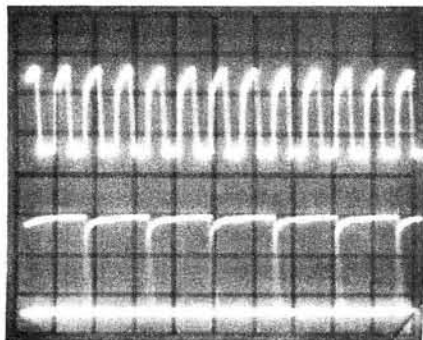
passive probe units which had been adjusted to suit the inputs of the Dual Trace Unit



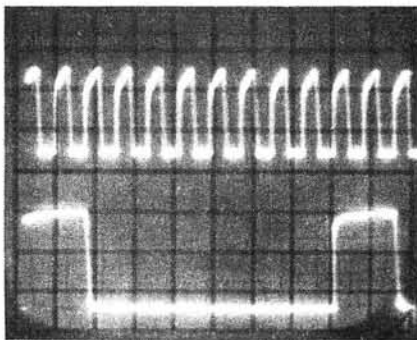
Photograph 1: This picture shows, at the top, the input to a 7400 series TTL decade divider. In this instance the Purbeck was being triggered from the divider input (upper trace) and as the timebase is set to display 13 pulses on the input trace the output trace (lower) will try to display 1.3 pulses. This accounts for the multiple and overlapping pulses on the lower trace



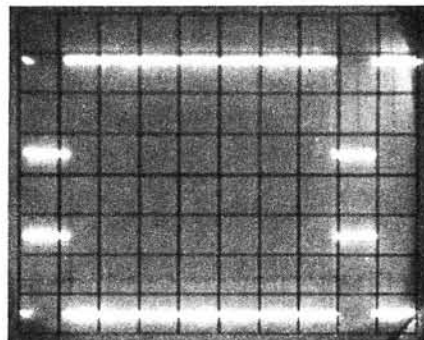
Photograph 2: Here we have the same basic information being displayed as in Photograph 1. However the oscilloscope is now being triggered from the lower trace with the result that both the input and output pulse trains are now displayed correctly on the screen and can be studied and measured without difficulty



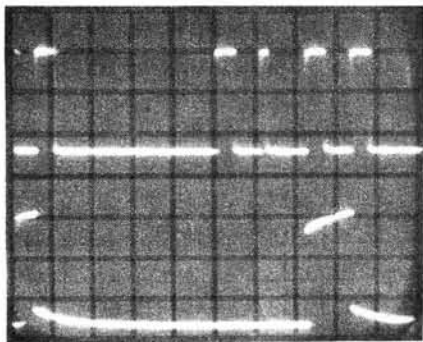
Photograph 3: This photograph shows how a twin beam oscilloscope can be used to indicate the differences between two pulse trains. The two traces shown are taken from the input and output pins of a TTL inverter and the display shows very clearly that when one trace is at 0V the other is at +5V. (Each trace is set to show 0V as its lower level and +5V at its higher position;



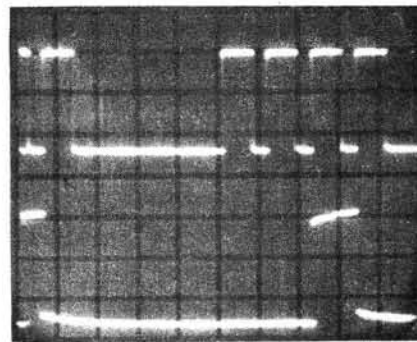
Photograph 4: A dual trace oscilloscope is extremely useful when dealing with digital proportional radio control equipment such as the advanced PW FM-80 system currently being described in these pages. This photograph, along with the next four show the outputs of the FM-80 encoder circuitry contained in the transmitter.



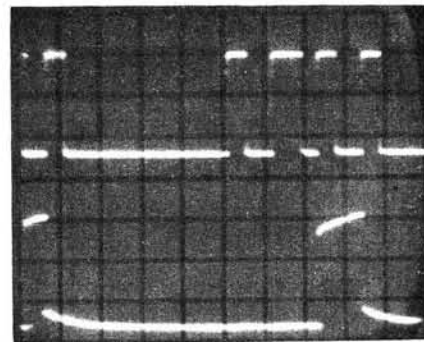
Photograph 5: The preceding photograph showed the FM-80 encoder output with Channel 2 set to 1.0ms pulse width (equivalent to full left at the servo output). This picture shows the same set up but with all channels set to 2.0ms pulse width (all servos full right). In these photos the lower trace is used as the triggering input, and is looking at the reset



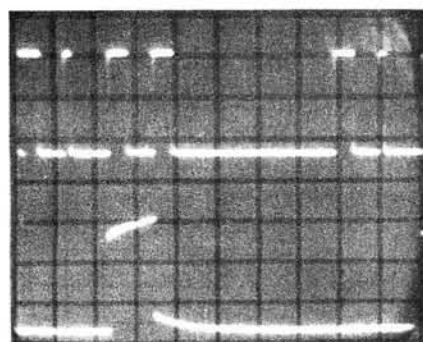
Photograph 6: Here we have Channel 2 set to 2.0ms (full right at the servo arm). The encoder can be set up so that with the control stick centred the pulse width for that particular channel is 1.5ms and with the stick at each end of its travel the pulse width changes from 1.0ms to 2.0ms. Comparing this picture with Photograph 9 the differences in operation of the FM-80 encoder can be seen



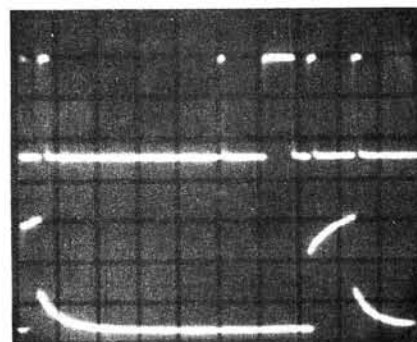Photograph 7: This is basically the same display as Photograph 4 but the triggering arrangements are slightly different. In Photograph 4 the scope is triggered from the lower trace on the positive going edge. This picture has the traces triggered from the upper trace. The Dual Trace Unit was set to CHOP with the HF REJ switched in for all the r.c. trace pictures



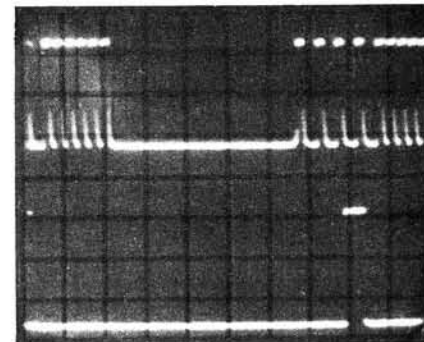Photograph 8: The output of the FM-80 encoder again but this time with all the channels set to 1.0ms except Channel 2 which is set to 2.0ms. From these pictures it will be seen that the Dual Trace Unit adds an extra dimension to the Purbeck oscilloscope enabling the operator to study pulse trains in particular with an ease that is not possible with a single beam



Photograph 9: Here we have the output of a more conventional radio control digital encoder circuit. This one is Micron's PL7-D f.m. system and shows how each channel pulse is formed. Again the Dual Trace Unit is set to CHOP with HF REJ in circuit. The lower trace shows the output associated with Channel 4 reset

Fig. 16: (Right) circuit diagram of a useful waveform generator. This will produce sine, square and triangular waveforms. The three outputs are all at the same frequency, making the circuit useful in checking out the Dual Trace Unit



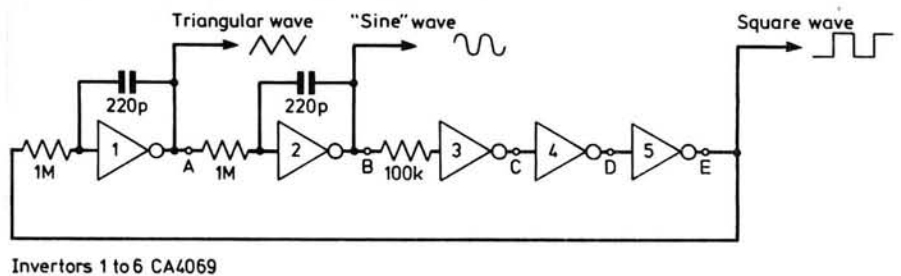
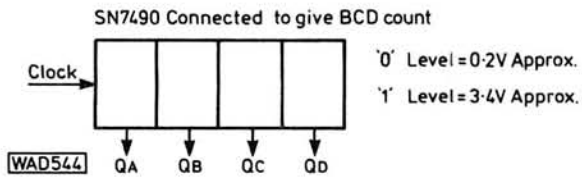


Fig. 17: (Below) the various waveforms of a t.t.l. decade divider of the 7490 type

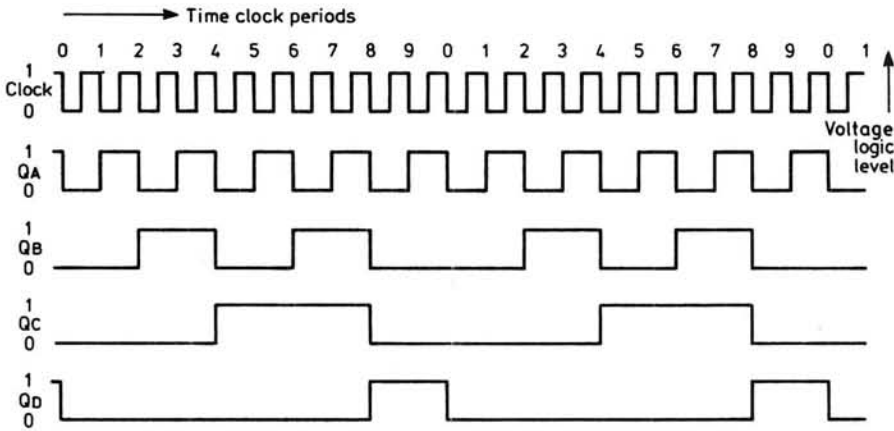

thought as to which channel it is best to trigger from. Fig. 17 gives the waveforms at the outputs of the four stages of a t.t.l. counter type SN7490: these are generally designated QA, QB, QC and QD; the clock waveform is also shown. The photograph shows the Purbeck displaying the clock waveform on the Y1 channel. (top trace) and the output of QD at one tenth the frequency on Y2. The TRIG selector switch of the Dual Trace Unit is set to Y2, ensuring a unique display of the QD waveform. Now switch the TRIG selector to Y1 and you will still have a clean display of the clock waveform, but most likely the Y2 trace will show the QD waveform at several different overlapping positions in the X direction. If however the X timebase variable is adjusted so that the scope retriggers after exactly 10, 20 or 30 clock pulses, a clear display of the divide by 10 QD output will again be obtained—but at the expense of having the timebase uncalibrated. This illustrates the reason for retriggering the oscilloscope from the lower frequency waveform when displaying two waveforms of different frequencies.

The QB waveform is a little more tricky, it can be seen that this spends two clock periods high, then two low, two high again and then four low. Consequently, depending on the clock frequency, it is quite likely you will get a split display when triggering from this waveform. One can always display the QD waveform on the other trace and trigger from that, but if it is particularly desired to display the QB and clock waveforms without having the timebase speed uncalibrated, the dodge is to connect the QD waveform direct to the EXT TRIG input of the Purbeck in place of the trigger output from the Dual Trace Unit. We now effectively have a three channel system, although only two of them are actually being displayed, and of course a single QB waveform will be obtained.

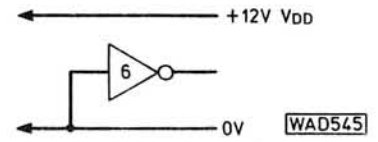

Having tried out all the foregoing, you will now feel much more at home when driving a dual trace oscilloscope. However the following points relating to the Purbeck plus its Dual Trace Unit in particular are well worth noting. Firstly, following the modifications described in Fig. 15, the external trigger facilities of the basic Purbeck oscilloscope now typically meet the following specification.

Divide by 100 input; a minimum of 3V peak-to-peak required for triggering, frequency response down to 10Hz. Maximum input voltage 250V r.m.s. down to 10Hz. Below this frequency, the sum of the peak a.c. voltage plus any d.c. level must not exceed 160V. The input impedance is 180kΩ.

Direct input, a minimum of 30mV peak-to-peak required for triggering, frequency response -3dB at 80Hz. Maximum input voltage 10V a.c. peak-to-peak, any associated d.c. level not to exceed 160V. Input impedance 2kΩ. (Note that at frequencies below about 100Hz, the phase shift associated with the falling amplitude response will result in the TRIG LEVEL control producing triggering over part of the other slope of the input waveform in addition to the slope selected by the TRIG POLARITY switch.)

Secondly, with the Y input controls of the Purbeck set to 100mV/div., the Dual Trace Unit provides exactly the same range of Y input sensitivities as the basic Purbeck. However, by setting the Purbeck Y input to 10mV/div. instead, the sensitivity of the Dual Trace Unit is increased by a factor of 10. (If the Purbeck Y input is d.c. coupled, the traces will probably be driven off screen, but can be returned by adjusting the Y1 and Y2 SHIFT controls on the Dual Trace Unit. However, it is easier simply to set the Purbeck Y input to a.c. coupled, as one is unlikely to want to make d.c. coupled measurements at this sensitivity.)

There will be noticeable thickening of the trace when working at this sensitivity, i.e., 500μV/div., due to the wide bandwidth, but with a x1 probe (a screened lead) and a reasonably low source impedance for the measured waveform, useful measurements can still be made. The trigger facilities in the Dual Trace Unit are sensitive enough to work at 500μV/div., provided the input waveform is large enough to produce 1 division vertical deflection, i.e., is at least 500μV peak-to-peak. In fact, the Purbeck can even be set to 10mV/div., with the variable gain control selected and set at maximum gain, giving a sensitivity at the Dual Trace Unit input of around 100μV/div. Using triggering via the Dual Trace Unit would require 4 or 5 divisions of vertical deflection to lock

continued on page 59

PRODUCTION LINES

alan martin

Latest from Casio

We recently received for review three of the very latest products from Casio.

On the left of our photograph is the MQ-6, a micro-card watch/calculator, which features a watch, stopwatch, calendar and an 8-digit calculator. The MQ-6 measures only 68 x 44 x 5mm thick.

In the centre is the ML-81, which offers the following functions, a clock, calendar, two alarms, timer, stopwatch, 8-digit calculator and a new musical instrument function.

Using the novel music function, the calculator keyboard doubles as the tonic sol-fa plus three octave notes. The timer, alarm 1 and 2 can be selected (when set) to operate a buzzer for 20 seconds or play its own programmed tune for 24 seconds. The three tunes are Frühlingslied, Träumerei and Moments Musicaux No. 3.


Finally, on the right is the F-80, an alarm chronograph. The regular timekeeping function has two optional displays; hour/minute/day/date or hour/minute/second/date.

Also featured is a three mode stopwatch, alarm and time-signal facility.

The F-80 is powered by one BR-2320 lithium battery which should run the watch for approximately three years.

These three products are available from Tempus at a discounted price, which includes VAT and P&P (the RRP is shown in parentheses). MQ-6 £19.95 (£24.95), ML-81 £22.95 (£27.95) and the F-80 £19.95 (£24.95).

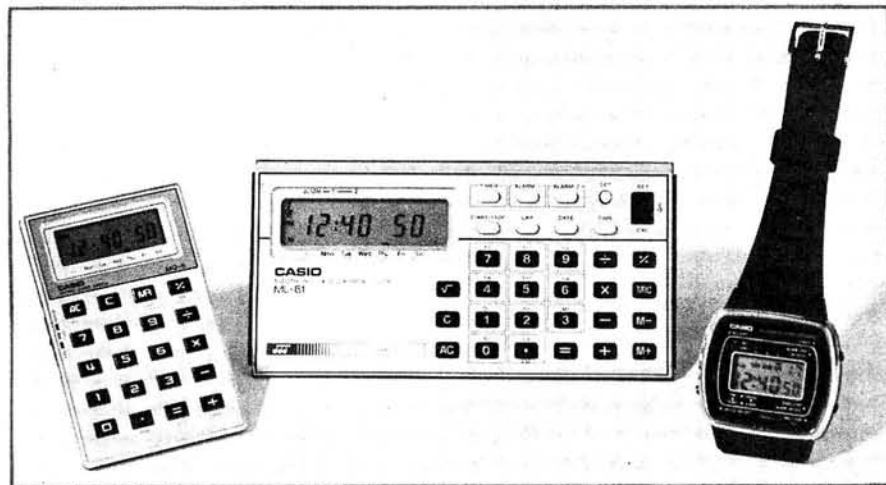Tempus, The Beaumont Centre, 164-167 East Road, Cambridge CB1 1DB. Tel: (0223) 312866.



Mini f.m. Handy

The very latest from Icom is the IC2E, a hand-held two metre f.m. transceiver, which is probably the smallest available.

The IC2E measures 116 high (without battery pack) x 65 wide x 35mm deep and weighs only 450 grams including power pack and antenna. Other features are; fully synthesised, covering 144-145.995MHz in 400 5kHz steps; BNC antenna

socket; transmit/battery state indicator; frequency selection by thumbwheel switches which indicates the tuned frequency; +5kHz switch; duplex simplex switch; hi-low switch which reduces power output from 1.5W to 150mW; external microphone jack and external speaker jack.

This little beauty is supplied ready to go, complete with NiCad battery pack, charger and antenna. Although

Safety Microphone

A very useful item for the amateur, operating a mobile rig is the MM-202 mobile microphone.

The "mini" capacitor-microphone weighs only five grams and is fitted with a lightweight clip enabling the microphone to be attached to the coat lapel or shirt front of the operator.

The p.t.t. switch unit incorporates a microphone pre-amp with preset gain control, a long-arm switch toggle, an i.e.d. transmit indicator and is also fitted with a sturdy clip for mounting on the vehicle's gear change lever.

With the microphone attached to the operator and the p.t.t. switch mounted on the gear change lever should facilitate a much safer operating condition, when considering the more usual handheld microphone with p.t.t. switch incorporated.

The MM-202 costs £20.95 inclusive of VAT, plus 50p P&P. When placing an order or making further enquiries please quote the make of transceiver on which the microphone is to be used. Connectors and wiring diagram are available.

The MM-202 is obtainable from: Waters and Stanton Electronics, 18-20 Main Road, Hockley, Essex. Tel: (03704) 6835.



the price has as yet, not been confirmed, I understand it will be highly competitive.

The IC2E will be available during March, for further details contact: Thanet Electronics, 143 Reculver Road, Herne Bay, Kent. Tel: (02273) 63859.

Memorial Lecture

The Verulam Amateur Radio Club will be holding the 1980 G3PAO Memorial Lecture in the Jubilee Centre, Catherine Street, St. Albans, Herts, on Thursday, 27 March at 7.30 for 8.00 p.m. This event is held to remember their former Chairman and Founder Member, George Slaughter, who passed away in 1977.

The Lecture this year entitled "Frequency Synthesis and Receiver Design" will be delivered by William Poel, G8CYK.

All radio amateurs, short wave listeners and other interested parties are invited to attend. Further details may be obtained from: *The Hon. Secretary G8MAE QTHR. Tel: Hemel Hempstead (0442) 64751.*

RNARS

The Royal Naval Amateur Radio Society will be operating an amateur radio station GB2RN aboard the preserved cruiser HMS BELFAST, moored in London's Upper Pool, opposite the historic Tower of London, commencing 0001 GMT Friday, 4 April 1980 and ending 1800 GMT Sunday, 13 April 1980.

Primary operating frequencies as follows: c.w. 1828(QSX 1802), 1838, 1858, 3520, 7020, 14052, 21052, 21120, 28052, 28152; s.s.b. 1875, 3660, 3780, 7070, 14140, 14245, 14340, 21175, 21433, 28470, 28933.

Schedules are welcomed—especially with other stations of special interest—and can be arranged via *Don Walmsley, G3HZL, 153 Worples Road, Isleworth, Middlesex TW7 7HT. Telephone: 01-892 3239, or via RNARS, Bridge Wireless Office, HMS BELFAST, Symons Wharf, Vine Lane, London SE1 2JH. Telephone: 01-407 6434 extension 39.*

Home Radio

Due to problems arising from a planning permission refusal, Home Radio (Components) Ltd. have been compelled to move to new premises.

Their new address for callers is: *269A Haydons Road, Wimbledon, London SW19 8TY. Temporary telephone number: 01-648 3077. Mail order correspondence should be sent to: P.O. Box 92, 215 London Road, Mitcham, Surrey.*

Club Diary

Harlow and District Amateur Radio Society meet at 8pm every Tuesday at their club house, Marks Hall Barn, First Avenue, Harlow, Essex.

On Tuesday, 1 April 1980 at the club house, they are holding an "All Fools Junk Sale". Payment of the £1 entry fee, permits the taking and carrying away of any of the "junk" displayed and the right to sell your own "junk". Sorry no dealers!

Further details from: *Hon. Sec., A. C. Keeble G4HPU, 4 Manor Cottages, Debden, Saffron Walden, Essex CB11 3JY.*

Irish Agents

Vero Electronics Ltd. have recently signed agreements for the distribution of their products throughout Ireland.

Vero products in Northern Ireland will be available from: *Hill Electronic (N.I.) Ltd., 4 Deerpark Parade, Oldpark Road, Belfast. Tel: Belfast 742371.*

In the Republic the agency will be handled by: *Electronic Manufacturing Co. Ltd., 17 Blessington Street, Dublin. Tel: Dublin 309044, 309188 and 309552.*

New Electronic Security for Hotels

A new ultra-secure electronic door locking system which speeds hotel guest check-ins and overcomes the problem of lost or stolen keys, is being introduced onto world markets by British Relay Electronics Limited.

This locking system, named the "AccessMaster", has an almost unlimited number of key combinations which are preset by a central control unit in the hotel. The low-cost disposable keys are made from virtually unbreakable plastic.

When each guest checks in, a key is selected at random from a storage pool and allocated to the room number. This information is fed into the hotel's central control unit which recognises the new combination and allows access to the room, only when, the correct key is inserted into the door lock.

The same key is used throughout a guest's stay. However, should the key be lost or stolen, another is issued at random, a new combination is allocated by the central control unit and the previous combination is cancelled.

When a guest checks out, the key is returned to the storage pool and the lock combination is deleted from the system.

Should an invalid key be inserted into any door lock, the system prevents the door from opening and immediately signals to the central control unit that an illegal key is being used.

In the event of a door being forced, or burst open, an alarm system is immediately activated.

For extra security, the door locking system is linked to a memory bank which records the exact time and key identification of the last two entries into a room.

The system also allows one key to be programmed to give access to a number of rooms during specific periods of time. The key is then allocated to one member of the hotel staff responsible for cleaning a series of rooms. At the end of the predetermined cleaning period the key combination is cancelled.

Similarly, one key can be programmed to open one or more storage rooms or cellars, and then invalidated when no longer required.

Other facilities include a security key for the central control unit and storage pool, and a buzzer system which signals whenever a door lock is opened.



The central control unit

The central control unit can be interfaced to the hotel's computer system to give automatic morning call, message waiting and room status information. Furthermore, the central control unit continues to operate in the event of a power failure.

British Relay Electronics Ltd., 41 Streatham High Road, London SW16 1EP. Tel: 01-677 2511.



LOW

P. LEAH

frequency

signal generator

Signal generators which employ discrete components in their construction commonly suffer from the problem of ensuring that the output waveform remains pure and stable over their frequency range. Either the mark-to-space ratio becomes irregular or the signal becomes distorted at the extremities of the range.

However, with the aid of microelectronics, most of these problems can be overcome by simply concentrating all the complex control circuitry into a single chip; the designer has then merely to select a handful of components to programme an integrated circuit which has been developed expressly to meet his needs.

One of the most versatile of the commercially available devices is the Intersil 8038 waveform generator. It produces simultaneous sine, square and triangular output waveforms and forms the basis of this constructional project. With additional circuitry for the power supply, the low impedance output buffer stage and the range selection and purity adjustment circuitry, this relatively simple l.f. generator has an output frequency range of 10Hz to 70kHz arranged in three stages: 10-700Hz; 100-7000Hz; 1-70kHz. It is also possible to extend the range to 500kHz.


The output voltage is variable up to 4V peak-to-peak

and the instrument is therefore suitable for both digital and analogue applications (it can be used to direct-drive either TTL or CMOS) and is a useful tool for testing audio or other low-frequency equipment.

Power Supply

The circuit of the power supply section is shown in Fig. 1; it produces a stabilised +11.3V and -11.3V from the 240V mains input. These particular voltages were chosen in order to combine optimum performance with minimum temperature drift.

The mains input is applied to the primary winding of T1. The output from the centre-tapped secondary of this 24V transformer is full-wave rectified by D1-D4 and then smoothed by C1 and C2 to produce unregulated voltages of approximately +17V and -17V at the collectors of Tr1 and Tr2 respectively. These transistors are used in the common base configuration, their base current being supplied via R2 and R3 and the base reference voltage being determined by the 12V Zener diodes D6 and D7. The out-

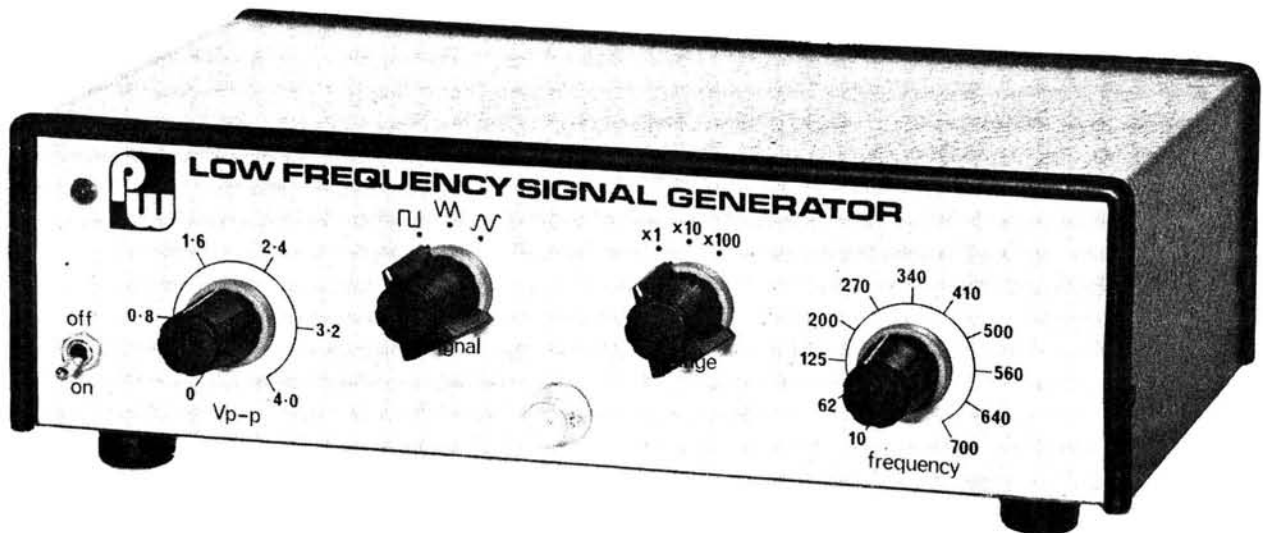

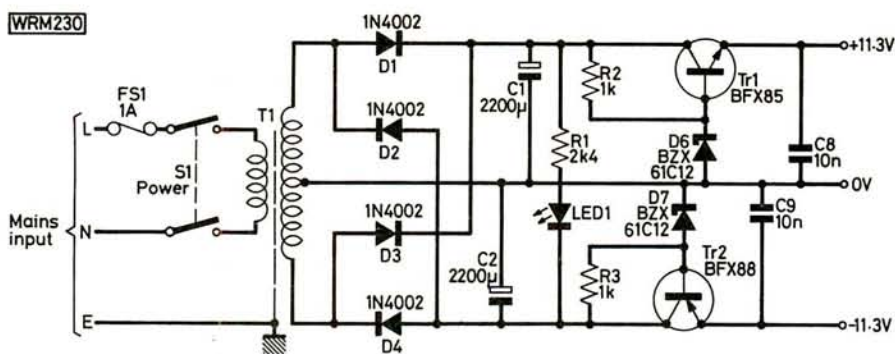


Fig. 1: Power Supply circuit diagram

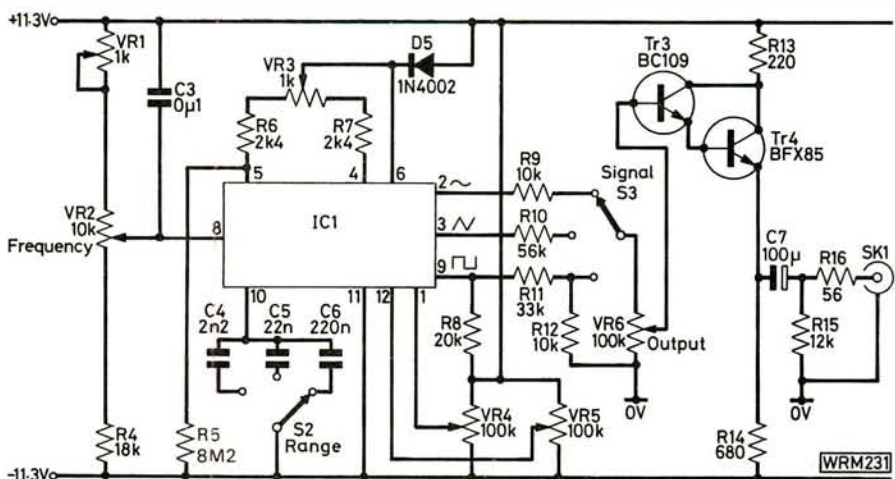


Fig. 2: Main circuit

put voltages from the emitters of Tr1 and Tr2 are stabilised at +11.3V and -11.3V with respect to the 0V line. An on-off indication is provided by LED1 which is connected across the unregulated output of the rectifier bridge (D1-D4) and which, like the power switch S1, is mounted on the front panel. The current through the l.e.d. is limited to approximately 12mA by R1.

Main Circuit

Figure 2 shows the 8038 with its associated range selection and waveform purity circuitry. The output impedances and amplitude of these waveforms vary considerably and the series resistors R9, R10 and R11 are included to produce waveforms equal in amplitude at approximately 4V peak-to-peak. The squarewave output is floating and must be connected to the supply voltage via R8; all of these output waveforms are balanced about 0V. The desired waveform is selected by means of S3 which is mounted on the front panel and the amplitude of the output is varied by VR6, also mounted on the front panel. The output from the i.c. is buffered and amplified by two

transistors Tr3 and Tr4 which are connected as a common-emitter Darlington pair—this configuration provides maximum current gain but negligible voltage gain. Resistors R13 and R14 provide d.c. bias to Tr3 and Tr4. Capacitor C7 provides d.c. insulation for the output waveform which is referenced to 0V by R15. Resistor R16 protects the instrument against damage should the output become short-circuited.

In the configuration shown, the output impedance of the instrument is approximately 100Ω.

Construction

With the exception of those which are mounted on the front panel, all components used in the construction of the i.f. signal generator are mounted on a single-sided printed circuit board. This is housed in a metal instrument case measuring 225 × 64 × 134mm. The main body of the case is drilled only to mount the 6BA bolts which support the p.c.b.; the location of the mounting holes is not critical but be sure to leave enough space between the front panel and the p.c.b. If you don't, the panel-mounted items will tangle

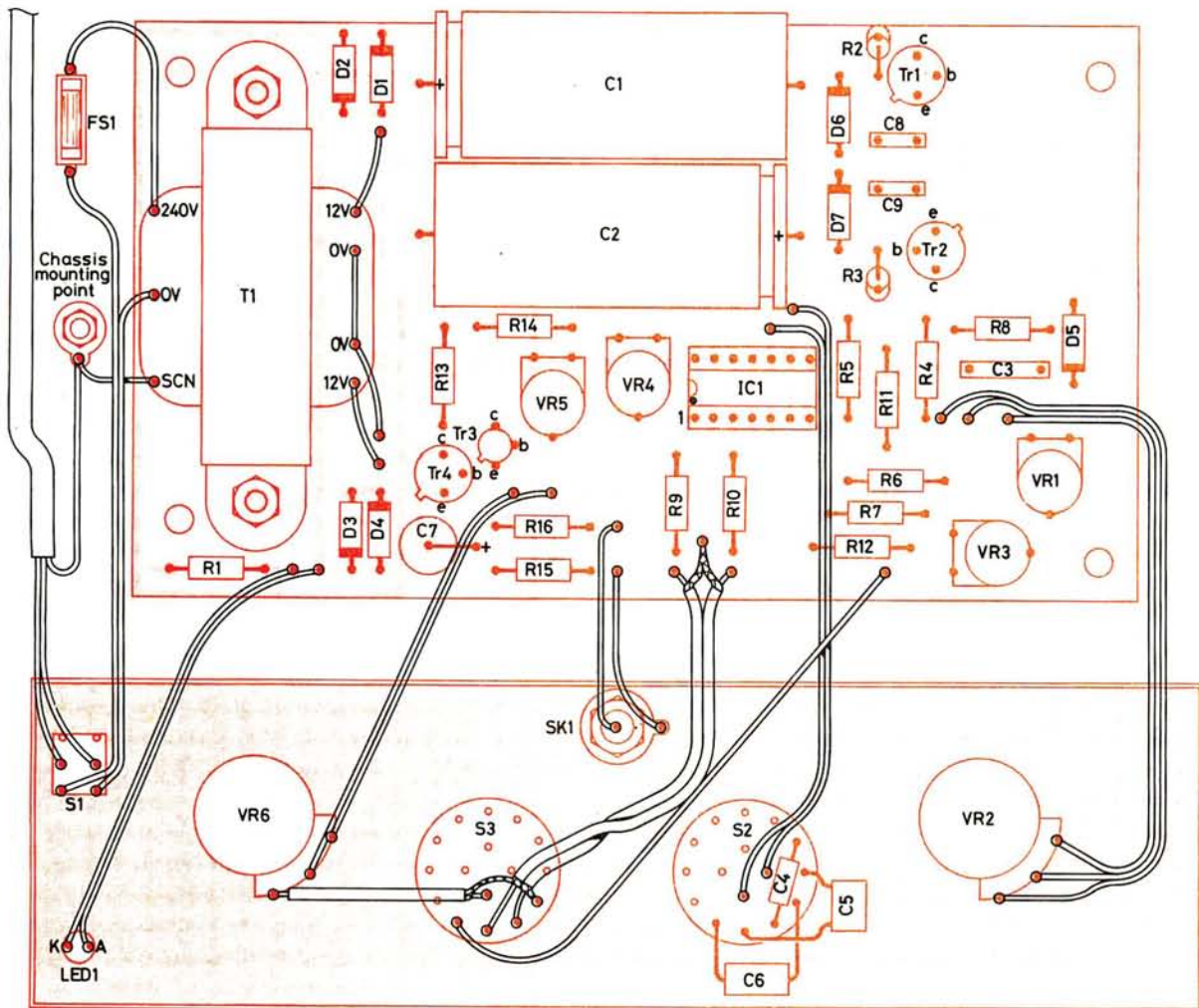
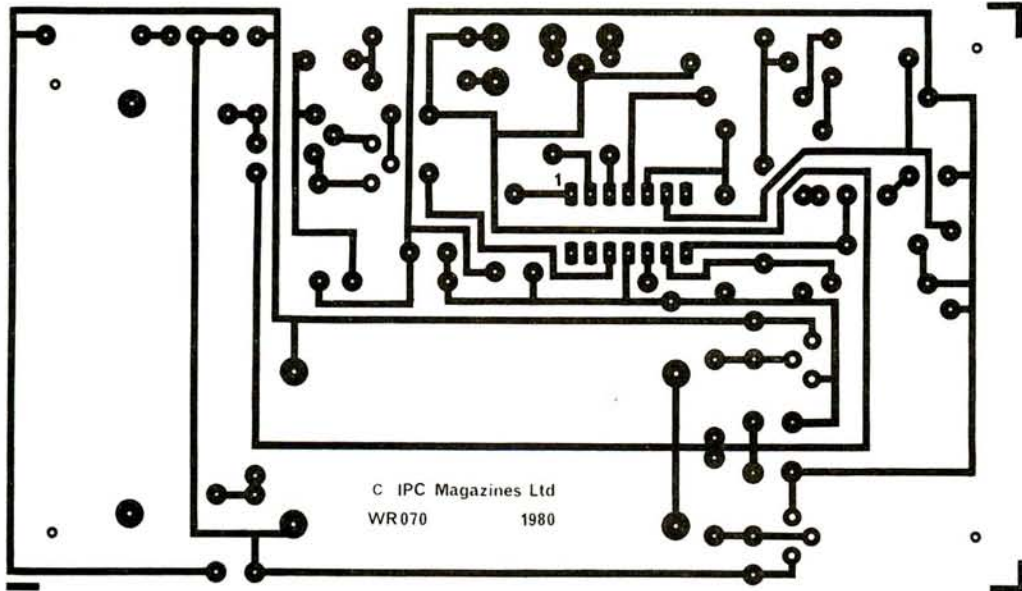


Fig. 3: Copper foil pattern, component layout and connections to front panel, shown full size

WRM229

★ components

Resistors

$\frac{1}{4}W$ 5%		
56 Ω	1	R16
220 Ω	1	R13
680 Ω	1	R14
1k Ω	2	R2,3
2.4k Ω	3	R1,6,7
10k Ω	2	R9,12
12k Ω	1	R15
18k Ω	1	R4
20k Ω	1	R8
33k Ω	1	R11
56k Ω	1	R10

$\frac{1}{2}W$ 5%		
8.2M Ω	1	R5

Semiconductors

Diodes

1N4002	5	D1,2,3,4,5
BZX61C12V	2	D6,7

Transistors

BC109	1	Tr3
BFX85	2	Tr1, 4
BFX88	1	Tr2

Integrated circuit

8038CC	1	IC1	Intersil
--------	---	-----	----------

Light emitting diode

Min. indicator type	1	LED1
---------------------	---	------

Switches

Midget rotary 4p3w	2	S2,3
Min. toggle d.p.d.t.	1	S1

Capacitors

Ceramic

10nF	2	C8,9
0.1 μ F	1	C3

Polystyrene 5%

2.2nF	1	C4
22nF	1	C5

Polycarbonate 5%

220nF	1	C6
-------	---	----

Electrolytic 16V

100 μ F	1	C7	P.c.b. type
-------------	---	----	-------------

Electrolytic 25V

2200 μ F	2	C1,2
--------------	---	------

Potentiometers

Min. preset, horizontal mounting, 0.1W

1k Ω	2	VR1,3
100k Ω	2	VR4,5

Midget, linear track

10k Ω	1	VR2
100k Ω	1	VR6

Miscellaneous

12-0-12V 6VA mains transformer (1); instrument case (Bazelli) 225 x 64 x 134mm (1); 50 Ω BNC coaxial socket, Type UG1094/U (1); 14-pin d.i.l. integrated circuit mounting socket (1); knobs, Sifan, 15mm collet type with wing (2), plain with white line (2); PW transparent panel overlay (1); mains cable entry clamp (1); 1A fuse and holder (1); printed circuit board (1); 50 Ω coaxial cable, equipment wire, etc.

with those mounted on the p.c.b.!

Only one hole is required in the rear panel—for the mains cable entry. In accordance with normal good practice (i.e., common sense), we recommend that you use a cable entry clamp (such as RS Components Type 544-263 or similar) in preference to an ordinary plain grommet. Fuse FS1 is easily accommodated within the case.

The front panel overlay (see Fig. 4) provides the necessary drilling information for the front panel. All the mounting holes for the switches and potentiometers are 9.5mm dia. (0.375in). The hole for the BNC output socket (SK1) should, however, be drilled to 10mm dia.; this hole is intentionally oversized as SK1 *must be isolated from the chassis* in order to avoid undesirable earth-loop effects. Figure 5 shows in detail how this may be achieved. A BNC socket was chosen for the output as this is the type most commonly used in test instrument applications—the individual constructor may, of course, vary the choice to

suit his own requirements. Indicator LED1 is mounted in a 4mm dia. hole.

Full details of the p.c.b. and the connections between it and the front panel are shown in Fig. 3.

Constructors should note that the sine and triangular outputs from the i.c. are high impedance and are therefore susceptible to crosstalk from its squarewave output. Consequently, the connections from the p.c.b. to S3 must use coaxial cable; the same applies to the connection between the common contact of S3 and VR6. Keep the lengths of these coaxial connections as short as possible; note that a spare tag on S3 is used in order to common together the earth screens.

The frequency selection capacitors C4, C5 and C6 are all mounted directly onto the back of S2—a twisted pair is all that is necessary to make the connection between these components and the p.c.b. The remaining interconnections are made with normal stranded equipment wire.

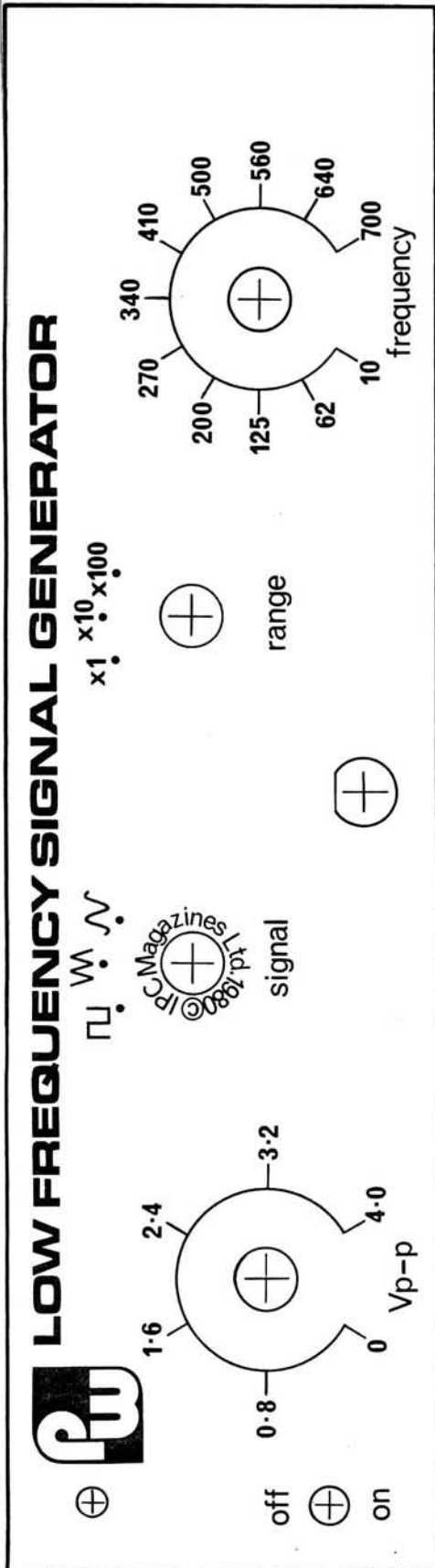



Fig. 4: Front panel (full size)

Testing

An oscilloscope is essential for calibrating the instrument and, if available, a frequency counter and an electronic voltmeter would also be very useful. Check first that the supply voltages (+11.3V and -11.3V) are correct to within 0.2V; the 8038 used in the prototype was socket-mounted and the i.c. was not placed into the socket until these voltages were verified as being correct.

The next step is to set all potentiometers and pre-sets to mid-travel and monitor the output waveforms from pins 2, 3 and 9 of the i.c. using the 'scope. The approximate peak-to-peak amplitudes of the waveforms should be 20V for the squarewave, 6.5V for the triangular output and 4V for the sinewave output. Changing ranges (S2) should alter the frequency by a factor of ten, of course.

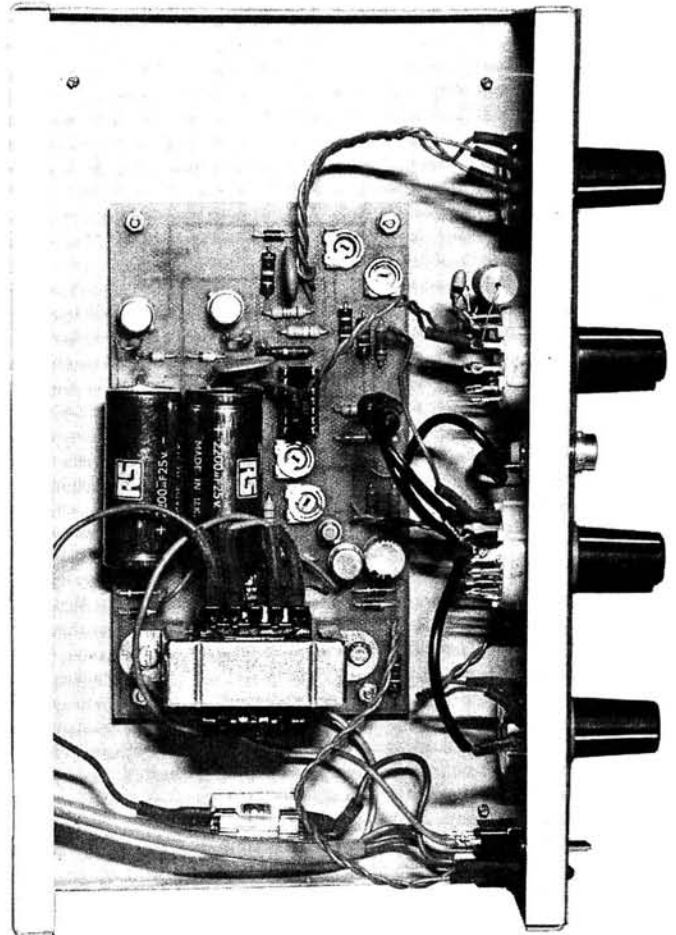Once you are satisfied that all is well with the i.c., test the output buffer by comparing the waveform at the wiper of VR6 (waveforms of up to 4V peak-to-peak should be available on all signal selections) with that emerging from the output socket (SK1). In all cases, the waveforms should be virtually identical at both points.



Interior view of the prototype unit

Calibration

A frequency counter is obviously the best instrument to use for calibration, although an oscilloscope may also be used if its timebase is known to be accurately calibrated. The l.f. generator range switch (S2) should be set to the $\times 1$ position, and VR2 should be turned fully anti-clockwise

(frequency at a minimum). Now adjust VR1 until the output frequency is 10Hz. Changing ranges should now result in output frequencies of approximately 100Hz and 1kHz. Repeating this procedure with VR2 set to its maximum frequency position (fully clockwise) should produce output frequencies of approximately 700Hz, 7kHz and 70kHz.

The purity of the sinewave output should be adjusted by using VR4 and VR5—do this with the output frequency set to approximately 1kHz on the $\times 10$ range. The adjustment is correct, of course, when the trace on the oscilloscope most closely resembles the classic sinewave shape!

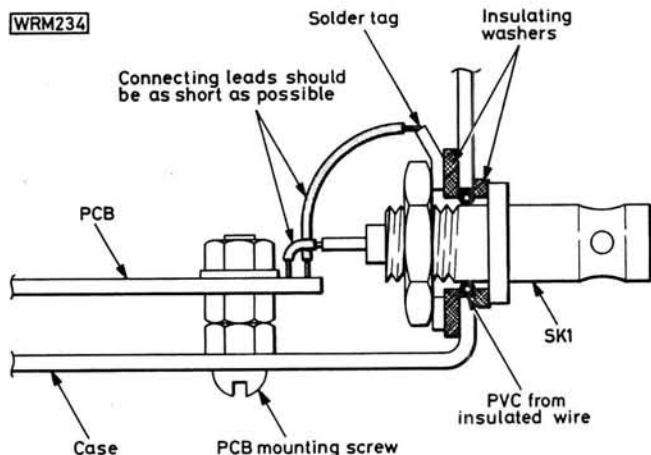


Fig. 5: How to mount SK1. The insulating washers should be cut from semi-rigid plastic sheet, such as the celluloid used in shirt-packaging, etc. The "O" ring is made by cutting pvc sleeving to length and then trapping it in position as shown

Accuracy

After calibration of the frequency scale, it is worth pointing out that the frequency set will be accurate only to $\pm 3\%$. This is due partly to the frequency drift of the i.c. with change in temperature (it does run fairly hot and therefore calibration is best performed after the instrument has been switched on for some time), and partly to the tolerance on the absolute values of the capacitors in the tuning circuit. The accuracy could probably be improved by adding extra trimmer capacitors in parallel with C4/C5/C6, but these additional components and the extra calibration required were not thought to be justified in this simple construction. This particular generator was never intended to achieve laboratory standards of accuracy!

Distortion

Distortion occurs at the low frequency limit, caused by variations in the mark-space ratio, and also at the high frequency limit—due to a reduction in the amplitude of the output waveform. The distortion is, however, within 4% over 95% of the frequency range.

Unfortunately, the distortion is a function of the i.c. itself and varies according to the waveform selected. The triangular output is the most affected as its amplitude reduces above 40kHz. If you decide to extend the range of the instrument as described below, it should be pointed out that the squarewave becomes distorted above 120kHz and the amplitude of the sinewave output becomes reduced above 75kHz.

Extension

If an extension of the output frequency range is desired (and you can stand the reduced amplitude of the output!), substitute a 3-pole 4-way wafer switch for the S2 specified in our components list and add a capacitor in similar fashion to C4/C5/C6. This should be 150pF in value with a polystyrene dielectric and will provide a further sinewave output range from 10kHz to 500kHz.

The reduction in the peak-to-peak output voltage is approximately 50% at the highest frequency. ●

The transparent front panel overlay for this project is available from the PW Editorial Office, price £1.60 including post and packing.

Multiple Choice—continued (see page 21)

Actually, none of the answers is correct. Ohm's Law states:

If the temperature of a conductor is kept constant, the current through it is proportional to the potential difference across it.

Note that the term "resistance" does not enter into the statement of the law as originally given.

"But", I hear you protest; "So what? In practical terms, Ohm's Law relates voltage, current and resistance." And so it does, but if you go back to the options offered, "d" expresses that relationship in words, "b" expresses it algebraically, and "a" gives a numerical example. So you must decide between them.

If I had encountered this question in an exam, knowing that none of the options is correct (or even if I hadn't known), I would have argued as follows: "c" is not relevant. It is probably a true statement but it is not a complete sentence (read it again if you don't believe me), so I cannot be sure. "a" is relevant and true, but not adequate as a definition, and laws are not usually expressed numerically, so it can be eliminated. "b" is relevant and true and adequate, being answer "d" turned into an equation. To choose between the two, I would argue that laws are more often stated in words than symbols, and plump for "d". I don't know if that's "right", but in any case, the decision doesn't seem relevant to my suitability to become a radio amateur, or does it?

Geoff Arnold

New Catalogues

Greenweld's latest 1980 catalogue is now available.

Many new products have been added, and surprisingly a great many prices have been reduced, giving even greater value.

Included with every catalogue is a first-class reply paid envelope, an order form, their latest bargain list and inside the back cover will be found five 12p discount vouchers.

As soon as the new Vero catalogue becomes available (early 1980), this will be included as well.

The catalogue costs 40p plus 20p P&P from: *Greenweld Electronics Ltd., 443 Millbrook Road, Southampton SO1 0HX. Tel: (0703) 772501.*

Transformers

Barrie Electronics Ltd. have extended their range of transformers, all available from stock.

In addition to their existing ranges of miniatures, output and mains input types are auto transformers, isolating transformers (with screens), low voltage ranges and low-cost split bobbin types.

Barrie also provide a specialist winding service for types not covered by standard ranges stocked, a catalogue is available for 20p stamps.

Barrie Electronics Ltd., 3 The Minories, London EC3N 1BJ. Tel: 01-488 3316/7/8.

Club News

A new AR society has been formed, The Eden Valley Radio Society. Meetings are held every third Thursday of the month at 7.30pm in the Two Lions Hotel, Penrith, Cumbria.

A comprehensive programme has been arranged for 1980, which includes field day stations.

A welcome is extended to all, who can obtain further details from: *David Shaw G8TXJ, 2 Low Wiend, Appleby-in-Westmorland, Cumbria CA16 6QP.*

North Devon Radio Club meets twice a month. On the 2nd Wednesday at Pilton Community College, Choddford Lane, Barnstable, and on the 4th Wednesday at 38 Clovelly Road, Bideford. All meetings start at 7.45pm.

Further details from: *The Secretary, H. G. Hughes G4CG, "Crinnis", High Wall, Sticklepath, Barnstaple EX31 2DP.*

Garrard Sold

The Plessey Company Limited announced recently that the worldwide business of its Swindon-based consumer electronics subsidiary, Garrard Engineering Limited, is to be sold as a going concern to Gradiente Electronica Limitada of Sao Paulo, Brazil, for £1 million cash.

Gradiente is a major audio products company with five factories in Brazil and one in Mexico. The Company employs 2,800 people and last year had a turnover of approximately £35 million. It markets a complete range of hi-fidelity audio products and presently manufactures Garrard products under licence in Brazil.

It is intended that Gradiente products and the existing Garrard range will both be marketed in future under the Garrard trade name throughout the world. The combination of the Garrard name and products and the Gradiente range will present an attractive, comprehensive and unified group of audio products.

Gradiente expects that Garrard with a wider range of products will trade profitably in the future.

Hi-Fi Homework

Building the power stage of a hi-fi amplifier awaits students starting the Open University's new second-level course on Introductory Electronics. The home experiment kit for the course also contains a dual-trace oscilloscope with its own power supply.

"Introductory Electronics" uses a systems approach concentrated on circuit design and offers a modern, practical way of teaching digital electronics, for example in focussing on the use of read-only memories specified by truth tables. It brings students to the point where they can begin to tackle work on microprocessors, as in "The Digital Computer", a related course from the Open University.

Equally, though, the new course is useful for people who simply want to find out what electronics is about.

It does, however, assume a basic knowledge of some mathematical concepts: sine and cosine functions, elementary differentiation and integration. Students could get to this stage by taking the Open University's course, "Modelling by Mathematics".

There are eleven television programmes associated with the course, and a joint summer school with the Open University's course on Instrumentation.

At present, "Introductory Electronics" is available to existing undergraduates of the Open University, but in 1981 will be introduced for Associate Students undertaking a "one off" period of study. (Applications from Associate Students will be invited in May this year.)

Nearly 1400 students have applied to start "Introductory Electronics" in January and, overall, more than 4000 people have applied to enrol on one of the Open University's four electronics courses: "Introductory Electronics", "Instrumentation", "Telecommunication Systems" and "The Digital Computer".

Open University students learn from study booklets sent through the post, from associated radio and television programmes, summer school and tutorials.

If you would like to become an undergraduate of the Open University, write to: *The Admissions Office, PO Box 48, Milton Keynes MK7 6AB.* No formal educational qualifications are required—entry is on a "first come, first served" basis. Applications are invited before May 30, to start studying in 1981, but apply early to stand the best chance of being accepted for next year.

Can You Help BAEC?

The British Amateur Electronics Club, formed in 1966, has its base at Penarth, S. Glamorgan. Members in other parts of the country have tried to start local meetings, but have run into many problems, principally that of finding a suitable room at a reasonable charge.

If you run an Electronics Group or Radio Club, the BAEC would greatly appreciate, if suitable arrangements could be made, for local BAEC members to attend your meetings. Naturally, those members would be prepared to pay an affiliation fee.

Can you help? If so, please contact: *The Chairman, BAEC, Cyril Bogod, "Dickens," 26 Forrest Road, Penarth, S. Glamorgan. Tel: (0222) 707813.*



NIMBUS

Modular 2m Transceiver System (Part 2)

Michael TOOLEY BA G8CKT
&
David WHITFIELD BA MSc G8FTB


Construction of the transceiver should not be attempted without the use of the recommended printed circuit design for the main transmitter/receiver module. No other form of construction will give satisfactory results, and even a small departure from the recommended layout may cause severe problems. Whereas a double-sided p.c.b. (with an extensive earth plane on the component side of the board) could have been used for this project, the obvious advantage of simplified track layout was considered to be outweighed by the comparatively high cost and fabrication problems when compared to a single-sided design. In particular, the requirement for accurate registration between the masks for the two sides of the board would have rendered it difficult, if not impossible, for the average amateur to manufacture.

The result (after many hours spent in playing a mind-bending version of three-dimensional jigsaw puzzles) was to produce a single-sided printed circuit design. The track layout is shown in Fig. 7, and the following section contains some notes for constructors who wish to manufacture their own p.c.b. for the transmitter/receiver module. The ensuing sections contain some specific constructional notes for the three basic circuit modules, but first a number of other general points which apply to all the modules. Assembly details for the transmitter and receiver tuned circuits are essentially the same and are therefore described together in a separate section.

It was mentioned in Part 1 that the basic transceiver could be built for around half the cost of an equivalent commercial unit. The economy achieved, however, is the result of careful design, rather than by the use of low cost surplus type components and the use of full-specification components is, in fact, essential to ensure good performance; surplus components should, therefore, be avoided. For example, surplus transistors may function quite adequately in many respects and in many applications, but

their performance in terms of noise, gain and cut-off frequency is often impaired, to the detriment of the overall circuit performance. Another important consideration is that the components used should fit into the spaces allocated to them on the printed circuit board. In particular, this is true of the electrolytic capacitors, which should be tantalum bead types. These are more expensive than other types, but represent the most compact way of achieving the required capacitance.

All the connections between the printed circuit boards and external controls, sockets, etc., are made to terminal pins on the p.c.b. the pins being employed are those used for standard 0.1in Veroboard. The various test points are also fitted with pins to allow measurements to be made easily from the top side of the board. When the component assembly has been completed a further visual examination is recommended and all protruding connections on the foil side of the board should be cut off as close to the board as possible to avoid any stray capacitance effects between connections. This side of the board may then be cleaned using a solvent cleanser and then treated with a light protective coating of printed circuit lacquer.

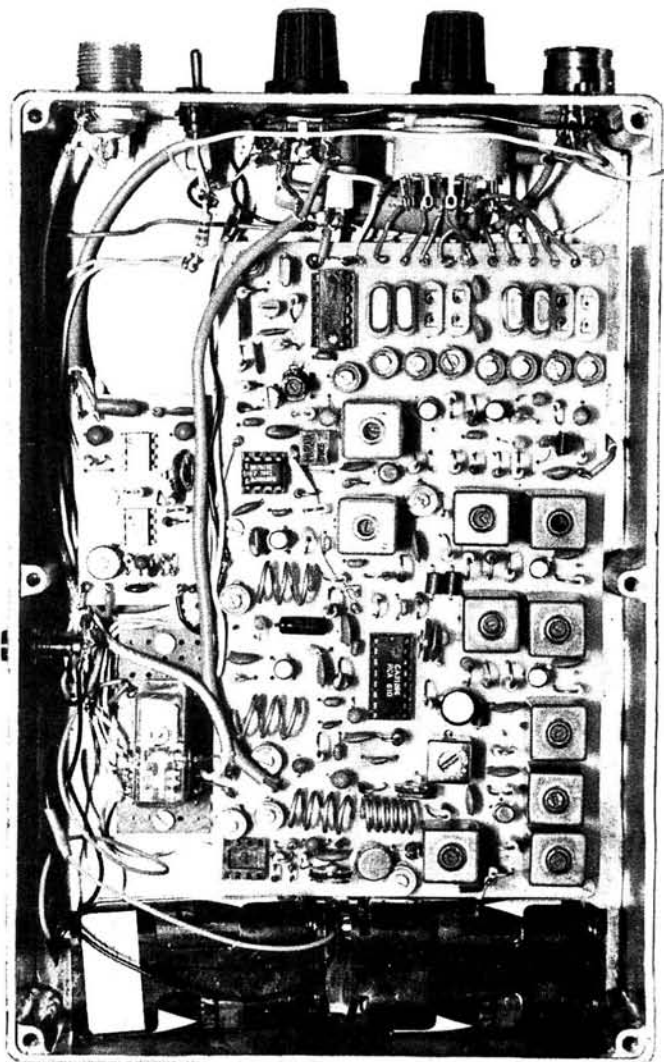

Internal view of the transceiver


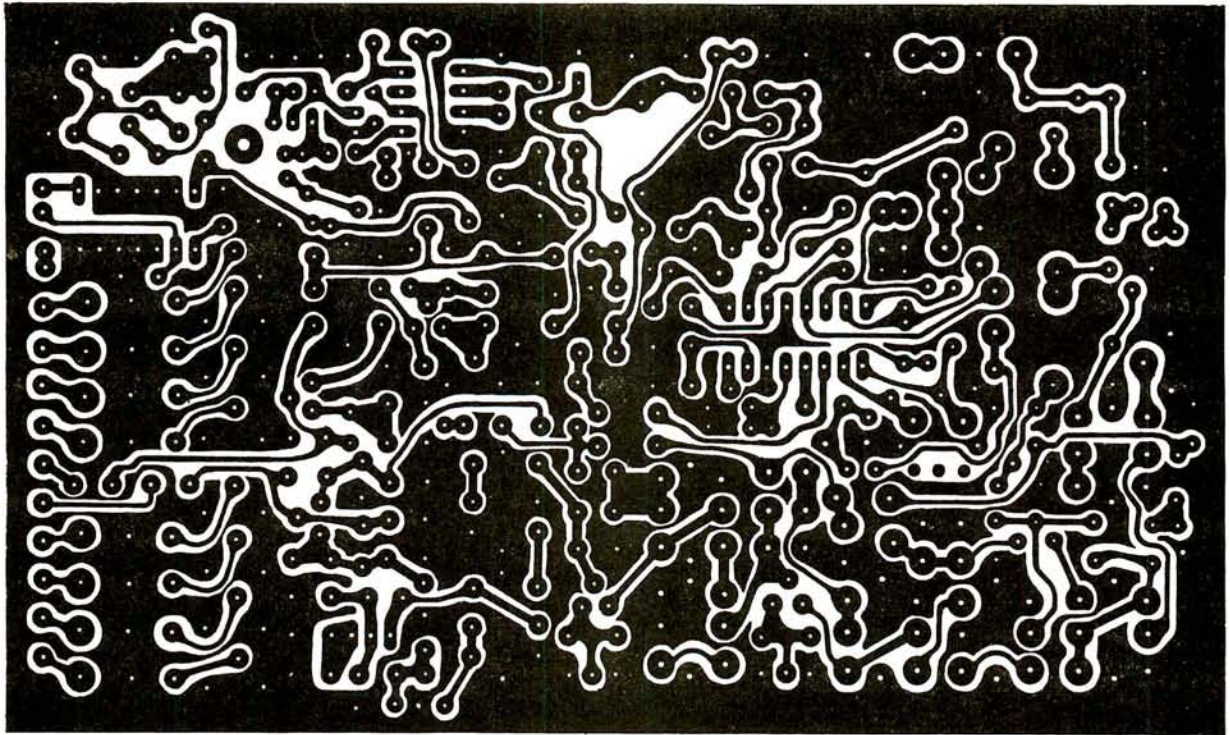


Fig. 7: Main printed circuit board track pattern shown full size

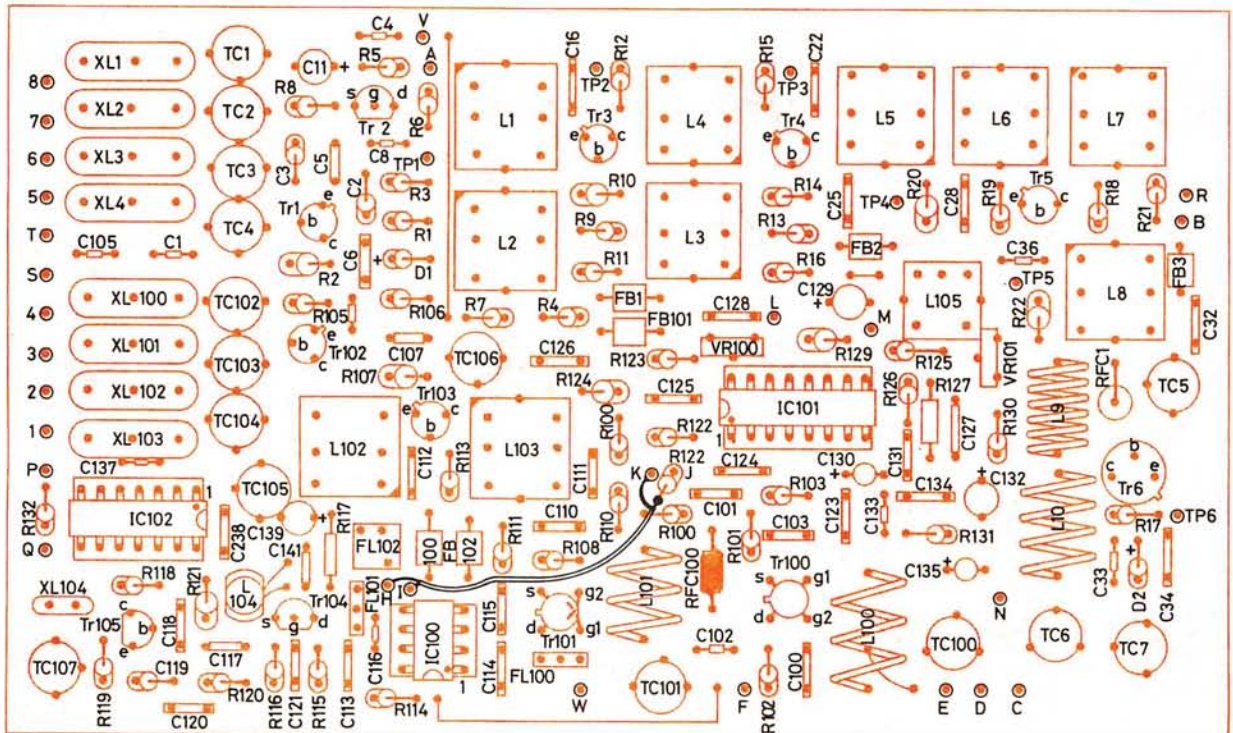

WRM236

Fig. 8: Component layout on the main printed circuit board

Printed Circuit Board

The manufacture of the p.c.b. for the transmitter/receiver module is a relatively straightforward undertaking provided that the necessary materials and facilities are available. The whole process can be completed in approximately 2 to 3 hours, including the time to drill the holes.

The first stage in the process is to make a transparent mask from the 1:1 p.c.b. layout shown in Fig. 7. This may be done photographically or with the aid of a suitable proprietary copying process. A piece of copper-clad single-sided fibreglass board of at least 160mm x 90mm should be coated with positive photo-resist using one of the proprietary sprays available, alternatively, pre-coated board is available from several sources. The mask is then laid over the coated board and the board is exposed to ultra-violet light through the mask. The directions supplied with the board indicate suitable exposure times and the exposed board is then immersed in developing solution (this is typically sodium hydroxide). After developing is complete, the board should be carefully washed.

It is worthwhile at this stage to subject the board to a careful visual examination. The developed resist pattern should be checked to ensure that there are no unwanted bridges between tracks. Any such extraneous resist should be removed with a fine scribe. When the pattern is considered to be satisfactory the board may be etched in the usual way. After etching and cleaning, the board should again be checked for unwanted copper bridges. The importance of such checking cannot be over emphasised; a few minutes well spent at this stage may save many hours of frustration later on!

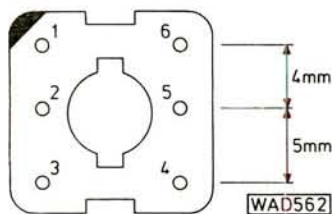


Fig. 9: Coil base connections viewed from above

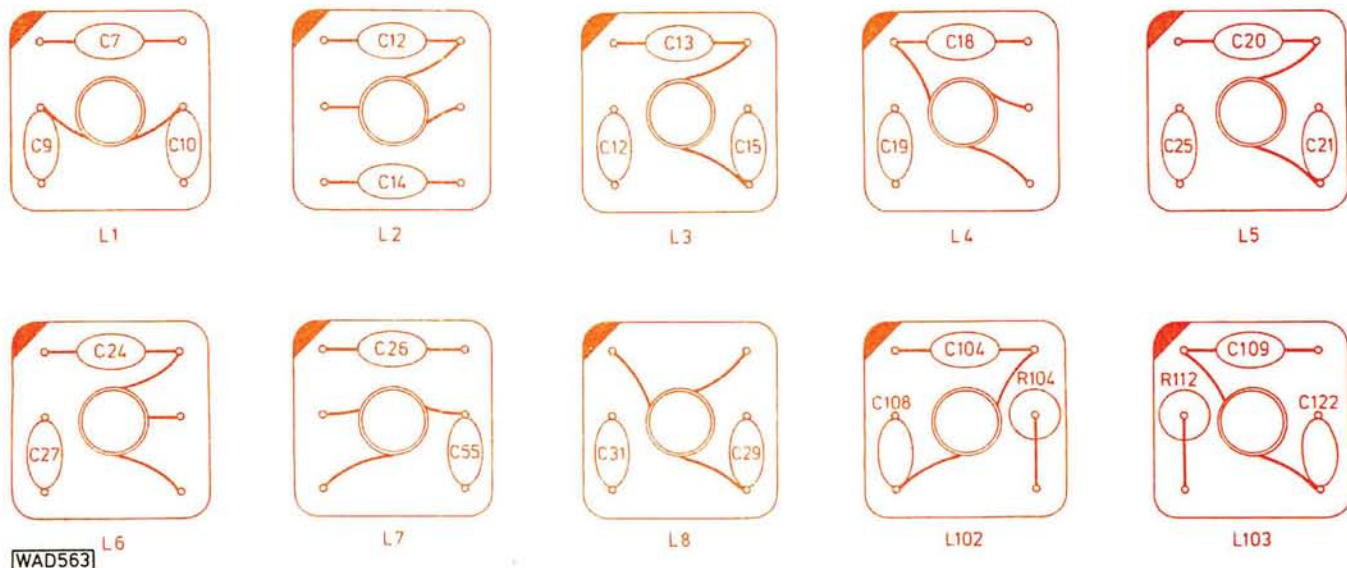


Fig. 10: Coil base connections viewed from above showing components



Fig. 11: Modulator printed circuit board (full size)

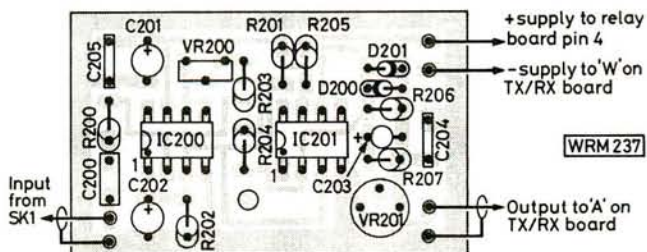


Fig. 12: Modulator board component layout

The board is now ready for drilling and it is recommended that initially all holes are drilled out with a No. 60 (1mm) drill. In view of the number of holes involved, it is likely that a quantity of such drill bits will be required; it is essential that sharp drills are used to ensure clean, burr-free holes. After all the holes have been drilled, specific holes should be enlarged where appropriate as follows:

- 1mm All test points, all wiring points (both to accept terminal pins as used on 0.1in Veroboard), all preset resistors and for the centre pins of the crystal sockets.
- 1.5mm All trimmer capacitors, end terminals of the crystal sockets, the coil bases (including the holes for the cans), L9, L10, L100, L101, and earth tags for L105.
- 3mm For mounting the board in the case.
- 6mm For the base of L104.

The board is now ready for the components to be assembled onto it.

Table 1: Tuned circuit coil winding details

Coil	Base and Can	Former	Tuning Slugs	Turns	Wire		Winding Length mm	Tap Details	Top	Pins Bottom	Tap	Notes
					s.w.g.	Type						
L1	✓	✓	✓	18½	36	enam.	close	—	2	5	—	
L2	✓	✓	✓	20	36	enam.	close	4½T from pin 5	6	5	2	
L3	✓	✓	✓	12	36	enam.	close	—	4	6	—	
L4	✓	✓	✓	12½	36	enam.	close	3T from pin 5	1	5	4	
L5	✓	✓	✓	6	22	t.c.	7.5	—	6	4	—	
L6	✓	✓	✓	7	22	t.c.	10	2T from pin 5	5	6	4	
L7	✓	✓	x	3½	18	t.c.	7.5	½T from pin 2	2	5	3	
L8	✓	✓	x	4	22	t.c.	7.5	1T from pin 6	4	6	1	
L9	x	x	x	6	18	t.c.	12.5	—	—	—	—	6mm i.d.
L10	x	x	x	4	18	t.c.	15	—	—	—	—	7.5mm i.d.
L100	x	x	x	3	18	t.c.	15	1T from chassis	—	—	—	7.5mm i.d.
L101	x	x	x	3	18	t.c.	12.5	—	—	—	—	7.5mm i.d.
L102	✓	✓	✓	8½	36	enam.	close	—	6	3	—	
L103	✓	✓	x	3½	22	t.c.	7.5	—	1	4	—	
L104	x	✓	✓	30	36	enam.	close	—	—	—	—	

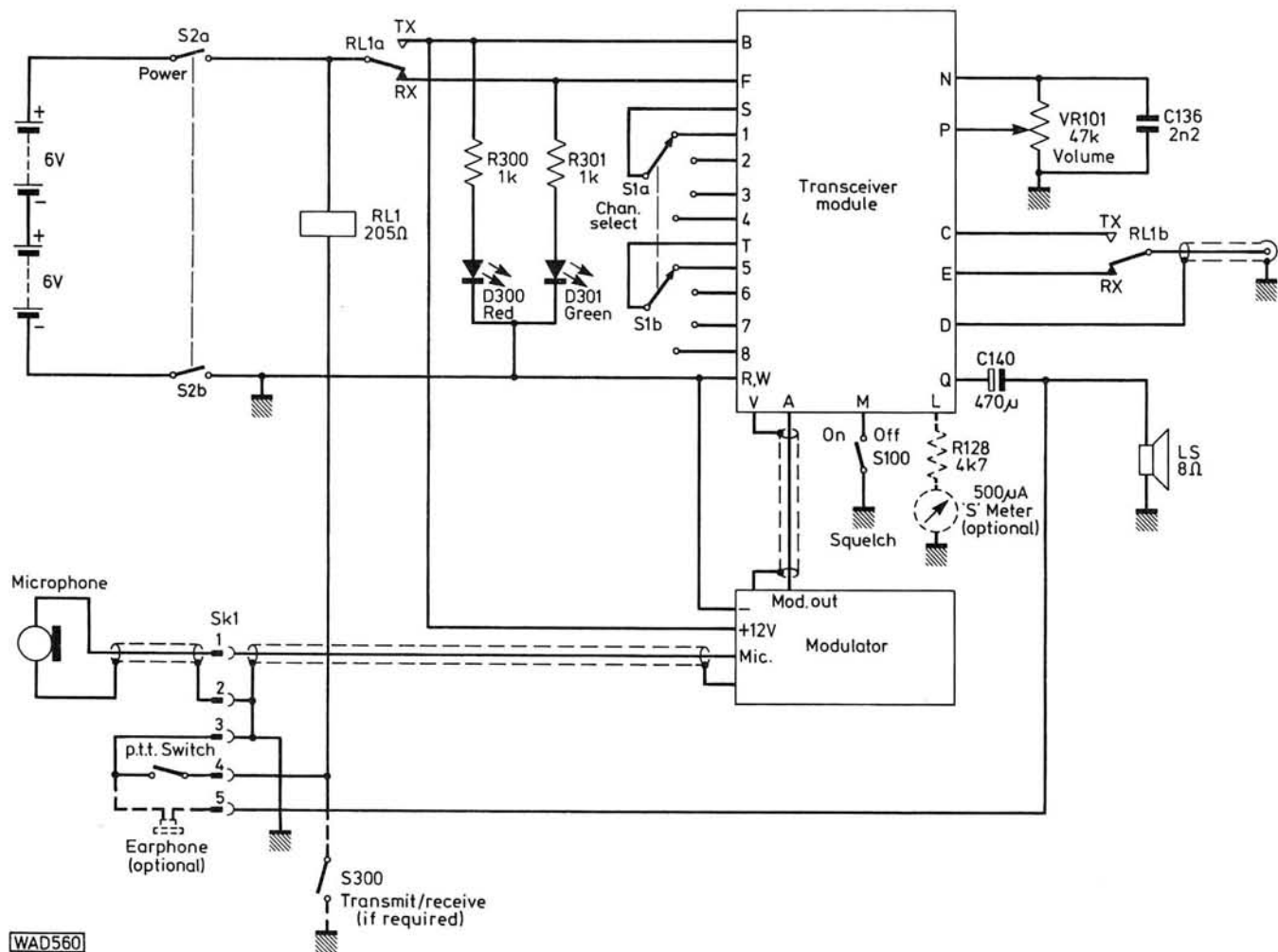


Fig. 13: Circuit diagram of interconnection wiring

Tuned Circuits

The construction of the various tuned circuits as described below depends on the use of the components as specified in detail in the parts lists. All but four of the coils used in the tuned circuits are wound on 4.8mm formers, the remainder (L9, L10, L100, L101) being self-supporting, air-spaced windings. The coil formers, with the exception of L104, are mounted on bases inside the screening cans; L104 uses a former mounted directly on the printed circuit board.

The convention which will be adopted to identify the base connections is illustrated in Fig. 9. The "flag" marker is used in the various illustrations to identify pin 1 of the base as viewed from the top side (the base itself carries no such marking in practice). The coils which are mounted in screening cans also have a number of passive components wired to the coil former base and the component layouts associated with these coils are shown in detail in Fig. 10, the coil windings themselves being specified in Table 1. It is recommended that the components on each coil base are all fitted before the completed unit is mounted on the printed circuit board. The windings themselves may be secured to their formers with a drop of polystyrene impregnant to prevent subsequent performance degradation arising from vibration-induced value changes.

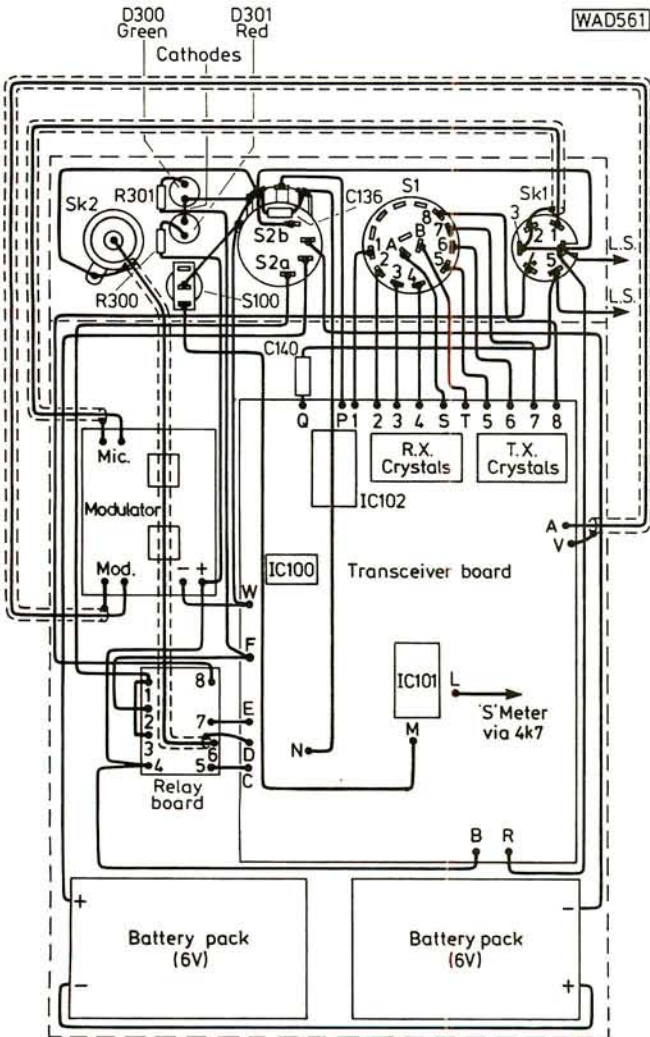


Fig. 14: Wiring and interconnection details

Transmitter Construction

The construction of the tuned circuits for the transmitter module should now be complete with the exception of L9 and L10 which are easily wound on the shank of a twist drill of the appropriate diameter and the winding length then adjusted while still on the drill. It is recommended that the tuned circuits and coils should not be fitted to the p.c.b. until after the remainder of the components are in place because this facilitates the insertion of the smaller components with much greater ease.

The component layout for the transmitter module is shown in Fig. 8. The use of fine insulated wire is recommended for the link adjacent to L1 and L2. The ferrite beads, FBI-3, are fitted and held in place by wire links through their centres as shown. The choke, RFC1, is constructed by close-winding turns of 30-36 s.w.g. enamelled copper wire along the length of a $\frac{1}{2}$ watt 1k Ω resistor, the ends of the winding being soldered to the resistor leads close to the body.

Receiver Construction

In most respects the construction of the receiver follows closely the pattern of the transmitter described in the previous section. However, there are a number of differences and additional considerations to be borne in mind. The receiver makes use of three integrated circuits and these may, if desired, be mounted in dual-in-line

Fig. 15(a): Copper foil layout of the relay board shown full size



WRM238

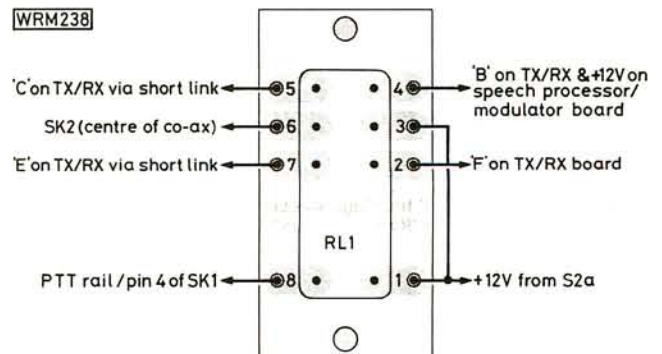


Fig. 15(b): Relay orientation and pin connections

sockets. In any event, the orientation of the integrated circuits should be very carefully checked before power is applied to the circuit.

The component layout for the receiver module is shown in Fig. 8, but this diagram has a link omitted for reasons of clarity. A coaxial connection is required between pins H and I, J and K, respectively. It should be noted that pin J is in fact one end of R133 which stands vertically in the position shown, i.e., the bottom of R133 is soldered to the p.c.b. while the top end acts as pin J.

The construction of the choke, RFC100, is similar to that of RFC1 described earlier, the difference is that the value of resistor used is 100k Ω . The inductor for the "trap" circuit, L104, is wound on a 4.8mm former which mounts directly onto the p.c.b. This should be a tight fit, but the former may be secured with a drop of adhesive taking care not to get any in the threads of the former.

Other points which may not be immediately obvious from Fig. 8 are as follows. The second local oscillator crystal, X104, is soldered in place without any socket. The gate connections of Tr101 cross over and so must have insulated sleeves. Choke RFC100 should be mounted horizontally on the p.c.b. The filters which define the performance of the first i.f. amplifier, FL100 and FL101, are Toko Type CFS10.7 which were designed for use in wide-band f.m. receivers and are used here to provide broad-band selectivity. The standard filters are available with 300kHz \pm 50kHz bandwidth (-3 dB), and attenuation of better than 20dB at ± 600 kHz. It is advisable to order filters in pairs to ensure matching characteristics, and filters with a narrower bandwidth (± 150 kHz at the 3dB points) are available from Ambit International under the description CFS10.7(150). All types are electrically symmetrical, and may be inserted either way round, with the centre pin always earthed.

The second i.f. filter is available in two forms. The CFU455H has a bandwidth of 6kHz (-6 dB), while the CFU455F has a bandwidth of 12kHz (-6 dB), both being ceramic filters in the same encapsulation. The filter used depends on the application, but the CFU455F is probably more suitable for general purpose applications.

Modulator Construction

The simple modulator circuit is built on its own single-sided p.c.b., the component layout for the board not being critical, but a good earth is desirable for decoupling purposes. A suitable p.c.b. track layout is shown in Fig. 11 with the corresponding layout in Fig. 12.

Constructors wishing to manufacture their own p.c.b. for the modulator should follow the same procedure as described for the main transmitter/receiver module. Alternatively, a suitable piece of 0.1in Veroboard may be used in place of a formal p.c.b. The two integrated circuits may be mounted in dual-in-line sockets if desired, but otherwise no special considerations apply to the mounting of the components.

Wiring and Internal Layout

The circuit diagram of the interconnecting wiring is shown in Fig. 13, the actual layout employed being very much a question of individual preference and the wiring diagram of Fig. 14 shows only one possible interpretation. In any layout, however, the following points should be borne in mind:

1. The aerial and microphone sockets should be physically separated. (Ideally at opposite ends of the front panel.)
2. Controls should be easily accessible and logically placed.
3. Controls and sockets should all be located on the front panel thus allowing the transceiver to be used in either the upright or the horizontal position. (The former is appropriate for "hand-held" use and the latter for dash mounting in a car.)
4. Links from the transceiver board to the crystal switch should be kept as short as possible, and 50 Ω coaxial cable should be used for all signal connections including linking the relay board to the aerial socket.
5. The relay board should not be placed in close proximity to the p.a. transistor, Tr6 and associated components.
6. The relay board can be located immediately beside points E, D and C on the transceiver board. In this case coaxial links are not required and short lengths of 22 s.w.g. tinned copper wire will be adequate. A suitable layout for the relay board is shown in Fig. 15. Constructors may, however, mount the relay on a small piece of 0.1in matrix Veroboard if preferred.
7. The printed circuit boards should be mounted so that all test points and preset components are readily accessible.

In Part 3 we will deal with the alignment of the transmitter and receiver, setting up the modulator controls and finishing the completed project. Also included will be information on the crystals required for the most popular of the v.h.f. f.m. channels.

Please note that Tr105 was incorrectly shown as BC458 in the receiver components list. It should read BC548 as shown on the circuit diagram.

STEREO AUTO FADER

▶▶▶ continued from page 28

Adjustment

With the input connected to a programme source and the output coupled to a tape deck or amplifier, the deck or amplifier controls are adjusted for the correct channel balance. VR2 is set to give a microphone signal of the appropriate level, and R8 is adjusted to correctly balance this signal. VR2 is set for the highest threshold level that gives reliable operation of the automatic fader circuitry. It is not advisable to use a lower setting as this could result in accidental operation of the fader action and could also considerably extend the decay time of the circuit. R11 is adjusted for the desired level of fade out in the left hand channel and then R16 is used to balance the two channels with the automatic fade in operation.

If desired, a higher level of fade can be achieved by increasing R12 and R19 in value. The time taken for the signal to return back up to its non-faded level is proportional to the value of C1, and can be altered by changing the value of this component should a different decay time be preferred. Similarly, the time that elapses before the signal begins to return to its normal level is proportional to the value of C3, and can easily be changed if a different delay time is considered to be desirable. ●



FT~7B



Mobile HF TRANSCEIVER

PART 2



In Part 1, last month, we looked at the circuit arrangements, and gave details and results of the transmitter section tests. The marine transmitter specifications were used as a "yardstick" for some of these, but it should be remembered that amateur equipment is designed to much less rigorous standards. Just as well, otherwise few amateurs could afford it! We now continue the receiver section tests and measurements.

Table 6 lists the internal whistles, and is produced by tuning carefully through each band in turn looking for the whistles, and then measuring the frequency and equivalent level. Table 7 lists external spurious, a much longer task. For this, the receiver is tuned to a frequency, and then the signal generator is set to a level of 10mV and swept, manually, from 500kHz to about 50MHz. Each whistle is then measured in level and frequency, and those above 100mV are ignored. This test is very laborious, but a signal generator of the type required for accurate measurement by sweeping costs about £16 000, and the authors employers haven't yet found sufficient justification for it!!

Table 8 lists the intermodulation performance. For this test, two equal signals spaced 20kHz apart are fed into the receiver, which is tuned 20kHz away from one of the signals. The levels of the signals are then adjusted, while maintaining equality of level, until the resultant received signal is equivalent to a 1µV input signal. For 2nd order intermodulation distortion, signals are chosen such that their sum or difference is equal to the frequency of tune. This test is very important in determining the receiver capabilities on an aerial.

Reciprocal mixing again uses two frequencies, and this test measures the noise sidebands of the local oscillator(s) in a receiver. It is especially important in synthesised receivers, and those using pre-mixed oscillators. Cross modulation is one of the most misunderstood terms in amateur radio, and rarely occurs in modern receivers—other effects mask it, and lead to operator intervention first! As can be seen from the results, cross modulation is masked by reciprocal mixing, and this seems a fairly common feature of modern receivers.

Finally, it may be noted that no measurements are made of selectivity as such. Because the equipment uses a com-

Table 6. Internal Spurious. Equivalent Input Levels

Band MHz	Frequency	Level µV
3.5	—	—
7.0	7.4155	0.07
14	14.165	0.1
	14.502	0.4
21	21.200	0.07
28.5	28.799	0.15

Table 7. External Spurious

Tune Frequency MHz	Spurious Frequency MHz	Spurious level for equivalent to 1µV i/p
3.7	3.915	87dB
	4.050	86dB
	4.500	80dB
	6.869	67dB
	9.000	90dB
7.2	14.289	73dB
	6.870	80dB
	7.808	78dB
14.2	9.000	70dB
	13.857	78dB
	32.212	80dB
21.2	39.202	70dB
	23.400	58dB
28.7	30.800	55dB
	33.200	75dB
	34.000	43dB
	39.300	65dB
	41.400	60dB
	46.700	50dB

Note: Spurious signals appearing at a level greater than 10mV have been disregarded.

No explanation is offered for the 10m band spurious being on multiples of 100kHz.

AMATEUR RADIO EXCHANGE



Brenda (G8 SXY) and Bernie (G4 AOG) invite you to the only shop in London where you can see and try all the leading makes of Amateur Radio Equipment under one roof . . . YAESU, ICOM, TRIO, STANDARD . . . compare them all . . . and have a cup of Brenda's coffee too!

★ JUST LOOK AT OUR PRICE ★

STAR OFFER



TRIO R-1000 **£289** Inc. VAT

STAR OFFER

A MUST for the serious FRG-7 owner . . .

Free standing external digital display giving accurate frequency readout while still retaining the analogue tuning facility.



PRICE **£49** inc. VAT

★ JUST LOOK AT OUR PRICE ★

Something different, the fabulous new synthesised VHF/UHF BEARCAT 220FB receiver from the USA. Covers three amateur bands plus aircraft, marine and public service bands on these frequencies: 66-88MHz, 118-136MHz, 144-148MHz, 148-174MHz and 420-512MHz. Scans between any two pre-set channels, and also offers a priority-channel signal-finder and a lock-out facility. Operates on mains or 12V, so use at home, in the car, or on the boat.



BEARCAT 220 FB **£241.50** inc. VAT



At its price you won't find a better communications receiver than the YAESU FRG-7. We like to summarise its specification by saying that the FRG-7 hears things that other receivers don't even know exist . . . all the way from 500kc to 30MHz. So come and try it, and see for yourself why it still represents the finest value-for-money in the communications receiver market today.

YAESU FRG-7 **£199** inc. VAT and free HELISCAN Aerial

. . . and this is the HELISCAN Wall-to-Wall Aerial

Only from us, a specially developed high-tensile receiving antenna giving superb results. Use it indoors or out – from wall-to-wall, from point-to-point, or from pillar-to-post.



INTRODUCTORY PRICE – JUST **£15** inc. VAT

CLOSED WEDNESDAY, BUT USE OUR 24-HOUR ANSAFONE SERVICE

EASY TERMS UP TO 2 YEARS



CREDIT SALES BY TELEPHONE



INSTANT HP FOR LICENSED AMATEURS

2 NORTHFIELD ROAD, EALING, LONDON W13 9SY. Tel: 01-579 5311

So easy for Overseas Visitors – Northfields Station is just seven stops from Heathrow on the Piccadilly Line – or phone your order and let us deliver it to you at the Airport.



TRIO R1000

THIS RECEIVER IS SO ADVANCED, IT MAKES EVERYTHING ELSE OBSOLETE
200KHz-30MHz continuous. Digital Readout. All Mode. Switched Filters. Clock & Timer.
AND ONLY £298 inc. VAT.

For all that's good in Amateur Radio, contact:
LOWE ELECTRONICS LTD., Bentley Bridge, Chesterfield Road, Matlock, Derbyshire. Tel: 0629 2430 or 2817.
For full catalogue, simply send 45p in stamps and request catalogue CPW.

**MAIL
ORDER**

**BREDHURST
AT
ELECTRONICS**

**0444 THE HIGH STREET
400786 HANDCROSS SUSSEX**

**RETAIL
PREMISES
OPEN
MON-SAT 9-5.30**

HF RECEIVERS

Lowe SRX 30	£178.00
Yaesu FRG7	£214.00
Trio R1000	£298.00
Yaesu FRG7000	£372.00

2 METRE FM RECEIVERS

Search 9	£59.00
FDK Scan TM56B (+ scan)	£105.00
Belcom AMR217B (+ scan)	£120.00
Bearcat 220	£241.00

MARINE VHF RECEIVERS

Search 9	£59.00
SR 11 (+ scan)	£87.00
FDK TM56B (+ scan)	£115.00
Bearcat 220	£241.00

AIR BAND RECEIVERS

Waltham W144	£29.95
R 517 (vfo + 3ch)	£49.50
AP12 (12 ch)	£120.00
Bearcat 220	£241.00

ROTATORS (CARR. £2.50)

TRI (TV - FM)	£31.00
Stolle 2050 (Light VHF)	£42.50
AR 30 (Light VHF)	£47.15
9502 Colorator (Med VHF)	£51.00
AR 40 (Large VHF)	£59.80
KR 400 (Med HF)	£105.00
CD 44 (Med HF)	£109.00
Ham 1V (Large HF)	£166.75

HEADPHONES (CARR. 75p)

Trio HS 4	£10.35
Trio HS 5	£21.85

PART EXCHANGE • ACCESS

**THE
ULTIMATE
VHF
RECEIVER**

BEARCAT 220



Have you ever wanted a VHF receiver that will cover all bands with facilities such as scanning, lockout of unwanted signals, programmable memories, priority channel checking etc. etc. etc.?

Well, now there is a set on the market that will do all this and much more. The BEARCAT 220 covers 4M, 2M, aircraft band, marine band, business band and 70cm amongst other frequency bands. It has up to 20 memories which can be programmed from a front keyboard. These can be scanned or locked out from scan as required, and any of them can be set to any frequency in the set's coverage. Normal mode is FM, switching to AM for the aircraft band. It is also possible to search entire bands or frequency segments between selected upper and lower limits.

Specification

Coverage	66-88 Mhz	Power	240v AC or 12v DC
	118-136 Mhz	Antenna	Built in telescopic
	144-148 Mhz	Size	10 1/2" x 3 1/2" x 8"
	148-174 Mhz	Built in speaker	
	420-512 Mhz	Weight	5lbs.

**PRICE
£241.00**

To order any of the above items simply write to the above address or telephone 0444 400786, giving your address or Barclaycard number to ensure same day despatch.

REMEMBER 0444 400786

HF TRANSCEIVERS

Trio 120V	£347.00
Dentron HF 200 A	£399.00
Yaesu FT7B	£430.00
Trio 120S	£432.00
Trio TS 520SE	£437.00
Yaesu FT 101Z	£574.00
Yaesu FT 101ZD	£661.00
Trio TS 820 S	£669.00
Trio 180S (with DFC)	£679.00

2 METRE FM MOBILES

FDK Multi 700EX	£195.00
Trio TR 7625	£246.00
Standard C 8800	£250.00
ICOM IC 255E	£255.00

2 METRE FM HANDHELDS

FDK Palm 11	£99.00
Yaesu FT 202R	£119.00
FDK Palmizer	£149.00
Trio TR 2300	£166.00
Yaesu FT 207R	£199.00
Trio TR 2400	£210.00

2 METRE MULTIMODES

ICOM IC 260E	£369.00
ICOM IC 251E	£475.00
Yaesu FT 225 RD	£575.00
FDK Multi 750	P.O.A.
Trio TR 9000	P.O.A.

POPULAR ACCESSORIES

Jaybeam Antenna	All at Competitive Prices
ASP Mobile Antenna	
Hygain HF Antenna	
Microwave Modules	

BARCLAYCARD • INSTANT H.P.

Table 8. Receiver Intermodulation

3rd Order			
Band MHz	Level for 1 μ V equivalent		
3.7	59		
7.2	57		
14.2	55		
21.2	58		
28.7	65		

2nd Order			
Tune Frequency MHz	Frequency	Frequency	Level for 1 μ V equivalent
3.7	1	2	61dB
28.7	15.0	42.7	70dB

With the Aerial Attenuator in use, the improvement is about 15dB on 3rd Order, and 20dB on 2nd Order.

Table 9. Reciprocal Mixing

An input signal on tune is adjusted in level for a 13dB SINAD ratio. An unwanted signal separated by 10kHz and in the unwanted sideband is increased in level until the SINAD is degraded to 10dB.

Frequency MHz	Level for 3dB degradation dB rel. 1 μ V
3.7	69dB
7.2	60dB
14.2	65dB
21.2	65dB
28.7	66dB

Cross Modulation

At 3.7MHz. A signal with 20dB SINAD is degraded to 17dB SINAD, with 10kHz separation, a 1kHz tone being the wanted signal, and the unwanted signal modulated at 400Hz.

Level for 10% c.m. 75dB μ V

Using the Aerial Attenuator 95dB μ V

On other bands, the cross modulation is not measurable, being masked by the effects due to reciprocal mixing.

Blocking. This is limited by Reciprocal mixing.

CW Filter Selectivity

Bandwidth Hz	Rejection dB
80	3
267	10
600	20
1153	30

Clarifier Range

At 14.000MHz: plus 4.800kHz minus 2.735kHz

At 14.500MHz: plus 3.783kHz minus 2.132kHz

Table 10. Drift

Time from switch on minutes	Frequency Hz
0	14 214 800
5	14 215 001
10	14 215 265
15	14 215 373
20	14 215 567
25	14 215 660
30	14 215 720
35	14 215 773
40	14 215 837
45	14 215 889
50	14 215 932
55	14 216 003
60	14 216 052
65	14 216 097
70	14 216 138

Dial Error

The dial is calibrated in 1kHz increments. When calibrated at the centre of the band (14 200kHz), the dial error did not exceed 500Hz at any point.

mon s.s.b. filter for receive and transmit, quite accurate information on the s.s.b. filter is derived from the transmitter modulation/frequency characteristic. Without making connections inside, it is not easy to actually measure the filter response, and as a fair amount of information can be deduced from the transmitter measurements, and the effectiveness of the filter from the reciprocal mixing measurements, it is not considered worthwhile to attempt these measurements. After all, if the rejection of the filter is 80 or 90dB at 10kHz off tune, it scarcely matters which if reciprocal mixing means that a signal 60dB higher than the wanted one drowns it out with noise!

The final measurements are drift from cold, c.w. filter response, and transmitter key characteristics and clarifier range. The result of all these measurements is a pretty daunting set of figures, most of which can be meaningless without some standards of comparison. However, they can be boiled down fairly easily, and the comments on the results should put them into perspective.

Comments

The results obtained from the FT-7B were, in the reviewers opinion, somewhat disappointing. Working through the results in order, and starting with the transmitter, it can be seen that the output power is around the 45 watt level. This can give a respectable mobile signal, and is about what should be expected from a 100 watt input transmitter. The intermodulation products are reasonably well reduced, while the spurious output levels (including harmonics) are at a level which can only be described as very satisfactory. Indeed, for a mobile rig, these levels are about 20dB lower than is required for interference-free use! The modulation frequency response gives a very good indication of the filter characteristics, and the results are very good when looked at in terms of unwanted sidebands. The out-of-channel radiation is reasonable, but not good enough to meet the usual commercial specifications, and the relative levels can be seen from Fig. 4. The carrier suppression and hum and noise levels are very satisfactory.

In view of the above comments, it may be wondered why the equipment was disappointing. This disappointment lies mainly in the receiver, but one item of the transmitter measurements needs mentioning, and this is the c.w. keying. At 25 bauds (approximately 30 w.p.m.), the distortion of the keying was about 75% when an equal mark-space ratio at the key was used. To reduce the distortion to a reasonable amount it was necessary to reduce the keying speed to about 15 w.p.m., because of the lengthening of the dots. At this speed, however, the signal does not suffer from clicks, although the rounding of the characters accounts for this. To what extent this distortion will effect the readability of the Morse is hard to say, but is unlikely to help, especially at reasonable speeds.

The receiver performance was notable for its extreme sensitivity—so much so that the measurements were repeated because of disbelief. The 10m band sensitivity could be improved, while the 80m performance really requires the attenuator in circuit at all times. The ultimate SINAD is not very good, representing around 5% equivalent distortion. However, the limitation was not distortion, but noise, indicating that the distribution of r.f. gain control could be improved. The a.f. output power is adequate for mobile use—3 watts makes a very loud noise, even overpowering the car noise in a rather old and noisy estate car! The a.g.c. performance is reasonable for signals above the 5 to 10 μ V level, but the threshold seems to be very high—most receivers would give somewhere around a 6dB increase for levels from 1 μ V to 10mV, and so overall, weak signals have a tendency to sound weak. Especially on 10m, the loss of gain is very noticeable.

Receivers using pre-mixed injection and a 5.0–5.5MHz v.f.o. are usually well provided with a number of internal spurious whistles, especially at 21.2MHz, where the 4th harmonic of the v.f.o. is on the tune frequency. The lack of internal spurious is surprising, and laudable, there being only three of them in band. External receiver spurs are quite acceptable, but as to why those appearing on the 10m are at multiples of 100kHz, no explanation can be offered.


Intermodulation is very disappointing. It is interesting that the 10m band, where the sensitivity is falling off, is also where the intermodulation is improving. This suggests that the step-up to the r.f. amplifier is rather less on this band. From a design point of view, the number of stages between the aerial and the main selectivity of the equipment is enough to cause large problems of intermodulation, and this is shown by the results. The 2nd order performance is just as disappointing, and the effects of introducing the aerial attenuator are completely at odds with the effects that are usual and predicted by theory. At signal levels below the point where overload takes place, the reduction of the input signal by 20dB by using the aerial attenuator should require an increase in signals from the generators of 20dB each to produce the same equivalent intermodulation product level. The increase was definitely less than 20dB, and was about 15dB on 3rd order IMD, and 20dB on 2nd order IMD.

It is possible that the switching of the aerial attenuator is responsible for this effect, but this is considered unlikely. A more probable cause is the number of diode switches in the signal path, and the diodes coupled to the aerial output for a.l.c. Nevertheless, a thorough explanation of this effect is difficult to find. Checks with the spectrum analyser show that signals at a level of +90dB μ V can be achieved with an intermodulation ratio of 90dB, so it is felt that the test set up can be considered innocent. However, the general level of intermodulation in the receiver was distinctly poor, and although the lower signals available in a mobile installation may reduce the importance of IMD in the receiver, the results are not very good. From a design point of view, there is just too much gain, and too many stages, between the aerial and the crystal filter. Reciprocal mixing is a very real test of the receiver performance capabilities in a real world of interfering signals, and here again the figures are not outstanding. More surprising is the fact that cross modulation is masked by reciprocal mixing.

There is a definite mathematical relationship between intermodulation and cross modulation, and this relationship is generally found to be borne out in practice, but not in this case. Taken with the intermodulation results, the reviewer suspects that the signal handling capability of the large number of pre-filter stages is insufficient, and that the compression point of the system is too low. The reciprocal mixing is noticeably better on 80m where the injection is not pre-mixed, but it should be noted that on 40m, for example, the noise sidebands were some 77dB down on the wanted signal. On 80m, the ratio was about 90dB, which is very acceptable when using a 6-pole filter. Blocking was not measurable, being well masked by reciprocal mixing—a strange result when considering the IMD performance and compression.

The other parameters—c.w. selectivity, clarifier range, and drift are satisfactory, although the clarifier may be considered by some to have excessive range.

The YC-7B digital readout unit was used at the same time as the equipment. For those desiring digital readout, it is doubtless a useful accessory, but is by no means necessary to be able to get on to frequency with reasonable accuracy—especially as the one tested had a 600Hz error! However, the connecting cable could well be made rather longer, as this was found somewhat annoying in its short length.

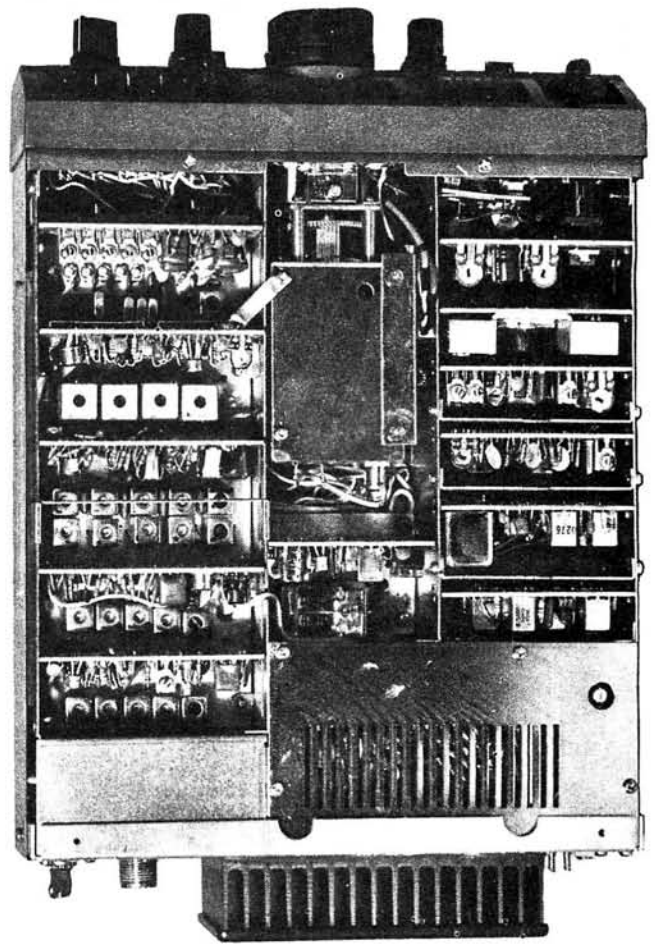

On the Air

The FT-7B was tried mobile, and was carefully set up as per the instruction book. The MIC GAIN was advanced to the point where the output was not rising, and the reports were of high distortion and almost unreadable signals. By reducing the MIC GAIN to the point where a whistle led to a p.a. current about two thirds of that achieved on two-toned test led to acceptable results. However, reports on speech quality were not as complimentary as on other rigs, and reports from stations knowing the reviewer were that the modulation was harsh. The noise blanker made little difference on 80m, but noise blankers are an area where results seem to be more than usually subjective, and the reviewer has been present at tests where one listener, equally experienced, found a major improvement while the reviewer couldn't tell the difference! Further tests then produced the opposite results, so the matter is one for further experiment.

On 80m, the aerial attenuator was vital at night, and on 40m, most of the time. Nevertheless, the number of strange signals that could be identified as due to intermodulation were considered excessive, and the change in noise levels when additional attenuation was used in the aerial lead was educational.

The final points that were found were that the jack sockets for phones and key were the small size, and the provision of standard 0.25in sockets would have been an advantage, although adaptors are apparently supplied normally. The knobs are of convenient size, although the concentric DRIVE and TUNE knobs suffer from mutual undesired mechanical coupling.

continued on page 60 ▶▶▶

BEARCAT 220 FB



£241.50 inc. VAT. Delivery by Securicor

FREQUENCY COVERAGE66 - 88 MHz FM; 118 - 136 MHz AM (Aircraft Band); 144 - 174 MHz FM; 420.45 - 512 MHz FM. This coverage includes the 70 cm; 2m; 4m FM AMATEUR BANDS. To programme this Receiver you simply punch in the frequencies you wish to monitor. To AUTOMATICALLY SEARCH MARINE FREQUENCIES YOU JUST PRESS ONE BUTTON. The Bearcat 220 FB will also AUTOMATICALLY SEARCH the AIRCRAFT BAND.

Power requirements: 240 VAC/12v DC. Accessories included in the price are - Mounting bracket and hardware, DC cord and telescoping antenna.

UK IMPORTERS & DISTRIBUTORS

Please send 25p stamps for details.

ACCESS

★ SALES ★ SERVICE ★

BARCLAYCARD



RADIO SHACK LTD. 188 BROADHURST GARDENS,
LONDON NW6 3AY



Giro Account No. 588 7151 Telephone: 01-624 7174 Cables: Radio Shack, NW6.
Telex: 23718

A GERMAN + WARTIME RECEIVER

Ron HAM

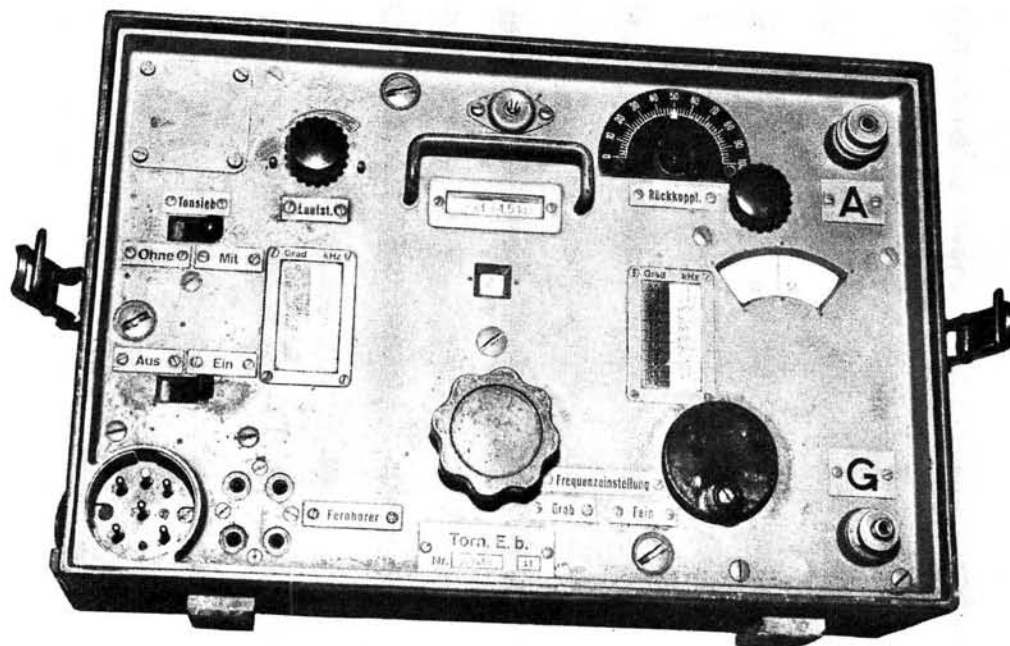


Fig. 1: Telefunken receiver made in 1941 for the German military

Although, after World War II, tons of military radio equipment used by the Allied forces was sold, almost at scrap prices, only a relatively small amount of German equipment was available. Therefore, any of the wireless sets used by the Luftwaffe and the Wehrmacht that appear today are sought after by collectors.

A recent addition to the author's collection is a Telefunken receiver (Fig. 1) in excellent condition, labelled Torn. E. b. and dated, 1941.

Like all military equipment, this set is beautifully engineered and is housed in a strong metal case, with carrying handle and the Eagle and Swastika emblem stamped inside. The complete unit measures 330 x 210 x 222mm, weighs 26lb and covers 96.6 to 7095kHz. The frequency range is divided into eight wavebands by a magnificent turret range selector which is 152mm diameter and occupies the centre of the main chassis (Fig. 2).

After rotation, the selected range is retained by a detent wheel under pressure from a 152mm long, 6-segment leaf spring visible behind the cable harness above the turret in Fig. 2.

There are three sections to each of the eight turret coil assemblies mounted on the rotatable frame, and each one, measuring 146 x 57mm (Fig. 3) is secured to the rotator by four screws and has 10 brass rings about 5mm wide,

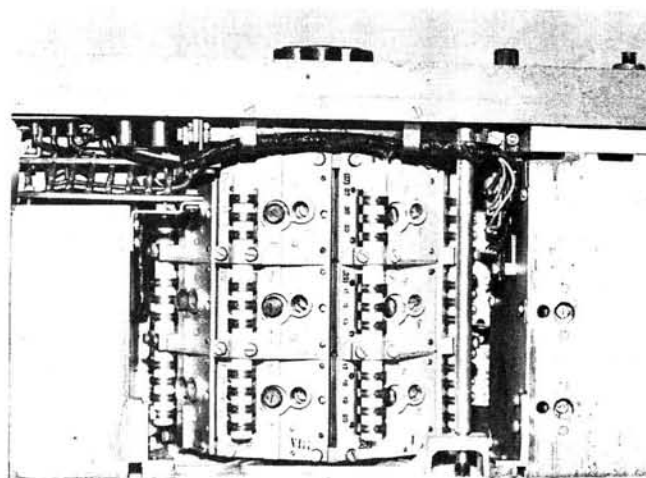


Fig. 2: Underside of the receiver, showing the turret range selector

(A somewhat similar turret, but with four sections to cope with two tuned r.f. stages, frequency changer and local oscillator, was used in the B21B h.f./d.f. ("huff-duff") receiver used by the Royal Navy—Editor).

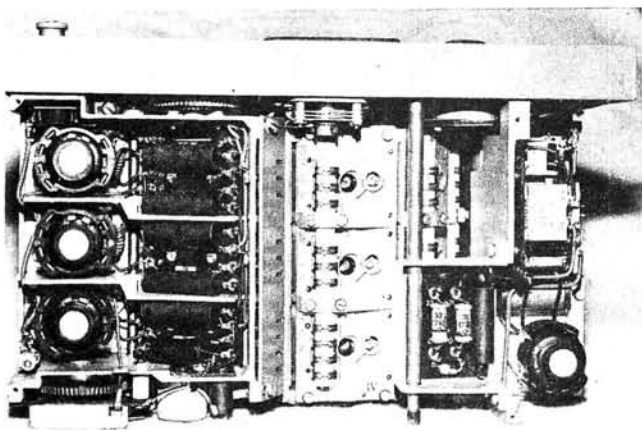


Fig. 3: Top side of the receiver, showing the valves in position and coils about to engage in the contact block on the left

which make contact with the receiver circuitry. The main tuner is built from three separate variable capacitors, each with an 8mm shaft supported by two 22mm ball races and all mounted in a sectionalised diecast box. The large tuning knob, seen on the right in Fig. 1, the ganged capacitors, and the scale marked 0-100 are coupled together by a series of gear wheels to avoid backlash and to give accuracy of tuning.

Although the four RV2P800 valves are themselves screened (Fig. 4), each one plugs into a long metal container with a ceramic insulated contact at the bottom for the pin, and side contacts at the top (Fig. 3), for the other valve connections.

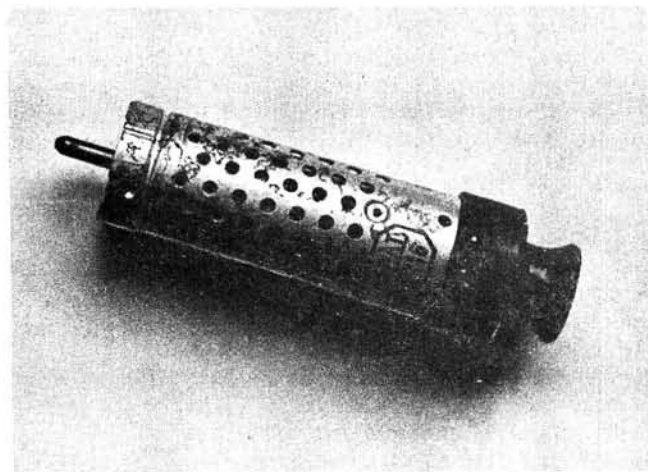


Fig. 4: One of the RV2P800 valves made for the German government by Telefunken

These directly-heated pentode valves, made by Telefunken for the German government, require 1.9 volts at 180mA for the filament, 120 volts on the anode and 80 volts on the screen grid. The set is supplied with power via the 6-pin plug on the left of the front panel (Fig. 1), and the headphones are connected to the four adjacent sockets.


Every part of this set, including the aerial and earth terminals, marked A and G, is very robust and more than adequate for the job to be done. ●

DUAL TRACE UNIT

▶▶▶ continued from page 36

the picture, but if Y1 only is selected, then the Purbeck can be set to Internal trigger thus avoiding this problem. Alternatively a larger version of the waveform under investigation may be available at some other point in the circuit, in which case the Y2 input can be connected to this and the Dual Trace Unit triggered from the Y2 channel. These very high sensitivities are of course mainly of use at audio frequencies, and in these circumstances, triggering stability can be improved by setting the TRIG selector switch of the Dual Trace Unit to LF REJ, thus limiting the bandwidth of the trigger channel. In fact, a simple but useful accessory for limiting the bandwidth of the signal channel itself, with a choice of cut-off frequencies, will be described in a future article.

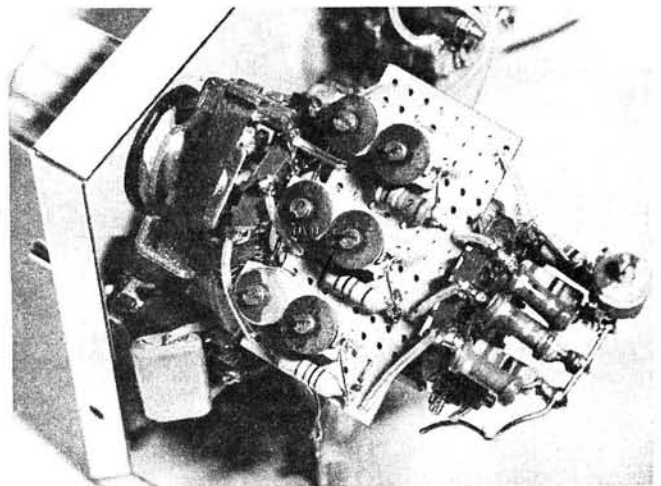Note that when working at these high sensitivities, great attention must be paid to earthing and screening arrangements, otherwise the signal it is desired to view may be swamped with hum pick-up. ●



Close-up detail of the input attenuator for one channel of the Dual Trace Unit. The other attenuator is built in the same way

Components

Several minor errors crept into the components list. R658 appears twice in the circuit diagrams and component overlay. The resistor shown on Fig. 11 as R658 and placed at an angle below C623 and to the top left of IC607 should be 100Ω and is the R658 associated with Fig. 3. The other R658, shown next to C625, is 100kΩ and is the one associated with Fig. 6.


R660 is 7.5kΩ not 1.5kΩ as shown in the caption to Fig. 6.

The twelve tantalum decoupling capacitors should be 47μF 16V not 17μF as shown in the components list. In most instances not all of these will be needed.

Three 4.7nF polyester capacitors are required, C521, 522, 523 and these, as with all components numbered in the 500 series are mounted on the front panel components.

The fourth 22kΩ resistor in the components list should be R659 not R657 and R644 is 47kΩ not 47Ω.

So You Want to Pass the RAE?

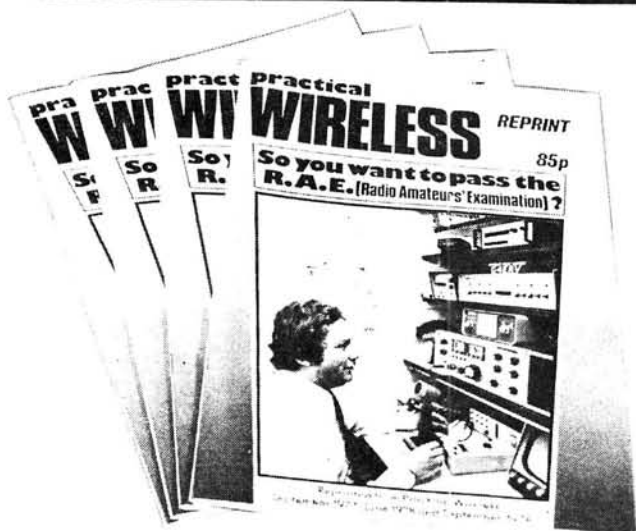

A reprint of the complete series, including details of the new examination format being introduced in 1979, is now available. The reprint costs 85p, including postage and packing to addresses within the United Kingdom.

Order your copy by completing and returning the coupon, together with your remittance, to IPC Magazines Ltd., Post Sales Department, Lavington House, 25 Lavington Street, London SE1 0PF. Please ensure that your name and address are clearly legible.

PRACTICAL WIRELESS—Radio Amateur Examination Reprint

Please send your order and remittance to:

**IPC Magazines Ltd., Post Sales Department,
Lavington House, 25 Lavington Street,
London SE1 0PF**

Please send me . . . copies at 85p each to include postage and packing

I enclose P.O./Cheque No. Value

Remittance must be crossed postal order or cheque (name and address on back please) and made payable to IPC MAGAZINES LTD

NAME
(BLOCK LETTERS)

ADDRESS
(BLOCK LETTERS)

.....

.....

..... Post Code

Remittances with overseas orders must be sufficient to cover despatch by sea or air mail as required. Payable by International Money Order only

Company registered in England. Regd. No. 53626

A subsidiary of Reed International Limited

Cut round dotted line

FT-7B REVIEW

▶▶▶continued from page 56

The handbook is remarkably detailed, and contains the necessary information for servicing the equipment. However, as mentioned earlier, without the card extenders, maintenance is very difficult, if not impossible, so the information may not be of as much help as at first envisaged. A large amount (for an amateur) of test equipment is required for alignment, including r.f. and a.f. signal generators, an oscilloscope, valve voltmeter and sweep generator. Possibly the skilled technician could improvise for many measurements, but it seems a pity that the bandpass filters could not be set up by a method not requiring a sweeper—for example, by Dishal's method. However, the famous Japanese English clangers seem noticeable by their absence, although there may be some that were overlooked.

The specifications given in the handbook are the usual meaningless ones. For example, the transmitter specifications list carrier suppression, sideband suppression, spurious and distortion products as being so many dB down, without saying whether the measurements are relative to p.e.p. or one tone of a two-tone signal, which give answers different by 6dB! Antenna output impedance is even more meaningless—the output impedance of a transmitter, like any power generator, should be as low as possible, and the correct term is design load impedance, which, it should be noticed, is not always the optimum load impedance achieved in practice! The receiver specification suffers similarly when it talks about audio output impedance, while the sensitivity is not defined as either e.m.f. or p.d., which again gives a 6dB difference. Spurious responses, other than image and i.f. rejection, with multiple signal tests see the handbook being extremely reticent, although this is unfortunately not uncommon.

Most of the semiconductor devices can either be replaced with near equivalents, or are readily obtainable European or American types, with the exception of two Toshiba i.c.s. For equipment destined for export to the USA or Europe, the use of more readily available i.c.s in these positions would possibly be welcome, and there is no shortage of suitable devices. This is however a fairly minor point, unless one has a rig out of use while spares are obtained. Apart from these two i.c.s and the r.f. power devices, however, the average largish town with some sort of electronic components shop could probably provide replacement devices for all of the semiconductors in the set from stock, which is more than can be said for many equipments!

Summing up, the results obtained from the transmitter are very good, with the exception of the speech quality and c.w. keying, while the reviewer rates the receiver performance as definitely very poor. The handbook is good, but the maintainability terrible, and Joe Q. Average Ham relies on the dealer with a well equipped workshop and well qualified staff for maintenance. A previously published review on the FT-7 did not investigate the receiver performance in any detail, and although there are a number of amateurs who can be heard praising the equipment very highly, there are a remarkable number of sets available second hand.

The reviewer's opinion is thus somewhat in conflict with many others, but it is a regrettable fact that analysis of receiver performance on the air is by no means as easy as some amateurs would like to believe.

Costing £431.25 including VAT (plus £69.00 for the YC-7B digital readout), the FT-7B reviewed was kindly loaned by South Midlands Communications Limited, S.M. House, Osborne Road, Totton, Southampton SO4 4DN. Tel: 0703 867333, and we would like to thank them for their invaluable assistance in this respect.



by Eric Dowdeswell G4AR

With several h.f. communications receivers now on the market intended for amateur radio listening, the potential customer will try to evaluate their various facilities and equate them to the cost, trying, naturally, to get the best value for money. If one is sufficiently knowledgeable the best way is to list the requirements for an acceptable receiver and see how the proposed set matches up to the list.

At the moment some of the features, usually listed under the assinine heading of "state-of-the-art technology" are of doubtful value and, indeed, some run contrary to good receiver design. But, first of all, let us look at the receiver used by **Bill Rendell** of Truro in Cornwall, who has an old valved Heathkit AR3 to which he has added numerous bits and pieces until he has, at the last count, some 18 different controls! But, he is able to copy s.s.b. and c.w. signals at signal levels which, I venture to suggest, cannot even be heard on some present-day receivers.

Why should this be so? Because every circuit on the r.f. side is separately tuned "on the nose" for the particular frequency concerned, by having fine tuning on the individual sections of the ganged tuning capacitor. Thus, there is maximum rejection of all signals on both sides of the required frequency and cross modulation effects are at a minimum.

I am not going to suggest that we all make carbon copies of the Rendell Wonder but the basic principles of good receiver design ought to be followed in commercially produced sets. Regretfully, this does not always happen. Certain controls and functions are sometimes omitted, ostensibly to make our lives easier but, in reality, to make the life of the manufacturer simpler, and these changes are thrust upon us as "progress".

Years ago the output stage of an amateur transmitter had two controls, tuning and loading, enabling the stage to be matched to a quite wide range of aerial feed impedances. The loading capacitor was then replaced by a fixed one, much cheaper, for a fixed output impedance of 50 ohms, immediately reducing the versatility of the stage. Now it is common to replace the tuning control too, replacing it with a fixed tuned band-pass filter that offers much reduced rejection of unwanted harmonics and spurs that now get radiated.

This band-pass filter now finds itself at the front end of

receivers, switched in automatically with operation of the band switch in the r.f. and mixer stages. Consequently every signal within the passband is being applied to the transistors or devices in these stages and cross modulation is inevitable, and some of those signals can be pretty hefty, running into many millivolts. Weak signals stand little chance of being resolved even if they can be heard.

The cross modulation problem, having been created, is ostensibly overcome by fitting an "r.f. attenuator" which, while reducing the input level of strong signals, also reduces the strength of the wanted weak one! The attenuator will improve the situation in some circumstances but why create the problem in the first place? The separate "pre-selector" tuning used on receivers for a long time past is infinitely superior to the band-pass filter idea, and when combined with separate r.f. and i.f. gain controls, offers the best possible chance of resolving that weak DX.

Receiver manufacturers naturally have to use all reasonable marketing techniques to further the sale of their products, hence the continuous flow of "innovations" which may sometimes be plain gimmicks or old ideas rejuvenated under another title. But it does seem wrong when the performance of a receiver suffers in the process.

How lovely it would be if a manufacturer could produce a receiver that met the requirements of good design at a reasonable price, leaving out all the fancy bits, and using a valve in a particular stage if it can be shown to perform better there than its solid-state counterpart. It would mean a few more controls on the front panel but we would, at least, get back to a receiver that did the job it is supposed to do. Namely, produce a signal with a minimum of noise and free of interference from other signals.

General Notes

In West Wickham, Kent, **John Dainty** is wisely spending more time swotting for his RAE than listening on his FRG-7. He is thinking of putting up a G5RV aerial which will serve as an all-band job when he gets his ticket and will perform well in the meantime. John had occasion to take his FRG-7 with him on jaunts to East Anglia and Newcastle, only to find the cold of the QTH's affecting the receiver to the extent that he could not resolve s.s.b., not an entirely unknown trouble with this set, he says. I suppose one could fix in a small heater to keep the temperature more or less constant on such occasions. No such troubles with valved sets! (*Not my experience! Ed.*)

Jim Rowland (Tetbury, Glos) says he is way out in the country where man-made noise, electrical that is, is at a very low level so he promptly noticed that something was wrong recently when an electric fence started to give trouble. Seemed the 6V system uses a transistorised unit run from dry batteries and someone decided it would be economical to use a 12V car battery! All was well, for-

tunately, when 6V was applied again. Jim comments that some cows seem to enjoy the "kicks" they get from the fence.

D. A. Day writes from 46A Seaside, Eastbourne, Sussex, to ask if anyone has any info on the old Hallcrafters Super Skyrider, as he has one he'd like to get back into working order. A circuit diagram or service information would be most welcome. In Aisby, near Grantham, Lincs, **Arthur White** is also keen on putting vintage equipment to rights, but at the moment would like any info on the Cossor 339A 'scope so if you can help I will gladly pass the gen on.

While on the subject of 'scopes, **F. Dickenson**, 5 Farmfields, Sanderstead, Surrey is also seeking assistance, on the Tektronix valved 561A oscilloscope where a manual would be of great help. In both cases cost and postage would be refunded with pleasure. Final appeal this month is from **Ian Haggart** G3JQL, 22 Alnwick Road, Newton Hall, Durham, who'd like to beg, borrow or steal a manual on the Eddystone S750 receiver. Ian, to use his own words, "has returned to the fold" after being QRT for eight years and asks "where have all the home-built stations gone"? Every station describes its equipment with a string of numbers! Too true Ian, and if you don't know what they mean an inferiority complex can develop! Ian likes the increased amateur radio content of *PW* compared to a few years ago. Don't we all!

Top to Ten

Dave Coggins in Knutsford, Cheshire, has parted with his old faithful DX160 and bought an FRG-7 so it's a log for all bands from 10 to 160m and very nice too. I do notice that a few readers with this set seem to ignore the fact that there are bands other than 20m so do try them. They can be a pleasant surprise if you can get on at the right time. With a 66ft aerial and a.t.u. Dave heard VP2MCK and SAX plus VU2USE on 10m, J3AAG (Grenada), VP1KS and 3D6BP on 15m, 40m produced AA7A/VP2A on Antigua and J6LOO on St Lucia and a rare one 5T5JW. Down in frequency and it was VP2MCK, again, and OX5AP on 80m with top band 160m revealing UQ2GBU, N4ASV and W8JI in an early morning session. Later Dave mentions VK2AVA most evenings around 1900 on 3680kHz.

Just to prove what I was saying earlier about **Bill Rendell** of Truro he found XE1UF on 40m, J3AH on Grenada, KG6RN and TN8AJ on 20m, the latter being a seldom heard call, while 15m came up with FG7AR/FS7 and J6LOO on St Lucia. Bill didn't knock off his task of hearing VK/ZL on successive days until he'd reached the 201 mark but it was dodgy on some days with stalwart VK3MO always there in the end, sometimes better than Radio Australia! Ha, ha! that means you sometimes sneak on to the BC bands! Shame on you.

Our RTTY king **Dennis Sheppard** (Sheerness, Kent) has been off work and feeling pretty grim to the extent that he has not been listening all that much. That must be bad so get well soon OM. Latest aerial is a 66ft top with feeder from the centre so being a top-loaded vertical it ought to be fine for the low angle DX stuff. 10m proved best this time with EA3BQQ, LU4EGE, VE1TX, W5ZNN, WD8IUP, YO2IS, 4U1ITU and 9H1ET all on RTTY with just JA1ACB on 15m. SSB reported includes HP3FL and 3V8AA on 80m plus VP9BO and W2HCW on 160m.

Allan Stevens of Crowthorne, Berkshire, was pretty disgusted to hear A7XA in Qatar say that he was using 30kW, yes kilowatts! I feel it was someone playing around with a BC transmitter in his time off rather than some exasperated DXer trying to work that final, final country! Pick of the bunch for Allan was VP9JR on 15m, 6W8FZ

on 20m and EA8AK and JA9UX on 40m, all s.s.b. Allan, like many more around the country, is champing on the bit waiting for the December RAE results!

Arthur White, mentioned previously, is not satisfied with his 265ft long wire, 80m inverted dipole and dipoles for 15, 20 and 40m but wants to put up a Beverage about a 1000ft long! He has a field adjoining his QTH and hopes the birds won't mind! They will welcome the extra perch OM! But seriously, I too would welcome information on a practical Beverage aerial with details of matching transformers, etc. Plenty of basic circuits in the books but nothing practical. Any ideas, anyone, of a source of info?

15-year-old **Sean Richards** of Maidenhead, Berkshire, has been listening for the last six months and decided to stick to the amateur bands after joining the Maidenhead and District ARC. He has an SX28 plus a 66ft wire. RAE is taking up some of his time and, optimistically, he is talking of taking it in May! I'm glad to hear that he has no interest in a G8 call and will take the code test as soon as possible. Quite a programme, but good luck all the same, Sean. Working down from 80m where he heard CN8AK, EA6CP, EA8FG, FM7WS, G2ACK/VP2M, JA6IEF, YV3AZL, ZS6HP, 4X4VL, 5B4CR and 7X4MO, 40m provided EA8JS and ZL4BO. On 20m it was 6W8GC, 9Y4VP, FM7BUL and VP2AZG with C6ANU, FR7RC, FM7AX, VQ9PC (QSL K9KLR), VP8SB, ZD7SO, 3B8CF, 3C1AC (QSL EA7FY) on 15m. Ten metres came up with AP2P, EA9GD, FG7AR/FS7, HP7XRK and K1CO/PJ7.

Club Time

Propagation is the subject of a talk by G3LEQ at the **Bury RS**, G3BRS, on March 11 at the Mosses Youth Centre, Cecil St., Bury, while one to note for next month is a TVI Seminar on April 8. These meetings on second Tuesdays are interspersed with informal meetings on the remaining Tuesdays where code practice and construction projects are the order of the day. Newly-elected PRO for the society Chris Marcroft says membership is now over 100 for the first time. Write him at 24 Lancaster Avenue, Ramsbottom, Bury or try Ramsbottom 2168.

Liverpool and District ARS also meets on Tuesdays, at the Conservative Rooms, Church Road, Wavergate at 8pm with a bring and buy sale on March 11, More Magic with G3SIW on the 18th and a constructional contest on the 25th. Thursdays 8.30pm sees G3AHD, the club station, on 144-250MHz with slow Morse practice. More from: Al Neilson G4CVZ, 78 Ackers Hall Avenue, Liverpool or 051-220 5470 after 6pm.

Northern Heights ARS will be glad to see you at 8pm any Wednesday at the Bradshaw Tavern, Illingworth, Halifax, with March 12 being construction contest night and the 26th devoted to microcomputer basics by three of the members G3TQA, G8CHN and G8SDE. NHARS News is a well produced newsletter and it is a pity that others do not follow this example. Believe it or not some newsletters I get aren't even readable! No information on where the club meets or its officers or, at least, the secretary's QTH. A pity, because if a job is to be done then it is worth doing well and it doesn't take a lot of effort to see that copies are readable and to scrap them if they are not.

The Watling Community Association, 145 Orange Hill Road, Burnt Oak, Edgware, Middx is the venue for the **Edgware and District RS** on March 13, when G3TDR talks on s.s.b. transceiver construction and that ought to draw the crowds. On the 27th the club station G3ASR will be on the air. Write to: Howard Drury G4HMD, 39 Wemborough Road, Stanmore, Middx for more info.

Ken Crouch G8KEN, chairman of the **Dover RC** and

NEW! TRIO R1000

UNBEATABLE PERFORMANCE
AT AN UNBEATABLE PRICE

£298 24 hour delivery
inc. vat. available

"It beats anything under £1000!"




0.2MHz-30MHz in 30 Bands

LOWE SRX 30

COMMUNICATIONS RECEIVER

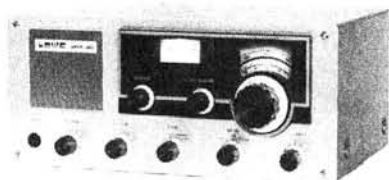24 hour Securicor delivery **£178** inc. vat.



0.5MHz-30MHz 30 Bands

FRG7 **£210** inc. vat.
24 hour delivery



0.5MHz-30MHz 30 bands

WHY BUY FROM US?

Its pretty well known amongst short wave listeners around the World that we specialise in communications receivers. Our workshops are staffed by enthusiasts and licensed radio amateurs, and each receiver is given a thorough pre-delivery check before despatch (yes a few do fail). Once we are satisfied, your receiver is carefully packed and despatched by Securicor for direct delivery to your door the following day. Mail order customers need simply quote us their Barclaycard or Access numbers or alternatively send us a cheque or postal order.

WATERS & STANTON ELECTRONICS

18-20 MAIN ROAD, HOCKLEY ESSEX
Tel: HOCKLEY (03704) 6835.

Callers welcome Mon-Sat 9-5.30 E.C. Wed. 1pm.

2 LOOK! SUPERB NEW KITS!



C300/ES200

high performance electronic ignition, to add power, economy, reliability, sustained smooth peak performance, instant all weather starting, to your car.

Surefire has sold in its thousands in ready made form from big name accessory firms, but it is now available in quality kit form to fit all vehicles with coil ignition up to 8 cylinders.

ES200. A high performance inductive discharge ignition incorporating a power integrated circuit (special selection); electronic variable dwell circuit (maximises spark energy at all speeds); pulse processor (overcomes contact breaker problems). Coil governor (protects coil). Long burn output. Negative earth only. Compatible with all rev. counters.

C300. In it's ready built form (C3000) it came top of all systems tested by an independent national authority July '79. A high energy capacitive discharge ignition incorporating a high output short circuit proof inverter, top grade Swedish output capacitor, pulse processor circuit, transient overload protection. Fast rise bidirectional output ideal for fuel injection, sports carburation, oily engines. Compatible with most rev. counters. (Low cost adaptors available for rare cases. Application list enclosed with each kit. Note: Vehicles with Smiths/Jaeger rev. counters code RVI on dial will require adaptor type TCI).

What's in the kits. Surefire's own precision anodised aluminium extruded case. P.C. mounted security changeover switch, static timing light. Special selection Motorola semi-conductors. Capacitors, resistors etc. selected after 5 years experience. Glass fibre pcb, solder, complete down to last washer. Fully illustrated comprehensive instructions and full technical back up service.



Suretron Systems (UK) Ltd. Dept. PW1
Piccadilly Place, London Rd., Bath BA1 6PW. Tel: Bath (0225) 23194

Name

Address

Phone order with Access: Barclaycard
VAT and P & P inc.

Quantity
required

ES200: Neg	£13.95	£11.95	
C300: Pos	£17.95	£15.95	
C300: Neg	£17.95	£15.95	
Tacho Adapt. TCI		£3.90	

I enclose
chq/PO's
£
Chq No



THE NEW K.D.K.



The KDK FM2025E is a 12V DC two-metre FM transceiver suitable for mobile or base station use. Although packed with more features than any previous model, operation has been made even easier, by the use of a 'custom built' microprocessor controller.

A digital frequency synthesizer provides full band coverage in 12.5KHz or 25KHz steps selectable by a slide switch. 'Single knob' frequency selection is provided by an optically coupled encoder (30 PPR) plus a dialling speed switch that increases the tuning steps tenfold to facilitate the selection of widely spaced frequencies.

An electronic memory, with on board Ni-Cd back up, provides 10 simplex (plus standard ± 600 KHz shift) and/or 5 semi duplex channels for the ten slot, two group store. This makes the 2025 as easy to use mobile as a crystal controlled transceiver. One memory slot is semi-dedicated to 'priority' use, and is programmable even when the 2025 transceiver is controlled by the dial.

The 2025 embodies the best non-lockout scanner available. It seeks occupied or empty channels and a flick switch hold facility enables immediate transmission on a desired frequency. The scanner functions on both memory channels and across any selected portion of the band, scan limits are defined by two of the memory channels.

2025 2m SYNTHESIZED TRANSCEIVER

- ★ Custom design micro control
- ★ 25KHz and 12.5KHz steps!!
- ★ 'Instant QSY', 10X rate button
- ★ 25 Watts of reliable RF output
- ★ Band scan between any limits
- ★ 10 write-in memory channels
- ★ Memory scanning with hold
- ★ Standard ± 600 KHz or any split

Dual gate UHF MOS.FETS are used in the RF and mixer to provide superior intermodulation characteristics with high sensitivity. This performance is maintained over the band by automatic varicap electronic tuning.

A monolithic crystal filter in the first IF and a commercial quality 15-pole ceramic filter in the second IF provides extremely sharp selectivity. The adoption of the latest one-chip multifunction IC for all the second conversion circuitry enhances receiver performance and reliability.

The single conversion transmitter uses a balanced mixer and a VCO on the signal frequency (direct modulated for superb FM) hybrid power module to 25W (or 3W) RF output. The PA is impervious to breakdowns under infinite VSWR and produces with the LPF a substantially spurious free signal.

All necessary control function instructions are programmed into the microprocessor itself. By re-arranging a diode matrix, the lower frequency transceive limit, the high frequency receive limit and the high frequency transmit limit may be altered to allow for changes of band plan or location after purchase of the transceiver.

Switchable autotone burst, RF attenuator, squelch, microphone, microphone clip, power lead, mounting bracket, hand book are, of course, part of the package.

Call SMC for further details and demonstration.

£250 inc. VAT at 15%
(£217.39 + VAT)

SEE ONE TODAY!

6 GOOD REASONS FOR DEALING WITH SMC

1. We only sell equipment we can honestly recommend.
2. 22 years of communications experience.
3. Direct access to manufacturers.
4. Probably the best equipped service facility in the U.K.
5. Over £10,000 worth of spares in stock.
6. Management and engineers are all licensed amateurs.



SOUTH MIDLANDS COMMUNICATIONS LIMITED

S. M. HOUSE, OSBORNE ROAD, TOTTON, SOUTHAMPTON, SO4 4DN, ENGLAND
Tel: Totton (0703) 867333, Telex: 477351 SMCMM G, Telegram: "Aerial" Southampton

S.M.C. (Jack Tweedy) LTD

Roger Baines, G3YBO
79 Chatsworth Road,
Chesterfield, Derbyshire
Chesterfield (0246) 34982
9-6: Tuesday-Saturday

NORTHERN (Leeds) BRANCH

Colin Thomas, G3PSM
257 Otley Road,
Leeds 16, Yorkshire.
Leeds (0532) 782326
9-5: Mon-Wed & Fri-Sat.

S.M.C. (Jack Tweedy) LTD

Jack Tweedy, G3ZY
150 Hornecastle Road,
Woodhall Spa, Lincolnshire
Woodhall Spa (0526) 52793
9-5: Tuesday-Sat (+ appointments)



G3ZUL	Brian	Stourbridge (03843) 5917	GW3TMP	Howarth Pontybodkin (035287) 846/324	GM8GEC	Jack	Edinburgh	(031665) 2420
GW4GSW	Alan	Swansea (0792) 24140	G13KDR	John Bangor (0247) 55162	G13WWY	Mervyn	Tandragee	(0762) 84056

the RSGB's SE Kent area rep. keeps me in touch with events in the club, like G8EGT on test equipment on March 12, activity night on 20m with the club station G3YMD on the 19th, and constructional competition judging on the 26th. The club station is also available at other times. Contact: Ken Crouch, 14 Victoria Road, Capel-le-Ferne, Folkestone, Kent, or ring 55241.

Two big events for the **Ipswich RC** in 1979 were the club callign G4IRC, for which they had obviously been waiting, and the first club magazine, and a fine effort it is too. QUA (have you any news?) is an 18-page job and one only hopes they can keep it up. It even includes info on other clubs in the area! March 12 has a talk from the PO Radio Interference department and on the 26th it's RAE question night with answers to candidates' problems. Meetings second and last Wednesday of the month during school term, at Handford House, Ranelagh Road, Ipswich but ring: Jack Tothill G4IFF, 76 Fircroft Road, Ipswich on 0473 44047.

Ian Daniels has taken it upon himself to talk of home-made colour TV cameras and 10GHz links on March 12 for the **West Kent ARS** at the Adult Education Centre, Monson Road, Tunbridge Wells, where they meet alternate Tuesdays with informal meetings at the Drill Hall, Victoria Road. You'll have to work it out from March 12! Or write/ring: Brian Castle G4DYF, 6 Pinewood Avenue, Sevenoaks, tel 0732 56708.

North of the border it is the **West of Scotland RS GM4AGG** that should interest readers in the Glasgow area. Meet every Friday at 22 Robertson, Glasgow where gear for h.f. and v.h.f. is in operation, but contact: Ian McGarvie, 3 Kelso Avenue, Paisley PA2 9JE.

Briefly

Lincoln SW Club, second and fourth Wednesday, 8pm, Lincoln Corporation Social Club, Waterside South. Mike Wells G8PNU, 4 Horner Close, Brant Road, Lincoln. **Stevenage and District ARS**, first and third Thursdays, Senior Staff Canteen, British Aerospace Site B, Gunnels Wood Road, Stevenage at 8.15pm. Peter Byrne G8MCV, 21 High Plash, Stevenage, 0438 64624. **St. Helens and District ARC**, Wednesday evenings YWCA HQ, 107 Corporation Street. St Helens at 7.45pm as there is code practice before getting down to business. Try Paul Gaskell G8PQD, 131 Greenfield Road, St.H. or ring 25472. Finally, **Maidenhead and District ARC** first Thursday and third Tuesday, 7.45pm, Red Cross Centre, The Crescent, M'head or contact John Patrick G3TWG, Bedford Lodge, Camden Place, Bourne End, Bucks or Bourne End 25275.

Do write to me direct and not via *PW*. My address is in the box in *On the Air* every month.

**PLEASE MENTION
PRACTICAL WIRELESS
WHEN REPLYING
TO ADVERTISEMENTS**



Bind it

It's so easy and tidy with the Easibind binder to file your copies away. Each binder is designed to hold approximately 12 issues and is attractively bound and blocked with the PRACTICAL WIRELESS logo. Gold Letra-set supplied for self blocking of volume numbers and years.

Price £4.10 including postage, packing and VAT. Why not place your order now and send the completed coupon below with remittance to: IPC Magazines Ltd., Post Sales Dept., Lavington House, 25 Lavington Street, London SE1 0PF.

it's easy with **EASIBIND**

Order form PRACTICAL WIRELESS

I enclose P.O./cheque value
for.....binders

Years required
(BLOCK LETTERS PLEASE)

Name

Address

Date




MEDIUM WAVE DX

by Charles Molloy G8BUS

The Regional Radio Conference of the Western Hemisphere, which meets in Buenos Aires this spring, has a proposal on its agenda that could have far-reaching consequences for the medium wave DXer. The United States is pressing for 9kHz separation between stations, in line with the Geneva Plan which applies to the rest of the world. If adopted, it will mean that the DX slots that currently exist in between European stations will disappear, since the m.w. band will be divided into a number of world-wide channels. Not a bad idea from some points of view but it would certainly make medium-wave DXing even more difficult than it is at the moment.

Reception Reports

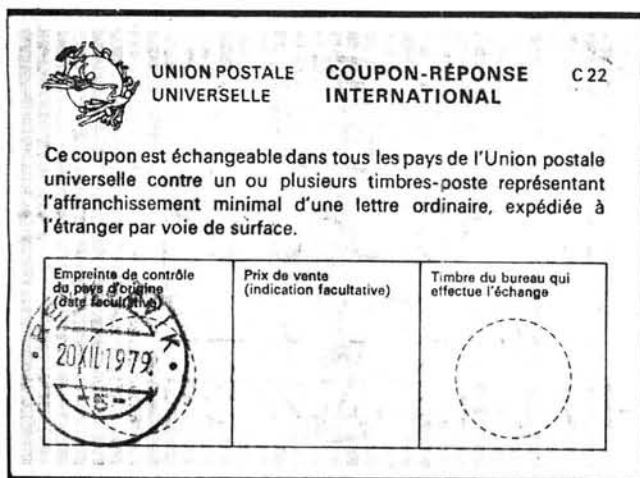"Can you tell me how to obtain QSL cards from the stations I log—" is a question often asked. Writing to a long-or medium-wave station requires quite a different approach than on the short-waves. You are outside the



service area of your DX and consequently you are not one of that station's intended listeners. So always send return postage, either unused postage stamps of the country concerned or an International Reply Coupon obtainable from main post offices for 25p each. The one illustrated was issued in Reykjavik and sent to me by a *PW* reader in Iceland.

Since you are relying on goodwill for a reply then write a more personalised report than usual. Tell the station your hobby is DXing, that you are using a — receiver and give the date and time and some programme details so that they can confirm that you did actually receive them. Ask for a verification of reception and if you receive one from a distant station then write back and thank them for it. An airletter form is not expensive and you will be enhancing the reputation of the hobby among m.w. broadcasters. The addresses of most stations are to be found in the *World Radio and TV Handbook* which had full page adverts in the January and February issues of *PW*.

Beginners' Corner

West Africa is not too difficult to pick up on the medium waves. Tune to 765kHz and when the French speaking station (Sottens in Switzerland) signs off, usually around 2300, then Radio Senegal in Dakar should be audible. It transmits on this channel well into the night and can easily be recognised by its African music, drums and singing. The station announcements are in French as well as in local languages and you will get a QSL if you send

RADIO - SÉNÉGAL
B. P. 1765 DAKAR (Sénégal)



them an IRC along with the reception report. The address is Radio Senegal, Boîte Postal 1765 Dakar, Senegal.

Now tune to 702kHz and at 2330 you should hear more African style music and singing until 2350 when the programme changes to readings from the Koran prior to close down at midnight. You are listening to Sebaa Aioun in Morocco which carries the Berber programmes of Radiodiffusion Television Marocaine, whose address is Rue el Brihi, Rabat, Morocco.

I have picked up Dakar and Sebaa Aioun with my Vega 204 (which is an earlier version of the 206) using its internal aerial, so both stations should be audible on most receivers. Remember the slow cyclic fading that is characteristic of a DX signal on the medium waves. It lasts a minute or two and is quite regular so it is very easy to miss DX if you only pause momentarily on a frequency.

Ougadougou

If you have been successful in picking up Radio Senegal then why not try for something a little more difficult? Tune down to 747kHz. The Dutch station on this channel closes down at 2315 and Radio Sofia goes off at 2330 leaving the frequency clear for DX. You may then pick up a weakish signal from the 100kW transmitter at Ougadougou in Upper Volta, a country located inland between Ghana and Mauretania. It is on the air until midnight, usually with African music. The announcements are in French, the slogan is "La Voix de la Renouveau" and the address for reports is B.P. 7029, Ougadougou, Upper Volta. This station QSLs if you send an IRC along with your report.

Ougadougou comes in quite well when I use the BRT400 and loop and I did once manage to hear it on the Vega 204 though not strongly enough to resolve it. There are times though when it is not audible at all, but then this is real DX and you have to be patient and persistent on the medium waves.

Filters

Reader **J. Radford** is puzzled by the different types of filter that are available, and he wonders if there is any literature that covers the subject. Try the *ARRL Handbook* but a few examples may help.

A 2MHz high-pass filter attenuates signals below 2MHz but allows frequencies above 2MHz to pass through it. A 2MHz low-pass filter does the opposite, it passes frequencies below 2MHz and would be useful between aerial and receiver when DXing on the medium waves. A band-pass filter allows through frequencies within its passband. One covering 463kHz to 467kHz would make a good 465kHz i.f. transformer with a passband of 4kHz.

A crystal filter uses one or more quartz crystals as resonators while a ceramic filter is a piezoelectric device that is used these days in place of the traditional i.f. transformer. The term mechanical filter is not a misnomer. The r.f. signals are actually converted into mechanical vibration in metallic discs and after passing through a number of them the mechanical vibrations are reconverted into electric signals. A passband with steep sides is the result.

Readers' Letters

A new navigation beacon has appeared on the medium waves. **Geoff Halligay** (Hitchin, Herts) writes to say that "WCO" on 730kHz is located near Aylesbury, Bucks. Geoff first heard WCO while listening for the new BBC Radio 4 relay for the London area on 720kHz which is located at Lots Road Power station in Chelsea. The Radio


Free Europe jammers operate on 719kHz which makes reception rather difficult at Geoff's QTH.

Local Radio DXing interests **John Radford** of Nottingham who used his FRG-7 and 65ft random wire (indoor) to pull in 18 local stations including Manx Radio IOM on 1368kHz, Radio Blackburn on 855 and R. Merseyside on 1484. **J. W. Boyd**, Kaitaia, New Zealand is building the *PW* loop to try to eliminate QRM from Australia. (I wish I had QRM from Australia!)

From Birmingham comes an interesting letter from **John Dennis Court** who uses a Vega 206 which he reckons is far superior to any transistor Rx he has used. DX heard included CJYQ in St John's Newfoundland on 930kHz and WINS in New York City on 1010. I do not have the address of the Volmet station you ask about John and it is, I suspect, illegal to listen to it anyway.

North American DX

Two useful logs of North American DX have been received. **A. C. Jacklin** managed to pick up 12 North Americans last December using his Realistic DX160 and 60ft loft aerial, the best of them being WCB in New York City on 880kHz, WTOP Washington DC on 1500, WITS in Boston on 1510, WQXR NYC on 1560 and CKLM Laval in Quebec on 1570, all heard between 0000 and 0300. Yes, the unidentified on 940 is most likely to be CBM in Montreal. Reader **D. R. Mayhew** uses a portable receiver (type not mentioned) at Yapton in Sussex coupled to a 40 inch loop. He reports hearing CFRB on 1010 and CHUM on 1050, both stations being in Toronto, plus WABC on 770 and WHN on 1050 both in NYC. A number of Latin Americans were also logged including Radio Oriental Montevideo in Uruguay on 770, La Voz de Mexico on 730 and WLTV, the missionary station in Puerto Rico on 1370kHz. All heard between midnight and 0400.

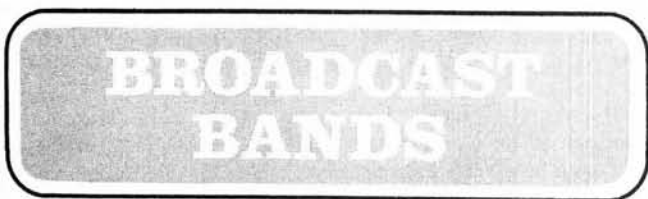

SHORT-WAVE BROADCASTS

by **Charles Molloy G8BUS**

The inexperienced short wave listener (s.w.l.) may wonder how it is that DX is ever heard at all amid the powerhouses, jamming, interference, etc., that is prevalent on the international broadcast bands today. The answer is of course that it depends on which band and what time of day you listen, whether any DX will be heard.

The high frequency bands, i.e. 13 metres (21MHz), 16m (17MHz) and 19m (15MHz) only propagate radio waves when the path between transmitter (Tx) and receiver (Rx), or most of it, is in daylight. If you listen at sunrise you will have a path of daylight to the east for DXing and one of darkness towards the west which will eliminate interference (QRM) from that direction.

Sunrise on the h.f. bands is the time to listen for Japan, India, Pakistan, Sri Lanka, Australia and New Zealand. Start DXing a couple of hours before sunrise, since the path opens up when the sun's radiation strikes the ionosphere some 2000km to the east of the UK. If you want to hear something exotic then listen on 15 170kHz at

0800 on a Sunday for Radio Tahiti. Try also on 11 825 kHz on the 25 metre band (11MHz). The interval signal is the Tahitian flute plus drums and reception is quite good in spite of the distance and low transmitter power which is only 20kW. Announcements are in French.

Radio New Zealand

A number of readers have tried without success to pick up RNZ in the UK. Certainly the stations are only 7.5kW and are not beamed to Europe which doesn't help much, but the main reason for failure is, I suspect, listening at the wrong time of day. Although reception of RNZ has been reported at all hours of day it is in the early morning that success is most likely.

Retired reader **George Lee** of Osset in West Yorkshire has rigged up an HRO receiver at his bedside. When used with a 75ft long wire it picked up RNZ on three successive Sunday mornings recently on 15 345kHz and also on December 9 on 17 860kHz. Exact times were not given. **Bryan Roberston** (Oxford) also heard RNZ on December 9 on 17 860 at 0505 SIO232 with QRM from Radio Moscow, the receiver being a Realistic DX300 used with a 60ft long wire.

BRT400

Reader **S. Wade** of Meonstoke, Hants says he "picked up a BRT400 from a junk shop for a few quid and after many hours of chipping away the rust, etc., it goes well on all bands". He wonders how many of these old receivers are still around.

Well, the BRT400 is not all that old. I first heard of it as a result of a short article in *Wireless World* in the early 1950s when they were being installed at BBC receiving stations. The receiver came onto the surplus market about ten years ago. The version I have is the BRT400D which is the basic table model (some are rack mounted), without crystal calibrator or 9kHz audio rejector filter. The date on the handbook is July 1952.

It is a 14-valve, single-conversion job covering 150 to 350kHz plus 510kHz to 30MHz in five bands. The i.f. is 455kHz and variable selectivity is provided by six switched bandwidths between 0.5kHz and 13kHz. A crystal filter is in use on the three narrowest positions together with a phasing control which can attenuate a signal 1kHz off tune by some 40dB. There are 16 switches and knobs on the front panel which include separate r.f. and i.f. gain controls, aerial trimmer, noise limiter, a.g.c. on/off, and speech/music which attenuates audio below 400Hz when in the speech position. The modern equivalent to this receiver would be beyond the means of most of us, but of course there are snags.

The receiver weighs 37kg, measures 500 x 430 x 305mm, spares including some of the valves are difficult to come by and it would, I think, be difficult to find anyone to repair or service it. Like many older receivers, the BRT400 is really for the technical DXer who can adjust, align, repair and modify it to suit his own requirements.

Get the Best Out of a Vintage Receiver

This is the title of a six-page article in the 1980 edition of the *World Radio and TV Handbook*. It takes the reader through a valve receiver, starting at the loudspeaker and finishing at the aerial socket, outlining on the way the various faults that might occur due to age, use or even lack of use. Anyone contemplating the overhaul of an old valve receiver should read this article. To quote from it: "There



SHORTWAVE SERVICE
RADIO NEW ZEALAND



are few specifications possessed by contemporary receivers that could not be found in sets well over a quarter of a century ago," which agrees with my own experience with the BRT400. Apart from a slight change to the alignment on the medium waves the only "mod" I have done is to fit an external commercially made digital readout, which turned out to be quite a simple job.

QSLs

Some readers like to display their QSLs on the walls of their "shack". **Julien Smith** is one of them and he thinks it is a pity that some cards do not have the name of the station and reception details printed on the front. I know how you feel Julien, as I keep mine in photographic albums and it is a nuisance having to take them out. **Lee Humphreys** has another problem which is encountered by many DXers, and that is with stations that do not reply to a reception report. Some like return postage, an IRC for example, while others take a long time to reply and there are a few that just do not QSL at all.

Sometimes there is a change of policy and a non-verifier suddenly begins to QSL. This seems to be the case with the Voice of Chile as a number of readers report receiving a verification from that station. **Bryan Robertson** enclosed

a photo-copy of the QSL folder he received, while **Rhys Thomas** had his report translated into Spanish by a teacher at the local school and when sent with an IRC it brought a reply. Some DX clubs have Spanish report forms which enable members to concoct their own using a standard type letter and a DX vocabulary.

Radio Canada International's QSL policy is raised by **W. Semmens**, who mentions that a do-it-yourself QSL card is issued once a year only and then only to listeners who are on their mailing list.

The Voice of the Andes

HCJB is the call sign of the Voice of the Andes, which is a station in Ecuador in South America owned and operated by the World Radio Missionary Fellowship. On Mondays, Thursdays and Saturdays a programme in English for DXers, called DX Party Line, is on the air at 2130 in the 16m and 19m bands, according to the current schedule. HCJB is generally a good signal in the UK.

A new steerable multiband antenna has come into use recently and there is a photo of it on page 349 of the current *WRTH*. HCJB will QSL on receipt of a complete reception report. Their latest QSL card shows a piece of sculpture from an early civilisation in Ecuador and the address for reports is HCJB, Casilla 691, Quito, Ecuador.

Readers' Letters

Radio New Zealand crops up again in a note from **A. D. Scholifield** who has sent me a rather pretty QSL card from this station. He reports hearing RNZ on 11 945kHz in the 25m band between 0730 and 0900, and he would like to hear from any reader who has listened regularly to the programmes from this station. Replies direct to 43 Fellside, South Shields, Tyne and Wear, NE34 8QX.

Thirteen-year-old **Andrew Harpur** of East Kilbride in Scotland has started the All Round DXers Course with Radio Nederland, which he says is very informative. Anyone interested in this or any of the other courses run by this station should write to Radio Nederland, 1200 JG Hilversum, Holland. I can thoroughly recommend this course as I followed it when it was broadcast in instalments a few years ago.



by Ron Ham BRS15744

Pictures from across the Atlantic, contributions from new young enthusiasts and reports of DX through meteor scatter, out of season sporadic-E and a super high atmospheric pressure. What more could a v.h.f. columnist ask for?

Solar

Although **Ted Waring**, Bristol, reported counting 30 sunspots on December 7, 31 on 11th, 21 on 20th, 24 on 29th, 14 on 31st, 20 on January 2, 25 on 4th, 37 on 6th and 55 on 13th, neither **Cmdr Henry Hatfield**, Sevenoaks,

THE SMALL PRINT STILL MAKES GOOD READING

Despite the increase in Bank Rate we're still able to save you a bomb – Still able to offer you a short sharp H.P. deal costing you no more than the cash price . . . Want to buy a FT 101ZD? Try borrowing £670 from your bank and work out your charges . . . PAINFUL? Try the average finance company – EVEN MORE PAINFUL! Well above 20% per annum no less! ENOUGH TO MAKE YOU CRY is'nt it? . . . Right – get your hankie out, wipe away those tears and focus your eyes down page to the deals we have listed – ENOUGH TO MAKE YOU SMILE is'nt it? . . . You've probably noticed the down payment is higher than last month – not our fault – the Chancellor again! ENOUGH TO MAKE YOU CRY is'nt it? . . . Never mind we've balanced this out by making your monthly repayments quite a bit lower – Go on work it out for yourself. ENOUGH TO MAKE YOU SMILE is'nt it . . . Of course if you're really clever you'll very quickly work out how to save even more money buying the AMCOMM WAY! If you can't see it – call us, we'll explain it! . . . If this lot hasn't wiped the tears from your face we have one more thing that will. With the deals listed below and for a short period only we'll offer ABSOLUTELY FREE one only pure Irish linen hankie !!!!!

Incidentally, we're happy to consider trade-ins (regret no free hankie) and still offer our absolutely no quibble guarantee. "Any goods purchased from this company which do not meet the manufacturer's published specification will be immediately rectified or replaced".

Yaesu FT901DM Cash Price £920.80 Deposit £352.00 12 monthly repayments of £47.40	Yaesu FT 101ZD Cash Price £670.20 Deposit £240.00 12 monthly repayments of £35.85	Yaesu FT 225RD Cash Price £557.76 Deposit £216.00 12 monthly repayments of £28.48	Yaesu FT 7B Cash Price £432.12 Deposit £168.00 12 monthly repayments of £22.01	Yaesu FT 101Z Cash Price £575.76 Deposit £234.00 12 monthly repayments of £28.48
Yaesu FT 107M/107E Cash Price £862.04 Deposit £335.00 12 monthly repayments of £43.92	Yaesu FRG 7000 Cash Price £377.04 Deposit £150.00 12 monthly repayments of £18.92	Yaesu FT 207R Cash Price £199.60 Deposit £91.00 12 monthly repayments of £9.05	Standard 8800 Cash Price £252.00 Deposit £99.00 12 monthly repayments of £12.75	Standard 8700 Cash Price £275.08 Deposit £109.00 12 monthly repayments of £13.84

Above offers subject to status report and MLR.

TRADE-INS
WELCOME



AMCOMM SERVICES

194A NORTHOLT ROAD, SOUTH HARROW, MIDDX. Tels: 01-864 1166 & 01-422 9585

OPENING
HOURS
Mon-Sat 9.30-5.00
Sunday 11.00-4.00



IF YOU ARE INTERESTED IN

AMATEUR RADIO

AND LIVE IN OR NEAR KENT

WHY NOT COME AND VISIT US

(or Phone us for a copy of our Catalogue)

WE STOCK

TRANSCEIVERS POCKET RECEIVERS
BOOKS RECEIVERS POWER SUPPLIES
ROTATORS AERIALS

FOR

AMATEUR, MARINE & PRIVATE MOBILE RADIO

THANET ELECTRONICS

143 RECVLVER ROAD, HERNE BAY, KENT

Tel: (02273) 63859

Telex: 965179

Western

THE COMMUNICATIONS SPECIALISTS
EVERYTHING FOR THE RADIO AMATEUR

ANTENNAS . . . FOR THE HF BANDS

BRITISH MADE BY **Western**

TRAP DIPOLES (3 types)

TD1/10-80	10, 40 and 80m	£25.30
TD1/15-80	15, 20, 40 and 80m	£25.30
TD-P	Portable type with winding spools	£30.48

(TD1 are of 14 gauge copper; TD-P is copper/terylene braid)

VERTICAL

DX-5V	10-80 metres; approx 26ft high; slimline	£60.32
-------	--	---------------

BEAM ANTENNAS (and Rotary Dipole)

DX-31	Rotary dipole for 10, 15, 20m	£46.00
DX-32	2-element beam for 10, 15, 20m	£80.50
DX-33	3- " " " " " "	£121.90
DX-34	4- " " " " " "	£161.00
DX-103	3-element monoband beam for 10m	£74.75
DX-105	5- " " " " " "	£97.75

★ Other Antenna Accessories available – see our Price List ★

ALL PRICES INCLUDE VAT (15%) AND FREE DELIVERY UK.

Send large SAE for further details of this and other equipment – or use our Answerphone after hours.

Western Electronics (UK) Ltd

HEAD OFFICE (All Mail/Enquiries)

FAIRFIELD ESTATE

LOUTH, LINCS, LN11 0JH

Tel: Louth (0507) 604955/6/7


ACCESS
VISA
H.P.

Eddystone

The Leaders in Short Wave

at **SONIC SOUND AUDIO**
BRITAIN'S No. 1
AUDIO STORE

SOLE RETAIL
DISTRIBUTORS
FOR EDDYSTONE

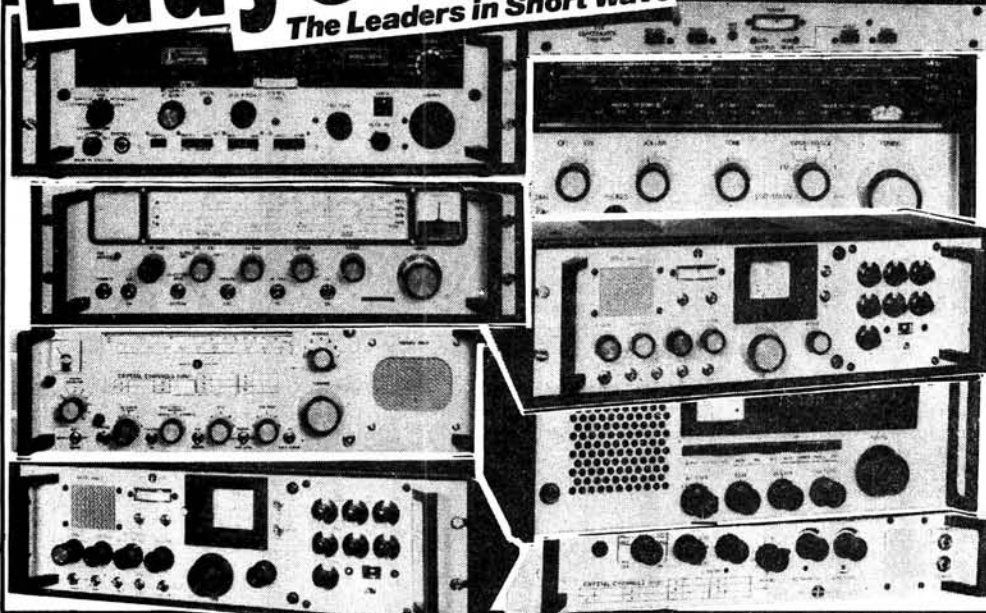

Sonic Sound, the premier home entertainment store have now added yet another big name in the field of sound equipment to further enhance their prestige in London's centre of the audio/visual and Hi-Fi field in Tottenham Court Road.

Eddystone, at the top of the tree since short wave began, have now appointed Sonic Sound Audio as sole retail distributors in the United Kingdom.

Anyone even contemplating purchasing short wave equipment, be they looking for the best possible available for their Embassy, press department or home use, should visit or contact Sonic where they will be able to view and listen to the most comprehensive range of the latest short wave equipment on the market today.

Listen and choose in comfort at Britain's most up-to-date air conditioned sound demonstration studios. Full ranges of Hi-Fi, Video equipment, In-car and portables, etc., from all leading manufacturers: B & O, Sanyo, Sony, Hitachi, Pioneer, J.V.C.



THE COMMUNICATION CENTRE

SONIC SOUND AUDIO

248-256 TOTTENHAM COURT ROAD LONDON W1 TEL: 01-637 1908

Eddystone

A Marconi Group Company.



STEPHENS-JAMES LIMITED

COMMUNICATION ENGINEERS

47 WARRINGTON ROAD, LEIGH WN7 3EA

ENGLAND

Telephone (0942) 676790

Everything for the Short Wave Listener.

We stock receivers and listening aids by most of the world's leading manufacturers. Full range of VHF receivers—transceivers. Mobile equipment pre-selectors—filters—antennas. Stabilised power supplies from 2 to 20 Amp.

Antenna switches—converters. Aluminium masts—clamps. Antenna rotators.

Trio R1000 Receiver

Digital readout general coverage receiver covering 200KHz to 30MHz with a P.L.L. synthesiser. Also incorporating quartz digital clock. £298.00.

Trio R820

Amateur Band Receiver £690.00.

Send for full specifications of our full range of receivers covering from 200KHz to 520MHz. Our secondhand equipment changes daily. Send SAE for up to date lists. Part exchange welcome. Good clean Equipment bought for cash.

Antenna Multituner MK2

Designed and manufactured by ourselves. Frequency coverage 500KHz to 30MHz. Will match any antenna over 5m in length to practically all receivers. In production for over four years and now used in over 55 countries.

Multifilter MK2

This unit incorporates Peak and Notch filter, and Band Pass filters. No internal connections to your receiver. Essential for users of FRG7, SRX30, SSR-1 etc.

Send for details including our Preselector and Crystal Calibrator.

FIT A DIGITAL DISPLAY TO YOUR FRG7 OR SRX30.

These units come complete, with only three wires to connect. The FDU7 for the Yeasu FRG7 can fit in place of the KHz dial, or can be supplied for external use. (Please state when ordering)
The FDU3 for the SRX30 is supplied for top of the set use only.

(Full Fitting Instructions are supplied.)

(FDU7) for FRG7

@ £49.00

(FDU3) for SRX30

@ £49.00

We also manufacture an R.T.T.Y. Converter. Active filtering throughout. Copies speeds up to at least 100 baud. ATC circuitry. Switch selectable shifts 170-425-850Hz.

The MB6R (Receive only) and the MB6R/T (Receive/Transmit).

We supply these units with single or double current loops for connection to teleprinter To Order.

T.T.L./C-MOS Logic Levels and Oscilloscope Outputs are provided. Dimensions (84X304X210).

(MB6R Double or single current) @ £85.75

(MB6R/T Double or single current) @ £91.57

All Units are fully Guaranteed, and come complete. No extras needed.

(All prices inclusive of postage and V.A.T.)


(Payment by P.O., Cheque or Access)

**B. BROOKES ELECTRONICS, 69 Leicester Street,
NORWICH NR2 2DZ, ENGLAND.**

Tel: 0603-24573.

H.A.C. SHORT-WAVE KITS

WORLD-WIDE RECEPTION

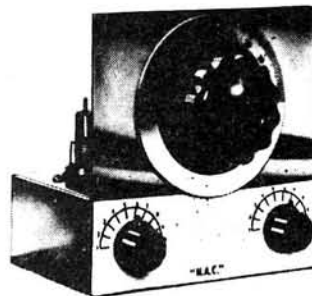

"H.A.C." well known by amateur constructors for its Short Wave receivers, now offers a complete range of kits and accessories which have been up-dated to suit the novice and the expert.

£12.00 INCLUSIVE—the ever popular and easy to construct DX receiver Mark III; containing all genuine short wave components, drilled chassis, valve, accessories and full instructions.

T TWIN TRANSISTOR RECEIVER, selective, sensitive and with fantastic reception, yet needing only a single PP3 battery, at £14.50 this receiver is outstanding value, and will give you hours of interest and entertainment.

NEW - TRIPLE-T RECEIVER, a more advanced super three transistor receiver, loud, clear reception, value unequalled at bargain introductory price of £20.00.

All orders despatched within 7 days. Send stamped and addressed envelope now for free descriptive catalogue of kits and accessories.

SORRY, NO CATALOGUES WITHOUT S.A.E.

"H.A.C." SHORT-WAVE PRODUCTS
P.O. Box No. 16, 10 Windmill Lane
Lewes Road, East Grinstead, West
Sussex RH19 3SZ

nor myself recorded any significant radio noise at metre wavelengths throughout the period.

Cross Band, 10m to 6m

Between November 20 and December 16, **Mike Allmark**, Leeds, logged VE1AVX, who has been predominantly strong in the UK when 6m is open, eight Ws and six Ks. Up to mid-December **John Branegan** GM4IHJ, Saline, Fife, has worked 75 stations, crossband, 10m to 6m, as far west as New Mexico and South Dakota. I noticed that when I heard strong s.s.b. signals from Canada and the USA on 6m, at midday on December 14 and 16 and January 7 and 8, signals from the north American continent were very strong on 10m.

The 10 Metre Band

It appears that my report of hearing the Norwegian beacon signal LA5TEN, was the first from outside Norway to reach the beacon keeper, **Paul Justnaes** LA5PN, who modified one of his own QSL cards to acknowledge the report (Fig. 1), many thanks Paul. LA5TEN is situated near Oslo and operates on 28.2375MHz. Paul also had a report from LA2PH/MM, near Florida, USA and said he would like more reports, his QTH is PO Box 10, N-1410 Kolbotn, Norway.

Ted Waring received signals from LA5TEN at midday on December 11, 12 and 13, at 549 and I heard it again, 569, at 1334 on the 16th. Ted heard the Canadian beacon VE3TEN, around 539, almost daily from December 4 to January 14 and, unlike me, only detected the Cyprus beacon, 5B4CY, occasionally. I received signals from the beacons in Bahrain A9XC and Germany DK0TE and DL0IGI, on each of the 38 days between December 14 and January 20. 5B4CY on 34 days and the Bermuda beacon VP9BA on 28 days. Although DL0IGI hit 599 at 1355 on January 4, all other beacon signals were well below 549. **Harold Brodribb**, St Leonards-on-Sea, Sussex, using an AR88LF and inverted "V" loft aerial, logged strong harmonics at several spots in the 10m band, from lower frequency broadcast stations, on December 15, 18, 20, 24, 26 and January 1, 5, 6 and 10. Generally speaking, the band was well open throughout the period with signals from Russian stations predominant in the early morning and from the USA at midday.

Slow Scan Television

Sam Faulkner received SSTV pictures, mainly around 28.680MHz, from WA4UUV on December 2, WB4ROY on the 5th, three Ws and two Ks 6th, WA7WOD 7th, OH2KM 8th, K1BZ 15th, KP4YD 25th, WA2YJD and W5ZR 26th, 17PQD 30th and KA1AQM, PA3API and KA5EJX on January 9 (Fig. 2). During the big tropospheric opening on November 28 and 29, **Richard Thurlow** G3WW, March, Cambs, had two-way SSTV QSOs with one Belgian, two Dutch, three French, six German and two UK stations in the 2m band, and his pictures were also received by ONIAFJ and ON5MK who, like Sam, have monitors only. Several times a week Richard has breakfast-time SSTV QSOs with Mel Shalveson W6VLH (Fig. 3), who has a 6ft monitor screen, and LA, W0, W9, W8, and W7. During 1979, Richard worked 247 first-time, two-way contacts to bring his SSTV total, by January 7, to 1423 stations worked. Among the awards Richard has earned is *CQ Magazine's* DX SSTV Certificate No. 3 (two-way contacts, 101 countries), and their Master SSTV Awards Certificate No. 1, for five two-way contacts on each of the five amateur bands, 80, 40, 20, 15 and 10m and six ditto in six bands, including 2m.

✕ NORWEGIAN AMATEUR RADIO STATION ✕

Zone 14

To radio

R.A.HAM

Date

5/11-79

GMT

0930

Pål (Paul) Justnaes

P. O. Box 10

N-1410 Kolbotn

LA5TEN

...Antenna work is fascinating!

QSL NO. 1

C for WALA

Mhz

3.5 21

7 28.2375

14 145

Mode

CW FSK RTTY

RST

589

TKS RPT

Vy 73 Pål

Fig. 1: The QSL Card received from the Norwegian beacon keeper in response to the author's report

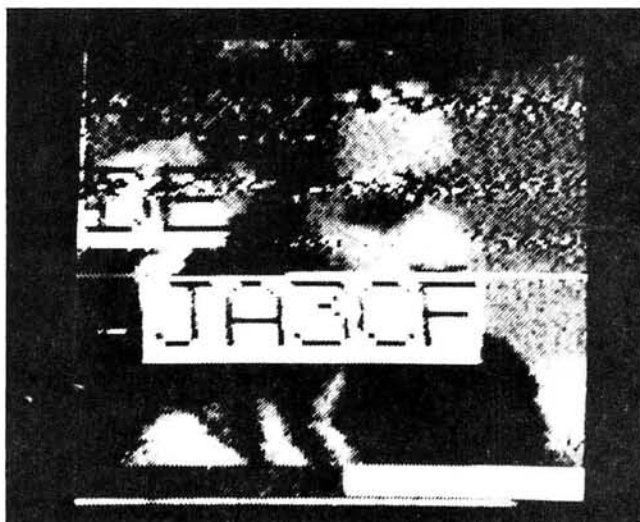


Fig. 2: SSTV picture received by Sam Faulkner from Japan



Fig. 3: The SSTV picture of W6VLH received by Richard Thurlow at 1633 on January 15

DXTV

Cyril Willis, Ely, Cambs, received Russian pictures on channel R1, 49.75MHz, for a short time at 1000 on

December 25, and again at 1615 on the 27th when he watched a news programme, followed by a ballet for about an hour. Cyril began TV DXing in June 1979 and has seen pictures from Austria, Czechoslovakia, Holland, Hungary, Iceland, Italy, Norway, Poland, Portugal, Russia, Sweden and Yugoslavia, in Band I, via sporadic-E. He has received, Belgium, Denmark, Holland, and W. Germany in Band III, and Belgium, France, Holland and W. Germany at u.h.f. via tropospheric openings. Cyril's converted Bush TV receiver is fed with a Vorta 14-element aerial for Band III, and a Maxiview, 4-element aerial for Band I, mounted on an Antiference rotator.

Nicholas Brown, Rugby, also began TV DXing last June and has received pictures in Band I from the same countries as Cyril. Nicholas uses a dual-standard receiver directly on u.h.f., and a v.h.f.-u.h.f. up-converter with a vertical dipole and a horizontal, omnidirectional, "X" array for the lower bands. He also tells me that the Bulgarian news is called, PO CBETAN Y HAC. **M. J. Wood**, Mablethorpe, Lincs, suggests that TV DXers should have a copy of the Russian alphabet which can be found in the *Teach Yourself* . . . series of books; this could be very useful when monitoring Band I. **George Grzebieniak** RS41733, London, is setting up television gear using a combined 5-element array for Bands I and III and a dual-standard HMV 2660 receiver. George's first target is to receive Southern Television and is considering giving the RS Components, Hybrid RF Amplifier module a try. This looks good George, I see that its recommended frequency range is 40 to 860MHz, it has a gain of 27dB, works on 24V and has an input and output impedance of 75Ω.

Fifteen-year-old **Alistair Dupres**, Cardiff, uses a Rigonda portable receiver, and with its own loop aerial he received the Dutch u.h.f. station Nederland-2, during the tropospheric opening on November 29 and watched the evening news programme *Nos Journaal*. Alistair then borrowed his father's Minolta camera, set it at f8 and 1/30th and photographed some of the DX (Fig. 4).

Sporadic-E

A sporadic-E disturbance, extending into Band II, occurred mainly during the afternoon of January 5. While I was trying to sort out a news programme from a cartoon and an American war film around channel E2 in Band I, **David Appleyard**, Uppsala, Sweden, sitting in his car outside Stockholm's International Airport, received signals of "unbelievable strength" on his car radio at 1650 from BBC Radio-2 on several adjacent frequencies between 88 and 88.6MHz and a further English station, which he could not identify, around 96.8MHz. "These conditions persisted until just after 1800 when, alas, the BBC faded out", writes David.

Andrew Rogers, Bristol, received pictures from Sweden, on E2 at 1800; by 1815 he was getting the same programme on E3, but it all faded out at 1915. During the event Andrew heard full stereo from Spain on 96.4MHz. It was beginner's luck for 15-year-old Andrew, because he only purchased an up-converter for his 12in Ferguson portable TV earlier in the day and was delighted to see his first DX so soon. **P. M. Farrugia**, also in Cardiff and another recent starter in TV DXing, was very excited on the 5th, because for the first time he saw the Austrian test card, ORF-FS1 (Fig. 5) at 1120 and, like me, the American war film plus Czechoslovakian and Russian test cards. P. M. Farrugia uses a JVC 3040 receiver fed with a wideband array on a rotator for Band I.

Sam Faulkner watched news and cartoons on R1 from 1750 to 1845 on the 4th and a Ballet from Russia around

1600 on the 5th. At 1630, Sam also received pictures and sound on E2 and E3 from Sweden. "The video and audio from Sweden at 1700 was fantastic, often equal to local level and the signals on both channels (transmitting the same programme) were excellent until 1900," writes Sam. "The first programme, a documentary about the fishing industry, was followed by the news headlines and weather forecast. The YL announcer then introduced a religious programme, which featured a very beautiful church. *A Comedy of Errors* from essentially serious films followed, then a film about a young Swedish family. *James at 15*, an American children's programme, began the early evening's viewing; by this time I was no longer alone in the shack having been joined by the rest of the family."

TV Across the Atlantic

Around 1600 on December 11 and 12, Mike Allmark received pictures from the USA on channel A2, 55.25MHz, via F2, and from 1430 to 1700 on the 13th, he saw *NBC News*, *Sesame St*, *Flinstones*, *Beverly Hill Billies* and weak sound, copied at times on 59.75MHz. He



Fig. 4: Dutch TV programme *Nos Journaal*, received on u.h.f. by Alistair Dupres

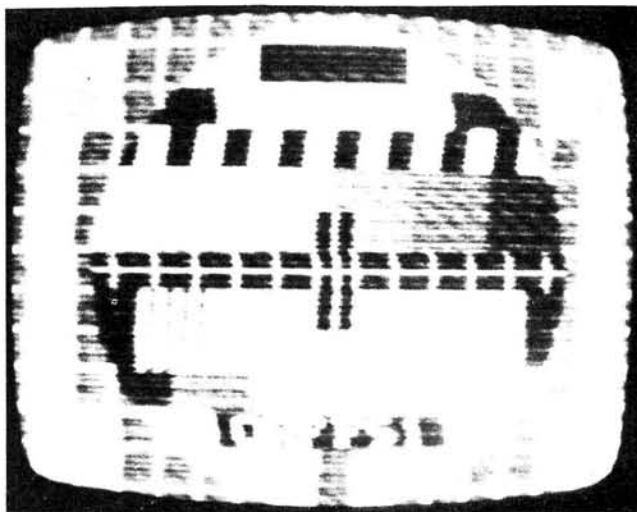


Fig. 5: An Austrian test card received in Band I by P. M. Farrugia at 1120 on January 5

again received pictures on A2 around 1300 on the 14th and during the afternoon of the 15th. Sam Faulkner received Canadian TV signals around 1300 on the 13th and 14th and writes: "I could see the newscaster and the programme format was similar on both days." A2 signals were received again briefly on the 15th and from 1320 he saw the Saturday morning children's programmes. With two transmitters coming up on the channel, Sam had some difficulty sorting out the *Muppets* from a craft programme. John Branegan received pictures on A2 at 1622 on the 14th and Mike Allmark recorded the sound of *CBS News* during the same afternoon.

Back on this side of the pond, on December 17 Mike received strong pictures on R1, E2 and E3 until about 1400. On E3 the PM5544 test card had what looked like UAE, a Gulf State, in the bottom identification panel. I found it impossible to identify anything from the mixture of pictures on R1, via F2, around 0930 on December 14 to 19 and January 16 and 17.

Meteor Scatter

"The Quadrantids meteor shower was good this year; 144MHz was alive, especially around 0200 on January 4," writes Mike Allmark, who heard signals from at least 10 countries. Among them was IT9FEJ at over 2000km, bouncing off the trails of ionised gas left by the meteor particles as they burnt up in the earth's atmosphere. Mike also identified bursts of picture from European and Scandinavian television stations in Band I, during the event. Between December 1 and 14, which includes the Geminids meteor shower, Mike heard signals on 144MHz from France, Germany, Italy, Scandinavia and Switzerland. Sam Faulkner monitored Band I between 0700 and 0750 throughout the period November 14 to December 11 and saw a multitude of "pings" of test cards from Czechoslovakian, Scandinavian and Russian TV stations.

At 1007 on January 4, I received strong bursts of test cards from Finland and Russia.

Tropospheric

The atmospheric pressure rose from 30.0in on January 10 to a real high of 30.7in at midday on the 12th. True to form, as it fell through the 13th and 14th, there was a tropospheric opening. During this time I heard signals through the 2m repeaters in Birmingham GB3BM (R5), and Bristol Channel GB3BC (R6), and at 1413 on the 13th the 70cm beacon at Emley Moor, GB3EM was 589, on my dipole! **Alan Baker** G4GNX, Newhaven, Sussex, worked through the new Dorset repeater GB3SC (R1) and heard signals through the Leicester repeater GB3CF.

Mike Allmark heard 2m signals from stations in DL, ON, OZ, PA0 and SM on the 13th along with u.h.f. TV pictures from Belgium, France, Holland and West Germany.

News Items

Within two days of **Eric Arnold**, Brighton, formerly G8OUK, receiving his new call, G4JDJ, he worked a VK on 10m s.s.b. and another new call, **Paul Corrigan** G8TJS, Bradford, was on the air 20 minutes after his licence dropped through his letter box. At present Paul has a Trio TR2300, a 4-element quad and Slim Jim aerials for 2m and a DX160 receiver with a 66ft long wire aerial for the h.f. bands. By January 4, Paul had made 775 contacts on 2m. **John Trimmer**, Brighton, formerly G8TMX is now G4JDM.

There has been a change to the 2m repeater system in London. GB3LO (R7) has been replaced by a network of repeaters at the compass points, GB3NL, north London (R7), GB3SL (R2), GB3EL (R0) and GB3WL (R1).

I hope to see some of you at the RSGB VHF Convention at Whitton, Twickenham, Middx, on March 8.

Roy BANNISTER G4GPX

Although Roy Bannister did not get his G8 licence until 1976, his interest in radio dates back more than 30 years to a time when he was a regular visitor to and transmitted from, (as one could under supervision in those days) the shacks of G2CSV, G3BRU and many others.

When Roy and his wife Joyce moved from Redcar to their present home in Lancing, Sussex in 1960, they developed a deep interest in tape recording. Since then they have won several national tape recording contests, in addition to making tapes for the Blind and Audio programmes transmitted by BBC Radio Brighton.

Through tape recording they met John Kuipers, who took the RAE with Roy. John attended college and Roy studied at home with Braille literature and tape recordings. Since getting his licence, Roy has worked a great deal of v.h.f. DX, using an FT221 and an 8-element Yagi from his home QTH, situated at sea level. He is usually very active during an aurora or tropospheric disturbance.

In 1977, Roy passed the Morse test and with his present callsign, G4GPX, has made many c.w. contacts using his FT101E and a Hustler vertical or a trapped inverted "L" aerial.

Both Roy and Joyce are members of the Worthing and District Amateur Radio Club and are frequently seen at mobile rallies and use an FT7 from their car. In addition to earning his living as a piano tuner, Roy has just completed forty years of playing the organ or piano in dance bands.



Britain's first comp

A complete personal computer for a third of the price of a bare board.

Also available ready assembled for £99⁹⁵

The Sinclair ZX80.

Until now, building your own computer could easily cost around £300—and still leave you with only a bare board for your trouble.

The Sinclair ZX80 changes all that. For just £79.95 you get *everything* you need to build a personal computer at home...PCB, with IC sockets for all ICs; case; leads for direct connection to your own cassette recorder and television; everything!

And yet the ZX80 really is a complete, powerful, full-facility computer, matching or surpassing other personal computers on the market at several times the price. The ZX80 is programmed in BASIC, and you could use it to do quite literally anything from playing chess to running a power station.

The ZX80 is pleasantly straightforward to assemble, using a fine-tipped soldering iron. Once assembled, it immediately proves what a good job you've done. Connect it to your TV set...link it to an appropriate power source*... and you're ready to go.


Your ZX80 kit contains...

- Printed circuit board, with IC sockets for all ICs.
- Complete components set, including all ICs—all manufactured by selected world-leading suppliers.
- New rugged Sinclair keyboard, touch-sensitive, wipe-clean.
- Ready-moulded case.
- Leads and plugs for connection to any portable cassette recorder (to store programs) and domestic TV (to act as VDU).
- FREE course in BASIC programming and user manual.

Optional extras

- Mains adaptor of 600 mA at 9 V DC nominal unregulated (available separately—see coupon).
- Additional memory expansion board plugs in to take up to 3K bytes extra RAM chips. (Chips also available—see coupon.)

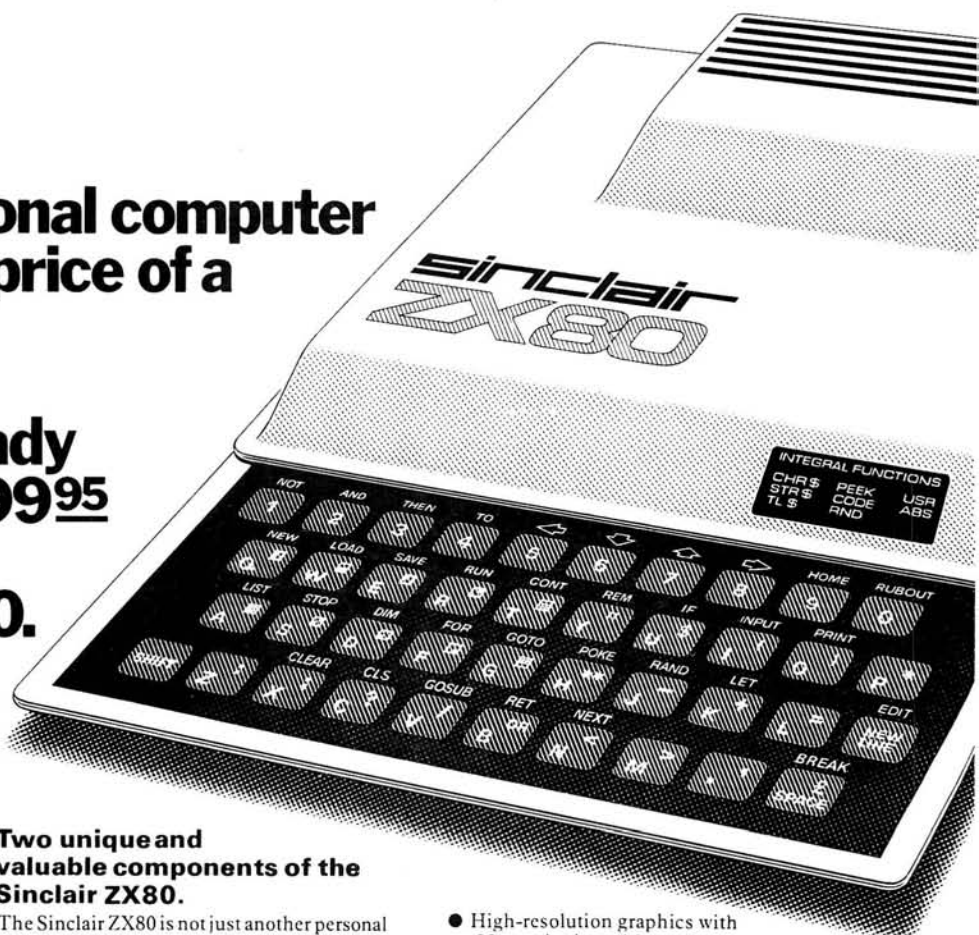*Use a 600 mA at 9 V DC nominal unregulated mains adaptor. Available from Sinclair if desired (see coupon).



Two unique and valuable components of the Sinclair ZX80.

The Sinclair ZX80 is not just another personal computer. Quite apart from its exceptionally low price, the ZX80 has two uniquely advanced components: the Sinclair BASIC interpreter; and the Sinclair teach-yourself BASIC manual.


The unique Sinclair BASIC interpreter... offers remarkable programming advantages:

- Unique 'one-touch' key word entry: the ZX80 eliminates a great deal of tiresome typing. Key words (RUN, PRINT, LIST, etc.) have their own single-key entry.
- Unique syntax check. Only lines with correct syntax are accepted into programs. A cursor identifies errors immediately. This prevents entry of long and complicated programs with faults only discovered when you try to run them.
- Excellent string-handling capability—takes up to 26 string variables of any length. All strings can undergo all relational tests (e.g. comparison). The ZX80 also has string input to request a line of text when necessary. Strings do *not* need to be dimensioned.
- Up to 26 single dimension arrays.
- FOR/NEXT loops nested up to 26.
- Variable names of any length.
- BASIC language also handles full Boolean arithmetic, conditional expressions, etc.
- Exceptionally powerful edit facilities, allows modification of existing program lines.
- Randomise function, useful for games and secret codes, as well as more serious applications.
- Timer under program control.
- PEEK and POKE enable entry of machine code instructions, USR causes jump to a user's machine language sub-routine.

- High-resolution graphics with 22 standard graphic symbols.
- All characters printable in reverse under program control.
- Lines of unlimited length.


... and the Sinclair teach-yourself BASIC manual.

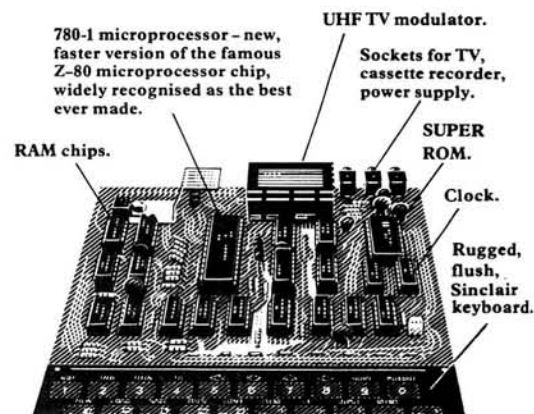If the features of the Sinclair interpreter listed alongside mean little to you—don't worry. They're all explained in the specially-written 96-page book *free* with every kit! The book makes learning easy, exciting and enjoyable, and represents a complete course in BASIC programming—from first principles to complex programs. (Available separately—purchase price refunded if you buy a ZX80 later.)




Practical Wireless, April 1980

Complete computer kit.

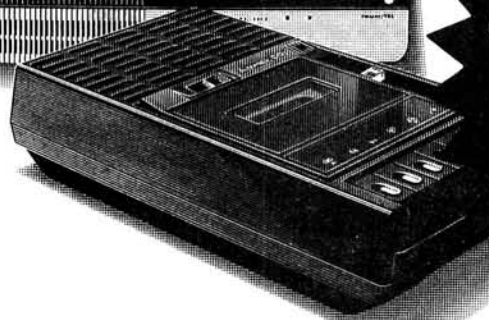

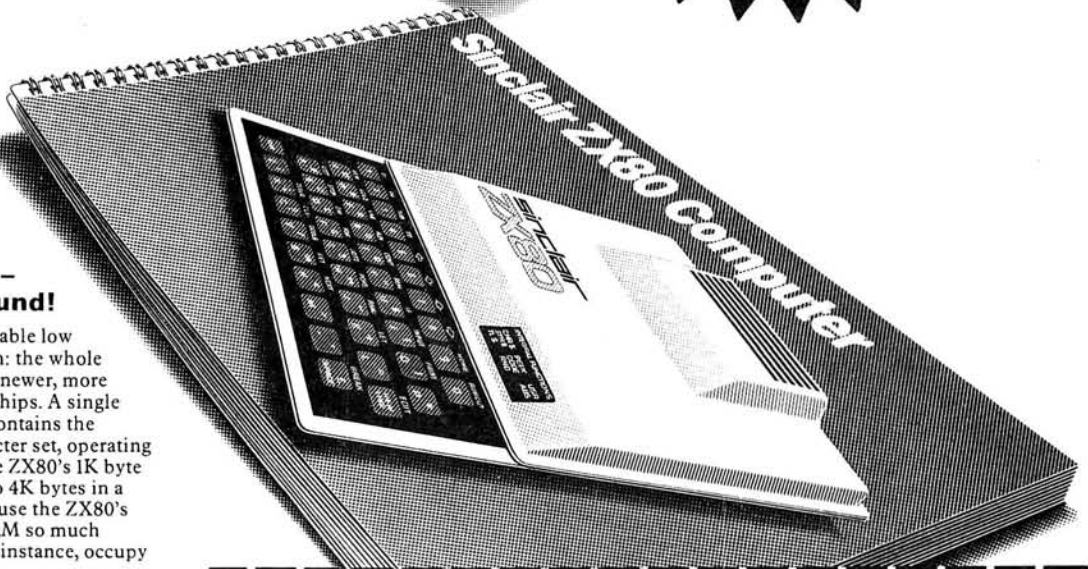£79⁹⁵
 Including VAT.
 Including post and packing.
 Including all leads and components



**Fewer chips,
compact design,
volume production –
more power per pound!**

The ZX80 owes its remarkable low price to its remarkable design: the whole system is packed onto fewer, newer, more powerful and advanced LSI chips. A single SUPER ROM, for instance, contains the BASIC interpreter, the character set, operating system, and monitor. And the ZX80's 1K byte RAM is roughly equivalent to 4K bytes in a conventional computer, because the ZX80's brilliant design packs the RAM so much more tightly. (Key words, for instance, occupy just a single byte.)

To all that, add volume production – and you've got that rare thing: a price breakthrough that really is a breakthrough.

The Sinclair ZX80. Kit: £79.95. Assembled: £99.95. Complete!

The ZX80 kit costs a mere £79.95. Can't wait to have a ZX80 up and running? No problem! It's also available, ready assembled, for only £99.95.

Whether you choose the kit or the ready-made, you can be sure of world-famous Sinclair technology – and years of satisfying use. (Science of Cambridge Ltd is one of the Sinclair companies owned and run by Clive Sinclair.)

To order, complete the coupon, and post to Science of Cambridge for delivery within 28 days. Return as received within 14 days for full money refund if not completely satisfied.

**sinclair
ZX80**

Science of Cambridge Ltd

6 Kings Parade, Cambridge, Cambs., CB2 1SN.
Tel: 0223 311488.

Order Form

To: Science of Cambridge Ltd, 6 Kings Parade, Cambridge, Cambs., CB2 1SN.
Remember: all prices shown include VAT, postage and packing. No hidden extras.

Please send me:

Quantity	Item	Item price	Total
	Sinclair ZX80 Personal Computer kit(s). Price includes ZX80 BASIC manual, excludes mains adaptor.	79.95	
	Ready-assembled Sinclair ZX80 Personal Computer(s). Price includes ZX80 BASIC manual, excludes mains adaptor.	99.95	
	Mains Adaptor(s) (600 mA at 9 V DC nominal unregulated).	8.95	
	Memory Expansion Board(s) (takes up to 3K bytes).	12.00	
	RAM Memory chips – standard 1K bytes capacity.	16.00	
	Sinclair ZX80 Manual(s) (manual free with every ZX80 kit or ready-made computer).	5.00	
	NB. Your Sinclair ZX80 may qualify as a business expense.	TOTAL	£

I enclose a cheque/postal order payable to Science of Cambridge Ltd for £

Please print

Name: Mr/Mrs/Miss _____

Address _____

PW/4/80

ELECTROVALUE CATALOGUE 10 HAD YOURS YET?

Our computer has already selected thousands of our customers to whom our new catalogue has automatically been sent. If you would like a copy too, simply send us your name and address. It's

FREE

(You don't even have to pay postage in U.K.)

IT'S A GOOD DEAL BETTER FROM ELECTROVALUE

- **We give discounts**
on C.W.O. orders, except for a few items market Net or N in our price lists.
5% on orders, list value £10 or more
10% on orders list value £25 or more.
Not applicable on Access or Barclaycard purchase orders.
- **We stabilise prices.**
by keeping to our printed price lists which appear but three or four times a year.
- **We guarantee**
all products brand new, clean and maker's spec. No seconds, no surplus.
- **We pay postage in U.K.**
on C.W.O. orders list value £5 or over. If under, add 30p handling charge.
- Appointed distributors for SIEMENS, VERO, ISKRA, NASCOM and many others.

OUR NEW CATALOGUE No 10

Full 128 pages. Thousands of items. Improved classification for easier selection. Valuable working information. Illustrations. Separate quick-ref price list.

ELECTROVALUE LTD

HEAD OFFICE (Mail Orders)

28(A) St. Judes Road, Englefield Green, Egham, Surrey TW20 0HB. Phone: 33603 (London prefix 87. STD 0784) Telex 264475.

NORTHERN BRANCH (Personal Shoppers Only)

680 Burnage Lane, Burnage, Manchester M19 1NA
Phone: (061) 432 4945.



Wilmslow Audio

THE firm for speakers!

SEND 15P STAMP FOR THE WORLD'S BEST CATALOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS ETC. AND DISCOUNT PRICE LIST.

AUDAX ● AUDIOMASTER ● BAKER ● BOWERS & WILKINS ● CASTLE ● CELESTION ● CHARTWELL COLES ● DALESFORD ● DECCA ● EMI ● EAGLE ● ELAC ● FANE ● GAUSS ● GOODMAN ● I.M.F. ● ISOPHON ● JR ● JORDAN WATTS ● KEF ● LEAK ● LOWTHER MCKENZIE ● MONITOR AUDIO ● PEERLESS ● RADFORD ● RAM ● RICHARD ALLAN ● SEAS ● SHACKMAN ● STAG ● TANGENT ● TANNON ● VIDEOTONE ● WHARFEDALE ● YAMAHA


WILMSLOW AUDIO (Dept. P.W.)

SWAN WORKS, BANK SQUARE, WILMSLOW,
CHESHIRE SK9 1HF

Discount Hi-Fi Etc. at 5 Swan Street

Speakers, Mail Order & Export 0625 529599 Hi-Fi 0625 526213

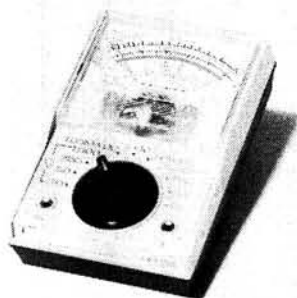GOOD QUALITY INEXPENSIVE POCKET SIZE MULTIMETER



SPECIFICATIONS

- DC VOLTAGE:
0-10, 50, 250, 1000 volts
2000 ohms/volt
- AC VOLTAGE:
0-10, 50, 250, 1000 volts
2000 ohms/volt
- DECIBEL:
- 10 to + 22dB
- DC CURRENT:
0-100mA
- OHMMETER:
0-1 0 kilohms, 0-1 megohms,
60 ohms centre scale
- POWER SUPPLY:
One 1.5V size "AA"
cell ohmmeter
- SIZE:
3-5/8", 2-3/8" x 1-1/8"
- WEIGHT:
4oz

Price: £5.30 inclusive V.A.T. & P & P

Cash with order

TRADE ENQUIRIES INVITED

ARMON PRODUCTS LIMITED

COTTERELL HOUSE, 53-63 WEMBLEY HILL ROAD, WEMBLEY, MIDD. HA9 8BH

TEL: 01-902 4321

TELEX: 923985


Conquer the chip.

Be it career, hobby or interest, like it or not the Silicon Chip will revolutionise every human activity over the next ten years.

Knowledge of its operation and its use is vital. Knowledge you can attain, through us, in simple, easy to understand stages.

Learn the technology of the future today in your own home.

ELECTRONICS

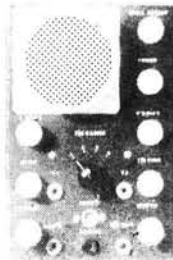

Build your own oscilloscope.

Learn to draw and understand circuits.

Carry out over 40 experiments.


DIGITAL TECHNIQUES

From watches to sophisticated instrumentation, Digital Electronics adds scope to hobby or career.



COMPUTER TECHNOLOGY

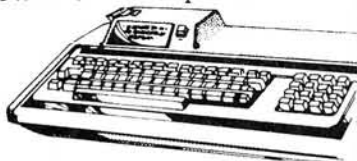
Learn to operate and programme your own home computer.



FREE BROCHURES



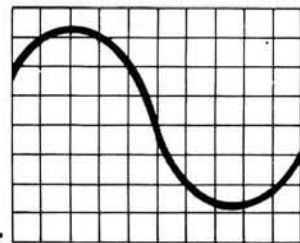No previous knowledge is necessary.
— Just clip the coupon for a brochure



TUTORCOURSE ELECTRONICS

Please rush me details of your ELECTRONICS COURSE

Name _____

Address _____


_____ WR4
Block Caps. Please

Post now, without obligation to:

British National Radio & Electronics School.

P.O.Box 156, Jersey, Channel Isles

The professional scopes you've always needed.

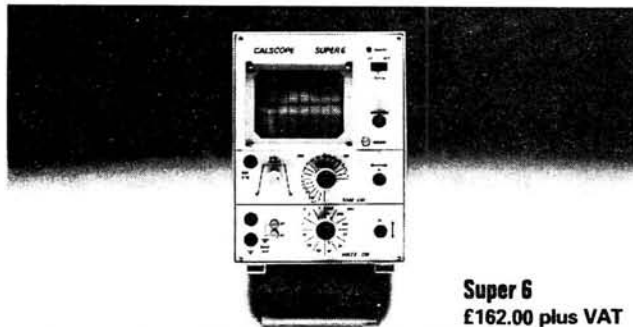

Super 6
£162.00 plus VAT



Super 10
£219.00 plus VAT

When it comes to oscilloscopes, you'll have to go a long way to equal the reliability and performance of Calscope.

Calscope set new standards in their products, as you'll discover when you compare specification and price against the competition.

The Calscope Super 10, dual trace 10 MHz has probably the highest standard anywhere for a low cost general purpose oscilloscope. A 3% accuracy is obtained by the use of stabilised power supplies which cope with mains fluctuations.

The price £219 plus VAT.

The Super 6 is a portable 6MHz single beam model with easy to use controls and has a time base range of 1µs to 100ms/cm with 10mV sensitivity. Price £162 plus VAT.

Prices correct at time of going to press.

CALSCOPE DISTRIBUTED BY

Watford Electronics
33-35 Cardiff Road,
Watford, Herts.
Tel: 0923 40588

Audio Electronics,
301 Edgware Road, London W.2.
Tel: 01-724 3564
Access and Barclay card facilities
(Personal Shoppers)

Maplin Electronics Supplies Ltd.
P.O. Box 3
Rayleigh, Essex.
Tel: 0702 715 155
Mail Order

CALSCOPE

P.C.B.'S FOR PRACTICAL WIRELESS PROJECTS

Jan. 79.	Sandbank Met. Det.	R035	Price £3.41 & 20 pence p & p.
March 79.	Hythe Receiver	WR038	Price £2.98 & 20 pence p & p.
March 79.	Soudlite Converter	WK001	Price £6.33 & 20 pence p & p.
March 79.	Tone Burst Generator	R023	Price £1.71 & 15 pence p & p.
March 79.	Wide Band Noise Source	WR036	Price £0.74 & 12 pence p & p.
April 79.	FM Multitester	WR040	Price £3.05 & 15 pence p & p.
May 79.	Car Test Probe	WR042	Price £0.96 & 15 pence p & p.
May 79.	Follow up to PW Gillingham	WR044	Price £1.45 & 15 pence p & p.
May 79.	PW Imp	WR043	Price £1.52 & 15 pence p & p.
May 79.	Inline Crystal Calibrator	WR041	Price £1.68 & 15 pence p & p.
June 79.	Jumbo Clock		Price £9.52 & 30 pence p & p.
June 79.	Logical 0's+X's	WR046/ 7/8/9	Price £12.84 & 30 pence p & p.
June 79.	Trent	WR050	Price £4.06 & 20 pence p & p.
July 79.	AAM/FM Frequency Readout	WR052	Price £3.66 & 20 pence p & p.
	V.MOS Top Band Transmitter	WR056	Price £4.08 & 20 pence p & p.
	Sound Operated Switch	WK005/6	Price £3.74 & 20 pence p & p.
	Inexpensive A/F Voltmeter	WR055	Price £1.15 & 15 pence p & p.
August 79.	Telephone Bell Repeater	WR053	Price £1.15 & 15 pence p & p.
August 79.	Automatic Intercom	WR045	Price £6.20 & 20 pence p & p.
Sept. 79.	Automatic Intercom Part 2	WR058	Price £0.60 & 12 pence p & p.
Sept. 79.	Noise Blanka	WR057	Price £1.24 & 12 pence p & p.
Oct. 79.	Burglar Alarms	WR059	Price £1.23 & 15 pence p & p.
Oct. 79.	Burglar Alarms	WR060	Price £1.91 & 20 pence p & p.
	Radio Control Receiver	WR064	Price £2.92 & 20 pence p & p.
Jan. 80.	A.F. Speech Processor	WR068	Price £2.28 & 20 pence p & p.
Jan. 80.	P.W. Parkhurst Burglar Alarm	WR063	Price £2.51 & 20 pence p & p.
Jan. 80.	Wide band R.F. Pre Amp	WR067	Price £0.70 & 15 pence p & p.
Jan. 80.	Radio Control Encoder	WR061	Price £2.28 & 20 pence p & p.
Jan. 80.	Radio Control T.X.	WR062	Price £2.26 & 20 pence p & p.

Send FULL RANGE OF R.S. COMPONENTS AVAILABLE
P.W. JUMBO CLOCK KIT £31.00 ALL PRICES INCLUDE VAT

C. BOWES & CO. LTD.,
4, Wood Street, Cheadle, Cheshire SK8 1AQ.
Tel. 061-428-4497.

Please state type number and enclose cheque or postal order.

PRACTICAL WIRELESS NIMBUS

Part Kit for Nimbus Transceiver System
Transmitter/Receiver Printed Circuit Board
plus parts
Modulator

£43.50

£4.50

General Assembly including Mike and Aerial together with case, nuts and bolts, etc.

£40.00

Further Mods and accessories will become available.
Prices subject to VAT.

Please allow 21 days minimum for delivery – dependent on component availability.

JOHN HEATHCOAT AND COMPANY

Tiverton, Devon, Department 26.7
Telephone: Tiverton (08842) 4949.
Extension 69.

PROGRESSIVE RADIO

ALL ORDERS DESPATCHED BY RETURN POST

SEMICONDUCTORS. 2N5062 (100V 800mA) SCR 18p. BX504 opto isolator 25p. CA3130 95p. TBA800 50p. Tag4443 SCR 45p. Texas R1038 power trans. 50p. TDA1151 25p.

SWITCHES. Min. toggles. SPST 8x5x7mm 42p. DPDT 8x7x7mm 55p. DPDT c/off 12x11x9mm 77p. HEAVY DUTY-DPDT 240VAC 10 Amp 35p. PUSH TYPE, push on 16x6mm 15p, push to break version 17p. 16 pin D.I.L. switch 40p.

DISPLAYS. 0.5" Led displays, com. cath. green 95p. 4 digit LED clock displays with message centre, 0.6" figures, com. cath. with data £3.25p. NSA1198 8½ digit multiplexed displays, com. cath. with data sheet £1.45p.

LIGHT DIMMER. Wall mounting 250VAC 800 watts max., has built in photo cell for automatic switch on when dark £4.50p.

RECORDING TAPE. Low noise Mylar, supplied spooled unboxed, 7" 1200' £1.00, 7" 1800' £1.45p, 10½" 3,600' £5.00. BLANK CASSETTES C60 10 for £2.75p, C90 10 for £3.85p.

EDGE CONNECTOR 48 way 0.1, double contact type 70p each.

ELECTRONIC IGNITION CAPACITOR, 0.5mfd 440VAC 1½x½" wire ended 35p each. 'AA' size nicads, 1.2v 500mAh £1.10p each or 4 for £3.75.

TOOLS. 5 piece precision screwdriver sets, individual handles only £1.05 set.

JUMPER TEST LEAD SETS. 10 pairs of leads with insulated cross each end 90p.

MURATA 40KHZ TRANSDUCERS, RX/TX £3.80 pair.

TELEPHONE PICK UP COIL suction type with lead and plug 62p.

MINIATURE SOLID STATE BUZZERS, 33x17x15mm, output at 3 feet 70db., 15ma drain, voltage range 4-15vdc 75p. Loud buzzers (mechanical) 6 volts 55p, 12 volt 65p.

Cash with order please, official orders welcome from schools etc., please add 30p postage and packing. VAT inclusive. SAE for latest illustrated stock list.

31, CHEAPSIDE, LIVERPOOL L2 2DY

MIDLAND TRADING CO

GENTS MEMORY CALENDAR ALARM CHRONOGRAPH

LATEST TECHNOLOGY! Constant display of hours, mins, secs, weekday and snooze alarm indication. A further two optional display modes are available. One being the calendar and month, which can be increased or decreased to give the appropriate month of the year. A 1/100th sec chronograph with split and lap mode facilities is built into the watch with a 12 hour capacity. Also a 24 hour alarm with a 10 minute snooze function is standard to the watch. Backlight and adjustable stainless steel strap.



OUTSTANDING VALUE **£19.95**

GENTS MULTI MELODY CHIME ALARM CHRONOGRAPH

LATEST TECHNOLOGY! Constant display of hours, mins, secs. Weekday, date and month, with mode and chime indication display. A musical alarm is built in and can be set to any time within 24 hours, once activated playing the tune "Oh Suzzana". Two further alarm systems are built in (i) 24 hour alarm and (ii) count down alarm. The watch can be set to chime on every full hour, and a 1/100th sec chrono with split and lap mode facilities is standard. Can be switched off. The face is finished in mineral glass. Backlight and infinite adjustable stainless steel strap.



VERY SPECIAL **£19.95**

GENTS FRONT BUTTON ALARM

LATEST STYLE! Constant display of hours, mins, secs, am/pm. Weekday and alarm indication. A further two optional display modes are available. The watch comprises of 7 digits. 12 function and is programmed to the year 2009. The alarm can be set to any time within 24 hours and operates for 30 seconds. Backlight and a closely woven adjustable stainless steel strap, finish the watch off with a really superb sleek look. Only 8mm thick.



£13.25

GENTS CHRONOGRAPH

PROBABLY THE BEST LOOKING Chrono on the market. Constant display of hours, mins, secs, with am/pm indication. Also month, date and weekday indication. 1/100th and 1/10th sec with split and lap mode facilities. Backlight. Closely woven adjustable stainless steel strap.



SPECIAL **£8.95**

LADIES SUGAR COATED

ANOTHER SUPERB LADIES WATCH with that extremely popular sugar frosted finish (Gold or Silver). Links can easily be removed from the strap and the clasp has a spring mechanism built in to give a comfortable fitting. Constant display of hours and mins, with month, date, secs, auto-calendar and backlight.

£10.50

LADIES COCKTAIL

ELEGANCE AND STYLE for the Lady with a discerning taste.

In Gold or Silver finish with matching adjustable bracelet. Constant display of hours and mins, with month, date, secs. Auto-calendar and backlight.

VERY SPECIAL PRICE **£10.50**



! ZETRON ! WHERE RELIABILITY, STYLE AND ELEGANCE REALLY COUNT ! ZETRON !

BEFORE BUYING A DIGITAL WATCH CONSIDER THE FOLLOWING POINTS WE OFFER.

- (i) 48 hour despatch guaranteed.
- (ii) Full instructions and 12 month guarantee.
- (iii) 10 day money back guarantee if not completely satisfied.
- (iv) Felt presentation case with each watch.

PHONE OR WRITE FOR FULL COMPREHENSIVE CATALOGUE ON THE COMPLETE RANGE OF WATCHES WE OFFER.

HUGE DISCOUNTS AVAILABLE for bulk buyers, Trade Lists on application.

P/P per item 75p which includes insurance.

Cheques or PO's should be made payable to:
MIDLAND TRADING COMPANY, and sent to (Dept. PW)
58, Windmill Ave, Kettering, Northants, NN16 8PA.
(0536) 522024

CASIO WATCHES

LATEST MODELS

83QS27B Alarm chrono 1/10th sec	£26.95
81QS33B Alarm chrono 1/100th sec	£26.95
81CS33B Alarm chrono 1/100th sec	£33.95

ALL OTHER CASIO MODELS P.O.A.

CASIO POCKET/CLOCK CALCULATORS

AQ2000 Calculator with clock & alarms	£23.95
MELODY 80 Calculator with clock musical alarm	£22.95
CQ82 Desk calculator with clock, 4 alarms	£18.95
FX80 Scientific 39 functions. Latest model	£14.95
FX68 Scientific card 39 functions	£18.95
FX2600 Slim scientific 43 functions	£18.95
FX3200 Slim scientific 43 functions	£20.95
FX310 Ultra slim scientific 50 functions	£16.95
FX510 Ultra slim 50 function scientific	£18.95
FX501P Programmable 128 steps 11 memories	£52.95
FX502P Programmable 256 steps 22 memories	£72.95
FA1 ADAPTOR For 501-502 only	£18.95

ALL OTHER CASIO CALCULATORS P.O.A.

SEIKO WATCHES CURRENT

MODELS minimum 25% discount

SPECIAL OFFERS

LAMBDA latest model chronograph. Displays hour, minutes, seconds, month, date, day. Chronograph 1/100th sec. 1st, 2nd place times. Fully adjustable stainless steel strap, and case back with battery hatch. Slim style with night light. 1 year guarantee

£10.45

SAXON ALARM CHRONOGRAPH Seiko style. Displays hours, minutes, seconds, am-pm and day indicator. Auto month, day, date. 24 hour alarm setting. Chronograph in 1/10th sec. 1st, 2nd place times. 12 or 24 hour display. Nightlight. 1 year guarantee.

£15.45

TERMS OF BUSINESS: please note all Casio products price includes VAT, P&P and insurance. Please send cheque/P.O. made payable, B. Bamber Electronics. C.O.D. by phoning (0353) 860185. Callers welcome Tues-Sat 9am-5pm.

SPECIAL OFFERS

A.C. ADAPTOR (Battery Charger) 120V AC input, 5.8V DC at 200mA output. USA type mains plug to 3.5mm jack plug. Brand new & boxed
£1.25 Plus VAT

A.C. ADAPTOR (Battery Charger) 117V AC input, 4.5V DC at 150mA output. USA type mains plug to 2.5mm jack plug. Brand new & boxed
£1.00 Plus VAT

VARICAP TUNER HEADS, 4 button type, 22K res. with AFC switch & station indicator. Brand new
£2.00 Plus VAT

SCREWS. Pack of nuts, bolts, washers, tags, self taps etc. Mixed BA & metric. Sold by weight.
£2.00 per Kilo. Plus VAT

LOW VOLTAGE ELECTROLYTICS. Pack of mixed values & voltages. Approx. 150 items
£1.50 Plus VAT

JAYBEAM STARBEAM UHF set top aerials. Brand new & boxed
£2.00 Plus VAT

MODERN TELEPHONES Type 746 with dials, colour cream, used but new condition
£8.00 Plus VAT

ERSIN MULTICORE SOLDER 3 core solder wound on a plastic reel. 20swg. Ally 60/40 tin lead. Available in 500gm reels
£5.70 Plus VAT

CHANNEL MASTER COLOROTOR aerial rotator Model 9502. Rotation speed 1 rpm, gear ratio 3200:1.3 conductor wire for economy. pinpoint positioning to within one degree.

Now only at £45.00 Plus VAT

We also stock Jaybeam T.V. and Radio aerials. SAE for lists.

ISEP SLOTTED HORIZONTAL RAIL available in 9 ft lengths.

£4.00 Plus VAT

WATCH STRAPS Black stainless steel 50p each. Black plastic 25p each. Watch spring bars 10p each. Discount for Quantity. Plus VAT

RADIOGRAM lid pumps £1.00 each 2 for £1.50 Plus VAT

RIBBON CABLE 19 way decimal coded, 4 metres for £1.25 Plus VAT

RIBBON CABLE 10 way decimal coded, 5 metres for £1.25 Plus VAT

PYE TELECOM Yagi aerials. 4 element, very rugged construction, 71.1MHz (Ideal for four metres). Brand new.
£10.00 Plus VAT

DISGUISED MOBILE AERIALS (dustbin lids). Available in mid-band & high band. Brand new.
£5.00 Plus VAT

BYX25-1000 & BYX25R Rectifiers, 1000V 20A mounted on finned heatsink. Ex-Equip. £1.25 Plus VAT

BZY93C75 Diodes, 75V 20W Zener mounted on finned heatsink Ex-Equip. 75p Plus VAT

BZY93C75 Diodes, 75V 20W Zener mounted on finned heatsink Ex-Equip. 75p Plus VAT

BZY93C75 Diodes, 75V 20W Zener mounted on finned heatsink Ex-Equip. 75p Plus VAT

BZY93C75 Diodes, 75V 20W Zener mounted on finned heatsink Ex-Equip. 75p Plus VAT

BUMPER 1980 CATALOGUE

A selection of items below from our 1980 catalogue, the products we stock are by Eagle, Weller, Draper, Spiralux, Knipex, Servisol, Barnard's & Babani, Newnes, Jaybeam, Vero, and others. If you send us £1.35 you will receive the catalogue plus five bi-monthly shortform catalogues to keep you up to date with prices and special offers. A free pack of Blob Board comes with this month's issue.

EAGLE MA780T Electric fully automatic 6 section retractable car aerial with built-in voltage sensor. Remote drive system makes fitting easier. Aerial length 1,000mm, below wing 220mm, lead length 9,000mm, flexible drive link 700mm.
Price £16.95 Plus VAT

EAGLE DD7 Paging microphone, impedance 600 ohm or 50K ohms, sensitivity 2.25mV at 50K ohms, frequency response 300-9000Hz. Desk or wall mounted.
Price £14.85 Plus VAT

EAGLE MULTIMETER EM50 50,000 opv. DC volts: 0-1200 volts, AC volts: 0-1200 volts, DC current 0-6A, Resistance 0-10 megohms.
Price £19.95 Plus VAT

DRAPER super-chrome 1/2" square drive socket sets, 38 piece, 9 AF hexagon sockets, 3 AF bi-square sockets, 11 MM hexagon sockets, 9 BA hexagon sockets, and 6 accessories.
Price £12.75 Plus VAT

SPIRALUX metric nut spinner sets, contains 8 nut spinners 4, 4.5, 5, 5.5, 6, 7, 8, 9, 10mm. Packaged in a plastic wallet with cellulose acetate handle.
Price £7.53 Plus VAT

WELLER TCP3 IRONS 24 volt series, 3 wire power units, for applications requiring earthed tip. TCP3 irons
£13.84
PUSD power units
£24.12 Plus VAT

WELLER instant heat guns Model No. 81000 £13.21 each Plus VAT

WELLER cordless soldering irons Model No. WC100 £25.47 Plus VAT

JAYBEAM "STEREOBEAM" VHF/FM antennas Model SM82, folded dipole and reflector with universal clamp.
£8.00 each

Full range of Jaybeam aerials and accessories available. (See 1980 Catalogue).


ECA TV778/78 semiconductor equivalent and data books. Data covering 12,000 transistors and more than 60,000 equivalents. 2 volumes for £6.00 Zero VAT

DRYX DE-SOLDER TOOLS model SR3A, de-soldering pump with built in safety guard.
Price £6.50 Plus VAT

TERMS OF BUSINESS: CHEQUE OR P.D. WITH ORDER. REMEMBER PLEASE ADD 15% VAT FOR ABOVE GOODS.

CARRIAGE: PACKING AND CARRIAGE CHARGES FOR ORDERS UNDER £5.00 NETT INVOICE VALUE 75p.
ORDERS OVER £5.00 BUT LESS THAN £20.00 50p.
ORDERS OF £20.00 CARRIAGE PAID.

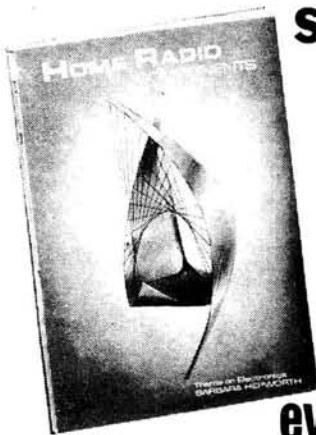B. BAMBER ELECTRONICS DEPT: P.W. 5 STATION ROAD LITTLEPORT CAMBS CB6 1QE



SOME THINGS YOU CAN DO WITHOUT... but the HOME RADIO CATALOGUE is Top Priority for every constructor

- About 2,500 items clearly listed and indexed.
- Profusely illustrated throughout.
- 128 A-4 size pages, bound in full-colour cover.
- Bargain list of unrepeatable offers included free.
- Catalogue contains details of simple Credit Scheme.

HOME RADIO (Components) LTD.,
Dept. PW., P.O. Box 92, 215 London Road, Mitcham, Surrey
Phone 01-648 8422.

POST THIS COUPON with cheque or P.O. for £1.30

Please write your Name and Address in block capitals

NAME _____

ADDRESS _____

HOME RADIO (Components) LTD., Dept. PW
P.O. Box 92, 215 London Road, Mitcham, Surrey



Regd. No.
912966 London



Model 146

ALSO

Model AO113. Sine/Square. 1 volt into 600 . Dist 0.2%. £31.60 (Kit version £26.50) p.p. £1.

LOW COST AUDIO SIGNAL GENERATORS


(Sine & Square Waves)
10Hz-100kHz
Very low distortion ($\times 0.015\%$)
£41.40 (or in kit form) £35.65
p.p. and ins. £2



TELERRADIO ELECTRONICS

325 Fore Street, Edmonton, London N9 0PE
S.A.E. for leaflets . . . Closed all day Thursdays . . . 01-807 3719

Model 1405

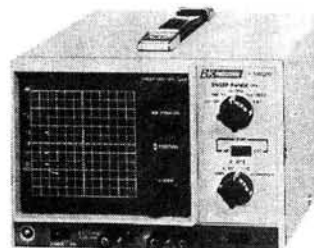

- ★ 5MHz oscilloscope
- ★ Single beam
- ★ 10mV sensitivity
- ★ Int/ext. sync.
- ★ Timebase 10Hz-110kHz cont. variable
- ★ £175.00 inc. VAT Post free

Barclaycard and Access taken
Large SAE for complete catalogue.

HAVANT INSTRUMENTS LTD


20 Portsmouth Rd, Horndean, Hants. Tel: Horndean (0705) 596020

IT'S HAPPENED AGAIN!

THE PART THREE CATALOGUE IS PUBLISHED & WE HAVE MOVED TO BIGGER PREMISES.

Yes, it's here at last - the all new Part Three Catalogue. Fun for all the family, and the usual update on all that is new, worthwhile and exciting in the world of Radio and Communications. A big section on frequency synthesis techniques covering broadcast tuners, to communication quality transmitter systems. More new products than ever - RADIO CONTROL parts, crystal filters, ceramic filters for 455kHz and the new range of TOKO CFSH low temperature coefficient types for 10.7MHz. Details on new radio ICs, including the new HA11225, the CA3189E look-alike with 84dB signal to noise, and adjustable muting threshold. Radio control ICs - and an updated version of the RCM&E 8 channel FM receiver - now with an Ambit designed screened front end, with 27MHz ceramic bandpass filter, LCD panel clock/timer modules - the neatest and best LCD panel DVM yet (only £19.45 each + VAT), the new 5 decade resolution DFM3 for LW/HF/VHF with LCD readout. The DFM6 with fluorescent display to 10kHz resolution on VHF, 1kHz on SW. A 1kHz HF synthesiser with five ICs - the list is endless. Get your copy of the catalogue now. Post publication price is 60p (inc PP etc). The previous two sections are also required for a complete picture: Parts 1 & 2 £1 the pair, All 3 £1.50. And don't miss our spot the gibbon contest, together with a quiz to see if you can spot the differences between a neolithic cave drawing and a circuit diagram of one of our competitor's tuners. (* Yes, we still haven't learnt how to spell.)


FM radio control RX kit

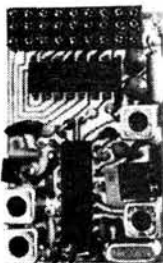

- 8 Channel RC receiver (FM)
- Single IC RF/IF/Detector
- Single IC decoder
- 27MHz ceramic filter input
- FET RF stage with double tuned bandpass filter
- Dual ceramic filter IF
- Best quality SLM servo connector block
- ONLY £16.10 inc VAT (kit) (includes new SLM case)


DOES YOUR ONE GLOW GREEN IN THE DARK ??

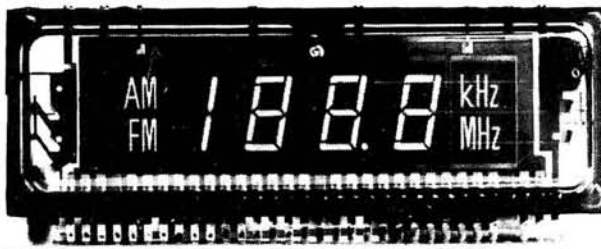Our DFM4 does, since it uses a vacuum fluorescent display for direct readout of MW/LW/FM. Basically the same as the DFM2, (LCD Version). £24.45 kit (inc VAT) Transformer with all necessary windings for DFM4 - £2.50 inc VAT.



Not illustrated here - but also now available is the DFM6. This is a vacuum fluorescent display version of our immensely popular DFM3 (LCD). Resolution is 100Hz to 3.9999MHz, 1kHz to 39.999MHz, and 10kHz to 200.00MHz+; all standard IF offsets (inc. 10.7MHz on shortwave) are available via diode programming.

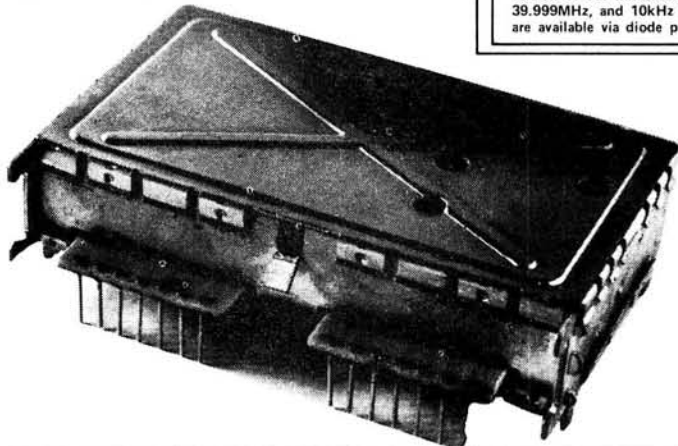New series of radio modules in fully screened cans:



UM1181 VHF band 2 VARICAP TUNERHEAD

5 tuned circuit, with image/spurii better than -80dB, buffered LO output, MOSFET RF stage, FET IF preamp, tunes with only 1½ to 8v. -9dBm 3rd order intercept. 10ff price £12.00 inc VAT. (100off/ OA)

911225 FM IF strip with all mod cons for the HiFi tuner: All types use 80+dB S/N Hitachi IC, with muting, AFC, AGC, meter outputs for signal level and centre zero. IF preamp stage.

'A' Dual linear phase ceramic filters, with MOSFET (AGC'd) IF preamp and a 3rd narrow filter with DC filter selection. Dual tuned FM detector stage. £23.95 inc VAT (built)

'B' Dual ceramic filters, single tuned detector stage £14.95 inc VAT (All 'A' series units are set up with a spectrum analyzer for best THD)

91072 AM RADIO TUNER MODULES - DC TUNED and DC SWITCHED Available February '80

All include buffered LO output, mechanical IF filter (TOKO CFMO) 1-10v tuning bias, switching by a single pole to earth
A MW/LW (150 to 350kHz LW range) with ferrite rod antenna
B As 'A' but also including SW1 or SW2 (specify.)
SW1 = 1.8 to 4MHz SW2 = 5 to 10MHz
C With both SW ranges

Prices one off inc VAT
'A' £14.43 'B' £15.90 'C' £17.50 (Custom types OA)

There is a danger - when advertizing in some magazines - that because we do not find space to list everything we sell in every ad., that some readers forget about half the ranges we stock. So to summarize the general ranges:

- TOKO Chokes, coils for AM/FM/SW/MPX, Audio filters etc
- Filters: Ceramic for AM/FM, LC for FM, MPX etc.
- Polyvaricons
- ICs for radio, clock LSI, radio control, MPX decoders etc
- Micrometals Dust iron cores for toroids for resonant and EMI filters
- Toroid mounts
- Hitachi Radio/audio/mpx linear ICs 100W MOSFETs, small signal FETs, MOSFETs and bipolar

And the following groups of products from a broad range of sources:

- Semiconductors - specializing in radio devices, Plessey SL1600, EUROPE's best selection of AM/FM and communications devices. Power MOSFETs, WORLD'S LOWEST NOISE AUDIO small signal transistors, BAR graph LED drivers for linear and log.
- CD4000 series CMOS, TTL/LPSNTTL, standard linears (741, 301, 3080 etc). MPUs, memories.
- Small signal transistors from AEG BC237/8/9 families etc. (1000 off BC239C : 5.2p ea)
- LEDs: AEG 3mm/5mm round, 2.5x5mm flat, red, green, orange, yellow. The best prices you will find for quality products.
- MOSFETs for RF signal processing, including the BF960 UHF device, and 3SK51 for VHF.
- Varicap diodes for 17:1 capacity ratio tuning

FREQUENCY READOUT LSI from OKI with a one-chip answer to most digital frequency display needs (and various modules).

Crystal and ceramic ladder filters from leading manufacturers, ferrite rods, various ferrite beads and a range of crystals for 'standard frequencies and both AM and FM radio control at 27MHz. Trimmer capacitors.

METERS - a new range of linear movement types, plus many 'indicator' types for VU, all types of tuning indicators etc.

SOCKETS - a new range that are better quality than Texas low profile, yet better priced.

Modules for AM/FM/STEREO, complete kits for tuners, audio amplifiers from Larshot.

SWITCHES - complete low cost DIY systems for push button arrays, keyboard switches.

DOUBLE BALANCED MIXERS - MCL SBL1, replacement for MD108 etc. And cheaper.

OUR LATEST MOVING EXPERIENCE :: At last, we have moved to the address below. There is car parking for customers approaching via North Service Road (an extension of North Road Avenue, entrance opposite the Brentwood Fire Station.) Pedestrian access from the High Street (alongside 117 High Street). The new building is six times bigger than our Gresham Road offices, and we will be installing a much expanded sales counter in the fullness of time. NEW TELEPHONE NUMBER (0277) 230909, TELEX NUMBER (as before) 995194 AMBIT G. See you there!

200 North Service Road, Brentwood, Essex.



Receivers and Components

VALVES

Radio - T.V. - Industrial - Transmitting
Projector Lamps and Semiconductors

We Dispatch Valves to all parts of the world by return of post. Air or Sea mail. 4000 Types in stock. 1930 to 1976 Obsolete types a speciality. List 50p. Quotations S.A.E. Open to callers Monday to Saturday 9.30 to 5.00 closed Wednesday 1.00. We wish to purchase all types of new and boxed Valves, Projector Lamps and Semiconductors.

COX RADIO (SUSSEX) LTD.
Dept. P.W. The Parade, East Wittering,
Sussex PO20 8BN
West Wittering 2023 (STD Code 024366)

ELECTRONIC COMPONENTS. Quick delivery, wide range from stock catalogue on request. J. R. Hartley Electronic Components, 78B High Street, Bridgnorth, Salop WV16 4DY.

BRAND NEW COMPONENTS BY RETURN

Electrolytic Capacitors 16V, 25V, 50V
0.47 - 1.0, 2.2, 4.7, & 10 mtds. — 5p.
22, 47 — 5p. (50V-6p.), 100 — 7p. (50V — 8p.)
220 — 8p. (50V-10p.), 470 — 11p. (40V-16p.)
1000/15V — 15p. 1000/25V — 18p. 1000/40V — 35p.

Subminiature bead tantalum electrolytics.
0.1, 0.22, 0.47, 1.0 = 35V 4.7 = 6.3V — 14p.
2.2/35V, 4.7/25V — 15p. 10/25V, 15/18V — 20p.
22/16V, 33/10V, 47/6, 68/3V & 100/3V — 30p.
15/25V, 22/25V, 47/10V — 35p. 47/16V — 60p.

Mullard Miniature Ceramic E12 Series 63V 2%
10 pf. to 47 pf. — 3p. 56 pf. to 330 pf. — 4p.
Vertical Mounting Ceramic Plate Caps 50V
E12 22 pf. — 1000 pf. E6 1500 pf. — 47000 pf. — 2p.

Polystyrene E12 Series 63V. Hor. Mounting.
10 pf. to 820 pf. — 3p. 1000 pf. to 10000 pf. 4p.
Miniature Polyester 250V. Vert. Mtg. E6 Series.
01 — 068 — 4p. 1 — 5p. 15, 22 — 6p. 33, 47 — 10p.
68 — 12p. 1.0 — 15p. 1.5 — 22p. 2 — 24p.

Mylar (Polyester) Film 100V Vertical Mounting.
.001, .0022, .0047 — 3p. .01, .022 — 4p. .04, .05, .01 — 5p.

Miniature Film Resistors Highstab. E12 5%
0.125 watt 10 Ω 2MΩ — 1p
0.250 watt 1 Ω to 10MΩ (10% over 1M) — 1p
0.500 watt 10 Ω to 2MΩ — 2p
1.000 watt 10 Ω to 10MΩ — 2p

1N4148 — 2p, 1N4002 — 4p, 1N4006 — 6p, 1N4007 — 7p
BC107/8/9, BC147/8/9, BC157/8/9, BF194 & 7 — 10p.
8 Pin Dil i.c.'s 741's — 18p, 555's — 24p.

20mm. fuses 15, 25, 5, 1.0, 2.0, 3.0 & 5A — 3p.
20mm. fuseholders P.C. or Chassis Mtg. — 5p.
Post 10p (Free over £4). Prices VAT inclusive.
THE C. R. SUPPLY CO.
127, Chesterfield Road, Sheffield S8 0RN

GRIMSBY ELECTRONIC COMPONENTS. Lambert Road, Grimsby. Hundreds Bargains for callers. List 14p.

AM/CW/SSB COMMUNICATION RECEIVER and preselector modules. The cheapest way to good amateur and BC DX.

CRYSTALS Brand new high-precision. You benefit from very large stocks held for industrial supplies. All normal freq standards, baud rates, MPU, and all magazine projects inc: HC33/U: 1.0, 1.008, 2.5625 MHz, £3.50, 1.280 MHz, £4.15, HC18/U: 4.0, 5.0, 6.0, 7.0, 8.0, 9.0, 10.0, 10.7, MHz £3.00, 12.0, 15.0, 16.0, 18.0, 20.0, 6.9375, 38.6667, MHz, £3.25. Selected freqs stocked in Glider, Marine and 27 MHz bands. Any freq made to order in 6 weeks from £3.90.

FILTERS Your best source for 6 and 8 pole and monolithics for AM, CV, SSB, FM, on 455 kHz, 1.6, 9.0, 10.7, 21.4 MHz, etc.
Prices inc. VAT and UK post. SAE lists.

P. R. GOLLEDGE ELECTRONICS
G3EDW, Marriott, Somerset, TA16 5NS.
Tel: 0480 73718

TUNBRIDGE WELLS COMPONENTS, BALLARD'S, 108 Camden Road, Tunbridge Wells, Tel: 31803. No Lists. Enquiries S.A.E.

SMALL ADS

The prepaid rate for classified advertisements is 24 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £8.00 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Practical Wireless and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance should be sent to the Classified Advertisement Manager, Practical Wireless, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846)

NOTICE TO READERS

Whilst prices of goods shown in classified advertisements are correct at the time of closing for press, readers are advised to check with the advertiser both prices and availability of goods before ordering from non-current issues of the magazine.

Southern Valve Co., 2nd Floor, 6 Potters Road, New Barnet, Herts.

Tel: 01-440 8641 for current prices & availability, all popular valves stocked. **NO CALLERS**, SAE Lists. Cash with order. Same Day Postal Despatch. Telephone afternoons preferred.

Valves, Tubes, Aerials etc by LEADING-MAKERS. Send SAE Lists or Phone for current prices. Counter or MAIL ORDER. NO COD. Speedy Despatch assured. No order under £1.

Philip Bearman, 6 Potters Road, New Barnet, Herts.
Tel: 01-449 1934/5 (1934 Recording Machine).
Telephone for Shop Hours.

10 LEDS. Mixed colours-sizes £1.15. Lists 15p. Sole Electronics, (P.W.) 37 Stanley Street, Ormskirk, Lancs.

NOSTALGIA COLLECTING THE VINTAGE WIRELESS COMPANY 1920 to 1950

Receivers, valves, components, service data, historical research books, magazines, repairs and restorations. A complete service for the collector and enthusiast of vintage radio.
S.a.e. with enquiries and for monthly newsheet. '1980 Catalogue £1.00.'

THE VINTAGE WIRELESS COMPANY, 64, Broad Street, Staple Hill, Bristol BS16 5NL. Tel. Bristol 565472.

VHF CONVERTER. 45-220MHz. 29-30MHz tuneable IF. £7.00 inc. post. SAE data, lists. H. Cocks, Bre Cottage, Staplecross, Robertsbridge, Sussex. Tel: 058083-317.

Record Accessories

STYLI, Cartridges for Music Centres, etc., FREE List No. 29 for S.A.E. includes Leads, Mikes, Phones etc. Felstead Electronics (PW), Longley Lane, Gatley, Cheadle, Ches. SK8 4EE.

Educational

TECHNICAL TRAINING

Get the training you need to move up into a higher paid job. Take the first step now—write or phone ICS for details of ICS specialist homestudy courses on Radio, TV, Audio Eng. and Servicing, Electronics, Computers, also self-build radio kits. Full details from:

ICS SCHOOL OF ELECTRONICS
Dept. T277 Intertext House, London SW8 4UJ
Tel. 01-622 9911 (all hours)
State if under 18

CITY & GUILDS EXAMS

Study for success with ICS. An ICS homestudy course will ensure that you pass your C. & G. exams. Special courses for: Telecoms, Technicians, Electrical Installations, Radio, TV & Electronics Technicians, Radio Amateurs, Full details from:

ICS SCHOOL OF ELECTRONICS
Dept. T277 Intertext House, London SW8 4UJ
Tel. 01-622 9911 (all hours)
State if under 18

COLOUR TV SERVICING

Learn the techniques of servicing Colour TV sets through new homestudy course approved by leading manufacturers. Covers principles, practice and alignment with numerous illustrations and diagrams. Other courses for radio and audio servicing. Full details from:

ICS SCHOOL OF ELECTRONICS
Dept. T277 Intertext House, London SW8 4UJ
Tel. 01-622 9911 (all hours)
State if under 18

TELEVISION & VIDEO SYSTEMS SERVICING

18 MONTHS full-time Diploma course to include a high percentage of practical work.

- ELECTRONIC PRINCIPLES
- MONO & COLOUR TELEVISION
- CLOSED CIRCUIT TELEVISION
- VIDEO CASSETTE RECORDING
- DIGITAL TECHNIQUES & TELETEXT
- COMPUTERS & MICROPROCESSORS

Shortened courses for applicants with suitable electronics background.

Next sessions starts April 21st.

(Also available 2½ year course in Marine Electronics & Radar for employment as ships Radio Officer.)

Prospectus from:

LONDON ELECTRONICS COLLEGE

Dept; B4, 20 Penywern Road,
London SW5 9SU. Tel. 01-373 8721.

Books and Publications

Build your own

P.A., GROUP & DISCO SPEAKERS

by R. F. C. Stephens

Save money with this practical guide. Plans for 17 different designs, line source, I.B., Horn and Reflex types, for 8"-18" drive units. £3-95 post free (£8 overseas).

THE INFRA-BASS LOUDSPEAKER

by G. Holliman

(full constructional details for versions using 15", 12" and 10" drive units) £2-95 post free (£6 overseas)

THE DALESFORD SPEAKER BOOK

by R. F. C. Stephens

This book is a must for the keen home constructor. Latest technology DIY designs. Plans for I.B., and Reflex designs for 10-100 watts. Also unusual centre-bass system. £2-20 post free (£5 overseas).

VAN KAREN PUBLISHING

5 SWAN STREET, WILMSLOW, CHESHIRE

FULL REPAIR data any named T.V. £5.50, with circuits, layouts, etc., £7. (AUSW) 76 Church Street, Larkhall, Lanarks ML9 1HE.

ASSISTANT FILM RECORDISTS AND TRAINEES

Would you like to specialise in sound with the BBC TV's Film Department?
There are vacancies in West London.

ASSISTANT FILM RECORDISTS work initially in sound transfer and dubbing areas operating sound recording and reproduction equipment for a wide range of programmes. There are prospects of progressing to mobile Film Recording work in due course. If you have professional experience in this field, the starting salary would be £4,185 p.a., perhaps higher if exceptionally qualified, rising to £5,605 p.a. An additional allowance is paid for shift work (not nights). Normal hearing essential.

EXCELLENT TRAINING is given if you have ambitions to do this type of work but lack

experience. You will need good 'O' level standard of education or equivalent, including Physics and Maths and a basic knowledge of electronics. You should be able to demonstrate a practical interest in sound and recording. Trainees will start at a salary of £3,800 p.a. at the end of August 1980, and should qualify for promotion to Assistant Film Recordists about a year later.

Salary review date April. Conditions of Service excellent. Contact us immediately for application form (quote ref. 2053/PW and enclose s.a.e.): **BBC Appointments, London W1A 1AA. Tel: 01-580 4468 Ext: 4619.**



TESTERS, Test Technicians, Test Engineers - Earn what you're really worth in London Working for a World Leader in Radio & Telecommunications. Phone Len Porter on 01-874 7281 or write - REDIFON TELECOMMUNICATIONS LTD., Broomhill Road, Wandsworth, London SW18.

Aerials

KILL THAT INTERFERENCE

G2DYM ANTI-T.V.I. TRAP DIPOLES:

S.W.L. Indoor models **£14.50 & £27.50**
S.W.L. Outdoor models **£30.00 & £34.50**
Tx-ing models **£42.50, £52.50 & £59.75**
Lists 10x8in SAE. Aerial Guide **50p.**
Indoor and invisible aerials for S.W.L.'s **£3.50.**

G2DYM, Uplowman, Tiverton, Devon.

AERIALS for T.V. (Bands 1 to U.H.F.), Radio (A.M./F.M.) plus large range of amplifiers, masts and mounting hardware for 'local' and DXing use listed in our NEW 6 page catalogue (20p stamps): SOUTH WEST AERIAL SYSTEMS (PW) 10, Old Boundary Road, Shaftesbury, Dorset. 0747 4370.

AERIAL BOOSTERS

Improves weak VHF Radio and Television reception.
B45-UHF TV, B11-VHF Radio. B11A-2 metres
For next to the set fitting. **Price £6.**

SIGNAL INJECTOR

A complete range of AF and RF frequencies up to the UHF Band. **Price £5.00.**
S.A.E. for Leaflets. ACCESS

ELECTRONIC MAILORDER LTD,
62 Bridge Street,
Ramsbottom, Bury, Lancs, BL0 9AG.

COPPER AERIALS WIRE 14swg hard drawn 70' **£3.50.**
140' **£7.00** inc. VAT. Postage £1.15. T.M.P. Electronics, Supplies, Britannia Stores, Leeswood, Nr. Mold, N. Wales.

Service Sheets

G.T. THE TECHNICAL INFORMATION SERVICE

76 CHURCH ST., LARKHALL, LANARKS ML9 1HE

Any single service sheet for £1 and large S.A.E.

1000's of different service sheets, service manuals and repair manuals always kept in stock for immediate despatch. S.A.E. brings newsletter; pricelist; bargain offers such as service sheets under 40p; quotations for any requested service sheets/manuals without obligation.

Save time and money - 2 giant catalogues listing thousands of service sheets/manuals plus £4 worth of vouchers free - send £2 + large S.A.E.

LARGE SUPPLIER OF SERVICE SHEETS

and Colour Manuals, TV Mono Radios, Tuners, Tape Recorders, Record Players, Transistors, Stereograms, all at 75p each + S.A.E. except colour TV from £1.00 and Car Radios £1.25. State if Circuit will do, if sheets are not in stock. All TV Sheets are full lengths 24 x 12, not in Bits & Pieces. Free Fault Finding Chart of TV Catalogue with order. All crossed PO's returned if service sheets are not in stock.

C. CARANNA
71, Beaufort Park, London, NW11 6BX
01-458 4882 (Mail Order)

Wanted

WANTED RADIO and Television Servicing Books from 1970 to present day. J. G. Bennett, "Malaga" Hollacombe Brake, Wembury, Plymouth. (Plymouth 862262).

ELECTRONIC COMPONENTS PURCHASED. All types considered - Must be new. Send detailed list - Offer by return - WALTONS, 55A Worcester Street, Wolverhampton.

REQUIRED Circuit Diagram and/or Manual for Erskine Laboratories Oscilloscope Type 13 (REF: IOS/825). Reply Box 148.

PX4, PX25 and equivalent valves, new or used, plus all types of bright emitter valves, Vintage Wireless Co., (see advert on Page 82).

SERVICE SHEETS from 50p and S.A.E. Catalogue 25p and S.A.E. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex.

SERVICE SHEETS, Radio TV etc., 10,000 Models. Catalogue 24p, plus SAE with orders, enquiries. Telfray, 154 Brook Street, Preston, PR1 7HP.

BELL'S TELEVISION SERVICES for Service Sheets on Radio, TV etc., £1.00 plus S.A.E. Colour TV Service Manuals on request. S.A.E., with enquiries to B.T.S., 190 Kings Road, Harrogate, N. Yorkshire. Tel: (0423) 55885.

For Sale

PRACTICAL TELEVISION first edition April 1950-Dec 1962 complete. Offers. C. Dykes, 162 Crofton Lane, Petts Wood, Kent.

OSCILLOSCOPE-DUAL BEAM Scopex 4D10A little used recently serviced £195 o.n.o. 12 Boskennal Drive, Hayle, TR27 4QX.

HRO COMMUNICATION RECEIVER Excellent Condition 9 Coils, 50KHz - 30MHz, Power pack, spare valves. What offers???. Tel: Greenham 672086.

HARTLEY/SOLARTRON C.T. 436 Oscilloscopes. Two only. full working order. £70 each. Manual £5. Rainford 4729 evenings.

NEW BACK ISSUES OF "PRACTICAL WIRELESS" available 80p each, post free. Open P.O./Cheque returned if not in stock - **BELL'S TELEVISION SERVICE**, 190 Kings Road, Harrogate, N.Yorks. Tel: (0423) 55885.

COMMUNICATIONS RECEIVER Yaesu FRG-7000 3 months old practically unused. Cost £375.00 accept £325.00. R. Hawkes, 40 Park Road, Colwyn Bay, North Wales. Telephone 31202.

Miscellaneous

PRACTICAL WIRELESS P.C.B.'s

Dec 78	Doorchime £2.90	Jan 79	P.W. Sandbanks £2.90
Feb 79	Hythe Ra £4.80	Mar 79	Hythe P.S.U. £2.40
Mar 79	Soundlite Converter £4.80	Apr 79	F.M. Multimeter £1.70
May 79	P.W. Imp £1.20	Jun 79	Logical D-X's test £11.00
July 79	V.M.O.S. Tx £3.20	July 79	Sound Operated Switch £2.85
July 79	A/F Voltmeter £0.90	Aug 79	Auto Intercom £4.78
Aug 79	Teletext Repeater £0.90	Sept 79	F.M. Noise Blanker £0.90
Sept 79	Door Unit £0.40	Oct 79	Burglar Alarm WNG50 £1.20
Oct 79	Burglar Alarm 059 £1.10	Dec 79	Radio Control Rx £1.50
Jan 80	Radio Control Encoder £2.00	Jan 80	Radio Control Tx £1.30
Jan 80	Speech Processor £1.80	Jan 80	Microwave Detector £1.50
Jan 80	Wideband Amp £0.70	Feb 80	Servo Unit £0.70

P.C.B.'s and fascia panels to your design at realistic prices. Boards not advertised sent on approval. All our P.C.B.'s high quality fibre glass to BS 4584 Mil Spec 139496 GAN.

H.T.E. (ELECTRONICS) DEPT. P.W.
50 MILNEFIELD AVE., ELGIN, MORAY

SUPERB INSTRUMENT CASES by Bazelli, manufactured from P.V.C. Faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range. Competitive prices start at a low £1.05. Chassis punching facilities at very competitive prices. 400 models to choose from. Suppliers only to Industry and the Trade. **BAZELLI**, (Dept No.25) St. Wilfreds, Foundry Lane, Halton, Lancaster. LA1 6LT.

QUALITY ELECTRONIC COMPONENTS AT LOW PRICES

Write or Telephone for free pamphlet to:-

HARRISON BROS, Dept. P.W.
P.O. Box 55, Westcliffe-on-Sea,
Essex SS0 7LQ.
Telephone:- Southend-on-Sea 32338

GUITAR/PA/ MUSIC AMPLIFIERS

100 watt superb treble/bass overdrive. 12 month guarantee. Unbeatable at £46; 60 watt £38; 40 watt £34; 200 watt £60; 100 watt twin channel sep. treble/bass per channel £58; 60 watt £48; 200 watt £72; 100 watt four channel sep. treble/bass per channel £75; 200 watt £92; slaves 100 watt £32; 200 watt £50; fuzz boxes, great sound £10; bass fuzz £10.90; overdriver fuzz with treble and bass boosters £18; 100 watt combo superb sound overdrive, sturdy construction, castors, unbeatable £92; twin channel £100; bass combo £105; speakers 15in. 100 watt £35; 12in. 100 watt £23; 60 watt £16; microphones Shure Unidyne B £26.

Send cheque or P.O. to:

WILLIAMSON AMPLIFICATION
62 Thorncliffe Avenue, Dukinfield, Cheshire.
or 061-308 2064.

THE SCIENTIFIC WIRE COMPANY

PO Box 30, London E.4
Reg. Office 22 Coningsby Gdns

ENAMELLED COPPER WIRE

SWG	1 lb	8 oz	4 oz	2 oz
10 to 29	3.10	1.86	1.10	.80
30 to 34	3.50	2.00	1.15	.80
35 to 39	3.95	2.36	1.34	.98
40 to 43	5.10	2.97	2.28	1.42
44 to 46	6.00	3.60	2.50	1.91
47	8.37	5.32	3.19	2.50
48 to 49	15.96	9.58	6.38	3.69

SILVER PLATED COPPER WIRE

14 to 22	5.30	3.03	1.85	1.20
24 to 30	6.50	3.75	2.20	1.40

Prices include P&P and VAT.

Orders under £2 please add 20p. SAE for list.
Dealer enquiries welcome.

C.W.A.S. ALARM. Send now for the latest discount catalogue of professional Burglar Alarm Equipment. C.W.A.S. Alarm, 11 Denbrook Walk, Bradford BD4 0QS, W. Yorks. Phone 0274 682674.

LEARN ELECTRONICS WITHOUT SOLDER

Build electronic circuits without solder on a Roden S-Dec. This has built-in contacts and holes into which you plug your components. Suitable for all ages. Can be used time after time. Ideal gift for students or experimenters. Full instructions and 2 circuit diagrams with each S-Dec.

Send cheque or P.O. to:-
Roden Products, Dept PW
High March, Daventry,
Northants, NN11 4QE

£3.85 plus 40p p.&p. each

EDDYSTONE 640 Receiver Loud Speaker Mains converter and valves. Construction details available. Glasgow Area. Box 149.

MORSE CODE TUITION AIDS

Cassette A: 1-12 w.p.m. for amateur radio examination. Cassette B: 12-24 w.p.m. for professional examination preparation. Each Cassette are type C90.

Morse Key and Buzzer unit for sending practice. Price each Cassette (including booklets) £4.75. Morse Key and Buzzer £4.75.

Prices include postage etc. Overseas Airmail £1.50 extra.

MHEL ELECTRONICS (Dept P.W.), 12 Longshore Way, Milton, Portsmouth PO4 8LS.

CHRISTIAN FRIENDSHIP introduction. All Ages. Nationwide. Singles Holidays. Weekend Houseparties. Local Groups. Details - C.F.F., Dept. B89, Edenthorpe, Doncaster. (SAE).

NICKEL CADMIUM BATTERIES

Rechargeable and suitable for fast charge HP7 (AA) £1.05. SUB C £1.36. HP II (C) £1.98. HP 2 (D) £3.02. PP 3 £3.79. PP 3 charger £5.40.

All the above nickel cadmium batteries are brand new and are guaranteed full spec. devices.

All cells are supplied complete with solder tags (except PP 3).

Brand new full spec. RECHARGABLE SEALED LEAD ACID maintenance free batteries suitable for burglar alarms etc. 1.2 amp hr. 6v £4.07 2.6 amp hr. 6v £5.23.

Quantity prices available on request. Data and charging circuits free on request with orders over £10, otherwise 30p post and handling (specify battery type). Please add 10% P&P on orders over £10 - 5% over £10. VAT at the current rate should be added to total order. Cheques, Postal Orders. Mail order to:-

SOLID STATE SECURITY DEPT. (PW),
10 Bradshaw Lane, Parbold, Wigan Lancs.
Tel: 02575 4728.

SEEN MY CAT? 5000 Odds and ends. Mechanical. Electrical. Cat. free. Whiston (Dept. PW) New Mills, Stockport.

KEEP ONE HANDY IN THE WORKSHOP



The unique aerosol treatment for minor burns and scalds. From Boots and other Chemists.

LOSING DX?

RARE ONES UNDER QRM? Dig them out with a Tuneable Audio Notch Filter, between your receiver and speaker. BOOST your DX/QRM ratio. 40dB notch. 350-5000Hz. MORE DX for only £8.90.

ABSOLUTE TIME? MSF Clock is always correct, never gains or loses. 8 digits show Date, Hours, Minutes and Seconds, also second-in-a-month STOP CLOCK and parallel BCD output, receives Rugby time signals, built-in antenna. EXACT TIME £48.80.

V.L.F. EXPLORE 10-150kHz. Receiver £10.70.

MISSING RARE DX? Get SPOT-ON with a Crystal Calibrator, between your antenna and receiver. 1MHz, 100, 25kHz markers. DIAL-UP the DX. £15.80.

LONG WAVE DX? Exciting 100-600kHz Converter to 4.1-4.6MHz, built-in tuner, GO LOW for £10.90.

SIG. GEN., 10Hz-200kHz, logic and variable sine and square wave outputs, ideal TESTING. £10.80.

Each fun-to-build kit includes all parts, printed circuit, case, postage etc. money back assurance so SEND off NOW.

CAMBRIDGE KITS

45 (PD) Old School Lane, Milton, Cambridge.

PRINTED CIRCUITS. Make your own simply, cheaply and quickly! Golden Fotolac Light Sensitive Lacquer - now greatly improved and very much faster. Aerosol cans with full instructions. £2.25. Developer 35p. Ferric Chloride 55p. Clear Acetate sheet for master 14p. Copper-clad Fibre-glass Board approx. 1mm thick £1.70 sq. ft. Post/Packing 60p. White House Electronics, P.O. Box 19, Penzance, Cornwall.

PLEASE MENTION PRACTICAL WIRELESS WHEN REPLYING TO ADVERTISEMENTS

ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Practical Wireless for insertions I enclose Cheque/P.O. for £.....

(Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Practical Wireless).

NAME.....

ADDRESS.....

Send to: Classified Advertisement Manager

PRACTICAL WIRELESS,
GMG, Classified Advertisement Dept., Rm. 2337,
King's Reach Tower, Stamford Street,
London SE1 9LS Telephone 01-261 5846

Rate
24p per word, minimum 12 words. Box No. 60p extra.

TRANSFORMERS

30 VOLT RANGE
Pri 220/240 sec 0-12-15-20-24-30V
Voltages available 3, 4, 5, 6, 8, 9, 10,
12, 15, 18, 20, 24, 30V or 12V-0-12V
and 15V-0-15V.

Ref	Amps	Price	P & P
112	0.5	2.90	0.90
117	1.0	3.93	1.10
3	2.0	6.35	1.10
20	3.0	6.82	1.31
21	4.0	10.79	1.31
51	5.0	10.86	1.52
117	6.0	12.29	1.67
88	8.0	16.45	1.89
89	10.0	18.98	1.89
90	12.0	21.09	2.24
91	15.0	24.18	2.39
92	2.0	32.40	O.A.

50 VOLT RANGE
Pri 220/240V Sec 0-20-25-33-40-
50V Voltages available 5, 7, 8, 10, 13,
15, 17, 20, 33, 40 or 20V-0-20V and
25V-0-25V.

Ref	Amps	Price	P & P
102	0.5	3.75	0.90
103	1.0	4.57	1.10
104	2.0	7.88	1.31
105	3.0	9.42	1.52
106	4.0	13.32	1.73
107	6.0	16.37	1.89
118	8.0	22.29	2.39
119	10.0	27.48	O.A.
109	12.0	31.89	O.A.

MAINS ISOLATORS (SCREENED)
PM 120/240 Sec 120/240V CT

Ref	VA	Price	P & P
*07	20	4.84	0.91
149	60	7.37	1.10
150	100	8.38	1.31
151	200	12.28	1.31
152	250	14.61	1.73
153	350	18.07	2.12
154	500	22.52	2.47
155	750	32.03	O.A.
156	1000	40.92	O.A.
157	1500	56.52	O.A.
158	2000	67.99	O.A.
159	3000	95.33	O.A.

*Pri 0-220-240V Sec 115 or 240V.
State sec. volts required.

CASED AUTO TRANSFORMERS
240V cable in 115V USA flat pin outlet

VA	Price	P & P	Ref
20	6.55	1.03	56W
75	8.50	1.31	64W
150	11.00	1.31	4W
200	12.02	1.67	65W
250	13.88	1.67	69W
500	20.13	1.89	67W
1K	30.67	2.65	84W
1.5K	42.82	O.A.	93W
2K	54.97	O.A.	95W

Continuous Ratings + VAT 15%

60 VOLT RANGE
Pri 220/240V sec 0-24-30-40-48-
60V. Voltages available 6, 8, 10, 12,
16, 18, 20, 24, 30, 36, 40, 48, 60 or
24V-0-24V or 30V-0-30V.

Ref	Amps	Price	P & P
124	0.5	4.27	1.10
126	1.0	6.50	1.10
127	2.0	8.36	1.31
125	3.0	12.10	1.31
123	4.0	13.77	2.12
40	5.0	17.42	1.89
120	6.0	19.87	2.12
121	8.0	27.92	O.A.
122	10.0	32.51	O.A.

END OF LINE OFFERS

Ref	Description	Price	P & P
30	Isolator 240V:240V 200VA	£4.62	£1.10
62	Isolator 240V:240V 250VA	£5.72	£1.10
M616	- 0-240V: Screen 1) 13-0-13 1A. 2) 12V 150ma	£2.10	60p
M489	- 0-240V: 1400V = 150ma, 6 3V = 4A	£5.50	£1.04
M708	- 6K to 3KΩ matching trans. 5 watt	90p	40p
M679	- 0-120V x 2: 36V 1.6A	£3.00	78p
M865	- 100V Line to 4Ω 10 watts	£1.90	60p
M973	- 100V Line to 8Ω 40 watts	£2.90	60p
M1020	- 0-240V 12-0-12V = 50ma	75p	30p
M1126	- 120/240V: 9-0-9V = 1A	£1.79	71p
M1130	- 0-240 4500V = 10ma	£4.86	£1.08
M1165	- 0-115-240V: 14V 50ma	75p	30p

Metal Oxide Resistors 1/2W 5% TR4 (Electrosil)

390Ω/470Ω/510Ω/560Ω/820Ω/1K/1K1/1K2/1K6
1K8/2K/2K4/3K/16K/20K/22K/24K/47K/82K/100K
110K/120K/130K/180K/220K/270K/300K

£1.50/100 + VAT.

Antex Soldering Irons 15W & 25W £4.58 each
Safety Stand £1.75 P & P 52p each

P.W. Purbeck oscilloscope transformer 250-0-250;
6-3V; 12-9V £7.51 £1.04

12 OR 24V OR 12-0-12V
Pri 220-240 volts

Ref	12V	24V	Price	P & P
111	0.5	0.25	2.42	0.52
213	1.0	0.5	2.90	0.90
71	2	1	3.86	0.90
18	4	2	4.46	1.10
85	0.5	2.5	6.16	1.10
70	6	3	6.99	1.10
108	8	4	8.16	1.31
72	10	5	8.93	1.31
116	12	6	9.89	1.52
17	16	8	11.79	1.52
115	20	10	15.38	2.39
187	30	15	19.72	2.39
226	60	30	40.41	O.A.

SPECIAL OFFER
Multimeter 20KΩ B/V
- with combined
audio/F. test oscillator
at 1 KHz and 465 KHz
AC/DC to 1000 volts
DC current to 500mA
resistance to 1KΩ. Size
160x97x40mm
£8.50 P & P £1.00
VAT 15%.

SCREENED MINIATURES

Ref	mA	Volts	£	P & P
238	200	3-0-3	2.83	0.63
212	1A, 1A	0-6-0-6	3.14	0.90
13	100	9-0-9	2.35	0.44
235	330, 330	0-9-0-9	2.19	0.44
207	500, 500	0-8-9-0-8-9	3.05	0.85
208	1A, 1A	0-8-9-0-8-9	3.88	0.90
236	200, 200	0-15-0-15	2.19	0.44
214	300, 300	0-20-0-20	3.08	0.90
212	700 (DC)	20-12-0-12-20-3.75	0.90	
206	1A, 1A	0-15-20-0-15-20	5.09	1.10
203	500, 500	0-15-27-0-15-27	4.39	1.10
204	1A, 1A	0-15-27-0-15-27	6.64	1.10
239	50	12-0-12	2.88	0.37

AVO TEST METERS

AVO 8 MK5	£91.50
AVO 71	£38.00
AVO 73	£50.70
AVO MM5 minor	£35.95
Wee Megger	£76.28
TT169 in circuit transistor tester	£41.53
EM272 316KΩ - Volts	£59.80
DA116 Digital	£110.90
BM/ Megger	£53.76
Clamp Meter to 300A	£54.60

All Avos Meggers and accessories available.
P & P £1.32 VAT 15%

20,000 ohm/V Multimeter, mirror scale
Ranges AC DC to 1000V DC current to 250mA
Resistance to 3 Mohms
5" x 3 1/2" x 1 1/2" £14.36 P & P £1.00 VAT 15%

U4315 Budget Meter, 20KΩ/V Ranges to
1000V 2.5A AC/DC 500KΩ Res. In steel case
£15.85. PP £1.15 VAT 15%

NEW RANGE TRANSFORMERS
2 windings 0-36V-48V/36V-0-36V 48V-0-48V
72V or 96V.

Amps	Ref	Price	P & P
1.0	430	4.88	0.76
1.0	431	8.12	0.99
2.0	432	13.35	1.31
3.0	433	16.17	1.40
4.0	434	20.65	2.11
5.0	435	29.30	2.47
8.0	436	36.69	O.A.
8.0	437	40.03	O.A.

PANEL METERS

43mm x 43mm	82mm x 78mm	
0.500mA	0.500A	6.70
0.500mA	0.500A	6.70
0.1mA	0.1mA	6.70
3.0V	0.30V	6.70
VU ind Panel 48mm x 45mm		2.60
VU Ind E/F 54 x 14mm		2.60
250µA F.S.D		2.60

Carriage 76p VAT 15%

Barrie Electronics Ltd.

3, THE MINORIES, LONDON EC3N 1BJ
TELEPHONE: 01-488 3316/7/8

TECHNICAL TRAINING IN ELECTRONICS TELEVISION AND RADIO SERVICING

ICS can provide the technical knowledge that is so essential to your success, knowledge that will enable you to take advantage of the many opportunities open to the trained person. You study in your own home, in your own time and at your own pace and if you are studying for an examination ICS guarantee coaching until you are successful.

City & Guilds Certificates:
Telecommunications Technicians
Radio, TV, Electronics Technicians
Technical Communications
Radio Amateurs
Electrical Installation Work

Diploma Courses:
Colour TV Servicing
Electronic Engineering and Maintenance
Computer Engineering and Programming
Radio, TV, Audio Engineering and Servicing
Electrical Engineering, Installation
and Contracting

POST OR PHONE TODAY FOR FREE BOOKLET

IGS To: International Correspondence Schools

Dept. T276 Intertext House, LONDON
SW8 4UJ or telephone 622 9911

Subject of interest.....

Name.....

Address.....

Tel:.....

PLEASE MENTION
**PRACTICAL
WIRELESS**
WHEN
REPLYING TO
ADVERTISEMENTS

PRACTICAL WIRELESS T.V. SOUND TUNER

(Nov. 75 article by A. C. Ainslie) Copy of original article supplied on request

IF Sub-Assembly (G8) £7.82. P & P 85p.
Mullard ELC1043 V'cap UHF Tuner £6.33. P & P 40p.
3-way Station Control Unit £1.38. P & P 30p.
6-way Station Control Unit (Special Offer) £1.15. P & P 35p.
Power Supply Prtd Circuit Board £1.15. P & P 35p.
Res, Caps, Semiconds, etc. for above £6.67. P & P 45p.
Mains Transformer for above £3.80. P & P 35p.
P & P all items £1.00.

(Price of goods and P & P includes 15% VAT)

Callers welcome at shop premises.

MANOR SUPPLIES

172 WEST END LANE, LONDON NW6

(Near W. Hampstead Tube Stn.) Tel. 01-794 8751

WATFORD ELECTRONICS

33/35, CARDIFF ROAD, WATFORD, HERTS, ENGLAND
MAIL ORDER, CALLERS WELCOME. Tel. Watford 40588/9

ALL DEVICES BRAND NEW. FULL SPEC. AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/ORDER/P.O. BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS OFFICIAL ORDERS ACCEPTED. TELEPHONE ORDERS BY ACCESS NOW ACCEPTED (Minimum order £10.00 please). TRADE AND EXPORT INQUIRY WELCOME. P & P ADD 30P TO ALL ORDERS UNDER £10.00. OVERSEAS ORDERS POSTAGE AT COST.

VAT Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 15% to the total cost.

We stock many more items. It pays to visit us. We are situated behind Watford Football Ground, Nearest Underground/Br. Rail Station: Watford High Street. Open Monday to Saturday 9 a.m.-6 p.m. Ample Free Car Parking space available.

POLYESTER RADIAL LEAD CAPACITORS: 250V:
10n, 15n, 22n, 27n 5p; 33n, 47n, 68n, 100n 7p; 150n 10p; 220n, 330n 13p; 470n 17p; 680n 19p; 1µ 22p; 1.5µ 30p; 2.2µ 34p.

ELECTROLYTIC CAPACITORS: Axial lead type (Values are in µF).
500V: 10 40p; 47 68p; 250V: 100 65p; 63V: 0.47, 1.0, 1.5, 2.2, 2.5, 3.3, 4.7, 6.8, 8, 10, 15, 22, 27, 33, 47, 50 12p; 63, 100, 270, 50V: 1.0 7p; 50, 100, 220 25p; 470 32p; 1000 50p; 40V: 2.2, 3.3µF 10p; 10µ 12p; 2200, 3300 85p; 4700 98p; 10, 33 7p; 330, 470 32p; 1000 50p; 25V: 10, 22, 47 6p; 80, 100, 180 8p; 220, 250 13p; 470, 640 25p; 1000 27p; 1500 30p; 2200 45p; 3300 62p; 4700 74p; 15µ: 10, 40, 47, 68 7p; 100, 125 8p; 220, 330 14p; 470 16p; 1000, 1500 20p; 2200 34p; 100V: 100 6p.

TAG-END TYPE 450V: 100µF 180p; 70V: 4700 165p; 64V: 3300 130p; 250V 38p; 50V: 3300 105p; 2200 99p; 40V: 15,000 399p; 4700, 1200, 4000 92p; 3300 95p; 2500 85p; 2200 85p; 2000, 2000 120p; 30V: 4700 90p; 25V: 6400 105p; 4700 85p; 3300 80p; 2200 60p.

TANTALUM BEAD CAPACITORS
35V: 0.1µF, 0.22, 0.33, 0.47, 0.68, 1.0, 2.2µF, 3.3, 4.7, 6.8, 25V: 1.5, 10, 20V: 1.5µ, 16V: 10µF, 13p each.
16V: 15p, 22 25p; 47, 100 22p, 40p.
10V: 15p, 22, 33 20p, 100 35p; 6V: 47p, 68, 100 30p; 3V: 100 20p.

POLYESTER (MYLAR) CAPACITORS
100V: 0.001, 0.002, 0.005, 0.01µF 5p
0.015, 0.02, 0.03, 0.04, 0.05, 0.05µF 7p
0.1µF 8p, 0.2 10p. 50V: 0.47µF 12p

CERAMIC CAPACITORS 50V
Range: 0.5pF to 10nF
15nF, 22nF, 33nF, 47nF 5p 100nF 7p

POLYSTYRENE CAPACITORS:
100pF to 1nF, 6p. 1.5nF to 47nF 10p.

RESISTORS—5% carbon, High Stab. Miniature. Low Noise
Range Val. 1-99 100-1000
1/4 202-4M7 E12 2p 1p
0.5W 202-4M7 E24 2p 1p
1W 202-10M E12 5p 3p
2" Metal Film 100-1M 6p 4p
1% 0.5W 10-1M E24 10p 8p
N.B. 100% spec. applies to Resistors of each type non-mixed values.

VEROBOARD
Pitch 0.1 0.15
(copper clad) (plain)
21-34 46p 39p 31p 24p
21-5 55p 50p — 31p
34-5 55p 50p — —
34-17 62p 67p 50p 43p
21-17 21p 18p 14p 12p
41-17 28p — — —
Pkt of 36 pins 20p VQ Board 90p
Spot face cutter 85p DIP Board 268p
Pin insertion tool 120p S' Board 1270p

COPPER CLAD BOARDS
Fibre Single-sided SRBP
Glass Double-sided 9.5" x 8.5"
6" x 6" 75p 90p 80p
6" x 12" 130p 175p

FERRIC CHLORIDE
1lb 95p 35p p&p

EURO BREAD-BOARD 530p

DALO ETCH RESIST PEN 75p

VERORINGING PEN
100 pins 50p; 500 pins £2.00

DIL SOCKETS
Low Wire profile wisp
8 pin 10p 25p
14 pin 12p 35p
16 pin 13p 46p
18 pin 16p 52p
20 pin 22p 65p
22 pin 25p 70p
24 pin 36p 78p
28 pin 39p 85p
40 pin 50p 109p

EDGE CONNECTORS
2 10 way — 156p
2 15 way — 99p
2 18 way 115p 120p
2 22 way 130p 135p
2 25 way 149p 160p
2 30 way 170p —
2 36 way 194p —
2 40 way 210p —
2 43 way 232p —

DENCO COILS
Dual Purpose 'DP'
VALVE TYPE
Ranges: 1-5 Bl. Yl.
Rd. Wht. 92p
6-7 B. Y. R 82p
1-5 Green 100p
T-type (Transistor Tuning).
Rd. Wht. 92p
1-5 Bl. Yl. 88p
MW/LFR 112p
MW/LFR 5FR 112p

JACKSONS VARIABLE CAPS.
Dielectric 0.2 to 365pF with slow motion Drive 345p
100/300pF 160p
500pF 180p
6:1 Ball Drive
4511/DAF 115p
motion Drive
Drum 54mm 650p
0.1-365pF 245p
0.2-265pF 275p
0.0-2-500pF 525p

TRANSISTORS

AC125	20	BC338	12	BSX20	18	TIS88A	00	2N3819	22	LS112	55	74LS398	276
AC126	20	BC441	36	BS95A	18	TIS90	20	2N3820	45	LS113	55	74LS399	230
AC127	20	BC461	36	BU105	140	TIS91	24	2N3866	20	LS114	50	74LS447	144
AC128	20	BC477	25	BU205	190	TX107	12	2N3870	12	LS122	70	74LS490	180
AC129	20	BC516	20	BU208	225	TX108	12	2N3903	20	LS123	70	74LS668	182
AC130	20	BC547	12	E421	188	TX109	14	2N3904	18	LS124	180	74LS670	248
AC131	40	BC548	12	MD8001	158	TX300	13	2N3905	18	LS125	60	74LS673	1050
AC132	40	BC549C	13	MJ191	180	TX302	20	2N3906	17	LS126	60	74LS674	1450
AC133	40	BC551	15	MJ295	105	TX303	25	2N4057	17	LS132	50		
AC134	40	BC552	15	MJ340	54	TX304	24	2N4058	17	LS136	55		
AC135	40	BC553	15	MJE370	58	TX314	24	2N4061	17	LS138	85		
AC136	40	BC559	20	MJE371	105	TX326	40	2N4427	75	LS139	85		
AC137	40	BC571	20	MJE2955	60	TX326	40	2N4457	75	LS153	76		
AC138	40	BCV72	20	MJ3055	70	TX500	15	2N4859	65	LS154	96		
AC139	78	BCV72	20	MPF102	66	TX501	15	2N4871	25	LS157	25		
AD149	40	BD131	45	MPF103	66	TX502	19	2N5172	25	LS158	96		
AD162	42	BD132	45	MPF104	36	TX503	19	2N5179	60	LS160	128		
AF114	50	BD133	45	MPF105	36	TX504	25	2N5191	70	LS161	96		
AF115	50	BD136	36	MPSA05	25	TX505	25	2N5305	40	LS162	138		
AF116	50	BD137	36	MPSA06	25	TX550	25	2N5458	32	LS163	102		
AF118	65	BD138	50	MPSA12	42	40311	60	2N5485	35	LS164	102		
AF139	35	BD139	40	MPSA55	25	40313	125	2N5642	750	LS165	75		
BF107	70	BD140	36	MPSA56	25	40315	55	2N5777	45	LS166	226		
BF108	70	BD141	36	MPSA57	25	40316	60	2N6027	40	LS168	155		
BF178	10	BD145	198	MPSU56	60	40361	42	3N121	52	LS169	150		
BC108	12	BD205	110	OC26	170	40362	48	3N140	112	LS170	105		
BC108B	12	BD214	115	OC28	150	40408	70			LS171	105		
BC108C	12	BD245	50	OC35	130	40411	295			LS174	106		
BC109	10	BD378	65	OC36	130	40467	60			LS175	110		
BC109B	12	BD517	65	OC42	48	40594	90			LS181	398		
BC140	35	BD695A	65	OC43	55	40595	98			LS183	298		
BC142	30	BD696A	65	OC44	31	40603	65			LS191	140		
BC143	30	BDY56	156	OC45	28	40673	68			LS192	132		
BC147	8	BF16	30	OC71	28	2N697	25			LS193	130		
BC147B	8	BF180	35	OC72	28	2N699	54			LS194	166		
BC148	8	BF194	12	OC74	55	2N706A	18			LS196	106		
BC148B	8	BF195	12	OC76	36	2N708	19			LS197	140		
BC148C	8	BF196	12	OC81	50	2N918	14			LS198	140		
BC149	8	BF197	14	OC82	50	2N1131	22			LS201	34		
BC149C	8	BF198	18	OC83	42	2N1132	22			LS202	36		
BC153	27	BF199	18	OC84	44	2N1303	50			LS203	36		
BC154	27	BF200	32	OC140	110	2N1304	50			LS204	36		
BC158	11	BF224	29	OC170	85	2N1305	28			LS205	36		
BC159	11	BF244	29	OC171	75	2N1671B	215			LS206	36		
BC160	42	BF245	29	OC172	85	2N1672A	22			LS207	36		
BC167A	10	BF246B	30	PIP29	43	2N2204A	26			LS208	36		
BC168	11	BF256	30	PIP29C	60	2N2221A	23			LS209	36		
BC169C	14	BF257	30	PIP30	47	2N2222A	20			LS210	36		
BC170	18	BF258	30	PIP30C	65	2N2369A	15			LS211	36		
BC172	11	BF259	30	PIP31A	52	2N2646	48			LS212	36		
BC173	12	BF274	18	PIP34	58	2N2904	22			LS213	36		
BC177	18	BF336	32	PIP32A	58	2N2905A	22			LS214	36		
BC178	18	BF354	40	PIP32C	75	2N2906	22			LS215	36		
BC179	18	BF355	38	PIP33A	85	2N2907A	22			LS216	36		
BC181	20	BF399	25	PIP33C	105	2N2966G	10			LS217	36		
BC182	9	BF440	25	PIP34A	85	2N3053	20			LS218	36		
BC183	9	BF441	28	PIP34B	110	2N3054	48			LS219	36		
BC184	11	BF480	28	PIP35C	220	2N3442	146			LS220	36		
BC184L	11	BF481	28	PIP36A	220	2N3663	26			LS221	36		
BC187	28	BF482	28	PIP36C	255	2N3702	11			LS222	36		
BC188	28	BF483	28	PIP37A	66	2N3703	11			LS223	36		
BC189	28	BF484	28	PIP37B	66	2N3704	11			LS224	36		
BC191	12	BF485	28	PIP42A	50	2N3705	11			LS225	36		
BC192	12	BF486	28	PIP42B	82	2N3706	11			LS226	36		
BC193L	12	BF487	28	PIP42C	72	2N3707	11			LS227	36		
BC194	10	BF488	28	PIP42D	90	2N3708	11			LS228	36		
BC194L	13	BF490	28	PIP42E	125	2N3709	11			LS229	36		
BC236	36	BF520	28	PIP43	145	2N3710	16			LS230	36		
BC237	36	BF521	28	PIP43A	155	2N3711	16			LS231	36		
BC238	36	BF522	28	PIP43B	155	2N3712	16			LS232	36		
BC239	36	BF523	28	PIP43C	155	2N3713	16			LS233	36		
BC240	36	BF524	28	PIP43D	155	2N3714	16			LS234	36		
BC241	36	BF525	28	PIP43E	155	2N3715	16			LS235	36		
BC242	36	BF526	28	PIP43F	155	2N3716	16			LS236	36		
BC243	36	BF527	28	PIP43G	155	2N3717	16			LS237	36		
BC244	36	BF528	28	PIP43H	155	2N3718	16			LS238	36		
BC245	36	BF529	28	PIP43I	155	2N3719	16			LS239	36		
BC246	36	BF530	28	PIP43J	155	2N3720	16			LS240	36		
BC247	36	BF531	28	PIP43K	155	2N3721	16			LS241	36		
BC248	36	BF532	28	PIP43L	155	2N3722	16			LS242	36		
BC249	36	BF533	28	PIP43M	155	2N3723	16			LS243	36		
BC250	36	BF534	28	PIP43N	155	2N3724	16			LS2			

INDEX TO ADVERTISERS

A. H. Supplies	12
Amateur Radio Exchange	53
Ambit International	81
Amcomm Services	69
Antex	Cover III
Armon Products	76
BBC TV	83
Bamber Electronics	80
Barrie Electronics	85
Bearman, Phillip	82
Bib Hi-Fi	4
Bi-Pak Limited	18, 19
Birkett, J.	16
Bowes, C.	78
Bredhurst	54
British National Radio & Electronics School	77
Brooks, B	70
Burneze	84
Calscope	78
Cambridge Kits	84
Caranna, C.	83
Catronics	2
Chordgate	6
Chromasonic Electronics	8
Codespeed	87
Colomor	14
Continental Specialities	15
Cox Radio (Sussex) Ltd.	82
C. R. Supply Co.	82
Electronic Design Associates	2
Electrovalve	76
Electronic Mail Order	83
Electro-Tech.	17
Fane Acoustics	8
Golledge Electronics, P.R.	82
G.T. Information Service	83
G2 Dym Aerials	83
HAC Shortwave	70
Harrison Bros.	84
Havant Instruments	80
Heathcoat, J.	78
Heathkit	13
Home Radio	80
HTE Electronics	84
I.L.P. Electronics	10, 11
Intel	16
Intertext I.C.S.	82, 85
London Electronics College	82
Lowe Electronics	54
Magnum Audio	6
Manor Supplies	85
Maplin Electronic Supplies	9, Cover IV
Marshall A. (London) Ltd.	29
Mears, J. H.	6
Metac	Cover II
Mhel Electronics	84
Midland Trading	79
Osmabert	87
Partridge Electronics	12
Progressive Radio	78
Quartslab	29
Radio Components Specialists	13
Radio Shack	57
Roden Products	84
R.S.C. (Realistic Sound Centres Ltd.)	3
R. & T.V. Components	5
Safgan	2
Science of Cambridge	74, 75
Scientific Wire Company	84
Solid State Security	84
Sonic Discount	87
Sonic Sound Audio	70
South Midlands Communications Ltd.	64
Stephen-James Ltd.	70
Surefire	63
Swanley Electronics	14
Tandy Corporation Ltd.	7
Technomatic Ltd.	88
Teleradio	16
Tempus	16
Thonet Electronics	69
T.T. Electronics	4
TUAC	14
Van Karen Publishing	82
V. & F. Smallcraft	6
Vintage Wireless Company	82
Waters & Stanton Electronics	63
Watford Electronics	86
Western Electronics	69
Williamson Amplification	84
Wilmslow Audio	76

Codespeed Electronics

P.O. BOX 23, 34 SEAFIELD ROAD, COPNOR, PORTSMOUTH, HANTS., PO3 5BJ

8 DIGIT 0.1" LED DISPLAY multiplexed, common cathode. 99p each. **DIGITAL ALARM CLOCK MODULE** with 0.7" display. With data £5.99 each. **4 DIGIT CLOCK L.C.D.** 0.5" digits, supplied with data, £4.99 each. **MM5316** digital alarm clock chip, with data £2.29 each. **REJECT CALCULATORS** Untested, but good value for spares. £2.50 each. **LED WRISTWATCH I.C.** Mostek MK5030, with data 95p each. **LED WRISTWATCH DISPLAY** type DIS501, 0.1" digits. With data 95p each. **SUPER SAVER** Purchase an MK5030 and a DIS501 for only £1.50 the pair. **NOTE** The MK5030 and DIS501 are housed in a 'legless flatpack' style package and require some fairly fine soldering. **20 KEY KEYBOARDS** calculator keyboards, 2 for 99p (not for use with NORTEC4204 calc. chip). **4 DIGIT 0.8" LED DISPLAY** common cathode, with data £3.75 each. **DIGITAL MULTIMETER CHIP** MM5330 I.C. to build a 4½ digit multimeter. With data £3.49 each. **SUPER QUALITY JACK SOCKETS** ¼" (6.35mm) jack sockets, mono 23p each, stereo 25p each. **SLIDE POT KNOBS** please state colour required, 11p each. **ROTARY VOLUME CONTROL KNOBS** nice style, 18mm diam. Black with coloured cap. Please state colour required, 18p each. **10 LED DISPLAYS** Untested material. 0.1" digits, common cathode, 95p. **6 DIGIT 0.1" LED DISPLAY** multiplexed, common cathode, 99p. **555 TIMER I.C.** with data and applications booklet, 23p. **POLARIZING FILM** max. 19" wide any length. Only 2p per sq. inch. Any size cut. **SLIDER SWITCHES** 2 pole, change over, 15p each. **PUSH BUTTON SWITCHES** spring loaded (momentary) with one n.o. contact 14p each. **CALCULATOR CHIP** Nortec 4204, 4 function and constant. With data 80p. **2102 MEMORIES** Dynamic memories for your micro's. With data 95p each. **WRISTWATCH I.C.D.** supplied with polarizers and data sheet, 99p each.

NEW CATALOGUE (No. 7) NOW AVAILABLE, SEND SAE FOR YOUR FREE COPY.

POST & PACKING PLEASE ADD 35p (OVERSEAS ORDERS ADD 90p)

V.A.T. ADD 15% TO THE TOTAL OF GOODS AND P & P.

Full SATISFACTION GUARANTEE on all items.

OSMABET LTD

We make transformers amongst other things.

LOW VOLTAGE TRANSFORMERS: Prim 240V a.c.
6.3V 1.5A £3.00; 3A £4.15; 6A CT £7.90; 12V 1.5A £3.75; 3A CT £7.90; 6A CT £9.75; 15V 0.5A £3.00; 18V 1.5A CT £7.90; 24V 1.5A CT £7.90; 3A CT £9.75; 5A CT £18.00; 8A CT £29.25; 12A CT £37.50; 40V 3A CT £13.50

TWIN SEC TRANSFORMERS: Prim 240V a.c.
6V 0.6A - 6V 0.6A; 9V 0.4A - 9V 0.4A; 12V 0.3A - 12V 0.3A; 20V 0.15A - 20V 0.15A; all at £4.15 each; 15V 0.75A - 15V 0.75A £6.40; 15V 1.5A - 15V 1.5A £8.25; 18V 1A - 18V 1A £7.90; 18V 1.5A - 18V 1.5A £9.75; 20V 1.5A - 20V 1.5A £9.75; 12V 4A - 12V 4A £12.00; 25V 2A - 25V 2A £12.00

MIDGET RECTIFIER TRANSFORMERS: Prim 240V a.c.
6.0-6V 1.5A or 9.0-9V 1A £3.40 each; 12.0-12V 1A or 20.0-20V 0.75A £4.15 each; 9.0-9V 0.3A or 12V-0.12V 0.25A or 20V-0.20V 0.15A £3.00 each.

LT TRANSFORMERS TAPPED SEC: Prim 240V a.c.
0-10-12-14-16-18V 2A £7.50; 4A £9.40; 0-12-15-20-24-30V 2A £8.25; 4A £12.00; 0-20-30-60V 1A £9.00; 2A £12.00; 0-40-50-60-80-100-110V 1A £12.00.

AUTO & ISOLATION TRANSFORMERS 240/110V a.c.
30 to 4000 watts, many types ex stock. Lists.

MAINS TRANSFORMERS, SPECIAL OFFER: Prim 240V a.c.
250-0-250V 60 Ma, 6.3V 1A £2.50; 250V 100Ma, 6.3V 2A £3.50; 9V 3A £2.50; 25V 300 Ma 90p.

LOUDSPEAKERS
1½", 14", 2½", 2½", 2½" 8u £1.25 each; 3" 35u, 3½" 3, 8, 16, 80u; 5.4" 3.8, 16; or 25u £1.50 each; 7.4" 3 or 80u £1.75; 8.5" 25u £2.50.

"INSTANT" BULK CASSETTE/TAPE ERASER
Instant erasure of cassettes, and any diameter of tape spools, demagnetises tape heads, 200/240V a.c. leaflet £7.50.

EDGWISE LEVEL METER FSD 200/µA
Size: 19" x 18" 20mm 800p, £1.50.

CHARGING METERS 1½in diameter
2A or 3A £1.25 each; 5A or 10A £1.50 each.

SINGLE STRANDED WIRE PVC COVERED
32/0.2mm (10A) black or blue, £6.50 100m, 0.5mm £2.50 100m special prices per 1000m and over.

O/P TRANSFORMERS FOR VALVE AMPLIFIERS
P.P. spec tapped 3-8-150V A-A 6K, 30W £17.50; A-A 3K 50W £26.00; 100W (EL31, KT88 etc) £35.00.

G.E.C. MANUAL OF POWER AMPLIFIERS
Covers valve amplifiers 30W to 400W £1.25.

MULTIWAY SCREENED CABLE, PVC COVERED
36 way £1.00; 25 way 75p; 14 way 50p; 6 way 25p; 4 way 20p; 2 way 10p; 1 way 8p; 4 way indiv screened 30p.

CONDENSERS
Electrolytic 400 = 400V 75p; 2000/30V 30p; 2200/40V 40p; 8 = 8mfd 450V 40p; Paper tubular, W/E, 4/160V; 6/160V 30p each, 2mfd 150V 25p, 0.1mfd 300V a.c. 25p.

CARRIAGE EXTRA ON ALL ORDERS

ALL PRICES INCLUDE V.A.T.

Callers by appointment only. S.A.E. Enquiries, Lists.

46, Kenilworth Road, Edgware, Middx.

HA8 8YG. Tel: 01-958 9314

Sonic

HI-FI DISCOUNT CENTRES



DISCOUNT SPEAKERS

Imp 8 or 15 as app. Guarantees:

TITAN 5 years
FANE LIFETIME
OTHERS 1 year
ALL PRICES INC. VAT

Prices correct at 25.1.80

GENERAL PURPOSE

5" FANE 501	£4.95
8" AF MODEL 80	£5.95
8" AF MODEL 83	£6.95
8" FANE 80BT DUAL CONE	£3.95
10" ELAC 10RM 10 WATTS 3 OHMS ONLY	£2.50

HI-FI KITS

AF FRI 8" + TWEETER	£14.95 pt
FANE MODE ONE 8" + TWEETER	£19.99 pt
WHARFEDALE DENTON KIT	£30.95 pt
WHARFEDALE SHELTON KIT	£38.95 pt
WHARFEDALE LINTON KIT	£52.95 pt
WHARFEDALE GLENDALE KIT	£65.95 pt

GROUP/DISCO TYPES

12" TITAN T12/50R	£16.95
12" TITAN T12/100A	£26.95
12" CELESTION G12H 30W	£14.95
12" CELESTION G12/50 50W	£12.95
12" GOODMANS PD	£22.95
12" GOODMANS PG	£21.95
12" FANE SPECIALIST PA85	£23.95
12" FANE SPECIALIST DISCO 80/2	£24.95
12" FANE SPECIALIST DISCO 100/2	£25.95
12" FANE SPECIALIST GUITAR 80L	£23.95
12" FANE SPECIALIST GUITAR 80B/2	£24.95
12" FANE CRESCENDO 80	£36.95
12" FANE CRESCENDO 80LT	£39.95
12" FANE CRESCENDO 12E	£51.95
15" TITAN T15/70 70W	£24.95
15" TITAN T15/85	£28.95
15" TITAN T15/100 100W	£35.95
15" FANE SPECIALIST BASS 100	£34.95
15" FANE CRES. COLOSSUS 15E 200W	£89.95
18" GOODMANS 18P	£46.95
18" TITAN T18/100 100W	£46.95
18" CELESTION G 18/200 std.	£48.95
18" FANE CRESCENDO 18E	£85.95
18" FANE CRES. COLOSSUS 18E 200W	£96.95

HORN UNITS

CELESTION MH1000 25W	£14.95
FANE J44	£5.95
FANE J73	£8.95
FANE J104	£13.95

CROSSOVERS (FOR ABOVE)

FANE HPX1R OR HPX2R	£2.95
---------------------	-------

Mail Orders/Export enquiries to address below. Add £1 carr. on Hi-Fi spkrs, or kits. Otherwise add £1.25 (12" Spkr) £1.50 (15") £2.50 (18") (U.K. Only).

SPECIAL OFFER! COLLARO RECORD DECKS

- * 'S' Shaped Arm * Auto or Manual
- * 11" Turntable * Ideal for Disco

£15.95 ea. or 2 for £30.

Carr. £1.00 ea.

AMPS, TTABLES, JINGLE MACHINES, DISCO CONSOLES, LIGHTING, CABINETS, CREDIT TERMS AVAILABLE orders £20 over

MAIL ORDER ONLY



GREENTHORPE MILLS
GREENTHORPE
LEEDS LS13 4LQ

TTLs BY TEXAS			LINEAR I.C.s			TRANSISTORS			DIODES						
7400	11p	7497	180p	74221	160p	74C157	250p	MC1496	100p	TIP41C	78p	2N3866	90p	DIODES	
7401	12p	74100	130p	74251	140p	74C160	155p	MC3340	120p	TIP42A	70p	2N3903/4	18p	BY127	12p
7402	12p	74104	65p	74259	250p	74C161	155p	MC3350	120p	TIP42C	82p	2N3905/6	20p	OA47	9p
7403	14p	74105	65p	74278	290p	74C162	155p	MN5058	750p	TIP2955	78p	2N4058/9	12p	OA81	15p
7404	14p	74107	34p	74279	140p	74C163	155p	NE531	100p	TIP3055	70p	2N4060	12p	OA85	15p
7405	18p	74109	55p	74283	140p	74C173	120p	NE543K	225p	TIS43	34p	2N4061/2	18p	OA90	9p
7406	32p	74110	55p	74284	400p	74C174	160p	NE555	25p	TIS93	30p	2N4061/2	18p	OA91	9p
7407	32p	74111	70p	74285	400p	74C175	210p	NE556	70p	BU108	250p	2N4123/2	22p	OA95	9p
7408	19p	74116	200p	74290	150p	74C192	150p	NE561B	425p	BU205	250p	2N4125/2	22p	OA200	9p
7409	19p	74118	130p	74294	150p	74C193	150p	NE562B	425p	BU208	240p	2N4289	20p	OA202	10p
7410	15p	74119	210p	74298	200p	74C194	220p	NE565	130p	BU406	145p	2N4401/3	27p	OA205	6p
7411	24p	74120	110p	74365	150p	74C195	110p	NE566	155p	BC117/2	12p	2N4427	90p	OA206	10p
7412	20p	74121	28p	74366	150p	74C221	175p	NE567	175p	BC117/3	12p	2N4871	60p	OA207	10p
7413	30p	74122	48p	74367	150p	4000 SERIES		RC4151	400p	MJ2501	225p	2N4872	60p	OA208	10p
7414	60p	74123	48p	74368	150p	4000 15p		SN76003N	175p	MJ2955	100p	2N5179	27p	OA209	10p
7416	27p	74125	55p	74369	150p	4001 17p		SN76013N	140p	MJE3055	70p	2N5191	65p	OA210	10p
7417	27p	74126	60p	74370	200p	4002 17p		SN76032ND	120p	MJE3057	70p	2N5194	90p	OA211	10p
7420	17p	74128	75p	74371	200p	4006 95p		SN76033ND	120p	MPF102	45p	2N5245	40p	OA212	10p
7421	40p	74132	75p	74372	200p	4007 18p		SN76033ND	120p	MPF103/4	40p	2N5246	40p	OA213	10p
7422	22p	74136	75p	74373	200p	4008 80p		SN76033ND	120p	MPF105/6	40p	2N5296	55p	OA214	10p
7423	34p	74141	70p	74374	200p	4009 40p		SN76033N	175p	MPSA06	30p	2N5401	50p	OA215	10p
7425	30p	74142	200p	74375	200p	4010 50p		SP8515	750p	2N1131/2	20p	2N5405	40p	OA216	10p
7426	40p	74145	90p	74376	200p	4011 17p		TBA6141B1		2N1613	25p	2N5457/8	40p	OA217	10p
7427	34p	74147	150p	74377	200p	4012 18p		TBA800	225p	2N1711	25p	2N5459	40p	OA218	10p
7428	38p	74148	150p	74378	200p	4013 17p		TBA810	160p	2N1712	25p	2N5460	40p	OA219	10p
7430	17p	74150	100p	74379	200p	4014 84p		TBA820	90p	2N1713	25p	2N5485	44p	OA220	10p
7432	30p	74151A	70p	74380	200p	4015 84p		TCA901	175p	2N2119A	30p	2N5485	44p	OA221	10p
7433	40p	74153	70p	74381	200p	4016 45p		TCA902	175p	2N2222A	20p	2N5485	44p	OA222	10p
7437	35p	74154	100p	74382	200p	4017 89p		TDA4500	280p	2N2222B	20p	2N5485	44p	OA223	10p
7438	35p	74155	90p	74383	200p	4018 89p		TDA1004	320p	2N2222C	20p	2N5485	44p	OA224	10p
7440	17p	74156	90p	74384	200p	4019 45p		TDA1008	300p	2N2222D	20p	2N5485	44p	OA225	10p
7441	70p	74157	70p	74385	200p	4020 110p		XR2205	400p	2N2222E	20p	2N5485	44p	OA226	10p
7442A	60p	74159	100p	74386	200p	4021 110p		XR2207	400p	2N2222F	20p	2N5485	44p	OA227	10p
7443	112p	74160	100p	74387	200p	4022 110p		XR2208	400p	2N2222G	20p	2N5485	44p	OA228	10p
7444	112p	74161	100p	74388	200p	4023 22p		XR2210	675p	2N2222H	20p	2N5485	44p	OA229	10p
7445	100p	74162	100p	74389	200p	4024 50p		XR2212	675p	2N2222J	20p	2N5485	44p	OA230	10p
7446A	93p	74163	100p	74390	200p	4025 20p		XR2215	675p	2N2222K	20p	2N5485	44p	OA231	10p
7447A	70p	74164	100p	74391	200p	4026 130p		XR2216	675p	2N2222L	20p	2N5485	44p	OA232	10p
7448	80p	74165	130p	74392	200p	4027 50p		XR2217	675p	2N2222M	20p	2N5485	44p	OA233	10p
7450	17p	74166	100p	74393	200p	4028 84p		XR2218	675p	2N2222N	20p	2N5485	44p	OA234	10p
7451	17p	74167	200p	74394	200p	4029 100p		XR2219	675p	2N2222P	20p	2N5485	44p	OA235	10p
7453	17p	74170	240p	74395	200p	4030 55p		XR2220	675p	2N2222Q	20p	2N5485	44p	OA236	10p
7454	17p	74172	220p	74396	200p	4031 180p		XR2221	675p	2N2222R	20p	2N5485	44p	OA237	10p
7455	17p	74173	220p	74397	200p	4032 130p		XR2222	675p	2N2222S	20p	2N5485	44p	OA238	10p
7470	36p	74174	93p	74398	200p	4033 130p		XR2223	675p	2N2222T	20p	2N5485	44p	OA239	10p
7472	30p	74175	85p	74399	200p	4034 200p		XR2224	675p	2N2222U	20p	2N5485	44p	OA240	10p
7473	34p	74176	90p	74400	200p	4035 110p		XR2225	675p	2N2222V	20p	2N5485	44p	OA241	10p
7474	30p	74177	90p	74401	200p	4036 100p		XR2226	675p	2N2222W	20p	2N5485	44p	OA242	10p
7475	30p	74178	160p	74402	200p	4037 100p		XR2227	675p	2N2222X	20p	2N5485	44p	OA243	10p
7476	35p	74180	90p	74403	200p	4038 80p		XR2228	675p	2N2222Y	20p	2N5485	44p	OA244	10p
7480	50p	74181	200p	74404	200p	4039 90p		XR2229	675p	2N2222Z	20p	2N5485	44p	OA245	10p
7481	100p	74182	90p	74405	200p	4040 110p		XR2230	675p	2N2222AA	20p	2N5485	44p	OA246	10p
7482	84p	74184A	150p	74406	200p	4041 100p		XR2231	675p	2N2222AB	20p	2N5485	44p	OA247	10p
7483A	90p	74185	150p	74407	200p	4042 110p		XR2232	675p	2N2222AC	20p	2N5485	44p	OA248	10p
7484	100p	74186	200p	74408	200p	4043 55p		XR2233	675p	2N2222AD	20p	2N5485	44p	OA249	10p
7485	110p	74190	100p	74409	200p	4044 80p		XR2234	675p	2N2222AE	20p	2N5485	44p	OA250	10p
7486	34p	74191	100p	74410	200p	4045 80p		XR2235	675p	2N2222AF	20p	2N5485	44p	OA251	10p
7489	175p	74192	100p	74411	200p	4046 100p		XR2236	675p	2N2222AG	20p	2N5485	44p	OA252	10p
7490A	30p	74193	100p	74412	200p	4047 110p		XR2237	675p	2N2222AH	20p	2N5485	44p	OA253	10p
7491	80p	74194	100p	74413	200p	4048 55p		XR2238	675p	2N2222AJ	20p	2N5485	44p	OA254	10p
7492A	46p	74195	95p	74414	200p	4049 49p		XR2239	675p	2N2222AK	20p	2N5485	44p	OA255	10p
7493A	30p	74196	95p	74415	200p	4050 80p		XR2240	675p	2N2222AL	20p	2N5485	44p	OA256	10p
7494	84p	74197	80p	74416	200p	4051 80p		XR2241	675p	2N2222AM	20p	2N5485	44p	OA257	10p
7495A	70p	74198	150p	74417	200p	4052 80p		XR2242	675p	2N2222AN	20p	2N5485	44p	OA258	10p
7496	65p	74199	150p	74418	200p	4053 125p		XR2243	675p	2N2222AO	20p	2N5485	44p	OA259	10p
				74419	200p	4054 135p		XR2244	675p	2N2222AP	20p	2N5485	44p	OA260	10p
				74420	200p	4055 125p		XR2245	675p	2N2222AQ	20p	2N5485	44p	OA261	10p
				74421	200p	4056 135p		XR2246	675p	2N2222AR	20p	2N5485	44p	OA262	10p
				74422	200p	4057 120p		XR2247	675p	2N2222AS	20p	2N5485	44p	OA263	10p
				74423	200p	4058 115p		XR2248	675p	2N2222AT	20p	2N5485	44p	OA264	10p
				74424	200p	4059 120p		XR2249	675p	2N2222AU	20p	2N5485	44p	OA265	10p
				74425	200p	4060 120p		XR2250	675p	2N2222AV	20p	2N5485	44p	OA266	10p
				74426	200p	4061 120p		XR2251	675p	2N2222AW	20p	2N5485	44p	OA267	10p
				74427	200p	4062 120p		XR2252	675p	2N2222AX	20p	2N5485	44p	OA268	10p
				74428	200p	4063 120p		XR2253	675p	2N2222AY	20p	2N5485	44p	OA269	10p
				74429	200p	4064 120p		XR2254	675p	2N2222AZ	20p	2N5485	44p	OA270	10p
				74430	200p	4065 120p		XR2255	675p	2N2222BA	20p	2N5485	44p	OA271	10p
				74431	200p	4066 120p		XR2256	675p	2N2222BB	20p	2N5485	44p</		



Micro-precision soldering

ANTEX TCSU1 with CTC

... its the perfect kit

Model TCSU1

Micro-Soldering Station

Accurate pin point temperature control between 65° and 400°C. Heating element and sensor built in tip of the iron for fast response. Interchangeable slide-on bits from 4.7 mm (3/16") down to 0.5mm. Zero voltage switching, no spikes. No magnetic field, no leakage. Supplied with miniature CTC (35-40watt) iron or XTC (50watt). TCSU1 soldering station with XTC or CTC iron £36 (6.44). Nett to industry.



Model CTC - 24 volts Priced at **£9.75** (1.87)



Model XTC - 24 volts Priced at **£9.75** (1.87)

Model CX 17watts - 230 volts



A miniature iron with the element enclosed first in a ceramic shaft, then in stainless steel. Virtually leak-free. Only 7 1/2" long. Fitted with a 3/32" bit. **£4.20** (98). Range of 5 other bits available from 1/4" down to 3/64". Also available for 24volts.



Spare element Model CX230E

Model X25 25 watts - 230 volts



A general purpose iron also with a ceramic and steel shaft to give you toughness combined with near-perfect insulation. Fitted with 1/8" bit and priced at **£4.20** (98). Range of 4 other bits available. Also available in 24volts.



Spare element Model X25 240E

Model SK3 Kit

Model SK4 Kit



Contains both the model CX230 soldering iron and the stand ST3. Priced at **£5.70** (1.49). It makes an excellent present for the radio amateur or hobbyist.



With the model X25/240 general purpose iron and the ST3 stand, this kit is a must for every toolkit in the home. Priced at **£5.70** (1.49).

Model SK1

Model MLX 12volts

ST3 Stand.



This kit contains a 15watt miniature soldering iron, complete with 2 spare bits, a coil of solder, a heat sink and a booklet. How to Solder. Priced at **£5.95** (1.53).



The soldering iron in this kit can be operated from any ordinary car battery. It is fitted with 15 feet flexible cable and battery clips. Packed in a strong plastic envelope it can be left in a car, a boat or a caravan ready for soldering in the field. Price **£4.55** (1.14).



A strong chromium plated steel spring screwed into a plastic base of high grade insulating material provides a safe and handy receptacle for all ANTEX models soldering irons. Priced at **£1.50** (57).

* VAT + P&P as shown in brackets ()



Stocked by many wholesalers and retailers or direct from us if you are desperate.

Please send me the Antex colour brochure I enclose cheque/P.O./Giro No 258 1000

Please send the following

Name

Address

Antex Ltd., Freepost, Plymouth PL1 1BR Tel. 0752 67377



STEP INTO A NEW WORLD WHEN YOU DISCOVER **MAPLIN**

For beginners or professionals, the Maplin catalogue will help you find just about everything you need for your project.

Over 5,000 of the most useful components — from resistors to microprocessors — clearly described and illustrated.

Send the coupon for your copy
and **STEP UP TO
MAPLIN SERVICE
NOW**



Post this coupon now for your copy of our 1979-80 catalogue price 70p.

Please send me a copy of your 280 page catalogue. I enclose 70p (plus 46p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the U.K. send £1.35 or ten International Reply Coupons. I enclose £1.16.

NAME _____

ADDRESS _____



PW480

MAPLIN

ELECTRONIC SUPPLIES LTD

All mail to:-

P.O. Box 3, Rayleigh, Essex SS6 8LR.

Telephone: Southend (0702) 554155.

Shop: 284 London Road, Westcliff-on-Sea, Essex. (Closed on Monday).


Telephone: Southend (0702) 554000.

PULL-OUT 8-PAGE SUPPLEMENT

RADIO SERVICING & ALIGNMENT PROCEDURES

PRACTICAL
WIRELESS

APRIL 1980

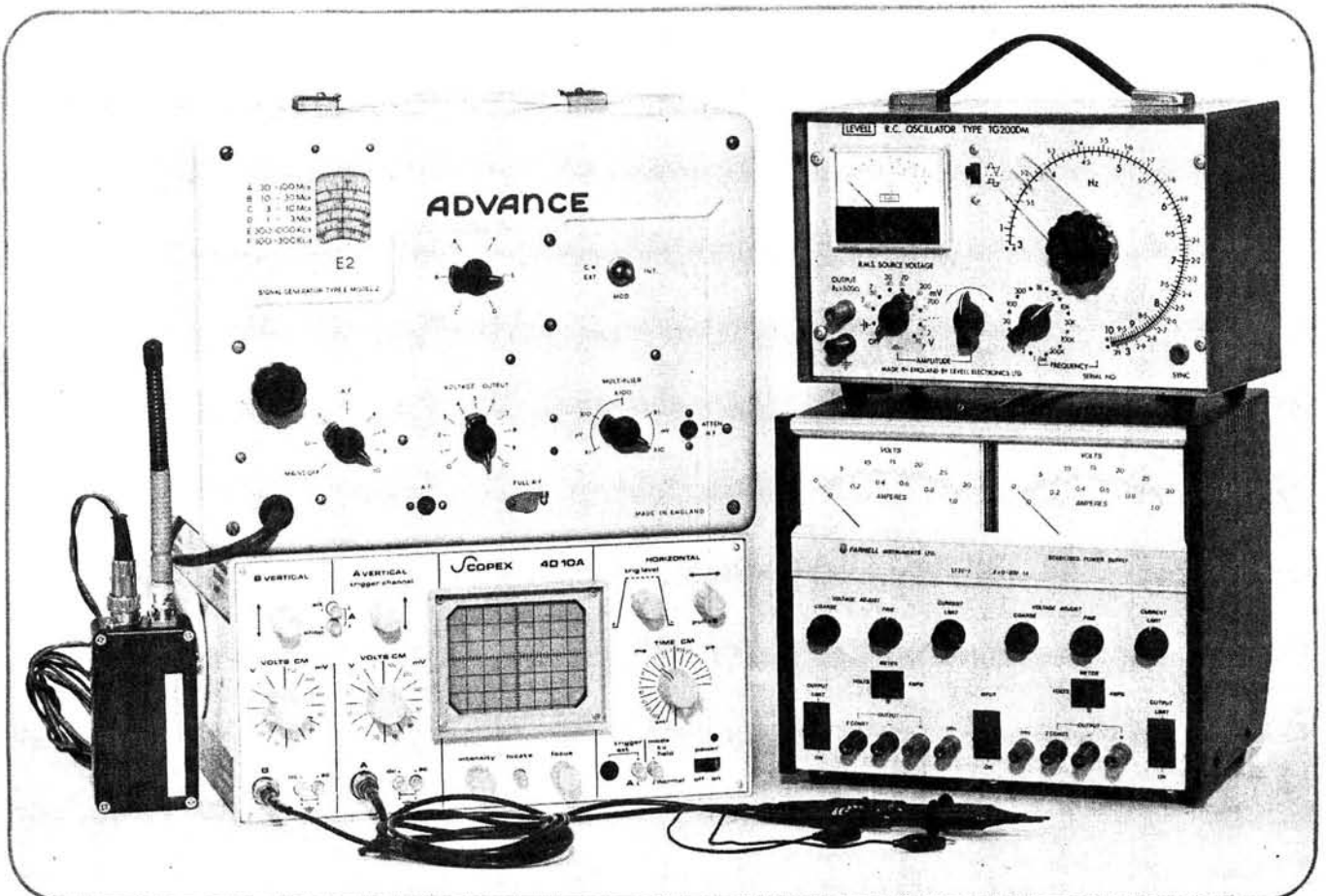

CONTENTS

TWO

Introduction
Equipment

THREE

Knowledge
Fault Finding Procedures
Method

FOUR

The Multirange Meter
The Simple Amplifier
Faulty Resistors

FIVE

Faulty Capacitors
Transistor Faults
Receiver Alignment

SIX

Alignment of I.F. Stages
The Local Oscillator
Padding and Trimming

SEVEN

Local Oscillator Alignment
Mixer Alignment
Alignment of R.F. Stage
Beat Frequency Oscillator


EIGHT

Final Points
Double and Triple Superhets
Conclusions

The first thing to realise when faced with a defective piece of equipment is that there is no magic formula for putting it right. What is required is a little knowledge, a logical approach, the correct tools for the job in hand, a reliable test meter and infinite patience. One needs to regard oneself as a detective, finding and acting on the clues presented, sorting out the red herrings and eventually arriving at the point where the fault is apparent.

This is half the job completed; the next step being to correct the fault, possibly by replacement of one or more components; fitting and soldering to be done to the highest standard possible and finally testing the completed job to make sure there are no further faults and that the equipment operates in a satisfactory manner.

Speed and efficiency in fault finding will not be achieved overnight; it takes a number of years for the professional to reach the standards required in the trade, but this should not deter the "amateur" from attempting to put things right himself, particularly where time is of no great consequence. For the author, fault finding presents a different challenge for each successive fault found and hence can never be boring. The feeling of elation and satisfaction when a totally defunct receiver bursts into life is hard to describe

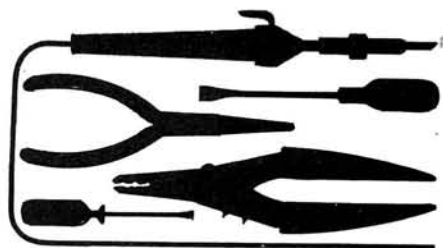

and has never diminished over the passing years.

Equipment

At least 80% of general faults can be found with the equipment shown in Fig. 1. The meter is an Avo 8, but any multi-range meter will suffice provided it has suitable voltage, current and ohms ranges and a resistance of no less than $20\,000\Omega/V$. The hand tools shown have done sterling service for the author for many years and I can only reiterate the point that money spent on quality tools is never a waste.

In Fig. 2 is shown a set of test equipment generally used by the more advanced fault finders to enable the remaining 20% of difficult faults to be cured. This equipment is also necessary for accurate alignment of receivers, but whilst desirable it is not essential for general broadcast receivers of the ordinary tran-

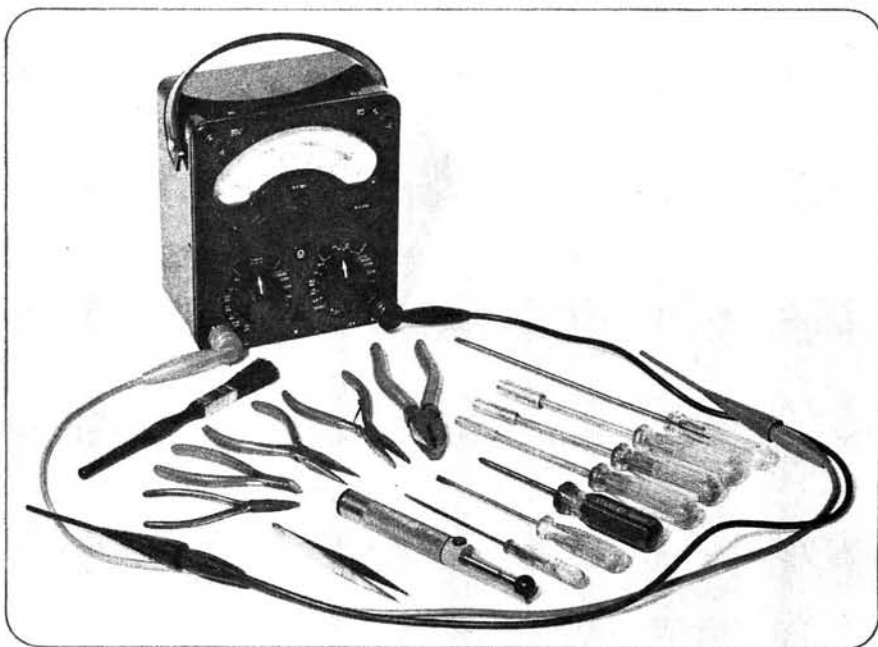


Fig. 1: The basic tools of the trade

sistor portable variety. With practice, a reasonably good job can be done on these without the use of this test gear.

Knowledge

The basic requirement is a fundamental understanding of the properties of electronic components and the ways in which they can be exploited to fulfill our requirements in a circuit. From this statement it can be seen that in any circuit diagram the function of any particular component can be deduced with reasonable accuracy and hence what the effect on the circuit would be if the component should suddenly go faulty.

Most basic faults will revolve around two major fault conditions, open circuits or short circuits and partial stages between these two limits. Resistors can go open-circuit or high or low value compared to their designated markings, whereas a capacitor can go either open-circuit or short-circuit; and inductors can go open-circuit or partial short-circuit depending on the type of inductor or transformer.

Any electronic circuit will possess capacitance, inductance and resistance, these being the three basic building blocks in electronics, apart from valves and transistors. Anything which causes a dramatic change in any of these three design conditions will constitute a fault and the circuit will therefore operate incorrectly. This is the area with which this article is concerned.

Fault Finding Procedures

There are two basic methods of fault finding which may be employed, one being to start at the output and work back to the input, the other preferred way being the half-split method. This involves applying a signal at approximately half way through the circuit and depending on whether there is an output or not,

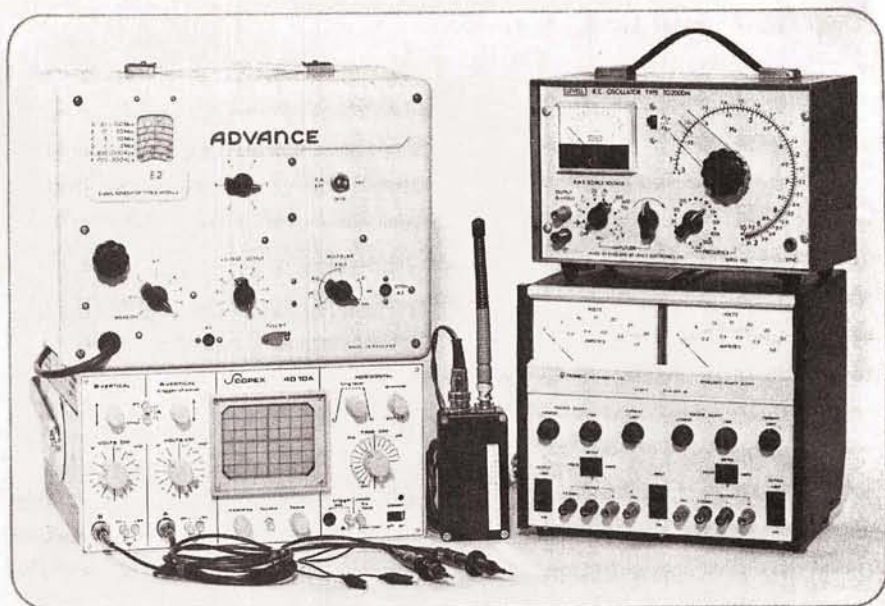
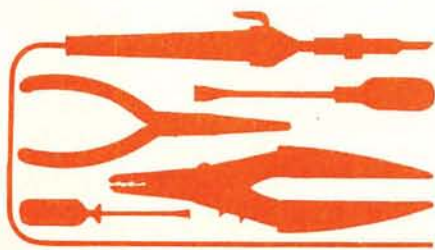


Fig. 2: Common test equipment used for more advanced fault finding

deciding in which direction from the point of injection the fault will be.

Having found in which direction the fault lies, the half-split method can now be repeated and the faulty stage will eventually be isolated. In Fig. 3 is shown the block diagram of a basic superhet receiver and if a fault occurs in any one of these blocks this will give rise to a certain set of symptoms. In block diagrams of this type, a power unit is assumed and is not shown diagrammatically.

The first thing that must be realised about fault finding is that components under large electrical stress are more likely to go faulty than components under little or no stress. With reference to Fig. 3 it will be obvious that the largest signals and hence voltage and currents will be present in the audio amplifier and output stage, it therefore follows that most of the electrical stress is concentrated in this area. Assuming Fig. 3 to be representative of a practical receiver, whether valve or solid-state is unimportant, and when switched on does not produce any sounds whatsoever, then the first checks should be concerned with the controls, e.g., volume control turned up, speaker connected, aerial connected, etc. If all is satisfactory then the next logical step is to check mains connections and or battery connections and indeed battery voltage on load; again, if all appears


correct, then it is safe to assume that the fault will be in one of the blocks shown in Fig. 3.

With practice, this seemingly long winded procedure can be accomplished up to this point in a matter of a few minutes, but could save a considerable amount of wasted time looking for a fault that was not really there in the first place. It will now be necessary to have to hand the circuit diagram of the equipment before proceeding further.

Method

The next step is to listen carefully with the ear near to the speaker to ascertain if there is any noise of any sort present, albeit of a low level. If nothing is heard at all, then it is safe to assume that the fault must lie in either the power supply to the audio amp. and output stage, or indeed the actual stage itself. Voltage checks with a meter comparing them to voltages marked on the circuit diagram should next be carried out and this should reveal the fault.

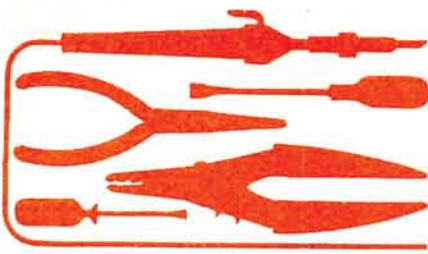Alternatively, if something can be heard in the speaker such as a slight hum or hiss, then we should immediately go for the half-split method and inject a signal at i.f. frequency, either from a signal generator or a squarewave signal injector, to a point A in Fig. 3. Again,



there will be two results, either an output from the speaker, or nothing.

If there is an output then the fault must be somewhere to the left of point A, if no output, then the fault must be to the right of point A. Assuming in this case no output was obtained, then the same frequency signal would now be injected at point B, the input to the detector, resulting again in either an audible signal or nothing. If still nothing is heard then the fault is most likely to be in the audio amp. stage; if an output was obtained, then the fault must be in the i.f. amp. stage.

Assuming now that we had an output when injecting a signal at point A; this means that the fault must be to the left of point A and we would inject a signal again at i.f. frequency to point D to check the operation of the mixer stage. If no signal resulted, then the mixer stage would be suspect, but if a signal was obtained then the fault may be in the local oscillator stage or the r.f. amplifier stage.

Quick d.c. voltage checks round the local oscillator stage should prove adequate to ascertain operation and the output can be checked with a frequency counter if available. If all is normal here, then the fault must be to the left of point

D and a signal from a generator tuned to the same frequency as the receiver should be injected at the aerial socket. Voltage checks on the r.f. amplifier stage should now reveal the fault. It must be pointed out that a large number of receivers do not have a separate r.f. amplifier stage and the aerial input would therefore go direct to point D via the input tuning assembly, obviating the need for the last step in the checks above.

All the steps now referred to represent the general plan of action in dealing with a fault in a receiver and to isolate the faulty section in a quick and efficient manner. It should be realised that this method is also applicable to all types of electronic circuits when broken down to their basic building blocks and we will now look at a simple circuit in detail to consider the effects caused and the results of failure of its various constituent components. This is the point at which some knowledge of the electrical properties of components used in a circuit is essential.

The Multirange Meter

Before any interpretation of meter readings can be made, it must be understood that any multirange moving coil meter of the AVO type will draw current when making a reading. In other words, across the meter leads will be present a certain resistance which will depend on the range selected. With a meter of $20\,000\Omega/V$ sensitivity switched to the 10V d.c. range, the resistance between the meter leads will be $20\,000 \times 10 = 200\,000\Omega$.

It follows that when making voltage checks, the resistance of the meter must be taken into account when interpreting readings otherwise an incorrect set of clues may be the result. When taking voltage readings across high source impedance points use a range which gives the highest internal resistance, having regard to the probable voltage that is to be measured.

The Simple Amplifier

The circuit shown in Fig. 4 is a simple, single stage audio amplifier. When the circuit is operating normally with 12V applied to the points indicated, then with a signal input applied to the negative side of C1 an amplified output of that signal would be expected to appear at the negative side of C3. Resistors R1 and R2 form the base bias supply circuit, R3 is the collector load resistor and R4 is the emitter stabilising resistor. Capacitors C1 and C3 are d.c. blocking capacitors coupling the signals into and out of the amplifier respectively. Capacitor C2 holds the emitter potential of Tr1 constant against signal level variations at the base, which would otherwise cause the base/emitter bias to change. We will now proceed to investigate the effect of specific faults, one at a time, as applied to the circuit in Fig 4.

Faulty Resistors

If R1 becomes open-circuit there will be no base voltage applied to Tr1, hence no forward bias, no collector current and no emitter potential. The transistor will be switched off and the collector potential will be 12V.

With R2 open-circuit, the base potential will be high, causing Tr1 to conduct very hard. Emitter current will be very high, giving rise to low collector volts and high emitter volts. This fault will give distortion and the transistor may run warm to the touch.

If R3 becomes open-circuit, there will be no collector voltage, but the emitter/base junction will still be forward biased. Base current increases as there is no emitter/collector current flowing and the base voltage will be reduced. The emitter voltage follows the base voltage so that the difference between the two is the turn-on voltage. A point to remember is that when a meter is connected to the

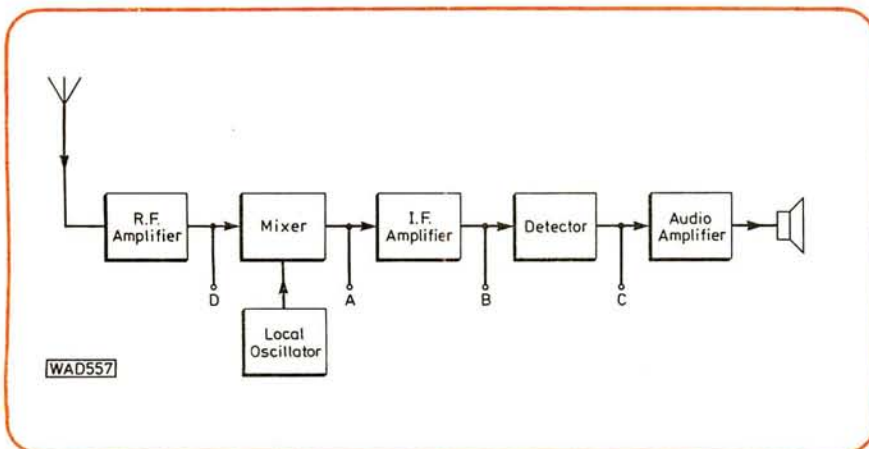


Fig. 3: Block diagram of basic superhet receiver

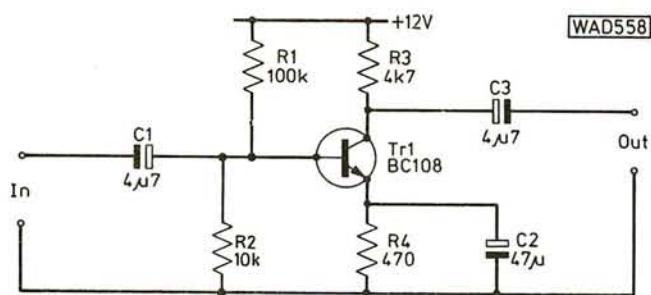


Fig. 4: Circuit diagram of simple audio amplifier

collector to read volts, it will not read 0V as expected since the collector/base junction will be forward biased via the meter and R1.

With R4 open-circuit, there will be no base/emitter current or collector/emitter current. The base voltage will be high and the collector voltage will be at supply potential. The transistor will be completely switched off, but when a meter is connected to read emitter voltage, then the emitter is connected to chassis via the resistance of the meter and a reading will be shown. Depending on the resistance of the meter, the circuit will be switched on and may partially function while the meter remains connected.

Faulty Capacitors

If C2 becomes short-circuit, then the emitter will be connected directly to chassis. The base current will increase and the collector current increases to a high value. Consequently, collector voltage will be very low and the transistor will be running warm to the touch giving bad distortion of any signals.

With C2 open-circuit, all d.c. voltages will be correct and transistor action will be as normal. What will be noticed is a marked lack of gain due to the ability of the emitter voltage to change in sympathy with the signal and hence altering the bias level. This capacitor has a large value giving a very low reactance at the operating frequency.

Capacitors C1 and C3 are d.c. blocking and are input and output coupling capaci-

tors, respectively. If either of these go open-circuit, then the d.c. conditions of the circuit will remain unaltered, but of course, there will be no signal coupling either in or out of the amplifier.

If either were to become short-circuit, then any effect on the amplifier would depend on the impedance of the coupling into, or out of, the amplifier. If d.c. voltages were present, e.g. coupling into the amplifier from the collector circuit of a previous stage, then this voltage would be passed on unhindered and consequently upset the working conditions of the circuit.

Transistor Faults

With the collector/base junction of Tr1 short-circuit, then current will flow via R2, the s/c junction and R3 to the supply. There will be a larger voltage drop across R3 and R4 and the collector voltage will be reduced. The result will be base and collector at the same potential.

If the base/emitter junction were to go short-circuit, then current will flow through R4 and R1 via the faulty junction. There will be increased base current with a consequent larger voltage drop across R1 and the base voltage will be of a very low value. There will be no collector current, therefore the collector voltage will be at the supply potential and the base and emitter voltages will, of course, be equal.


With the base/emitter junction open-circuit, there will be no base current flowing and less voltage drop across R1, giv-

ing rise to a higher base potential. Also, there can be no emitter/collector current flowing so the emitter will be at chassis potential and the collector at supply potential.

With the collector/base junction open-circuit, there can be no collector/emitter current. Base current will flow but will be larger than normal. As only the base current will flow through R4, then the emitter potential will be low and the collector will be at supply potential.

This concludes the fault finding section which the author hopes will have dissipated some of the fears and the old wives tales concerning the processes involved.

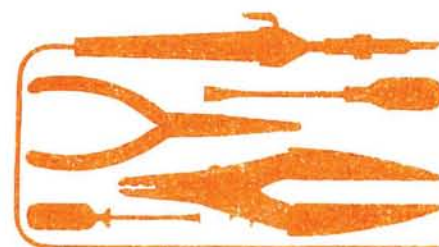It was not intended that this should be a complete fault finding manual, but rather a guide as to the best way to set about the job using ones own knowledge and abilities but hopefully guided in the right direction.



Receiver Alignment

No receiver however complicated or simple will perform satisfactorily without being correctly aligned; indeed, a badly mis-aligned superhet receiver can cause severe interference to other receivers over a large area and thus may bring down the wrath of the Home Office round ones head. To align any receiver is basically a simple process, but involves a large number of steps if the receiver is a complicated one. All these steps must be completed in the correct sequence as laid down in the service manual, otherwise it will never work correctly.

Generally speaking, the correct service manual for the receiver must be available because some adjustments may be very critical and if completed in the wrong sequence, will give rise to all manner of spurious effects. Most adjustments in modern receivers are by ferrite dust cores and it is IMPERATIVE that the correct type of

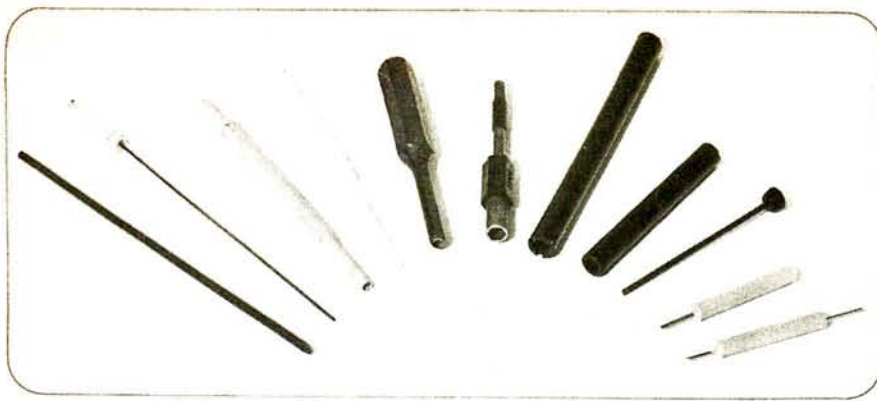


Fig. 5: A selection of trimming tools

trimming tool is used for adjustment of these. The use of an incorrect trimming tool or too much force will only result in a broken core, which will be very difficult to remove without extensive damage to the coil.

A wide selection of trimming tools is shown in Fig. 5 some of which can be purchased as a complete kit or built up from individual items bought separately. Poor quality plastic tools should be avoided, only good quality nylon types are worthy of the professional's tool box.

General

With any superhet receiver the first step in the alignment procedure is to align the i.f. strip. In ordinary receivers, most i.f. strips will be aligned to a frequency between 450 and 470kHz, commonly the latter, and in the majority of simple cases transistor receivers will have three tuned circuits and valve receivers four tuned circuits to adjust. They must be set EXACTLY to the frequencies stated in the manual, or the bandwidth and gain of the receiver will be seriously affected. Provided the alignment is not drastically out, then the signal would be injected at point D in Fig. 3. With the volume control turned full up and the aerial disconnected, the signal generator input level should be increased until an audible signal is heard in the loudspeaker.

Alignment of I.F. Stages

We start by aligning the last tuned circuit first and proceed until all tuned cir-

cuits are brought into line, repeating the process at least three times because there will be a pulling effect between mutually coupled tuned circuits when approaching resonance. It must also be borne in mind that the type of modulation from the generator must be the same as the detector in the receiver is designed to demodulate and as alignment proceeds, the signal generator output level should be continuously reduced as the circuits come into line to avoid undue damping caused by a.g.c. action.

From the block diagram in Fig. 3 it will be seen that the local oscillator is the major driving force behind the operation of the receiver and it is this which controls the actual frequency coverage. All other circuits, except the i.f. amplifier stages, are subordinate to this section and unless the l.o. is correct, then the receiver will track across the dial receiving frequencies other than that indicated. It is therefore essential that in all cases the local oscillator is the section which must be aligned next for each band covered by the receiver.

The Local Oscillator

In a standard type of receiver, this section will contain an oscillatory circuit the heart of which will be a tuned circuit of the type shown in Fig. 6. It should be appreciated that there are many different variations on this theme, but all are designed to fulfill the same purpose and that is to provide a signal which, when mixed with the incoming r.f., will produce a constant frequency signal from the mixer which is the resultant i.f.

In most broadcast and h.f. band receivers covering up to 30MHz, the local oscillator is normally the i.f. above the incoming r.f. in frequency. For example, if we tuned to 1MHz on the receiver dial, then the corresponding local oscillator frequency would be $1\text{MHz} + 470\text{kHz} = 1.470\text{MHz}$ for an i.f. of 470kHz. Throughout the receiver's tuning range the correct i.f. must always be maintained, so a two section ganged tuning capacitor must be used, one section to tune the incoming r.f. and the other section to tune the local oscillator. If the receiver has an r.f. amplifier stage, then a three gang tuning capacitor must be used.


At this point it should be appreciated that the tuning gang sections are normally manufactured with all sections identical, having maximum values commonly up to 500pF and will thus give rise to a major alignment problem.

Because the local oscillator must track at a higher frequency than the incoming r.f. and uses the same value of tuning capacitor, it follows that the tuning inductance must of necessity be smaller in value than the inductance of the coil used for tuning the incoming r.f. If this arrangement resulted in the correct i.f. with the tuning capacitors at minimum value, then at maximum value the local oscillator frequency would be wildly out, in no way would it remain correct with the tuning dial. We must, therefore, resort to the type of circuit shown in Fig. 6.

Padding And Trimming

Capacitor C1 and coil L1 are the normal tuned circuit, but with the addition of Cp and Ct. Capacitor Cp is called a padding capacitor and is effectively in series with C1, the main tuning capacitor; Ct is called a trimmer capacitor and is in parallel with C1.

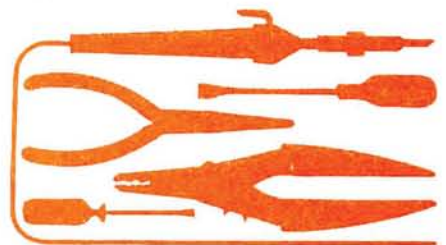The value of Cp will depend upon the frequency range covered and the value of Ct will be approximately equal to the



minimum capacitance of C1; sometimes being part of the tuning gang assembly. Each frequency range of the receiver will involve switching a different L1 and Cp into circuit as well as switching coils in the mixer input stage and the r.f. stage if used.

The effect of Cp on the operation of the circuit is as follows. Depending on its value, its reactance will change with frequency over a certain range. This reactance, in conjunction with the reactance of C1, being in series with it, causes the maximum capacity effect of C1 on the coil L1 to be reduced, but at the h.f. end of the band the reactance of Cp will have fallen to a value such as to have little effect on the capacity of C1. Hence Cp, or in most cases the core of L1, is adjusted at the l.f. end of the band where the tuning capacitor, C1, is exerting maximum influence on L1. Either Cp or the coil can be made adjustable as the net effect is the same, but it is far more convenient to adjust a coil and have the capacity fixed.

The trimmer, Ct, being of small value will have very little effect with C1 at maximum capacity; but when C1 is at minimum capacity it has the maximum effect, hence Ct is adjusted at the h.f. end of the band.

Local Oscillator Alignment

With the receiver tuned to the l.f. end of the band, inject a signal, tuned to the same frequency as shown on the receiver dial, via the aerial socket and adjust the coil core for maximum output.

Tune the receiver to the h.f. end of the band and inject a signal of the same frequency as that shown on the dial. Adjust the trimmer capacitor for maximum output. This process will need repeating a number of times until the tracking becomes correct. It is then useful to tune the receiver to the centre of the band and check again with the signal generator to see if tracking at the centre is correct. If it is not, then mechanical adjustment of the tuning mechanism is indicated and then repeat the full alignment process.

These two adjustments will then be made for each band the receiver covers, in turn, starting with the l.f. bands and finishing with the h.f. bands. This now completes the alignment of the local oscillator circuits.


Mixer Alignment

This section is concerned with the adjustment of the r.f. input coils to the mixer. There will be padding and trimming adjustments to be made for each band covered by the receiver; again, padding or coil core adjustments at the l.f. end first, followed by trimmer capacitor adjustments at the h.f. end of the band. In these circuits there will be no fixed padding capacitance such as Cp in Fig. 6.

It should be noted that these adjustments should be carried out at the same tuning points that the local oscillator was set up to, unless stated otherwise in the receiver manual. Unless the receiver is fitted with an r.f. stage preceding the mixer, then this completes the alignment of the receiver.

Alignment of R.F. Stage

The only coils which usually require alignment in this part of the receiver are again the input coils to the stage, the output generally being broadbanded using either an r.f. choke as a load or just simple CR coupling to the mixer input. The tuning points selected for alignment should be those used for the oscillator and mixer input circuits previously described. Again, the coil core padding adjustment should be completed first followed by the trimmer adjustment and again note that there will be no fixed padding capacitance used. There will be one coil for each band in use and should

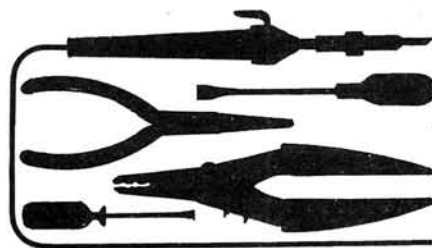

be aligned in the usual order, namely, l.f. bands first finishing with the highest h.f. band.

It will be noticed that during alignment of this stage, the signal generator output will have had to be progressively reduced, possibly to its lowest output level, to facilitate easy peaking of the circuits. If the receiver being aligned is a sensitive type communications receiver, then an external attenuator will probably be necessary if using a cheaper type signal generator, to reduce the generator attenuator output to 1μV or less. The use of good quality coaxial cable is recommended for connection of the signal generator to the receiver to reduce r.f. leakage which could cause erroneous readings. This completes the alignment of the receiver and it should now perform in a most satisfactory manner.

Beat Frequency Oscillator

The majority of communications type receivers are fitted with a b.f.o. to enable the listener to copy either s.s.b. or Morse code transmissions. A small trimmer type capacitor is usually brought out to the


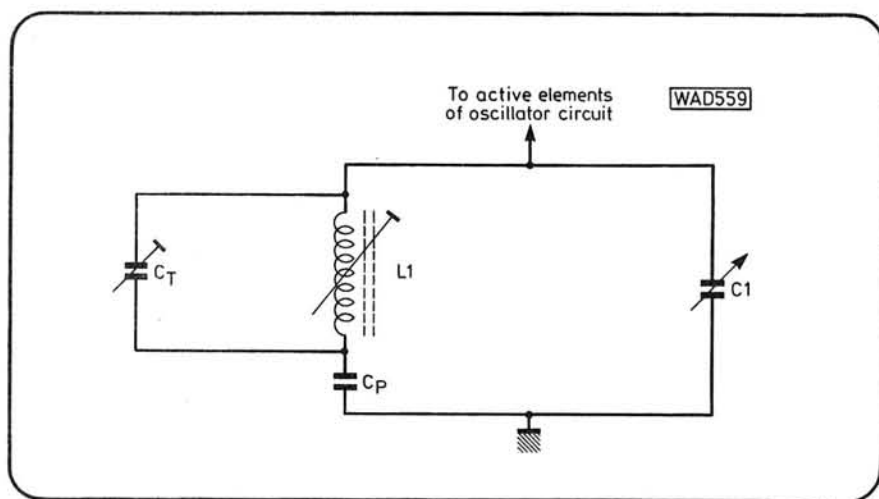


Fig. 6: Local oscillator tuned circuit

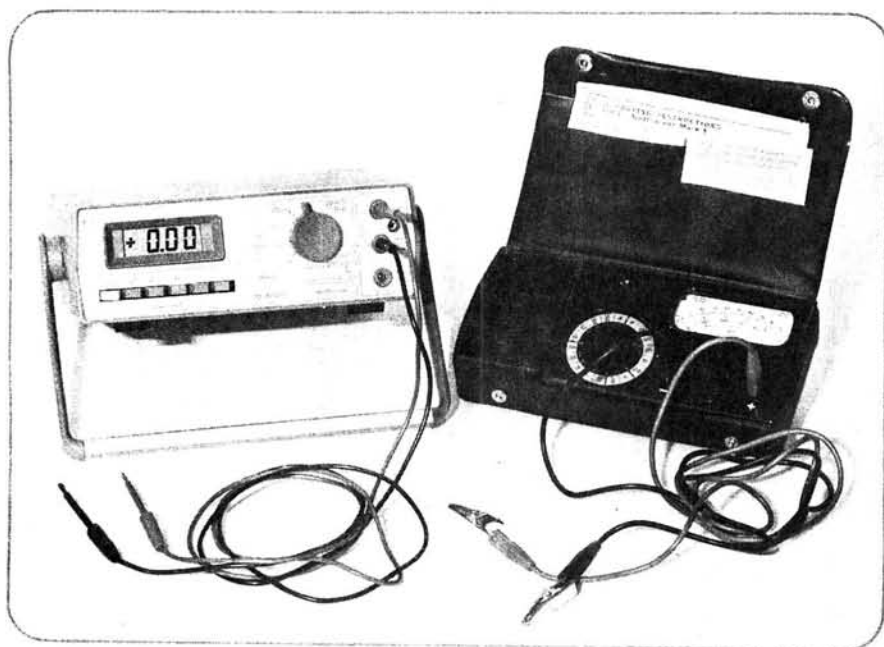

Two other commonly used meters

front panel to enable the frequency to be adjusted in the range ± 5 kHz. The main adjustment is by ferrite core in the b.f.o. coil assembly.

To align the b.f.o. correctly, set up the test equipment as for i.f. alignment, but without any modulation present. Set the signal generator to exactly the correct i.f. frequency, preferably with a counter, and then switch on the b.f.o. With the panel control set to zero, or mid-scale, depending on marking, adjust the coil core to zero beat with the generator input. When adjustments are completed, make sure the front panel trimmer swings the frequency of the beat note equally in both directions. This completes the alignment of the b.f.o.

Final Points

Although alignment can be performed reasonably well by ear alone, a more exact method to indicate maximum output is to connect a multimeter, switched to the 2-5V a.c. range across the speaker speech coil, taking care not to cause the meter to go beyond full scale deflection during the alignment process.

In those cases where the receiver is fitted with a ferrite rod aerial and no separate external aerial socket is provided, then injection from the signal generator should be via a coil of about

5 or 6 turns and 25mm diameter made from stout insulated wire placed over one end of the ferrite rod aerial. When actually adjusting the position of the coils on the ferrite rod, this sometimes being the r.f. input padding adjustment, then the injection coil should be kept well away from the coil being adjusted, otherwise coupling effects will reduce the Q of the tuned winding and alter the tuning point.

This guide is intended to give a general impression of the method employed for carrying out alignment and it must be realised that receivers vary considerably both in physical makeup, sensitivity and bandwidth and in all cases but the most simple, the steps in the maker's manual should be followed to the letter!

Double And Triple Superhets

These types of receiver are in common use and have distinct advantages in the way of bandwidth and rejection of unwanted signals, both internally generated and coming in via the aerial circuit.

The double superhet will have two conversion frequencies; probably a first i.f. of 1.6MHz and a second i.f. of 470 kHz to give superior image and second channel rejection performance over the

single conversion superhet. The triple conversion receiver goes a stage further and can give superior narrow i.f. bandwidth performance over the previous examples, by using a third i.f. stage of the order of 85kHz following the 470kHz amplifier stage and sometimes incorporating a mechanical filter.

In these receivers, only the first local oscillator is tuned by the main tuning control, the other oscillators will be preset and in some cases will be crystal controlled. The maker's manual is absolutely essential when aligning these receivers and must be adhered to in every detail during alignment, otherwise the receiver will never work satisfactorily. Also, alignment of these receivers should never be attempted unless essential and certainly not without the use of a device for measuring accurately the output frequency of the signal generator to be used.

Conclusions

Realignment of any receiver can usually be relied on to give a good indication of that receiver's general condition. During alignment, various faults may become apparent which would otherwise not be noticed and these faults should be dealt with prior to completing the alignment process.

When the job is completed, do not forget to reassemble the cabinet correctly as this forms the major screening device for the receiver; very important if of the solid-state type. Finally, do not forget to wipe off all the dirty fingermarks from the dial assembly, control panel and knobs. A useful tip for cleaning knobs is to use a stout toothbrush and some methylated spirit to scrub the dirt from the depths of the knurled parts, finishing off with a soft cloth. Do remember, please, NO SMOKING whilst this operation is in progress! A clean and tidy receiver is always a pleasure to look at as well as to operate.

