


- ① Add a dominant pole without changing any of the given poles.  
 ② The dominant pole will be at a low frequency and will give  $90^\circ$  of phase shift at high frequencies. To obtain a  $P_m = 45^\circ$ ,  $|T| = 1$  at 300 KHz because the pole at 300 KHz contributes  $45^\circ$  here, and the other poles contribute little phase shift. Since the GBW is constant after the dominant pole until 300 KHz,  $1 \cdot 300k = 5000 f_{dom} \rightarrow f_{dom} = \boxed{60 \text{ Hz}}$   
 Bandwidth with feedback  $\approx \boxed{300 \text{ KHz}}$

- ③ Because  $A_{CL} \approx 1/f$ , the feedback factor required to make  $A_{CL} = 20dB = 10$  is  $f = 1/10 = -20dB$ . Therefore  $1 \cdot 300k = 500 f_{dom} \rightarrow f_{dom} = \boxed{600 \text{ Hz}}$   
 Bandwidth with feedback still  $\approx \boxed{300 \text{ KHz}}$

- ④ Move the pole at 300 KHz to a low-enough frequency. After moving this pole, it will contribute  $90^\circ$  at the unity gain frequency, which must now be 2 MHz.  $1 \cdot 2 \text{ meg} = 5000 f_{dom} \rightarrow f_{dom} = \boxed{400 \text{ Hz}}$   
 Bandwidth with feedback  $\approx \boxed{2 \text{ MHz}}$

- ⑤  $f = 1/10$  as in (1b) above  $1 \cdot 2 \text{ meg} = 500 f_{dom} \rightarrow f_{dom} = \boxed{4 \text{ KHz}}$   
 Bandwidth with feedback still  $\approx \boxed{2 \text{ MHz}}$

③  $L_{eff} = L - 2L_d - X_d = 1 - 2(0.09) - 0.1 = 0.72 \mu\text{m}$   
 $|I_D| = 200 \mu\text{A}$  for  $M_8, M_5, M_7$  and  $M_6$ .  $|I_D| = 100 \mu\text{A}$  for  $M_1 - M_4$   
 $\frac{1}{r_o} = \frac{\partial I_D}{\partial V_{DS}} = \frac{I_D}{L_{eff}} \frac{dX_d}{dV_{DS}}$  From Table 2.4,  $\frac{dX_d}{dV_{DS}} = 0.02 \mu\text{m/V}$  (NMOS) or  $0.04 \mu\text{m/V}$  (PMOS)  
 $1/r_{o2} = (100 \mu / 0.72) (0.04 \mu) = 5.55 \mu\text{A/V}$   $1/r_{o4} = (100 \mu / 0.72 \mu) (0.02 \mu) = 2.78 \mu\text{A/V}$   
 $C_{ox} = \epsilon_{ox} / t_{ox} = 3.9 (8.85 \times 10^{-14}) / 80 \times 10^{-8} = 4.32 \times 10^{-7} \text{ F/cm}^2$   
 $K_p' = \mu_p C_{ox} = 150 (4.32 \times 10^{-7} \text{ F/cm}^2) = 64.7 \mu\text{A/V}^2$   
 $K_n' = \mu_n C_{ox} = 450 (4.32 \times 10^{-7} \text{ F/cm}^2) = 194 \mu\text{A/V}^2$   
 $q_{m2} = \sqrt{2 (64.7) (150 / 0.72) (100)} = 1.64 \text{ mA/V}$   
 $q_{m6} = \sqrt{2 (194) (100 / 0.72) (200)} = 3.28 \text{ mA/V}$   
 $1/r_{o7} = (200 \mu / 0.72 \mu) (0.04 \mu) = 11.1 \mu\text{A/V}$   $1/r_{o6} = (200 \mu / 0.72 \mu) (0.02 \mu) = 5.55 \mu\text{A/V}$   
 $N_o/N_i = q_{m2} (r_{o2} || r_{o4}) q_{m6} (r_{o6} || r_{o7}) = (1.64 \text{ mA} / 8.33 \mu) (3.28 \text{ mA} / 16.7 \mu) = \boxed{38700}$

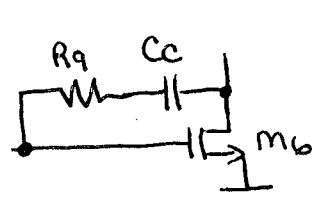

$Z = \frac{1}{(1/q_{m6} - R_q) C_c}$  Cancel this zero by moving it to  $\infty$   
 $R_q = 1/q_{m6} = 305 \Omega$   
 $\frac{1}{R_q} = \frac{\partial I_D}{\partial V_{DS}} = K' \left(\frac{W}{L}\right)_q (V_{GSq} - V_{Tq} - V_{DSq})$  and  $V_{DSq} = 0$   
 $= K' \left(\frac{W}{L}\right)_q (V_{Gq} - \frac{V_{S9} - V_{Tq}}{V_{S9} + V_{GS6}})$

Assume  $\delta = 0$   $1/R_q = K' \left(\frac{W}{L}\right)_q (1.5 - V_{GS6} - V_{Tq} + 1.5)$   
 $V_{GS6} = V_{T6} + V_{OV6}$   $V_{OV6} = \sqrt{\frac{2(200)}{194(100/0.72)}} = 0.122 \text{ V}$   
 $= 0.6 + 0.122$   
 $= 0.722 \text{ V}$

$1/305 = 194 \left(\frac{W}{L}\right)_q (3 - 0.722 - 0.6)$   
 $\left(\frac{W}{L}\right)_q = 10.0 = \omega q / [1 - 2(0.09)] = \omega q / 0.82 \mu \rightarrow \omega q = \boxed{18.3 \mu\text{m}}$   
 Use the same drawn length as for  $M_6$   $\leftarrow X_d$  for  $M_q = 0$  (Triode Region)

42-389 100% RECYCLED WHITE 5 SQUARE 42-389 200 RECYCLED WHITE 5 SQUARE 42-389 200 RECYCLED WHITE 5 SQUARE

③ continued  
The unity-gain frequency is the freq where  $|A(\omega)| = \left| \frac{g_{m1}}{j\omega C_c} \right| = 1$

$$f_{\text{unity}} = \frac{g_{m1}}{2\pi C_c} = \frac{1.64 \times 10^{-3} \text{ A/V}}{2\pi (5 \times 10^{-12} \text{ F})} = \boxed{52.2 \text{ MHz}}$$

$$\text{SlewRate} = \left. \frac{dV_o}{dt} \right|_{\text{max}} = \frac{I_{\text{max}}}{C_c} = \frac{200 \mu\text{A}}{5 \text{ pF}} = \boxed{40 \text{ V}/\mu\text{s}}$$

④ From ③,  $1/R_q = k'(\omega/L)_q (V_{GSq} - V_{tq})$

From KVL,  $V_{GSq} = V_{GS11} + V_{GS12} - V_{GS6}$

Since  $I_{D12} = I_{D6}$  and since  $(\omega/L)_{12} = (\omega/L)_6$ ,  $V_{OV12} = V_{OV6}$

Therefore  $V_{SB11} = V_{GS12} = V_{t12} + V_{OV12} = V_{SBq} = V_{GS6} = V_{t6} + V_{OV6}$   
because  $V_{t12} = V_{t6}$  (neither transistor has body effect)

Since  $V_{SB11} = V_{SBq}$ ,  $V_{t11} = V_{tq}$  (including body effect)

Also,  $V_{OV11} = V_{OV12}$  because  $I_{D11} = I_{D12}$  and  $(\omega/L)_{11} = (\omega/L)_{12}$

→ Therefore  $V_{GSq} = V_{t11} + V_{OV11} + V_{t12} + V_{OV12} - V_{t6} - V_{OV6}$   
 $= V_{t11} + V_{OV}$  where  $V_{OV} = V_{OV6} = V_{OV11} = V_{OV12}$

So  $V_{GSq} - V_{tq} = V_{t11} + V_{OV} - V_{tq} = V_{OV}$

Since  $V_{GSq} - V_{tq} = V_{GS6} - V_{t6}$  and since  $1/R_q$  should =  $g_{m6}$   
to cancel the RHP zero,

$$1/R_q = k'(\omega/L)_q (V_{GSq} - V_{tq}) = g_{m6} = k'(\omega/L)_6 (V_{GS6} - V_{t6})$$

$$(\omega/L)_q = (\omega/L)_6 = 100/1$$

⑤ To obtain 45° phase margin, set 2<sup>nd</sup> pole = unity gain frequency

$$|P_2| = \frac{g_{m6} C_c}{C_L C_1 + C_c C_L + C_1 C_c} = \frac{g_{m6}}{C_c} = \frac{1.64 \text{ mA/V}}{5 \text{ pF}} = 328 \text{ meg rad/s}$$

$C_1$  is dominated by the gate of  $m_6$

Minimum estimate for  $C_1 = C_{gs6(i)} + C_{gs6(oL)}$   
 $= \frac{2}{3}(100)(0.72)(4.3) + 0.35(100) = 241 \text{ fF}$

Maximum estimate for  $C_1 = C_{gs6(i)} + C_{gs6(oL)} + C_{gs9(i)} + C_{gs9(oL)}$   
 $+ C_{gd2(oL)} + C_{gd4(oL)}$

$$= \frac{2}{3}(100)(0.72)(4.3) + 0.35(100) + \frac{1}{2}(100)(0.82) + 0.35(100) + 0.35(150) + 0.35(50) = 387 \text{ fF}$$

$$328 \text{ meg rad/s} = \frac{3.28 \text{ m (5p)}}{C_L C_1 + C_L(5p) + C_1(5p)}$$

mq is in the triode region

Case 1 (min  $C_1$ )

$$C_L(241 \text{ fF}) + C_L(5 \text{ p}) + 241 \text{ fF}(5 \text{ p}) = 5 \times 10^{-23}$$

$$C_L = 9.3 \text{ pF}$$

Case 2 (max  $C_1$ )

$$C_L(387 \text{ fF}) + C_L(5 \text{ p}) + 387 \text{ fF}(5 \text{ p}) = 5 \times 10^{-23}$$

$$C_L = 8.9 \text{ pF}$$

Therefore,  $C_L$  should be less than about  $\boxed{8.9 \text{ pF}}$