

one dollar

# ham radio


magazine

hr 
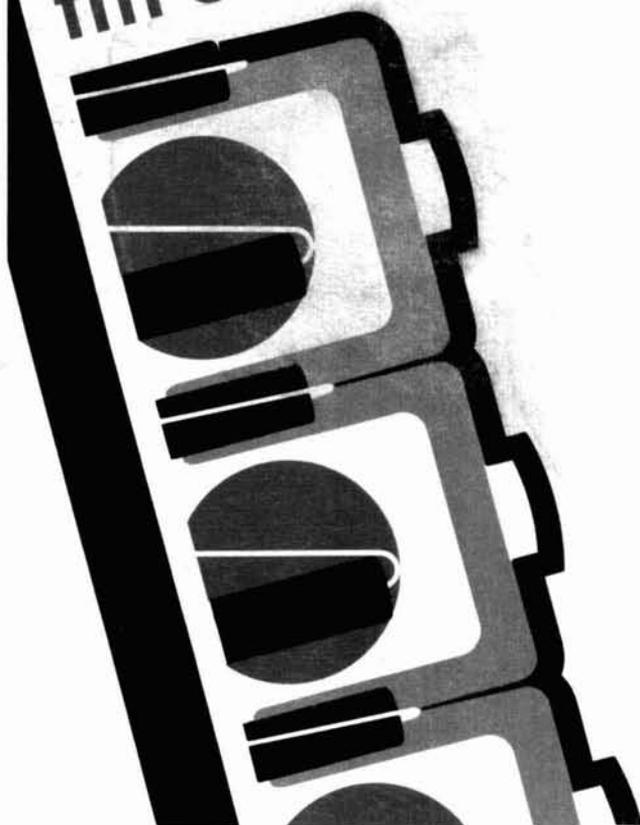
## AUGUST 1976

- RTTY demodulator 16
- television scan converters 44
- coaxial dipole antennas 46
- differential keying circuit 60
- microprocessors 74
- and much more . . .

high-performance  
two-meter  
fm exciter



# INTRODUCING



- \*Phase lock-loop (PLL) oscillator circuit minimizes unwanted spurious responses.
- \*Hybrid Digital Frequency Presentation.
- \*Advanced Solid-state design...only 3 tubes.
- \*Built-in AC and 12 VDC power supplies.
- \*CW filter standard equipment...not an accessory.
- \*Rugged 6146-B final amplifier tubes.
- \*Cooling fan standard equipment...not an accessory.
- \*High performance noise-blanker is standard equipment ...not an accessory.
- \*Built-in VOX and semi-break in CW keying.
- \*Crystal Calibrator and WWV receiving capability.

## The **TEMPO 2020**

**A BRILLIANT NEW SSB TRANSCEIVER PROVIDING AN UNBEATABLE COMBINATION OF ADVANCED ENGINEERING AND UNIQUE OPERATING FEATURES.**

**YOU MAY NEVER HAVE OWNED A TRANSCEIVER THAT OFFERS SO MUCH.**


Send for descriptive information on this fine new transceiver, or on the time proven Tempo ONE transceiver which continues to offer reliable, low cost performance.

- \*Microphone provided.
- \*Dual RIT control allows both broad and narrow tuning.
- \*All band 80 through 10 meter coverage.
- \*Multi-mode USB, LSB, CW and AM operation.
- \*Extraordinary receiver sensitivity (.3u S/N 10 db) and oscillator stability (100 Hz 30 min. after warm-up)
- \*Fixed channel crystal control on two available positions.
- \*RF Attenuator.
- \*Adjustable ALC action.
- \*Phone patch in and out jacks.
- \*Separate PTT jack for foot switch.
- \*Built-in speaker.
- \*The TEMPO 2020 ...\$759.00.  
Model 8120 external speaker...\$29.95.  
Model 8010 remote VFO...\$139.00.

## *Henry Radio*

11240 W. Olympic Blvd., Los Angeles, Calif. 90064 213/477-6701  
931 N. Euclid, Anaheim, Calif. 92801 714/772-9200  
Butler, Missouri 64730 816/679-3127

# 2 METERS...

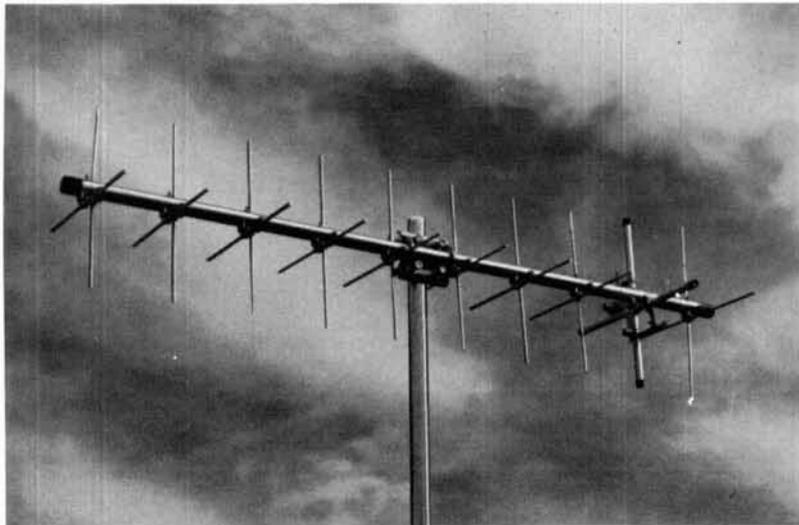

... *Alive* with activity at *both* ends of the band! Be a part of the total 2 Meter picture with the Cush Craft Twist Antenna. Actually two, easily assembled, 10 element yagis in one — the vertical elements are cut for the high end, the horizontal elements for the low end, and separate feed lines are used. The A147-20T is tailored to meet the demands of the operator who enjoys the best of both worlds


— FM and SSB/CW.

A147-20T

\$47.50
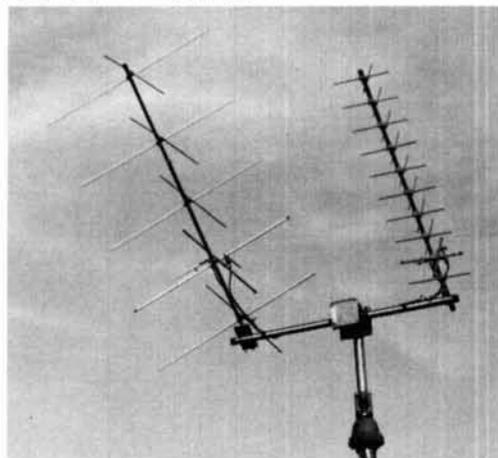
# CQ OSCAR

... *Extend your horizon* — Explore the exciting new world of amateur satellite communications using low power with our multi-polarized Twist Antennas. All models include phasing harness for selectable linear or right/left circular polarization. Two of these Twists may be mounted on the A14T-MB mounting boom which is complete with a pre-drilled plate for a readily available mast-through rotator. *Face this challenging frontier — Become a Specialist!*




A144-10T \$32.50

A432-20T \$45.00

A144-20T \$47.50

A14T-MB \$13.95

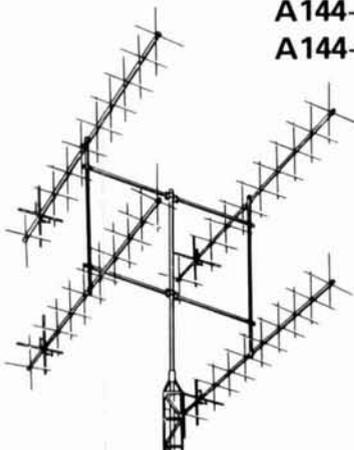

## PERFORMANCE ARRAYS . . .

Enjoy fade-free contacts on VHF/UHF with Twist Antennas and Arrays. Excellent for scatter and other long-haul techniques. Double your effective radiated power by stacking two Twists, or quadruple ERP by stacking four Twists. Arrays are easily assembled for your special communications requirement. Write for stacking and phasing harness details concerning amateur and commercial frequencies.

*Dependable communications — Now Yours!*

### SPECIFICATIONS

Model	A147-20T	A144-10T	A144-20T	A432-20T
Center Freq. (MHz)	144.5/146.5	145.9	145.9	432
No. Elements	10/10	10	20	20
Weight (lbs.)	6	3.5	6	3.5
Wind Surf. Area (ft. <sup>2</sup> )	1.42	.74	1.42	.37
Mounting	Center	Rear	Center	Rear
Dimensions (Inches)	40x40x140	40x40x70	40x40x140	14x14x57
Front-to-Back Ratio (dB)	22	22	22	22
Forward Gain (dBd) circular	—	10.8	13.6	13.6
linear	12.4	9.6	12.4	12.4

IN STOCK WITH  
DISTRIBUTORS WORLDWIDE

**cushcraft**  
CORPORATION

621 HAYWARD ST., MANCHESTER, N. H. 03103

# Stay tuned for future programs.



The HAL ST-6000 demodulator/keyer and the DS-3000 and DS-4000 KSR/RO series of communications terminals are designed to give you superlative TTY performance today—and in the future. DS series terminals, for example, are re-programmable, assuring you freedom from obsolescence. Sophisticated systems all, these HAL products are attractively priced—for industry, government and serious amateur radio operators.

The HAL ST-6000 operates at standard shifts of 850, 425, and 170 Hz. The tone keyer is crystal-controlled. Loop supply is internal. Active filters allow flexibility in estab-

lishing different tone pairs. You can select AM or hard-limiting FM modes of operation to accommodate different operating conditions. An internal monitor scope (shown on model above) allows fast, accurate tuning. The ST-6000 has an outstandingly high dynamic range of operation. Data I/O can be RS-232C, MIL-188C or current loop.

The DS-3000 and DS-4000 series of KSR and RO terminals provide silent, reliable, all-electronic TTY transmission and reception, or read-only (RO) operation of different combinations

of codes, including Baudot, ASCII and Morse. The powerful, programmable 8080A microprocessor is included in the circuitry to assure maximum flexibility for your present needs—and for the future. The KSR models offer you full editing capability. The video display is a convenient 16-line format, of 72 characters per line.

These are some of the highlights. The full range of features and specifications for the ST-6000 and the DS series of KSR and RO terminals is covered in comprehensive data sheets available on request. Write for them now—and tune in to the most sophisticated TTY operation you can have today... or in the future.



HAL Communications Corp., Box 365, 807 E. Green Street  
Urbana, Illinois 61801 • Telephone: (217) 367-7373

# ham radio

magazine

**AUGUST 1976**  
volume 9, number 8

**editorial staff**

James R. Fisk, W1DTY  
editor-in-chief

Patricia A. Hawes, WN1WPM  
Alfred Wilson, W6NIF  
assistant editors

J. Jay O'Brien, W6GO  
fm editor

Joseph J. Schroeder, W9JUV  
associate editor

Wayne T. Pierce, K3SUK  
cover

**publishing staff**

T. H. Tenney, Jr., W1NLB  
publisher

Harold P. Kent, WN1WPP  
assistant publisher

Fred D. Moller, Jr., WN1USO  
advertising manager

Cynthia M. Schlosser  
assistant advertising manager

Therese R. Bourgault  
circulation manager

ham radio magazine is published monthly by  
Communications Technology, Inc  
Greenville, New Hampshire 03048  
Telephone: 603-878-1441

**subscription rates**

U.S. and Canada: one year, \$10.00  
three years, \$20.00  
Worldwide: one year, \$12.00  
three years, \$24.00

**foreign subscription agents**

Ham Radio Canada  
Box 114, Goderich  
Ontario, Canada, N7A 3Y5

Ham Radio Europe  
Box 444  
194 04 Upplands Vasby, Sweden

Ham Radio France  
20 bis, Avenue des Clarions  
89000 Auxerre, France

Ham Radio Holland  
Postbus 3051  
Delft 2200, Holland

Ham Radio Italy  
STE, Via Maniago 15  
I-20134 Milano, Italy

Ham Radio UK  
Post Office Box 64, Harrow  
Middlesex HA3 6HS, England

Holland Radio, 143 Greenway  
Greenside, Johannesburg  
Republic of South Africa

Copyright 1976 by  
Communications Technology, Inc  
Title registered at U.S. Patent Office

Microfilm copies  
are available from  
University Microfilms  
Ann Arbor, Michigan 48103

Second-class postage  
paid at Greenville, N.H. 03048  
and at additional mailing offices



## contents

**10 high-performance vhf fm transmitter**

G. Francis Vogt, WA2GCF

**16 RTTY demodulator**

Nathan H. Stinnette, W4AYV

**18 application and use of the  
hand-held calculator**

Robert P. Haviland, W4MB

**24 syllabic vox system for Drake equipment**

Ray W. Hitchcock, W6RM

**30 derivation of electrical units**

Robert R. Simmons, WB6EYV

**34 i-f and detector module**

M. A. Chapman, K6SDX

**44 digital television scan converters**

David L. Ingram, K4TWJ

**46 coaxial dipole antennas:  
facts and fallacies**

M. Walter Maxwell, W2DU

**60 differential keying circuit**

Fred M. Griffee, W4IYB

**66 TTL IC tester**

Kenneth H. Leiner, WA4LCO

**70 vhf bandpass filter**

Paul H. Sellers, W4EKO

**74 microprocessors**


David G. Larsen, WB4HYJ

Peter R. Rony

Jonathan A. Titus

4 a second look  
126 advertisers index  
101 flea market  
116 ham mart  
80 ham notebook

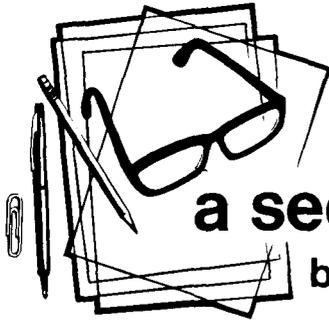88 new products  
30 novice reading  
126 reader service  
6 stop press



## a second look

by Jim Fisk

"At this very minute, with almost absolute certainty, radio waves sent forth by other intelligent civilizations are falling on earth. A telescope can be built that, pointed in the right place, and tuned to the right frequency, could discover these waves. Someday, from somewhere out among the stars, will come the answers to many of the oldest, most important, and most exciting questions mankind has asked."

Frank D. Drake

*Intelligent Life in Space*

In the late 1950s, soon after the United States became involved in a concentrated effort to place an astronaut into orbit around the earth, several scientific groups began to think seriously about using radio telescopes to search for extraterrestrial intelligence. Inspired by articles in such prestigious magazines as *Scientific American* and *Sky and Telescope*, amateur radio astronomers began taking part in Project Ozma, pointing their antennas toward the heavens, looking for radio signals from intelligent beings in outer space. They didn't know where to look, nor what frequency to tune, so it's not surprising that when nothing was found for several years, enthusiasm began to wane. Then an English radio astronomer discovered the first pulsar, many scientists postulated that it might be a controlled radio beam from intelligent life in another galaxy, and a whole new search for extraterrestrial communications was soon underway.

Unfortunately, there was no organized follow-up to Project Ozma, so it's not known today how many individuals or groups are still listening, nor who and where they are. Nick Marshall, W6OLO, a member of the very first Oscar group back in 1960, became interested in this problem and announced the formation of a "Reviva Ozma" committee at the 1975 Project Oscar meeting at Foothill College in California. One of the goals of Reviva Ozma (now known as Starquest) would be to locate and communicate with individuals and groups who were still listening, and to help them publish their findings. Another goal was to assemble a state-of-the-art listening post which would be dedicated to continuing the search for radio signals of extraterrestrial origin.

In late 1975 Marshall contacted Dr. John Billingham at the NASA-Ames Research Center for further information on the Project Cyclops follow-on, a NASA study of a system for detecting intelligent extraterrestrial life. It became immediately apparent that Starquest could serve an interim purpose by disseminating correct information about Project Cyclops and, more importantly, assist in trying to keep various listening frequencies clear of occupancy by commercial, industrial, and government radio services.

Marshall also made contact with members of Operation Serendip, a study being conducted by a small group from the University of California at Berkeley. This group has been using an 82-foot (25m) dish near Mt. Lassen to listen and record extraterrestrial signals on 1420 MHz and process the data on a pdp-8 computer.

Foothill College graciously offered the Starquest group an antenna location near their observatory, and work is now underway on a spherical dish which is patterned after the 1000-foot (305m) dish at Arecibo, Puerto Rico, although on a much smaller scale. The initial Starquest dish will have a 35- to 50-foot (10.7m-15.2m) center section which can be expended later to about 100 feet (30m) in diameter. Starquest members are also formulating plans for a state-of-the-art receiving and data-processing system which will be used in the station. In the near future the group is expected to start publishing a quarterly *Starquest Bulletin* which will be mailed to members and affiliates.

In addition to their other activities, Starquest has established a world-wide amateur-radio net on 20 meters for gathering and disseminating information relating to the search for extraterrestrial signals. This net, which meets on 14.280 MHz ( $\pm 5$  kHz) at 1900 GMT, the first Sunday of every month, is now operational. It is hoped that interested amateurs and experimenters will listen in, and help Starquest locate other interested groups in their own local areas who are involved in the search for intelligence in outer space. Amateurs living in Northern California who would like to participate directly in the construction of the Starquest listening station are invited to contact W6OLO for more information.

Jim Fisk, W1DTY  
editor-in-chief



# Now It's Crystal Clear

Yes, now ICOM helps you steer clear of all the hassles of channel crystals. The new **IC-22S** is the same surprising radio you've come to know and love as the **IC-22A**, except that it is totally crystal independent. **Zero crystals.** Solid state engineering enables you to program 23 channels of your choice without waiting. Now the ICOM performance you've demanded comes with the convenience you've wanted, with your new **IC-22S**.

VHF/UHF AMATEUR AND MARINE COMMUNICATION EQUIPMENT

Distributed by:



**ICOM WEST, INC.**  
Suite 3  
13256 Northrup Way  
Bellevue, Wash. 98005  
(206) 747-9020

**ICOM EAST, INC.**  
Suite 307  
3331 Towerwood Drive  
Dallas, Texas 75234  
(214) 620-2780



FCC'S FIRST ACTION ON RESTRUCTURING was taken in mid June, and Novices and Technicians became the principal beneficiaries. This first Report and Order on Docket 20282 liberalizes both license classes' privileges but appears to reject the "Dual Ladder" approach to restructuring that was such an integral part of the Docket's original philosophy.

Technician Class Licensees receive the most significant benefit in the form of full Novice privileges — CW on 80, 40, 15 and 10 meters. No other Technician privileges were changed at this time, so it's still possible that 10-meter phone and/or expansion of Technician frequencies on the bottom of two or six meters may be part of expected later actions on 20282. Technician exams will no longer be "mail order," either — the Report and Order makes administration of Tech exams an FCC Field Office job.

Novices Receive two benefits under the just announced Rules changes. Power limits for Novices have been raised to 250 watts, and a Novice who has failed to upgrade during his two-year license term will be permitted to continue as a Novice by taking another Novice exam — the requirement for a one-year delay before going for another Novice license has been dropped. The new 250 watt Novice power limit actually applies to Novice frequencies, by the way — any station operating in the Novice sub bands will be limited to 250 watts, regardless of license class.

All "Mail Order" Amateur Exams except Novice are effectively being eliminated. The one exception that will remain is for an applicant who cannot travel because of medical reasons and who can back it up with a physician's statement.

Deletion Of Conditional Amateur Licenses won't shut the door on Americans overseas such as servicemen and missionaries who can't get to an FCC Field Office for their exams. Procedures to take care of such people are being developed and they will be taken care of on a case-by-case basis. One idea being considered is a "Conditional" license good only while the holder remains out of the country — he'd have to be re-examined by the FCC on return if he wished to continue his Amateur activities.

All Present Conditional and Technician (C) license holders will be "grandfathered" into straight Technician and General Class licenses as their present licenses come up for renewal. No re-examinations will be required, which should make at least a few present license holders breathe easier!

AMATEUR LICENSING TIMES have definitely dropped since our last report, with several recent renewals returned 37 to 45 days after they went into the mail. As of early July the FCC was handling requests for volunteer exams in about two weeks, down from six weeks in early June.

The Next Big Hurdle is the phase-in of WD calls, where computer programming problems have developed. Until they're overcome, significant delays in getting new licenses out are likely to begin to occur despite efforts to head the problems off.

AMATEUR RADIO IS VERY PROMINENT in the Smithsonian Institution's newest displays. OSCAR 1 is on display in the Communications Satellite area of the new Hall of Satellites, and NN3SI, the Institution's new Amateur station located in the Museum of History and Technology, was dedicated on June 8th. First contact from NN3SI was on CW with trustee W4KFC working W1AW with the same key General Sarnoff used in 1912 when he participated in the Titanic disaster.

NN3SI is the Institution's special events call — WB3APS is its regular call — and NN3SI has been authorized for a year with operation on all bands and OSCAR planned.

Smithsonian's New Amateur Station can be a bit tricky to get to, warns K8NHR. It's almost directly under the antennas, and can be found by bearing hard left after entering the building's main entrance.

UNLICENSED 27 MHZ OPERATORS are protected by a legal loophole — the Communications Act of 1934 gives FCC jurisdiction only over licensees. Justice Department is the agency with the power to go after unlicensed operators, but it has neither the tools (as FCC does) nor time to chase down all such violators.

This "Catch 22" May Change shortly, however — FCC Chairman Wiley said at the CES show in Chicago in mid June that there is legislation pending before both houses of Congress that would give the FCC power to prosecute unlicensed operators and confiscate their equipment, and he expects it to become law very quickly.

TWO-LETTER CALLSIGN availability chart has been prepared by the ARRL from current FCC records and can be had for the asking. It covers all ten districts and includes instructions on the procedure for requesting a two-letter call. Send an SASE with 24¢ postage to ARRL for a copy.

MOONBOUNCE ENTHUSIASTS are going to get a crack at Alaska thanks to K6YNB/KL7. Wayne plans to open up from Ketchikan, August 11th on 144 and switch to 432 about the 18th. He also plans to be on 50 and 220 MHz, but not with the same big gun antennas that he'll use on the other bands. Meteor scatter (the Perseids shower occurs during that period) as well as possible tropo and Aurora contacts are also expected during the trip.

# Does Your Transmitter Love Your Antenna?



If you're fighting the constant battle of limited band width, high SWR ratios, inefficient low-pass TVI filter operation due to high SWR you're not alone.

## DenTron makes the Problem Solvers.

The DenTron tuners give you maximum power transfer from your transmitter to your antenna, and isn't that where it really counts?

Our Super Tuners (A, B, & E.) are the only tuners on the market that match everything between 160 and 10 meters. Whether you have balanced line, coax cable, random or long wire the DenTron Super Tuners will match the antenna impedance to your transmitter.

**NEW:** The Monitor Tuner (E.) was designed because of overwhelming demand. Hams told us they wanted a 3 kilowatt tuner with a built-in wattmeter, a front panel antenna selector for coax, balanced line and random wire. So we engineered the 160-10m Monitor Tuner. It's a life time investment at \$299.50

The DenTron 80-10 AT (D.) is a random wire, 80-10 meter tuner which is ideal for portable operation or apartment dwellers.

Every serious ham knows he must read both forward and reverse wattage simultaneously for that perfect match. So upgrade with the DenTron W-2 Dual in line Wattmeter. (C.)

The flexibility we build into our Tuners make any previous tuner you might have owned obsolete.

A. Super Tuner 1KW PEP	\$129.50
B. Super Super Tuner 3 KW PEP	\$229.50
C. W-2 Wattmeter	\$ 99.50
D. 80-10 AT 500 W PEP	\$ 59.50
E. Monitor Tuner 3 KW PEP	\$299.50

All DenTron products are made in U.S.A.

**DenTron**  
Radio Co., Inc.

2100 Enterprise Parkway  
Twinsburg, Ohio 44087  
(216)425-3173

*Dedicated to Making Amateur Radio MORE FUN!*

# KENWOOD'S TS-520

*...worth waiting for!*



Why wait any longer for a rig that offers top performance, dependability and versatility... the TS-520 has proven itself in the shacks of thousands of discriminating amateurs, in field day sites, in DX and contest stations, and in countless mobile installations.

Superb craftsmanship is evident throughout... in its engineering concepts as well as its construction and styling... craftsmanship that is a Kenwood hallmark.

Maybe the Kenwood TS-520 is the one you have been waiting for.

Kenwood offers accessories guaranteed to add to the pleasure of owning the TS-520. The TV-502 transverter puts you on 2-meters the easy way. (It's completely compatible with the TS-520.) Simply plug it in and you're on the air. Two more units designed to match the TS-520 are the VFO-520 external VFO and the model SP-520 external speaker. All with Kenwood quality built in.



## TS-520 Specifications

MODES: USB, LSB, CW  
POWER: 200 watts PEP input on SSB, 160 watts DC input on CW  
ANTENNA IMPEDANCE: 50-75 Ohms, unbalanced  
CARRIER SUPPRESSION: Better than -45 dB  
UNWANTED SIDEBAND SUPPRESSION: Better than -40 dB  
HARMONIC RADIATION: Better than -40 dB  
AF RESPONSE: 400 to 2600 Hz (-6 dB)  
AUDIO INPUT SENSITIVITY: 0.25 $\mu$ V for 10 dB (S+N)/N  
SELECTIVITY: SSB 2.4 kHz (-6 dB), 4.4 kHz (-60 dB) CW 0.5 kHz (-6 dB), 1.5 kHz (-60 dB) (with accessory filter)  
FREQUENCY STABILITY: 100 Hz per 30 minutes after warmup  
IMAGE RATIO: Better than 50 dB  
IF REJECTION: Better than 50 dB  
TUBE & SEMICONDUCTOR COMPLEMENT: 3 tubes (2 x 6146B, 12BY7A), 1 IC, 18 FET, 44 transistors, 84 diodes  
DIMENSIONS: 13.1" W x 5.9" H x 13.2" D  
WEIGHT: 35.2 lbs.  
SUGGESTED PRICE: \$629.00

### VFO-520

Provides high stability with precision gearing. Function switch provides any combination with the TS-520. Both are equipped with VFO indicators showing at a glance which VFO is being used. Connects with a single cable and obtains its power from the TS-520. Suggested price: \$115.00.

### SP-520

Although the TS-520 has a built-in speaker, the addition of the SP-520 provides improved tonal quality. A perfect match in both design and performance. Suggested price: \$22.95.

### TV-502

TRANSMITTING/RECEIVING FREQUENCY: 144.145.7 MHz, 145.0-146.0 MHz (option)  
INPUT/OUTPUT IF FREQUENCY: 28.0-29.7 MHz  
TYPE OF EMISSION: SSB (A3J), CW (A1)  
RATED OUTPUT: 8W (AC operation)  
ANTENNA INPUT/OUTPUT IMPEDANCE: 50 $\Omega$   
UNWANTED RADIATION: Less than -60 dB  
RECEIVING SENSITIVITY: More than 1 $\mu$ V at S/N 10 dB  
IMAGE RATIO: More than 60 dB  
IF REJECTION: More than 60 dB  
FREQUENCY STABILITY: Less than  $\pm 2.5$  kHz during 1-60 min after power switch is ON and within 150 Hz (per 30 min) thereafter.  
POWER CONSUMPTION: AC 220/120V, Transmission 50W max., Reception 12W max. DC 13.8V, Transmission 2A max., Reception 0.4A max.  
POWER REQUIREMENT: AC 220/120V, DC 12-16V (standard voltage 13.8V)  
SEMI CONDUCTOR: FET 5, Transistor 15, Diode 10.  
DIMENSIONS: 6 $\frac{1}{4}$ " W x 6" H x 13 $\frac{1}{4}$ " D  
WEIGHT: 11.5 lbs.  
SUGGESTED PRICE: \$249.00

**CW-520**  
500 Hz CW Crystal Filter: \$45.00.

Prices subject to change without notice

TRIO-KENWOOD COMMUNICATIONS INC

# KENWOOD GIVES YOU A CHOICE FOR 2-METER SSB



**KENWOOD'S TV-502 TRANSVERTER PUTS YOUR TS-520 OR TS-820 ON THE 2-METER BAND...SSB AND CW. SIMPLY PLUG IT IN AND YOU'RE ON THE AIR**



**OR GO ALL THE WAY WITH THE BEST...THE TS-700A**

Ever tried 2 meter SSB or CW? How about the OSCAR satellite? Tune the band with a VFO instead of fixed channel crystals and experience DX-ing on VHF. In fact, there's a VHF QSO party coming up on September 11 thru 13. FMers improve your scores...beginners try it for the first time. You don't need a big antenna to do it either...anything from a coat hanger to ---? The OSCAR satellites (6 & 7) are waiting for you too! Or go exotic with meteor scatter or tropospheric ducting. The "Sky is the limit" on VHF SSB and CW.

116 EAST ALONDRA/GARDENA, CA 90248



**KENWOOD**  
...pacesetter in amateur radio

# high-performance two-meter fm exciter

Eleven channels,  
superior modulation and  
complete kit availability  
are just  
a few features  
of this little jewel

After reviewing the limited number of two-meter fm transmitter construction articles available to the homebrew enthusiast, I decided it was time to break away from the Sonobuoy-type design and try to generate some interest in building a more conventional commercial-type exciter. This article is the result of the overwhelming response to an earlier construction article for an fm receiver<sup>1</sup> of the type of design I am encouraging.

Before dismissing the Sonobuoy-type exciter completely, I'd like to mention that these designs, which have appeared in the amateur literature for the past few years, deserve a great deal of credit. They were easy to build and were the first solid-state transmitters to gain wide popularity and to be constructed in quantity. However, they had some disadvantages that I've attempted to correct:

1. The Sonobuoy designs used direct frequency modulation of the oscillator with a varicap diode. Although sometimes described as a feature such modulation often resulted in unsymmetrical modulation because of improper dc biasing. For some reason, this flaw has been perpetuated in several spinoffs of the Sonobuoy transmitter that I've seen.
2. Direct fm circuits made crystal switching difficult. Such circuits could not be used with a frequency synthesizer.
3. Audio circuits weren't really optimized for voice operation with a variety of microphones; not surprising since Sonobuoys were designed for a different purpose.
4. Tuned circuits were unshielded and construction, in general, was intended to be of the "disposable" type

By **Jerry Vogt, WA2GCF**, 182 Belmont Road,  
Rochester, New York 14162

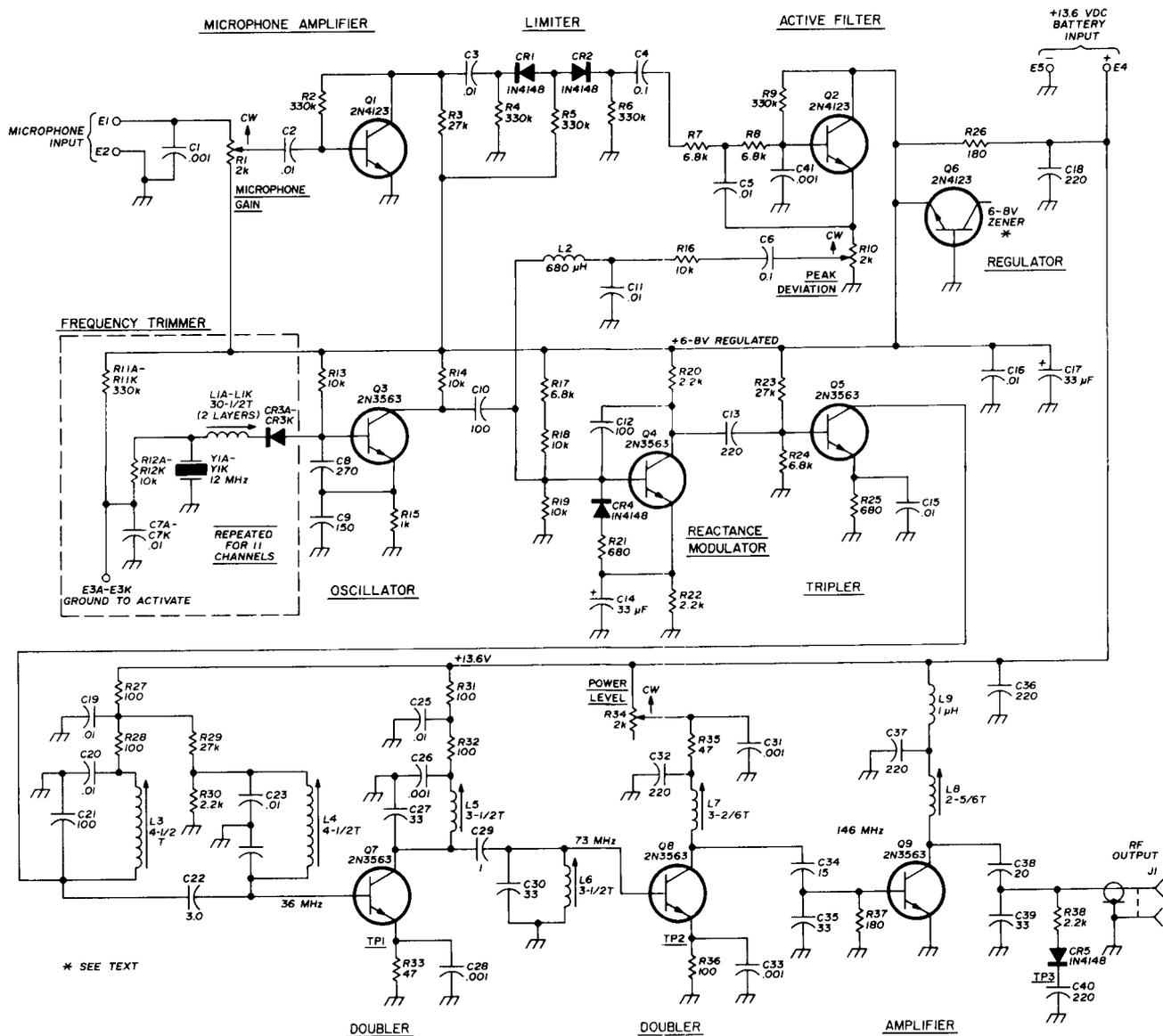


fig. 1. Schematic of the high-performance 2-meter fm exciter. A complete parts kit is available together with other accessories at modest cost.

because of the original intended design function. You can readily see the difference when such a unit sits next to a commercially designed two-way radio.

### design goals

After sorting through the many available circuits for a two-meter fm transmitter, design objectives were based

Here's an example of *ham radio's* promise to bring you construction articles based on available kits so that parts scrounging will be a thing of the past. This two-meter fm exciter has been designed with the homebrewer in mind — easy to build and easy to align and get working. You'll find many features that are included in the latest commercial designs. Best of all, the parts kit price won't fracture your pocketbook. **Editor**

on the best features of some of these circuits that could be implemented with readily available parts and simple construction.\* The design goals were:

1. Superior modulation — quality to be proud of in either a repeater or home station.
2. Inclusion of both deviation and microphone gain controls.
3. Effective lowpass filter following the modulation limiter to eliminate raspy voice signals.
4. Compatibility with either carbon or transistor-amplified dynamic microphones.

\*A list of kits and accessories for the transmitter will be found at the end of this article.

5. Phase modulation suitable for use with multichannel operation and frequency synthesizers.
6. Shielded coils and sufficient tuned circuits between multiplier stages to reject harmonics and spurious signals.
7. A maximum number of electronically switched and individually adjustable channels, consistent with the selected board size along with exciter and multiplier stages.



Top view of the completed 2-meter fm exciter showing clean layout of parts without overcrowding.

8. An oscillator using common 12-MHz series-resonant crystals.
9. Voltage regulator for oscillator, modulator, and audio stages to minimize effects of line-voltage variation and noise.
10. Adjustable output level.
11. Sufficient output power (150-200 milliwatts) to drive the new rf power modules now available.
12. A design easy to build, align, and test.

### features and technical characteristics

The exciter measures 3 x 7½ x 1 inches (7.6 x 19 x 2.5cm) and weighs 5 ounces (142gm). Operating power is +13 volts at 70 mA. Sufficient power is provided for use as a control link, or the exciter can be used as a low-power transmitter. It can be adapted easily to 50 or 220 MHz by changing the multiplier tuned circuits, or it can be adapted to 450 MHz by adding tripler/driver stages on a separate board.

Eleven oscillator channels are used. Multilayer oscillator frequency-netting coils provide vernier adjustment on each channel. A simple ground-on diode channel-switching scheme allows easy adaptation to trunk mounting (important in these days of ripoffs) or other remote-control application. CW operation is possible by keying the B+ line to the multiplier and output-amplifier stages.

The exciter can also be used as an inexpensive multi-

channel frequency standard or fm signal generator. A convenient output-level control, used with an external fixed attenuator, provides variable output level.

The exciter schematic is shown in fig. 1. Audio signals from a carbon or transistor-amplified dynamic microphone are applied to microphone amplifier Q1 through microphone gain control R1. This control, normally not provided in most transmitters, allows the audio level to the limiter stage to be adjusted independently of deviation level, so that sufficient audio punch is obtained without excessive clipping. Limiter CR1, CR2 consists of back-to-back diodes forward biased a small amount. When audio peaks exceeding the bias level are applied, clipping action limits the audio transferred to the next stage. Q2 is a lowpass filter with a cutoff frequency just above the normal voice range to remove the audio harmonic components generated by clipping the audio signal. This stage, together with its separate microphone gain and deviation controls, is primarily responsible for the professional-sounding modulation of this exciter.

The 12-MHz injection to the modulator is provided by Clapp oscillator Q3. Eleven channels are diode switched by grounding the appropriate control lines. The diodes are reverse biased except the one having its control line activated to cause dc conduction, thereby completing the path to one crystal circuit from the base of Q3. The variable coil allows the crystal load reactance to be varied for frequency netting.

The phase-modulated 12-MHz signal from reactance-modulator stage Q4 is multiplied in tripler stage Q5, doubler Q7, and doubler Q8. Double-tuned circuits between multiplier stages provide rejection of spurious frequencies. (Multipliers create more than one harmonic, of course; and if tuned circuits of sufficiently high Q are not used, undesired frequencies will be passed through the multiplier chains to cause spurs in the transmitter output).

The B+ voltage to doubler Q8 is adjustable with series potentiometer R34 to provide output power level control. This control is normally set fully clockwise but may be used to reduce output level if desired. (For example, to limit drive to a power amplifier or provide variable output when used as an alignment generator). Amplifier Q9 provides 150-200 mW output to a 50-ohm load (2-3 volts). This level was chosen to drive an rf power module and is also suitable for several other applications. If desired, a simple one-watt PA stage could be added as well as many other types of amplifiers, although the rf power module is simplest by far.

To allow for easy alignment with only a vtm, three test points provide dc signals as a function of rf levels at several stages. TP1 and TP2 provide indications of emitter current in the two doubler stages. TP3, in conjunction with rf detector CR5, C40, provides an indication of rf output to the antenna or power amplifier.

### power amplifiers

There is only one word to describe the new rf power modules by TRW and Motorola: "fantastic." You have probably seen them in advertisements for various radios.

The photo of a power amplifier using one of the rf power modules shows how simple it is to make a PA of moderate power level today. The exciter in this article was designed to drive these power-module PAs.

The rf power modules, or "bricks" as they're sometimes called, are magic compared to the alternative. Each PA brick is an integrated circuit containing several power amplifier stages with decoupling and tuned circuits to provide many watts output for 150-200 mW input. All

## construction

The exciter is assembled on a single-sided 3 x 7½ inch (7.6x19cm) PC board. Construction details are shown in fig. 2. The following details of coil assembly and other suggestions are given to facilitate assembly.

Plastic coil forms of ¼ inch (6mm) OD are used with ½ inch (13mm) square shields and vhf tuning slugs. The coils (fig. 1) are wound in a clockwise direction as viewed from the top, using the solderable wire supplied

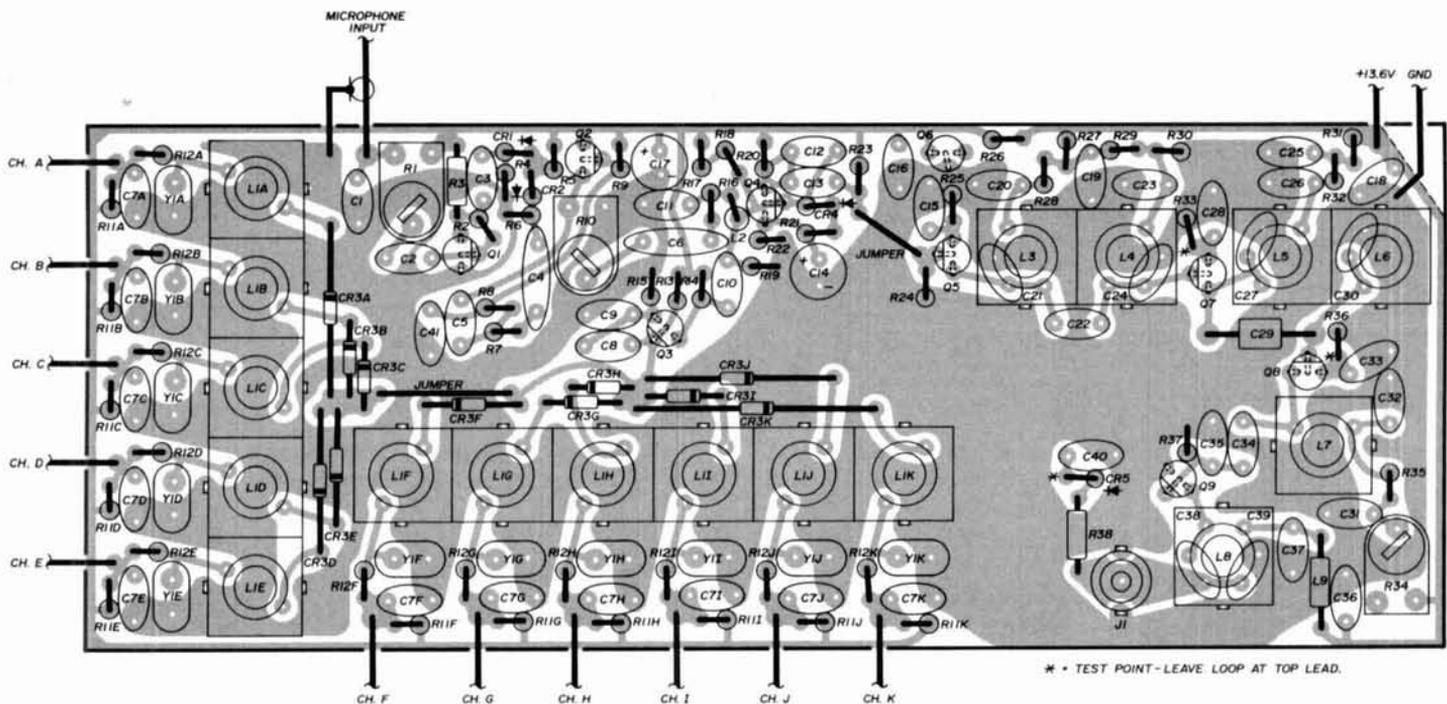


fig. 2. PC-board component layout for the 2-meter fm exciter. Eleven channels are included plus microphone gain and deviation-level controls all on a 3 x 7½ inch (7.6x19cm) printed-circuit board.

that's required externally is a means of connection (a PC board) and low-frequency decoupling components.

Operated at normal 13.6 volts from a battery supply, the PA bricks provide 20 watts of rf at 145 MHz, or 13 watts at 432-450 MHz. (A tripler/driver module kit, model T-20, is available for 450-MHz operation). At this power level, no damage will occur even when operating into a load of infinite vswr. Usually, the bricks can be driven to 25 watts at 2 meters or 15 watts at 450 MHz or higher if loaded properly and operated with sufficient drive and B+ supply. Of course, the greatest feature is that absolutely no tuning is ever required! Current requirement is 2-4 amperes, depending on rf level. Efficiency is 30 to 50 per cent.


No doubt it's more expensive, watt-for-watt, to use an rf power module instead of an amplifier with discrete components. However, considering the difficulties you can have with discrete PAs and the careful tuning and special packaging required, the brick is a bargain and certainly adds a lot of pleasure to homebrewing transmitters.

with the kit. All turns are close spaced. The diagram of fig. 3 is exaggerated for clarity. However, all leads should be pulled tight, no fancy bends are required, and no Q dope is needed. Holes in the base of the form are numbered as shown. Fractions of turns relate to the number of funnels on the form; for example, 2/6 turns beyond a full number (as in L7, fig. 1) means ending two funnels beyond the starting funnel.

Oscillator trimmer coils are wound with no. 26 (0.3mm) wire in two layers, with just over half the turns on the first layer and the remaining turns on the second layer. Wind from bottom to top, going directly back to the bottom and winding up again to the top on the second layer. All other coils are wound in one layer with no. 24 (0.5mm) wire. Coils with capacitors will have capacitor leads inserted through coil-form funnels after the coils are wound. The capacitors should be seated down onto the board as much as possible, as should all parts. This is important at vhf!

Don't be over concerned with coil winding. Neatness isn't important; turns can overlap and windings need not

be uniform. Start coil leads through board holes while the coil form is above the board, then seat the coil into place onto the board. Don't attempt to insert capacitor leads with the coil form tight against board. After coils are installed, apply heat from a very hot soldering iron

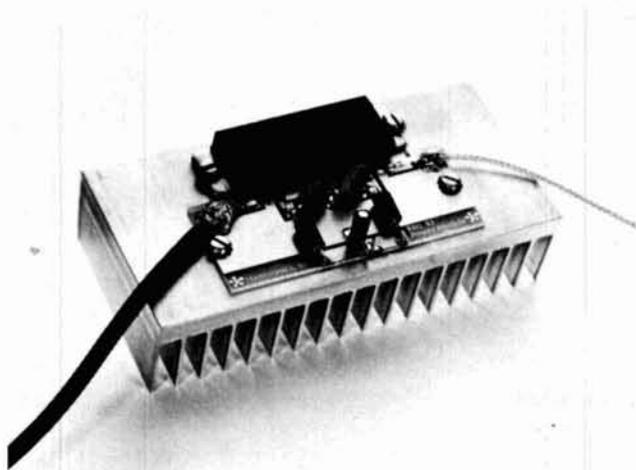

The 2-meter fm exciter married to one of the "instant PAs" for increased power output.

for 10-15 seconds with solder applied. This will automatically strip the wire and allow solder bonding to occur. If you prefer, the leads may be stripped in the conventional way before installation in the board. Don't solder-strip the leads unless the coil is mounted on the board, or the leads will migrate in the warm plastic.

Shield-can tabs should be soldered to the board for proper grounding and mechanical support. It is unnecessary to bend the tabs. Diodes and electrolytic capacitors must be installed with proper polarity. The top leads of R33, R36, and CR5 should be installed with loops accessible for probe connection. The extra length allows the top of the component to serve as a test point. Crystal sockets may be used with the popular HC-25/U type crystal, or crystals may be soldered directly to the board.

External leads should be connected by soldering them into large pads on the PC board. The microphone shield may be easily terminated by wrapping a few turns of bus wire around the shield and soldering. The channel switch should ground the desired channel line for activation. It's sometimes possible to use a common switch for both transmit- and receive-channel selection if the receive switching scheme also uses a ground.

### mounting

The T40 PC board is designed to slide into a vertical groove in a companion cabinet just forward of the rf power module mounted on the rear panel. The components should face forward, and the board should be oriented upward as shown in the component location diagram. The upper right-hand corner may be cut off as

indicated in **fig. 2** to allow cables to be routed past the board in the cabinet. If the companion cabinet is not used, appropriate holes may be drilled in ground areas of the PC board to allow standoff mounting to your own chassis or panel.

### crystals

The exciter uses HC-25/U series-resonant crystals. The crystal frequency, in the 12-MHz region, is determined by dividing the 2-meter channel frequency by 12. When adapted for other bands, the divisor changes accordingly; e.g., 36 for 450 MHz, 18 for 220 MHz, and 4 for 52 MHz.

### alignment

After constructing and visually checking the PC board for proper assembly and soldering, you are ready to apply power and perform alignment and testing. Caution: Use a proper tuning tool; a loosely fitting tool may crack the powdered-iron tuning slugs.

1. Install one crystal at the approximate center of the desired frequency range, and ground the corresponding channel control line.
2. Set the audio controls R1 and R10 to full counter clockwise, and set power control R34 fully clockwise.
3. Preset all tuning slugs to half range.
4. Connect 50-ohm load to output connector J1.
5. Apply 13.6 Vdc (battery power, etc.). *Observe polarity.*
6. Check regulated voltage. It should be approximately +6 to +9 Vdc.
7. Connect vtvm, set to 0.5 Vdc range, to TP1 (loop at top of R33 at first doubler Q7).
8. Peak L3; then peak L4. Dip L5. Dc voltage should be roughly +0.3 to +0.4 volt.
9. Connect vtvm, set to 1.5 Vdc range, to TP2 (top of R36 at second doubler Q8).
10. Peak L6; then peak L5. Dip L7. Dc voltage should be roughly +1 to +2 volts.
11. Connect vtvm, set to 1.5 Vdc range, to TP3 (top of CR5 at final amplifier Q9).
12. Peak L8; then peak L7. Dc voltage should be roughly +1 to +2 volts.
13. Repeat all above steps to eliminate effects of interaction and to check tuning. When you're finished, the dc current drain should be about 70 mA. If you have an accurate rf probe arrangement, the rf voltage at the 50-ohm load should be about 2-3 volts (150-200mW), which is the level required to drive the rf power module. Note that output will be somewhat less if the power supply voltage is below 13.6 Vdc. *Note:* Do not attempt to tune in any manner other than described. In particular, multiplier stages should *not* be re-peaked for maximum at the antenna connector.

14. One, by one, ground each channel control line with crystals installed, and adjust the corresponding oscillator trimmer coil to net each channel to the proper frequency.

### troubleshooting

The usual troubleshooting techniques of checking dc voltages at transistor elements and tracing ac signals, with a voltmeter and an rf probe where applicable, apply in this case. Don't overlook the possibility that parts may be installed incorrectly.

For convenience, the regulated voltage is obtained for the low-level stages by using a 2N4123 as a zener diode (Q6 in fig. 1). Since transistors are not calibrated for this parameter, the zener voltage should be checked the first time the board is fired up to ensure that a zener voltage in the range of 6 to 9 Vdc occurs. If lower, you may wish to substitute another 2N4123 to find one with a useful zener voltage. The exact voltage is unimportant; it is only necessary that the voltage be held stable under varying line conditions.

If trouble is encountered in netting one or more channels, check the number of turns on the corresponding oscillator trimmer coils. Make sure the coil is wound in two layers, as described earlier. If a channel won't oscillate at all, check the corresponding diode and other components in the control-line circuit. The following typical test voltages will serve as a rough guide to proper transistor operation, based on 13.6 Vdc input.

transistor	emitter	base	collector
Q1	0	0.6	2
Q2	2.2	2.9	7*
Q3	3.8	4.4	6*
Q4	2.6	3.2	4.5*
Q5	1.2	1.8	13.4
Q6	7*	0	-----
Q7	0.35†	0.6†	13.4
Q8	1.7†	1.7†	13.6

\*Assumes 7 volts from a regulated supply, but supply ranges between 6-9 V in actual units.

†Rough indication of drive level.

Base and collector voltages of Q9 cannot be measured with drive applied because of rf effects on meter.

### microphone and audio adjustments

The exciter is designed to operate with either a carbon microphone or a transistorized dynamic microphone. The microphone should be connected with shielded cable to avoid rf pickup. To adjust deviation level, preset R1 and R10 both fully clockwise. Key the exciter, and make sure that the carrier is adjusted properly to frequency. Speak into the microphone and observe the deviation meter on the receiver, or listen to the audio with the squelch set tight. Reduce deviation control R10 setting until all noticeable effects of over-deviation are removed; e.g., distortion, meter swing on peaks, squelch pumping.

The setting of microphone gain control R1 is a refine-

ment not found on most transmitters. It should be set to provide sufficient audio for full modulation on voice peaks but low enough to remove background noise and obvious clipping effects, which normally result from overdriving a clipper.

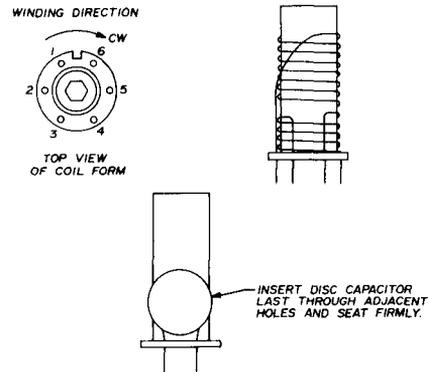


fig. 3 Diagram for winding coils (exaggerated for clarity). The number of turns for all coils is shown in the schematic. All turns are close spaced; winding direction is extremely important.

Since the amount of deviation depends on the frequency band to which the exciter signal is multiplied, resistor R16 is provided to allow the amount of deviation at full control setting to be altered. The value of R16 may be reduced to obtain wider deviation if required, and it may be increased to reduce the range of the deviation control. (R16 is also a part of the lowpass filter following the limiter).

The following kits and accessories are being made available in conjunction with this article.

part number	description	price
T40	Two-meter fm exciter module kit	\$39.95
T80-150	Two-meter rf power module PA	\$79.95
T80-450	432-450 MHz rf power module PA	\$79.95

#### note

Rf power module PAs are wired and tested and are complete with heat sink. No construction or tuning is required, ever.

T20	Two-meter to 450 MHz tripler/driver module kit	\$19.95
A25	Cyclac cabinet, 7 x 7 1/4 x 3 1/2 inches (17.8x19.7x8.9cm) with aluminum panels, to house exciter, rf power module PA, and other modules	\$24.95
	Crystals for any desired channel frequencies	\$ 5.50

When ordering, please add \$1.00 for UPS or parcel post shipping. New York State residents, please add 4% sales tax. Other kits offered include fm receivers, converters, preamps, scanner and multifrequency adapters. Send a self-addressed, stamped envelope for a complete catalog to Hamtronics, Inc., 182 Belmont Road, Rochester, New York 14612.

### reference

1. G. Francis Vogt, WA2GCF, "High Performance VHF FM Receiver," *ham radio*, November, 1975, page 8.

ham radio

# update of the phase-locked loop RTTY demodulator

Here are the answers  
to your questions  
about this terminal unit  
plus a modified circuit  
for upward shift

Since the NS-1 phase-locked loop RTTY demodulator first appeared in the *RTTY Journal*, October, 1974, and later in *ham radio*,<sup>1</sup> I have received numerous inquiries about its operation. I hope this article will answer some of the questions and also provide some added tips.

First, as an explanation, the NS-1 was developed primarily for fsk downward shift on the high-frequency bands, using low tones to take advantage of a narrow receiver passband. The 741 op-amp limiter drops off around 2000 Hz, so the tones must be within this limit. On fsk the tones can be varied by receiver tuning, so it's easy to obtain these low tones. Shift reversal is accomplished by changing sidebands if receiving in the ssb mode or by moving the bfo to the other side of zero beat if receiving in the CW mode.


## meter adjustment

I suppose the most-often asked question concerned the value of the zero-center, meter-adjustment pot. This

value depends on the meter movement; i.e., whether it's 50  $\mu$ A, 200  $\mu$ A, 1 mA, etc. The easiest way to determine this value is to put a 500k pot in series with the meter and gradually reduce the resistance until full scale (+) is obtained on the mark/hold signal. This resistance can then be measured and a fixed resistor substituted.

If you don't have a zero-center meter, fig. 1 shows such a circuit using a regular 0-1 mA meter. Before connecting the 18k resistor to the *M* terminal, set the 25k pot about midway, ground the 18k resistor to the chassis, and adjust the pot until the meter reads center scale (0.5mA). Now, when the 18k resistor is connected to

fig. 1. Using a 0-1 mA meter for zero-center indication. Connected as shown, the meter will indicate plus to the right and minus to the left. See text for adjustment instructions.

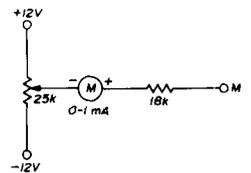

the *M* terminal, the meter will act like a zero-center meter with plus to the right and minus to the left.

## cross pattern

Several readers asked where to connect a scope to receive a cross pattern. A scope cross pattern requires tuned filters to distinguish between the mark and space tones, one displayed vertically and the other horizontally. Since the NS-1 has no filters, there is no place to connect the scope. However, if you have a scope with tuned filters that will produce a cross pattern, connect the scope ahead of the NS-1 or at the receiver output. Tune in a signal that gives a good cross pattern, then adjust R1, the 5k vco pot, until you get good copy. Thereafter you can use the cross pattern for tuning.

Some readers complained that they were unable to

By Nat Stinnette, W4AYV, P.O. Box 1043, Tavares, Florida 32778

get wide-shift copy. The usual 2125/2975 Hz tones will not work, as the 741 limiter will not accept frequencies much above 2000 Hz, as stated previously. So tones, say, around 2125/1275 Hz should be used. A compromise setting of R1 can be found that will permit copy of both wide and narrow shifts.

### other tips

The purpose of the switch is to put the teletype machine in a "hold" condition. Random noise and signals will produce garble when tuning. Also the switch

changes were tried including reversal of the two inputs to the 741. This change worked, but best results were obtained after installing a transistor just ahead of the 2N5655. A 2N706 was used. It switches the keying transistor off and on and has the effect of reversing the voltage from the 741 output, which permits smooth upward-shift copy.

The 741 limiter was eliminated since it is restricted to around 2000 Hz; thus high tones such as 2125/2975 Hz can be used. Two reversed diodes were placed ahead of the 565 PLL. These give good limiting and prevent PLL

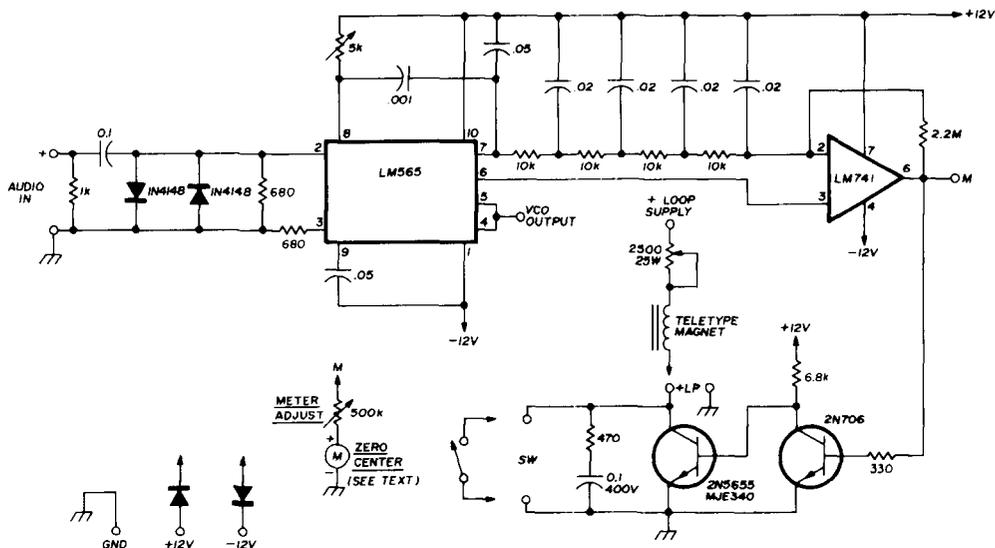


fig. 2. Schematic of the NS-1A phase-locked loop demodulator for copying afsk/fsk (upward shift). The 2N706 switches the 2N5655 on and off, which reverses the polarity of the voltage from the LM741 comparator on mark/hold. This permits smooth upward-shift copy.

should be closed when transmitting, as interaction between the receiver and TU will also produce garble.

Remember that the NS-1 will act very much like any other fm demodulator. If a stronger signal is near the one you're trying to copy, the stronger signal will take over. I've found that a receiver T-notch filter is quite effective at times. Also, use the narrowest selectivity you have on your receiver that will permit copy of the tones; this reduces the effects of interference. One amateur wrote that he installed an active audio filter (2100-2300 Hz) ahead of the NS-1 and adjusted the unit for 2295/2125 Hz. He said this arrangement compared very favorably with the ST-type terminal units.

### modified unit for upward shift

A few people have tried to use the NS-1 on afsk on the six- and two-meter bands and found it would not work. This is because afsk is usually upward shift (mark low, space high), and the NS-1 will not copy this way. Afsk tones are fixed. Nothing can be done at the receiving end to reverse the shift, and there are no provisions for it on the TU.

To achieve copy with upward shift, it's necessary to reverse the polarity of the voltage coming out of the 741 comparator on the mark/hold signal. Several circuit

overload. The 565 is very sensitive, so no amplifier is needed. This modified arrangement works equally well on afsk and fsk, wide or narrow shift. The revised circuit diagram is shown in fig. 2 and has been designated the NS-1A.\* The same adjustment procedure as used on the NS-1 should be used for the NS-1A. The zero-center tuning meter will now show full scale minus (left) reading on the mark/hold signal. The tuning meter may not even be needed on afsk.

### acknowledgements

I wish to thank Ron, W8BBB; Buck, WAØLEM; and Rick, WB5FHU for their tests and evaluation of the NS-1A on afsk. The added feature of afsk copy should encourage more activity on two- and six-meter RTTY with this simple terminal unit.

\*At present no modified boards are available; however, wired and tested NS-1A units are available for \$29.95 postpaid; the circuit board is \$4.75 postpaid. For more information, contact the author.

### reference

1. Nat Stinnette, W4AYV, "Phase-Locked Loop RTTY Terminal Unit," *ham radio*, February, 1975, page 36.

ham radio

# the hand-held electronic calculator: its function and use

First of a  
four-part series  
on how to apply  
the simple  
four-function machine  
to math problems  
encountered in radio work

This is the first of four articles on the hand-held electronic calculator — how it works and how it can work for you to solve even the most complex problems encountered in radio work. The operating principles of the four-function machine are discussed first, with examples illustrating how the basic arithmetic functions are performed in response to input-key manipulations. Discussed next are some of the more important operations that can be performed with larger and more expensive machines: chain operation, the use of constants, and the use of various memories. Finally, some suggestions are given to help you choose the best machine to fit your needs.

In the second article, which will be published in the next issue of *ham radio*, the power of the simple four-function calculator is expanded for solving problems in radio work. Examples are given on using approximations as substitutes for special calculator functions, the use of problem-organization technique to overcome the limitations of simple machines, and the use of the "scratch pad" as a substitute for calculator memory. Examples are given on using the simple four-function machine to solve problems involving transcendental functions and numerical integration. The following articles will cover transmission-line calculations and use of the new programmable calculators.

These articles should help dispel the mystery of how to use the four-function electronic calculator in solving electronics problems by providing basic information on the logic of operations within the machine and providing the approximations and tools available.

## basic calculator principles

**Addition.** In digital electronics, a *register* is a place to store numbers. Actually, these don't have to be electronic devices; a chain of relays, a toothed wheel, or even knots in a piece of string can serve as a register. But in the small calculator registers are always electronic and are almost always made using field-effect transistors.

To be useful there must be a way of putting numbers into the register, of taking them out, and, for at least some registers, of telling what number is stored. Hand-held calculators have standardized on a set of push-buttons or *keys* for *input*, and a stylized *display* for presenting the content or number stored.

Suppose we wish to perform the simple arithmetic operation of addition. We could use three registers, one for the *addend*, or first number, a second for the *augend*, or second number, and a third for the result, or *sum*. Actually it's easier to do this with only two registers by a technique called "add to storage." In this, the addend, when received, is first placed in the sum register, then the augend is added to it to get the final sum. The two

By R.P. Haviland, W4MB, 2100 South Nova Road, Box 45, Daytona Beach, Florida 32019

registers involved can be called the keyboard register and the answer register.

To make a small calculator, we need the two registers, the keyboard, and the display. We also need some control circuitry to tell the register how to work. For convenience, the control can also be arranged to switch the display from the keyboard to the answer register. In block diagram form, these elements are shown in fig. 1.

We can see these registers in operation on any calculator by considering only the ten number input keys 0 through 9, and the *add* key. This key is usually marked  $+/=$  in small calculators, but may be marked  $+$ . When the calculator is first turned on, a 0 will appear at the extreme right of the display (a decimal point may appear also, but ignore this for now). Suppose we wish the addend to be the number 123. Pressing the 1 key causes the 0 to change to a 1. Pressing the 2 key causes the 1 to jump, or shift, to the second position from the right and a 2 to appear at the rightmost position. Similarly, pressing the 3 key causes the numbers displayed to shift again, the display now reading 123. We have now entered the desired number, 123.

To transfer this number to the answer register, we now press the add key ( $+/=$  or  $+$ ). All that seems to happen is a blink of the display, but the display is now presenting the number in the answer register. We can show this as follows. Press the 0 key, which causes the display to change to a zero. Now press the add key again: the display changes to 123, the number stored in the answer register. This display will continue to show the number in the answer register until another operation is started.

In this test we are actually performing an addition,  $123 + 0 = 123$ . We can continue addition by entering another number then pressing the add key. Each time, the display switches to the keyboard register then back to the answer register as the add key is pressed. The answer register always shows the sum of all numbers entered.

When pressing the number keys it's possible to make a mistake, say by pressing 132 instead of the desired 123. This is easily seen, since the display shows the number actually entered; this is the reason for switching the display back and forth.

To correct a mistake in entry, it's necessary to wipe out the entire number entered, or *clear* the keyboard register, and start over. On most small calculators this is done by pressing a special control key marked *CE* for *Clear Entry*. In this example, pressing *CE* causes the display (and the keyboard register) to change from 132 to 0. The correct number is then entered.

Let's leave addition and go on to other operations. To get ready for these, the number stored in the answer register must be removed lest it make an error in the next calculation. To do this, another control key is pressed, marked *C* for *Clear*, which sets the internal register to zero. The same result could be obtained by switching off the calculator; the internal circuits in most calculators are arranged to clear the registers when the power is first switched on.

In some calculators *Clear Entry* and *Clear* are combined into a single key, usually marked *C* or *CLR*. Pressing this key once clears the entry, and pressing it twice in succession clears all registers.

**Subtraction.** As far as the user is concerned, the operation of subtraction is almost identical to that of addition, the one difference being that a different operation key, marked  $-$  or  $-/=$  is used. Suppose we wish to subtract 456 from 123. The number 123 is first entered into the keyboard register then transferred to the answer register by pressing the  $+$  key. The number 456 is entered into the keyboard register then transferred to the answer register with the proper sign by pressing  $=$  (equals). The answer,  $-333$  appears immediately. In some calculators the minus sign appears next to the left number; in others it's at the extreme left. The number is called a "*signed number*" to indicate that the sign relates to the number rather than to the operation (subtract).

When working with signed numbers the order of entering the numbers isn't important providing the signs associated with the numbers are entered properly. For example,  $123 - 456$  may be handled as follows:

enter	press	display
	C	0
	+	0
123	-	123
456	=	-333

Alternatively, the operation may be:

enter	press	display
	C	0
	-	0
456	+	-456
123	=	-333

**Multiplication.** Recall that multiplication is just a method of successive addition. Suppose we wish to multiply 456 by 123. The answer is equal to  $456 + 456 + 456$ , plus  $4560 + 4560$  plus  $45600$ . This can be confirmed by making the addition, the sum being 56088.

To solve this problem in a calculator, the internal controls cause the multiplicand to be added to itself three times, and the result is stored in the answer register. The multiplicand is then multiplied by 10, and this value is added to the answer register twice. Finally, the multiplicand is again multiplied by ten, and this value is added to the answer register to get the result, 56088. This process requires a place to store the multiplicand, a third register, as shown in block form in fig. 2. In most small calculators the contents of this register can't be displayed so it's often called a *hidden register*.

To the user the operations for multiplication are not much different than for addition. The first number, the *multiplicand* is first entered, followed by  $\times$ . This operation stores the number in the hidden register. The second number, the *multiplier*, is then entered. Pressing the  $=$  or  $+/=$  key gives the answer, the *product*.

In very small calculators, it's not possible to multiply

negative numbers directly. The easiest way to handle this is to remember that, from algebra, the product is positive if *both multiplier and multiplicand have the same sign*; if not, the product is negative.

**Overflow.** Recall that the number of digits in the product is either equal to the sum of digits of the multiplier and multiplicand, or is one less than the sum. When two large numbers are multiplied, the product may have more digits than the register (and display) capacity. This condition is called *overflow*. It can also occur in addition, since the number of digits in the sum can be one greater than the largest number of digits of the two numbers being added.

Most calculators have some form of indication of overflow. It may be a special symbol at the left of the display, a glowing dot, or a blink. Some small calculators eliminate the need for this by making the answer register twice the size of the keyboard register: pressing a special key marked with a right-pointing arrow causes the additional digits to be displayed. Also overflow can be avoided by a technique called *multiple precision*, described in the next article.

**Division: underflow.** Just as the calculator handles multiplication by successive addition, it handles division by successive subtraction. For example, to divide 56088 by 123, the calculator first subtracts 123 from the left 3 digits, 560, leaving 437. This is a positive number, so 123 is subtracted again, to get 314, then again to get 191, and still again to get 68. Another subtraction of 123 causes the sign to change to minus, producing a reading of -55, a signal that subtraction has proceeded too far. Accordingly, 123 is added, to get 68 again. This number is shifted one position to the left, bringing in the next digit, for an internal reading of 688. The net number of subtractions, 4, is recorded as the first digit of the *quotient*. The process of subtract, test, adjust when necessary, then shift continues until the answer is obtained, 456 in this case.

Suppose we wish to divide a very small number by a larger one, say, 3 divided by 987654. On the small calculators the number appearing as an answer is a zero. This answer is obviously wrong, since the actual answer must be greater than zero. This condition is called *underflow*. It is handled in one of several ways, depending on calculator design. In some, an underflow signal is presented; in others, a special conversion may be used as described below.

**Decimals and calculator notation.** So far we have ignored the decimal point and have looked at whole number problems. A few types of calculators do the same thing. It's up to the user to keep track of the decimal. This is not difficult if three simple rules are remembered:

1. In addition and subtraction, zeros must be added to the right as needed to make the number of places to the right of the decimal the same for all numbers. Example:  $7.6 + 0.25$  must be entered as  $760 + 25$ . The indicated answer, 785, is read as 7.85.

2. In multiplication, the number of places to the right of the decimal in the product is equal to the sum of the number of places of the multiplier and multiplicand.

3. In division, a simple method is to use zeros to give the same number of places in divisor and dividend. The answer displayed is the part of the quotient to the right of the decimal point. On most no-decimal calculators, the decimal part of the quotient can then be displayed by pressing a key marked  $\rightarrow$ .

By far the largest number of calculators on the market have decimal provision, indicated by a key labeled with a decimal dot. There are, however, several ways of handling the decimal. Some calculators allow entry of the decimal point at any place up to a limit — often 2, 4, or 5 places. The answer is given to the same number of places (fixed decimal).

Some assume that the number to be entered has two decimal places, as in dollars and cents. Answers show two places (adding machine entry).

Some allow the decimal to occur at any place on the display for both entry and answer. The answer display starts with the first digit, or with a decimal, as necessary (floating decimal).

Some express the answer as a number multiplied by a power of ten, such as  $1.2345 \times 10^{-3}$  (scientific notation).

Some restrict the power of ten to  $10^0$ ,  $10^3$ ,  $10^6$  (engineering notation).

In complex machines, there may be manual or automatic change from one notation to the other. The method of handling the decimal is very important, and time should be spent with the instructions and in practice until the mode of operation is thoroughly understood.

## simple and extended calculators

So far we've looked at the elements basic to all calculators. As seen with respect to the keyboard, these are:

numericals: 0 to 9, and . (decimal point)  
operations: +, -,  $\times$ ,  $\div$ , =  
instructions: C, CE

Depending on the design, these can be placed on 15 to 17 keys, 16 being the most common. In simple calculators only these keys are found. There are however, a number of other instructions and operations that can be added and which will be found in various combinations in the larger and more expensive machines.

**Chain calculations.** In the simplest calculator the number in the answer register is available only to the display. As a result, this register must be cleared at the end of each calculation before starting another to prevent error.

More advanced calculators, by internal switching, make this number available to the keyboard or to the hidden register, to serve as the input for a new series of calculations. This technique is called *chain*, since it allows linking or chaining of successive operations.

Where this method of construction really pays off is in mixed calculations. For example, the problem  $\frac{2 \times 3}{4} + 6$  is solved by the successive entries of 2, x, 3, ÷, 4, +=, 6, +=, (calculators with no separate = key), for an answer of 7.5. Without chain, the entries would be 2, x, 3, +=, C, 6, ÷, 4, +=, C, 1.5, +, 6, += again for an answer of 7.5 but with the necessity of remembering the result of each step long enough to input it for the next step.

There are some things to be aware of with chain operation. For example if you wish to solve  $2^3 = 8$  and you press the keys 2, x, x, x the display will show 16. In the multiply, divide, and add operation above, omission of the intermediate equal sign gives the erroneous result of 6 instead of 7.5. More important, the order of operations must be correct. In most simple calculators, multiply/divide can be mixed in any order as can add/subtract; but multiply/divide must precede add/subtract in a chain.

**Percent.** Many small calculators have a key marked with the symbol for percent, %. This is used exactly like the = key to obtain an answer, but it has the effect of shifting the decimal point two places to the right on divide and two places to the left on multiply. For example, 2, ÷, 3, % gives 66.6666, and 2, x, 3, % gives 0.06. On divide, the result answers the question, "What percent of the second number is the first?" and on multiply, the question, "What is the second number percentage of the first number?"

**Values of constants.** When a register is cleared, it is actually set to contain zeros. It is no great problem to design it to be set to some other number.

In the small calculator, such "set to a value" capability is rarely provided. Even the larger ones include only a single value, that of  $\pi$ , or 3.141592654. An exception is the family of special calculators designed for metric conversion. In these, the multiplying factors for feet to meters, pounds to kilograms, etc., are built in and come into play as the appropriately marked key is pressed.

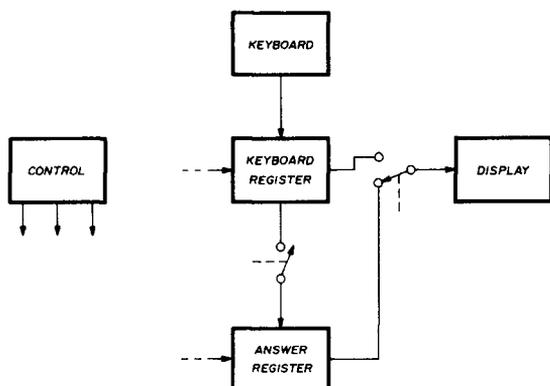


fig. 1. Elements of the basic hand-held electronic calculator. The registers store information input from the keyboard, and the display provides a readout of calculation results based on instructions to the registers from the control circuits.

**Change sign.** In many small calculators, operations such as division by a negative number are not directly possible, since the - is an instruction to subtract. However, some avoid the problem by providing a special key, usually marked +/-, i.e., *change sign*. This operates only on the keyboard register, causing its sign to change + to - or - to +.

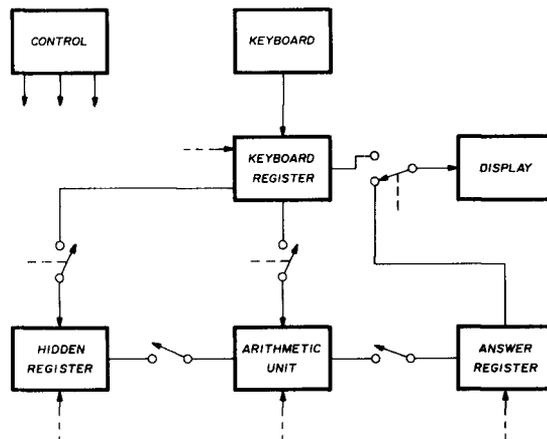


fig. 2. Calculator with add, subtract, divide, and multiply functions. A third register is used to store the multiplicand during problems involving multiplication. Its contents can't be displayed, hence the name "hidden register."

**Exchange.** In fig. 2, the number in the third, or hidden, register can't be seen; it can't be checked; nor is it available except for specifically intended operations. To increase flexibility, a key may be provided that causes the contents of the keyboard and hidden registers to be exchanged. Usually the key is marked *EX*; i.e., *exchange*. Pressing the key once allows the contents of the hidden register to be examined; a second action returns the contents to the initial condition. Alternatively, after the first actuation, an operation can be performed, say, addition.

**Memory 1: constant.** One function of the registers shown in figs. 1 and 2 is to remember the numbers placed in them. It seems obvious that calculators would be more flexible in use and would have more calculating power if more memory capability were provided, just as the calculator of fig. 2 has more capability than the simpler unit of fig. 1. In practice this is true.

The simplest type of added memory is called *constant*. When provided, it is usually made evident by a slide switch, one position being marked *K*. When this key is depressed, a number can be loaded into this memory by pressing an arithmetic operation key. Thereafter, entering another number followed by = causes the operation to be performed between two numbers. For example, suppose *constant* is on, and has been loaded by pressing 3.14159, x. Pressing 120, =, gives the answer, 376.9908, or  $120\pi$ . Now pressing 2, = gives 6.28318. The constant is retained until replaced by keying a number and some operation other than =.

Quite a range of variation is possible in the method of operation. Some calculators require two numbers to be loaded and place the second in the constant memory. In others, the constant memory holds the first entry. Another variation is *automatic constant*, which seems to be coupled with the chain. It operates the same as the switchable constant described above but is always available without switching. In other variations, *constant* can be used with multiply and divide but not with add and subtract. However, despite its exact form, this simple form of memory adds greatly to the calculator power.

**Memory 2: four-function memory.** A further increase in calculation power can be secured by making the memory more flexible so that it can be loaded or recalled at any point in the calculation cycle. Typically, this is done by providing four keys, *+M*, *-M*, *RM*, *CM*, indicating: add number displayed to the number in memory, subtract number displayed from the number in memory, read memory (transfer number in memory to the keyboard register, leaving the number in memory intact), and clear memory (set the memory number to zero). Some calculators include a flag to show when memory is loaded. Some may omit one or more keys, usually the *-M* key.

The major use of this form of memory is to store intermediate results while making a continuing calculation. For example, to solve  $(A \cdot B) - (Y \cdot Z)$ , the key strokes are *A*, *x*, *B*, *=*, *+M*, *Y*, *x*, *Z*, *=*, *-M*, *RM*. Another use is storage for constants, such as  $\pi$ , or the rate of sales tax, for example.

**Memory 3: stacks.** As problems become more complex, it is found that several numbers must be "remembered" at the same time. One way of accomplishing this is to provide several memory registers arranged so that each successive call for memory input causes a number already in memory to be displaced into another register. These registers are said to form a *stack*.

Stack memory appears in two forms. One is based on conventional algebraic notation and usually appears on the keyboard as a pair of keys marked [ ( and ) ], standing for inner and outer parentheses. Successive keying of the left parenthesis causes the stack shift. The other stack arrangement is based on a special notation called Polish reverse notation (no one can pronounce the mathematician's name!).\* The two keys for this are usually marked *ENTER*↑, and *RCL* for recall. A key marked *R*↓ for *roll* may be provided to allow reading the memories successively. This type has no equals key; the notation arrangement makes it unnecessary. Readout of both of these memories is automatic, occurring as the logic of the problem demands.

**Memory 4: addressable memory: programs.** As the amount of memory provided is increased, the stack arrangement becomes too limiting. To avoid this problem each memory can be assigned to a symbol, so a number can be placed into any memory cell, or the number in any cell can be read out without calculation. This arrangement is called *addressable memory*.

\*The Polish logician, Jan Lukasiewicz.

Addressable memory may be found combined with a special memory, one which remembers the successive steps needed to solve a problem. The assembly of steps is called a *program*. In some calculators the program is stored internally and is lost when the power is shut off. Other calculators store the program on a card, usually similar to magnetic tape. The power of these addressable memory and programmable calculators approaches the capability of computers.

**Functions.** A function of a quantity bears a definable relationship to the quantity. If  $X$  represents the quantity, the quantity  $Y = X \cdot X$  or  $Y = X^2$  is a function of  $X$ .

Small calculators have no built-in provisions for these specific functions. Slightly larger ones may provide  $X^2$ ,  $\sqrt{X}$  and  $1/X$ , by special keys. Still more powerful ones may provide  $\sin X$ ,  $\cos X$ ,  $\sin^{-1} X$ ,  $e^x$ ,  $X^y$ , etc. These additional functions are generated by special circuits in the control section of the calculator. They are calculated each time they are needed, using the number present in the keyboard register. Usually the calculation takes a noticeable time period, during which the display is blank, or flashing.

The next article in this series describes methods of approximating these functions on the smaller calculators.

### which calculator?

Which calculator to buy should be based on expected use, problems to be solved, and cost. A simple calculator is best for simple problems; there is much less chance of error. If more complex problems are to be solved or much repetition is involved, the calculator power should be increased accordingly. However, if complex problems are encountered only at rare intervals, it's best to stay with the simpler calculators, using scratch pads and function tables as substitutes for calculator power (discussed in the next article). Not only is the cost lower, but the time wasted is less — it's easy to forget the tricks of the larger calculators.

The four-function, 16-key calculator with constant is about the simplest usable machine for routine radio calculations. The type with four-function memory (usually 20 keys) is appreciably better. Of course, the regular user should consider the advanced calculator. Regardless of the type used, practice is in order. A good technique for refreshing your memory of problems, and at the same time becoming acquainted with the calculator, is to solve the example problems in *The Radio Amateurs Handbook*, or *The Radio Handbook*. In running these problems, it's a good idea to practice approximate mental solution at the same time — the best way to avoid error.

### bibliography

1. Don Lancaster, "Understanding Calculator ICs," *Radio Electronics*, April, 1974, page 38.
2. J.M. Smith, *Scientific Analysis of the Pocket Calculator*, John Wiley & Sons, New York, 1975.
3. Henry Mullish, *How to Get the Most Out of Your Pocket Calculator*, P.F. Collier, New York, 1974.

ham radio

# Call 1-800-633-3410 for Kenwood\*

(\*Plus Drake, HyGain, CDE, Newtronics, Spec Comm, Rohn and Tristao)



## The Kenwood TS-820 transceiver

The TS-820 covers 10 thru 160 meters - has 200 watts P.E.P. - Integral IF shift - RF speech processor - Digital readout DG-1 (optional, 170.00) - Complete solid state, except driver and final stages - Heater switch - VOX circuit - Noise blanker - PLL circuitry - Full metering - DRS dial - Built in 25 kHz calibrator - CW sidetone and semi-break in - Rear panel terminals for linear amplifier, IF OUT, RTTY, and XVTR. Phone patch IN and OUT terminals - Options: VFO-820, DS-1A, DC-DC converter, TV-502 2 meter transverter .....list price **830.00**

## The Kenwood TS-700A transceiver

The TS-700A is an all-mode, solid-state transceiver - Frequency range: 144 to 148 MHz - Repeater activation - Built-in SSB, FM, AM, and CW - High stability FET VFO - 11 fixed channels (crystals optional) - 44 channels with 11 crystals, heterodyne switching circuitry - AC/DC operation, built-in - Dual tuning with band spread - Noise blanker - Amplified-type AGC circuit - S-meter, RIT - Built-in marker oscillator - Squelch circuit - VOX operation (optional) - Fully equipped RF circuitry with dual gate-type 3SK35 MOS FET .....list price **700.00**

## More exceptional ham radio values...

**Kenwood TS-7200A 2 meter transceiver** - 10 watt output - 22 channels, - 6 supplied: 94/94/, 34/94, 52/52, 16/76, 22/82, 28/88 - Complete w/mic., slide-out bracket - PS5 power supply (optional) .....list price **249.00**

**Kenwood TS-2200A portable 2 meter Fm transceiver** - Solid-state - High ZW and low 0.4W out put - 12 fixed channels (6 supplied) - ¼ wave telescoping antenna - rechargeable Ni-Cd batteries - lighted channel indicators .....list price **229.00**

**Kenwood TS-520 SSB transceiver** - covers 10 thru 180 meters - Solid-state thru out except for final and drive stages - FET VFO - WWV - Amplified-type AGC - VOX/PTT/MOX circuit - Dual gate MOS FET 3SK35 .....list price **629.00**

## A word from Jim...

I'm sure it does not impress you to see a hundred different manufacturers trademarks listed beside our name and nothing in stock. At Long's Electronics we try to stock all of the items in the product lines we carry. So, call us toll-free **1-800-633-3410**, and see if we can help you. We also service what we sell.

Sincerely,  
Jim Long W4ZRZ

## Call toll-free

**1-800-633-3410** for  
Long's Electronics price on any ham item

# Long's Electronics

3521 10th Avenue North, Birmingham, Alabama 35234

# syllabic vox system for Drake equipment

Elimination of  
conventional vox delays  
is featured in  
this novel system  
adapted to the popular  
Drake T-4XB and R-4B

Radiotelephone conversations without speech delays caused by conventional vox systems is truly a delightful experience. The system described here has been designed for the Drake T-4XB and R-4B transmitter and receiver. It eliminates poor speech habits induced by vox relay delay and also eliminates vox relay contact-bounce transients. In addition, true break-in CW keying is possible with this system.

Dr. Hildreth, WØIP, described his system for instantaneous voice interruption (IVI) in *QST*.<sup>1</sup> While IVI clearly demonstrated the feasibility of rapid-switching syllabic voice response in the control of rf transmission, I experienced difficulties when trying to use conventional vox with IVI.

## conventional vox systems

Vox, anti-vox, and delay circuits in most popular transmitters are similar in design principles. Therefore, these techniques might be called "conventional vox." Conventional vox depends on passive integrals developed from the audio signal by rectified dc charges to a control capacitor. Output from the capacitor appears at the grid of a relay-switching tube; or, in solid-state circuits, as current to the base of a relay switching transistor. When a positive charge provides vox activation during transmis-

sion, anti-vox during reception requires a negative charge to inhibit operation of the vox relay.

A significant period of time is required for both vox and anti-vox functions because the control capacitor can't be charged or discharged instantaneously. Time, dependent on source and load resistance, together with the value of the control capacitor, is extended accordingly. Likewise, time is equally important to the anti-vox input, which requires similar processing of opposite polarity. A delay of many milliseconds, or even seconds, may be involved, which varies with the amplitudes of vox input and anti-vox receiver output. Usually, these functions are mutually dependent. Such factors contribute to annoying and compromised operating adjustments, often leading to abandonment of vox in favor of PTT.

In the use of conventional vox systems, the operating-point bias to the final amplifier tubes is active throughout the vox relay *on* time. This, of course, means that final-amplifier bias current is present between speech syllables, words, and code elements. Power used in this manner, without rf transmission, is wasted. Also, a T-R switch loses merit, because final-amplifier tube noise appears at the switch and receiver input.

Both these undesirable conditions are eliminated by the syllabic vox method. Final-amplifier operational bias is applied only during rf transmission. At all other times, the final amplifier tubes are cut off completely and no plate current flows. Significant improvement in transmission efficiency results.

## adaptation to Drake equipment

Using this system with the Drake R-4B and T-4XB requires no hole drilling or component changes. The only outboard unit required is a small circuit board containing the 5-volt power supply, which is mounted in the Drake MS-4 speaker cabinet. During operation, all controls and transmission modes are in accordance with the Drake instruction manual.

All components except the T-R switch and power supply are mounted on a 3.5 by 4.75-inch (89 by 121 mm) Vector board. The components are self supporting on the board and no heatsinks are required. The circuit board is mounted in the upper right-hand corner of the T-4XB transmitter, where adequate space is available without crowding. Two small L-brackets secure the board to the chassis. Existing chassis screws secure the board. No critical or difficult wiring problems were encountered. Total component cost is about \$50.00.

By R.W. Hitchcock, W6RM, 667 West Arrow Highway, Upland, California 91786

Referring to **fig. 1**, all logic components are in the 7400-series ICs, U2, U3, and U4. The retriggerable monostable, U3, is the most important single component in this circuit. With the RC values shown, a single positive pulse at U3A pin 3 would deliver a *low* output at U3A pin 6 for 8.4 milliseconds, plus or minus the tolerance of the RC combination. However, the device offers retriggering capability at all audio frequencies between 120 and 4000 Hz in this application, which means that pin 6 of U3A or U3C will remain low during voice syllables. Upon cessation of voice signals, U3A-6 or U3C-6 will go high after 8.4 milliseconds, which is the time required for one CW dot at 140 wpm. Obviously, this cutoff time is insignificant with respect to voice syllable duration.

U1, an LM3900 quad operation amplifier, was chosen for front-end application to both vox and anti-vox channels. In each case, the first stage offers negligible loading to a high-impedance source and delivers approximately unity gain throughout the range of the source. The second stage produces the required signal gain and stabilization. Use of this amplifier group assures circuit reproducibility with no concern for the varying parameters of discrete devices.

Output from each two-stage amplifier is introduced directly to Schmitt triggers U2A and U2B for square-wave shaping necessary to following logic. The Schmitt triggers have hysteresis values of nearly one volt between upper and lower trigger points. This characteristic is quite important to noise immunity when setting vox and anti-vox gain during operation. Signal inversion occurs in the vox amplifier channel, but no inversion is present in the anti-vox amplifier.

These conditions are essential to the positive CW start pulse and the negative CW stop pulse but they have no influence on radiotelephone transmission. In this way, activation and inhibition of CW vox occurs at the start and stop points of all code elements. Thus true break-in follows with only the inherent delay of the receiver mute circuit.

One section of the 7400 NAND gate, U4, provides a low at either U4A pin 1 or U4A pin 2, which will deliver a high at U4A pin 3. This condition is essential to the solid transmission *on* requirement for *tune*, and *PTT*, while retaining the syllabic voice response capability of normal vox transmission.

U4A drives U4B, an inverter, which activates Q1 into the open-collector cutoff condition during transmission and into saturation during reception. Under the open-collector transmission mode, 50 mA flows through CR5 and the 2.5 mH rf choke in the T-R switch. This action places the node at the junction of C11, CR5, C12, and the rfc at virtual ground during transmission. In the receiving mode, this nodal point offers no loading to the received signal other than the desired receiver input. Diodes CR4, CR6, and CR7 are protective devices in the event forward bias fails.

Output of CR9 from Q1 also drives the base input of Q4 to saturation during transmission. This condition allows Q5 to operate in the open-collector mode and permits full muting to the receiver through the mute

line. While receiving, Q4 is cut off. Now, current flows through the 430-ohm collector resistor and CR15 to saturate Q5. The mute line is brought to ground in this manner for normal reception by the R-4B.

Transistor Q4 also drives Q6, which is emitter-biased to +1.5 volts by CR17 and CR18. When Q4 is saturated during transmission, Q6's base goes negative with respect to the emitter and saturates. When saturated, the collector potential of Q6 is approximately +1.5 V with respect to the collector of Q7. This action results in saturation of Q7, which removes cutoff bias to a kW power amplifier, if one is used.

Returning to the output, U4A pin 3, this point also triggers U3B pin 3. The output at U3B pin 6 now goes low for a constant period of 100 microseconds. With U3B pin 6 low, U4D pin 13 is held low and U4D pin 11 remains high during the 100-microsecond delay. The high at U4D pin 11 holds Q2 at saturation with a collector potential approaching ground. This condition holds cathode switch Q8 at cutoff for the delay period. The 100-microsecond delay for the T-4XB final amplifier is not significant, operationally. However, it provides full assurance that the T-4XB rf output cannot appear at the T-R switch until 100 microseconds *after* the T-R switch, mute line, and kW final-amplifier bias have been activated for transmission.

Both U4D pin 12 and U4D pin 13 must be high to force a low at U4D pin 11 during transmission. During reception U4B pin 6, driving inverter U4C, delivers a low at U4C pin 8. As long as U4C pin 8 remains low, no change of state at U4D pin 13 can alter the high at U4D pin 11. However, when both U4D pin 12 and U4D pin 13 are high, a low will hold at U4D pin 11. Propagation time for a change of state through U3B is somewhat greater than that of U4B and U4C. So, a small delay in the change from low to high at U4D pin 12 is desired. This delay is accomplished by means of a 270-ohm resistor and C15 (0.01  $\mu$ F), which are shown at the output, U4C pin 8. This step permits propagation time for U3B and eliminates the possibility of a short, unwanted low transient at U4D pin 11.

The anti-vox signal is picked up through an extension cable from a point near the anti-vox gain pot in the T-4XB, and routed to the circuit board. This signal performs the inhibit function to U3A. If the output at U3C pin 6 goes low, any low existing at U3A pin 6 will promptly go high, having been inhibited by U3C. Also, when U3C pin 6 is held low, no activation of U3A can occur. This is an important and useful feature of the retriggerable monostable. Transmission, then, must be initiated between syllables and words. This is a normal occurrence in landline telephone conversations. The anti-vox circuit is quite similar to the audio and sidetone circuit, making further description of anti-vox unnecessary.

Note that no variable adjustments by pots and no component tailoring are required in this design. However, the normal T-4XB vox gain and anti-vox gain controls are used for noncritical settings of each function. The vox delay pot in the T-4XB is not used. In operation of the new vox method, no time delays are

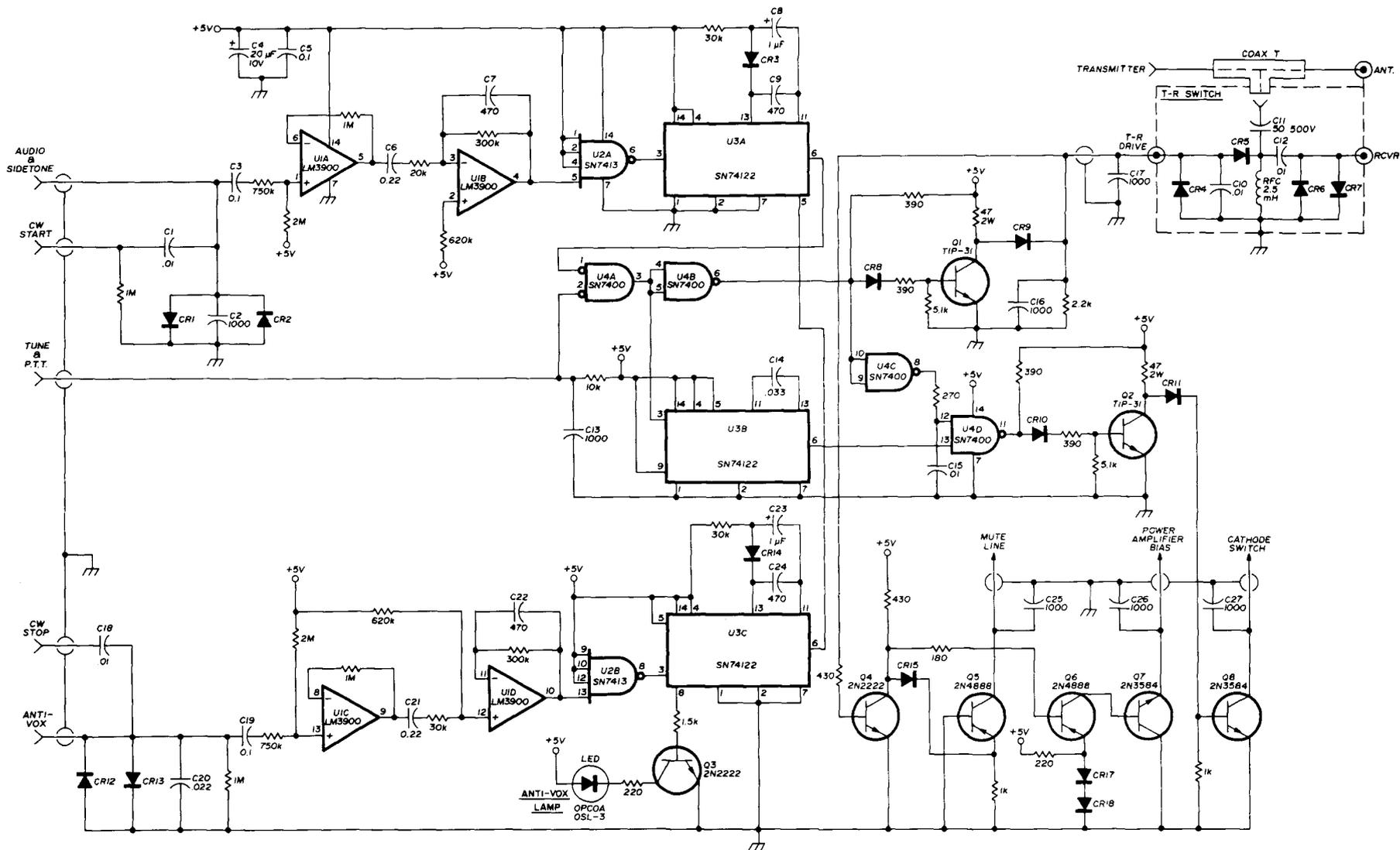


fig. 1. Syllabic vox and CW break-in system schematic for use with the Drake T-4XB and R-4B transmitter and receiver. Circuit provides instantaneous speech communication without conventional voxA relays. Diodes CR4, CR5, CR6, CR7, CR9 and CR11 are 1N4004 or equivalent; all other diodes are 1N914 or equivalent. The rf choke is a 2.5 mH transmitting type (100 mA). All resistors are 1/2 watt, 10% unless otherwise specified.

present that can be observed by unaided human senses. Also no vox/anti-vox interaction occurs. During the initial setup, the threshold for vox activation is established by the vox gain adjustment. After this setting, an increase in voice level does not alter the vox response in any way. Similarly, the anti-vox signal threshold assumes a constant level for activation after adjustment of anti-vox gain.

### setup procedure

The setup procedure is no more difficult and is perhaps simpler than that of conventional vox.

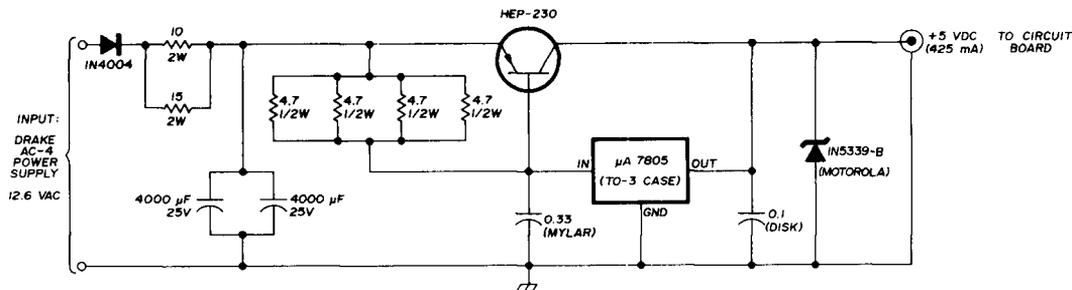


fig. 2. Simple 5-volt power supply for the syllabic system. Input power is supplied by the Drake AC-4 power supply. Unit is installed in the Drake MS-4 speaker cabinet.

**Step 1.** With the receiver and transmitter in the ssb mode, the anti-vox gain, vox gain, and receiver audio gain pots should be set to minimum gain. With the voice at normal audio level and the microphone in its customary position, bring up the vox gain sensitivity only enough to observe vox enabling, which will be shown by a fluttering action of the S-meter between syllables and words. A sustained audio note will hold the S-meter at maximum indication. Do not change this setting of the vox gain pot in the next step.

**Step 2.** With receiver band noise only, turn up the receiver audio gain until the vox is triggered occasionally, which is indicated on the S-meter as in the first step. This audio gain level should be high relative to that used in normal signal reception. Continuing with the band noise conditions, increase the anti-vox gain until the anti-vox LED glows intermittently, while the S-meter remains at zero.

The anti-vox LED is useful when communicating with a very weak signal under high-level noise conditions. These conditions combine to present a "worst-case" operational example. In this situation, it is advisable to reduce receiver audio gain until the anti-vox LED does not glow intermittently due to adjacent frequency audio interference.

### CW transmission

The CW start pulse in the T-4XB is used for fast vox initiation upon key or keyer contact closure at the start of a dot or dash code element. After starting, the side-tone signal holds the vox system *on* throughout the time duration of a dot or dash. However, the end of a dot or

dash must inhibit the vox circuit promptly to prevent holding the mute line open for 8.4 milliseconds after the end of a dot or dash. This requirement is accomplished by negative pulse differentiation upon restoration of the grid bias line in the T-4XB. Then, the negative-going CW stop pulse is routed to the circuit board anti-vox circuit, which inhibits U3A.

### power supply

The T-4XB normally uses a 6EV7 for vox gain and vox relay driving. Neither the vox relay nor the 6EV7 are used with the new vox system. So a simple heater

wiring change is made that eliminates the 6EV7 heater load of nearly 4 watts. The new circuit board requires a separate, regulated power supply that delivers 5 volts dc at 425 mA. Elimination of the 6EV7 suggested use of the Drake AC-4 power supply for the 5 Vdc requirement without adding an additional load to the AC-4 unit. Consequently, a 5-Vdc power supply was designed for use with the 12.6 Vac transformer winding of the AC-4 (fig. 2).

A small circuit board was prepared to support all components of the 5-Vdc power supply. Then 12.6 Vac and ground leads were soldered directly to these transformer terminals inside the AC-4 unit. The new leads were brought out of the AC-4 case through ventilation holes and connected to the input of the 5-Vdc power supply. This new supply was then located between the AC-4 power supply and the speaker in the Drake MS-4 speaker cabinet. This location offers more than adequate space for the 5-Vdc power supply, and there is no temperature problem. Incidentally, this method of connecting the available 12.6 Vac power automatically places the 5 Vdc power under the control of the power *on/off* switch on the T-4XB panel.

### T-R switch

The T-R switch used in this system is a compromise with respect to electromechanical relays. The titles "T-R switch" or "diode switch" are erroneous in technical fact. But these titles are used since correct and definitive nomenclature is not immediately available. Casual observation of the circuit may lead to the false conclusion that the T-R switch is a simple device for receiver protection. However, a rigorous, quantitative analysis of this

device is beyond the scope of this article. The interested reader is invited to bypass the T-R switch with a continuous 50-ohm line from antenna to receiver for comparison testing. Such tests conducted at my station displayed no discernible difference of signal strength on the S-meter.

Like other electronic T-R switches, this switch must be handled properly to avoid signal suckout. In this case, the switch enclosure is mounted directly to the T-4XB output connector. Rigid coaxial hardware is used and provides secure mechanical support for the small T-R

be wired so that *on/off* control of this relay is performed by the *power on* switch on the kW amplifier panel *only*.

These changes were made to an NCL-2000 amplifier in less than one hour. The end result was a pleasing lack of clacking noise from the cumbersome relay in dynamic operation.

### T-4XB changes

The following steps define installation of all extension leads, minor changes, and cabling required to the T-4XB chassis. No holes are drilled, no switches added

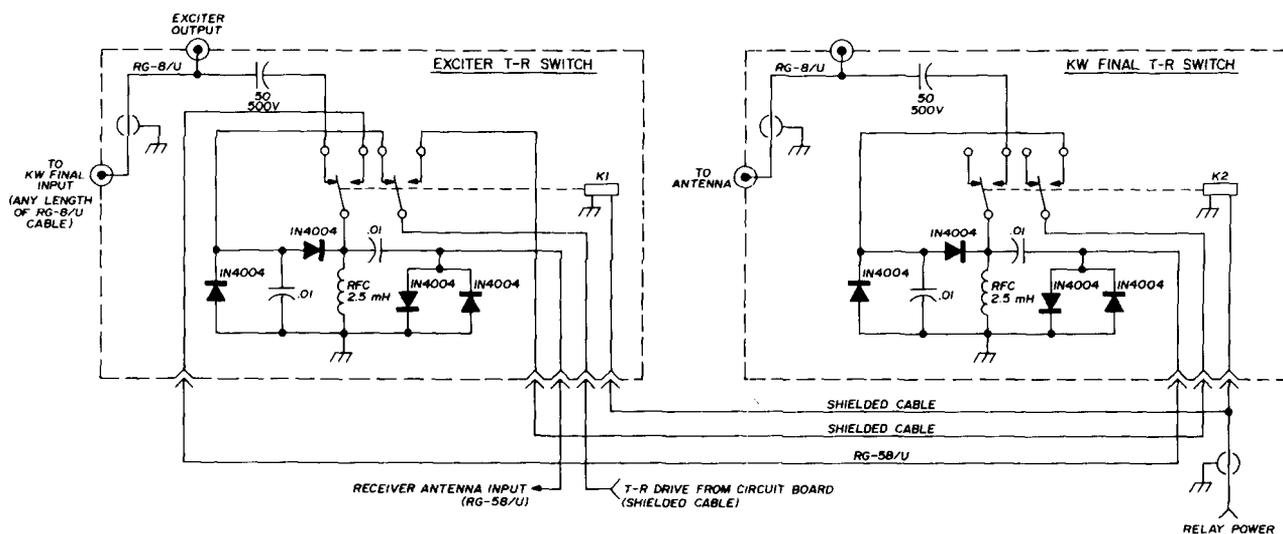


fig. 3. T-R switch schematic for use with kilowatt final amplifiers. Suggested relays are Potter & Brumfield type KT-11D. Each T-R enclosure should be mounted to each output by rigid coaxial connectors. A bud type CU-234 utility box is suggested for each T-R switch.

switch can. No signal suckout will occur with this installation of the switch unless the receiver and transmitter are tuned in different bands. When operating normally in a given band, improvement in signal-to-noise ratio may be observed. This is because the received signal looks into the output tank of the transmitter before appearing at the receiver.

### T-R switch with linear amplifier

When a final amplifier is used, the dual T-R switch method should be used, and the second T-R switch should be mounted rigidly to the output of the kW amplifier. See fig. 3 for a schematic and component details. In this case, two changes must be made in the control of the kW amplifier:

First, the power amplifier bias control must be removed from the antenna relay section that normally switches cutoff bias control to ground. Then, the bias control lead should be a direct, isolated conductor from the bias control point in the linear amplifier to the power amplifier bias terminal on the new circuit board in the T-4XB. It is assumed that the bias control point in the final amplifier has a negative potential not exceeding -150 Vdc and current loading not greater than 150 mA when grounded. Positive cathode bias is not considered in this article.

Second, the antenna relay in the kW amplifier must

and no defacement of components or chassis are required. (The Drake T-4XB manual is referenced).

1. Connect a jumper wire between socket terminals 4 and 5 of V10.
2. Disconnect lead from pin 5 of V9 to pin 3 of V11.
3. Disconnect lead from pin 9 of V9 to ground.
4. Connect new lead from pin 9 of V9 to pin 3 of V11.
5. At the vox relay *ant* section to J7, connect a jumper wire between the normally open contact and the movable contact. Then disconnect the lead to *rcvr* J6 from the normally closed contact.
6. At the vox relay *mute* section to J8, disconnect the movable contact from ground. Connect a board extension lead labelled "mute line" to the normally closed contact. Then connect another extension lead labelled "cathode switch" to the normally open contact using no. 22 AWG (0.6 mm) or larger shielded wire.
7. The third section of the vox relay is not specified but is used to control the *grounding of kW-amplifier negative bias* in this application. Connect an extension lead labelled "power amplifier bias" to the normally open contact of this section. The 2N3584 will easily handle a 150-mA load at -150 Vdc if required.

8. Locate the PTT contact on microphone jack J3 and connect an extension lead labelled "tune and PTT" to this contact.

9. Locate diode CR7 on the small circuit board at the right rear section of the T-4XB chassis. Apply soldering iron and pull out the cathode end of CR7. Then connect an extension lead labelled "CW start" to the exposed cathode of CR7.

10. The anode of CR7 connects to capacitor C131 (0.01  $\mu$ F), and the other side of C131 is connected to R78 (1M). At the junction of R78 and C131, connect an extension lead labelled "CW stop." Now solder a 1000-pF disc capacitor across R78. (Incidentally, this is the only component added to the T-4XB chassis).

11. Locate C92 (0.02  $\mu$ F) and CR12 in the anti-vox circuit. Then connect an extension lead labelled "anti-vox" at the junction between C92 and CR12.

12. C142 (0.02  $\mu$ F) is connected at the junction of R98 (3.3M) and CR9. Connect a jumper across C142.

13. Connect an extension lead labelled "audio and sidetone" to the center wiper contact of the vox gain pot, R89.

14. A shielded cable is connected to the T-R terminal on the circuit board and routed outside the T-4XB cabinet to the designated terminal of the T-R switch. The cable delivering +5 Vdc power to the circuit board and the cable to the T-R switch may be held together and clamped by a convenient screw already located on the T-4XB chassis.

This completes all changes and extension-lead connections to the T-4XB chassis. None of these terminals lack adequate access and offer no problem in location. At trade-in time, the T-4XB may be quickly restored to its original design with no loss in value.

## results

In radiotelephone practice, you'll experience some new and pleasant features when using this system. There is no vox-on presence between words or after a word of transmission. Only words and syllables of words appear on the air. Also there are no vox rf transients. The operator may be broken at any time and "doubling" is eliminated. Extraneous local noise does not appear on the air because the voice frequencies overwhelm the noise. If the transmitting operator wishes to force transmission, he may use PTT in the normal manner.


In CW service, the only locally generated noise is from the handkey, keyer, or power-amplifier blower. Only sidetone is heard in the earphones or speaker. Clicks and TVI are absent.

## references

1. H.R. Hildreth, WØIP, "Instantaneous Voice Interruption," *QST*, October, 1968, page 40.
2. H.R. Hildreth, WØIP, "More on Instant Voice Interruption," *QST*, June, 1972, page 19.

ham radio

# Vertical Performance DenTron Style.

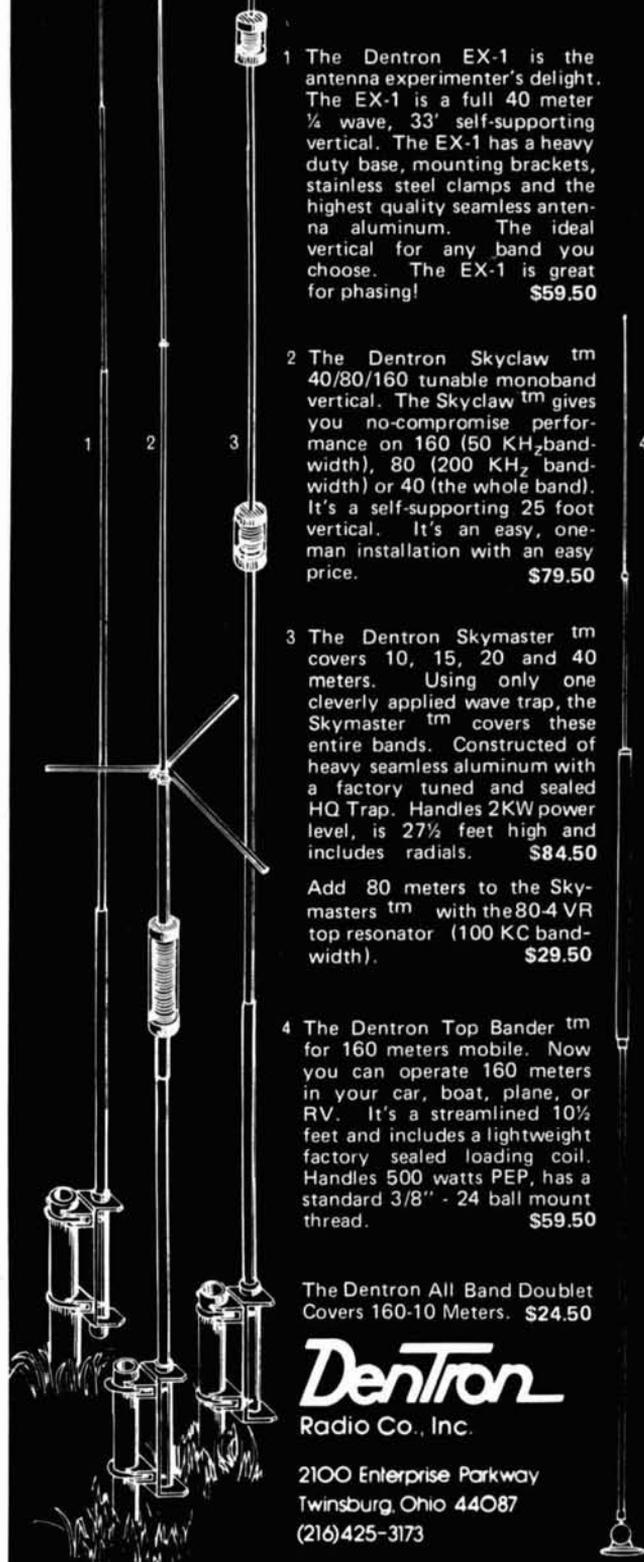

- 1 The Dentron EX-1 is the antenna experimenter's delight. The EX-1 is a full 40 meter  $\frac{1}{4}$  wave, 33' self-supporting vertical. The EX-1 has a heavy duty base, mounting brackets, stainless steel clamps and the highest quality seamless antenna aluminum. The ideal vertical for any band you choose. The EX-1 is great for phasing! **\$59.50**
- 2 The Dentron Skyclaw <sup>tm</sup> 40/80/160 tunable monoband vertical. The Skyclaw <sup>tm</sup> gives you no-compromise performance on 160 (50 KHz band-width), 80 (200 KHz band-width) or 40 (the whole band). It's a self-supporting 25 foot vertical. It's an easy, one-man installation with an easy price. **\$79.50**
- 3 The Dentron Skymaster <sup>tm</sup> covers 10, 15, 20 and 40 meters. Using only one cleverly applied wave trap, the Skymaster <sup>tm</sup> covers these entire bands. Constructed of heavy seamless aluminum with a factory tuned and sealed HQ Trap. Handles 2KW power level, is 27 $\frac{1}{2}$  feet high and includes radials. **\$84.50**  
Add 80 meters to the Skymasters <sup>tm</sup> with the 80-4 VR top resonator (100 KC band-width). **\$29.50**
- 4 The Dentron Top Bander <sup>tm</sup> for 160 meters mobile. Now you can operate 160 meters in your car, boat, plane, or RV. It's a streamlined 10 $\frac{1}{2}$  feet and includes a lightweight factory sealed loading coil. Handles 500 watts PEP, has a standard 3/8" - 24 ball mount thread. **\$59.50**

The Dentron All Band Doublet Covers 160-10 Meters. **\$24.50**

## Dentron

Radio Co., Inc.

2100 Enterprise Parkway  
Twinsburg, Ohio 44087  
(216)425-3173

# electrical units:

## their derivation and history

### An interesting sidelight on measurement units and their relationship to the metric system

A lot of people who work in electronics have to deal on a day-to-day basis with quantities such as voltage, resistance, and current and the units used to measure these quantities. Surprisingly few, however, know how the units of measurement were established, and it almost never fails to raise an eyebrow when they find out that all the basic quantities — volts, amperes, etc — are metric units that can be defined in terms of kilograms, seconds, and meters.<sup>1</sup>

It's strange to think that the amount of inductance we call 1 henry can be traced back to the diameter of the earth, or that 1 farad of capacitance owes part of its definition to the weight of water. It's stranger yet to realize that these quantities wouldn't have the values they do if it hadn't been for the downfall of King Louis XVI in the French revolution of 1789 — but that's how it is.

#### basic units

The watt, as a unit of power, and the ampere, as a unit of current, provide the foundation for defining the other units in electronics. Watts and amperes owe their definitions to the field of physics, which we'll look at later. The ohm, as a unit of resistance, arises naturally from the ampere and the watt. It was found that only a specific amount of resistance would produce 1 watt of heat if 1 ampere were flowing through it. This value of resistance is *defined* as 1 ohm, and the potential drop developed across this resistance under these conditions is *defined* as 1 volt. Even though an infinite number of combinations of voltage and current will produce 1 watt of heat in a resistor, there is only one value of emf that will do it with 1 ampere of current, just as there is only one value of resistance that will draw 1 ampere with 1 volt across it. Accordingly, there is no ambiguity in the values: they are clearly defined and have no "double values."

The ampere, as a unit of current, is commonly thought of as a quantity, but actually it is a *rate*, or quantity per unit of time. Its hydraulic equivalent would be gallons per unit of time, or liters per unit of time if

you want to stay in the metric system. The electrical equivalent of these gallons or liters is the coulomb, which signifies the actual quantity or number of electrons that will sustain 1 ampere of current for 1 second. In round numbers, 1 coulomb equals  $6.25 \times 10^{18}$  electrons. It's more commonly called the unit of charge, and since it defines a quantity instead of a rate, its symbol is Q. Incidentally, the ampere was originally described as the unit defining the *intensity* of a current, hence the use of the letter *I* in Ohm's and Kirchoff's laws to symbolize it.

#### derived units

The units of capacitance and inductance owe their definitions to the volt, ampere, and second. In the case of capacitance, it was discovered that no current would flow into or out of a capacitor unless the voltage across it was *changing*. A further investigation revealed that if the voltage changed at a constant rate, the current would also be constant. If the voltage increased, the current would be a charging current; if it decreased, the capacitor would discharge current back into the circuit. A still closer look revealed that, by doubling or tripling the rate of voltage change, the current would proportionately be doubled or tripled. As a result of these discoveries, 1 farad of capacitance is *defined* as the amount of capacitance that will draw a 1-ampere charging current if the voltage across it increases at the rate of 1 volt per second.

Inductance was found to have similar qualities, but with the roles of voltage and current interchanged. That is, no voltage would exist across a coil unless the current flowing through it was changing. If the current was increased at a constant rate, the voltage developed across the terminals of the coil would also be constant; and doubling or tripling the rate of current change would proportionately double or triple the voltage developed across the coil.

One henry of inductance was therefore *defined* as the amount of inductance that would sustain a 1-volt drop across its terminals if the current increased at a rate of 1 ampere per second.

Thanks to this system of definitions, proportionality constants are conspicuously missing in the equations used in electronics. The factor  $2\pi$ , which crops up in the equations for reactance and resonant frequency, is the only exception; and even here it is unnecessary if the frequency is expressed in terms of radians per second instead of cycles per second — but that's another story.

#### power and energy

It was stated earlier that the ampere is not a quantity but is a rate of change per unit of time. It would be just as correct to say that a given current was 50 millicoulombs per second as it would be to call it 50 milliamperes. The watt, as a measure of power, is also a measure

By Robert R. Simmons, WB6EYV, 1640 Walnut Avenue, Long Beach, California 90873

of rate instead of quantity. Just as 1 coulomb per second is commonly called 1 ampere, 1 watt could also be called 1 joule per second. Here arises the distinction between power and energy: energy is a *quantity*, whereas power expresses the *rate* at which this energy is expended.

An example would be appropriate here. Suppose we have a quantity of water at room temperature and wish to heat it to 10 degrees above room temperature. Let's further specify that the quantity of water is chosen so that it will require 5000 joules of heat energy to do this. We could put a resistor into the water and adjust the power fed to the resistor so that it dissipated 50 watts of heat into the water. At this rate, it would take 100 seconds to heat the water. If the power were increased to 200 watts, it would take only 25 seconds; at 500 watts, 10 seconds; and so on. In each case the same amount of work is accomplished; the only difference is in the rate at which it was done and the amount of time required. The joule is a unit of work or energy and has its definition in the roots of the metric system.

### measurement systems

A few words about measurement systems are in order. Basically, there are three major systems used in the world to measure quantities and rates on a scientific basis. These are a) the familiar English system, based on the foot for length, the pound as a unit of *force* (not mass), and the second for time; b) the CGS system; and c) the MKS system.

The CGS system (centimeter-gram-second) is the system that Einstein used in his work in relativity. The MKS system (meter-kilogram-second) is the system on which electronic units are based. These last two systems are metric and are based on the meter, gram, and second, which were established in France as a new system of measurement after the downfall of the ruling nobility in 1789. The meter, as a measure of distance, was defined at the time as representing one ten-millionth of the distance from the North Pole to the equator. The gram was also defined as the amount of mass represented by 1 cubic centimeter of distilled water cooled to 4 degrees Celsius. (This is the temperature at which water is most dense). As a unit of time, the second was retained, having its definition in the motion of the earth. The liter, as a unit of volume, was incidentally defined as representing 1000 cubic centimeters.

### force and work

In the MKS system, the first derived unit of measure is the newton, which is a measure of force, and is

*Ham Radio* is designed to provide something for everyone. This broadbush treatment of electrical units, their derivation, and history is presented to encourage further reading in the world of physics, the basis of our electronic heritage. A more rigorous definition of international units including a table of physical constants with their symbols, values, units, prefixes and least-squares error adjustments appears in reference 1. Also included in reference 1 are ten pages of conversion factors to get you out of the awkward English system and into the scientific metric system of measurement. **Editor**

defined as follows: If a 1-kilogram mass were placed on a frictionless surface, this mass could be accelerated from a dead stop to any speed by exerting force on it. The greater the force, the more quickly the mass would accelerate. One newton of force, if exerted on this 1-kilogram mass for 1 second of time, would bring it from a dead stop to a speed of 1 meter per second.

The unit of work in the MKS system is the joule and derives its meaning from the newton and the meter. It is defined as the amount of work expended by moving an object across a rough surface for a distance of 1 meter, if 1 newton of force is required to move it. If the object requires 2 newtons to move it, and it is pushed 2 meters, the work would be 4 joules. The work expended equals the product of the force and the distance.

### power

Notice that the amount of time required to perform this work does not change the amount of work that is done. Whether the work is done slowly or quickly, the same amount of energy is expended to move the object. The rate at which this work is done is called the *power*, or energy per unit of time. In the first example above, 1 watt of power would accomplish the job in 1 second. In fact, this is the definition of 1 watt: expending energy at the rate of 1 joule per second. In the second example, 1 watt would accomplish the job in 4 seconds, 2 watts in 2 seconds, or 4 watts in 1 second.

So much for the newton, joule, and watt as mechanical units. Only the ampere now has to be defined in mechanical units to completely relate all the electronic units to the world of physics. The ampere is defined under these conditions: If two very long wires (theoretically, infinitely long) are placed parallel to each other and spaced 1 meter apart, and if current is run through them (same value of current for each wire), then the magnetic fields they set up will tend to force the two wires either together or apart, depending on whether the currents are flowing in opposite or in the same direction, respectively.

If the amount of this force exerted on a 1-meter length of either of the wires has a magnitude of  $2 \times 10^{-7}$  newtons then the current is defined as having an intensity of 1 ampere. I don't know why  $1 \times 10^{-7}$  newtons wasn't chosen to define the force created by one ampere, but perhaps it was thought that each wire actually does exert this force, so that the total force acting on a 1-meter length would be  $2 \times 10^{-7}$  newtons — half of it due to each wire's magnetic field. This is all pure speculation, however, and should not be construed as accurate.

I hope this article has shed some light on our heritage in the field of physics without too much confusion. In a country that must go through the withdrawal pains of the English system of measurement, it's reassuring to know that we work in a field that has always been metric.

### reference

1. *The International System of Units*, NASA Publication SP-7012, Superintendent of Documents, U.S. Government Printing Office, Washington, D.C. 20402, price 30 cents.

ham radio

# Wilson Electronics Corp.

"FACTORY DIRECT ONLY"



## WILSON "WE-224" MOBILE

# SUMMER SPECIAL

## \$199<sup>95</sup>



### FEATURES

- 24 Channel Operation
- One priority Channel
- Selectable 1 or 10 Watts Out
- 10.7 Monolithic Filter Installed
- 455 KHz Ceramic Filter
- .3 Microvolt Sensitivity for 20 dB Quieting
- Numerical Read-out on each Channel
- Built-in Adjustable "Tone Burst" Generator
- Front Panel "Tone Burst" Control
- Accepts Wilson 1402 & 1405SM Xtals
- Individual Trimmer Capacitors for both TX/RX
- Mosfet Front End
- Helical Resonator
- High VSWR Protection Circuit
- Reverse Polarity Protection Circuit
- NBFM - 15 KHz Channel Separation
- Built-in Speaker
- External Speaker Jack
- Dynamic Microphone Included
- Mobile Mounting Bracket Included
- Quick Disconnect Power Cable
- Frequency Range 144-148 MHz
- 6 1/2" W x 2 1/2" H x 9 1/2" D
- Weight: 5 1/2 lbs.
- Power Requirements:
  - Source: 13.5 VDC ± 10%
  - Receive: .45A
  - Transmit: 2.6A (10W), .7A (1W)

### SPECIAL INCLUDES:

- WILSON "WE-224"
- MOBILE MIKE
- MOUNTING BRACKET
- 146.52/52 SIMPLEX CRYSTALS

90  
Day  
Warranty

10 Day  
Money Back  
Guarantee

## SUMMER SPECIAL on Wilson Hand Held 220 and 450

### 2202 SM

FREQUENCY RANGE 220 - 225 MHz

- 6 Channel Operation
- Individual Trimmers on all TX/RX Crystals
- All Crystals Plug In
- 12 KHz Ceramic Filter
- 10.7 and 455 KC IF
- .3 Microvolt Sensitivity for 20 dB Quieting
- Weight: 1 lb. 14 oz. less Battery
- Battery Indicator
- Size: 8 7/8 x 1 3/4 x 2 7/8
- Switchable 1 & 2.5 Watts Output @ 12 VDC
- Current Drain: RX 14 MA, TX 500 MA
- Microswitch Mike Button
- Unbreakable Lexan® Case

USES SAME ACCESSORIES AS 1405

SUMMER SPECIAL

## \$239<sup>95</sup>

INCLUDES

- 2202 SM
- Flex Antenna
- 223.50 Simplex Installed



### 4502 SM

FREQUENCY RANGE 420 - 450 MHz

- 6 Channel Operation
- Individual Trimmers on all TX/RX Crystals
- All Crystals Plug In
- 12 KHz Ceramic Filter
- 21.4 and 455 KC IF
- .3 Microvolt Sensitivity for 20 dB Quieting
- Weight: 1 lb. 14 oz. less Battery
- Battery Indicator
- Size: 8 7/8 x 1 3/4 x 2 7/8
- Switchable 1 & 1.8 Watts Output @ 12 VDC
- Current Drain: RX 14 MA, TX 500 MA
- Microswitch Mike Button
- Unbreakable Lexan® Case

USES SAME ACCESSORIES AS 1405

SUMMER SPECIAL

## \$279<sup>95</sup>

INCLUDES

- 4502 SM
- Flex Antenna
- 446.00 Simplex Installed

### ACCESSORY SPECIALS

DESCRIPTION	SPECIAL PRICE
BC1 BATTERY CHARGER	\$34.95
BP1 10 EA. AA GOULD NICAD BATTERIES	14.95
BT1 EXTRA BATTERY TRAY	6.00
LC1 LEATHER CASE 1402	11.95
LC2 LEATHER CASE 1405, 2202, 4502	11.95
SM1 SPEAKER MIKE FOR EARLY MODEL 1402 9 PIN CONNECTOR	24.95
SM2 SPEAKER MIKE FOR ALL NEW HAND HELDS WITH ROUND 6 PIN CONNECTOR	24.95
TE-1 SUB-AUDIBLE TONE ENCODER INSTALLED	34.95
TTP TOUCH-TONE PAD	49.95
INSTALLATION AT TIME OF RADIO PURCHASE	FREE
INSTALLATION AT LATER DATE, ADD	15.00
XF-1 10.7 KC MONOLITHIC XTAL FILTER	9.95
CRYSTALS TX or RX (Common Frequency Only)	3.75



BC-1 BATTERY CHARGER

# Wilson Electronics Corp.

FACTORY DIRECT ONLY

## SUMMER SPECIAL

1402SM  
HAND HELD  
2.5 WATT  
TRANSCIVER  
144-148 MHz

**\$164<sup>95</sup>**

1405SM  
HAND HELD  
5 WATT  
TRANSCIVER  
144-148 MHz

**\$239<sup>95</sup>**


### FEATURES

#### 1402 SM

- 6 Channel Operation
- Individual Trimmers on all TX/RX Crystals
- All Crystals Plug In
- 12 KHz Ceramic Filter
- 10.7 IF and 455 KC IF
- .3 Microvolt Sensitivity for 20 dB Quieting
- Weight: 1 lb. 14 oz. less Battery
- S-Meter/Battery Indicator
- Size: 8 7/8 x 1 7/8 x 2 7/8
- 2.5 Watts Minimum Output @ 12 VDC
- Current Drain RX 14 MA TX 500 MA
- Microswitch Mike Button
- High Impact Plastic Case
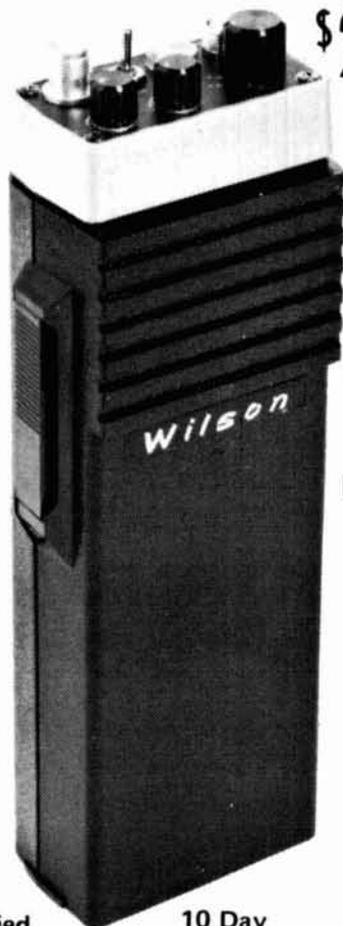
#### 1405 SM

- 6 Channel Operation
- Individual Trimmers on all TX/RX Crystals
- All Crystals Plug In
- 12 KHz Ceramic Filter
- 10.7 and 455 KC IF
- .3 Microvolt Sensitivity for 20 dB Quieting
- Weight: 1 lb. 14 oz. less Battery
- Battery Indicator
- Size: 8 7/8 x 1 3/4 x 2 7/8
- Switchable 1 & 5 Watts Minimum Output @ 12 VDC
- Current Drain: RX 14 MA TX 400 MA (1w) 900 MA (5W)
- Microswitch Mike Button
- Unbreakable Lexan® Case



**SPECIAL ON EACH RADIO INCLUDES:**

Flex Antenna  
52/52  
Simplex Xtal

Shown With  
Optional  
Touch-Tone Pad

Can be Modified  
for  
MARS or CAP

10 Day  
Money Back  
Guarantee

90  
Day  
Warranty

TO: WILSON ELECTRONICS CORP., 4288 S. POLARIS AVE., LAS VEGAS, NEVADA 89103, (702) 739-1931

### SUMMER SPECIAL DIRECT SALE ORDER BLANK

- 1402SM @ \$164.95
- 1405SM @ \$239.95
- WE224 @ \$199.95
- 2202SM @ \$239.95
- 4502SM @ \$279.95
- BC1 @ \$34.95
- BP1 @ \$14.95
- BT1 @ \$6.00
- LC1 @ \$11.95
- LC2 @ \$11.95
- SM1 @ \$24.95
- SM2 @ \$24.95
- TE1 @ \$34.95
- TTP @ \$49.95
- XF1 @ \$9.95
- TX or RX XTALS @ \$3.75 ea.
- FACTORY XTAL INSTALLATION/NETTING @ \$7.50/Radio

#### EQUIP TRANSCIVER AS FOLLOWS:

	XTALS	TX	RX	XTALS	TX	RX
A.	52		52	G.		
B.				H.		
C.				I.		
D.				J.		
E.				K.		
F.				L.		

(SPECIFY FREQUENCY \_\_\_\_\_)

ENCLOSED IS  CHECK  MONEY ORDER  
 MC  BAC

CARD # \_\_\_\_\_

EXPIRATION DATE \_\_\_\_\_

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_

STATE \_\_\_\_\_ ZIP \_\_\_\_\_

SIGNATURE \_\_\_\_\_

SHIPPING & HANDLING PREPAID FOR SUMMER SPECIAL

NEVADA RESIDENTS ADD SALES TAX

HR VALID ONLY AUG 1 THRU 31

# i-f/detector

## receiver module

Design and construction data for an i-f strip, detector, and audio filter that can be used for a high-performance amateur-band receiver

This article provides design and construction details for a high-performance i-f/detector receiver module. By itself the circuit is an 80-meter-band receiver, requiring only a frequency-determining oscillator and an audio stage for on-the-air use on the high-frequency amateur band. Performance data is given in table 1.

The sensitivity of this receiver is less than 0.1 microvolt rms for a signal-to-noise ratio of 10 dB. What does this really mean? Looking through the ads, you'll find a number of claims as to the sensitivity of a receiver at some signal-to-noise ratio. What's most important (and always missing in these claims) is a definition of terms. For example, one manufacturer tells us that his receiver has a sensitivity of 1 microvolt for a 10-dB signal-to-noise ratio. The question is, "Is this 1 microvolt rms or 1 microvolt peak-to-peak?" By proper attention to details in the construction of the receiver described here, you should be able to measure its sensitivity at less than 0.1 microvolt rms for a 10-dB s/n ratio, not 0.1 microvolt peak. At 1 microvolt rms, you should be able to measure a 10:1 voltage difference (20 dB) between signal and noise. I made my measurements using an HP-606A signal generator and a Tektronix 513 oscilloscope.

### design features

The block diagram of the i-f/detector (fig. 1) illustrates the overall design. Good image rejection is obtained by initial amplification at the higher frequency followed by a mixer stage with low noise and modest conversion gain. Amplification and passband characteristics are obtained with a multipurpose IC, using either a crystal or ceramic filter, or an LC tuned circuit at the conversion frequency. In any receiver system the detected audio will contain beat oscillator and spurious

noise components; these are reduced by passing the signal through an active low-pass filter IC, which is matched to an IC amplifier stage.

The i-f/detector schematic is shown in figs. 2A and 2B. Values for resonant-circuit components are shown in table 2. Note that in the schematics, capacitors are shown as a fraction; for example, 0.1/C. This means that the capacitor is a 0.1  $\mu$ F ceramic. An M below the value means the capacitor is mica.

The 3.5 to 4.0 MHz rf signal is amplified by Q1 and Q2. Tuning of both stages is accomplished using a varactor diode, which eliminates the need for a large variable capacitor. Dual-gate mosfets allow external agc and rf gain control if desired. For applications where an agc and rf gain control isn't required, a single-gate device could be directly substituted, or the control gates, G2, of Q1 and Q2 may be tied to some fixed voltage value. Down-frequency conversion is accomplished by Q3, a standard mosfet mixer. The input tuned circuit of Q3 is fixed and broadly tuned; the output is matched to a commercial i-f transformer. Biasing of gate 2 is accomplished by using a gate-to-source resistance that establishes the operating point for the device.

Overall system voltage gain, detection, and passband characteristics are developed by U1, a multipurpose IC. The schematic illustrates a Collins mechanical filter for

table 1. Performance data for the high-performance i-f/detector module.

frequency range	3.1 to 4.5 MHz with suitable hfo
nominal operating frequency range	3.5 to 4.0 MHz
high frequency oscillator range	3.045 to 3.545 MHz $\approx$ 2V, peak-to-peak
sensitivity	<0.1 $\mu$ V rms for 10 dB s/n ratio (distinguishable signal of 1 kHz)
noise margin	>20 dB at 1 $\mu$ V rms
shape factor	dependent upon filter. Normally 60 dB with Collins or Murata ceramic filters
in-band spurious signals	none using chassis and shields as indicated
audio	0 to 3 kHz; 5 kHz notch; 15 to 20 dB minimum attenuation on signals >5 kHz
nominal gain	80 to 100 dB depending on link positioning and control voltages

By M.A. Chapman, K6SDX, 935 Elmview Drive, Encinitas, California 92024

passband shaping. You may prefer a ceramic or simple transformer-type component instead; the overall operation of U1 will remain the same regardless of the type of filter used. Variations in gain can be expected using crystal and transformer filters, which have operating impedances differing from the ceramic type shown.

output of the stages arranged along the LMB 850 chassis sides through feed through terminals.\* This circuit is a classic i-f amplifier approach that will provide excellent interstage shielding and minimum feedback coupling which will eliminate oscillation. Interstage shields are aluminum strips fastened to the PC board and chassis

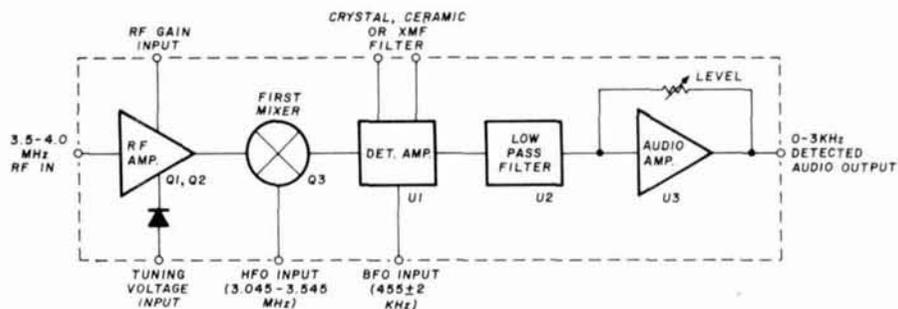


fig. 1. Block diagram, high-performance i-f/detector receiver module.


The detected audio signal on U1, pin 7, will contain many beat-oscillator audio components or hiss-type noises in addition to the desired detected audio. The most common method of eliminating these undesirable noise products is to use a toroidal LC or multiple op-amp active low-pass filter. These methods work well but require large areas on the chassis and can be expensive.

An inexpensive active device is available that operates as an elliptic lowpass filter having a rolloff frequency of 2.5 kHz. The attenuation at 5 kHz is approximately 18

sides. These shields provide all the mechanical rigidity required.

There are two methods of building the i-f/detector module: the right way and the sure-failure way. The right way is to build the assembly one stage at a time, testing each stage as you go. The sure-failure way is to install all components, assemble, and apply power expecting it to work!

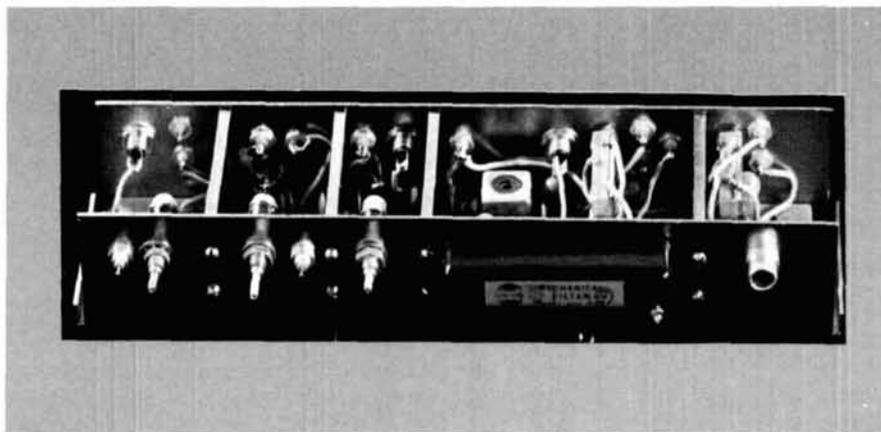Construction should start with U3. Install its associated components, temporarily apply power and signal



High-performance i-f/detector receiver module, cover removed. Enclosure is an LMB 850 box. Rf input is at right; audio output at left.

dB with increasing attenuation of all higher-order components. U2's output is matched to the input of U3, which operates as a voltage amplifier to compensate for the loss in gain through U2. U3 is a straightforward operational amplifier with internal frequency compensation.

### construction

The photographs show the construction approach. A PC board carries all active components with input-

inputs, then verify the correct output signal. The next step is to install U2, its associated components, and temporarily apply power and signal levels to U2 to verify its operation. This procedure should continue with U1, Q3, Q2, and finally Q1. Proceed through each stage to ensure proper operation. Using the step-by-step approach, you'll become familiar with circuit operation and can optimize the stages for your own preference.

Figs. 3A and 3B illustrate the PC board component locations. The board is designed to accommodate 1/4-watt resistors and low-voltage capacitors; larger components may be used by mounting them vertically with respect to the PC board.

\*Printed-circuit boards are available from the author for \$3.00 plus postage.

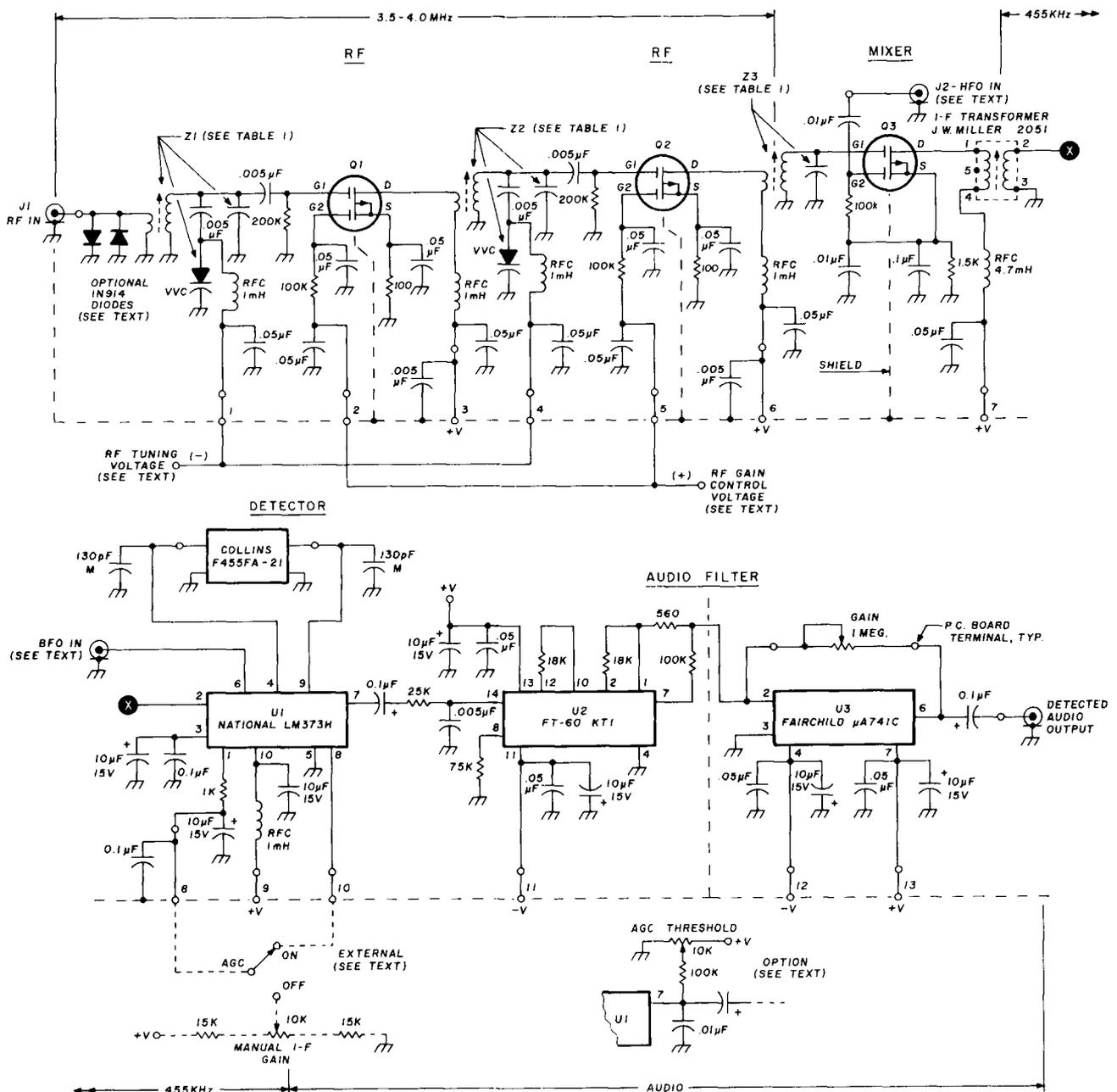


fig. 2. Schematic diagram of the high-performance i-f/detector module. Tuned circuit values are listed in table 2.

**step 1. U3 installation.** Install U3 and all associated fixed PC-board components. The 1-megohm feedback resistor may be left freely supported over the top of U3 using bus wires from the PC board. Temporarily install one end of a 100-ohm resistor in the +12 and -12V terminals. These resistors limit the current during test in the event of a wiring or circuit error. Apply a 15mV 1-kHz audio signal to pin 2 of U3, and with power applied, adjust the feedback pot for an output voltage of 100 to 150 mV. Increasing the frequency of the audio input signal should show decreasing output values at frequencies above 3 kHz.

**step 2. U2 installation.** Install U2 and all associated


components up to the 0.1/C coupling capacitor from pin 7 of U1. Install the 100-ohm current-limiting resistors for both the +12 and -12V terminals, as you did for U3. With power on both U2 and U3, apply a 100mV 1-kHz audio signal to the U1 pin 7 side of the 0.1/C capacitor. While monitoring the output of U3, adjust the U3 feedback pot for an output voltage of 100 to 150 mV. Increasing the frequency of the audio input signal should show decreasing output values at frequencies above 3 kHz.

**step 2. U2 installation.** Install U2 and all associated



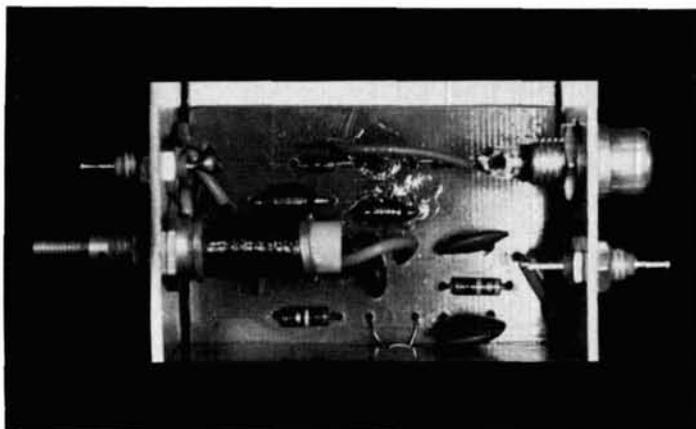455.95-kHz crystal for the bfo frequency, which develops an easily distinguishable 1-kHz audio signal at the output with unmodulated carrier injection.

**step 4. Q3 installation.** Install all components associated with Q3. Adjust Z3 coil slug for resonance at 3.750 MHz. The input link should be loose along the outside of the coil but terminated to the PC board. Apply power to Q3 and U1 only, and inject a carrier voltage of 3.750 MHz at the link of Z3 and a beat oscillator signal from an external oscillator into G2 of Q3. Reference 1 discusses the design of a suitable high-frequency oscillator that matches this unit. By spreading and sliding the link portion of the Z3 coil input for maximum signal output,



Mixer input section. Q3 gates are on the right; HFO input is through phono jack at upper left.

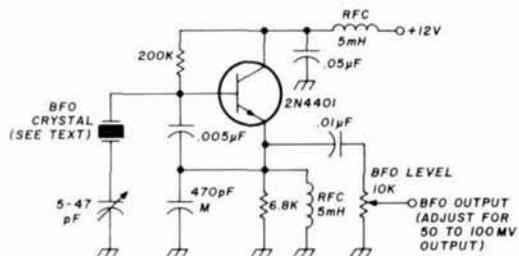


fig. 4. Bfo schematic. Crystal frequency depends on filter, as discussed in text.

a 50- $\mu$ V signal at Q3 link input should provide a 30-mV detected audio signal at U1, pin 7.

**step 5. Q2 installation** Install Q2 and all associated components except Z2. Apply power to Q2 and Q3 only, and inject a 3.750-MHz carrier into G1 of Q2 while monitoring the drain of Q3. Temporarily apply +12 volts to the input side of the 100-k resistors of G2. Make the final link adjustment on the output of Q2 for a voltage gain of Q2 equal to 8 or 10. Apply a small amount of

approximately -10 volts while positioning Z2 slug for resonance. The link may be moved over the surface to the coil to optimize this coupling.

**step 6. Q1 installation.** Repeat all installation procedures used for Q2 on Q1. Adjust Z1 slug so that the same corresponding VVC tuning voltage is applied to both resonant circuits in the Q1 and Q2 stages. The operating characteristics of Q1 and Q2 can be verified by alternating grounding G2 of Q1 and Q2 for a short time while monitoring the output of Q3 at either the drain or at the i-f transformer secondary. Temporary grounding of G2 for either Q1 or Q2 should result in an immediate decrease in the output signal level. This should demonstrate the AGC operating feature of the dual-gate mosfet. With the ground removed, the output signal should slowly rise to full value. If you're not interested in using an external rf gain control, you could substitute a single-channel fet for Q1 and Q2 and adjust the source


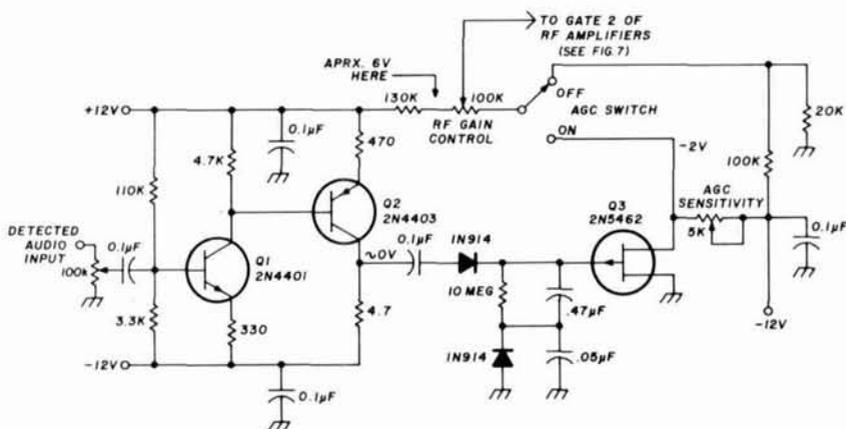


fig. 5. Suggested circuit for agc and rf gain control.

coil dope to the link to secure it in this position. Install Z2 and the associated VVC components. Apply power to Q2 and Q3 while injecting a low-amplitude 3.750-MHz carrier to the link of Z2. Apply -20 Vdc through 100k pot, and adjust the voltage on the VVC to

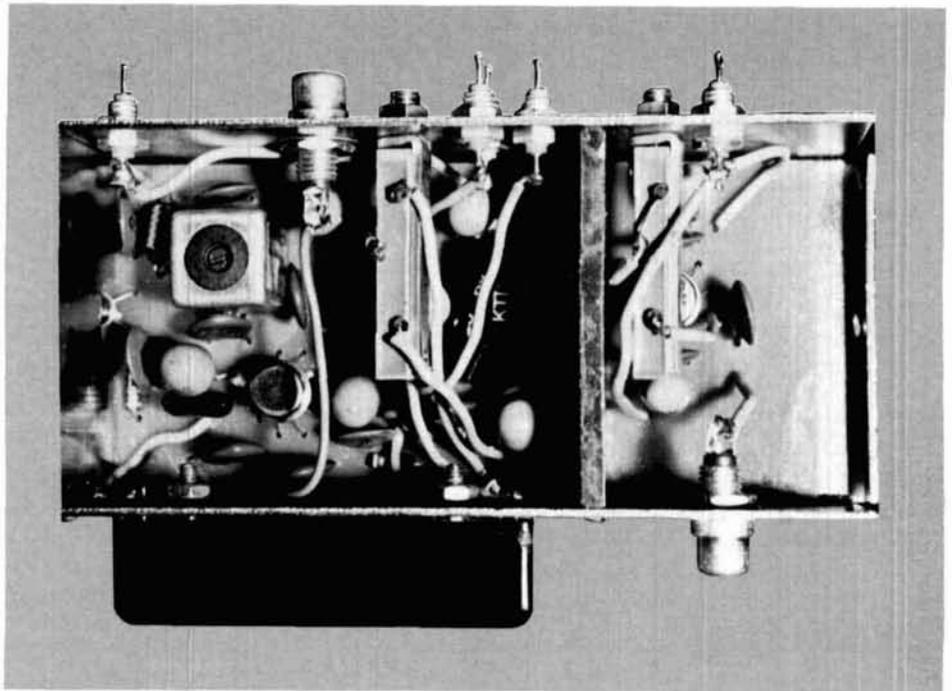resistance for adequate feedback. Maximum gain is achieved when the source terminals of Q1 and Q2 are at ground potential; however, optimum noise margins are obtained using a source resistance of approximately 220 ohms.



Mixer output, i-f amplifier, and audio filter. Bfo input is through phono jack at right of the 455-kHz i-f transformer. Audio output is at phono jack, lower right.

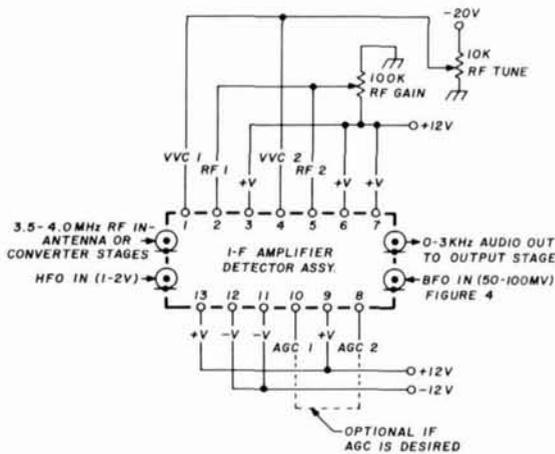


fig. 6. Simplified operating mode for the i-f/detector module.

**step 7. Initial i-f testing.** During this step if oscillation is apparent, look for feedback caused by the temporary clip leads. Care in placement of clip leads and wire routing to the bfo and hfo is imperative. Improper grounding and bypassing will couple unexpected rf components into the system. As an example, if your bfo is at approximately 456 kHz, then the 8th harmonic is at 3.468 MHz, which can be picked up by the module if you have poor shielding in the high-gain stages.

While keeping the current-limiting resistors in place, carefully apply power to each succeeding resistors, starting at U3 and proceeding through Q1. If you haven't made a polarity error, poor positioning of clip leads, or injected too much bfo voltage into U1, the system should be quite stable. Monitoring the output of U3 should display low-level random audio output noise, which should not change even while Q1 input is alternately grounded or

left open when the hfo is tuned over the entire input range.

Inject a  $5 \mu\text{V}$  rms signal at 3.750 MHz into Q1 input. While monitoring U3 output with the hfo tuned to the beat frequency, an audio signal of approximately 0.1 V peak-to-peak at 1 kHz should be obtained. Some adjustment in the VVC tuning pot may be necessary to peak the signal.

Strictly speaking, the gain of a system is defined as:

$$dB = 10 \log \frac{|V_2|^2 / R_2}{|V_1|^2 / R_1}$$

$$\text{If } R_1 = R_2 \text{ then } dB = 20 \log \left| \frac{V_2}{V_1} \right|$$

This relationship is widely misused, and in voltage ratios the gains are expressed in decibels even though  $R_1 \neq R_2$ .

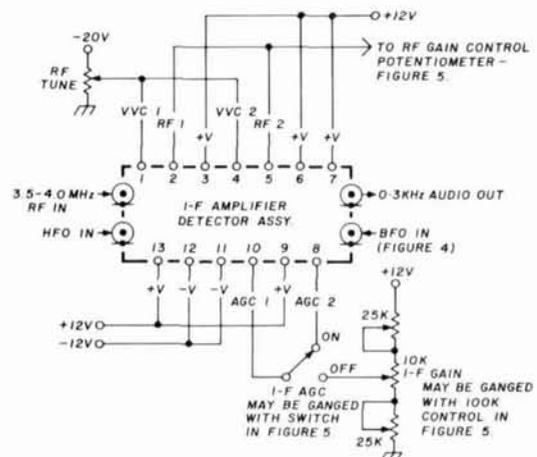


fig. 7. Sophisticated operating mode for the i-f/detector module.



fig. 8. Printed-circuit board layout for the rf amplifier and mixer (left side of board) and the detector and audio filter. Board is 7-7/8" (20cm) long by 2-1/8" (5.4cm) wide.

Furthermore, we had a carrier of 3.750 MHz on the input and are examining an audio signal on the output. If we ignore this small impropriety, we can calculate the i-f/detector gain as:

$$dB = 20 \log \left| \frac{\text{output voltage}}{\text{input voltage}} \right|$$

The measured output voltage is 0.1V peak-to-peak, or

$$V_2 \text{ rms} = \frac{0.1}{2.828} = 0.0353 \text{ rms}$$

and the input

$$V_1 \text{ rms} = 5(10^{-6}) \text{ V}$$

$$dB = 20 \log \frac{0.0353}{5(10^{-6})} = 76.9 \text{ dB}$$

### final assembly

Remove the temporarily installed current-limiting resistors and install short pieces of bus wire for feed-through access from the chassis. Install the PC board assembly into the chassis as shown in the photographs, terminating the bus jumpers to feedthrough terminals. Twist the inductors slightly then slide them into mounting holes along the side of the chassis.

For final testing the assembly should be wired as shown in fig. 6. Readjust the coils slightly, and if the agc threshold trimmer is used, adjust it for approximately 1 volt. The agc jumper wire between pins 8 and 10 may be removed for initial testing. Apply a 1- $\mu$ V signal to the input, adjusting the coil slugs and the rf gain and rf tune resistors. A detected 0.1 volt audio signal should appear at the output, which represents a maximum gain of 90.9 dB. The slug settings on Q1, Q2, and Q3 may be adjusted to optimize the tracking characteristics. It won't be necessary to use the full voltage range control from the 10k rf tuning pot since only a few volts are necessary for maximum gain in the rf stages. Peak gain for the mosfet is achieved between 4 to 10 V. Where fixed gain of the i-f/detector is desired, pins 2 and 5 may be tied directly to the +12 volt lines through 100k current-limiting resistors.

By experimenting with the 100k agc-threshold setting, you'll find that a 4 to 5 volt setting on U1 pin 7 will provide a 50% decrease in gain at 300  $\mu$ V input. You might wish to vary this setting to suit your specific

needs. For strictly CW applications this option is not necessary and the circuit shown in fig. 6 will be easiest to implement. For maximum operation flexibility, the assembly should be operated as shown in fig. 7. This arrangement provides agc control at both the rf and i-f stages and, additionally, allows a variable control in the rf and i-f gain to achieve the most ideal signal-to-noise margin in receiving both CW and ssb signals. Referring to fig. 7, with the trimpots shown on the i-f gain, a setting range for both the rf and i-f gain control can be achieved that will allow the pots to be ganged, which is also true of the agc switches shown in figs. 5 and 7.

With both crystal and ceramic i-f bandpass filters, the ideal ssb bfo frequency is at the plus and minus 20-dB points from center frequency. CW reception is most easily distinguishable at 800 to 1000 Hz. The crystal oscillating frequency then is usually determined after obtaining the filter and measuring the center and 20-dB points. For both upper and lower ssb and CW reception, individual bfo circuits can be used following the design suggested in fig. 4, having a common output bus and separate 12-volt control lines so that the desired frequency may be selected.

The selection of Q1, Q2, and Q3 is a matter of preference. The Motorola MFE3006, MFE3008, and RCA 40673 work well in the circuit shown. Recently, RCA announced an economy device, the 40841. Comparison tests between the 40841 and MFE3006 indicate that the RCA device is a comparable unit and could become the receiver builder's most versatile transistor. It may be used as a single-gate device by tying the gates together for most fet oscillator and amplifier applications, or as a general-purpose unit operating to 50 MHz.

### references

1. M. A. Chapman, K6SDX, "A Master Frequency Oscillator," *ham radio*, November, 1975, page 50.
2. National Semiconductor Corp., "A Complete Monolithic AM/FM/SSB IF Strip," AN-54, April, 1972.
3. Kinetic Technology, Inc., "FS-60 Hybrid Universal Active Filter," August, 1971.
4. Collins Radio Co., Drawing No. 562-9427, "Mechanical Filter F455fA-21," August, 1970.
5. RCA Solid State Division, "RF Applications of the Dual Gate MOS/FET up to 500 MHz," Application Note AN-4431, 1975 Data Book Series.

ham radio



## Great cost cutting ideas we've rejected for 20 years

**Unplated hardware.** We use a nickel-chrome plating that defies corrosion.

**Cheaper stainless steel.**

Our 17-7PH steel whips bend 180° and return to perfect vertical.

**Erratic coil winding.**

Tight, precisely wound coils are vital to maximum range.

**Smaller set screws.** Unlike some competitors, ours are rustproof stainless steel that stand up to a wrench.

Cost cutting ideas are fine...until they affect quality and performance. Don't settle for second best. Look for the stripes of quality.



© "Stripes of Quality"

### the antenna specialists co.

a member of The Allen Group Inc.  
12435 Euclid Avenue, Cleveland, Ohio 44106  
Export: 2200 Shames Drive, Westbury, LI NY 11590  
Canada: A. C. Simmonds & Sons, Ltd.

# There is no substitute.



3854

3750

3855

 **hy-gain**<sup>®</sup>  
Amateur Radio Systems.

There is no substitute for quality, nor performance, nor the satisfaction of owning equipment that is the very best.

Hence, the incomparable Hy-Gain 3750 Amateur Transceiver. It is unquestionably the finest unit available today.

The 3750 covers all amateur bands from 1.8 through 30 MHz (160-10 meters). It utilizes advanced Phase-Lock-Loop circuitry, dual-gate MOS FET's at all critical RF amplifier and mixer stages, a narrow band SSB crystal filter and a 50 kHz T-notch filter. And that's just the beginning.

The 3750 also incorporates audio and microphone compression circuits, ALC, specially developed S-2002 tubes, and a VFO section that's so stable drift is less than 100 Hz (after a 30 minute warm-up.)

There's a rotating dial for low-speed frequency indication and easy band-scanning. And an electronic frequency counter with four-place digital readout to 100 Hz for pinpoint accuracy. The tuning section also includes a memory circuit for remembering frequencies with a flip of a switch. A 10 MHz WWV receive position eliminates the need for a crystal calibrator.

A speaker unit (3854) with tailored audio response frequency and a complete external VFO(3855) with provision for 7 crystal controlled channels are available in matching cabinets.

See your amateur radio dealer for complete details on the Hy-Gain 3750, or write our Department MM. There is no substitute.

## SPECIFICATIONS

### Frequency coverage

1.8 MHz Band	1.8 - 2.0 MHz
3.5 MHz Band	3.5 - 4.0 MHz
7.0 MHz Band	7.0 - 7.5 MHz
14 MHz Band	14.0 - 14.5 MHz
21 MHz Band	21.0 - 21.5 MHz
28 MHz Band A	28.0 - 28.5 MHz
28 MHz Band B	28.5 - 29.0 MHz
28 MHz Band C	29.0 - 29.5 MHz
28 MHz Band D	29.5 - 30.0 MHz
WWV	RX only 10.0 MHz

**MIC, input impedance**  
50K $\Omega$

**Frequency**  
300 - 2700Hz (-6dB)

**Sensitivity**  
SSB less than .25  $\mu$ v for  
10 dB S/N+N ratio  
CW less than .15  $\mu$ v for  
10 dB S/N+N ratio

### Modes of operation

SSB (LSB or USB)  
CW

### Input power

200W  
1.8-21.5MHz  
100W  
28-30MHz

**ANT, impedance**  
50 $\Omega$  - 75 $\Omega$  Unbalanced

**Carrier suppression**

More than 50dB

**Side band suppression**

More than 50dB

**Spurious and harmonic suppression**

Greater than 40dB

**3rd order distortion products suppression**

Greater than 30dB

### IF Frequencies

1st IF 9MHz  
2nd IF 50kHz

### Selectivity

SSB 2.4kHz (-6dB)  
4.0kHz (-66dB)  
CW 400Hz (-6dB)  
1.8kHz (-66dB)

### Audio output into 8 $\Omega$ load

2.5W (10% distortion)  
3.0W (MAX)

### Power source

AC 120V 50/60 Hz (can be re-wired for 240V)

### Power drain

400VA TX  
78VA RX  
48VA RX (Power tube OFF)

### Semi-conductors

Transistor	98
IC	43
Diode	120
Tube	3
Digital Ind.	1

### Weight

44 lbs. 6 ozs. (23kg)

### Dimensions

16-3/4" x 7" x 13-5/8" (420 x 172 x 340mm)

 **hy-gain**<sup>®</sup>  
**Amateur Radio Systems.**

Hy-Gain Electronics Corporation  
8601 Northeast Highway Six; Lincoln, NE 68505

# an introduction to slow-to-fast-scan television converters

Digital scan converters  
are a new innovation  
in slow-scan television —  
here's how they work

One aspect of amateur radio that appears to be leading all others in technical advancement is slow-scan television. Unquestionably, the accelerated advancements in this field are due to the application of digital techniques to circuit design. Most digitized sstv units are also available on PC boards. This means that an enthusiastic amateur can build highly sophisticated sstv circuits without a full knowledge of how they operate. With these thoughts in mind, this article is presented as a guide to understanding one of sstv's latest innovations: the slow-to-fast-scan converter. I'd like to stress that this is an explanatory rather than a construction article. Amateurs can build kits; I'm attempting to describe how their circuits operate — in this case, the slow-to-fast-scan converter.

If you haven't kept abreast of sstv evolution, here's a thought worth considering: begin with a technical starting point (such as this article), expand from there, then follow subsequent advancements. This beats following behind new innovations because you're not familiar with in-between areas.

## converter memories

Dynamic mos shift-register memories are the heart of all scan converters. The typical converter memory has about 16,000 digital words by four-bit plane capacity. This means that about 64,000 bits can be stored in such a memory. The four-bit planes usually store from binary 0000 to 1111, or 16 shades of gray. A simplified example of this type memory is shown in fig. 1. The top left corner of this hypothetical unit is shown storing a 5. Its binary equivalent is written into the corresponding four-bit planes. Similarly, the binary equivalent of 8 is written into its corresponding planes, and zeros are written into the four right-hand planes. The number of digital words showing on the memory's front area indicate video resolution capability, while the number of bit planes determine gray levels.

If you can visualize 1800 memory cubes as in fig. 1 wired in series, you'll have a good idea of the memory size used in a slow-to-fast-scan converter. Also, gray coding would be used rather than straight binary-coded decimal coding. This gray code is easier to use because only one bit changes state between successive digital words. Now let's consider the overall concept of scan conversion.

## slow-to-fast-scan converter

This converter represents a revolution in sstv technology because it allows you to view slow-scan television pictures on a conventional (fast scan) home television set. Although there are presently only two basic designs of this unit,<sup>1,2</sup> their operational concepts follow a definite pattern. A typical slow-to-fast-scan converter is shown in fig. 2. Incoming slow-scan television signals are fed to an sstv demodulator and sync separator. These circuits, shown in the dotted lines of fig. 2, represent a typical P7 sstv monitor without a cathode-ray tube and high-voltage supply. In fact, a conventional sstv monitor could be used for this part of the converter if desired.

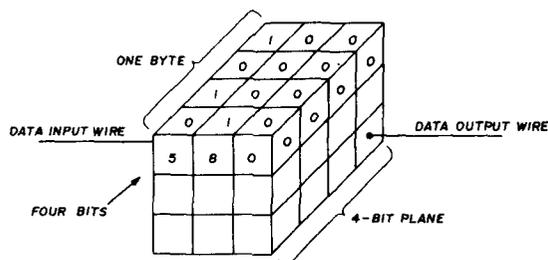


fig. 1. Three-dimensional representation of a shift-register memory used in a slow-to-fast-scan television converter. In this example the total memory capacity is 9 bytes or 36 bits.

Varying video voltages from the demodulator enter the analog-to-digital converter, which changes these voltages to their binary equivalents. This A/D converter employs a voltage divider string connected to voltage comparators to produce digitized equivalents proportional to the varying video levels. This conversion is accomplished periodically by sampling each line of slow-scan video, as illustrated in fig. 3. The sampling rate is usually 256 times per line. This sampling rate results in 256 words, each containing four bits of gray-code information. Immediately following each line of sstv video, the sync separator extracts a slow-scan sync pulse, which

By Dave Ingram, K4TWJ, Eastwood Village, 604N,  
Route 11, Box 499, Birmingham, Alabama 35210

triggers the slow-speed clock (fig. 2). This clock, in turn, opens the proper line buffer input to allow each digitized line to enter the 65,000-bit shift register memory. (Meanwhile, the fast-speed clock directs "read from memory" and "recirculate fast scan information" functions. It does this by sending high-speed shift pulses to the memory and timed, binary-1-level signals to the D/A converter).

this operation for, say, 20 times, you'll see that the red cars will again be on the track. This rather poor analogy is similar to scan-converter memory functions.

### concluding remarks

This information has been presented with the hope of enlightening interested amateurs on the basic concepts of digital slow-to-fast-scan conversion. Remember that

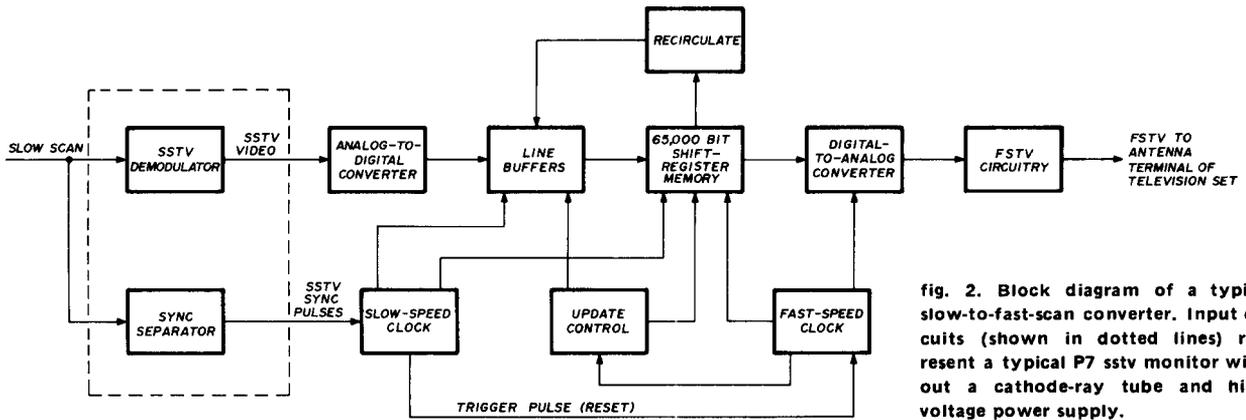


fig. 2. Block diagram of a typical slow-to-fast-scan converter. Input circuits (shown in dotted lines) represent a typical P7 sstv monitor without a cathode-ray tube and high-voltage power supply.

Now, at the precise start of the proper fast-scan line, the fast-speed clock sends a pulse to the update control. This control then directs a binary-1-level signal to the appropriate buffer output, which allows a full line of slow-scan information to enter the fast-speed 65,000-bit memory. This controlled loading operation is performed approximately 128 times during an eight-second period to load a complete sstv picture into memory.

phenomenal progress is being made in slow-scan television technology. While by no means describing the final word in scan-converter design, I think you'll find this article helpful in following the operation of these circuits.

The shift register memory continuously operates at a fast-scan rate, so this information is output (at the proper times) into the D/A converter, where it's converted to fast-scan video. Every 1/15750 second the fast-speed clock sends a sync level pulse to the D/A converter to produce sync-level signals. The D/A converter uses a resistor-transistor network arranged in a ladder adder configuration to produce voltage level equivalents to the binary weight of incoming counts.

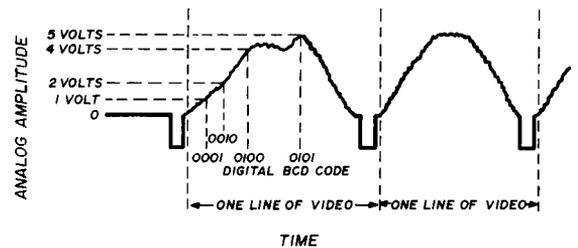


fig. 3. Each line of slow-scan video voltage is sampled at a periodic rate (approximately 256 times per line), which results in 256 digital words per line, each containing four bits of gray-code information.

The final step involves modulating a simple uhf signal generator with the composite fast-scan television signal. This signal is applied to the antenna terminals of a conventional television receiver. Now the resultant slow-scan television picture can be viewed in a well illuminated room.

Other sstv innovations are being developed, such as the color system that uses a 500-Hz subcarrier to carry I and Q color information, while black and white information is contained in the usual 1200 to 2300 Hz range. You'll probably be hearing more on slow-scan television developments in the near future.

### memory analogy

Memory operation could be illustrated by using an automobile race track to symbolize data flow. First, consider the race track as a circle filled to capacity with very fast blue cars. Fifty green cars are on the entry ramp at one end of this circle, and fifty red cars are on the exit ramp at the opposite end of the circle. A horn sounds and ten red cars quickly leave the exit ramp. At the same time, ten blue cars quickly enter the exit ramp, and ten green cars slowly enter the race track (but quickly gain speed). The red cars then drive around the track and wait in line with the green cars. If we follow

I'd like to thank Dr. Robert Suding, W0LMD, for his criticism on the final version of this article. If reader interest warrants, future articles on digital electronics or slow-scan television may be presented.

### references

1. David Ingram, K4TWJ, *Slow Scan TV for Amateurs*, TAB Books, 1976, (W0LMD scan converter on page 110).
2. Dr. George Steber, WB8LVI, "SSTV to Fast-Scan Converter," *QST*, Part I, March, 1975, page 33; Part II, May, 1975, page 28.

ham radio

# a revealing analysis of the coaxial dipole antenna

This analysis of the  
coaxial dipole antenna  
shatters many  
of the myths —  
it also explains why  
its swr bandwidth  
doesn't measure up  
to some of the claims

At some time or another most radio amateurs have used a folded-dipole antenna. And, wisely or not, more and more amateurs are now trying the *coaxial* dipole, sometimes called the "double bazooka."<sup>1</sup> Those amateurs who favor the folded dipole generally do so because of its flexible input-impedance characteristics; many amateurs are also acquainted with its somewhat broader bandwidth characteristics as compared with the single-conductor dipole. Many amateurs also try coaxial dipoles in hopes of obtaining increased bandwidth.

Some of the proponents of the coaxial dipole apparently use it because they have been misled into believing it also possesses certain other exotic characteristics, such as supplying its own balun when fed with a coaxial transmission line, as if providing an inherent unbalanced-to-balanced input (not so); exhibiting more than 1.5 dB gain over a simple dipole<sup>2</sup> (not so); and even offering a noise-cancelling capability because the antenna is said to be "shielded" (some amateurs have claimed that "the coaxial dipole has no man-made noise pickup whatever").

One purpose of this article is to show why the coaxial dipole cannot perform according to these utopian specifications and that, except for restricted differences in

bandwidth and impedance, its performance is the *same* as that of a simple dipole. Although the coaxial dipole can provide a limited broadening of the impedance bandwidth as compared to a simple dipole *if* engineered correctly, the coaxial dipole configuration in general use by amateurs is not engineered correctly. Consequently, it does not provide the broadband operation erroneously attributed to it.

A second reason for this article is to discuss the *reasons* why the engineering requirements for broadband operation are *not* fulfilled in the amateur configuration, thereby alerting the eager but unsuspecting builder before he wastes valuable time and expensive coax in building a complex dipole that will perform no better than a simple dipole.

## impedance bandwidth

The impedance bandwidth of an antenna is derived from the impedance mismatch between the antenna and its feedline as the operating frequency is varied between specified limits. The principal contributor to increased mismatch, as the operating frequency departs from the self-resonant frequency of the antenna, is the reactance which appears in the input impedance of the antenna. The effect of reactance and other parameters is shown in appendix 1. This reactance is developed whenever current reflected from the ends of the radiating elements arrives back at the input terminals with other than a 0° or 180° phase relative to the incoming current from the feedline. A zero or 180 degree relation is obtained only when the operating frequency is the same as the self-resonant frequency. This is why the resonant frequency of an antenna is sensitive to the length of the radiating element.<sup>3</sup>

In an *ideal* antenna having infinite bandwidth all the power delivered by the feedline would be radiated by the time the outward-flowing current reaches the end of the radiator, so no reflected current would return to generate a reactance at the input terminals. In other words, the ideal antenna would simply be a broadband transformer, matching the feedline impedance to the 377-ohm intrinsic impedance of free space at *all* frequencies. In our quest for increasing dipole bandwidth we are looking for some scheme which will either cancel or compensate this reactance as it appears (as in folded and

By Walt Maxwell, W2DU, Box 215, Georges Road, Dayton, New Jersey 08810

coaxial dipoles), or reduce the reactance by reducing the amount of out-of-phase current reflected from the ends of the radiator. The out-of-phase currents arriving from the ends of a conically-shaped radiator (or a fan-shaped multi-wire dipole) are smaller than those in a thin dipole so less off-resonance reactance is generated in wider-ended radiators.

The reactance compensation obtained in folded and coaxial dipoles results from applying reactance of the opposite kind, contributed by shorted stub sections, as shown in fig. 1B for the folded dipole, and in figs. 1A, 1C and 1E for the coaxial configuration. Each half of the folded dipole and the internal portion of each coaxial section in the coaxial dipole forms a resonant quarter-wavelength stub near the resonant frequency of the dipole, short-circuited at the end opposite the feed point. The two stubs of the coaxial dipole are connected in series through their inner conductors. The series combination is shunted across the dipole input terminals as shown in fig. 1E. The shunt-connected stub combination reduces the off-resonance reactance appearing at the dipole input terminals because the stub reactance is inductive below resonance, while the dipole impedance is capacitive, and vice versa. Thus, the off-resonance mismatch to the feedline is reduced.

However, the analysis which follows reveals some facts which will probably come as a distinct surprise to many amateurs, and may cause those who are using the coaxial dipole to contemplate replacing it. The facts are, one, whatever increase in bandwidth is obtained solely by the two coaxial stub sections inside the dipole, the same bandwidth can be obtained by using a simple wire dipole of the same outside diameter, but having an external shunt stub (equivalent to the internal stubs) connected directly across the dipole input terminals as shown in fig. 1D. Stuffing the stubs inside the radiator does nothing except to provide a convenient place to hide them. This is because the stub currents flowing on the inner side of the coaxial outer conductor are completely separate from the antenna currents flowing on the outside, and the outside antenna currents are unaffected whether the conductor is the outer portion of a coaxial cable, or simply a solid conductor.

Secondly, the amount of bandwidth improvement actually obtainable using the shunt-stub technique depends directly on the relationship between the values of the conductance term of the dipole admittance and the characteristic impedances of both the feedline and the shunt-stub lines. This relationship, which will be explained, involves conversion between equivalent series and parallel circuits. It limits feedlines to those having impedance values,  $Z_c$ , within a range whose lower limit is well above those commonly used (50 or 75 ohms). The stub lines must have  $Z_c$  values in the range from five to ten ohms, which are practically unattainable.

These requirements warrant an explanation which will follow shortly. But first, for the reader who is using a coaxial dipole fed with a fifty-ohm transmission line, how about trying an experiment which will prove that the stubs don't provide the heralded broadbanding? Measure and record the vswr at regular frequency inter-

vals across the entire band. Then open the center conductor of the coaxial sections between the two dipole halves at point A in fig. 1E, and replace the antenna to the original height. Now remeasure the swr at the same frequency points and prepare for a shock. I predict that you will find an insignificant difference between the two sets of swr readings.

### control of mismatch by R and X

To utilize frequencies in any part of a band, antennas are operated off resonance (except at one frequency).

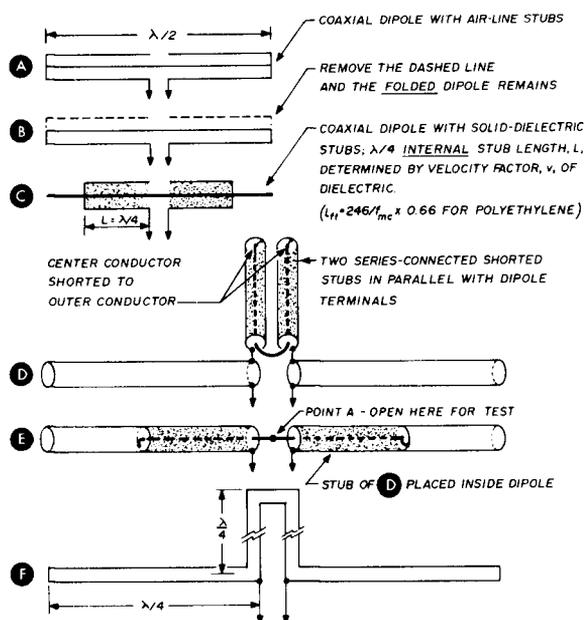


fig. 1. Reactance compensation in coaxial and folded dipoles results from reactance contributed by shorted stub sections. Coaxial dipole with air-line stubs at (A) reduces to a folded dipole (B). Each half of the folded dipole, and the internal portion of each coaxial section in the coaxial dipole (C), form a resonant quarter-wavelength stub. The same bandwidth can be obtained with a simple dipole which has the same outside diameter by using an external shunt stub across the feedpoint (D). Placing the stubs inside the dipole at (E) does not change bandwidth performance. The equivalent configuration is shown at (F).

When operated off resonance we know that the dipole antenna impedance,  $Z_d$ , contains both resistance,  $R$ , and reactance,  $X$ . To obtain zero mismatch at resonance, we know that the line impedance,  $Z_c$ , must equal the antenna load impedance,  $Z_d = (R + jX)$ , which is  $R + j0$ . To obtain minimum mismatch (which can't be zero) off resonance, the line impedance,  $Z_c$ , must equal the absolute value, or magnitude of the load impedance,  $|Z_d|$ , i.e.

$$Z_c = |Z_d| = \sqrt{R^2 + X^2}$$

A feedline having an impedance which will vary the same as  $|Z_d|$  over the desired frequency range does not exist. Therefore a compromise must be found which will now be discussed.

As seen in table 1 of appendix 1, for a value of line impedance which equals load impedance,  $|Z_d|$ , the

mismatch is smaller when  $X$  is low and  $R$  is high; mismatch is zero for a load impedance of  $R + j0$ . We know that the magnitude of the dipole impedance,  $|Z_d|$  rises *above* its resonant impedance on *both sides* of resonance because of the off-resonant reactance component which appears in the dipole impedance (fig. 2). I will show later in the analysis that, when applying the stub-compensation technique, the reactance of the stub shunting the dipole *tends* to cancel the off-resonant dipole reactance.

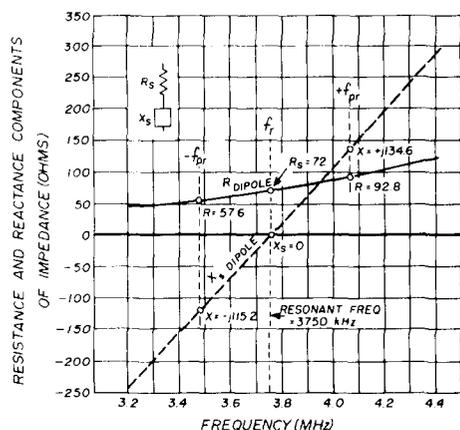


fig. 2. The series resistance,  $R_s$  and reactance,  $X_s$  components of uncompensated dipole impedance versus frequency. Values shown here are for a half-wavelength thin-wire dipole in free space.<sup>11</sup>

In our stubbing operations the following relationship between equivalent series and parallel circuits is of great importance.

When a series circuit containing both resistance and reactance is shunted with a reactance of the opposite kind, the absolute value of the circuit impedance  $|Z|$  is increased. However, in applying the technique of shunt-stubbing to thin half-wavelength dipoles, the transformation between series and parallel circuits appears to have been ignored in amateur literature and applications. The impact of ignoring this important relationship is evident when you see that, while the shunt reactance of the stub is *cancelling* the dipole reactance, the stub reactance simultaneously raises the series-circuit resistance in the *resulting parallel circuit*.

Therefore, even though the effective reactance in the load impedance is lowered by the stub reactance, the resulting increase in resistance increases the magnitude,  $|Z|$ , of the load to values which are even higher than those of the off-resonant impedance of the dipole alone. Thus you have simply exchanged a mismatch caused by reactance for a similar mismatch caused by the increased resistance.\* These relationships are illustrated in the following example:

Consider an 80-meter dipole antenna at a height yielding a resonant impedance,  $Z_d$ , of  $55 + j0$  ohms at 3750 kHz. At 200 kHz below resonance (3550 kHz)

the impedance  $Z_d$  is  $50 - j90$  ohms. Here  $|Z_d| = 103$  ohms, and the mismatch is 5.04:1 on a 50-ohm line (see appendix 2 for calculation method). Since stubbing is a shunting operation, we now examine the equivalent parallel circuit. The component values of the equivalent parallel circuit are  $R_p = 212$  and  $X_p = -117.8$  ohms. If the capacitive 117.8 ohms were entirely cancelled, the new load impedance would be  $212 + j0$  ohms, and the mismatch would be reduced only to  $212/50 = 4.24:1$ .

Note that the poor swr improvement is because the resistance has been raised from 50 to 212 ohms. However, the situation is even worse if the reactance compensation is performed with RG-58/U stubs generally found in amateur coaxial dipoles. Two 50-ohm RG-58/U stubs in series, resonant at 3750 kHz, yield an inductive shunting reactance of 1190.9 ohms at 3550 kHz. If they are shunted across the above parallel circuit of  $R_p = 212$  and  $X_p = -117.8$  ohms, the resulting values are  $R_p = 212$  and  $X_p = -130.7$  ohms. The equivalent series impedance is now  $58.4 - j94.7$  ohms,  $|Z_d| = 111.3$  ohms, and the mismatch is 4.9:1. Obviously neither of these two mismatch reductions is worthwhile.

However, a stub can provide broadbanding if it is properly engineered. The approach is clarified if we recall how mismatch is produced by a constant value of  $|Z_d|$  when its components  $X$  and  $R$  vary if line impedance,  $Z_c$ , is nearly identical to dipole impedance,  $|Z_d|$ : low mismatch when  $X$  is low and  $R$  is high, as shown in appendix 1, table 1. However, in the example above the dipole impedance  $Z_d = 55 + j0$ , and the line impedance,  $Z_c = 50$  ohms, are nearly identical *at resonance*. Thus the mismatch is lowest at resonance:  $Z_d/Z_c = 55/50 = 1.1:1$ . But as we depart from resonance the minimum obtainable mismatch increases for either of two reasons: The uncompensated dipole impedance,  $|Z_d|$  becomes increasingly higher than the line impedance,  $Z_c$ , or the parallel-circuit resistance,  $R_p$ , becomes increasingly higher than the line impedance. These reasons explain why, in the example, so little mismatch reduction is obtained with stubbing, even with the reactance entirely cancelled. In other words, if there is a substantial difference between the line impedance and the absolute magnitude of the load impedance, it makes little practical difference in the amount of the resulting mismatch whether the load is predominantly resistive or reactive.

On the other hand, as will be shown later, you can reduce the mismatch (using stubs) over a limited frequency range by choosing a line impedance,  $Z_c$ , intermediate between the extreme values of the compensated dipole impedance encountered over the frequency range of interest. Since the magnitude of the complex

\*A typical article contributing to the misunderstanding on this point, by failing to appreciate the fundamental reactions resulting from *parallel-connected circuit elements*, may be found in 73 Magazine, June, 1973, page 80 (John Schultz, W2EEY, "The Double-Coaxial Antenna"). The author's statement that a 50-ohm feedline must be used to feed coaxial-dipole antennas further illustrates his lack of appreciation for the actual principles involved.

dipole impedance rises off resonance (and is raised still further by the shunt compensation), the line impedance required to reduce off-resonance mismatch must be higher than that which yields the best match at resonance. Thus we must accept a compromise in the match at resonance in exchange for an improvement in match at frequencies off resonance.

Because our control over the conductance values for high-frequency dipoles of any practical length and length-to-diameter ratio is limited by nature, the rela-

external stub is used, or from 5 to 10 ohms each for two stubs *in series*. In typical amateur coaxial-dipole configurations series-connected stubs of RG-8/U or RG-58/U present such high reactance, they are incapable of providing any significant compensation, even if the feedline impedance is of the proper value to obtain *optimum* improvement. Thus two fundamental parameters — low feedline impedance and high stub impedance — cause the typical amateur version of the coaxial dipole to fall short of its goal. The ineffectiveness of these parameters is illustrated in the 80-meter example discussed earlier.

Although this entire situation may seem a bit incredible, the facts are supported explicitly in the published works of Kraus (W8JK),<sup>4</sup> Everitt,<sup>5</sup> Jordan,<sup>6</sup> Coleman,<sup>7</sup> Borton (W9VMQ),<sup>8</sup> and others, in addition to my own experiments and the analysis which follows.\* In view of this, how do we account for the apparent success of the coaxial dipole as claimed by so many happy users? There are probably several reasons. First, how many of those happy users performed the test described earlier to obtain a true comparison between the same dipole with and without the coaxial feature? Probably very few, if any. If not, how many amateurs know the *absolute* accuracy of their swr indicators in the *actual* 4:1 or 5:1 swr range? Many indicators give erroneous readings in this range, far *lower* than the true value, resulting in an indication of a wider bandwidth than actually exists.

Secondly, the apparent bandwidth improvement claimed by those using the coaxial dipole with stubs built from 50-ohm cable and fed with a 50-ohm feedline includes the cumulative effects of additional phenomena which are overlooked without realizing that an insignificant amount of improvement is actually contributed by the coaxial configuration itself.

If we assume the swr values presented by Charles Whysall are accurate, they seem to show acceptable results obtained with his Double-Bazooka antenna.<sup>1</sup> However, his design includes *two* broadbanding features which contribute simultaneously — the coax stubs plus capacitive loading of the dipole end sections using two-wire ladder line extending beyond the coaxial portion to obtain a full half-wavelength radiator. This type of multi-wire construction increases dipole capacitance and decreases inductance in the same way as increasing the radiator diameter. It can be shown that this type of loading provides a greater contribution to the increased bandwidth than the coaxial feature, yet Whysall makes no mention of any analysis or experiment performed to determine the *amount of bandwidth* contributed separately by each feature; he simply states that the effective reduction of length-to-diameter ratio provided by the ladderline contributes to a lowered radiator Q.

This is not intended as a criticism of his method of obtaining more bandwidth, or of his article, which con-

\*My analysis and experiments were reviewed by QST's Associate Technical Editor, Gerald Hall, K1PLP, who performed a verifying experiment at the ARRL Lab. Result: The coaxial-dipole antenna has not been included in the *ARRL Antenna Book*.

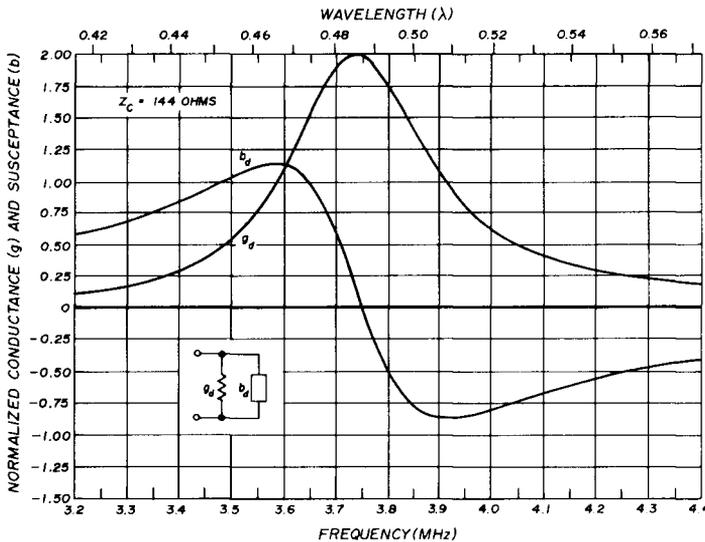


fig. 3. For ease of calculation, the impedance values of fig. 2 have been converted to admittance and plotted in terms of normalized conductance,  $g$ , and susceptance,  $b$ . Feedline impedance of 144 ohms yields optimum bandwidth, as discussed in the text.

tionships just described yield the following important facts concerning the feeding of coaxial-dipole antennas: A useful increase in bandwidth over a simple dipole can be obtained with a coaxially-stubbed *monopole* over a ground plane fed with a 50-ohm feedline because the antenna impedance at resonance is *less* than the feedline impedance. A similar bandwidth increase results when a thin, balanced-feed, half-wavelength coaxial dipole is fed with a feedline having a  $Z_c$  of 100 ohms or more. However, *no* significant increase in bandwidth can be obtained using the shunt-stub technique when a balanced, thin, half-wavelength coaxial dipole is fed with a 50-ohm transmission line, because the antenna impedance at resonance is usually near to, or greater than, the 50-ohm line impedance.

A further requirement for obtaining *significant* bandwidth improvement when using a feedline of suitable impedance is that the shunting-stub reactance drops appropriately with deviation from anti-resonance to compensate the antenna reactance as it increases with deviation from resonance. This requires a stub with a low value of characteristic impedance which is difficult to attain. To satisfy this requirement, the analysis will show that the impedance of the stub-line must be in the range from 10 to 20 ohms if a single

tains valuable and pertinent information; it simply isn't correct to attribute the combined effect of *both* features to the coaxial feature alone because it's misleading to the uninitiated.

Since the mechanical construction of the coaxial dipole is not simple, another purpose of this article is to help you to understand what is actually happening so you can reorient your design approach toward a construction method which will yield increased bandwidth performance. Antennas which meet this requirement include the multi-wire, fan-shaped, bow-tie dipole mentioned earlier, invented by Philip S. Carter of RCA in 1937 to obtain the bandwidth necessary for television.<sup>9</sup> Since the beginning of television broadcasting millions of TV receiving antennas have used the Carter bow-tie configuration, and in 1955 it was suggested for 80-meter use by Camillo and Purinton,<sup>10</sup> and again in 1975 by Borton.<sup>8</sup> Additional information on the fan dipole has also been published by Meier.<sup>7</sup>

### coaxial dipole principles

In this section we will examine broadbanding principles using stubs under four different conditions. The first two will provide useful bandwidth improvement, while the third and fourth illustrations will provide negligible improvement.

For the analysis to be realistic it will be centered around a half-wavelength dipole which has the physical characteristics of a typical amateur coaxial-dipole antenna, as shown in **figs. 1C** and **1E**. Since the characteristic impedances of both the feedline and the shunt-stub line are critical factors in controlling bandwidth, I will first show how to determine the value of feedline impedance which will yield the maximum possible dipole bandwidth with a given mismatch, or *swr*, and the impedance required of the shunt-stub line. Next, for comparison, I will determine the bandwidths obtainable (and the stub-line impedances required) when using feedlines of 100 and 50 ohms, respectively. Finally I will show graphically how to assess the bandwidth performance with 50-ohm feedline and 50-ohm stubs.

Since the parallel-circuit relation of the two stubs with respect to the dipole terminals is sometimes difficult to perceive, I will also show why the shorted stub lines are actually in shunt with the input terminals in *both* types of dipoles. Since I will be discussing circuit elements connected in shunt, or parallel, it is convenient to use the less familiar terms of conductance *G*, and susceptance, *B*, (components of admittance, *Y*,) in addition to the somewhat more familiar resistance, *R*, and reactance, *X*, components of impedance, *Z*. Since conductance and susceptance are the reciprocals of *parallel-circuit* resistance and reactance, respectively, they permit the use of direct algebraic addition of the component values associated with each of the parallel-connected elements to determine the total value of the combination. Handling susceptances in this way simplifies the understanding of reactance compensation, especially in the graphical representation in the illustrations.

As an aid to understanding the relationship between equivalent series and parallel circuits, if the series com-

ponents of impedance are represented by  $R_s$  and  $X_s$ , and the parallel components by  $R_p$  and  $X_p$ , then

$$R_p = \frac{R_s^2 + X_s^2}{R_s} \quad X_p = \frac{R_s^2 + X_s^2}{X_s}$$

$$\text{while} \quad G = \frac{R_s}{R_s^2 + X_s^2} \quad B = \frac{-X_s}{R_s^2 + X_s^2}$$

The series resistance and reactance components of the *free-space*, uncompensated, thin-wire dipole impedance versus frequency are plotted in **fig. 2**. This graph shows an impedance of  $72 + j0$  ohms<sup>11</sup> at resonance.\* However, since the effect of elements added in *parallel* with the antenna is best shown on an admittance diagram, the impedance values have been converted to admittance and replotted in **fig. 3** in terms of *normalized* conductance, *g*, and susceptance, *b*. The normalizing technique will be explained presently. The fundamental relationship between dipole conductance, feedline impedance, and bandwidth will now be described for conditions which yield the maximum possible bandwidth.

As a point of departure, we decide on a maximum practical value of mismatch, or *swr*, which can be tolerated over the band of interest. We will identify this value by either "swr limit," or "mismatch limit." We will define the band of interest, or bandwidth, as the difference between the frequency extremes where the mismatch limit is reached. As is well known, maximum bandwidth is obtained in the conventional, uncompensated, coax-fed dipole when the feedline impedance,  $Z_c$ , closely matches the antenna impedance,  $Z_d$ , at resonance. However, as I pointed out earlier, to increase bandwidth we must accept a mismatch at resonance in exchange. In fact, I will show that for any *swr* limit we may select, we obtain maximum bandwidth by deliberately causing the mismatch to attain the selected limit at resonance. We cause the mismatch to reach the limit at resonance by choosing the line impedance,  $Z_c$ , higher than the dipole resonant impedance,  $Z_d = R_d + j0$ , by the ratio equal to the desired mismatch limit. Thus to obtain maximum bandwidth for any *swr* limit, the line impedance,  $Z_c$ , must be  $Z_c = R_d \times swr_{\text{limit}}$ , where  $R_d$  is the value of the dipole resistance at resonance. We will use a mismatch limit of 2 for this entire discussion. Thus the proper line impedance,  $Z_c$ , for feeding a 72-ohm

\*A free-space dipole was chosen for illustrating the shunt-stub broadbanding principle because its resistance and reactance components of impedance are precisely known. It also avoids complicating the presentation with the effects of mutual coupling with the ground-reflected dipole image at different heights above the ground. Impedances and bandwidths obtained with actual earth-oriented dipoles will therefore differ slightly from the values presented here. The bandwidth of an uncompensated 80-meter dipole at typical heights of  $0.25\lambda$ , or less, with a 50-ohm feedline will be slightly wider than that of the free-space dipole because the resistance of the earth-oriented dipole at resonance is reduced from 72 ohms to some value closer to 50 ohms, due to the mutual coupling with its image. However, the percentage bandwidth *improvement* obtained when using shunt stubs with earth-oriented dipoles will not differ significantly from that presented herein using the free-space dipole data.

stub-compensated dipole to obtain maximum bandwidth over 2:1 swr limits is  $Z_c = 72 \times 2 = 144 \text{ ohms}$ .

I will now explain the normalizing procedure and conversion between resistance and conductance, which we will be using in the analysis which follows. An impedance,  $Z$ , is normalized by dividing it by the line impedance  $Z_c$ , to which it is being referenced; it is indicated by the lower case,  $z$ . In our example the normalized resonant-dipole impedance  $z_d = r_d + j0 = R_d/Z_c = 72/144 = 0.5$ . Conductance,  $G$ , is the reciprocal

similarly the minimum dipole impedance,  $z_d$ , at resonance equals 0.5, as seen in fig. 4A.

Since maximum  $g_d$  occurs at resonance this establishes the center frequency. The line impedance chosen establishes the band edges of the mismatch limit at the frequencies on either side of resonance where  $g_d$  equals the reciprocal of the mismatch limit (where  $g_d = 0.5$ ). Application of this rule in the analysis will be presented shortly. However, it can be seen in fig. 4 that this relationship between  $Z_c$  and  $g_d$  is chosen for the com-

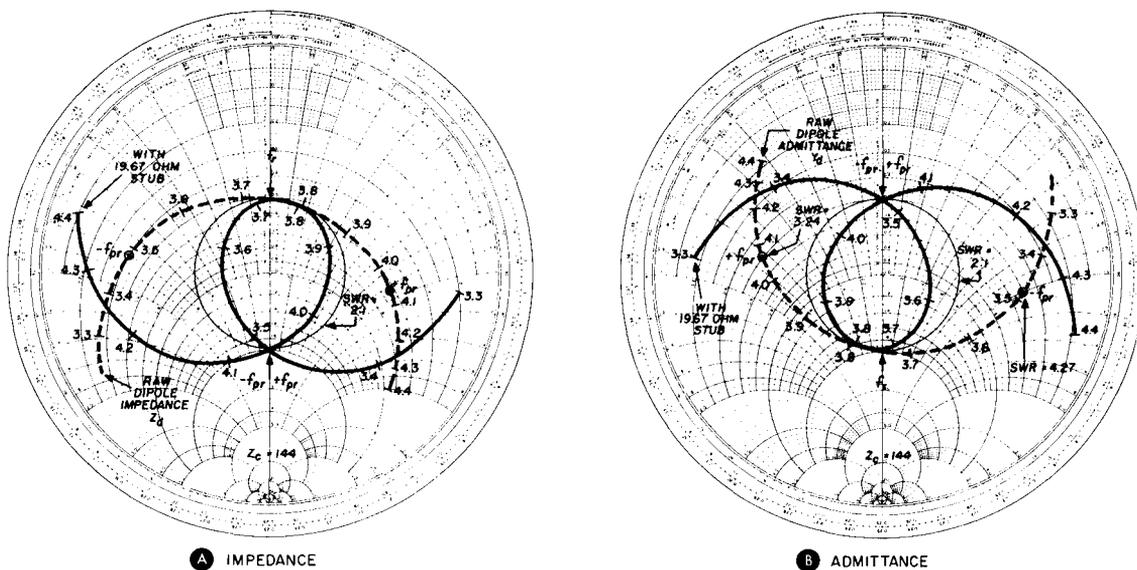


fig. 4. Smith chart plots of normalized impedance (A) and normalized admittance (B) from 3.3 to 4.4 MHz for both uncompensated and stub-compensated dipoles, based on the use of a 144-ohm feedline. Selection of 19.7 ohm stubline impedance is discussed in text.

of resistance,  $R$ , so  $G_d = 1/R_d = 1/72 = 0.0139 \text{ mhos}$  (13.9 millimhos). Normalized conductance,  $g_d = Z_c \times 1/R = Z_c \times G$ . Thus the normalized resonant dipole conductance,  $g_d = 144 \times 1/72 = 2.0$ .

These relations are sometimes best appreciated when displayed on Smith charts, because, in general, plots appearing on a Smith chart represent the normalized values of impedance or admittance. Figs. 4A and 4B show Smith chart plots of the normalized dipole impedance,  $z_d$ , and admittance,  $y_d$ , respectively; they show conditions both with and without stub compensation. Because of their reciprocal relation these impedance and admittance plots are seen to be mutually inverted. The circle marked "swr = 2:1" encloses all impedances (or admittances) which give rise to mismatch values less than the selected 2:1 limit. These plots will be explained later on.

Since our analysis will be using admittance parameters, the following rule is convenient for determining maximum bandwidth obtained with stub matching in relation to dipole conductance, line impedance, and mismatch limit: The optimum line impedance,  $Z_c$ , must be chosen (as explained above) so that the normalized maximum dipole-conductance value,  $g_d$ , is equal to the mismatch limit. The maximum conductance,  $g_d$ , equals 2 at the dipole-resonant frequency,  $f_r$ , as seen in fig. 4B;

compensated dipole to yield an identical mismatch value at the center frequency and at the band edges.

Fig. 4 also shows that selecting the line impedance,  $Z_c$ , at 144 ohms gives rise to the 2:1 limiting mismatch at resonance, and places the normalized uncompensated dipole-impedance (or admittance) locus on the graph so it intersects the 2:1 swr-limit circle at resonance ( $f_r$ ). The importance of this line-impedance selection will be more fully appreciated after an explanation of the reactance-cancelling action. However, it can be seen that placing the uncompensated impedance (or admittance) locus on the graph as just described allows the maximum length (frequency range) of the locus to be warped inside the swr-limit circle as the result of stub compensation. Note that although the mismatch reaches the swr limit at both band center and band edges (because the compensated locus passes through the swr-limit circle at these points), the mismatch is less than the limit everywhere between the center and the edges. This is because all impedances represented by the stub-warped locus lying inside the swr-limit circle give rise to mismatches that are less than 2:1.


The importance of selecting proper line impedance is further emphasized in fig. 10. Observe the dramatic reduction in frequency range of dipole impedances warped into the swr-limit circle using 100- and 50-ohm

lines shown in **fig. 10**, in contrast with the range obtained with the optimum 144-ohm line (**fig. 4**). The impedances plotted in **fig. 10B** illustrate the ineffectiveness of stub compensation when using 50-ohm feedline, with either an optimum stub, or 50-ohm RG-58/U stubs. The frequency range of impedances moved into the swr-limit circle with compensation is nearly the same as with no compensation. Thus with 50-ohm feedline, the only conceivable purpose a stub can serve is to enlarge the antenna profile as an announcement to the neighbors, "here is a ham, a potential source of RFI."

This early comparison of the plots in **figs. 4** and **10** was simply a preliminary view of the results obtained by examining the four broadbanding conditions using stub-reactance compensation. So we will now return to the explanation of how these results were obtained. It is

the mismatch value to the 2:1 limit. The normalized compensated-dipole resistance  $r_d$ , at the band edges is 2.0, as previously stated, and shown in **fig. 4A**. Thus the real resistance at the band edges equals  $r_d \times Z_c = 2 \times 144 = 288$  ohms. This reemphasizes that the resistances 72 ohms (at the center frequency) and 288 ohms (at the band edges) yield the selected 2:1 swr limit when they terminate the optimum 144-ohm feedline. Note that this value of line impedance, which yields the maximum bandwidth with a 2:1 swr, is centered between 72 and 288 ohms; it is thus the geometric mean value between the resonant, band-center dipole resistance and the band-edge circuit resistance. With these values and procedures established, we can delve into the operation of the shunt-stub configuration to see how the reactance compensation is effected.

**fig. 5.** Normalized admittance parameters of a half-wavelength, shunt-compensated dipole. Conductance,  $g_d$  and susceptance  $b_d$  of the dipole itself are the same as in **fig. 3**. Since the stub susceptance,  $b_s$ , tunes out the dipole susceptance,  $b_d$ , at the upper and lower parallel resonant frequencies  $-f_{pr}$  and  $+f_{pr}$ , the resultant susceptance  $b_{res}$  is zero at these frequencies.

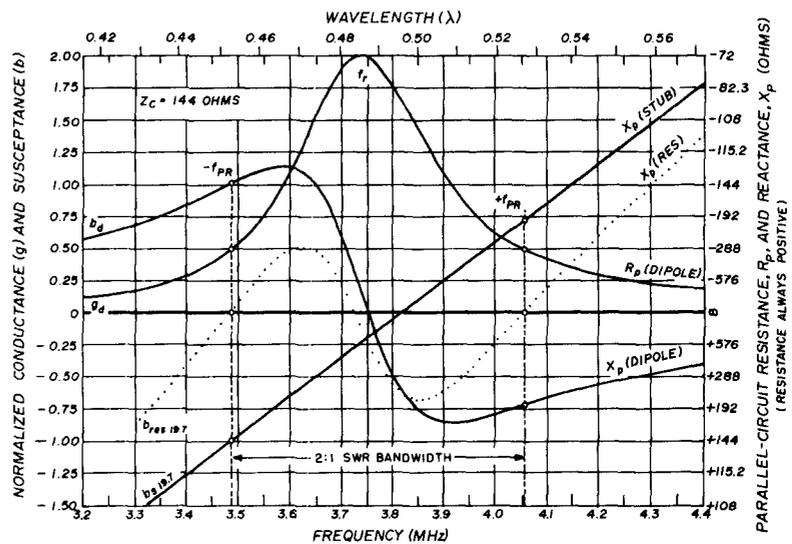

convenient to use a graph containing dipole admittance data as a worksheet in determining the stub parameters and the bandwidth obtained through compensation using various feedline and stub combinations. We will use the Smith admittance graph of **fig. 4B** as a worksheet a little later, but we will now use the rectangular-coordinate graph of **fig. 5**, because it affords graphical construction advantages that assist in clarifying the principles of stub matching. **Fig. 5** replots **fig. 3**, the dipole conductance,  $g_d$ , and susceptance  $b_d$  (normalized to the optimum 144-ohm line), plus other parameters which will be explained as we proceed.

Using **fig. 5**, the band edges of the 2:1 mismatch are determined from the dipole conductance curve,  $g_d$ , by finding the frequencies on each side of resonance (shown at  $f_r$ ) where the normalized conductance is 0.5 (the reciprocal of the mismatch limit 2.0). We then find a shunt stub of proper impedance to completely cancel the dipole susceptance,  $b_d$ , simultaneously at both of these frequencies. As seen in both **figs. 4B** and **5**, complete cancellation of dipole susceptance at each band-edge frequency leaves a normalized, pure conductance of 0.5 at both of these frequencies, as required to reduce

### shunt stubs

Referring now to **fig. 1F**, you can see the terminals of the half-wavelength dipole (shortened to resonance) connected in parallel with a shorted quarter-wave stub transmission line. It is well known that the impedance at the input terminals of a shorted quarter-wavelength line of any characteristic impedance,  $Z_c$ , is a pure resistance of a very high value. Thus, at the resonant frequency,  $f_r$ , the stub connection has a negligible effect on the 72-ohm dipole impedance. However, at frequencies below resonance both the dipole and shorted stub line become electrically shorter, and the dipole becomes capacitive, while the stub line becomes inductive. Due to the parallel connection the inductance of the stub line tends to cancel the capacitance of the dipole.

Conversely, at frequencies above resonance the dipole impedance becomes inductive and the stub line becomes capacitive so a similar compensation is again obtained. Unfortunately, the compensation is far from perfect because, although the dipole and stub susceptances are of opposite polarity, they are not equal nor do they change at the same rate. You can see this in **fig. 5** which shows how the dipole susceptance,  $b_d$ , varies with fre-

quency in contrast to the stub susceptance shown by the straight line,  $b_s$ . The resultant susceptance remaining from the imperfect compensation equals the sum,  $b_d + b_s$ , shown in the curve  $b_{res}$ . This resultant susceptance,  $b_{res}$ , combined with the dipole conductance,  $g_d$ , will yield the locus of the compensated-dipole admittance in fig. 4B, and the corresponding impedance locus in fig. 4A.

Still referring to fig. 5, if you look far enough above dipole resonance you will find a frequency where the dipole and stub susceptances are equal and opposite, and a perfect susceptance compensation is obtained because this is the higher of the two band-edge frequencies at which the stub line was selected to cancel the dipole susceptance. These equal and opposite susceptance values,  $b_d = -0.725$ , and  $b_s = +0.725$ , are seen at points on the ordinate line which intersects the dipole conductance curve at  $g = 0.5$ , and the frequency scale at  $+f_{pr}$  ( $f_{pr}$  = parallel-resonant frequency). Since the stub susceptance,  $b_s$ , tunes out the dipole susceptance,  $b_d$ , at this frequency, the resultant susceptance,  $b_{res} = 0.0$ , and parallel resonance is established. (These values may also be seen in fig. 4B.) From network theory we know that when parallel resonance is obtained by cancelling dipole reactance with a shunt-stub reactance of the opposite sign, then the relatively-low value of series dipole resistance is converted to the higher value of its equivalent parallel-circuit resistance component.

Thus the impedance at the antenna terminals is a pure resistance of 288 ohms for an swr of 2.0 as stated previously. Fig. 2 shows the raw (uncompensated) dipole impedance at this frequency to be  $Z_d = 92.8 + j134.6$  ohms ( $|Z_d| = 163.5$  ohms). This impedance would yield a 3.24:1 swr on the 144-ohm line in the absence of the stub. However, the equivalent parallel-circuit components are  $R_p = 288$  and  $X_p = +198.6$  ohms, but with the susceptance cancelled, leaving the 288 ohms of pure resistance as shown in both figs. 5 and 6.

Similarly, a second parallel-resonance frequency,  $-f_{pr}$ , will be found below the dipole resonant frequency where the dipole conductance again equals 0.5. This can

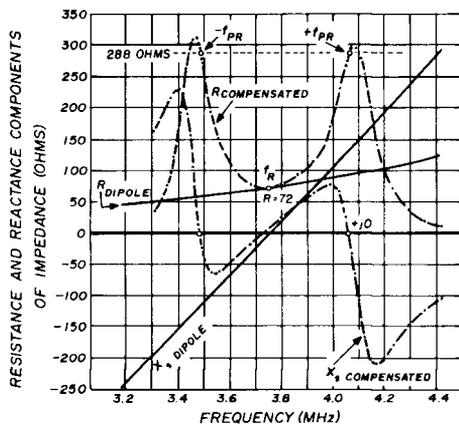


fig. 6. Resistance and reactance components of compensated and uncompensated half-wavelength antennas. Reactance is cancelled at the upper and lower parallel-resonant frequencies  $+f_{pr}$  and  $-f_{pr}$  leaving a resistive component of 288 ohms.

be seen in figs. 4B and 5. This is the lower band-edge frequency at which the stub was selected to cancel the dipole susceptance. The susceptance values at this frequency are  $b_s = -1.0$ , and  $b_d = +1.0$ , while the raw dipole impedance shown in fig. 2 is  $Z_d = 57.6 - j115.2$  ohms, ( $|Z_d| = 128.8$  ohms) for an swr of 4.27:1 without the stubs. The equivalent parallel-circuit components are

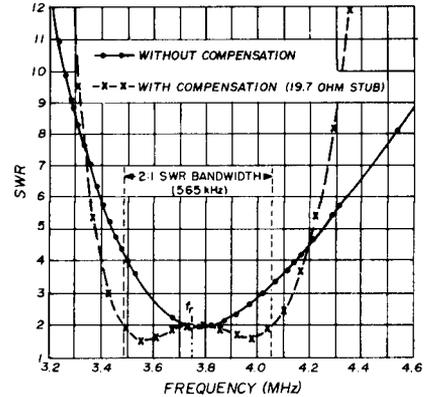


fig. 7. Swr vs frequency for compensated and uncompensated dipoles fed with a 144-ohm feedline. Characteristic impedance of compensating stub is 19.7 ohms.

$R_p = 288$  and  $X_p = -144$  ohms, and as at  $+f_{pr}$ , with susceptances and reactances cancelled, the circuit impedance is again  $288 + j0$  ohms for an swr of 2.0:1.

The procedure for calculating the precise value of the shunt-stub line impedance,  $Z_c$ , which cancels the dipole susceptance at both band-edge frequencies, from the slope of the stub susceptance line  $b_s$ , in fig. 5, requires more space than is available here, but sufficient accuracy will be obtained by using the procedure outlined in appendix 3. However, the  $Z_c$  value for this slope is 19.7 ohms and must be divided by two if two stubs are used in series.

We know the mismatch and impedance values at the band center and at the band edges. So we now want to determine impedance and mismatch in the frequency range between the band center and the edges. Susceptance,  $b_{res}$ , (and reactance) are present in this frequency range, because the stub provided complete susceptance cancellation only at the band-edge frequencies. Determining impedance and mismatch in this range is simplified by using the Smith admittance chart of fig. 4B to calculate graphically the effect of the stub compensation. While we see conductance and susceptance components of admittance plotted separately in fig. 5, these components are plotted together in a single continuous locus in the locus of the uncompensated dipole admittance,  $y_d$ , on

fig. 4B. Plotting the results of these additions yields the locus of the stub-compensated dipole admittance. Corresponding values of impedances are found by simply inverting the plots on the admittance graph (fig. 4B); we thus have plots of the equivalent impedances, as shown in fig. 4A. To show how this works, the normalized, uncompensated dipole admittance is seen to be  $0.5 -$

of the stub to "pull" or warp the  $0.5 - j0.725$  point on the uncompensated dipole admittance locus to the new, compensated admittance point,  $0.5 + j0$ . Going to the corresponding point in fig. 4A, the admittance-impedance inversion yields the expected normalized impedance of 2.0. The band-edge point used in this example was chosen for simplicity, but the same proce-

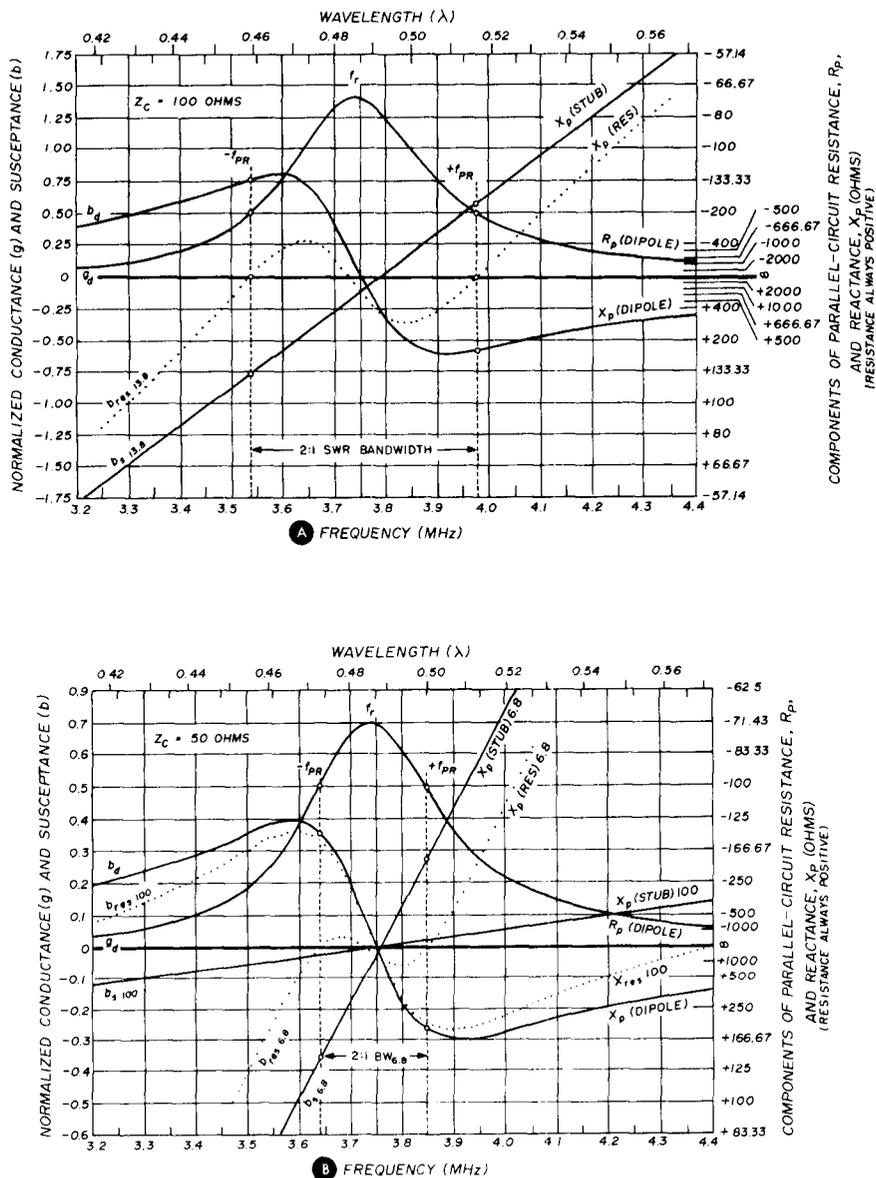


fig. 8. Normalized admittance parameters for uncompensated and compensated half-wavelength dipoles fed with 100-ohm (A) and 50-ohm (B) feedlines. Conductance,  $g_d$ , and susceptance,  $b_d$ , are for the uncompensated case. Stub susceptance,  $b_s$ , and resultant susceptance,  $b_{res}$ , are also shown. The optimum stub susceptance for the 50-ohm case ( $b_s = 6.8$  ohms) gives maximum swr bandwidth.

$j0.725$  at the upper band-edge frequency,  $+f_{pr}$ . From fig 5 the stub susceptance,  $b_s$ , is  $+j0.725$  at  $+f_{pr}$ . Returning to fig. 4B, we add these dipole and stub susceptances graphically: Following the arrow line along the  $g = 0.5$  circle, we move point  $+f_{pr}$  clockwise for a distance of 0.725 units of normalized conductance, to the chart center where  $b = 0$ . This move represents the capability

of the stub to "pull" or warp the  $0.5 - j0.725$  point on the uncompensated dipole admittance locus to the new, compensated admittance point,  $0.5 + j0$ . Going to the corresponding point in fig. 4A, the admittance-impedance inversion yields the expected normalized impedance of 2.0. The band-edge point used in this example was chosen for simplicity, but the same proce-

sure may be used to convert any point on the uncompensated dipole admittance locus to determine the corresponding compensated value. The concept of shunt-stub compensation will now be further clarified by a brief review of some relationships between equivalent series and parallel circuits which form the basis for our operations. These relationships

were stated earlier in the mathematical expressions for converting between series and parallel circuits. This review which follows describes those expressions:

1. Provided  $Q$  is greater than 1, the component value of a parallel-circuit resistance,  $R_p$ , is higher than its corresponding series-circuit value,  $R_s$ .
2. When a series circuit containing resistance,  $R_s$ , and reactance,  $X_s$ , (an antenna) is shunted by a pure reactance of the opposite kind (a stub), the following changes result:

- a. The resistance,  $R_p$ , and the conductance,  $G$ , components of the equivalent parallel circuit remain constant;
- b. The reactance component,  $X_p$ , of the equivalent parallel circuit is increased, and the susceptance,  $B$ , is decreased.
- c. The series-circuit resistance,  $R_s$ , is increased, and as the value of the shunting reactance (the stub) is changed in the direction toward cancellation of the net reactance, the series-circuit resistance,  $R_s$ , continues to rise until the circuit becomes parallel resonant. At this point the series-circuit resistance,  $R_s$ , becomes equal to the parallel-circuit resistance,  $R_p$ .\*

In view of these relationships, it is important to remember that parallel-circuit resonance exists at both band-edge frequencies because the stub and dipole susceptances cancelled each other to zero. The pure resistance of 288 ohms at the dipole terminals at the band-edge frequencies has been raised to this value because it is the *parallel-circuit resistance* value of the uncompensated dipole impedance, which at both of these frequencies is simply the reciprocal of dipole conductance.

Let's now look at the effect of stub compensation on the separate series resistance,  $R_s$ , and reactance  $X_s$ , components of the dipole impedance over the entire frequency range extending somewhat beyond the band edges. To observe this effect the dipole conductance and *resultant* susceptance components from fig. 5 are converted into their equivalent series resistance and reactance components of impedance, then plotted in fig. 6 along with dipole resistance and reactance values plotted from fig. 2 for direct comparison with the original, uncompensated dipole impedance components. Note the remarkable change in both the resistance and reactance components which resulted from a change in susceptance *only* — the dipole conductance remained *unchanged* by the stub compensation.

In addition to displaying the bandwidth in the Smith charts of figs. 4A and 4B, the bandwidth obtained with shunt-stub compensation of the half-wavelength dipole

\*The basis of the hairpin match used in Yagi arrays. The 20-ohm (approximate) driven element is shortened to introduce enough series capacitance to raise the equivalent parallel-circuit resistance to 50 ohms. The resulting series capacitive reactance (-24.5 ohms) is then cancelled by the hairpin shunt-stub inductance, leaving the feedpoint impedance at  $50 + j0$  ohms.

in combination with the 144-ohm optimum-impedance feedline is also illustrated in fig. 7 by plotting the feedline mismatch versus frequency. (The mismatch values were computed from the dipole conductance and *resultant* susceptance values in fig. 5 using a technique applicable to pocket calculators described in appendix 2.) For comparison with the bandwidth of the uncom-

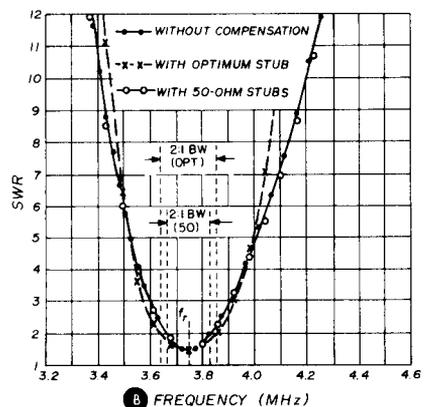
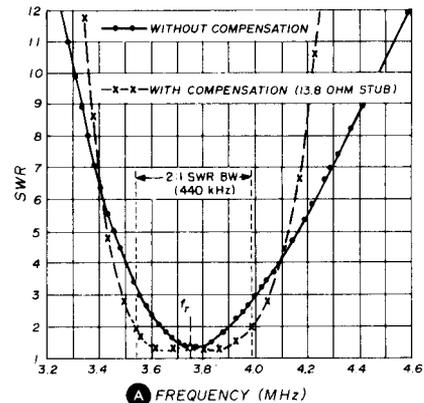


fig. 9. Swr vs frequency for compensated and uncompensated dipoles fed with 100-ohm (A) and 50-ohm (B) feedlines.


compensated dipole, the mismatch values for the uncompensated dipole were computed from the dipole impedance components in fig. 2 and plotted in fig. 7 along with the compensated values.

In contrast to the data shown in fig. 5 for a 144-ohm feedline, figs. 8A and 8B show the effects of using feedline impedances of 100 ohms and 50 ohms, respectively. These are less suitably related to the dipole impedance values encountered over the frequency range than those using the optimum-bandwidth 144-ohm feedline impedance. These graphs show the corresponding normalized conductance and susceptance relationships in the same manner as the 144-ohm case shown in fig. 5. Figs. 9A and 9B illustrate the bandwidths obtained using 100- and 50-ohm feedlines, both with and without compensation. As in the Smith-chart plots of figs. 10A and 10B, they show clearly how the bandwidth drops as the line impedance is reduced from the 144-ohm optimum to 50 ohms.

From this graphical data you can see why the bandwidth decreases as feedline impedance is reduced. We compare resistance data in **figs. 5, 8A and 8B** at the 2:1 mismatch band-edge frequencies, where the normalized dipole conductance is 0.5. It is seen that the parallel-circuit resistance component of the dipole impedance produces the 2:1 mismatch in each case of the three line impedances; the resistance at the 0.5 conductance point being equal to twice the line impedance. This mismatch-conductance relationship holds for any value of feedline

susceptance available with a 100-ohm stub, as obtained with two series-connected 50 ohm stubs made from RG-8/U or RG-58/U coaxial cable.

The low slope of this plot is a clue to its meager compensating capability, vividly emphasized by the almost negligible difference between the raw dipole susceptance,  $b_d$ , and its corresponding resultant susceptance  $b_{res100}$ . Here the uncompensated 2.33:1 mismatch at the  $-f_{Dr}$  point is reduced only to 2.28:1 with the 50-ohm stubs. The bandwidth increase over the

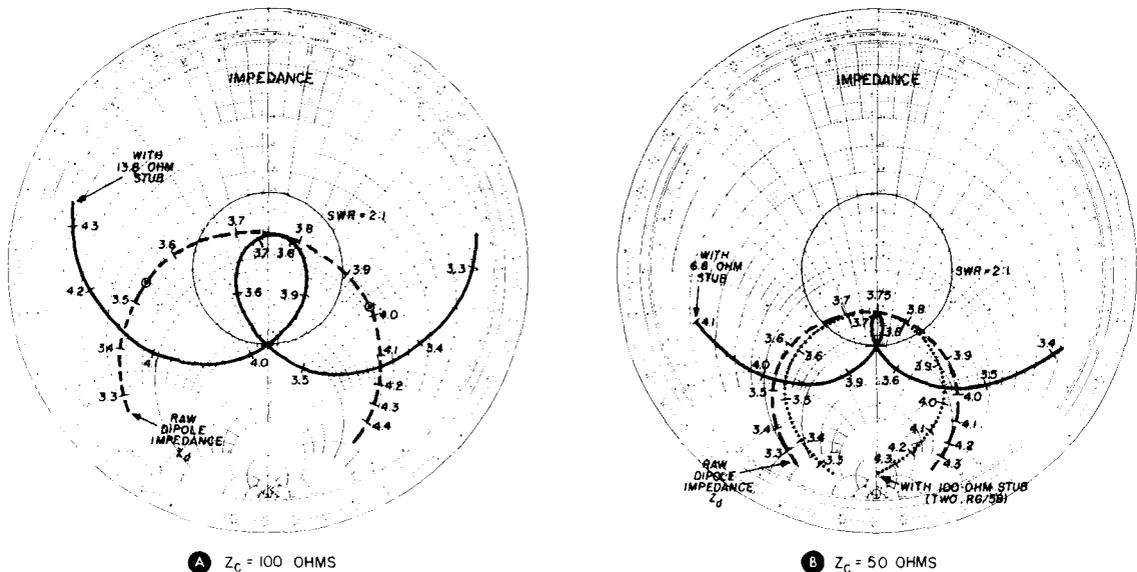

**fig. 10. Smith chart plots of normalized impedance for compensated and uncompensated half-wavelength dipoles fed with 100-ohm (A) and 50-ohm (B) feedlines. Optimum stub impedance for 100 ohm case is 13.8 ohms; optimum stub impedance for 50-ohm feedlines is 6.8 ohms.**

impedance. Therefore, because the parallel-circuit resistance decreases with the use of lower values of feedline impedance, the bandwidth decreases between the two frequencies where the values of equal resistance appear on either side of resonance. Since these dipole-resistance values determine the frequencies of the 2:1 mismatch points, this demonstrates that the maximum obtainable 2:1 bandwidth decreases as the feedline impedance is reduced from 144 ohms.

Let's return to **fig 8B** for a closer look at the 50-ohm feedline case. This graph contains susceptance plots of two different shunt stubs with 6.8 and 100 ohms impedance respectively, along with their corresponding resultant susceptance plots. The straight line labelled  $b_{s6.8}$  plots the susceptance of the stub which completely cancels the dipole susceptance at the 2:1 mismatch points, as shown in the corresponding resultant susceptance plot,  $b_{res6.8}$ . The uncompensated mismatches of 2.33:1 and the 2.34:1 at  $-f_{Dr}$  and  $+f_{Dr}$ , respectively, are thus reduced to 2:1. (Not a very significant reduction.) While the impedance of this shunting stub is  $Z_c = 6.8$  ohms, it requires a characteristic impedance of 3.4 ohms if two stubs are used in series (not a practical value of  $Z_c$ ). The bandwidth is increased from 165 kHz (no stub) up to 210 kHz. On the other hand, the plot labelled  $b_{s100}$  shows the compensating

no-stub, 165-kHz width is negligible; it is even too small to show graphically in **fig. 9B**. The Smith chart plot of **fig. 10B** verifies the disappointing performance of the coaxial dipole when it is fed with 50-ohm line — with either 6.8- or 100-ohm stubs.

This analysis of the 50-ohm feedline case, in addition to the mismatch graphs (**fig. 9B**) and the Smith chart impedance plots, clearly shows that there is no significant bandwidth improvement when feeding a coaxial dipole with 50-ohm feedline, especially when 50-ohm coax is used for the shunt-stub lines. Unfortunately, even the optimum 144-ohm line presents nearly insurmountable problems for amateur use. It is true that 144-ohm line could be built using two 72-ohm coax lines in a series, balanced relation — with the outer conductors tied together at both ends, and each inner conductor feeding one dipole half. This would be fine, except that at 80 meters the dipole resistance is usually less than 72 ohms. Unless we find a feedline having an impedance equal to *twice* the resonant dipole resistance,  $R_d + j0$ , the maximum 2:1 swr bandwidth will not be obtained. Another problem is that determining the optimum feedline impedance ( $Z_c = 2R_d$ ) is simply an academic exercise unless its entire 2:1 swr range of impedances is transformed to the corresponding nominal 50-ohm range required by most amateur transmitters. A

possible solution to this problem may be a broadband transformer described by Jerry Sevick, W2FMI,<sup>12</sup> but probably not without some loss in bandwidth. However, the most severe problem of all is the required low stub impedance — less than 20 ohms. This would require a balanced configuration of two series connected stubs, each less than 10 ohms. Their construction would involve an unwieldy combination of series-parallel quarter-wavelength sections of 50- and 75-ohm coax. Further, the positioning of such a kluge with respect to both its supporting members and the feedline presents additional complications which require more space to explain than is available here.

Since the mismatch values associated with the 50-ohm feedline case in fig. 9B and 10B are higher than those measured by many coaxial dipole users, it is tempting to assume that this analysis is incorrect. However, the following factors responsible for lower measured values should be kept in mind.

1. The mismatch values plotted here are those which appear at the antenna-feedline junction. Mismatch values measured at the input end of the transmission line will be lower than at the antenna because of line attenuation (the greater the attenuation, the lower the input mismatch).\*
2. In many cases swr indicators read lower than the true value.
3. The use of any additional broadbanding feature such as multiwire end loading, or larger radiator diameter when using RG-8/U coax as the radiator, reduces the inherent reactance which is developed, thereby lowering the mismatch.

Let's now consider WA9PIV's assertions concerning the gain and self-balun characteristics of the coaxial-dipole antenna. Antenna gain is obtained by adding the far-field radiations from each, separate element of any array consisting of more than one dipole element. The coaxial-dipole antenna is not an array, but a single dipole element, and thus has the same radiation pattern and the same gain as a simple dipole.

Regarding the self-balun characteristics, the bazooka formed by the shorted quarter-wavelength coaxial skirt surrounding a coaxial feedline, as shown in fig. 11, does indeed achieve a balanced-to-unbalanced (balun) action, resulting in cancellation of radiation from the feedline; this would otherwise occur as a result of current on the inside surface of the outer conductor flowing around the top and down the outside of the outer conductor in an admittance path which is in parallel with that half of the dipole fed by the outer feedline conductor. The term "bazooka" cannot be applied to the coaxial-stub configuration within the dipole. As a result, the balun function of the bazooka has been wrongly and unwittingly attributed to the coaxial feature of the coaxial-dipole antenna. The coaxial-dipole antenna is strictly a

balanced-input device, and as stated in the opening paragraph, it is the same as the simple wire dipole, except for its impedance and bandwidth characteristics.

WA9PIV's further assertion that all harmonics are rejected by the coaxial dipole is not true because only the even harmonics are rejected. The reason is that the shorted stubs are multiples of a half-wavelength on even multiples of the fundamental frequency, and odd multiples of a quarter-wavelength on odd multiples of the fundamental. Thus a short circuit is reflected across the

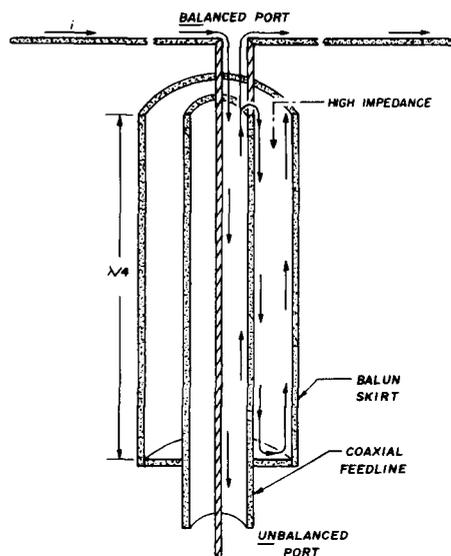


fig. 11. True bazooka formed by shorted quarter-wavelength coaxial skirt surrounding a coaxial feedline provides balanced to unbalanced transformation. This is not the case for the mis-named "bazooka antenna" which is strictly a balanced-input antenna. The high impedance (low admittance) appearing across the open end of the  $\lambda/4$  resonant cavity of the bazooka shown here impedes current flow into the cavity, thus admitting practically all of the feedline current into the low impedance (high admittance) of the dipole. Removal of the coaxial skirt increases the admittance of current along the outside of the feedline.

input terminals to energy appearing at frequencies of the even-numbered harmonics, while an open circuit is reflected at odd-harmonic frequencies. As a result, harmonic energy is not suppressed at frequencies which are odd-harmonics of the fundamental frequency. These principles also hold true for the folded dipole.

Incidentally, WA9PIV specifies dimensions for his coaxial dipole which make the stubs resonant at a frequency higher than the resonant frequency of the dipole. This simply shifts both band edges to frequencies slightly higher than those occurring when the stubs and dipole both resonate at the same frequency. However, regardless of his statement that mismatch is not greater than 1.5:1 over the entire 3.5 to 4.0 MHz band using his stub dimensions, the overall bandwidth is substantially the same as that shown in figs. 9B and 10B.

It is clear, in listening on the amateur bands, that many amateurs, in their attempts to reduce swr, are afflicted with the coaxial-dipole syndrome. It is also clear that many are still placing unwarranted emphasis

\*Instructions for calculating the corresponding mismatches appearing at opposite ends of the transmission line, for any value of line attenuation, are presented in appendix 4.

on low swr, usually for the wrong reasons. However, response to my series of articles on this subject<sup>13</sup> indicates that many amateurs are learning that when low-loss feedlines are used (which is generally the case on the high-frequency amateur bands), a low swr on the feedline does not save any significant amount of power, nor does it noticeably enhance the level of the radiated signal.

The only significant benefit of a low standing-wave ratio over an entire amateur band is the ease of matching your transmitter output to the *input* to the feedline anywhere in the band. Obtaining an acceptable impedance match is not too difficult on 40 meters, but on 80 meters the line input impedance varies so widely across the band (unless unknown losses reduce the mismatch at the input), it is possible to match the transmitter directly to the line only over a very limited frequency range. Unfortunately, hope for curing this ailment by using the coaxial dipole has been shattered, and anyone dispensing it as a cure should study this analysis.

Following are two suggested prescriptions for an effective-cure of the mismatch problem. As a partial cure try a dose of either W1SX's<sup>10</sup> or W9VMQ's<sup>8</sup> bow-tie dipole configuration mentioned earlier. This antenna provides some improvement over the thin-wire dipole, though not quite enough to permit coupling the average transmitter directly to the feedline across the entire 80-meter band. For a more complete cure, review the QST "Reflections" series (especially parts VI and VII),<sup>13</sup> and discover why the mismatch at the antenna-feedline junction that can't be cancelled by the stubs of the coaxial dipole *can be* compensated by conjugate matching at the input terminals of the feedline. Once this is understood, you can live with a three-, four-, or five-to-one swr on the feedline, and still make your transmitter happy by using a tuner to transform whatever impedance appears at the line input to 50 ohms of pure resistance at the tuner input at *any* frequency in the band.

Recommended out-patient treatment for this cure: One hour of operating per day for three or four days using this technique. This treatment will provide sufficient therapy to warrant discharge of the patient, and to guarantee a complete and permanent cure of the coaxial-dipole antenna syndrome.

### references

1. Charles Whysall, W8TV (now K4WZ), "The Double-Bazooka Antenna," *QST*, July, 1968, page 38.
2. Lynn Pequignot, WA9PIV, mimeographed data sheets distributed by the author.
3. *The ARRL Antenna Book*, any edition, see chapter entitled "Fundamentals."
4. John Kraus, *Antennas*, McGraw-Hill, New York, 1950, pages 434-441.
5. Everitt and Anner, *Communication Engineering*, 3rd Edition, McGraw-Hill, New York, 1956, pages 492-498.
6. Edward C. Jordan, *Electromagnetic Waves and Radiating Systems*, 1st Edition, Prentice-Hall, 1950, pages 473-479, 493, 534-539.
7. Bennett, Coleman, and Meier, "The Design of Broad-Band Aircraft Antenna Systems," *Proceedings of the IRE*, October, 1945, pages 682-700.

8. Dwight Borton, W9VMQ, "80-Meter Bow-Tie Antenna," *ham radio*, May, 1975, page 56.
9. Philip S. Carter, "Simple Television Antennas," *RCA Review*, October, 1939, page 168 (Carter Patent no. 2,175,253).
10. Charles C. Camillo, W9GZJ, and Richard M. Purinton, W1SX, "A Broadband Antenna for 75 Meters," *QST*, June, 1955, page 11.
11. Ronald W. P. King, *Theory of Linear Antennas*, Harvard University Press, Cambridge, Massachusetts, 1956, page 176.
12. Jerry Sevick, W2FMI, "Simple Broadband Matching Networks," *QST*, January, 1976, page 20.
13. Walter Maxwell, W2DU, "Another Look At Reflections," *QST*, Part I, April, 1973; Part II, June, 1973; Part III, August, 1973; Part IV, October, 1973; Part V, April, 1974; Part VI, December, 1974; Part VII, August, 1976, page 15.

## appendix 1

The magnitude of an impedance mismatch may be determined as swr from the relationships  $R/Z_c$  or  $Z_c/R$  *only* when the load is a pure resistance. When the load is a complex impedance,  $Z_L = R + jX$ , the exact mismatch may be determined in terms of the complex reflection coefficient (Eq. 1 of reference 13, part III) from

$$\bar{\rho} = \rho \angle \theta = \frac{Z_L - Z_c}{Z_L + Z_c} \quad (1)$$

The value of swr may then be obtained from the expression

$$swr = \frac{1 + \rho}{1 - \rho} \quad (2)$$

Swr, however, cannot be determined from any relationship between the feedline impedance,  $Z_c$ , and the simple absolute magnitude,  $|Z|$ , of the complex load impedance. This is evident from table 1 where it can be seen that different values of load impedance,  $Z_L$ , can have the same magnitude,  $|Z| = 50$  ohms, yet produce different values of mismatch on a given feedline.

Furthermore, it is improper to specify impedance as a pure number such as 50 ohms (as it is often heard on the amateur bands) unless it is in some way implied to be resistive, as when referring to the characteristic impedance of a low-loss transmission line. The proper way to specify impedance is to either use the complete polar form (magnitude and angle) or the equivalent rectangular form ( $R + jX$ ) as shown in table 1.

table 1. Different swr values on a 50-ohm transmission line as a result of terminating the line with various values of impedance,  $Z$ , (different  $R$  and  $X$ ) which have the same magnitude,  $|Z| = \sqrt{R^2 + X^2} = 50$  ohms.

load impedance, Z			swr value (50 ohm line)
polar form  Z  angle	rectangular form R X		
50 $\angle 0^\circ$	50 + j0		1.00
50 $\angle 25.84^\circ$	45 + j21.79		1.59
50 $\angle 36.9^\circ$	40 + j30		2.00
50 $\angle 53.1^\circ$	30 + j40		3.00
50 $\angle 66.42^\circ$	20 + j45.83		4.79
50 $\angle 72.54^\circ$	15 + j47.7		6.51
50 $\angle 78.46^\circ$	10 + j48.99		9.90
50 $\angle 84.26^\circ$	5 + j49.75		19.95
50 $\angle 87.13^\circ$	2.5 + j49.94		39.98
50 $\angle 88.85^\circ$	1 + j49.99		99.99
50 $\angle 90^\circ$	0 + j50		$\infty$

## appendix 2

Another method for calculating the exact swr from  $R \pm jX$  (or  $G \pm jB$ ), developed by the author after a suggestion by W2KF, and derived from eq. 1 in appendix 1, is shown in the following steps:

1. Normalize by dividing the complex impedance (or multiplying the complex admittance) by the characteristic impedance of the transmission line,  $Z_c$ .

$$\frac{R \pm jX}{Z_c} = r \pm jx \quad (G \pm jB)Z_c = g \pm jb$$

Note that normalized values are in lower case letters.

2. Find the  $b$  term of the quadratic formula

$$\frac{b \pm \sqrt{b^2 - 4ac}}{2a}$$

using values of  $r$  and  $x$  (or  $g$  and  $b$ ) in the expression

$$b = \left( \frac{x^2 + 1}{r} \right) + r \quad b = \left( \frac{b^2 + 1}{g} \right) + g$$

3. Calculate the swr from the simplified quadratic formula

$$swr = \frac{b + \sqrt{b^2 - 4}}{2}$$

Note that the  $a$  and  $c$  terms of the complete quadratic formula in step 2 reduce to one during the derivation due to the normalizing procedure and can be ignored. The negative root of the discriminant

$$-\sqrt{b^2 - 4ac}$$

is also disregarded.

**Example:** Determine the swr generated on a 50-ohm transmission line by a load impedance of  $40 + j30$  ohms.

Normalizing:  $r + jx = \frac{40 + j30}{50} = 0.8 + j0.6$

Find the  $b$  term:  $b = \left( \frac{0.6^2 + 1}{0.8} \right) + 0.8 = 2.50$

Calculate the swr:  $swr = \frac{2.50 + \sqrt{2.50^2 - 4}}{2} = 2.000$

This is a very good example because the answer is exactly 2.0:1 with no fractional remainder. Other examples that give exact answers (50-ohm lines) are  $30 + j40$ , swr = 3.0:1; and  $80 + j90$ , swr = 4.0:1.

To show that different values of load impedance can yield the same swr, the following complex loads (50-ohm transmission line), will generate an swr of 2.6180:1 –  $25 + j25$ ,  $50 + j50$ ,  $100 + j50$ , and  $130 + j10$ .

### appendix 3

Use the following procedure to determine the approximate value of the characteristic impedance,  $Z_c$ , of a shunt-compensating stub line from the slope of the susceptance plot:

1. Let  $\theta$  equal the length in electrical degrees between  $-f_{pr}$  and  $+f_{pr}$ . Find  $\theta$  by determining the wavelength difference,  $\Delta\lambda$ , between  $-f_{pr}$  and  $+f_{pr}$ , then multiply by 360 degrees

$$\theta = (\Delta\lambda)360^\circ$$

2. Let  $X_{av}$  equal the average of the parallel-circuit dipole reactances appearing at  $-f_{pr}$  and  $+f_{pr}$  without regard for the sign.

3. The approximate impedance of the stub line can be found from

$$Z_c \approx \frac{X_{av}}{\tan(90^\circ - \theta)}$$

**Example:** Determine the impedance of the stub line from the  $b_s$ , susceptance plot in fig. 5 ( $-f_{pr} = 3490$  kHz,  $\lambda = 0.453$ ;  $+f_{pr} = 4055$  kHz,  $\lambda = 0.527$ ).

$$\Delta\lambda = 0.527 - 0.453 = 0.074$$

$$\theta = 0.074 \cdot 360^\circ = 26.64 \text{ degrees}$$

parallel-circuit reactances:  $-f_{pr}$  144 ohms  
 $+f_{pr}$  192 ohms  
 $X_{av}$  168 ohms

$$Z_c \approx \frac{168}{\tan(90 - 26.64)} = \frac{168}{\tan 83.34} = \frac{168}{8.56} = 19.62 \text{ ohms}$$

### appendix 4

The mismatch  $SWR_A$  at the antenna feedline junction is higher than the mismatch  $SWR_I$  measured at the input to the transmission line because of line loss. When one mismatch is known use the following procedure to calculate the unknown mismatch at the opposite end of the line. Let

$\rho_A$  = reflection coefficient at antenna (point A)

$\rho_I$  = reflection coefficient at input (point I)

$\alpha$  = line attenuation in dB (multiply dB per foot times length of the line in feet)

$r$  = decimal value of the output/input power-loss ratio of the feedline:

$$r = \text{antilog}_{10} \left( \frac{\alpha \text{ in dB}}{10} \right)$$

**Example:** If the line attenuation is 0.5 dB, what is the output/input power-loss ratio? (0.5 dB is expressed as a negative quantity since it is loss.)

$$r = \text{antilog}_{10} (-0.5/10) = 0.891$$

A. Use the following steps to calculate the mismatch at the antenna ( $SWR_A$ ) from an swr measurement at the input to the transmission line ( $SWR_I$ ).

1. Calculate  $\rho_I$  from  $SWR_I$   $\rho_I = \frac{SWR_I - 1}{SWR_I + 1}$
2. Calculate output/input power-loss ratio,  $r$ , from line attenuation,  $\alpha$
3. Calculate  $\rho_A$  from  $\rho_I/r$  ( $\rho_A$  is larger than  $\rho_I$ )
4. Calculate  $SWR_A$  from  $\rho_A$   $SWR_A = \frac{1 + \rho_A}{1 - \rho_A}$

**Example:** The input swr to a 120-foot RG-8/U feedline is 3.5:1 at 4.0 MHz. What is the swr at the antenna? (Attenuation of RG-8/U is 0.32 dB per 100 feet at 4.0 MHz so attenuation of 120 feet is 0.384 dB.)

$$\rho_I = \frac{SWR_I - 1}{SWR_I + 1} = \frac{3.5 - 1}{3.5 + 1} = \frac{2.5}{4.5} = 0.556$$

$$r = \text{antilog}_{10} \frac{-0.384}{10} = 0.915$$

$$\rho_A = \frac{\rho_I}{r} = \frac{0.556}{0.915} = 0.607$$

$$SWR_A = \frac{1 + \rho_A}{1 - \rho_A} = \frac{1 + 0.607}{1 - 0.607} = \frac{1.607}{0.393} = 4.093:1$$

B. Use the following steps to calculate the swr at the input of the transmission line ( $SWR_I$ ) from a mismatch measurement at the input to the antenna ( $SWR_A$ ):

1. Calculate  $\rho_A$  from  $SWR_A$   $\rho_A = \frac{SWR_A - 1}{SWR_A + 1}$
2. Calculate  $r$  from line attenuation,  $\alpha$
3. Calculate  $\rho_I$   $\rho_I = \rho_A \times r$  ( $\rho_I$  is smaller than  $\rho_A$ )
4. Calculate  $SWR_I$  from  $\rho_I$   $SWR_I = \frac{1 + \rho_I}{1 - \rho_I}$

**Example:** The swr at the input to an antenna is 5:1 at 4.0 MHz. What is the swr at the input of a 156.25 foot length of RG-8/U transmission line? (Attenuation of RG-8/U is 0.32 dB per 100 feet at 4.0 MHz so attenuation of 156.25 feet is 0.5 dB.)

$$\rho_A = \frac{SWR_A - 1}{SWR_A + 1} = \frac{5.0 - 1}{5.0 + 1} = \frac{4.0}{6.0} = 0.667$$

$$r = \text{antilog}_{10} \frac{-0.5}{10} = 0.891$$

$$\rho_I = \rho_A \times r = 0.667 \times 0.891 = 0.594$$

$$SWR_I = \frac{1 + \rho_I}{1 - \rho_I} = \frac{1 + 0.594}{1 - 0.594} = \frac{1.594}{0.406} = 3.926:1$$

ham radio

# differential keying circuit

Low-cost  
TTL logic devices  
are combined  
in a keyer design  
with optional  
weight control

An investigation of differential keying circuits in tube, transistor and relay form revealed that such circuits could be designed using TTL or cmos IC logic. Some IC multivibrators were found in the Texas Instruments *TTL Data Book*.<sup>1</sup> One was the SN 74123, which has two multivibrators in one package, and the other was the SN74121, which has only one. The SN74123 was chosen since this meant only one 16-pin socket, and the second multivibrator could be used for another function such as weight control.

## circuit description

Reference 2 indicated that the SN74121, SN74123-series inputs require a clamped threshold near ground or at a slightly negative voltage (about -1.2 volt). I selected a clamp at ground because otherwise another power-supply bias level would be necessary; this clamped threshold at ground was adequate for the keyer application.

Waveforms and a diagram of the circuit are shown in **figs. 1** and **2** respectively. By following these two illustrations, we can run through the operation of how the differential keying is formed. The NOR and NAND logic is necessary to develop the gating needed. An SN7402 was selected as the NOR gate (J or N type — the pin-out

is different for other types), and the SN7410 was selected as the NAND element simply because I had some left over from a previous purchase from Poly Paks (one of many sources for these devices). **Fig. 2** shows one of the four dual-input NOR gates used as an inverter and the clamp to ground for the input of the SN74123 (U1A-B). Both inputs are connected through a current-limiting resistor to a high logic level, thus producing a low at the output, which is very close to ground (0.8 volt or so). The input biasing by means of R1 also provides bias to my keyer output transistor switching stage.

When the keyer output goes to ground U3C output goes high and U1A, being connected for a positive trigger input, produces the inhibit pulse, P3, seen in **fig. 1A**. The completion of the keyer pulse, P1, results in a negative trigger, which is received by the second half of the SN74123, (U1B). Thus, U1B develops pulse P5. Pulses P2 and P3 are processed by NAND gate U2. The output conforms to NAND logic in that an output will occur only with like inputs (positive logic is used, so this means both the inputs must be high). Therefore pulse P3, being negative, inhibits the output during its time interval, and output pulse P4 is formed.

Now the gate pulse that will keep the oscillator on must be developed. This gate pulse is formed by adding the output of U3C with that of U1B (positive or Q output in this case). The final gate output becomes that shown by P6. The third NOR gate of the SN7402, U3B, is used for another inverter, so a positive pulse, P7, is generated.

## interface circuits

We now come to the all-important function of interfacing the developed logic pulses with the equipment being considered. Transistors Q2 and Q3 perform this interface and are general-purpose, high-voltage npn and pnp transistors needed for the hybrid interface between logic IC levels and the usual high bias levels of vacuum tubes. R7 provides limiting for the NOR load current, and Q2 base current. The positive output pulse, P7, switches Q2 on, which in turn switches Q3 on, and the

By Fred Griffie, W4IYB, 8809 Stark Road, Annandale, Virginia 22003

transmitter oscillator plate and/or screen receives its positive bias voltage.

Instead of using complete on-off switching of bias voltage or voltages, a resistor should be added between the positive bias and the oscillator circuit being controlled, so that the bias level is decreased but still allows low-level oscillation. When full positive bias is applied, the output increases to its normal level in a smooth transition from low to high levels rather than starting from zero oscillator output, which could result in transients. R8 limits Q3 base current and provides additional isolation should the transistors fail. The output switching transistor collector and emitter can be connected in various ways to satisfy the interface requirement of whatever circuit switching is needed.

The keying-pulse interface is made fairly easy by merely using the same type pnp transistor used in the gate interface and turning it on when the NAND gate output goes on (pulse-switches from a high positive level to a low-level ground). R6 provides the gate load and transistor base-current limiting, while Q1 switches the grid-block circuit to ground, thus keying the transmitter exciter and starting the pulse shaping process. The keying pulse is symmetrically located within the gate time interval and therefore performs the desired differential keying function. Normally, grid-block keying circuits are of a high-impedance level so that no further protection is needed should the transistor fail. If Q1 failed, the exciter would remain keyed to ground, but no harm would befall integrated circuit U2.

### weight control addition

If weight control is not included in the keyer (or if a bug or hand key is used), then another multivibrator, such as the SN74121, must be used with an additional NOR gate. In fact, the NOR gate used for forming the acceptance gate must be a three-input type (the SN7427 is available from most sources). The three-input NOR can also be used for the two-input requirement by merely connecting two of the three inputs together (see fig. 3).

The logic of these gate arrangements is most easily understood by describing the different timing waveforms again (see fig. 1B). Input pulse P1 is the keyer or hand-key output and turns off U3C when grounded or when the contacts are closed. This action increases positive

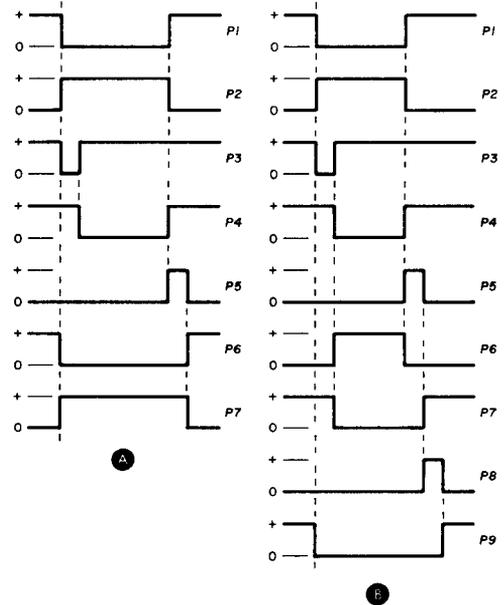


fig. 1. Timing waveforms of differential keyer logic with weight control included in keyer (A) and with weight control added (B).

pulse P2 from ground (about 0.8 volt) to about +3.4 volts. One-half of the SN74123 still forms the negative-going inhibit pulse, which forms the keyer output pulse delay, P3, by preventing any output from NAND gate U3A until all inputs are at a high level. The second half of the dual multivibrator U1B (SN74123) is connected to accept a negative trigger input, thus forming the weight-control pulse, P5.

The trailing edge of P5 triggers acceptance-gate pulse


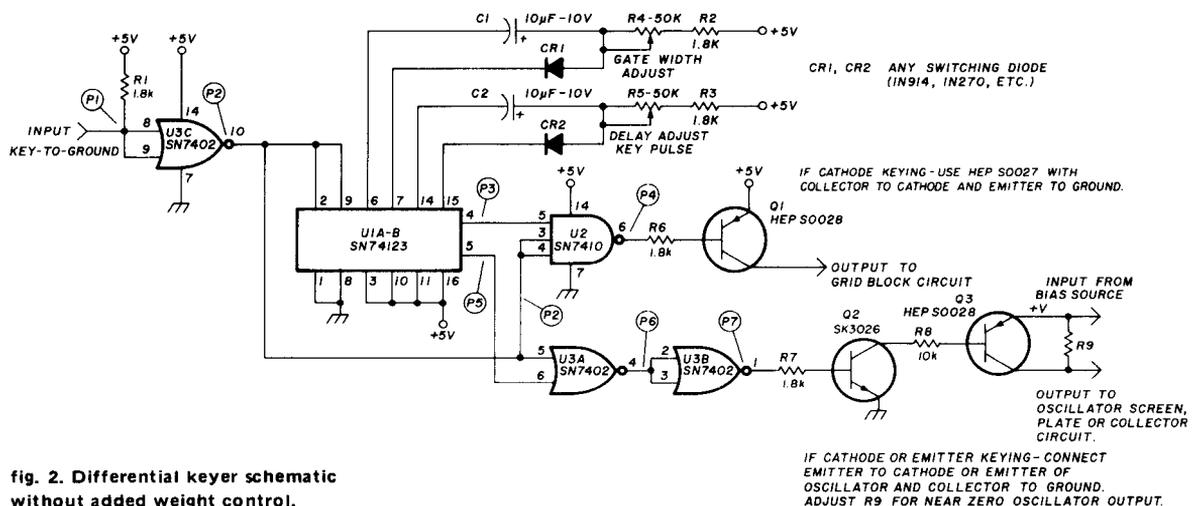


fig. 2. Differential keyer schematic without added weight control.

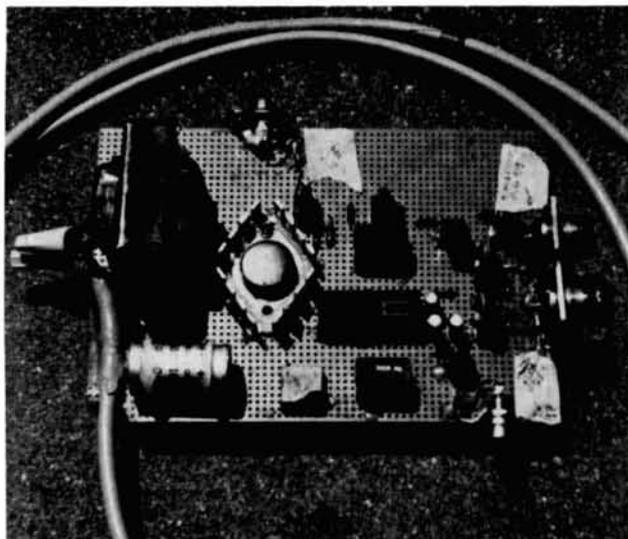

Component side of perf board showing general layout.

stretcher multivibrator U2 (SN74121) and forms P8. Now, P2, P5, and P8 are added by the three-input NOR gate, U4B, producing the required acceptance-gate pulse, P9, that will turn on the VFO or oscillator before and after the keying pulses have been completed (P5 and P6). Keying pulse P4 is inverted by U3B, forming P6, which is then added to the weight-control, multivibrator (U1B) output P5 by U4A, forming the desired keying-pulse interval, P7.

Note that the acceptance-gate interval, P9, is formed by the keying-pulse width, P2, the weight-control multivibrator output, P5, and the gate-extension pulse width, P8, such that any variation in the weight-control pulse also varies the gate acceptance interval, thus inadvertent extension of the keying pulse interval, P7, beyond the acceptance-gate interval, P9 is prevented. Such extension

of P7 would cause spurious radiation in the form of key clicks. Also, if any variation is desired, only the weight-control multivibrator time interval adjustment is necessary.

It may be found that when the speed is varied, the weight control may have to be changed slightly. Since exciter or transmitter keying characteristics are usually fixed and drive levels change with frequency, the weight control may have to be changed to obtain the same desired keying quality or characteristic (with class-C amplifiers).

The same low-to-high level interface transistor switching used in the differential key circuit without weight control is used here; however, U3B was required to allow the proper positive level input for U4A with respect to the keyer pulse, P4. U3B merely serves as an inverter by connecting all inputs together.

### construction

Nothing is critical in this circuit. Straightforward point-to-point insulated wiring was used. One rf decoupling capacitor was found necessary at the input of the differential keyer circuit (0.001  $\mu$ F ceramic). My glue gun came in very handy for strapping down sockets and components before wiring. The glue takes a minimum length of time to dry, but be careful about using the glue on temperature-sensitive components since it's initially very hot.

The power supply consists of a filament transformer rated at one ampere (much more than required), an LM309K regulator, and a bridge rectifier IC. All were mounted on the same board. The filter capacitor is a 1500  $\mu$ F 10V electrolytic. A zener diode would work as well as the LM309K and requires less space.

### alignment

Alignment was easily accomplished with the aid of an oscilloscope such as an EICO model 460. Alignment


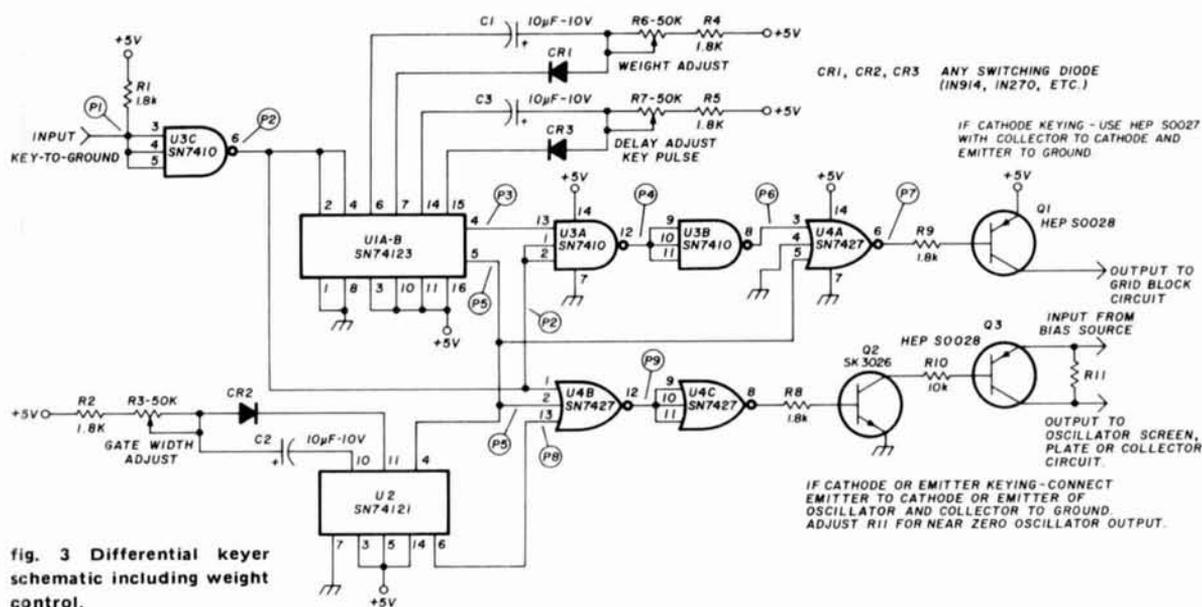


fig. 3 Differential keyer schematic including weight control.

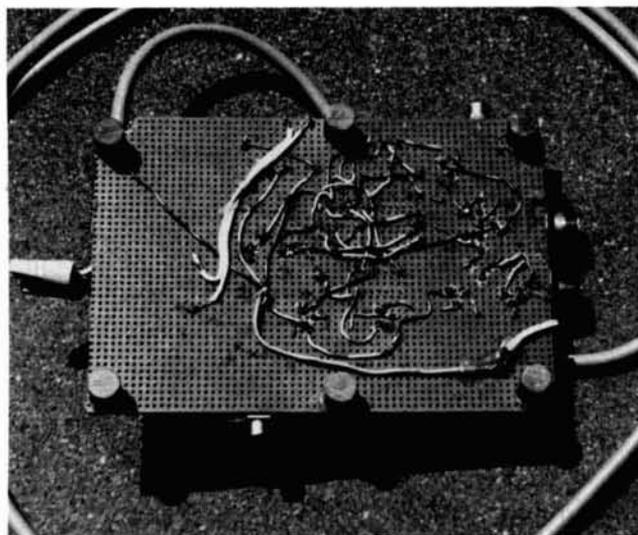would be almost impossible without an oscilloscope. My Johnson T/R switch has an rf output test point, which allows the transmitted wave shape to be observed when it's within the oscilloscope bandpass, otherwise the scope detector probe can be used and the envelope observed.



Underside of perf board showing point-to-point wiring.

Delay multivibrator U1A pulse width was adjusted by R5, fig. 2, until the front of the shaped pulse started to decay with near zero rise time, then R5 was backed off until the shaped pulse reappeared. This procedure was also used by varying R4 while observing the pulse trailing edge with respect to the acceptance-gate pulse-width stretcher multivibrator, U1B. These controls require no further adjustment, and the keyer weight control is used for any differences that may be experienced with varying code speeds.

If the weight-control logic is added the weight control multivibrator would be set at minimum pulse width, while the acceptance-gate multivibrator pulse width would be varied to eliminate any decay of the shaped-pulse trailing edge. The weight control can then be adjusted to produce the desired keying characteristic.

The circuit has worked well without any malfunctions. Incidentally, the TTL logic has bias limits. It will not work properly or will fail completely if the bias becomes greater than 5.5 volts. A bias value between 4.7 and 5 volts with good regulation by means of a zener or IC regulator device is recommended.

#### references

1. *The TTL Data Book for Design Engineers*, First Edition, Texas Instruments, Inc., Dallas, Texas 1973.
2. *Designing with TTL Integrated Circuits*, Texas Instruments, Inc., McGraw-Hill Book Company, New York, 1972.

ham radio

## KENWOOD HEADQUARTERS



TS-820  
160-10M TRANSCEIVER



TS-700A  
2M TRANSCEIVER



TS-520  
80-10M TRANSCEIVER



TR-7200A  
2M MOBILE TRANSCVR

TR-2200A  
2M PORTABLE TRANSCVR

PS-5  
AC/DC POWER SUPPLY



R-599D  
160-10M RECEIVER

T-599D  
160-10M TRANSMITTER

Request EDI Wholesale Catalog Today!

All Models of Kenwood Gear and Accessories  
Always Available at:


**ELECTRONIC DISTRIBUTORS, Inc.**

*Communication Specialists for over 37 years*

1960 PECK ST., MUSKOGON, MICH. 49441

TEL. (616) 726-3196 TELEX 22-8411

# Heathkit Transceivers

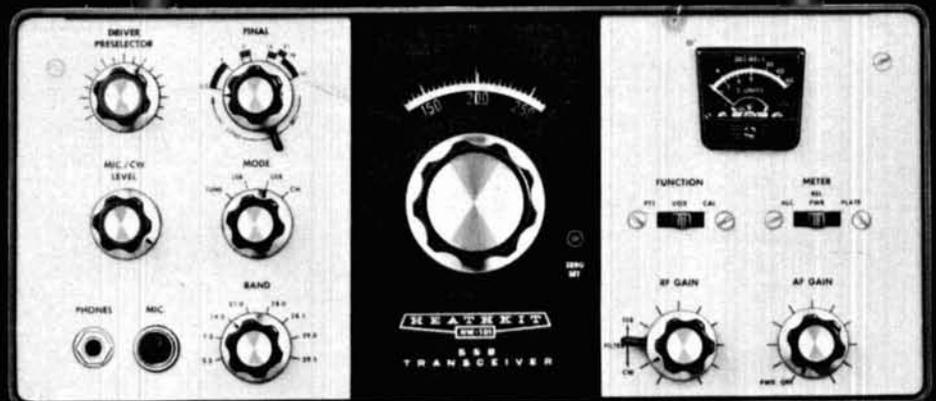

**FREE**



Read about these and all the other outstanding Heathkit Amateur Radio products in the NEW Heathkit Catalog. Yours FREE! Send coupon today!

Heath Company, Dept. 122-20  
Benton Harbor, Michigan 49022

# ...YOUR BEST CHOICE

THE SB-104. Acclaimed as the world's finest Amateur Transceiver. For features and operating convenience, for specifications and performance, you simply won't find a better transceiver than the SB-104. Completely solid-state, totally broadbanded, TRUE digital readout with resolution to 100 Hz! Instant QSY - choose the band, dial the frequency, select your mode and go - no more preselector, load or tune controls. The transmitter delivers 100 watts output and, for QRP'ers, a front panel switch selects 1 watt out. The signal is clean and strong, with harmonic and spurious radiation below 2  $\mu$ V, third order distortion down 30 dB and unwanted

THE HW-104. Broadbanded design for instant QSY at a new low price! Has the same outstanding features and specifications of the SW-104 above, but with calibrated dial and 3.5 MHz to 29.0 MHz amateur band frequency coverage. A built-in 100 kHz and 25 kHz calibrator assures dial accuracy to within 2 kHz, the dial is calibrated in 5 kHz increments with 15 kHz per knob revolution. The VFO uses the same basic circuitry as the SB-104 and

THE HW-101. A truly exceptional Amateur radio value. Has the features you NEED for operating ease, convenience and versatility. 180 watts input PEP, 170 watts input CW gives you the power you need for first-class operation. Receiver sensitivity is 0.35  $\mu$ V for 10 dB S+N/N (SSB) and selectivity is 2.1 kHz minimum at 6 dB down. Has a stable FET VFO; PTT and VOX with anti-trip; triple action level control. The smooth dial drive has a 36-1 ratio and a built-in 100 kHz crystal calibrator lets you accurately calibrate the dial at 100 kHz intervals. A four-function front panel meter

sideband suppression down 55 dB. Receiver sensitivity is 1  $\mu$ V for 10 dB S+N/N; selectivity is 2.1 kHz at 8 dB down. There's a 15 MHz WWV position on the bandswitch; 30 kHz per revolution spinner knob; tune button for loading linears; ALC/relative power/"S" meter and more. The SB-104 operates directly from a 12-volt electrical system; for fixed station operation, use the HP-1144 power supply.

KIT SB-104 .....\$669.95

Fixed Station Power Supply.

KIT HP-1144 .....\$89.95

Speaker and cabinet.

KIT SB-604 .....\$29.95

provides extremely stable operation with less than 100 Hz/hr. drift after warm-up. Operates from a 12-volt electrical system, use the HP-1144 power supply for fixed stations.

KIT HW-104 .....\$489.95

Speaker and cabinet.

KIT HS-1661 .....\$19.95

KIT HWA-104-1, 10-meter accessory for coverage to 29.7 MHz. ....\$16.95

shows signal strength, ALC transmit voltage, relative power output or final cathode current. Has full controls, inputs and outputs, full 80-10 meter amateur band coverage. Operates fixed station or mobile with power supplies below.

KIT HW-101 .....\$339.95

Fixed Station Power Supply.

KIT HP-23B .....\$57.95

Mobile Power Supply.

KIT HP-13B .....\$84.95

400 Hz CW Crystal Filter.

SBA-301-2 .....\$29.95

Prices and Specifications subject to change without notice.

Heath Company, Dept. 122-20  
Benton Harbor, Michigan 49022

Please send my FREE Heathkit Catalog. I am not  
on your mailing list.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

AM-336

HEATH

Schlumberger

# TTL IC tester

IC sockets  
too expensive?  
With this tester  
you can check ICs  
before soldering them  
into place

I can remember when you could plug a one-dollar vacuum tube into a ten-cent socket. The situation now seems to be reversed: a twenty-cent integrated circuit plugs into a socket costing anywhere from fifty cents to a dollar or more. When I was planning a construction project that would require 63 ICs, sockets were out of the question — just too darned expensive. This simple tester was then constructed so that each IC could be tested before it was soldered into place. The ICs shown were for the project mentioned above. Some could be deleted or other types added according to your favorites or the contents of your junk box.

## circuit description

Nine input stimuli are generated by feeding +5 volts through resistors R1 through R9 as shown in fig. 1. Each input stimulus is either a 1 (+5V) or a 0 (ground), depending on the position of its corresponding switch S1 through S9. The output states are indicated by lamps DS1 through DS6. If the lamp is ON, a 1 is indicated; OFF indicates a 0 state. Q1 through Q6 can be any npn transistor that will carry the 150-mA lamp current. I used some TO-5 germanium transistors removed from computer PC boards. An alternative output indicator circuit could be an LED with the proper current-limiting resistor in place of the transistor and lamp. The 7413 Schmitt trigger is used as a "de-bouncer," allowing a single pulse to be produced by manually depressing switch S11 (fig. 2). This pulse is used in testing JK flip-flops.

## construction

The test sockets and lamp drivers are mounted on a piece of perf board approximately 4½ x 2-3/8 inches

(114 x 60mm) (fig. 3). This board is mounted on 5/16-inch (8mm) spacers above an aluminum chassis, which is 4 x 5 x 1½ inches (101 x 127 x 38mm). All switches and lamps are mounted on the aluminum chassis, and resistors R1 through R9 are mounted underneath. The test sockets are wired in parallel; that is, all pins requiring a no. 1 input are connected together and to S1 and R1; all

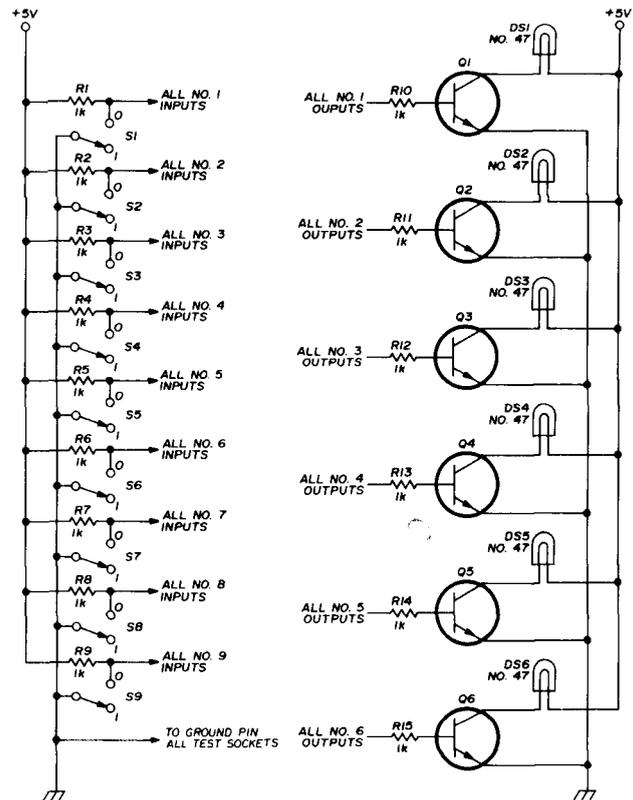


fig. 1. Schematic of the IC tester.

no. 2 inputs pins are connected together and to S2 and R2, etc. A 5-volt power supply at 1 ampere is required to power the IC tester. If you're careful not to light more than two lamps at a time, 0.3 ampere would be sufficient.

## operation

The diagrams shown in fig. 2 may be used as a guide when operating the tester. Perhaps, when testing JK flip-flops, it would also be advantageous to have the specifi-

By Kenneth H. Leiner, WA4LCO, 3254 Inverness Court, Orlando, Florida 32806

table 1. Logic matrix for selected ICs.

IC	S1	S2	S3	S4	S5	S6	S7	S8	S9	S10	S11	DS1	DS2	DS3	DS4	DS5	DS6
7400	1	1	1	1	1	1	1	1	NU	NU	NU	OFF	OFF	OFF	OFF	NU	NU
	1	0	1	0	1	0	1	0	NU	NU	NU	ON	ON	ON	ON	NU	NU
	0	1	0	1	0	1	0	1	NU	NU	NU	ON	ON	ON	ON	NU	NU
	0	0	0	0	0	0	0	0	NU	NU	NU	ON	ON	ON	ON	NU	NU
7402	1	1	1	1	1	1	1	1	NU	NU	NU	OFF	OFF	OFF	OFF	NU	NU
	1	0	1	0	1	0	1	0	NU	NU	NU	OFF	OFF	OFF	OFF	NU	NU
	0	1	0	1	0	1	0	1	NU	NU	NU	OFF	OFF	OFF	OFF	NU	NU
	0	0	0	0	0	0	0	0	NU	NU	NU	ON	ON	ON	ON	NU	NU
7404	1	1	1	1	1	1	1	1	NU	NU	OFF	OFF	OFF	OFF	OFF	OFF	OFF
	0	0	0	0	0	0	0	0	NU	NU	ON	ON	ON	ON	ON	ON	ON
7410	1	1	1	1	1	1	1	1	1	NU	NU	OFF	OFF	OFF	NU	NU	NU
	1	1	0	1	1	0	1	1	0	NU	NU	ON	ON	ON	NU	NU	NU
	1	0	1	1	0	1	1	0	1	NU	NU	ON	ON	ON	NU	NU	NU
	0	1	1	0	1	1	0	1	1	NU	NU	ON	ON	ON	NU	NU	NU
7473	0	1	0	1	1	1	1	1	NU	X	YES	OFF	ON	OFF	ON	NU	NU
	1	0	1	0	1	0	1	1	NU	X	YES	ON	OFF	ON	OFF	NU	NU
	X	X	X	X	0	0	1	1	NU	X	NO	OFF	ON	OFF	ON	NU	NU
	1	1	1	1	1	1	1	1	NU	X	YES	TOGGLE	TOGGLE	TOGGLE	NU	NU	
7476	1	0	1	0	1	1	1	1	NU	X	YES	ON	OFF	ON	OFF	NU	NU
	0	1	0	1	1	1	1	1	NU	X	YES	OFF	ON	OFF	ON	NU	NU
	X	X	X	X	1	1	0	0	NU	X	NO	ON	OFF	ON	OFF	NU	NU
	X	X	X	X	0	0	1	1	NU	X	NO	OFF	ON	OFF	ON	NU	NU
	1	1	1	1	1	1	1	1	NU	X	YES	TOGGLE	TOGGLE	TOGGLE	NU	NU	

X = Don't-care condition (1 or 0). NU = Not used. TOGGLE = DS1 and DS2 (DS3 and DS4) alternate with each S11 pulse.

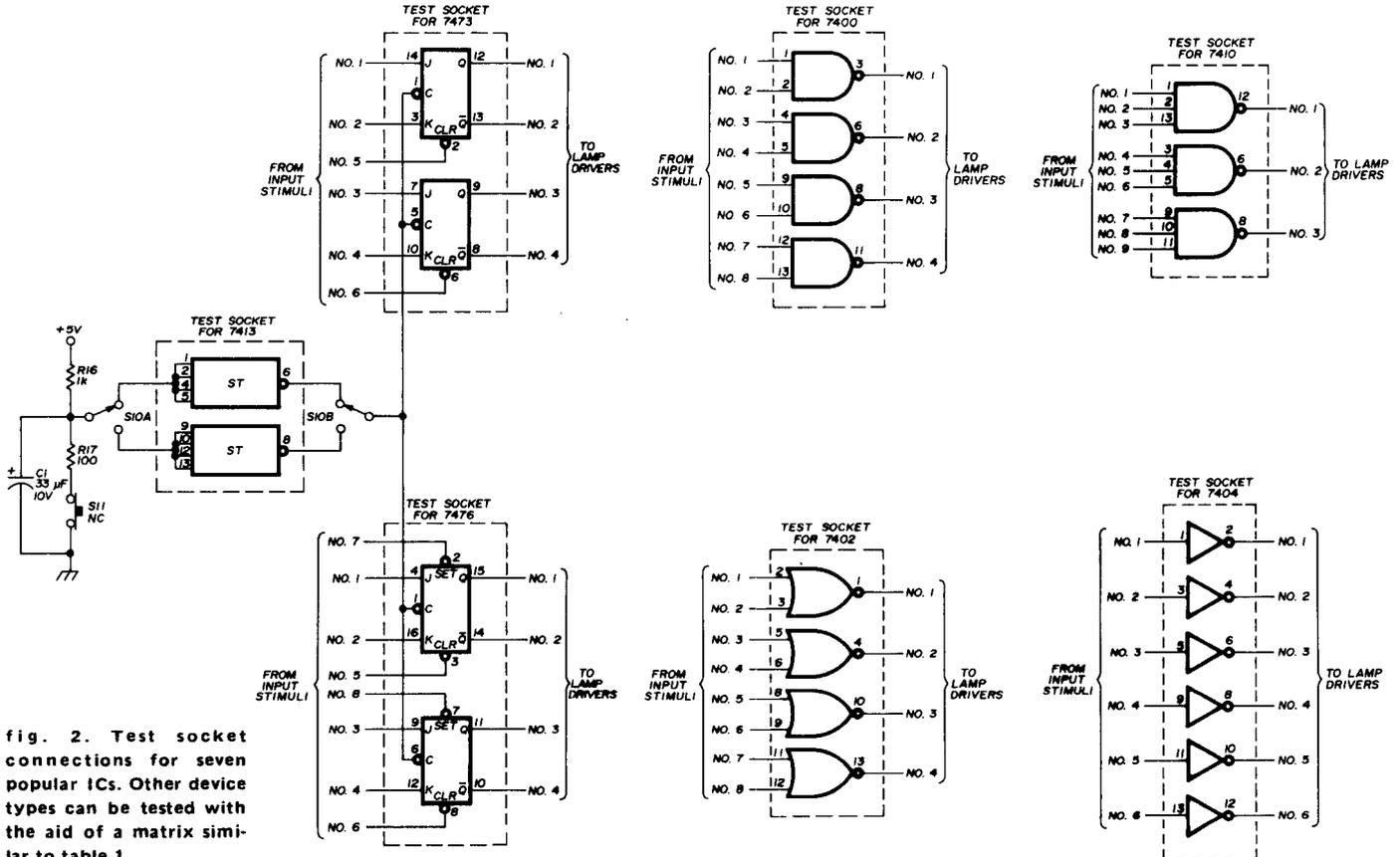


fig. 2. Test socket connections for seven popular ICs. Other device types can be tested with the aid of a matrix similar to table 1.

# ramsey electronics



**6 DIGIT  
LED CLOCK  
KIT  
\$22.95**

A SUPER QUALITY kit that features:

- Handsome extruded aluminum case in black, gold, silver, bronze or blue
- Large .33" bright LED display
- 12 or 24 hour readout format
- All parts included – no extras to buy
- Alarm version (12 hour only)

**\$24.95**

## 60 Hz TIME BASE KIT

Run any digital clock in your car, boat or airplane. Features zener regulation, output buffering, CMOS circuitry and small size. Kit includes all parts and instructions to hook up to any clock. **\$4.95 6/\$25.00**

**\$3.95**  
with clock  
purchase

## FM WIRELESS MIKE KIT

Transmit up to 300' to any FM broadcast radio. Sensitive mic. input requires crystal, ceramic or dynamic mike. Runs on 3 to 9V. Small one inch square size.  
**Complete Kit \$2.95**

## SIREN KIT

Produces police-type wail of siren at toy volume. Runs speaker from 3 – 45 Ohms to 200 mW output. Requires power source of 3 to 6 volts. A neat toy for the kids.  
**Complete Kit \$2.95**

## 600 MHz PRESCALER

Extend the range of your counter to 600 MHz. Works with most any counter. Completely assembled and tested. Sensitivity of 100 millivolts. Choice of  $\times 10$  or  $\times 100$ , specify with order. **\$59.95**



## FERRITE BEADS

Beads come with valuable info on uses and specs 15/\$1.00  
6 hole BALUN beads also available . . . . . 5/\$1.00

LED  
DECADE  
COUNTER  
PARTS KIT **\$2.95**

- INCLUDES:
- 7490A 33 MHz decade counter
  - 7475 latch
  - 7447 LED driver
  - 7 – 100 Ohm current limit resistors
  - 7 segment LED readout

Complete with hook-up instructions on how to build an easy, low-cost frequency counter.

SLIDE POT – 10k linear taper . . . SPECIAL 4/\$1.00

1000 uf 15v FILTER CAP . . . . . 5/\$1.00

# ramsey electronics

P.O. Box 4072E Rochester, NY 14610



**48 HOUR  
SERVICE**

Satisfaction guaranteed or money refunded. NO COD. Orders under \$10.00 add \$.75. NY residents add 7% tax.

ication sheet handy. If desired, tables may be constructed similar to **table 1**. Always turn off the 5-volt power when inserting or removing an IC from the socket. In removing ICs from the test sockets, slip a small screwdriver blade under the IC. Then rock the IC gently up and down, raising first one end slightly, then the other end. Repeat until the device is free of the socket. This procedure usually removed the IC without bending any of the metal pins.

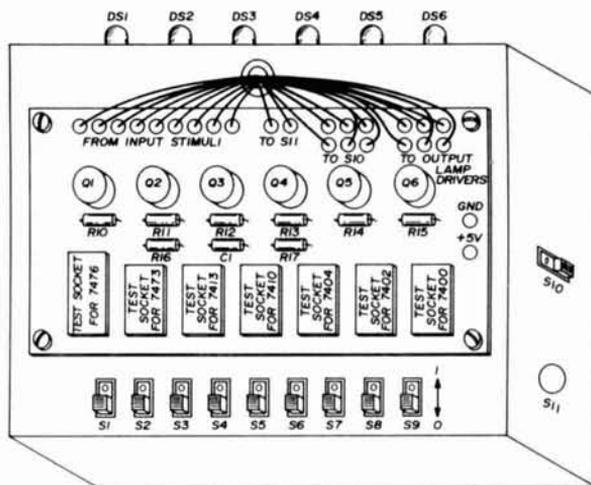


fig. 3. Suggested component layout.

When testing JK flip-flops, a 7413 must also be inserted in its socket. Also, a 7413 can only be tested if a 7473 or a 7476 is in the tester. As wired here, the 7413 has all its input pins connected together, so the test for the 7413 is not complete. The 7413 was really included to produce clock pulses for testing JK flip-flops, so whatever test is available for the 7413 is a bonus. Switch S10 allows both Schmitt triggers of a 7413 to be tested. At all other times, only one IC at a time is inserted into the tester. In testing flip-flops, when power is first applied it is sometimes necessary to depress S11 twice in making the first test. Probably this is because when power is turned on the various internal flip-flops may assume any state, and it takes one pulse to get them into the proper relationship.

## conclusion

The tester was used to check about 100 integrated circuits. Three defective units were found. A 7410 had a defective gate; pin 6 remained high at all times. A 7402 showed a dim glow on DS2 and DS4 when they should have been OFF. (This trouble may not have been found if LEDs had been used as output indicators.) Finally, one-half of a dual JK flip-flop remained in the 1 state at all times.

It may be doubtful at times who'll win, but at least when debugging the 63-IC project I had a head start on Murphy and his wretched laws.

ham radio

# How do you work a ham when he's not in his shack?

## By telephone.

**It's only 21¢ or less plus tax for a one-minute night or weekend call. If you dial direct.**

You can't work a ham when he's away from his rig, but you *can* set up contact by phone. It's quick and it's reasonable, especially when you dial direct. The Night & Weekend rate is the lowest.

Check the chart below for other low dial-direct rates.

NEW RATES FOR COAST-TO-COAST INTERSTATE CALLS			
DIAL-AND-SAVE ONE-MINUTE RATES			OPERATOR-ASSISTED THREE-MINUTE RATES
FULL RATE	35% DISCOUNT	60% DISCOUNT	
<b>WEEKDAYS</b> Monday-Friday 8 a.m.-5 p.m.	<b>EVENINGS</b> Sunday-Friday 5 p.m.-11 p.m.	<b>NIGHTS &amp; WEEKENDS</b> Every night 11 p.m.-8 a.m. Saturday— day and night Sunday— day and night except 5 p.m. to 11 p.m.	<b>STATION-TO-STATION</b> Full rates apply at all times First 3 minutes <b>\$2.25</b>
<b>First Minute</b> <b>54¢</b>	<b>First Minute</b> <b>35¢</b>	<b>First Minute</b> <b>21¢</b>	<b>PERSON-TO-PERSON</b> Full rates apply at all times First 3 minutes <b>\$3.35</b>
<p><b>Additional minutes cost less than the first minute.</b> Dial direct rates apply on all interstate calls, completed from a residence or business phone without operator assistance. They also apply on calls placed with an operator from a residence or business phone where dial-direct facilities are not available. For dial direct rates to Hawaii and Alaska, check your operator. Dial direct rates do not apply to person-to-person, coin, hotel-guest, credit card or collect calls, or to calls charged to another number, because an operator must assist on such calls. Rates quoted do not include tax.</p>			<p>Additional minutes same as dial rate. Applicable discounts apply to additional minutes during Evening and Night &amp; Weekend periods.</p>

Cut this chart out and put it in your phone book.



# 50-MHz bandpass filter

A bandpass filter  
of unusual design  
that provides  
6% bandwidth at 50.5 MHz  
with only 4-dB  
insertion loss

The design of highpass, lowpass, and bandpass filters for use at hf and vhf has been covered in recent amateur literature.<sup>1,2,3</sup> The professional literature has also offered design aids in the form of slide-rule devices for use in filter synthesis<sup>4</sup> and in graphs.<sup>5</sup> The article on hf bandpass filters for receivers by W7ZO1<sup>3</sup> is an excellent example of showing what can be done and how simple these filters can be. W7ZO1 is to be commended for combining amateur know-how with laboratory equipment to demonstrate the selectivity of his designs. His fig. 7 (reference 3) at first appeared too complex and at

the same time reminded me of a similar filter I had hiding in the garage.

## filter characteristics

The garage relic is of unknown origin and as fig. 1 shows, is rather sophisticated. Fig. 2 is a plot of this filter's response taken from an x-y recorder (using a hand-tuned signal generator). The insertion loss (4 dB) and a bandwidth of 6 percent at the 3-dB points seem pretty good, considering the 50.5-MHz center frequency and the amount of wire on the coils.

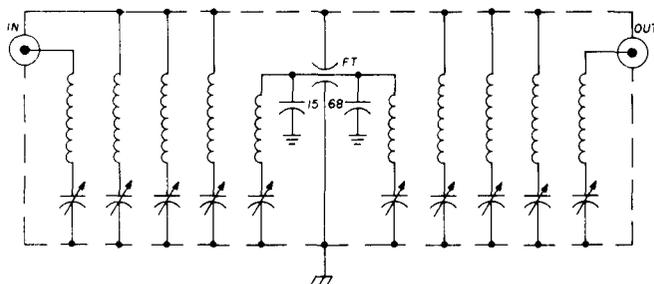


fig. 1. Schematic of the vhf bandpass filter. Center frequency is 50.5 MHz, bandwidth 6 percent, and insertion loss 4 dB. Each of the inductors is about 2.2  $\mu$ H; variable trimmers are 1.5-7 pF.


A photo from a Hewlett-Packard spectrum analyzer (fig. 3) shows the skirt slope. Vertical divisions are 10 dB and the horizontal scale is 1 MHz/cm.

## construction

I don't recommend construction of this filter unless you have a sweep signal generator and a 5-inch (13cm)

By Paul H. Sellers, W4EKO, 4002 Columbus Avenue, Norfolk, Virginia 23504

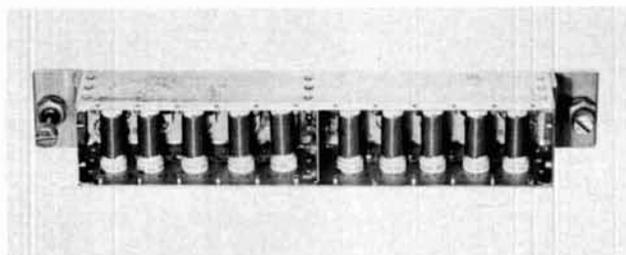oscilloscope for alignment. Alignment is tedious and quite ticklish. For those brave enough to attempt to duplicate this filter, the photo and fig. 4 are provided. The coils forms are ribbed Teflon rod, 1/2 inch (12.5mm)



Inside the 50-MHz bandpass filter showing coil arrangement and center shield. (Photo courtesy Paul Ireland).

in diameter. Each of the coils are 21 turns no. 20 AWG (0.8mm) wire; winding length is 1-3/64 inches (26.5mm). Coil ends are inserted through holes in each end of the Teflon rod (fig. 4A). Overall coil diameter,

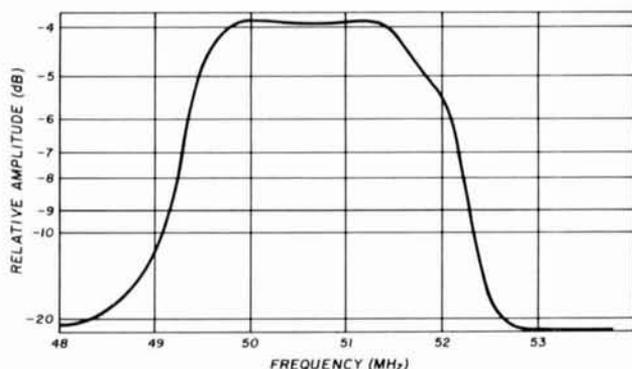


fig. 2. X-Y recorder plot of filter response. Filter insertion loss pushes down the peak of the curve allowing skirts to show out-of-band values of signals passed.

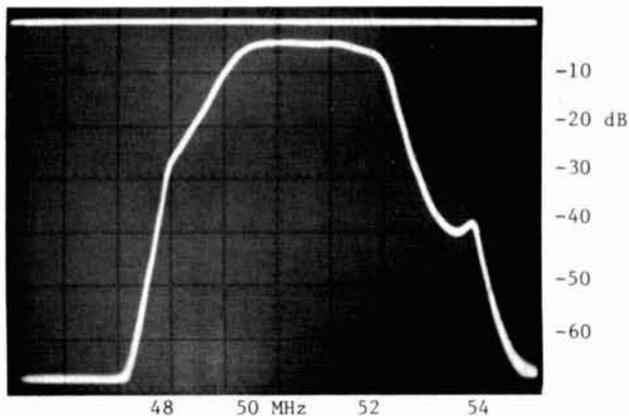


fig. 3. Photo from H-P spectrum analyzer showing filter skirt slope. Vertical scale: 10 dB/division; horizontal scale: 1 MHz/cm.

including wire and ribs, is 9/16 inch (14.5mm). The coils are spaced as in fig. 4B, which is a side view of the filter showing the hold-down screws for the coils. The variable capacitors are about 1.5-7 pF, and the fixed capacitors are Corning type CY10C, 150J and 680J.

I'm sure you'll appreciate the design of this filter, including the unusual input/output circuits and the purely inductive coupling between stages.

#### references

1. Bob Myers, W1FBY, and Clarke Green, WA1JLD, "Field Day Filter," *QST*, April 1973, page 11.
2. Neil Johnson, W2OLU, "High-Frequency Low-pass Filter," *ham radio*, March, 1975, page 24.
3. Wes Hayward, W7ZOI, "Bandpass Filters for Receiver Pre-selectors," *ham radio*, February, 1975, page 18.
4. *Genistron Filter Slide Rule*, Genistron Inc., Los Angeles, California, 1965.
5. "Pick a Filter From this Chart," *Electronic Design No. 24*, November 23, 1972.

ham radio

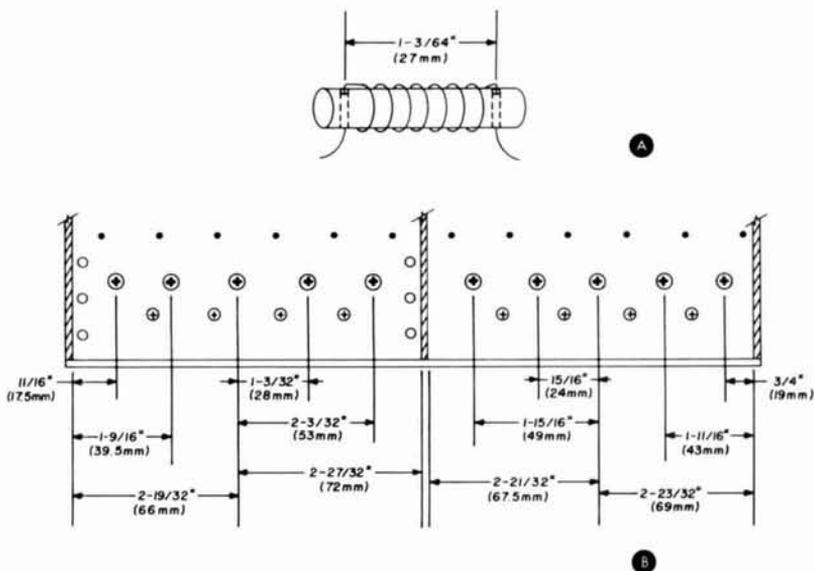


fig. 4. Coil construction details (A) and side view of filter box showing coil spacing (B). Enclosure dimensions are 2-1/8 inches (54mm) deep and 1-7/8 inches (47.6mm) across opening.


Logic Probe 1 is a compact, enormously versatile design, test and troubleshooting tool for all types of digital applications. By simply connecting the clip leads to the circuit's power supply, setting a switch to the proper logic family and touching the probe tip to the node under test, you get an instant picture of circuit conditions.

LP-1's unique circuitry—which combines the functions of level detector, pulse detector, pulse stretcher and memory—makes one-shot, low-rep-rate, narrow pulses—nearly impossible to see, even with a fast scope—easily detectable and visible. HI LED indicates logic "1", LO LED, logic "0", and all pulse transitions—positive and negative as narrow as 50 nanoseconds—are stretched to 1/3 second and displayed on the PULSE LED.

By setting the PULSE/MEMORY switch to MEMORY, single-shot events as well as low-rep-rate events can be stored indefinitely.

While high-frequency (5-10MHz) signals cause the "pulse" LED to blink at a 3Hz rate, there is an additional indication with unsymmetrical pulses: with duty cycles of less than 30%, the LO LED will light, while duty cycles over 70% will light the HI LED.

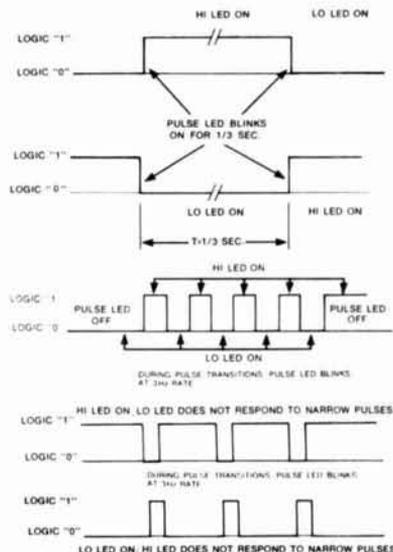In all modes, high input impedance (100K) virtually eliminates loading problems, and impedance is constant for all states. LP-1 also features over-voltage and reverse-polarity protection. Housed in a rugged, high-impact plastic case with strain-relieved power cables, it's built to provide reliable day-in, day-out service for years to come.



## CSC'S MULTI-FAMILY LOGIC PROBE 1. AT \$44.95, IT DIGS UP A LOT OF INFORMATION WITHOUT BURYING YOUR BUDGET.

**HI/LO LED's**—Display level (HI-logic "1", LO-logic "0") of signal activity at node under test

**PULSE LED**—Lets you know what's going on—and off. Indicates positive and negative pulse and level transitions. LP-1 stretches pulses as narrow as 50 nanoseconds to full 1/3 sec. (3Hz pulse rate)

**PULSE/MEMORY Switch**—PULSE position detects and stretches pulses as narrow as 1/3 sec. Switch to MEMORY and it stores single shot and low-rep-rate events indefinitely; HI/LO LED's remain active

**Logic Family Switch**—TTL/DTL or CMOS matches Logic "1" and "0" levels, for greater versatility. High Input Impedance—100K virtually eliminates circuit loading problems and is constant in both "0" and "1" states. CMOS position also compatible with HTL, HiNIL and MOS logic

**Non-corrosive nickel-plated probe tip and clip leads**—For reliable contacts and maximum life

**Rugged high impact plastic case**—Built to take it... in the lab or in the field

**Protected**—Features built-in reverse polarity and over-voltage protection; strain-relieved power cable

**\$44.95 Price tag**—Costs so little it can be your personal property



For more information, see your distributor or write for our catalog and distributor list.  
44 Kendall St, Box 1942 New Haven, CT 06509 • 203-624-3103 TWX: 710-465-1227 West Coast office:  
Box 7809, San Francisco, CA 94119 • 415-421-8872 TWX: 910-372-7992 Canada: Len Finkler Ltd., Ontario

THE LOGICAL CHOICE: Third in a series

SYMMETRICAL AND  
UNSYMMETRICAL PULSES  
0.5Hz-5MHz.

CONTINUOUS, MANUAL  
ONE-SHOT & EXTERNAL  
TRIGGER OPERATION  
External triggering to 10MHz

INDEPENDENTLY-  
CONTROLLABLE PULSE  
WIDTH & SPACING  
100 nanosec-1 sec in 7 overlap-  
ping ranges 10<sup>7</sup>:1 duty cycle  
range



INDEPENDENT CMOS AND  
TTL OUTPUTS Fan-out to  
40 TTL loads

SYNCHRONOUS OUTPUT  
GATING

100mV-10V POSITIVE  
OUTPUT Less than 30  
nanosec rise/fall times

# CSC'S DESIGN-MATE™ 4: \$124.95. NO OTHER DIGITAL PULSE GENERATOR GIVES YOU SO MUCH, FOR SO LITTLE.

Sounds hard to believe... but even a brief look at Design-Mate 4's specifications proves CSC's engineers have done it again. Whatever your application—whether you're looking for precision, flexibility or just plain economy—this compact source of fast, clean digital pulses offers the performance you need... at a price that discourages procrastination.

Use it as a clock source, delayed pulse generator, synchronous clock, manual system stepper, pulse stretcher, clock burst generator or in dozens of other applications. Use it alone or in tandem with other DM-4's for gated control. The


wide range of controls and multiple outputs give you enormous versatility... plus compatibility with all major logic families, for research, design, development, quality control, production testing, maintenance, troubleshooting... you name it.

Now, read the specs that follow... and check the price again. Or better yet, try DM-4 for yourself at your local CSC distributor. Once you do, we think you'll find it's as hard to do without as it is easy to own.

For more information about CSC's other fine products, and a list of distributors, please call or write.

## DM-4 SPECIFICATIONS

<b>Frequency Range:</b> 0.5 Hz to 5 MHz	<b>ONE-SHOT</b> Pushbutton for single pulse. Output pulse occurs each time push-button is pressed
<b>Pulse Width and Spacing Controls:</b> 100 nanosec to 1 sec. in 7 overlapping decade ranges. A single-turn vernier control provides continuous adjustment between ranges. 10 <sup>-1</sup> -to 1 Range: adjustable over entire pulse width/spacing range. 100 nanosec 'ON' 1 sec 'OFF' to 1 sec 'ON' and 100 nanosec 'OFF'	
<b>Duty Cycle:</b> 10 <sup>-1</sup> -to 1 Range: adjustable over entire pulse width/spacing range. 100 nanosec 'ON' 1 sec 'OFF' to 1 sec 'ON' and 100 nanosec 'OFF'	<b>OUTPUTS:</b>
<b>Operating Modes:</b>	<b>VAR OUT</b> Amplitude 0.1-10 V positive
<b>RUN</b> 0.5 Hz to 5 MHz as per width/spacing and amplitude control settings	<b>Rise/fall time</b> Less than 30 nanosec
<b>TRIG</b> DC to approx. 10 MHz	<b>Impedance</b> 400Ω max
<b>Input requirements:</b> Sine waves 2 VP-P, pulses 1 V peak, >40 nanosec wide, maximum input ±10 V (Input Impedance Approx. 10KΩDC coupled)	<b>TTL OUT</b> Fan-out 40 TTL Loads
<b>GATE</b> Synchronous gating. Leading edge of gate signal turns generator ON. Last pulse is completed, even if gate ends during pulse	<b>Sink</b> 160 milliamps—0.8 V max.
<b>Input requirements:</b> Same as TRIG Mode	<b>Rise/fall time</b> Less than 20 nanosec
	<b>SYNC OUT</b> Pulse width Approx. 40 nanosec. Other sync pulse specs same as TTL out
	<b>Pulse lead time</b> Sync pulse leads outputs by approx. 20 nanosec
	<b>POWER</b> 117 VAC ±10%, 50/60 Hz, 5 watts (220 VAC, 50/60 Hz also available, at slightly higher cost)
	<b>SIZE</b> 7.5 x 6.5 x 3.25"
	<b>WEIGHT</b> 191 x 165 x 83 mm
	2 lbs (0.91 Kg)

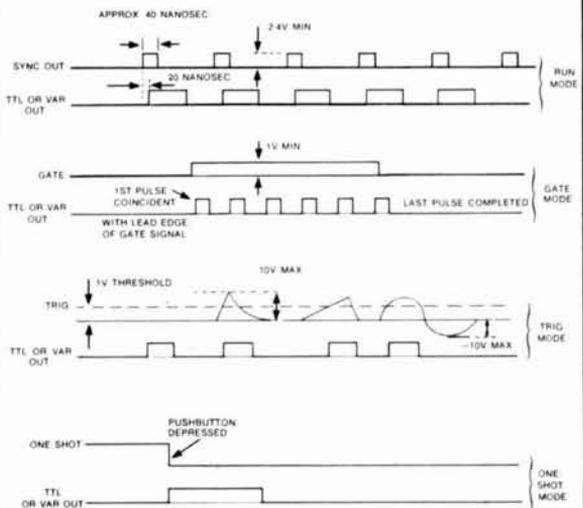


CONTINENTAL SPECIALTIES CORPORATION



EASY DOES IT

44 Kendall Street, Box 1942 New Haven, CT 06509 • 203-624-3103 TWX: 710-465-1227  
West Coast office: Box 7809, San Francisco, CA 94119 • 415-421-8872 TWX: 910-372-7992  
Canada: Len Finkler Ltd., Ontario

© 1976, Continental Specialties Corp.

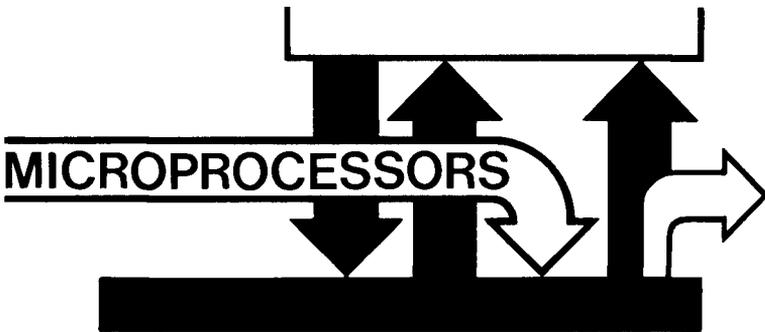

## microcomputer interfacing: how does a microcomputer make a decision?

One of the most important programming characteristics in any digital computer, including a microcomputer, is the ability to make a decision. For a typical microcomputer, we can define a *decision* as the process of determining further action based on the logic state of a *flag*. A *flag* is a single flip-flop that can be either set or cleared in response to operations occurring within the microcomputer system. A change of state of the flag is usually an indication either that a particular operation has been completed, or that a certain condition exists as a result of a microcomputer operation. Flags can be located either internally or externally to the microprocessor chip; those discussed here are the internal flags, which are set or cleared in response to specific types of microprocessor instructions, such as arithmetic and logical instructions.

The flags located within the microprocessor chip are typically associated with the *arithmetic-logic unit (ALU)*, a region within the chip where all arithmetic and logical operations are performed. In the 8080 microprocessor chip, for example, five flags indicate the following conditions;

By Jonathan Titus, David G. Larsen, WBHYJ, and Peter R. Rony

Mr. Larsen, Department of Chemistry, and Dr. Rony, Department of Chemical Engineering, are with the Virginia Polytechnic Institute and State University, Blacksburg, Virginia. Mr. Jonathan Titus is President of Tychon Inc., Blacksburg, Virginia.

**Zero flag** If the result of an arithmetic or logical operation is zero, the zero flag is set to logic 1; if nonzero, the zero flag is reset to logic 0.

**Sign flag** If the result of an arithmetic or logical operation is negative, the sign flag is set to logic 1; if positive, the sign flag is reset to logic 0.

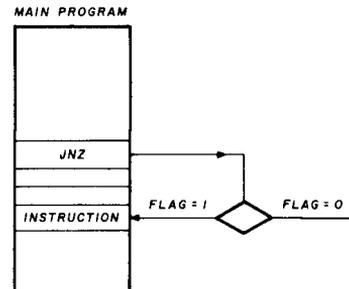



fig. 1. The JNZ instruction. If the zero flag is at logic 1, the instruction is ignored and program control passes to the following instruction.

**Parity flag** If the result of an arithmetic or logical operation has even parity, the parity flag is set to logic 1; if odd parity the parity flag is reset to logic 0.

**Carry flag** If the result of an arithmetic or rotate operation has a carry out of the most-significant bit of the 8-bit result, the carry flag is set to logic 1; if not, the carry flag is reset to logic 0. The carry flag is reset to logic 0 after all logical operations.

**Auxiliary carry flag** If the result of an arithmetic operation has a carry out of bit 3 into bit 4 of the 8-bit result, the auxiliary carry flag is set to logic 1; if not, the auxiliary carry flag is reset to logic 0. The auxiliary carry flag is reset to logic 0 after most logical operations.

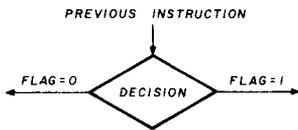Insufficient space is available in this column to discuss all of the above flags, so we shall restrict our attention to the zero flag. Shown below is the traditional flow chart *decision symbol* applied to an 8080 microprocessor decision:



The next instruction executed depends on the logic state of the flag associated with this specific decision. For example, consider the JNZ instruction, where JNZ means "Jump if Not Zero:"

instruction code	mnemonic	description
302	JNZ	If the zero flag is at logic 0, jump to the 16-bit memory address given in bytes <B2> and <B3> of this three-byte instruction; if the zero flag is at logic 1, ignore this instruction and proceed to the following instruction.
<B2>		
<B3>		

The statement "Jump if Not Zero" refers to the 8-bit result of a preceding instruction, not to the logic state of the zero flag. When this result is zero, the zero flag is set at logic 1 and program control passes to the next instruction, as shown in fig. 1.

The JNZ instruction is widely used in the creation of programmed *time delay loops*, an example of which is provided in table 1. In this program, both the address and instruction bytes are in octal code; it is assumed that the HI memory address byte is 000. The program first moves an 8-bit timing byte into register B; this byte, indicated by an asterisk, has any value between 000 and 377. The value of the byte will determine the duration of the time delay.

At LO memory address 002, a device-select pulse is generated to set the SN7474 flip-flop shown in fig. 2. The contents of register B are then decreased by 1.

table 1. Microcomputer program that demonstrates a simple time delay loop based on a decision made on the logic state of the zero flag. This program generates a single output pulse, the duration of which is determined by the timing byte at location 001, at the Q output of the SN7474 flip-flop.

LO memory address	instruction byte	mnemonic	clock cycles	description
000	006	MVI B	7	Move following timing byte into register B
001	*	—	—	Timing byte for register B
002	323	OUT 2	10	Generate device-select pulse that sets the SN-7474 flip-flop
003	002	—	—	Device code for set input to SN7474 flip-flop
004	005	DCR B	5	Decrement contents of register B by 1
005	302	JNZ	10	If zero flag is at logic 0, jump to the memory address given by the following two address bytes; otherwise, ignore this instruction
006	004	—	—	LO memory address byte
007	000	—	—	HI memory address byte
010	323	OUT 3	10	Generate device select pulse that clears the SN7474 flip-flop
011	003	—	—	Device code for clear input to SN-7474 flip-flop
012	166	HLT	7	Halt the micro-computer

\*May have any value between 000 and 377. Its value determines time-delay duration.

The JNZ instruction immediately tests the logic state of the zero flag; if the contents of register B are not zero, the flag is at logic 0 and a jump occurs back to LO memory address 004. The DCR B and JNZ instructions are executed repeatedly until the contents of register B become zero, at which time the zero flag becomes logic 1. The JNZ instruction tests the flag for the last time

Reprinted with permission from *American Laboratory*, March, 1976, copyright © International Scientific Communications, Inc., Fairfield, Connecticut 1975.

## microcomputer seminars

*An introduction to interfacing, programming and applications.*

The course so widely acclaimed at SAROC & DAYTON

For individuals interested in learning about microcomputers and how to get started in applying them to real-world situations.

### BOSTON, MASSACHUSETTS

In conjunction with the 1976  
New England ARRL Convention

#### An all-day program including:

What is a microprocessor? A Microcomputer?

Where do microcomputers fit? What are appropriate applications?

Microcomputer interfacing: a. Bus structure; b. Control signals; c. Data flow

Microcomputer memory: a. Types of memory: RAM, ROM, and PROM; b. ROM/RAM trade-offs

Microcomputer Input/Output: a. Device addressing; b. Control of Input/Output; c. Communication with the outside world

Microcomputer interrupts and flags: a. Hardware vs software; b. Advantages and disadvantages of interrupt schemes; c. Timing

Microcomputer software: a. As a replacement for hardware; b. Modular approaches

Microcomputer peripherals and I/O port implementation: a. UARTS and communications chips; b. FIFOs and buffer storage; c. PPI chips; d. I/O port chips

Microcomputer software development: a. Machine language; b. Assembly language and editor/assemblers

How do I get started?: a. equipment and materials; b. Texts; c. Costs: projections of time and money

#### Your instructors — one or more of the following

**David G. Larsen, WB4HYJ\***

Instructor, Department of Chemistry, Virginia Polytechnic Institute & State University

**Dr. Peter R. Rony\***

Professor, Department of Chemical Engineering, Virginia Polytechnic Institute & State University

**Mr. Jonathan A. Titus\***

President, Nanotran Inc., (Microcomputer consulting firm), General manager, Tychon, Inc.

**Mr. Christopher Titus**

Consultant \*One of the authors of the famous Bugbook series

#### Dates & Location:

Friday, Sept. 10 and Saturday, Sept. 11

Statler Hilton Hotel, Park Square, Boston, Mass.

**Fee: \$25 plus \$35** for required textbooks (A complete set of Bugbooks I, II, IIa, and III.)

**To enroll:** Send \$60 along with your name, address and telephone number to **HAM RADIO**. Be sure to indicate your choice of dates. May we suggest you hurry as registration is limited.

Greenville, NH 03048

603-878-1441

and shifts program control to the OUT 3 instruction at LO memory address 010. This output instruction generates a device-select pulse that clears the SN7474 flip-flop. Once this has been done, the microcomputer comes to a halt.

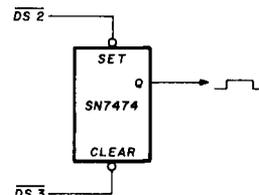


fig. 2. SN7474 flip-flop used as a monostable multivibrator.

The program shown in table 1 generates a single output pulse, the duration of which can take any value between 0.0125 and 1.925 ms in steps of 0.0075 ms. Some typical pulse widths are summarized in table 2 for an 8080-based microcomputer that operates at a clock rate of 2 MHz. The calculations associated with the conversion of clock cycles to pulse width were discussed in reference 1. The number of clock cycles is a measure of the actual time it takes the microcomputer to execute a single instruction or group of instructions.

table 2. Examples of output pulse widths generated by the program in table 1 with an 8080 microcomputer operating at a clock rate of 2 MHz.

timing byte at LO  
memory address

001	number of clock cycles	pulse width (ms)
000	3850	1.925
001	25	0.0125
002	40	0.02
003	55	0.0275
004	70	0.035
005	85	0.0425
010	130	0.065
020	250	0.125
050	610	0.305
100	970	0.485
200	1930	0.965
300	2890	1.445
350	3490	1.745
377	3835	1.9175

For a 2-MHz microcomputer, a single clock cycle has a duration of 500 ns. The program in table 1 and associated SN7474 flip-flop provide an example of what we mean by "the substitution of hardware by software" namely a simple program and a single flip-flop replace a much more complicated hardwired programmable monostable circuit.

#### reference

1. *Bugbook III. Microcomputer Interfacing Experiments Using the Mark 80 Microcomputer, an 8080 System*, (E&L Instruments, Inc., Derby, Conn., 1975. Available for \$14.95 from Ham Radio Books, Greenville, N.H. 03048).

# DIGITAL DATA RECORDER

## for Computer or Teletype Use

### Up to 4800 Baud

Uses the industry standard tape saturation (NRZ) method to beat all FSK systems ten to one. No modems or FSK decoders required. Loads 8K of memory in 17 seconds. This recorder enables you to back up your computer by loading and dumping programs and data fast as you go, thus enabling you to get by with less memory. Great for small business bookkeeping. Imagine! A year's books on one cassette.

Can be software controlled. Comes complete with a software program used to test the units in production (8080). Manual includes software control hook up data and programs for 8080 and 6800.



#### SPECIFICATIONS — MODEL CC7:

- A. Recording Mode: Tape saturation binary (NRZ). This is not an FSK or Home type recorder. No voice capability. No Modem. Runs at 2400 baud or less Asynchronous and 4800 baud Synchronous. Runs at 3.1"/sec. Speed mechanically regulated  $\pm .5\%$  or better.
- B. Two channels (1) Clock, (2) Data. Or two data channels providing four (4) tracks on the cassette. Can also be used for Bi-Phase, Manchester, etc.
- C. Inputs: Two (2). Will accept TTY, TTL or RS 232 digital.
- D. Outputs: Two (2). Board changeable from TTY, RS232 or TTL digital.
- E. Erase: Erases while recording one track at a time. Record new data on one track and preserve three or record on two and preserve two.
- F. Compatibility: Will interface any computer using a UART or ACIA board. (Altair, Sphere, IMSAI, M6800, etc.)
- G. Other Data: 110-220 V - (50-60) Hz; 3 Watts total; UL listed; three wire line cord; on/off switch; audio, meter and light operation monitors. Remote control of motor optional. Four foot, seven conductor remoting cable provided.
- H. Warrantee: 90 days. All units tested at 300 and 2400 baud before shipment. Test cassette with 8080 software program included.

**Also available — MODEL CC7A** with variable motor speed which is electronically regulated. Runs 4800 baud Synchronous or Asynchronous. Recommended for quantity users who require tape interchangeability. Comes with speed calibration tape to set exact speed against 60 cycle line.

**\$169.95**

#### **NEW** — 8080 I/O BOARD with ROM

Permanent Relief from "Bootstrap Chafing"  
This is our new "turnkey" board. Turn on your Altair or Imsai and go (No Bootstrapping). Controls one terminal (CRT or TTY) and one or two cassettes with all programs in ROM. Enables you to turn on and just type in what you want done. Loads, Dumps, Examines, Modifies from the keyboard in Hex. Loads Octal. For the cassettes, it is a fully software controlled Load and Dump at the touch of a key. Even loads MITS Basic. Ends "Bootstrap Chafe" forever. Uses 512 bytes of ROM, one UART for the terminal and one USART for the Cassettes. Our orders are backing up on this one. #2SIO (R)

**Kit form \$140.00**

**Fully assembled and tested \$170.00**

Fill out form and send check or money

Mailing Label — PRINT

#### **NATIONAL MULTIPLEX CORPORATION**

3474 Rand Avenue, Box 288  
South Plainfield, New Jersey 07080 201-561-3600

SHIP TO:

CARD NO. \_\_\_\_\_ ZIP \_\_\_\_\_

EXPIRATION DATE \_\_\_\_\_

.....Data Recorder CC-7 @ \$149.95

.....Data Recorder CC-7A @ \$169.95

Please enclose \$2.00 Shipping & Handling on each Recorder or I/O Board.

.....Operating & Technical Manual (Schematics) Includes Software & Hookups for 8080, 6800, and I/O. \$2.00

N. J. Residents add 5% Sales Tax



# SAROC™

## HAWAII WEEK

INCLUDING

### SAROC'S SECOND HAWAIIAN CONVENTION August 24 to 31, 1976

SPEND 8 FABULOUS DAYS IN EXCITING HAWAII ON SAROC'S HAWAII WEEK



Your holiday includes:

- Attendance at the SAROC Hawaiian Convention, Saturday, August 28.
- Seven nights at Del Webb's fabulous KUILIMA RESORT HOTEL and COUNTRY CLUB On Oahu's North Shore.
- Roundtrip air transportation, double occupancy in hotel room and SAROC Advance Registration just \$300 per person. Limit 2 pieces of luggage per person. Tax and gratuity included.
- Departs Los Angeles August 24, 1976 — Returns August 31, 1976.
- \$100 deposit by June 1, 1976, full payment by July 10, 1976.
- SAROC Advance Registration \$3.00, with Saturday Banquet \$10 per person.

*Write for further details*

### SAROC™

BOX 945, BOULDER CITY, NEVADA 89005

# COMPARE

Feature	SWTP®-6800	Theirs—Your Choice
Processor—	The best "Motorola MC6800". Two accumulators, automatic vectoring, seven addressing modes and complete set of branch instruction. The more powerful instruction set and memory orientated architecture makes programming very straight forward and easy to learn. Operates from a single +5 Volt supply.	Some are almost as good in one respect or another. None can offer all of the features of a real MC6800.
Memory—	Static 2102-1 type memories. Fast enough to allow the processor to run at full speed at all times. No refresh cycles, no problems with glitches and flakey dynamic memories.	Various types available. Often not included in the basic kit, and must be purchased as an extra cost option. (this is an option?)
Power Supply—	10 Amp. Capacity. More than enough to power a fully expanded system. Power supply uses a rugged 25 amp bridge rectifier and a 91,000 mfd computer grade filter. Regulators on the individual plug-in cards.	Some expand more than others with the supply provided. Check carefully.
Expansion—	Seven slots for processor and memory boards. Eight I/O slots. I/O's are programmable type. All decoding and clocking provided from mother board making additional interfaces very inexpensive. Baud rates may be independently selected for each interface card.	Varies from "0" to 16, or more.
Start Up—	Automatic start and reset provided by "Motorola" Mikbug® ROM. No fiddling with switches and status lights. Just push the button and go. Use of standard Motorola firmware makes software 100% compatible with Motorola evaluation module programs.	Anything from switch and status light to automatic ROM loading. If ROM is not a standard part, the software may be unique to that machine.
Clock—	Crystal controlled master clock oscillator with high power clock drivers. Insures reliable, consistent operation with no noise problems. Baud rate divider operating from the master clock oscillator provides the various baud rates for the I/O devices with crystal accuracy. No adjustments necessary to lock everything in at the proper frequency.	Anything from cheap dual monostable systems to crystal control. Crystal oscillators are best. Dual one-shots can develop phase overlap problems and are more susceptible to noise problems.
Buffering—	Tri-state bi-directional buffers on all data lines, address lines and clock lines on <u>ALL</u> boards. Insures trouble free noise immune operation.	Various—from full buffering to almost no buffering. Lack of full buffering can lead to noise problems.
Documentation—	Very complete. Our own notebook, plus the "Motorola" Programming Manual and Applications Manual. Detailed instructions along with sample programs help you to understand programming. You will be ready and able to write your own programs after mastering these instructions.	
Price—	<b>\$395.00</b> For the whole thing. You get the case, power supply, processor 2K word memory and serial interface. No extras to buy. Just connect a terminal and start operating.	As we said—COMPARE.

© Registered Trademark Motorola

## COMING ATTRACTIONS

**CASSETTE INTERFACE**—Our new AC-30 will make it possible to load and dump programs to cassette tape using ordinary inexpensive recorders. Uses the standard "Kansas City" recording format for compatibility.

**LINE PRINTER**—At last—hard copy at a reasonable price. Our new PR-40 printer will print program listings, or any other material you might want to keep in printed form. A dot matrix printer at a price you are not going to believe.


**GRAPHICS TERMINAL**—A universal—works with any computer—graphics terminal. With this connected to your computer you can play games in style. May be used with our CT-1024 to put both graphics and alpha-numerics on the screen simultaneously.

**PLEASE**—Don't call or write. We will have details on these projects in our next ad. Government regulations prevent us from giving prices, or taking orders yet.

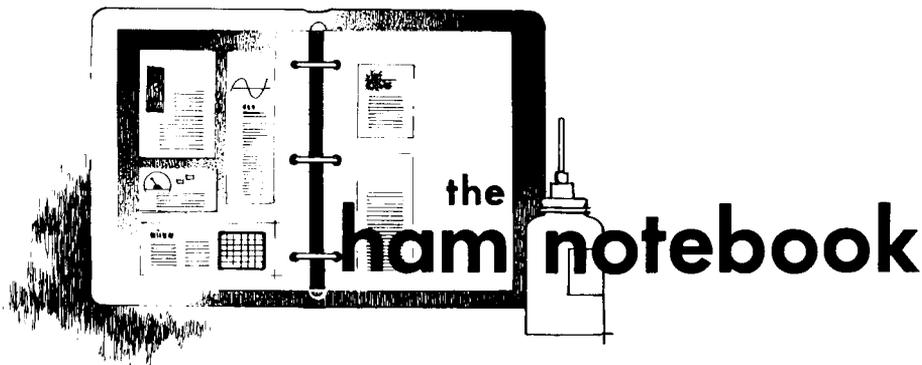**SOFTWARE**—The flood is near. Editor and assembler now available. BASIC and more games right away. Yours for the cost of copying. **WE DON'T SELL SOFTWARE—WE GIVE IT TO YOU. ENJOY IT, COPY IT, WE WON'T COMPLAIN...**



**SWTP** Southwest Technical Products Corp., Box 32040, San Antonio, Texas 78284



## keyer modification

Many CW operators who use electronic keyers prefer a single-shaft paddle of the non-iambic variety, such as the *Vibro Key*. As they develop their speed level and go to close spacing on the paddle, many operators notice the effect of paddle bounce when using keyers with dot memory.

What happens is that after the operator strikes the paddle for a dash, the return motion of the paddle overshoots and causes the dot mechanism to close momentarily, which sets the dot memory. This, in turn, generates an unexpected (and unwanted) dot.

Careful adjustment of the paddle will minimize this effect, but it will still occur whenever the dash side is firmly hit. This is not, perhaps, a problem for the operator with a precise fist, but not all of us meet that description, and the extra bounced dot is very disturbing.

The cure is relatively simple and can be utilized with any TTL keyer. I have installed the circuit in fig. 1 in both a Data Signal 21B keyer and a keyer built around the new Curtis keyer chip, and

in both cases the bounce problem was cured.

The circuit uses a 74121 monostable multivibrator and a 7432 AND gate. The output of the 74121 stays low if the paddle is not in use, if dots are being sent, or if dashes are being sent. However, as soon as the dash paddle is released, the transition from the low to high state causes the 74121 to transmit a high level pulse of short duration to the AND gate. The duration of the pulse is controlled by the values of R1 and C1.

When either of the inputs to the AND gate is in the high state, the output of the gate stays high so the paddle cannot transmit a dot into the dot memory. The duration of the pulse from the 74121 is selected so that it is only long enough to block a dot caused by the dash bounce from being placed in the dot memory. The duration of the pulse is short enough that the operator cannot possibly "reverse fields" with his hand fast enough to lose a dot he intentionally sends.

In fact, with the circuit installed, the only change the operator will notice is that he no longer sends erroneous dots which are caused by the key bounce. Installation in any TTL or CMOS keyer is very simple -- the keyed lines from the paddle are fed through the circuit and connection is made to the +5 volt line. (It should be noted that some CMOS keyers use voltages other than 5 volts, in which case this circuit will not work).

The values of R1 and C1 shown in the circuit were determined experimentally, and should work fine. If you notice any blocking of intentional dots, either R1 or C1 should be reduced in value until the problem disappears.

Bob Locher, W9KNI

## Collins KWM-2/KWM-2A modifications

Over the years the Collins KWM-2 and KWM-2A ssb transceiver has undergone a number of modifications, some of which were made during the period the unit was used in military service. Available through MARS libraries, and possibly the Government Printing Office, is an Air Force Technical Manual that lists over 50 modifications to the KWM-2/KWM-2A along with expanded, fold-out diagrams of the circuitry which are a great improvement (over the amateur-style instruction manual) for the bifocal crowd.

Of interest to all KWM-2/KWM-2A owners is a simple modification that consists of adding a 0.01  $\mu$ F, 400-volt capacitor from the screen (pin 8) of the 6EB8 audio amplifier to ground. This eliminates an ultrasonic oscillation that caused increased noise and audio distortion in some models.

The title of this technical manual is: *TO-31R2-4-183-3. KWM-2A Transceiver*. It also covers changes to the 30L-1 and 30S-1 rf amplifiers. A second technical manual of interest to KWM-2/KWM-2A owners is TO-31R2-4-183-2 entitled, *Technical Manual (Service) KWM-2A Transceiver*. It also covers the previously mentioned amplifiers. This publication provides detailed alignment instructions for the transceiver and linear amplifiers.

William I. Orr, W6SAI

## IC holders

A convenient method for storing integrated circuits in your parts cabinets is to line the bottom of the drawers with 3/8 inch (1cm) of the polyfoam packing

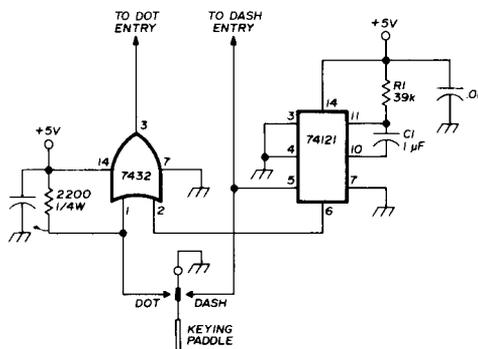


fig. 1. Simple circuit eliminates erroneous dots from being generated by paddle contact bounce (in keyers with dot memory).

material used to ship electronic equipment. Push the IC leads into the soft material, keeping the ICs in neat rows and all facing the same direction. This way you can see at a glance which circuits you have in stock and keep them damage free.

Gary L. Tater, W3HUC

## receiver incremental tuning for the Heath SB-102

A limited amount of receiver incremental tuning (RIT) may be obtained with the SB-102 quite easily. I own a unit with the transistorized linear master oscillator (LMO). At the rear of the LMO is a terminal marked FSK. Unless you are operating RTTY (which does not appear to be recommended in the SB-102 manual) with genuine FSK, this terminal is not used. However, it will provide up to a 1 kHz shift in frequency when directly grounded. By using the circuit shown in fig. 2, plus or minus 400-500 Hz shift may be obtained. As

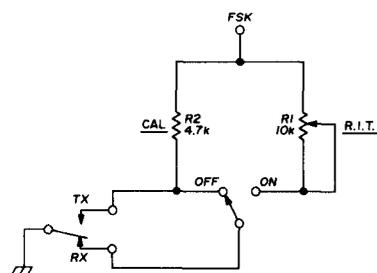


fig. 2. Receiver incremental tuning (RIT) circuit for the Heath SB-102 makes use of the built-in FSK circuit. R1 and R2 are added components.

shown, the circuit provides a useable amount of RIT which is convenient for netting ssb signals. When used in conjunction with the optional 400 Hz CW filter, it really shines.

The calibration resistor, R2, provides an essential mid-point setting and, with R1 centered, a beat note should be of equal pitch. A 10k multiturn pot could be used at R2 if extreme accuracy is desired. The dial calibration will shift approximately 400-500 Hz, but this is easily restored by the zero-set knob. The LMO shaft may be slipped slightly if you're finicky.

Paul K. Pagel, K1KXA

## repairing R390 rf transformers

The rf transformers in the R390 and R390A receivers can be used for more than one band. The tuning ranges are: 0.5 to 1, 1 to 2, 2 to 4, 4 to 8, and 8 to 16 MHz. If there is a loss of sensitivity on some bands, or there is difficulty in obtaining proper alignment, here is a trouble to look for. It is more common in the R390 but may also show up in an R390A. In several first rf transformers I have found that the tuning core sticks because of lumps on the inside of the coil form. This is quite easy to check for.\*

Look carefully at the rf tuning-slug racks as the mechanism tunes through its complete range on the band in question (or check them all as a precaution). The racks should move up and down smoothly. Check several times from different angles. Also check by pulling them up and down by hand while at the bottom of their range. Look for one end pushing up or causing the rack to deviate from the horizontal.

If you think there is trouble, it is easy to verify. Carefully remove the springs from each end of the slug rack and hang them out of the way under tension (use a bent paper clip). If you let go of the spring it can drop down inside the set and will be difficult to retrieve and reconnect. Lift up on the rack and it will come out quite easily. (When putting the rack back, work slowly, as it is easy to chip the edges of the coil forms when reinserting the tuning cores). When the rack has been removed, shine a light down inside the coil form and look at the side. Lumps show up immediately.

If you have this trouble it is easy to fix, but it must be done with care or the coil form will break. To remove the rf transformer, insert a Phillips screwdriver into the two little holes on the top of the transformer case and loosen the two captive screws. Then wiggle the transformer loose as you pull up. It may help to pry gently with another screwdriver.

\*While the coils described are those for the Collins R390 and R390A series of receivers, there are many surplus and commercial receivers which use similar permeability-tuned mechanisms that might be susceptible to the same problem. The repair technique described here could be easily adapted to other, similar tuning mechanisms.

Don't back off on the captive screws any more than you have to. They can go past the point of releasing the transformer, come out of their mounting threads and rattle around loose inside the case. If this happens, take the top off the transformer and use a pair of needle nose pliers to hold the screws in position while you rethread them back.

To repair the coil form you have to remove the lumps from the inside. They appear to be bubbles of varnish or whatever finish was applied to the coil by the manufacturer. The first thing to do is to strengthen the coil form. To do this, spread several layers of *Elmer's Glue-all* on the outside of the form. Be sure each layer has plenty of time to dry; leave it overnight. This will give added strength to the form and coil and help keep either from breaking.

Next, go to work with your box of electric drill bits. Start with 13/64 inch (5mm). Gently insert it into the coil form and twist it by hand to begin removing the crud. When that cuts through, use a 7/32 inch (5.5mm) bit and do the same thing. Finish up with a 1/4 inch (6.5mm) bit. This will take most of it off.

Now make a tube of emery paper (fine sandpaper might work) long enough to reach to the bottom of the coil form and still leave a hand hold. Insert that into the coil form. Take a drill bit thin enough to slip easily inside emery paper but thick enough to give it support. Twist the emery paper around inside the coil form, moving it up and down at the same time. This will smooth off the inside again.

The thing to watch out for here is that you don't chip the top edge of the coil form. If it is chipped or looks about ready to go, it can be strengthened with a thin strip of typewriter paper, spread with *Elmer's Glue-all*, wrapped a few turns around the outside of the coil form top.

Every so often, remove the drill and emery paper and try the tuning core back inside. It should move up and down the entire length of the coil form without binding. When you have completed the operation, clean out the emery and coil form dust by blowing or using a pipe cleaner. Before you put the slug rack back in the set, give the inside of the coil forms and the tuning cores a squirt of silicon spray.

Alexander MacLean, WA2SUT



# CRYSTAL FILTERS and DISCRIMINATORS



### 9.0 MHz FILTERS

XF9-A	2.5 kHz
XF9-B	2.4 kHz
XF9-C	3.75 kHz
XF9-D	5.0 kHz
XF9-E	12.0 kHz
XF9-M	0.5 kHz
XF9-NB	0.5 kHz

SSB TX	\$31.95
SSB RX	\$45.45
AM	\$48.95
AM	\$48.95
NBFM	\$48.95
CW	\$34.25
CW	\$63.95

### 9.0 MHz CRYSTALS (Hc25/u)

XF900	9000.0 kHz Carrier	\$3.80
XF901	8998.5 kHz USB	\$3.80
XF902	9001.5 kHz LSB	\$3.80
XF903	8999.0 kHz BFO	\$3.80
F-05	Hc25/u Socket	.50

### 9.0 MHz DISCRIMINATORS

XD9-01	± 5 kHz RTTY	\$24.10
XD9-02	± 10 kHz NBFM	\$24.10
XD9-03	± 12 kHz NBFM	\$24.10

Export Inquiries Invited  
Shipping \$1.00 per filter

## VHF VARACTOR TRIPLERS UHF

Model	MMv432	MMv432M	MMv432H	MMv1296	MMv1296H
Frequency Range					
Output (MHz)		420 to 450		1260 to 1350	
Input (MHz)		140 to 150		420 to 450	
Input Power, max.	30 W.	50 W.	70 W.	20 W.	35 W.
Output Power, at maximum input					
Typical	20 W.	30 W.	40 W.	14 W.	23 W.
Minimum	18 W.	25 W.	35 W.	12 W.	20 W.

High Power (H) models also available as matched pair.  
Pre-aligned broad band design.  
No power supply required.  
1 1/4" x 2 1/2" x 4 1/2" plus connectors.  
Heat sink on 432M and 432H.  
Write for detailed specifications.

## 146 ↔ 440 FM TRANSVERTER

Use your 2 meter FM Transceiver on the 440 MHz band with the addition of the FMT440 TRANSVERTER. No changes required to your 2 meter Transceiver. Connect FMT440 in place of regular 2 meter antenna. Connect 2 M and 440 antennas (also 12 v) to FMT440. Change bands automatically with switch on FMT440.

**FMT440 Specifications:**  
Transmit Section  
Receive Section  
General

Drive Power 25 watts max  
Efficiency 50% typical  
Sensitivity 0.5 μvolt  
Gain 22 dB nom  
Bandwidth 5 MHz  
Freq. Range 430-450 MHz  
145-150 MHz

Price \$179.95 Shipping \$3.00  
Repeater Groups write for details. Application note available.



SPECTRUM INTERNATIONAL, INC. P. O. BOX 1084 CONCORD, MASS. 01742 U.S.A.

### "MINI-PORTABLE" DIPOLE KIT

Mounts vertical or horizontal - Electrical 1/2 wave length  
For mast, window sill, boat, mobile home, or auto  
Quick erect - Up to 500 watt PEP. Hi-Q resonators  
Tuneable tip rod - 15' approximately length  
40 or 20 meter band models

\$39.95

MOBILE  
\* \$8.95  
12 ME



\* BASE  
\$6.95  
12 BE



#### ENCLOSURES

\* Wired with clear, easily lighted W.E. pad (ready to use) \$49.95

16MPW	16 Digit Min. Encoder Wired w/Motorola Chip	\$39.95
16MPWE (enclosed)		\$49.95


All prices PREPAID shipping Cont'l USA

## KING PRODUCTS

(Dealer Inquiries Invited)

P. O. BOX A, LOMITA, CA 90717 • (213) 534-4402

## K-ENTERPRISES

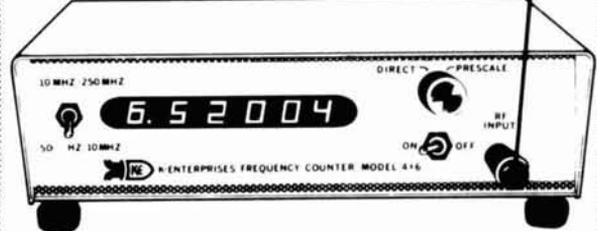

### MODEL 4X6C

50 HZ—250 MHZ ..... \$270.00

- 300 and 500 MHZ PRESCALERS
- FREQUENCY STANDARDS
- MARKER and PEAKING GENERATORS
- POWER SUPPLIES AMPLIFIERS

WRITE FOR FREE CATALOG



Phone: 405-273-9024



K-ENTERPRISES

1401 N. Tucker

Shawnee, Okla. 74801

# Laser Beam Digital Watch

Never press another button, day or night, with America's first digital watch that glows in the dark.

Announcing Sensor's new Laser 220—the first really new innovation in digital watch technology.



It's ingenious, it's simple and it makes every other digital watch obsolete. Scientists have perfected a digital watch with a self-contained automatic light source—a major scientific breakthrough.

## SELF-CONTAINED LIGHT SOURCE

The Laser 220 uses laser beams and advanced display technology in its manufacture. A glass ampoule charged with tritium and phosphor is hermetically sealed by a laser beam. The ampoule is then placed behind the new Sensor CDR (crystal diffusion reflection) display.

The high-contrast CDR display shows the time constantly—in sunlight or normal room light. But, when the room lights dim, the self-contained tritium light source automatically compensates for the absence of light, glows brightly, and illuminates the display.

No matter when you wear your watch—day or night—just a glance will give you the correct time. There's no button to press, no special viewing angle required, and most important, you don't need two hands to read the time.



Replace the battery yourself by just opening the battery compartment with a penny. Free batteries are provided whenever you need them during the five-year warranty.

## A WORRY-FREE WATCH

Solid-state watches pose their own problems. They're fragile, they must be pampered, and they require frequent service. Not the Laser 220. Here are just five common solid-state watch problems you can forget about with this advanced space-age timepiece:

**1. Forget about batteries** The Laser 220 is powered by a single EverReady battery that will actually last years without replacement—even if you keep the 220 in complete darkness. In fact, JS&A will supply you with the few batteries you need, free of charge, during the next five years. To change the battery, you simply unscrew the battery compartment at the back with a penny and replace the battery yourself.

**2. Forget about water** Take a shower or go swimming. The Laser 220 is so water-resistant that it withstands depths of up to 100 feet.

**3. Forget about shocks** A three-foot drop onto a solid hardwood floor or a sudden jar. Sensor's solid case construction, dual-strata crystal, and cushioned quartz timing circuit make it one of the most rugged solid-state quartz watches ever produced.

**4. Forget about service** The Laser 220 has an unprecedented five-year parts and labor

warranty. Each watch goes through weeks of aging, testing and quality control before assembly and final inspection. Service should never be required. Even the laser-sealed light source should last more than 25 years with normal use. But if it should require service anytime during the five year warranty period, we will pick up your Sensor, at your door, and send you a loaner watch while yours is repaired—all at our expense.

**5. Forget about changing technology** The Sensor Laser 220 is so far ahead of every other watch in durability and technology that the watch you buy today, will still be years ahead of all others.


## THE ULTIMATE ACHIEVEMENT

Other manufacturers have devised unique ways to produce a watch you can read at a glance. The new \$300 LED Pulsar requires a snap of the wrist to turn on the display, but the Pulsar cannot be read in sunlight. The new \$400 Longine's Gemini combines both an LED and liquid crystal display. (Press a button at night for the LED display, and view it easily in sunlight with the liquid crystal display.) But you must still press a button to read the time. All these applications of existing technology still fail to produce the ultimate digital watch: one you can read under all light conditions without using two hands. Until the introduction of the Sensor.

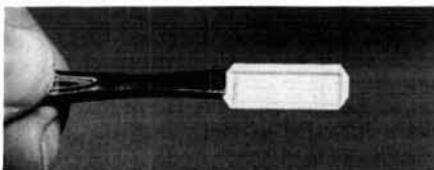
## PLENTY OF ADVANCED FUNCTIONS

Sensor's five time functions give you everything you really need in a solid-state watch. Your watch displays the hours and minutes constantly, with no button to press. But depress the function button and the month and the date appear. Depress the button again and the seconds appear. To quickly set the time, insert a ball-point pen into the recessed time-control switch on the side. It's just that easy.

Sensor's accuracy is unparalleled. All solid-state digitals use a quartz crystal. So does the Sensor. But crystals change frequency from aging and shock. And to reset them, the watch case must be opened and an airtight seal broken which may affect the performance. In the Sensor, the crystal is first aged before it is installed, and secondly, it is actually cushioned in the case to absorb tremendous shock. The quartz crystal can also be adjusted through the battery compart-



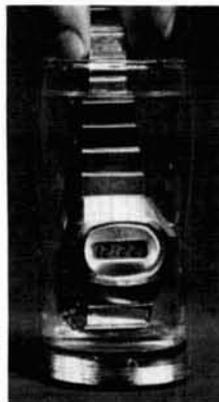The new exclusive laser-sealed tritium and phosphor light source is a thin solid-state tube that automatically illuminates the display when the lights dim.



Would you do this with your solid-state watch? Of course not. Most solid-state watches require care and pampering but not the Sensor. You can dunk it, drop it and abuse it without fear during its unprecedented five-year parts and labor warranty.

ment without opening the case. In short, your watch should be accurate to within 5 seconds per month and maintain that accuracy for years without adjustment and without ever opening the watch case.

## STANDING BEHIND A PRODUCT

JS&A is America's largest single source of digital watches and other space-age products. We have selected the Sensor Laser 220 as the most advanced American-made, solid-state timepiece ever produced. And we put our company and its full resources behind that selection. JS&A will warranty the Sensor (even the batteries) for five full years. We'll even send you a loaner watch to use while your watch is being repaired should it ever require repair. And Sensor's advanced technology guarantees that your digital watch will be years ahead of any other watch at any price.

Wear the Laser 220 for one full month. If you are not convinced that it is the most rugged, precise, dependable and the finest quality solid-state digital watch in the world, return it for a prompt and courteous refund. We're just that proud of it.

To order your Sensor, credit card buyers may simply call our toll-free number below or mail us a check in the amount indicated below plus \$2.50 for postage, insurance and handling. (Illinois residents add 5% sales tax.) We urge you, however, to act promptly and reserve your Laser 220 today.

Stainless steel w/leather strap . . . . . \$129.95  
(Add \$10 for matching metal band)  
Gold plated w/leather strap . . . . . \$149.95  
(Add \$10 for matching metal band)

**JS&A** NATIONAL SALES GROUP

Dept. HM JS&A Plaza  
Northbrook, Illinois 60062  
CALL TOLL-FREE . . . 800 323-6400  
In Illinois call . . . (312) 498-6900

© JS&A Group, Inc., 1976

# Your Next Purchase.



**ELECTRONIC KEYSER  
MODEL 10B**

Reed relay output (1 amp, 250V, 20VA). 10-30 WPM @ 6V-DC supply, 12 MA drain. 15-45 WPM @ 9V-DC supply, 15 MA drain, 3 MA idle current drain. Fixed spacing. Dots 1:1, Dash 1:3. Self-completing Dot/Dash. Manual dash in tune position. (Batteries not included.) Use the Model 10B Keyer with your paddle or our Model 11B matching paddle.

MODEL 10BWA KEYSER with Sidetone assembled \$39.95  
 MODEL 10BWA assembled \$29.95  
 MODEL 10BK (Kit) \$23.95  
 200-2K PC BOARD KIT \$14.95  
 200-3K SIDETONE KIT \$ 5.95  
 Ship. Wt. 1 Lb., add \$ 1.00

(PA RES. ADD 6% SALES TAX)



**PADDLE  
MODEL 11B**

Dit/Dah travel adjustment. No mechanical switches. No bearings to fail. Paddle assembly weight is 1.5 pounds. Reversible Dit and Dah connections. Rubber feet. Damping on paddle operator lever. Feather glide paddle movement.

MODEL 11BW assembled \$11.95  
 MODEL 11BK (Kit) \$ 8.95  
 Ship. Wt. 2 Lb., add \$ 1.35

(PA RES. ADD 6% SALES TAX)



**CW TRANSMITTER  
MODEL 50**

15 watts input. Full break-in keying. All solid state. Crystal control. 160, 80 or 40M plug-in coil. Zener regulated chirpless keying. Has built-in 120 Vac power supply. OPTIONS: Built-in keyer and/or sidetone. Paddle Model 11B is compatible with built-in keyer option.

MODEL 50K (Kit) \$49.95  
 MODEL 50W (Wired) \$69.95

Add-on options:  
 SIDETONE 200-21 Kit \$ 5.95  
 200-21 Wired \$ 8.95  
 KEYSER 200-22 Kit \$13.95  
 200-22 Wired \$18.95  
 Ship. Wt. 4 Lb., add \$ 2.10

(PA RES. ADD 6% SALES TAX)

(All units come with 40M plug-in coil unless otherwise specified. (Additional coil kits \$3.95 each postpaid.)



**ELECTRONIC KEYSER WITH PADDLE  
MORSE-1835  
MODEL 12**

C-MOS circuitry. Solid state output switch. (250V, 1 AMP MAX.) 8-45 WPM. Fixed spacing. Dot 1:1, Dash 1:3. Self-completing Dot/Dash. No on/off switch required. Sidetone has 2-inch speaker. Paddle travel adjustment. Rubber feet. 4 penlight batteries (not included).

MODEL 12 assembled \$49.95  
 Ship. Wt. 2 Lb., add \$ 1.35

(PA RES. ADD 6% SALES TAX)



**SPEECH PROCESSOR  
MODEL 60A**

200K/500 OHM inputs. PTT on connector. Instantaneous attack and release. 2, 9V-DC batteries (not included). 1.5 MA drain. Frequency is  $\pm 1/2$  db., 300-3000 Hz. Process gain control has an in/out switch. The process threshold is: 1.5 MV-RMS (HI-Z). 400 micro V-RMS (LO-Z). Output voltage 100 MV-RMS nom.

MODEL 60AW assembled \$29.95  
 MODEL 60AK (Kit) \$23.95  
 Ship. Wt. 1 Lb., add \$ 1.00

(PA RES. ADD 6% SALES TAX)

## THE WORLD AT YOUR FINGERTIPS!

**SEND FOR CATALOG & DEALER LIST.  
ORDER FROM DEALER OR DIRECT.  
FOR U.P.S., C.O.D SHIPMENTS—ADD 85¢**




RD-1 • BOX 185A • FRANKLIN, PA. 16323  
 TELEPHONE (814) 432-3647



6 digit AUTOMOTIVE CLOCK KIT complete with a CRYSTAL TIMEBASE accurate to .01 percent. 12 volts d.c. operation — built in noise suppression and voltage spike protection. Readouts blank when ignition is off — draws 25 mA in standby mode. Has .3 in. readouts. Use it in your car or for all applications where a battery-operated clock is needed. Approximate size 3" x 3.5" x 1.75"

WITH BLACK PLASTIC CASE \$34.95 ppd.  
 WITHOUT CASE \$29.95 ppd.  
 ASSEMBLED AND TESTED \$45.95 ppd.

CMOS CRYSTAL TIMEBASE KITS with .01 percent accuracy. 5-15 v.d.c. operation. Draws only 3 mA at 12 volts. Single I.C. — very small size — the P.C. board is 7/8" x 1-5/8". Choose a main output of 50 or 100 Hz., 60 Hz., 500 or 1000 Hz., or 1 Hz. Several related frequencies are also available on each board, in addition to the main ones listed above. Be sure to specify the Frequency you want. All kits are \$10.95 ppd.

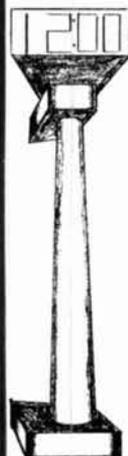

Flyer available —

**NEXUS  
TRADING CO.**

Box 3357 San Leandro, Ca 94578

## ME-3 microminiature tone encoder

Compatible with all sub-audible tone systems such as: Private Line, Channel Guard, Quiet Channel, etc.

- Powered by 6-16vdc, unregulated
- Microminiature in size to fit inside all mobile units and most portable units
- Field replaceable, plug-in, frequency determining elements
- Excellent frequency accuracy and temperature stability
- Output level adjustment potentiometer
- Low distortion sinewave output
- Available in all EIA tone frequencies, 67.0 Hz-203.5 Hz
- Complete immunity to RF
- Reverse polarity protection built-in



\$29.95 each  
 Wired and tested, complete with K-1 element

communication specialists  
 P. O. BOX 152  
 BREA, CALIFORNIA 92621  
 (714) 998-3021

K-1 FIELD REPLACEABLE,  
 PLUG-IN, FREQUENCY  
 DETERMINING ELEMENTS  
 \$3.00 each

# HOW'S YOUR BIRD??

WATTMETER THAT IS . . . IF YOU HAVE BEEN HAVING DIFFICULTY LOCATING THE WATTMETER JUST RIGHT FOR YOU OR IF YOU CAN'T FIND THE CORRECT ELEMENT FOR YOUR MODEL 43, YOU MAY HAVE BEEN LOOKING IN THE WRONG PLACES. OUR LARGE INVENTORY OF MOST COMMON ELEMENTS LETS YOU GET WHAT YOU WANT WHEN YOU NEED IT. GIVE US A CALL FIRST FOR YOUR BIRD NEEDS.



## MODEL 43 \$110.00

ELEMENT TABLE 1 SUFFIX H ..... \$40.00 ea.  
SUFFIXES A, B, C, D, E ..... \$35.00 ea.  
ALSO AVAILABLE . . . MODEL CC1, CARRY CASE  
FOR MODEL 43 ..... \$22.00  
EC-1, CARRY CASE FOR XTRA ELEMENTS \$14.00  
ABOVE PRICES DO NOT INCLUDE SHIPPING.

PLUG-IN ELEMENTS for use with Model 43 THRULINE Wattmeter. Select one or more elements to suit your frequency and power ranges. When ordering, specify catalog number and THRULINE model number.

Table 1

STANDARD ELEMENTS (CATALOG NUMBERS)

Power Range	Frequency Bands (MHz)					
	2-30	25-60	50-125	100-250	200-500	400-1000
5 watts	—	5A	5B	5C	5D	5E
10 watts	—	10A	10B	10C	10D	10E
25 watts	—	25A	25B	25C	25D	25E
50 watts	50H	50A	50B	50C	50D	50E
100 watts	100H	100A	100B	100C	100D	100E
250 watts	250H	250A	250B	250C	250D	250E
500 watts	500H	500A	500B	500C	500D	500E
1000 watts	1000H	1000A	1000B	1000C	1000D	1000E
2500 watts	2500H					
5000 watts	5000H					

## BIG, BIG SELLER AT DAYTON!

**NEW**



LOW  
PROFILE  
YET  
ALMOST  
1/16" STROKE

This very popular item at the 1976 Dayton Hamvention is **NOW OFFERED TO YOU** at these low prices. Incorporates the ideal "tactile feel" leaving no doubt that contact has been made. These **NEW** keyboards, manufactured by **THE DIGITRAN COMPANY**, are furnished with instructions for combining with a **MOSTEK** or **MOTOROLA** chip and a crystal (plus several small components) to become a Tone Encoder.

12 Key (2 of 7 Matrix) 2" x 2.7" x 5/16" \$8.00  
16 Key (2 of 8 Matrix) 2.8" x 2.7" x 5/16" \$10.00

Please add 75¢ Shipping/Handling



- Uses inexpensive 3.58 MHz Crystal
- Dual tones mixed internally no external mixing circuitry required.
- Constructed from CMOS for RF immunity
- Transmitter switching transistor on chip
- Completely compatible with Digitran keyboard
- Typ. 5 external components req'd (incl. crystal)

**Only \$9.00**

plus 75¢ Shipping/Handling

## NOW AT SPECTRONICS

*Full Line*

*Dentron*

including:

- 160-10 mtr Super Tuner
- 160-10 mtr Super Super Tuner
- 160-10 mtr Super Amp  
1 KW CW, 2 KW PEP for  
less than \$500.00
- 20 mtr Trim-Tenna  
2 el. beam with 8½ foot  
turning radius.



## SPECTRONICS, INC.

1009 GARFIELD  
OAK PARK, IL. 60304  
312-848-6777  
TELEX 72:8310

## HOURS

STORE HOURS:

Mon-Thurs 9:30-6:00, Fri. 9:30-8:00  
Sat. 9:30-3:00, Closed Sun. & Holidays.



# SWAN METERS HELP YOU GIVE IT YOUR ALL

## SWR Bridge for 21.95

Our little dual meter SWR bridge indicates relative forward power and SWR simultaneously.

The unit is capable of handling up to 1000 watts and will indicate 1:1 to infinity

VSWR from 3.5 MHz to 150 MHz on 100 microampere meters. Ideal for mobile or home operation with low in-line insertion loss.

Use your Swan credit card. Applications at your dealer or write to Swan.

**SWAN**<sup>®</sup>  
ELECTRONICS

A subsidiary of Cubic Corporation  
305 Airport Rd. Oceanside, CA  
92054 (714)  
757-7525



(Prices FOB Oceanside, CA)



**GREGORY ELECTRONICS**  
*The FM Used  
Equipment People.*

## SUMMER SPECIALS



**MOTOROLA,  
SOLID STATE  
MONITOR  
RECEIVER  
MO1CNB**


1101A, 30-42 MHz 12 V.D.C. and 110 VAC all transistorized, single freq. receiver with A.C. power cord. May be used as a single tone alerting receiver (decoder presently on 2250 Hz). Can also be used as a mobile (12 volt Neg. GND.) with the addition of D.C. power cable NKN6123A (available from Motorola).

**\$98.00**

For tuning from 30-42 MHz, add **\$25.00**


**MOTOROLA 450 MHz  
"MK" I.M.T.S.**

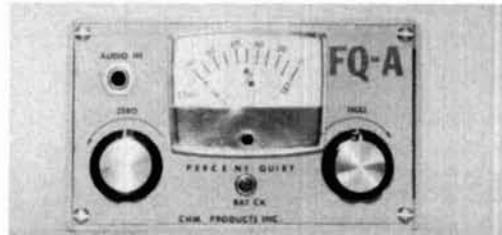12 frequency dial control heads (less mounting bracket) **\$75.00**  
Power/Control cable for above unit **\$25.00**



FINELY, A SYSTEM TO MEASURE THE PERCENT OF QUIETING IN FM RECEPTION. ACCURATE AND CONSISTENT PERCENT QUIETING REPORTS PLUS FINE TUNING FM RECEIVERS AND ANTENNA SYSTEMS MAKES THIS A WINNER! THIS PIECE OF GEAR IS A MUST FOR THE SERIOUS VHF'ER.

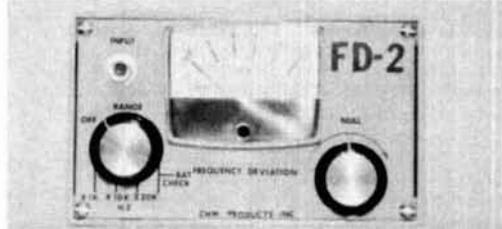FQ-A assembled **\$65.** FQ-A KIT **\$48.**



A 2 METER FREQUENCY DEVIATION METER AT ITS BEST. STABLE, ACCURATE AND EASY TO OPERATE. MULTI-RANGE FOR WIDE OR NARROW FM DEVIATION. SUPPLIED WITH BATTERY AND 146.94 XTAL (other freq avail).

FD-2 assembled **\$85.** FD-2 KIT **\$74.**  
SORRY - NO COD'S CALIF. RES ADD 6% TAX

**CHM products inc.**

p.o. box 6193  
san bernardino, california 92412



**GREGORY ELECTRONICS CORP.**

245 Rt. 46, Saddle Brook, N.J. 07662  
Phone: (201) 489-9000

*KLM exclusive*

# 2-way channel scan

*plus 23 fixed channels*



Now ... continuous, sequential monitoring of your favorite four repeaters or fixed/mobile stations ... safely conveniently ... eyes on the road.

Four channel scanning **both** receive **and** transmit. A transmit control crystal, selected for simplex or repeater duplex as required, switches with each electronically-scanned position. Just flip the

"manual" toggle and break in.

In **addition** ... both **Multi-11** and **U-11** also give you 23 switchable, crystal controlled transmit and receive channels.

Compare prices, operating features (many exclusive) of either transceiver with any other available. You'll find the KLM feature-per-dollar ratio very hard to beat.

- All solid-state ... no tubes.
- Double conversion receiver.
- Two stage crystal filter.
- Two RF stages w/ dual gate MOS FET.
- Fractional microvolt sensitivity.
- Sensitive squelch w/ 0.5uV threshold.
- RIT for receiver  $\pm 5$  kHz.
- Multi-function metering: Power out/"S" units. Also switchable to FM centering.

#### MULTI-11 TRANSCEIVER

Freq.: 144-146MHz (or 146-148MHz)  
Channels: 23, manually switchable, 4, auto-scan.  
Freq. control: Quartz crystals. External VFO or synthesizer input.

**\$325**

- Auto or manual scan (Four channels), transmitter and receiver.
- NBFM, 10W output (switchable to 1W)
- Protective circuit for output transistor.
- Available solid-state amplifiers boost output 70-160 watts.
- Tone osc. w/ sw. For test, control, etc.
- 13.5VDC negative ground.
- Compact: 2.2" (56mm)H, 6.41" (163mm)W, 9" (230 mm) D. Wgt: Approx. 4.4 lbs(2KG).

#### MULTI-U-11

Freq.: 420-450MHz (any 4MHz segment).  
Channels: 23, manually switchable, 4, auto-scan.  
Freq. control: Quartz crystals. External VFO or synthesizer input.

**\$379**

**MULTI-7,  
FULL-FEATURED  
COMPACT, LOW PRICE,  
2-METER  
TRANSCEIVER**



23 xtl chans. (external VFO). NBFM. 10W power out. Sensitive, double-conversion receiver. Mobile. 13.5VDC

**\$239**


# KLM electronics

17025 Laurel Road, Morgan Hill CA 95037 (408) 226-1780, (408) 779-7363



# NEW products

## programmable cw identification kit

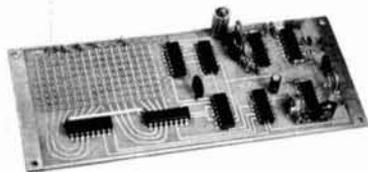

With the new CW ID kit offered by VHF Engineering, you can build a complete identifier for commercial or amateur repeaters in about one evening. The CW ID kit uses high-grade components and comes complete with a drilled epoxy-glass circuit board and programming diodes.

Sufficient diodes are included to allow you to program virtually all repeater calls. To program, all you do is solder the appropriate diodes directly to a matrix on the PC board furnished. The diodes are mounted on the board in a straight-line fashion: three diodes for a dash, one for a dot, and none for a space. Programmed calls can be changed easily by rearranging the diodes. You can program the board for either CW or RTTY, which means added flexibility.

The CW ID kit is available for \$39.95 plus postage; wired and tested it's \$49.95 plus postage from the manufacturer. Drop a note to VHF Engineering, 320 Water Street, P.O. Box 1921, Binghamton, New York 13902 for more information, or use *check-off* on page 126.

## vhf wideband preamplifier

Twin-output preamplifiers are something new offered by Spectrum International for the vhf buff. Designated

MMA50, MMA144, and MMA220 (for the 50-, 144- and 220-MHz bands), these preamps feature two untuned stages with twin outputs for feeding two independent receivers. The preamps are built on a glass-epoxy G10 PC board, which is mounted in a standard die-cast aluminum box. Gain and noise figure are quite respectable as shown in the following table:

	MMA50	MMA144	MMA220
freq range, MHz	50-54	144-148	220-225
nominal gain, dB	20	16	15
noise figure, dB	2.5	2.8	3.4

Power requirements are 12 volts dc at 20 milliamperes; size is 1¼ x 2½ x 4½ inches (32x64x114mm). The specifications apply to a 50-ohm input-output system. The MMA50 and MMA144 sell for \$29.95 each; the MMA220 for \$34.95. Add \$1.00 shipping charge for each unit. Write Spectrum International, P.O. Box 1084, Concord, Massachusetts 01742 for more information, or use *check-off* on page 126.

## rf wattmeter




The trend today in radio transmitters is to have a wattmeter in the transmission line feeding the antenna. The model LPM-880, a new product by Leader Instruments Corporation, is a direct-reading wattmeter that measures radio-frequency power in the 0.5-120 watt range. Power range is selectable by front-panel pushbuttons. Also included is a dummy load for off-the-air power measurements. You can use the LPM-880 for measuring power loss in low-pass filters and coax cables as well as transmitter output. It's supplied with

a sturdy tilt stand for easy reading. Input impedance is 50 ohms.

The LPM-880 is priced at \$149.95. If you'd like more information contact Pat Redko, Leader Instruments Corporation, 151 Dupont Street, Plainview, Long Island, New York 11903 or use *check-off* on page 126.

## power modules for mobile transmitters

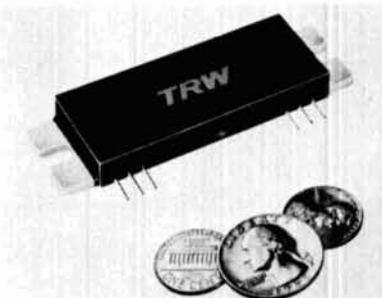

Two new vhf rf power modules designed for mobile or marine transmitter applications are now available from TRW Semiconductors. The modules, designated MV20 and MV30, provide in excess of 20 watts and 30 watts output power respectively across the 140-175 MHz band. The modules operate from standard 12-volt automotive supplies and withstand infinite vswr at any angle, with 2 dB overdrive and 16 volts dc applied. The modules also feature 50-ohm input and output impedances, more than 20 dB gain, and are stable when operating into load vswr's as high as 5:1.

When compared to discrete component designs, these modules offer significant savings in size as well as cost of design, production, and repair. Small quantity pricing is \$39.50 for the MV20 and \$41.50 for the MV30. For further information, contact Sales Manager, Mobile Products, TRW RF Semiconductors, 14520 Aviation Blvd., Lawndale, California 90260 or use *check-off* on page 126.

## loudspeaker for voice communications

The Kriket<sup>®</sup> model KC-55 speaker, new from Acoustic Fiber Sound Systems Incorporated, is designed to reproduce the human voice with maximum intelligibility. It has a frequency

response between 80-10,000 Hz, essential for voice communications. The secret is in the Kriket<sup>®</sup> 5-inch-diameter (127mm) permanent-magnet speaker and an exclusive AFS Working Wall<sup>®</sup> enclosure, which controls sound by eliminating distortion. A snap-lock mounting bracket permits adjusting the speaker in any desired direction. The KC-55 speaker is packaged for base-station use, but you can adapt it for mobile use simply by removing the base for easy mounting inside a vehicle.

The KC-55 handles 7 watts rms of audio, has an input impedance of 8 ohms, and is furnished with a 6-foot (1.8m) connector cord and a standard miniplug. More information is available from acoustic Fiber Sound Systems, Incorporated, 2831 North Webster Avenue, Indianapolis, Indiana 46219, or use *check-off* on page 126.

## digital multimeter



Non Linear Systems of Del Mar, California, announces a new addition to their Volksmeter family. It's the LM-3.5 Volksmeter Plus, a 3½-digit multimeter that fits into the palm of your hand. The 3½-digit feature means that the instrument reads out three digits plus 100 percent overrange. It's a true multi-function, multirange meter, rugged enough for field use yet useful for production or hobby work. Rechargeable nicad batteries and a 115-volt charger are standard equipment.

The LM-3.5 has four ranges for dc and ac volts, to 1000 volts dc or 1000 volts peak ac, with 1-millivolt resolution on the 2-volt scale. The resistance scale has one-ohm resolution and five ranges, from 2000 ohms to 20 megohms full scale. Ac and dc current can be measured in three ranges using shunts furnished. Automatic polarity is featured. Input impedance is 10 megohms on all voltage ranges. A large light-emitting diode display (0.3 inch or



## INTRODUCES THE VERSATILE NEW



# HR-312

-  **More Channels...at the flip of a switch**  
 Unlock the unique mode switch and 12 channels become 144
-  **More Sensitivity, Less Interference.**  
 .25  $\mu$ V Sensitivity plus 75 db adjacent channel selectivity and 70 db image rejection
-  **More Power Out**  
 35 watts nominal with a minimum of 30 watts across the band

... for a lot less

**\$269<sup>00</sup>**

Amateur Net

© 1976  **Regency ELECTRONICS, INC.** 7707 Records Street  
 Indianapolis, Indiana 46226

## THE FM LEADER

2 METER 

220 MHz 

6 METER 

440 MHz 

# NOW . . . from KLAUS RADIO

## Kenwood's TS-700A



This is the 2-meter rig you've been hearing about. Forty-four channels, tunable VFO, SSB-CW plus that hard-to-beat Kenwood quality.

### Features:

144 to 148 MHz coverage - SSB (upper & lower), FM, AM, and CW - Solid State Circuitry - Complete with mic and built-in speaker - operates on 120/220V, 50/60 Hz or 12-16V D.C. - Size: 278 (w) x 124 (h) x 320 (d) mm. - Wt: 11 Kg.

All this and much, much more for .....\$700.00 ppd. in U.S.A.

## The Yaesu FT-221

is something else. One beautiful 2 meter Transceiver for Mobile or Base Station Duty. Here's another winner from Yaesu that you'll want to own.



### Features:

144 to 148 MHz band coverage - SSB (upper & lower), AM, FM or CW - operates on 120/220V, 50/60 Hz or 13.5V D.C. - 11 crystal channels per band segment equals 88 channels - Built-in speaker - Size: 200 (w) x 125 (h) x 295 (d) mm. - Wt: 8.5 Kg

Lots of Performance and Quality for .....\$679.00 ppd. in U.S.A.

Send SASE NOW for detailed info on these systems as well as on many other fine lines. Or, better still, visit our store Monday thru Friday from 8:00 a.m. thru 5:00 p.m.

# KLAUS RADIO Inc.

8400 N. Pioneer Parkway, Peoria, IL 61614  
Jim Plack WB9BGS — Phone 309-691-4840

## ANTENNA SUPERMARKET - PO Box 338, Dept. H, Chambersburg, PA 17201

**DIPOLES AND WIRE ANTENNAS**, complete with 100' Mil. Spec. Coax, Balun, Connector, 100' Rope, Copper Ant. Wire, Insulators:

80/40/15 parallel dipole .....	\$36.95	160 short, 130' length .....	\$36.95
40/20/15 parallel dipole .....	\$30.95	80 short, 63' length .....	\$31.95
80/40 trap dipole .....	\$41.95	40 short, 33' length .....	\$28.95
40/20 trap dipole .....	\$36.95	Single band models from .....	\$24.95

**VERTICALS** — complete with Universal Mounting Base, Folds to 5' for Easy Transport. Hvy Duty Aluminum Tubing.

20/15 trap, 13' hgt. ....	\$29.95	160 compact 23' hgt. ....	\$44.95
40/20/15 trap 22' hgt. ....	\$44.95	80 compact 20' hgt. ....	\$39.95
80/40/20 trap 30' hgt. ....	\$69.95	40 compact 15' hgt. ....	\$34.95
80/40/15 trap 20' hgt. ....	\$59.95	20/15/10 full size vertical	\$29.95
10 meter cov. for above add .....	\$9.95		

TO ORDER — Include \$1.95 shipping (\$2.95 West Coast)  
24 hour shipment. 30 day guarantee.  
For Info: SASE or 1st Class Stamp.



### NEW Apartment/Portable


Apt. roof or patio, camper, trailer, motor home. All bands 80-10, folds to 5' easily. 13' height.

80-40-20-15-10 \$49.95

7.6mm) and small package size of 1.9 x 2.7 x 4 inches (48x69x102mm) is a good example of what can be done with large-scale integration technology.

The LM-3.5 Voltmeter Plus retails for \$147.00, including input leads, rechargeable nicads, battery charger and current shunts. Optional accessories, such as carrying case, high-voltage probe, desk stand, panel-mount flange, and universal test-lead set are also available. For information on these accessories as well as other data, write Non Linear Systems, Incorporated, P.O. Box N, Del Mar, California 92014, or use *check-off* on page 126.

## pc design template

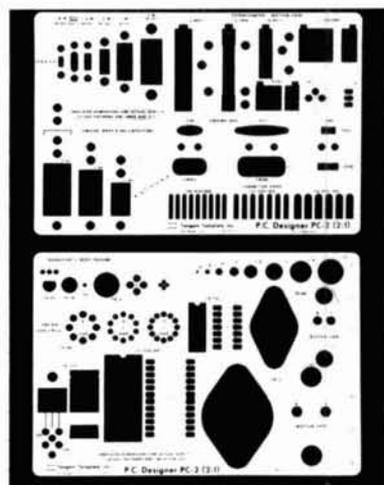

The new *PC Designer* template set has been updated to include additional, frequently used component packages and mounting patterns for printed-circuit layouts and assembly drawings. All patterns conform to guidelines established by Mil-Std 275C and The Institute of Printed Circuits bulletin CM-770. Component mounting patterns are on grid centers which enable the designer to design for automatic insertion assembly equipment.

Fixed and variable resistors, axial and radial lead capacitors, and several semiconductor packages are included. Template use reduces circuit-board design time by eliminating constant referral to manuals and data sheets for package dimensions. The template sets are available from stock in actual, twice, and four times size layout ratios and are priced from \$12.00 to \$20.00 per set. Write Tangent Template, Inc., Post Office Box 20704, San Diego, California or use *check-off* on page 126.

## multipurpose cw-operating aid

From SEA International comes the RST 599, an instrument that combines four features in one to enhance CW operation. Packaged in an attractive cabinet, the RST 599 includes a universal keying monitor, code-practice oscillator, CW filter, and a feature called the 599 function.

The RST 599 can be used with any key, keyer, transmitter or transceiver. The CW filter has a nominal center frequency of 850 Hz, with a nominal 3-dB bandwidth. The 599 function extracts and reconstructs the selected signal and, according to the manufacturer, "makes it noise free and RST 599 every time." Inputs are *audio in*, for connection to any receiver output line, and *key in*, for connection to any key or keyer. Outputs are *speaker out*, which drives any speaker of 4 ohms or more; *headphones*, for phones of 4 ohms or more and *transmitter*, which connects your key to any transmitter or receiver. When the 599 function is switched off, receiver output is connected directly to your speaker.

The RST 599 is priced in the \$90.00 range and is fully warranted for one year against material or manufacturing defects. If you'd like more information, write SEA International, P.O. Box 32, Milpitas, California 95035, or use *check-off* on page 126.

## programmable scanning receiver



The Opti/Scan, a 10-channel scanning monitor receiver by SBE (Linear Systems, Incorporated), offers some unusual features that will appeal to the vhf enthusiast. Frequencies are digitally synthesized, which means you can forget about buying crystals to obtain desired coverage. You program the receiver yourself to scan channels of interest. Programming is easy. You simply refer to a code list supplied for desired scanning frequencies, program a

# 6 Digit LED Clock Kit - 12/24 hr.

**\$950** ea. IN QUANTITIES OF 1 TO 5

**\$850** ea. IN QUANTITIES OF 6 OR MORE

### KIT INCLUDES:

- INSTRUCTIONS
- QUALITY COMPONENTS
- MONEY BACK GUARANTEE
- 50 or 60 Hz OPERATION
- 12 or 24 HR OPERATION

- 6 — LED Readouts (FND-70 .25 in. Red, com. cathode)
- 1 — MM5314 Clock Chip (24 pin)
- 13 — Transistors
- 3 — Switches
- 5 — Capacitors
- 5 — Diodes
- 9 — Resistors
- 24 — Molex pins for IC socket

ORDER KIT #850  
AN INCREDIBLE VALUE!

"Kit #850 will furnish a complete set of clock components as listed. The only additional items required are a 7-11 VAC transformer, a circuit board and a cabinet, if desired."

Printed Circuit Board for Kit #850 or #850-4 (etched & drilled Fiberglass)	\$2.95
Standard Transformer 115VAC/8VAC	\$1.50
Molded Plug Transformer 115VAC/10VAC (With Cord)	\$2.50
Plexiglas Cabinet II Red Chassis, White Case (see below)	\$5.95
"Mini-brite" discrete LED's (for colon in clock display)	pkg. of 5 for \$1.00

KIT #850-4 SAME AS #850 BUT .4" LED's ..... **\$11.95**

60 HZ XTAL TIME BASE KIT — Use your digital clock from any 12 Volt DC source:

Power req: 5-15 VDC/2.5 mA @ 12 VDC Car—Boat—Etc. **\$5.95 ea.**  
Accuracy: (adjustable) 2 PPM/3.6 MHz xtal **6/\$28.95**  
Size: PC board approx. 1" x 2"  
Complete - Single IC kit with info for easy hook-up to most IC clock.

**\$4.95** purchased with any clock kit

NOW AVAILABLE — TB-IC (wired, tested & calibrated) ..... **\$9.95**

**JUMBO DIGIT CONVERSION KIT** — For LED Clocks. Kit provides a multiplex display PC board and six .5" brite LED's, (FND-503's or FND-510's). LED's require only 5 mA/seg and can be driven by most any LED clock circuit. Data for displays and hook-up included. (This PC board will mate point to point with kit #850 circuit board) specify Common Cathode or Anode **\$9.95**

**JUMBO DIGIT CLOCK KIT COMPLETE** — Kit features six .5" red LED's, all components, PC boards, plug transformer, line cord, etc. 50/60 HZ op., 12 or 24 hr, MM5314 IC. (Will fit Cab. I) **Kit #5314-5 Complete Less Case \$19.95**

# 6 Digit LED Clock - Calendar - Alarm Kit

● 12/24 HR TIME ● JUMBO DIGITS (MAN-64) ● 28-30-31 DAY CALENDAR ● AC FAILURE/BATTERY BACK-UP ● 24 HR ALARM — 10 MIN. SNOOZE ● ALTER-NATES TIME (8 SEC) and DATE (2 SEC) OR DISPLAYS TIME ONLY AND DATE ON DEMAND ● 50/60 Hz OP. ● THIS KIT USES THE FANTASTIC CT-7001 CHIP. FOR THE PERSON THAT WANTS A SUPER CLOCK KIT (TOO MANY FEATURES TO LIST)! THIS IS A COMPLETE KIT (LESS CASE) including Power Supply, Line Cord, Drilled PC Boards, etc.

**39.95** ORDER KIT #7001B (CASE NOT INCLUDED)

KIT #7001-C SAME AS #7001-B BUT HAS DIFFERENT LED's. USES 4 DL-747 .63" DIGITS & 2 MAN-7 .3" DIGITS FOR SECONDS. COMPLETE KIT, Less Case. **\$42.95**

**PRINTED CIRCUIT BOARDS** for CT-7001 Kits sold separately with assembly info. PC Boards are drilled Fiberglass, solder plated and screened with component layout. Specify for #7001B or #7001C. (Set of 2) **\$7.95**

### CABINET I

3" HIGH  
6 1/4" WIDE  
5 1/2" DEEP



Chassis Serves As Bezel To Increase Contrast of Digital Displays. Use Gray With Any Color — Red With Red Displays Only (Red LED's with Red Chassis Brightest)

**\$6.95 ea.**

**GREAT FOR CLOCK & Clock-Calendar Kits**  
White Plexiglas Case  
Specify RED or GRAY  
Plexiglas Chassis

### CABINET II

2 1/2" HIGH  
4 1/2" WIDE  
5 1/2" DEEP



Red Chassis Serves As Bezel To Increase Contrast of LED Displays

**\$5.95 ea.**

**GREAT FOR SMALLER CLOCK KITS.** (Ideal for Kit #850 or #850-4 above) All Plexiglas Red Chassis, White Case.

### PLEXIGLAS FOR DIGITAL BEZELS

Gray or Red Filter **95¢ ea.**

3" x 6" x 1/8" Approx. Size **4/\$3.00**

### 7-SEG LED READOUTS

**95¢ ea. or 10/\$8.50**

MAN-7	Red	CA	.3"
MAN-8	Yellow	CA	.3"
DL-707	Red	CA	.3"
FND-359	Red	CC	.4"

Your Choice — Guaranteed Good

LM-309K **5V. REG.**  
**\$1.25 ea. or 5/\$5.00**

IN914 **25/\$1.00**

IN4148 **25/\$1.00**

IN4005 **12/\$1.00**

**25 AMP FULL WAVE BRIDGE 100 PIV**

**\$1.95 ea.**  
**3/\$5.00**

### Fairchild Super Digit FND-359



.4" Char. Ht.  
7 segment LED  
RED Com. Cath.  
Direct pin replacement for popular FND-70.

**95¢ ea, 10/\$8.50**  
**100/\$79.00**

# OPTOELECTRONICS, inc.

BOX 219 • HOLLYWOOD, FLA. 33022 • (305) 921-2056

master charge




BankAmericard, Mastercharge or C.O.D. orders accepted by phone day or evening.

We Pay All Shipping in Continental U.S.A. Orders under \$15 add \$1 handling. Fla. res. add 4%.
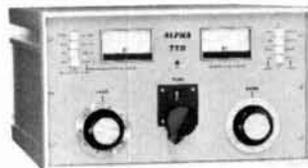
# Why Buy An ALPHA?

BECAUSE EVERY ALPHA HAS SIGNIFICANT CAPABILITIES THAT SIMPLY AREN'T AVAILABLE IN ANY OTHER LINEAR . . . LIKE UNLIMITED OPERATION AT A FULL KILOWATT AVERAGE INPUT - ALL MODES - COMBINED WITH TABLE TOP CONVENIENCE. FOR POWER, EVERY ALPHA USES A 1.5 KVA (OR LARGER) CONTINUOUS DUTY TRANSFORMER, MODERN CERAMIC TUBES DESIGNED BY EIMAC FOR HEAVY DUTY APPLICATIONS, AND A COOLING SYSTEM THAT KEEPS EVERYTHING COOL - EVEN IN CONTESTS!



ALPHA 77D is widely recognized as 'THE ULTIMATE' in linears. Nothing else combines its power, quality, and versatility . . . including full break-in, 1.8-30 MHz coverage, and whisper-quiet operation. \$2995. Contact ETO for current delivery information.

ALPHA 374 - the most convenient linear you can buy - provides "no-tune-up" 10-80 meter operation plus the smallest size and weight of any maximum-legal-power linear amplifier. Its performance and durability are thoroughly proven. Immediate delivery from ETO at \$1395.



The new ALPHA 76 carries a price tag that no other "full tilt" linear can beat, plus ALPHA quality, 10 thru 160 meter coverage, and ETO's full-year factory warranty. This modern powerhouse is available from ETO now at just \$895.

WHY BUY AN ALPHA? BECAUSE YOU JUST CAN'T GET THE SAME CAPABILITIES ANYWHERE ELSE. Write or call ETO direct for illustrated literature . . . or to order your ALPHA.

**ETO** EHRHORN TECHNOLOGICAL OPERATIONS, INC.  
BROOKSVILLE, FLORIDA 33512  
(904) 796-1428

**NOW  
CFP COMMUNICATIONS  
HAS YAESU  
IN STOCK!**



FT-101E TRANSCEIVER

Mail Orders accepted. N. Y. residents add sales tax. See us for all your Amateur Radio needs. SASE will get our list of used Amateur Equipment.

Jim Beckett WA2KTJ  
Manager  
Bryant Hozempa, WB2LVW  
Sales  
Dave Fliinn, W2CFP  
Owner

**CFP COMMUNICATIONS**

211 NORTH MAIN STREET  
HORSEHEADS, N. Y. 14845  
PHONE: 607-739-0187



Expanded Store Hours  
Tues.-Thurs. 10:00-7:00 p.m.  
Fri. 10:00-9:00 p.m.  
Sat. 10:00-7:00 p.m.  
Fri. & Sat. subject to  
Hamfest weekends  
Closed Sun. & Mon.

plastic card according to instructions, insert the card into a slot on the receiver front panel, and internal circuits do the rest. No need to worry about programming errors - you can see what you've programmed and can check for accuracy. As many cards as desired may be programmed - up to 16,000 frequencies may be selected. Program cards are only \$2.25 each.


Any ten channels are available between 30-50, 150-170, 450-470, and 490-510 MHz. Two-meter-band coverage (140-160 MHz) is available on special order. The Opti/Scan receiver is furnished with antennas that cover the vhf-uhf utility bands mentioned above. Receiver sensitivity is 0.5 microvolt for 12 dB SINAD. Dimensions are 2½ inches high, 7-¾ inches wide, and 10 inches deep (6.4x19.7x25.4cm). Operating voltages are 13.8 Vdc or 115 Vac 60 Hz. The list price is \$369.95. For further information contact Linear Systems, Incorporated, 220 Airport Boulevard, Watsonville, California 95075, or use check-off on page 126.

## 1976 Allied catalog

Now available from Allied Electronics is the 1976 *Engineering Manual and Purchasing Guide*. This up-to-date manual is a must for the service bench or engineering library. Engineers, radio amateurs, technicians, and hobbyists will appreciate the complete specifications, illustrations and information which describe each product.

This newest edition of the well-known Allied Guide offers 228 pages of high-quality electronic parts and equipment from Allied and other leading manufacturers. You can choose from a wide variety of new products, in addition to traditional items which have set in the industry's standards. The guide contains cable, solid-state devices, test equipment, connectors, relays, tools, capacitors, and countless other electronic parts for virtually any application. Allied offers bulk pricing for quantity buyers, and nationwide warehouses assure prompt delivery of these often hard-to-get items.

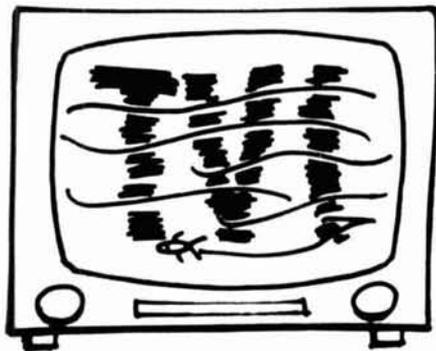A \$5 value for only \$1 to help cover postage and handling. Contact Allied Electronics, Dept. 76, 401 East 8th Street, Fort Worth, Texas 76102 or use check-off on page 126.




# A properly designed filter can tame the beast...

Whatever you call it, the common denominator is "I" for Interference.

The study of interference to consumer products such as TV sets, hi-fis, and the like from radio transmitters is a complex subject. For a primer, see p. 11, "QST Magazine" for March, 1976. We do know that radiation interference can be greatly reduced and perhaps eliminated by the use of a well-engineered, quality-built TVI filter. The low-pass type for the transmitter is at times not enough...a high-pass type for the TV set may also be required. But, here's the rub! If a filter is not properly designed and engineered, it may not work like a filter at all. At the R. L. Drake Company, we've been designing and building filters for over 30 years...since before the days of "Uncle Miltie." And, these are real filters...not toys.

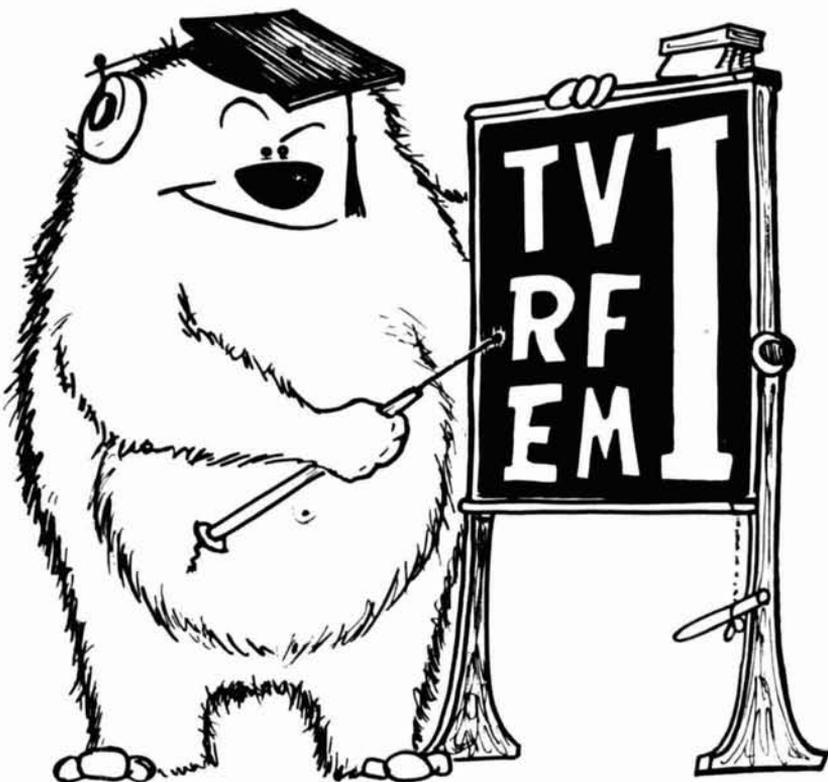For your TVI answer, choose one or more of the following:



## High Pass Filters for TV Sets...

provide more than 40 dB attenuation at 52 MC and lower. Protect the TV set from amateur transmitters 6-160 meters.



**TV-300-HP**  
For 300 ohm twin lead



**TV-75-HP**  
For 75 ohm coaxial cable

**DRAKE**

## Low Pass Filters for Transmitters

have four pi sections for sharp cut off below channel 2, and to attenuate transmitter harmonics falling in any TV channel and FM band. 52 ohm. SO-239 connectors built in.



### TV-3300-LP

1000 watts max. below 30 MHz. Attenuation better than 80 dB above 41 MHz. Helps TV i-f interference, as well as TV front-end problems.



### TV-5200-LP

200 watts to 52 MHz. Ideal for six meters. For operation below six meters, use TV-3300-LP or TV-42-LP.



### TV-42-LP

is a four section filter designed with 43.2 MC cut-off and extremely high attenuation in all TV channels for transmitters operating at 30 MHz and lower. Rated 100 watts input.

For more information on these and other fine Drake products, please contact:

**R. L. DRAKE COMPANY**



540 Richard St., Miamisburg, Ohio 45342  
Phone: (513) 866-2421 • Telex: 288-017

When you step up to big power we've got the block-buster linear amplifier that will give you a full 2000 watts P.E.P.—all the law allows—with the features you need for a clean signal with great linearity.

It's the Swan Mark II, an amateur radio standard for top power single sideband rigs. One-hundred watts of drive is all you need to go all the way on all bands from 10 to 80 meters. And with the Mark II, the price includes the separate, matching power supply. Both RF deck and power supply are forced-air cooled with high-volume, low-RPM, low-noise blowers.

But if you prefer finesse to force, our

Cygnets 1200X is your ticket to new kicks in amateur radio. Linearity is excellent, efficiency is exceptionally high, power supply is built in, and features like provision for external ALC give you the flexibility you want to get the most out of your rig on all bands.

And there's more to come: The Swan Cygnets 1200X gives you a solid 1200 watts P.E.P. on single sideband—as much power as most people ever need—and you come away with your pockets bulging with change.

Whether you do it by force or finesse, seize power today with a Swan linear amplifier. You can get it with a Swan credit card. Applications at your dealer or write to us.

Mark II 2000-watt linear amplifier with 120/220V power supply. . . . . \$849.95  
 Cygnets 1200X 1200-watt linear amplifier complete with built in 110/220V power supply. . . . . \$349.95

(Prices FOB Oceanside, CA)

Dealers throughout the world



A subsidiary of Cubic Corporation  
 305 Airport Road, Oceanside, CA 92054  
 (714) 757-7525

# WHETHER YOU GO FOR POWER OR FINESSE, SWAN LINEARS ARE THE WAY TO GO.



# SWAN AUTHORIZED DEALERS.

## ARKANSAS

Moory's Electronics, DeWitt

## ARIZONA

The Radio Shop, Kingman

## CALIFORNIA

Antenna King, Torrance  
Fontana Electronics, Fontana  
Gary Radio, Inc., San Diego\*  
Ham Radio Outlet, Burlingame  
Henry Radio, Inc., Los Angeles\*  
Henry Radio, Inc., Anaheim\*  
Quement Electronics, San Jose  
Western Radio, San Diego

## COLORADO

CW Electronics Sales, Denver\*

## FLORIDA

Amateur Radio Center, Inc., Miami\*  
Amateur Electronics Supply, Orlando\*

## ILLINOIS

Erickson Communications, Inc., Chicago

## INDIANA

Hoosier Electronics, Terre Haute

## IOWA

Bob Smith Electronics, Ft. Dodge

## KANSAS

Associated Radio Communications, Overland Park  
Electronics Inc., Salina\*

## LOUISIANA

ALS Electronics, Alexandria

## MARYLAND

Amateur Radio, Limited, Silver Spring  
Professional Electronics, Baltimore

## MASSACHUSETTS

Tufts Radio Electronics, Medford

## MICHIGAN

Electronics Distributors, Inc., Muskegon\*  
Radio Supply & Engineering Co., Clawson

## MINNESOTA

Electronics Center, Inc., Minneapolis\*

## MISSISSIPPI

Electronics World Inc., Pascagoula

## MISSOURI

Esco Amateur Sales, St. Joseph  
Ham Radio Center, St. Louis  
Henry Radio, Inc., Butler\*

## MONTANA

Conley Radio Supply, Billings

## NEW HAMPSHIRE

Evans Radio, Concord\*

## NEW JERSEY

Atkinson & Smith, Inc., Eatontown  
George Marko, Little Falls\*\*

## NEW MEXICO

Electronics Module, Hobbs  
Gene Hansen Company, Corrales\*

## NEW YORK

Harrison Radio, Farmingdale  
Westchester Communications Specialists, Yonkers\*\*

## NORTH CAROLINA

Freck Radio & Supply Company, Asheville  
Slep Electronics Company, Otto

## OHIO

Amateur Electronics Supply, Cleveland\*  
Coston Electronics, Cincinnati

## OKLAHOMA

Radio Store Inc., Oklahoma City

## OREGON

Portland Radio, Portland\*

## PENNSYLVANIA

Hamtronics, Trevoze  
Whiteside Electronics, Pittsburg

## SOUTH CAROLINA

Amateur Radio Electronics, Inc., Cayce

## SOUTH DAKOTA

Burghardt Amateur Center, Watertown

## TENNESSEE

Freck Radio & Supply Co., Johnson City

## TEXAS

Appliance and Equipment Co., San Antonio  
Electronic Module, Odessa  
Electronics Center Inc., Dallas\*  
Madison Electronics Supply, Inc., Houston  
Waco Communications, Waco

## WASHINGTON

ABC Communications, Seattle  
Amateur Radio Supply Co., Seattle\*  
HCJ Electronics, Spokane

## WISCONSIN

Amateur Electronic Supply, Milwaukee\*

\*Sales and warranty repair station

\*\*Warranty repair only



A subsidiary of Cubic Corporation  
305 Airport Road, Oceanside, CA 92054  
(714) 757-7525

## How You Can Convert Your Rohn 25G Tower to a FOLD-OVER

**CHANGE, ADJUST OR JUST  
PLAIN WORK ON YOUR  
ANTENNA AND NEVER LEAVE  
THE GROUND.**

If you have a Rohn 25G Tower, you can convert it to a Fold-over by simply using a conversion kit. Or, buy an inexpensive standard Rohn 25G tower now and convert to a Fold-over later.

Rohn Fold-overs allow you to work completely on the ground when installing or servicing antennas or rotors. This eliminates the fear of climbing and working at heights. Use the tower that reduces the need to climb. When you need to "get at" your antenna . . . just turn the handle and there it is. Rohn Fold-overs offer unbeatable utility.



Yes! You can convert to a Fold-over. Check with your distributor for a kit now and keep your feet on the ground.

**AT ROHN YOU GET THE BEST**



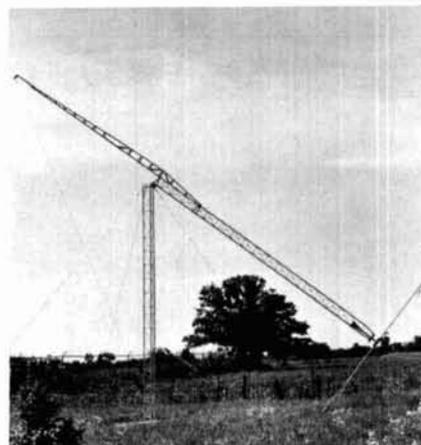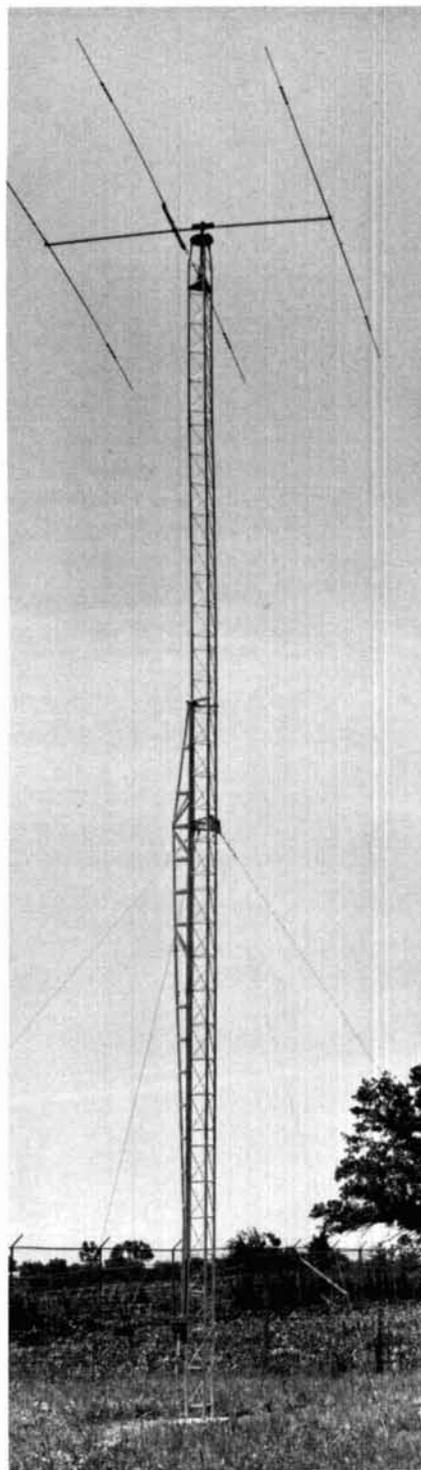**Unarco-Rohn**

Division of Unarco Industries, Inc.  
P.O. Box 2000, Peoria, Illinois 61601



# GO AUTO-PATCH THE EASY WAY!

**BUY AN ICOM IC-230 AT THE  
REGULAR PRICE \$489.00 AND GET THE  
TOUCH TONE HANDSET FREE!**

PLUGS DIRECTLY INTO IC-230  
AND YOU ARE READY TO GO.

Works with IC-22A and others by  
wiring accessory socket for handset.  
TOUCH TONE HANDSET ONLY \$79.00

**IMMEDIATE DELIVERY FROM STOCK**

UTAH FM SALES  
1365 East 5360 South  
Salt Lake City, Utah 84117  
801 533-0101  
24 hour message  
recorder  
801 278-3156



## Now! LED Displays for: Experimenters Schools Hams

Calculators • Counters  
• Clocks • Instruments



Guaranteed No. 1 Industrial Quality

All Displays Are RED, COMMON-CATHODE MULTIPLEX

- 0.11 Inch, Standard 9 Digit Calculator & Counter R7H-122-9 ..... \$4.30 ea
- 0.12 Inch, 12 Digit Scientific & Micro-Processor R7H-11S-12 ..... \$5.75 ea
- 0.20 Inch, 3-1/2 Digit Meter & Instrument Display R7H-192-4 ..... \$4.30 ea
- 0.50 Inch, Clock & Timer Display R7R-502-4 ..... \$5.25 ea
- 0.27 Inch, Single Digit For All Applications B27R ..... \$1.00 ea


SPECIFICATIONS INCLUDED WITH EACH SHIPMENT

Send Check or Money Order to:

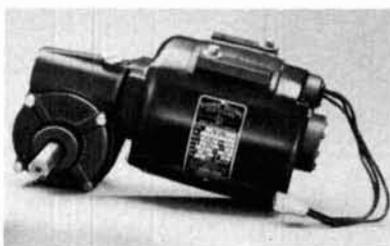**Bowmar**

4900 East Indian School Road  
Phoenix, Arizona 85018  
Phone: (602) 959-4760

Minimum Order \$10.00 Please  
Arizona Residents Include 5% Sales Tax  
Quantity Inquiries Invited



**HIGH QUALITY HEAVY DUTY GEAR-  
MOTORS** — made by **BODINE** as  
used by Xerox — surplus but guar-  
anteed perfect.

Gear Input 1650 RPM — Output 28  
RPM — Shaft  $\frac{5}{8}$ " steel with  $\frac{1}{8}$ "  
Key and Keyway — capacity 44  
Inch/lbs.

115 V 60 Cycle 1/15 HP Complete  
with Capacitor.

Price \$16. F.O.B. Dallas, Shipping  
Weight 20#. Send Cash with order  
— shipped UPS or advise.



5626 DYER ST., DALLAS, 75206

### Radio Amateurs Reference Library of Maps and Atlas



**WORLD PREFIX MAP** — Full color, 40" x 28",  
shows prefixes on each country . . . DX zones,  
time zones, cities, cross referenced tables

**\$1.25**

**RADIO AMATEURS GREAT CIRCLE CHART OF  
THE WORLD** — from the center of the United  
States! Full color, 30" x 25", listing Great Circle  
bearings in degrees for six major U.S. cities:  
Boston, Washington, D.C., Miami, Seattle, San  
Francisco & Los Angeles.

**\$1.25**

**RADIO AMATEURS MAP OF NORTH AMERICA!**  
Full color, 30" x 25" — includes Central Amer-  
ica and the Caribbean to the equator, showing  
call areas, zone boundaries, prefixes and time  
zones, FCC frequency chart, plus useful informa-  
tion on each of the 50 United States and other  
Countries

**\$1.25**

**WORLD ATLAS** — Only atlas compiled for radio  
amateurs. Packed with world-wide information  
— includes 11 maps, in 4 colors with zone  
boundaries and country prefixes on each map.  
Also includes a polar projection map of the  
world plus a map of the Antarctica — a com-  
plete set of maps of the world. 20 pages. Size  
8 3/4" x 12"

**\$2.50**

Complete reference library of maps — set of 4  
as listed above

**\$3.75**

See your favorite dealer or order direct.

Mail orders please include 75¢ per order  
for postage and handling.

RADIO AMATEUR

**callbook INC.**

**WRITE FOR  
FREE  
BROCHURE!**



Dept. E 925 Sherwood Drive  
Lake Bluff, Ill. 60044

# IF YOU ARE ON 144, 220 OR 432 AND HAVE WORKED A REPEATER...

It was probably this one.



The RPT 144B, RPT 220B and RPT 432 are self-contained — all solid state machines. Conservatively rated, high quality components, assures EXCELLENT RELIABILITY. Careful consideration has been given to both interfacing and control flexibility.

RPT 144B or RPT 220B Kit .....	\$465.96
RPT 432B Kit .....	515.95
RPT 144B or RPT 220B factory wired and tested .....	695.95
RPT 432B factory wired and tested .....	795.95
RPT 50B soon to be announced .....	N.A.
RPT 28B soon to be announced .....	N.A.

## WORK ALL REPEATERS WITH OUR NEW SYNTHESIZER II



The Synthesizer II is a two meter frequency synthesizer. Frequency is adjustable in 5 KHz steps from 140.00 MHz to 149.995 MHz with its digital readout thumb wheel switching. Transmit offsets are digitally programmed on a diode matrix, and can range from 10 KHz to 10 MHz. No additional components are necessary!

Kit . . . . . \$169.95    Wired and tested . . . . . \$239.95  
*Export prices slightly higher.*

### Available at these dealers:

- A-B-C Communications  
Seattle, WA 98155
- A-B-C Communications  
Everett, WA
- Alpha Electronic Labs  
Columbia, Missouri 65201
- Amateur Electronic Supply  
Milwaukee, Wisc. 53216
- Amateur Wholesale Electronics  
Miami, FL 33156
- Amateur Wholesale Electronics  
Ashland, KY 41101
- Ayre's Ltd.  
St. John's, Newfoundland
- Barry Electronics Corp.  
New York, NY 10012
- Frank L. Beier Radio, Inc.  
New Orleans, LA 70118
- Burghardt Amateur Center, Inc.  
Watertown, SD 57201
- C & A Electronic Enterprises  
Carson, CA 90745
- CDS Electronics & Hobbies Unltd.  
Emerado, ND 58228
- CFP Enterprises  
Horseheads, NY 14845
- Communications Electronics  
Fond du Lac, WI 54935
- Communication Specialties Co.  
Aurora, CO 80012
- Communication Systems  
Bourbon, IN 46504
- Communication Unlimited  
Whitmore Lake, MI 48189
- COSYSCO, Inc.  
Sodus, NY 14551 (Export only)
- Harry G. Crofts  
Northville, Mich. 48167
- Delmar Electronics, Inc.  
West Babylon, L.I., NY 11704
- Derrick Electronics, Inc.  
Broken Arrow, OK 74012
- Edison Electronics, Inc.  
Santurce, P.R.
- Electronic Enterprises  
Rio Linda, CA 95673
- GFL Electronics Co.  
Pickering, Ontario Canada
- Klaus Radio, Inc.  
Peoria, IL 61614
- Loffler Electronics  
Ogdensburg, NY 13669
- Radio Communications Co., Inc.  
Roanoke, VA 24106
- Radio Store, Inc.  
Oklahoma City, OK 73100
- Radio Supply & Engineering Co., Inc.  
Detroit, Mich. 48200
- SON Electric  
Fresno, CA 93727
- Soundcom (VHF-UHF Outlet)  
Akron, OH 44314
- Spectronics, Inc.  
Oak Park, IL 60304
- W. Spindler Electronic Service  
Rome, NY 13440
- Teco Electronics  
Garland, TX 75040
- Tele-Com Electronics  
San Jose, CA 95100
- Tufts Radio Electronics  
Medford, Mass. 02155
- Vegas Radio  
Las Vegas, NV 89106
- VHF Communications  
Jamestown, NY 14701
- Vickers Electronics  
Durham, NC 27702
- Westcom  
San Marcos, CA 92069
- West Indies Sales Co., Ltd.  
Miami, FL 33166

**Vhf engineering**  
DIVISION OF BROWNIAN ELECTRONICS CORP.

320 WATER ST. • P.O. BOX 1921  
 BINGHAMTON, N.Y. 13902 • 607-723-9574



WE HONOR  
master charge  
THE INTERBANK CARD



BANKAMERICARD

# DON & BOB'S SUPER BUYS

HY GAIN TH6DXX .....	\$192.00
MOSLEY CLASSIC 33 .....	\$179.00
GREAT BUYS ON 204BA, 402BA BN86 .....	\$15.95
CDE HAM-II ROTOR .....	\$129.00
18HT HY TOWER .....	\$218.00
TRI-EX W SERIES TOWERS (FOB CALIF.) BELDEN 8214 RG-8/U FOAM COAX .....	23¢/FT.
BELDEN 8237 RG-8/U .....	19¢/FT.
BELDEN 8 WIRE ROTOR CABLE #8448 .....	14¢/FT.
AMPHENOL PL-259 .....	59¢
CALL FOR QUOTES — TS-520, TS-820, TS-700A, 210X. MORE HY-GAIN SPECIALS (Limited Quantity):	
2BDQ, 40-80M DOUBLET .....	\$39.00
TH3MK3, 3 ELEMENT BEAM, 20, 15, 10 .....	\$160.00
HY-GAIN 18 AVT-WB VERTICAL plus 100 ft. of Belden RG-8/U Coax .....	\$100.00
KLM MULTI 2000A (Limited Quantity) .....	\$579.00
SWAN SWR-1 .....	\$18.95
ELECTRA BEARCAT 101 .....	\$319.00
TELSTAR 12V, 2 AMP REGULATED SUPPLY .....	\$30.00
BOOKS .....	

CALL TODAY FOR ITEMS NOT LISTED!

ALL PRICES FOB HOUSTON

## MADISON ELECTRONICS SUPPLY, INC.

1508 MCKINNEY AVENUE

HOUSTON, TEXAS 77002

713/658-0268

Nites 713/497-5683

### TOUCH-TONE DECODER



• Dual tone decoder decodes one Touch-Tone digit.

• Available for 1, 2, 3, 4, 5, 6, 7, 8, 9, 0, F, A and other dual tones 700-3000 Hz.

• Latch and reset capability built-in.

• Operates on any dc voltage from +9 to +30 v.

- COR control built-in.
- Relay output SPST 1/2-amp.
- Octal plug-in case.
- Compact 1-3/4" square, 3" high.
- Free descriptive brochure on request.

T-2 Touch-Tone Decoder...\$39.95 PPD.  
Specify digit or tone frequencies.  
(Include sales tax in Calif.)

### PALOMAR ENGINEERS

BOX 455, ESCONDIDO, CA 92025

Phone: (714) 747-3343

### 2 METER CRYSTALS IN STOCK

FOR THESE RADIOS ON  
STANDARD ARRL REPEATER  
FREQUENCIES:

- DRAKE — TR-22
- GENAVE
- ICOM/VHF ENGINEERING
- KEN/WILSON
- REGENCY HR-2A/HR-212
- HEATHKIT HW-202
- REGENCY HR-2B
- S.B.E.
- STANDARD 146/826
- STANDARD HORIZON

Send for free frequency  
list and order blank to:

### KENSCO COMMUNICATIONS INC.

DEPT. 10876

BOX 469, QUINCY, MA. 02169

PHONE: (617) 471-6427



**LOGIC PROBE KIT**—Use with CMOS, TTL, DTL, RTL, HTL, HINIL and most MOS IC's. Built in protection against polarity reversal and overvoltage. Draws only a few mA from circuit under test. Dual LED readout. Complete kit includes case and test leads. \$8.95

**VARIABLE REGULATED POWER SUPPLY KIT**—Continuously variable from 3 to over 15 Volts. Short circuit proof with electronic current limiting at 300 mA. Compact size and typical regulation of 0.1% make this a great bench or lab power supply. \$11.95

**FIXED REGULATED POWER SUPPLY KITS**—Short circuit proof with thermal current limiting. Compact size and typical regulation of 0.5%. Make these ideal for most electronic projects. Available for 5V @ 500mA, 6V @ 500mA, 9V @ 500mA, 12V @ 400mA, 15V @ 300mA. Specify voltage when ordering. \$8.95 ea.

These easy-to-assemble kits include all components, complete detailed instructions and plated fiberglass PC boards. Power supply kits do not include case or meters. Add \$1.25 per kit for postage and handling.

<b>TRANSISTORS (NPN)</b>	
2N918 TYPE RF Amp & Oscillator to 1 GHz	3/51.00
2N3563 TYPE RF Amp & Osc to 1 GHz (pl. 2N918)	6/51.00
2N3565 TYPE Gen. Purpose Gain (TO-92/106)	6/51.00
2N3866 TYPE RF Power Amp 1.5 W @ 450 MHz	\$0.75
2N3904 TYPE GP Amp & Sw to 100 mA hFE 100	6/51.00
Assort. NPN GP TYPES, e.g. 2N3694, 2N3903, etc. (15)	\$2.00
2N3638 TYPE (PNP) GP Amp & Sw to 300 mA	6/51.00
2N3906 TYPE (PNP) GP Amp & Sw to 30 MHz	6/51.00

<b>FET'S:</b>	
<b>N-CHANNEL (LOW-NOISE)</b>	
2N4091 TYPE RF Amp & Switch (TO-18/106)	3/51.00
2N4416 TYPE RF Amplifier to 450 MHz (TO-72)	2/51.00
2N5163 TYPE Gen. Purpose Amp & Sw (TO-106)	3/51.00
2N5486 TYPE RF Amp to 450 MHz (plastic 2N4416)	2/51.00
E100 TYPE Low-Cost Audio Amplifier	4/51.00
IT4868 TYPE Ultra-Low Noise Audio Amp	2/51.00
TI574 TYPE High-Speed Switch 40!	3/51.00
Assort. RF & GP FET'S, e.g. 2N5163, MPF102, etc. (8)	\$2.00
<b>P-CHANNEL:</b>	
2N4360 TYPE Gen. Purpose Amp & Sw (TO-106)	3/51.00
E175 TYPE High-Speed Switch 125!(TO-106)	3/51.00

### SUPER SPECIALS:

2N2222 NPN TRANSISTOR GP Amp & Switch	6/51.00
2N2467 PNP TRANSISTOR GP Amp & Switch	6/51.00
2N3553 RF Power Amp 5 W @ 150 MHz, 7 W @ 50 MHz	\$1.50
MPF102 N-CHANNEL FET RF Amp 200 MHz	3/51.00
556 DUAL 555 TIMER 1 usec to 1 hour (DIP)	\$0.90
723 VOLT. REGULATOR 3-30 V @ 1-200 mA (DIP/TO-5)	3/51.00
2740 FET Op Amp, Like NE536 and $\mu$ A740 (TO-5)	\$1.95
$\mu$ A7805 VOLTAGE REGULATOR 5 V @ 1 A (TO-220)	\$1.25
8038 WAVEFORM GENERATOR Wave w/ckts	\$4.50
1N4154 DIODE 30 V/10mA-1N914 except 30 V	25/51.00
BR1 BRIDGE RECTIFIER 50 V PIV, 500 mA (DIP)	4/51.00
MM5314 DIGITAL CLOCK CHIP With Specs/Schematics	\$4.95

<b>LINEAR IC'S:</b>	
308 Micro-Power Op Amp (TO-5/MINI-DIP)	\$1.00
309K Voltage Regulator 5 V @ 1 A (TO-3)	\$1.25
324 Quad 741 Op Amp, Compensated (DIP)	\$1.50
340T Volt. Reg. 1 Amp Specify 5, 6, 12, 15 or 24 V w/ckts	\$1.75
380 2-5 Watt Audio Amplifier 34 dB (DIP)	\$1.29
555 Timer 1 $\mu$ s to 1 hr. NE555, LM555, etc. (MINI-DIP)	2/51.00
709 Popular Op Amp (DIP/TO-5)	\$0.29
739 Dual Low-Noise Audio Preamp/Op Amp (DIP)	\$1.00
1458 Dual 741 Op Amp (MINI-DIP)	2/51.00
741 Freq. Comp. Op Amp (DIP/TO-5/MINI-DIP)	4/51.00


**DIODES:**  
ZENERS—Specify Voltage 3.3, 3.9, 4.3, 5.1, 6.8, 8.2, 9.1, 10, 12, 15, 16, 18, 20, 22, 24, 27, or 33V (+10%) 400mW 4/51.00  
1 Watt 3/51.00  
1N914 or 1N4148 TYPE General Purpose 100V/10mA 15/51.00  
1N3893 TYPE RECTIFIER Stud Mount 400 V/1/2 A 2/51.00  
05 VARACTOR 5-50 V Output @ 30-250 MHz, 7-70 pF \$5.00  
F7 VARACTOR 1-3 W Output @ 100-500 MHz, 5-30 pF \$1.00

\*MAIL NOW! FREE DATA SHEETS supplied with every item from this ad.  
FREE ON REQUEST—741 Op Amp with every order of \$5 or more—749 Dual Op Amp or two E100 FET'S with every order of \$10 or more, postmarked prior to 8/31/76. One free item per order.  
**ORDER TODAY!**—All items subject to prior sale and prices subject to change without notice. All items are new surplus parts—100% functionally tested.  
**WRITE FOR FREE CATALOG #7510** offering over 350 semiconductor carriers in stock. Send 13¢ stamp.  
**TERMS:** Send check or money order (U.S. funds) with order. We pay 1st Class postage to U.S., Canada and Mexico (except on kits) \$1.00 handling charge on orders under \$10. Residents add 6% sales tax. Foreign orders add postage. COD orders—add \$1.00 service charge.

## ADVA

ELECTRONICS  
BOX 4181 BZ, WOODSIDE, CA 94062  
Tel. (415) 851-0455

### 2mtr/220 MHz MOBILE ANTENNAS

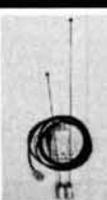

Install this Gutter-Mount Antenna System on your auto and merely change 1/4 wavelength elements (vinyl clad resilient steel) to bounce from 2 meters to 220 MHz.

**VERY POPULAR AT  
HAMFESTS!**

<b>GUTTER MOUNT® PLUS ELEMENT</b>	<b>ELEMENT ONLY</b>
FM-146 ..... \$15.95	FME-146 ..... \$4.95
FM-220 ..... \$15.95	FME-220 ..... \$4.95

\*Includes 10 feet of low loss RG-58 coax.  
Prices include postage in continental U.S.A.  
Penn. residents: Add 6% Sales Tax.

### HamLine Electronics

Box 52, Sweet Valley, Pennsylvania 18656

# FIRST

Make this comparison:

The GTX-1 gives the high quality performance that compares with Motorola, GE, RCA or any other hand-helds that sell for \$700 or more.

# THEN

Check these features:

**Small:** only 8"x2.6"x1.28" ...  
**Appearance:** slim silhouette all black metal ...  
**Serviceable:** easy access to separate receive and transmit circuit boards ...  
**PLUS:** 6 pole xtal filter for superlative receiver operation ...  
**and:** trimmers on receive and transmit xtals: standard 10.7 MHz 1st IF.

and specs:

**Rec. Sens.:** .2 $\mu$ v for 12 db SINAD ...  
**Adjacent channel rejection:**  $\pm$ 30 kHz 55 db ...  
**Spur. Resp.:** more than 65 db ...  
**Audio Output:** 500 mw ...  
**Power output:** Hi 3 w, Lo 1 w ...  
**Audio Quality:** Distortion free, crisp, clear receive and transmit.



# NOW

Look at the Price:

**GTX-1**  
 2 Meter 6 channel Hand-Held (without encoder)  
**\$249<sup>95</sup>**  
 (Bat. Not Incl.)

**GTX-1T**  
 with Built-In Tone Encoder  
**\$299<sup>95</sup>**  
 (Bat. Not Incl.)

GENAVE stocks most common 2-M Xtals for immediate delivery



Use This Handy Order Form

4141 Kingman Dr., Indianapolis, IN 46226  
 Phone-in orders accepted (317+546-1111)

NAME \_\_\_\_\_  
 ADDRESS \_\_\_\_\_ CITY \_\_\_\_\_  
 STATE & ZIP \_\_\_\_\_ AMATEUR CALL \_\_\_\_\_

CLIP OUT AND ORDER NOW

**GTX-200-T**

2-meter FM, 100 channel combinations, 30 watts with factory installed tone encoder (Incl. 146.94 MHz)



**\$249<sup>95</sup>**

**GTX-200**

2-meter FM, 100 channel combinations, 30 watts (Incl. 146.94 MHz)



**\$199<sup>95</sup>**

**GTX-10-S**

2-meter FM, 10 channels, 10 watts (Xtals not included)



**\$149<sup>95</sup>**

**GTX-2**

2-meter FM, 10 channels, 30 watts with pushbutton frequency selector (Incl. 146.94 MHz)



**\$189<sup>95</sup>**

**GTX-1**

2-meter FM, 6-channel, 3.5 watts Hand-Held

**\$249<sup>95</sup>**  
 (Bat. not incl.)



**GTX-1T**

Same as GTX-1, plus Factory Installed Tone Encoder

Operate Auto Patch  
**\$299<sup>95</sup>**  
 (Bat. not incl.)

Ringo Ranger ARX-2 6 db 2-M Base Antenna @ \$29.95 \$ \_\_\_\_\_

Lambda/4 2-M and 6-M Trunk Antenna @ \$29.95 \$ \_\_\_\_\_

TE-I Tone Encoder Pad for plug-in installation on most amateur transceivers @ \$59.95 \$ \_\_\_\_\_



TE-II Tone Encoder Pad for installation on most Hand-Helds @ \$49.95 \$ \_\_\_\_\_

PS-1 AC Power Supply for use with all makes of transceivers 14 VDC-6 amps @ \$69.95 \$ \_\_\_\_\_

and the following standard crystals @ \$4.50 each \$ \_\_\_\_\_  
 Non-standard crystals @ \$6.50 each: \$ \_\_\_\_\_

### ACCESSORIES FOR GTX-1 and GTX-1T

PSI-18 Optional Nicad battery pack \$29.95 \$ \_\_\_\_\_

PS-2 Charger for GTX-1(T) battery pack \$39.95 \$ \_\_\_\_\_

GLC-1 Leather carrying case \$12.95 \$ \_\_\_\_\_

TE-III Tone Encoder (for use with GTX-1) \$49.95 \$ \_\_\_\_\_

Add \$4 per Radio for Shipping, Handling, and Crystal Netting.

Payment by:

Certified Check/Money Order  Personal Check  
 C.O.D. Include 20% Down

Note: Orders accompanied by personal checks will require about two weeks to process.

20% Down Payment Enclosed. Charge Balance To:

BankAmericard # \_\_\_\_\_ Expires \_\_\_\_\_  
 Master Charge # \_\_\_\_\_ Expires \_\_\_\_\_  
 Interbank # \_\_\_\_\_ Expires \_\_\_\_\_

IN residents add 4% sales tax: \$ \_\_\_\_\_  
 CA residents add 6% sales tax: \$ \_\_\_\_\_  
 All orders shipped post-paid within continental U.S.  
 (allow 8 weeks delivery.)

CLIP OUT AND ORDER NOW

# Poly Pak's EXCLUSIVE Avg. Ship. \$1.98 Wt. 6 ozs.



YOUR CHOICE OF ANY KIT

100'S OF BARRELS PURCHASED! TEST 'EM YOURSELF 'N SAVE!

For the first time anywhere, Poly Pak merchandisers introduce a new way in buying the economical way. Raw stock from the "barrel". Remember the "good ole days"? They're back again. The same way merchandisers

throughout the United States buy from various factories... their overruns in barrels. Poly Pak has done the same. Therefore you are getting the same type of material as the RE-TESTERS DO!

Every kit carries a money back guarantee!

**BARREL KIT #1**  
SMT 40 DIP IC'S  
**75 for \$1.98**  
Master 11 and/or with 16 pin dips, may include gates, registers, flip flops, counters. Who knows? UNTESTED SATISFACTION!  
Cat.No. 8H2415 Untested.

**BARREL KIT #2**  
LINEAR OP. AMPS, DIPS  
**75 for \$1.98**  
Un- tested  
May include 709's, 741's, 703's, 600 series, 655 includes marked and unmarked. Cat.No. 8H2416

**BARREL KIT #3**  
1N4148/914  
SWITCHING DIODES  
**100 for \$1.98**  
You never saw this before. Imagine famous switching diodes at these prices!  
Cat.No. 8H2418 Untested.

**BARREL KIT #4**  
"4000" RECTIFIERS  
**100 for \$1.98**  
These shunt diode micro miniature rectifiers of the 1N4000 series. May include 45, 50, 100, 200, 400, 600, 800 and 1000 voltages. Cat.No. 8H2417

**BARREL KIT #5**  
SCRS, TRIACS, DIAC'S  
**40 for \$1.98**  
All the famous plastic power- tab types. Raw factory stock! All the 10 amp types. Cat.No. 8H2419 Untested.

**BARREL KIT #7**  
VOLUME CONTROL BONANZA!  
**40 for \$1.98**  
100% good  
Singles, duos, variety of values, styles, big ones - small ones. Cat.No. 8H2421

**BARREL KIT #8**  
SUBMINIATURE IF TRANSFORMERS  
**100 for \$1.98**  
Amazing, includes 455kcs, osc. antenna, who knows? From transistor radio manufacturers. Cat.No. 8H2422

**BARREL KIT #10**  
ROMS-REGISTERS  
**50 for \$1.98**  
28 to 40 pin devices, marked, internal factory numbers, etc. Cat.No. 8H2423

**BARREL KIT #12**  
POWER TAB TRANSISTORS  
**40 for \$1.98**  
PNP, plastic TO220 type. Associated 2N numbers. Cat.No. 8H2426 Untested.

**BARREL KIT #13**  
RESISTOR NETWORKS  
**60 for \$1.98**  
Untested.  
By Corning Glass, in 11-pin dip packs. Cat.No. 8H2427

**BARREL KIT #14**  
PRECISION RESISTORS  
**200 for \$1.98**  
Marked and unmarked 1/4, 1/2, 2 watts. No. 8H2428

**BARREL KIT #15**  
MOSFET TRANSISTORS  
**60 for \$1.98**  
All 4 lead TO-18 case includes 100% (100) Cat.No. 8H2429

**BARREL KIT #17**  
LINEAR & 7400 DIPS  
**100 for \$1.98**  
Marked and unmarked, internal numbers of raw factory stock. Cat.No. 8H2431

**BARREL KIT #19**  
DIPPED MYLARS  
**60 for \$1.98**  
Finest capacitors made, shunt type. Imagine factors dumping 'em in barrels. Cat.No. 8H2597 100% good.

**BARREL KIT #20**  
LONG LEAD DISCS  
**150 for \$1.98**  
Factory distributor stock. Prime, marked only. Long leads. Cat.No. 8H2598 100% good

**BARREL KIT #30**  
PREFORMED RESISTORS  
**250 for \$1.98**  
We got barrels of 1/4 and 1/2 watt for pc use. You'll get, even amount. 100% 1/4, 100 1/2 watters. Cat.No. 8H2608 100% good

**BARREL KIT #31**  
METALLIC RESISTORS  
**100 for \$1.98**  
Made mostly by Corning. The finest resistor made. Mostly 1/2 watters, 1% to 6% tol., & a barrel of values. Cat. No. 8H2609

**BARREL KIT #32**  
TRANSISTORS WITH A HOLE IN IT  
**50 for \$1.98**  
Cat.No. 8H2610 Untested.  
Can't name factory but we bought barrels of 25 watters with mfg. hole in middle. PNP's and NPN's.

**BARREL KIT #35**  
NEON LAMPS  
**40 for \$1.98**  
100% good.  
Famous NE-2's. All prime, but factory made millions and barrel'd 'em. Four advantages. Cat.No. 8H2613

**BARREL KIT #37**  
1 AMP "BULLET" RECTIFIERS  
**100 for \$1.98**  
Famous maker, popular item. Never grows old. But this is the way the RE-TESTERS buy 'em from factories. Cat.No. 8H2614

**BARREL KIT #40**  
PNP HIGH-POWER TRANSISTORS  
**20 for \$1.98**  
Popular germanium TO-3 case units, now available at "good ole barrel" prices. Cat.No. 8H2618 100% good.

**BARREL KIT #46**  
G.E. 3.3 WATT AMPLIFIERS  
**25 for \$1.98**  
Untested.  
Hobby type, factory fallouts, we purchased them in barrels. These are unmarked. Cat.No. 8H2624

**BARREL KIT #50**  
SIGNAL SILICON DIODES  
**200 for \$1.98**  
Includes many, many types of switching, signal silicon types, all axial leads, variety of colors. Cat.No. 8H2628 Untested.

**BARREL KIT #53**  
JUMBO RESISTOR PAK  
**100-pc. \$1.98**  
Cat.No. 8H2721  
Assortm metal films, precision, carbons, metal oxide powers, from 1/2 watt to 10 watts. Color coded & 100% good. Wurtz \$10.

**BARREL KIT #58**  
SLIDE SWITCHES  
**30 for \$1.98**  
All shapes, sizes, spat, opti, monometaries, etc. Tremendous shop pak for 100's of switching projects. Cat.No. 8H2726 100% good

**BARREL KIT #61**  
POLYSTYRENE CAPS  
**100 for \$1.98**  
Finest caps made. As a gimmie we bought 10 barrels from factory, mixed values, all good. Cat.No. 8H2729

**BARREL KIT #65**  
MIXED READOUTS  
**15 for \$1.98**  
Factory returns - such numbers as MAN-4's, MAN-5's, MAN-11 barrels & no time to separate. Cat.No. 8H2733 Untested.

**BARREL KIT #68**  
2 WATERS  
**100 for \$1.98**  
100% good.  
Nobody seems to want 'em. So many suppliers don't count, but throw 'em in the barrel. It's a lil' good mize. All marked. Cat.No. 8H2735

**BARREL KIT #71**  
CAPACITOR SPECIAL  
**100 pcs. \$1.98**  
Emptied stockrooms into barrels of mylars, poly's, micas, moideds, plastics, ceramics, discs, etc. Nifty 100% good. Cat.No. 8H2735

**BARREL KIT #73**  
TRANSISTOR ELECTROS  
**50 for \$1.98**  
It "bugs" us why the factories dump 'em in barrels. We don't wish to separate waste ass't voltages & values up to 300 mV. Cat.No. 8H2747

**BARREL KIT #77**  
"BROWN" BODY TRANSISTORS  
**40 for \$1.98**  
G.E. 10-10 series; has built voltage, Darlingtons, h-current, mp's. Factory line discontinued. Price cut. Cat.No. 8H2742 Untested.

**BARREL KIT #78**  
"RED" BODY TRANSISTORS  
**40 for \$1.98**  
D-42 series. You test - go into your own biz! High returns to us in a barrel. Cat.No. 8H2743 Untested

**BARREL KIT #81**  
SUBMINI RESISTORS  
**200 for \$1.98**  
100% good.  
PC, upright type, color coded, 1/2 watt. Ass't values. Variety of colors. Yield. Cat.No. 8H2748

**BARREL KIT #83**  
LM-340T VOLTAGE REGULATORS  
**15 for \$1.98**  
Untested.  
Factory rejected them for COMES to us in a barrel. Power tab. Cat.No. 8H2635

**BARREL KIT #86**  
HOBBY LEDS  
**40 for \$1.98**  
Untested.  
Wow! A Litronics dump of all kinds of mixed discrete LEDS, shapes, colors, good, poor, etc. 8H2859

**BARREL KIT #91**  
SILVER MICAS  
**100 for \$1.98**  
Cat.No. 8H3011  
For the first time silver micas so low in price! Axial, red case, variety of physical sizes & values. Big savings from distributor prices. Wt. 1 lb.

**BARREL KIT #93**  
HALF WATERS  
**200 for \$1.98**  
Untested.  
Resistor factory tried to fool us by mixing 100% color-coded resistors in barrel. But value in there. 4 oz. Cat. No. 8H3046

**BARREL KIT #99**  
PHOTO ELECTRIC CELLS  
**10 for \$1.98**  
Asst. GE types, CDS types. Mixed by factory. Big job for us to separate. 100% good. Cat.No. 8H3063

**BARREL KIT #101**  
RESISTOR SPECIAL  
**200 for \$1.98**  
Includes: 1/4, 1/2, 1, 2, 3, 5 watters, carbon, 100% good. 8H3054

**BARREL KIT #104**  
SLIDE VOLUME CONTROLS  
**10 for \$1.98**  
Cat.No. 8H3057  
Used in hi-fi, volume control maker unloads. Ass't. values, what a buy. Worth \$1 ea. We've got barrels of 100% material.

**BARREL KIT #109**  
TERMINAL STRIPS  
**150 for \$1.98**  
Wide asst. of terminal strip connectors, from 1 contact up. Strip manufacturer barrels dump in your gain. Wt. 1 lb. Cat.No. 8H3136

**BARREL KIT #110**  
SUPPRESSOR DIODES  
**50 for \$1.98**  
Cat.No. 8H3137  
Keeps ignition noises out axial. Untested, but the of your eqpt., car, industrial, etc. Double buy!

**BARREL KIT #112**  
MICRO MINI LEDS  
**40 for \$1.98**  
All the tiny leds, axial, up-right of Monsanto, Litronics, variety of colors. Yield. 60% or better. Cat.No. 8H3139

**BARREL KIT #114**  
CALCULATOR CHIPS  
**15 for \$1.98**  
NMM5716, 3N, etc. They have discontinued these chips. FIND A USE. Untested. Cat. No. 8H3258

**BARREL KIT #115**  
MOLEX SOCKETS  
**200 for \$1.98**  
100% good.  
Calculator maker dump! We got a zillion 'em. Used for IC sockets, etc. Cat.No. 8H3144

**BARREL KIT #123**  
CD-4002 C-MOS IC  
**15 for \$1.98**  
Mostly good. But we have 260,000. Can never sell 'em out. YOU'LL GAIN! Their number is CD-5602. Cat. No. 8H3217

**BARREL KIT #126**  
UPRIGHT ELECTROS  
**40 for \$1.98**  
Wide asst. of values from 1mf to 300mf in mixture of voltages. 100% marked in good. Why barrel'd? U-got-a-buy! Cat.No. 8H3226

**BARREL KIT #127**  
AXIAL ELECTROS  
**40 for \$1.98**  
Truthfully the factories (by mixing 'em in barrels) do all of us a favor. WUT A BUY! Ass't. capacitors and voltages. Cat. No. 8H3227

**BARREL KIT #128**  
MINI DIP IC'S  
**75 for \$1.98**  
Lark mtr dumped 100's of lbs into barrels. Includes 741's, LM-380-K, 703, 607, 665, 555—but who knows? factory to you. All mixed, you test. Wt. 1 lb. Cat. No. 8H3245

**BARREL KIT #131**  
TANTALUM ELECTROS  
**30 for \$1.98**  
Mixed, marked prime, top grade ass't. values, voltages. GE, Centralab, etc. Cat.No. 8H3255

**BARREL KIT #140**  
LAMPS  
**20 for \$1.98**  
Precision, mini lamp all metal, panel, with intg hardware. Lamp makers' overstock. 8H3287

**BARREL KIT #141**  
10 WATT ZENERS  
**15 for \$1.98**  
Mfr dumps to prepare for new styling, voltages all over the place. Good yield. Cat.No. 8H3298

**BARREL KIT #142**  
DARLINGTON TRANSISTORS  
**40 for \$1.98**  
TO-92, a Motorola dump, unknown numbers, but high yield to good darlington's. Re-testers didn't get 'em! You will. 8H3285

**BARREL KIT #144**  
RCA PHONO PLUGS  
**40 for \$1.98**  
1,000,000 RCA phono plugs for this one. You hi-fers know what they are & 100% material. Look at the price. 8H3293

©Poly Paks Inc. Wakefield, Mass., U.S.A. 1976

<p><b>BARREL KIT #145</b> MINI TRANSFORMER <b>15 for \$1.98</b> Miniature transformer back again. Ass't. outputs, inter-stage and audio. Wt. 1 1/2 lbs. Wt. 2 lbs. 8H3294</p>	<p><b>BARREL KIT #147</b> OVER-FLO FLUORESCENT NIXIES <b>5 for \$1.98</b> Used originally in table-top calculators. Brand new. Gas discharge type, color. Cat. No. 8H3288</p>
<p><b>BARREL KIT #154</b> CLOCK CHIPS <b>10 for \$1.98</b> We gathered an assortment of clock chip, alarm, calendar, beepers, who knows, all mixed. At these prices? Cat. No. 8H3308</p>	<p><b>BARREL KIT #152</b> VOLUME CONTROLS <b>15 for \$1.98</b> Control maker discontinued line; dumps controls with switches at ridiculous prices. Ass't values. Cat. No. 8H3306</p>
<p><b>BARREL KIT #155</b> MOLDED CAPACITORS <b>75 for \$1.98</b> Ass't. size voltages, red, green, yellow, blue plastic cases, axial leads. Cat. No. 8H3311</p>	<p><b>BARREL KIT #157</b> MOLEX CONNECTORS <b>75 for \$1.98</b> Nylon, white cable connectors, ass't. factory over-run. NO PICKLE! Mixed in barrels. Cat. No. 8H3324</p>
<p><b>BARREL KIT #158</b> MAGNIFIED MAN-3's <b>15 for \$1.98</b> Famous rejects Famous style MAN-3. 7-seg readout, with built-on magnifier. Factory discontinued line. 100% material. Cat. No. 8H3325</p>	<p><b>BARREL KIT #159</b> MODULAR SWITCHES <b>25 for \$1.98</b> Centralab "push-ON" switches. TV-makers excess. Dpdt, 6pdt, etc. Brand new. Cat. No. 8H3150</p>
<p><b>BARREL KIT #25</b> MILITARY CAN TRANSISTORS <b>100 for \$1.98</b> Untested. Includes: TO-5, TO-18, TO-18E, etc. assorted 2N numbers, unmarked etc. Cat.No. 8H2603</p>	<p><b>BARREL KIT #26</b> PLASTIC TRANSISTORS <b>100 for \$1.98</b> Untested. Type TO-92 (TO-18), all manufacturers. Variety of 2N #'s. Cat.No. 8H2604</p>
<p><b>BARREL KIT #39</b> 2N3055 HOBBY TRANSISTORS <b>15 for \$1.98</b> 100% good. From factory to you, these fallouts of the famous 2N3055. We have 10 barrels. Cat.No. 8H2617</p>	<p><b>BARREL KIT #59</b> POWER TRANSISTORS <b>40 for \$1.98</b> 15 watt Bendix B-5000 pellet transistors, n.p.m. all purchased from a pretreater, have millions of 100% good. Cat.No. 8H2727</p>
<p><b>BARREL KIT #75</b> 400M ZENERS <b>150 for \$1.98</b> Factory out of biz! Amazing offer: 6, 8, 10, 12 to 15V. You test. Hermetically sealed with double plug. Cat.No. 8H2740</p>	<p><b>BARREL KIT #76</b> 1-WATT ZENERS <b>100 for \$1.98</b> Untested. Factory same as 400-mw's. Never-to-see-again offer. 6, 8, 10, 12, 15V, under glass. Double plug. Cat.No. 8H2741</p>
<p><b>BARREL KIT #87</b> NATIONAL IC BONANZA <b>100 for \$1.98</b> Factory dumps into barrels. Type: 400, 7400 series. PNP, DTL, registers, clock &amp; calc. chips, linear, etc. Cat.No. 8H2860 Untested.</p>	<p><b>BARREL KIT #88</b> LITRONICS LED READOUTS <b>10 for \$1.98</b> 747's, 727's, singles, tri-ples, etc., etc. to 0.6. Bot from factory, all mixed, have fun! No. 8H2861</p>
<p><b>BARREL KIT #116</b> BUTTONS IN FEEDTHRU'S <b>100 for \$1.98</b> 100% good. Truthfully worth a small fortune. Wide asst. of but-tons from factory. HAMS TAKE NOTE! RE. DJF, etc. Wt. 1 lb. Cat.No. 8H3141</p>	<p><b>BARREL KIT #118</b> MINI SCRS <b>50 for \$1.98</b> UNBELIEVABLE! TO-92 plastic SCRS in barrels... rite from factory. Includes all voltages up thru 200 mv. 8H3138</p>
<p><b>BARREL KIT #133</b> C-MOS IC'S <b>60 for \$1.98</b> Deliberately thrown in barrels, so we can't test 'em! The famous CD4000 series. How good? Who knows? If you know it's only 3c ea. Cat. No. 8H3257</p>	<p><b>BARREL KIT #138</b> PANEL SWITCHES <b>30 for \$1.98</b> Did you hear of OAK? Another eqpt. maker barrelled all types of rotaries, electric, slides, etc. 8H3268</p>

Terms: Add postage. Rated: net 30  
Phone: Wakefield, Mass. (617) 245-3829  
Retail: 16-18 Del Carmine St., Wakefield,  
MINIMUM ORDER - \$6.00

C.O.D.'S MAY BE PHONED

**POLY PAKS** Send for FREE Summer-Fall CATALOG  
P.O. BOX 942H LYNNFIELD, MASS. 01940

# DRAKE EXPANDS SERVICE FACILITIES

Effective August 1, 1976 warranty and non-warranty customer service as well as parts for R. L. Drake Co. Amateur Radio Products will be available from the R. L. Drake Co. Western Region Sales & Service Center, 2020 Western St., Las Vegas, Nevada 89106.

William Gaible, WA8ADI, the Manager of this new Drake Company Service Center can be contacted by calling 702-382-9470.

This Western Service Center was established in order to better serve the needs of R. L. Drake Co. customers in the states of:

- Hawaii
- Alaska
- Washington
- Oregon
- California
- Montana
- Idaho
- Wyoming
- Nevada
- Utah
- Colorado
- Arizona
- New Mexico

as well as:

- Western Canada
- Mexico

The office will be staffed with experienced R. L. Drake factory Customer Service employees.

# flea market



**RATES** Non-commercial ads 10¢ per word; commercial ads 40¢ per word both payable in advance. No cash discounts or agency commissions allowed.

**HAMFESTS** Sponsored by non-profit organizations receive one free Flea Market ad (subject to our editing). Repeat insertions of hamfest ads pay the non-commercial rate.

**COPY** No special layout or arrangements available. Material should be typewritten or clearly printed and must include full name and address. We reserve the right to reject unsuitable copy. **Ham Radio** can not check each advertiser and thus cannot be held responsible for claims made. Liability for correctness of material limited to corrected ad in next available issue.

**DEADLINE** 15th of second preceding month.

**SEND MATERIAL TO:** Flea Market, Ham Radio, Greenville, N. H. 03048.

**BUY — SELL — TRADE.** Write for free mailer. Give name, address, call letters. Complete stock of major brands. New and reconditioned equipment. Call us for best deals. We buy Collins, Drake, Swan, etc., SSB & FM. Associated Radio, 8012 Conser, Overland Park, Ks. 66204. 913-381-5901.

**STOP** don't junk that television set. ASE manufactures the world's most complete line of television picture tubes. Over 1700 types. Most types, immediate delivery. Tubes for Old or New TV's, black & white and color. 2 year factory warranty. Lowest prices anywhere. Allied Sales & Engineering, Inc., Dept. 22, Pimento, IN 47866. Telephone 812-495-6555.

**COMPUTER POWER SUPPLY,** +24V/27V/3A, +12V/350ma, +5V/5A, -12V/500ma. Compact, extraordinary regulated and filtered. Pulled from new computer. With schematic. \$25.00. Many Cartrivision VTR parts. SASE. W6DOM, 6017 Majorca Ct., San Jose, Calif. 95120.

**WYOMING RANCH LAND.** Wild horses, antelope, deer, elk. 10 acres \$30 down, \$30 month. Owner - K6ICS, Mike Gauthier, 9550K Gallatin, Downey, CA. 90240.

**WANTED.** Only 1 copy Ham Radio, May, 1973. Tom Ierlan, WA2SPM, 725 Proctor Ave., Ogdensburg, N. Y. 13669.

**VERY in-ter-est-ing!** Next 4 big issues \$1. "The Ham Trader," Sycamore, IL 60178.

**CUSTOM EMBROIDERED EMBLEMS,** your design, low minimum. Emblems, Dept. 709, Littleton, New Hampshire 03561.

**RECONDITIONED TEST EQUIPMENT** for sale. Catalog \$.50. Walter, 2697 Nickel, San Pablo, Ca. 94806.

**WANTED:** Tektronix types P80 probe, 81 adapter, and 82 plug-in. State price. Mark Hudson, 1218 E. 36th St., Odessa, Tx. 79762.

**MOBILE IGNITION SHIELDING** provides more range with no noise. Available most engines. Many other suppression accessories. Literature, Estes Engineering, 930 Marine Dr., Port Angeles, WA 93862.

**NEW POWERFUL THREE OUTPUT REGULATED POWER SUPPLY,** plus 900 parts worth \$400.00 list. Solid state TV recorder electronic unit. Schematics, parts cross reference. Free brochure. \$17.95 plus \$3.50 S&H, USA. Master Charge, BankAmericard. Satisfaction guaranteed. Madison Electronics Company, Incorporated, Box 369, D77, Madison, Alabama 35758.

**AMATEUR CALL SIGN PINS \$1.00.** 1" x 3". 1 or 2 lines engraved. Blue, black, red, green. Guaranteed. Holly, Box 3926-S, Hollywood, Florida 33023.

**FREQUENCY COUNTER BOARDS,** Jan. 76 HR, double sided glass epoxy includes 500 MHz prescaler circuitry and LED board, instructions and parts source listing \$15.00 complete. Popular electronic keyer board \$2.00. CSJ Electronics, 5201 Cameron Court, Lincoln, NE 68512.

**GOVERNMENT SURPLUS** Communication Equipment, FREE catalog. Colonel Russell, 9410 Walhampton, Louisville, KY 40222.

**WANTED —** Housekeeper YL, (1KW Rig) Suburban-W2ISL, A. Porterfield P.E., 41 Winnebago Rd., Yonkers, N. Y. 10710.

**KLM PRODUCTS,** Larsen ants., Icom, police and fire scanners. Send for prices. Not given over phone. Narwid Electronics, 61 Bellot Road, Ringwood, N. J. 07456.

**HOMEBREWERS:** Stamp brings list of high quality components. CPO Surplus, Box 189, Braintree, Mass. 02184.

**SAVE!** Bomar FM, xtals \$4.00 ppd. Dentrone, Hustler, CushCraft, W. M. Nye, Ameco. Used gear. Complete catalog - write Ferris Radio, 308 E. Harry, Hazel Park, Mich. 48030.

**FERRITE BEADS:** Ferroxcube beads w/specification and application sheet — 10 @ \$1.00 postpaid. Includes latest catalog. CPO Surplus, Box 189, Braintree, Mass. 02184.

**COMPUTER HOBBYISTS!** Bargain hunt and sell via ON\_LINE. 18 issues/year - \$3.75. Free sample issue from: ON\_LINE, 24695 Santa Cruz Hwy., Los Gatos, CA 95030.

**COLLINS 75S1, 32S1, 516F-2, \$765.** General Radio Type 916-A radio frequency bridge, \$245. Heath SB-200, \$215. Rohn No. 25, never used, complete - 90 ft., my cost \$635 - now \$450. Copper jacket, low loss 50 ohm coax 280 feet \$95. Ham-M rotor complete \$100. 4 el. 10 meter beam HB (20' boom) \$40. TA-33Jr. tri-band beam \$70. Small prop-pitch rotor - items for complete system \$175. "Large" prop-pitch rotor \$75. QST, 29 years (328 issues) \$90. CQ, 28 years (305 issues) \$65. 73 Magazine, 14 yrs. (167 issues) \$30. U ship. Moving to W6. M. M. Kovar, W2ZN, 3 Puddingstone Ct., Morristown, N. J. 07960. (201) 386-2512 day - (201) 267-0657 eve.

**MANUFACTURERS, DISTRIBUTORS, DEALERS!** The Memphis Hamfest had 3,500 registrations last year — even more expected this year! Saturday and Sunday, October 2 & 3, at State Technical Institute, Interstate 40 at Macon Road. Security, motels, restaurants — a great location for a great event! Contact Harry Simpson W4SCF, Box 27015, Memphis, TN 38127. Telephone 901 358-5707.

**TECH MANUALS** for Govt. surplus gear — \$6.50 each: SP-600JX, URM-25D, OS-8A/U, PRC-8, 9, 10, Thousands more available. Send 50¢ (coin) for 22-page list. W3IHD, 7218 Roanne Drive, Washington, D. C. 20021.

**RUBBER STAMP,** name/call/QTH \$2.50 ppd. (CA residents add tax). LWM Press, Box 22161, San Diego, CA 92122.

**CANADIAN JUMBO SURPLUS** and Parts Catalogs. Bargains Galore. Send \$1. ETCO-HR, Box 741, Montreal "A" H3C 2V2.

**WANT** Wireless book; daughter, Dr. Mahlon Loomis, 1920's. W9LL.

**PORTA-PAK** the accessory that makes your mobile really portable. \$59.95 and \$39.95. Dealer inquiries invited. P. O. Box 67, Somers, Wisc. 53171.

**DESKFAX PAPER** \$10 per 1000 sheets, Tom White. 3325 W. Altadena, Phoenix, AZ 85029.

**DIRECT CONVERSION RECEIVER KITS** for AM or CW. Write WB9MBH, 3132 North Lowell Avenue, Chicago, Illinois 60641.

**WANTED:** HRO-50 in repairable condition. WA5INP, Art Smith, 5446 Grafton St., Jackson, Mississippi 39206.

**FREE** Electronics Surplus Catalog. Electronic Specialties, 1659 Wetmore, Tucson, AZ 85705.

**H-P 400D** \$45.00. H-P 650A \$75.00, good cond., manuals. FOB Ray Harland, 2602 Mary Ln., Escondido, Ca. 92025.

**MOTOROLA CONVERTA-COM CONSOLES.** One each, VHF & UHF. Complete with speakers and cables. Make offer. Mike, WA2ZOW, 65 Richard St., Clark, N. J. 07066. (201) 382-0879.

**SIDESWIPER** only \$13. Airmailed USA. Kungsimport, Box 257, Kungsbacka, Sweden.

**CIRCUIT BOARDS.** Artwork, negatives, etching. SASE for details. Karl Raup, WB4OXG, 630 Albertson Place, Orlando, Fla. 32806.

## TRANSFORMER RIOT

American made, 115V Primarys:  
6.3 V, 1 Amp, Shielded \$1.75 Ea. ppd.  
12V — 250 mls — for P.C. Board. Size:  
1 1/2" x 1 1/8" x 1 1/8", 3.5 OZ.  
\$1.40 ea. ppd.  
12 volt 1/2 amp. \$1.68 ppd.  
12V 1.2 Amp \$2.57 ppd.  
12V, 3 Amp \$4.15 ppd.




## NEW NEW NEW

Dual Secondarys: 18-0-18V @ 1.2 Amp and 7-0-7V @ 400 MA, 1 lb. 5 oz., Shielded, 2 3/8" x 2" x 2 1/4" (3 1/4" MTG) — \$3.85 ppd.  
22-0-22V — 1 Amp, 6.3V, Tap 1/4 Amp — 2" x 2 1/4" x 2 3/8" (MTG 2 3/8") Leads from top of shield, 1 lb. 4 oz. \$3.20 ppd.  
24-0-24 @ 1 amp with tap at 6.3 volt for pilot light. \$3.15 ea. ppd.

**TRANSISTOR OUTPUT TRANSFORMER** — One watt rating 200 ohm Center-tapped primary, 8 ohm secondary 85¢ Each ppd.

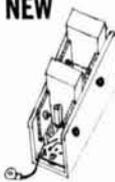**NEW** Transistor and Relay Assembly — consists of (2) MJE3055 and (2) MJE2955 transistors (10 amp, 90V, 60V complementary pairs) mounted in "U" channel heat sink 2 1/2" x 1 1/2" x 1 1/2", (2) XTAL CAN RELAYS, DPDT, 28V, 8000Ω, 5.8 ma DC, 1 amp contacts mounted on PC board with resistors. \$2.85 ea. ppd.



## NEW SIZES — VERTICAL MOUNT PC BOARD POTENTIOMETERS

American made (CRL) Cermet size: 25K, 100K ohms. 5/\$1.30 ppd. CTS Blue wheel. Values: 750, 1K, 1.5K, 50K, 300K ohms. 5/\$1.20 ppd.



**NEW** MINI Imported vertical pots (1/2", 3/8", 1/16") Values: 1000, 2.5K, 5K, 50K ohms. Slot adj. Price: 5 for \$1.20 ppd.

## NEW CAPACITORS

### BACK IN STOCK ONCE AGAIN

3000 MFD @ 30 Volt Capacitors. Size 1" Diameter x 3" Long. 90¢ Each or 3 For \$2.25 ppd.

3000 MFD @ 20V Capacitors. Same size as above. 80¢ ea. or 3 for \$2.00 ppd.

ALSO 3000 MFD @ 50V 95¢ ea. or 3/\$2.65 ppd

### ELECTROLYTIC CAPACITOR — PHILCO

Quad section 100x150 MFD @ 400V and at 350V D.C. and 20x50 MFD @ 250V — TWISTAB MTG. A very nice unit for Transceiver Power Supplies etc. Price is only \$1.10 ea. or 3/\$2.95 ppd.

DUAL Electrolytic 1000 & 500 MFD. 15V, long leads. 3/4" dia. x 2 1/4" long. 55¢ each 3/\$1.50 ppd.

Dual Electrolytic 1000 MFD @ 16V, 500 MFD @ 12V. 3/4" dia. x 2 1/4" long. 60¢ ea. or 3/\$1.55 ppd.

1 1/4 inch miniature alligator clips. Bright vinyl red or black. Nickel plated 9 for \$1.00

UNPOTTED TOROIDS — center tapped 88MHY Limited Qty's 44 MHY 5/\$2.95 5/\$3.95 ppd.

CRL DISC CAPACITORS .1 MFD, 10V 3/8" dia., long leads. 10 for \$1.00 ppd.

Red 6 foot #18-2 line cord with flanged safety plug — 55¢ ea. or 3/\$1.45 ppd. Gray 6 foot, 7A, plugs into auto liter socket — 95¢ ea. or 3/\$2.55

General Purpose Germanium Diodes. Similar to 1N34a etc. All Cathode banded Full leads. 16 for \$1.00 ppd.

Small, glass, silicon diodes. Fairchild FD-type. Full leads and guaranteed. Price: 16 for \$1.00 ppd.

SEND STAMP FOR BARGIN LIST PENNSYLVANIA RESIDENTS - ADD 6% ALL ITEMS PPD. USA

Canadian orders for less than \$5.00 add \$1.00 to cover additional mailing costs. UPS requires your street address.

# flea market

**NEW CANADIAN MAGAZINE.** "Electronics Work Shop". \$5.00 yearly, sample \$1.00. ETCOB, Box 741, Montreal, H3C 2V2.

**FREE CATALOG.** LEDs, strobe lights, UARTS, memories, RF transistors, microphones, IC's, relays, ultrasonic devices, precision trimmer capacitors, digital thermometers, unique components. Chaney's, Box 15431, Lakewood, Colo. 80215.

**FOR SALE:** Genave GTX-200T, factory tone pad, 4 channels, mint condx. \$240. Heathkit SB-102 A-1 shape, make offer, WA@NZQ, Curtis R. Olson, P. O. Box 215, Regent, N. Dak. 58650.

**WANTED:** Boehme, Creed, McElroy, G.N.T., Wheatstone equipment. ATKO Minikey, ATKO, ECCO, Navy 8M3 training set. Manuals booklets. Fisher, 235 Adams Street, Brooklyn, New York 11201.

**MODERN 60 MIN. CODE CASSETTES.** Novice 0-5 wpm, Progressive 5-13 wpm, General 13-15 wpm, Extra 20-22 wpm. \$3 each, 4/\$10. Royal, Box 2174, Sandusky, Ohio 44870.

**QRP TRANSMATCH** for HW7, Ten-Tec, and others. Send stamp for details to Peter Meacham Associates, 19 Loretta Road, Waltham, Mass. 02154.

**COMPLETE LINE KLM, CushCraft, Covercraft** dust covers, SCS amplifiers, Regency, Triex Towers. Call or write Radios Unlimited, 86 Balch Ave., Piscataway, N. J. 08854. 201-762-4307.

**NAMEBADGES** \$1.25, name and call sign \$1.75. Engraved plastic with pin or clutches. Black, white, red, blue, green, woodgrain. Include payment with order. Club emblem and hamfest badges. SASE for catalog. Donan's Engraving, P. O. Box 07155, Lakewood, Ohio 44107.

**SALE:** Model 28 ASR's - KSR's repairs - keyboards TD's - printers parts - all priced for hams. All in excellent condition. A.D.M. Communications, Inc., 1322 Industrial Avenue, Escondido, Ca. 92025. (714) 747-0374.

**MOTOROLA HT220, HT200, Pageboy,** and other popular 2M FM transceiver (Standard, Regency, etc.) service and modifications performed at reasonable rates. WA4FRV, (804) 272-8403.

**MOD-U-LINE CABINETS,** ST-6 style MCP3-17-12 gray \$27.97. 500 styles available. Many other electronic parts available. Stamp brings info. NuData, 104 N. Emerson St., Mt. Prospect, IL 60056.

**DEFLECTION YOKES** — For 1" Vidicon with transistor deflection circuits. New precision yokes, \$10.00 each while they last. Add 50¢ each for shipping. Apron Laboratories, P. O. Box 323, Bloomington, IN. 47401.

**TS520 NEVER USED.** With CW filter and external VFO. AC only. \$675. Heath SB300/401 combo with VFO switching, all filters, Heath desk microphone. Mint. \$400. Linear \$175. W6TC, 415-854-4649.

**BAZOOKA. DIPOLE** . . . Ready to use, with fiberglass center SO239, end insulator 80M, \$29.50; 40M, \$26.50; 20-15-10M, \$23.50. Fiberglass central insulator with SO239, 1000 pound test, \$5.95. Trap 2 KW 80/40, 40/20, \$18.50, ppd. Jac-Tenna, 13850 Victorin, Tracy, P. Que., Canada.

**TRAVEL-PAK QSL KIT** — Send call and 25¢; receive your call sample kit in return. Samco, Box 203, Wynantskill, N. Y. 12198.


**MANUALS** for most ham gear, 1939/70. List \$1.00. Send SASE (or 25¢) for one specific model quote. Hobby Industry, W@JJK, Box H864, Council Bluffs, Iowa 51501.

**CRYSTALS** for Collins S Line and KWM 2. Full frequency coverage 3.4 to 30 MHz. Complete kit 126 crystals \$2.00 per crystal plus postage. Single units or any combination. W8MEN, 184 Crandall Drive, Worthington, Ohio 43085. Phone 614 885-6725.

**IC APPLICATIONS MANUAL** — Analog/Digital \$3.95. Digital IC manual - latest edition-3000 latest types/pinout diagrams/cross references \$6.95. Electronetics-HRM, P. O. Box 127, Hopedale, MA. 01747.

**RADIO MUSEUM** now open. Free admission. 15,000 pieces of equipment from 1850 telegraph instruments to amateur and commercial transmitters of the 1920's. Amateur station W2AN. Write for information. Antique Wireless Assn., Main St., Holcomb, N. Y. 14469.

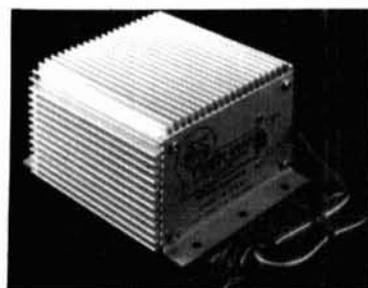**TELL YOUR FRIENDS** about the BIG NEW Ham Radio Magazine!



## THE TIGER

### 15% Savings on Gas

A Capacitive Discharge Ignition system absolutely guaranteed NOT to interfere with your radios & equally guaranteed to improve your auto's operation and gas mileage.

No rewiring necessary. Engine cannot be damaged by improper installation. Either of three models fits any vehicle or stationary engine with 12 volt negative ground, alternator or generator system. Uses standard coil & distributor now on your engine. Dual switch permits motor work or tune-up with any standard test equipment.

Write for free booklet that not only is the BEST description of CDIs, but also explains the need for such a system. Current prices assured till July 1, '76.

## D-D ENTERPRISES

P. O. Box 7776

San Francisco, CA 94119



## test for resonant resistance with an omega-t antenna noise bridge



The Omega-t Noise Bridge is an inexpensive and flexible testing device that can effectively measure antenna resonant frequency and impedance. This unique piece of test equipment does the work of more expensive devices by using an existing receiver for a bridge detector. There is no longer a need for power loss because of impedance mismatch. Get more details or order now!

Model TE7-01 for 1-100 MHz Range \$29.95  
Model TE7-02 for 1-300 MHz Range \$39.95

**ELECTROSPACE SYSTEMS, INC.**

320 TERRACE VILLAGE  
RICHARDSON, TEXAS 75080  
TELEPHONE (214) 231-9303

Sold at Amateur Radio Dealers or Direct from Electrospace Systems, Inc.

**m. weinschenker**  
electronic specialties-BOX 353, IRWIN, PA 15642

# Get more operating pleasure with your Atlas Transceiver!



## Introducing the new **ATLAS Auxiliary VFO**

The Model 206 provides:

- Digital Dial L.E.D. Readout
- Separate control of transmit and receive frequency
- Expanded frequency coverage
- Frequency Counter Capability
- Digital Hold

The Model 206 Auxiliary VFO is designed for simple plug-in installation with all Atlas Transceivers providing increased versatility, greater frequency coverage including full coverage of the 10 meter band, and more flexible operating capability.

#### DIGITAL DIAL READOUT

All L.E.D. Matrix 6 digit display reads within 100Hz (just 1/10 kHz) of your actual operating frequency. Reads on both Receive and Transmit.

A **DIGITAL HOLD** feature permits retention of a frequency reading while tuning to other frequencies.

#### SEPARATE TRANSMIT-RECEIVE FREQUENCY CONTROL

The 206 provides for transmitting on one frequency while receiving on another frequency. Transceive operation on the same frequency may be with either the 206 or 210x/215x.

#### EXPANDED FREQUENCY COVERAGE

Complete coverage from 1.8 to 3 MHz (with Model 215x only), also 3 to 5, 6 to 8, 8 to 10, 14 to 16, 20 to 22, and with the 210x from 28 to 30 MHz. This permits MARS operation as well as reception over large segments of the HF spectrum.

#### FREQUENCY COUNTER CAPABILITY

In addition to being a VFO Digital Dial, the 206 will also function as a sensitive frequency counter from 100 Hz to 40 MHz for general use around the ham shack or lab.

The Model 206 is housed in an attractive cabinet matching the Atlas AC console.

With the addition of the 206 to your Atlas station, you have the ultimate in a high performance, maximum versatility, compact, amateur radio station. **\$299.**

For complete details see your Atlas dealer, or drop us a card and we'll mail you a brochure with dealer list.



417 Via Del Monte Oceanside, CA 92054 Phone (714) 433-1983

# YOUR NEW H-P CALCULATOR MAY COST YOU NOTHING!



## WE NEED USED HAM EQUIPMENT!

The Hewlett-Packard calculator you've always wanted may cost you little or nothing! As the Southwest's leading Ham Radio Dealer we have a continuous need for good used amateur radio equipment. As an authorized Hewlett-Packard dealer we have an excellent supply of these superb scientific and financial calculators, and we're offering you a legitimate trading opportunity.

HEWLETT  PACKARD

HP21	\$100--less trade-in
HP22	\$165--less trade-in
HP25	\$165--less trade-in
HP55	\$335--less trade-in
HP65	\$795--less trade-in

For an estimate on the value of your used equipment call our Ham Dept. Mgr., Walt Van Arsdale (K5SXO).

**CALL TOLL FREE**  
800-527-4642  
(In Texas call...214-348-1560)

Upon receipt and check-out of your trade we'll confirm our allowance to you. Your price on any of the above units can be substantially reduced or eliminated with a good trade-in. This is a limited offer--don't delay--trade up to Hewlett-Packard, the finest hand held calculator you can own!



**TECO**  
Electronics  
Superstore

1717 S. Jupiter Rd.  
P.O. BOX 1050  
GARLAND, TEXAS 75040

# flea market

**KEYER KITS**, automatic with weight control. Use ordinary paddle or homebrew "touch" paddle. Draws less than 2 ma at 9 volts. Ideal for portable operation. Includes all P.C.B. components and full instructions. Send S.A.S.E. for details or send \$17 to NS. Circuits, Jacob Sollenberger, Route 7, Chambersburg, Pa. 17201.

**PC's**, Send large S.A.S.E. for list. Semtronics, Rt. #3, Box 1, Bellaire, Ohio 43906.

**MAG TAPE**, 2,400' of 1/2 inch tape for UTRS \$7.00/reel. Interested in video, ATV or SSTV? Get on mailing list for free copy of new magazine. W6LVY, Dennis Trimble, 5835 Herma St., San Jose, Ca. 95123.

**FIGHT TVI** with the RSO Low Pass Filter. For brochure write: Taylor Communications Manufacturing Company, Box 126, Agincourt, Ontario, Canada. MIS 3B4.

**FREE flyer** of unusual surplus equipment and components: military, RF, semiconductors, coils, capacitors, etc. Free gift with first order. Gold Electronics Company, Dept. H, Box 1814, Rochester, NY 14603.

**ENGRAVED RADIO LICENSE**. Exact reproduction in solid brass. Permanent identification. Send good Xerox copy, with \$5.00, to Metal Art Graphics, 1136 Potomac Ave., Hagerstown, Md. 21740.

**TELETYPE EQUIPMENT FOR SALE** for beginners and experienced operators. RTTY machines, parts, supplies. Special beginners package consists of Model 15 page printer and 1H5-TG demodulator, \$125.00. Atlantic Surplus Sales, 3730 Nautilus Ave., Brooklyn, N. Y. 11224. Tel: (212) 372-0349.

**TELETYPEWRITER PARTS**, gears, manuals, supplies, tape, toroids. SASE list. Typetronics, Box 8873, Ft. Lauderdale, Fl. 33310. Buy parts, late machines.

**QSL'S — BROWNIE W3CJ1** — 3035B Lehigh. Allentown, Pa. 18103. Samples with cut catalog 50¢.

**NEED HELP** holding your PC board while you solder the components? My fixture will sit on your kitchen table and adjusts to fit PC boards up to 6 3/4" wide (length unlimited). Order now. Only \$7.95 ppd in USA (Mo. residents add 25¢). W. N. Wellman Co., Box 722A, 451 Saline Rd., Fenton, Mo. 63026.

**EXCLUSIVELY HAM TELETYPE** 21st year, RTTY Journal, articles, news, DX, VHF, classified ads. Sample 35¢. \$3.50 per year. Box 837, Royal Oak, Michigan 48068.

**OSCAR 7, SSB-CW TRANSMIT CONVERTERS**. For 28 or 50 MHz input at 20 mw. 432 MHz output at 1 watt. Solid state, for 12 volt supply. 35 watt solid state amplifier available for this converter. Units designed and built by W0ENC. Write for information. UHF-VHF Communications, 53 St. Andrew, Rapid City, S. D. 57701.

**YOUR AD** belongs here too. Why not send it in today.


## Coming Events

**WALTHAM, MASS.** 1st Annual WRIABV Repeater Flea Market sponsored by advisory committee. August 15, 1976 10 AM to 6 PM. Municipal parking lot, corner of Moody & Pine Streets, Waltham. Refreshments available. Talk-in on 146/64 and 449.05. Sellers \$4, Buyers \$1, to benefit the WRIABV Repeater. Contact W1KSZ for further information.

**MEMPHIS IS BEAUTIFUL IN OCTOBER!** The Memphis Hamfest, bigger and better than the 3,500 who attended last year, will be held at State Technical Institute, Interstate 40 at Macon Road, on Saturday and Sunday, October 2 and 3. Demonstrations, displays, MARS meetings, flea market, ladies' flea market, too! Hospitality room, informal dinners, XYL entertainment, many outstanding prizes. Dealers and distributors welcome, too! Contact Harry Simpson, W4SCF, Box 27015, Memphis, TN 38127, phone 901 358-5707.

**HAMBURG INTERNATIONAL HAMFEST**, Sept. 18, 1976 at the Erie County Fairgrounds, Hamburg, N. Y., near Buffalo and Niagara Falls. Registration \$3/\$2.50 (advance). Flea market space \$1.00/\$5.00. Fri. evening hospitality get-together with pre-registration drawing of a valuable prize, technical and organizational meetings, equipment displays, women's program, R/V and picnic facilities, fun, prizes. Talk in freqs: 146.52, 7.255 (ECARS), and 3.925 MHz. Info: Bert Jones, W2CUU, 143 Orchard Drive, Kenmore, N. Y. 14223, Phone: (716) 873-3984.

— CLEAN SIGNAL —  
— ALL CHANNELS —

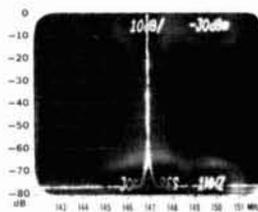

Actual Spectrum Analyzer Photograph of an RP Synthesized Radio

ONLY RP GIVES YOU BOTH  
PLUS

- SUPER ACCURACY (.0005%)
- FULL 2M FM COVERAGE

144-148 MHz  
WORKS WITH MOST FINE AMATEUR  
OR COMMERCIAL GRADE RADIOS

## MFA-22 SYNTHESIZER

PRICED \$325  
PLUS \$3 Shpg.

**RP Electronics**

SEND FOR FULL DETAILS



BOX 1201H  
CHAMPAIGN, ILL.  
61820

# ALUMA TOWERS

LOW PRICED

MADE IN ALUMINUM

★ TELESCOPING  
(CRANK UP)

★ GUYED

QUALITY MADE

*Excellent for*

**HAM  
COMMUNICATIONS**

10 MODELS MFG.

Towers to 100 feet. Specials designed & made. See dealer or send for free catalog.

ALUMA TOWER DIVISION

**FRED FRANKE, INC.**

BOX 2806HR  
VERO BEACH, FLA. 32460  
PHONE (305) 567-3415

### 7400N TTL


SN7400N	16	SN7425N	27	SN7415N	70
SN7401N	18	SN7454N	20	SN74151N	100
SN7402N	21	SN7459A	25	SN74153N	89
SN7403N	16	SN7460N	22	SN74154N	125
SN7404N	18	SN7470N	45	SN74156N	99
SN7405N	24	SN7471N	69	SN74157N	99
SN7406N	20	SN7472N	39	SN74157N	99
SN7407N	29	SN7473N	37	SN74160N	125
SN7408N	25	SN7474N	32	SN74161N	99
SN7409N	25	SN7475N	50	SN74162N	99
SN7410N	18	SN7476N	32	SN74164N	110
SN7411N	30	SN7479N	5.00	SN74165N	1.10
SN7412N	33	SN7480N	50	SN74166N	1.25
SN7413N	45	SN7482N	98	SN74167N	5.00
SN7414N	70	SN7483N	70	SN74170N	2.10
SN7416A	35	SN7485A	89	SN74172N	18.00
SN7417N	15	SN7486N	38	SN74173N	1.50
SN7420N	21	SN7488N	3.50	SN74174N	1.25
SN7421N	33	SN7489N	2.25	SN74175N	99
SN7422N	49	SN7490N	45	SN74176N	90
SN7423N	37	SN7491N	75	SN74177N	90
SN7424N	29	SN7492N	49	SN74180N	99
SN7426N	29	SN7493N	49	SN74181N	2.49
SN7427N	37	SN7494N	79	SN74182N	99
SN7429N	37	SN7495N	79	SN74184N	1.95
SN7430N	26	SN7496N	89	SN74185N	2.20
SN7432N	31	SN7497N	4.00	SN74186N	5.00
SN7433N	27	SN74100N	1.00	SN74187N	1.50
SN7438N	27	SN74107N	39	SN74190N	1.19
SN7439N	25	SN74111N	39	SN74191N	1.25
SN7440N	15	SN74122N	39	SN74192N	89
SN7441N	89	SN74123N	70	SN74193N	89
SN7442N	59	SN74124N	50	SN74194N	60
SN7443N	75	SN74126N	60	SN74195N	7.5
SN7444N	75	SN74128N	1.09	SN74196N	1.25
SN7445N	75	SN74136N	95	SN74197N	7.5
SN7446A	81	SN74148N	1.15	SN74198N	1.75
SN7447N	69	SN74142N	1.00	SN74199N	1.50
SN7448N	79	SN74143N	4.50	SN74200N	5.59
SN7450N	69	SN74144N	4.50	SN74209N	9.90
SN74C	N	SN74145N	1.15	SN74215N	1.79
		SN74146N	2.25	SN74284N	6.00
		SN74147N	2.00		

MANY OTHERS AVAILABLE ON REQUEST  
20% Discount for 100 Combined 2400's
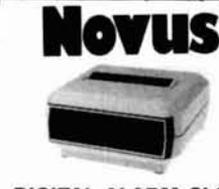
### CONSUMER ELECTRONICS



**EXELAR**  
DIGITAL WATCH  
This watch is manufactured by National Semiconductor. It provides 5 functions. Hours, minutes, seconds, date, A.M. indicator dot. Accuracy is assured to 5 seconds per month by precision quartz crystal. If something should go wrong with the watch, repair is assured within 48 hours after it is received. Complete with steel black leather band.



**NOVUS**  
DIGITAL ALARM CLOCK  
This 4 digit Novus Alarm Clock is a very reliable and smartly styled unit. It provides such features as an alarm settable to any minute of the day, a 7 feature snooze alarm, a power failure indicator, and even an A.M./P.M. indicator.

ES4-Y5  
3 MIRON GOLD  
PLATE BEZEL  
\$29.95  
NOT A KIT

NOT A KIT \$19.95

### XCITON LITRONIX OPTO ELECTRONICS

XC209R	5/51	XC526R	5/51	XC111R	5/51
XC209G	4/51	XC526G	4/51	XC111G	4/51
XC209Y	4/51	XC526Y	4/51	XC111Y	4/51
XC209B	4/51	XC526B	4/51	XC111B	4/51

125" dia.	185" dia.	190" dia.	200" dia.	200" dia.	085" dia.
XC229R	5/51	XC556R	5/51	MV50	085 dia. Micro red led
XC229G	4/51	XC556G	4/51		
XC229Y	4/51	XC556Y	4/51		
XC229B	4/51	XC556B	4/51		

TYPE	POLARITY	HT	\$3.25	TYPE	POLARITY	HT	\$3.25
MAN 1	COMMON ANODE	MAN 2	5 x 7 DOT MATRIX	MAN 3	COMMON CATHODE	MAN 4	COMMON ANODE
MAN 4	COMMON CATHODE	MAN 5	COMMON ANODE	MAN 6	COMMON ANODE	MAN 7	COMMON ANODE
MAN 7	COMMON ANODE	MAN 8	COMMON ANODE	MAN 9	COMMON ANODE	MAN 10	COMMON ANODE
MAN 10	COMMON ANODE	MAN 11	COMMON ANODE	MAN 12	COMMON ANODE	MAN 13	COMMON ANODE
MAN 13	COMMON ANODE	MAN 14	COMMON ANODE	MAN 15	COMMON ANODE	MAN 16	COMMON ANODE
MAN 16	COMMON ANODE	MAN 17	COMMON ANODE	MAN 18	COMMON ANODE	MAN 19	COMMON ANODE
MAN 19	COMMON ANODE	MAN 20	COMMON ANODE	MAN 21	COMMON ANODE	MAN 22	COMMON ANODE
MAN 22	COMMON ANODE	MAN 23	COMMON ANODE	MAN 24	COMMON ANODE	MAN 25	COMMON ANODE
MAN 25	COMMON ANODE	MAN 26	COMMON ANODE	MAN 27	COMMON ANODE	MAN 28	COMMON ANODE
MAN 28	COMMON ANODE	MAN 29	COMMON ANODE	MAN 30	COMMON ANODE	MAN 31	COMMON ANODE
MAN 31	COMMON ANODE	MAN 32	COMMON ANODE	MAN 33	COMMON ANODE	MAN 34	COMMON ANODE
MAN 34	COMMON ANODE	MAN 35	COMMON ANODE	MAN 36	COMMON ANODE	MAN 37	COMMON ANODE
MAN 37	COMMON ANODE	MAN 38	COMMON ANODE	MAN 39	COMMON ANODE	MAN 40	COMMON ANODE
MAN 40	COMMON ANODE	MAN 41	COMMON ANODE	MAN 42	COMMON ANODE	MAN 43	COMMON ANODE
MAN 43	COMMON ANODE	MAN 44	COMMON ANODE	MAN 45	COMMON ANODE	MAN 46	COMMON ANODE
MAN 46	COMMON ANODE	MAN 47	COMMON ANODE	MAN 48	COMMON ANODE	MAN 49	COMMON ANODE
MAN 49	COMMON ANODE	MAN 50	COMMON ANODE	MAN 51	COMMON ANODE	MAN 52	COMMON ANODE
MAN 52	COMMON ANODE	MAN 53	COMMON ANODE	MAN 54	COMMON ANODE	MAN 55	COMMON ANODE
MAN 55	COMMON ANODE	MAN 56	COMMON ANODE	MAN 57	COMMON ANODE	MAN 58	COMMON ANODE
MAN 58	COMMON ANODE	MAN 59	COMMON ANODE	MAN 60	COMMON ANODE	MAN 61	COMMON ANODE
MAN 61	COMMON ANODE	MAN 62	COMMON ANODE	MAN 63	COMMON ANODE	MAN 64	COMMON ANODE
MAN 64	COMMON ANODE	MAN 65	COMMON ANODE	MAN 66	COMMON ANODE	MAN 67	COMMON ANODE
MAN 67	COMMON ANODE	MAN 68	COMMON ANODE	MAN 69	COMMON ANODE	MAN 70	COMMON ANODE
MAN 70	COMMON ANODE	MAN 71	COMMON ANODE	MAN 72	COMMON ANODE	MAN 73	COMMON ANODE
MAN 73	COMMON ANODE	MAN 74	COMMON ANODE	MAN 75	COMMON ANODE	MAN 76	COMMON ANODE
MAN 76	COMMON ANODE	MAN 77	COMMON ANODE	MAN 78	COMMON ANODE	MAN 79	COMMON ANODE
MAN 79	COMMON ANODE	MAN 80	COMMON ANODE	MAN 81	COMMON ANODE	MAN 82	COMMON ANODE
MAN 82	COMMON ANODE	MAN 83	COMMON ANODE	MAN 84	COMMON ANODE	MAN 85	COMMON ANODE
MAN 85	COMMON ANODE	MAN 86	COMMON ANODE	MAN 87	COMMON ANODE	MAN 88	COMMON ANODE
MAN 88	COMMON ANODE	MAN 89	COMMON ANODE	MAN 90	COMMON ANODE	MAN 91	COMMON ANODE
MAN 91	COMMON ANODE	MAN 92	COMMON ANODE	MAN 93	COMMON ANODE	MAN 94	COMMON ANODE
MAN 94	COMMON ANODE	MAN 95	COMMON ANODE	MAN 96	COMMON ANODE	MAN 97	COMMON ANODE
MAN 97	COMMON ANODE	MAN 98	COMMON ANODE	MAN 99	COMMON ANODE	MAN 100	COMMON ANODE

TYPE	POLARITY	HT	\$3.25	TYPE	POLARITY	HT	\$3.25
MAN 1	COMMON ANODE	MAN 2	5 x 7 DOT MATRIX	MAN 3	COMMON CATHODE	MAN 4	COMMON ANODE
MAN 4	COMMON CATHODE	MAN 5	COMMON ANODE	MAN 6	COMMON ANODE	MAN 7	COMMON ANODE
MAN 7	COMMON ANODE	MAN 8	COMMON ANODE	MAN 9	COMMON ANODE	MAN 10	COMMON ANODE
MAN 10	COMMON ANODE	MAN 11	COMMON ANODE	MAN 12	COMMON ANODE	MAN 13	COMMON ANODE
MAN 13	COMMON ANODE	MAN 14	COMMON ANODE	MAN 15	COMMON ANODE	MAN 16	COMMON ANODE
MAN 16	COMMON ANODE	MAN 17	COMMON ANODE	MAN 18	COMMON ANODE	MAN 19	COMMON ANODE
MAN 19	COMMON ANODE	MAN 20	COMMON ANODE	MAN 21	COMMON ANODE	MAN 22	COMMON ANODE
MAN 22	COMMON ANODE	MAN 23	COMMON ANODE	MAN 24	COMMON ANODE	MAN 25	COMMON ANODE
MAN 25	COMMON ANODE	MAN 26	COMMON ANODE	MAN 27	COMMON ANODE	MAN 28	COMMON ANODE
MAN 28	COMMON ANODE	MAN 29	COMMON ANODE	MAN 30	COMMON ANODE	MAN 31	COMMON ANODE
MAN 31	COMMON ANODE	MAN 32	COMMON ANODE	MAN 33	COMMON ANODE	MAN 34	COMMON ANODE
MAN 34	COMMON ANODE	MAN 35	COMMON ANODE	MAN 36	COMMON ANODE	MAN 37	COMMON ANODE
MAN 37	COMMON ANODE	MAN 38	COMMON ANODE	MAN 39	COMMON ANODE	MAN 40	COMMON ANODE
MAN 40	COMMON ANODE	MAN 41	COMMON ANODE	MAN 42	COMMON ANODE	MAN 43	COMMON ANODE
MAN 43	COMMON ANODE	MAN 44	COMMON ANODE	MAN 45	COMMON ANODE	MAN 46	COMMON ANODE
MAN 46	COMMON ANODE	MAN 47	COMMON ANODE	MAN 48	COMMON ANODE	MAN 49	COMMON ANODE
MAN 49	COMMON ANODE	MAN 50	COMMON ANODE	MAN 51	COMMON ANODE	MAN 52	COMMON ANODE
MAN 52	COMMON ANODE	MAN 53	COMMON ANODE	MAN 54	COMMON ANODE	MAN 55	COMMON ANODE
MAN 55	COMMON ANODE	MAN 56	COMMON ANODE	MAN 57	COMMON ANODE	MAN 58	COMMON ANODE
MAN 58	COMMON ANODE	MAN 59	COMMON ANODE	MAN 60	COMMON ANODE	MAN 61	COMMON ANODE
MAN 61	COMMON ANODE	MAN 62	COMMON ANODE	MAN 63	COMMON ANODE	MAN 64	COMMON ANODE
MAN 64	COMMON ANODE	MAN 65	COMMON ANODE	MAN 66	COMMON ANODE	MAN 67	COMMON ANODE
MAN 67	COMMON ANODE	MAN 68	COMMON ANODE	MAN 69	COMMON ANODE	MAN 70	COMMON ANODE
MAN 70	COMMON ANODE	MAN 71	COMMON ANODE	MAN 72	COMMON ANODE	MAN 73	COMMON ANODE
MAN 73	COMMON ANODE	MAN 74	COMMON ANODE	MAN 75	COMMON ANODE	MAN 76	COMMON ANODE
MAN 76	COMMON ANODE	MAN 77	COMMON ANODE	MAN 78	COMMON ANODE	MAN 79	COMMON ANODE
MAN 79	COMMON ANODE	MAN 80	COMMON ANODE	MAN 81	COMMON ANODE	MAN 82	COMMON ANODE
MAN 82	COMMON ANODE	MAN 83	COMMON ANODE	MAN 84	COMMON ANODE	MAN 85	COMMON ANODE
MAN 85	COMMON ANODE	MAN 86	COMMON ANODE	MAN 87	COMMON ANODE	MAN 88	COMMON ANODE
MAN 88	COMMON ANODE	MAN 89	COMMON ANODE	MAN 90	COMMON ANODE	MAN 91	COMMON ANODE
MAN 91	COMMON ANODE	MAN 92	COMMON ANODE	MAN 93	COMMON ANODE	MAN 94	COMMON ANODE
MAN 94	COMMON ANODE	MAN 95	COMMON ANODE	MAN 96	COMMON ANODE	MAN 97	COMMON ANODE
MAN 97	COMMON ANODE	MAN 98	COMMON ANODE	MAN 99	COMMON ANODE	MAN 100	COMMON ANODE

### 50 PCS. RESISTOR ASSORTMENT \$1.25 PER ASST.

ASST.	1 ea.	10 OHM	12 OHM	15 OHM	18 OHM	22 OHM	1/4 WATT 5% - 50 PCS.
ASST. 1	5 ea.	27 OHM	33 OHM	39 OHM	47 OHM	56 OHM	1/4 WATT 5% - 50 PCS.
ASST. 2	5 ea.	68 OHM	82 OHM	100 OHM	120 OHM	150 OHM	1/4 WATT 5% - 50 PCS.
ASST. 3	5 ea.	180 OHM	220 OHM	270 OHM	330 OHM	390 OHM	1/4 WATT 5% - 50 PCS.
ASST. 4	5 ea.	470 OHM	560 OHM	680 OHM	820 OHM	1K	1/4 WATT 5% - 50 PCS.
ASST. 5	5 ea.	1.2K	1.5K	1.8K	2.2K	2.7K	1/4 WATT 5% - 50 PCS.
ASST. 6	5 ea.	3.3K	3.9K	4.7K	5.6K	6.8K	1/4 WATT 5% - 50 PCS.
ASST. 7	5 ea.	8.2K	10K	12K	15K	18K	1/4 WATT 5% - 50 PCS.
ASST. 8	5 ea.	22K	27K	33K	39K	47K	1/4 WATT 5% - 50 PCS.
ASST. 9	5 ea.	56K	68K	82K	100K	120K	1/4 WATT 5% - 50 PCS.
ASST. 10	5 ea.	150K	180K	220K	270K	330K	1/4 WATT 5% - 50 PCS.
ASST. 11	5 ea.	390K	470K	560K	680K	820K	1/4 WATT 5% - 50 PCS.
ASST. 12	5 ea.	1M	1.2M	1.5M	1.8M	2.2M	1/4 WATT 5% - 50 PCS.
ASST. 13	5 ea.	2.7M	3.3M	3.9M	4.7M	5.6M	1/4 WATT 5% - 50 PCS.

ASST.	1 ea.	10 OHM	20 OHM	50 OHM	100 OHM	250 OHM	500 OHM
ASST. A 2 ea.	10 OHM <td>20 OHM<td>50 OHM<td>100 OHM<td>250 OHM<td>500 OHM<td>1K</td></td></td></td></td></td>	20 OHM <td>50 OHM<td>100 OHM<td>250 OHM<td>500 OHM<td>1K</td></td></td></td></td>	50 OHM <td>100 OHM<td>250 OHM<td>500 OHM<td>1K</td></td></td></td>	100 OHM <td>250 OHM<td>500 OHM<td>1K</td></td></td>	250 OHM <td>500 OHM<td>1K</td></td>	500 OHM <td>1K</td>	1K
ASST. B 2 ea.	1K	2K	5K	10K	20K	50K	100K
ASST. C 2 ea.	10K	20K	50K	100K	250K	500K	1M

Each assortment contains 14 pcs of 10 turn pots. All pots are available in single unit quantities. \$9.95 Per Ass't.

\*Astrisk Denotes Items On Special For This Month\*  
Satisfaction Guaranteed. \$5.00 Min. Order. U.S. Funds.  
California Residents - Add 6% Sales Tax - Data Sheets 25c each  
Send a 13c Stamp (postage) for a FREE 1976 Catalog

# JAMES

1021 HOWARD AVE., SAN CARLOS, CA. 94070  
PHONE ORDERS - (415) 592-8097

### 74LS00 TTL

74LS00	39	74LS55	39	74LS151	1.55
74LS01	39	74LS73	65	74LS153	1.89
74LS02	39	74LS74	65	74LS157	1.55
74LS04	45	74LS75	79	74LS162	2.25
74LS05	45	74LS76	65	74LS163	2.25
74LS08	39	74LS83	2.19	74LS164	2.25
74LS10	39	74LS86	65	74LS181	3.69
74LS13	79	74LS90	1.29	74LS180	2.85
74LS14	2.19	74LS92	1.25	74LS181	2.85
74LS20	39	74LS93	1.25	74LS192	2.85
74LS26	49	74LS95	2.19	74LS193	2.85
74LS27	45	74LS98	1.50	74LS194	2.25
74LS28	49	74LS107	65	74LS195	2.25
74LS30	39	74LS112	65	74LS257	1.89
74LS32	45	74LS132	1.55	74LS260	55
74LS40	49	74LS136	65	74LS279	79
74LS51	39	74LS138	1.89	74LS670	5.95

THIS MONTH ONLY!! DL728  
The DL728 is a dual 0's common cathode red display. It is ideal for use with clock chips. See segments are already multiplexed.  
\$1.95

QDPT	ON	OFF	ON	221	2.06	2.06	10.28	30.99	MINIATURE TOGGLE
	ON	OFF	ON	223	2.06	2.06	1.68	1.61	
	ON	OFF	ON	121	2.36	1.96	1.43	1.30	
	ON	OFF	ON	123	2.06	1.86	1.31	1.10	

QDPT - SERIES PA. P01	Model	1	Quantity per
-----------------------	-------	---	--------------

## This Month's Specials

### NEW Fairchild VHF Prescaler Chips

Type	Description	Price
11C01FC	High Speed Dual 5-4 Input OR/NOR	\$15.40
11C05DC	1 GHZ Counter Divide By 4	\$74.35
11C05DM	1 GHZ Counter Divide By 4	\$110.50
11C06DC	UHF Prescaler 750 MHz D Type Flip/Flop	\$12.30
11C24DC	Dual TTL VCM	\$2.60
11C44DC	Phase Freq. Detector	\$2.60
11C58DC	ECL VCM	\$4.53
11C70DC	600 MHz Flip/Flop With Reset	\$12.30
11C83DC	1 GHZ 248/256 Prescaler	\$29.90
11C90DC	650 MHz ECL/TTL Prescaler	\$16.00
11C90DM	650 MHz ECL/TTL Prescaler	\$24.60
11C91DC	650 MHz ECL/TTL Prescaler	\$16.00
11C91DM	650 MHz ECL/TTL Prescaler	\$24.60
95H90DC	250 MHz Prescaler	\$9.50
95H90DM	250 MHz Prescaler	\$16.55
95H91DC	250 MHz Prescaler	\$9.50
95H91DM	250 MHz Prescaler	\$16.50

### RF TRANSISTORS

#### New

RCA 40290	12.5v, Ft. Typ. 500MHz 2 watts min. at p. in 0.5 watts	\$2.48
2N2857	\$1.85	2N6080 \$5.45
2N3375	\$7.00	2N6081 \$8.60
2N3866	\$1.08	2N6082 \$11.25
2N4072	\$1.50	2N6083 \$12.95
2N4427	\$1.20	2N6084 \$13.75
2N5179	\$6.28	2N6166 \$85.00
2N5589	\$4.60	MRF511 \$8.60
2N5590	\$6.30	MCM918 \$2.50
2N5591	\$10.35	MMT2857 \$2.50
2N5637	\$20.70	

### TUBES

1P21	\$19.95	6146B/8298A	\$5.50
2E26	\$4.00	6360	\$5.50
4X150C	\$18.00	6661	\$1.00
4X150A	\$15.00	6680	\$1.00
4CX250B	\$24.00	6681	\$1.00
4X250F	\$22.00	6939	\$5.50
DX415	\$25.00	7984	\$3.95
572B/T160L	\$22.00	8072	\$32.00
811A	\$7.95	8106	\$1.95
813	\$19.00	8156	\$3.95
931A	\$9.95	8950	\$5.50
4652/8042	\$6.95	6106	\$3.95
5894	\$32.00	7289/2C39A 10/12.50	
6146A	\$4.25		

**JUST ARRIVED!** These radios have just been pulled out of service. Set up for approx. 150 MHz. Clean. All tubes included. No accessories. Prices FOB Phoenix.

Motorola U43 GGT	\$49.95
GE TPL	\$99.95
GE MT-33	\$39.95

Collins KWI Transmitter, Mint, extra set of tubes plus manual \$499.95

We have all types of test equipment.

# MHz electronics

2543 N. 32ND STREET  
PHOENIX, ARIZONA 85008  
PH. 602-957-0786

# flea market

**HAMFAIR-76, TACOMA, Washington, August 21 & 22.** The Radio Club of Tacoma (W7DK) presents HAMFAIR-76 at Pierce County Fairgrounds, 11 miles south of Puyallup, Washington. Contests, flea market, seminars, women & children's activities, contests, Saturday evening dinner and Sunday morning loggers breakfast. Free camping with electrical hook-ups. First prize ICOM IC-230. Contact W7GPR, 3421 E. 138th St., Tacoma, WA 98446. Phone: 531-3821.

**RADIO EXPO '76, September 18, 19, near Chicago.** Exhibits, seminars, giant flea market open Friday night. Campers welcome. Advance ticket \$1.50. Box 1014, Arlington Heights, Ill. 60006.

**VIRGINIA.** Shenandoah Valley Amateur Radio Club Hamfest, August 1, 1976. Clarke County Ruritan Fairgrounds, Berryville, VA (8 mi. east of Winchester on Route #7). New and better facilities. Exhibitors no charge. Further info from Neil Woods, W4LOG.

**MELBOURNE, FL., SEPT. 11-12.** The 11th Annual Melbourne, Florida Hamfest will be held Saturday and Sunday, September 11-12, 1976, from 9 a.m. to 5 p.m. each day in the air conditioned Melbourne Civic Auditorium located on Hibiscus Boulevard. Donation is \$2.50 per adult. Full program includes forums, meetings, auction, swap tables, commercial exhibits, awards, prizes, etc. Talk in on 25/85 and 52/52. Sponsored by Platinum Coast Amateur Radio Society. For more info write P. O. Box 1004, Melbourne, FL 32901.

**FLORIDA.** Melbourne Hamfest, September 11 & 12, Melbourne Auditorium. Contact Mike Waters, VE3BYO/W4, 965 Golden Beach Blvd., Indian Harbour Beach, FL 32937.

**MEMPHIS, TN.** Hamfest sponsored by Mid-South Amateur Radio Association, Delta Amateur Radio Club and Mid-South VHF Club. October 2 & 3 at State Technical Institute, 5983 Macon Cove, Memphis. Large flea market, no charge for exhibitors. Contact D. H. Powell, 4662 Crossover Lane, Memphis, TN 38117 for details.

**MISSOURI.** SCARC Hamfest, August 22 at Diermann Lake (located about 15 miles southwest of St. Charles, Missouri on State Highway K). Admission \$1. Large flea market (no charge for set up). For more info contact St. Charles Amateur Radio Club, 3032 Mockingbird Dr., St. Charles, MO 63301.

**WELCOME — Bicentennial Edition Golden Spread Hamfest.** Quality Inn, Amarillo, Tex. Aug. 14, 15, 1976. Full info - write to 4408 Mesa Circle, Amarillo, Tex. 79109.

**HAMFEST — Springfield, Illinois!** First. Sangamon Valley Radio Club invites everyone. Sunday, September 26th. Rain-shine. Sangamon County Fairgrounds, New Berlin, Illinois on U.S. 36. Write K9HDZ, 622 Magnolia, Rochester, Illinois 62561.

**ELMIRA, N. Y. HAMFEST:** Sept. 25, 1976. Chemung County Fairgrounds. Flea market, dealer displays, technical talks. Talk in 10/70-146.52. \$2.00 advance sale - \$2.50 at gate. For further information, WA2SMM, 320 W. Ave., Elmira, N. Y. 14904.

**CINCINNATI HAMFEST:** 40th Anniversary Hamfest - Sunday, September 19, 1976 at the New Improved Stricker's Grove on State Route 128, one mile west of Ross (Venice) Ohio. Flea market, exhibits, contests, model aircraft flying, food and beverages all day. Advance ticket sales \$7.00 - Tickets at the gate \$8.00 - covers everything. For further information: Lillian Abbott, 1424 Main Street, Cincinnati, Ohio 45210.

**K2DEL.** Knight Raiders VHF Club's auction and flea market will be held on Saturday, August 14th, at St. Joseph's Church of East Rutherford, Hoboken Road, East Rutherford. Free admission, free parking, refreshments available. Talk-in will be on 146.52. Doors will open 10 AM. Flea market tables: \$6.00 for a full table, \$3.50 for a half table. Reserve your tables in advance by writing to The Knight Raiders VHF Club, K2DEL, P. O. Box 1054, Passaic, New Jersey 07055.

**CAST YOUR BALLOT** Nov. 6th and 7th for Southern Hospitality at the Florida Section Convention on the beach at the Sheraton Sand Key hotel, Clearwater Beach. Technical sessions on the latest advances in Amateur Radio and orientation for the newcomer. Family attractions nearby, including Disney World and Busch Gardens. Early snowbirds can catch season activity at its best. Bonus gift for early registration of \$3.00. Saturday night banquet with ARRL President Dannels and others at \$9.00 per. Write Florida Gulf Coast Amateur Radio Council - FGARC, Inc., P. O. Box 157, Clearwater, Florida 33517.



### the indispensable BIRD 43 THRULINE® WATTMETER

Read RF Watts Directly.

0.45-2300 MHz, 1-10,000 watts ± 5%, Low Insertion VSWR — 1.05.

Unequaled economy and flexibility: Buy only the element(s) covering your present frequency and power needs, add extra ranges later if your requirements expand.

AUTHORIZED

## BIRD DISTRIBUTOR

WEBSTER COMMUNICATIONS  
115 BELLARMINE  
ROCHESTER, MICHIGAN 48063  
(313) 375-0420

\*T.M. of BIRD ELECTRONIC CORP.

## TEST EQUIPMENT

All equipment listed is operational and unconditionally guaranteed. Money back if not satisfied—equipment being returned must be shipped prepaid. Include check or money order with order. Prices include UPS or motor freight charges.

BECKMAN 7570A Counter Freq conv	
10-1000MHz	275
BOONTON 190A Q-mtr 30-200MHz	325
BOONTON 202B AM-FM sig gen	
54 216MHz	275
DEI TDU 2 30MHz video display	55
GR546C Audio microvoltage	65
GR821A Twin-T imp bridge to 40MHz	165
GR1302A Audio Osc .01-100kHz	75
HP160B (USM105) 15MHz scope with norm horiz, dual trace vert plugs	375
HP166B (Mil) Delay sweep for above	130
HP185A Sampling Scope 1 GHz 186B xsfr rise plug	335
HP202B LF Osc .5Hz-50kHz 10v. out	75
HP205AG Lab Audio Gen .02-20kHz	195
HP212A Pulse Gen .06-5kHz PRR	65
HP430CR Microwave Pwr Mtr	40
HP540B Transfer Osc to 12.4GHz for use with HP524 type counters	115
HP571B-561B Digital clock/rcdr	245
HP608D (TS510) std sig gen 10-420MHz	425
HP616 Sig gen 1.8-49Hz FM-CW	385
HP686 Sweep Gen 8.2-12.49Hz Sweep range 4.4mHz-4.49Hz	595
HP803A VHF Ant bridge 50-500MHz	95
SINGER SSB4 Sideband spec anal 0-40MHz, res. to 10Hz	685
TEK 181 Time-mark scope calib.	45
TEK 190 Sig gen (const ampl) 50MHz	125
TEK 551 Dual beam 27MHz scope less plug-ins	735
TEK 565 Dual beam 10MHz scope less plug-ins	525
TS 505 Std VTVM (rt to 500mHz)	65


For complete list of all test equipment send stamped, self-addressed envelope

## GRAY Electronics

P.O. Box 941, Monroe, Mich. 48161  
Specializing in used test equipment.
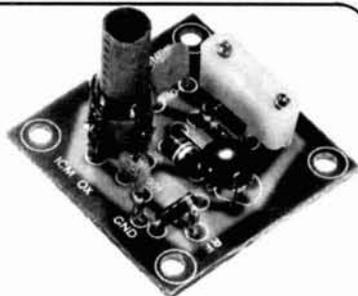
# for the experimenter!

INTERNATIONAL CRYSTALS & KITS  
OSCILLATORS • RF MIXER • RF AMPLIFIER • POWER AMPLIFIER



### OX OSCILLATOR

Crystal controlled transistor type. 3 to 20 MHz, OX-Lo, Cat. No. 035100. 20 to 60 MHz, OX-Hi, Cat. No. 035101  
*Specify when ordering.*

\$3.95 ea.



### MXX-1 TRANSISTOR RF MIXER

A single tuned circuit intended for signal conversion in the 30 to 170 MHz range. Harmonics of the OX or OF-1 oscillator are used for injection in the 60 to 179 MHz range. 3 to 20 MHz, Lo Kit, Cat. No. 035105. 20 to 170 MHz, Hi Kit, Cat. No. 035106  
*Specify when ordering.*

\$4.50 ea.



### PAX-1 TRANSISTOR RF POWER AMP

A single tuned output amplifier designed to follow the OX or OF-1 oscillator. Outputs up to 200 mw, depending on frequency and voltage. Amplifier can be amplitude modulated. 3 to 30 MHz, Cat. No. 035104  
*Specify when ordering.*


\$4.75 ea.



### OF-1 OSCILLATOR

Resistor/capacitor circuit provides osc over a range of freq with the desired crystal. 2 to 22 MHz, OF-1 LO, Cat. No. 035108. 18 to 60 MHz, OF-1 HI, Cat. No. 035109  
*Specify when ordering.*

\$3.25 ea.

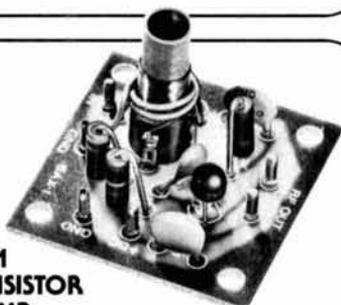

### SAX-1 TRANSISTOR RF AMP

A small signal amplifier to drive the MXX-1 Mixer. Single tuned input and link output. 3 to 20 MHz, Lo Kit, Cat. No. 035102. 20 to 170 MHz, Hi Kit, Cat. No. 035103.  
*Specify when ordering.*

\$4.50 ea.



### DAX-1 BROADBAND AMP

General purpose amplifier which may be used as a tuned or untuned unit in RF and audio applications. 20 Hz to 150 MHz with 6 to 30 db gain. Cat No. 035107  
*Specify when ordering*

\$4.75 ea.



.02% Calibration Tolerance  
**EXPERIMENTER CRYSTALS**  
(HC 6/U Holder)

Cat. No.	Specifications	
031080	3 to 20 MHz — for use in OX OSC Lo <i>Specify when ordering</i>	\$4.95 ea.
031081	20 to 60 MHz — For use in OX OSC Hi <i>Specify when ordering</i>	\$4.95 ea.
031300	3 to 20 MHz — For use in OF-1L OSC <i>Specify when ordering</i>	\$4.25 ea.
031310	20 to 60 MHz — For use in OF-1H OSC <i>Specify when ordering.</i>	\$4.25 ea.


Shipping and postage (inside U.S., Canada and Mexico only) will be prepaid by International. Prices quoted for U.S., Canada and Mexico orders only. Orders for shipment to other countries will be quoted on request. Address orders to:  
M/S Dept., P.O. Box 32497,  
Oklahoma City, Oklahoma 73132.



**International Crystal Mfg. Co., Inc.**  
10 North Lee  
Oklahoma City, Oklahoma 73102
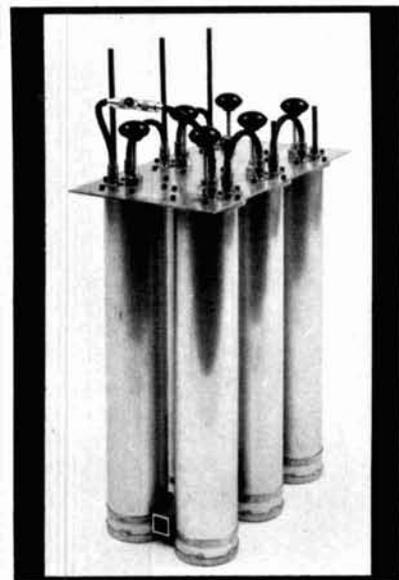
# DUPLEXER & CAVITY KITS

**NOW** Temperature Compensated ...with Invar®!



• Easier than ever to assemble and tune • Rugged Construction • Easy maintenance • Low Cost

**Mod. 62-3...** 6 cav., 2 mtr., insertion loss 0.6 db with isolation 100 db typical. pwr. 350 w \$349 ea.

**Mod. 4220-3...** 4 cav. 220 MHz insertion loss 0.6 db with 80 db isolation typical. pwr. 350 w \$249 ea.

**Mod. 4440-3...** 4 cav. 440 MHz, insertion loss 0.6 db with 80 db isolation typical, pwr. 350 w \$249 ea.

**Mod...** 30 Cavity Kits 2 mtr. \$65 ea., 220 MHz \$65. ea., 440 MHz \$65 ea.; 6 mtr. \$115 ea.

Also available: 6 mtr., 4 cav. \$399, 2 mtr. 4 cav. \$249, 440 MHz TV Repeater Duplexer

Only hand tools are necessary to assemble Kits!

All of our Kits are available assembled and tuned. Call or write for prices to Distributor: **TUFTS RADIO**, 386 Main St., Medford, Mass. 02155. Phone (617) 395-8280.

(Prices F.O.B. Medford, Mass. All units can be shipped U.P.S.-C.O.D. orders require \$50 deposit. —Mass. residents add 5% sales tax.)

# flea market

**OHIO:** 34th Annual Findlay Hamfest - Sept. 12, Riverside Park, Findlay, Ohio. Talk-in 146.52. For advanced tickets and/or info write: (SASE please for under 5 tickets) Clark Foltz, W8UN, 122 W. Hobart St., Findlay, Ohio 45840.

**LA PORTE, INDIANA** — The combined La Porte County Amateur Radio Clubs will hold their Fall Hamfest on Sunday, August 29th, 1976 at the La Porte County Fairgrounds in La Porte, beginning at 7 a.m. Chicago time. Overnight camping available. Indoors in case of rain. No table or set-up charge. Paved midway, good food and drink. \$2.00 donation at the gate. For info write, P. O. Box 30, La Porte, IN 46350. Talk-in on .01-.61 & 94 Simplex.

**MICHIGAN:** The Fourth Annual L'Anse Creuse ARC Swap & Shop will be held on September 19, 1976 at the L'Anse Creuse High School in Mount Clemens, Michigan. Doors will be open from 0900 to 1500 EDST. First prize \$200.00 cash. Talk-in on 146.52 and 146.94. Admission \$1.50 at door, \$1.00 in advance. For tickets enclose \$1.00 and S.A.S.E. and send to, Robert Harder, WB8IL1, 51769 Base, New Baltimore, Mich. 48047.

**MICHIGAN:** The Jewish Community Center Amateur Radio Club of Metropolitan Detroit's fourth Annual Swap 'n Shop is Sunday, August 22, from 9:00 a.m. to 3:00 p.m. at the new Center at Maple and Drake Rds., W. Bloomfield. Talk in on 146.94. For more information, contact Bob, W8DGR at 6600 W. Maple Rd., W. Bloomfield, Mi. 48033.

**SOUTH JERSEY RADIO ASSN.,** 28th Annual Hamfest: Sept. 12, 1976, 10-5 p.m. at Molia Farms, Malaga, N. J. Lake, picnic grounds and food available. Tailgate sales, swap shop and door prizes. Family tickets: advance sales - \$2.50, gate sales - \$3.50. Advance sales send S.A.S.E. to Jack Koch, Box 103, Cherry Hill, N. J. 08002. Talk in 146.52.

**AURORA, ILLINOIS,** August 22, 1976. The Fox River Radio League - W9CEQ Hamfest will be held August 22, 1976 at beautiful Phillips Park, east edge of Aurora, U.S. Hwy. Rt. #30. Talk in on 146.94. All day family fun, picnic, zoo, lake and flowers. Same old price. \$1.00 advanced with S.A.S.E. to F.R.R.L., P. O. Box 443, Aurora, Ill. 60507.

**1976 DELTA QSO PARTY.** All amateurs are invited to participate. Contacts must take place from 2000Z Sept. 25 to 0200Z Sept. 27. No time or power restrictions. Amateurs outside Delta Division will attempt to contact as many amateurs inside Delta Division (Ark-La-Miss-Tenn) as possible. Delta Division Amateurs will attempt to contact as many amateurs as possible both inside and outside of Delta Division. For rules and complete details, send SASE to Malcolm P. Keown, W5RUB, 213 Moonmist, Vicksburg, MS 39180.

**BLOSSOMLAND SWAP-SHOP,** October 3rd, Berrien County Fair Grounds, Berrien Springs, Michigan. Greatly expanded facilities, 150 tables, entertainment, refreshments. Advance ticket donation \$1.50, tables \$2.00. Write: John Sullivan, P. O. Box 345, St. Joseph, Michigan 49085. Make checks payable to: Blossomland Hamfest.

## Stolen Equipment

**ICOM IC-22A** transceiver, s/n1216, 16/76, 31/91, 01/61 xtals plus standard Icom xtals. Motorola type microphone. Realistic PRO-11 scanner, s/n 08370930. Xtals for 155.79 & 155.685 MHz in the unit. Sanyo FT-867 AM/FM 8 trk in dash car radio, sn/87661611. Realistic MPA-10 PA amplifier, non-stock mike w/PA amp. Name and SSN (214-68-9618) engraved on each unit. Any info contact Steve Martin, WA3SAD (phone 301-627-4933).

**UNITMETRICS ULTRA-COM 25,** SN 080213, stolen from locked auto parked in residence driveway about 5 AM, May 12. Unit engraved N. C. driver license #2067134. Contact Greensboro, N. C. Police Department or W4DWR.

**ICOM IC230** two meter FM transceiver with mount and 32 xtal, ser. no. 2835. TPL model 1002 two meter power amplifier ser. no. 0426. Regency 10 channel scanner, model ACTR 10HLU with all crystals and antenna junction box, ser. no. 185A88279. If located, advise San Diego Police Dept., Burglary Div. at 236-6281. Case #76-33350 or Zane Sprague, K6WK (714) 481-0594.

## ! HELP !



**MIXED VALUES. DISC CERAMIC CAPACITORS \$5.00/LB. PPD. IN U.S.A.**

If you don't like the pound you get — call or write and we'll send another pound FREE. (And you keep the first pound.)

.7-9pF Glass Piston Trimmer, JFD, VC-1 \$2.25 ea  
10 for \$1.75 ea  
4.7 MFD/10V Sprague 158D \$7.50/Hundred



215-265 MHz — Plug in front-end and video unit with BW 1.5 KC to 1 MC built-in deviation meter. Defense Electronics Model TMR-5A. Only 2 in stock \$315.00



RVCR 2 to 30 MHz depending on the plug-in front end. Provision for XTAL control. Makes a fine single-channel H.F. RCVR (Westcars, etc.) \$125.00

P.S. — We only have 2-4 & 4-8 MHz plug-ins. First order gets choice.

**SPECIAL OFFER . . . 1 G.E. Prog. Line 30W, 4 Freq., Table Top Base Station, on 2 meters (01/61, 69/09, 84/24 and 99/39) \$200.00**  
WE ARE BUYERS as well as sellers. What have you? We don't have a catalog, by the time we'd publish it the merchandise would be gone.

**DISC-CAP, 19075 BRAEMORE RD. NORTHBRIDGE, CA. 91326 213-360-3387**

## SYNTHESIZERS

We have the worlds largest selection of synthesizers for receivers, transmitters and transceivers. For complete details see our 1/3 page ad in the April 1976 issue of this magazine or call or write for additional information. Phone orders accepted between 9 AM and 4 PM EDT. (212) 468-2720

## VANGUARD LABS

196-23 JAMAICA AVENUE  
HOLLIS, N. Y. 11423

## FIRST CLASS FCC LICENSE


CIE will help you pass the government-administered First Class FCC License exam . . . broaden your career opportunities in electronics. In-depth electronics career training to help you add to your technical skills and knowledge, prepare for valuable First Class FCC License at the same time. Basic and advanced training. Study at home, spare time. Fully accredited career courses.

Send today for Free FCC License booklet and school catalog. G. I. Bill info on request. For your convenience, we'll try to have a school rep contact you. No obligation. Write CIE — Cleveland Institute of Electronics, Inc., Dept. WHM-01, 1776 East 17th Street, Cleveland, Ohio 44114.

# BULLET ELECTRONICS

PO BOX 1465 LAKE WORTH, FLORIDA 33460

## TB 03 TIMEBASE KIT

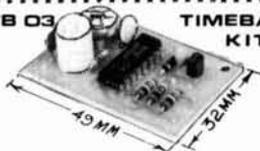

- ULTRA LOW CURRENT CMOS CIRCUIT
- BUFFERED OUTPUT
- WORKS DIRECTLY WITH 50252, 5314, 5316, 5375 ETC.
- QUALITY DRILLED PLATED GLASS BOARD
- ADJUSTABLE OSC FREQUENCY
- .01% ACCURACY
- LOW COST

**\$5.00** EA.

- 10% REFUND ON ALL ORDERS NOT SHIPPED IN 48HRS!
- QUALITY PARTS AND KITS
- POSTAGE PAID ON ALL ORDERS OVER \$10.00 (unless noted)



HAPPY BIRTHDAY AMERICA!

**LOUD!**  
**10 WATT WARBLE ALARM KIT**  
 All the components you need to build a dual tone warble alarm but the speaker.  
 Complete with PC Board  
 6-15VDC \$2.50 complete

BULLET WAS THE FIRST ON THE MARKET WITH A 60HZ TIMEBASE FOR LESS THAN \$10.00 (TB-01). THE TB-02 WAS A NEWER MODEL THAT HAD A SMALLER CRYSTAL AND LOWER CURRENT DRAIN. NOW WE ANNOUNCE THE TB-03. AVAILABLE IN 50 OR 60HZ OUTPUT MODELS. PLEASE SPECIFY OUTPUT FREQUENCY DESIRED.

## 607 \$17.76 SPECIAL OFFER!!


### MOBILE CLOCK KIT

DRILLED AND PLATED BOARDS .01% LOW CURRENT TIMEBASE (60HZ)  
 EVERYTHING YOU NEED BUT THE CASE  
 3 3/4" wide (2 1/2" for readouts)  
 +9 to +16 Volts DC  
 ADJUSTABLE BRIGHTNESS  
 LARGE .4" LED READOUTS (RED)  
 CAN BE USED AS A TIMER  
 SORRY: 12 HOUR FORMAT ONLY.  
 (FULL 24 HOUR ALARM CAPABILITY FOR CAMPERS, TRUCKS AND VANS)  
 SPECIAL NOISE SUPPRESSION CIRCUITRY

\* THIS PRICE GOOD TILL AUGUST 31, 1976 ONLY !!
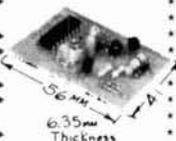
## TOUCHTONE ENCODER KIT

A Single 18 pin IC chip that locks onto a 560KHz resonator and produces 16 different tone pairs that will work directly with the Western Electric Touchtone System. Can be acoustically coupled.



- Low standby current (8ma to 10ma).
- Wide voltage range (6 to 20volts).
- No tuning required.
- Delayed PTT circuit sinks 100MA and holds carrier in between tones.
- Adjustable output level to match most radios.
- Plug compatible with Digitran Keyboards.
- 12 or 16 tone capability.
- Audio drive circuit allows tone monitoring or acoustic coupling (speaker not included).
- Small size.
- Low cost.

TE 01 \$12.00

YOU GET EVERYTHING THAT THE TE-01 HAS, BUT LESS THE PTT CIRCUIT AND AUDIO OUTPUT CIRCUIT. THE EXCLUSION OF THESE FEATURES ALLOWS US TO MAKE THE UNIT SMALLER FOR OPERATION WITH HT'S. CONNECTS DIRECTLY INTO THE MIKE CIRCUIT

TE 02 \$10.00

## AIRCRAFT CLOCK-TIMER

NEED TO KNOW REAL TIME AND ELAPSED TIME FROM ONE COMPACT INSTRUMENT? THIS KIT USES TWO MOS CLOCK CHIPS AND A SPECIAL SWITCHING CIRCUIT TO GIVE YOU 24 HOUR ZULU TIME AND A RESETTABLE ELAPSED TIME INDICATOR FOR CHECKPOINTS AND INSTRUMENT APPROACHES. THE TIMEBASE MAKES IT PORTABLE FOR USE ON 9 TO 15 VOLTS. THE WHOLE THING WILL MOUNT UP IN A STANDARD PANEL INSTRUMENT CASE. YOU WILL HAVE TO FURNISH THE SWITCHES AND CASE BUT WE GIVE YOU THE REST.

26.95

**MK 03 KIT**

FLORIDA RESIDENTS ADD 4%

TERMS

NO COD- check or MO

FOREIGN ORDERS ADD 10% 20% for Air Mail

ALL ORDERS SHIPPED P.P. ADD 5% For Air Mail

ORDERS UNDER \$10.00 ADD 60c HANDLING.

**ORDERS OVER \$50 TAKE 10% DISC**

DU TO THE NUMEROUS REQUESTS WE HAVE DECIDED TO OFFER THE VARIOUS SECTIONS OF REGULATED POWER SUPPLIES AS "SEMI KITS" MANY OF OUR REQUESTS HAVE BEEN FROM PEOPLE WITH TRANSFORMERS THAT NEED THE OTHER ITEMS TO BUILD A GOOD BENCH SUPPLY.

PSB-01 BASIC REGULATOR BOARD, GIVES YOU THE REGULATOR SECTION

TO BUILD JUST ABOUT ANY SUPPLY YOU WANT. HAS ADJUSTABLE OUTPUT, ADJUSTABLE CURRENT LIMITING, RIPPLE REJECTION, FIXED OR VARIABLE OPERATION, SHORT CIRCUIT PROTECTION AND 100MV REGULATION! THIS KIT COMES WITH: REGULATOR IC DRILLED AND PLATED PC BOARD, RESISTORS, CAPACITORS AND COMPLETE INSTRUCTIONS TO BUILD SEVERAL TYPES OF POWER SUPPLIES.

**\$9.95**

PSB-02 20 AMP ADD-ON COMPONENTS, GIVES YOU THE POWER COMPONENTS TO BUILD A 20 AMP SUPPLY WHEN USING THE PSB-01 KIT:

- 2 HIGH CURRENT PASS TRANSISTORS
- 1 MEDIUM POWER DRIVER TRANSISTOR
- LARGE PRE-DRILLED HEATSINK (120Watts)
- TRANSISTOR MOUNTING KITS AND HARDWARE
- #10 INSULATED HOOKUP WIRE
- SPECIAL .032 OHM EMITTER RESISTORS (10Watts)
- COMPLETE CHARTS FOR CURRENT LIMIT AND VOLTAGE OUTPUT SELECTION.

**\$7.95**

PSB-03 RECTIFIER AND FILTER SECTION (up to 25 amps)

- 2 LARGE 35AMP STUO MOUNT DIODES
- DRILLED AND TAPPED HEATSINK
- SPECIAL CERAMIC INSULATORS
- QUALITY COMPUTER GRADE CAP. 40,000MFD @ 35V
- CAP MOUNTING BRACKET

**\$7.95**

PSB-03 for use with center tapped transformer ONLY

PSB-03B RECTIFIER AND FILTER SECTION (same as PSB-03 but with 4 diodes and insulators to build full wave bridge for use with transformers WITHOUT A CENTER TAPPED SECONDARY.

**9.90**

PSB-04 LOWER CURRENT POWER SUPPLY KIT, GIVES YOU THE PARTS (less the transformer) TO BUILD A WELL REGULATED, CURRENT LIMITED, SHORT PROOF SUPPLY THAT WILL HANDLE UP TO 5AMPS.

- TO-3 NPN PASS TRANSISTOR
- MEDIUM POWER DRIVER TRANSISTOR
- TRANSISTOR MOUNTING KIT
- CURRENT EMITTER RESISTORS
- 10,000MFD @ 60V COMPUTER GRADE CAP
- COMPLETE INSTRUCTIONS
- FOR USE WITH PSB-01 Basic regulator board

**\$5.95**

HEATSINK INCLUDED!

A WORD ABOUT TRANSFORMERS: The output of your transformer should total about five volts greater than the desired output voltage while the transformer is loaded to the maximum load the supply is designed for. Too little output means loss of regulation, while too much means the excess power must be dissipated in the pass transistors. If a center tapped transformer is used the voltage from either leg to the center tap should be five volts greater than desired output. If you are unsure about your transformer, drop us a line with the specifications and we will tell you what kind of supply you can build. We need RMS AC Voltage out of all windings at full operating load.

# NEW

from the  
RSGB

## VHF-UHF MANUAL

3rd Edition

by D. S. Evans, G3RPE & G. R. Jessop, G6JP

Here is the most comprehensive and up-to-date book on VHF & UHF ever prepared for the Radio Amateur.

In over 400 pages it thoroughly covers such topics as receivers, transmitters, space communications, filters, antennas and FM. Included is a major new section on Microwave work.

This latest edition is a handsome hardbound book and is sure to become the standard reference for anyone involved in the world above 30 MHz.

ORDER BY PHONE 800-258-5353

**ONLY \$12.95**

### HAM RADIO

GREENVILLE, N. H. 03048



# CLOSE OUT SPECIAL

## • REFERENCE DATA FOR RADIO ENGINEERS

We have just purchased the complete inventory of the recently superseded 5th edition of REFERENCE DATA FOR RADIO ENGINEERS. Here is a unique opportunity to own copies of this outstanding reference book at a very attractive price.

A must for any serious amateur. In 45 chapters it covers not only every area of basic radio theory, but also goes into such modern areas as micro-miniature electronics and space communications. Probably the most complete reference of this type. Sales of over 350,000 testify to its wide acceptance. 1,196 pages, hardbound.



Was \$23.00

**Now Only \$14.95**

Order 20678

ORDER BY PHONE 800-258-5353

### HAM RADIO

GREENVILLE, NH 03048

## HERE THEY ARE!

### TRANSFORMERS, Dual Secondary

110 V Primary — 10.5 volt, 1.5 amp and  
12 volt 1 amp secondary  
110 V Primary — dual 36 volt C.T. Secondary at 3 amp

### LEDs

High Dome, Red, Green, Yellow

Red ..... 8 for \$1  
Green ..... 6 for \$1  
Yellow ..... 6 for \$1

### CAPACITORS

5 PF at 15 volt ..... 20 for \$1  
330 PF at 15 volt ..... 20 for \$1  
120 PF at 5 kV ..... 10 for \$1  
180 PF at 5 kV ..... 10 for \$1  
.1 mfd at 200 v ..... 20 for \$1

### ELECTROLYTICS

1000 mfd at 6.3 volt ..... 6 for \$1  
220 mfd at 16 volt ..... 6 for \$1  
.0068 uf at 100 volt ..... 10 for \$1

### N.O. MOMENTARY PUSH BUTTON

7 for \$1

Cherry Micro Switch, 3.25 am. at 125V 3 for \$1

Magnetic Mike Holders ..... 99¢ each

Line Cord Strain Relief ..... 25 for \$1

5.8 mH Chokes ..... 15 for \$1

9V Battery Clips ..... 15 for \$1

Prime NE-2 Neon Bulbs ..... 8 for \$1

DIODES — 2.5 amp at 1000V ..... 5 for \$1

10 K Mini Pots ..... 3 for \$1

6.3 Mini Bulbs with pigtails ..... 10 for \$1

Orders over \$5 will be shipped prepaid in continental USA

Use "Check-Off" for complete product catalog.

# HOSFELT

## electronics

2610 SUNSET BLVD.  
STEUBENVILLE, OHIO 43925  
Phone 614 264-6464



## BARRY ELECTRONICS HAM HEADQUARTERS

Stocking Distr. for: Bird Wattmeters, Collins, Drake, ICOM, VHF Eng., EBC, Venus, B & W, Millen, Antenna Specialists, Hy-Gain, Mosley, CushCraft, DX Engineering, Savoy, Ten-Tec, Tri-Ex, Vibroplex — **THOUSANDS OF TUBES & SOCKETS IN STOCK — — HAM II ROTORS IN STOCK!** Eimac 8877, KLM Multi 2000, CD 44, Bird 43 Wattmeters, Cetron 572B. **In Stock for immediate delivery:** The NEW SPECTRONICS COUNTER, DDI, DDIC - Also KLM Multi 2000A. **In Stock 572B's, 8877's!** Also Hy-Gain Mobile Antennas.

Top Trades given on your used Collins gear! Fair Dealing since 1938! Write for best deals! Export inquiries expertly handled. Hours: Mon.-Fri. 9:00-6:00, Sat. 10:00-5:00. We buy unused tubes, vacuum variables and rcvrs for cash. Send your list too:

## Barry Electronics

512 BROADWAY, NY, NY 10012  
212-925-7000

## COME TO VERMONT

for

### 1976 INTERNATIONAL FIELD DAY

Bring your family for a weekend of camping and Amateur Radio activities.

**Sat., Aug. 14** — FCC tests for those who send in \$4 and Form 610, 3 weeks prior — Camping on the grounds.

**Sun., Aug. 15** — International Field Day — Exhibits, Flea Market, Contests, Raffle.

Contact Skip Sharpe, WA1REL, for early bird registration, FCC tests, etc. at 148 Sand Hill Road, Essex Junction, VT 05452.

## NOW AVAILABLE IN KIT FORM

6:1, 4:1 and 1:1 Baluns

• Frequency Range 3-30 MHz

• 2 KW Rating

• Lightning Protection Built In

All Prices Postpaid in USA / Add Shipping outside USA

Shipping Wt. 1 lb.

[California Residents Add 6% Sales Tax]

# 59+

## FIVE NINE PLUS

3402 Campus  
Claremont, Ca 91711  
(714) 621-1658



6:1 Assembled — 22.95

Kit — 16.95

1:1 & 4:1 Assembled — 16.95


Kit — 11.95

Case Only — 7.95

Core Only — 3.50

Antenna Products for the Amateur

**X NEW**

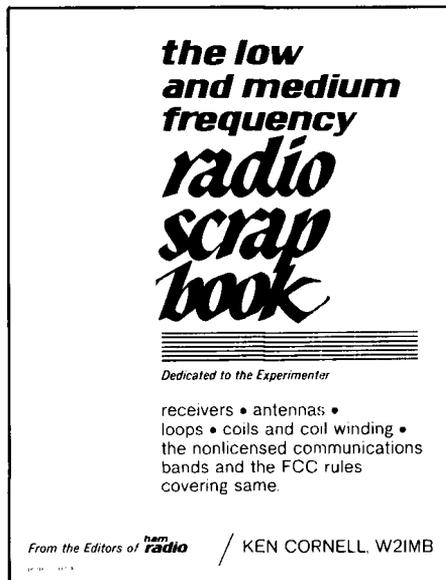

## **LOW & MEDIUM FREQUENCY SCRAPBOOK**

by Ken Cornell, W2IMB

Here in informal scrapbook form is the first book to explore the enticing world of those low frequencies you've been hearing about. This book shows how you can get on the air legally without any license in the 160 kHz region with simple, effective and easily built equipment. Full information is given regarding FCC rules and regulations. This may become a new Amateur band after WARC '79 — why not get a head start today with this valuable new book?

Order HR-LF **Only \$6.95**

In special custom loose leaf binder

Order HR-LFB **Just \$8.95**

**Available Now  
from**

**ham  
radio**

GREENVILLE, NH 03048

**Order by Phone TOLL FREE 800-258-5353**

# ANNOUNCING **SCS**'s NEW HF-10-100L

for use with



YAESU FT-301 Series  
160-10M, 10W, SSB  
Available in Fall

HF-10-100L  
SPECIAL  
BI-CENTENNIAL  
OFFER \$177.60  
VALID THROUGH 8-31-76  
FOR DIRECT ORDERS ONLY

## HF-10-100L AMPLIFIER

Frequency Range 3-30 MHz  
Input Power 10 W Nom., 5-20 W PEP range  
Output Power 100 W Nom.,  $\pm 1/2$  dB across band, 200-250W PEP output  
Input Impedance 50  $\Omega$  nom, adjustable to match exciter range under 2:1 across band  
Output Impedance 50  $\Omega$  nom, up to 3:1 VSWR acceptable with little degradation  
Current Drain 16 A nom, 20 A supply recommended at 13.6 VDC  
Power Supply 13.6 VDC recommended for best results, 11-14 VDC acceptable positive or negative ground  
Pre-amp 18 dB nom gain across entire HF band, 15 dB typ at 50 MHz, 3-4 dB NF  
Size 19.1 x 16.5 x 8.9 cm wt 1 1/2 Kg

The high level of quality of workmanship and performance will make the HF-10-100L very popular in short order. Now being used by West Coast Amateurs. Includes built-in low pass filter which cuts off at 35 MHz. User to supply additional low pass filters for bands below 15 meters. Class AB operation insures proper linearity and min. distortion.

HF-10-100L

\$219.95

SEE YOUR FAVORITE DEALER OR ORDER DIRECT FROM:



# SCS SPECIALTY COMMUNICATIONS SYSTEMS, INC.

8160 Miramar Rd., San Diego, CA 92126 • Louis N. Anciaux, WB6NMT, (714) 271-6310

**Webster** says:  
radio, inc.

Everything from A to Z  
in quality TRANSCEIVERS!



The TS 820 **KENWOOD** \$830.  
160 thru 10 meter. Solid state Transceiver  
with passband tuning.



The FT-221 YAESU Transceiver \$679.  
Solid state 2 meters SSB/FM/CW/AM

CTC UHF/VHF  
POWER TRANSISTORS FOR AMATEUR USE  
J101 UNDERWOOD CAPACITORS

Order Direct 1. Check or M.O. with order  
3 E-Z Ways 2. Bank Americard or Mastercharge  
3. C.O.D. (20% deposit, please!)

Write for FREE brochures and particulars on all models

**Webster**  
radio, inc.

2602 E. Ashlan  
Fresno, CA 93726  
Phone (209) 224-5111

## WHAT'S HAPPENING TONIGHT?



~~\$179.95~~ now \$132.50

The BEARCAT IV. The ultimate scanning monitor. Hear any eight channels of action, excitement and information from the nation's four public service frequency bands!

Please send me \_\_\_\_\_ Bearcat IVs  
@ \$132.50 ea.

Please send me \_\_\_\_\_ Crystal Certificates  
@ \$3.25 ea.

(Minimum order \$10.00)

COD's require 20% deposit)

Send check or money order to:

**BETA ELECTRONICS**

P. O. BOX 5869

PITTSBURGH, PA. 15209

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

## IRON POWDER TOROIDS

Chart showing uH per 100 turns

CORE SIZE	MIX 2	MIX 6	MIX 12	SIZE OD (in.)	PRICE USA \$
	5-30MHz u=10	10-90MHz u=8.5	60-200MHz u=4		
T-200	120			2.00	3.25
T-106	135			1.06	1.50
T-80	55			.80	.80
T-68	57	47		.68	.65
T-50	51	40		.50	.55
T-25	34	27	12	.25	.40

Ferrite beads 20-500 MHz \$2.00 Doz.

Wideband chokes 20-500MHz 95¢ Ea.

Specify core size and mix. Pack and ship 50¢  
USA & Canada. Air parcel post delivery  
worldwide \$2.00. 6 percent tax in Calif. Send  
for free brochure.

**PALOMAR ENGINEERS**

BOX 455 ESCONDIDO CA 92025

MAKE  
PROFESSIONAL LOOKING  
PC. BOARDS FAST  
AND EASY

•SENSATIONAL  
•REVOLUTIONARY  
•FANTASTIC

**STAMP-IT  
ETCH-IT**

Resistors Printed Circuit Boards All Work From 2 Hours to 10 Min

Simple as A.B.C.


A. Stamp Components on P.C. Board B. Use Paste to Interconnect Lines C. Etch Board

SE-2 KIT CONTAINS



PLUS  
UNLIT  
\$9.95

ADDITIONAL STAMPS

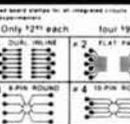

**M-TECH**

ENGINEERING, INC

BOX C

SPRINGFIELD, VIRGINIA 22151

703/334-0573



# TS-1 MICROMINIATURE ENCODER-DECODER


- Available in all EIA standard tones 67.0Hz-203.5Hz
- Microminiature in size, 1.25x2.0x.65" high
- Hi-pass tone rejection filter on board
- Powered by 6-16vdc, unregulated, at 3-9ma.
- Decode sensitivity better than 10mvRMS, bandwidth,  $\pm 2$ Hz max., limited
- Low distortion adjustable sinewave output
- Frequency accuracy,  $\pm 25$ Hz, frequency stability  $\pm 1$ Hz
- Encodes continuously and simultaneously during decode, independent of mike hang-up
- Totally immune to RF

Wired and tested, complete with K-1 element

**\$59.95**

K-1 field replaceable, plug-in, frequency determining elements

**\$3.00 each**

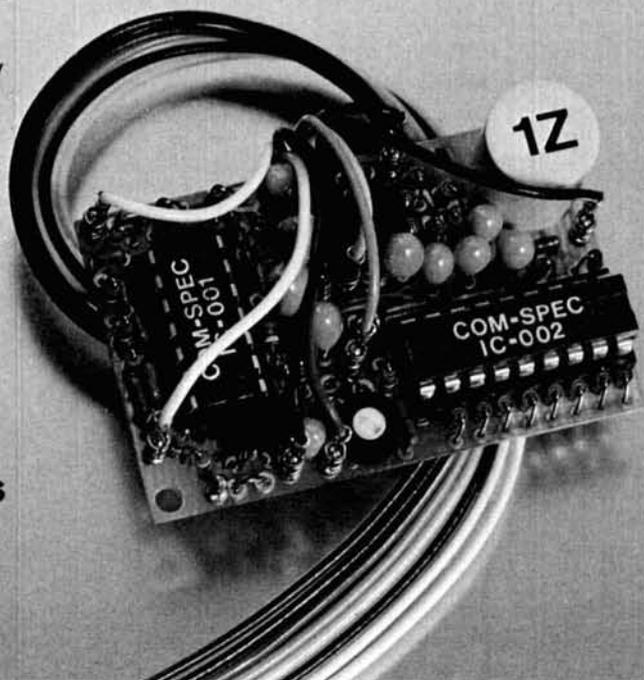

## COMMUNICATIONS SPECIALISTS

P.O. BOX 153  
BREA, CALIFORNIA 92621  
(714) 998-3021

### ALDELCO SEMI-CONDUCTOR SUPERMARKET

#### RF DEVICES

2N3375 3W 400 MHz.....	5.50	2N6080 4W 175 MHz.....	5.40
2N3866 1W 400 MHz.....	.99	2N6081 15W 175 MHz.....	7.95
2N5589 3W 175 MHz.....	4.75	2N6082 25W 175 MHz.....	10.95
2N5590 10W 175 MHz.....	7.80	2N6083 30W 175 MHz.....	12.30
2N5591 25W 175 MHz.....	10.95	2N6084 40W 175 MHz.....	16.30

#### HEAVY DUTY RECTIFIERS

200 Volt 100 Amp D08.....	8.50
200 Volt 250 Amp D09.....	12.50
400 Volt 2 Amp Silicon Rectifier RCA.....	15 for .99
1000 Volt 2 Amp Silicon Rectifier RCA.....	10 for .99
10,000 Volt Silicon Rectifier Erie, 65 mA.....	2.95

#### ALDELCO KITS

Digital Clock Kit. Hours, Minutes & Seconds. Large Half Inch LED readouts. Elapsed time indicator. 12 hour format with 24 hour alarm. Snooze feature, AM PM indicator. Power Supply, power failure indicator. Complete with wood grain cabinet. \$23.95

#### LOGIC PROBE KIT. LED INDICATORS

**\$14.95**

#### LEDs

Jumbo Reds. Long or Short bulb	6 for \$1.00
Jumbo Orange, Green, Clear Red or Green.	5 for \$1.00
209 Series. Green, Orange, Yellow or Red.	5 for \$1.00
RL2 Red or Micro Red.	5 for \$1.00

#### ZENERS


1N746 to 1N759 400 Mw ea. .25	1N4728 to 1N4764 1 w.....	35
10 assorted zener diodes unmarked		1.98

TC1068.....	.65	TTL's	
MPSA14.....	.90	7400.....	.20
2N3055.....	.99	7401.....	.20
2N2926 NPN.....	10/99	7403.....	.20
2N3904 or 2N3906.....	10/99	7404.....	.25
2N5496 or 2N6108.....	.35	7405.....	.25
FT0601 FET.....	.99	7406.....	.45
40673.....	\$1.55	7407.....	.45
741 or 709 14 Pin DIP.....	.25	7411.....	.30
555 Timer.....	.75	7413.....	.85
556 (Dual 555).....	\$1.75	7430.....	.20
200 Volt 25 Amp Bridge.....	\$1.00	7437.....	.50
1N914 - 1N4148.....	10 for .99	7442.....	1.10
1N34 - 1N60 - 1N64.....	10 for .99	we have others	

We quote on any device at any quantity. All items postpaid. \$5.00 min. order. Send stamp for catalog. NYS add tax.

# ALDELCO

2281H Babylon Tnpk., Merrick, NY 11566

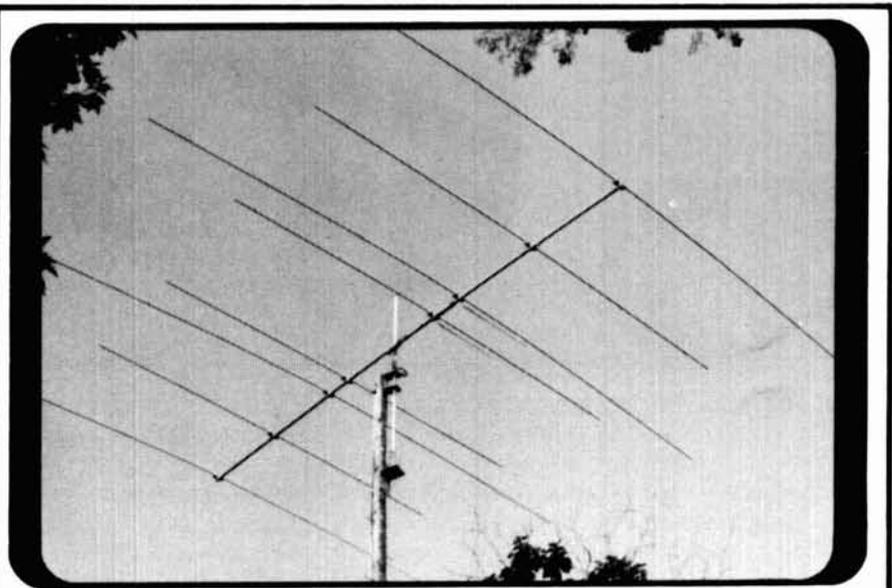

**QUALITY  
CONSTRUCTION  
IS THE  
DIFFERENCE**

**PERFORMANCE-ENGINEERED  
MONO & DUOBANDERS BY**

**antech labs INC.**  
8144 Big Bend St. Louis, Mo. 63119 (314) 822-7720

For More Information Write Or Call  
For Antech Specpak

MASTER CHARGE & BANK AMERICARD WELCOME

# Bind 'em and find 'em

**HAM RADIO BINDERS** . . . beautiful washable buckram binders complete with date labels. Available in two sizes, one to handle magazines through 1975 and a new large size to handle 1976 and on. Specify size.

Order HR-BDS (Small) **Just \$5.00 each**

Order HR-BOL (Large) **3 for \$13.50**

Order today from

**ham  
radio**

GREENVILLE, NH 03048

CALL TOLL FREE 800-258-5353



Aha, the SECRET of PC Board success finally revealed. A perfectly balanced lighting tool combining magnification with cool fluorescence. Excellent for fine detail, component assembly, etc. Lens is precision ground and polished.

Regularly \$70.00. Now, over 30% discount (only **\$49.00**) to all licensed Hams, verified in Callbook. Uses T-9 bulb (not supplied).

Include \$3.00 U.S. postage, or \$4.00 in Canada. \$5.00 elsewhere. California Residents include 6% sales tax. Or send stamped envelope for free brochure of other incandescent or fluorescent lamps suitable for all engineers, architects, students, etc.

Mastercharge and BankAmericard accepted

## D-D ENTERPRISES

Dept. A, P. O. Box 7776  
San Francisco, CA 94119

**NEW**



### COMPACT VHF RCVR PREAMP

- ONLY 1/2 x 2 3/8 INCHES
- STABLE, ADJUSTABLE CIRCUIT
- USES 2 LOW-NOISE FET'S
- EASY TO BUILD AND INSTALL
- KIT \$7.95, WIRED \$16.95

ALSO FM RCVR, XMTR, AND CONVERTER KITS. SEND SASE FOR CAT.

**hamtronics, inc.**


182 BELMONT RD., ROCHESTER, NY 14612

## We're Fighting Inflation No Price Rise for '76


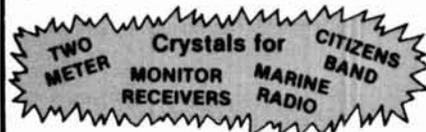
### FOR FREQUENCY STABILITY

Depend on JAN Crystals. Our large stock of quartz crystal materials and components assures Fast Delivery from us!



### CRYSTAL SPECIALS

Frequency Standards	
100 KHz (HC 13/U)	\$4.50
1000 KHz (HC 6/U)	4.50
Almost all CB sets, TR or Rec	\$2.50
(CB Synthesizer Crystal on request)	
Amateur Band in FT-243	ea. \$1.50
	4/\$5.00
80-Meter	\$3.00 (160-meter not avail.)

For 1st class mail, add 20¢ per crystal. For Airmail, add 25¢. Send check or money order. No dealers, please.



Div. of  
Bob Whan & Son Electronics, Inc.  
2400 Crystal Dr.,  
Ft. Myers, Fla. 33901  
All Phones: (813) 936-2397  
Send 10¢ for new catalog

### GROTH-Type

### COUNTS & DISPLAYS YOUR TURNS



- 99.99 Turns
- One Hole Panel Mount
- Handy Logging Area
- Spinner Handle Available

Case: 2x4"; shaft 1/4"x3"

**PRICES** POST PAID  
TC 2 — \$8.00  
TC 3 — \$8.75  
Spinner (S) — \$1.00  
Add \$0.75 for Air or UPS


Model TC2: Skirt 2-1/8";  
Knob 1-5/8"  
Model TC3: Skirt 3";  
Knob 2-3/8"

**R. H. BAUMAN SALES**

P.O. Box 122, Itasca, Ill. 60143
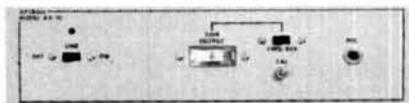
## FAST SCAN AMATEUR TELEVISION EQUIPMENT

- SOLID STATE
- BROADCAST QUALITY PERFORMANCE
- FOR TECHNICAL DATA AND PRICING, WRITE TO:



AX-10 TRANSMITTER



AM-1A RCVR MODEM

**APTRON LABORATORIES** BOX 323, BLOOMINGTON, IN 47401

You can be  
Among the  
best informed  
people in  
Amateur Radio  
with  
**hr** REPORT

Others have tried to equal HR Report in bringing their readers the important news of Amateur Radio, but only HR Report has survived to be the **first, quickest and most dependable source of Amateur news** that you will find anywhere. We bring you news as it happens each week, not many weeks or even months later as do the familiar monthly magazines.

**A completely new concept** in Amateur Radio publishing, this exciting newsletter covers the FCC, ARRL, Hamfests, New Products, AMSAT, Amateur Radio employment opportunities, Contests, DX, Propagation, Industry News — just about anything you might want to know about what is going on in Amateur Radio.

Read the report that government officials, leading amateurs, elected amateur officials and industry management all depend on each week to find out just what is going on in Amateur Radio. **There is nowhere else that you will find such news** reported so quickly, with such accuracy, on so wide ranging a number of subjects and presented in such a fair and unbiased manner.

We not only publish **each week**, we also send HR Report via first class letter mail. This means that you will often have stories in as little as 72 hours after we have learned of them. **Be among the best informed people** in Amateur Radio today with HR Report.

**Only \$16** for 52 issues U.S. & Canada

**\$26** World Wide Airmail

Order by Phone

TOLL FREE 800-258-5353

**hr** REPORT  
GREENVILLE, NH 03048





*Ham Radio's guide to help you find your local*

### *Alabama*

**LONG'S ELECTRONICS**  
3521 TENTH AVE. NORTH  
BIRMINGHAM, AL 35234  
800-633-3410  
Call us Toll Free to place your order

### *California*

**ANTENNA KING**  
25326 SOUTH CRENSHAW  
TORRANCE, CA 90505  
213-534-KING  
Retail sales — Mon. to Thurs., 9-5.  
48 hour mail order.

**HENRY RADIO**  
931 N. EUCLID AVE.  
ANAHEIM, CA 92801  
714-772-9200  
The world's largest distributor of  
Amateur Radio equipment.

**HENRY RADIO CO., INC.**  
11240 W. OLYMPIC BLVD.  
LOS ANGELES, CA 90064  
213-477-6701  
The world's largest distributor of  
Amateur Radio equipment

**HAM RADIO OUTLET**  
999 HOWARD AVENUE  
BURLINGAME, CA 94010  
415-342-5757  
Northern California's largest  
new and used ham inventory.

**M-TRON**  
2811 TELEGRAPH AVENUE  
OAKLAND, CA 94609  
415-763-6262  
We service what we sell.

**QUEMENT ELECTRONICS**  
1000 SO. BASCOM AVENUE  
SAN JOSE, CA 95128  
408-998-5900  
Serving the world's Radio Amateurs  
since 1933.

### *Colorado*

**C W ELECTRONIC SALES CO.**  
1401 BLAKE ST.  
DENVER, CO 80202  
303-573-1386  
Rocky Mountain area's complete  
ham radio distributor.

### *Florida*

**GRICE ELECTRONICS**  
320 EAST GREGORY  
PENSACOLA, FL 32502  
904-434-2481  
Your Gulf Coast Drake & Kenwood  
dealer.

### *Illinois*

**ERICKSON COMMUNICATIONS, INC.**  
5935 NORTH MILWAUKEE AVE.  
CHICAGO, IL 60646  
312-631-5181  
Headquarters for all your Amateur  
Radio needs.

**KLAUS RADIO, INC.**  
8400 NORTH PIONEER PARKWAY  
PEORIA, IL 61614  
309-691-4840  
Let us quote your Amateur needs.

**SPECTRONICS, INC.**  
1009 GARFIELD STREET  
OAK PARK, IL 60304  
312-848-6778  
Chicagoland's Amateur Radio  
leader.

### *Indiana*

**HOOSIER ELECTRONICS**  
P. O. BOX 2001  
TERRE HAUTE, IN 47802  
812-238-1456  
Ham Headquarters of the Midwest.  
Store in Meadow Shopping Center.

### *Kansas*

**ASSOCIATED RADIO**  
8012 CONSER P.O.B. 4327  
OVERLAND PARK, KS 66204  
913-381-5901  
Amateur Radio's Top Dealer.  
Buy — Sell — Trade.

### *Kentucky*

**COHOON AMATEUR SUPPLY**  
HIGHWAY 475  
TRENTON, KY 42286  
502-886-4535  
Ten-Tec dealer — Call 24 hours  
for best deal

### *Massachusetts*

**TUFTS RADIO ELECTRONICS**  
386 MAIN STREET  
MEDFORD, MA 02155  
617-395-8280  
New England's friendliest  
ham store.

### *Michigan*

**AUDIOLAND**  
36633 SOUTH GRATIOT  
MT. CLEMENS, MI 48043  
313-791-1400  
All major brands, new/used  
equipment & accessories.

**PURCHASE RADIO SUPPLY**  
327 E. HOOVER  
ANN ARBOR, MI 48104  
313-668-8696 or 668-8262  
We still sell Ham parts!

**RADIO SUPPLY & ENGINEERING**  
1203 WEST 14 MILE ROAD  
CLAWSON, MI 48017  
313-435-5660  
10001 Chalmers, Detroit, MI  
48213, 313-371-9050.

### *Minnesota*

**ELECTRONIC CENTER, INC.**  
127 THIRD AVENUE NORTH  
MINNEAPOLIS, MN 55401  
612-338-5881  
ECI is still your best buy.

### *Missouri*

**HAM RADIO CENTER, INC.**  
8342 OLIVE BLVD.  
P. O. BOX 28271  
ST. LOUIS, MO 63132  
800-325-3636  
Call toll free.

**MIDCOM ELECTRONICS, INC.**  
2506 SO. BRENTWOOD BLVD.  
ST. LOUIS, MO 63144  
314-961-9990  
At Midcom you can try before you  
buy!

*Dealers - You should be here too! Contact Ham Radio today for complete details.*

# Amateur Radio Dealer

## New Jersey

**ATKINSON & SMITH, INC.**  
17 LEWIS ST.  
EATONTOWN, NJ 07724  
201-542-2447  
Ham supplies since "55".

## New Mexico

**JIM'S TV AND ELECTRONICS**  
805 N. FIRST  
GRANTS, NM 87020  
505-287-8148  
Stocking Icom. Sales & service open  
6 days.

## New York

**ADIRONDACK RADIO SUPPLY, INC.**  
185 W. MAIN STREET  
AMSTERDAM, NY 12010  
518-842-8350  
Yaesu dealer for the Northeast.

**CFP COMMUNICATIONS**  
211 NORTH MAIN STREET  
HORSEHEADS, NY 14845  
607-739-0187  
Jim Beckett, WA2KTJ, Manager  
Dave Flinn, W2CFP, Owner

**GRAND CENTRAL RADIO**  
124 EAST 44 STREET  
NEW YORK, NY 10017  
212-682-3869  
Drake, Atlas, Ten-Tec, Midland,  
Hy-Gain, Mosley in stock

**HARRISON**  
"HAM HEADQUARTERS, USA"  
ROUTE 110 & SMITH STREET  
FARMINGDALE, L. I., N. Y. 11735  
516-293-7990  
Since 1925 . . . Service, Satisfaction,  
Savings. Try Us!

## Ohio

**UNIVERSAL SERVICE**  
114 N. THIRD STREET  
COLUMBUS, OH 43215  
614-221-2335  
Give U.S. a try when ready to buy.

## Oklahoma

**RADIO STORE, INC.**  
2102 SOUTHWEST 59th ST.  
(AT 59th & S. PENNSYLVANIA)  
OKLAHOMA CITY, OK 73119  
405-682-2929  
New and used equipment —  
parts and supply.

## Oregon

**OREGON HAM SALES**  
409 WEST FIRST AVENUE  
ALBANY, OR 97321  
503-926-4591  
Yaesu dealer for the Northwest.

## Pennsylvania

**ARTCO ELECTRONICS**  
302 WYOMING AVE.  
KINGSTON, PA 18704  
717-288-8585  
The largest variety of crystals  
in N. E. Penn.

**ELECTRONIC EXCHANGE**  
136 N. MAIN STREET  
SOUDERTON, PA 18964  
215-723-1200  
New & Used Amateur Radio  
sales and service.

**"HAM" BUERGER, INC.**  
68 N. YORK ROAD  
WILLOW GROVE, PA 19090  
215-659-5900  
Communications specialists.  
Sales and service.

**HAMTRONICS, INC.**  
4033 BROWNSVILLE ROAD  
TREVOSE, PA 19047  
215-357-1400  
Same location for 25 years.

## Puerto Rico

**COMMUNICATIONS ENGINEERING**  
C-4 DOMENECH STREET  
SIERRA BERDECIA  
GUAYNABO, PR 00923  
Kenwood, Atlas, CDE, Hy-Gain.  
Home operation, 24 hours.

## South Dakota

**BURGHARDT AMATEUR CENTER**  
124 FIRST AVE. N.W. P.O. BOX 73  
WATERTOWN, SD 57201  
605-886-7314  
America's most reliable Amateur  
Radio Dealer — Nationwide!

## Texas

**ALTEC COMMUNICATIONS**  
1800 S. GREEN STREET  
LONGVIEW, TX 75601  
214-757-2831  
Specializing in ham equipment for  
the Ark-La-Tex.

**TECO ELECTRONICS SUPER STORE**  
1717 S. JUPITER ROAD  
GARLAND, TX 75040  
800-527-4642  
Call Toll Free for Service Today!

## Virginia

**ARCADE ELECTRONICS**  
7048 COLUMBIA PIKE  
ANNANDALE, VA 22003  
703-256-4610  
Serving Maryland, D.C., and Virginia  
area since 1962.

## Washington

**AMATEUR RADIO SUPPLY CO.**  
6213 13TH AVE. SO.  
SEATTLE, WA 98108  
206-767-3222  
Amateur center of the  
Northwest.

## Wisconsin

**AMATEUR  
ELECTRONIC SUPPLY, INC.**  
4828 WEST FOND du LAC AVENUE  
MILWAUKEE, WI 53216  
414-442-4200  
Open Mon & Fri 9-9, Tues, Wed,  
Thurs, 9-5:30, Sat, 9-3.

# SPECIAL INTRODUCTORY OFFER

## TECO CODE TRAINING SYSTEM

### SPECIAL TECO NOVICE CLASS PACKAGE \$9.95

A complete course designed for the code beginner. "Learning the Radio Telegraph Code" by the ARRL covers the basics on up to high speed "copy", a 90 minute code introduction tape based on proven training methods, two 1 hour practice tapes of coded groups at 5 WPM & 7 WPM.

### TECO GENERAL CLASS PACKAGE \$9.95

Three one hour practice tapes of coded groups at 10 WPM, 13 WPM, and 15 WPM.

### TECO EXTRA CLASS PACKAGE \$9.95

Three one hour practice tapes of coded groups at 17 WPM, 20 WPM, and 22 WPM.

### TECO HIGH SPEED PACKAGE \$6.95

Two one hour practice tapes of coded groups — 30 minutes each side at 25 WPM, 30 WPM, 35 WPM and 40 WPM.

INDIVIDUAL TAPES DESCRIBED ABOVE..... \$3.95 EACH

### NYE CODE PRACTICE SET \$17.95

Standard transmitting key, oscillator, and amplifier with built-in speaker on a heavy duty aluminum base with non-skid feet. Operates on 9V transistor battery (not included).



\$17.95

### SANKYO CASSETTE RECORDER \$34.95

A high quality cassette player/recorder featuring ALC automatic recording level control, 2 way power supply (115V, 60 Hz AC or 4 "C" size batteries), and built-in condenser mike. Comes complete with AC power cord and earphone (batteries not included).



\$34.95

### ENTIRE TECO CODE TRAINING SYSTEM \$84.95

Includes all tapes, code practice set, and cassette recorder. SAVE \$4.75.

CALL TOLL-FREE 800-527-4642 (IN TEXAS CALL 214-348-1560).

WE ACCEPT BANKAMERICARD, MASTER CHARGE, AND AMERICAN EXPRESS.

WRITE IN TODAY FOR YOUR FREE COPY OF THE 1976 TECO HAM CATALOG.



## SW-5 — \$87.50



The SW-5 is a remote controlled RF switch with indicator lights telling which antenna is in use. It will handle 4 kW PEP and more. Remote switch is housed in weather tight hinged box. A six wire #18 cable is required to operate the SW-5. Ham M control cable works fine up to 150'. Heavier cable necessary for longer distances. Remote switch operates off 28 VDC built in power supply. No visible effects on SWR. Zero dB insertion loss. Not recommended above 30 MHz. Standard unit is equipped with UHF connectors but BNC, N, HN, C connectors are available at additional charge. Models available are SW3, 4, 5, 6, 7, 8, 9. Also heavy duty 10kW units. Special switching systems are available. Tell us your needs.

## ANTENNA MART

Box 1010 ISU Station

Ames, IA 50010

Phone: 515-292-7114

# TECO

## ELECTRONICS SUPERSTORE

P.O. Box 1050 Garland, Texas 75040

### STOP MOBILE RIP-OFFS

ORDER YOURS TODAY or write for further info.

Plus \$1.00 Shipping & Handling

\$14.95

### PRUITT ENTERPRISES

Box 41HB, Tonopah, NV 89049

702-482-3473

**WOW!** Look for Madison Electronic's SUPER BUYS in this issue!

### 125 Hz Crystal Filter for Drake R-4C

Cuts QRM. Ideal for DX and Contest Work

Does what no audio filter can do

A must for CW operators who want the best 125 Hz @ -6 db, 325 Hz @ -60 db, 8 poles

Sherwood Engineering Inc. CF-125/8 \$125

Department A Return in 10 days

1268 South Ogden Street for full refund

Denver, Colorado 80210 if not satisfied.

(303) 722-2257 Master Charge, BankAmericard

# NEW! ATRONICS Visual Code Reader Kit \$149



Model KCR101

ReadyMade Model CR101 \$225

USE YOUR BANKAMERICARD

Now you can have the famous Atronic Code Reader, that displays decoded Morse Code signals visually, in kit form. Assembly is simple, and can be completed in as little as 5 hours. Complete, step by step, illustrated instructions are included.

The Atronic Code Reader:

- Displays letters, numbers, and commonly used punctuation visually as Morse Code signal is received.
- Operating speed 5 to 50 WPM at selected speed.
- All Solid State

- Make code learning faster and easier
- One single connection to your speaker receiver or transceiver puts it into operation
- Hard copy read out of CW available with TU-102 TTY Interface Module accessory.

Buy Factory Direct & Save! Send for Free Literature Today.

**ATRONICS** P.O. Box 77, Escondido, CA 92025 Call (714) 745-1971

### DIPLOLE ANTENNA CONNECTOR

**HYE-QUE (HQ-1)** dipole connector has coax SO-239 socket molded into glass filled plastic body to accept coax PL-259 plug on feedline. Drip-cap keeps coax fittings dry. Instructions included! Guaranteed. At your dealers, or \$3.95, postpaid. Companion insulators 2/\$.99.

**BUDWIG MFG. Co.** PO Box 97H, Ramona, CA 92065

## QUALITY USED TEST EQUIPMENT TEKTRONIX

Oscilloscopes

Plug-ins

Signal generators

Probes

HEWLETT PACKARD

Meters

Probes

For a catalog, write: P T I


Div. 16, P.O. Box 8699,

White Bear Lake, Mn, 55110

# TYCOL COMMUNICATIONS features KLM, LARSEN & ARCOS

products for "Your" specialized amateur equipment needs

**NEW**

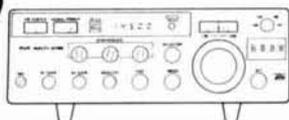

**KLM MULTI 2700**

The one 2M rig with everything fully synthesized plus full VFO FM/SSB/CW/AM - 10W Power Out. \*PLUS - a self contained 29.5MHz receiver for Oscar 6/7A. \$795 Available late August

**KLM ANTENNAS**  
7.0-7.3 - 4 el \$495  
14.0-14.5 - 5 el \$249  
21.0-21.6 - 6 el \$225  
6M/2M/220 MHz & 432 MHz beams for all applications

**ARCOS**  
432 MHz Transverters  
432 MHz KW Amplifiers

**KLM VHF/UHF AMPLIFIERS**  
Complete line of Class C & linears to 160W output

**LARSEN**  
Complete line of mobile VHF/UHF antennas

— NEW —



**KLM ECHO 70 CM**

The only 432 MHz SSB/CW synthesized transceiver on the market. \*Excellent for OSCAR 7/Mode B \$495 in stock

WE OFFER EXCELLENT HEATHKIT (AND OTHER) BUILDING/TESTING SERVICES

**TYCOL COMMUNICATIONS**

301-831-7086

WRITE OR CALL FOR CATALOGS & INFORMATION

ROUTE 3 - MT. AIRY, MD. 21771

JACK COLSON, W3TMZ, OWNER




## CW Sendin' Machine

IAMBIC MEMORY KEYSER WITH DOT AND DASH MEMORIES STORES UP TO EIGHT DIFFERENT MESSAGES IN 2048 BITS OF MEMORY.

**\$137.00** Prepaid Shipping USA

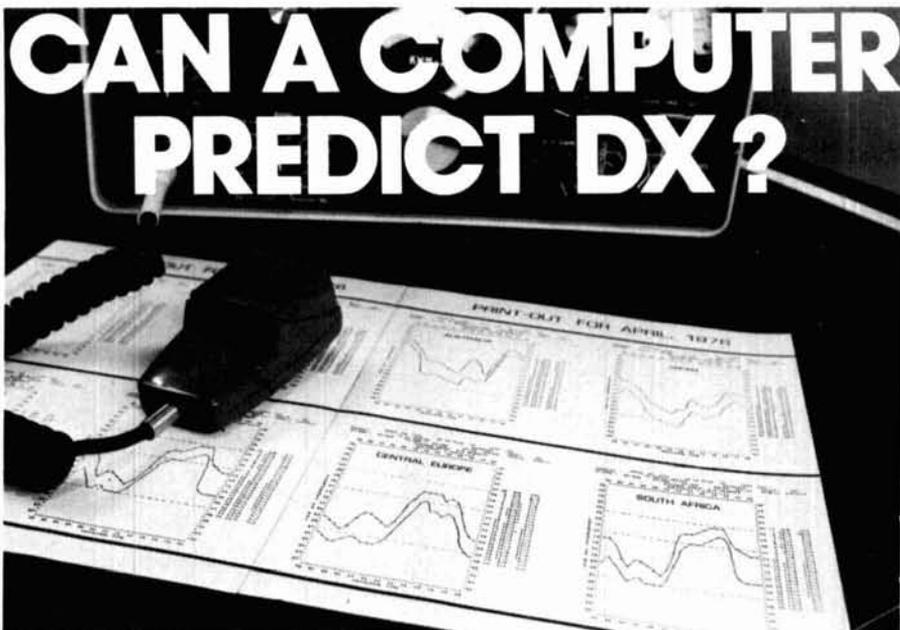H. ALAN HARP WA4SVH  
718 MAGNOLIA DR.  
LAKE PARK, FLA. 33403



### Yes indeed!

It's been doing it for years. Trouble is, only big corporations and government communicators could afford it. Not anymore.


May we introduce you to Compu/Prop . . . computerized DX predictions.

Now you can have computer print-outs of precise times of band openings to your favorite parts of the world. Plan your operating for maximum DX. Know what hours of the day that "rare one" will come thru. These are just a few ways Compu/Prop can increase your enjoyment of ham radio.

Compu/Prop is a monthly computer print-out to 8 major DX areas of the world. And it's 90% accurate. The computer program was originally developed over many years by the government Office of Telecommunications. This multi-million dollar data base is now available to you via Compu/Prop.

Main Electronics is making these monthly computer predictions available on a special introductory offer.

## GOT A MATCH?

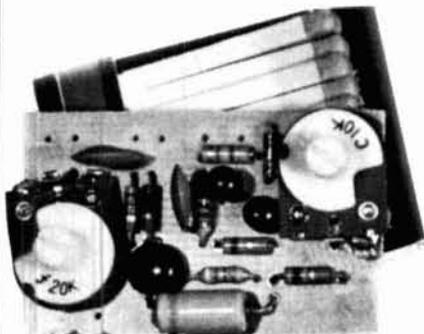

OUR TOUCH TONE INTERFACE WILL MATCH ALMOST ANY TOUCH TONE PAD TO YOUR RIG AND IT'S NO LARGER THAN A PACK OF MATCHES.

### — CHECK THE FEATURES —

- IT KEYS TRANSMITTER EACH TIME A TONE BUTTON IS DEPRESSED.
- CAN HOLD TRANSMITTER KEYS — ADJUSTABLE TO SEVERAL SECONDS TO ALLOW FOR A LONG SERIES OF TONES.
- PROVIDES ADJUSTMENT OF PAD OUTPUT LEVEL.
- SUPPLIES VOLTAGE TO POWER PAD.
- ONLY ONE SHIELDED CONDUCTOR NEEDED BETWEEN PAD AND RIG.
- NOT A KIT — SIMPLE 4 WIRE INSTALLATION.

ALL THIS FOR ONLY

**\$7.95** PLUS 45¢ POST & HAND N.Y. res add 7% tax.

TREVOR INDUSTRIES, INC.

P.O. BOX 102  
GETZVILLE, N.Y. 14068



You can receive a FREE print-out to any one of eight DX areas of the world by simply filling out and mailing the coupon below. You will also receive full details on how to obtain a subscription to Compu/Prop.

**Start planning your DX NOW!**



**ELECTRONICS, INC. / EDC Division / 225 Ida / Wichita, Ks. 67211**

Yes, I would like a FREE print-out for my area to the point checked below. (check only ONE)

- Japan  Central Europe  S.E. Asia  S. Central Asia  
 Central S. America  Australia  Mideast  S. Africa

NAME \_\_\_\_\_ CALL \_\_\_\_\_

STREET \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

## 5 KW PEP INPUT

WITH THIS NEW BALUN



on all bands 160 to 10 meters. Runs cool as a cucumber at its CCS rating of 2 KW (Continuous output power through the balun at matched load). 4" dia. Wt. 24 oz. \$32.50 PPD.

### AND FOR FULL LEGAL POWER

the time tested Model 1K balun is still available. Rated at 1 KW CCS (3 KW PEP input). 2 1/4" dia. Wt. 9 oz. \$16.95 PPD.

### ONLY PALOMAR BALUNS HAVE ALL THESE FEATURES

- Toroidal core for highest efficiency.
- Teflon insulated wire to prevent arc-over. OK for tuned feeders.
- Stainless steel eyebolts take antenna tension. Won't rust, won't pull apart.
- Epoxy filled case. Absolutely waterproof.
- Lightning protection built-in.
- Wideband 1.7 to 30 MHz.
- Hang-up hook provided.
- Now available in either 1:1 or 4:1 ratio. 1:1 ratio matches 50 or 75 ohm coax to 50 or 75 ohm balanced load (dipoles and inverted Vees). 4:1 ratio matches 50 or 75 ohm coax to 200 to 300 ohm balanced load.


Free descriptive brochure on request. Order direct.

Model 2K \$32.50    Model 1K \$16.95  
Center insulator without balun \$7.95  
Postpaid U.S. & Canada.  
Specify ratio 1:1 or 4:1  
California residents add 6% tax.  
Send check or money order to:

**PALOMAR ENGINEERS**  
BOX 455, ESCONDIDO, CA 92025  
Phone: (714) 747-3343
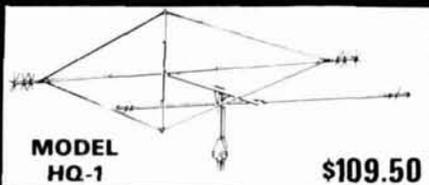
## WANT SOMETHING REALLY SMALL AND EFFICIENT?

Then you want the antenna that's known around the world for its small size and superior performance...  
The Mini-Products Multiband HYBRID QUAD



MODEL HQ-1

\$109.50

- ELEMENT LENGTH - 11 ft.
- BOOM LENGTH - 54 INCHES
- WEIGHT - 15 POUNDS
- WIND SURVIVAL - 75 MPH
- BANDS COVERED - 6, 10, 15 & 20
- 1200 WATTS P.E.P.
- FEED LINE - 50 OHMS

**Mini-Products, Inc.**

1001 W. 18th St. Erie, Pa. 16502

## HW-202 OWNERS

NOW HEAR MORE OF WHAT IS HAPPENING. ADD A SCANNER TO YOUR HW-202.

- SIX L.E.D.'s VISIBLE FROM FRONT WITH NO HOLES TO DRILL.
- EASY TO INSTALL - ONLY 9 COLOR-CODED WIRES TO CONNECT. PLUS GRND.
- NO WIRES TO CUT.
- AUTOMATICALLY STOPS SCANNING EITHER WHEN SIGNAL IS RECEIVED, OR YOU MAKE PUSH-BUTTON SELECTION.
- DOESN'T INTERFERE WITH NORMAL OPERATION.
- COMPLETELY ASSEMBLED, TESTED AND GUARANTEED.

ONLY \$24.95 PLUS \$1.00 SHIPPING

Georgia Residents add 3% Sales Tax.  
Designed by WB4QDB/Larry Sandlin

**SANDLIN ELECTRONICS ENGINEERING**

P. O. BOX 4909  
MARTINEZ, GEORGIA 30907  
TELEPHONE (404) 863-5852

## MILITARY SURPLUS WANTED

Space buys more and pays more. Highest prices ever on U.S. Military surplus, especially on Collins equipment or parts. We pay freight. Call collect now for our high offer. 201 440-8787.

**SPACE ELECTRONICS CO.**  
div. of Military Electronics Corp.  
35 Ruta Court, S. Hackensack, N.J. 07606

### CASH FOR 2-WAY FM RADIO MOTOROLA, GE, RCA, ETC. EQUIPMENT

MOBILES, BASES, PORTABLES, MOBILE-TELEPHONES, REPEATERS, REMOTE CONTROLS, TONE EQUIPMENT, 2-WAY TEST EQUIPMENT  
Operational Units Only  
Commissions/Finders Fees  
**CAL-COM SYSTEMS, INC.**  
701-51A KINGS ROW, SAN JOSE, CALIF. 95112  
Telephone 24 Hours 408/998-4444

**MODSET:** precision modulation measurements for AM-SSB, 0.2 to 300 MHz, \$29.50 (Kit: \$19.50)

**D. R. CORBIN MFG. CO.**

P. O. Box 44, North Bend, Ore. 97459

DE-120 Speech Compressor provides over 10db of compression \$59.95

12 VDC CW & SSB filters with AF power amplifiers.  
DE-102B SSB filter \$39.95  
DE-103B CW & SSB \$48.95  
DE-104B CW filter \$37.95  
Add \$2 shipping.

Dealer Inquiries  
DYNAMIC ELECTRONICS, Box 896, Hartselle, AL 35640

## FERRROMAGNETIC PRODUCTS



FAST SERVICE SINCE 1963



AMIDON Associates • 12033 OTSEGO STREET • NORTH HOLLYWOOD, CALIF. 91607

# start 'em right!

Here are just the products you need to get your novice training classes off to a fast start.



## special ham radio beginner's training packages

HERE ARE TWO BRAND NEW COMPLETE TRAINING PROGRAMS, EACH OF WHICH PROVIDES EVERYTHING THAT IS NEEDED TO PREPARE FOR THE NOVICE LICENSE.

**THE STANDARD PACKAGE** consists of MFJ's exciting new CPO-555 Code Practice Oscillator with every feature you could want including self-contained speaker, volume and tone controls, handsome aluminum case, quality U.S. construction and including the necessary built-in battery. You also receive a telegraph key to go along with your CPO-555 plus ARRL's fabulous new "Tune in The World with Ham Radio" described below. Not only do you get all this, you also save \$4.00 off of the regular total list price of these items.



### HAM RADIO STANDARD BEGINNER'S TRAINING PACKAGE

MFJ CPO-555 Code Practice Oscillator	\$15.95
Battery	1.00
Telegraph Key	1.95
ARRL "Tune in the World with Ham Radio"	7.00

Total List \$25.90

**Save \$4.00!** YOUR PRICE **\$21.90**

Order HR-BTP

Write for Special Quantity Prices!

**OUR DELUXE PACKAGE** is even more outstanding! In addition to the standard package you also are given Ameco's outstanding Radio Amateur Theory Course, the best known book of its type in print today, the Ameco Radio Amateur Q & A guide, the finest way to check your progress plus Ham Radio's own Novice Radio Guide, a complete introduction and how to do it book for the prospective Novice. A super package and a super deal as you save \$7.00 over the total individual list prices.



### HAM RADIO DELUXE BEGINNER'S TRAINING PACKAGE

MFJ CPO-555 Code Practice Oscillator	\$15.95
Battery	1.00
Telegraph Key	1.95
ARRL "Tune in the World with Ham Radio"	7.00
Ameco Radio Amateur Theory Course	4.95
Ameco Radio Amateur Q & A Guide	1.00
Ham Radio "Novice Radio Guide"	3.95

Total List \$35.85

**Save \$7.00!** YOUR PRICE **\$28.85**

Order HR-DBTP

# also:

### TUNE IN THE WORLD WITH HAM RADIO by ARRL Staff

Your open door to the fascinating world of amateur radio. This nifty new package tells you what Amateur Radio is, and then assuming no prior knowledge of radio the reader is taught how to pass his Novice License exam and how to set up his first station. An extremely useful U.S. call area map is included. In addition there is a cassette tape narrated by TV and radio star Jean Shepherd, W2ORC, which provides the necessary instruction in the Morse Code. All in all it is just what we have been looking for — a perfect and complete introduction to our fascinating hobby.

Order AR-HR

Just \$7.00

### NOVICE RADIO GUIDE by Jim Ashe, W1E2T

A complete handbook for the beginning amateur. Covers basic communications theory. How to build transmitters and simple receiving equipment. How to set up antennas. Putting your station together, plus valuable appendices. How to learn the code and more. Any beginner will go further faster and have more fun with this exciting book.

Order HR-NR

144 pages, \$3.95



Remember Ham Radio has more training manuals than anyone and the best quantity prices around.

ham radio Greenville, NH 03248

Call Toll Free 800-258-5353

# Dependability THAT'S WHAT YOU GET FROM SENTRY CRYSTALS.

Because Sentry communication crystals are the most stable, reliable crystals available. Anywhere. At any price.

Sentry crystals are made to the latest state-of-the-art specifications from the finest quartz. And they're gold-plated for long-term reliability.

Since Sentry has the largest semi-processed crystal bank in the world, we can custom-make crystals for any rig. Any frequency. Faster than anyone else in the business.

We process our orders quickly and efficiently, too. And we stand behind our work. With solid guarantees.

Maybe that's why people who count on communications count on Sentry.

Send for our complete 1976 catalog. It's just \$1.50, deductible from your first order. It may be one of the best communications investments you'll ever make.

Sentry Manufacturing Company  
Tuned-In to Quality  
Crystal Park, Chickasha, Oklahoma 73018

## Sentry



Phone: 405/224-6780  
TWX 910-830-6425

Sentry Mfg. Co.  
Crystal Park  
Chickasha, Okla. 73018

Please send me the complete 1976 Sentry Catalog immediately. Enclosed is a check or money order for \$1.50.

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

## YOUR BEST BUY IN KITS



### ANALOG-DIGI-LAB

Features 3 Regulated power Supplies. 3 Output wave forms. 8 digital level switches. 2 no bounce pulser switches.

8 LEDs with drivers. 1 AP Super strip. Easily constructed. Designed by RETS Electronic Schools.  
1st time offer ..... \$139.00

Clock Kit (complete less case) ..... \$12.95  
Function Generator Kit ..... \$10.95

Please add \$1.00 Shipping/Handling on any order under \$15.00  
Send SASE for flyer. Featuring Electronic components and kits available.

## HAL-TRONIX

P. O. Box 1101 • Southgate, Mich. 48195  
(313) 285-1782




### FREQUENCY COUNTER

7 Digit 0-300 MHz Freq. counter ..... \$99.00  
7 Digit 0-500 MHz Freq. Counter ..... \$139.00  
8 Digit 0-30 MHz Counter with Options ..... \$99.00  
0-300 MHz Prescaler ..... \$19.95  
for 8 Digit Counter ..... \$19.95  
Cabinet accessory package available for all of the above ..... \$24.95  
Digital Alarm Clock complete with case ..... \$24.95
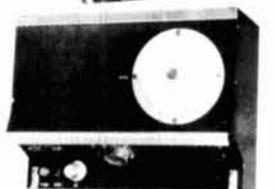
## WANTED FOR CASH



618-T TRANSCEIVER (also known as MRC95, ARC94, ARC102, or VC102)  
490-T AIRT. TUNING UNIT (Also known as CU1658 and CU1669)  
Highest price paid for these units. Parts purchased. Phone Fed. WZKLUW collect. We will trade for new amateur gear. GRC106 and PRC74 also required.



## THE TED DAMES CO.

308 Hickory Street ..... Arlington, N. J. 07032  
(201) 998-4246 ..... Evening (201) 998-6475

## SPECIAL IC PRICES

		MM SERIES	
7401	.10		
7406	.35	1101	1.75
7410	.10	2501	3.75
7430	.15	5230	3.95
7439	.35	5260	3.45
7442	.85	5261	4.95
7445	.80	5262	4.45
7460	.15	5725	3.10
7472	.35	5738	3.45
7474	.35	LM	
7475	.70	301H	.20
74123	.85	307N	.20
74141	.95	308H	.75
74145	.95	311H	.70
74153	1.25	371H	1.05
74161	1.40	376N	.35
74162	1.30	741H/CN	.20
74173	1.55	3067CN	1.40
74189	2.50	5741N	.20
74192	1.10	752B	1.45
74193	1.10	8223	2.50

1. Add 50¢ for postage & handling on orders under \$10. 2. All items guaranteed. 3. Send SASE for Bargain Flyer. 4. SEND YOUR ORDER ALONG WITH CHECK OR MONEY ORDER TO: WEIRNU, P. O. Box 942, Cotton, CA 92324 (Calif. residents include 6% tax).

## REPROGRAMMABLE MEMORY KEYS



ONLY \$169.95

The MK-1 Memory Keyer features a reprogrammable 1024 bit MOS memory for storing up to 80 characters. Automatic stop allows manual insertion between messages stacked in memory. Messages can be interrupted and continued. Perfect character and word spacing. Iambic keyer with dot and dash memories. 120 VAC and 12 VDC operation.

Write for more information

Add \$1.50 for postage, Wis. res. add 4% sales tax  
**DGM ELECTRONICS**  
787 BRIAR LANE, BELOIT, WIS. 53511

## WHAT AN OPPORTUNITY!

Radio Communication is certainly one of the finest foreign Amateur Radio magazines.

This monthly magazine covers the whole Amateur Radio scene in Great Britain offering both a wide range of technical information and a description of many activities both on and off the air.

Of particular interest is the monthly column **Technical Topics** by Pat Hawker, G3VA. Here is a great rundown on new technical ideas from around the world. It touches on virtually all phases of Amateur Radio and is sure to have just the hint you need.

To: **Radio Communication**  
Greenville, NH 03048

Enclosed is \$14.00. Please sign me up for a one year subscription.

Name \_\_\_\_\_ Call \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Allow 60-90 days to begin receiving issues

## VHF/UHF CONVERTERS PREAMPS


Ten meters through 432 MHz. A post card will bring our full 1976 Catalog.



**JANEL laboratories**

3312 S.E. VAN BUREN BLVD.  
CORVALLIS, OREGON 97330  
Telephone: 503-757-1134

## SST T-1 RANDOM WIRE ANTENNA TUNER

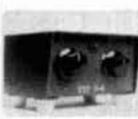

All band operation (160-10 meters) with most any random length wire. 200 watt power capability. Ideal for portable or home operation. A must for Field Day. Size: 2 x 4 1/2 x 2 3/8. Built-in neon tune-up indicator. Guaranteed for 90 days. Compact - easy to use - only \$29.95 postpaid. (Add Sales Tax in Calif.)

SST ELECTRONICS, P.O. BOX 1, LAWDALE, CA. 90260

## NEW MULTI-BAND ANTENNA




Guaranteed. Pat. Pend.  
60 to 6 Meters plus 1601.5 SWL Bands.  
Built-in balun. 1 KW ICAS rating.  
60 to 120 ft inverted-V or horizontal.  
Available in kit form or assembled.  
Kit 80K \$54.95 cash PPD in USA,  
Kit 80K+BF with 100 ft R/U foam cable  
and two PL259 \$82.95 cash PPD in USA.

Universal Radio Co. Dept H  
Box 26041 El Paso, TX 79926  
Telephone (915) 592-1910  
Texas residents add 5% sales tax.  
Order direct. Master Charge accepted.  
Send stamped envelope for information.

# HT-220
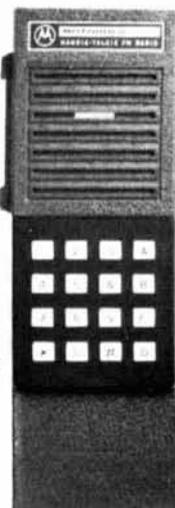
## TONE ENCODER FRONT

- Fully assembled and tested tone encoder front, just add your mike, speaker, & harness
- No standby power drain
- Crystal controlled tones
- No additional wiring to your radio
- Precision "calculator like" keypad
- Keypad & front are a welded assembly
- Fits unmodified charger sleeve



Model PLO-220 \$74.50 CAL. RES. ADD 6% TAX  
PL length & OMNI depth

WRITE FOR INFO ON:  
Silvered fronts, Slimline fronts,  
complete fronts, & other products

### BK PRODUCTS

P.O. Box 391  
Harbor City, Ca. 90710

## SUB-AUDIBLE GENERATOR for FM

THE CUBE



.5 x .6 x .8 in.

- Inexpensive multi tone system
- Compatible with PL-CG-QC
- Low distortion sine-wave
- Adjustable frequency (98-250 Hz), Lower available
- Rugged, plastic encased with leads, easy to mount
- Input 8-18 VDC unregulated
- Excellent stability

Lyle Products  
P.O. Box 2083  
Santa Clara Calif.  
95051

Price \$19.95

Calif. res. add 6%

Freq. set at factory \$5.00 extra

Send for more information

## WORLD RECORD 6-BAND ANTENNA

won W6TYP QRP ARC  
1,000,000 miles/watt award.

### THE JOYSTICK VFA

160 thru 10 plus BC & SW  
TRANSMIT-RECEIVE

Only 7' 6" long, with ATU, easily assembled. Air Mail from UK manuf., take advantage of exch. rates and save!

SYSTEM 'A' \$69.90  
250 w. p.e.p.

SYSTEM 'J' \$91.33

500 w. p.e.p. (improved Q on receive)

SEND MASTER CHARGE NUMBER OR  
CHECK OR ASK FOR BROCHURE

Partridge (HR) Electronics Ltd.

Broadstairs, Kent, England

G3CED Phone Thanet 62535 G3VFA

# the BRIMSTONE 144



## 2 METER FM TRANSCEIVER



Size 9 1/2" x 10 1/2" x 3 1/4"

- ★ 143 to 149.99 MHz in digitally dialed 5 KHZ steps without buying a single crystal! 142 MHz coverage optional.
  - ★ 25 Watts RF output
  - ★ 25 uV, 12 Db. SINAD sensitivity
  - ★ Completely independent transmit/Receive frequency control, yet simplex with the flip of a single switch.
- Includes dynamic microphone and mobile mounting bracket

AMATEUR NET  
\$650.00

- ★ TWO YEAR WARRANTY!
- ★ Very low transmitter spurious output
- ★ Beryllium copper printed circuit card guides provide SOLID retention of plug in modules, as well as excellent ground connection to the modules.

All of this plus optional plug in modules for Tone Burst, Dial Tone, Sub-Audible Tone, and a Touch Tone® interface module.

Send for our six page COLOR brochure which gives you the full story, inside and out!

Touch Tone® — trademark of the Western Electric Co.

## NEW PRODUCTS!



- ★ REPEATER AUTOPATCH AND CONTROL  
3 digit access, single digit disconnect.  
3 digit repeater ON-OFF control.  
AGC with 30 Db dynamic range on all inputs and outputs! Just connect repeater Rcvr, TX, Ider, Touch-Tone line and power.  
Size 9 1/8" x 4 1/8" \$199.95 Assembled



- ★ REPEATER AND RTTY CW IDENTIFIER  
254 bit capacity allows you to send your call plus other desirable information.  
Easily programmed.  
Size 6" x 4 1/8" \$62.50 Assembled



SATAN ELECTRONICS, INC.

BLDG. 317 - AIRPORT INDUSTRIAL AREA  
SALINA, KANSAS 67401  
913/823-2235



- ★ 650 MHz PRESCALER KIT  
Why pay \$75.00 to \$100.00 or more for a 250 MHz prescaler when you can get one that goes all the way to 650 MHz for just  
Size 1" x 1 1/8" 12V or 5VDC \$47.50



- ★ TOUCH-TONE KEY BOARD  
Positive snap-action push-button switches!  
No need to worry about long finger nails.  
No more mis-dialing because of intermittent switch contacts.  
Standard touch-tone format.  
Size 2 1/8" x 2" x 3/16" \$14.40

- ★ COMING SOON . . . the P.A.D. The PROGRAMMABLE AUTOMATIC DIALER. Send for more information.

## COMPETITIVELY PRICED!

ALL PRODUCTS FULLY ASSEMBLED, TESTED AND WARRANTED.  
PRICES INCLUDE ALL POSTAGE FEES WITHIN THE USA.  
FOREIGN ORDERS, ADD \$3.00 TO COVER POSTAGE & HANDLING.

Arizona Residents  
Add 5% Sales Tax



\$49.95  
EPC-300  
300 MHz Prescaler

- o Built-in 117 vac 60 HZ power supply
- o Size 3 1/4" w x 2 1/4" h x 4" L
- o BNC input, output connectors
- o Input impedance = 50 ohms
- o Output TTL, Fan out of 1
- o Sensitivity 14 mv @ 150 MHz, 150 mv @ 300 MHz

JULY & AUGUST SPECIAL  
Save \$5.00  
Order the LA-144  
and EPC-144 together  
Pay Only \$67.90

Send Self-Addressed Stamped  
Envelope For More Information



\$32.95  
EPC-144-B  
2 Meter FM Transmitter

- o 2 Channels, 144-148 MHz
- o Power Output 2 watts typical, 1 watt min @ 12.5 VDC
- o 50 ohm output impedance
- o Narrow band FM ± 5 KHZ
- o Rugged balanced emitter output transistor
- o Small size 1 7/8" w x 1" h x 3 1/2" L



\$39.95  
LA-144  
30 Watt 2 Meter Power Amplifier

- o Frequency range 144-148 MHz
- o Maximum RF output power 30 watts
- o Maximum RF input power 5 watts
- o Supply voltage 13.6 VDC
- o Small size 1 7/8" w x 5/8" h x 3 1/2" L
- o Virtually burn-out proof balanced emitter output transistor.
- o Fully compatible with the EPC-144-B
- o 50 ohm input & output impedance
- o Sold as a fully tested & assembled circuit board less case, connectors and heat sink

Input Watts	Output Watts Min.	Typical
1	15	20
2	20	25
4	30	30

Elprocon  
ELECTRONIC PROTOTYPE CONSULTANTS  
1907 W. Campbell / Phoenix, Arizona 85015

## PALMER INDUSTRIES

INTRODUCES

THE  
NEW  
MODEL

# 52' TRISTAO SUPER MINI-MAST

Featuring an exclusive three-section, crank-up, self-supporting 52' mast with automatic brake winch. Constructed of high-strength steel tubing, designed to handle 9 to 10 sq. ft. of antenna and withstand winds of 50 to 60 MPH.

Only TRISTAO'S Mini-Mast features as an exclusive option, a rotor base assembly allowing rotor to be mounted at ground level for easy maintenance.

We offer a complete assortment of accessory bases and raising fixtures for the Mini-Mast.

**NORMALLY STOCKED  
FOR IMMEDIATE  
SHIPMENT**

40' MODEL ALSO IN STOCK

Call or write for FREE catalog covering all the other fine Tristao towers and masts.

**TRISTAO TOWER  
DIVISION**

PALMER INDUSTRIES, INC. Dept. HR  
3900 San Fernando Road Glendale, Calif. 91204  
(213) 246-8333

## LOWEST PRICES

WE OFFER THE IDENTICAL PRODUCT AS THE OTHER HOUSE AT ABOUT ONE HALF THE COST




Iron Powder Toroidal Cores		Ferrite Toroidal Cores	
Size	Price	Size	Price
T-200-2	\$1.60	FT-50-61	.35
T-80-3	.40	FT-82-61	.40
T-80-2	.40	<b>Ferrite Shielding Beads</b>	
T-68-2	.35	Size	Price
T-68-6	.35	FB-73-101	\$1.00 Doz.
T-50-2	.30	FB-43-101	1.00 Doz.
T-50-6	.30	FB-73-801	1.50 Doz.
T-37-2	.25	FB-43-801	1.50 Doz.
T-37-6	.25		

**G.R. WHITEHOUSE & CO.**  
10 Newbury Drive, Amherst, N. H. 03031

Packing & shipping in U.S.A. — 50¢.  
SEND FIRST CLASS STAMP FOR PARTS FLYER.

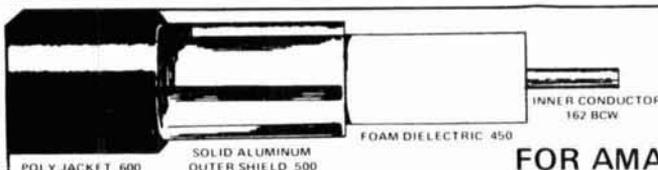Other sizes and mixes available at comparable savings.



**NEW**

order now  
and save

**FOR AMATEUR USE  
50 OHM JACKETED HARDLINE**

Call us...

We are ready to serve you...

**WIRE CONCEPTS INC.**

WIRE CONCEPTS INC.

**WC**

"The Wire People"


**201-227-1751**

198 Passaic Ave.,  
Fairfield, N.J. 07006

- very low loss per 100 ft.
- improved receiver sensitivity
  - .45 DB to 50 MHZ
  - .90 DB to 146 MHZ
  - 1.90 DB to 450 MHZ
  - 4.20 DB to 1296 MHZ
- longer life

**SALE 49¢ per foot**

### WANTED FOR CASH

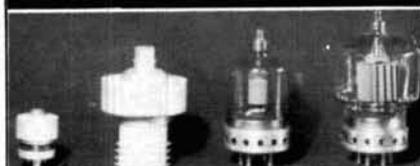

4CX150 4CX1000 4-65 4-250  
4CX250 4CX1500 4-125A 4-400  
4CX300A 4CX3000 4-1000  
4CX350A 4CX5000 304TL  
4CX10,000  
5CX1500

Other tubes and Klystrons also wanted.

**The Ted Dames Company**

308 Hickory St. Arlington, N.J. 07032  
(201) 998-4246 Evenings (201) 998-6475

### Shortwave Listening


1976 World Radio TV Handbook - \$10.95  
Gated 1000/100/50/25/10 kHz Calibrator - \$54.00  
Barlow Wadley & R.L. Drake Receivers  
1976 "Confidential" Frequency List - \$5.45  
**GILFER, Box 239, Park Ridge, NJ 07656**

**OM, WANT A SUPER BUY?  
MADISON ELECTRONICS  
has 'em in this issue!**
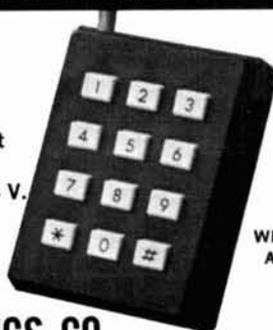
## TONE ENCODER PAD

MODEL TTP-03

- A Better Keyboard
- Output Level Set Pot
- Crystal Controlled-Digitally Synthesized Tones
- Strapping for Hi-Low Z Output
- Internal 5 V. Regulator  
Supply Voltage Range 7 to 24 V.
- RFI Suppression
- Velcro and Case Included
- Size 2.80 - 2.00 - 0.60 Inches



**\$54.95**

POSTPAID  
IN U.S.A.

TEXAS RESIDENTS  
ADD 5% SALES TAX

CHECK OR M.O.  
WRITE FOR BROCHURE ON  
AUTOMATIC UNIT ATD-30

**CLENG ELECTRONICS CO.**

BOX 12171 — DALLAS, TEXAS 75225

# SWAN METERS HELP YOU GET IT ALL ON

Keep things in tune for a song.

Our SWR-3 SWR meter and FS-1 field strength meter help you make sure you've got it all on

the air and going in the right direction. Both are pocket sized with easy-on-the-pocket prices. Use your Swan credit card. Applications at your dealer or write to us.



**SWR-3 SWR Meter.** Why bother with big, bulky meters when this one does the job just as well? Measures 1:1 to 3:1 SWR from 1.7 MHz to 55 MHz with all the accuracy you need. . . . . \$10.95

(Prices FOB Oceanside, CA)

**FS-1 Field Strength Meter.** Get field strength readings just about anywhere with this fit-anywhere meter. Telescoping antenna, level adjust knob, 1.5 MHz to 200 MHz, 0-10 relative scale meter. . . . . \$9.95

**SWAN ELECTRONICS**  
A subsidiary of Cubic Corporation  
305 Airport Road, Oceanside, CA 92054  
(714) 757-7525

**NEW from NRI**

## Home training in AMATEUR RADIO

NRI, leader in Communications, Television, Electronics and TV-Radio home training, now offers the first in Amateur Radio courses, designed to prepare you for the FCC Amateur License you want or need.

### Don't lose your favorite frequency

The FCC has said "either-or" on licensing, but to pass Advanced and Extra Class exams, you need the technical guidance as offered by NRI. NRI Advanced Amateur Radio is for the ham who already has a General, Conditional or Tech Class ticket. Basic Amateur Radio is for the beginner and includes transmitter, 3-band receiver, code practice equipment. Three training plans offered. Get all the facts. Mail coupon. No obligation. No salesman will call on you. NATIONAL RADIO INSTITUTE, Washington, D.C. 20016.



## 2 IN 1 FREQUENCY COUNTER DIGITAL MULTIMETER \$179.95 KIT



150 MHz Frequency Counter Only \$139.95 Kit

### FREQUENCY COUNTER —

6 Digit .33 inch 7 seg. LED Latched Display (Can be expanded to 8 digit) Crystal Oscillator Timebase .001% ± 1 count. Readout MHZ or KHZ to over 40 MHZ.

### MULTIMETER —

11 Megohm Input Impedance. 100% Overrange except 1 amp range. AC-DCV 0-1,000, 10,00, 100,0, 1000. AC-DCMA 0-1,000, 10,00, 100,0, 1000. OHMS 0-100, 0-10K, 0-1Megohm. Input protection, auto polarity, overrange and negative sign indication.

Add \$3.00 Shipping/Handling Allow 5 Weeks for delivery



### FOR THE EXPERIMENTER ASSEMBLED — TESTED MODULES

1. Crystal Timebase, 1MHZ with six divide by 10 Outputs 1HZ to 1MHZ (size 3" x 5") \$21.95
2. Freq. Counter Gate Module includes 80 MHZ ÷ 10 Schottky (Size 3" x 5") \$16.95
3. Four digit 7 seg. .33 inch LED Latched Display (Size 4" x 5" x 2 1/4" high) \$34.95 (Above Require 5 VDC)
4. Function Generator Module Sine, Saw, and Squarewave Outputs 1HZ - 100KHZ to 10 Volt output. Requires Switches & Pots. \$19.95
5. Function Generator Kit Includes assembled/tested module, Switches, Case, Hardware, (Requires two 9 Volt Batteries.) \$39.95

Add \$1.00 Shipping Any Above Allow 3 Week Delivery



### NEW

AT A PRICE THE HOBBYIST CAN AFFORD

KIT \$69.95

### DIGITAL CAPACITANCE COUNTER

4 Digit LED Display Ranges to 1000 MFD.

± 0.5% (± 1 PFD Below 100 PFD)

Add \$2.00 Shipping/Handling Allow 4 Weeks Delivery

California Residents add 6% Sales Tax Send Check or Money Order to  
**LIN CORPORATION**  
15311 S. Broadway Gardena, Ca. 90248  
(213) 532-8809

**MAIL NOW**

NATIONAL RADIO INSTITUTE 46-016  
Washington, D.C. 20016  
Please send me information on Amateur Radio training.

Name \_\_\_\_\_ Age \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

ACCREDITED MEMBER NATIONAL HOME STUDY COUNCIL

# Advertisers check-off

... for literature, in a hurry — we'll rush your name to the companies whose names you "check-off"

Place your check mark in the space between name and number. Ex: Ham Radio  234

## INDEX

A. F. S. S. 462	Kenwood 341
Adva 265	King 077
Aidelco 347	Klaus 430
Allied 204	Leader 412
Amidon 005	Lin 451
Antech 257	Linear Systems 081
Antenna Mart 009	Long's 468
Antenna Spec. 010	Lyle 373
Supermarket 404	MFJ 082
Apron 380	MHz 415
Ashcraft *	Madison 431
Atlas 198	Main 452
Atronics 382	Matric 084
B K Products 463	Micro Seminar *
Barry *	Mini-Products 395
Bauman 017	M-Tech 357
Bell *	National Multi 396
Beta 447	N. R. I. 397
Bowmar *	Nexus 454
Budwig 233	Non-Linear 469
Bullet 328	Northshore RF 296
CFP 022	Optoelectronics 352
CHM 464	P T I 470
Cal-Com 282	Palomar 093
Cleng 465	Partridge 439
C. I. E. *	Poly Paks 096
Comm. Spec. 330	Pruitt 365
Cont. Spec. 348	RP 098
Corbin 349	Callbook 100
Cush Craft 035	Ramsey 442
D-D 269	Regency 102
DGM 458	Rohn 410
Dames 324	SST 375
Dentron 259	Sandlin 471
Disc-Cap 449	SAROC *
Drake 039	Satan 443
Dynamic 041	SEA 472
E. T. O. 042	Sentry *
Elec. Dist. 044	Sherwood 435
Electrospace 407	Southwest
ELPROCON 301	Tech. 263
Exper *	Space 107
59+ 429	Spec. Comm.
Franke 289	Sys. 318
Genave 168	Spectronics 191
Gilfer 207	Spec. Int. 108
Gray 055	Standard 109
Gregory 201	Swan 111
Hal 057	TRW 473
Hal-Tronix 254	Tangent 166
HamLine 466	Teco 113
Ham Radio 150	Ten-Tec *
Hamtronics 246	Trevor 474
Harp 460	Tristao 118
Heath 060	Tycol 475
Henry 062	Universal 444
Hosfelt 390	Utah FM 445
Hy-Gain 064	VHF 121
Icom 065	Vanguard
Int'l Xtal 066	Varian 043
Field Day *	Webster Comm. 423
JS & A *	Webster Radio 255
James 333	Weinschenker 122
Jan 067	Weirnu 379
Janel 068	Whitehouse 378
K-Enterprises 071	Wilson 123
KLM 073	Wire Concepts 476
Kensco 394	Yaesu 127

\*Please contact this advertiser directly.

Limit 15 inquiries per request.

## August 1976

Please use before September 30, 1976

Tear off and mail to  
HAM RADIO MAGAZINE — "check off"  
Greenville, N. H. 03048

NAME .....

CALL .....

STREET .....

CITY .....

STATE ..... ZIP .....

NOW  
is the time to order  
YOUR

# 76 callbook

If you don't already have your 1976 Callbooks there is no better time than right now to go to your local dealer (or mail direct to the publisher) and get the most up to date QSL information available anywhere.

The new 1976 U. S. Callbook has over 300,000 W & K listings. It has calls, license classes, names and addresses plus the many valuable back-up charts and references you have come to expect from the Callbook.

Specialize in DX? Then you're looking for the new, larger than ever 1976 Foreign Callbook with over 225,000 calls, names and addresses of amateurs outside of the USA.

On dealer shelves NOW!

United States Callbook All W & K Listings \$13.95 with 3 Service Editions \$19.95

Foreign Radio Amateur Callbook DX Listings \$12.95 with 3 Service Editions \$18.95

RADIO AMATEUR  
**callbook** INC  
Dept. E 925 Sherwood Drive  
Lake Bluff, Ill. 60044

Order from your favorite electronics dealer or direct from the publisher. All direct orders add \$1.00 shipping and handling per Callbook.

# Advertisers index

Adva Electronics	98
Aidelco	113
Amidon Associates	120
Antech Labs	113
Antenna Mart	118
Antenna Specialists Co.	41
Antenna Supermarket	90
Apron	114
J. P. Ashcraft Co.	96
Atlas Radio	103
Atronics	118
B K Products	123
Barry	110
Bauman	114
Bell System	69
Beta Electronics	112
Bowmar	96
Budwig Mfg. Co.	118
Bullet	109
CFP Communications	92
CHM Products, Inc.	86
Cal-Com Systems, Inc.	120
Cieng Electronics	124
Cleveland Institute of Electronics	108
Communications Specialists	84, 113
Continental Specialties	72, 73
D. R. Corbin Mfg. Co.	120
Cush Craft	1
D-D Enterprises	102, 114
DGM Electronics	122
Dames, Ted	122, 124
Dentron Radio Co.	7, 29
Disc-Cap	108
Drake Co. R. L.	93, 101
Dynamic Electronics	120
Ehrhorn Technological Operations	92
Electronic Distributors	63
Electrospace	102
ELPROCON	123
Exper Printing	112
Five Nine Plus	110
Fred Franke, Inc.	104
General Aviation	99
Gilfer Associates	124
Gray Electronics	106
Gregory Electronics	86
Hal Communications Corp.	2
Hal-Tronix	122
HamLine Electronics	98
Ham Radio	111, 114, 115, 121
Hamtronics, Inc.	114
H. Alan Harp	119
Heath Company	64, 65
Henry Radio Stores	Cover II
Hosfelt Electronics	98
Hy-Gain Electronics Corp.	42, 43
Icom	5
International Crystal	107
International Field Day	110
JS & A Group, Inc.	83
James Electronics	105
Jan Crystals	114
Janel Labs	122
K-Enterprises	82
KLM Electronics, Inc.	82
Kensco Communications, Inc.	98
Trio-Kenwood Communications, Inc.	8, 9
King Products	82
Klaus Radio	90
Lin Corp.	125
Long's Electronics	23
Lyle Products	123
MFJ Enterprises	128
MHz Electronics	106
Madison Electronics Supply	98
Main Electronics, Inc.	119
Matric	84
Microcomputer Seminar	76
Mini-Products	120
M-Tech	112
National Multiplex Corp.	77
National Radio Institute	125
Nexus Trading Company	84
Northshore RF Technology	108
Optoelectronics	91
P T I	118
Palomar Engineers	98, 112, 120
Partridge (HR) Electronics	123
Poly Paks	100
Pruitt Enterprises	118
RP Electronics	104
Radio Amateur Callbook	96, 126
Ramsey Electronics	68
Regency Electronics	89
Rohn	95
SST Electronics	122
Sandlin Electronics Engineering	120
SAROC Hawaii	78
Satan Electronics	123
Sentry Mfg. Corp.	122
Sherwood	118
Southwest Technical Products	79
Space Electronics Corp.	120
Specialty Communications Systems	112
Spectronics	85
Spectrum International	82
Standard Communications	110
Swan Electronics	86, 94, 95, 125
Teco Electronics	104, 118
Ten-Tec	127
Trevor Industries	119
Tristao, Div. of Palmer	124
Tycol	119
Universal Radio	122
Utah FM Sales	96
VHF Engineering, Div. of Brownian	97
Vanguard Labs	108
Varian, Elm Division	Cover IV
Webster Communications	106
Webster Radio	112
Weinschenker	102
Weirnu	122
G. R. Whitehouse & Co.	124
Wilson Electronics	32, 33
Wire Concepts, Inc.	124
Yaesu Musen USA	Cover III

# *“They don't make 'em like they used to..”*

*(lucky for you, if your next HF transceiver is a TRITON)*

The new ultra-modern fully solid-state TRITON makes operating easier and a lot more fun, without the limitations of vacuum tubes.

For one thing, you can change bands with the flick of a switch and no danger of off-resonance damage. And no deterioration of performance with age.

But that's not all. A superlative 8-pole i-f filter and less than 2% audio distortion, transmitting and receiving, makes it the smoothest and cleanest signal on the air.

The TRITON IV specifications are impeccable. For selectivity, stability and receiver sensitivity. And it has features such as *full* CW break-in, pre-selectable ALC, off-set tuning, separate AC power supply, 12 VDC operation, perfectly shaped CW wave form, built-in SWR bridge and on and on.

For new standards of SSB and CW communication, write for full details or talk it over with your TEN-TEC dealer. We'd like to tell you why “They Don't Make 'Em Like They Used To” makes Ham Radio even more fun.

PRICE \$699.00



**TEN-TEC**


SEVIERVILLE, TENNESSEE 37862  
EXPORT: 5715 LINCOLN AVE.  
CHICAGO, ILLINOIS, 60646
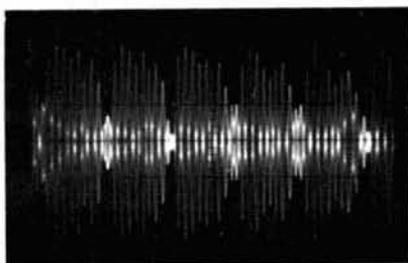
# 400% MORE RF POWER

WITH THE NEW **MFJ** SUPER LOGARITHMIC SPEECH PROCESSOR



SSB Signal **Before** Processing. The weak valleys and high peaks give a low average power output, resulting in a real lack of punch.



SSB Signal **After** Processing. The once weak valleys are now strong peaks giving up to a 400% increase in average power output. The result is a signal full of punch with power to slice through QRM.

These actual unretouched "before" and "after" photographs of the SSB RF Output of our NCX-3 Transceiver proves the effectiveness of the sophisticated MFJ Super Logarithmic Speech Processor.

Two active high pass filters (switch selectable) remove wasteful low speech frequencies. These frequencies contain 50% of the total speech power but contribute only 10% to intelligibility.

A specially designed I.C. logarithmic amplifier instantaneously changes gain with a minimum of distortion. This strengthens weak valleys and flattens peaks of normal speech patterns. A steep roll-off 6 pole lowpass filter removes harmonic distortion.

TWO MODELS TO CHOOSE FROM —  
PLUGS BETWEEN YOUR MICROPHONE AND TRANSMITTER



**\$49.95**

**LSP-520 BX.** 2-3/16 x 3 1/4 x 4 inches. Uses 9 volt battery. RF protected. 3 conductor, 1/4" phone jacks for input and output.



**\$59.95**

**LSP-520 BX II.** Same as LSP-520BX but in a beautiful 2 1/2 x 3 3/8 x 5-9/16 inch Ten-Tec enclosure with uncommitted 4 pin Mic jack, output cable, rotary function switch.




**\$27.95**
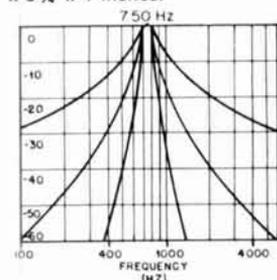
### CWF-2BX SUPER CW FILTER

By far the leader. Over 5000 in use. Razor sharp selectivity. 80 Hz bandwidth, extremely steep skirts (See Response Curves).

- No ringing • Bandwidth: 80 Hz, 110 Hz, 180 Hz (selectable) • Skirt rejection: at least 60 dB down one octave from center frequency for 80 Hz bandwidth • Center frequency 750 Hz • Drastically reduces all background noise (up to 15 dB improvement in S/N ratio) • Provides gain • No impedance matching • 8 pole active filter uses ICs • 9 volt transistor battery provides months of operation • 400 Hz or 1000 Hz center frequency optional. Add \$3.00. • Size: 2-3/16 x 3 1/4 x 4 inches.



CWF-2PC  
wired PC  
board  
**\$18.95**

CWF-2PCK  
kit PC  
board  
**\$15.95**



**\$49.95**

### CMOS-8043 ELECTRONIC KEYS

- Uses Curtis 8043 Keyer IC • Built-in key • Dot memory • Iambic operation with external squeeze key • 8 to 50 WPM • Sidetone and speaker • Volume, tone, weight controls • Solid State Keying  $\pm 300$  volts max. • Uses 4 penlight cells • 2-3/16 x 3 1/4 x 4 inches.



**\$49.95**

### MFJ-1030 BX RECEIVER PRESELECTOR

- Dramatically improves weak signal reception • Significantly rejects out of band signals • 20 dB gain, min. • 10 to 30 MHz • Dual gate MOS FET • Separate input and output tuning • Uses 9 volt battery • Beautiful Ten-Tec enclosure • 2 1/2 x 3 3/8 x 5-9/16 inches.

**NEW**  
**\$39.95**

### MFJ-16010 ANTENNA TUNER

- All bands 160 thru 10 meters • Matches almost any random length of wire to any Transceiver or Transmitter • Rated at 200 watts RF Output to handle virtually any transceiver running barefoot • Ultra compact 2-3/16 x 3 1/4 x 4 inches • Matches low and high impedances by interchanging input and output • SO-239 coaxial connectors • Unique wide range, high performance, 12 position tapped inductor. Uses two stacked toroid cores • High quality specially designed variable capacitors • Heavy duty construction • All aluminum cabinet.

Order now. Shipments begin on or before August 31, 1976.

ORDER TODAY. MONEY BACK IF NOT DELIGHTED. ONE YEAR UNCONDITIONAL GUARANTEE.

ORDER BY MAIL OR CALL 1-601-323-5869 AND CHARGE IT ON



Please add \$2.00 per item for Shipping/Handling

**MFJ ENTERPRISES** • P. O. BOX 494(H) • MISSISSIPPI STATE • MISSISSIPPI 39762

# From YAESU The Outstanding New GOLD LINE FT-301D



**ALL SOLID STATE**

**200W PEP**

**DIGITAL DIAL TRANSCEIVER**



■ 6 - Digit Readout ■ All Modes – SSB/CW/AM/FSK ■ 160 thru 10 Meters ■ TX & RX Clarifier ■ RF Feedback ■ 3 - Position AGC ■ Rejection Tuning (Tuneable IF Crystal Filter) ■ Built-in DC Power Supply ■ Optional AC Power Supply & Speaker Unit with 12 or 24 Hr. Digital Clock ■ Noise Blanker ■ RF Speech Processor ■ Computer Type Plug-In Module Construction ■ Size: 11 in. (w) × 5 in. (h) × 13½ in. (d) ■ Light Weight: 22 lbs.


The Model FT-301D is a precision-built, all solid-state, compact high performance transceiver of advanced design. All circuits are fully transistorized with ICs and FETs for reliability. A wide-band tuning system with preset pass band tuning combined with wide-band amplifier eliminates final amplifier tuning for band change. Also available as an option is an automatic CW identifier (programmable).

*Whether you judge it on price, performance or operational features, the FT-301D comes out a winner!*
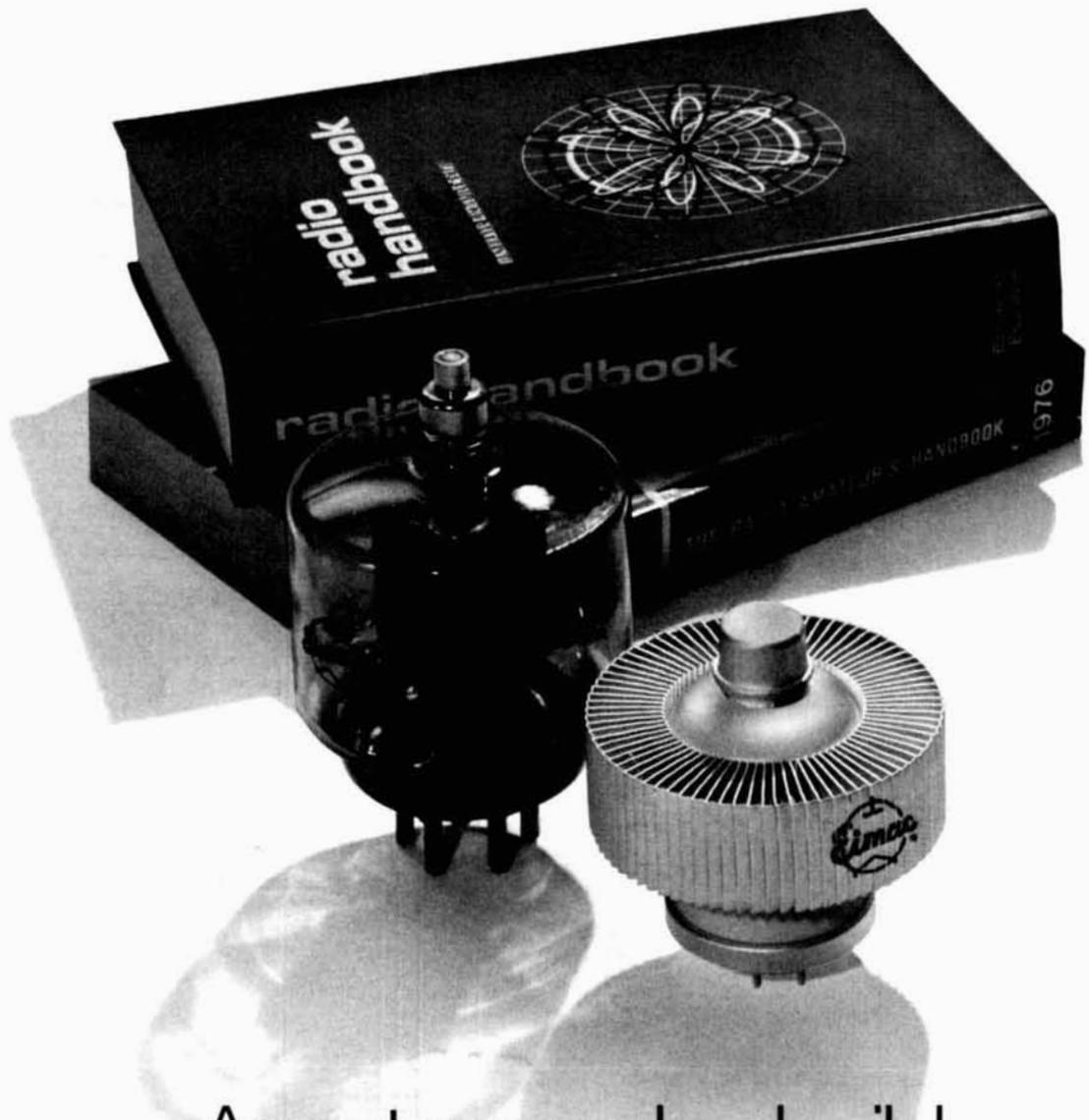
## YAESU *The radio.*

Yaesu Musen USA Inc., 7625 E. Rosecrans, No. 29, Paramount, California 90723

Yaesu Musen USA Inc., Eastern Service Center • 613 Redna Terrace, Cincinnati, OH 45215



## Amateurs who build their own equipment go EIMAC.

Building HF or VHF power amplifiers? You'll find them described in detail in both the *ARRL Handbook* and the *Radio Handbook*. And you'll find that EIMAC tubes are the overwhelming choice of expert equipment designers for 1.8 to 1296 MHz service.

The *Radio Handbook* features a deluxe amplifier using the 3-1000Z for HF service plus other HF or VHF designs built around the 3-500Z, 4CX1500B, 8877 and the 8874. The *ARRL Handbook* describes a multiband HF amplifier using the 8877, plus other designs featur-

ing the 3-500Z, 8873, 4CX250B and 3CX100A5. And there's plenty of information about design and construction of transmitting equipment using EIMAC power tubes in both handbooks.

For tube information, contact Varian, EIMAC Division, 301 Industrial Way, San Carlos, California 94070. Or contact any of the more than 30 Varian Electron Device Group Sales Offices throughout the world.

