

**Radio-Electronics**

**INDUSTRIAL TEST EQUIPMENT—METERS**

75c ■ NOV. 1975

3-1140 IND

# Radio-Electronics

THE MAGAZINE FOR NEW IDEAS IN ELECTRONICS

**CHANGE CALCULATOR INTO  
A DIGITAL STOPWATCH  
With Simple IC Add On**

**WHAT'S A PROM?  
Discover This Special  
Kind Of Memory IC**

**BUYING  
BOOKSHELF SPEAKERS  
You've Got To Know  
What You're Doing**

**SCREEN-READ BOARD  
For TV Typewriter II**

**SQUAREWAVES &  
AUDIO TESTING  
How One  
Affects The Other**

**NEW COLOR  
TV KIT  
It's Made  
To Work Wrong**



**PLUS**

**Jack Darr's Service Clinic • Lab Tested Hi-Fi Reports  
Technicians Questions & Answers • Equipment Reports**




**NEW  
MUSIC SYNTHESIZER  
A Portable  
Sound-Effects Machine**

The image shows a portable music synthesizer. It consists of a control panel with several knobs and buttons, and a separate circuit board with various electronic components like resistors, capacitors, and integrated circuits. The control panel is white with black knobs and text, and the circuit board is yellow with various components mounted on it. The entire setup is mounted on a wooden frame.

# PTS ELECTRONICS

## Precision Tuner Service

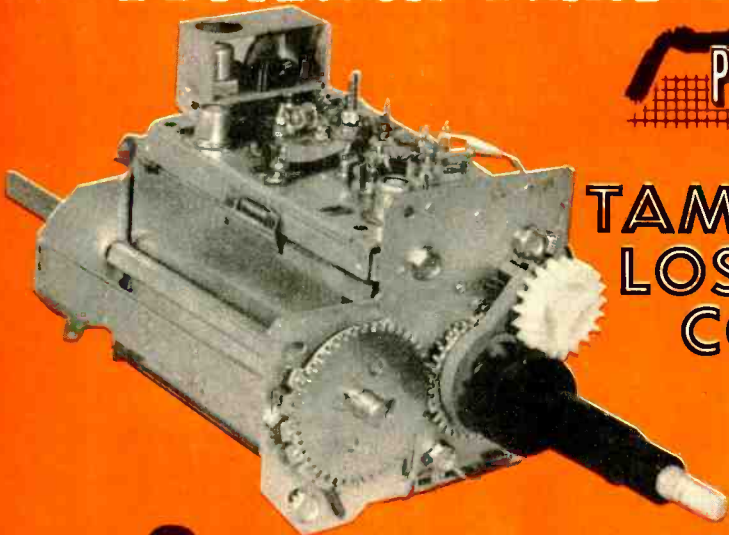

is proud to announce the  
**GRAND OPENING**  
of our new Service Centers in

**TAMPA**  
**LOS ANGELES**  
**COLUMBUS, OHIO**  
**PHOENIX**  
**BOSTON**  
**NORFOLK**  
**INDIANAPOLIS**

*Fast* **8** hr. Service!

### LET US TAKE CARE OF YOUR TUNER PROBLEMS...

PTS will repair any tuner—no matter how old or new. Fastest Service—8 hour—in and out the same day. Overnight transit to one of our strategically located plants. Best Quality—you and your customers are satisfied.  
PTS uses only ORIGINAL PARTS! No homemade or make-do, inferior merchandise (this is why we charge for major parts!). You get your tuner back in ORIGINAL EQUIPMENT condition.  
PTS is recommended by more TV Manufacturers than any other tuner company and is overhauling more tuners than all other tuner services combined.

VHF, UHF \$10.95  
UV-COMBO 17.95  
IF-SUBCHASSIS 12.50

Major parts and shipping charged at cost. (Dealer net!)

## PTS ELECTRONICS, INC.

HOME OFFICE	BLOOMINGTON, INDIANA 47401	5233 S. HIGHWAY 37	812-824-9331
ALABAMA	BIRMINGHAM, ALABAMA 35222	524 32ND ST. SO.	205-323-2657
ARIZONA	PHOENIX, ARIZONA 85061	2412 W. INDIAN SCHOOL RD.	602-279-8718
CALIFORNIA CENTRAL	LOS ANGELES, CA. 90023	4184 PACIFIC WAY	213-266-3728
CALIFORNIA NORTH	SACRAMENTO, CA. NO. 95841	4611 AUBURN BLVD.	916-482-6220
CALIFORNIA SOUTH	SAN DIEGO, CA. SO. 92105	5111 UNIVERSITY AVE.	714-280-7070
COLORADO	ARVADA, COLORADO 80001	4958 ALLISON ST.	303-423-7080
FLORIDA NORTH	JACKSONVILLE, FLA. NO. 32210	1918 BLANDING BLVD.	904-389-9952
FLORIDA CENTRAL	TAMPA, FLA. 33690	2703 S. MACDILL	813-839-5521
FLORIDA SOUTH	MIAMI, FLA. SO. 33168	12934 N.W. 7TH AVE.	305-685-9811
INDIANA CENTRAL	INDIANAPOLIS, IND. 46202	28 E. 14TH ST.	317-631-1551
INDIANA	BLOOMINGTON, IND. 47401	5233 S. HIGHWAY 37	812-824-9331
KANSAS	KANSAS CITY, KANSAS 66106	3116 MERRIAM LANE	913-831-1222
LOUISIANA	METAIRIE, LA. 70003	2914 WYCHWOOD DR.	504-885-2349
MARYLAND	SILVER SPRINGS, MD. 20919	8880 BROOKVILLE RD.	301-565-0025
MASSACHUSETTS EAST	SOMERVILLE, MASS. 02144	52 HOLLAND ST.	617-666-4770
MASSACHUSETTS WEST	SPRINGFIELD, MASS. 01103	191 CHESTNUT ST.	413-734-2737
MICHIGAN	DETROIT, MICH. 48235	13709 W. 8 MILE RD.	313-862-1783
MINNESOTA	MINNEAPOLIS, MINN. 55408	815 W. LAKE ST.	612-824-2333
MISSOURI	ST. LOUIS, MO. 63130	8456 PAGE BLVD.	314-428-1299
NEW JERSEY	E. PATERSON, N. JERSEY 07407	158 MARKET ST.	201-791-6380
NEW YORK	BUFFALO, NEW YORK 14212	993 SYCAMORE ST.	716-891-4935
NORTH CAROLINA	CHARLOTTE, N. CAR. 28205	724 SEIGLE AVE.	704-332-8007
OHIO SOUTH	CINCINNATI, OHIO 45215	8180 VINE ST.	513-821-2298
OHIO CENTRAL	COLUMBUS, OHIO 43227	4003 E. LIVINGSTON AVE.	614-237-3820
OHIO NORTH	PARMA, OHIO 44134	5682 STATE RD.	216-845-4480
OKLAHOMA	OKLAHOMA CITY, OK. 73106	3007 N. MAY	405-947-2013
OREGON	PORTLAND, OREGON 97213	5220 NE SANDY BLVD.	503-282-9636
PENNSYLVANIA WEST	PITTSBURGH, PA. 15202	257 RIVERVIEW AVE. W.	412-761-7648
PENNSYLVANIA EAST	UPPER DARBY, PA. 19082	1742-44 STATE RD.	215-352-6609
TENNESSEE	MEMPHIS, TENN. 38118	3614 LAMAR AVE.	901-365-1918
TEXAS SOUTH	HOUSTON, TEXAS 77032	4324-26 TELEPHONE AVE.	713-644-6793
TEXAS NORTH	LONGVIEW, TEXAS 75601	MOPAC RD.	214-753-4334
VIRGINIA	NORFOLK, VA. 23504	3118 E. PRINCESS ANNE RD.	804-625-2030
WASHINGTON	SEATTLE, WASH. 98108	432 YALE AVE.	206-623-2320
WISCONSIN	MILWAUKEE, WIS. 53215	3509 W. NATIONAL	414-643-8800

We offer you finer, faster...

... Precision  
Tuner Service



ELECTRONICS, INC. ...

... Number ONE and still trying harder!  
(Not a Franchise Company)

**1 YEAR**  
**GUARANTEE**

**P**  
**T**  
**S**  
**No.**  
**1**

Circle 1 on reader service card

# If Santa had a Altair®...

## Santa might be possible!

Have you ever wondered how Santa keeps track of all the addresses of all the children in the world? How he knows who gets what?

With an Altair 8800, Santa might have a fighting chance. He might be able to keep up with the ever-expanding toy industry. He might be able to remember who's been naughty and nice.

With an Altair 8800, Santa might be possible.

**This Christmas you can do something that's never before been possible.** You can put an Altair under your tree or under the tree of a friend. Or you can start with our special Christmas 75 time payment plan!\*

The Altair 8800 is the **NUMBER ONE** hobby computer in the whole world. No other computer offers you the power and versatility—the proven track record—of the Altair 8800 at a comparable price. No other hobby computer offers you the sophistication of Altair BASIC software or the wide variety of Altair modules and peripherals. No other hobby computer offers you the customer support of an Altair (free membership in the Altair Users Club, free access to the Altair Service Department and the Altair Software Library, and a free subscription to the Altair monthly publication, *Computer Notes*).

Order now and avoid the last minute Christmas rush!

### \* Christmas 75 Time Payment Plan

1K Altair for just \$68.00 a month!

The Altair time payment plans allow you to be the owner of an Altair 8800 with 1,024 bytes of memory for just \$68.00 a month. Each month (for 8 months) you send in your payment and we send you part of an Altair kit until you have the complete system. The advantages of this plan are **NO interest** or financing charge, **GUARANTEED price** based on today's price, and free, **immediate membership** to the Altair Users Group including subscription to *Computer Notes*.

Our terms are cash with order, BankAmericard or Master Charge. If you send in an early payment we will make an early shipment. By the same token, a late payment will result in a late shipment. (After 60 days past due, the balance of the deal is cancelled. All payments must be made within 10 months).

**Total Price: \$544** (Retail price: Altair \$439, Memory \$97, Postage and handling \$8—total \$544)

#### HARDWARE PRICES:

Altair Computer kit with complete assembly instructions	\$439
Assembled and tested Altair Computer	\$621
1,024 Byte Static Memory Card	\$97 kit and \$139 assembled
2,048 Byte Static Memory Card	\$145 kit and \$195 assembled
4,096 Byte Dynamic Memory Card	\$264 kit and \$338 assembled
Full Parallel Interface Card	\$92 kit and \$114 assembled
Serial Interface Card RS232	\$119 kit and \$138 assembled
Serial Interface Card (TTL or Teletype)	\$124 kit and \$146 assembled
Audio Cassette Record Interface	\$128 kit and \$174 assembled
COMTER II*	\$780 kit and \$920 assembled



\*The Comter II Computer Terminal has a full alpha-numeric keyboard and a highly readable 32-character display. It has its own internal memory of 256 characters and complete cursor control. Also has its own built-in audio cassette interface that allows you to connect the Comter II to any tape recorder for both storing data from the computer and feeding it into the computer. Requires an RS232 Interface Card.

#### SOFTWARE PRICES:

Altair 4K BASIC	\$350
Purchasers of an Altair 8800, 4K of Altair Memory, and Altair Serial I/O or Audio-Cassette I/O	ONLY \$60
Altair 8K BASIC	\$500
Purchasers of an Altair 8800, 8K of Altair Memory, and Altair Serial I/O or Audio-Cassette I/O	ONLY \$75
Altair EXTENDED BASIC	\$750
Purchasers of an Altair 8800, 12K of Altair Memory, and Altair Serial I/O or Audio-Cassette I/O	ONLY \$150

Altair PACKAGE ONE (assembler, text editor, system monitor)

Purchasers of an Altair 8800, 8K of Altair Memory, and Altair I/O ONLY \$30

NOTE: When ordering software, specify paper tape or cassette tape.

Warranty: 90 days on parts for kits and 90 days on parts and labor for assembled units. Prices, specifications, and delivery subject to change.

# MITTS

"Creative Electronics"

MITTS/6328 Linn N.E., Albuquerque, NM 87108 505/265-7553 or 262-1951

#### MAIL THIS COUPON TODAY!

Enclosed is check for \$\_\_\_\_\_

BankAmericard # \_\_\_\_\_  or Master Charge # \_\_\_\_\_

Altair 8800  Kit  Assembled  Options

(List on separate sheet)

Include \$8 for postage & handling

Altair Time Payment Plan

Please send free literature  Please send my order to different address

(List on separate sheet)

NAME \_\_\_\_\_


ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE & ZIP \_\_\_\_\_

MITTS/6328 Linn N.E., Albuquerque, NM 87108 505/265-7553 or 262-1951

NOTE: Personal checks take 2-3 weeks for clearance. For immediate processing send money order or use charge card.

Circle 2 on reader service card

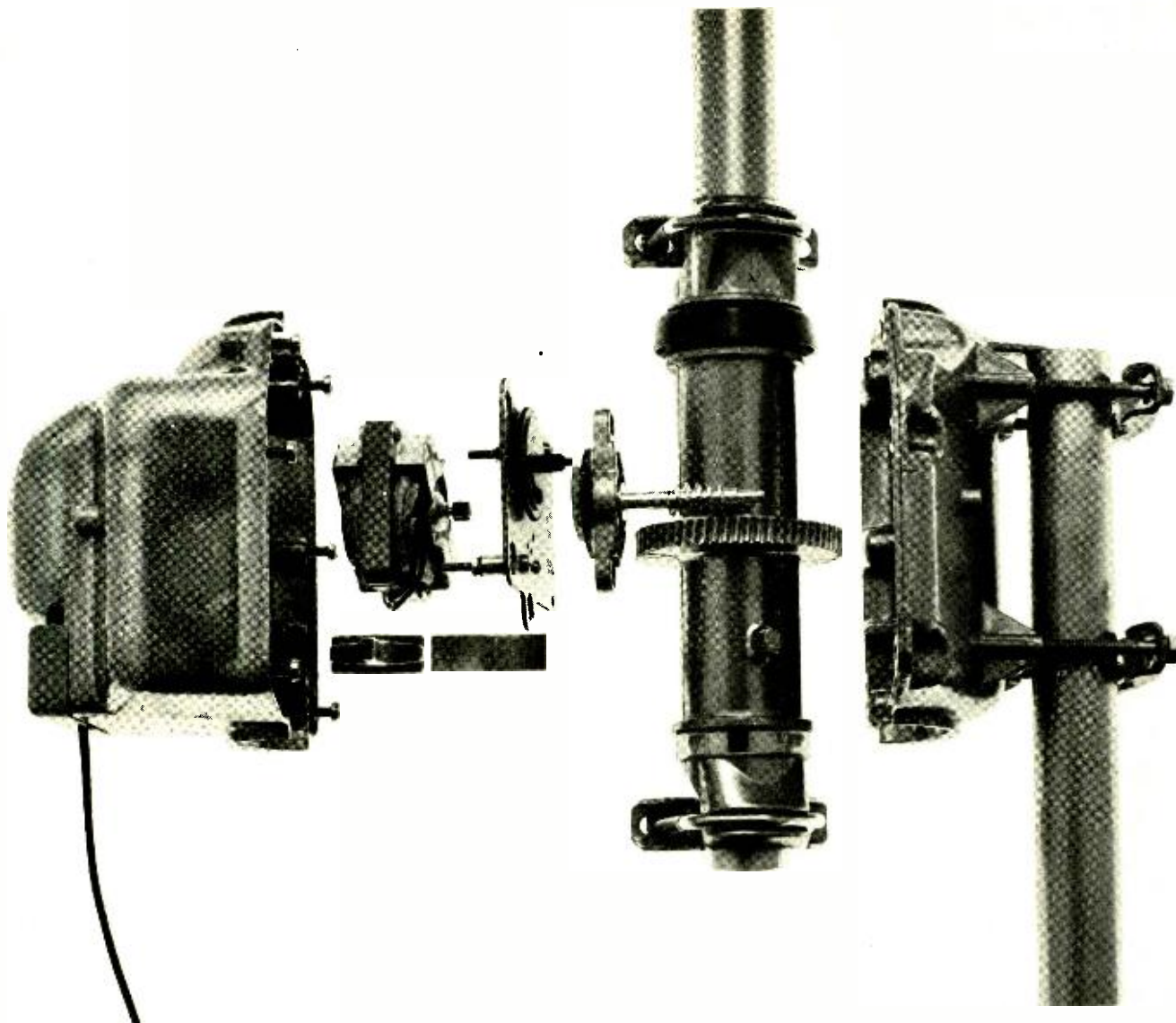

**“RCA warrants this product against defects in materials and workmanship for a period of two years from date of purchase...”**

**RCA's Selecta-Channel Automatic Rotator carries the only 2-year warranty from a major company.**

The Drive Unit for model 10W606 (shown above) features an easily removable high-tensile aluminum alloy housing. Inside, a powerful high efficiency motor. Permanently lubricated oversize stainless steel bearings — no external thrust bearings are required. Quick-connect pressure terminals. A new mast mounting that won't snag lead-in wires. Premounted hardware, and a reinforced shaft.



The Control Unit is an attractive chrome-trimmed beige, with cushioned base. The transparent “direct select” control knob has a moving direction indicator light showing the antenna's exact position. And, it's quiet: no click-clack sound.

For more information on the 10W606 or the deluxe Automatic Rotator 10W707, call your RCA Distributor. Or contact RCA Distributor and Special Products Division, Building 206-2, Cherry Hill Offices, Camden, New Jersey 08101.

**RCA**  
**Rotators**

# Radio-Electronics®

THE MAGAZINE FOR NEW IDEAS IN ELECTRONICS

Electronics publishers since 1908

NOVEMBER 1975 Vol. 46 No. 11

## BUILD ONE OF THESE

- 37 **Portable Electronic Music Synthesizer**  
*Part I:* How it works and the special effects it can produce.  
by John Simonton
- 43 **Calculator Doubles As Stopwatch**  
Add-on circuit converts pocket calculator into an accurate stopwatch that measures hundredths of a second.  
by Tommy Tyler
- 50 **Manual Cursor Board**  
Another add-on for TV Typewriter II. by Ed Colle

## GENERAL ELECTRONICS

- 4 **Looking Ahead**  
Sneak preview of tomorrow's news.  
by David Lachenbruch
- 6 **Publisher's Memo**  
R-E earns NESDA awards. by M. Harvey Gernsback
- 108 **NESDA Convention News**  
Photographic report on the annual convention of the National Electronics Service Dealers Association.

## SOLID-STATE ELECTRONICS

- 22 **State-Of-Solid-State**  
Timely report on the latest developments in solid-state devices and applications. by Karl Savon
- 72 **How PROM's Work**  
A look at what a PROM really is and how it works and can be used. by Roger L. Smith

## HI-FI STEREO 4-CHANNEL

- 52 **Squarewaves And Audio Performance**  
What squarewave reproduction tells you about the performance of hi-fi equipment. by Len Feldman
- 54 **R-E Lab Tests Radio Shack QTA-770**  
Detailed report on a moderate price receiver.  
by Len Feldman
- 61 **R-E Lab Tests Shure M95ED**  
See how this new cartridge performs. by Len Feldman
- 63 **How To Buy Bookshelf Speakers**  
*Part II:* Distortion and other specifications that must be considered. by Art Kleiman

## TEST EQUIPMENT

- 40 **Test Equipment For Industrial Servicing**  
Roundup of new and interesting equipment for the industrial electronics service technician. by Jack Darr
- 116 **Equipment Report**  
B & K model 280 digital multimeter.
- 122 **Equipment Report**  
Heathkit IM-2202 digital multimeter.

## TELEVISION

- 78 **Service Clinic**  
High-voltage shut-down circuits. by Jack Darr
- 80 **Reader Questions**  
R-E's Service Editor solves reader problems.
- 106 **Service Notes**  
Technician problems and their solutions.
- 114 **Color TV Kit That Teaches Electronics**  
Learn how circuits work while you build this kit.  
by Chester H. Lawrence

## DEPARTMENTS


- |                              |                         |
|------------------------------|-------------------------|
| 14 Advertising Sales Offices | 96 New Literature       |
| 134 Advertising Index        | 92 New Products         |
| 16 Letters                   | 118 Next Month          |
| 12 New & Timely              | 137 Reader Service Card |
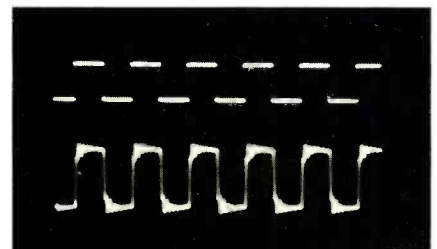
### ON THE COVER

Floating on that sea of Mylar and a sky of blue paper is a portable music synthesizer that produces effects that border on magic. Find out how you can build your own. Turn to page 37 now.



**NEED A STOPWATCH?** Just take a calculator, add an IC and a few other components and you'll have one—inexpensive and accurate . . . see page 43.



**SQUAREWAVES ARE A KEY** element in testing hi-fi gear. Learn how to use them effectively . . . see page 52.

Radio-Electronics, Published monthly by Gernsback Publications, Inc., 200 Park Avenue South, New York, NY 10003. Phone: 212-777-6400. Second-class postage paid at New York, NY and additional mailing offices. One-year subscription rate: U.S.A., U.S. possessions and Canada, \$8.75. Pan-American countries, \$10.25. Other countries, \$10.75. Single copies 75c. © 1975 by Gernsback Publications, Inc. All rights reserved. Printed in U.S.A.

**Subscription Service:** Mail all subscription orders, changes, correspondence and Postmaster Notices of undelivered copies (Form 3579) to Radio-Electronics Subscription Service, Boulder, CO 80302.

A stamped self-addressed envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

As a service to readers, Radio-Electronics publishes available plans or information relating to newsworthy products, techniques and scientific and technological developments. Because of possible variances in the quality and condition of materials and workmanship used by readers, Radio-Electronics disclaims any responsibility for the safe and proper functioning of reader-built projects based upon or from plans or information published in this magazine.

# looking ahead

## New CB rules

The FCC has relaxed Citizens band rules to legalize some practices that many CB operators have been doing for years. It discontinued its prohibition against hobbyist use of the band. It dropped restrictions against contacts between stations, eliminating the general requirement that conversations must be between units of the same station. It established Channel 11 as a nationwide calling channel—for use in establishing first contact and arranging to move to another channel. Call letters must now be given only at the beginning and end of each conversation, with “handles”—or nicknames—permitted as supplementary identification.

Crowding of the band could be relieved somewhat by two new rules: Conversations are limited to five minutes maximum, with a minute of silence between conversations. Receiving antenna heights are limited, as well as transmitting antennas. Still pending before FCC are proposals to allocate more frequencies to CB, to switch much of the band to single-sideband use, to lower the licensing age to 16 from 18 and to give the Commission direct engineering jurisdiction over antenna design through a type-acceptance program.

## TV's future

Everybody's peering into the future of television. This month it's New York ad agency Needham, Harper & Steers, which studied how television will be in 1985. Here are the forecasts: (1) Cable will be “the dominant TV industry of the 1980's.” Some 38,800,000 homes, or 45.7% of all homes that have television will be connected to cable by January 1, 1975. (2) Pay-TV will feed 15.5% of these 38,800,000 cable homes. (3) The average home will have about 2.6 television sets,

up from 1.8 today. (4) There will be 85,000,000 homes that have television, and more than 98% of these will have color. (5) Videodiscs—forget it. Only 750,000 homes will have videoplayer systems, less than 1% of all TV-equipped homes, because of the cost of players and discs and compatibility problems.

## Microwave pay TV

The initial success of Pay-TV via cable, as opposed to its inability to get moving via broadcast stations, has raised a new question: Why not eliminate the cable and beam programs directly to homes by microwave? This is exactly what is being attempted now in several cities, using Multi-point Distribution Service (MDS), a common-carrier super high frequency (2150–2160 MHz) service authorized by the FCC to transmit specialized material to specific locations.

Microband National System, a national MDS marketing organization, plans to start non-cable Pay-TV immediately in Atlanta, moving to Pittsburgh, Minneapolis and Indianapolis by February, and eventually to Hartford, Cleveland, Akron, Milwaukee, Denver, Seattle and Portland, OR by early next year. MDS is useful for Pay-TV when there are large concentrations of people living in apartment buildings. The signal is beamed selectively to special directional receiving antennas on apartment buildings or hotels and then converted to an unused VHF channel (or special VHF channel to be fed to set-top Pay-TV converter) and funneled into the MATV system. This system is claimed to be more economical than cable for cities with large apartment-building concentrations, and also makes closed-circuit Pay TV available in areas without cable and to people who wish only Pay TV and not cable service as well. In many areas served by cable Pay-TV, the customer must pay eight or

nine dollars a month for cable service and another six to nine dollars for Pay TV. Under the MDS system, the customer would pay \$6.50 to \$8.50 monthly for Pay-TV only and continue to pick up off-the-air broadcasts.

## Magnavox factory service

Joining RCA, G-E and Sylvania in providing factory service for its products is Magnavox. At least, Magnavox is dipping its toes tentatively into the captive-service waters. Magnavox is opening its own consumer electronics repair center in Torrance, CA, to service Magnavox products only. Magnavox says only that it wants to get first-hand information on “product performance, reliability and user satisfaction.” This undoubtedly is true but it may also be true that Magnavox's new parent organization, profit-minded North American Philips, has studied the situation and found what some others have learned—that servicing can be more profitable than sales.

## Console comeback

A funny thing happened on the way to the funeral of the color TV console: Console-TV sales actually have turned around and increased their share of the color-TV market in the first half of 1975 for the first time in history. Ever since the introduction of table models and portables, the share occupied by consoles (including TV-radio-phono combinations) has been decreasing at an accelerating pace. But during January 1975 through June 1975, consoles and combinations actually represented nearly 33% of the American color-TV market, up from 29% one year earlier.

Most experts cite the growing replacement market as the primary reason. Pioneer color-TV buyers generally bought consoles—not only because

they represented an affluent group, but because many of them bought color-TV in the days when smaller-screen sets were rare or even nonexistent. Now they're coming back for seconds—and presumably many don't want to trade down to smaller-screen sets, or to leave that big space in the home vacant (where the old console was).

## Tighter UHF specs

A group of broadcasters' associations led by the Council for UHF Broadcasting (CUB) has petitioned the FCC to order a progressive tightening of permissible noise-figures in UHF tuners. The present upper limit is 18-dB, and CUB wants the FCC to reduce this to 14-dB in six months, 12-dB in 18 months and 10-dB in 30 months. In addition, the CUB urged the FCC to require that an “effective” indoor UHF antenna must be affixed to any TV set that is sold with a VHF antenna attached. The CUB cited recent tests that indicated the average noise figure of American UHF tuners was 12.7-dB, while the VHF tuner had only 6.9-dB.

CUB maintains that changes in receivers could be made at minimal charge, perhaps a nine-dollar increase at retail. As spokesman for receiver makers, EIA replies that price increases would be far higher with minimal benefits. The EIA also considers the proposed rules retrogressive since the television industry is now concentrating its energies on developing all-electronic varactor tuners while the decreases in noise, if decreed by FCC, would make it go back and concentrate on improvements in the current mechanical tuners. Some set makers say improvements in noise figures could increase susceptibility to interference, thereby worsening rather than improving UHF performance.

by DAVID LACHENBRUCH  
CONTRIBUTING EDITOR

# TUNER SERVICE CORPORATION

**SUBSTITUNER**

INTRODUCING  
AT JUST

**\$44.95**  
U.S.A. ONLY

WITH CABLES



ONE YEAR  
GUARANTEE

STILL ONLY

**\$9.95**  
U.S.A. ONLY

MAJOR PARTS  
AND  
SHIPPING  
CHARGED AT COST



PROVIDES YOU WITH A COMPLETE SERVICE  
FOR ALL YOUR TELEVISION TUNER REQUIREMENTS.

## FEATURES

- A UHF Tuner with 70 channels which are detented and indicated just like VHF channels.
- A VHF Hi Gain Solid State Tuner.
- AC Powered.
- 90 Day Warranty.

Demonstrate the **SUBSTITUNER** to your customers and show improved reception with their TV sets.

You may place your order through any of the Centers listed below.

## REPAIR

VHF OR UHF ANY TYPE ..... (U.S.A. ONLY) \$ 9.95  
UHF/VHF COMBINATION .....(U.S.A. ONLY) \$15.00

MAJOR PARTS AND SHIPPING  
CHARGED AT COST

- Fast, efficient service at our conveniently located Service Centers.
- All tuners are ultrasonically cleaned, repaired, realigned, and air tested.

## REPLACE

UNIVERSAL REPLACEMENT TUNER \$12.95 (U.S.A. ONLY)

- This price buys you a complete new tuner built specifically by Sarkes Tarzian Inc. for this purpose.
- All shafts have a maximum length of 10½" which can be cut to 1½".
- Specify heater type parallel and series 450 mA. or 600 mA.

## CUSTOMIZE

- Customized tuners are available at a cost of only \$15.95. With trade-in \$13.95. (U.S.A. ONLY)
- Send in your original tuner for comparison purposes to any of the centers listed below.



HEADQUARTERS	BLOOMINGTON, INDIANA 47401	537 South Walnut Street	Tel. 812-334-0411
ARIZONA	TUCSON, ARIZONA 85713	1528 S. 6th Ave.	Tel. 602-791-9243
CALIFORNIA	NORTH HOLLYWOOD, CALIF. 91601	10654 Magnolia Boulevard	Tel. 213-769-2720
	BURLINGAME, CALIF. 94010	1324 Marsten Road	Tel. 415-347-5728
	MODESTO, CALIF. 95351	123 Phoenix Avenue	Tel. 209-521-6051
FLORIDA	TAMPA, FLORIDA 33606	1505 Cypress Street	Tel. 813-253-0324
	FT. LAUDERDALE, FLORIDA 33315	1045 W. 23rd Street, Box 16	Tel. 305-524-0914
GEORGIA	ATLANTA, GEORGIA 30310	646 Evans Street, S.W.	Tel. 404-758-2232
ILLINOIS	CHAMPAIGN, ILLINOIS 61820	405 East University Street	Tel. 217-356-6400
	SKOKIE, ILLINOIS 60076	5110 West Brown Street	Tel. 312-875-0230
INDIANA	INDIANAPOLIS, INDIANA 46024	112 West St. Clair Street	Tel. 317-632-3493
IOWA	WEST DES MOINES, IOWA 50265	822 10th Street	Tel. 615-277-0155
KENTUCKY	LOUISVILLE, KENTUCKY 40205	2244 Taylorsville Road	Tel. 502-452-1191
LOUISIANA	SHREVEPORT, LOUISIANA 71104	3025 Highland Avenue	Tel. 504-221-3027
MARYLAND	BALTIMORE, MARYLAND 21215	5505 Reisterstown Rd., Box 2824	Tel. 301-358-1186
MASSACHUSETTS	SPRINGFIELD, MASSACHUSETTS 01108	405 Dickinson Street	Tel. 413-788-8206
MISSOURI	ST. LOUIS, MISSOURI 63132	10530 Page Avenue	Tel. 314-429-0633
NEVADA	LAS VEGAS, NEVADA 89102	1412 Western Avenue, No. 1	Tel. 702-384-4235
NEW JERSEY	TRENTON, NEW JERSEY 08638	901 North Olden Avenue	Tel. 609-393-0999
	JERSEY CITY, NEW JERSEY 07307	547-49 Tonnelle Ave., Hwy. 1 & 9	Tel. 201-792-3730
NORTH CAROLINA	GREENSBORO, NORTH CAROLINA 27405	2914 East Market Street	Tel. 919-273-6276
OHIO	CINCINNATI, OHIO 45216	7450 Vine Street	Tel. 513-821-5080
	CLEVELAND, OHIO 44109	4525 Pearl Road	Tel. 216-741-2314
OREGON	PORTLAND, OREGON 97210	1732 N.W. 25th Avenue	Tel. 503-222-9059
PENNSYLVANIA	PITTSBURGH, PENNSYLVANIA 15209	503 1/2 Grant Avenue	Tel. 412-821-4004
TENNESSEE	GREENEVILLE, TENNESSEE 37743	1215 Snapps Ferry Road	Tel. 615-639-8451
	MEMPHIS, TENNESSEE 38111	3158 Barron Avenue	Tel. 901-458-2355
TEXAS	DALLAS, TEXAS 75218	11540 Garland Road	Tel. 214-327-8413
VIRGINIA	NORFOLK, VIRGINIA 23513	3295 Santos Street	Tel. 804-855-2518
CANADA	ST. LAURENT, QUEBEC; CALGARY, ALBERTA		

WATCH US  
GROW

IF YOU WANT TO BRANCH OUT INTO THE TV TUNER REPAIR BUSINESS,  
WRITE TO THE BLOOMINGTON HEADQUARTERS ABOUT A FRANCHISE.

Circle 3 on reader service card

www.americanradiohistory.com

# **publisher's memo**

## **R-E Earns Awards**



NESDA, the nation's largest organization of independent service technicians and dealers, recently held their 1975 National Convention in Winston Salem, North Carolina.

During the convention, NESDA honored Larry Steckler, Editor of RADIO-ELECTRONICS Magazine, by giving him their Man Of The Year Award. This award is presented annually to the person whom the NESDA membership determines has done the most for the independent electronic service industry in the previous year.

The award is in the form of an engraved plaque (see photo) which states: "In Appreciation For Personal Efforts And Leadership To Achieve The Goals Of N.E.S.D.A. And To Further The Interest Of The Nation's Independent Electronic Service Dealers And Technicians."

The NESDA membership made a second award to RADIO-ELECTRONICS Magazine in the form of a Recognition Certificate: "For the use of their editor [Larry Steckler] as ISCET chairman and their support of the yearbook and convention activities at the convention."

Steckler was re-elected chairman of ISCET (the International Society of Certified Electronic Technicians) for 1975-76.

RADIO-ELECTRONICS is honored to receive these awards and takes this opportunity to thank the NESDA's membership for them. Editor Steckler has devoted a great deal of time and effort to the NESDA and ISCET because he and we believe in the importance of a strong independent service movement.

Although RADIO-ELECTRONICS Magazine is not a "service-only" magazine, it has always been strongly service oriented editorially and repeated readership studies have shown that a majority of its readers are engaged in service activities.

We will continue on this editorial path and redouble our efforts to support the service industry and justify its faith in us.

We also take this opportunity to congratulate Larry Steckler for NESDA's recognition of his efforts.

M. Harvey Gernsback,  
Editor-In-Chief and Publisher



## JBL Loudspeaker Components



Twelve brand new pages. Forty-seven JBL components — dividing networks, lenses, horns, transducers, everything.

Lots of these goodies have never been available as individual components before. (They've been performing inside JBL's newest professional studio monitors.)

Write us. We'll send you the catalogue, free, along with the name and location of your nearest

authorized JBL Loudspeaker Components Dealer.

He's important. Besides all those components he's got a fresh supply of the new JBL Enclosure Construction Kits that tell you everything you need to know about building your own JBL enclosure.

Fill out this coupon and send it along to JBL, the people who wrote the book on sound.



3249 Casitas Avenue  
Los Angeles 90039

Gentlemen:  
I can't beat the price. Send  
me the book.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

James B. Lansing Sound, Inc.  
High fidelity loudspeakers  
from \$99 to \$3210.

# The real way to learn digital electronics!

## NRI is the only school to train you at home on a real digital computer.



Learn computer design, construction, maintenance and programming techniques on your own digital computer using a professional digital multimeter!

Qualified technicians are urgently needed for careers in the exciting new field of digital and computer electronics . . . and the best way to learn digital logic and operations is now available to you in NRI's Complete Computer Electronics Course.

This exclusive course trains you at home on your own digital computer! This is no beginner's "logic trainer", but a complete programmable digital computer that contains a memory and is fully automatic. You build it yourself and use it to define and flow-chart a program, code your program, store your program and data in the memory bank. Press the start button and the computer solves your

**NOW . . .  
YOUR OWN DIGITAL (3½ DIGITS)  
MULTIMETER INCLUDED  
AT NO EXTRA COST!**

The latest in digital testing equipment . . . along with valuable training experiments in digital techniques.

problem and displays the result instantly.

The NRI digital computer is one of 10 kits you receive in the NRI Complete Computer Electronics Course. You build and use your own 3½ digit digital multimeter . . . while you perform hundreds of experiments, building hundreds of circuits, learning organization, operation, troubleshooting and programming.

## Only NRI offers you five TV/Audio Servicing Courses



Color TV repair is another big opportunity field right now and NRI can train you at home to service and repair any color or black & white TV, hi-fi equipment, AM-FM radios, and sound systems.

You can choose from 5 courses, starting with a basic servicing course with 65 lessons . . . up to a Master Color TV course, complete with 25" diagonal solid state color TV in handsome woodgrain cabinet. No other school offers so many choices or so much value.

All courses are available with low down payment and convenient monthly payments to fit your budget. And all courses provide professional tools and equipment along with NRI-designed kits for hands-on training. With the Master Course, for instance, you receive your own 5" wide-band triggered sweep solid state oscilloscope, TV pattern generator, 3½ digit digital multimeter and a NRI 25" diagonal solid state television receiver expressly designed for color TV training.

### YOU PAY LESS WITH NRI TRAINING AND YOU GET MORE FOR YOUR MONEY.

NRI employs no salesmen, pays no commissions. We pass the savings on to you in reduced tuitions and extras in the way of professional equipment, testing instruments, etc. You can pay more, but you can't get better training.

## NRI's complete communication course includes your own CB Training Transceiver



NRI prepares you for a career in the rapidly expanding field of communications . . . a field destined to double in the next decade! NRI can train you at home for one of the thousands of service and

maintenance jobs opening in AM and FM Transmission and Reception, TV Broadcasting, Microwave Systems, Teletype, Radar, Marine Electronics, Mobile Communications and Aircraft Electronics. You train on your own 23-channel Johnson Transceiver and AC power supply; a digital multimeter, for digital experiments and precise testing; bite-size lessons leading to your FCC license and the communications field of your choice.

### NEARLY ONE MILLION STUDENTS IN 60 YEARS HAVE LEARNED AT HOME THE NRI WAY.

Mail the insert card and discover for yourself why NRI is the recognized leader in home study training. No salesman will call. Do it today and get started on that new career.

#### APPROVED UNDER GI BILL

For the career minded, we are approved for veterans benefits. Check box on card for details.

### MAIL THE INSERT CARD FOR YOUR FREE NRI CATALOG

No salesman will call



**NRI SCHOOLS**  
McGraw-Hill Continuing Education Center  
3939 Wisconsin Avenue,  
Washington, D.C. 20016

3-115

# new & timely

## Zenith co-founder dies at 79

Karl E. Hassel, radio industry pioneer and one of the founders of Zenith Radio Corp., died July 7 in Evanston, IL. His age was 79.

A radio amateur since 1912, Hassel and a friend, R.H.G. Mathews, both Navy radio operators, started the Chicago Radio Laboratory when they left the Navy in 1918. Using a kitchen table as a workbench and a soldering iron that had to be heated over a gas burner, the "laboratory" manufactured amateur radio receivers, at the rate of about one a week. They operated a ham station with the call letters 9ZN, from which came the name "Zenith."



KARL E. HASSEL

The late Commander E. F. McDonald joined the young organization and became general manager and Zenith's founder-president. The assets and business of the Chicago Radio Laboratory were purchased by Zenith Radio Corp. in 1923. Mr. Hassel was active in the reorganized corporation and was a director of Zenith until his retirement in 1973.

## Broadcast type resolution in solid-state TV camera

"The first solid-state TV camera that meets the resolution requirements for commercial broadcast use," is what Bell Labs scientists claim for their latest device, an experimental camera that measures only 2.5 x 2.5 x 6 inches. In spite of its lack of size, its imaging area is designed to be equivalent to the scanning area of a 1-inch diameter TV camera of the type used in conventional TV work.

The solid-state imaging unit is a Charge Coupled Device (CCD) in which the light falling on each scan line is converted into a series of charges on tiny plates. At the end of each field, the lines are all shifted to corresponding lines in a storage area, from which a line at a

time is stepped out to form a regular television signal while the next field is being imaged.



THE CHARGE-COUPLED IMAGE SENSOR is a single chip of silicon covered with an array of more than 235,000 electrodes.

The CCD in this camera contains nearly a quarter of a million sensing elements—a significant improvement in resolution over older solid-state imagers. It has 496 vertical interlaced scan lines as well as the 475 horizontal picture elements.

To fabricate this extremely large (16 x 20 mm) device, Bell Labs engineers used an electron beam exposure system, similar to the one developed at the Labs for making large-scale integrated circuits.

## Audiomen get Debby awards

The Society of Audio Consultants, at its fourth annual Debby Awards dinner-dance held in Chicago in early summer, gave Debby awards to several individuals who have been foremost in the recent improvement and development of audio techniques. (The name Debby is a true audio term, derived from decibel.)

Foremost among those awarded Debby's for technical achievement was Ben Bauer of CBS Labs. With him were cited Ryoosuke Ito and Susumu Takahashi of Sansui Electronics. All three were honored for their work in 4-channel recording and reproduction.

A special Debby was given to Leonard Feldman, who among his other activities is Instruction Chairman of the Society. He was cited for educational work and development of IHF (Institute of High Fidelity) standards. John Koss of Koss Corp. was awarded a special Debby for being first to introduce high-fidelity headphones and for maintaining world leadership through continuous research and development.

A number of other Debby's were awarded to consultants, manufacturers, managers and dealers in the audio field.

## SOUND-VISION



AUSTRALIAN SOUND-VISION SYSTEM has a combination disc and film cassette, with the film cassette in the center of the disc. Cassette thickness can be reduced to 3-mm (about the thickness of some old-time 78-rpm discs). Sound is on the disc, vision on the film cassette. Inventor, Czech-born Rudolph Stepanek, says the sound is excellent but image at present is not as sharp as a videotape picture. The new device has been named a Poly Gramo-Vision.

## Gernsback Scholarship awards to Waylin Goodman, Marvin Baker

This month's Hugo Gernsback Scholarship award, a prize of \$150 given each month to a student in one of eight leading home study electronics schools, goes to Waylin Goodman, Grand Island, NE. Nominated by his school, ICS (International Correspondence Schools) he is an electronic technician employed by the FCC and is owner of his own part-time business, Waylin's Color TV Service. He writes:

"After being separated from the Navy, I planned to go into broadcasting. I had experience in programming but no working knowledge of electronics, so I took a beginning course to improve my chances. I was surprised to find that I liked working on the equipment.

I worked on the lessons every second I could spare, and soon converted a large walk-in closet into a TV repair shop. I was really enjoying my endeavors for the

(continued on page 14)

410 to 1  
 you'll find  
 the  
 devices  
 you need  
 here.

Over 103,200 devices can be replaced by 250 RCA SK Series types. That's 410 to 1! Best ratio in the industry. Which means the odds are, SK is your best, fastest way to get what you need. With minimum inventory. And RCA provides the top quality you'd expect from a top manufacturer of OEM devices. Same strict AQL standards, same strict Director of Quality Assurance. Get SK devices and your free 1975 SK Series Replacement Guide from your local RCA distributor.



It's OK if it's **sk**

Circle 4 on reader service card

Hugo Gernsback (1884-1967) founder

**M. Harvey Gernsback**  
editor-in-chief and publisher

**Larry Steckler, CET**, editor

**Robert F. Scott, W2PWG, CET**,  
technical editor

**Arthur Kleiman**, associate editor

**Jack Darr, CET** service editor

**Leonard Feldman**  
contributing high-fidelity editor

**David Lachenbruch**, contributing editor

**Karl Savon**, semiconductor editor

**Vincent P. Cicenja**, production manager

**Irene Feldman**, production assistant

**Harriet I. Matysko**, circulation director

**Arline R. Bailey**, advertising coordinator

Cover photo courtesy Walter Herstatt

Cover design by Louis G. Rubsamen

**Radio Electronics** is a member of the *Institute of High Fidelity* and is indexed in *Applied Science & Technology Index* and *Readers Guide to Periodical Literature*.




first time in years, and was making money within a month after I started.

I am an electronics technician with the Federal Communications Commission, and by using the training from ICS and the training the FCC is giving me, I have a good career going. I am repairing radio and television part-time and hope to open my own television sales and service center. I was recently accepted as a warranty repair center by Quasar and General Electric companies.



**WAYLIN O. GOODMAN**

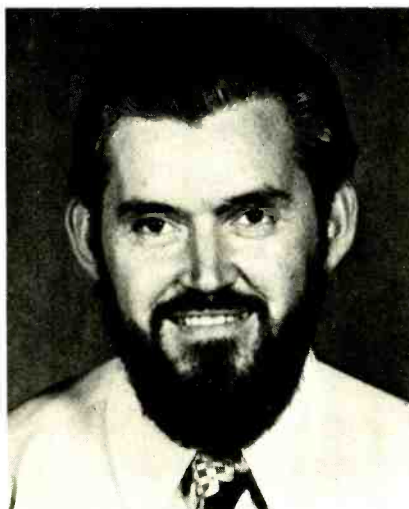

**MARVIN R. BAKER**

In addition to my career with the FCC, I am becoming known as a good, reliable television technician. These two endeavors are in pursuit of a career in electronics and I love it! I owe a great deal to electronics and the ICS."


Marvin R. Baker of Greenville, OH, is the winner of the second-place award, a

WV-529A service VOM donated monthly by RCA to the second most deserving student. Mr. Baker is employed by Inland Steel Container Co. He writes:

"The most important benefits received from my course in Industrial Electronics are capability to service photoelectric eyes and industrial electronic welders as used by Inland Steel Container in their Greenville plant."
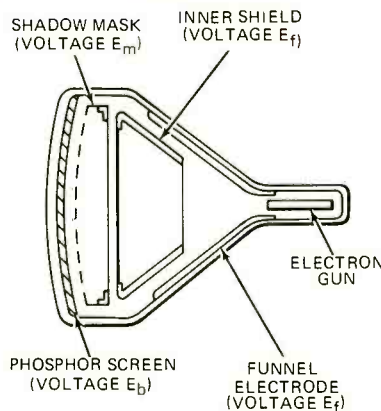
### Newest Hitachi picture tube has post-deflection focusing

A new "mask-focusing" color television picture tube by Hitachi claims a picture 50% brighter than that of conventional picture tubes. The increased brightness, Hitachi reports, is produced by maintaining the mask at a lower voltage than the phosphor screen; thus accelerating and focusing the electrons as they proceed from mask to screen; and by absorbing secondary electrons with an intermediate voltage applied to a special funnel electrode in the tube (see sketch). The mask-focusing makes it possible to use a mask with slightly larger holes, giving it twice the transparency of a conventional mask.



**MASK-FOCUSING PIX TUBE provides a 50% increase in brightness.**

The voltage ratios between the electrodes must be maintained very closely for maximum brightness, and much of the work of designing the new tube was in determining and setting those ratios. To improve voltage stability, a special rectifying and adding circuit is used for the funnel electrode. The primary-winding pulse of the feedback transformer is rectified to obtain 0.7 kV. This is added to the shadow mask voltage of 12.1 kV, bringing the funnel electrode voltage up a little higher than that of the shadow mask to better absorb secondary electrons. The voltages on the elements are thus: screen, 25 kV; shadow mask, 12.1 kV; funnel electrode, 12.8 kV. **R-E**

**Radio-Electronics** is published by Gernsback Publications, Inc. 200 Park Ave. S. New York, NY 10003 (212) 777-6400

President: M. Harvey Gernsback

Secretary: Bertina Baer

### ADVERTISING SALES

#### EAST

Stanley Levitan, Sales Manager  
Radio-Electronics  
200 Park Ave. South  
New York, NY 10003  
(212) 777-6400

#### MIDWEST/Texas/Arkansas/Okla.

Ralph Bergen  
The Ralph Bergen Co.  
6319 N. Central Ave.  
Chicago, IL 60646  
(312) 792-3646

#### PACIFIC COAST/Mountain States


Jay Eisenberg  
J.E. Publishers Representative Co.,  
8732 Sunset Blvd.,  
4th Floor,  
Los Angeles, CA 90069  
(213) 659-3810

Sales Mart Building  
1485 Bayshore Blvd., Box 140  
San Francisco, CA 94124  
(415) 467-0125

# Radio Shack®

A TANDY CORPORATION COMPANY
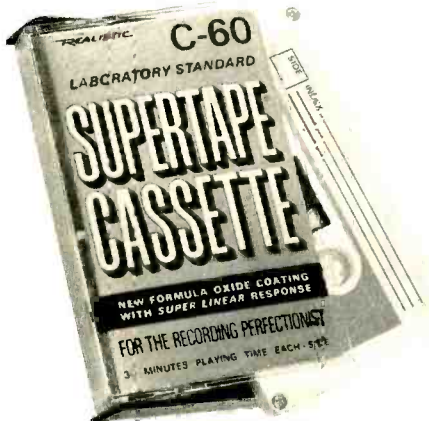
## 50%-OFF TAPE SALE\* TO GET YOU INTO REALISTIC SUPERTAPE® (even if you're there already)



CASSETTE



OPEN REEL



8-TRACK

Join the big switch to Supertape and save a neat 50% on your trial order at any participating Radio Shack store or Dealer. It's made in our factory on the newest equipment and to the highest standard we could set. It's internationally sold and acclaimed. Let your recorder and your ears be the judge. Not our advertising. Not theirs. Try Supertape today. There's only one place you can find it . . . Radio Shack!

\*At Participating Radio Shack Stores and Dealers Now Through Nov. 30, 1975

Radio Shack's  
Own tape factory  
in Fort Worth, Texas



The nation's newest  
tape manufacturing operation  
devoted exclusively to audio tape

## CLIP COUPONS. BRING TO RADIO SHACK

600  
**GET ONE  
SUPERTAPE  
CASSETTE  
AT NO EXTRA COST**

when you buy the same cassette at the regular price at any participating Radio Shack store or Dealer. Limit one. This coupon must accompany your in-person purchase. None sent by mail.

STORE # \_\_\_\_\_  
Sale Ends Nov. 30, 1975.

600  
**GET ONE  
SUPERTAPE  
OPEN REEL  
AT NO EXTRA COST**

when you buy the same reel at the regular price at any participating Radio Shack store or Dealer. Limit one. This coupon must accompany your in-person purchase. None sent by mail.

STORE # \_\_\_\_\_  
Sale Ends Nov. 30, 1975.

600  
**GET ONE  
SUPERTAPE  
CARTRIDGE  
AT NO EXTRA COST**

when you buy the same 8-track cartridge at the regular price at any participating Radio Shack store or Dealer. Limit one. This coupon must accompany your in-person purchase. None sent by mail.

STORE # \_\_\_\_\_  
Sale Ends Nov. 30, 1975.

NOVEMBER 1975

Circle 5 on reader service card

15

# 8080 with POWER


You'd never expect on a

## MICRO-PROCESSOR

Our interpreter has the power  
also ask about

• Monitor • Assembler • Text Editor

**Bulletin Available**

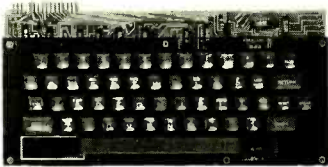

**NEW!!** Not better — but the best  
keyboard in a kit.

Key switches by Cherry.

**Only \$69.95**

### PRICE LIST

— P.C. BOARDS ONLY —

Mother-Power supply board to  
support 10 modules, Processor  
Board, Memory Board, I/O  
Boards..... \$27.50 ea.

Mother Board Solder  
Tab Connectors .... \$ 7.50 ea.

— KITS —

Processor Board — 8080A

1K ROM, 1K RAM

Plus timing and

control .....\$ 395.00

Memory Board-4K Static Ram

Compatible w/Altair

8800 .....\$ 152.50

I/O Board — 2 serial ports

1-16 Bit Parallel

Port .....\$ 147.50

Keyboard — 53 key

ASCII .....\$ 69.95

Mother Board — Power

Supply .....\$ 87.50

— ASSEMBLED & TESTED —

Processor .....\$ 450.00

Memory Board .....\$ 195.00

I/O Board .....\$ 190.00

Keyboard .....\$ 99.00

Mother Board — Power

Supply .....\$ 105.00

Mother Board Solder

Tab Connectors .....\$ 10.00

Ask about

other low cost peripherals

**NO EXTRA CHARGE**

- Hardware Bootstrap
- 450 NS Static Ram
- Strap Selectable Ports  
for RS 232, TTL, or 20 MIL.
- Strap Selectable Baud Rates
- Above software

— WRITE TO —

**COMPUTER-EASE, INC.**

2107 Walker

Houston, Texas 77003

Phone: 713/236-1448

Circle 6 on reader service card

# letters

## AM VS. FM

In a recent issue of your fine publication I noted a review of a receiver marketed by Sansui. The review was conducted by, I believe, Len Feldman of your staff.

This review contained detailed analysis of the receiver's FM reception section, as well as the amplifier section. However, no review of the AM section was included.

I cannot help but feel that your exclusion of the AM section does your many readers a disservice. The state-of-the-art is helped greatly by comparative analysis in publications such as yours, as the consumer tends toward those products that achieve excellence in reviews.

You might wish to note that FCC figures as of May 31st, 1975, indicated that commercial AM stations far outnumber commercial FM stations. In fact, there are presently 4,414 AM stations, compared to 2,630 commercial FM operations in this country.

We are not unaware of the trait toward enthusiasts listening on the FM bands, largely because of the specialization in music available there. However, the preponderance of listening is still with the broadcaster who uses amplitude modulation, and there are advances to be made in the quality of receivers used in that service.

As you may—or may not—know, the AM broadcaster is capable of *transmitting* a signal of comparable fidelity to that found on the FM band. Directing your attention toward the broadcast equipment presently in use, you would find very little difference in the frequency response characteristics. RCA, which supplies the great part of transmitters currently in use, has published figures indicating the great similarity between AM and FM transmitters of equal output power. The frequency response specifications and distortion specifications are very very close in comparing two 5,000 watt transmitters, a common output power in the industry.

Some of the belief that AM is a low-fidelity only medium certainly dates back to the past, when most AM broadcasters could achieve a bandpass of only 5,000 Hz—poor by today's standards. A quick check of the modern proof-of-performance standards indicates that the situation has changed. You will note that the RCA "Ampliphase" AM transmitters achieve an audio bandpass of 30—15,000 Hz ± 1.5 dB (BTA-5L1 5,000 watts) at less than 2% distortion. The FM BTF-5E1 RCA transmitter (5,000 watts) achieves an audio bandpass of 50—15,000 Hz ± 1.0 dB at less than .5% distortion.

The AM band is an important part of broadcasting, and I believe that you

would do your readers a service by including specifications of the AM sections of receivers reviewed.

NELSON E. DAHL  
Dahl Broadcasting Co.  
North Platte, NE


## SHOCK HAZARD IN LCD CLOCK

I am very upset about the shock hazard that exists in the LCD clock featured in the August 1975 issue. The clock has a unique construction and because of this, many readers are likely to copy its construction right down to the grain if the wood. This same uniqueness can cause people to handle it with possible fatal results.

I urge you to publish a warning regarding this hazard and suggest that the readers that construct this project install a 1:1 isolation transformer.

DAVID LUNNEY  
Greenville, NC

## TV TYPEWRITER

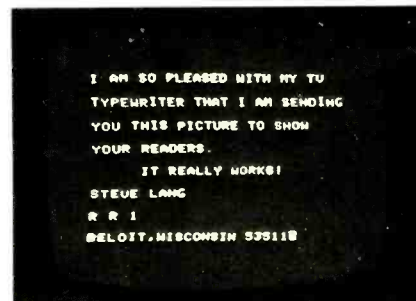

## OOOOPS!

Please note that there is a misprint contained in the article "All About Oscilloscopes, Part Three," by Charles Gilmore, appearing on page 54 of the August issue. The equation given for phase-angle measurement in Figure 23 should read:

$$\theta = \text{ARC SIN } \frac{B}{A}$$


GEOFFREY M. LANGDON  
Technical Manager  
AKG/PHILIPS  
Montvale, NJ





**Ask AmpereX**  
about  
**Replacement Tubes**  
for  
**Scientific Instruments**

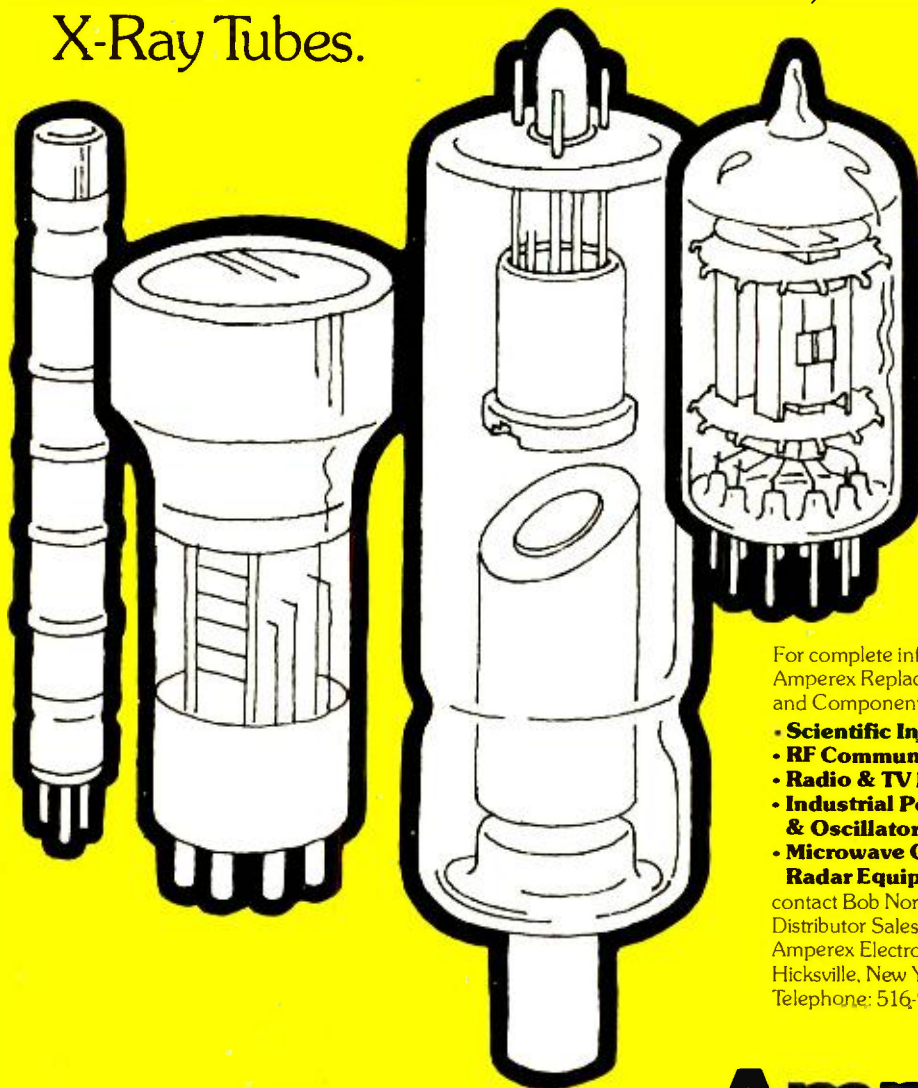Photomultipliers, Geiger-Mueller Tubes,  
PQ Tubes, RF Power Transistors,  
Neutron Generators, Numerical Indicators,  
Trigger Tubes, Silicon Rectifier Stacks,  
Industrial CRT's, Plumbicons,\* Vidicons,  
Solid State Radiation Detectors,  
X-Ray Tubes.



For complete information on  
AmpereX Replacement Tubes  
and Components for:

- **Scientific Instruments**
- **RF Communications Transmitters**
- **Radio & TV Broadcast Equipment**
- **Industrial Power Supplies  
& Oscillators**
- **Microwave Ovens & Commercial  
Radar Equipment**

contact Bob Norris,  
Distributor Sales Operation,  
AmpereX Electronic Corporation,  
Hicksville, New York 11802.  
Telephone: 516-931-6210.

**AmpereX**<sup>®</sup>

TOMORROW'S THINKING IN TODAY'S PRODUCTS

A NORTH AMERICAN PHILIPS COMPANY

Circle 7 on reader service card

\*Registered trademark of N. V. Philips of the Netherlands


# 400 Heathkit gift ideas

## efficient, creative values for everyone

①
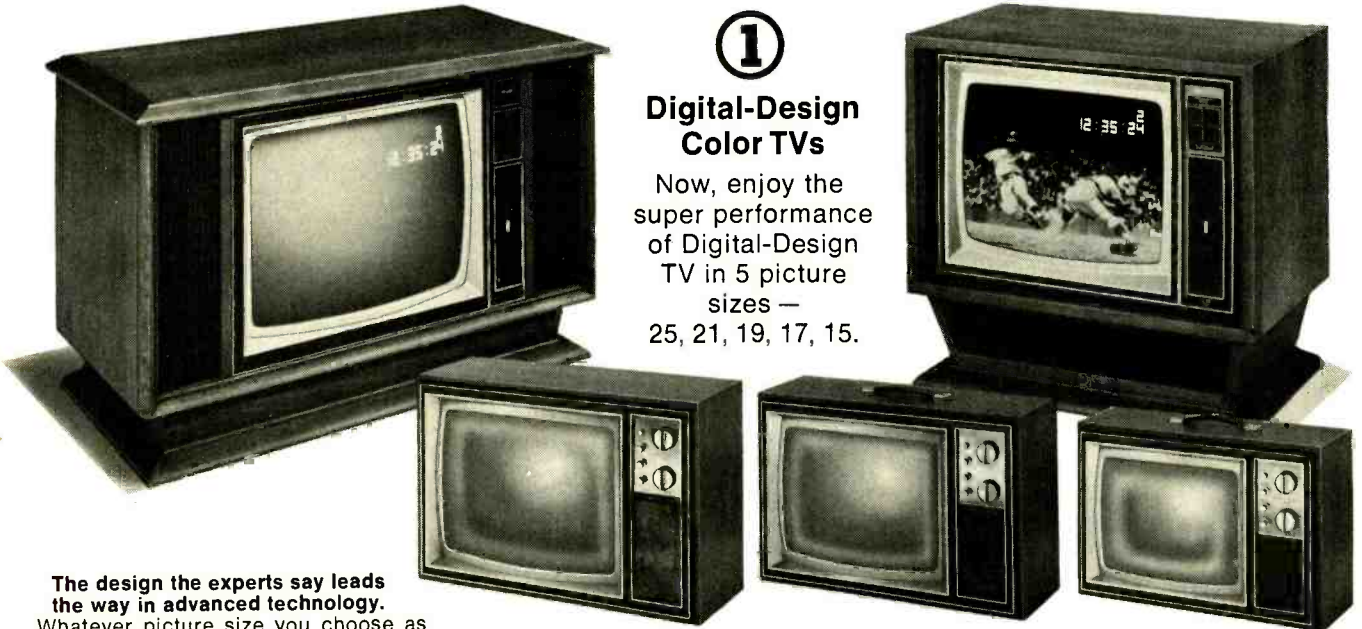
### Digital-Design Color TVs

Now, enjoy the super performance of Digital-Design TV in 5 picture sizes — 25, 21, 19, 17, 15.



#### The design the experts say leads the way in advanced technology.

Whatever picture size you choose as best for you, the technical advances of the design that startled the industry are yours in Heathkit Color TV.

#### On-Screen Channel Numbers

Big, bright, white numbers you can see from any angle, even across the room. Adjustable in brightness. Positionable anywhere on the screen. Adjustable for time duration of up to 1½ minutes or they can remain on all the time, at your option. The numbers change as you change channels. No other channel readout is as convenient.



#### On-Screen Clock Time

Here's a \$29.95 option that's a marvel of convenience, too. Big ¾" numbers appearing just below the channel numbers tell you the exact time every time you change channels. Right down to the second, if you wish. And it displays in 12 or 24-hour format.

#### Fixed-Filter for Best Pictures Longer

Unique. Exclusive. Heath-designed circuitry incorporates a fixed L-C type filter with an integrated-circuit IF amplifier to

produce an ideally shaped bandpass. That means you not only get less adjacent channel interference, but also consistently excellent color pictures year after year because it never needs periodic instrument alignment. These Heathkit Color TVs always look better.

#### 100% Solid-State

And more integrated circuits than any. The only tube in these sets is the picture tube. This sophisticated circuitry gives you less interference, truer colors, more precise, reliable tints, improved sensitivity, greater noise immunity, and better picture definition. Solid long-life performance.

#### The Differences

**Tuning.** In the 25v and 21v sizes, you get Total Electronic Touch Tuning. Silent varactor tuners, no moving parts. A programmable digital counter controls the tuning—sweeping up or down the 16 pre-selected channels. And remote control of all functions is just \$89.95. In the small screen sizes, the tuning is all-channel detent type.

**One-Button Picture Control** in the three

smaller sets restores brightness, contrast, color and tint to pre-set levels at the touch of a button. Child-proof performance.

**Latest-design, Picture Tubes.** In the two larger sets you enjoy brighter pictures with greater contrast thanks to the deluxe Black (negative) Matrix tubes. The three table models use picture tubes with the new precision in-line gun and slotted shadow mask for greater light output and picture realism.

#### Easier to build and service.

Plug-in circuit modules and wiring harnesses make these sets the easiest to build of all. And the new digital-design Dot Generator, slide-out Service Drawer and Test Meter make self-service easier.

#### Compare the value.

Send for your free Heathkit catalog, choose the model you prefer. Then compare it with any brand—we think you'll agree you get more for your money with Heathkit Digital-Design Color TV.

**For as low as \$399.95, you can enjoy Heathkit Digital Design Color TV.**



② **NEW High Fidelity AM/FM Table Radio**

At last, a table radio worth listening to... one that performs like hi-fi components. 5 μV sensitivity; ceramic filters for 60 dB selectivity; and an output power of 5 watts, minimum rms, at less than 1% total harmonic distortion, from 60 to 15,000 Hz into its 8 ohm full range high compliance speaker. The closed cabinet features a teak wood grain vinyl covering and black, molded double-knit jersey front panel. Kit GR-1085, \$99.95



③ **NEW Programmable Electronic "Doorbell"**

Put a song at your doorstep with this unique kit. Program it to play your favorite song. C through C' "keyboard" with plug-in leads for up to 16 notes. Change your tune when you wish to celebrate a season, anniversary, birthday, or special party. One watt sound power; controls for tuning, volume, speed, and decay characteristics. Kit TD-1089, \$44.95



④ **NEW versatile, low cost 5-digit counter**

Measures frequency from 5 Hz to 30 MHz, period to 99.999 seconds, counts events to 99,999, and it will operate on 120 VAC or 12 VDC. As a freq. counter it will resolve to 1 Hz; sensitivity is 15 mV above 50 Hz, 50 mV below 50 Hz. In the period mode, it will resolve to 1 msec. Has Over-range indicator; gate lamp; 3-position input attenuator; 10 MHz time base. Kit IM-4100, \$129.95

5

### MODULUS™

The new total-flexibility music system. For your changing needs.

Heath proudly introduces MODULUS. The totally modular music system that enables you to make of it what you will, change it when you like. With complete freedom. Without obsolescence.

#### As you like it.

Performance and versatility as in the finest of separate components, yet with the convenience of an integrated receiver.

Your MODULUS custom music system begins with Module I, the AN-2016 Digital AM/FM Tuner/Preamplifier. A superb FM tuner with sophisticated circuitry and exceptional specifications (four 1/2" LEDs display frequencies; dual JFET, 4-gang tuner with 1.7 μV sensitivity; digital discriminator; LC IF filter with over 100 dB selectivity; phase-locked loop multiplex with over 40 dB separation). AM you'll really enjoy hearing (dual-gate MOSFET tuner and mixer stages; computer-designed 9-pole LC IF filter for no alignment; shielded loop antenna). A superlative preamplifier that functions in stereo or 4-channel modes with specifications unlike any component we've ever offered. Distortion below 0.05% even at full out-



6

### NEW 3-Way Speaker

Looks and sounds like it should cost \$100 more! High performance 3-way system has a 10" woofer, 4 1/2" mid-range, 1" dome tweeter. Drives with 10 watts, yet a super-power amp reveals its unusual dynamic range and high power handling capabilities. Enclosure has walnut veneer on all sides and front for use without the black foam grille. Tweeter and front-mounted switch plate are interchangeable for optimum imaging in horizontal or vertical position. Kit AS-1373, \$149.95

392

other gift ideas in the free Heathkit catalog. Send today.

HEATHKIT ELECTRONIC CENTERS —  
Units of Schlumberger Products Corporation  
Retail prices slightly higher.

ARIZ.: Phoenix; CALIF.: Anaheim, El Cerrito, Los Angeles, Pomona, Redwood City, San Diego (La Mesa), Woodland Hills; COLO.: Denver; CONN.: Hartford (Avon); FLA.: Miami (Hialeah), Tampa; GA.: Atlanta; ILL.: Chicago, Downers Grove; IND.: Indianapolis; KANSAS: Kansas City (Mission); KY.: Louisville; LA.: New Orleans (Kenner); MD.: Baltimore, Rockville; MASS.: Boston (Wellesley), Boston (Peabody); MICH.: Detroit; MINN.: Minneapolis (Hopkins); MO.: St. Louis (Bridgeton); NEB.: Omaha; N.J.: Fair Lawn; N.Y.: Buffalo (Amherst), New York City, Jericho (L.I.), Rochester, White Plains; OHIO: Cincinnati (Woodlawn), Cleveland, Columbus, Toledo; PA.: Philadelphia, Pittsburgh; R.I.: Providence (Warwick); TEXAS: Dallas, Houston; VA.: Norfolk (Va. Beach); WASH.: Seattle; WIS.: Milwaukee.



put. Hum and noise are 80 dB below a 0.25 v. input even in the high-level section. A phono preamp with over 94 dB dynamic range — better than most records! Versatile control center. Special speaker protecting circuitry. Four lighted output meters with 40 dB dynamic range. Separate bass, treble, and level controls for front and back channels. Master volume control. 21 pushbutton switches that light when activated. They include: output; inputs (stereo phono, CD-4, aux., tape, tape monitor, dubbing AM and FM); mode (mono, stereo front channels, stereo 4 channels, SQ, and discrete 4-channel); high filter; low filter; loudness; tone flat; squelch defeat; FM Dolby; and power. Use it as a tuner only, as a driver for your present power amps, as a control center for taping, so good you can even use it as a broadcast station monitor. Kit AN-2016, \$599.95


Expand your MODULUS system with your choice of stereo power amplifiers. Module II is the medium power AA-1505. Module III is the high power AA-1506.

35 or 60 watts, min. RMS, per channel into 8 ohms at less than 0.1% distortion from 20-20,000 Hz. Styled to match the Module I tuner/preamp. Add one of either power level for a stereo receiver; add two for a 4-channel receiver. Kit AA-1505, \$159.95; AA-1506, \$179.95

Choose your mode and input. Module IV is the FM Dolby module AD-1504 for reduced noise and greater dynamic broadcast range (\$39.95). Module V is the CD-4 Demodulator for the spacious sound of CD-4 discrete 4-channel records (\$79.95). Module VI is the SQ Decoder for quadraphonic separation of matrixed material; full logic and variable blend (\$49.95). All are housed inside the tuner/preamp module.
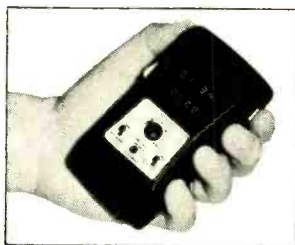
#### A "Living" music system.


MODULUS is designed for you — the way you live — today and tomorrow. It can grow with you, adapt to your changing life style, flex with changing technology. Whatever your desires in music systems, now and later, MODULUS.



7
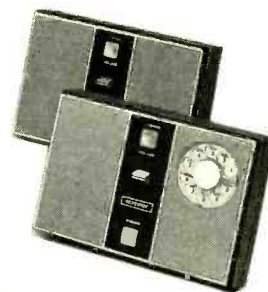
### NEW Digital Stopwatch

Programmable — for the time of your sporting life. You program in a time (up to 9 hours, 59 min., 59 secs.) and it will count up to that time or down from it to zero. Or it will count 99 hours, 59 mins., 59:99 secs. in the five other functions which include: Start/Stop Elapsed; Sequential; Total Activity; Split; & Start/Stop Activity. 8 digits & 2 IC counters with accuracy to ±0.003% & resolution to 1/100th second. Jacks for external trigger and alarm. Includes nickel-cad. batteries & charger. Kit GB-1201, \$99.95



8

### NEW 2-Way Telephone Amps

Amplified "talk" and amplified "listen", with or without dialer. Real hands-free convenience — use from 10' away. VOX control silently switches from built-in microphone to speaker without clipped words or feedback squeals. GD-1112 works with regular phone. GD-1162 with built-in dial and electronic ringer works like an extension phone. Easy to build, convenient for use at home or office. Kit GD-1112, \$49.95; Kit GD-1162, \$69.95.

HEATH Schlumberger	Heath Company, Dept. 20-11 Benton Harbor, MI 49022
<input type="checkbox"/> Please send my free new Heathkit Catalog. <input type="checkbox"/> Enclosed is \$_____ plus shipping. Please send model(s) _____	
NAME _____	
ADDRESS _____	
CITY _____	STATE _____ ZIP _____
<small>PRICES ARE FACTORY MAIL ORDER, FOB PRICES &amp; SPECIFICATIONS SUBJECT TO CHANGE WITHOUT NOTICE.</small>	
CL-575	



Circle 100 on reader service card

# State of SOLID STATE

by **KARL SAVON**  
SEMICONDUCTOR EDITOR

THAT NEW ELECTRONIC CASH REGISTER at the downtown department store has a heart of silicon. Microcomputers are taking over the number shuffling and inventory tasks at the checkout counter. Hidden by familiar equipment, the microcomputer also controls some of those "smart" multiple-way traffic signals. They flex with changing traffic  
*(continued on page 26)*

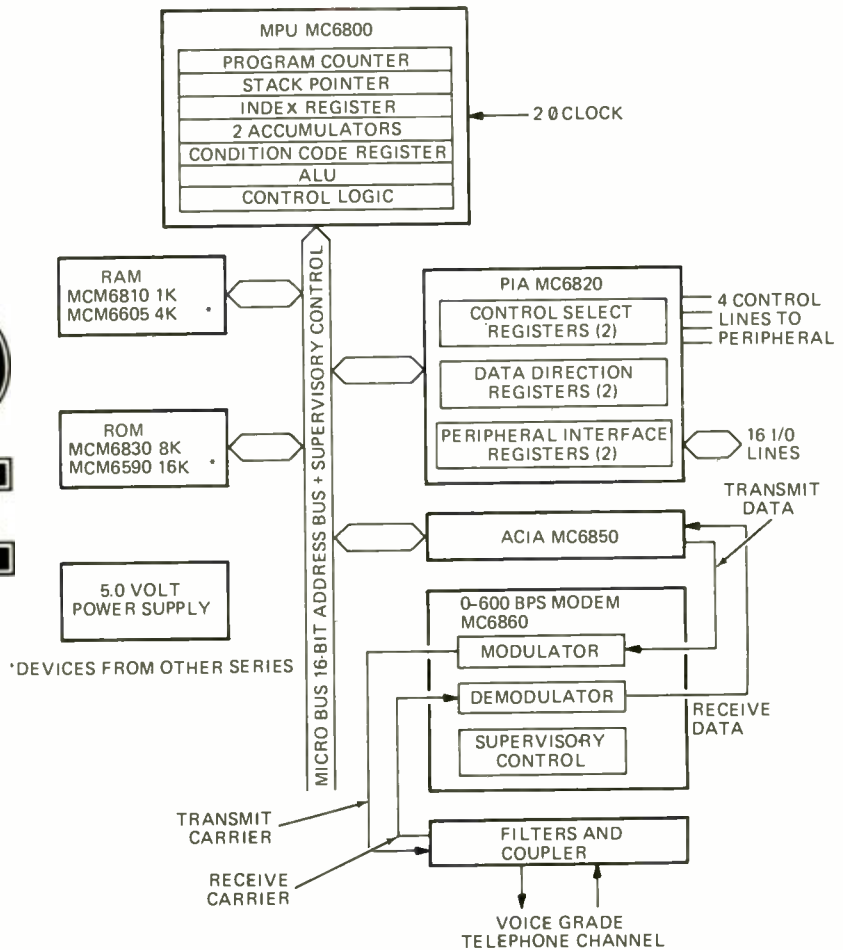


FIG. 1—MOTOROLA'S M6800 microcomputer system.

**PIX  
FIX**



Suggested price  
**\$249.90**

## The new Triple-Threat renewer.

RCA's unique WT-333B is 3 ways better than conventional picture tube tester/renewers.

It puts 3 proven methods of cathode-emission renewal at your finger tips: *High current Pulses. Steady Direct Current Flow. Elevated Heater Voltage.*

It helps solve your picture tube problems in 3 easy steps: *Determines if tube is actually the source of set trouble and isolates fault by testing under simulated picture conditions. Repairs shorts, cleans blocked grid apertures, welds cathodes, renews cathode emission — where possible. Tests quality level of repairs.*

The WT-333B also compares all three guns of color tubes simultaneously with exclusive Simul-Test 3-meter system. You get quantitative, meaningful and instant indication of tube condition and renewal.

You can buy the new WT-333B with PIX-FIX at any one of the more than 1,000 RCA Distributors worldwide. Or for further information, contact RCA Distributor and Special Products Division, Bldg. 206-2, Cherry Hill Offices, Camden, N.J. 08101 (Phone 609-779-5715).

**RCA** Electronic Instruments

# LIVE IN THE WORLD OF TOMORROW... TODAY!

And our FREE 164 PAGE CATALOG is packed with exciting and unusual values in electronic, hobby and science items — plus 4,500 finds for fun, study or profit... for every member of the family.

## A BETTER LIFE STARTS HERE

### WORLD'S SMALLEST CALCULATOR!

Small but mighty! 8-digit, 4-function electronic calculator does everything big ones do—even has automatic % key... for only \$19.95. Take it anywhere. Fits in your pocket—1/3 size of cigarette pack. 2-oz. dynamo features floating decimal, constant key, lead zero depression, more! Operates on two 1.5v Mallory PX 825 camera batteries (included). 2 x 2.8 x 0.4" with plenty of room for most fingers. Another Edmund first with advanced technology.



No. 1945EH ..... \$19.95 Ppd.

### RUN A WORKING STEAM ROLLER!

Authentic English hand-crafted model made of heavy-gauge metal, powered by steam so you can run it forward, backward, regulate speed, pull other models, lock roller and run engine independently. Just set steering or use the 12" extension steering rod and drive it yourself! The fun even includes a traditional black chimney for the exhaust, which can power the mighty whistle. To run, fill the safe vaporizing spirit lamp w/wood alcohol (not incl).



No. 71,934 EH (4 lb.; 10 1/4 x 6 x 7") ..... \$44.50 Ppd.

### PRO ELECTRONIC SOUND CATCHER

Parabolic mike w/ 18 3/4" transparent reflecting shield & 2 I.C.'s in amplifier magnifies signals 100x that of omni-direction mikes. Catch sounds never before heard! Highest signal to noise ratio poss. Earphones, tape recorder output, tripod socket; req. two 9v trans, batt. (not incl).



No. 1649EH (5 1/2 LB.) ..... \$299.00 Ppd.

LOW COST MODEL: NO EARPHONES, ELECTR. CIRC. No. 1665 EH ..... \$199.95 Ppd.

LOWER SENSITIVITY ECON. MOD. W/O ELECTR. No. 80,242 EH ..... \$89.50 Ppd.

### AN ALPHA MONITOR FOR \$34.95?

Yes, because you built it! Use your ability to tune in your brainwaves, an aid to relaxation, concentration. Kit incl. everything you need (except 9v trans. batt.) to own a portable self-cont. BIOFEEDBACK unit for a pittance; steth. earphones, electrode headband, solid-state circuitry; 5 microvolt sensitivity, more! Compl. assembly instructions & op. manual. With basic electronics knowledge, you can do it!




No. 61,069 EH (KIT) ..... \$34.95 Ppd.

No. 71,809 EH (FULLY ASSEMBLED) ..... \$55.00 Ppd.

WHEN YOU COME TO PHILADELPHIA BE SURE TO SEE  
**FREE BICENTENNIAL LIGHT SHOW**  
IN BARRINGTON, N.J. ONLY 10 MINUTES AWAY AT  
**EDMUND FACTORY STORE**


### NEW! AUTOMATIC TIME-LAPSE PIX

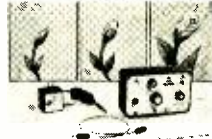

Terrific bargain! Under \$200! Compares w/others at \$450-\$700. Get fabulous time/motion shots with the versatile 37-ounce portable Edmund Time Machine. Converts almost any camera to a total time lapse system. Comes w/20" cable release for socket cameras 20" electric cable for electronic remote or single frame socket types. Continuous variable interval from 0.5 to 300 seconds; built-in photo-cell control, more! Rechargeable power supply.

No. 72,122 EH (6 x 3 1/2 x 2") ..... \$199.95 Ppd.

### TOTAL KIRLIAN PHOTOGRAPHY SET

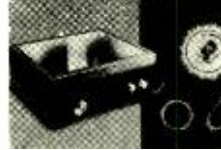

Explore "aura" photography w/ superb new self-contained Kirlian Electrophotography Research Unit. Terrific value — introduced at \$99.95 (\$140 in Sept.)! Has everything but vinyl photo changing bag. Ideal for color or b/w 35mm, sheet or Polaroid film for photos up to 5x7" all without camera or lens. Variable voltage 12v to 32kv. Ultimate safety design—fully encased in plastic; patented electronics. Instrs.

No. 72,104 EH (3x5 1/4 x 7 1/4") ..... \$99.95 Ppd.

No. 42,240 EH (CHANGING BAG) ..... \$6.50 Ppd.

### LOW COST 7X INFRA-RED VIEWER




For Infra-red crime detection surveillance, security system alignment, I.R. Detection, laser checking, nite wildlife study, any work req. I.R. detection & conv. to visible spectrum. Self cont. scope w/everything incl. I.R. light source, 6v or 12v power, 6032 I.R. converter tube, f/4.5 objective lens, adjust. triplet eyepiece. Focuses from 10' to infinity.

No. 1659 EH (11x14 1/4 x 3") ..... \$275.00 Ppd.

WITHOUT LIGHT SOURCE No. 1648 EH ..... \$225.00 Ppd.

### BUILD THIS COMPUTER, SAVE \$27

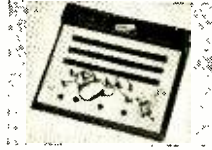

Assembled, our amazing electronic digital computer is \$45. New kit lets you build it for almost 1/3 that! Easy to program, fun to operate; solve problems, play games, try to outwit it. Program it, give it problems, get results from electronic readout. Quickly learn "what makes a computer tick," how to program, soon program w/your problems, data. 14 x 15" unit has 3 movable registers, patch cords & plugs; 2 manuals, cards, dice. Req. 3 AA batts., soldering.

No. 72,105 EH (HI-IMPACT PLASTIC) ..... \$17.95 Ppd.

### ELECTRONIC DIGITAL STOPWATCH: \$69.95



A price breakthrough! New pocket size 4 oz. timer acc. to ± 2% of last digit (1/100 sec. increments). Compares with others twice the price! Instant error-free read-outs to 9999.99 sec. (over 2 3/4 hr.). Starts, stops, re-starts (accumulates). Mechanical pushbutton & electrical remote on/off w/ any 3.5-150v AC/DC source. Plug-in jack. Incls. 9v batt. Solid state.

No. 1943 EH (2 1/4 x 4 1/2 x 7 1/8") ..... \$69.95 Ppd.

DELUXE 2 EVENT STOPWATCH (± 0.01% OF LAST DIGIT) No. 1653 EH ..... \$149.95 Ppd.

## MAIL COUPON FOR GIANT FREE CATALOG!

164 PAGES • MORE THAN  
**4500 UNUSUAL BARGAINS**

Completely new 1976 edition. New items, categories, illustrations. Dozens of electrical and electromagnetic parts, accessories. Enormous selection of Astronomical Telescopes. Unique lighting and ecological items. Microscopes, Binoculars, Magnifiers, Magnets, Lenses, Prisms. Hard-to-get surplus bargains, ingenious scientific tools, 1000's of components.

**EDMUND SCIENTIFIC CO.**  
300 Edscorp Building, Barrington, N.J. 08007  
Please rush Free Giant Catalog "EH".

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_



COMPLETE AND MAIL WITH CHECK, M. O. OR CHARGE NO.

**EDMUND SCIENTIFIC CO.** 300 Edscorp Building, Barrington, N.J. 08007

How Many	Stock No.	Description	Price Each	Total

PLEASE SEND GIANT FREE CATALOG "EH"

Charge my BankAmericard

Charge my Master Charge \* Add Handling Chg.: \$1.00, Orders Under \$5.00 50¢, Orders Over \$5.00

Interbank No.

My Card No. Is

Card Expiration Date

**30-DAY MONEY-BACK GUARANTEE.** You must be satisfied or return any purchase in 30 days for full refund. \*\$15.00 minimum


Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Signature \_\_\_\_\_

I enclose  check  money order for TOTAL \$ \_\_\_\_\_

Circle 9 on reader service card

www.americanradiohistory.com

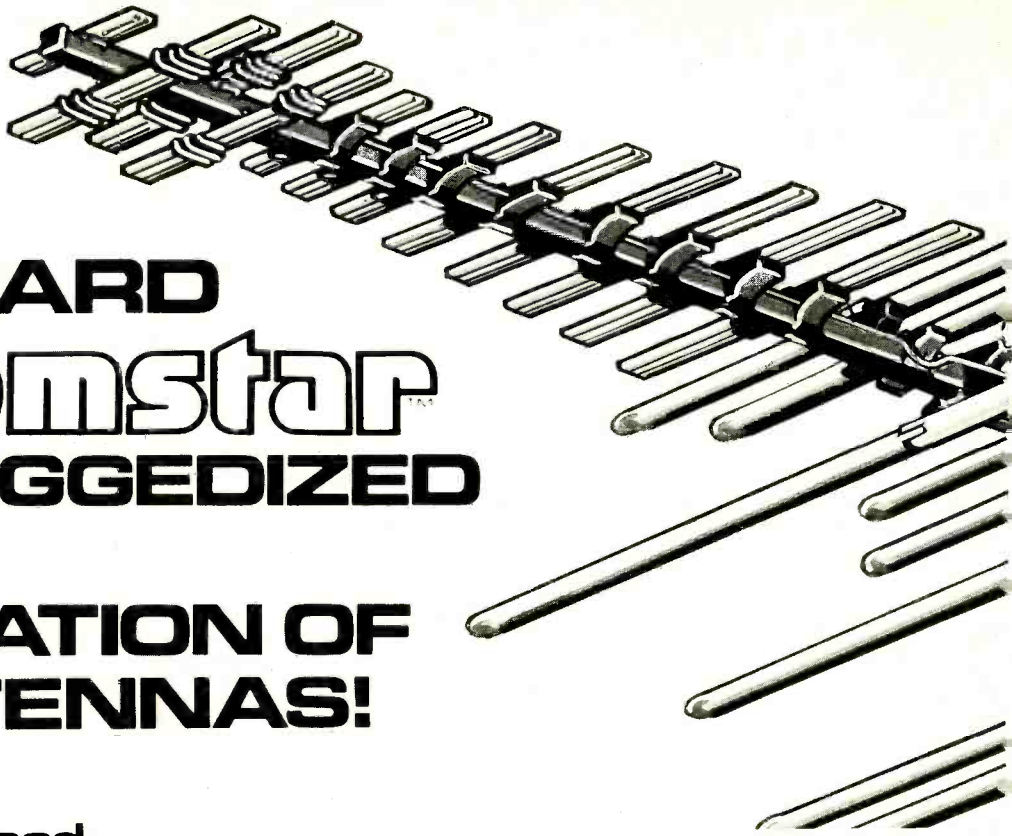

# WINEGARD Chromstar™ THE RUGGEDIZED NEW GENERATION OF TV ANTENNAS!

**40 Models  
With Far-Ahead  
Features For  
Finest Color  
Reception Ever!**

**Ask your distributor  
for complete information!**

- New Standard Of Excellence In Construction And Performance.
- Anodized and Ruggedized for Weather Protection and Long Life.
- Models To Solve Every Area Reception Problem.
- Most Powerful UHF and VHF Performance Ever.
- New Tri-Linear UHF Director System Extends UHF Reception Distance Up To 30 Miles Farther From Station in Many Areas.

**PLUS...** New Generation FM Antennas.  
High Performance Ruggedized Yagis.  
New Solid State Preamplifiers.

## NEW TRI-LINEAR UHF DIRECTOR SYSTEM\*

Increases Gain up to 30%!

Provides broader signal capture area in a more compact configuration.

### ORDINARY UHF Director System.




5 1/2"

Uses half-wave directors approximately 5 1/4" long which respond primarily to the high end of the band, with very little gain on the low end.



55"

Boom length required for 12 directors

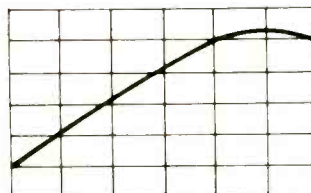


Typical gain curve with ordinary UHF directors. Note low response on low end of band.
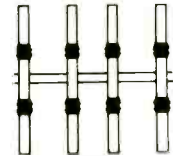
### WINEGARD High Gain Tri-Linear® Directors




15 1/4"

Act as 3 half-wave directors on the high end of the band, and re-resonate as a loaded half-wave director on the low end of the band. This results in high linear gain on all UHF channels, giving the antenna sharper directivity and up to 30% more gain over other high gain UHF antennas.



10"

Boom length required for 12 directors

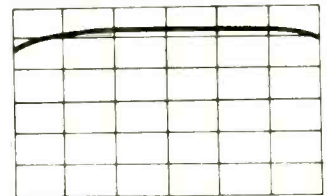

Typical gain curve with Winegard Tri-Linear directors. Note high uniform gain across entire band.




**WINEGARD**  
TELEVISION SYSTEMS

3000 KIRKWOOD  
BURLINGTON, IOWA 52601
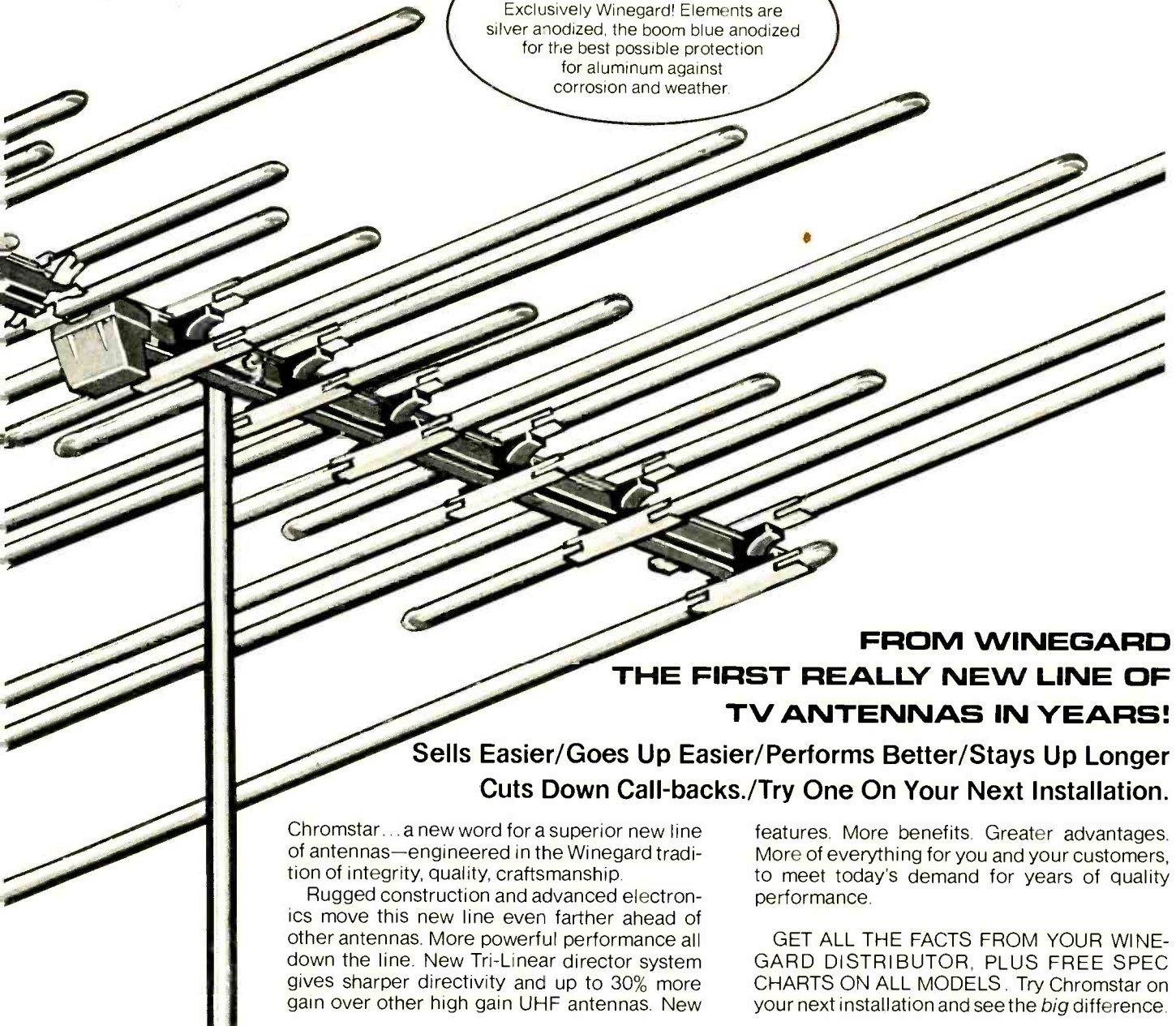
## ANODIZED!

Exclusively Winegard! Elements are silver anodized, the boom blue anodized for the best possible protection for aluminum against corrosion and weather.



## FROM WINEGARD THE FIRST REALLY NEW LINE OF TV ANTENNAS IN YEARS!

**Sells Easier/Goes Up Easier/Performs Better/Stays Up Longer  
Cuts Down Call-backs./Try One On Your Next Installation.**


Chromstar... a new word for a superior new line of antennas—engineered in the Winegard tradition of integrity, quality, craftsmanship.

Rugged construction and advanced electronics move this new line even farther ahead of other antennas. More powerful performance all down the line. New Tri-Linear director system gives sharper directivity and up to 30% more gain over other high gain UHF antennas. New


features. More benefits. Greater advantages. More of everything for you and your customers, to meet today's demand for years of quality performance.

GET ALL THE FACTS FROM YOUR WINEGARD DISTRIBUTOR. PLUS FREE SPEC CHARTS ON ALL MODELS. Try Chromstar on your next installation and see the *big* difference.

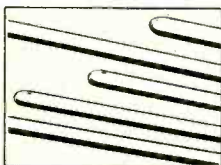
**RUGGEDIZED!** Chromstar antennas are designed to defy weather and wear—are engineered for extra strength at all points of stress. You can actually see the difference in the rugged construction.



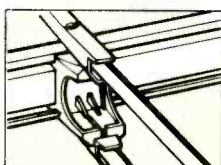
Exclusive 7/8" diameter aluminum tubing for 30% greater strength, better performance, longer life. Winegard is the first and only manufacturer to use this larger diameter.



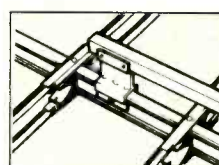
New truss-type phasing bars, top and bottom, with more conductive surface, give maximum transfer of signal. Truss-type "bridge" construction more than doubles boom strength.



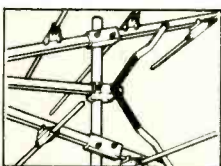
Double boom on longer flat line models for extra strength & rigidity.



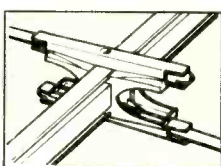New scissors-type struts between upper and lower booms and center boom on wedge models, for extra support, easier installation.



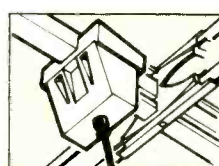High-impact girder design support insulators are moulded of super-tough Noryl G-E plastic. Four positive locks give maximum support and permanent alignment.



Critical-point weather protection! \*New compact weatherproof cartridge housing for downlead preamplifiers and filter modules. New printed circuit downlead module with both twin lead and 75 ohm coax connections. No separate matching transformer required.


## TV ANTENNAS MORE PEOPLE LOOK UP TO

Circle 10 on reader service card

# NOW . . . at a price that's right!
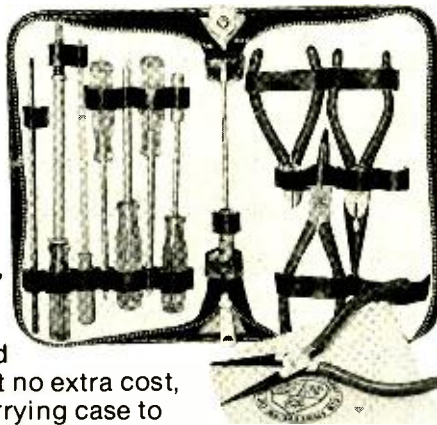
## "Technician-TOUGH" Electronics TOOL SET

Designed to stand up  
under rugged  
on-the-job-use.



Technician-tough, quality-crafted, 12-piece tool set. Tools you need. Tools you'll use over and over again for electronics assembly and troubleshooting work. Included, at no extra cost, a custom-made vinyl, zippered carrying case to put an end to that pain-in-the-neck fumbling around in your bag for the right tool . . . PLUS a specially-treated cloth to clean and polish your tools.

**4 Pliers . . . .** Curved Needle-Nose, Flush Diagonal Cutter, Long-Nose, Long Needle-Nose. All drop-forged, heat-treated cutting edges, vinyl insulated grips for shock-free, non-skid performance.

**6 Screwdrivers . . . . .** "One-Touch", Plastic Alignment, 2 Phillips (7 $\frac{1}{8}$ ", 8 $\frac{1}{8}$ "), 2 standard (6", 7 $\frac{1}{8}$ "). All blades are nickle-plated steel, solidly fixed in shock resistant plastic handles.

**Plus Nut Driver . . . . .** Forged hollow shaft allows greater versatility. Lightweight. Easy to use.

**Plus Flat File . . . . .** Precision-hardened. Smooths the roughest, toughest surfaces.

The right tools for the jobs you're faced with. The right tools to help make your work easier, more efficient, more organized.

Order your set TODAY and qualify for this special BONUS offer.

**BONUS OFFER** Order now and receive a one-year FREE subscription to the bi-monthly *CIE Electron* newspaper. Packed with timely, thought-provoking electronics articles— new developments — service tips — job opportunities. Free with each order.

**You must be completely satisfied or return the material within 10 days for a complete — no questions asked — refund.**

**RUSH** me your CIE Tool Set, and put me down for a FREE one-year subscription to the *CIE Electron*.

#01-100 (CIE Tool Set) **\$24.95** (Ohio Res. add 4 $\frac{1}{2}$ % Sales Tax)

Enclosed is my . . .  Check  Money Order BC-14-75

Print Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_ Apt. \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

**CIE Bookstore**

1776 E. 17th Street • Cleveland, Ohio 44114

Educational Entertainment values by mail

Subsidiary of Cleveland Institute of Electronics Inc

Circle 11 on reader service card

## STATE-OF-SOLID-STATE

(continued from page 22)

patterns and shorten the wait on secondary roads when the traffic permits.

But the real potential of the "computer on a chip" is just beginning to be realized. "Micro" may tell something about the size of the machine, but some of the best things come in small packages. Microcomputers are replacing conventional logic designs. Chip count of complex logic systems can often be reduced ten fold or more. And microcomputers are starting to show up in general purpose minicomputers. This time the prefix "mini" is misleading since many minicomputers outflank their big brothers of a few years ago in both price and performance. The general purpose computer, no matter what its prefix, will probably be a common household fixture in about ten years. Even sooner, dedicated microcomputer systems will control home heating and automotive systems.

So you see, microcomputers fall into two basic user categories—dedicated preprogrammed controllers, and more general user programmed types. Many of the specially programmed units do not operate at high speeds. On the other hand, high speed is a definite advantage in the general purpose computer. If you've spent any time with scientific calculators you know that the calculation time for trigonometric and logarithmic functions can run into seconds. Iterative series evaluation of algorithms proceed step after step until the calculation error falls below a preset level. In a computer, thousands of steps transpire during relatively simple procedures.

Motorola has a microcomputer system with an architecture aimed at both these categories. It runs towards the higher end of the speed range and is relatively easy to program.

### Motorola M6800 microcomputer system

Like some other microcomputer systems, the M6800 is actually a series of IC's: the MC6800, MCM6810, MC6820, MCM6830, MC6850, and the MC6860. Motorola has chosen not just to build a single microprocessor chip but to support an entire complementary system. Five of the circuits are already available and the sixth should be on the market about the time you read this. The circuits fit together in the neat organizational plan shown in Fig. 1. The whole computer works from a single 5 volt power supply for economy, pin utilization, and compatibility with TTL and CMOS logic. There are also some preexisting 5 volt static memories. MOS N-Channel Silicon Gate processing is used throughout.

(continued on page 32)



# Another introductory offer to new members of the ELECTRONICS AND CONTROL ENGINEERS' BOOK CLUB

	404/445 <b>ELECTRONIC CIRCUITS MANUAL</b> by J. Markus Pub. price, \$22.00 Club price, \$15.75		286/515 <b>INTEGRATED CIRCUITS: A Basic Course for Engineers and Technicians</b> by R. G. Hibberd Pub. price, \$10.25 Club price, \$8.45
	637/458 <b>DESIGNING WITH TTL INTEGRATED CIRCUITS</b> by Texas Instruments Inc. Pub. price, \$19.50 Club price, \$13.50		100/810 <b>MOS/LSI DESIGN AND APPLICATION</b> by Carr & Mize Pub. price, \$18.50 Club price, \$13.50
	404/437 <b>SOURCEBOOK OF ELECTRONIC CIRCUITS</b> by J. Markus Pub. price, \$21.50 Club price, \$17.50		388/458 <b>MAGNETIC RECORDING</b> by C. E. Lowman Pub. price, \$14.50 Club price, \$9.75
	389/756 <b>SEMI-CONDUCTOR MEMORY DESIGN AND APPLICATION</b> by Texas Instruments Inc. Pub. price, \$18.50 Club price, \$13.75		287/341 <b>STANDARD HANDBOOK OF ENGINEERING CALCULATIONS</b> by T. G. Hicks Pub. price, \$19.50 Club price, \$14.25
	491/364 <b>THE DESIGN OF DIGITAL SYSTEMS</b> by J. B. Peatman Pub. Price, \$18.50 Club Price, \$12.95		124/035 <b>HANDBOOK OF PHYSICS, 2/e</b> by Condon and Odishaw Pub. price, \$37.45 Club price, \$14.95
			238/901 <b>APPLICATIONS OF OPERATIONAL AMPLIFIERS</b> by J. G. Graeme Pub. Price, \$16.00 Club Price, \$10.50
			649/170 <b>OPERATIONAL AMPLIFIERS</b> by Tobey, Graeme & Huelsman Pub. price, \$15.00 Club price, \$11.50
			353/387 <b>MINICOMPUTERS FOR ENGINEERS &amp; SCIENTISTS</b> by G. Korn Pub. price, \$17.75 Club price, \$10.50
			209/731 <b>STANDARD HANDBOOK FOR ELECTRICAL ENGINEERS, 10/e</b> by Fink and Carroll Pub. Price, \$38.50 Club Price, \$28.50

**ANY ONE**  
of these great professional books  
for only **\$1.00**  
VALUES FROM \$8.45 to \$37.45  
Special \$1.00 bonus book comes to you with your first club selection

## Save time and money by joining the Electronics and Control Engineers' Book Club



HERE is a professional club designed specifically to meet your day-to-day engineering needs by providing practical books in your field on a regular basis at below publisher prices.

**How the Club operates:** Basic to the Club's service is its publication, the *Electronics and Control Engineers' Book Club Bulletin*, which brings you news of books in your field. Sent to members without cost, it announces and describes in detail the Club's featured book of the month as well as alternate selections which are available at special members' prices.

When you want to examine the Club's feature of the month, you do nothing. The book will be mailed to you as a regular part of your Club service. If you prefer one of the alternate selections—or if you want no book at all for that month—you notify the Club by returning the convenient card enclosed with each *Bulletin*.

As a Club member, you agree only to the purchase of four books over a two-year period. Considering the many books published annually in your field, there will surely be at least four that you would want to own anyway. By joining the Club, you save both money and the trouble of searching for the best books.

### MAIL THIS COUPON TODAY

**ELECTRONICS AND CONTROL ENGINEERS' BOOK CLUB**  
582 Princeton Road, Hightstown, New Jersey 08520

Please enroll me as a member of the Electronics and Control Engineers' Book Club and send me the two books indicated below. I am to receive the higher priced of the two for just \$1, and my first selection at the special Club price. Actual postage, plus 25¢ handling charge will be added (sales tax, also, if applicable). These books are to be shipped on approval, and I may return them both without cost or further obligation. If I decide to keep the books, I agree to purchase as few as four additional books (including this first selection) during the next two years at special Club prices (guaranteed 15% discount, often more).

Write Code No. of  
bonus book  
here

Write Code No. of  
first selection  
here

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

E33282

NOVEMBER 1975

Circle 12 on reader service card

# Learning with CIE is



# Electronics no picnic.

**It takes work.  
And a few  
sacrifices.  
But  
it's worth it!**

The minute you start your CIE course you'll see why CIE is different than other home-study schools.

Because as a CIE student you'll get the kind of electronics training that prepares you for a career, not just a job. We'll give you a meaningful, well-rounded foundation in electronics theory and practice. And with our special Auto-Programmed® Lessons, we'll make sure you grasp the key theories and methods of modern Electronics. No "fun and games" frills. No time-wasting, superficial lesson material. No "snap" exams.

We'll challenge your thinking.

We have to. Because after you graduate, employers will expect you to really know how to analyze and troubleshoot virtually all kinds of electronics equipment. Some employers of electronics personnel have told us that our graduates have what it takes.

That's why we're so thorough. We've got a 40-year reputation to uphold and we're going to keep it by giving our students the best *independent home-study* training we can.

Sure, some of our weaker students drop out. (Learning Electronics with CIE is no free ride.) But you can bet on this... the ones who do make it are ready! Ready to go out and make it in the rewarding world of Electronics. And that's the reason you want to learn, isn't it?

## **You can have attractive job opportunities**

There have already been many exciting developments and breakthroughs in

Electronics and some people might assume there will be no new frontiers... no new worlds to conquer. Not so.

Electronics is still growing. In nearly every one of the new and exciting fields of the Seventies you'll find electronics skills and knowledge in demand. Computers and data processing. Air traffic control. Medical technology. Pollution control. Broadcasting and communications.

### **Importance of an FCC License**

If you want to work in commercial broadcasting... television or AM or FM broadcasting... as a broadcast engineer, federal law requires you to have a First Class Radiotelephone License. Or if you plan to operate or to maintain mobile two-way communications systems, microwave relay stations or radar and signaling devices, a Second Class FCC License is required.

But even if you aren't planning a career which involves radio transmission of any kind, an FCC "ticket" is valuable to have as Government certification of certain technical skills. It's a job credential recognized by some employers as evidence that you know your stuff.

A good way to prepare for your FCC License exam is to take one of the CIE career courses which include FCC License preparation. We are confident you can successfully earn your license, if you're willing to put forth an effort,

because the vast majority of CIE students have. In fact, based on continuing surveys, close to 9 out of 10 CIE graduates have passed their FCC exams!

So if you are serious about getting ahead in Electronics... if you are willing to put in the extra work... get in touch with us.

We have many *career* courses for you to select from. If you already have some electronics training, you may want to skip our beginner-level courses and enroll in an intermediate program. Or, if you're really hot, there's a tough, college-level course called "Electronics Engineering" that can make you even better.

### **Send today for FREE school catalog**

Send today for our FREE school catalog and complete package of *independent home-study* career information. For your convenience, we will try to have a representative call to assist in course selection. Mail reply card or coupon to CIE... or write: Cleveland Institute of Electronics, Inc., 1776 East 17th Street, Cleveland, Ohio 44114.

Do it TODAY.

### **G.I. Bill Benefits**

All CIE career courses are approved for educational benefits under the G.I. Bill. If you are a Veteran or in service now, check box for G.I. Bill information.

## **CIE** **Cleveland Institute of Electronics, Inc.**

1776 East 17th Street, Cleveland, Ohio 44114

Accredited Member National Home Study Council

Yes, I want your FREE school catalog and career information package today.

I am especially interested in:

- |  |  |       |
|--|--|-------|
| <input type="checkbox"/> Electronics Technology  | <input type="checkbox"/> Industrial Electronics  | RE-60 |
| <input type="checkbox"/> FCC License Preparation | <input type="checkbox"/> Electronics Engineering |       |
| <input type="checkbox"/> Color TV Maintenance    | <input type="checkbox"/> Other _____             |       |
| <input type="checkbox"/> Mobile Communications   | _____  |       |

Print Name \_\_\_\_\_

Address \_\_\_\_\_ Apt. \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_ Age \_\_\_\_\_

Check box for G.I. Bill information.  Veteran  On Active Duty

Circle 13 on reader service card

## STATE-OF-SOLID-STATE

(continued from page 26)

Motorola's Micro Bus is a universal bus system where all communications between system components takes place over the same set of wires. It is an approach being used by a number of the minicomputer manufacturers with success. The M6800 strongly resembles Digital Equipment's well known PDP-11 minicomputer. Input and output functions are similar to memory instructions. Peripheral devices are addressed as part of a total 65K word address space.

Computer systems are designed



MOTOROLA MC6800 CPU

around a CPU (Central Processing Unit). The CPU for the M6800 is the MC6800 chip. It contains the control logic to sequentially fetch instructions from memory and decode each of a set of 72 instructions. Each instruction can either be 1, 2 or 3 bytes long. One byte is an 8-bit word. The CPU gener-

ates control signals to carry out logic, shift, memory reference, skip, and arithmetic instructions.

Arithmetic operations are carried out in two's complement or decimal formats. Two's complement is a binary number system widely adopted by the computer industry partly because of the ease of converting to negative numbers. A positive number that is complemented simply by changing all zeros to ones and ones to zeros, and then incremented by 1 becomes a negative number. There are also interrupt instructions that peripherals can use to direct the computer to jump to programmed service routines.

Interrupt programming lets the computer to continue with its business during the time it takes a printing device such as a teletype to print a character. "Push-down" and "pop-up" instructions take care of an assigned portion of memory called a stack where return addresses are stored and reclaimed during execution of nested subroutines.

CPU's use registers to keep track of things and help do arithmetic. The MC6800 has six. A 2-byte (16-bit) program counter increments its contents to select the next instruction from the program stored in memory. The increments are unity except when multiple word instructions or jump instructions are used. A jump instruction inserts the calculated address portion of the instruction into the program counter causing the next instruction to come from the "jumped to" address. Another two-byte register holds the stack pointer, the address of the next available location in the stack. The third two-byte register is the index register used to index or add to the address in a memory reference instruction. This addressing mode is useful in list processing. The remaining three registers are a single-byte in length. Two are accumulators that operate with the ALU (Arithmetic and Logical Unit) portion of the CPU. A condition code register holds sign and overflow information used for conditional branching decisions.

Addressing modes are an important consideration in overall programming. Beginning programmers may be surprised at the large program segments used to calculate addresses. The number of instructions alone is a poor guide to programming ease and efficiency. A better indicator is the number of steps required to carry out benchmark procedures. The MC6800 has a wide assortment of addressing modes, seven in all—direct, relative, immediate, indexed, extended, implied, and accumulator.

Memory is an essential part of any computer system. Both the data and program steps are stored in memory.

(continued on page 34)

**Beautiful Enough  
To Grace  
A Jeweler's Window**

... and the real beauty of these CHANNELLOCK Little Champs is the way they ease hundreds of delicate, fine jobs that need firm treatment. Precision made of highest grade forged steel. High luster polished finish. Perfectly mated, hand honed cutters. Blue dipped plastic comfort grips. Specify CHANNELLOCK Little Champ precision pliers. You'll like 'em. Send for our free Catalog. CHANNELLOCK, INC., Meadville, Pa. 16335

**CHAN NEL LOCK**

Little Champ Precision Pliers

Circle 14 on reader service card

# 4K Computer!



## Still, our price goes down a lot easier.

Now's your chance to bite into a complete computer system. We at SPHERE CORPORATION have used the latest micro-processing technology along with some real innovations in mini-circuit design to develop the lowest-cost complete computer systems available. Every system comes complete with TV CRT display, ROM monitor, a real time clock, and typewriter, cursor editing, and numeric keyboards. Every SPHERE SYSTEM has ample memory to run YOUR particular program, whether it's a complicated inventory control system, or keeping detailed track of finances, or monitoring and protecting your home or office . . . use your imagination! And SPHERE offers manuals with plenty of information for the

first-time computer users. In addition, every SPHERE SYSTEM is expandable as desired. It will run an extended BASIC compiler and/or a most complete line of peripherals. All systems come with complete usage, programming, and application manuals, as well as software supports to make its functions almost limitless. We wanted to make something a lot better; and we did!

The mail order offer you see here is limited. Take advantage of it! If you like, also inquire about our full color graphics CRT display, and SPHERE's most complete line of low-cost peripherals on the market today. Use the coupon below right away!

### We make the difference count.


SPHERE CORPORATION  
791 South 500 West #6  
Bountiful, Utah 84010  
(801) 295-1368

Dear SPHERE:  
The facts I read here convinced me!

Enclosed is my check or money order for \$860.00. Please rush me a SPHERE I System.

Please rush me more details on your low-cost computer system and peripherals. (Specific questions, if any, are attached.)

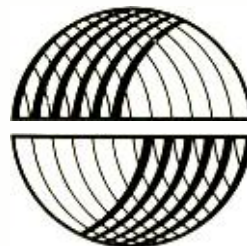Print Name: \_\_\_\_\_  
Address: \_\_\_\_\_  
City: \_\_\_\_\_  
State, Zip: \_\_\_\_\_




# SPHERE

SPHERE CORPORATION 791 South 500 West #6  
Bountiful, Utah 84010 (801) 295-1368
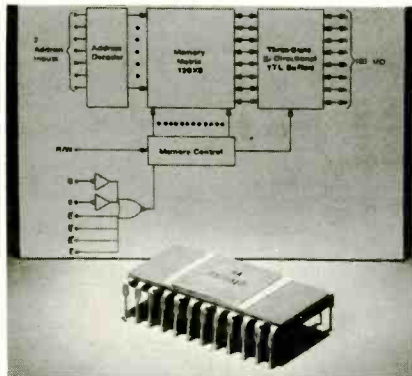
## STATE-OF-SOLID-STATE


(continued from page 32)

Random-access memory, read-only memory, or a combination of both are used in any one system. RAM's are the most versatile but are more expensive and often slower than ROM's. The MC6800 series includes the MCM6810 128 × 8 bit static-RAM and the



MOTOROLA MC6810 128 × 8 BIT RAM

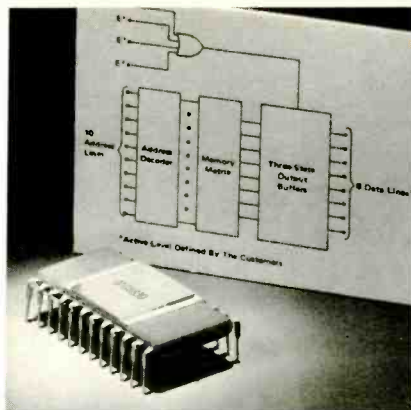
MCM6830 1024 × 8-bit ROM. General purpose machines have a large amount of random-access memory since they must handle any conceivable program that the user wants to store. In contrast, the task dedicated machine often only has to follow a single pro-



MOTOROLA MC6830 8K ROM

gram permanently stored in its ROM. The MCM6830 8K static ROM does not have clock or refresh inputs. Maximum read-access-time is 575 nanoseconds. The MCM6810 1K RAM is also a static memory and is neither clocked nor refreshed. The MCM6810 is available in two versions; the L unit has a maximum access-time of 1 microsecond and the L-1, 600 nanoseconds. Larger sized RAM's are predominantly dynamic and slower since the stored bit charges leak off with time and must be systematically rewritten. Both memory chips have three-state outputs. They can be paralleled and then enabled one at a time by select inputs.

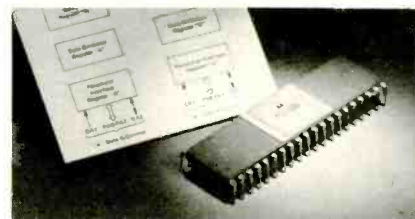Motorola calls the MC6820 Peripheral Interface Adapter (PIA) the articulate interface. The PIA eliminates much ancillary logic when interfacing many peripherals. By making the pe-



MOTOROLA MC6820 PERIPHERAL INTERFACE ADAPTER

ripherals addressable like memory, the device can be programmed by the user to meet a wide range on input and output applications. The MC6820 is a 16-bit parallel interface that lets the computer interconnect with devices such as keyboards, magnetic disks, and cartridges, CRT displays and terminals, numerical control equipment—anything you want the computer to control or be controlled by. The bus connections between the CPU and any PIA is 8-bits and bi-directional. Peripherals connect to the PIA on two 8-bit bi-directional busses. Any of the 16 lines can be programmed as an input or output of the adapter. (There are four addi-

*(continued on page 97)*

### 10MHz 5" scope with easier calibration and voltage measurement



Model 1465 \$428

Here are some B&K extra touches. Besides DC-to-10MHz bandwidth, triggered sweep, automatic sync, 16.6mV/cm vertical sensitivity, DC-coupled amplifier and front-panel Vectorscope capability, Model 1465 also has 5X magnification to increase sweep speed to 0.2usec/cm for complex waveform analysis. And Cali-Brain®, which collapses horizontal sweep to let you measure instantaneous peak-to-peak voltage easily while simultaneously displaying the full-scale voltage range. Now in stock at your local distributor or write Dynascan.

**B&K** PRODUCTS OF  
**DYNASCAN**

1801 W. Belle Plaine Ave.  
Chicago, IL 60613 • (312) 327-7270

Circle 16 on reader service card

### You'd probably expect a portable oscilloscope as rugged and reliable as this one to cost a lot.

**You'd be wrong.**

Introducing the B&K Model 1403 3" Solid-state oscilloscope. It's so compact, reliable, and inexpensive that it's the perfect scope for most on-the-line monitoring applications. Look at its specs: DC to 2MHz bandwidth at 20mV/cm. Recurrent sweep speeds from 10Hz to 100k Hz. New wide-angle CRT to reduce case depth to a minimum. Direct-deflection terminals for waveforms up to 150 MHz. Weighs only 8½ pounds. And has a smoked acrylic graticule for trace sharpness and easy reading. All the reliability and accuracy you need in a monitor scope — at a surprisingly low price.

Contact your distributor, or write  
Dynascan Corporation.


**\$189<sup>00</sup>**



**B&K** Very good equipment at a very good price.  
Dynascan Corporation.  
1801 West Belle Plaine Avenue, Chicago, Illinois 60613

Circle 17 on reader service card
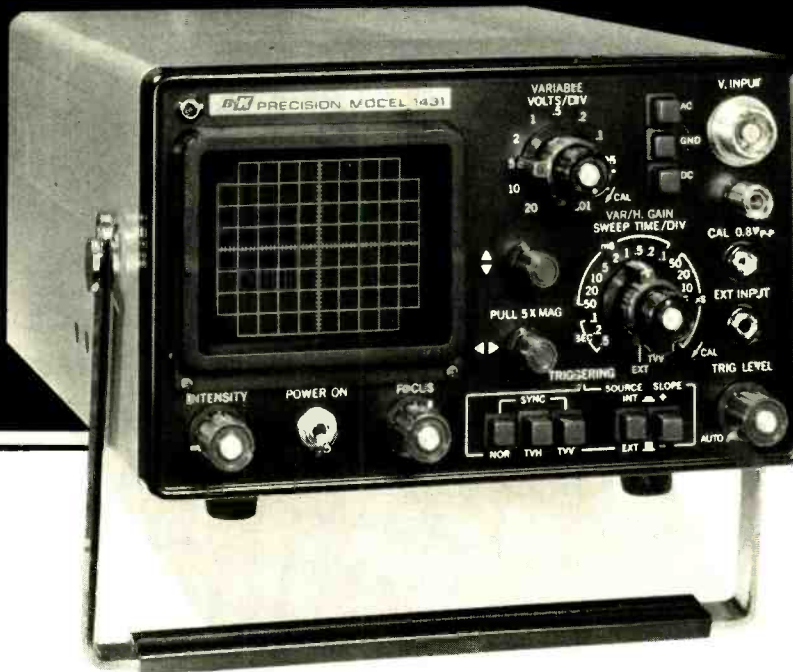
# This 10 MHz Triggered Scope is 1/3 the size of comparably performing scopes.



**MODEL 1431 \$399.00**

It's a lightweight 13 pounds in your hand and a heavyweight performance wideband scope with a 35 nanosecond rise time on your bench or jobsite. Whether you're servicing or designing industrial equipment or TV, there's the right sweep speed and sync for easiest operation. If you know our Model 1460, the leader in wideband 5" CRT scopes, you know our new 3" Model 1431 which gives you the same high performance in one third the size. (Only 4 $\frac{3}{4}$ " H x 7 $\frac{7}{8}$ " W x 12 $\frac{1}{2}$ " L)

Servicing, production, inspection, quality control and lab applications are all easier with this versatile all solid-state instrument. Triggering is accomplished with only 0.5V peak-to-peak. Ten millivolts per division sensitivity, 0.5 usec/cm to 0.5 sec/cm automatic and triggered sweep in 19 calibrated ranges, and external trigger input are just a few of the reasons you'll like it.

If you have been waiting to buy a portable scope until you could get all the features you'll ever need at a price you want to pay, you've been waiting for Model 1431. Contact your distributor or write Dynascan Corporation.




Shown with optional carrying cover and probe pouch.

**B&K** PRODUCTS OF  
**DYNASCAN**  
1801 W. Belle Plaine Ave.  
Chicago, IL 60613 • (312) 327-7270

Circle 18 on reader service card

# NEW!

## THE DESIGN MATE SERIES

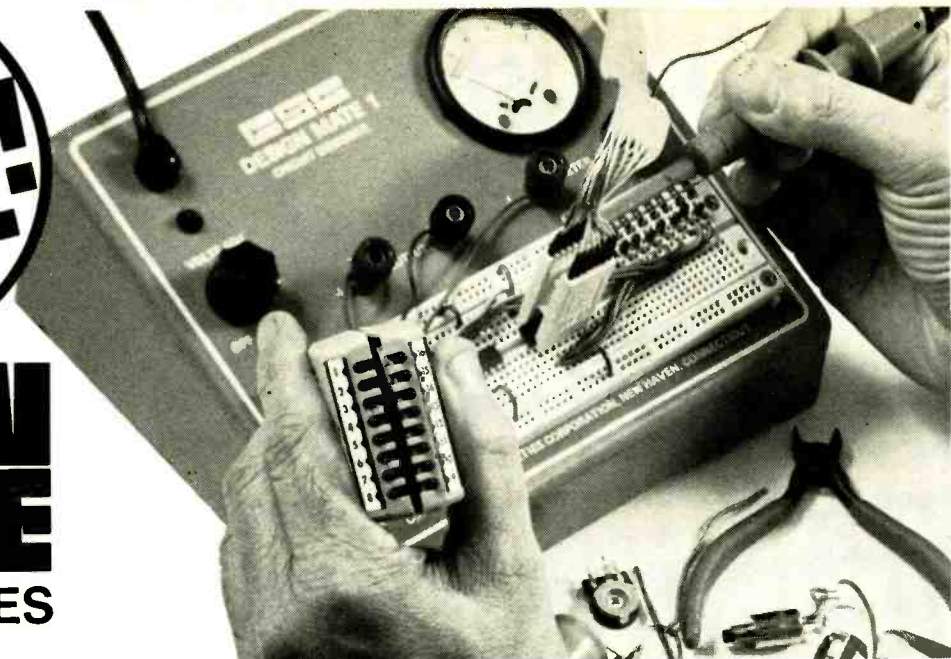

**At last! High quality, laboratory-grade test instruments . . . for the professional and hobbyist . . . at prices everyone can afford!**

### DESIGN MATE 1

**CIRCUIT DESIGNER**

Now you can build/test electronic circuits **WITHOUT SOLDER** . . . using solid #22 AWG wire to interconnect discrete components . . . resistors, transistors, linear/digital ICs in TO5 or DIP packages (8-40 pins), and more. Plus, you get 5-15VDC up to 600ma (9 watts) of variable regulated power, with a built-in 0-15V voltmeter to monitor internal power and/or external circuits. Now, that's design flexibility! And look at the low, low price!

**49<sup>95</sup>**

Add \$2.50 shipping/handling



#### SPECIFICATIONS

**Power Supply:** Output: 5-15V @ 600ma. **Ripple and Noise:** less than 20mv @ full load. Load/Line regulation: <1%. Meter: 0-15V DC. **Connectors:** 1 QT-59S, 2 QT-59B, 2 power supply 5-way binding posts, 2 meter 5-way binding posts. **Wght:** 3 lbs. **Power Needed:** 117V, AC @ 60 Hz 12W.\* **Patent #235,554.**

Each measures 6.75" L x 7.5" W x 3.25" H.; completely assembled, ready to start testing at once. Order your DESIGN MATES today!  
\*220V @ 50Hz available at slightly higher cost.

All DESIGN MATES are made in USA; available off-the-shelf from your local distributor. Direct purchases from CSC can be charged on Bank Americard, Master Charge, American Express. Plus, you get a FREE English/Metric Conversion Slide Rule with each order. Foreign orders please add 10% for shipping/handling. Prices are subject to change.

**64<sup>95</sup>**



Add \$2.50 shipping/handling

### DESIGN MATE 2

**FUNCTION GENERATOR**

Troubleshooting? Design Testing? DM-2 gives you all the signal source capacity you need . . . at a very modest price. This 3-wave form Function Generator has: short-proof output, variable signal amplitude and constant output impedance. Completely wired, tested, calibrated, ready to test audio amplifiers, op-amp and educational lab designs . . . as well as complex industrial lab projects. Complete with easy-to-read instructions/operations manual, application notes, operation theory and more, DM-2 works hand-in-hand with DM-1 for total versatility.

#### SPECIFICATIONS

**Frequency Range:** 1Hz-100KHz (5 ranges: 1-10Hz, 10-100Hz, 100-1000Hz, 1-10KHz, 10-100KHz). **Dial Accuracy:** Calibrated @ 10Hz, 100Hz, 1KHz, 10KHz, freq. accurate to 5% of dial setting. **Wave Forms:** Sine <2% THD over freq. range. **Triangle wave** linearity, <1% over range. **Square wave** rise/fall <0.5 microseconds — 600Ω-20p termination. **Output Amplitude:** (all wave forms) variable-0.1V-10V peak to peak into open circuit. **Output Impedance:** 600Ω-constant over ampli./freq. ranges. **Wght:** 2 lbs. **Power Needed:** 117V, AC @ 60Hz 5W.\*

### DESIGN MATE 3

**R/C BRIDGE**

Have you been bugged by color codes or unreadable component markings? Forget it! DM-3, the low cost R/C Bridge, measures true component values . . . in seconds . . . to better than 5%. And, it's all done with only 2 operating controls and a unique solid-state null detector, to zero-in on exact component selection . . . instantly! Completely wired, calibrated and tested, DM-3 includes an extensive instruction/applications manual, and operational theory too.

#### SPECIFICATIONS

**Resistance Range:** 10Ω-100 megΩ. (6 Ranges: 10-100Ω, 100-1000Ω, 1K-10KΩ, 100K-1 megΩ, 1 megΩ-10 megΩ) **Capacitance Range:** 10pFd-1mFd- (5 Ranges: 10-100 pFd, 100-1000pFd, .001-.01 mFd, .01mFd-.1mFd, .1- 1.mFd.) **Null Detector:** 2 hi-intensity LEDs-hi/lo markings. **Accuracy:** <5% of null dial, range switch setting. **Wght:** 2 lbs. **Power Needed:** 117V, AC @ 60Hz 3W.\*

**54<sup>95</sup>**

Add \$2.50 shipping/handling




**CSC**  
**CONTINENTAL SPECIALTIES CORPORATION**

44 Kendall Street, Box 1942, New Haven, CT 06509 • 203/624-3103  
West Coast Office: Box 7809, San Francisco, CA 94119 • 415/421-8872  
Canada: Len Finkler Ltd., Ontario

© Copyright Continental Specialties Corporation 1975



# For Special Music Effects

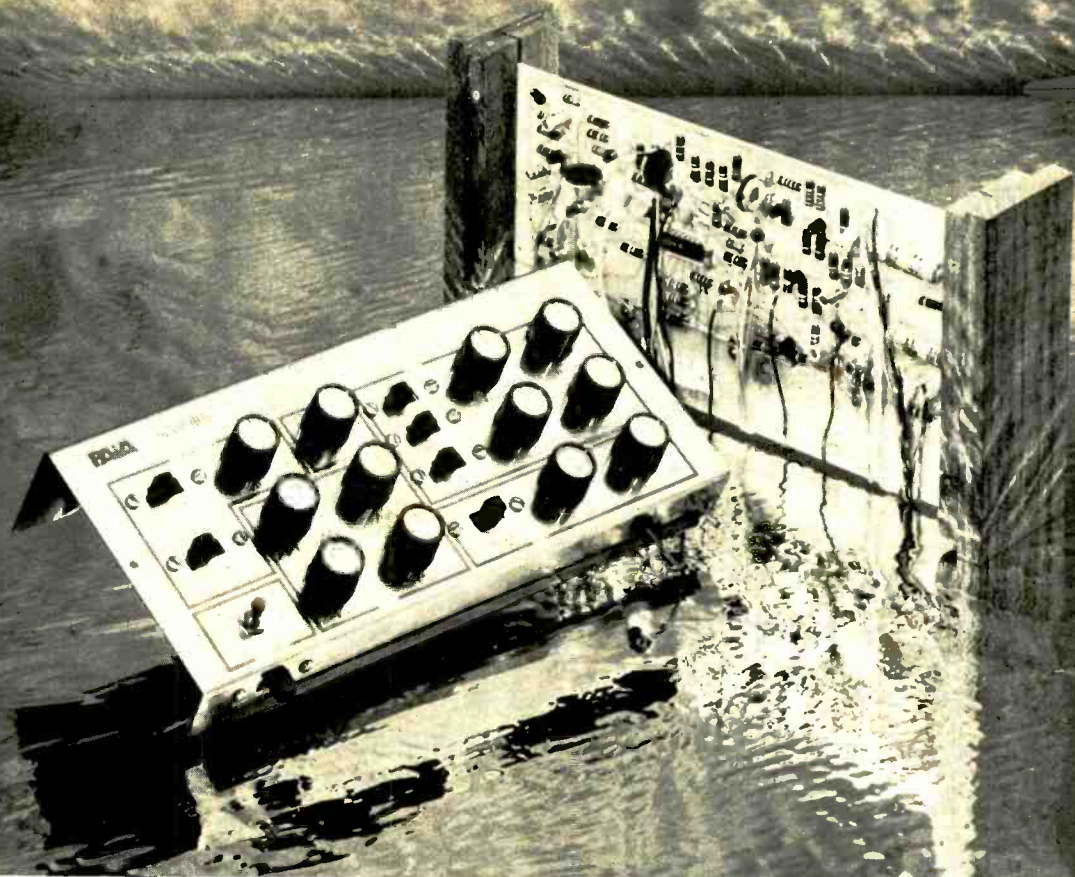

## BUILD A PORTABLE SYNTHESIZER

*Connect it to a hi-fi amplifier and  
create your own special music effects.*

by JOHN S. SIMONTON, JR.

IF THE TERM "ELECTRONIC MUSIC SYNTHESIZER" calls to your mind a picture of Walter Carlos wandering glassy eyed among a room full of equipment festooned with thousands of knobs and switches and draped with miles of cable, you're a little out of touch.

After years of patching together the amplifiers, oscillator, filters and other individual modules of the early day synthesizers, an interesting pattern began to emerge. Manufacturers and users alike discovered that most of the useful sounds that the equipment could produce were obtainable with a handfull of different patching arrangements. That was the beginning of the "normalized" performing synthesizer.

Basically a normalized synthesizer is one in which the separate elements are pre-arranged in a specific configuration (oscillators feeding amplifiers feeding filters feeding the output, ordinarily) with front panel controls to select various oscillator waveforms and set the level of audio and control signals. Except in studio, University or hobby machines, patch cords are rare and sounds are changed simply by turning a knob or flipping a switch.

To show how normalization works, and to give you a really low cost introduction to synthesis generally, we present the GNOME. The GNOME is a micro-synthesizer that employs the same voltage control techniques that give synthesizers their almost unlimited versatility while featuring controls that are so simple to operate even children can pick out sounds and tunes in the first few minutes.

### What's a synthesizer?

The currently fashionable way of thinking of synthesizers is in terms of analog computers. This has the double advantage of giving the electronics technician lacking a musical background a starting point closer to his home stomping ground. It also gives the musician an equivalency between electronic elements and the mechanical counterparts that he already knows. For example, the oscillator of a synthesizer corresponds to the vibrating strings, reeds, or whatever of a musical instrument. The filters correspond to the resonant properties of the body of the instrument. The instrument dynamics (attack and decay) correspond to the voltage-controlled amplifier/function generator combination in the synthesizer.

Once a synthesizer is viewed in these terms, it becomes immediately apparent what the real strengths of the equipment are. It would be difficult to build a mechanical instrument that combined the harmonic structure of a vibrating string with the resonant characteristics of a slide trombone. But with the electronic equivalents of these elements such strange "cross-breeding" is relatively simple.

### The GNOME

A block diagram of the normalization scheme is shown in Fig. 1. The built-in controller (a simple voltage divider) provides a control voltage that is proportional to the position of the wiper probe along the strip of conductive elastomer. The front-panel switches routes this control voltage to either the voltage controlled oscillator (VCO) or voltage controlled filter (VCF).

The VCO has two basic output waveforms; a triangle and a square wave. A SKEW control on the input of the oscillator changes the triangular-waveform output to a ramp while the square-wave changes to a short duration pulse, giving the user the option of four waveforms from a low-cost oscillator. Individual level controls

on the oscillator's two outputs allow for selecting or mixing the desired waveforms.

The outputs of the oscillator feed a common audio bus as does the output of the GNOME's internal noise source, also with its own level control. The audio bus always drives the GNOME's VCF, but a switch at the input of the voltage-controlled amplifier (VCA) allows the user to bypass the action of the filter if desired.

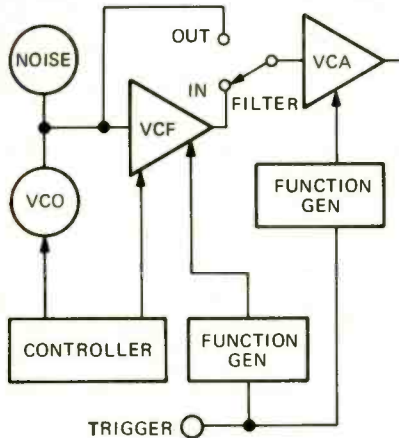


FIG. 1—NORMALIZATION SCHEME of the GNOME.

There are two internal function generators, one dedicated to providing a control voltage for the VCF and the other dedicated to the VCA. Each of these function generators provide for either percussion or sustained envelopes and the VCF's function generator has the added feature of a REPEAT switch that allows it to serve as its own trigger source for low speed cyclic effects similar to tremolo. Both function generators are normally triggered from a front panel TRIGGER button but provision has also been made for external trigger sources such as foot switches or sequencers.

There are many other features to the circuits of the GNOME but these will be covered in the individual circuit descriptions.

### Controller

The schematic diagram of the controller, noise source, trigger and power supply is shown in Fig. 2. The "sawtooth" geometry of the conductive elastomer that forms the control strip of the GNOME combines with the paralleling resistors R8 through R11 to produce an exponential voltage distribution along the surface of the strip. The RANGE potentiometer R78 is in series with the effective resistance of the control strip forming a voltage divider. Increasing the resistance of R78 decreases the voltage that appears across the length of the strip.

The wiper probe of the control strip is decoupled by an emitter follower in the VCO to prevent loading of the controller. This probe picks a voltage from the strip that is proportional to the position of the probe along the length of the strip. Switches S2 and S3 allow this voltage to be routed either to the VCO, VCF or both simultaneously.

The diodes at the bottom end of the control strip provide a constant voltage drop of approximately 1.5 volts insuring that there will be sufficient voltage on the

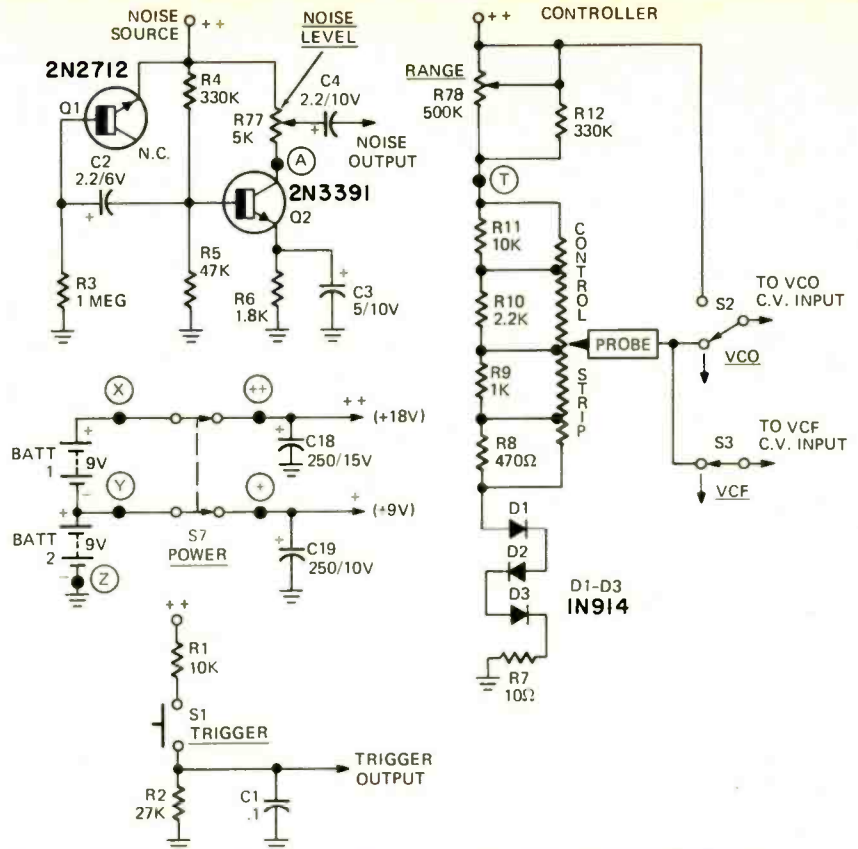


FIG. 2—CONTROLLER, noise source, trigger and power supply schematic diagram.

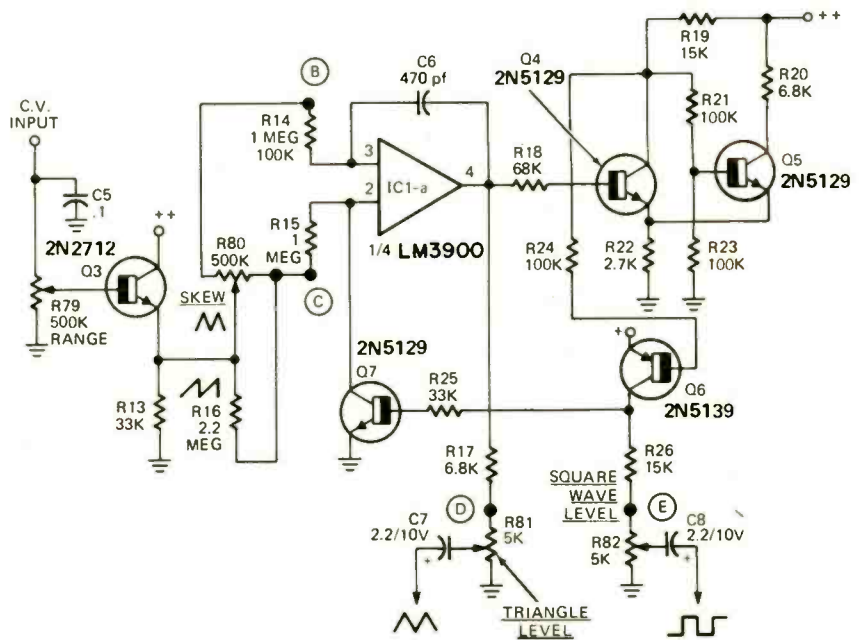


FIG. 3—VOLTAGE-CONTROLLED OSCILLATOR schematic diagram.

strip to drive the VCO regardless of the setting of R78.

### Noise source and trigger

The GNOME's noise source (see Fig. 2) is a standard design employing the shot-noise that results from the avalanching process of the reverse-biased base-emitter junction of transistor Q1. The noise appears across resistor R3 and is coupled by capacitor C2 to the single-stage amplifier comprising Q2, R4, R5 and R6. Potentiometer R77 is the level control for the noise source and as the wiper of this con-

trol is moved toward the collector of Q2, the amount of noise introduced in to the common audio bus is increased.

The TRIGGER push-button S1 (see Fig. 2) connects the +18-volt supply line to the trigger bus through R1. Capacitor C1 bypasses contact-bounce impulses to ground.

### VCO

The schematic diagram of the VCO is shown in Fig. 3. Control voltages are applied to the oscillator at the point marked "c.v. input". Capacitor C5 bypasses to

## Parts List

All resistors 1/2-watt, 10% unless noted.

- R1,R11,R34,R36,R40,R41,R61,R69—10,000 ohms  
 R2—27,000 ohms  
 R3,R14,R28,R31,R37,R48,R63,R64,R72—1 megohm  
 R4,R12—333,000 ohms  
 R5,R35,R51—47,000 ohms  
 R6,R33—1800 ohms  
 R7—10 ohms  
 R8—470 ohms  
 R9,R53,R76—1000 ohms  
 R10,R68—2200 ohms  
 R13,R25,R38,R55,R54,R67,R73,R75—33,000 ohms  
 R15,R21,R23,R24,R45,R44,R59,R71—100,000 ohms  
 R16,R46,R49—2.2 megohms  
 R17,R20,R27,R50,R52,R74—6800 ohms  
 R18—68,000 ohms  
 R19,R26,R32,R58—15,000 ohms  
 R22—2700 ohms  
 R29,R56,R57—100 ohms  
 R30,R60—150,000 ohms  
 R39,R70—470,000 ohms  
 R42,R66—4700 ohms  
 R43—22,000 ohms  
 R47—3.9 megohms  
 R62—220,000 ohms  
 R65—680,000 ohms  
 R77,R81,R82,R84—5000 ohm linear taper potentiometer  
 R78,R79,R80,R85,R86,R87,R89,R90—500,000 ohm linear taper potentiometer  
 R83,R88,R91—50,000 ohm linear taper trimmer pot.  
 C1,C5—.1 $\mu$ F Mylar  
 C2—2.2  $\mu$ F 6V electrolytic  
 C3—5  $\mu$ F 10V electrolytic  
 C4,C7,C8,C12,C14,C15,C16—2.2  $\mu$ F 10V electrolytic  
 C6—470 pF ceramic disk  
 C9,C10—.001  $\mu$ F ceramic disk  
 C11—33  $\mu$ F 10V electrolytic  
 C13,C17—.005  $\mu$ F ceramic disk  
 C18—220  $\mu$ F 15V electrolytic  
 C19—220  $\mu$ F 10V electrolytic  
 D1-D11—1N914 diode  
 IC1—LM3900 quad current differential amp  
 Q1—2N2712 selected low noise transistor  
 Q2,Q12,Q13—2N3391 transistor  
 Q3,Q14,Q15—2N2712 transistor  
 Q4,Q5,Q7,Q9,Q10,Q16—2N5129 transistor  
 Q6,Q11,Q17—2N5139 transistor  
 Q8—MPF-102 transistor  
 S1—SPST normally-open push-button  
 S2,S3,S6,S8—SPDT slide switch  
 S4,S5,S7—DPDT slide switch  
 BATT 1,2—9-Volt transistor battery (NEDA 1604 or equal)  
 MISC.—9-lug terminal strips (2), pin jack, pin plug, miniature phone jack, circuit board, control strip, battery snaps, 1/4-in. grommet, knobs (12), wire, solder, hardware, etc.

**NOTE—The following are available from PAIA Electronics, Inc. 1020 W. Wilshire Blvd. Okla. City OK 73116**

**Circuit board and control strip**  
 Order #3740-P—\$8.50 postpaid  
**Complete kit of all parts except batteries**  
 Order #3740-K—\$48.95 plus postage and insurance for 4 lbs.

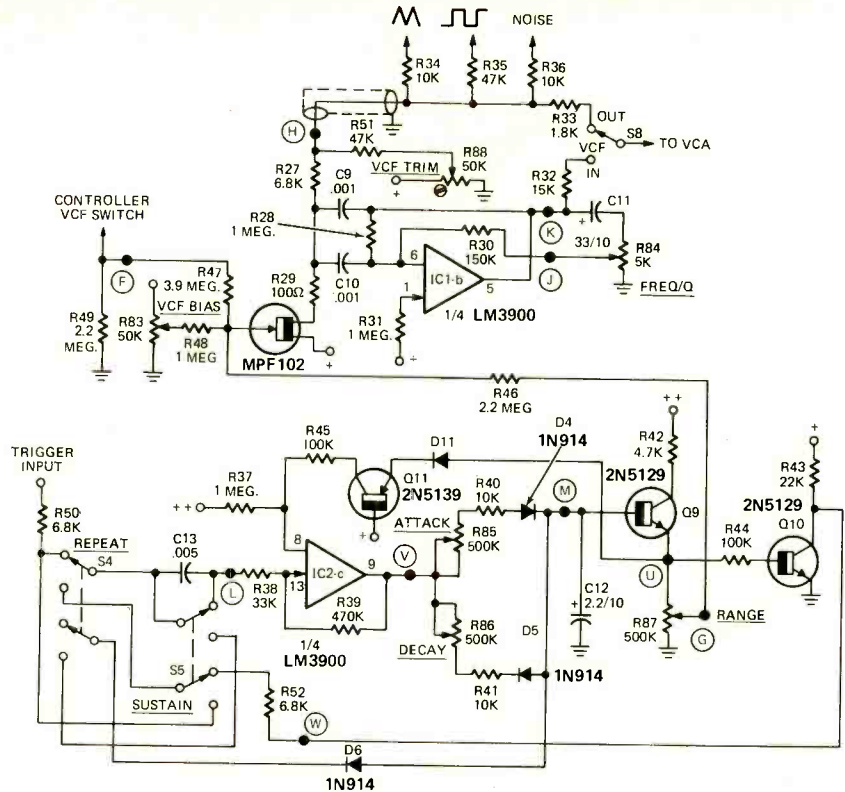


FIG. 4—VOLTAGE-CONTROLLED FILTER schematic diagram.

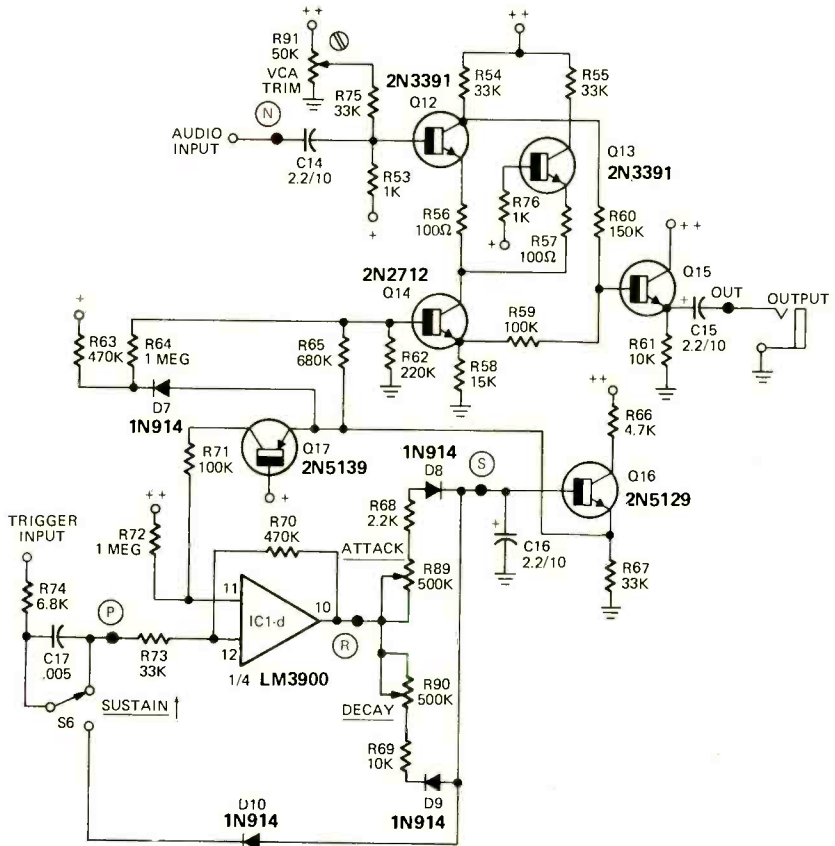


FIG. 5—VOLTAGE-CONTROLLED AMPLIFIER schematic diagram.

ground contact-noise originating at the control strip. The control voltage is then applied to the VCO RANGE control R79 which serves as an attenuator on the control-voltage line. Emitter-follower Q3 serves as an impedance-matching device between the control-voltage input and the

oscillator circuitry.

The oscillator is a relatively common type consisting of an integrator (IC1-a) and a Schmitt-trigger comprising discrete transistors Q4 and Q5 and associated components.

(continued on page 100)

# Test Equipment for Industrial Servicing



FIG. 1—B & K VOM's. Model 101 is shown above. Model 102 is shown at right.

*Specialized servicing requires specialized test equipment. Here's a round-up article on industrial test equipment.*

by JACK DARR  
SERVICE EDITOR

"INDUSTRIAL ELECTRONICS" IS A SHORT phrase that covers many different things. Here, it means *control*. The machine does the work, and the electronics tell it what to do. Electronic controls tell it when to start and stop, and if it isn't doing something right, they shut down the whole process. These controls come in a great variety of sizes and shapes, all the way from a simple SCR and a few resistors up to large arrays of IC's and logic.

TV viewers may have the impression that complicated electronic machinery is made up of big panels full of flashing lights, which go "a'BEEP'm, a'BEEP'm" all the time. Fortunately, this isn't true. When the crisis occurs, great arcs and sparks fly, and clouds of smoke boil out. Evidently the designers of this complicated electronic machinery never heard of fuses or circuit breakers.

Real life electronic controls are not noisy, and are much better protected. They do not go "a'BEEP'm"; when something happens, they just click quietly and stop the machine. They have two major functions; control of operations, and protection against damage. Monotonous operations can be broken down into a series of simple steps, each with its own set of electronic control units.

As briefly as possible, such a system starts with a "transducer". This is a device that detects quantities; movement, heat, pressure, flow, or any thing else that will provide the information needed. The transducer converts this into an electrical signal. This goes to an amplifier, where it is processed into signals needed to do the actual controlling. If the transducer reading shows that the machine is out of tolerance, or doing something wrong, it actuates a circuit to stop the machine. This can be a relay (usually called a "contactor" if it's big enough) or solid-state switches. Every known form of electronic reaction is used in transducers; resistance, voltage, current, magnetic fields, capacitance, inductance, photoelectric, thermoelectric

and piezoelectric reactions, and even radioactivity. There are a lot of these; one reference work lists 1250 different types.

The name of the game is "downtime"; this must be avoided, or reduced to an absolute minimum. Most electronic control systems are designed so that they can be serviced quickly and easily, to get the machine back on-line as soon as possible. In one real machine, an electronically controlled lathe, there are ten steps in its process. Each one is controlled by a small PC board ("card") that plugs into a rack in the control cabinet. If the machine goes to step 8 and stops, the technician starts testing by pulling card 8 and trying a new one. If this clears the trouble, the bad card is taken back to the bench and checked out. In quite a few machines like this, the cards are all the same which makes servicing much faster.

Power supplies for the control units are well overrated for cool running, and protected by fuses and circuit breakers. Plug-in rectifier cards, and similar devices are also used to speed testing. The cards themselves are comparatively simple, with "switching" done by circuit-conductors, and control functions by SCR's, switching transistors and diodes, and so on. They may be tested and repaired with very little trouble.

## Specialty-built test gear

Industrial electronics work, therefore, requires test equipment that can be used to check out all parts of the system quickly and accurately. This may require checking high voltage AC or DC, currents, as well as reading lower voltages used on transistors and other solid-state devices. The test equipment is an essential part of the whole system. It must be versatile, to cover the wide range of quantities to be measured, and rugged, to withstand the normal wear and tear of daily work. It must also maintain its accuracy over long periods.

The test instrument that will do all of these things; read AC or DC voltages and

currents over a wide range, resistances, and make continuity tests, is the good old volt-ohmmeter (VOM). Later on in this series, we'll get to some highly specialized and complex instruments. However, at the "primary level", most of the load is carried by the VOM.

There are a great many of these. The ones you'll see here are mainly the units designed to do this type of work. They're well-built, rugged, and protected against accidental physical damage from dropping, and from electrical damage from accidental overloads. All are high-quality test instruments; they will last longer and cost far less. The "\$9.95 wonders" just won't hack it. One fall off the bench, or one instant contact with high voltage, and all you have left is a little black box making ominous noises and leaking foul-smelling smoke, all full of tiny bits of carbon.

All of the high-quality industrial VOM's will have very close to the same vital statistics. The size and shape will differ, but the essential functions will be there. This reads something like this: sensitivity, 20,000 ohms-per-volt (or more); AC and DC voltage and current reading from a very low range up to perhaps 1000 volts; ohmmeter ranges from a very low range up to  $\times 10K$  scale; DC current from a few microamperes up to several amperes, and DC millivolt ranges to an astonishingly low level.

Physically, most of them are built in high-impact plastic cases, with the meter face and control knobs recessed for safety. Electrically, most have protective diodes across the meter movement to protect against overloads. Very small valve fast-acting fuses are used, together with fast-acting relays and circuit breakers. Quite a few of these are used in the ohmmeter ranges, for those embarrassing moments when we try to read the AC line voltage on the  $R \times 10$  scale. Spare fuses are provided inside the case.

Many accessories are available that in-



FIG. 2—RCA model WV-547A.



FIG. 3—TRIPLETT model 310.

crease the usefulness of the basic VOM. High voltage probes let you take readings up to 50 kV; heavy shunts let you read direct currents up to many amperes; clamp-on units allow reading alternating currents up to hundreds of amperes. There are other special accessories, that will be dealt with as we get to them. Special carrying cases protect the VOM, and have storage space for test leads, probes and other accessories.

#### About test leads

Speaking of test leads; this is one point that has been almost overlooked in the past. Not any more. The test leads are light, flexible, and made with long, thin tips so you can get into tight places. Slip-on clips let you hook the test leads in place and leave your hands free; the cases often come with straps or handles so that the VOM can be hung on the machine.

Now let's look at a few good examples of the typical industrial VOM, from the country's leading test equipment makers. The listing is in alphabetical order; these are all "good ones", and will give you your money's worth in long service.

For convenience, I've divided them into three groups, by physical size. First is the "shirt-pocket" types, then a bunch that could be called mediums, and last the full-sized VOM.

#### Shirt-pocket types

Alphabetically, first come the B&K 101



FIG. 4—B&K model 120P.



FIG. 5—RCA WV-520A.

and 102. These are compact types, 20,000 ohms per volt, with AC and DC volts, ohms and current. The difference between them is that the 101 has a top voltage range of 1000 volts, AC or DC, and the 102 goes on up to 5000 volts with a special panel jack. No external multiplier probe is needed. Figure 1 shows both of them. They will also go down to a full-scale reading of 250 mV.

RCA's entry in the small-meter field is their *Tech-VOM*, Model WV-547A (Fig. 2). Up to 1000 volts AC or DC, with a 500-mV range. Resistance readings from 2 ohms to 1.0 megohm, and DC current up to 250 mA. Compact, and rugged; taut-band meter suspension and high impact plastic case.

The Simpson Electric Co. of Elgin, IL also has a line of *Micro-Testers*, in this size case. There are eight of these little fellows, AC/DC VOM's, AC ammeter, DC milliammeter, battery tester, low-range ohmmeter, and so on.

Next in the alphabet is a "mini" that's been around a long time, and is still going. This is the Triplett 310, Fig. 3. This is the latest ruggedized version, with normal ranges as well as special jacks for reading up to 1200 volts AC or DC. The tip of the negative test lead can be taken out, and plugged into a jack on the end of the case; this gives you one-hand operation. The case is a drop-resistant type, with special finger-tread design on the sides to make it easier to hold.

Next come the medium-sized units, about halfway between the shirt-pocket types and the old "standard-size VOM's". Alphabetically again, here is the B&K



FIG. 6—SIMPSON model 160.



FIG. 7—TRIPLETT model 60.

120P. Standard VOM ranges, and fully protected against electrical overload by a built-in electronic system. When there's an overload, the red RESET button pops up; it can't be reset until the overload has been removed. You can see this in Fig. 4.

RCA's WV-520A is another general purpose VOM, this one with a 100,000 ohms per volt movement, and a scale for reading 0-15 M.A. A polarity-reversing switch is provided. The meter is protected by diodes. Top voltage ranges are 1500 volts AC or DC, and an 0-5 ampere range can be used for high current (Fig. 5). A similar model is the WV-532A, which has a special fast-acting relay circuit to protect the instrument against damage from overloads.

Next, the Simpson 160 (Fig. 6). All of the standard ranges, including a 50- $\mu$ A (250 mV), which we will take up later, with polarity reversing switch, and protective diodes across the meter.

Figure 7 shows the latest Triplett *Tough Guy*, the model 60. This has a very rugged plastic case, taut-band meter suspension, for drop-proofing. Electrically, the model 60 is well protected, too. Diodes across the meter movement, and two separate fuses, 1/8-A and 10.0-A help with normal overloads. (Spare fuses inside the case.) For a really bad one, a special 2A 1-kV fuse is provided. This protects against those cases when you make accidental contact with the kind of high voltage that could cause explosive arcs inside the case. It has no exposed metal parts, for protection against shock hazards.

Now we get to the "full-sized" types. Figure 8 shows the familiar Simpson 260. This new model is fully protected against electrical overload, and ruggedized to take hard service. The same bunch of plug-in adapters can be used with this.



FIG. 8—SIMPSON model 260.



FIG. 9—TRIPLETT model 630-PLK.

Figure 9 shows another familiar "face", the Triplett 630 PLK. "PLK" in the model number means that the complete meter is protected by a solid-state switching circuit, on all ranges. It is driven by the ohmmeter battery, and draws so little current that battery life is shelf life. The relay instantly opens the input circuits when there is an overload equal to about 3 times normal full-scale reading. Fuses are also used, just in case.

Next we come to something new: this is the specialized industrial VOM. These instruments have all of the features of the preceding ones, and special ranges, functions and accessories to make them more useful in industrial electronic and electrical work. The most compact of these is RCA's *WV-531A*, in Fig. 10. Some of the accessory test leads and probes are seen. One novel feature of this instrument is an LED Probe which can be used to make continuity tests without having to look at the meter. The carrying case holds the meter and all test leads.

The Triplett Co. has a specialized Industrial VOM in their *model 615* (Fig. 11). Quite a few special functions and tests are "built-in"; three thermocouples can be plugged into sockets on the panel, and any one read by moving the switch. Three different temperatures can be read and compared. There are three millivolt ranges, 60, 300 and 1500. A plug-in AC ammeter clamp-on can be used; Fig. 12 shows this with a *model 630*. Figure 13 shows the *model 615* in its very well-padded carrying case with space for the various adapters.



FIG. 10—RCA model WV-531A.



FIG. 11—TRIPLETT model 615.

Figure 14 shows the new *model 60* in its carrying case, with the adapters.

Now that you've seen the instruments, what can you do with them? The answer to this is limited only by the ingenuity of the technician. With one of these VOM's, and a good instruction manual, you can check an amazing number of things. A great many of the transducers can be checked for operation.

### Thermocouple testing

You'll find quite a few thermocouples. They're used in special transducers, as thermometers, and also as both the control and source of power in many systems. These are called the "millivolt" systems. The output is very low. It will run from the 10 mV output of a platinum/platinum-rhodium thermocouple used for very high temperature testing, to about 30 mV for the common iron-Constantan types, and up to 70 mV from a Chromel-Constantan type.

Here's where we can use the millivolt ranges mentioned before. Many of the VOM's have a 50- $\mu$ A range that can be used as an 0-250-mV voltmeter. Others provide several millivolt ranges. Check the instruction book with your VOM; this will give you the exact value of the millivolt ranges. There is a small difference.

Since the DC output of a thermocouple is so low, the  $\mu$ V range can be connected right across the output of a thermocouple. The actual voltage depends on the temperature of the thermocouple junction. In the millivolt control systems, the junction should be in the flame of the pilot light, and have a certain minimum output; usually about 70 mV. For precise tests such as transducers and thermometers, you'll need a calibrated source of heat, and an



FIG. 12—TRIPLETT models 630 and 10.



FIG. 13—TRIPLETT model 615.



FIG. 14—TRIPLETT model 60.

accurate standard thermometer.

### Photoelectric cell tests

Photoelectric controls are used in several applications. Counting, start-stop on certain operations (the work-piece must be in a certain place before the process can start), indication of the presence of pilot flame on heavy-duty gas boilers, and so on.

There are two main types of photocells; "photovoltaic" meaning those which generate a voltage when exposed to light, and "photoresistive"; these change resistance when illuminated. The original photocells were vacuum tubes, which were photoresistive. They have to have a fairly high voltage supply before they can work. However, these can be tested with an ohmmeter. Connect the meter across the cell, on a high range, with the cell covered. Note the resistance reading. Now uncover the cell, and shine a light on it. A penlight is very handy for this. Note the change in resistance. If there is no change, the cell is probably defective. The reading will usually be very high, but there will be a definite change with light.

(continued on page 113)

# BUILD THIS ELECTRONIC STOPWATCH



Simple circuit adds elapsed time measurement feature to basic calculator circuit without affecting calculator operation.

by TOMMY N. TYLER

WITHIN THE PAST YEAR SEVERAL 6-DIGIT hand-held calculators have appeared on the market, often retailing for less than \$15. These units are fairly limited in their calculating abilities. They are fine for adding up the grocery bill or balancing the check book, but they do not have a floating decimal point and operate with whole numbers only. Nevertheless, considering the functions they perform, these little calculators are a marvel of simplicity as well as a bargain source of components for digital display projects. With less than \$10 worth of additional parts you can modify one of them to provide a handy digital stopwatch as well as a calculator. This is not only a fun and useful project, but also a chance to learn more about the techniques of keyboard scanning and display multiplexing used in many current calculators.

The best calculator to use is the Minuteman-6 manufactured by Commodore Business Machines, although the National Semiconductor Model 600, or the Model 650 "Mathbox" manufactured by the Novus Division of National Semiconductor are essentially equivalent except for styling and keyboard construction. These units use a National Semiconductor type MM5736 calculator chip which features an automatic constant on all four functions. The automatic constant enables the calculator to perform as a counter by entering a "1" and then pressing the "ADD" key repetitively, each opera-

tion adding 1 to the previous total. By operating the ADD key electronically with a precision oscillator which is gated on and off, we can measure elapsed time quite effectively. The 6-digit display counts up to 9999.99 seconds, which is over 2¾ hours. If you would prefer to build just the stopwatch alone, the MM5736 calculator chip is being offered at under \$4 (check the advertisements in the back of this issue.)

## Basic calculator operation

Figure 1 shows a schematic diagram of a typical calculator. The MM5736 calculator chip has three inputs (K1, K2, and K3) and two sets of outputs. One set of outputs (digits 1 through 6) drives the 6-digit display in multiplex fashion, using a 75492 digit driver IC. The other set of outputs (*a* through *g*) provides a 7-segment coded output of the calculator's display register. It is also multiplexed so that the segments for digit 1 appear during digit-time 1, the segments for digit 2 appear during digit-time 2, and so on. Both the digit and segment drive signals return to zero momentarily between digits to prevent ghosting or smear. This is referred to as interdigit blanking. Figure 2 shows a timing diagram of the digit and segment outputs for a display reading of "654321." Digit 1 is at the far right of the display, and the digits are scanned from right to left.


Numbers or functions are entered into the calculator by connecting one

of the strobed digit outputs to one of the three inputs. The digit outputs are therefore performing double duty by scanning the keyboard and display simultaneously. It's tricks like this that enable the chip manufacturer to put the entire calculator into a DIP package with only 18 pins.

Battery B1 is an ordinary 9 volt transistor radio battery. An alkaline battery will power the calculator for about 10 to 20 hours, depending on how it is used. Adding the stopwatch reduces this by only a few hours. Note that the artificial decimal point on these calculators is merely a single LED between the second and third digits which is driven through resistor R1. This fixed decimal point is in just the right place for our stopwatch.
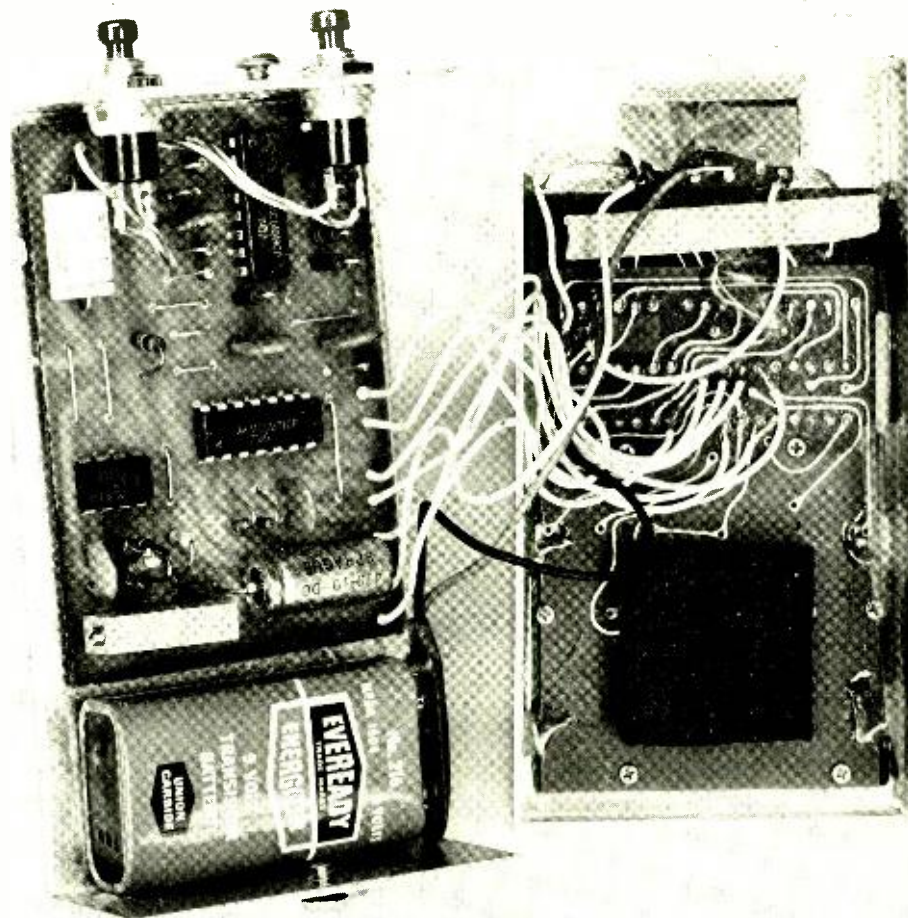
## Keyboard debounce

Keyboard debounce refers to an operation performed in the calculator chip to discriminate against noisy key contacts which might otherwise cause multiple entries. It is both a blessing and a curse in that it allows the calculator to operate reliably with "cheap and dirty" keyboards, but it also limits the speed of operation in a way that affects our stopwatch. Debounce is accomplished by requiring that one of the three inputs remain connected to one of the three inputs for at least 8 consecutive keyboard scan cycles before the entry is executed in the chip. Before another entry can be made, at



STOPWATCH printed circuit board (left) is added to basic calculator circuit (right). Both the calculator printed circuit board and display remains intact.

least 8 consecutive scan cycles must elapse during which *none* of the digit outputs are connected to any of the K inputs. When using the calculator as a counter, the counting speed is limited by this requirement for a minimum of 16 scan cycles per count.

Figure 3 shows a block diagram of the stopwatch. Pressing the RESET switch clears the calculator and then enters a "1." Pressing the START/STOP switch turns on the oscillator, which electronically "presses" the "+" key 100 times per second. The first timing pulse to the ADD circuit merely transfers the original "1" to the accumulator register. The second pulse adds another 1, giving a total of 2. The third pulse brings the total to 3, and so on. The calculator is, in effect, counting time in hundredths of a second.

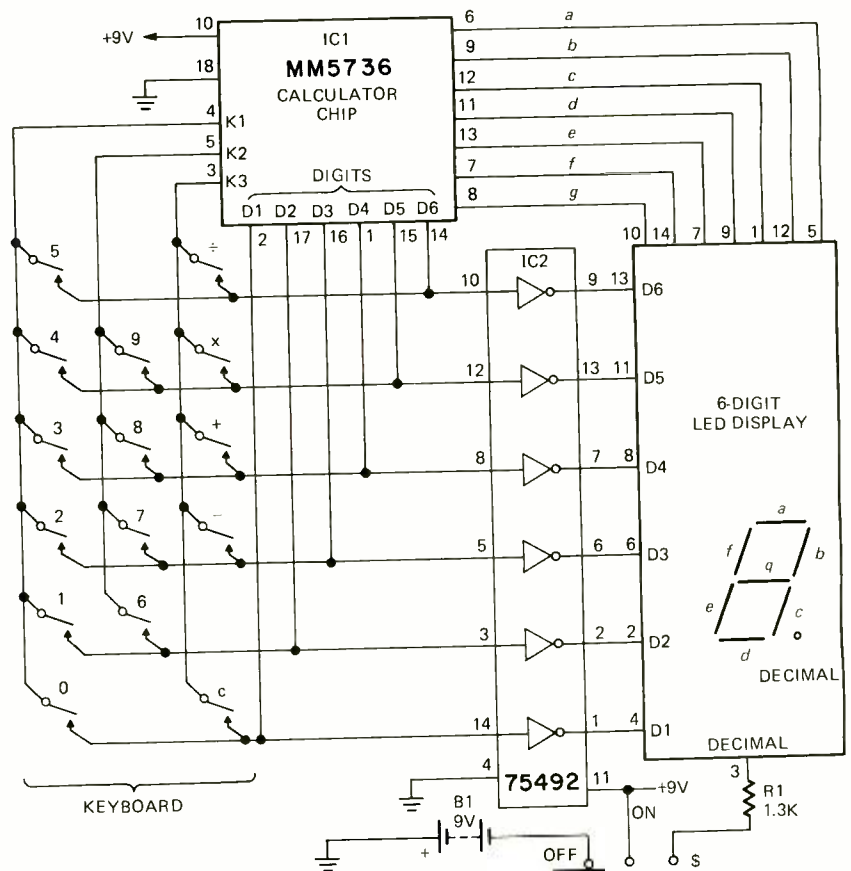


FIG. 1—BASIC CALCULATOR consists of two IC's, keyboard, display and switched DC power source. The keyboard and display are multiplexed.

S3



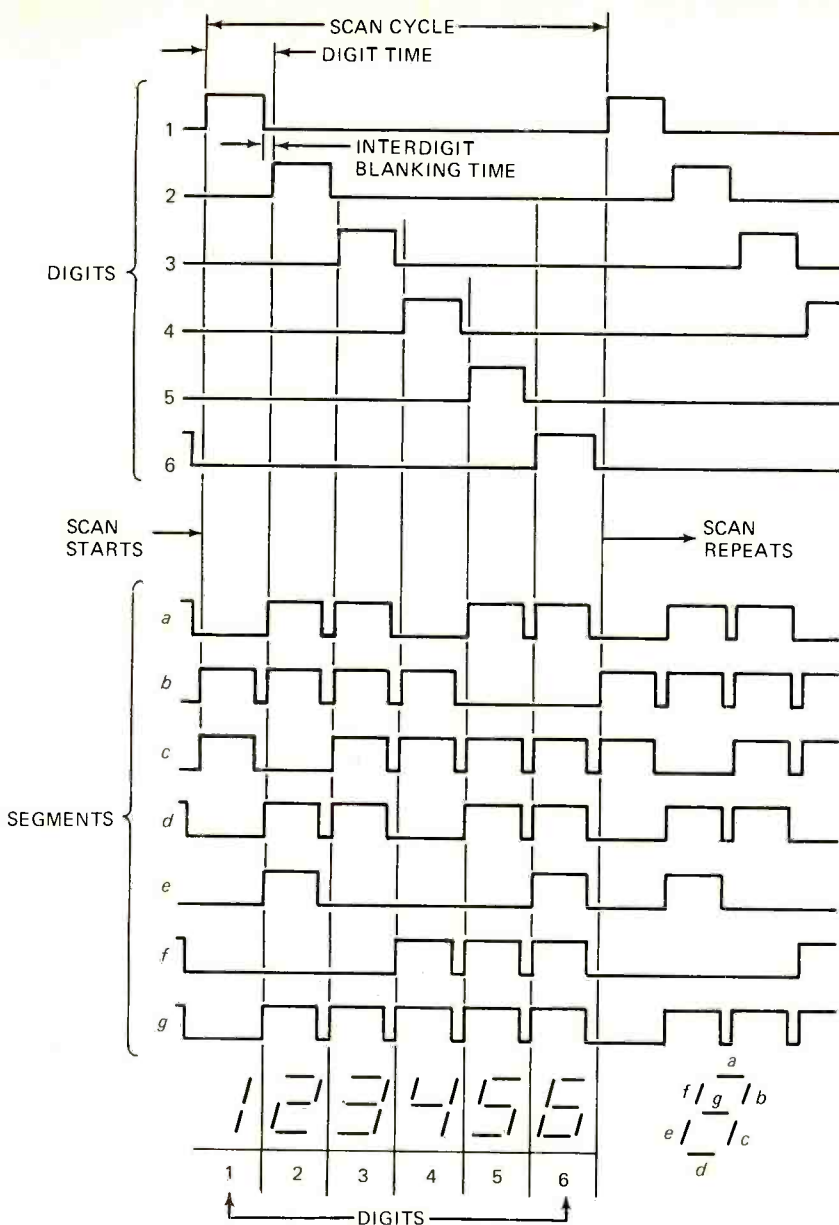


FIG. 2—TIMING DIAGRAM showing digit and segment output waveforms from the calculator chip. The display appears as "654321" because of right to left scanning provided by the calculator chip.

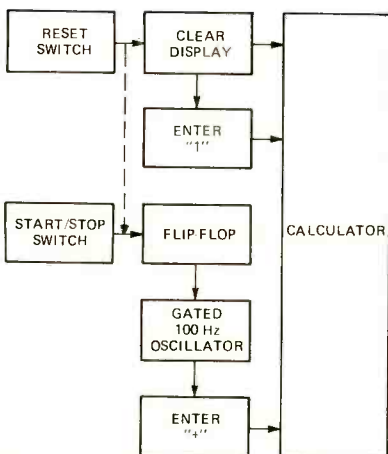


FIG. 3—STOPWATCH circuitry automatically enters a "1" when the reset button is depressed. The gated 100 Hz oscillator then enters "+" repeatedly.

### Counting speed

The MM5736 calculator chip has a built-in clock oscillator which provides a typical keyboard scanning rate of 1 kHz, with some running as slow as 700 Hz and some faster than 2 kHz due to inherent variations in chip parameters during manufacture. If we satisfy the debounce requirement of 8 scans closed and 8 scans open per count, our maximum counting speed is typically 60 Hz, with some as slow as 40 Hz or as fast as 150 Hz.

Fortunately there is a way to speed up the counting rate by using the circuit shown in Figure 4. The maximum counting rate attainable with this circuit will depend on the particular chip used, but will run from about 80 Hz up to about 300 Hz. The increase in

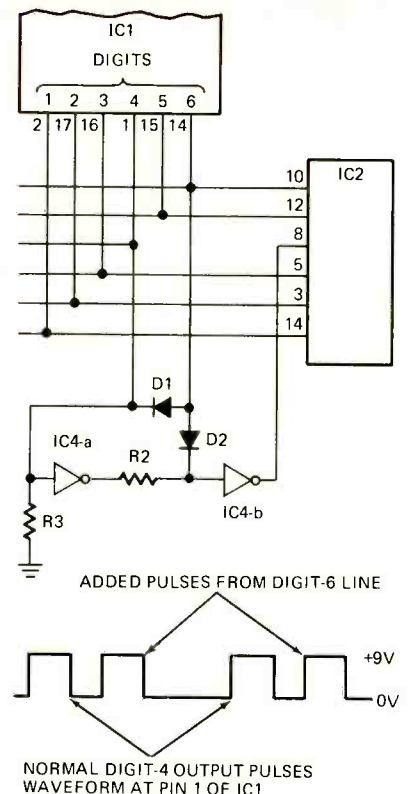


FIG. 4—ADDED COMPONENTS fool calculator into cycling at double speed. The components are only for those calculator chips that will not count at the 100-Hz speed.

counting rate is obtained by feeding the digit-6 output pulse back to the digit-4 display driver input, through diode D1. This fools some internal logic in the chip so that the debounce requirement is satisfied whenever a key remains closed at least 4 scan-cycles, followed by at least 4 scan-cycles during which no key is closed. The other components are necessary to prevent the double pulse from appearing on the digit-4 display driver input, which would cause digit-4 to display a ghost image of digit 6. During digit-4 time, the output pulse from digit-4 line is fed through inverters IC4-a and IC4-b to the driver input, lighting digit 4. During digit-6 time, the digit-4 line is again driven high through D1, but this time D2 conducts and the digit-6 pulse holds the input of IC4-b high to prevent digit 4 from being lighted at the same time as digit 6.


Most chips will count at 100 Hz after the addition of the speedup circuit. For those that don't, the stopwatch can still be built to measure time to the nearest 1/50 second. Referring to Fig. 3, this is done by arranging the RESET switch to enter a "2" instead of a "1," and slowing the oscillator to 50 Hz.

Next month, the article will continue with the schematic and the parts list. The foil pattern, component placement, construction details and operation and calibration procedures will also appear next month.



R-E
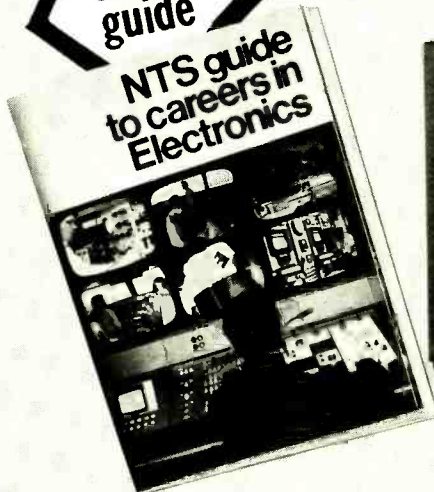
# The better the training the better you'll


Send for  
**FREE**  
illustrated  
career  
guide



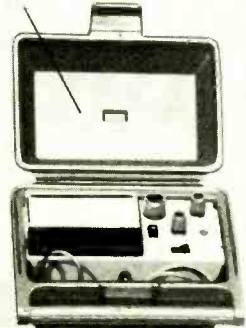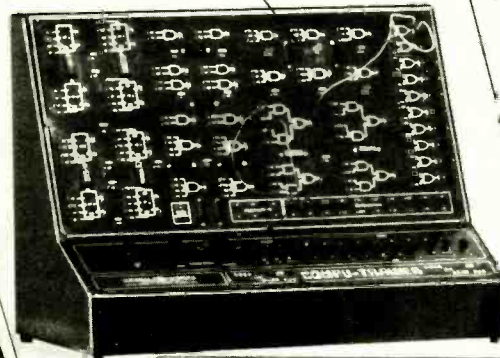IN-CIRCUIT TRANSISTOR TESTER  
COMPU-TRAINER  
TROUBLESHOOTER  
VOM



SOLID-STATE  
OSCILLOSCOPE

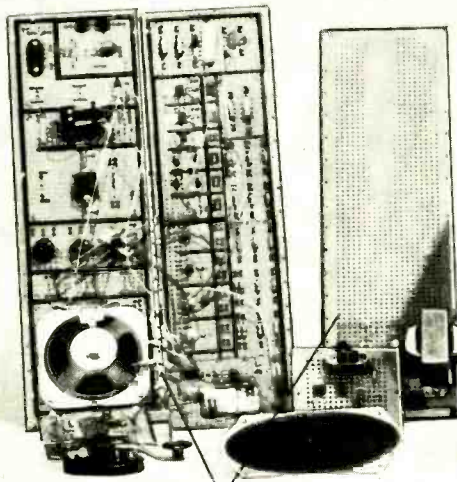

ELECTRO-LAB



(Simulated TV Reception)

As an NTS student you'll acquire the know-how that comes with first-hand training on NTS professional equipment. **Equipment you'll build and keep.** Our courses include equipment like the **NTS/Heath Digital GR-2000 Solid State color TV** with first-ever features like silent varactor diode tuning; digital channel selection, (with optional digital clock), and big 315 sq. in. ultra-rectangular screen.

Also pictured above are other units — 5" solid state oscilloscope, vector monitor scope, solid-state stereo AM-FM receiver with twin speakers, digital multi-meter, and more. It's the kind of better equipment that gets you better equipped for the electronics industry.


This electronic gear is not only designed for training; it's field-type — like you'll meet on the job, or when you're making service calls. And with NTS easy-to-read, profusely illustrated lessons you learn the theory behind these tools of the trade.

**Choose from 12 NTS courses** covering a wide range of fields in electronics, each complete with equipment, lessons, and manuals to make your training more practical and interesting.

**Compare our training; compare our lower tuition.** We employ no salesmen, pay no commissions. You receive all home-study information by mail only. All Kits, lessons, and experiments are described in full color. Most liberal refund policy and cancella-
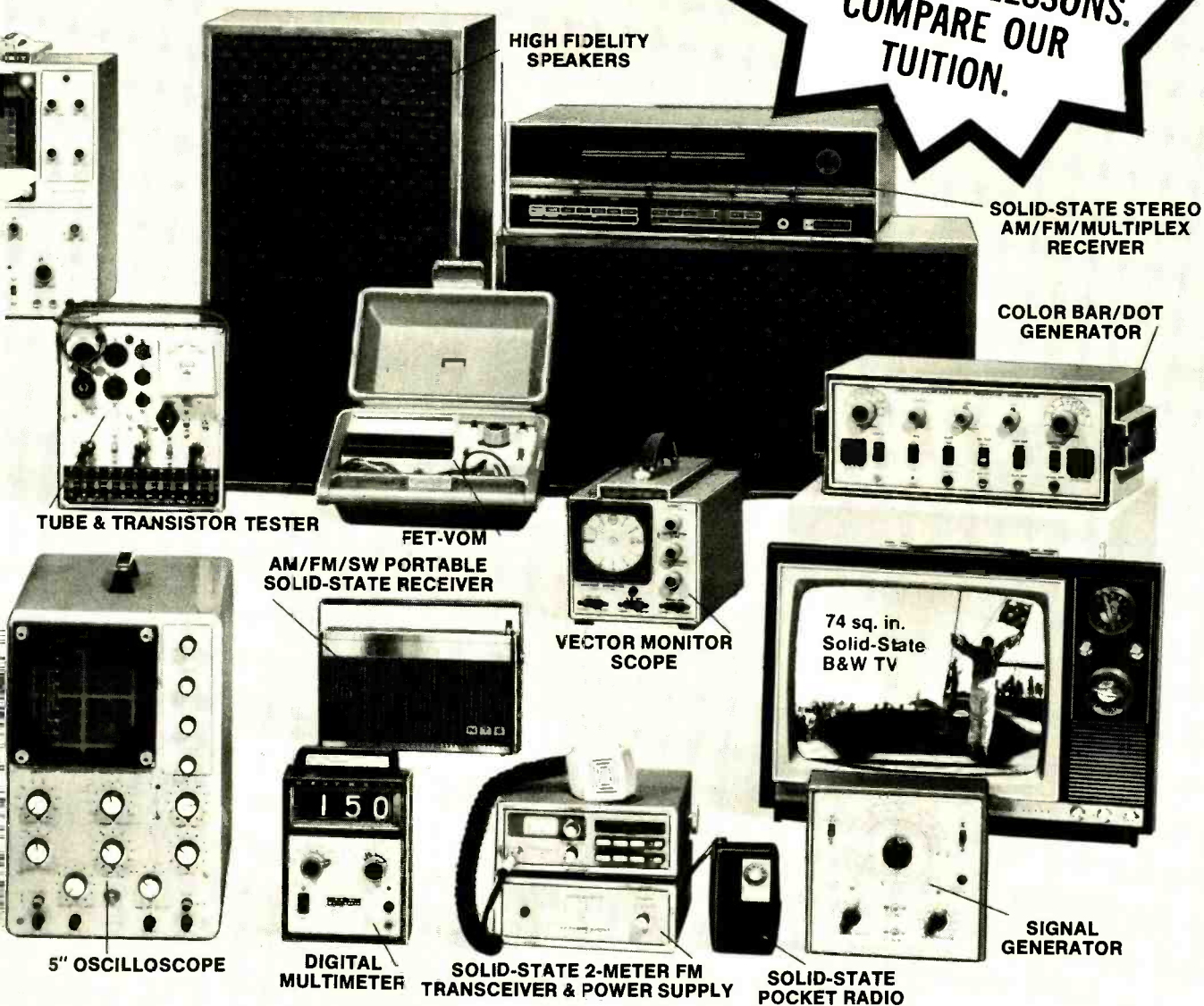
# and the equipment be equipped.

COMPARE OUR  
KITS AND LESSONS.  
COMPARE OUR  
TUITION.



tion privileges spelled out. Make your own comparisons, your own decision. Mail card today, or clip coupon if card is missing.

**NO OBLIGATION. NO SALESMAN WILL CALL**

**APPROVED FOR VETERAN TRAINING**

Get facts on new 2-year extension

**NATIONAL TECHNICAL SCHOOLS**

TECHNICAL-TRADE TRAINING SINCE 1905  
Resident and Home-Study Schools  
4000 So. Figueroa St., Los Angeles, Calif. 90037

**NATIONAL TECHNICAL SCHOOLS**  
4000 South Figueroa St., Los Angeles, Calif. 90037 Dept. 206-115  
Please send FREE Color Catalog and Sample Lesson.  
NO OBLIGATION. NO SALESMAN WILL CALL.

<input type="checkbox"/> Color TV Servicing	<input type="checkbox"/> Electronics Technology
<input type="checkbox"/> B & W TV and Radio Servicing	<input type="checkbox"/> Computer Electronics
<input type="checkbox"/> Electronic Communications	<input type="checkbox"/> Basic Electronics
<input type="checkbox"/> FCC License Course	<input type="checkbox"/> Audio Electronics Servicing

NAME \_\_\_\_\_ AGE \_\_\_\_\_  
ADDRESS \_\_\_\_\_ APT # \_\_\_\_\_  
CITY \_\_\_\_\_ STATE \_\_\_\_\_

Please fill in Zip Code for fast service \_\_\_\_\_  
 Check if interested in G.I. Bill information.  
 Check if interested ONLY in classroom training in Los Angeles.

# TV Typewriter II

## manual cursor board

Add this optional plug-in board to the TV Typewriter II and you can manually position the cursor anywhere on the TV screen.

by ED COLLE

IF YOU HAVE BUILT THE TV TYPEWRITER II that has recently appeared in **Radio Electronics** (see Feb. 1975 issue), you've probably been waiting for the manual cursor plug-in option. This board allows you to manually, with pushbutton switches, move the cursor one space left, right, up or down as well as home-up, erase to end of line (EOL) and erase to end of frame (EOF). The last three options, home-up, erase EOL and erase EOF do not require the cursor board but it is recommended.

The circuitry provides the switch debouncing necessary to prevent multiple cursor counting thus insuring the cursor jumps only one position each time a directional button is depressed. The control switches themselves are SPST normally open pushbutton switches that should be mounted on an aluminum strip just in front of the keyboard. The debouncing delay provided is 100 milliseconds, but longer delays can be achieved by increasing the capacitance of C1 (see Fig. 1). The entire circuit is built on a 3-1/16 in. x 4-1/2 in. fiberglass circuit board that plugs into the main board of the TV Typewriter II on connector strips J3 and J4 just behind the memory board. Switch connections to the cursor board are provided on the nine pin connector attached to the circuit board.

### How it works

Since all of the pushbutton control switches are normally open, the switch inputs are all tied high with resistors

### PARTS LIST

All resistors are 1/4 watt, 10%, unless noted.

R1-R7, R10, R12, R13—1000 ohms  
R8, R9—5600 ohms  
R11—2200 ohms

C1—33- $\mu$ F, 6 volts, electrolytic  
C2, C3—100-pF polystyrene  
C4—0.1- $\mu$ F, 12 volts

D1—1N914 silicon diode

IC1, IC5—7403 quad NAND gate  
IC2—74123 dual one-shot multivibrator  
IC3—7430 eight-input NAND gate  
IC4—7404 hex inverter  
Q1—2N5129 transistor.

R1-R7. The input commands are directed to the output NAND gates (IC1, IC5-a, IC5-b and IC5-c) through inverters IC4 and IC5. Note that none of the control switches affect the output gates unless the logic signal from pin 5 of IC2-b is high. IC3 monitors the control switches and its output goes high when any one of the seven switches are depressed. This forces the  $\bar{Q}$  output of IC2-a low where it will remain for ap-

proximately 100 ms. After the 100-ms delay, the  $\bar{Q}$  output of IC2-a goes high again. This triggers IC2-b forcing its  $\bar{Q}$  output high for 1  $\mu$ s. This gates the appropriate control command into the TV Typewriter II circuitry.

### Assembly and use

It's not very difficult to assemble the unit, just be sure to orient the integrated circuits, diode, electrolytic capacitor,

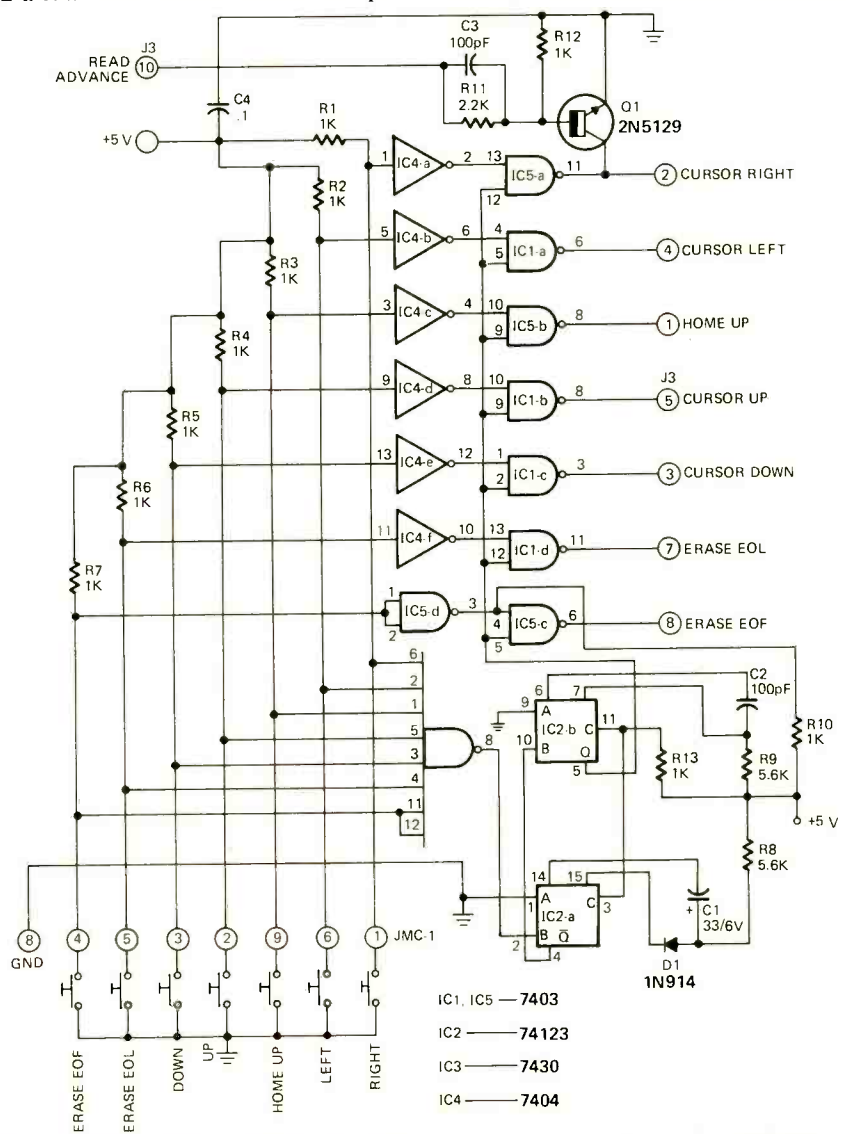


FIG. 1—MANUAL CURSOR BOARD schematic.


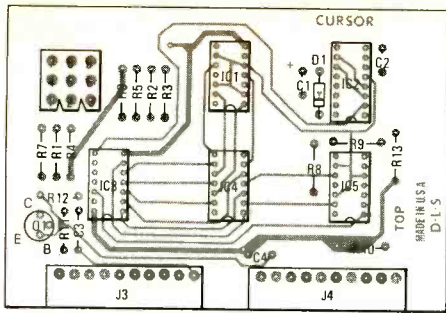


FIG. 2—COMPONENT PLACEMENT diagram.

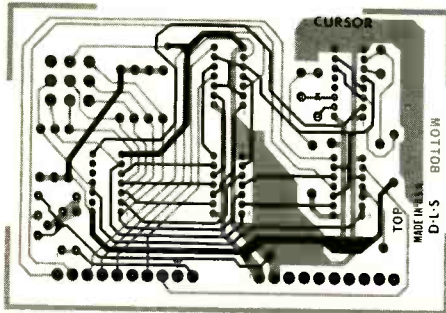

X-RAY VIEW of the double-sided printed circuit board.

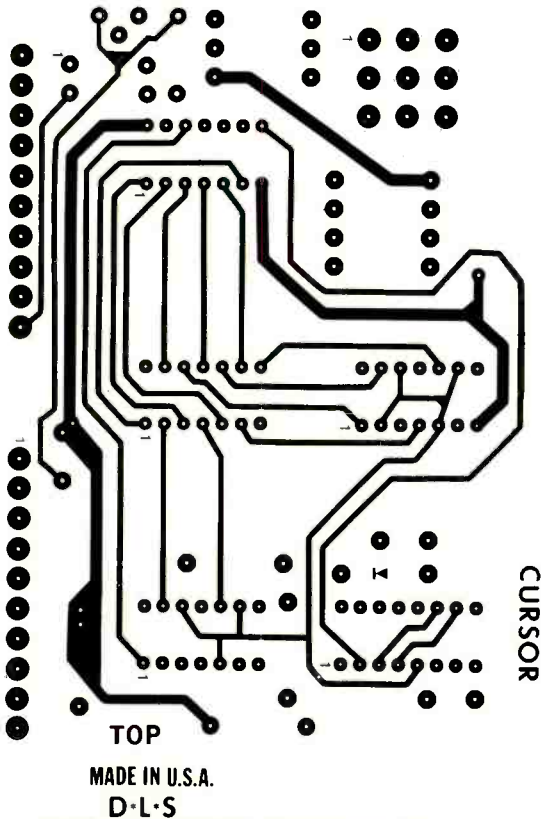


FIG. 3—FOIL PATTERN of component side of double-sided board shown full size.

transistor and connector correctly. Figure 2 shows the component layout. The connector is notched and must be installed exactly as shown in the component side of the foil pattern (Fig. 3). There is a provision for an indexing key on the mounting connectors, J3 and J4, so after soldering the connectors insert a nylon plug in J3 pin 9. This pin is marked with an arrow on the foil side of the board (See Fig. 4). If you have

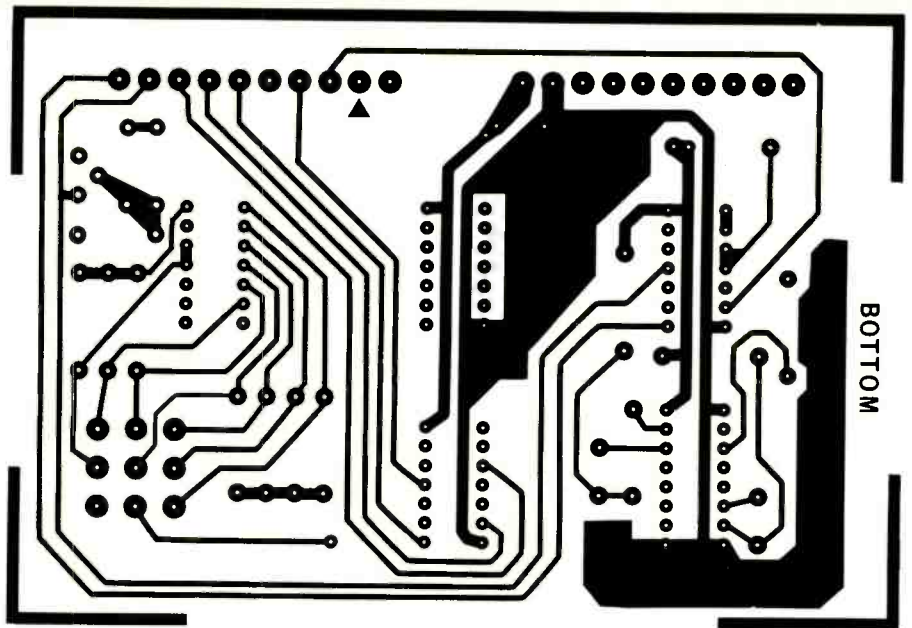


FIG. 4—FOIL PATTERN of foil side of double-sided board shown full size.

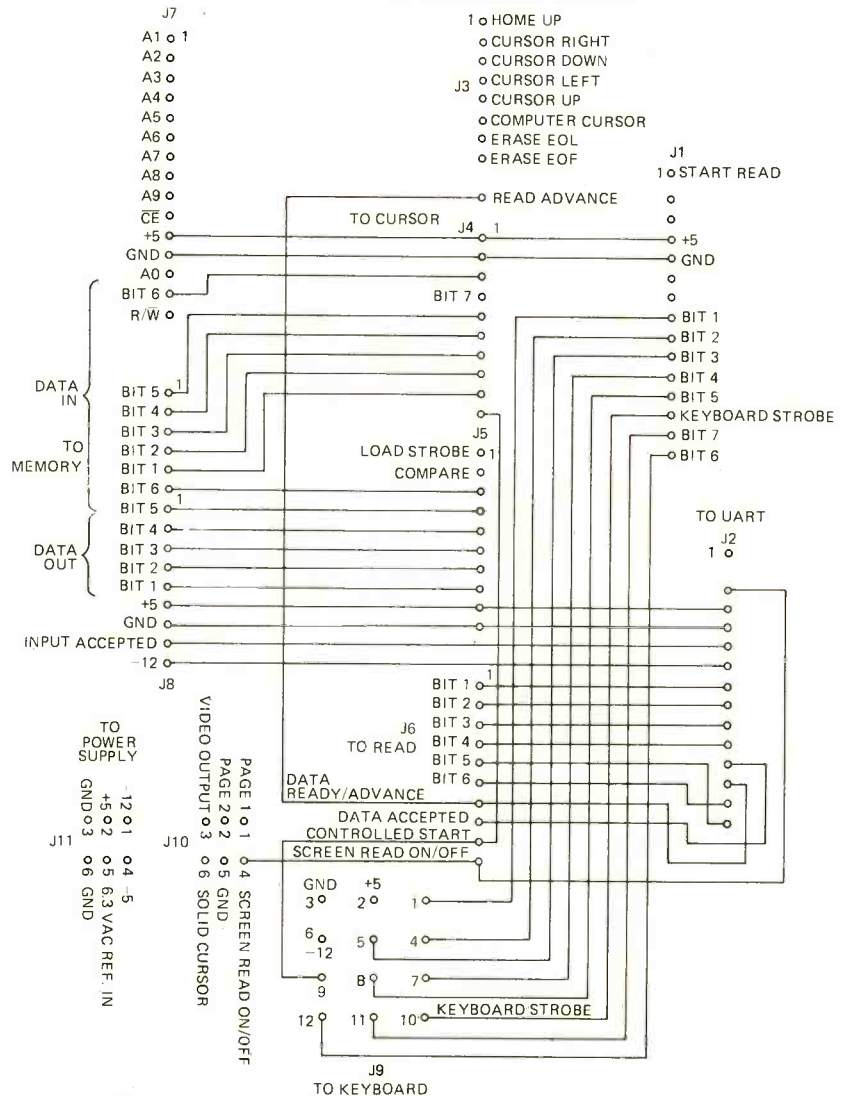


FIG. 5—JACK INTERCONNECTION DIAGRAM of TV Typewriter II.

any problems, check to see if the cursor board is working correctly by checking it with a voltmeter and scope. If your TV Typewriter II has never been used, be sure to check it out first without the

cursor board. The cursor board should not be plugged in until the main board has been thoroughly checked out. The jack interconnection diagram of TV Typewriter II is shown in Fig. 5. R-E

# S Q U A R E W A V E S

## and Audio Performance

*Square waves can quickly identify amplifier limitations. Here are some interesting facts regarding the use of square wave testing and interpretation of the results.*

by LEN FELDMAN

DESPITE THE STRIDES THAT HAVE BEEN made in recent years in improving audio amplifier performance, there are still many vague areas left in attempting to define *all* the desirable qualities of an audio amplifier. Why, for example, can two amplifiers with identical power output ratings, frequency response and low distortion (harmonic as well as intermodulation) "sound" different when auditioned on an A-B basis? For that matter, why is it possible to detect differences in "amplifier sounds" when, in fact, distortion produced by speaker systems is far greater than the almost unmeasurable percentages of distortion produced by the amplifiers that are used to drive those speakers?

These and other subjects which might be classified as "audio philosophy" occupied an entire afternoon, recently, when a group of editors and audio journalists attended a round-table discussion at the offices of Harman-Kardon Company, in Plainview, Long Island. Readers who have followed the literature on audio over the last decade will know that Harman-Kardon is a staunch supporter of the "wideband" school of thought when it comes to amplifier design. That is, they firmly believe that an amplifier must have uniform frequency and phase response from well below the lowest frequency we can hear to as high as five-times the arbitrary 20 kHz frequency that is normally considered to be the high-end of human hearing.

Countering this point of view are such well-known companies as Bose Corporation (they deliberately restrict their amplifier's response), who maintain that phase shift of complex waveforms above certain frequencies are inaudible. Taking a middle-of-the road view, the makers of the Accuphase line

of components (distributed by Teac Corporation of America) maintain that a frequency response range from 20 Hz to 20 kHz is sufficient. But, in a statement of basic engineering policy they go on to say, "What is more important as far as frequencies beyond human hearing are concerned, is "phase characteristic", to prevent overshoot distortion and vibration with input pulses within the audible range. This problem extends to several hundred kHz, so we cannot be content with a flat frequency response that is only wide."

While we do not propose to "take sides" in this never-ending controversy, some interesting facts regarding the use of square wave testing and interpretation came to light as we were discussing Harman-Kardon's new *Citation 16* power amplifier, shown in Fig. 1. This amplifier boasts a square wave rise time of better than 3 microseconds and the choice of output devices and low-level amplifying transistors used in the amplifier result in an overall slew-rate of 30 volts-per-microsecond. The significance of both of these specifications will become clear shortly.

### Square waves and music

Music is composed predominantly of sine waves, but these are rarely heard

as *separate* sine waves. A sound produced by a musical instrument (or a voice) is a combination of sine waves at different frequencies. The fundamental frequency identifies the basic pitch of the sound while the harmonics, generally of lower amplitude, determine its timbre. It is clear that a musical sound, even in its simplest form, is much more complex than the pure sound waves audio engineers and technicians use to measure power output, distortion and frequency response of an amplifier. The people at Harman-Kardon (and engineers from many other audio firms) feel that the square wave is a more useful signal for measuring amplifier performance. It is constant, periodic and repeatable like a sine wave, but its added usefulness is a direct function of its similarity to a musical sound. Square waves, too, are composed of fundamental frequencies and harmonics. The harmonics are arranged in a specific amplitude relationship to one another and are further related with respect to time—all harmonics being "in phase" with each other. The slightest change of amplitude or phase of any of the harmonic components of a square wave will alter its shape. Testing audio products with square waves can therefore illustrate such characteristics as phase response, transient response, frequency response and certain forms of instability if one understands the output waveforms displayed on an oscilloscope.

### Transient intermodulation distortion

A new form of distortion has recently been given much attention in analyzing the performance of audio amplifiers. It is called transient intermodulation distortion and many experts now feel that it is responsible for much of the stridency that critical lis-

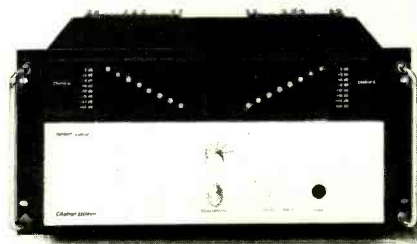


FIG. 1—HARMAN-KARDON CITATION 16 power amplifier. Design emphasis was on wide-bandwidth and linear phase response.

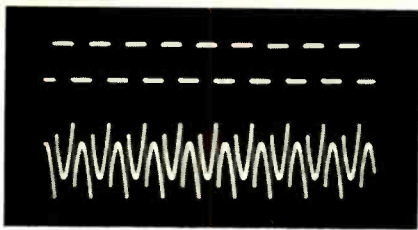


FIG. 2—20-Hz SQUARE WAVE with fundamental frequency filtered out is shown in lower trace.

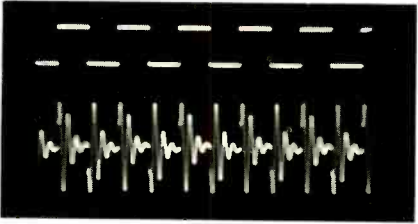


FIG. 5—FILTERING out the fundamental and third harmonic from this 1-kHz square wave makes the waveform look remarkably like "musical" waveforms often seen on monitoring scopes.

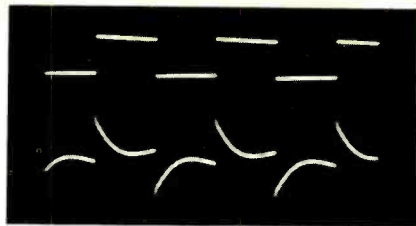


FIG. 3—ROLL-OFF at sub-sonic frequencies distorts 20-Hz square wave.

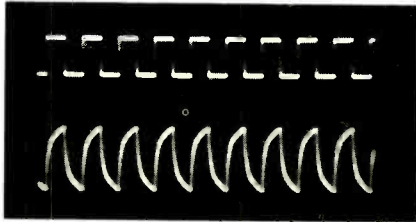


FIG. 6—ROUNDING of leading and trailing edges of 10-kHz square wave results when the bandwidth of the amplifier is limited.

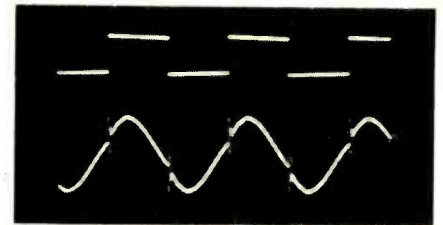


FIG. 4—A 20-Hz SQUARE WAVE contains frequencies at or beyond the high-frequency limits of human hearing.

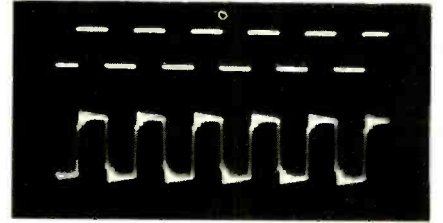


FIG. 7—HIGH-FREQUENCY square waves are useful in detecting amplifier instability with reactive loads.

teners have sometimes associated with solid-state amplifiers. All semiconductors have a limitation in their ability to follow very rapid signal fluctuations or transient pulses. Unlike vacuum tubes that, in theory at least, are controllable at speeds approaching the speed of light (or the speed of the electron flow in a vacuum), solid-state transistors have a fixed slew-rate that determines the length of time an amplifier will be in saturation when a transient waveform is applied to it. This saturation and its associated hysteresis are considered to be the prime factors in the generation of transient intermodulation distortion.

An audio amplifier possessing feedback is driven by the difference signal that results from the combination of the original input waveform and the portion of the output waveform used for negative feedback. If the slew-rate of an amplifier is less than that called for by a steep transient input signal, the output will lag behind the input, and the difference between the feedback and input signals may then exceed the dynamic range of the input stage. A period of input-stage saturation will result during which the amplifier's output will no longer be identical in shape to its input. The condition will continue until the amplifier's output "catches up" to the input signal. This sort of amplifier limitation can also be readily perceived in examining high-frequency square waves.

### Square wave analysis

The square wave photos that appear in this article were not taken by comparing input and output waveshapes from any audio power amplifier, for no single audio amplifier could possibly produce all the waveform distortions we hoped to demonstrate. Instead, we

availed ourselves of the Soundcraftsmen model RP-2212 audio equalizer that permitted us to alter frequency response drastically to create the effects we wished to analyze. For example, we could apply a square wave of known frequency and attenuate only that frequency so that the output waveform would contain all the harmonics of the squarewave minus the fundamental. Such a waveform is shown in Fig. 2. In this and all subsequent photos, the upper waveform is the input signal while the lower waveform is the output signal. No actual amplifier is likely to produce the waveform of Fig. 2, since frequency-response non-linearity in an audio amplifier occurs gradually rather than as an abrupt "notch" which was used to produce this effect.

The waveform shown in Fig. 3 is more typical of what may be encountered, to varying degrees, with an amplifier that has a limited low-frequency response below 20 Hz. The frequency of the input signal was also 20 Hz. This is an extreme case where the "slope" or "tilt" of the normally horizontal portion of the square wave is severe and the square wave begins to look like an interrupted sinewave. Until recently, the response of an amplifier to a 20-Hz square wave input signal was considered unimportant by most audio designers. With the advent of DC-coupled amplifier designs, it became possible to extend low-frequency response all the way down to DC, if desired, and many astute listeners maintain that flat sub-sonic response *does* make a difference when listening to bass content of music. Harman-Kardon believes that phase-shift is an audible form of distortion that masks and muddies music. Excessive phase-shift at low frequencies, they claim, muddies the music and causes bass and mid-bass sounds to lose their

clarity and transparency and to become dull and boomy.

Just to convince ourselves (and you) that even a 20 Hz square wave contains very high frequencies, we adjusted our filters on the equalizer so that all frequencies but the 20 Hz fundamental and the very highest octave (10 kHz and above) were attenuated, while the two frequency regions of interest were boosted as much as the controls would permit. The results are shown in Fig. 4. As expected, we see the fundamental 20-Hz signal represented almost as a pure sine wave. We can also clearly see tiny bursts of a very high-frequency signal. This high-frequency signal shows a frequency content in the output signal above 10 kHz!

At mid-frequencies and above, phase-shift and low-frequency loss in an amplifier are rarely a problem. Nevertheless, to illustrate the similarity between mid-frequency square waves and musical tones, we eliminated the fundamental and the third harmonic of a 1 kHz square-wave. The output waveform, shown in the lower trace of Fig. 5, strikes a familiar note (pardon the pun) for anyone who has watched musical waveforms displayed on a scope for any length of time. What we see are all the higher-order harmonics of the square wave, clearly visible now that the fundamental and third harmonic contributions are eliminated from the signal.

High-frequency square waves are used to quickly determine the upper limits of bandwidth in an amplifier. To accurately reproduce 10-kHz square waves through an amplifier, the amplifier must be capable of handling at least the eleventh harmonic of that fundamental frequency (110 kHz) in the correct phase and amplitude relation-

(continued on page 115)



1

## Tests Radio Shack Model QTA-770

by **LEN FELDMAN**  
CONTRIBUTING HI-FI EDITOR

THE REALISTIC LINE OF HIGH-FIDELITY COMPONENTS (and other electronic products) is manufactured for the Radio Shack chain of electronic stores located throughout the United States. Such products are commonly referred to in the trade as "private label" components, as opposed to "name brand" components which are manufactured by well known firms around the world who sell to a variety of retail outlets. Radio Shack sells only its own Realistic brand of merchandise in this category.

An overall view of the front panel of this quadruphonic receiver is shown in Fig. 1. The panel is equipped with the now familiar slide-rule blacked-out dial area with calibrated FM and AM scales plus a "0 to 100" logging scale for convenient pin-pointing of stations. The single tuning meter at the right of the dial scale is normally illuminated in white, but if the useful AUTO-M (for Auto-Magic) pushbutton is depressed, lighting changes to light green when a station is locked-in, indicating proper center-tuning. This novel automatic frequency-control circuit is deactivated by simply touching the tuning knob at the right. When the Auto-Magic feature is used, the words "Auto Magic" appear near the tuning meter and meter illumination changes to white so long as the user is tuning or touching the knob. When the signal strength meter indicates best tuning, releasing the knob causes the AFC circuit to "pull in" for best tuning and the meter color changes to green. Further use of colored illumination is made

by having the illuminated dial pointer change to a bright red color whenever a stereo station is tuned to. A closeup view of this area of the panel is shown in Fig. 2.

Along the center portion of the front panel are pushbuttons for power on/off, main and remote speaker system selection, high and low filter selection, loudness circuit activation, FM interstation muting, tape monitor circuit and the aforementioned AUTO-M switch. A pair of lights indicate the playing of a discrete CD-4 recording and also of stereo (or matrix 4-channel) discs. At the extreme right of


the panel are two slide controls for adjusting front and rear channel volume.

Other controls located along the lower edge of the panel include BASS, MIDRANGE and TREBLE tone controls, program SELECTOR switch, front channel and rear channel BALANCE controls (left-right), a MODE switch and a four position control that Radio Shack calls Auditorotor. The AUDIOTOR control permits the listener to shift channel locations in 90 degree increments—all around the listening room. The MODE switch has positions for discrete 4-channel listening, matrix SQ decoding, stereo listening (in which front and rear speakers reproduce the same program information), a QUATRAVOX position: that synthesizes 4-channel sound from 2-channel program sources and a MONO position. A closeup view of the tone control area of the panel is shown in Fig. 3.


The speaker connection arrangement on the rear panel, shown in Fig. 4, permits connection of two quartets of speakers for main and remote quadruphonic listening. Main speakers can be connected either by stripping cable ends in the usual manner or by equipping cable ends with standard phono-tip pin plugs. The latter method has the advantage of "permanent" reconnection of speakers in proper phase, once that correct phase has been established.



3

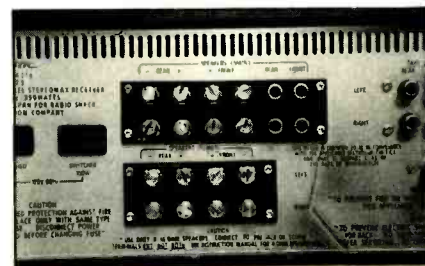

4

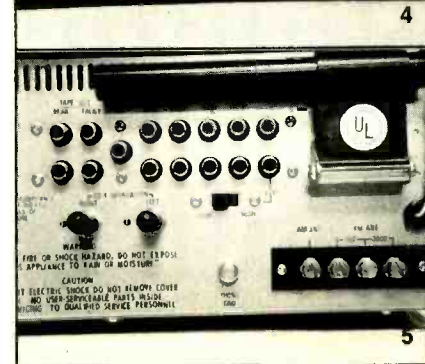

5

### SUMMARY OF MANUFACTURER'S SPECIFICATIONS:

#### TUNER SECTION: (FM)

IHF Sensitivity: 1.9  $\mu$ V. S/N Ratio: 60 dB. Selectivity: 60 dB. Capture Ratio: 1.5 dB. Harmonic Distortion: (Mono): 0.8% or better; (Stereo): 1.0% or better. Image Rejection: 60 dB or better. Stereo Separation: 35 dB at 1 kHz.

#### TUNER SECTION: (AM)

Sensitivity: 250  $\mu$ V/meter. Image Rejection: 50 dB.


#### AUDIO AMPLIFIER SECTION:

Continuous Power Output: (4-channels driven, 8 ohm loads, 20 Hz to 20 kHz): 25 watts per channel. Rated Harmonic Distortion: 1.0%. Rated IM Distortion: 1.0% Frequency Response: 20 Hz to 20,000 Hz. Signal-to-Noise Ratio: (Phono) 60 dB; (Aux.): 70 dB.
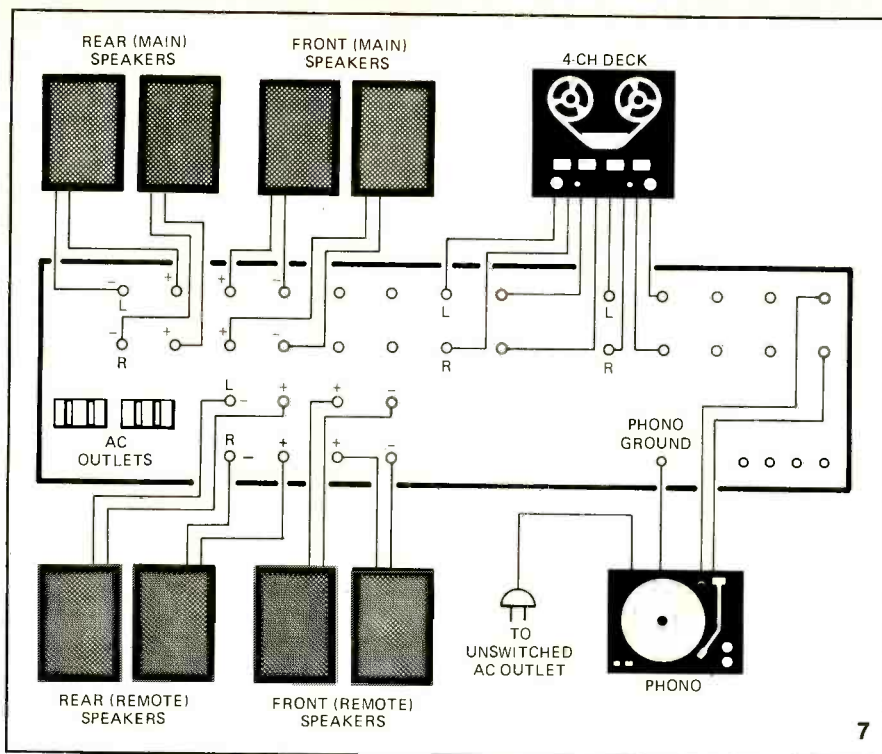
#### GENERAL SPECIFICATIONS:

Power Requirements: 120 VAC, 60 Hz. Dimensions (measured by R-E): 19 $\frac{1}{4}$ " wide by 6" high by 14" deep. Suggested retail price: \$600.00






Antenna connections are provided for 300-ohm and 75-ohm FM and external AM. TAPE IN and TAPE OUT jacks, AUX input jacks and PHONO inputs are logically arranged on the rear panel along with an output jack for future use with FM 4-channel decoders and a pair of CD-4 separation adjustment controls that come capped to prevent accidental altering of optimum control settings. While there is only one pair of phono inputs, a slide switch adjusts input sensitivity to match low- and high-output cartridges. This section of the rear panel is shown in Fig. 5, in which the phono ground terminal is also clearly seen. The rear panel is also fitted with a pivotable AM ferrite bar antenna and switched and unswitched AC receptacles.

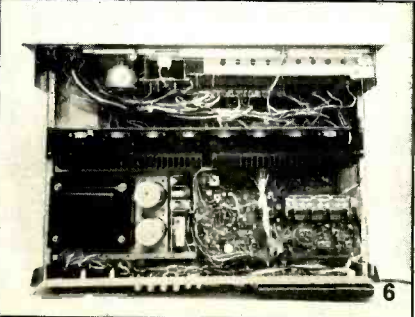**Circuit configuration and features**

There are five major circuit board modules in the QTA-770, all of them well supported mechanically. The eight output power transistors seem adequately heat-sunked with fin-type heat sinks running the full width of the chassis. The front end of the receiver uses a dual-gate MOS-FET transistor and a four-gang variable capacitor. The FM IF section uses ceramic filters between stages and contains three IC's plus two bipolar transistors. FM detection is accomplished by a conventional



ratio detector. The multiplex stereo decoder contains a phase-locked-loop IC circuit that requires no tuning coils. The CD-4 demodulator board is perhaps the most elaborate circuit of all containing no less than 31 bipolar transistors, 4 FET's and 2 IC's. The SQ decoding function is performed primarily by the familiar Motorola MC-1312P chip designed for that purpose. No logic enhancement circuits are included, and the matrix parameters are changed to provide the stereo-to-4-channel synthesis feature.

Tone control circuitry is of the popular feedback type. Power amplifiers have differential amplifier input stages and are direct coupled to speakers, using  $\pm 33$ -VDC supply voltage derived from a full-wave bridge rectifier with primary filtering accomplished by 8000  $\mu$ F capacitors. Protective circuitry includes a thermal switch that turns off all power to the receiver in the event of a thermal overload. An internal view of the chassis is shown in Fig. 6. A diagram of possible interconnection of additional components is shown in Fig. 7.

**FM tuner section measurements**  
Results of our FM performance measurements are listed in Table I. Radio

**TABLE I**  
**RADIO-ELECTRONICS PRODUCT TEST REPORT**

Manufacturer: **Realistic (Radio Shack)** Model: **QTA-770**

**FM PERFORMANCE MEASUREMENTS**

**SENSITIVITY, NOISE AND FREEDOM FROM INTERFERENCE**

	R-E MEASUREMENT	R-E EVALUATION
IHF sensitivity, Mono ( $\mu$ V)	2.5	Acceptable
Sensitivity, Stereo ( $\mu$ V)	11.0	Acceptable
50 dB quieting signal, Mono ( $\mu$ V)	3.5	Very good
50 dB quieting signal, Stereo ( $\mu$ V)	50.0	Acceptable
Maximum S/N ratio, Mono (dB)	74	Excellent
Maximum S/N ratio, Stereo (dB)	61	Very good
Capture ratio (dB)	1.5 dB	Very good
AM suppression (dB)	50	Good
Image rejection (dB)	70	Very good
IF rejection (dB)	80	Very good
Spurious rejection (dB)	85	Very good
Alternate channel selectivity (dB)	60	Good

**FIDELITY AND DISTORTION MEASUREMENTS**

Frequency response, 50 Hz to 15 kHz ( $\pm$ dB)	0.8	Very good
Harmonic distortion, 1 kHz, Mono (%)	0.18	Excellent
Harmonic distortion, 1 kHz, Stereo (%)	0.38	Very good
Harmonic distortion, 100 Hz, Mono (%)	0.12	Excellent
Harmonic distortion, 100 Hz, Stereo (%)	0.21	Excellent
Harmonic distortion, 6 kHz, Mono (%)	0.24	Very good
Harmonic distortion, 6 kHz, Stereo (%)	1.4	Acceptable
Distortion at 50 dB quieting, Mono (%)	0.65	Very good
Distortion at 50 dB quieting, Stereo (%)	0.58	Very good

**STEREO PERFORMANCE MEASUREMENTS**

Stereo threshold ( $\mu$ V)	11	Good
Separation, 1 kHz (dB)	39	Very good
Separation, 100 Hz (dB)	42	Excellent
Separation, 10 kHz (dB)	23	Good

**MISCELLANEOUS MEASUREMENTS**

Muting threshold ( $\mu$ V)	12	Fair
Dial calibration accuracy ( $\pm$ kHz @ mHz)	-200, 88	Fair

**EVALUATION OF CONTROLS, DESIGN, CONSTRUCTION**

Control layout	Good
Ease of tuning	Excellent
Accuracy of meters or other tuning aids	Fair
Usefulness of other controls	Good
Construction and internal layout	Very good
Ease of servicing	Good
Evaluation of extra features, if any	Very good

**OVERALL FM PERFORMANCE RATING** Good

# Build it yourself...

With a learn-at-home program as fascinating as home entertainment electronics, reading about it is just not enough!

Once you discover something that really fascinates you, no matter what it is, reading about it is just not enough. You want to be involved. You want firsthand experience.

That's exactly how Bell & Howell Schools' exciting learn-at-home program in electronics works. You learn by doing, experimenting, trying it yourself. That's why throughout this unique program you get practical "hands on" experience with some of today's latest electronics training tools.

**Throughout your learning adventure with Bell & Howell Schools, the key word is build.**

It doesn't matter if you've never had any training in electronics before. We start you off with the basics and help you work your way up one step at a time. As a matter of fact, with your very first lesson, you receive a special Lab Starter Kit to give you immediate working experience on equipment as you are picking up the fundamentals. It makes the learning process faster and certainly a lot more interesting.

You'll build and work with remarkable educational tools as you explore advances in electronics—"State-of-the-art" equipment that's being used today—and will be used tomorrow. So the skills and knowledge you will acquire will be useful for years to come.

**You'll build your own electronics laboratory!**

With Bell & Howell's Electro-Lab® electronic training system—theory comes to life. And you'll make it happen! In building each of these modern test instruments you'll get experience in wiring, soldering, assembling. Then you'll use the lab for testing, trouble-shooting and circuit analyzing.

First, the **design console**. After you assemble it, you'll be able to set up and examine circuits without having to solder them in place.

Next, you'll build a **digital multimeter**. This important instrument measures voltage, current and resistance, and displays its findings in big, clear numbers like on a digital clock.

Then comes the **solid-state "triggered sweep" oscilloscope** similar in principle to the kind used in hospitals to monitor heartbeats.

You'll use it to analyze tiny integrated circuits. The triggered sweep feature locks in signals for easier observation.

**You'll actually build and work with the new generation color TV...investigating features you've probably never seen before!**

This 25" diagonal color TV has digital features that are likely to appear on all TV's of the future. Features made possible by the applications of digital electronics to home entertainment.

You'll probe into the technology behind all-electronic tuning. And into the digital circuitry of channel numbers that appear on the screen! You'll build-in an on-the-screen digital clock and learn to program a special automatic channel selector that

goes directly to the channels of your choice.

You'll also better understand the exceptional color clarity of the Black Matrix picture tube, and gain working knowledge of "state-of-the-art" integrated circuitry and the 100% solid-state chassis.

**After building and experimenting with this TV, you'll be equipped with the kinds of skills that could put you ahead in electronics know-how.**

Once you've completed this program, your skills in electronic trouble-shooting could lead you in exciting new directions. While we cannot offer assurance of income opportunities you can use your training: to seek out a job in the electronics industry, to upgrade your current job, or as a foundation for advanced programs in electronics.

**Building. Learning. Growing. Without missing a day of work or a single paycheck!**

Because this is a home study program, you study at your convenience—without being a classroom captive. That means there'll be no conflicts with your job or other interests.

And even though you're on your own, we'll be there to help if you should ever run into a rough spot. Most schools make you mail in all your questions. We have a toll-free line you can call when you have a question that can't wait.

For even more personal attention, Bell & Howell Schools' "help sessions" are held in 50 major cities at various times throughout the year, where you can meet and talk with your instructors and fellow students.

**A school's reputation can't be built on what it is going to do.**

...but rather on what it has done and is doing right now. That's why Bell & Howell Schools' 43 years of experience in electronics home study is your best guarantee that our "hands-on" learning method really works.

Many thousands of people each year choose Bell & Howell Schools' home learning programs to start or further their electronics education. Discover this fascinating program in home entertainment electronics for yourself.

**Mail in the postage-paid card for full details!**

Taken for vocational purposes, this program is approved by the state approval agency for Veterans' Benefits.

If card has been detached, please write to:

An Electronics Home Study School  
DEVRY INSTITUTE OF TECHNOLOGY

ONE OF THE



**BELL & HOWELL SCHOOLS**

4141 Belmont, Chicago, Illinois 60641

727/8R



"Electro-Lab®" is a registered trademark of the Bell & Howell Company

Simulated TV test pattern.

Shack chooses to list very few operating specifications in their owner's manual, but a few comparisons between published and measured results are possible. While the tuner section did not meet its 1.9  $\mu\text{V}$  sensitivity figure, the 2.5  $\mu\text{V}$  figure obtained is deemed adequate in this price range and the 3.5- $\mu\text{V}$  50-db quieting point is very good. Ultimate S/N at high signal-levels was excellent for mono and very good for stereo. Distortion levels are quite low for both mono and stereo and, while we generally are suspicious of AFC circuits (they often add distortion and, being first-order closed loop feedback circuits, usually "tune" somewhat off-center) we must admit that the AFC circuit as incorporated in the Auto-Magic feature of the QTA-770 tuned so close to perfect center-of-channel that we could not improve upon observed distortion figures by tuning manually (with the feature defeated). Muting threshold might have been set a bit lower, in our view, so that weaker stations could be received without having to defeat the convenience of silent interstation tuning.

### Amplifier performance measurements

Basic amplifier and preamplifier performance measurements are listed in Table II. It should be noted that in the STEREO MAX position of the front panel MODE switch, the rear and front pairs of channels are paralleled or "strapped" together to provide approximately double the output power available from each channel in the 4-channel mode. We checked this feature at mid-frequencies only and found that in the "strapped" setting, the QTA-770 delivered 55 watts per channel at rated distortion. In the more commonly used 4-channel configuration, at mid-band frequencies, power output exceeded claims by a wide margin and met claims nearly exactly at the low frequency (20 Hz) extreme. At lower output power levels, THD and IM tend to rise slightly but remain below the rated 1.0% figure all the way down to 250 milliwatts, as required in the new Federal Trade Commission standards on amplifier power and distortion ratings. Very little increase in power capability was noted with 4-ohm loads, so a user might just as well select 8-ohm speakers for use with this instrument to insure output-circuit protection when using either a single or double set of speakers.

A serious failing of the phono preamplifier section is its inability to accept high levels of input signals from the phono cartridge without first-stage overload distortion. Even in the low sensitivity setting, overload occurs at an input signal level of 25 mV—a level which is too low in terms of today's dynamically recorded discs. Users should choose a low output cartridge and possibly operate the receiver in the low-sensitivity position besides. Hum and noise in phono, on the other hand, was quite good—better than claimed. The one saving grace about the overload problem discussed is the fact that when used with a CD-4 cartridge and when playing CD-4 records, the phono input level is likely to be on the low side and less difficulty will be encountered.

Tone controls operated well and sym-



**TABLE II**  
**RADIO-ELECTRONICS PRODUCT TEST REPORT**

Manufacturer: **Realistic (Radio Shack)**

Model: **QTA-770**

### AMPLIFIER PERFORMANCE MEASUREMENTS

POWER OUTPUT CAPABILITY	R-E MEASUREMENT	R-E EVALUATION
RMS power/channel, 8-ohms, 1 kHz (watts)	33	Very good
RMS power/channel, 8-ohms, 20 Hz (watts)	25.5	Acceptable
RMS power/channel, 8-ohms, 20 kHz (watts)	33	Very good
RMS power/channel, 4-ohms, 1 kHz (watts)	34	Good
RMS power/channel, 4-ohms, 20 Hz (watts)	27	Good
RMS power/channel, 4-ohms, 20 kHz (watts)	34	Very good
Frequency limits for rated output (Hz-kHz)	19-44	Very good
<b>DISTORTION MEASUREMENTS</b>		
Harmonic distortion at rated output, 1 kHz (%)	0.1	Good
Intermodulation distortion, rated output (%)	0.03	Excellent
Harmonic distortion at 1 watt output, 1 kHz (%)	0.5	Acceptable
Intermodulation distortion at 1 watt output (%)	0.06	Excellent
<b>DAMPING FACTOR, AT 8 OHMS</b>	20	Good
<b>PHONO PREAMPLIFIER MEASUREMENTS</b>		
Frequency response (RIAA $\pm$ ___dB)	1	Good
Maximum input before overload (mV)	25/16	Poor
Hum/noise referred to full output (dB) (at rated input sensitivity)	67/62	Very good
<b>HIGH LEVEL INPUT MEASUREMENTS</b>		
Frequency response (Hz-kHz, $\pm$ ___dB)	20-20, 1	Good
Hum/noise referred to full output (dB)	86	Excellent
Residual hum/noise (min. volume) (dB)	94	Excellent
<b>TONAL COMPENSATION MEASUREMENTS</b>		
Action of bass and treble controls	See Fig. 8	Very good
Action of secondary tone controls	See Fig. 8	Excellent
Action of low frequency filter(s)	See Fig. 9	Very good
Action of high frequency filter(s)	See Fig. 9	Very good
<b>COMPONENT MATCHING MEASUREMENTS</b>		
Input sensitivity, phono 1/phono 2 (mV)	2.5/1.5	
Input sensitivity, auxiliary input(s) (mV)	250	
Input sensitivity, tape input(s) (mV)	250	
Output level, tape output(s) (mV)	620	
Output level, headphone jack(s) (V or mV)	1.5V	
<b>EVALUATION OF CONTROLS, CONSTRUCTION AND DESIGN</b>		
Adequacy of program source and monitor switching		Acceptable
Adequacy of input facilities		Good
Arrangement of controls (panel layout)		Good
Action of controls and switches		Good
Design and construction		Good
Ease of servicing		Good
<b>OVERALL AMPLIFIER PERFORMANCE RATING</b>		Very good

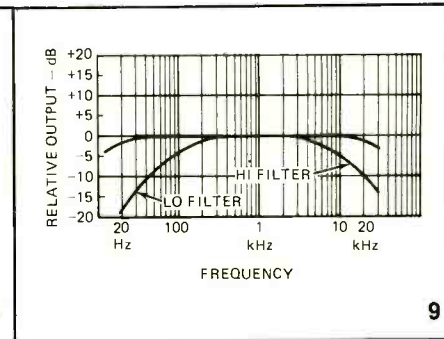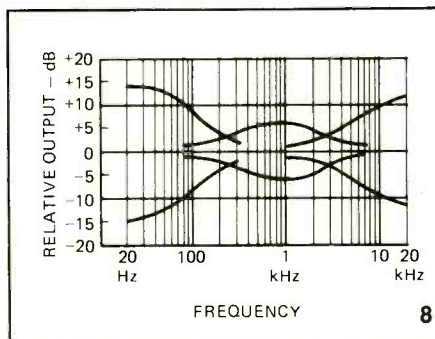

metrically. Response of the tone controls are shown in Fig. 8. The MID-RANGE tone control acts effectively as a presence control and is a useful addition. High and low filter response is shown in Fig. 9 and crossover or cut-off points for both these circuits were ideally set.

### Utilization and listening tests

Most of our listening tests were confined to FM stereo and CD-4. We did play a few SQ and QS matrix records, but as expected, separation is minimal and the listening position becomes quite critical

**TABLE III**  
**RADIO-ELECTRONICS PRODUCT TEST REPORT**

Manufacturer: **Realistic (Radio Shack)**

Model: **QTA-770**

**OVERALL PRODUCT ANALYSIS**

Retail price	<b>\$599.95</b>
Price category	<b>Low-medium</b>
Price/performance ratio	<b>Acceptable</b>
Styling and appearance	<b>Good</b>
Sound quality	<b>Good</b>
Mechanical performance	<b>Very good</b>

Comments: Not every hi-fi enthusiast is willing to spend upwards of \$700.00 for a "state of the art" quadriphonic receiver with sophisticated logic circuitry and a host of extra control features. The Radio Shack QTA-770 offers a reasonable alternative for under \$600. Power output is excellent for the price category. The rotating sound field control (Audio-rotor) seems like an unnecessary frill to us. Even the control-happy audiophile would tire of it after a few moments, and design effort might well have been expended in beefing up the preamplifier input stage. Overall sound quality is good, and the receiver seems reliably built and designed. For better SQ decoding, we would add an external SQ decoder (several good ones are available), since 4-channel emphasis was placed on "discrete" reproduction rather than matrix formats. If you are interested only in a stereo receiver, better value can be had at the price, even considering the stereo strapping feature. But, if you long for quadriphonics at a non-inhibiting price, the QTA-770 may be worth auditioning.

because of the limited separation capability. SQ image placement is particularly ambiguous with this "basic" matrix decoder. CD-4 record reproduction was much better, but we had to experiment with several cartridges to find the one that works best with the receiver. Among those that did well were the Empire 4000/III and the Audio-Technica AT-15S. Our Bang and Olufsen MMC-6000, while an excellent CD-4 pickup when used with other demodulators, did not put out enough 30 kHz carrier signal to properly activate the built-in demodulator of the QTA-770.

FM reception was good and stereo switching was noiseless. We recommend using the Auto-Magic AFC feature for most accurate tuning since the single signal-strength meter is of little help in pinpointing exact center-of-channel tuning. Power output was adequate for our medium-to-low efficiency bookshelf air-suspension speakers. Our capsule summary, along with overall comments, is listed in Table III. **R-E**

# Radio-Electronics®




# Tests Shure Model M95ED

by **LEN FELDMAN**  
CONTRIBUTING HI-FI EDITOR


THE SHURE PEOPLE DESCRIBE THIS NEW cartridge as their "number two" unit in their well accepted line of phono pickups. The implication, of course, is that its performance is second only to their top-of-the-line model V15 Type III which has a suggested retail price of \$72.00. A close-up photo of the cartridge, shown in Fig. 1, confirms a similarity in outer construction between the two cartridges, down to the

pivotable stylus guard. Unlike the more expensive model, long screws are required to mount the cartridge, since these screws traverse the entire depth of the cartridge body. Of course, an assortment of screws and other hardware is supplied in the package, including four tiny terminal connectors (just in case your pickup arm shell is equipped only with loose wires). The easily replaced stylus assembly is color coded in yellow and carries a suggested retail price of \$27.00. A spherical stylus assembly, designated as N95-3, and color coded

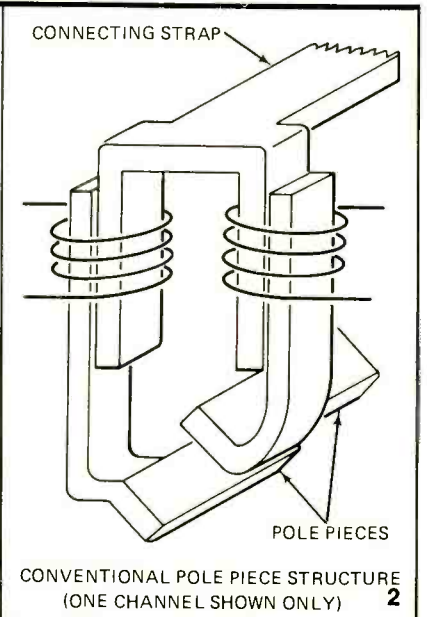


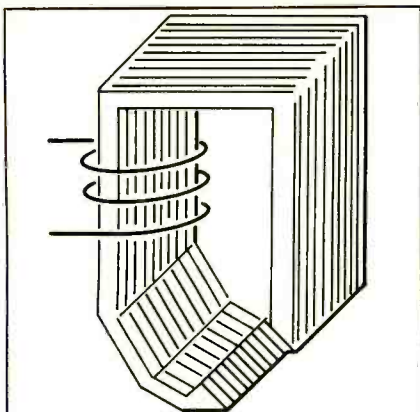**SUMMARY OF MANUFACTURER'S PUBLISHED SPECIFICATIONS:**


**Frequency Response:** 20 Hz to 20,000 Hz. **Tracking Force Range:** 0.75 to 1.5 grams. **Output Voltage:** 4.7 mV per channel at 1 kHz, at 5.0 cm/s peak velocity. **Channel Separation:** 25 dB at 1 kHz. **Channel Balance:** within 2 dB. **Trackability:** 24 cm/s at 400 Hz; 33 cm/s at 1kHz, 28 cm/s at 5 kHz; 19 cm/s at 10 kHz. **Optimum Load:** 47000 ohms in parallel with 400 to 500 pF capacitance per channel. **Stylus Type and Dimensions:** elliptical "nude" diamond tip, .0007" x .0002". **Resistance:** 1550 ohms. **Inductance:** 650 mH. **Weight:** 6 grams. **Mounting Centers:** 0.5 inch. **Suggested Retail Price:** \$59.95.




LAMINATED "POLE PIECE STACK"

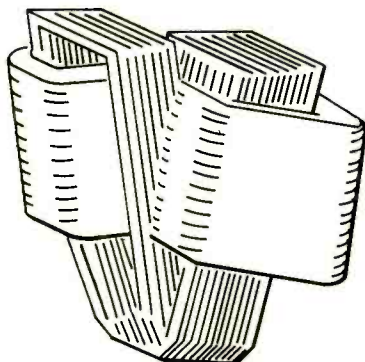

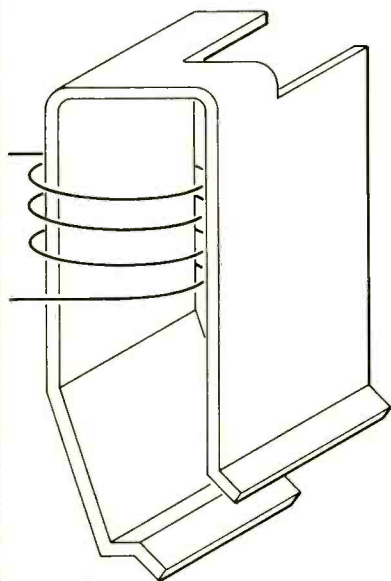"POLE PIECE STACK" ASSEMBLY AS USED IN SHURE V15 III 3



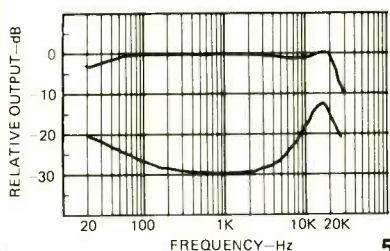POLE PIECE - SINGLE CHANNEL, AS DEVELOPED FOR SHURE M95ED 4



5

**TABLE I**  
**RADIO-ELECTRONICS PRODUCT TEST REPORT**

Manufacturer **Shure Bros., Inc.** Model **M95ED**

**PHONOGRAPH CARTRIDGE MEASUREMENTS**

	R-E Measurements	R-E Evaluation
<b>FREQUENCY RESPONSE</b> (Hz-kHz, $\pm$ — dB)	20, -20, $\pm 2.5$ See Fig. 5	<b>Excellent</b>
<b>STEREO SEPARATION</b>		
Separation, 1 kHz (dB)	28	<b>Very good</b>
Separation, 10 kHz (dB)	16	<b>Good</b>
Separation, 30 kHz (dB)	Not applicable	.....
<b>CHANNEL BALANCE</b> , 1 kHz (dB)	1.8 dB	<b>Good</b>
<b>TRACKABILITY MEASUREMENTS</b>		
Stylus Velocity at 1 kHz (cm/s)	30	<b>Excellent</b>
Stylus Velocity at 10 kHz (cm/s)	18	<b>Very good</b>
<b>COMPONENT MATCHING CHARACTERISTICS</b>		
Output Level, 1 kHz, 3.54 cm/s (mV)	4.5	
Optimum Load Impedance (Ohms)	47,000	
Tracking Force Range (- to - grams)	$\frac{3}{4}$ -1 $\frac{1}{2}$	
Cartridge Weight (grams)	6	
<b>OVERALL PHONO CARTRIDGE RATING</b>		<b>Very good</b>

**TABLE II**  
**RADIO-ELECTRONICS PRODUCT TEST REPORT**

Manufacturer **Shure Brothers, Inc.** Model **M95ED**

**OVERALL PRODUCT ANALYSIS**

Retail Price	<b>\$59.95</b>
Price Category	<b>Medium-high</b>
Price/Performance Ratio	<b>Very good</b>
Styling and Appearance	<b>Good</b>
Sound Quality	<b>Excellent</b>
Mechanical Performance	<b>Very good</b>
Comments:	In one respect, at least, the new Shure M95ED actually offers an advantage over that company's more expensive top-of-the-line V15 Type III phonograph cartridge. It offers approximately 3-dB greater output without an audible sacrifice of fidelity. This can be important if your preamplifier signal-to-noise ratio is marginally acceptable when used with lower output cartridges, since the higher output relates directly to S/N ratio. Since we had access to the more expensive V15 Type III during these tests, we naturally compared listening results between the two models. We could detect virtually no difference in coloration or musical accuracy between the two, despite the slightly better response claimed for the more expensive unit. At equal tracking forces (1 gram), the V15 Type III is able to track somewhat higher recorded velocities, particularly where high-frequency signals are involved, but both units came through Shure's new "obstacle course" test record surprisingly well. Only a rare recording is likely to make greater tracking demands of a cartridge than are within the capability of the new M95ED unit from Shure. We heard no evidence of the high-frequency resonant point of the cartridge, even though it occurs at 19 kHz compared with 23 kHz for the more expensive V15 Type III.

dark green is available for 78 RPM record playing and costs \$11.00.

**Internal construction**

One of the important structural features of the Shure V15 Type III was its laminated pole piece construction. This design eliminated the need for a connecting strap that is usually provided on top of the pole piece structure to provide a path for the magnetic lines of force, as shown in Fig. 2. The continuous-loop pole pieces are laminated together and stacked to form a com-

plete assembly, as used in the V15 Type III is shown in Fig. 3. The M95ED cartridge does *not* have a laminated pole piece but does have a single-piece pole assembly (see Fig. 4). In other words, there is no need for a shorting strap at the top, or a connecting bar. This new magnetic structure arrangement is highly efficient and is, in part, responsible for the higher-than-usual output of the M95ED.

Shure supplied us with a table comparing the effective mass of stylus tips for  
*(continued on page 121)*

# BOOKSHELF SPEAKERS

How To Buy

*Understanding the specifications is the first step.  
But there's more. Knowing how to conduct listening tests,  
speaker placement and room acoustics are just as important.*

by **ARTHUR KLEIMAN**  
ASSOCIATE EDITOR

LAST MONTH, WE COVERED SUCH CONSIDERATIONS as size and the types of enclosures. We also discussed frequency response and dispersion specifications of many speaker systems.

In this article we will look at more specifications including distortion, linearity, efficiency, power-handling capacity, maximum sound output and impedance.

## Distortion is important

There are two types of distortion in speaker systems—harmonic and intermodulation. Both types are directly related to the electromechanical structure of the drivers. In most cases, when one type of distortion is reduced, the other is also reduced. Also, harmonic distortion comprises the majority of the total distortion produced by a speaker system. Therefore, **Radio-Electronics** requested that only a harmonic distortion specification be provided by the manufacturers.

The mechanical sources of distortion affect both halves of the frequency cycle equally. This is similar to a push-pull system. Readers who are familiar with push-pull systems will remember that the even-order components of distortion are cancelled while the odd-order components remain. For this reason, unless the speakers are assembled incorrectly, a speaker system produces the odd-order components only—predominantly the third. Many hi-fi writers insist on referring to this as speaker "doubling". Doubling just doesn't exist. A better term and the correct one is speaker tripling.

Harmonic distortion varies with frequency and amplitude. It increases as the frequency is reduced and the amplitude is increased. It is not unusual for a speaker system to produce as much as 40% or more total harmonic distortion at a frequency of 20 Hz when driven with a 1-watt drive signal. So, don't expect the distortion figures to be preceded by the decimal points and zeros so commonly found in amplifier and tuner specs.

Ideally, distortion should be presented as a frequency versus amplitude graph. Figure 5 shows the harmonic distortion graphs for seven speaker systems manufactured by Acoustical Research, Inc. Figure 6 shows the harmonic distortion graph for a speaker system manufactured by Avid. Unfortunately, space limitations

prevent us from presenting the rest of the specifications from the other manufacturers in that form. Instead, **Radio-Electronics** requested that the manufacturers provide the total harmonic distortion produced at 90-, 95-, and 100-dB SPL (Sound Pressure Level) for any frequency in the audio spectrum. Some manufacturers, however, preferred to

specify the lower frequency limit. This lower frequency limit appears in the chart for those manufacturers that provided us with it. (Remember, these are manufacturers specs and we have no way to authenticate their accuracy.)


If you've ever wondered why a guitar sounds different from a banjo, or a flute sounds different from a trombone, it's the different harmonic content in the musical notes that each instrument produces. Harmonic distortion tends to obscure the musical character. Excessive harmonic distortion garbles reproduced voices. Choose a speaker system with a minimum amount of distortion.

## Linearity graphs

A linearity graph is a plot of input power versus output power (constant frequency) of a speaker system. In effect, this is a plot of efficiency (more about efficiency later on). A speaker system with perfect linearity will produce a straight-line plot. A practical nonlinear speaker system will produce a plot that tends to curve downwards (less efficiency) at the low input-power end of the graph. Figure 7 shows linearity graphs of five speaker systems manufactured by H. H. Scott, Inc. The solid line is the plot of the actual speaker system while the dotted line shows the plot that would be obtained if the speaker system had perfect linearity.

Conceivably, it can be argued that non-linearity of this type can actually increase dynamic range and, therefore, it is good. In effect, it is the compression half of a compression-expansion characteristic. Unfortunately, there is no way to control the amount of nonlinearity and, therefore, the amount of compression that takes place. It would be better to provide compression-expansion through electronic means rather than have it built into the speaker system. Also, some speakers are described as not being able to "open up" unless they are driven to high-output levels. This effect can only be traced to nonlinearity. For these reasons, we treat nonlinearity as a disagreeable effect.

Due to space limitations, the linearity specification is presented as a deviation from the straight-line plot that would be obtained from a speaker system with perfect linearity. It is expressed as a  $\pm$  dB deviation over a range of input power. When considering linearity, look for a speaker system that offers a minimum deviation over the widest range of input power. (text continues on page 70)

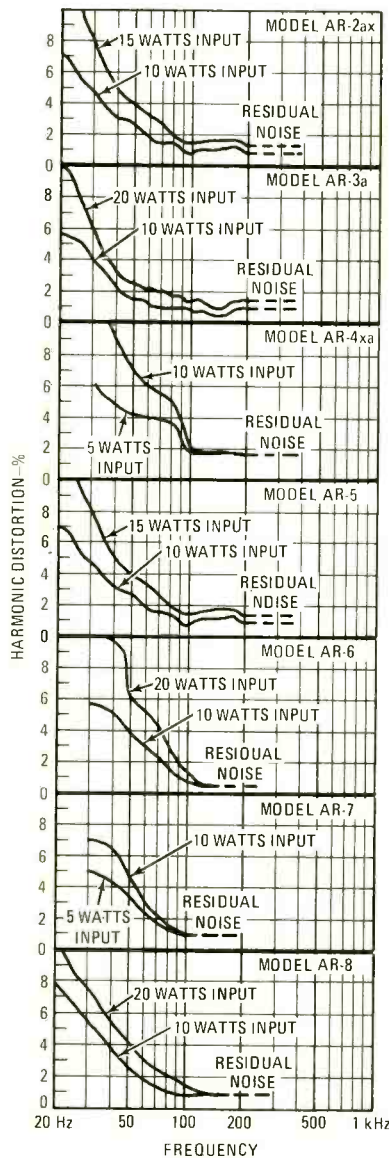

**FIG. 5—HARMONIC DISTORTION CURVES for seven speaker systems from Acoustical Research.**

MANUFACTURER'S SPECIFICATIONS

MANUFACTURER	MODEL	HARMONIC DISTORTION (%) AT ANY FREQUENCY AT SOUND PRESSURE LEVEL UP TO -						LINEARITY		EFFICIENCY dB SPL FOR 1 CONTINUOUS WATT AT 1 kHz MEASURED AT 1 METER ON AXIS	POWER HANDLING CAPACITY						MANUFACTURER'S RECOMMENDED AMPLIFIER POWER RATING		MAXIMUM OUTPUT dB SPL AT 1 METER ON AXIS WITH LESS THAN 3% THD AND 1% DISTORTION FROM 100Hz TO 10 kHz
		90dB			100dB			FROM	TO		CONTINUOUS TONE			INTERMITTENT POWER			MIN RATING RMS WATTS	MAX RATING RMS WATTS	
		90dB	95dB	100dB	± dB	CONTINUOUS WATTS	CONTINUOUS WATTS	CONTINUOUS WATTS	AT ANY FREQ BETWEEN		FOR PERIODS NOT EXCEEDING								
									HERTZ		HERTZ	MINUTES	SECONDS						
ACOUSTIC RESEARCH	AR-2aa	1	2	4	1	0.1	50		25	20	5K	300	0	2	20	130	110		
	AR-5	1	2	4	1	0.1	60		30	20	5K	400	0	2	25	150	112		
	AR-6	1	3	8	1	0.1	45		20	20	20K	200	0	2	20	100	106		
	AR-7	1	2	6	1	0.1	45		20	20	20K	200	0	2	15	100	106		
AUDIOANALYST	A-76X	1.3	1.6	2.8	1	0.5	100		90	32	20	800	450	0	1	10	100		
	A-100X	1	1.3	1.6	0.5	0.5	100		92	36	20	800	450	0	1	10	100		
AVID	100	<1	<1	<2	+0 -1	0	75		86	25	65	8K	75*	1	-	15	75		
AZTEC BY PMDC CORP.	MINUET								88*							10	50		
	OU LANE II								88*							10	70		
	PICASSO								90*							10	70		
BANG AND OLUFSEN	1702	<2.5	<2.5	<2.5						20	50	20K	40*	-	-	4	20		
	2702	<2	<2	<2						25	45	20K	45*	-	-	3.5	25		
	3702	<1	<1	<1						40	40	20K	75*	-	-	3	40		
	4703	<1	<1	<1						60	30	20K	100*	-	-	4	60		
DYNACO	A-10VN								87	30*	-	-				15	50		
	A-25								90	45*	-	-				20	75		
	A-25XL								92	50*	-	-				20	85		
	A-35								90	45*	-	-				20	75		
ESS	AMT-5	5 100Hz- 22 kHz	5 100Hz- 22 kHz	1 100Hz- 22 kHz	3 100- 22 kHz	1	20		92	30	100	1K				20	60		
ELECTRO- VOICE	EV-13A				5				89	20	60	1K	100	0	0.1	10	60		
	EV-14A				5				90	20	50	1K	100	0	0.1	10	60		
	EV-15A				5				91	20	50	700	100	0	0.1	10	60		
	EV-16A				5				92	20	40	700	100	0	0.1	10	60		
	INTERFACE A				5				90	25	32	1500	100	0	0.1	10	60		
HEATH	AS-48									50*	-	-							
	AS-104									60	30	300				10			
IMF	SUPER COMPACT															20	50		
JENSEN SOUND LABS	OPC-21								88*	40*						10			
	OPC-22								90*	45*						10			
	OPC-23								91*	60*						10			
LAFAYETTE RADIO ELECTRONICS	CRITERION 777	1.9	2.9	4.9					90	64	100	9K	310	0	15	15	80		
	CRITERION 888	1.8	2.9	4.8					90	73	100	9K	375	0	15	15	100		
MARANTZ	IMPERIAL 4G			0.9					95	15	40	18K	40	0	30	5	60		
	IMPERIAL 5G			0.7					92	15	35	20K	40	0	30	5	60		
PIONEER	CS-44G								91.5										
	CS-66G								92.5										
	CS-500G								94										
	R-300								92										
	R-500B								91										
	PROJECT 60																		
	PROJECT 80																		
PROJECT 100																			
QUADRA FLEX	RS-3				1	.01	20			20	20	1K	25	0	10	10	50		
	RS-4				1	.01	20			25	20	1K	25	0	10	10	75		
RTR	EXP-8	1	2	3	1	1	20		90	50	40	1K	100	2	0	20	60		
H. H. SCOTT	S-110	0.8 @ 100Hz	0.7 @ 100Hz	0.85 @ 100Hz	0.1	0.55	50		76.7	20	30	20K	60	1	0	10	60		
	S-15	0.8 @ 100Hz	0.8 @ 100Hz	1.5 @ 100Hz	0.1	0.5	25		78.2	20	40	18K	60	1	0	7	50		
	S-42	0.8 @ 100Hz	1.0 @ 100Hz	2.2 @ 100Hz	0.1	0.4	35		81.5	15	40	20K	35	1	0	10	35		
	S-52	0.7 @ 100Hz	0.7 @ 100Hz	0.7 @ 100Hz	0.2	0.5	55		83	20	20	18K	60	1	0	18	60		
	S-61	0.7 @ 100Hz	0.7 @ 100Hz	0.7 @ 100Hz	0.2	0.5	45		79.5	25	20	20K	75	1	0	18	75		
SOUND CELI	SC-100									4.0	15	40K				065	4.5		

NOTES:  
 \* SPECIFICATION NOT MEASURED PER SPECIFIED CONDITIONS  
 \*\* PRICE SLIGHTLY HIGHER ON WEST COAST  
 † PRICE INCLUDES EQUALIZER  
 †† KIT FORM  
 BLANK SPACES INDICATE SPECIFICATIONS NOT PROVIDED BY MANUFACTURER.



MANUFACTURER'S SPECIFICATIONS

IMPEDANCE			WOOFERS			MID-RANGE			TWEETERS			OPERATING PRINCIPLE	MANUFACTURER'S RECOMMENDED ORIENTATION (HORIZONTAL, VERTICAL)	MANUFACTURER'S RECOMMENDED POSITION	SIZE (INCHES)			WHT (LBS)	PRICE		
NOMINAL	MIN	MAX	TOTAL NO.	SIZE	TYPE	TOTAL NO.	SIZE	TYPE	TOTAL NO.	SIZE	TYPE				H	W	D				
DHMS	DHMS	Hz	DHMS	Hz		DHMS	Hz		DHMS	Hz											
8					1	254 mm	CONE	1	89 mm	CONE DAMPED	1	19 mm	DOME	ACOUSTIC SUSPENSION	EITHER	CTR MID-WALL	13 1/2	24	11 1/2	36 1/2	\$165.00 EACH
8					1	754 mm	CONE	1	38 mm	DOME	1	19 mm	DOME	ACOUSTIC SUSPENSION	EITHER	CTR MID-WALL	13	24	11 1/2	39	\$215.00 EACH
8					1	203 mm	CONE	0	-	-	1	32 mm	CONE	ACOUSTIC SUSPENSION	EITHER	CTR MID-WALL	12	19 1/2	7	20	\$89.00 EACH
8					1	203 mm	CONE	0	-	-	1	32 mm	CONE	ACOUSTIC SUSPENSION	EITHER	CTR MID-WALL	9 3/4	15 3/4	6 1/4	11	\$75.00 EACH
8	6	140	18	52	1	10 in.	CONE	0	-	-	1	2 in.	RING	ACOUSTIC SUSPENSION	EITHER	MID-WALL	12 1/4	21	10 1/2	30	\$84.00 EACH
8	6.5	115	25	48	1	10 in.	CONE	1	2 in.	RING	1	1 1/2 in.	DOME	ACOUSTIC SUSPENSION	EITHER	MID-WALL WOOFER AT EAR LEVEL	13 3/4	24	12	37	\$138.00 EACH
8	8.8	200	21	60	1	8 in.	CONE	0	-	-	1	3/4 in.	CONE	AIR SUSPENSION	EITHER	MID-WALL	12 3/4	21	8 1/2	22	\$85.00 EACH
8	6	150	26	65	1	8 in.	CONE	0	-	-	1	3 in.	RING	ACOUSTIC SUSPENSION	NOT CRITICAL	NOT CRITICAL	18	11	9 3/8	19	\$75.00 EACH
8	5	50	15	23	1	10 in.	CONE	0	-	-	1	3 in.	RING	ADJUSTABLE DISTRIBUTED BASS-REFLEX PORTED	NOT CRITICAL	NOT CRITICAL	23	13 1/2	9 3/8	30	\$108.00 EACH
8	7	55	30	20	1	10 in.	CONE	1	6 in.	CONE	1	3 1/2 in.	HORN	ADJUSTABLE DISTRIBUTED BASS-REFLEX PORTED	NOT CRITICAL	NOT CRITICAL	23 7/8	13 1/2	11 3/4	38	\$148.00 EACH
4					1	6 in.	-	0	-	-	1	1 in.	DOME	PRESSURE CHAMBER	EITHER	EAR LEVEL IN CORNERS	13	7	7	9	\$170.00 PAIR
4					1	7 in.	-	0	-	-	1	1 1/2 in.	DOME	PRESSURE CHAMBER	EITHER	EAR LEVEL CLOSE TO CORNER	16 1/8	8 1/16	8 1/16	12	\$200.00 PAIR
4					1	8 in.	-	1	3 3/8 in.	-	1	1 in.	DOME	PRESSURE CHAMBER	EITHER	EAR LEVEL IN CORNERS	19 3/4	9 7/8	9 7/8	20	\$250.00 PAIR
4					2	7 in.	-	1	5 in.	-	1	1 in.	DOME	PRESSURE CHAMBER	EITHER	EAR LEVEL IN CORNERS	22 7/8	11 7/16	11 7/16	28	\$440.00 PAIR
8	7	200	24	1200	1	6 1/2 in.	-	0	-	-	1	1 1/2 in.	DOME	APERIODIC ACOUSTIC SLOT	VERTICAL	MID-WALL	15	8 1/2	8	15	\$110.00 PAIR
8	8	150	24	1800	1	10 in.	-	0	-	-	1	1 1/2 in.	DOME	APERIODIC ACOUSTIC SLOT	VERTICAL	MID-WALL	20	11 1/2	10	24	\$82.00 EACH
8	6.5	10K	20	1200	1	10 in.	-	0	-	-	1	1 in.	DOME	APERIODIC ACOUSTIC SLOT	VERTICAL	MID-WALL	20	11 1/2	10	25	\$108.00 EACH
8	6.5	5K	14	70	1	10 in.	-	0	-	-	1	1 1/2 in.	DOME	APERIODIC DUAL CHAMBER	VERTICAL	MID-WALL	22 1/2	12 1/2	10	30	\$128.00 EACH
5	4	120	26	55	1	12 in.	-	0	-	-	1		HEIL AIR-MOTION TRANSFORMER	ACOUSTIC SUSPENSION	HORIZONTAL	FLOOR	24	14 1/2	11 7/8	45	\$158.00 EACH
8	5.5	150	20	75	1	8 in.	CONE	0	-	-	1	2 in.	CONE	SEALED SYSTEM	EITHER	MID-WALL	10	19	8 1/2	15	\$89.95 EACH
8	6	150	20	60	1	10 in.	CONE	0	-	-	1	2 in.	CONE	SEALED SYSTEM	EITHER	MID-WALL	13 1/2	24	11 3/4	36	\$109.95 EACH
8	5	1500	20	60	1	10 in.	CONE	1	5 in.	CONE	1	2 1/4 in.	CONE	SEALED SYSTEM	EITHER	MID-WALL	13 1/2	24	11 3/4	44	\$129.95 EACH
8	5	1500	30	50	1	12 in.	CONE	1	5 in.	CONE	1	2 1/2 in.	CONE	SEALED SYSTEM	EITHER	MID-WALL	14 1/2	25	13 3/4	46	\$148.95 EACH
8	5	32 & 150	23	1500	1	8 in.	CONE	0	-	-	2	2 1/2 in.	CONE	EQUALIZED VENTED SYSTEM	EITHER	MID-WALL	14	22	7 3/4	27	\$450.00 PAIR
8					1	14 in.	-	0	-	-	1	2 in.	-	TUNED PORT, DAMPED REFLEX	EITHER	MID-WALL	14	23 1/2	12	42	\$249.95 EACH
8	6				1	10 in.	-	1	4 1/2 in.	-	1	3 1/2 in.	-	INFINITE Baffle	EITHER	MID-WALL	24	13 1/2	11 1/2	36	\$109.95 EACH
8	7	200	12	55	1	8 in.	CONE	1	5 in.	CONE	1	1 in.	DOME	RESISTIVE TUNNEL/ TRANSMISSION LINE	VERTICAL	ON STAND, AWAY FROM CORNERS	18	11 3/4	11	20	\$200.00 EACH
8	6	200	14	3000	1	8 in.	-	0	-	-	1	2 in.	CONE	ACOUSTIC SUSPENSION	EITHER		18 1/4	11	8 3/8		\$69.00 EA **
8	6	200	14	3000	1	10 in.	-	0	-	-	1	2 in.	CONE	ACOUSTIC SUSPENSION	EITHER		22 1/2	12 1/4	10 3/4		\$89.00 EA **
8	6	3000	11	600	1	10 in.	-	0	-	-	1	1 1/2 in.	DOME	ACOUSTIC SUSPENSION	EITHER		24	13	12		\$128.00 EA **
8	7	95	22	1500	1	10 in.	-	1	6 in.	-	1	2 in.	DOME	ACOUSTIC SUSPENSION	EITHER		23	15	12	36	\$119.95 EACH
8	7	100	22	1500	1	12 in.	-	1	8 in.	-	1	2 in.	DOME	ACOUSTIC SUSPENSION	EITHER		24	15 1/2	12	52	\$169.95 EACH
8	6	200	12	75	1	8 in.	-	0	-	-	1	3/4 in.	-	ACOUSTIC SUSPENSION	EITHER	MID-WALL	19 1/8	11 1/4	8 1/2	20	\$59.95 EACH
8	6	200	16	70	1	8 in.	-	0	-	-	1	3/4 in.	-	BASS REFLEX PORTED	EITHER	MID-WALL	23	12	9 1/2	23.5	\$89.95 EACH
8					1	8 in.	CONE	0	-	-	1	2 9/16 in.	CONE	INFINITE Baffle	EITHER	MID-WALL	17 3/4	11	10 1/4	19	\$79.95 EACH
8					1	10 in.	CONE	1	6 1/2 in.	CONE	1	3 in.	CONE	INFINITE Baffle	EITHER	NEAR CORNER	21 5/8	12 1/2	11 3/8	26	\$119.95 EACH
8					1	10 in.	CONE	1	5 in.	CONE	1	3 in.	CONE	INFINITE Baffle	EITHER	NEAR CORNER	22 1/2	12 3/4	12 3/4	32	\$149.95 EACH
8					1	10 in.	CONE	0	-	-	1	-	HORN	BASS REFLEX	EITHER	NEAR CORNER	22 15/32	13	10 9/16	26	\$119.95 EACH
8					1	10 in.	CONE	1	5 in.	CONE	1	-	HORN	BASS REFLEX	EITHER	NEAR CORNER	24 1/32	12 25/32	12 1/16	38	\$169.95 EACH
8					1	8 in.	CONE	0	-	-	1	2 1/2 in.	HORN	BASS REFLEX	EITHER	NEAR CORNER	18 1/2	10 5/8	8 1/2	11	\$79.95 EACH
8					1	10 in.	CONE	0	-	-	1	1 1/2 in.	DOME	AIR SUSPENSION	EITHER	MID-WALL	20 3/4	11 3/4	11	25	\$89.95 EACH
8					1	10 in.	CONE	0	-	-	1	1 1/2 in.	DOME	AIR SUSPENSION	EITHER	MID-WALL	23	13	10 1/2	40	\$129.95 EACH
8	5.3	200	23.5	65	1	8 in.	-	0	-	-	1	3 in.	CONE	ACOUSTIC SUSPENSION	EITHER	EAR LEVEL	21 1/4	12 3/8	8	26	\$89.95 EACH
6	4	200	7	60	1	10 in.	-	0	-	-	1	3 in.	CONE	ACOUSTIC SUSPENSION	EITHER	EAR LEVEL	23 1/2	13 3/8	11	30	\$89.95 EACH
8	6.5	150	10	20K	1	8 in.	-	0	-	-	1	-	-	ACOUSTIC SUSPENSION	NOT CRITICAL	NOT CRITICAL	11 1/4	19 1/8	8 1/2	25	\$89.95 EACH
8	6.5	5K	16	47	1	10 in.	-	1	4 1/2 in.	CONE	1	1 in.	DOME	ACOUSTIC SUSPENSION	VERTICAL	4 INCHES ABOVE FLOOR, MID-WALL	24	14 1/2	11 1/4	36	\$148.95 EACH
8	6.5	3500	25	70	1	10 in.	-	1	4 1/2 in.	CONE	1	3 in.	CONE	ACOUSTIC SUSPENSION	VERTICAL	4 INCHES ABOVE FLOOR, MID-WALL	23 1/2	11 3/4	9	24	\$134.95 EACH
8	6	2K	20	65	1	8 in.	-	0	-	-	1	1 in.	DOME	ACOUSTIC SUSPENSION	EITHER	10 INCHES ABOVE FLOOR, MID-WALL	22	11 1/4	8 1/2	22	\$79.95 EACH
8	6	150	25	42	1	10 in.	-	0	-	-	1	1 1/2 in.	DOME	ACOUSTIC SUSPENSION	EITHER	4 INCHES ABOVE FLOOR, MID-WALL	24	14 1/2	10 1/2	40	\$114.95 EACH
8	6	6K	30	45	1	10 in.	-	1	4 1/2 in.	CONE	1	1 in.	DOME	ACOUSTIC SUSPENSION	EITHER	4 INCHES ABOVE FLOOR, MID-WALL	25	14 1/2	11 1/2	43	\$169.95 EACH
8					0	-	-	1	-	-	0	-	-	CENTER EXCITED PIPE	HORIZONTAL		8 3/4	10 1/2	8 3/4		\$75.00 EACH

(chart continues on page 70)

If you've ever said...

# "There must be a better

Send for a free Career Guidance Booklet that could start you on the road to success in a rewarding new career.

It happens to all of us, sooner or later. No matter what kind of job we have.

One day, it suddenly strikes home that we're going to have to work for a living, the rest of our lives. And most of us are horrified at the thought of forever being locked into the jobs we now hold.

"Surely," we tell ourselves, "there must be a way to get more satisfaction out of working. Surely, there must be a way to find a job that's more rewarding."

"Surely," in other words, "there must be a better way to earn a living!"

If you, too, have been thinking these same thoughts, you'll find one of our free Career Guidance Booklets very helpful at this time. We invite you to send for one.

Your free booklet will describe the opportunities for higher income and greater job security you might expect in one of the career fields listed on card or coupon. It will also explain why ICS can prepare you for this new career field...right in your own home...in your spare time...regardless of your education or past experience.

Of course, no school — not even ICS — can guar-



# way to earn a living..”

antee you a better job. But ICS *can* give you the first-rate training you need—especially if you’re interested in one of the growing careers where ICS concentrates its training. Like Electrician. Engineer. Auto Mechanic. TV Repairman. Air Conditioning Serviceman. (Check your choice on card or coupon.)

Along with your Career Guidance Booklet, you’ll also receive a free Demonstration Lesson.

Please bear in mind that ICS has a long and distinguished record of success. In fact, since 1890, millions of men and women around the world have turned to ICS for career training.

More than 70 of America’s largest 100 corporations (including Ford, U.S. Steel, Mobil Oil, GE and RCA) use ICS training for their own employees.

## Earn a College Degree

You could even earn a college degree from the ICS Center for Degree Studies, which is authorized by the Pennsylvania Department of Education to grant the Associate in Specialized Business Degree in Accounting and Business Management, and the Associate in Specialized Technology Degree in Engineering—Civil, Mechanical, Chemical, and Electrical. These are all two-year degree programs, available through home study, in fields in which job openings are expected to increase in the years ahead.

If you already have some college education, you may be able to receive advanced standing toward your degree. With a degree from ICS, you’ll be able to apply with pride for jobs that call for college training.

## An Ideal Way to Learn

Whether you choose a degree program or a non-degree program, as an ICS student you study at home, on your own schedule. You waste no time traveling to and from class. And you never have to miss a paycheck.

But you’re never alone. Skilled instructors are ready to help you.

If you ever have doubts or problems or just want to talk to an instructor, you can call ICS from anywhere in the continental United States, day or

night, using our special toll-free Dial-a-Question® service.

No one can promise success, but if you *want* more—more money, more security, more day-to-day satisfaction and more future—our free Career Guidance Booklet and free Demonstration Lesson can help you get started in the right direction. Just check the box next to the field that interests you most and mail the postpaid card or coupon today. There’s no obligation.

Remember, it’s your life. You might as well make the most of it.

© 1975 Intext, Inc.

**ICS** International Correspondence Schools  
Scranton, Pa. 18515 XA813K

Please mail me the Free Career Guidance Booklet and Free Demonstration Lesson for the field I have checked below. I understand I am under no obligation.

<input type="checkbox"/> Electrician	<input type="checkbox"/> Automotive Mechanics
<input type="checkbox"/> Engineering	<input type="checkbox"/> Business Management
<input type="checkbox"/> Accounting	<input type="checkbox"/> Appliance Service and Repair
<input type="checkbox"/> Drafting	<input type="checkbox"/> Civil Engineering
<input type="checkbox"/> Electronics Technician	<input type="checkbox"/> Interior Decorating
<input type="checkbox"/> TV Service and Repair	<input type="checkbox"/> Restaurant/Club Mgt.
<input type="checkbox"/> Airline/Travel	<input type="checkbox"/> Income Tax
<input type="checkbox"/> Surveying and Mapping	<input type="checkbox"/> Motel/Hotel Management
<input type="checkbox"/> Construction Electrician	<input type="checkbox"/> Mechanical Engineering
<input type="checkbox"/> Diesel Mechanic	<input type="checkbox"/> ICS High School Diploma
<input type="checkbox"/> Air Conditioning and Refrigeration	<input type="checkbox"/> High School Equivalency

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Telephone \_\_\_\_\_

**Earn A College Degree**

The ICS Center for Degree Studies is authorized by the Pennsylvania Department of Education to offer college programs at home leading to Associate in Specialized Business and Associate in Specialized Technology Degrees. For more information at no cost or obligation, check the field of your choice.

<input type="checkbox"/> Accounting	<input type="checkbox"/> Mechanical Engineering
<input type="checkbox"/> Business Management	<input type="checkbox"/> Chemical Engineering
<input type="checkbox"/> Civil Engineering	<input type="checkbox"/> Electrical Engineering

Canadian residents use Scranton, Pa. address for service from ICS Canadian, Ltd. In Hawaii: 931 University Ave., Honolulu, Hawaii 96814.

APPROVED FOR VETERANS' TRAINING. APPROVED FOR FEDERALLY INSURED STUDENT LOANS. ACCREDITED MEMBER NATIONAL HOME STUDY COUNCIL.

MANUFACTURER'S SPECIFICATIONS (CONT)

MANUFACTURER	MODEL	HARMONIC DISTORTION (%) AT ANY FREQUENCY AT SOUND PRESSURE LEVEL UP TO —						LINEARITY		EFFICIENCY						POWER HANDLING CAPACITY				MANUFACTURER'S RECOMMENDED AMPLIFIER POWER RATING		MAXIMUM OUTPUT dB SPL AT 1 METER ON-AXIS WITH LESS THAN 3% THD AND 1M DISTORTION FROM 100Hz TO 10 kHz
		90dB			100dB			FROM:	TO:	CONTINUOUS TONE		INTERMITTENT POWER				MIN RATING	MAX RATING					
		90dB	95dB	100dB	dB	CONTINUOUS WATTS	CONTINUOUS WATTS	dB SPL FOR 1 CONTINUOUS WATT AT 1 kHz MEASURED AT 1 METER ON-AXIS	CONTINUOUS WATTS	AT ANY FREQ. BETWEEN		FOR PERIODS NOT EXCEEDING		MIN WATTS	MAX WATTS							
		50 Hz-15 kHz	50 Hz-15 kHz	50 Hz-15 kHz						HERTZ	HERTZ	CONTINUOUS WATTS	MINUTES	SECONDS								
STR	ALPHA	1	1	3			96	40	20	20K	100	0	10	5	75	100						
SUPERSCOPE	S-16A	2	5				95	5	80	17K	15	0	30	2	20	93						
	S-26A	3	5				88	5	60	18K	20	0	30	2	20	92						
	S-212A	1	2	3			90	50	30	20K	100	0	30	5	100	100						
TECHNICS BY PANASONIC	T-200						73.3				40	5	0	10								
	T-300						73.3				50	5	0	10								
TEMPEST	LAB SERIES 2	<.5	<.5	<.1	2	1	15	96	30	100	1K			8	40	120						
	LAB SERIES 3 & 3E	<.5	<.5	<.1	2	1	15	96	30	100	1K			8	40	120						
YAMAHA	NS-670													6.3	50							
ZENITH	E9012 ALLEGRO 1000								20	80	15K			3	30							
	E9014 ALLEGRO 2000								20	50	15K			3	40							
	E9018 ALLEGRO 3000								20	40	15K			3	50							

NOTES:  
 \*SPECIFICATION NOT MEASURED PER SPECIFIED CONDITIONS  
 \*\*PRICE SLIGHTLY HIGHER ON WEST COAST  
 †PRICE INCLUDES EQUALIZER  
 †† KIT FORM  
 BLANK SPACES INDICATE SPECIFICATIONS NOT PROVIDED BY MANUFACTURER.

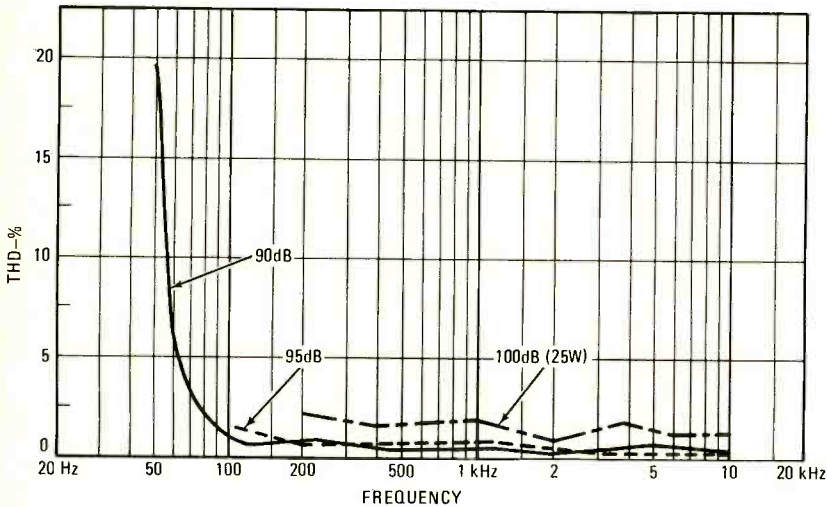


FIG. 6—HARMONIC DISTORTION CURVE of Avid's model 100.

**Efficiency and sound levels**

Efficiency refers to the ability of a speaker system to convert electrical input power into acoustical power. Not all the power fed to a bookshelf speaker system is converted into acoustical power. The majority of power is dissipated in the form of heat by the individual drivers. A speaker system with a relatively high efficiency will convert more input power into acoustical power and achieve higher sound levels from an amplifier with a given power rating than a low-efficiency system.

To provide realistic sounding reproduction, a hi-fi system must be able to deliver the same sound levels that are produced at a live concert. (Unfortunately, not very many of us live where we can run our systems at these levels without the neighbors running us out of town.) Normal listening levels produced by an orchestra in a concert hall rarely exceed 90-dB as experienced by the audience. At a live rock concert, the sound levels can approach 110—115 dB, and more. To provide a reference level, the threshold of pain for the human ear is 130-dB. Consider the fact

that an increase of 10 dB will only double the loudness level. This is a ten-fold increase in the power that must be provided by the amplifier.

The average power consumed by a speaker system at normal, not too loud, listening levels is a fraction of one watt. The program material, however, contains transient peaks that can demand from the amplifier as much as 100 times the average power level. To prevent the amplifier from clipping these transient peaks, and thus causing distortion, either the amplifier power rating can be increased or the average power consumed at normal listening levels can be decreased. This latter alternative is done by choosing a speaker system with a high-efficiency rating.

The efficiency specification is presented as the number of dB SPL produced by the speaker system when it is driven with a 1000-Hz, 1-watt drive signal measured at a distance of 1-meter on axis. There is no direct relationship between efficiency and sound quality. However, a more efficient speaker system demands less power from the amplifier. Consider this point (along

with power-handling and impedance specifications) when selecting an appropriate amplifier to drive the speaker system. If you already own an amplifier, choose a speaker system that will match the amplifier based on these considerations.

**Power handling capacity**

A speaker system is rated for the maximum number of watts that it can handle safely. Beyond this point, the speaker system will be destroyed. Excessive power usually results in the voice coil of one of the drivers being melted. So this specification is important when selecting an amplifier that will safely drive the speaker system.

The power handling capacity of a speaker system is dependent upon frequency. Each driver in the speaker system has a different power handling capacity. Normal program material is not made up of equal amounts of power in the bass, mid-range, and treble portions of the audio spectrum. Also, each driver in the speaker system (woofer, mid-range and tweeter) has a different efficiency. As a result, it is not necessary for each driver to handle the same amount of power. For example, in a typical three-way speaker system, the mid-range will be capable of handling 25% of the total system power while the tweeter will be capable of handling 5%. The woofer will be capable of handling 100% of the total system power. For this reason, the first specification for power handling capacity is expressed in continuous watts electrical input signal over a range of input frequencies. In addition, this is a continuous tone specification. The speaker system will be capable of handling this amount of power for an infinite amount of time—forever.

The continuous-tone specification is the average power that the speaker system can handle. This specification coupled with the efficiency and the power delivered by the amplifier will determine the listening levels that will safely be achieved by the speaker system. Normal program material however, is not composed of constant level

IMPEDANCE			WOOFERS			MID-RANGE			TWEETERS			OPERATING PRINCIPLE	MANUFACTURER'S RECOMMENDED ORIENTATION (HORIZONTAL, VERTICAL)	MANUFACTURER'S RECOMMENDED POSITION	SIZE (INCHES)			WHT (LBS)	PRICE			
NOMINAL	MIN	MAX	TOTAL NO.	SIZE	TYPE	TOTAL NO.	SIZE	TYPE	TOTAL NO.	SIZE	TYPE				H	W	D					
OHMS	OHMS	Hz	OHMS	Hz		OHMS	Hz		OHMS	Hz												
8	5	140	18	50	1	10 in.			1	12 cm			PIEZOELECTRIC	TUBE VENTED REFLEX	VERTICAL	2 FT. OFF FLOOR, 2 FT. FROM WALL	23 7/8	14 3/4	12 1/2	45	\$139.00 EACH	
8	8	500	25	20K	1		6 1/2 IN. FULL RANGE							BASS REFLEX	EITHER	NEAR CORNER	17	10 1/2	7	7	\$69.95 PAIR	
8	8	400	15	150	1	6 1/2 in.			1	2 in.			CONE	BASS REFLEX	EITHER	NEAR CORNER	19 1/8	11 1/4	7	9.5	\$79.95 PAIR	
8	8	150	30	1500	1	12 in.			1	3 in.				AIR SUSPENSION	EITHER		23 1/2	14 1/2	11	27	\$169.95 EACH	
8	6.5	200-400			1	10 in.		CONE	0			1	1 3/4 in.	RING	ACOUSTIC SUSPENSION	EITHER	MID-WALL	21 3/4	12	10 1/2	27	\$39.95 EACH
8	6.5	200-400			1	10 in.		CONE	1	3	CONE	1	2 in.	DOVE	ACOUSTIC SUSPENSION	EITHER	MID-WALL	24 3/8	13 3/4	12 1/2	33	\$179.95 EACH
5	4	150	22	60	1	10 in.			1				HEIL AIR MOTION TRANSFORMER	SHELF PORT REFLEX	HORIZONTAL	FLOOR	24 1/4	13 1/4	13 1/4	40	\$169.00 EACH	
5	4	170	20	65	1	8 in.			1				HEIL AIR MOTION TRANSFORMER	SHELF PORT REFLEX	HORIZONTAL	FLOOR	22	12 1/4	10 5/8	30	\$129.00 EACH	
8					1	250 mm		CONE	1	60 mm		1	30 mm	DOVE	ACOUSTIC SUSPENSION	HORIZONTAL	FLOOR, NEAR CORNER	22 3/4	12 5/8	10 5/8	42	\$460.00 PAIR
8	8	250	48	105	1	6 1/2 in.			1	3 1/2 in.				BASS REFLEX PORTED	EITHER		16 1/2	10 1/2	7 1/2	12	\$54.95 EACH	
16	10	8K	90	90	1	8 in.			1	3 1/2 in.				BASS REFLEX PORTED	EITHER		18 5/8	12 3/8	7 7/8	17	\$64.95 EACH	
16	11	8K	100	70	1	10 in.			1	3 1/2 in.				BASS REFLEX PORTED	EITHER		22 3/4	14 1/4	8 7/8	22	\$79.95 EACH	

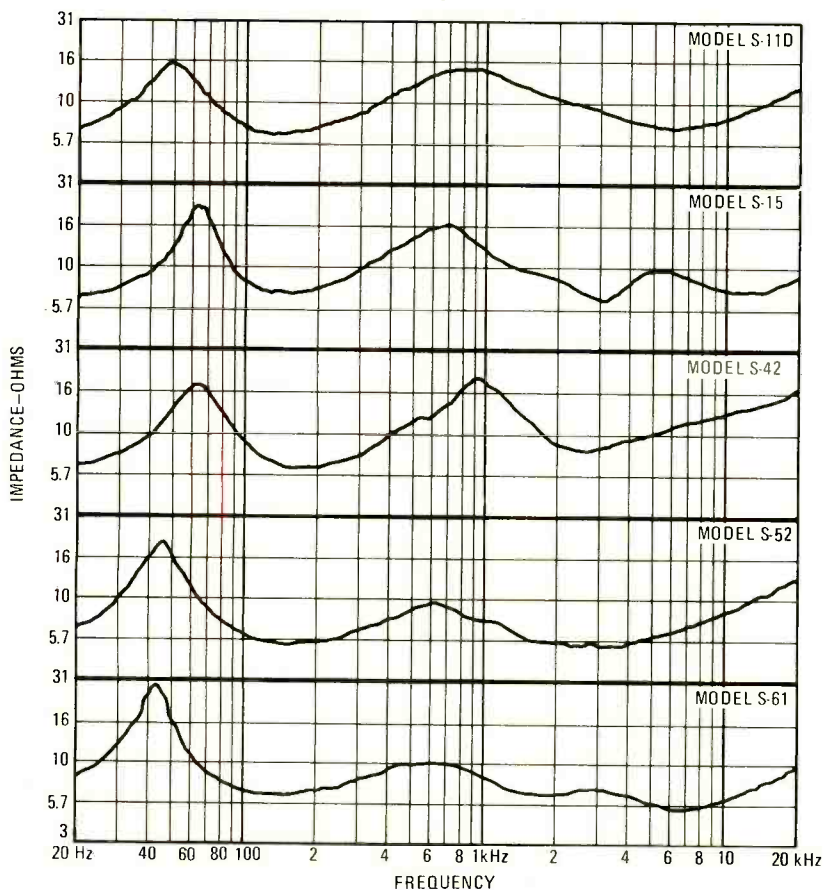


FIG. 8—IMPEDANCE CURVES for acoustic suspension speaker systems from H. H. Scott.

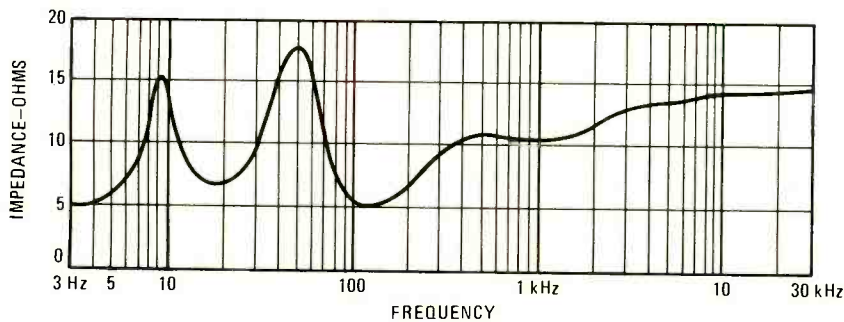


FIG. 9—IMPEDANCE CURVE of STR's model Alpha bass-reflex speaker system.

signals. It is made up of transient peaks. Therefore, the amplifier delivers short bursts of power to the speaker system that are much greater than the average level. For example, suppose an amplifier rated at 100 watts RMS is driving a speaker system. If the volume control was turned up to the point where the peaks of the program material were just being clipped, the average power delivered to the speaker system would only be 15 watts RMS. The power delivered on the program peaks would be 100 watts.

The intermittent power handling specification is referenced to time. The ability of a speaker system to handle short bursts of power is much greater than its ability to handle power for long periods of time.

There is no direct relationship between power handling capacity and the sound quality that a speaker system will produce. However, if the actual input power to a speaker system is quite a bit less than its power handling capacity, the distortion will be less. In addition, this as an important consideration to prevent damage from an amplifier whose maximum output is too powerful for the speaker system. Therefore, choose a speaker system with a large power handling capacity. For the continuous-tone specification this means the largest power rating over the widest range of frequencies. The intermittent specification should be the largest power rating over the longest period of time.

**Recommended amplifier power**

In addition to the power handling capacity, **Radio-Electronics** requested that the manufacturers provide their recommendations concerning the proper power rating of the amplifier that should drive the speaker system. This recommendation is in two parts—minimum power and maximum power. The recommendation of the maximum power rating of the amplifier is directly related to the maximum power handling capacity of the speaker system. The power rating of the amplifier (RMS) should not exceed this recommendation to avoid possible damage to the speaker system. Otherwise some protective device must be used to protect the speakers

(continued on page 76)

# how a PROM works

Programmable Read Only Memories are manufactured using various technologies. This article describes each type of PROM and its advantages and disadvantages.

by ROGER L. SMITH

REMEMBER WHEN SOMEONE MENTIONED a PROM, we all thought of a high school dance? Well, in today's age of electronics, a PROM is a Programmable Read Only Memory. Incidentally, PROM is a trademark of Harris Semiconductor Div. of Harris Inter-type Co.; however, the word has become generic because of its widespread use in describing all field programmable ROM's.

Speaking of ROM's, let's cover some of the basics of memories and the terms used before going any further. The first memories that were used with computers (and a computer is not a computer without a memory) were ferrite-core memories. These core memories—provided they were properly powered down and up—were non-volatile, meaning the data in them was not lost when power was removed. In a volatile memory, all data is lost in powering down. Most core memories are also classified as DRO, although a few are NRDO. The DRO (Destructive Read-Out) uses a read-write cycle to restore data to the cores. An NDRO (Non-Destructive Read-Out) memory does not require rewriting the data after a read cycle is completed.

With the advent of LSI (Large Scale Integration) techniques and the decreasing cost of semiconductors, the use of semiconductors as memory elements became possible. Various types of semiconductor memories evolved—from simple diodes arranged in a matrix to flip-flops, stored-charge devices and amorphous semiconductors. These new types of memories permitted designers to implement the ROM for cases where the memory was to be used for fixed conditions such as program control.

These ROM's presented logic designers with options not previously available. Now it became possible to replace complex logic circuits with ROM's. You can imagine how difficult it would be to design the logic for a code conversion—a simple job for a ROM. Another unique use for ROM's is in custom waveform generators. A

sequential counter feeds the ROM inputs and the outputs go to a digital-to-analog (D-to-A) converter. In another use, the inputs are treated as separate logic inputs and the ROM acts as a Programmable Logic Array (PLA). For more information, refer to the article "What Is A ROM?" in the February, 1974 issue of *Radio-Electronics*.

## What PROMs are available?

The simplest PROM's—diode matrices—are available in 14-pin packages (Harris HM1-034-2, a  $6 \times 8$  array) containing diode arrays with fusible links. These diode matrices can be programmed by "burning out" the fusible links and thus can be classified as PROM's. Such memories are used primarily in encoding and decoding functions.

## Amorphous semiconductor

An interesting type of memory that is also field-programmable is the amorphous semiconductor memory. This memory consists of amorphous glass semiconductor resistors (called

ovonic memory switches by Energy Conversion Devices, Inc.) in series with silicon diodes in a matrix array. The glass semiconductor can exist in either of two phases—amorphous or polycrystalline. The resistors in the amorphous phase show a resistance of about 300K ohms, and in the crystalline phase about 500 ohms. The low-resistance, or set state, is achieved by applying a 15 millisecond pulse to the bit to be set. The high-resistance, or reset state, requires applying 8 to 10 five-microsecond pulses at  $80 \mu\text{s}$  intervals.

These amorphous memories thus have a slow write-cycle time and are called by the manufacturer (Energy Conversion Devices) Ovonic Read-Mostly Memories (RMM). These devices are non-volatile like PROM's but they can also be written into like Random Access Memories (RAM's).

## Fusible links

The semiconductor PROM most often used at this time is the bipolar type containing memory elements composed of nichrome fusible-links. Intel is

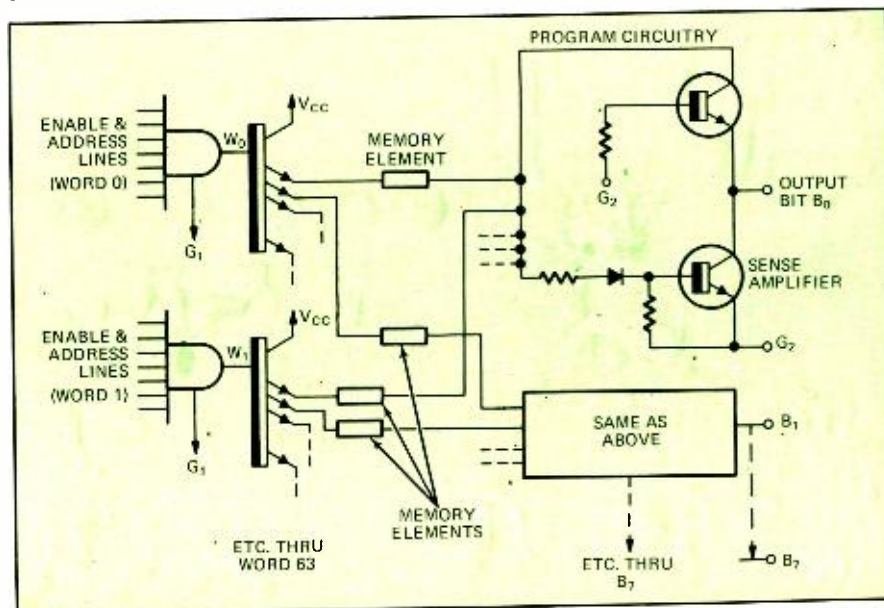


FIG. 1—512-BIT PROM schematic shows the word transistors (64 of them) connected to the sense and program circuits via memory elements.

TABLE 1

Manufacturer	Part No.	Organi- zation	Bits	Supply Voltage		Memory Element	Special Notes
				Normal	Program		
Advanced Micro Devices	AmS08	32x8	256	+5V	10V to 15V	polysilicon	open col. out. { +2 words 3 state out. } 9th bit,
	AmS09	32x8	256	+5V		polysilicon	
Harris Semiconductor	HPROM-0512	64x8	512	+5V	+5V,+15V	nichrome fuse	Program similar to Signetics.
	HPROM-1256	256x1	256	+5V	+5V,+15V	nichrome fuse	
	HPROM-8256	32x8	256	+5V	+5V,+15V	nichrome fuse	
	HPROM-1024/A	256x4	1024	+5V	+5V,+15V	nichrome fuse	
	HPROM-2048/A	512x4	2048	+5V	+5V,+15V	nichrome fuse	
Intel Co.	1602A/1702A	256x8	2048	+5V-9V	+12V,-45V	FAMOS device	1702A is erasable all outputs norm. high (1) 3 state out
	3604	512x8	4096	+5V	+10V,+15V	polysilicon	
	8702A	256x8	2048	+5V-9V	+12V,-45V	FAMOS device	
	3601	256x4	1024	+5V	+10V,+15V	polysilicon	
Intersil	IM5600C/IM5610	32x8	256	+5V	+5V,+28V	"AIM" device	open coll. 5610=3 state special pulse programmer
	IM5603A/IM5623	256x4	1024	+5V	+5V,+28V	"AIM" device	
	IM5604/IM5624	512x4	2048	+5V	+5V,+28V	"AIM" device	
Motorola Semiconductor	MCM5003AL	64x8	512	+5V	+5V,-6V	nichrome	9th bit. Prog. manually has 2K on output
	MCM5004AL	64x8	512	+5V	+5V,-6V	nichrome	
National Semiconductor	MM5202A	256x8	2048	+5V-9V	+12V,-45V	FAMOS device	Q suffix has quartz lid for erasing.
	MM5203	256x8	2048	+5V-9V	+12V,-45V	FAMOS device	
	MM5204	512x8	4096	+5V-9V	+12V,-45V	FAMOS device	
Signetics	8223	32x8	256	+5V	+5V,+12.5V	nichrome	open coll. Prog. manually 82S123=3 state 26=open coll. 29=3 state
	82S23/82S123	32x8	256	+5V	+5V,+12.5V	nichrome	
	82S26/82S29	256x4	1024	+5V	+5V,+12.5V	nichrome	
Texas Instr.	SN74186	64x8	512	+5V	+5,-5V	nichrome	9th bit & extra word tested by mfg. Prog. manually. open collector output.
	SN74188A	32x8	256	+5V	+5V,+10V	nichrome	

All types are 0° to 75°C

presently making bipolar PROM's (up to 4096 bits) using polycrystalline silicon fuses (instead of nichrome). Advanced Micro Devices also makes 256 bit PROM's with silicon fuses. A look at Fig. 1 will help you to understand the operation of this type of fuse-link PROM. This figure is a block diagram of a 64-word, 8-bit PROM (512 bits). The 6-bit ADDRESS input is buffered and inverted to provide true or complement addresses to each of six inputs on the 64 multiple-emitter AND gates. A seventh input provides the chip enable signal. Since only one of the 64 AND gates will be activated for a particular address, that gate will generate a high level on one of the 64 word lines connected to each gate output. These word lines are connected to the bases of 64 multiple-emitter transistors located in the memory section of the circuit.

The selected (1 of 64) multiple-emitter transistor drives the output transistors thru the eight memory elements. With the proper resistive load connected to their collectors, these transistors will saturate and a low voltage, or logic "0," will appear at the output. Thus the normal output of such a PROM, with the memory elements intact, is a "0." This PROM is programmed by opening the appropriate memory elements and causing a logic "1" to appear at the output for a specific address.

Memory elements of this type (as in the Motorola MCM5003) are fused

open by connecting a negative voltage (-6V) to the output collector of the desired bit, applying a voltage (+5V) to V<sub>cc</sub>, grounding pin G2, and connecting G1 to a negative voltage (-6V).

Then the desired word is addressed (with -6V as a "0" and -4V to +5V as a "1"). Notice in Fig. 1 that this forward biases the program transistor for that bit so that when the address is

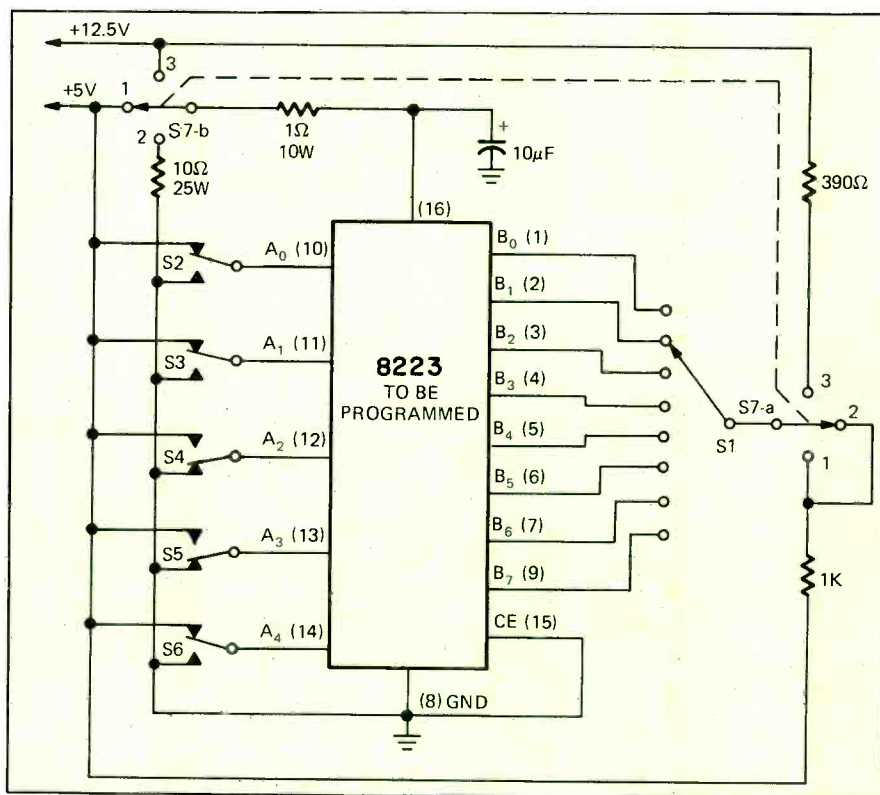


FIG. 2—MANUAL PROGRAMMER schematic. During programming, switch S7 is moved to position 2 long enough to discharge the 10-µF capacitor. Switch S7 should not be in position 3 for longer than one second.

selected, current thru the memory element is increased (to 30 mA). This is sufficient to cause the metal fuse to flow and separate. The current is applied as a ramp and limited to 60-mA maximum to prevent sputtering, metal splatter, or oxide damage.

Programming voltages for other nichrome type PROM's such as Signetics' 8223, vary somewhat. However, the basic idea is to allow a heavy current to pass thru the nichrome "fuse" to a program transistor that is biased into saturation. Figure 2 shows a manual programmer that can be used to program the Signetics 8223. When using this programmer, current should not be applied to a bit for over one second.

Two precautions should be observed when programming this type of PROM. One is to limit the application of programming current to one output at a time. This current passes thru the multiple-emitter "word transistor" whose design doesn't allow it to conduct more current than required to open one element. Another precaution is to maintain the case temperature of the PROM at or below 75°C. This is easy to do if you program manually and remove voltages as soon as the memory element opens. Automatic programming may require a heat sink.

The above description of programming the fuse-link type of PROM illustrated a manual technique. Manual programming is possible with most types of nichrome fuse-link PROM's provided that the currents are limited in some manner. Most often, the rise time must be controlled and the duration and amplitude of the programming current must be limited. This is easily done with a pulsing technique. All of this of course, can be accomplished with an automatic programmer that also sequences thru the addresses and bit patterns. Automatic programmers are desirable when more than three or four PROM's are to be programmed, and are required equipment for some of the PROM's to be described next.

#### AIM

Another type of memory element is used by Intersil in their PROM's. They have patented *Avalanche Induced Migration* (AIM) programming system. Each memory element in an open-base NPN transistor whose base-emitter junction is shorted out when it is programmed.

A partial schematic of an AIM matrix is shown in Fig. 3. Notice that the matrix is constructed using conventional TTL processes. Collectors on the "X" lines are common and emitters on the "Y" lines are common, allowing for simple fabrication steps. No connection is provided for the bases. To program an element, a high current

is forced thru it from emitter to collector. The emitter-base junction is forced beyond normal avalanche and into a second breakdown mode. Aluminum moves into the junction and causes a short. The result is a low-resistance path to the base and a base-collector diode as shown in Fig. 3.

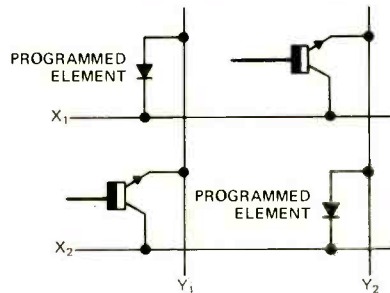


FIG. 3—PARTIAL AIM PROM matrix with two bits programmed as "1".

The programming is done using a 200 mA pulse (at about 32V) of about 2.5  $\mu$ s duration followed by a 20 mA, 1.5  $\mu$ s sense pulse. These pulses are repeated a number of times until a change in the bit has been detected. The programmer then moves on to the next bit automatically.

#### FAMOS

The last type of PROM we will investigate is the stored-charge type made by Intel and National Semiconductor. This type of PROM falls in the same category as the ovonic amorphous semiconductor type mentioned earlier in that it can be re-programmed (however, not electrically). The advantage of this type of PROM is obvious. If you make a mistake, or change your bit requirements, you can change your PROM by erasing all bits and programming it over again! Erasure is accomplished with ultraviolet light or X-rays (although X-rays are not recommended).

The memory element consists of a floating-gate avalanche-injection MOS charge-storage device (which has been shortened to FAMOS transistor). Notice in Fig. 4 that the FAMOS transistor is essentially a P-channel silicon gate MOS field-effect transistor in which no contact is provided to the silicon gate. In programming, a voltage pulse in excess of -30 volts is applied to the drain or source PN junction re-

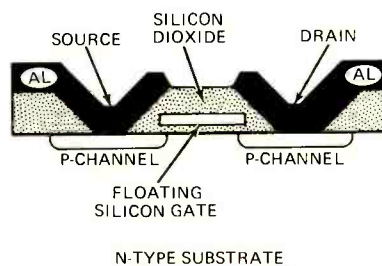


FIG. 4—CROSS-SECTION OF FAMOS structure. Negative charge on floating gate causes conduction between source and drain.

sulting in the injection of high-energy electrons from the PN junction surface avalanche region to the floating silicon gate. This negative charge on the gate results in current flow between source and drain of the P-channel FAMOS transistor.

The FAMOS transistors are arranged in a matrix on the silicon chip along with an X and Y decoders, input drivers, output sensors and buffers to form the complete MOS memory device. Programming these PROM's (typically the Intel 1702A, 2048-bit PROM) requires special programmers that pulse the device with a minimum of 32 program pulses for each 8-bit word to be programmed. Note in this PROM that all 8 bits of a word are programmed simultaneously. In addition to the program pulse, voltages  $V_{DD}$  and  $V_{DD}$  are also pulsed. The Intel Company will furnish you schematics for the MP7-03 PROM Programmer, or of course, you could buy an assembled unit.

The Intel 1702A PROM comes with a transparent quartz lid which permits you to erase the bit pattern. You can erase a device by exposing it to high intensity ultraviolet light at a wavelength of 2537 Å. Just put the 1702A about 1 inch away from the lamp tube for 10 to 20 minutes. Recommended lamps are Models UVS-54 or S-52 ultraviolet lamps manufactured by Ultra-Violet Products Inc., San Gabriel, CA. Physically, the erasing action creates an ionizing effect that causes the excess electrons on the floating gate to flow back to the substrate.

You have no doubt noticed that many of the PROM's we have covered use irreversible memory elements. Aside from the fact that such a PROM cannot be reprogrammed, there is also the problem of testing the PROM initially. If you order a ROM, the manufacturer programs it to your specification and tests it to be sure the bit pattern and output circuits are OK. However, if you buy a PROM, there most likely was no way for the manufacturer to test it so you won't know if it is any good until you program it. Most manufacturers build PROM's with experience and quality control. Several PROM manufacturers have decided that this method is not good enough (Motorola and Advanced Micro Devices among them). They have solved the testing problem by adding a ninth bit to all 8-bit PROM's. Some have even added several extra words to the memory. In the Motorola MCM5003 there are 32 of these ninth bits that have already been programmed to "1s," and the remaining 32 bits may be used by the customer to check out the capabilities of his programming circuitry.

Table 1 has been prepared to help  
(continued on page 119)



# Introducing... the Money Generator



MODEL ATC-10  
Patent Pend.

8.25"Dx2.6"Hx8.25"W

## A Better Approach to TV Analyzing

### ATC-10's Unique Patterns



UNIFORM  
RED  
RASTER

#### RED RASTER


Check and adjust purity at the flip of a switch without disabling blue and green electron guns.



TEN  
BANDS  
OF  
FREE  
RUNNING  
COLORS
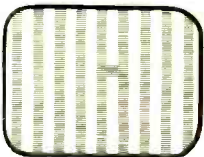
#### 3.58 MONITOR


Check and adjust color Sync. OSC. Freq. at the flip of a switch (No need to ground AFPC Test Point.)



#### COLOR BARS

Sixth bar marked for identification.

Luminance pedestal shows color fit.

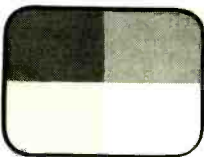


#### GRAY QUAD

Gray scale tracking checks/adjustments.


Yoke orientation.

L.F. video response.

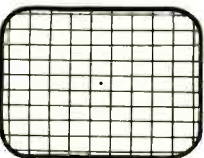
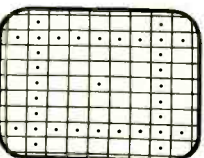
#### HATCHDOT

Composite convergence patterns enable you to complete an entire convergence series with no need to alternately select separate patterns for DC and dynamic convergence.



#### HATCHDOTS

The hatchdots pattern with its frame-of-dots is also great for size, linearity, centering, and pincushion checks and/or adjustments.

### Great Money Generating Features

The ATC-10 offers portability with a variety of new money-generating features for faster in-home servicing. It is also a superior analyzing device for troubleshooting tough dogs in the shop. A sample of its outstanding features include the following.

- CRYSTAL CONTROL AND PHASE LOCK OF ALL CHROMA AND SWEEP FREQUENCIES PROVIDE PATTERNS WITH UNMATCHED CLARITY AND FREEDOM FROM INTERFERENCE — CHROMA WAVEFORMS ARE VIEWED AS STATIONARY SINE WAVES USING H TRIGGER.
- IN-HOME BANDPASS CHECKS AT 1.78 MHz AND 3.58 MHz.
- ALL CRYSTAL-CONTROL / SOLID-STATE / DIGITAL IC DESIGN PROVIDES MAXIMUM RELIABILITY AND COMPLETE FREEDOM FROM VERTICAL LINE WIDTH AND COUNTER STABILITY ADJUSTMENTS.
- EXTRA WIDE RANGE RF/IF OUTPUT ATTENUATOR TESTS RECEIVER SENSITIVITY AND DYNAMIC RANGE.
- IF AND VIDEO INJECTION OUTPUTS WITH "FUSELESS" PROTECTIVE CIRCUITS.
- INTERLACE SELECTABLE FOR H/V COUNTDOWN TV'S.
- SQUARE WAVE PROVIDED FOR VIDEO PEAKING TEST.
- HORIZ. AND VERT. TRIGGER OUTPUTS OPTIMIZED FOR EXPANDED OSCILLOSCOPE PRESENTATIONS.
- 2 YEAR FACTORY WARRANTY AGAINST DEFECTIVE WORKMANSHIP AND MATERIALS.
- 30 DAY MONEY BACK GUARANTEE.

### American Technology Corporation

225 MAIN, DEPT. 11C, CANON CITY, COLORADO 81212

- Please send additional information on the MOD. ATC-10.
- Include a copy of the 2-volume (Home/Shop) ATC-10 Owner's Manual. \$1.00 enclosed to cover postage and handling.
- Please ship \_\_\_\_\_ Model ATC-10's at \$299.95 with:
- Chan. 2 RF CRYSTAL (std.) installed.  
(NO Chan. 2 transmitter in our area.)
  - Chan. 3 (optional) crystal installed.  
(Chan. 2 transmitter in our area.)
- Subtotal \_\_\_\_\_
- 3% sales tax (Colorado residents only) \_\_\_\_\_
- TOTAL REMITTANCE ENCLOSED \_\_\_\_\_

Send certified check or M.O. for fastest shipment to American Technology Corp., 225 Main, Dept. 11C, Canon City, CO 81212.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

## BOOKSHELF SPEAKERS

(continued from page 71)

against excessive power.

There are valid reasons however, for using super power (150 watts-per-channel and up) amplifiers. As stated earlier, the amplifier may be called upon to deliver as much as 100 times the average power during the transient peaks. Many audiophiles believe that to reproduce these transients without clipping them, super power amplifiers are necessary. To safely use these amplifiers, you must insure that the intermittent power handling capacity of the speaker system is great enough to handle the transient power that these amplifiers will deliver. In addition, you must insure that the average power delivered by the amplifier does not exceed the continuous-

tone power handling capacity of the speaker system. This is especially important in light of the logarithmic response of the human ear. Remember, it requires a ten-fold increase to double the volume level. So, it is possible for you to turn up the volume control to a point where the continuous-tone capacity of the speaker system is exceeded and not hear a substantial increase in the volume level. To prevent this from occurring, the speaker system must be properly fused when using these super-power amplifiers.

There are two reasons for observing the minimum power recommendation. First, there is a definite minimum amount of power that is required to drive the speaker system. If an amplifier with less power is used, the speaker system will not be driven to an adequate listening level and will not produce satisfactory music reproduction.

The second reason concerns possible damage. Yes, damage! With the amplifier delivering too little power, it's only natural to turn up the volume control to drive the speaker system to an adequate listening level. If the amplifier is not capable of delivering the necessary power, it will clip the peaks of the program material. This clipping action will produce harmonic distortion with its associated high-frequency components. As a result, the amplifier will deliver substantially more power to the high-frequency end of the spectrum. Remember, the tweeter in most systems can handle only 5% of the total system power. This extra power due to amplifier clipping is over and above the normal high-frequency power delivered as a result of the program material. The result is possible damage to the tweeters.

If you already own an amplifier, choose a speaker system so that the output power of the amplifier falls within the minimum and maximum power recommendations. Should you decide to go the route of the super-power amplifier, make sure the speaker systems are properly fused. If you don't own an amplifier, choose the speaker system first and then choose an amplifier based on these recommendations and the impedance specification (a discussion on impedance is forthcoming). These power recommendations refer to the RMS power-per-channel rating of the amplifier.

### Maximum sound output

This specification is a combination of the distortion, efficiency and power handling specifications. It states the maximum safe output sound level of the speaker system. In addition, the speaker system will not produce more than 3% total harmonic and intermodulation distortion when driven to this output level. Its measured at a distance of 1-meter on-axis over a frequency range of 100-Hz to 10-kHz and stated in so many dB's of sound pressure level.

The speaker system's dynamic range is determined by this specification. Dynamic range refers to the range of output levels that the hi-fi system is able to produce. The total dynamic range of the hi-fi system is determined by the minimum dynamic range of any component in the system. Dynamic range adds to the realism of the reproduced sound, and therefore adds to the accuracy of reproduction. Choose a speaker system that is capable of producing a high output level.

### Impedance

The speaker system acts as an electrical load for the amplifier's circuitry. This is a reactive load that varies widely with frequency and it therefore, is termed impedance. The total amount of impedance presented to the amplifier will determine the amount of power that the amplifier delivers to the speaker system. To illustrate the variation in impedance, Fig. 8 shows the impedance graphs of five acoustical suspension speaker systems manufactured by H. H. Scott, Inc. Figure 9 shows an impedance graph of a bass reflex speaker system manufactured by STR, Inc. These graphs are typical of high-quality speaker systems.

The impedance specification is pre-  
(continued on page 120)


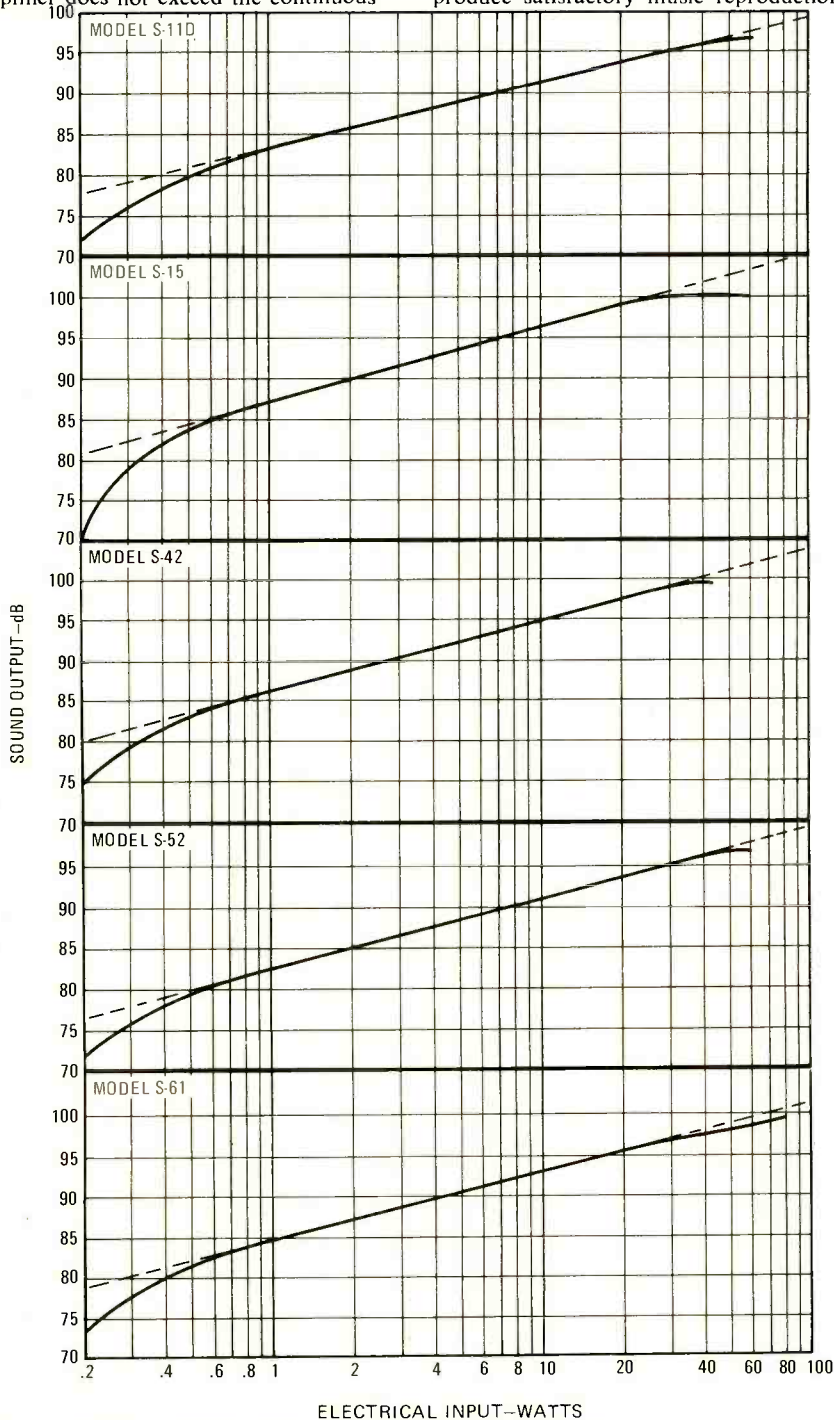


FIG. 7—LINEARITY CURVES for five speaker systems from H. H. Scott

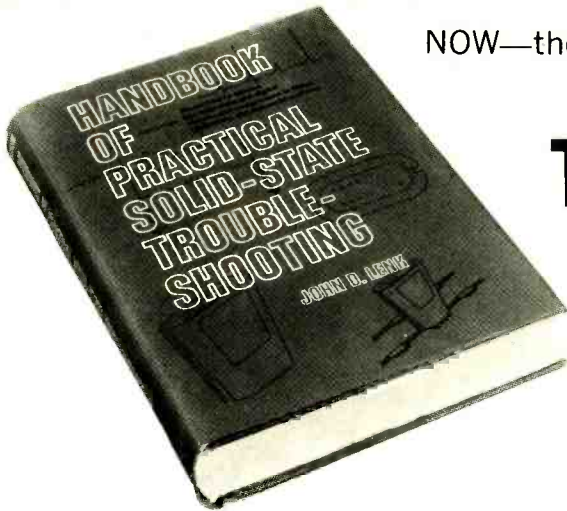NOW—the book that brings you speed, ease and accuracy—



# The Handbook of Practical Solid-State Troubleshooting

—yours for just \$2.98!

**And you'll also receive a RISK-FREE trial Membership in The Electronics Book Service. (No obligation ever to buy ANY minimum number of books.)**

Now you can tackle malfunctioning solid-state circuits and equipment with new *speed, ease and accuracy!* A broad promise—but one you're sure to agree with when you see the *hundreds* of techniques available to you in John D. Lenk's HANDBOOK OF PRACTICAL SOLID-STATE TROUBLESHOOTING. **\$14.95**

This book, now selling actively at \$14.98, is one you should own. It is also typical of the kind of practical books offered to members of the *Electronics Book Service*. And you may have a copy for a token price of \$2.98 as a means of introducing you—on a no-obligation basis—to a trial membership in the *Electronics Book Service*.

Covering a complete cross-section of solid-state circuits and equipment including Basic Circuits, Home Entertainment, Laboratory and Industrial Instruments and Digital Equipment and Systems, this conveniently indexed book gives you shortcut techniques for:

- Finding out how to deal with any specific problem area—determining primary symptoms of poor performance
- Discovering the right way of tracking down and isolating the problem to a particular circuit in trouble
- Localizing the trouble right down to the functional circuit unit itself

With the instant help of HANDBOOK OF PRACTICAL SOLID-STATE TROUBLESHOOTING, you'll rapidly become adept at servicing even the most complex solid-state circuits and components! And without ever relying on time-consuming trial and error!

Through simple explanations and detailed illustrations, all the troubleshooting techniques in this book are made *easy* for you. And they cover just about every malfunction you might encounter in solid-state electronics. For instance, in the big section on troubleshooting TV receivers, you'll find techniques for quickly locating the source of such problems as:

No Sound and No Picture Raster . . . No Sound, No Picture Raster, and Transformer Buzzing . . . Distorted Sound and No Picture Raster . . . Picture Pulling and Excessive Vertical Height . . . Dark Screen . . . Picture Overscan . . . Narrow Picture . . . Foldback or Foldover . . . Nonlinear Horizontal Display . . . and over 40 more possible malfunctions in any circuit!

What's more—to contribute to your speed and proficiency—*more than 180 illustrations* clearly show you the tests and troubleshooting procedures for:

- In-and Out-Circuit Transistors
- Amplifiers, Inverters and Phase Splitters
- Video Amplifier Circuits
- Diodes
- Delays
- Pulse Delay, Time and Width
- Sound IF and Audio Circuits
- Multivibrators
- Gate Circuits
- RF Tuners and AGC Circuits
- Basic Power Supplies

The depth and breadth of coverage you'll find in HANDBOOK OF PRACTICAL SOLID-STATE TROUBLESHOOTING is unmatched anywhere—and its clearly outlined techniques will give you new *speed, ease and accuracy* in troubleshooting all kinds of solid-state circuits and equipment!

**A point of significance to you: the *Electronic Book Service* has NO minimum purchase requirements, as most book clubs do. Once you have paid \$2.98 for your copy of HANDBOOK OF PRACTICAL SOLID-STATE TROUBLESHOOTING, you need purchase no further selections.**

So act *now*. Just mail the coupon below to get your copy of HANDBOOK OF PRACTICAL SOLID-STATE TROUBLESHOOTING for just **\$2.98**—and to receive all the benefits of membership in the *Electronics Book Service* on a RISK-FREE trial basis. *Send the coupon right now!*

## What membership in the ELECTRONICS BOOK SERVICE means to you

1. When you enroll as a member, you receive—for only \$2.98 (plus postage and handling with tax where applicable)—your copy of HANDBOOK OF PRACTICAL SOLID-STATE TROUBLESHOOTING. This is the *only* obligation you are committed to make.

2. You are under *no* obligation to accept any minimum number of selections within any time limit. You can make as many or as few as you wish. And, you may resign at any time with no obligation once you have paid for your copy of HANDBOOK OF PRACTICAL SOLID-STATE TROUBLESHOOTING.

3. On selections you do accept, your membership entitles you to a discount from the publisher's list price. This discount is available to members only and provides you with substantial savings.

4. Every four weeks we'll send you a free bulletin describing the current selection. If you want the selection, no action is required; you will receive it automatically. If you don't want it, just return the card enclosed with the bulletin.

5. You have at least 10 days to decide whether you want the selection or not. Return the card so we receive it no later than the date specified. If you don't have 10 days to answer and receive an unwanted selection, return it at our expense.

6. Each bulletin also describes a number of alternate or additional selections, also available to you at the special discount price for members.

## ELECTRONICS BOOK SERVICE

Dept. 6699-P1(4)  
Englewood Cliffs, New Jersey 07632

Please enroll me in Electronics Book Service on a risk-free trial basis. I am to receive all announcements, free of charge, and will be entitled to full privileges as a Member without obligation to buy any specific number of club selections. As my first selection under this trial membership, send me the HANDBOOK OF PRACTICAL SOLID-STATE TROUBLESHOOTING for only \$2.98

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Circle 29 on reader service card

# R-E's Service Clinic

## High-voltage shut-down circuits

How they work and how to service them

by JACK DARR  
SERVICE EDITOR

THE DEPARTMENT OF HEALTH, EDUCATION and Welfare (HEW) has come up with some interesting requirements for color TV sets. (Some of these may not do too much for our Health or our Welfare but they can certainly be Educational, especially if you don't know they're in there!) One of the best among these is the high-voltage shut-down circuit. The purpose of this circuit is to shut down the set if the high-

voltage rises above a preset level to avoid X-Ray radiation.

This isn't really too new. It's been in effect for some time. RCA has a version of it in the CTC-38XP chassis and some others (RCA TV Service Data File No. 1968-T18-S2). Figure 1 shows the basic circuit. A silicon diode is installed in series with the 6BK4 high-voltage regulator tube cathode. The cathode current flows through it from the +405-V source. From the anode end of the diode (on 6BK4 cathode), an 8.2 megohm resistor is connected directly to the 6LQ6 control grid. This serves the same purpose as the familiar 10-megohm resistor to a high positive voltage; it feeds in a small positive voltage to keep the 6LQ6 grid from driving itself too far negative. Beside this, a pulse regulator circuit using a VDR also helps to control the 6LQ6 grid voltage. Normal operating bias on the 6LQ6 grid is about a -55 volts.

Now, if the 6BK4 regulator tube goes out, the diode stops conducting. The normal positive voltage fed to the 6LQ6 is lost and the tube drives itself so far negative that the high-voltage is cut away down. Typical symptoms of this condition are about 100 mA 6LQ6 cathode current (normal 200-220 mA). High-voltage is about 10 kV, and usually no raster or a very dim narrow one appears. The 6LQ6 grid voltage will be about a -70 volts. The key clue here is the -60 volts or so you'll see on the 6BK4 cathode, it should be +405 volts. If you find these symptoms, look for a 6BK4 with an open heater.

In other RCA's, especially the solid-state types, the shut-down circuit is designed to upset the horizontal oscillator frequency. This reduces the high-voltage. Typical symptom, you can not get the picture to lock in horizontally at all. The shutdown circuit can be disabled for testing, check the service data.

Quasar, Zenith, and others use SCR's in the shut-down circuitry. In some of these, service problems have been encountered. Most of these are due to the SCR being just a little bit too eager; they'll shut off on small transients, sometimes when changing channels. This of course applies in cases where the horizontal oscillator stage, high-voltage, etc., are *not* at fault. Most of them are modular, try a new shut-down module to find out. In others, especially if the SCR is a plug-in type, try a new

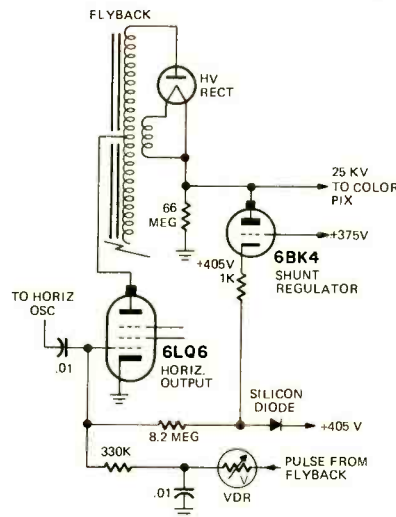


FIG. 1

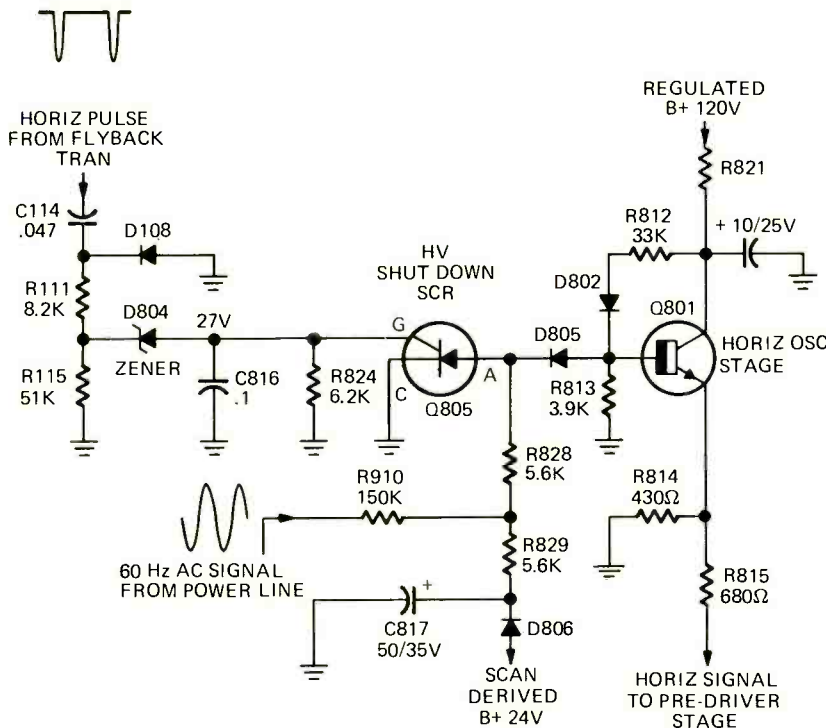


FIG. 2



# ANNOUNCING the TEKTRONIX T900 Oscilloscopes

from \$695  
probes included and more...

Here's important news for engineers, technicians and educators who want the quality, reliability and support associated with TEKTRONIX Oscilloscopes - all at a moderate price. T900\* Oscilloscopes are an entirely new line designed for cost savings without sacrifice of basic performance.

#### This New Line Includes:

- T921—Dc to 15 MHz; single-trace, mono time-base ..... \$ 695\*\*
- T922—Dc to 15 MHz; dual-trace, mono time-base ..... \$ 850\*\*
- T932—Dc to 35 MHz; dual-trace, mono time-base ..... \$1050\*\*
- T935—Dc to 35 MHz; dual-trace, dual time-base with delayed sweep .... \$1250\*\*
- T912—(Storage model) Dc to 10 MHz, dual-trace mono time-base . . \$1195\*\*

#### Easy to Use

T900 Oscilloscopes are simple to use. All have a large, bright (8 x 10 cm) crt, beam finder, single knob trigger control, delay line to enable viewing of waveform leading edge, automatic selection of tv line or frame display and functionally color-coded control panels. Convenience is also enhanced by a full complement of accessories including 10X probes (included in price), optional scope stand, camera, rain jacket and more... T900 Oscilloscopes are easy to handle and fit into small spaces. They weigh only 15-18 lbs. and measure only 7" x 10" x 19".

#### Tektronix Support

T900 Oscilloscopes are warranted against defective materials and workmanship for one year. There are over 37 service centers and 50

field offices across the U.S. Whenever you need help in the selection, operation, application or servicing of T900 Oscilloscopes your local field engineer is available to help you...no extra charge...just extra value.

For a copy of the new T900 Brochure (includes complete specifications), or ordering information write to Tektronix, Inc., P.O. Box 500, Beaverton, Oregon 97077. For immediate information call your local Tektronix field engineer or Tektronix, Inc. (503) 644-0161 extension T900.




**TEKTRONIX®**

committed to  
technical excellence

\*Available presently in U.S.A. only.  
\*\*U.S.A. price FOB Beaverton, Oregon.

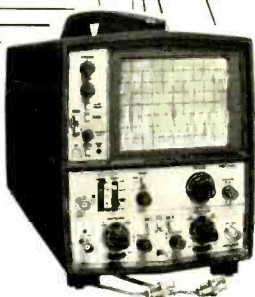
Circle 61 on reader service card for demonstration




T912



T921

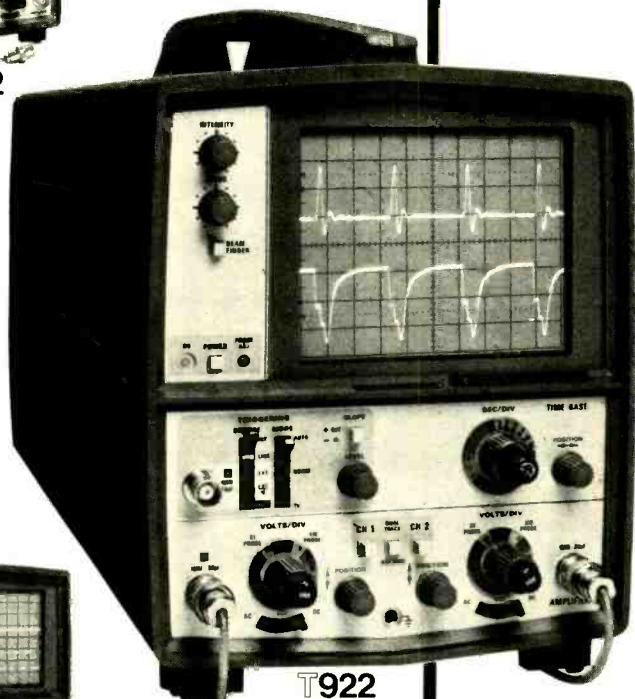

T922

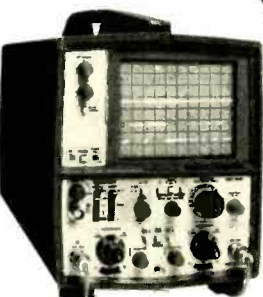

T935



T932

Circle 30 on reader service card

# Everything we make has you in mind.

When you're looking for profitable electronic lines, look to RCA Distributor and Special Products Division:

## TEST EQUIPMENT & ACCESSORIES

## EXACT REPLACEMENT PARTS

## SK REPLACEMENT SEMICONDUCTORS

## FLAMEPROOF RESISTORS

## COLOR & BLACK-AND-WHITE PICTURE TUBES

## RECEIVING TUBES

## INDOOR & OUTDOOR ANTENNAS

## ANTENNA HARDWARE

## ANTENNA ROTATORS

## CAR RADIOS & TAPE PLAYERS

## STEREO SPEAKER SYSTEMS

## SCANNERS

## BATTERIES

## ... AND MORE

See your RCA distributor. Or, for more information, contact RCA Distributor and Special Products Division, Bldg. 206-2 Cherry Hill Offices, Camden, New Jersey 08101.

# RCA

Distributor and Special Products Division

## SERVICE CLINIC

(continued from page 78)

SCR to see if the original is just a little too quick on the trigger.

Admiral's M10 chassis has an SCR shut-down circuit with a highly novel reaction. This one could wipe you out completely if you didn't know about it. Let's look at this and see how it works. Figure 2 shows the *basic* circuitry used.

The SCR is normally turned off. Its anode is connected to the base of the horizontal oscillator transistor through a blocking diode. The cathode of the SCR is grounded. A negative-going pulse from the flyback is fed to a 27-volt Zener diode. A clamp diode, D108, holds the negative peak of this pulse to  $-0.6$  volt below ground. The Zener diode, normally not conducting, is connected to the SCR gate.

If a problem occurs which makes the flyback pulse increase, this makes the *positive* peaks higher. The Zener goes into conduction and turns the SCR on. When this happens, the SCR grounds the base of the horizontal oscillator transistor, killing the oscillator. Since this chassis derives most of its operating DC voltages from the *flyback*, this brings everything to a screeching halt.

Don't go away! We're just getting a good start. This circuit doesn't just turn things off and sit there. Note the connection to the +24 volt DC line on the SCR anode through two resistors and a diode. (Which we carefully haven't mentioned till now.) When things are working, capacitor C817 charges up to the +24 volt line, minus the drop across the diode. When the SCR is gated on, its anode voltage drops to zero; the +24 volt line also goes to zero. The capacitor starts to discharge through the two resistors.

There's more! Note the AC voltage connected to the junction of those two resistors. This is a very small sample AC voltage from the main power supply, about 3.6 volts peak. (Remember the peak.) When the charge on the capacitor has dropped to 3.6 volts, the anode voltage of the SCR will go to zero on the next negative going peak of the AC voltage. (The SCR, having DC on its anode, has stayed on.) When the SCR anode goes to zero, it turns itself off again. The circuit is reset.

This reaction takes about one second. If it was caused by a short transient spike, things will now go on normally. The raster will reappear. However, if the fault is still there, the shutoff cycle will start over again, and it will keep on until the set is turned off!

This gives you the oddball symptoms; the raster will flash on and off at a one-per-second rate, accompanied by a "Poot!" in the sound! As I said, if you didn't know about this circuit, something like this could blow your mind.

There is a quick-check procedure for this circuit. Start by checking the +120 volt regulated line, with a 120 volt AC line voltage. Turn the set to a blank channel and turn the brightness completely off. Next, turn the horizontal oscillator adjustment (T800) counterclockwise until the shutdown circuit triggers. (That is, if it isn't triggering itself.) You'll have to bend the little tab on the can up to allow the core to be turned this far.

Now, disable the shutdown circuit by connecting a jumper across the SCR gate resistor. This is R824, a  $6.2K \frac{1}{4}$ -watt. If everything else is in the ballpark, the horizontal oscillator should start and the raster will appear. If it doesn't, try a new M-700 module. If the raster comes on, the high-voltage should read between 29 kV and 33 kV (zero beam current). If it does, take the jumper off and readjust the horizontal oscillator, on a signal, until it holds sync. Check by changing channels. If the SCR keeps on triggering, check it, and the diodes, resistors, etc. in the circuit. If the  $50\text{-}\mu\text{F}$  charging capacitor should open, there would be no time-delay action. If you have other troubles, try turning the horizontal oscillator control shaft clockwise until the raster begins to shrink in at the sides. This should reduce the high-voltage far enough to stop the shut-down circuit from triggering and allow you time for making tests. R-E

## reader questions

### ODD COLOR

*I have odd color problems in this G-E KC chassis. I notice that the little neon glow lamp on the chassis goes out. Does this have anything to do with the color? Also, if it does, where can I get a substitute; they call it an 8315AH?—A.A., La Vale, MD.*

Does that little neon lamp have anything to do with the color in a KC chassis? Yea, verily, brother! The *burst* goes through it! If this lamp is not glowing, no color, or very odd colors. Check the bulb; if it's blackened, clip it off and replace it. You can use a stock NE-2 or NE-2H. I've used these and it seems to work very well. You replace it from the top of the chassis by clipping off the leads of the old one and tacking the new one in.


### THIN VERTICAL LINE?

*All I've got on the screen of this G-E D2 TV is a thin, bright vertical line. I changed the deflection yoke; no luck. Any ideas?—R.B., Los Angeles, CA.*

(continued on page 82)
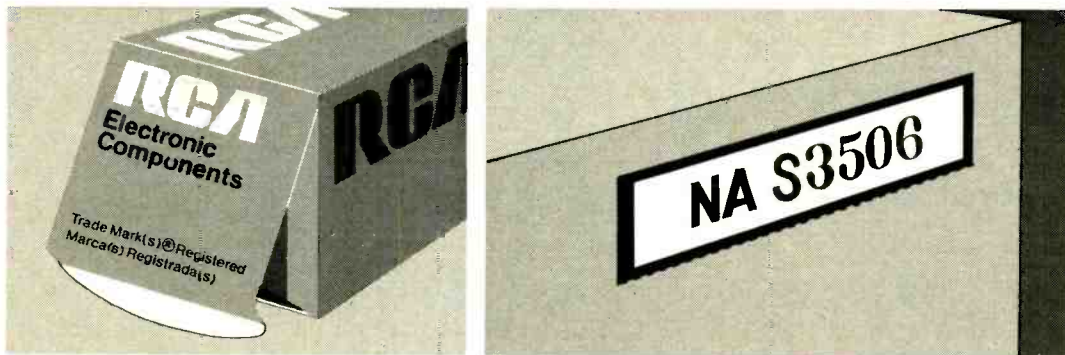
# Tear 'n Share

Save your RCA entertainment receiving tube carton ends\* and color picture tube warranty serial number stickers\* . . . and redeem them for discount certificates or valuable premiums. Just tear and you'll share!



\*Save the receiving tube carton end that is solid red reading RCA Electronic Components and the warranty serial number sticker that appears above the warranty envelope on the upper right hand corner of the RCA color picture tube carton. *One* color picture tube warranty serial number sticker is equal in value to 20 receiving tube carton ends.

Your RCA receiving tube carton ends are valuable! So are your RCA color picture tube warranty serial number stickers. Save them. In various quantities, they will bring you:

- Discount certificates. You can apply these toward purchases of more RCA receiving tubes and color picture tubes from your RCA Distributor.
- Popular merchandise premiums. You can choose from a wide selection for yourself, your family, or your home.

Here's how you do it. See your participating RCA Distributor. Pick up your copy of the RCA "Tear 'n Share" Prize Book and saver envelope. Mail the required number of RCA receiving tube carton ends or RCA color picture tube warranty serial number stickers in the envelope provided, specifying discount certificates or the premium you've selected to:

RCA Tear 'n Share Headquarters,  
P.O. Box 154, Dayton, Ohio 45401.




# RCA

Distributor and Special Products Division, Cherry Hill Offices, Camden, N.J. 08101

NOVEMBER 1975

81

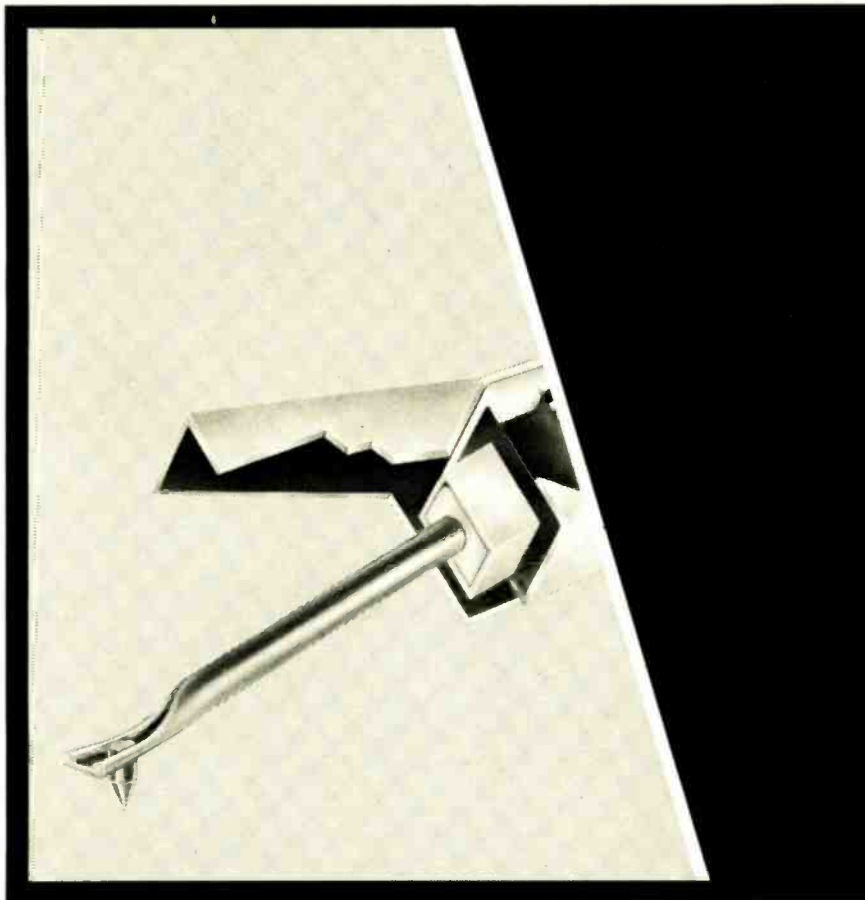

## This...protects your most expensive hi-fi investment.

Recognizing that a penny saved is a penny earned, may we suggest that trying to economize by putting off the replacement of a worn stylus could be like throwing away five dollars every time you play a record. (Multiply that by the number of records you own!) Since the stylus is the single point of contact between the record and the balance of the system, it is the most critical component for faithfully reproducing sound and protecting your record investment. A worn stylus could irreparably damage your valuable record collection. Insure against this, easily and inexpensively, simply by having your dealer check your Shure stylus regularly. And, when required, replace it immediately with a genuine Shure replacement stylus. It will bring the entire cartridge back to original specification performance. Stamp out waste: see your Shure dealer or write:



Look for the name SHURE on the stylus grip and the words "This Stereo Dynetic® stylus is precision manufactured by Shure Brothers Inc." on the box.

**Shure Brothers Inc.**  
222 Hartrey Ave., Evanston, IL 60204  
In Canada: A. C. Simmonds & Sons Limited

Manufacturers of high fidelity components, microphones, sound systems and related circuitry.



Circle 21 on reader service card

## CLINIC QUESTIONS

(continued from page 80)

A thin bright vertical line shows that you do have high voltage and vertical sweep, but no *horizontal* sweep. If you have high voltage, the horizontal output stage must be working. A good possibility for this would be an open yoke-return capacitor; this is C45, .039  $\mu$ F. This capacitor completes the *return* circuit from the horizontal winding of the yoke. Try bridging it. (Feedback; that was it!)

### NO VERTICAL SWEEP

*There's no vertical sweep on this Panasonic CT-26, and I can't find a schematic on it. Can you help?—T.G., Prairie Village, KS.*

The service data on this is in Sams Photofacts 1371-1. (That's the accurate part of the answer! Now for the regular stuff.) Check the voltages around that 9AQ8, and the 12FQ7-25HX5; the last two make up the vertical multivibrator. Just for luck, check the service switch for a short on the 25HX5 pin-1 grid. Should show a very high resistance.

(Feedback from reader: that wasn't it! R477, a plate load resistor, was open! Oh, well.)

### VERTICAL PROBLEM

*This Hitachi CT901 has an odd vertical problem. After two hours or so, it starts to roll, and then shrinks. Vertical height decreases to only 2-3 inches. I checked and changed transistors, etc.; no luck. Then I noticed that the +12-volt supply to this stage was increasing when the trouble started! Finally disconnected it and used a regulated 12-volt external supply. This cured the problem.*

*Now what? This supply comes from the horizontal output stage. Where do I go from here?—J.S., Montezuma, GA.*

I believe that I'd go to that horizontal output stage, and from there back to the regulated DC voltage supply for it. Check the regulated +120 volt supply. It looks as if you have a thermal problem, and very likely in the error-amplifier transistor of the regulator. Check all of the transistors in the regulator circuit while you're at it. (Try spray-cooling them just to see what happens.)

### PICTURE TUBE REPLACEMENT

*I want to replace the picture tube in my set, a 25AP22, with one of the new black matrix types. Can I do this?—P.J., Baltimore, MD.*

Yes, indeed. Just order a Matrix type with the same type number as your original tube. You'll probably see it listed as "25AP22BM" or some kind



(continued on page 88)





# CREI—the only home-study college-level training

## and now

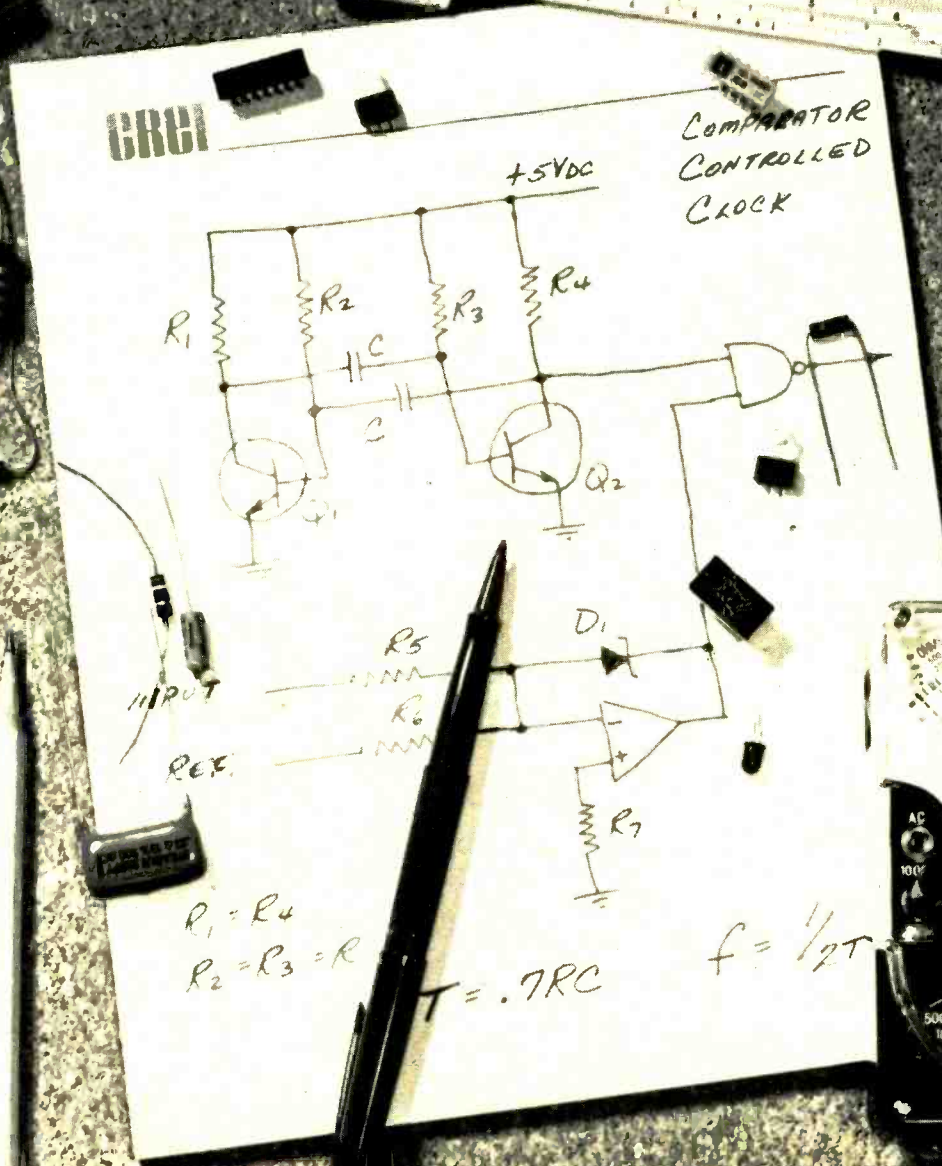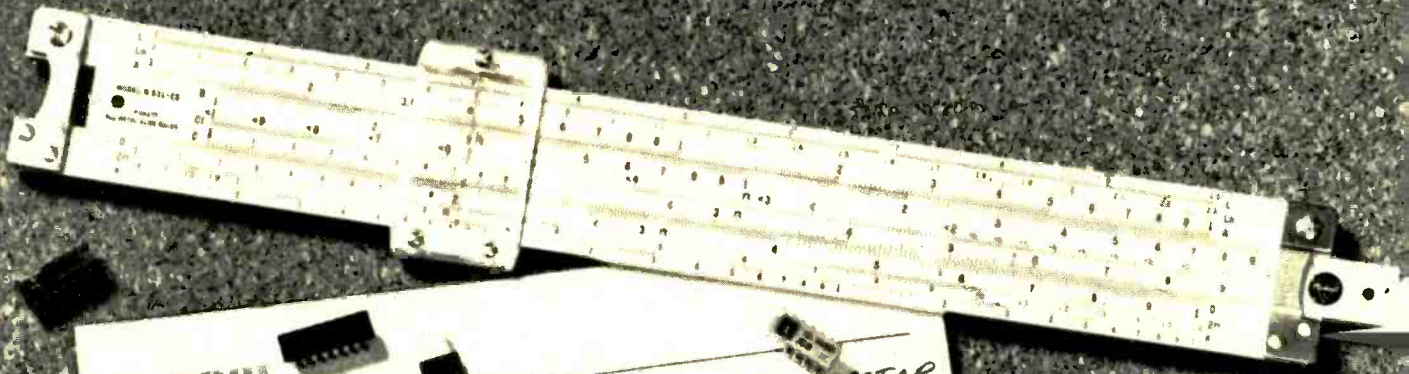

# program which gives you in electronic circuit design

## only CREI offers you a complete college-level Electronic Design Laboratory to speed your learning

**Electronic circuit design**—source of all new development in the application of electronics to new products and services. Without this skill, we would be unable to monitor the heartbeat of men in space. Without it, the computer revolution would never have occurred. And we would have yet to see our first TV show. *Yet, only CREI teaches electronic circuit design at home.*

### ELECTRONIC CIRCUIT DESIGN

A key skill which paces our nation's progress in countless fields—from pollution control to satellite tracking to modern medicine to exploring the ocean's depths. And beyond. A skill which *you* must have to move to the top in advanced electronics.

### CREI programs open up new worlds of opportunity for you.

In addition to electronic circuit design, CREI provides you with a full advanced electronics education in any of thirteen fields of specialization you choose. Communications, computers, space operations, television, nuclear power, industrial electronics—to mention just a few of the career fields for which CREI training is qualifying. With such preparation, you will have the background for a career which can take you to the frontiers of the nation's most exciting new developments. And around the world.

### This free book can change your life. Send for it.

If you are a high-school graduate (or equivalent) and have previous training or experience in electronics, then you are qualified to enroll in a CREI program to move you ahead in advanced electronics.



Send now for our full-color, eighty-page book on careers in advanced electronics. In it, you will find full facts on the exciting kinds of work which CREI programs open up to you. And full facts on the comprehensive courses of instruction, the strong *personal* help, and the professional laboratory equipment which CREI makes available to you. All at a surprisingly low tuition cost.

### And when you have it, talk with your employer about it.

Tell him you're considering enrolling with CREI. He'll undoubtedly be happy to know you are planning to increase your value to him. *And he may offer to pay all or part of your tuition cost.* Hundreds of employers and government agencies do. Large and small. Including some of the giants in electronics. *If they are willing to pay for CREI training for their employees, you know it must be good.*

**Send for Advanced Electronics today. You'll be glad you did.**

CREI Dept. E-1405F  
3939 Wisconsin Avenue  
Washington, D.C. 20016

Rush me your FREE book describing my opportunities in advanced electronics. I am a high school graduate.

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_


City \_\_\_\_\_ State \_\_\_\_\_ ZIP \_\_\_\_\_

If you have previous training in electronics, check here

Employed by \_\_\_\_\_

Type of Present Work \_\_\_\_\_

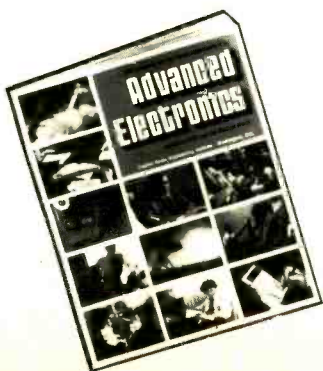Veterans and servicemen, check here for G. I. Bill information



# CREI

**CAPITOL  
RADIO  
ENGINEERING  
INSTITUTE**

WASHINGTON, D.C. 20016

# ARROW AUTOMATIC STAPLE GUNS


## CUT WIRE & CABLE INSTALLATION COSTS

... without cutting into insulation!

**SAFE!** Grooved Guide positions wire for proper staple envelopment! Grooved Driving Blade stops staple at right depth of penetration to prevent cutting into wire or cable insulation!

**No. T-18**—Fits wires up to 3/16" in diameter.

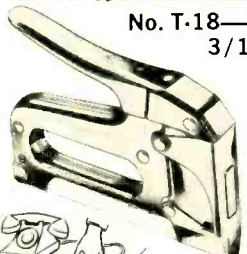BELL, TELEPHONE, THERMOSTAT, INTERCOM, BURGLAR ALARM and other low voltage wiring.




Uses T-18 staples with 3/16" round crown in 3/8" and 7/16" leg lengths.

**No. T-25**—Fits wires up to 1/4" in diameter.

Same basic construction and fastens same wires as No. T-18.

Also used for RADIANT HEAT WIRE

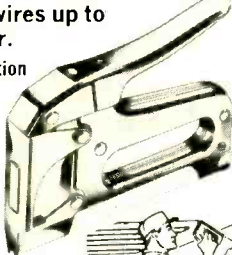


Uses T-25 staples with 1/4" round crown in 9/32", 3/8", 7/16" and 9/16" leg lengths

**NEW! Intermediate**

**No. T-37**—Fits wires and cables up to 5/16" in diameter.

Same basic construction as Nos. T-18 & T-25.

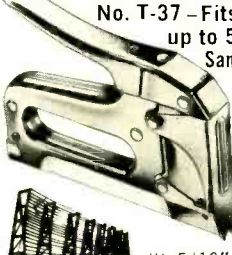Also used for CATV and DRIVE RINGS in stringing wires.




Uses T-37 staples with 5/16" round crown in 3/8", 1/2" and 9/16" leg lengths.

**No. T-75**—Fits wires and cables up to 1/2" in diameter.

RADIANT HEAT CABLE, UF CABLE, WIRE CONDUIT COPPER TUBING or any non-metallic sheathed cable.

Also used as DRIVE RINGS in stringing wires.



Uses T-75 staples with 1/2" flat crown in 9/16", 5/8" and 7/8" leg lengths.

ARROW FASTENER COMPANY, INC.  
271 Mayhill Street, Saddle Brook, N. J. 07663

## CLINIC QUESTIONS (continued from page 80)

of designation identifying a matrix tube. Incidentally, in the new tube type listings, a 23VALP22 is an exact replacement for your 25AP22.

### BAD FOLDOVER


*This Philco 15J27 has a massive foldover at the bottom of the screen. Checking capacitors showed nothing. I checked the 5.6-megohm resistor from the VERTICAL SIZE control to the +340-volt boost (see diagram); checked OK out of circuit. I left it disconnected and tried the set. Foldover gone! I don't get it.—H.D., Buffalo, NY.*

I don't either, but there's something out of pocket in there. The classic answer to questions about foldover is "something is upsetting the grid bias on the vertical output stage." This is

*good. I made several tests with no results, then I found that I could get an audio signal through to the screen from point 21. Nothing came through to the screen from point 20. Tying a jumper across these points, I had good sync. So, I replaced L7 and C24 (see diagram); no luck. Then I put the jumper back and it works nicely. I don't understand this!—M.G., Springfield, NJ.*

This happens. When you change a picture tube, quite often some little thing will show up; probably due to moving the chassis, pulling wires and so on. (My pet is pulling a yoke lead out and not noticing it).

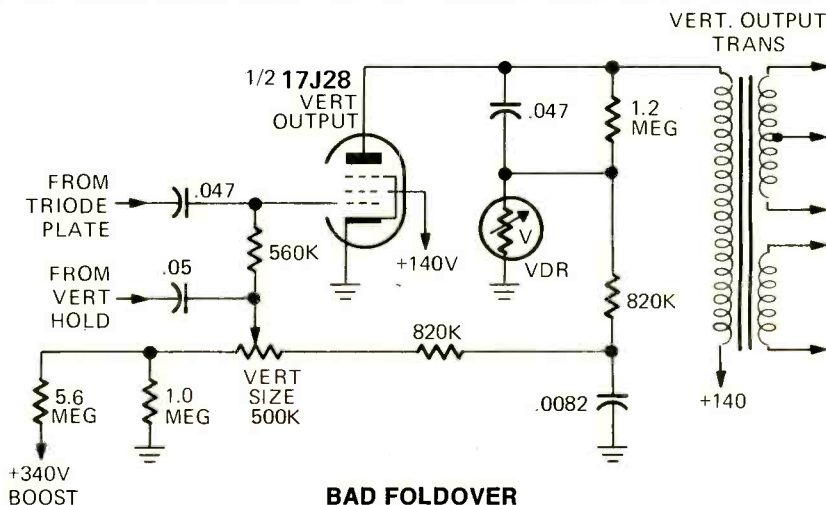You won't do too much harm by leaving the jumper in there. L7 is just a tiny peaking coil. The crystal ball says that the original parts are probably OK and that you have a hairline crack in the PC conductors somewhere between them. Check from the video detector output with an ohmmeter.



**BAD FOLDOVER**

apparently true here. Disconnect all of the resistors in the voltage-divider circuit around the vertical size control, and check them. This is quite a bag of worms, and one of them could be off. If that VDR turns out to be defective, try an Oneida GB-808; 1.0 mA at 290-330 volts. This is a replacement for the original Philco part.

### HARMONICS OF AM

*Broadcast band AM stations aren't supposed to radiate harmonics, are they? Still, I can pick up two or three AM stations on my four-band SW receiver, at double and sometimes triple their carrier frequencies. If these aren't radiating harmonics, then what is going on here?—G.K., Yardley, PA.*


You can tune in AM broadcast stations at what seems to be their second harmonic, especially if the stations are fairly close, as yours are. However, it is very likely that these "harmonics" are being generated in your own mixer stage! This is a non-linear stage. If it weren't, it wouldn't work. So, a very strong RF signal can develop beats and actually harmonics, but it's in this stage and not at the station.

I have made tests on radio stations and found practically no harmonic radiation. Then, the next day, heard this same thing on a SW radio. If you add a sharply tuned RF amplifier stage, this will usually get rid of this kind of a problem.


**R-E**
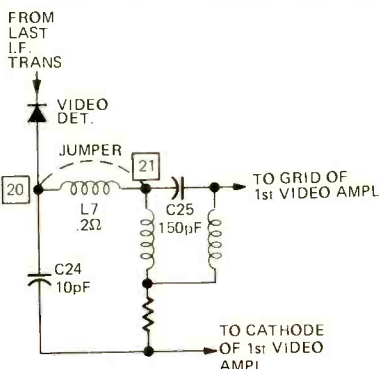
### NO SYNC

*After I replaced the picture tube in this RCA CTC-31A, I had no horizontal or vertical sync! Before, both were*



# It's your game.

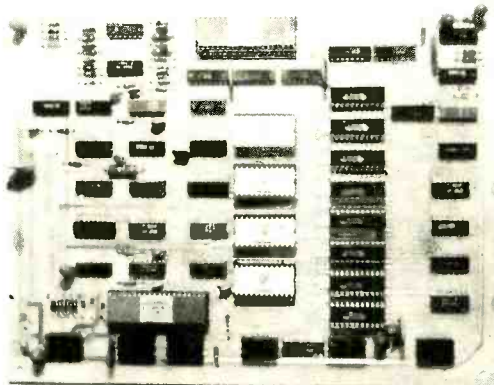

- real-time clock
- 16 digital I/O lines
- 4k RAM
- 512 times 8 PROM
- serial teletype interface
- hardwired ROM monitor (console emulator)

(Complete with usage, programming, and application manuals.)

## Still, our price goes down a lot easier.

Take the SPHERE CPU board and you can name a game, play it, and invent your own. It is a totally programmable computer base for fun or serious use. Only real design innovation by the TEAM at SPHERE CORPORATION could make the advances in micro-processing technology that could increase the capabilities and bring the price down. There have been no compromises and no short cuts... look at the features! You might even be interested in the complete 4K computer system kit for \$860.00! In fact, we

at SPHERE have a whole line of fine micro-processing parts, kits, peripherals and even full-blown systems.

Take advantage of the special mail order offer on our CPU board, and get one board at the OEM's 100-quantity price complete with the 3 manuals as listed. Use the coupon and have it delivered right away. It's your game and we at SPHERE CORPORATION make the difference count!

\* The Special OEM 100-quantity-price is extended to the hobby user for a single CPU board through mail order only. Offer ends without notice.

### We make the difference count.

SPHERE CORPORATION  
791 South 500 West # 7  
Bountiful, Utah 84010  
(801) 295-1368

Dear SPHERE:

The facts I read here convinced me!

Enclosed is my check or money order for \$860.00. Please rush me a SPHERE I System.


Please rush me more details on your low-cost computer system and peripherals. (Specific questions, if any, are attached.)

Print Name: \_\_\_\_\_

Address: \_\_\_\_\_

City: \_\_\_\_\_

State, Zip: \_\_\_\_\_

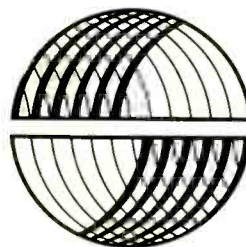

# SPHERE

SPHERE CORPORATION 791 South 500 West # 7  
Bountiful, Utah 84010 (801) 295-1368

# DON'T GET STUCK WITH THE TAB.

**Do your Christmas shopping before  
midnight Nov. 30th.**

If you've been saving Sylvania tube tabs, your time has come.

Unless your tabs are received at award headquarters by midnight Nov. 30th, all you'll have is a bunch of tabs.

And that includes those color picture tube labels that are worth 20 receiving-tube tabs.

But before that magic hour you can have anything in the '75 Save-a-Tab catalog.

After midnight your tabs will be as valuable as Cinderella's pumpkin.

Do your Christmas shopping now for everyone (especially yourself) from the catalog available at your Sylvania distributor.

But have your tabs at award headquarters by midnight Nov. 30th.

Nov. 30th, the world.

Dec. 1st, just tabs.

**GTE SYLVANIA**





# new products

More information on new products is available from the manufacturers of items identified by a Reader Service number. Use the Reader Service Card inside the back cover.

**TUNER SUBBER, Mark IV—CUV**, incorporates these features; tunes all VHF & UHF channels, electronic fine-tuning, dual 40 MHz IF output jacks and a battery condition indicator.

It tunes all 82 VHF and UHF channels for substitution tests of the tuner and the entire IF system of any 40-MHz TV receiver, and permits signal injection after the AGC controlled stages for a high speed AGC system



analyzing procedure. Use it anywhere. Battery or 120-VAC line powered, instrument automatically changes over to internal battery power when AC power is disconnected. The price is \$64.95.—**Castle TV Tuner Service, Inc.**, 5710 N. Western Ave., Chicago, IL 60645.

Circle 31 on reader service card

**STEREO RECEIVER, model 540**, features a sensitive tuner and a unconditionally stable amplifier. The tuner section features a 4-gang MOSFET front end combined with a compensated ceramic IF filter, a quadrature FM detector and a phase-locked-loop multiplexer. Specifications include an IHF sensitivity of 1.8  $\mu$ V, a capture ratio of 1.5 dB and stereo separation of more than 40 dB at 400 Hz and better than 30 dB across the band. The control center of the model 540



has dual concentric bass and treble controls, 12 dB per octave high-filter and volume and balance controls. In addition, there are 2 phono inputs, microphone, headphone and tape jacks on the front panel as well as main and remote speaker switching. The power amplifier section provides 40 watts per channel minimum RMS into 8 ohms from 20 to

20 kHz with no more than 0.3% total harmonic distortion. Rear panel jumpers permits separation of the amplifier and power amplifier sections. The unit measures 5 1/8" high  $\times$  15" wide  $\times$  11 1/2" deep and weighs 30 pounds. The suggested retail price is \$419.90.—**Pilot Radio Sales**, 165 West Putnam Avenue, Greenwich, CT 06830.

Circle 32 on reader service card


**DIGITAL MULTIMETER, model 334**, is designed for continuous operation in service, laboratory and testing applications. It has 5 ranges of AC and DC voltage and current and 6 ranges of resistance. Features include 3 1/2-digit resolution, automatic decimal point,



automatic overrange indication, 200-mV AC and DC ranges, fuseless protection on volts and ohms, and fast response. Power input is 105–125-VAC/210–250-VAC, 50–400-Hz. It measures 8 1/2-in W  $\times$  4-in. H  $\times$  6-in. D and weighs 3 1/2 lbs.—**Hickock Electrical Instrument Co.**, 10514 Dupont Ave., Cleveland, OH 44108.

Circle 33 on reader service card

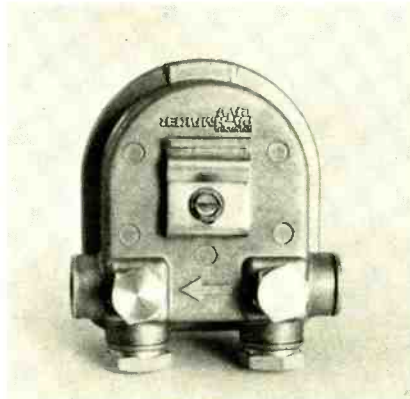**CATV MULTI-TAP, series 3800**, is for two or four subscriber service. Special features include a cable seizure that does not damage




center conductor or strain the internal circuitry, cast-in labyrinth RFI seal, and collars for direct application of shrink-sleeving to the housing. Specifications include—bandpass, 5

to 300 MHz, return loss, 23-dB minimum; tap-to-tap isolation, 30 dB; hum modulation, -65 dB at 6A tap value for 0 dBmV level.

The 3800 series can be pedestal or aerial mounted. The unit measures 3 1/4 in. wide  $\times$  3 3/4 in. high  $\times$  1 1/4 in. deep, less connector and mounting hardware. The suggested retail prices are \$6.25 each for the two-tap models and \$6.50 each for the four-tap models.—**GTE Sylvania**, Marketing Department, 114 S. Oregon St., El Paso, TX 79901.

Circle 34 on reader service card

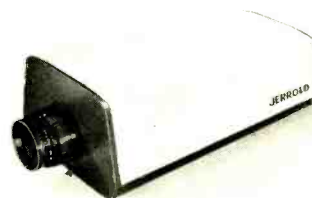**CCTV CAMERA, model TVC-501**, is a solid-state compact closed-circuit TV vidicon camera. The vidicon is a 2 1/2" separate mesh type with electrostatic focus and magnetic deflection. The position of the vidicon can be easily



adjusted for mechanical focusing and for operation with different lenses. An F/1.6 16mm lens is supplied with the camera. The center resolution of the camera exceeds 550 lines. The output is video, 1.4 volts P-P across 75 ohms. Automatic light compensation is 8000:1. The grey scale includes at least 10 steps. Signal to noise ratio exceeds 40 dB. Suggested retail price is \$495.00.—**Jerrod Electronics Corp.**, 200 Witmer Road, Horsham, PA 19044.

Circle 35 on reader service card

**CONDENSER MICROPHONE, model CM-1000**, features a cardioid pick-up pattern and an extended dynamic range. A gold metalized polyester film diaphragm provides exceptional high frequency transient performance. A bat-



tery operated power supply energizes the model CM-1000, but it may also be powered directly from a console (45V–50V). Switchable 10-dB and 20-dB attenuator pads and low-frequency rolloff network (-10 dB at



100 Hz) guard against amplifier and input overload.

Specifications include: Frequency response, 2–20,000 Hz  $\pm 2.5$  dB; output impedance (1 kHz), 600 ohms  $\pm 15\%$ ; sensitivity,  $-67$  dB  $\pm 1.5$  dB; signal-to-noise ratio, better than 50 dB; maximum SPL at 3% distortion, 139 dB; current consumption, less than 1.5 mA; operating voltage, 8.5V–9.1V; dynamic range, 115 dB.

An optional pinpoint capsule is also available, model CP-102, to convert the microphone to a super-omni-directional pick-up pattern. Suggested retail price is \$290.00 including preamplifier, battery power supply, windscreen, connecting cables and swivel stand adaptor. The suggested retail price for the optional model CP-102 is \$100.00.—Nakamichi Research, Inc., 220 Westbury Ave., Carle Place, NY 11514.

Circle 36 on reader service card


**GUTTER CLAMP ANTENNA MOUNT** features a high-tension spring that clamps the unit fast to any make vehicle. A special rubber bumper prevents marring the car's finish. Clamp styles are available to fit all popular makes of antennas and complete mounts.



Also, antennas of both the quarter wave type and gain antennas for low, high and VHF bands complete with the clamp are available. Provisions are also made to assure a proper ground plane for maximum radiation efficiency of the antenna.—Larsen Antennas, P.O. Box 1696, Vancouver, WA 98663.

Circle 37 on reader service card

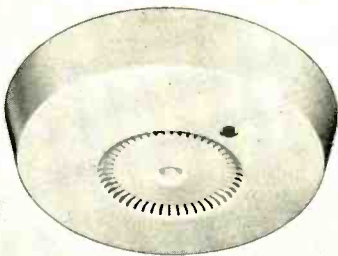**COMBUSTION DETECTORS**, models 580 and 600, operate on the ionization principal, detecting fire at its earliest stage before smoke,



heat and flames develop. Both models contain built-in batteries that are constantly monitored. When battery voltage drops to a pre-set warning level, a built-in horn will sound,

indicating trouble. The battery is easily replaced and will last approximately one year. **Alarm Device Manufacturing Company**, Syosset, NY 11791.


Circle 38 on reader service card

**STEREO PREAMPLIFIER**, model SP 5200, is a linear flat-response preamplifier that has provisions for the connection of external signal processing devices. There is a five-input

monitor selector that allows listening to the signal source whether the source is processed by an external device or not.

Operating controls consist of a record source selector, a monitor selector, a mode switch and a pair of volume controls. The volume control consists of a pair of slide potentiometers. The gain of the input preamplifier is adjustable from 27 dB to 55 dB so that it can accommodate any cartridge re-
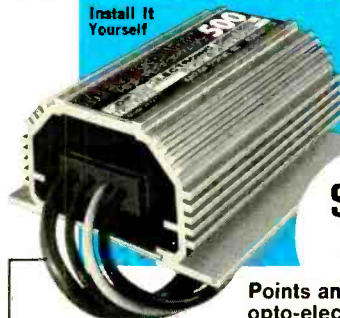
## MEGASPARK™ BREAKERLESS ELECTRONIC IGNITION FOR ALL CARS



NOW optically-controlled MEGASPARK—the next generation in dependable electronic ignition—gives you:

- Peak Engine Performance
- Reduced Maintenance
- Perfect Engine Timing and Dwell
- Unmatched Fuel Economy
- Lowest Operating Expense
- Lifetime Guarantee

Only  
**\$48.50**  
Std. Md. 400

Points and condenser are replaced by a supremely accurate opto-electronic sensor, so you eliminate tune-ups forever; timing and dwell never need resetting.

Made in U.S.A.

**MEGASPARK IS A SUPERIOR PRODUCT** absolutely improves economy, pickup and performance on every car under every operating condition. Optical trigger and fast switching is the secret. With the new High-Power Darlington Amplifier you get a fatter, longer duration "complete combustion" spark - great for today's lean mixture engines. Fast,  $\frac{1}{4}$  microsecond switching time means cool, long-life, trouble-free operation.


**OPTICAL TRIGGER ELIMINATES MECHANICAL PROBLEMS.** MEGASPARK'S infra-red opto-electronic sensor eliminates points and condenser. No more worries over corroded, pitted points. The modern opto-electronic trigger device never wears out, never needs adjustment. It is totally accurate - for the life of the car. Timing is not retarded as it is with other add-on units using magnetic pickup sensors.

Installation? No Problem; Detailed Instructions Furnished! Fits All Cars - 4, 6, 8, Cylinder. Domestic and Foreign - Rotarys, too.

Use your standard coil or check the box below for our special discount offer on famous Mallory Voltmaster Mark II Coils.
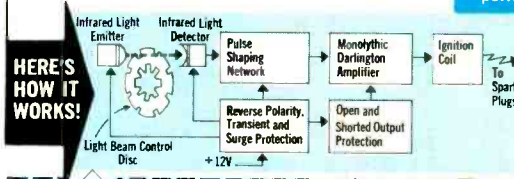
### LIFETIME WARRANTY

Each MEGASPARK carries a lifetime free repair or replacement warranty. No time limit.



**POWER TO SPARE IN SUB-ZERO WEATHER.** MEGASPARK means quick starts on cold, damp mornings. Solid state, controlled optical triggering is rugged and reliable. It eliminates all problems associated with the points and condenser. It provides for cylinder-to-cylinder firing accuracy simply unattainable with any other system - a key factor in gas economy. Extended dwell means increased coil saturation and higher spark intensity.

**CUT MAINTENANCE AND FUEL COSTS.** MEGASPARK pays for itself quickly. It costs less than most tuneups and it locks the tuneup in... indefinitely. MEGASPARK saves you money thru increased efficiency and gas mileage, decreased maintenance costs. You will get better gas mileage; spark plugs last longer; pickup and power is enhanced; service costs go way down.

**RELIABILITY AND DESIGN ARE SECOND TO NONE.** Made with top-quality, U.S. made components housed in a heavy aluminum case, each unit is fully protected against reverse polarity, open secondary and power surges. Completely waterproof and heat resistant.

### ATTENTION CD IGNITION OWNERS

Convert your CD to opto-electronic operation with MEGASPARK 300 for only \$34.50. Works perfectly with ALL CD units.

**MODEL 500** High performance model for superior sparking and engine efficiency. Delivers 20% more power than Model 400.

**MODEL 400** Standard model exceeds requirements of all cars.

**MODEL 300** Trigger Unit modernizes previously installed CD ignitions.

**IGNITION SYSTEMS INC., 2547 - 8th St., Space S, Berkeley, CA 94710, (415) 845-3584**

Enclosed is my check ; money order ; in the amount indicated. Please RUSH — Satisfaction Guaranteed.

- MEGASPARK 500 @ \$64.50
- MEGASPARK 400 @ \$48.50
- MEGASPARK 300 @ \$34.50
- VOLTMASTER Mark II Coil @ \$19.95

Add for Postage and Insurance. \$1.00  
California residents add sales tax

TOTAL: \_\_\_\_\_

SEND FREE ILLUSTRATED BROCHURE

Charge my  
 MASTER CHARGE  
 BANKAMERICARD  
(Please provide full credit card info)

**IMPORTANT:** Indicate make and model of car, engine displacement and number of cylinders.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_

STATE \_\_\_\_\_

ZIP \_\_\_\_\_

Circle 26 on reader service card


# More chances to be right



Thousands more cross references



Transistor kit for foreign sets

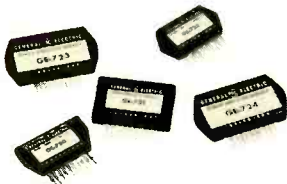

Replacement amplifier modules



All the help you need at your authorized distributor

Tube Products Department  
General Electric Company  
Owensboro, Kentucky 42301

**GENERAL ELECTRIC**


ardless of its output voltage. Specifications include a frequency response of 20 Hz to 20 kHz  $\pm 0.1$  dB, total harmonic distortion of 0.05% maximum from 20 Hz to 10 kHz and a



rated signal output of 2.5 volts. At rated output, noise is 95 dB minimum measured from 20 Hz to 20 kHz. Suggested retail price is \$489.95.—**Burwen Laboratories**, 209 Middlesex Turnpike, Burlington, MA 01803.

Circle 39 on reader service card

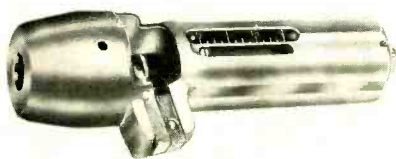**CABLE PREPARATION TOOLS.** A new series of coaxial cable stripping tools save time by preparing cables for their connectors in less than 15 seconds. The cut dimensions are accurate to within 20 thousandths of an inch. To use the tool, just insert the cable in one end and rotate it to either expose the center conductor or strip the outer jacket, depending



on the specific tool used. Then insert the cable into the other end of the tool and it is rotated to either remove the outer jacket or to remove the dielectric cable. The cutter blade will not nick the center conductor of the coax nor will it leave loose strands of wire. The tools are available for cable sizes from RG-59 to 0.75-in. aluminum cable. A set of replacement cutting blades is also available for use in the stripping tools.—**Blonder-Tongue Laboratories, Inc.**, Old Bridge, NJ 08857.

Circle 40 on reader service card

**CRT RESTORER/ANALYZER**, model 467, employs an exclusive test method that tests all three guns of a color CRT simultaneously under actual operating conditions. The guns are tested in sequence, 20 times per second, and the results are displayed simultaneously on three color coded meters. The model 467



tests for true beam current—current that passes through the G1 aperture to the screen. Restoration is performed with minimal

danger of cathode stripping. The model 467 can be used to test and restore any type of color or black-and-white picture tube without calculation or reference to charts. It also provides tube-life indication, finds and removes shorts, and identifies and corrects tracking deficiencies in color CRT's. The price is \$279.00.—**B&K-Precision**, Div. of Dynascan Corp., Chicago, IL 60613.

Circle 41 on reader service card

**TURNTABLE**, model SA-525, is a manual single-record direct-drive turntable that is driven by a 20-pole, 30-slot DC brushless motor. The motor is servo-controlled. Two



speeds are available, 33 $\frac{1}{3}$  or 45 RPM, with a fine adjustment for both speeds. Speed control is aided with the help of an illuminated stroboscope with markings on the platter. The platter has a diameter of 12 $\frac{1}{4}$ -in., is aluminum die-cast and weighs 3.1 lbs. The tonearm is S-shaped, incorporating a special resonance absorber. The unit has bias and lateral balance compensation and a separate lever at the arm base for cueing.—**Sansui Electronics Corp.**, 55-11 Queens Boulevard, Woodside NY 11377.

Circle 42 on reader service card

**SOLDERING STATION**, WTCP series, features an exclusive "closed loop" method of controlling maximum tip temperature. This protects temperature sensitive components.

The complete station includes a low-voltage stainless steel pencil-grip iron, 700° F screwdriver tip, holder, sponge and receptacle, and a three-wire non-burning silicone power cord. Model WTCP-L adds a built-in on/off switch and red pilot light.



The 60-watt units control temperatures in three ranges—600°, 700° and 800° F, determined by choice of quick-change, anti-oxidation-coated tips in many configurations and sizes.—**Weller-Xcelite Div., The Cooper Group**, Apex, NC 27502.

Circle 43 on reader service card

**AUDIO GENERATOR**, model LAG-26. Fast rising square waves for testing transient response and low distortion sine waves are among the features. It has a sine wave output range of 20 Hz—200 kHz at 0-5 VRMS


with  $\pm 1$ -dB flatness and with distortion at less than 0.5% below 20 Hz. Square wave output is 20 Hz–20 kHz in the 0-10V P-P voltage range with 0.5- $\mu$ s rise time. The generator can synchronize signals from an ex-



ternal source and has a calibration accuracy of  $\pm 3\%$ . Output impedance is 600-ohms unbalanced and the frequency range is in 4 decade-bands. The unit measures 6-in. H  $\times$  10-in. W  $\times$  5-in. D and weighs 5.5 lbs. The price is \$139.95.—**Leader Instruments Corp.**, 151 Dupont St., Plainview, NY 11803.

Circle 44 on reader service card

**MOBILE PA AMPLIFIER**, *Realistic MPA-10*, is designed for 12-volt operation in cars, trucks, campers or boats. The unit measures 1 1/2 in.  $\times$  4 1/2 in.  $\times$  6 1/2 in. and comes with a dynamic mike and hanger for clipping it to the side of the unit. Separate microphone and auxiliary input jacks allow connection of a tuner, ceramic phono or tape player to the amplifier with pushbutton selection of either or both for paging over music. Output power is 10 watts RMS into 8 ohms. Frequency response is 200 Hz to 10 kHz at full power. A

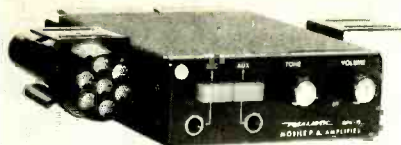

tone control allows adjustment for best tonal quality. Suggested retail price is \$39.95 complete with microphone and mounting hardware.—**Radio Shack**, 2617 West Seventh Street, Fort Worth TX 76107.

Circle 45 on reader service card



"Which one of you fellas is the best TV repairman?"

## MOVING?

Don't miss a single copy of **Radio-Electronics**. Give us:

Six weeks' notice

Your old address and zip code

Your new address and zip code

ATTACH  
LABEL  
HERE

name (please print)

address

city state zip code

Mail to: **Radio-Electronics**  
**SUBSCRIPTION DEPT., BOULDER, COLO.**  
80302

## You don't have to buy a new car to get an electronic ignition.



Most of you know the evaluation of automotive electrical systems . . . an evaluation characterized only occasionally by efficiency and performance. I know that, and that's why I use the Delta Mark Ten B CDI on all my cars, new and old. And believe me, you don't have to have a new car to appreciate the best electronic ignition available today. Study these features and you'll know what I mean.

1. Mark Ten and Mark Ten B Capacitive Discharge Ignition Systems are manufactured by Delta Products, Inc., a company with a conscience, and with a proven record of reliability both in product and in customer relations.
2. The Mark Ten CDI's really do save money by eliminating the need for 2 out of 3 tune-ups. Figure it out for yourself. The first tune-up or two saved pays for the unit, the rest is money in your pocket. No bunk!
3. Because the Mark Ten CDI's keep your car in better tune, you actually can save on expensive gasoline.
4. With a Mark Ten, spark plugs stay clean and last longer . . . fouling is virtually eliminated.



No matter what kind of car you drive, it too can use a Delta quality lift.

I want to know more about Mark Ten B CDI's. Send me complete no-nonsense information on how they can improve the performance of my car.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_



**DELTA PRODUCTS, INC.**

P.O. Box 1147, Dept. RE, Grand Junction, Colo. 81501  
303-242-9000

Mark Ten B, assembled	\$64.95 ppd	Standard Mark Ten, assembled	\$49.95 ppd
Mark Ten B, kit	\$49.95 ppd	Deltakit®	\$34.95 ppd

Circle 27 on reader service card

# DIGITAL PERFORMANCE YOU CAN RELY ON.



The Hickok Model 334 DMM is a rugged, non-temperamental, hardworking tool that's easy to use and easy on your eyes. Hickok has established a unique reputation in digital electronics during the past 10 years. The Model 334 is another example of our engineering expertise — an economical lab quality instrument with exceptional durability and accuracy.

- Easy reading, green fluorescent display
- 3½ digit — auto polarity
- 26 ranges including 200 mV AC & DC ranges
- Fast response — 2.5 readings/sec

Basic Accuracies (% of reading)  
 DC Volts;  $\pm 0.2\%$  ( $\pm 0.5\%$  on 200V, 1200V ranges)  
 AC Volts;  $\pm 0.5\%$  ( $\pm 2.0\%$  on 200 mV, 2V ranges)  
 OHMS;  $\pm 0.5\%$   
 DC Current;  $\pm 1.5\%$   
 AC Current;  $\pm 2.0\%$

Ask to see the Model 334 at your Hickok distributor. It's a no compromise DMM at a price you can afford.

**\$22900**

## HICKOK

**the value innovator**

INSTRUMENTATION & CONTROLS DIVISION  
 THE HICKOK ELECTRICAL INSTRUMENT CO.  
 10514 Dupont Avenue • Cleveland, Ohio 44108  
 (216) 541-8060 • TWX: 810-421-8286

Circle 62 on reader service card

## new lit

All booklets, catalogs, charts, data sheets and other literature listed here with a Reader Service number are free. Use the Reader Service Card inside the back cover.

**SERVICEMAN/TECHNICIAN CATALOG.** A 48-page illustrated mail-order catalog which has been specifically designed as a quick reference ordering guide for use by radio/TV servicemen, electronic technicians and hobbyists. Included are tools, service and repair kits, test equipment, tubes, phono cartridges, speakers and microphones, antennas, components and many other servicing aids of various major manufacturers.—**Fordham Radio Supply Co.**, 558 Morris Avenue, Bronx, NY 10451.

Circle 46 on reader service card

**ENGINEERING MANUAL & PURCHASING GUIDE.** 228-page catalog of electronic components. Included are complete specifications, illustrations and information which describe each product. You'll find wire, cable, solid-state devices, test equipment, timers, connectors, relays, tools, capacitors and other electronic parts for virtually any application.—**Allied Electronics**, Dept. 76, 401 East 8th Street, Fort Worth, TX 76102.

**COSMOS CIRCUITS.** 246-page catalog and applications manual that describes two lines of CMOS logic circuits—the 54C/74C and CD4000 series. This paperback handbook contains data sheets, specifications, diagrams, charts, graphs, applications information, and a cross reference.—**National Semiconductor Corporation**, 2900 Semiconductor Drive, Santa Clara, CA 95051.

Circle 47 on reader service card

**STEREOPHONES.** 6-page brochure describes five headphones plus a 4-channel converter. These include two stereo lightweight models, a stereo high-performance model and a Electret model. In addition, there's a 4-channel headphone that uses the Fixler Effect for enhancing separation. A 4-channel converter that is designed to be used with the 4-channel headphone synthesizes the 4-channel effect from existing 2-channel program material. Brochure includes specifications and features.—**Telephonics**, 770 Park Avenue, Huntington, NY 11743.

Circle 48 on reader service card

**SPEAKER BROCHURE.** 8-page brochure describes six hi-fi speakers incorporating the Heil air-motion transformer. Specifications are listed for each speaker. The brochure also explains the principal behind the Heil air-motion transformer.—**ESS, Inc.**, 9613 Oates Drive, Sacramento, CA 95827.

Circle 49 on reader service card

**VOM BROCHURE.** 4-page brochure describes the new model 60 series VOM's. The brochure lists specifications, features and application data for the model 60, model 60-A ( $\pm 1\frac{1}{2}\%$  DC accuracy) and the model 60-K. These 28-range VOM's feature drop-proof and burnout-proof protection. They can be safely dropped from 5-foot heights and have diode and fuse protection. The brochure includes complete specifications and lists a host of optional accessories.—**Triplet Corp.**, Bluffton, OH 45817. **R-E**

Circle 50 on reader service card

## INTERMITTENT BRIGHTNESS

*The brightness level jumps up and down on this CTC-25X RCA. When this happens, the picture blurs and loses focus. I can rap the chassis and make it come back. The voltages on the picture tube vary when this trouble shows up. High voltage goes down. I suspected a bad picture tube, but I tried an isolation brightener and it didn't help—so, I need yours!—A.G., Westminster, Calif.*

If this is a "jar intermittent", you can find it much more easily. Most likely cause is a bad solder joint somewhere on the PC board. Take a new lead pencil, and tap *lightly* around at different points. Find out where the most sensitive place is; where you can

just barely tap it and make the problem appear. When you get here, start moving various parts gently; if you can find one that makes the picture cut out when you move it, OK. One end of it is probably intermittent.


Some parts which could cause this would be the common cathode resistor of the color-difference amplifiers; the B+ or boost feed to the screen controls, and so on. Check the horizontal *blinker* stage, especially the 0.22-mf coupling capacitor to the difference amplifiers. If this is opening intermittently, it will upset the bias on the three difference amplifier tubes and cause some problems.

**STATE-OF-SOLID-STATE**

*(continued from page 34)*

tional control lines that are a supervisory link between the CPU and the peripheral. Each PIA has six registers that function like standard memory locations.

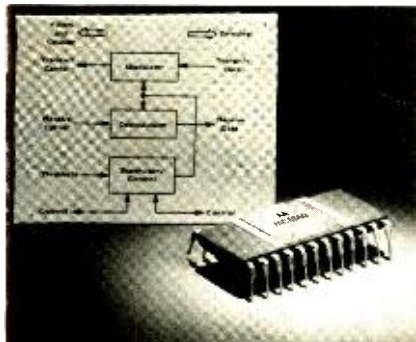
The Asynchronous Communications Interface Adapter (ACIA) is a serial output circuit. The output data is in a sequential form one bit after the other.



**MOTOROLA MC6860 MODEM**

Sequential data is processed and sent out over voice grade telephone lines to remote terminals or other computers. The actual modulator-demodulator job of putting the serial data onto the phone line is done by the remaining circuit type, the MC6860, 0 to 600 bit-per-second MODEM.

1 0 : 3 5

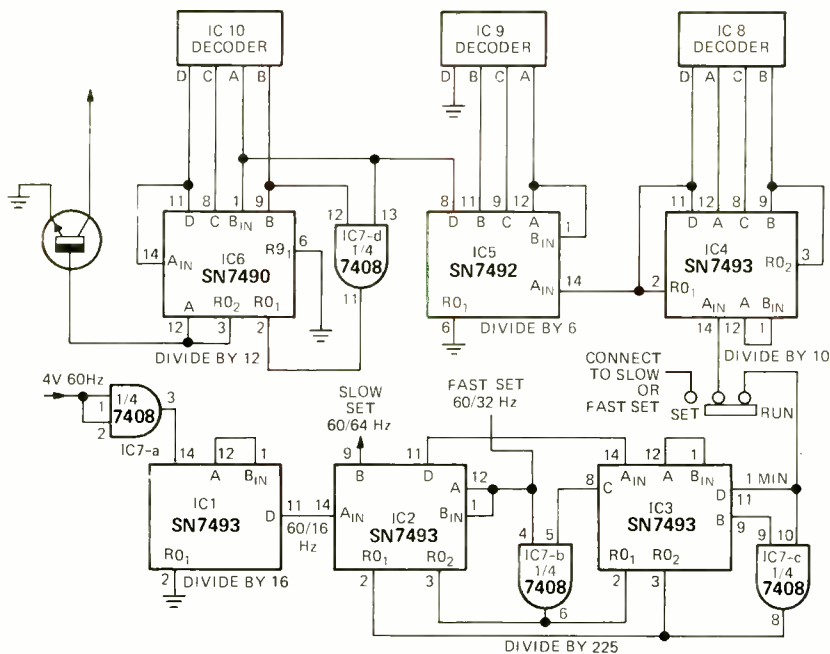


**FIG. 2—TTL CLOCK circuit.**

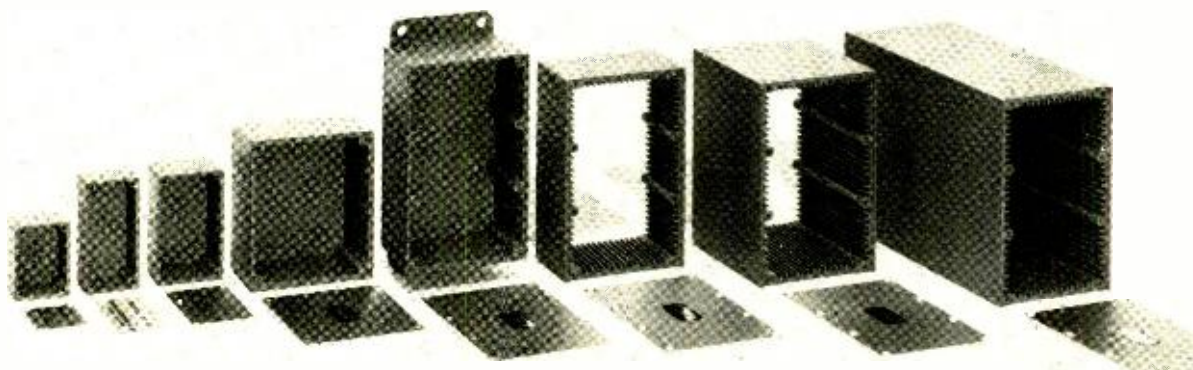Prices of the five available circuit types are: MC6800, \$360; MCM6810L, \$30.50; MCM6810L-1, \$37.50; MCM6820, \$20; MCM6830L, \$35; MC6860, \$75. All prices are for 1 to 24 quanti-

ties. The MC6800 and MC6820 are 40-pin ceramic dual-in-line devices and the others are 24-pin units. Software (programming) support now includes a *(turn page)*

# MEET OUR FAMILY



## of shielded "black boxes"

Almost 10 years ago (1966 to be exact) we introduced our first two series of shielded electronic enclosures. They became an overnight success. Since then the demand for different sizes, shapes and applications has increased our family to eight series of models, each with a noise rejection greater than 70db.

Sizes range from 1.50" x 1.13" x 0.88" to 4.13" x 2.68" x 6.0"; in blank versions or with a complete choice of coaxial connectors; painted or unpainted; with or without printed circuit card guides; with mounting flanges or bottom mounting plates. All models supplied with aluminum covers and screws.



**POMONA ELECTRONICS**  
A Division of ITT

1500 East Ninth St., Pomona, California 91766 Tel: (714) 623-3463

Circle 63 on reader service card

**SOLD ONLY THROUGH ELECTRONIC DISTRIBUTORS**

NOVEMBER 1975

cross-assembler and interactive simulator, with more on the way. American Microsystems Inc. will second-source the microcomputer circuits.

### TTL clock circuit

Kenneth Bagnall of Bagnall Electronics sent me a clock circuit (Fig. 2) that is timed by the 60-Hz power-line frequency. The circuit has ten IC's plus some digit driver-transistors, the exact number depending upon the display chosen. Especially interesting are the instructive 7400 TTL counter feedback strategies.

The input to IC7-a, the first section of the SN7408 Quad 2-Input AND Gate

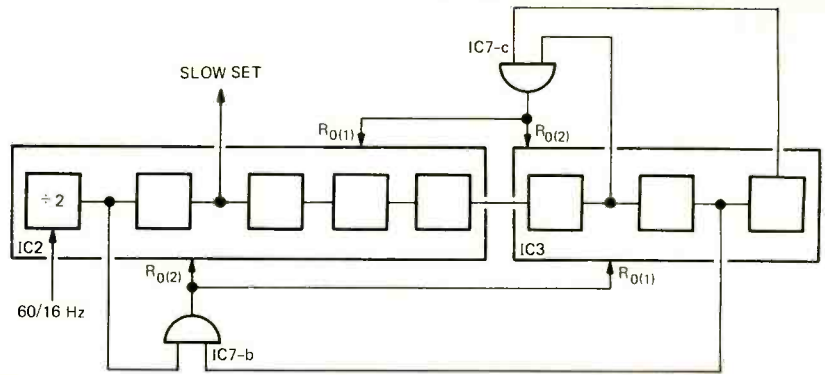


FIG. 3—DIVIDE-BY-225 counter from TTL clock circuit.

is a 4-volt 60-Hz sine wave. The gate converts the sine wave into a square wave that drives an SN7493 4-bit Binary Counter (IC1), the first of 6 counter devices in the clock. IC1 operates as a straight divide-by-sixteen with the four stages cascaded by connecting pins 1 and 12. The output frequency at pin 11 is 60/16 Hz.

The clock displays hours and minutes so the basic frequency needed to drive the display counters is one cycle per minute. After the initial division by 16, another division by 225 gives a combined division of 3600.  $60 \text{ Hz} / 3600 = 1/60 \text{ Hz}$  or one cycle per minute. The divide-by-225 function is accomplished by two SN7493's with a total of eight series-connected binary dividers. Two gates from the SN7408 IC is used for resetting the binary dividers (See Fig. 3.) The 7493 IC has two reset inputs— $R_{0(1)}$  and  $R_{0(2)}$ . The zero in the subscript indicates that the counter is reset to zero when the reset function is activated. An on-the-chip NAND gate requires that both inputs be 1's to reset all the counter stages.

The output of each of the 7408 gates (IC7-b and IC7-c) drives one of the reset inputs on IC2 and IC3. Staggering the AND gate outputs so that each gate controls one reset input to both IC2 and IC3 causes the counters to reset when the four inputs to IC7-b and IC7-c are simultaneously high. The counter state at which the reset condition is satisfied is from left to right 1XXXX111, where the X's are "don't cares" and may be either 0's or 1's. But as the counter steps in binary fashion starting from 0, the first situation that meets the reset pattern is 10000111. From left to right the counter digits represent weights of 1, 2, 4, 8, 16, 32, 64, and 128. Adding the weights of the stages set to 1:  $1 + 32 + 64 + 128 = 225$ . At the 225th pulse the divider resets to zero.

When the set switch is in the RUN position, the 1/60 Hz signal (1 pulse-per-minute) clocks IC4, the SN7493 minute-units display counter. By connecting the B and D (2 weighted and 8 weighted, respectively) outputs to the two reset input terminals, the count is

## BARGAIN BONANZA OF EDLIE HIGHEST QUALITY KITS ONLY NEW PRODUCTS

- (H175) 70 1/2w CARBON RESISTORS \$1.00  
Asst. values. Some 5%.
- (H154) 150 CUT LEAD RESISTORS \$1.00  
Carbon, all leads long enough for soldering.
- (H149) 20 POLYSTYRENE TOP GRADE CAPACITORS \$1.00
- (H132) 20 DUAL POTS \$1.00
- (H138) 10 SLIDE SWITCHES \$1.00  
All types: DPDT, SPST.
- (H134) 8 ROTARY SWITCHES \$1.00  
Some multiple gang.
- (H128) 13 MINIATURE ELECTROLYTIC CAPACITORS \$1.00  
Axial & upright, popular values.
- (H144) TRANSISTOR REPAIR KIT \$1.19  
Various parts used to repair transistorized devices.
- (H137) 10 INSTRUMENT KNOBS \$1.00  
Made by Ratheon, etc. With set screws. "1/4" shaft."
- (H164) 4 ROLLS OF WIRE \$1.00  
Approx. 25 ft. per roll, 20-28ga.
- (H140) TAPE RECORDER SPARE PARTS KIT \$2.95  
Parts for repairing most tape recorders: capacitors, meter, pilot lamp, jacks, and MUCH MORE.
- (H167) 10 MINIATURE POTENTIOMETERS \$1.00
- (H182) 2 MISC. METERS \$1.00  
Miniature.
- (H156) 60 DISC CAPACITORS \$1.00  
Asst. from .0001 to .1, most 600v, Z5U, NPO, N750, etc.

### SURPLUS TUBES

All guaranteed for 1 full year.  
**ANY 3 FOR \$1.25**

Acquired from U.S. Defense depots or removed from equipment (new and used). These are laboratory tested and guaranteed for one full year. Most are of such standard makers as RCA, GE, etc.

3A4	6AU6	6EB8	12AL5
3AF4	6AV6	6EJ7	12AL11
3BN6	6AV11	6EM7	12AT7
3DG4	6AX4	6ER5	12AU7
3KT6	6AX5	6EY6	12AV6
3Q4	6AY3	6GF7	12BE6
4BC5	6AY11	6GH8	12BH7
4BN6	6BA6	6GN8	12C8
4BU8	6BG6	6GU7	17J28
4BZ7	6B8	6K6	18FW6
4CY5	6BQ6	6K11	21KQ6
5V6	6B26	6LB6	25L6
5Y3	6CB6	6SN7	35EH5
6AF4	6CG7	6T8	35Z5
6AG5	6CM7	6V6	36AM3
6AG7	6DE4	6W4	50A5
6AL5	6DR7	6X4	50L6
6AQ7	6DW4	10EW7	
6AT6	6EA8	12AE7	

- (H147) 4 lb. GRAB BAG SPECIAL \$1.00  
Full of exotic and exciting electronics parts.
- (H155) TUBE BONANZA! \$1.00  
20 asst. popular tubes, untested.
- (H141) 6 RCA JACK STRIPS \$1.00  
From 2-6 per strip.
- (H142) 50 PRECISION RESISTORS \$1.00  
All 1%, 1/2w and 1w, low and high ohmages.
- (H150) 15 HI-FI KNOBS \$1.00  
Every one superb! Purchased from Harmon, Kardon, Fisher, etc.
- (H102) CALCULATOR KEYBOARD \$2.95  
Wild Rover C-1380. Can be used with CT5001. 4 function, clear, clear entry and constant. 7 cm x 9 cm.
- (H010) MJ4032/MJ4035 DARTINGTON PAIR. High power 150W, HFE 2500 typ. TO-3 case. With data. \$7.50 pair
- (H009) TC-3 MICA WAFERS 10 for 25¢
- (H1104) IC REMOVAL AND INSERTION TOOL \$4.95  
"Pul-n-sertic" extracts and inserts ICs without damage.
- (H271) 1N4148 High Speed switching diode. Full leads. 12 for \$1.00

**MONEY BACK GUARANTEE**  
Terms: Minimum order \$4.00. Include postage. Either full payment with order or 20% deposit, balance C.O.D.

**WRITE FOR FREE VALUE PACKED CATALOG**  
Listing thousands of components, tubes, transistors, IC's, kits, test equipment.

**BONUS FREE CAPACITOR KIT**  
With Every \$5 Purchase

- ### 30 AMP STUD RECTIFIERS
- (HLSS54) 50V \$1.19
  - (HLSS55) 100V \$1.39
  - (HLSS56) 200V \$1.59
  - (HLSS57) 400V \$1.79
  - (HLSS58) 750V \$1.99
  - (H1336) TO-3 TRANSISTOR sockets. 12 for \$1.00
  - (H298) 1 WATT ZENERS 60¢ available in 5V, 9.1V, 12V, 24V.
  - (H1092) Z-5 SILICONE HEAT SINK COMPOUND \$2.95  
1 oz. tube
  - (H008) 14 pin DIP sockets 3 for \$1.00
  - (H260) 2N3638A PNP high speed switch. HFE 100 TO-105 case. 2 for \$1.00

- ### THIS MONTH'S SPECIALS!
- |            |                                      |                                    |
|------------|--------------------------------------|------------------------------------|
| <b>TTL</b> | <input type="checkbox"/> 7400 16¢    | <input type="checkbox"/> 7446 80¢  |
|            | <input type="checkbox"/> 7401 18¢    | <input type="checkbox"/> 7447 80¢  |
|            | <input type="checkbox"/> 7402 23¢    | <input type="checkbox"/> 7448 80¢  |
|            | <input type="checkbox"/> 7403 23¢    | <input type="checkbox"/> 7473 49¢  |
|            | <input type="checkbox"/> 7404 23¢    | <input type="checkbox"/> 7474 49¢  |
|            | <input type="checkbox"/> 7405 23¢    | <input type="checkbox"/> 7475 85¢  |
|            | <input type="checkbox"/> 7406 23¢    | <input type="checkbox"/> 7476 53¢  |
|            | <input type="checkbox"/> 7410 23¢    | <input type="checkbox"/> 7490 79¢  |
|            | <input type="checkbox"/> 7411 27¢    | <input type="checkbox"/> 7492 79¢  |
|            | <input type="checkbox"/> 7413 40¢    | <input type="checkbox"/> 7493 69¢  |
|            | <input type="checkbox"/> 7420 23¢    | <input type="checkbox"/> 7495 79¢  |
|            | <input type="checkbox"/> 7430 23¢    | <input type="checkbox"/> 74121 57¢ |
|            | <input type="checkbox"/> 7440 30¢    | <input type="checkbox"/> 74122 57¢ |
|            | <input type="checkbox"/> 7442 \$1.12 | <input type="checkbox"/> 74123 67¢ |

- ### LINEARS
- LM309K 5v la reg. \$1.15
  - 555 Timer 75¢
  - 566 Function gen. \$1.75
  - 567 Tone decoder \$1.95
  - 709 Op amp 40¢
  - 741 comp. op amp 39¢
  - 2102 1024 bit RAM \$4.95
  - 8038 volt cont osc \$4.25

- ### CLOCK CHIPS WITH DATA
- MM5314 6 dig clock \$4.95
  - (MK50250) alarm \$4.95

- ### LED'S
- (H223) 10 Asst LEDs \$1.00
  - (H242) 5 Jumbo Green LEDs \$1.00
  - (H242) 5 Med Yellow LEDs \$1.00
  - (H001) 5 Jumbo Red LEDs \$1.00
  - (H011) 5 Med Red LEDs \$1.00
  - (H012) 5 Mini Red LEDs \$1.00
  - (H293) DL707 (equiv) 7 seg red LED, .3" char, comm anode \$1.00
  - (H007) DL747 7 seg red LED, .6" char, comm anode \$1.95
  - (H013) MAN 5 (equiv) 7 seg green LED, .27 char, comm anode \$1.49
  - (H014) MAN 8 (equiv) 7 seg yellow LED, .27 char, comm anode \$1.49

- ### IC BREADBOARDS & TERMINALS
- Boards have .042 holes. Made of 1/16" polyester glass.
- (HB663) 3"x4" 94¢
  - (HB664) 3"x6" \$1.29
  - (HB665) 4"x6" \$1.65
  - (FB666) 4"x8" \$2.12
- Push-in terminals
- (HP6601-20) pkg 20/90¢
  - (HB6601-100) pkg 100/\$2.89
- Push-in flanged pins
- (HB6602-20) pkg 20/90¢
  - (HB6602-100) pkg 100/\$2.89
- Push-in flea clips
- (HB6603-20) pkg 20/90¢
  - (FB6603-100) pkg 100/\$2.89

**EDLIE ELECTRONICS, INC., 2700-H HEMPSTEAD TPKE., LEVITTOWN, N.Y. 11756**

# FREE EICO CATALOG

## 346 Ways To Save On Instruments, Burglar Alarms, Automotive & Hobby Electronics!

The more you know about electronics, the more you'll appreciate EICO. We have a wide range of products for you to choose from, each designed to provide you with the most pleasure and quality performance for your money. The fact that more than 3 million EICO products are in use attests to their quality and performance.

**"Build-it-Yourself" and save up to 50% with our famous electronic kits.**

For latest EICO Catalog on Test Instruments, Automotive and Hobby Electronics, Eicocraft Project kits, Burglar-Fire Alarm Systems and name of nearest EICO Distributor, check reader service card or send 50¢ for fast first class mail service.

**EICO—283 Malta Street,  
Brooklyn, N.Y. 11207**

*Leadership in creative electronics  
since 1945.*



Circle 65 on reader service card

NOVEMBER 1975

99


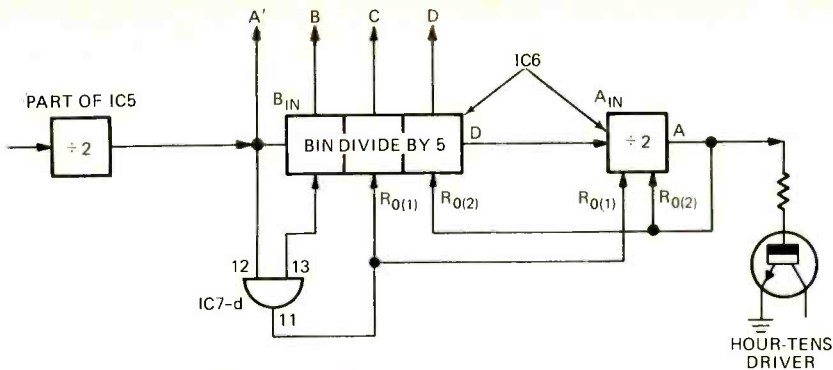


FIG. 4—HOUR COUNTER from TTL clock circuit.

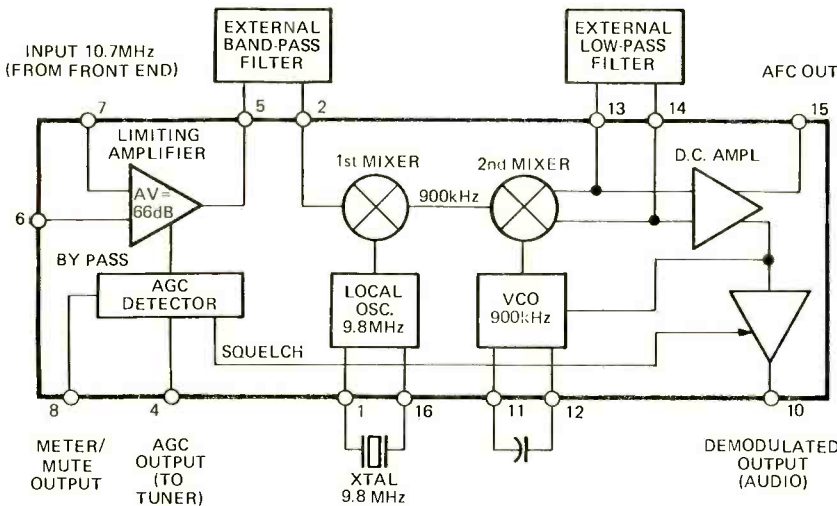

INPUT FREQUENCY TO 2nd MIXER  
IS 10.7MHz-9.8MHz = 900kHz

FIG. 5—SIGNETICS' NE563 IC contains 1/3 of an FM stereo receiver.

shortened to 10. No external gating is used because the states of only two stages have to be sensed, and the internal reset-gate on the 7493 IC can handle it. The minute-units digit cycles from 0 through 9 and the A, B, C, D binary coded decimal outputs drive an output decoder.

The minute-tens digit must count from 0 through 5 for 00 through 59 minutes. A divide-by-six counter is necessary. The 7492 is a divide-by-twelve partitioned into a divide-by-two stage and a three stage divide-by-six. The divide-by-six counter stages A, B, and C are used for the minute-tens digit display. The D output is a symmetrical divide-by-twelve that is used by the hour counter. The A, B, and C outputs of IC5 are decoded by IC9. The D input to the decoder is grounded since a count of eight is never reached.

The divide-by-twelve counter is comprised of the last section of IC5, IC6 and IC7-d. Figure 4 shows this arrangement more clearly. The SN7490 (IC6) is a decade counter broken into a divide-by-two stage and a divide-by-five counter. The A, B, C and D outputs sequence through the first 10 hours in a normal binary manner. At 10 o'clock, the A output switches to a 1 turning on the hour-tens digit. In addition, the A output also applies a 1 to the R<sub>02</sub> reset

input. The counter waits for a high output from pin 11 of IC7-d for resetting. Three counts later, at thirteen, the A and B outputs are high and the reset occurs putting the four stages of the 7490 counter at 0. Resetting is very quick, only hindered by the short propagation times through the circuits and the momentary state of 13 is never actually seen on the display.

A wide variety of BCD decoders are available; the choice hinges on the voltage and current demands of the specific indicator that is to be used and its display format.

The SN7441A, 7442, and 7445 are all BCD-to-Decimal decoders. Cold-cathode indicator tubes can be interfaced directly with the SN7441A. If segment displays such as LED's are used, one of the SN7446, SN7447, SN7448, SN7449 BCD-to-Seven-Segment decoders should be used.

For information on a mounting board with silkscreened power supply and readout circuits for this clock circuit write: Bagnall Electronics, 179 May Street, Fairfield, CT 06430. Bagnall proposes a wire wrap method of assembly that does not use soldering or printed circuit boards. Wires are run from pin-to-pin using a specially designed tool.

(continued on page 112)

# IMPROVE ANY BRAND TEST RIG

SERVICE SOLID STATE

ON ANY TEST RIG

with the PLUG IN TRANSVERTER NO WIRING




TeleMatic

ADD-A METER TO YOUR RIG

HVM - 3900

\$33<sup>00</sup>

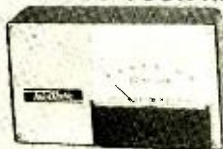

- MONITORS ANODE VOLTS
- CONVENIENT MOUNTING
- SIMPLE INSTALLATION

TeleMatic

ADD-A FOCUS SUPPLY

SERVICES THE NEW LOW FOCUS VOLTAGE TV's.



FVS - 3950

\$22<sup>95</sup>

- ADJUSTABLE
- SAFETY LIGHT
- E-Z HOOK-UP

TeleMatic

ADAPTORS YOKE-CONVERGENCE ADAPTOR

FOR ALL BRANDS TV.

FREE



TeleMatic  
2862 Fulton Street  
Brooklyn, N.Y. 11207

Name \_\_\_\_\_

Street \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

My Supplier is:

SOLD THROUGH DISTRIBUTORS ONLY

Circle 66 on reader service card

## MUSIC SYNTHESIZER

(continued from page 39)

The configuration of the integrator is such that the amplifier will work to make identical currents flow into its inverting (IC1-a pin 3) and non-inverting (IC1-a pin 2) inputs. Because of the values of resistors R14, R15 and R80, the current into the non-inverting input will always be at least twice the current into the inverting input except when transistor Q7 is turned on. To make up for this difference in current, the output voltage of the amplifier rises linearly to force current through capacitor C6 into the inverting input. At some point, the integrator output voltage exceeds the threshold established by the Schmitt trigger causing the collector voltage of Q4 to switch from essentially +18 volts to approximately +3 volts. Under these conditions, the base-emitter junction of Q6 is forward biased causing the collector of this transistor to rise to approximately +9 volts. The resulting current flow through R25 into the base of Q7 turns this transistor on. This in turn effectively shunts the current that was previously flowing into the non-inverting input of the integrator to ground. The integrator's amplifier now tries to make up for the surplus current flow into the inverting input by linearly decreasing its output voltage to pull current out of this input through C6. When the amplifier's output voltage falls below the threshold level, the Schmitt trigger resets. The collector voltage of Q4 goes high again and turns off Q6 and Q7 and restores the current flow into the integrator's non-inverting input so that the cycle can start over.

The cycle is identical when the SKEW control is rotated toward the RAMP position except that the decreased resistance in the non-inverting input circuit allows a greater current flow. This causes the integrator's output ramp to rise more quickly. Simultaneously, the decreased resistance in the non-inverting input circuit is added to the inverting input to cause the integrator's output to fall more slowly. The combination of increasing rise-time while decreasing fall-time keeps the total period of the waveform approximately constant.

The ramping output of the integrator is applied to resistor R17 and potentiometer R81. The setting of potentiometer R81 determines the level of the triangle/ramp waveform that is applied to the audio bus. Similarly, potentiometer R82 is in the collector circuit of transistor Q6 and this control adjusts the level of the square wave applied to the audio bus.

### VCF

The voltage-controlled filter is a common design built around one amplifier section of the LM-3900 and is tuned by varying the effective resistance of field-effect transistor Q8. The schematic diagram of the VCF is shown in Fig. 4.

The three signals applied to the audio bus are mixed together by resistors R34, R35 and R36 and applied to the input of the filter through resistor R27. Switch S8 allows either the filtered or the unfiltered audio bus signal to be applied to the VCA

(Voltage-Controlled Amplifier).

The control voltage for the filter can originate at either the control strip or the filter's dedicated function generator. Voltages from the control strip appear across resistor R49 and are applied to the gate of FET Q8 through R47 while voltages from the function generator are applied through R46.

The function generator comprises one section of the LM-3900. Trigger voltages that appear at R38 produce a current flow into the amplifier's non-inverting input that switches the output of the amplifier to a high level. This high output voltage charges the timing capacitor C12 through R40, the ATTACK control R85 and the forward biased diode D4. The voltage across C12 is sensed by the high-impedance emitter-follower Q9 with the voltage at the emitter of this transistor being a diode drop less than the voltage across the capacitor.

Once the amplifier is turned on by the trigger signal, it is held on by feedback current through R39 even if the trigger is removed. As long as the voltage at the emitter of Q9 is low, Q11 is off and there is no current flow through R45 into the inverting input of the amplifier. As soon as the voltage at the emitter of Q9 exceeds two diode-drops (D11 and the base-emitter junction of Q11) above the +9-volt reference at the base of Q11, this transistor starts to conduct causing current to flow through R45 into the inverting input of the amplifier. If the triggering signal has been removed by this time, the amplifier's output resets to a low voltage causing the charge on C12 to drain off through R41, the DECAY control R86 and diode D5 which is forward biased under these conditions. If the triggering signal is still present, it provides enough current into the amplifier's non-inverting input to hold the output high for a sustained interval.

Slide switch S5 provides for either sustained or non-sustained outputs from the function generator by allowing either a direct or capacitively coupled input for the trigger signal. Slide switch S4 provides for a repeat function by allowing the trigger signal from the trigger pushbutton to be replaced by the collector voltage of Q10. Transistor Q10 is a simple inverter stage that changes to a high output voltage when the output of the function generator approaches its lowest level.

Diode D6 provides a discharge path from capacitor C12 back into the triggering network when a "mute" function is desired from the function generator (SUSTAIN OFF, REPEAT ON).

### VCA

The schematic diagram of the voltage-controlled amplifier is shown in Fig. 5. With the deletion of the components that provide for repeat, the operation of the function generator associated with the VCA is identical to that of the VCF's function generator.

The VCA is a common design employing a differential pair (Q12 and Q13) sharing a common constant current sink in their emitter circuits. Since the gain of a transistor is proportional to its collector current, more current flow through the current sink (Q14) increases the gain of the transistors in the differential stage.



In more expensive VCA's, the differential outputs form the collectors of Q12 and Q13 would be applied to the inverting and non-inverting inputs of an operational amplifier so that the DC voltage level changes associated with increasing and decreasing the gain of the pair would be rejected as a common-mode voltage. In this circuit, the DC voltage changes are cancelled out in R59 and R60 and this is based on the fact that as the voltage at the collector of Q12 drops with increased gain, the voltage at the emitter of Q14 rises by a proportional amount because of current flow through R58. The ratio of R59 to R60 cancels the DC level changes while acting only as an attenuator on the audio signal present at the collector of Q12.

Emitter follower Q15 provides a high input-impedance to the output of the VCA while presenting a desirable low output-impedance to drive the power amplifier being used with the GNOME.

The last two parts of this article will cover the construction details including the foil patterns and component placement diagrams. Also, testing and calibration, and operating procedures will be given.

A short tutorial on synthesizers will also be presented to help the readers understand the principles behind synthesizers.

**You'll never know  
how much good  
you can do  
until you do it.**

You can help people.

In fact, there's a crying need for you. Your talents. Your training. Your concerns. They can make you priceless as a volunteer in your community.

There are probably several local organizations hard at work doing things you'd be proud to be part of. We'll put you in touch with them. Join one. Or, if you see the need, start a new one.

If you can spare even a few hours a week, call the Voluntary Action Center in your town. Or write: "Volunteer," Washington, D.C. 20013.

It'll do you good to see how much good you can do.

**Volunteer.**

The National Center for Voluntary Action

A Public Service of This Magazine & The Advertising Council



# ISO TIP® QUICK CHARGE

Recharges in 1/3rd the time of any other cordless iron.

Complete line of accessories available:



No. 7566  
Micro Soldering Tip



No. 7535  
Regular Tip



No. 7546  
Heavy Duty Tip



No. 7596  
Knife Tip



No. 7545  
Fine Tip



No. 7577  
Chisel Tip



No. 7574  
Concave Tip



No. 7569  
"V" Tip



No. 7573  
Tinning Tip



No. 7572  
Blunt Tip

No. 7556

Tuner  
Extension Tip



**WAHL CLIPPER CORPORATION**

ORIGINATORS OF PRACTICAL CORDLESS SOLDERING

Sterling, Illinois 61081 (815) 625-6525

"Manufacturing Excellence Since 1919"

Circle 67 on reader service card

## Now...the most enjoyable do-it-yourself project of your life—a Schober Electronic Organ!


You'll never reap greater reward, more fun and proud accomplishment, more benefit for the whole family, than by assembling your own Schober Electronic Organ.

You need no knowledge of electronics, woodwork or music. Schober's complete kits and crystal-clear instructions show you — whoever you are, whatever your skill (or lack of it) — how to turn the hundreds of quality parts into one of the world's most beautiful, most musical organs, worth up to twice the cost of the kit.

Five superb models with kit prices from \$575 to around \$2,300, each an authentic musical instrument actually superior to most you see in stores, easy for any musically minded adult to learn to play, yet completely satisfying for the accomplished professional. And there are accessories you can add any time after your organ is finished — lifelike big auditorium reverberation, automatic rhythm, presets, chimes, and more.

Join the thousands of Schober Organ builders-owners who live in every state of the Union. Often starting without technical or music skills, they have the time of their lives — first assembling, then learning to play the modern King of Instruments through our superlative instructions and playing courses.

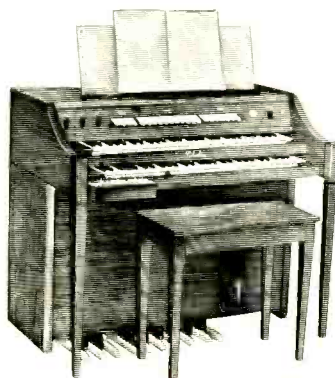Get the full story FREE by mailing the coupon TODAY for the big Schober color catalog, with all the fascinating details!



The Schober Organ Corp., Dept. RE-144  
43 West 61st Street, New York, N. Y. 10023

Please send me Schober Organ Catalog.  
 Enclosed please find \$1.00 for 12-inch L.P. record of Schober Organ music.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_

STATE \_\_\_\_\_

ZIP \_\_\_\_\_

Circle 68 on reader service card

NOVEMBER 1975

101

# Build this set...



# And build your career in electronics at the same time.

You build and keep a *future* when you learn electronics the ETI way.

“Building” is a key word through all the 16 ETI electronics courses and programs. Whether your goal is to get into TV repair and service, get your FCC license, move into computers,



advance in your present job through learning solid-state technology, or become an electronics draftsman... you build your tomorrow. You build a lot more than TV sets.

You build a solid future in the field where—despite all recent changes in the economy—the action has to come.

You build that future on a foundation of learning that is useful... practical... step-by-step... hands-on.

You build it from the beginning by a special, simplified, building-block teaching system called *Autotext*, exclusive with Electronics Technical Institute, that makes learning fun. You keep building, combining hands-mind-equipment in the most practical way, so you can “talk shop” or present an idea *effectively*, but you can also *do the job*. You’ve learned by doing, and you gain all the confidence that comes with it.


You build with the concerned personal help of a licensed instructor who knows the subject and wants to know *you*. You build with the reputation of the school that began as the Marconi Institute back in 1909.

In many phases of building your technical know-how, you use specially developed Project Kits that move in a logical sequence, hands-on, from the first step through completion of basic units. There is no surer way to build solid electronics knowledge *and* your own confidence in what you can do.

And it’s simple to check it all out right now, with no obligation—and no salesman will call. All it takes to get the colorful new 44-page ETI Career Book is a card or coupon. If you like electronics, you’ll enjoy reading about it. You owe it to yourself to get the facts.

The Career Book itself may be worth real money to you, as you make plans for your future and consider the many opportunities open to you through 16 different courses and programs in electronics.

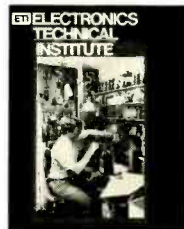To build a future in electronics, the first step is to send for your free ETI Career Book today!



## Electronics Technical Institute

Division of Technical Home Study Schools

Electronics Technical Institute, Dept. 2-479-115  
Little Falls, New Jersey 07424

Send me the Electronics Technical Institute Career Book.

Tell me how I can get ahead in Electronics through ETI. I've checked the fields of special interest to me.

- |   |   |                                    |   |
|---|---|------------------------------------|---|
| <input type="checkbox"/> TV/Audio Servicing | <input type="checkbox"/> Communications | <input type="checkbox"/> Computers | <input type="checkbox"/> Business and Engineering |
| Black and White                             | FCC License                             | Digital Electronics                | Electronics Fundamentals                          |
| Color                                       | Aircraft                                | Computer Technology                | Electronics Drafting                              |
| Solid-State                                 | Marine                                  | Computer Programming               | Industrial Electronics                            |
| CATV  | Mobile Two-Way                          |                                    | Advanced Electronics                              |
| Closed Circuit                              | Microwave                               |                                    | Industrial Instrumentation                        |
| Video Recorders                             |   |                                    | Electronics Technology                            |
| Radio                                       |   |                                    | Medical Electronics                               |
| Hi-Fi Stereo                                |   |                                    |   |

Check here for Veterans information.

Name \_\_\_\_\_ (please print)

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

NOVEMBER 1975

# Particular? try this high-performance circuit-builder's Super-strip™

840  
solderless  
plug-in  
tie-points

holds  
up to 9  
14-pin  
DIP's

Size  
2.25"  
x 6.5"

fastest, most reliable  
method known...to build, test  
and modify experimental circuits

8-bus distribution system  
plus universal .1" by .1" matrix  
of solderless, plug-in tie points  
all in one integral device.

Accepts all DIP's and discretes  
with leads up to .032" dia.

Interconnect with any solid wire  
up to No. 20 A.W.G.

ORDER BY PART NUMBER  
923252 (nickel-silver terminals)..... \$17.00  
923748 (gold-plated terminals)..... \$18.90

We honor M.C. and B.A.C. charges.  
Add sales tax on OH and CA orders.  
(F.O.B. Painesville on company P.O.'s.)  
Dealer inquiries invited

High-performance A P Super-Strip component matrices consist of 128 terminals of 5 tie points each. The 8 buses of 5 connected 5-tie-point terminals are for voltage, ground, reset and clock lines, shift command, etc. New, non-shorting, instant-mount backing and quick-removal screws are supplied... use several Super-Strips to create large-scale breadboards on panels up to 1/8" thick.

Add → fees from this chart.	SHIPPING/HANDLING C.O.D.	
	Up to \$10.00	\$1.00 \$ .70
	\$10.01 to \$25.00	1.50 .80
	25.01 to 50.00	2.00 .90



All products guaranteed to meet or exceed published specifications

**A P PRODUCTS INCORPORATED**  
Box 110-R • Painesville, OH 44077 • 216/354-2101

Circle 69 on reader service card

# SERVICE

## LIGHT GREEN RASTER ON WARMUP

This RCA CTC-24 shows a light green raster on warm up, for 10 minutes (almost exactly), then wham, good picture. All tubes tested and wiggled in sockets. Where to look? —E.G., N. Bellmore, NY.

Could be something intermittent in one of the color-difference amplifier stages. Most likely cause, the G-Y amplifier, with a small thermal leakage or something. Check its plate load resistor connections for solder joint trouble, too.

(Field Feedback; the crystal ball was right on frequency today. It was the 6GH8 tube in the G-Y amp. Even a blind pig gets an acorn once in a while.)

## QUESTIONS AND ANSWERS

- Q. Will a 19DVP4 picture tube work in place of a 19ECP4 picture tube?  
A. Should; base the same, etc.
- Q. Doesn't work! Why?  
A. Still ought to! Recheck.
- Q. Woops! It will work if you put the picture tube socket on right instead of turning it halfway around! (Thanks to W. J., San Diego, CA.)

## A NEW CAUSE FOR JAIL-BARS!

The original complaint in this Admiral G13 chassis was bars (similar to Jail-Bars) on the left side of the screen. We suggested the stock tests such as blanking diodes, "diodehausen radiation," etc. Later, the reader wrote again. They found that pulling any of the IF tubes would kill the bars, though shorting the IF input to ground had no effect. Blanking diodes were checked, and putting an ion-trap magnet on the horizontal output tube didn't help the situation either.

Finally, they looked into the high-voltage cage and noticed "some sort of leakage into the focus rectifier, coming from a very small crack in the cap of the high-voltage rectifier tube"! Replacing this cap cleared up the problem. Thanks to Albert M. Dryer of the Division of Engineering, and David L. Smith, 2d year Electronics Technician Student, at Lord Fairfax Community College, Winchester, VA, for the feedback and a new cause for jail-bars!

## EXCESSIVE BRIGHTNESS


I can't control the brightness on this Admiral 4H12. Too high at all times. The DC voltages seem to be OK, but the 6AF9 (video output) plate voltage is only 180 volts. Normal is 216 volts. Can you tell me where to look for the trouble?—J.V., Scottsdale, AZ.

Right where you are. The video output plate voltage is the picture tube cathode voltage. Since this is "too far negative," your picture tube bias is too far toward conduction. This could well be due to incorrect bias on the 6AF9, if the plate load resistors, etc. are all good.

Check the DC voltages on the brightness control. You have a positive voltage fed from the three background controls; this is balanced by a negative voltage developed by a flyback pulse on a diode rectifier. If this diode is bad, the voltage here would be too far positive.
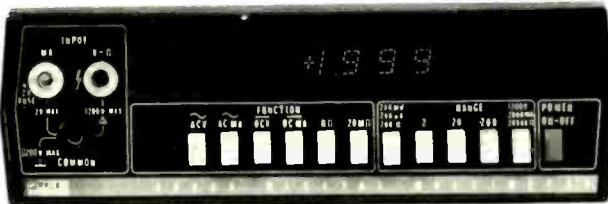
## ONE-COLOR SCREEN PROBLEMS

When this Sylvania D-12 was first turned on, the screen was all green. After a warmup, it would work. Then, it started showing all red. Stays until switch is turned on and off sev-



## Think of it as the best tester in your bag. Only \$299

Now you can get a high performance Model 8000A Digital V.O.M. from Fluke, America's foremost maker of quality digital multimeters, especially designed for TV, radio, stereo and audio service. No other digital V.O.M. gives you the resistance range to check breakers and switches, the high resolution voltage to look at emitter base and other transistor voltages, excellent ac accuracy and full accuracy with a 30 second warm-up.

Measures in 26 ranges 100  $\mu$ V to 1200 V, 0.1  $\mu$ A to 2A, and 100 milli $\Omega$  to 20 meg $\Omega$  with a basic dc accuracy of 0.1%. Full year guarantee. Low cost options include rechargeable battery pack, printer output, deluxe test leads, HV, RF & 600-amp ac current probes, carrying case, and rack mount. There's new high voltage protection on all ac/dc voltage ranges. The instrument will take transients up to 6 KV, 10  $\mu$ seconds wide over a duty cycle of 60 per second.



John Fluke Mfg. Co., Inc.  
P.O. Box 43210  
Mountlake Terrace, WA 98043

Get all the details from your nearest Fluke sales office. Dial toll-free 800-426-0361 for address of office nearest you.

Circle 70 on reader service card



# NOTES

eral times. Have you seen a freak like this?—H.S., Milwaukee, WI.

Yep. There are a couple of things that can do this. One is an intermittent heater-cathode short in one gun. However, this can be caught by a picture tube test, and it isn't likely that you'd have two. (Possible of course, but unlikely.)

Here's the other. Replace the 6MD8 (color-difference amplifier triple-triode) tube. If this doesn't work, then check the tube-socket (same tube) very carefully. I have seen this type of symptom in cases where one of the plate pins of this tube wasn't making contact with the tube-socket, or where there was a "pocket-joint" between the tube socket terminal and the board. (Cold solder joint which looks good from outside!) Plate voltage goes up, and tube flares up.

## AUTOMATIC NOISE ELIMINATOR ON AM/FM?

*I want to build the Automatic Noise Eliminator (R-E, May 1974). My problem is that my radio is an AM/FM stereo. Should I use two lamps, or one lamp and two photocells?—P.S., Troy, MI.*

Your receiver has two complete audio circuits with one section of the volume control in each channel. The lamp in the emitter circuit of Q4 in the noise eliminator will have to excite two photocells—one in each channel. You'll have to pick up electrical audio signals from both channels so you'll need a second audio transformer in series with the secondary of T1.

## VIDEO DETECTORS BLOW

*I had a very bad picture on this Packard-Bell 23T7. Found that the video detector had very low back-resistance, and replaced it. Found a couple of resistors bad; still no picture. Checked the diode I'd just put in, and it was bad. Put in new Motorola diode. Fine picture.*

*For two days. Diode blew again. Replaced it with a different one. Two days and poof. I'm getting pretty good at replacing video detectors, but no closer to a solution. What the heck's going on?—E.P., Torrance, CA.*

I've seen this before, on other sets, including G-E's, Truetone's, etc. Frankly, I don't know the cause (though I made very exhaustive tests on some of them) but I can tell you the cure. Replace the diode with a special RCA type, No. 125844. This is a video detector diode with a very high voltage rating, somewhere around 200 volts. These will hold, or at least they have in all the sets I've put them in. R-E



Camp Fire is for everyone. It is an adventure in living — exciting, creative and fun.



INTERNATIONAL FM 2400CH

## FREQUENCY METER for testing mobile transmitters and receivers



- Tests Predetermined Frequencies 25 to 1000 MHz
- Extended Range Covers 950 MHz Band
- Pin Diode Attenuator for Full Range Coverage as Signal Generator
- Measures FM Deviation

The FM-2400CH provides an accurate frequency standard for testing and adjustment of mobile transmitters and receivers at predetermined frequencies.


The FM-2400CH with its extended range covers 25 to 1000 MHz. The frequencies can be those of the radio frequency channels of operation and/or the intermediate frequencies of the receiver between 5 MHz and 40 MHz.

Frequency Stability:  $\pm .0005\%$  from  $+50^\circ$  to  $+104^\circ\text{F}$ .

Frequency stability with built-in thermometer and temperature corrected charts:  $\pm .00025\%$  from  $+25^\circ$  to  $+125^\circ$  (.000125% special 450 MHz crystals available).

Self-contained in small portable case. Complete solid state circuitry. Rechargeable batteries.

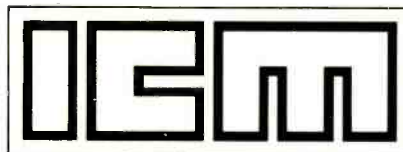FM-2400CH (meter only) ..... \$595.00  
 RF crystals (with temperature correction) ... 24.00 ea.  
 RF crystals (less temperature correction) .... 18.00 ea.  
 IF crystals ..... catalog price



International Crystal Manufacturing Company, Inc.


10 North Lee, Oklahoma City, Oklahoma 73102

Circle 71 on reader service card

# MINI-BAR<sup>®</sup> color generator

# NESDA

\$89.50

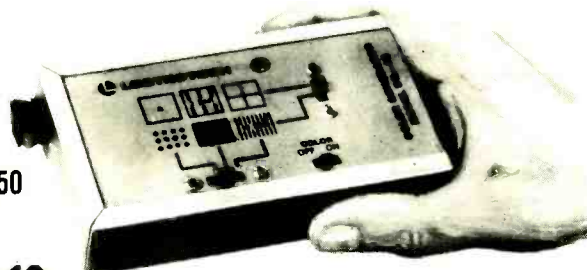

## BG-10 battery-operated, fits in shirt pocket!

No AC plug in . . . automatic on & off with LED indicator . . . fast, easy hook-up with coaxial cable . . . all essential patterns . . . • Low power consumption for extended battery life (Uses inexpensive 9 volt batteries) • Shuts off when not in use • Enclosed RF cable compartment • Size: 5 1/2" x 3" x 1 1/8". Only 12 ounces • TV station type sync signals • CMOS LSI IC for all counting functions . . . no internal adjustments • RF output on Ch. 3, 4 or 5.

BG-10 (less battery) ..... \$89.50  
CC-1 Carrying Pouch ..... \$ 2.95



See your distributor or write

### LECTROTECH, INC.

5810 N. Western Ave.,  
Chicago, Illinois 60659  
(312) 769-6262

Circle 72 on reader service card



### RELAXING! REFRESHING!

TAKE A BREAK FROM TODAY'S PRESSURES -  
Browse with us through the old days of  
wireless, radio and early TV.

Young or old, you'll be fascinated by our two great books VINTAGE RADIO (1887-1929) and A FLICK OF THE SWITCH (1930-1950). Just relax and wander through thousands of pictures, many old ads and interesting stories of early radio. You don't have to be an expert to revel in these fine books.

Next, browse through our authentic reproduction of Gernsback's 1927 RADIO ENCYCLOPEDIA to meet the heroes (Who's Marconi?) and see the hardware (what's a coherer?) of early days.

Our RADIO COLLECTOR'S GUIDE will make you an "instant expert" as you go prospecting for those fine old collectible radios. Then you'll need Morris Beitman's 1926-1938 RADIO DIAGRAMS book to restore them. Also, we'll send you the diagram for any pre-1951 set for \$3.50.

NEW GIFT IDEA! BEAUTIFUL COLOR PRINTS from original artwork of the famous Progress in Electronics stamp set. Four different 8" x 10" prints with colorful matte backgrounds.

SEND TODAY to Vintage Radio, Dep't R, Box 2045, Palos Verdes, CA. 90274. Postage Paid. California residents add 6% tax.

- VINTAGE RADIO; \$7.95 hard-cover, \$5.95 handbook
- A FLICK OF THE SWITCH; \$9.95 hard-cover, \$6.95 handbook
- 1927 RADIO ENCYCLOPEDIA; \$12.95 hard, \$9.95 hndbk
- RADIO COLLECTOR'S GUIDE; \$4.45 handbook
- 1926-1938 RADIO DIAGRAMS; \$7.00 handbook
- COLOR PRINTS, Set of four; \$7.50 prints, \$18.50 Plaques
- Diagram for \_\_\_\_\_ radio @ \$3.50

TOTAL \_\_\_\_\_

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ St. \_\_\_\_\_ Zip \_\_\_\_\_

TREAT YOURSELF TO A HOLIDAY GIFT -  
**1254 PAGES OF PLEASURE!**



THIS PAST SUMMER, THE NATIONAL ELECTRONIC SERVICE Dealers Association (NESDA) held its annual convention. Members of the **Radio-Electronics** staff attended and participated in the convention activities (see publisher's memo, page 6 this issue). The convention was held in Winston-Salem, NC and here is a photographic report.



NESDA'S EXECUTIVE COMMITTEE got down to business early during the convention. Here is the scene at that meeting as Mike Horewitch, NESDA's new insurance agent, explained the new casualty and health program for the membership.



THE GIANT TRADE SHOW, the NESDA Electronic Circus was a big success. Here are the Quasar and O. W. Donald Co. booths. Traffic was heavy all day long.



AWARDS CHAIRMAN JACK KELLEY, CET (left), Sage & Sand TV, Litchfield Park, AR presents the runner-up award for the "Technician of the Year" award presented by ISCET to Clarence Saatkamp, CET; Saatkamp's TV, Milwaukee, WI. To the right of the podium is Gene Jadwin, Host of this breakfast and George Camp.

# Convention News



SERVICEABILITY INSPECTIONS were conducted at the convention by ISCET personnel. Seen here is Carl Saffer, CET, Louisville, KY closely examining features of one of the sets checked.



RADIO-ELECTRONICS' EDITOR, Larry Steckler, CET, won the NESDA "Man Of The Year" award. Here Larry (center) receives the award from O. W. Donald of Fort Smith (at podium). O. W. Donald is the sponsor of this award. Seated on the right are Toby Mack, Staff Vice President, Distributor Products Division, EIA, the NESDA Awards Banquet Speaker and M. F. Finneburgh, Sr., EHF (far right). At the left is Dick Glass, CET the MC.



OUTSTANDING NESDA COMMITTEE CHAIRMAN award plaque went to Jerry Hall, NESDA's membership chairman. Accepting for Jerry is Frank Schroeder (standing right) of the Wisconsin affiliate. Jack Kelly (standing left) made the presentation. (turn page)

## If You Work In Electronics:


# GRANTHAM OFFERS YOU College-Level Training and a college degree.

Electronic Circuit Design, Engineering Analysis (including mathematics thru calculus), Classical and Solid-State Physics, Engineering Design, etc., etc., are all part of the Grantham home-study degree program in Electronics Engineering.
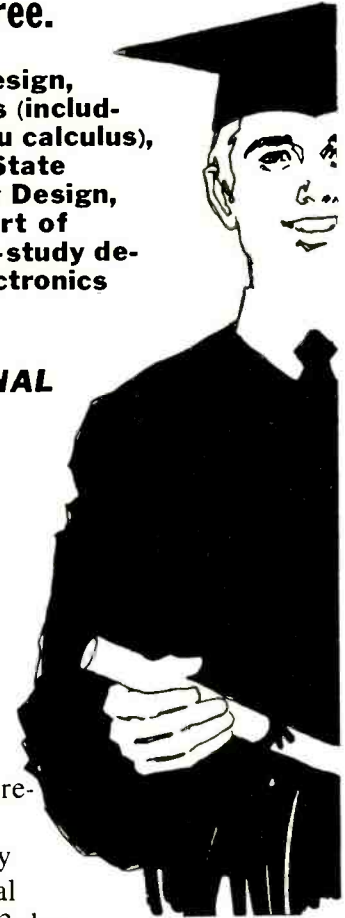
### PUT PROFESSIONAL RECOGNITION IN YOUR CAREER.

By adding college-level home training and a college degree to your experience, you can *move up* to greater opportunities in electronics.

Grantham offers the A.S.E.T. degree by correspondence. After earning this degree, you may continue with additional correspondence plus a 3-day residential seminar and certain transfer credits, to earn the B.S.E.T. degree. Then, the B.S.E.E. is available through further study.



## GRANTHAM SCHOOL OF ENGINEERING

2000 Stoner Ave., Los Angeles CA 90025

● Telephone (213) 477-1901 ●

Worldwide Career Training thru Home Study

Mail the coupon below for free bulletin.

**Grantham School of Engineering** RE 11-75

2000 Stoner Ave., Los Angeles, CA 90025

I have been in electronics for \_\_\_\_\_ years. Please mail me your free bulletin which gives details concerning your electronics degree programs.

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Circle 73 on reader service card

**ONE MARK AHEAD OF THE REST....**



ADR Audio, one mark ahead of its competitors with the lowest prices of Famous Brand audio components, has now added complete CB & Video depts. All orders promptly shipped from the ADR warehouse in factory sealed cartons, fully warranted, fully insured. Send for our special price quote & newest money saving catalogue. Its your move...

**FOR IMMEDIATE QUOTE  
CALL (202) 723-6060**

**A.D.R. AUDIO**  
6200 CHILLUM PLACE N.W.  
WASHINGTON, D.C. 20011

Circle 74 on reader service card

**1 out of 2 who have it don't know it...**

**Do you?**

21 million Americans have high blood pressure. But 50 percent of those who have it, don't know it.

When blood pressure goes higher than it should, and stays high, it sets the stage for heart attack or stroke.

Most cases of high blood pressure can be controlled with drugs and other advances in treatment. That's why you should see your doctor regularly. Only he can tell if you need help.

A public service message from your Heart Association



Contributed by the Publisher



**SPECIAL RECOGNITION AWARD CERTIFICATES** were presented to many individuals and companies. Here is a look at the recipients as they received their certificates at the NESDA Awards Banquet in Winston-Salem. These certificates are presented in recognition of those who made special contributions to the service industry during the past year.




**AT THE SPECIAL FTC SEMINAR**, Gerry McCann, CET; president of ETA of Louisiana, answers some questions raised by the talk from FTC spokesman John Phelan (seated on the right). Miles Sterling, CET; Electro TV, Garder Grove, CA (seated on the left) chaired the seminar.



**A PROFITABLE SERVICE-MANAGEMENT SCHOOL** was held during the convention that had over 150 attendees. They heard top business leaders show how they make a success of the service business. At the podium is Jesse Leach, CET, owner of Lee's TV in Linthicum, MD., explaining how he takes two months vacation each year, even though he is a one-man shop owner. The Profitable Service Management School is only one of the many ways that NESDA strives to make its members more successful in their chosen profession. It is held in many different places during the year.

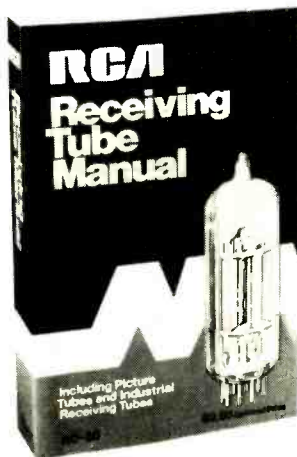**Brand new edition of an RCA best seller.**



One of the most widely-used manuals in the electronics industry, the RCA Receiving Tube Manual, is now available in a new, updated edition, especially designed for use by technicians, engineers, educators, students and electronic hobbyists.

With 754 pages of tube information, the new manual — RC-30 — includes chapters on basic principles of operation, electrical characteristics, and circuit applications. It also features terminal diagrams, picture tube characteristics chart, and an updated receiving tube replacement guide.

Ask your RCA distributor for a copy of the new RC-30 at only \$2.95 (suggested price). Or send your check or money order for \$2.95 (plus 50¢ for postage and handling per order) to: RCA Distributor and Special Products Division, P.O. Box 85, Runnemede, N.J. 08078.

**RCA** Distributor and Special Products Division





FOR RON CROW'S EFFORTS during the past year as Director of IS CET and the CET programs, he was presented a painting of his son and home. The award was made by Radio-Electronics Editor, Larry Steckler, CET; who was re-elected IS CET Chairman.

By any standards, the convention was a rousing success. It was marked by heavy attendance, enthusiastic manufacturer participation, important industry speakers (EIA and FTC) and an atmosphere of something getting done . . . something worth doing. Those who attended, came away with a feeling that solid progress was made on many fronts including professionalism of the technician, strengthening of the association, recognition by industry and a true co-operative effort to continue to enhance the status of the service technician in the United States. R-E

## How you live helps determine how long you live.

Nobody can promise you that regular exercise will guarantee you a longer life.

But it sure helps the odds.

Exercise is one of the good things you can do for yourself.

Check with your family doctor first. Then take your pick.

Row, ride, swim, ski, hike, bike, walk, dance, jog, smack a handball, swing a tennis racket.

Exercise is good for your weight, your lungs and the 600 muscles in your body including your most important one, your heart.

The President's Council on Physical Fitness and Sports.

**We want you to live longer.**



## Design Engineers rely on Data Precision DMM's. Now you can too. At Affordable Prices

Data Precision multimeters have been on the job and in the field with design engineers and technicians for a long time.

When reliable measurements are needed . . . they are proven performers.

### A Full Range, 5-Function, 4½ Digit Portable Multimeter.



**\$295.00**


Model 245 is the smallest, lightest, and most accurate 4½ digit portable DMM you can buy.

It's rugged. Dependable. Precise.

Model 245 measures DC and AC current, DC and AC volts, and resistance with .005% resolution and a basic accuracy of ±.05%.

It features a bright .33" display, autopolarity, auto-decimal positioning, rechargeable battery or line operation, fused probes, carrying case and one year warranty.
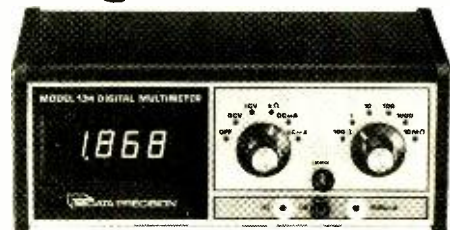
### A Full Range, 5-Function, 3½ Digit Multimeter.



**\$189.00**

Competitively priced to its analog equivalent, the Model 134 is 5 to 10 times more accurate and it is convenient, readable and free from operator error.

Model 134 measures DC volts, AC volts, DC current, AC current and resistance with a basic accuracy of ±0.2% through a total of 22 range scales.

It features auto-decimal positioning, autopolarity, 100% overranging, and a full ½ inch, bright, easy-to-read display, fused probes and one year warranty.

Contact Data Precision or the Data Precision representative nearest you. Data Precision Corporation Audubon Road Wakefield, MA 01880, Phone (617) 246-1600

**DATA PRECISION®**  
...years ahead

Circle 75 on reader service card

**\$5 REBATE**  
CERTIFICATES  
(see below)

**Polaris**  
**40 KV**  
DUAL RANGE  
**Probe**

MEASURES  
VOLTAGE  
AND  
CURRENT

FOR  
TODAY  
AND  
TOMORROW

MODEL  
#651

Only  
**\$29<sup>95</sup>**

**SPECIFICATIONS**

Range One:  
40,000 Volts D.C.  
Range Two: 0-400 MA.D.C.  
Accuracy:  $\pm 2\%$  Full Scale  
Meter Movement: 50 $\mu$ A

**Polaris**  
**DC POWER SUPPLY**  
0-25 VOLTS 250 MA

TEST & SERVICE  
SOLID STATE EQUIPMENT

MODEL  
TPS 225

Only  
**\$29<sup>95</sup>**




- Operates on 105/125 V.A.C.
- Adjustable Voltage Output
- Meter Measures Voltage & Current
- Extremely Low Ripple

**Polaris**  
**COBRA CURVE TRACER**

RAPID TRANSISTOR  
& DIODE TESTER

MODEL CT 751

Only  
**\$22<sup>95</sup>**

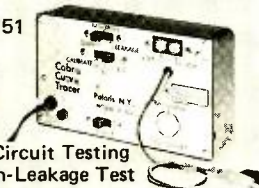

- In & Out of Circuit Testing
- Gain-Junction-Leakage Test
- In Circuit Test Leads
- Checks Diodes for Function & Polarity

**Polaris New York**

2862 Fulton St., Bklyn, N.Y. 11207

Please send me rebate certificates and information on  
Expires in 60 Days.

Probe  Power Supply  Curve Tracer

Name \_\_\_\_\_

Street \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

My supplier is \_\_\_\_\_

**SOLD THROUGH DISTRIBUTORS ONLY**

Circle 76 on reader service card

**STATE-OF-SOLID-STATE**

(continued from page 99)

**Signetic's FM microcircuit**

Just tacking on a phase-locked-loop to an old limiter design is not Signetic's way of doing things. The NE563 FM IC is new from the ground up. Things begin in an ordinary enough way in Fig. 5 by taking the 10.7 MHz tuner IF output and passing it through a 66-dB limiter.

Signal level sensing by an AGC detector generates control voltages that drives a signal-strength meter, regulates the gain of the tuner to prevent overloading, and squelch the receiver's audio output.

The signal leaves the chip for band limiting by an external ceramic filter and then reenters into the 1st mixer. This second conversion mixes down to 900 kHz by taking the 10.7 - 9.8 MHz difference component and sending it on the IC's second mixer.



SIGNETICS NE563

Crystals, ceramic resonators or LC tanks can tune the local oscillator. What remains on the chip are the three components that make up the PLL. The second mixer is the loop's phase detector. Frequency shifts to either side of the 900 kHz center frequency forces the VCO to track by a corresponding change in its control voltage. Where does the voltage change come from? What happens is the phase difference between the phase detector signal input and the VCO output slips just enough to generate the exact voltage needed. The external low-pass filter separates the DC component from the phase detector output.

During capture when the frequency of the VCO first attempts to match that of the input, the filter smooths the beat note between the two signals. Selection of filter parameters affects the pull-in range and time, and the noise bandwidth of the detector.

The PLL does not have an easily identified tuned circuit like a diode discriminator would. It is there though, and if the NE563 had used an LC tank instead of a capacitor tuned oscillator it would be more conspicuous. The initial tuning of the oscillator by whatever method, defines the equivalent center frequency and the low-pass filter restricts the bandwidth around center.

The recovered audio signal out of the NE563 is 500 mV RMS with 75 kHz deviation. Distortion with 1 kHz modulation frequency is .05% typical and the AM rejection is a respectable 70 dB.

In lots of 100, the NE563 sells for \$2.55.


**New releases**

From time to time I get letters asking about interfacing reader projects with different types of displays. National and Sprague have display driver guides that will be of interest to these readers.

National makes a series of common-cathode and common-anode, segment and digit drivers useful in clock and calculator readout circuits. They've published a single page LED Driver Selection Guide with 23 LED devices. Each IC is grouped according to its output type. The number of outputs and current capabilities are listed. For a copy write to the Marketing Service Department of the National Semiconductor Corp., 2900 Semiconductor Drive, Santa Clara, CA 95051.

The Sprague short form catalogue lists gas discharge and power display drivers. Fourteen devices interface between TTL, CMOS, or PMOS IC's and gas discharge displays as well as relays, solenoids, lamps and LED's. Ask for "Display/Interface and Transistor Arrays for the Digital Decade" from Sprague Electric Co., Technical Literature Service, 81 Marshall St., North Adams, MA 01247.

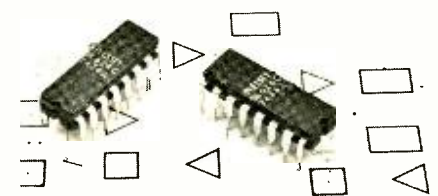Plessey Semiconductor's SL624 will demodulate AM, FM or SSB. The circuit works as a synchronous detector




PLESSEY SL624 AM, FM, SSB demodulator.

for AM, a quadrature detector for FM and as a product detector with its own oscillator for SSB. The SL624 is tailored for multi-detection mode receivers. Power supply requirements for the 16 pin ceramic DIP are 9 to 12 volts with 12 mA current drain at the highest voltage. Price is \$4.44 in quantities above 100.

**R-E**

# In/Out Of Circuit TRANSISTOR TESTER

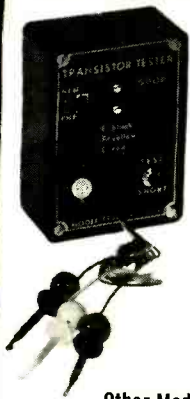

Model TT26AK\*

**\$995**  
pp.

Kit Form  
w/Alligator  
Clips

(Photo shown:  
#TT26EZ w/E-Z Hooks)

**Features:**

- Tests Transistors
- Checks Diodes
- Checks Continuity
- Gold-Plated Socket for Extra Reliability

**Other Models Available:**

Made in U.S.A.

#TT26EZ  
(Completely assembled  
w/E-Z Hooks) .....\$19.55 pp.

#TT26A  
(Completely assembled  
w/Alligator Clips) .....\$17.95 pp.

#TT26EZK\*  
(In Kit Form,  
w/E-Z Hooks) .....\$12.55 pp.

\*Kits assembled in less than 1 hour

All orders shipped within 48 hours.


Send check or money order. N.Y. residents add 8% tax. Write for full line of electronic accessories.

**TOKYO ELECTRONICS INC.**


1467 — 48th Street, Brooklyn, N.Y. 11219

Circle 77 on reader service card


## DIGITAL

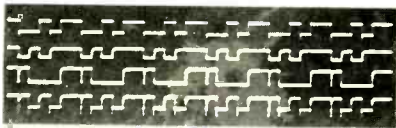

## ANALOG

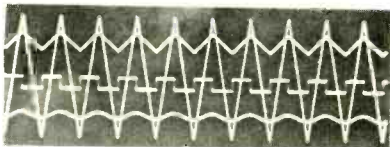

## YOUR SCOPE PLUS MODE 4

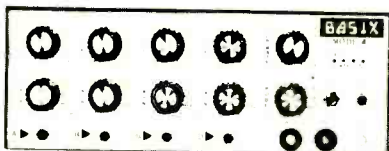

**INCREASE YOUR CAPABILITIES**

MODE 4 displays four .001 to 100 V p-p signals on any unmodified scope from DC to 10 MHz. Featuring individual channel gain (x .01 to x 100 in decade steps), serial and parallel multiplex modes, and the latest in linear and digital IC technology, MODE 4 affords you an indispensable working tool at a fraction of the single-channel scope price.

\$189 w/standard I/O; shielded I/O w/min. coax connectors \$10 more.

BASIX, 1067 Seneca Street, Bethlehem, Pa. 18015

Circle 78 on reader service card

## INDUSTRIAL TEST EQUIPMENT

(continued from page 42)

The solid-state cells can be of either type. A great many of them are photo-voltaic, generating a small DC voltage when illuminated. Here again we can use the millivolt ranges to check the output.

You'll also find LASCRA's (Light Activated SCR's) used for controls in some systems. Tests on these are slightly different, but look for the same basic reaction; a change in the output when the photo-sensitive surface is illuminated.

### AC leakage tests

Many of the "Consumer Safety" regulations deal with possible AC leakage from the line to the frame or case of a unit. This applies not only to appliances, but to industrial machines as well. For production-line testing, safety checking of machines after repair, and on general principles, every AC powered unit should be checked. The standard ANSI (American National Standards Institute) test for this limits the allowable leakage in appliances and other units, with either two-wire line cords or three-wire "safety" cords, to not more than 0.5-mA AC. For non-portable units with three-wire cords, third wire ground, the limit goes up but not much; only 0.75 mA.

There is a standard test for this. A 1500-ohm resistor, shunted by a 0.15- $\mu$ F capacitor, is connected from the frame of the appliance to a good earth ground. The AC ammeter is connected across this network. Several of the industrial VOM's seen before have this test built in; all you have to do is switch to AC LEAKAGE and hook it up. RCA also has a "dedicated" AC leakage tester, the model WT-540A, in Fig. 15. Dedicated means that this is a



### MODEL WT-540A LEAKAGE TESTER.

special leakage tester only. It will catch shorts and excessive leakage, for example in production line final tests.

### Let's wrap it up

Now you've seen some of the high quality modern test instruments that are available. These are *Ready, Rugged and Reliable*; the Three R's of test equipment. Since practically all jobs start with the use of a VOM, we covered these first. In the next article, we'll look at amplified VOM's; the FETVOM units. From there on, we will go into other specialized equipment, for testing any kind of unit used in Industrial Electronics.

R-E

# FREE!

## the 1976 Lafayette Electronics Catalog



The most comprehensive  
consumer electronics  
catalog available!

Features Lafayette and Criterion  
Products Plus Major Brands

Stereo/Quad Hi-Fi Components •  
Tape Equipment • Car Stereo • CB  
and Communications Gear • Police/  
Public Service Scanners • TV/FM &  
Communication Antennas • PA and  
Test Equipment • Tools • Electronic  
Calculators and Watches • Portable  
Radios • Security Systems • PLUS  
an exciting new Parts Line, Tubes,  
Batteries, Hardware and More!

- Stores Coast-to-Coast
- BankAmericard and  
Master Charge

# Lafayette

the electronics shopping center

Mail Coupon  
Today!

**FREE**

Dept. 17115

Lafayette Radio Electronics  
111 Jericho Turnpike  
Syosset, L.I., N.Y. 11791

Send me your FREE 1976 Catalog.

Name \_\_\_\_\_ Apt. \_\_\_\_\_

Street \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_

Zip

Send a 1976 Catalog to my friend.

Name \_\_\_\_\_ Apt. \_\_\_\_\_

Street \_\_\_\_\_


City \_\_\_\_\_ State \_\_\_\_\_

Zip

Circle 79 on reader service card

NOVEMBER 1975

**no  
strings  
attached**

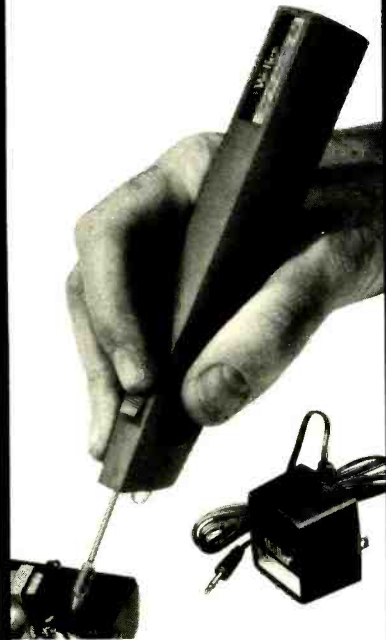

**NEW Weller<sup>®</sup>  
CORDLESS  
SOLDERING IRON...  
GOES ANYWHERE**

Weller's WC-100... the professional quality, feather-light cordless. Can be used anywhere. Without AC source.

Fingertip touch on exclusive sliding safety switch activates long-life, nickel-cadmium battery. Heats tip to over 700°F in 6 sec. Locks in "off" position to prevent accidental discharge in use or while restoring energy with fast-power recharger (UL listed).

Simple, instant change to any of 4 tips... for any job. Built-in light focuses on tip and work area.

It's display-card packaged, backed by strong national promotion, and ready to step up with your fastest moving lines. Request literature and prices.

**Weller-Xcelite  
Electronics Division**



**The Cooper Group**

P. O. BOX 728,  
APEX, NORTH CAROLINA 27502

Circle 80 on reader service card

# color TV kit teaches electronics

*It's a whole new concept in  
learn at home techniques. Build this  
color TV and learn electronics  
even if you build it wrong.*


IS WRONG EVER RIGHT? THAT'S A QUESTION that has been debated for ages. But in this new color TV kit, that you build as a part of a television servicing course, wrong is learning.

You see, if you build this set wrong, you find out about immediately and learn some important lessons about the kind of electronic circuits used in modern color TV sets at the same time. Here's how it all works.


When you build most kits, you don't

different. You build it in sections, (like most other kits) but when you complete a section you submit it to a series of experiments that show whether it is working or not and explain the circuit to you at the same time. In effect, each circuit becomes a laboratory in which you check for proper operation and then learn how that particular circuit works.

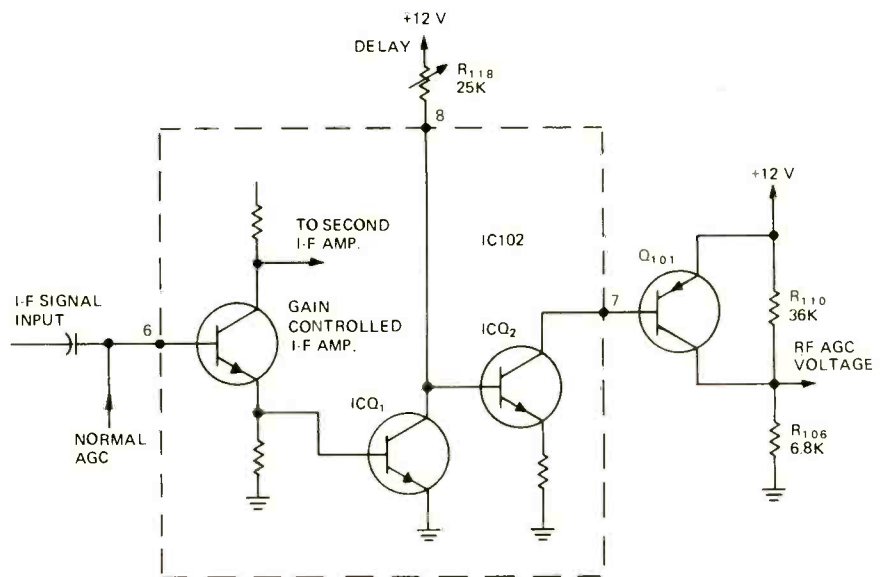First step in this kit is the power supply. There's nothing very special here.



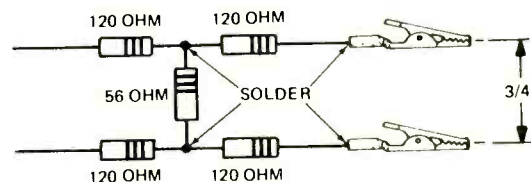**SIMPLIFIED SCHEMATIC** of the delayed AGC system as presented in the NRI training kit manual. An example of the way data is presented to students.



**THIS H-PAD** is built while performing experiments on the tuner of the color set. It's an important part of the experiment program.

ordinarily know whether it will work or not until the entire kit is completed and turned on. But the model 315 from the National Radio Institute is rather

You build it onto a circuit board that is part of the basic color TV chassis. The different part starts after you have com-  
*(continued on page 117)*

## SQUAREWAVES

(continued from page 53)


ship with respect to the rest of the frequency content of that waveform. The rounding of the leading and trailing edges of the 10-kHz waveform shown in the lower trace of Fig. 6 indicates either that the system (in this case our equalizer filter) is limited in frequency response above 20 kHz, or is introducing phase distortion. If this system was a power amplifier, the waveform might also indicate a "speed" or transient response limitation in one or more of the transistors used in its circuitry. A 10-kHz waveform has a period of 100 microseconds (1/10,000 second). For a circuit to respond to the eleventh harmonic of such a square wave would require a rise time of 9 microseconds. The Harman-Kardon amplifier shown earlier boasts a square-wave rise-time (to 90% of full amplitude) of only 3 microseconds.

### Amplifier instability

High-frequency square waves can be used to determine another problem present in some audio amplifier designs—instability. In Fig. 7 we see a "ringing" effect indicative of such instability. Highly capacitive loads connected to the output terminals of some amplifiers will cause such instability and are part of the reason why some amplifiers cannot be used properly with full-range electrostatic speakers, no matter how powerful they are and no matter how wide their bandwidth may be.

While experts may disagree regarding the need for such ultra-wide bandwidth and phase linearity as has been designed into Harman-Kardon's new Citation 16 amplifier and other products of its kind, it should be obvious that there is a great deal to be learned from examining the square wave response of any amplifier. Since function generators are now available at very moderate cost and can produce square waves as well as more traditional sine waves for testing purposes, there seems to be no reason why audio technicians and engineers should not avail themselves of this useful "tool."

R-E

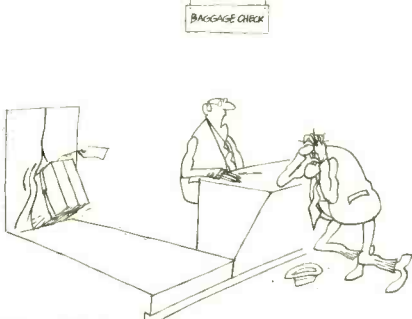

Why didn't you tell me it was a mini-computer and I wouldn't have thrown it...

# LEADER Automatic Dual Channel/Dual Trace 5" Scope/Vectorscope



- Automatic Trigger
- Automatic Horizontal Sweep
- Automatic Vertical Input

And that means virtually error-free, easy operation. You can even read between ranges in any position as with analog VTVM's. Features: separate and simult. sweep display, Ch 1 & 2 - alternate, chopped, auto/normal trigger; 10MHz b'width; 10mVp-p/cm to 20Vp-p/cm vert. sen-

sitivity, 11 calib. steps; 0.5μs/cm to 0.25/cm sweep range, 18 steps calib.; X5 sweep mag.; XY & vectorscope display. Compact, lightweight with low power consumption.

**\$569.95** Complete with probes, terminal adapters, test leads.  
MODEL LBO-506

## LEADER "Put Us To The Test"

Instruments Corp. 151 Dupont St. Plainview, L.I., N.Y. 11803 (516) 822-9300

Circle 81 on reader service card

### BEST IN RADIO-TV-ELECTRONICS BOOKS!

- Adv. Applications for Pocket Calculators. 304p. 275 il. \$5.95
- 111 Digital/Linear IC Projects. 210 p. 275 il. \$5.95
- Integrated Circuits Guidebook. 196 p. 124 il. \$5.95
- Practical CB Radio Trblshg/Repair. 210 p. 108 il. \$5.95
- Basic Digital Electronics. 210 p. 117 il. \$4.95
- Prac. Cir. Design for the Experimenter. 196p. 119 il. \$4.95
- Electronic Music Production. 156 p. 79 il. \$3.95
- Handbook of Multichannel Recording. 322 p. 196 il. \$7.95
- Computer Programming Handbook. 518 p. 114 il. \$8.95
- Jack Darr's Service Clinic No. 3. 252 p. 124 il. \$4.95
- Digital Electronics/Principles/Practice. 288 p. 191 il. \$5.95
- 2nd Class FCC Encyclopedia. 602 p. 445 il. \$7.95
- Small-Screen TV Servicing Man. 240 p. 367 il. \$6.95
- Transistor Theory for Technicians & Engineers. 224 p. \$5.95
- International Transistor Selector. 140 p. \$4.95
- Radio Astronomy for the Amateur. 252 p. 88 il. \$5.95
- Amateur Radio Novice Class License Study Gde. 224 p. \$5.95
- Radio Control for Models. 350 p. 417 il. \$6.95
- CATV Circuit Engineering. 294 p. 138 il. \$14.95
- Complete FM 2-Way Radio Handbook. 294 p. 111 il. \$6.95
- RF/Digital Test Equip. You Can Build. 252 p. 217 il. \$5.95
- CB Radio Operator's Guide. 256 p. scores of il. \$5.95
- Amateur Radio Gen. Class License Study Gde. 448 p. \$7.95
- Amateur Filmmaker's Hdbk. of Sound Sync/Scoring. \$5.95
- Directional Broadcast Antennas. 210 p. 60 il. \$12.95
- Amateur FM Conversion & Construction Proj. 256 p. \$5.95
- Commercial FCC License Handbook. 444 p. 150 il. \$5.95
- Citizens Band Radio Service Manual. 228 p. \$5.95
- Amateur Radio Adv. Class License Study Gde. 252 p. \$5.95
- Effective Trblshg. With EVM & Scopes. 238 p. 185 il. \$5.95
- CET License Handbook. 276 p. 244 il. \$5.95
- Solid-State Circuits Guidebook. 252 p. 227 il. \$5.95
- Prac. Triac/SCR Proj. For Experimenters. 192 p. 146 il. \$4.95
- Elect. Unraveled/New Commonsense Approach. 228 p. \$4.95
- Cassette Tape Recorders/How They Work/Care/Repair. \$4.95
- Pictorial Gde. to CB Radio Installation & Repair. 256 p. \$5.95
- Electronics For Shutterbugs. 204 p. 109 il. \$5.95
- Mod. Communications Switching Sys. 276 p. 171 il. \$17.95
- Electrical Wiring/Lighting For Home/Office. 204p.155 il. \$4.95
- Pract. Test Instruments You Can Build. 204 p. 157 il. \$4.95
- Experimenting With Electronic Music. 180 p. 103 il. \$4.95
- Understanding & Using the Oscilloscope. 272 p. 170 il. \$4.95
- FM Stereo/Quad Receiver Svcg. Manual. 192 p. 130 il. \$4.95
- Acoustic Techniques for Home & Studio. 224 p. 168 il. \$5.95
- Installing TV & FM Antennas. 168 p. 158 il. \$3.95
- Complete Shortwave Listener's Hdbk. 288 p. 101 il. \$6.95
- Using Elec. Testers for Auto Tune-up. 252 p. 226 il. \$4.95
- How to Build Solid-State Audio Circuits. 320 p. il. \$5.95

SEND NO MONEY! We'll invoice you on 10-DAY FREE TRIAL. Clip entire ad to order. 100% guaranteed—used by hundreds of thousands to learn.

**TAB BOOKS** DEPT RE-115  
BLUE RIDGE SUMMIT, PA. 17214


Circle 82 on reader service card

## projection television

Convert color TV to Giant Screen with the



### New MIAMI Projection TV Lens

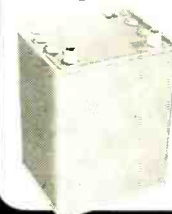

Send for further information including HV Boosters and Hi-efficiency screens.


## MIAMI PROJECTION TELEVISION

304 N.E. 79th St., Miami, Florida 33138  
(305) 759-3124

Circle 83 on reader service card

# ALLISON
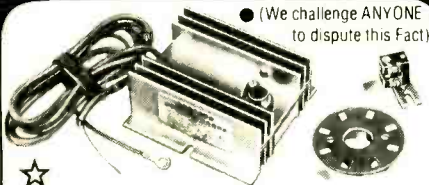
## 'OPTO-ELECTRIC' The BEST...the ULTIMATE of ALL Ignition Systems!



● (We challenge ANYONE  
to dispute this Fact)

★ Never wears out or needs any Maintenance!



● gives you Maximum Power  
with continuous PEAK PERFORMANCE

...while reducing Maintenance  
and Operating Costs!



★ The Allison OPTO-ELECTRIC System eliminates the Points and Condenser, replacing them with an OPTO-ELECTRONIC TRIGGER, using a Light-Emitting Diode and Photo transistor. The System operates on a beam of Light. As there are NO moving parts in rubbing contact, Friction-wear is completely eliminated. Timing adjustments are PERMANENT.


● Gives 40-Times more Timing accuracy than ANY system using "Mechanical Breaker-Points!" UNLIMITED RPM!  
"Electronically-Controlled" DWELL automatically supplies HIGHEST Performance at both Low and High speeds. Spark strength does not fall off at high RPM. POSITIVE SPARK helps eliminate Mixture for faster acceleration and improved Engine Performance. Sparkplugs LAST 3 to 10-Times LONGER.

● Easier Starting under any condition! Smoother running... (NO TIMING FLUCTUATION as with Magnetic Impulse Units)  
All SOLID-STATE Components. UNAFFECTED By Temperature, Moisture, or Vibration! Only Highest grade materials used. Guarantees you Solid, Dependable Performance!

● PERFECT TIMING INCREASES Engine Efficiency and Gas Mileage. SAVES Precious Fuel! Allison gives you MAXIMUM Engine Efficiency 100% of the Time and that's the name of the game for the BEST in GAS MILEAGE AND ECONOMY.

★ Perfect Timing and Dwell never change.

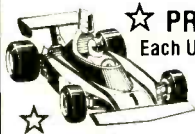● Pays for itself! Eliminates ignition Tune-Ups forever!  
"INFINITE LIFE!" Once installed. Never needs replacing!



★ PROVEN RELIABILITY!

Each Unit Tested to 15,000 RPM.

● Road and Race Proven.  
(Opto-Electric Systems won at  
INDY Two years in a row!)

★ You CAN install the ALLISON System in ALL  
the U.S. made & Foreign Cars! (4, 6, or 8-Cylinder).

"EASIEST-TO-INSTALL" UNIT ON THE MARKET.  
(Not necessary to dismantle Distributor as with other systems)

★ If you want the BEST, and SAVE! This is IT!

ORDER with CONFIDENCE...  
SATISFACTION GUARANTEED

10-YEAR FACTORY WARRANTY!  
(Free Repair or Replacement)

● Send Check or M O  
State Make, Year, Engine Size (Call! Res. add Tax)

★ (So New...it's Sold ONLY FROM FACTORY DIRECT).

● You may use your MASTER CHARGE or BANKAMERICARD.  
Send us (1) Your Number, (2) Interbank No. (3) Exp. Date.

★ Before buying any other Type ignition system.

Send Postcard for our FREE BROCHURE.

★ If you have already installed a C-D ignition system,  
Modernize and Increase its Efficiency...  
CONVERT YOUR "C-D" UNIT TO BREAKERLESS!  
Opto-Electric "TRIGGER UNIT"...Only \$34.95

● Our BEST Salesmen are the users of our ALLISON System!



● America's Oldest and Largest Mfg. of  
Opto-Electronic Ignition Systems.

**ALLISON**  
AUTOMOTIVE COMPANY

1267-L, East EDNA PL., COVINA, CAL. 91722

Circle 84 on reader service card

# equipment reports

## B&K-Precision Model 280 DMM



Circle 104 on reader service card

THE B&K-PRECISION TEST EQUIPMENT DIVISION of the Dynascan Corp. has introduced a new digital multimeter. When they say "multimeter", they're not kidding. This compact little instrument measures AC and DC voltages at 10 megohms input impedance, resistance and both AC and DC current. The voltage ranges go from 1,000 millivolts to 1,000 volts. Resistance ranges go from 100 ohms (full-scale!) up to 10 megohms. The current ranges go from 1,000 microamps up to 1,000 milliamps (which is very close to 1.0 ampere). The bad joke about "close to 1.0 ampere" is really true. On the 0-1,000 scale, you'll see 0.999, which is pretty close to 1,000 mA. If you can get within 1.0 mA, that's close!

The accuracy of the model 280 is excellent, within  $\pm 1\%$  of full-scale on all ranges except DC volts; this is  $\pm 0.5\%$ . When you go over the full-scale value on any range, the whole display blinks at you. Polarity reading is automatic, no setting to "+ volts" or "- volts", etc. If you see a minus sign, the voltage is negative; no minus sign, it's assumed to be positive. There is also a ZERO ADJUST control; just set it to DC volts, short the test leads and turn the control until you see "000" with the minus sign blinking slowly off and on.

The display uses 7-segment LED's with good brightness. Decimal point location is automatic. It's bright enough to read even fairly close to a bright bench-light. They're big enough to be read easily at any reasonable distance.

Overload protection is provided on all ranges. This will protect up to 1,000 volts. Even the low-ohms ranges, 100 and 1,000 ohms, will withstand the full 125 volt AC line voltage continuously. It is not recommended that you read the resistance of the AC line voltage, of course, but if you do, you'll be safe. There is a 1.0-A fuse in the negative jack and a special fusible resistor in the input to the electronics.

The ohms ranges of the model 280 have the new low-voltage ohms feature. Alternate ranges are low-voltage; this is read out by a H or L appearing in a little window just below the range switch. This can be used for in-circuit testing of transistor circuitry or out-of-circuit testing of transistor junctions. Blinking of the display in both polarities means that the junction is open. Zero or very low reading both ways, it's shorted. Overrange one way and an in-range reading the other shows that the junction is good.

A built-in battery test feature is also provided. Set the range switch to 10 volts DC and touch the positive probe to a terminal in a hole on the right side. A reading of .001 or more means that the batteries are good, for standard dry cells. Four size-C cells are used. Rechargeable NiCad batteries may be used; a jack on the top of the case connects the charger. The reading on these should be 090 or more. If you see 090, this means that it's time to recharge. With alkaline batteries, a service life of more than 50 hours of continuous duty is claimed.

The model 280 does all of these tricks with solid-state circuitry, of course. Numerous IC's and transistors are used. In the input, a special dual JFET (two transistors in the same case, so that they will be accurately matched) gives it the very high input-impedance. Even though the instrument is battery-powered, an IC voltage regulator is used in the DC power supply. This gives it very good stability under temperature changes and battery aging. It will hold its accuracy down to a 4-volt level though the battery gives a 6-volt supply.

The model 280 is built into a case of tough Cyclocac high-impact plastic. It has a "nubby" texture to make it easier to hold. There are no exposed metal parts for protection against accidental shock to the user.

One attractive feature of the model 280 is its price. This is less than \$100.00. For an instrument with this versatility and accuracy, this is good! Its performance compares well with instruments costing quite a bit more.

R-E


**COLOR TV KIT**

(continued from page 114)

pleted wiring this section of the TV. For that's when you read through a detailed description of how the circuit works. Then you take a series of measurements with your scope (you built

color set. A hands-on education.

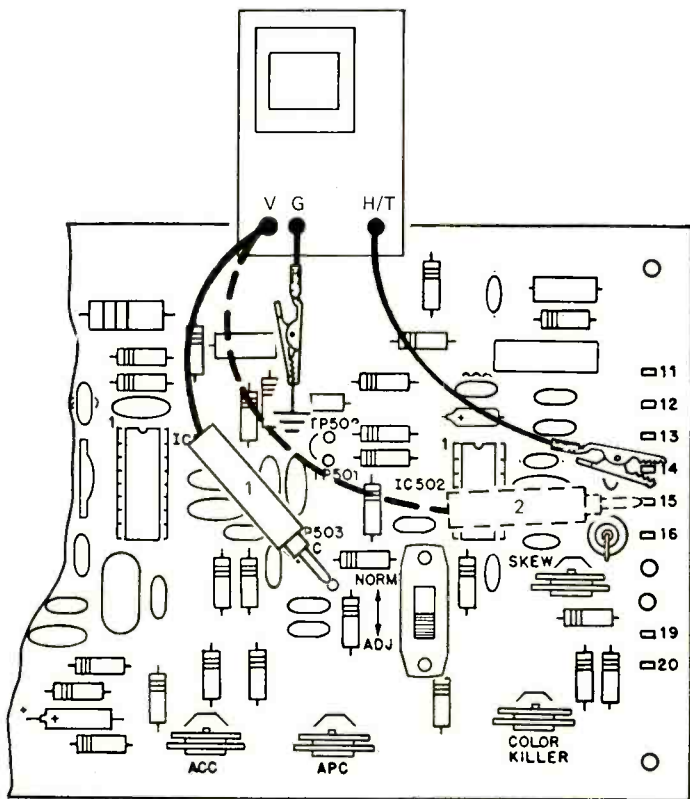The end result is a large-screen color TV in a console-type cabinet and an excellent working knowledge of color TV circuitry. You've also discovered what the various components that go into a color set look like and how they are wired into place. And you've been working with some of the newest solid-




USING THE SCOPE to observe the operation of the automatic color control is another experiment that is performed during the construction of the set.

it earlier in the course) that tells you if the power supply regulator is working the way it should. If it isn't, you troubleshoot the regulator and repair the fault. Then you go on to check out

state circuits used in today's equipment.

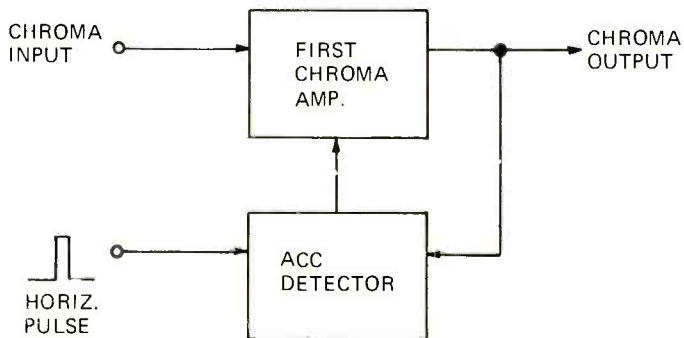Remember, this is only one part of the total color television servicing course. The complete course offers a lot more basic theory, construction of



ANOTHER BLOCK DIAGRAM, this one of the ACC section and where it connects into the video circuitry. It's also a part of the construction manual.

another section of the power supply.


This procedure continues as you assemble each section of the set until you have a complete working color TV. In the process you have learned just how each circuit operates and the part it plays in the performance of the total

test equipment, experiments and necessary data. The total course is a full education in color TV servicing techniques and should be considered as one of the ways you can learn more about electronics. It's certainly well worth looking into.

R-E

# XMAS SALE

Test Equipment  
CB Equipment  
Electronic Parts



**RCA 3-inch Oscilloscope**  
Model WO-33B **212<sup>50</sup>**



**B&K 3-Digit Portable Multimeter**  
Model 280 with case and stand **96**



**B&K 40 MHz Autoranging Counter**  
Model 1801 **195<sup>50</sup>**



**NON LINEAR SYSTEMS Digital Multimeter**  
Model LM-3 with tilt stand **113<sup>50</sup>**



**MIDLAND Scanner**  
Model 13-919 VHF/UHF Bands  
HI/LO VHF Bands (150-170 MHz and 430-470 MHz) **112<sup>50</sup> ea**



**MIDLAND Walkie-Talkies**  
3-Channel Model 13-763 **69<sup>95</sup> ea**



**MIDLAND Walkie-Talkies**  
6-Channel Model 13-777 **79<sup>95</sup> ea**



**GEMTRONICS 23 Channel CB Transceiver**  
Model GTX-36 **96**




**CASTLE Master Subber Mark V** **144<sup>50</sup>**



**WAHL Cordless Soldering Iron**  
Model 7500 **16<sup>95</sup>**

FREE CATALOG



Send check, money order or for Master Charge include MC card No. and expiration date. Add \$2.00 for shipping and insurance.

## FORDHAM

Radio Supply Co., Inc.  
Dept. 975  
558 Morris Ave., Bronx, N.Y. 10451  
Tel: [212] 585-0330

DECEMBER 1975

## ■ Project Omega

Code name for a new digital color TV varactor tuning system featuring a non-volatile programmable memory. Also, other new color TV circuits including RCA ColorTrak and Zenith zoom.

## ■ TV Games For Your Living Room

Video games have finally made it into your home, courtesy of Magnavox and Broadmoor. Here's how they work and what they can do.

## ■ All About Digital Panel Meters

State-of-the-art answer to the D'Arsonval movement. Round-up of who's making what.

## ■ Vertical FET In Audio Power Amplifiers

A new semiconductor made even newer to take over an old job.

## ■ Build A Logic Probe

Using an LED indicator to show logic levels, this probe can test digital circuits fast.

## ■ Radio-Electronics Hi-Fi Lab Tests


In-depth reports on the Marantz model 4400 4-channel receiver and the Marantz CD-4 decoder.

## PLUS

**State-Of-Solid-State**

**Jack Darr's Service Clinic**

**Step-By-Step Troubleshooting Charts**

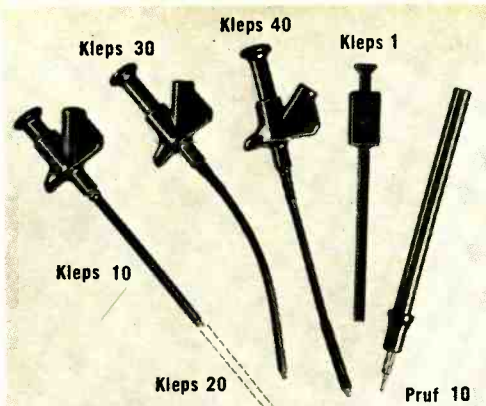

## Clever Kleps

Test probes designed by your needs — Push to seize, push to release (all Kleps spring loaded).

**Kleps 10.** Boathook clamp grips wires, lugs, terminals. Accepts banana plug or bare wire lead. 4¾" long. **\$1.39**

**Kleps 20.** Same, but 7" long. **\$1.49**

**Kleps 30.** Completely flexible. Forked-tongue gripper. Accepts banana plug or bare lead. 6" long. **\$1.79**

**Kleps 40.** Completely flexible. 3-segment automatic collet firmly grips wire ends, PC-board terminals, connector pins. Accepts banana plug or plain wire. 6¼" long. **\$2.59**

**Kleps 1.** Economy Kleps for light line work (not lab quality). Meshing claws. 4½" long. **\$.99**

**Prof 10.** Versatile test prod. Solder connection. Molded phenolic. Doubles as scribing tool. "Bunch" pin fits banana jack. Phone tip. 5½" long. **\$.89**

All in red or black - specify. (Add 50¢ postage and handling).

Write for complete catalog of - test probes, plugs, sockets, connectors, earphones, headsets, miniature components.

Available through your local distributor, or write to:

**RYE INDUSTRIES INC.**


130 Spencer Place, Mamaroneck, N.Y. 10543

In Canada: Rye Industries (Canada) Ltd.

Circle 86 on reader service card



# New

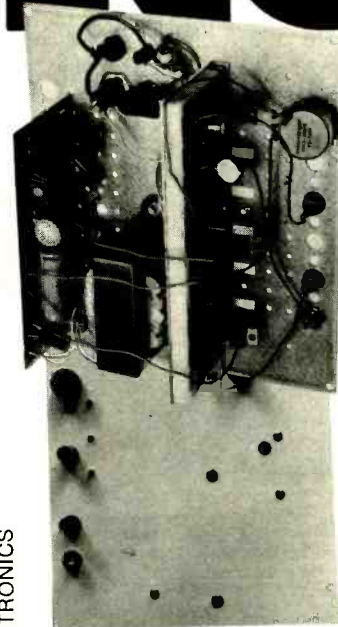

... **UNIVERSAL ELECTRONIC INSTRUMENT DESIGN AND BUILD YOUR OWN ELECTRONIC INSTRUMENT IN HOURS, NOT DAYS!**

Think of it. No circuit board to assemble or solder; just push your electronic components into the SK-10; no panels to lay out and machine — simply mount your parts . . . combine your design with the self-contained power supplies and you've got a finished instrument.

Available in 3 kit versions to meet your unique requirements, it combines the SK-10 socket with the UMP-01 universal panel and gives the designer an instrument in 1/10th the time it would take with custom instruments.

From \$50.00 to \$85.00 depending on the power supplies you want. Write for free literature.

RADIO-ELECTRONICS

**CIRCUIT DESIGN, INC.**

Div. of E&L Instruments

P.O. Box 24

Shelton, Conn. 06484



## HOW A PROM WORKS

(continued from page 74)

you in selecting a PROM. This table includes most of the presently available PROM's along with the number of bits and the bit organization of each. Also included are voltage requirements for both the read and write (programming) modes. Comments in the special notes column may also be helpful in choosing a PROM that exactly fits your requirements.


The main thing for you to remember in selecting a PROM is how you are going to program it. Unless you are prepared to spend some extra time and money for automatic or pulsing type programmers, it is advisable to stick with the fuse-link PROM's that can be programmed manually (Signetics 8223, Motorola MCM5003 etc.). Whichever way you go, remember to proceed slowly. Once you decide on your bit pattern (program), set it aside and check it over from the beginning the next day. It's easy to change an error on paper, but impossible in most PROM's.

Another hint for those of you who want to try out some PROM's: several of the PROM's we have mentioned in this article are available from companies advertising in the back pages of **Radio-Electronics**. For instance, the Signetics 8223 was noted in a couple of ads for under \$5, and the National Semiconductor MM203 (similar to Intel's 1702A) can be found for around \$20. R-E
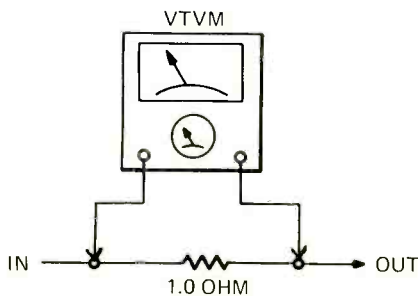
### READ CURRENT ON VTVM

*I've got an old vtvm without any current ranges. How can I read current with this instrument?—C.B., Bronx, N.Y.*

Make up an adapter with a small value, precise resistor. Connect this into the circuit, and read the voltage drop across it. For example, a 1.0-ohm resistor will show 1.0-volt drop if there is 1.0 ampere flowing, and so on.



This will work on AC or DC. If you want to read low currents, in high impedance circuits, use a 1000 ohm resistor. Now, you'll read 1.0 volt for each milliampere of current. This works only in circuits with high resistance, so that the added 1000 ohms won't upset things. R-E

## THE DYNAMIC DUO!



**Pygmy Portable Amplifier**  
\$39.95

**GNOME micro-Synthesizer**  
\$48.95

If you're into electronic music, PAIA's Pygmy Portable Amp and GNOME Micro-Synthesizer are a pair that's hard to beat. And now we offer them together, as a package, at a price that can't be beat — \$84.50 plus 10 lbs shipping — catalog #3741.

**DEMO LINE**—Use Ma Bell's low night rates to get a one minute demo of PAIA Synthesizers. Our recording equipment also takes catalog requests, charge orders, etc. (405) 843-7396.

—FREE CATALOG—



Dept. 11-R  
1020 W. Wilshire Blvd.  
Oklahoma City, OK 73116

Circle 88 on reader service card

## MATHEMATICS ELECTRONICS

We are proud to announce two great new courses for the electronic industry.

These unusual courses are the result of many years of study and thought by the President of Indiana Home Study, who has *personally* lectured in the classroom to *thousands* of men, from all walks of life, on mathematics, and electrical and electronic engineering.

You will have to see the lessons to appreciate them!

NOW you can master mathematics and electronics and actually *enjoy* doing it!

**WE ARE THIS SURE:** you sign no contracts—you order your lessons on a money-back guarantee.

In plain language, *if you aren't satisfied you don't pay*, and there are no strings attached.

Write today for more information and your outline of courses.

You have nothing to lose, and everything to gain!

### The INDIANA HOME STUDY INSTITUTE

DEPT. RE-1175 P.O. BOX 1189  
PANAMA CITY, FLA 32401


Circle 89 on reader service card

For  
faster  
service

USE  
ZIP  
CODE

on  
all  
mail

## EIGHT INSTRUMENTS IN ONE

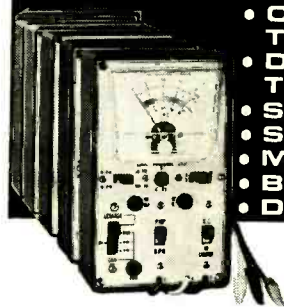

- Out-of-Circuit Transistor Analyzer
- Dynamic In-Circuit Transistor & Radio Tester
- Signal Generator
- Signal Tracer • Voltmeter
- Milliammeter
- Battery Tester
- Diode Checker

### Transistor Analyzer Model 212

Factory Wired & Tested—\$26.95  
Easy-to-Assemble Kit—\$17.95

**YOU DON'T NEED A BENCH FULL OF EQUIPMENT TO TEST TRANSISTOR RADIOS!** All the facilities you need to check the transistors themselves — and the radios or other circuits in which they are used — have been ingeniously engineered into the compact, 6-inch high case of the Model 212. It's the transistor radio troubleshooter with all the features found only in more expensive units. Find defective transistors and circuit troubles speedily with a single, streamlined instrument instead of an elaborate hook-up.

#### Features:

Checks all transistor types — high or low power. Checks DC current gain (beta) to 200 in 3 ranges. Checks leakage. Universal test socket accepts different base configurations. Identifies unknown transistors as NPN or PNP.

Dynamic test for all transistors as signal amplifiers (oscillator check), in or out of circuit. Develops test signal for AF, IF, or RF circuits. Signal traces all circuits. Checks condition of diodes. Measures battery or other transistor-circuit power-supply voltages on 12-volt scale. No external power source needed. Measures circuit drain or other DC currents to 80 milliamperes. Supplied with three external leads for in-circuit testing and a pair of test leads for measuring voltage and current. Comes complete with instruction manual and transistor listing.

EMC, 625 Broadway, New York 12, N. Y.

Send me **FREE** catalog of the complete value-packed EMC line, and name of local distributor.

NAME \_\_\_\_\_ RE-11

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ ZONE \_\_\_\_\_ STATE \_\_\_\_\_

## EMC

ELECTRONIC MEASUREMENTS CORP.  
625 Broadway, New York, N. Y. 10012

NOVEMBER 1975



**You  
can study  
FM  
two-way  
radio  
at  
home!**

Thousands have increased their knowledge of FM two-way radio through the MTI home-study courses. Now, newly revised and better than ever!

Cut me in, send free information. (No salesman will call)

Name \_\_\_\_\_  
Address \_\_\_\_\_

Code \_\_\_\_\_

I am a Veteran       I am a serviceman on active duty



Formerly

**MOTOROLA TRAINING INSTITUTE**

College Hill Road, Summerdale, Pennsylvania 17093

Circle 91 on reader service card

## MACHINE LANGUAGE PROGRAMMING

for the  
**8008**

(and SIMILAR MICROCOMPUTERS)

Written to provide you with the detailed knowledge you need to know in order to successfully develop your own MACHINE LANGUAGE PROGRAMS! This information packed publication discusses and provides numerous examples of algorithms and routines that can be immediately applied to practical problems. Coverage includes:

**DETAILED PRESENTATION OF THE '8008' INSTRUCTION SET • FLOW CHARTING • MAPPING • EDITING AND ASSEMBLING • DEBUGGING TIPS • FUNDAMENTAL PROGRAMMING TECHNIQUES: LOOPS, COUNTERS, POINTERS, MASKS • ORGANIZING TABLES • SEARCH AND SORT ROUTINES • MATHEMATICAL OPERATIONS • MULTIPLE-PRECISION ARITHMETIC • FLOATING-POINT PACKAGE • MAXIMIZING MEMORY UTILIZATION • I/O PROGRAMMING • REAL-TIME PROGRAMMING • PROGRAMMING FOR "PROMS" • CREATIVE PROGRAMMING CONCEPTS.**

Virtually all techniques and routines illustrated also applicable to '8080' and similar types of micro/minicomputers, with appropriate machine code substitution. Orders now being accepted for immediate delivery at the LOW price of just \$19.95.\* Add \$3.00 if PRIORITY mailing service desired. (\*Domestic prices.) Order direct from—

### SCELBI COMPUTER CONSULTING, INC.

1322 REAR • BOSTON POST ROAD  
MILFORD, CONNECTICUT 06460

MASTER CHARGE ACCEPTED. MASTER CHARGE customers must submit Card #, Bank #, Expiration Date, and card holder's personal signature.

**DON'T DELAY—ORDER TODAY!**

RADIO-ELECTRONICS

120

Circle 92 on reader service card



**NEW!**  
**One hand soldering...**

with the "Freehand" Solder Feeder


Once you use the new "Freehand" way of soldering, you will wonder how you ever got along without it. As you control the gun heat with your finger, you easily feed the amount of solder needed with an easy, natural thumb-motion. Solder with pinpoint accuracy, save time, use your free hand to hold pliers, heat sinks, parts, etc.

Specify make and model number of your solder gun or use our order number below:

Free, five-foot starter spool of rosin core solder included — just **\$11.95**

**Order Number**  
SF8200 fits Weller 8200, Archer 6431, Millers Falls 641  
SF4400 fits Weller 440  
SF5500 fits Weller 550, Archer 6432

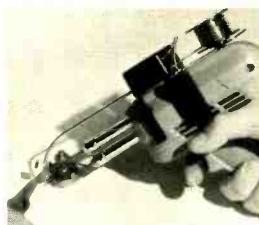Send to: **Schurman Products, Incorporated**  
P.O. Box 13  
Weymouth Landing, MA 02188



Circle 93 on reader service card

## BOOKSHELF SPEAKERS


(continued from page 76)

**LOOK FOR  
THE  
DECEMBER  
ISSUE OF  
RADIO-  
ELECTRONICS  
AT YOUR  
NEWSDEALER  
NOV. 20**

sented in three parts. The first part is termed nominal impedance and it is usually measured at a frequency of 400 Hz. The speaker industry has standardized the nominal impedance rating so that the speaker systems are either 4, 8, or 16 ohms. This specification does not affect the sound quality of the speaker system but it does affect the total amount of power that the amplifier will deliver. Most speaker systems are 8 ohms. As such the output power of most amplifiers are referenced to 8-ohm loads. There is no problem in using a 16-ohm speaker with a solid-state amplifier rated for an 8-ohm load. However, be aware that the amplifier will deliver less power to the speaker system—approximately half as much. Similarly, the amplifier will deliver approximately twice as much power to a 4-ohm speaker system.

The second impedance specification refers to the minimum amount of impedance that the speaker system will present to the amplifier and it includes the frequency that this minimum impedance will occur at. Caution—impedances of less than 3-ohms can play havoc with some amplifiers. Most speaker systems will not present less than this value to the amplifier. However, you should consider this specification if you plan on using more than one set of speaker systems in your hi-fi system. For example, if you plan on using main and remote speaker systems, the parallel combination of two speaker systems should not present less than 3 ohms to the amplifier at any frequency in the audio spectrum.

The last impedance specification is the maximum impedance that the speaker system presents to the amplifier and it includes the frequency that this impedance occurs at. This maximum impedance usually occurs in the bass frequency range of the audio spectrum. Maximum impedances as high as 25 or 30 ohms are not uncommon in speaker systems. This maximum impedance will decrease the power that the amplifier will deliver. Although the output sound level will also be reduced, this effect has been accounted for in the frequency response curves. Modern amplifiers can handle this increase in impedance fairly well. However, it is still a good idea to choose a speaker system with a minimum amount of impedance variation. (to be continued)

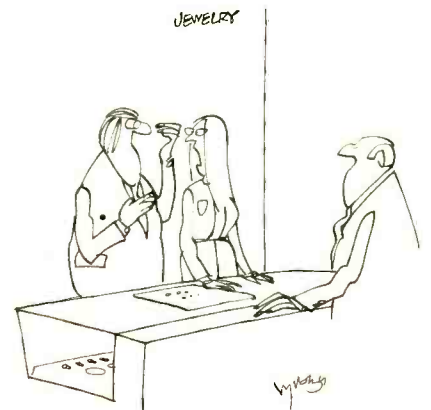

Look, we're buying a diamond, forget you're in micro miniatures.

**R-E TESTS SHURE M95ED**  
(continued from page 62)

their various cartridges. The effective mass of the stylus tip of the M95ED is a low 0.5 milligrams compared to 0.33 milligrams for the V15 Type III. For comparison, Shure's well known "work-horse" cartridge, the M3D, has an effective stylus tip mass of 2.2 milligrams and the V15 Type I (ancestor of the V15 Type III) boasted a stylus tip mass of 1.2 milligrams.

**Laboratory measurements**

Frequency response of the Shure M95ED is shown in Fig. 5 and extends within  $\pm 2$  dB from 20 Hz to 20 kHz. Cartridge resonant point is approximately at 19 kHz and the slight dip below that frequency and down to about 10 kHz is hardly significant. Other measured results are listed in Table I. It should be noted that the 400 to 500 pF capacitive loading called for in Shure's published specifications is extremely important to obtain the response shown in Fig. 5. With the recent interest in CD-4 cartridges that require much lower capacitive loading (generally 100 pF or lower), many turntable manufacturers are now supplying low-capacitance audio cables with their products in order to insure their compatibility with the CD-4 cartridges. In our first measurements, we ignored the capacitance requirement and came up with a curve that had nearly a 5 dB peak at the high end. A return to a pair of 4-foot cables of earlier vintage, added to the tonearm wiring capacitance, tamed things down considerably. Alternatively, we could have soldered in a pair of 300 pF fixed capacitors across the phono input terminals of our preamplifier and accomplished the same smoothing of the response curve. The difference is not only plottable, but audible!

Shure invented the term trackability which has almost universally replaced compliance as a meaningful measurement of cartridge capability. Since our lab is equipped with a Shure Cartridge tester and a Shure TTR-103 trackability test record (not to mention a dozen or so other test records including CBS's newly repressed STR-112 tracking and IM test record), it was a simple matter to check out Shure's claims for the trackability of the M95ED. We could not come up to the 33 cm/s velocity at 1 kHz claimed by Shure and had to settle for a very impressive 30 cm/s. The slight difference may well be due to the fact that they specify their own SME pick-up arm for making this measurement whereas we used a different high quality arm that is a part of our reference turntable system.


Separation at mid-frequencies exceeded the 25 dB minimum claimed by 3 dB and tapered off to 16 dB at 10 kHz. An overall product analysis of the M95ED, together with our comments and results of our listening tests, is contained in Table II. When properly loaded, we feel that the M95ED represents very good value in a phono cartridge and find it suitable for use in high quality single-play turntable systems and better automatics. Its low tracking force requirements preclude its use in low-cost record changers where its full potential cannot be realized.

R-E


**THE ALPHA PROFITMETER**

**AUTO ZERO/POLARITY 3½ DIGIT MULTIMETER KIT**

**WITH BRIGHT RED LED DISPLAY**

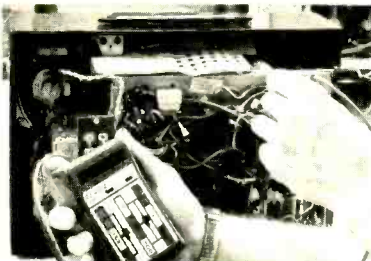

ON THE SERVICE BENCH

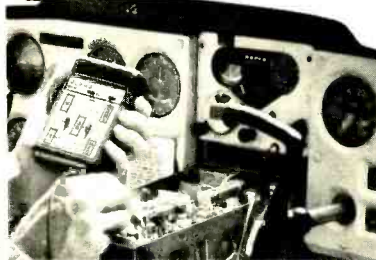

IN THE FIELD

WHEREVER AND WHATEVER THE JOB, YOU'LL NEED ITS BATTERY OPERATED PORTABILITY AND ITS HIGH ACCURACY: .1% DCV & OHMS, 1% CURRENT AND ACV.

**\$79.95** +2.95 P&H  
Less test leads & batteries



**ALPHA ELECTRONICS**  
DEPT 2 PO BOX 1005  
MERRITT ISLAND, FLA. 32952

TO ORDER OR FOR INFORMATION  
**CALL TOLL FREE**  
**800-327-2084**

**SPECIAL OFFER: "PROFIT" AND SAVE \$40.00**

NOW, BUY THE PROFITMETER AND GET OUR RALLY IV STOPWATCH KIT FOR \$29.95 OR OUR LED-1 OR DD12/24 (HR/MN/SEC/DATE) DIGITAL WRISTWATCH KIT FOR ONLY \$9.95 WITH THIS AD.

Circle 94 on reader service card

**FREE catalog**  
over 2000



unique tools, handy kits, precision instruments, technical supplies.

Our 23rd year of service to the World's finest craftsmen and technicians.

A carefully selected and tested assortment of unique, hard-to-find tools, clever gadgets, precision instruments, bargain kits. One-stop shopping for the technician, craftsman, hobbyist, lab specialist, production supervisor. Many tools and measuring instruments available nowhere else. One of the most unusual and complete tool catalogs anywhere. Get your copy of the NC FLASHER today.

**National Camera** 2000 West Union Ave. Dept. GBA  
Englewood, Colorado, 80110  
Phone (303) 789-1893

Circle 95 on reader service card



**12 REASONS YOUR CAR NEEDS TIGER CDI**

Instant starting in any weather - Eliminates tune-ups - Increases gas mileage - Increases horsepower 15% - Improves acceleration and performance - Spark plugs last up to 70,000 miles - Reduces engine maintenance expense - Amplifies spark plug voltage to 45,000 volts - Maintains spark plug voltage to 10,000 RPM - Reduces exhaust emissions - Dual ignition switch - An Unconditional LIFETIME GUARANTEE - Installs in 10 minutes on any car with 12 volt negative ground - No rewiring - Most powerful, efficient and reliable Solid State Ignition made.

SATISFACTION GUARANTEED or money back

TIGER 500 assembled . . . . . \$53.95  
TIGER SST assembled . . . . . \$42.95  
Post Paid in U.S.A.

Send check or money order with order to:

**Tri-Star Corporation**  
P. O. Box 1727 B  
Grand Junction, Colorado 81501

DEALER INQUIRIES INVITED

Circle 96 on reader service card

NOVEMBER 1975

the original  
"wedge-type" screwdriver

# QUICK- WEDGE®

SCREW-HOLDING  
SCREWDRIVER

Does all the job!

**HOLDS,  
STARTS,  
DRIVES,  
AND SETS**

the screw  
normal tightness!

**GET A SET TODAY!**  
At your dealer's  
or write

**KEDMAN  
COMPANY**  
Box 267  
Salt Lake City,  
Utah 84110

**17  
SIZES**  
© 1975 by  
Kedman Company

Circle 97 on reader service card

## FREE burglar — fire alarm catalog



over 500  
systems,  
detectors,  
controls,  
sounders,  
tools, locks,  
supplies

### TO PROTECT HOMES, BUSINESSES, INDUSTRY

Huge selection of hard-to-find security equipment from stock. 96 fact-filled pages loaded with 100's of highest quality professional alarm products, technical notes, diagrams.

#### ONE-STOP SUPERMARKET SELECTION INCLUDES:

ultrasonics, radar, infrared, undercarpet mats, magnetic contacts, smoke & heat detectors; Controls; Alarms: bells, sirens, phone dialers, lights, guard panels. Large selection of tools, relays, wire, holdup alarms, books. Fills need for industry, alarm cos., businesses, homes, institutions. Order your copy today.



mountain west alarm  
4215 n. 16th st.  
phoenix, az. 85016  
(602) 263-8831

Circle 98 on reader service card

# equipment report

## Heath IM-2202 Portable Digital Multimeter



Circle 100 on reader service card

NOT VERY LONG AGO THE DIGITAL VOLT-meter was a very expensive, laboratory instrument. Recently, the release of a number of revolutionary analog-to-digital conversion IC's have drastically changed the picture. The IM-2202 uses one of these, the MK6013, that contains all of the instrument's logic circuitry. Without it, the 3½-digit auto-polarity indicating meter would be about twice as complicated (and costly). The Heath multimeter measures AC and DC voltage, AC and DC current, and resistance.

The dual-slope analog-to-digital converter scales DC inputs of either 1 volt or 100 millivolts to a full count of 1000. Readings up to 1999 are indicated with the meter's 100% overrange capacity. The decimal point is automatically positioned as the scales are changed. Readings are updated at a 5-per-second rate on the non-blinking display. The main feature of the widely accepted dual-slope method is its high accuracy despite long term drifts of the clock oscillator frequency.

When the instrument is switched to the ohms scale, precise current sources are connected to the unknown external component. The voltage across it is then measured by the converter. This ohmmeter scheme is great for checking semiconductor junctions. On the 1K ohm scale, a test current of 1 mA is passed through the device. In effect you are measuring the forward drop of the junction at 1 mA. In the reverse direction the meter will read overrange. Though some reversed-biased junctions, like the base-to-emitter of silicon NPN's, break down below the 10 volt possible terminal voltage, anything over 1.999 volts is interpreted as an overrange resistance.

Kit construction is a procedure of wiring three tightly packed PC boards, interconnecting them with a wire harness, and installing them in a battery and transformer power supply main chassis. Even with the MK6013, there are still plenty of parts in the analog and display circuitry, so you're kept pretty busy putting it all together. I counted 39 transistors, 26 diodes, and 3 IC's in all. Careful soldering is called for. Closely spaced PC runs are prerequisites for the small 3" × 8¼" × 8" final package. Troubleshooting is not too

bad considering the packing density. Removing a few screws and the front panel exposes just about everything.

The IM-2202 has basic accuracies of ±0.2% on DC and ±0.75% on AC when calibrated with laboratory standards. Internal calibration references will bring DC and AC accuracy within ±0.5 and ±1.5% respectively. The ohmmeter scales are calibrated against built-in ±0.1% resistors. Instructions for extra care when mounting these critical components are aimed at preventing heat from affecting their values. I found that on the DC ranges, lab-standard accuracy was approached by interpolating and readjusting the plus and minus potentiometers so an externally applied voltage reads the same magnitude when the test leads are reversed. In general, the amount of improvement using this trick depends on the statistical variation of the two built in Zener diodes. These diodes are pre-measured by Heath with their precise voltages marked on their envelopes.

The digital readout tubes are Sperry gas-discharge types. They have excellent readability because of their large 0.55-in. high digits. Plugging them into the connector pins used for sockets was a bit tricky, but eventually yielded to some gentle pin bending. I'm sure the choice of display was the subject of some discussion over at Heath because of the 170 volt DC supply the gas tubes require. It would have been simpler to use LED's, but they would seriously compromise the convenience of the meter. An extra winding on the DC-to-DC power supply converter is used to generate the 170 volts. The same converter chops the 5-volt primary supply to produce the ±12-volt main voltages.

Four NiCad batteries are used to power the unit and when fully charged will run the multimeter for eight hours of field operation. Differential voltage measurements are eased by disconnecting from the capacitive loading AC power line. A special function position connects the meter to read its own battery voltage. The batteries should not be allowed to fall below 4.6 volts. When the batteries are being checked, the counter latches are disabled. Count accumulation is no longer blanked and all segments of the three right-hand digits are exercised as a readout check.

The digital multimeter is not a replacement for the FET analog meter but rather a complementary instrument. Once you own one, you will probably use the digital meter 90% of the time. But null adjustments or monitoring of changing voltages is usually best done with the analog meter.

The IM-2202 gives more accurate and faster readings than analog meters. Errors in making a measurement such as using the wrong scale or wrong interpolation are minimized. For \$179.95 it is a lot of measurement power.

R-E

# Market Center

**CLASSIFIED COMMERCIAL RATE** (for firms or individuals offering commercial products or services). \$1.40 per word . . . minimum 15 words.

**NONCOMMERCIAL RATE** (for individuals who want to buy or sell personal items) 85¢ per word . . . no minimum.

**ONLY FIRST WORD AND NAME** set in bold caps. Additional bold face (not available as all caps) at 10c per word. Payment must accompany all ads except those placed by accredited advertising agencies. 10% discount on 12 consecutive insertions, if paid in advance. All copy subject to publisher's approval. Advertisements using P.O. Box address will not be accepted until advertiser supplies publisher with permanent address and phone number. Copy to be in our hands on the 26th of the third month preceding the date of the issue (i.e. August issue closes May 26). When normal closing date falls on Saturday, Sunday or a holiday, issue closes on preceding working day.


## BUSINESS OPPORTUNITIES

**START** small, highly profitable electronic production in your basement, garage. Investment unnecessary. Details: BARTA, Box 248BX, Walnut Creek, CA 94596
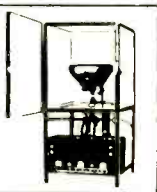
### OWN YOUR OWN PICTURE TUBE REBUILDING BUSINESS

With Lakeside Industries re-building equipment you can rebuild any picture tube!

For complete details send name, address, zip code to  
LAKESIDE INDUSTRIES  
3520 W. Fullerton Ave.  
Chicago, Ill. 60647  
Phone: 312-342-3399



## EDUCATION & INSTRUCTION

**TELEPHONE** bugged? Don't be Watergated! Countermeasures brochure \$1.00. NEGEYE LABORATORIES, Box 547-RE, Pennsboro, WV 26415

**SEMICONDUCTOR** and parts literature, J. & J. ELECTRONICS, Box 1437R, Winnipeg, Manitoba, Canada, U.S. Inquiries Invited

**FREE** educational electronics catalog. Home study courses. Write to: EDUKITS WORKSHOP, Dept. 273G, Hewlett, NY 11557

**UNLOCK** your future. Become professional locksmith by spare time homestudy. \$13 in an hour possible. All tools, equipment included. Facts free. Send name. LOCKSMITHING INSTITUTE (homestudy), Dept. 1339-115, Little Falls, NJ 07424

# BE A LOCKSMITH



"I have already master keyed my Elks Lodge and 38 apartments . . . so you see my locksmith course is practically paid for!"  
Adelindo Orsi, Jr.  
Azusa, Calif.

You'll enjoy your work as a Locksmith because it is more fascinating than a hobby—and highly paid besides! You'll go on enjoying the fascinating work, year after year. In good times or bad because you'll be the man in demand in an evergrowing field offering big pay jobs, big profits as your own boss. What more could you ask!

Train at Home—Earn Extra \$\$\$\$ Right Away!

### LOCKSMITHING INSTITUTE

Div. Technical Home Study Schools  
Dept 1479-115 Little Falls, N. J. 07424

Name \_\_\_\_\_ (Please Print)  
Address \_\_\_\_\_  
City/State/Zip \_\_\_\_\_  
 Check here if Eligible for Veteran Training

**MANUALS** for Govt. surplus radios, test sets, scopes, List 50¢ (coin). **BOOKS**, 7218 Roanne Drive, Washington, DC 20021

## F.C.C. EXAM MANUAL

PASS FCC EXAMS! Memorize, study—Tests—Answers for FCC 1st and 2nd class Radio-telephone licenses. Newly revised multiple choice questions and diagrams cover all areas tested in FCC exams, plus Self-Study Ability Test. \$9.95 postpaid. Money-back guarantee.



COMMAND PRODUCTIONS P.O. Box 76348 E  
RADIO ENGINEERING DIV SAN FRANCISCO, CAL. 94176

## FOR SALE

**CARTRIVISION**—Color video tape recorders, TV cameras, face plates, heads, blank tapes, spare electronics. Send SASE for price list. PHOENIX SERVICES, Dept. RE, P.O. Box 6509, San Jose, CA 95150

## PRINTED CIRCUIT

**EPOXY GLASS CIRCUIT BOARD STOCK; CARBIDE DRILL BITS; TAPE RESIST; ARTWORK; BUBBLE ETCHERS**  
SEND S.A.S.E. FOR FLYER  
TRUMBULL  
833 BALRA DR., EL CERRITO, CA. 94530

**COMPUTER** accessories, kits, surplus, semi-conductors—DIP TTL FF ten for \$1.26, telecommunications, catalog \$0.50. E/S LAB, Box 738B, College Park, MD 20740

**GUIDE** to electronic assembly business. Big profits. Start home, spare time. No investment. Free literature: BARTA, Box AX, Walnut Creek, CA 94596

**GET** into broadcasting—become disc jockey, engineer. Start own station, get free tapes—records. Free details. EGW, Box 5516-FM, Walnut Creek, CA 94596

**TTL** and other stock. Send for free list. RARICK, Box 29, Cornwells Heights, PA 19020

**TEKTRONIX** and Hewlett-Packard oscilloscopes and test equipment. Free information. Special: OS8/U portable oscilloscope. DC-2MHz recurrent sweep, 115VAC, and 3" CRT. Used and tested operational, \$63.00 postpaid except COD. Georgia residents add 3%. 10 day money back guarantee. Send check or money order to AMERICAN CALIBRATION SERVICES, Box 8104, Athens, Georgia 30601

**FREE** catalog. Ultrasonic devices, LED's, transistors, IC's, keyboards, unique components. Low prices! CHANEY'S, Box 15431, Lakewood, CO 80215

# Olson Electronics Parts and Accessories SALE

**DUAL IN-LINE IC'S**  
Made in U.S. These IC's are guaranteed against defects. With diagram. Shpg. wt. 1/4 lb.

**LOW AS 29¢**  
Type 7400 Quad 2-Input pos. NAND Gate. High speed. diode-clamped inputs.  
Type 7402 Quad 2-Input pos. NOR Gate. Low-noise Propagation delay 12 ns  
Type 7403 Reg. 69¢ Sale 29¢  
Type 7404 Hex Inverter. Low noise, low power dissipation.  
Type 7405 Reg. 79¢ Sale 29¢  
Type 7410 Triple 3-Input pos. NAND Gate. Low output impedance. diode-clamped inputs.  
Type 7434 Reg. 69¢ Sale 29¢  
Type 7447 BCD to 7-Segment Decoder/Driver. With common anode displays.  
TR-435 Reg. 2.99 Sale 59¢  
Type 7473 Dual J-K Master/Slave Flip-Flop.  
TR-436 Reg. 1.19 Sale 39¢  
Type 7474 Dual D-Type Edge Triggered Flip-Flop.  
TR-438 Reg. 69¢ Sale 39¢  
Type 7475 4-Bit Latch. Temp. stores binary coded info.  
TR-437 Reg. 1.89 Sale 79¢  
Type 7490 Decade Counter. Binary coded decimal counter with symmetrical divide.  
TR-439 Reg. 1.89 Sale 79¢

**Rechargeable Battery With Charger**  
6 VDC alkaline rated @ 5 amp/hr. Max. current 1.25 amp. Eveready Reg. #565 4 lbs. 9.98 BA-307. Sale 4.99

**500-ft. Hook-Up Wire**  
For almost any type of printed circuit or wiring project. 2 lbs. 9.98 WW-579. Sale 1.69

**3-6 VDC Motors**  
Kit / 5 Small 1/2 lb MO-333. Sale 55¢  
Kit / 4 Med. 1 lb MO-334. Sale 79¢  
Kit / 4 Ass'd. 2 lbs MO-335. Sale 99¢

**12-Digit IC Calculator Chip**  
40-pin DIP single CAL-Tech #CT-5001 7 - seg decoded display output, overflow lock-out. Specs Incl.  
Reg. 5.98 XM-330. Sale 1.59

**50-Pc. 1 Amp Diode Kit**  
Polarity is unmarked but easily identified with ohm meter. 200 PIV rated. 1/2 lb. DI-051. Sale 69¢

**Switching Diodes**  
Pkg. of 10 1N4148 for low current applications. 10 mA. 75 PIV. 1/4 lb. XM-382. Sale 59¢

**FREE Olson Catalogs**  
Next 7 issues FREE!

**Olson electronics** Dept. LD  
260 S. Forge St., Akron, Ohio 44327

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_ APT \_\_\_\_\_  
CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

**BIG 1 LB. Resistor Kit**  
Over 400 pieces of 1/4, 1/2 1 watt sizes. All color coded. 2 1/2 lbs. RS-239. 99¢

**PNP Transistors**  
Big 10 pc kit. For general 10 & hi-gain & audio. Germanium types. Untested. 1/4 lb. TR-445. Sale 39¢  
TR-444. NPN. 39¢

**Three 60-Min. Cassettes**  
Pkg. / 3 quality cassette recording tapes. 60-Min. each. 1/2 lb. TA-879. Sale 99¢

**8-T Blank Tape**  
Famous manufacturer's high quality low priced tapes. 1/2 lb. TA-854. 40-Min. 89¢  
TA-855. 60-Min. 99¢

**Silicon Rectifiers**  
1 Amp Epoxy Type Pkg. / 5. 4 oz. Reg. Sale  
DI-028 50 PIV IN4001 89¢ 39¢  
DI-029 100 PIV IN4002 99¢ 39¢  
DI-030 200 PIV IN4003 119 39¢  
DI-031 400 PIV IN4004 139 39¢

**LED'S 2V 10 mA**  
Gallium phosphide. Large red. high quality LED. Wt. 1/4 lb. Pkg/5. Reg. 1.19 PL-233. Sale 59¢

**SCR Assortment**  
Hobby Pak of 25. Pkg. of 25. Untested. Wt. 1 lb. TR-446. Sale 99¢

**ORDER TODAY!** (Send to Olson Electronics, 260 S. Forge St., Akron, Ohio 44327. Allow for postage. C.O.D. 20% Deposit. Ohio Residents Add 4% Sales Tax)

Circle 105 on reader service card

**MAGNETS.** All types. Specials—20 disc, or 10 bar, or 2 stick, or 8 assorted magnets, \$1.00. **MAGNETS**, Box 192-F, Randallstown, MD 21133

**8080 CPU: \$120.00; 8008 CPU: \$23.00; XR205: \$7.25; XR210: \$4.50; 8111, 8101, 1K RAM: \$6.50 each; 2103, 1K RAM: \$3.50; 3 1/2 digit, .4" reflective liquid xtal: \$8.50; 44 pin edge connector (2x22) \$1.25; cassette computer interface board: \$14.50; TVT-II main & memory board: \$35.00. **ELECTRONIC DISCOUNT SALES**, 138 N81st, Mesa, AZ 85207**

**RECONDITIONED** test equipment. \$0.50 for catalog. **WALTER**, 2697 Nickel, San Pablo, CA 94806

**FREE flyer.** Semis, components, electronic hardware. Lowest prices. **VANGUARD ELECTRONICS LTD.**, Box 1193, Edmonton, Alberta, Canada T5J 2M5

**TV cameras** with zoom lens, \$125 (new); Car-trivision front panels, heads. **BOB ALLEN**, 124 Lundy Lane, Palo Alto, CA 94306 (415) 493-6146

**POWER** supplies, signal generators, H.O. transistor throttles, signal compressors. Free catalog. **MINITRON**, Box 184, Anoka, MN 55303

**SURPRISE!** Build inexpensively, the most unusual test instruments, futuristic gadgets using numerical readouts! Catalogue free! **GBS**, Box 100B, Greenbank, WV 24944

**NEW** Canadian Magazine, "Electronics Workshop," \$5.00 yearly, sample \$1.00. **ETHCO**, Box 741 "A", Montreal

**DMM?** Have it calibrated. 2 1/2 and 3 1/2 digit DMM's. Postcard for details. **XENOPHONICS**, P. O. Box 1667, Annapolis, MD 21403

**PARTS! CORNELL TUBES!**  
 Send For FREE CORNELL'S New Color Catalog  
**33¢** per tube  
**36¢** per tube  
 ORDER FREE IF NOT SHIPPED IN 24 HOURS  
 48 Pgs. New Items IN LOTS OF 100  
**4215 E UNIVERSITY AVE. SAN DIEGO, CALIF. 92135**

**CANADIAN** discount and factory clearouts catalog. Top brand stereo equipment, calculators, test gear, CB & communications, telephones. Factory dumps—government surplus. Amazing bargains. Unusual items. Rush \$1. **ETCO-RE**, 521 5th Ave., NYC, 10017

**HARD-to-get** repair supplies for police radar. **ELECTRONIC SPECIALISTS, INC.** Box 122-RE, Natick, MA 01760

**LOW-cost** digital/analog test equipment. Logic probes from \$9.95. Free catalog. **ELECTRO INDUSTRIES**, 4201 Irving Park, Chicago, IL 60641

**RECORDS-TAPES!** Discounts to 73%; all labels; no purchase obligations; newsletter; discount dividend certificates; 100% guarantees. Free details. **DISCOUNT MUSIC CLUB**, 650 Main St., Dept. 3-115, New Rochelle, NY 10801

**FREE** catalog. IC's, Semis. **CORNET ELECTRONICS**, 649A Notre Dame W., Montreal, Que. Canada, H3C-1H8 US Inquiries.

**FREE** catalog, plus **FREE** diagrams & instructions for constructing a novel **ELECTRONIC ORGAN** with the parts you probably have on hand. We'll include a circuit and complete directions for assembling an amazing **XYLOPHONE**  
 Phone or write. Our Telephone Machine will record your name, address & zip. Night calls cost only 22¢  
**CORTLANDT ELECTR.**, 114 West Broadway (Dial 212-964-8044) New York, N.Y. 10013

**RADIO & TV tubes** 36¢ each. One year guaranteed. Plus many unusual electronic bargains. Free catalog. **CORNELL**, 4217-E University, San Diego, CA 92105

**ELECTRONICS DESIGN NEWSLETTER**  
 ★ Logic Design Techniques  
 ★ Digital & Linear Design Theory & Procedures  
 ★ Construction Projects  
 Subscription \$6 Sample Copy \$1.  
**VALLEY WEST** Box 2119-L Sunnyvale, CA 94087

INTEL 8080 CPU	\$139.00
8008 8 BIT MICRO PROCESS- ING CHIP (with Data Book)	\$ 35.00
2102-2 1024 BT RAM	\$ 2.95
5202A UV PROM	\$ 19.00
MMS203 UV PROM	\$ 19.00
1702A UV PROM	\$ 19.95
5204-4K PROM	\$ 24.95
MINIATURE TRIM POTS 100, 500 5K, 10K, 25K, 50K, 100K, 200K \$.75 ea.	3/\$2.00
MULTI-TURN TRIM POTS Similar to Bourns 3010 style, 3/4" x 5/8" x 1 1/4"; 50, 100, 2000, 10,000 ohms \$1.50 ea.	3/\$4.00
LIGHT ACTIVATED SCR's TO-18, 200V 1A	\$1.75
PRINTED CIRCUIT BOARD 4 1/2" x 6 1/2" single sided epoxy board, 1/16" thick, unetched \$50 ea.	5/\$2.20
PHENOLIC 4.5" x 6.5" VECTOR BOARD .1" SPACING	\$1.50
4 WATT IR LASER DIODE	\$7.95
2N 5460 P FET	\$.45
TIS 73 N FET	\$.45
2N 4891 UJT	\$.45
ER 900 TRIGGER DIODES 4/100 2N 6028 PROG. UJT	\$1.00 \$.65
VERIPAX PC BOARD This board is a 1/4" single sided paper epoxy board, 4 1/2" x 6 1/2", DRILLED AND ETCHED which will hold up to 21 single 14 pin IC's or 8, 16 or LSI DIP IC's with buses for power supply connector.	\$5.25
MT-2 PHOTO TRANS	\$.60
RED, YELLOW, GREEN OR	
AMBER LARGE LED's ea.	\$.20
14 PIN DIP SOCKETS	\$.40
16 PIN DIP SOCKETS	\$.50
MOLEX PINS	100/\$1.00
8 PIN MINI DIP SOCKETS	\$.32
10 PIN TO-5 TEFLON PC SOCKETS	\$.60
10 WATT ZENERS 3.9, 4.7, 12, 18, OR 22V	ea. \$.75
1 WATT ZENERS 4.7, 5.6, 10, 12, 15, 18 or 22V	ea. \$.40
Silicon Power Rectifiers	
PRV 1A 3A 12A 50A 125A	
100 .06 .14 .30 .80	
200 .07 .20 .35 1.15 4.25	
400 .09 .25 .50 1.40 6.50	
600 .11 .30 .70 1.80 8.50	
800 .15 .35 .90 2.30 10.50	
1000 .20 .45 1.10 2.75 12.50	
REGULATED MODULAR POWER SUPPLIES	
+ -15VDC AT 100ma	
115VAC INPUT	\$24.95
5VDC AT 1A, 115VAC INPUT	\$19.95
12V .5A	\$24.95
IN 4148 (IN914)	14/\$1.00
1103, 1024 bit RAM	\$2.75
NEC 6003 2048 bit RAM	\$6.00
1101 256 bit RAM	\$1.40
8223 PROM	\$2.50
7489 RAM	\$2.30

TRANSISTOR SPECIALS	
2N1546 PNP GE TO-3	\$ .95
2N5086 PNP Si TO-92 4/\$1.00	
2N4898 PNP TO-66	\$ .60
2N404 PNP GE TO-5	5/\$1.00
2N3919 NPN Si TO-3 RF	\$1.50
MPSA13 NPN Si TO-92 3/\$1.00	
2N3767 NPN Si TO-66	\$.70
2N2222 NPN Si TO-18 5/\$1.00	
2N3055 NPN Si TO-3	\$.80
2N3904 NPN Si TO-92 5/\$1.00	
2N3906 NPN Si TO-220 5/\$1.00	
2N6109 PNP Si TO-220 5/\$1.00	
2N3866 NPN Si TO-5	\$.75
SI RF POW	\$.75
MJ252 NPN Si TO-66	\$.90
2N3638 NPN Si TO-5 5/\$1.00	
2N6517 NPN TO-92 Si 3/\$1.00	
CAPACITORS	
35V at .47 uf TANT 5/\$1.00	
35V at 6.8 uf TANT 3/\$1.00	
20V at 150 uf TANT .4	\$.40
6V 30 uf TANT	5/\$1.00
12V 200 uf ELEC	\$.30
200V 4.7 uf ELEC	\$.30
DO-33-A 3 DIG. LED	
ARRAY READOUT	\$1.65
MAN-1 READOUT	\$1.75
MAN-3 READOUT	\$1.00
MAN-4 READOUT	\$1.30
MAN-7 READOUT	\$1.25
DL 747	\$3.50
CD 110 LINEAR 256 XI BIT SELF SCANNING CHARGED COUPLED DEVICE	\$125.00
SANKEN AUDIO POWER AMPS	
Si 1010 G 10 WATTS	\$ 6.90
Si 1020 G 20 WATTS	\$13.95
Si 1050 G 50 WATTS	\$24.95
LINEAR CIRCUITS	
LM 309K 5V 1A REGULATOR	\$1.35
723 -40 +40V REGULATOR	\$.54
301/748-HI Per. Op. Amp.	\$.28
320T 5, 12, 15, OR 24V	
NEGATIVE REG.	
741A OR 741C OP. AMP.	\$.31
709C OPER. AMP.	\$.25
307 OP AMP	\$.25
CA 3047 HI PERF. OP AMP	\$.95
CA 3089 FM IF SYSTEM	\$3.25
340T-5, 8, 12, 15, 18, 24V	
101 OPER. AMP. HI PERFORM.	\$1.75
LM 308 Oper. Amp., Low Power	\$1.05
747-DUAL 741	\$.65
556-DUAL TIMER	\$1.30
537-PRECISION OP. AMP.	\$2.60
LM 3900-QUAD OP. AMP.	\$.49
LM 324-QUAD 741	\$1.50
560-PHASE LOCK LOOP	\$2.50
561-PHASE LOCK LOOP	\$2.50
565-PHASE LOCK LOOP	\$1.75
566 FUNCTION GEN.	\$2.50
567-TONE DECODER	\$2.00
703-RF-IF AMP.	\$.41
8038 IC VOLTAGE CONT. OSC.	\$3.90
LM370-AGC SQUELCH AMP.	\$1.15
555-2 µs-2 HR. TIMER	\$.53
553 QUAD TIMER	\$3.50
FCD 810 OPTO-ISOLATOR	\$.80
1458 DUAL OP. AMP.	\$.65
LM 380-2W AUDIO AMP.	\$1.10
LM 377-2W Stereo Audio Amp.	\$2.50
LM 381-STEREO PREAMP.	\$1.50
LM 382-DUAL AUDIO PREAMP	\$1.50
LM 311-HI PER. COMPARATOR	\$.95
LM 319-Dual HI Speed Comp.	\$1.10
LM 339-QUAD COMPARTOR	\$1.25
TRIACS	
PRV 1A 10A 25A 1.5A 6A 35A	
100 .40 .70 1.30 .40 .50 1.20	
200 .70 1.10 1.75 .60 .70 1.60	
400 1.10 1.60 2.60 1.00 1.20 2.20	
600 1.70 2.30 3.60 1.50 3.00	
SCR'S	
Send 20c for our catalog featuring Transistors and Rectifiers 145 Hampshire St., Cambridge, Mass.	

C/MOS (DIODE CLAMPED)	
74C02-26	4013-45 4026-1.90
74C10-30	4015-1.24 4027-.55
74C157-1.75	4016-.50 4028-.95
4001-.24	4017-1.15 4030-.49
4002-.24	4018-1.24 4035-1.50
4006-1.35	4019-.50 4042-.75
4007-.24	4022-1.24 4046-2.75
4009-.50	4023-.24 4047-3.50
4010-.50	4024-.95 4050-.49
4011-.24	4025-.24 4055-1.95
4012-.24	
MMS5013-1024 BIT DYN SHIFT REG.	\$10.95
MMS5016-512 BIT DYN SHIFT REG.	\$ 6.95
MMS508-STATIC SHIFT REG. 1024-BIT	\$ 5.40
COUPLE DEVICES	
FPA 711-7 LEVEL Diode Array Optical Tape Readers	\$5.95
Low cost Digital Volt Meter Kit. Kit contains Integ. Circuit Schem. IC Boards, LCD Dis- plays, Regulator, Resistors, Cap- acitors and Transistors. Outer case and battery not supplied. Accurate to ± one count, has range of 1 mV to 1,999 V DC. It features one 5V power supply + the oscillator is built into the chip. Overall dimensions 1 1/2" x 3 1/2" x 3 1/2" \$44.00	
TTL IC SERIES	
74L00-.26	7476-.35
7400-.14	7480-.48
7401-.15	7483-.75
7402-.15	7485-1.05
7403-.15	7486-.34
7404-.18	7490-.49
7405-.18	7491-.79
7406-.35	7492-.49
7407-.33	7493-.49
7408-.18	7495-.74
7409-.15	7496-.79
7410-.15	74107-.34
7411-.25	74121-.38
7412-.30	74123-.74
7413-.45	74125-.54
7414-.45	74126-.54
7416-.33	74150-.92
7417-.33	74151-.69
7420-.15	74153-.79
7425-.27	74154-1.05
7426-.24	74155-1.05
7427-.27	74157-.75
7430-.15	74161-.95
7432-.24	74163-.95
7437-.29	74164-1.10
7438-.29	74165-1.10
7440-.15	74173-1.35
7441-.95	74175-.95
7442-.50	74177-.75
7445-.79	74181-2.30
7446-.87	74192-1.10
7447-.87	74193-1.10
7448-.85	74195-.74
7472-.28	74196-.95
7473-.34	8267-1.95
7474-.35	75324-1.75
7475-.49	75491-1.10
CT7001 CALENDAR ALARM CLOCK CHIP	\$5.75
SPDT MIN. TOGGLE SWITCH MTA-105	\$1.50
DPDT MIN. TOGGLE SWITCH MTA-206	\$2.25

# SEMICONDUCTOR SUPERMARKET

## FREE CATALOG

### NAME BRAND PRIME QUALITY SEMICONDUCTORS

- MOTOROLA
- RCA
- FAIRCHILD
- MOSTEK

ALSO OTHER PARTS FOR DO-IT-YOURSELF PROJECTS

### CIRCUIT SPECIALISTS CO.

Box 3047 Scottsdale, AZ 85257

RADIO-ELECTRONICS

Terms: FOB Cambridge, Mass. Send Check or Money Order, include Postage. Minimum Order \$5.00. COD's \$20.00.

**SOLID STATE SALES**  
 P.O. BOX 740  
 SOMERVILLE, MASS. 02143  
 TEL. 617 547-4005

WE SHIP OVER 95% OF OUR ORDERS THE DAY WE RECEIVE THEM

**P**ROCESSING  
**A**ND  
**C**ONTROL  
**E**LEMENT  
**\$125**

FROM NATIONAL SEMICONDUCTOR, FORMERLY THE "SECRET MICROCOMPUTER COMPANY": REAL 16 BIT PARALLEL MICROPROCESSOR. 40 PIN DIP--CAPABILITY FOR 45 CLASSES OF INSTRUCTIONS AND UP TO 337 INSTRUCTIONS. A POWERFUL  $\mu P$  --- AND IN STOCK! INTERFACE CHIPS SUPPLIED SO THAT EVERYTHING IS TTL COMPATIBLE... & DATA,

NOW AVAILABLE: "PACE DATA PACKET". FOR \$2.50 (TO COVER PRINTING AND POSTAGE; REFUNDABLE WITH PACE ORDER) YOU GET MANY PAGES OF DETAILED AND SPECIFIC INFORMATION ON THE CHIP ITSELF, SYSTEM ORGANIZATION, SOFTWARE, ETC. NOT JUST A DATA SHEET---A COMPLETE PACE REFERENCE PACKAGE. AN EXPERIENCED COMPUTER BUILDER COULD BUILD A COMPLETE SYSTEM FROM INFORMATION PROVIDED IN THIS PACE PACKET ALONE.

OEMS PLEASE NOTE: NATIONAL IS COOPERATING WITH US SO THAT SCHOOLS, HOBBYISTS, AND EXPERIMENTERS CAN HAVE EASY ACCESS TO THIS POWERFUL NEW 16 BIT MICROPROCESSOR FOR IMMEDIATE EVALUATION, PROTOTYPING, AND EXPERIMENTING. HOWEVER, WE ARE NOT EQUIPPED TO HANDLE OEM ORDERS: OEMS SHOULD CONTACT THEIR LOCAL NATIONAL DISTRIBUTOR OR NATIONAL SALES OFFICE. THANK YOU!

OUR PACE CHIPS ARE FULLY FUNCTIONAL WITH RELAXED ENVIRONMENTAL AND ELECTRICAL PARAMETERS.

TWISTED PAIR: 20 FT./\$4.95  
15 TWISTED PAIRS, YELLOW/BLACK



RIBBON CABLE: 20 FT./ \$2.95  
17 CONDUCTOR, COLOR-CODED; WIRE WIDTH SPACED FOR LOW INTERLEAD CAPACITANCE.

COLOR-CODED SPECTRA-STRIP Multiconductor, flat wire, in multiples of 10 conductors up to 100 total. Cost: 1¢/conductor foot. 20 ft lengths only.



WE'RE CONTINUING OUR  
2<sup>ND</sup> ANNIVERSARY  
SPECIAL!

2102 1K STATIC RAM  
★\$1.95★

DISCOUNTS: BUY 100, TAKE 20% - BUY 1000, TAKE 30%

GUARANTEED < 750 NS.

THANK YOU VERY MUCH FOR YOUR  
OVERWHELMING RESPONSE TO OUR SPECIAL!

SOCKETS

G-Gold plated contacts T-Bright tin  
14 pin T...11/\$1.95 14 pin G...10/\$1.95  
16 pin G...10/\$3.75 24 pin T...5/\$1.95  
28 pin T...5/\$1.95 40 pin T...5/\$2.95  
LOW PROFILE SOCKETS:  
16 pin G...10/\$1.95 40 pin G...5/\$2.95

**COMPUTER  
KIT NEWS**


This ad is being prepared in mid-August, so all the details aren't nailed down yet; but we've had our system up and running in Berkeley, executing instructions and waiting for its case and panel. Target price: UNDER \$600--and this includes cassette I/O, bit serial interface for teletype, editor and assembler, 1K x 16 integral RAM, readouts, keyboard, and more. By the time this ad appears, we'll have a system data package for a nominal fee.

**GODBOUT**

BILL GODBOUT ELECTRONICS  
BOX 2355, OAKLAND AIRPORT, CA 94614

**DIGITAL CLOCK KIT**

ALL PARTS INCLUDED

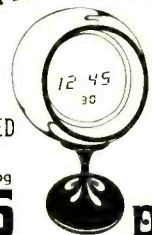

ONE EVENING PROJECT

+2 lbs shpg  
**\$19.95** **SIX DIGITS!**

**BOOK--\$8.95**  
"Electronic Projects for Musicians"

Craig Anderton's new book tells you how to build the 19 projects below---even if you've never built anything before. It contains an introduction to basic electronics with emphasis on practical construction techniques, detailed instructions on the projects, how to troubleshoot, and where to find more information. Craig has selected us to provide parts kits for the projects, as we have for his how-to articles in the past. Our kits save you the trouble of locating parts and making circuit boards. Send address & stamp for latest prices, or \$6.95+ postage for the book. It contains a record that demonstrates the sounds of the projects, and a forward by Joe Walsh. HAVE FUN!

- PREAMP ■ PASSIVE TONE CONTROL ■ LOW COST, EXPANDABLE MIXER ■ MINIAMP ■ BATTERY ELIMINATOR ■ TRIGGERED, NOISELESS TYPE FUZZ
- AC TESTER ■ HI-FI TYPE TONE CONTROLS
- HEADPHONE AMP ■ STEREO WA-WA ■ SYNTHESIZER LIKE SUPER FILTER ■ DUAL BATTERY ELIMINATOR ■ BALANCED MODULATOR
- METRONOME ■ ELECTRONIC FOOTSWITCH SYSTEM ■ TREBLE BOOSTER ■ TUNING STANDARD
- BASS FUZZ ■ COMPRESSOR-SUSTAINER

GET YOUR MITTS ON A GODBOUT  
4K X 8 RAM KIT  
\$109.22 \* 1/3¢ per bit

TRI-STATE BUFFERED OUT DRIVES 20 TTL LOADS FOR GOOD BUS DRIVE. LOW NOISE SUSCEPTIBILITY. EXTEND FEATURE, MEMORY PROTECT, ON BOARD VOLTAGE REGULATION. PRESENTS 1 LPTTL LOAD TO ALTAIR & OTHER BUSES. PLATED-THROUGH INDUSTRIAL QUALITY BOARD, AS WELL AS THE OTHER NICE THINGS YOU HAVE COME TO EXPECT FROM US.

**LOW POWER EROM BOARD KITS**

4K x 8 \$200 ADD \$25 AND WE'LL PROGRAM  
2K x 8 \$125 ADD \$15 AND WE'LL PROGRAM

FOR YOUR EDITOR/ASSEMBLER OR WHATEVER. FAST--1 usec, 1 wait. Full 4K needs 5V @ 1/2A and -12 @ 100 ma; board runs cool, supply doesn't grunt

ALTAIR 8800 OWNERS, TAKE NOTE: ALL ABOVE MEMORY BOARDS ARE DIRECTLY PLUG-IN COMPATIBLE! NO JUMPERS, NO RASSLE, NO HASSLE; ALSO ELECTRICALY COMPATIBLE WITH OTHER 8 BIT MACHINES.


**INTEGRATED CIRCUITS**

DM8097	\$1.20	TRI-STATE HEX BUFFER
DM8131	\$2.50	6 BIT UNIFIED BUS COMPARATOR WITH HI Z INPUTS AND HYSTERESIS
DM8544	\$0.90	QUAD TRI-STATE SWITCH DEBOUNCER
DM8833	\$1.90	QUAD TRI-STATE TRANSCIEVER WITH HYSTERESIS
DM8837	\$1.85	HEX UNIFIED BUS RECEIVER WITH HYSTERESIS
DS0026	\$3.00	DUAL CLOCK DRIVER
DS3608	\$3.00	HEX TRI-STATE MOS TO TTL CONVERTER WITH PROGRAMMABLE INPUT CURRENT
8008	\$17.95	POPULAR 8 BIT MICROPROCESSOR---IDEAL FOR PERIPHERAL CONTROL
5204	\$24.50	SIMILAR TO 5203 (SEE BELOW), BUT 4K BITS WORTH OF EROM

**SPECIAL! ORDERS POSTMARKED BEFORE NOVEMBER 30: 5203 2K EROM. PROGRAMMABLE AND ERASEABLE, STATIC AND NON-VOLATILE. \$9.95!**

**ANOTHER SPECIAL---8 BIT MICROCOMPUTER CHIP SET: 1-8008 8 BIT MICROPROCESSOR, 8-2102s (1K STATIC RAMS), CHIP SET: \$32.50.**

LOOPSTICK 3 FOR  
ANTENNA \$2.00

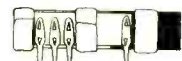

EXPERIMENTERS Ferrite type; for AM transistor radio.

**2" SPEAKER**



For acoustic couplers, toys, radios, monitor spkr. The price is 3 right, too. **FOR \$2.50**

TERMS: ADD 50¢ TO ORDERS UNDER \$10; ADD SHIPPING AS SHOWN. CALIFORNIANS ADD TAX. SORRY, NO COD.

TO PLACE YOUR MASTERCARD®/BANKAMERICARD® ORDERS, CALL OUR 24 HOUR ORDER LINE: (415) 357-7007.

Circle 107 on reader service card



### POTTER BRUMFIELD

Type KHP Relay  
4 PDT 3A Contacts

24 VDC (650 coil) \$1.50 Ea.  
120 VAC (10.5 MA coil) \$1.75 Ea.

### RCA 2010

Numitron Digital Display Tube  
Incandescent 5-volt 7-segment  
with .6" high numeral visible  
from 30 ft., standard 9-pin  
base (solderable), and left  
hand decimal point.  
EACH \$5.00 5 FOR \$20.00

### CMOS

CD4000	\$ .29	CD4016	\$ .69
CD4001	.29	CD4019	.69
CD4002	.29	CD4023	.29
CD4007	.29	CD4024	1.50
CD4008	1.98	CD4025	.34
CD4009	.59	CD4030	.65
CD4010	.59	74C20	.65
CD4011	.29	74C42	2.00
CD4012	.29	74C157	2.50
CD4013	.69	74C161	3.00
CD4015	1.98	74C195	2.00

### Numeric Display 1/4" Single Digit GaAsP LED

SUPER SPECIAL \$ 59  
TEN for \$4.95



COMMON CATHODE WITH RH DECIMA. ACTUAL SIZE  
Compact - 10 digits in 3" panel width  
Highly legible - bright red '5' character easily read  
within 10 feet over a wide viewing angle (140°)  
Low power - 125 mW per digit at typical brightness

### 2102-2 MOS 1024 BIT MEMORY (DIP)

FULLY DECODED STATIC RANDOM ACCESS MEMORY  
DIRECTLY TTL COMPATIBLE INPUTS AND OUTPUT  
SINGLE 5V SUPPLY - NO CLOCKS OR REFRESH  
\$4.00 EA. 8 FOR \$27.95

### TTL

7400	\$ .20	7453	\$ .15
74H00	.25	7454	.20
7401	.30	74L54	.25
74H01	.25	74L55	.25
7402	.25	7460	.16
7403	.25	74L71	.25
7404	.25	7472	.40
74H04	.30	74L72	.60
7405	.30	7473	.25
7406	.40	74L73	.75
7408	.30	7474	.45
7410	.15	74H74	.75
7413	.75	7475	.80
7417	.40	7476	.55
7420	.20	74L78	.70
74L20	.30	7480	.50
74H20	.30	7483	.70
74H22	.30	7489	3.00
7430	.15	7490	1.00
74H30	.30	7492	.45
74L30	.30	7493	1.00
7440	.20	7495	.65
74H40	.30	74L95	1.00
7442	1.00	74107	.25
7447	1.50	74145	1.25
7450	.15	74180	1.00
74H50	.30	74193	1.50
7451	.20	74195	.65
74H51	.25		

### NEW!



FULL WAVE BRIDGE RECTIFIERS  
25 AMP 500 PIV  
EACH \$2.00 10 FOR \$16.50

### CD-2 COUNTER KIT

Unit includes board, 7490, 7475, quad  
latch, 7447 seven-segment driver, and  
RCA DR2010.



COMPLETE KIT \$10.95  
FULLY ASSEMBLED \$15.00  
Boards can be supplied separately at  
\$2.50 per digit.

### NPN TO3 POWER TRANSISTORS

410 (RCA) 200V - 10A  
2N3772 70V - 30A (max.)  
Each \$1.75 10 for \$15.00

2N3055 Transistor (power): PD-115W  
VCE-60V; HFE-50; FT-30K; Case TO-3  
Each \$1.15 10 pak \$6.95

## See the bargains at our YEAR-END SALE!

FREE!! CT5001  
With \$25.00 prepaid order  
4 Function, 12 Digit Calculator IC  
With Data

All IC's are new and fully-tested.  
Leads are plated with gold or solder.  
Orders for \$5 or more will be shipped  
prepaid. Add 55¢ for handling and  
postage for smaller orders; residents  
of California add sales tax. IC orders  
are shipped within 2 workdays-kits  
are shipped within 10 days of receipt  
of order. \$10 minimum on C.O.D.'s

Mail Orders to: Phone:  
P.O. Box 41778 (916) 334-2161  
Sacramento, CA TWX:  
95841 910-367-3521

## BABYLON ELECTRONICS

MONEY BACK GUARANTEE ON ALL GOODS!  
SEND FOR FREE FLYER LISTING 100's OF  
MONEY-SAVING BARGAINS!

### Specials DIP TRIMMER



-12 turn trimpots  
which plug into  
a DIP socket  
-5K and 200K  
-1/2" x 1/2" x 1/2"  
-4 leads spaced  
.3" x .2"

Each \$ .65 10 for \$4.95

### MEMORY CHIPS

8223 PROM  
8 BIT-32 WORD  
MEMORY

\$3.00 EACH 10 FOR \$29.00  
WE PROGRAM FOR \$5.00 EACH

82S129 SIGNETIC  
1024 BIT-256/4  
FIELD PROGRAMMABLE  
{WE WILL NOT PROGRAM}  
EACH \$5.00 8 FOR \$34.95

### TRANSISTOR

2N3904 - HEP3E  
TO92 PLASTIC - NPN  
300 MW - 60V - 8100-300  
NEW - FAIRCHILD - MARKED

EACH \$ .15 10 FOR \$1.00

For  
faster  
service  
  
USE  
ZIP  
CODE  
  
on  
all  
mail

### OPTICALLY COUPLED ISOLATOR

Gallium Arsenide diode light source optically coupled to silicon NPN photo transistor. Mini dip package.

#SOC \$1.00 6/\$5.00

### 480 AMP THYRISTOR (SCR)

Perfect for control of electric cars, hi current battery charging, plating, etc.

480 amps 200 PIV \$20 6/\$1.00

### POWER SUPPLY KIT

Puts out 24-12-6 volt DC 2 amps. Includes xfmr, line cord, filter, silicon bridge.

#PK-2B \$9.00

### B & L HELIUM NEON GAS LASER

Fully assembled, runs on 115 volts AC. Less Laser tube \$15.00

### POWER AMP TRANSFORMER \$9.00

115 volts input, output of 96 VCT 2 amps. \$9.00 each 3/\$25

1N1131 Sil. Signal Diode 0.3 amp.	
1500 PIV	2/\$1.00
2N2222 (HEP 555)	8/\$1.00
1103A 1024 bit RAM	\$2.50 each 5/\$10
MC 1440G Sense Amp	2/\$1.00


*Meshna* SURPLUS  
ELECTRONIC  
MATERIAL  
P.O. Box 62  
19 ALLERTON STREET  
E. LYNN MASS. 01904

Circle 109 on reader service card

### COMPUTER BOARD SPECIALS



R9121

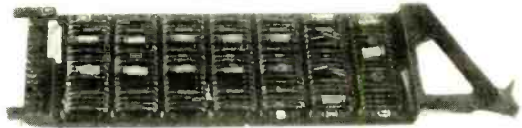

R9082



R9380

We have several sets of HONEYWELL computer boards that are a great source of parts, such as transistors, diodes, capacitors, heat sinks, SCRs, trimpots, precision resistors and capacitors etc. The 3 different numbers above represent real value, and provide a real inventory of parts.

STOCK NO.R9121 2 boards 4"x12" \$1.50 8/5.00  
STOCK NO.R9082 2 boards 4"x13" \$1.50 8/5.00  
STOCK NO.R9380 3 boards 5 1/2"x5 1/2" \$2.00 9/5.00

Include sufficient postage. Excess is refunded. Send for new Fall Catalog 15, our largest yet. MINIMUM ORDER \$5.00



## DELTA ELECTRONICS CO.

BOX 1, LYNN, MASSACHUSETTS 01903  
Phone (617) 388-4705

Circle 110 on reader service card



**5% OFF ON ORDERS OVER \$50.00**  
**10% OFF ON ORDERS OVER \$100.00**  
**15% OFF ON ORDERS OVER \$250.00**

TTL			
7400	\$.14	7451	.17
7401	.16	7453	.17
7402	.15	7454	.17
7403	.16	7460	.17
7404	.19	7461	.35
7405	.19	7465	.35
7406	.35	7470	.30
7407	.35	7472	.30
7408	.18	7473	.35
7409	.19	7474	.35
7410	.16	7475	.57
7411	.25	7476	.39
7413	.55	7483	.79
7416	.35	7485	1.10
7417	.35	7486	.40
7420	.16	7489	2.48
7422	.26	7490	.59
7423	.29	7491	.97
7425	.27	7492	.71
7426	.26	7493	.60
7427	.29	7494	.94
7430	.20	7495	.79
7432	.23	7496	.79
7437	.35	74100	1.30
7438	.35	74105	.44
7440	.17	74107	.40
7441	.98	74121	.42
7442	.77	74122	.45
7443	.87	74123	.85
7444	.87	74125	.54
7445	.89	74126	.63
7446	.93	74141	1.04
7447	.89	74145	1.04
7448	1.04	74151	.97
7450	.17	74153	.99

**LOW POWER TTL**

74L00	\$.25	74L51	\$.29	75L90	\$.149
74L02	.25	74L55	.33	74L91	1.45
74L03	.25	74L71	.25	74L93	1.69
74L04	.25	74L72	.39	74L95	1.69
74L06	.25	74L73	.49	74L98	2.79
74L10	.25	74L74	.49	74L164	2.79
74L20	.33	74L78	.79	74L165	2.79
74L30	.33	74L85	1.25		
74L42	1.49	74L86	.69		

**HIGH SPEED TTL**

74H00	\$.25	74H21	\$.25	74H55	\$.25
74H01	.25	74H22	.25	74H60	.25
74H04	.25	74H30	.25	74H61	.25
74H08	.25	74H40	.25	74H62	.25
74H10	.25	74H50	.25	74H72	.39
74H11	.25	74H52	.25	74H74	.39
74H20	.25	74H53	.25	74H76	.49

**8000 SERIES**

8091	\$.53	8214	\$1.49	8811	\$.59
8092	.53	8220	1.49	8812	.89
8095	1.25	8230	2.19	8822	2.19
8121	.80	8520	1.16	8830	2.19
8123	1.43	8551	1.39	8831	2.19
8130	1.97	8552	2.19	8836	.25
8200	2.33	8554	2.19	8880	1.19
8210	2.79	8810	.69	8263	5.79
				8267	2.59

**9000 SERIES**

9002	\$.35	9309	\$.79	9601	\$.89
9301	1.03	9312	.79	9602	.79

**CMOS**

4000A	\$.26	4016A	.56	4050A	.59
4001A	.25	4017A	1.19	4066A	.89
4002A	.25	4020A	1.49	4068A	.44
4006A	1.35	4021A	1.39	4069A	.44
4007A	.26	4022A	1.10	4071A	.26
4008A	1.79	4023A	.25	4072A	.35
4009A	.57	4024A	.89	4073A	.39
4010A	.54	4025A	.25	4075A	.39
4011A	.29	4027A	.59	4078A	.39
4011A	.29	4028A	.98	4081A	.26
4012A	.25	4030A	.44	4082A	.35
4013A	.45	4035A	1.27	4528A	1.60
4014A	1.49	4042A	1.47	4585A	2.10
4015A	1.49	4049A	.59		

74C00	\$.22	74C74	\$1.04	74C162	\$2.93
74C02	.26	74C76	1.34	74C163	2.66
74C04	.44	74C107	1.13	74C164	2.66
74C08	.68	74C151	2.61	74C173	2.61
74C10	.35	74C154	3.15	74C195	2.66
74C20	.35	74C157	1.76	80C95	1.35
74C42	1.61	74C160	2.48	80C97	1.13
74C73	1.04	74C161	2.93		

**NOVEMBER SPECIALS**

**CALCULATOR CHIPS**

5738 8 digit multiplexed — five function — chain operation 2 key memory — floating decimal — independent constant — interfaces with led with only digit driver — 9 V batt. oper. 24 pin ..... **\$3.95**

5739 9 digit — 4 function — chain operation — 9V battery operation — 16 sec turn-off 22 PIN DIP ..... **\$3.95**

**CLOCK CHIP**

5311 6 digit multiplexed — 50-60 Hz — BCD and 7 seg out — fast, slow set 12-24 Hr — 28 PIN DIP ..... **\$3.95**

**TIMERS**

555 Multipurpose timer 8 PIN DIP ..... \$ .69

556A Dual 555 14 DIP ..... \$1.29

**TTL (DIP)**

7432	\$.19	7493	\$.49
7448	.89	74107	.33
7475	.45	74121	.35
7490	.49	9601	.75

**POCKET CALCULATOR KIT**

5 function plus constant — addressable memory with individual recall — 8 digit display plus overflow — battery saver — uses standard or rechargeable batteries — all necessary parts in ready to assemble form — instructions included



CALC KIT (WITH BATTERIES) ..... **\$12.95**  
 BATTERIES ONLY (DISPOSABLE) SET ..... **\$2.00**

**9 DIGIT LED DISPLAY FNA 37**

On multiplexed substrate, comm. cathode compatible with all 8 digit calculator chips, 7 segment right hand decimal, red with clear magnifying lens, .12" character, 1 to 4 MA, 1.8 V typ 2 3/8" x 1/4" x 1/16" high ..... **\$3.95**

**VOLTAGE REGULATORS**

309K	TO-3	\$1.00
340T-5V	TO-220	\$1.00
340T-15V	TO-220	\$1.00

**MEMORIES**

1103	\$ 1.29
5203	12.95
5260	.99
5262	3.19

Data sheets on request  
 With order add \$.30 for items less than \$1.00 ea.

**LINEAR CIRCUITS**

300	Pos V Reg (super 723)	TO-5	\$.71
301	Hi Peri Op Amp	mDIP TO-5	.29
302	Volt follower	TO-5	.53
304	Neg V Reg	TO-5	.80
305	Pos V Reg	TO-5	.71
307	Op AMP (super 741)	mDIP TO-5	.26
308	Micro Peri Op Amp	mDIP TO-5	.89
309K	5V 1A regulator	TO-3	1.35
310	V Follower Op Amp	mDIP	1.07
311	Hi peri V Comp	mDIP TO-5	.95
319	Hi Speed Dual Comp	mDIP	1.13
320	Neg Reg 5.2, 12, 15	TO-3	1.19
322	Precision Timer	DIP	1.70
324	Quad Op Amp	DIP	1.52
339	Quad Comparator	DIP	1.58
340K	Pos V reg (5V, 6V, 8V, 12V, 15V, 18V, 24V)	TO-3	1.69
340T	Pos V reg (5V, 6V, 8V, 12V, 15V, 18V, 24V)	TO-220	1.49
372	AF-IF Strip detector	DIP	2.93
373	AM/FM/SSB Strip	DIP	.53
376	Pos V Reg	mDIP	2.42
377	2w Stereo amp	DIP	1.16
380	2w Audio Amp	DIP	1.13
380-B	5w Audio Amp	mDIP	1.52
381	Lo Noise Dual preamp	DIP	1.52
382	Lo Noise Dual preamp	DIP	.71
550	Pres V Reg	DIP	.89
555	Timer	mDIP	.89
556A	Dual 555 Timer	DIP	1.49
560	Phase Locked Loop	DIP	2.48
562	Phase Locked Loop	DIP	2.48
565	Phase Locked Loop	DIP TO-5	2.38
566	Function Gen	mDIP TO-5	2.25
567	Tone Decoder	mDIP	2.66
709	Operational AMPL	TO-5 or DIP	.26
710	Hi Speed Volt Comp	DIP	.35
711	Dual Difference Compar V Reg	DIP	.26
723	V Reg	DIP	.62
739	Dual Hi Peri Op Amp	DIP	1.07
741	Comp Op AMP	mDIP TO-5	.32
747	Dual 741 Op Amp	DIP or TO-5	.71
748	Freq Adj 741	mDIP	.35
1304	FM MulpX Stereo Demod	DIP	1.07
1307	FM MulpX Stereo Demod	DIP	.74
1458	Dual Comp Op Amp	mDIP	.62
1800	Stereo multiplexer	DIP	2.48
LH2111	Dual LM 211 V Comp	DIP	1.70
3900	Quad Amplifier	DIP	.35
7524	Core Mem Sense AMPL	DIP	.71
8038	Voltage contr. osc.	DIP	4.25
8864	9 DIG Led Cath Drvr	DIP	2.25
75150	Dual Line Driver	DIP	1.75
75451	Dual Peripheral Driver	mDIP	.35
75452	Dual Peripheral Driver	mDIP	.35
75453	(351) Dual Periph Driver	mDIP	.35
75491	Quad Seq Driver for LED	DIP	.71
75492	Hex Digit driver	DIP	.80

**MEMORIES**

1101	256 bit RAM MOS	\$ 1.50
1103	1024 bit RAM MOS	3.95
1702A	2048 bit static PROM UV eras.	17.95
2102	1024 bit static RAM	4.25
5203	2048 bit UV eras PROM	17.95
5260	1024 bit RAM	2.49
5261	1024 bit RAM	2.69
5262	2048 bit RAM	5.95
7489	64 bit ROM TTL	2.48
8223	Programmable ROM	3.69
74200	256 bit RAM tri-state	5.90

**CALCULATOR & CLOCK CHIPS**

5001	12 DIG 4 funct fix dec	\$2.49
5002	Same as 5001 exc btry pwr	2.79
5005	12 DIG 4 funct w/mem	2.99
MMS5725	8 DIG 4 funct chain & dec	1.98
MMS5736	18 pin 6 DIG 4 funct	4.45
MMS5738	8 DIG 5 funct K & mem	5.35
MMS5739	9 DIG 4 funct (btry sur)	5.35
MMS5311	28 pin BCD 6 dig mux	4.45
MMS5312	24 pin 1 pps BCD 4 dig mux	3.95
MMS5313	28 pin 1 pps BCD 6 dig mux	4.45
MMS5314	24 pin 6 dig mux	4.45
MMS5316	40 pin alarm 4 dig	5.39

**LED's**

MV10B	Red TO 18	\$.22
MV50	Axial leads	.18
MV5020	Jumbo Vis. Red (Red Dome)	.22
	Jumbo Vis. Red (Clear Dome)	.22
ME4	Infra red diff. dome	.54
MAN1	Red 7 seg. .270"	2.19
MAN2	Red alpha num .32"	4.39
MAN4	Red 7 seg. .190"	1.95
MAN5	Green 7 seg. .270"	3.45
MAN6	.6" high solid seq.	4.25
MAN7	Red 7 seg. .270"	1.19
MAN3	Red 7 seg. .127" straight pins	.29
MAN8	Yellow 7 seg. .270"	3.45
MAN66	.6" high spaced seq.	3.75
MCT2	Opto-iso transistor	.61

**MULTIPLE DISPLAYS**

NSN33	3 digit .12" red led 12 pin fits IC skt.	\$1.79
HP5082	5 digit .11 led magn. lens com. cath	3.49
HP5082	4 digit .11 LED magn. lens comm. cath.	\$3.25
7414	FNA37	
	9 digit 7 seg led RH dec clr. magn. lens	4.95
SP-425-09	9 digit .25" neon direct interface with MOS/LSI, 180 VDC. 7 seg 1.79	

**SHIFT REGISTERS**

MMS5013	1024 bit accum. dynamic mDIP	\$1.75
MMS5016	500/512 bit dynamic mDIP	1.59

**DTL**

930	\$.15	937	.15	949	.15
932	.15	944	.15	962	.15
936	.15	946	.15	963	.15


Satisfaction guaranteed. Shipment will be made via first class mail in U.S., Canada and Mexico within 3 days from receipt of order. Add \$.50 to cover shipping and handling for orders under \$25.00. Minimum order \$5.00. California residents add sales tax.

**INTERNATIONAL ELECTRONICS UNLIMITED**  
 P.O. BOX 1708/ MONTEREY, CA. 93940 USA  
 PHONE (408) 659-3171



# 2 in 1

5" wide x 4" deep x 2 1/2" high

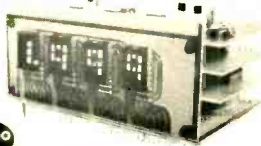

\$75.00

## FREQ. COUNTER DIGITAL MULTIMETER

- MODULES**
- (1) **DECADE COUNTER MODULE** \$24.95  
4 digit 7 seg LED TTL circuitry
  - (2) **TIME BASE-DIVIDER CHAIN MODULE** 18.95  
1MHz crystal controlled oscillator. 6 decade divider. 1MHz, 100KHz, 10KHz, 1KHz, 100Hz, 10Hz, 1Hz outputs. Accuracy better than .001%. No delay constant delay. Full Flight for stopwatch timer application.
  - (3) **FREQUENCY COUNTER GATE MODULE** 12.95  
Schmidt trigger input requires IV. Freq range basic 30MHz. Has 1 stage schottky prescaler extending freq. range to 100MHz.
  - (4) **DIGITAL MULTIMETER MODULE** 20.95  
(See freq counter digital multimeter specs for ranges and speed.)  
(a) DVM module (DC volt & current).  
(b) AC converter OHM module (AC volt & current, OHM)

- SYSTEMS**
- (A) **FREQUENCY COUNTER DIGITAL MULTIMETER** 74.95  
(Also stopwatch, timer, crystal calibrator)  
Consists of module (1), (2), (3), (4a), and (4b).

- 4 DIGIT FREQUENCY COUNTER**  
30MHz range basic with one schottky prescaler extending range to 100MHz.  
Schmidt trigger input requires IV. Freq range basic 30MHz. Has 1 stage schottky

- DIGITAL MULTIMETER**  
11 MEG OHM input impedance on all ranges.  
100% over-range, i.e. 0-1.999 on 0-1.000V range.  
AC & DC voltage range: 0-1.000V, 10.00V, 100.0V, 1000V  
AC & DC current range: 0-1.000mA, 10.00mA, 100.0mA, 1000mA  
OHMS range: 0-100 OHM, 1K, 10K, 100K, 1MEG.  
All measuring & display network of precision resistors.  
Accuracy: ±1 count ±1%.

- (B) **FREQUENCY COUNTER MODULE (1), (2), and (3)** 54.95
- (C) **STOPWATCH-TIMER-TIME BASE & GATE** 42.95  
Consists of module (1) and (2). Time range from 10us in 9999 seconds.  
(166.65 hours) two input gate. Start & stop.

- (D) **POWER SUPPLY** 15.95  
5V & 15V supply for frequency counter digital multimeter, can be used with other modules.

(Systems do not include hardware such as rotary switches, etc.)  
Add \$1.50 Postage and Handling  
ALL MODULES ASSEMBLED AND TESTED

## LIN CORPORATION


17313 Denker Avenue  
Gardena, California 90247

(213) 532-8537

Mail Order and CDD Accepted.

Circle 111 on reader service card

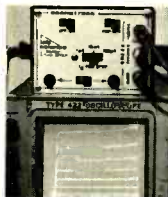NEW color telephones, wiring details, accessories, schematics. Details free. **QUEENS VILLAGE TELEPHONE SUPPLY, P.O. Box 29002, Queens Village, NY 11429**



— econotrace —  
EQUIP YOUR LAB OR SHOP WITH A GENUINE QUALITY SEMICONDUCTOR CURVE TRACER. MEASURES BETA, LEAKAGE, BVCEO, NOISE, MATCH PAIRS, ETC. USES LATEST CMOS CIRCUITRY. COMPLETE WITH BATTERY. COMPARES WITH TRACERS SELLING FOR \$150.00 OR MORE AND EASIER TO OPERATE. SEND CHECK FOR \$39.50 PLUS PSTG. MONEY BACK GUARANTEE.  
**lab science** PO BOX 1972  
BOULDER, COLO. 80302

**ELECTRONIC** components, meters, surplus receivers and test equipment. Catalog free. **E. FRENCH, P.O. Box 249, Aurora, IL 60507**

## CASSETTES

Plain white cassette labels. Norelco cassette cleaners, famous brand cassettes. Send for open reel and cassette discount catalog.

	1-9	10-99	100	1000	10M
Cassette Labels	.65	.02	.015	.01	.006
Norelco Cassette Cleaner	.65	.60	.55	.50	.45
10" Metal, NAB, Used Reel	1.00	1.00	.90	.80	.75
10" Fiberglass used 3/8" Hole	5.00	.50	.40	.35	.30
Scotch Cassette SC90HE	2.72	2.55	2.44		

\*Buy 2, SC90HE, get 1 free.  
Plus Postage by Weight and Zone. Minimum Order \$5.00

**OPEN REEL STEREO TAPE BUYERS!**  
At last! An open reel catalog, including titles, songs, etc. of 95 long play, 2-3 hour albums by American Airlines or Ampex 4 track stereo tapes. Send \$1.00 — and we will also mail you a 140-page Harrison stereo tape guide — so you'll get both for \$1.00 — and this \$1.00 is refundable on your first \$10.00 purchase of open reel stereo tapes at our 30% discount.

We've Got the "Spirit" The Prices And The Address To Prove It  
**Saxitone's Bicentennial Tape Shoppe**  
1776 Columbia Rd., N.W., Wash. D.C. 20009

**LOW-noise resistors**—1/4W, 5%, carbon film from 10—3.3 megohms for 3 1/2¢ each. Fifty of one value for \$1.25. 1N4148 diodes for 6¢. 75¢ postage. Free samples/specifications. **COMPONENTS CENTER—RE**, Box 134, New York, NY 10038

**DYNACO-A-R**, transistors, repairs—boards—& units, speaker service. Send for prices & details: **BEAR ELECTRONICS, 177-R, Hillcrest Road, Mt. Vernon, NY 10552**

# TOUCH TONE® PADS



**NEW \$19.50** Postpaid

COMPLETE WITH DIAGRAM

WESTERN ELECTRIC  
MODEL NO. 35N1A

HIGH STABILITY — L. C. TYPE

REPEATER — COMPUTER  
PHONE — SECURITY — ETC.

SEND \$19.50 TO  
DOLLAR VALUE ELECTRONIC SUPPLY  
20748 PLUMMER STREET  
CHATSWORTH, CALIF. 91311  
CALIF. RESIDENCE ADD 6% TAX

Circle 113 on reader service card

## CB SPECIALS—R.F. DRIVERS—R.F. POWER OUTPUTS—FETS

2SC481	1.85	2SC767	15.75	2SC866	5.85	2SC1449-1	1.60	40081	1.50
2SC482	1.75	2SC773	.85	2SC1013	1.50	2SC1475	1.50	40082	3.00
2SC495	1.10	2SC774	1.75	2SC1014	1.50	2SC1678	5.75	40581	3.70
2SC502	3.75	2SC775	2.75	2SC1017	1.50	2SC1679	5.75	SK3046	2.15
2SC517	4.75	2SC776	3.00	2SC1018	1.50	2SC1728	2.15	SK3047	3.75
2SC614	3.80	2SC777	4.75	2SC1173	1.25	2SC1760	2.15	ST2095	3.50
2SC615	3.90	2SC778	3.25	2SC1226A	1.25	2SC1816	5.50	SK3048	3.25
2SC616	4.15	2SC797	2.50	2SC1237	4.50	2SC1908	7.70	SK3049	4.75
2SC617	4.25	2SC798	3.10	2SC1239	3.50	2SC1957	3.50		
2SC699	4.75	2SC781	3.00	2SC1243	1.50	2SF8	3.00	2SK19	1.75
2SC710	.70	2SC789	1.00	2SC1306	4.75	HEP-S 3001	3.25	2SK30	1.00
2SC711	.70	2SC796	3.15	2SC1306-1	4.90	2SD235	1.00	2SK33	1.20
2SC735	.70	2SC799	4.25	2SC1307	5.75	MRF8004	3.00		
2SC756	3.00	2SC802	3.75	2SC1307-1	6.00	4004	3.00	3SK40	4.50
2SC765	9.50	2SC803	4.00	2SC1377	5.50	4005	3.00	3SK45	4.50
2SC766	10.15	2SC839	.85	2SC1449	3.50	40080	1.25	3SK49	4.50

## JAPANESE TRANSISTORS

2SA52	.60	2SB187	.60	2SC458	.70	2SC815	.75	2SC1569	1.25
2SA316	.75	2SB235	1.75	2SC460	.70	2SC828	.75	2SC1756	1.25
2SA473	.75	2SB303	.65	2SC478	.80	2SC829	.75		
2SA483	1.95	2SB324	1.00	2SC491	2.50	2SC830	1.60	2SD30	.95
2SA489	.80	2SB337	2.10	2SC497	1.60	2SC839	.85	2SD45	2.00
2SA490	.70	2SB367	1.60	2SC515	.80	2SC845	.65	2SD65	.75
2SA505	.70	2SB370	.65	2SC535	.95	2SC1010	.80	2SD68	.90
2SA564	.50	2SB405	.85	2SC536	.65	2SC1012	.80	2SD72	1.00
2SA628	.65	2SB407	1.65	2SC537	.70	2SC1051	2.50	2SD88	1.50
2SA643	.85	2SB415	.85	2SC563	2.50	2SC1061	1.65	2SD151	2.25
2SA647	2.75	2SB461	1.25	2SC605	1.00	2SC1079	3.75	2SD170	2.00
2SA673	.85	2SB463	1.65	2SC620	.80	2SC1096	1.20	2SD180	2.75
2SA679	3.75	2SB471	1.75	2SC627	1.75	2SC1098	1.15	2SD201	1.95
2SA682	.85	2SB474	1.50	2SC642	3.50	2SC1115	2.75	2SD218	4.75
2SA699	1.30	2SB476	1.25	2SC643	3.75	2SC1166	.70	2SD300	2.50
2SA699A	1.75	2SB481	2.10	2SC644	.70	2SC1170	4.00	2SD313	1.10
2SA705	.55	2SB492	1.25	2SC681	2.50	2SC1172B	4.25	2SD315	.75
2SA815	.85	2SB495	.95	2SC684	2.10	2SC1209	.55	2SD318	.95
2SA816	.85	2SB507	.90	2SC687	2.50	2SC1213	.75	2SD341	.95
		2SB511	.70	2SC696	2.35	2SC1226	1.25	2SD350	3.25
				2SC712	.70	2SC1243	1.50	2SD352	.80
2SB22	.65			2SC713	.70	2SC1293	.85	2SD380	5.70
2SB54	.70	2SC206	1.00	2SC732	.70	2SC1308	4.75	2SD389	.90
2SB56	.70	2SC240	1.10	2SC733	.70	2SC1347	.80	2SD390	.75
2SB77	.70	2SC261	.65	2SC733	.70	2SC1383	.75	2SD437	5.50
2SB128	2.25	2SC291	.65	2SC739	.70	2SC1383	.75	2SD437	5.50
2SB135	.95	2SC320	.75	2SC756	2.00	2SC1409	1.25		
2SB152	4.50	2SC352	.75	2SC762	1.90	2SC1410	1.25		
2SB173	.55	2SC353	.75	2SC783	1.00	2SC1447	1.25		
2SB175	.55	2SC371	.70	2SC784	.70	2SC1448	1.25		
2SB178	1.00	2SC372	.70	2SC785	1.00	2SC1507	1.25		
2SB186	.60	2SC394	.70	2SC793	2.50	2SC1509	1.25		

## POWER-TRANSISTORS HIGH-VOLT. TV. TYPE

BU204	1300V	3.90	BU207	1300V	5.40	2SC1172B	1100V	4.25
BU205	1500V	4.70	BU208	1500V	6.25	2SC1308	1100V	4.95
BU206	1700V	5.90	2SC1170	1100V	4.00	2SC1325	1100V	4.95

## OEM SPECIALS

1N270	.10	2N960	.55	2N2219A	.30	2N2913	.75	2N3740	1.00	2N4401	.20
1N914	.10	2N962	.40	2N2221	.25	2N2914	1.20	2N3771	1.75	2N4402	.20
		2N967	.50	2N2221A	.30	2N2916A	3.65	2N3772	1.90	2N4403	.20
				2N2222	.25	2N3019	.50	2N3773	3.00	2N4409	.20
2N173	1.75	2N1136	1.35	2N2222A	.30	2N3053	.30	2N3819	.32	2N4410	.25
2N178	.90	2N1142	2.25	2N2222A	.30	2N3054	.70	2N3823	.70	2N4416	.75
2N327A	1.15	2N1302	.25	2N2270	.40	2N3055	.75	2N3856	.20	2N4441	.85
2N334	1.20	2N1305	.30	2N2322	1.00	2N3227	1.00	2N3866	.85	2N4442	.90
2N336	.90	2N1377	.75	2N2323	1.00	2N3247	3.40	2N3903	.20	2N4443	1.20
2N338A	1.05	2N1420	.20	2N2324	1.35	2N3250	3.00	2N3904	.20	2N4852	.55
2N398B	.90	2N1483	.95	2N2325	2.00	2N3375	6.50	2N3905	.20	2N5061	.30
2N404	.30	2N1540	.90	2N2326	2.85	2N3393	3.80	2N3906	.25	2N5064	.50
2N443	1.75	2N1543	2.70	2N2327	3.80	2N3394	.17	2N3925	3.75	2N5130	.20
2N456	1.10	2N1544	.80	2N2328	4.20	2N3394	.17	2N3954A	3.75	2N5133	.15
2N501A	3.00	2N1549	1.25	2N2329	4.75	2N3414	.17	2N3955	2.45	2N5198	3.75
2N508A	4.05	2N1551	2.50	2N2368	.25	2N3415	.19	2N3957	1.25	2N5294	.50
2N555	.45	2N1552	3.25	2N2369	.25	2N3416	.19	2N3958	1.20	2N5296	.50
2N652A	.85	2N1554	1.25	2N2484	.32	2N3417	.20	2N3959	1.25	2N5306	.20
2N677C	6.00	2N1557	1.15	2N2712	.18	2N3442	1.85	2N3958	1.20	2N5306	.20
2N706	.25	2N1560	2.80	2N2894	.40	2N3553	1.50	2N4037	.60	2N5354	.20
2N706B	.40	2N1605	.35	2N2903	3.30	2N3563	.20	2N4093	.85	2N5354	.20
2N711	.50	2N1613	.30	2N2904	.25	2N3565	.20	2N4124	.20	2N5369	.20
2N711B	.60	2N1711	.30	2N2904A	.30	2N3638	.20	2N4126	.20	2N5400	.40
2N718	.25	2N1907	4.10	2N2905	.25	2N3642	.				

**Wow!**  
INCREDIBLE  
PRICES

**BUY ANY 10  
TAKE 15%  
BUY 100  
TAKE 25%**



SN7400	\$.16	SN7462	\$.22
SN7401	\$.16	SN7470	\$.29
SN7402	\$.16	SN7471	\$.29
SN7403	\$.16	SN7472	\$.29
SN7404	\$.19	SN7473	\$.36
SN7405	\$.19	SN7474	\$.36
SN7406	\$.35	SN7475	\$.59
SN7407	\$.35	SN7476	\$.39
SN7408	\$.19	SN7477	\$.52
SN7409	\$.19	SN7480	\$.52
SN7410	\$.16	SN7481	\$.99
SN7411	\$.25	SN7482	\$.99
SN7413	\$.59	SN7483	1.25
SN7414	1.65	SN7485	1.25
SN7416	\$.34	SN7486	\$.37
SN7417	\$.34	SN7488	3.15
SN7420	\$.16	SN7489	2.45
SN7412	\$.45	SN7490	\$.59
SN7423	\$.29	SN7491	1.10
SN7425	\$.29	SN7492	\$.59
SN7426	\$.16	SN7493	\$.59
SN7427	\$.29	SN7494	\$.59
SN7430	\$.16	SN7495	\$.79
SN7432	\$.25	SN7496	\$.79
SN7433	\$.49	SN74100	1.40
SN7437	\$.34	SN74104	\$.44
SN7438	\$.16	SN74105	\$.44
SN7440	\$.16	SN74106	\$.52
SN7441	1.00	SN74107	\$.44
SN7442	\$.70	SN74108	\$.89
SN7444	1.25	SN74112	\$.89
SN7445	\$.45	SN74113	\$.89
SN7446	1.19	SN74114	\$.89
SN7447	\$.99	SN74121	\$.49
SN7448	\$.99		
SN7450	\$.16		
SN7451	\$.17		
SN7452	\$.17		
SN7453	\$.17		
SN7454	\$.17		
SN7455	\$.22		
SN7460	\$.17		

SN74122	\$.48
SN74123	\$.85
SN74125	\$.99
SN74126	\$.59
SN74132	1.75
SN74140	2.10
SN74145	1.05
SN74148	2.25
SN74150	\$.98
SN74151	\$.75
SN74153	\$.90
SN74154	1.35
SN74155	\$.95
SN74156	\$.95
SN74157	\$.95
SN74158	\$.95
SN74160	1.35
SN74161	1.25
SN74163	1.35
SN74164	1.50
SN74165	1.50
SN74166	1.50
SN74173	1.45
SN74174	1.39
SN74175	1.30
SN74176	1.20
SN74177	1.20
SN74180	2.98
SN74182	\$.74
SN74185	1.98
SN74190	1.40
SN74191	1.40
SN74192	1.25
SN74193	1.25
SN74194	1.20
SN74195	\$.85
SN74196	1.80
SN74197	\$.90
SN74199	1.75
SN74200	4.95

**9-FUNCTION, 8-DIGIT MEMORY CALCULATOR KIT**

It's the easiest multi-function kit today!  
KIT INCLUDES: case, 22-key keyboard kit, ON-OFF switch (part of keyboard), PC board, driver and memory calculator chips, 9-digit "bubble" magnifier LED array, array cable, AC adapter jack & wires, battery case, 6 battery card display, instruction and pictorial step-by-step construction booklet. AC/DC too!



**\$19.95**

**"QUAD" TAPE DECK BY TELEDYNE PACKARD-BELL**

Other features: 4-program indicator lights, automatic or manual program change, push-button channel selector switch, built-in triggering switch that enables you to automatically use 8-track or quad tapes; heavy-duty flywheel for WOW & FLUTTER PROOF sound; humping front panel tape door mounting front panel flange. Heavy duty cool-proof 115 VAC motor. Requires external 12 VDC supply, for all electronics. Includes schematic, hookups, cables. Size: 6 1/2 x 6 1/2 x 3 1/2". IT'S READY TO GO!



**\$16.95**  
DOUBLE MEMORY  
Percent. Constant.  
Display Restore  
4-Function  
Arithmetic  
22 KEYS!

**RAYTHEON-RCA NATIONAL SIGNETICS LINEAR IC'S**

Type	Sale		
LM300	\$.69	LMS62	2.50
LM301	\$.29	LM565	2.50
LM302	\$.69	LM566	2.50
LM303	\$.79	LM567	2.50
LM305	\$.89	LM702	.49
LM308	1.05	LM703	.41
LM309H	1.05	LM703M	.41
LM309K	1.50	LM705	.29
LM310	1.10	LM710	.25
LM311	\$.99	LM711	.29
LM318	1.75	LM723	.61
LM319	1.19	LM733	1.75
LM320*	1.25	LM741	.31
LM322	1.85	LM741CV	.31
LM324 (Q)	1.25	LM747 (D)	.31
LM339 (Q)	1.45	LM748	.35
LM340*	2.50	LM753	1.79
LM341*	1.75	LM758 (D)	.69
LM350*	1.05	LM1458	.99
LM370	1.05	LM1800	3.50
LM371	1.05	CA3026	\$.59
LM373	1.95	CA3045	\$.59
LM374	1.95	CA3054	\$.59
LM376	1.95	CA3085	\$.59
LM377	2.50	CA3082	\$.59
LM380-8	1.10	LM3900	\$.49
LM380	1.39	RC4136 (Q)	1.95
LM381	1.69	RC495	2.50
LM382	1.69	LM4200	2.10
LM531	1.95	LM750	.59
LM532	1.95	LM7521	.59
LM533	1.95	LM7522	.59
LM555	.88	LM7523	.59
LM558	2.50	LM7525	.59
LM559 (D)	.69	LM7528	.59
LM560	2.50	LM7529	.59
LM561	2.50	LM7535	.59

**4 1/2 DIGIT DIGITAL VOLTMETER DVM CHIP**

Type MM5330 by National utilizes P channel low-threshold enhancement mode devices and ion implanted depletion mode devices. Provides logic circuit for 4 1/2 digit DVM. To 400 KHz operation. TTL compatible. With instruction sheets and diagram on "how-to-build a 4 1/2 digit DVM". Ideal with our Lironix 1/2" single, 1 1/2" and dual digit. 16-pin DIP.



**\$14.95**

CLOCK CHIPS ON A "DIP"	MM5311	6-digit 28-Pin	\$5.50
	MM5312	6-digit 28-Pin	5.50
	MM5313	6-digit 28-Pin	5.50
	MM5316	6-digit 40-Pin, alarm	5.50
	MM5316-A	no alarm	3.95

**4-DIGIT AM-PM "PANEL FLUORESCENT CLOCK PANEL" \$9.99**

YOU ASKED FOR IT! Found only at Poly Paks at this low price! It's ONLY 1 3/4" x 1 3/16" x 3/8" deep panel. Designed specifically for our MM-5316 fluorescent driving clock chip. Indicates 4-digits, AM-PM, pulsating second indicator, requires minimum of parts to build. Color: BLUE-GREEN. Requires RED or GREEN filters. Character height: 0.5". Filament voltage is 1.75 VAC or DC @ 160 mAs. Anode voltage 250 @ 250 microamps per segment. Includes schematic, clock construction diagrams, P.C. board layouts specs. A DIGITAL CLOCK BUILDER'S SPECIAL.



TUNG-SOL D2004

**POSTAGE STAMP MOBILE MIKE SPKR \$1.98**

This unit is not advertised anywhere! Made for Motorola Communications at the original cost of \$4.60 each (for insertion in their Walkie Talkie Program). It's a 60-ohm imp MIKE. It's an excellent speaker too, covering broad range in sound. Extremely well-made.



**NATIONAL LM-340T VR's \$1.75 Each**

Type	Volt
LM-340-08T	8V
LM-340-08T	8V
LM-340-08T	8V
LM-340-13T	13V
LM-340-13T	13V
LM-340-24T	24V

**"BLASTAWAY" ON IN4000 RECTIFIER PRICES**

Type	PIV	Sale
IN4001	50 10	for 45c
IN4002	100 10	for 55c
IN4003	200 10	for 65c
IN4004	400 10	for 75c
IN4005	600 10	for 85c
IN4006	800 10	for 95c
IN4007	1000 10	for 1.29

**INDUSTRIAL SPEED CONTROL \$4.95**

A \$30 item from G.E. Model 533A (made for Aerox) that controls home, shop and industrial lighting too! A very elaborate circuit with controlling many electrical and electronic devices. Easily controls speeds of electric drills, brush type motors, etc. 115vac, rated at 1100 watts. With variable speed or dimming control in heavy-duty aluminum case. 3 x 2 3/4 x 2. With diagram and hookups.



**PROGRAMMABLE TIMER DELAYS UP TO 5 DAYS \$4.95**

XR-2340 14-pin DIP Consists of a self-contained 8-bit programmable binary counter, oscillator, and controlled flip-flop. 4V to 15V supply. Temp. and power supply stability outperforms all others. Power only 12 mW @ 4V. Programmable capability 256 steps, 8 separate outputs, one for each counter.



**'BEEPER' AND 'DATER' CLOCK ON THE CHIPS**

Imagine a chip (MK50250) of alarm, date of the month 'Beeper' and audible alarm. All others are external. It also features internal brightness control. The CT7001 requires external triggering. Requires external triggering. Hours, AM and PM.



**MICROPROCESSORS! ROMS! RAMS! MEMORIES!**

Timer	555	2 for \$1
OR	558	3 for \$1
Dual 741		
8008 Microprocessor	\$29.95	
8080 Super 8008	\$50.00	
2101 256 bit RAM	3.95	
1103 1024 bit RAM	2.95	
MM5260 1024 RAM	2.95	
MM5262 2048 bit RAM	6.50	
2513 Character generator	12.50	
MM5203 Erasable PROM	14.95	
MM5202Q Erasable PROM	14.95	
1702A Erasable PROM	19.95	
8223 Programmable ROM	2.95	

**LED Revolution! 5 for \$1**

**MONSANTO! XCITON! LITRONIX! OPCOA!**

3.40x.260	2.40x.200
Jumbo	Medium
Red	Red
Green	Yellow
Yellow	Green
Clear	Clear

Micro (Axial) MV-50 style	2.10x.125
MV-50 Clear	10 for \$1.
MV-55 Red	6 for \$1.

**7-SEGMENT READOUT SALE!**

Up to 20 mls per seg. at 5V.	MAN-1			
All fit into 14-pin IC socket.				
Type	Size	Color	Sale	3 for
MAN-1	.27	Red	\$2.50	\$6.00
MAN-3MA	.12	Red	.69	2.00
MAN-4AB	.27	Red	1.95	5.00
MAN-5	.27	Green	1.50	4.00
MAN-7	.27	Red	1.00	2.50
MAN-8	.27	Yellow	1.50	4.00

**Fabulous POLY PAKS**

**BARREL SALE**

25 BARRELS PURCHASED FOR THIS SALE! BUY 'EM FROM THE "BARREL" AND SAVE!

Your choice of any kit \$1.98

BARREL KIT #1: 75 for SN7400 DIP IC'S \$1.98	BARREL KIT #2: 75 for LINEAR OP AMPS \$1.98	BARREL KIT #3: 100 for 1N4148/814 SWITCHING DIODES \$1.98	BARREL KIT #4: 100 for 1N4000 series. May include 25, 50, 100, 200, 400, 600, 800 and 1000V \$1.98	BARREL KIT #5: 40 for SCRS, TRIACS, QUADRACS \$1.98	BARREL KIT #6: 40 for 1N4000 series. May include 25, 50, 100, 200, 400, 600, 800 and 1000V \$1.98	BARREL KIT #7: 40 for 1N4000 series. May include 25, 50, 100, 200, 400, 600, 800 and 1000V \$1.98	BARREL KIT #8: 40 for 1N4000 series. May include 25, 50, 100, 200, 400, 600, 800 and 1000V \$1.98	BARREL KIT #9: 40 for 1N4000 series. May include 25, 50, 100, 200, 400, 600, 800 and 1000V \$1.98	BARREL KIT #10: 40 for 1N4000 series. May include 25, 50, 100, 200, 400, 600, 800 and 1000V \$1.98	BARREL KIT #11: 40 for 1N4000 series. May include 25, 50, 100, 200, 400, 600, 800 and 1000V \$1.98	BARREL KIT #12: 40 for 1N4000 series. May include 25, 50, 100, 200, 400, 600, 800 and 1000V \$1.98	BARREL KIT #13: 40 for 1N4000 series. May include 25, 50, 100, 200, 400, 600, 800 and 1000V \$1.98	BARREL KIT #14: 40 for 1N4000 series. May include 25, 50, 100, 200, 400, 600, 800 and 1000V \$1.98	BARREL KIT #15: 40 for 1N4000 series. May include 25, 50, 100, 200, 400, 600, 800 and 1000V \$1.98	BARREL KIT #16: 40 for 1N4000 series. May include 25, 50, 100, 200, 400, 600, 800 and 1000V \$1.98	BARREL KIT #17: 40 for 1N4000 series. May include 25, 50, 100, 200, 400, 600, 800 and 1000V \$1.98	BARREL KIT #18: 40 for 1N4000 series. May include 25, 50, 100, 200, 400, 600, 800 and 1000V \$1.98	BARREL KIT #19: 40 for 1N4000 series. May include 25, 50, 100, 200, 400, 600, 800 and 1000V \$1.98	BARREL KIT #20: 40 for 1N4000 series. May include 25, 50, 100, 200, 400, 600, 800 and 1000V \$1.98	BARREL KIT #21: 40 for 1N4000 series. May include 25, 50, 100, 200, 400, 600, 800 and 1000V \$1.98	BARREL KIT #22: 40 for 1N4000 series. May include 25, 50, 100, 200, 400, 600, 800 and 1000V \$1.98	BARREL KIT #23: 40 for 1N4000 series. May include 25, 50, 100, 200, 400, 600, 800 and 1000V \$1.98	BARREL KIT #24: 40 for 1N4000 series. May include 25, 50, 100, 200, 400, 600, 800 and 1000V \$1.98	BARREL KIT #25: 40 for 1N4000 series. May include 25, 50, 100, 200, 400, 600, 800 and 1000V \$1.98	BARREL KIT #26: 40 for 1N4000 series. May include 25, 50, 100, 200, 400, 600, 800 and 1000V \$1.98	BARREL KIT #27: 40 for 1N4000 series. May include 25, 50, 100, 200, 400, 600, 800 and 1000V \$1.98	BARREL KIT #28: 40 for 1N4000 series. May include 25, 50, 100, 200, 400, 600, 800 and 1000V \$1.98	BARREL KIT #29: 40 for 1N4000 series. May include 25, 50, 100, 200, 400, 600, 800 and 1000V \$1.98	BARREL KIT #30: 40 for 1N4000 series. May include 25, 50, 100, 200, 400, 600, 800 and 1000V \$1.98	BARREL KIT #31: 40 for 1N4000 series. May include 25, 50, 100, 200, 400, 600, 800 and 1000V \$1.98	BARREL KIT #32: 40 for 1N4000 series. May include 25, 50, 100, 200, 400, 600, 800 and 1000V \$1.98	BARREL KIT #33: 40 for 1N4000 series. May include 25, 50, 100, 200, 400, 600, 800 and 1000V \$1.98	BARREL KIT #34: 40 for 1N4000 series. May include 25, 50, 100, 200, 400, 600, 800 and 1000V \$1.98	BARREL KIT #35: 40 for 1N4000 series. May include 25, 50, 100, 200, 400, 600, 800 and 1000V \$1.98	BARREL KIT #36: 40 for 1N4000 series. May include 25, 50, 100, 200, 400, 600, 800 and 1000V \$1.98	BARREL KIT #37: 40 for 1N4000 series. May include 25, 50, 100, 200, 400, 600, 800 and 1000V \$1.98	BARREL KIT #38: 40 for 1N4000 series. May include 25, 50, 100, 200, 400, 600, 800 and 1000V \$1.98	BARREL KIT #39: 40 for 1N4000 series. May include 25, 50, 100, 200, 400, 600, 800 and 1000V \$1.98	BARREL KIT #40: 40 for 1N4000 series. May include 25, 50, 100, 200, 400, 600, 800 and 1000V \$1.98
--	---	---	--	---	---	---	---	---	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**LITRONIX "JUMBO'S"**

Single size: 1 x 3/4 x 5/16				
Dual size: .8 x .9 x .29				
7-Segment, 25-mils per segment				
Type	Size	Color	Sale	3 for
721D	.5	Red	\$5.95	\$15.00
727E	.5	Red	5.95	15.00
746F	.6	Red	3.95	11.00
747	.6	Red	3.95	11.00

D-Plus or Minus 1 plus a digit (1 1/2 digits)  
D-Dual digits  
F-Plus or Minus 1

Terms: add postage. Rated: net 30  
Phone Orders: Wakefield, Mass. (617) 245-3829  
Retail: 16-18 Del Carmine St., Wakefield, Mass.  
(off Water Street) C.O.D.'S MAY BE PHONED

20c CATALOG on Fiber Optics, IC's, Semi's, Parts  
MINIMUM ORDER — \$4.00

**P**

# SUPER BUYS!

FAMOUS MAKE, NEW JOBBER-BOXED TUBES  
80% OFF LIST

1B3	5 for \$5.00	6HA5	5 for \$4.80
1V2	5 for \$3.00	6HB7	5 for \$4.85
2AV2	5 for \$3.95	6HQ5	5 for \$6.35
3A3	5 for \$5.05	6HV5	5 for \$11.80
3AT2	5 for \$4.90	6JC6	5 for \$5.65
3GK5	5 for \$4.85	6JE6	5 for \$11.15
3HA5	5 for \$4.80	6JS6	5 for \$9.30
3HM5	5 for \$4.80	6JL8	5 for \$5.55
4BZ6	5 for \$4.70	6KA8	5 for \$6.15
5GH8	5 for \$5.90	6KE8	5 for \$7.65
6AX4	5 for \$5.05	6KM6	5 for \$11.25
6AY3	5 for \$5.05	6KN6	5 for \$9.85
6BK4	5 for \$9.35	6KT8	5 for \$6.85
6CG3	5 for \$4.95	6KZ6	5 for \$5.15
6CG8	5 for \$5.40	6LB6	5 for \$10.75
6CJ3	5 for \$4.70	6LQ6	5 for \$11.15
6DQ6	5 for \$6.75	8FQ7	5 for \$3.75
6DW4	5 for \$4.70	12BY7	5 for \$4.50
6EA8	5 for \$4.95	12GN7	5 for \$7.00
6EH7	5 for \$4.80	17JZ8	5 for \$4.50
6EJ7	5 for \$4.50	21GY5	5 for \$6.30
6FQ7	5 for \$3.75	23Z9	5 for \$6.00
6GF7	5 for \$6.65	31LQ6	5 for \$10.15
6GH8	5 for \$3.95	33GY7	5 for \$8.05
6GJ7	5 for \$3.40	36MC6	5 for \$11.40
6GM6	5 for \$5.25	38HE7	5 for \$9.20
6GU7	5 for \$5.25	38HK7	5 for \$9.00
6GV6	5 for \$4.35	42KNG	5 for \$9.15

CORDLESS SOLDERING IRON	\$12.95
SONOTONE 8-T CARTRIDGE-NEEDLE	\$ 1.00
BSR TC8S-CARTRIDGE-NEEDLES	\$ 1.00
BSR-SC5MD-EV5540D-CART.-NEEDLE	\$ 1.25
2 SET COUPLER	2 for \$ 3.00
4 Set Coupler	2 for \$ 4.00
VHF-UHF-Splitter—300 Ohm	Ea. \$ 1.49
TUNER CLEANER 8 Oz. Spray Can	Ea. \$ 1.00
ZEN. VOLT TRIP. 212-136	Ea. \$ 4.95
ZEN. CONV. DIODE PAK—212-72	2 for \$ 1.00
YOKE REPL. DY95AC-Y109	\$ 5.95
10-15KV FOCUS RECTIFIERS	\$ 4.50
70% COLOR YOKE (21" CRT)	\$ 4.95
JAP YOKE (GRAB BAG) COLOR	\$ 4.50
50 Assorted Controls	\$ 2.59
50 Assorted Wire Wound Res.	\$ 2.69
100 Ass't'd Resistors (Cut Leads)	\$ 1.19
50 Assorted Disc Cond.	\$ 1.98
25 Assorted Filters (CANS)	\$ 3.95
25 Ass't'd Filters (Axial)	\$ 3.95
6 GLOBAL RES 120 OHM COLD	\$ 2.98
10 Ass't'd Slide Switches	\$ 1.00
20 Ass't'd By-Pass Cond.	\$ 1.00
20 Ass't'd Tube Sockets	\$ 1.00
6 Ass't'd Aligning Tools	\$ 1.00
70% Convergence Assembly	\$ 1.00
90% Convergence Assembly	\$ 1.59
10 HV ANODE LEADS 40KV	\$ 1.19

<b>COLOR FLYBACKS</b>	
PHILCO 32-10132-1	Ea. \$3.95
MAGNAVOX 361461-2L	Ea. \$6.95
RCA—136640	Ea. \$5.95
RCA—137545	Ea. \$5.95

<b>THORD. MEISSNER B/W Yokes</b>	
Y-105 UNIVERSAL MANY CHASSIS	Ea. \$ 7.95
Y-130 ZENITH MANY CHASSIS	Ea. \$ 7.95
70% COLOR CRT BOOSTERS	3 for \$11.00
90% COLOR CRT BOOSTERS	3 for \$11.50

<b>TUNERS—NEW—TUBES—TRANSISTORS</b>	
MOTOR. OPTT399YA 6KZ8-6HA5	\$2.75
SYLV. TRANS. 54-29331-3	\$4.95
SYLV. TRANS. 54-29331-8	\$4.95
RCA—KRK-128	\$4.95
G.I. Par. 6GS7-6HA5	2 for \$5.00
Curt. Math. 6GJ7-6HQ5	2 for \$5.00

**SEND FOR FREE CATALOG**

TUBES UP TO 80% OFF  
MINIMUM ORDER \$25.00

SEND CHECK OR M.O.

**TV TECH SPECIALS**

P.O. BOX 603  
KINGS PARK, L.I., NEW YORK 11754  
PHONE 516-269-0805

**BURGLAR alarm dialing unit automatically calls police. \$29.95. Free literature. S&S SYSTEMS, Box 12375G, North Kansas City, MO 64116**

## PLANS & KITS

**TV ping pong game. Plays through your set's antenna terminals: Plans \$3.25. ARS SYSTEMS, Box 1922, Sunnyvale, CA 94088**

**BUILD that electronic organ you always wanted at a price you can afford. Third edition of "Organ Builder's Guide," pictured product kit line, circuits, block diagrams, design rationale using IC divider and independent generators with diode keying. \$3.00 Postpaid. Also, free brochure on keyboards. DEVTRONIX ORGAN PRODUCTS, Dept. B, 5872 Amapola Drive, San Jose, CA 95129**


**GUITAR synthesizer creates new sounds with your electric guitar. Send \$5.00 for plans to: ELECTRAX, Box 149, Tarzana, CA 91356**

**UNIVERSAL TTL/DTL/CMOS IC tester. Set programming switches; plug in; press to test; errors displayed. Tests 16/14 pin digital IC's! Easy circuit construction with TTL. DS/PCB available. Illustrated info/plans: \$2.50 NORTHSTAR ENGINEERING, 3617 Northchre Drive, Charleston, WV 25302**

**DIGITAL construction plans, design manuals, others. Free info. T. WONG, 103 E. Bway, Dept. 4G, New York, NY 10002**
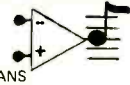
## ELECTRONIC MUSIC SYNTHESIS

- COMPONENTS
- CIRCUITS
- DESIGNS
- KITS AND PLANS



For free info send SASE or 25¢ To:  
CFR ASSOCIATES POB F NEWTON, N. H. 03858

**8008 based system users. We offer game routines, scientific calculator operational routines, interpretive packages and more. Write for details. SOLIDTRONICS, Box 218—R.D. 1, Geneva, NY 14456**

# VISTA


## DIGITAL CROSSHATCH

Gives professional, accurate Color T.V. convergence. Digital IC's coupled with a crystal time-base oscillator provide sync for precise horizontal & vertical lines. Accurate 8 x 7 dot or cross-hatch pattern A.C. power 2 x 3 3/4 x 6 in. Wt. 24 oz. Fits in tool kit.

**COMES COMPLETE WITH ALL PARTS, CASE CRYSTAL AND GUIDE TO ASSEMBLY & USE.**

KIT  
**\$31.95**

COMPLETELY ASSEMBLED  
**\$41.95**

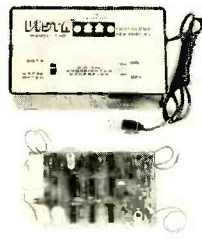

Shipping Prepaid in USA & Canada  
NY State Add Sales Tax  
**PHOTOLUME CORP.**  
118 EAST 28 STREET  
NEW YORK, N.Y. 10018

# LOWEST PRICES IN THE COUNTRY!



MODEL MM  
COMPLETE CLOCK KIT  
ONLY \$22.50

KIT INCLUDES: MM5314 Clock Chip, Power Transformer, easy to follow PC board, 6 0.4" green colour readouts, specially designed plastic case, all resistors, transistors, diodes, capacitors and switches.



MODEL CT  
CASE for CT 7001

Case Includes: PC board with schematic for CT7001, alarm on/off switch and snooze switch  
ONLY \$9.50

QUARTZ  
LED WATCH

- Shows Month, Date, Hour, Minute and Second.
- No moving parts, all Solid-State
- Exclusive Single Button Control
- 14 K Gold Plate
- One Year Fully Warranted

ONLY \$84.50



LED READ OUTS

DL 727	0.5" Common Anode Double Digits Led	\$ 2.80
DL 747	0.6" Common Anode Red	2.20
DL 707	0.3" Common Anode Red	1.50
Fairchild FND 500	0.5" Common Cathode	2.00
Fairchild FND 70	0.25" Common Cathode	.60

FLOURESCENT READOUTS

NEC LD 8132 0.5" Com. Anode 4 digits Multiplex with AM/PM Display. Green colour. Supply voltage 24 volt. (Used in our CT 7001 PC board)

ONLY \$13.50



CLOCK CHIPS

MM 5311	28 Pin	BCD & 7 seg. 6 digits MUX	3.80
MM 5313	28 Pin	1pps BCD & 7 seg 6 digits	3.80
MM 5314	24 Pin	7 seg 6 digits MUX	3.50
MM 5315	28 Pin	BCD & 7 Seg Stopwatch	4.00
MM 5316	40 Pin	Alarm AM/PM Direct Drive	4.50
FND 500 Led			4.50
CT 7001	28 Pin	Alarm, Date AM/PM stopwatch	6.50

IC SOCKETS

Maxix Pins		\$10.00 per 100
14 Pins	Wire wrap or solder	.36
16 Pins	Wire wrap or solder	.38
24 Pins	Wire wrap	1.20
28 Pins	Solder Type	1.00
24 Pins	Solder Type	1.25
40 Pins	Solder Type	1.50

LED LAMPS

Red Colour	\$ .15 ea	\$12.00 per 100
Green Colour	.20 ea	16.00 per 100
Orange Colour	.20 ea	16.00 per 100
Yellow Colour	.20 ea	16.00 per 100
Clear Colour	.20 ea	16.00 per 100
Wide Angle Red	.20 ea	16.00 per 100
Mixed Colour Package		14.00 per 100
Opto-isolator Mini Dip		10 for \$3.00

COMPUTER KEYBOARDS

Modified ACS 11 Output with Decoders		
for Teletype		29.50
Teletype Keyboard without Electronic Parts		19.50

MEMORIES

National 1702A	Erasable Prom		
1.5 pcs.	5.9 pcs.	10.25 pcs.	25 pcs. up
15.50 each	14.50 each	13.50 each	12.50
National 2102-1	1024 Bit Static Ram		
10 pcs.	53.30 each	20 inc.	\$3.00 each
		30 pcs.	\$2.60 each
		50 pcs.	\$2.20 each

LINEAR I.C.

LM 309K	5V 1A Regulator	1.20	1.00
LM 340T	Pos. 1A V. Regulator		
	(5V, 6V, 12V, 15V.)	1.20	1.00
LM 380	2W Audio Amp	1.00	.80
LM 381	Lo Noise Pre Amp	1.20	1.00
LM 555	Timer Min. Dip	.65	.55
LM 556	Dual 555 Timer	1.00	.85
LM 565	Phase Locked Loop	1.80	1.50
LM 567	Form Decoder	1.75	1.50
UA 709	Operational Amp	.25	.20
UA 741	Comp Op Amp	.30	.25
LM 747	Dual 741 Op Amp	.65	.55
LM 1458	Dual Comp Op Amp	.65	.55
LM 3900	Quad Op Amp	.60	.50
DM 8864	9 Digit Led Driver	1.70	1.40
74591	Quad MOS to Led Seg Drivers	.60	.55
75492	HEX MUX to Led Dig Drivers	.60	.55

POWER TRANSFORMER

12 V AC 300MA output Wall Type Adapter		
(Designed for Clock to limited space)		3.50 ea
12V 0.12V or 24V 1 Amp output		2.25 ea
0.0 8V-12V 300MA output		
(For our LD 8051 Fluorescent Tubes)		2.50 ea
0.3V 12V 24V 500 MA output		
(For CT 7001 Drive Ld 8132 Readouts)		2.50 ea
0.15V 160V 150MA output		
(For Gas discharge Readouts)		1.00 ea

MIN. ORDER \$10.00

Send Money Order for Mail Order  
California residents add 6% sales tax.  
Postpaid in Ca. Other states add \$1.00 postage.

**FORMULA INTERNATIONAL INC.**  
12603 CRENSHAW BLVD.  
HAWTHORNE, CA. 90250  
FOR INFORMATION PLEASE CALL  
(213) 679-5162  
BUSINESS HOURS 10-7 MON. - FRI.

**7400N TTL**

SN7400N	16	SN7451N	27	SN74151N	125
SN7401N	16	SN7453N	27	SN74153N	135
SN7402N	21	SN7454N	41	SN74154N	125
SN7403N	16	SN7459A	25	SN74155N	121
SN7404N	21	SN7460N	22	SN74156N	130
SN7405N	24	SN7470N	45	SN74157N	130
SN7406N	16	SN7472N	38	SN74160N	175
SN7407N	45	SN7473N	45	SN74161N	145
SN7408N	25	SN7474N	45	SN74163N	165
SN7409N	25	SN7475N	80	SN74164N	165
SN7410N	30	SN7476N	47	SN74165N	165
SN7411N	30	SN7480N	50	SN74166N	170
SN7412N	42	SN7482N	175	SN74167N	170
SN7413N	85	SN7483N	115	SN74170N	300
SN7414N	70	SN7485N	112	SN74172N	180
SN7416N	43	SN7486N	45	SN74173N	170
SN7417N	43	SN7488N	350	SN74174N	195
SN7418N	25	SN7489N	300	SN74175N	195
SN7420N	21	SN7490N	358	SN74176N	325
SN7421N	59	SN7491N	120	SN74177N	300
SN7422N	37	SN7492N	82	SN74180N	105
SN7425N	43	SN7493N	82	SN74181N	355
SN7426N	31	SN7494N	91	SN74182N	95
SN7427N	37	SN7495N	91	SN74184N	230
SN7428N	42	SN7496N	91	SN74185N	230
SN7430N	26	SN74100N	125	SN74186N	230
SN7432N	31	SN74107N	49	SN74190N	150
SN7437N	47	SN74121N	55	SN74191N	150
SN7438N	40	SN74122N	49	SN74192N	150
SN7439A	25	SN74123N	105	SN74193N	140
SN7440N	21	SN74124N	60	SN74194N	140
SN7441N	110	SN74125N	61	SN74195N	100
SN7442N	108	SN74126N	300	SN74196N	125
SN7443N	105	SN74127N	115	SN74197N	100
SN7444N	110	SN74128N	650	SN74198N	225
SN7445N	110	SN74129N	700	SN74199N	225
SN7446N	115	SN74144N	700	SN74200N	700
SN7447N	89	SN74145N	115	SN74201N	700
SN7448N	99	SN74148N	250	SN74202N	600
SN7450N	26	SN74150N	110	SN74205N	600

20% Discount for 100 Combined 7400's

**CMOS**

CD4001	25	74C100N	65
CD4002	25	74C20N	65
CD4003	25	74C03N	65
CD4006	250	74C035	185
CD4007	25	74C04N	245
CD4009	59	74C02	190
CD4010	59	74C05	150
CD4011	25	74C06	251
CD4012	25	74C047	275
CD4013	47	74C049	79
CD4016	56	74C050	79
CD4017	135	74C051	298
CD4019	55	74C053	298
CD4020	140	74C054	325
CD4022	125	74C066	175
CD4023	25	74C069	45
CD4024	150	74C071	15
CD4025	25	74C081	45
CD4027	89	74C08N	39
CD4028	185	74C09N	55
CD4029	290	74C09N	15

**LINEAR**

LM100H	1500	LM1310N	295
LM106H	250	LM1420N	65
LM117H	375	LM1412N	175
LM121H	70	LM1456C	65
LM300H	80	LM1498N	95
LM301H	3100	LM3800N	105
LM301H 3	100	LM381N	179
LM302H	75	LM382N	235
LM304H	100	NE501K	800
LM305H	95	NE510A	500
LM307CN	35	NE531H	300
LM308H	100	NE536T	600
LM309H	100	NE540L	600
LM309H 1	110	NE540N	79
LM309K	125	NE553	250
LM310H	115	NE555V	49
LM311H	90	NE565H	99
LM311N	90	NE565N	125
LM318CN	150	NE566N	195
LM319N	130	NE567N	125
LM319D	900	NE567V	150
LM320K 5	135	LM703CN	45
LM320K 5.2	135	LM703H	29
LM320K 12	135	LM709N	29
LM320K 15	135	LM710N	29
LM320K 5	1050	LM711N	29
LM324N	180	LM723N	55
LM329N	170	LM723H	55
LM340K 5	195	LM733N	100
LM340K 12	195	LM739N	129
LM340K 15	195	LM741CH	3100
LM340K 24	195	LM741CN	3100
LM340T 5	175	LM741H	39
LM340T 6	175	LM747H	79
LM340T 12	175	LM748H	39
LM340T 15	175	LM748N	39
LM340T 24	175	LM749N	39
LM350N	100	LM1033N	90
LM1035CN	65	LM1035N	119
LM370N	115	LM1035N 140	CA3123
LM370H	115	LM1037N	85

**DATA HANDBOOKS**  
Pin-out & Description of 5400/7400 ICs \$2.95  
Pin-out & Description of 4000 Series ICs \$2.95  
Pin-out & Functional Description of Linear Circuits \$2.95

**6' POWER SUPPLY CORDS** . . . .  
2 CONDUCTORS SPECIAL 3/\$1.00

**THUMBWHEEL SWITCHES**

THUMBWHEEL SWITCH ONLY

Part No.	Description	Price
SW-1	1 Pole, 1 Position	\$0.20
SW-2	2 Pole, 1 Position	\$0.25
SW-3	3 Pole, 1 Position	\$0.30
SW-4	4 Pole, 1 Position	\$0.35
SW-5	5 Pole, 1 Position	\$0.40
SW-6	6 Pole, 1 Position	\$0.45
SW-7	7 Pole, 1 Position	\$0.50
SW-8	8 Pole, 1 Position	\$0.55
SW-9	9 Pole, 1 Position	\$0.60
SW-10	10 Pole, 1 Position	\$0.65

Ordering: Order desired switch or switches and add necessary accessories for your particular application.

**JAMES NOVEMBER SPECIALS**

DIODES		TTL/LINEAR		CLOCK & CALC. CHIPS			
IN4001	50V @ 1 Amp	15 \$1.00	7400 Gate	7 \$1.00	MM5311N	6 Digit	\$2.95
IN4002	100V @ 1 Amp	15 \$1.00	74147 Decoder	79	MM5312N	4 Digit	2.95
IN4003	200V @ 1 Amp	15 \$1.00	7490 Counter	49	MM5313N	6 Digit	2.95
IN4004	400V @ 1 Amp	15 \$1.00	74100 8 Bit Latch	99	MM5314N	6 Digit	2.95
IN4148	Switching	20 \$1.00	74154 Decoder	99	MM5316N	6 Digit Alarm	3.95
			74157 Counter	75	MM5325N	8 Digit 4 Funt.	1.98
			LM301H-LM341H	4 \$1.00	MM5338N	6 Digit 4 Funt.	3.95
			LM324N-Reg 10.5	1.19	MM5338N	8 Digit 5 Funt.	4.95
			LM309H 5V Reg T.O.5	79			
			LM309K 5V Reg T.O.3	99			
			PNP Amp	6 \$1.00			
			NPN RF	6 \$1.00			
			NPN JFt	6 \$1.00			
			MM500H MM501H MM5010H	2 FOR			
			MM5016N	\$1.00			

**PARTS SURVEY**  
I read the letter from Robert Briner in the June issue of R-E about his problem of obtaining parts overseas for projects. I now have nine months experience with several firms and received all the parts I ordered. The time it took to receive the parts varied from firm to firm. Here is a list of my experiences with the firms.

**James Belmont, CA** 7-10 days  
**Electronics**  
**Poly Paks** Lynnfield, MA 2-3 weeks (getting better)  
**International Electronics** Monterey, CA 2-3 weeks  
**Unlimited**  
**Southwest Technical Products** San Antonio, TX 3-4 weeks  
**Mesma Electronics** Lynnfield, MA 2-3 weeks  
**Delta Electronics** Lynnfield, MA 3-4 weeks  
**Solid State Sales** Somerville, MA 3-4 weeks  
**Howard W. Sams & Co.** Indianapolis, IN 7 weeks  
**Alteq Electronics** Dallas, TX 1-1/2 months

**HP-5082-7300**  
3" Dot Matrix type numeric readouts with decoder/line/latch built on the chip. Only 8 pins (ICD in, DP, Latch, +5v ground).  
HP-5082-7300 \$5.95  
HP-5082-7304 \$4.95  
1 1/4" x 1 1/2" XFEMERS P.C. Mount  
They were designed for clock type applications: 110 Vac primary @50Hz. Secondary: 8.10V @ 300mA-500mA  
50 Vac @ 30mA-50mA  
Excellent for miniature power supplies & gas discharge displays.  
SPECIAL \$9.99

**1/16 VECTOR BOARD**  
P-Pattern  
0.1" Hole Spacing

PHENOLIC	68PA 062KXKFP	1.50	6.50	1.72	1.54
EPXY GLASS	68PA 062K	4.50	1.90	3.88	3.24
EPXY GLASS	68PA 062	4.50	8.50	1.56	2.31
EPXY GLASS	68PA 062	4.50	17.00	2.22	3.20
EPXY GLASS	68PA 062C	4.50	17.00	6.80	6.12

**PROTO BOARD-100**  
Here's a low cost, but 10 IC capacity breadboard kit with all the quality of DT Sockets and the best of the Proto Board series - complete down to the screw-in, both and screw-includes.  
2 D1 35S Sockets, 1 DT 35S Bus Strip, 2.5 way binding posts, 4 rubber feet, screws, nuts, bolts, and easy assembly instructions.  
COMPLETE KIT...  
\*Special \$17.95

**DPST C & K ROCKER SWITCH**  
They are rated at 125 Vac @ 5A.  
They are excellent in application such as Microcomputer Panel Switches.  
Dim: 1" x 1" x 1/4" \$0.69

**DISPLAY LEDS**

FND70	Com. Cath.	.250	59
MAN 1	Com. Anod.	.270	\$1.95
MAN 2	5x7 Matrix	.300	3.95
MAN 3	Com. Cath.	.125	39
MAN 4	Com. Cath.	.187	1.95
MAN 7	Com. Anod.	.30	1.50
DL133	Com. Cath.	.125	1.95
DL747	Com. Anod.	.625	1.95

**DISCRETE LEDS**

MV 10	Red	5 \$1.00
MV 10	Red	8 \$1.00
MV 5024	Red	5 \$1.00
MV 5024	Green	4 \$1.00
MV 5024	Yellow	4 \$1.00
MV 5024	Orange	4 \$1.00
MV 50	Red 1/2"	5 \$1.00

**IC SOLDER TAIL - LOW PROFILE (TIN) SOCKETS**

8 pin	1.23	25-49	50-100	1.24	25-49	50-100
14 pin	5.17	16	15	24 pin	5.28	37
16 pin	20	19	18	28 pin	45	44
18 pin	22	23	22	36 pin	60	59
27 pin	39	28	27	40 pin	63	62

**SOLDER TAIL STANDARD (GOLD)**

8 pin	\$3.00	207	24	24 pin	\$ 7.70	63	57
14 pin	35	32	29	28 pin	1.10	100	90
16 pin	38	35	32	36 pin	1.55	140	126
18 pin	52	47	43	40 pin	1.75	159	145

**WIRE WRAP SOCKETS (GOLD) LEVEL 3**

10 pin	\$4.45	41	37	24 pin	\$1.05	95	85
14 pin	39	38	37	28 pin	1.40	125	110
16 pin	43	42	41	36 pin	1.59	145	130
18 pin	75	68	62	40 pin	1.75	155	140

**50 PCS. RESISTOR ASSORTMENTS \$1.75 PER ASS'T.**

ASS'T. 1	5 ea.	10 OHM	12 OHM	15 OHM	18 OHM	22 OHM	27 OHM	33 OHM	39 OHM	47 OHM	56 OHM	1/4 WATT 5% - 50 PCS.
ASS'T. 2	5 ea.	180 OHM	220 OHM	270 OHM	330 OHM	390 OHM	470 OHM	560 OHM	680 OHM	820 OHM	1K	1/4 WATT 5% - 50 PCS.
ASS'T. 3	5 ea.	1.2K	1.5K	1.8K	2.2K	2.7K	3.3K	3.9K	4.7K	5.6K	6.8K	1/4 WATT 5% - 50 PCS.
ASS'T. 4	5 ea.	8.2K	10K	12K	15K	18K	22K	27K	33K	39K	47K	1/4 WATT 5% - 50 PCS.
ASS'T. 5	5 ea.	56K	68K	82K	100K	120K	150K	180K	220K	270K	330K	1/4 WATT 5% - 50 PCS.
ASS'T. 6	5 ea.	390K	470K	560K	680K	820K	1M	1.2M	1.5M	1.8M	2.2M	1/4 WATT 5% - 50 PCS.
ASS'T. 7	5 ea.	2.7M	3.3M	3.9M	4.7M	5.6M						1/4 WATT 5% - 50 PCS.

**PRIME INTEGRATED CIRCUIT ASSORTMENTS**

ASS'T. 8	3 ea.	SN7400	7401	7402	7403	7404	SSI/TTL	\$9.95 ASS'T.
ASS'T. 9	2 ea.	SN7410	7430	7438	7440	7472	MSI/TTL	\$8.95 ASS'T.
ASS'T. 10	2 ea.	SN7415	7475	7476	74180	74191	74193	\$8.95 ASS'T.
ASS'T. 11	2 ea.	CD4001	4002	4011	4012	4013	CMOS	\$9.95 ASS'T.
ASS'T. 12	2 ea.	LM301H	301N	302T	307T	309K	LINEAR	\$10.95 ASS'T.

Satisfaction Guaranteed. \$5.00 Min. Order. U.S. Funds.  
California Residents - Add 6% Sales Tax  
Write for FREE 1975 F Catalog - Data Sheets .25c each

**JAMES**  
P.O. BOX 822, BELMONT, CA. 94002  
PHONE ORDERS - (415) 592-8097

**MICROPROCESSOR COMPONENTS**

8008 - \$19.95		2102 - \$2.95	
6008	CPU'S	RAM'S	
8008	8 bit CPU	1103	256 x 1
4040	4 bit CPU	2102	1K x 1
AY-5-1013	PARMS	2102	4K x 1
8223	32x8 Prom	300	8101
1702A	7K E Prom	1700	8111
52000	2K E Prom	1495	8589
74527	1Kx1 Prom	795	91102
2401	SR'S	795	7400
2533	1K SR'S	985	7415670
		985	93410

**91L02** 1K Static RAM Direct Replacement for 2102-1 with 40 - Less Current Drawn 3.95  
Vector General Purpose Logic CARD Board 14.95  
\*Very High Noise Immunity \* Holds 12 e 14 pin DIPS \*44 pin Edge Connection

**THE KILOBYTE RAM CARD** Per Kit \$49.95  
\*Complete 1Kx8 Memory \* High Noise Immunity Components \*Single vs. Multiple Access Times & Kit includes sockets, IC'S & Board

**KITS EXAR IC'S**  
FREE With each \$75 order of Microprocessor components, \$12.00 get a one year subscription to RFE the magazine for Value computer PHREAKS FREE FREE FREE

**KR-2206KA** SPECIAL \$17.95  
Includes monolithic function generator IC, PC board, and assembly instruction manual.

**KR-2206KB** SPECIAL \$27.95  
Same as KR-2206KA above and includes external components for PC board.

**TIMERS**

XR-555CP	SPECIAL \$ .69	XR-13
----------	----------------	-------

**QUALITY ELECTRONIC COMPONENTS**  
— SAME DAY SERVICE —

**NEW DISCOUNT SCHEDULE SAVES YOU EVEN MORE!**

**1024 BIT STATIC MOS RAM**  
**2102 . . . \$3.50**

**INTEGRATED CIRCUITS — TTL, CMOS, LINEAR & MOS**

7400N	24c	7453N	22c	74155N	77c	4010AE	58c	4518AE	\$1.28
7401N	24c	7454N	22c	74156N	77c	4020AE	\$1.56	4520AE	\$1.28
7402N	24c	7455N	22c	74157N	77c	4030AE	\$1.56	4522AE	\$1.28
7403N	24c	7470N	34c	74160N	\$1.19	4022AE	\$1.18	4528AE	\$1.04
7404N	24c	7472N	34c	74161N	\$1.11	4023AE	24c	4530AE	\$1.04
7405N	24c	7473N	31c	74162N	\$1.19	4024AE	24c	4532AE	\$1.04
7406N	24c	7474N	31c	74163N	\$1.19	4025AE	24c	4534AE	\$1.04
7407N	24c	7475N	31c	74164N	\$1.28	4026AE	\$1.67	4535AE	\$1.04
7408N	24c	7476N	34c	74165N	\$1.11	4027AE	44c	4536AE	\$1.04
7409N	24c	7480N	48c	74175N	\$1.02	4028AE	\$1.04	4538AE	\$1.04
7410N	24c	7482N	48c	74180N	77c	4029AE	\$1.30	4539AE	\$1.04
7411N	24c	7483N	48c	74181N	\$2.13	4030AE	50c	4540AE	\$1.04
7412N	24c	7485N	\$1.11	74187N	85c	4033AE	\$1.67	4542AE	\$1.04
7413N	24c	7487N	31c	74190N	\$1.45	4034AE	\$2.34	4544AE	\$1.04
7414N	\$1.02	7489N	\$2.13	74191N	\$1.45	4035AE	\$1.38	4546AE	\$1.04
7416N	24c	7490N	48c	74192N	\$1.19	4040AE	\$1.60	4A79CA	43c
7417N	24c	7491N	48c	74193N	\$1.11	4041AE	90c	4A79CA	43c
7420N	24c	7492N	48c	74194N	\$1.11	4042AE	82c	4A79CA	37c
7421N	24c	7493N	48c	74195N	\$1.11	4043AE	67c	4A79CA	40c
7422N	24c	7494N	48c	74196N	77c	4044AE	67c	4A79CA	43c
7428N	24c	7495N	85c	4000A1	24c	4048AE	\$2.35	4A79CA	40c
7429N	43c	7496N	85c	4000A2	24c	4049AE	52c	4A79CA	41c
7430N	24c	7497N	\$1.24	4000A3	24c	4050AE	52c	4A79CA	41c
7431N	24c	7498N	31c	4000A4	\$1.50	4051AE	\$1.44	4A79CA	\$1.25
7432N	24c	7499N	31c	4000A5	24c	4052AE	24c	4A79CA	\$1.25
7433N	24c	7500N	34c	4000A6	24c	4053AE	24c	4A79CA	\$1.25
7434N	24c	7501N	34c	4000A7	24c	4054AE	\$1.44	4A79CA	\$1.25
7435N	\$1.11	7502N	34c	4000A8	24c	4055AE	\$1.44	4A79CA	\$1.25
7436N	24c	7503N	34c	4000A9	24c	4056AE	\$1.44	4A79CA	\$1.25
7437N	24c	7504N	34c	4000A10	24c	4057AE	\$1.44	4A79CA	\$1.25
7438N	24c	7505N	34c	4000A11	24c	4058AE	\$1.44	4A79CA	\$1.25
7439N	24c	7506N	34c	4000A12	24c	4059AE	\$1.44	4A79CA	\$1.25
7440N	24c	7507N	34c	4000A13	24c	4060AE	\$1.44	4A79CA	\$1.25
7441N	24c	7508N	34c	4000A14	24c	4061AE	\$1.44	4A79CA	\$1.25
7442N	24c	7509N	34c	4000A15	24c	4062AE	\$1.44	4A79CA	\$1.25
7443N	24c	7510N	34c	4000A16	24c	4063AE	\$1.44	4A79CA	\$1.25
7444N	24c	7511N	34c	4000A17	24c	4064AE	\$1.44	4A79CA	\$1.25
7445N	24c	7512N	34c	4000A18	24c	4065AE	\$1.44	4A79CA	\$1.25
7446N	24c	7513N	34c	4000A19	24c	4066AE	\$1.44	4A79CA	\$1.25
7447N	24c	7514N	34c	4000A20	24c	4067AE	\$1.44	4A79CA	\$1.25
7448N	24c	7515N	34c	4000A21	24c	4068AE	\$1.44	4A79CA	\$1.25
7449N	24c	7516N	34c	4000A22	24c	4069AE	\$1.44	4A79CA	\$1.25
7450N	24c	7517N	34c	4000A23	24c	4070AE	\$1.44	4A79CA	\$1.25
7451N	24c	7518N	34c	4000A24	24c	4071AE	\$1.44	4A79CA	\$1.25

**SILICON TRANSISTORS**

2N918	21c	10/52.00	1C/517.85	2N3640	21c	10/52.00	1C/517.85
2N918	16c	10/51.55	1C/513.60	2N3641	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3642	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3643	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3644	21c	10/52.00	1C/517.85
2N918	16c	10/51.55	1C/513.60	2N3645	21c	10/52.00	1C/517.85
2N918	16c	10/51.55	1C/513.60	2N3646	21c	10/52.00	1C/517.85
2N918	16c	10/51.55	1C/513.60	2N3647	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3648	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3649	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3650	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3651	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3652	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3653	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3654	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3655	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3656	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3657	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3658	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3659	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3660	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3661	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3662	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3663	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3664	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3665	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3666	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3667	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3668	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3669	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3670	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3671	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3672	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3673	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3674	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3675	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3676	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3677	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3678	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3679	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3680	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3681	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3682	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3683	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3684	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3685	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3686	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3687	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3688	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3689	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3690	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3691	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3692	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3693	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3694	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3695	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3696	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3697	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3698	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3699	16c	10/51.55	1C/513.60
2N918	16c	10/51.55	1C/513.60	2N3700	16c	10/51.55	1C/513.60

**ELECTROLYTIC CAPACITORS**

Radial Lead		Axial Lead	
100uf/50v	8c	10/64c	1C/5 5.41
2.2uf/50v	8c	10/64c	1C/5 5.41
3.3uf/50v	8c	10/64c	1C/5 5.41
4.7uf/25v	8c	10/64c	1C/5 5.41
10uf/25v	8c	10/67c	1C/5 5.66
100uf/50v	10c	10/77c	1C/5 5.68
5.0uf/25v	8c	10/77c	1C/5 5.68
22uf/25v	12c	10/51.00	1C/5 8.48
100uf/63v	9c	10/74c	1C/5 6.32
100uf/16v	11c	10/86c	1C/5 7.28
100uf/25v	13c	10/51.08	1C/5 9.15
Axial Lead		Axial Lead	
10uf/50v	11c	10/90c	1C/5 7.65
2.2uf/50v	12c	10/92c	1C/5 7.82
3.3uf/50v	12c	10/93c	1C/5 7.97
3.3uf/25v	12c	10/98c	1C/5 8.31
4.7uf/25v	12c	10/93c	1C/5 7.91
10uf/16v	11c	10/90c	1C/5 7.65
10uf/25v	12c	10/98c	1C/5 8.31
10uf/50v	11c	10/90c	1C/5 7.65
2.2uf/50v	12c	10/92c	1C/5 7.82
3.3uf/50v	12c	10/93c	1C/5 7.97
3.3uf/25v	12c	10/98c	1C/5 8.31
4.7uf/25v	12c	10/93c	1C/5 7.91
10uf/16v	11c	10/90c	1C/5 7.65
10uf/25v	12c	10/98c	1C/5 8.31

**DISC CAPS**

100pf/500v	4c	10/36c	2C/5 6.09
220pf/500v	4c	10/36c	2C/5 6.09
470pf/500v	4c	10/36c	

**EXAR  
FUNCTION  
GENERATOR  
KITS**



features sine, triangle and square wave; THD 0.5% typ.; AM/FM capability

XR-2206KA Includes monolithic function generator IC, PC board, and assembly instruction manual. **SPECIAL \$16.95**

Same as XR-2206KA above and includes external components for PC board. **SPECIAL \$26.95**

**TIMERS**  
XR-555CP Monolithic Timer **SPECIAL \$ .68**  
XR-320P Precision Timer 1.50  
XR-556CP Dual 555 Timer 1.70  
XR-2556CP Dual Timing Circuit 3.10  
XR-2240CP Programmable Counter/Timer **SPECIAL 3.20**

**PHASE LOCKED LOOPS**  
XR-210 FSK Demodulator 5.10  
XR-215 High Frequency PLL 6.50  
XR-567CP Tone Decoder (mini DIP) 1.90  
XR-567CT Tone Decoder (TO-18) **SPECIAL .99**

**STEREO DECODERS**  
XR-1310P PLL Stereo Decoder 3.10  
XR-1310EP PLL Stereo Decoder 3.10  
XR-1800P PLL Stereo Decoder 3.10

**WAVEFORM GENERATORS**  
XR-205 Waveform Generator 8.30  
XR-2206CP Monolithic Function Generator **SPECIAL 4.39**  
XR-2207CP Voltage-Controlled Oscillator 3.75

**OTHER EXAR**  
XR-1468CN Dual +15V Tracking Regulator **SPECIAL 2.90**  
XR-1488N Quad Line Driver 5.70  
XR-1489N Quad Line Receiver 4.70  
XR-2208CP Operational Multiplier 5.10  
XR-2211CP Monolithic Proportional Servo IC System 6.60  
w/4 ea. Driver Transistor 3.70

**7400N TTL**  
7400N .53 7443N .95 74104N 1.20 74165N 1.30  
7401N .16 7444N 1.05 74105N .50 74166N 1.30  
7402N .14 7445N .90 74107N .30 74170N 2.50  
7403N .16 7446N .90 74108N .90 74173N 1.50  
7404N .19 7447N .90 74110N .72 74174N 1.10  
7405N .20 7448N .80 74114N .93 74175N 1.20  
7406N .29 7450N .16 74118N 1.52 74176N 1.25  
7407N .29 7451N .16 74121N .45 74177N 1.40  
7408N .18 7453N .16 74122N .45 74180N .73  
7409N .20 7474N .59 74123N .70 74181N 3.00  
7410N .18 7460N .16 74125N .50 74196N 1.70  
7411N .26 7470N .30 74126N .50 74184N 2.00  
7412N .33 7472N .30 74128N .90 74185N 2.29  
7413N .58 7473N .37 74132N 1.00 74188N 4.80  
7414N 1.23 7474N .32 74136N .95 74190N 1.20  
7416N .28 7475N .59 74141N 1.20 74191N 1.20  
7417N .33 7476N .32 74145N 1.00 74192N 1.20  
7419N .17 7480N .59 74147N 2.40 74193N 1.00  
7421N .33 7481N 1.18 74148N 1.80 74194N 1.15  
7422N .50 7482N .89 74150N 1.00 74195N .80  
7423N .57 7483N .65 74151N .80 74196N 1.70  
7425N .34 7484N 3.00 74152N 1.40 74197N .80  
7426N .25 7485N 1.20 74153N 1.00 74198N 1.75  
7427N .31 7486N .35 74154N 1.40 74199N 1.40  
7428N .50 7489N 2.30 74155N 1.00 74200N 5.60  
7430N .29 7490N .50 74156N 1.18 74221N 1.70  
7432N .24 7491N .90 74157N 1.00 74251N 2.00  
7433N .60 7492N .55 74158N 1.20 74278N 2.95  
7437N .35 7493N .58 74160N 1.30 74279N .90  
7438N .33 7494N .80 74161N 1.20 74293N 1.00  
7439N .38 7495N .80 74162N .74 74298N 2.20  
7440N .16 7496N 1.50 74163N 1.40  
7441N .95 74100N 1.00 74164N 1.30  
7442N .50

**7400N TTL**

7400N .53	7443N .95	74104N 1.20	74165N 1.30
7401N .16	7444N 1.05	74105N .50	74166N 1.30
7402N .14	7445N .90	74107N .30	74170N 2.50
7403N .16	7446N .90	74108N .90	74173N 1.50
7404N .19	7447N .90	74110N .72	74174N 1.10
7405N .20	7448N .80	74114N .93	74175N 1.20
7406N .29	7450N .16	74118N 1.52	74176N 1.25
7407N .29	7451N .16	74121N .45	74177N 1.40
7408N .18	7453N .16	74122N .45	74180N .73
7409N .20	7474N .59	74123N .70	74181N 3.00
7410N .18	7460N .16	74125N .50	74196N 1.70
7411N .26	7470N .30	74126N .50	74184N 2.00
7412N .33	7472N .30	74128N .90	74185N 2.29
7413N .58	7473N .37	74132N 1.00	74188N 4.80
7414N 1.23	7474N .32	74136N .95	74190N 1.20
7416N .28	7475N .59	74141N 1.20	74191N 1.20
7417N .33	7476N .32	74145N 1.00	74192N 1.20
7419N .17	7480N .59	74147N 2.40	74193N 1.00
7421N .33	7481N 1.18	74148N 1.80	74194N 1.15
7422N .50	7482N .89	74150N 1.00	74195N .80
7423N .57	7483N .65	74151N .80	74196N 1.70
7425N .34	7484N 3.00	74152N 1.40	74197N .80
7426N .25	7485N 1.20	74153N 1.00	74198N 1.75
7427N .31	7486N .35	74154N 1.40	74199N 1.40
7428N .50	7489N 2.30	74155N 1.00	74200N 5.60
7430N .29	7490N .50	74156N 1.18	74221N 1.70
7432N .24	7491N .90	74157N 1.00	74251N 2.00
7433N .60	7492N .55	74158N 1.20	74278N 2.95
7437N .35	7493N .58	74160N 1.30	74279N .90
7438N .33	7494N .80	74161N 1.20	74293N 1.00
7439N .38	7495N .80	74162N .74	74298N 2.20
7440N .16	7496N 1.50	74163N 1.40	
7441N .95	74100N 1.00	74164N 1.30	
7442N .50			

**HIGH SPEED TTL**

74H00N .33	74H20N .33	74H53N .36	74H73N .90
74H01N .25	74H21N .33	74H54N .36	74H74N .87
74H02N .30	74H22N .33	74H55N .36	74H76N .90
74H04N .33	74H30N .33	74H60N .36	74H101N .80
74H05N .33	74H40N .36	74H61N .36	74H102N .80
74H08N .40	74H50N .36	74H62N .36	74H103N 1.10
74H10N .33	74H51N .36	74H71N .80	74H106N .95
74H11N .33	74H52N .36	74H72N .74	

**LOW POWER TTL**

74L00N .31	74L10N .33	74L51N .34	74L90N 1.62
74L01N .33	74L20N .33	74L73N .69	74L93N 1.74
74L04N .33	74L42N 1.49	74L74N .90	74L95N 1.62

**74LS**

74LS00 .46	74LS27 .50	74LS112 .58	74LS170 5.80
74LS01 .58	74LS30 .46	74LS113 .92	74LS174 2.20
74LS02 .46	74LS32 .50	74LS138 2.06	74LS175 2.42
74LS03 .50	74LS38 .46	74LS139 2.06	74LS181 7.00
74LS04 .50	74LS51 .50	74LS151 1.92	74LS194 2.40
74LS05 .46	74LS58 .58	74LS153 1.92	74LS195A 2.40
74LS09 .58	74LS55 .58	74LS157 1.68	74LS196 2.76
74LS10 .46	74LS73 .58	74LS158 1.68	74LS251 2.06
74LS11 .46	74LS74 .58	74LS160 3.06	74LS253 2.42
74LS15 .58	74LS76 .92	74LS161 3.06	74LS257 2.06
74LS20 .46	74LS78 .92	74LS162 3.06	74LS258 2.06
74LS21 .58	74LS107 .92	74LS163 2.90	74LS260 .58
74LS22 .58	74LS109 .92		

**SCHOTTKY TTL**

74S00N .44	74S51N .80	74S140N .80	74S189N 4.40
74S02N .60	74S64N .80	74S151N 2.20	74S194N 3.30
74S03N .75	74S74N 1.20	74S153N 3.40	74S195N 3.30
74S04N .55	74S85N 6.10	74S167N 2.40	74S251N 2.20
74S08N .80	74S90N 2.50	74S158N 2.40	74S253N 2.40
74S10N .95	74S112N 1.00	74S160N 3.90	74S257N 2.40
74S11N .65	74S113N 1.50	74S161N 4.70	74S258N 2.40
74S20N .65	74S132N 3.60	74S174N 3.00	74S260N 1.20
74S30N .80	74S133N .80	74S175N 2.90	74S280N 5.70
74S32N .80	74S138N 2.20	74S181N 4.40	74S289N 4.00
74S40N .65	74S139N 2.20		

**9300 SERIES**

9300PC \$1.00	93018PC 2.30	9366PC 1.75	93L18 3.50
9301PC 1.20	9321PC 1.20	93L00 1.50	93L21 1.50
9304PC 1.50	9322PC 1.30	93L01 1.60	93L22 1.80
9306PC 6.90	9324PC 2.00	93L08 3.20	93L24 2.80
9308PC 2.50	9328PC 2.50	93L09 1.80	93L28 3.70
9309PC 1.60	9334PC 2.95	93L10 2.80	93L34 4.00
9310PC 1.50	9338PC 3.30	93L11 4.20	93L38 4.20
9311PC 2.30	9340PC 5.00	93L12 1.80	93L40 6.50
9312PC 1.20	9341PC 1.10	93L14 1.70	93L41 6.50
9314PC 1.30	9342PC 1.15	93L16 3.20	93L60 3.00
9316PC 1.50	9360PC 1.75	93L18 3.50	93L66 2.70

**AUDIO AMPS**

TYPE	V	W	Ω	PRICE
LM352	6-15	1.15	8	1.60
TA-A611B12	6-15	1.15	8	2.00
TA-A621A12	6-27	4.0	8	2.00
TA-A641B11	6-18	2.20	4	3.00
TB-800	5-30	4.70	8	2.00
TB-810AS	4-20	2.50	4	3.00
TB-820	3-12	0.75	4	1.70
TC-830	3-20	2.00	4	2.20
TC-840	6-24	6.50	8	4.40

**IC SOCKETS**

SOLDER-TIN DIP		WIRE-WRAP GOLD		TEFLON TO-5	
PIN 1-24	25 100	PIN 1-24	25 100	3 PIN	55 EA
8	21 19 17 14	45	41 37	4 PIN	65 EA
14	25 22 20 16	54	49 44	6 PIN	90 EA
16	28 25 23			8 PIN	110 EA
24	67 61 55	<b>SOLDER - GOLD</b>		10 PIN	140 EA
28	88 80 72				
36	1.09 98 89	14	34 28		
40	1.24 1.12 92	16	37 31		

**LEDs**

.125" dia.	.160" dia.	.200" dia.			
209 RED	\$ .25	216 RED	\$ .25	220 RED	\$ .25
209 YELLOW	.35	216 YELLOW	.30	220 YELLOW	.30
209 GREEN	.35	216 GREEN	.30	220 GREEN	.30

**LOW PROFILE**

226 RED	\$ .25	5053 RED	\$ .35	MV50 RED	\$ .30
226 YELLOW	.30	5053 YELLOW	.40		
226 GREEN	.30	5053 GREEN	.40	216 = MV5024	
226 ORANGE	.30	5053 ORANGE	.40	5053 = MV5053	

**DISPLAYS**

LITRONIX		EP 9125 9-DIGIT DISPLAY	
DL80 RED	6.00	1/8" Character Ht.	Compact, Thin Pk.
DL81 RED	6.00	1/8" Character Ht.	Compact, Thin Pk.
DL10 RED	6.00	1/8" Character Ht.	Compact, Thin Pk.
DL10A RED	4.00	1/8" Character Ht.	Compact, Thin Pk.
DL101 RED	4.00	1/8" Character Ht.	Compact, Thin Pk.
DL57 RED	9.00	1/8" Character Ht.	Wide Viewing Angle
DL61 RED	12.00	1/8" Character Ht.	Wide Viewing Angle
DL33 RED	4.00		
DL44 RED	6.00		
DL402 RED	4.00		
DL701 RED	3.40		
DL70A RED	4.00		
DL702 RED	2.25		
DL707 RED	2.35		
DL747 RED	2.50		
IL12	1.30	25	\$21.00
IL12	1.40	100	14.00
IL16	1.80	EA 1500ASJ	
IL74	1.35	1-24	\$16.00
ILD74	1.75	25	14.00
ILQ74	3.40	100	12.40

**OPCOA**

SLA1 RED	2.25	DL61 RED	12.00
SLA11 GREEN	3.50	DL33 RED	4.00

**XCITON**

XAN72 RED	2.00	DL70A RED	2.25
XAN52 GREEN	2.00	DL707 RED	2.35

**OPTOISOLATORS**

MONSANTO	1.40	IL16	1.80	EA 1500ASJ
MCT2 1.35		IL74	1.35	1-24 \$16.00
		ILD74	1.75	25 14.00
		ILQ74	3.40	100 12.40

**PREMIUM QUALITY COMPONENTS**

We've been buying and selling top quality components for nearly ten years. Our annual volume exceeds \$3 million. We handle only original parts, from the world's leading manufacturers and our customers include some of the largest and most quality-conscious companies. Now you can take advantage of our component buying skills and power and select from a broad range of advanced circuits.



**COMPUTER INTERFACE**

DM8822N	2.40	P1101A	2.20	BIPOLAR MEMORY	
DM8820AN	2.40	P1101A1	3.50	C3101	6.50
DM8830N	2.40	1402AN	2.90	C3101	4.90
DM8831N	2.40	1403AH	4.00	C3101A	7.30
DM8832N	6.00	1404AH	3.80	P3101A	5.80
N8T268	4.40	1404AN	2.90	IM5501CDE	7.30
9600PC	1.30	1405A	4.00	MM5560D	7.30
9601PC	1.20	1506	3.00	MM5560N	5.80
9602PC	2.10	1602	3.00	MM5599N	5.80
9614PC	2.30	1702	15.00	93403PC	5.80
9615PC	2.40	C2102	5.00		
9616PC	5.00	C2102	2.90	MM404H	12.00
9617PC	3.50	P2102-1	5.00	MM405H	23.00
9620PC	4.00	P2102-2	4.00	MM406H	6.50
9621PC	4.00	C2102-2	6.00	MM407H	6.50
		C2102-2	3.00	MM451H	11.40

**NEW KITS! NEW KITS!**

**JAMES ELECTRONICS**

P. O. BOX 822 BELMONT, CALIFORNIA 94002  
(415) 592-8097

**DIGITAL VOLTMETER**



**GENERAL DESCRIPTION**

The JE601 is a three and one half digit, auto polarity digital voltmeter, in a kit form. It features several options not available in any commercial digital voltmeter. Its low cost is perhaps the most important feature, which is achieved by offering it in a kit form. A kit allows the unit to be used by small OEM's whose cost effectiveness is an important factor, and by the hobbyist who has to be concerned with cost. The unit also requires no line regulators, allowing it to be operated off a single plug and mount fifteen volt, unregulated power supply. The unit has a small size of three inches width, three and three quarters of an inch height, and one and a quarter inch depth.

**\$39.95 Per Kit** printed circuit board

**LOGIC PROBE**

The Logic Probe is a unit which is for the most part indispensable in trouble shooting logic families: TTL, DTL, RTL, CMOS. It derives the power it needs to operate directly off of the circuit under test, drawing a scant 10 mA max. It uses a MAN3 readout to indicate any of the following states by these symbols: (H) - 1 (LOW) - 0 (PULSE) - P. The Probe can detect high frequency pulses to 45 MHz; it can't be used at MOS levels or circuit damage will result.



printed circuit board  
**\$9.95 Per Kit**

**MINI POWER SUPPLIES**

These power supplies offer small size, with a wide choice of voltage outputs. They are all capable of delivering 300mA and have dimensions of 1" x 1" x 3". The voltages available are +5V, -5V, +6V, -6V, +12V, -12V. All of these units easily assemble in less than a half an hour, because of the fiberglass printed circuit board construction. Please specify voltage when ordering.


**\$9.95 per kit**

**LOW COST DIGITAL CLOCK KIT**

Other companies have offered a low cost digital clock kit, but do not offer important extras such as, printed circuit boards, power supplies cases, etc. We at James are doing just the opposite by offering a complete clock kit, that includes everything down to the line cord. This kit uses 25' FND 70 displays, for HOURS, MINUTES, and SECONDS, in conjunction with the MM5514 clock chip. The printed circuit board is of high quality fiberglass, which is plated. The case is a 6 x 1 1/2 x 1 walnut case with a plexi-glass front, and is similar to the one in our TV WALL Digital clock. It is available without the case for \$16.95.

**\$19.95 per kit.**

**ELECTRONIC ROULETTE**

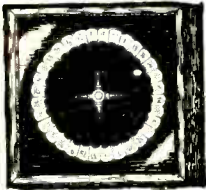

Complete kit with all components case and transformer.





8" x 8" x 1"

A 56 page book on the facts of Roulette included.

**\$29.95 Per Kit**

**ELECTRONIC CRAPS**

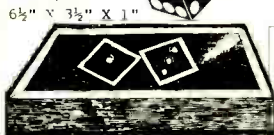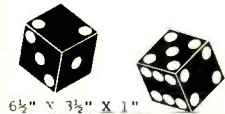

Complete kit with all components case and transformer.



A 56 page book on the facts of Craps included.

**\$19.95 Per Kit**

Satisfaction Guaranteed. \$5.00 Min. Order. U.S. Funds. Add \$1.25 for Postage — Write for FREE 1975 Catalog California Residents — Add 6% Sales Tax

**JAMES**

P.O. BOX 822, BELMONT, CA. 94002  
PHONE ORDERS — (415) 592-8097

**ADVERTISING INDEX**

**RADIO-ELECTRONICS does not assume responsibility for any errors which may appear in the index below.**

**READER SERVICE CARD NO. PAGE**

74	A.D.R. Audio	110
84	Allison Automotive Co.	116
94	Alpha Electronics	121
28	American Technology Corp.	75
7	Amperex Electronic Corp.	17
69	AP Products, Inc.	106
23	Arrow Fastener	88
16,17,18	B & K Division of Dynascan Corp.	34, 35
78	Basix	113
	Bell & Howell Schools	56-59
102	Castle TV Tuner Service Corp.	Cover IV
14	Channelock, Inc.	32
11,13	CIE, Cleveland Institute of Electronics	26, 28-31
6	Computer Ease	16
19	Continental Specialties Corp.	36
	CREI, Division of McGraw-Hill Continuing Education Center	84-87
75	Data Precision	111
27	Delta Products	95
87	E & L Electronics	118
64	Edlie Electronics	98
9,99	Edmund Scientific	23, 136
65	EICO, Electronic Instrument, Inc.	99
25	Electronics Technical Institute, Division of Technical Home Study Schools	102-103
	EMC, Electronics Measurement Corp.	119
85	Fordham Radio Supply Co.	117
70	John Fluke Mfg. Co.	106
	General Electric Tube Division	94
73	Grantham School of Electronics	109
	GTE Sylvania Electronic Components	90, 91
100	Heath Co.	18-21, 122
62	Hickok Electrical Instrument Co.	96
	ICS, International Correspondence Schools	66-69
26	Ignitions Systems	93
89	Indiana Home Study Inst.	119
71	International Crystal Mfg. Co.	107
97	Kedman Co.	122
79	Lafayette Radio Electronic Corp.	113
	J. B. Lansing	7
81	Leader Instruments Corp.	115
72	Lectrotech, Inc.	108
12	McGraw-Hill Book Co.	27
83	Miami Projection TV	115
2	MITS, Micro-Instrumentation Telemetry Systems, Inc.	1
98	Mountain West Alarm Supply Co.	122

**CONVERT** any television to sensitive, big-screen oscilloscope. Only minor changes required. No electronic experience necessary. Illustrated plans \$2.00. **SANDERS**, Dept A-25, Box 92102, Houston, TX 77010

**WANTED**

**QUICK** cash . . . for electronic equipment, components, unused tubes. Send list now! **BARRY**, 512 Broadway, New York, NY 10012, 212 Walker 5-7000

**READER SERVICE CARD NO. PAGE**

91	MTI, Motorola Training Institute	120
95	National Camera Co.	121
	National Technical Schools	46-49
	NRI, Division of McGraw-Hill	8-11
88	PAIA Electronics, Inc.	119
63	Pomona Electronics	97
29	Prentice Hall Books	77
1	PTS Electronics, Inc.	Cover I
5	Radio Shack	15
	RCA Distributor & Special Products (Parts & Accessories)	2
4	RCA Solid State Division	13
	RCA Distributor & Special Products Picture Tubes Division	81
	RCA Distributor & Special Products Picture Tubes Division	110
	RCA Distributor & Special Products Accessories	80
8	RCA Distributor & Special Products Test Equipment	22
86	Rye Industries	118
92	Scelbi Computer Consulting, Inc.	120
68	Schober Organ Corp.	101
93	Shurman Products	120
21	Shure Brothers, Inc.	82
101	Simpson Electric Co.	Cover III
15,24	Sphere	33, 89
22	Southwest Technical Products	83
82	Tab Books	115
66,76	Telematic	100, 112
30,61	Tektronix, Inc.	79
77	Tokyo Electronics, Inc.	113
96	Tri-Star Corp.	121
3	Tuner Service Corp.	5
67	Vintage Radio	108
10	Wahl Clipper Corp.	101
80	Winegard Co.	24, 25
	Weller X-Cellite Electronics Division	114
	<b>MARKET CENTER</b>	
58,60	Ancrona Corp.	133, 135
108	Babylon Electronics	126
	CFR Associates	130
106	Circuit Specialists	124
	Command Productions	123
	Cornell	124
	Cortland Electronics	124
110	Delta Electronics	126, 132
119	Digi Key	132
113	Dollar Value	128
117	Formula International, Inc.	130
107	Bill Godbout Electronics	125
	International Electronics Unlimited	130
57	James Electronics	131, 134
118,59	Lab Science	128
	Lakeside Industries	123
111	Stanley Lin	128
	Locksmithing Institute	123
109	Meshna Electronics, John Jr.	126
112	New-Tone Electronics	128
105	Olson Electronics	123
116	Photolume Corp.	130
114	Poly Paks	129
120	Processor Technology Corp.	132
	Saxitone Tape Sales	128
	Solid State Sales	124
	Trumbull	123
115	TV Tech Specials	130
	Valley West	123



# High Quality CARBON FILM RESISTORS

1/4 Watt 5%

\$1.69 per 100

Only in multiples of 100 per value

● 150 different values in stock

## PLESSEY RADIO COMMUNICATIONS CIRCUITS

SL610C	RF amplifier	4.07	3.56	3.06	SL621C	AGC generator	6.15	5.39	4.62	SL624C	Multimode det. AF amp	5.70	5.00	4.28	SL645C	Square law device	7.55	6.60	5.65
SL611C	RF amplifier	4.07	3.56	3.06	SL622C	AF amp/VOGAD	15.21	13.31	11.41	SL630C	AF amplifier	3.85	3.38	2.90	SL650B	Mod./phase loc. loop	10.86	9.31	7.76
SL612C	IF amplifier	4.07	3.56	3.06	SL623C	sidetone amplifier				SL640C	Dbl. bal. modulator	7.55	6.60	5.65	SL650C	Mod./phase loc. loop	6.80	5.83	4.86
SL613C	Limiting amp/det.	8.66	7.58	4.9						SL641C	Receiver mixer	7.55	6.60	5.65	SL651B	Mod./phase loc. loop	12.06	10.34	8.62
SL620C	VOGAD	6.15	5.39	4.62										SL651C	Mod./phase loc. loop	7.56	6.84	5.40	

## PREMIUM QUALITY TRANSISTORS

2N125	1.40	2N967	.48	2N2192	.60	2N2833	3.90	2N3793	.25	2N4142	.17	2N4988	.95	2N5311	.44	2N5813	.42
2N173	2.15	2N916	1.80	2N2192A	.66	2N2850	112.50	2N3796	3.00	2N4143	.16	2N4989	1.40	2N5322	.70	2N5815	.36
2N293	.60	2N984	.95	2N2193	2.44	2N2857	3.00	2N3799	3.15	2N4220A	1.00	2N4990	.75	2N5323	.66	2N5816	.38
2N321	.50	2N1035	1.90	2N2197	2.40	2N2880	10.90	2N3804	8.00	2N4225	3.75	2N4991	.75	2N5354	.30	2N5817	.38
2N324	.55	2N1132	.30	2N2217	.80	2N2893	9.70	2N3805	10.40	2N4226	3.90	2N4992	1.10	2N5355	.35	2N5818	.40
2N336	1.00	2N1136	1.40	2N2218	.25	2N2894	.45	2N3819	.30	2N4227	.34	2N4993	1.60	2N5365	.40	2N5819	.42
2N338A	1.25	2N1137A	1.90	2N2218A	.48	2N2895	1.00	2N3821	1.35	2N4228	.49	2N4994	.25	2N5366	.40	2N5821	.60
2N389	9.00	2N1143	1.90	2N2219	.29	2N2903	4.10	2N3822	1.40	2N4235	1.90	2N4995	.26	2N5367	.42	2N5822	.56
2N389A	1.20	2N1168	.65	2N2219A	.36	2N2904	.30	2N3823	.69	2N4248	1.7	2N5016	12.70	2N5368	.24	2N5823	.66
2N397	1.20	2N1204	1.40	2N2221	.24	2N2904A	.34	2N3824	1.00	2N4249	.20	2N5036	1.17	2N5369	.25	2N5824	.24
2N398B	1.00	2N1302	.30	2N2221A	.25	2N2905	.32	2N3824	1.00	2N4250	.22	2N5064	.50	2N5370	.26	2N5825	.26
2N404	.30	2N1303	.80	2N2222	.24	2N2905A	.34	2N3825	.28	2N4256	.28	2N5068	.45	2N5371	.22	2N5826	.28
2N444	.65	2N1305	.35	2N2222A	.26	2N2906	.17	2N3826	.26	2N4258	.34	2N5089	.80	2N5373	.26	2N5827	.30
2N417	1.15	2N1309	.80	2N2270	.40	2N2907	.19	2N3827	.42	2N4259	.28	2N5105	3.05	2N5375	.25	2N5828	.32
2N456	1.30	2N1377	1.40	2N2289	3.60	2N2907A	.26	2N3828	.28	2N4268	.35	2N5109	2.40	2N5380	.50	2N5828A	.38
2N491	5.10	2N1408	.60	2N2290	5.90	2N2911	21.00	2N3829	7.10	2N4341	1.35	2N5131	.20	2N5383	.56	2N6002	.50
2N508A	.40	2N1420	.60	2N2297	.95	2N2913	.69	2N3830	2.1	2N4347	2.0	2N5133	.17	2N5397	2.90	2N6004	.54
2N511A	3.50	2N1485	2.60	2N2323	1.90	2N2925	.20	2N3831	3.90	2N4348	2.10	2N5134	.18	2N5407	28.00	2N6010	.62
2N512B	2.90	2N1521	4.80	2N2326	3.30	2N2926	.14	2N3832	1.8	2N4349	2.2	2N5130	.20	2N5382	.50	2N6011	.52
2N525	.90	2N1523	5.00	2N2356	5.90	2N2947	14.40	2N3833	1.8	2N4350	.20	2N5135	.16	2N5409	31.90	2N6011	.64
2N526	.90	2N1534	1.00	2N2356A	6.90	2N2949	5.90	2N3834	1.6	2N4351	.25	2N5137	.26	2N5418	.30	2N6014	.66
2N527	.90	2N1540	1.05	2N2359	15.90	2N2950	6.40	2N3835	1.24	2N4352	2.00	2N5135	.16	2N5409	31.90	2N6011	.64
2N555	.50	2N1543	3.40	2N2368	.29	2N2958	1.90	2N3836	1.50	2N4353	1.25	2N5137	.26	2N5419	.34	2N6015	.68
2N585	1.00	2N1549	1.30	2N2369	.22	2N2959	30.90	2N3837	1.8	2N4400	.29	2N5138	.17	2N5419	.34	2N6015	.68
2N594	1.50	2N1551	3.90	2N2382	4.40	2N3019	.50	2N3838	1.80	2N4401	1.00	2N5155	3.20	2N5447	.26	2N6028	.64
2N630	4.00	2N1552	3.90	2N2440	3.45	2N3022	17.90	2N3839	2.0	2N4402	.35	2N5155	3.20	2N5447	.26	2N6028	.64
2N652	.40	2N1554	1.90	2N2465	7.40	2N3053	.34	2N3840	1.80	2N4403	.30	2N5157	9.85	2N5448	.27	2N6076	.16
2N652A	.40	2N1557	1.70	2N2468	1.00	2N3054	.80	2N3841	1.80	2N4404	1.00	2N5157	9.85	2N5448	.27	2N6079	1.00
2N657A	.40	2N1560	3.20	2N2475	.55	2N3058	.65	2N3842	1.80	2N4405	.30	2N5158	1.00	2N5450	.27	2N6101	.95
2N677C	5.50	2N1613	.40	2N2476	.79	2N3060	2.95	2N3843	1.80	2N4406	.30	2N5158	1.00	2N5450	.27	2N6101	.95
2N683	.20	2N1671	2.00	2N2483	.28	2N3066A	1.19	2N3844	1.80	2N4407	.30	2N5158	1.00	2N5450	.27	2N6101	.95
2N697	1.25	2N1678	2.10	2N2484	.25	2N3107	.78	2N3845	1.80	2N4408	.30	2N5158	1.00	2N5450	.27	2N6101	.95
2N697A	.50	2N1693	14.90	2N2492	4.00	2N3117	1.50	2N3846	1.60	2N4409	.30	2N5158	1.00	2N5450	.27	2N6101	.95
2N699	.66	2N1711	.40	2N2518	5.90	2N3130	4.90	2N3847	1.60	2N4410	.30	2N5158	1.00	2N5450	.27	2N6101	.95
2N700	3.50	2N1715	.70	2N2528	4.40	2N3202	15.90	2N3848	1.60	2N4411	.30	2N5158	1.00	2N5450	.27	2N6101	.95
2N705	.50	2N1720	4.90	2N2527	5.40	2N3209	.89	2N3849	1.60	2N4412	.30	2N5158	1.00	2N5450	.27	2N6101	.95
2N706	.20	2N1893	.36	2N2538	2.40	2N3227	2.30	2N3850	1.60	2N4413	.30	2N5158	1.00	2N5450	.27	2N6101	.95
2N706B	.40	2N1898	1.00	2N2600	7.00	2N3239	2.90	2N3851	1.60	2N4414	.30	2N5158	1.00	2N5450	.27	2N6101	.95
2N711	.36	2N1907	4.90	2N2605	.49	2N3249	.90	2N3852	1.60	2N4415	.30	2N5158	1.00	2N5450	.27	2N6101	.95
2N711B	.60	2N1921	2.50	2N2605A	.58	2N3249	.90	2N3853	1.60	2N4416	.30	2N5158	1.00	2N5450	.27	2N6101	.95
2N718	.28	2N1924	1.25	2N2606	3.50	2N3249	.90	2N3854	1.60	2N4417	.30	2N5158	1.00	2N5450	.27	2N6101	.95
2N718B	.40	2N1934	9.30	2N2647	1.30	2N3249	.90	2N3855	1.60	2N4418	.30	2N5158	1.00	2N5450	.27	2N6101	.95
2N720A	.50	2N1990	.75	2N2648	3.90	2N3249	.90	2N3856	1.60	2N4419	.30	2N5158	1.00	2N5450	.27	2N6101	.95
2N744	.35	2N2060	2.05	2N2658	6.90	2N3249	.90	2N3857	1.60	2N4420	.30	2N5158	1.00	2N5450	.27	2N6101	.95
2N829	2.90	2N2080	4.90	2N2708	.25	2N3249	.90	2N3858	1.60	2N4421	.30	2N5158	1.00	2N5450	.27	2N6101	.95
2N834	.35	2N2081A	2.50	2N2712	.30	2N3249	.90	2N3859	1.60	2N4422	.30	2N5158	1.00	2N5450	.27	2N6101	.95
2N851	.80	2N2100	2.90	2N2713	.14	2N3249	.90	2N3860	1.60	2N4423	.30	2N5158	1.00	2N5450	.27	2N6101	.95
2N918	.40	2N2102	.45	2N2714	.18	2N3249	.90	2N3861	1.60	2N4424	.30	2N5158	1.00	2N5450	.27	2N6101	.95
2N929	.26	2N1924	1.50	2N2715	.18	2N3249	.90	2N3862	1.60	2N4425	.30	2N5158	1.00	2N5450	.27	2N6101	.95
2N930	.28	2N2147	1.40	2N2716	.18	2N3249	.90	2N3863	1.60	2N4426	.30	2N5158	1.00	2N5450	.27	2N6101	.95
2N960	.45	2N2148	.68	2N2754	94.00	2N3249	.90	2N3864	1.60	2N4427	.30	2N5158	1.00	2N5450	.27	2N6101	.95
2N962	.45	2N2152	3.00	2N2802	9.70	2N3249	.90	2N3865	1.60	2N4428	.30	2N5158	1.00	2N5450	.27	2N6101	.95

Minimum Order: \$10.00. Add \$1.00 to cover postage & handling.

SEND CHECK OR MONEY ORDER TO:

California residents add 6% sales tax.



MAIL ORDER: P.O. Box 2208R, Culver City, CA 90230

Visit our Electronic Shop: 11080 Jefferson Blvd., Culver City, CA

(Studio Village Shopping Center) PHONE ORDERS: (213) 641-0064

SPECIFICATIONS SHEETS \$ .25 EACH

NOVEMBER 1975


# LIVE IN THE WORLD OF TOMORROW... TODAY!

And our FREE 164 PAGE CATALOG is packed with exciting and unusual values in electronic, hobby and science items — plus 4,500 finds for fun, study or profit... for every member of the family.

## A BETTER LIFE STARTS HERE
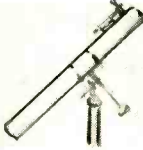
### 4 1/4" ASTRONOMICAL TELESCOPE

See moon craters, rings of Saturn, double stars. New equatorial mount. f/10, 1/4 wave mirror (Pyrex®). Gives theoretical limit of resolution. Rack & pinion focusing. Aluminum tube, 6X finder. 1" F.L. 45X Kellner achromatic eyepiece and Barlow lens to double & triple power up to 135X. Free Star Chart plus 2 Books.



- Stock No. 85,105EH... (Shipping Wt. 42 lbs.) \$159.50 FOB  
 4 1/4" WITH CLOCK DRIVE #85,107EH \$219.50 FOB  
 6" REFLECTOR TELESCOPE (48X to 360X) #85,187EH \$249.50 FOB  
 6" WITH CLOCK DRIVE #85,086EH \$285.00 FOB  
 3" DELUXE REFLECTOR (30 to 90X) #80,162EH \$ 89.95 Ppd.  
 STANDARD 3" REFLECTOR #85,240EH \$ 59.95 Ppd.

### SEE MUSIC IN PULSATING COLOR

New 3-Channel Color Organ adds to music listening pleasure, lets you modulate 3 independent strings of colored lamps with intensity of your music to create an audio "light show." They flash, vary in brightness related to music's rhythm, pitch, volume—pulsating lighting performance to music! Fully assembled & priced half that of others, the Edmund Sound To Light Control is a terrific value. Plug in, turn on!



- No. 42,309 EH (ASSEMBLED) \$17.95 Ppd.  
 No. 42,336 EH (UNASSEMBLED) \$13.95 Ppd.

### NEW VISUAL EFFECTS PROJECTOR

Revolutionary 2-WHEEL set lets you create wild far-out visual effects with no worry about nuts & bolts—you change programming as fast as you drop in a new disc! Attach any 35mm slide you have, or use your 35mm camera to program. Make rotating images, bleemer effects, Kaleidoscopic patterns, 3-D plus mind-blowing Moiré effects right on your screen. Incl. 2 internal drive motors, 3-way Kaleidoscope Lens, Hexidoscope, Lenticular Wheel, Moiré Wheel, instrs.



- Stock No. 72,071EH \$99.95 Ppd.

### WHICH ARE YOUR CRITICAL DAYS?

Can Bio-rhythm tell you? We're not sure, but we're told that vast mood shifts are caused by your body's Internal Time Clock whose rhythms can be charted ahead to possibly warn you of "critical" days. Some are great, some blah. Maybe it's your physical, emotional & intellectual rhythms converging at the right or wrong time. Compute your cycles with our Bio-rhythm kit and judge for yourself. Incl. Charting kit, metal Diagraph Calc. instrs.



- Stock No. 71,949 EH \$14.50 Ppd.  
 1 YR. PERSONALIZED REPORT—BY COMPUTER  
 Stock No. 19,200 EH (Send Birthdate) \$15.95 Ppd.

★ WHEN YOU COME TO PHILADELPHIA BE SURE TO SEE ★  
**FREE BICENTENNIAL LIGHT SHOW**  
 IN BARRINGTON, N.J. ONLY 10 MINUTES AWAY AT  
**EDMUND FACTORY STORE**

### He-Ne LASERS... \$115.00 up!



Top quality lasers feature TEM<sub>00</sub> mode, internal mirror plasma tubes w/10,000 hr. life, self-starting cold aluminum cathodes, low noise & ripple, guaranteed output power stability and more for demanding lab work. 18-mo. mfr. wty. 115v AC

- (A) 0.5mW... 0.88 Beam Dia., 1 mRad Diverg. \$115.00 Ppd.  
 #79,070 EH (2.6x8.5x14.8")  
 (B) 1.0mW... (as above) #79,073 EH \$150.00 Ppd.  
 (C) 4.0mW... 0.8 Beam Dia., 1.1 mRad Diverg. \$485.00 Ppd.  
 #79,079 EH (3.9x5.5x15.6")

### QUALITY DETECTOR UNDER \$40



New Edmund developed, fully transistorized BFO unit capable of locating quarter at 18"—powerful 6 trans. oscillator-amplifier circuit. Easily compares to others priced 50% higher! Aluminum pole and housing—not plastic! 6" waterproof search coil (Faraday shielded to elim. outside interference); long 50 hr battery (9V) life; powerful 2" speaker; 1-knob on-off tune control. Perfect balance; lightweight (2 lb). Great buy!

- Stock No. 80,222EH \$ 39.95 Ppd.  
 Deluxe Unit w/Earphones, Meter No. 80,134EH (11" Coil) \$169.00 Ppd.

### SOLAR ENERGY CUBE!



Unique demonstrator dramatically shows how sunlight converts to kinetic energy. Clear plastic Solar Energy Cube placed in the sun with its 3 highly efficient silicon solar cells powers the motor to whirl the propeller! Unit actually produces 1.5v DC, 825ma. Same cells found in our mighty panels. Speed directly related to sunlight available. Nothing to wear out! Great for executives, hobbyists, teachers.

- No. 42,287EH... (4X4X4") \$19.95 Ppd.

### NEW! COMPLETE "KIRLIAN" LAB



Self-contained! Super sensitive! Variable energy controls! All the most wanted electrophotography features in one compact unit to take B & W, color pix, without camera or lens. Terrific value! Includes: classic ringing oscillator circuit; glass covered electrode w/ optimum dielectric isolation (sensitivity/safety); timing adjust. to assure quality pix; more! AC & 12v DC.

- No. 72,106 EH (8x10x4") \$145.00 Ppd.  
 PRO MODEL: No. 72,053 EH \$399.00 Ppd.  
 "STARTER'S" KIT: No. 71,938 EH \$ 49.95 Ppd.

### KNOW YOUR ALPHA FROM THETA!



For greater relaxation, concentration, listen to your Alpha-Theta brainwaves. Ultra-sensitive electrode head-band slips on/off in seconds—eliminates need for messy creams, etc. Atch'd to amplifier, filters brainwaves, signals beep for ea. Alpha or Theta wave passed. Monitoring button simulates Alpha sound; audio & visual (L.E.D.) feedback. Reliable, easy-to-use unit—comparable to costlier models. Completely safe. Comprehensive instruction booklet.

- No. 1635 EH (8x3x4"; 24 oz.) \$149.50 Ppd.  
 LOW COST "STARTER" UNIT  
 No. 71,809 EH \$ 55.00 Ppd.

- DELUXE "ON" TIME MONITOR MEASURES & RECORDS %  
 No. 1652 EH \$299.95 Ppd.



## MAIL COUPON FOR GIANT FREE CATALOG!

164 PAGES • MORE THAN 4500 UNUSUAL BARGAINS

Completely new 1976 edition. New items, categories, illustrations. Dozens of electrical and electromagnetic parts, accessories. Enormous selection of Astronomical Telescopes. Unique lighting and ecological items. Microscopes, Binoculars, Magnifiers, Magnets, Lenses, Prisms. Hard-to-get surplus bargains. Ingenious scientific tools. 1000's of components.

EDMUND SCIENTIFIC CO.  
 300 Edscorp Building, Barrington, N.J. 08007  
 Please rush Free Giant Catalog "EH".

Name \_\_\_\_\_  
 Address \_\_\_\_\_  
 City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_




## COMPLETE AND MAIL WITH CHECK, M. O. OR CHARGE NO.

EDMUND SCIENTIFIC CO. 300 Edscorp Building, Barrington, N.J. 08007

How Many	Stock No.	Description	Price Each	Total
<input type="checkbox"/>		PLEASE SEND GIANT FREE CATALOG "EH"		
<input type="checkbox"/>		Charge my BankAmericard*		
<input type="checkbox"/>		Charge my Master Charge*		
Add Handling Chg.: \$1.00, Orders Under \$5.00 50¢, Orders Over \$5.00				
Interbank No. _____		I enclose <input type="checkbox"/> check <input type="checkbox"/> money order for TOTAL \$ _____		
My Card No. Is _____		Signature _____		
Card Expiration Date _____		Name _____		
30-DAY MONEY-BACK GUARANTEE.		Address _____		
You must be satisfied or return any purchase in 30 days for full refund. *\$15.00 minimum		City _____ State _____ Zip _____		
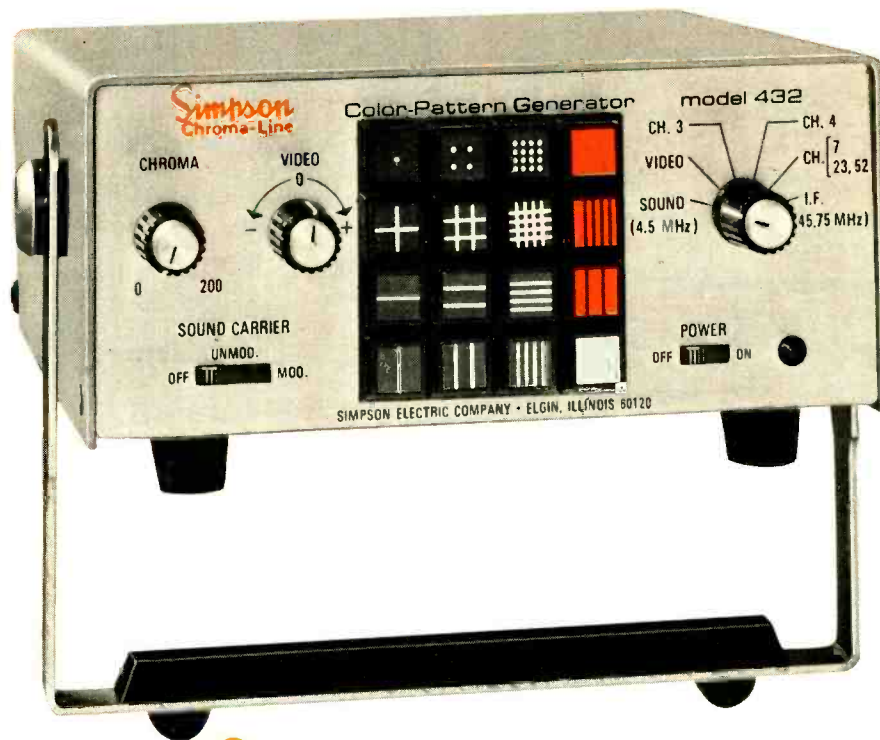
# A NEW DIMENSION

has been  
added to  
professional  
color TV  
servicing



The  
new

## Simpson<sup>®</sup> Model 432 Chroma-Line

### COLOR-PATTERN GENERATOR

*For Faster, Easier  
Color TV Servicing*

This new Simpson model is an all solid-state instrument incorporating the latest digital LSI and SSI technology for maximized color-pattern stability and reliability. Today's professional TV technicians will appreciate its many extra features and performance characteristics.

- 16 "touch command" patterns instantly available in a 4 x 4 pushbutton matrix
- 3 VHF channels: 3, 4 and 7, channels 3 and 4 fully crystal controlled
- 2 UHF channels: 23 and 52
- IF Output: 45.75 MHz
- Composite Video Output: Sync, pattern and sound
- Built-in cable storage compartment

- Sound Output: 4.5 MHz carrier, unmodulated and 1000 Hz FM modulated
- Adjustable RF, IF and Video signal level
- 75 Coax and 300  $\Omega$  Balun Outputs
- Red, Blue and Green gun killers
- Transformer-isolated, line powered, for instant-ready use

FOR COMPLETE SPECIFICATIONS, WRITE FOR BULLETIN T829

**MODEL 432** Complete with two cable assemblies, for Coax and 300 $\Omega$  inputs, and Operator's Manual ..... **\$179.**

AVAILABLE NOW FROM ELECTRONIC PART DISTRIBUTORS




### SIMPSON ELECTRIC COMPANY

853 Dundee Avenue, Elgin, Illinois 60120  
(312) 697-2260 • Telex: 72-2416 • Cable: SIMELCO



Circle 101 on reader service card

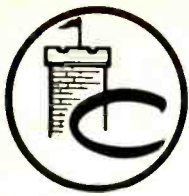

# CASTLE Timesavers ... for the Professional

## SUBBER® TV signal circuit analysts

Analyze the ENTIRE signal circuit system of any Color or Black & White Television receiver . . . by signal substitution.

Outputs at video i.f., sound i.f., video and audio.

- Inbuilt monopole antenna • Inbuilt loudspeaker • Video carrier level meter • Battery indicator meter


Use on the bench or in the home . . . anywhere.

Complete with 120vac wall plug-in transformer and matched test cables.



**MASTER SUBBER® Analyst Mk V net \$169.95**

**UHF-VHF  
TV tuner and i-f  
signal analyst  
120 VAC + Battery**

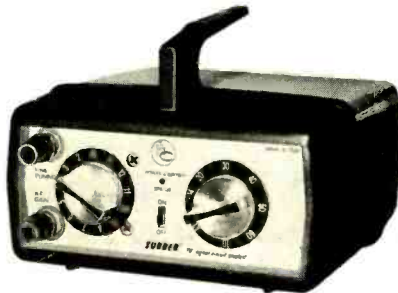

**Mark IV-CUV  
net \$64.95**

**TV tuner and i-f  
signal analyst  
120 VAC + Battery**



**Mark IV-C  
net \$54.95**

## MEZZER™ TV Field Strength Meters

Use for measurements of TV signals in:—


- Antenna installation • Antenna evaluation • CATV
- MATV • Output calibration of TV signal generators.

### TV Service VHF Field Strength Meter

- Simple to operate
- Measures 300uV to 30,000uV.
- Uses ordinary 9v transistor batteries

**Model TVS**


**net \$69.95**

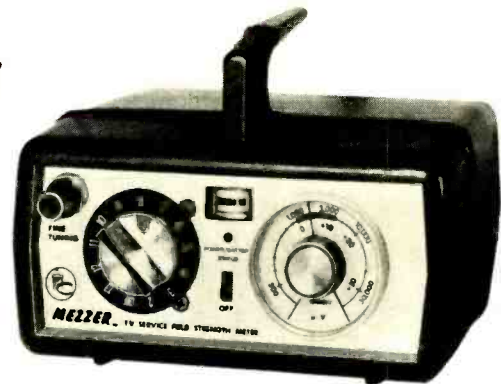

### VHF Field Strength Meter

Range: 20 microvolts to 100 millivolts.  
Attenuator: x 1, x 10, x 100.  
Inputs: 75 & 300 ohms.  
120vac & batteries

**Model FSM-V  
net \$119.95**

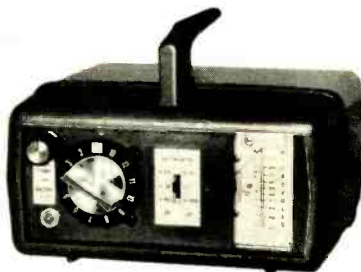

### UHF Field Strength Meter

Range: 20 microvolts to 10 millivolts.  
Attenuator: x 1 and x 10.  
Inputs: 75 & 300 ohms.  
120vac & batteries

**Model FSM-U  
net \$99.95**



Castle products — advanced technology — modern styling — and they work!

Ask your electronic distributor for them . . . or write for more details.

# CASTLE ELECTRONICS, INC.

5715 N. Western Ave., Chicago, Ill. 60645  
Ph. (312) 728-1800

Circle 102 on reader service card