

Radio-Electronics

THE MAGAZINE FOR NEW IDEAS IN ELECTRONICS

**6-Foot
PROJECTION TV KIT**
Exclusive preview

SUPER HI-FI AMP
You can build

CUSTOMIZE PC BOARDS
Reconfigure existing circuits


BETTER DOLBY
Improved noise reduction

AUDIO OSCILLATORS
Measurements you can do

TRS-80 BREADBOARD
Build this interface

TELEPHONE DIALERS
What's available now

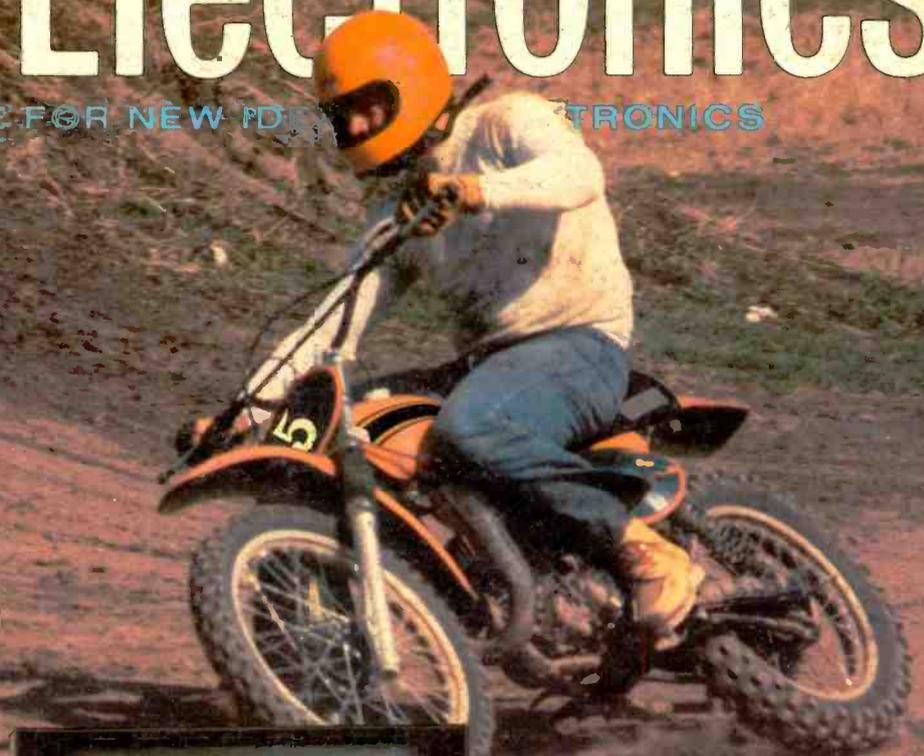DRUM SYNTHESIZER
More accessories to build



PLUS:

- ★ CET Test
- ★ Service Clinic
- ★ Equipment Reports
- ★ Communications Corner
- ★ REAL Sound Lab Test Report

64H108 SLI 7810EQ97 04 A MAY82
L309283021
STEVE S SULIK
7810 EVA ST
PHILADELPHIA PA 19128

12

The 90-minute miracle


Solderless saves time like you wouldn't believe. Our Proto-Board® solderless breadboards put everything you need to get your circuit up and running on an aluminum backplane that lets you work at frequencies from DC to half a Giga-Hertz. Three Proto-Board® models feature built-in regulated power supplies—and one of them's a build-it-yourself kit!

CSC solderless breadboards save energy, too. Especially yours. Because circuit building becomes a simple plug-and-chug process, straight from an idea to a working circuit.

That's why we've become the easiest-to-find solderless breadboards in the world—available at more stores than anybody else in the business. Because people who know solderless best insist on CSC.

Save time and energy. Get a head start with CSC.

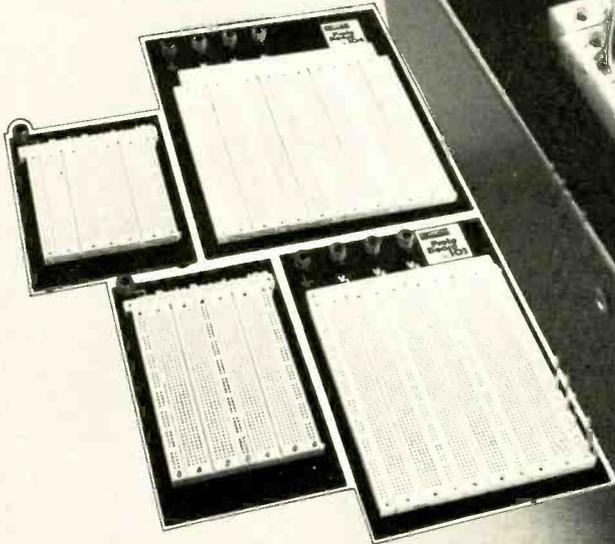There are 9 Proto-Boards® in all, manufacturer's suggested U.S. resale prices from \$15.95 to \$124.95.



CONTINENTAL SPECIALTIES CORPORATION



70 Fulton Terrace, New Haven, CT 06509 (203) 624-3103, TWX 710-465-1227

OTHER OFFICES: San Francisco: (415) 421-8872, TWX 910-372-7322

Europe: CSC UK LTD. Phone Saffron-Walden 0799-21682, TLX 817477

Canada: Len Finkler Ltd., Ontario


1-800-243-6077
Call toll-free for details

* Suggested U.S. resale. Available at selected local distributors. Prices & specifications subject to change without notice.
© Copyright 1979 Continental Specialties Corporation

CIRCLE 9 ON FREE INFORMATION CARD

www.americanradiohistory.com

STEREO BREAKTHROUGH

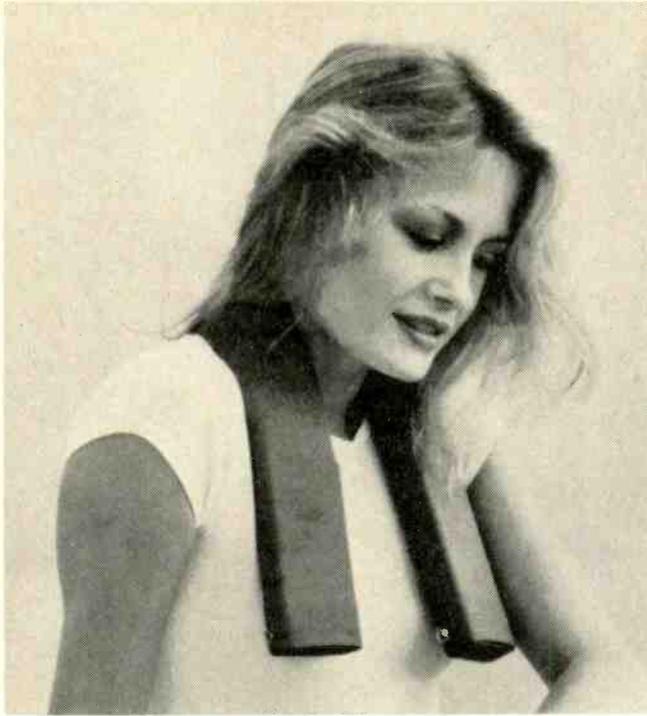

Bone Fone^{T.M.}

A new concept in sound technology may revolutionize the way we listen to stereo music.

The Bone Fone surrounds your entire body with a sound almost impossible to imagine.

You're standing in an open field. Suddenly there's music from all directions. Your bones resonate as if you're listening to beautiful stereo music in front of a powerful home stereo system.

But there's no radio in sight and nobody else hears what you do. It's an unbelievable experience that will send chills through your body when you first hear it.

AROUND YOU

And nobody will know you're listening to a stereo. The entire sound system is actually draped around you like a scarf and can be hidden under a jacket or worn over clothes.

The Bone Fone is actually an AM/FM stereo multiplex radio with its speakers located near your ears. When you tune in a stereo station, you get the same stereo separation you'd expect from earphones but without the bulk and inconvenience. And you also get something you won't expect.

INNER EAR BONES

The sound will also resonate through your bones—all the way to the sensitive bones of your inner ear. It's like feeling the vibrations of a powerful stereo system or sitting in the first row listening to a symphony orchestra—it's breathtaking.

Now you can listen to beautiful stereo music everywhere—not just in your living room. Imagine walking your dog to beautiful stereo music or roller skating to a strong disco beat.

You can ride a bicycle or motorcycle, jog and even do headstands—the Bone Fone stays on no matter what the activity. The Bone Fone stereo brings beautiful music and convenience to every indoor and outdoor activity without disturbing those around you and without anything covering your ear.

SKI INVENTION

The Bone Fone was invented by an engineer who liked to ski. Every time he took a long lift ride, he noticed other skiers carrying transistor radios and cassette players and wondered if there was a better way to keep your hands free and listen to stereo music.

So he invented the Bone Fone stereo. When he put it around his neck, he couldn't believe his ears. He was not only hearing the music

and stereo separation, but the sound was resonating through his bones giving him the sensation of standing in front of a powerful stereo system.

AWARDED PATENT

The inventor took his invention to a friend who also tried it on. His friend couldn't believe what he heard and at first thought someone was playing a trick on him.

The inventor was awarded a patent for his idea and brought it to JS&A. We took the idea and our engineers produced a very sensitive yet powerful AM/FM multiplex radio called the Bone Fone.

The entire battery-powered system is self-contained and uses four integrated circuits and two ceramic filters for high station selectivity. The Bone Fone weighs only 15 ounces, so when worn over your shoulders, the weight is not even a factor.

BUILT TO TAKE IT

The Bone Fone was built to take abuse. The large 70 millimeter speakers are protected in flexible water and crush resistant cases. The case that houses the radio itself is made of rugged ABS plastic with a special reinforcement system. We knew that the Bone Fone stereo may take a great deal of abuse so we designed it with the quality needed to withstand the worst treatment.

The Bone Fone stereo is covered with a sleeve made of Lycra Spandex—the same material used to make expensive swim suits, so it's easily washable. You simply remove the sleeve, dip it in soapy water, rinse and let the sleeve dry. It's just that easy. The entire system is also protected against damage from moisture and sweat making it ideal for jogging or bicycling.

The sleeve comes in brilliant Bone Fone blue—a color designed especially for the system. An optional set of four sleeves in orange, red, green and black is also available for \$10. You can design your own sleeve using the pattern supplied free with the optional kit.

YOUR OWN SPACE

Several people could be in a car, each tuned to his own program or bring the Bone Fone to a ball game for the play by play. Cyclists,

joggers, roller skaters, sports fans, golfers, housewives, executives—everybody can find a use for the Bone Fone. It's the perfect gift.

Why not order one on our free trial program and let your entire family try it out? Use it outdoors, while you drive, at ball games or while you golf, jog or walk the dog. But most important—compare the Bone Fone with your expensive home stereo system. Only then will you fully appreciate the major breakthrough this product represents.

GET ONE SOON

To order your Bone Fone, simply send your check or money order for **\$69.95** plus \$2.50 postage and handling to the address shown below. (Illinois residents add 5% sales tax.) Credit card buyers may call our toll-free number below. Add \$10 if you wish to also receive the accessory pack of four additional sleeves.

We'll send you the entire Bone Fone stereo complete with four AA cell batteries, instructions, and 90-day limited warranty including our prompt service-by-mail address.

When you receive your unit, use it for two weeks. Take it with you to work, or wear it in your car. Take walks with it, ride your bicycle or roller skate with it. Let your friends try it out. If after our two-week free trial, you do not feel that the Bone Fone is the incredible stereo experience we've described, return it for a prompt and courteous refund, including your \$2.50 postage and handling. You can't lose and you'll be the first to discover the greatest new space-age audio product of the year.

Discover the freedom, enjoyment, and quality of the first major breakthrough in portable entertainment since the transistor radio. Order a Bone Fone stereo at no obligation, today. *Pending FCC approval.

JS&A PRODUCTS
THAT THINK[®]

Dept. RE One JS&A Plaza
Northbrook, Ill. 60062 (312) 564-7000
Call TOLL-FREE 800 323-6400
In Illinois Call (312) 564-7000

© JS&A Group, Inc., 1979

HITACHI OSCILLOSCOPES

Single and dual trace, 15 and 30 MHz. All four high sensitivity Hitachi oscilloscopes are built to demanding Hitachi quality standards and are backed by a 2-year warranty. They're able to measure signals as low as 1mV/division (with X5 vertical magnifier). It's a specification you won't find on any other 15 or 30 MHz scopes. Plus: Z-axis modulation, trace rotation, front panel X-Y operation for all four scope models, and X10 sweep magnification. And, both 30 MHz oscilloscopes offer internal signal delay lines. For ease of operation, functionally-related controls are grouped into three blocks on the color coded front panel. Now here's the clincher: For what you'd expect to pay more, you actually pay less. Suggested list price of our top line V-302 dual trace 30 MHz is only \$945.00. The other models comparably less. Check our scopes before you decide.

Hitachi...The measure of quality.


- V-302 30 MHz Dual Trace \$945.00
- V-301 30 MHz Single Trace \$745.00
- V-152 15 MHz Dual Trace \$695.00
- V-151 15 MHz Single Trace \$545.00



HITACHI

Hitachi Denshi America, Ltd.

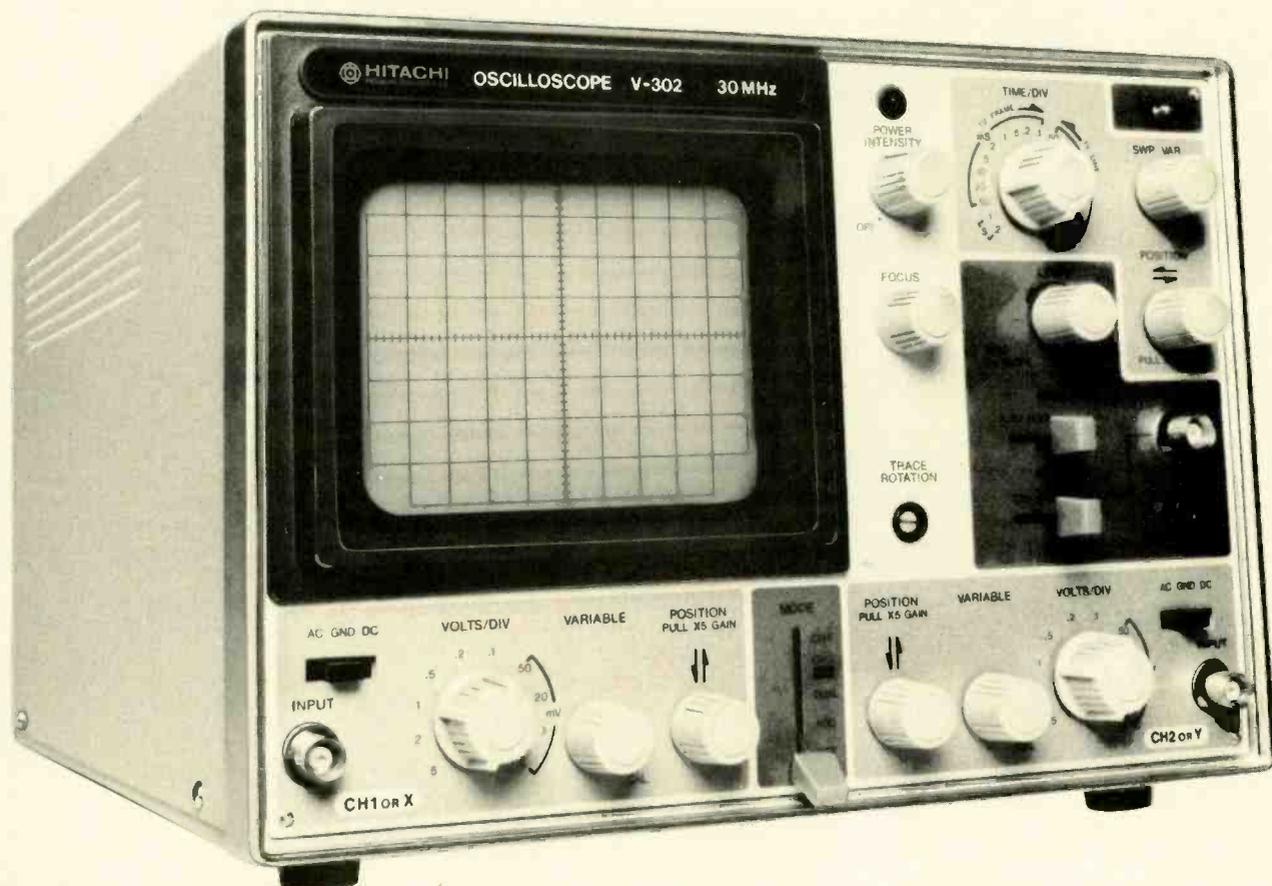For more information, contact
Hitachi Denshi America, Ltd.,
175 Crossways Park West, Woodbury, N.Y. 11797
(516) 921-7200.



More sensitive to your input.

Radio-Electronics®

THE MAGAZINE FOR NEW IDEAS IN ELECTRONICS

Electronics publishers since 1908

DECEMBER 1979 Vol. 50 No. 12



- BUILD**
- 47 **PERCUSSION SYNTHESIZER ACCESSORIES**
Add a snare synthesizer and sequencer to expand your music system. **James Barbarello**
 - 51 **TRS-80 BREADBOARD**
Part 2: Interfaces the TRS-80 with all the circuits that are used when designing or prototyping. **Jon Titus, Chris Titus, David Larsen**
 - 55 **SUPER AUDIO AMPLIFIER**
Bridge-type power-output configuration lets you use inexpensive transistors to provide a wide frequency response and a 100 dB signal-to-noise ratio. **Dan Talbot**

- TECHNOLOGY**
- 5 **LOOKING AHEAD**
Tomorrow's news today. **David Lachenbruch**
 - 43 **TELEPHONE DIALER ROUNDUP**
Part 2: A look at the equipment and how it works. **Fred Blechman**
 - 64 **CUSTOMIZE YOUR PC BOARDS**
How to re-work finished PC boards so that they fit into desirable cabinets. **Earl "Doc" Savage, K4SDS**
 - 66 **ALL ABOUT AUDIO OSCILLATORS**
How to get the most out of your test equipment. **Charles Gilmore**
 - 78 **STATE-OF-SOLID STATE**
Two new IC's make a DMM. **Karl Savon**

- VIDEO**
- 39 **6-FOOT PROJECTION TV FROM A KIT**
Heath's newest TV saves you dollars. **Larry Steckler**
 - 70 **CET TEST**
Check your technical knowledge. **Dick Glass**
 - 83 **JACK DARR'S SERVICE CLINIC**
Identifying blanking problems. **Jack Darr**
 - 84 **SERVICE QUESTIONS**
R-E's Service Editor solves technician problems.

- STEREO**
- 58 **DOLBY HX NOISE REDUCING SYSTEM**
New Dolby system for tape provides better headroom. **Len Feldman**
 - 61 **R.E.A.L. SOUND LAB TESTS SHERWOOD RECEIVER**
Sherwood model S-7210CP
AM/FM receiver earns a "very good". **Len Feldman**

- RADIO**
- 74 **COMMUNICATIONS CORNER**
Directional Wattmeter—What it will do for you. **Herb Friedman**

- EQUIPMENT REPORTS**
- 24 **LEADER LCR-740 LCR BRIDGE**
 - 32 **MFJ-721 COMMUNICATIONS FILTER**
 - 33 **MICRO SOFTWARE SYSTEMS PET PROGRAMS**
 - 34 **SST T-4 ANTENNA TUNER**


- DEPARTMENTS**
- | | |
|-------------------------------------|---------------------------|
| 120 ADVERTISING INDEX | 99 MARKET CENTER |
| 16 ADVERTISING SALES OFFICES | 92 NEW PRODUCTS |
| 16 EDITORIAL | 90 STEREO PRODUCTS |
| 121 FREE-INFORMATION CARD | 12 WHAT'S NEWS |
| 22 LETTERS | |

ON THE COVER

Projection TV is one of the most rapidly growing consumer products available today. This newest set comes in a kit and delivers 6-foot pictures. Learn more about it. Turn to page 39 now.



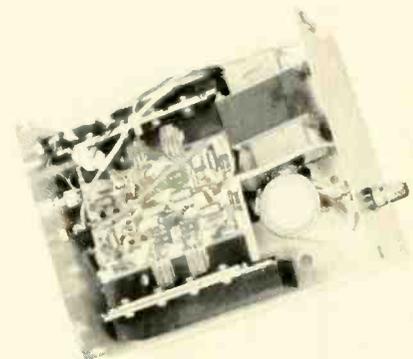FREEDOM DIALER IS JUST ONE of the many electronic telephone dialers covered in this issue. To see them all turn to page 43.



SUPER AUDIO AMPLIFIER has a bridge-type power-output configuration you'll want to know more about. Find the details on page 55.

Radio-Electronics, Published monthly by Gernsback Publications, Inc., 200 Park Avenue South, New York, NY 10003. Phone: 212-777-6400. Controlled Circulation Postage Paid at Concord, NH. One-year subscription rate: U.S.A. and U.S. possessions, \$9.98, Canada, \$12.98. Other countries, \$14.98. Single copies \$1.25. © 1979 by Gernsback Publications, Inc. All rights reserved. Printed in U.S.A. (ISSN 0033-7862)

Subscription Service: Mail all subscription orders, changes, correspondence and Postmaster Notices of undelivered copies (Form 3579) to Radio-Electronics Subscription Service, Box 2520, Boulder, CO 80322.

A stamped self-addressed envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

As a service to readers, Radio-Electronics publishes available plans or information relating to newsworthy products, techniques and scientific and technological developments. Because of possible variances in the quality and condition of materials and workmanship used by readers, Radio-Electronics disclaims any responsibility for the safe and proper functioning of reader-built projects based upon or from plans or information published in this magazine.

Six professional scopes offer build-it-yourself savings.

Save up to 46% when you build it yourself.

Only in the Heathkit Catalog will you find this selection of six professional oscilloscopes, each with its own special features and low price. Compare Heathkit prices with similar assembled scopes and see how much you can save when you build it yourself.

Heathkit Model	Trace	Bandwidth MHz	Vertical Sensitivity*	Delay Lines	Regulated high voltage	Mu-metal shielding	Low kit price
IO-4235	dual	DC-35	2mV/cm to 10V/cm	yes	yes	full	\$869.95
IO-4510	dual	DC-15	1mV/cm to 5V/cm	yes	yes	full	\$649.95
IO-4550	dual	DC-10	10mV/cm to 20V/cm	no	yes	full	\$399.95
IO-4555	single	DC-10	10mV/cm to 20V/cm	no	yes	full	\$349.95
IO-4205	dual	DC-5	10mV/cm	no	no	partial	\$279.95
IO-4105	single	DC-5	10mV/cm	no	no	partial	\$199.95

*Under full bandwidth


Heathkit manuals make kitbuilding easy



Easy-to-follow Heathkit assembly manuals take you step by step from unpacking to final plug-in. Anyone can do it. And when you build it yourself, you can service it yourself.

Your manual becomes a handy service guide.

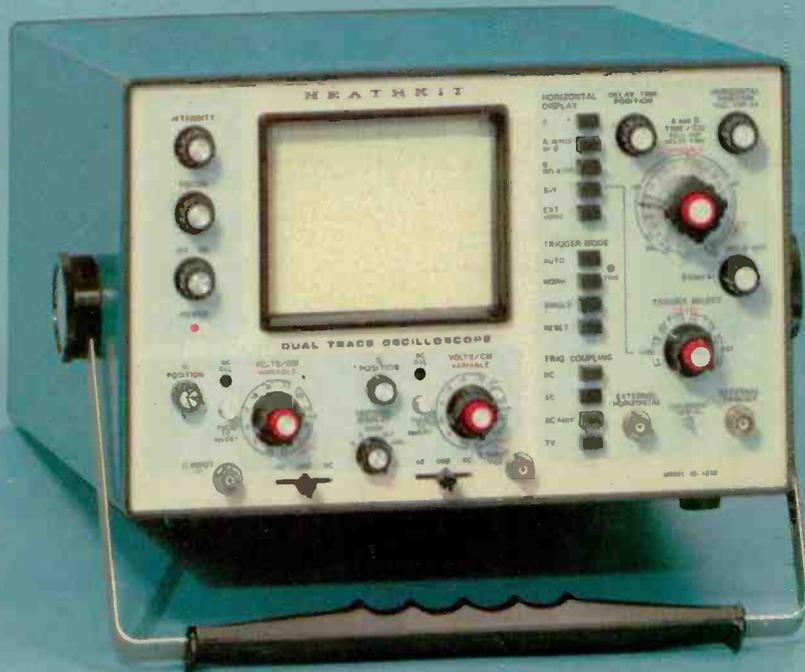Replacement parts are readily available from the Heathkit factory or from Heathkit Electronic Centers. And experienced service techs are just a phone call away to help you during building or servicing.



FREE Catalog



Complete details on Heathkit Oscilloscopes and nearly 400 other Heath electronic kits for your home, work or pleasure are in the new Heathkit Catalog. Send for yours today or pick one up at your Heathkit Electronic Center.

Heathkit®

Heathkit Products are also sold and serviced at Heathkit Electronic Centers (Units of Schlumberger Products Corp.) in major cities throughout the U.S. See your white pages.

Heath Company, Dept. 020-600, Benton Harbor, MI 49022

GX-371

looking ahead

IBM into videodiscs: Mighty IBM has formed a partnership with MCA Inc. to develop and manufacture videodiscs. The new joint venture, DiscoVision Associates, takes over MCA's optical videodisc plant in California as well as its 50% ownership (with Pioneer) in Universal Pioneer, the Japanese company that manufactures optical videodisc players. MCA will continue to market videodiscs for both the player made by Universal Pioneer and the one made by Magnavox. IBM says its primary interest isn't in the consumer market at the present time, and it's understood to believe that the disc is ideally adaptable to many different information-handling applications, including—but certainly not limited to—entertainment. The formation of DiscoVision Associates, with IBM as a partner, appears to assure the development of the optical disc into a major product for commercial, industrial and educational as well as entertainment use.

OK for modulators: The FCC acted to stamp out a growing black market for RF modulators that connect personal computers to TV sets—by legalizing them. The Commission, responding to a petition by Texas Instruments, said it would permit sale of these devices in the future if their manufacturers certify that they comply with radiation regulations. In the past, computers that *included* modulators (in other words, were designed to be attached to a TV's antenna terminals) were OK if tested and approved by FCC Labs, but the rules forbade sale of modulator attachments. The new ruling is expected to save money for home computer users, letting them use home sets as an alternative to monitors.

Excitement over LVR: The first U.S. demonstration of a longitudinal video recorder (LVR) got rave reviews from American manufacturers and recording experts. Demonstrated by Toshiba (see **Radio-Electronics**, July 1979), the system was invented by Norikazu Sawazaki, inventor of helical-scan recording, who described the technique as "the second generation in VTR's" and forecast it would become "the most advanced and least expensive on the market." The LVR represents a return to the longitudinal-track fixed-head method used in audio tape recorders.

BASF demonstrated an LVR two years ago in Germany and is setting up a plant in Fountain Valley, California, to produce it for the U.S. and European markets. BASF's multiple-track recorder uses a two-reel cassette, records one track, rapidly reverses direction and records the next track, then reverses again, and so forth. Toshiba's system is somewhat similar, but with one major difference—the tape continually moves in the same direction without reversing direction or even changing speed at the end of each track. This is accomplished by use of a single-reel endless-loop cassette.

Toshiba's LVR uses a cassette with 100 meters of half-inch tape, passing a fixed head at 6 meters-per-second (about 236 inches-per-second), with 220 parallel longitudinal tracks. At the end of each track, the head merely moves down to the next track. Each track takes 17 seconds to record, and an MPU random-access keyboard thus can locate any part of the one-hour recording in 17 seconds. The developmental machine demonstrated was about half

the size of a conventional VCR (but had no tuner or timer). Toshiba says it has one-third the mechanical parts of a conventional VCR and can be produced to sell at about half the price—or around \$500 retail. An interesting byproduct is that, at least theoretically, pre-recorded tapes could be replicated at $\frac{1}{220}$ th of real time (an hour tape in 17 seconds) by laying down all the tracks at the same time. Toshiba says it could produce the machine in about a year, hopes for further miniaturization to make possible a hand-carried combination VCR-color camera (after the perfection of a CCD camera, still a couple of years away). The latest version of BASF's LVR is scheduled for demonstration in Europe this fall—presumably in a production model. I hope to bring you an eye-witness report.


UHF tuning: About 40% of all color sets produced in the first half of 1979, and virtually no black-and-white sets, used all-electronic varactor tuning. Some day, perhaps, all sets will be electronically tuned. However, the FCC seems to want some day to come much sooner, and is considering proposing a rule requiring TV manufacturers to build electronic tuners into all TV sets to improve UHF reception and make UHF tuning completely comparable to VHF tuning. FCC staff members are currently studying whether the Commission has the authority to require this kind of change in tuning systems. The FCC's intentions were revealed at an FCC meeting when the UHF Comparability Task Force presented the results of its study to the Commission. The study found that UHF stations suffer in comparison to VHF because of lack of tuning comparability, poorer picture quality due to low signal strength, and comparatively poorer programming.

Antenna safety: Although there are now mandatory safety labels for CB and TV antennas, the Consumer Products Safety Commission says this isn't enough to stem an alarming tide of electrocutions, most of them resulting from contact with power lines while the antennas are being installed. So the Commission is asking for proposed safety standards for omnidirectional CB base-station antennas, in an attempt to make them electrocution-proof. The CPSC says that antennas are the major cause of electrocution among consumer products, estimates 220 people were electrocuted while installing communications antennas in 1975, 275 in 1976 and 220 in 1977. Only 100 lost their lives last year, largely as the result of poor CB sales.

Home earth stations: The first three private satellite earth stations approved by FCC since its go-ahead for home reception all involved \$20,000 systems built by Homesat with 4.6-meter dishes in remote rural areas. Other firms are starting to offer lower prices. Channel One, Newton, Mass., is offering a 3-meter installation for \$15,000. The Starscan Division of Gardiner is quoting \$11,000, and Avcom of Richmond, Va., has a do-it-yourself system at \$4,000. Nippon Electric says it could offer half-meter home earth stations in the U.S. for \$350 to \$500, but this would require quantity orders and the authorization to the K-band (12-14 GHz).

DAVE LACHENBRUCH
CONTRIBUTING EDITOR

Facts from Fluke on low-

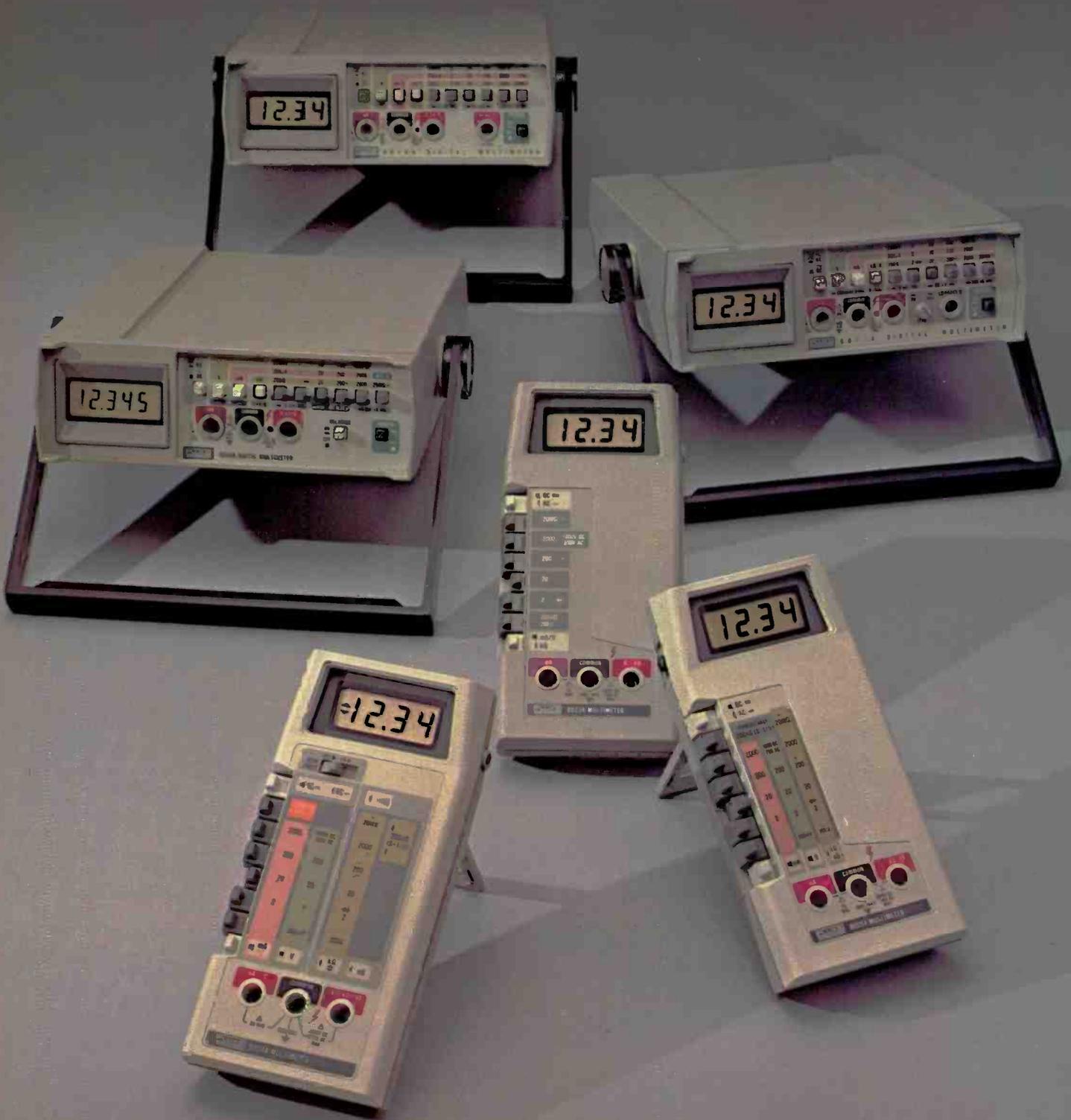

cost digital multimeters.

When you're looking for genuine value in a low-cost DMM you have a lot more to consider than price. You need information about ruggedness, reliability and ease of operation. Accuracy is important. And so are special measurement capabilities. But above all, you must consider the source, and that company's reputation for service and support.

Fact is, as electronics become more a part of our daily lives, dozens of new manufacturers are rushing to market their "new" DMM's. In theory, this is healthy; but in practice, crowding is confusion.

To help you deal with this flood of new products, here are some facts you should know about low-cost DMM's.

The economics of endurance.

Even the least expensive DMM isn't disposable. Accidents happen, and test instruments should be built to take the abuses of life as we live it.

Look for a DMM with a low parts count for reliability, and rugged internal construction protected by a high-impact shell. Make sure the unit meets severe military tests for shock and vibration.

Another feature to check out is protection against overloading, whether from unexpected inputs, transients, or human errors.

Just for the record, all Fluke low-cost DMM's meet or exceed military specs, and feature extensive overload protection.

The importance of being honest.

Just because a multimeter is digital doesn't mean it's automatically more accurate than a VOM - even though the LCD might give you that impression. The benchmark for accuracy in DMM's is *basic dc accuracy*. The specs will list it as a percentage of the reading for various dc voltage ranges.

Of course accuracy is more critical in some applications than others, and increasing precision and resolution in a DMM usually means increasing price. In the Fluke line, you can choose a model with a basic accuracy of 0.25% (the 8022A), others rated at 0.1%, or the new 8050A bench/portable at 0.03%.

Special measurements: getting more from your DMM.

Actually, for all the variations in size, shape and semantics, most DMM's perform five basic measurements: ac and dc voltage and current, and resistance. Prices vary according to the number of ranges and functions a DMM delivers.

	PRODUCT	FUNCTIONS	RANGES	DIGITS	BASIC DC ACCURACY	CONDUCTANCE OTHER SPECIAL FEATURES	PRICE
HANDHELD MODELS	8022A	6	24	3½	0.25%	Basic six-function DMM; lowest-priced	\$129
	8020A	7	26	3½	0.1%	X High accuracy; pioneer in conductance; exclusive two year warranty.	\$169
	8024A	9	26	3½	0.1%	X Direct temperature readings; continuity/ input level detector with selectable audible signal; peak hold capability.	Available soon
BENCH/PORTABLES	8010A	7	31	3½	0.1%	X True RMS; extra 10A range.	\$239
	8012A	7	31	3½	0.1%	X True RMS; two extra low resistance ranges.	\$299
	8050A	9	39	4½	0.03%	X True RMS; selectable reference impedances with direct readouts in dBm; offset feature.	\$329

The Fluke line includes DMM's with from 24 to 39 ranges, 3½ and 4½-digit resolution, and some unique functions you won't find in any other DMM. Additional measurement capabilities like temperature, dB, conductance and circuit level detection.

If your work involves temperature measurements, the new 8024A delivers direct temperature readings via any K-type thermocouple. This is especially useful in testing component heat rise and checking refrigeration systems.

Another talented instrument is our new 8050A bench/portable. The micro-processor-based 8050A features a self-calculating dB mode in which dBm readings are displayed automatically referenced to one of 16 selectable impedance ranges - a real timesaver when servicing audio equipment.

And of course no discussion of DMM's is complete without considering conductance - a Fluke exclusive featured on five of our low-cost DMM's - which allows you to make accurate resistance measurements to 100,000 Megohms. You can't do that with any ordinary multimeter, but it's a must for checking leakage in capacitors and measuring transistor gain.

A handful of efficiency.

When every minute matters, your schedule is tight and so is your work space, you need a portable DMM that's fast and easy to operate. We designed our handheld DMM's with color-coded in-line pushbuttons for true one-hand operation: no need to hang onto the meter with one hand while twisting a

rotary dial with the other.

But there's more to convenience than fingertip control. The 8024A, for example, is also designed to function as an instant continuity tester, with a selectable audio tone to indicate shorts or opens. It also has a peak hold feature to capture transients.



A word about warranties.

Last but not least, look closely at the company that manufactures a low-cost DMM. Their service is just as important as their product. Look for no-nonsense warranties, a large family of accessories, an established network of service centers and technical experts you can rely on.

That's how you'll recognize a knowledgeable supplier of low-cost DMM's, a company with experience, resources and a commitment to leadership in the industry.

Incidentally, you'll find it all at Fluke.

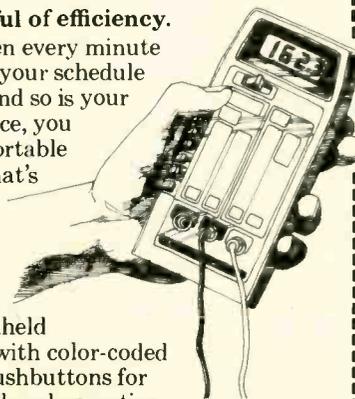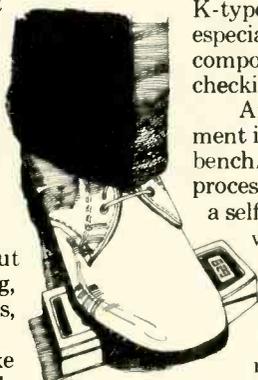Look for more facts from Fluke in future issues of this publication. Or call toll free 800-426-0361; use the coupon below; or contact your Fluke stocking distributor, sales office or representative.



IN THE U.S. AND NON-EUROPEAN COUNTRIES:
 John Fluke Mfg. Co., Inc.
 P.O. Box 43210 MS#2B
 Mountlake Terrace, WA 98043
 (206) 774-2481
 Telex: 32-0013

IN EUROPE:
 Fluke (Holland) B.V.
 P.O. Box 5053, 5004 EB
 Tilburg, The Netherlands
 (013) 673 973
 Telex: 52237

- Please send the facts on Fluke low-cost DMM's - specifications, applications information, and selection considerations.
- Please have a salesman call.

Name _____

Title _____ Mail Stop _____

Company _____

Address _____


City _____ State _____ Zip _____

Telephone () _____ Ext. _____

For literature circle no. 33 RE 12/79

New from NRI! **25" color TV that tunes** DIAGONAL **by computer, programs** **an entire evening's** **entertainment.**

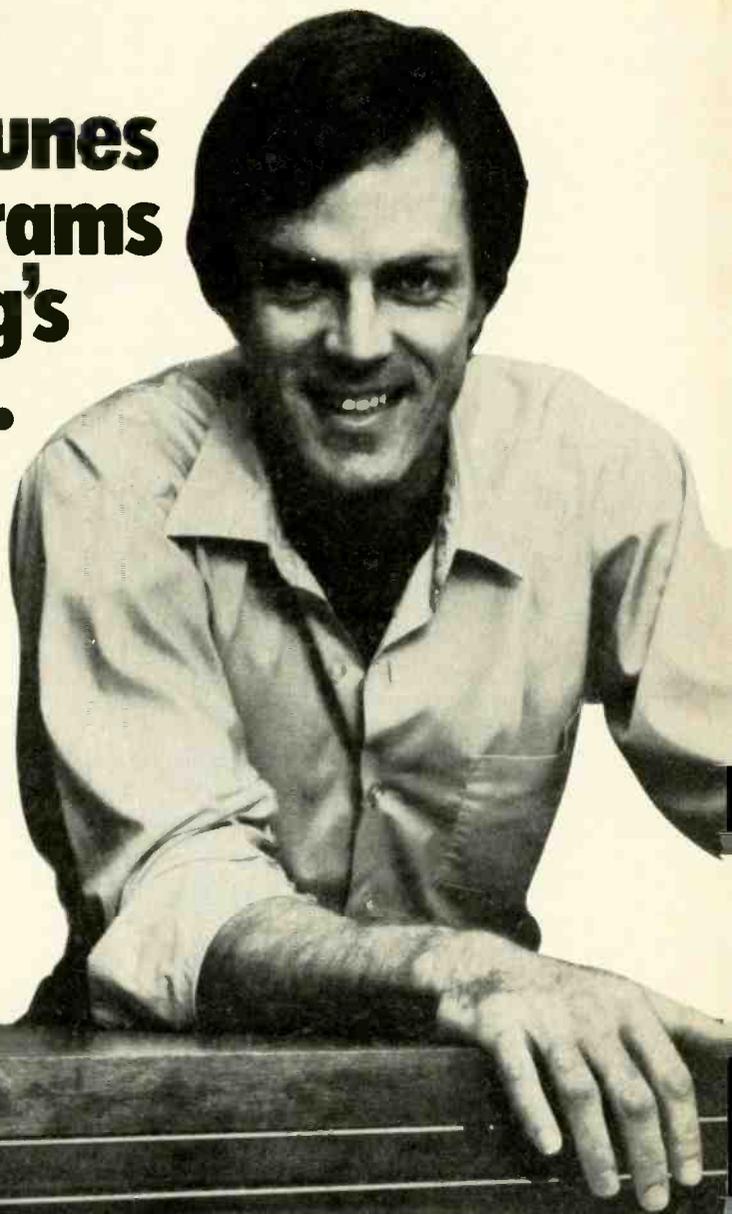Just part of NRI's training in servicing TV, stereo systems, video tape and disc players, car and portable radios.



STAGE-PAID

OUR
ALOG.

LESMAN
CALL.

NEW FROM NRI...

- TV/Audio/Video servicing courses with computerized TV that programs an entire evening's entertainment
- All-new Computer Electronics courses with designed-for-learning microcomputer you build and keep
- New Professional Appliance Servicing courses with training in solid-state and electronic controls
- Complete Communications course with digitally synthesized transceiver you assemble as you learn



Name _____ (Please Print) _____ Age _____

Street _____

City _____ State _____ Zip _____

Accredited by the Accrediting Commission of
the National Home Study Council

3-129

CHECK ONE:

- Color TV, Audio, and Video System Servicing
- Computer Electronics Including Microcomputers
- Communications with CB • Complete Communications Electronics • FCC Licenses • Aircraft Electronics • Mobile Communications • Marine Electronics
- CB Specialist Course
- Amateur Radio • Basic and Advanced Courses
- Industrial & Business Electronics • Digital Electronics • Electronic Technology • Basic Electronics
- Small Engine Servicing
- Electrical Appliance Servicing
- Automotive Mechanics
- Auto Air Conditioning Specialist
- Air Conditioning, Refrigeration, Heating and Solar Technology Courses

All career courses approved under GI Bill. Check for facts.

RADIO ELECTRONICS



UNITED STATES

BUSINESS REPLY CARD

FIRST CLASS PERMIT NO. 10008 WASHINGTON, D.C.

POSTAGE WILL BE PAID BY ADDRESSEE

NRI Schools
McGraw Hill Continuing
Education Center
3939 Wisconsin Avenue
Washington, D.C. 20016



Only NRI home training prepares you so thoroughly for the next great leap forward in TV and audio... digital systems. Already, top-of-the-line TV's feature digital tuning, computer programming is appearing, and new digital audio recording equipment is about to go on the market.

NRI is the only home study school to give you the actual "hands-on" training you need to handle servicing problems on tomorrow's electronic equipment. Because only NRI includes this designed-for-learning, 25" diagonal color TV with electronic tuning, built-in digital clock, and computer programmer as part of your training. With this advanced feature, you can pre-program an entire evening's entertainment... even key lock it in to control children's viewing.

As you assemble it, you learn how digital tuning systems work, how to adjust and service them. You work with the same advanced features used in the new programmable TV's and video tape recorders. It's exclusive NRI training that keeps you up with the leading edge of technology.

**Exclusive
Designed-for-learning
Concept**

The color TV you build as part of NRI's Master Course looks, operates, and performs like the very finest commercial sets. But behind that pretty picture is a unique designed-for-learning chassis...



the only such unit in the world. Rather than retrofit lessons to a hobby kit or an already-built commercial set, NRI instructor/engineers have designed this television so each step of construction is a learning experience.

As you build it, you perform meaningful experiments. You see what makes each circuit work, what it does, how it interacts with other circuits. You even introduce defects, troubleshoot and correct them as you would in actual practice. And you end up with a magnificent, big-picture TV with advanced features. One you can sell or use in your home.

**Also Build Stereo,
Test Instruments**

That's just a start. You demonstrate basic principles and circuits on the unique NRI Discovery Lab[®] then apply them as you assemble a fine AM/FM stereo receiver, complete with speakers. You also get practical experience as you build your own test instruments, including a 5" triggered sweep oscilloscope, CMOS digital frequency counter, color bar generator, and transistorized volt-ohm meter. Use them for learning, use them for earning as a full- or part-time TV, audio, and video systems technician.

**Complete, Effective Training
Includes Video Systems**

Using NRI's exclusive methods, you learn far more than TV servicing. You'll be prepared to work with stereo systems, car radios, record and tape players, transistor radios, short-wave receivers, PA systems, musical instrument amplifiers, electronic TV games, even video tape recorders and tape or disc


video players. Your training covers just about every kind of electronic entertainment equipment available now or in the near future.

And because NRI has unmatched experience gained in over 60 years and a million students worth of training, your course is designed for ease of learning and practical utility. You need no previous experience of any kind. Starting with the basics, exclusive "bite-size" lessons cover subjects thoroughly, clearly, and concisely. "Hands-on" experiments reinforce theory for better comprehension and retention. And your personal NRI instructor is always available for consultation, ready with explanations, answers, and advice.

**Send for Free
Detailed Catalog...
No Salesman Will Call**

Get all the facts on this exciting course and its potential for you by mailing the postage-paid card today. Our free 100-page catalog includes color photos of all kits and equipment, complete lesson plans, convenient time payment plans, and information on other electronics courses. You'll also find out about NRI's new Computer Technology

Course that includes your personal

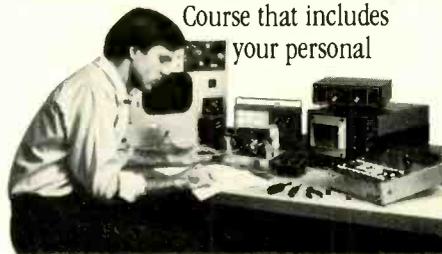

microcomputer. Or Complete Communications with 2-meter transceiver that gets you ready for opportunities in broadcasting, 2-way radio, microwave, and other growing fields. If card has been removed, write to:



NRI Schools
McGraw-Hill Continuing
Education Center
3939 Wisconsin Ave.
Washington, D.C. 20016



Color TV imports down in first half of 1979

A drop of more than a third in the imports of color television sets—from 1,212,522 in the first half of 1978 to 754,717 in the same period this year—has taken place, reports the Electronic Industries Association. The drop in the second quarter of 1979—almost exactly 50 percent—was much sharper than in the first quarter.

United States imports of monochrome TV increased in the first half of this year, from 2,610,738 in the 1978 period to 2,666,849 in the first half of 1979. Home radio imports declined 31.1 percent in the second quarter of 1979 to 6,654,064 units from the same period last year.

Customs value of color TV, home radio, phonographs, record players, changers and turntables and home audio tape players declined in the first half of 1979 and increased for black-and-white TV, auto radio, audio and video tape recorder/players, auto audio and video tape players, compared to the first half of last year.

The EIA reports that imports of radios, record changers and turntables also declined in the same periods, while imports of phonographs and tape recorders and players increased.

Weather forecasts available for 90 percent of United States

The National Oceanic and Atmospheric Administration (NOAA) is now expanding its Weather Radio program to make it possible for 90 percent of the United States population to receive reliable local weather reports. A network of weather stations (345 when completed) now reaches into practi-

cally all parts of the country, with the exception of a few "shaded" spots—like deep valleys behind high mountains—and some sparsely populated areas.

Each of the stations has a reliable service range of about 40 miles. Broadcasts run from four to six minutes, and include a general forecast, temperature and precipitation summaries, and other useful warnings and information (such as marine conditions, if the station is in a coastal area). To avoid interference, adjacent stations are on slightly different frequencies. Three are used: 162.40, 162.475 and 162.55 MHz. Transmission is FM.

Receivers (ranging in price from less than \$20) are obtainable at most electronics supply stores. An important feature of the better ones is an automatic Weather Alarm, or Weather Alert. The weather station sends out a tone before all urgent broadcasts. This tone activates the Weather Alarm type of receivers, which then turn on automatically. Thus a tornado warning, for example, can be heard by a set-owner who would not have received it on a receiver not Weather-Alarm equipped.

Education and play combine in new "Sesame" project

A series of small-scale educational play parks, each to be called "Sesame Place," is planned by the Children's Television Workshop, creator of "Sesame Street," and Busch Gardens, operator of theme parks. Work on the first has already been started. Located near the Oxford Valley Mall in lower Bucks County, PA, it is about a 30-minute drive from Philadelphia and 20 minutes from Trenton, NJ.

Sesame Place play parks will have more than 60 outdoor play activities aimed at children 3 to 11 years old, and a balancing 60 computer-type games and science exhibits in an indoor Science and Game Pavilion. Play elements throughout the parks will be themed with such familiar Sesame Street characters as Big Bird, Oscar and the Cookie Monster.

The games—tailored to children's different skills and ages—range from talking typewriters featuring Sesame Street characters to remote mechanical hands like those used in some industrial plants. Games and other features are selected not only to arouse the immediate interest of the players, but to stimulate their intellectual curiosity as they explore through play, states the director of research and planning for the parks, environmental psychologist Dr. Marilyn Rothenberg.

Work on the first park has been going on since June, and it is expected to open in early summer 1980. Admission price has not yet been set, but it is expected to be such as to encourage frequent visits, and "will be substantially less than a typical theme park."

CB'ers: Don't ask the FCC for a license refund now!

Please do *not* apply at this time, says the FCC for refund of a CB license fee. Any applications received for the refund of fees that were \$20 or less will not be considered under Phase I of the FCC's Fee Refund Program.

CB license fees and other fees that were \$20 or less will be included in Phase II, which is expected to begin early in 1980.


600 enthusiasts gather for seminar that nearly wasn't

Despite opposition from satellite broadcasters, who sued to prevent it from being held, more than 600 persons attended the first "Satellite Seminar," held at South Oklahoma City Junior College last August.

The seminar was organized by Bob Cooper, old-time electronics technician and writer, who was a columnist in this magazine in the early days of television. Calling himself the first builder of a home-style satellite receiver, and author of a handbook on building satellite television terminals, he promised to show attendees how to build a receiver that can pick up satellite broadcasts direct.

The association of carriers who have contracted to relay Home Box Office (HBO) satellite broadcasts filed suit to enjoin the seminar, alleging that it would give the par-

continued on page 14

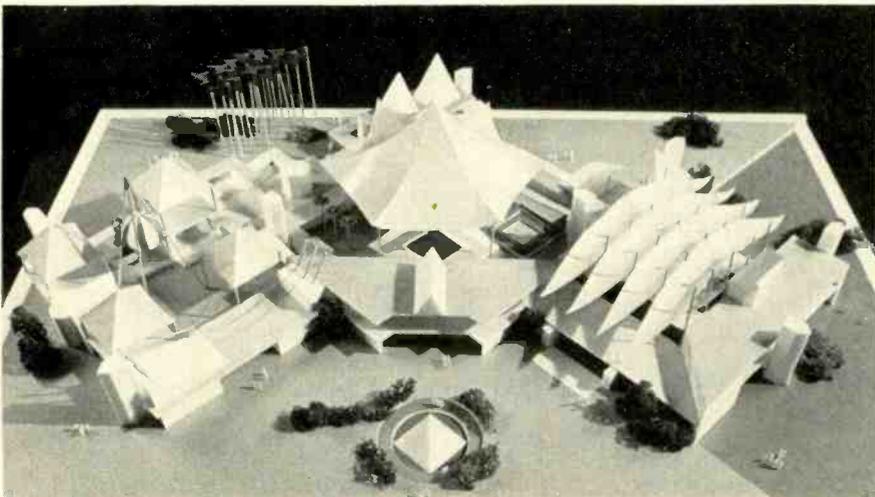

DESIGNER'S MODEL of the first Sesame Place play park. Occupying only 2.5 acres, it will contain about 60 outdoor play elements under canvas canopies, and—in the buildings—60 electronic games and science demonstrations, plus a restaurant and retail store.

continued from page 12

ticipants the information necessary to receive the HBO transmissions illegally, without paying for them. A federal judge threw out the suit, pointing out that such dissemination of knowledge is not illegal.

NESDA and ISCET relocate in Fort Worth, Texas

Headquarters of the National Electronics Service Dealers Association and the International Society of Certified Electronics Technicians is now 2708 West Berry St., Fort Worth, TX 76109. The NESDA phone is 817-921-9061 and ISCET's is 817-921-9101.

The two organizations' work was being taken care of on a temporary basis by Miss Marti McPherson, as interim administrator, since the resignation of Charles L. Porter, CET, as NESDA Executive Vice President last February. In June, the Executive Council received and approved an offer from J.W. Williams, CET, of Fort Worth, to serve as agent to manage and administer the affairs of the Association, its divisions and subsidiaries. NESDA President Bob Villont, CES/CET, and ISCET's acting chairman, Forest Belt, CET, concurred in the agreement. Mr. Williams has been Executive Director of the Texas state association since 1964.

Also at their June meeting, the Executive Council voted to change the official publication, *ServiceShop*, from a monthly to a bimonthly magazine, beginning with the July-August issue, which was also the official edition for the 1979 National Electronics Service Convention. Bob Harrison, former Publications Editor for NESDA and Editor/Publisher of *ServiceShop*, has been retained by the Williams Agency as Publications Editor and Editor-in-Chief of the magazine. Marti McPherson will continue as Editor-in-Chief of *Genesis II*, the 1980 edition of the annual NESDA/ISCET yearbook. Miss McPherson may be contacted at 8437 H Devonshire Court, Indianapolis, IN 46260, phone 317-253-7822.

Mr. Williams will assume most of the duties of the associations' Chief Executive Officer. He stresses that he hopes to improve NESDA's ability to communicate and respond to the membership, and solicits candid comments about any subject of concern, as well as suggestions for association improvement.

Record sales falling off after 25 years of increases

The record business, which has grown steadily for 25 years to its present \$4 billion a year standing, is declining at what some consider an alarming rate. CBS showed a drop in net income of 28 percent in the first quarter of 1979, and blamed its record department for most of the decrease. Warner Communications showed a drop in

operating income of 6 percent in the first quarter of the year, and 18 percent in the second quarter. Practically all the other companies show profit reductions.

Not only are sales of new records slumping, but dealers are returning unsold records in loads, straining the financial resources of smaller companies. Probably not coincidentally, there have been larger numbers of mergers and company purchases than normal.

Inflation and recession are the prime suspects: "Five dollars more for a tank of gas is one record less," says Joe Smith, president of Elektra/Asylum Records.

A second suspected cause is that there is an increased tendency to tape programs from radio or records. Sales of blank recording tapes is up, giving support to that theory.

Another suggestion, which executives tend to dismiss as unimportant, is that higher prices may be one cause of the decline. Stan Cornyn of Warner Bros. Records feels however that diversion of expenditures to "unnecessary market and merchandising gimmicks," is an important factor in profit drops.

The situation has reached a serious point with some companies. CBS Records has reduced its staff by 52, and 80 employees were let go by the RCA, Casablanca and MCA labels, while 20 were laid off by Elektra/Asylum.

Black market videocassettes eat into legitimate earnings

Video piracy is becoming a threat to the movie and TV industry. "Without question," says Ted L. Gunderson, a West Coast authority on the subject, "it's one of the fastest-growing white-collar crimes in the world." He estimates that video piracy costs the industry at least \$100 million a year in lost sales and revenue from secondary markets. (Other industry estimates are higher—up to \$700 million.)

Strangely enough, some of the bigger alleged purchasers of pirate records are large and outwardly respectable firms. "American mutinational companies are the worst transgressors," reports Richard Bloeser, film security chief for the Motion Picture Association of America. "Instead of going through legitimate channels, they are buying videocassettes of movie and television shows and shipping them to movie-starved employees overseas." Other companies illegally tape movies off cable and pay television and ship them to their employees, Mr. Bloeser says.

Other large markets are Middle Eastern countries where there are few movie theaters, and confused copyright laws make prosecution impossible. Substantial quantities of pirated videocassettes are shipped into South Africa, where strict censorship

prohibits most American movies or cuts them ruinously. In the United States, a number of the larger pirates have been apprehended and convicted.

Hospital admissions tied to geomagnetic activity?

Two physicians writing in the British magazine *Nature*—Dr. R. C. Malin and B.J. Srivastava—report an apparent link between the daily number of admissions to the cardiac-thoracic wards of two hospitals in India and the daily planetary index of geomagnetic activity, normally used as a measure of the effect of solar particle flux. The data suggests that admissions increase with magnetic activity to a much greater extent than could be explained by chance.

Another English publication, *Radio Communication*, refers to a "strange but strong correlation that has been found between sunspot maxima and virulent flu epidemics." It might be well for persons subject to heart problems and those susceptible to thoracic difficulties to take extra precautions during the present rise in sunspot activity!

FCC asks for discussion on AM channel spacing

The FCC is considering a proposal to reduce AM broadcast channel spacing from the present 10 kHz to 9 kHz, to make room for additional AM stations in the band. The Commission has put out a call for comments, asking if there is a need to increase the number of radio channels, and if so, should the FCC reserve new channels for special groups (minorities, educators, daytime-only stations, others). Other questions are: "Do you believe there is enough night-time service? Should daytime broadcasters be permitted to continue operating at night?" If your existing AM radio would pick up the new 9-kHz channels but with increased interference, would you buy a new radio?"

Opponents of the idea fear diminished reception quality if channel widths are reduced, and point out that present electronically tuned receivers, constructed for 10-kHz spacing, would become obsolete. Proponents stress the opportunity for increased minority station ownership and more night-time broadcasting as among the advantages of the proposed change.

The matter is not one that can be decided by the United States alone, but must be considered by Region 2 of the Telecommunications Union, which takes in both North and South America. There will be a Region 2 Broadcast Conference in March 1980. Participants in the Conference will probably be influenced to some extent by the fact that the rest of the world already uses 9-kHz spacing for AM broadcasting.

How much organ can you expect for \$650?

Eight rhythm patterns with five realistic rhythm instrument sounds—create your own combinations, play them separately or in combination.

Adjustable tempo control. Speed up or slow down the rhythm, plus a Special Extra Slow tempo for practice.

Steady or rhythmic chords—or combined at the touch of a key. Alternating and walking bass. Great for jazz, ballads, pops.

Add three arpeggio patterns and one finger creates more music than two people combined.

Automatic and manual harmonies with memory. Greater musical depth for either beginner or expert.

Plexiglas music stand.

Latest state-of-the-art circuitry and gadgetry.

Five melody voices and three kinds of vibrato (one wah wah). For varied melodic effects.

Separate volume controls for rhythm instruments, bass, harmony and melody sounds.

Genuine high-quality walnut veneer and solids. Not cheaper imitations.

Two keyboards—discover endless musical combinations, with or without use of 'automatics.'

Headphone jack for silent practice.

Three chord pedals. (Creates an incredible 60 different automatic chords.)

Bench included.

This much.

Give some people a box. Add some lights. A keyboard. Some funky sound. Call it an organ and you've made them happy. At least for a while.

We don't hold with that philosophy. We're unabashed music lovers who for over 24 years have taken great pride in designing some of the world's finest electronic organs. Organs you build yourself at savings of 50% and more over comparable assembled models. Our reputation? The best for less.

So you can imagine how we felt about the recent success of the popular fun organs which permit a novice to sit at the keyboard and get instant results.

The music lovers in us rebelled at even the thought of designing such a toy.

But what if we could design one that was a quality musical instrument? A true Schober organ filled with automatic electronics. It would have to be superbly engineered, utilizing the most up-to-the-minute integrated-circuit technology. Be constructed of superior quality wood, not simple construction wood of questionable origin or cheap plastics.

But most important its sound would have to be Schober. Combining all the latest, most desired features in automatic playing with the most desirable features of our more advanced organs. And true to our tradition, it would sell for less than the lowest-priced competition (an organ with far

less quality, features and sound.)

A staggering undertaking, considering the spiralling costs of quality materials. But now—thanks to some major electronic breakthroughs (and a lot of hard work by our designers and engineers) . . . the unbelievable!

The Schober Showman™ Automatic Electronic Organ kit.

Real, ready . . . and only \$650!

It's hard to explain how superb an instrument it is without your sitting before its well-appointed keyboard. Thrilling to its sound and quality. Instantly, at the touch of a key, playing latin, disco, soul, jazz, waltz, country, pop or standards. Even if you've never played before. (Our unique instruction book will make you a

total believer in minutes.) And even if you've never joined anything more than two pieces of paper, nothing could be simpler than assembling it yourself. All the parts are pre-cut, drilled and numbered. Complete, easy to understand instructions make this the do-it-yourself project of a lifetime.

Whether you're a complete beginner, hobbyist, professional or just a music lover, you will absolutely love all this organ can do. Order yours today. Only \$650 (you pay shipping charges or delivery). VISA, or MASTER CHARGE. N.Y.S. residents please add tax. Or call 212-586-7552 to order. It's by far the greatest bargain in America today.

Schober

The Schober Organ Corp. Dept. RE88
43 West 61st Street, New York, N.Y. 10023
To order enclose Check Money Order
for \$650 (N.Y. Residents please add tax. Shipping
charges C.O.D.) or charge to: M/C Visa
Account # _____ Interbank # _____
Expiration Date _____
Or call (212) 586-7552 to order.

Name _____

Address _____

City _____ State _____ Zip _____

For additional free information

CIRCLE 32 ON FREE INFORMATION CARD

www.americanradiohistory.com

Where Do The Articles Come From?


From our readers, of course! Take a quick look at this month's cover. Notice that line under Radio-Electronics? It has been there for quite some time. It says "The Magazine For New Ideas In Electronics." It's a true statement because they are your ideas.

We package those ideas; we help turn them into articles. But none of it would be possible without your feedback. Each month we receive hundreds of letters from readers. Those letters fall into four major categories—compliments, criticisms, complaints and suggestions (*IDEAS!*). We answer all of them and all are important to us, because they tell us what kind of magazine you want to read.

However, the "idea" letters are the most important of all, because that's where the really great articles start. That's where our first computer story came from; that's where our first videodisc story came from; that's where our satellite TV story came from and that's where next year's great articles will come from—ideas.

Some ideas are impossible—the technology just isn't here yet. Others are impossible because they are too basic or even old. But some are right on target and those are the ones we will turn into articles that keep you reading and looking for each issue of Radio-Electronics.

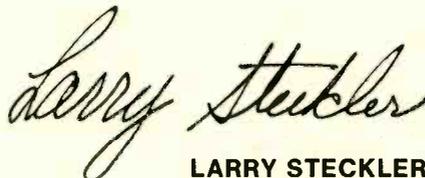So keep writing Tell us when we're wrong Pat us on the back when we're right Complain when we do something silly And keep those wonderful ideas coming They help keep us going.



LARRY STECKLER
Editor

Radio-Electronics®

Hugo Gernsback (1884-1967) founder
M. Harvey Gernsback, editor-in-chief and publisher
Larry Steckler, KTX-3644, CET, editor
Arthur Kleiman, KTZ-3288, managing editor
Robert F. Scott, CET, W2PWG, KXX-8533, technical editor
Jack Darr, CET service editor
Leonard Feldman, contributing high-fidelity editor
Karl Savon, semiconductor editor
Herb Freidman, communications editor
David Lachenbruch, contributing editor
Earl "Doc" Savage, K4SDS, hobby editor
Ruby Yee, production manager
Robert A. W. Lowndes, production associate
Marie J. Stolfi, production assistant
Gabriele Margules, circulation director
Arline R. Fishman, advertising coordinator

Cover design by Louis G. Rubsamen
Cover photo by James R. Lersch

Radio Electronics is a member of the *Institute of High Fidelity* and is indexed in *Applied Science & Technology Index* and *Readers Guide to Periodical Literature*.

Gernsback Publications, Inc.
200 Park Ave. S., New York, NY 10003
(212) 777-6400
President: M. Harvey Gernsback
Vice President: Larry Steckler
Secretary/Treasurer: Carol A. Gernsback

ADVERTISING SALES

Paul McGinnis
Director of Marketing

EAST

Stanley Levitan
Radio-Electronics
200 Park Ave. South
New York, NY 10003
(212) 777-6400

MIDWEST/Texas/Arkansas/Okla.

Ralph Bergen
The Ralph Bergen Co.
540 Frontage Road—Suite 361-A
Northfield, Illinois 60093
(312) 446-1444

PACIFIC COAST Mountain States

Jay Eisenberg
J.E. Publishers Representative Co.,
8732 Sunset Blvd.,
4th Floor,
Los Angeles, CA 90069
(213) 659-3810
Sales Mart Building
1485 Bayshore Blvd., Box 140
San Francisco, CA 94124
(415) 467-0125

NMPA



When quality counts

Do not be fooled by the low prices, these brand new lab quality frequency counters have important advantages over instruments costing much more. The models 7010 and 8010 are not old counters repackaged but 100% new designs using the latest LSI state-of-the-art circuitry. With only 4 IC's, our new 7010 offers a host of features including 10 Hz to 600 MHz operation, 9 digit display, 3 gate times and more. This outperforms units using 10-15 IC's at several times the size and power consumption. The older designs using many more parts increase the possibility of failure and complexity of troubleshooting. Look closely at our impressive specifications and note you can buy these lab quality counters for similar or less money than hobby quality units with TV xtal time bases and plastic cases!

Both the new 7010 and 8010 have new amplifier circuits with amazingly flat frequency response and improved dynamic range. Sensitivity is excellent and charted below for all frequencies covered by the instruments.

Both counters use a modern, no warm up, 10 MHz TCXO (temperature compensated xtal oscillator) time base with external clock capability - no economical 3.575545 MHz TV xtal.

Quality metal cases with machine screws and heavy gauge black anodized aluminum provide RF shielding, light weight and are rugged and attractive - not economical plastic.

For improved resolution there are 3 gate times on the 7010 and 8 gate times on the 8010 with rapid display update. For example, the 10 second gate time on either model will update the continuous display every 10.2 seconds. Some competitive counters offering a 10 second gate time may require 20 seconds between display updates.

The 7010 and 8010 carry a 100% parts and labor guarantee for a full year. No "limited" guarantee here! Fast service when you need it too, 90% of all serviced instruments are on the way back to the user within two business days.

We have earned a reputation for state-of-the-art designs, quality products, fast service and honest advertising. All of our products are manufactured and shipped from our modern 13,000 square foot facility in Ft. Lauderdale, Florida.

When quality counts...count on Optoelectronics.

CIRCLE 27 ON FREE INFORMATION CARD

MODEL 8010 1 GHz



MODEL 7010 630 MHz

- 100% U.S.A. FACTORY ASSEMBLED
- 100% PARTS & LABOR YEAR GUARANTEE
- CERTIFIED NBS TRACEABLE CALIBRATION
- EXTERNAL CLOCK INPUT

- DISPLAY HOLD FUNCTION
- 9 RED LED DIGITS 4" HIGH
- 1 Hz RESOLUTION
- 0.1 PPM 10 MHz TCXO TIME BASE

- LAB/PORTABLE-AC ADAPTER INCLUDED
- 1 MEGOHM & 50 OHM INPUTS
- STATE-OF-THE-ART LSI DESIGNS
- COMPREHENSIVE USER MANUAL PROVIDED

COMPACT SIZES—7010- 1-3/4" Hx4-1/4" Wx5-1/4" D 8010- 3" Hx7-1/2" Wx6-1/2" D

MODEL	\$ PRICE	RANGE MHz to	LED DIGITS	SENSITIVITY			HI-Z INPUT 10Hz - 60 MHz	GATE TIMES	RESOLUTION			TCXO TIME BASE		EXT CLOCK INPUT	NI-CAD BATT PACK
				25-250 MHz	250-450 MHz	450 MHz- 1 GHz			12 MHz	60 MHz	MAX. FREQ.	20 - 40 °C	FREQ.		
7010 *7C10.1	145.00 225.00	600 MHz	9	5-20 mV	10-30 mV	20-40 mV to 600 MHz	1-10 mV	[3], .1, 1, 10 SEC	.1 Hz	1 Hz	10 Hz 600 MHz	1 PPM 0.1 PPM	10 MHz	YES OPTION \$25	YES OPTION \$15.
8010 *8C10.1	325.00 405.00	1 GHz	9	1-10 mV	5-20 mV	10-25 mV	1-10 mV	[8], .01-20 SEC	.1 Hz	1 Hz	10 Hz 1 GHz	1 PPM 0.1 PPM	10 MHz	YES STD	YES OPTION \$39.

* Has precision 0.1 PPM TCXO time base.

MODEL 7010

- #7010 600 MHz Counter - 1 PPM TCXO \$145.00
- #7010.1 600 MHz Counter - 0.1 PPM TCXO \$225.00

OPTIONS

- #NI-Cad-7C1 Ni-Cad Battery Pack & charging circuitry
installs inside unit \$ 15.00
- #EC-70 External Clock Input, 10 MHz \$ 25.00
- #CC-70 Carry Case, Padded Black Vinyl \$ 8.95

MODEL 8010

- #8010 1 GHz Counter - 1 PPM TCXO \$325.00
- #8010.1 1 GHz Counter - 0.1 PPM TCXO \$405.00
- #8010.1-13 1.3 GHz Counter - 0.1 PPM TCXO \$495.00

OPTIONS

- #NI-Cad-801 Ni-Cad Battery Pack & charging circuitry
Installs inside unit \$ 39.00
- #CC-80 Carry Case, Padded Black Vinyl \$ 9.95

ACCESSORIES

- #TA-100 Telescope Ant with Right Angle BNC \$ 9.95
- #P-100 Probe, 50 ohm, 1k \$13.95
- #P-101 Probe, Lo-Pass, Audio Usage \$16.95
- #P-102 Probe, Hi-Z, General Purpose \$16.95



ORDER FACTORY DIRECT • CALL TOLL FREE



Optoelectronics inc

1-800-327-5912

5821 N.E. 14th Avenue, Fort Lauderdale, Florida 33334

FROM FLORIDA (305) 771-2051/2


TERMS: Orders to U.S. and Canada, add 5% for shipping, handling and insurance to a maximum of \$10.00. All other orders add 10%. C.O.D. collection fee \$1.00. Orders under \$15.00 add extra \$1.00 handling. Regular checks must clear before order is shipped. Florida residents add 4% sales tax.

At CIE, you get electronics career training from specialists.

If you're interested in learning how to fix air conditioners, service cars or install heating systems – talk to some other school. But if you're serious about electronics, come to CIE – The Electronics Specialists.

John E. Cunningham

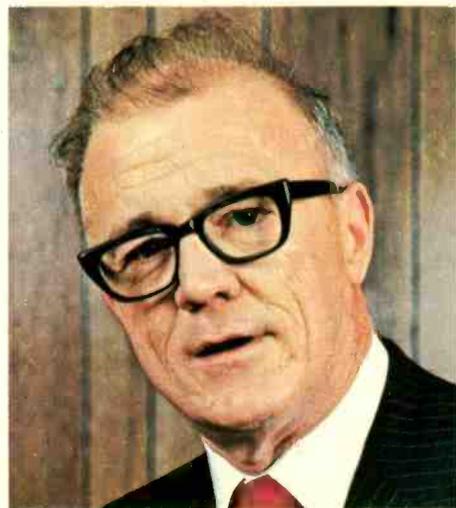**Special Projects Director
Cleveland Institute of Electronics**



My father always told me that there were certain advantages to putting all your eggs in one basket. "John," he said, "learn to do one important thing better than anyone else, and you'll always be in demand."

I believe he was right. Today is the age of specialization. And I think that's a very good thing.

Consider doctors. You wouldn't expect your family doctor to perform open heart surgery or your dentist to set a broken bone, either. Would you?

For these things, you'd want a specialist. And you'd trust him. Because you'd know if he weren't any good, he'd be out of business.

Why trust your education and career future to anything less than a specialist?

You shouldn't. And you certainly don't have to.

FACT: CIE is the largest independent home study school in the world that specializes exclusively in electronics.

We have to be good at it because we put all our eggs in one basket: electronics. If we hadn't done a good job, we'd have closed our doors long ago.

Specialists aren't for everyone.

I'll tell it to you straight. If you think electronics would make a nice hobby, check with other schools.

But if you think you have the cool — and want the training it takes — to make sure that a sound blackout during a prime time TV show will be corrected in seconds — then answer this ad. You'll probably find CIE has a course that's just right for you!

At CIE, we combine theory and practice. You learn the best of both.

Learning electronics is a lot more than memorizing a laundry list of facts about circuits and transistors. Electronics is interesting because it's based on some fairly recent scientific discoveries. It's built on ideas. So, look for a program that starts with ideas — and builds on them.

That's what happens with CIE's Auto-Programmed® Lessons. Each lesson uses world-famous "programmed learning" methods to teach you important principles. You explore them, master them completely . . . before you start to apply them!

But beyond theory, some of our courses come fully equipped with the electronics gear to actually let you perform hundreds of checking, testing and analyzing projects.

In fact, depending on the course you take, you'll do most of the basic things professionals do every day — things like servicing a beauty of a Zenith color TV set . . . or studying a variety of screen display patterns with the help of a color bar generator.

Plus there's a professional quality oscilloscope you build and use to "see" and "read" the characteristic waveform patterns of electronic equipment.

You work with experienced specialists.

When you send us a completed lesson, you can be sure it will be reviewed and graded by a trained electronics instructor, backed by a team of technical specialists. If you need specialized help, you get it fast . . . in writing from the faculty specialists best qualified to handle your question.

People who have known us a long time, think of us as the "FCC License School."

We don't mind. We have a fine record of preparing people to take . . . and pass . . . the government-administered FCC License exams. In fact, in continuing surveys nearly 4 out of 5 of our graduates who take

the exams get their Licenses. You may already know that an FCC License is needed for some careers in electronics — and it can be a valuable credential anytime.

Find out more! Mail this card for your FREE CATALOG today!

If the card is gone, cut out and mail the coupon.

I'll send you a copy of CIE's FREE school catalog, along with a complete package of independent home study information.

For your convenience, I'll try to arrange for a CIE representative to contact you to answer any questions you may have.

Remember, if you are serious about learning electronics . . . or building upon your present skills, your best bet is to go with the electronics specialists — CIE. Mail the card or coupon today or write CIE (and mention the name and date of this magazine), 1776 East 17th Street, Cleveland, Ohio 44114.



Patterns shown on TV and oscilloscope screens are simulated.

CIE Cleveland Institute of Electronics, Inc.

1776 East 17th Street, Cleveland, Ohio 44114
Accredited Member National Home Study Council

YES . . . John, I want to learn from the specialists in electronics — CIE. Send me my FREE CIE school catalog — including details about troubleshooting courses — plus my FREE package of home study information.

RE-77

Print Name _____

Address _____ Apt. _____

City _____

State _____ Zip _____

Age _____ Phone (area code) _____

Check box for G.I. Bill information: Veteran Active Duty

Mail today!

letters

SATELLITE TV

I would like to draw your readers' attention to the fact that it is now quite possible to receive high quality TV signals on backyard earth stations. All across the country thousands of dish antenna are capturing up to 48 channels direct from our orbiting communications satellites. Public ignorance of this new phenomenon will soon be replaced by "satellite awareness."

Perhaps some readers would be interested in submitting contributions to our new publication *Earth Station Magazine*. Response to our *Earth Station Information Manual* demonstrates that many rural Americans are desperate for what the rest of us take for granted. The selection and quality of the programming is literally out of this world.

Regarding deregulation, the FCC's main concern with Earth Station licensing is to protect the operator from future interference caused by terrestrial microwave communications on the same 3.7 to 4.2 GHz band. NASA is also very interested in promoting direct TV reception from satellites. It seems to me that the major resistance is

coming from the broadcast networks and it is easy to see why. The long established network-affiliate monopolization of American TV is approaching a shakeup.

Please continue to feature articles on TV Earth Stations.

STEPHEN REED
Spacecoast Research
Box 442
Altamonte Springs, FL 32701

I read the articles by Bob Cooper on the subject of Satellite TV Reception and would like to point out some additional information about equipment availability.

There are perhaps 10 suppliers of Satellite TV Earth Stations for the CATV market and there are perhaps four to six distributors of that equipment who will serve the private individual as well as the CATV system. However, I believe that Channel One, Inc. and Homesat, Inc., the subsidiary of Scientific-Atlanta, are serving the private owner exclusively.

Channel One, Inc., offers turnkey home systems. Our 3 meter *Earth-Link* costs \$15,500, plus site preparation (a clearing

and a concrete pad.) In some areas, a 5-meter antenna is required. Here the cost is \$18,500, plus site preparation. The prices include installation, a one year limited warranty and nationwide after-sales service.

Some sites are not suitable for an Earth Station. Channel One does a computerized survey of terrestrial microwave transmissions to ascertain if a proposed site is suitable. The cost is \$125, which is refunded if the proposed site proves unsuitable. If the results are positive, the \$125 becomes a credit towards the 25% down payment required when placing an order. Financing is available.

FRED HOPENGARTEN
Channel One, Inc.
68 Avalon Rd.
Newton MA 02168
617-527-1025

INTELLIGENT THERMOSTAT


I was very interested in the article in the June issue describing the Intelligent Thermostat. Since I am considering a project similar to this for my senior project at Purdue University I went through the article

BATTERY-WRAP

WIRE WRAPPING TOOL

MODEL BW-2630

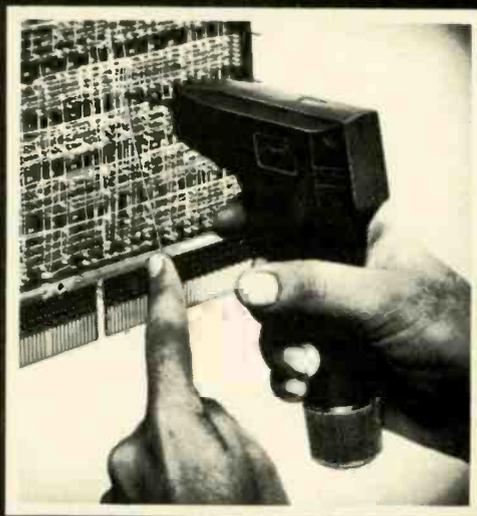- POSITIVE INDEXING
- ANTI-OVERWRAPPING
- BITS AVAILABLE FOR AWG 26, 28 & 30
- BATTERY OPERATED
- LIGHT WEIGHT



\$19⁸⁵*

BATTERIES AND BIT NOT INCLUDED

U.S.A.
FOREIGN
PATENTS
PENDING



OK MACHINE & TOOL CORPORATION

3455 CONNER STREET, BRONX, N.Y. 10475, U.S.A.

PHONE (212) 994-6600 • TELEX: 125091


BW-2630	BATTERY-WRAP TOOL	\$19.85
BT-30	BIT FOR AWG 30	\$ 3.95
BT-2628	BIT FOR AWG 26 & 28	\$ 7.95
RB-20	TWO NI-CAD BATTERIES	\$10.75

*MINIMUM BILLING \$25.00 / ADD SHIPPING CHARGE \$2.00 / NEW YORK CITY / STATE RESIDENTS ADD APPLICABLE TAX.

CIRCLE 40 ON FREE INFORMATION CARD

www.americanradiohistory.com

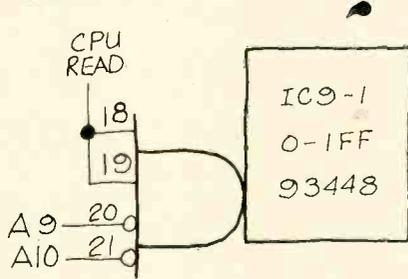rather intently. While studying the schematic I noticed that IC9-1 and IC9-2 had the same address. The schematic for the enable should rather be as shown in the diagram.



All other connections are as shown in the article and the PC layout for this IC appear to be right. Thank you very much for the fine article. The only thing I would like to have seen was a better description of the software.

MICHAEL KOST
Croydon, IN

ENERGY CRISIS

In the July 1979 "Letters" column, I read of an interesting proposal to solve the energy crisis that involved using a linear accelerator to smash particles together. This theoretically would produce large amounts of power. I point out that to accelerate a mere particle is insufficient, and in fact has been going on for several years at the Stanford Linear Accelerator.

However, it would become efficient if something were to smash into something

else at greater than 50% of the speed of light. The piece of matter must weigh about 100 grams (50 grams for each chunk).

The technology to produce this kind of power does, however, exist. A device consisting of a series of super-conducting magnets, spaced about one meter apart, and totalling many kilometers on a side, could produce the required power by accelerating a ferromagnetic "car" at several hundred gravities. Such a device could be placed in space, where the matter could be held in a magnetic field so that any material warpage would not affect it, as it would on earth. Also, in space, you could get rid of heat better and reduce energy demand.

However, in Mr. Rimmer's letter, he stated that you would need a superfast computer to control the accelerating magnets. This is about the biggest understatement of the century! When an object is moving at half the speed of light, it crosses a space of one meter in 1.67×10^{-3} microseconds. The problem comes in when you find that the fastest computer in the world could only process the data for *one* accelerator magnet in 0.25 microseconds. It becomes obvious that no *conventional* computer could handle that kind of data requirement. Besides that, the response time of a data sensor is limited by the speed of light and quantum theory.

Here I come to the real point of this letter. There is a family of subatomic particles that move faster than the speed of light. These particles are called tychons. They supposedly exist in some other dimension, but have some effect on ours.

Studies are going on that indicate that

tychons could interact with materials in our own dimension, and vice-versa. It soon becomes obvious that an ultra-fast computer could be constructed using tychons instead of electrons.

A material could be synthesized that could function as tychon adder. Tychons could be fed down tubes about 100 angstroms wide (1 angstrom = 10^{-10} meters), and when two words are mixed, there would be a material that would eliminate one and pass one onto the next (carry) column. The number of these interactions that could take place, (the number of chunks of adding material) would be the word length plus one, the carry bit.

Sensory input data could be transmitted by passing a beam along the edge of the mass driver and then having it interact with material that would cut off one frequency of the tychon beam, except that the beam was being attenuated.

Such a computer could solve many problems that have before been impossible because of the complexity of the problem. (See "Intrinsically Difficult Problems," *Scientific American*, May 1979).

The problem is that this kind of computer *could not communicate with any other machine without a buffer* that could sink the inputs of several large system memory-oriented mainframe operators.

The advent of such a computer system would mean a great advance in all fields of science. I think that a project should be started to determine the feasibility of such a system. The sooner the better.

BRAD BROWN

Toronto, Ontario, Canada

R-E

INTRODUCING...

THE ROAD RUNNER ADMM™

FROM WESTON



AUDIO RESPONSE™ PLUS DIGITAL DISPLAY

- 5 RANGE AUDIBLE SIGNALING FUNCTION
- RUGGED FIELD SERVICE DESIGN
- 0.5" LCD DISPLAY
- 6 FUNCTIONS
- 29 RANGES

WESTON INSTRUMENTS
THE MEASUREMENT PEOPLE®
614 Frellinghuysen Ave.,
Newark, NJ 07114


SANGAMO WESTON
Schlumberger

CIRCLE 38 ON FREE INFORMATION CARD

www.americanradiohistory.com

equipment reports

Leader LCR-740 Transistorized LCR Bridge

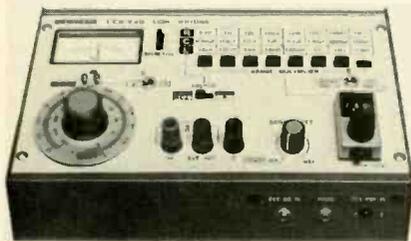

CIRCLE 101 ON FREE INFORMATION CARD

ONE OF THE HANDIEST PIECES OF TEST EQUIPMENT we've seen in a long time is the LCR bridge from Leader Instruments Corporation. It is a portable unit measuring $3\frac{1}{2} \times 9\frac{1}{2} \times 6\frac{3}{4}$ inches and weighing 2 pounds. A convenient carrying strap is attached for safe transport.

Functionally, the LCR-740 is a portable component testing laboratory. It measures capacitance from 1 pF to 11,000 μ F, resistance from .001 ohm to 11 megohms, and inductance

from .1 μ H to 1100 henries. Accuracy is $\pm .5\%$. Readout on all scales is to three digits, provided by a turns-counting potentiometer.

Ten percent overrange is provided on all scales for convenience at end-of-scale measurements. Loss factor on the inductance scale is measurable from .01-31.

All functions are powered by a standard 9-volt battery. An optional AC adaptor is available for continuous use.

Both DC resistance measurements and impedance measurements are provided. An internal 1 kHz generator is used for reactance (impedance) tests on all three functions. Optionally, an external frequency source of from 50 Hz to 40 kHz may be injected into the 740 for additional capacitance and inductance measurements. Inserting a plug into the external signal input jack automatically disconnects the internal 1 kHz oscillator.

An earphone is included for audio null measurements in conjunction with the meter readings. Connection to an oscilloscope can also be made from the earphone jack. The LCR-740 is not available as a kit, and it is just as well. Final calibration of an accurate piece of test equipment like this RCL bridge is a

tricky business, requiring close-tolerance test components for alignment. The internal circuitry of the LCR-740 is carefully assembled, showing the care of hand soldering. PC board material and component selection are both high quality.

Upon prompt registration of the warranty card, the owner is entitled to a liberal two-year warranty policy. Free repair will be provided during the first six months of ownership of the instrument.

Comment

Although a period of familiarization will be required for the user to feel comfortable with the LCR-740, its actual operation is very simple. Resistance, capacitance, and inductance ranges are all pushbutton selectable. All value readings are taken from the same linear scale, a digital-dial multiturn potentiometer. While adjusting the instrument to make inductance measurements, three dials must be adjusted to find the sharpest dip in the meter reading. Although this may sound cumbersome, the procedure became routine after a few minutes, and values of unknown compo-

continued on page 32

Now, an automotive computer plus cruise control at your fingertips!

This is CompuCruise! The first true computer for your car, truck or RV. It's the most effective and functional cruise control ever designed, PLUS complete trip computing, an efficient fuel management system, and a split-second-accuracy quartz time system.

CompuCruise is a cruise control with a memory. A unique seek-and-hold capability makes highway driving easier and more enjoyable. Fully electronic, making it more accurate and reliable.

CompuCruise is a true computer, constantly reacting via automatic sensors to changing conditions, updating vital data for you every second. Just look at what CompuCruise gives you:

- Time, E. T. Lap timing, Alarm
- Time, Distance, Fuel to arrival
- Time, Distance, Fuel to empty
- Time, Distance fuel on trip
- Current or average MPH, MPG, GPH
- Fuel used, Distance since fillup
- Inside, outside or coolant temp.
- Battery voltage
- English or Metric display

CompuCruise works on foreign or American cars (except Diesel and fuel-injected vehicles). It's priced for the budget-minded, and easily installable by you or your automotive outlet.

Only \$199.95 with Cruise Control, \$159.50 without. Fully warranted for 90 days from date of purchase. Delivered

complete with easy-to-follow installation guide. And backed by a 100% satisfaction guarantee. If not fully satisfied when you receive your unit, return it before installation and your money will be fully refunded without question.

For the name of your nearest dealer, call or write us right now: ZEMCO, 12907 Alcosta Blvd., San Ramon, CA 94583. Phone (415) 838-8060.

Do it today—for a better cruise control and more automotive information than you've ever had before.


 **COMPUCRUISE**



CIRCLE 14 ON FREE INFORMATION CARD

PLUG IT IN AND TAKE COMMAND

CHRISTMAS SPECIALS!

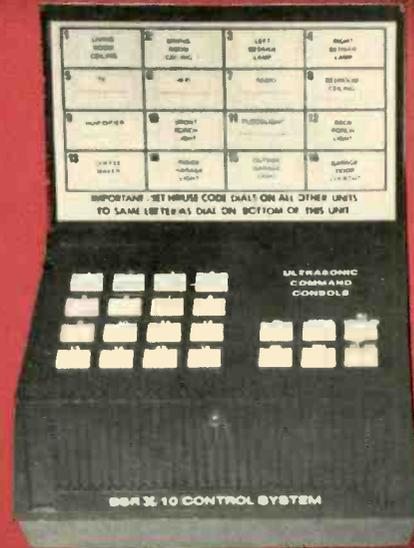

X-10 Remote Control For Lights and Appliances

NO WIRES NO HASSLES

System X-10 requires no special wiring or complicated installation. Simply plug a Command Console into your wall outlet in any desired location in your home. Plug each Lamp or appliance into the appropriate module and then plug that module into any wall outlet. Any number of Command Consoles may be used in a single system.

TOTAL CONVENIENCE

With System X-10 you can operate almost every light and electrical appliance in your home without leaving the comfort of your easy chair. Imagine turning on a TV set or stereo, even dimming a light, in the next room without moving from your chair.

Think of the money you can save on electric bills with System X-10. Turn off heaters or appliances from any location in your home without a lot of running around.

DELUXE ULTRASONIC COMMAND SYSTEM

The Console controls all modules from its built-in keyboard, plus it completely controls all modules from its wireless hand held ultrasonic control unit. Simply aim the hand held unit at the Console, press any appropriate Command button to turn on and off, dim and brighten lights, or turn on and off appliances. Hand held unit operates at distances of up to thirty feet line of sight of console (does not operate through walls). A worthwhile addition to any existing X-10 system or an excellent way to begin.

STANDARD COMMAND CONSOLE

Fully controls all modules as above system, but will not respond to hand held remote unit commands - may be intermixed with the deluxe Command System or used separately, to form independent control systems.

MICROPROCESSOR BASED DESIGN

The BSR X-10 System uses the latest digital techniques for trouble-free operation. Digital pulse codes are sent through the house power lines to assure reliable control throughout the system. Amazingly compact: The Command Consoles measure only 4 3/4" X 3 1/2" X 3 1/2".

LAMP MODULE

Each module will control any incandescent lamp rated up to 300 watts from control signals received from the Command units. Functions include on and off, brighter and dim. UL listed.

APPLIANCE MODULE

Each module receives signals from the Command units to turn appliances on and off, such as TV, stereo, fan, etc. Maximum appliance ratings: Resistive load - 15 amps. Motor load - 1/4 HP. Incandescent lamp - 500 watts. UL listed.

WALL SWITCH MODULE

Receives signals from the Command units to control incandescent lamps normally operated by a wall switch up to 500 watts. Installs just like any normal wall switch. Functions include on and off by remote or local control and brighter and dim by remote control. UL listed.

GETTING STARTED

Deluxe-Ultrasonic starter kit includes: 1-Deluxe Ultrasonic Command Console, 1-Hand Held Remote Unit, 2-Lamp Modules, 1-Appliance Module. Reg. \$112.95 now **\$99.95**.

Standard starter kit includes: 1-Standard Command Console, 2-Lamp Modules, 1-Appliance Module. Reg. \$87.95 now **\$77.95**. Extra Lamp, Appliance or Wall Switch Modules only \$16.00 each.

Extra Deluxe Ultrasonic Command Console with Hand Held Remote Unit, \$64.95.

Extra Standard Command Console \$39.95.

Please include \$3.00 shipping and handling on all orders.



To order — use this coupon or call
TOLL FREE HOT LINE
800-223-0474

54 West 35 Street New York N.Y. 10036 IN NEW YORK STATE 212-687-2224

Please send me

BSF 5 piece Deluxe Ultrasonic starter kit.....	\$112.95 set.....	\$99.95 set
BSF 4 piece Standard starter kit.....	\$87.95 set.....	\$77.95 set
Lamp Mod..... Appliance Mod..... Wall Switch Mod.....		\$16.00 each
Deluxe Ultrasonic Console with Handheld Remote Unit.....		\$64.95 each
Standard Command Console.....		\$39.95 each

Payment: Enclosed Bill my MASTER CHARGE VISA RE-02

Acct. # _____ Exp. Date _____

Name _____

Address _____

City _____ State _____ Zip _____

Add \$3.00 Shipping and Handling. N.Y.S. Res. add sales tax.

SALE EFFECTIVE NOV. 12, 1979 THRU JAN. 31, 1980



HEATHKIT

Introducing the new Heathkit® Screen Star:

It's 8 times bigger than the screen you're watching now.*

Now the things that just have to be seen on the big screen can be seen on your own big screen right at home.

The new Heathkit Screen Star TV has a 6-foot diagonal screen that's eight times bigger than a 25-inch screen.

Three projection tubes give you bright, vivid color. And the finest F1.0 lenses you can buy keep your picture sharp and clear.

Your favorite movies, musicals and sports never looked so good.

**Easy adjustment.
Roll-away convenience.**

The new Heathkit Screen Star is designed to require minimal convergence adjustment. Convenient front panel controls let you adjust to a beautiful picture in seconds.



Swivel casters make it easy to roll away the cabinet when not in use, so it doesn't take up a lot of room.

Surprisingly low price.

Heath engineers have built in quality while maintaining a price you can afford. The new Heathkit Screen Star is one of the lowest-priced three-tube TV's you can buy. Your Heathkit Catalog lists all prices.

Build it yourself – service it yourself.

This is Heath's easiest-to-build solid-state TV. It's actually easier than conventional TV's. Like all Heath electronic kits, it comes with an easy-to-follow assembly manual that takes you step-by-step through every phase of assembly.

And when you build it yourself, you can service it yourself. Every set includes a detailed service manual that can save you money over the years.

Free Heathkit Catalog with complete details.



Complete details and prices on the Heathkit Screen Star are in the new Heathkit Catalog. It's free and it contains nearly 400 beautiful electronic kits for your home, work or pleasure. Send for yours today or pick one up at your nearest Heathkit Electronic Center.

*If the screen you're watching now is a 25" diagonal. If it's smaller, the Heathkit Screen-Star is proportionately larger. Simulated TV picture.

Heathkit

Heath Company, Dept. 020-600, Benton Harbor, MI 49022

Heathkit Products are also sold and serviced at Heathkit Electronic Centers (Units of Schlumberger Products Corporation) in major cities throughout the U.S. and Canada. See your white pages.

CIRCLE 100 ON FREE INFORMATION CARD


www.americanradiohistory.com

GX-364


DECEMBER 1979

27

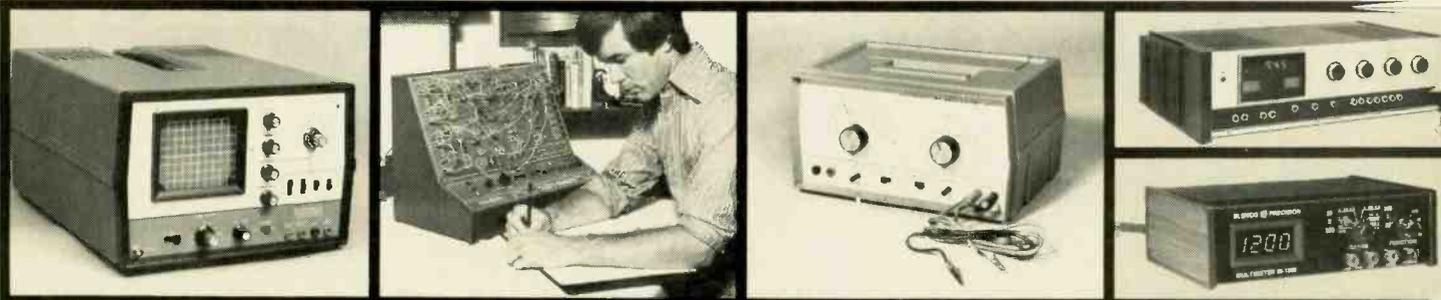Train with NTS for the MicroComputers, digital the first name



MicroComputers

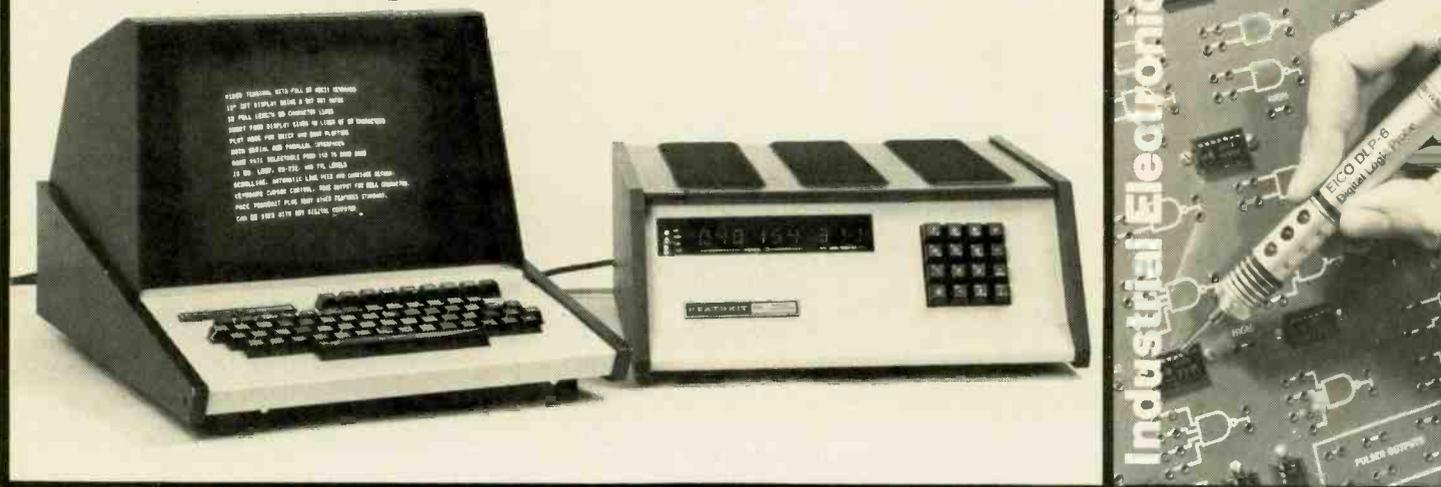

The world of electronics is daily becoming more challenging. Technology is growing more specialized, and the importance of digital systems increases every day. Test instruments, home entertainment units and industrial control systems are all going digital. And now, NTS training programs include a wider choice of solid-state and digital equipment than ever before offered in any home study course: Advanced NTS/Heath digital color TV (25" diagonal with optional programming capability), NTS/Heath microcomputer, digital test equipment, digital stereo receiver (70 watts per channel), NTS compu-trainer, plus much more state-of-the-art equipment to make your training exciting and relevant.


The equipment you receive with NTS training programs is selected to provide you with a solid

background in electronic systems. Kits and lessons are designed to work together to demonstrate electronic principles and applications. The kit-building not only shows you how electronic hardware functions, but how various circuit designs accomplish different purposes. Your lessons guide you through any number of experiments associated with many projects. This is the Project-Method, and it works. Step-by-step, you learn how and why digital electronics has become a part of our world, and the even bigger role it is sure to play in the future.


Whether you are looking for training in Consumer, Commercial, or Industrial electronics, NTS offers fourteen courses, some basic, many advanced, in several areas of electronics. An all-new full-color NTS catalog shows you what each course covers,

electronics of the future.

systems and more...from
in home study.

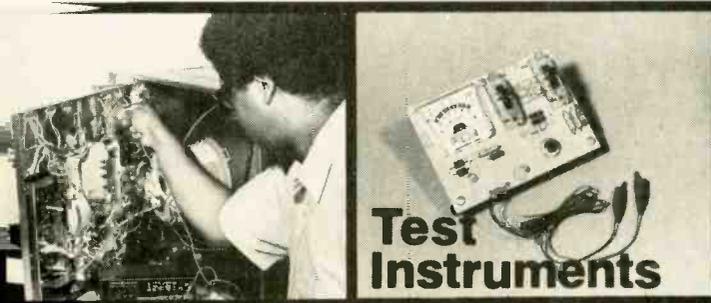

Test Instruments

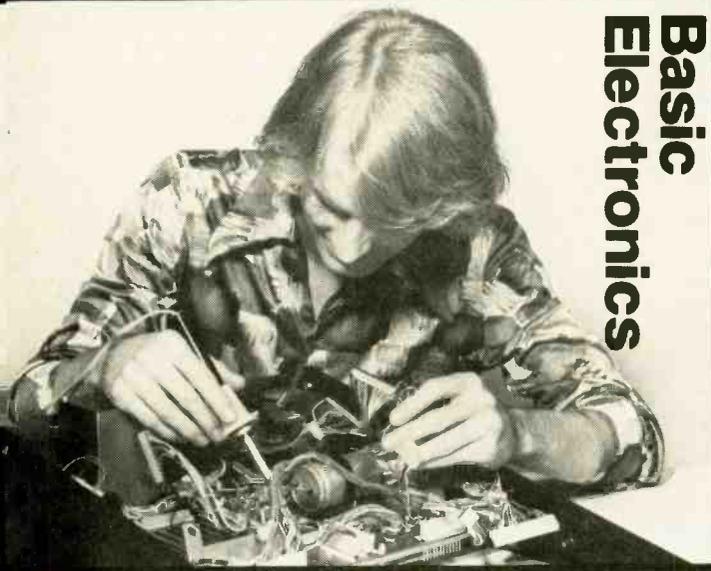


Basic Electronics



Digital Color TV

Simulated TV Reception

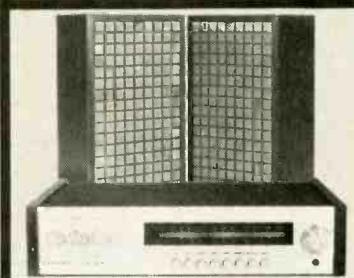

and every piece of equipment included.
Send for it today, and see for yourself what's really happening in electronics training technology at NTS. Find out how much has changed, and what new directions the field is taking. You'll probably want to be a part of it.
It's free. Just mail the card or coupon. Today.

**NO OBLIGATION. NO SALESMAN WILL CALL.
APPROVED FOR VETERAN TRAINING.**

NATIONAL TECHNICAL SCHOOLS

TECHNICAL-TRADE TRAINING SINCE 1905
Resident and Home-Study Schools
4000 South Figueroa St., Los Angeles, Calif. 90037

NATIONAL TECHNICAL SCHOOLS Dept. 206-129

4000 South Figueroa Street, Los Angeles, California 90037

Please send FREE Color Catalog and Sample Lesson.

- Color TV Servicing
- B & W TV and Radio Servicing
- FCC License Course
- Electronic Communications
- Electronics Technology
- Audio Electronics Servicing
- Digital Electronics
- MicroComputers/MicroProcessors

Name _____

Address _____

Apartment Number _____ Age _____

City _____

State _____ Zip _____

- Check if interested in G.I. Bill information.
- Check if interested ONLY in classroom training in Los Angeles.

fact:
you can cut conference clutter—and improve the sound in the bargain!



Eliminate your conference room's "electronic jungle" with the new, inconspicuous Shure Lo-Profile™ SM18 unidirectional microphones designed to lie flat on the table. Distracting (and intimidating) chrome-plated hardware give way to unobtrusive brown foam-encased units... even the brown cables blend into wood-finished table tops.

The Model SM18 is ideal for seminars, press conferences, speakers' platforms, and sales meetings.



But appearance isn't the only advantage. A special "Surface Reflection Effect" configuration eliminates the unnatural hollow sound caused by reflected sounds bouncing off table surfaces. The Model SM18 picks up sound from the front while suppressing audience noise. It is especially engineered for voice range pickup. What you say is what the audience hears... period.

For full details, check with your firm's audio visual expert, your sound installer, or send for our new brochure (AL630).

What you can't see... lets you hear better!



Also available in white.

**New SM18
 LO-PROFILE™
 microphone by**



Shure Brothers Inc., 222 Hartrey Ave., Evanston, IL 60204

In Canada: A. C. Simmonds & Sons Limited Outside the U.S. or Canada, write to Shure Brothers Inc., Attn: Dept. J6 for information on your local Shure distributor.

Manufacturers of high fidelity components, microphones, sound systems and related circuitry.

CIRCLE 61 ON FREE INFORMATION CARD

EQUIPMENT REPORTS

continued from page 24

nents could be successfully pinned down relatively quickly.

Range expanders are provided for both adjustable bridge resistances. This allows for additional resistance to be introduced to accommodate critical null balancing that is too close to the end of the normal adjustment ranges.

To avoid confusion, any component under test is attached to the same two binding posts. Nulls are sharply-defined, and readouts are easy to see. Based upon standard-value components kept for test purposes, we would judge the LCR-740 to be well within its advertised accuracy.

The manual that is included with the bridge is comprehensive, listing a wide variety of techniques and hints for effective component testing. Some typographical errors are present, and occasionally awkward translation to English is difficult to comprehend. Neither of these minor shortcomings detracts from the flexibility of the instrument or the value of the manual.

The LCR-740 is a useful addition to any engineering bench or electronic experimenter's workshop. The ranges that the instrument will test include virtually 100% of those values likely to be encountered.

With some values of inductance it is extremely difficult to find the deepest null. Adjustments are very touchy. But this must be expected when using a single instrument for such a wide range of possible component values.

After using the little LCR bridge for several hours, it was difficult to return it after evaluation. It is one of those items that you never realized how much you needed until you actually used one! The LCR-740 transistorized LCR bridge has a suggested retail price of \$320 and is available from Leader Instruments Corporation, 151 Dupont Street, Plainview, NY 11803.

R-E

**MFJ Enterprise Model
 MFJ-721 Communications
 Filter**



CIRCLE 102 ON FREE INFORMATION CARD

HAMS, CB'ERS AND SHORTWAVE LISTENERS will appreciate a handy accessory recently introduced by MFJ Enterprises. The MFJ-721 Super Selector is an active audio filter that can be used with a speaker or with headphones. The filter is designed to discriminate sharply against unwanted background noises, while permitting the desirable signal to be heard. This is accomplished by a series of IC stages. With the model MFJ-721 in the voice mode (AM or SSB), three progressively sharper passbands remove hiss, sideband splatter, heterodyne interference, hum and even static crashes. In the CW mode, four bandwidths can

be selected, one as razor-sharp as 80 Hz. Stages are cascaded and Q is kept to a minimum to reduce ringing. A built-in noise limiter reduces impulse noise that is useful both in voice and CW reception.

An internal 2-watt audio amplifier (LM380N) can be used alone. A stereo headphone jack allows CW operators to enjoy the simulated stereo comparison of input and output signals.

All functions are switch-selectable from the front panel. A switch position allows the audio signal to bypass the active filter if defeat is desirable, as during excellent signal copy.

The unit's rear apron contains a jack for the external speaker (not provided), and two phono jacks for separate audio inputs (switch-selectable from the rear panel).

The filter requires an external power supply; any 9- to 18-volt supply will do. An optional 9-volt AC adapter is available for \$7.95.

To try out our unit, we plugged it into the external speaker jack of a general-coverage communications receiver. In the high-pass position, we selected a standard amplitude-modulated voice signal with moderate background hiss and some heterodyne interference. We then began to advance the selectivity switch. Immediately, the voice began to sound clearer. The hiss virtually disappeared, as did the annoying whistle of the interfering signal.

On extremely weak SSB signals with strong interference, the most selective position had to be used. Even then, with the restricted audio passband, the voice could be copied.

On CW the unit performed admirably. Dialing through the Novice CW band, we purposefully adjusted the receiver to hear a barrage of signals of varying strength and pitch. With the filter switched in, single-signal reception was accomplished. Again, as with the voice reception, progressive switch positions tighten up the audio passband. The sharpest selectivity should be used only with the worst interference.

Using stereo headphones improves CW enhancement enormously. When you compare input and output signals, the CW signal seems to float in the center of your head! Additional improvement is noted when strong pulse-noise interference (such as line noise and static) is present. The noise limiter acts like a scrubber, repressing the noise while passing the audio tone.

The model MFJ-721 filter is constructed on a single PC board, uses high-quality components (it features stable polystyrene capacitors), and is well engineered. For the serious hobbyist, the model MFJ-721 would be an asset. It is available for \$59.95 from MFJ Enterprises, P. O. Box 494, Mississippi State, MS 39762. R-E

Micro Software Systems PET Programs

CIRCLE 103 ON FREE INFORMATION CARD
METRIC-CALC, CHEQUE-CHECK AND MICRO-SET I are three interestingly different programs that underline the great versatility of the ever-growing personal computer. All the programs run on an 8K Commodore PET (Personal Electronic Transactor) computer.

Metric-Calc turns a PET into a Reverse Polish Notation (RPN) scientific calculator; and it will be quickly adopted by Hewlett-Packard calculator owners. For those not familiar with RPN, the basic idea is to key in
continued on page 34


Interface your TRS-80 to the "real world" the faster and easier way.

A P has the hardware you need
to build the Interface breadboard
described in the article on page 51.


The Jumper. A 24" 40 conductor flat ribbon cable assembly with a socket connector on one end, a card-edge connector on the other. It's preassembled and every line is pretested. 924150-24 \$11.95



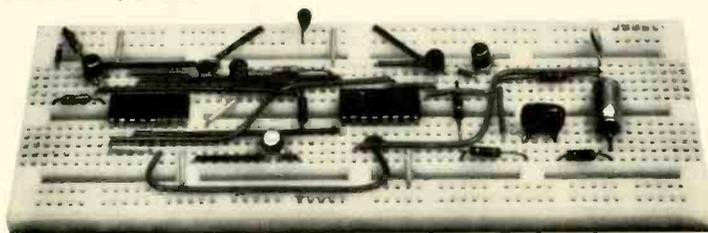The Solderless Breadboard. It's our famous "Superstrip" for unlimited freedom in the layout and implementation of your circuits. 923252-R \$17.00



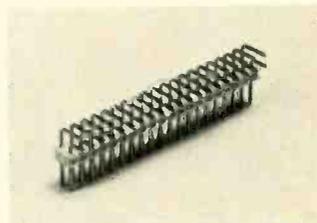The Header. Copper alloy 770 for instant plug-in access to the PC board. 923875-R \$2.79



Available at your dealer; for the nearest one, phone (toll-free) 800-321-9668. And ask for the complete A P catalog, *The Faster and Easier Book*.



"Faster and Easier is
what we're all about."



AP PRODUCTS
INCORPORATED
Box 110B • 72 Corwin Drive
Painesville, Ohio 44077
Tel. 216/354-2101
TWX: 810-425-2250

CIRCLE 60 ON FREE INFORMATION CARD

EQUIPMENT REPORTS
continued from page 32

the operators first (i.e., the numbers) followed by the operation itself. The method has some advantages over more conventional algebraic key sequences, including fewer memory-store operations. Its disadvantages are having to learn a new entry method, and the unavailability of parentheses operations.

You might ask why a computer should act like a calculator. Isn't this diminishing the power of a sophisticated programmable machine? The answer is yes and no! Yes, the computer loses its programming and general flexibility, but only for the time you are running this particular program; and no, it makes available functions that are not other-

wise directly addressable.

There are times when my calculator is not at hand or I'm already working at the PET keyboard, when it is convenient to use the PET as a calculator in the immediate mode via PRINT commands. But you have to realize that while PET BASIC is an extended version of the interpreter, many scientific functions are not in its vocabulary. Although sine, cosine, tangent and arctangent are included in the PET, secant, cosecant, arcsine and the other trigonometric functions are not. Natural logarithms are built-in, but common logarithms which are needed for example to calculate attenuation in dB are not.

The *Metric-Calc* program has two modes of operation that can be quickly interchanged while saving the results of the previous mode. In each mode a menu is displayed showing the

keyboard operations that represent the various calculator functions. The first mode is the scientific calculator in which the five top values of the stack are continuously displayed. Any value in the 20-level stack can be retrieved on command. By contrast, hand-held calculators typically display one stack element at a time and have a stack that is only four elements deep. Changes in stack contents are indicated by blinking digits even when the previous values and the new values are identical. The second operational mode provides conversions between English and Metric, linear, area, volume, weight and temperature units.

The *Cheque-Check* program helps you balance your monthly checkbook statement. The system provides a choice of six functions that allow you to view or change checkbook entries. Each operation is followed by an automatic summary display that ends with the amount your checkbook balance differs from the adjusted statement balance.

First, you enter the balances on the bank statement and checkbook. Then, as you enter checks and deposits, the total outstanding balance is displayed. After the summary display you can review your entries and attempt to correct the error, each correction being followed by another updated summary. Your final success is rewarded with a congratulatory message. The program itself is much more extensive than the level of necessary math might suggest. Clear instructions and formatted summary displays contribute to program complexity.

The third program is *Micro-Set I* (version 1.72), an improved version of a program reviewed in the March 1979 issue. I am happy to report that the problems I encountered the first time around have been corrected. Briefly, *Micro-Set I* is a programming aid that includes the following capabilities: it can renumber lines, delete lines, create and add from specially formatted ASCII program files, and report information about your BASIC program.

I experienced one problem while trying to combine two long programs that had a total memory requirement exceeding 8K. I could not successfully add all of the second program to the first program using the ADD command even though the machine I used was equipped with 24K of memory. I followed the total procedure twice. Each time the second load operation terminated at the same place. The cursor was lost and the machine would not respond to any operation. When power is interrupted, this causes the loss of the program. There appears to be some inherent program-size limitation although there were no such warnings in the instructions. Shorter programs did merge correctly, and combined program lengths of less than 8K minus the memory used by *Micro-Set I* are presumably all right.

Metric-Calc and *Cheque-Check* sell for \$7.95 a copy, and *Micro-Set I* costs \$14.95. All are available from Micro Software Systems, P.O. Box 1442, Woodbridge, VA 22193. **R-E**

SST Model T-4 Antenna Tuner

THERE IS LITTLE QUESTION THAT THE ANTENNA is as important as any other component in radio communications. A properly tuned antenna may make the difference between effective transmission and marginal performance.

Many antennas are designed to be self-resonant to conveniently match coaxial-cable im-



PROFESSIONAL TOOL CASE

Interchangeable Screwdrivers, Nutdrivers, Other Tools and Handles -

- 99-1, 1-R, & 4-R Handles (regular, straight and Tee ratchets)
- 99X2 Square Adaptor
- 99K5 & X10 Extensions
- 99-38 & 39 Reamers
- 99-70 Awl/Scriber
- 99-125, 250, 312, & 811 Slotted Screw Blades
- 99-820, 821, & 822 Phillips Screw Blades

Pliers, Wrenches, Cutters

- 42H Straight Nose Seizer
- 46C Adjustable Wrench 16"
- 50CG Midget Slip Joint Plier (5")
- 51CG Long Nose Plier (6-1/2")
- 53CG Utility Plier (7")

- 54CG & 66CG Diagonal Pliers (4" & 6")
- 57CG Needle Nose Plier (5-1/2")
- 59CG Cham Nose Plier (8")
- 86CG Electronic Sizer
- 103-S Wire Stripper/Cutter
- K-22 Electrician's Knife

Sets & Kits

- 99-PS-40 Hex Socket Screwdriver Blades & Handle
- 99-PS-60 Bristol Multiple Spine Screwdriver Blades & Handle
- M-60 Mini Drivers
- PS-120 Compact Convertible Nutdrivers
- XL-75 Offset Ratchet Screwdrivers

600 Combination Screwdriver/Nutdriver Tool

Screwdrivers

- Slotted Screws: R-144 R-3323
 - R-146 R-5325
 - R-181 S-388
 - R-184 S-3161
 - R-3164 S-5161
 - R-3166 S-5166
- Phillips Screws: SX-101 XST-101
- Hex Socket: XST-100 XST-102
- P-18 & 19 (028 & 035)
- Nutdrivers** HS-8, 8, 10, 11, 12, 14, 16, 18 Hollow Shaft
- 8M & 10M Magnetic

MODEL TC-100

Larger, more elaborate of the two cases. Contains 41 individual tools, 16 Series 99 interchangeable screwdriver/nutdriver blades and handles, and 5 specialized screwdriver/nutdriver kits, as listed. Case (11-1/2" x 13-1/2" x 6-3/4") covered with attractive, tough, chestnut-brown, weathergram Marvlon. Removable three-panel, hinged pallet and tray outfitted with elastic loop and transparent plastic pocket tool holders. Solid brass locks, latches, and hardware. Padded handle. Partitioned bottom compartment for other tools.

CHRISTMAS SPECIAL

\$289.95

Shipping not included.

Xcelite List Price \$495. Offers ends Feb. 29, 1980

THE TEST EQUIPMENT SPECIALISTS


TOLL FREE HOT LINE
800-223-0474

ADVANCE ELECTRONICS

54 West 45 Street, New York, N.Y. 10036 212-687-2224

Grandfather's Clock Was Never Like This!

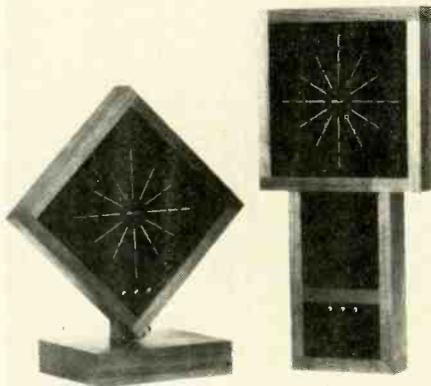But Santa is delighted—He knows that the **AMELECT** clock is the gift that keeps on giving!



If you love contemporary design but want the more traditional, here is *the* clock for you. In creating our own version of the ever popular Grandfather Clock, we use the electronic eye to display each second, minute, and hour, and also the simulated pendulum motion.

The diagonal model which has no simulated pendulum is available for wall mounting or with base as a desk clock.

Our synthesized sounds composed of tic toc, modified Westminster Chimes and Bongs are available for any **AMELECT** clock. The chimes and bongs are composed of six frequencies, providing realistic bell sounds. They are totally within clock cabinet.

The **AMELECT** clocks, cabinets may be your choice of Cherry, Mahogany, Maple, or Walnut hardwoods.

Special Christmas prices
until December 15th only

	Assembled	Kit	Base
CL7401A Diagonal	\$64.50	\$49.50	\$9.60
CL7402 Grandpa	\$84.50	\$66.50	
Chimes	\$40.00	\$35.00	

Indiana residents include 4% sales tax.
Shipping and Handling \$3.50
To order write or call 1-219-297-3320

Allow 4 to 6 weeks for delivery

AMELECT

INCORPORATED

Postoffice Box 367

GOODLAND, INDIANA 47948



CIRCLE 104 ON FREE INFORMATION CARD

pedance. An antenna tuner, or transmatch, is effective in providing optimum signal transfer between a radio transmitter (or receiver) and any antenna system.

The *model T-4 Ultra Tuner* from SST Electronics provides continuous operation between 1.8 MHz and 30 MHz. It can withstand 300 watts of RF power, and a built-in SWR meter is sensitive enough for low-power CB applications.

The manufacturer claims that the tuner will match any antenna—either coax-fed or random-wire—on any frequency within its tuning range. A switch located on the rear apron allows you to switch between two antennas.

High-quality components are used: For example, the 200-pF tuning capacitors have 1000-volt spacing; SO-239 connectors are used for coax input/output attachment; and Johnson binding posts are used for random-wire and ground connections.


One minor weakness is the location of the low-frequency toroidal coil—it dangles by its own leads within the larger air-wound inductor. This could result in metal fatigue and subsequent coil failure as a result of continuous bouncing and vibrations of a mobile installation. Additionally, if the toroidal coil shifts position it could cause some detuning of the air-wound inductor. The toroidal coil could be secured with a dab of silicone rubber cement if it presented a problem. In a fixed operating location the unit performs very satisfactorily.

The accompanying instructions are very superficial; they are adequate however for acquainting you with the basic tuning procedure. The schematic is only a partial diagram, and component values are not given. None of these criticisms affects the operational performance of the *model T-4 Ultra Tuner*. The instrument is well constructed, carefully wired and easily met the claimed performance specifications in our on-air tests. The *Ultra Tuner* sells for \$69.95 and is available from SST Electronics, P.O. Box 1, Lawndale, CA 90260. **R-E**



"What do you have in the way of a TV that uses an indoor antenna?"


Time Saving/Money Saving Precision Tools

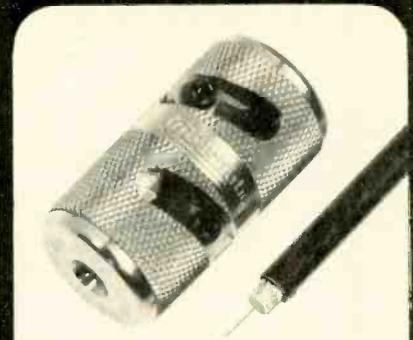

Coax Cable Stripper

This little tool can make the big difference in signal reception! Prepares cable for connector perfectly without nicks or scratches and in seconds!

MODEL	CABLE	CONNECTOR
UT-5800	trims RG-58/U	for PL-259
UT-5900	trims RG-59/U	for "F"
UT-5901	trims RG-59/U	for PL-259 or TV wall plate
UT-6000	trims RG-6/U	for "F"
UT-8000	trims RG-8/U	for PL-259

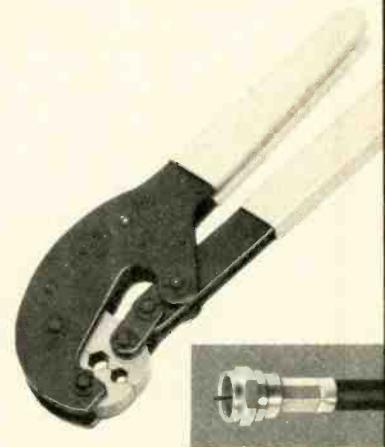

Hex Crimp Tool

For the installer using the long crimp rings for better connector retention and improved shielding—the extremely rugged CR-596 Hex Crimp Tool is the ideal answer. The CR-596 is designed for crimping the "F" connector for both the RG-59/U and RG-6/U.



RIPLEY COMPANY, INC.
UTILITY TOOL DIVISION
CROMWELL, CT 06416 (203) 635-2200

CIRCLE 31 ON FREE INFORMATION CARD

Sabtronics new counter gives you 600 MHz capability for only \$89.95



This highly accurate frequency counter can be yours at the unbelievably low price of \$89.95. The Sabtronics 8610A is your best buy today in a lab-quality instrument.

We spent our efforts where they count: applying Sabtronics' advanced digital technology in the design and engineering of a superior frequency counter — in simple kit form.

You count your savings:

You spend a little time (and a lot less

BRIEF SPECIFICATIONS

- Frequency Range: 10 Hz to 600 MHz guaranteed (5 Hz to 750 MHz typical).
- Sensitivity: ≤ 10 mV RMS, 10 Hz to 100 MHz, prescaler mode; 50 mV RMS, 100 MHz to 450 MHz; 70 mV RMS, 450 MHz to 600 MHz.
- Impedance: 1 M Ω , 10 MHz & 100 MHz range; 50 Ω , 600 MHz.
- Temperature Stability: 0.1 ppm/ $^{\circ}$ C.
- Gate Time: Switch-selectable, 0.1 sec., 1 sec., 10 sec.
- Ageing Rate: $\leq \pm 5$ ppm/yr.
- Accuracy: 1 ppm + 1 digit.
- Input Protection: 150 V RMS, 5 Hz to 10 kHz; 90 V RMS, 10 kHz to 2 MHz; 30 V RMS, 2 MHz to 100 MHz; 10 V RMS, 100 MHz to 750 MHz.
- Power Requirement: Battery-operated, 4.5 to 6.5 VDC @ 300 mA. External power supply, 7.5 to 9 VDC @ 300 mA.
- Size: 8"W x 6.5"D x 3"H (203 x 165 x 76 mm).
- Weight: Without batteries, 1.2 lbs. (0.54 kg).

money!) for a compact bench-portable counter that measures up to 600MHz (typically even higher).

Measures up on every count:

It has what you want. Guaranteed from 10Hz to 600MHz in three ranges (typically 5Hz to 750MHz). Sensitivity that holds well over the entire range. Selectable gate time for optimum resolution: 0.1, 1, or 10 seconds. With a stability of 0.1 ppm/ $^{\circ}$ C. And the guaranteed frequency range has a measurement accuracy of 1 ppm + 1 digit -0.0001%.

Highly accurate time base and excellent ageing rate. 8-digit LED display with automatic decimal point placement, leading zero suppression and overflow indicator.

Start counting the day you receive it: You can assemble your 8610A in an evening with our easy-to-follow, step-by-step instruction manual.

Count on satisfaction: Keep our kit for 10 days' free trial examination. If you're not completely satisfied for any reason whatsoever, simply return it unassembled for a prompt and courteous refund of your purchase price.

Making Performance Affordable

sabtronics 
INTERNATIONAL INC.

13426 Floyd Circle M/S 35 Dallas, Texas 75243
Telephone 214/783-0994

To: Sabtronics International, Inc. 13426 Floyd Cr., M/S 35, Dallas, TX 75243 USA

Please send me _____ Model 8610A
Frequency Counter Kits @ \$89.95 ea.

\$ _____

Shipping & handling, per kit, \$6.00*

\$ _____

Texas residents add 5% sales tax

\$ _____

Total enclosed

\$ _____

I enclose check money order. (For faster delivery, send cashier's check or money order. Please allow time for personal checks to clear bank.)

Charge: Visa Master Charge

Account No. _____

Exp. Date _____

Name _____

Address _____

City _____

State _____

Zip _____

*US only. Canada: \$7.50. Foreign, air mail, \$21.00.

Sabtronics NEW Hand-held Digital Multimeters . . .

The only thing that beats their performance is their price.

Accurate performance you can rely on, time after time. That's what you expect from a quality DMM. But don't expect to pay as much for it any more. Because now Sabtronics brings you top quality DMMs with more features and better accuracy than other comparable units on the market today. And they cost surprisingly less!

We cut the price. Not the quality.

What you get is a precision crafted unit that features single-chip LSI logic, laser trimmed resistor network and a stable band-gap reference element for better long term accuracy. Basic DCV accuracy is 0.1%. The Model 2035A gives you 32 measurement ranges over 6 functions and the Model 2037A an additional two temperature ranges.

First in features. First in price.

Both models feature touch-and-hold capability with the optional probe - its so convenient, you'll wonder why the expensive models haven't got it yet! And two-terminal input for all measurement functions - this eliminates lead switching and makes your job easier. The Model 2037A even has a built-in temperature measuring circuit with a -50°C to +150°C range (-58°F to +302°F) and is supplied complete with the sensor

probe. Of course, auto zero, auto polarity and overload protection are standard. And you get 200 hour operation from a single 9V transistor battery. A low battery indicator warns you of the last 20% of battery life. The large, crisp LCD readouts allow easy viewing even in bright sunlight.

Assembling either kit is simple with our easy-to-follow, step-by-step instructions. And the built-in calibration references allow you to calibrate the unit any time, any place.

We've even eliminated difficult inter-connect wires. All parts mount on the PC board. The only wires you solder are the two battery-snap leads.

Biggest value in small DMMs


To sell hand-held DMMs with all these features at such low prices, we had to sacrifice profits. But we never sacrificed quality or performance. We are so sure that the Model 2035A and 2037A are the best values available that we offer a money-back guarantee. Examine either unit in your own home for 10 days, and if you are not convinced that it is the best value for your money, return it in its original condition for a prompt

and courteous refund of the purchase price (less shipping and handling). Order yours today! Use the convenient order form or call us with your Master Charge or Visa number.

Making Performance Affordable

sabtronics INTERNATIONAL INC.

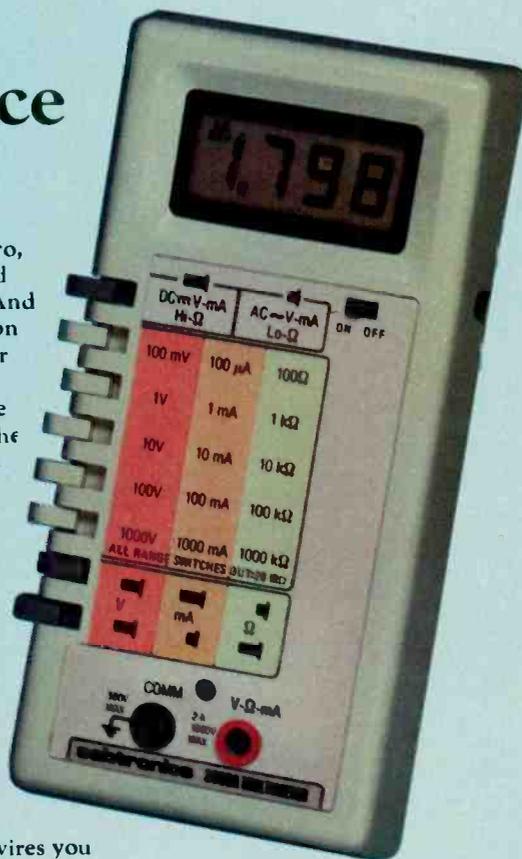13426 Floyd Circle M/S 35 • Dallas Texas 75243
Telephone 214/783-0994



BRIEF SPECIFICATIONS:

DC VOLTS: 100 μ V - 1000V, 5 ranges
AC VOLTS: 100 μ V - 1000V, 5 ranges
DC CURRENT: 0.1 μ A - 2A, 5 ranges
AC CURRENT: 0.1 μ A - 2A, 5 ranges
Hi-OHMS: 0.1 Ω - 20M Ω , 6 ranges
Lo-OHMS: 0.1 Ω - 20M Ω , 6 ranges
TEMPERATURE: -50°C - +150°C
(-58°F - +302°F), 2 ranges
(Model 2037A only).

WEIGHT: 11 oz. (excl. battery)
OVERLOAD PROTECTION: 1000V DC or AC peak all voltage ranges; 250V DC or AC peak all Ohms ranges; 2A/250V fuse all current ranges.

Mail to: Sabtronics International, Inc., 13426 Floyd Circle, M/S 35, Dallas, Tx 75243.

Please send me . . .

_____ Model 2035A Hand-held Multimeter kit(s) @ \$74.95 each	\$ _____
_____ Model 2035A Hand-held Multimeter assembled @ \$99.95 each	\$ _____
_____ Model 2037A Hand-held Multimeter kit(s) @ \$89.95 each	\$ _____
_____ Model 2037A Hand-held Multimeter assembled @ \$119.95 each	\$ _____
_____ #THP-20 Touch-and-hold Probe(s) @ \$19.95	\$ _____
_____ Shipping and Handling @ \$5.00 per instrument*	\$ _____
For delivery in Texas, add 5% Sales Tax	\$ _____
I enclose <input type="checkbox"/> check <input type="checkbox"/> money order <input type="checkbox"/> Master Charge <input type="checkbox"/> Visa	TOTAL \$ _____
(Allow 2-3 weeks clearance time for personal checks). 10% deposit for C.O.D.	
Charge my credit card # _____ Expiry Date _____	

Name _____
Street _____ Apt. _____
City _____ State _____ Zip _____
*Continental U.S. only. AK, HI & PR: \$6.00. Canada: \$7.50. Foreign: \$19.00 Airmail.

Yesterday you could admire all-band digital tuning in a short wave receiver.* Today you can afford it.



RF-4900

Tune in the Panasonic Command Series™ top-of-the-line RF-4900. Everything you want in short wave at a surprisingly affordable price. Like fluorescent all-band readout with a five-digit frequency display. It's so accurate (within 1 kHz, to be exact), you can tune in a station even before it's broadcasting. And with the RF-4900's eight short wave bands, you can choose any broadcast between 1.6 and 31 MHz. That's all short wave bands. That's Panasonic.

And what you see on the outside is just a small part of what Panasonic gives you inside. There's a double superheterodyne system for sharp reception stability and selectivity as well as image rejection. An input-tuned RF amplifier with a 3-ganged variable tuning capacitor for excellent sensitivity and frequency linearity. Ladder-type ceramic filters to reduce frequency interference. And even an antenna trimmer that changes the front-end capacitance for reception of weak broadcast signals.

To help you control all that sophisticated circuitry, Panasonic's RF-4900 gives you all these sophisticated controls. Like an all-gear-drive

tuning control to prevent "backlash." Separate wide/narrow bandwidth selectors for crisp reception even in crowded conditions. Adjustable calibration for easy tuning to exact frequencies. A 3FO pitch control. RF-gain control for improved reception in strong signal areas. An ANL switch. Even separate bass and treble controls.

And if all that short wave isn't enough. There's more. Like SSB (single sideband) amateur radio. All 40 CB channels. Ship to shore. Even Morse communications. AC/DC operation. And with

Panasonic's 4" full-range speaker, the big sound of AM and FM will really sound big. There's also the Panasonic RF-2900. It has most of the features of the RF-4900, but it costs a lot less.

The Command Series from Panasonic. If you had short wave receivers as good. You wouldn't still be reading. You'd be listening.


*Short wave reception will vary with antenna, weather conditions, operator's geographic location and other factors. An outside antenna may be required for maximum short wave reception.



RF-2900

Panasonic
just slightly ahead of our time.

CIRCLE 37 ON FREE INFORMATION CARD

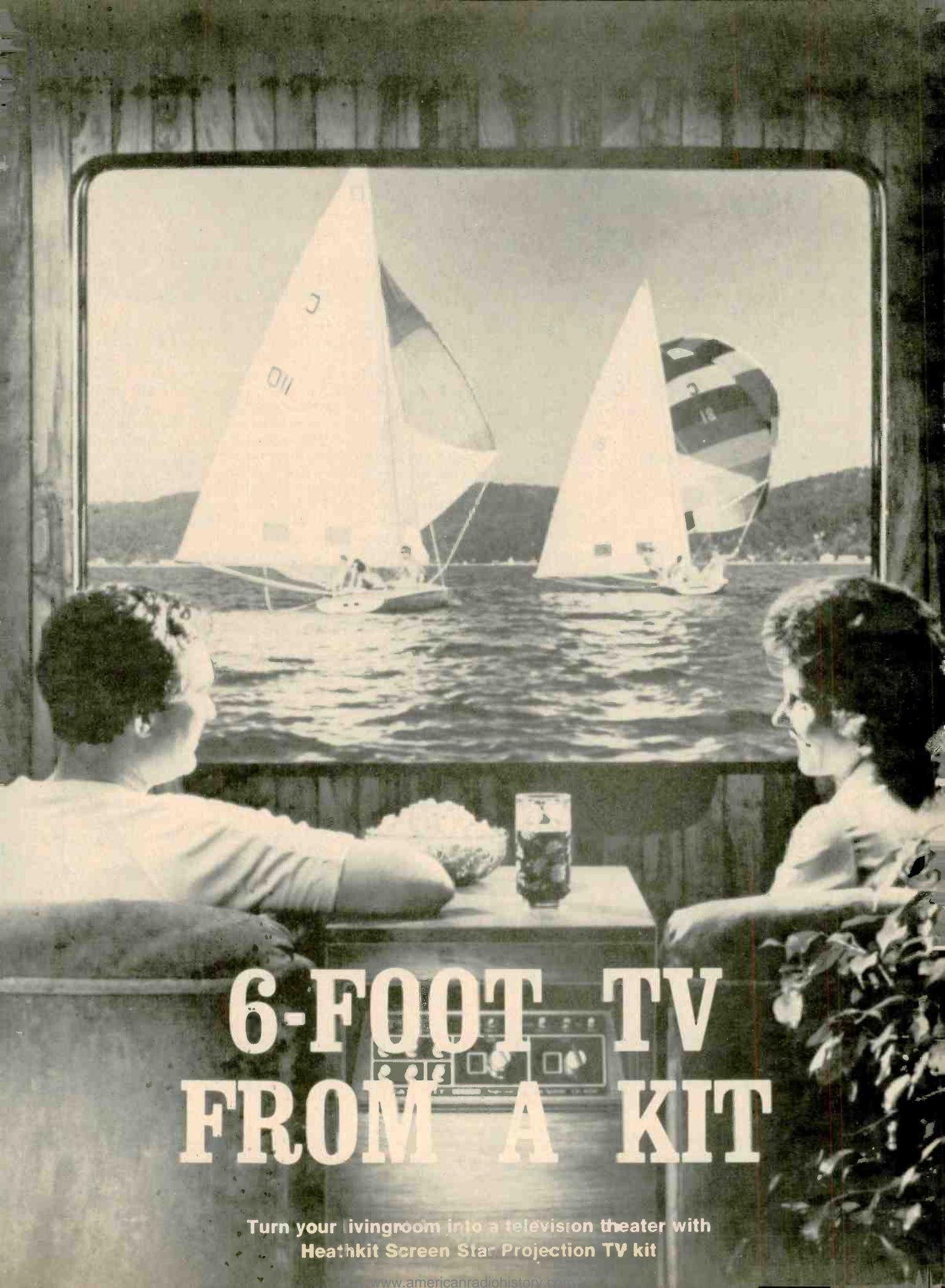

6-FOOT TV FROM A KIT

Turn your livingroom into a television theater with
Heathkit Screen Star Projection TV kit

Sworn to secrecy, I was ushered in the hi-fi listening room at the Heath Company plant in Benton Harbor, Michigan early last June. And that's when I first saw the new Heath projection color TV system. I remember remarking then on the really bright picture it produced (even in that brightly lighted room with its overhead fluorescent lighting) and the anticipated low price of the set. Today I'm free of my promise and in this exclusive preview report can reveal to you the details of what I consider a rather fantastic color TV projection system.

First let's take a look at what this set is and what it isn't. It is in the new Heath Catalog, neatly numbered as their model GR-4000 (all Heath color TVs are given a GR number). It has been named the *Star Projection TV Kit* and carries a price tag of \$2195 including the wall-mounted screen. An optional stand for the viewing screen that makes the screen portable and easy to mount will set you back an additional \$79.95. It's important to note that the \$2195 price tag makes it really worthwhile to build this kit. I don't believe that you can find a comparable set for less than \$2600 or \$2700. And that makes the 40 hours it is likely to take you to build the set worth \$400 or \$500.

As the title of this article points out, the Star Projection system delivers a picture that measures 6-feet across the diagonal of the screen. That's the same way that we measure that 19-inch, 25-inch or 26-inch set you now watch. It means that the GR-4000 delivers a picture that is eight times as large as that on the screen of a 25-inch set. For the rest of the specifications of the unit, check the table on this page.

Inside the chassis

Unlike the GR-2001, this projection set is not a state-of-the-art receiver. It does not have digital tuning with random access. It does not put the time or channel number on the screen. It does have a very solid and very conventional solid-state chassis right up through the video amplifiers. There it starts getting different, so there is where we will start looking at the circuit.

In this set there are three separate 3-stage video amplifiers—one for the blue, one for the red and one for the green. All are fed directly from the output of the chroma demodulator. The three stages consist of a matrix amplifier, a driver and an output. All are solid-state stages as is the entire set with the exception of the picture tubes.

The video signals are applied to the cathodes of the three separate projection tubes. The face of each CRT is coated with a different color phosphor—like the video amplifiers one is blue, one is red and one is green. As the electron beam strikes the phosphor, the phosphor lights up, emitting that color from its surface.

The intensity of each electron gun is controlled by chroma information fed to its cathode. By projecting these colors from the three tubes, through a lens system onto a screen and careful-

ly overlapping the three pictures and by varying the intensity of the colors being projected, different colors, including white, can be produced on the screen.

Vertical and horizontal deflection of the electron beam in each projection CRT is controlled by two sets of deflection coils in the yoke mounted on the CRT, just as is done in a black-and-white set. As current flows through the horizontal coil the electron beam is drawn across the screen. As current flows through the vertical coils the beam traces down the screen.

The picture that is created by the electron beams on the phosphors of the projection tubes is projected onto the 6-foot screen through a lens system. The lenses and the CRT's are carefully prealigned so that when the projector is positioned the proper distance from the screen, the three pictures overlap to produce a giant, but otherwise conventional color TV picture.


Setting up the screen

While we're talking about the screen let's break away from the circuitry for just a moment and talk about screen location. When you select a place for your screen, you must first consider the dimensions of your room, room lighting and traffic and where people will sit when viewing the set. For good TV viewing, people should be seated further from the screen than the distance between the screen and the projector. Since the projector must be positioned 7-feet from the screen for proper focus, viewers should be seated at least 9-feet from the screen.


The screen itself has a textured reflecting surface that acts like a mirror. It will reflect *any light* striking its surface. Any light source (such as a window or a door) that permits light to shine on the screen will also be reflected, and will detract from the picture brightness, contrast and viewability. Because of this problem it is important that the user position the screen so that it is in front of (on the same wall as) the light sources, rather

GR-4000 SPECIFICATIONS

Antenna Input Impedance: 75 ohms, with internal UHF/VHF splitter. **Tuning Range:** UHF channels 14 through 83, VHF channels 2 through 13. **AFT Pull-In Range:** 0.7 to 1.8 MHz. **Audio Output:** 5W at speaker and external 8-ohm speaker jack. **Total Harmonic Distortion:** Less than 0.5%. **30-dB Sound Quieting:** Greater than 100 dB at 1V. **Video IF Bandwidth:** 4.08 MHz at 6-dB down. **Peak Picture Sensitivity:** Greater than 100 dB. **Video Cassette Recorder:** IV composite video in/out at 75 ohms, 0.75 VRMS audio in/out at 600 ohms. **Projector Lenses:** 127-mm focal length, f1.0/1. **Projector Distance From Screen:** Approximately 98 inches. **Screen dimensions:** 45" high x 60" wide. **Projector Dimensions:** 28" high, 16 1/2" wide, 32" deep. **Power Requirements:** 120 VAC, 60 Hz, 150 watts.

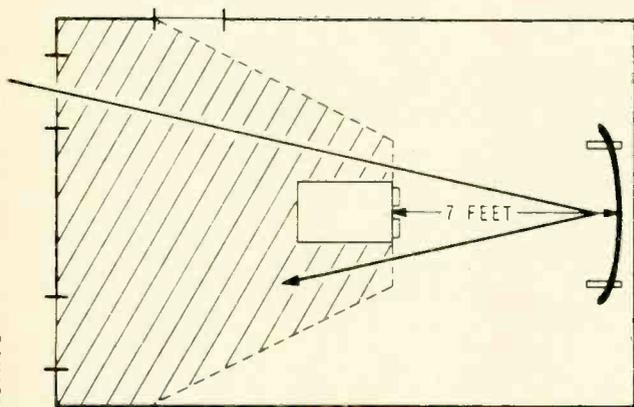

BAD

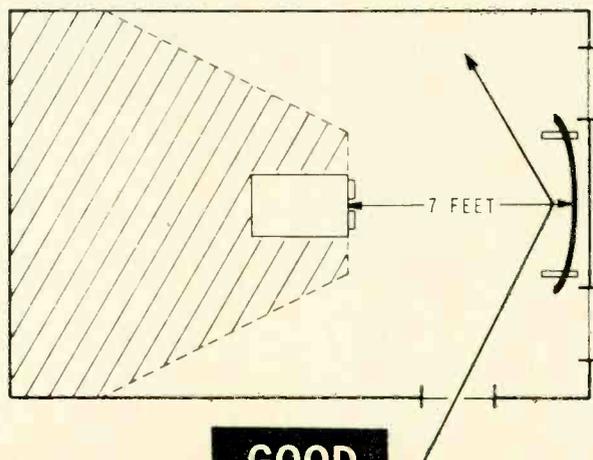

GOOD

FIG. 1—LOCATE THE SCREEN WHERE LIGHT from doors and windows cannot reflect off its surface. Good and bad screen locations are illustrated above.

than across the room from them. Figure 1 illustrates both good and bad screen positions and shows how light can be reflected back from the screen.

You've also got to be careful when setting up the screen to allow for traffic patterns (people traffic) through the viewing room. You certainly won't want other members of the family walking between the projector and the screen. Nor will you want them bumping into the screen. While the screen is not fragile—it can be handled with bare hands; it can be washed—it is not indestructible. If you should knock it down it could crack, so be careful. Also be careful when you hook up antenna, power, external speaker or VCR connections.

The projector sits in the middle of the floor. Remember it must be 7-feet from the screen. So you will have to be careful to run cables under carpets, around behind furniture or through protective trip-free conduit.

The audio system

The Star Projection TV has three separate audio outputs. First there is the connection to the internal speaker. This is a 6 x 9-inch oval speaker that can handle the full 5-watt output of the audio amplifier. And if you refer back the specifications box once more you'll note that third harmonic distortion is less than 0.5%. That means really good sound from the built in audio system. Second there is a jack for direct connection to an external speaker. It too has the low distortion 5-watt audio signal available and offers an 8-ohm impedance. Third is the audio output intended for use with a video tape recorder (you can also use this output to connect to your hi-fi system's auxiliary input). It delivers 0.75 VRMS at 600 ohms.

Features and construction

Plan on spending 40 hours to build this set. Some readers will find they can do it faster and some will need even more time, but at whatever pace you work take the time to doublecheck yourself. I've built more than one kit so hurriedly that when I was finished, I'd find that I'd have to spend the time I saved in assembly on troubleshooting.

When looking over the assembled unit (I have not built one of these so I cannot give you a personal report on assembly) I quickly noticed the relatively open chassis. In addition the plug-in ICs and circuit boards make any needed troubleshooting that much simpler. The chassis swings back to improve accessibility. All convergence control are located on the upper chassis where they are easy to reach. Separate focus controls for each of the three projection tubes helps keep pictures sharp. To help speed construction, the picture tube-lens assembly, high-voltage power supply and UHF and VHF tuners are all factory assembled and adjusted. A built-in crosshatch generator makes it possible

to reset convergence without external instrumentation. And as in other color TV's in the Heath kit GR series, there's a test meter included for making circuit checks before the projector is plugged in and turned on. It can also be used for servicing at a later date should repairs become necessary.

The electronics

Included in the circuitry is AFT (automatic fine tuning) and an exclusive Heath LC filter to maintain IF alignment and reduce drift, keeping the picture in tune when you switch channels. Heath says the IF amplifier never needs re-alignment. Special black-level clamps maintain constant blacks and greys for more accurate brightness levels.

Bridge-type power supplies are used for maximum voltage regulation. A ferro-resonant power transformer keeps supply voltages constant even when line voltages drop too low or climb too high. Proper voltage regulation guarantees constant brightness and picture size, even during a brownout.


The antenna splitter is built-in. This means only one antenna connection is required. And only one antenna cable to run across your livingroom. The true 75-ohm antenna hookup combined with shielded tuners helps when you're hooked up to a cable system by minimizing stray pickup of off-the-air signals.

Reception problems

All TV receivers are subject to the same reception problems—ghosts, focus, noise, etc. Unfortunately, as the picture gets larger these problems become more noticeable. That little spot of ignition noise on a 19-inch screen is now a foot long. So it is vital that you provide the best signal possible to your projection set. Don't

skimp. You've spent \$2195 and a lot of your time so make sure you have the very best antenna for your area. Use the best coax or foam-filled twin lead. If you need a preamplifier, get a good one. You won't be sorry if you do, you will be sorry if you don't.

R-E

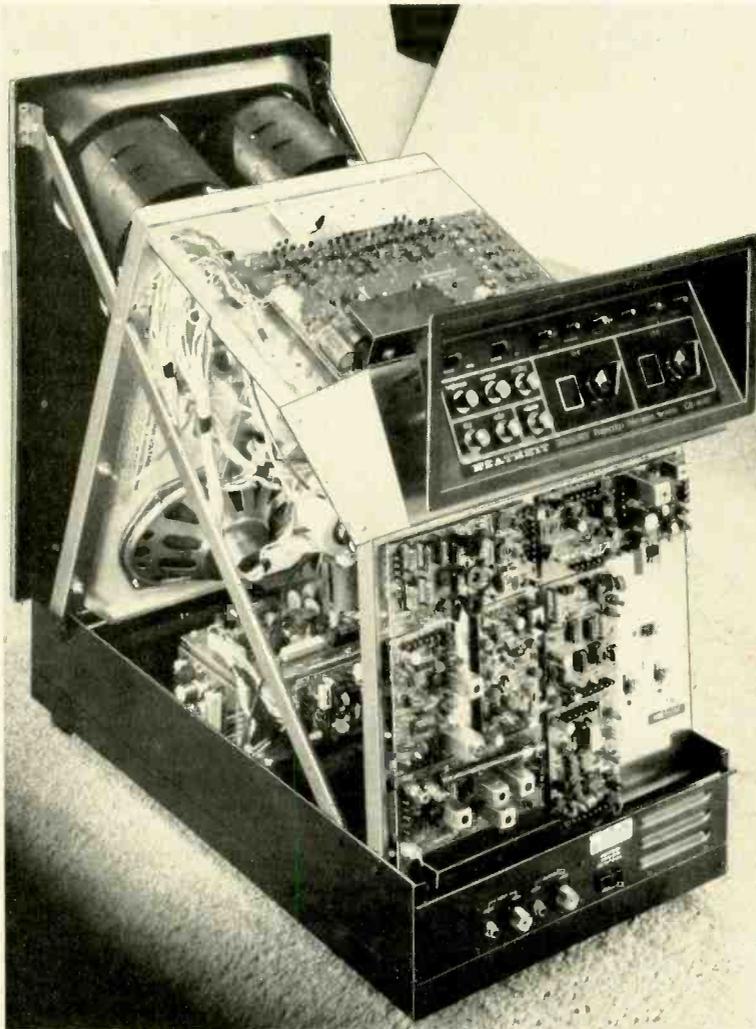

INSIDE THE PROJECTION TV CABINET you can get a good look at the chassis. It really isn't very different from any other high-quality TV receiver.



4-Bit Bipolar Microprocessor

The IDM2901A bipolar microprocessor from National Semiconductor is a 4-bit slice designed for high-speed applications in high-performance central processing units and programmable controllers. Figure 1 is the block diagram of the IDM2901A. It includes a high-speed ALU (Arithmetic Logic Unit), a microinstruction decoder, a 16-word by 4-bit 2-port RAM, and the necessary shifting, decoding and multiplexing circuits. The microprocessor has *tristate* outputs and four status flags. The 16-word memory has two 4-bit outputs that are indepen-

dently addressed by two separate address fields. In other words, two memory locations can be read simultaneously; for example, to be used as inputs to the ALU. Writing is done through a single additional input port, each bit of which is fed through a 3-input multiplexer.

The ALU performs binary addition and subtraction, as well as OR, AND, exclusive OR and exclusive NOR logic operations. An inhibit on either of the ALU inputs is equivalent to a zero operand. A left or right shift can be performed with an arithmetic operation

in the same machine cycle.

Processors can be cascaded for longer word lengths in 4-bit multiples. Carry-generate (\bar{G}) and carry-propagate (\bar{P}) outputs are used for carry-look-ahead for high-speed operation when units are cascaded. The IDM2901A uses low-power Schottky technology, and operates with clock frequencies of up to 20 MHz and read-modify-write cycle times of 60 ns.

Data sheets are available from National Semiconductor Corporation, 2900 Semiconductor Drive, Santa Clara, CA 95051. **R-E**

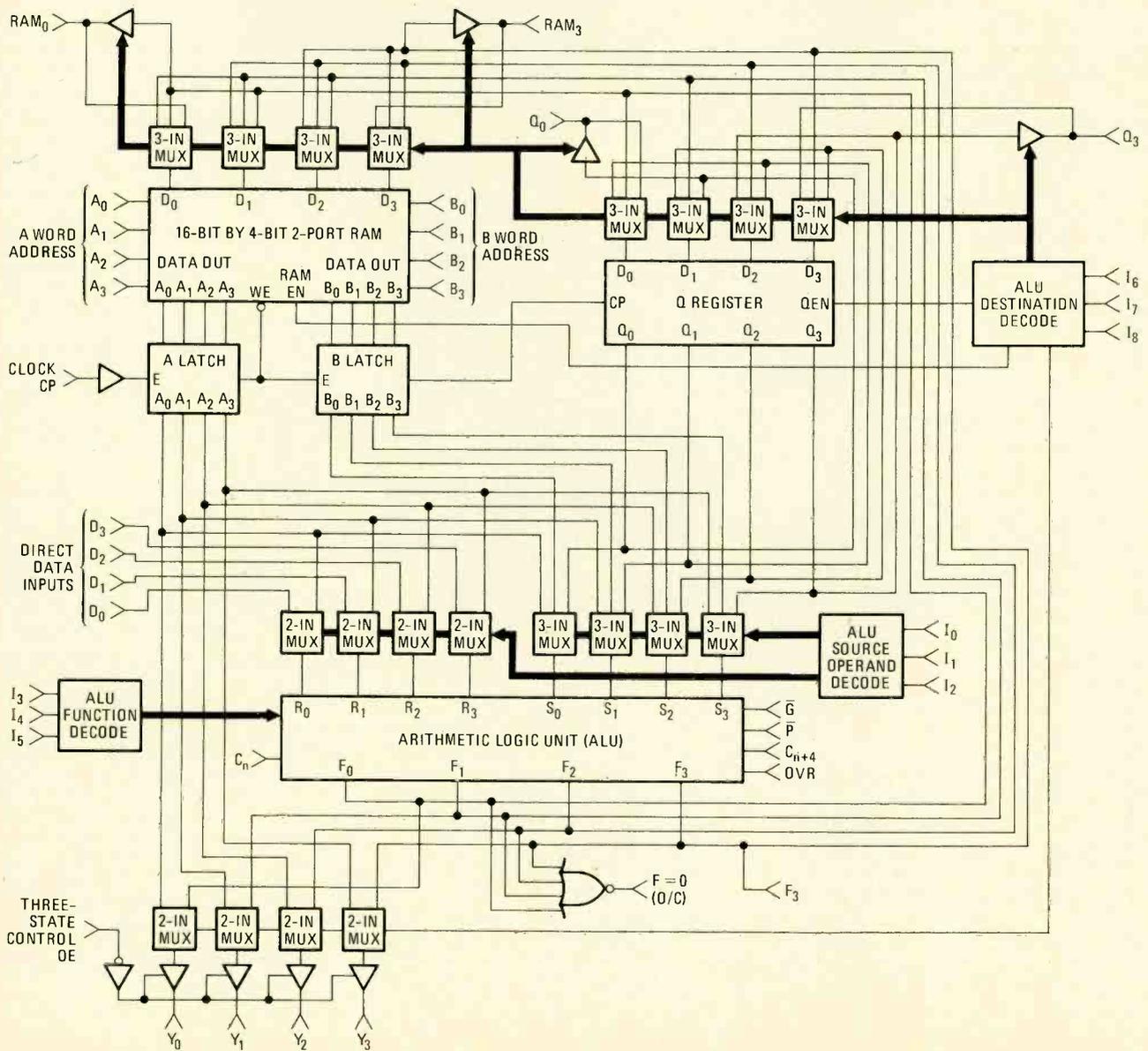


FIG. 1—BIPOLAR BIT-SLICE MICROPROCESSOR, block diagram of the IDM2901A.

Automatic Telephone Dialers

FRED BLECHMAN, K6UGT

Part 2—We've gone over the basics of automatic dialers, DTMF dialing and feature phones. Now we are going to take an in-depth look at the features and characteristics of the units listed last month.

LAST MONTH WE LOOKED AT DIALERS AND feature phones, DTMF dialing and installations, and a Comparison Chart summarized the characteristics and features of 19 units. This month we will examine each of the units in detail, in alphabetical order. All units (except the *TRS-80 Dialer Program*) are supplied with AC wall-plug transformers, and have adequate instruction manuals for normal use. Most units are also usable with PBX (Private Business Exchange) and WATS (Wide Area Telephone Service). However, if your intended use is special in any way, write the source listed with specific questions. All units carry reasonable guarantees (at least 90 days; some 1 year).


Blechman Enterprises, 7217 Bernadine Avenue, Canoga Park, CA 91307: The *TRS-80 Dialer Program* is a microcomputer cassette tape containing a program written in the BASIC Language for the Radio-Shack *TRS-80 Level II Microcomputer*. The tape is supplied with a program listing and instructions for entering up to 500 names and telephone numbers in a 16K RAM memory TRS-80 (or about 40 numbers with a 4K memory). A simple serial telephone interface can be built for less than \$5 using standard components. The program shows all names entered in memory in alphabetical order on the display screen. You type in the desired name on your keyboard and the computer puts the name and phone number (up to 14 digits) on the screen,

then actually pulse-dials the number. (The pulsing speed is set by the user in the program.) When the party at the other end answers, you hit ENTER and the screen tells you that you've been charged for one minute so far, displays running seconds and updates the minutes charged every 60 seconds! You can stop the timing at any time and either redial the last number, or relist all names, or dial any number from the keyboard. The timer automatically resets to zero.

If you have a computer other than the *TRS-80*, the documentation (listing and instructions alone—no tape) are \$5. You will probably be able to modify the program to run on your machine if you have expanded BASIC.

Ford Industries, Inc., 5001 S.E. Johnson Creek Blvd., Portland, OR 97222: (Phone toll free (800) 547-4683 for local distributor). These units carry the *Code-A-Phone* brand name. They make seven different units, of which two, The Dialer II and III, are distributed by JS&A. The others are described here.

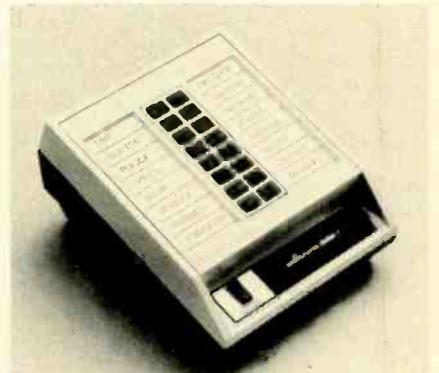The *Electronic Dialer I* is a very basic unit with no display and few special features. It is one of the most compact and stylish dialers available, but has a relatively low capacity of 16 numbers in memory (up to 15 digits each). Programming (with 3 button under a lift-up cover) is easy. Two silver-oxide watch batteries (supplied) provide power-failure backup to the memory. The button layout is



ELECTRONIC DIALER 1 from Ford Industries.

very orderly and a large space next to each button is provided for writing the stored name on easily replaceable ruled cards (extras supplied). Ten or 20 pulses-per-second (pps) dialing speed is selected with a switch. A CANCEL button allows you to break the connection if the line is busy and a dial-tone reappears automatically if the phone is not hung up—so you can try again. A special HOI-163 dual modular adapter is supplied for easy plug-in installation, with special instructions to telephone installers for the unusual cases.

The *Electronic Dialer VI* is just like the Dialer III (See JS & A listing), but has tone dialing as a switch selected option, in addition to 10 or 20 pps.

The *Electronic Dialer 32* is a double-capacity version of the *Electronic Dialer*

III. It uses a two-position memory switch so that each of the 16 buttons can be used for two distinct programmed numbers. Of course, you must be sure to put this 1-16 or 17-32 selector switch in the correct position, or when you push a button you may dial the wrong number! The display however, verifies the number being dialed. The CANCEL button, which is physically replaced by the two-position selector switch, is not needed; the ON/OFF switch does this.

The *Deluxe Electronic Dialer* has 32 separate buttons, each with a large space alongside to write names on removable cards. A 1/2" high 4-digit clock reads hours and minutes, and a second smaller



DELUXE ELECTRONIC DIALER is also from Ford Industries.

display reads the phone numbers being programmed or dialed. A moving decimal point shows the digit being dialed. The built-in speaker allows hands-off dialing and a volume control is used for conference calls—that is, the person on the other end of the line is heard through the dialer's speaker (although you must speak directly into the telephone to your party). A 3-way position switch selects 10 or 20 pps or tone dialing.

The *Memory-Phone* is a push-button feature phone with a 16-number memory. A one-way speaker allows hands-off dialing. Non-programmed numbers are dialed with the pushbuttons, and you can redial the last personally-dialed number by pushing the ON button and then the # button—all this without lifting the telephone. Instead of a loud bell, the *Memory Phone* uses a gentle electric tone ringer. There is no display—but neither does a regular phone have a display! Dialing is performed only at 10pps.

Heath Company, Benton Harbor, MI 49022: The only dialer we found sold in




HEATH ELECTRONIC DIRECTORY/DIALER model GT-1217

kit form is the *Heath Electronic Directory/Dialer*. The manual is up to Heath's normal high standard, and no errors were noted. Assembly time was 2 1/2 hours working slowly and carefully. A small portion of the printed circuit board has 2 relays and an integrated circuit pre-assembled and soldered to it to qualify the unit for FCC approval. A 9-volt battery is used for memory-power back-up.

The finished unit is very easy to program and use, with three LED's showing READY (phone off the hook), PULSE (dialing—10pps only) and STORE (used when programming). You can redial without hanging up the phone. Just push REDIAL and the phone disconnects for 2 1/2 seconds, then reconnects and dials. You can also hold the last number dialed in memory by pressing REDIAL.

The memory holds only 16 numbers, with 8 buttons in two columns staggered to allow a single name list between them. The name list is a dull-finished plastic strip that allows you to write in pencil and erase and reuse any number of times—a very worthwhile feature not found on any of the other units reviewed. Also, the name strips are pre-printed so that EMERGENCY, FIRE and POLICE will appear on the strip if you desire, or they can be cut off. A clear plastic removable window protects the written names. The back panel has two slots for wall mounting if desired. Connection to the phone line is through a 12-foot cable and interface block that you wire as part of the kit. Although this unit lacks some exotic features, it's very simple to learn to use, and wall-mounting can save desk space.

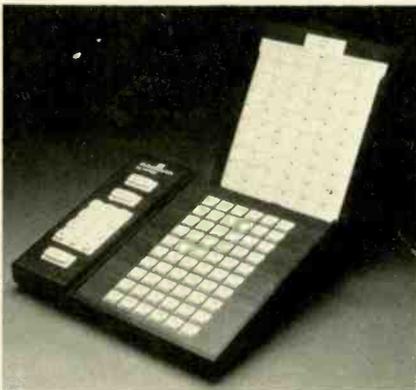HI-TEK Corp., Consumer Products Division, 12311 Industry, Garden Grove, CA 92641: There are **SIX** Autotouch by



AUTOTOUCH M60 from Hi-Tek

Hi-Tek models available or planned by Christmas of 1979. Only the M20 low-end and M60 high-end are shown in the chart to save space. The M20 has a 10/20pps switch and re-dial capability, and will allow programming up to 24 digits using adjacent storage locations. The M40 (\$199.95) is the same with 40 storage locations, and the M60 (\$249.95) is the same with 60 locations. The M42 (\$229.95) is the same as the M40 but with a speaker added for hands-free dial-

ing, and a HOLD button. The M62 (\$279.95) is the same as the M42, but with 60 storage locations. The top-of-the-line M63 adds tone dialing, a 12-digit LED display, clock, elapsed-timer, alarm and will redial a busy number automatically 17 times. Also, each storage location will hold 17 digits, and two adjacent locations can be used for a total of 34 digits! Easy programming is a feature of all the autotouch units.

Integrated Circuits Packaging, Inc., 750 North Mary Ave., Sunnyvale, CA 94086, Attn: Cliff Denchfield, Marketing Director: The *Superphone 7700* is a full-feature telephone, calculator, clock, alarm, calendar, call timer and 20 number dialer, with last number redial and manual dial capability. Dialing speed is 10pps only. The 8-digit calculator can be used anytime except when dialing (even during a call). When the 4-digit clock is displayed, A or P (for AM or PM) is also displayed, as well as the day-of-the-week and date-of-the-month, and a decimal



SUPERPHONE 7700 from Integrated Circuits Packaging, Inc.

point blinks each second. The month is not displayed, but is held in memory so that the proper number of days per month is correct (except on leap year!) The keyboard is like a *Touch-Tone* phone, but with 8 additional keys for dialer, clock, calendar, timer and alarm functions. The keys are clearly marked, and the white non-standard keys are protected with plastic covers.

It takes a while to get familiar with all the various features the *Superphone 7700* offers. The elapsed timer, which reads minutes and seconds and has a 1-second blinking decimal, can be activated at any time (except when dialing). It stops automatically when the phone is hung up and "freezes" (including the blinking decimal) until you press a button, so you can jot down the time anytime after the call is completed. It can also be used without the phone off the hook, and stopped manually. The single alarm buzzes for 2 seconds, and can be set for any hour and minute setting, AM or PM.

If you get a busy signal when calling, press REDIAL and even without hanging up, a dial-tone reappears and the last number redials. The *Superphone 7700* connects to the phone line just like any regular telephone, except the wall-plug transformer normally is also plugged in. Unlike the other feature phones tested,


the internal rechargeable batteries not only hold programmed numbers in memory, but also allow the *Superphone 7700* to dial—up to two hours—if there is a power failure! Five different colors are available: white, antique white, beige, brown and black. There are two models. The American model (7710) and the European model (7720) that comes with a 220V adapter and displays time in the 24-hour mode. (Contact Cliff Denchfield, Marketing Director for European model prices.)

JS & A National Sales Group, One JS & A Plaza, Northbrook, IL 60062: The *Code-A-Phone Electronic Dialers II and III* are made by Ford Industries and distributed by JS & A (among others). They are step-up versions of the *Ford Electronic Dialer I*, previously described. The *Dialer II* (\$149.95, not shown in the chart) has the added convenience of a built-in speaker to allow hands-free dialing. The *Dialer III* has the speaker plus a display that shows the number being programmed or dialed, with a decimal point that follows each digit as it is dialed. Otherwise, these units are virtually identical to the *Dialer I* in appearance and function.

The *Busy-Buster* is a feature phone with several special capabilities but one primary purpose—to bust through the busy-number barrier! You dial a number in the normal way, with regular pushbuttons (although the *Busy-Buster* actually dials with either 10 or 20pps, switch selected). If the line you're calling is busy, hang up and press a black button on the *Busy Buster*. A green light goes on. Forty seconds later the red LED pulses as *Busy Buster* redials the number! If it gets a busy signal again, it automatically dials again after another 40 second wait. It keeps doing this for up to 30 minutes! If your call goes through, you hear a loud, piercing tone from a piezo element. If you get an incoming call during the 40-second redial pause or you wish to make an outgoing call, the *Busy Buster* patiently waits for you to hang up, and then goes back into the automatic redialing mode! Also, by picking up the receiver and pressing the "*" button, the *Busy Buster* re-dials the last manually-dialed number, without forgetting the busy number. The automatic redial mode is cancelled by simply pressing the "#" button. You can dial up to 12 digits, including pauses programmed by the "*" button.

The *Busy Buster* is built into a modified ITT telephone case, but with a surprising amount of circuitry and versatility not found in a regular phone. The normal adjustable-loudness bell is retained. The *Busy-Buster* connects to the phone line with a modular plug, like a regular telephone, but with the addition of a wall-plug AC power pack. No batteries are needed.

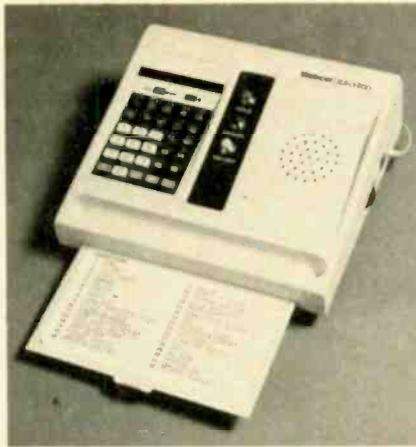Leisurecraft Products, Ltd., 28 S. Terminal Dr., Plainview, NY 11803: The




WEBCOR DIAL-A-TRON model 747 from Leisurecraft Products.

Webcor Dial-A-Tron model 747 is the only truly-portable dialer in this survey. Six "C" cells (included) provide adequate power for phone dialing as well as memory, although the AC adapter is recommended for normal use and required for pulse dialing. The *Dial-A-Tron* has switch selected pulse (10 or 20pps) or tone dialing. It can even be acoustically coupled to a telephone that has a tone-dialing exchange. By simply placing the phone mouthpiece over the *Dial-A-Tron* speaker, and putting the *Dial-A-Tron* in tone-mode dialing, the speaker tones "dial" any of the programmed numbers! This means the *Dial-A-Tron* does not have to be plugged into either the phone line or the AC line for programmed tone dialing. Manual dialing is not provided.

Thirty-two 10-digit numbers can be held in memory and displayed during programming or dialing. Another unique feature is a HOLD button, with flashing LED, even if your phone doesn't have one. A volume control allows group listening, and a hidden directory tray slides out from the front of the unit for reference. Special buttons hold long distance and access codes in memory.

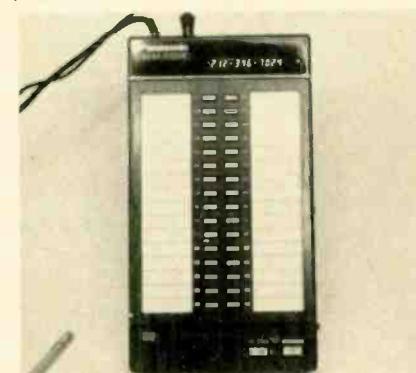Panasonic Consumer Affairs, One Panasonic Way, Secaucus, NJ 07094: The *Easa-Phone KX-T1210* has the lowest



PANASONIC EASA-PHONE model KX-T1220

height of any of the units in this survey, and is first class in appearance and operation. The top and sides of the cabinet are simulated wood. The AC adapter plugs into a socket in the rear of the unit, and

two back-up pencell batteries fit in a compartment at the bottom. Thirty-two individual clearly labeled keys are used, with plenty of write-in space for programmed names alongside the keys on long slide-out cards. Ten of the call keys are also used for programming. Underneath a flip-top panel are some additional programming buttons. A flip-top wire frame raises the rear of the unit for better visibility, if desired, and a special bracket and screws are provided for optional wall-mounting.

Up to 30 digits can be stored in adjoining memory locations. Hands-off dialing is set at 10pps, and a speaker is built-in. The programming keys even beep for entry verification. Programming and operation are simple. If the called party doesn't answer, the unit turns off automatically after the phone rings for approximately 1 minute. If the unit gets a busy signal, it automatically turns off after about seven seconds. However, suppose you wish to redial the last automatically dialed number; simply press the REDIAL button. If the line is busy or no one answers, the unit stops calling. But after about 30 seconds it will call automatically again and repeat this sequence 16 times before giving up! You can be nearby listening to the speaker, but don't have to lift the phone unless the connection is made.

The *KX-T1220* is almost identical, but has several step-up features. A 12-digit green fluorescent 1/4 inch high display shows digits when programming or dialing. Pulse dialing can be selected at 10 or 20pps, and a volume control is provided for the speaker.

Radio Shack, Forth Worth, TX 76102: The *Automatic Telephone Memory Dialer DuoPHONE-32* is available at all



DUOPHONE-32 from Radio-Shack

Radio Shack stores, or mail order. Although it is one of the least expensive dialers in this survey, it has more useful features than many of the others. It holds 32 programmed numbers in memory, using 16 buttons and an A-B selector switch. The slanted LED display not only shows each number as it's being programmed, but when you memory dial the entire number is displayed (up to 7 digits and a hyphen at a time) and each digit blinks as it is being dialed. The display normally shows hours and minutes with a 1-second blinking hyphen, but press the timer button and you have a minute/second elapsed timer that stops and holds when the timer button is pressed again.

You can then either clear the timer, or accumulate total time for several calls.

Programming is very straightforward using some additional buttons under a lift-up cover. There are REDIAL and CANCEL buttons to make operation simple. Unfortunately, the cover has no lifting tabs and is difficult to grasp. Also, the A-B programming switch is marked in a confusing manner that seems backwards. When the cover is lifted, the name cards, on which you can write 16 names, are easily replaced, and extra cards are supplied. Thoughtfully, Radio Shack also provides red self-adhesive stickers labeled DOCTOR, HOSPITAL, POLICE, FIRE and AMBULANCE to stick on the name cards if desired.

Installation is extremely simple. Plug in the AC adaptor, plug your phone into the dialer and insert the dialer modular plug into your phone jack. The AC adaptor cord and modular plug from the dialer are each over 6 feet long. Three pennell batteries are used for backup memory power. A 10- or 20-pps dialing speed switch is on the back. The pulsing relay is easily heard when in operation; a reassuring sound. Also, if the phone is left on the hook when a programmed button is pressed, the unit displays the number and pulses, but does not actually dial, so you can confirm the stored number. The last number dialed can be held in a redial memory, and a cancel button stops any dialing in progress.

Royce Electronics Corp., 1746 Levee Road, North Kansas City, MS 64116: This feature phone holds up to 35 numbers in memory (including specially-labelled POLICE & FIRE buttons) and has a



FREEDOM-DIALER from Royce Electronics

relatively large wide-angle LED display that normally changes every five seconds from time (hours, minutes, seconds) to month and date. When programming or dialing, the numbers appear on the display. When the elapsed time is commanded, minutes and running seconds are displayed until the phone is hung up or the CANCEL button is pressed. The 20 keys are color coded, with brown for memory programming, orange for time and date programming, blue for police, red for fire and beige for numbers 0-9. The keys are labeled on the front panel below each key—rather than on the key


tops—and this is confusing until you get used to it.

Automatic dialing first requires pressing the A/DIAL button, then the storage location number. Hand dialing is supported, with a 10 or 20pps switch underneath. Redialing the last number dialed (either manually or automatically) is accomplished with a single button.

When using the elapsed timer, a piezoelectric element sounds a reminder at 2-minutes and 48 seconds that 3-minutes (a minimum billing time on operator-assisted calls) is coming up. The piezo element also is used in place of the telephone bell, with a distinctive, pleasant tone.

A convenient phone number reminder, including operating instructions, is also supplied. It fits under the Freedom Dialer and pulls out when needed. Rechargeable batteries hold numbers in the memory for up to 3 hours, but the AC adapter is required for dialing.

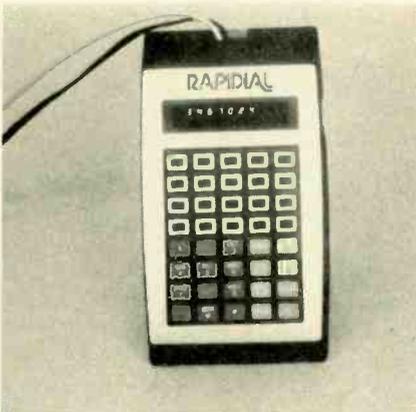Technology Applications Corp., 2660 Marine Way, Mountain View, CA 94043: The original *Rapidial* is an extremely versatile dialer in a small hand-



RAPIDIAL from Technology Applications

held calculator style case. Color-coded snap-action keys program 20 memories plus a re-dial memory, or allow hand dialing. The memory keys are blank, but lots of self-adhesive pre-printed and blank labels are supplied to identify memory contents. Hands-off dialing is supported by a small speaker, and the unit automatically disconnects from the line at the end of 30 seconds if you haven't picked up the phone.

The *Rapidial* is the lowest price tone-dialing unit available, with a 10pps switchable option for non-tone exchanges. The 8-digit LED display lets you see the numbers being dialed, or held in memory at each location. You can redial the last number dialed. Special buttons are used for "1", "0", PBX or WATS acquisition. Because *Rapidial* uses true DTMF *Touch-Tone*, it can be even used effectively for rapid dialing with specialized tone systems.

The *Rapidial*, despite its many features, has very compact circuitry all on a single, small PC board—by far the best packaging of the units reviewed.

The *Rapidial* manual includes use for electronic banking, installation on multi-line phones and international calls. Using DTMF, where such service is provided, *Rapidial* can be used for scheduling cable TV programming, credit verification/authorization, voice-response computer access, stock exchange floor paging and ordering (via FM transmission) and security alarm dialing. Hams can utilize the DTMF mode for repeater access by connecting the *Rapidial* output to their microphone circuit. Similarly, *Rapidial* can be used with mobile telephones.

The *Rapidial II* is the lowest-priced assembled dialer we found. It uses 10pps dialing (no DTMF), and two discrete LED indicators replace the digital display and speaker. Otherwise, it has the same small size, compact circuitry and excellent features of the *Rapidial*.

Wintron Merchandise Corp., 110 West 40th St., NY 10018: The *Otron CD8050* (other models may be available by the time you read this) is the Cadillac of dialers. In addition to holding 20 phone numbers in memory (2 banks of 10, switch-selected) it displays up to 14 digits on a relatively large display, has keys that "beep" when pressed for audible entry verification, functions as a 12-digit 5-function calculator or 6-digit clock when not dialing, has FIVE programmable, repeatable AM/PM beeping alarms, and automatically disconnects from the line after 90 seconds of hands-off dialing. Numbers can be dialed manually, with single-button redial of last number dialed. A volume control sets speaker loudness. Five discrete LED indicators keep you informed of status (dial, calculator, time-setting, upper or lower memory bank). Separate key pads are used for number entry and memory locations. Surprisingly, although a 6-digit is included, an elapsed time mode is *not* provided.



COMPUTER DIALER model CD-8050 from Wintron Merchandise.


Using all these functions takes some training, but the detailed manual guides you through the procedure with lots of illustrations.

Incidentally, one switch is shown, but not described in the manual. The DIALER-TEL switch on the back of the unit must be placed in the DIALER position for keyboard dialing—but this disables your reg-

continued on page 98

BUILD THIS

Percussion Synthesizer Accessories

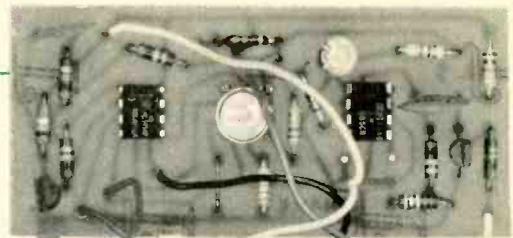

INSIDE VIEW OF THE SNARE accessory.

The PerSyn Percussion Synthesizer described earlier is a versatile instrument that generates the sounds of many common instruments. Round-out the range of percussive effects with these two easy-to-build accessories.

JAMES BARBARELLO

THE PERSYN PERCUSSION SYNTHESIZER SYSTEM DESCRIBED IN the September and October 1979 issues is a versatile instrument capable of synthesizing most any simple drum sound, gong, chime and other metallic sounds plus special effects. To complement this low-cost, versatile system, two additional accessories are described here that will greatly increase the system's capabilities.

The two conventional percussion sounds that could not be generated by PerSyn are the snare drum and cymbal. Both these sounds can be synthesized with a triggerable envelope-shaped white-noise source and, in the case of the snare drum, a coincident drumstick strike pulse. The Snare accessory described here produces both these effects. It can also be triggered with a pulse generator to create such effects as a steam engine and biplane.

The other accessory described here is a 3-channel, 8-bit trigger-pattern generator. This device produces three distinct 8-bit repeating trigger sequences. Each channel can trigger a PerSyn Generator and/or Snare accessory. Each bit in each pattern is user selectable on or off. This device will allow your PerSyn to double as a complex rhythm unit which will allow you to play while the sequencer is operating. Such features as $\frac{3}{4}$ or $\frac{1}{4}$ time selection, a CANCEL footswitch provision and start-of-pattern visual indication are included.

Both accessories use standard components and construction techniques and can be powered from the PerSyn TAP jack.

The snare accessory


Circuit operation: Referring to the schematic diagram in Fig. 1, we see that the emitter-base junction of transistor Q1 is reverse biased to produce an approximate white noise signal that is AC-coupled through C1 to the input of amplifier IC1-a. The output of IC1-a in turn drives transconductance amplifier IC2. The output signal amplitude of IC2 is determined by the voltage applied to pin 5.

A positive-going trigger pulse applied to J1 (or J2) is inverted by Q2 and AC-coupled through C3 to trigger the 555 timer, IC3. When triggered, IC3 produces a 25-millisecond positive-going pulse with a base voltage of -9 volts. This pulse quickly charges C6 through R16. After reaching its peak value, the voltage on C6 begins to exponentially decrease. The time for C6 to discharge is determined by the values of R13, R16 and the setting of DECAY control R14. During this discharging period, diode D1 is reverse-biased as the output of IC3 returns low. This prevents IC3 from rapidly discharging C6 when IC3 returns to the low state. The output of IC3 is also differentiated by C2 and coupled to amplifier IC1-a. The values of C2 and R8 result in a sharp "crack" (characteristic of a drumstick strike sound).

The voltage envelope developed across C6 and R16 is fed through R15 and is the envelope control voltage for IC2. The output of IC2 is buffered by IC1-b. The negative portion of the signal is clipped by D2, producing a more realistic snare or cymbal effect. A portion of this signal is tapped off LEVEL control R7 and provided to output jack J3. Power (± 9 volts) is provided through the "ring" (-9 V) and "tip" ($+9$ V) of PWR-jacks J4 or J5.

Construction: A PC board is recommended for assembling this device. The foil layout is shown in Fig. 2 and component placement in Fig. 3. If the CA3080 device is obtained in the 8-pin can (TO-5), the leads should be pre-formed to a DIP configuration before installing on the PC Board. All controls and jacks should be mounted in a suitable enclosure. Final wiring of the jacks, controls and PC Board can be performed using Fig. 4 as a guide. If a metal enclosure is used, the bodies of J4 and J5 (which are at -9 volts) should be isolated from the other jack bodies (which are at ground potential).

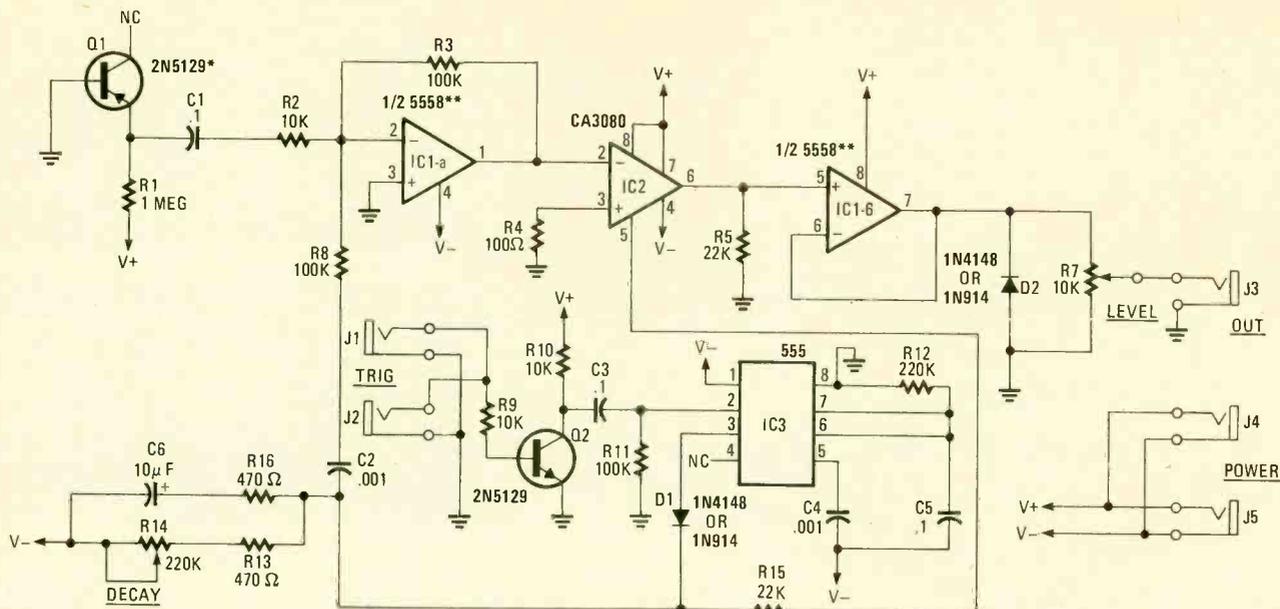Use: If the Snare accessory is to be used for Cymbal or special effects, remove C2 or R8 to eliminate the Strike sound. Connect either POWER jack (J4 or J5) to the TAP jack on PerSyn (or to



NOTE: R6 NOT USED
 *SELECT FOR NOISE CHARACTERISTICS
 **5558 OR LM1458 8-PIN DIP

FIG. 1—SNARE DRUM SIMULATOR accessory. Most of the circuitry is devoted to processing the "white noise" generated by transistor Q1.

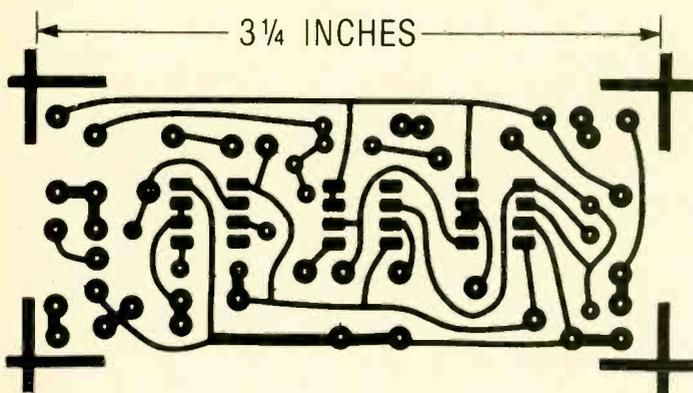


FIG. 2—FOIL PATTERN for the Snare accessory.

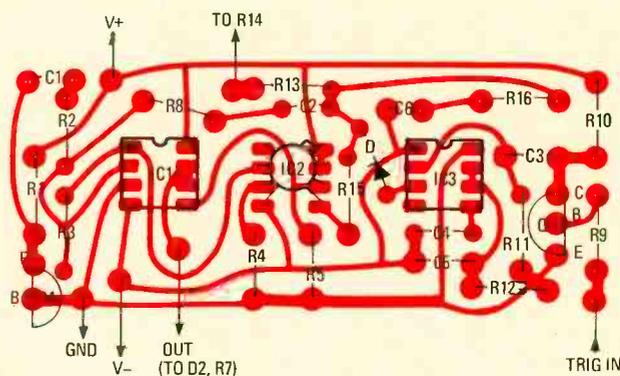


FIG. 3—COMPONENT LAYOUT for the Snare simulator accessory.

SNARE PARTS LIST

Resistors 1/4 watt, 5% or better

- R1—1 megohm
- R2, R9, R10—10,000 ohms
- R3, R8, R11—100,000 ohms
- R4—100 ohms
- R5, R15—22,000 ohms
- R6—not used
- R7—10,000 ohms, 1/2-watt potentiometer
- R12—220,000 ohms
- R13, R16—470 ohms
- R14—220,000 ohms, 1/2-watt potentiometer
- C1, C3, C5—0.1 µF disk ceramic
- C2, C4—.001 µF dlsc ceramic
- C6—10 µF, 10 volts or higher. Radial-lead electrolytic
- D1, D2—1N4248 or 1N914
- Q1, Q2—2N5129 (Select Q1 for its noise characteristics)
- IC1—5558 or LM1458 dual op-amp
- IC2—CA3080S, CA3080E or CA3080 (Form CA3080 leads to DIP configuration)
- IC3—555 timer
- J1—J5—phono jack, 1/8 inch

Miscellaneous: PC board, enclosure, wire, solder, knobs, etc.

Note: The following is available from BNB Kits, RD1, Box 241H, Tennent Road, Englishtown, NJ 07726: PC board (PSN-PC) \$15.00. Price includes shipping. No COD's. Please allow up to 6 weeks for delivery.

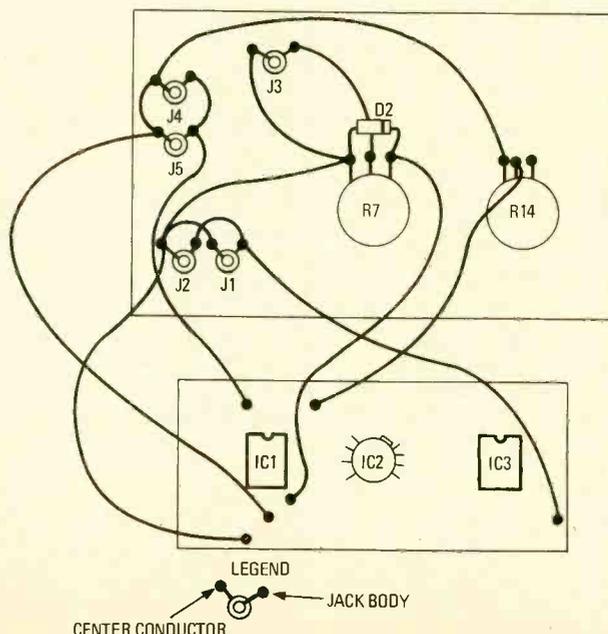


FIG. 4—FINAL WIRING diagram shows interconnections between the PC board and components on the instrument's panel.

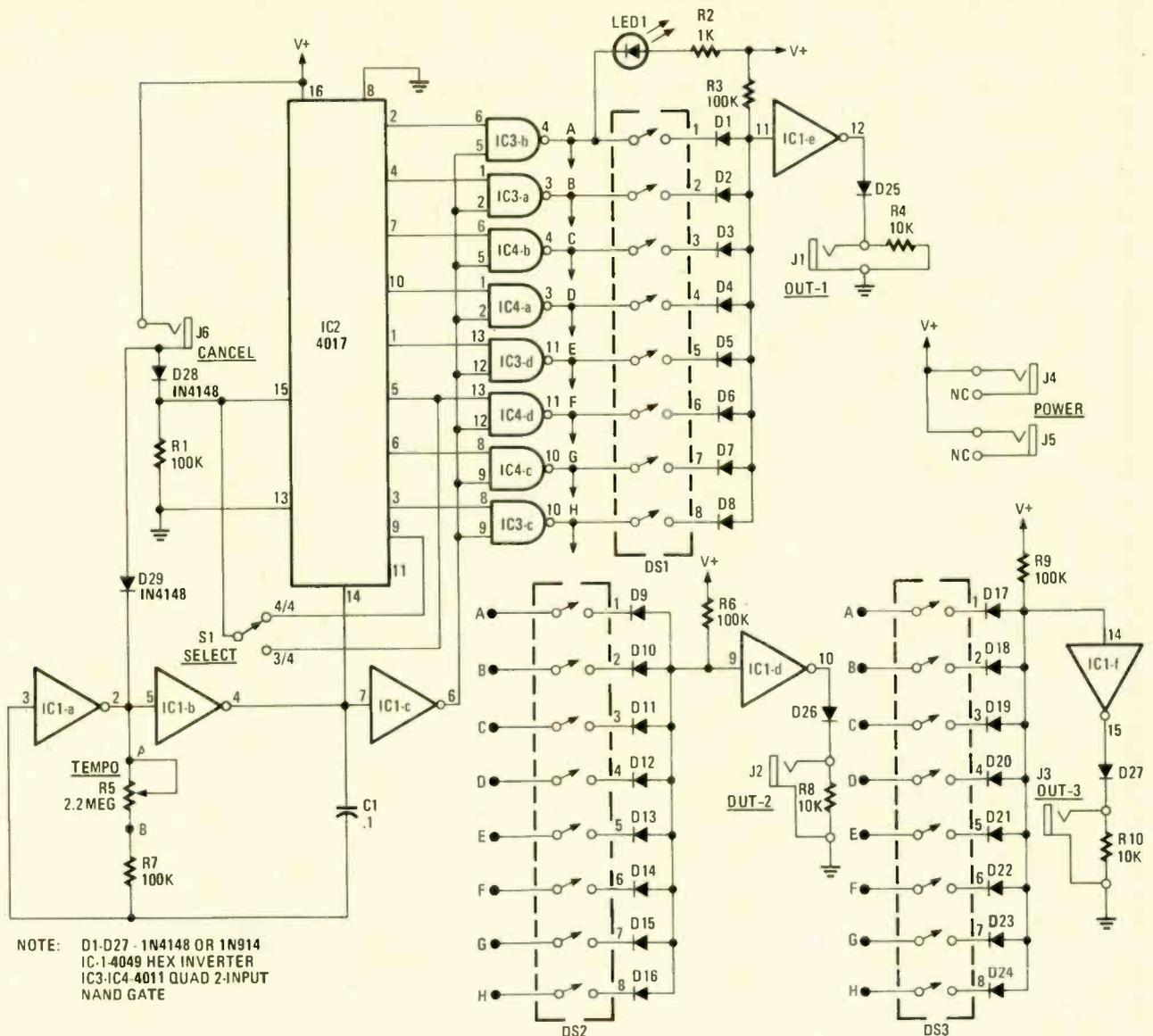


FIG. 5—SEQUENCER CIRCUIT. A variable-frequency oscillator clocks counter IC2. The eight NAND gates feed decoded outputs through a network of DIP-type switches to produce a complex serial output pulse train.

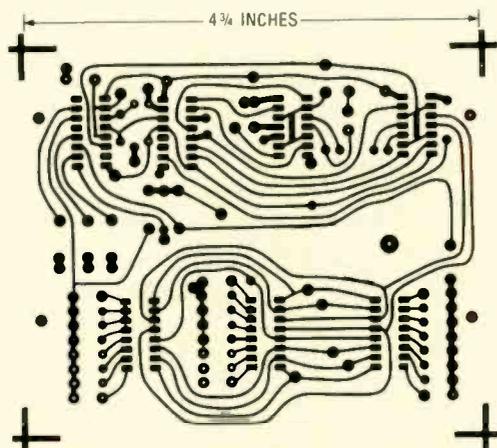


FIG. 6—THE SEQUENCER foil pattern. The component side of the board serves as the control panel.

another accessory POWER jack), and the OUTPUT jack to a MIXER IN jack on PerSyn. The TRIG jack can be connected to the Sequencer or Pulse Generator for Automatic triggering.

For manual triggering, connect a pushbutton switch between the "tips" of a TRIG and POWER jack. Depressing this switch will trigger the unit. To synthesize a realistic snare drum, connect a

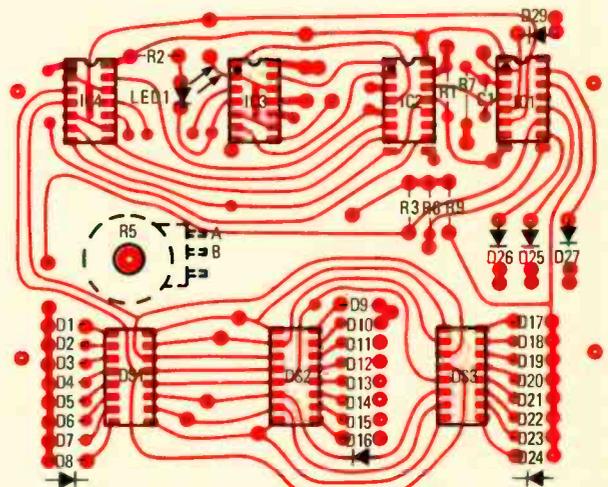


FIG. 7—PARTS LAYOUT for the Sequencer board. Be sure to check the polarity of the many diodes that are used.

TRIG jack on the Snare to a TRIG jack on the PerSyn. Adjust that generator for a midsized Tom-Tom effect. Adjust the DECAY control on the Snare for a short decay. As you tap the appropriate strike surface box, adjust the GEN and Snare volumes until a true snare effect is produced. This approach produces a true representation of a snare drum since it includes the synthesized

SEQUENCER PARTS LIST

Resistors 1/4 watt, 10% or better

R1, R3, R6, R7, R9— 100,000 ohms

R2— 1000 ohms

R4, R8, R10— 10,000 ohms

R5—2.2 megohms, 1/2-watt potentiometer

C1—0.1 μF, disc ceramic

D1-D27—1N4148 or 1N914

LED1—general-purpose LED diode, 1/8 inch

IC1—4090 CMOS hex inverter

IC2—4027 CMOS decade counter

IC3, IC4—CMOS quad 2-input NAND gate

J1-J5—phono jack, 1/8 inch


J6—phono jack, 1/4 inch

S1—SPDT or DPDT slide switch

DS1—DS3—8-circuit DIP switch

Miscellaneous: PC board, enclosure, knob, wire, solder, etc.

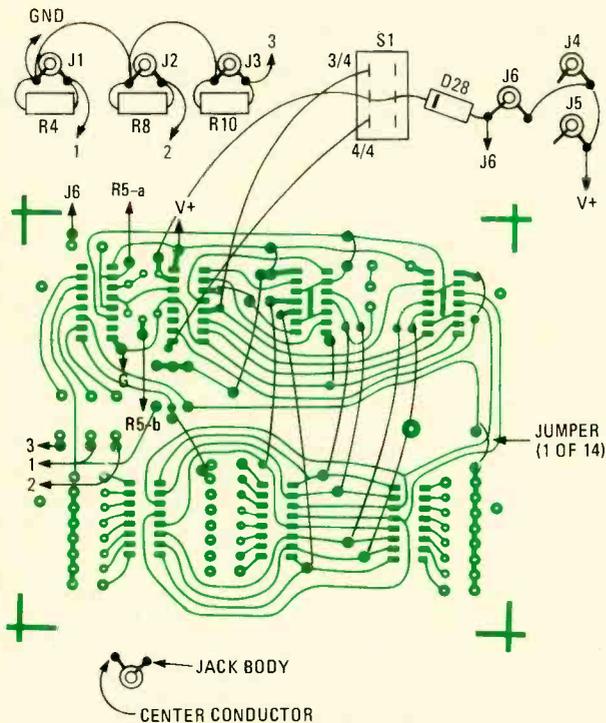Note: The following is available from BNB Kits, RD2, Box 242H, Tennent Road, Englishtown, NJ 07726. PC board (PSQ-PC) \$25.00. Price includes shipping. No COD's. Please allow up to 6 weeks for delivery.



NOTE: ALL WIRE CONNECTIONS ON FOIL SIDE OF BOARD TACK-SOLDERED TO PADS INDICATED

FIG. 8—JUMPERS AND CONNECTIONS that are made to the foil side of the Sequencer board. Leads are tack-soldered to the pads indicated.

sound of the snare drum wires (snare), the drumstick strike as well as the drum itself.

To use the Snare accessory for steam engine or biplane effects, trigger the unit with the Pulse Generator or Sequencer, adjusting frequency (or tempo) as required.

The sequencer accessory

Circuit operation: Referring to the schematic diagram in Fig. 5, we see that IC1-a and IC1-b, R5, R7 and C1 form a variable-frequency oscillator. The oscillator clocks IC2, a decade counter with decoded outputs. The eight NAND gates in IC3 and IC4 allow the clock signal, inverted in IC1c, to pass when the corresponding output from IC2 is high. The NAND gate outputs are combined in the discrete negative-logic OR gates (D1-D8 and R3, D9-D16 and R6, D17-D24 and R9). Each OR gate input is provided through a switch. If the switch is closed, the pulse is transmitted to the OR gate. If the switch is open, no signal is provided. By opening or closing appropriate switches,

TABLE 1

PROGRAM 1—BASIC ROCK:			
1=Bass, 2=Snare, 3=Tom-Tom			
NOTE: 0=Switch Off 1=Switch On			
Switch	Sequencer Channel		
	1	2	3
1	1	0	0
2	1	0	0
3	0	1	0
4	0	0	1
5	1	0	0
6	1	0	0
7	0	1	0
8	0	0	1

PROGRAM 2—BASIC ROCK (Modified)			
1=Bass, 2=Snare, 3=Tom-Tom			
NOTE: Play at twice the Tempo of Basic Rock			
Switch	Sequencer Channel		
	1	2	3
1	1	0	0
2	0	0	0
3	1	0	0
4	0	0	0
5	0	1	0
6	0	0	0
7	0	0	0
8	0	0	1


PROGRAM 3—BONGO ROCK:			
1=Bass, 2=Bongo (High Pitched), 3=Bongo (Medium Pitched)			
Switch	Sequencer Channel		
	1	2	3
1	1	1	0
2	0	1	0
3	0	1	0
4	0	1	0
5	1	0	1
6	0	1	0
7	0	1	0
8	0	1	0

PROGRAM 4—DISCO BEAT:			
1=Bass, 2=Cymbal or Snare			
Switch	Sequencer Channel		
	1	2	3
1	1	0	NOT USED
2	0	1	
3	0	1	
4	0	1	
5	1	0	
6	0	1	
7	0	1	
8	0	1	

Legend: "1=Bass" means connect Sequencer output to a Generator tuned for a Bass Drum effect.

continued on page 96

BUILD THIS

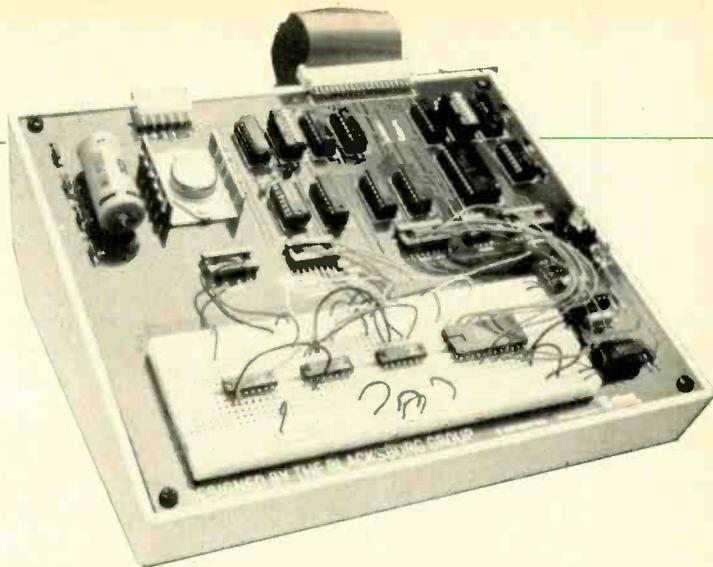

TRS-80 BREADBOARD

Part 2—Build this breadboarding device that serves as an interface between the TRS-80 microcomputer and any circuits that you are designing or prototyping. Its design makes it easy to use.

JON TITUS, CHRIS TITUS, and DAVID LARSEN

LAST MONTH WE DISCUSSED THE NEED FOR AN INTERFACE DEVICE for the TRS-80 and began a discussion of its operation. Now, we'll complete that discussion and present the construction details.

Let's look at an example of how the decoder works. Suppose that the address switches at positions 7-4 were preset to 1011. This would set up the device address decoder so that it would be able to decode addresses of 10110000 through 10111111, although only addresses 1011000 through 10110111 would be available at the decoder's outputs. These address outputs correspond to the decimal addresses 176 through 183. The lowest switch setting at S2 must be in the open or in the D position for the decoder to operate in the device mode.

The decoder's address outputs are available at socket SO5. They are labeled "0," "1," and so on, through "7." The entire section is labeled, ADDRESS. Note that there is a bar over all of the numbers. This is to remind you that the logic zero is the asserted state for decoded addresses. The numbers are sequential, and they should help you in determining which output should be connected to your interface.

In most cases, the actual numbers, 0-7, do not correspond to the actual address values selected at the decoder. In the example just described, the "0" output would be a logic zero when address 176 (decimal) was output by the TRS-80 on address lines A7-A0. Thus, the "0" output would correspond to an input to the decoder of 0000, while the "7" output would correspond to an input of 0111. Of course, the decoder must be enabled by the comparator before the actual decoding can take place. The decoder outputs are shown in Table 3.

Connections for address bus signals A3-A0 (unbuffered) have been provided at pins 8-5, respectively of socket SO4. These signals may be required when you are interfacing some of the advanced programmable IC's, but caution is advised since these signals are not buffered on the breadboard.

Memory addresses may also be decoded on the breadboard, if you wish to use the memory-mapped I/O technique, or if you wish to experiment with other I/O techniques. Two additional digital comparator chips, IC3 and IC4 are provided so that

address bits A15-A8 may be compared with an eight-bit preset HI address. When the address bus is split into bits A15-A8 and A7-A0, the portions are often called the HI address bus, and the LO address bus, respectively.

To decode the entire 16-bit address bus, the mode switch S2 must be placed in the ON or the M position. In the memory mode, the decoder is enabled only when there is a match between the eight preset HI address bits, and the eight HI address bus signals, and when a similar match takes place between the four preset LO address bits, A7-A4, and their respective signals on the address bus. In this way, the decoder can now decode addresses that are within the range of zero to 65,536, but you should be careful not to select addresses that are presently used in your TRS-80 system. Just as problems developed when I/O devices had the same address, similar problems can occur when devices and memory locations have the same address.

If you choose to use the memory-mapped I/O scheme, you will have to use the RD signal in place of the IN signal, and the WR signal in place of the OUT signal. In this case, the PEEK and POKE commands are used in place of the INP and OUT commands. We see little advantage in using the memory-mapped I/O technique instead of the device I/O technique, and we will not discuss it further. The memory address decoder section of the breadboard still needs some further explanation, though.

TABLE 3—ADDRESS DECODER
Connections for address information

PIN (SO5)	LABEL	SN74154 OUTPUT PIN
1, 16	0	1
2, 15	1	2
3, 14	2	3
4, 13	3	4
5, 12	4	5
6, 11	5	6
7, 10	6	7
8, 9	7	8

Since the SN74154 decoder will only be enabled when there is a match between the preset 12 address bits, A15-A4, and the actual address bits on the address bus, the decoder can be used to decode any of the addresses between 00000000 00000000 and 11111111 11111111. These decoded addresses are indicated by a logic zero at the respective output from the decoder. Remember that only the first eight addresses in each block of 16 addresses is available at these outputs.

Let's see how a 16-bit address is decoded. We will assume that the HI address switches have been preset to 10000001, while the four LO address switches have been preset to 1110. In this way, addresses 33,248 through 33,256 would generate logic zero pulses at outputs "0" through "7," at the ADDRESS socket, SO5. If you decide to switch back and forth between the two address decoding modes, be sure that you change the switch setting of the mode control switch so that it matches the mode that you wish to use: M for 16-bit memory address decoding, and D for eight-bit device address decoding.

Two non-inverting bus buffer IC's, IC10 and IC11, are used to buffer the bus as shown in Fig. 9. This means that the TRS-80's eight-bit data bus is available with a fan-out of about 30. Thus, it can directly drive up to 30 standard SN7400-series logic inputs. The bus buffers isolate the breadboarded interface circuits from the TRS-80's main data bus. The eight data bus signals are available at the socket SO3. The information provided in Table 4 shows the various data bus connections.

The bus buffers are always enabled, and the normal mode of operation is for the transfer of information from the TRS-80 to the interface breadboard. This means that you could monitor the activity of the data bus with a logic probe, logic analyzer, or oscilloscope. Output ports are implemented simply by connecting them to the data bus, and controlling them with the proper control signals. Input ports, however, must be implemented so that they can turn the bus buffers in the opposite direction to drive information into the TRS-80. Actually, there are two buffers for each line in the 8216 buffer IC. The EN input at pin 15 is used to select which buffer is to be used, the output buffer or the input buffer, thus directing the flow on the data bus either to, or from, the TRS-80. All input operations must activate the proper set of buffers, so that the information is properly transferred to the TRS-80. Special control circuitry has been included so that this is easily implemented.

The control circuitry on the breadboard is rather simple, consisting mainly of buffers to buffer the six useful control signals that are output by the TRS-80—IN, RD, OUT, WR, RESET and INTAK. This is shown in Fig. 10. The interrupt input, INT, has also been buffered, to protect the computer. Connections to these signals may be made at socket SO2 as noted in Table 5.

You are probably not familiar with the INTAK, INT, or RESET signals. The RESET signal is a short logic zero pulse that may be used to clear circuits, to get them ready for normal operation. The pulse is generated when the TRS-80 is turned on, and when the RESET pushbutton is depressed. The RESET pushbutton is next to the interface connector on the rear of the TRS-80's keyboard enclosure. The interrupt signals, INT and INTAK will not be described further, being beyond our present scope.

The control circuitry can also generate a signal that will switch the 8216 bus buffers into the input mode, so that information may be transmitted to the TRS-80 when an INP command is executed. To handle the input ports properly, the input port's device select signal is used to gate information onto the data bus, and also to control the mode of the 8216 bus buffers. In effect, up to four input port device select pulses may be OR'ed together to place the breadboard's bus buffers in their input mode. This means that the bus buffers are placed in the input mode only when a breadboarded input port has been selected. The INP REQ, (input request) signals are required to be logic zero pulses, and they may be applied to pins 16, 15, 14 or 13 on the socket at IC17. These positions have been labeled "W," "X," "Y," and "Z."

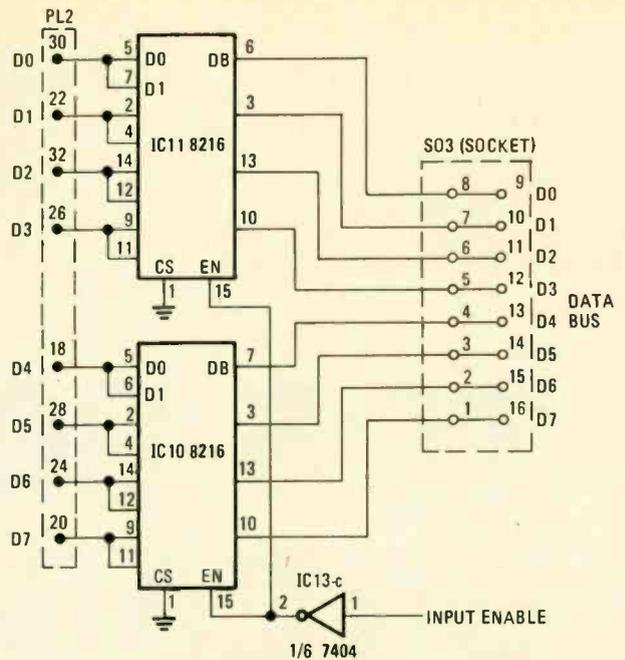


FIG. 9—THE DATA BUS BUFFERS. The EN input controls the flow of information through the 8216 buffers.

TABLE 4—DATA BUS CONNECTIONS	
PIN (IC13)	DATA BUS SIGNAL
1, 16	D7
2, 15	D6
3, 14	D5
4, 13	D4
5, 12	D3
6, 11	D2
7, 10	D1
8, 9	D0

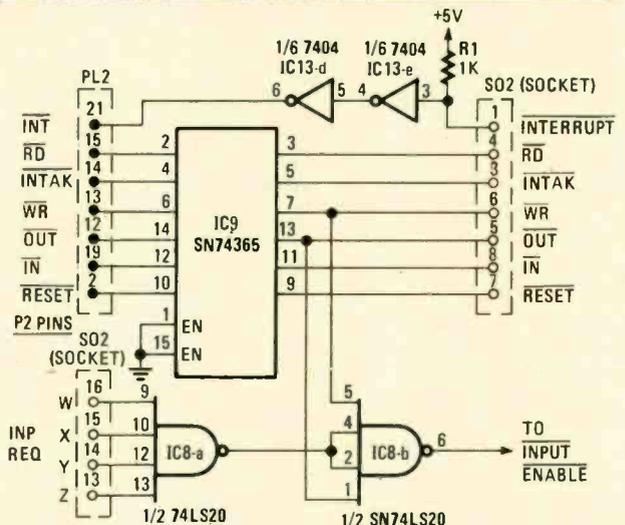


FIG. 10—SCHEMATIC DIAGRAM of the circuit used for control-circuit buffering and for control of the 8216 bus buffers.

TABLE 5—CONTROL SIGNAL CONNECTIONS		
PIN (SO2)	CONTROL SIGNAL	DIRECTION
1	INT	To TRS-80
2	Not Used	—
3	INTAK	From TRS-80
4	RD	From TRS-80
5	OUT	From TRS-80
6	WR	From TRS-80
7	RESET	From TRS-80
8	IN	From TRS-80

PARTS LIST

Resistors 1/4 watt, 5%

R1, R8—1000 ohms
 R2, R3—220 ohms
 R4, R5—47,000 ohms
 R6—3900 ohms
 R7—2200 ohms
 C1—2200 μ F, 16 volts, electrolytic, axial leads
 C2, C4, C5—0.1 μ F, 50 volts, disc ceramic
 C3, C6—1 μ F, 35 volts, tantalum electrolytic
 C7, C8—3.3 μ F, 50 volts, electrolytic, axial leads

Semiconductors

IC1, IC7—16-pin resistor network (eight 1K resistors)
 IC2, IC6—Not used
 IC3—IC5—SN74LS85 quad comparator (do not substitute SN74L85)
 IC8—SN74LS20 dual 4-input NAND gate
 IC9—SN74365 or DM8095 three-state buffer
 IC10, IC11—8216 non-inverting bus buffer (Intel or equal)
 IC12—SN74154 4-line to 16-line decoder
 IC13—SN7404 hex inverter
 IC14—SN74123 or SN74LS123—dual retriggerable one-shot

IC15—LM319N dual comparator (14-pin package)
 IC16—LM309K, voltage regulator, 5 volts, 1 amp.
 D1—D4—1N4001 or equal, 50 PIV, 1-amp, diode
 D5, D6—1N4148 or 1N4154 small-signal diode
 LED1—yellow LED
 LED2—red LED
 LED3—green LED
 S01, S02, S03, S05—High-quality 16-pin DIP socket (Augat 516-AG-10D or equal)
 S04—high-quality 8-pin DIP socket (Augat 508-AG-10D or equal)
 PL1—Molex right-angle 6-pin connector (PN 09-75-1061) optional. Requires 1 mating female housing (PN 09-50-7061) and 6 connector pins (PN 08-50-0106 or 08-50-0108)
 PL2—40-pin right-angle jumper header, AP Products 923875R or equal
 T1—transformer, 12.6 volts, 1 amp
Miscellaneous
 Solderless breadboard socket. E&L Instruments model SK-10, AP Products model Superstrip II, Continental Specialties model EXP-300 or equal.

Cable assembly, 40-pin header on one end and 40-pin card-edge connector on the other—facing the same direction.
The following parts are available from E & L Instruments, Inc., 61 First St., Derby, CT 06418.

Order No. 355-6125—Complete kit including PC board, case and all parts. Does not include interconnect cable. Specify 117V or 230V version. \$139.00.

Order No. 355-6175—Interconnect cable assembly (connects breadboard to TRS-80 computer). \$25.00.

Order No. 355-6100—Assembled 117-volt version. \$185.00.

Order No. 355-6150—Assembled 230-volt version. \$185.00.

Connecticut residents add state and local taxes as applicable.

A pre-drilled and etched PC board is available from Techniques, Inc., 235 Jackson St., Englewood, NJ 07631, for \$24.50 postpaid. New Jersey residents add 5% sales tax.

Copies of the book TRS-80 Interfacing (published by Howard W. Sams and Co.) is available for \$7.95 plus 79¢ for shipping and handling from Group Technology, Ltd., PO Box 87, Check, VA 24072

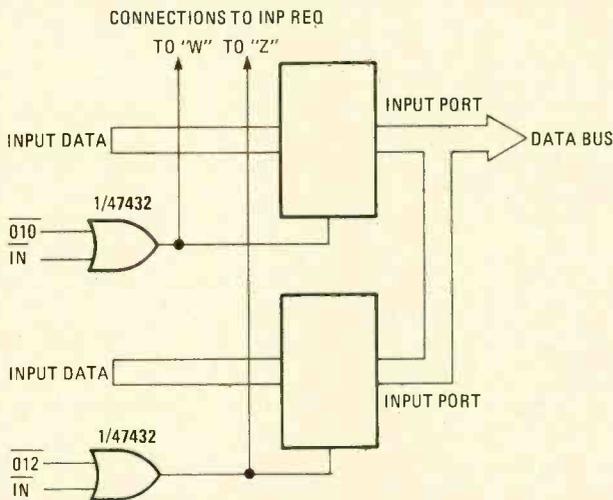


FIG. 11—BLOCK DIAGRAM of two input ports, showing the generation of the required input request (INP REQ) signal for bus control.

Figure 11 shows how these INP REQ signals are generated. Actually, they are the same signal that has been used for the selection and control of the input port, itself. Thus, whenever an input port is constructed, the logic zero device select pulse (\overline{IN} and the device address) is used to control the input mode of the bus buffers. The actual OR'ing of the various INP REQ signals is performed by IC8. The input request signal that is generated by IC8 is further gated with both \overline{OUT} and \overline{WR} . This additional gating provides a safety interlock, so that the bus can not be mistakenly placed in the input mode while the TRS-80 is performing an output, or a memory write operation. The resulting control signal, INPUT REQUEST, BUT NOT OUT OR WR, is what turns the bus drivers around, placing them in the input mode.

Construction

The interface breadboard circuits may be constructed using the wire-wrap technique, but this may mean that the breadboard is somewhat difficult to use. A printed circuit board has been developed, and we recommend its use for this project. The foil

patterns are shown in Figs. 12 and 13, with a parts placement overlay shown in Fig. 14.

In addition to the parts listed for the construction of the TRS-80 interface breadboard, you will need the following to perform various tests on the interface. These are general-purpose parts, and they are readily obtained from many sources. You will find that they are used in many interfaces, since they are not specific to the tests outlined in this article.

1. One solderless breadboard (may be available on your breadboard)
2. Two SN7402 quad NOR gates
3. Three SN74LS373 octal buffer-latches
4. Two DM8095 or SN74365 three-state buffers
5. Eight LED's (red)
6. Jumper wires (No. 24) stripped at both ends

If you are going to use a printed circuit board inspect the board carefully before you start. Pay careful attention to the etched areas, and to the remaining conductor paths, looking for bridging of conductor paths, and for over-etched sections that may cause a conductor to be open. Once you are satisfied that your circuit board is properly etched, you are ready to start the construction of the interface breadboard.

Start your construction with the power supply section. Install and solder power diodes D1—D4, filter capacitor C1 and regulator IC16 if you plan to use the on-board regulator circuit. As mentioned previously, we recommend a small heat sink for the voltage regulator. If you will be using an external +5-volt power supply, these parts are not required, and they should not be installed on the board. Connector PL1 is used to make connections with the power supply, or the external transformer. Pins 1 and 2 are used to connect the on-board power circuit with a 12.6 VAC transformer, while pins 5 and 6 are used for connections to +5 volts and ground, respectively, when an external power supply is used. Two spare pins, 3 and 4, have been provided, so that other voltages may be connected to the POWER socket on the breadboard. These connections may also be made by soldering directly to the PC board.

Once the proper power supply connections have been made, connect power to your system, and check for +5 volts at pins 7 and 10 at socket SO1. You should also be able to detect ground (zero volts) at pins 5 and 12 on the same socket.

With the power supply section of the breadboard operating

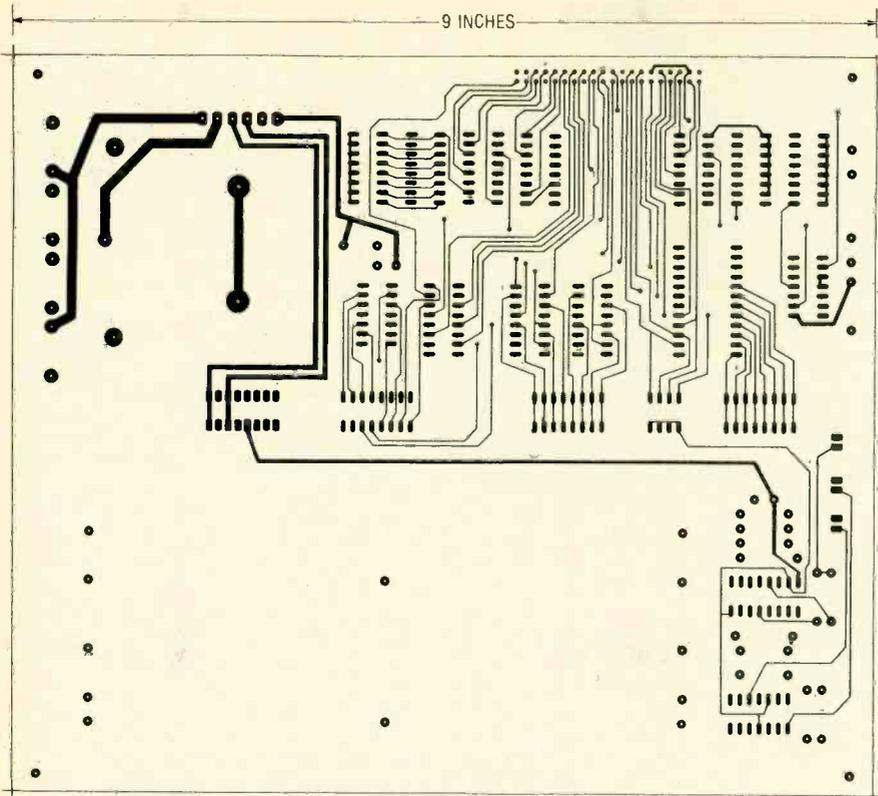


FIG. 12—FOIL PATTERN for the component side of the PC board.

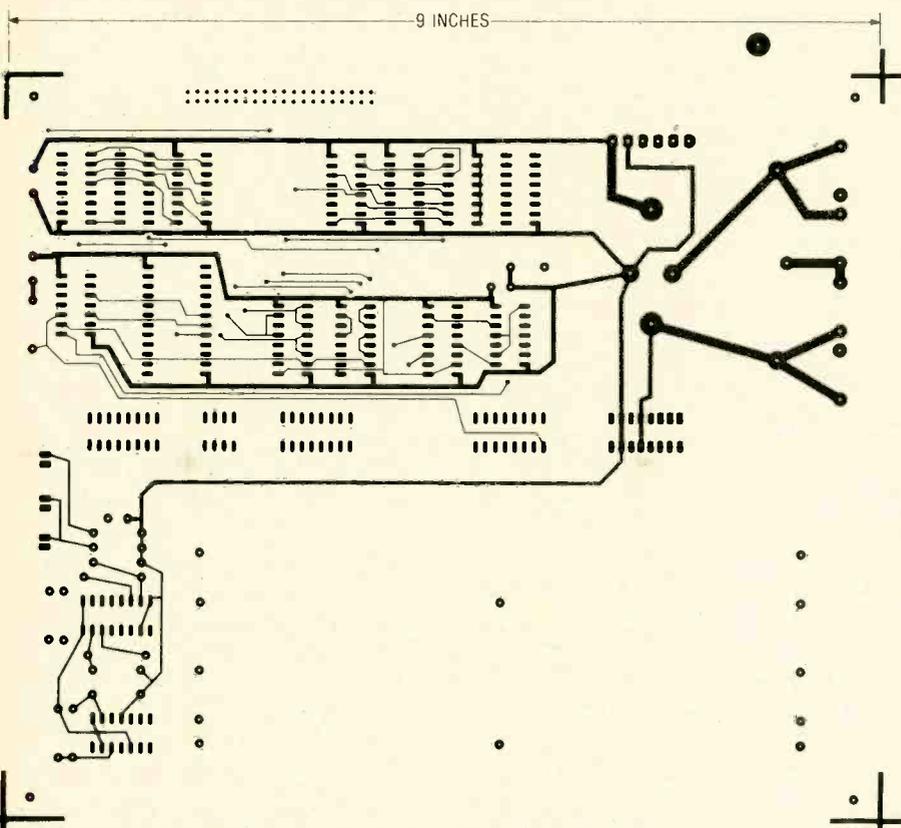


FIG. 13—FOIL PATTERN for the under side of the printed-circuit board.

SO1-SO5. These are the high-quality sockets that are used to make contact with the interfacing signals. Once these have been installed, turn the power on once again and place a jumper wire (8 to 10 inches long) in one of the P inputs of SO4. Connect the other end to the +5-volt pin of SO1. The "1" LED should be lit. Now connect it to the ground pin. The "0" LED should be lit.

The remaining IC's should now be added to the PC board, along with the 40-pin male connector (PL2), and the remaining components. If you are going to substitute individual 1000-ohm 1/4-watt resistors for the two dual in-line resistor packages, IC1 and IC7, you will need 13 individual resistors. These resistors should be soldered between pin 1 and pin 16, and so on, across the space left for the integrated circuits at IC1 and IC7. All eight of the resistors should be soldered in at IC1, while only five are required at IC7.

Do not install the two 8216 bus buffers at this time. They will be added to the circuit later. Pay careful attention to the orientation of the two eight-switch dual in-line packages. The switches' on position should be on the left side. Initially set the switches so that A15-A8 are all logic zero, or on, and so that the switches for A7-A0 are all logic zero, or on. The mode switch should be in the D mode.

To test the control signals, connect the TRS-80 and the interface breadboard with the 40-conductor flat cable. The connectors should be oriented so that they face in the same direction; that is, they should be on the same side of the cable. When connected to the TRS-80, the flat cable should come up from the socket access hatch.

Check out

Apply power to the TRS-80 and to the breadboard, and then enter and run the following short test program:

```
10 A=INP(5):GOTO 10
```

You should be able to monitor pulse activity at the IN signal output at the CONTROL SIGNALS socket. Once you have been able to monitor these pulses, enter and run the following program:

```
10 OUT 7,0:GOTO 10
```

When this program is being run, you should be able to monitor pulse activity at the OUT signal output pin. If you were not able to monitor these pulses, check both the DM8095 (or SN74365) buffer, and the SN74LS123 (or SN74123) monostable. You are testing two things here, the availability of the control signals, and the correct operation of the logic probe's pulse detecting circuit. If the probe is operating properly, you should observe that the "1" LED is lit, while the IN or the OUT pulse also causes the P LED to be lit. This indicates that the normal logic state is logic one, while the pulses are logic zero pulses.

continued on page 94

properly, the logic probe should be constructed next. You may skip this section if you have chosen to use an external probe. Add those parts to the breadboard that are located to the lower right of SO5. These parts include LED1-LED3, D5, R2-R8, C6-C8 and IC14 and IC15.

apply power to your system. None of the logic probe LED's should be lit. If either the "1" or the "0" LED is lit, check the comparator circuit. If the P LED flashes as power is applied, this is acceptable. If it remains lit, test the SN74LS123, or the SN74123, that you have used.

Once this section has been constructed,

Remove the power and install sockets

Super Audio Amplifier



Bridge-type power output configuration lets you use inexpensive "plastic" transistors and a simpler power supply to provide a wide frequency response and a signal-to-noise ratio of 100 dB.

DAN TALBOT

THIS AUDIO POWER AMPLIFIER ELIMINATES the need to AC-couple the loudspeaker, uses only one power supply polarity, and needs only half the power supply voltage of a conventional circuit approach, allowing the use of inexpensive plastic transistors in the output stages! In addition, its frequency response goes "way down" and, since no large output coupling capacitors are used, space is saved on the chassis, especially important for quadriphonic applications.

The circuit, shown in Fig. 1, is basically a differential-output design ("bridge" output circuitry) where *both* sides of the loudspeaker are driven 180° out of phase. This amplifier delivers 60 watts RMS using a 38-volt DC power supply, or 100 watts RMS using a 44-volt supply, into an 8-ohm speaker. Conventional amplifiers drive only one terminal of the loudspeaker and fix the other speaker terminal at ground. This approach requires twice the power supply voltage for the same output power as the circuit described in this article. A conventional circuit would, therefore, require output transistors having 80-volt (or higher) breakdown ratings, and large "safe area" operating regions. Additionally, a conventional circuit approach would require a coupling capacitor to the loudspeaker (usually about 4000 μ F at 50 volts) or would require a two-polarity power supply (in which case the capacitor is not really "saved," but is required for filtering the additional supply).

The amplifier in this article can be built for about \$35.00 per channel, less power supply. Frequency response is flat from 10 Hz to over 30 kHz, and distortion is less than 0.5%.

There are other advantages, also, to a true differential-output power amplifier such as this one. If both halves of the amplifier have the opposite phase-versus-frequency characteristics, as in this independent-twin amplifier approach, then 180° shift across the loudspeaker terminals will be maintained out to very high frequencies. This means that the loudspeaker will see symmetrical slew-rate limiting, a factor important in minimizing the so-called "transient intermodulation distortion" components. Also, in this particular configuration, the constant 180° phase shift across the loudspeaker results in the power output holding up at high frequencies, even though the individual halves of the amplifier twin-configuration are undergoing severe phase-shift relative to the audio input signal. This results in greatly reduced group-delay (time-dispersion) versus frequency compared to many other possible bridge configurations.

All of these technical advantages trans-

late into a highly pleasing amplifier for the serious audiophile who is content with 100 watts. (The sound of an amplifier which clips before the loudspeaker clips is vastly preferable to the sound of a loudspeaker being driven "against the stops.") The 100-watts level is ideal for most standard loudspeaker configurations.

Other variations of the circuit realization of a paraphase-output amplifier are possible, but this approach was settled on as the ultimate for simplicity and performance, using inexpensive components.

Notice the deliberate absence of electronic protection circuits. A fuse in the +V_{cc} (B+) line of the power supply, see Fig. 2, protects the loudspeakers in the event of a transistor short. The absence of electronic protection circuitry ensures that transient "spiking" will not occur as a result of constant-current limit drive to an inductive load.

When an ordinary protection circuit is activated, the amplifier output impedance is suddenly forced to a very high value

R-E TESTS IT

Input sensitivity: 1.7V input, for 60 watts output across 8-ohm load
Frequency response: 8Hz to 62 kHz (-1 dB rolloff points)

8-OHM LOAD

Output at clipping, 20 Hz: 52 Watts
Output at clipping, 20 kHz: 62 watts
Output for 0.5% THD, at 1 kHz: 60 watts

4-OHM LOAD

Output for 0.5% THD, 1 kHz: 72 watts (author claimed 70 watts)
Signal-to-Noise Ratio (re: 60 W output, 8 ohms): 100 dB

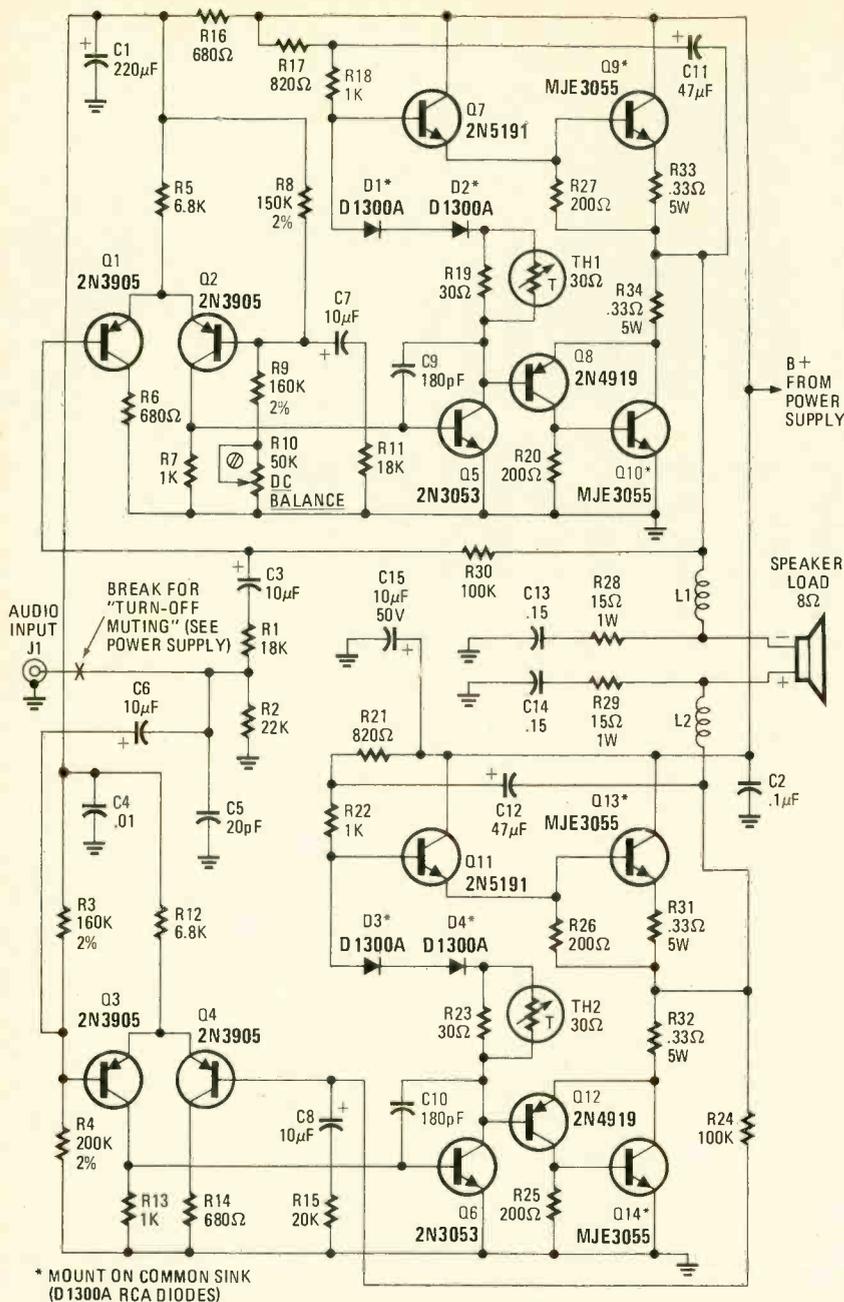


FIG. 1—SCHEMATIC DIAGRAM of the bridge-type amplifier. Output power is determined by the B+ (V_{cc}) voltage from the power supply.

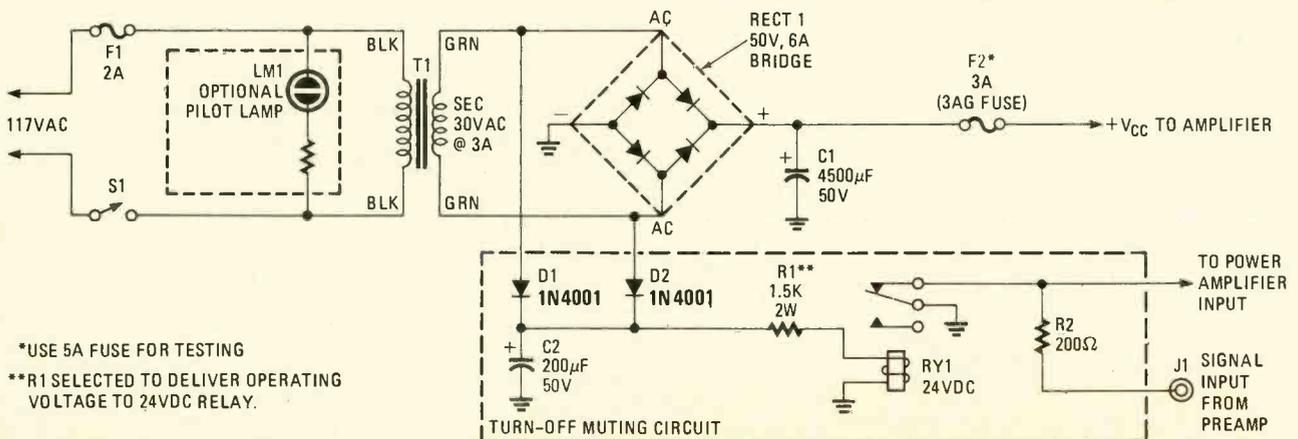


FIG. 2—THE POWER SUPPLY circuit with an optional circuit for turn-off muting. Use two supplies for stereo.

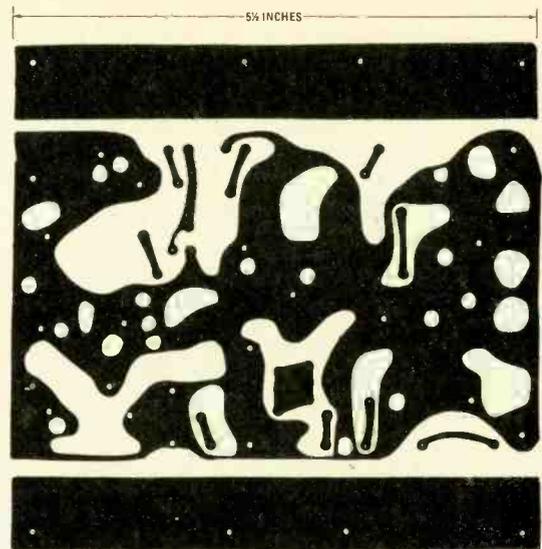


FIG. 3—FOIL PATTERN for the top surface of the double-sided PC board.

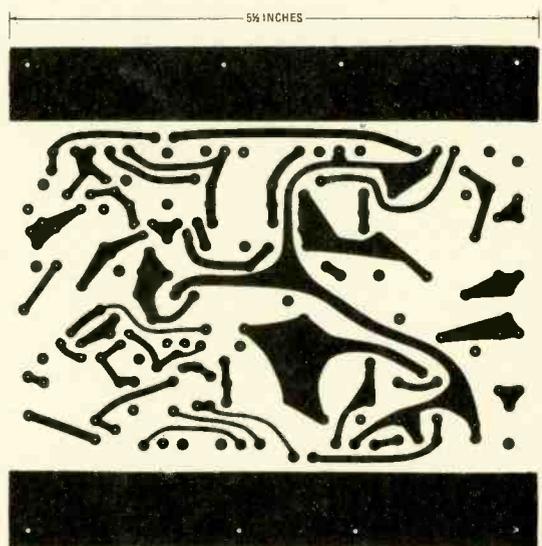


FIG. 4—PATTERN for the foil on the bottom surface of the amplifier board.

(that of a constant-current-mode output). This allows any load inductance to “reverse-kick,” causing spiking in the output waveform. Musical transients can quite frequently activate the current-limiting protective circuitry in many amplifiers. This may possibly explain their inferior sound when driving loudspeakers that are

AMPLIFIER PARTS LIST

Order two of each for stereo

Resistors 1/4 watt, 5% carbon unless otherwise specified

- R1, R11—18,000 ohms
- R2—22,000 ohms
- R3, R9—160,000 ohms, 2% (may be selected from 5% units)
- R4—200,000 ohms, 2% (may be selected from 5% units)
- R5, R12—6800 ohms
- R6, R14, R16—680 ohms
- R7, R13, R18, R22—1000 ohms
- R8—150,000 ohms, 2% (may be selected from 5% units)
- R10—50,000 ohms, trimmer
- R15—20,000 ohms
- R17, R21—820 ohms
- R19, R23—30 ohms
- R24, R30—100,000 ohms
- R20, R25—R27—200 ohms
- R28, R29—15 ohms, 1 watt (may be two 30-ohm, 1/2-watt resistors in parallel)
- R31—R34—0.33 ohm, 5 watts (may be three 1-ohm 20%, 2-watt resistors in parallel)

Capacitors

- C1—220 μ F, 50 volts, electrolytic

- C2—0.1 μ F, 100 volts, Mylar
- C3, C6—C8—10 μ F, 35 volts, electrolytic
- C4—0.01 μ F, 100 volts, ceramic disc
- C5—20 pF, ceramic disc, mica or polypropylene
- C9, C10—180 pF, ceramic disc, mica or polypropylene
- C11, C12—47 μ F, 50 volts, electrolytic
- C13, C14—0.15 μ F, 100 volt Mylar
- C15—10 μ F, 50 volts, electrolytic
- D1—D4—D1300A diode (RCA)
- Q1—Q4—2N3905 or 2N3906
- Q5, Q6—2N3053
- Q7, Q11—2N5191 (do not heat sink)
- Q8, Q12—2N4919 (do not heat sink)
- Q9, Q10, Q13, Q14—MJE3055 (Motorola) or 2N3055 on heat sinks
- TH1, TH2—30 ohms, thermistor (CAL-R No. 1B202 or 1B302, or Keystone RL2004-16.4-59-D1 or equal. See text)
- L1, L2—3 1/2 turns of No. 16 enameled copper wire air-wound to 3/8-inch inside diameter. Turns closer-spaced

Miscellaneous

Heat sinks—two Delco No. 7281352 if using 2N3055's or "Z" brackets made of 1/8-inch-thick aluminum when using the MJE3055.

Four metal cable clamps for 1/4-inch cable. These clamp the compensating diodes to their respective heat sinks.

POWER SUPPLY PARTS LIST

Order two of each for stereo

- R1—1500 ohms, 2 watts (see Note 1 on Fig. 2)
- R2—200 ohms, 1/2 watt
- C1—4500 μ F, 50 volts (Mallory CG452U50D1 or equal)
- C2—200 μ F, 50 volts
- D1, D2—1N4003 or 1N4004 1-amp diode
- T1—power transformer, secondary 30 volts & 3 amps (Stancor P-8614 or equal)
- RY1—SPDT relay, 24 volts DC, 2K-3K ohms
- RECT1—50 PIV, 6 amps full-wave bridge rectifier
- S1—SPST toggle switch
- F1—fuse, 2 amps, slow-blow with holder
- F2—fuse, 3 amps, fast-blow with holder
- LM1—neon pilot lamp assembly, optional (Drake 22k-6073-000-634)
- Line cord, chassis, hardware

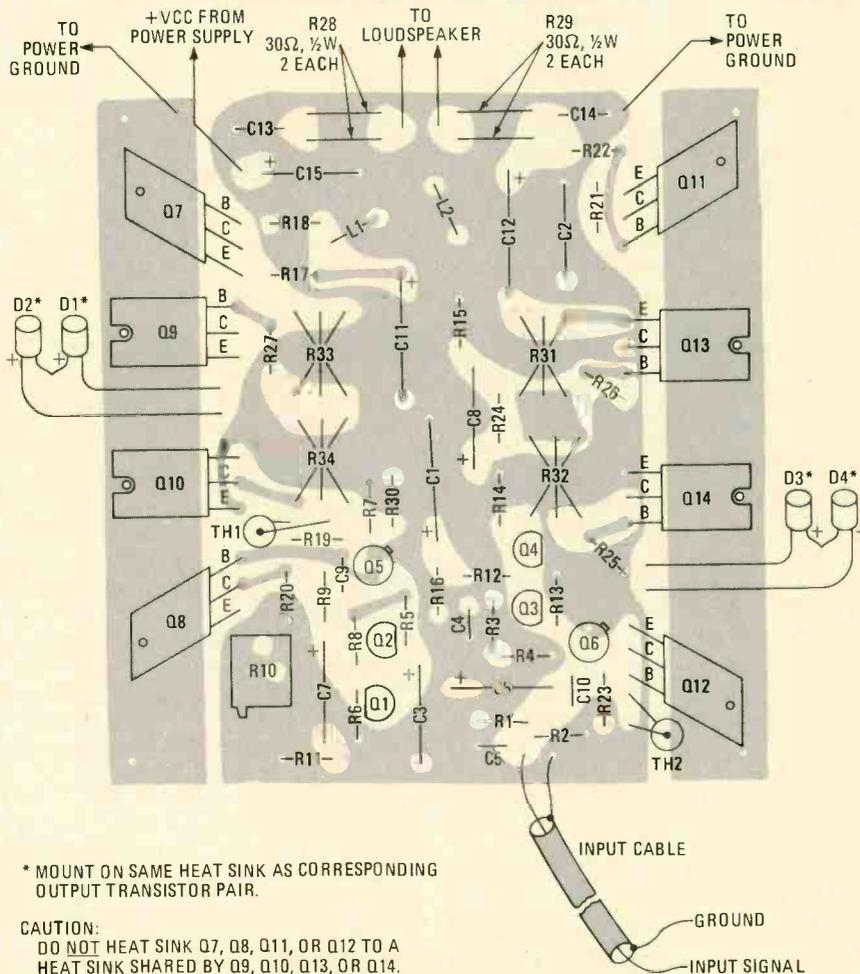


FIG. 5—COMPONENT PLACEMENT DIAGRAM. Some component leads appear to end in "space" because only the top foil is shown.

highly inductive, and may even cause instability (oscillation) on large signals when driving long speaker cables.

How it works

The amplifier basically consists of two halves that are operated in opposite phase

relationships, with negative feedback independently operating around each half.

Transistors Q1, Q2, Q5, Q7, Q8, Q9, and Q10 comprise one complete inverting amplifier with input resistor R1 and feedback resistor R30 establishing a gain of about minus 5.5. Transistors Q3, Q4, Q6,

Q11, Q13, and Q14 comprise one complete noninverting operational power amplifier whose gain is set by R24 and R15 at about plus 5.5.

The outputs of these two independent amplifiers face each side of the speaker load, respectively, through stabilization networks L1, R28, C13; and L2, R29, and C14. Capacitors C9 and C10 roll-off the open-loop response of each amplifier half to prevent oscillation when feedback is applied.

Potentiometer R10 adjusts the output DC quiescent voltage of the amplifier whose output devices drive L1 so that this DC voltage matches that developed by the other amplifier (half) driving L2. This results in a net zero voltage across the speaker load.

Since both amplifiers behave nearly identically, the transient-overload characteristics and AC-recovery effects cancel at the load, yielding very little turn-on "thump." However, on turnoff, the audio may modulate the voltage on the power-supply filter-capacitor(s), causing "motorboating" if the preamplifier output impedance is not low at all times. For this reason, we recommend the anti-thump turn-off muting circuit shown with the power supply in Fig. 2. The circuit is optional; prevention of motorboating on turnoff is accomplished through the use of a shorting relay at the amplifier input or preamplifier output, which activates when the power amplifier is turned off.

Construction

Circuit layout is basically noncritical, but compactness is very important—especially the lead lengths to the output transistors. Keep input lead dress away from amplifier output signal wires! If you

continued on page 98

DOLBY HX

New Noise Reduction

LEONARD FELDMAN

DOLBY LABORATORIES AND, IN PARTICULAR, Dr. Ray Dolby is often credited with providing the technological breakthrough that changed the tape cassette recording format from a low-fidelity voice-dictation medium to the high-fidelity recording format that it has become in recent years. In all fairness, there have been other major advances, such as improved tape formulations (chromium dioxide, cobalt-ferric, ferric-chromium and now the new pure-metal particle tapes), improvements in tape-head designs and improvements in tape transport mechanisms. But most audio experts will agree that the 10 dB of noise reduction above 5 kHz offered by the so-called Dolby-B noise reduction system provided the largest single improvement in cassette tape recording quality when it was introduced into home stereo cassette decks some 10 years ago.

While other noise-reduction techniques have appeared since Dolby B was licensed to cassette deck manufacturers (notably the dbx compander system and, more recently, a system developed by Telefunken of West Germany that is said to provide 20 dB of noise reduction), virtually every manufacturer of cassette decks intended for home use is now a Dolby licensee and incorporates the Dolby B system in all but his least expensive tape decks.

The Dolby B noise-reduction system is two-sided and thus requires that the signal be encoded prior to being recorded and decoded when played back. Quite simply, the Dolby encoding circuit senses the presence and average amplitude of high-frequency energy in signal to be recorded and progressively boosts recording levels when high-frequency content is low in amplitude, literally "lifting" such material up and out of the "noise floor" of the tape. During playback, the converse action takes place, restoring flat frequency response insofar as the program material is concerned, while attenuating tape hiss or other high frequency unwanted noise generated during the re-

cord-play process by 10 dB.

But tape hiss is not the only problem that prevents cassette recordists from enjoying musical reproduction from their tape decks, no matter how costly the machine used. Specifically, it is difficult and often impossible to record program material that is rich in high-frequency energy without suffering either a loss of highs or having to record at lower recording levels, with the attendant reduction in dynamic range and signal-to-noise ratio. The problem is called tape saturation that, at high frequencies, places a limit on cassette performance. To compound the problem, some of today's new program sources—the new direct-to-disc records, as well as the digitally mastered records that are starting to appear on the market—do contain far more high-amplitude, high-frequency energy than did more conventionally made records of the past.

The problem of tape saturation

Tape saturation results primarily from the need to provide a compromise bias level and record equalization characteristic in cassette recorders, no matter what type of tape is used. That compromise has been necessary because recording tape behaves differently with respect to bias at lower frequencies than it does at higher frequencies. As shown in Fig. 1, when bias is increased over the range illustrated, the maximum useful playback level for a given distortion *increases* at lower frequencies while it *decreases* at higher frequencies. In other words, a conflict exists. The bias level that would give best performance in one part of the audio frequency range degrades performance at other frequencies.

A relatively high bias level for low frequencies maximizes useful recording level, minimizes distortion, and even minimizes modulation noise and the effects of drop-outs (because high bias creates a large recording field that magnetizes even those oxide particles that are pushed away from the recording head by tape surface

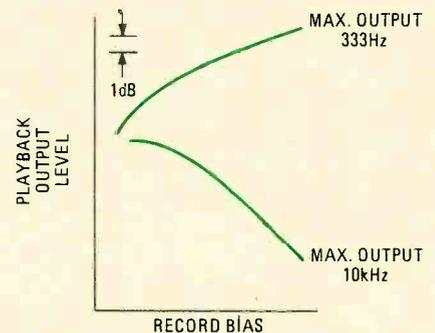


FIG. 1—BIAS REQUIREMENTS for a given brand of recording tape changes with respect to the frequency of the signal being recorded.

irregularities). However, the same large recording field has an erasing effect on high frequencies, particularly at high signal levels. As a result, relatively low bias is desirable for capturing high-level highs on tape.

Makers of cassette decks have dealt with that conflicting bias requirement by compromising on a bias level that favors lower-frequency performance at the expense of high-level high-frequencies. Figure 2 shows typical response curves of a high-quality deck using high-grade cassette tape. The upper curve is record-play response made at a recording level of 0 dB, which, in the case of the particular deck, corresponds to 200 nWb-per-meter. Note the extreme roll-off of response beginning at around 2 kHz. (The frequency scale is logarithmic from 20 Hz to 20 kHz while the vertical scale is a linear 10 dB-per-division in this display.) At a record level of -10 dB, response improves somewhat, but it is only when recordings are made at a level of -20 or -30 dB (lower two traces) that response extends essentially out to the 20 kHz limit.

Favoring high bias (for improved low and mid-frequency performance) requires record equalization with a substantial high-frequency *boost*, that further reduces high-frequency headroom. But even that compromise does not always provide ideal performance at lower fre-

SYSTEM

This new noise-reduction system for cassette tape decks uses continuously varying recording bias level and varying equalization to make possible better mid- and low-frequency response.

quencies, because bias is often not set as high as a further sacrifice in high frequency performance would permit. The result is often a recording system with fixed parameters of bias and equalization

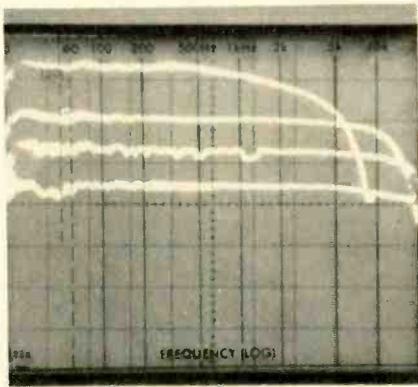


FIG. 2—RESPONSE CURVES of a high quality tape deck using a high grade tape shows the compromise in record bias level.

that may be appropriate for recording some types of program material but is woefully inadequate for other types of music that contain constantly changing levels of high-frequency spectral content. The critical listener finds that he or she cannot record material rich in high-level highs without an audible dulling of the highs. If recording levels are lowered to compensate, there is often an audible sacrifice of signal-to-noise ratio.

Dolby HX system

Now, Dolby Laboratories has come up with a system for dealing with this problem. Introduced in June 1979, the system is called Dolby HX (for *Headroom Extension*). It varies record bias level and record equalization automatically and continuously, in an attempt to optimize both in response to changes in the music's level and high-frequency content.

When the overall signal level is low, or when the program contains primarily low and mid frequencies, a high quiescent bias is used for optimum low-frequency performance.

Since, under these recording signal

conditions, high-level high-frequency response is not important, the quiescent bias with certain tapes can be made higher than the fixed bias of conventional recorders, so that better low and mid-frequency performance might actually be obtained.

When the program material contains high-level, high-frequency energy, bias is automatically lowered to maximize high-frequency output, as shown in Fig. 3. In each of the response plots of Fig. 3, the curve designated "a" is obtained by using the new Dolby HX system; curves "b" are those that would be obtained from the same recorder, using the same tape, but with built-in fixed bias and equalization.

In describing the new system, Dolby admits that lowering the bias in this

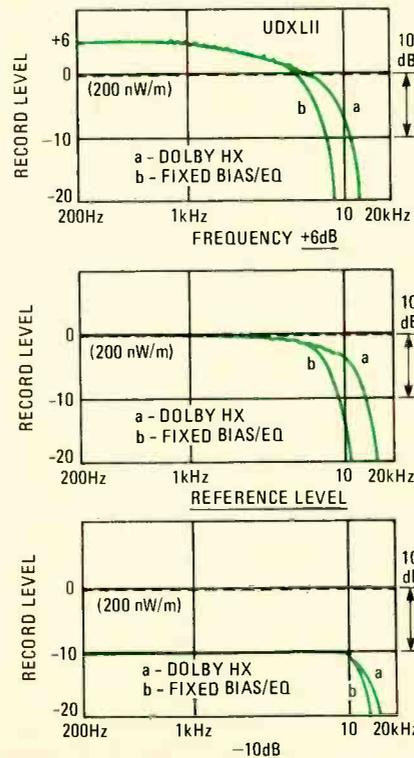


FIG. 3—DOLBY HX record/playback response curves versus a standard recorder with fixed bias and equalization.

manner involves a trade-off: an increase in distortion at lower frequencies. They maintain, however, that the trade-off will be of little or no audible significance because the distortion components generated will be masked by the strong high-frequencies simultaneously present in the music being recorded and reproduced.

The Dolby HX system varies record equalization in addition to bias because tape sensitivity varies with changing bias by different amounts at different frequencies, as illustrated in Fig. 4. A decrease in bias level tends to increase sensitivity at high frequencies by a rather

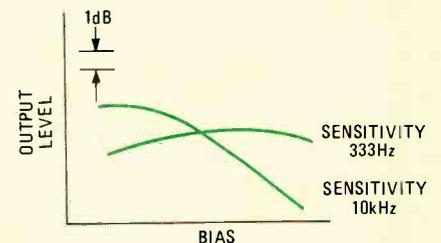


FIG. 4—DOLBY HX SYSTEM varies bias level and record equalization continuously in response to input signal frequency because tape sensitivity also changes with frequency.

substantial amount, while the same decrease in bias lowers sensitivity by a lesser amount in the low to mid-frequency range. The continuous varying of equali-

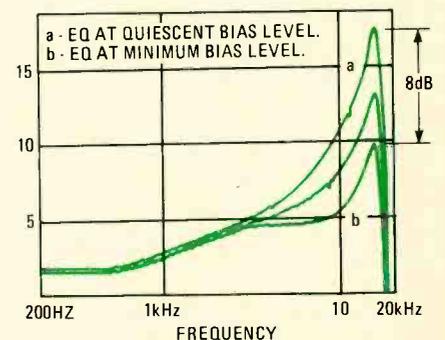


FIG. 5—DOLBY HX SYSTEM varies record equalization so that high-frequency pre-emphasis is reduced when the bias level is reduced resulting in increased headroom at high frequencies.

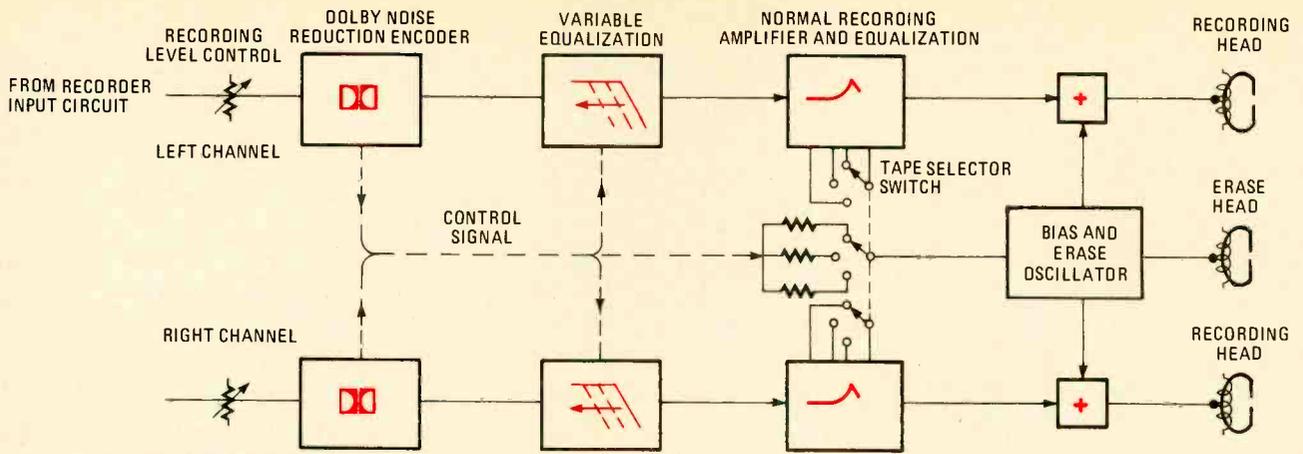


FIG. 6—BLOCK DIAGRAM of Dolby HX system.

zation in the Dolby HX system is therefore necessary for flat playback response with standard playback equalization. Bear in mind that only the *record* equalization is varied in the Dolby HX system, since playback equalization must be maintained at standard values of 120 μ S for standard tapes and 70 μ S for chromium-dioxide, cobalt-ferric and the new metal-particle tapes if compatibility is to be maintained. Dolby maintains that altering record equalization in this manner provides a further benefit beyond the flat frequency response. Since high-frequency pre-emphasis is reduced along with bias level, as shown in Fig. 5, the reduction in treble boost occurs when minimum boost is most desirable for maximum headroom: that is, when the signal contains high-level high frequencies.

How it works

Some control signal is needed to vary the bias and equalization based upon level and high-frequency content of the music being recorded for the Dolby HX system to work properly. But such a control signal already exists in the Dolby B noise reduction system. To reduce noise, that system develops a control signal based upon exactly the same parameters needed to operate the new headroom extension system. (The prior existence of the Dolby noise reduction system, and the fact that this control signal can be used for this further purpose, is what makes the new system practical from a cost point of view.) A block diagram of the Dolby HX Headroom Extension System is shown in Fig. 6, in which we see how the control signal developed by the Dolby noise reduction encoder is now used to vary equalization as well as bias levels on a dynamic basis.

Right now, no cassette recorders are available with the Dolby HX circuits built into them. However, this headroom extension system *will* be made available to all Dolby licensees for incorporation in cassette recorders that already have Dolby B noise reduction, without further royalty or licensing charges. According to Dolby, the parts required for the new

system add only about one-third to the manufacturing cost of the Dolby noise reduction circuits within a recorder.

Since there were no recorders available with the new headroom extension, we attempted to simulate the effect by using a recorder in our lab that provided easy access to bias adjustment and equalization. After several "rehearsals" and, with the aid of an assistant, I was able to plot the curves of Fig. 7 which simulate the headroom improvement that will be gained by Dolby HX system. As the frequencies were slowly swept from low to high, we *decreased* bias and pre-emphasis *manually*, attempting to approximate what the control signal of the

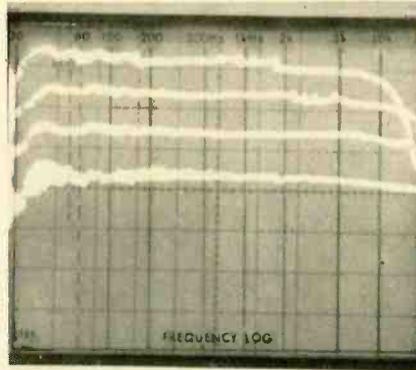


FIG. 7—RESPONSE CURVES of a manually simulated Dolby HX system.

Dolby system would do automatically (and perhaps more smoothly judging by some of the "glitches" in our curves). Though those curves were simulated manually, a comparison of each curve of Fig. 7 with corresponding curves of Fig. 2 reveals just how much improvement in recording headroom is gained.

Total playback compatibility

It is important to understand that since all of the additional processing of record, bias, and equalization with the Dolby HX system occurs during the *recording* process only, no special playback processing over and above standard Dolby noise reduction is required. A cassette of the future, recorded on a machine equipped


with the extra Dolby feature, can be played back on older decks equipped with standard Dolby B noise reduction; only improved high-frequency response should be detected. Dolby claims that in some cases, improved performance at lower frequencies may be noted as well since, as we said earlier, effects of drop-outs and modulation noise are minimized by providing optimum quiescent bias for lower frequency signals. Finally, Dolby suggests that a further reduction in noise may be noticed in some program material, simply because recordists who tend to under-record difficult material—to prevent high frequency tape saturation—can now increase the record level and thereby avoid sacrificing signal-to-noise ratio.

Are there any disadvantages to this new system? In discussing the development with the people from Dolby, I questioned whether their single control signal could be expected to "track" all of the parameters involved, with any degree of accuracy. Dolby correctly pointed out that *any* tape deck is usually calibrated to work best with *one* type of tape (or, one type for each tape selector setting), and that the Dolby HX system will also work best when used with the tape for which it was specifically calibrated by the maker of the tape deck.

It remains to be seen how great the tracking errors will be if other generically similar tapes are used on a machine equipped with the new Dolby HX system. That question notwithstanding, the Dolby HX idea is certainly a brilliant one, and one which should further improve overall cassette deck performance in the future. As Dr. Dolby put it, 10 years or more ago, he turned his attention to lowering the noise-floor in cassette recordings. Now, 10 years later, he has concentrated on the other end of the dynamic range scale of cassette recording and has been able to contribute approximately 10 dB of headroom (at high frequencies) in addition to the 10 dB of noise reduction contributed earlier. The resulting 20 dB of improvement from one man is quite a bit, we would have to agree!

R-E

R.E.A.L. SOUND

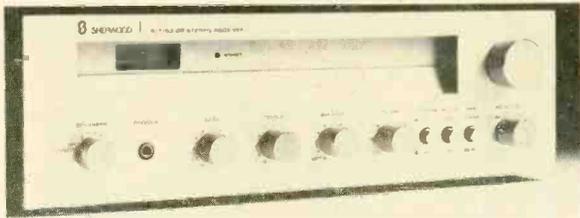

1 CIRCLE 106 ON FREE INFORMATION CARD

SHERWOOD S-7210CP AM/FM Receiver

LEN FELDMAN
CONTRIBUTING HI-FI EDITOR

HERE'S A LITTLE GEM OF A RECEIVER THAT IS actually the lowest-priced and lowest-powered unit manufactured by Sherwood Electronic Laboratories, Inc. (4300 N. California St., Chicago, IL 60618). This company has been around almost since high-fidelity became a buzz-word in a music lover's vocabulary.

What can you get in a stereo receiver for little over \$200? Quite a bit, judging from the model S-7150CP shown in Fig. 1. Certainly some control features are missing (such as an extra or second tape-monitor circuit and perhaps a couple of user-selectable filters), but if your source material is in good condition, you won't need any filtering other than the built-in 6-dB subsonic filter that is included (not visible on the front panel) to reduce rumble from any less-than-perfect turntables you may be using.

But consider what features are included at

this price: The front panel shows a speaker selector switch on the left (for choosing one or two pairs of connected speakers) that also serves as the POWER on/off switch. The mandatory phone jack is next to it, followed by fully detented BASS and TREBLE controls; a channel BALANCE control; the master VOLUME control; LOUDNESS, FM MUTING and TAPE MONITOR pushbutton switches; the program SELECTOR switch; and a large flywheel-coupled tuning knob in the upper right.

The highly visible FM frequency numerals are linearly calibrated with markings at every 200 kHz (one-channel width) with the AM frequencies below them; while above the frequency scales to the left are a stereo indicator light and a single meter that acts as a center-of-channel tuning meter for FM reception and as a signal-strength meter in the AM reception mode.

RADIO-ELECTRONICS AUDIO LAB

R.E.A.L. SOUND

RATES

SHERWOOD
S-7210CP RECEIVER

VERY GOOD

Copyright © Gernsback Publications Inc., 1979

The rear panel of the model S-7150CP contains two rows of color-coded, speaker-connection screw terminals; a single AC convenience outlet; a line fuseholder; a chassis ground terminal; the required tape-input and tape-output jacks; plus four screw terminals to connect an external AM and 75-ohm or 300-ohm FM



2

MANUFACTURER'S PUBLISHED SPECIFICATIONS:

FM TUNER SECTION:

Usable Sensitivity: mono, 1.9 μ V (10.8 dBf). **50-dB Quieting:** mono, 3.5 μ V (16.11 dBf); stereo, 39 μ V (37.1 dBf). **Harmonic Distortion at 1 kHz:** mono, 0.15%; stereo, 0.25%. **S/N Ratio:** mono, 70 dB; stereo, 66 dB. **Capture Ratio:** 1.2 dB. **Selectivity:** 60 dB. **IF Rejection:** 75 dB. **AM Suppression:** 55 dB. **Image Rejection:** 55 dB. **Frequency Response:** 20 Hz to 15 kHz, +1, -2.0 dB. **Muting and Stereo Threshold:** 4 μ V (17.2 dBf). **Stereo Separation:** 40 dB at 1 kHz; 30 dB from 20 Hz to 10 kHz.

AM TUNER SECTION:


Sensitivity: 20 μ V. **Selectivity:** 25 dB. **Frequency Response:** -6 dB at 4 kHz. **Image and IF Rejection:** 40 dB.

AMPLIFIER SECTION:

Power Output: 15 watts-per-channel into 8 ohms, 20 Hz to 20 kHz (25 watts at 1 kHz into 4 ohms). **Rated Harmonic Distortion:** 0.2%. **IM Distortion:** 0.2%. **Damping Factor:** 20 at 8 ohms. **Input Sensitivity for Rated Output:** phono, 2.5 mV; high level, 160 mV. **Photo Overload:** 140 mV at 1 kHz; 680 mV at 10 kHz. **S/N Ratio (Phono, Referenced to 10-mV Input, "A"-Weighted):** 91 dB, (77 dB unweighted); high level, 85 dB unweighted (95 dB weighted). **Frequency Response:** phono, RIAA \pm 0.5 dB; high level, \pm 0.5 dB, from 20 Hz to 20 kHz. **Bass and Treble Tone Control Range:** \pm 10 dB at 50 Hz and 15 kHz.

GENERAL SPECIFICATIONS:

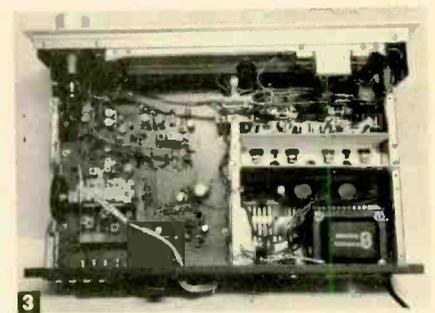Power Requirements: 115 to 126 VAC, 50 to 60 Hz, 20 to 100 watts. **Dimensions:** 16 $\frac{1}{8}$ " W \times 5 $\frac{1}{8}$ " H \times 12 $\frac{1}{2}$ " D. **Weight (Shipping):** 20 lbs. **Suggested Retail Price:** \$225.



3

antennas. A pivotable ferrite-bar AM loopstick antenna completes the rear-panel layout (See Fig. 2).

Circuit highlights

Figure 3 shows the internal layout of the chassis. Two major PC boards contain most of the receiver's circuitry: a tuner PC board and an amplifier module. The FM front end uses a three-gang tuning capacitor, with an FET used as an RF amplifier stage. Phase-linear ceramic filters are used in the IF section, with much of the active circuitry (including a wideband quadrature detector circuit) contained in a single IC preceded by a discrete bipolar transistor


stage. Multiplex decoding circuitry incorporates a phase-locked-loop IC and is followed by separate discrete amplifiers for each channel plus the required de-emphasis and filtering networks.

The phono preamplifier/equalizers use a three-transistor circuit with negative feedback used for RIAA equalization. The tone-control amplifier is handled by the familiar Baxandall negative-feedback circuit. The power-amplifier section includes a differential-amplifier input stage and the now-familiar, direct-coupled complementary-symmetry NPN-PNP output stage. Two-ampere fuses are built into the output lines to protect the amplifier against speaker shorts. Power-output stages are powered from filtered ± 23 -volt DC supplies while a fully electronically regulated 14-volt supply takes care of the tuner and low-level amplifier circuits. Dual-polarity voltages are used to power the phono preamplifier/equalizer sections of the receiver.

Tuner measurements

Table 1 summarizes measurements made for the FM tuner section. Note that both for mono and stereo FM performance, the signal-to-noise (S/N) ratio obtainable with strong (65-dBf) signals is far better than that claimed by the manufacturer. We must point out, however, that these signal-to-noise measurements were made in accordance with IHF Tuner Measurement Standards, in which a 200-Hz to 15-kHz bandpass filter is included in the test procedure. In the case of mono measurements, using this bandpass filter made very little difference.

In the case of stereo measurements, however, without using the filter we would have read an erroneous S/N ratio, which would have been a result of the presence of a fair amount of subcarrier signal (19-kHz, 38kHz, and harmonics) that could not be totally filtered out. Of course, this ultrasonic signal is not audible to a listener and in no way affects tuner performance. We have noted its presence, however, only as it might affect cassette tape recordings made from off-the-air stereo FM programs (causing possible beats and the miscalibration of any Dolby noise-reduction system on the recorder) unless your deck is equipped with a multiplex filter. Many modern cassette decks have such a circuit (a switch is included on their front panels), and we advise prospective purchasers of the *model S-7150CP* choose

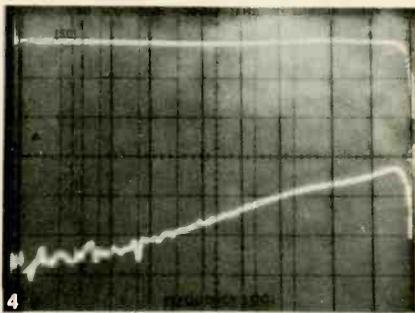

such a cassette deck to use with this receiver.

Figure 4 is a spectrum analysis of FM frequency response (shown by the upper trace) and stereo FM channel separation (the lower trace). The scale used is 10 dB-per-vertical-division; response is extremely uniform. It is flat all the way out to 15 kHz,—the upper-frequency limit of FM broadcasting.


TABLE 1 RADIO-ELECTRONICS PRODUCT TEST REPORT

Manufacturer: Sherwood Laboratories

Model: S-7150CP

FM PERFORMANCE MEASUREMENTS


SENSITIVITY, NOISE AND FREEDOM FROM INTERFERENCE	R-E	R-E
	Measurement	Evaluation
IHF Sensitivity, mono: (μ V) (dBf)	2.0 (11.2)	Good
Sensitivity, Stereo (μ V) (dBf)	5.0 (19.2)	Excellent
50-dB quieting signal, mono (μ V) (dBf)	3.0 (14.7)	Excellent
50-dB quieting signal, stereo (μ V) (dBf)	40 (37.2)	Fair
Maximum S/N ratio, mono (dB)	75	Excellent
Maximum S/N ratio, stereo (dB)	70	Excellent
Capture ratio (dB)	1.2	Very good
AM Suppression (dB)	56	Very good
Image rejection (dB)	57	Fair
IF rejection (dB)	75	Good
Spurious rejection (dB)	82	Very good
Alternate channel selectivity (dB)	63	Good
FIDELITY AND DISTORTION MEASUREMENTS		
Frequency response, 50 Hz to 15 kHz (\pm dB)	2.0	Fair
Harmonic distortion, 1 kHz, mono (%)	0.12	Excellent
Harmonic distortion, 1 kHz, stereo (%)	0.075	Superb
Harmonic distortion, 100 Hz, mono (%)	0.13	Excellent
Harmonic distortion, 100 Hz, stereo (%)	0.13	Good
Harmonic distortion, 6 kHz, mono (%)	0.18	Very good
Harmonic distortion, 6 kHz, stereo (%)	0.15	Excellent
Distortion at 50-dB quieting, mono (%)	0.5	Good
Distortion at 50-dB quieting, stereo (%)	0.28	Excellent
STEREO PERFORMANCE MEASUREMENTS		
Stereo threshold (μ V) (dBf)	4.0 (17.2)	Excellent
Separation, 1 kHz (dB)	45	Excellent
Separation, 100 Hz (dB)	49	Superb
Separation, 10 kHz (dB)	33	Good
MISCELLANEOUS MEASUREMENTS		
Muting threshold (μ V) (dBf)	3.5 (16.1)	Very good
Dial calibration accuracy (\pm kHz at MHz)	-200, 98/108	Fair
EVALUATION OF CONTROLS, DESIGN, CONSTRUCTION		
Control layout		Very good
Ease of tuning		Very good
Accuracy of meters or other tuning aids		Excellent
Usefulness of other controls		Good
Construction and internal layout		Very good
Ease of servicing		Good
Evaluation of extra features, if any		Good
OVERALL FM PERFORMANCE RATING		Very good

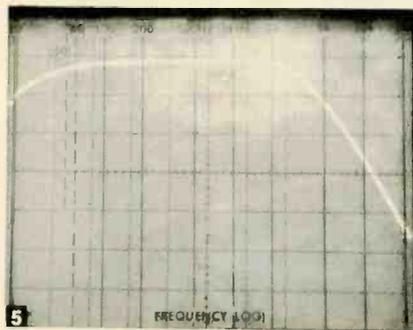

Sherwood is one of the few manufacturers that is honest enough to quote AM frequency response. In the case of the *model S-7150CP*, the specification states that response extends out to 4 kHz for the -6-dB rolloff point, and this is exactly what we measured, as shown in Fig. 5. This response measurement may not seem like much to a dyed-in-the-wool audiophile, but compared with some AM tuners in much more expensive stereo receivers (many of which begin to roll off at 2.0 kHz or 2.5 kHz), it really isn't bad at all, and response is quite flat over its useful frequency range. The improvement was also audible in our subsequent listening tests, during which we always check out AM fidelity.


Amplifier measurements

The amplifier of the *model S-7150CP* delivered considerably more power than its rated 15 watts-per-channel into 8 ohms at mid-frequencies and at the high-frequency extremes. Even at 20 Hz, its power output reached 18 watts-per-channel before the rated distortion of 0.2% was observed. In examining the measurements shown in Table 2, note the extremely wide frequency range (power bandwidth) over which the amplifier is able to deliver its rated output at or below rated distortion. At rated power output, mid-frequency test signals were reproduced at distortion levels that were well below the 0.2% value specified, and intermodulation distortion was even a bit lower than the total harmonic distortion.

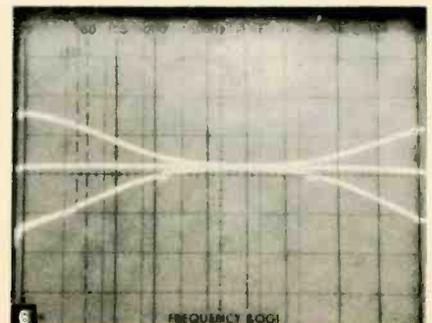

When you examine S/N and sensitivity figures in Table 2—Amplifier Performance Measurements—you will not be able to compare our results directly with the manufacturer's specifications. Sherwood has not yet adopted the 1978 Amplifier Measurement Standards at the time this report was written.

Figure 6 shows the total bass and treble control range. Note that the important mid-frequencies (from around 200 Hz to 2.5 kHz) are totally unaffected by either the bass or treble

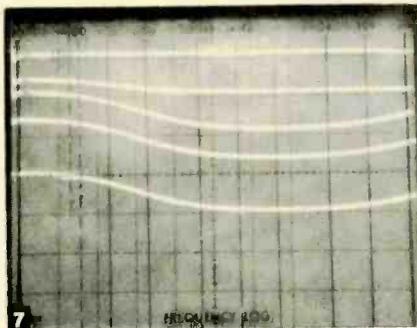

controls—a design approach of which we heartily approve. Sherwood has also kept the maximum boost of these controls within reason, another wise approach in view of the receiver's rather limited power-output.

The action of the loudness-compensation circuitry, shown in Fig. 7, is typical of this type of circuit, with most of the emphasis at low listening levels applied to the bass end and only a very moderate amount of treble boost introduced at lower levels.

Summary

Table 3 contains our overall product analysis as well as our summary comments concerning the audible performance and design of this receiver. We were well impressed with the model S-7150CP, especially in view of its welcome low price and no-compromise approach to circuitry and sonic quality. It's nice to discover that some audio-component manufacturers have not overlooked the less-affluent sound buffs among us.

R-E

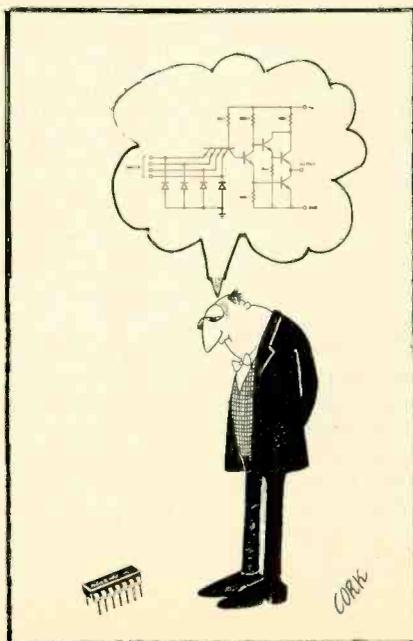


TABLE 2
RADIO-ELECTRONICS PRODUCT TEST REPORT

Manufacturer: Sherwood Laboratories

Model: S-7150CP

AMPLIFIER PERFORMANCE MEASUREMENTS

	R-E Measurement	R-E Evaluation
POWER OUTPUT CAPABILITY		
RMS power/channel, 8-ohms, 1 kHz (watts)	25.2	Excellent
RMS power/channel, 8-ohms, 20 Hz (watts)	18.0	Very good
RMS power/channel, 8-ohms, 20 kHz (watts)	24.5	Excellent
RMS power/channel, 4-ohms, 1 kHz (watts)	33.3	Excellent
RMS power/channel, 4-ohms, 20 Hz (watts)	22.1	Good
RMS power/channel, 4-ohms, 20 kHz (watts)	33.0	Excellent
Frequency limits for rated output (Hz-kHz)	10-65	Superb
Dynamic headroom (dB)	0.63	Not rated
DISTORTION MEASUREMENTS		
Harmonic distortion at rated output, 1 kHz (%)	0.065	Excellent
Intermodulation distortion, rated output (%)	0.050	Excellent
Harmonic distortion at 1-watt output, 1 kHz (%)	0.024	Excellent
Intermodulation distortion at 1-watt output (%)	0.022	Excellent
DAMPING FACTOR AT 8 OHMS, 50 Hz		
	36	Good
PHONO PREAMPLIFIER MEASUREMENTS		
Frequency response (RIAA ± dB)	0.5	Very good
Maximum input before overload (mV)	150	Very good
Hum/noise, "A"-weighted, referenced to 1-watt or 0.5-volt output, for 5-mV input (dB)	82	Excellent
HIGH LEVEL INPUT MEASUREMENTS		
Frequency response (Hz-kHz, ± dB)	8-28, 1.0	Very good
Hum/noise, "A"-wt'd, referenced to 0.5- or 1-watt output, 0.5-volt input (dB)	86	Excellent
Residual noise, "A"-wt'd, minimum volume, referenced to 1-watt output (dB)	88	Good
TONAL COMPENSATION MEASUREMENTS		
Action of bass and treble controls	See Fig. 7	Excellent
Action of secondary tone controls		N/A
Action of high- and low-cut filters		N/A
COMPONENT MATCHING MEASUREMENTS		
Input sensitivity, phono 1/phono 2, referenced to 1-watt or 0.5-volt output (mV)	0.65	
Input sensitivity, high level, referenced to 1-watt or 0.5-volt output (mV)	40	
Output level, tape outputs, at rated output (mV)	154	
Output level, headphone jack, at rated output (mV or mW)	12 mW/8 ohms	
EVALUATION OF CONTROLS, CONSTRUCTION AND DESIGN		
Adequacy of program source and monitor switching		Fair
Adequacy of input facilities		Good
Front-panel layout		Very good
Action of controls and switches		Very good
Design and construction		Excellent
Ease of servicing		Very good
OVERALL AMPLIFIER PERFORMANCE RATING		
		Very good

TABLE 3
OVERALL PRODUCT ANALYSIS

Retail price	\$225
Price category	Low
Price/performance ratio	Excellent
Styling and appearance	Very good
Sound quality	Very good
Mechanical performance	Very good

Comments: In the past, we have tested high-priced receivers whose manufacturers have "guaranteed" the consumer that the published specifications would be met or exceeded. Some even include their own hand-written data based upon internally conducted measurements and quality control of each unit. Usually, though, once you get down to the level of a low-powered, low-cost receiver, such extra quality control seems to vanish. Not so in the case of the model S-7150CP. Although it is extremely modest in power and price, Sherwood's Certified Performance program (a program of total quality control) applies to this unit just as it does to the company's higher-powered receivers and separate components. We believe this is all to the good since we always sympathized with the budget-limited hi-fi consumer who requires only moderate power levels but wants high-quality in every other aspect. Such buyers are increasing in number, now that there is a trend towards high-efficiency speakers that don't require a lot of power to deliver realistic sound pressure levels.

When the receiver was listened to with any of the recently designed vented-port speakers, it performed admirably, and (as you can confirm by comparing published specifications with the results in Table 2) every single specification was either met or exceeded, in some cases by a wide margin. In our opinion, the model S-7150CP makes it possible to assemble a good-sounding stereo system for well under \$500—rather amazing in view of the inflationary trends that have caused every other consumer product to rise in the last few years. If you plan to equip your home with stereo components and your funds are limited, this receiver should definitely be auditioned.

HOW TO

CUSTOMIZE YOUR PC BOARDS

The dimensions and shape of many finished PC boards are such that the board won't fit into a case or cabinet you want to use. Read how one experimenter solves the problem.

EARL "DOC" SAVAGE, K4SDS
HOBBY EDITOR

THE TWO PIECES OF EQUIPMENT SHOWN IN Fig. 1 provide outstanding performance and have a fairly nice appearance. On that basis, you would probably assume that they were custom made. Well, in a way they were—but those instruments contain pre-designed circuit boards that would not fit into either cabinet. This is the story of how they got in there.

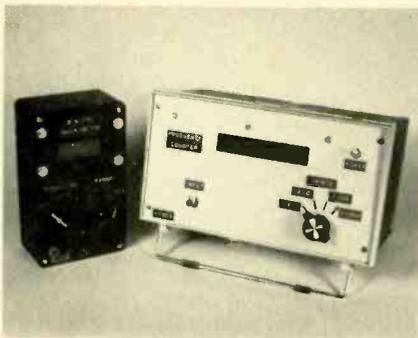


FIG. 1—PREFABRICATED PC BOARDS were used in building these two test instruments. The PC boards were "repackaged" so that they would fit inside the cabinets.

The problem of size can arise when you build on a surplus or prefabricated PC board; you must find a box of just the right size. You may have to settle for one that is too big, or the wrong shape, unless you know how to squeeze a board into a smaller box.

An even worse problem is to have a piece of equipment already on a board that won't fit into anything reasonable. Did you ever try to put a 6 × 7 inch PC board into a 6 × 3½ × 2½ inch box? Or would you rather put it into a box that is 6 × 7 by 1 inch deep—or worse, one that is 5 inches deep? In the first case, something has to give. In the second, you have a piece of equipment with a very strange and awkward shape or a lot of wasted space inside.

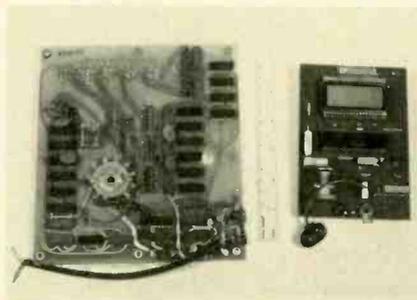


FIG. 2—TWO TYPICAL PC boards with problem shapes. They won't fit into standard cabinets.

Two such problems can be seen in Fig. 2. The board on the left is a complete frequency counter less a 5-volt power supply (as you will see later, the digits are mounted on the other side of the board). That particular board is a sub-assembly from a big piece of surplus gear. It works excellently but it should be put into a cabinet of some sort.

The board on the right is an Intersil digital panel meter with a liquid crystal display. It is a sweet little 200.0 milli-volt meter that just cries out for some accessory input circuits and a cabinet to be most useful. But everything you see in Fig. 3 simply won't fit into the desired box "as is".

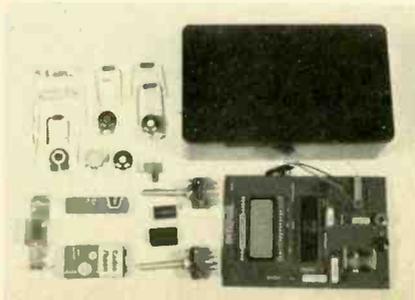


FIG. 3—MULTIMETER BOARD and components simply won't fit into intended cabinet.



FIG. 4—STRAIGHT CUTS in PC board is made with modeling saw.

Those really are problems because enclosing the PC boards "as is" would result in awkward shapes and much wasted space. In addition, the digital readouts would be recessed way behind the panel—and who wants to look down tunnels all the time? Even locating the controls on the side of the cabinet (ugh!) won't help much.

Possible solutions

Of course, there are several ways to solve the problem. First, the boards might be used just as they are, without cabinets. But that would probably result in physical and electronic damage.

A second possibility is to put them into odd-shaped boxes. Probable result: being unable to find such a cabinet, you would have to spend a lot of time making it.

A third way would be to remove the parts from the board and make new ones of different shapes. The probable result would be some parts damaged in removal.

Those three "solutions" all have much the same disadvantages—unsafe, inconvenient, unaesthetic, and/or a lot of work. They *might* do the job but there is an

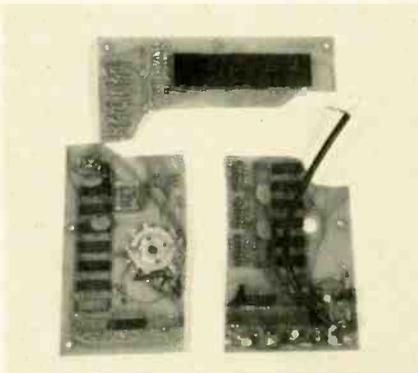


FIG. 5—CURVED CUTS are made with a coping saw.

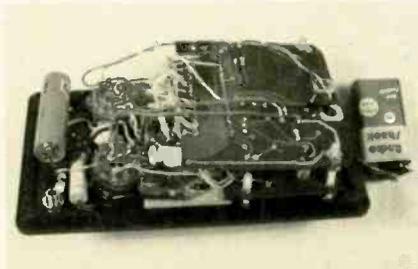


FIG. 6—MULTIMETER PC BOARD, after being cut, fits nicely into cabinet along with input circuitry and front panel controls.

easier more preferable way.

Cut the board up into pieces of manageable size to fit the cabinet of your choice. That's right: Saw the board into smaller pieces; then all you have to do is put the boards in layers, or however you want them, and wire them together.

How to do it

Let's see how it was done with those two boards; you can use the same techniques with your problems. Here are the steps in the process.

First, study the board and the available cabinet size(s) to determine the best place(s) to cut. Give attention to both sides of the board. Obviously, the fewer copper traces or runs you cut, the less wiring you will have to do later. Then, too, there may be sub-circuits that would be better undisturbed—as in the case of the counter board. Here, the cuts were planned to leave the crystal oscillator and divider chain in one piece. At times, you'll have to compromise, but don't start hacking away until you think it through. Usually the cuts will *not* be straight and square.

Next, saw the board according to your plan. Go slow and easy and you won't tear anything up. If the board is small, a very fine-tooth modeler's saw works well. An Xacto saw was used on the Intersil board (Fig. 4). The size of the counter board and the needed shapes made another type of saw necessary—in that case, a fine

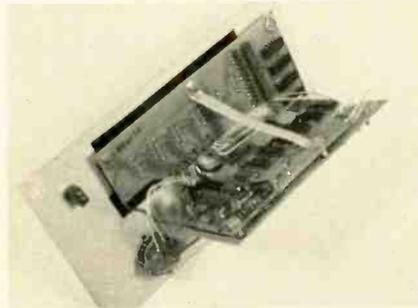


FIG. 7—REPACKAGED COUNTER PC board also fits nicely in its intended cabinet.

blade in a regular coping saw (Fig. 5).

After sawing, clean up the new edges with a file. This will keep debris from coming loose later. Even more important: It cleans up the raw edges of the runs and removes possible shorts.

If there is a lot of wiring to do—and especially if the board is double-sided—write some identifying letters/numbers on the runs that were cut. With the board back in its original shape, and flat on the workbench, put the same number or letter beside a trace on each side of the cut. Later, all you have to do is wire A to A and 3 to 3 and so on. Take note: It is easy to get confused when one piece of a board is reversed and inverted in relation to another piece!

Use a variety of wire colors as a further help in preventing miswiring. Frequently it will not be possible to solder both ends of a wire, one after another. When you are trying to attach the free ends of a dozen wires to one board, it is much easier to get them right if all are not the same color.

The soldering iron *must* have a very small tip or you will simply make a mess. To help protect MOS devices from static charges, the tip should be grounded or at least isolated from the AC line. The Wahl Iso-Tip No. 7545 is a good choice on both counts.

On fine, narrow runs it is a good idea *not* to solder a wire right at the cut edge, since the run could be pulled from the board. In such cases, work back $\frac{3}{8}$ inch or more from the edge.

Soldering wires to the board runs can be tedious unless you use the "reflow" technique which requires only *two* hands. Here is the procedure found most satisfactory:

- Heat the run at the intended point of attachment and deposit a small amount of solder there. To avoid damage, do that quickly with a *hot* iron.
- Strip and tin about $\frac{1}{8}$ inch of the end of a *solid* wire (stranded wire tends to spread too much).
- Bend the end of the wire slightly so it will lie flat on the run.

d. Lay the tinned wire *flat* on the re-soldered portion of the run and touch the top of the wire briefly with a hot iron. This causes the solder to "reflow" and make a good connection.

e. Examine the area of the new joint carefully with a magnifying lens to be sure that no solder has flowed over to an adjacent run.

Many times a run will be short and you can as easily solder the wire to a component lead sticking through a pad. Given a choice, wire to a lead and pad instead of to a run. Just make a small hook in the end of the wire and use the reflow technique.

When the board pieces have been wired and mounted, the results may look like those in Figs. 6 and 7. Those will win no prizes for beauty but they work *very* well.

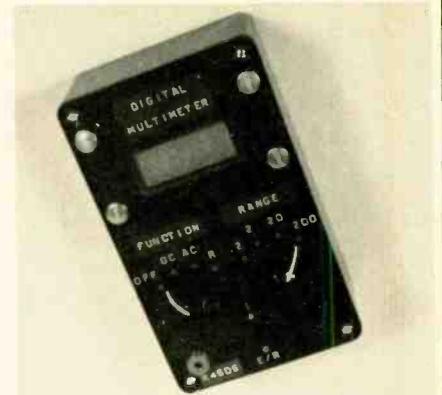


FIG. 8—COMPLETED DIGITAL MULTIMETER.



FIG. 9—COMPLETED FREQUENCY COUNTER.

Conclusion

There is no way the Intersil-based multimeter shown in Fig. 8 could have been packaged without complete rewiring or re-boarding short of cutting the original board. The same is true of the frequency counter in the Radio Shack cabinet shown in Fig. 9.

On the basis of function and appearance, the repackaging effort was worthwhile. Those instruments would find a place in any workshop. Yours can look equally as good; get out your saw and repack your loose boards.

Audio Oscillator Applications

The audio oscillator/generator is one of the oldest electronic test instruments. Its specifications and features have been greatly up-graded so it is suited for a myriad of applications. This article tells how the audio generator is used in nine important test procedures.

CHARLES GILMORE



HEATHKIT MODEL IG-5218

IT IS DIFFICULT TO ENUMERATE ALL THE applications for an audio oscillator. Briefly, the instrument can be used in any situation requiring a source of relatively pure sinewaves within the frequency range covered. A large majority of applications are found in audio measurements because of the high degree of concentration on reproduction fidelity. However, there are enough applications for a good audio oscillator that a general laboratory or service shop should place it on the priority list for low-frequency sources (right after a function generator). Of course, if the shop specializes in audio measurements and repairs, the audio oscillator is a *must*.

Total harmonic distortion

The THD measurement determines the amount of harmonic energy added to the output signal of a device by the device itself. With the audio amplifier—or any

other amplifier for that matter—the test is performed by supplying a distortionless signal to the input and then measuring the harmonic content at the output. Most THD analyzers reject the fundamental signal with a notch filter and measure all other energy within the audio spectrum. The THD then becomes:

$$\% \text{ THD} = \frac{\text{Harmonics} \times 100}{\sqrt{(\text{Fundamental})^2 + (\text{Harmonics})^2}}$$

The THD measurements for audio equipment are usually made at a number of input and output levels, since the harmonic distortion introduced by the amplifier depends on the gain and the power output at which it is operated. Harmonic distortion is a direct result of nonlinearities within the amplifier.

Note that the described technique for measuring THD includes noise, hum or other nonharmonically related signals not rejected by the notch filter tuned to the fundamental frequency. Two points

therefore must be considered. First, the amplifier itself must be thoroughly analyzed for its own hum and noise prior to using it for THD measurements. Any such components should be eliminated before the measurement. Second, the oscillator supplying the distortion-free signal must also be free of hum and noise.

A method of measuring THD that eliminates this problem uses a wave analyzer. This consists of an extremely sharply tuned filter followed by an AC voltmeter. Although measuring THD with a wave analyzer is more tedious, the result is more accurate. The ultra-low distortion characteristics of the generator are still required, and, of course, there must be no hum and noise. However, levels of hum are permitted with this system of measurement.

The wave analyzer is first tuned to the fundamental frequency and an amplitude measurement is taken. It is then tuned to the second, third, fourth, fifth, etc., har-

monics, and amplitude measurements are taken. THD is then calculated using the following formula:

$$\% \text{ THD} = \frac{\sqrt{(2\text{nd})^2 + (3\text{rd})^2}}{\text{Fundamental}} \times 100\%.$$

Although truly broadband noise contributes throughout to this measurement, hum and other nonharmonically related spurious signals are eliminated.

When making THD measurements with an analyzer that uses the notch filter, a few basic testing precautions are necessary. Since hum contributes significantly to the harmonic distortion measurement, ground loops must be carefully avoided. A ground loop consists of a second path through which the ground or return signals for the test may pass. Frequently, this second path also contains significant line-frequency currents, which could enter into the measurement and contribute an undesired signal to the output. This signal is generated by neither the amplifier nor the oscillator, but affects the measurement.

Two forms of THD analyzers use the notch technique: With the first and simplest form, the notch filter is manually tuned. The second technique uses manual tuning to within a few percent of the desired center frequency, when an automatic nulling circuit takes over to center the analyzer on the fundamental frequen-

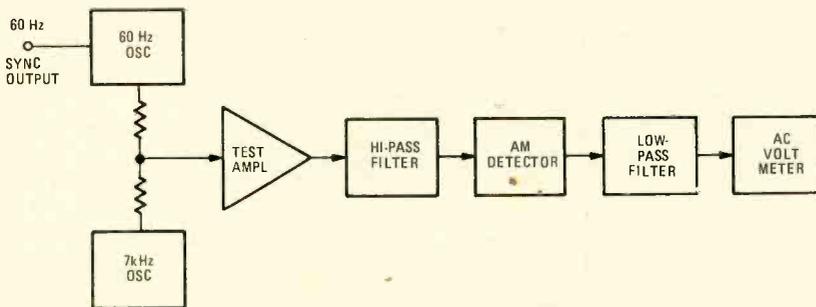


FIG. 1—INTERMODULATION ANALYZER. Two signals are sent through the amplifier; then the effect of one on the other is measured.

cy. Errors can occur in the analysis if the generator drifts from the fundamental frequency to which the analyzer was tuned. An analysis with automatic null compensates for minor drifts. However, drifting introduces errors to measurements made with the manually tuned analyzer.

A note of caution regarding THD measurements: It seems logical that one could measure both the THD of the generator and the THD at the output of the unit under test and subtract, thus arriving at the THD contributed by the device under test. Unfortunately, because of the complex qualities of the signals, this technique does not lead to a proper measurement. The THD of the audio oscillator must be substantially less than that expected from the amplifier being tested.

Intermodulation distortion

Distortion is any difference, other than

a difference in magnitude, between the input and the output signals, either expressed as percentage or as an absolute value. We know from the previous section that THD represents components added to the output signal whose frequencies are exact multiples of the fundamental signal but which did not appear at the input. Intermodulation effects also contribute to distortion in an amplifier, and also take place where there are nonlinearities. The added signals are the sum and difference products of two or more amplified signals.

An audio amplifier test for intermodulation (IM) distortion usually consists of mixing a 60-Hz signal with a 7-kHz signal—that is, signals at 7,060 Hz and signals at 6,940 Hz are measured. These signals are generated in the amplifier by intermodulation. Figure 1 is the block diagram of a test configuration for measuring IM distortion. Because this technique requires two audio oscillators, two filters, a detector and an audio voltmeter, an IM analyzer is used that incorporates those instruments in a single package.

The measurement process is relatively simple. A high-pass filter eliminates the 60-Hz component at the input of the audio amplifier under test, but passes the 7-kHz signal. Once the 60-Hz component has been removed, the modulated 7-kHz signal (the 7-kHz signal with the two 60-

Hz sidebands created by any IM distortion of the amplifier) is applied to an AM detector. The detector output is a 60-Hz signal whose amplitude is in direct proportion to the amount of IM present. Any 7-kHz signal passing through the AM detectors is removed by the low-pass filter. The 60-Hz product is measured by the voltmeter.

The audio oscillators used for this particular application must be almost free of hum, especially the one generating the 7-kHz signal. Extremely low harmonic content is required of the one that generates the 60-Hz signal. To avoid spurious beats caused by interaction between the 60-Hz line frequency, the 60-Hz test signal is usually synchronized to the line. (The 60-Hz line itself is not used for the measurement since its harmonic content and amplitude variations with time are too great to permit successful measurements.) It should be noted that the 4-to-1 combiner

mixing the 60-Hz and 7-kHz signals must produce no IM of its own.

Intermodulation distortion, while most frequently produced by the active components of amplification, can also be produced by electromechanical connections on the output of an amplifier. Intermodulation distortion produced in such connections is most frequent under high power conditions, and is usually measured at both high- and low-power levels.

Power output

The audio oscillator is used to drive audio amplifiers to a desired output level to make power measurements. The power output is usually increased until a certain harmonic-distortion value is reached. Measurements are made at this level with the formula $P = E^2/R$, or by $P = E \times I$ if a current meter is available. When the first formula (the most common) is used, a purely resistive load is mandatory. A speaker does *not* provide a constant impedance over frequency.

Audio response

These measurements determine the uniformity of the amplifier's amplitude response with changes in input frequency. Usually this is plotted as decibels variation, with the frequency plotted on a logarithmic scale for compression. Frequency response measurements use the audio oscillator as a signal source because the audio oscillator has a known flat output. Metered audio oscillators tend to reduce setup time. Audio response measurements may be made at various power levels and for different control settings, such as TREBLE and BASS.

Impedance

Both input and output impedance measurements may be made with the audio test oscillator as a signal source. These measurements most frequently establish an output voltage level from the amplifier, and either insert a series resistance for input measurements or a parallel load resistance for output measurements. The inserted resistance is then varied until the output voltage is reduced by 6 dB (50%). At this point, the variable resistor is equal to the unknown impedance.

Damping factor

The damping factor of an audio amplifier is the ratio of output impedance to the rated load impedance. This damping factor is measured by driving the unloaded amplifier to maximum output without introducing distortion. The no-load output voltage is measured (V_{NL}). The rated load (usually 4, 8 or 16 ohms) is now connected and the full-load output voltage is measured (V_{FL}). The damping factor is then given by:

$$\text{Damping Factor} = \frac{V_{FL}}{V_{NL} - V_{FL}}$$

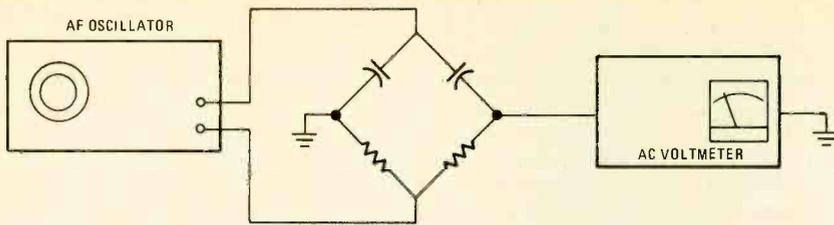


FIG. 2—A SIGNAL GENERATOR for an AC bridge. If oscillator output is balanced to ground, the amplifier can have a single-ended input.

An amplifier whose output impedance is matched to the load impedance has a damping factor of 1. Audio amplifiers, however, commonly have damping factors of 50 or greater.

Miscellaneous measurements

Input sensitivity and input overload are two measurements frequently made on audio amplifiers. Both measurements depend on reaching a low-distortion performance level, and so require a low-distortion oscillator. Channel separation measurements determine the amount of crosstalk between two channels in a stereo or quadriphonic system.

Bridge measurement

The audio oscillator is often chosen as a signal source for bridge measurements simply because many of them have a balanced output. The simple test configuration of Fig. 2 is used. A very high degree of balance can be provided by the audio oscillator if a battery-operated type is selected.

In addition to the balanced output requirements, the audio oscillator also provides low-distortion signals and low hum and noise. Deficiencies in any of these areas cause some imbalance in the bridge, since the undesired signals can make it difficult or impossible to null the bridge effectively. To successfully maintain bridge balance for extended measurements, the oscillator frequency must be constant. Therefore, the good frequency stability properties of the audio oscillator make it a popular choice for bridge measurements. Bridge measurements also generally require a constant amplitude. Amplitude variations of the signal driving the bridge appear as amplitude variations at the bridge output. The audio

oscillator, with its extreme amplitude stability, is most satisfactory for this purpose.

Synchronized oscillator

The audio oscillator in the synchronizing mode can be used for signal regeneration. Often in a laboratory situation, processing or transmission causes the measured signal to be too noisy, too high in distortion, or to have excessive amplitude variations. Applying this signal to the synchronizing input of an audio oscillator results in an output signal in which noise, amplitude variations and distortion are highly suppressed. The audio oscillator acts as a high-quality filter, and when used in this mode, tracks frequency changes of the synchronizing signal over short excursions within the oscillator's lock range. If the synchronizing signal leaves the oscillator's lock range, the oscillator output signal reverts to its natural frequency indicated on the front-panel dial setting.

A typical example is period measurement of signals with a high noise content. Period measurement is susceptible to a high degree of error if there is signal noise. Filtering by a synchronized oscillator substantially improves period measurement accuracy.

A fixed degree of phase shift can be inserted between the synchronizing signal and the audio oscillator output signal by adjusting the front-panel variable-frequency control. Within certain limits, the synchronized audio oscillator can be used to achieve a specified phase shift or time delay.

Frequency response and phase-shift analysis of many of the extremely selective electronic filters available require the signal source to have excellent frequency

stability. The signal source also must have very good spectral purity. However, the excellent frequency stability requirements may exceed either the setability or stability capabilities of the audio oscillator. To make such measurements, the audio oscillator may be locked to a digitally derived source having a high degree of frequency stability but with poor spectral characteristics.

The synchronizing input of an audio oscillator does not reject harmonics. Therefore, the audio oscillator can be easily locked to the second, third, fourth, fifth, or higher harmonic of the synchronizing signal, if the harmonic content is great enough. In some cases this is advantageous. For example, a number of oscillators can be synchronized to one particular signal with a high harmonic content. Each oscillator is synchronized to a different harmonic. The output signals of the various oscillators are combined in a resistive adder.

Extremely complex waveforms can be synthesized by this technique. For example, the squarewave contains a fundamental signal plus a signal at the third harmonic of the fundamental whose amplitude is one-third that of the fundamental, and so on up the odd harmonic spectrum. An extremely pure squarewave could therefore be synthesized by this technique (see Fig. 3). Because all other waveforms are combinations of a fundamental sine wave and its various harmonic amplitudes and phases, they also can be created through such a technique.

A synchronized audio oscillator can reduce frequency jitter or phase-noise problems on the incoming signal. Again, the synchronized audio test oscillator filters out these modulating components from another frequency. The ability of the audio test oscillator to remove these components is limited by the short-term frequency stability of the oscillator itself.

Summary

Although the audio oscillator is no longer the sole low-frequency signal source for all laboratory and service work, there is a wide range of applications in which this most useful instrument should be applied. The audio oscillator has improved considerably in some of the most fundamental and desired specifications. It has moved from its original general-purpose usage into the category of a specialty measurement instrument. It is used whenever only a high-purity audio test oscillator is good enough to provide the signals required. When an instrument evolves in this manner, it very often moves out of the low-cost category and into the special laboratory instrument classification. The audio test oscillator has definitely not done that. Although a good laboratory tool, it is also a fundamental service tool in shops that service quality audio gear. **R-E**


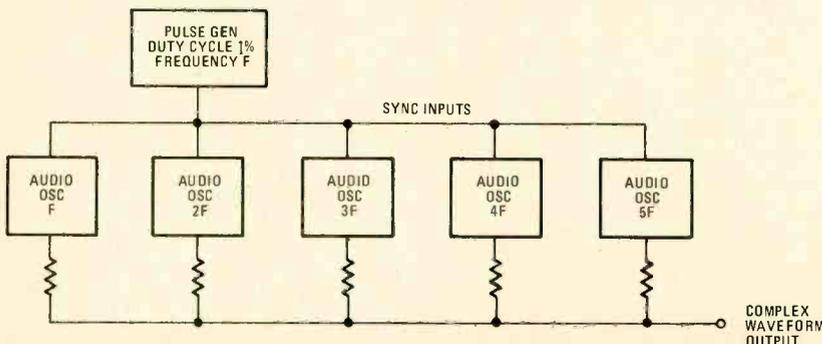
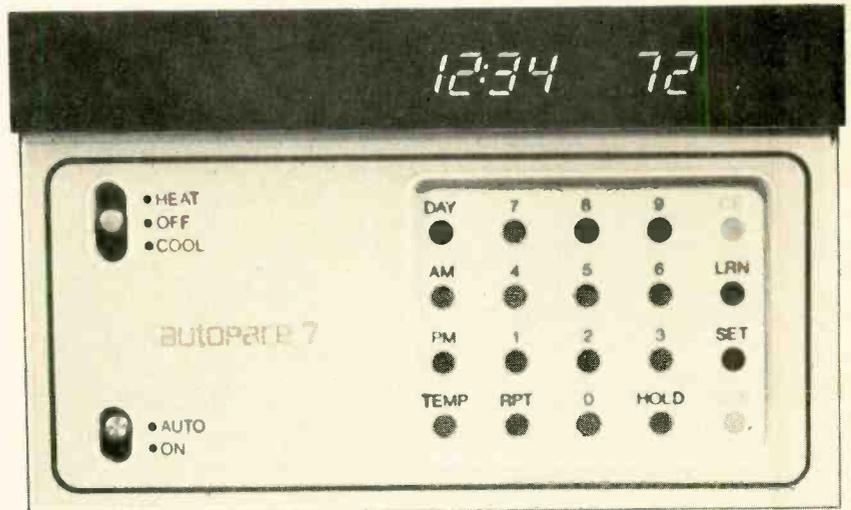


FIG. 3—A FOURIER SYNTHESIZER consists of a combination of oscillators that can produce square-waves or other complex waveforms by adding synchronized harmonics to the fundamental.

cut your fuel costs

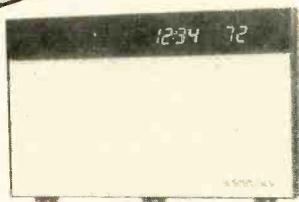

VERSATILE AND EFFICIENT

Don't waste fuel or electricity heating or cooling your home or office when it is unoccupied. With this revolutionary new microprocessor controlled thermostat you can effectively tailor your heating and cooling usage to maximum efficiency with no loss of comfort. Program your schedule into the AutoPace 7 and it will automatically cut back temperatures just prior to your leaving and then re-establish a comfortable temperature just slightly ahead of your arrival. You retain full comfort at a substantial saving of energy. Additional programmed nighttime cutback periods save even more, all automatically. Seven consecutive days may be individually programmed with up to four different time-temperature settings per day, giving you 28 energy saving settings you can live with. This unit is so effective that it qualifies for the Federal Income Tax Credit for energy saving devices.

EASILY ADAPTED TO YOUR PRESENT SYSTEM

AutoPace 7 is compatible with most 24vac 4 wire heating-cooling installations and may be adapted for use with 2 wire heating systems. Simple to install, the unit comes with all necessary hardware and full instructions. The manufacturer, Autotronics, has even set up a Toll Free Technical Information "Hot Line" to answer any questions.

SIMPLE KEYBOARD OPERATION

Simpler to use than a calculator, all program instructions are easily entered via the self contained keyboard. Just enter the days, times and temperatures you desire, AutoPace 7 will do the rest. You can even temporarily override a setting for as long as you wish. If you desire, the Anti-Tamper security feature assures only authorized changes of programming. After programming is completed, simply flip up to the decorative cover to conceal all controls. The attractive Lo-Profile design blends in with any decor.

MICROPROCESSOR BASED DESIGN

Solid State temperature sensing plus Microprocessor circuitry insures reliability. Far more accurate than conventional thermostats, AutoPace 7's unique digital control will maintain temperatures accurately for maximum comfort. Easy to read digital display provides continuous readout of both temperature and time. The AutoPace 7 is so well designed that even in the event of a power failure it automatically resets itself to 68 degrees in the heating mode or 78 degrees in the cooling mode.

HOW MUCH CAN YOU SAVE

Savings of up to 30% can be achieved with the AutoPace 7 as compared to conventional thermostats. The actual amount of your savings will vary according to geographical location and temperature settings used. AutoPace 7, at only \$199.95, will pay for itself in a very short period of time due to today's high cost of fuel and electricity. Additional savings are effected by taking advantage of the Federal Income Tax Credit for Energy Saving Devices. The quickest way to start saving is to call us on our Toll Free Hot Line 800-223-0474, or fill in the handy coupon today.

ADVANCE ELECTRONICS

To order — use this coupon or call

TOLL FREE HOT LINE
800-223-0474

54 West 45 Street, New York, N.Y. 10036 —IN NEW YORK STATE 212-687-2224

Please send me _____ AutoPace 7 Thermostat at \$199.⁹⁵ each

Payment enclosed Bill my MASTER CHARGE VISA

Acct. # _____ Exp. Date _____


Name _____

Address _____

City _____ State _____ Zip _____

N.Y. State Residents Please Add Sales Tax
Orders Outside Continental U.S. Add \$5.00

RE-12

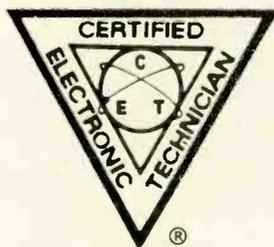

You Can

An installment of a continuing series
readiness to qualify as a

ARE YOU TAKING ADVANTAGE OF THE OPPORTUNITIES to take the sample CET tests that appear on a space-available basis in **Radio-Electronics**? (The first five chapters appeared in the May, July, September and November 1978 and February 1979 issues.) If you feel you are ready to sit for the Associate-level or full exam, write to ISCET, 1715 Expo Lane, Indianapolis, IN 46224 for the name and address of the examiner nearest to you. Now, dig in and see how well you do on this month's test questions. See if you can get 75% or more correct. Also, review the questions and the answers to the previous test.

Chapter 6 questions—Instruments

- In which of the following circuits would testing with a low impedance voltmeter be expected to affect normal operation?
 - () a. An AVC (Automatic Volume Control) voltage bus.
 - () b. An audio output tube cathode circuit.

- () c. A multivibrator grid circuit.
 - () d. A bridge rectifier circuit in a low-voltage power supply.
- The best way to view unmodulated RF frequencies in CB radios is:
 - () a. with an oscilloscope using a demodulator probe.
 - () b. with a distortion analyzer.
 - () c. with an oscilloscope having a horizontal amplifier bandwidth exceeding 30 MHz.
 - () d. with an oscilloscope that has a vertical amplifier bandwidth exceeding 30 MHz.
 - A signal strength meter is used for:
 - () a. checking antennas
 - () b. checking resonant circuits
 - () c. checking oscilloscope bandwidth
 - () d. checking sweep generator bandwidth
 - A dual-trace oscilloscope has both an

alternate and a chopped mode. Which mode would be most likely to be used for low frequencies?

- () a. chopped
 - () b. alternate
 - () c. either
- Which of the following two-waveform examples resembles the horizontal sweep voltage of a: a recurrent sweep; and b: a triggered sweep oscilloscope?
 - An oscilloscope calibrated to read 1 volt-per-division would show how

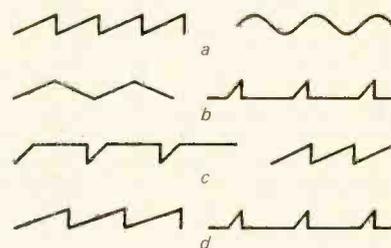


FIG. 1

Correct answers to Chapter 5 Questions about electronic components and circuits

Here are the answers to the questions on electronic components and circuits that appeared in the February 1979 issue.

- Correct answer is "b."** The resonant tank circuit will act as a high impedance or load to only a narrow band of frequencies at and near the resonant frequency of the L—C combination.

The resonant frequency f_r is the frequency at which $X_L = X_C$. Frequencies above the resonant frequency will be by-passed through C. Frequencies below the f_r will be by-passed through L.

- Correct answer is "a."**
- Correct answer is "C."** The Zener "D" will conduct when the E2 voltage goes higher than the diode's breakdown potential. Zener diodes

ANSWERS TO

are constructed so that they have different voltage points at which they avalanche, drawing heavy current until the voltage has been reduced below the breakdown point again. The circuit in Fig. 3 is commonly used to provide regulation in power supplies.

- Correct answer is "d."** The two oppositely connected diodes would truly act as a short for large signals. However, for signals whose desired maxi-

Be A CET



of questions aimed at checking your Certified Electronic Technician

DICK GLASS

much vertical deflection when reading a voltage which shows 2 volts on an AC meter?

- a. 2 divisions
- b. 4 divisions
- c. over 5 divisions
- d. 2.8 divisions

7. An oscilloscope calibrated to read 1 volt-per-division would show how much deflection if reading a voltage which shows 2 volts on a DC meter?

- a. 2 divisions
- b. 4 divisions
- c. over 5 divisions
- d. 2.8 divisions

8. To connect an ammeter how should it be inserted with respect to the load?

- a. In series
- b. In parallel

9. A generator which produces 88 to

108 MHz RF; L + R; L - R; and 19 kHz modulation is a:

- a. TV sweep generator
- b. CB test generator
- c. color bar generator
- d. FM-stereo generator

horizontal sweep rate of 10 ms-per-div. What is the frequency of the waveform?

- a. 500 Hz
- b. 50 Hz
- c. 25 Hz
- d. 250 Hz

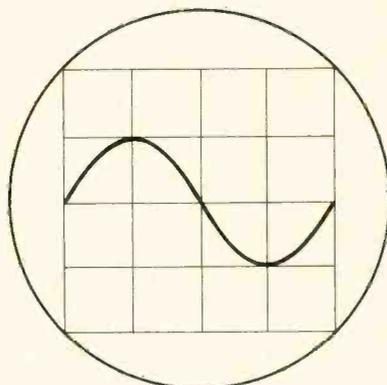


FIG. 2

Be sure to keep this issue handy so you can check your answers in the next chapter of the CET test. The new questions in the next chapter will be on "test and measurements." You may find it a little tough if you haven't brushed-up on the subject.

R-E

10. The scope producing Fig. 2 is set on a

PRIOR QUIZ

mum level is less than the contact potential of the diodes (perhaps signals whose peaks are less than .5 volts, as an example), the arrangement would allow passage of desired-size frequencies, but would act as a short to unwanted noise spikes, either negative or positive.

5. **Correct answer is "a."** Fig. 5 is a drawing for a simple crystal radio. It will work best with a high-impedance headset connected from terminal

"E" to ground.

6. **Correct answer is "a."** The uppermost component shown in Fig. 6 is a photoresistor which varies its resistance according to the light directed on it. Thus it can be used to vary the bias on the transistor, turning it on and activating the relay. The relay can be connected to a light switch, alarm, etc.

7. **Correct answer is "c."**

8. **Correct answer is "a."**

9. **Correct answer is "a."** About the easiest way to tell the difference between a discriminator and a ratio detector is to remember that a ratio detector has the diodes hooked up oppositely and has a large-value capacitor across the circuit (4 μ F in this case)

10. **Correct answer is "a."**

HITACHI

VIZ formerly **rcs**

TRIPLETT



PHILIPS

HICKOK

FLUKE

New Portable Digital Capacitance Meter

MODEL 820



BK PRECISION

- Measures capacitance from 0.1pF to 1 Farad
- Resolves to 0.1pF
- 10 ranges for accuracy and resolution
- 4 digit easy-to-read LED display
- 0.5% accuracy
- Special lead insertion jacks or banana jacks
- Fuse protected
- Uses either rechargeable or disposable batteries
- Overrange indication

Call For Our Price

3-1/2 Digit DMM with .5% Accuracy

BK PRECISION

MODEL 2810

- 3 1/2 digit easy to read LED display
- 0.5% DC accuracy typical
- 100µV, .01 resolution
- 10 ohm range and control to zero lead resistance
- Selectable High-/Low-power ohms on four ranges
- Auto zeroing




Call For Our Price

80MHz Counter with Period Function

MODEL 1820

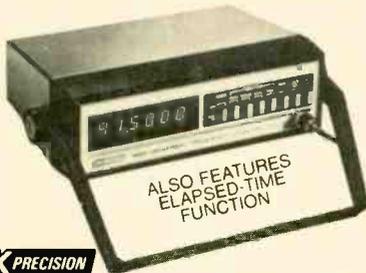- 5Hz to 80MHz reading guaranteed—100MHz typical
- Period measurements from 5Hz to 1MHz.
- Period average, auto and manual positions
- One PPM resolution
- Totalizes to 999999 plus overflow
- Elapsed time measurements from 0.1 to 9999.99 seconds plus overflow
- One-megohm input resistance
- Bright 43' high LED readouts



BK PRECISION

Call For Our Price

New Low Distortion Function Generator

BK PRECISION



Call For Our Price

MODEL 3010

- Generates sine, square and triangle waveforms
- Variable amplitude and fixed TTL square-wave outputs
- 0.1 Hz to 1MHz in six ranges
- Push button range and function selection
- Typical sine wave distortion under 0.5% from 0.1Hz to 100kHz
- Variable DC offset for engineering applications
- VCO external input for sweep-frequency tests

FLUKE

DIGITAL MULTIMETERS

NEW 8022A

- Extensive overload and transient protection
- Rugged construction
- Hi/Lo power ohms for in-circuit resistance and diode testing
- 10 MΩ input impedance doesn't load circuit
- 200 hour battery life — low battery indicator
- Large LCD readout — 2000 counts
- 1 year calibration cycle
- One-hand operation

NOW \$129.

BASIC SPECIFICATIONS

Range	DC Volts	AC Volts	DC Current	AC Current	Ohm
	0.2-1000V	0.2-750V	0.002-2A	0.002-2A	200-20k
Resolution	100 µV	100 µV	1 µA	1 µA	0.1%
Accuracy*	(0.25+1)	1, +2%	(0.75+1)	(1.5+2%)	(0.2+2)



FLUKE


DIGITAL MULTIMETERS

8020A NOW 0.1% Basic dc accuracy

- 26 Ranges—5 Functions plus New Conductance Function for up to 10,000 MΩ Leakage Measurements
- Extensive Overload and Transient Protection
- Rugged Construction—2 Year Warranty
- Hi/Lo Power Ohms for In-circuit Resistance and Diode Testing
- 10 MΩ AC/DC Input Impedance Doesn't Load Circuit
- 200 Hour, 9V-Battery Life—Low Battery Indicator
- Large LCD Readout—2000 Counts
- 0.1% Basic dc accuracy
- One Hand Operation
- Complete with Battery and Test Leads

The new Fluke 8020A continues the standard of excellence set by the highly successful 8000A multimeter family. Many features set the 8020A apart as a truly exceptional instrument. Twenty-four ranges and 5 functions include measuring capability up to 1000V dc, 750V ac, 2A ac/dc and 20 MΩ. Hi/Lo ohms are included for in-circuit resistance and diode test capability. In addition, a new Conductance function allows resistance and leakage measurements up to 10,000 MΩ, a must for circuit board work and component checking.

The 8020A has been designed with the user in mind and features exclusive one-hand operation. For harsh service environments, the 8020A has a ruggedized case and extensive overload/transient protection backed up by a 1-year warranty. Long term stability (1-year calibration cycle) is excellent with only three cal adjustments. Up to 200 hours of continuous operation can be expected from a single 9V alkaline battery.

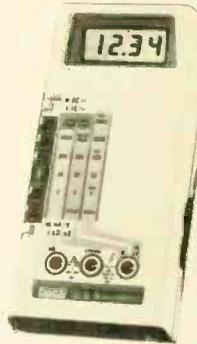

\$169.

FREE CASE WITH 8020A

LCR-740

Transistorized LCR Bridge

LEADER
Instruments Corp.

Regular price \$350

\$299.95

- Highly accurate 3 unit digital readout.
- Measures inductance (L), Capacitance (C), and Resistance (R), within ± 0.5% accuracy.
- Operates on one 9V battery



New Sweep/Function Generator

BK PRECISION



Call For Our Price

MODEL 3020

- Four instruments in one package—sweep generator, function generator, pulse generator, tone-burst generator.
- Covers 0.02Hz-2MHz
- 1000: 1 tuning range
- Low-distortion high-accuracy outputs
- Three-step attenuator plus vernier control
- Internal linear and log sweeps
- Tone-burst output is front-panel externally programmable

Simpson

BK PRECISION

LEADER

DORIC



Non-Linear Systems



DATA PRECISION

FINAL CLOSE-OUT

DUAL-TRACE 5" 30MHz TRIGGERED SCOPE...

BK PRECISION MODEL 1474



Call For Our Price

- Rise time 11.7 nS or less
- Built-in signal delay line permits view of leading edge of high frequency pulse rise time
- Triggers on signals up to 50MHz
- 5mV cm vertical sensitivity
- Mode automatically shifts between CHOP and ALTERNATE as you change sweep time
- Checks most digital logic circuitry, including ECL
- High accuracy ten position vertical input attenuator
- Flat response with smooth rolloff past 30 MHz
- PDA CRT with P31 phosphor
- Built-in high- and low-pass filters
- Maintains calibration accuracy from over 105-130 VAC and 205-260 VAC
- 20 calibrated sweeps — 0.2 uS cm — 0.5 S cm
- Differential input capability
- Algebraic addition and subtraction
- Built-in RF detector for modulation envelope display
- Illuminated graticule

PORTABLE OSCILLOSCOPES

BATTERY OPERATED



Non-Linear Systems

MS15

MS215

NEW MS230



Single Trace 15MHz

Dual Trace 15 MHz

Dual Trace 30MHz

Reg. price \$349.
\$299⁹⁵

Reg. price \$465.
\$399⁹⁵

Regular price \$598.
\$499⁹⁵

Automatic Transistor Checker

LEADER Instruments Corp.

MODEL LTC-906

Regular price \$189
\$159.⁹⁵



Lights Up. Sounds Off. Measures. Identifies. Displays.

- A multipurpose, portable, transistor checker automatically better for laboratory, shop and school.
- Checks transistors, FETs, diodes, good or bad & in or out of circuit.
- Automatically tests a broad range of parameters with simple, program on-off switches—no confusing buttons or lead changes.
- Automatically identifies Germanium or Silicon, plus emitter base and collector.
- LED display plus audible tone indicates defective or good performance.
- Absolute meter readout of DC parameters.

Lab-Quality Semiconductor Tester...

MODEL 530



BK PRECISION

- Measure F_T of bipolar transistors up to 1500 MHz
- Nondestructive testing of transistor and diode breakdown voltages
- Measures transistor beta or FET gm
- Measures all transistor breakdown and leakage parameters
- Fast testing of transistors, FET's, and SCR's—in or out-of-circuit
- Base diagrams are not required
- No biasing information required
- Identifies all leads of transistors and SCR's
- Automatic identification of PNP/NPN types and N- or P-channel FET's

Call For Our Price

MASTER CHARGE

THE TEST EQUIPMENT SPECIALISTS

VISA

TOLL FREE HOT LINE
800-223-0474

54 WEST 45th STREET, NEW YORK, N.Y. 10036 212-687-2224

ADVANCE ELECTRONICS

RF directional wattmeters

HERB FRIEDMAN, COMMUNICATIONS EDITOR

IN ALL COMMERCIAL RADIO COMMUNICATION services *reliability* is the most important parameter next to maintaining FCC performance specifications. (Some technicians might argue that reliability is *more* important than FCC requirements, but that's a subject for another time.)

In a sense, many of us were spoiled by CB when it came to output power measurements. While output power was formerly measured with laboratory-grade instruments, the 4-watt AM/12-watt PEP SSB maximum of CB easily lent itself to budget-priced RF power metering, and one could often run across combination RF output/VSWR meters for anywhere from under \$5 to \$25, the exact price depending more on the size of the meter(s) and its cabinet than the reliability of the instrument.

In most instances, the calibration of the CB power/VSWR meter depends on a factory-adjusted potentiometer of the least expensive variety and quality. As long as the meter sits on a shelf it is accurate; but after being bounced around in the bottom of a tool box one would not even take long odds on its accuracy. It might be OK for CB—but would you trust it for testing or adjusting a marine or aircraft radio, where someone's life could depend on the fact that the output power measurement might reflect some form of improper operation? In short, for professional use *reliability* must be a prime consideration at all times.

In the area of power meters the *transmission line directional wattmeter* has been the general service and lab standard. As implied, the sensing device is a coax-

line section (usually from about 3 to 12 inches depending on total power capacity) with an impedance equal to the transmission line with which it will be used—50 ohms is more or less standard for amateur, VHF, and HF communications. The coax-line section has an opening into which the user plugs an RF element specifically rated for maximum power and frequency limits. An attached calibrated meter is driven from a detector within the element. When the element is turned one way the meter indicates forward output power. When the element is rotated 180°, the meter indicates reflected power. (A supplied chart that we have mentioned in previous columns can be used to interpret the two power readings in terms of system VSWR.)


The coax-line sections come in all sizes, depending on the manufacturer. There are itty-bitty models with special elements for indicating in terms of milliwatts; finger-size sections rated up to about 1 kW; and even (nominally) 3- and 5-inch sections for up to 50,000 watts. As a general rule, the sections intended for use up to about 1 kW are available with interchangeable end connections; the user can almost instantly change to N, BNC or UHF type connectors.

To make life a bit easier for the service technician, the coax-line section and meter are often combined in a rugged metal case. The classic Bird *model 43* wattmeter is the most familiar example. Among the modern styled designs is the *model 1000-A* from Dielectric Communications shown in the photographs. The *1000-A* accepts plug-in elements (sensors) from 0.1 to 5000 watts full scale and covers the range of 2 to 1000 MHz. It is available in a *Wattkit* that consists of the *1000-A*, a padded luggage-type case, a UHF connector and patch cable, storage compartments for additional elements and coax-cable connectors of various types, and a device called a *Sniffer*. That brings us to the next part of this column

Performance specifications

The FCC has minimum standards for harmonic, sideband, and spurious radiation for virtually all transmitters. In addition to insuring that a transmitter meets the specifications for those parameters, a technician is responsible for insuring that the carrier frequency is within what has become rather stringent limits. As a general rule, the service technician checks for spurious signals and the carrier frequency

continued on page 76

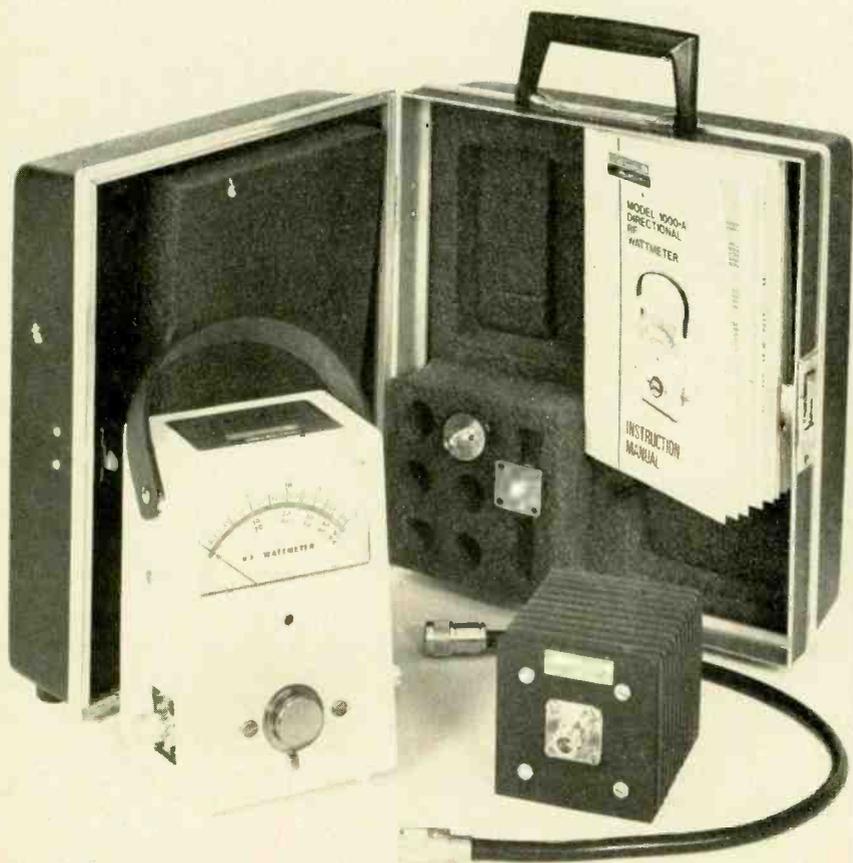

COMPLETE WATTKITS for the service technician are available. These include a basic meter, a padded carrying case, patch coax cable, storage compartments for power sensing elements and line connectors. A larger kit includes a 100-watt *dry* (air cooled) dummy load, and a larger carrying case.

ITEM NO.
WK-7

CMOS SAFE

IC INSERTION/EXTRACTION KIT

- KIT INCLUDES**
- MOS-1416 14-16 CMOS SAFE INSERTER
 - MOS-2428 24-28 CMOS SAFE INSERTER
 - MOS-40 36-40 CMOS SAFE INSERTER
 - EX-1 14-16 EXTRACTOR
 - EX-2 24-40 CMOS SAFE EXTRACTOR




OK MACHINE & TOOL CORPORATION
3455 CONNER ST., BRONX, N.Y. 10475 U.S.A.
PHONE (212) 994-6600 TELEX NO 125091



PRINTED IN U.S.A.

PATENT PENDING

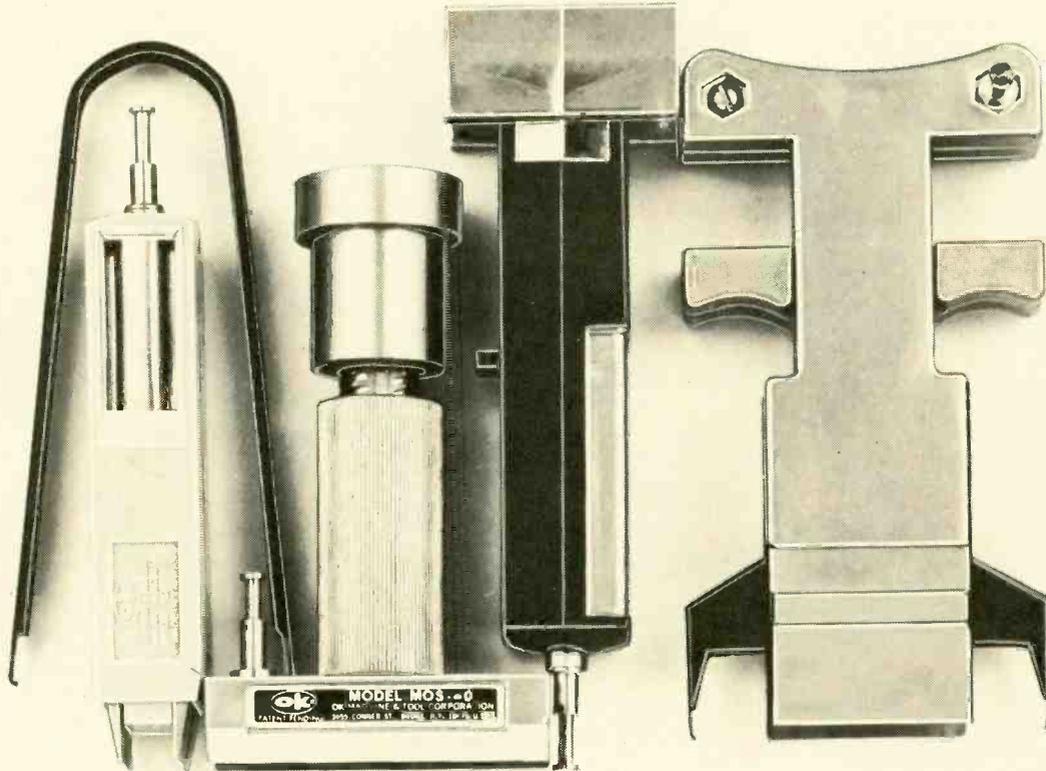

INS-1416	14-16 PIN DIP IC INSERTER	\$ 3.49
MOS-1416	14-16 PIN MOS CMOS SAFE INSERTER	\$ 7.95
MOS-2428	24-28 PIN MOS CMOS SAFE INSERTER	\$ 7.95
MOS-40	36-40 PIN MOS CMOS SAFE INSERTER	\$ 7.95
EX-1	14-16 PIN EXTRACTOR TOOL	\$ 1.49
EX-2	24-40 PIN CMOS SAFE EXTRACTOR TOOL	\$ 7.95
WK-7	COMPLETE IC INSERTER/EXTRACTOR KIT	\$29.95

MINIMUM BILLING \$25.00. ADD SHIPPING CHARGE \$2.00. NEW YORK RESIDENTS ADD APPLICABLE TAX.

OK MACHINE & TOOL CORPORATION 3455 CONNER ST., BRONX, N.Y. 10475 (212) 994-6600/TELEX 125091

CIRCLE 41 ON FREE INFORMATION CARD



Write and run programs—the very first night—even if you've never used a computer before!

You're up and running with video graphics for just \$99.95 — then use low cost add-ons to create your own personal system that rivals home computers sold for 5-times ELF II's low price!

Featuring **RCA 1802 COSMAC CPU**

Own a powerful home computer system, starting for just \$99.95—a price that gets you up and running the very first night... with your own TV for a video display. \$99.95 ELF II includes RCA 1802 8 bit microprocessor addressable to 64k bytes with DMA, interrupt, 16 registers, ALU, 256 byte RAM, full hex keyboard, two digit hex output display, stable crystal clock for timing purposes, RCA 1801 video IC to display your programs on an video monitor or TV screen and 5-slot plug-in expansion bus (less connectors) to expand ELF II into a giant!

ELF II Explodes Into A Giant!

Master ELF II's \$99.95 capabilities, then expand with GIANT BOARD... KLUDGE BOARD... 4k RAM BOARDS... TINY BASIC... ASCII KEYBOARD... LIGHT PEN... ELF-BUG MONITOR... COLOR GRAPHICS & MUSIC SYSTEM... TEXT EDITOR... ASSEMBLER... DISASSEMBLER... VIDEO DISPLAY BOARD... and, another great reason for getting your ELF now—

BREAKTHROUGH!

Netronics proudly announced the release of the first 1802 FULL BASIC, written by L. Sandlin, with a hardware floating point RPN math package (requires 8k RAM plus ASCII and video display boards), \$79.95 plus \$2 p&h. Also available for RCA VIP and other 1802 systems (send for details)!

Master This Computer In A Flash!

Regardless of how minimal your computer background is now, you can learn to program an ELF II in almost no time at all. Our Short Course On Microprocessor & Computer Programming—written in non-technical language—guides you through each of the RCA COSMAC 1802's capabilities, so you'll understand everything ELF II can do... and how to get ELF II to do it! Don't worry if you've been stumped by computer books before. The Short Course represents a major advance in literary clarity in the computer field. You don't have to be a computer engineer in order to understand it. Keyed to ELF II, it's loaded with "hands on" illustrations. When you're finished with the Short Course, neither ELF II nor the RCA 1802 will hold any mysteries for you.

In fact, not only will you now be able to use a personal computer creatively, you'll also be able to read magazines such as BYTE, INTERFACE, AGE, POPULAR ELECTRONICS and PERSONAL COMPUTING and fully understand the articles. And, you'll understand how to expand ELF II to give you the exact capabilities you need!

If you work with large computers, ELF II and the Short Course will help you understand what they're doing.

Get Started For Just \$99.95, Complete!

\$99.95 ELF II includes all the hardware and software you need to start writing and running programs at home, displaying video graphics on your TV screen and designing circuits using a microprocessor—the very first night—even if you've never used a computer before.

ELF II connects directly to the video input of your TV set, without any additional hardware. Or, with an \$8.95 RF modulator (see coupon below), you can connect ELF II to your TV's antenna terminals instead.

ELF II has been designed to play all the video games you want, including a fascinating new target/missile gun game that was developed specifically for ELF II. But games are only the icing on the cake. The real value of ELF II is that it gives you a chance to write machine language programs—and machine language is the fundamental language of all computers. Of course, machine language is only a starting point. You can also program ELF II with assembly language and TINY BASIC. But ELF II's machine language capability gives you a chance to develop a working knowledge of computers that you can't get from running only

ELF II Gives You The Power To Make Things Happen!

Expanded, ELF II can give you more power to make things happen in the real world than heavily advertised home computers that sell for a lot more money. Thanks to an ongoing commitment to develop the RCA 1802 for home computer use, the ELF II products—being introduced by Netronics—keep you right on the outer fringe of today's small computer technology. It's a perfect computer for engineering, business, industrial, scientific and personal applications.

Plug in the GIANT BOARD to record and play back programs, edit and debug programs, communicate with remote devices and make things happen in the outside world. Add Kluge (prototyping) Board and you can use ELF II to solve special problems such as operating a complex alarm system or controlling a printing press. Add 4k RAM Boards to write longer programs, store more information and solve more sophisticated problems.

ELF II add-ons already include the ELF II Light Pen and the amazing ELF-BUG Monitor—two extremely recent breakthroughs that have not yet been duplicated by any other manufacturer.

The ELF-BUG Monitor lets you debug programs with lightning speed because the key to debugging is to know what's inside the registers of the microprocessor. And, with the ELF-BUG Monitor, instead of single stepping through your programs, you can now display the entire contents of the registers on your TV screen. You find out immediately what's going on and can make any necessary changes.

The incredible ELF II Light Pen lets you write or draw anything you want on a TV screen with just a wave of the "magic wand." Netronics has also introduced the ELF II Color Graphics & Music System—more breakthroughs that ELF II owners were the first to enjoy!

ELF II Tiny BASIC

Ultimately, ELF II understands only machine language—the fundamental coding required by all computers. But, to simplify your relationship with ELF II, we've introduced an ELF II Tiny BASIC that makes communicating with ELF II a breeze.

Now Available! Text Editor, Assembler, Disassembler And A New Video Display Board!

The Text Editor gives you word processing ability and the ability to edit programs or text while it is displayed on your video monitor. Lines and characters may be quickly inserted, deleted or changed. Add a printer and ELF II can type letters for you—error free—plus print names and addresses from your mailing list!

ELF II's Assembler translates assembly language programs into hexadecimal machine code for ELF II use. The Assembler features mnemonic abbreviations rather than numerics so that the instructions on your programs are easier to read—this is a big help in catching errors.

ELF II's Disassembler takes machine code programs and produces assembly language source listings. This helps you understand the programs you are working with... and improve them when required.

The new ELF II Video Display Board lets you generate a sharp, professional 32 or 64 character by 16 line upper and lower case display on your TV screen or video monitor—dramatically improving your unexpanded \$99.95 ELF II. When you get into longer programs, the Video Display Board is a real blessing!

Now Available!


- A-D/D-A Board Kit includes 1 channel (expandable to 4) D-A, A-D converters, \$39.95 plus \$2 postage & handling.
- PILOT Language—A new text-oriented language that allows you to write educational programs on ELF II with speed and ease! Write programs for games... unscrambling sentences... spelling drills... "fill in the missing word" tests, etc. PILOT is a must for any ELF II owner with children. PILOT Language on cassette tape, only \$19.95 postpaid!
- Game Package on cassette tape (requires 4k RAM), \$9.95 plus \$2 postage & handling.

Clip Here and Attach to Your Order Below!

Netronics R&D Ltd., Dept RE-12
333 Litchfield Road, New Milford, CT 06776

PHONE ORDERS ACCEPTED!
Call (203) 354-9375

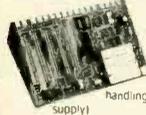Yes! I want my own computer! Please rush me—



- RCA COSMAC ELF II kit at \$99.95 plus \$3 postage and handling (requires 6.3 to 8 volt AC power supply)
- Power Supply (required) \$4.95 postpaid
- RCA 1802 User's Manual \$5 postpaid
- Tom Pittman's Short Course On Microprocessor & Computer Programming teaches you just about everything there is to know about ELF II or any RCA 1802 computer. Written in non-technical language, it's a learning breakthrough for engineers and laymen alike \$5 postpaid
- Deluxe Metal Cabinet with plexiglas dust cover for ELF II, \$29.95 plus \$2.50 p&h
- I am also enclosing payment (including postage & handling) for the items checked below!
- I want my ELF II wired and tested with power supply, RCA 1802 User's Manual and Short Course—all for just \$149.95 plus \$3 p&h.

ALSO AVAILABLE FOR ELF II—

- GIANT BOARD™ kit with cassette I/O, RS 232 C/TTY I/O, 8-bit P/I/O decoders for 14 separate I/O instructions and a system monitor/editor. \$39.95 plus \$2 p&h
- Kluge (Prototyping) Board accepts up to 36 IC's \$17.00 plus \$1 p&h
- 4k Static RAM kit. Addressable to any 4k page to 64k. \$89.95 plus \$3 p&h
- Gold plated 86-pin connectors (one required for each plug-in board) \$5.70 ea. postpaid
- Expansion Power Supply (required when adding 4k RAM) \$34.95 plus \$2 p&h
- Professional ASCII Keyboard kit with 128 ASCII upper/lower case set, 96 printable characters, onboard regulator, parity logic selection and choice of 4 hand-spacing signals to mate with almost any computer. \$64.95 plus \$2 p&h
- Deluxe metal cabinet for ASCII Keyboard. \$19.95 plus \$2.50 p&h
- Video Display Board kit lets you generate a sharp, professional 32 or 64 character by 16 line upper and lower case display on your TV screen or video monitor—dramatically improving your unexpanded \$99.95 ELF II (fits inside ASCII Keyboard cabinet) \$89.95 plus \$2 p&h
- ELF II Tiny BASIC on cassette tape. Commands include SAVE, LOAD, ±, ×, ÷ (!)

- 26 variables A-Z LET, IF/THEN, INPUT, PRINT, GO TO, GO SUB, RETURN, END, REM, CLEAR, LIST, RUN, PLOT, PEEK, POKE. Comes fully documented and includes alphabetic generator required to display alphanumeric characters directly on your TV screen without additional hardware. Also plays tick-tack-toe plus a drawing game that uses ELF II's hex keyboard as a joystick. 4k memory required. \$14.95 postpaid
- Tom Pittman's Short Course on Tiny Basic for ELF II \$5 postpaid
- ELF-BUG™ Deluxe System Monitor on cassette tape. Allows displaying the contents of all registers on your TV at any point in your program. Also displays 24 bytes of memory with full addresses, banking cursor and auto scrolling. A must for the serious programmer! \$14.95 postpaid
- Text Editor on cassette tape gives you the ability to insert, delete or edit lines and words from your programs while they are displayed on your video monitor. (Add printer and you can use ELF II to type error-free letters plus insert names and addresses from your mailing list) \$19.95 postpaid
- Assembler on cassette tape translates assembly language programs into hexadecimal machine code for ELF II use. Mnemonic abbreviations for instructions (rather than numerics) make programs easier to read and help prevent errors. \$19.95 postpaid
- Disassembler on cassette tape takes machine code


Total Enclosed \$
(Conn. res. add tax)
CHARGE IT! Exp. Date
 Visa Master Charge
(Bank #)
Account #

programs and produces assembly language source listings to help you understand and improve your programs \$19.95 on cassette tape.
SAVE \$9.95—Text Editor, Assembler & Disassembler purchased together, only \$49.95! (Require Video Display Board plus 4k memory.)
 ELF II Light Pen, assembled & tested. \$7.95 plus \$1 p&h
 ELF II Color Graphics & Music System Board kit \$49.95 plus \$2 p&h
 ELF II connects directly to the video input of your TV set without additional hardware. To connect ELF II to your antenna terminals instead, order RF Modulator. \$8.95 postpaid.
Coming Soon: A, D, D-A Converter, Controller Board and more!
Print Name
Address
City
State Zip
DEALER INQUIRIES INVITED

COMMUNICATIONS CORNER continued from page 74

by visually observing the transmitter's output on a spectrum analyzer and/or a frequency meter. The problem is: Most spectrum analyzers and many frequency counters (depending on the frequency range and type) are rated for a maximum input of about 1-watt RF. If you hit the input with more than the rated power or voltage, the analyzer and/or counter generates its own spurious signals that you can't distinguish from the spurious signals of the transmitter being tested.

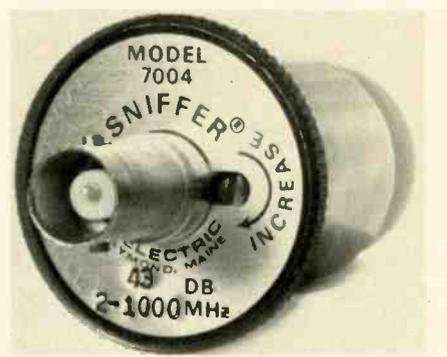So how do we handle transmitter outputs greater than 1-watt? Better still; how would we tap off an RF sample from a transmission line carrying up to 1 kW without cutting into the line? The answer is a Sniffer.



MINUTE SAMPLES OF RF are tapped from a transmission line with a Sniffer or similar device. The Sniffer plugs into the power meter just like a measuring element, or you can use just a coax line section by itself. It provides 43 dB attenuation at the BNC connector. ±8 dB. The attenuation vernier is the small screw adjacent to the BNC connector. On a transmission line carrying 1 kW, the Sniffer can knock the sample down to 316 mW, a safe value for virtually all test equipment.

A Sniffer (also called a transmission-line tap, or Variable RF Signal Sampler) is simply an adjustable RF sensor that plugs into the same type of coax line section used in RF power meters.

Closely resembling a power element, the Sniffer has a BNC connector to which you connect the test equipment. There is 43 dB ±8 dB attenuation between the power in the line and the output of the BNC connector. (A small screw adjacent to the BNC connector is the ±8 dB adjustment.) Thus if you have 100 watts in the transmission line, the BNC output will be at least 31.6 mW.

Since the coax line section and the Sniffer are transparent to RF in the transmission line (except for the extremely minute amount tapped off), like a coax line power meter, they can be left permanently connected to the antenna system.

For additional information on directional wattmeters and the RF Sniffer write to the manufacturer, Diectric Communications, Tower Hill Rd, Raymond, ME 04071. R-E

Master the art of color with the High-Performance NTSC Generator


The best foundation for accurate color reproduction is an accurate and stable test signal source. B&K-PRECISION's new NTSC color pattern generator is all that and more.

The B&K-PRECISION "1250" is a state-of-the-art generator intended for color broadcast, CATV and industrial applications. Its simple operation also makes it a time-saving tool for aligning and trouble-shooting video tape recorders.

The primary pattern generated by the 1250 is NTSC color bars with or without an -IWQ signal (occupying the lower quarter of the pattern). Other features are a five-step staircase pattern with selectable chroma levels; convergence dot, cross-hatch, dothatch and center-cross patterns; and a choice of eight color rasters (including black burst). The 1250 doesn't stop at video patterns though, it

also generates a stable 4.5 MHz sound carrier, modulated by 1 kHz or 3 kHz signals or any external audio signal. RF outputs can be generated on channels 3 or 4, or the standard TV i-f frequency. Each output is crystal controlled for stability.

For trouble-shooting applications, in-

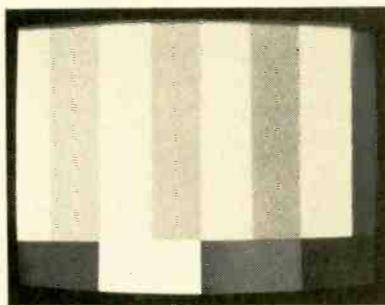

circuit analysis of custom ICs can be done by using the NTSC bar signal and an oscilloscope to examine the inputs and outputs at each IC pin. These results can then be compared to that of a known good unit or reference diagram. The presence of NTSC sync, color bars, luminance components and sound carrier make possible a thorough evaluation of all video circuits. The internal RF modulator can be fed by an internal test signal or any external composite video source. In addition, an RF output can be selected independently of the composite video output, so that a waveform monitor and a television receiver can be fed simultaneously.

The B&K-PRECISION 1250 will give you the master's touch for color. For immediate delivery or additional information, contact your local B&K-PRECISION distributor.

BK PRECISION DYNASCAN CORPORATION

6460 W. Cortland Street • Chicago, IL 60635 • 312/889-9087

B&K-PRECISION
Model 1250
\$795

In Canada: Atlas Electronics Ontario International Sales: Empire Exporters, Inc. 270 Newtown Road, Plainview, L.I., N.Y. 11803



CIRCLE 66 ON FREE INFORMATION CARD

state of solid state

Two new IC's from RCA make DMM design a cinch. Plus other nifty new releases. **KARL SAVON**, SEMICONDUCTOR EDITOR

CONSTRUCTING A DIGITAL VOLTMETER was once a major undertaking. There was an overall system to design, multiple power supplies to be considered, many digital IC's to be designed and interconnected, and display-segment driver transistors to be wired. Now RCA has designed two IC's that make voltmeter construction easy and inexpensive.

The CA3161E and CA3162E IC's are constructed with I²L/bipolar technology. They use integrated injection logic for low power and high-chip density. The I²L construction uses inverted transistors in which conventional emitters become collectors. This means that the usually high-breakdown voltage collector-base junctions are really relatively low-breakdown voltage emitter-base junctions. Bipolar devices are used where higher breakdown voltage and greater current capacity are required.

The CA3162E analog-to-digital (A/D) converter is a three-digit resolution system that measures input voltages between -99 mV and +999 mV. Negative input voltages can be measured even though the IC power source is a single +5-volt nominal supply. Figure 1 is the block diagram of the circuitry on the 107 × 130-mil IC in a 16-lead dual in-line package (DIP).

The system uses the dual-slope technique. The input voltage is converted to a proportional current that charges a capacitor for a specific time interval (about 1.3 ms). At the end of the time interval, the input-current source is disconnected and an internal constant-current source discharges the capacitor. The number of clock cycles that elapse from this time until the voltage reaches its initial value at the start of the charge period are counted. If properly scaled, the accumulated count directly corresponds to the DC input voltage. Dual-slope A/D conversion has the advantage of being independent of the internal clock frequency. Charge intervals are inversely proportional to frequency, and the counted clock cycles are directly proportional to frequency, so the two effects cancel each other. An internal ring oscillator supplies all the timing control signals, and no external oscillator components are necessary or even provided for by the RCA IC's.

However, there must be some kind of accurate reference voltage against which to judge the input voltage. The CA3162E reference voltage is a band-gap supply that is transformed into the reference-

capacitor discharge current. This current is pitted against the converted input voltage and therefore becomes the standard for the measurement.

The 786-kHz ring-oscillator frequency is divided by 2048 to produce the 384-Hz multiplex signal. A further division by 96 results in a 4-Hz conversion rate. Con-

continued on page 80

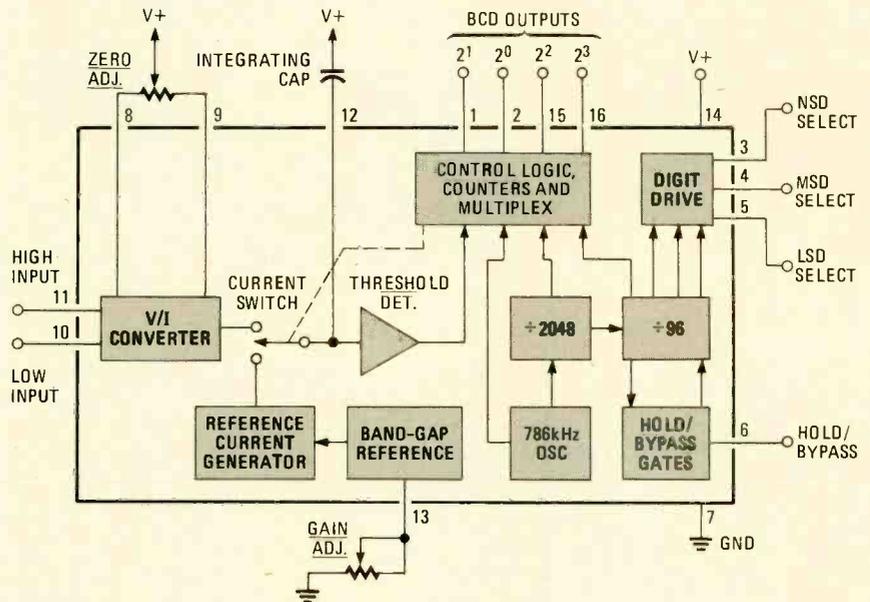


FIG. 1


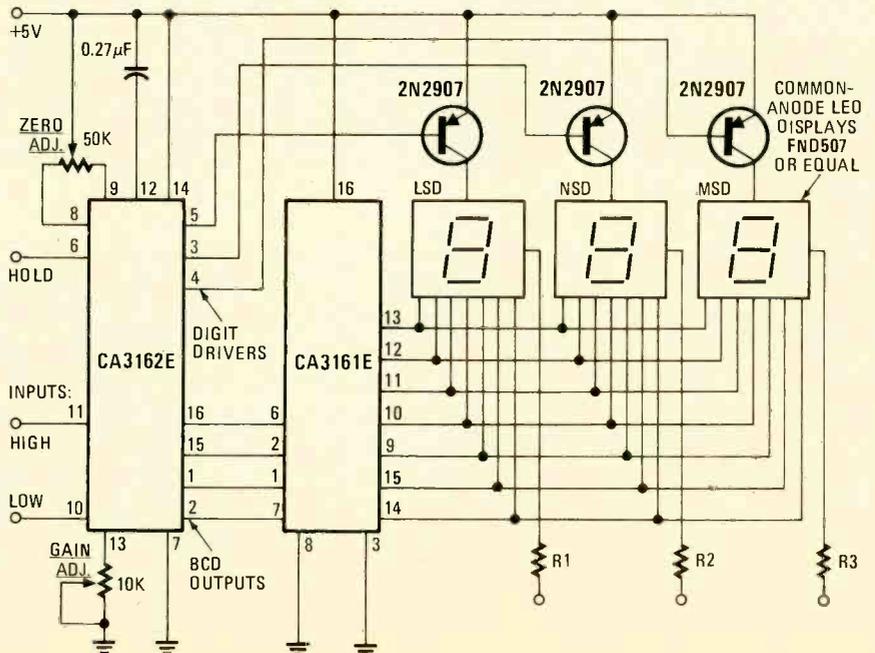


FIG. 2


DIGITAL ACCURACY AT YOUR FINGERTIPS

LX 303
by
Hickok

**ONLY
74.⁹⁵**

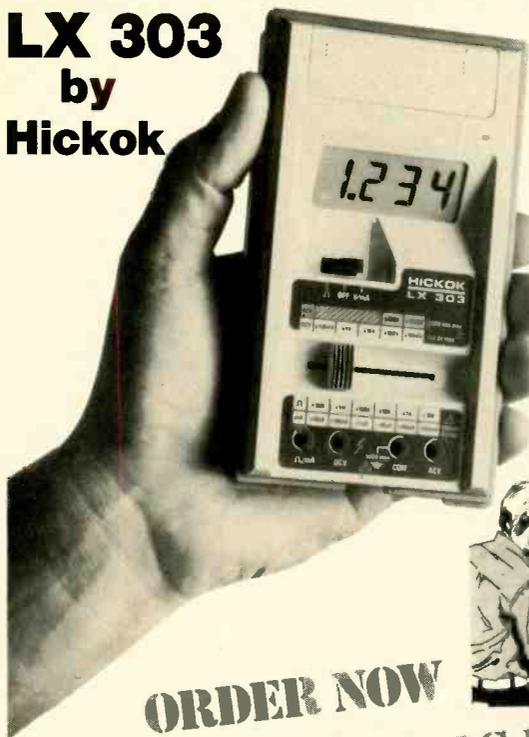

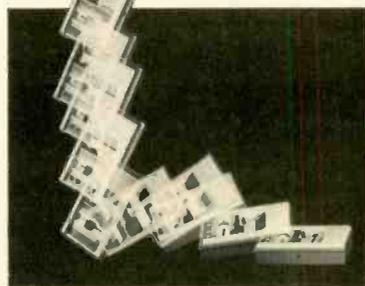adapter (model VP-10) provides protection of up to 10,000 volts when making DC voltage measurements.



The LX303 is designed to withstand a drop from 4 feet without damage.

**ORDER NOW
FOR CHRISTMAS DELIVERY!**

On the bench, in your hand or on-the-go, LX303 is your number one value in a compact DVOM. Even though it is low priced, the LX303 provides the level of performance you'd expect to find in more expensive instruments. A full 3½ digit display (1.999 full-scale reading) provides range-to-range overlap for best accuracy and typical precision of better than 1%. The 100 mV DCV range gives you low level measurement capability usually found on instruments costing nearly twice the price. The maximum resolution of 0.1 ohms lets you accurately check ballast resistors, windings, coils, etc. The low-power output (0.35 V max. full-scale voltage) makes in-circuit resistance measurements sure and easy.

Fast, easy, one hand operation. Automatic polarity, automatic zero, automatic over-range indication and a rapid (3 per second) reading rate speed up and simplify operation. R. F. shielding assures you of jitter free

readings on the big, ½ inch high, easy reading, wide angle, LCD display. Panel switches are human engineered for easy one hand operation.

Years of hassle-free reliability. The 300 hour typical battery life means you'll only need to install a new battery once every 6 months or so (at 2 hours/day, 5 days/week). A convenient battery check capability is built in. The LX303's excellent overload characteristics also assure long reliable operation. All DC V ranges will take 1000 volts without damage except the 100 mV range which will handle 500 volts. All AC V ranges will withstand 600 volts. The ohms ranges are fully protected too — up to 120 volts AC or DC without damage — up to 240 volts short term.

10,000 Volt Protection (optional). For applications where the LX303 will be used around voltages over 1000 volts — such as TV chassis, etc., the optional x10 probe

Built to "take it". The high impact thermoplastic case and cover protect the LX303 from abuse in transportation, and storage. Glass-epoxy pc board construction with a minimum of hand-wiring greatly reduces the possibility of field failures. Even the operating panel nomenclature is protected by a .010" thick layer of GE Lexan® to keep it clean and easily readable even after extended usage. LSI circuitry and a laser-trimmed thick film resistor network provide a very low parts count inside, so there's less to go wrong in a variety of temperatures, climates and working situations. All plugs and jacks are recessed and all metal parts fully insulated for your safety even in hand-held usage.

Order with confidence. Thousands of these units are already in use by engineers and technicians from many of the largest U.S. corporations. LX303 is manufactured in the U.S.A. and carries a full one year warranty from the Hickok Electrical Instrument Company with over 65 years of test equipment production experience. Your LX303 comes to you fully assembled and calibrated, complete with test leads and instruction manual.

As one of Hickok's leading national distributors we unconditionally recommend the LX303 as an outstanding value. Use this coupon or phone to place your order directly to us.

ADVANCE ELECTRONICS

54 West 45th Street, New York, N.Y. 10036

LX 303 SPECIFICATIONS

DC Volts (5 RANGES): 200mV to 1000V full scale, RESOLUTION 0.1mV ACCURACY: ±(0.5% rdg + 0.5% f.s.); INPUT IMPEDANCE: 10MΩ; OVERLOAD PROTECTION, 1000VDC or peak AC all ranges. AC VOLTS (40 Hz to 5kHz): 200V to 600V full scale; RESOLUTION: 0.1V; ACCURACY: ±(1.0% rdg - 0.5% f.s.); 2.0 db at 5kHz; OVERLOAD PROTECTION: 600VDC or rms. RESISTANCE (6 RANGES, LOW POWER): 200Ω to 20MΩ full scale; RESOLUTION: 0.1Ω; ACCURACY: ±(0.5% rdg + 0.5% f.s.) ±(1.5% rdg + 0.5% f.s.) on 20MΩ range; OVERLOAD PROTECTION: 120VDC or rms all ranges, 240V rms for 30 sec. DC CURRENT (6 RANGES): 20 nA to 200 mA full scale; ACCURACY: ±(0.5% rdg + 0.5% f.s.); OVERLOAD PROTECTION: 80V on 10 nA to 10 μA ranges, 25 mA on 100 μA range and 500 mA on 100 mA range. GENERAL: DIMENSIONS: 5½ x 3¾ x 1½" (14.7 x 8.5 x 4.3cm); WEIGHT: 12 oz (0.33kg); POWER 9V battery (not incl.) or Hickok AC Adapter; BATTERY LIFE: Alkaline, 300 hours typical READ RATE: 3/sec.; TEMPERATURE: 0 C to 50 C operating. - 35 C to + 60 C storage.

ADVANCE ELECTRONICS

TO ORDER CALL TOLL FREE
800-223-0474

54 West 45th Street, New York, N.Y. 10036 212-687-2224

PLEASE SEND ME

- _____ Hickok LX303 Digital Multimeters @ 74.95 ea.
- _____ RC-3 AC Adapter, 115VAC (220VAC avail.) @ 8.00 ea.
- _____ CC-3 Deluxe Carrying Case @ 8.00 ea.
- _____ VP-10 x10 DCV Probe Adapter @ 16.50 ea.
- _____ CS-1 10A DC Current Shunt @ 16.50 ea.
- _____ TP-20 Temperature Probe (Specify C or F) @ 39.95 ea.

Payment encl. Bill my: Master Charge VISA

Account # _____ Exp. Date _____

Name _____

Address _____

City _____

State _____


Zip _____

Add \$3.00 Postage and Handling, N.Y. residents add sales tax.

CIRCLE 63 ON FREE INFORMATION CARD

www.americanradiohistory.com

\$140 Gets It All.

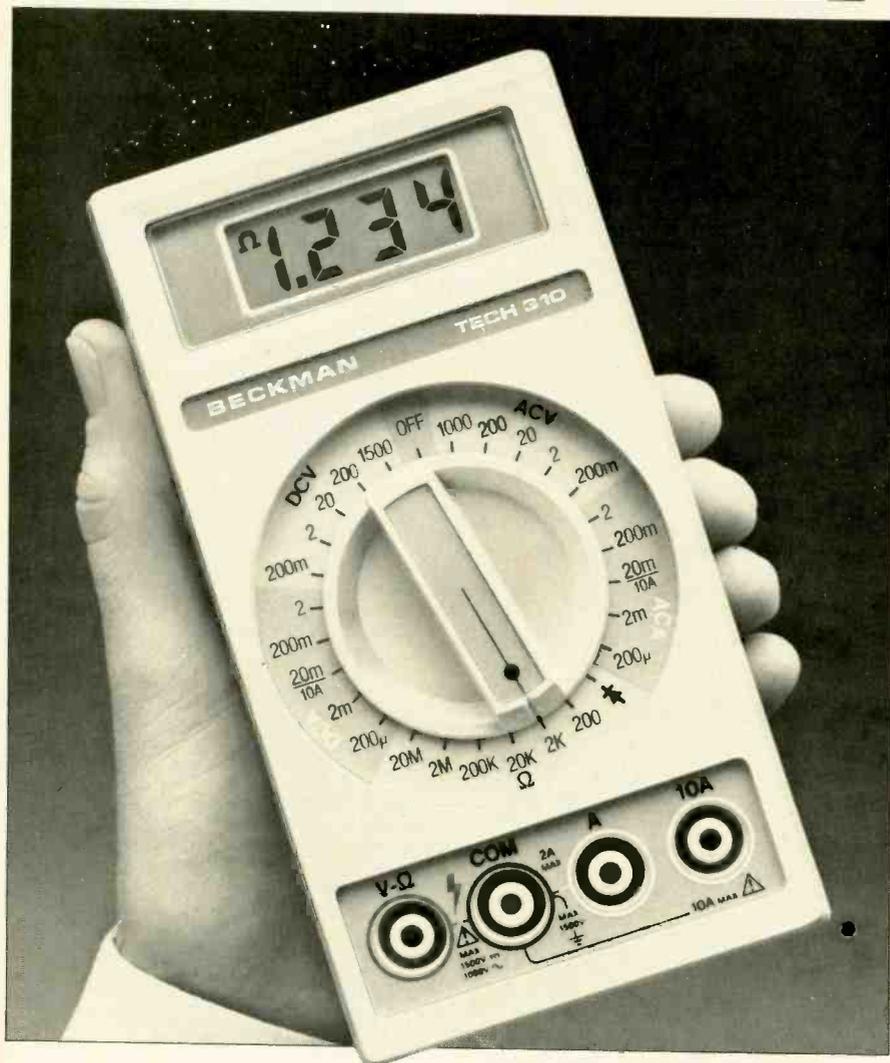

We just knocked down the last reasons for not going digital in a multimeter. Fast continuity measurement. And price.

Beckman's exclusive Insta-Ohms™ feature lets you do continuity checks as fast as the analogs. And Beckman's superior technology and experience let you own this beauty for such a reasonable price.

Of course you get a lot more. Like 7 functions and 29 ranges including 10 amp ac/dc current capability. 0.25% Vdc accuracy. In-circuit resistance measurements and diode/transistor test function. Two years' typical operation from a common 9-volt battery. In other words, all the features you want in one hand-held unit of exceptional good looks and design.

With 1500 Vdc overload protection, 100% instrument burn-in, plus rugged, impact-resistant case, you're assured of the utmost in dependability and long-term accuracy. You get a tough meter that keeps on going, no matter how tough the going gets.

So visit your dealer today and get your hands on the DMM that does it all. Or call (714) 871-4848, ext. 3651 for your nearest distributor.

BECKMAN

CIRCLE 29 ON FREE INFORMATION CARD

STATE OF SOLID STATE

continued from page 78

sion rates can be speeded up to 96 Hz by reducing the second division ratio to four.

The outputs of the discharge counters produce a binary-coded-decimal (BCD) output for each of three decimal digits. Three-digit select outputs indicate which digit is currently being multiplexed to the four BCD output leads, and are used to multiplex a display. When the input is below -99 millivolts, all BCD outputs are coded to 1010 binary (decimal 10). Analog inputs exceeding the +999-mV upper limit switch the BCD outputs to 1011 binary (decimal 11). These two codes are outside the normal 0-to-9 decimal-digit range, and can be used by the display decoder to produce distinctive out-of-range indications.

The hold terminal (see Fig. 1) doubles as the conversion-rate select pin. Biased to 2.5 volts, pin 6 halts the A/D conversion and retains the last reading. The digit multiplexer continues to exercise the three-digit driver leads sequentially so that an interfaced display continues to show the most recently converted reading. Biasing pin 6 to +5 volts increases the conversion rate to 96 Hz without changing the multiplex rate. Terminal 6 can either be left open or grounded for the slow-conversion mode.

The CA3161E IC is a BCD-to-7-segment decoder driver that converts the four outputs of the A/D converter, or any other TTL-compatible device, to seven current-source outputs to drive LED display segments. For each of the 16 logic-level combinations on the four input leads, the 7-segment output leads are activated to form specific LED displays. While there are only 10 numerals, the other six codes are letters, a dash or a blank. The particular codes that are used with the A/D IC are the 10 numerals, the dash for under-range code 1010, and the letter "E" for over-range code 1011.

The CA3161E IC contains the decoding logic and output drivers that typically supply 15 mA for each LED segment. Constant-current outputs eliminate the need for external current-limiting resistors.

Figure 2 shows a complete meter system based on the two RCA IC's. The total digit current for a decimal 8 display is typically 7×15 , or 105 mA. Three external segment-select transistors source the relatively high total currents. The digit-select outputs sink a minimum of 1.6 mA each, which is sufficient to drive PNP digit drivers. The CA3162E data sheet includes a full-scale $1\frac{1}{4} \times 3\frac{1}{8}$ -inch foil pattern for a PC board. Two potentiometers are used for gain and zero adjustment. The unadjusted zero offset is ± 12 mV, and the unadjusted gain is between 846 mV and 954 mV with a 900-mV input. The typical temperature coeffi-

cient with the ZERO potentiometer centered is 10 μ V-per-degree-C, and the gain temperature coefficient is typically 0.005%-per-degree-C with a 2.4-K GAIN potentiometer.

Some applications for the meter system include electronic weighing equipment, medical diagnostics, welding controls, electronic games, temperature measurement, power supplies, and automotive accessories.

Hundred-quantity prices for these circuits are \$1.20 for the CA3161E, and \$4.30 for the CA3162E. For additional information, write for data bulletins Nos. 1079 and 1080 from RCA Solid State Division, Box 3200, Somerville, NJ 08876. Also available is RCA's brochure 2M1215 describing the use of both devices in a three-digit readout system.

Microcomputer with A/D converter


Intel's 8022 is the first low-cost single-IC microcomputer that includes an A/D converter. Frequently, A/D conversion is required to accommodate analog inputs. Thus, combining a converter with the microprocessor is ideal for many home-appliance, test and measurement systems, automotive and process-control applications. For example, if you wanted to measure the temperature in a microprocessor-controlled microwave oven, a voltage generated in a temperature sensor would have to be digitized.

The 8-bit converter has two multiplexed input channels. Each channel is selected by software using the SEL AN0 and SEL AN1 instructions that simultaneously start the conversion process. Conversions are completed every 40 μ s, which corresponds to each of four instruction cycles. The converter is implemented in NMOS, using a successive approximation hardware approach. A separate power supply and voltage reference pins isolate the converter from power-supply noise.

The 8022 has an 8-bit central processor, 64 bytes of random-access memory (RAM), 2048 bytes of program read-only memory (ROM), and 28 input/output (I/O) lines. The I/O leads consist of three 8-bit ports, two test pins and two A/D multiplexer inputs. The 8022 is the most recent member of the MCS-48 family, which is headed by the 8048. Instruction time is 10 μ s, and the set of more than 70 instructions is a subset of the 8048's set. No instruction takes more than two clock-cycles. The IC contains an oscillator that can be used with an external crystal or clock signal, or operated with a single external timing resistor or inductor. The IC operates over a range of 4.5 volts to 6.5 volts.

Input port 0 uses comparators to correlate the inputs against the threshold reference pin. These eight inputs are used to interface with analog inputs and directly drive capacitive touch panels. One of the two test pins senses zero crossings for

BUILD A MASTERPIECE OF SOUND

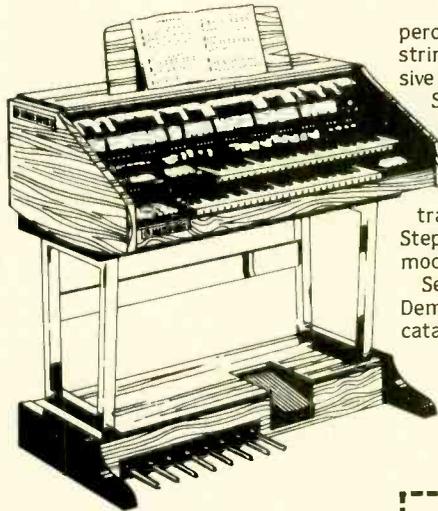

percussion and sustain. Wersi's famous string orchestra and bass guitar. Exclusive Sound Computer for 32-128 "One Stop Sounds" (total organ presets). Transposer. And lots more.

Build your own masterpiece of sound. No technical knowledge required. Just follow the clearly illustrated, easy to understand instructions. Step by step. Choose from at least 10 models. (Also factory assembled.)

Send \$6.00 with coupon for your Wersi Demo-Package (LP with 104-page color catalog).

WERSI

Wersi has combined select features of the electronic music field, added its own creations and years of research by top engineers and musicians, to produce an incomparable line of organs.


Space-age technology. True-to-life voicing with full drawbar system. Polyphonic

Wersi Electronics, Inc. or Wersi Organs & Kits
1720 Hempstead Road 14104 E. Firestone Blvd.
Lancaster, PA 17601 Santa Fe Springs, CA 90670

Enclosed is \$6.00 for my Demo-Package (LP with 104-page color catalog.)

Name _____
Address _____
City _____ State _____ Zip _____

CIRCLE 28 ON FREE INFORMATION CARD

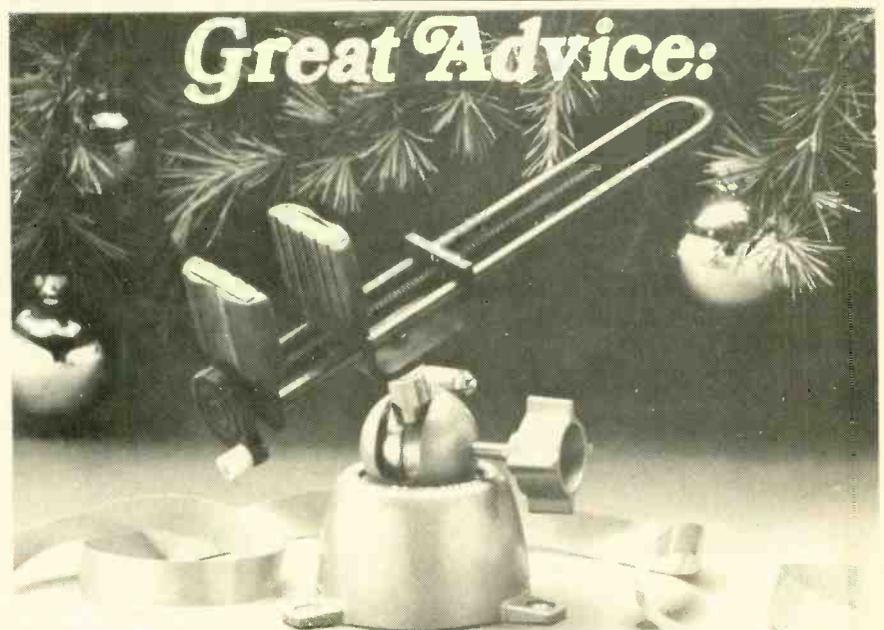

Give a Great Vise!

PanaVise ... a great gift idea. Everyone loves a PanaVise. It tilts, turns and rotates every which way to quickly and securely position electronic parts and PC boards exactly where wanted.

Sturdy all metal construction. Model 396 PanaVise shown. Available at your electronic distributors, boxed ready to go, along with a variety of other PanaVise interchangeable bases, holders and accessories.

PANA VISE® Write for FREE brochure and distributor list.
Dept. CE5, 2850 29th Street, Long Beach, CA 90806

CIRCLE 2 ON FREE INFORMATION CARD

Start Computing For Just \$129.95 With An 8085-Based Professional Computer Kit—

Explorer/85

100% compatible with all 8080A and 8085 software & development tools!

No matter what your future computing plans may be, Level "A"—at \$129.95—is your starting point.

Starting at just \$129.95 for a Level "A" operating system, you can now build the exact computer you want. Explorer/85 can be your beginner's system, OEM controller, or IBM-formatted 8" disk small business system... yet you're never forced to spend a penny for a component or feature you don't want and you can expand in small, affordable steps!

Now, for just \$129.95, you can own the first level of a fully expandable computer with professional capabilities—a computer which features the advanced Intel 8085 cpu, thereby giving you immediate access to all software and development tools that exist for both the 8085 and its 8080A predecessor (they are 100% software compatible)—a computer which features onboard S-100 bus expansion—plus instant conversion to mass storage disk memory with either 5-1/4" diskettes or standard IBM-formatted 8" disks.

For just \$129.95 (plus the cost of a power supply, keyboard/terminal and RF modulator, if you don't have them already), Explorer/85 lets you begin computing on a significant level... applying the principles discussed in leading computer magazines... developing "state of the art" computer solutions for both the industrial and leisure environment.

Level "A" Specifications

Explorer/85's Level "A" system features the advanced Intel 8085 cpu, an 8355 ROM with 2k deluxe monitor/operating system, and an 8155 ROM-I/O—all on a single motherboard with room for RAM/ROM/PROM/EPROM and S-100 expansion, plus generous prototyping space.

(Level "A" makes a perfect OEM controller for industrial applications and is available in a special Hex Version which can be programmed using the Netronics Hex Keypad/Display.)

PC Board: glass epoxy, plated through holes with solder mask

- I/O: provisions for 25-pin (DB25) connector for terminal serial I/O, which can also support a paper tape reader
- provision for 24-pin DIP socket for hex keypad/display
- cassette tape recorder input
- cassette tape recorder output
- speaker output
- LED output indicator on SOD (serial output) line
- printer interface (less drivers)
- total of four 8-bit plus one 6-bit I/O ports
- Crystal Frequency: 6.144 MHz
- Control Switches: reset and user (RST 7.5) interrupt
- additional provisions for RST 5.5, 6.5 and TRAP interrupts onboard
- Counter/Timer: programmable, 14-bit binary
- System RAM: 256 bytes located at F800, ideal for smaller systems and for use as an isolated stack area in expanded systems
- RAM expandable to 64k via S-100 bus or 4K on motherboard.

System Monitor (Terminal Version): 2k bytes of deluxe system monitor ROM located at F000 leaving 0000 free for user RAM/ROM. Features include tape load with labeling... tape dump with labeling... examine/change contents of memory... insert data... warm start... examine and change all registers... single step with register display at each break point, a debugging/training feature... go to execution address... move blocks of memory from one location to another... fill blocks of memory with a constant... display blocks of memory... automatic baud rate selection... variable display line length control (1-255 characters/line)... channelized I/O monitor routine with 8-bit parallel output for high speed printer... serial console in and console out channel so that monitor can communicate with I/O ports.

System Monitor (Hex Version): Tape load with labeling... tape dump with labeling... examine/change contents of memory... insert data... warm start... examine and change all

By Netronics



registers... single step with register display at each break point... go to execution address. Level "A" in the Hex Version makes a perfect controller for industrial applications and can be programmed using the Netronics Hex Keypad/Display.



Hex Keypad/Display.

Level "B" Specifications

Level "B" provides the S-100 signals plus buffers/drivers to support up to six S-100 bus boards and includes: address decoding for onboard 4k RAM expansion select-able in 4k blocks... address decoding for onboard 8k EPROM expansion select-able in 8k blocks... address and data bus drivers for onboard expansion... wait state generator (jumper select-able), to allow the use of slower memories... two separate 5 volt regulators.



Explorer/85 with Level "C" card cage.

Level "C" Specifications

Level "C" expands Explorer's motherboard with a card cage, allowing you to plug up to six S-100 cards directly into the motherboard. Both cage and cards are neatly contained inside Explorer's deluxe steel cabinet.

Level "C" includes a sheet metal superstructure, a 5-card gold plated S-100 extension PC board which plugs into the motherboard. Just add required number of S-100 connectors

Level "D" Specifications

Level "D" provides 4k or RAM, power supply regulation, filtering decoupling components and sockets to expand your Explorer/85 memory to 4k (plus the original 256 bytes located in the 8155A). The static RAM can be located anywhere from 0000 to EFFF in 4k blocks.

Level "E" Specifications

Level "E" adds sockets for 8k of EPROM to use the popular Intel 2716 or the TI 2516. It includes all sockets, power supply regulator, heat sink, filtering and decoupling components. Sockets may also be used for soon to be available RAM IC's (allowing for up to 12k of onboard RAM).

Order A Coordinated Explorer/85 Applications Pak!

Experimenter's Pak (SAVE \$12.50)—Buy Level "A" and Hex Keypad/Display for \$199.90 and get FREE Intel 8085 user's manual plus FREE postage & handling!

Student Pak (SAVE \$24.45)—Buy Level "A," ASCII Keyboard/Computer Terminal, and Power Supply for \$319.85 and get FREE RF Modulator plus FREE Intel 8085 user's manual plus FREE postage & handling!

Engineering Pak (SAVE \$41.00)—Buy Levels "A," "B," "C," "D," and "E" with Power Supply, ASCII Keyboard/Computer Terminal, and six S-100 Bus Connectors for \$514.75 and get 10 FREE computer grade cassette tapes plus FREE 8085 user's manual plus FREE postage & handling!

Business Pak (SAVE \$89.95)—Buy Explorer/85 Levels "A," "B," and "C" (with cabinet), Power Supply, ASCII Keyboard/Computer Terminal (with cabinet), 16k RAM, 12" Video Monitor, North Star 5-1/4" Disk Drive (includes North Star BASIC) with power supply and cabinet, all for just \$1599.40 and get 10 FREE 5-1/4" minidiskettes (\$49.95 value) plus FREE 8085 user's manual plus FREE postage & handling!

Continental U.S.A. Credit Card Buyers Outside Connecticut
CALL TOLL FREE 800-243-7428

To Order From Connecticut Or For Technical Assistance, Etc. Call (203) 354-9375

Netronics R&D Ltd., Dept. RE-12

333 Litchfield Road, New Milford, CT 06776

Please send the items checked below—

- Explorer/85 Level "A" Kit (ASCII Version), \$129.95 plus \$3 p&h.
- Explorer/85 Level "A" Kit (Hex Version), \$129.95 plus \$3 p&h.
- 8k Microsoft BASIC on cassette tape, \$64.95 postpaid.
- 8k Microsoft BASIC in ROM Kit (requires Levels "B," "D," and "E"), \$99.95 plus \$2 p&h.
- Level "B" (S-100) Kit, \$49.95 plus \$2 p&h.
- Level "C" (S-100 6-card expander) Kit, \$39.95 plus \$2 p&h.
- Level "D" (4k RAM) Kit, \$69.95 plus \$2 p&h.
- Level "E" (EPROM/ROM) Kit, \$5.95 plus 50¢ p&h.
- Deluxe Steel Cabinet for Explorer/85, \$49.95 plus \$3 p&h.
- ASCII Keyboard/Computer Terminal Kit (features a full 128 character set, upper & lower case, full cursor control, 75 ohm video output convertible to baudot output, selectable baud rate, RS232-C or 20 ma. I/O, 32 or 64 character by 16 line formats, and can be used with either a CRT monitor or a TV set (if you have an RF modulator), \$149.95 plus \$2.50 p&h.
- Hex Keypad/Display Kit, \$69.95 plus \$2 p&h.
- Deluxe Steel Cabinet for ASCII Keyboard/Terminal, \$19.95 plus \$2.50 p&h.
- Power Supply Kit (± 8V @ 5 amps) in deluxe steel cabinet, \$39.95 plus \$2 p&h.
- Gold Plated S-100 Bus Connectors, \$4.85 each, postpaid.
- RF Modulator Kit (allows you to use your TV set as a monitor), \$8.95 postpaid.
- 16k RAM Kit (S-100 Board expands to 64k), \$199.95 plus \$2 p&h.
- 32k RAM Kit, \$329.95 plus \$2 p&h.
- 48k RAM Kit, \$459.95 plus \$2 p&h.
- 64k RAM Kit, \$589.95 plus \$2 p&h.
- 16k RAM Expansion Kit (to expand any of the above up to 64k), \$139.95 plus \$2 p&h each.
- Intel 8085 cpu User's Manual, \$7.50 postpaid.
- Special Computer Grade Cassette Tapes, \$1.90 each or 3 for \$5, postpaid.
- 12" Video Monitor (10 MHz bandwidth), \$139.95 plus \$5 p&h.
- North Star Double Density Floppy Disk Kit (One Drive) for Explorer/85 (includes 3 drive S-100 controller, DOS, and extended BASIC with per-

sonalized disk operating system—just plug it in and you're up and running!), \$699.95 plus \$5 p&h.

Power Supply Kit for North Star Disk Drive, \$39.95 plus \$2 p&h.

Deluxe Case for North Star Disk Drive, \$39.95 plus \$2 p&h.

Experimenter's Pak (see above), \$199.90 postpaid.

Student Pak (see above), \$319.85 postpaid.

Engineering Pak (see above), \$514.75 postpaid.

Business Pak (see above), \$1599.40 postpaid.

Total Enclosed \$ (Conn. res. add sales tax) By—

Personal Check M.O./Cashier's Check Visa Master Charge

(Bank # _____)

Acct. # _____ Exp. Date _____

Signature _____ Print Name _____

Address _____

City _____

State _____ Zip _____

Send Me Information

STATE OF SOLID STATE

continued from page 81

timing applications; by counting power-line zero crossings, you can create a time-of-day clock. Two of the No. 1 port output lines each drive 7-mA loads, or (when paralleled) one 14-mA load such as an LED.

The 8022 has full MCS-48 support, including Intel's *Intellec* Microcomputer Development System. The new EM-2 emulator board uses an Intel 2K EPROM (Erasable Programmable Read-Only Memory) for program development. Intel Corporation, 3065 Bowers Avenue, Santa Clara, CA 95051.

CRT controller

A combined-technology IC developed by National Semiconductor simplifies video-terminal design. Large blocks of discrete logic are replaced by the DP8350 CRT controller that uses a combination of I²L (Integrated Injection Logic), low-power Schottky process and linear components.

The DP8350 contains an oscillator, a timing function, CRT refresh logic and video-control circuits. On-chip functions take the place of as many as 30 to 40 MSI, SSI and discrete devices. Compared with other LSI controllers, component count is reduced by three to five times. The advantage lies in the IC's built-in high-speed logic. Other MOS LSI controllers do not implement the high-speed logic functions; thus, additional external components must be used.

The DP8350 displays 5 × 7 dot matrix characters in a 7 × 10 field, with 24 lines of 80 characters each. Refresh frequencies of 50 Hz and 60 Hz produce 312 and 260 lines-per-frame, respectively. Horizontal scan frequency is 15.6 kHz.

An 11-line bus provides video and system outputs, including horizontal and vertical synchronization, vertical blanking, cursor enable, and character-generation control signals. It also accommodates external blinking, blanking, intensity control and underline inputs.

The DP8350 is also available in mask-programmed format to user specifications. The on-chip ROM can be factory-modified for field sizes of up to 16 × 16 dot matrix. The character-set elements can also be customized to provide from 5 to 110 characters-per-row and between 1 and 64 rows. The horizontal and vertical synchronization width, front- and back-porch widths, cursor-enable output and vertical-blanking outputs can also be programmed.

The standard and semicustom versions of the DP8350 operate from a single 5-volt power supply and draws 150 mA. The device is available in small quantities, with a suggested price of \$49. National Semiconductor, 2900 Semiconductor Drive, Santa Clara, CA 95051.

Many symptoms can be the result of blanking problems.

JACK DARR, SERVICE EDITOR

THE OLDEST TV SETS HAD BLANKING CIRCUITS to keep the horizontal and vertical sync from getting into the picture. The blanking circuit feeds a voltage pulse to the picture tube to cause it to cut off. Now we use several different forms of blanking, for many things. We still have blanking problems, but now they can be more complicated. If the symptom is recognized as being a blanking problem, the diagnosis can be much faster.

The simplest blanking problem is the familiar hum-bars. With one horizontal bar visible, the cause is a 60-Hz signal; with two bars visible, the cause is a 120-Hz signal from the full-wave rectified power supplies. The problem is almost always the same: bad filter capacitors that allow excess ripple voltage on the DC supply. The voltage variation causes the B+ to fluctuate and the peaks of this blank the raster, fully or partially.

Another symptom is the horizontal bar that floats up through the picture. The bar may be dark or light. What now? Check the vertical sweep! In tube sets, and often in solid-state TV models, the vertical output stage draws a large pulse of current once each field. If this pulse is not filtered properly, it will cause ripple on the B+ line that in turn partially blanks the picture. Since the power supply ripple is 60 Hz and the vertical sweep actually 59.94 Hz, there is just a small phase difference. This is what makes the bar float up through the picture. To verify this, scope the B+ ripple at the filter output. The normal waveform is a kind of sawtooth. If you can see an extra ripple that makes the waveform "writhe" and change, this is the signal from the vertical sweep getting into things. The cure is more filtering. In some sets, the original design simply wasn't filtered enough. If so, just add more capacitance. In some sets I've added as much as 100 μ F of extra capacitance before the bar went away. Figure 1 shows the odd ripple waveform.

The type of fault and the screen symptoms give us the clue to what frequency is causing it. Horizontal bars, vertical frequency. Vertical bars, horizontal frequency. The classic example of this is the "jail-bars" symptom. The screen shows 5 or 6 black vertical bars, evenly spaced. Between the bars, a normal color picture can be seen.

This is caused by a shorted diode in the horizontal blanking circuit. It feeds a clipped pulse from the flyback into the 1st video amplifier stage. A normal pulse has a tall thin spike (the blanking pulse) and a "baseline" (the horizontal part of the waveform, or scan time). The waveform is shown in Fig. 2. Note that there are 5 or 6 cycles of ringing on this waveform. The ringing is normal. In normal operation, the diode is biased so that the ringing is clipped. If the diode shorts, the whole thing goes sailing on through and the ringing on the baseline blanks the raster. You can confirm this with the scope on the output of the diode.

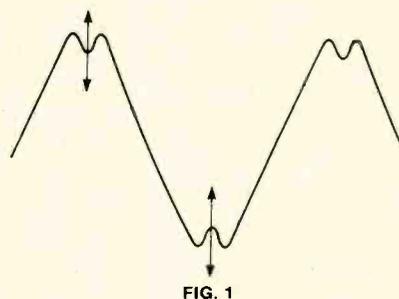


FIG. 1

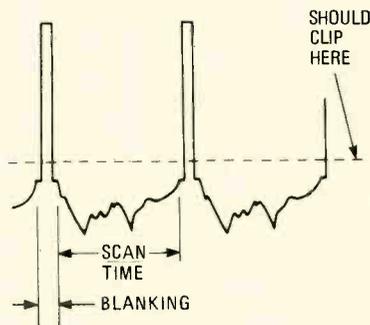


FIG. 2

Other odd blanking problems can be found in the horizontal blanking circuits. For one, if the raster seems to be 1-2 inches narrow on the left, turn the set to a dead channel and see if you can get a full raster. If you do, this can be a horizontal blanking problem. Feed in a color-bar signal and see how many bars are visible. If this is a color TV, and the raster starts with the red bar (3d from left) it is a blanking problem. It may or may not be in the horizontal blanking circuit itself. Scope the output of the horizontal blanking circuit and see if the blanking pulse is

of the correct width; something like 15-18 microseconds duration. If so, the blanking circuit is OK. Something is feeding a horizontal pulse into the video circuit that is much wider than it ought to be. Look for this pulse at points where it could be coupled into the video circuit from leakage, stray capacitance, coupling between leads, etc.

A similar case can be found where normal colors appear on only one half of the screen, and a B/W picture on the rest. Something is blanking out the color signal. The scope should show you this pulse and you can trace it back to find where it gets in. This symptom can be due to a bad bypass capacitor. Scope the top end of each bypass capacitor in the color circuits. If you see any *signal*, this capacitor is not doing its job. (If the capacitor checks "good", try changing the *ground-point!* I've seen this one happen.)


The reverse!

Up to now, we've been saying "blanking" in the sense that part of the picture/raster has been blacked out. As usual, we have the reverse symptom. This symptom showed up in one Sears chassis. The raster was very light; on the left 1/4 of the screen, there was very weak video, looking as if the picture tube was almost dead. The rest of the screen was completely whited out. This was obviously some kind of horizontal symptom. (Things to make a note of: In modern sets with flyback-derived low voltage power supplies, "ripple" will be at the *horizontal* frequency!) Checking the schematic showed two DC voltage sources from the flyback into the video IF-preamp IC. The scope showed these supply lines to be clean. However, we found that the video output stage was fed from a +166-volt DC source also from the flyback. Replacing the 2.2 μ F filter capacitor on this cleared up the problem. Here, we had a typical blanking problem but the polarity of the symptom was reversed so that the screen was being over-driven and simply wiping out the video signal.

Finally, don't be surprised at any symptom. We ran across a TS-938 Quasar; the picture looked like something out of a horror movie! Raster was small and there was a black "blob" coming down from the top. Here again, the cause was a filter capacitor. Not an open one this time; the 500 μ F electrolytic under the power supply chassis had broken loose

continued on page 84

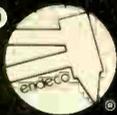9 reasons why the real pros prefer Endeco desoldering irons



1. Operates at 120v, 40w. Idles at 20w for longer tip life
2. Flexible, burn resistant Neoprene cord set
3. Cool, unbreakable polycarbonate handle
4. Exclusive bracket insures alignment, prevents damage
5. Safety light in handle tells when it's on
6. Stainless steel construction
7. Temperature control. Low, high or off.
8. Eight tip sizes. Comes with .063 I.D.
9. Converts to soldering iron with 1/4" shank type tip

See your distributor or write . . .

Enterprise Development Corp.

5127 E. 65th St. • Indianapolis IN 46220
PHONE (317) 251-1231

CIRCLE 50 ON FREE INFORMATION CARD

SERVICE CLINIC

continued from page 83

from its ground connection.

Needless to say, this doesn't cover all of the possibilities. The general term "blanking problem" can be of many types. However, if you look closely at the screen and see that the main problem is blanking or brightening of a part of the raster, start looking for stray pulses floating around where they shouldn't be. The scope is an essential weapon in this. Use it intelligently and your troubles will be much smaller!

R-E

service questions

BRIGHTNESS SOLUTION

Donald F. Morin, general manager, Spaceport TV, Cocoa Beach, FL, has another idea about the Sony model KV-1910 raster problem described in the January 1979 issue.

He writes: "Your response was close but not the cure! Tell 'D.L.' that if he changes capacitor C707 (4.7 μ F on the CRT's PC board) this will cure the screen brightness problem. If C707 is open, flyback pulses go through the +199-volt line to the CRT cathodes."

That sounds very much like Mr. Batis' solution, except that Mr. Morin pinpoints the exact part. Many thanks, everyone, for letting us in on the data. I've already filed it, and everybody else should, too. It's always good to get genuine field feedback.

BAD FOCUS RECTIFIER

I have an unknown Japanese TV color set that has a bad focus rectifier tube. This is a real oddball part, and I can't find a substitute anywhere. Can I use a solid-state focus rectifier for it?—J.M., Baldwin, NY.


Yes, you can! The solid-state focus rectifiers can be used instead of any of the focus rectifier tubes. The only problem you may have is in mounting. Try putting the solid-state unit on a couple of terminal strips, wherever there's room for it. Just watch out for possible arcing to the cage; if there's enough clearance, this should do the trick.

HIGH VOLTAGE BOOST

Here's an odd one. This Motorola model TS-594 has too much high voltage and boost! It has good sound and a fair picture (although it could focus better). The high voltage reads 23 kV (it should be 17.5 kV) and the boost reads 560 volts. (it should be +470 volts). The 6JN6 voltages all look OK and there's plenty of grid

continued on page 86

This chip changed your life.

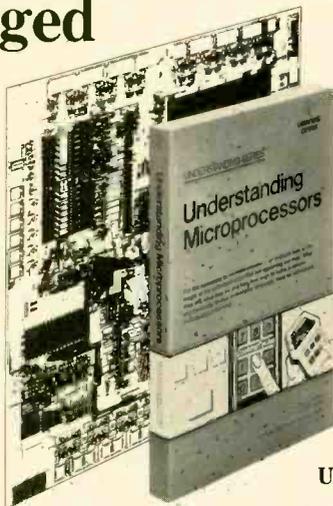

This book tells you how. And why.

Understanding Microprocessors. From the Texas Instruments Learning Center. 288 pages. \$4.95.


Learn quickly and easily about the explosive impact microprocessors have had on electronics technology.

How the "miracle chip" works to make those things you use everyday—calculators, appliances, microwave ovens, stereos, tv, automobiles—even toys and games—do the remarkable things they do.

Understanding Microprocessors is the latest addition to the Texas Instruments Understanding Series™.

All TI Understanding Series books are ideal for those who want to learn about today's technology—without having to devote years to the study.

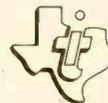Written in bright, clear, down-to-earth language, and fully illustrated, you'll find these books to be invaluable tools for your personal entry into the microelectronics revolution. See coupon for all details.



- LCW8161 **Basic Electricity and DC Circuits** \$19.95
1026 pages. Building blocks for a thorough working knowledge of DC circuits.
- LCB3361 **Understanding Solid-State Electronics** \$3.95
270 pages—New 3rd edition. Individualized approach for learning microelectronic basics.
- LCB3311 **Understanding Digital Electronics** \$3.95
265 pages. The springboard for a look into the fascinating world of today's electronic logic devices, circuits and systems.
- LCB4023 **Understanding Microprocessors** \$4.95
288 pages. For the newcomer to microprocessors. What they are, what they do and how they work.
- LCB3321 **Understanding Calculator Math** \$3.95
224 pages. Unlocks the real power of your handheld calculator—loaded with practical applications.

Add sales tax, except AK, DE, MT, NH, OR.

Mail check or money order to Texas Instruments, P.O. Box 3640, M/S 84, Dallas, Texas 75285.

Orders in Continental U.S. shipped prepaid. Foreign orders: Prepaid in U.S. dollars only. Include shipping costs.

Prices subject to change without notice.


RE-1279

Name _____

Address _____

City _____ State _____ Zip _____

TEXAS INSTRUMENTS
INCORPORATED

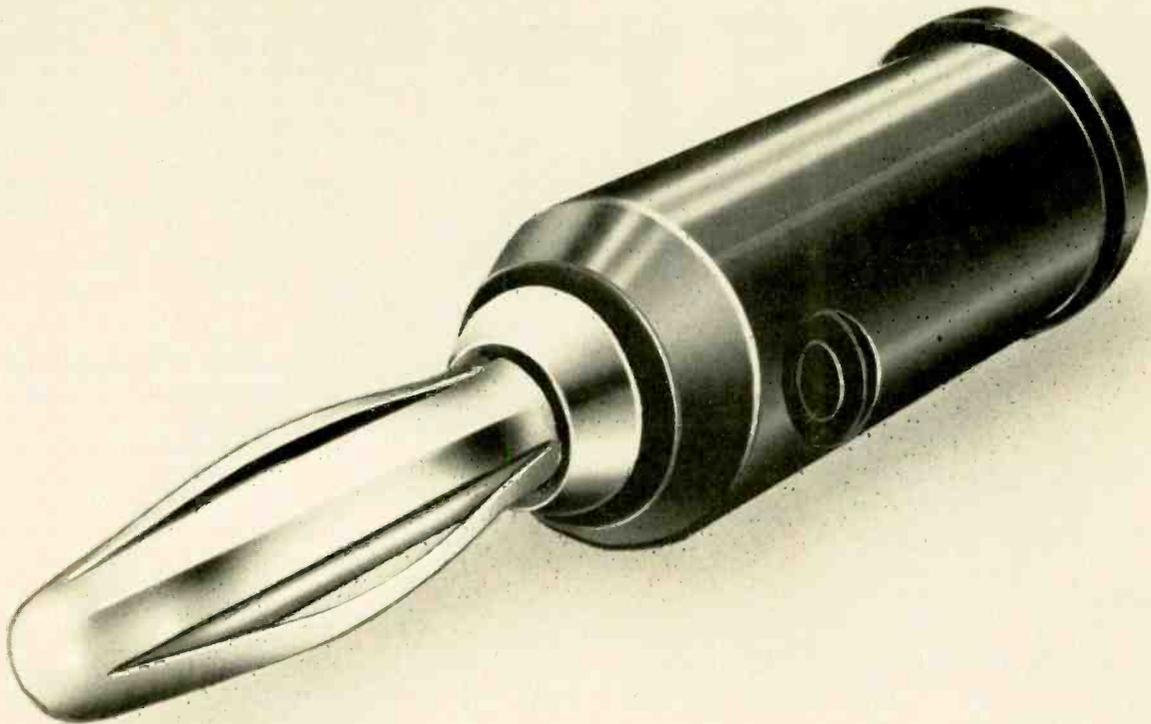

TOP BANANA SINCE 1951.

In 1951, our faith in the future was a lot bigger than our finances. We started with less than \$1,000 in a "factory" smaller than a 2-car garage.

But there was one thing we thought we could do better than anybody — design and make banana plugs. A lot of people agreed, and we prospered.

As time went by, we improved upon our own pioneering work. Pomona Electronics became synonymous with quality banana plugs.

FREE 1979 YEARBOOK CATALOG

Contains 100 pages of adapters, cable assemblies, jacks, plugs, boxes, sockets, connectors, jumpers, clips, probes, patch cords, wire, and much more. Yours free upon request. See our pages in EEM.



Today, we're still the top banana. And we manufacture more than 640 other top quality products industry professionals know and trust.

We even have a big factory, now that we're a division of prestigious International Telephone and Telegraph Corporation.

Most important, ITT Pomona Electronics hasn't forgotten the ideals that helped create great banana plugs.

Because we don't ever want to become just one of the "bunch," ITT Pomona Electronics, 1500 East Ninth Street, Pomona, CA 91766 • Phone: (714) 623-3463 • TWX: 910-581-3822

AVAILABLE THROUGH YOUR FAVORITE
ELECTRONIC PARTS DISTRIBUTOR

Pomona Electronics **ITT**

CIRCLE 10 ON FREE INFORMATION CARD


NEW FROM PTS

HIGH CURRENT POWER SUPPLIES



DG-2 Regulated Digital Power Supply/Digital Voltmeter.

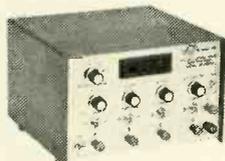Single source regulated high current supply with 200V voltmeter for internal and external voltage measurement.




DG-5 Regulated Voltage Control Center/Digital Voltmeter.

Same high current features as DG-2 plus four independent, variable DC supply voltages. Includes 200V voltmeter for internal and external voltage measurement.



MSP-501 Regulated Microprocessor Power Supply.

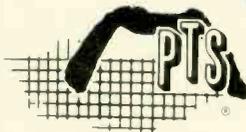Supply preset to 5 VDC. Adjustable from 4.5 VDC-6.0 VDC. 5 amp.



PTS ELECTRONICS, INC.

The Only Name You Need To Know

P.O. BOX 272, BLOOMINGTON, IN 47402

See the Yellow Pages for the PTS stocking distributor or Tuner/Module Servicenter nearest you.

CIRCLE 65 ON FREE INFORMATION CARD

SERVICE QUESTIONS

continued from page 84

drive. How can I get the high voltage and boost down to the right level?—R. S., Johnson City, TN.

Some time ago a reader in New Mexico and I worked on a similar problem in an RCA set. Like the Motorola you describe, all the voltages were OK. Finally, he *reduced* the screen grid voltage on the horizontal-output tube. This worked! You could try bringing this voltage down until you start to lose width. I think you'll find that the 6JN6 cathode current will come down with it. This is kind of a "quick-and-dirty" fix but it seems to work.

GROUND SPRING ARCING

In this RCA model CTC-43, the ground spring arcs continuously to the aquadag coating of the picture tube. I ran into this problem before but I forget what I did to fix it!—L.H., Bergenfield, NJ.

I do. You've got a very poor contact between the ground spring and the dag coating of the tube. Just get a small bottle of graphite coating from your local radio-tv supply house. Paint the whole length of the spring with the coating and move it back and forth to make sure you cover it well. This should do it.

RECHECKS HELP

I just want you to know I checked the things you suggested in the GE C-2 chassis with a horizontal-sync problem. I was about ready to give up, then I checked the 39K resistor R251 in the plate circuit of the horizontal AFC tube. I was sure I'd checked it before. But it was open! A new resistor fixed it.—R.R., Pottstown, PA.

Moral: Never be afraid to go back and recheck. Especially if your memory isn't any better than mine!


VCR "FLAG-WAVING"

We've received a couple of letters on the subject of "flag-waving" in TV receivers used with VCR's or VTR's. This old term means there's an instability of horizontal sync that causes the vertical lines near the top of the picture to jitter and bend sideways. I must admit I don't know very much about VCR's, but fortunately some readers do!

Maurice R. Brice of San Mateo, CA, found that it helps to change the value of the grid-to-ground capacitor in the horizontal AFC stage. This is a "cut and try" process, but it can be done with a capacitor substitute box or by trying various capacitor values. He also sent along a note from an RCA manual that states: "Instability in TV sets with an unstable picture from VTR/VCR may be due to long time-constant in the horizontal AFC of the set." This, of course, depends on the capacitor and resistor values in this circuit. A bit of experimenting may help if you run into this problem. R-E

This is easy- anyone can solder- WITH KESTER SOLDER

**KESTER
SOLDER**

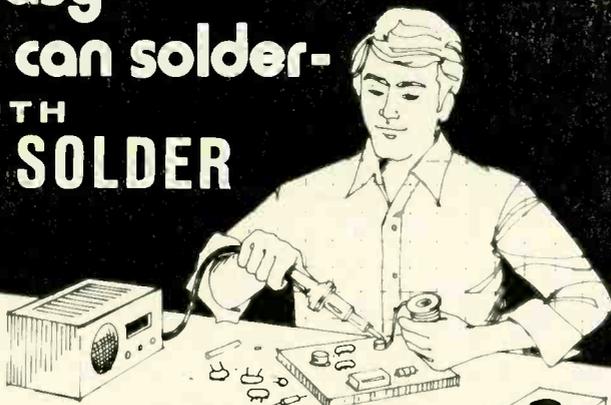

Handymen! Hobbyists! DO-IT-YOURSELFERS!

Let Kester Solder aid you in your home repairs or hobbies. For that household item that needs repairing — a radio, TV, model train, jewelry, appliances, minor electrical repairs, plumbing, etc. — Save money — repair it yourself. Soldering with Kester is a simple, inexpensive way to permanently join two metals.

When you Solder go "First Class" — use Kester Solder.

For valuable soldering information send self-addressed stamped envelope to Kester for a FREE Copy of "Soldering Simplified".



KESTER SOLDER

Litton 4201 WRIGHTWOOD AVENUE/CHICAGO, ILLINOIS 60639

CIRCLE 24 ON FREE INFORMATION CARD

See how easy it is to build your own electronics – and how much you save!



Packed with new kits for gift giving

Even if you've never built anything before, Heath's famous easy-to-follow instructions assure you of success. Besides the pride of doing it yourself, electronics kits from Heath save you money when you build...and in upkeep. If technical assistance is needed, it's a phone call away at the Heath factory, or at 55 sales and service locations* nationwide.

Something for everyone in the Heathkit catalog!

- Energy conservation • Computers • Stereo systems • Electronics test instruments • Home security • Amateur radio • Family health • Treasure hunting • Color television • Weather • Aeronautics • Education • Automotive • Short wave listening • Radio control modeling • Marine

If coupon is missing, write:
Heath Company, Dept. 020-600
Benton Harbor, MI 49022

*Heathkit products are displayed, sold and serviced nationwide at Heathkit Electronics Centers (Units of Schlumberger Products Corporation) listed in the white pages of your phone book.


Send for the big, all-new

FREE

HEATHKIT® CATALOG

The colorful 104-page Heathkit catalog describes nearly 400 exciting and useful electronics kits you can build yourself. Send for your free copy now!

NEW! Giant-screen Projection Television

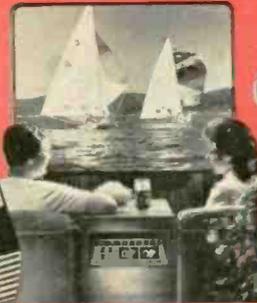

Simulated TV Picture



NEW! All-in-One Computer for hobby or business



NEW! Pinball fun for the entire family to enjoy

NEW! Portable solid-state VOM for field tests



NEW! Dual VHF Wattmeter for the Ham



NEW! State-of-the-art AM/FM Stereo Receiver

NEW! Digital Darkroom Timer for the photo buff



Heathkit

Heath Company, Dept. 020-600
Benton Harbor, MI 49022

Please send me my FREE Heathkit Catalog.
I am not currently receiving your catalogs.

Name _____

Address _____

City _____ State _____

CL-722 _____ Zip _____

FREE CATALOG

CIRCLE 100 ON FREE INFORMATION CARD

stereo products

More information on stereo products is available from manufacturers of items identified by a Free Information number. Free Information Card is inside the back cover.

DIRECT-DRIVE TURNTABLE, model 1750DD, is a quartz-controlled, two-speed direct-drive turn-




CIRCLE 131 ON FREE INFORMATION CARD

table that provides resonance-free performance. A pickup arm is not included but the unit is com-

patible with many arms. Other turntable features include PLL circuitry, electronic speed and pitch controls, digital speed display, aluminum platter and hinged dust cover. Suggested retail price: \$179.95.—**ADC Professional Products Group**, BSR (USA) Ltd., Route 303, Blauvelt, NY 10913.

MINIATURE STEREO SPEAKERS, *Mini-Mesa 15* and *Mini-Mesa 50*. The *Mini-Mesa 15* speakers (shown) are designed for both mobile and base installation and measure 3 1/4" W x 6 H x 3 inches D. The system provides a frequency response of 60 Hz–20 kHz ± 6 dB, with a peak power rating of 30 watts-per-channel, 15 watts RMS. Speakers come packaged two per kit with brackets, cable and instructions. The *Mini-Mesa 50* three-way speakers feature a 5-inch-diameter foam woofer with ferrite magnet; a 1.25-inch aluminum bobbin voice coil; a 25-mm by 12-mm horn-type tweeter; and a 3-inch midrange driver. The system has a power rating of 50 watts RMS per channel with 80 watts peak, and a frequency response of 50 Hz–20 kHz. The speakers measure 6 W x 9 1/4 H x 4 3/4 inches D, weigh 6 lb., and have a walnut

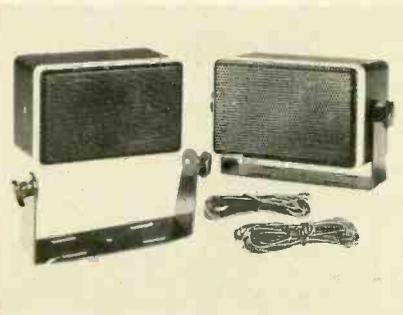

CIRCLE 132 ON FREE INFORMATION CARD

vinyl veneer and black grille cloth.

Also available are the *Mini-Mesa 30* two-way stereo system and the *Mini-Mesa Bass Booster*, a 5 1/4-inch-round bass extender designed for automotive installation. Suggested retail prices: the *Mini-Mesa 15* system, \$129.95 per pair; the *Mini-Mesa 50* speakers, \$150 each; *Mini-Mesa Bass Booster*, \$49.95 per pair; *Mini-Mesa 30* speakers, \$238 per pair.—**Mesa Electronics Sales Ltd.**, 2940 Malmo Drive, Arlington Heights, IL 60005.

PEAK-RESPONDING LED DISPLAY, model 510, is a combined peak-power indicator and line-level monitor that provides 16 red LED's-per-chan-

BSR SYSTEM X-10™ REMOTE CONTROL for Lights & Appliances

- No wires: plug-in operation
- Microprocessor based design
- Built-in keyboard control
- Central Command Console (standard)
- Wireless ultrasonic command system (deluxe)
- Electronic Security & convenience at your fingertips.



4 Pc Standard Starter Kit - One (1) Standard Command Console • Two (2) Lamp Modules • One (1) Appliance Module
Reg. \$87.95 ... **OUR PRICE \$79.50**

5 Pc Ultrasonic Starter Kit - One (1) Deluxe Ultrasonic Command Console • One (1) Hand Held Remote Unit • Two (2) Lamp Modules • One (1) Appliance Unit
Reg. \$112.95 ... **OUR PRICE \$99.95**

Lamp Modules Reg \$16 ... **OUR PRICE \$14.95**

Appliance Modules Reg \$16 ... **OUR PRICE \$14.95**

Wall Switch Modules Reg \$16 ... **OUR PRICE \$14.95**

Standard Command Console Reg \$39.95 ... **OUR PRICE \$36.95**

Ultrasonic Command Console

with Hand Held Remote Reg \$65.00 ... **OUR PRICE \$59.95**


FORDHAM

Call TOLL FREE (800) 645-9518

In N.Y. State call (516) 752-0050

855 Conklin Street
Farmingdale, New York 11735
MasterCharge • VISA • Check
• Money Order • COD
Add \$3.00 for shipping and insurance • COD's extra N.Y. Res. add sales tax

AUTO best buys STEREO

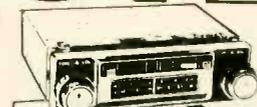

In-Dash 8-Track Stereo Player with AM/FM MPX Radio

- Push button eject

Model C777
\$52.50



In-Dash Cassette Stereo Player with AM/FM MPX Radio

- Push button eject

Model CAS 888
\$57.50



In-Dash Auto Reverse Cassette Stereo Player with AM/FM MPX Radio

- Fast forward rewind
- Push button eject

Model CAS 999
\$79.95

Stereo Power Booster
Model POW-40
• 40 Watts Stereo • 20 Watts/Channel
\$24.95



Miniature High Fidelity Stereo Speaker System



6" x 9" 3-Way Speaker

\$14.95 ea.

Model BP 2000-69TR

- 20 oz ceramic magnet
- Freq Response: 60-18000 Hz
- Peak Watts: 25W
- Impedance: 8 ohms



3-Way
Reg \$139.00

\$69.50
Per Pr with brackets

FORDHAM


Call TOLL FREE (800) 645-9518

In N.Y. State call (516) 752-0050

MasterCharge • Bank Americard
• COD • Check • Money Order
Add \$3.00 for shipping and insurance
COD's Extra New York State residents add approx. sales tax

855 Conklin St Farmingdale, N.Y. 11735

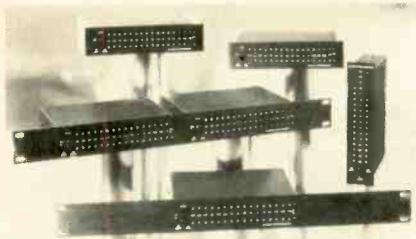
nel covering a -39 dB to +6 dB range with an amber LED at "0 dB" indication. Used in the power mode, the *model 510* helps prevent clipping; rear-panel switches are used to set the 0-dB reference level to 25, 50 or 100 watts and to match



CIRCLE 133 ON FREE INFORMATION CARD

4-, 8- or 16-ohm impedances. The unit includes a calibration feature for channel balance. Also available is the *model 510B* with green LED's indicating the range from -39 dB to -1 dB, and amber LED for "0 dB" and red LED's for the range from +1 dB to +6 dB. Four interchangeable front panels allow horizontal or vertical use and permit two displays to be rack-mounted. The unit measures 7 1/2 x 1 1/4 x 5 1/2 inches. Suggested retail prices: the *model 510*, \$139.95; *model 510B*, \$149.95; vertical panel, \$6.95; oak end panels, \$7.95 per pair; rack-mount panels, \$11.95 and \$13.95; and mounting clips, \$3.95 per pair.—**Audio Technology**, 1169 Tower Rd., Schaumburg, IL 60195.

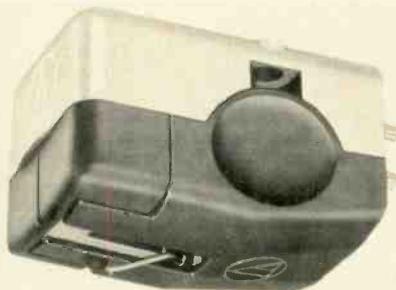
MOVING-MAGNET PHONO CARTRIDGE, model TK3E, has a tubular cantilever and a 0.3 x 0.7-mil elliptical nude-mounted diamond stylus. The cartridge also accepts many optional stylus assemblies—carbon fiber, beryllium, titanium and boron cantilevers—with conical, elliptical or Shi-



CIRCLE 134 ON FREE INFORMATION CARD

bata styluses. Suggested retail price, \$55.—**Signal**, Div. A-T U.S., Inc., 33 Shiawassee Ave., Fairlawn, OH 44313.

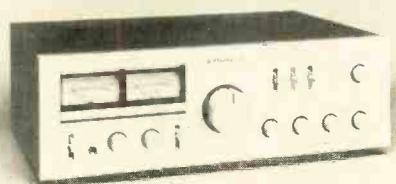DC POWER AMPLIFIERS, models KA-907, KA-801, KA-701, provide fast risetimes and slew rates. The specifications for the three DC integrated amplifiers are as follows: The *model KA-907* delivers 150 watts-per-channel into 8 ohms



CIRCLE 135 ON FREE INFORMATION CARD

minimum RMS, 20 Hz-20 kHz, -0.01% THD; risetime, 0.8 μs and slew rate, ±230V per μs. The *model KA-801* (shown) has a power output of 100 watts-per-channel minimum RMS into 8 ohms, 20 Hz-20 kHz, -0.15% THD; risetime, 0.8 μs and slew rate, ±150V per μs. The *model KA-701*

delivers 80 watts-per-channel minimum RMS into 8 ohms, 20 Hz-20 kHz, -0.02% THD; risetime, 0.9 μs and slew rate, ±120V per μs. Suggested retail prices: the *KA-907*, \$1000; the *KA-801*, \$600; the *KA-701*, \$499.—**Kenwood Electronics, Inc.**, 1315 E. Watsoncenter Rd., Carson, CA 90745.

AM/FM STEREO TUNER, model TU-919, incorporates a quartz-crystal reference oscillator to lock in stations, a dual-bandwidth IF section for both FM and AM and features 4-digit frequency readout along with center-channel tuning and VU meters. Front-panel controls include POWER on-off switch, AM/FM bandwidth selection switches, muting switch, filter switch, selector switch and output level control. Specifications include: IHF sensitivity, 8.7 dBf (1.5 μV); 50-dB quieting at 12.5 dB; distortion, 0.03%, mono, 0.05%, stereo; signal-to-noise ratio, 86 dB; and capture ratio, 0.8 dB. The *model TU-919* is housed in a matte black



CIRCLE 136 ON FREE INFORMATION CARD

cabinet with detachable rack-mounting handles. Suggested retail price: \$585.—**Sansui Electronics Corp.**, 1250 Valley Brook Ave., Lyndhurst, NJ 07071. **R-E**

International's 6024B 40 Channel CB Frequency Meter

- Power Meter
- Signal Generator
- Secondary Frequency Standard

Complete with connecting cable, dummy load, rechargeable battery and charger.

\$448³⁷

Cat. No. 035311

The 6024B provides three test instruments in one convenient case for professional servicing on all makes of Citizens Radio transceivers.

1. Secondary Frequency Standard, range 26.965 to 27.405 MHz, including the newly authorized frequencies 27.235 to 27.405 MHz. Plus a counter circuit, zero to 2500 Hz.
2. Signal Generator 26.965 to 27.405 MHz.
3. Dummy Load/Power Meter, up to 5 watts.



International Crystals are available from 70 KHz to 160 MHz.

Write for information.
ICM
M/S Dept. P.O. Box 32497
Oklahoma City, Okla. 73132



INTERNATIONAL CRYSTAL MFG. CO., INC.
10 North Lee / Oklahoma City, Okla. 73102

CIRCLE 19 ON FREE INFORMATION CARD

BIG 2½"
DISPLAY!

12:59:46

**SOLID STATE
CLOCK/CALENDAR KIT**

0101 Displays time of day, date or alternate between both automatically. May be connected to 8 ohm speaker for alarm clock. Operates from 120 VAC 60 Hz.

\$49.95 Walnut case extra, \$24.95

AUTO CLOCK CALENDAR KIT




0106 Displays either hours and minutes, month and day, or seconds. Requires only 2 mA of current while ignition is off. Also operates on 9V battery. Mounts easily in compact two-inch enclosure (Not included)

\$29.95
\$39.95 assembled

**UNIVERSAL
DESIGNER
KIT**

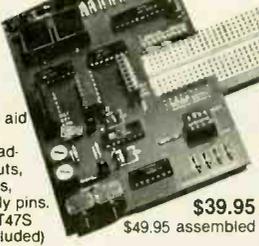6100 Indispensable aid to digital IC design. 2 pushbuttons, 2 readouts, 4 switch outputs, 8 LEDs, 2 generators, 2 counters, 5V supply pins. Shown with CSC QT47S Breadboard (not included)



\$39.95
\$49.95 assembled



SEND FOR FREE 8-PAGE CATALOG

Add \$2.50 per order postage and handling.



PACCOM

14905 N.E. 40th Street, R-12
Redmond, WA 98052 (206) 883-9200

CIRCLE 62 ON FREE INFORMATION CARD

FREE SWTH

CATALOG

Audio—Computers
Instruments
Kits & Assembled

COMPUTER
PRODUCTS
CATALOGUE



Southwest Technical Products Corporation
219 W. RHAPSODY
SAN ANTONIO, TEXAS 78216

CIRCLE 51 ON FREE INFORMATION CARD

new products

More information on new products is available from manufacturers of items identified by a Free Information number. Free Information Card is inside the back cover.


NUT DRIVER KIT, No. K7, contains 7 hollow-shaft hex-nut drivers in the following sizes: 3/16-, 1/4-, 5/16-, 3/8-, 7/16- and 1/2-inch. Hollow shafts accommodate any size stud; and both sockets



CIRCLE 151 ON FREE INFORMATION CARD

and shafts are made of top-grade steel with nickel-chrome exterior surfaces and color-coded (for hex-drive size) handles. Packaged in attractive stand-up hang-up box, kit No. K7 is available from distributors. Vaco Products Co., 1510 Skokie Blvd., Northbrook, IL 60062.

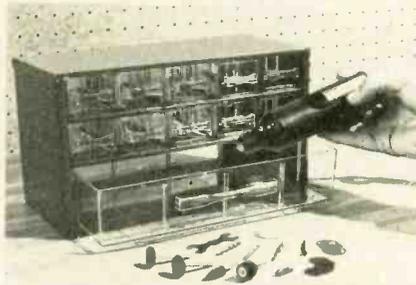11-DRAWER WORKSHOP ORGANIZER, model 2712, is an easy-to-store cabinet available "free" with the purchase of the Moto-Tool kit; tool and accessories come packaged inside the attractive, blue steel cabinet. The workshop organizer mea-



CIRCLE 152 ON FREE INFORMATION CARD

sures 12 L x 6 1/2 H x 5 1/8-inches D, and is ideal for holding small components for hobby or craft projects. Clear plastic drawers provide easy visibility. Both the Moto-Tool kit and organizer are available for \$52.95.—Dremel, Division of Emerson Electric Co., 4915 21st St., Racine, WI 53406.

AUTORANGING CAPACITANCE METER, model CM-500, measures capacitance in 9 ranges, from 1 pF to 200,000 µF, with a basic accuracy of 0.1% ± 1 LSD. The display uses four 1/2-inch-high LED's; a 26-pin connector allows a digital BCD



CIRCLE 153 ON FREE INFORMATION CARD

output to be interfaced with microprocessor, recorder, printer, etc. The optional model CLC-502 Capacitance Limits Comparator provides a GO/NO GO output. Power is supplied by five D batteries; an optional AC adapter is also available. The model CM-500 measures 7.4 x 4.33 x 2.36 inches and comes housed in a sturdy polystyrene case with a handle that doubles as a tilt stand; batteries, clip, leads and operator's manual are included. Suggested retail price: \$299.—IET Labs, Inc., 761 Old Country Rd., Westbury, NY 11590.

8-TRANSISTOR AM RADIO KIT, model 536, contains a separate oscillator circuit, complete breadboarding materials, and PC assembly. The kit comes with all necessary components and



CIRCLE 154 ON FREE INFORMATION CARD

instruction manual. Instruction section of manual covers AM radio theory. Kit sells for \$16.45.—Graymark International, Inc., 1751 McGaw, Irvine, CA 92714.

AUTOMATIC PHONE DIALER, Dial-a-Tron, can be coupled with telephone receiver acoustically or by direct hookup. When hooked up to phone, the built-in speaker allows incoming conversations to be heard; the unit is compatible with Rotary or TouchTone systems. The dialer stores up to 32 ten-digit telephone numbers in memory; features a CANCEL pushbutton to disconnect outgoing calls plus automatic shut-off capability. The Dial-a-Tron measures 7 1/4 by 6 1/2 inches, and has

Put Professional Knowledge and a
COLLEGE DEGREE
in your Electronics Career through
HOME STUDY

Earn Your DEGREE


by correspondence, while continuing your present job. No commuting to class. Study at your own pace. Learn from complete and explicit lesson materials, with additional assistance from our home-study instructors. Advance as fast as you wish, but take all the time you need to master each topic.

The Grantham electronics degree program begins with basics, leads first to the A.S.E.T. degree, and then to the B.S.E.T. degree. Our free bulletin gives complete details of the program itself, the degrees awarded, the requirements for each degree, and how to enroll. (We are located at 2500 S. LaCienega Bl., Los Angeles, Calif.) Write to our mailing address shown below for Bulletin R-79.

Grantham College of Engineering
P. O. Box 35499
Los Angeles, California 90035

Worldwide Career Training thru Home Study
CIRCLE 55 ON FREE INFORMATION CARD

The world of electronics gee-wizardry

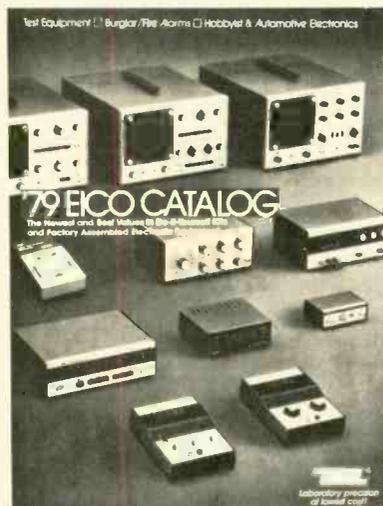

-YOURS FREE.

32-pages of test instruments — from the latest digital multimeters to the famous EICO scopes. Security systems. Automotive and hobbyist products. Kits and assembled. EICO quality. EICO value. For FREE catalog, check reader service card or send 50¢ for first class mail.

EICO 108 New South Road
Hicksville, N.Y. 11801

CIRCLE 47 ON FREE INFORMATION CARD



CIRCLE 155 ON FREE INFORMATION CARD

a suggested retail price of \$150.—Leisurecraft Products, Ltd., 28 S. Terminal Dr., Plainview, NY 11803.


CAR RADAR DETECTOR, The Supertox, is a superheterodyne remote system with adjustable sensitivity control. The unit has extreme sensitivity for receiving radar signals—even over hills and around curves. A built-in microwave lens helps



CIRCLE 156 ON FREE INFORMATION CARD

improve antenna gain. *The Supertox* has the ability to detect all band radar frequencies and to block out false signals. The main chassis can mount behind the car's grille and the control box mounts under the dash. Price is \$299.95.—Comradar Corp., 4518 Taylorsville Rd., Dayton, OH 45424.

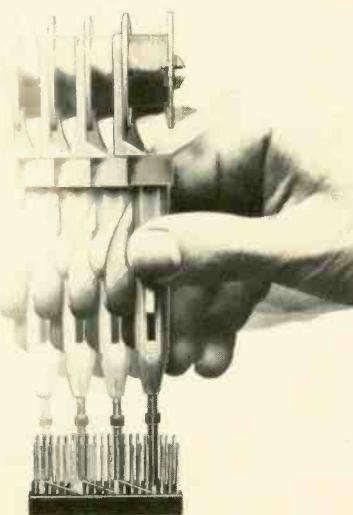
WIRE WRAP TOOL, Model JW-1, is designed to make wire-wrapped connections without having to strip wire insulation. Can wrap on .025 inch square posts and carries a 50 ft. spool of 30 AWG wire which is available in 4 colors. Wraps continuously through any number of pins and includes a



CIRCLE 157 ON FREE INFORMATION CARD

built-in wire cutter. Price is \$14.95, refill spools \$2.98.—O.K. Machine and Tool Corp., 3455 Conner St., Bronx, NY 10475. R-E

NO strings attached

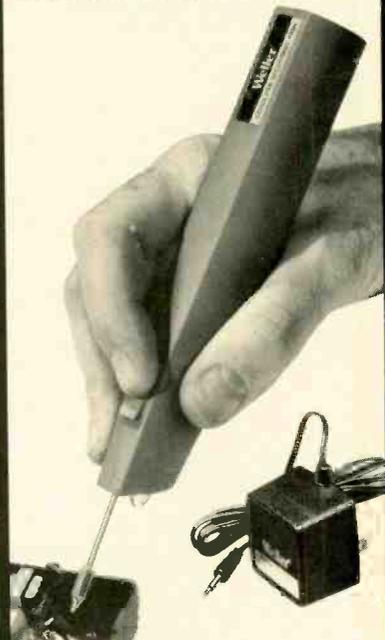

NEW Weller® CORDLESS SOLDERING IRON... GOES ANYWHERE

Weller's WC-100 . . . the professional quality, feather-light cordless. Lets you make connections anywhere. Without AC cord and outlet.

Fingertip touch on exclusive sliding safety switch activates long-life, nickel-cadmium battery. Heats tip to over 700°F in 6 sec. Locks in "off" position to prevent accidental discharge in use or while restoring energy with fast-power recharger (UL listed).

Simple, instant change to any of 4 tips . . . for any job. Built-in light focuses on tip and work area.

Get this! It's at your dealer or distributor now . . . waiting for you. Need more info first? Request literature.



The Cooper Group
Electronics Division

WELLER® · WISS® · XCELITE®
P.O. BOX 728, APEX, NORTH CAROLINA 27502 919/362-7511

CIRCLE 23 ON FREE INFORMATION CARD

BEST IN NEW ELECTRONICS BOOKS!

- The Complete Microcomputer Systems Handbook 322 p. \$9.95
- Buyer's Guide To Everything Electronic For The Home 224 p. \$5.95
- Master Hdbk of 1001 MORE Prac. Electronic Circuits 700 p. \$12.95
- The GIANT Handbook of Computer Projects 504 p. 217 il. \$9.95
- Model Radio Control—3rd Edition 256 p., 252 il. \$6.95
- Microprocessor Cookbook 266 p., 124 il. \$5.95
- T'shooting With Modern Electronic Test Instruments 304 p. \$7.95
- How To Repair Clocks 182 p., 90 il. \$5.95
- All About Telephones 192 p., 140 il. \$4.95
- The Laser Experimenter's Handbook 210 p., 187 il. \$6.95
- Design, Build & Program Your Own Working Computer System \$7.95
- How to Select & Install Your Own Speakers 238 p., 131 il. \$5.95
- The Master Handbook of ALL Home Heating Systems 352 p. \$7.95
- Practical Troubleshooting With the Modern Oscilloscope 288 p. \$7.95
- Basic Gunsmithing 288 p., 152 il. \$7.95
- The A to Z Book of Computer Games 308 p., 73 il. \$7.95
- OSCAR, The Ham Radio Satellites 128 p., 95 il. \$4.95
- Making & Using Electricity From The Sun 144 p., 73 il. \$5.95
- How To Build Your Own Working Robot Pet 238 p., 86 il. \$6.95
- Antenna Data Reference Man.—incl. dimension tables 266 p. \$7.95
- Build a Small Budget Recording Studio From Scratch 336 p. \$8.95
- How To Make Your Own Solar Electricity 168 p., 87 il. \$5.95
- Adding Solar Heat To Your Home 280 p., 185 il. \$7.95
- How To Build Your Own Self-Programming Robot 238 p. \$7.95
- Handbook of Electrical Noise, Msmnt. & Technology 280 p. \$6.95
- Radio Control Handbook—4th Edition 420 p., 315 il. \$9.95
- The Giant Book of Amateur Radio Antennas 462 p., 255 il. \$8.95
- Lasers, the Light Fantastic 294 p., 158 il. \$6.95
- The Power Supply Handbook 420 p., 292 il. \$7.95
- The Complete Handbook of Robotics 384 p., 137 il. \$7.95
- Artificial Intelligence 252 p., 118 il. \$7.95
- Hdbk of Remote Control & Automation Tech. 294 p., 250 il. \$7.95
- Build Your Own Working Robot 238 p., 117 il. \$5.95
- The "Computer" Book 322 p., 224 il. \$7.95
- Miniprocessors: From Calculators to Computers 192 p., 67 il. \$5.95
- Complete Hdbk of Public Address Sound Sys 272 p., 148 il. \$7.95
- Home-Brew HF/VHF Antenna Handbook 210 p., 143 il. \$5.95
- IC Function Locator 224 p., 28 il. \$5.95
- Beginner's Guide to Making Electronic Gadgets 140 p. \$4.95
- Microprocessor Programming for Computer Hobbyists 378 p. \$8.95
- Illus. Dic't. of Broadcast-CATV-Telecommunications 420 p. \$8.95
- Linear IC Applications Handbook 280 p., 184 il. \$6.95
- Build-It Book of Optoelectronic Projects 238 p., 175 il. \$5.95
- Solid-State Motor Controls 322 p., 162 il. \$8.95
- Model Railroad Electronics 308 p., 224 il. \$5.95
- The ABC Book of Hi-Fi/Audio Projects 182 p., 131 il. \$4.95
- Repair Small Gasoline Engines, 2nd Ed 392 p., 251 il. \$6.95
- 88 Practical Op Amp Circuits You Can Build 140 p., 120 il. \$4.95
- How to Build Metal/Treasure Locators 140 p., 58 il. \$3.95
- Build-It Book of Digital Electronic Timepieces 294 p., 209 il. \$6.95
- C.E.T. License Handbook, 2nd Edition 448 p., 381 il. \$9.95
- Third Class FCC License Study Guide 322 p., 88 il. \$6.95
- Practical Solid-State DC Power Supplies 196 p., 151 il. \$6.95
- 106 Easy Electronics Proj.—Beyond the Transistor 244 p. \$5.95

SEND NO MONEY! We'll invoice you on 10-DAY FREE TRIAL. Clip entire ad to order. 100% guaranteed or your money refunded.

TAB BOOKS DEPT RE-129 BLUE RIDGE SUMMIT PA 17214

CIRCLE 3 ON FREE INFORMATION CARD

TRS-80 BREADBOARD

continued from page 54

To test the decoder section of the breadboard, you will need a NOR gate integrated circuit, such as the SN7402, and a solderless breadboard that can be used to help you set up a test circuit. Wire the circuit that is shown in Fig. 15. The \overline{IN} and \overline{OUT} signals are provided at SO2, while the $\overline{6}$ and $\overline{7}$ signals may be found at the ADDRESS socket SO5. Once the switches have been set to the positions noted previously (all zeros, mode D), run the following program:

10 A=INP(7): GOTO 10

You should observe pulse activity at point A, but not at either B or C. Change the program, so that input port 6 is accessed:

10 A=INP(6): GOTO 10

You should observe activity at point B. To test the output control, use the following program:

the interface. It simply causes the TRS-80 to generate the proper 16-bit address. Thus, to access a location, or a memory-mapped I/O device, with an address of 36871, the following short program could be used:

```
10 POKE -1*(36871-32767),0
20 A = PEEK (-1*(36871-32767))
30 PRINT A: GOTO 10
```

If you wish to observe this program in operation, you would have to replace the \overline{IN} signal with \overline{RD} , and the \overline{OUT} signal with \overline{WR} , as previously shown in Fig. 15. You would also have to switch to the memory address mode, M, and then set the address bits so that they corresponded to the binary equivalent of 36,871; that is 10010000 00000111. If you run the program shown above, you would be able to monitor pulse activity at point A as shown in Fig. 15. Point A would correspond to the pulse generated by a read operation at location 36,871, corresponding to the PEEK operation. No pulse activity would


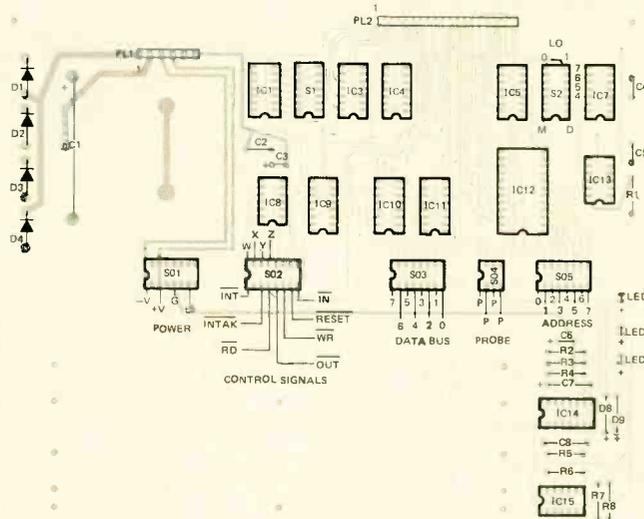


FIG. 14—HOW COMPONENTS ARE PLACED on the PC board. Several of the IC sockets are used for connections to point-to-point jumpers.

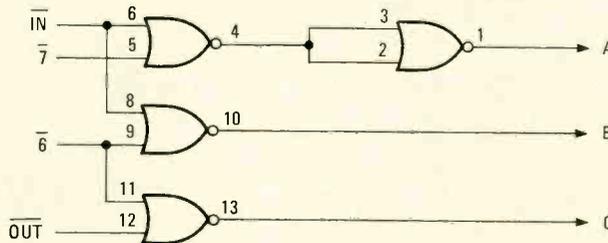

THE FOUR NOR GATES ARE FROM SN7402

FIG. 15—SCHEMATIC DIAGRAM of the NOR gate circuit used for testing the breadboard.

10 OUT 6,0: GOTO 10

When this program is run, you should observe activity at point C. You may wish to try other addresses, and also the PEEK and POKE commands, so that the HI address decoders are accessed. If you use the address decoders for memory addresses, remember to use the formula:

$$\text{Address} = -1 * (\text{Desired Address} - 32,767)$$

when the address that you wish to access is above 32,767. This has no effect upon

be observed at points B or C, since there is no address 36,870 being used in the program. Again, we see no advantage in using memory-mapped I/O, but we have presented this example so that you can check out the HI address decoding section of the interface breadboard. If you perform these tests, remember to place the mode switch in position, D when you have completed the test.

You are now ready to test the data bus buffers. Add bus buffers IC10 and IC11.

Get A GNOME
the original micro-synthesizer

John Simonton's time-proven design provides two envelope generators VCA, VCO & VCF in a low cost, easy to use package.

Use alone with its built-in ribbon controller or modify to use with guitar, electronic piano, polytonic keyboards, etc.

The perfect introduction to electronic music and best of all, the Gnome is only \$59.95 in easy to assemble kit form. Is it any wonder why we've sold thousands?

- Send GNOME MICRO-SYNTHESIZER Kit (\$59.95 plus \$2.00 postage)
- GNOME MICRO-SYNTHESIZER (Fully Assembled) \$100.00 plus \$2 postage
- Send FREE CATALOG

name: _____
address: _____
city: _____ state: _____ zip: _____

BAC/VISA MC card no. _____
DEPT. 12-R
1020 W. WILSHIRE, OKLAHOMA CITY, OK 73116

CIRCLE 12 ON FREE INFORMATION CARD

The TRS-80 should run properly with these IC's in place, and with the power applied to the breadboard. If it does not, remove the IC's and check their orientation. If this still doesn't cure the problem, you may wish to breadboard a test circuit for the 8216's. You want to be sure that the EN input to both IC's, pin 15, is in the logic zero state for normal operation. If this condition is not found, check back through the two SN74LS20 NAND gates.

Once the TRS-80 is operational, as it probably will be in almost all cases, you will need to construct an input port, and an output port to thoroughly test the data bus connections. Refer to Figs. 4 and 5 for the details of each port. You may use the test circuit in Fig. 15 to generate the device select pulses required to control each port. If you have performed the memory address tests, be sure to rewire the test circuit so that the IN and OUT signals are used, as shown in Fig. 15. Output A from the test circuit may be used as the DEVICE SELECT pulse for the input port IC's (DM8095's or SN74365's), while output C may be used to control the output port (SN74LS373). The lamp monitors may be LED's, and the logic switches may be simply jumper wires that are easily switched between connections with +5 volts (logic one), and ground (logic zero). Once this has been wired, make a connection between

the SN7402's A output, and one of the INP REQ pins at S02.

Enter and run the following program, with power applied to the breadboard:

```
10 FOR A=0 TO 255
20 OUT 6,A
30 NEXT A
40 GOTO 10
```

This program will generate an incrementing count at the output port, and you should be able to observe an eight-bit binary count on the LED's that are connected to the SN74LS373. If this counting action is not observable, check output C on the SN7402, to be sure that the output port is being activated by the computer. You should also be sure that the SN74LS373 is operating properly, and that all of the connections have been properly made. When wiring an interface of this type, it is often easy to "twist" a data bus wire, so that data bit D4 appears where bit D5 should, and vice versa. Recheck your bus wiring. If a bit is not observed to be counting (constantly on, or constantly off), switch the 8216's. If the "bad bit" moves, you probably need to replace the 8216 bus buffer. Don't forget that if you can't observe any action on the LED's, the logic probe can be used.

Once the output port has been tested, enter and run the following program:

```
10 A=INP(7)
20 PRINT A
30 OUT 6,A
40 GOTO 10
```

This program transfers information from the logic switches to the TRS-80. The TRS-80 prints the decimal value on the screen, and it then outputs the information to the output port. When the program is running, you should be able to change the logic switch or jumper settings and then observe the effect upon the displayed value, and the value printed on the TRS-80's screen.

Before you dismantle the two ports that you have constructed, you may wish to try and use them in other ways. Space has been left on the PC board so that a solderless breadboard may be added to make your experimenting easy. We think that you will find the breadboard to be a valuable tool, since all of the generally used TRS-80 I/O control signals have been provided for you, along with a suitable decoding scheme, and an on-board logic probe. If you are interested in some of the things that can be done with the breadboard, we suggest that you obtain a copy of the TRS-80 Interfacing book mentioned previously. It contains 18 experiments that you can do on the interface breadboard, including experiments on decoders, I/O ports, flags and A/D and D/A converters. But for now, let's look at two experiments you can do. Next month we'll develop the software for controlling a traffic light and then see how to use the TRS-80 to develop analog control voltages. **R-E**

YOU DESERVE IT!

GET IT EVERY MONTH!

Come on, treat yourself—and save money, too. Subscribe to Radio-Electronics today, and make sure you get all of the most interesting, most exciting and authoritative electronics reporting in any magazine, month after month. Don't miss a single one of the upcoming issues jam-packed with new-equipment test reports, projects to build, servicing ideas, and news of solid state, computers, hi-fi, hobbies and everything electronic. Save money, too—as much as \$11 off the newsstand price when you subscribe to Radio-Electronics. Come on, you deserve it—check off the money-saving offer you prefer on the handy coupon, and start enjoying Radio-Electronics every month.



Get The Authority—Every Month

40M9

Name (Please print) _____

Address _____

City _____

State _____

Zip Code _____

Indicate the offer you prefer:

1 Year—12 issues ONLY \$9.98
(You save \$5.00 off newsstand price.)

2 Years—24 issues ONLY \$19.00
(Save More! \$11.00 off newsstand price.)

Payment enclosed (send one extra issue)

Bill me

Check here if you are extending or renewing your subscription.

Extra Shipping: Canada \$3.00 per year, all other countries \$5.00 per year.


Mail to: **Radio-Electronics**

SUBSCRIPTION DEPT., P.O. BOX 2520 BOULDER, COLO. 80322

Make Custom S-100 Boards EASY... with VECTOR 8800R2

- +Positive Photo Resist coating over 2 oz. copper on 2 sides.
- Accurate S-100 standard size (5.3 in. x 10 in.) with pre-etched gold contacts, 50 per side, 0.125 sp.
- 2 mylar sheets and strong etching bag supplied free with 8800R2.
- Expose with sunlamp - No camera or darkroom needed.

copper free borders both sides

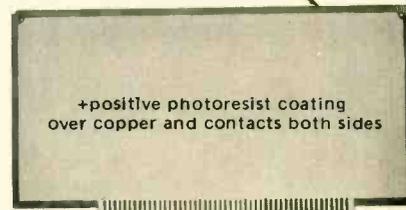

+positive photoresist coating
over copper and contacts both sides

\$19.95 ea.

Simply expose board to film master image, etch and drill holes. Film may be photographically prepared or home-made using clear mylar supplied. Make circuit art work with Vector R407 rub transfer art work set (\$2.65) or use alternate stick on tape. If not available locally factory order - include \$3.00 shipping, U.S. only.

prices subject to change without notice

Vector Electronic Company

12460 Gladstone Ave.

700979 Sylmar, CA 91342

CIRCLE 34 ON FREE INFORMATION CARD

These rates are not guaranteed after 9 months.



30,000 Ω/V, Rugged Taut Band Meter, Only \$49!

Also: mirrored meter, protective guard edge around front, separate audio jack for dB measurement. 6 functions, 20 ranges include 5Aac/dc. WV-518B. \$49.

THE VIZ BLUE LINE VOMs. Superb quality. Modest prices.



20,000Ω/V Taut band meter 5 functions, 18 ranges from 0.3V and 60μA/dc. WV-517B. \$36



20,000Ω/V Taut band, high-impact orange case. 5 functions, 19 ranges from 0.5 to 1000Vdc. WV-547B. \$33



2,000 Ω/V Measures to 250 ac/dc, 250mAac, 500KΩ plus dB. Includes battery and probes. WV-516B. \$19.95

See your nearby VIZ distributor.

VIZ TEST INSTRUMENTS GROUP

335 E. Price Street, Philadelphia, Pennsylvania 19144

WANTED WRITERS — AUTHORS

The *Blacksburg Group*, originators of the BUG-BOOKS, is interested in finding new book authors for its popular "Blacksburg Continuing Education Series." The following topics are of particular interest:

- Fiber Optics
- Microcomputer Applications
- Telephone Applications
- Special IC's
- PET Interfacing
- TRS-80 Applications
- Software (All types)
- IEEE-488 Bus
- Word Processing
- Robotics
- Home/Solar Control
- Digital Troubleshooting
- 16-Bit Microcomputers
- Timers-Controllers
- Operating Systems
- Plus many others

Our 30+ current titles cover 8080/8085/Z-80/6800/6502/TRS-80 programming and interfacing, op-amps, PLL's, data processing, digital electronics, etc., and we are always interested in talking with people about their ideas for new books. Our writers, consultants and editors are ready to review your ideas, outlines or manuscripts for possible inclusion in the "Blacksburg Series." Royalties and advances are competitive, plus additional benefits.

For an author packet, plus a free book list, please write or call:

Blacksburg Group,
P. O. Box 715, Blacksburg, VA 24060
(703) 951-9030



PERSYN ACCESSORIES

continued from page 50

the OR gate can be made to provide a complex serial-output pulse train.

The OR gate outputs are buffered and inverted in the inverters IC1-d, -e and -f and coupled to the output jacks through isolation diodes. Resistors R4, R8 and R10 provide a ground reference for the isolation diodes. When connected in the PerSyn system, the isolating diodes prevent manual trigger pulses from the strike surface boxes from interacting with the sequencer.


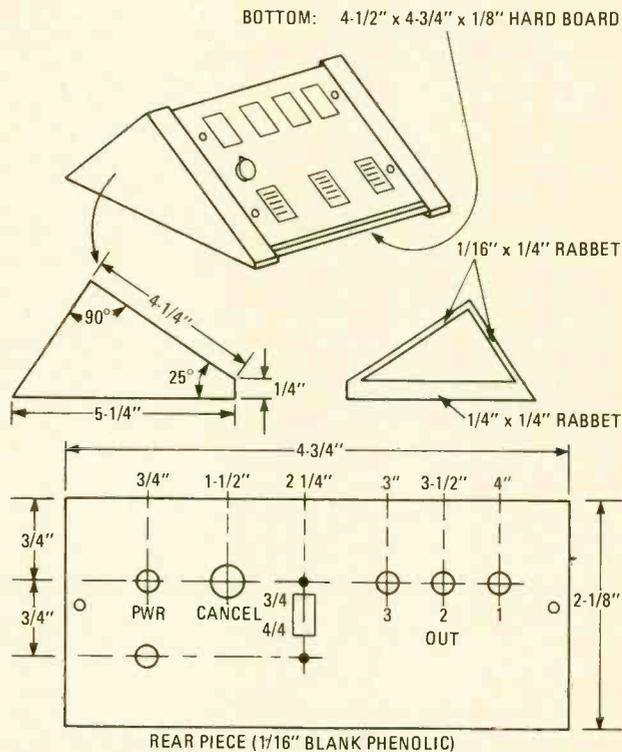


FIG. 9—CONSTRUCTION of the Sequencer enclosure. The side pieces are made of three-quarter inch stock.


If CANCEL jack J6 is shorted through a switch, IC2 is reset. When the short is removed, operation will resume with the first output (pin 2). Light emitting diode LED1 is energized when the first output goes high, indicating the start of the pattern.

Power (+9 volts) is provided through the "tip" (+9) or POWER jacks J4 or J5. Ground reference is obtained through either of the "rings" of output jacks J1, J2 or J3. No connections are made to the "rings" of J4 or J5.

Construction: Construction of the circuit is simplified by using a PC Board, the foil pattern and components placement for which are shown in Figs. 6 and 7. All IC's are CMOS devices and, therefore, standard handling precautions should be observed. When mounting DIP switches DS1-DS3, be sure to observe the proper orientation. Also observe proper orientation for all diodes and IC's. When mounting the TEMPO control on the PC Board, use an additional mounting nut so that the bushing of R5 protrudes about 3/16 inch above the board. This will insure that the body of R5 will not touch the foil side of the board, thus preventing any possibility of accidental shorting. Install all 14 jumpers on the foil side of the PC Board as in Fig. 8. Use insulated wire. Install wiring between switch S1, J1 through J6 and the PC Board as indicated in Fig. 8. Solder the wires to the appropriate pads on the foil side of the PC Board. The unit can be housed in a "case" similar to that shown in Fig. 9. You can, of course, house the PC board in a standard case and use discrete switches in place of DS1 through DS3. In this case, wires from the switches would be connected to the appropriate PC holes for DS1 through DS3. If using a metal enclosure, be sure to isolate the body of J6 (at +9 volt potential) from the

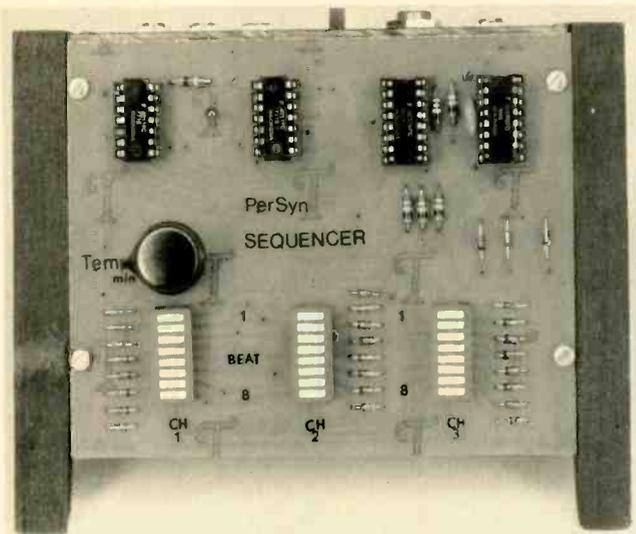

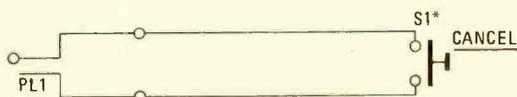FRONT VIEW of the Sequencer. The three DIP switches across the bottom feed the OR gates and determine the beat.



*S1 IS PUSH-TO-MAKE PUSH-TO-BREAK SWITCH

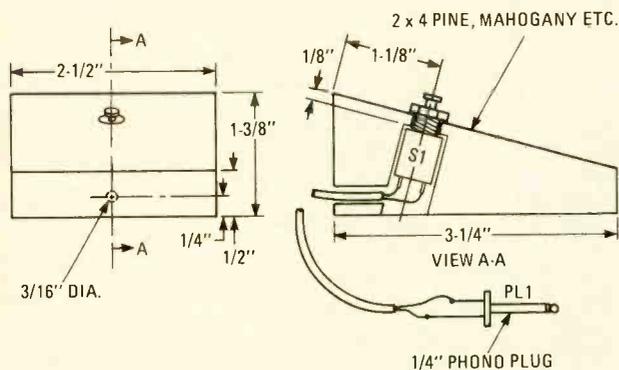


FIG. 10—CONSTRUCTION and wiring of the footswitch.


bodies of J1 through J5 (at ground potential).

Use: Connect either POWER jack to the TAP jack on PerSyn (or to a POWER jack of an accessory being used). Connect the OUTPUT jacks to the TRIG jacks of the devices to be triggered. A standard ON/OFF footswitch should be used to control the operation of the Sequencer. If not available, one can be made from a small piece of wood as shown in Fig. 10. Insert the footswitch plug into J6 and place TEMPO control R5 to midposition. If the CANCEL switch in the footswitch is closed LED1 will blink. If not, depress the CANCEL switch to start the Sequencer. Once PATTERN switches DS1 through DS3 are appropriately programmed, adjust TEMPO as desired.

Programming: The counting structure for a basic 1/4 bar of music is "ONE-and-TWO-and-THREE-and-FOUR-and". The eight switches on DS1, 2 or 3 correspond to this counting with the top switch corresponding to "ONE" and so on (switch 7 corresponds to "FOUR"). In 3/4 time, the counting sequence is "ONE-and-TWO-and-THREE-and". Therefore, with S1 set for 3/4 operation, switches 7 and 8 are not used.

Many complex rhythm and special effects patterns can be generated with the sequencer. Four basic programming examples are listed in Table 1 on page 50 to acquaint you with the operation of the Sequencer.

R-E

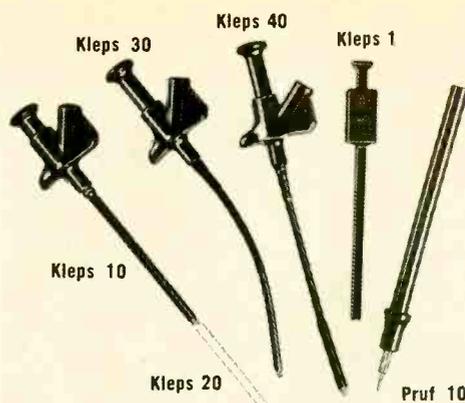

Clever Kleps

Test probes designed by your needs — Push to seize, push to release (all Kleps spring loaded).

- Kleps 10.** Boathook clamp-grips wires, lugs, terminals. Accepts banana plug or bare wire lead. 4 3/4" long. \$2.64
- Kleps 20.** Same, but 7" long. \$4.49
- Kleps 30.** Completely flexible. Forked-tongue gripper. Accepts banana plug or bare lead. 6" long. \$3.19
- Kleps 40.** Completely flexible. 3-segment automatic collet firmly grips wire ends, PC-board terminals, connector pins. Accepts banana plug or plain wire. 6 1/4" long. \$4.59
- Kleps 1.** Economy Kleps for light line work (not lab quality). Meshing claws. 4 1/2" long. \$2.49
- Prof 10.** Versatile test prod. Solder connection. Molded phenolic. Doubles as scribing tool. "Bunch" pin fits banana jack. Phone tip. 5 1/2" long. \$2.37

All in red or black - specify. (Add 50¢ postage and handling.)

Write for complete catalog of - test probes, plugs, sockets, connectors, earphones, headsets, miniature components.

Available through your local distributor, or write to:

rye INDUSTRIES RYE INDUSTRIES INC.
133 Spencer Place, Mamaroneck, N.Y. 10543
In Canada: Rye Industries (Canada) Ltd.

CIRCLE 18 ON FREE INFORMATION CARD

THE BIG PLUS + Graphic Equalizer

ASSEMBLED
\$200⁰⁰

KIT
\$110⁰⁰



LOADED with Quality Features!

- Stereo . . . Eleven Bands Per Channel • Extremely Low Noise & Distortion • LED Peak Indicators • Center Detent ("flat") sliders • Built-in "record" Switching • Line and Microphone Level Inputs/Outputs • Regulated Power Supply • Fully Guaranteed • Horizontal or Vertical Cabinets • Kit or Fully Assembled • Plus Much, Much More!

Absolutely equals or exceeds overall performance and features of any graphic equalizer made today!

AARON-GAVIN INSTRUMENTS, INC.
17231 Corla Avenue Tustin, California 92680

Yes! I've enclosed \$ _____, RUSH me _____ cabinet send brochure

_____ assembled equalizers at \$200.00, p.p.d. _____

_____ unassembled equalizer kits at \$110.00, p.p.d. Horizontal (flat) Vertical (top-right)

California residents include 6% sales tax. Visa & Master Charge orders accepted

Name _____ Card No. _____ Bank _____
Address _____ Exp. Date _____ No. _____
City _____ State _____ Zip _____

Dealer inquiries invited

CIRCLE 56 ON FREE INFORMATION CARD

TELEPHONE DIALERS
continued from page 46


ular phone dial! In the TEL position, your phone dial is enabled, but the *Otron* dialer capability is disabled.

Which is the best unit?

This "loaded" question has no real answer, since needs vary. The *Rapidial II*



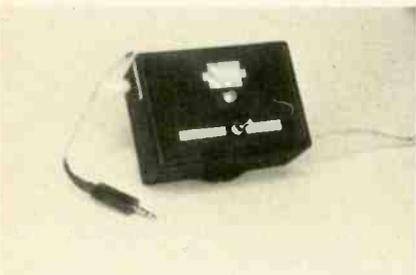INSIDE VIEW of the Superphone 7710. The buzzer is used as an alarm signal. Rechargeable batteries retain memory if the power fails.



DIALER INTERFACE from Blechman Enterprises. It contains a relay, LED, switch and battery.

is the lowest-priced assembled unit and probably offers the most telephone-associated versatility in the smallest package. The Heath unit is simple to assemble and use, at the same price. Next up are the *Busy-Buster* and Radio Shack units in the price scale, but with totally different capabilities. If you have need for a fast, multi-purpose dialer, the *Rapidial* used on DTMF tone-dialing is outstanding.

Then come the special features, like calculator, calendar and alarm functions—but are they worth twice the price of the Radio Shack with its clock and timer? As executive gift items, the *Superphone* or *Freedom Dialer* are hard to beat, since they include the telephone and almost everything but the kitchen sink. As for me, I want them all! **R-E**

JOIN

the
great
american
smokeout


American Cancer Society

Stop

" KIDDING YOURSELF " electronics is for those who know basic electricity

THE AE-10

simple
easy
reading
manual

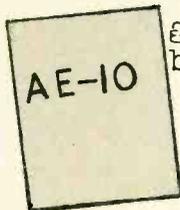

good
basics

yes send ___ copy(s) of the AE10 basic manual on electricity at only \$9.00 each.

Name _____

Address _____

City-State _____

Asante Enterprise Ltd.
Georgetowne Unit 1s3
Lindenwold, N.J. 08021

NEW TYPE PROJECTION LENS



Barrel-shaped, professional-quality lens is 8" in diameter, has 12" focal length, and comes with mounting ring. Provides bright high-resolution picture with 12", 13" and 15" TV's. Priced at \$69. Quantity discounts available. For further information on converting standard TV's into projection sets, call or write Bill Spellman.

Also available: 3, 4, 5, 6' and 7' high-efficiency projection screens.

MFE COMPANY, INC.

304 N.E. 79th Street
Miami, Florida 33138
Tel. 305/759-3124

Manufacturers of High Voltage Electronic Equipment/Projection Lenses/Projection Television Systems for over 30 years.

CIRCLE 42 ON FREE INFORMATION CARD

AUDIO AMPLIFIER
continued from page 57

have the ability to make double-sided printed circuit boards, you can use the foil pattern shown in Figs. 3 and 4 which I've used to build over twenty of these amplifiers. The component placement diagram is shown in Fig. 5.

The thermistor is a 30-ohm cold, negative temperature coefficient type (the higher the coefficient the better, but the 30 ohms should be referred to room temperature).

Mount the thermal-feedback diodes (D1-D4) and the output transistors on heat sinks. Do *not* heat-sink the 2N5191 and 2N4919. They must be held at the ambient temperature sensed by the 30-ohm thermistors. Preferably, separate heat sinks, such as those suggested in the parts list, should be used for each half of the amplifier. Either the 2N3055 or its plastic equivalent, the MJE3055, can be used in the output stages. Be sure to use mica insulating washers in the mounting process. The thermal sensing diodes (D1-D4) should be mounted so as to thermally couple tightly to sense the temperature of the output devices.

Checkout and adjustment

Before operating the amplifier, disconnect any loads (speakers) and connect a DC voltmeter across the output terminals. Apply power, allow one or two minutes for capacitors to charge fully, then adjust the DC BALANCE potentiometer for zero volts across the output terminals. If you cannot achieve this, and a gross unbalance exists (more than 1 volt), perform the following checks.

With your DC meter, check each amplifier output terminal's voltage *with respect to ground*. It should be very nearly half the power supply voltage. If one half of the amplifier does not pass this test, check wiring and components in that half.

Now connect a 16-ohm dummy load and an audio input signal. Verify, using an AC voltmeter, that the signal across the load is about ten times the input RMS signal, and that, using a DC meter, no DC component in excess of 1.8 volts exists across the load for a 10-volt RMS output (about 1-volt RMS input).

Now connect a loudspeaker load, fused with a 1-amp fast-blow temporary fuse connected in series with the speaker. Feed a signal from your preamp into the power amplifier and listen to the sound for an hour or so. If it is pleasant, and the amplifier doesn't overheat, remove the temporary fuse in series with the speaker. This will improve damping. You may reduce the fuse to 2 amps fast-blow, if driving a bookshelf-speaker.

Parallel a suitable resistor (try values around 200K) across R1 until the audio amplifier output amplitude at L1 matches that at L2. This maximizes the output power before clipping occurs. **R-E**

market center

CLASSIFIED COMMERCIAL RATE (for firms or individuals offering commercial products or services) **\$1.50 per word** (no charge for zip code) . . . minimum 15 words.

NONCOMMERCIAL RATE (for individuals who want to buy or sell personal items) **85¢ per word** . . . no minimum.

ONLY FIRST WORD AND NAME set in bold caps. Additional bold face (not available as all caps) at 10¢ per word. Payment must accompany all ads except those placed by accredited advertising agencies. 5% discount for 6 issues, 10% for 12 issues within one year, if paid in advance. All copy subject to publisher's approval. Advertisements using P.O. Box address will not be accepted until advertiser supplies publisher with permanent address and phone number. Copy to be in our hands on the 26th of the third month preceding the date of the issue (i.e., August issue closes May 26). When normal closing date falls on Saturday, Sunday, or a holiday, issue closes on preceding working day.

EDUCATION & INSTRUCTION

TELEPHONE bugged? Don't be Watergated! Countermeasures brochure \$1.00. **NEGEYE LABORATORIES**, Box 547-RE, Pennsboro, WV 26415

UNIVERSITY degrees by mail! Bachelors, Masters, Ph.D's . . . Free revealing details. **COUNSELING**, Box 317-RE12, Tustin, CA 92680

COLLEGE students! Improve your grades. Send \$1.00 for 356-page, collegiate research papers catalog. 10,250 available. **RESEARCH ASSISTANCE**, Box 25097RE, Los Angeles, CA 90025. (213) 477-8226.

ELECTRONIC MUSIC

ELECTRONIC music and home recording in Polyphony magazine. Advanced applications, interviews, projects, computer music. Sample, \$1.50. Subscription (6 issues), \$8 US/\$10 foreign. **POLYPHONY**, Box R20305, Okla. City, OK 73156.

BUSINESS OPPORTUNITIES

MECHANICALLY inclined individuals desiring ownership of Small Electronics Manufacturing Business—without investment. Write: **BUSINESS-ES**, 92-R, Brighton 11th, Brooklyn, NY 11235

LEARN to repair PLL or crystal synthesis CB for profit, 30 PLL's covered. Send \$12.95 for instruction book. **A.P. SYSTEMS**, PO Box 488, Milford, PA 18337, Dept. RE

TUBE CADDY

TUBE caddys: just like the old favorite, only better. Free catalog: 800-233-8851 **MHP INC.**, 107 Avenue L, Matamoras, PA 18336.

GRAPHIC EQUALIZER

TWELVE bands/channel \$100 kit. still available; see May 1978 R/E cover story or write: **SYMMETRIC SOUND SYSTEMS**, 912 Knobcone Place, Dept. R, Loveland, CO 80537

BREATHE REFRESHING

"VITAMINS OF THE AIR"

with an amazing
NEGATIVE ION GENERATOR

ROOM-PORTABLE-CAR
UNITS, TESTERS AND
ACCESSORIES

(Dealers Wanted)

\$129.00

Or
Send \$1.00 for
fascinating
details to

GOLDEN ENTERPRISES, INC.
P.O. Box 1282-RE
Glendale, Arizona 85311

PLANS & KITS

CONSTRUCTION plans for profitable business ideas. Catalog \$1.00. **GARLING**, 438 N. Garfield Street, Lombard, IL 60148

BUILD your own speaker system. Write for free catalogue. **McGEE RADIO**, 1901 McGee St., Kansas City, MO 64108

ELECTRONICS completed kits. No wiring. FM mic. VU meter. Touch control switch. Programmable music block. Wheel fortune game. Etc. Save up to 50%. Write for free catalog today. Postcard will do. **SUPERTRONICS INC.**, 39 Bowery, Box 88, New York, NY 10002

TELEPHONE circuits for hobbyist, construction plans. Catalog \$1.00. **SEACOMP**, Box 4276T, Mountain View, CA 94040

AUDIO mixers, preamps, meters. Schematics, construction guides. SASE brings free list. **PAM ELECTRONICS**, 3424 Memorial St., Alexandria, VA 22306

To run your own classified ad, put one word on each of the lines below and send this form along with your check for \$1.50 per word (minimum 15 words) to:

Radio-Electronics, 200 Park Avenue South, N.Y., N.Y. 10003

ORDER FORM


PLEASE INDICATE in which category of classified advertising you wish your ad to appear. For special headings, there is a surcharge of \$10.

() Plans/Kits () Business Opportunities () For Sale
() Education/Instruction () Wanted ()

Special Category: \$10

(PLEASE PRINT EACH WORD SEPARATELY, IN BLOCK LETTERS.)

1	2	3	4	5
6	7	8	9	10
11	12	13	14	15
16	17	18	19	20
21	22	23	24	25
26	27	28	29	30
31	32	33	34	35

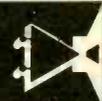

CFR Associates, Inc.
Newton, N.H. 03858

SURPLUS OFFER IBM Selectric PRINTERS

Model "B" Printer/Plotter

Removed from equipment. Features x-y servos for graphics, etc. Includes edge connector print-out drawing plus all circuit diagrams. These terrific Selectric-based printers were part of an electronic word processor system and may be used as an electronic word processor/typewriter or even a terminal. Features IBM "SELECTRIC" 17" 735 top quality printer, orig. priced at over \$2500.00 EACH!! Shipped complete with schematics, AS-IS, whole D.C. stepper driven carrier & platen. **Model "B" Printer/Plotter** Only \$359.00



Model "A" Printer/Typewriter

Similar in appearance to the Model "B", the "A" version offers typewriter capability immediately, and is a standard IBM 735 printer. Needs only +26VDC to activate shift (capitals) and tab solenoids. This machine has the standard escapement and platen control. Used in word processors, good condition. AS-IS.

Model "A" Printer/Typewriter \$389.00
Limited supply. Call now to reserve your printer. Prices do not include shipping and handling.



RS-232C CONNECTERS

Removed from equipment, otherwise like-new. Specify male or female type. Solder cup conn's. **ONLY \$2.59 ea.; 2/\$5.00**

UNIVERSAL ACTIVE FILTER HYBRID

Identical to Nat'l AF-100-ICJ. State-variable filter hybrid w/4 on-board op amps, capacitors, etc. A complete active filter with hi-pass, bandpass, lo-pass, and notch outputs. Makes simple, low disto sine-wave oscillator. Easily tuned with 2 ext'l resistors or pots. Range DC-10kHz. With data Only \$4.95 ea.

CFR Associates now stocks many exotic computer printers & other peripherals.

Call us for further information. Remember too, we cannot accept collect calls.

•Centronics •Diablo •Wang Labs •Memorex •CDC •Selectric


•Minimum Order: \$15.00
•MC, VISA, & C.O.D. Accepted •Phone Orders Are Welcome
SATISFACTION GUARANTEED
(603)382-5179

We have many unusual and unique bargains in our CATALOG. Send a stamp or 25¢ for postage for a FREE COPY, and get on our mailing list.

CIRCLE 44 ON FREE INFORMATION CARD

SpeakerGuts.

The absolute latest in advanced speaker technology. Wave Aperture™ Drivers, the Patented Nestrivic Wooler System, raw speaker components selected for their excellence. Horns, crossovers, subwoofers, woofers, midranges, horn and dome tweeters. Over 30 in all. Build your own speaker system and we'll provide top quality speakers and design information. Send for FREE 48 page color catalog from the largest, most experienced speaker kit manufacturer in the world. **DON'T DELAY. Write today!**

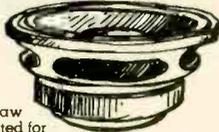

Dept. 12-RE, 735 N. Northlake Way
Seattle, Washington 98103

PLANS AND KITS

SHOCKING. Build versatile high voltage supply up to 12 kV. Great for negative ion generators, bug zappers and many experimental devices. Plans \$5.00. **LUNATRIX**, Box 891, Yucaipa, CA 92399

ELECTRONIC organ kits. The ultimate design. Sounds like a pipe organ. Build it to sell or build it to keep. Models for churches, homes, clubs, pizza parlors. Send \$1.00 for demo record and catalog. **DEVTRONIX**, Dept. 70, 6101 Warehouse Way, Sacramento, CA 95826

NR-2 adaptive noise filter kit as featured in **Radio-Electronics August, September issues.** Reduces audio noise 12 dB. Works with all program sources; tape, or FM broadcast. Even works with Dolby systems. \$69.95. Free information. Dealer inquiries invited. **ADVANCED AUDIO SYSTEMS**, P.O. Box 24, Los Altos, CA 94022

DYNACO Mark III Kits, last available new units, factory sealed sent UPS freight C.O.D., \$200.00 each; Two for \$375.00. **CHARLES RAIBLE**, 1726 Bentley #5, Los Angeles, CA 90025

COMPONENTS by APOLLO

electronics components div
SEMICONDUCTORS—SWITCHES—INTEGRATED CIRCUITS—POTS—RELAYS—CMOS
OUR SPECIALITY HARD TO GET IC's.....CMOS
There's more to distribution than just having the right parts. . . **LIKE SERVICE!**

COMPONENTS BY APOLLO
Rt 23, RIVERDALE, N.J. 07457 phone 201-838-4910

FOR SALE

RADIO & TV tubes 36¢ each. One year guaranteed. Plus many unusual electronic bargains. Free catalog. **CORNELL**, 4217-E University, San Diego, Calif. 92105

NAME brand test equipment. Guaranteed discounts up to 50%. Free catalog. **SALEN ELECTRONICS**, Box 82-M, Skokie, IL 60077

PRINTED-circuit boards, reasonable. Also, artwork, prototypes, designs, fabrication and testing. **MICROCON INC.**, Box 43, Glenview, IL 60025

AUDIO noise reduction kit—318 silencer for tapes, records, FM. Free brochure. **LOGICAL SYSTEMS**, 3314 "H" St., Vancouver, Washington 98663.

SCANNER/monitor accessories—kits and factory assembled. Free catalog. **CAPRI ELECTRONICS**, Route 1R, Canon, GA 30520

FREE catalog, IC's, LED's, semi's, parts. **CORNET ELECTRONICS**, 649A Notre Dame W., Montreal, Que., Canada H3C 1H8. U.S. inquiries.

RECONDITIONED test equipment. \$1.00 for catalog. **JAMES WALTER TEST EQUIPMENT**, 2697 Nickel, San Pablo, CA 94806

FREE KIT Catalog

AUTORANGE DIGITAL CAP-METER KIT. Still the best for only \$74.95
Phone 415-447-3433
Write or Phone for FREE CATALOG.
Average 1 minute Saturday call is 21¢.

DAGE SCIENTIFIC INSTRUMENTS
BOX 1054R LIVERMORE CA 94550

KRAZY CB business cards, radio checks, other printed fun stuff. Catalog and samples for 15¢ stamp. **PRINTRONICS CO.**, Dept. R, 110 N. Keswick Ave., Glenside, PA 19038

B & K test equipment. 18% discount. Free catalog. Free shipping. **SPACETRON-DB**, 948 Prospect, Elmhurst, IL 60126

PARTS 1¢ each, 200 minimum order, over 10% are Prime Semiconductors. Free gift with \$5.00 order. **CUNNINGHAM**, Box 123, Leetonia, OH 44431

HAMS, CBers, SWLs—eight character morse-A-word morse code reader; **RTTY reader.** Decodes signals off the air. Send for details. **MICROCRAFT CORPORATION**, Box 513R, Thiensville, WI 53092 1-414-241-8144.

AMAZING "no-touch" switch. A wave of your hand activates lights, lamps, stereo, appliances etc. Free brochure. **DMD SCIENTIFIC**, Box 6251-B, Flint, MI 48508

POLARAD spectrum analyzer, mod. SA-84W, 10 MHz to 40 GHz \$300. Call: **BILL** 714/688-3060

CARBIDE drills—No. 28, size for 6-32 machine screw. New \$6.75 @ postpaid. **CM CIRCUITS**, 22 Maple Avenue, Lackawanna, NY 14218

PICTURE TUBE MACHINE
We buy and sell NEW and USED CRT rebuilding machinery. **COMPLETE TRAINING.** Buy with CONFIDENCE from the ORIGINAL MFR.
For complete details send name, address, zip to:
LAKESIDE INDUSTRIES
4071 N. Elston Avenue
Chicago, Ill. 60618
Phone: 312-583-6565

10th Anniversary Sale

Featuring DELTA GRAB-A-BAGS!

It is the custom of some mail-order suppliers to create grab bags of various items in which they can unload all their accumulated junk on unsuspecting customers! Not so at Delta!!! Our philosophy is different..... Our grab bags contain the same high-quality merchandise we offer throughout our catalogs and flyers. Our Delta Grab-A-Bags are made up of items in which we have small lots that cannot make the catalog. The contents of each exceeds by many times the low "close-out" bargain prices! 100% guaranteed!

Anniversary Gift
Buy 9
GRAB-A-BAGS
10 Free

ERIE 2% Resistors

Our prices for these Erie 2% carbon film resistors are far lower than most 1% & 10% resistors. Full length leads.

<input type="checkbox"/> 1/8 WATT Assortment from 30 ohms to 240K Delta 8760R	<input type="checkbox"/> 1/4 WATT Assortment from 51 ohms to 150K Delta 8761R	<input type="checkbox"/> 1/2 WATT Assortment from 75 ohms to 2 megs Delta 8762R	GRAB-A-BAGS 300 PCS. FOR \$4
---	---	---	---

Potentiometer
GRAB-A-BAG
10 for \$1

100 for \$9

We have a large selection....all different sizes.... shapes....and values! About 60% are still in factory cartons. Made by Allen Bradley, CTS, Clarostat, etc. Wt. 1 lb. Delta No. 8989R

Gang Pots
40 FOR \$6

Delta No. 8902R
18 for \$3

2-gang, 3-gang, 4-gang, 5-gang, and 6-gang pots; almost all also include line switch. These are made by C-T-S (American made). All the popular resistance values, tapers & many of the pots are tapped. Any one of these pots would cost you more than the whole pack of 18 pieces.

Power Resistor 50 PCS. FOR \$3.50
GRAB-A-BAG

Quite a catch!....this assortment of 4 and 5 watt resistors of different resistance values. Very handy. Delta 8763R

Precision Resistor 35 PCS \$1.50
GRAB-A-BAG

4 Pcs \$5 No. 8764R

Build up your stocks the low-cost Delta way! We have accumulated a large number of precision resistors of many different values....ranging from a fraction of an ohm to several megohms...in power ranges from .01% to 1%. We are offering a well-assorted bag of 35 pcs of precision resistors at a price less than the cost of a single resistor.

Capacitor 1/4 LB. FOR \$2
GRAB-A-BAG 3 Pcs \$5

Every lab & experimenters' bench needs an assortment of disc capacitors. This Delta Grab-A-Bag contains values from a few pf to .2mf....and voltages ranging from 12V to 3 KV. They are marked and unmarked....mostly full length leads...some are P.C. mounts. A 1/4-lb. grosses approx. 100 to 250 assorted disc caps. Delta No. 2547R

\$100 STEREO AUTO RADIO

UNBELIEVABLE Push Buttons
12.99 AM / FM MULTIPLEX

One of America's largest independent manufacturers of automobile radios has given up! We've been fortunate in acquiring some of the last auto radios in production. These were AM-FM-MPX-Stereo sets....designed for new cars. The sets came right off the production line, and when the line stopped, they did not have the top metal cover & front bezel. They are, however, 100% operational & come complete with knobs & mounting nuts & push buttons. These high-quality sets are ideal for installing in your auto, camper, boat or any other place where 12 VDC is available. Delta No. 5725R

5730R	SPEAKERS\$5.95	2 for \$10
5726R	Dual imp. coil, 4/8ohms	\$8.95	2 for \$16
5727R	4-Ohms Ford speaker	\$5.95	2 for \$10
5728R	4-Ohms (not illus.)	\$7.95	2 for \$14

1980 Catalog Available!

Computer Board
GRAB-A-BAG

FREE

6 LBS FOR \$5 TTLs-C-MOS-V Reg. Transistors-Op Amps

Here's your chance to build your stock pile or replenish it! Well....DELTA's Computer Board Grab-A-Bag is one of the most inexpensive ways of doing it. We have a very wide & varied selection of computer boards. The parts on these boards can be easily removed with a Benz-O-Matic torch & a pair of tweezers. Complete instructions on parts removal are included. The following is a list of SOME of the parts found on these boards.

TTL & CMOS ICs..Voltage Regulators..Transistors..Power Transistors..Op Amps..Optical Couplers..Relays..Reed Relays..small Transformers..heat sinks..diodes..resistors..capacitors..SORS..etc.

Delta No. 9801R

MAIL-ORDER ADDRESS:

FREE 120-PG. 'SURPLUS' CATALOG

DELTA ELECTRONICS

176 SECOND AVE.
WALTHAM, MASS.
02154
Minimum Order \$8.00
TEL. (617) 388-4705

BANKAMERICARD
master charge

When in our area, northeastern Mass. or southern N.H. visit our retail at 7 Oakland St., Amesbury, Mass.

CIRCLE 25 ON FREE INFORMATION CARD

BULLET ELECTRONICS

P.O. Box 401244-R Garland, Texas 75040 (214) 278-3553

AY3-8910 PROGRAMMABLE SOUND GENERATOR


The AY3-8910 is a 40 pin LSI chip with three oscillators, three amplitude controls, programmable noise generator, three mixers, an envelope generator, and three D/A converters that are controlled by 8 BIT WORDS. No external pots or caps required. This chip hooked to an 8 bit microprocessor chip or Buss (8080, Z80, 6800 etc.) can be software controlled to produce almost any sound. It will play three note chords, make bangs, whistles, sirens, gunshots, explosions, bleets, whines, or grunts. In addition, it has provisions to control its own memory chips with two IO ports. The chip requires +5V @ 75ma and a standard TTL clock oscillator. A truly incredible circuit.

\$14.95 w/Basic Spec Sheet (4 pages)
60 page manual with S-100 interface instructions and several programming examples, \$3.00 extra

SE-01 SOUND EFFECTS KIT

* 76477 CHIP IS INCLUDED. EXTRA CHIPS \$2.95 EACH

* \$16.95
LESS SPEAKER & BATTERY

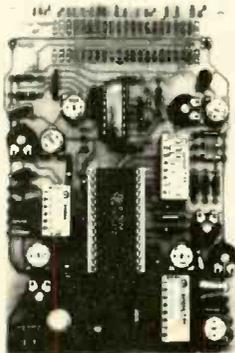


The SE-01 is a complete kit that contains all the parts to build a programmable sound effects generator. Designed around the new Texas Instruments SN76477 Sound Chip, the board provides banks of MINI DIP switches and pots to program the various combinations of the SLF Oscillator, VCO, Noise, One Shot, and Envelope Controls. A Quad Op Amp IC is used to implement an Adjustable Pulse Generator, Level Comparator and Multiplex Oscillator for even more versatility. The 3 1/4" x 5" PC Board features a prototype area to allow for user added circuitry. Easily programmed to duplicate Explosions, Phasor Guns, Steam Trains, or almost an infinite number of other sounds. The unit has a multiple of applications. The low price includes all parts,

assembly manual, programming charts, and detailed 76477 chip specifications. It runs on a 9V battery (not included). On board 100MW amp will drive a small speaker directly, or the unit can be connected to your stereo with incredible results! (Speaker not included).

ALLOW 3 WKS. FOR DELIVERY

A RARE FIND!

LAMBDA HIGH POWER REGULATOR 3205 MODULE

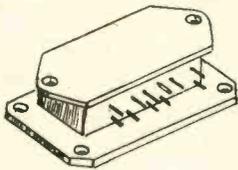

\$12.95
W/SPECS
LIMITED QTY.

- 5V @ 10A with 8-30VDC input.
- Current limiting, thermal shutdown and short protection.
- 2% Load regulation.
- Only 2 external components needed.

All you need to add is a transformer, rectifier, heatsink and filter cap to have a super regulated supply for 5 volts at 10 amps!


SPECIAL BONUS! Order the 3205 Module and get FREE a LAMBDA L-20-5 overvoltage protector that triggers at 6.6 volts up to 20 amps.

LAS15U - 1.5A Four Terminal Adjustable Regulator. 3-30V W/current limiting, short protection and thermal shutdown. TO-3 style. All units are prime. Spec sheets included. **\$2.50**

- * NO C.O.D.'s
- * SEND CHECK M.O. OR CHARGE CARD NO.
- * PHONE ORDERS ACCEPTED ON VISA AND MASTERCARD ONLY.
- (214) 278-3553 9:00 AM - 6:00 PM CST
- * ORDERS OVER 1 LB. SHIPPED VIA UPS

P
O
L
I
C
I
E
S

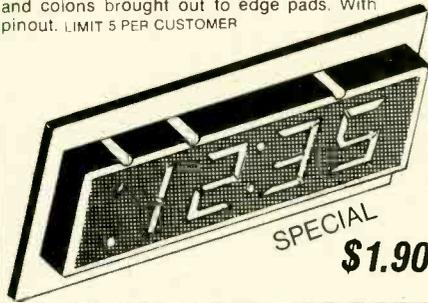4 DIGIT 1/2 INCH CHARACTER LED DISPLAY
Bowmar readout stick with colons. COMMON CATHODE ONLY. 100% Prime. All segments and colons brought out to edge pads. With pinout. LIMIT 5 PER CUSTOMER



SPECIAL
\$1.90

From T.I.: TL490 BAR/DOT DRIVER IC. Drives 10 LED's with adjustable analog steps. Units are cascadable up to 10 (100 steps). Drives LED's directly. Great for voltage, current, or audio displays. Similar in features to LM3914 with specs and circuit notes.

2.95

NEW!




XAN SUPER DIGITS

.6" JUMBO LED
7 SEGMENT
RED

99¢

6640 COMMON ANODE
6920 COMMON CATHODE

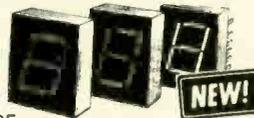

NEW!

NOW A SUPER READOUT AT A SUPER BUY! These are factory fresh prime LED readouts, not seconds or rejects as sold by others. Compare our price and send for yours today, but hurry, the supply is limited!

SPECIFY: COMMON ANODE OR COMMON CATHODE

NEW ITEMS

LM3046	(CA3046) Transistor Array	.75
LM3909	Led Flasher	.50
CA3086	RCA Transistor Array	.80
MC1438R	Power Op Amp/Driver	.50
1N4148	Prime, Full Lead	100/2.50
LM3302	Quad Comparator	.89
2SC1849	High Freq NPN TO-92	6/1.00

POTENTIOMETER ASSORTMENT

A mix of new, panel mount 3/8" bushing pots in various values. Some dual, some with switches.

10/2.00

1/2W RESISTOR ASSORTMENT

A good mix of 5% and 10% values in both full lead and PC lead devices. All new, first quality.

(Asst.) 200 pieces/ 2.00

SLIDE SWITCH ASSORTMENT

An outstanding bargain. Includes miniature and standard sizes and multiposition units. All new first quality, name brand switches. Try one pack and you'll reorder more: **SPECIAL - 12 for \$1.20** (Assortment)

- * ADD 5% FOR SHIPPING
 - * TX. RES. ADD 5% STATE SALES TAX
 - * FOREIGN ORDERS ADD 10% (EXCEPT CANADA) (20% AIRMAIL) U.S. FUNDS ONLY
 - * SORRY WE CANNOT SHIP INSURED TO MEXICO
- PRICES SUBJECT TO CHANGE WITHOUT NOTICE

9500@75V Filter Cap
Computer 2"x5 1/2"
Grade 2.95

ZENER GRAB BAG

A very nice assortment of 1/4, 1/8 & 1W zeners. Voltage ranges are from 2.7 to 30 VDC. Most have house # but we provide a cross over list to standard numbers. A great buy for any shop. 12 different types.

.50 ea.

MC1469R POSITIVE VOLTAGE REGULATOR

1/2 AMP COMPLETE SPECS AND APPLICATIONS SHOW HOW TO BUILD FIXED OR VARIABLE POWER SUPPLIES FROM 3 TO 30VDC. DRIVE EXTERNAL SERIES PASS FOR CURRENT TO 20 AMPS.

1.25 EA.
10/10.00
HOUSE #



QUAD MATCHED DIODES

4 1N914 type diodes that have been closely matched for use in bridge and balanced modulator circuits.

50¢ ONE SET (4)

PARTS

301 OP AMP 8 LEAD CAN	3/1.00
723 VOLT REG. 10 LEAD CAN	.50
13741 FET INPUT 741 MINI DIP	3/1.10
30.000 @ 15V COMPUTER GRADE	2.10
2N4000 NPN GEN. PURPOSE	8/1.00
2N4002 PNP COMPLIMENT	8/1.00
2N6028 P.U.T. W/SPECS	.50
LM380 2W AUDIO IC W/SPECS	1.05
LM377 DUAL LM380 W/SPECS	2.50
7815 VOLT REG. 1A 15V	.69
725 LOW NOISE OP AMP	.99
11-1 OPTO ISOLATOR MINI DIP	.60
*MEM 631 DUAL GATE MOSFET	
DIODE PROTECTED SIMILAR	
TO 40673	.50
MV1624 VARICAP DIODE 10 PFD	.49
1N4003 1A 200V DIODE	15/1.00
TIP30 TAB PNP POWER	3/1.00
*MC1351P FM IF. DISC IC	.50

*INDICATES ITEM IS "HOUSE NUMBERED"

LED'S

JUMBO GREEN	4/ .89
JUMBO RED	5/ .89
MEDIUM RED (1/8")	.15
MEDIUM GRN OR YELLOW	.16

7 WATT AUDIO AMP KIT

SMALL, SINGLE HYBRID IC AND COMPONENTS FIT ON A 2" x 3" PC BOARD (INCLUDED). RUNS ON 12 VDC. GREAT FOR ANY PROJECT THAT NEEDS AN INEXPENSIVE AMP. LESS THAN 3% THD @ 5 WATTS. COMPATIBLE WITH SE-01 SOUND KIT. **\$5.95**

6 DIGIT AUTO/VAN CLOCK

- LARGE 1" CHARACTERS (LED)
- QUARTZ XTAL TIMEBASE
- ALARM & SNOOZE OPTIONS
- NOISE FILTERING
- EASY TO ASSEMBLE
- 4 1/2" x 3" x 1 1/2"
- DRILLED & PLATED PC BOARDS

COMPLETE KIT
12 VDC **\$16.95**

ULTRASONIC RELAY KIT


INVISIBLE BEAM WORKS LIKE A PHOTO ELECTRIC EYE. USE UP TO 25 FT APART. COMPLETE KIT. ALL PARTS & PC BOARDS. **\$21.50**

100 W CLASS A POWER AMP KIT

Dynamic Bias Class "A" circuit design makes this unit unique in its class. Crystal clear, 100 watts power output will satisfy the most picky fans. A perfect combination with the TA-1020 low T.I.M. stereo pre-amp.

Specifications:

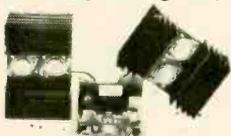- Output power: 100W RMS into 8-ohm 125W RMS into 4-ohm
- Frequency response: 10Hz - 100 KHz
- T.H.D.: less than 0.008%
- S/N ratio: better than 80dB
- Input sensitivity: 1V max.
- Power supply: $\pm 40V @ 5 amp$



TA-1000 KIT \$51.95
Power transformer \$15.00 each

SANWA

COMPACT - LIGHTWEIGHT - ULTRA SLIM BATTERY CHECKER - LED TESTER
T-55D (w/o temp probe) \$44.50
T-55THD (temp probe) \$66.50

SPECIFICATIONS

Ranges

DC Voltage: 150mV, 500mV, 1.5V, 6V, 15V, 50V, 250V, 1kV (All 20k Ω /V)

25kV *Using HV probe)

DC Current: 50 μ A, 2.5mA, 25mA, 250mA (500mV drop)

AC Voltage: 15V, 500V, (9k Ω /V) AC Current: 6mA, 6A (2V and 55mV drop)

Resistance: 10k Ω 100k Ω 1M Ω 5M Ω (max. calbtn) 100 Ω 1k Ω 10k Ω 50k Ω (mid scale) 10k Ω 100k Ω

Load Current: 30mA 3mA 300mA

Load Voltage: 3V 3V 3V

Decibels: -10 to +55dB

Batt Check: 0.9 to 1.5V (10 Ω load)

LED Check: (Available)

Temperature: -50 $^{\circ}$ to +100 $^{\circ}$ C and 0 $^{\circ}$ to +200 $^{\circ}$ C

*Probe not supplied with T-55D)

Accuracy

DC Voltage: $\pm 2.5\%$ f.s.d.

DC Current: $\pm 2.5\%$ f.s.d.

Batt Check: $\pm 2.5\%$ f.s.d.

AC Voltage/Power on 1.5V range: $\pm 5\%$ f.s.d.

AC Voltage/Power above 15V range: $\pm 3.5\%$ f.s.d.

AC Current: $\pm 5\%$ f.s.d.

Resistance/Temperature: $\pm 3\%$ of arc

Dimensions: 146 x 97 x 28mm thick

Weight: 240g

Instrument supplied with Batteries 1.5V (UM-3 or R6)x2

Fuse & Spare: 500mA 250V

Temperature Probe: (T-55THD only)



NEW MARK III 9 Steps 4 Colors LED VU

Stereo level indicator kit with arc-shape display panel!!! This Mark III LED level indicator is a new design PC board with an arc-shape 4 colors LED display (change color from red, yellow, green and the peak output indicated by rose). The power range is very large, from -30dB to +5dB. The Mark III indicator is applicable to 1 watt - 200 watts amplifier operating voltage is 3V - 9V DC at max 400 MA. The circuit uses 10 LEDs per channel. It is very easy to connect to the amplifier. Just hook up with the speaker output!

IN KIT FORM \$18.50

MARK II SOUND ACTIVATED SWITCH KIT

A new designed circuit employed 2 I.C., a DPDT relay with a led indicator. A condenser microphone comes with the kit. The relay can handle up to 200 watts contact to allow to control most things. Just click the finger, the relay will close, the second click will release it. Sensitivity can be adjusted by an on board trim-pot. Operating voltage 9V D.C. TY-18 \$8.50 PER KIT



MARK IV 15 STEPS LED POWER LEVEL INDICATOR KIT

This new stereo level indicator kit consists of 36 4-color LED (15 per channel) to indicate the sound level output of your amplifier from -36dB ~ +3dB. Comes with a well-designed silk screen printed plastic panel and has a selector switch to allow floating or gradual output indicating. Power supply is 6 ~ 12V D.C. with THG on board input sensitivity controls. This unit can work with any amplifier from 1W to 200W!

Kit includes 70 pcs. driver transistors, 38 pcs. matched 4-color LED, all other electronic components. PC board and front panel.



MARK IV KIT \$31.50

30W + 30W STEREO HYBRID AMPLIFIER KIT

It works in 12V DC as well! Kit includes 1 PC SANYO STK-043 stereo power amp. IC LM 1458 as pre amp, all other electronic parts, PC Board, all control pots and special heat sink for hybrid. Power transformer not included. It produces ultra hi-fi output up to 60 watts (30 watts per channel) yet gives out less than 0.1% total harmonic distortion between 100MHz and 10KHz



\$32.50 PER KIT

BATTERY POWERED FLUORESCENT LANTERN MODEL 888 R

FEATURES

- Circuitry: designed for operation by high efficient, high power silicon transistor which enable illumination maintain in a standard level even the battery supply drops to a certain low voltage.
- 9" 6W cool/daylight miniature fluorescent tube.
- 8 x 1.5V UM-1 (size D) dry cell battery.
- Easy sliding door for changing batteries.
- Stainless reflector with wide angle increasing illumination of the lantern.



\$10.50 EA

STEREO AMPLIFIER



60 W

60 W

COMPLETED UNIT - NOT A KIT!

OCL pre amp. & power stereo amp. with bass, middle, treble 3-way tone control. Fully assembled and tested, ready to work! Total harmonic distortion less than 0.5% at full power. Output maximum is 60 watts per channel at 8 Ω . Power supply is 24 - 36V AC or DC. Complete unit. Assembled \$49.50 ea. Power transformer \$ 8.50 ea.

5W AUDIO AMP KIT

2 LM 380 with Volume Control

Power Suply 6 18V DC

ONLY \$6.00 EACH



PROFESSIONAL PANEL METERS



Type MU-52E

A. 0-50UA 8.50 ea.

B. 0-30VDC 8.50 ea.

C. 0-50VDC 8.50 ea.

D. 0-3ADC 9.00 ea.

E. 0-100VDC 9.00 ea.

All meters white face with black scales. Plastic cover.

0.5" LED ALARM CLOCK MODULE

ASSEMBLED! NOT A KIT!

Features: • 4 digits 0.5" LED Displays • 12 hours real time format • 24 hours alarm audio output • 59 min. countdown timer • 10 min. snooze control.

ONLY \$7.00 EACH

SPECIAL TRANSFORMER FOR CLOCK \$1.50 EACH



DIGITAL AUTO SECURITY SYSTEM

4 DIGITS PERSONAL CODE!!
SPECIAL \$19.95



- proximity triggered
- voltage triggered
- mechanically triggered

This alarm protects you and itself! Entering protected area will set it off, sounding your car horn or siren you add. Any change in voltage will also trigger the alarm into action. If cables within passenger compartment are cut, the unit protects itself by sounding the alarm.

3-WAY PROTECTION!

All units factory assembled and tested - Not a kit!

A NEW LED ARRAY AND DRIVER FOR LEVEL METERS

This series covers a wide range of level indication uses, output and input voltage, time related change, temperature, light measurement and sound level. The problem of uneven brilliance often encountered with LED arrangements as well as design problems caused by using several units of varying size are substantially reduced. 12 LEDs in one bar:

LED ARRAY

GL-112R3 Red, Red, Red \$5.50
GL-112N3 Green, Yellow, Red \$6.50
GL-112M2 Green, Green, Red \$6.50
GL-112G3 Green, Green, Green \$6.50



LED DRIVERS

1R 2406G is an I.C. specially designed to drive 12 LED. The number of LED is linearly illuminated according to the control voltage input terminal 21. Operating voltage is 9 12V D.C. \$5.35 EACH

PROFESSIONAL FM WIRELESS MICROPHONE

TCT model WEM-16 is a factory assembled FM wireless microphone powered by an AA size battery. Transmits in the range of 88-108MHz with 3 transistor circuits and an omni-directional electric condenser. Element built-in plastic tube type case; mike is 6 1/4" long. With a standard FM radio, can be heard anywhere on a one-acre lot; sound quality was judged very good.

\$16.50

FLASHER LED

Ur ique design combines a jumbo red LED with an IC flasher chip in one package. Operates directly from 5V-7V DC. No dropping resistor needed. Pulse rate 3Hz @ 5V 20mA.

2 for \$2.20

LCD CLOCK MODULE!

• 0.5" LCD 4 digits display • X'tal controlled circuits • D.C. powered (1.5V battery) • 12 hr. or 24 hr. display • 24 hr. alarm set • 60 min. countdown timer • On board dual back-up lights • Dual time zone display • Stop watch function.

NIC1200 (12 hr) \$24.50 EA.

NIC2400 (24 hr) \$26.50 EA.



MINI-SIZED I.C. AM RADIO

Size smaller than a box of matches!

Receives all AM stations.

Batteries and ear phones included.

Only \$10.50




12 DC MINI RELAY

6V SPDT 2 AMP 1.30
12V SPDT 3 AMP 1.60
12V DPDT 2 AMP 2.50
12V DPDT 3 AMP 3.50



LINEAR SLIDE POT

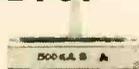500 Ω SINGLE
Metal Case 3" Long
2 FOR \$1.20



CONDENSER MICROPHONE

Sub-Mini Size

FET Transistor Built-in \$2.50 each



FLUORESCENT LIGHT DRIVER KIT



With Case Only
\$6.50 Per Kit

12V DC POWERED
Lights up 8 ~ 15 Watt Fluorescent Light Tubes. Ideal for camper, outdoor, auto or boat. Kit includes high voltage coil, power transistor, heat sink, all other electronic parts and PC Board, light tube not included!

THE MOST ADVANCED TIMEPIECE OF ITS KIND IN THE WORLD!

LCD Quartz Alarm Chronograph with calendar and dual time zone!! Watch is the same as Seiko but you pay a lot more for the name!



- 24 hour alarm • Chronograph counts up to 12 hrs., 59 mins. 59.9 sec. • Precision of chrono up to 1/10 sec. indicated by 10 moving arrows!! • Lap time (with chrono running uninterrupted) • Time displays by LCD for hour, min., sec., day, date of the week and AM/PM. • Calendar gives out date-day • Dual time zone for any two cities of the world at your own choice. • With light switch to allow you to see the time in the dark!

Regular Price \$85.50
SPECIAL \$49.95

One Year Full Warranty

ELECTRONIC DUAL SPEAKER PROTECTOR



Cut off when circuit is shorted or over load to protect your amplifier as well as your speakers. A must for OCL circuits.

KIT FORM
\$8.75 EA.

"FISHER" 30 WATT STEREO AMP



Super Buy
Only \$18.50

MAIN AMP (15W x 2)
Kit includes 2 pcs. Fisher PA 301 Hybrid IC all electronic parts with PC Board. Power supply \pm 16V DC (not included). Power band with (KF 1% \pm 3dB). Voltage gain 33dB. 20Hz - 20KHz.

SUPER 15 WATT AUDIO AMP KIT

Uses STK-015 Hybrid Power Amp
Kit includes: STK-015 Hybrid IC, power supply with power transformer, front Amp with tone control, all electronic parts as well as PC Board. Less than 0.5% harmonic distortion at full power 1/2dB response from 20-100,000 Hz. This amplifier has QUASI - Complimentary class B output. Output max is watt (10 watt RMS) at 4 Ω . ONLY \$23.50 each



HICKOK LX303 DIGITAL LCD MULTIMETER



• 3 1/2 digits display • 200 hours 9V battery life • Auto zero; polarity; overrange indication • 100MV DC F.S. sensitivity • 19 ranges and functions • D.C. volt: 0.1 MV to 1000V • A.C. volt: 0.1 V to 600 V • Resistance: 0.1 Ω to 20 M Ω • D.C. current: 0.01 A to 100 MA

OUR PRICE \$71.45

PUSH-BUTTON SWITCH



N/Open Contact
Color: Red, White, Blue, Green, Black
3/\$1.00
N/Close also Available
50¢ each
LARGE QTY. AVAILABLE

HEAVY DUTY CLIP LEADS



10 pairs - 5 colors Alligator clips on a 22" long lead. Ideal for any testing.
\$2.20/pack

MANY SOUND DECISIONS!



\$3.60 EACH

Solid state sound indicator operating voltage 6V DC 30mA. Small size approximately 3/4" x 1 1/4".

Model EB2116 (Continuous)
Model EB2126 (Slow Pulse)
Model EB2136 (Fast Pulse)



Continuous



Slow pulse



Fast pulse

ELECTRET CONDENSER MICROPHONE W TIE-CLIP



Sensitivity: 65dB \pm 3dB (At 1KHz)
Impedance: 600 OHM Freq. Response: Material: Aluminum 50 15,000 Hz
Cord: 10 ft. Length \$19.50 EACH

ELECTRONIC ALARM SIREN COMPLETE UNIT



AU-999 \$7.50

Ideal for use as an Alarm Unit or hookup to your car back-up to make a reverse indicator. Light Output up to 130dB. Voltage supply 6 12V



Sub Mini Size
PANEL METER
500 UA
ONLY \$1.60 ea.

TRANSFORMERS ALL 117 VOLT INPUT

30V	4 AMP	\$8.50 EA.
36V CT	3 AMP	\$10.50 EA.
48V CT	3 AMP	\$10.50 EA.
24V CT	3 AMP	\$10.50 EA.
24V CT	0.8 AMP	\$2.50 EA.
12V CT	0.5 AMP	\$2.50 EA.
12V CT	120 MA	\$1.80 EA.

AC POWER SUPPLY

12V AC	Output	200 MA	\$2.75 EA.
16V CT AC	Output	100 MA	\$2.10 EA.
6V DC	Output	120 MA	\$1.90 EA.
12V DC	Output	100 MA	\$1.90 EA.



ULTRASONIC SWITCH KIT

Kit includes the Ultra Sonic Transducers, 2 PC Boards for transmitter and receiver. All electronic parts and instructions. Easy to build and a lot of uses such as remote control for TV, garage door, alarm system or counter. Unit operates by 9-12 DC. \$15.50

COMPLETE TIME MODULE

0.3" digits LCD Clock Module with month and date, hour, minute and seconds. As well as stop watch function!! Battery and back up light is with the module. Size of the module is 1" dia. Ideal for use in auto panel, computer, instrument and many others! \$8.95 EACH



SOUND ACTIVATED SWITCH



\$1.75 ea.

All parts completed on a PC Board SCR will turn on relay, buzzer or trigger other circuit for 2 - 10 sec. (adjustable). Ideal for use as door alarm, sound controlled toys and many other projects. Supply voltage 4.5V 9V D.C. 2 for \$3.00

FM WIRELESS MIC KIT



It is not a pack of cigarettes. It is a new FM wireless mic kit! New design PC board fits into a plastic cigarette box (case included). Uses a condenser microphone to allow you to have a better response in sound pick-up. Transmits up to 350 ft.! With an LED indicator to signal the unit is on #FMM2 KIT FORM \$7.95

REGULATED DUAL VOLTAGE SUPPLY KIT

\pm 30V DC 800 MA adjustable, fully regulated by Fairchild 78MG and 79MG voltage regulator I.C. Kit includes all electronic parts, filter capacitors, I.C., heat sinks and P.C. board.
\$12.50 PER KIT

3 AA size fast charge (4 hours), NI-CD by Sanyo. All brand new and fresh 450 mah per cell. Limited supply. \$5.40 PER PAK

BECKMAN FET LIQUID CRYSTAL DISPLAY

Overall size 2" x 1.2" 0.5" characters reflective type.



737-01

Model 737-01 - for clock 4 digits with PM, alarm, snooze, colon indicators. Model 739-04 - for panel meter 4 digits.



739-04

Model 739-03 - for panel meter 3 1/2 digits with \pm sign and over range indicator.



739-03

All displays include zeber connectors and front bezel. With data sheets. Your choice - any model \$7.50 EACH

POWER SUPPLY KIT

0-30V D.C. REGULATED
Uses UA723 and ZN3055 Power TR output can be adjusted from 0-30V, 2 AMP. Complete with PC board and all electronic parts. Transformer for Power Supply. 0-30 Power Supply 2 AMP 24V x 2 \$8.50 \$10.50 each



I.C. TEST CLIPS

Same as the E-Z clips \$2.75
With 20" Long Leads
In Black and Red Colors per pair



SOUND GENERATOR I.C.

Creates almost any type of sound - gun shot, explosion, train, car crash, star war, birds, organ ext. A built-in audio amplifier provides high level output. Operates from one 9V battery, 28 pin dip; we supply the datas. \$2.90 EACH



ELECTRONIC SWITCH KIT

CONDENSER TYPE
Touch On Touch Off
uses 7473 I.C. and
12V relay
\$5.50 each



1 WATT AUDIO AMP

All parts are pre-assembled on a mini PC Board. Supply Voltage 6 9V D.C. SPECIAL PRICE \$1.95 ea.



LOW TIM DC STEREO PRE-AMP KIT TA-10 20

Incorporates brand-new D.C. design that gives a frequency response from 0Hz - 100KHz \pm 0.5dB! Added features like tone defeat and loudness control let you tailor your own frequency supplies to eliminate power fluctuation! Specifications: • T.H.D. less than .005% • T.I.M. less than .005% • Frequency response: DC to 100KHz \pm 0.5dB • RIAA deviation: \pm 0.2dB • S/N ratio: better than 70dB • Sensitivity: Phono 2MV 47K/Aux. 100MV 100K • Output level: 1.3V • Max. output: 15V • Tone control: bass \pm 10dB @ 50Hz/treble \pm 10dB @ 15Hz • Power supply: \pm 24 D.C. @ 0.5A
Kit comes with regulated power supply, all you need is a 48V C.T. transformer @ 0.5A
ONLY \$44.50
X'former



SOLID STATE ELECTRONIC BUZZER

Mini size 1" x 3/4" x 3/4"
Supply voltage 1.5V - 12V
Ideal for Alarm or Tone Indicator



\$1.50 each

FORMULA INTERNATIONAL INC.

	SHIPPING AND HANDLING CHARGES	
	Under \$50.00 purchase	Over \$50.00 purchase
Inside California	10%	5%
Outside Calif. (Includes Mexico & Canada)	15%	10%
Overseas	25%	20%

Minimum Order \$10.00/Calif. Residents Add 6% Sales Tax
Phone Orders Accepted on Visa or MC ONLY, NO C.O.D./Store Hours 10-7 Mon. thru Sat.

12/79
Send \$1.00
For Detailed
Catalogue

12603 CRENSHAW BLVD., HAWTHORNE, CA 90250
PHONE: (213) 973-1521 • (213) 675-1162

TREMENDOUS BUYS In New And Gov't Surplus Equipment

Dial Telephone "SUPER BUY"

• Save us the labor costs of cleaning and polishing and save \$553 on standard dial telephones. Work on any commercial system. Complete. (no parts missing) in good working order. Your choice of desk or wall models. These are take-outs from commercial service (not toys). Instructions furnished.



Wall Model: #735-WBE
Desk Model: #715-DE

\$7.95

PREPAID IN U.S.A. Does not include HAWAII, ALASKA, P.R.

FREE CATALOG Shows BIG SAVINGS On

- ELECTRONICS • ELECTRICAL • ALARM SYSTEMS • TELEPHONES • PUMPS
- BINOCULARS • GEAR MOTORS • WINCHES • SURVIVING INSTRUMENTS
- GENERATORS • COMPRESSORS • HYDRAULICS • POWER TOOLS • WELDERS
- POWER PLANTS • CHEMICAL SPRAYING • TARPOLYMS • MANY OTHERS

Surplus Center Box 82209-RE Lincoln, Ne. 68501

Govt. SURPLUS ELECTRONIC EQUIPMENT CATALOG

New ITEMS . . . New BARGAINS!
FREE UPON REQUEST!
Send today for FREE copy of NEW CATALOG WS-79. Address Dept. RE

FAIR RADIO SALES
1016 E. EUREKA • Box 1105 • LIMA, OHIO • 45802

New **SATELLITE** For the TV home.



Supersharp Reception—Color Like Never Before
Get over 50 channels of television directly from the satellite! HBO, Showtime, the Superstations, and sports from around the world!



Works Anywhere!

Buy complete or build and save. Our book tells everything! Send \$7.95 today or call our 24 hr. C.O.D. Hotline!

(305) 869-4283

SPACECOAST RESEARCH
P.O. Box 442, Dept. F, Altamonte Springs, FL 32701

PASS FCC EXAMS

The Original FCC Tests-Answers exam manual that prepares you at home for FCC First and Second class Radiotelephone licenses. Newly revised multiple-choice exams cover all areas tested on the actual FCC exam. Plus "Self-Study" Ability Test. Proven! \$9.95 postpaid. Moneyback Guarantee.



COMMAND PRODUCTIONS P.O. Box 26348 • E
Radio Engineering Division San Francisco, CA 94126

BEARFINDER RADAR DETECTOR

2999 AU-561
Reg. ~~399~~

- Sensitivity Control • Lighter Plug
- Detects Stationary & Moving Radar
- For 12 Volt Systems • Easy mount/dismount.
- 6 x 3 x 4 1/2" • Shpg. Wt. 2 lbs.

(Prohibited in some States)

RECORDING TAPES 8-TRACK CASSETTE

Reg. 1.49

69¢ EA. TA-907

\$1 Pkg. of 3 TA-879

FULL RANGE SPEAKER SYSTEM

1499 PR. SP-638

- Mar-Proof Walnut Vinyl Finish Over Particle Board
- Complete With 9' Hook-Up Cable W/ RCA Pin Plug
- 17 1/4" x 10" x 4 1/4"
- 8 Ohms • 17 lbs.

3 1/2" PIEZO ELECTIC SUPER TWEETER

549 Reg. 799
SP-403

Maximum driving voltage of 35V RMS continuously. 20 watts. 3 1/2 x 2 1/4". Wt. 2 lbs.

AM TRANSISTOR RADIO

99¢ AS IS XM-857

- Pocket Type • All Are in Need of Repairs
- Great for Parts Bargain • Styles May Vary
- No Instructions or Schematic • Wt. 1 lb.

6 x 9" 5.5 OZ. MAGNET HEAVY-DUTY SPEAKER

299 Reg. 699
SP-626

- 4-8 Ohms • Dust Cover
- For Auto, Van, RV and Home Use • Wt. 3 lbs.

PARTS BARGAIN 20 lb. SURPRISE KIT

399 Reg. 1099
XX-197

- You Could Find Capacitors, Motors, Resistors, Parts & Hardware Needed By Hobbyists

SOUND EFFECTS GENERATOR BASIC KIT

Now CHANEY ELECTRONICS MAKES IT POSSIBLE TO BUILD YOUR OWN SOUND EFFECTS GENERATOR WITHOUT SPENDING A FORTUNE. WE SUPPLY YOU WITH THE 1176477 SOUND CHIP PLUS AN ETCHED AND DRILLED GLASS EPOXY PC BOARD WITH SCHEMATIC AND LAYOUT INSTRUCTIONS. THIS BOARD MAKES IT SIMPLE TO BUILD A GENERATOR CAPABLE OF PHASED SOUNDS, LOCOMOTIVE, SIRENS, AIRPLANES, CLOCKS, ETC. DOES NOT REQUIRE DIP SWITCHES OR OTHER EXPENSIVE UNUSUAL COMPONENTS. YOU SUPPLY ONLY A FEW STANDARD RESISTORS, CAPACITORS, SWITCHES, POTS, SPEAKER, 2N2222 TRANSISTOR AND 9V BATTERY.

BASIC KIT CONTAINING 1176477, PC BOARD AND INSTRUCTIONS C23883 DMI **\$5.95**

2N2222 TRANSISTOR FOR ABOVE C23884 .39 EACH

IF YOU HAVE ALREADY PURCHASED THE 1176477 CHIP YOU MAY BUY THE PC BOARD AND INSTRUCTIONS ONLY. C23885 \$4.00

LA/CR SLAVE TRIGGER KIT

WE SUPPLY ALL THE COMPONENTS PLUS SCHEMATIC TO MAKE A SENSITIVE SLAVE TRIGGER WHICH WILL FIRE YOUR SLAVE STROBE WHEN YOU TRIGGER YOUR MASTER STROBE. C23886 \$1.50

LED Flasher Kit

Simple to build and fun to use. Includes 100 LEDs, transistors, and PC board. C23887 \$2.49

6VDC Xenon Flasher Kit

Simple to build and fun to use. Includes 100 LEDs, transistors, and PC board. C23888 \$2.00

120 VAC Xenon Strobe Kit

Complete, yet simple to use. Includes 100 LEDs, transistors, and PC board. C23889 \$7.50

Wheel of Fortune

Popular game device. Includes 100 LEDs, transistors, and PC board. C23890 \$8.99

LED Panel Mounting Kit

12 sets for \$1.00. C23891

SLA-1 Readout

4 sets for \$2.00. C23892

Jumbo Red LED

10 for \$1.00. C23798

RO170 Rectifier

100 for \$15.00. C23894

GE Sub-C Nical

2 for \$2.00. C23876

Color Crystal

1 for \$1.00. C23877

Tube Specials

2 for \$1.00. C23878

Alco Knob

2 for \$1.00. C23879

AA Nicalds & Charger

2 for \$6.95. C23880

CHANEY Electronics inc.

P.O. BOX 27038, DENVER, CO. 80227 (303) 781-5750

Send for our free giant catalog of unique items!!!

Olson electronics

Dept. LW 260 S. Forge St. Akron, Ohio 44327

NAME _____

ADDRESS _____

CITY _____

STATE _____ ZIP _____

Qty	Stk #	Description	Price Ea.	Total

CHARGE CARD ORDERS OVER \$25
CALL FREE 1-800-321-2424
OHIO RESIDENTS CALL 1-216-535-1800

PLEASE send me a free subscription to Olson Value Packed Catalog. (Within the Continental USA Only)

Tax _____
Postage _____
Total _____

FREE!

RADIO-ELECTRONICS

AVAILABLE NOW!

ONLY \$3.95
Add \$1.00 for shipping

JAPANESE TRANSISTOR SUBSTITUTION MANUAL



An invaluable Japanese to Japanese substitution guide for approximately 3000 transistors.

- * Covers the 2SA, 2SD, 2SC and 2SD series
- * Introduction includes a guide to understanding Japanese transistors
- * A 90 page 8 1/2" by 11" soft cover book

PARTS PROCUREMENT PROBLEMS

FUJI-SVEA Has the Largest Inventory of Original Japanese Parts Anywhere

Seeking Original Japanese Replacement Parts for CB, TV and Stereo Repair Use?

TYPE	25-UP	10-24	1-9	TYPE	25-UP	10-24	1-9	TYPE	25-UP	10-24	1-9	TYPE	25-UP	10-24	1-9	TYPE	25-UP	10-24	1-9
2SA 473	4.05	.55	.60	2SB 346	30	35	40	2SC 693F	20	27	30	2SC 1226A	50	55	60	2SD 234	60	70	.80
2SA 483	2.00	2.20	2.50	2SB 367	1.10	1.25	1.40	2SC 696	1.00	1.20	1.30	2SC 1237	1.80	2.00	2.25	2SD 235	60	70	.80
2SA 484	1.50	1.75	1.95	2SB 368B	1.80	2.00	2.25	2SC 708	1.30	1.45	1.60	2SC 1238	2.20	2.70	2.90	2SD 261	35	40	45
2SA 485	1.40	1.60	1.80	2SB 395	70	80	90	2SC 710	20	27	30	2SC 1279	50	55	60	2SD 287	2.50	2.70	2.90
2SA 489	1.10	1.25	1.40	2SB 381	30	35	40	2SC 711	20	27	30	2SC 1306	1.30	1.45	1.60	2SD 300	4.50	5.00	5.60
2SA 490	70	80	90	2SB 400	30	35	40	2SC 712	20	27	30	2SC 1307	1.90	2.10	2.40	2SD 313	60	70	.80
2SA 493	45	53	59	2SB 405	30	35	40	2SC 715	30	35	40	2SC 1310	20	27	30	2SD 315	60	70	.80
2SA 495	30	35	40	2SB 407	80	90	100	2SC 717	35	40	45	2SC 1312	20	27	30	2SD 325	60	70	.80
2SA 496	50	64	70	2SB 415	30	35	40	2SC 717B	1.00	1.20	1.30	2SC 1319G	20	27	30	2SD 330	60	70	.80
2SA 497	1.00	1.20	1.30	2SB 434	80	90	100	2SC 730	3.00	3.20	3.40	2SC 1316	4.20	4.40	4.90	2SD 350	3.80	4.00	4.40
2SA 505	50	64	70	2SB 435	80	1.10	1.20	2SC 731	2.50	2.70	2.90	2SC 1317	20	27	30	2SD 380	5.20	5.40	5.95
2SA 509	30	35	40	2SB 440	40	53	59	2SC 732	20	27	30	2SC 1318	35	40	45	2SD 381	85	100	1.10
2SA 525	50	64	70	2SB 449	1.30	1.45	1.60	2SC 733	20	27	30	2SC 1325A	6.50	6.90	7.60	2SD 424	3.80	4.00	4.40
2SA 530	1.50	1.70	1.90	2SB 461	90	1.10	1.20	2SC 734	20	27	30	2SC 1327	20	27	30	2SD 425	2.90	3.20	3.40
2SA 537A	1.50	1.70	1.90	2SB 463	90	1.10	1.20	2SC 735	20	27	30	2SC 1330	50	55	60	2SD 426	60	70	.80
2SA 539	40	45	50	2SB 471	1.10	1.25	1.40	2SC 738	20	27	30	2SC 1335	50	55	60	2SD 427	1.80	2.00	2.25
2SA 545	45	53	59	2SB 472	2.10	2.50	2.80	2SC 756	1.50	1.80	2.00	2SC 1342	45	53	59	2SD 525	90	1.10	1.20
2SA 561	30	35	40	2SB 473	80	90	100	2SC 756A	1.50	1.80	2.00	2SC 1344	45	53	59	2SD 526	60	70	.80
2SA 562	30	35	40	2SB 474	70	80	90	2SC 763	.35	40	45	2SC 1358	4.20	4.40	4.90	2SK 19BL	50	55	60
2SA 564A	20	27	30	2SB 481	90	1.10	1.20	2SD 772	30	35	40	2SC 1359	30	35	40	3SK 22Y	1.40	1.60	1.80
2SA 565	70	80	90	2SB 492	60	70	80	2SC 773	35	40	45	2SC 1360	50	55	60	3SK 39	90	1.10	1.20
2SA 566	2.50	2.70	3.00	2SB 507	80	90	100	2SC 774	1.00	1.20	1.30	2SC 1362	35	40	45	3SK 40	90	1.10	1.20
2SA 606	1.00	1.20	1.30	2SB 509	1.10	1.20	1.30	2SC 775	1.40	1.60	1.80	2SC 1364	35	40	45	3SK 41	1.30	1.45	1.60
2SA 607	1.10	1.25	1.40	2SB 511	10	80	90	2SC 776	2.00	2.20	2.50	2SC 1377	3.20	3.40	3.70	3SK 45	1.30	1.45	1.60
2SA 624	70	80	90	2SB 514	70	80	90	2SC 777	3.00	3.25	3.50	2SC 1383	30	35	40	AN 203	1.40	1.60	1.80
2SA 627	3.10	3.30	3.60	2SB 523	70	80	90	2SC 777	2.90	3.20	3.40	2SC 1384	35	40	45	AN 2140	1.50	1.70	1.90
2SA 628	30	35	40	2SB 526C	70	80	90	2SC 781	1.90	2.10	2.40	2SC 1396	45	53	59	AN 239	4.20	4.40	4.90
2SA 634	40	45	50	2SB 527	90	1.10	1.20	2SC 783	2.10	2.50	2.80	2SC 1398	70	80	90	AN 247	2.50	2.70	3.00
2SA 640	30	35	40	2SB 528D	70	80	90	2SC 784	30	35	40	2SC 1402	45	53	59	AN 274	1.50	1.75	1.95
2SA 642	30	35	40	2SB 529	70	80	90	2SC 785	35	40	45	2SC 1403	3.0	3.40	3.70	AN 313	3.00	3.20	3.40
2SA 643	30	40	45	2SB 530	3.20	3.40	3.70	2SC 785	35	40	45	2SC 1407	50	55	60	AN 315	1.80	2.00	2.25
2SA 653	1.90	2.10	2.40	2SB 531	1.80	2.00	2.25	2SC 790	80	90	100	2SC 1419	60	70	80	BA 511A	1.80	2.00	2.25
2SA 659	35	40	45	2SB 536	1.00	1.20	1.30	2SC 793	2.00	2.20	2.50	2SC 1444	1.60	1.80	2.00	HA 521	1.90	2.10	2.40
2SA 661	50	64	70	2SB 537	1.00	1.20	1.30	2SC 799	2.00	2.20	2.50	2SC 1445	2.50	2.70	2.90	HA 1151	1.50	1.75	1.95
2SA 663	3.65	3.80	4.20	2SB 539	3.20	3.40	3.70	2SC 828	20	27	30	2SC 1447	60	70	80	HA 1156W	1.60	1.80	2.00
2SA 666	35	40	45	2SB 540	3.40	3.70	4.00	2SC 829	20	27	30	2SC 1448	60	70	80	HA 1306W	2.00	2.20	2.50
2SA 671	80	90	100	2SB 554	3.00	3.20	3.50	2SC 830H	2.5	2.70	3.00	2SC 1449	60	70	80	HA 1339	2.50	2.70	3.00
2SA 672	30	35	40	2SB 556	2.20	2.40	2.70	2SC 831	35	40	45	2SC 1451	1.00	1.10	1.20	HA 1339A	2.50	2.70	3.00
2SA 673	35	40	45	2SB 557	2.10	2.50	2.80	2SC 839	30	35	40	2SC 1454	3.20	3.40	3.70	HA 1342A	2.50	2.70	3.00
2SA 678	35	40	45	2SB 561B	35	40	45	2SC 853	70	80	90	2SC 1475	50	55	60	HA 1366W	4.20	4.40	4.90
2SA 679	4.20	4.40	4.90	2SB 564	40	53	59	2SC 867	3.20	3.40	3.70	2SC 1478	50	55	60	LA 4031P	1.80	2.00	2.25
2SA 680	4.20	4.40	4.90	2SB 585	1.10	1.40	1.50	2SC 877A	3.20	3.40	3.70	2SC 1509	50	55	60	LA 4032P	1.80	2.00	2.25
2SA 682	80	90	100	2SB 591	10	140	150	2SC 878	35	40	45	2SC 1567	60	70	80	LA 4051P	1.80	2.00	2.25
2SA 684	30	35	40	2SB 600	5.00	6.00	6.60	2SC 871	35	40	45	2SC 1567A	60	70	80	LA 4400	1.90	2.10	2.40
2SA 684	35	40	45	2SC 183	40	53	59	2SC 895	4.20	4.40	4.90	2SC 1584	6.00	6.30	7.00	LA 4400Y	2.00	2.20	2.50
2SA 695	40	53	59	2SC 184	40	53	59	2SC 897	2.00	2.20	2.50	2SC 1586	6.50	6.90	7.60	LA 4420	2.00	2.20	2.50
2SA 697	40	53	59	2SC 281	30	35	40	2SC 898	2.50	2.70	3.00	2SC 1624	60	70	80	LD 3001	2.00	2.20	2.50
2SA 699A	50	64	70	2SC 283	40	53	59	2SC 900	20	27	30	2SC 1626	60	70	80	M5 1513L	2.00	2.20	2.50
2SA 705	40	53	59	2SC 284	40	53	59	2SC 923	20	27	30	2SC 1628	60	70	80	STK 011	3.80	4.00	4.40
2SA 706	80	90	100	2SC 317	40	53	59	2SC 929	20	27	30	2SC 1647	70	80	90	STK 013	7.60	8.00	8.80
2SA 715	60	70	80	2SC 352A	2.00	2.20	2.50	2SC 930	20	27	30	2SC 1667	3.00	3.20	3.40	STK 015	4.20	4.40	4.90
2SA 719	30	35	40	2SC 353A	1.40	1.60	1.80	2SC 941	20	27	30	2SC 1669	4.90	1.00	1.10	STK 435	4.50	4.90	5.60
2SA 720	30	35	40	2SC 367	60	70	80	2SC 943	35	40	45	2SC 1675	20	27	30	STK 439	7.90	8.00	8.80
2SA 721	30	35	40	2SC 369	30	35	40	2SC 945	20	27	30	2SC 1678	1.10	1.25	1.40	TA 7045M	2.00	2.20	2.50
2SA 725	30	35	40	2SC 370	20	27	30	2SC 959	1.00	1.20	1.30	2SC 1679	3.00	3.20	3.40	TA 7055P	2.00	2.20	2.50
2SA 726	30	35	40	2SC 371	20	27	30	2SC 971	70	80	90	2SC 1681	30	35	40	TA 7061AP	90	1.10	1.20
2SA 733	20	27	30	2SC 372	20	27	30	2SC 982	70	80	90	2SC 1682	30	35	40	TA 7062P	1.10	1.25	1.40
2SA 738	40	53	59	2SC 373	20	27	30	2SC 983	50	64	70	2SC 1684	30	35	40	TA 7203P	2.00	2.20	2.50
2SA 740	1.50	1.70	1.90	2SC 374	30	35	40	2SC 1000	35	40	45	2SC 1687	40	45	50	TA 7204P	2.00	2.20	2.50
2SA 743A	85	1.00	1.10	2SC 375	30	35	40	2SC 1012	1.20	1.40	1.50	2SC 1688	35	40	45	TA 7205P	1.60	1.80	2.00
2SA 744	4.20	4.40	4.90	2SC 377	30	35	40	2SC 1013	50	64	70	2SC 1689	35	40	45	TA 7222P	3.40	3.55	3.90
2SA 745R	3.80	4.00	4.40	2SC 380	20	27	30	2SC 1014	50	64	70	2SC 1708	30	35	40	TA 7310P	1.30	1.45	1.60
2SA 747	4.20	4.40	4.90	2SC 381	35	40	45	2SC 1017	80	90	100	2SC 1728	70	80	90	TBA 8105H	1.90	2.10	2.40
2SA 748	70	80	90	2SC 382	35	40	45	2SC 1018	60	70	80	2SC 1730	45	53	59	TC 5080P	5.00	5.20	5.80
2SA 750	35	40	45	2SC 383	75	40	45	2SC 1030	1.80	2.10	2.40	2SC 1756	50	55	60	TC			

HobbyWorld®

CALL TOLL FREE: (800) 423-5387 USA
 IN CALIF: (800) 382-3651
 LOCAL & OUTSIDE USA (213) 886-9200

YOUR #1 SOURCE FOR COMPUTER ELECTRONICS

THIS MONTH'S SPECIALS

Cat No.	Description	Price
KR2378-ST	ASCII ENCODER ROM, 128 char	\$4.50
1142	C-10 DATA CASSETTES, for TRS-80, Apple, Exidy	4 for 1.00
1944	4" CABLE TIES, like Bar-Lok or Ty-Wrap	20 for 1.00
1205	TO-3 HEATSINKS, black anodized	4 for 2.00
2006	TO-3 HEATSINKS, black anodized	4 for 1.00
1386	COMPUTER MAINFRAME TRANSFORMER, 8V, 16A @ 16V-4A	39.00
1855	SOLID STATE MINI BEEPERS, 9VDC	2.00
1536	2 1/2" PANEL METER, D'Arsonval, 200uA, zero adjust	2.00
1853	2 3/8" PANEL METER, D'Arsonval, 175uA, zero adjust	2.00
1952	N-CAD POWER PAK, 2-AVDC, sub-c cells	3.50
1931	ALPHA-NUMERIC READOUT, TIL305, MAN-28 equal, 5.7	5.50
1473	DB25 FEMALE CONNECTOR, solder tail	4.35
1474	DB25 MALE CONNECTOR, solder tail	2.95
1477	DB25 CONNECTOR HOODS	1.36
2041	IC EXTRACTOR, for 8-24 pin dips	1.75
1471	20V, 6A POWER TRANSFORMER, 110/220 pri.	5.50
1398	24VCT, 800mA POWER XFORM, 110 pri.	3.75
1470	12.5V, 750mA POWER XFORM, 110 pri.	4.00
1546	5.8V @ 850mA, 5V @ 190mA, PLUG-IN XFORM	4.00
1339	9V 3A POWER TRANSFORMER, 110 pri.	4.00
1607	12V, 300mA TRANSFORMER, 110 pri.	.75
1487	40-PIN IC SOCKETS, in-profile	3 for 1.00
1797	TO-3 HEATSINK, 100 watts, Wakefield #423	2.50
1862	INLINE FUSE HOLDER, 3AG	3 for 1.00
1854	TV MODULATOR, computers, video games, kit	6.00
1539	2.4V N-CAD BATTERIES, 750mAh, rechargeable	3.00
1847	CHEVY KEYBOARD SWITCHES, SPST, n.o.c.	10 for 2.00
1909	1.4V MERCURY BATTERY, 1/2 penlite	2 for 1.50
1525	TO-3 HEATSINKS, slides on TO-5's	5 for 1.00
1117-14	14 PIN IC SOCKETS, TI, in-profile	10 for 1.40
117-16	16 PIN IC SOCKETS, TI, in-profile	10 for 1.60
1236	LINE CORDS, M, 18ga, with molded plug	3 for 1.00
1233	1N4148A SWITCHING DIODES	25 for 1.00
1399	6 PIN CONNECTOR SET, male & female, screw lock	1.50
1524	1uH CHOKER, axial leads	3 for 1.00
1749	SPOT RELAY, 24V, 700, 2A cont.	2.00
1521	24V PIGTAIL LAMPS, SYLVANIA ZES	4 for 1.00
1150-3/7	TIME BASE CRYSTAL, 3.579545 MHz, .02%	2.00
1493	3" LCD LOCK MODULE, 4 digit, FK10CM, 1.5VDC	25.00
1743	5" LED CLOCK MODULE, 4 digit, FK10CM, 1.5VDC	9.00
1119-6800	COMPUTER GRADE CAP, 6800uF, 25V	2 for 1.00
1537	TILT SWITCH, mercury, metal encase	2 for 1.00
1119-120K	COMPUTER GRADE CAP, 120,000uF, 15V	3.50
1001-50	1N4001 RECTIFIERS, 1A, 50PIV	20 for 1.00
1001-100	1N4002 RECTIFIERS, 1A, 100PIV	16 for 1.00
1001-200	1N4003 RECTIFIERS, 1A, 200PIV	12 for 1.00
1289	4 POS DIP SWITCH	1.25
1290	7 POS DIP SWITCH	1.40
1291	8 POS DIP SWITCH	1.60
1099	MINI PUSH SWITCHES, SPST, red button	3 for 1.00
1270	HEAT SINK CLIPS, protection, 1/4" x 1/2"	10 for 1.00
1378	AC UTILITY OUTLET, 2 prong, solder lugs	2 for 1.00
1914	2 DIGIT READOUT, MAN66, 5", com anode	1.50
1915	1 1/2 DIGIT READOUT, MAN66, 3", com anode	1.25
1454	MJE1555 TIMER TRANSISTOR, power lab 2N3055	2.00
1453	2N2222 SWITCHING TRANSISTORS, NPN	4 for 1.00

RAMS-EPROMS

Order by Cat. No. 999 and type	Type/Speed	Price
21102-250	2512	\$1.25
21102-450	4512	1.10
21102-650	6512	.90
2114-200	2012	.975
2114-250	2512	.875
2114-300	3012	.725
2114-450	4512	6.50
2114-200	2012	11.00
4116-250	2512	10.00
4116-300	3012	9.25
2708-450	4512	9.15
2716-450 (5V)	4400	44.00

SPECIAL PURPOSE IC'S

Order by Cat. No. 999 and type	Type/Speed	Price
SN76477NF	32.25	
LM1889	1.75	
MK2002P	2.45	
ICM7107	11.00	
8018	3.95	
KC14410	6.00	
KR2378-ST	9.50	
AYS-1013A	5.50	


Send for FREE CATALOG

The best selection of computer accessories, add-ons, factory fresh IC's, led's, semi-s software, PC aids, prototyping aids, books, test equipment, and more!
 Always updated! Dozens of new products every issue!

HOW TO ORDER


Pay by check, COD, VISA, or MasterCard. Charge orders include expiration date. Order by phone or mail. Minimum order \$10. Please include phone number and magazine issue you are ordering from. USA: add \$2 for shipping/handling ground, add \$3 for air. FOREIGN: add \$3 for shipping/handling surface, \$6 for air. COD's \$1 addtl. Guaranteed satisfaction for 120 days or your money back! Not responsible for typographical errors. We reserve the right to limit quantities.

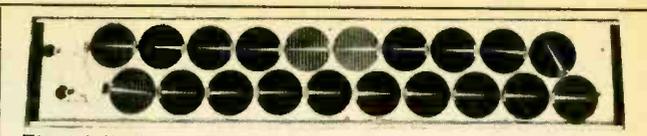**1951 BUSINESS CENTER DRIVE Dept. R12
 NORTHIDGE, CA. 91324**
 CIRCLE 35 ON FREE INFORMATION CARD



Electricity from the sun.
 5 Volt panel 1/4 amp \$50 2.5 Volt panel 1/2 amp \$40
GIANT 3 1/2 inch cell, delivers 1 amp \$8.50
 Above cell with special motor & prop, runs in sun \$10.25

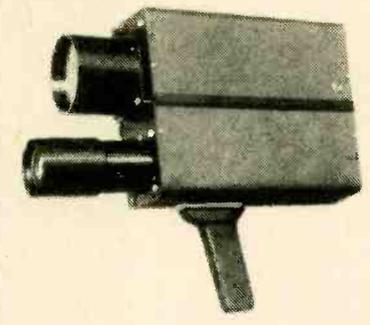LOGIC power supplies, unused, solid state construction.
 5 Volt 4 amp \$35 5 Volt 15 amp \$45 5 Volt 25 amp \$45
 5 volt 35 amp \$50 12 Volt 15 amp \$40



Govt surplus walky talky, used cond.
 47-55.4 mc range.
 Ant. \$5 each extra.
 With data.
 \$25 ea 2 for \$45
AN/PRC-6

SEE IN THE DARKNESS
 IR viewer, portable, new with choice of one lens...close up, telephoto or gen. purpose.
 Requires 6 volt DC btry.
 \$250
 Shipping extra on all merchandise



Meshna Inc., PO Box 62, E. Lynn, Mass. 01904
 CIRCLE 7 ON FREE INFORMATION CARD

CMOS (DIODE CLAMPED)

4001	22	4024	-75	4069	-45	74C03	-95
4002	22	4025	-75	4071	-20	74C151	-178
4007	27	4027	-45	4072	-35	74C157	-175
4009	45	4028	-80	4081	-22	74C180	-120
4010	45	4029	-80	4082	-20	74C181	-120
4011	22	4030	-35	74C00	-27	74C165	-125
4012	22	4035	-97	74C02	-27	74C173	-130
4013	40	4036	-75	74C08	-20	74C174	-130
4014	120	4044	-85	74C10	-27	74C175	-120
4015	100	4045	-45	74C11A	-27	74C192	-130
4016	-45	4046	-75	74C12	-27	74C193	-140
4017	105	4049	-75	74C13	-20	74C901	-50
4018	30	4050	-45	74C14	-75	74C902	-50
4019	45	4051	-75	74C15	-75	74C914	-190
4020	-110	4053	-110	74C83	-130		
4021	-110	4055	-125	74C86	-90		
4022	100	4066	70	74C90	-95		
4028	-22						

PRINTED CIRCUIT BOARD

4" x 8" DOUBLE SIDED EPOXY BOARD 1/16" thick \$6 ea 5 (\$2.60)

EPOXY glass vector board 1/16" thick with 1/10" spacing \$1.95

VERIPAX PC BOARD... \$12.95

Our new Prototyping board is a hi density 4 1/2 x 6 1/2" single sided 1/16" G-10 board. It will hold 40, 16 1/2 pin DIP units, 14 8 pin IC's. There are three buses, +5V, ground and a floating bus. There is a pad for a TO-220 regulator. There is a 22 pin edge connector with 156" spacing.

7 WATT LD-65 LASER DIODE IR \$8.95
 25 watt Infra Red Pulse (SG 2006 equiv.)
 Laser Diode (Spec sheet included) \$24.95

MINIATURE MULTI-TURN TRIM POTS 10K, 1K, 2K, 5K, 10K, 20K, 50K, 200K, 1Meg, 2Meg, \$75 each 3/\$200

2N 3820 P FET \$4.50
 2N 5457 N FET \$4.45
 2N2646 JUT \$4.45
 ER 900 TRIGGER DIODES 4 \$1.00
 2N 6028 PROG UJT \$6.00

FP 100 PHOTO TRANS RED, YELLOW, GREEN \$5.50

LARGE LED'S: 2" RED/GREEN BIPOLAR LED'S 2" .95
 TIL-118 OPTO-ISOLATOR \$7.95
 MCT-6 OPTO-ISOLATOR \$8.80
 1 WATT ZENERS: 3.3, 4.7, 5.1, 5.6, 9.1, 10, 12, 15, 18, or 22V \$6.50
 MCM 6571A 7 x 9 character org. \$10.75

TRANSISTOR SPECIALS

2N6233-NPN SWITCHING POWER	\$1.95
MRF-8004 A CB RF Transistor NPN	\$7.75
2N3772 NPN Si TO-3	\$1.00
2N1546 PNP GE TO-3	\$7.75
2N4908 PNP Si TO-3	\$1.00
2N5086 PNP Si TO-92	4 \$1.00
2N3137 NPN Si RF	\$5.95
2N3919 NPN Si TO-3 RF	\$1.50
2N1420 NPN Si TO-6	3/\$1.00
2N3767 NPN Si TO-6	\$7.70
2N2222 NPN Si TO-18	5 \$1.00
2N3055 PNP Si TO-3	\$6.00
2N3904 NPN Si TO-92	6/\$1.00
2N3906 PNP Si TO-92	6/\$1.00
2N5296 NPN Si TO-220	\$5.50
2N6109 PNP Si TO-220	\$5.50
2N6338 PNP Si TO-5	5 \$1.00
MPSA 13 NPN Si	4/\$1.00

Full Wave Bridges

PRV	2A	6A	25A	DIP SOCKETS
100	1.40	1.40	1.40	8 PIN 17 24 PIN .35
200	80	1.30	2.20	14 PIN 20 28 PIN .30
400	1.00	1.65	3.30	16 PIN 22 40 PIN .60
600	1.30	1.90	4.40	18 PIN 25

SANKEN AUDIO POWER AMPS

Si 1010 G 10 WATTS	\$7.80
Si 1020 G 20 WATTS	\$15.70
Si 1050 G 50 WATTS	\$28.50

TANTALUM CAPACITORS

2.2UF 35V \$/1.00	6.8UF 35V 4/1.00
4.7UF 35V 5/1.00	10UF 10V \$.25
6.8UF 35V 5/1.00	22UF 25V \$.40
1UF 35V 5/1.00	15UF 35V 3/1.00
2.2UF 20V 5/1.00	30UF 6V 5/1.00
3.3UF 20V 4/1.00	150UF 16V \$.95
4.7UF 15V 5/1.00	68UF 15V \$.50

8" DISKETTES - HARD SECTOR \$1.75, 10/\$16.00

CRYSTALS \$3.45 ea.
 2.000 MHz 6.144 MHz
 4.000 MHz 8.000 MHz
 3.57 MHz 10.000 MHz
 5.000 MHz 20.000 MHz
 6.000 MHz

RIBBON CABLE FLAT (COLOR CODED) #30 WIRE \$2.99
 26 cond. 50/over foot
 40 cond. 75/over foot
 50 cond. 90/over foot

UNIVERSAL 4Kx8 MEMORY BOARD KIT \$69.95
 32-2102-1 fully buffered, 16 address lines, on board decoding for any 4 of 64 pages, standard 44 pin bus, may be used with F & K IM

SILICON SOLAR CELLS 4" diameter 4V at 1 AMP \$10.00

LED READOUTS
 FCS 8024 4 digit DL-707 C.A. 3" \$7.75
 C.C. 8" display \$5.95 DL 747 C.A. 6" \$1.50
 FND 503 C.C. \$5.85 HP3400, 8" C.A. \$1.95
 FND 510 C.A. 5" \$1.85 HP3405, 8" C.C. \$1.95
 DL 706 C.C. \$1.85

Silicon Power Rectifiers

PRV	1A	3A	12A	50A	125A	240A
100	06	14	35	90	370	5.00
200	07	20	40	130	425	6.50
400	09	25	65	150	6.50	8.50
600	11	30	80	200	8.50	12.50
800	15	35	100	250	10.00	16.50
1000	20	45	125	300	12.50	20.00

SAD 1024 a REDICON 1024 stage analog 'Bucket Brigade' shift register. \$14.95

IN 3148 (IN314) 16/\$1.00
 1 or 10 of 25V ceramic disc caps. 16/\$1.00, \$5.00/100

RS232 DB 25P male \$2.95
 CONNECTORS DB 25S female \$3.50
 HOODS \$1.50

REGULATORS
 323K 5V 3A \$5.75 340K 12, 15, 30V \$1.60 or 24 V. \$1.50
 320V \$5.00 340T 6, 6.8, 12, 15, 18 or 24V \$1.30
 5, 12, or 16 V \$1.30 78M05 \$7.75

TTL IC SERIES

7400	-17	7430	-17	74195	-75
7401	-17	7472	-35	74197	-65
7402	-17	7473	-35	74198	-65
7403	-17	7474	-42	74199	-80
7404	-24	7475	-48	74192	-120
7405	-24	7476	-45	74193	82
7406	-33	7480	-45	74194	-80
7407	-27	7485	-50	74195	-80
7408	-24	7486	-75	74197	130
7410	-17	7488	-42	74174	-85
7411	-22	7489	-60	74175	-75
7412	-22	7490	-62	74176	-75
7413	-42	7491	-55	74177	-75
7414	-90	7492	-50	74180	-75
7416	-31	7493	-50	74181	-190
7417	-31	7494	-80	74180	-120
7420	-17	7495	-80	74191	-120
7425	-35	7496	-50	74192	-70
7426	-33	74107	-35	74193	-70
7427	-35	74121	-35	74194	-85
7430	-17	74122	-39	74195	-65
7432	-27	74123	-42	74196	-65
7433	-27	74125	-45	74197	-85
7438	-27	74126	-45	74278	-75
7440	-17	74145	-75	74168	-65
7441	-85	74148	-110	74279	-25
7442	-60	74150	-110	15401	-105
7445	-60	74151	-55	75497	-105
7447	-60	74152	-55		
7448	-75	75154	-110		

MALS SERIES

74L500	74L5193	LM 201	-75
74L501	74L5194	LM 301/748	25
74L502	74L5195	LM307</	



WE'RE BACK WITH OUR WORLD FAMOUS INFLATION FIGHTIN'

"ONE CENTERS"

Only 2 FOR \$14.99 \$15

DIAL DESK TELEPHONE

Cat. No. 92CUS683

HY-GAIN ONE ARM BANDIT MIKES

Only \$14.99 2 FOR \$15

Take one hand command of your mobile or base rig with Hy-Gain's One Arm Bandit Mike. ON/OFF, VOLUME, SQUELCH, CHANNEL SELECTOR, SPEAKER, and DIGITAL DISPLAY are all conveniently located where your fingers do the talking. Comes with 6 ft. multi-conductor, color coded, shielded cable. (Separate for easy integration into any type of rig. Size: 4 1/2" x 2 1/2" x 1 1/2". Wt. 9 oz. No. 92CUS886

40 CHANNEL CB BOARD \$12.50

WITH 2 FOR SWITCH \$12.51

Poly Pak buys up factory close out from Hy Gain so you gain! Boards have: Heated 9 Watt Amp Chip, RF and Mod Transistors, and Motorola MC series PLL. May be used for 10 meter conversion. See continuing series "CB to 10" in 72 magazine! The parts alone make it an offer you can't refuse. Wt. 9 oz. Cat. No. 92CUS554

LEDS! LEDS! LEDS!

YOUR CHOICE 5 for \$1.29 1¢ SALE 10 for \$1.30

Cat. No. Type

1788	MICRO TOPHAT RED
1802	MICRO SINGLE PIN RED
1948	MICRO YELLOW
2139	JUMBO RED
2136	JUMBO TAPER RED
2137	MICRO RED
1944	Jumbo Yellow
2138	Jumbo Green

6 AMP EPOXY "BULLET" RECTIFIERS

Order by Cat. No. 92CUG095 and Voltage

PRV	PRICE	SALE
2	4r	.40
100	.49	2 for .50
200	.59	2 for .60
400	.69	2 for .70
2	1r	.80
600	.89	2 for 1.00

25 AMP BRIDGE RECTIFIERS

PIV	SALE	2 FOR
25	1.25	2.24
50	1.95	1.96
100	2.25	2.26
200	2.85	2.96
400	4.50	4.51
600	4.25	4.26
800	4.85	4.96

Order No. 2273 & Voltage

ULTRASONIC TRANSDUCER

2 for \$3.98 \$3.99

Perfect for dozens of projects, including remote control devices, alarms, etc. Sends and Receives 1" diameter, 1/4" deep, with standard RCA type phono jack. Wt. 2 oz. Cat. No. 92CUS375

FANTASTIC? YOU BET IT IS! LOOK WHAT YOU GET FOR 1¢ MORE!

- | | | |
|--|------|---------------|
| 1-LASER COUPLER, type H11C3, mini dip, (#5700) | 1.29 | 2 for 1.30 |
| 3-LINE CORD, 6 ft. 18 gauge, 2 cond. white w/plug, (#3787) | 1.29 | 6 for 1.30 |
| 15-SINGLE PIN MICRO RED LEDS, 100% material, 3 volts @ 10 mls, (#5886) | 1.29 | 30 for 1.30 |
| 40-FEEDTHRU CAPACITORS, used for hams, RF, UHF circuitry, (#5668) | 1.29 | 80 for 1.30 |
| 40-PLASTIC TRANSISTORS, ass'd & untested and hobby, (#2604A) | 1.29 | 80 for 1.30 |
| 6-6V INDICATORS, w/leads, test lamp manufacturers excess, (#5893) | 1.29 | 12 for 1.30 |
| 40-METAL CAN TRANSISTORS, ass'd & untested, (#2603A) | 1.29 | 80 for 1.30 |
| 10-UPRIGHT ELECTROS, 100% ass'd values and voltages, (#5900) | 1.29 | 80 for 1.30 |
| 40-SEMI-CON SUPPLIES, zeners, rectifiers, transistors, etc. U-test, (#2226) | 1.29 | 80 for 1.30 |
| 65-TRANSISTORS, axial, for regulators & computers, U-test, (#3140) | 1.29 | 130 for 1.30 |
| 40-SQUARE PCB COILS uprights, assorted values, for PC applications, (#3188) | 1.29 | 80 for 1.30 |
| 50-1 AMP ZENERS, 3.3, 10, 12.15V, etc., double plug, untested, (#1964) | 1.29 | 100 for 1.30 |
| 4-ROCKER SWITCHES, DPDT, solder eyelet terminals, (#3302) | 1.29 | 8 for 1.30 |
| 60-LONG LEAD DISCS, 100% prime, marked capacitors, (#5899) | 1.29 | 120 for 1.30 |
| 6-MINI TRANSFORMERS, ass'd outputs, interstage & audio, 1" sq, (#3295) | 1.29 | 12 for 1.30 |
| 1-TV/AUDIO SHIELDED CABLE, 2 cond. 15 ft. w/RCA phone plugs, (#5812) | 1.29 | 2 for 1.30 |
| 25-DATA ENTRY KEYCAPS, 1/4" sq. #'s & functions, ass't. colors, (#4013) | 1.29 | 4 for 1.30 |
| 2-GE 3W AUDIO AMP, type PA-263 IC chip, mono, (#1522) | 1.29 | 2 for 1.30 |
| 1-MERCURY TILT SWITCH, N.C. rated 24VDC @ .05A, w/leads, (#5686) | 1.29 | 2 for 1.30 |
| 6-POWER TAB TRIACS, 100% prime, 100V, TO-220, (#5888) | 1.29 | 12 for 1.30 |
| 6-POWER TAB SCRs, 100% prime, 100V, TO-220, (#5904) | 1.29 | 12 for 1.30 |
| 2-WATCH LCD'S, 3 1/2 digit, ass't. types, size: 1" x 1 1/2" (approx.), (#5066) | 1.29 | 4 for 1.30 |
| 4-TV INTERLOCK JACKS for TV/power mt. ctr. solder tab terms., (#5519) | 1.29 | 8 for 1.30 |
| 4-MOS FETS, 3N128, by Fairchild & RCA, TO-18, some duals, (#1686) | 1.29 | 8 for 1.30 |
| 4-PHOTO ELECTRIC DARLINGTON TRANSISTORS, 2N5777, (#3276) | 1.29 | 8 for 1.30 |
| 6-AC "UTILITY" OUTLETS, for 1 1/2" mt. ctr., solder jugs, (#3582) | 1.29 | 30 for 1.30 |
| 15-NE-2 LAMPS, nrm. red, for 110VAC, inc. resistor, (#1435) | 1.29 | 40 for 1.30 |
| 20-1N4148 SWITCHING DIODES, 4N5, 100V @ 10mA, axial, 100%, (#3000) | 1.29 | 40 for 1.30 |
| 2-4 AMP SILICON BRIDGE RECTIFIER, 200V, block style, (#5928) | 1.29 | 4 for 1.30 |
| 4-VARACTOR DIODES, var. tuner capacitance, 20-50 pf., (#5887) | 1.29 | 8 for 1.30 |
| 50-PRECISION RESISTORS, 1/4, 1/2, & 2 watts, 1%, assorted types, (#363) | 1.29 | 100 for 1.30 |
| 60-CERAMIC CAPS, ass'd val. & styles, incl; tubular, NPO's, etc., (#590) | 1.29 | 120 for 1.30 |
| 25-PLASTIC SCRs, incl; 200V, untested, high yield, TO-220, (#3192) | 1.29 | 50 for 1.30 |
| 40-MOLDED CAPACITORS, tubular, ass'd volt. to 1 ml. axial leads, (#348642) | 1.29 | 80 for 1.30 |
| 60-MICRO ZENER & RECT. KIT, ass'd voltages, only 1/8" sq., U-test, (#1251) | 1.29 | 2 for 1.30 |
| 1-LINE COIL, 6 ft. 2 cond., 16 gauge, vinyl molded plug, & Grommet, (#3429) | 1.29 | 12 for 1.30 |
| 6-SPDT MICRO SLIDE SWITCH, only 3/77" speaker, etc., (#402) | 1.29 | 20 for 1.30 |
| 10-PR.-RCA PLUGS & JACKS, for audio, speakers, etc., (#402) | 1.29 | 20 for 1.30 |
| 5-2N3505 HOBBY TRANSISTORS, TO-3, (#3771) | 1.29 | 20 for 1.30 |
| 10-ZENERS, 1 watt 9.1 volts axial leads 100% (#5370A) | 1.29 | 80 for 1.30 |
| 40-1N4148, 4 NANO, SWITCHING DIODE, axial leads untested (#5923) | 1.29 | 4 for 1.30 |
| 2-RELAYS, BABCOCK 6VDC, SPST, plastic case, (#5807) | 1.29 | 2 for 1.30 |
| 1-25 AMP BRIDGE RECTIFIER, 50 volts, 100% (#5948) | 1.29 | 4 for 1.30 |
| 2-QUADRICS, 10 amp 200 PRV, TO-220 100% (#5915) | 1.29 | 120 for 1.30 |
| 60-MINI RESISTORS, 50-12W, 30-1/4 watt, axial, color coded, (#5922) | 1.29 | 24 for 1.30 |
| 12-SCRS-TRIC-QUADRICS, ass't. volts, TO-220 case, (#2087) | 1.29 | 20 for 1.30 |
| 10-BULB PLATES, ass't. resistor/capacitor networks, various styles, (#5880) | 1.29 | 4 for 1.30 |
| 2-AIR TRIMMER CAPS, alum. plates, 1/8" shaft, panel mt. solder jugs, (#5658) | 1.29 | 60 for 1.30 |
| 30-MOLEX CONNECTORS, nylon, ass'd styles, colors, & # of cond., (#5835) | 1.29 | 2 for 1.30 |
| 1-3 COND. LINE CORD, 8 ft. flat, w/ring terminals, 2 AC, 1 GND, (#5703) | 1.29 | 8 for 1.30 |
| 4-12 VOLT LAMPS, w/leads, popular voltage, 100% of uses, (#5942) | 1.29 | 40 for 1.30 |
| 25-TTL IC'S, untested, ass'd gates, flip flops, etc. 14-16 pin, (#5903) | 1.29 | 2 for 1.30 |
| 10-100 PIV GLASS ANPS, micro-mini, axial, silicon, rated @ 1A, (#5937) | 1.29 | 2 for 1.30 |
| 1-12 VCT 200 mA TRANSFORMER, 115 V prim, PC mount, (#5977) | 1.29 | 40 for 1.30 |
| 20-400 mV 15V ZENERS, micro-style, ass't. epoxy & glass, 100%, axial, (#5914) | 1.29 | 200 for 1.30 |
| 100-UNMARKED CAPS, popular values, mylars & polystyrene, 100%, (#5892) | 1.29 | 100 for 1.30 |
| 60-ONE WATT ZENERS, assorted voltages, glass pak, dbl. plug, U-test, (#5947) | 1.29 | 120 for 1.30 |
| 60-MICRO ZENERS, 1 watt, 2-30V, DO-7 & micro epoxy, axial, 100%, (#5905) | 1.29 | 1000 for 1.30 |
| 500pc-HARDWARE SURPRISE, ass't screws nuts & washers, (#5891) | 1.29 | 400 for 1.30 |
| 60-GLASS ANPS, up to 1KV, 1N4000 series, glass encased, untested, (#5982) | 1.29 | 12 for 1.30 |
| 200-PC BOARD PARTS, boards loaded w/100% parts, hobby bonanza, (#5946) | 1.29 | 12 for 1.30 |
| 6-RF NPN TRANSISTORS, type-2N105, BVcb: 40V, TO-22, 100%, (#5895) | 1.29 | 4 for 1.30 |
| 2-BRASS DOOR LOCKS, w/key, for doors/windows, etc. 2-1/8" mt. ctr., (#5949) | 1.29 | 2 for 1.30 |
| 1-PUSH-PUSH CB SWITCH, DPDT, 1 x 1/4 x 3/8", 100% of uses, (#3463) | 1.29 | 60 for 1.30 |
| 30-"CRIMP-ON" TERMINALS, rings and spades, for # 12-20 wire, (#3955) | 1.29 | 100 for 1.30 |
| 50-ONE-WATT RESISTORS, popular assort. some 5Wers, 100% of uses, (#3844) | 1.29 | 120 for 1.30 |
| 50-METALLIC FILM W WATERS, ass't. values, marked, axial leads, (#1605) | 1.29 | 8 for 1.30 |
| 4-RIBBON CABLE CONNECTOR, single-sided, 9 contacts, PC leads, (#5967) | 1.29 | 2 for 1.30 |
| 3-"SUPER" 2N2222, NPN, ICBO: 60V, hfe: 100-1W @ 2A, TO-92, 100%, (#5952) | 1.29 | 2 for 1.30 |
| 1-12 VDC MINI BLOCK RELAY, spdt, 1 x 3/4 x 5/8", 175 ohm, 1A, (#5937) | 1.29 | 20 for 1.30 |
| 10-IF-IMP OP. AMPS, by RCA, FM-UHF circuitry, TO-5, 10 leads, RD51, (#6002) | 1.29 | 20 for 1.30 |
| 10-NPN SWITCHING TRANSISTORS, ass'd gen. audio & switching, (#2595) | 1.29 | 20 for 1.30 |
| 1-12 VDC SOLENOID, similar to Guardian 16-P, w/plunger, 1/2" stroke, (#6013) | 1.29 | 2 for 1.30 |

FOREIGN AND CANADIAN POSTAGE

CANADIANS ADD \$5.00 (U.S. Funds)

FOREIGN ADD \$10.00

EXCESS WILL BE RETURNED

we accept

"SKINNY-TRIMS" POTENTIOMETERS

3/8" square! Single turn styl. Serw driver adjust 20 Tolerance 0.5 Watt ratings - constant contact PC leads ORDER 92CUB86 AND VALUE

6 for \$2.49 12 for \$2.50

SINGLE TURN FLAT

10	100	1K	5K	25K	50K
20	200	2K	10K	50K	200K
50	500	2.5K	20K	100K	1Meg

"TIE-PIN" CONDENSER MIKE

It's a little giant in sound quality! Metal mesh and outstanding sound! Frequency response 20-20,000 Hz! Least expensive! 1/2" dia. 1/2" long! 600 ohm impedance! 1.5 VDC. Cat. No. 5730

\$3.95 2 for \$3.96

HOW TO ORDER

When ordering, always use catalog number, type no., the name of the magazine you are ordering from and the month.

POLY PAKS®

P.O. BOX 942-R12
S.O. LYNNFIELD, MA 01940

Terms: Add Postage. Rated: Net 30
Phone: (617) 245-3828
Retail: 16-18 Del Carmine St.
MINIMUM ORDER: \$8 Wakefield, MA

DIG-KEY CORPORATION

TOLL FREE 1-800-346-5544

Quality Electronic Components

FREE I.C.'s • RESISTORS • TRANSISTORS • CAPACITORS • DIODES • I.C. SOCKETS & PINS • SWITCHES • CLOCK MODULES • OPTOELECTRONICS • BREADBOARD & TESTING DEVICES • DRAFTING SUPPLIES • DATA BOOKS • HEAT SINKS • WIRE • TOOLS... AND MORE... WRITE FOR FREE CATALOG.....

DON'T FORGET OUR DISCOUNTS WHEN COMPARING PRICES

TIME-TEMPERATURE PROGRAMMABLE MODULE USER PROGRAMMABLE FOR:

- 12 to 74 Hour Durability
- 1" and 1/2" ICs with virtually any number of temperature sensors
- 100 to 1000 Hz Frequency
- 50 to 400 Hz Resonance



FEATURES

- Operates 0.7" high & 10" long display with red LEDs
- Full, custom design and assembly
- 4 display modes - Temp, Rate, Secs, and Temp and Rate
- 4 display modes - Temp, Rate, Secs, and Temp and Rate
- 4 display modes - Temp, Rate, Secs, and Temp and Rate
- 4 display modes - Temp, Rate, Secs, and Temp and Rate

TEXAS INSTRUMENTS I.C. SOCKETS

SOLDER TAIL DIP SOCKETS




TIN INLAY SOLDER TAIL



GOLD INLAY SOLDER TAIL

WIRE WRAP DIP SOCKETS

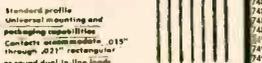

TIN PLATED WIRE WRAP

GOLD INLAY WIRE WRAP

MOLEX I.C. SOCKET PINS

TEXAS INSTRUMENTS GOLD EDGEBOARD CONNECTORS

RELIABLE, COST-EFFECTIVE CONTACT DESIGN

0.7" HIGH DIGITS - RED LED DISPLAY



MA1023

THE "PROGRAMMABLE" CLOCK MODULE

RELIABLE, COST-EFFECTIVE CONTACT DESIGN

0.7" HIGH DIGITS - RED LED DISPLAY

MA1023

THE "PROGRAMMABLE" CLOCK MODULE

RELIABLE, COST-EFFECTIVE CONTACT DESIGN

0.7" HIGH DIGITS - RED LED DISPLAY

MA1023

THE "PROGRAMMABLE" CLOCK MODULE

RELIABLE, COST-EFFECTIVE CONTACT DESIGN

0.7" HIGH DIGITS - RED LED DISPLAY

MA1023

INTEGRATED CIRCUITS

NEW! DIGI-KEY ONLY \$1995

5% CARBON FILM RESISTORS

1/2 WATT RESISTOR ASSORTMENTS

1/4 WATT RESISTOR ASSORTMENTS

SILICON TRANSISTORS

1000'S OF 1/2 WATT CARBON FILM RESISTORS

1000'S OF 1/4 WATT CARBON FILM RESISTORS

1000'S OF 1/2 WATT CARBON FILM RESISTORS

1000'S OF 1/4 WATT CARBON FILM RESISTORS

1000'S OF 1/2 WATT CARBON FILM RESISTORS

1000'S OF 1/4 WATT CARBON FILM RESISTORS

1000'S OF 1/2 WATT CARBON FILM RESISTORS

1000'S OF 1/4 WATT CARBON FILM RESISTORS

1000'S OF 1/2 WATT CARBON FILM RESISTORS

1000'S OF 1/4 WATT CARBON FILM RESISTORS

1000'S OF 1/2 WATT CARBON FILM RESISTORS

1000'S OF 1/4 WATT CARBON FILM RESISTORS

1000'S OF 1/2 WATT CARBON FILM RESISTORS

1000'S OF 1/4 WATT CARBON FILM RESISTORS

1000'S OF 1/2 WATT CARBON FILM RESISTORS

1000'S OF 1/4 WATT CARBON FILM RESISTORS

1000'S OF 1/2 WATT CARBON FILM RESISTORS

1000'S OF 1/4 WATT CARBON FILM RESISTORS

1000'S OF 1/2 WATT CARBON FILM RESISTORS

1000'S OF 1/4 WATT CARBON FILM RESISTORS

1000'S OF 1/2 WATT CARBON FILM RESISTORS

1000'S OF 1/4 WATT CARBON FILM RESISTORS

PANASONIC ELECTROLYTIC CAPACITORS

ADJ. LEADS

PANASONIC POLYESTER CAPACITORS

ADJ. LEADS

Digi-Key Stocks

STRAINED

AP Products Line

DIODES

DIODES

DIODES

FREE CATALOG

Digi-Key Stocks

STRAINED

AP Products Line

DIODES

DIODES

DOUBLE DIGIT DISCOUNTS SAVE YOU EVEN MORE!

HANDLING CHARGES

\$ 0.00-\$9.99, Add \$2.00

\$ 10.00-\$29.99, Add \$0.75

\$ 30.00-\$49.99, Add \$0.50

\$ 50.00-\$99.99, Add \$0.25

VOLUME DISCOUNT

VOLUME DISCOUNT

\$ 0.00-\$99.99, NET

\$ 100.00-\$249.99, Less 10%

\$ 250.00-\$499.99, Less 15%

\$ 500.00-\$999.99, Less 20%

1/2 WATT ZENER DIODES

1/2 WATT ZENER DIODES

CARBON FILM 1/4W-5% Resistors

| OHMS |
|------|------|------|------|------|------|------|------|------|
| 2.7 | 11 | 47 | 200 | 820 | 3600 | 15K | 62K | 270K |
| 3.0 | 12 | 51 | 220 | 910 | 3900 | 16K | 68K | 300K |
| 3.3 | 13 | 56 | 240 | 1000 | 4300 | 18K | 75K | 330K |
| 3.6 | 15 | 62 | 270 | 1100 | 4700 | 20K | 82K | 360K |
| 3.9 | 16 | 68 | 300 | 1200 | 5100 | 22K | 91K | 390K |
| 4.3 | 18 | 75 | 330 | 1300 | 5600 | 24K | 100K | 430K |
| 4.7 | 20 | 82 | 360 | 1500 | 6200 | 27K | 110K | 470K |
| 5.1 | 22 | 91 | 390 | 1600 | 6800 | 30K | 120K | 510K |
| 5.6 | 24 | 100 | 430 | 1800 | 7500 | 33K | 130K | 560K |
| 6.2 | 27 | 110 | 470 | 2000 | 8200 | 36K | 150K | 620K |
| 6.8 | 30 | 120 | 510 | 2200 | 9100 | 39K | 160K | 680K |
| 7.5 | 33 | 130 | 560 | 2400 | 10K | 43K | 180K | 750K |
| 8.2 | 36 | 150 | 620 | 2700 | 11K | 47K | 200K | 820K |
| 9.1 | 39 | 160 | 680 | 3000 | 12K | 51K | 220K | 910K |
| 10 | 43 | 180 | 750 | 3300 | 13K | 56K | 240K | 1.0M |

HIGH QUALITY... LOW O.E.M. PRICE
5 for .25 | 10 for .40 | 100-\$1.60 - 1000-
one value | one value | 100 per value **at \$14.**

CMOS BOARD \$2.95
 CONTAINS:
 4553 3 digit decade counter
 4511 4bit latch 7 seg. decoder
 driver for LED display
 4060 oscillator w/4 stage binary counter.
 4011 CMOS gate
 2 switches, resistors, capacitors.
 HP 2 digit LED display

RCA to 220 8A, 600V TRIAC ea. 99¢ ten-\$9.50 \$89/ct

BISTABLE RELAY OPTO ISOLATOR
 Ge or Si SIGNAL DIODES
 High quality, marked
 computer grade signal
 diodes. Leads trimmed
 for PCB mounting....

P.U.T. PROGRAMMABLE UNIJUNCTION
 Prime 2N6026
 50¢ ea. ten \$4. 100-\$30
 removed from boards

VOICE ACTUATED SWITCH 95¢ ea
 COMPUTED ASSEMBLED ON CIRCUIT BOARD AS SEEN
 CONTAINS CRYSTAL MICROPHONE, OLIN CONTROL,
 TRANSFORMER AND SPEAKER AND 4 AMP. SW. WHICH IS TURNED
 ON BY AUDIO FROM MICROPHONE... HIGH SPEED
 VCC FOR REPEATERS.
 MICROPHONE CAN BE REPLACED BY ONE PROVIDED
 FOR LIGHT ACTIVATION.

VIBRASONIC dual delay \$12.95
SUPER SAVER

DIP BRIDGE 50¢ ea.
 1A, 100V
 Varo VM18
 ten \$4. 100-\$30
 removed from boards

DIODE ARRAY 10 IN914's
 20 PIN PACKAGE WITH
 100 OHM RESISTORS
 TWO STAGGED HIND
 25¢ each
 CLAIKEX
 PHOTOCONDUCTIVE CELLS

PO BOX 41778 SEND FOR FREE FLYER TODAY
 Sacramento California 95841

AMAZING ELECTRONIC PROJECTS and PRODUCTS:
 Lasers Super Powered, Burning, Cutting, Rifle, Pistol, Pocket. See in Dark—Shotgun Directional Mike—Unscramblers—Giant Tesla—Stunwand—TV Disrupter—Energy Producing, Surveillance, Detection, Electrifying, Ultrasonic, CB, Auto and Mech. Devices, Hundreds More—All New Plus INFO UNLTD PARTS SERVICE. Catalog \$1. Information Unlimited, Dept. R8 Box 716 Amherst, N.H. 03031.

10 HOUR TAPE RECORDER
 Top quality AC-DC cassette recorder, modified to provide 5 continuous hours of recording and playback of true fidelity, distortion-free sound on each side of cassette for a total of 10 hours. Unit has many special built-in features. TDK D-C180 cassette supplied. \$155.00*

PHONE RECORDING ADAPTER
 Record incoming and outgoing calls automatically with this all solid state unit connected to your telephone jack and tape recorder. Starts recording when phone is lifted. Stops when you hang up, making a permanent record. Approved Easily installed. No monthly charges. \$24.50*

VOX VOICE ACTIVATED CONTROL SWITCH
 Solid state. Self contained. Excellent adjustable sensitivity. Voices or other sounds activate recorder. Uses recorder mike or remote mike. 2 1/4 x 1 3/4 x 3/4" \$24.95*

Burglar-Fire Protection
 Protect Your Life, Home, Business, Auto, etc.
 Our catalog shows how. Install your own alarm systems and devices and save \$\$\$\$! We offer FREE write-in engineering service.

FREE CATALOG Lowest Prices on Reliable, High Quality Alarm Systems and Devices
 Burdax Security Co. Box 82802-RE Lincoln, Ne. 68501

DELTRONIKS
1. EMM 4200A, 4K Static RAMs, Ceramic
 A local memory boards manufacturers closed. We bought the new memory boards and took these 4200A static RAMs out. They are tested and 90-day guaranteed 100% good.
Prime tested 4200A 4K RAMs \$5.50 ea., 32/\$160.00, 300 pieces or more \$4.50 ea.
2. Static RAMs MK4104 4KX1 (350 nS) Ltd. Qty..... \$4.00 ea.
3. Power SCR's (GEC50A) 100 volt @ 110 amps..... \$6.95 ea.
4. Squirrel Cage Fans (Howard). \$7.00 ea.
5. Power Diode 1N1202A, 200 volt @ 12 amp..... 4 for \$1.00
6. LM 323 5 Volt 3 amps, voltage regulator 4.95 each or 10/45.00.
7. Super Saver, Micro PD4 11. Ceramic 4K x 1 dynamic RAMs..... 8 for \$10.00.



save on gas!

Enjoy the benefits of 20% better gas mileage, quicker starting, elimination of tune-ups, reduced pollution, and 50,000 miles on plugs and points.

Update your car with a TIGER solid state electronic ignition system. Easily installed in 30 minutes... even on new cars.

Tiger 500 CD
 Assembled \$49.95
 Simplikit \$29.95

Postpaid USA.
 Master Charge & BankAmericard accepted.

Tri-Star Corporation
 Phone (303) 243-5200
 P.O. Box 1727
 Grand Junction, Colorado 81501

CIRCLE 13 ON FREE INFORMATION CARD

POTTER BRUMFIELD 4PDT RELAYS
 • 14 pin style
 • 3 amp contacts
 • 24 volt a.c. or
 • 120 volt a.c. coil
\$1.25 each
 specify coil voltage
LARGE QUANTITIES AVAILABLE

ELECTRONIC SIREN MODULE \$7.50 Each
 12 - 15 vdc 400 - 750 ma
 wattle sound @ 110 db
 Sweeping 1000 - 2300 cps
 will drive two 8 ohm spks
 2-1/2 dia 1-1/4" high

HEAT SINK DRILLED FOR TWO TO-3 TRANSISTORS
 Approx. 4"x4"x1"

SPECIAL PRICE \$1.50 each

1 OHM 175 WATT WIREWOUND RESISTOR \$1.75 each
 8 3/4" long, 1-1/8" dia.

HOUSE MARKED DARLINGTON TRANSISTOR
 16 Amps 60 Volts
 150 Watts
 Similar to MJ4030 PNP
 Specify NPN or PNP
\$1.50 each

COMPUTER GRADE CAPACITORS
 All Brand New
 • 63.000 mfd 15v dc 2" x 6" \$2.00
 • 6.000 mfd 75 vdc 3" x 1 1/4" \$2.00
 • 3.000 mfd 150 vdc 2-1/2" x 4-1/2" \$2.00
 • 1.700 mfd 150 vdc 2-1/2" x 4-1/2" \$2.00
 • 100.000 mfd 6 vdc 2-1/2" x 4-3/4" \$2.00

15 for \$1.00
 12 MFD 6VOLTS
TANTALUM CAPACITORS
 • 115 vac 14 watts
 • 4 5/8 inch x 4 5/8 inch
 SIMILAR TO TIP 121NPN
 TIP 126 PNP
75¢ each
 10220

ROTRON 3 BLADE COOLING FANS
 • used but fully tested
 • 115 vac 14 watts
 • 4 5/8 inch x 4 5/8 inch
 SIMILAR TO TIP 121NPN
 TIP 126 PNP
\$8.00 each

ALL ELECTRONICS CORP.
 SEND FOR OUR FREE FLIER
 905 S. Vermont Ave.
 Los Angeles, CA 90006
 (213) 380-8000
 Store & Warehouse Hours
 9 AM - 5 PM
 Monday thru Friday

RADIO-ELECTRONICS

BABY'S FIRST ORDER NOW!
ELECTRONICS

DELTRONIKS
 PO BOX 29363 ✓D28
 ATLANTA, GA 30359
CIRCLE 64 ON FREE INFORMATION CARD
www.americanradiohistory.com

CIRCLE 6 ON FREE INFORMATION CARD

Low Cost...High Performance

DIGITAL MULTIMETER



\$99.95 WIRED

Low Cost, high performance, that's the DM-700. Unlike some of the hobby grade DMMs available, the DM-700 offers professional quality performance and appearance at a hobbyist price. It features 26 different ranges and 5 functions, all arranged in a convenient, easy to use format. Measurements are displayed on a large 3 1/2 digit, 1/2 inch high LED display, with automatic decimal placement, automatic polarity, and overrange indication. You can depend upon the DM-700, state-of-the-art components such as a precision laser trimmed resistor array, semiconductor band gap reference, and reliable LSI circuitry insure lab quality performance for years to come. Basic DC volts and ohms accuracy is 0.1%, and you can measure voltage all the way from 100 μ V to 1000 volts, current from 0.1 μ A to 2.0 amps and resistance from 0.1 ohms to 20 megohms. Overload protection is inherent in the design of the DM-700, 1250 volts, AC or DC on all ranges, making it virtually goof proof. Power is supplied by four 'C' size cells, making the DM-700 portable, and, as options, a nicad battery pack and AC adapter are available. The DM-700 features a handsome, jet black, rugged ABS case with convenient retractable tilt bail. All factory wired units are covered by a one year limited warranty and kits have a 90 day parts warranty.

Order a DM-700, examine it for 10 days, and if you're not satisfied in every way, return it in original form for a prompt refund.

Specifications

DC and AC volts: 100 μ V to 1000 Volts, 5 ranges
 DC and AC current: 0.1 μ A to 2.0 Amps, 5 ranges
 Resistance: 0.1 Ω to 20 megohms, 6 ranges
 Input protection: 1250 volts AC/DC all ranges fuse protected for overcurrent
 Input impedance: 1C megohms, DC/AC volts
 Display: 3 1/2 digits, 0.5 inch LED
 Accuracy: 0.1% basic DC volts
 Power: 4 'C' cells, optional nicad pack, or AC adapter
 Size: 6"W x 3"H x 6"D
 Weight: 2 lbs with batteries

Prices

DM-700 wired + tested	\$99.95
DM-700 kit form	79.95
AC adapter/charger	4.95
Nicad battery pack	16.95
Probe kit	3.95

TERMS: Satisfaction guaranteed or money refunded, COD, add \$1.50. Minimum order \$6.00. Orders under \$10.00, add \$7.50. Add 5% for postage, insurance, handling. Overseas, add 15%. NY residents, add 7% tax.



600 mHz COUNTER



\$99.95 WIRED

The CT-70 breaks the price barrier on lab quality frequency counters. No longer do you have to settle for a kit, half-kit or poor performance, the CT-70 is completely wired and tested, features professional quality construction and specifications, plus is covered by a one year warranty. Power for the CT-70 is provided by four 'AA' size batteries or 12 volts, AC or DC, available as options are a nicad battery pack, and AC adapter. Three selectable frequency ranges, each with its own pre-amp, enable you to make accurate measurements from less than 10 Hz to greater than 600 mHz. All switches are conveniently located on the front panel for ease of operation, and a single input jack eliminates the need to change cables as different ranges are selected. Accurate readings are insured by the use of a large 0.4 inch seven digit LED display, a 1.0 ppm TCXO time base and a handy LED gate light indicator.

The CT-70 is the answer to all your measurement needs, in the field, in the lab, or in the ham shack. Order yours today, examine it for 10 days, if you're not completely satisfied, return the unit for a prompt and courteous refund.

Specifications

Frequency range: 10 Hz to over 600 mHz
 Sensitivity: less than 25 mv to 150 mHz
 less than 150 mv to 600 mHz
 Stability: 1.0 ppm, 20-40°C; 0.05 ppm/°C TCXO crystal time base
 Display: 7 digits, LED, 0.4 inch height
 Input protection: 50 VAC to 60 mHz, 10 VAC to 600 mHz
 Input impedance: 1 megohm, 6 and 60 mHz ranges 50 ohms, 600 mHz range
 Power: 4 'AA' cells, 12 V AC/DC
 Gate: 0.1 sec and 1.0 sec LED gate light
 Decimal point: Automatic, all ranges
 Size: 5"W x 1 1/2"H x 5 1/2"D
 Weight: 1 lb with batteries

Prices

CT-70 wired + tested	\$99.95
AC adapter	4.95
Nicad pack with AC adapter/charger	14.95
Telescopic whip antenna, BNC plug	7.95
Tilt bail assembly	3.95
CT-70 Kit Form	75.95

ramsey electronics

BOX 4072, ROCHESTER, N.Y. 14610
 PHONE ORDERS CALL
 (716) 271-6487

7400 TTL

SN7400N	.16	SN7400N	.29	SN74160N	.89
SN7401N	.18	SN7401N	.35	SN74161N	.89
SN7402N	.18	SN7402N	.35	SN74162N	1.95
SN7403N	.18	SN7403N	.35	SN74163N	.89
SN7404N	.18	SN7404N	5.00	SN74164N	.89
SN7405N	.20	SN7405N	.50	SN74165N	.89
SN7406N	.29	SN7406N	.99	SN74166N	1.25
SN7407N	.29	SN7407N	.99	SN74167N	1.95
SN7408N	.29	SN7408N	.99	SN74170N	.50
SN7409N	.20	SN7409N	5.00	SN74171N	6.00
SN7410N	.18	SN7410N	1.75	SN74173N	1.25
SN7411N	.25	SN7411N	.45	SN74174N	.89
SN7412N	.25	SN7412N	.59	SN74175N	.79
SN7413N	.40	SN7413N	.40	SN74176N	.79
SN7414N	.20	SN7414N	.43	SN74177N	.79
SN7415N	.25	SN7415N	.65	SN74179N	1.95
SN7417N	.25	SN7417N	.85	SN74180N	.79
SN7420N	.20	SN7420N	1.95	SN74181N	1.95
SN7421N	.29	SN7421N	3.00	SN74182N	.79
SN7422N	.39	SN7422N	.89	SN74184N	.95
SN7423N	.25	SN7423N	.35	SN74185N	1.95
SN7425N	.29	SN7425N	.59	SN74186N	9.95
SN7426N	.29	SN7426N	1.95	SN74187N	3.95
SN7427N	.25	SN7427N	1.25	SN74190N	1.25
SN7429N	.39	SN7429N	.39	SN74191N	1.25
SN7430N	.20	SN7430N	.49	SN74192N	.79
SN7432N	.25	SN7432N	.49	SN74193N	.79
SN7437N	.25	SN7437N	.49	SN74194N	.79
SN7438N	.25	SN7438N	.75	SN74195N	.69
SN7439N	.25	SN7439N	.75	SN74196N	.89
SN7440N	.20	SN7440N	.79	SN74197N	.89
SN7441N	.39	SN7441N	2.95	SN74198N	3.95
SN7442N	.49	SN7442N	2.95	SN74199N	1.49
SN7443N	.75	SN7443N	2.95	SN74200N	4.95
SN7444N	.75	SN7444N	.99	SN74201N	.99
SN7445N	.75	SN7445N	1.95	SN74202N	.99
SN7446N	.69	SN7446N	1.29	SN74203N	2.25
SN7447N	.59	SN7447N	.89	SN74204N	3.95
SN7448N	.79	SN7448N	.95	SN74205N	3.95
SN7450N	.20	SN7450N	.95	SN74206N	.95
SN7451N	.20	SN7451N	.95	SN74207N	.69
SN7452N	.20	SN7452N	.95	SN74208N	.69
SN7454N	.20	SN7454N	.79	SN74209N	1.95
SN7459A	.25	SN7459A	.79	SN74300N	1.95
SN7460N	.20	SN7459N	.65	SN74393N	1.95

Cromemco
Incorporated

Z80-4MHz Single Card Computer



Cromemco's Single Card Computer is a complete computer which brings the power of the Z80 and the flexibility of the S-100 into the dedicated computer environment.

The unit offers 4MB of operation, 8K bytes of on-board 2716 PROM, and 16 bytes of static RAM memory. The dual in-line package (DIP) ROM is on-board (2K or 16K) and can be changed without any special tools. The unit is designed for 7.680 MHz operation. It has an industrial grade I/O, and 5 ports for external devices. On-board ROM is available in 16K or 32K bytes for operation. The Single Card Computer is available in 16K or 32K bytes for operation. The Single Card Computer is available in 16K or 32K bytes for operation.


SCC-W (Assembled) \$450.00

Processor: 4MHz Z80
Instructions: 800,000 per sec.
ROM: 4MB (2716 PROM) or 16MB (2716 PROM)
RAM: 4MB (6264 RAM) or 16MB (6264 RAM)
Power: 100W (100W AC)
Dimensions: 10" x 10" x 10"

DISCRETE LEDS

XC556R	red	5/51	XC209R	red	5/51
XC556G	green	4/51	XC209G	green	4/51
XC556Y	yellow	4/51	XC209Y	yellow	4/51
XC556C	clear	4/51	XC209C	clear	4/51

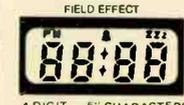TIMEX T1001
LIQUID CRYSTAL DISPLAY
CLASS II
FIELD EFFECT



4 DIGIT - 5" CHARACTERS
THREE ENUNCIATORS
2.00" x 1.20" PACKAGE
INCLUDES CONNECTOR
T1001-Transmissive \$7.95
T1001A-Reflective 8.25

DISPLAY LEDS

TYPE	POLARITY	HT	PRICE	TYPE	POLARITY	HT	PRICE
MAN 1	Common Anode-red	270	2.95	MAN 6730	Common Anode-red	1	560 .99
MAN 2	5 x 7 Dot Matrix-red	300	4.95	MAN 6740	Common Cathode-red-D	1	560 .99
MAN 3	Common Cathode-red	125	2.25	MAN 6750	Common Anode-red	1	560 .99
MAN 4	Common Cathode-red	187	1.95	MAN 6760	Common Cathode-red	1	560 .99
MAN 7G	Common Anode-green	300	1.25	MAN 6780	Common Cathode-red	1	560 .99
MAN 7Y	Common Anode-yellow	300	.99	DL701	Common Anode-red	1	300 .99
MAN 7Z	Common Anode-red	300	.99	DL704	Common Cathode-red	300	.99
MAN 7A	Common Cathode-red	300	1.25	DL707	Common Anode-red	300	.99
MAN 82	Common Cathode-yellow	300	.49	DL728	Common Cathode-red	500	1.49
MAN 84	Common Cathode-yellow	300	.99	DL741	Common Anode-red	600	1.25
MAN 3520	Common Anode-orange	300	.49	DL746	Common Anode-red	1	630 1.49
MAN 3530	Common Anode-orange	1	300 .99	DL749	Common Anode-red	1	630 1.49
MAN 4740	Common Cathode-red	300	.49	FND359	Common Cathode-red	357	.75
MAN 4510	Common Anode-orange	300	.99	FND360	Common Cathode-red	1	530 1.49
MAN 4540	Common Cathode-orange	400	.99	LDL38	Common Cathode-red	1	110 .35
MAN 4710	Common Anode-red	400	.99	FND70	Common Cathode-red	250	.99
MAN 4730	Common Anode-red	400	.99	FND358	Common Cathode	1	357 .75
MAN 4740	Common Cathode-red	400	.99	FND359	Common Cathode(FND500)	500	.99
MAN 4810	Common Anode-yellow	400	.99	FND503	Common Cathode(FND500)	500	.99
MAN 4840	Common Cathode-yellow	400	.99	FND507	Common Anode (FND510)	500	.99
MAN 6610	Common Anode-orange-D	560	.99	5082-7730	Common Anode-red	300	.99
MAN 6630	Common Anode-orange	1	560 .99	H03P-3400	Common Anode-red	800	1.50
MAN 6640	Common Cathode-orange-D	560	.99	H03P-3403	Common Cathode-red	800	1.50
MAN 6650	Common Cathode-orange	1	560 .99	5082-7300	4 x 7 Sgl. Digit-LHDP	600	19.95
MAN 6660	Common Anode-orange	560	.99	5082-7302	4 x 7 Sgl. Digit-LHDP	600	19.95
MAN 6680	Common Cathode-orange	560	.99	5082-7304	Overrange character (±1)	600	15.00
MAN 6710	Common Anode-red-D	560	.99	5082-7340	4 x 7 Sgl. Digit-Hexazodigital	600	22.50

RCA LINEAR

CA3013T	2.15	CA3028N	2.00
CA3023T	2.95	CA3036N	1.80
CA3035T	2.48	CA3066N	.85
CA3039T	1.35	CA3098N	3.75
CA3046N	1.00	CA3130T	1.39
CA3059N	3.25	CA3140T	1.25
CA3062N	3.85	CA3150T	1.25
CA3080T	.85	CA3401N	.99
CA3081N	2.00	CA3600N	3.50

IC SOLDERABLE - LOW PROFILE (TIN) SOCKETS

8 pin LP	1-24	25-49	50-100
14 pin LP	1-17	16	15
16 pin LP	2-21	20	20
18 pin LP	2-28	27	27
20 pin LP	3-4	32	30
14 pin ST	5-27	25	24
16 pin ST	30	27	25
18 pin ST	3-32	30	30
24 pin ST	4-45	45	42
8 pin SG	5-30	27	24
14 pin SG	3-35	32	29
16 pin SG	3-38	35	32
18 pin SG	5-47	47	43

WIRE WRAP SOCKETS (GOLD) LEVEL #3

8 pin WW	5-39	38	31
14 pin WW	4-45	41	37
16 pin WW	3-49	38	37
18 pin WW	5-57	54	49
18 pin WW	7-5	68	62
20 pin WW	8-5	79	72

1/4 WATT RESISTOR ASSORTMENTS - 5%

ASST. 1	5 ea.	27 OHM	33 OHM	39 OHM	47 OHM	56 OHM	50 PCS	\$1.75
ASST. 2	5 ea.	68 OHM	82 OHM	100 OHM	120 OHM	150 OHM	50 PCS	1.75
ASST. 3	5 ea.	1.2K	1.5K	1.8K	2.2K	2.7K	50 PCS	1.75
ASST. 4	5 ea.	82K	10K	12K	15K	18K	50 PCS	1.75
ASST. 5	5 ea.	56K	68K	82K	100K	120K	50 PCS	1.75
ASST. 6	5 ea.	390K	470K	560K	680K	820K	50 PCS	1.75
ASST. 8R	Includes Resistor Assortments 1-7 (30 PCS.)							\$9.95 ea.

Jameco ELECTRONICS

MAIL ORDER ELECTRONICS - WORLDWIDE
1021 HOWARD AVENUE, SAN CARLOS, CA 94070
ADVERTISED PRICES GOOD THRU DECEMBER

PHONE ORDERS WELCOME (415) 592-8097

TELEPHONE/KEYBOARD CHIPS

A5-Y-9100	Push Button Telephone Dialler	\$14.95
A5-Y-9200	Memory Dialler	4.95
A5-Y-9300	CMOS Clock Generator	14.95
A5-Y-9400	Keyboard Encoder (16 keys)	14.95
A5-Y-9500	Keyboard Encoder (16 keys)	7.95
A5-Y-9600	Keyboard Encoder (16 keys)	7.95
A5-Y-9700	Keyboard Encoder (20 keys)	6.25

ICM CHIPS

ICM7045	CMOS Prescaler	24.95
ICM7205	CMOS LED Stopwatch/Timer	19.95
ICM7207	Oscillator Controller	7.50
ICM7208	Seven Decade Counter	19.95
ICM7209	Clock Generator	6.95

NMOS READ ONLY MEMORIES

MCM6571	128 X 9 X 7 ASCII Shifted with Greek	13.50
MCM6574	128 X 9 X 7 Math Symbol & Pictures	13.50
MCM6575	128 X 9 X 7 Alpha Character Gen	13.50

MISCELLANEOUS

TL074CN	Quad Low Noise Bi-Dir Op Amp	2.49
TL494CN	Switching Regulator	4.49
TL496CP	Single Switching Regulator	1.67
TL1090	Divide 10/1 Prescaler	RC2567
95H90	Hi-Speed Divide 10/1 Prescaler	11.95
4N33	Photo-Darlington Opto-Isolator	3.95
MM530240	Top Offset Pwr. Generator	17.50
MM530250	5MHz 2-phase CMOS clock driver	3.75
TL1308	27' read mem. display w/integ. logic chip	10.95
MM5320	TV Camera Sync. Generator	14.95
MM5330	4 1/2 Digit DPM Logic Block (Special)	3.95
LD110111	3 1/2 Digit A/D Converter Set	25.00/set
MC1433P	3 1/2 Digit A/D Converter	13.95

LITRNDX ISO-LIT 1

Photo Transistor Opto-Isolator
(Same as MC92 or 4N25)

49¢ each

TV GAME CHIP AND CRYSTAL

AY-3-8500-1 and 2.01 MHz Crystal (Chip & Crystal includes score display, 6 games and select angles, etc.)

7.95/set

EXAR

XR205	\$8.40	XR224CP	\$1.20
XR210	4.40	XR226A	4.25
XR215	4.40	XR256E	3.20
XR220	1.55	XR256F	2.99
XR-L555	1.50	J22206K	19.95
XR555	.39	XR1800	3.20
XR556	.99	XR2206	4.40
XR567CT	.99	XR2207	3.85
XR1310PT	1.25	XR2008	3.80
XR1468CN	3.85	XR2211	5.25
XR1488	1.95	XR2212	4.35
XR1489	1.95	XR2240	3.45
		XR4741	1.47

DIODES

TYPE	VOLTS	PRICE	TYPE	VOLTS	PRICE
1N4745	3.3	400m	1N4003	200 PIV 1 AMP	12/1.00
1N4751	5.1	400m	1N4004	400 PIV 1 AMP	12/1.00
1N4752	6.2	400m	1N4005	600 PIV 1 AMP	10/1.00
1N4753	8.2	400m	1N4006	800 PIV 1 AMP	10/1.00
1N4754	8.0	400m	1N4007	1000 PIV 1 AMP	10/1.00
1N4757	8.0	400m	1N4148	75 10m	15/1.00
1N4759	12.0	400m	1N4154	35 10m	12/1.00
1N4850	6.2	400m	1N4155	35 10m	28
1N4851	6.2	400m	1N4156	35 10m	28
1N4852	6.2	400m	1N4157	35 10m	28
1N4853	6.2	400m	1N4158	35 10m	28
1N4854	6.2	400m	1N4159	35 10m	28
1N4855	6.2	400m	1N4160	35 10m	28
1N4856	6.2	400m	1N4161	35 10m	28
1N4857	6.2	400m	1N4162	35 10m	28
1N4858	6.2	400m	1N4163	35 10m	28
1N4859	6.2	400m	1N4164	35 10m	28
1N4860	6.2	400m	1N4165	35 10m	28
1N4861	6.2	400m	1N4166	35 10m	28
1N4862	6.2	400m	1N4167	35 10m	28
1N4863	6.2	400m	1N4168	35 10m	28
1N4864	6.2	400m	1N4169	35 10m	28
1N4865	6.2	400m	1N4170	35 10m	28
1N4866	6.2	400m	1N4171	35 10m	28
1N4867	6.2	400m	1N4172	35 10m	28
1N4868	6.2	400m	1N4173	35 10m	28
1N4869	6.2	400m	1N4174	35 10m	28
1N4870	6.2	400m	1N4175	35 10m	28
1N4871	6.2	400m	1N4176	35 10m	28
1N4872	6.2	400m	1N4177	35 10m	28
1N4873	6.2	400m	1N4178	35 10m	28
1N4874	6.2	400m	1N4179	35 10m	28
1N4875	6.2	400m	1N4180	35 10m	28
1N4876	6.2	400m	1N4181	35 10m	28
1N4877	6.2	400m	1N4182	35 10m	28
1N4878	6.2	400m	1N4183	35 10m	28

ULN2001 High-current Drivers. Darlington's 75¢

P1103A 1024X1 Dynamic RAM 24¢

MH0026CJ DUAL CLOCK DRIVER \$100

8212 8 BIT I/O PORT \$199

8216 BUS DRIVER

MODEL 7016A 16K DYNAMIC MEMORY ADD-ON

THE 7016A IS A 16K MEMORY ADD-ON FOR THE APPLE II™ OR TRS-80™. THE KIT INCLUDES JUMPERS AND INSTRUCTION

California Computer Systems Model 7016A \$109.95

MC1488P LINE DRIVER ★89¢

MC1489P LINE RECEIVER

78H05 5 AMP 5VOLT REGULATOR IN TO-3 PKG \$6.95

2716 450ns single+5V TI, HIT., INT., SGS 16K EPROM \$38.50

TASA's Solid State Micro Proximity Keyboards



Full 128 position 8-bit ASCII output plus continuous strobe parity select. Completely solid state, washable sealed construction. 55 micro proximity sensor positions, three-color coded to function. Immune to static charge or external noise. Low power requirement: 18V DC, 35mA @ 0.65 watt built-in regulator.

Additional TASA Model 55 Keyboard Features:

- Tough polycarbonate surface - skived from environment fully enclosed
- Built-in electronic shift lock and lock key-releaser
- Electronic "hysteresis" for lock "leak"
- Signal activation time approximately 1 millisecond - no "bounce"
- Parallel output - Active pull down, direct TTL compatible line loads - 3200 ohm connector system
- CMOS compatible with pull-up resistor
- Continuous strobe and latched data signals for easy timing or logging
- Standard 0.54 inch center 13.9mm 1.8 position dual in-line thru hole edge connector

General Description: The TASA Model 55 and all other TASA keyboards are truly solid state touch-activated systems, combining the cost advantages of above-mentioned IC components with fully integrated, single chip security. Not a "dummy" 55 ASCII keyboard provides full function capability in all modes. It is (low priced) parallel output for all computers. It is (low priced) parallel output for all computers. It is (low priced) parallel output for all computers. It is (low priced) parallel output for all computers.

\$75.00 FROM STOCK



Model 2016B 16K STATIC MEMORY

- ★ FULLY STATIC OPERATION
- ★ USES 214 TYPE STATIC RAMS
- ★ +8 VDC INPUT AT LESS THAN 2 AMPS
- ★ BANK SELECT AVAILABLE BY BANK PORT AND BANK BYTE
- ★ PHANTOM LINE CAPABILITY
- ★ ADDRESSABLE IN 4K BLOCKS IN 4K INCREMENTS
- ★ 4K BLOCKS CAN BE LOCATED ANYWHERE WITHIN 64K BANK
- ★ MAY BE USED AS A 4K, 8K, 12K OR 16K MEMORY BOARD
- ★ LED INDICATORS FOR BOARD/BANK ACTIVE INDICATION
- ★ SOLDER MASK ON BOTH SIDES OF BOARD
- ★ SILK SCREEN WITH PART AND REFERENCE DESIGNATION

ASSEMBLED & TESTED California Computer Systems \$297.95

6301-1J 256X4 PROM \$165

SOROC TERMINAL IQ 120 \$759.00

8038C VCO Waveform Gen w/sine \$2.75

7400 TTL		7400 TTL CON'T	
7400	.18	74107	.35
7408	.21	74141	.85
7410	.18	74155	.80
7412	.34	74157	.80
7413	.65	74161	.85
7416	.32	74165	.85
7420	.20	74175	.90
7425	.30	74181	1.35
7427	.32	74195	.95
7437	.28	74279	.75
7438	.28	74367	.75
7440	.18	74393	1.95
7451	.18		
7454	.18	74LS00	.40
7454	.18	74LS03	.35
7474	.35	74LS09	.55
7475	.55	74LS20	.40
7485	.85	74LS26	.50
7490	.40	74LS27	.45
7492	.50	74LS74	.99
7493	.50	74LS122	.55
7495	.70	74LS157	1.50

MISC TTL

T.I./M.M.I. 74LS241 IN 74LS244 \$2.45

74LS243 STOCK 74LS373

74LS374 LIMIT 10 EACH

I.C. MASTER 1979 \$34.95

2708 450ns AMD, SGS 1024X8 EPROM \$8.50

CSC Logic Probe Kit. \$17.95

Complete, easy-to-follow instructions help make this a one-night project.

CONCORD COMPUTER COMPONENTS

1973 SO. STATE COLLEGE - ANAHEIM, CA. 92806

Visa - Master Charge
Check or M.O. (714) 937-0641
No COD

Minimum Order - 10.00
Add 1.00 for Frt.
Cal. Res. add 6%

MISC TTL CON'T

74LS165	1.65	LM556	.85
74LS197	.75	LM711/H	.38
74S03	.65	LM720N	2.75
74S05	.65	LM723N	.55
74S51	.60	LM725H	3.25
74S182	.99	LM733N	.95
		LM741N/H	.35
LM102H	3.00	LM747H	.80
LM108H	4.50	LM3900	.75
LM300H	1.25	TRANSISTORS	DIODES
LM301N	.35	2N2222A	5/1.00
LM311N	.79	2N2907A	5/1.00
LM320T5	1.25	2N3055	.85
LM320M5	1.25	2N3904	6/1.00
LM320T12	1.25	2N3906	6/1.00
LM320T15	1.25	2N4401	6/1.00
LM322N	1.75	2N4403	6/1.00
LM323K	5.50	1N4003	15/1.00
LM320K5	5.00	1N4005	12/1.00
LM340T5	1.25	1N4007	10/1.00
LM340T12	1.25	1N4148	20/1.00
LM340T15	1.25	1N5237B	10/1.00

CIRCLE 54 ON FREE INFORMATION CARD

We bought 350,000 LED's. And you get the savings. Reds, greens, yellows, orange, small, medium, large. Bags of 25 - mixed \$2.75. That's only 11¢ each. Compare this bargain up to twice our price.

FACTORY PRIME
SBI - Polar LED 59¢ ea. or 10 for \$5

LAB-BENCH VARIABLE POWER SUPPLY KIT
5 to 20 VDC at 1 AMP. Short circuit protected by current limit. Uses IC regulator and 10 AMP Power Darlington. Very good regulation and low ripple. Kit includes PC Board, all parts, large heatsink and shielded transformer. 50 MV. TYP. Regulation. \$15.99 KIT

LED BAR GRAPH AND ANALOG METER DRIVER
New from National Semi. #LM3914. Drives 10 LED directly for making bar graphs, audio power meters, analog meters, LED oscilloscopes, etc. Units can be stacked for more LED's. A super versatile and truly remarkable IC. Just out!
SPECIAL PRICE: \$3.99 INCLUDES 12 Page Spec. Sheet

CLOCK MODULE OPTIONS
MA1008 A and D MA1013

Switches and pot for all options.

Includes:
5 push buttons
1 toggle
1 10K pot \$2.50
Alarm Parts (including high impedance transducer) Much more efficient than a speaker \$1.50
Transducer only (unbelievably loud!) \$1.10

SONY 23 WATT AUDIO AMP MODULE
#STK-054. 23 WATTS SUPER CLEAN AUDIO. 20HZ to 100 KHZ ± 2 DB. HYBRID, SILICON, SELF-CONTAINED MODULE. ONLY 1 1/4 x 2 1/2 IN. WITH DATA.
COMPARE AT UP TO TWICE OUR PRICE! \$8.99 each

16K DYNAMIC RAM CHIP
WORKS IN TRS-80 OR APPLE II

16K X 1 Bits. 16 Pin Package. Same as Mostek 4116-4. 250 NS access. 410 NS cycle time. Our best price yet for this state of the art RAM. 32K and 64K RAM boards using this chip are readily available. These are new fully guaranteed devices by a major mfg.
VERY LIMITED STOCK!
"MAGAZINE SPECIAL" - 8/\$79.50

60 Hz CRYSTAL TIME BASE
\$4.95 (Complete Kit)

Uses MM5369 CMOS divider IC with high accuracy 3.579545 MHZ Crystal. Use with all MOS Clock Chips or Modules. Draws only 1.5 MA. All parts, data and PC Board included. 100 Hz. same as above, except \$5.95.

MICRO MINI TOGGLE SWITCHES
6 for \$5 with hardware.

Sound Activated Switch not a kit. Already assembled. Clap your hands and turn on lights, music boxes, coffee pots, etc. Full spec. sheet with each unit.
69¢ ea. 10 for \$5.50

FAIRCHILD PNP "SUPER TRANSISTOR"
2N4402. TO-92 Plastic. Silicon PNP Driver. High Current. VCEO-40HFE-50 to 150 at 150 MA. FT-150 MHZ A super "BEEFED-UP" Version of the 2N3906.
8 FOR \$1.19

JUMBO IC ASSORTMENT
All new not rejects. BIG computer mfg. Surplus. Some standard marked, many house numbered. TTL, DTL, LINEAR. All prime. 1st line.
50 for \$1.59 500 for \$12.95

NATIONAL SEMICONDUCTOR "COLOSSUS JR." JUMBO CLOCK MODULE MA1013 BRAND NEW!



\$8.50 (3 FOR \$15) (AC XFMR \$1.95)

ASSEMBLED! NOT A KIT! MANUFACTURER'S CLOSEOUT! PERFECT FOR USE WITH A TIMEBASE.

- Bright 4 digit 0.7" LED Display
- Complete - Add only Transformer and Switches
- 24 Hour Alarm Signal Output
- 12 Hour Real Time Format
- 50 or 60 Hz Operation
- Power Failure Indication
- LED Brightness Control
- Sleep and Snooze Timers
- Alarm "on" and PM Indicators
- Direct Drive - No RFI
- Direct Replacement for MA1012
- Comes with Full Data

TOSHIBA POWER AUDIO AMP
5.8 WATTS RMS Typical Output. 50 to 30,000 HZ ± 3 DB. For CB's, tape decks, PA's, etc. Works off of a single supply voltage from 10.5 to 18 VDC. 10 Pin plastic DIP with special built in heat sink tab. Perfect for use on 12VDC.
\$3.99 each

Digital Research: Parts (OF TEXAS)

P.O. BOX 401247 • GARLAND, TEXAS 75041 • (214) 271-2461

TERMS: Add 50¢ postage, we pay balance. Orders under \$15 add 75¢ handling. No C.O.D. We accept Visa, MasterCharge and American Express cards. Tex. Res. add 5% Tax. Foreign orders (except Canada) add 20% P&H. 90 Day Money Back Guarantee on all items.
Write for our free catalog full of many useful bargains.

2 YEAR WARRANTY

LEADER Instruments Corp.

OSCILLOSCOPES

2 YEAR WARRANTY




Model LBO-507

20 MHz, TRIGGERED
 ■ Single trace, automatic trigger for highly stable, bright display.
 ■ 17.5nSec rise time, 10mV/cm to 20V/cm Vertical Sensitivity, 11 steps.



Model LBO-508

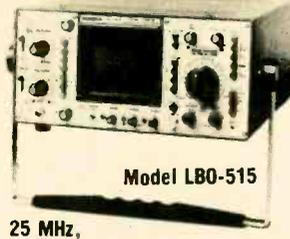20 MHz, DUAL TRACE
 ■ Add, subtract modes on CH-1 & CH-2 facilitate easy checkup for simultaneous pulses, signal levels, distortion & noise cancelling.



Model LBO-515

25 MHz, DELAYED SWEEP, DUAL TRACE
 ■ Built in variable delay circuitry — 1µSec to 5 Sec. ■ 5mV/Div. Vertical Sensitivity.



Model LBO-520

30 MHz, FIXED DELAY, DUAL TRACE
 ■ Dual trace, 30 MHz bandwidth.
 ■ 5mV/cm Vertical Sensitivity.

COLOR BAR GENERATORS, BRIDGES, TESTERS.

NTSC Color Bar Pattern Generator



Model LCG-396

- NTSC color bars
- Provides full-field or 10W insertion, plus on-off control of chroma and luminance
- Better checking and adjusting of purity and white balance via red, blue, green, white sliders
- Data and single crosshairs for convergence, raster and all other alignment requirements
- 75i Video (1 Volt fixed) and RF output for TV and VTR equipment
- Equalizing pulse phase locked to color sub-carrier
- Adjustable scanning control permits progressive or interlaced scanning to eliminate flicker
- Provides all signals required to time, test & evaluate all MATV, CATV, VTR/VCR, color and base systems.

Completely Portable, Battery Operated TV Color Analyzer



Model LCG-397

- RF, IF, composite video outputs
- 0-100% variable color burst for easy chroma service
- 18 convergence patterns — 10 bar gated, 3 bar gated and rainbow patterns
- 3 dot patterns, 2 crosshairs patterns
- 3 vertical lines and 3 horizontal lines plus gray scale
- Oscilloscope trigger outputs
- Battery operated 4 standard "C" cells, 1.5V each

Transistorized LCR Bridge



Model LCR-740

- Highly accurate 3 digit readout.
- Measures Inductance (L), Capacitance (C) and Resistance (R) within 0.5% accuracy
- Readouts variable with built-in 10% overrange
- Loss Factor scale (D)
- Operates on 1.9V battery or through built-in AC adapter

The Automatic Transistor Checker



Model LTC-906

- Automatically checks transistors, FET's, diodes, good/bad, in or out of circuit.
- Automatically identifies Germanium or Silicon
- Automatically identifies elements
- Automatically tests broad range of parameters with simple, program on/off switches
- LED display plus audible tone indicates defective or good performance
- Absolute meter readout of H_{FE} , B_{DC} and Leakage current.
- Totally portable, battery operated — 9V battery.

Before you buy, check our prices...
Call TOLL FREE (800) 645-9518
 In N.Y. State call (516) 752-0050

FORDHAM

RADIO SUPPLY CO. INC.
 855R Conklin St.
 Farmingdale, N.Y. 11735

YOUR ONE STOP DISCOUNT CENTER
 Master Charge, Bank Americard, Visa, C.O.D.'s accepted.
"We Will Beat Any Advertised Price"

ADD \$3.00 TO COVER SHIPPING, HANDLING & INSURANCE N.Y.
 Res. add approx. sales tax.

HICKOK 3 1/2 Digit Mini-Multimeter
 MODEL LX 303 \$69.50

Sinclair PDM35 digital MultiMeter
 \$52.95

BK-PRECISION 3 1/2-Digit Portable DMM
 • Overhead Protected • Battery or AC operation • 3" high LED Display
 • Auto Zeroing Model 2800 comes complete with test leads, operating manual, and spare fuse

NLS 15 MHz Mini Oscilloscope
 Model MS 15
 Reg. \$318.00 \$269.95

- Battery or line operation
 - Automatic and line sync modes
 - Power consumption less than 15W
- NOW AVAILABLE**
- 15MHz Dual Trace - Model MS 215 Reg. \$435.00... \$369.95
 - 30 MHz Dual Trace - Model MS 230 Reg. \$559... \$479.95

GOULD 15 MHz Dual Trace
 • Triggers in excess of 25 MHz
 Model DS255 \$795 including probes

Weller Controlled Output Soldering Station
 \$45.00
 Reg. \$75.00 Model WTCP-N

Weller Xcelite

Service Master Attache Style Tool Kit Tool Cases
 Model 995M \$42.95
 Model TC 100/ST \$269.95 Reg. \$283.00
 Model 99P Roll Kit \$15.95

Miniature High Fidelity Stereo Speaker System.
 Reg. \$139.00 \$69.50

Magnifier LAMP
 Model MG 10A \$49.50

700 Series Precision ground and polished magnification lens. Uses 22W T-9 Circine Fluorescent.
 RC Circuit Box/RCA-VIZ
 • 36 resistors
 • 15 ohms to 10 megohms
 • 18 capacitors (10p to 0.22 uF)
 Model WC 412A Reg. \$40 \$36 includes test leads

30MHz Dual Trace with Delay Line
 Reg. \$1050 \$889.95 with probes

Function Generator
 Model LCX \$127.50
 Size square, triangle and separate TTL Square wave output

Chess Challenger
 • Ten levels of play
 Model LCX \$179.95

SENCORE TV-VTR-MATV and Video Analyzer

Model VA48 \$875.00 Reg. \$975.00

ES CONTINENTAL SPECIALTIES 100 MHz 8-Digit Counter \$119.00
 • 20 Hz 100 MHz Range • 6" LED Display • Fully Automatic
 • Includes 100 IPC clip lead input cable/insulator

BK-PRECISION Digital Capacitance Meter
 Model 820 \$249.95

Logic Monitor
 • Automically displays static and dynamic logic • Works with DTL, HTL, TTL and CMOS • 16 LED display
 • Circuit powered design
 Model LM-1 \$52.95 complete

Remote System for Lights & Appliances
 4 Piece Starter Kit Reg. \$87.95 \$79.95

Bearcat Scanner
 Model 250 \$299.95

Touch K100 Scanner
 Reg. \$269 \$199.95

"We Will Beat Any Advertised Price"

PS500 500MHZ Prescaler \$52.95

CODE-A-PHONE Telephone Answering Devices
 Wiremate Command Model 1400 \$199.95

WAHL NEW ISO-TIP "Quick Charge"
 1-7 units Model 7500 Cordless Soldering Iron \$17.95
 Model 5800 Thermal Spot Circuit Tester \$22.50

BSR Changer Accessories
 Model BSR-129 \$29.95

Function Generator
 Model 270 \$169.15

Stereo Power Booster
 POW 40 \$24.95

FREE 1979 Catalog

Model MAX-100

BSR Changer Accessories
 Model BSR-129 \$29.95

Microflame Deluxe Gas Torch Kit
 Model 4400 Reg. \$39.95 \$29.95

In-Dash AM/FM 8 Track Stereo
 C-777 \$52.50

AM/FM Cassette Stereo
 CAS 888 \$57.50

Stereo Power Booster
 POW 40 \$24.95

FREE 1979 Catalog

Call TOLL FREE (800) 645-9518
 For N.Y. State call (516) 752-0050
 Master Charge • Bank Americard
 • C.O.D. • Check • Money Order
 Add \$3.00 for shipping and insurance
 C.O.D.'s Extra New York State residents add approx. sales tax

FORDHAM
 855R Conklin St. Farmingdale, N.Y. 11735

Active Electronic Sales Corp.

Zilog

Z8000/1	\$195.00	16 Bit CPU with segmented address space to 8 Megabytes.	
Z8000/2	\$150.00	16 Bit CPU with non segmented address space to 64K bytes.	
Z80-CPU	2.5 Mhz \$ 9.95	Z80-DMA	2.5 Mhz \$26.85
Z80A-CPU	4.0 Mhz \$11.95	Z80A-DMA	4.0 Mhz \$33.60
Z80-PIO	2.5 Mhz \$7.20	Z80-SIO/O	2.5 Mhz \$36.00
Z80A-PIO	4.0 Mhz \$8.40	Z80A-SIO/O	4.0 Mhz \$39.50
Z80-CTC	2.5 Mhz \$7.20	Z80-SIO/1	2.5 Mhz \$36.00
Z80A-CTC	4.0 Mhz \$8.40	Z80A-SIO/1	4.0 Mhz \$39.50
		Z80-SIO/2	2.5 Mhz \$36.00
		Z80A-SIO/2	4.0 Mhz \$39.50

MICROPROCESSOR CHIP SETS

Part No.	Price	Part No.	Price
8080A	9.95 \$5.95	6800	6.95
8085	12.95	6802	11.95
8212	3.45	6810	3.95
8214	3.95	6820	3.95
8216	3.25	6821	3.95
8224	2.95	6850	4.25
8226	2.25	6852	3.95
8228	3.98		
8238	4.75	SCP1802LE	9.95
8251	5.75	SCP1824LE	3.50
8253	14.95	SCP1852LE	1.50
8255	5.75	SCP1853LE	1.45
8257	10.95	SCP1854LE	6.95
8259	14.95	SCP1856LE	1.95
		SCP1858LE	1.95
		SCP1859LE	1.50

Metal Power Transistors

Homotaxial - Best Quality

2N3054	.65	60V NPN	TO-66
2N3055	.69	70V NPN	TO-3
2N3442	1.50	160V NPN	TO-3
2N3771	1.95	50V NPN	TO-3
2N3772	1.95	100V NPN	TO-3
2N3773	2.50	160V NPN	TO-3

Universal SCR

C106D .34 5.0 AMP 400V TO-220

E PROM'S Special of the Month

C1702A-6	\$4.95
256 x 8 1.5 us	
C2708	\$9.95
1K x 8 450 ns	
TMS2716	\$34.95 \$29.95
16K (2K x 8) 450 ns	
(3 power supplies) T.I. Version	
C2716/TMS2516	\$49.95 \$47.95
16K (2K x 8) 450 ns	
(Single 5V supply - Intel version)	

"TTL" We are overstocked - SPECIAL OFFER - Major Manufacturer: TTL

7401N	.09	Quad 2 input NAND gate o/c
7430N	.16	8 input NAND gate
7437N	.19	Quad 2 input NAND buffer
7440N	.12	Dual 4 input NAND buffer
7443N	.35	Excess 3 to decimal decoder
7450N	.12	Exp. dual 2 x 2 input and or invert gate
7453N	.12	Exp. 4 x 2 input and or invert gate
7460N	.12	Dual 4 input expander
7464N	.09	4-2-3-2 input and or invert gate
7465N	.09	4-2-3-2 input and or invert gate o/c
7482N	.29	2 Bit binary full adder
74158N	.24	Dual 2 to 4 line decoder/demultiplexer o/c
74176N	.29	Presetable decade counter
74182N	.29	Look ahead carry generator
74195N	.29	4 Bit Parallel in, parallel out s/r
74402N	.09	Quad 2 input NOR gate
74403N	.09	Quad 2 input NAND gate o/c
74405N	.09	Hex inverter o/c
74412N	.09	Triple 3 input NAND gate o/c
74415N	.09	Triple 3 input AND gate o/c
74473N	.09	Dual J-K Master slave flip flop
74465N	.09	4-2-3-2 Input and or invert
744113N	.15	Dual J-K neg. edge trig. flip flop
744114N	.15	Dual J-K neg. edge trig. flip flop
744181N	.15	4 Bit arithmetic logic unit

Texas Instruments Low Profile Sockets

Lowest prices anywhere for the highest quality, an unbeatable combination. Over one million pieces in stock.

Contacts	Price	Contacts	Price
8 PIN	.08	22 PIN	.22
14 PIN	.12	24 PIN	.24
16 PIN	.14	28 PIN	.28
18 PIN	.18	40 PIN	.40
20 PIN	.20		

1979 IC MASTER

Complete integrated circuit data selector. Master guide to the latest I.C.'s including microprocessors and consumer circuits.

~~\$29.95~~

2500 pages

"New Special Offer"

\$27.95

VOLTAGE REGULATORS

7800UC Series (TO-220 Plastic)	Positive 1 AMP	5, 6, 8, 12, 15, 18, 24, Volts	\$0.99
			Data Available on Request

High Current (TO-3)

78H05SC	\$4.92	5 volts/5 amps
78H12SC	\$5.07	12 volts/5 amps
78H15SC	\$5.07	15 volts/5 amps
78P05SC	\$7.56	5 volts/10 amps
78HGKC	\$5.75	5V-24V/5A Positive Adjustable
79HGKC	\$8.32	-24V to 211V/5A Negative Adjustable
SH1605	\$12.22	3V-30V/5A Adj. Step Down Switching
SH1705	\$7.56	5V/5A Fixed Positive

Prices in this ad are valid only until Nov. 30, 1979

P.O. BOX 1035 FRAMINGHAM, MASSACHUSETTS 01701

Over the counter sales, 12 Mercer Rd., Natick, Mass 01760 Behind Zayres on Rte. 9 Telephone Orders & Enquiries (617) 879-0077

IN CANADA

5651 FERRIER ST
MONTREAL, QUEBEC
H4P 2K5
Tel: (514) 735-6425

4800 DUFFERIN ST
DOWNSVIEW, ONTARIO
M3H 5S9
Tel: (416) 661-1115

MINIMUM ORDER \$10.00 • ADD \$2.00 TO COVER POSTAGE & HANDLING

Foreign customers please remit payment on an international bank draft or international postal money order in American dollars

BAXTER CENTRE
1050 BAXTER ROAD
OTTAWA, ONTARIO
K2C 3P2
Tel: (613) 820-9471

3070 KINGSWAY
VANCOUVER, B.C.
V5R 5J7
Tel: (604) 438-3321





ATTENTION ELF OWNERS: QUEST SUPER BASIC

Quest, the leader in inexpensive 1802 systems announces another first. Quest is the first company worldwide to ship a full size Basic for 1802 systems. A complete function Super Basic by Ron Cenko including floating point capability with scientific notation (number range $\pm 1.7E^{20}$), 32 bit integer ± 2 billion, Multidim arrays, String arrays, String manipulation, Cassette I/O, Save and load, Basic, Data and machine language programs and over 75 Statements, Functions and Operators.

Easily adaptable on most 1802 systems. Requires 12K RAM minimum for Basic and user programs. Cassette version in stock now. ROM

RCA Cosmac Super Elf Computer \$106.95

Compare features before you decide to buy any other computer. There is no other computer on the market today that has all the desirable benefits of the Super Elf for so little money. The Super Elf is a small single board computer that does many big things. It is an excellent computer for training and for learning programming with its machine language and yet it is easily expanded with additional memory, Full Basic, ASCII Keyboards, video character generation, etc.

Before you buy another small computer, see if it includes the following features: ROM monitor; State and Mode displays; Single step; Optional address displays; Power Supply; Audio Amplifier and Speaker; Fully socketed for all IC's; Real cost of in warranty repairs; Full documentation.

The Super Elf includes a ROM monitor for program loading, editing and execution with SINGLE STEP for program debugging which is not included in others at the same price. With SINGLE STEP you can see the microprocessor chip operating with the unique Quest address and data bus displays before, during and after executing instructions. Also, CPU mode and instruction cycle are decoded and displayed on 8 LED indicators.

An RCA 1861 video graphics chip allows you to connect to your own TV with an inexpensive video modulator to do graphics and games. There is a speaker system included for writing your own music or using many music programs already written. The speaker amplifier may also be used to drive relays for control purposes.

Super Expansion Board with Cassette Interface \$89.95

This is truly an astounding value! This board has been designed to allow you to decide how you want it optioned. The Super Expansion Board comes with 4K of low power RAM fully addressable anywhere in 64K with built-in memory protect and a cassette interface. Provisions have been made for all other options on the same board and it fits neatly into the hardwood cabinet alongside the Super Elf. The board includes slots for up to 6K of EPROM (2708, 2758, 2716 or TI 2716) and is fully socketed. EPROM can be used for the monitor and Tiny Basic or other purposes.

A 1K Super ROM Monitor \$19.95 is available as an on board option in 2708 EPROM which has been preprogrammed with a program loader/editor and error checking multi file cassette read/write software, (relocatable cassette file) another exclusive from Quest. It includes register save and readout, block move capability and video graphics driver with blinking cursor. Break points can be used with the register save feature to isolate program bugs quickly, then follow with single step. The Super Monitor is written with

versions coming soon with exchange privilege allowing some credit for cassette version.

Super Basic on Cassette \$40.00

Tom Pittman's 1802 Tiny Basic Source listing now available. Find out how Tom Pittman wrote Tiny Basic and how to get the most out of it. Never offered before. \$19.00

S-100 Slot Expansion \$9.95

Coming Soon: Assembler and Editor; Elf II Adapter Board. High resolution alpha/numeric with color graphics expandable up to 256 x 192 resolution for less than \$100.

16K Dynam. RAM bd. expand. 32K; less than \$150.

A 24 key HEX keyboard includes 16 HEX keys plus load, reset, run, wall, input, memory protect, monitor select and single step. Large, on board displays provide output and optional high and low address. There is a 44 pin standard connector slot for PC cards and a 50 pin connector slot for the Quest Super Expansion Board. Power supply and sockets for all IC's are included in the price plus a detailed 127 pg. instruction manual which now includes over 40 pgs. of software info. including a series of lessons to help get you started and a music program and graphics target game.

Many schools and universities are using the Super Elf as a course of study. OEM's use it for training and research and development.

Remember, other computers only offer Super Elf features at additional cost or not at all. Compare before you buy. Super Elf Kit \$106.95, High address option \$8.95, Low address option \$9.95, Custom Cabinet with drilled and labelled plexiglass front panel \$24.95, Expansion Cabinet with room for 4 S-100 boards \$41.00, NiCad Battery Memory Saver Kit \$6.95. All kits and options also completely assembled and tested.

Questdata, a 12 page monthly software publication for 1802 computer users is available by subscription for \$12.00 per year.

Tiny Basic Cassette \$10.00, on ROM \$38.00, original Elf kit board \$14.95. 1802 software; Moews Video Graphics \$3.50. Games and Music \$3.00, Chip 8 Interpreter \$5.50.

subroutines allowing users to take advantage of monitor functions simply by calling them up. Improvements and revisions are easily done with the monitor. If you have the Super Expansion Board and Super Monitor the monitor is up and running at the push of a button.

Other on board options include Parallel Input and Output Ports with full handshake. They allow easy connection of an ASCII keyboard to the input port. RS 232 and 20 ma Current Loop for teletype or other device are on board and if you need more memory there are two S-100 slots for static RAM or video boards. Also a 1K Super Monitor version 2 with video driver for full capability display with Tiny Basic and a video interface board. Parallel I/O Ports \$9.85, RS 232 \$4.50, TTY 20 ma I/F \$1.95, S-100 \$4.50. A 50 pin connector set with ribbon cable is available at \$12.50 for easy connection between the Super Elf and the Super Expansion Board.

Power Supply Kit for the complete system (See Multi-volt Power Supply below).

Multi-volt Computer Power Supply
8v 5 amp, $\pm 18v$.5 amp, 5v 1.5 amp, $\pm 5v$.5 amp, 12v 5 amp, $\pm 12v$ option, $\pm 5v$, $\pm 12v$ are regulated. Kit \$29.95. Kit with punched frame \$37.45, \$4.00 shipping. Woodgrain case \$10.00, \$1.50 shipping.

60 Hz Crystal Time Base Kit \$4.40
Converts digital clocks from AC line frequency to crystal time base. Outstanding accuracy. Kit includes: PC board, IC, crystal, resistors, capacitors and trimmer.

Same day shipment. First line parts only. Factory tested. Guaranteed money back. Quality IC's and other components at factory prices.

INTEGRATED CIRCUITS

7400TL	1.50	CD4021	1.25
7400N	1.17	CD4022	1.10
7402N	1.17	CD4023	1.10
7404N	1.17	CD4024	1.10
7409N	2.3	CD4025	2.00
7410N	1.17	CD4026	1.10
7414N	1.17	CD4027	1.10
7414N	1.17	CD4028	1.10
7420N	1.17	CD4029	1.10
7422N	1.17	CD4030	1.10
7423N	1.17	CD4031	1.10
7424N	1.17	CD4032	1.10
7632N	1.17	CD4240	1.10
7633N	1.17	CD	

3rd Generation S-100

We're expanding the options for professional level S-100 systems by using the experience we've acquired in the past, mixing in the best technology offered by the present, and building products for the future... products that meet, and often exceed, the demands of a new wave of S-100 users. When you move up to S-100, move up to the CompuPro™ line from Godbout Electronics.

NEW! HIGH-PERFORMANCE S-100 MOTHERBOARDS

19 slot: \$174 unkit, \$214 assm
12 slot: \$129 unkit, \$169 assm
6 slot: \$89 unkit, \$129 assm

(Unkits have edge connectors and termination resistors pre-soldered in place for easy assembly.)

These 3rd generation motherboards are shielded, terminated, and designed to work with the latest 5 and 10 MHz CPUs coming on line. Fits in Godbout, Vector, IMSAI, TEI, and similar enclosures. These high quality products are a welcome addition to any system — or the start of a great one.

2S "Interfacer" S-100 I/O board \$189 unkit, \$249 assm, \$324 CSC*

Dual serial port with 2 full duplex parallel ports for RS-232 handshake. Crystal timebase, Baud rates to 19.2 Kbaud selectable for each port, much more. This no-excuses serial board does things the others only dream about.

NEW! 3P + S "Interfacer II" S-100 I/O board \$189 unkit, \$249 assm, \$324 CSC*

Incorporates 1 channel of serial I/O (with all the features of a port from the 2S "Interfacer"), along with 3 full duplex parallel ports with attention/enable/strobe bits for each parallel port and individual interrupts. The versatility of each port contributes to a very versatile, and extremely flexible, I/O board.

NEW! Memory Manager \$59 kit, \$85 assm, \$100 CSC*

Add bank select and extended addressing to older S-100 machines — boost memory capacity beyond 64K, up to 1/2 megabyte! Use our new extended addressing memories, or retrofit existing memories that have phantom or extra qualifier lines.

SEND FOR OUR HOT-OFF-THE-PRESSES CATALOGUE

CIRCLE 52 ON FREE INFORMATION CARD

... AND DON'T FORGET OUR MEMORIES!

All our memory boards are fully static, are zip along with 5 MHz systems, include a 1 year warranty, and are available in 3 different configurations. Here are just some selections from our roster of 14 Econoram™...

Name	Buss & notes	Unkit	Assm	CSC*
8K Econoram II A	S-100	\$149	\$179	\$239
32K Econoram X	S-100	\$529	\$649	\$789
24K Econoram XII	S-100 (1)	\$329	\$419	\$519
16K Econoram XIV	S-100 (2)	\$289	\$349	\$448
16K Econoram XV-16	Heath HB (3)	\$329	\$395	n/a
32K Econoram XV-32	Heath HB (3)	\$599	\$729	n/a

Notes
(1) Bank select board — 2 independent banks addressable on 8K boundaries.
(2) Extended addressing (24 address lines).
(3) Bank select option for implementing memory systems greater than 64K.

* CSC boards are qualified under our high-reliability Certified System component program (200 hour burn-in, replacement in event of failure within 1 year of invoice date)

** Econoram is a trademark of Godbout Electronics.

It's time for a holiday special...

The MA1003 is a superior clock module, with built-in timebase, that needs no introduction. Put it in our case (designed specifically for this module), and you've got a real winner. The price? \$19.95 for both clock and case — while they last.

GODBOUT

GODBOUT ELECTRONICS
Bldg. 725, Oakland Airport, CA 94614

TERMS: Cal res add tax. Allow 5% for shipping, excess refunded. VISA/Mastercharge* call our 24 hour order desk at (415) 562-0636. COD OK with street address for UPS. Prices good through cover month of magazine.

SEASON'S GREETINGS!

SEND FOR OUR FREE FLYER THIS MONTH'S SPECIALS

ASCII KEYBOARD

\$9.88

Keyboard Contains 82 keys (minus caps), Hex board, 74XX and CMOS chips, and a complete array of driver transistors.

Cat. No. X-1341 Wt. 3 lbs.



FLOPPY DISC CONTROLLER BOARD

\$28.88

Boards contain 86 I.C.s. and as many .01 glass or disk decoupling caps. All boards are in excellent condition. Ready to go, with gold plated sockets and connectors.

Cat. No. 1000 Wt. 1 lb.



QUAD "JOYSTICK" POTENTIOMETER

\$4.49

Each assembly contains four miniature pots. Pots are 100K ohms.

Cat. No. X-1440 Wt. 5 oz.



TERMS: Add Postage MINIMUM ORDER: \$10.00

Mastercharge and Visa accepted

P.O. Box 2361R
Woburn, MA 01888
TEK-EL Corp.



NEW RETAIL STORE

27 GILL ST., WOBURN, MA 01801
Store & Warehouse open 9-5 Sat. 9-1
Tel. 617-935-7328

CIRCLE 45 ON FREE INFORMATION CARD

AUDIOVOX CB RECEIVER


IDEAL CHRISTMAS GIFT

\$9.95



The CBC-100 Converter uses your regular car radio and antenna to receive 23 citizens band channels. Micro in size, this unit utilizes 10 crystals, 10 transistors, 7 diodes, dual conversion superheterodyne with crystal filter and built-in noise limiter circuit. No FCC license required.

SOLID STATE DIGITAL AMPLIFIER

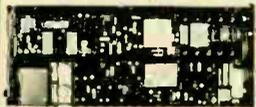

MADE FOR NASA

IDEAL FOR EXPERIMENTORS - Contains 69 transistors, 175 resistors, 45 diodes, 14 50K pots, 41 silver mica caps, 11 wirewound resistors, 4 mylar capacitors, 1 bridge rectifier, 6 coils, 1 relay, 1 24 volt power supply, & assorted switches, connectors, heat sinks, & other components.

HUNDREDS OF DOLLARS IN PRECISION PARTS \$12.95

POTTER & BLUMFIELD RELAY

4 PDT
24 VDC
3 AMPS
28 VDC RESISTANCE

\$1.69



CONTINENTAL SPECIALTIES CORP


EXP 300

PUT YOUR CIRCUIT IDEAS TO WORK... THE EASY WAY

EXPERIMENT SOLDERLESS BREADBOARD

LENGTH 6.0"

\$9.95

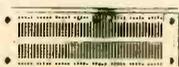

ITC Supermarket Of Electronics

GENERAL ELECTRIC BATTERY CHARGER

GREAT HOLIDAY ITEM
FRESH BATTERIES... WHEN YOU NEED THEM

REG. \$14.95

NOW \$12.95

With additional \$2.00 Factory Rebate Coupon GE batteries recharge up to 1000 times... call last for years! Keep a spare set on charge. charges AA, C, D, and 9 volt size GE batteries UL listed



2 WATT SOLID STATE AMPLIFIER

99¢

Pre-assembled on mini PC board. schematic included



NEW FROM WELLER

INSTANT HEAT HOBBY/SOLDERING GUN

INSTANTLY CUT THRU: Vinyl Tile, Plastic Cord, Thermoplastic Material

Smooth plastics as well as traditional soldering gun for metal or electrical connections

REG. \$16.25

HOLIDAY SPECIAL \$14.39



IRRADIATED POLYOLEFIN SHRINKABLE TUBING

PERFECT INSULATION COVER SHRINKS TO LESS THAN HALF OF SUPPLIED DIAMETER.

6 Ea. - 6" lengths to a bag

DIAMETER COLORS Please Specify
1/8" Red, Black, Clear, White
3/16"
1/4"

\$1.99 per bag of 6




CONTINENTAL SPECIALTIES CORP LP-2 MEMORY LOGIC PROBE

DETECTS PULSE WIDTHS DOWN TO 300 NSEC. REPETITION RATES UP TO 1.5 MHz

REVERSE & OVER-VOLTAGE PROTECTED

Detects pulse widths down to 300 NSEC. Repetition rates up to 1.5 MHz Reverse & over-voltage protected.

\$24.95

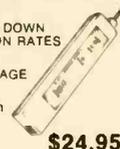

MINIATURE ALUMINUM RADIAL LEAD ELECTROLYTIC CAPACITORS

A must for PC work

	1-9	10-99	100-
22 mf/25V	12 ea	10 ea	.08 ea
33 mf/25V	12 ea	10 ea	.08 ea
100 mf/25V	17 ea	14 ea	10 ea
220 mf/25V	19 ea	16 ea	13 ea
1000 mf/25V	49 ea	41 ea	35 ea
10 mf/35V	12 ea	09 ea	.07 ea
10 mf/50V	12 ea	09 ea	.07 ea

Please specify value
Other values upon request

POTTER & BLUMFIELD RELAY

DPDT
6 VDC
600 MW
COIL RESISTANCE
60 OHMS



R50S-E2-Y2-6

MAY BE DRIVEN DIRECTLY FROM

- TTL PERIPHERAL DRIVER
- TTL BUFFER
- CMOS BUFFER
- HTL BUFFER
- CMOS PERIPHERAL DRIVER

\$1.49

6 DIGIT 24 VDC COUNTER

CONTINUOUS 2.71 WATTS

USE FOR: TAPE RECORDERS
PIN BALL MACHINES
MINI-COMPUTERS

REG. \$6.00

LOW \$1.99



1 1/2" h 1 3/4" w 2 1/4" d

RECTIFIER

MOST POPULAR
1000V at 2.5 Amp
SAME AS HEP 170

5 for \$1.00

100 for \$15.00

'AA' NICAD

FAST CHARGE
BRAND NEW

99¢

6 for \$5.50



ITC ELECTRONIC SUPERMARKET

2772 W. Olympic Blvd.
Los Angeles, CA 90006
(213) 388-0621

Happy Holidays

Minimum Order \$5.00. Please add \$2.00 postage and handling. California residents add 6% Sales Tax. VISA/ Master Charge: State number and expiration date. OEM and Institutional inquiries invited.

Radio Shack — Your No. 1 Parts Place™

Low Prices and New Items Every Day!

Low-Power Schottky ICs

Low As **49¢**
 • 100% Prime
 • Guaranteed Specs



Improved 5-volt logic devices use Schottky diode technology for minimum propagation delay and high speed at minimum power.

Type	Cat. No.	ONLY
74LS00	276-1900	.49
74LS02	276-1902	.59
74LS04	276-1904	.59
74LS08	276-1908	.49
74LS10	276-1910	.59
74LS13	276-1911	.99
74LS20	276-1912	.59
74LS27	276-1913	.69
74LS30	276-1914	.59
74LS32	276-1915	.69
74LS47	276-1916	1.29
74LS51	276-1917	.59
74LS73	276-1918	.69
74LS74	276-1919	.69
74LS75	276-1920	.99
74LS76	276-1921	.79
74LS85	276-1922	1.29
74LS90	276-1923	.99
74LS92	276-1924	.99
74LS93	276-1925	.99
74LS123	276-1926	1.19
74LS132	276-1927	.99
74LS151	276-1929	.99
74LS157	276-1930	1.19
74LS161	276-1931	1.49
74LS164	276-1932	1.49
74LS175	276-1934	1.19
74LS192	276-1935	1.49
74LS193	276-1936	1.49
74LS194	276-1937	1.49
74LS196	276-1938	1.59
74LS367	276-1939	1.19
74LS368	276-1939	1.19
74LS373	276-1943	2.39
74LS374	276-1944	2.39

4000-Series CMOS ICs

Type	Cat. No.	EACH
4001	276-2401	.69
4011	276-2411	.69
4012	276-2412	.79
4013	276-2413	.99
4017	276-2417	1.69
4020	276-2420	1.69
4021	276-2421	1.69
4023	276-2423	.69
4027	276-2427	.99
4028	276-2428	1.29
4046	276-2446	1.89
4511	276-2447	1.69
4049	276-2449	.79
4050	276-2450	.79
4051	276-2451	1.49
4066	276-2466	1.39
4070	276-2470	.79
4518	276-2490	1.49
4543	276-2491	1.99

All Prime from Major Semiconductor Manufacturers. Specs and Pin Out Diagram Included with Each Device.

MC14553 3-Digit BCD Counter IC **2.99**

CMOS chip replaces over 8 separate ICs in a digital display circuit. Input pulse shaping. Master reset pin. 16-pin DIP. 276-2498 2.99

RAM Memory ICs **2.49**

Low As
 2102 1024 x 1 Array. Low-cost static memory chip. 16-pin DIP. Buy 8 and save! 276-2501 2.49 Ea. or 8/14.95
 2114L 1024 x 4 Array. NMOS static RAM. 18-pin DIP. 276-2504 10.99

NEW! Silicon Solar Cells



Convert light to electrical power. All deliver 0.45V at rated current. Use several in series/parallel for higher voltages or current.
 276-122. 1/2 3" cell. Rated 500 mA 5.99
 276-123. Full 3" cell. Rated 1 amp 8.99

Hall-Effect Sensors




1.98 Pkg. of 3
Open-Collector Output
 Detects magnetic fields electronically. 750 gauss "on" threshold. Constant amplitude independent of frequency. Similar to type ULN 3006. Ideal for tachs, position sensing, pulse counting. 5 to 16V supply. TO-92 case. With data. 276-1646 Pkg. of 3/1.98

Unique LEDs



A Tri-Color. Displays red, green, yellow. Uniform light output of 0.6 mcd. Forward voltage: 2.2VDC. Max. current: 25mA. T1-¼ case style. 276-035 1.39
B Red Flasher. Operates directly from 5VDC power source. Pulse rate: 3 Hz. Max. current: 20 mA at 5VDC. 276-036 1.29

NEW! Switches

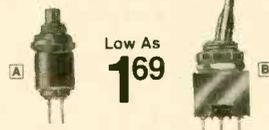

A Submini Push Switches. One red, one black. SPST momentary contacts rated 0.5A, 125VAC. Normally open. 275-1571 Pkg. 2/1.69
B Compact Lever Switches. 6A at 125VAC. SPST. 275-257 2.49
 DPDT. 275-259 2.99

BIFET Op Amps




Feature very high input impedance, low noise. Fast 13V/µs slew rate is ideal for low TIM distortion audio amplifiers. Internally compensated. Up to ±18V supply.
A LF 353N. Dual BIFET Op amp. 8-pin DIP. 276-1715 1.89
B TL 084C. Quad BIFET Op amp. 14-pin DIP. 276-1714 2.99

NEW! BNC Connectors




A Type 1094 Female BNC. Mounts in single 3/16" hole. 278-105 1.49
B Type UG-88 Male BNC. No soldering! Screws onto standard coax cable. Plated finish. For RG-58/U Cable. 278-103 2.19
 For RG-59/U Cable. 278-104 2.19

SN-76477 "Music Synthesizer" IC

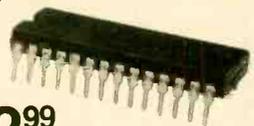

2.99
 Creates almost any type of sound! High level op amp output. Includes 2 VCOs, low frequency osc., noise generator, filter, 2 mixers, timing logic. 28-pin DIP. With data. 276-1765 2.99

AC and DC Relays

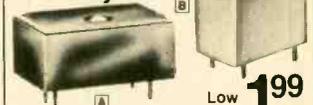

A SPST Solid State AC Relay. Handles 24 to 280VAC at up to 1.5A. TTL compatible 5VDC control input. 1500V RMS isolation. 275-236 1.99
B 12VDC SPDT. Silver-plated contacts. 1A at 125VAC. 275-231 2.49

Manufacturer's Data Books




Low As **2.95**
Need Info? — Find it at Radio Shack!
A Motorola RF Data Manual. Power and small-signal RF transistors, hybrid amplifier modules, more. 62-1380 4.95
B Motorola Low-Power Schottky TTL. Data and diagrams plus selection guide for choosing best device. 62-1381 3.95
C Linear Applications, Vol. 2. Latest data, diagrams, applications briefs and articles. Indexed. 62-1374 2.95
D CMOS Integrated Circuits. Covers 74C, CD4000-series with complete data, diagrams. Cross referenced. 62-1375 3.95
E Memory Data Book. Complete info on MOS and bipolar memory components, support circuits. 62-1376 3.95

4" Cooling Fan

12.95

Super Quiet Operation

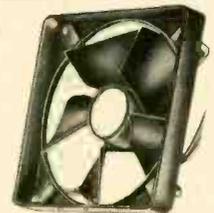

Ideal for cooling power supplies, microcomputers, hi-fi and Ham gear. Delivers up to 70 CFM. Diecast venturi. U.L. recognized motor. For 120VAC, 60 Hz. 273-241 12.95

12/24-Hr. LCD Clock Module

19.95



24-Hour Alarm Shows Time/Day/Date
Actual Size
 Complete clock module — just add switches and battery! 0.25" LCD display has built-in backlight, alarm set, PM and snooze indicators. Operates up to a year on single 1.5V battery. Accuracy: ±13 seconds per month. 277-1005 19.95

WHY WAIT FOR MAIL ORDER DELIVERY?
 IN STOCK NOW AT OUR STORE NEAR YOU!

Radio Shack®

A DIVISION OF TANDY CORPORATION • FORT WORTH, TEXAS 76102
 OVER 7000 LOCATIONS IN 40 COUNTRIES

CIRCLE 8 ON FREE INFORMATION CARD

LOW, LOW DISCOUNT PRICES

POPULAR COMPONENTS INC.

OFFERS YOU:

- HARD TO GET COMPONENTS
- MONEY SAVING DISCOUNT PRICES
- TOP SELECTION OF FIRST QUALITY POPULAR COMPONENTS
- ALL COMPONENTS GUARANTEED TO BE FACTORY PERFECT (MONEY BACK GUARANTEE)

UARTS	
AY-5-1013A	\$4.20
TR1602B	3.90
AY-3-1015D	5.20
AY-3-1014A	6.75
TELECOMMUNICATIONS	
AY-5-9100	Push Button Telephone Dialer Circuit 13.95
AY-5-9200	Repertory Dialer 13.95
AY-5-9500	C-MOS Generator 4.25
GENERATOR/ENCODERS	
RD-3-2513	Character Generator (upper or lower case) 6.50
AY-5-2376	Keyboard Encoder 12.10
AY-5-3600	Keyboard Encoder 12.95
8080/8085 SUPPORT CHIPS	
UPD8080AFC	8-Bit N-Channel Microprocessor 5.35
UPD8085AC	Single Chip 8-Bit N-Channel Microprocessor 12.75
UPD8155C	2048 Bit Static MOS RAM with I/O Ports & Timer 18.95
UPB8212C	8-Bit I/O Port 2.40
UPB8214C	Priority Interrupt Controller 3.90
UPB8216C	4-Bit Parallel Bidirectional Bus Driver 2.40
UPB8224C	Clock Generator & Driver for 8080A Processor 2.55
UPB8226C	4-Bit Parallel Bidirectional Bus Driver 3.35
UPB8228C	8080A System Controller & Bus Driver 3.95
UPB8238C	8080A System Controller & Bus Driver 3.95
UPD8251C	Prog. Communication Interface 5.40
UPD8253C	Prog. Interval Timer 13.95
UPD8255C	Prog. Peripheral Interface 5.40
UPD8257C	Prog. DMA Controller 16.95
UPD8259C	Prog. Interrupt Controller 14.90
MICROPROCESSOR CHIPS	
UPD780C(1Z80)	8-Bit N-Channel Microprocessor completely Z80 compatible 13.50
UPD780C(1Z80A)	8-Bit N-Channel Microprocessor completely Z80 compatible (4MHz) 15.95
CONTROLLER CHIPS	
UP0765	Single/Dense Density Floppy Disk Controller 59.95
FD1771B	Single Density Floppy Disk Controller 59.95
FD1791B	Dual Density Floppy Disk Controller (IBM compatible) 59.95
CR15027	CRT Controller 39.95
UPD372D	Floppy Disk Controller 39.95
RAMS	
UPD2102ALC-4	1024 Bit Fully Decoded Static MOS RAM (low power) 2.60
UPD2101ALC-4	1024 Bit (256x4) Static MOS RAM with separate I/O (low power) 2.75
UPD2111ALC-4	1024 Bit (256x4) Static MOS RAM with common I/O & output disable (low power) 3.50
2114UCB	4K Static RAM 450ns 6.95
UPD5101C-E	1024 Bit (256x4) Static CMOS RAM 4.35
UPD4114C	4K Dynamic RAM 4.95
UPD416C	16K (16384x1) Bit Dynamic MDS RAM 12.75
BAUD RATE GENERATORS	
COM5016	Dual Baud Rate Generator 15.50
COM5036	Dual Baud Rate Generator 15.50
BR1941L	Dual Baud Rate Generator 9.80
SOUND GENERATOR	
SN75477	Complex Sound Generator 3.65
ASTRO	
COM1671	Asynchronous/Synchronous Receiver-Transmitter 24.50
LINEAR	
SG3524N/J	Switching Regulator Converter 5.40

TO ORDER: Specify part number, name, price & quantity. Check or money order must accompany order. Add \$1.75 for postage & handling. New York State residents add 7% sales tax. Foreign Customers: Payment must be in U.S. dollars by international postal money order or cashier's check. Add 20% for shipping & handling.

FREE WITH EACH ORDER. WE WELCOME INQUIRIES FROM MANUFACTURERS, DISTRIBUTORS, & INSTITUTIONS. NO C.O.D., MINIMUM ORDER \$10.00.

(PRICES GOOD THRU DECEMBER 15, 1979)

Order Today from:

POPULAR COMPONENTS INC.
DEPT. RE 1279
P.O. BOX 866
MELVILLE, N.Y. 11747

CIRCLE 4 ON FREE INFORMATION CARD

ADVERTISING INDEX

RADIO-ELECTRONICS does not assume any responsibility for errors that may appear in the index below.

Free Information Number Page

—	AMC Sales	110
60	AP Products, Inc.	33
56	Aaron-Gavin Instruments	97
5	Active Electronics	116
—	Advance Electronics	25,34,69,72-73
20	Advanced Computer Products	108
6	All Electronics	110
59	Amelect, Inc.	35
30	American Antenna	Cov. 4
—	Apollo	100
—	Asante Enterprise Ltd.	98
66	B & K Dynascan Corp.	77
53	Babylon Electronics	110
—	Karel Barta	104
29	Beckman	80
67	Blacksburg Group	96
—	Bullet Electronics	101
—	Burdex Security	110
44	C F R Associates	99
—	Camelot Direct	13
—	Chaney Electronics	104
—	C I E—Cleveland Institute of Electronics	18-21
—	Command Productions	104
54	Concord-Computer Components	114
9	Continental Specialties	Cov. 2
23	The Cooper Group	93
—	Dage Scientific	100
25	Delta Electronics	100
64	Deltronics	110
15	Digi-Key	109
—	D R C—Digital Research Corporation	114
47	E I C O	93
50	Enterprise Development Corp.	84
—	Fair Radio Sales	104
33	Fluke	6-7
16	Fordham Radio Supply	90,115
21 & 22	Formula International	102-103
36	Fuji-Svea	105
—	Golden Enterprises	99
52	Godbout Electronics	118
55	Grantham College of Engineering	93
100	Heath	4,26-27,87-89 & Cov. 3
63	Hickok Electrical Instruments	79
39	Hitachi-Denshi	2
35	Hobby World	106
17	ITC—Electronic Supermarket	118
—	Information Unlimited	110
19	International Crystal Mfg. Co.	91
—	J S & A	1
57 & 58	Jameco Electronics	112-113
24	Kester Solder	86
—	Lakeside Industries	100
42	MFE Company	98
7	Meshna	106

—	National Radio Institute (NRI)—Div. of McGraw Hill	8-11
—	National Technical Schools (NTS)	28-31
48,49	Netronics	76,82
40,41	O.K. Machine & Tool	22,75
—	Olson	104
27	Optoelectronics	17
12	PAIA	94
65	PTS Electronics	86
62	Pac-Com	92
37	Panasonic	38
2	Panavise	81
26	Poly Paks	107
10	Pomona Electronics	85
4	Popular Components	120
11	Quest	117
8	Radio Shack	119
43	Ramsey Electronics	111
31	Ripley Co., Inc.	35
18	Rye Industries	97
—	Sabtronics	36-37
32	Schober Organ	15
61	Shure	32
46	Solid State Sales	106
51	Southwest Technical Products	92
—	Spacecoast Research	104
—	Speakerlab	100
—	Surplus Center	104
3	Tab Books	94
45	Tek-EI Corp.	118
—	Texas Instruments	84
13	Tri-Star	110
—	V.I.Z. Mfg.	96
34	Vector	95
28	Wersi Electronics	81
38	Weston Instruments	23
14	Zemco	24

MOVING?

Don't miss a single copy of **Radio-Electronics**. Give us:

Six weeks' notice

Your old address and zip code

Your new address and zip code

ATTACH LABEL HERE

name (please print)


address

city state zip code

Mail to: Radio-Electronics
SUBSCRIPTION DEPT., P.O. BOX 2520,
BOULDER, COLO. 80322

no loose ends

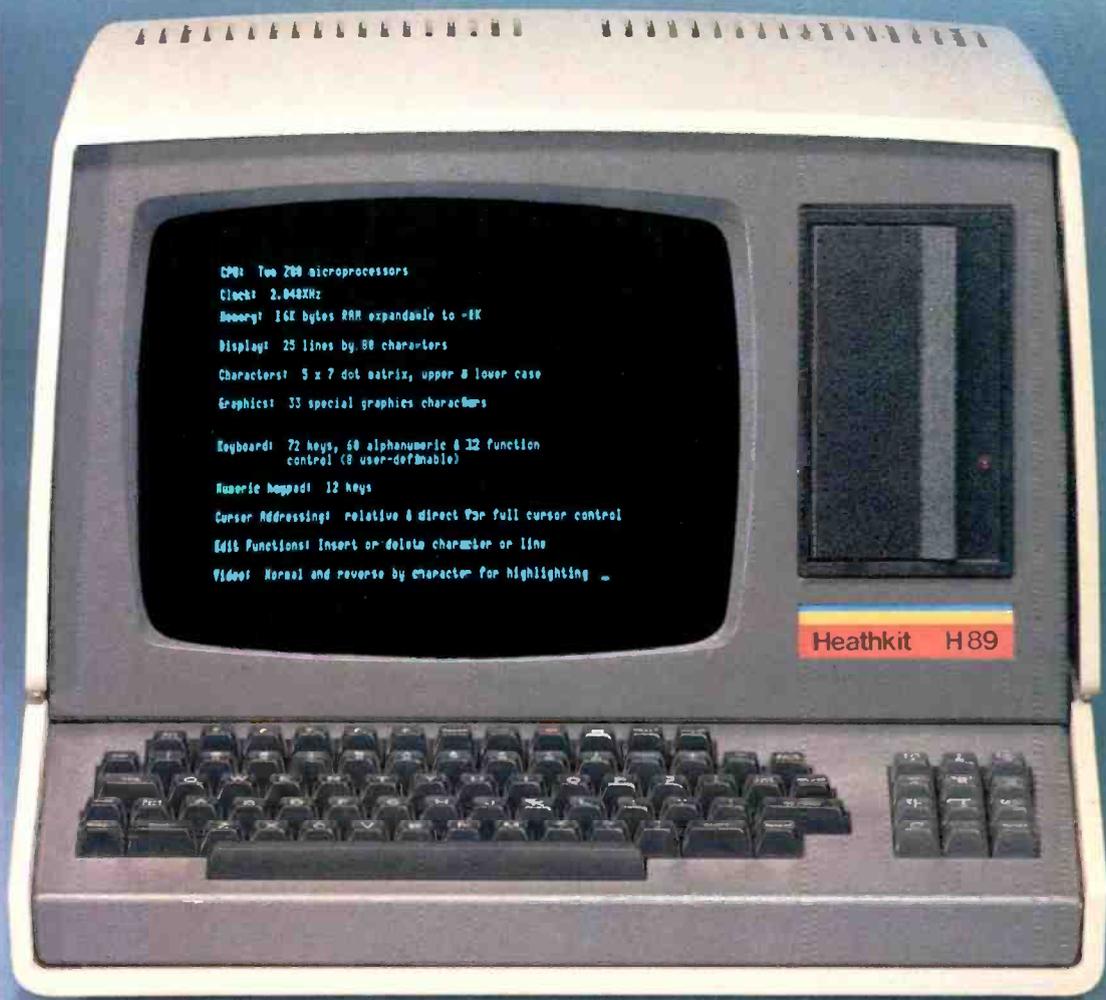All-In-One: computer, floppy, I/O, 16K RAM. \$1595*



New Heathkit® H89 All-In-One Computer

Heath takes the risk out of selecting a balanced computer system. Now, video terminal, floppy, keyboard and 8-bit computer are brought together in one self-contained, compact unit. Nothing hangs out.

Two Z80's

The personal computer has never been simpler. Or smarter. Two Z80 microprocessors mean terminal never shares power with computer, as do most desk-top units. So this terminal is capable of a multitude of high-speed functions, all controllable by keyboard or software.

*\$1195 without floppy. Mail order kit price, F.O.B. Benton Harbor, MI. Also available at Heathkit Electronic Centers at slightly higher prices. Prices subject to change without notice.

102K bytes storage

Built-in floppy disk system gives you fast access to programs and data. Each 5¼-inch diskette has more than 102K bytes of storage area, enough to hold entire files. The All-In-One comes with 16K RAM, expandable to 48K.

Hundreds of uses at home or work

The All-In-One Computer runs programs written in MICROSOFT™ BASIC and ASSEMBLER Languages. And it accepts all current software written for the popular Heathkit HE computer. You can choose from scores of practical programs for home and business.

Learn by building

What better way to learn about computers than to build one yourself? The All-In-One is available in easy-to-build kit form, as well as completely assembled. Like all Heath electronic kits, it comes to you with its own easy-to-follow assembly manual and a nationwide network of service centers to assure smooth sailing.

FREE CATALOG



For complete details on the Heathkit H89 All-In-One Computer and nearly 400 other electronic kits for your home, work or pleasure, send today for the latest Heathkit Catalog of values.

Heathkit®

HEATH COMPANY, DEPT. 020-600, BENTON HARBOR, MI 49022

CP-165

CIRCLE 100 ON FREE INFORMATION CARD

www.americanradiohistory.com

In one year our **K40**™ antenna has become the largest selling CB antenna in the world!

1. It's the most expensive ...

2. It's made better...

3. It's proven best!
...Here's what the leading CB publications said.

\$42.50

suggested retail

And when you pay more, you expect more!

MORE PERFORMANCE:

The K40 is guaranteed to transmit further or receive clearer than any antenna it replaces. We know it will. We've tested it with 771 CB'ers just like you for one year.

MORE FLEXIBILITY:

You can fit your K40 to any mounting surface. It will fit any vehicle you'll ever own! That includes choppers, dune buggies, gutters, mirror mounts, luggage racks, trunks, hatchbacks, through roofs, semis, pick ups and RV's.

MORE QUALITY:

It's not imported. It's not made in Taiwan, Korea or Japan. It's American made in an American town. It's made with better materials that cost more and by professional people we pay more. And we designed it right here in the U.S.A.

*Including optional mounts at extra cost.

... This Antenna is so DYNAMITE you receive a ...

DOUBLE GUARANTEE

GUARANTEE I: The K40 will transmit farther and receive more clearly than the antenna it replaces or the customer will receive a prompt and full refund from the Registered K40 Dealer who installed and tuned it.

GUARANTEE II: Unconditionally guaranteed for 12 months. Guaranteed against cracking, chipping or rusting. Guaranteed against mechanical failure. Guaranteed against electrical failure. Guaranteed against accidental breakage. No exclusions. No gimmicks. For a full 12 months.



CB TIMES: "... it's not often that a product bursts onto the market scene, dominates and improves CB'ing for everyone. American Antenna and the K40 are doing it—repeated tests showed the K40 could out-perform the major competitive brands."

RADIO ELECTRONICS: "The results of our tests showed that, in three different positions of the monitoring receiver, the model K40 equaled or out-performed the competitive antenna. Apparently, American Antenna's advertising is not merely Madison Avenue showmanship."

PERSONAL COMMUNICATIONS: "... an impressive 95% of the trials, the K40 out-performed the existing mobile antennas. We had to try one for ourselves. ... in every case, the K40 either equaled or out-performed its competitor."

"No ifs, ands, or buts! The K40 Antenna from American Antenna would have to be just about the best antenna around."

CB MAGAZINE: "Introduced in October, 1977, the K40 quickly became the top seller and in mid 1978, became the number one selling antenna in the nation."

...Here's what CB'ers all across the country said.

ANTENNA SPECIALISTS: "... truck driver and CB'er for 10 years ... 50% further than my M410 'Big Momma'."

—J.H. Collett, 207 McFee, Bastrop, LA

AVANTI: "I'm an electronic technician with a Second Class FCC license ... I was able to transmit 70% further and tune the SWR 75% lower than my Avanti."

—H.R. Castro, VRB, Monserrante D-67, Salinas, Puerto Rico

PAL: "... 20% better in transmission and reception than my 5/8 wave Pal Firestik."

—John A. Blum, Box 446, Zellenople, PA

SHAKESPEARE: "... I've been a CB'er for three years and the K40 is the best I've ever had. Better in reception and transmission than my Shakespeare."

—H. Bachert, Jr., 15 King Rd., Park Ridge, NJ

HUSTLER: "Compared to my Hustler XBLT-4, the K40 can consistently transmit 40% further and the reception was better. The K40 is the perfect way to complete a CB system."

—Jerome R. Brown, 7800 S. Linder, Burbank, IL



(SPECIAL NOTE) IF YOU'RE A BEGINNER:

Our K40 Dealers will be happy to sell you any of the older style and less expensive antennas that are great bargains for any beginning CB'er.

AMERICAN ANTENNA
ELGIN, IL 60120
© COPYRIGHT AMERICAN ANTENNA 1979

K40
POWER!

... Sold exclusively by 3500 American K40 Dealers throughout the U.S. & Canada.

CIRCLE 30 ON FREE INFORMATION CARD

www.americanradiohistory.com