

# Radio- Electronics

**BUILD THE PICTURE PHONE  
ADAPTER AND SEND VIDEO  
OVER YOUR TELEPHONE**

\$1.25 SEPT. 1982

THE MAGAZINE FOR NEW IDEAS IN ELECTRONICS

**Build this  
HEART RATE MONITOR**

**The ins and outs of  
BUYING MAILORDER PARTS**

**How to  
BIAS TRANSISTORS CORRECTLY  
when designing analog circuits**

**Build a  
STEREO IMAGE EXPANDER  
for concert hall effects**

**Troubleshoot and repair  
MINI-CASSETTE RECORDERS**

tep



390736 DHM 09976093 6V A NOV82  
MR ROBERT DAHM 09#22  
997 GRAND AV  
AURORA IL 60505



# If we only tell you the features you'll never guess the price.

Leader has 6 great oscilloscopes from 15 to 35 MHz, with more features and the lowest list prices ever.

We've designed brand new low and medium bandwidth oscilloscopes and built in many features you may never have seen in similar units. Then we priced them well below the units they replace. Surprising? Not any more. It's exactly the kind of innovative technology and superb quality you've come to expect from Leader.

**Ever see trigger holdoff on a 20 MHz scope?  
Or 500  $\mu$ V sensitivity?**

Now Leader gives you these and so much more. Check it out:

## **LBO-524/LBO-524L: 35 MHz**


- CALIBRATED DUAL TIME BASE
- 500  $\mu$ V SENSITIVITY
- 7 kV PDA 6" RECTANGULAR CRT
- INTERNAL GRATICULE
- DELAYED SWEEP TRIGGERED FUNCTION
- VARIABLE SWEEP HOLDOFF
- ALTERNATE CHANNEL TRIGGERING
- AUTO FOCUS
- CHANNEL 1 OUTPUT

## **LBO-523: 35 MHz**

- 7 kV PDA 6" RECTANGULAR CRT
- INTERNAL GRATICULE
- 500  $\mu$ V SENSITIVITY
- VARIABLE SWEEP HOLDOFF
- ALTERNATE CHANNEL TRIGGERING
- AUTO FOCUS
- CHANNEL 1 OUTPUT

CIRCLE 4 FOR PRODUCT DEMONSTRATION

CIRCLE 5 FOR PRODUCT INFORMATION

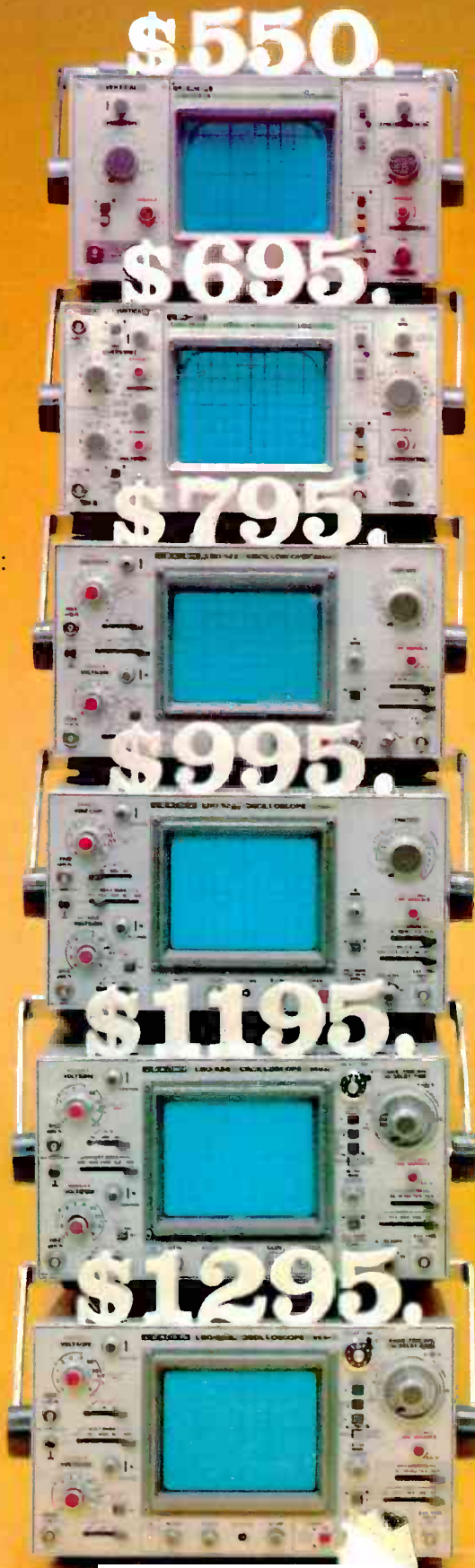

## **LBO-522: 20 MHz**

- 500  $\mu$ V SENSITIVITY
- 6" RECTANGULAR CRT
- INTERNAL GRATICULE
- ALTERNATE CHANNEL TRIGGERING
- VARIABLE SWEEP HOLDOFF
- AUTO FOCUS
- CHANNEL 1 OUTPUT

## **LBO-514A/LBO-513A: 15 MHz**

- 1 mV SENSITIVITY
- 0.5  $\mu$ S SWEEP SPEED
- X-Y MODE CAPABILITY
- LBO-514A AVAILABLE WITH 6 kV ACCELERATING POTENTIAL

Our two-year warranty (even on the CRT) is backed by factory service depots on both coasts. Evaluation units are available to qualified customers.

**Call toll-free  
(800) 645-5104**

Contact us today for an evaluation unit, catalog showing over 60 Leader test instruments, the name of your nearest "Select" distributor and more information.

For professionals  
who know  
the  
difference.

**LEADER**  
Instruments Corporation

330 Oser Avenue  
Hauppauge, N.Y. 11788 (516) 231-6900  
Regional Offices:  
Chicago Los Angeles, Dallas

Introducing incredible tuning accuracy at an incredibly affordable price: The Command Series RF-3100 31-band AM/FM/SW receiver.\* No other shortwave receiver brings in PLL quartz synthesized tuning and all-band digital readout for as low a price.† The tuner tracks and "locks" onto your signal, and the 5-digit display shows exactly what frequency you're on.

There are other ways the RF-3100 commands the airways: It can travel the full length of the shortwave band (that's 1.6 to 30 MHz). It eliminates interference when stations overlap by narrowing the broadcast band. It improves reception in strong signal areas with RF Gain Control. And the RF-3100 catches Morse

communications accurately with BFO Pitch Control. Want to bring in your favorite programs without lifting a finger? Then consider the Panasonic RF-6300 8-band AM/FM/SW receiver (1.6 to 30 MHz) has microcomputerized preset pushbutton tuning, for programming 12 different broadcasts, or the same broadcast 12 days in a row. Automatically. It even has a quartz alarm clock that turns the radio on and off to play your favorite broadcasts.



The Command Series RF-3100 and RF-6300. Two more ways to roam the globe at the speed of sound. Only from Panasonic.

\*Shortwave reception will vary with antenna, weather conditions, operator's geographic location and other factors. An outside antenna may be required for maximum shortwave reception.

†Based on a comparison of suggested retail prices.

## This Panasonic Command Series™ shortwave receiver brings the state of the art closer to the state of your pocketbook.



With PLL Quartz Synthesized Tuning and Digital Frequency Readout.

**Panasonic**  
just slightly ahead of our time

# Why use their flexible discs:

BASF, Control Data, Dysan, IBM, Kybe, Maxell, Nashua, Scotch, Syncom, Verbatim or Wabash  
when you could be using

# MEMOREX

## high quality error free discs?

| Product Description                          | Part # | CE quant.<br>100 price<br>per disc (\$) |
|--|--------|---|
| 8" SSSD IBM Compatible (128 B/S, 26 Sectors) | 3062   | 2.09                                    |
| 8" SSSD Shugart Compatible, 32 Hard Sector   | 3015   | 2.09                                    |
| 8" SSSD CPT 8000 Compatible, Soft Sector     | 3045   | 2.99                                    |
| 8" SSDD IBM Compatible (128 B/S, 26 Sectors) | 3090   | 2.74                                    |
| 8" DSDD Soft Sector (Unformatted)            | 3102   | 3.34                                    |
| 8" DSDD Soft Sector (128 B/S, 26 Sectors)    | 3115   | 3.34                                    |
| 8" DSDD Soft Sector (256 B/S, 26 Sectors)    | 3103   | 3.34                                    |
| 8" DSDD Soft Sector (512 B/S, 15 Sectors)    | 3114   | 3.34                                    |
| 8" DSDD Soft Sector (1024 B/S, 8 Sectors)    | 3104   | 3.34                                    |
| 5 1/4" SSDD Soft Sector w/Hub Ring           | 3481   | 2.34                                    |
| 5 1/4" SSDD 10 Hard Sector w/Hub Ring        | 3483   | 2.34                                    |
| 5 1/4" SSDD 16 Hard Sector w/Hub Ring        | 3485   | 2.34                                    |
| 5 1/4" DSDD Soft Sector w/Hub Ring           | 3491   | 3.09                                    |
| 5 1/4" DSDD 10 Hard Sector w/Hub Ring        | 3493   | 3.09                                    |
| 5 1/4" DSDD 16 Hard Sector w/Hub Ring        | 3495   | 3.09                                    |
| 5 1/4" SSDD Soft Sector w/Hub Ring (96 TPI)  | 3504   | 2.99                                    |
| 5 1/4" DSDD Soft Sector w/Hub Ring (96 TPI)  | 3501   | 3.99                                    |

SSSD = Single Sided Single Density; SSDD = Single Sided Double Density  
DSDD = Double Sided Double Density; TPI = Tracks per inch

### Memorex Flexible Discs... The Ultimate in Memory Excellence

**Free Memorex Mini-Disc Offer - Save 10%**  
Every carton of 10 Memorex 5 1/4 inch mini-discs sold by Communications Electronics, now has a coupon good for a free Memorex mini-disc. For every case of 100 Memorex mini-discs you buy from CE, you'll get 10 free mini-discs directly from Memorex. There is no limit to the number of discs you can purchase on this special offer. This offer is good only in the U.S.A. and ends on December 31, 1982.

**Quality**  
Memorex means quality products that you can depend on. Quality control at Memorex means starting with the best materials available and continual surveillance throughout the entire manufacturing process. The benefit of Memorex's years of experience in magnetic media production, resulting, for instance, in proprietary coating formulations. The most sophisticated testing procedures you'll find anywhere in the business.

**100 Percent Error Free**  
Each and every Memorex Flexible Disc is certified to be 100 percent error free. Each track of each flexible disc is tested, individually, to Memorex's stringent standards of excellence. They test signal amplitude, resolution, low-pass modulation, overwrite, missing pulse error and extra pulse error. Rigid quality audits are built into every step of the manufacturing process and stringent testing result in a standard of excellence that assures you, our customer, of a quality product designed for increased reliability and consistent top performance.

**Customer-Oriented Packaging**  
The desk-top box containing ten discs is convenient for filing and storage. Both box labels and jacket labels provide full information on compatibility, density, sectoring, and record length. Envelopes with multi-language care and handling instructions and color-coded removable labels are included. A write-protect feature is available to provide data security.

**Full One Year Warranty - Your Assurance of Quality**  
Memorex Flexible Discs will be replaced free of charge by Memorex if they are found to be defective in materials or workmanship within one year of the date of purchase. Other than replacement, Memorex will not be responsible for any damages or losses (including consequential damages) caused by the use of Memorex Flexible Discs.

#### Quantity Discounts Available

Memorex Flexible Discs are packed 10 discs to a carton and 10 cartons to a case. Please order only in increments of 100 units for quantity 100 pricing. We are also willing to accommodate your smaller orders. Quantities less than 100 units are available in increments of 10 units at a 10% surcharge. Quantity discounts are also available. Order 500 or more discs at the same time and deduct 1%; 1,000 or more saves you 2%; 2,000 or more saves you 3%; 5,000 or more saves you 4%; 10,000 or more saves you 5%; 25,000 or more saves you 6%; 50,000 or more saves you 7% and 100,000 or more discs earns you an 8% discount off our super low quantity 100 price. Almost all Memorex Flexible Discs are immediately available from CE. Our warehouse facilities are equipped to help us get you the quality product you need, when you need it. If you need further assistance to find the flexible disc that's right for you, call the Memorex compatibility hotline. Dial toll-free 800-538-8080 and ask for the flexible disc hotline extension 0997. In California dial 800-672-3525 extension 0997. Outside the U.S.A. dial 408-987-0997.

#### Buy with Confidence

To get the fastest delivery from CE of your Memorex Flexible Discs, send or phone your order directly to our Computer Products Division. Be sure to calculate your price using the CE prices in this ad. Michigan residents please add 4% sales tax. Written purchase orders are accepted from approved government agencies and most well rated firms at a 30% surcharge for net 30 billing. All sales are subject to availability, acceptance and verification. All sales are final. Prices, terms and specifications are subject to change without notice. Out of stock items will be placed on backorder automatically unless CE is instructed differently. Minimum prepaid order \$50.00. Minimum purchase order \$200.00. International orders are invited with a \$20.00 surcharge for special handling in addition to shipping charges. All shipments are F.O.B. Ann Arbor, Michigan. No COD's please. Non-certified and foreign checks require bank clearance.

Mail orders to: Communications Electronics, Box 1002, Ann Arbor, Michigan 48106 U.S.A. Add \$8.00 per case or partial-case of 100 8-inch discs or \$6.00 per case or partial case of 100 5 1/4-inch mini-discs for U.P.S. ground shipping and handling in the continental U.S.A. If you have a MasterCard or Visa card, you may call anytime and place a credit card order. Order toll-free in the U.S. Dial 800-521-4414. If you are outside the U.S. or in Michigan, dial 313-994-4444. If you are high quality, error free Memorex discs today.

Copyright © 1982 Communications Electronics™


Ad #051782

## Free disc offer Save 10%



Order Toll-Free!  
(800) 521-4414

In Michigan (313) 994-4444

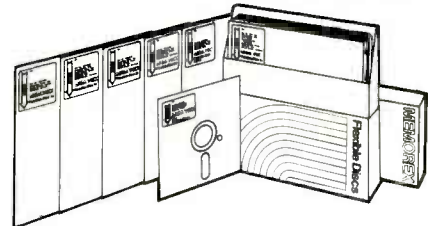

For Data Reliability—Memorex Flexible Discs

# COMMUNICATIONS ELECTRONICS™

Computer Products Division

854 Phoenix □ Box 1002 □ Ann Arbor, Michigan 48106 U.S.A.  
Call TOLL-FREE (800) 521-4414 or outside U.S.A. (313) 994-4444

CIRCLE 16 ON FREE INFORMATION CARD

www.americanradiohistory.com

**SPECIAL FEATURE**

- 53 **BUYING MAIL-ORDER COMPONENTS**  
Mail-order is sometimes the only way to obtain the components you need. Here are some tips you should know and pitfalls you should avoid. **Karl T. Thurber, Jr., W8FX**

**BUILD THIS**

- 45 **HEART-RATE MONITOR**  
Know the state of your health and fitness. This project displays your heart rate in beats-per-minute by simply attaching an opto-electronic sensor to your finger. **Robert Grossblatt**
- 49 **PICTURE PHONE**  
Part 2—Adapter sends video pictures over the telephone line to a remote location. **Josef Bernard**
- 63 **STEREO IMAGE EXPANDER**  
Part 2—Hi-fi adapter adds an extra dimension to your recorded music. **Joel Cohen**

**TECHNOLOGY**

- 4 **VIDEO ELECTRONICS**  
Tomorrow's news and technology in this quickly changing industry. **David Lachenbruch**
- 40 **SATELLITE TV NEWS**  
The latest happenings in communications technology. **Gary H. Arlen**
- 71 **ALL ABOUT PULSE GENERATORS**  
How to use a pulse generator to test an analog circuit. **Charles Gilmore**
- 84 **STATE-OF-SOLID-STATE**  
DC voltage-controlled switches. **Robert F. Scott**

**CIRCUITS AND COMPONENTS**

- 42 **NEW IDEA**  
Electronic thermometer.
- 59 **HOW TO DESIGN ANALOG CIRCUITS**  
Proper transistor operation requires proper biasing. Learn about biasing circuits and how to design them. **Mannie Horowitz**
- 74 **HOBBY CORNER**  
Learning about microprocessors. **Earl "Doc" Savage, K4SDS**

**VIDEO**

- 92 **SERVICE CLINIC**  
Color-burst reference oscillators. **Jack Darr**
- 92 **SERVICE QUESTIONS**  
Radio-Electronics' Service Editor solves technicians' problems.

**AUDIO**

- 66 **REPAIRING PORTABLE CASSETTE RECORDERS**  
How to troubleshoot and repair these popular recorders. **Homer L. Davidson**

**RADIO**

- 78 **COMMUNICATIONS CORNER**  
Touch-Tone devices and FM Adjustments. **Herb Friedman**

**COMPUTERS**

- 80 **COMPUTER CORNER**  
Electronic worksheets. **Les Spindle**

**EQUIPMENT REPORTS**


- 26 **Sencore Model SC61 Waveform Analyzer.**
- 32 **McKay/Dymek General Coverage Receiving System**

**DEPARTMENTS**


- |                                  |                    |
|----------------------------------|--------------------|
| 12 Advertising and Sales Offices | 22 Letters         |
| 138 Advertising Index            | 114 Market Center  |
| 111 Books                        | 106 New Literature |
| 14 Editorial                     | 95 New Products    |
| 139 Free Information Card        | 6 What's News      |

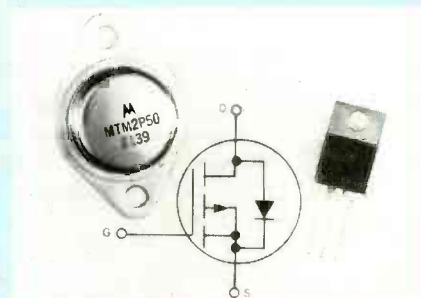**ON THE COVER**

Using an opto-electronic sensor that attaches to your finger, this battery-powered monitor displays your heart rate in beats-per-minute on a digital display. Knowing how your heart rate varies under different circumstances can give you an idea of your physical condition. Get started building yours today. The story starts on page 45.



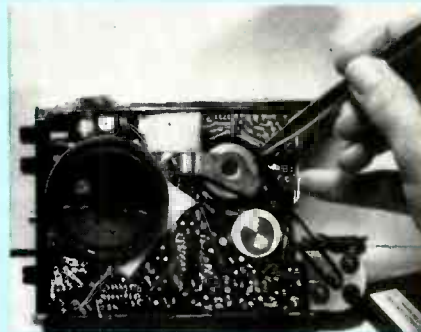HOW TO PROPERLY BIAS a transistor circuit is the subject of this month's analog design series. Must reading if your designs are to function the first time you plug them in. The story starts on page 59.



HOW TO TROUBLESHOOT AND REPAIR portable cassette recorders. The best results are obtained with a logical troubleshooting approach. The story starts on page 66.

Radio-Electronics, (ISSN 0033-7862) Published monthly by Gernsback Publications, Inc., 200 Park Avenue South, New York, NY 10003. Second-Class Postage Paid at New York, N.Y. and additional mailing offices. One-year subscription rate: U.S.A. and U.S. possessions, \$13.00, Canada, \$16.00. Other countries, \$20.50 (cash orders only, payable in U.S.A. currency.) Single copies \$1.25. © 1982 by Gernsback Publications, Inc. All rights reserved. Printed in U.S.A.

**Subscription Service:** Mail all subscription orders, changes, correspondence and Postmaster Notices of undelivered copies (Form 3579) to Radio-Electronics Subscription Service, Box 2520, Boulder, CO 80322.

A stamped self-addressed envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

# VIDEO ELECTRONICS

DAVID LACHENBRUCH  
CONTRIBUTING EDITOR



## DISC DATA

The often-postponed market launch of the Japanese VHD videodisc system is now scheduled for summer 1983. Pioneer (see photo) has expanded its line of LaserVision players to three—the original model at about \$750, a new remote-control unit at \$800, and a version without remote and random frame access at \$600. RCA added a fourth CED player to its line described here last month—a model with wireless remote control and all-electronic on-set controls at \$449.95.

## DIGITAL TV

"Computer TV" could become a byword—or an advertising point—next year when the first sets with completely digital signal-processing circuits are scheduled to be introduced. The circuits are contained on five VLSI IC's developed by ITT Semiconductor and being offered worldwide to TV set makers. ITT claims the IC's replace an average of 20 IC's, 500 to 600 transistors and other components, and make possible production of a better TV set for the same or less money. Among the claimed advantages: The set can be self-testing and self-adjusting, automatically compensating for picture-tube aging. The same set can be "programmed" to accommodate NTSC or PAL color. Stereo audio, when available, comes "free" (except for the speakers), merely by programming. The design will accommodate digital sound input, or digital input from a computer. It makes possible the later addition of low-cost "peripherals," such as digital ghost elimination, high-definition by means of line interpolation, and elimination of flicker by interpolation of additional fields or frames. The first production prototype digital TV will be shown by ITT's Standard Elektrik Lorenz of Germany. Among at least eight set makers working with the ITT circuits is Zenith, which could be the first to introduce a digital set here.

## BETA HI-FI

How can you get true high-fidelity stereo from a half-inch home video recorder? The VHS manufacturers are adding a second audio track and Dolby noise reduction, but that provides a 50-10,000 Hz frequency response, at most. Headed by Sony, the Beta group has been showing a proposed new "Beta Hi-Fi" system that can provide better audio specs than an open-reel tape recorder, but is still compatible with existing Beta recorders and tapes.

Beta's magic trick is to leave the current longitudinal audio track alone and put a new stereo sound track on an FM carrier in the helical video track. The result is "nearly digital" sound, with an 80-dB range, far above the 30- to 40-dB range of current recorders, with a frequency response of 20-20,000 Hz at 0.3% distortion, and inaudible wow and flutter. Recorders built for the hi-fi system would also be able to play the longitudinal track on old tapes, and new prerecorded tapes would have a longitudinal mono track plus the helical hi-fi stereo pair, to preserve compatibility. An extra bonus is the ability to have three separate soundtracks on mono tapes—three different languages, for example. Sony claims that such a helical-audio feat can't be accomplished on VHS recorders because their head drums are too small, resulting in picture degradation. But the VHS camp has yet to be heard from on the subject. If they go ahead with the project, Beta manufacturers say they can have recorders in the hi-fi format on the market around mid-1983.

R-E

**No one else gives you as many functions in a handheld DMM.**

**Now you can move up to Fluke."**

We've got great news for people who've been holding out for a high quality, high performance DMM at a moderate price: Fluke's new nine-function model D 804 is now available at select electronics supply stores.

With a suggested U.S. price of only \$249 and features you won't find in any other handheld DMM, the D 804 is an exceptional value. Here's why.

**Logic level and continuity testing:** A real time-saver for troubleshooting passive circuits in pcb's, cables, relay panels and the like. The D 804 has a switch-selectable audible tone and visual symbols to indicate continuity or logic levels.

**Direct temperature readings in °C:** Used with any K type

thermocouple, the D 804 delivers fully-compensated readings in °C from -20°C to +1265°C, for checking heating and refrigeration systems.

**Peak hold feature captures transients:** A short-term memory in the D 804 captures and holds the peak reading of a motor starting current.

**And more:** 0.1% basic dc accuracy, conductance, 26 measurement ranges, battery, safety-designed test leads and a one year parts and labor warranty. A full line of accessories is also available to extend the measurement capabilities of your DMM.

Ask your dealer about the powerful, versatile D 804 and the rest of Fluke's new Series D line of low-cost digital multimeters.



**From the world leader in DMM's. Now we've designed one for you.**



Suggested U.S. list price  
technical data circle No. 15  
1330-0/D804  
RE 9/82

If your dealer doesn't carry Series D  
Multimeters yet, call this number. We'll be  
happy to tell you who does. 1-800-426-0361

**FLUKE**

# WHAT'S NEWS

## Sharp reducing copier talks back to user

A new dry, any-paper desktop copier that talks to its user, makes reduced-size copies, can be automated, and helps diagnose its own troubles, has been introduced by Sharp Electronics Corp., headquartered in the United States at Paramus, NJ.

The new model SF-781 speaks from a built-in voice synthesizer that emits electronic tones in a series that the ear hears as clear, easily understood sentences. When the user makes a reduced-size copy, the machine reminds

him: "Check the paper size," and if he leaves his material in the machine and starts to walk away, it calls out: "Remove the original." If there is a paper misfeed, the SF-781 warns the user and tells where to look for the cause.

The machine also warns if paper or toner needs replenishing, and if the machine is out of order. The copier's total vocabulary is nine sentences, all selected to boost efficiency and save time.

An advanced self-diagnostic system, aided by a microcomputer, pinpoints many problems by voice or LED alphanumeric display—quick but thorough diagnos-

tic tests can be run from the front panel by pressing buttons.

The copier will take originals up to 11 × 17 inches. From that size, copies can be reduced to 8½ × 14 or 8½ × 11 inches. Line artwork can often be reduced so cleanly that it can be used for reproduction. Two 8½ × 11-inch pieces can be placed side-by-side for reproduction. The SF-781 picks up a broad range of colors, including the difficult blue tones.

## Transistors move into high-voltage range

Motorola, in what it refers to as "a major expansion of MOS power transistor technology," has introduced eight new devices in the "sparsely populated 550-volt and up" field. The new devices are intended for power supplies operating from 230 and 460-volt lines. They are supplied in four voltages, with breakdown rating from 550 to 900 volts, and up to 3 amperes of continuous drain current.

The new devices are intended for such equipment as transmitters, radar, and medical electronics using high-power, high-voltage, tube-operated circuitry. Prices are in the \$7 to \$10 range. Data sheets are available from Motorola at P.O. Box 20912, Phoenix, AZ 85036.

## Children, aged 3 to 13, are new computer market

The Learning Co. of Portola Valley, CA, is henceforth devoting its efforts to developing and selling interactive computer software for children whose ages range from 3 to 13 years. The programs are for use in the home, and include play with learning, encouraging participation by both children and their parents.

The first two programs offered are *Moptown* and *Magic Spells*. They are available from Apple Computer distributors under Apple's Special Delivery Software programs. *Moptown* is a set of 11 logic games; *Magic Spells* is a word game that combines large text, color graphics, and music.

The games are designed for parents who wish to encourage their

children to learn in an entertaining and unthreatening way. The program guides the child through a series of adventures that promote original thinking. There is no violence and no wrong answers to discourage the child.

Founded in 1980 as Advanced Learning Technology by Dr. Ann Piestrup, the company pioneered the development of children's programs with interactive software featuring color graphics and animation, working under grants from the National Science Foundation and the Apple Education Foundation. Its change of name marks its move from a grant-funded organization to a commercial firm.

## New plant will meet videodisc demands

RCA has commenced construction in Indianapolis of a new \$19 million facility for manufacturing the compound essential in making "CED" videodiscs. That will be used to support the expanding disc manufacture at the company's Rockville Road plant in Indianapolis, as well as to supply other manufacturers worldwide.

The compounding facility blends the plastic, carbon, and other materials that are used in pressing the conductive RCA discs. The blended material is in the form of pellets, which are formed into a mass and then placed between the two stampers of an automatic compression molding press to make the final disc. The new plant will be able to process 50,000 pounds of raw material daily.

In addition to the new 55,000-square-foot compounding facility, RCA has completed a new power plant that will be able to produce the energy that will be needed for 60 disc presses.

## Satellite-to-home broadcasts in sight

The Satellite Television Corp (STC) a subsidiary of COMSAT, has received four bids to construct direct-broadcast satellites (DBS) for STC's satellite-to-home pay-TV service. The companies bidding were Ford Aerospace and Communications Corp, General Elec-


*continued on page 12*



SECRETARY IS USING THE SF-781 with SF-461 automatic document feeder (right) and SF-410 sorter (in front of the secretary). Those can be added to the copier to permit the equipment to grow as the user's needs may require.


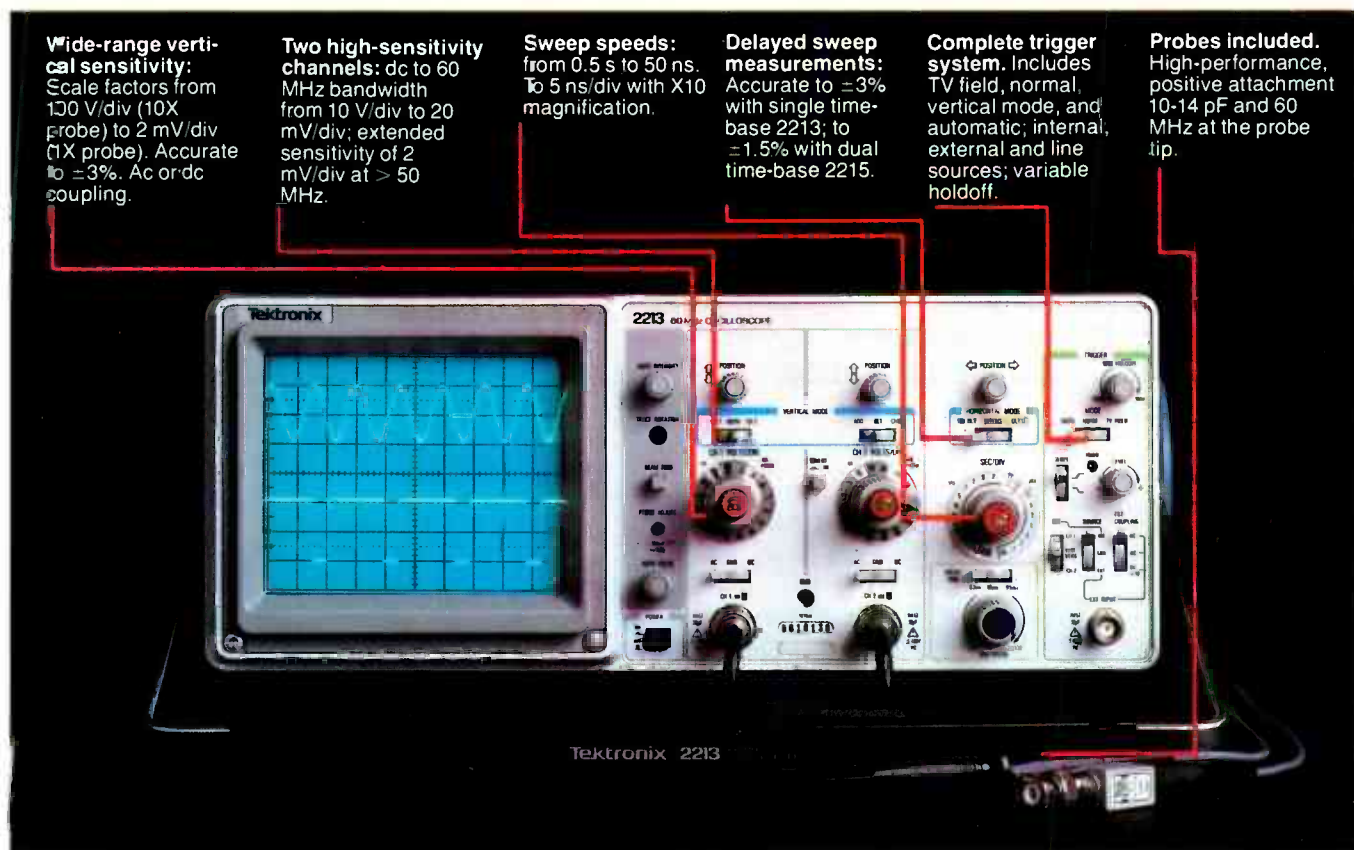
# Now! A 60 MHz Tektronix scope built for your bench.



**Wide-range vertical sensitivity:** Scale factors from 100 V/div (10X probe) to 2 mV/div (1X probe). Accurate to  $\pm 3\%$ . Ac or dc coupling.

**Two high-sensitivity channels:** dc to 60 MHz bandwidth from 10 V/div to 20 mV/div; extended sensitivity of 2 mV/div at  $> 50$  MHz.

**Sweep speeds:** from 0.5 s to 50 ns. To 5 ns/div with X10 magnification.

**Delayed sweep measurements:** Accurate to  $\pm 3\%$  with single time-base 2213; to  $\pm 1.5\%$  with dual time-base 2215.

**Complete trigger system.** Includes TV field, normal, vertical mode, and automatic; internal, external and line sources; variable holdoff.

**Probes included.** High-performance, positive attachment 10-14 pF and 60 MHz at the probe tip.

**In 30 years of Tektronix oscilloscope leadership, no other scopes have recorded the immediate popular appeal of the Tek 2200 Series.** The Tek 2213 and 2215 are unapproached for the performance and reliability they offer at a surprisingly affordable price.

There's no compromise with Tektronix quality: The low cost is the result of a new design concept that cut mechanical parts by 65%. Cut cabling by 90%. Virtually eliminated board electrical connectors. And obviated the usual cooling fan.

Yet performance is written all over the front panels. There's the bandwidth for digital and analog circuits. The sensitivity for low signal measurements. The sweep speeds for fast logic families. And delayed sweep for fast, accurate timing measurements.

**The cost: \$1100 for the 2213\*, \$1400 for the dual time base 2215.**

You can order, or obtain more information, through the Tektronix National Marketing Center, where technical personnel can answer your questions and expedite delivery. Your direct order includes

probes, operating manuals, 15-day return policy and full Tektronix warranty.

For a demonstration stop by your local Tektronix Sales Office.


**ORDER TOLL FREE  
1-800-426-2200**

**Ask for Department J0133**  
In the state of Washington,  
Call (206) 253-5353 collect.

\*Price F.O.B. Beaverton, OR
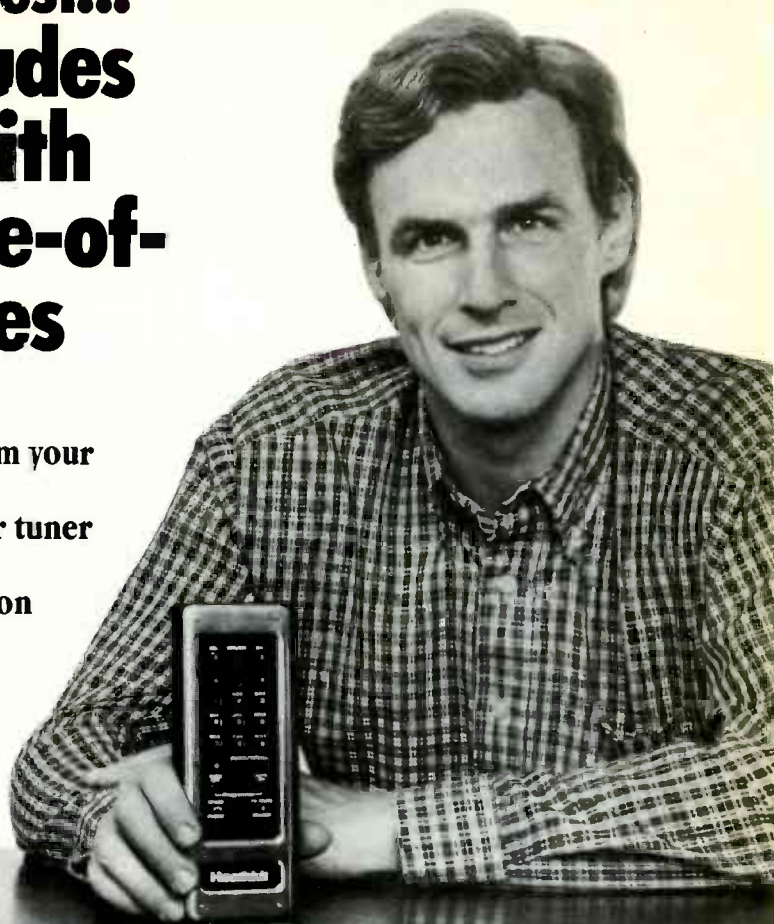
# Now! Learn on the latest... NRI training includes 25" Heath/Zenith color TV with state-of- the-art features

- 6-function infrared remote control
- space phone lets you answer or call from your chair
- microprocessor-controlled PLL varactor tuner
- 82 VHF/UHF, 35 cable channels
- 24-hour programmable channel selection
- electronic time display
- 4-speaker FM sound system
- choice of three cabinets at student discount



We've taken the finest, most advanced, most complete TV/Audio/Video course available and made it even better. Now NRI brings your training up to and even beyond today's technology with the exciting, advanced performance Heath/Zenith Model 2501 TV. Now you can learn how to service even the latest circuitry on the most expensive TV sets as you assemble and perform experiments on your Heathkit/Zenith. Only NRI combines such complete training with such up-to-date equipment.



Choice of specialty training on TV, stereo, or VCR

### Choice of Three Specialties


And only NRI gives you the opportunity to specialize in any of three areas. You get the same complete training covering TV, audio systems, and video recorders, but you select your own specialty for practical, hands-on training.

You can choose to build the Heath/Zenith color TV; specialize in audio systems and build your own AM/FM stereo system; or take your bench training with remote-controlled videocassette recorder featuring NRI training on videotape. No matter

which specialty you elect, your practical training also includes experiments and demonstrations with the exclusive NRI Discovery Lab® and your own professional digital multimeter. All equipment is yours to use and keep.
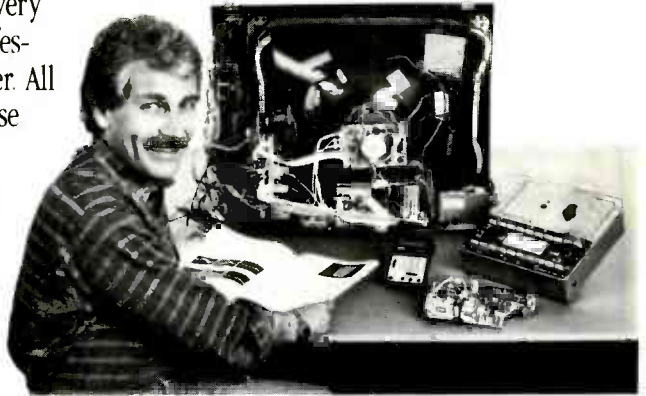
### Learn in Your Spare Time

No need to quit your job or tie up your evenings with night school...no classroom competition or rigid schedules. NRI trains you in your own home at your convenience. You're a class of one with complete course materials, practical training on the latest equipment, and the backing of a full staff of professional electronics educators. NRI brings it all to you.



Practical training on a real state-of-the-art TV using professional equipment

### The Professional's Choice

A million and a half students have already chosen the NRI way. And over half the practicing TV service technicians in the U.S. have advanced their careers with convenient home training. Among them, it's NRI 3 to 1 over any other school (summary of national survey on request).

### Free Catalog... No Salesman Will Call

Get all the facts on complete, convenient NRI training. See all the equipment, look over complete lesson plans, check out our convenient time payment plans. And see the many other opportunities in fields like Microcomputers, Electronic Design, Communications Electronics, and more. Send postage-paid card and see what advanced training is all about. If card has been removed, please write to us.



**NRI Schools**  
McGraw-Hill Continuing  
Education Center  
3939 Wisconsin Ave.  
Washington, D.C. 20016

**We'll give you tomorrow.**

# WHAT'S NEWS

continued from page 16

tric Co., Hughes Aircraft Co., and RCA Astro Electronics.

STC's Request for Proposals (issued January 13) were for construction of two satellites (one operating and one spare) which STC would use for satellite-to-home pay-TV service over an area approximating the U.S. Eastern Time Zone. The satellites are scheduled to operate on the 12- and 17-GHz bands.

The construction program is expected to take more than three years, and the service would begin in late 1985 or early 1986. STC will offer three channels of premium pay television, without advertising. Individual subscribers would receive STC's pay-TV service on small, inexpensive home receiving-antennas.

## Optical system tracks distant satellites

The first of five Ground-based Electro-Optical Deep Space Surveillance Systems (GEODSS) has gone into action at the White Sands Missile Range in New Mexico. It will track optically satellites that orbit well above the range of most radars. GEODSS replaces an older camera system that required developing photographic plates and examining them with a microscope, usually about an

hour's work. Sighting and identification with GEODSS is almost instantaneous.

GEODSS's telescopes can pinpoint the location of all satellites above 3,000 miles, especially those that orbit at 22,000 miles above the equator. The telescopes combine camera optics and computers and can see objects 10,000 times dimmer than the human eye can detect. They are able to spot an object the size of a soccer ball more than 22,000 miles away. In operation, they fix on the stars and pick up any objects moving in front of them.

The telescope search is automatic, and the images it captures are recorded on a television camera. One hundred pictures a minute are converted into digital pulses and fed into a computer that filters out the (relatively) stationary surrounding stars and displays the satellites as streaks of light on video monitors.

To protect its own satellites from possible destruction, the Air Force must know what is in space and whether it is friend or foe. That information will be supplied by the GEODSS network. Sites in Korea and Hawaii are expected to be operational sometime this year, and an Eastern Atlantic and an Indian Ocean station will be in operation by the mid-1980's.

## Anti-scanner ordinance tossed out in Philly

Municipal Court Judge J. Earl Simons ruled that Section 10-817 of the Code of Philadelphia Ordinances is unconstitutional. The ordinance, enacted in 1967, made access to police and fire radio channels illegal. It was not enforced until late in 1981, when the city interpreted the law to apply to radio scanners and arrested several owners and employees of retail stores for selling scanners.

The judge stated, among other things: "Individuals use scanner radios for personal entertainment or security purposes. Group use is endorsed—and in fact encouraged—by local law enforcement agencies, which conduct programs to teach the use of such scanner radios as a crime combatant. ... There is no evidence to support the contention that access to police or fire channels increases crime, or the risk thereof ... on the contrary, it demonstrates a markedly decreased risk of criminality when such scanners are employed by the citizenry. The conclusion is compelled that the ordinance is unconstitutional."

The judge then ruled that the citations be dismissed and the defendants discharged.

## New state voice network promises greater economy

The State of Washington has contracted with the Action Communications System Div of Honeywell for a *Roadrunner* Network Management System, to replace a Common Channel Switching Arrangement (CCSA) leased from Pacific Northwest Bell.

The state has spent nearly \$12 million annually for long-distance telephone services provided by the CCSA leased network system. It is expected that the new systems can save about \$5 million in annual long-distance costs. Average calling rates will be reduced from 12 cents to 6.5 cents per minute by using the least-cost routing and management possibilities offered.

A network of intermachine trunks and PBX tie lines will interconnect four switching centers at Olympia, Seattle, Spokane, and Vancouver with government PBX

facilities across the state. The 2,656 port statewide network will utilize 4,800-baud data links between the four switching centers for "look ahead" routing and database maintenance and diagnostics.

## G-E applies for a new consumer phone service

The General Electric Co. has applied for a total of 9 MHz in the 900-MHz band, for a new consumer-oriented mobile communications service. The allocation would be divided into two 4.5-MHz bands separated by 45 MHz. That would provide 150 channels of 30 kHz each.

The new Personal Radio Home Communications Service (PRCS) would be designed to augment the limited communications services already available to mobile consumers. It would provide the user with an affordable quality service for private communications within a user's normal driving area.

The system will consist of a base station tied into the user's telephone, and mobile units installed by users in their vehicles. The typical range with the system would be in the order of 5 miles, which can be increased to approximately 15 miles by using strategically located repeater stations. There would be a nominal charge access of any of those. Repeaters would not be interconnected.

An additional communications feature is automatic interconnection to the public telephone network through the base station.

## New photovoltaic cell works with low light

A high-performance photovoltaic module that produces 40 watts of peak power with 35 solar cells has been developed by Arco Solar (a subsidiary of Atlantic Richfield) at Chatsworth, CA.

Using single-crystal silicon cells, the module can charge batteries at 5 to 10 percent of noontime sun. The manufacturer claims that under such low light conditions, the new cells can deliver up to 25 percent more energy than typical modules of polycrystalline design.

The new module, M51, measures 1 x 4 feet and is 10.75 percent efficient.

R-E



AIR FORCE TECHNICIANS TRACK SATELLITES at the ground-based Electro-Optical Deep Space Surveillance System facility in New Mexico. It is the first of five world-wide stations that will keep track of all man-made satellites in orbit within a range of 22,000 miles.

# The Workbench



**SOLDER AID**

**OK Machine & Tool Corporation**  
3455 Conner St., Bronx, N.Y. 10475 U.S.A.  
Tel. (212) 994-6600 Telex 125091

CIRCLE 17 ON FREE INFORMATION CARD

**ok**

[www.americanradiohistory.com](http://www.americanradiohistory.com)

# EDITORIAL

## "My Kingdom For A ....."

How many times have you decided to build a project only to find that the parts list contains components that are almost impossible to obtain locally? Or, how many times have you used your best troubleshooting skills to locate a bad component on a PC board only to find that the component might as well be a proprietary unit from a Titan missile. Unfortunately, we've all found ourselves faced with that situation at one time or another.

Let's face it, in today's "high-technology" society, the electronic components that we very often need are becoming more and more difficult to obtain locally. Perhaps it is because the components that we are looking for are becoming more complex. Or, perhaps our local suppliers are finding it necessary to become more specialized. Whatever the reasons may be, understanding them won't help us when we're faced with the situation of trying to obtain a specific component.

As bad as the situation might seem, especially to those of us that are not living in or near a large metropolitan area, we are not totally helpless. Fortunately, there are a large number of mail-order firms that supply electronics components. While I'll admit that ordering an electronic component from a mail-order supplier is not as convenient as walking into your local supplier, at least the mail-order supplier is more likely to have a larger and more diversified inventory.

While the majority of the mail-order suppliers are quite reputable, not all of them are on the up and up. Screen the mail-order suppliers before you buy from them. First, if the ads appear month after month in **Radio-Electronics** magazine, you can be confident that they are reputable. Use the free information card at the back of the magazine to order catalogs from those suppliers and keep them handy. Catalogs are great for locating components that you need and they contain valuable ordering information when you're actually ready to order a component.

I can't possibly cover all the aspects of purchasing mail-order components in just one editorial page. The subject is important and we are presenting part 1 of a two-part series entitled "The Ins and Outs of Buying Mail-Order Components." Read the series and request as many catalogs as you can from the mail-order suppliers. They will be your best protection against being stuck for hard-to-find components in the future.



**ART KLEIMAN**  
Editor

## Radio- Electronics

**Hugo Gernsback** (1884-1967) founder  
**M. Harvey Gernsback**, editor-in-chief  
**Larry Steckler**, CET, publisher  
**Arthur Kleiman**, editor  
**Josef Bernard**, K2HUF, technical editor  
**Carl Laron**, WB2SLR, assistant editor  
**Jack Darr**, CET, service editor  
**Robert F. Scott**, semiconductor editor  
**Herb Friedman**, communications editor  
**Gary H. Arlen**, contributing editor  
**David Lachenbruch**, contributing editor  
**Earl "Doc" Savage**, K4SDS, hobby editor  
**Ruby M. Yee**, production manager  
**Robert A. W. Lowndes**, production associate  
**Stefanie A. Mas**, production assistant  
**Joan Roman**, circulation director  
**Arline R. Fishman**, advertising coordinator

**Radio-Electronics** is indexed in *Applied Science & Technology Index* and *Readers Guide to Periodical Literature*.

Gernsback Publications, Inc.  
200 Park Ave. S., New York, NY 10003  
President: M. Harvey Gernsback  
Vice President: Larry Steckler

### ADVERTISING SALES 212-777-6400

Larry Steckler  
Publisher

### EAST

Stanley Levitan  
Radio-Electronics  
200 Park Ave. South  
New York, NY 10003  
212-777-6400

### MIDWEST/Texas/Arkansas/Okla.


Ralph Bergen  
The Ralph Bergen Co., Inc.  
540 Frontage Road—Suite 325  
Northfield, Illinois 60093  
312-446-1444

### PACIFIC COAST Mountain States

Marvin Green  
Radio-Electronics  
413 So. La Brea Ave.  
Los Angeles, Ca 90036  
213-938-0166-7
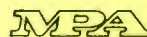
### SOUTHEAST

Paul McGinnis  
Paul McGinnis Company  
60 East 42nd Street  
New York, N.Y. 10017  
212-490-1021



# NEW! Here's a professional, portable DC-20 MHz Oscilloscope with build-it-yourself Heathkit savings



**Compact enough to fit under an airplane seat, the Heathkit IO-3220 represents outstanding value in its class. Weighing only 16 pounds, the IO-3220 is designed for field service troubleshooters who need a light, portable battery-operated scope for use where AC power is not available.**

**Dual-trace versatility:** The IO-3220 allows you to compare two different signals simultaneously – to make input/output comparisons, check phase relationships and accomplish other complex measurements. Algebraic functions add versatility.

**Special invert display function:** Enables you to compare two waveforms that are nearly 180 degrees out of phase – by inverting one of the waveforms.

## FREE CATALOG

Complete details on Heathkit oscilloscopes – and nearly 400 other electronic kits for your home, work or pleasure – are in the new Heathkit catalog. Send the coupon at right for yours today, or pick one up at any of the 65 convenient Heathkit Electronic Centers\*\* located throughout the U.S. and Canada.

If coupon is missing, write Heath Co., Dept. 020-934, Benton Harbor, MI 49022.



# Heathkit®

\*Mail Order, F.O.B. Benton Harbor, MI. Also available assembled, mail order priced at \$995.00, F.O.B. Prices, specifications and product availability subject to change without notice. \*\* See the white pages of your telephone book for the Heathkit Electronic Center nearest you. Heathkit Electronic Centers in the U.S. are operated by Veritechnology Electronics Corporation, a wholly-owned subsidiary of Zenith Radio Corporation. GX-387



**X-Y inputs for Lissajous measurements:** Feed two separate input signals to the IO-3220.

**Wide DC-20 MHz bandwidth:** The IO-3220 can measure a very wide range of input signals.

**Outstanding sensitivity:** Vertical signals as low as 2 millivolts can be accurately measured by the very sensitive IO-3220. Accuracy is as

high as 3 percent (from 20-30 deg. C), on both vertical and horizontal measurements.

**Save more than 30% when you build it yourself:** The IO-3220 Portable 20 MHz Oscilloscope Kit is value-priced at just \$689.95\*.

**Easy to build:** Thorough Heathkit assembly manuals take you step-by-step, from unpacking to final plug-in. Anyone can do it. And experienced service techs are just a phone call away, to help you during building or servicing.

MAIL TO: Heath Company, Dept. 020-934  
Benton Harbor, MI 49022

YES, Please send me your free Heathkit Catalog.  
I'm not currently receiving your catalog.


Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_

GX-387 \_\_\_\_\_ Zip \_\_\_\_\_

# ZX81

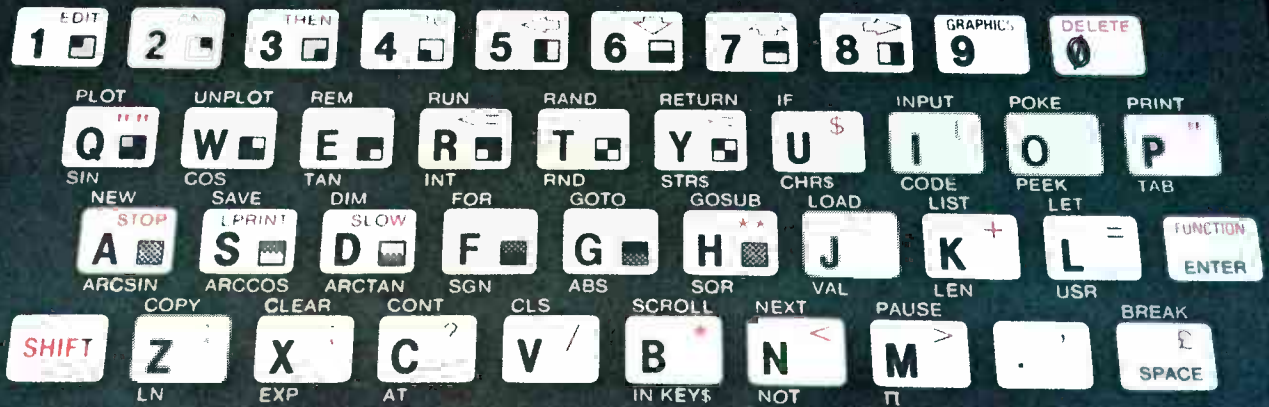

## Introducing the Sinclair ZX81.

If you're ever going to buy a personal computer, now is the time to do it.

The Sinclair ZX81 is the most powerful, yet easy-to-use computer ever offered for anywhere near the price: only \$99.95\* completely assembled.

Don't let the price fool you. The ZX81 has just about everything you could ask for in a personal computer.

### A breakthrough in personal computers.

The ZX81 is a major advance over the original Sinclair ZX80 – the first personal computer to break the price barrier at \$200.

In fact, the ZX81's 8K extended BASIC offers features found only on computers costing two or three times as much.

Just look at what you get:

- Continuous display, including moving graphics

# THE \$99.95 PERSONAL COMPUTER.

- Multi-dimensional string and numerical arrays
- Mathematical and scientific functions accurate to 8 decimal places
- Unique one-touch entry of key words like PRINT, RUN and LIST
- Automatic syntax error detection and easy editing
- Randomize function

useful for both games and serious applications

- 1K of memory expandable to 16K
- A comprehensive programming guide and operating manual

The ZX81 is also very convenient to use. It hooks up to any television set to produce a clear 32-column by 24-line display. It comes with a comprehensive programming guide and operating manual designed for both beginners and experienced computer users. And you can use a regular cassette recorder to store and recall programs by name.

Sinclair technology is also available in Timex/Sinclair computers under a license from Sinclair Research Ltd.



**Order at no risk.\*\***

We'll give you 10 days to try out the ZX81. If you're not completely satisfied, just return it to Sinclair Research and we'll give you a full refund.

And if you have a problem with your ZX81, send it to Sinclair Research within 90 days and we'll repair or replace it at no charge.

**Introducing the ZX81 kit.**

If you really want to save money, and you enjoy building electronic kits, you can order the ZX81 in kit form for the incredible price of just \$79.95.\* It's the same, full-featured computer, only you put it together yourself. We'll send complete, easy-to-follow instructions on how you can assemble your ZX81 in just a few hours. All you have to supply is the soldering iron.

**A leader in microelectronics.**

The ZX81 represents the latest technology in microelectronics. More than 10,000 are sold every week. In fact, the ZX81 is the fastest selling personal computer in the world.

We urge you to place your order for the ZX81 today.

**To order.**


To order, simply call toll free. Or use the coupon below. Remember, you can try it for 10 days at no risk.\*\* The sooner you order, the sooner you can start enjoying your own computer.

**Call toll free 800-543-3000.**

Ask for operator #509. In Ohio call: 800-582-1364; in Canada call: 513-729-4300. Ask for operator #509. Phones open 24 hours a day, 7 days a week. Have your MasterCard or VISA ready.

These numbers are for orders only. If you just want information, please write: Sinclair Research Ltd., 2 Sinclair Plaza, Nashua, NH 03061.

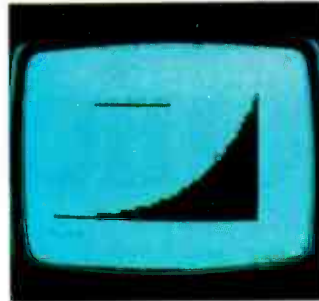\*Plus shipping and handling. Price includes connectors for TV and cassette, AC adaptor, and FREE manual.  
\*\*Does not apply to ZX81 kits.



**NEW SOFTWARE:** Sinclair has published pre-recorded programs on cassettes for your ZX81. We're constantly coming out with new programs, so we'll send you our latest software catalog with your computer.

**16K MEMORY MODULE:** Like any powerful, full fledged computer, the ZX81 is expandable. Sinclair's 16K memory module plugs right onto the back of your ZX81. Cost is \$49.95, plus shipping and handling.

# sinclair

To order call toll free: 800-543-3000

| Ad Code               | Price*  | Qty. | Amount |
|-----------------------|---------|------|--------|
| 09RE                  |         |      |        |
| ZX81                  | \$99.95 |      |        |
| ZX81 Kit              | 79.95   |      |        |
| 16K Memory Module     | 49.95   |      |        |
| Shipping and Handling | 4.95    |      | \$4.95 |
| TOTAL                 |         |      |        |

**MAIL TO:** Sinclair Research Ltd.,  
One Sinclair Plaza, Nashua, NH 03061.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

\*U.S. dollars



# If you have put off learning more electronics for any of these reasons, act now!

- I don't have the time.
- High school was hard for me and electronics sounds like it may be hard to learn.
- I can't afford any more education.
- I have a family now.
- I'm here. You're there. I've never learned that way before. I'm not sure it will work for me.

**Be honest with yourself. Are the reasons really excuses? You already know enough about electronics to be interested in reading this magazine. So why not learn more? If you need encouragement, read on and see how excuses can be turned into results.**

**You don't have the time.** Be realistic. All you have in life is a period of time. Use it. Try to know more tomorrow than you do today. That's the proven way to success. CIE studies require just about 12 hours of your time a week, two hours a day. You probably do have the time.

**Electronics sounds like it may be hard to learn.** You already know something about electronics or you wouldn't be reading this. Now, build on that. CIE Auto-Programmed® Lessons help you learn. Topics are presented in simple, logical sequence. All text is clear and concise for quick, easy understanding. You learn step by step, at your own pace. No classes to attend. Nobody pressures you. You can learn.


**You can't afford any more education.** Actually, you can't afford NOT to gain the skills that can put you ahead of the others. You know what inflation is doing to you now. Education—learning a skill—is an inflation-fighter that can be yours. If you are not able to pay full tuition now, CIE will lend you funds on a monthly payment plan.

**You have a family now.** All the more reason why you have the responsibility to advance yourself. For the sake of your family. Do you want them to have what you had or have more than you had? The choice is yours. Electronics is a rewarding career choice. CIE can help you to get started on that career.

**You're there. We're here. How does CIE help you learn?** First, we want you to succeed. You may study at home, but you are not alone. When you have a question about a lesson, a postage stamp gets you your answer fast. You may find this even better than having a classroom teacher. CIE understands people need to learn at their own pace. When CIE receives your completed lesson before noon any day of the week, it will be graded and mailed back the same day with appropriate instructional help. Your satisfaction with your progress comes by return mail. That's how CIE helps you learn.
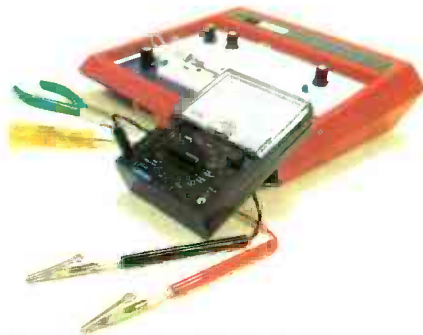
## NOW, IF YOU AGREE CIE TRAINING CAN WORK FOR YOU, HOW ELSE CAN CIE HELP YOU?

Cleveland Institute of Electronics is the largest independent home study school in the world that specializes exclusively in electronics. Although "big" does not always mean "best," it is evidence that CIE is a strong, successful institution with the people and resources to help you succeed.



### Step-by-step learning includes "hands-on" training.

The kind of professional you want to be needs more than theory. That's why some of our courses include the Personal Training Laboratory, which helps you put lesson theory into actual practice. Other courses train you to use tools of the trade such as a 5MHz triggered-sweep, solid-state oscilloscope you build yourself—and use to practice troubleshooting. Or a Digital Learning Laboratory to let you apply the digital theory that's essential today for anyone who wants to keep pace with electronics in the eighties.



### Your FCC License can impress employers.

For some electronics jobs, you must have your FCC License. For others, employers usually consider it a mark in your favor. Either way, your License is government-certified proof of your knowledge and skills. More than half of CIE's courses prepare you to pass this exam. Surveys show that some 80% of CIE graduates who take the exam are successful.

### Find out more! Today. Now.

There's a card with this ad. Fill it in and return. If some other ambitious person has already removed it, use the coupon.

You'll get a copy of CIE's free school catalog, along with a complete package of personal home study information.

For your convenience, we'll try to arrange for a CIE representative to contact you to answer any questions you may have.

If you are serious about a rewarding career, about learning electronics or building on your present skills, your best bet is to go with the electronics specialists—CIE. Mail the card or coupon today or write CIE (please mention the name and date of this magazine), 1776 East 17th Street, Cleveland, Ohio 44114.

This could be the best decision you've made all year.

### Associate Degree

Now, CIE offers an Associate in Applied Science Degree in Electronics Engineering Technology. In fact, all or most of every CIE Career Course is directly creditable towards the Associate Degree.

**"If you're going to learn electronics, you might as well learn it right!"**

*John Cunningham  
Senior Technical Director*



## CIE Cleveland Institute of Electronics, Inc.

1776 East 17th Street, Cleveland, Ohio 44114  
Accredited Member National Home Study Council

**YES...** I want to learn from the specialists in electronics—CIE. Send me my FREE CIE school catalog...including details about the Associate Degree program...plus my FREE package of home study information.

Print Name \_\_\_\_\_

Address \_\_\_\_\_ Apt. \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

Age \_\_\_\_\_ Phone (area code) \_\_\_\_\_

Check box for G.I. Bill bulletin on Educational Benefits:  Veteran  Active Duty

**MAIL TODAY!**

RE-44

# LETTERS

Address your comments to: Letters, **Radio-Electronics**,  
200 Park Avenue South, New York, NY 10003

## DATABASE MANAGEMENT SYSTEMS

I have just finished reading the June 1982 issue of **Radio-Electronics**. Your article on database management systems was an interesting summary of available products and vendors, but I should like to correct a few oversights.

First, Compco has had to move to a larger facility. I don't believe that the post office is forwarding our mail any longer (it's been a year), so I would appreciate having this letter published with our correct address. It is:

Compco, 7110 W. Fond Du Lac Avenue, Milwaukee, WI 53218. We can be reached by telephone through calling (414) 438-0610 or (414) 438-8611.

Secondly, Compco carries a wide variety of database management packages, for many different computers. Apple, Altos, and DEC are the principle lines. CP/M, MP/M, Apple

DOS 3.3, Apple CP/M, and RT-11 are the principal operating systems that our products run under. We also carry a variety of word processing, scientific, and entertainment software and hardware.

THOMAS M. PETERS,  
*Compco, Sales Manager*

## OPENING THE DOOR

What a wonderful "opening of the door" to the world of electronics the simple building blocks described in "Hobby Corner," in **Radio-Electronics**, June 1982 provide!

The beginner is generally confronted with completely enclosed "black boxes" that defy understanding. First encounters are most important; and since most learning is through the eyes, the inner working parts should be exposed by removing all covers.

Touching is another great avenue for learning. (Beginners will soon be adjusting battery

clips and switch tensions on their own.)

As learning progresses, open-type potentiometers and transformers with visible windings may be added. Also, the *name* of each component may be lettered simply on each block, along with its schematic symbol.

You cannot imagine how fast your youngster can learn, or how importantly those beginning blocks can shape his or her life!

GENE BRIZENDINE, W4ATE,  
*Huntsville, AL*

## DIGITAL THERMOMETER

This is an addition to the digital thermometer article by Michael Ribby that appeared in the February 1982 issue of **Radio-Electronics**. I have used this circuit on my MA1026 clock module to vary the brightness of the LED display automatically with changes in the room light. The circuit uses only three components, all of which are readi-



ly available, and I have had it in service for over a year.

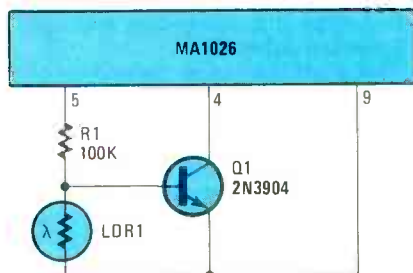


FIG. 1

Figure 1 tells the story. As the room light goes down, the resistance of LDR1 (Radio-Shack No. 276-116) increases. At a given point, determined by the value of R1, Q1 begins to conduct. That lowers the voltage on pin 4, and dims the display. Use any low-leakage transistor for Q1, with a gain ( $h_{fe}$ ) of 100 or more. Select the value of R1 to get the desired dimming action, and remember that raising the value of R1 will slow the dimming action.

HERBERT DEAN,  
Orono, ME

### NIKOLA TESLA'S CONTRIBUTIONS

In your comment on Vince Marasco's letter about Nikola Tesla ("Letters," *Radio-Electronics*, June 1982) you pointed out that

Mr. Marasco had failed to list any of the principles relating to everyday things that nearly all of us now take for granted that Tesla discovered.

The list is impressive: First, there is the AC motor. It is doubtful that there are any motor-driven devices in the home that do *not* use an AC motor, rather than the older DC units. Air conditioners, refrigerators, fans—all are built on Tesla's principle that he developed for Westinghouse.

Add to that his discovery in 1890 of applying high-frequency electricity to the body for deep heat treatment. Diathermy, in other words.

Then there is the Tesla coil—an air core transformer with resonating primary and secondary coils. Such units are used to test the effects of high-frequency electricity on switches and regulating circuits in the utility industry.

Marconi's patents on radio were upset by the U.S. Supreme Court, which ruled that they were an infringement on another's idea—Tesla. Robots, radar, and radio-controlled ships for military use, as well as the basic idea for a plane with vertical take-off and landing capabilities give you some idea—though really far from adequate—of the scope of that man's creative genius.

To anyone interested in Nikola Tesla, I recommend Margaret Cheney's book, an excellent biography titled, *Tesla, Man Out of Time*. In spite of one or two technical faults, it is worth reading; you will understand why there are so many who rate Edison second to Tesla, without denying the worth of Edison's contributions.

GEORGE deLUCENAY LEON,  
New York, NY

### SPEAKING OUT

I can keep silent no longer!

I'm an electronics buff, and have been receiving *Radio-Electronics* for about a year. I am also currently subscribing to a number of other somewhat similar magazines, but have decided that the only ones to which I shall renew my subscription are *Radio-Electronics* and *The Audio Amateur*.

I consider *Radio-Electronics* to be by far the best electronics magazine on the market at the present time, and look forward to receiving it each month. I cannot recommend it too highly!

To date, I have built eight of the construction projects that you have published. They were easy to complete, and all function as intended. I would like to compliment you on the clarity and completeness of your projects—such that one does not need a high degree of electronics theory or expertise to build them, nor run into difficulty because of exotic or highly expensive components. I also applaud the fact that, to date, you have resisted the temptation to make *Radio-Electronics* into a computer magazine; there are a plethora of those available. Please continue your emphasis on construction electronics with a broad-base appeal.

PAUL T. KELLY,  
Fort Wayne, IN

### POCKET CALIBRATOR

Gary McClellan's statement that the LM723N voltage regulator has more stable temperature characteristics than the LM723C ("Pocket Calibrator for Volts and Ohms," *Radio-Electronics*, June 1982) is

TEK 2300 SERIES  
PORTABLE OSCILLOSCOPES

THE FIELD  
SERVICE SCOPES

## Built for field service. Tough enough for the road.

**The 2300 Series is unassailable proof that sensitive instruments needn't be delicate.** No other scopes are so immune to abuse and to day-to-day wear and tear. They feature 50Gs shock resistance, our highest electromagnetic compatibility, and high-performance

measurement—all in an ultra-durable 17-lb. package.

**Bottom line: the lowest life cycle costs of any high performance portable.** Thanks to fewer components. Easier access to internal parts. Plus less downtime and fewer back-up instruments re-

quired, as proven by the toughest reliability testing we know of—our own.

**All that, and Tek performance too! Select dc to 100 MHz with 5 ns horizontal sweep. 2mV/div vertical sensitivity. Built-in delta time and DMM.** This time, get the scopes

that can handle the hard knocks of your business ... wherever the business takes you. Order today—or ask for the full Tek 2300 story! Call toll free:

**1-800-547-1845**

Ask for Department B0129 (Oregon, Alaska and Hawaii: 503-627-5402 Call collect.)

**Tektronix**  
COMMITTED TO EXCELLENCE



# Simpson®

Lets you select from 12 Safety Listed DMMs

Only Simpson offers a full line of DMMs that are listed under UL-1244 Standard for Safety — Electrical and Electronic Measuring and Testing Equipment.

### SIMPSON DIGITAL MULTIMETER SELECTION CHART

| Model              | Hand portable DMMs<br>All 2x5.6x4.6", weight 1½ lbs.  |                              |  |                     |                         | Bench portable DMMs<br>All 2.7x8.4x9", weight 3 lbs.                         |                                       |  |
|--------------------|---|------------------------------|--|---------------------|-------------------------|--|---------------------------------------|--|
|                    | 467/467B#   | 463                          | 461-2  | 461-2R              | 462                     | 464-2A/2D*   | 465-2A/2D*                            | 460-4A/4D*   |
| Features           | Deluxe unit with true RMS, pulse detection, differential peak hold, visual/audible continuity indication. #Black case | Basic low cost cordless unit | Low cost basic unit                                    | True RMS responding | Auto and manual ranging | Low cost bench DMM with 10 amp range   | Auto and manual ranging, 10 amp range | Deluxe unit. Low power ohms, aux. analog meter, 10 amp range |
| Ranges             | 26  | 26                           | 26   | 26                  | 23                      | 28   | 27                                    | 32   |
| Display (3½ digit) | LCD Digalog® display  | LCD                          | LED  | LED                 | LED                     | LED  | LED                                   | LED  |
| Basic Accuracy     | 0.1%  | 0.1%                         | 0.1%   | 0.1%                | 0.25%                   | 0.1%   | 0.1%                                  | 0.1%   |
| Power Source       | 9 V battery supplied, 200-hour battery life   |                              | Rechargeable batteries and AC adapter/charger supplied |                     |                         | AC operation standard. *AC/battery version optional (batteries not included) |                                       |  |
| Price              | \$257   | \$200                        | \$194  | \$234               | \$244                   | \$290/*\$338   | \$403/*\$453                          | \$378/*\$431   |

Choose the one that's best for you! Available at leading electrical/electronics distributors worldwide.



**SIMPSON ELECTRIC COMPANY**  
A Katy Industries Subsidiary

853 Dundee Avenue, Elgin, IL 60120  
(312) 697-2260 • Telex 72-2416 • Cable SIMELCO  
IN CANADA: Bach-Simpson Ltd., London, Ontario  
IN ENGLAND: Bach-Simpson (U.K.) Ltd., Wadebridge, Cornwall

CIRCLE 21 ON FREE INFORMATION CARD

open to misinterpretation. The premium device is the LM723. The relaxed-specifications version is the LM723C. The suffix "N" refers not to quality but to package type, in this case a dual-in-line plastic one.

Thus, an LM723N would, indeed, be superior to an LM723CN, or any other LM723C type. Unfortunately, it has been my experience that if one orders a 723N from advertisers in your Market Section, one will receive a 723CN. Of course, in most applications for the hobbyist, the "C" version will be quite adequate. However, if an LM723N (or LM723H) is really preferred, as in Mr. McClellan's nice little project your readers may have to order it from one of the major electronics parts distributors.  
LAWRENCE WALLCAVE,  
Santa Rosa, CA

### THE IBM COMPUTER

I have just finished reading your April 1982 issue, and noticed an article about IBM's first personal computer. In 1975, IBM was testing a rather heavy portable computer that was configured much like the *Osborne 1*. It had a non-removable keyboard, a small (perhaps 5 x 6-inch) monitor screen, and used data cassettes for loading. It was, I believe, the brain-child of Dick Doyle.

Time and time again, we see IBM showing all the youthful vigor of a tortoise, and, in personal-computer hardware, they've shown it again. I think that's a shame, because I like them.

JESSE THARIN,  
Tucson, AZ

R-E

### ATTENTION SINCLAIR ZX81 OWNERS!!!

Here's an inexpensive little book (Programming With The ZX81) that tells you how to use the features of that ZX81 you recently bought. It shows you programs that fit into the 1K machine and are still fun to use. Learn how the random number generator works and use it to simulate coin tossing and dice throwing. Look at the patterns the ZX81 graphics can produce. Animated graphics are also covered and complete programs for games such as Lunar Lander and Cannon Ball are included. Seven information packed chapters in this quality book. Order your copy today. Price is \$5.75 post-paid in the US.

**ELECTRONIC TECHNOLOGY TODAY INC.** 9-82  
P.O. Box 83, Massapequa Park, NY 11762

Send me my copy of "Programming With The ZX81"

Send me your complete catalog

Price of Book including Postage \_\_\_\_\_ \$5.75

NY State Residents include Sales Tax \_\_\_\_\_

TOTAL ENCLOSED \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

# THIS DEVICE MAKES ORDINARY TELEPHONES OBSOLETE.



Actual size.  
(1" x 5 $\frac{1}{8}$ " x 2 $\frac{3}{4}$ " )

*The Freedom Phone® Cordless Telephone Model FF-3500 has more features than any ordinary telephone. But one ordinary feature is missing.*

*There's no cord to tie you down. The compact handset measures 1" x 5 $\frac{1}{8}$ " x 2 $\frac{3}{4}$ " and weighs just 7 ounces. So it's really easy to take or make calls anywhere within its operational range. That's upstairs, downstairs, in the front yard, backyard, at the neighbors, up the street, or down the block.*

*Instead of going to the phone to talk, you take the phone with you.*

*Buying a Freedom Phone Cordless Telephone is an intelligent move if you prefer the convenient over the conventional. But there's more to it than meets the eye or ear.*

*Designed and built exclusively for the Electra Company, makers of Bearcat® Scanners, the Freedom Phone 3500 provides crisp and clear cordless calls. An audible tone and pulsing light confirm dialing. The touch of a button automatically redials the last number entered.*

*The Freedom Phone Cordless Telephone is as easy to install as it is to use. Its attractive and compact base station plugs into your existing phone line and electrical outlet.*

*If the idea of using a Freedom Phone Cordless Telephone has a nice ring to it, get up, walk to your obsolete telephone, and call 800-428-4315 (800-382-1076 in Indiana). You'll learn more about the Model FF-3500 and get the name of the nearest Freedom Phone Dealer.*

## THE FREEDOM PHONE® CORDLESS TELEPHONE.

**Electra** Electra Company

Division of Masco Corp. of Indiana • 300 East County Line Road • Cumberland, Indiana 46229 • International Business Office • Suite 102, 1828 Swift • North Kansas City, Missouri 64116

© 1981 Masco Corp. of Indiana

CIRCLE 19 ON FREE INFORMATION CARD

# EQUIPMENT REPORTS

## Sencore Model SC61 Waveform Analyzer



CIRCLE 106 ON FREE INFORMATION CARD

| Sencore            |  | model SC61 |   |      |   |   |      |   |   |           |    |  |  |  |
|--------------------|--|------------|---|------|---|---|------|---|---|-----------|----|--|--|--|
| OVERALL PRICE      |  |            |   |      |   |   |      |   |   |           |    |  |  |  |
| EASE OF USE        |  |            |   |      |   |   |      |   |   |           |    |  |  |  |
| INSTRUCTION MANUAL |  |            |   |      |   |   |      |   |   |           |    |  |  |  |
| PRICE/VALUE        |  |            |   |      |   |   |      |   |   |           |    |  |  |  |
|                    |  | 1          | 2 | 3    | 4 | 5 | 6    | 7 | 8 | 9         | 10 |  |  |  |
|                    |  | Poor       |   | Fair |   |   | Good |   |   | Excellent |    |  |  |  |

FOR QUITE A FEW YEARS NOW, SENCORE (3200 Sencore Drive, Sioux Falls, SD 57107) has been manufacturing "analyzers"—composite instruments that

are useful for a wide variety of electronics testing and measuring. One of their newest products is the *model SC61* waveform analyzer. Whether you're working with

analog or digital circuitry, you'll find a great many applications for this device no matter what kind of electronics work you do. It is really a quite versatile instrument, as you'll soon see.

The *model SC61* has two main sections. One is a dual-trace scope that can be used with waveforms of up to 100 MHz and voltages from 2 millivolts to 2 kilovolts. The unit's wide bandwidth (60 MHz), which is useable right up to the upper frequency limit, can come in very handy when working with high-speed digital circuitry. All of the standard features are there, including triggered sweep, a special delayed sweep mode called the delta mode (more on that later), and sync separators. The other section of this instrument is a built-in digital voltmeter with a 6-digit LCD display. The DVM display, incidently, is located right across  
*continued on page 30*

## 137 new RCA flameproof metal resistors.


### Now . . . 780 Types For More Applications

With values from 0.1 ohm to 22 megohms, RCA Flameproof Metal Resistors cover the great majority of resistor replacement needs in TV, video, and industrial servicing.

- Can replace composition, carbon film, wire-wound and other metal types.
- Tolerance ratings of  $\pm 2\%$  on most values. Ratings of  $\frac{1}{4}$ ,  $\frac{1}{2}$ , 1 and 2 watts.

Get your RCA Flameproof Metal Resistors in convenient, colorful packages from your RCA Distributor today. Or, for further information, write: RCA Distributor and Special Products Division, 2000 Clements Bridge Road, Deptford, N.J. 08096. Attn: Sales Promotion Services.

## RCA Flameproof Metal Resistors

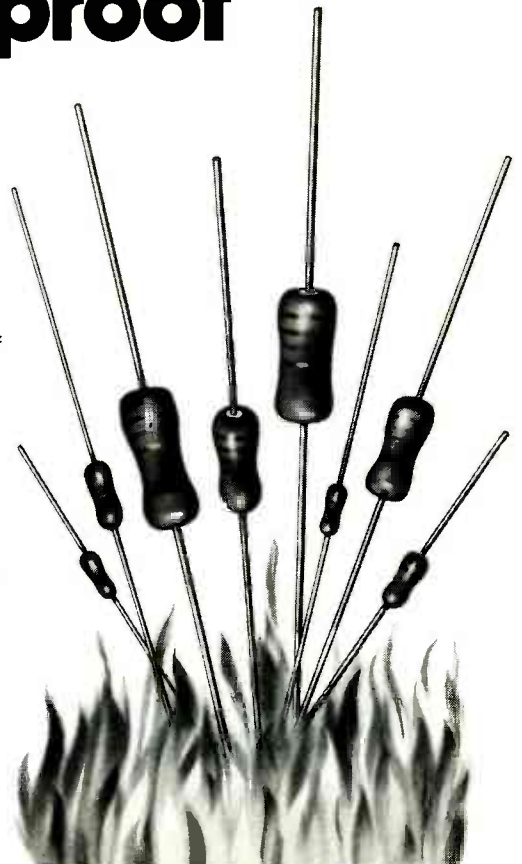



# Your guide to the world of microprocessors.

## The Micro-Professor™ - A low cost tool for learning, teaching and prototyping.

Here in one attractive package and at a price of only \$149.00 is a Z80\* based microcomputer to lead you step by step to a thorough knowledge of the world of microprocessors.

The Micro-Professor is a complete hardware and software system whose extensive teaching

\* Z80 is a trademark of Zilog Inc.

manual gives you detailed schematics and examples of program code. A superb learning tool for students, hobbyists and microprocessor enthusiasts, as well as an excellent teaching aid for instructors of electrical engineering and computer science courses.

But the Micro-Professor is much more than a teaching device. With it you can do breadboarding and prototyping, designing your own custom hardware and software applications with Z80, 8080 and 8085 compatible code.

The standard 2K bytes of RAM is expandable to 4K, and the standard 2K bytes of ROM can be increased to 8K.


All this plus a built-in speaker, a cassette interface, and

sockets to accept optional CTC/PIO. Bus is extendable.

As well as being an exciting learning tool, the Micro-Professor is a great low-cost board for OEM's. Call for details.
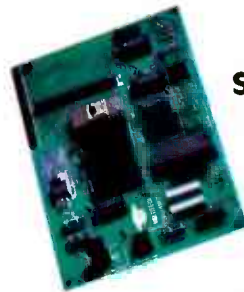
### SSB-MPF Speech Synthesizer Board \$129

A vocabulary of up to 400 words based on the TMS 5200 chip.



### EPB-MPF EPROM Programming Board \$169

For all +5V 1KB/2KB/4KB EPROMs. Read/Copy/List/Verify Capability.



### BASIC-MPF Tiny Basic \$19

2KB BASIC interpreter with hardware control capability. Machine-code subroutine accessible.



Multitech Electronics Inc.



I'm ready to enter the world of microprocessing

Call toll free to order.

|                                     | Price    | Qty. | Amount |
|-------------------------------------|----------|------|--------|
| MPF-I Micro-Professor               | \$149.00 |      |        |
| SSB-MPF Speech Synthesizer Board    | \$129.00 |      |        |
| EPB-MPF EPROM Programming Board     | \$169.00 |      |        |
| BASIC-MPF                           | \$ 19.00 |      |        |
| Shipping and Handling               | \$ 4.95  |      | 4.95   |
| California residents add sales tax. |          |      |        |
| <b>TOTAL</b>                        |          |      |        |

In U.S. and Canada mail to:

Multitech Electronics Inc.  
195 West El Camino Real  
Sunnyvale, CA 94086  
California Tel. (408) 773-8400  
Elsewhere (800) 538-1542


Outside of North America mail to:

Multitech Industrial Corporation  
977 Min Shen E Road, 105  
Taipei, Taiwan, ROC  
Tel. 02-769-1225  
TWX 19162 MULTIIC.  
23756 MULTIIC

Check or money order enclosed  
 Visa  Mastercharge

Card No. \_\_\_\_\_ Expires \_\_\_\_\_  
Signature \_\_\_\_\_  
Name (Please Print) \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

CIRCLE 9 ON FREE INFORMATION CARD

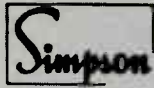

TRIPLETT

KEITHLEY

LEADER



Non-Linear Systems

### FLUKE DIGITAL MULTIMETERS

- Two New 4½-Digit Handheld DMM's from Fluke
- Wideband True RMS AC Measurements (100 kHz-8060A, 30 kHz-8062A)
- 0.04% Basic DC Accuracy (8062A = 0.05%)
- Full Range Capability (200  $\mu$ A, 200 mV, 200  $\Omega$  ranges)
- Autoranging M $\Omega$  to 300 M $\Omega$
- Relative (Offset or Zero) Mode
- Audible and Visual Continuity Indicators
- Frequency Measurement to 200 kHz, 0.01 Hz Resolution to 200 Hz, 1 Second Response Time (8060A only)
- dBm Referenced to 600  $\Omega$  (8060A only)
- Relative dB measurement (8060A only)
- Conductance (8060A only)
- Separate Constant Current Source Diode Test
- Self Diagnostics

\$349.

8060A


\$279.

8062A



**Display:** 4½ digit duplex LCD (19,999 count)  
**A/D Converter:** Dual slope converter, autozero, autopolarity.  
**Conversion:** TRMS, AC coupled  
**Display Annunciators:** BT, low battery indication.  
**REL,** relative reference mode activated. [8060A: (k)Hz, frequency function activated. dB, dB function activated.]  
**REL** (continuity activated.)), continuity tone activated.—, continuity detected indicator.  
**Temperature:** 0° to +50°C operating, -35° to +60°C storage.  
**Temperature Coefficient:** (0° to +18°C or +28° to +50°C)° .1 times the applicable accuracy specification per degree C plus the initial +18° to +28° specification.
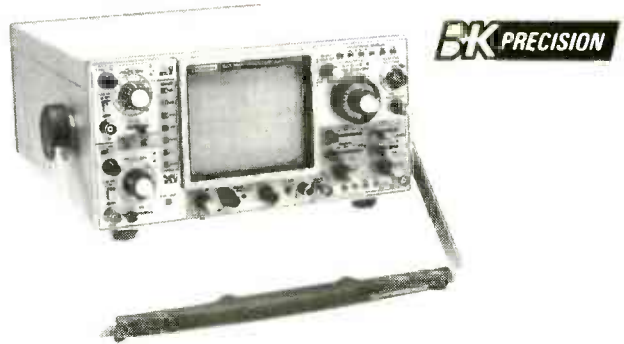
### THESE 1983 B&K OSCILLOSCOPES ARE IN STOCK AND AVAILABLE FOR IMMEDIATE DELIVERY



1590 1500 Dual Trace Dual Time Base 100MHz  
 1570 Dual Trace Dual Time Base 70MHz

1525 1530 1535 Delayed Trigger Scopes  
 1466 1476 1477 1479 High Performance Scopes

CALL FOR OUR SPECIAL DEAL ON B&K SCOPES

### New Low Distortion Function Generator



MODEL 3010

- Generates sine, square and triangle waveforms
- Variable amplitude and fixed TTL square-wave outputs
- 0.1 Hz to 1MHz in six ranges
- Push button range and function selection
- Typical sine wave distortion under 0.5% from 0.1Hz to 100kHz
- Variable DC offset for engineering applications
- VCO external input for sweep-frequency tests

Call For Our Price

### DATA PRECISION Model 938

#### 0.1%, 3½-Digit, LCD DIGITAL CAPACITANCE METER



\$219

- **WIDE RANGING** — from 199.9 pF full scale (0.1 pF resolution) up to 1999  $\mu$ F full scale, in eight ranges...virtually every capacitance you'll ever need to measure.
- **FAST AND EASY TO USE** — Direct reading, pushbutton ranges. Just plug in and read.
- **EXCEPTIONALLY ACCURATE** — provides  $\pm$ 0.1% basic accuracy.
- **TOUGH AND COMPACT** — Built to take rough usage without loss of calibration accuracy. Fits and goes anywhere; takes very little bench space; always handy for quick capacitance checkout, matching, calibration, and tracking.
- **PORTABLE** — Palm-sized, light-weight, operates up to approximately 200 hours on a single 9V alkaline battery.
- **EASY READING** — big, clear, high-contrast 3½-digit LCD display, a full 0.5" high, readable anywhere.
- **VALUE PACKED** — Outstanding measurement capability and dependability. Outperforms DC time-constant meters, and even bridges costing 2 to 5 times as much.
- **RELIABLE** — warranted for 2 full years.

### 80MHz Counter with Period Function



MODEL 1820

- 5Hz to 80MHz reading guaranteed—100MHz typical
- Period measurements from 5Hz to 1MHz.
- Period average, auto and manual positions
- One PPM resolution
- Totalizes to 999999 plus overflow
- Elapsed time measurements from .01 to 9999.99 seconds plus overflow
- One-megohm input resistance
- Bright .43" high LED readouts

Call For Our Price

We carry a full line of multimeters, oscilloscopes, frequency counters, audio and RF generators, power supplies and accessories.

Just call our Toll-Free number and one of our experts will answer all your questions about test equipment.

**BK PRECISION**

**HITACHI**


**FLUKE**

**VIZ** formerly **ROA**

**HICKOK**

**DATA PRECISION**

**DORIC**

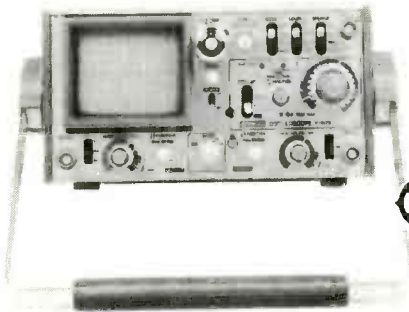

**NEW —  
NOW  
AVAILABLE**

**HITACHI**

V209 20 MHz, Dual Trace, Portable,  
Complete with built-in Battery Pack.

V509 50 MHz, Dual Trace, Dual  
Time Base, Portable (Battery pack  
optional).




**FULL LINE OF THE NEW  
B&K POWER SUPPLIES.  
CALL FOR OUR PRICES.**

**HITACHI**

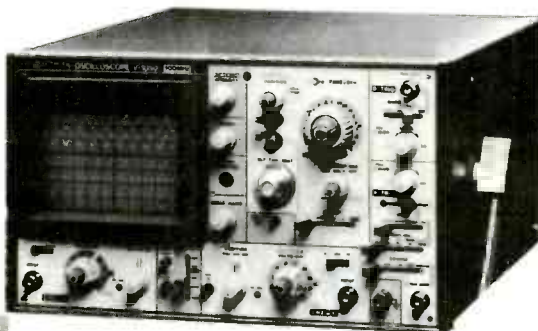**SAVE UP TO \$800**

- V-151B 15 MHz Single Trace
- V-152B 15 MHz Dual Trace
- V-202 20 MHz Dual Trace
- V-301 30 MHz Single Trace
- V-302B 30 MHz Dual Trace
- V-352 35 MHz Dual Trace
- V-550B 50 MHz Dual Trace,  
Dual Time Base
- V-1050 100 MHz Dual Trace,  
Dual Time Base



**Call For  
Special  
REBATE OFFER**

**PORTABLE  
OSCILLOSCOPES**  
BATTERY OPERATED

**NLS** Non-Linear Systems

**Call For Our Prices**

**MS-15**



Single Trace 15MHz

**MS-215**



Dual Trace 15 MHz

**MS-230**



Dual Trace 30MHz

**KEITHLEY**

**Model 169  
BENCH/PORTABLE DMM**

- 3½ Digit liquid crystal display
- 0.25% basic accuracy
- 26 Ranges

**\$189.00**



**New Sweep/Function Generator**

**BK PRECISION**

**MODEL 3020**

- Four instruments in one package—sweep generator, function generator, pulse generator, tone-burst generator.
- Covers 0.02Hz-2MHz
- 1000: 1 tuning range
- Low-distortion high-accuracy outputs



**Call For Our Price**

- Three-step attenuator plus vernier control
- Internal linear and log sweeps
- Tone-burst output is front-panel or externally programmable



**TOLL FREE HOT LINE  
800-223-0474**

**THE TEST EQUIPMENT SPECIALISTS**

54 WEST 45th STREET, NEW YORK, N.Y. 10036 212-687-2224

**ADVANCE  
ELECTRONICS**

## EQUIPMENT REPORTS

continued from page 26

the top of the scope screen for easy reading. Pushbuttons are used for ease of operation. You can read the peak-to-peak voltage of any waveform on the screen and then simply push a button and read the DC level in the circuit (more on that later), or push another button and read the frequency of the displayed signal.

All of the circuitry of the *model SC61*, aside from the manual scope controls, is microprocessor-controlled. That microprocessor monitors the vertical and hori-

zontal circuits at all times; to make any kind of measurement, just push a button and the microprocessor does the rest. It controls the digital readout, and also "lights" one of the 12 display annunciators that tell you what you're reading, and where (which channel). The decimal point is automatically set for all ranges and functions.

Getting back to the scope, the TIME-BASE-FREQ switch controls the horizontal sweep. That switch has 19 calibrated ranges. Those are set up in the usual 1-2-5 sequence and range from 0.1 microsecond to 100 milliseconds; a frequency scale is also provided. That switch is also used to place the unit in the video-preset


mode that is used to analyze video signals. In the video-preset mode, pushing one of two buttons will display either two vertical fields or two horizontal lines. The sync here is very steady due to the use of special sync-separators. The horizontal position control positions the trace; pull the knob and the waveform is expanded 10 times. While you could take an analog reading of time or frequency from the sweep-setting and the graticule, if you want to, it is much easier and faster to use the frequency readout for that, and the readings will be much more accurate. The readout is not affected by the setting of the timebase switch, whether you display one cycle, or several, the frequency will be picked off and read out by the microprocessor.

The sweep trigger circuits can be used on either channel, the AC line, or external trigger. A LEVEL control selects triggering on either positive- or negative-going edges of the displayed signal. When analyzing video signals, the peak-to-peak voltage of either horizontal or vertical waveforms can be measured by adjusting the LEVEL control. One thing that can cause problems in horizontal waveforms is the presence of some of the vertical sync; that also can be eliminated by adjusting the LEVEL control. The presence of the vertical sync can confuse the microprocessor, which will throw the peak-to-peak voltage readings off.

The unit has special sync-separator circuitry that helps in eliminating that confusion. That circuitry triggers on the vertical or horizontal pulses present in almost all TV signals. However, the manual mentions that if you're trying to read the output of a stage like the color-bandpass amplifier, where sync pulses are removed by the filtering action of the circuits, you may have instability. To eliminate that problem, simply hook the probe of the other channel to some point that does have sync, such as the video-detector output, etc. Now, trigger the sweep with the pulses from that channel.

Every one of the tests mentioned, as well as others we'll look at later on, can be done by just hooking up a probe and a ground lead. When that is done, just about anything about the circuit can be measured simply by pushing the appropriate buttons. Incidentally, while two of the probes supplied look like the standard hook-tipped probes, they are not. They are, instead, 10:1 low-capacitance probes; each has a special "separator" circuit built into it. That circuit lets you read waveforms and DC voltages at the same time! A separate, isolated, DC connector on the probe is plugged into a jack labeled DCV. The DC component is picked off by that separator circuit before the scope input and fed to the microprocessor, which does the rest. Because of that, both the reading displayed on the meter and the trace displayed on the scope are correct.
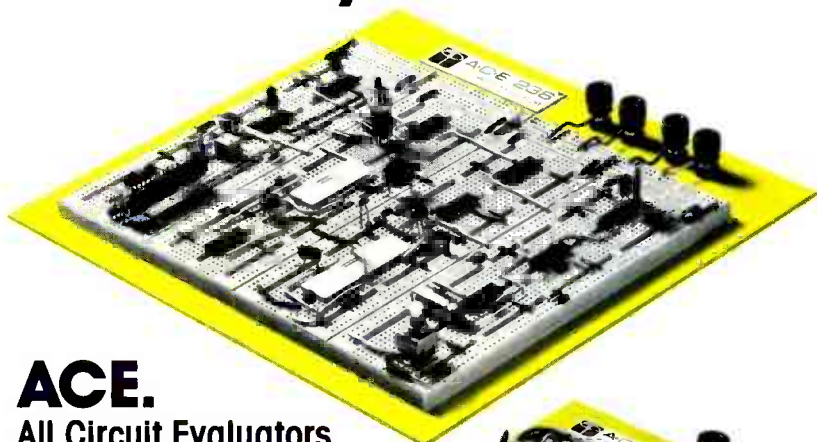
# You've seen the rest... now try the best.



## ACE.

### All Circuit Evaluators for solderless circuit building and testing.

A P made the first solderless breadboard way back in 1968, and we still make them best. Because our experience taught us to avoid the pitfalls that can mean circuit errors. We do it by paying attention to details. Like using noncorrosive nickel-silver in our frankly superior terminals. And like sealing each contact cell with an adhesive-coated polyethylene foam that prevents short circuiting. That's why you can count on the reliability of our solderless boards when you specify any one of the 7 different ACE models that offer from 728 to 3648 tie points, and 2 to 36 buses.

A P made the first modern solderless breadboard, and we still make the best.

**Call Toll Free 800-321-9668 for the name of the distributor nearest you. In Ohio, call collect (216) 354-2101.**



A P PRODUCTS INCORPORATED  
9450 Pineneedle Drive  
P.O. Box 603  
Mentor, Ohio 44060  
(216) 354-2101  
TWX: 810-425-2250

In Europe, contact A P PRODUCTS GmbH Baeumlesweg 21 • D-7031 Weil 1 • W. Germany

CIRCLE 26 ON FREE INFORMATION CARD

[www.americanradiohistory.com](http://www.americanradiohistory.com)

# INSTANT PC BOARDS


WITH

**E-Z CIRCUIT™** Pressure-Sensitive  
by **Bishop Graphics, Inc.**


## COPPER DESIGN PRODUCTS!

**NO Artwork! NO Photography! NO Screening! NO Etching!**


**And It's As Easy As 1...2...3...**

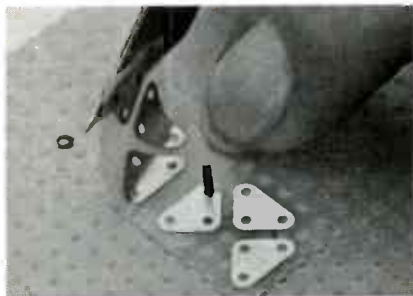

**1. APPLY COPPER MTG. CONFIGURATIONS**

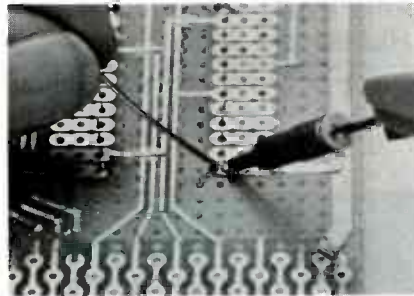

**2. SOLDER COMPONENT CONNECTIONS**

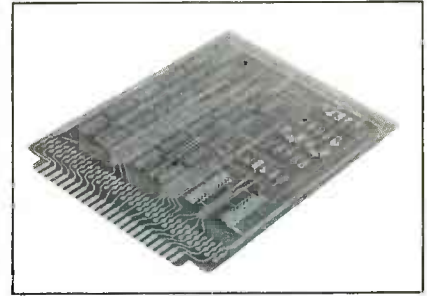

**3. IT'S READY TO USE!**


Now, thanks to this revolutionary new E-Z CIRCUIT concept, you can build professional quality printed circuit boards right in your own home or shop

- ... **without messy chemicals**
- ... **without artwork**
- ... **without photography**
- ... **without screening or etching**

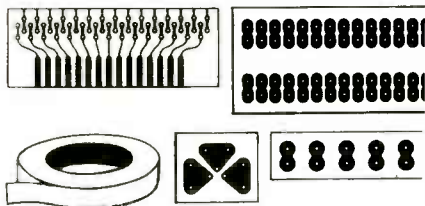**Read What RADIO-ELECTRONICS Hobby Editor, "Doc" Savage Says About the E-Z CIRCUIT System!**

"Those patterns are not for making artwork — they are *copper*. When you have pressed them down on a board, you are ready to mount the circuit components, solder them in place and turn on the power! *That* is what I call instant PC boards."

"Having used this E-Z CIRCUIT system, I can report that it is quick, easy and reliable. It is the best way I have found to make one or two-of-a-kind PC boards."



**The Secret? E-Z CIRCUIT's Unique Pressure-Sensitive COPPER Tapes & Patterns!**

Each E-Z CIRCUIT copper mounting configuration is made of super-thin, epoxy

glass with a special two-phase, adhesive on one side, and a one-ounce copper pattern laminated on the other. When applied to your PC board, these copper patterns work like the circuitry on a conventional *etched* printed circuit board. You solder the components directly to them.

**Make A Mistake? With E-Z CIRCUIT, You Won't Waste A Board!**

Thanks to E-Z CIRCUIT's special, two-phase adhesive, you have — within the first few minutes — the opportunity to reposition the copper patterns and tapes to make corrections, modifications and improvements ... *without* harming the appearance and performance of your board.




**Use Them For Repairing And Modifying Existing Circuitry, Too!**

Besides creating an actual, professional functioning circuit board, you can use E-Z CIRCUIT Pressure-Sensitive Copper PC design products to repair or modify existing circuitry.

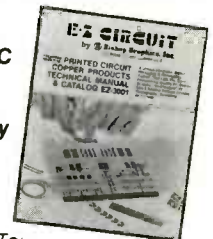**Unique E-Z CIRCUIT Technical Manual ... A "Gold Mine" of Usable, "How To" Information!**

We even show you how easy it is. The new E-Z CIRCUIT PC Copper Products Technical Manual & Catalog EZ-3001 leads you through every step with fully illustrated instructions written in clear, simple language to make it easy for you to produce a professional quality, PC board. It's packed with invaluable technical "How To" information that tells you:

- **How to build a PC board**
- **How to repair damaged circuitry**
- **How to solder professionally**



Send For Your **FREE Copy Today To:**

**E-Z CIRCUIT™**  
by **Bishop Graphics, Inc.**

P.O. Box 5007RE Westlake Village, CA 91359

Please send me a free copy of  
**E-Z CIRCUIT PC Copper Products  
Technical Manual & Catalog EZ-3001**

Name \_\_\_\_\_  
Street \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_  
(DEALER INQUIRIES WELCOME)

CIRCLE 10 ON FREE INFORMATION CARD

The scope settings, as we said before, do not affect the meter readings in any way. In addition to the 10:1 low-capacitance probes, the unit is also supplied with a direct-reading DC probe and a 48-inch-long ground lead.

Among the features that sets this unit apart is its special delayed sweep mode that is called the delta-measurement mode. That mode lets you measure the peak-to-peak voltage, frequency, or period of only the section of the waveform that you are interested in. It can be set for any portion of the waveform using the  $\Delta$ BEGIN and the  $\Delta$ END controls. Those controls position the beginning and end of a bright "bar" on the display. The part of

the waveform within the span of that bar is the only part that is measured when the scope is in the delta mode. Trigger controls work in the usual manner in that mode.

Among other things, the delta mode is useful for reading the frequency of only one cycle. If you have more than one frequency present, such as with a modulated waveform, you can read any one by isolating that part of the waveform within the delta bar.

To try out the delta mode, we used it to troubleshoot a DC supply in a solid-state television set. That supply's output waveform showed some unusual symptoms, but ones that were obviously caused by

feedback. On what should have been a clean DC signal, we found tiny high-frequency "bursts;" the frequency of those bursts turned out to be about 40 kHz, the ringing frequency of the flyback pulse. As the DC supply came from the flyback, that seemed to indicate that the DC supply was not adequately filtered. From that point it was relatively easy to track the problem down to an open filter capacitor in the DC line; that open capacitor was allowing the ringing to get into the signal circuits.

This instrument is a real pleasure to use. All the controls are grouped by function and channel for maximum efficiency. The built-in digital display eliminates the need for graticule counting, allowing you to analyze a waveform quicker, and more accurately, than ever before. All this sophistication comes at a price, of course, as the *model SC61* lists for \$3275.00, including probes. However, if you do a lot of work with a scope, and consider the time and eye strain this instrument will save you, the price is well worth it. **R-E**

**ADVANCE IS PROUD TO INTRODUCE the KEITHLEY Line of High Quality Digital Multimeters Featuring The New 130 Hand-Held DMM**

Keithley handheld DMMs keep you right on top of your field service applications. They're rugged, offer complete capabilities, are easy to use and won't break your budget.



**Model 128:** Beeper DMM designed to meet the tough specifications of a major computer manufacturer. See/hear display includes over/under arrow and on/off beeper.

**Model 131:** 0.25% accuracy added to the easiest to use handheld DMM. Color-coded front panels for maximum clarity, minimum confusion.

Model 128: \$139.00  
Model 130: \$124.00

**Model 130:** Keithley user research led to unique DMM designs. Easy to read LCDs, largest DMM displays on the market.

**Model 135:** First 4 1/2-digit handheld DMM, ideal for analytical/bio-medical service. 10A range standard on all Keithley handhelds.

Model 131: \$139.00  
Model 135: \$235.00

A full line of accessories expands these values even further.

**McKay/Dymek General Coverage Receiving System**



CIRCLE 107 ON FREE INFORMATION CARD

| McKay/Dymek        |  | DR-44-6 |   |      |   |   |      |   |   |           |    |  |  |  |
|--------------------|--|---------|---|------|---|---|------|---|---|-----------|----|--|--|--|
| OVERALL PRICE      |  |         |   |      |   |   |      |   |   |           |    |  |  |  |
| EASE OF USE        |  |         |   |      |   |   |      |   |   |           |    |  |  |  |
| INSTRUCTION MANUAL |  |         |   |      |   |   |      |   |   |           |    |  |  |  |
| PRICE/VALUE        |  |         |   |      |   |   |      |   |   |           |    |  |  |  |
|                    |  | 1       | 2 | 3    | 4 | 5 | 6    | 7 | 8 | 9         | 10 |  |  |  |
|                    |  | Poor    |   | Fair |   |   | Good |   |   | Excellent |    |  |  |  |

ALTHOUGH A LARGE PERCENTAGE OF McKay/Dymek (Post Office Box 5000, Department B, Claremont, CA 91711) products are for shipboard use on vessels of foreign registry, many items in their catalog are of interest to serious short-wave/longwave listeners as well. One such system consists of the DR44-6 receiver (shown), the DP4044 preselector, and the DS111 audio processing speaker. We'll look at each one of those individually, with the main emphasis on the DR44-6 receiver.

**The DR44-6 receiver**

Designed to fit in a standard 19-inch rack-panel mount, the *model DR44-6* is a

**THE TEST EQUIPMENT SPECIALISTS**  
TOLL FREE HOT LINE  
**800-223-0474**  
54 WEST 45th STREET, NEW YORK, N.Y. 10036 212-687-2224

**ADVANCE ELECTRONICS**




# When you need a semiconductor that fits and works, turn to the Master.


You can search high and low for some replacement parts. Or you can turn to the Master—the Sylvania ECG® Semiconductor Master Replacement Guide.

It's called the Master because it's far and away the industry's most comprehensive source for getting the parts you need, when you need them. Including most hard-to-find foreign parts. And ECG universal replacement part specifications generally exceed the original JEDEC or application specs.

Not surprisingly, the Master comes from the people who first mastered the universal replacement principle—a system that allows a minimum number of premium quality replacement devices to replace almost every original equipment semiconductor on the market.

With the Master working for you, there is no need to turn elsewhere for replacement semiconductors.

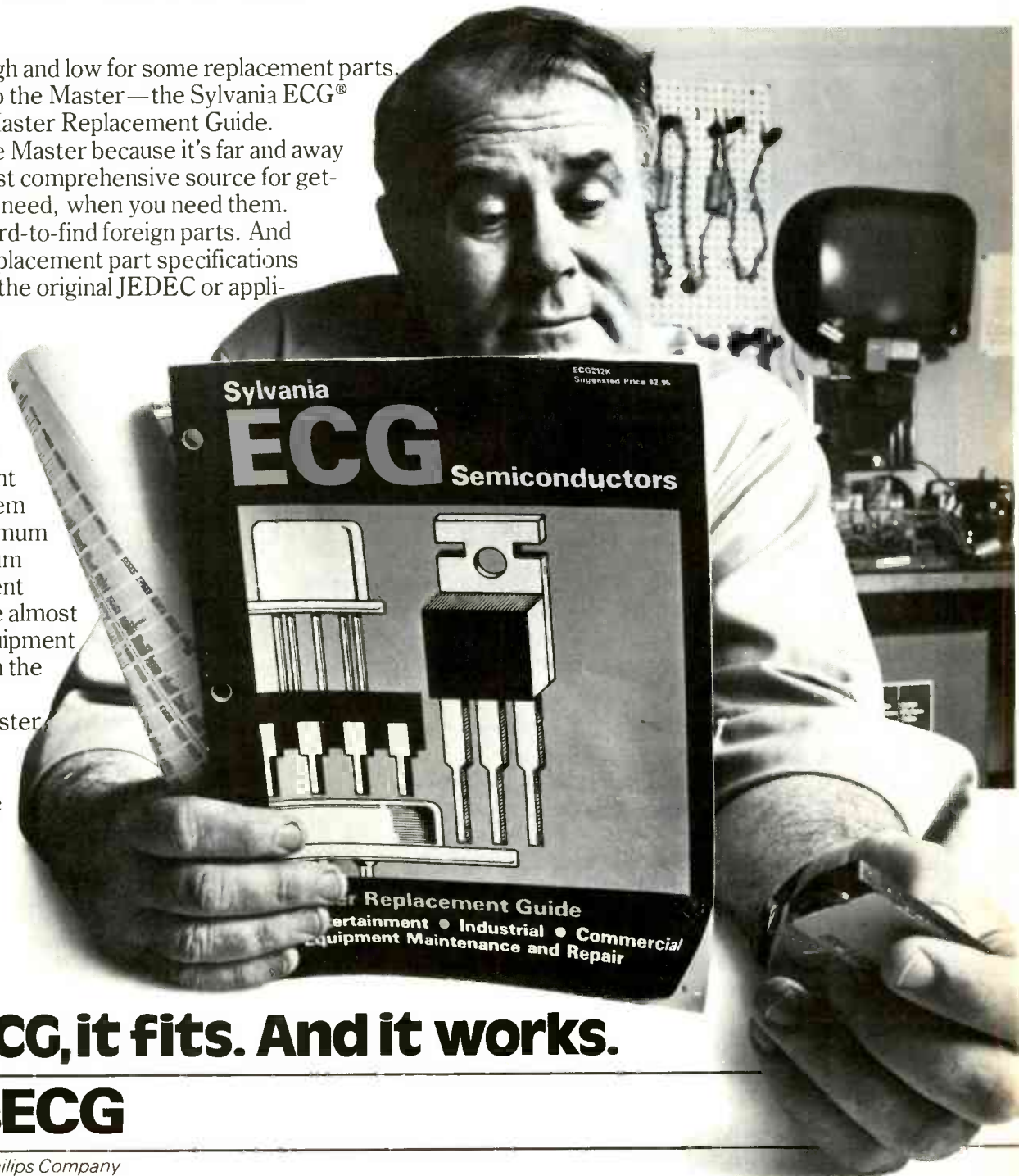For your nearest ECG distributor, call 1-800-225-8326.



**If it's ECG, it fits. And it works.**

**Philips ECG**

*A North American Philips Company*

general-coverage frequency-synthesized receiver that displays the received frequency on six large (0.5 inch) LED characters with an accuracy of 100 Hz.

The rear panel features a variety of connectors for increased flexibility in custom installations. Those include a high-impedance audio output with an associated level control, a mute jack, a 50-ohm BNC antenna connector, a low-impedance speaker output and a separate 600-ohm line output (both available from spring-loaded terminals), and an IF output (455 kHz) for a panoramic display or teletype converter.

Receiving modes include AM, SSB, CW, and RTTY. A separate rotary switch

allows selection of either 4- or 8-kHz bandwidth filtering of the upper/lower sidebands. Two additional unoccupied positions can accommodate the installation of optional filters by the user.

A noise-limiter circuit provides attenuation of pulse-type interference on any mode except AM. The AGC decay rates (fast or slow) may be selected or defeated entirely.

Frequency is selected through the combined use of 5 rotary controls, each adding or subtracting a frequency interval on the display (10 MHz, 1 MHz, 100 kHz, 5 kHz). The 5th control is variable, providing infinite resolution of the last 5 kHz.

Frequency displacement on upper and

lower sidebands is compensated in the readout so that the user will see the actual window frequency (suppressed carrier) without the mental gymnastics frequently necessary with other receivers.

### Our lab tests

The *DR44-6* was used with a 135-foot dipole antenna and in conjunction with its companion *DP4044* preselector.

We found little advantage in using the preselector for the vast majority of applications; the preselector would best be used when there is a nearby source of strong RF interference.

Thermal and mechanical stability of the receiver were excellent. Little or no frequency drift was observed during reasonable periods of listening time after initial warmup. Frequency coverage for the *DR44-6* is specified as 50 kHz through 29.7 MHz. Actual reception over that frequency range was confirmed.

RF sensitivity was excellent, certainly equivalent to or greater than that of most competitors.

"Birdies" are spurious signals caused by the frequency synthesizer. They are always present on receivers that use a frequency synthesizer to generate the local oscillator signal. While also present on the *DR44-6*, none was found too loud to detract from the readability of incoming radio signals. Two extremely loud birdies appeared to have been generated by the BFO, and were heard on 10 and 20 MHz; but those two frequencies are occupied by full-carrier WWV, and they disappeared in the AM mode.

Image rejection is specified as 70 dB, and in our lab tests images were certainly no problem. Additional specifications include cross-modulation and intermodulation suppression of 65 dB (referred to 1 microvolt) and RF blocking of 100 dB (also referred to 1 microvolt). A 25-dB 5-kHz audio-notch filter removes any heterodyne interference from adjacent channel broadcasts.

A 2-MHz high-pass filter provides useful suppression of interfering signals from the AM broadcast bands and below when the receiver is being used only for shortwave reception. RF signal attenuation may be used to reduce overload from strong signals.

Two watts of audio output into a 4-ohm load impedance is available at the rear panel as well as a 1-volt RMS line output (5,000-ohms impedance). AC power required is 120 or 240 volts, 50/60 Hz (30 watts).

The internal circuitry is very clean and well laid out, featuring 56 IC's, 31 FET's, 20 transistors, and 66 diodes.

The accompanying instruction manual is well written and comprehensive, presenting descriptions of each portion of the receiver's circuitry, including both component layout and schematic drawings.

*continued on page 104*

## PRINT THE WORLD



### See What You've Been Missing!

Stay in touch with world events, monitor weather, ship traffic, and radio amateurs. Connect to your receiver and display shortwave radio teleprinter and Morse code transmissions with the new receive-only **HAL CWR-6700 Telereader**.

- Receive ASCII or Baudot RTTY
- Six standard RTTY speeds
- 3 RTTY shifts for low or high tones
- Adjustable space for fine tuning
- Receive Morse code — 4 to 50 wpm
- 16 lines by 36 or 72 character display
- Two page video display
- Parallel ASCII printer output
- Requires +12 VDC and external TV monitor
- One year limited warranty
- Small size (8" x 3" x 12.75")

Write or call for more details. See the CWR-6700 at your favorite HAL dealer.



**HAL COMMUNICATIONS CORP.**

BOX 365


URBANA, ILLINOIS 61801

217-367-7373




# Modular Components... The Soldering Choice is Yours
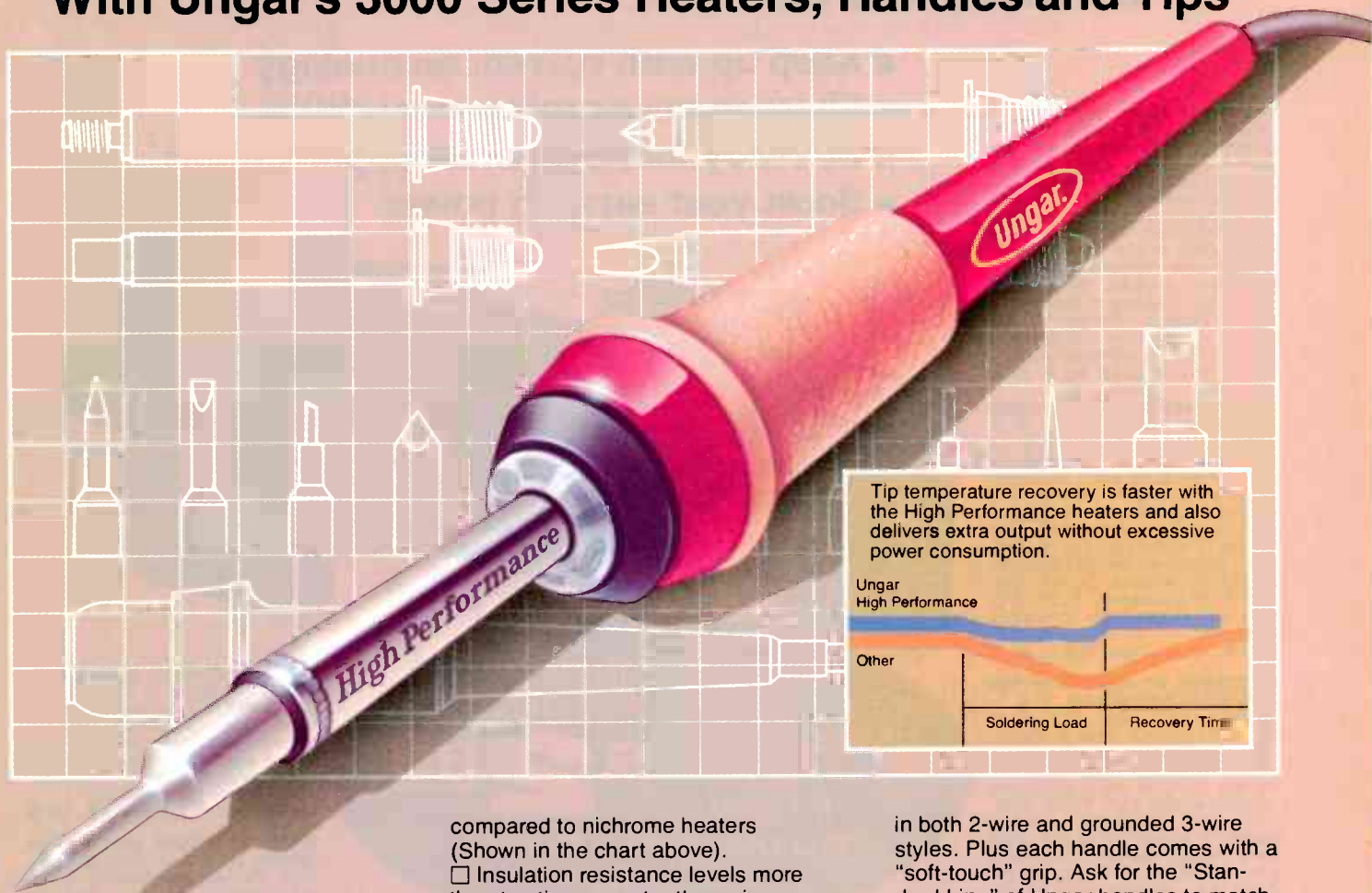
## With Ungar's 3000 Series Heaters, Handles and Tips



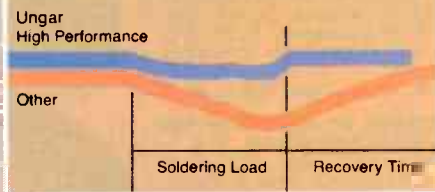Tip temperature recovery is faster with the High Performance heaters and also delivers extra output without excessive power consumption.



When it comes to making a choice, Ungar gives you lots to choose from. We have one of the broadest lines of soldering components available to precisely meet your needs.

Take our lineup of heaters, handles and tips, for example. We've got you covered with a variety of heat ranges and tips so you can custom-design the soldering iron to fulfill your requirements.

### 15 NEW THERMO-DURIC™ HIGH PERFORMANCE HEATERS

Our 3000 Series heaters are the state-of-the-art in soldering today. Their improved performance is thanks to modern "thick film" technology, which has allowed the design of our exclusive, revolutionary THERMO-DURIC™ heater element.

The benefits include:

- Faster heat-up—typically 1.5 minutes vs. 2.5 minutes.
- Quicker temperature recovery

compared to nichrome heaters (Shown in the chart above).

- Insulation resistance levels more than ten times greater than wire-wound elements. This means significant reduction in leakage currents that can damage sensitive micro-electronics.
  - Lower power consumption—our 50 watt heater outperforms a conventional 80 watt iron.
  - Less energy consumed at no-load idle temperatures—typically 15% less!
  - Better results with thread-in and thread-on tips.
- And that's not all!

You can choose from a wide selection of body styles. Ranging from integral tip models to the thread-in and thread-on styles. Plus each style is available in wattage ratings to cover soldering temperatures from approximately 700°F to 1,000°F.

### HANDLES—WE OFFER YOU THREE CHOICES

To complement our 3000 Series heaters, we have three handles. They are perfectly balanced for added comfort and reduced fatigue. They're available

in both 2-wire and grounded 3-wire styles. Plus each handle comes with a "soft-touch" grip. Ask for the "Standard Line" of Ungar handles to match up with the ultimate in heaters, the 3000 series!

### SELECT FROM 15 TIPS

No matter your requirements, we've got the tip for you! Available in both thread-in and thread-on styles to mate with our 3000 Series heaters.

### AND IT'S ALL MODULAR!

That's the beauty of the Ungar system. Every piece is modular, so if one unit wears, instead of buying a totally new soldering iron—simply replace that one component. Fast, Easy, and Economical. You have unparalleled flexibility to combine handle, heater and tips to create any one of 234 custom irons.

To find out more about this amazing lineup from Ungar, call the Ungar Hotline, toll-free 1-800-421-1538, in California, call collect, 1-213-774-5950.



Division of Eldon Industries,  
Compton, California-90220  
In Canada, Markham,  
Ontario, Canada L3R 1H5

# Professional Books That Help You Get Ahead—And Stay Ahead!

## Join the **Electronics and Control Engineers' Book Club** and...

- Keep up with current technology
- Sharpen your professional skills
- Be ready for new career opportunities
- Boost your earning power


**INTUITIVE IC ELECTRONICS: A Sophisticated Primer for Engineers and Technicians.** By T. M. Frederiksen. 208 pp., illus. Covering both the simplest and the most complicated IC designs, this lively, easy-to-read volume provides a sophisticated, nonmathematical explanation of the basic internal mechanisms common to all semiconductor devices. Gives you a solid understanding of devices like MOS transistors, the new I<sup>2</sup>L designs, the bipolar digital logic families, JFETs, and much more. 219/230 Pub. Pr., \$18.50 Club Pr., \$14.50

**MICROPROCESSOR APPLICATIONS HANDBOOK.** Editor-in Chief, D. F. Stout. 472 pp., 284 illus. At last—a reference guide to microprocessor applications to help you make your systems timely, versatile, and cost-effective. Emphasizing applications that are immediately useful, the 16 experts provide in-depth treatments of each topic so you can completely analyze, design, construct, and program. Both hardware and software are thoroughly discussed. 617/988 Pub. Pr., \$35.00 Club Pr., \$26.50

**HANDBOOK OF SEMICONDUCTOR AND BUBBLE MEMORIES.** By W. A. Triebel and A. D. Chu. 416 pp., illus., over 50 worked-out problems. This detailed, comprehensive guide brings you right up to the minute on such newly developed devices as the PLA, FIFO, CAM, CCD, and magnetic bubble memory—as well as all the standard storage devices from ROMs and RAMs to shift registers. Analyzes, categorizes, and explains in full working detail more than 75 different semiconductor ICs and MBM devices. 582376-4 Pub. Pr., \$24.95 Club Pr., \$18.50

**PCM AND DIGITAL TRANSMISSION SYSTEMS.** By R. Owen. 320 pp., 186 illus. This useful volume arranges the latest thinking in pulse code modulation (PCM) and digital transmission technology into a logical, step-by-step format. The result is a book which allows newcomers to this field to familiarize themselves with its problems and equipment in two weeks, instead of the three months it would ordinarily take. 479/542 Pub. Pr., \$30.00 Club Pr., \$23.50

**MAGNETIC CORE SELECTION FOR TRANSFORMERS AND INDUCTORS: A User's Guide to Practice and Specifications.** By W. T. McLyman. 768 pp., 400 illus. This giant volume is brimming with time-saving tips, plus tables to help you select the right magnetic core for virtually any application. The book instantly gives you everything from strip width to window length to iron weight to the area product. Sixteen different variables are provided, all in standard units of measurement for ease of comparison, and data are provided for more than 6,000 different cores. 582494-9 Pub. Pr., \$65.00 Club Pr., \$45.00

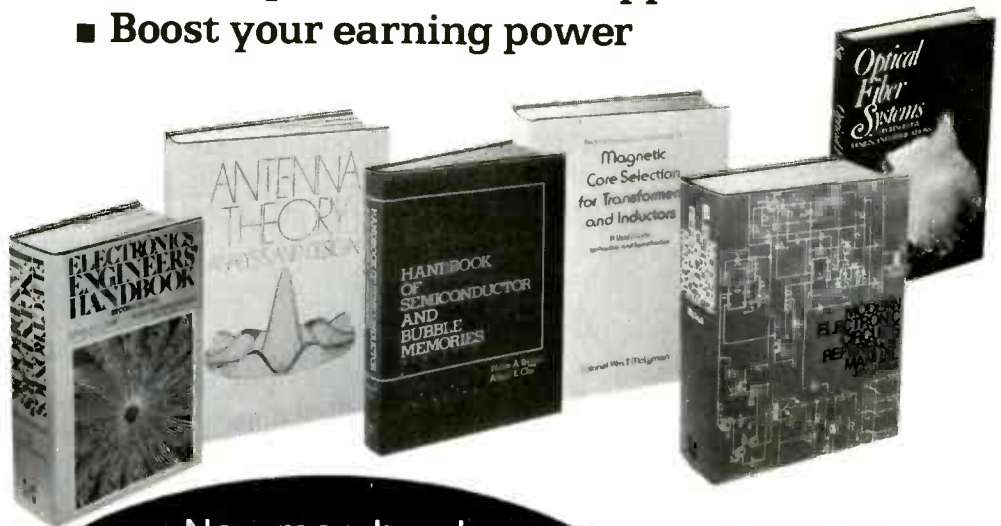

New members!  
Any one of these great  
professional books  
for only **\$289**  
as a premium with your  
1st selection!

Spectacular values up to **\$75.00**

**OPTICAL FIBER SYSTEMS: Technology, Design, and Applications.** By C. K. Kao. 197 pp., illus. From a basic explanation of optical fiber systems to the economic ramifications of their use, this volume provides full coverage of a rapidly changing field. The working engineer will find this a valuable source of both data and design concepts—and newcomers will appreciate its step-by-step explanation of component technology, and design processes. 332/770 Pub. Pr., \$23.50 Club Pr., \$17.95

**ELECTRONICS ENGINEERS' HANDBOOK.** Edited by D. O. Fink; D. Christiansen, Associate Editor. 2nd Ed., 2,272 pp., 2,189 illus., 43 photos. The leading electronics reference work is now totally revised and updated to cover the latest developments in the field. Its 28 giant sections cover everything from basic principles, materials, devices, and components to electronic circuits and their functions and electronic systems and applications. 209/812 Pub. Pr., \$75.00 Club Pr., \$57.50

**ELECTRONICS CIRCUITS NOTE BOOK: Proven Designs for Systems Applications.** By S. Weber, Editor in Chief. 344 pp., illus. Containing 268 ready-to-use or adapt circuits—each a proven solution—this book brings you the best of the best articles published in *Electronics'* popular Designer's Casebook section. Covers display circuits, encoders and decoders, filters, function generators, logic and memory circuits, microprocessors, and more. 192/448 Pub. Pr., \$32.50 Club Pr., \$25.50

**RADIO HANDBOOK.** By W. Orr. 22nd Ed., 1,136 pp., more than 1,300 illus. Here's the latest edition of what is universally regarded as the most useful reference in the industry. All the newest technology is explained and illustrated, and there's a wealth of data about receivers, transmitters, antennas, and auxiliary equipment of every description. It's a "course" in communications, a fact-packed reference, and a how-to guide—all in a single book! 582442-6 Pub. Pr., \$39.95 Club Pr., \$33.95

**INTRODUCTION TO RADAR SYSTEMS, 2/e.** By M. I. Skolnik. 698 pp., 244 illus. This new edition of a widely used text on radar from the systems engineer's point of view brings you full discussions of the many major changes that have occurred in the field recently. 579/091 Pub. Pr., \$38.50 Club Pr., \$30.50

**ANTENNA THEORY: Analysis and Design.** By C. A. Balanis. 816 pp., illus. Packed with equations, design procedures, and plenty of nuts-and-bolts know-how, this is the first place to turn for answers to all your antenna design questions. But it's much more than a valuable on-the-job reference. It's a complete A-to-Z course in antenna design for those who are new to the field. 582493-0 Pub. Pr., \$39.50 Club Pr., \$29.95

**RADAR TRANSMITTERS.** By G. W. Ewell. 252 pp., 211 illus. This all-around reference provides complete, up-to-date details on device capabilities and design procedures—with plenty of specific design examples. Helps you know your radar transmitter capabilities inside out—brings you abreast of latest design techniques to improve your designs—cuts your design time in half! 198/438 Pub. Pr., \$24.50 Club Pr., \$18.50

**MODERN ELECTRONIC CIRCUITS REFERENCE MANUAL.** By J. Markus. 1,264 pp., 3,666 circuit diagrams. This 103-chapter guide means you can speed up the production of new electronic devices with ease and thereby lower your production costs. Complete with values of components and suggestions for revisions, plus the original source of each circuit in case you want additional performance or construction details. 404/461 Pub. Pr., \$61.50 Club Pr., \$48.50

**McGraw-Hill's NATIONAL ELECTRICAL CODE® HANDBOOK, 17/e.** By J. F. McPartland. 1,162 pp., 1,096 illus. Bigger and better than ever! This mammoth reference explains and clarifies the many complex provisions of the current (1981) Code\* to help you meet rules exactly and pass inspections the very first time.

456/933 Pub. Pr., \$26.50 Club Pr., \$20.50

**DIGITAL HARDWARE DESIGN** By J. B. Peatman. 428 pp., over 400 illus. Taking you beyond the microcomputer, this guide re-examines traditional techniques and focuses maintainability as a key goal, on the design of circuitry too fast for the microcomputer alone, and on designing for usefulness. It covers everything from algorithmic state machines to separately clocked circuits—with scores of examples.

491/321 Pub. Pr., \$33.00 Club Pr., \$26.00

**INTRODUCTION TO THE THEORY AND DESIGN OF ACTIVE FILTERS.**

By L. P. Huelsman and P. E. Allen. 430 pp., illus. Once you add active filter design to your repertoire of specialties, you'll possess a skill that's in great demand today. Here's one of the best texts we know on the theory, design, application, and evaluation of modern active filters and the various techniques used today.

308/543 Pub. Pr., \$32.50 Club Pr., \$25.50

**ELECTRONICS ENGINEERING FOR PROFESSIONAL ENGINEERS' EXAMINATIONS.**

By C. R. Hafer. 336 pp., more than 200 illus. Actually two books in one—a quick preparation manual to help you pass your P.E. exams on the first try and a rich source of practical electronics engineering information and know-how.

254/303 Pub. Pr., \$24.75 Club Pr., \$19.50

**ELECTRONIC COMMUNICATION, 4/e.**

By R. L. Shrader. 801 pp., 870 illus. This thoroughly updated edition offers all the theory and fundamentals you need to prepare yourself for the FCC commercial and amateur grade license examinations—and pass them the first time!

571/503 Pub. Pr., \$24.10 Club Pr., \$18.95

**STANDARD HANDBOOK FOR ELECTRICAL ENGINEERS, 11/e.**

By D. G. Fink and H. Beaty. 2,448 pp., 1,414 illus. Today's most widely used source of electrical engineering information and data serves you as no other single work when you need detailed, timely, and reliable facts and how-to on the generation, transmission, distribution, control, conversion, and application of electric power.

209/74X Pub. Pr., \$65.95 Club Pr., \$48.95

**DIGITAL CIRCUITS AND MICROPROCESSORS.**

By H. Taub. 608 pp., heavily illus. This fast-paced, carefully written guide gives you thorough explanations of all the basic principles of digital systems and logic design—plus a solid introduction to microprocessors and microprocessor-based designs. Anticipates every conceivable question you could have to make sure you understand every detail.

629/455 Pub. Pr., \$29.95 Club Pr., \$23.50

**Be sure to consider these important titles as well!**

**USER'S GUIDEBOOK OF DIGITAL CMOS INTEGRATED CIRCUITS.** By E. R. Hnatek.

290/679 Pub. Pr., \$26.90 Club Pr., \$20.50

**DESIGNING WITH FIELD-EFFECT TRANSISTORS.** By Siliconix, Inc.

574/499 Pub. Pr., \$26.90 Club Pr., \$20.50

**BIT-SLICE MICROPROCESSOR DESIGN.** By J. Mick & J. Brick.

417/814 Pub. Pr., \$26.50 Club Pr., \$20.50

**MICROPROCESSORS/MICROCOMPUTERS/SYSTEM DESIGN.** By Texas Instruments Learning Center & Engineering Staff.

637/58X Pub. Pr., \$26.95 Club Pr., \$20.95

**ENGINEERING MATHEMATICS HANDBOOK, 2/e.** By J. J. Tuma.

654/298 Pub. Pr., \$29.50 Club Pr., \$22.95

**HANDBOOK OF OPERATIONAL AMPLIFIER CIRCUIT DESIGN.** By D. E. Stout & M. Kaufman.

617/97X Pub. Pr., \$38.00 Club Pr., \$29.00

**OPTICAL FIBRE COMMUNICATION.** By Technical Staff of CSELT.

148/821 Pub. Pr., \$39.50 Club Pr., \$29.50

**ELECTRONIC FILTER DESIGN HANDBOOK.** By A. B. Williams.

704/309 Pub. Pr., \$37.50 Club Pr., \$28.50

**MICROCOMPUTER-BASED DESIGN.** By J. Peatman.

491/380 Pub. Pr., \$35.00 Club Pr., \$27.00

**MICROELECTRONICS.** By J. Millman.

423/27X Pub. Pr., \$34.00 Club Pr., \$26.50



**MAIL THIS COUPON TODAY**

McGraw-Hill Book Clubs  
**Electronics and Control Engineers' Book Club**  
 P.O. Box 582, Hightstown, New Jersey 08520

Please enroll me as a member and send me the two books indicated, billing me for the \$2.89 premium and my first selection at the discounted member's price, plus local tax, shipping, and handling charges. I agree to purchase a minimum of two additional books during my first year of membership as outlined under the Club plan described in this ad. A shipping and handling charge is added to all shipments.

Write Code No. of \$2.89 selection here

Write Code No. of first selection here



Signature \_\_\_\_\_

Name \_\_\_\_\_

Address/Apt. # \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

This order subject to acceptance by McGraw-Hill. All prices subject to change without notice. Offer good only to new members. Orders from outside the U.S. cannot be accepted.

E33564

**Why YOU should join now!**

■ **BEST AND NEWEST BOOKS IN YOUR FIELD** — Books are selected from a wide range of publishers by expert editors and consultants to give you continuing access to the best and latest books in your field.

■ **BIG SAVINGS** — Build your library and save money too! Savings ranging up to 30% or more off publishers' list prices — usually 20% to 25%.

**BONUS BOOKS** — You will immediately begin to participate in our Bonus Book Plan that allows you savings of between 70% — 80% off the publishers' prices of many professional and general interest books!

■ **CONVENIENCE** — 12-14 times a year (about once every 3-4 weeks) you receive the Club Bulletin FREE. It fully describes the Main Selection and Alternate Selections. A dated Reply Card is included. If you want the Main Selection, you simply do nothing — it will be shipped automatically. If you want an Alternate Selection — or no book at all — you simply indicate it on the Reply Card and return it by the date specified. You will have at least 10 days to decide. If, because of late delivery of the Bulletin you receive a Main Selection you do not want, you may return it for credit at the Club's expense.

As a Club member you agree only to the purchase of three books (including your first selection) during your first year of membership. Membership may be discontinued by either you or the Club at any time after you have purchased the first selection plus two additional books. Orders from outside the U.S. cannot be accepted.

**Other McGraw-Hill Book Clubs:** Accountants' and Controllers' Book Club • Architects' Book Club • Chemical Engineers' Book Club • Civil Engineers' Book Club • Computer Professionals' Book Club • Mechanical Engineers' Book Club

For more information, write to:

McGraw-Hill Book Clubs, 26th fl., 1221 Avenue of the Americas, New York, NY 10020

# SATELLITE/TELETEXT NEWS

GARY ARLEN  
CONTRIBUTING EDITOR

## WIRELESS CABLE PLAN

*Urbanet*, a multi-channel microwave hybrid service that can be used for teletext, data transmission, pay-TV, and other entertainment services, is being proposed by Microband Corp. of America, the nation's largest operator of Multipoint Distribution Service (MDS) stations. Microband's proposal for "wireless cable" would create up to 14 video channels in the top 50 U.S. cities. The channels would operate in the 2500 MHz band, and would be first cousins of the MDS pay-TV services now offered in many markets in the 2160 MHz range. The *Urbanet* arrangement would accommodate national and local transmissions in a variety of modes: one-way, two-way, interactive, and asymmetrical. For example, the broadband MDS channel could be used to transmit video programming; an asymmetrical variation could be used to download video-games or for electronic mail.

For services requiring two-way or interactive capability, the telephone will be used in conjunction with value-added data communications networks. By augmenting current software and data-storage capabilities, services can be developed to handle teletext and home banking. The Microband plan comes in response to a long-simmering FCC study about reallocating the 2500 MHz band that is now underused as an educational TV band.

## HIGH- DEFINITION TV

High-definition television (HDTV), with 1125-line video resolution, stereo sound, wide-screen pictures, and other enhanced features, seems to be moving ever closer to reality—and satellite distribution will be a major factor in its development. CBS and Japanese-TV network NHK recently demonstrated their latest refinements of HDTV, along with a hint that the service could begin in less than five years on a limited basis. Because of its sizeable spectrum demands—about 30 MHz-per-channel (five times the bandwidth of conventional TV)—HDTV will probably be used for special purposes. Direct-broadcasting satellites (DBS), cable-TV, and home-videocassette/disc distribution are possible, because bandwidth limitations are not a problem as they are on current broadcast-TV systems. However, engineers are now working on bandwidth-compression systems to bring down the spectrum requirements for HDTV.

Satellite service is a high priority because a DBS transmission of a high-definition TV signal would offer theater-quality video projection. The 1125-line resolution will provide picture quality at least five times better than today's TV signal—richer colors, higher resolution, and better contrast. The 3 × 5 screen ratio (compared to today's 3 × 4 ratio) provides wide-screen capabilities. HDTV also offers Hollywood studios a new opportunity to produce movies directly as electronic cinema, rather than shoot on film and then transfer to videotape.

## TEXT VIA SATELLITE

Text and data services will be transmitted nationwide via subcarriers on National Public Radio's transponders aboard Westar starting late this year. The project is part of public radio's effort to find new financial sources to support its non-commercial audio programming. According to this plan, the national satellite feed will be transmitted in hundreds of communities by local public radio stations, again using subcarriers on their standard broadcast signals. In many cases, the local stations will also insert additional data aimed solely at receivers in their communities.

Data will be transmitted using an SCA (Subsidiary Channel Authorization) that is piggy-backed to an audio circuit. Each signal will carry an identifying code, and customers will be equipped with an addressable receiver to pick up the data. Customers would only be permitted to receive material designated for their specific decoder. Initially, most receiver locations would plug their decoders into hard-copy printers, but the data could also be displayed on a video screen.

A new organization, Information Network Corp. (INC) has been set up by NPR and a Washington-area company called National Information Utilities Corp. that will develop databases and services for the network, including videogames, shopping information, computer information, and business information. INC expects to deliver services almost entirely to business customers. The plan, however, is one of a growing number of projects seeking to piggy-back auxiliary services into the scarce satellite circuits.

R-E

# Moving up to Philips just moved down in price.

**Make your move today.  
To top quality professional  
test equipment—Philips.**

All over the world Philips produces the test that more people trust. That's because the same superior engineering and ergonomic principles that go into our over \$6000 digital storage scope can be found in our 15MHz scope and our super smart counters.

We put more into every scope and counter. More wanted features. More precision. More rock-solid

quality. So you get more. And now for a whole lot less!

Check our specs. Check our new low prices. Then check yourself into the world of professional testing—with Philips.

### Philips PM3207 Dual Trace Scope

- 15MHz/Dual Trace • Auto triggering
- Bright, clear CRT • 5mV sensitivity
- Same sensitivity X and Y
- B-Invert • Triggering from A or B
- TV triggering

### Super Smart Counters with seven digit high/low frequency readouts in one second!

- Microprocessor control • 120MHz or 1GHz frequency range
- Auto triggering on all waveforms
- High-contrast liquid crystal display
- High stability TCXO oscillator: 10<sup>-7</sup>/mth
- Line and battery options
- 15mV RMS sensitivity
- Self-test and self-diagnosis routine
- Easy operation through built-in intelligence

**PM6667  
120MHz  
High Resolution  
Counter  
\$430**

**PM3207  
15MHz Dual Trace  
Oscilloscope  
\$725**

**PM6668  
1GHz  
High Resolution  
Counter  
\$595**

## From Philips, of course.



**Test & Measuring  
Instruments**

**ORDER TOLL-FREE  
800-631-7172**  
Call now or mail coupon  
for further information

Send me spec sheets on the following:

- PM3207 15MHz/Dual Trace Oscilloscope  
 PM6667 120MHz High Resolution Counter  
 PM6668 1GHz High Resolution Counter

NAME: \_\_\_\_\_

STREET: \_\_\_\_\_

CITY: \_\_\_\_\_ STATE: \_\_\_\_\_ ZIP: \_\_\_\_\_

RE-09-2

## PHILIPS

For more information call 800-631-7172, except Hawaii, Alaska and New Jersey. In New Jersey call collect (201) 529-3800, or contact Philips Test & Measuring Instruments, Inc., 85 McKee Drive, Mahwah, NJ 07430. In Canada: 2375 Steeles Ave. W., Unit 126, Downsview, Ont., Can. M3J 3A8. (416) 665-8470.

CIRCLE 13 ON FREE INFORMATION CARD

[www.americanradiohistory.com](http://www.americanradiohistory.com)

# NEW IDEAS

## Electronic Thermometer

HERE IS AN INEXPENSIVE ELECTRONIC thermometer that can be built in just one evening. It is capable of measuring temperatures over a range of from  $-30^{\circ}\text{F}$  to  $+120^{\circ}\text{F}$ .

The circuit is shown in Fig. 1; its operation is fairly straightforward. A diode-connected 2N3904 transistor forms a voltage divider with R1. The transistor is used as the temperature sensor and, for best results, should be connected to the rest of the circuit using twisted wire as shown. As temperature increases, the voltage drop across the transistor changes by approximately  $-1.166$  millivolts-per- $^{\circ}\text{F}$ . As a result, the current at pin 3 of IC1, a 741 op-amp with a gain of 5, decreases as the temperature measured by the sensor increases.

A second 741 op-amp, IC2, is configured as an inverting amplifier. Since pin 3 of that IC is grounded, pin 2 is at a virtual ground and the sum of all currents into that pin must be zero. Resistors R5 and R6 are used to calibrate the circuit. Once R6 is adjusted (more on that later), the current flow through those resistors will be constant. At a temperature of about  $-30^{\circ}\text{F}$ , the current through R4 (that resistor is formed by connecting a 910- and a 1600-ohm resistor in parallel) should equal the current through R5 and R6.

At higher temperatures, the current through R4 will be less than the current through R5 and R6. Since the sum of the currents at pin 2 of IC2 should be zero, current will be drawn from the output (pin 6) of that IC to offset the difference. That current must pass through M1, and the

amount of current drawn is, of course, measured by the meter. As the relationship between the amount of current drawn and the measured temperature is linear, it is relatively easy to calibrate the meter to indicate measured temperature.

If the temperature goes below  $-30^{\circ}\text{F}$  a reverse current will be generated. As that reverse current is undesirable, its flow is prevented by inserting D1 into the circuit as shown.

Calibration is also straightforward. When properly done, a temperature of  $-30^{\circ}\text{F}$  will result in a meter reading of 0 milliamps, while a temperature of  $120^{\circ}\text{F}$  will result in a meter reading of 1 milliamp. Divide the scale between those points into equal segments and mark the divisions with the appropriate corresponding temperatures. Note that dividing the scale into more parts will result in greater accuracy; if you divide it into 150 equal segments, for instance, each division will equal one degree. The calibration is completed by placing the sensor in an environment with a known temperature, such as an ice-point bath. The ice point of water is approximately  $32^{\circ}\text{F}$ . That is the temperature at which water and ice can co-exist in the same container. To prepare the bath, place water and ice in a large glass beaker or similar container, wait a few minutes for the temperature of the bath to stabilize, and verify that the temperature is indeed  $32^{\circ}\text{F}$  using another thermometer that is known to be accurate. Then, simply place the sensor in the bath and adjust R6 until you get the correct meter reading.

—David McNeill

R-E


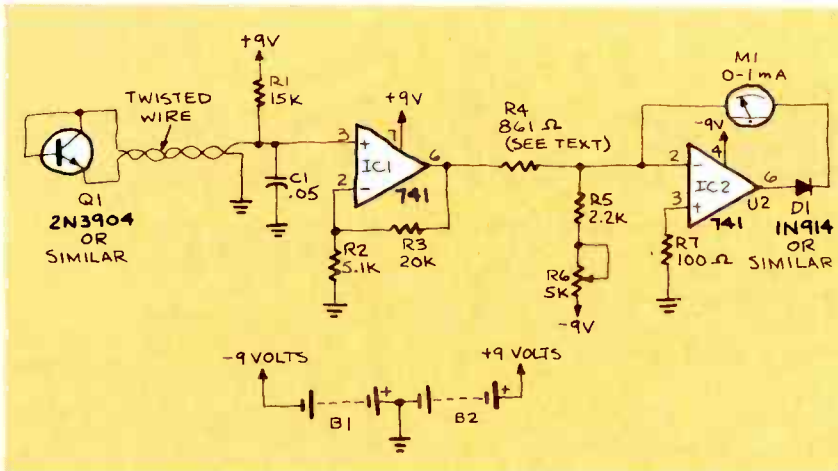


FIG. 1
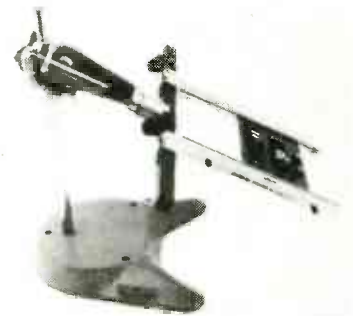
### NEW IDEAS

This column is devoted to new ideas, circuits, device applications, construction techniques, helpful hints, etc.

All published entries, upon publication, will earn \$25. In addition, Panavise will donate their model 333—The Rapid Assembly Circuit Board Holder, having a retail price of \$39.95. It features an eight-position rotating adjustment, indexing at 45-degree increments, and six positive lock positions in the vertical plane, giving you a full ten-inch height adjustment for comfortable working. (See photo below.)



I agree to the above terms, and grant Radio-Electronics Magazine the right to publish my idea and to subsequently republish my idea in collections or compilations of reprints of similar articles. I declare that the attached idea is my own original material and that its publication does not violate any other copyright. I also declare that this material had not been previously published.

Title of Idea \_\_\_\_\_

Signature \_\_\_\_\_

Print Name \_\_\_\_\_

Date \_\_\_\_\_

Street \_\_\_\_\_

City \_\_\_\_\_


State \_\_\_\_\_

Zip \_\_\_\_\_

Mail your idea along with this coupon to: New Ideas Radio-Electronics, 200 Park Ave. South, New York, NY 10003

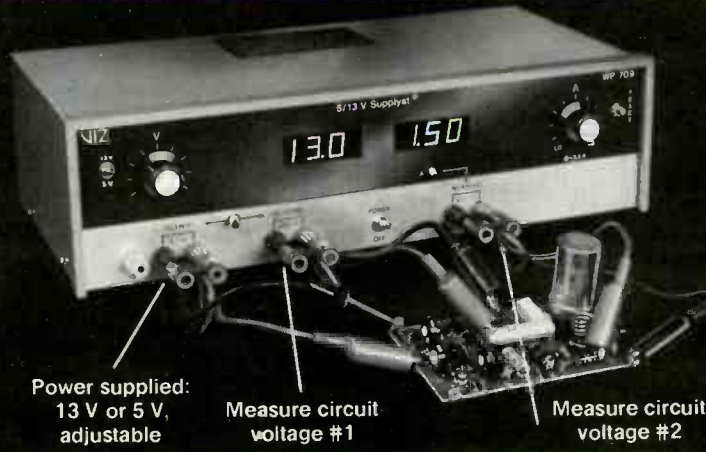**NEW!**

**WP-709.  
Double-slot  
Supplyst™  
power supply.**



Power supplied:  
13 V or 5 V,  
adjustable

Measure circuit  
voltage #1

Measure circuit  
voltage #2

Outputs: 5V or 13V DC,  
adjustable  $\pm 1\frac{1}{2}V$   
Zero to 7.5 amp, each voltage.  
Two LED displays,  
monitor V or A—  
or two DC voltmeters  
Adjustable current limiting

Only  
**\$324.95**

# DC power to test logic or mobile equipment. Another VIZ Value

### HERE'S REAL PRECISION

Select the precise voltage you want: 5V or 13V, adjustable  $\pm 1\frac{1}{2}V$  at each range. Output is laboratory quality. Ripple less than 10mV, peak to peak. Regulation better than 0.1%.

### HERE'S REAL POWER

Up to 7.5 amp. at each voltage—

plenty for computer circuits, PA systems, mobile transmitters, autos, boats, planes.

### HERE'S REAL CONVENIENCE

Front panel controls for instant voltage adjustment and precise fine adjustment to within 0.1V. Two 3-digit LED displays permit continuous

monitoring of both voltage and current during use. Current limiting control with instant pushbutton reset.

The WP-709 is like two precision power supplies for a price less than you might pay for one— PLUS two digital DC voltmeters.

## VIZ Supplyst™

power supplies with digital displays of voltage and current



**WP-705 \$315.95**

Single output  
0-50VDC, 0-2A.



**WP-707 \$409.95**

Dual output  
Two 0-25VDC, 0-2A.

**WP-706 \$329.95**

Single output  
0-25VDC, 0-4A.



**WP-708 \$479.95**

Triple output Two 0-20VDC, 0-2A.  
One 5VDC, 0-4A.



## VIZ DC power supplies

Fully regulated, continuously adjustable voltage outputs with short circuit protection. Analog meters and overload indicators.



Dual WP-702A Two 0-20VDC, 0-200mA **\$167.00**



Single WP-703A  
0-20VDC, 0-500mA **\$119.00**



Single WP-704A  
0-40VDC, 0-250mA **\$125.95**

### VIZ RELIABILITY

VIZ is a 50 year-old company. Our instruments are fully warranted, parts and labor, for a year.

All items tested to NBS standards. We offer service and parts availability for a minimum of ten years. Over 15 repair depots in U.S.A.

Want full technical details and a demonstration? Call toll-free. 1-800-523-3696, for the VIZ distributor nearest you



**Look to VIZ for value, quality, availability.  
Over 70 instruments in the line— PLUS full accessories.**

VIZ Mfg. Co., 335 E. Price St., Philadelphia, PA 19144

CIRCLE 8 ON FREE INFORMATION CARD

## Hitachi V-202 and V-352 Dual Trace Oscilloscopes

When you get exceptional capability per dollar, that's superior cost-performance. And that's the 35 MHz Hitachi V-352 and the 20 MHz Hitachi V-202 dual trace oscilloscopes.

Proof? Just skim these features, then note the price. For starters, both scopes have a 2-year limited warranty. And then there are features like square CRT's with internal graticules, vertical sensitivity

of 1 mV/division, and a wide dynamic range for vertical amplifier of 8 divisions or more. Each scope features front panel X-Y operation, 10X sweep magnification, 3% vertical deflection and sweep accuracy, and low vertical drift. For ease of operation, functionally related controls are grouped into 3 color-coded front panel blocks.

How do we build in all that capability at such low cost? Chalk it up to two decades of oscilloscope design experience and some of the most modern production methods around.

Hitachi V-352 and V-202 are

stocked by your authorized industrial distributor and ready for fast delivery.

Ask for a demonstration and see more performance than you expected for less than you thought possible.

**Hitachi...  
the measure of quality.**




**HITACHI**

Hitachi Denshi America, Ltd.  
175 Crossways Park West  
Woodbury, NY 11797  
(516) 921-7200

CIRCLE 14 ON FREE INFORMATION CARD
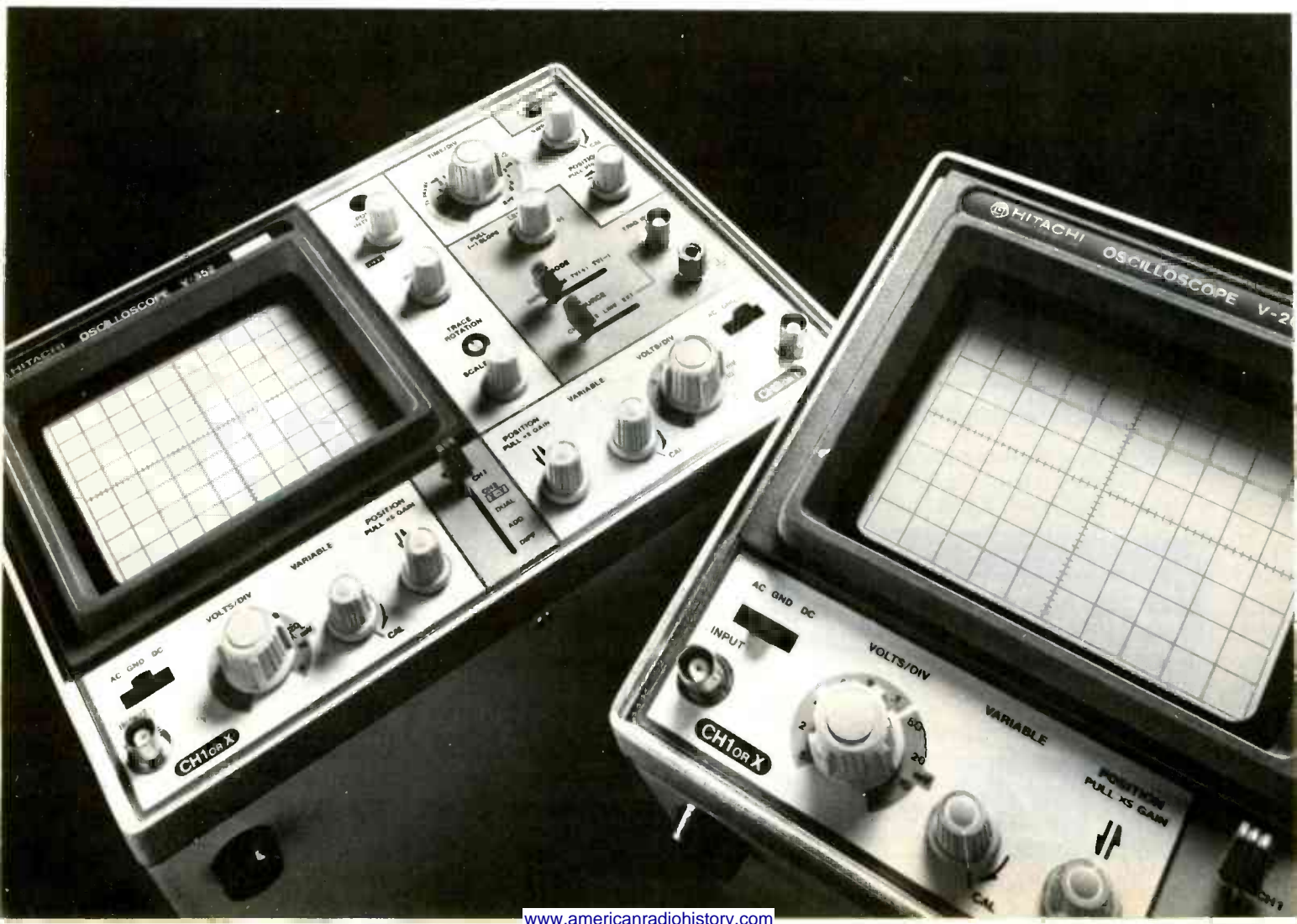
# You'll recognize the name... appreciate the quality.





# BUILD THIS



ROBERT GROSSBLATT

MEDICAL TECHNOLOGY HAS GROWN tremendously over the past 20 years. So much so that the consumer now has instruments available to him that at one time could only be found in hospitals. One such instrument, a machine to monitor a heart rate, used to occupy an entire room and required a sizeable endowment to buy; now you can build one that runs on batteries for under a hundred dollars.

The Heart-a-Matic described here gives a digital readout of your heart rate and can be built from readily available parts; it features both an audible and a visual heart-rate indication.

### Design considerations

There are two basic problems that have

## Heart Rate Monitor

*Knowing your heart rate and how it varies under different circumstances can give you an idea of your physical condition. Build the Heart-a-Matic and keep track of the state of your health and fitness.*

to be overcome in designing a reliable heart-rate monitor. The first is that each heartbeat is actually made up of several beats; the second is that the heart is not crystal-controlled—even a healthy heart beats somewhat irregularly.

The heart is a four-chambered pump and consequently each heartbeat is composed of several parts (everyone is familiar with the "lub-dub" heard through a stethoscope). Figure 1 shows the various components of a heartbeat. The Heart-a-Matic is designed to integrate the "P" and "T" portions of the waveform with the "R" portion.

Even during rest, the rate at which the heart beats varies; irregularity between beats is a natural characteristic of the heart. Several beats have to be sampled and averaged to provide a result that has any useful meaning. The Heart-a-Matic heart-rate monitor uses an eight-beat sample to obtain an average reading. That number of beats was chosen as a good middle ground to minimize irregularity, on the one hand, and to provide reasonable response-time, on the other.

Commercially available machines use multi-beat samples and update at the end of each sampling period.

The Heart-a-Matic, however, gives a running average. In other words, whenever it adds a new beat to its sample,

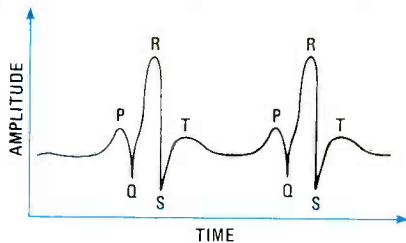


FIG. 1—THE PARTS OF A HEARTBEAT. The Heart-a-Matic integrates the P and T portions with the R portion.

it drops the first beat of the sample. Consequently, it's able to update with each beat and still give a meaningful readout.

### How it works

As shown in Fig. 2, the Heart-a-Matic is composed of eight sections. A complete schematic of the device is shown in Fig. 3. The sensor, IC24, is an FPA104 infrared emitter-sensor combination in one housing. The two elements are side by side and there is no direct way for the radiation from the emitter to be seen by the detector, because they are separated by part of the case. The sensor is designed to be placed against a person's finger. The IR (InfraRed) radiation emitted by the LED in IC24 penetrates the outer skin-layer and is reflected back to the detector. As the heart beats, a new volume of blood is pumped into the finger and changes the amount of infrared light reflected back to the photo-transistor. That change in blood density (and, consequently, in reflected IR) is used by the Heart-a-Matic to determine the heart rate.

The input amplifier, composed of Q1 and IC1, has two main jobs. It amplifies the weak signal from the detector, and integrates the several components of the heartbeat into one pulse. The waveform emerging from the output of IC1, however, is far from being a clean single pulse. Even though the peaks and valleys of the heartbeat have been smoothed out, the

pulse still has to be conditioned before it can meet the somewhat snobbish square-wave requirements of the digital circuitry that will process it later. That is a problem with *any* system that combines digital and analog techniques. While digital systems require strictly "yes" or "no" answers, the analog world usually provides just "maybes."

The conditioning circuit, consisting of Q2 and IC2, squares the wave presented to it by IC1 and raises its voltage level so it can be reliably detected by IC2, a 555 configured as a monostable multivibrator, or pulse generator. Capacitor C8 and resistor R9 give the output pulse of the 555 a width of about 100 milliseconds. That serves two purposes. First, it insures that the high level of the pulse will be seen as a logic one by the digital circuitry that follows and, second, it helps eliminate the "maybes" of the analog world. Once the 555 is triggered, it ignores all other signals for 100 milliseconds.

Should some signal ambiguity still manage to emerge from the analog portion of the heart-rate monitor, the first part of the digital portion should take care of it. Integrated circuit IC3-a is a Schmitt trigger set up as a half monostable with an output-pulse width of about 20 milliseconds. That signal is one of the two that control the interlock portion of the circuit made up of the three other NAND gates of IC3 and IC5. A set-reset latch formed by IC3-b and IC3-c controls the calculation of the heart rate started by each heartbeat detected.

When a positive pulse appears at the output of IC3-a it causes the output of the latch to go—and remain—high. That output is inverted by IC3-d and presented, through inverter IC22-f, to the clock input of IC21, a 4017 decade counter. Each pulse will make one of that IC's outputs go high in sequence.

We are sure of starting with number one because C18 performs a power-on-

reset function. That means that IC21 will start with its first output at a logic-high and will then clock along with incoming heartbeats for eight beats, at which point it will reset back to one. That happens because the ninth output (which, coincidentally, is also pin 9) is also connected to the RESET pin. The outputs of the IC21 are connected in successive pairs to IC20's 2-input NOR gates. As a result, we have repeating sequential logic ones that are used in the section of the heart-rate meter that measures the period and calculates the heart-rate frequency.

Integrated circuit IC23 and its associated components provide an extremely accurate source of 60-Hz square waves that are counted by IC16-IC19, 4040 binary ripple counters. Each of the 4040's is connected to the "D" inputs of a 4508 (IC12-IC15) configured as 3-state eight-bit hold-and-follow latch.

When a heartbeat is detected, one of the outputs of IC20 goes high and causes two things to happen. The first is that its associated 4508 is enabled, and the data present at that moment at its "D" inputs is stored in the latch and presented at its "Q" outputs. The second thing that happens is that an inverter (a section of IC22) set up as a half-monostable outputs a positive pulse, lasting about 70 microseconds, that resets the 4040 to zero. The counter immediately starts counting again; but the latch is now disabled and it ignores the changing data at its inputs. The period of each heartbeat is counted at a 60-Hz rate and appears on the data bus.

Next comes a bit of arithmetic. Since the device knows the period of the heartbeat, it now has to calculate its frequency. Those are reciprocals of each other and the form of the calculation that has to be performed is also simple. Sixty Hz (cycles-per-second) times 60 (seconds-per-minute) equals 3600 cycles-per-minute. The number of beats per minute is therefore the number of cycles per minute divided by the number of cycles per beat. Since we are using a period of eight heartbeats, the magic number becomes 28,800 ( $8 \times 3600$ ). The division is carried out in two ways. The first way is sneaky and the second is interesting.

The sneaky way is to ignore the two least-significant outputs of the 4040's. By doing that we immediately divide the count by four. That also gives us the advantage of smoothing out any "bobble" in the circuitry by dropping the two least-significant figures, which is where it would show up. All we have to do now is divide by 7200 ( $28,800 \div 4$ ), and the way that is done is one of the most interesting features of the Heart-a-Matic. The secret lies in an often overlooked, frequently misunderstood, and extremely useful type of IC—the rate multiplier.

There are two types of rate multipliers—binary and decimal. The difference between them is much the same as

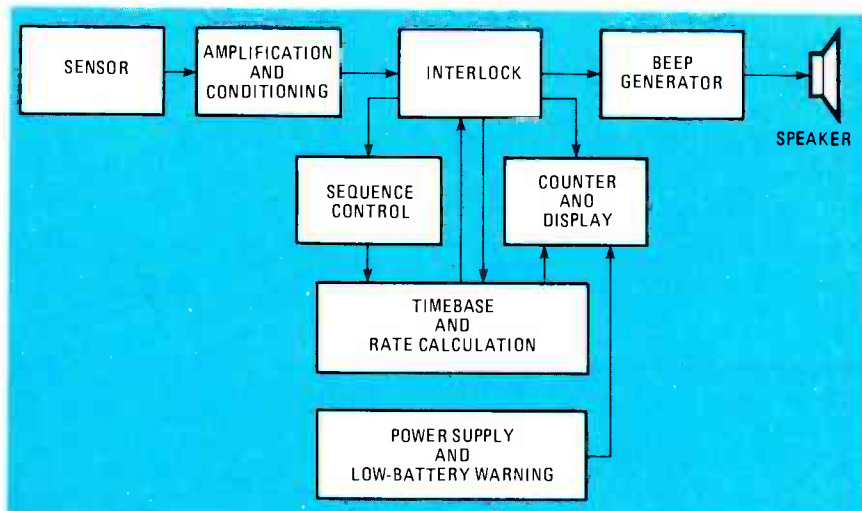


FIG. 2—THE HEART-A-MATIC is made up of eight main sections as shown in this block diagram of the device.

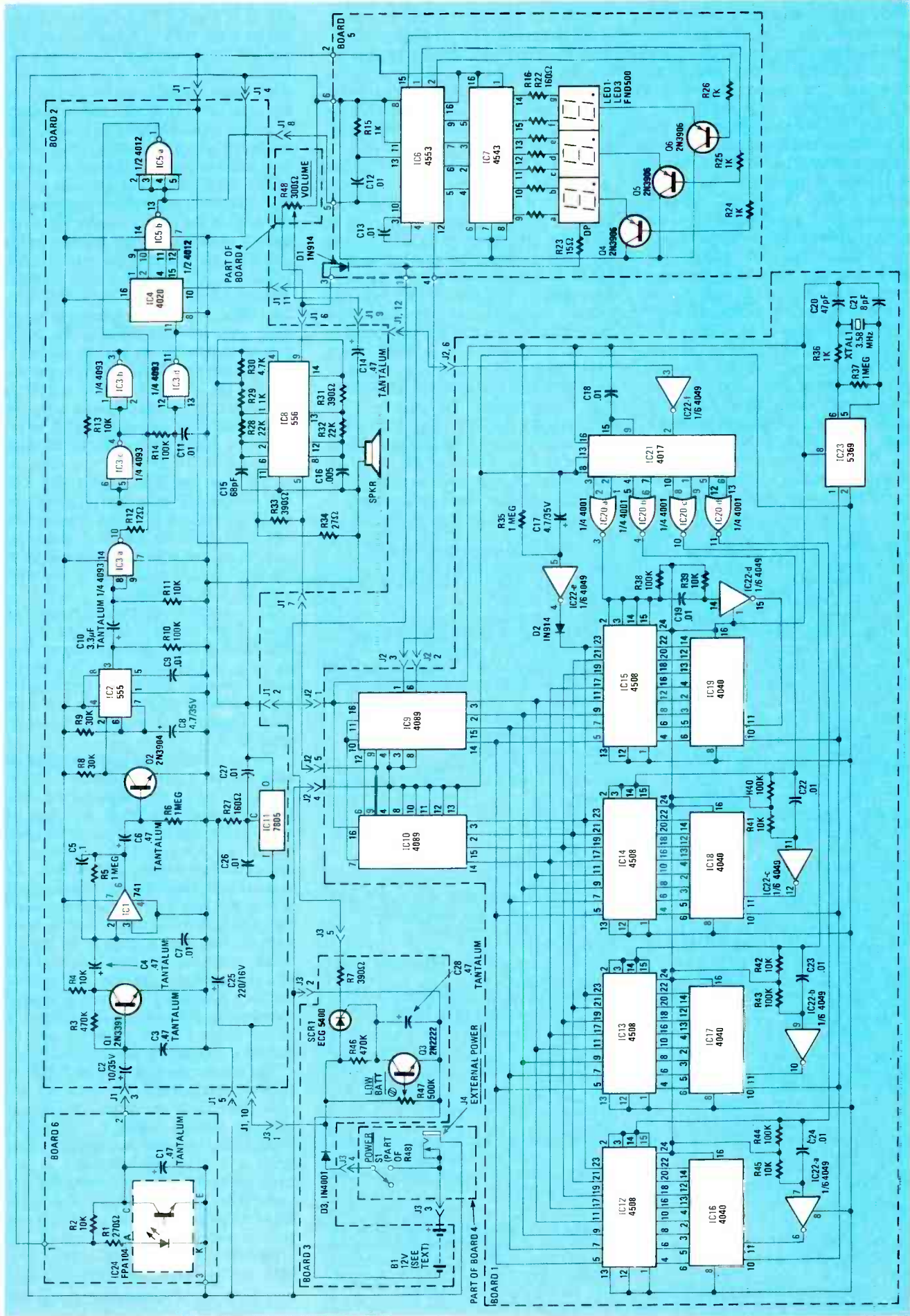


FIG. 3 SCHEMATIC DIAGRAM of the Heart-a-Matic. The device is built on six separate PC boards.

the difference between a counter such as the 4520 that counts strictly in binary and its companion, the 4518, that counts in BCD (Binary-Coded Decimal). Since BCD isn't needed by this part of the Heart-a-Matic, the choice is the 4089, a binary rate-multiplier (IC9 and IC10).

The 4089 has two types of outputs. The first, which we'll discuss shortly, is  $\frac{1}{16}$  the input frequency; if a 16-kHz signal were applied to the input, the output would be 1 kHz. The second output is "programmable" and is equal to  $\frac{1}{16}$  the frequency applied to its clock input multiplied by whatever number is applied to its binary inputs. For example, if the input frequency is 16 kHz, and a binary four is presented to the binary inputs, the 4089 will output a frequency of 4 kHz. Unfortunately, a rate multiplier will not always do exactly what you expect it to—output a number of pulses that is always an average of  $\frac{1}{16}$  the input frequency multiplied by the input number. While the example presented above works out very nicely, the rate multiplier may have to work with a frequency of 17 kHz as well. Since that figure is not evenly divisible by

2 (or multiples of two), the output pulse will be unevenly spaced and of uneven width. Fortunately for the Heart-a-Matic, however, that is unimportant because we are only interested in the number of pulses and not in a particularly smooth waveform. Rate-multipliers IC9 and IC10 are cascaded so they can handle division by an eight-bit number.

Half of IC8, a 556 dual timer, is used as an astable multivibrator, or frequency generator. With the component values indicated, the free-running frequency is about 400 kHz, although the actual figure is not critical. That's because the signal is fed to the cascaded 4089's and all we're interested in is the ratio of their base rate to their multiplied rate. The multiplied rate is output at pin 6 of IC9 and routed to the clock input of IC4, a 4020 binary ripple-counter. The base rate, output at pin 1 of IC9, is sent to IC6, a 4553 three-digit binary counter. The outputs of the 4020 that are decoded all go high when the counter reaches a number you should remember from earlier—7200. With all that behind us, we can now explain the device's operation much more simply.

The controlling key is the interlock section of IC3 and IC5, and the heart of the device is the 4089's. When the output of the IC3 latch goes high following a detected heartbeat, one of the octal-latch 4508's puts a number on the data bus. At the same time, two other things happen. A high is applied to pin 4 of the 400-kHz frequency generator, setting it in operation, and a low is applied to the RESET pin of IC4, the 4020 counter, enabling it. The rate multipliers begin outputting pulses to the 4020 at the rate of  $\frac{1}{16}$  the 556's frequency multiplied by the number on the data bus, and sending the base-rate frequency to IC6, the three-digit counter. When the count at the 4020 reaches 7200, the output of IC5-b, a four-input NAND gate, goes low and transfers the count present at IC6 into its internal latch.

The same signal also travels to the RESET pin, pin 13, of IC6 via C12 and clears the counter to zero in preparation for the next count. The output of IC5-b is inverted by IC5-a and returns to the latch formed by IC3-a and IC3-b, causing its output to go low. That disables the 400-kHz frequency generator, causes the 4020, via inverter IC3-d, to reset to zero and hold there for the next heart-rate calculation, and returns the clock input of the 4017 decade counter to a low state until the next heartbeat.

The sequence of events resembles those of the classic "do-nothing box." The Heart-a-Matic gets turned on, does its thing, and then turns itself off. In this case, however, the device performs a complex series of operations and then waits for the next incoming signal to retrigger it.

The other half of IC8 is also configured as a frequency generator and is frequency-modulated by the output of the 400-kHz generator. The result is a tone of about 1 kHz, that lasts as long as the other oscillator is running. That tone is fed to the speaker via volume-control R48. An unusual side-effect of that is that the duration of the beep changes with the heart rate. The reason is that the lower the heart rate, the less time it takes to do the internal arithmetic and the less time the 400-kHz oscillator operates and enables the beep generator. The beep generator also supplies power to the decimal points of the displays for a visual as well as audible indication of the heartbeat.

The counter section, IC6 and IC7, is fairly straightforward. The latter is a decoder that feeds the three multiplexed common-cathode displays. The actual multiplexing is done by an internal oscillator in IC6 whose frequency is determined by the capacitor connected between pins 3 and 4. Resistor R15 holds the RESET pin of IC6 low until it receives a positive reset-pulse from IC5-b via C12.

Inverter IC22-e is present because of a basic law of mathematics that says that

#### PARTS LIST

**All resistors  $\frac{1}{4}$ -watt, 5% unless otherwise noted**

R1—270 ohms  
R2, R4, R11, R13, R39, R41, R43, R45—10,000 ohms  
R3, R46—470,000 ohms  
R5, R6, R35—1 megohm  
R7, R31, R33—390 ohms  
R8, R9—30,000 ohms  
R10, R14, R38, R40, R42, R44—100,000 ohms  
R12—12 ohms  
R15, R24-R26, R29, R36—1000 ohms  
R16-R22, R27—160 ohms  
R16-R22, R27—160 ohms  
R23—15 ohms  
R28, R32—22,000 ohms  
R30—4700 ohms  
R34—27 ohms  
R37—10 megohms  
R47—500,000 ohms, multiturn potentiometer, PC-mount  
R48—300 ohms, potentiometer, panel-mount with switch (commonly used in TV receivers)

#### Capacitors

C1, C3, C4, C6, C14, C28—0.47  $\mu$ F, 35 volts, tantalum  
C2—10  $\mu$ F, 35 volts, electrolytic  
C5—0.1  $\mu$ F, ceramic disc  
C7, C9, C11-C13, C18, C19, C22-C24, C26, C27—0.01  $\mu$ F, ceramic disc  
C8, C17—4.7  $\mu$ F, 35 volts, electrolytic  
C10—3.3  $\mu$ F, 35 volts, tantalum  
C15—68 pF, ceramic disc  
C16—.005  $\mu$ F, ceramic disc  
C20—47 pF, ceramic disc  
C21—8 pF, ceramic disc  
C25—2200  $\mu$ F, 16 volts, electrolytic

#### Semiconductors

IC1—741 op-amp  
IC2—555 timer  
IC3—4093 quad 2-input NAND Schmitt trigger  
IC4—4020 14-stage binary ripple counter

IC5—4012 dual 4-input NAND gate  
IC6—4553 3-digit binary counter  
IC7—4543 BCD-to-7-segment latch/decoder/driver  
IC8—556 dual timer  
IC9, IC10—4089 binary rate multiplier  
IC11—7805 5-volt regulator  
IC12-IC15—4508 dual 3-state 4-bit latch  
IC16-IC19—4040 12-stage binary ripple counter  
IC20—4001 quad 2-input NOR gate  
IC21—4017 decade counter  
IC22—4049 hex inverter  
IC23—5369 60-Hz timebase  
IC24—FPA104 infra-red emitter/sensor array  
Q1—2N3391  
Q2—2N3904  
Q3—2N2222  
Q4-Q6—2N3906  
SCR1—ECG 5400  
LED1-LED3—FND500 0.5-inch common-cathode 7-segment display  
D1, D2—1N914 or 1N4148  
D3—1N4001  
XTAL1—3.579545 MHz color-burst reference crystal  
SPKR—8 ohms, 2-inch diameter  
S1—SPST switch (part of R48)  
J1—12-contact edge connector  
J2, J36-contact edge connector  
J4—subminiature N.C., chassis-mount  
B1-B8—1.5-volt "AA" cell

**Miscellaneous:** PC boards, two "AA" side-by-side battery holders, Velcro strip, plastic for cases, wire, shielded cable, solder, etc.

**The following are available from Hal-Tronix, P.O. Box 1101, Southgate, MI 48195: Set of six etched and drilled PC boards, \$29.95; Board 1 (double-sided), \$19.95. Add \$2.00 for shipping & handling; MI residents add 4% tax.**

*continued on page 109*

# BUILD THIS

**Part 2** THE FIRST PART OF THIS article discussed the theory of operation of a good portion of the main board of the Picture Phone. We'll now complete that discussion; it will be helpful if you have Part 1 handy.

## Fast-scan counters

The fast-scan counters are IC6, IC8, IC23 and IC39. Each IC is a four-stage binary counter that is cleared to all zeroes when pin 1 is taken to a logic-low state. When pin 9 is low, the counter stages are preset to the value hard-wired at pins 3-6. Pin 2 receives the clock pulses, and responds to their positive-going edges. Both clear and load operations are synchronous—that is, they take place only on the positive-going edge of the clock pulse. When the LOAD or CLEAR pin is taken low, the counter stops and retains its value. If a clock pulse occurs while the appropriate pin is low, the counter will load or clear.

The fast-scan dot counters are IC6 and IC8 (dots are the pixels along a line of video). The dot counter is analogous to the horizontal sweep in the camera and display. The dot counters have two modes, one for the camera and one for all other operations.

Let's consider non-camera operation first. The crystal oscillator supplies clock pulses to pin 2 of the dot counters. Note that pin 15 of IC6 is connected to pin 10 of IC8. That is the "carry" from the first IC to the second, and provides synchronous operation of both IC's.

Figure 5 shows the timing of the dot counters. The counter CLEAR pulse is provided by IC10 at a count of 215. That means that the counter advances to 215, is reset to zero, and begins to count again. The internal horizontal-sync pulse (IFH) is produced by counter inputs applied to IC42. The clock frequency, divided by 218 (the count from zero to 215), generates the correct horizontal-sync frequency.

Signal "J," which is low between the counts of zero and 127, serves several purposes. It is delayed by one clock pulse

to form IFHB, the internal fast-scan blanking signal, which blanks the display in all modes. That signal is also applied to IC28 to control when data can be written to memory. Memory-write takes place, and the display is unblanked, when the counter is between zero and 127.

Now let's look at the operation of the dot counter in the "snatch" and camera-display modes. The clocking signal is derived from the synchronous oscillator;

starts with the same polarity.

The fast-scan line counters are IC23 and IC39. Let's first look at how they work during the non-camera mode. Dot-counter signal "J" is used as the clock pulse, making the line counter advance one step for each line. Nine count-stages are needed; the extra stage is supplied by IC32 and is the least significant bit.

Figure 6 shows that the counter advances to a count of 262, is cleared, and starts again at zero.

The clear pulse is supplied by IC47, which is hard-wired with the eight most-significant bits of the line counter. The CLEAR pin is held inactive when the camera is in use by connecting it to the logic-1 present at pin 10 of IC48.

The internal fast-scan vertical sync (IFV) comes from IC31.

When the camera display is viewed, the CLEAR function is disabled and the line counter is preset whenever a vertical-sync pulse occurs. When the counter is preset and the sync pulse from the camera is completed, the counter starts counting. When the count reaches 511, the next count, zero, allows display and writing to memory to begin. The time that is spent in counting from the preset

value to zero is used to allow the camera's blanking-function to be completed.

The line counter advances two counts for each slow-scan line to allow each line to be displayed twice for an easier-to-view picture. There are 128 slow-scan lines, which means that 256 lines-per-field (or 512 lines-per-frame) will be displayed. Since NTSC standards call for 525 lines per frame, a small portion of the picture at the top and bottom is blanked.

## Slow-scan clocks

There are two slow-scan clocks. One is derived from the master crystal oscillator and is used for all functions except slow-scan reception. The second clock is free-running, and is synchronized to the slow-scan horizontal-sync pulses. The clocks are selected by IC13, a 4PDT multiplexer.

# Picture Phone



*Before you build your Picture Phone, you should know how the device works. We'll conclude our discussion of that topic in this part.*

**JOSEF BERNARD,**  
TECHNICAL EDITOR

and IC10, which supplies the CLEAR pulse, is disabled. The counter advances until a horizontal-sync pulse from the camera (EFH) takes the LOAD pin low. The counter is preset to a value of 217, as determined by the fixed inputs to pins 3-6 of IC6 and IC8. The counter resumes counting at a preset value of 217 when EFH is no longer present. When it reaches its maximum count of 255, it resets to zero and starts counting again. The time spent counting from 217 to 255 represents blanking of the left-hand edge of the picture; the time between 128 and EFH is used for right-hand blanking.

The LOAD pin is controlled by an RS flip-flop made from IC15-c and IC15-d. That flip-flop insures that the LOAD pin remains low until a clock pulse to load the counter has arrived.

The EFH signal is applied to the CLEAR pin of IC32 to insure that the clock always

## PARTS LIST

### All resistors 1/4-watt, 5% unless otherwise noted

R1-R3, R43, R78, R139, R202—22,000 ohms  
 R4, R201—10 megohms  
 R5, R6, R8, R9, R50, R80—15,000 ohms  
 R7—620 ohms  
 R10, R12, R15, R54, R93-R95, R102, R110, R209, R211, R714-R716—4700 ohms  
 R11, R13, R14, R16-R18, R86, R99—10,000 ohms, 1%  
 R19, R20, R27, R147—39,000 ohms  
 R21—20,000 ohms  
 R22, R23—18,000 ohms  
 R24—8200 ohms  
 R25, R26, R145, R146—82,000 ohms  
 R28, R42, R51, R136, R140, R142, R204, R205, R710, R711—10,000 ohms  
 R29—470,000 ohms  
 R30, R47-R49, R53—2200 ohms  
 R31, R79, R148—100,000 ohms  
 R32, R108—2700 ohms  
 R33—150,000 ohms  
 R34, R40, R52, R96, R109, R137, R144, R704, R717—1000 ohms  
 R35-R39—not used  
 R41—680,000 ohms  
 R44—47,000 ohms  
 R46—33,000 ohms  
 R55, R76, R112, R707—100 ohms  
 R56—100 ohms, trimmer potentiometer  
 R57—3300 ohms  
 R58, R77, R111—330 ohms  
 R59, R703, R712, R713—470 ohms  
 R60—100 ohms, 1%  
 R61-R75—26.1 ohms, 1%  
 R81-R84—not used  
 R85, R98—20,000 ohms, 1%  
 R87, R100—4990 ohms, 1%  
 R88, R101—2490 ohms, 1%  
 R89-R91—not used  
 R92, R200—680 ohms  
 R97—47 ohms  
 R103—820 ohms  
 R104—2000 ohms, trimmer potentiometer  
 R105—1200 ohms  
 R106, R107, R138, R141, R143, R203—1000 ohms, trimmer potentiometer  
 F113-R116, R125-R135—33 ohms  
 R117-R123—not used  
 R144—68,000 ohms  
 R149-R199—not used  
 R206, R207—220 ohms  
 R210—560 ohms  
 R212, R213—33.2 ohms, 1%  
 R314, R315, R317, R318—0.33 ohms, 2 watts  
 R316—220 ohms, 2 watts  
 R601—130 ohms, 2 watts  
 R701—1000 ohms, panel-mount potentiometer  
 R702—10,000 ohms, panel-mount potentiometer  
 R706—1 megohm  
 R708, R709—1800 ohms, 1 watt

### All capacitors Mylar or mica unless otherwise specified

C1-C6—.022 $\mu$ F  
 C7, C24, C25, C38, C200, C240-C243—.01  $\mu$ F ceramic disc  
 C8, C10, C12, C17—.0047  $\mu$ F  
 C9—.0068  $\mu$ F  
 C11, C207—.018  $\mu$ F  
 C13, C15, C18, C19, C23, C263-C266—22  $\mu$ F, tantalum

C14—10  $\mu$ F, tantalum  
 C16, C22, C206, C703—.001  $\mu$ F, monolithic or ceramic disc  
 C20, C201—27 pF, monolithic or ceramic disc  
 C21, C28-C31—470 pF  
 C26—not used  
 C27—33 pF, monolithic or ceramic disc  
 C32, C220-C227—0.1  $\mu$ F, ceramic disc  
 C33, C41, C208, C317-C320—2.2  $\mu$ F, tantalum  
 C34, C230-C237, C250-C262, C702—0.1  $\mu$ F, ceramic disc  
 C35, C202-C205—100 pF  
 C37, C39—not used  
 C40—.047  $\mu$ F  
 C309—500  $\mu$ F, 12 volts, electrolytic  
 C310—9200  $\mu$ F, 15 volts, electrolytic  
 C311—450  $\mu$ F, 25 volts, electrolytic  
 C312—5800  $\mu$ F, 25 volts, electrolytic  
 C601—500  $\mu$ F, 25 volts, electrolytic  
 C701—2  $\mu$ F, tantalum

### Semiconductors

IC1-IC4, IC17-IC20, IC33-IC36, IC49-IC52— $\mu$ PD411 (MM5280) 4K  $\times$  1 dynamic RAM  
 IC5, IC13, IC21, IC37, IC46, IC48, IC55—74LS157 quad 2-1 multiplexer  
 IC6, IC8, IC9, IC23, IC24, IC39-IC41—74LS163 presettable binary counter W/clear  
 IC7, IC26, IC57, IC58, IC61—75LS04 hex inverter  
 IC10, IC31, IC47—74LS30 8-input NAND gate  
 IC11, IC32—74LS107 dual JK negative-edge-trigger flip-flop  
 IC12—4046 CMOS phase-locked loop  
 IC14, IC15, IC45—74LS00 quad 2-input NAND gate  
 IC16, IC29, IC65—74LS74 dual D flip-flop  
 IC22, IC38, IC71, IC72—74LS153 dual 4-input multiplexer  
 IC25, IC42, IC88—74LS20 dual 4-input NAND gate  
 IC27, IC67, IC68—74LS10 triple 3-unit NAND gate  
 IC28, IC43, IC66—74LS25 dual 4-input NOR gate  
 IC30—74LS221 dual one-shot  
 IC44, IC62—74LS32 quad 2-input positive OR gate  
 IC54, IC56—74LS175 quad D flip-flop  
 IC59—74LS08 quad 2-input AND gate  
 IC60, IC63, IC64—74LS13 dual Schmitt trigger  
 IC66—3245 quad TTL-to-NMOS memory driver  
 IC69, IC70—74LS02 quad 2-input NOR gate  
 IC73-IC80—LM711 dual difference-comparator  
 IC81-IC84—not used  
 IC85, IC86—74LS86 quad EXCLUSIVE-OR gate  
 IC87—4066 CMOS quad bilateral switch  
 IC89—566 function generator  
 IC90-IC94, IC105—1458 dual 741 op-amp  
 IC95-IC104—not used  
 Q1, Q2, Q4, Q5, Q8-Q13—2N4124 or equivalent  
 Q3, Q6—not used  
 Q7—2N4126 or equivalent  
 LED1-LED3—jumbo red LED  
 D1-D11, D13-D18, D27-D33—1N914 or 1N4148  
 D12—not used  
 D19-D26, D601, D602—1N4007  
 DT601—gas discharge tube (Joslyn Electronics type 2022-44 or equivalent)

CB1—0.6-amp circuit breaker  
 T1—dual-secondary type: 1st secondary: 25VCT, 1 amp; 2nd secondary: 12.6VCT, 1.5 amps (see text and below)  
 T601—phone-line matching transformer (Microtran type 6112 or equivalent)  
 S1—4P5T rotary switch  
 S2-S4—N.O. momentary pushbutton switch  
 S5—SPDT toggle switch  
 S6—SPST toggle switch  
 J1-J2—not used  
 J3—36/72-pin PC-board edge connector (36 contacts for *each side* of board, two contacts per pin)  
 J4—socket for modular telephone connector, panel-mount  
 J5—DB25-S 25-pin female "date-type" socket, panel-mount  
 J6, J7—RCA-type phone jack, panel-mount  
 J8, J9—female coaxial connector, panel-mount (BNC- or SO230-type)  
 TB601—miniature 8-terminal barrier strip, PC-mount  
 RY601, RY602—4P2T 12-volts, PC-mount (Potter & Brumfield T10-E2-Z4-12VDC or equivalent)

**Miscellaneous:** PC boards, perforated construction board, IC sockets, RG59 cable, shielded audio cable, 4-conductor telephone cable w/modular plug, 3-conductor line cord w/plug, enclosure, hardware, etc.

The following are available from Robot Research Inc., 7591 Convo Court, San Diego, CA 92111, (714) 279-9430: Assembled & tested Model 535 Picture Phone, FCC registered for direct connection to telephone line (KIT-1) (14 lbs.), \$1195.00; assembled and tested No. 400929C main PC board (KIT-2) (4 lbs.), \$495.00; assembled and tested Picture Phone chassis, including telephone adaptor board, but *less main board*, (KIT-3) (12 lbs.), \$695.00; kit of No. 400929C main PC board with all main-board parts (KIT-4) (5 lbs.), \$295.00; kit including chassis and chassis parts, and telephone adaptor board and parts, but *less main board*, (KIT-5) (12 lbs.), \$445.00; telephone adaptor board kit including board and parts (KIT-6) (3 lbs.), \$79.50; etched, drilled, and plated-through main board (KIT-7) (3 lbs.), \$59.00; etched, drilled, and plated-through telephone adaptor board (KIT-8) (2 lbs.), \$19.95; T1 (KIT-9) (4 lbs.), \$29.50; T601 (KIT-10) (2 lbs.), \$24.50; DT1 (KIT-11) (1 lb.), \$8.50; kit of 32 1% resistors for main board (KIT-12) (1 lb.), \$12.00; individual 1% resistor (KIT-13) (1 lb.), \$0.35; Model 535 Picture Phone enclosure kit with mounting rails for main board and back plate for controls (KIT-14) (6 lbs.), \$99.50; kit of *front panel parts only*, (KIT-15) (2 lbs.), \$59.50; assembled & tested RF modulator, less power supply and enclosure (KIT-16) (1 lb.), \$29.00; RF-modulator kit, less power supply and enclosure (KIT-17) (1 lb.), \$19.50. For information on other parts, write to Robot Research.

CA residents please add 6% sales tax. All prices F.O.B. San Diego—check with UPS for shipping charges; please add \$0.50 per \$100.00 of value above first \$100.00 for insurance. MC and Visa accepted.

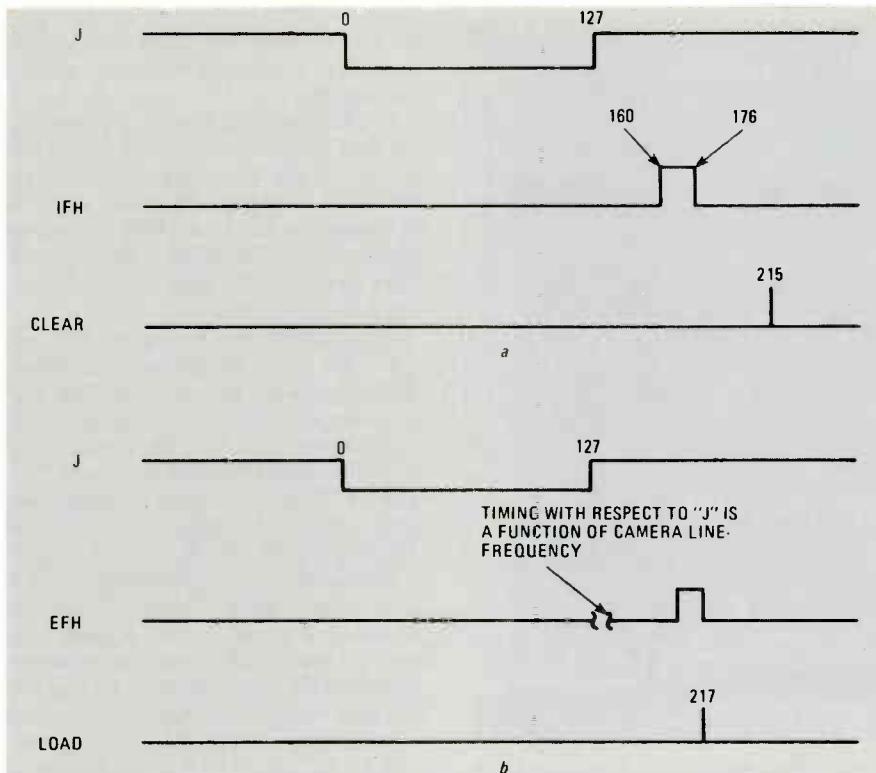


FIG. 5—FAST-SCAN dot counter has two modes—*a* is used for memory display, *b* for frame grabbing and camera display.

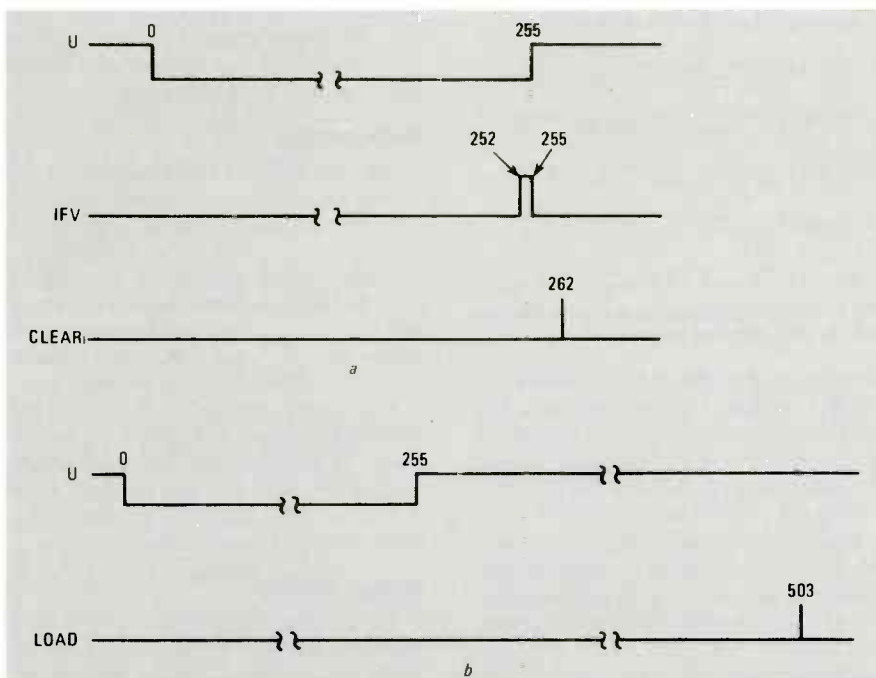


FIG. 6—FAST-SCAN line counter timing for memory display (*a*), and camera display (*b*).

The crystal-derived clock pulses begin with the 60-Hz "U" output of the fast-scan counter. It is divided by four by IC11. The resulting 15-Hz pulse train is applied to one input of PLL (Phase-Locked Loop) IC12. The other input to that IC is the clock oscillator's output divided by 139, making the output of the PLL  $15 \times 139$ , or 2085 Hz. That becomes the slow-scan clock. It allows for 128 pixels and 11 sync counts per slow-scan line.

The synchronized clock pulses are

generated by IC60. Its free-running frequency is controlled by R143. As the frequency is increased, the counter takes less time to address 128 memory "cells" and a shorter line is displayed. The clock is synchronized with the incoming signal by having the incoming slow-scan sync pulses cause the oscillator to stop and restart in phase with them.

The slow-scan clock is aligned with the fast-scan system by retiming the leading and trailing edges of the clock pulses with a section of IC16. A control signal,

#### CAUTION:

FCC regulations prohibit the connection of this device to telephone lines without the use of an approved coupling device. The *only* exception to this is the assembled and tested unit available from the suppliers indicated in the Parts List. A coupler that meets FCC requirements will be described in the next part of this article. *Do not attempt to connect the Picture Phone you build without it—it's illegal to do so.*

"Z," controls all the slow-scan functions. It is in operation only for the duration of the slow-scan memory-write cycle. Its use for retiming the slow-scan insures that the clock will not change during a slow-scan read or write memory access.

#### Slow-scan counters

The slow-scan counter is made up of IC9, IC24, IC40 and IC41. They function the same way as their counterparts in the fast-scan circuit.

The slow-scan dot counter uses IC9 and IC24. It has two modes of operation—one to write slow scan to memory, and one to read it. Let's look at the read-mode first. The clock signal is derived from the crystal oscillator. The CLEAR signal is derived from IC25; the LOAD function is inactive. The counter is cleared at a count of 128 memory "cells" per line and 11 sync counts.


When slow scan information is to be written to memory, the free-running clock is used. The CLEAR signal is derived from a flip-flop formed from IC14-a and IC14-b. The flip-flop is set by an incoming sync pulse, and reset by a clock pulse. That is done to make sure that a clock pulse to clear the counter occurs while the CLEAR pin is low. The slow-scan sync pulse is allowed to reset the counter only after 128 counts (the end of a line) to insure noise immunity. In other words, false pulses can't interrupt a line as it is being written.

The line counter uses IC40 and IC41. A clock pulse occurs when each slow-scan line has been completed. The counter is reset to zero in the "read" mode at a count of 127 by the "U" signal. In the "write" mode it is cleared by the external vertical-sync signal applied to an RS flip-flop made from IC14-c and IC14-d. The flip-flop is reset by IC43 and IC45-a.

When a picture is grabbed from the camera, the line counter is set to all ones, and on the next clock pulse to all zeroes. That one-line time generates a slow-scan vertical-sync pulse.
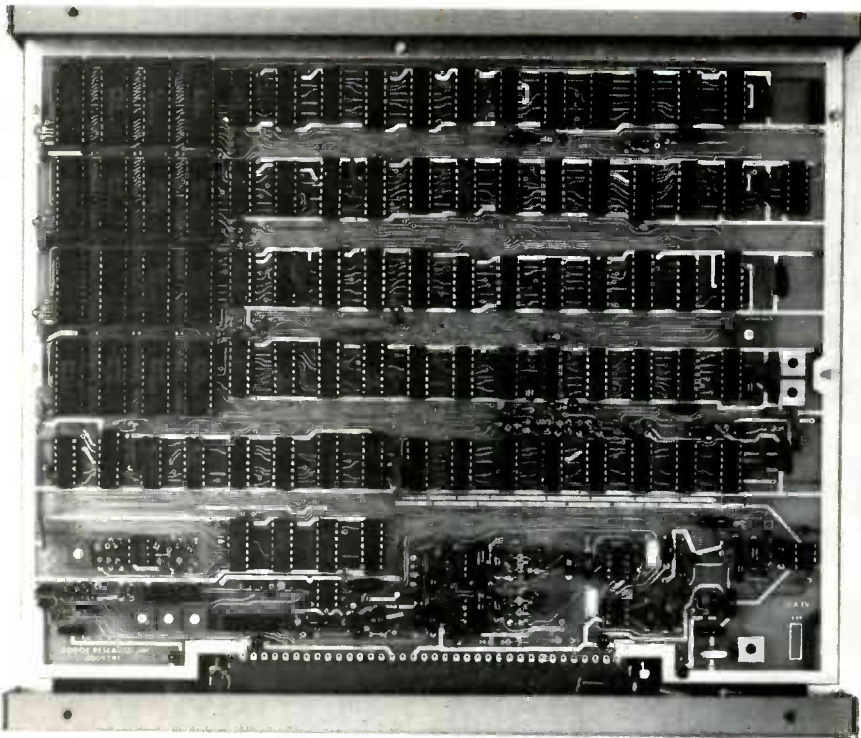
#### Address selector

The memory address-lines are driven by the fast-scan counter to generate a video signal for fast-scan display, and also by the slow-scan counter to generate a slow-scan signal. The memory address-



COMPLETED MAIN BOARD of the Picture Phone plugs into 36/72-pin edge connector mounted at front of enclosure.

lines are connected to the appropriate counter by an address multiplexer made up of IC5, IC21 and IC37—4PDT switches, each of which switches four address lines. Resistors on the leads to the memory IC's damp reflections so that the address voltages will not ring.

The address lines are in the "slow scan" mode during time "Z," which takes place for 16 dots following the right-hand edge of the fast-scan picture. In other words, slow-scan memory access takes place just after fast-scan access for the current line is completed. When "Z" becomes active, the address multiplexer switches to slow scan, and the slow-scan counter is inhibited from changing state. The "Z" signal is generated by IC25-b.

#### Fast-scan memory multiplex

To obtain the speed required for fast-scan operation, memory operation is multiplexed. The multiplexing is done with the memory *CE* (Chip Enable) pulse. Figure 7 shows the *CE* pattern. Note that successive memory columns are overlapped by 50%.

The *CE* signal is formed by a delay flip-flop, IC65, that uses "B" as data and "A" (delayed) as a clock signal. Signal "A" is delayed by an RC circuit that feeds Schmitt trigger IC60. The delay is provided to insure that memory address-lines are stable before *CE* goes high.

The *CE* signal is a zero-to-+12-volt pulse translated from 5-volts by IC66.

#### Slow-scan memory multiplex

Memory multiplexing is performed by the two lowest-order bits on the memory address-lines. In other words, each bit of

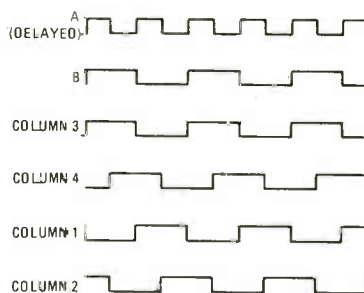


FIG. 7—EACH COLUMN of memory overlaps the next by 50%. See text for details.

the 4-bit pixel nybble requires four memory IC's, arranged in four columns. The two lowest-order address bits determine which column is to be addressed. Memory-speed increase is achieved by overlapping the column-select address.

Slow-scan memory addressing must also be able to select the desired memory column as part of the complete address. The two lowest-order bits from the slow-scan counter, "a" and "b," are combined into column-select pulses by IC69.

Each of the 16 memory IC's has a *CS* (Chip Select) pin that is used for slow-scan memory column selections. The *CS*

pulses come from IC69 and are passed on by IC70 during the slow-scan access time. That IC holds all IC's selected at all other times.

In addition to addressing the memory for slow scan, it is necessary to time the storage of the incoming slow-scan information. The required timing signal is generated by IC71, a DP4T switch of which only one pole is used. The inputs of IC71 consist of the slow-scan *CS* pulses generated by IC69.

The signals used to control IC71 are "X" and "Y," the fast-scan *CS* pulses. Therefore, when the slow- and fast-scan *CS* pulses coincide, a "read store" pulse will be generated. In other words, when IC69 has selected column one, and "X" and "Y" have also selected column one, then—and only then—will a "read store" pulse be generated.

Multiplexer IC71 is enabled by a control signal called SSME (Slow-Scan Memory Enable), which is active for exactly four consecutive fast-scan addresses. That means that SSME is active just long enough to sample each memory column once. The SSME signal is generated by IC27-b. It is a small portion of "Z," which is the time for slow-scan address to be applied to the memory. Since SSME takes place later than "Z," any transients created by the address switchover from fast- to slow-scan die out before a read sample is taken.

#### Write control

The *WE* (Write Enable) signal to the memory IC's must also be multiplexed so that the write and *CE* inputs to an IC will coincide.

Write-control signals are formed by IC67 and IC68-b. Those signals are active one column at a time in response to the values of "A" and "B," the lowest-order bits of the fast-scan counter.

A common control-line to the *WE* encoder determines when writing is to take place. That control line has two sources, one for fast scan and one for slow scan.

The control signals, generated by IC28, are combined by IC44-b.

#### Snatch control

When the *SNATCH* button is pressed, a one-shot puts out a pulse that lasts for several fast-scan fields. The pulse is retimed by a section of delay flip-flop IC29 so that the useful *SNATCH* command starts and ends at the bottom of a TV picture. That prevents any errors that might result from the *SNATCH* pulse ending in the middle of a picture. Another section of IC29 retimes display selection so that the changeover between display memory and the camera takes place when the picture is blanked.

In the next part of this article we'll discuss the telephone interface and power-supply circuits. We will also begin to look at the construction and alignment of the device.



REAR PANEL of Picture Phone. Circuit-breaker reset is located above line cord at left.



## The INS and OUTS of BUYING MAILORDER COMPONENTS

*Often, the hardest task in building a project is obtaining the various parts that you need. Keeping a well-stocked junk box can save you a considerable amount of time, effort, and money!*

KARL T. THURBER, JR., W8FX

ONE OF THE MOST REWARDING WAYS TO GAIN EXPERIENCE IN ELECTRONICS IS to build electronics projects. Besides the satisfaction of accomplishment, you learn a great deal in the process involved.

Today, it isn't an easy matter to obtain the right parts, at the right time, and at the right price. The search for and selection of electronic components for projects can be a very disheartening job, particularly when it's seemingly impossible to obtain certain parts, or the price you must pay for them is excessive. You *can* get the parts you need, when you need them, and at a reasonable price, if you are willing to take an organized approach to parts procurement and do a good deal of preparatory spade work before picking up soldering iron and pliers.

In this article, we will examine the need to get organized for the task; look at parts-selection criteria and the question of substitutions; review various sources of parts; and discuss details of component identification and testing.

As you'll see, once you have a clear view of the process, shopping for parts is no longer the formidable challenge it might otherwise be.

### **Catalogs and reference material**

Before buying parts, it pays to be organized—to have done some pre-planning before you start looking for specific parts for a given project. Some of the things you can do in advance include laying in a good store of catalogs, reference sheets, and reference books; buying-in-advance "staple" and bargain-priced parts; and setting up a well-stocked junk box.

It surely pays to accumulate a broad range of catalogs. No builder's library is complete without them. With a little effort, you will find that virtually any desired part, or a usable substitute, will be listed in *someone's* catalog or cross-reference. You may also find that a single firm may

have all, or almost all, of the parts required for a given project, eliminating the need for repeated shopping forays or inefficient orders to a number of mail-order firms. Having a number of catalogs at hand also allows ready price comparisons between firms.

Having a good reference file, or recent issues of major electronics publications such as **Radio-Electronics**; amateur magazines such as *CQ*, *Ham Radio*, and *QST*; and a variety of computer-oriented magazines, *Byte*, *Microcomputing*, and *Popular Computing* will provide a good background. The magazines also list the addresses of the major suppliers, along with their ordering policies. Of course, single-page magazine ads can't include a supplier's full stock, and are no substitute for the catalogs themselves.

Another reason for obtaining the larger catalogs is that those serve as excellent reference files for various components, and often provide good sources of cross-reference data, particularly for solid-state components. Note that many of the distributors offer two or more catalogs, such as a consumer-type catalog oriented to hi-fi or CB, and an industrial catalog that would normally be more suitable.

In addition, you should acquire the factory service manual, schematic diagram, and component parts list for any item of electronics gear you buy. A surprising quantity of semi-professional and professional-electronics equipment is sold today with no more than a *user's manual*, which is of little help in servicing and parts replacement. Obtaining the proper manuals and parts lists while equipment is currently being manufactured is much easier than trying to obtain such materials later on, when needed information may no longer be readily available.

To facilitate original construction, it's worthwhile to have on hand a selection of standard reference books and manuals, as well. The publications required, of course, will depend upon the particular type of project work undertaken. Some of the more important, all-round useful reference texts include the Editors and Engineers' *Radio Handbook*, the *Master Tube Substitution Handbook*, *Transistor Substitution Handbook*, *TTL Data Book*, *Transistor Specifications Manual*, and *Reference Data for Radio Engineers*; the ARRL *Electronics Data Book* and *Radio Amateur's Handbook*, and several others. A handy cross-reference manual is the *Archer Semiconductor Reference Handbook*, a useful guide to Radio Shack's semiconductors that's also a substitution and cross-reference guide for more than 100,000 solid state devices. Another Radio Shack reference is Forrest Mims' *Engineers Notebook*, which contains tried-and-tested applications for most popular linear and digital IC's. Other helpful parts information sources are

Photos courtesy of Radio Shack and GC Electronics.

Motorola's *Semiconductor Cross-Reference Guide* and *Discrete Hybrid Components Handbook*, Sylvania's *ECG Semiconductor Replacement Guide*; and RCA's *SK Replacement Guide*.

### Buying in advance of needs

Is stocking parts in advance of specific project needs a good idea? It's true that with a few judicious purchases, you can stockpile many of the components needed for future projects. On the other hand, an apparent bargain isn't one, unless there's a real prospect of the part or parts ultimately being used.



**BUYING LARGE ASSORTMENTS** of components and hardware can result in savings, but only if the parts are likely to be used.

Mail-order dealers offer all kinds of special deals—hardware assortments, resistors, knobs, transistors, IC's, potentiometers, transformers, diodes, capacitors, and various surplus components and assemblies. Many of those offerings are indeed bargains, if carefully surveyed and even more carefully purchased. It's generally worthwhile to take advantage of quantity offerings and specialized assortments, tempering one's enthusiasm for a "good deal" with a realistic expectation of when, and if, the contemplated bulk purchase will likely be put to use. A small investment in component assortments usually represents money well spent; however, there is usually little that can be done about a poor choice—you take what you get and hope to be able to use most of it.

For initial stock-up, some useful components include poly-bag assortments of disc ceramic, mica, and small electrolytic capacitors; low-wattage resistors; diodes, and hardware. On the other hand, assortments of precision resistors, large electrolytic capacitors, IC's, and transistors are probably *too* specialized and may not represent good value. The key to selecting true bargains lies in choosing components that you are most likely to use in your projects.

There are some cautions to keep in

mind. Buying in advance of your needs is intended to build an inventory of common parts, not to produce specific parts for an intended project. It's unusual to find just what you need for a particular project from a grab-bag assortment. Whenever you need a *specific* part, order *that* part.

Carefully note the makeup of parts assortments. Are the parts offered all of one (possibly oddball) value, or are they of different values? What are the tolerances and power ratings? Are the leads full-length or too-short PC-board length? Are the components new, used, or surplus; tested or untested; firsts or seconds; marked or unmarked; old or fresh; usable or dubious?

All of those considerations play an important part in determining whether buying in advance of needs is a worthwhile approach or a waste of money.

### Acquiring a junk box

Most builders have a junk box that can be a handy and money-saving device for both construction projects and repair jobs. Not only does the well stocked junk box satisfy convenience and economic needs, but it can also provide a valuable educational experience in component identification and substitution practices for the beginner.

Assembling a useful junk box is a prime objective of most electronics hobbyists. The accumulation gives you the parts you need for projects, when you need them, at reasonable prices—sometimes even at *no* cost. While you may have to spend some money to acquire a foundation, it's possible to accumulate a large assortment of components inexpensively, if you aggressively search for bargains.



**ELECTRONICS FLEA MARKETS** often are a good place to acquire parts at a reasonable cost.

The sources for junk box parts are myriad, and they include local purchases, surplus/salvage, mail order, flea markets, auctions, and other sources. Probably the best, lowest-cost way to build an initial parts inventory is to salvage usable components from junked electronics gear. Components such as switches, potentiometers, coils, diodes, transformers, resistors, and capacitors are often salvaged from such equipment. In earlier days many of those components could be obtained from old radios, defective TV

sets, discarded amateur equipment, and government surplus gear—components large and small being saved with the expectation that they could be used again in some future project.

Those were the good old days, and by and large, junked gear—particularly that of the tube-type variety—provides a shrinking source of junk box parts. With the advent of solid-state equipment, printed circuits and specialized transistors, and IC's, it's harder to "recycle" those components into useful junk box parts than it was 15 or 20 years ago. The trend in junk box acquisition is toward judicious buying of discrete components in advance. We've already discussed parts-selection tips and cautions, and they apply equally to purchases for the junk box.


Regardless of what methods are used to procure for the junk box, the components—particularly the smaller, easily damaged ones—should be carefully segregated by type and value, and placed in labeled jars, plastic drawers, or even small boxes—whichever suits your particular style. The key is that the storage procedures used should allow fast and positive recovery of the parts when needed. Components that can be tested should not be used without first checking their electrical condition, regardless of how good they may look physically. We'll delve into component identification and testing later; suffice it to say at this point that a multimeter and grid-dip oscillator are two very important testing devices for builders.

A final point on junk boxes: After you've developed a respectable junk box, don't hesitate to *use* it for your projects or repairs. You will save money using "pre-owned" parts, and the risk of improper substitution of a part in a circuit is *usually* not too great (except to that particular part). Even if a substituted junk box part fails, a good deal of learning has taken place!
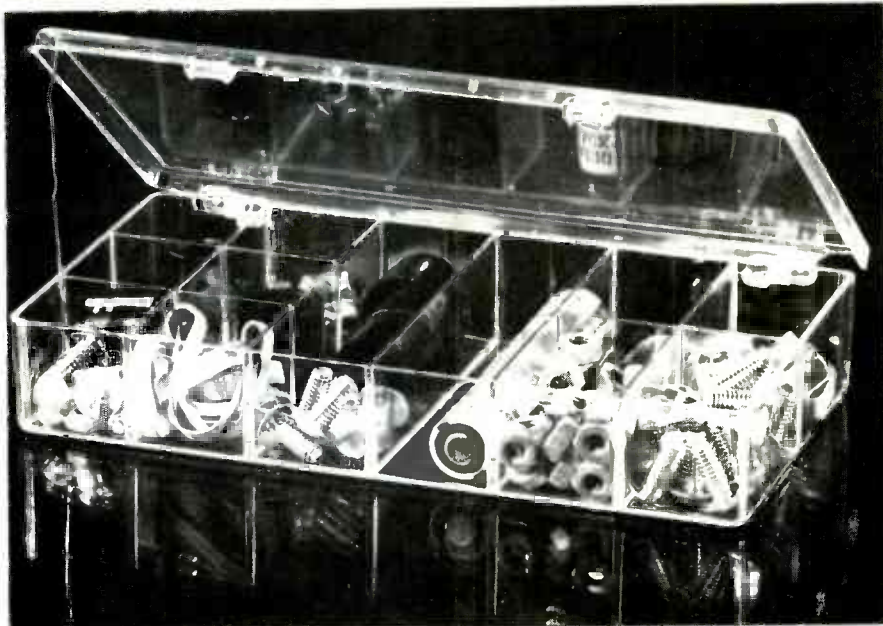
### Developing the parts lists

Most published projects include an itemized parts list that identifies the various components' size, value, and nomenclature, as well as required voltage, current, and power-handling capability. Some parts lists even state brand names and recommend sources for hard-to-find and critical components.

Even when a clear and definitive parts list is provided, you should carefully review the construction project, looking closely at the schematic diagram, photos, and explanations of special circuitry and parts requirements. In many cases, the author will point out critical components that should not be changed. Based on your judgment, other parts may be substituted, possibly from existing junk box stocks. We'll talk more later on the question of parts substitution and how far one can deviate from specified values without



CLEAR PLASTIC STORAGE BOXES can be extremely useful for quick, positive part identification.

affecting performance.

The author's parts list should trigger you to work up additional subsidiary parts lists. Those may logically take the form of lists showing which parts are best procured from your junk box; which are best procured by mail-order; which are best acquired from surplus or salvage sources, and which can be purchased locally. After checking your junk box, look over the local purchase and surplus lists next, with unavailable items added to the mail-order list. In large, complicated projects, it may also be useful to have each list further divided by type of component for convenience in searching for the required parts.

From practical and economic standpoints, it's often wise—even necessary—to make appropriate component substitutions. We'll turn to those next.

### Parts selection and substitution

As the prices of individual components increase, it's important to "make do" with the parts you have on hand. It's possible to substitute components within limits, and yet have a device function as intended. Besides the financial advantages of using existing stocks, it's a real time saver to be able to use on-hand components rather than having to shop for new ones. Also, it's worthwhile to get a feel for the range and types of substitutions that can be made so as to develop flexibility when shopping for components—since local suppliers and mail-order houses will not always have exact specified components in stock.

Many inexperienced electronics enthusiasts have an unnecessary fixation on obtaining the exact parts and values indicated in a construction piece, fearing that the finished equipment will not function correctly if any liberties are taken

with the stated parts list. Usually such fears are exaggerated. Unless a "mirror image" of the item is required, *identical* parts are not needed. In most cases, parts substitutions can be made, within reasonable bounds. Component specifications are not "graven in stone," as the saying goes. There is usually a tolerance range within which the hobbyist may work. Sometimes those are stated, though mostly they are not. The trick to intelligent parts substitution, of course, lies in knowing just what the boundaries of wise substitution are.

Obviously, if the construction article's author or circuit designer has highlighted critical components, you shouldn't change them. Special-purpose or close-tolerance IC's, transistors, tubes, capacitors, resistors, and other parts are best not substituted. But in many cases the component specified is what the designer had on hand, and represents an arbitrary specification. So, bearing in mind that most hobbyists are also experimenters, when you have trouble finding components with the exact specifications, try some substitutions of your own, using a combination of good judgment and close attention to available reference guides, catalogs, and substitution manuals. You may not have the experience to ascertain whether or not you'll be successful in making the substitution, but you'll never know unless you try!

Most components, such as resistors, capacitors, inductors, transformers, and transistors, have *ratings* that are important. Those include power and maximum voltage and current ratings. The ratings of substituted components should be equal to or greater than those specified for the project. Generally speaking, over-rated components *can* be used in electronics projects. For example, a 1-watt resistor

can be substituted for a 1/2-watt resistor of the same value without concern, unless the larger physical size of the 1-watt unit causes a space problem.

Active devices, such as transistors, are more difficult to substitute on a "rating" basis, due to the multiplicity of rating parameters involved. Still, similar guidelines hold for those components, as long as the substitute has equivalent design parameters. One must be cautious in trying to substitute components with over-rated ones when the device is to perform a specific function at a particular value of current or voltage. In such a case, a "larger" unit would not be satisfactory. Zener diodes and other current- and voltage-regulating devices, for example, would fit into that category.

Making a proper "ratings" substitution is a great deal easier than making a "value" substitution. Each type of component is affected by different rules and guidelines, so it's worthwhile to look at each individually:

**1. Resistors.** Fixed resistors are often easily substituted. Unless specified otherwise, fixed resistors commonly have a tolerance of  $\pm 10$  or 20%. Knowing that, you can usually safely substitute any resistor. If no tolerance is specified, working in the  $\pm 10\%$  or 20% range is usually safe. One general exception is high-voltage power-supply bleeder resistors—those can be as much as 25% lower or 50% higher than specified.

In some applications, metal-film precision resistors, manufactured to tolerances of  $\pm 1\%$  or better, are required. That type of resistor is frequently specified for high-stability/ultra-low-noise circuits in computers, voltage dividers, test equipment, and active filters. The stated tolerance must be maintained when substituting those types of resistors.


Frequently, you can find resistors in your junk box that can be adapted for a substitution, using series and parallel combinations whose net resistance is close to the desired value. Resistors connected in series have the total resistance of the sum of the resistors—two 2000-ohm resistors in series have a total resistance of 4000 ohms. To find the effective resistance ( $R_t$ ) for resistors in series use the formula:

$$R_t = R_1 + R_2 + R_3 + \dots$$

Two or more resistors can be connected in parallel to obtain the desired circuit resistance. When you do that, total resistance is always less than the lowest value used in the combination. Use the following simple formula to calculate the value of two resistors connected in parallel:

$$R_t = \frac{R_1 \times R_2}{R_1 + R_2}$$

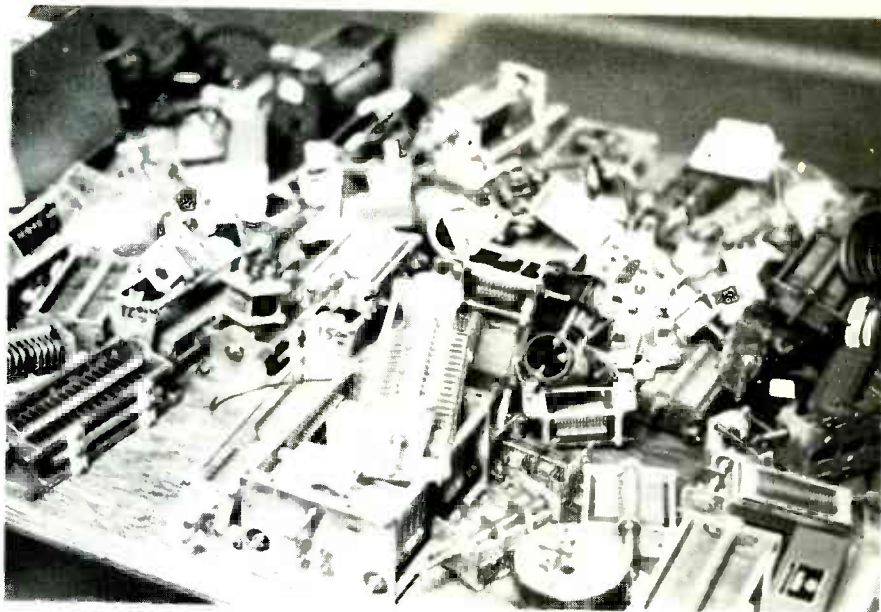There are two major kinds of fixed resistors: composition or carbon, and wire-wound. Normally, do not use wire-wound resistors in circuits carrying RF



**APPROPRIATE SUBSTITUTES** can be found for most electronic components, including variable capacitors. Flea markets are a good source for those components.

since they have a certain amount of inductance that can upset the associated RF circuit. However, carbon-type resistors of the appropriate power rating can be used to substitute for wire-wound types.

**2. Potentiometers.** Substitutes can usually be made having somewhat higher or lower values than those specified. Surplus pots can be bargains, but physical characteristics such as shaft length and type of shaft are important. Consider: Is the unit for screwdriver adjustment, or is the shaft designed to accept a knob? What about the pot's electrical characteristics, such as the "taper"—is it usable? Pots with "linear" or "audio" tapers are the types most frequently called for in construction projects. And is an on-off switch required on the control?

*One caution:* Wire-wound pots are frequently found in surplus. Those pots are most suitable for low-frequency, high-power applications, not for delicate solid-state circuitry. They are not for circuits that require high precision (resolution). Thus, for most work, standard carbon-composition pots represent the best selection.

When shopping for new pots, quality is paramount; cheap materials are synonymous with inferior performance, often evidenced by a pot that is hard to turn because of high-friction bearings. Cheap imports should be avoided; stick to top-quality pots in all construction projects.

**3. Capacitors.** Fixed capacitors come in a surprising variety. There are mica, Mylar, silver-mica, ceramic, oil-filled, paper, and electrolytic types. Each has specific applications. Mica types (especially silver-micas) and zero-temperature-coefficient ceramics are usually specified where low losses and high stability are essential; normally, you

should not substitute other types for them. Probably the best all-round capacitor for general purpose use is the Mylar polystyrene type—also one of the cheapest, and typically available for values between 5 pF and 0.5  $\mu$ F.

Standard tolerance ratings for most project-grade capacitors is  $\pm 10$  to 20%, though for some inexpensive general-purpose ceramic capacitors (including disc types) it's as wide as  $-30\%$  to  $+100\%$ . Exact capacitance is relatively unimportant in typical bypassing/filtering and coupling applications, and you can easily deviate as much as 50% from the spec value without trouble, sometimes much more (except at VHF and UHF). Mylar polystyrene capacitors also run in the 10–20% tolerance range, with 5% Mylars readily available, and 2.5% and 1% units available at somewhat higher prices.

As with resistors, capacitors can be substituted in series or parallel to yield different equivalent values, though the combining effects are the opposite to those of resistors: capacitors in series act like resistors in parallel, while capacitors in parallel act like resistors in series.

When two capacitors are placed in series, the total capacitance is less than that of either one, as determined by the simplified formula:

$$C_t = \frac{C_1 \times C_2}{C_1 + C_2}$$

Capacitors are additive when placed in parallel:

$$C_t = C_1 + C_2 + C_3 + \dots$$

Another handy formula is one to use when you need a lower value of capacitance and want to find the value needed to place in series with an available unit to

obtain the desired value. That value is given by the formula:

$$C_1 = \frac{C_2}{(C_2/C_1)-1}$$

The voltage-handling capability of the resulting capacitor chain should be considered, as should power-handling capability of series/parallel resistors. A standard electronics text should be consulted for more on that.


Most capacitors above 1  $\mu$ F are aluminum electrolytics and are polarized. Tolerances tend to be fairly loose because filtering and coupling applications usually don't call for precise values. Those types are often available with capacitances of 100,000  $\mu$ F or more, though usually at very low voltage ratings at those high capacitances. A related though more expensive capacitor is the tantalum type. The tantalum capacitor is generally superior to the standard electrolytic, and boasts tighter tolerance, smaller size (for equivalent capacitance), and lower leakage.

Except in specialized applications, such as in timing circuits where tantalums are generally preferred over aluminum electrolytics, exact capacitance isn't terribly important. When substituting, it's generally wise to err on the side of too-high capacitance rather than too-low. Surplus oil-filled types can normally be substituted for electrolytics having equivalent characteristics.

Substitutions are also possible with variable capacitors. The main considerations here relate to minimum and maximum capacitance. As a general rule, you can substitute a capacitor having a greater capacitance than the value specified. It may also be possible to substitute a variable capacitor that has somewhat less range than that specified, if you can determine the actual tuning range required in the circuit. That involves figuring the amount of circuit inductance and amount of capacitance required for a given tuning range, and is best done with the aid of a device such as the ARRL *LCF Calculator*, or using a computer. Note that junk box variables can be modified to become lower-value capacitors simply by removing rotor plates, and multi-section receiving variables can be paralleled to get higher capacitance.

In high-voltage circuits, be sure you observe maximum operating voltages that depend on plate spacing. Plate spacing should be equal to or greater than that specified by the designer, or you can refer to a catalog to convert spacings to voltage-handling capacities. Knowing the voltages in the circuit, you can easily check to see if your particular substitute is adequate for your purpose.

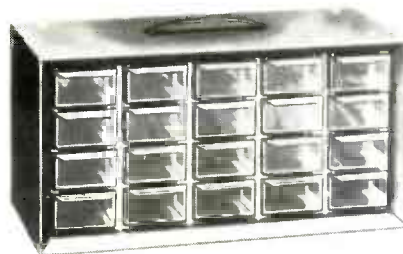**4. Diodes.** Besides resistors and capacitors, you'll often be faced with making substitutions for diodes of various kinds, both rectifier and small-signal types. The



**A 20-DRAWER CABINET** such as this is ideal for maintaining a well-organized junk box.

former are generally specified according to their maximum current and reverse breakdown ratings. It's possible, in many instances, to come up with a suitable replacement without having to resort to checking a data book. The 1N4148 is a good all-around small-signal type diode to have in the junk box as it is able to meet a wide range of substitution needs.

**5. Transistors.** Besides diodes, other types of discrete semiconductors that present substitution questions include bipolar transistors, FET's, SCR's, and UJT's. As with diodes, practically everyone sells some transistors, but few distributors stock each and every part number, particularly highly specialized and Japanese types.


Many transistor suppliers and manufacturers overly emphasize the difficulty of transistor substitution. From a practical standpoint, the many different types of transistors and related economic con-

siderations make it imperative that some substitutions be attempted. You'll need a transistor data book to determine proper specifications; once those numbers are available, you can apply them to select appropriate substitutes. Even using abbreviated substitution guides such as found in the Radio Shack catalogue can make the purchase of bargain-priced blister-pack replacement transistors practical and useful.

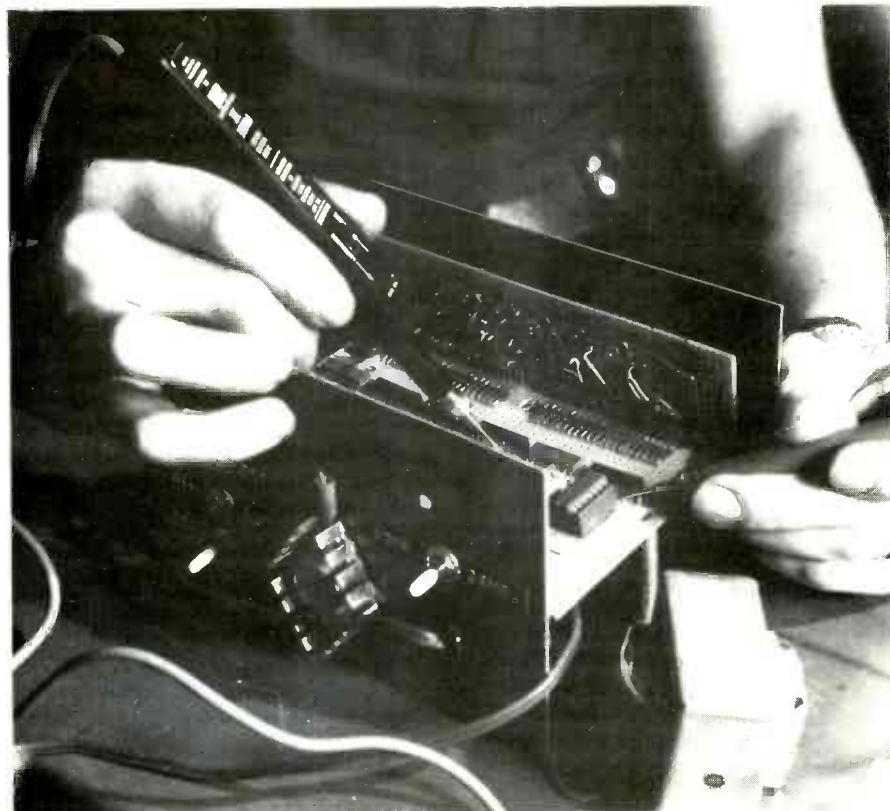**6. Integrated Circuits.** The silicon chemistry of integrated circuitry constitutes a key element of most sophisticated electronics construction projects. Because of their importance and widespread use, those devices are sold by most electronics suppliers. The devices range over a wide spectrum, and include linear, CMOS, TTL, DTL, ECL, LSI, and other types. The variety encountered precludes stocking up on any but the most common types.

There is little latitude in substituting IC types. A circuit specifying a particular IC usually requires *that* particular IC. In fact, it's usually not worthwhile to salvage IC's from scrap equipment unless the IC's can be clearly identified and there is some prospect of actual use for that particular device.

However, it's important to point out that IC designations often include alphabetical prefixes that simply indicate the device's manufacturer. There is no need to use an IC made by a particular manufacturer if the same basic device is available from other firms. You'll find that IC suffix letters aren't terribly critic-



**A MULTI-FUNCTION TEST PROBE**, such as the one shown here, is handy for finding good components in surplus or salvaged equipment.

## TABLE I—COMPONENT SUBSTITUTION GUIDELINES

The following constitute *general* guidelines for substitution of the most-used components: resistors, capacitors, inductors, rectifier diodes, and transistors. Refer to the text for discussion of other factors that should be considered in making parts substitutions, and for guidelines for other components.

### RESISTORS

*Resistance value:* within  $\pm 20\%$  of that specified.

*Resistance tolerance:* equal to or better than specified, but usually not critical.

*Power rating:* equal to or greater than specified.

### CAPACITORS

*Capacitance value:* within  $\pm 20\%$  of that specified, except in critical timing and tuning circuits.

*Capacitance tolerance:* equal to or better than specified, but usually not critical.

*Voltage rating:* equal to or greater than specified, or twice the maximum supply voltage.

*Type:* generally not important except in critical timing and tuning circuits.

### COILS/INDUCTORS

*Inductance value:* within  $\pm 20\%$  of that specified.

*Current rating:* equal to or greater than specified.

### RECTIFIER DIODES AND BRIDGE ASSEMBLIES

*Current rating:* equal to or greater than specified.

*Reverse breakdown voltage:* equal to or greater than specified.

### TRANSISTORS

*Type:* as specified (PNP or NPN, etc.).

*Collector current rating ( $I_c$ ):* equal to or greater than specified.

*Reverse breakdown voltage:* equal to or greater than specified.

*Gain (Beta or  $h_{fe}$ ):* equal to or greater than specified.

*Power rating:* equal to or greater than specified.

*Cutoff frequency:* equal to or greater than specified.

*Case style:* usually not important.

**NOTE:** *A transistor data book must be consulted for determining most of the specifications necessary for making substitutions.*

al, either. They usually indicate a change in the internal IC configuration that does not alter the basic function, though the suffix letter may indicate the package style. But, if you find a letter (or two) inserted between some of the numbers, it may indicate a significant modification that precludes easy substitution. In such cases, it's wise to consult a data book, paying particular attention to possible changes in pin numbering.

### 7. Power transformers and chokes.

When your project requires a very specific transformer, it may be best to order it directly from the manufacturer or his distributor.

On the other hand, if specs aren't too tight, or it's possible to connect windings in various configurations to obtain required voltages, it may pay to take advantage of specials and closeouts by mail-order distributors—though transformer offerings are usually limited in variety. Industrial surplus dealers generally have the best selection; transformers with the most unusual characteristics can turn up in surplus.

One of the main considerations in making transformer substitutions is adequate current/power handling capacity. You can substitute if the transformer in question has the same voltage rating with more current-carrying capacity, but it's risky to go the other way. However, if the transformer is rated in terms of continuous duty, and its intended use will be intermittent, a rating reduction of up to about 25% may prove to be quite acceptable.

Minor primary and secondary voltage substitutions can be made without

adverse effect. If you have a transformer that delivers a higher voltage than you want, you can drop the voltage with a series resistor or a voltage-divider system.

As for power-supply chokes, substitutions are usually easy. The specified value of a filter choke can usually be regarded as a minimum value. The inductance of chokes in series is additive; conversely, chokes in parallel function like resistors in parallel. The amount of capacitance required in a power supply is affected by the power-supply choke inductance—the choke and electrolytic capacitor work together to bring ripple down to an acceptable level.

In addition to inductance ratings, you must also take into account the current the choke must carry. Of course, you can use a choke with a higher current rating than specified. Using a somewhat lesser-rated choke is probably OK, unless the choke is rated at less than 75% of expected current. The inductance becomes less if more current is drawn through the choke than the unit is rated for, thus reducing the choke's filtering effectiveness.



**A DESOLDERING TOOL** makes removing parts from a surplus or salvaged piece of equipment simple.

**8. Switches.** Substituting switches can be tricky because of the numerous possible switching configurations and applications. You can always use a switch that has more contacts or sections than are required for a given circuit, as long as it has an adequate voltage rating. Often that information can be obtained from manufacturers' and distributors' catalogs. Similar considerations apply to relays, but selection criteria are complicated by relay coil voltage and current, and other operating characteristics.

**9. Tubes.** Most contemporary circuitry has abandoned the once-common vacuum tube, though a few tube designs survive, and there is still demand for tubes for replacement purposes. Tubes are becoming extremely expensive and difficult to find, and few are still manufactured in the United States. One good, low-cost source of once-common receiving tubes is *Cornell Electronics Company*, 4217 University Avenue, San Diego, CA 92105; the firm stocks a wide variety of bargain-priced receiving tubes. *Radio Shack* also provides a special-order service that includes about 2000 different types. If you don't have the tube you need, of course, you'll have to buy it. But a quick check of a tube-substitution manual, or the ARRL's *Radio Amateur's Handbook* (it lists different tube types and possible substitutions if available) may prove worthwhile.

**10. Other components.** There are many other components that the project builder will find useful to keep in his junk box or bench stock for the purpose of convenient substitution in construction projects.

We can't treat all of them here. But some that come to mind include plugs, jacks, audio and IF transformers, transistor and IC sockets, battery clips, terminals, hardware, alligator and crocodile clips, meters, connectors, chassis, PC boards, and cabinets.

In many instances your best guide to making intelligent substitutions is simple, ordinary common sense, as well as an understanding of when not to use substitute parts but to go out and acquire a specified part.


Getting into the practice of breadboarding project circuitry will not only help refine a circuit before commitment to a final design, but will make substitutions easier because it gives you a chance to double-check your choices. Solderless breadboards eliminate a great deal of the trouble involved in circuit development and make desk-top experimentation—and substitution—much easier.

Table 1 lists popular component substitution considerations in tabular form.

When we continue this article, we'll take a closer look at where you can obtain your parts for projects. Among the topics we'll cover will be how to successfully use surplus and salvaged parts, including how to test and identify them

R-E
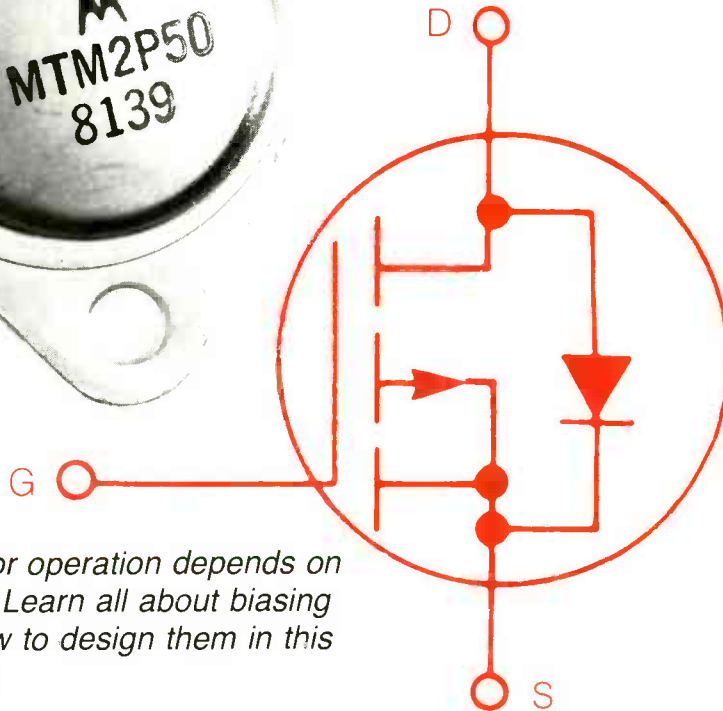
## How to Design Analog Circuits - Biasing Transistors



Proper transistor operation depends on proper biasing. Learn all about biasing circuits and how to design them in this month's article.

MANNY HOROWITZ

**Part 5** LAST MONTH, WE BEGAN our discussion of bipolar and FET transistors by looking at the structure of those devices and at some basic transistor circuits. One of the things we mentioned was that if a bipolar device were used in a Class A common-emitter circuit, for linear operation the collector voltage (with no input signal present), should be set at one half the supply voltage. The no-input-signal condition is commonly referred to as the quiescent operating point. (Similarly, in the case of an FET in a common-source circuit, the drain voltage should be one half the supply voltage). That, however, is merely an approximation; the actual operating point varies with the specific requirements of the circuit. In any event, once the proper operating point has been selected, the device must be *biased* for that point. Just how that is done is the topic of this month's article.

### Bipolar transistors

There are essentially two types of bias circuits that are used with bipolar devices. Although there may appear to be many more, the others are simply variations of

those two circuits. And even the two circuits are variations of each other.

But why do we need many bias circuits? They arose mainly because of the high leakage current,  $I_{CBO}$ , that flowed from the collector to the base in early germanium transistors. If that leakage current also flowed through the base-emitter junctions (as it normally did), it was multiplied by beta ( $\beta$ ) to make it into a large undesirable leakage current,  $I_{CEO}$ , that flowed in the collector and emitter circuits. And to compound the problem,  $I_{CBO}$  and  $I_{CEO}$  doubled every time the temperature of the transistor increased by  $10^\circ\text{C}$ . Although those factors are still important in modern silicon transistors, the effect on the collector current is reduced considerably because the leakage current in silicon transistors is frequently low enough to be ignored.

In addition to leakage current, variations in the operating parameters from device to device, as well as with temperature, can cause problems. The value of  $\beta$ , for instance, will vary from device-to-device of the same type, as well as with

temperature and collector current,  $I_C$ . In addition, the value of  $I_C$  at the operating point will vary with several parameters. Among those are  $V_{BE}$ , the voltage drop across the base-emitter junction, which itself varies with temperature;  $V_{BB}$ , the base supply-voltage;  $r_c$ , the collector-to-base resistance in a common-base circuit, and  $r_d$  the collector-to-base resistance in either a common-emitter or common-collector circuit.

But, once the operating point has been established for a circuit, ideally it should not be effected by differences in parameters from device-to-device, or by any external factors such as temperature. That is the reason for all of the bias-circuit variations—they are designed to help stabilize the operating point. In theory, if the proper bias circuit is used, the operating point will not change regardless of any change in any of the factors mentioned. However, theory and what really happens are not always the same. But even so, using the proper bias circuit will minimize any variations of the operating point sufficiently so that the circuit will

still operate as intended.

To design a bias circuit properly, it is important to know how a variation in one variable will effect the other variables in the circuit. Because of that, three *stability factors* that relate the change of one factor to the change in another have been derived. They are:

$$S = \frac{\Delta I_C}{\Delta I_{CBO}} \quad (1)$$

which relates the change of collector current to the change in leakage current. The stability factor relating the change of collector current to the change in  $V_{BB}$  is:

$$S_E = \frac{\Delta I_C}{\Delta V_{BB}} \quad (2)$$

while the equation relating the collector current change to the change in  $\beta$  is:

$$S_B = \frac{\Delta I_C}{\Delta \beta} \quad (3)$$

Equations used to relate the various components in the circuit to the various stability factors, will be noted as each bias circuit is described. In each case, it is desirable that stability factors be as close to 1 (the perfect stability factor) as possible. Should more than one stability factor differ from 1, the effects of all variations must be taken into account when evaluating the design.

### Bipolar transistor bias circuits

The simplest bias circuit to be described here is shown in Fig. 1. The base current,  $I_B$ , originates at  $V_{BB}$  and is delivered to the base through  $R_B$ . However,  $V_{BB}$  often does not exist as an independent supply; instead  $V_{CC}$  is used to supply both base and collector current. In that case,  $R_B$  is connected to  $V_{CC}$ , and that supply serves as both  $V_{CC}$  and  $V_{BB}$ .

In Fig. 1, all base current from  $V_{BB}$  flows through the base-emitter junction. If we consider the voltage across that junction,  $V_{BE}$ , as negligible when compared to  $V_{BB}$ , the base current due to the supply is  $V_{BB}/R_B$ . Collector current due to that base current is approximately equal to  $\beta I_B$ .

Next, let us add the effect of  $I_{CBO}$ , the leakage current that flows from the collector to the base. After flowing through the base-emitter junction, it is multiplied by beta. That  $\beta I_{CBO}$  flows in the collector and emitter circuits and substantially effects the collector and emitter currents. Collector current due to  $I_{CBO}$  is thus  $\beta I_{CBO} = I_{CEO}$ . (Note that in our discussions beta has been assumed to be much greater than 1. Thus only  $\beta$  is shown in formulas rather than  $\beta + 1$ .)

Finally, we have some collector current flowing due to  $r_d$ , the collector-to-

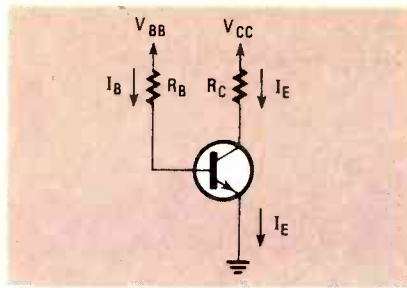


FIG. 1—A SIMPLE CIRCUIT for biasing bipolar transistors. Often there is no separate  $V_{BB}$  supply; instead  $V_{CC}$  is used to supply both the collector and base.

emitter resistance of the transistor. That resistance can be determined from the common-emitter collector-characteristics curve shown in Fig. 2. Using the procedure described in our last article (see the August 1982 issue of **Radio-Electronics**, draw the load line on the curve. The next step is to determine the operating or quiescent point needed to insure linear operation. If, for instance, you require that the collector current swing from 0 to  $I_{C(MAX)}$ , the collector current at the quiescent operating point,  $I_{CQ}$ , would be equal to  $I_{C(MAX)}/2$ . Find that point on the  $I_C$  axis. The voltage at the quiescent point,  $V_{CEQ}$ , is usually equal to about  $V_{CC}/2$ . Drawing a line perpendicular to the  $I_C$  axis at  $I_{CQ}$ , and a line perpendicular to the  $V_{CE}$  axis at  $V_{CEQ}$ , the point at which the two lines cross is the operating point. As drawn, that point falls on the  $I_B = 100 \mu A$  curve. Collector resistance,  $r_d$ , is the slope of that  $I_B$  curve around the operating point. The slope is found by noting two points that are equidistant from the operating point, and finding  $I_C$  and  $V_{CE}$  for those points. Assuming that the collector voltage and current at one point are  $V_{CE1}$  and  $I_{CE1}$ , and  $V_{CE2}$  and  $I_{CE2}$  at the other, then:

$$r_d = \frac{V_{CE2} - V_{CE1}}{I_{CE2} - I_{CE1}} \quad (4)$$

As indicated,  $r_d$  is the collector-emitter resistance of the transistor when it is used

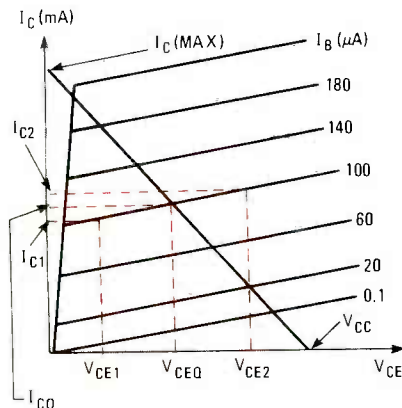


FIG. 2—ONCE THE QUIESCENT POINT has been found, the value of  $r_d$  is equal to the slope of the  $I_B$  curve around that point.

in a common-emitter or common-collector circuit. In a common-base circuit, that collector-emitter resistance is much higher and equal to  $\beta r_d$ ; that quantity is called  $r_c$ .

A portion of the total collector current is due to the presence of  $r_d$  in the circuit. It is equal to the collector-emitter voltage,  $V_{CE}$ , divided by  $r_d$ . Obviously,  $V_{CE}$  is equal to the supply voltage less the voltage drop across the collector resistor,  $R_D$ , or  $V_{CC} - I_C R_C$ . Consequently, the total quiescent collector current flowing in the circuit of Fig. 1 is:

$$I_C = \beta I_B + I_{CEO} + \frac{V_{CC} - I_C R_C}{r_d}$$

which simplifies to:

$$I_C = \frac{\beta I_B + I_{CEO} + V_{CC}/r_d}{R_C/r_d + 1} \quad (5)$$

Should  $R_C$  be less than 10% of  $r_d$ , the effect of  $r_d$  becomes negligible, and all factors in the equation involving that term can be eliminated. We will then end up with the simple relationship:

$$I_C = \beta I_B + I_{CEO}$$

Finally, remembering that  $I_B = V_{BB}/R_B$ , we get:

$$I_C = \frac{\beta(V_{BB} + R_B I_{CBO})}{R_B} \quad (6)$$

You can usually use equation 6 and ignore  $r_d$  in most designs. But do not forget about  $r_d$ . It will be important later on when we discuss AC gain and the output impedance of transistor circuits.

The various stability factors for the circuit shown in Fig. 1 are:

$$S = \beta \quad (7)$$

$$S_E = \beta/R_B \quad (8)$$

$$S_B = \frac{I_{CBO} R_B + V_{BB}}{R_B} \quad (9)$$

Equation 9 indicates by how much the collector current will change for a specific change in  $\beta$ . Thus if a transistor with a  $\beta$  of 80 is substituted for one with a  $\beta$  of 40, the quiescent collector-current will double. To see how we came to that conclusion, let's digress a bit. First, as we saw in equation 3,  $S_B = \Delta I_C/\Delta \beta$ . Expanding further, equation 3 can be rewritten as  $\Delta I_C = \Delta \beta(I_B)$ . Secondly, since  $I_{CBO}$  is generally small enough to be ignored, and since  $V_{BB}/R_B$  is equal to  $I_B$ , in this case, the stability factor,  $S_B$ , defined by equation 9 is approximately equal to  $I_B$ . Thus  $\Delta I_C = \Delta \beta(I_B)$ . Originally,  $I_C$  was equal to the initial  $\beta$  of 40 multiplied by  $I_B$ , or  $40I_B$ . If  $\Delta \beta = 40$ , and  $\Delta I_C = \Delta \beta I_B$ , then



$\Delta I_C = 40I_B$ . Finally, the total collector current when  $\beta$  is increased from 40 to 80 is  $I_C + \Delta I_C$ , or  $40I_B + 40I_B = 80I_B$ .

### Improving stability

Stability can be improved by adding an emitter resistor,  $R_E$ , to the circuit in Fig. 1. If that is done, equations 7, 8, and 9 are modified to become:

$$S = \frac{\beta(R_E + R_B)}{\beta R_E + R_B} \quad (10)$$

$$S_E = \frac{\beta}{\beta R_E + R_B} \quad (11)$$

$$S_{\beta} = \frac{(R_E + R_B) V_{BB} + I_{CBO} R_B (R_E + R_B)}{(\beta R_E + R_B)^2} \quad (12)$$

In this arrangement, base current is less than it was when there was no emitter resistor. It is reduced because the emitter resistor,  $R_E$ , is reflected into the base circuit as a resistor equal to  $\beta R_E$ . Because of that, the base current becomes  $(V_{BB}/(R_B + \beta R_E)) + I_{CBO}$ . In addition,  $I_C$  becomes equal to  $\beta I_B$ .

The bias circuit shown in Fig. 3 is used when stability is a very important consideration. The circuit in Fig. 1, and the variation we created by adding an emitter resistor, are simplified versions of that circuit. In it,  $V_{BB}$  has been eliminated; instead,  $V_{CC}$  is used as both the collector and base supply.

*Thevenin's theorem* must be used in order to determine the base current in the circuit in Fig. 3. That theorem states, in part, that any network of voltage sources and resistances can be simplified to a single voltage source in series with a single resistance. Use the following steps to apply that theorem to the circuit. Those steps are shown in Fig. 4.

First, as shown in Fig. 4-a, separate the bias resistor circuit from the rest of the circuit.

The second step, as shown in Fig. 4-b, is to determine the voltage at the junction of  $R_B$  and  $R_X$ . That voltage is called the *Thevenin voltage*,  $V_{TH}$ , and, since  $R_B$  and  $R_X$  make up a simple voltage divider, is

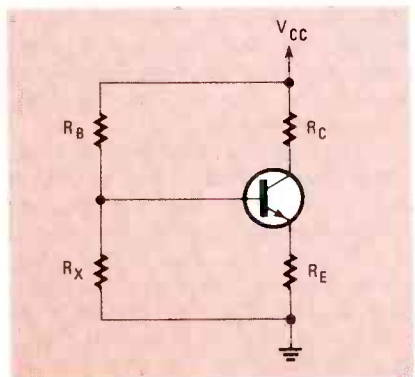


FIG. 3—IF BETTER STABILITY IS REQUIRED, the bias circuit shown here can be used.

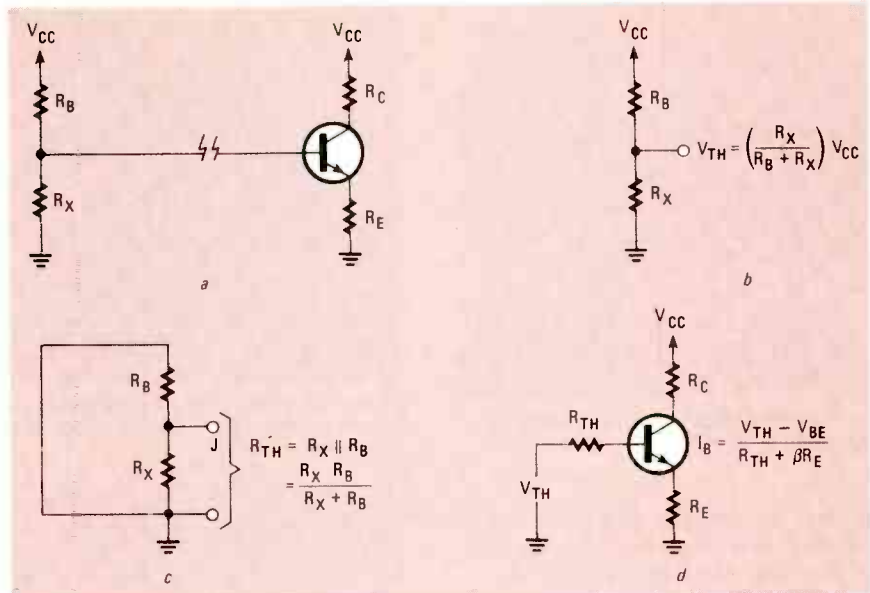


FIG. 4—TO EVALUATE THE BASE CURRENT of the circuit shown in Fig. 3, Thevenin's theorem must be used. The steps followed in applying that theorem are shown here.

equal to  $V_{CC}(R_X/(R_B + R_X))$ .

The third step, as shown in Fig. 4-c, is to short the supply to ground and determine the *Thevenin resistance*,  $R_{TH}$ . That is the resistance seen when looking back toward  $R_X$ ; in other words, the resistance between the junction "J" and ground. In this case, it is the parallel combination of  $R_X$  and  $R_B$ , which, of course, is equal to  $R_X R_B / (R_X + R_B)$ .

The fourth, and final step, shown in Fig. 4-d, is to reconstruct the original circuit, substituting  $V_{TH}$  for  $V_{CC}$ , and  $R_{TH}$  for  $R_B$  and  $R_X$ . The Thevenin voltage,  $V_{TH}$ , and the Thevenin resistance,  $R_{TH}$ , are connected in series with the base of the transistor as shown. The base current can now be calculated from the formula:

$$I_B = \frac{V_{TH} - V_{BE}}{R_{TH} + \beta R_E}$$

The value of  $V_{BE}$  is usually .017-volt for a silicon transistor, and 0.2- to 0.3-volt for a germanium device. Once you've calculated  $I_B$ , the collector current is simply  $\beta I_B$ .

In this type of circuit, the effect of leakage current,  $I_{CBO}$ , is reduced because some of it is diverted from the base-emitter junction to  $R_X$ . A good rule of thumb to use when designing this type of circuit is to make  $R_X$  equal to less than ten times the size of  $R_E$ .

As we mentioned earlier, there are two basic types of bias circuits. So far, all of the circuits we've examined were variations of one type. Let's now turn our attention to the second type. It is shown in Fig. 5. Here,  $R_B$  is connected to the collector of the transistor being biased instead of to  $V_{CC}$ . In that circuit, negative feedback from the collector to the base acts to reduce the value of the stability

factors, a desirable result. In determining the operating point, the simplest approach is to again use Thevenin's theorem. Just adapt the method described for the circuit in Fig. 3 to this circuit, using the value of  $V_{CE}$  that you are designing for instead of  $V_{CC}$ . A reasonably accurate formula for determining collector current is shown as equation 13. Note that  $R_C$  and  $I_{CBO}$  are included in the equation. Stability factors for this circuit are shown in equations 14, 15, and 16.

$$I_C = \frac{\beta[R_X V_{CC} + I_{CBO}(A + R_X R_B)]}{\beta A + R_X R_B} \quad (13)$$

$$S = \frac{\beta(A + R_X R_B)}{\beta A + R_X R_B} \quad (14)$$

$$S_E = \frac{\beta R_X}{\beta A + R_X R_B} \quad (15)$$

$$S_{\beta} = \frac{(R_X V_{CC} + R_X R_B I_{CBO})(A + R_X R_B)}{(\beta A + R_X R_B)^2} \quad (16)$$

Where  $A = R_E R_C + R_E R_B + R_E R_X + R_X R_C$ .

Those current and stability equations can be applied easily, with just slight modifications, to the circuit in Fig. 3. In equations 13 through 16,  $R_C$  is an important factor in determining the bias. It plays no part, however, in determining the stability and quiescent current for the circuit in Fig. 3. When applying those equations to that circuit, let  $R_C$  equal 0. That eliminates all terms containing  $R_C$ . If, in addition to setting  $R_C$  equal to 0,  $R_X$  was made infinite by removing it from the circuit and  $R_E$  was made equal to 0, or

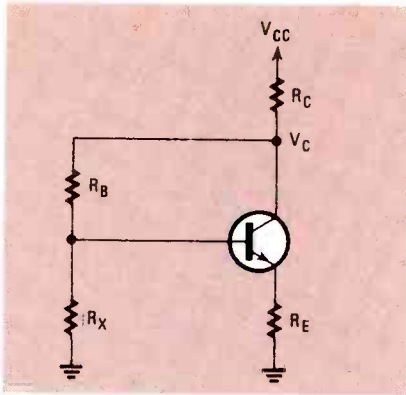


FIG. 5—THIS CIRCUIT is one of the many variations of the two basic bias circuits.

shorted, we end up with equations 6 through 9; those were, as you recall, used for the circuit shown in Fig. 1. Should  $R_E$  be left in the circuit, the equations will be identical to equations 10, 11, and 12. Thus, equations 6 through 12 are simply variations of equations 14, 15, and 16.

There are many variations of the simple circuits we have presented thus far. One of those is to remove  $R_X$  from the circuit of Fig. 5. That does reduce stability somewhat, however. Equations 13 through 16 still apply, but are modified by removing all terms containing the expression  $R_X$ .

### Temperature compensation

Base-emitter voltage variation with temperature is an important consideration, especially in power circuits, because in those the temperature of the transistors tends to increase by a considerable amount. The circuit most-commonly used to compensate for that is shown in Fig. 6.

Diode D is placed into the circuit as shown so that it is always on. The diode used should have the same voltage/temperature characteristic as the forward biased base-emitter junction of the transistor. It should also be placed close to the transistor so that both of their temperatures will vary in a similar manner. With this configuration, the voltages across the diode and the base-emitter junction are always identical. Because of that, the voltage across  $R_E$  and  $R_X$  are also always identical, regardless of any changes in  $V_{BE}$  caused by temperature. Thus stability is improved.

The final variation we'll discuss here, is the one shown in Fig. 7. In most bias circuits,  $R_E$  is connected between the emitter and ground. Here, however, a battery or other voltage source,  $V_{EE}$ , is inserted between the emitter and ground. As a result, the base current,  $I_B$  is approximately equal to  $V_{EE}/(R_X + \beta R_E)$ ; the collector current, as usual, is equal to  $\beta I_B$ . The stability factors for that circuit are essentially the same as those calculated using equations 10 through 12. When applying the equations here,

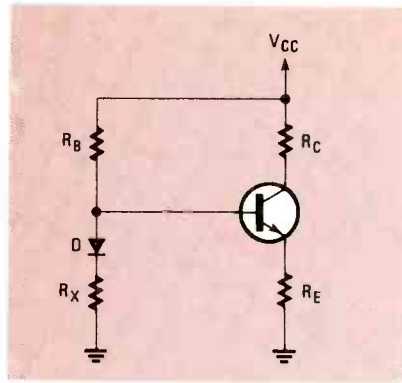


FIG. 6—TO COMPENSATE for variations caused by temperature, a diode can be placed in the base circuit as shown.

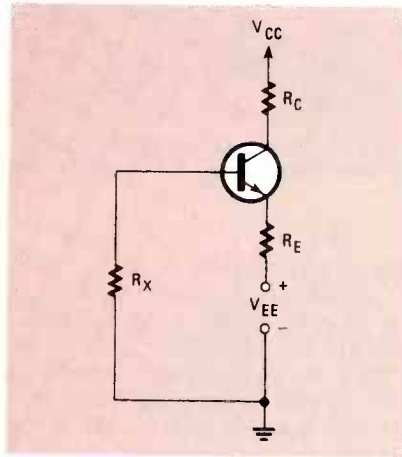


FIG. 7—IN THIS VARIATION, a battery or other voltage source is inserted between the emitter and ground.

however, substitute  $V_{EE}$  for  $V_{CC}$ , and  $R_X$  for  $R_B$ .

In summary, as a general procedure when designing bias circuits, first determine the ideal quiescent collector voltage and current. Divide the collector current by  $\beta$  to find approximately what the base current should be. Next design a base circuit to establish those conditions. Remember that those conditions should be relatively insensitive to temperature changes, as well as parameter variations from device to device. To make certain that they are, you must check the stability factors. Any of the circuits we've discussed, as well as many other variations, can be used when biasing bipolar transistors. You must determine how much operating point instability your design can tolerate. Start with the simplest circuit and calculate the stability factors. If collector current variations due to these factors are too great, increase the complexity one step at a time. Never go beyond the simplest circuit you can use to satisfy your requirements.

### Biasing JFET's

Gates of n-channel JFET's are usually made negative with respect to the source. But, as no gate current flows if the gate is made just slightly positive with respect to

the source of a JFET, up to +0.5 volt may be placed at the gate. Two arrangements used for establishing the proper bias voltage are shown in Fig. 8.

In Fig. 8-a, drain current,  $I_D$ , flows through  $R_D$  and  $R_S$ . Thus, the source current,  $I_S$ , and  $I_D$  are equal to each other. A voltage equal to  $I_D R_S$  is developed across  $R_S$ . That voltage is called  $V_{RS}$  and has the polarity shown.

A leakage current,  $I_{GSS}$ , flows from the gate to the source. The value of  $I_{GSS}$  at 25°C is often found on the specification sheets of the device. That leakage current, however, increases with temperature—usually doubling with each increase of 10°C. The leakage current flows through  $R_G$ , developing a voltage,  $V_{RG}$  equal to  $I_{GSS} R_G$ . The polarity of that voltage is also shown in Fig. 8-a.

Voltage between the gate and source is equal to  $V_{RS} - V_{RG}$ . The value of  $V_{RS}$  is usually adjusted to be larger than the value of  $V_{RG}$  so that the gate will be biased negative with respect to the source. That's how the bias for the circuit shown in Fig. 8-a is established.

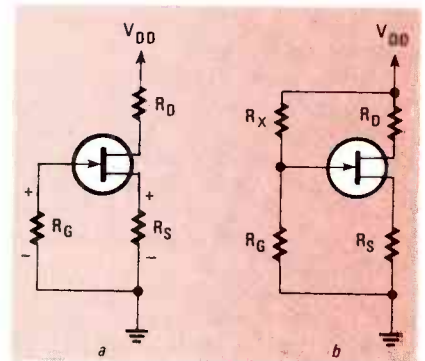


FIG. 8—EITHER OF THESE CIRCUITS can be used when biasing either JFET's or MOSFET's.


The source resistor is an important factor in enhancing the stability of the circuit as it is used to counteract any increase of  $I_{GSS}$  caused by a change in temperature. Circuit stability can be improved by increasing the size of  $R_S$ . But there is a limit to this. Should  $R_S$  be increased too much, the voltage developed across it can be high enough to bias the transistor near or at pinch-off. That is, of course, undesirable. The value of the source resistor must be chosen so that the proper bias point is established when the voltage developed across  $R_G$  is subtracted from the voltage developed across  $R_S$ .

A larger source resistor can be used with the circuit shown in Fig. 8-b. In that circuit, a sizable positive voltage can be developed across  $R_G$  due to the presence of  $+V_{DD}$  and the action of the voltage divider made up of resistors  $R_X$  and  $R_G$ . That positive voltage is increased somewhat by the presence of leakage current  $I_{GSS}$ . To determine the gate-to-source bias voltage, subtract the voltage de-

*continued on page 102*

# BUILD THIS

## STEREO IMAGE

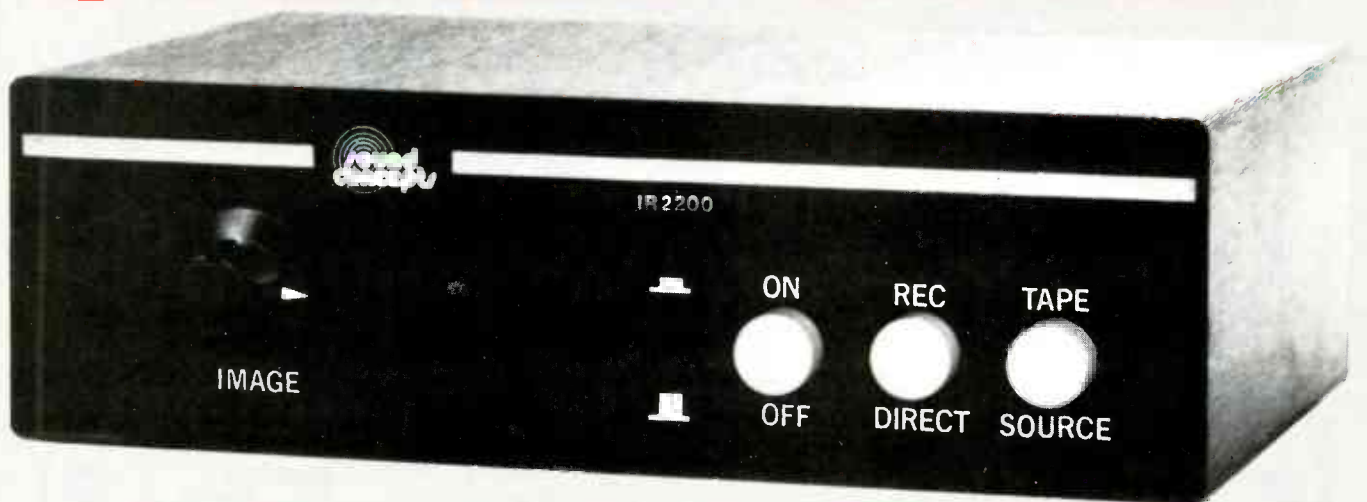

## EXPANDER

*Add an extra dimension to your recorded music with this Stereo Image Expander. Build it and hear what you've been missing.*

JOEL COHEN

**Part 2** IN THE FIRST PART OF this article, we looked at the theory behind the Stereo Image Expander. This time we'll apply what we've learned and build our own.

### Assembly

A foil pattern for the expander PC-board is shown in Fig. 11, and a parts placement diagram in Fig. 12. Figure 13 will also help you in completing the board. Some of the instructions here pertain specifically to the parts supplied with the kit available from the supplier indicated in the Parts List, but may also be applicable to you if you're building from scratch.

Pin 1 of each IC is indicated by an indented dot and all but IC5 are mounted with pin 1 facing towards the rear of the board. The bucket-brigade device, IC6, is subject to damage from static charge—it's a good idea to be sure that you are grounded before handling it. The use of IC sockets is recommended.

The BBD, incidentally, can be either an SAD512 or SAD1024—the pinouts are identical. The SAD1024 contains two SAD512's, and one of them will simply not be used.

Be sure to observe the polarities of the electrolytic capacitors and diodes. Note that regulators IC1 and IC2 are mounted

with their center leads bent back toward the curved part of the package, while the transistors they resemble have their center leads bent slightly forward, toward the flat sides of the packages. Don't forget the two jumpers shown in the parts placement diagram.

The transformer must be installed with pins 1 and 2 toward the rear of the board. Bend the two mounting tabs away from the transformer and solder them to the foil side of the board. If you are using the phono jacks provided by the supplier shown in the Part List, cut off the plastic tabs at their rear corners before attaching them and be sure they are firmly seated parallel to the board before soldering. The switch bodies must be spaced .093-inch above the top of the board if the cabinet supplied with the kit is used. If the switches do not have shoulders on their mounting pins, use three plastic spacers over the pins at the front of S3 and the rear of S1 and S2. Be sure the switches and IMAGE control are seated parallel to the board so they will fit into the holes in the chassis.

To mount the LED, bend its leads at a 90° angle while holding it towards you with the anode lead on your right. Solder it in so that the bend is 1/2-inch above the top of the board. Install the completed board in its enclosure, and attach the line cord. Be careful of stray strands of wire,

especially near the grounded board-mounting screw at the rear corner.

### Alignment

Only one adjustment is required; the BBD bias which is set by R7. There is about a 2-volt window for signals to pass through the BBD and the bias is set for the center of that range so that the maximum peak-to-peak signal can pass through without clipping. There is enough headroom in the design of the expander to allow for individual IC variations if the bias is simply set to +3.5 volts.

If you want to "fine tune" the expander, apply about 1.5-volts RMS at 1 kHz to just the left input and observe the waveform present at jumper J1. If the bias is too high, the top of the sinewave will be clipped; if it's too low, the bottom will be clipped. At the optimum setting the waveform will be just slightly clipped at both top and bottom.

### Rooms and loudspeakers

While most of us would find it difficult to tell the difference between one amplifier and another by ear, we all know that different speaker-systems have different qualities and that the sound from a particular system can vary depending on where it is located in a room. Most of the sound energy reaching our ears comes not

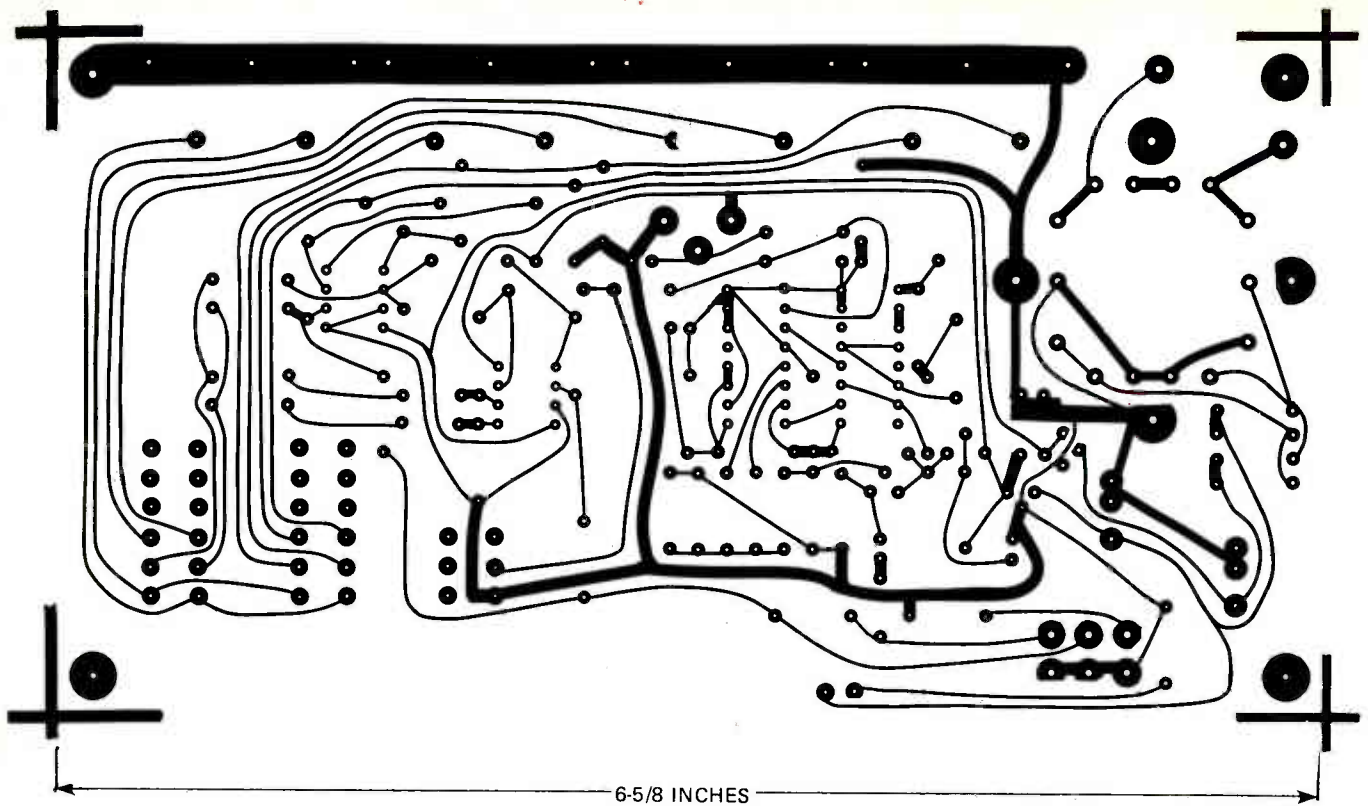


FIG. 11—STEREO IMAGE EXPANDER is constructed on single-sided PC board. The use of IC sockets is recommended.

directly from the speakers, but from secondary reflections of the sound from the walls, floor, and ceiling. The frequency response of that sound energy is shaped by the absorption characteristics of the surface it reflects from. The stereo image, however, is formed entirely by the first-arrival sound traveling directly from the loudspeakers to our ears.

Several conditions are needed for a good stereo image, and they are the same whether that image is expanded or not. First, the listening position must be the same distance from each speaker so that each ear hears its own speaker first. It is also helpful to point the speakers in toward the listening position. Second, the first-arrival sound from the speakers should precede the arrival of the first *reflected* sound by as long a time as practical, with one or two milliseconds being the minimum. That usually requires that the speakers be two feet or more from any wall or large piece of furniture and no more than 10 or 12 feet from the listening position. Third, the two speakers should be separated by an angle of 40°; that is, an imaginary line drawn to each speaker should form a 20° angle with one drawn from the listener to a point directly between them. That means that the distance between the centers of the two speakers should be 7/10 of the distance from each speaker to the listening position. Fourth, the speakers must be connected in phase. The easiest way to test that once they are positioned is to tune in some FM interstation hiss or a monophonic program. If the

**All resistors 1/4-watt, 5%, unless otherwise specified**

- R1, R6, R14, R16, R17—1000 ohms
- R2, R4, R25, R26, R30, R31—100,000 ohms
- R3, R5—47,000 ohms
- R7, R15, R23, R24, R27-R29—20,000 ohms
- R3, R5—47,000 ohms
- R7, R15, R23, R24, R27-R29—20,000 ohms
- R8—100,000 ohms, PC-mount potentiometer
- R9, R13—4.7 ohms
- R10, R20, R22, R34—4700 ohms
- R11—100 ohms
- R12—2000 ohms
- R18, R19—10,000 ohms
- R21—100,000 ohms, potentiometer, audio taper
- R32, R33—390 ohms

**Capacitors**

- C1, C2—470  $\mu$ F, 35 volts, electrolytic
- C3, C4, C6-C8, C12—0.1  $\mu$ F, ceramic disc
- C5—47  $\mu$ F, 16 volts, electrolytic
- C9, C17, C18—0.01  $\mu$ F, axial ceramic or ceramic disc
- C10, C13, C16—10  $\mu$ F, 16 volts, electrolytic
- C11—100 pF, axial ceramic or ceramic disc
- C14—390 pF, axial ceramic or ceramic disc
- C15—1500 pF, axial ceramic or ceramic disc

**Semiconductors**

- IC1—LM340L15, 15-volt positive regulator

**PARTS LIST**

- IC2—LM320L15, 15-volt negative regulator
- IC3, IC4—MC4558 dual op-amp
- IC5—CD4049 CMOS hex inverter
- IC6—SAD512 or SAD1024 N-channel bucket-brigade device (Reticon. Also Radio Shack 276-1761.) (See text.)
- Q1, Q2—2N2222, 2N3904 or similar
- D1-D4—1N4002 or 1N4003
- LED1—jumbo red LED
- T1—35 volts, center-tapped, PC-mount (Dale PL-12-09 or similar)
- S1-S3—pushbutton switch assembly: 3 DPDT or 1 DPDT, 2 4PDT (Schadow F-series or Centralab PB20-series)
- J1-J8—RCA-type phono jack, right-angle PC-mount

**Miscellaneous:** PC board, IC sockets, enclosure, line cord, strain relief, hardware, etc.

The following are available from Sound Concepts, Inc., P.O. Box 135, Brookline, MA 02146: assembled and tested IR2200 stereo image expander, \$169.00; kit of all parts (KIR-1), \$95.00; PC board (KIR-2), \$16.00; T1 (KIR-3), \$7.50; all pots, knobs, switches and jacks (KIR-4), \$12.50; all semiconductors and sockets for them (KIR-5), \$19.00. Please add \$2.00 for shipping and handling; MA residents add 5% sales tax. If at all possible give street address for UPS delivery. Please add 10% (\$5.00 minimum) for parcel post outside continental U.S.A.

speakers are in phase the sound will appear to come from a point directly between them. If they are out of phase, it will seem to come from the sides, or from each speaker individually. If the apparent

source is diffuse, the speakers should be repositioned as described above and again checked for phasing.

Finally, the speakers themselves must produce a sharp coherent wavefront.

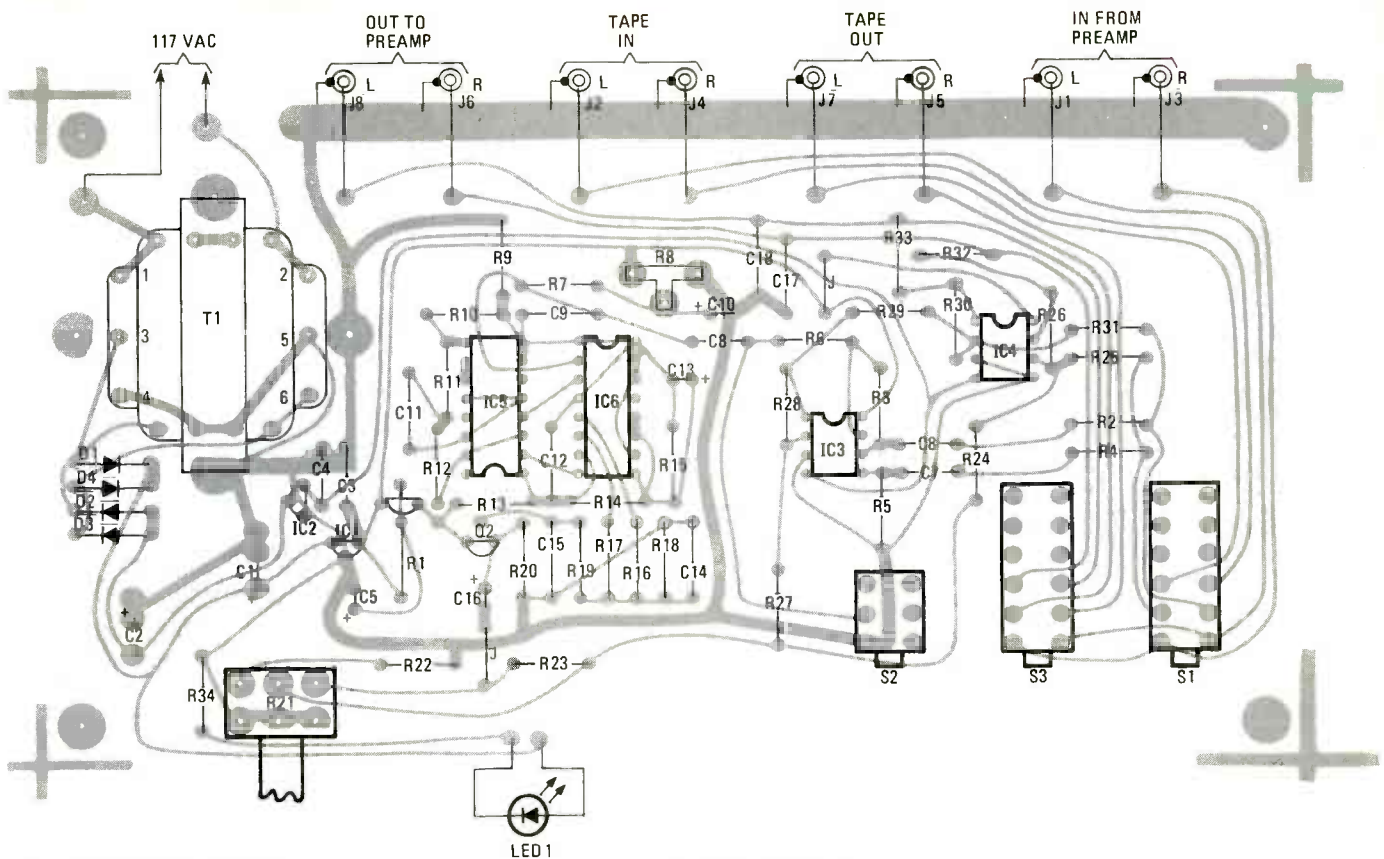


FIG. 12—PROVISION IS MADE for mounting right-angle input and output jacks directly on board.

Two- and three-way speaker systems with a single in-line vertical array of drivers usually work best. Omnidirectional speakers, or those with multiple drivers covering the same frequency range, cannot create as sharply focused an image.

You can actually check all this out before trying an image enhancer. Using a mono signal to get a tightly focused single sound-source located between the speakers is the best and easiest way to judge the imaging capability of your speakers in your listening room. Once you are set up correctly, you will probably be impressed with how much better your stereo system sounds—even without expansion.

#### Installation and use

The stereo image expander is intended to be connected in the tape-monitor loop of your preamplifier or receiver. Provision is made in the expander for connecting a tape recorder. The recorder can be used in the normal manner when the preamp's tape-monitor switch is on and S1 of the expander is in the TAPE position. Image-enhanced tapes that can be played back *without* the expander can be made when S3 is in the REC position. You should never have S1 and S3 pushed in at the same time since that effectively connects the recorder's output back to its input.

The recorder-output jacks from your receiver or preamp should be connected to the INPUT FROM PREAMP jacks, J1 and

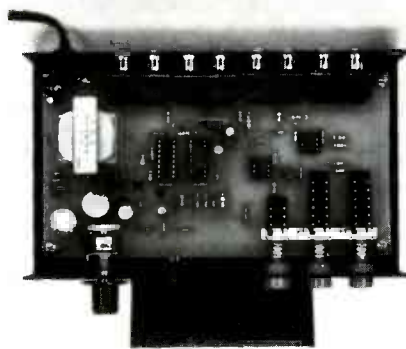


FIG. 13—NOTE HOW LED is mounted *above* the board, not flush with it. All components including transformer and switches, are soldered to board.

J3, on the expander and the OUTPUT TO PREAMP jacks, J6 and J8, to your tape-input or tape-monitor jacks. The expander's TAPE OUTPUT jacks, J5 and J7, are connected to the line-input jacks on the recorder and its line-output jacks connected back to the TAPE INPUT jacks, J2 and J4, on the expander.

If you are using two tape-loops and two recorders, place the expander in loop 2. To play unenhanced tapes through the expander, use the tape-monitor switch corresponding to the loop the recorder is in. With S1 in the TAPE position, the signal comes directly from the recorder connected to the expander, and in the SOURCE

position the signal is supplied by the receiver or preamp. If the expander is in loop 2 and you want to listen to the recorder in loop 1, either engage both tape monitor switches or—if you have them—the TAPE MONITOR 2 and DUB 1 TO 2 switches on the preamp or receiver.

If you have other signal processors in your system the expander should be the last one in the chain so that there is a minimum loss of phase integrity. If, for example, you already have an equalizer in your tape loop with a recorder plugged into it, plug the expander into the equalizer's tape jacks and the recorder into the expander's tape jacks. The expander can also be connected to the external-processor loop or between the preamp and power amp if you don't wish to use it for recording.

#### Listening

Before you make a critical evaluation of the stereo image expander's capabilities, make sure your system is set up as described earlier. Start with a record or tape of a good live or concert hall performance, preferably of a large orchestral work so you have a realistic frame of reference. (Most of the recent Telarc records have excellent imaging.) You may want to turn up the image level slightly with some other records, particularly those that were originally recorded using multiple-mike techniques and whose

*continued on page 91*

## Troubleshoot and Repair Portable Cassette Recorders

HOMER L. DAVIDSON

PORTABLE CASSETTE PLAYERS AND RECORDERS (the ones that use standard Philips cassettes, not to be confused with mini- or micro-cassette devices) can be repaired as easily as any other tape units. Don't be afraid of their small size—the components may be a little closer together and you may have to work in a tighter space, but that's all. Servicing them can be easy when you follow the tips and information here.

If you have a well-equipped workbench you shouldn't need much in the way of additional equipment. If you don't have one, a take-up torque gauge may be needed for mechanical components. A VTVM (Vacuum Tube Volt-Meter) will do nicely for making head-azimuth adjustments, and for troubleshooting the amplifier section, you can use your signal generator, signal tracer, and scope.

### Cleaning and lubrication

Most sound and speed problems can be solved by a good clean-up and "lube job." A dirty record/playback head may be responsible for weak and distorted sound, and under- (or over-) lubrication can cause tape-speed to vary erratically.

When a recorder develops speed or sound problems, it's time for a cleanup and lubrication. Start at the erase and record/playback heads and clean them with alcohol and a soft-tipped cleaning stick. Critical points for cleaning are shown in Fig. 1. *Do not* use rubbing alcohol—it contains an additive that may leave a gummy deposit. Use pure isopropyl alcohol (available at your drugstore's prescription counter). If some oxide is packed into the gap area of the record/playback head, gently use the round end of the cleaning stick to remove it. You can get at the heads easily by putting the recorder in the RECORD mode; that moves them out into the open.


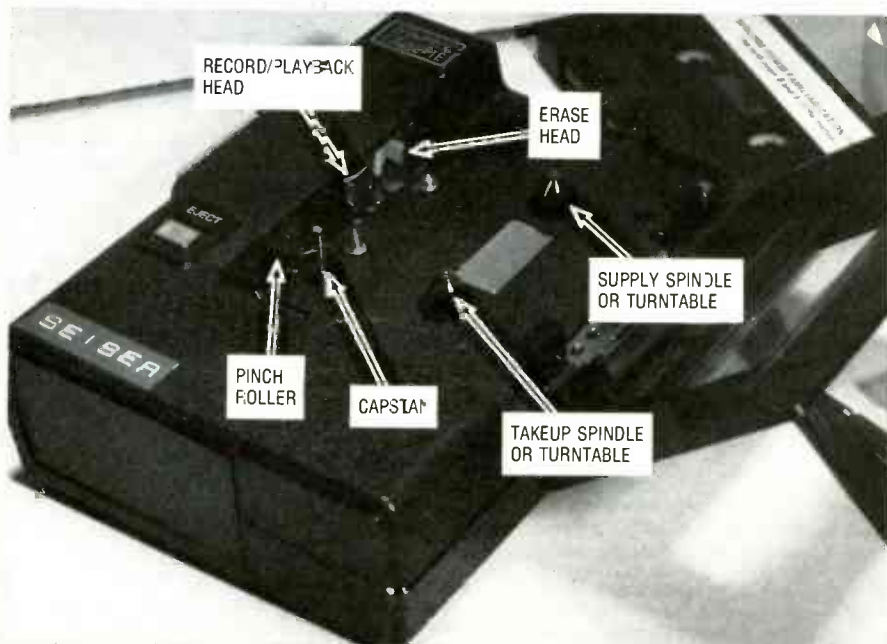


FIG. 1—CRITICAL POINTS FOR CLEANING are indicated above. A good cleaning can be all that's needed to solve many problems.

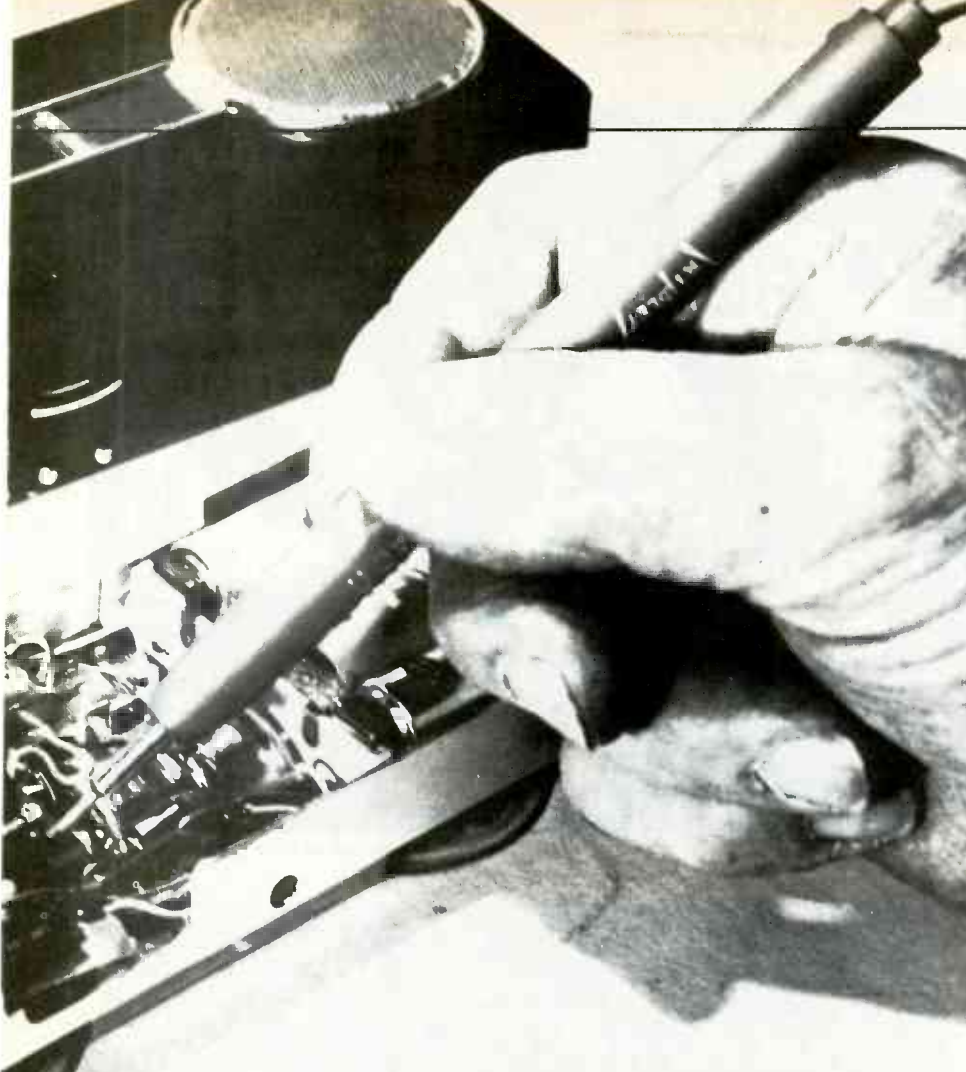

*Don't let their size scare you—small, portable cassette recorders are as easy to troubleshoot as their larger brothers. Here are a number of hints and kinks to help you out.*

You may find more oxide on the pinch roller and capstan than on the tape heads. Remove it with alcohol. Apply a drop of light oil to the pinch-roller bearing and wipe off any excess. Also, always dry off parts that have been cleaned with alcohol since it can damage many rubber and plastic components if it remains on them too long.

If the capstan flywheel appears sluggish, remove it and clean it with alcohol. Also clean around the flywheel-bearing area using a cleaning stick dipped in alcohol. Place a drop of oil upon the capstan bearing and replace the capstan. Wipe off any excess oil with a paper towel or cloth. Clean the capstan-drive area well to remove any remaining oil.

A dry capstan-bearing may be responsible for erratic or slow tape motion, and noisy and squeaky sounds may be caused by dry motor or pulley bearings. Excess oxide on the pinch roller can also be the cause of slow speed or tape pulling. Oil on any drive surface may produce slow—or no—motion in the parts it contacts.

Erratic bunching of tape from the cassette may be caused by a drop of oil on the drive surface of the take-up turntable.

All rubber or plastic drive-pulley surfaces should be cleaned with a cleaning stick, and a drop of light oil placed on the pulley bearings. Any excess oil should be wiped off. All sliding parts should receive a thin coat of light grease. Finally, most motors have sealed bearings and never needed lubricating.

After cleanup and lubrication, it's always a good idea to demagnetize the record/playback head to insure best frequency-response, and then to check the unit out to see how it performs.

Now we'll discuss some commonly encountered problems, and their causes and remedies.

#### **No play or fast-forward**


When the recorder's in the **PLAY** or **RECORD** mode, the capstan and pinch roller pull the tape across the record/playback head, with the takeup turntable causing the tape to be wound on the cas-

sette's takeup hub. In **FAST FORWARD**, the tape moves in the same direction, but the takeup turntable runs at a faster rate of speed; the capstan and pinch roller are disengaged. It's possible for one defective component to affect *all* of those functions.

If the capstan or tape will not move with the **PLAY** switch engaged, check for a defective **ON/OFF** switch. Hold the unit close to your ear and see if you can hear the motor running. If the motor is dead, check the power switch and see whether the voltage is being applied to the motor. If the motor is operating, check for a loose or broken drive belt. If the unit works on AC, but not from its batteries, make sure that batteries are not weak or dead.

Erratic fast-forward action can be caused by a dirty, worn, or binding turntable. Check for oil on the idler wheel or drive pulley (see Fig. 2).

Sometimes the fast-forward lever may bend and not permit the drive pulley to

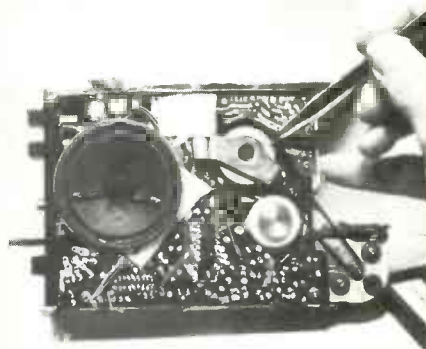

**FIG. 2—FAST-FORWARD** problems may be caused by oil on the idler pulley or capstan/flywheel.

engage the capstan. Check for a weak spring or an out-of-position lever mechanism. A good cleanup of the take-up turntable and a drop of oil on the drive pulley bearing may cure erratic fast-forward motion.

#### **No rewind**

If a recorder/player operates normally in the **PLAY** and **FAST FORWARD** modes, but not in **REWIND**, suspect that the idler or drive pulley is not engaging the supply turntable. In some units the idler pulley gets shifted to the left and rotates the supply spindle in the opposite direction. A dry or worn supply turntable may be the cause of erratic rewind, as well as of slow speeds.

To remedy erratic rewind, remove the supply turntable and clean it with a cloth dampened with alcohol. Don't forget to dry it off afterwards. Place a drop of light oil on the turntable bearing, and then replace the turntable. Clean the rubber or plastic drive area with alcohol and use a

cleaning stick to clean off the idler or drive-pulley surface area. Also check for a worn or binding idler-pulley.

If a loud chattering noise is heard when the cassette is almost rewound, suspect dry hub areas in the cassette itself. A tiny drop of oil in the plastic hub area may help, but be careful; you don't want to ruin the tape.

### Slow speed and wow

Slow-speed problems may be caused by a dry-capstan-bearing or by oil on the drive surface. A dry or worn pinch roller can also be responsible for slow speeds or wow. Replace the pinch roller if you find it's out of round after cleanup. (A defective pinch roller can also cause the tape to ride high or to pull from the cassette.)

Check for a loose drive belt, or oil on it, when wow or slow-speed symptoms are noted. You may find that the motor belt slips right at the drive-motor pulley. Some of the important points to check are shown in Fig. 3.

Also, look for a black area or small particle of rubber on the motor pulley; those signs indicate that the belt is slipping. Since the belts are very small in diameter and stretch easily, it's best to use an exact belt replacement. Finally, don't overlook the possibility of a defective cassette being responsible for wow.

### Check the motor

A defective motor can cause slow speed and wow conditions. Generally, a defective motor will start at normal speed, and then slow down. Sometimes if you tap the motor housing, it will speed up again. In most units you will find a motor-speed potentiometer that can be used to adjust the speed over a certain range. If the speed adjustment has no effect, check the speed-control circuit and motor. (A typical circuit is shown in Fig. 4.)

In some cases you may find that the motor is running too fast. Adjust the speed control, using a piano or music selection as a reference. You can also use a frequency counter to determine the correct speed.

If the motor is still running too fast, see whether the belt is riding too high on the motor pulley. If none of the above adjustments help, install a new motor, using an exact replacement.

### Pulling and bunching tape

Bunching and unraveling of tape in a cassette player may be caused by an erratic or inoperative take-up turntable. The take-up turntable or spindle winds the tape coming from the capstan into the cassette. When the take-up spindle becomes dirty or starts to bind, the excess tape will bunch up and pull out of the cassette. Remove the take-up turntable and clean it with alcohol. Apply a drop of oil to the bearing area. Also, clean the turntable-drive area. Check the idler and

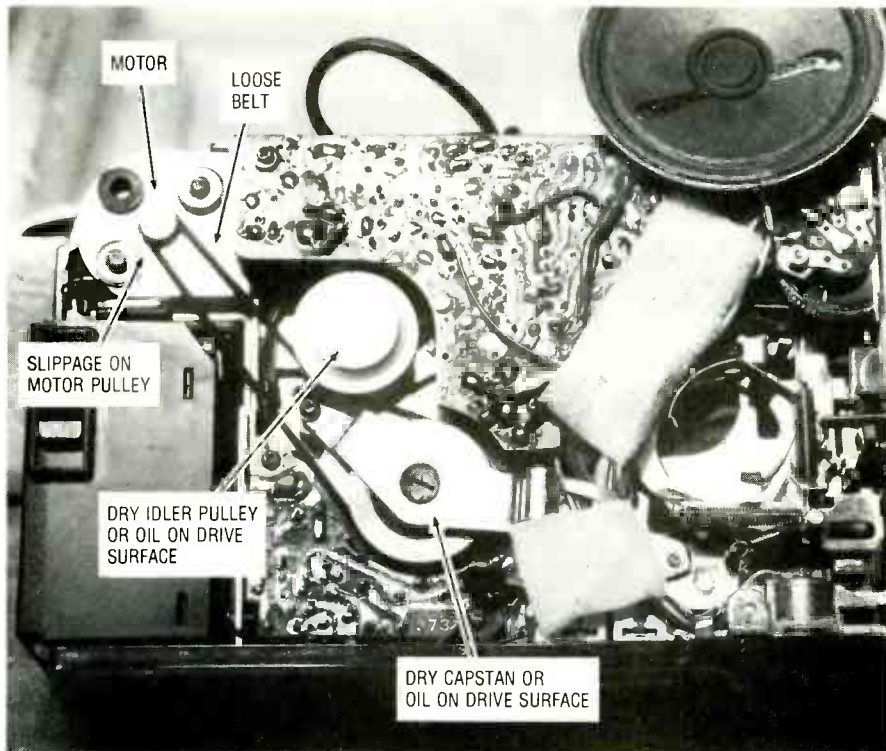


FIG. 3—CHECK THESE AREAS if you are experiencing slow-speed or wow problems.

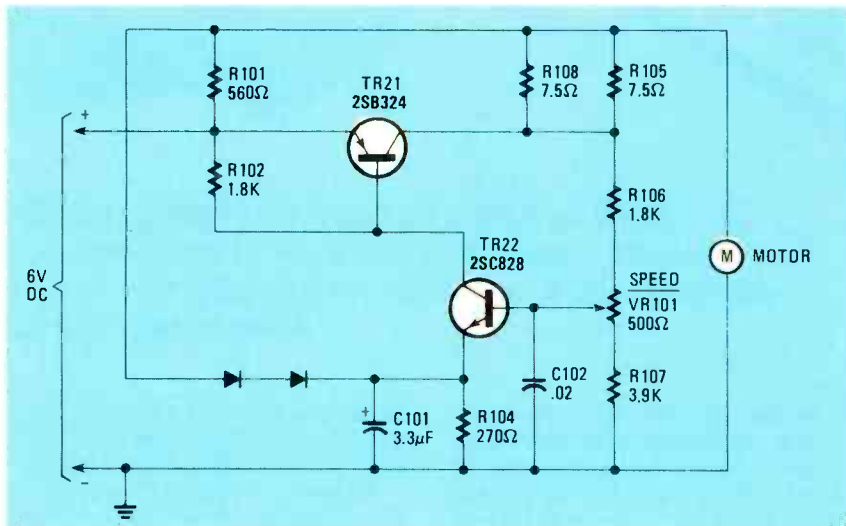


FIG. 4—MOTOR-SPEED CONTROL circuit used by J.C. Penny model 6541. Circuits in other recorders should be similar.

drive pulleys for oil or dirty drive-surfaces.

Sometimes the pressure roller may become worn or out of round, and cause the tape to ride high and pull out of its proper path. In that case, try cleaning the pinch roller and capstan with alcohol. A bent capstan may also cause tape pulling.

If the take-up turntable, pinch roller, and capstan appear to be normal and the player is still pulling tape, check the take-up torque with a torque gauge. Finally, remember that a defective cassette can cause tape to unravel or bunch up.

### No sound

If the tape is moving but there's no

sound, suspect the record/playback head or the amplifier section. Quickly rotate the volume control up and down and listen for a scratchy sound from the speaker. If you can hear some noise, it's an indication that the amplifier is working, so suspect the record/playback head. If you hear a loud hum with the volume wide open, check for a broken wire at the record/playback head. Since the head assembly moves forward every time the PLAY or RECORD buttons are pushed, the wires leading to it have a tendency to break with time.

To determine whether the record/playback head is defective, pass a small screwdriver-blade rapidly across the head



area. You should hear a flutter from the speaker. If you don't, dismantle the top cover by removing both the top and bottom covers. Check the head contact for broken wires. Touch the indicator blade to the ungrounded defective head. With volume control set to 800 Hz and 800

Remove the audio resistor at the first AF stage. Step by step. When the signal is located, measure the out-of-line voltages. (A must when servicing cassette-recorder amplifier circuits.)

In some earlier units you may find five or more small transistors in the amplifier stages, while in present-day ones only one or two transistors may precede a power-IC output circuit. Such a circuit is shown in Fig. 5. To signal-trace the IC circuits, inject an audio signal at the IC's input pin and use the speaker as the indicator. To make sure the IC really is defective, measure the voltages at each pin. With correct voltages, but no signal from the IC, you can safely assume that the IC is defective. If the IC is leaky, even the supply voltage may be affected.

**Weak and distorted sound**

Weak and distorted sound may be caused by a dirty record/playback head. Clean the head with alcohol and a cleaning stick, as described earlier, before tearing into the amplifier. A weak battery or insufficient operating voltage can also affect the quality of the sound.

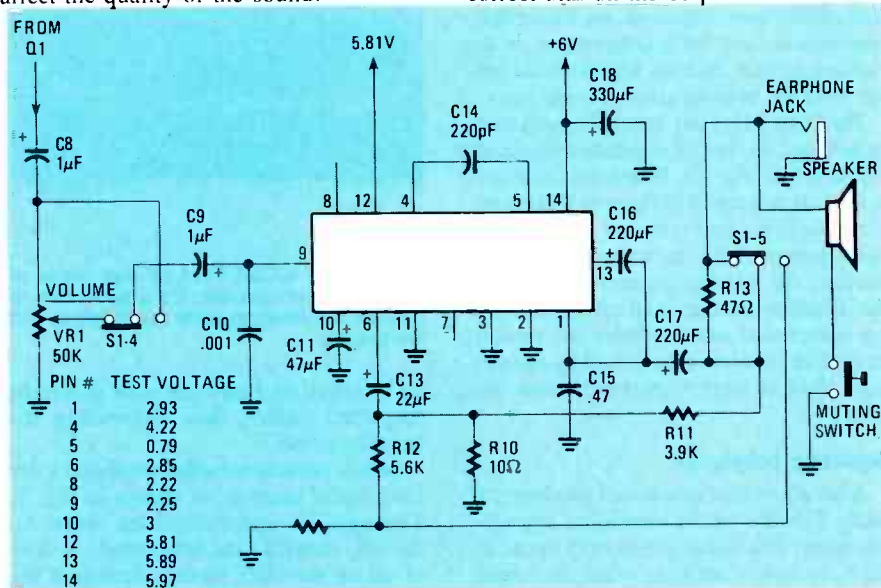


FIG. 5—IC OUTPUT CIRCUIT used in Sanyo model M1000. Voltages shown are typical for this unit but may be different in others.

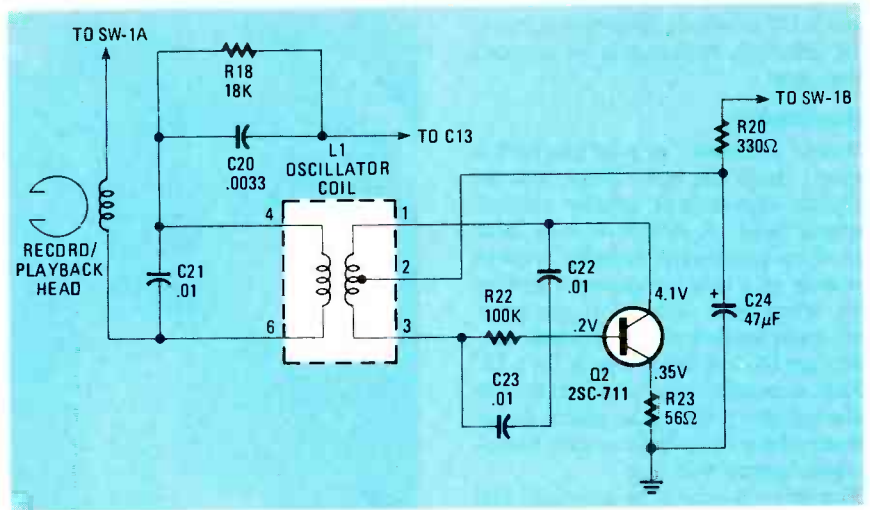


FIG. 6—RECORD OSCILLATOR CIRCUIT used by Sharp model RD-428UA. Use a scope on L1 to determine whether the oscillator is working.

The best method for locating a weak audio-stage is to inject an audio signal, with a scope connected to the output of the recorder/player so that you can observe the audio waveform. Start at the record/play-head connections. The signal should be the same on both sides of the electrolytic coupling-capacitor. (Most weak-sound problems are caused by small coupling-capacitors and transistors in the amplifier section.) If it is not, shunt a new capacitor across the suspected one and see whether the sound returns. Each transistor in the amplifier section should have a large gain from its base to collector terminals.

Excessive distortion may accompany a weak-signal condition. Most distortion in small amplifiers takes place in the output stages. In push-pull transistor output-circuits, an open or leaky transistor can produce weak and distorted sound. Since most circuits of that type are DC-coupled, check the driver or AF transistor for incorrect bias on the output transistors.

Remove both transistors when distortion is located in a push-pull output circuit—it's best to check each transistor for leakage out-of-circuit. Before replacing the output transistors, check the emitter and bias resistors for correct values. Generally, a burnt emitter-resistor will be found along with a shorted or leaky output-transistor.

A leaky IC can also produce weak and distorted audio. Replace the suspected IC when no signal will pass through it or if incorrect voltages are measured at its pins. Use a wick-type solder absorber (like Solder-Wik) to remove the excessive solder from the IC pins to make removing the part easy. Then use a low-wattage pencil iron to install the new IC.

**No record function**

If the unit will play but not record, suspect a dirty PLAY/RECORD switch or defective record circuits. First, make sure the record/playback head is clean. Then spray the PLAY/RECORD switch with contact-cleaner. Work the switch back and forth to clean the contacts and then try to record once again.

Although most portable recorders do not have an oscillator stage to excite the record tape-head, you may run across one that does. A representative circuit is shown in Fig. 6. To determine whether the oscillator is operating, use the scope and check the waveforms at the primary and secondary windings of L1. Transistor testing of Q2 and voltage measurements can indicate whether the transistor is functioning properly.

Check for poor connections to the built-in microphone. Most built-in mikes are electret-capacitor types and require a DC-voltage to work, so test for that voltage at one of the microphone terminals. A defective microphone may be responsible for weak or erratic recordings. Substitute a dynamic microphone across the shielded wires to the built-in mike terminals (but do not connect it to the DC

source). If the built-in microphone proves to be defective, exchange it for an exact replacement.

### Adjustments

When "crosstalk" or poor playback is noticed, check the erase head, and the azimuth adjustment of the record/playback head. A defective erase head may allow previously-recorded material to remain on a tape, producing a garbled mess when new material is recorded. Most erase heads found in portable recorders are DC-operated. Check for a DC voltage across the erase head with the unit in the RECORD mode. Also check the resistance of the erase head in case there's an open internal winding.

The only adjustment on a portable recorder's record/playback head is for azimuth (elevation). The azimuth-adjustment screw is usually located on one side of the head, with a coiled spring underneath it. Connect a VTVM with an eight-ohm dummy load to the earphone jack. Insert a 3-kHz or 6.3-kHz test tape and start it playing. Adjust the azimuth screw for the highest reading on the VTVM. After that has been done, you may want to dab the adjustment screw with paint or glue to secure it in place.

The only other mechanical adjustments are for take-up torque and adjustment of the pressure roller. (You may find that either one or both adjustments are fixed in some models.) The pressure-roller adjustment can be made using a spring scale and changing the position of the pressure-roller spring to vary the tension it puts on the mechanism.

Take-up torque should be measured on the take-up turntable with a torque gauge while in PLAYBACK mode. Most take-up torque readings should be between 35-60 gr-cm. For greater tension, bend the tension spring and, if necessary, replace the take-up pulley. It's best to follow the manufacturer's service literature for correct tension adjustment.

Now let's take a look at some typical case histories.

### Weak and distorted output

A GE *NBR-35311C* had weak and distorted sound. Although the symptoms indicated possible output-transistor problems, the tape head, pinch roller, and capstan were cleaned with alcohol as a matter of routine. The weak condition still remained, as expected.

When the back cover was removed we noticed that new batteries had been installed. Only 2.7-volts was measured at the adjustment transistors. Either the transistors were defective or something in the circuit was loading down the voltage source. A bench supply was connected to the player for servicing and everything worked normally. It turns out that one of the new batteries was practically dead, and the battery terminals were corroded. A good cleanup of the battery terminals



FIG. 7—The UNINSULATED switch lever shorted out the power-supply voltage in this Sharp model RD-428UA.

and a set of fresh batteries solved the weak-audio/distortion condition.

### No play, no record

In a Sharp *RD-428UA*, we found that the motor was turning, but we couldn't play or record. Both REWIND and FAST FORWARD modes were normal. When both covers were removed, we found that the motor did not run in either the PLAY or RECORD modes, and the sound would cut out with the volume control wide open.

The "no play, no record" symptom turned out to be an electromechanical problem (see Fig. 7). When the RECORD/PLAY switch's metal plunger touched one of the switch's leaf contacts, which provided power to the motor and amplifier circuits, the voltage source was shorted out. It seems that the small rubber insulating sleeve was missing from the switch lever. The problem was solved by epoxying a piece of large "spaghetti" over the lever.

### Squeaky playback

After about five minutes of playback, a Sharp *RD-428* would develop a squeaking noise. The noise would only occur in the PLAY mode, and only when the wheel or pulley came around to a certain position. Sometimes by probing around with

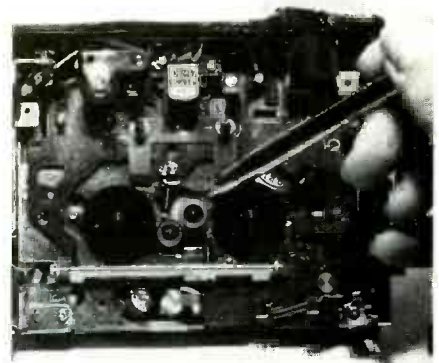


FIG. 8—DRY IDLER PULLEY was cause of squeak in this recorder. It's a good idea to remove the problem parts for cleaning and lubrication.

an insulated tool you can slow down the suspected pulley, thus eliminating the squeaky noise.

In this particular model we found a dry idler-wheel bearing, as shown in Fig. 8. The spindle and turntables were removed, cleaned, and lubricated. A drop of oil on the idler wheel eliminated the squeaking noise.

*continued on page 107*

## ALL ABOUT PULSE GENERATORS



*This month we'll look at another pulse-generator application, testing analog circuits, as well as some problems that you might run into when you use that device.*

CHARLES GILMORE

**Part 4** SO FAR WE HAVE CONFINED our discussion to using the pulse generator in logic-circuit analysis. While that is one of the prime functions of the pulse generator, it is not its only one. Let's begin this month by looking at another area where the pulse generator is useful—testing and analyzing analog circuitry.

### Analog circuits

Using a pulse generator as a signal source can simplify many of the measurements that are often made when testing analog circuits. That's because, generally speaking, pulse generators are useful over a very wide frequency range, which can come in handy when working with broadband amplifiers, etc.

For instance, a single, conventional, pulse generator is the only signal source you need to test an amplifier whose frequency response extends from below 1 Hz to considerably more than 10 MHz. Otherwise, testing that amplifier would require using an audio generator for the low end and an RF generator for the upper end, or perhaps a very wide-range function generator.

The reason for that becomes apparent if the nature of a pulse is analyzed. Such analysis would reveal that the pulse's fast rise and fall times are caused by the pulse's high-frequency components, while the interval between the rise and fall times (i.e. the top of the pulse) is caused by the low-frequency components; in some cases, the frequency of those components is so low that it is approaching DC. Those high- and low-frequency components are what gives the pulse generator its wide frequency range.

Frequency-response measurements on an amplifier are usually made at the 3-dB points; that is, the point at which amplifier delivers half its rated power output, or

70 percent of its rated voltage output. That 3-dB point is considered the upper and lower cutoff frequency of an amplifier. The simplest method to measure the low-frequency 3-dB cutoff is by adjusting the pulse generator so that the pulse *droop* is 25 percent. Pulse droop (the difference between the amplitude immediately following the leading edge and the amplitude at which the trailing edge begins) is expressed as a percentage of the amplitude at the leading edge (see Fig. 11).

When the pulse droop is adjusted to 25 percent, the width of the pulse is related to the frequency (in Hz) of the lower 3-dB point through the formula:

$$f_{\text{low}} \approx \frac{0.0456}{t}$$

where  $t$  is the width of the pulse. The constant (0.0456) is derived from a Fourier analysis of the pulse.

To measure the frequency of the upper 3-dB cutoff, the following formula is used:

$$f_{\text{upper}} = \frac{0.35}{t_r}$$

where  $f_{\text{upper}}$  is the upper 3-dB cutoff frequency (MHz), and  $t_r$  is the pulse risetime in nanoseconds.

While that formula has been idealized and is for a circuit where the product of the capacitance and inductance is 0, the formula will hold until that product exceeds 0.25. After that point, some overshoot begins to occur at the end of the leading edge, lowering the value of the constant, 0.35, in the formula. With overshoot of 25 percent, for instance, that constant would be lowered to 0.28.

Some additional information about the frequency response of a broadband amplifier can be obtained using a pulse generator. Remember that a pulse con-

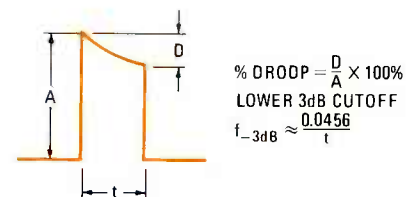


FIG. 11—PULSE DROOP is useful in finding the lower 3-dB point of an amplifier.

sists of a fundamental frequency plus a great number of even and odd harmonic components with specific phase relationships with each other, as well as with the fundamental frequency. If that phase relationship is not maintained, the waveshape of the pulse deteriorates. If an essentially stable pulse waveform is passed through an amplifier, the amplifier's output can be examined for any aberrations in that waveform. The presence of those aberrations indicates that the phase response of the amplifier is not uniform—i.e., that there are peaks and/or valleys in the amplifier's frequency-response curve. That would be caused by either leading or lagging reactive elements in the circuit. At that point, further analysis with a sweep generator or a low-distortion audio oscilloscope is needed.

As noted earlier, rise-time measurements let you determine approximately the upper frequency-response limits of a broadband amplifier. A few precautions must be taken when making such rise-time measurements. One thing that must be considered is the effect of the test setup. Each part of that setup plays a role in determining the rise time of the output that is displayed; in other words, the rise time of the pulse is changed slightly as it passes through the various parts of the test setup. The displayed rise time, therefore, is actually a function of the rise times

through each part of that setup and can be found from:

$$T_R = 1.1 \sqrt{T_G^2 + T_A^2 + T_P^2 + T_O^2}$$

where  $T_R$  is the display rise time,  $T_G$  is the rise time of the pulse generator,  $T_A$  is the rise time of the amplifier under test,  $T_P$  is the rise time of the probe, and  $T_O$  is the rise time of the oscilloscope.

Because of its exceedingly fast rise time, a pulse generator is extremely convenient for measuring propagation delay and phase delay. Both analog and digital circuits introduce some fixed time delay to signals that pass through them. For example, if a J-K flip-flop is clocked, it will take several nanoseconds for the results of that clocking to appear at the output of the flip-flop. That delay in response is called the propagation delay of the flip-flop.

Analog amplifiers also suffer from propagation delay. The easiest way to measure that delay is to use a dual-trace oscilloscope and a pulse generator. The pulse-generator output is applied to the amplifier's input and to one oscilloscope channel. The amplifier output is the applied to the second channel of the oscilloscope, and a comparison is made.

If a dual-trace oscilloscope is not available, you can use a pulse generator with a pulse-delay capability. In that case, the input to the amplifier is connected to the delayed generator output. The amplifier output and the non-delayed pulse-generator output are both applied to the oscilloscope. The pulse-delay control of the generator is then adjusted until a single pulse is obtained. The amount of delay necessary to display the single pulse is equal to the propagation delay of the amplifier.

In order to successfully combine the amplifier output with the pulse-generator output, some series-limiting resistance must be used. Great care must be taken to insure that the added circuitry does not contribute additional phase shift. Figure 12 shows an example of such a situation.

Pulse generators are also useful in evaluating the high-frequency characteristics of diodes and transistors. The diodes used in either radio-frequency or digital applications are required to recover very rapidly from switches between reverse- and forward-bias.

When a diode is forward-biased, the area at the junction is filled with majority carriers. ("Majority carrier" is a term used in semiconductor electronics to describe the predominant type of carrier in a semiconductor material. In n-type material, the predominant carrier is the electron; in p-type material it is the absence of an electron, which is called a *hole*.) When the diode is reverse-biased, the junction has few majority carriers. Obviously, the change in the number of majority carriers at the junction can not occur instantaneously.

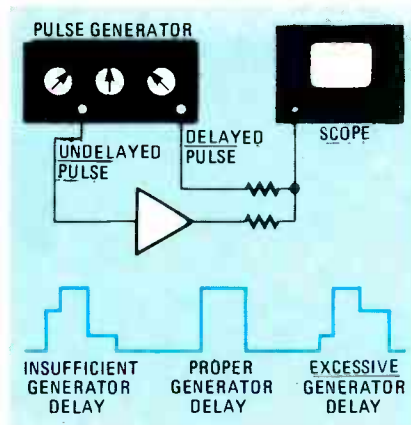


FIG. 12—A PULSE GENERATOR is used here to measure the propagation delay through an amplifier.

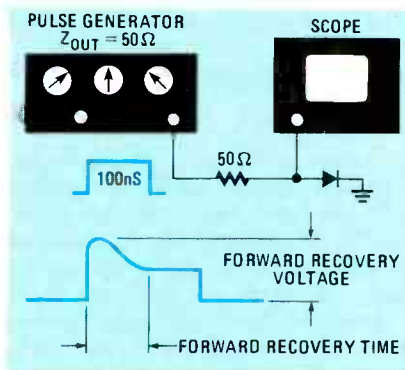


FIG. 13—MEASURING THE FORWARD recovery voltage and forward recovery time of a switching diode. The pulse generator should be set for a 100-nanosecond pulse width with a less than 1 percent duty cycle. The output voltage of the generator should be set to produce a specified steady-state current in the diode.

Let's first look at what happens when a diode is suddenly switched from reverse- to forward-bias. When that happens, the majority carriers move to the area around the junction. But, until that area is filled with those majority carriers, the voltage across the diode is considerably greater than its normal forward-biased voltage. That voltage *transient* is of concern if the diode is to be used in switching applications. Figure 13 shows a test setup that can be used to measure that *transient*, as well as the waveform that would be displayed on the scope. The size and duration of the transient can be found by inspecting the waveform as shown.

The forward-recovery specifications of a diode are normally given for some steady forward-current value, once the transient conditions have subsided. It is that forward current, combined with a 50-ohm resistor, that determines the pulse generator's output voltage; pulse duration should be 100 nanoseconds. A generator having a 10- to 20-nanosecond rise time is suitable for that test, and no offset voltage is required.

Now, let's consider what happens when a diode is suddenly reverse-biased.

When that happens, a large reverse current flows until there are few majority carriers left around the junction. How long that current flows is important if a diode is to be used in a switching application. Figure 14 shows the test setup used to measure that, as well as the waveform that is likely to be seen on the scope.

The requirements placed on the pulse generator and the oscilloscope used to measure reverse-recovery time are somewhat greater than those for forward-recovery time. Reverse-recovery time in diodes is on the order of a few nanoseconds, and the rise time of the pulse generator must be considerably less. In many cases, the rise time of both the pulse generator and the scope must be less than 1 nanosecond. However, generators with more moderate specifications can be used to test slower diodes.

Figure 15 shows the test setup used to measure the turn-on and turn-off times of a switching transistor, as well as the typical waveforms that would be displayed on the scope. That test is one of the most important ones done when you are analyzing the operation of a switching transistor.

As with a diode, transistor specifications are given at some specified base- and collector-current levels. The bias and  $B+$  voltages supplied to the circuit establish proper transistor operation and should be selected so that those currents are at the proper level. Note that turn-on time is determined by noting the point where the generator's output rises to 10 percent of its final value and the point where the transistor's output drops to 90 percent of its initial value. Conversely, turn-off time is measured between the points where the generator's output drops 10 percent from its maximum level, and the transistor's output rises to 90 percent of its initial value. Once again, for transistors with reasonable switching speeds, the pulse generator and the oscilloscope must have relatively good rise-time specifications. However, pulse generators with more moderate capabilities can be used to perform those tests on some slower transistors. Other transistor measurements that can be made include storage time, stage rise time, and voltage breakdowns.

Using a pulse generator when testing transistors and diodes has several advantages. Two of the most obvious are that they can be used to supply a bias offset voltage, (eliminating additional power supplies) and that their sharp rise times eliminate the need to measure the rise time of the generator itself. In addition, pulse generators can be operated at extremely low duty cycles. For instance, in the diode and transistor tests we just discussed, duty cycles of one percent or less are called for. Such low duty cycles let you perform tests that could not be safely done under steady-state conditions. Such steady-state testing would overheat many

of the devices, possibly destroying them, or at least changing their electronic characteristics. Even though peak power developed in a circuit when using a pulse generator may far exceed the maximum permissible continuous power, with that device's low duty-cycle the average power is well within its ratings.

### Sources of error

A pulse generator is probably one of the easiest instruments to use improperly. The vast number of settings and modes make it easy to set up improperly. Therefore, using a pulse generator without an oscilloscope is not advisable. With a scope, you can easily spot setup errors and correct them.

The most frequent errors in using a pulse generator are human errors. For example, a common mistake is exceeding the allowable duty cycle. As noted earlier, a 70 percent duty cycle is common for most pulse generators. The most usual mistake here, however, does not involve exceeding the duty cycle by a small amount (such as 75 percent as opposed to 70 percent, for example), but by exceeding it by orders of magnitude. That happens when, for instance, a pulse-repetition rate of 1 kHz has been established, but a pulse width of 10 milliseconds is chosen instead of 10 microseconds. In that situation, the duty cycle has been exceeded by a factor of 10.

On pulse generators with a pulse-delay feature, a similar error occurs. In that case, the delay time exceeds the time established by the pulse-repetition rate. A pulse generator set for a repetition rate of 1 pulse-per-millisecond might have the delay generator set at 10 milliseconds. Due to the nature of the monostable multivibrator used to generate the delay time, the first pulse is chosen to generate the 10-millisecond delay interval, and the following nine pulses are ignored. The result is one pulse-per-10 milliseconds, even though the pulse-repetition rate has been set for 1 pulse-per-millisecond.


Variable rise- and fall-times, although a useful feature, can also give rise to errors. For instance, assume a pulse width of 20 nanoseconds is desired. If, however, the rise- and fall-times are set at 15 nanoseconds, the time required to reach the maximum output and drop back to zero would be a total of 30 nanoseconds, 10 nanoseconds greater than the pulse width. Thus, the pulse does not have enough time to reach the proper levels, making any measures of amplitude incorrect.

As noted previously, improper transmission lines or terminations can seriously degrade pulse characteristics. Care must be taken to prevent pulses that are distorted beyond recognition.


In similar fashion, certain situations require the pulse to be split between two different transmission lines and later re-

combined by some form of circuitry. If narrow pulses at a high rate, and relatively long cables are used, great care must be taken to insure that both pulses arrive at the proper termination simultaneously. If that is not done, pulse-stretching may occur.

In many cases, both the amplitude and the offset controls of the pulse generator have extremely coarse calibration; that can cause misadjustment. Errors can easily occur when setting the generator's output amplitude. A 50 percent setting, for instance, does not mean 50 percent of the rated amplitude. The output specification of the generator indicates a maximum output, but that output is usually given in terms of "not less than." In many cases, the actual output can exceed that rated output by as much as 20 to 25 percent. As

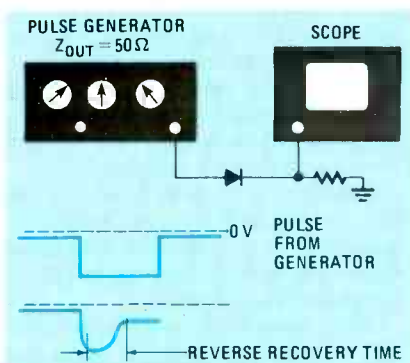

**FIG. 14—MEASURING DIODE reverse-recovery time.** A 100-nanosecond pulse-width with a duty cycle of less than 1 percent should be used. The generator rise time should be less than the expected reverse-recovery time. The positive pulse offset is set to generate the specified forward current. A 60-ohm resistor converts the output current to voltage for display on the oscilloscope.

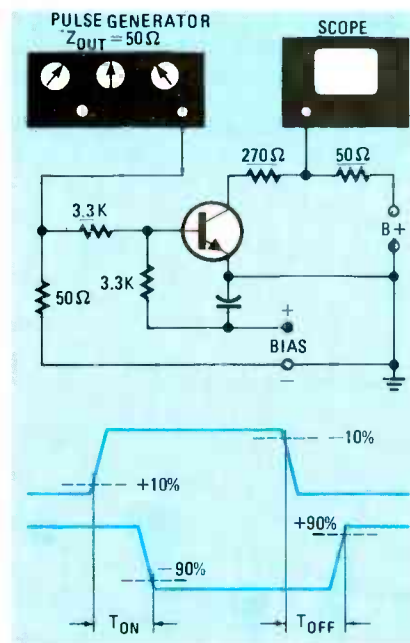

**FIG. 15—MEASURING THE SWITCHING time of a transistor.** The pulse generator is set for a 100-nanosecond pulse-width with a duty cycle of less than one percent.

a result, the most accurate way to set the output amplitude is to monitor the generator's output on a scope. Another possible error in setting the output amplitude can be introduced by using an output attenuator. Those errors are caused by using the wrong level of attenuation and are quite large—at least one order of magnitude.

### Generator-induced errors

A pulse generator is usually not calibrated very precisely. However, if you are fully aware of all its specifications and what they mean, you will have little or no problem in getting maximum use from the instrument. However, failure to recognize some of these specifications can result in generator-induced measurement errors. Jitter can occur in the repetition rate, the amount of pulse delay, and the pulse width. The amount of jitter must be taken into consideration when a rather stable pulse-width, delay, or repetition-rate is required.


When using a pulse generator, especially over extended periods of time, it is necessary to reset the operating parameters, many of which can vary over time, or with changes in temperature and other factors. Certain pulse-generator characteristics are affected by changes in the load (for example, the baseline offset, which is often simply a current generator operating into a known load).

Frequently, certain pulse-generator controls interact somewhat. For example, any changes in the rise time and fall time of the output pulse can cause changes in the pulse width and amplitude.

When you use the dual-pulse or twin-pulse mode, make sure that the delay time is long enough to permit the first pulse to return to zero before the second pulse is generated. It is possible to set two pulses with such a short delay time between them that they never return to the baseline.

Finally, it is important to remember that the best way to get the most out of a pulse generator is to use it with a good oscilloscope.

R-E

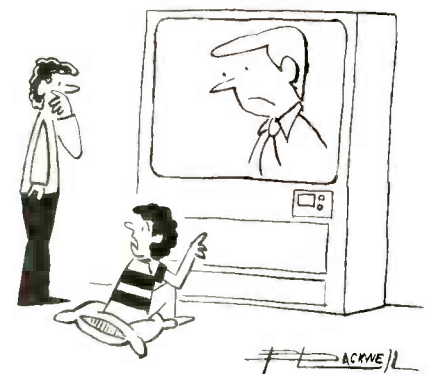

"I'd like to turn it off, father, but he's telling me to stay tuned, and he's bigger than you!"

# HOBBY CORNER

## Learning about microprocessors

EARL "DOC" SAVAGE K4SDS, HOBBY EDITOR

WHAT DO YOU KNOW ABOUT MICRO-processors? If nothing else, I hope you know at least that a microprocessor is the "heart" or "brains" of a microcomputer. Actually, maybe "brains" is the wrong word to use, because a microcomputer is just as dumb as an electric motor, in spite of appearances to the contrary—but that's another story.

You should certainly be aware that a microprocessor is not a microcomputer, and vice versa. You will find that, through carelessness or ignorance, those terms are used interchangeably on occasion. Do not be confused. A microprocessor is one small integrated circuit. A microcomputer is made up of a group of IC's that includes a microprocessor as the "controller of operations." The microprocessor, then, can be thought of as the foreman of a crew that, together constitutes a microcomputer. (We will ignore for now the so-called "single-chip computer.")

Why should you be concerned about microprocessors since you have no interest in microcomputers? There are two good reasons. The first is that more and more, microcomputers are effecting every aspect of our lives; whether you like it or not, in all likelihood, you will, eventually have to learn at least a little about them.

The second reason is perhaps more important. In the past, microprocessors

were found only in computers. Today, you can find them in microwave ovens, television and radio receivers, cars, games, and other devices. Before long, you will find them in everything except the simplest devices.

If you don't learn what microprocessors are, how they function, and what they can and can't do, you are going to be left out of the most interesting developments in electronics. You won't even be able to fix many of the electrical things around the house. Your hobby activities will become outdated.

Consider the plight of those who know how to work with tubes but are lost with transistors. (I, too, was once in that boat.) Others know transistors but never have gotten the hang of IC's.

When those hobbyists write, invariably they want to know how and where to get started in catching up. I hope you won't let progress pass *you* by too. Microprocessors are here and they are already becoming common in many applications.

Make no mistake—in spite of anything you may have heard of the contrary, a microprocessor is not just another "run-of-the-mill" IC. They are complex little devils that can be made to do some remarkable things. Yet, they are not all that difficult to work with and understand if you tackle them in an organized, logical manner.

One of the most thorough in-depth

treatments of microprocessors that I have found is published by the McGraw-Hill Book Company, Gregg Division, (1221 Avenue of the Americas, New York, NY 10020). *Introduction To Microprocessors*, by Charles M. Gilmore, is a textbook that can be used in a classroom or for independent study. The treatment of the material is quite thorough and, in one way at least, unique.

That text is not about the Z80, 6809, 8085, 1802, or any of the other available microprocessors. It is, in fact, about an imaginary microprocessor. Because of that, you learn about microprocessors in general and not just a specific one. It is a relatively easy matter to apply what you've learned to any microprocessor you work with later. Do not misunderstand—this book is not simply an introduction to microprocessors; the author gets right down to the nitty-gritty of the subject.

Don't get caught having to play catch-up later—do yourself a favor and find out about microprocessors now.

### Flashing-light "doorbell"

Tom Haase of Oklahoma City sent the schematic shown in Fig. 1. That is his simple answer to a request we ran asking for a way to let deaf persons know the doorbell is ringing.

As indicated, the reed switch is placed very close to the coil in the doorbell or buzzer. The magnetic field of the coil causes the switch to close, activating the 555 one-shot. That, in turn, starts the 3909 LED flasher, which pulses the relay and flashes the light.

Tom has installed three of those devices for friends who are deaf. Tom also suggests that a strobe light could be used by omitting the 3909 flasher.

Thanks, Tom, for a neat solution to a serious problem.

### A shocking project

I got a nice letter from a fellow in Australia the other day. He asked for some help on a project. At least that was his intention, but he was really asking me to help get him in trouble.

My Australian friend wanted to hot-wire his car with a "shocker" to keep vandals away from it. Well, it is possible to shock a person without killing him but who is to say who might touch the car?

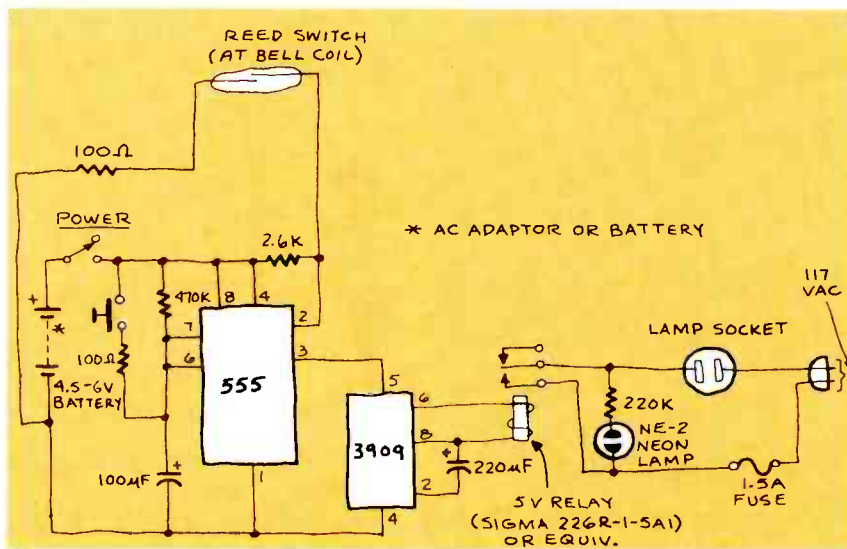


FIG. 1

# FOR ONLY \$129.95 Learn Computing From The Ground Up

Build a Computer kit that grows with you, and can expand to 64K RAM, Microsoft BASIC, Text Editor/Assembler, Word Processor, Floppy Disks and more.

## EXPLORER/85

Here's the low cost way to learn the fundamentals of computing, the all important basics you'll need more as you advance in computer skills. For just \$129.95 you get the advanced design Explorer/85 motherboard, with all the features you need to learn how to write and use programs. And it can grow into a system that is a match for any personal computer on the market. Look at these features: 8085 Central Processing Unit, the microprocessor "heart" of the Explorer/85 (Join the millions who will buy and use the 8080/8085 this year alone); Four half plus one bit input/output ports from which you can input and output your programs, as well as control exterior switches, relays, lights, etc. a cassette interface that lets you store and reload programs you've learned to write; a deluxe 2,000 byte operating system/monitor makes it easy to learn computing in several important ways. • It allows simpler, faster writing and entering of programs. • It permits access by you to all parts of the system so you can check on the status of any point in the program. • It allows tracing each program step by step with comparison for displaying all the contents of the CPU (registers, flags, etc.) • and it does much more!

You get all this in the starting level (Level A) of the Explorer/85 for only \$129.95. To use, just plug in your 6VDC power supply and terminal or keyboard/display — if you don't have them, see our special offers below.

Level A computer kit (Terminal Version) . . . \$129.95 plus \$3 P&I\*  
Level A kit (Hex Keypad/Display Version) . . . \$129.95 plus \$3 P&I\*

LEVEL B — This "building block" converts the motherboard into a two-slot S100 bus (industry standard) computer. Now you can plug in any of the hundreds of S100 cards available.

Level B kit . . . \$49.95 plus \$2 P&I\*  
S100 bus connectors (two required) . . . \$4.85 each, postpaid.

LEVEL C — Add still more computing power, this "building block" mounts directly on the motherboard and expands the S100 bus to six slots.

Level C kit . . . \$39.95 plus \$2 P&I\*  
S100 bus connectors (five required) . . . \$4.85 each, postpaid.

LEVEL D — When you reach the point in learning that requires more memory, we offer two choices either add 4K of a memory device on the motherboard, or add 16K, 32K or 64K of memory by means of a single S100 card, our famous "JAWS".

Level D kit (CHECK ONE):  
4K on-board . . . \$49.95 plus \$2 P&I\*  
16K S100 "JAWS" . . . \$149.95 plus \$2 P&I\*  
32K S100 "JAWS" . . . \$199.95 plus \$2 P&I\*  
64K S100 "JAWS" . . . \$249.95 plus \$2 P&I\*  
8K S100 "JAWS" . . . \$299.95 plus \$2 P&I\*

LEVEL E — An important "building block" it activates the 8K ROM/EPROM space on the motherboard. Now just plug in our 8K Microsoft BASIC or your own custom programs.

Level E kit . . . \$5.95 plus \$2 P&I\*  
Microsoft BASIC — It's the language that allows you to talk English to your computer! It is available three ways:  
8K cassette version on the motherboard, or add 16K, 32K, 64K and 128K of RAM minimum, we suggest a 16K S100 "JAWS" — see above) . . . \$64.95 postpaid.  
8K ROM version of Microsoft BASIC, requires Level B & Level E and 4K RAM, just plug into your Level E sockets. We suggest either the 4K Level D RAM expansion or a 16K S100 "JAWS" . . . \$99.95 plus \$2 P&I\*  
Disk version of Microsoft BASIC, requires Level B & 32K of RAM, floppy disk controller, 8" floppy disk drive) . . . \$225 postpaid.

TEXT EDITOR/ASSEMBLER — The editor/assembler is a software tool (a program) designed to simplify the task of writing programs. As your programs become longer and more complex, the assembler can save you many hours of programming time. This software includes an editor program that enters the programs you write, makes changes, and saves the programs on cassettes. The assembler performs the clerical task of translating symbolic code into the computer-readable object code. The editor/assembler program is available either in cassette or a ROM version.

Editor/Assembler (Cassette version, requires Level 'B' and 8K (min) of RAM — we suggest 16K "JAWS" — see above) . . . \$59.95 plus \$2 P&I\*  
Editor/Assembler (ROM version — supplied on an S100 card, requires Level B and 4K RAM, 8" floppy disk drive, either Level D or 16K "JAWS" . . . \$99.95 plus \$2 P&I\*  
8" FLOPPY DISK — A remarkable "building block." Add our 8" floppy disk when you need faster operation, more convenient program storage, perhaps a business application, and access to the literally thousands of programs and program languages available today. You simply plug them into your Explorer/85 disk system — it accepts all IBM-formatted CP/M programs.

8" Floppy Disk Drive . . . \$499.95 plus \$12 P&I\*  
Floppy Controller Card . . . \$199.95 plus \$2 P&I\*  
Disk Drive Cabinet & Power Supply . . . \$69.95 plus \$3 P&I\*  
Drive Cables (set up for two drives) . . . \$25.00 plus \$1 P&I\*  
CP/M 2.2 Disk Operating System, includes Text Editor/Assembler, dynamic debugger, and other features that give your Explorer/85 access to thousands of existing CP/M-based programs . . . \$150.00 postpaid.

NEED A POWER SUPPLY? Consider our AP-1. It can supply all the power you need for a fully expanded Explorer/85 (note disk drives are on their own power supply). Plus the AP-1 fits neatly into the attractive Explorer steel cabinet (see below).  
AP-1 Power Supply kit (8V @ 5 amps) in deluxe steel cabinet . . . \$39.95 plus \$2 P&I\*

NEED A TERMINAL? We offer you choices, the least expensive one is our Hex Keypad/Display kit that displays the information on a calculator-type screen. The other choice is our ASCII Keyboard/Computer Terminal kit, that can be used with either



1. Plug in Netronics's Hex Keypad/Display
2. Add Level B to convert to 8K RAM
3. Add 4K RAM
4. Plug in Level E here, or edit Microsoft BASIC or Editor/Assembler in ROM
5. Add five S100 boards
6. Add your own custom circuits (prototype circuit)
7. Connect terminal

a CRT monitor or a TV set (if you have an RF modulator)  
Hex Keypad/Display kit . . . \$69.95 plus \$2 P&I\*

**FASTERM-64 TERMINAL KIT** — Featuring a 56 key ASCII Keyboard, 128 character set upper and lower case, 75 ohm output, 8 baud rates: 150 to 19,200 (switch selectable), RS232C or 20 baud output, 32 or 64 character by 16 line formats, complete with Deluxe Steel Cabinet and Power Supply . . . \$199.95 plus \$3 P&I\*



RF Modulator kit (allows you to use your TV set as a monitor) . . . \$8.95 postpaid  
12" Video Monitor (10MHz bandwidth) . . . \$139.95 plus \$5 P&I\*

Deluxe Steel Cabinet for the Explorer/85 . . . \$49.95 plus \$3 P&I\*  
Fan for cabinet . . . \$15.00 plus \$1.50 P&I\*

## ORDER A SPECIAL-PRIce EXPLORER/85 PAK — THERE'S ONE FOR EVERY NEED.

**Beginner Pak** (Save \$26.00) — You get Level A (Terminal Version) with Monitor Source Listing (\$25 value), AP-1, 5-amp power supply, Intel 8085 User's Manual (Free \$19.95) SPECIAL \$169.95 plus \$4 P&I\*  
**Experimenter Pak** (Save \$53.40) — You get Level A (Hex Keypad/Display Version) with Hex Keypad/Display, Intel 8085 User's Manual, Level A Hex Monitor Source Listing, and AP-1, 5-amp power supply (Reg. \$279.95) SPECIAL \$219.95 plus \$6 P&I\*  
**Special Microsoft BASIC Pak** (Save \$103.00) — You get Levels A (Terminal Version), B, D (4K RAM), E, 8K Microsoft BASIC in ROM, Intel 8085 User's Manual, Level A Hex Monitor Source Listing, and AP-1, 5-amp power supply (Reg. \$439.70) SPECIAL \$329.95 plus \$7 P&I\*  
Add a Rom-Version Text Editor/Assembler (Requires levels B and D or S100 Memory) . . . \$99.95 plus \$2 P&I\*

**Starter 8" Disk System** — Includes Level A, B floppy disk controller, one CFC 8" disk-drive, two-draw cable, two S100 connectors, just add your own power supplies, cabinets and hardware. (Reg. \$1085.00) SPECIAL \$999.95 plus \$13 P&I\*  
Add to any of above Explorer steel cabinet, AP-1 five amp power supply, Level C with two S100 connectors, disk drive cabinet and power supply, two sub-D connectors for connecting your printer and terminal (Reg. \$225.95) SPECIAL \$199.95 plus \$13 P&I\*  
Complete 64K System — Wired & tested \$1650.00 plus \$6 P&I\*  
Special Complete Business Software Pak (Save \$825.00) — Includes CP/M 2.2 Microsoft BASIC, General Ledger, Accounts Receivable, Accounts Payable, Payroll Package. (Reg. \$1325) SPECIAL \$699.95 postpaid.

\*P&I stands for "postage & insurance." For Canadian orders, double this amount.

Continental Credit Card Buyers Outside Connecticut:

**TO ORDER**

**Call Toll Free:**

**800-243-7428**

To Order From Connecticut, or For Technical Assistance, Call (203) 354-9375

CP/M is a reg. trademark of Digital Research.

★ (Clip and mail entries cut) ★

SEND ME THE ITEMS CHECKED ABOVE

Total Enclosed (Conn. Residents add sales tax) \$\_\_\_\_\_ Paid by

Personal Check  Cashier's Check/Money Order

VISA  MASTER CARD (Bank No. \_\_\_\_\_)

Acct. No. \_\_\_\_\_ Exp. Date \_\_\_\_\_

Signature \_\_\_\_\_

Print Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

COMPLETE FASTERM-64 TERMINAL (includes FASTVID-64 video board ASCII-3 keyboard, steel cabinet and power supply) . . . kit \$199.95 plus \$3 P&I\* . . . wired & tested \$249.95 plus \$3 P&I\* . . . graphics option: add \$19.95 to each of above

COMPLETE SMARTERM-80 TERMINAL (includes SMARTVID-80 video board, ASCII-3 keyboard, steel cabinet and power supply) . . . kit \$299.95 plus \$3 P&I\* . . . wired and tested \$369.95 plus \$3 P&I\*

FASTVID-64 VIDEO BOARD (requires +5 & -12V DC) . . . kit \$99.95 plus \$3 P&I\* . . . graphics option add \$19.95 . . . wired & tested \$129.95 plus \$3 P&I\* . . . graphics option add \$19.95

SMARTVID-80 VIDEO BOARD (requires +5 & +/-12V DC) . . . kit \$199.95 plus \$3 P&I\* . . . wired & tested \$249.95 plus \$3 P&I\*

DELUXE STEEL TERMINAL CABINET . . . \$19.95 plus \$3 P&I\*

ASCII-3 KEYBOARD (requires +5 & -12VDC) . . . kit \$69.95 plus \$3 P&I\* . . . wired and tested \$89.95 plus \$3 P&I\*

POWER SUPPLY (powers ASCII-3 keyboard & video boards) . . . kit only \$19.95 plus \$2 P&I\*

ZENITH VIDEO MONITOR (high resolution green phosphor) . . . wired & tested \$149.95 plus \$6 P&I\*

TELEPHONE MODEM MODEL 103 O/A . . . wired & tested \$189.95 plus \$3 P&I\*

DOT MATRIX PRINTER Comet I . . . wired & tested \$299.95 plus \$10 P&I\*

RF-MODULATOR MOD RF-1 . . . kit only \$8.95 plus \$1 P&I\*

3FT-25 LEAD MODEM/TERMINAL OR PRINTER/TERMINAL CONNECTOR CABLE . . . \$14.95 ea plus \$2 P&I\*

For Canadian orders, double the postage. Conn. res. add sales tax.

Total Enclosed \$\_\_\_\_\_

Personal Check  Cashier's Check/Money Order

VISA  MasterCard (Bank No. \_\_\_\_\_)

Acct. No. \_\_\_\_\_ Exp. Date \_\_\_\_\_

Signature \_\_\_\_\_

Print Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

# ANNOUNCING TWO NEW TERMINALS

Smart • Fast • Graphics • Matching Modem and \$295 Printer

Netronics announces a state of the art breakthrough in terminals, now at prices you can afford, you can go on-line with data-bank and computer phone-line services. It's all yours — electronic newspapers, educational services, Dow-Jones stock reports, games, recipes, personal computing with any level language, program exchanges, electronic bulletin boards . . . and more every day!!!



Netronics offers two new terminals, both feature a full 56 key/128 character typewriter-style keyboard, baud rates to 19.2 kilobaud, a rugged steel cabinet and power supply. The FASTERM-64 is a 16 line by 64 or 32 character per line unit, with a serial printer port for making hard copy of all incoming data, and optional provisions for block and special character graphics. The "smart" version, SMARTERM-80, features either 24 line by 80 characters per line or 16 by 40 characters per line, it offers on-screen editing with page-at-a-time printing, 1200 pixel graphics, line graphics, absolute cursor addressing, underlining, reverse video, one-half intensity and much more . . . simply plug them into your computer or our phone modem and be on-line instantly. Use your TV set (RF modulator required) or our deluxe green phosphor monitor pictured above. For hard copy just add our matched printer.

Price breakthrough!!! Own the FASTERM-64, a complete terminal kit, ready to plug in for just \$199.95 or order the SMARTERM-80 kit for just \$299.95 (both available wired and tested). Be on-line with the million-dollar computers and data services today . . . we even supply the necessary subscription forms.

More good news: All the components in our terminals are available separately (see coupon), so you buy only what you need!!!

**FASTERM-64** . . . DISPLAY FORMAT: 64 or 32 characters/line by 16 lines . . . 96 displayable ASCII characters (upper & lower case) . . . 8 baud rates: 150, 300, 600, 1200, 2400, 4800, 9600, 19,200, (switch sel.) . . . LINE OUTPUT: RS232C or 20 ma current loop . . . VIDEO OUTPUT: 1V pp (EIA RS-170) . . . CURSOR MODES: home & clear screen, erase to end of line, erase cursor line, cursor up & down, auto carriage return/line feed at end of line & auto scrolling. REVERSE VIDEO . . . BLINKING CURSOR . . . PARITY: off, even or odd . . . STOP BITS: 1, 1.5, 2 . . . DATA BITS PER CHARACTER: 5, 6, 7 or 8 . . . CHARACTER OUTPUT: 5 by 7 dot matrix in a 7 by 12 cell . . . PRINTER OUTPUT: prints all incoming data . . . 1K ON BOARD RAM . . . 2K ON BOARD ROM . . . CRYSTAL CONTROLLED . . . COMPLETE WITH POWER SUPPLY. OPTIONAL GRAPHICS MODE — includes 34 Greek & math characters plus 30 special graphics characters. ASCII ENCODED KEYBOARD: 56 key/128 characters. SMARTERM-80 . . . DISPLAY FORMAT: 80 characters by 24 lines or 40 characters by 16 lines 128 displayable ASCII characters (upper & lower case) 8 baud rates: 110, 300, 600, 1200, 2400, 4800, 9600, 19,200 . . . LINE OUTPUT: RS232C or 20 ma current loop . . . VIDEO OUTPUT: 1V pp (EIA RS-170) . . . EDITING FEATURES: insert/delete line, insert/delete character, forward/back tab . . . LINE OR PAGE TRANSMIT . . . PAGE PRINT FUNCTION . . . CURSOR POSITIONING: up, down, right, left, plus absolute cursor positioning with read back . . . VISUAL ATTRIBUTES: underline, blink, reverse video, half intensity, & blank . . . GRAPHICS: 12,000 pixel resolution block plus line graphics . . . ON-SCREEN PARITY INDICATOR . . . PARITY: off, even or odd . . . STOP BITS: 110 baud 2, all other 51 . . . CHAR. OUTPUT: 7 by 11 character in a 9 by 12 cell . . . PRINTER OUTPUT . . . 60 OR 50 Hz VERTICAL REFRESH . . . BLINKING BLOCK CURSOR . . . CRYSTAL CONTROLLED . . . 2K ON BOARD RAM . . . ASCII ENCODED KEYBOARD: 56 key/128 character . . . 4K ON BOARD ROM . . . COMPLETE WITH POWER SUPPLY.

TELEPHONE MODEM 103 O/A . . . FULL DUPLEX, FCC APPROVED . . . DATA RATE: 300 baud . . . INTERFACE: RS232C and TTY . . . CONTROLS: talk/data switch (no need to connect and disconnect phone), originate/answer switch on rear panel . . . NO POWER SUPPLY REQUIRED. ASCII KEYBOARD ASCII-3 . . . 56 KEY/128 CHARACTER ASCII ENCODED . . . UPPER & LOWER CASE . . . FULLY DEBOUNDED . . . 2 KEY ROLLOVER . . . POS OR NEG LOGIC WITH POS STROBE . . . REQUIREMENTS +5 & -12V DC (SUPPLIED FROM VIDEO BOARDS) PRINTER COMET I . . . SERIAL I/O TO 9600 BAUD . . . 80 CHARACTER COLUMN (132 COMPRESSED) . . . 10" TRACTOR FEED . . . UPPER/LOWER CASE . . . INDUSTRY STANDARD RIBBONS . . . 4 CHARACTER SIZES . . . 9 BY 7 DOT MATRIX . . . BIDIRECTIONAL PRINTING



Continental U.S.A. Credit Card Buyers Outside Connecticut

**CALL TOLL FREE 800-243-7428**

To Order From Connecticut Or For Tech. Assist. Call (203) 354-9375

**NETRONICS R&D LTD. Dept.**

333 Litchfield Road, New Milford, CT 06776

Please send the items checked below:

COMPLETE FASTERM-64 TERMINAL (includes FASTVID-64 video board ASCII-3 keyboard, steel cabinet and power supply) . . . kit \$199.95 plus \$3 P&I\* . . . wired & tested \$249.95 plus \$3 P&I\* . . . graphics option: add \$19.95 to each of above

COMPLETE SMARTERM-80 TERMINAL (includes SMARTVID-80 video board, ASCII-3 keyboard, steel cabinet and power supply) . . . kit \$299.95 plus \$3 P&I\* . . . wired and tested \$369.95 plus \$3 P&I\*

FASTVID-64 VIDEO BOARD (requires +5 & -12V DC) . . . kit \$99.95 plus \$3 P&I\* . . . graphics option add \$19.95 . . . wired & tested \$129.95 plus \$3 P&I\* . . . graphics option add \$19.95

SMARTVID-80 VIDEO BOARD (requires +5 & +/-12V DC) . . . kit \$199.95 plus \$3 P&I\* . . . wired & tested \$249.95 plus \$3 P&I\*

DELUXE STEEL TERMINAL CABINET . . . \$19.95 plus \$3 P&I\*

ASCII-3 KEYBOARD (requires +5 & -12VDC) . . . kit \$69.95 plus \$3 P&I\* . . . wired and tested \$89.95 plus \$3 P&I\*

POWER SUPPLY (powers ASCII-3 keyboard & video boards) . . . kit only \$19.95 plus \$2 P&I\*

ZENITH VIDEO MONITOR (high resolution green phosphor) . . . wired & tested \$149.95 plus \$6 P&I\*

TELEPHONE MODEM MODEL 103 O/A . . . wired & tested \$189.95 plus \$3 P&I\*

DOT MATRIX PRINTER Comet I . . . wired & tested \$299.95 plus \$10 P&I\*

RF-MODULATOR MOD RF-1 . . . kit only \$8.95 plus \$1 P&I\*

3FT-25 LEAD MODEM/TERMINAL OR PRINTER/TERMINAL CONNECTOR CABLE . . . \$14.95 ea plus \$2 P&I\*

For Canadian orders, double the postage. Conn. res. add sales tax.

Total Enclosed \$\_\_\_\_\_

Personal Check  Cashier's Check/Money Order

VISA  MasterCard (Bank No. \_\_\_\_\_)

Acct. No. \_\_\_\_\_ Exp. Date \_\_\_\_\_

Signature \_\_\_\_\_

Print Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

**NETRONICS Research & Development Ltd.**

333 Litchfield Road, New Milford, CT 06776

SEPTEMBER 1982

# 28K Commodore VIC Personal Computer \$299

(60% more powerful than VIC-20)

FOR THE SPECIAL SALE PRICE of \$299.00, you get the Commodore VIC-20 computer, plus we add 60% more programming power. This powerful full sized extra featured computer includes the 6502 microprocessor (LIKE APPLE), 20,000 bytes ROM with a 16K extended microsoft LEVEL 11 BASIC, 8000 bytes user RAM, plug in expandable to 32K RAM, 66 key typewriter professional keyboard with graphic symbols on keys, 16 colors with command keys, sound and music, real time, upper/lower case, full screen editing cursor, floating point decimal and trig functions, has high resolution graphics, 512 displayable characters, test display is 23 lines, 22 characters, will accept TAPE-DISK-PLUG IN CARTRIDGES. We have great games and many other programs. It has low cost, direct plug in peripherals, does not require an expensive interface board for modems, printers or floppy disks, connects to any TV, includes AC adapter, RF modulator, switch box, self teaching instruction book, 90 day immediate replacement warranty! Comes in a beautiful console case for only \$299. (You can get a 41K COMMODORE VIC for \$379). We stock more VIC-20 programs than anyone! — WRITE FOR FREE CATALOG!

**15 DAY FREE TRIAL** Return within 15 days complete and undamaged for refund of purchase price.

**DON'T MISS THIS FANTASTIC SALE!!** Phone 312/382-5244 to order and get delivery in 2 to 7 days, or send a certified check, money order or personal check to **PROTECTO ENTERPRIZES, BOX 550, BARRINGTON, ILLINOIS 60010**. We honor Visa and Master Charge, Ship C.O.D Add \$10.00 for shipping, handling and insurance. Illinois residents add 6% tax.

CIRCLE 38 ON FREE INFORMATION CARD

Someone with a weak heart could brush by it accidentally and suffer a fatal shock.

The letter reminded me of a guy who wired his garbage cans to raw AC "to keep the dogs out of them." That nut could have electrocuted someone.

Be smart. Don't let your knowledge of electronics overcome good sense. I don't know about the laws in Australia, but I suspect that there, as well as here, a guy could get himself in serious trouble by pulling a stunt like that.

### Something for nothing

Seldom, if ever, does one get something for nothing. There is another scam going around that I'd like to warn you about; you should be on guard if it comes your way.

You know, of course, about the illegal chain letters that promise riches. It seems that someone has come up with a new version.


One of our readers from Welland, Ontario, Canada sent me a "membership form" from a "Book Club." Most of the chain letters that I've seen ask for money, but this one asks for books and magazines instead. Interestingly, almost half of the names/addresses on the list are from Central America (the rest are from the U.S.). The reader thinks that they got his name and address from a letter published in a magazine.

R-E

# TOTAL CONVENIENCE

**Model 324**  
THE ELECTRONIC  
WORK CENTER

SUGGESTED  
RETAIL PRICE  
**\$49.95**

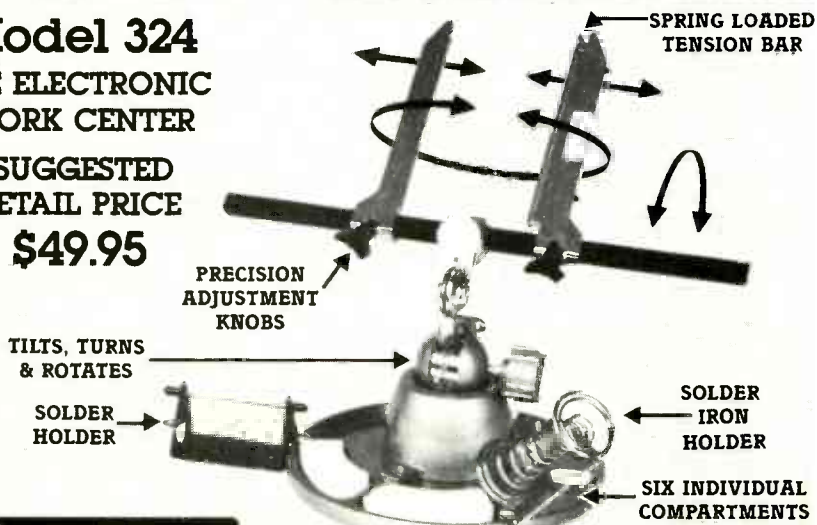

Contact your local dealer today.

PANAVISE PRODUCTS, INC. 2850 E. 29th St., Long Beach, Ca. (213) 595-7621

CIRCLE 39 ON FREE INFORMATION CARD

## Aaron-Gavin Kits




LED meter



EQUALIZERS PRICED FROM \$119. to \$690.  
LED METERS PRICES \$48. to \$219.

A Unique MIXER for DJ's—Studio's—Broadcasters

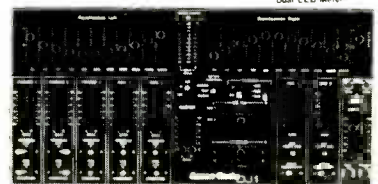- Two MIC inputs
- Two AUX Channels
- 3 Turntable inputs
- Talkover Switch
- Crossfade
- Auto Cue
- Beat Match
- Subsonic Filters
- Even Band Stereo EQUALIZER
- Headphones
- Mono Test Tone
- Dual LED Meter



Call or write for full product information, and pricing to:  
AARON-GAVIN  
123 South McClay Street, Unit F,  
Santa Ana, CA 92701, (714) 957-8710



**ADVANCE IS PROUD TO INTRODUCE**  
**The HITACHI Line**  
**of High Quality Oscilloscopes**  
**All Hitachi Instruments**  
**Are Backed by**  
**A Two-Year Warranty**

**AT LAST A 100MHz OSCILLOSCOPE**  
**WORTH WAITING FOR**  
**WITH NO WAITING**



**CALL FOR INTRODUCTORY OFFER**

**HITACHI 100MHz OSCILLOSCOPE MODEL V-1050**

**V-202 & V352**  
**20MHz & 35MHz DUAL TRACE OSCILLOSCOPES**



- 20kV CRT supply
- Large, bright 8 x 10 cm screen
- Four-trace operation (Ch1, Ch2, A trigger, B trigger)
- High sensitivity 500 uV/div (5MHz)
- High accuracy  $\pm 2\%$  (+10°C to 35°C)
- Alternate timebase operation
- Full TV triggering

**IN STOCK FOR IMMEDIATE DELIVERY**

- NEW**
1. Square CRT with internal graticule (illuminated scale)
  2. High-accuracy voltage axis and time axis set at  $\pm 3\%$  (certified at 0° to 35°C)
  3. High-sensitivity 1mV/div
  4. Low drift
  5. Dynamic range 8 div.
  6. TV sync-separator circuit
  7. Built-in signal delay line (V-352)
  8. X-Y operation
  9. Sweep-time magnifier (10 times)
  10. Trace rotation system
  11. Fine-adjusting, click-positioning function

**C.R.T.**

Type Hitachi 150BNB31 rectangular mesh type tube with 20kV acceleration potential and metal backed phosphor.

**VERTICAL DEFLECTION (2 Identical Channels)**

Bandwidth and Rise Time DC to at least 100MHz and rise time 3.5ns or less. 10x to at least 5MHz and rise time 70ns or less at 10 X magnification. Lower 3db point, AC coupling 10Hz or less. 10x Probe: 1Hz or less.

**HORIZONTAL DEFLECTION**

Time Base A 20ns/div. to 0.5s/div. in 23 calibrated steps, 1-2.5 sequence. Uncalibrated continuous control between steps 1: < 2.5

Time Base B 20ns/div. to 50ms/div. in 20 calibrated steps 1-2.5 sequence. 10x mag extends fastest sweep rate to 2ns/div.

Calibrated Sweep Delay Continuous calibrated control between 0.5 and 10x time base A setting.

**V-550B 50MHz, DUAL TRACE DELAYED SWEEP PORTABLE OSCILLOSCOPE**



Delayed sweep permits 1,000 X Magnification

Variable Hold-off Circuitry Facilitates Pulse Measurement

- Large, Bright 8 x 10cm Screen
- High Sensitivity 1mv/div (10MHz)
- 5 ns/div Sweep Rate
- 3rd Channel Display (Trigger View)
- Variable Trigger Hold-off
- Full TV Triggering
- Single Sweep
- Automatic Focus Correction

**ADVANCE ELECTRONICS**

**THE TEST EQUIPMENT SPECIALISTS**

**TOLL FREE HOT LINE**  
**800-223-0474**



54 WEST 45th STREET, NEW YORK, N.Y. 10036 212-687-2224

# COMMUNICATIONS CORNER

## Touch-Tone devices and FM adjustments

HERB FRIEDMAN, COMMUNICATIONS EDITOR

AS MORE AND MORE COMMUNICATIONS systems requiring *Touch-Tone* signals for access and operation made their appearance, I found that the *Touch-Tone* pad I had purchased several years ago had become a constant companion.

The pad was purchased from a **Radio-Electronics** advertiser and was either standard Bell System "surplus," or salvage from a *Touch-Tone* phone. I installed it in a matching plastic case, for which I paid a couple of dollars (it's now selling for \$10-\$15), added a battery for power and a set of output-signal clip leads, and I carried it in my attache case or the glove compartment of my car.

If I needed to access my 2-meter repeater's autopatch I plugged the pad into a small jack I had installed on my 2-meter mobile rig. (That was before I got Heathkit's combination mobile mike and *Touch-Tone* pad.) To enter information into my computer from a remote point I clipped the leads from the pad across the phone line if I couldn't locate a *Touch-Tone* phone during my travels.

Like just about all other Bell System equipment, the gadget has never failed. The only problem is that its frequencies



FIG. 1

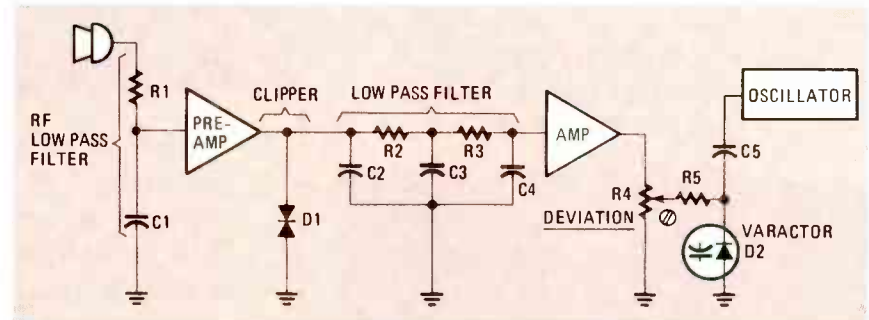


FIG. 2

are determined by pot coils (inductors) that are huge by contemporary standards. Until recently I was always lugging around some sort of case just to carry the pad.

Though the earliest users of portable *Touch-Tone* pads were radio amateurs and other hobbyists, with the tremendous expansion in communications circuits and computers requiring *Touch-Tone* signals for control or data, there has been created a need for a truly portable *Touch-Tone* generator that can be easily coupled to a standard telephone. One of the earliest—and still popular—devices was the *Soft Touch*. That was a gizmo the user substituted for the telephone transmitter (mouthpiece) by unscrewing the handset's transmitter and temporarily replacing it with the device, which consists of a small microphone surrounded by 12 *Touch-Tone* "buttons." Unfortunately, if the phone's assembler gave the mouthpiece an extra twist when assembling it, nothing short of a special strap wrench would be able to get it loose.

A much easier way to handle "portable" signaling with *Touch-Tones* is Radio-Shack's *Mini Tonedialer*, which is certain to be the first of many similar gadgets.

The device, shown in Fig. 1, is a battery-powered, shirt-pocket-sized device with the standard *Touch-Tone* keypad arrangement on one side and a small speaker on the other. To transmit *Touch-Tones*, you simply place the side with the speaker against a telephone's transmitter (or a microphone), and press the key corresponding to the desired number (0-9) or symbol (\* or #). The speaker reproduces the corresponding tones for as long as the key is depressed.

Unlike my old authentic telephone pad

that had to be carried around in a briefcase or in a small camera bag, Radio Shack's unit actually fits in a shirt pocket because it measures only 2.4 × 4.4 × 0.7 inches. (You can even button the pocket of a Western-style shirt with it inside.) Its overall weight, including batteries, is about 1.5 ounces—less than that of some pocket pens.

What makes all that possible, of course, is the integrated circuit. The entire dialer consists of a single IC that generates the tones; a miniature crystal for the time-base reference; a transistor "output" stage that drives a 1.6-inch speaker; three resistors, and a capacitor. Except for the speaker, everything—including the batteries—is installed on a printed-circuit board whose foils also serve as the switch contacts. The low parts-count is the reason the whole thing costs only about \$35.

### Setting FM levels

Lately, it seems that there's a lot of commercial VHF and UHF FM gear floating around the surplus dealers and flea markets. The stuff is obviously good because I've worked on many that were converted to the amateur frequencies. Often, though, I've found that the hobbyists get lost in the modulator.

Actually, frequency-modulation systems are rather simple: A typical block diagram is shown in Fig. 2. The output from the microphone is usually fed to the preamplifier through an R-C network (R1/C1) that serves as a low-pass filter to keep RF that might be picked up by the microphone cable out of the preamplifier. To equalize the loud and soft voice levels, the preamp's output is clipped by diode(s) D1. The clipper simply sets a ceiling on

*continued on page 110*

“Mobile antenna mounting and cable routing on today’s cars are a nightmare”


“We just can’t find a high performance antenna that doesn’t need a ground plane”


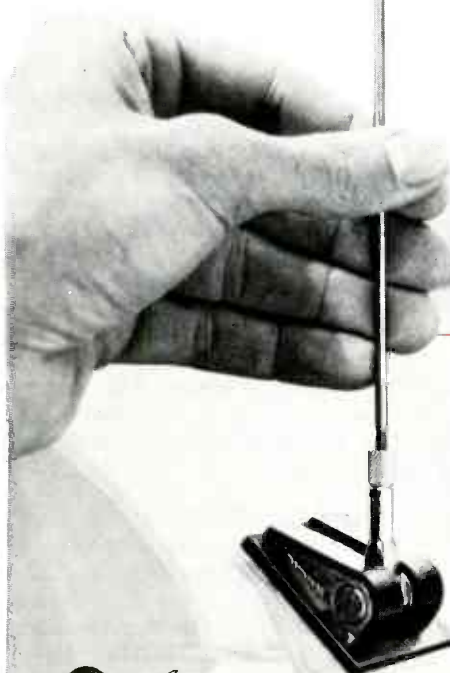
# Avanti. The on-glass, halfwave, 15-minute solution from the antenna specialists co.

**Model AV-240 Moon Fantom™** CB antenna, ideal for vans, motorcycles... even apartment windows!

- **Co-inductive coupling** establishes highly tuned circuit through glass or any non-conductive material up to 3/4" thick, with no measurable signal loss.
- **No ground plane:** full electrical halfwave design provides omnidirectional performance equal to practical 5/8 wave installations.
- **New DUO-BOND mounting system** for firm, resilient, waterproof bonding in minutes—yet removable without damage to car or antenna.
- **No holes to drill, no damage to vehicle**... easy, fast cable routing.




**MS-119 Super Scanner™**  
Search with 5.75 dB gain... instantly zero in with 8.75 dB electronic beam—no rotator.

**New MON-64 DISCAN™** monitor antenna.  
Lightweight, economical. Excellent performance, all bands.

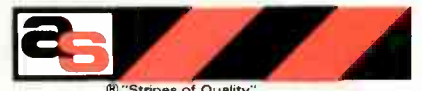**the antenna specialists co.**

the antenna specialists co.  
a member of The Allen Group Inc.  
12435 Euclid Ave., Cleveland, OH 44106  
Canada: A. C. Simmonds & Sons, Ltd.



® "Stripes of Quality"

**we design solutions.**



Support your local REACT Team... We do!®

CIRCLE 20 ON FREE INFORMATION CARD

# COMPUTER CORNER

## Electronic worksheets for your computer

LES SPINDLE\*

THE BUSINESS SOFTWARE FIELD IS A dynamic market nowadays. Competition and improved technology are combining to make each new product just a little more sophisticated than the one that preceded it. Computer programs now serve not only as proofreaders and grammarians, but also as program writers, teachers of languages and operating systems, and sophisticated accountants. But no single software development has had the impact of VisiCorp's (formerly Personal Software) 1980 introduction of *VisiCalc*.

Dozens of current software releases are fashioned after the simple, but revolutionary, concept that *VisiCalc* pioneered—the micro as an electronic worksheet for financial planning.

The "Visiclones" (as they are sometimes referred to) enable the user to format a "worksheet" of figures on the screen, then modify those figures in any number of different ways and see the results of the modifications.

Mathematical relationships between any of the rows and/or columns can be defined. Suppose, for instance, that you want the bottom row to be the sum of all the rows above it. That can be accomplished with one simple command. Other mathematical calculations—log and trig functions, percentages, etc.—can easily be accomplished in the same manner.

If one item on the worksheet is changed, every other item whose value depends on that item is automatically changed at the same time. It is possible to add new rows and columns or to change the order of existing ones. Meanwhile, the items whose values depend on the new setups are also automatically changed.

The program is an ideal tool for projecting budgets, planning expenditures, and charting various business strategies. Printouts of the various combinations can be made, for a step-by-step presentation of the pros and cons of each strategy. Presenting the various phases of an operation to a board of directors' meeting, for instance, can be both efficient and impressive. But even more important than that is the time saved by the user as he works out his options in the planning process.

For example, suppose a retail sales manager wants to make an intelligent guess as to sales trends over a yearly



FIG. 1

period. He devises a format consisting of several variables, such as interest rates, his best-selling products, his slow-moving merchandise, the number of salesmen in the field, and the previous year's sales. To further enhance the credibility of the outcome, he takes into account the fact that in his line, winter is the heaviest selling season. With his format completed, he enters all the necessary data, then begins to examine the results.

His analysis will take much less time than if he had sat down with adding machine, scratchpad, and a big eraser. His report will project sales for each of the next 18 months. After consulting with his associates, he will likely have dozens of data changes to enter when he returns to re-work the projections. But, once the initial program has been set up, making those changes is simple.

### How they're used

How does a user format the worksheet to fit his particular application? Most of the programs are well-documented with simple commands and self-prompting menus that lead him step-by-step through

the formatting process. Using his computer's available internal memory, he formats a model consisting of the rows and columns that he will need. The size of the model is restricted only by the available memory. Filing and retrieving of data is done using disks, so that is usually not a factor in the size of the worksheet model.

Once the model is visible on the CRT screen, the user can decide how to define each row and column on the "blank" worksheet. Each coordinate location is assigned either an alphanumeric comment, a label (such as a row description), or a constant or formula that relates the contents of several coordinates to each other. When that is done, the worksheet is ready for use.

### Choosing a program

With the number of products on the market, it is sometimes difficult to decide on the best one for your particular application. You are restricted somewhat by your computer's operating system, memory capacity, and microprocessor. Some versions are configured for a particular computer and its specific operat-

\*Managing Editor, *Interface Age* magazine

# How to get an 8-channel scope for \$349.50


Add our Model 8001 8-channel multiplexer to your present oscilloscope: It's the perfect way to view and compare signals occurring at different points in a circuit or system—in their real time and amplitude relationships. As well as one of the best bargains in test equipment today.

Now you can have multi-channel capability wherever and whenever you need it. In the lab. On the production line. In quality control. And service—on the bench or in the field. All for just \$349.50\*!

Just connect its eight 1-megOhm inputs to your circuit via the front-panel BNC connectors. It's flat to 12MHz (-3dB at 20MHz) and will handle digital and analog signals up to  $\pm 5V$  (10V p-p) in any combination. There's plenty of flexibility, too. Thanks to a variety of switch-select-

able display/output combinations, multiplexer rates and operating modes that enable you to view each channel individually or all, simultaneously—with pushbutton calibration. And a vertical master gain control that's continuously variable from 0-75mV/cm/channel.

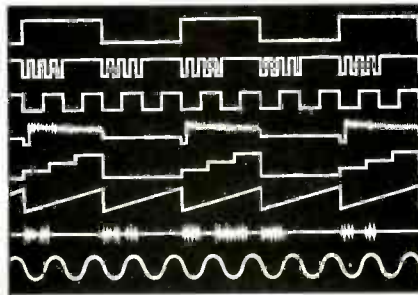The trigger input, with switch-selectable polarity, is assigned to



View up to eight digital and/or analog signals (up to 10V p-p) on your present scope!

channel one with continuously variable trigger level ( $\pm 5V$  range). And you can choose a switch-selectable 0.1 or 1.0 usec TTL-level pulse at the trigger output.

It's simple: When you consider how much time our 8001 multiplexer can save you... how much versatility it offers... and how little it costs, there's only one thing you'll want to know. How quickly you can get your hands on one. Which we'll be glad to tell you when you dial the toll-free number below.

**GLOBAL SPECIALTIES**

70 Fulton Terr., New Haven, CT 06509  
(203) 624-3103, TWX 710-465-1227

\*Suggested U.S. resale. Prices, specifications subject to change without notice.



**Call Toll-Free for Details 1-800-243-6077**

During Business Hours, 9AM to 6PM Eastern Time

OTHER OFFICES: San Francisco (415) 648-0611, TWX 910-372-7952,  
Europe: Phore-Saffron-Walden 0799-21682, T\_X 817477, Canada: Len Finkler Ltd. Downsview, Ontario.

CF-CLE 11 ON FREE INFORMATION CARD

# WE TAKE YOU BY THE HAND!

You'll learn all about computers: how to build, program, service, even play TV games—without knowing the first thing about it!



## The New ELF II "Beginners" Package

Your own expandable micro-computer kit, 5 diagnostic analyzers plus circuit, programming, diagnostic manuals, even games you can play on TV. All only \$139.95.

Even if you don't know bits from bytes, now it's easy and inexpensive to build your own micro-computer. Learn how it works, program it, service it—even play games with it on your TV! It's here in the New ELF II "Beginners" Package, only from Netronics. Only \$139.95. Here's the package: 1. your own micro-computer, the famous ELF II (featuring the RCA 1802 CMOS microprocessor) in kit form with step-by-step instructions on how to build it. Diagnostic Analyzers including 2. your own Logic Probe, 3. Pulse Catcher, 4. 8 bit Test Register, 5. Logic Analyzer, 6. Gate Arrays, 7. Non-Technical Manuals on how to use analyzers, how to get into the guts of the computer, what makes it tick, how to service it. 8. Sample Programs that teach you machine language programming plus how to correct or "debug" any programming mistakes. 9. TV games you can play. If your TV set has no video input, an optional converter (RF Modulator), is available. Then, once you've got this "Beginners" Package under your belt, keep on expanding your ELF II with additions like the Typewriter Key Board, added RAM, Full Basic Interpreter, Electric Mouth Talking Board, Color/Music, A/D-D/A Boards for Robot Controls and much, much more. We'll take you by the hand with the New ELF II "Beginners" Package. Only \$139.95. Mail or phone in your order today and begin.

### Specifications: ELF II "Beginners" Package

The computer features an RCA CMOS 1802 8 bit microprocessor, addressable to 64K bytes with DMA, interrupt, 18 Registers, ALU, 256 byte RAM expandable to 64K bytes. Professional Hex keyboard, fully decoded so there's no need to waste memory with keyboard scanning circuits, built-in power regulator, 5 slot plug-in expansion BUS (less connectors), stable crystal clock, for timing purposes and a double-sided, plated through PCB board plus RCA 1861 video IC to display any segment of memory on a video monitor or TV screen along with the logic and support circuitry you need to learn every one of the RCA 1802's capabilities. The diagnostic analyzers aid in understanding and trouble shooting your ELF II, as well as other computer and microprocessor products.

Continental U.S.A. Credit Card Buyers Outside Connecticut

**CALL TOLL FREE 800-243-7428**

To Order From Connecticut or For Technical Assistance, Etc.,

Call (203) 354-9375

**NETRONICS R&D LTD.** [Dept. RE 32]  
333 Litchfield Road, New Milford, CT 06776

Please send the items checked below:

- ELF II "Beginners" Kit ..... \$139.95  
 RF Modulator ..... \$ 8.95

Plus \$3.00 for postage, handling and insurance  
(\$6.00 Canada)

Connecticut Residents add sales tax

Total Enclosed \$ \_\_\_\_\_

- Personal Check     Cashier's Check/Money Order  
 Visa                 Master Charge (Bank No. \_\_\_\_\_)

Acct. No. \_\_\_\_\_

Signature \_\_\_\_\_ Exp. Date \_\_\_\_\_

Print Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

ing system, such as TRSDOS for the TRS-80 or CDOS for Cromemco. A number of new products, though, are CP/M-based, and can be used on any computer that can run the CP/M disk-operating system. In most cases, however, you should be able to find several options for your setup.

Once you've found the products, you can examine the specific features offered by each program to determine which is best suited for your applications. Following are some of the features to keep in mind as you make your choice. Keep a checklist handy as you shop.

First, determine the size of the matrix. Find out how many rows and columns are possible and analyze your needs to see whether their capacity is sufficient for your applications. Be aware that it is seldom possible to use all the rows and columns at the same time since both are affected by the total memory-capacity of the computer.

Investigate the arithmetic precision of the program. There are limitations on the number of digits that certain programs can accommodate, and they may affect you if your calculations involve very large or very small numbers.

See whether the program allows for a "comment column." That is a position, of varying length, that allows you to write some description of the row beside it. The feature can be useful for complex transactions that require more description.

Does the program include graphics capabilities? Bar charts and the like are sometimes desirable, especially for meetings and formal presentations.

Is split-screen capability available? Some of the more advanced programs allow it, and it can be a tremendous asset in comparing the results of related plans.

Can the program interface with other programs? If data from word-processing, general ledger, payroll, or other programs at work in your system can be used directly by your worksheet, or vice-versa, the door is opened for a wealth of time-saving features. Suppose you are producing a written sales-report and would like to integrate a worksheet as part of the presentation. Without word-processor-interfacing capabilities, you would have to re-enter the entire sheet in order to integrate it into the report.

For clarity of reading, the ability to line up figures in a row correctly is crucial. For instance, if the decimal points in the numbers 596.83 and 9344.7 were not aligned vertically, it would be hard to distinguish which were the fractional elements simply by glancing at the column.

Does the program allow for partial printouts? Can you print one row or column, or a section of a report without taking the time to run the entire program?


Is it possible to jump to one point in the model instantaneously from another? If you are in column C, row 7, can you

*continued on page 108*

## The FEATURES you want in a

**20 MHz DUAL TRACE OSCILLOSCOPE**

DC-20 MHz dual trace @ 5mV to 10V/Div on 11 ranges. Operating modes Ch 1, Ch 2, dual, add, sub., chop, X-Y. Sweep Time 0.5  $\mu$  sec to 0.5 sec/Div on 19 ranges plus X5 mag. 5 trigger selections; 3 filters; auto free run; TV-V/H. 5 1/2" rect. CRT with internal graticule and 2kV acceleration. TTL intensity modulation. Switching regulator power supply. Comes complete with two 10:1 hook-on probes. Detachable 3 conductor AC cord, spare fuses, and full one year ltd. warranty.

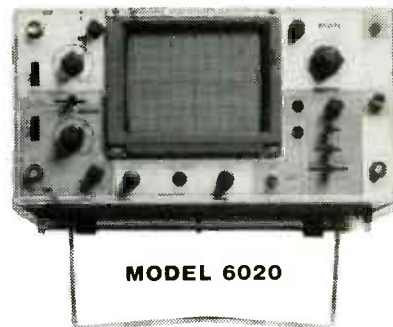

**MODEL 6020**


## At PRICES you can AFFORD!

|                                 | 1-9<br>Ea. | 10 up<br>Ea. |
|---------------------------------|------------|--------------|
| MS-6020 Described               | \$649.00   | \$585.00     |
| MS-6021 with Delay Sweep        | 699.00     | 630.00       |
| MS-6120 with Built-in 3 1/2 DMM | 765.00     | 690.00       |

Available at selected distributors or write/phone:

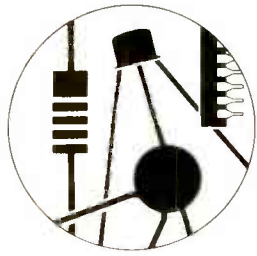**NORTH AMERICAN** 

1126 Cornell Avenue  
Cherry Hill, NJ 08002  
Tel. (609) 488-1060



Looking for new ideas,  
projects, and  
money-saving tips?

The **ELECTRONICS BOOK CLUB**  
has hundreds of titles  
most-wanted by hobbyists  
and experimenters!

Select 6 info-packed volumes  
for only **\$2.95** (total value up to \$115.70)



Join the Electronics Book Club! Get 6 Best  
Selling Books for only \$2.95 (VALUES TO \$115.70)  
Seven reasons why you belong  
in the Electronics Book Club

- You save money.** Save up to 75% on books and ideas sure to increase your know-how. You'll save even more because you'll be able to perform many tasks without calling in outside help.
- Your satisfaction guaranteed.** Any book you buy is returnable within 10 days without obligation.
- You receive news of new books and ideas.** About 13 times a year, you will get a Club News Bulletin with current book selections and bonus offers—dozens of up-to-the-minute titles you can pick from, each with exciting new ideas.
- You receive books automatically.** You will receive automatically a new book selected by the Editorial Board as a Main Selection. But, you can choose another book or no book at all by mailing the business reply form contained in each News Bulletin.
- You get special bonuses.** The club has special sales and added-value promotions for members to increase your library of knowledge. And, after fulfilling your membership obligation, you will receive a dividend certificate with each book purchased to qualify for even greater discounts.
- You'll have a library of exceptional quality.** Each Electronics volume is a full-length publisher's edition, filled with useful, up-to-the-minute information.
- You'll gain practical knowledge and confidence.** EBC will add to your practical skills about jobs that you face every day. All books contain easy-to-understand language that will add to your confidence in completing almost any task.

**ELECTRONICS BOOK CLUB**  
Blue Ridge Summit, PA 17214

Please accept my membership in Electronics Book Club and send the 6 volumes circled below. I understand the cost of the books selected is \$2.95 (plus shipping/handling). If not satisfied, I may return the books within ten days without obligation and have my membership cancelled. I agree to purchase 4 or more books at reduced Club prices during the next 12 months, and may resign any time thereafter.

335 652 829 926 1108 1128 1160  
1169 1199 1218 1225 1249 1296 1306 1316  
1337 1338 1346 1367 1380 1390 1396  
1397 1402 1406 1409 1417 1420 1465 1475

Name \_\_\_\_\_ Phone \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_  
State \_\_\_\_\_ Zip \_\_\_\_\_

(Valid for new members only. Foreign and Canada add 20%. Orders outside U.S. or Canada must be prepaid with international money orders in U.S. dollars.)  
This order subject to acceptance by Electronics Book Club RE-982

CIRCLE 18 ON FREE INFORMATION CARD

# STATE OF SOLID STATE

## DC voltage-controlled switches

ROBERT F. SCOTT, SEMICONDUCTOR EDITOR

THIS MONTH WE'LL TAKE A LOOK AT A DC-controlled switch that can replace the usual rotary or pushbutton used to connect various signal sources to the input of an audio amplifier. In this case, the selector switch feeds the input to the graphic equalizer circuit that we discussed in the June 1982 issue.

National Semiconductor has just announced the LM1037 and LM1038 DC Controlled Audio Switches. Both are designed to allow any one of four stereo-input sources to be connected to the stereo-output lines. Channels are selected by applying a DC voltage level to the channel-select control pins. Features of the LM1037/38 switches are:

- Wide supply-voltage range (5 to 30 volts)
- Click-free operation
- Low distortion, 0.04% typical
- High signal-to-noise ratio
- High audio-input impedance
- Low audio-output impedance
- Wide control-voltage range (2 to 50 volts)
- High input-impedance on select pin

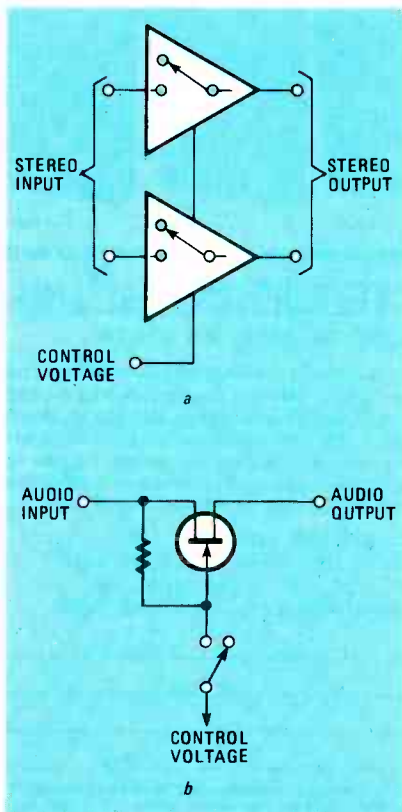


FIG. 1

**TABLE 1**

| Parameter  | Min  | Typ  | Max | Units                | Conditions                      |
|--|------|------|-----|----------------------|---------------------------------|
| Supply voltage                                       | 5    | 12   | 30  | volts                |                                 |
| Supply current (LM1037)                              |      | 7    |     | mA                   | $V_{\text{supply}} = 12$        |
| Supply current (LM1037)                              |      | 10   |     | mA                   | $V_{\text{supply}} = 30$        |
| Supply current (LM1038)                              |      | 14   |     | mA                   | $V_{\text{supply}} = 12$        |
| Supply current (LM1038)                              |      | 20   |     | mA                   | $V_{\text{supply}} = 30$        |
| Voltage gain   | -0.2 | 0    |     | dB                   |                                 |
| Signal handling                                      |      |      | 3.2 | volts <sub>rms</sub> | $V_{\text{supply}} = 12$        |
| Distortion (THD)                                     |      | 0.04 | 0.1 | percent              | $1V_{\text{rms}}$ input @ 1 kHz |
| S/N Ratio (CCIR)                                     |      | -100 |     | dB                   | $1V_{\text{rms}}$ input @ 1 kHz |
| Crosstalk between stereo channels                    | -80  | -100 |     | dB                   | $1V_{\text{rms}}$ @ 1 kHz       |
| Crosstalk between connected and unconnected channels | -80  | -100 |     | dB                   | $1V_{\text{rms}}$ @ 1 kHz       |
| Relative output in muted state                       | -80  | -90  |     | dB                   | $1V_{\text{rms}}$ @ 1 kHz       |

The LM1037 has four control or channel-select pins; one for each stereo-input source. If no channel is selected, the outputs are muted and clamped to the DC output level.

The LM1038 is designed so that channels can be selected by BCD input pulses. Two input pins feed clock-enabled latches so that the BCD pulses can be strobed from a bus. Or, the clock-input pin can be permanently enabled and the channels selected by DC voltage levels. A separate pin allows the output to be muted, via either a pulse or a DC level.

To date, only preliminary specifications (Table 1) on the LM1037/38 have been released, so we don't have complete details on the structure of the semiconductor device used as the switch elements; but I'll bet that the switch is some form of FET. In similar analog switches from other manufacturers, JFET's, MOSFET's and CMOS (N-channel and P-channel FET's in parallel) have been used as gates or switches. Figure 1-a is a functional diagram of a stereo-audio switch. When the control voltage is ap-

plied, the switches close so that the input signals pass through to the output terminals. Figure 1-b is the circuit of a basic analog switch using a JFET as the switch element.

Figure 2 is the functional block diagram of the LM1037. The channel-selection details are outlined in Table 2 (See page 86).

### Emitter and detector product guide

The *Infrared/Photodetector Product Guide* lists a line of GaAs IR emitting diodes and photodiodes, phototransistors, and photovoltaic cells. The IR emitters develop a wavelength of either 820 or 950 nm (nanometers) depending on the device. Detectors can be selected with maximum sensitivity specified at wavelengths ranging from 555 to 950 nm. The guide includes dimensioned outline drawings.—**Litronix**, 19000 Homestead Road, Cupertino, CA 95014.

### Unique monolithic active filter

National Semiconductor's MF10 is the first monolithic active filter that does not



## SWD-1 VIDEO CONVERTER

FOR CABLE TV



SWD-1 Video Converter Kit ..... \$69.95

The SWD-1 Video Converter is utilized on cable TV systems to remove the KH<sub>2</sub> signal from a distorted video (channel 3 in/out) and also pass thru the normal undistorted/detected audio signal. Rocker switch selects operating mode to remove KH<sub>2</sub>'s distortion from the video or pass all other channels normally. Simple to assemble—less than 30 minutes. Pre-tuned. Input/output Channel 3. Impedance 75 ohms. 117VAC.

## VTR ACCESSORIES


### SIMPLE SIMON VIDEO STABILIZER



VS-125 Video Stabilizer, wired ..... \$54.95

Simple Simon Video Stabilizer, Model VS-125, eliminates the vertical roll and jitter from "copy guard" video tapes when playing through large screen projectors or on another VTR. Simple to use, just adjust the lock control for a stable picture. Once the control is set, the tape will play all the way through without further adjustments. Includes 12V power supply.

### SIMPLE SIMON VIDEO SWITCHING BOX

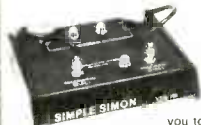

VSB-300 Video Switching Box, wired ..... \$19.95

#### The Affordable Video Control Center

Excellent in isolation and no loss routing system. Simple Simons VSB-300 Video Switching Box enables you to bring a variety of video components together for easy viewing/dubbing. Also you gain the ability to record one channel while viewing another. Unit includes two F-type quick connector end cables.

## UHF ANTENNAS and ACCESSORIES

### MDS-AMATEUR-ETV 32 ELEMENT YAGI ANTENNA



MAE-2 32 Element YAGI Antenna ..... \$23.95

- Not A Kit
- 1.9-2.5 GHz
- 38 1/2" Long
- 23dB Average Gain
- Commercial Grade
- Die Cast Waterproof Housing with 4 1/4" x 2 1/2" Area for Electronics
- Includes P.C. Probe, F-61 Connector and Mounting Hardware

### Kato Sons' Down Converter Kit ★ 1.9 - 2.5GHz★

Designed for Simple Simon by former Japanese CO Amateur Magazine's UHF Editor/Engineer. Unit utilizes new ingenious Printed Circuit Probe for maximum gain. Circuit board fits inside MAE-2 antennahousing. Requires 1 hour assembly. IC and capacitors pre-soldered.

Model KSDC-KIT 1.9 - 2.5GHz Down Converter Kit ..... \$34.95

**Kato Sons' Regulated Variable DC Power Supply**  
For use with KSDC-KIT 1.9 - 2.5GHz Down Converter. Completely assembled with Attractive Cabinet, TV/Converter Mode Switch, Frequency Control and LED Indicator.

Model KSPS-1A Assembled Power Supply ..... \$23.95

### ORDER ALL THREE ITEMS

MAE-2, KSDC-KIT and KSPS-1A for Only **\$74.95**

Regular price if ordered separately \$82.85

CO-AX CABLES ARE NOT INCLUDED

### ZYZZX VHF-UHF Wideband Antenna Amplifier



#### Revolutionary New HYBRID IC Broadband Amplifiers

50 MHz - 900 MHz  
Model ALL-1 12dB Gain  
Model ALL-2 35dB Gain

These units are not available anywhere else in the world. Each unit will serve many purposes and is available in Kit or Assembled form. Ideal for outdoor or indoor use. I/O impedance is 75 ohms. Amplifiers include separate co-ax feed power supply. Easily assembled in 25 minutes. No coils, capacitors to tune or adjust.

ALL-1 Complete kit w/power supply ..... \$24.95  
ALL-2 Complete kit w/power supply ..... \$34.95  
ALL-1 Wired/TESTED w/pwr supply ..... \$34.95  
ALL-2 Wired/TESTED w/pwr supply ..... \$44.95

### Our New STVA 14.5dB GAIN, 14 ELEMENT CORNER REFLECTOR YAGI ANTENNA



STVA-3 Yagi Antenna, 14.5dB Gain, Selectable 75 or 300 ohm Channel 60-80 ..... \$19.95

STVA-4 Yagi Antenna, 14.5dB Gain, Selectable 75 or 300 ohm Channel 44-52 ..... \$19.95

RG-59/U 75 ohm Low Loss Coax Cable ..... \$1.29/ft.  
F-58 Coax Connector ..... \$ .39 ea.

MT-1 Special UHF 75-300 ohm Matching Transformer ..... \$1.45 ea.

# Switch to Bambi!

## Electronically

Bambi Electronic Video Switch ... makes switching of your VCR/VTR, Pay TV Decoders, Cable TV, Video Discs, Video Games, Closed Circuit TV, Antennae and Microcomputer as easy as pushing buttons.


The Bambi Electronic Video Switch is an electronic switching network which can accept up to six different sources of video signals and provide the flexibility of directing the inputs to any or all of the three outputs.

Now you can eliminate ... the drudgery of disconnecting and reconnecting your video equipment each time you use it ... the tangled mess of cables which are impossible to trace out ... not being able to use more than one function at a time.

Bambi lets you enjoy using your video equipment the way it should be ... electronically and on line at the push of a button.

Model BEVS-1 Wired

\$129.95

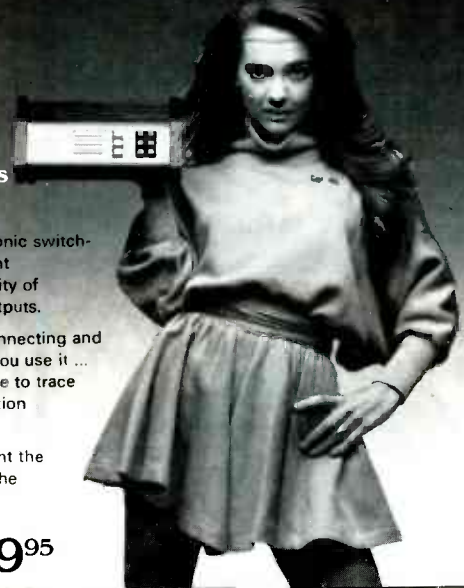

Bambi's front panel was designed with the user in mind. Computer styled construction, with soft-touch keyboard (rated for over 10 million operations), arranged in matrix form allows easy input/output selection without referring to charts. Functions selected through the keyboard are immediately displayed on the 18 LED status indicators.



Check the quality of Bambi against that of much higher priced competition. All solid state electronic switching provides low attenuation (3dB), wide frequency response (40-890 MHz), and excellent isolation between signal sources (each I/O section individually shielded for 65dB min. isolation).




Bambi's Specifications:  
 • Input/Output Impedance 75 ohm  
 • Signal Loss 3dB ±1dB  
 • Noise 4dB ±1dB  
 • Input Return Loss 12dB min  
 • Isolation 65dB min  
 • Power Req. 117VAC 60 Hz, 2W  
 • Dimensions 10 1/4" W x 6" D x 3 1/4" H  
 • Weight 4 1/2 lbs

## 7+11 SWD PARTS KITS
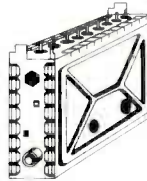
### mitsumi VARACTOR UHF TUNER Model UES-A56F \$24.95

Freq. Range UHF470 - 889MHz  
Antenna Input 75 ohms  
Channels 14-83 Output Channel 3



| KIT NO  | PART NO | DESCRIPTION   | PRICE   |
|---|---------|---|---------|
| 1   | VT1-SW  | Varactor UHF Tuner, Model UES-A56F  | \$24.95 |
| 2   | CB1-SW  | Printed Circuit Board, Pre-Drilled  | 18.95   |
| 3   | TP7-SW  | P.C.B. Potentiometers, 1-20K, 1-1K, and 5-10K ohms, 7-pieces  | 5.95    |
| 4   | FR35-SW | Resistor Kit, 1/4 Watt, 5% Carbon Film, 32-pieces   | 4.95    |
| 5   | PT1-SW  | Power Transformer, PRI-117VAC, SEC-24VAC, 250ma   | 6.95    |
| 6   | PP2-SW  | Panel Mount Potentiometers and Knobs, 1-1KBT and 1-5KAT w/Switch  | 5.95    |
| 7   | SS14-SW | IC's 7-pcs, Diodes 4-pcs, Regulators 2-pcs Heat Sink 1-piece  | 29.95   |
| 8   | CE9-SW  | Electrolytic Capacitor Kit, 9-pieces  | 9.95    |
| 9   | CC33-SW | Ceramic Disk Capacitor Kit, 50 WV., 33-pieces   | 7.95    |
| 10  | CT-SW   | Variable Ceramic Trimmer Capacitor Kit, 5-65pfd, 6-pieces   | 5.95    |
| 11  | L4-SW   | Coil Kit, 18mHs 2-pieces, 22uHs 1-piece (prewound inductors) and 1 T37-12 Ferrite Torroid Core with 3 ft. of #26 wire.          | 5.00    |
| 12  | ICS-SW  | IC Sockets, Tin inlay, 8-pin 5-pieces and 14-pin 2-pieces   | 1.95    |
| 13  | SR-SW   | Speaker, 4x6" Oval and Prepunched Wood Enclosure  | 14.95   |
| 14  | MISC-SW | Misc. Parts Kit Includes Hardware, (6/32, 8/32 Nuts & Bolts), Hookup Wire, Ant. Terms, DPDT Ant. Switch, Fuse, Fuseholder, etc. | 9.95    |
| When Ordering All Items, (1 thru 14), Total Price |         |   | 139.95  |

## 7+11 PWD PARTS KITS

### INTRODUCING OUR 7+11 PWD PARTS KITS



| KIT No                                       | PART NO    | DESCRIPTION   | PRICE   |
|--|------------|---|---------|
| 1  | VT1-PWD    | Varactor UHF Tuner, Model UES-A56F  | \$24.95 |
| 2  | CB1-PWD    | Printed Circuit Board, Pre-drilled  | 18.95   |
| 3  | 3TP11-PWD  | PCB Potentiometers 4-20K, 1-5K, 2-10K, 2-5K, 1-1K, and 1-50k (11 pieces)  | 8.95    |
| 4  | 4FR-31-PWD | Resistor Kit, 1/4W, 5% 29-pcs. 1/2 W 2-pcs  | 4.95    |
| 5  | 5PT1-PWD   | Power Transformer, PRI-117VAC, SEC-24VAC at 500ma.  | 9.95    |
| 6  | 6PP2-PWD   | Panel Mount Potentiometers and Knobs, 1-1KBT and 1-5KAT with switch   | 5.95    |
| 7  | 7SS17-PWD  | IC's 7-pcs, Diodes 4-pcs, Regulators 2-pcs Transistors 2-pcs, Heat Sinks 2-pcs  | 29.95   |
| 8  | 8CE14-PWD  | Electrolytic Capacitor Kit, 14-pieces   | 6.95    |
| 9  | 9CC20-PWD  | Ceramic Disk Capacitor Kit, 50 WV., 20-pcs  | 7.95    |
| 10   | 10CT5-PWD  | Variable Ceramic Trimmer Capacitor, 5-65pfd, 5-pieces   | 4.95    |
| 11   | 11L5-PWD   | Coil Kit, 18mHs 3-pcs, 22uHs 1-piece (prewound inductors) and 2 T37-12 Ferrite Torroid cores with 6 ft. #26 wire.                       | 6.00    |
| 12   | 12ICS-PWD  | IC Sockets, Tin inlay, 8 pin 4-pcs, 14 pin 1-pc and 16 pin 2-pcs.   | 2.95    |
| 13   | 13SR-PWD   | Enclosure with PM Speaker and Pre-drilled Backpanel for mounting PCB and Ant. Terms   | 14.95   |
| 14   | 14MISC-PWD | Misc. Parts Kit, includes Hardware, (6/32, 8/32 Nuts & Bolts), Hookup Wire, Solder, Ant. Terms DPDT Ant. Switch, Fuse, Fuseholder, etc. | 9.95    |
| 15   | 15MC16-PWD | Mylar Capacitors, 14-pcs and Silver Mica Capacitors 2-pieces  | 7.95    |
| When Ordering All Items, (1-15), Total Price |            |   | 159.95  |

## SIMPLE SIMON ELECTRONIC KITS, Inc.

3871 S. Valley View, Suite 12, Dept. R, Las Vegas, NV 89103

In Nevada Call: **702-871-2892**

**1-800-782-3716**

NEED 6 OR MORE OF AN ITEM? WRITE FOR QUANTITY DISCOUNTS

Available by Mail Order Only  
Send Check\* or Money Order. Minimum Order: \$16.95. Add 10% Shipping and Handling on orders under \$40.00. For orders over \$40.00, add 5%. Minimum Shipping and Handling \$2.00. Cat. \$1.00  
\*VISA and Mastercard Acceptable  
\*Check orders will be held 30 days before shipping

# FAST RELIEF

from

## SOLID STATE HEADACHES

### Model 216



### SEMICONDUCTOR ANALYZER

Easy, automatic, "hands off" operation (Frees both hands for troubleshooting)

Simple to use — no set up — no data books

In, or out of circuit, GOOD-BAD analysis of NPN's, PNP's, FET's, diodes and SCR's

Instant, in or out-of-circuit leakage detection

Digital scanning circuit automatically determines lead configuration

Low-power CMOS design for extended battery life

Uses two standard 9V batteries (not included)

Weighs only 12 ounces — fits in your pocket

High impact thermoplastic case with snap-shut protective cover

**PRICED UNDER \$150**  
THE MODEL 216 IS FAST,  
RUGGED AND AFFORDABLE



THE HICKOK ELECTRICAL INSTRUMENT CO.  
10514 Dupont Avenue • Cleveland, Ohio 44108  
(216) 541-8060 • TWX: 810-421-8286

RADIO-ELECTRONICS

TABLE 2

Inputs switched to output pins

| Input channel                |    | 1A | 2A | 1B | 2B | 1C | 2C | 1D | 2D            |
|------------------------------|----|----|----|----|----|----|----|----|---------------|
| Pin no.                      |    | 2  | 4  | 6  | 8  | 11 | 13 | 17 | 15 12         |
| DC control conditions (pins) | 1  | VL | VL | VL | VL | VH | VH | VL | VL            |
|                              | 3  | VL | VL | VL | VL | VL | VL | VH | VH            |
|                              | 16 | VH | VH | VL | VL | VL | VL | VL | VL            |
|                              | 18 | VL | VL | VH | VH | VL | VL | VL | VL            |
| Output pin                   |    | 10 | 9  | 10 | 9  | 10 | 9  | 10 | 9             |
|                              |    |    |    |    |    |    |    |    | 9 & 10 (MUTE) |
| Output channel               |    | 1  | 2  | 1  | 2  | 1  | 2  | 1  | 2             |

Low switching-level: VL < 0.8 volts

High switching-level: VH > 2.0 volts

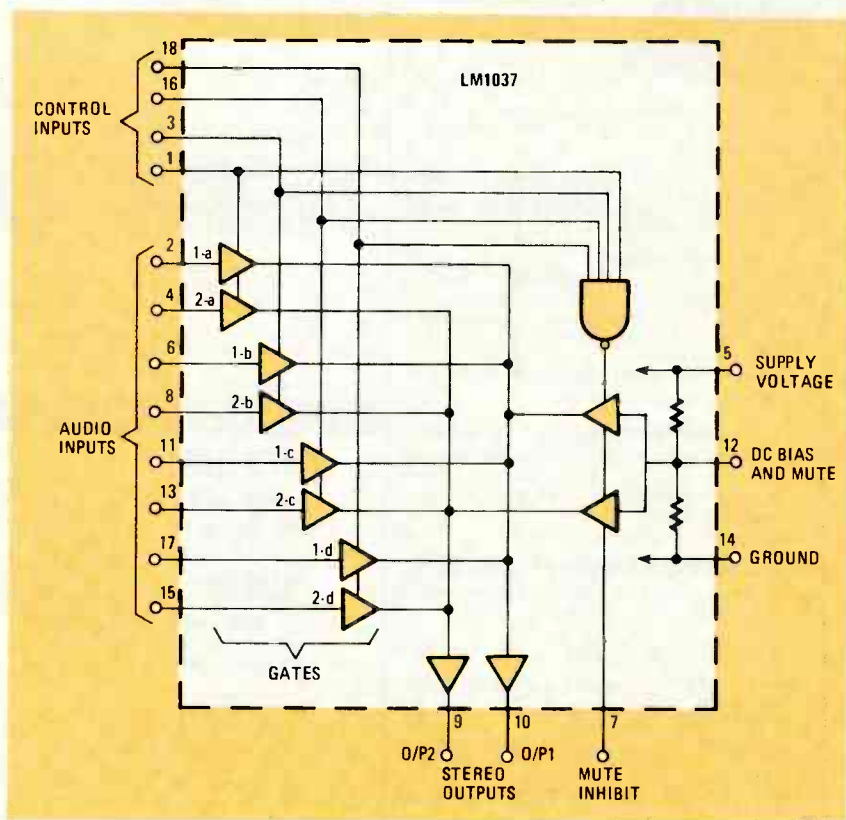


FIG. 2

require external capacitors to operate, and is capable of performing a variety of functions. It is ideal for signal processing, telecommunications, modems, instrumentation, and audio equipment. The center frequencies of all previously available active filters are adjusted with external resistors and/or capacitors. The MF10 filter is unique in that the center frequencies of its various second-order functions are directly proportional to an external clock frequency and fixed at an accuracy of 0.6%, or directly proportional to both the clock frequency and external resistor ratios. Gain and selectivity (Q) are adjusted using external resistors.

The clock and three or four resistors are the only external components necessary to operate the MF10 so the device is less sensitive to external component variations. Frequency stability is directly dependent on the quality of the clock. A single clock can be used to drive an almost infinite number of MF10 filters.

Unlike other available monolithic filters which have been designed for a specific function, the general-purpose MF10 can perform a wide variety of functions including allpass, highpass, bandpass, and notch. Up to fourth-order functions, and any configurations such as Butterworth, Bessel, Cauer, and Chebyshev

*continued on page 90*



Courses in Computers and Programming




Disk Drives and Peripherals



All-in-One Computer



High-Speed Dot Matrix Printer

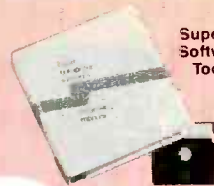

Superior Software Tools



Fully Portable Test Instruments



Hand-held Digital Multimeter



Programmable Automobile Horn



Emergency Power System



Hydraulic Log Splitter



Domestic Solar Water Heater



Space Phone Television



Home Earth Station Receiver

# FREE Heathkit® CATALOG



Educational Self-Study Courses



Pro-Series Audio Components



Digital Marine Depth Sounder



Amateur Radio Gear



Computerized Weather Station

**450 kits and products:** solar hot water systems, satellite TV, all-in-one computers, test instruments, amateur radio gear, self-study courses in computer literacy and state-of-the-art electronics, energy conservation and home security devices, fine stereo components, color televisions, automotive or marine aids, home conveniences and more – things you've always wanted and needed, right now at low kit prices from Heath.

**For people with imagination,** there's nothing to compare with the exclusive thrill of hand-built satisfaction.

**Discover the fun of kitbuilding** – it's a great way to relax in your spare time and share a rewarding pastime with your whole family. The great kits you build will reflect the pride of your craftsmanship, too. The famous Heathkit illustrated manuals make it easy for *anyone* to build reliable, professional-quality kits.

### SEND FOR FREE CATALOG

Our 104-page catalog is Free! If coupon is missing write: Heath Company, Dept. 020-932, Benton Harbor, MI 49022

**Heathkit** Heath Company, Dept. 020-932  
Benton Harbor, MI 49022

Send me the latest free Heathkit Catalog now. I want to "build in" the quality difference.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_


CL-727-Rf \_\_\_\_\_ Zip \_\_\_\_\_

**FREE CATALOG**

Heathkit products are also displayed, sold and serviced at 60 Heathkit Electronic Centers\* nationwide. Consult telephone directory white pages for location.  
\*Operated by Veritechnology Electronics Corporation, a wholly owned subsidiary of Zenith Radio Corporation. Some retail prices may be slightly higher.

# BIG PERFORMANCE small PACKAGE

Model 240

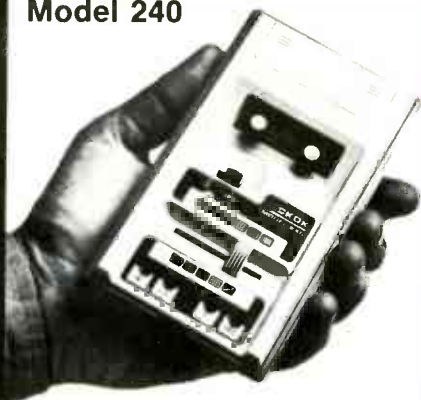

## Video Generator

- Video output for all VCR, CCTV and Monitor Applications  $\uparrow$  1 volt into 75  $\Omega$  load
- RF output: CH 2, 3, 4
- Scope trigger output for V or H sync
- 10 step gray-scale staircase signal for video circuit analysis
- 10 bar and 3 bar gated rainbow pattern
- 8 other dot, bar and line patterns
- Operates from 2 std. 9V batteries or 115VAC
- Single slide switch control
- Complete with test leads, protective cover, AC adapter, comprehensive instruction manual

**PRICED UNDER \$200.**  
**THE 240 DOES SO MUCH FOR SO LITTLE!!**



THE HICKOK ELECTRICAL INSTRUMENT CO.  
10514 Dupont Avenue • Cleveland, Ohio 44108  
(216) 541-8060 • TWX: 810-421-8286

CIRCLE 36 ON FREE INFORMATION CARD

## STATE OF SOLID STATE

continued from page 86

can be had by cascading the two second-order building blocks. The center frequency can be as high as 20 kHz with a Q of 500. Typically, the lowpass and band-pass outputs can sink 0.75 mA and source 3 mA while the notch, allpass, and high-pass outputs sink 1.5 mA and source 3 mA. The devices come in 20-pin DIP packages and cost \$3.50 in lots of 100.—**National Semiconductor**, 2900 Semiconductor Drive, Santa Clara, CA 95051.

### Optocouplers feature back-to-back LED's

Motorola has introduced two new dual-LED Optocouplers designed specifically for AC input applications. The devices—the H1AA1 and H1AA2—consist of two gallium-arsenide (GaAs) infrared-emitting diodes connected in inverse parallel, and optically coupled to a single silicon phototransistor (detector) in the standard 6-pin DIP package.

The Optocouplers can be used to detect the presence, absence, or interruption of AC power and trigger a desired action. A major application is the detection of a ring signal on telephone lines while providing isolation from the ring lines. The H1AA1 and H1AA2 are directly interchangeable with GE devices bearing the same type numbers, while providing for up to 7500 volts. The H1AA1 has a current transfer ratio of 20% and costs \$1.98 in lots of 1 to 99. The H1AA2 has a 10% current transfer ratio and costs \$1.70 in lots of 1 to 99.—**Motorola Semiconductor Products**, P.O. Box 20912, Phoenix, AZ 85036.


### Tunable low-pass sampled-data filters

The MC145414 dual-tunable low-pass filter from the Motorola MOS Integrated Circuits Group is the latest addition to the growing family of CMOS switched-capacitor filters.

The MC145414 has a typical power dissipation of 30 mW when active and 1 mW in the power-down condition. Operating voltage can be obtained either from a single or split power-supply with a voltage range of 10 to 16 volts. It can interface to either TTL or CMOS devices. The device is useful in LPC (Linear Predictive Coding) or CVSD (Continuously Variable Slope Detection) speech applications, modems, or other applications where a precision low-pass filter is needed. Specifications include a dynamic range better than 80 dB, passband ripple less than 0.3 dB, and idle noise typically 100 dBnC0 (Decible RMS noise C-message weighted referenced to zero). The device is offered in a 16-pin DIP plastic or ceramic package and is available for \$4.50 each in lots of 1000.—**Motorola Inc.**, 3501 Ed Bleustein Blvd., Austin, TX 78721.

R-E
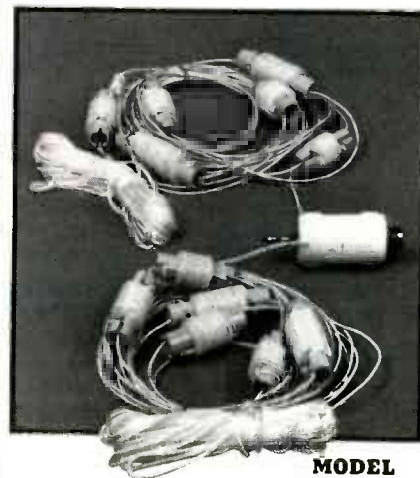
## INTRODUCING THE SWL ANTENNA WITH NEW HIGH EFFICIENCY TRAPS



MODEL ASWJ11-49

- Only 40 feet long
- NEW PATENTED HIGH EFFICIENCY TRAPS
- Automatically tunes the popular 11, 13, 16, 19, 25, 31 and 49 short wave bands.
- Can be installed as a flat top, sloper or inverted V.
- Weatherproof construction for long trouble free service.
- Completely assembled. (Less feed cable.) Center insulator terminated with SO-239 Connector.
- Designed to be fed with RG59 coax for maximum efficiency.

**PRICE \$37.50** plus \$2.00 shipping

**RG59 coax cable available. Terminated with PL-259 connectors on each end.**

| MODEL     | LENGTH  | PRICE PLUS 10% SHIPPING |
|-----------|---------|-------------------------|
| AA-C-5925 | 25 Ft.  | \$ 7.00                 |
| AA-C-5950 | 50 Ft.  | 9.00                    |
| AA-C-5975 | 75 Ft.  | 12.75                   |
| AA-C-5910 | 100 Ft. | 15.50                   |



Quality Communication  
Products Since 1932  
All Made in the USA

**BARKER & WILLIAMSON**  
10 Canal St., Bristol, PA 19007  
**215-788-5581**



At your distributor  
write or call



CIRCLE 34 ON FREE INFORMATION CARD

# A 10 HOUR TAPE RECORDER

WAS \$125.00

**NOW only \$95.00\***

LONG PLAY

Modified Panasonic Slimline high quality AC-DC Recorder provides 5 continuous hrs. of recording & play back of top quality sound on each side of cassette for a total of 10 hrs. Built-in features include:

- Voice level control
- Digital counter, etc.



**PHONE RECORDING ADAPTER**  
 Records calls automatically. All Solid State connects to your telephone jack and tape recorder. Starts recording when phone is lifted.  
**\$24.50\***  
 FCC APPROVED



**VOX VOICE ACTIVATED CONTROL SWITCH**  
 Solid state. Self contained. Adjustable sensitivity. Voices or other sounds automatically activate and control recorder. Uses either remote control or remote mike.  
**\$24.95\***



\*Add for ship. & hdlg. Phone Call Adapter & VOX \$1.50 ea - Recorder \$4.00. Cal. Res. add tax. Mail order, VISA, M/C, cod's ok. Qty. disc. avail. Money back guar. Free data. Dir. inv. AMC SALES, Dept. A, 9335 Lubec St., Box 928, Downey, CA (213) 90241 Phone 869-8519

CIRCLE 50 ON FREE INFORMATION CARD

## STEREO IMAGE EXPANDER

continued from page 65

stereo effect comes primarily from the studio's mixer-board. You can "A/B" the effect with the ON/OFF switch.

The majority of studio recordings are made from a mix of simultaneous "dry" sources and create an artificial image based on intensity differences between channels rather than on time and phase information. Even so, most of them will open up and sound more spacious—the speakers will become "transparent." Some recordings will do fascinating—and frequently spectacular—things when turned loose by the expander. Try any of Pink Floyd's or Tomita's releases to really put the expander through its paces.

### Background reading

The first mention of loudspeaker crosscoupling and its effects appeared in a paper given by B.B. Bauer to the AES in 1961. A detailed exploration of the problem, a solution and test results appear in an article entitled:

"Head related two channel stereophony with loudspeaker reproduction" by P. Damaske, pp. 1109 to 1115 of the *Journal of the Acoustic Society of America*, Vol. 50, No. 4, Part 2, 1972

R-E

## YOUR EXCITING NEW HOBBY!

- Enjoy fantastic savings by assembling your own organ or piano.
- It's easy. No technical knowledge required.
- Just follow our clear, pictured instructions.
- Choose from many models from portables to consoles.
- Ask about our interest-free installment plan.

## WERSI ORGAN & PIANO KITS



For Free Information Pack M40  
 Call Toll Free 800-233-3865  
 in PA 717-299-4327  
 or send coupon below

Free Info Pack:  Organ  Piano  
 Catalog & Demo Record (enclose \$6)

Name \_\_\_\_\_  
 Address \_\_\_\_\_  
 City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_  
 Phone (\_\_\_\_) \_\_\_\_\_

Rep inquiries invited

CIRCLE 51 ON FREE INFORMATION CARD

## FIRST QUALITY COMPONENTS - NOT MAIL ORDER "SECONDS" Min. order \$10.00 - add 5% Shpg and \$1.00 Ins

### ARIES ZERO INSERTION FORCE SOCKETS

cam actuated, true zero insertion - tin plated solder tail pins - capable of being plugged into dip sockets. Inserting wire wrap

| Stock No. | No. Pins | 1-24    | 25-50   |
|-----------|----------|---------|---------|
| 11055     | 24       | \$ 4.35 | \$ 3.90 |
| 11056     | 28       | 4.50    | 4.05    |
| 11057     | 40       | 5.95    | 5.35    |
| 11058     | 64       | 10.50   | 9.45    |

### RESISTOR ASSORTMENT 82508 - 700 pcs (1 each below assortment) \$22.50

Stock No. 82501 10 ea. of 10-12-15-18-22-27-33-39-47-56 OHM \$3.95 each for any assortment

Stock No. 83502 10 ea. of 68-82-100-120-150-180-220-270-330-390 OHM

Stock No. 82503 10 ea. of 470-560-680-820-1K-1.2K-1.5K-1.8K-2K-2.2K-2.7 OHM

Stock No. 82504 10 ea. of 3.3K-3.9K-4.7K-5.6K-6.8K-8.2K-10K-12K-15K-18K OHM

Stock No. 82505 10 ea. of 22K-27K-33K-39K-47K-56K-68K-82K-100K-120K OHM

Stock No. 82506 10 ea. of 150K-180K-220K-270K-330K-390K-470K-560K-680K-820K OHM

Stock No. 82507 10 ea. of IM-1.2M-1.5M-1.8M-2.2M-2.7M-3.3M-3.9M-4.7M-5.6M OHM

### WILD ROVER

Touch switch capsule. Operating motion is .005" without the use of a levered arm. Extremely fast on and off with low resistance. Normally open - rated 115 VAC, 1.6 amp-30 million resistance - 615 radius by 160 thick.

| Stock No. | 1-9    | 10     | 25     |
|-----------|--------|--------|--------|
| 12098     | \$1.28 | \$1.12 | \$1.95 |

### 60/40 ROSIN CORE SOLDER

| Stock No. | Die (feet) | (oz.)  | Price  |
|-----------|------------|--------|--------|
| 50075     | 062        | 9 1.5  | \$3.28 |
| 50076     | 062        | 25 4   | 4.35   |
| 50077     | 062        | 50 8   | 6.02   |
| 50078     | 032        | 33 1.5 | 4.08   |
| 50079     | 032        | 88.5 4 | 5.16   |
| 50080     | 032        | 175 8  | 6.82   |

### T1 WIRE WRAP SOCKETS

Tin plated phosphor bronze contact - 3 wrap

| Stock No. | No. Pins | 1-24    | 25-100  |
|-----------|----------|---------|---------|
| 11301     | 8        | \$ 4.55 | \$ 4.05 |
| 11302     | 14       | 8.66    | 5.54    |
| 11303     | 18       | 7.2     | 6.58    |
| 11304     | 18       | 82      | 73      |
| 11305     | 20       | 1.11    | .99     |
| 11306     | 22       | 1.26    | 1.12    |
| 11307     | 24       | 1.41    | 1.25    |
| 11308     | 28       | 1.71    | 1.52    |
| 11309     | 40       | 2.31    | 2.05    |

### T1 LOW PROFILE SOCKETS

Tin plated phosphor bronze contact pins with gas tight seal

| Stock No. | No. Pins | 1-24    | 25-100  |
|-----------|----------|---------|---------|
| 11201     | 8        | \$ 1.15 | \$ 1.12 |
| 11202     | 14       | 1.18    | 1.15    |
| 11203     | 18       | 21      | 18      |
| 11204     | 18       | 24      | 21      |
| 11205     | 20       | 27      | 24      |
| 11206     | 22       | 30      | 28      |
| 11207     | 24       | 33      | 30      |
| 11208     | 28       | 38      | 34      |
| 11209     | 40       | 53      | 45      |

### ELPAC POWER SUPPLIES - DC/DC CONVERTERS

| SINTEC Stock No. | ELPAC Part No. | Input Voltage (VDC) | Output Voltage (VDC) | Output Current (mA) | Dimensions (HxWxD) in Inches | Price |
|------------------|----------------|---------------------|----------------------|---------------------|------------------------------|-------|
| 13625            | CB3801         | 3-0-7.0             | 12-0-0               | 0-25                | 48x51x3.05                   | 7.95  |
| 13626            | CB3811         | 3-0-7.0             | 12-0-0               | 0-25                | 48x51x3.05                   | 7.95  |
| 13627            | CB3802         | 3-0-7.0             | 15-0-7               | 0-30                | 48x51x3.05                   | 7.95  |
| 13628            | CB3812         | 3-0-7.0             | 15-0-7               | 0-30                | 48x51x3.05                   | 7.95  |
| 13629            | CB3804         | 3-0-7.0             | 28-1-7               | 0-10                | 48x51x3.05                   | 7.95  |
| 13630            | CB3814         | 3-0-7.0             | 28-1-7               | 0-10                | 48x51x3.05                   | 7.95  |

1.5 W TYPE

|       |        |         |        |     |             |       |
|-------|--------|---------|--------|-----|-------------|-------|
| 13631 | CL3801 | 4-0-7.0 | 12-0-0 | 125 | 85x112x1.77 | 59.95 |
| 13632 | CL3811 | 4-0-7.0 | 12-0-0 | 125 | 85x112x1.77 | 59.95 |
| 13633 | CL3802 | 4-0-7.0 | 15-0-7 | 100 | 85x112x1.77 | 59.95 |
| 13634 | CL3812 | 4-0-7.0 | 15-0-7 | 100 | 85x112x1.77 | 59.95 |
| 13635 | CL3804 | 4-0-7.0 | 28-1.4 | 50  | 85x112x1.77 | 59.95 |
| 13636 | CL3814 | 4-0-7.0 | 28-1.4 | 50  | 85x112x1.77 | 59.95 |

13625-1 DATA SHEET FOR DC/DC CONVERTERS 25

### Special of the Month!

### DIGITAL MULTIMETER

Large easy to read 5 1/2 digit display-200 hours operating life with single 9v alkaline battery-low battery & polarity indicators - Five functions (DC Volts, Ohms, DC mA, AC Volts, Diode and transistor junction check in circuit)

Stock No. 82501 **\$54.95**

Stock No. 82502 **\$49.95**

Kit Form, with Instructions

### MODUTEC

Miniclamp AC Volt-Ammeter allows singling one conductor out of many without disarrangement

Stock No. AC Amperes Price  
 13730 0-25A \$39.50  
 13731 0-50A 39.50  
 13732 0-100A 39.50

### ACCESSORY LINE SPLITTER

allows fast readings of AC power consumption of plug in equipment without separation of leads.

Stock No. 13727 **\$9.95**

### POCKET SIZED BATTERY TESTER

for all types of small batteries from 1.35v to 4.5v

Stock No. 13733 **\$13.95**

### VOLT-ICATOR

automotive diagnostic meter plugs into lighter socket and indicates battery condition and charging rates.

Stock No. 13736 **\$12.95**

### AC VOLTAGE TESTER

plugs into any 110v service receptacle to check time voltage over 50-150 VAC

Stock No. 13735 **\$9.95**

### ELPAC POWER SUPPLIES - SOLV SERIES FULLY REGULATED

| SINTEC Stock No. | ELPAC Part No. | Output Voltage | Output Current Rating | Dimensions (HxWxD) in Inches | OVP            | Price   |
|------------------|----------------|----------------|-----------------------|------------------------------|----------------|---------|
| 13802            | SOLV15-5       | 5              | 3.0A                  | 4.7/18x4.2                   | Fixed Included | \$39.95 |
| 13803            | SOLV15-12      | 12             | 1.5A                  | 4.7/18x4.2                   | Fixed Included | 39.95   |
| 13804            | SOLV15-15      | 15             | 1.2A                  | 4.7/18x4.2                   | Fixed included | 39.95   |
| 13806            | SOLV15-24      | 24             | 0.75A                 | 4.7/18x4.2                   | Fixed included | 39.95   |
| 13808            | SOLV30-5       | 5              | 8.0A                  | 5.5/84x7/8x3/16              | OVP-4          | 59.95   |
| 13809            | SOLV30-12      | 12             | 4.0A                  | 5.5/84x7/8x3/16              | OVP-4          | 59.95   |
| 13810            | SOLV30-15      | 15             | 3.3A                  | 5.5/84x7/8x3/16              | OVP-4          | 59.95   |
| 13812            | SOLV30-24      | 24             | 2.0A                  | 5.5/84x7/8x3/16              | OVP-4          | 59.95   |

13802-1 Data Sheet for SOLV Series 25

### PIN FORMING TOOL

puts IC's on their true row to row spacing. One side is for 300 centers. Flip tool over for devices on 600 centers. Put device in tool and squeeze.

ONE TOOL DOES 8 THRU 40 PINS!

Stock No. 11059 **\$12.95**

CRIMPS #10 - #24 wire STRIPS solid #12-22 and stranded #14-24

SCREW CUTTER for 6 most common screw sizes CUTTER and PLIERS

THE PIKE 5 in 1 Tool Stock No. 51005 **\$12.95**

**SINTEC** Drawer Q Milford co. NJ 08848-9990

VISA MasterCard

TOLL 800-526-5960 FREE in NJ (201) 996-4093

Send for Free Catalog over 1100 parts.


CIRCLE 27 ON FREE INFORMATION CARD

# SERVICE CLINIC
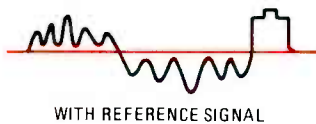
## Color-burst reference oscillators

JACK DARR, SERVICE EDITOR

A TV SET'S COLOR-REFERENCE-oscillator signal, with a frequency of 3.58 MHz (actually 3.579545 MHz), is a very important one. If it isn't present—with a few exceptions that will be noted soon—no color will be seen. Figure 1 shows how the video signal, with and without the reference signal, would appear on a scope. The frequency of the signal must be precise; if the oscillator shifts in frequency by as little as  $\frac{1}{4}$ -Hz, you will see a very obvious tint change. That means that the AFC must be very tight.



Two basic types of circuit are found in older sets, and are still in use in current ones. The older circuit is a crystal-controlled oscillator; the crystal determines the frequency, and an amplifier stage does the rest. The circuit can be made to free-wheel by killing the color sync. Its tuning can be set very near the precise point needed and when the sync is restored, it locks in and stays. Precise control is obtained by comparing the output of the oscillator with the color-burst signal, which is transmitted along with the rest of the TV signal. Many circuits of that type use an AFC circuit almost identical to those used in horizontal-oscillator stages.

The second type of circuit also uses a crystal, but not as the frequency-determining element in an oscillator circuit. In fact, there is no true oscillator. The color-burst signal is fed to a pre-amplifier stage, and then through the crystal, which is actually used as a very-narrow-band filter. The signal from the crystal "filter" is fed to a very-high-gain amplifier stage (often mislabelled a "3.58-MHz oscillator"). It isn't an oscillator; what it does is amplify the burst signal, which makes it "ring" longer. In fact, there is still signal present when the next color-burst signal comes along, so it's clipped and becomes a standard RF-signal, which is fed to the demodulators. The frequency of those circuits isn't controlled. There's no need to, because we're using the color-burst frequency itself as the oscillator signal.

The crystals used in the two circuits are not identical. They oscillate at the same frequency, of course; but apparently they're different cuts (one for use as an oscillator; the other for use as a filter) and neither one will work satisfactorily in the other circuit. (I determined that from experience—and a whole afternoon of work!)

The symptoms of oscillator failure are obvious. The black-and-white picture will be good, but there will be no color at all. If you run into that situation, the first

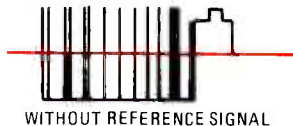


FIG. 1

and best test is to scope the output of the 3.58-MHz circuit, looking for an RF signal of the correct amplitude. Incidentally, you don't really need a wideband scope for that test. If there's a signal present you may see it as a blur, but the *amplitude* of the signal is the important thing; if the level is too low, the demodulators will not work properly.

The first step is to check the active device (tube or transistor) by substitution. If that doesn't bring things back to normal, check all the DC voltages around the stage to make sure that they're normal. As a last resort, try a new crystal, making sure you use the right type! If the crystal fails to work in the "oscillator" circuit, there'll be no feedback. In the filter circuit, you'll see RF on the input side of the crystal but nothing on the output side. In filter circuits, make sure that the color-burst signal is present, too.

In some sets, (mainly the "oscillator" type) sometimes you can see an odd symptom. (I got a letter only this week that complained, "...I've lost the red. The screen is a bluish green but there's no color where it ought to be.") A color-bar signal shows no colors in the bars, but the white spaces between them will be a definite bluish-green. That indicates that the oscillator is dead, but somehow there is enough of the color-burst signal getting through to the demodulators to make the screen glow bluish-green, which is the result of the phase of that signal.

The problem isn't confined to older sets. In one solid-state set, a middle-aged

Philco, the 3.58-MHz oscillator is a small IC op-amp. The original part has a history of failure at odd intervals. The best cure I've found is replacement with a different brand of IC—practically every one of the replacement-transistor/IC makers has a substitute for it.

Loss of the oscillator signal kills the color. If, on the other hand, you lose the color sync, you get fairly bright color showing on the screen, but as "rainbows"—narrow bands of red, green, and blue, slanted exactly like the bars you see when the horizontal oscillator's out of sync. The picture itself, though, will be steady. Start by checking for the color-burst signal; a dead burst-amplifier can be one cause of the problem. For a definite check, run a complete setup procedure on the oscillator. If the oscillator will make colors in the bars at the right places, but they float, the problem is narrowed down to the sync. In a few cases, the crystal can cause that. It'll be *almost* on frequency, but "right on the edge", and the sync won't lock.

Another problem, found mainly in older sets, is good horizontal lock, but very poor color sync. Before running the setup on the oscillator, check the position of the horizontal-hold control. If the color suddenly locks in when you move it toward the center of its range, you've solved the problem.

The reason why the color sync is lost is that if the horizontal oscillator is almost to the fallout point, there will be a small phase-shift in the gating pulse. That's the pulse that "gates out" the color-burst signal from the rest. If the pulse is off frequency, it gets there a little too late or too early and you lose the color-burst signal, and thus the color sync. Always check the horizontal-hold control setting first; it may save you a lot of trouble! R-E

## SERVICE QUESTIONS

### SHORTED CRT

*There's a arcing in the neck of the picture tube in this RCA CTC-58. My tube checker shows a heater-to-cathode short in the green gun (I have an isolation transformer for that kind of test). With the tube socket off, I can read 25 kV on the focus*

*pin of the tube. Please help!—D.W., Taos, NM*

There's a good chance that the CRT is bad. At times you'll find "particle shorts" between grids G3 and G4; G3 is the focus grid and G4 is connected directly to the high-voltage supply. You might try disconnecting the tube socket and HV lead, and discharging a medium-size capacitor (around 20–30  $\mu$ F) across the focus pin and ultor button (charge the capacitor from the B+ supply). If there is a particle short there, that may blow it out. While the spacing between those two electrodes is very small, there shouldn't be any leakage at all there. Also check the focus circuit to see if any of its components have been damaged.

### RESISTOR BURNOUT

*In this Zenith 19HC50, resistor R221 (1½-ohms, ½-watt) in the base return of the horizontal-output transistor, keeps burning up. I replace it, and it's out again in three or four weeks. Last time I used two 3-ohm, ½-watt resistors in parallel to increase the current-handling capacity, but they burned up too. That resistor's very hard to get at; I'd sure like a permanent fix!—D.M., Chicago, IL*

I know what you mean; it's always the hard-to-reach parts that have to be replaced. Now—what makes a resistor burn up? Excess current! In your case, it can't be too much DC or the set wouldn't work at all. The only thing left is pulse-current, and there is a sizable pulse—about 15-volts peak-to-peak—across that resistor.

There's also a 50- $\mu$ F electrolytic capacitor across the resistor to bypass that pulse to ground. If it's open, the pulse could generate enough current to overload the resistor. Replace the 50- $\mu$ F capacitor, and stay with 1-watt resistors to be safe.

### POOR FOCUS

*The focus is poor on this Zenith 19EC45. I replaced the tripler and the HV is now OK, but the focus voltage is only 500 volts. When I disconnect the lead to the picture tube the voltage rises to 4.6 kV, but when I connect it again, the voltage drops back down. Could the focus electrode in the CRT be shorted?—A.G., Binghamton, NY*

It's possible, but not likely. More probably, there's leakage across the arc-gap in the CRT socket. Take it apart and check for carbon paths, etc.

(Feedback: Bingo! A.G. says, "I took the socket apart and found a burnt path from the focus pin to the CRT ground lead, which apparently was shorting the focus voltage to ground. Thanks.")

### ASSORTED HINTS

Problem: Poor vertical size (two or three inches short of filling the screen) in a Toshiba TAC-9330 (Sams 1500-3).

Solution: Check the two-ohm resistor from ground to IC302 (vertical osc/amp/output)—the one I had read about five ohms. That isn't the only possible cause of the problem, but it's easy to overlook unless you're using a digital meter.

Problem: Intermittent but repeated failure of power-supply diodes in a Philco E-21.

Solution: Try replacing the tripler. I did that and the set's worked well ever since. It must be that the tripler was intermittent.

Now for a request. I need a power transformer for a Lectrotech V-7 vector-scope. I wrote to the company, but got no reply; maybe you can help.

*Thanks to A.Y. of Lexington, NC for the hints. To answer your request, call (800) 851-3584 and a nice fellow by the name of John Evans at Thordarson will try to help you out. I'm almost sure they have something that will do the job, since they have quite a few scope power-transformers in their catalog.*

### HORIZONTAL HOLD PROBLEM

*I've got a Magnavox T936 with very poor horizontal hold. I'm not having any luck with it, and could sure use some advice.—C.D., Hightstown, NJ*

Take out the AFC diode unit and check it for balance. Also, check all the resistors and capacitors around the AFC circuit. To make sure that the problem is in the AFC, ground the grid of the AFC tube and see if you can get a floating picture with one straight side. If you can, the oscillator is OK and the cause is due to the AFC section.

(Feedback: "I tried the test and it worked—the AFC diode-unit wasn't balanced. I also checked the resistors and found that a 68K unit that was supposed to drop the voltage to +33-volts was open, even though it looked perfect. A new resistor and new diode unit fixed everything.")

### OPEN CAPACITOR BURNS RESISTOR

I noticed a question here recently about an RCA CTC-31 that was burning up R163. You said it was the plate load for the horizontal oscillator, but I think it's an isolation resistor. It burns up because filter capacitor C118B is open. Therefore the AC from the oscillator must go to ground through C119A, so it also goes through R163 and burns it up.

I've run into the problem in a number of 1967/1968 RCA chassis.

*Thanks to B.W., of Loew's TV in Central City, NE for that information.*

### SPECIAL RESISTOR

This Portland RP-209HN had no sound or video, and only a faint raster. Those sets are made in Korea by the Taihan Corp., and there is no Sam's Photofact for them as yet. However, I was able to get a


## BASIC TRAINING

Learn to write concise, effective programs in BASIC with two great books from Sams.

**BASIC PROGRAMMING PRIMER**, by Mitchell Waite and Michael Pardee, is an excellent, user-friendly guide to BASIC-language programming fundamentals. It's ideal for beginning or advanced computerists, and comes with a handy, tear-out reference card listing condensed BASIC commands.

**BASIC PROGRAMMER'S NOTEBOOK** contains a number of programming secrets and shortcuts usually known only to highly experienced programmers, as well as workable ways to trim both the size and the running time of some of your larger programs. Program statements are in Level II BASIC, but most of the concepts can readily be translated to other BASIC dialects.

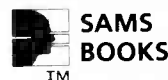Complete your BASIC training with Sams, America's leader in the field of microcomputer knowledge!



Mail to: Howard W. Sams & Co., Inc., 4300 West 62nd St., P.O. Box 7092, Indianapolis, IN 46206

|                             | Quantity  |         |
|-----------------------------|-----------|---------|
| BASIC PROGRAMMING PRIMER    | No. 21586 | \$11.95 |
| BASIC PROGRAMMER'S NOTEBOOK | No. 21841 | \$14.95 |
| Two Volume Set              | No. 22025 | \$22.95 |

ORDER BOTH BOOKS AND SAVE 15%!

Amount of Order \$ \_\_\_\_\_  
Add Handling Costs \$ 2.00

Add Local Sales Tax Where Applicable \$ \_\_\_\_\_  
Total Amount of Order \$ \_\_\_\_\_

Payment Enclosed:  Check  Money Order  
 VISA  MasterCard Interbank No. \_\_\_\_\_

Account No. \_\_\_\_\_  
Expiration Date \_\_\_\_\_

Name (Print) \_\_\_\_\_  
Signature \_\_\_\_\_

Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Call toll free 800-428-3696 for the name of your local Sams Book outlet or to order by phone (give Sams Operator the code number in the box below). Offer good in U.S.A. only. Offer expires 12/31/82. Prices subject to change without notice. AD212

# New Value+Plus™ DMM's

## B&K-PRECISION gives you more value than ever.

B&K-PRECISION's new Value+Plus DMMs give you outstanding performance and price, plus extras you'd expect to pay more for.

The new 2801 and 2805 DMMs are compact 3½-digit instruments, featuring LCD readouts, auto-zeroing, auto-polarity, ten megohm input impedance and full overload protection.

+Plus extras, at no additional cost, include high-energy fusing for added safety, low battery indicator, durable test leads and carrying case. Both offer rugged construction and LSI technology, for long-life reliability.

**Model 2801**  
**\$65.00**



- Ideal for field service
- Very compact—5.4" x 3.4" x 1.4"
- Large 0.4" LCD readout
- 1% typical DC accuracy

**Model 2805**  
**\$100.00**



- 200 mV to 1,000 V ac/dc voltage ranges
- 200 µA to 10 A ac/dc current ranges
- 0.8% typical dc accuracy
- Measures resistance to 20 MΩ

Value+Plus DMMs are available for immediate delivery at your local B&K-PRECISION distributor. For additional information or the name of your local distributor call

**1-800-621-4627**

**BK PRECISION** DYNASCAN CORPORATION

6460 West Cortland Street  
Chicago, Illinois 60635 • 312/889-9087

Int'l. Sis., 6460 W. Cortland St., Chicago, IL 60635  
Canadian Sales: Atlas Electronics, Ontario

service manual from the U.S. office of the manufacturer; that address is Taihan (America) Corp., 8960 Lurline Ave., Chatsworth, CA 91311. Once that problem was solved, however, I ran into a new one. Turns out that the cause of the problem was R905, one of the critical "safety" parts. That being the case, I decided to order one from the company. That was until I found out that it could take up to six months to get one. Instead I used a 62-ohm Sylvania Flameproof resistor and it seems to work perfectly. By the way, there is a mistake on the parts list concerning that resistor—they list it as R05 instead of R905.—*M.B. Danish, Aberdeen Proving Ground, MD*

### VERTICAL PROBLEM

*I had no vertical sweep on this RCA CTC-71. Tried changing C120, a 470-µF capacitor. The raster came back and I thought that all was well. Not long after, however, the set came back with the same problem. I've been told that this capacitor has a high failure rate, but I'd like your opinion—R.C., Philadelphia, PA*

Considering that two of those failed in a short period of time, I'd try using a replacement with a higher working voltage. Many times if a part fails repeatedly it's due to the original rating being a bit too low.

(Feedback: That was it—used a higher working voltage as you recommended and it appears to have solved the problem for good. Thanks!)

### FINDING INTERMITTENTS

I've recently come across a new method for finding intermittents. I've used it with good success and I'd like to share it with you. I use an electric engraving-pencil—the type used for engraving names on personal belongings—as a "vibration tool." Just put a six-inch piece of rubber or plastic tubing on the end of it, set the pencil for its lowest speed, and hold it against the piece of equipment you are working on. That will dig out intermittent solder joints, etc. quite quickly. In case you are worried that this method could damage your gear, NASA uses a "shaker table" to test out its equipment and this tool is not nearly as rough.—*R.E. Grist, Bayside, CA*

### WEAK VERTICAL SYNC

*I can stop the vertical roll on this RCA CTC-66 using the vertical-hold control, but the slightest disturbance causes the picture to begin rolling again—any ideas?—S.C., Mentone, CA*

The symptoms you're describing indicate that the problem is weak vertical sync. Check the sync separator and all the DC voltages, etc. Sometimes that is caused also by leaky shunt capacitors in the vertical integrators.

(Feedback: The sync separator, Q503, showed leakage. Replaced it with an RCA SK-3024 everything's fine.) R - E

**64K** For Sinclair  
**ZX81**  
**\$179.95**



### Memotech 64K Memopak

The Memopak is a 64K RAM pack which extends the memory of the ZX81 by a further 56K. Designed to be in the price range expected by Sinclair owners. Plugs directly into the back of the ZX81 and does not inhibit the use of the printer or other add-on boards. There is no need for additional power supply or cables. The Memopak together with the ZX81 gives a full 64K, which is neither switched nor paged, and is directly addressable. The unit is user transparent, and accepts such basic commands such as 10DIM A(9000). With the Memopak extension the ZX81 is transformed into a powerful computer, suitable for business, leisure and educational use, at a fraction of the cost of comparable systems.

## GLADSTONE

Electronics, 901 Fuhrmann Blvd., Buffalo, NY 14203.  
Call (716) 849-0735 to order. Have your VISA or MASTERCARD ready. \$3.00 shipping and handling.

In Canada, call (416) 787-1448.  
Mail orders send check or money order. Sorry no CODs. Circle reader service card for Sinclair software catalogue.

CIRCLE 54 ON FREE INFORMATION CARD

## Audio Modules



### MOSFET Power Amplifiers

\*BUILT-IN HEATSINKS \*ONLY 5 CONNECTIONS REQUIRED \* 5 YEAR WARRANTY

Choose ILP MOSFET power amps when you need the utmost in performance without spending big money. They provide the fastest possible slew rate, low distortion at high frequencies, + better thermal stability. MOSFET power amps work with complex loads without difficulty and without crossover distortion. Three models are available, with integral heatsink to mount on your own chassis (optional rack mount cabinet available). Connection is simple — via 5 pins. MOSFETs can be combined with other ILP modules to create almost any audio system, whatever your age or experience. Ultra-fi specifications. Slew rate 20V/us. Rise time 3 us. SIN ratio 100 db. Frequency response (-3 db) 15 Hz - 100 kHz. THD (Typical at 1kHz) < 0.005%. IMD (50Hz/7kHz 4:1) < 0.005%.

|                                   |          |
|-----------------------------------|----------|
| MOS120 60W/4-8Ω (requires ± 45V)  | \$79.95  |
| MOS200 120W/4-8Ω (requires ± 55V) | \$129.95 |
| MOS400 240W/4Ω (requires ± 55V)   | \$199.95 |

WRITE FOR FREE CATALOGUE LISTING.  
\*BIPOLAR POWER AMPLIFIERS \*HI-FI PREAMPS  
\*MIXERS \*POWER SUPPLY UNITS \*CABINETS  
\*GUITAR PREAMP and more

## GLADSTONE

Electronics 901 Fuhrmann Blvd., Buffalo, NY, 14203

CALL (716) 849-0735 to order. Have your VISA or MasterCard ready. Dealer/OEM enquiries (416) 787-1488. In Canada: Gladstone Electronics, Toronto.

CIRCLE 53 ON FREE INFORMATION CARD



# NEW PRODUCTS

For more details use free information card inside back cover.

**CURVE TRACER**, the model 501A, is designed to work in association with an oscilloscope to display characteristic curves for a wide variety of discrete semiconductor devices. It displays the unique characteristic



CIRCLE 151 ON FREE INFORMATION CARD

curves for each type of semiconductor device. By examining those curves, the user can determine all significant operating characteristics of the device under test.

Test parameters measured include gain (beta), cutoff current, leakage current, output admittance, and breakdown voltage. The instrument can be used to evaluate bipolar and FET transistors, diodes, SCR's, diacs, triacs, and other devices.

The model 501A is priced at \$300.00.—**B&K PRECISION**, Dynascan Corporation, 6460 West Cortland Avenue, Chicago, IL 60635.

**SCANNER CONVERTER**, the Scanverter CVR-1, allows complete coverage of the 225-400 MHz military/federal-government aircraft band when used with a standard aircraft-band scanner. Listeners can hear NASA space-shuttle radio links to Earth, military air-tactical war games, Coast Guard search and rescue missions, FLEETSATCOM military



CIRCLE 152 ON FREE INFORMATION CARD

satellites, Federal government agencies' in-flight communications, and more.


An exclusive development called "bandstacking" allows the entire 175 MHz-wide UHF aircraft band to be compressed into the 118-136 MHz range tunable on any scanner capable of standard aircraft recep-

*continued on page 100*

## 2300 MHz VARIABLE DOWNCONVERTER

### ANTENNA KIT


\$16.95

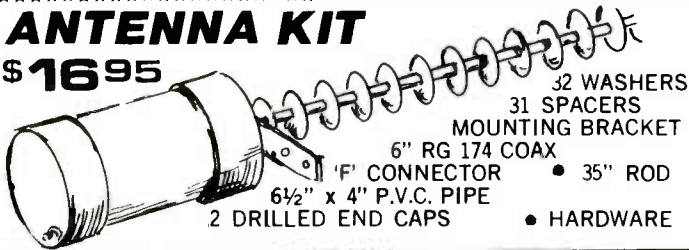

- 32 WASHERS
- 31 SPACERS
- MOUNTING BRACKET
- 6" RG 174 COAX
- 'F' CONNECTOR
- 6 1/2" x 4" P.V.C. PIPE
- 2 DRILLED END CAPS
- 35" ROD
- HARDWARE

### POWER SUPPLY KIT

\$16.95

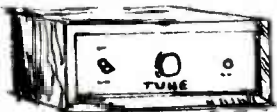

- POWER TRANSFORMER
- COURSE TUNE POT.
- FINE TUNE POT.
- 3 'F' CONNECTORS
- RESISTORS & CAPS
- LED WITH HOLDER
- TERMINAL STRIP

- P.C. BOARD
- RF CHOKE
- KNOB
- WIRE
- 2 SWITCHES
- 4 DIODES
- LM 317 REG.

**WOOD GRAIN CABINET WITH SILK SCREENED front and back \$10.95 Extra**  
**BUILT POWER SUPPLY \$34.95**

Complete Down Converter System  
 INCLUDES  
 ANTENNA KIT  
 POWER SUPPLY KIT  
 CONVERTER KIT  
**SPECIAL \$49.95**

**QUANTITY DISCOUNTS**  
 Any Price in Adv.

|           |         |
|-----------|---------|
| 10 pcs.   | 12% off |
| 25 pcs.   | 18% off |
| 50 pcs.   | 25% off |
| 100 pcs.  | 30% off |
| 1000 pcs. | 35% off |


No Mixing for Quantity Discount

### PARTS

- Converter P.C. Board Plated through holes for stability.....\$4.95
- Power Supply
- P.C. Board .....2.95
- MRF 901 .....2.00
- NEO2135 .....4.95
- 2835 Diodes ..... .95
- .001 Chip Caps. .... 10/3.95
- Choke Set of 4.....1.95
- LM 317 Regulator 1.25
- 'F' Connectors
- Chassis ..... .50
- Wall Transformer
- 12 VAC 700 MA...4.95
- 'U' Bolt ..... .95
- BALUN
- 75 to 300 ohm.....1.95
- BALUN
- for rabbit ears...2.95
- \*RG 59/U COAX
- WITH CONNECTORS
- FACTORY MADE
- 100 Ft. .... \$17.50
- 50 Ft. .... 9.50
- 25 Ft. .... 5.75
- 3 Ft. .... 2.50

### CONVERTER KIT

\$16.95

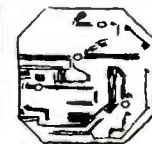

P.C. BOARD PRE-DRILLED SOLDER PLATED WITH PLATED THROUGH HOLES FOR A MORE STABLE PICTURE.

NEW!!

2137 HOT TRANS...

- 3 MRF 901 TRANSISTOR
- 2 HP 2835 Diodes
- 6 .001 Chip Caps.
- 9 Resistors
- 4 Prewound chokes
- 1 Electrolytic Cap.
- 1 Pre Made Probe



**\* WIRED P.C. BOARD TESTED, READY TO CONNECT TO CAN WITH PROBE & CABLE CONNECTOR ATTACHED. \$24.95**

We will tune converter board for \$12.50  
 trouble shoot  
 add .....7.50  
 trouble shoot  
 power supply..\$12.50  
 plus any parts needed.

We will accept collect call for orders only on Visa and Master Card  
 No C.O.D. Orders

To Order Call 1-317-255-7776

Complete Kit Weighs 5 pounds. Please add Sufficient Postage

**6950 NORTH MICHIGAN ROAD  
 INDIANAPOLIS, IN 46268**

# ELECTRONIC RAINBOW

CIRCLE 25 ON FREE INFORMATION CARD

[www.americanradiohistory.com](http://www.americanradiohistory.com)

# EQUIPMENT AND TRAINING NO OTHER SCHOOL CAN MATCH.

**NTS HOME TRAINING INVITES YOU TO EXPLORE MICROCOMPUTERS,  
DIGITAL SYSTEMS AND MORE, WITH STATE-OF-THE-ART EQUIPMENT  
YOU ASSEMBLE AND KEEP.**

Without question, microcomputers are the state of the art in electronics. And NTS is the only home study school that offers you training for this booming field with a choice of 3 production-model micro computers.

We'll explain the principles of troubleshooting and testing your microcomputer and, best of all, we'll show you how to program it to do what you want.

You'll use a digital multimeter, a digital logic probe and other sophisticated testing gear to learn how to localize problems and solve them.

Send for the full color catalog in the electronics area of your choice—discover *all* the advantages of home study with NTS!

NTS also offers courses in Auto Mechanics, Air Conditioning and Home Appliances. Check card for more information.



We believe that training on production-model equipment, rather than home-made learning devices, makes home study more exciting and relevant. That's why you'll find such gear in most of NTS's electronic programs.

For instance, to learn Color TV Servicing you'll build and keep the 25" (diagonal) NTS/HEATH digital color TV.

In Communications Electronics you'll be able to assemble and keep your own NTS/HEATH 2-meter FM transceiver, plus test equipment.

But no matter which program you choose, NTS's Project Method of instruction helps you quickly acquire practical know-how.



Simulated TV Reception

4.

3. The NTS/Heath HN-89A Microcomputer features floppy disk storage, "smart" video terminal, two Z80 microprocessors, with 32K RAM Memory, expandable to 64K on board. 4. The NTS/Heath GR 2001 Digital Color TV (25" diagonal) features specialized AGC-SYNC muting, filtered color and new solid-state high voltage tripler rectifier.

1. The NTS/Rockwell AIM 65 Dedicated Microcomputer A Single board unit featuring on board printer and display—4K RAM (expandable). Application Functions: Central processor—Controller/Monitor—Development System. 2. "The NTS/SYM-1 Microcomputer" 6502 Based CPU—4K bytes ROM (expandable)—1K RAM (expandable). 51 active I/O lines for versatile interfacing: disk drives, ASCII key boards, cassette tape, etc.

## NTS NATIONAL TECHNICAL SCHOOLS

TECHNICAL-TRADE TRAINING SINCE 1905  
Resident and Home-Study Schools  
4000 SO. FIGUEROA ST., LOS ANGELES, CA. 90037



### NATIONAL TECHNICAL SCHOOLS

4000 South Figueroa Street. Dept. 206-092  
Los Angeles, California 90037

Please rush FREE color catalog on course checked below

- |   |   |
|---|---|
| <input type="checkbox"/> MicroComputers/MicroProcessors | <input type="checkbox"/> Auto Mechanics     |
| <input type="checkbox"/> Communications Electronics     | <input type="checkbox"/> Air Conditioning   |
| <input type="checkbox"/> Digital Electronics            | <input type="checkbox"/> Home Appliances    |
| <input type="checkbox"/> Industrial Technology          | <input type="checkbox"/> Color TV Servicing |

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

Apt. \_\_\_\_\_ City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

- Check if interested in G.I. information.  
 Check if interested ONLY in classroom training in Los Angeles.

## NEW PRODUCTS

continued from page 95

tion. No tuning or adjustments are necessary with the fully automatic converter. Reception for hundreds of miles is possible with the use of an outside antenna.

A handy list of active nationwide UHF aircraft channels is included, and the unit comes complete with power cord, interconnect cable, and full instructions.

The *Scanverter CVR-1* is priced at \$99.95, plus \$2.00 shipping.—**Grove Enterprises, Inc.**, Brasstown, NC 28902.

**MINI CARD CAGE**, model *CCK19S*, is a miniature card rack for STD bus microcomputer systems. It occupies only .21 cubic feet,



CIRCLE 153 ON FREE INFORMATION CARD

yet holds up to 10 STD bus cards; it can easily be installed in desk-top consoles, video terminals, printers, controllers, or other equipment with limited space.

The rack accepts either mother boards from Vector and other manufacturers, or card edge connectors with 28/56 .125-inch spaced contacts. It is form-compatible with all 4.48-inch wide by 6.5-inch long STD microcomputer cards. It is shipped disassembled with all hardware and can be assembled quickly. The captive screws in the cage T-struts permit easy locating of the mother board or discrete connectors. The model *CCK19S* is priced at \$39.50.—**Vector Electronic Co., Inc.**, 12460 Gladstone Ave., Sylmar, CA 91342.

**DMM**, model *6502*, features six versatile computing functions not available on similarly priced competitive instruments. A total of 14 pushbuttons, combined with a self-prompting display, provides flexibility in the manipulating and recording of data. Two storage registers allow a display to be scaled by any slope and offset. A single NULL key stores a display as a "zero" value and automatically subtracts that value from all subsequent measurements. Two keys store any entered value as a reference, and display future measurements as a percent deviation from that value. High and low limits can also be stored, and a LIMIT key then allows the display of values within those limits, or HI and LO annunciators if the measured value is outside of the limits. A START key initiates the continuous storage of maximum and minimum values. A MIN key similarly displays the minimum value. A RESET key allows the instrument to return temporar-



CIRCLE 154 ON FREE INFORMATION CARD

ily to the DMM mode without losing any programmed computation.

A FILTER mode activates a binary weighted average of the last four measurement conversions, assuring more accurate and stable readings in the presence of noise. To assure a rapid response to step changes, the filter function is automatically inhibited when successive conversions differ by more than 2% of full scale. All computing functions may be operated singly or chained, if desired, to perform more multiple operations.


The model *6502* is priced at \$758.00.—**Weston Instruments**, 614 Frelinghuysen Avenue, Newark, NJ 07114.

CIRCLE 00 ON FREE INFORMATION CARD

**ANTENNA TUNER**, model *PT-407*, is a general-purpose tuner for 1.8-30 MHz to match antennas fed with coaxial or open-wire lines, single wire, or mobile antennas. The 300-watt power rating makes it suitable for most amateur-radio setups.

The model *PT-407* has a large airwound coil, a large balun for open-wire feed, and has ceramic insulation throughout. It is housed in an 8 x 4 x 7-inch aluminum cabinet with

## THE performers.

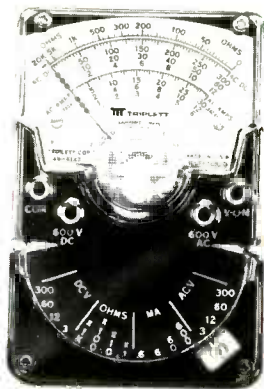

Model 310  
\$70.00


1. Drop-resistant, hand-size V-O-M with high-impact thermoplastic case.
2. 20,000 Ohms per volt DC and 5,000 Ohms per volt AC; diode overload protection with fused Rx1 Ohms range.
3. Single range switch; direct reading AC Amp range to facilitate clamp-on AC Ammeter usage.

Contact your local Triplett Distributor or Factory.  
Phone 419-358-5015, TWX 810-490-2400.

**Triplett performance**  
a tough act to follow

CIRCLE 46 ON FREE INFORMATION CARD

## THE performers.

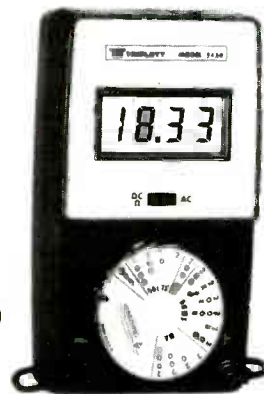

NEW  
Model 3450  
\$150

1. AUDIBLE CONTINUITY TONE plus actual resistance reading with no range change. Hi and Low Power ohms and single range switch.
2. OVERLOAD PROTECTION—Protected up to 1000 volts with special 2A / 250V fuse arrangement; no nuisance fuse blows in volt and ohm ranges.
3. BATTERY LIFE—500 hour typical with 9V battery, display has low battery indication with 8 hours battery life remaining.

Contact your local Triplett Distributor or Factory.  
Phone 419-358-5015, TWX 810-490-2400.

**Triplett performance**  
a tough act to follow

CIRCLE 47 ON FREE INFORMATION CARD

brushed-aluminum control panel and black-vinyl cover. All controls are on the front panel; coaxial connectors are SO-230, and porcelain feedthrough insulators are used for balanced line and single-wire inputs.



CIRCLE 155 ON FREE INFORMATION CARD

The *model PT-407* is priced at \$149.95.—**Palomar Engineers**, PO Box 455, 1924-F W. Mission Road, Escondido, CA 92025.

**MULTITESTER**, *model M110*, has 21 ranges, designed for servicing electronic equipment, gas appliances, heating, air-conditioning, and refrigeration equipment. The ranges are specifically chosen to place most measurements near mid-scale. For example: mid-scale on the low-ohm range, 5 ohms, facilitates testing motor windings, relay, and contactor coils.



CIRCLE 156 ON FREE INFORMATION CARD


The *model M110* features a fuse-protected OHM circuit, mirrored scale-diode-protected movements, and easy-to-read three-color-coded scale plate and front panel. Accuracy specifications for the *model M110* are: DC,  $\pm 3\%$  full-scale; resistance,  $\pm 3\%$  of scale length; AC,  $\pm 4\%$  full-scale. Input impedance is 30,000 ohms-per-volt DC; 15,000 ohms-per-volt AC.

The *model M110* is supplied with carrying case, test leads, batteries, and instructions, and is covered by a one-year warranty; the suggested retail price is \$44.95.—**Universal Enterprises**, 14270 N.W. Science Park Drive, Suite 101, Portland, Oregon 97229.

**DIGITAL THERMOMETER**, *model 871*, is an improved second-generation instrument that offers the versatility and performance of

laboratory-bench thermometers. It is designed for situations in which temperature is a critical concern, particularly in electronics design and manufacturing. The *model 871*'s dual-channel capacity is practical and convenient, allowing the user to monitor inlet/outlet temperatures, do wet-bulb/dry-bulb measurements, and check other situations where temperature differential is important.

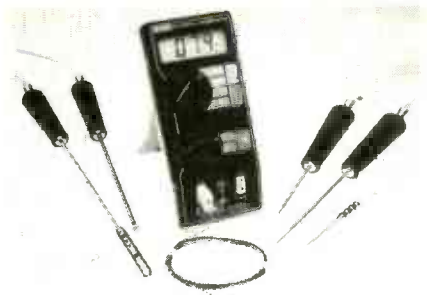The *model 871* is supplied with a three-foot, beaded-junction sensor, so that the user may begin taking measurements at once; it is the only thermometer sold with a sensor. A broad selection of optional probes is available, and includes immersion, penetration, surface, air/gas, and hypodermic types to handle any application; custom and special-purpose probes may also be obtained.



CIRCLE 157 ON FREE INFORMATION CARD

The *model 871* is priced at \$225.00.—**Keithley Instruments, Inc.**, 28775 Aurora Road, Cleveland, OH 44139. R-E

# Take a good look at VACO.



THE SUPER CASE  
70260

The world famous Super Case. Complete with 48 of the most popular and professional problem-solving tools. From screwdrivers and nutdrivers to pliers, wrenches, crimping tools and more. A super variety and super value. All unconditionally warranted from Vaco, of course. The Super Case and all the other fine Vaco tools can be seen in our new 1982 catalog. It's free, just write. Say you want to take a good look at VACO.

Vaco Products Company, 1510 Skokie Blvd.  
Northbrook, IL 60062 U.S.A.

**VACO**

CIRCLE 29 ON FREE INFORMATION CARD

# ANALOG DESIGN

continued from page 62

veloped across  $R_G$  from that developed across  $R_S$ . If it is desirable to make  $R_S$  very large, all you need do to compensate for the voltage,  $V_{RS}$ , that is developed across it, is to either increase  $R_G$  or reduce  $R_X$ . The larger voltage now developed across  $R_G$ , subtracted from the increased voltage developed across  $R_S$  due to its increased value, establishes a reasonable negative bias voltage.

Before calculating the values of  $R_X$  and  $R_G$ , we should know what values of  $I_D$  and  $R_S$  are desirable. That can readily be done by averaging values that are found on the JFET's specification sheet.

First determine the average pinch-off voltage,  $\overline{V_P}$ . It is midway between the maximum and minimum pinch-off voltages specified for the device.

In a similar fashion, calculate the average  $I_{DSS}$ ,  $\overline{I_{DSS}}$ , the drain current when  $V_{GS} = 0$ .

Finally, choose a reasonable value for an average gate-to-source bias voltage,  $\overline{V_{GS}}$ . It frequently is equal to about  $0.4 \times \overline{V_P}$ .

All those factors are then substituted into the following equation to determine the average quiescent drain current,  $\overline{I_D}$ :

$$\overline{I_D} = \overline{I_{DSS}} \left( 1 - \frac{|\overline{V_{GS}}|}{|\overline{V_P}|} \right) \quad (17)$$

Absolute values of  $\overline{V_{GS}}$  and  $\overline{V_P}$  are used so that polarities can be ignored.

Now that we have determined  $\overline{I_D}$ , we can turn our attention to establishing a relationship between  $R_S$  and  $V_G$ , the voltage between the gate and ground. It is:

$$V_G = \overline{I_D} R_S - \overline{V_{GS}} \quad (18)$$

We obviously want to make  $R_S$  as large as possible to improve stability, but there are some limitations. Voltages are developed across  $R_S$  and  $R_D$  due to the presence of  $I_D$ . When  $I_D$  is at its maximum,

the sum of the voltages across  $R_S$  and  $R_D$  should be several volts less than  $V_{DD}$  if the transistor is to operate in the pinch-off region. Hence  $(R_S + R_D)I_D$  must be less than  $V_{DD}$ . The value of  $R_D$  is usually determined by other circuit requirements, so that limits the value of  $R_S$ . Once the maximum value for  $R_S$  has been determined, the value of  $V_G$  is found from:

$$V_G = \left( \frac{R_G}{R_G + R_X} \right) V_{DD} \quad (19)$$

But the values for  $R_G$  and  $R_X$  cannot be selected at random because of the presence of the leakage current,  $I_{GSS}$ . If  $\Delta V_{GS}$  is the allowable bias voltage variation in the design,  $\Delta I_D$  is the allowable drain

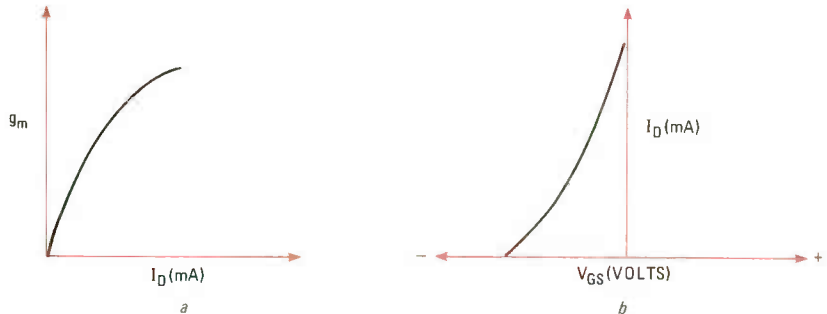


FIG. 9—THESE CURVES are extremely useful when designing MOSFET bias circuits. The curves for the device you are designing for can be found on that device's specification sheet.

## OMNITRON: The Source for Quality at Low Cost

Silicon  
H.V. Triplers  
**HIGH VOLTAGE  
MULTIPLIERS**



### SYLVANIA Triplers

**ECG-500A**  
212-139  
212-139-01  
212-139-02  
**\$12<sup>95</sup> ea.**



**ECG-523**  
212-141  
212-141-01  
**\$15<sup>00</sup> ea.**

**ECG-526A**  
212-141-02  
212-141-03  
212-141-04  
**\$16<sup>99</sup> ea.**

**REMEMBER!**  
Sylvania  
Tubes  
70% + 10%  
OFF  
LIST

**Sylvania ECG  
Replacement  
Semiconductors  
and Components**  
Full line in stock.  
The best quality  
semiconductor.

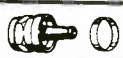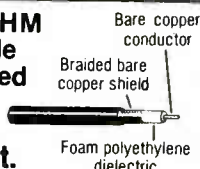**RG-59/U 75 OHM  
Co-Axial Cable  
Copper Braided  
Shield**  
White or Black  
**\$44<sup>50</sup>/1000 ft.**



**F-59 Connector  
with Separate Ferrule  
10¢/100 lot**



**Matching Transformer  
75-300 Ohm  
MT-1 59¢ ea. \$44<sup>00</sup>/100**




**2 Way - 75 Ohm Coupler  
MT-2 \$1<sup>49</sup>ea. \$89<sup>00</sup>/100**



**2 SC1172B  
\$1<sup>99</sup>**

### VERY POPULAR

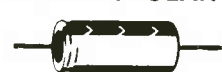

**80 MFD x 450 Volts... .99  
100 MFD x 450 Volts... 1.09**

**SOLDER** (60/40 Rosin Core)  
1 lb. .062 dia.  
(regular size)  
**\$7<sup>99</sup> SOL-1**



**SILICON RECTIFIER 2.5 Amp/1000 PIV  
100/\$9<sup>95</sup> SL-100**

**GLOBAR DISC - 120 Ohms Cold  
107191 RCA 99¢**

**CHEATER CORDS  
Polarized C Clip  
Price: 39¢ 24620**



**Standard C Clip  
Price: 39¢ 24623**



### REPLACEMENT RODS

4 Section LAR-4 69¢  
5 Section LAR-5 89¢  
6 Section LAR-6 99¢  
7 Section LAR-7 99¢

### G.E. OM-300

**\$1<sup>49</sup>**

### PANASONIC OM-500

**\$1<sup>59</sup>**

**SOLDER WICK 99¢**  
Solder Removal SW-5  
1/4" Wide (Thick Type)-5 feet



**10 ASSORTED CIRCUIT BREAKERS  
10/\$7<sup>99</sup> Good Assortment  
CB-10**



# OMNITRON

**ELECTRONICS**  
770 Amsterdam Ave., New York, NY 10025

► Also ask for Free 100 Page Catalog ◀

Send Purchase Order, Check or Money Order  
**or Call Toll Free 800-223-0826**

in NY STATE (212) 865-5580

All ORDERS SHIPPED UPS/COD F.O.B., N.Y.C.

MASTER CARD • VISA

current variation.  $\Delta I_{GSS}$  is the amount the leakage gate current changes over the operating temperature range, and  $R_S$  is the value of the source resistor, the parallel equivalent resistance,  $R_P$ , of  $R_G$  and  $R_X$  can be no larger than:

$$R_P = \frac{R_G R_X}{R_G + R_X} < \frac{\Delta I_D R_S - \Delta V_{GS}}{\Delta I_{GSS}} \quad (20)$$

Once you've calculated  $R_P$ , you can find  $R_G$  and  $R_X$  from:

$$R_X = \frac{R_P V_{DD}}{V_{GS}} \quad (21)$$

$$R_G = \frac{R_P V_{DD}}{V_{DD} - V_{GS}} \quad (22)$$

Substituting that information into equation 19, we can determine  $V_G$ .

### Biasing MOSFET's

MOSFET gates are insulated from their substrates and channels. Because of that, the leakage current is much lower than the  $I_{GSS}$  of a JFET. Furthermore, this leakage current remains constant regardless of the MOSFET's temperature.

Leakage current was a very important factor in bipolar device designs because it affected the output current. Collector current increased rapidly with leakage current and temperature causing the temperature and current to keep rising until the transistor, in many instances, destroyed itself. As for the MOSFET, that is not a problem because the output current here actually drops as the temperature of the transistor rises.

As for bias voltage, no gate current other than leakage current flows regardless of the gate's polarity with respect to the source. Despite that, n-channel enhancement/depletion-type MOSFET's are usually biased so that the gate is negative with respect to the source. But they could, if desired, be biased so that the gate is positive with respect to the source. Enhancement-type devices, however, MUST be biased so that the gate is positive with respect to the source.

The circuits we used to bias the JFET, shown in Fig. 8, can also be used for biasing MOSFET's. There is one additional consideration, however. Some MOSFET's have a lead from the substrate. If that should be the case connect that lead to the source of the transistor.

Two curves, a plot of  $g_m$  vs.  $I_D$  and a plot of  $I_D$  vs.  $V_{GS}$ , are useful when designing MOSFET bias circuits; a typical example of each of those is shown in Fig. 9-a and Fig. 9-b, respectively. Be aware that those curves will, of course, vary greatly among different types of MOSFET's; the curves for the specific device you are working with will be found on the device's specification sheet.

For a specific  $V_{DS}$ , calculating the values for the circuit shown in Fig. 8-a is relatively easy if you follow these steps.

1. Determine the  $g_m$  required for the circuit being designed.

2. Extend a line from that point on the vertical ( $g_m$ ) axis of the plot of  $g_m$  vs.  $I_D$  found in the device's specification sheet to the curve itself. Drop a vertical line from the intersection point to the  $I_D$  axis. Where that line crosses the  $I_D$  axis is the desired value of  $I_D$ .

3. Following a procedure similar to the one in the last step, use the value of  $I_D$  to find the desired value of  $V_{GS}$  from the plot of  $I_D$  vs.  $V_{GS}$  found in the device's

specification sheet. Once that is done, the values of  $I_D$ ,  $V_{GS}$ , and  $V_{DS}$  are known.

4. Calculate  $R_S$ . For the circuit shown in Fig. 8-a, it is equal to  $V_{GS}/I_D$ .

5. As the voltage across  $R_D$  must be equal to  $I_D R_D$ ,  $V_{DD}$  must be equal to  $I_D R_D + V_{DS}$ .

The design procedure is somewhat more complex when working on the bias network for the circuit shown in Fig. 8-b. Here, the bias voltage is the sum of the voltage across  $R_S$ , as just determined, and the voltage across  $R_G$ . If the voltage across  $R_G$  is to be positive with respect to ground, the voltage across the resistor can

*continued on page 110*



## CAMBRIDGE LEARNING Inc.

# A PRACTICAL DIGITAL ELECTRONICS KIT FOR LESS THAN \$40 ! Suitable for Beginners

Learn the wonders of digital electronics and see how quickly you are designing your own circuits. The kit contains:

Seven LS TTL integrated circuits, breadboard, LED's, and all the DIL switches, resistors, capacitors and other components to build interesting digital circuits; plus a very clear and thoroughly tested instruction manual (also available separately). All this comes in a pocket size plastic wallet for only \$39.95. This course is for true beginners:

- Needs no soldering iron.
- Asks plenty of questions, but never leaves you stuck for an answer.
- Teaches you about fault-finding improvisation and sub-system checking.
- The only extra you need is a 4.5 volt battery or a stabilized 5 volt supply.

Using the same breadboard you may construct literally millions of different circuits.

This course teaches Boolean logic, gating, R-S and J-K flipflops, shift registers, ripple counters and half adders.

Look out for our supplementary kits which will demonstrate advanced arithmetic circuits, opto-electronics, 7-segment displays etc.

### NO RISK GUARANTEE

There's absolutely no risk to you. If you're not completely satisfied with your Courses, simply return them in good condition to CLI within 30 days. We'll send you a full refund.

### AIR MAIL

The prices shown include surface mail postage anywhere in the World. For Air-Mail shipment please write for additional cost, specifying Courses you will order.

### CAMBRIDGE LEARNING Inc.

1 Judith Drive  
North Reading,  
MA 01864

(617) 664-3657

- Order free by phone
- Mastercard / VISA
- No shipping charges.
- Money-back guarantee
- Tax deductible

### ALSO AVAILABLE

We also have available 2 written Courses to complement SUPERKIT - Digital Computer Logic & Electronics and Design of Digital Systems.

-Digital Computer Logic & Electronics is designed as an introduction to digital electronics and is written at a pace that suits the raw beginner. No mathematical knowledge is assumed other than simple arithmetic and no electronic knowledge is expected at all. .... **\$14.95**

-Design of Digital Systems is written in the same question and answer style as Digital Computer Logic & Electronics but moves at a much faster pace and goes into the subject in far greater depth. Ideally suited to scientists or engineers who want to know more about digital electronics ..... **\$19.95**

### PHONE ORDERS - FREE

To order by phone, call (617) 664-3657 with your credit card information. It won't cost you a dime, because we'll deduct the cost of the call from the price of the Courses you order.

### TO ORDER BY MAIL

You may use the order form below if you wish, but you don't need to. Just sent your check or money order (payable to Cambridge Learning Inc.) to the address below. If you don't use the order form make sure you enclose your address and you specify which Courses you are ordering.

Mass. Residents and 5% sales tax. We pay all surface shipping costs.

Company Purchase Orders also accepted.


TO: Cambridge Learning Inc., 1 Judith Drive, North Reading, MA 01864

Please send me

SUPERKITS ..... \$39.95 \$ \_\_\_\_\_  
 sets of Design of Digital Systems ..... \$19.95 \$ \_\_\_\_\_  
 sets of Digital Computer Logic & Electronics ..... \$14.95 \$ \_\_\_\_\_

Enclosed is check/money order for total \$ \_\_\_\_\_  
 (payable to Cambridge Learning Inc.) Mass. Residents add 5% Sales Tax.

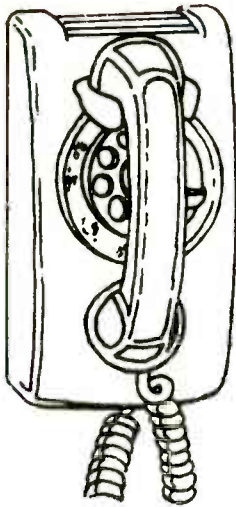
NAME .....  
 ADDRESS .....  
 CITY / STATE / ZIP .....



**CALL NOW  
AND  
RESERVE  
YOUR SPACE**

- 6 × rate \$550 per each insertion.
- Reaches 220,500 readers
- Fast reader service cycle
- Short lead time for the placement of ads.
- We typeset and layout the ad at no additional charge.

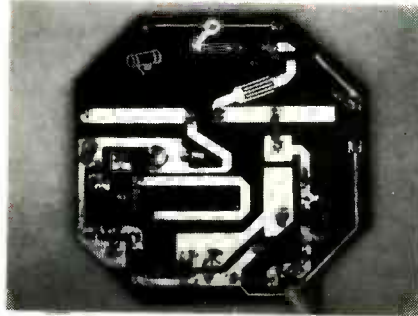
Call 212-777-6400 to reserve space. Ask for Arline Fishman. Limited number of pages available. Mail materials to: mini-ADS, RADIO-ELECTRONICS, 200 Park Ave. South, New York, NY 10003.




**2300 MHz DOWNCONVERTER kit** for Amateur microwave reception. \$37.95 postpaid. Includes NE 64535 high-performance RF stages and highest quality components for superior performance. Send SASE for information filled catalog of other converter kits, preamps, accessories and parts. VISA and MASTERCARD accepted. **SMP - Superior Microwave Products, Inc.** PO Box 1241 Vienna, VA 22180 1-800-368-3028 1-703-255-2918 **CIRCLE 62 ON FREE INFORMATION CARD**



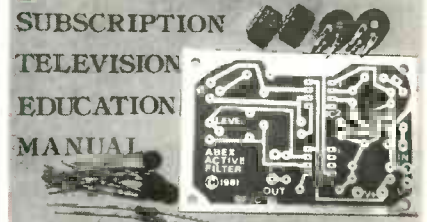**LPI-60**, New, simple to operate **Logic Pulse Injector**. Tests digital IC's—TTL, CMOS, etc. Generates six kinds of pulse modes, two each in single pulse (0.5μs/5μs), pulse train (10HZ/100HZ), and pulse burst (10/100 pulses). **LPI-60 \$54.95 plus \$3.45 shipping & handling.** CHK, M/O. VISA & M/C (Calif add tax). Send for free catalogue of other products.—**MASCO ELECTRONICS P.O. BOX 45922, Los Angeles, Calif 90045.** **CIRCLE 63 ON FREE INFORMATION CARD**



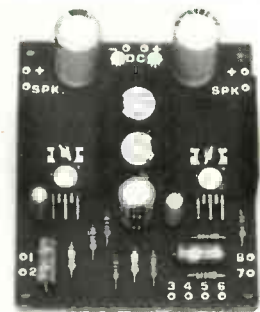**SUBSCRIPTION TELEVISION EDUCATION MANUAL** includes detailed schematics, theory, and practices: \$14.95. **MICROWAVE TELEVISION EDUCATION MANUAL:** \$16.25. Both manuals only \$26.95. **15.7 KHz SINE WAVE ACTIVE FILTER KIT** includes parts and instructions: \$22.70. **INFORMATIVE CATALOG** on all VIDEO PRODUCTS, KITS, and MANUALS: \$2.00 (Refundable). Visa and MasterCard accepted. Add 5% shipping and handling.—**ABEX, P.O. Box 26601-RS, San Francisco, CA 94126.** **CIRCLE 65 ON FREE INFORMATION CARD**



**THE MS-15 Power Amplifier** can be wired for either monoral or stereo. When hooked up to a Walkman AM-FM radio or any similar type of radio it will become a power-full Hi fidelity music system for the home, auto, van, or boat. It also makes a great P.A. system for schools, church or for out door use. \$19.50 check or money order. Satisfaction guaranteed.—**SPECTRUM PRODUCTS, P.O. BOX 8011, FOUNTAIN VALLEY, CALIF. 92708.** **CIRCLE 59 ON FREE INFORMATION CARD**

## EQUIPMENT REPORTS

*continued from page 34*

The **DR44-6** has a suggested retail price of \$2125.00.

### **DP4044 preselector**

Enclosed in a matching 19-inch rack-panel metal enclosure, the **DP4044** Pre-selector features two-stage tuning accomplished by a concentric-control variable capacitor (dual section, 365-pF-per-section).

All RF coils are fully shielded. A 4-gang rotary switch selects the reactive components for each band within the 0- to 30-MHz range of the unit.

Both the input and output impedances of the **DP4044** are 50 ohms. The **DP4044** is not designed to match other impedances and may display insertion loss if the line impedance deviates from the nominal value.

We measured the insertion loss of the unit and it followed closely the specified table provided by the manufacturer, averaging 3 to 6 dB throughout the short-wave range. The loss becomes progressively greater at lower frequencies.

The RF selectivity is very sharp, requiring slight peaking every time the receiver is tuned more than a few percent past the peak position. The tuning range is continuous from 150 kHz through 30 MHz; the 0-150 kHz position is an untuned low-pass filter.


We found the **DP4044** to be quite effective in isolating discrete frequencies throughout its tuning range, although attention must be given to proper impedance-matching to avoid insertion losses. Users must remember that this is a preselector and *not* an impedance-matching antenna tuner.

As with all other passive preselectors, the user must not expect an increase in signal strength—only isolation of the frequency of interest. For that application, the **DP4044** works well. The **DP4044** has a suggested retail price of \$235.00.
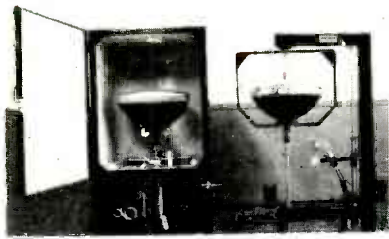
### **The DS111 speaker**

A companion matching speaker is also available; it includes several switch-selectable filtering combinations.






**ONE MAN CRT FACTORY**, easy operation. Process new or rebuild old CRT's for tv's, bus. machines, monitors, scopes, etc. Color, b&w, 20mm, foreign or domestic. 3x6 ft. space required. Profits???. Average CRT rebuilding cost — \$5. Sell for \$100 = \$95 profit; x 5 CRT's = \$475 daily; x 5 days = \$2375 weekly profit. Higher profits outside U.S.A. Investigate this opportunity today. We service the entire world. Write or call:

**CRT Factory, 1909 Louise St., Crystal Lake, Il. 60014, (815) 459-0666.**

**CIRCLE 67 ON FREE INFORMATION CARD**

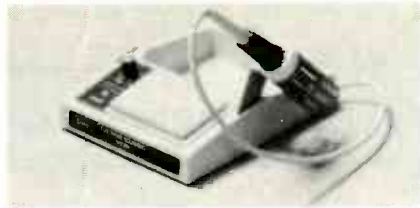

**NEW UNGAR SYSTEM 9100**...gives you a lower cost alternative for many applications requiring operator adjustable temperature control! 0.053 New, THERMO-DURIC 10eater element • Non-magnetic temperature control • Grounded • Interchangeable tips • Operator-adjustable 400°F-800°F Micro-handle, cool operation • U.L. Listed. Suggested Resale **\$91.00**. See your Ungar distributor or contact **Ungar Division of Eldon Industries, Inc., P.O. Box 6005, Compton, CA 90220, (213)774-5950, (800)421-1538.**

**CIRCLE 68 ON FREE INFORMATION CARD**

# STOP COPY GUARD


Make professional quality duplicates of your favorite (VHS, BETA) tapes with this **state-of-the-art** controller. Includes: **stabilizer**: defeats rolling **enhancer**: preserves picture detail at slow speed **RF converter**: simplifies real time viewing **distribution amp**: drive 3 VCR's **easy to build kit** lowest price **\$133.00** 206-693-3834 M/C, **Visa order now save 10%**.—Video Control Inc., 3314 H Street, Vancouver, WA. 98663. USA

**CIRCLE 60 ON FREE INFORMATION CARD**



**DM25 DIGITAL MULTIMETER**, compact 3½-digit multimeter with basic accuracy of ±0.2% of f.s. Measures DC volts, 0.1V to 1,000V; DC current 0.1mA to 200mA; AC volts from 1V to 600V; resistance 1 ohm to 2 megohms. Features overload protection all ranges, fuse-protected current and resistance ranges, automatic zeroing and polarity, over-range and low-battery indication. Complete with test leads and carrying case, **only \$69.95**. **UNIVERSAL ENTERPRISES, INC., -14270 N.W. Science Park Drive, Portland, Oregon 97229, (503) 644-8723, Telex 15-1240 UEIPTLD PTL.**

**CIRCLE 64 ON FREE INFORMATION CARD**

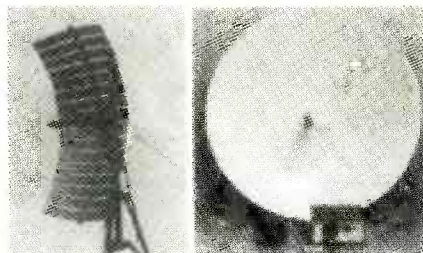

**Amateur Microwave Systems—M-21 System:** (left) 55 db gain, 36" parabolic antenna, microwave downconverter, aluminum die-cast case. **\$179.95** (regular \$199.95). **T-1 System:** (right) over 35 db gain, 22" parabolic antenna, microwave downconverter in probe. **\$129.95** (regular \$144.95) Send for free catalog. Dealer inquiries invited. **SRS, PO Box 50, East Detroit, MI 48021 (313) 791-5551. Visa and Mastercharge accepted.**

**CIRCLE 66 ON FREE INFORMATION CARD**



**Still the best GRAPHIC EQUALIZER kit**  
\* See **Radio-Electronics** 5/78 cover story  
\* 12 bands/channel - \* .02% distortion -  
\* 92dB S/N ratio - \* Solid walnut ends -  
\* Kit only \$100 postpaid via UPS

VISA, M/C add shipping. \$1 handling (303) 667-1662

**Symmetric Sound Systems, 912D Knobcone, Loveland, CO 80537. Free catalog.**  
**CIRCLE 61 ON FREE INFORMATION CARD**

It is housed in a 10½-inch wide × 5-inch high × 6 ½-inch deep black and aluminum cabinet containing a 3 inch × 5 inch oval speaker. The **DS111** audio-processing speaker accessory features two front-panel controls: and on/off switch (switched off, the unit is simply disconnected; no external speaker jack is provided) and a rotary control with positions labeled **LOUDNESS/FLAT/SSB/CW/HI PASS/LO PASS**.

The speaker system is passive, designed around a tapped toroidal inductor that is used in combination with a series of four electrolytic capacitors. Because of the size of the windings on the toroid, very little insertion loss was noted.

In the **LOUDNESS** position, the bass and treble frequencies are passed, while mid-


range frequencies are attenuated. In the **FLAT** position, the internal speaker is connected directly to the audio-input terminals (a pair of spring-loaded push terminals on the rear apron).

The **SSB** position attenuates both bass and treble frequencies while passing the midrange frequencies. In the **CW** position, a narrow midrange (800 Hz) is passed, while bass and treble are rolled off more steeply than the **SSB** position.

The **HI PASS** and **LO PASS** positions provide bass and treble roll-off respectively.

The **DS111** is certainly useful, especially when used with a receiver's selectivity controls, but that is no substitute for good IF selectivity in a receiver. The **DS111** has a suggested retail price of **\$85.00**

**R-E**

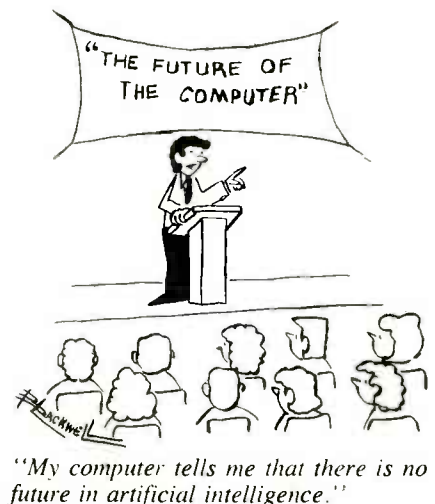

# NEW LIT

For more details use free information card inside back cover.

**COMPUTER BOOKS CATALOG** is 28 pages in color, and is an up-to-date reference guide to all current editions of the wide range of books and software published by SYBEX.

Starting with books of general interest (*Your First Computer*, etc.) such areas as CP/M, Hardware, Pascal, Programs for Scientists and Engineers, 6502, Z80 and Z8000, and word processing are covered.

A special feature of the catalog is a listing of the nine languages that SYBEX books are translated into, and information on how to find foreign-language editions. The catalog is free upon request.—**SYBEX**, 2344 Sixth Street, Berkeley, CA 94710.

**CIRCLE 141 ON FREE INFORMATION CARD**

**DC POWER-SUPPLY CATALOG** is 36 pages and lists more than 250 different power-supply products that cover a range of 10 to 1,000 watts, 3 to 320 volts DC, and current ratings from 35 milliamps to 200 amps. A wide variety of open-frame, covered, and en-

capsulated power supplies used for nearly all electronics and electrical applications, such as microprocessors, computer peripherals, memories, terminals, mini-computers, and communications and general electronics applications. Switchers, linears, and unregulated circuits are also included in the line. The information includes specifications, weights, sizes, photos, dimensions drawings, prices, and electronic/electrical parameters. The catalog is free on request.—**Standard Power, Inc.**, 1400 So. Village Way, PO Box 15547, Santa Ana, CA 92705.

**CIRCLE 142 ON FREE INFORMATION CARD**


**SOLDER CATALOG** is eight pages in color, published by Multicore Solders, and illustrates their complete line of products: wire core solders; soldering fluxes; bar solder; cleaning solvents; special-purpose chemicals; PC-board fabricating materials; desoldering wicks; solder creams; preforms and tapes; solder resists, and Xerxin—the

new cost-effective chemical system that eliminates the need to clean PC boards. Free upon request.—**Multicore Solders**, Cantiague Rock Road, Westbury, NY 11590.

**CIRCLE 143 ON FREE INFORMATION CARD**

**MAIL-ORDER CATALOG** is a fully illustrated, 104-page catalog, with many photographs in color. It offers more than 400 state-of-the-art electronics and mechanical kits for the home, hobby, or business. Products described relate to computers, energy-saving devices, satellite Earth-station technology, amateur radio equipment, hi-fi-stereo components, color TV's, marine and aviation gear, radio-control monitoring, test instruments, tools, video recording, solar power, and many more. In addition, over 30 self-instruction courses in electronics, computers, and programming are offered. The catalog is available, free, from **Heath Company**, Dept. 350-435, Benton Harbor, MI 49022. R-E

**CIRCLE 144 ON FREE INFORMATION CARD**

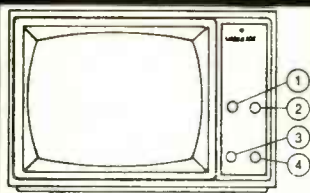

1. CONTRAST  
2. POWER-BRIGHT  
3. V-HOLD  
4. H-HOLD

**VIDEO 100**  
12" Black & White  
MONITOR  
**\$89.50**

by AMDEK

### Fourth Dimension Systems FLOPPY DISK DRIVE FOR APPLE<sup>®</sup> COMP.

The unit features a track zero micro-switch and read/write electronics DOS 3.2.1., DOS 3.3, PASCAL or CP/M.

**\$349.95**

### DISKETTES

5 1/4" BULK "OEM" PACK  
FOR YOUR  
APPLE  
Box of 100 **\$149**

## BROAD BAND MICROWAVE RECEIVER SYSTEM 1.8GHZ to 2.4 GHZ

only  
**\$295.00**

RANGE: Line of sight to 250 miles

SCOPE: Will receive within the frequency band from satellites, primary microwave stations, and repeater microwave booster stations.

CONTENTS: Packaged in 19"x19"x4 1/2" corrugated carton complete with:

- 24" Dish
- Feed-Horn Receiver
- Mounting Bracket
- Mounting Clamp
- Instructions
- 300 Ohm to 75 Ohm Adapter
- 750 Ohm to 300 Ohm Adapter
- 60 Feet Coax Cable with Connectors
- 3 Feet Coax Cable with Connectors

**SUPER BUY!**

16K RAM EXPANSION CARD  
For Your APPLE<sup>®</sup>

LANGUAGE TRANSPARENT  
ALL NINE RAMS INSTALLED!

**\$79.95**



## VISION-80<sup>®</sup> 80x24 Video

Display Card **\$269**

Vista Computer Company's new Vision-80 board is a sophisticated yet easy to use video display card for the Apple<sup>™</sup> computer.

TERMS OF SALE: Cash, checks, credit cards, C.O.D. Calif. residents add 6% sales tax.

"HAVE YOU KISSED YOUR COMPUTER LATELY?"

# Components Express, Inc.

1380 E. Edinger • Santa Ana, Calif. 92705 • 714/558-3972 TWX 910-595-1565

## INTERNATIONAL FM-2400CH FREQUENCY METER FOR MOBILE TRANSMITTERS/RECEIVERS

Portable • Solid State • Rechargeable Batteries

The **FM-2400CH** provides an accurate frequency standard for adjustment of mobile transmitters and receivers at predetermined frequencies.

The FM-2400CH with its extended range covers 25 to 1000 MHz.

The frequencies can be those of the radio frequency channels of operation and/or the intermediate frequencies of the receiver between 5 MHz and 40MHz.

Frequency stability:  $\pm .0005\%$  from  $+50^\circ$  to  $+104^\circ\text{F}$ .

Frequency stability with built-in thermometer and temperature corrected charts:  $\pm .00025\%$  from  $+25^\circ$  to  $+125^\circ$  (.000125% special 450 MHz crystals available).

- Tests Predetermined Frequencies 25 to 1000 MHz
- Pin Diode Attenuator for Full Range Coverage as Signal Generator
- Measures FM Deviation



FM-2400CH (meter only) \$690.49  
 RF crystals (with temp. correction) ..... \$28.89 ea.  
 RF crystals (levs temp. correction) ..... \$21.92 ea.  
 IF crystals ..... catalog price

Write for catalog



INTERNATIONAL CRYSTAL MFG. CO., INC.  
 10 North Lee Oklahoma City, Okla. 73102

CIRCLE 49 ON FREE INFORMATION CARD

## CASSETTE RECORDERS

continued from page 70

### Normal tape movement, no audio

A Sanyo *M1000* cassette recorder ran nicely, but had no audio output. Rotating the volume control back and forth did not generate any sound from the speaker. A 1-kHz signal was injected at the volume control, but there was still no sound. Even when the signal was injected at pin 9 of the audio-amplifier IC nothing happened. An electrolytic coupling-capacitor was soldered to pin 13 of the IC and connected to an external speaker, but there was *still* no output.

Although the voltages at the IC were near normal, the IC was determined to be defective. Another LA4100 power-IC was installed and that solved the no-sound problem.

In summary, troubleshooting portable cassette-recorder/players is no different from working on other cassette players. You may find the components a little more compact and closer together but—then again—you may find fewer components to worry about. In fact, working with portable units can prove to be a pleasant diversion. R-E

## Remove Vocals

Remove the lead vocal and substitute your own voice with most stereo recordings using our new, low cost VOCAL ZAPPER™. Great for practice, professional demos or just for fun.

WITH THE

# VOCAL ZAPPER™



CHARGE TO VISA OR MC TOLL-FREE  
 1-800-654-8657 9AM to 5PM CST MON-FRI

DIRECT INQUIRIES TO:

### PAIA Electronics, Inc.

1020 W. Wilshire, Oklahoma City, OK 73116 (405)843-9626


Rush my Vocal Zapper Kit, \$24.95 plus \$3 postage & handling enclosed.  
 Send assembled Vocal Zapper, \$39.95 plus \$3 postage enclosed.  Send Free Catalog

name \_\_\_\_\_  
 address \_\_\_\_\_  
 city \_\_\_\_\_ state \_\_\_\_\_ zip \_\_\_\_\_

PAIA Electronics, dept 9R, 1020 W. Wilshire, Okla. City, OK 73116

CIRCLE 55 ON FREE INFORMATION CARD

## An enclosure as good as your idea.

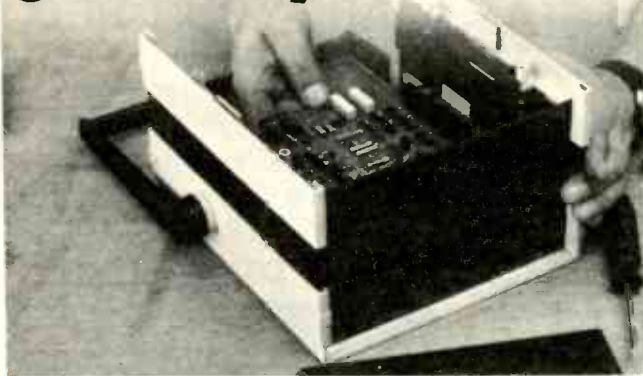

You've turned a good idea into a piece of equipment—now you need a good enclosure. Here's how PacTec can help you with our versatile enclosures:

- Attractive yet inexpensive.
- Durable ABS construction.
- Many sizes, colors, accessories.
- Built in bosses and slots speed component mounting.
- Available off-the-shelf from single unit to production quantities. See them at your PacTec Distributor. And ask him for your free catalog.




**PACITEC**™ Corp.  
 subsidiary of La France Corp.  
 Enterprise and Executive Avenues  
 Philadelphia, PA 19153 (215) 365-8400

CIRCLE 43 ON FREE INFORMATION CARD

## VECTOR PROTOTYPING PLUGBOARDS FOR IBM\* PERSONAL COMPUTER

New!

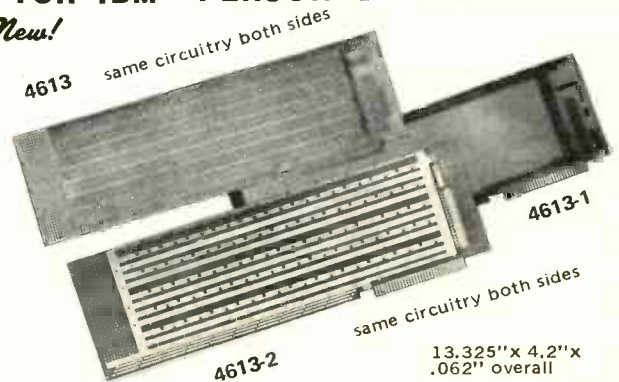

- Fit any slot in IBM Personal Computer
  - 31/62 gold plated contacts on .1" ctrs.
  - Tinned buses terminate to edge contacts per IBM standard
  - Punched universal I/O connector mounting bracket, card guide layout sheets, instructions included
  - Accept any width DIP ICs
  - .043" dia. drilled holes on 0.1" grid
- 4613-1 -bare board with Peripheral Buses for unlimited component placement \$37.00
- 4613-2 -Wire Wrapping Bus Board with full power & ground plane. Plated thru holes \$59.00
- 4613 3-hole-Pads & Bus Board for soldering or wire wrapping. Plated thru holes. \$59.00
- 3690-22 -5.7" H x 3.2" W extender card with attached connector & mounting bracket, labeled test points \$22.35

\*IBM Reg. T.M. of International Business Machines Corporation  
 Prices subject to change without notice

Vector Electronic Company  
 INCORPORATED



12460 Gladstone AV  
 Sylmar CA 91342  
 phone (213) 365-9661

86827

CIRCLE 48 ON FREE INFORMATION CARD

Electronic Troubleshooting

# WINNER



Hickok's MX333 with VARI-PITCH® and LOGI-TRAK®

Instantaneous VARI-PITCH speeds:

- Voltage tracing
- Troubleshooting in hard-to-reach locations
- Tuning type adjustments
- Resistance checks
- Digital logic troubleshooting

And . . . Detects signal characteristics and abnormalities not possible with digital or analog meters.

LOGI-TRAK replaces the best 100MHz logic probes and offers:

- Eyes on the probe tip, HI/LO indication
- Instant identification of marginal states and fault conditions
- 100MHz response
- 5n sec pulse detection

LISTEN to what the MX333 can do for you. Ask about our NO RISK 30 day Free Trial.



THE HICKOK ELECTRICAL INSTRUMENT CO.  
10514 Dupont Avenue • Cleveland, Ohio 44108  
(216) 541-8060

## COMPUTER CORNER

continued from page 82

suddenly switch to column A, row 3 if you need to access that information?

Can data be stored separately from the model? For instance, do you have to access the model itself in order to check the contents of row 5 (say that's for August), or can you access a separate file that will indicate the August sales?

Is there backup capability during the model-construction process? If a power failure or operator error occurs, will the entire model be lost, or is it backed up as it is created, so that only a small part of the work will have to be repeated?

Several computational features can make significant differences in the flexibility of your system. Are boolean-algebra functions (AND, OR, NOR, etc.) available for problems involving logic? Does the program allow for net-present-value computations that are often necessary in financial projections? For engineering and statistical projects, are roots and exponential functions available? Can the program compute percentages of increase; for instance, can it be determined that column A (sales for summer months), was 45% down from column B (October-December sales)?

All those features—and more—can be found among the various packages. You should investigate all the features offered by a package before committing yourself to it.

Where do you begin your search? The tried-and-true *VisiCalc* (VisiCorp, 2895 Zander Rd., San Jose, CA 95134) is a good place to start. Originally available just for the *Apple II*, the program is now available for the *Atari 800*, the *IBM Personal Computer*, the *TRS-80*, and Hewlett-Packard and Commodore systems.

If you are using *CP/M*, your choices include *T/MarkerII* (Lifeboat Associates, 1651 Third Ave., New York, NY 10028) (see Fig. 1), *Microplan* (Chang Labs, 10228 N. Stelling Rd., Cupertino, CA 95014), *MagiCalc* (Peachtree Software, 3 Corporate Square, #700, Atlanta, GA 30329), *SuperCalc* (Sorcim, 405 Aldo Ave., Santa Clara, CA 95050), *Multiplan* (Microsoft, 10700 Northrup Way, Bellevue, WA 98004), and *CalcStar* (MicroPro, 1299 4th St., San Rafael, CA 94901).

Phase One Systems (7700 Edgewater Dr., Oakland, CA 94621) produces *Masterplan*, a spreadsheet program to run under the *OASIS* operating system.

The business-software market has its share of programs for general ledger, accounts payable/receivable, and payroll. But financial-planning programs are in a class by themselves, providing a practical, time-saving service for the business environment.

R-E

### WARNING!

Electric Power Pollution, Spikes, Interference & Lightning HAZARDOUS to HIGH TECH EQUIPMENT!!



MicroComputers, VTR, Hi-Fi, Lasers, Spectrometers are often damaged or disrupted due to Power Pollution.

High Tech components may interact!

Our patented ISOLATORS eliminate equipment interaction, curb damaging Power Line Spikes, Tame Lightning bursts & clean up interference.

Isolated 3-prong sockets; integral Spike/Lightning Suppressor. 125 V, 15 A, 1875 W Total, 1 KW per socket.

ISO-1 ISOLATOR. 3 Isolated Sockets; Quality Spike Suppression; Basic Protection . . . . . \$69.95

ISO-3 SUPER-ISOLATOR. 3 DUAL Isolated Sockets; Suppressor; Commercial Protection . . . . . \$104.95

ISO-17MAGNUM ISOLATOR. 4 QUAD Isolated Skts; Suppressor; Laboratory Grade Protection . . . . \$181.95

Master-Charge, Visa, American Express  
TOLL FREE ORDER DESK 1-800-225-4876  
(except AK, HI, MA, PR & Canada)

SATISFACTION GUARANTEED!

Electronic Specialists, Inc.

171 South Main Street, Natick, MA 01760

Technical & Non-800: 1-617-655-1532

## ATTENTION TECHNICIANS

### ARE YOU TIRED of being

"only a serviceman"

or

"just a technician"?

THE LETTERS "CET AFTER YOUR NAME SPELLS

### "PRIDE"

## TRY IT.

Take pride in your profession—  
Decide to be a CET



For information about: \_\_\_ exam dates; \_\_\_ requirements; \_\_\_ study guides; other \_\_\_\_\_

Send to: NESDA/ISCRET  
2708 W. Berry St.  
Fort Worth, TX 76109  
(817) 921-9101

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ St. \_\_\_\_\_ Zip \_\_\_\_\_

Put Professional Knowledge and a  
**COLLEGE DEGREE**  
in your Electronics Career through  
**HOME STUDY**

**Earn Your DEGREE**

No commuting to class. Study at your own pace, while continuing your present job. Learn from easy-to-understand lessons, with help from your home-study instructors whenever you need it.

In the Grantham electronics program, you first earn your A.S.E.T. degree, and then your B.S.E.T. These degrees are accredited by the Accrediting Commission of the National Home Study Council.

Our free bulletin gives full details of the home-study program, the degrees awarded, and the requirements for each degree. Write for *Bulletin R-82*.

**Grantham College of Engineering**  
2500 So. LaCienega Blvd.  
Los Angeles, California 90034

SEND FOR THIS  
FREE CATALOG NOW



SAVE MONEY  
HIGH QUALITY  
FAST DELIVERY

We are utilizing the latest equipment and technology to maintain our quality at reasonable prices.

**JAN**  
CRYSTALS

- General Communication
- Industry
- Marine VHF
- Scanners
- Amateur Bands
- CB Standard
- CB Special
- Microprocessor

Call or Write

**JAN CRYSTALS**

P.O. Box 06017  
Ft. Myers, Fl. 33906-6017  
All Phones (813) 936-2397



CIRCLE 56 ON FREE INFORMATION CARD

**HEART RATE MONITOR**

*continued from page 48*

you cannot divide by zero. When the Heart-a-Matic is first turned on, there is no guarantee as to what data will be present on the data bus. The 4508 that controls the bus at power-up will come up with data that seems to vary with the particular IC used. In a nutshell, there is no guarantee that there won't be all zeros on the data bus when the power is first supplied. The problem is resolved by IC22-e. It is configured as a half-monostable that outputs a pulse about one

and a quarter seconds long. The IC is connected, via diode D2, to the most-significant-bit on the data bus.

When power is first turned on, the output pulse insures that there is some number greater than zero on the bus. Without that half-monostable and the "Mickey Mouse Logic" (M<sup>2</sup>L) using D2, all zeros might appear and the Heart-a-Matic would try to divide by zero. If that happened, the batteries would give out before the answer showed up in the display.

The 12-volt power supply is made up of eight "AA" cells connected in series. Its output is fed to a standard 7805 regulator used in a slightly non-standard way. Be-

*continued on page 113*

**AUDIO CRITICS  
RAVE ABOUT THE  
V15 TYPE V:**



"Our tests show that the Shure V15 Type V not only lives up to the claims made for it, but in virtually every respect OUTPERFORMS the best cartridges we have previously tested....It is hard to imagine how the V15 Type V could be improved significantly. It offers the MOST PERFORMANCE in the most areas, plus the most convenience and safety in installation and operation." — **Julian Hirsch, Stereo Review, June, 1982**

"... (The V15 Type V) is definitely the FINEST pickup Shure has ever made, which makes it one of the finest ever made, period." — **High Fidelity, July, 1982**

"... In a world of audiophile discs with demanding tracking requirements, the Shure V15 Type V KEEPS AHEAD of the times." —

**Rich Warren, Chicago Sun-Times, June 4, 1982**

"(The V15 Type V) REDEFINES its maker as a pioneer in cartridge

design not only from the beginnings of micro-groove technology but well into the future of the LP disc." — **FM Guide (Canada), June, 1982**

"... It may be safe to say that this cartridge's excellent tracking ability is NUMBER ONE in the world. Provides exquisite and elaborate sound." — **Swing Journal (Japan), May, 1982**

Find out why the critics are so excited. Send for free fact-filled brochure AL694A.

**SHURE**

Call for the name of the dealer nearest you  
**800-323-6556**. Ask for Dept. R15.  
In Illinois: 800-942-6345. Ask for Dept. R15.



Shure Brothers Inc., 222 Hartrey Avenue, Evanston, IL 60204


CIRCLE 104 ON FREE INFORMATION CARD

OF THE EIGHT MAJOR  
CAPACITANCE INSTRUMENTS  
MADE, ONLY THE CM-100...

# DETECTS LEAKAGE

(and at half the price!)

**\$89<sup>95</sup>**

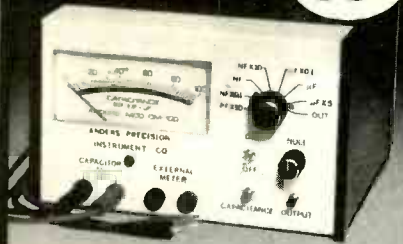

**Usefulness**—Measure capacitors 10pF—500µF\* leakage 1 nA or .005 C.V., whichever is greater. **Accuracy**—To 2% depending on range. **Dependability**—Ruggedized construction; 1 yr. warranty. **Versatility**—In circuit measurement of capacitance and leakage. Output signal proportionate to measurement. **Portability**—350 Hr. Battery Life.

\*To 25,000µF with external voltmeter

Send check, address (NO P.O. BOX) plus \$3.50 Handling. CT res. add 7½% tax.

Phone orders: (203) 423-7940

**ANDERS PRECISION INSTRUMENT CO., INC.**  
4 Bridge St. Plaza, P. O. Box 75 Willimantic, CT 06226

CIRCLE 52 ON FREE INFORMATION CARD

# FREE 10 L.E.D.s

A \$2.00 VALUE

You can now receive ten prime T-1¼ or T-1 red LEDs absolutely free. It is our way of introducing you to the quality parts we offer.

## ETRONIX

14803 N.E. 40th Dept. RE092  
Redmond, WA 98052

Yes, Please send me 10 Free LEDs, plus your brochures on additional products available. I prefer  T-1  T-1¼.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ ST \_\_\_\_\_ ZIP \_\_\_\_\_

Please include \$1.00 to help cover postage and handling.

RADIO-ELECTRONICS

110 CIRCLE 57 ON FREE INFORMATION CARD

## COMMUNICATIONS CORNER

*continued from page 78*

the volume level: The loud sounds are clipped, while the soft sounds are allowed to pass through unprocessed.

Clipping the audio waveform causes distortion, and results in the generation of odd-order harmonics. For example, if the modulating signal is 1.5 kHz, clipping will produce substantial output at the third harmonic of 4.5 kHz and the fifth harmonic of 7.5 kHz, which are outside the upper narrow-band FM limit of 3 kHz. A low-pass filter consisting of R2/R3 and C2/C3/C4 strips out everything above 3 kHz before the signal gets to the next modulation amplifier.

The output from the amplifier is fed to a potentiometer, R4, which serves as a "deviation" (modulation level) adjustment, and then on to a varactor diode that's connected to the master oscillator. In that type of circuit it's necessary only to adjust the deviation control until the test equipment indicates the desired deviation.

Confusion sometimes sets in if a separate clipping adjustment is provided. Note that in the circuit shown, the clipping level in relation to the microphone signal is fixed; it's established by the pre-amplifier's gain and by diode D1. You will often find that there's a gain control for the preamp, or a level adjustment between the preamp's output and the clipper; either way, you can set the degree of clipping for a specific level into the microphone, or tailor the clipping level to the voice level of a specific user. Just remember that the transmitter's deviation—the modulation of the RF signal—is set with a single control. **R-E**

## ANALOG DESIGN

*continued from page 103*

be found using equation 19. Complications arise if that voltage must be negative with respect to ground. Now the upper terminal of  $R_X$  should no longer be connected to  $+V_{DD}$ , but is instead connected to a negative supply. That supply is called  $-V_{GG}$ . Equation 19 still applies, except that  $-V_{GG}$  is substituted for  $V_{DD}$ . The values of  $R_X$ ,  $R_G$ , and  $R_S$  are still found as outlined above for the JFET.

### Transistor applications

From here on, we will concentrate on designing practical circuits that use bipolar and FET transistors. We will start with small signal audio applications and continue our discussion detailing high frequency circuits, feedback, and so on. Regardless of what type of circuit you are designing, you will need to apply the material we've detailed over the past two months if you are to be successful. **R-E**

## GIANT HEAVY DUTY TRUCK TARPULINS

|         |      |          |       |
|---------|------|----------|-------|
| 12 x 16 | \$23 | 26 x 40  | \$89  |
| 16 x 20 | \$32 | 26 x 55  | \$115 |
| 20 x 20 | \$36 | 30 x 60  | \$145 |
| 18 x 24 | \$38 | 50 x 100 | \$390 |
| 18 x 32 | \$50 | 60 x 120 | \$547 |
| 20 x 30 | \$50 | 50 x 150 | \$562 |

*Before Midnight Oct. 17*

Firestone Tarp Mfg. will send any of the above truck size tarpulins to any reader of this publication who reads and responds to this test before midnight Oct. 17. Each tarpaulin Lot (#Z-18, PVC) is constructed of high density fabric (with virgin grade ingredient, supplied by Gulf Oil Co., Dow Chemical Co., and Union Oil Co.) with nylon reinforced rope hems, double lock stitched hems, electronically welded seams, 100% water proof, #4 (½" dia.) metal grommets set on 3 ft. centers with reinforced triangular corner patches and are recommended for all heavy duty use, and all bulk or pallet riding materials, and will be accompanied with a LIFETIME guarantee that it must perform 100% or it will be replaced free. Add \$7 handling & crating for each tarp ordered. Firestone Tarp Mfg. pays all shipping. Should you wish to return your tarpulins you may do so for a full refund. Any letter postmarked later than Oct. 17, will be returned. LIMIT: Fifty (50) tarps per address, no exceptions. Send appropriate sum together with your name & address to: Tarp Test Dept. #496FA, Firestone Tarp Mfg., Inc., 6314 Santa Monica Blvd., L.A., CA., 90038, or for fastest service from any part of the country call collect, before midnight 7 days a week (213) 462-1914 (Ask Operator for) TARP TEST #496FA, have credit card ready.

CIRCLE 58 ON FREE INFORMATION CARD

## COMPUTERS

Complete Microprocessors line, peripherals & Terminals.

|                |         |                 |         |
|----------------|---------|-----------------|---------|
| Viscalc        | 200.00  | SORC IQ 130     | 590.00  |
| Microsoft Z/80 | 320.00  | TI-99/4A        | 279.00  |
| IDS PRISM 80   | call us | Epson MX-80     | call us |
| IDS Prism 132  | call us | Color Monitor   | call us |
| Epson MX-100   | call us | TI-810          | 1395.00 |
| TI-745         | 1440.00 | 80 Column Board | 245.00  |

## Texas Instruments

|             |          |                   |          |
|-------------|----------|-------------------|----------|
| Invest Anal | \$ 42.00 | TI-59             | \$175.00 |
| Accessories | Call us  | TI-55 II          | 39.95    |
| TI-58C      | 80.00    | Speak & Spell     | 49.95    |
| PC100C      | 155.00   | TI Programmer LCD | 54.95    |
| TI BAIL     | 39.00    | MBA               | 49.95    |

## HEWLETT-PACKARD

|                |         |                   |         |
|----------------|---------|-------------------|---------|
| HP/37E         | 72.00   | HP-11C NEW        | call us |
| HP-33C         | .85.00  | HP-12C NEW        | call us |
| HP-34C         | 115.00  | HP-41C Mem Module | .26.00  |
| HP-38C         | 114.99  | HP-67             | 295.00  |
| HP-41C Prog    | 180.00  | HP-97             | 570.00  |
| HP-41CV        | 234.00  | Quad Ram          | call us |
| HP-41C Printer | 285.00  | Application Pac   | call us |
| HP-41C CRD RDR | 169.00  | HP/83             | 1470.00 |
| HP/85          | 1990.00 | HP/125 Computer   | call us |

## SCM TYPEWRITER SPECIALS

|          |          |            |          |
|----------|----------|------------|----------|
| SCM 2200 | \$284.00 | INTREPID   | \$274.00 |
| SCM 2500 | 294.00   | CLASSIC 12 | 164.00   |

All units shipped in original cartons with accessories according to manufacturer's specification. Send money orders, personal check 2 weeks to clear. In Illinois add 6% sales tax. Add \$6.95 minimum shipping & handling charges per unit. We ship UPS. Subject to availability. Written warranty for specific products can be obtained free upon request. Above prices are for mail order and prepaid only. Prices and specifications subject to change without notice. Send mail orders.

*Nabik's, Inc.*

519 DAVIS EVANSTON, ILL. 60201 TEL 312-869-6144

# NEW BOOKS

For more details use free information card inside back cover.

**FREQUENCY SYNTHESIZERS THEORY AND DESIGN (Second Edition)** by Vadim Manassewitsch. John Wiley & Sons, Inc., One Wiley Drive, Somerset, NJ 08873. 582 pp including appendices and index; 6 1/4 x 9 1/4 inches; hardcover; \$36.00.

The original edition of *Frequency Synthesizers* was the first book to provide designers and users with a comprehensive treatment of the basic principles of synthesizer design, and an understanding of the problems often associated with it. This second edition is a significant expansion and updating of that volume. As with the first edition, this book recommends design procedures, provides useful design tools, and demonstrates the implementation of theory and circuit design with numerous practical examples.

Definitions and comprehensive descriptions of important concepts, such as phase noise and spurious outputs, and techniques for their analysis and measurement, are also provided. Detailed descriptions of some synthesizers are given to show the practical use of the design techniques that are presented in the text.

New to this second edition are two approaches—coherent direct digital synthesis and fractional-N phase-locked loop—in the chapter on frequency synthesis; updated test-equipment information; two new state-of-the-art synthesizers illustrating the application of design principles, and an entirely new chapter of troubleshooting techniques.

CIRCLE 111 ON FREE INFORMATION CARD

**AMATEUR RADIO THEORY AND PRACTICE**, by Robert L. Shrad-  
er W6BNB. Gregg Division, McGraw-Hill Book Company, 1221  
Avenue of the Americas, New York, NY 10020. 340 pp including  
appendices and index; 7 1/4 x 9 1/4 inches; softcover; \$14.95.

For those who want to get an amateur-radio license, here is a complete beginner's text that requires of the reader no previous background in radio or electronics. It explains in simple terms all of the basic theory that is needed to pass any and all of the amateur-radio license examinations given by the Federal Communications Commission (FCC). This volume is also valuable for the licensed amateur as it contains much information that the amateur needs to know in order to operate a radio station and its equipment properly.

The first chapter discusses the scope of the Amateur Radio Service, the five grades of amateur licenses available, and some of the interesting phases of amateur radio that a license will allow one to enjoy. Chapters 2 through 20 present the basic electrical, electronics, and radio theory that should prepare the reader to pass any of the written license tests. Chapter 21 is a "how to" that outlines how the reader can learn to send and receive Morse code at the speed required for any of the amateur licenses. Chapter 22 contains a nontechnical condensation of many of the important amateur-radio rules and regulations that were not included in the earlier chapters.

Each chapter contains its main body of information plus a very

## DISCOUNT TEST EQUIPMENT

LOWEST PRICES AND IMMEDIATE DELIVERY FOR OVER 40 YEARS

### KEITHLEY

130



3 1/2 Digit • 5  
Functions •  
0.5% DCV  
Accuracy

**\$122**

135



4 1/2 Digit •  
0.05% DCV  
Accuracy •  
5 Functions

**\$229**

### B & K

1405



5 MHz 3" Scope •  
10mV/Division Vertical  
Sensitivity • More

**\$285**

1479BP



Dual Trace 30 MHz Trig-  
gered • 11.7nS Rise Time  
• 5mV/cm Vertical Sen-  
sitivity • Probes • More

**\$882.**

### FLUKE

8024B



3 1/2 Digit • 11  
Functions •  
0.1% DC Ac-  
curacy •  
Safety  
Designed  
Test Leads

**\$229**

8062A



4 1/2 Digit •  
Full Func-  
tions And  
Ranges •  
True RMS to  
30 kHz •  
0.05% DC  
Accuracy

**\$269**

### BECKMAN

TECH 310



3 1/2 Digit • 7  
Functions •  
29 Ranges •  
0.25% DC  
Accuracy

**\$135**

HD-100



3 1/2 Digit • 7  
Functions •  
29 Ranges •  
0.25% DC  
Accuracy •  
Drop Proof •  
Water Proof

**\$162**

### LEADER


LBO 522



New Model • 20 MHz  
Dual Trace • 0.5 mV Sen-  
sitivity • More

**\$740**

LBO 524L

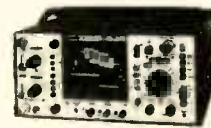

New Model • 35 MHz  
Dual Trace • 0.5 mV Sen-  
sitivity • More

**\$1206**

### HICKOCK

LX303



3 1/2 Digit •  
19 Ranges  
And Func-  
tions • Auto  
Zero • 1%  
DC Accuracy

**\$91**

LX304



All Features  
of LX303 •  
Auto Dec-  
imal • Low  
Battery In-  
dicator •  
Diode And  
Transistor  
Test

**\$96**

## WM. B. ALLEN SUPPLY

1601 Basin Street, New Orleans, LA 70116



Over 70,000 electronic items  
in stock for immediate delivery.



CALL TOLL FREE

**800 535-9593**

LOUISIANA TOLL FREE 800 462-9520

CIRCLE 22 ON FREE INFORMATION CARD



**FREE!**

# Introductory OFFER-



As an introduction to our fine line of deluxe soldering tool holders, EDSYN is offering the following FREE special. With the purchase of holder models IP289, B-170, or TL194, you receive at no further cost an Ersa® TIP 16 16W/115V soldering tool featuring mechanical temperature adjustment as well as two Loner® combination tip and nut wrenches.


## IP289 *idle-rest*® SOLDERING TOOL POD



Internal construction with air vents keeps the temperature of the holder safe to the touch. Includes tip cleaning sponge and bench top mounting boss. Designed for use

only with Ersa® TIP 16 and Loner® model soldering instruments.

## B-170 *Base 1* *idle-rest*®

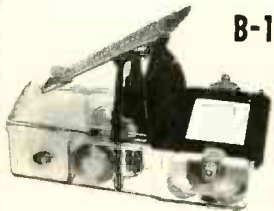

Fully engineered soldering station designed with safety in mind. Numerous deluxe features include:

safe-lock release, thermal cover, sponge, cleaning basins, reservoir, and solder spool. Designed for use with Ersa® TIP 16 and all Loner® model soldering instruments only.

## TL194 *General Purpose* *idle-rest*®



A complete soldering station containing: tip sponge, water reservoir, parts tray, roll of

solder & wick. Suitable for bench mounting. May be used with most types of soldering tools.

For more information, see your local EDSYN Service Center distributor or call EDSYN at (617) 747-3346.

Send for FREE WIGAPRY™ on your company letterhead



and 70 Page FORM 325A

COMPLETE Catalog



of 21st CENTURY Soldering Products

EDSYN® SERVICE CENTER

65 COLUMBIA CIRCLE, PLYMOUTH, MASS. 02360 (617) 747-3346

**GOOD TOOLS REDUCE**

*Unemployment Pools!*

WORLD'S MOST PRACTICAL SOLDER HANDLING TOOLS

helpful checkup quiz, every few pages—answers to be found on the following page. And at the end of chapters, you will find representative questions listed under the five amateur-license grades.

CIRCLE 112 ON FREE INFORMATION CARD

**PET BASIC: TRAINING YOUR PET COMPUTER**, by Ramon Zamora, Robert Albrecht, and William Scarvie. Reston Publishing Company, Inc., Reston, VA 22090. 310 pp including appendices and index; 5 7/8 x 8 7/8 inches; softcover; \$12.95.

If you are a newcomer to the PET, you'll find that each chapter in this book has been written for those learning to use the PET. There are many examples, do-it-yourself exercises, and fun-filled explorations. The text will encourage the user to experiment and try out the numerous features and capabilities of the PET; it even shows how to create graphical images on the PET screen without difficulty.

For those who have been PET owners for some time, this book will prove to be a handy reference source, and a means of discovering new things that the PET can do. Each chapter includes a set of exercises for review that will help the owner to learn more, and develop greater skill in using that dynamic machine.

CIRCLE 113 ON FREE INFORMATION CARD

**INTRODUCTION TO RADIO FREQUENCY DESIGN**, by W.H. Hayward. Prentice-Hall, Inc., Englewood Cliffs, NJ 07632. 383 pp including index; 7 x 9 1/2 inches; \$27.95.

This book is designed for three specific reader groups: the working engineer, scientist, technician, or manager; the student of engineering or computer science, and the electronics hobbyist, including the radio amateur.

A central theme emphasized throughout the book is simplicity. More formal treatments of individual subjects are found in the references listed at the end of the individual chapters. Mathematics is used in the text as required to convey information to the reader.

The individual chapters cover: low-frequency transistor models, filter basics, coupled resonator filters, transmission lines, two-port networks, practical amplifiers and mixers, oscillators and frequency synthesizers, and the receiver: an RF system.

R-E

CIRCLE 114 ON FREE INFORMATION CARD



## IT TAKES THICK SKIN AND GUTS TO MAKE A TOUGH TOOL CASE.

With rising production costs and smaller profit margins there must be a really strong commitment to excellence if superior tool cases are to continue being produced.

Platt is making this commitment. Their thick skinned tool cases are still made of the finest, high grade industrial materials. (Like durable ABS thermoplastic, for instance.)

Their guts still feature the industries only one-piece molded pallet.\* There are no seams, stitches or rivets—the pockets can't tear loose.

And Platt has the only one year warranty on case and pallet.

So, contact Platt for complete information on their full line of tough, durable tool cases and your nearest distributor.

\*Pat. No. 3,880,285

platt

Cases for business and industry.  
2301 S. Prairie Ave., Chicago, Ill. 60616 (312) 225-6670



## HEART RATE MONITOR

*continued from page 109*

cause R27 is placed on the ground leg of the regulator, we are able to trick the device into putting out six volts instead of the standard five. That operating voltage was chosen for the Heart-a-Matic to provide a compromise between battery life and reliable operation. The monitor draws an average of 60 milliamps during operation allowing long battery life.

A low-battery warning is provided by R47, Q3, and SCR1. The voltage at the base of Q3 determines the voltage drop

across R46. When it reaches a particular level, enough current will flow through the resistor to provide sufficient current to trigger SCR1. When the rectifier fires, the signal is routed to the decimal points of the display with the help of another bit of M<sup>2</sup>L logic, causing them to remain lit constantly. Diode D1 allows the beep generator to continue operating, and resistor R7 was chosen to make the decimal points light up much more brightly than they do during the heartbeat—so there will be no mistaking that the batteries are getting low and should be replaced.

The trip point of SCR1 is set with R47, a 500 kilohm multi-turn potentiometer.

Once the decimal points light, the SCR's latching action will keep them lit. Note that if the Heart-A-Matic is rapidly turned on, off, and back on again, the low-battery warning will appear. That's because C25 has not had time to discharge completely and the remaining charge fools the low-battery circuit into thinking that the batteries—not the capacitor—are not putting out enough voltage. A wait of about ten seconds is sufficient to prevent that from happening.

Now that we know how the Heart-a-Matic works, the next step is to build one. We will show you just how that is done in the next part of this article. **R-E**

## TRS-80™ by RADIO SHACK - BUY DIRECT-DISCOUNT PRICES

**VIC-20**  
The friendly computer

PURE RADIO SHACK EQUIPMENT - FREE COPY OF WARRANTY UPON REQUEST

**SCM SMITH-CORONA**

**TOLL FREE 1-800-841-0860**

TRS-80 Model II. . . . . From **'2988**  
 TRS-80 Model 16. . . . . From **'4158**  
 TRS-80 Color Computer. From **'299**  
 TRS-80 Model III. . . . . From **'609**  
 Centronics 739-1. . . . . **'469**  
**Smith Corona TP-1**  
**Daisy Wheel Printer... '639**  
**VIC-20 Computer..... '249**



*Thousands of Satisfied Customers Since 1978*

TM - Tandy Corporation

**WE CARRY THE FULL TRS-80 PRODUCT LINE**  
**\*WRITE FOR FREE CATALOG\***  
**MICRO MANAGEMENT SYSTEMS, INC.**

PARCEL DIVISION - DEPT NO. 15

2803 Thomasville Road East

Cairo, Georgia 31728


GA. & INFO 912-377-7120

CIRCLE 42 ON FREE INFORMATION CARD

## MICROWAVE TV CONVERTERS

MODEL DCV-1-A

DOWN CONVERTER/ANTENNA COMBINATION

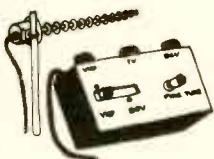

- 2 MICROWAVE PREAMP STAGES for maximum gain
- ONE PIECE CONSTRUCTION simplifies installation
- ALUMINUM AND ZINC PLATED STEEL for durability
- BUILT IN A/B SWITCH with more than 95dB isolation
- 2.1-2.8 GHz Covers all ham, commercial and ITFS channels

Years of enjoyment are yours with our model DCV-1-A. Two preamp stages coupled with the yagi antenna/housing provide a typical system gain of 53dB.

YOU GET: 75' downlead  
 3' jumper  
 300 ohm matching transformer  
 detailed instructions

ASSEMBLED & TESTED  
 LIST - \$175.00

**ONLY \$149.95**

INTRODUCTORY PRICE

WE CARRY A COMPLETE LINE INCLUDING PARABOLICS

**DEALER INQUIRIES INVITED**

**TRITON**  
MARKETING CORP.

VISA, MASTERCARD ACCEPTED



679 REMSEN AVENUE  
 BROOKLYN, NEW YORK 11236

**212-345-8000**

CIRCLE 44 ON FREE INFORMATION CARD

ANNOUNCING . . .



## SATELLITE TELEVISION SYSTEMS

From

**TRITON MARKETING CORP.**

THE LEADER IN MICROWAVE ENTERTAINMENT DEVICES

COMPLETE SYSTEM PACKAGES

FOR HOME AND COMMERCIAL APPLICATIONS

DISTRIBUTORS OF QUALITY;

- ANTENNAS
- LNA'S
- REMOTE ACTUATORS
- SMATV EQUIPMENT
- ACCESSORIES
- RECEIVERS

We Invite Quotations for Export

TRITON  
MARKETING CORP.

679 REMSEN AVENUE  
 BROOKLYN, NEW YORK 11236

**212-345-8000**

CIRCLE 45 ON FREE INFORMATION CARD

# MARKET CENTER

## SATELLITE TELEVISION

**SATELLITE TELEVISION!** Super discount prices. Don't spend too much—call us! **COMMUNICATIONS CONSULTANTS** 501-452-3149

**SATELLITE TV** antenna, 10 ft. fiberglass, complete, polar mount, \$1950.00, electronics at cost also. **TRI-STAR COMMUNICATIONS**, Box 843, Erie, MI 48133 (419) 726-1095

**SATELLITE** television ... Howard/Coleman boards to build your own receiver. For more information write: **ROBERT COLEMAN**, Rt. 3, Box 58-ARE, Travelers Rest, SC 29690

**SATELLITE Super-Mixer: DBM-4150A.** Clean up your TVRO receiver! Near theoretical performance; flat response, DC-1500IF SMA connectors; \$69.50—CK/MO/COD **RIGEL SYSTEMS**, 2974 Scott Blvd., Santa Clara, CA 95050 (408) 727-3628

**LAST CHANCE for FREE \$200.00 value TVRO P.C. board set** when you join our development group. Prices are going up. Build your own complete system low as \$700.00. Newest designs, group purchasing, etc. Aiming chart and data \$1.00. Construction plans \$10.00, membership \$50.00. PC board sets \$75.00. **COMPUTER SATELLITE SERVICES**, 1604 N Smith St., Spokane, WA 99207 (509)534-8088 6-9 PM PST

**SATELLITE** equipment catalog. Over 25 of the best manufacturers and suppliers. LNA's, receivers, antennas, and complete systems covered in four dif-

ferent sections. Free satellite aiming chart and microwave interference handbook (\$10.00 value) included. \$9.95. **TMS CO.**, P.O. Box 8369, Roseville, MN 55113

**MICROWAVE TV downconverter, assembled and tested \$44.95, kit \$29.95, power supply kit \$29.95. Fully illustrated instruction manual included. Satisfaction guaranteed. Check, MO, COD. XANDI**, Dept. 41, Box 25647, Tempe, AZ 85282

**DRAKE** satellite receiver with modulator installed only \$969.00. Satellite and microwave catalog \$1.00. **TEM MICROWAVE**, 22518 97th Ave. No., Corcoran, MN 55374 (612) 498-8014



## SATELLITE TV FANTASTIC 80 TV CHANNELS

New antenna construction plans plus big 8x11 book loaded with aiming info, kits, LNAs and receivers at wholesale prices. Far better than cable TV! Enjoy crystal clear reception. Send \$9.95 today. Add \$2.00 for 1st class (air mail) or call our 24 hr. COD order line (305)862-5068 Now.

Global TV Electronics, P.O. Box 219-F, Maitland, FL 32751

## SATELLITE TV WEEK

The most complete weekly listings. We cover more than just SATCOM 3. Send \$1 for sample copy.

## Satellite TV Week

P.O. Box 308, Fortuna, California 95540  
Call toll free: (800) 358-9997 • California (707) 725-2476

## BUSINESS OPPORTUNITIES

**LAWYER** Business litigation, patents, appeals. **JEROME FIELD**, B 292, Brooklyn 11230. Phone (212) 434-0781. Eves. 434-1825

**ASSEMBLE** profitable devices at home. Exceptional opportunities—without investment. **ENTERPRISES**, 1133-R, Linwood Place, Utica, NY 13501

**ATARI** repair business. Start your own. Send \$5.00 for more information to: **IRATA REPAIRS**, 2562 East Glade, Mesa AZ, 85204

**USED TV's**—tougher the economy—more the demand. Get started in this lucrative part or full time business out of your own home. Complete details on how to buy, sell, price service tips, much more. \$5.00. **USED TV's**, Dept. RE, Box 19754, Indianapolis, IN 46219

**PROJECTION TV** ... Make \$200.00+ per evening assembling projectors ... Easy ... Results total to \$2,500.00 projectors ... Your total cost less than \$15.00. ... Plans, lens & dealer's information \$14.00. ... Illustrated information free ... **MACROM-GAX**, Washington Crossing, PA 18977. Credit card orders 24 hours. (215) 736-2880

**MAJOR Northern California** electronic replacement parts retailer. Solidly established, high profit, recession resistant business. \$750,000.00 includes all assets, ten year lease, and flexible terms. **GBS, Inc.** agt. (916) 381-8020

**MECHANICALLY** inclined individuals desiring ownership of Small Electronics Manufacturing Business—without investment. Write: **BUSINESSES**, 92-R, Brighton 11th, Brooklyn, NY 11235

## HIGHLY PROFITABLE

## ELECTRONIC FACTORY

Investment unnecessary. knowledge not required. sales handled by professionals. Ideal home business. Write today for facts! Postcard will do, **Barta-RE-X**, Box 248, Walnut Creek, CA 94597.

**MAKE** money selling electronics. Wholesale dealer catalog \$5.00 (redeemable). **ETCO**, Dept. 533, Box 840, Champlain, NY 12919

**MAIL** order—electronic components—well established high profit market. Start your own business. I have the expertise and working tools to send you on your way to an exciting future. For further details write to: **STAN L.**, 45 E. 17th St., Suite 1101, NYC, NY 10003

## McKay SETS THE STANDARD FOR COMPACT AM RECEIVING

### ANTENNAS

**DA100D OUTDOOR ANTENNA and DA9-DL4 LOOP ANTENNA**

For specs & details contact these dealers

**HARVEY RADIO & BARRY ELECTRONICS** New York City  
**HENRY RADIO** Los Angeles, CA  
**GILFER ASSOCIATES** Park Ridge, NJ  
**EDMOND SCIENTIFIC CO.** Burlington, NJ  
**ELECTRONIC EQUIPMENT BANK** Vienna, VA (D.C. Area)  
**PROMAR** Tampa, FL  
**FRANK L. BEIER RADIO INC.** Jefferson, LA  
**THE BASE STATION** Concord, CA  
**J-MAR ELECTRONICS** Toronto, Canada  
**INTERNATIONAL RADIO WORLD INC** Vancouver, Canada

**800/854-7769** Local • 714/621-6711  
except Telex • 910-581-4990

Calif., Alaska, Hawaii

**G. E. McKAY & CO.**  
111 S. College Ave.  
PO Box 5000  
Claremont, CA 91711



# DCE

## SATELLITE — COMPUTER — TEST EQUIPMENT —

**DISCRETE 70 MHz PLL** — Replaces NE564 video demodulator with out the need for an ECL divider. (70 MHz I.F.). Guaranteed tracking to 85 MHz. Wide bandwidth. Lower C/N. reduced 'tearing'. May be remotely tuned.  
Kit (M82-010X) ..... \$124.95  
A & T (M82-010T) ..... \$159.95

**TUNABLE AUDIO DEMODULATOR** — Tunes from 5.4 to 8.2 MHz. Switchable 5 MHz LP filter for Canadian birds. Tuning diodes included. Two of these and a couple op-amps required for stereo. (MTV)

Bare Board (M81-020B) ..... \$24.95  
Two Boards (M81-021B) ..... 39.95

**CANADIAN AUDIO DESCRAMBLER** — Tune in those 'chirping' sub-carriers and hear what you've been missing

Bare Board (R82-010B) ..... \$24.95  
Kit (R81-010X) ..... \$59.95  
A & T (R81-010T) ..... \$94.95

**LO—OHMS ADAPTOR** — Adapts normal VOM or OVM to measure from 001 ohm to 5 ohms using single 9-volt battery. Super simple calibrations.

Bare Board (M82-100X) ..... \$14.95  
Kit (M82-100X) ..... \$29.95  
A & T (M82-100T) ..... \$49.95

**MODEM** — Bell 103 (300 bps) compatible Answer/Originate modem. No acoustic coupler required. RS-232 serial I/O.

Bare Board (R81-100B) ..... \$24.95  
Kit (R81-100X) ..... \$69.95  
A & T (R81-100T) ..... \$99.95

All prices include complete and comprehensive documentation, postage and handling. C.O.D. orders accepted. Call or write for catalog. Dealer inquiries invited.

## DIGICOM ENGINEERING, INC.

P. O. Box 1656, KODIAK, ALASKA 99615  
907-486-5118 907-486-6215

OPEN 10 AM TO 8 PM PST

DESIGNS IN CONSUMER ELECTRONICS  
DC TO LIGHT


**SANYO**  
STK-0050  
**\$620**

(Minimum 10)



**SANYO**  
2SD613  
**70¢**

(Minimum 10)

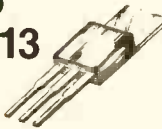


**Matching XFMR**  
JB-300  
**44¢**  
(100-up)

**48¢** (10-99)



**Popular Diode**  
GH3F (for SONY)  
**95¢**

(Minimum 10) (Minimum 10)

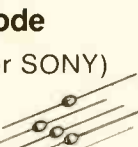

(The above special prices are effective until October 1, 1982)

## semiconductors

| Transistors | 30-99 | 100-29 | 1-9  | B605   | 80   | 70   | 80   | C1307  | 2.10 | 2.40 | 2.80 | C1913  | 80   | 90   | 1.00 | C2813 | 30   | 35   | 40   | D895  | 2.20 | 2.60 | 2.90 |
|-------------|-------|--------|------|--------|------|------|------|--------|------|------|------|--------|------|------|------|-------|------|------|------|-------|------|------|------|
| 2SA497      | 1.20  | 1.30   | 1.40 | A908   | 7.00 | 7.40 | 7.80 | C1308K | 2.60 | 2.90 | 3.40 | C1914A | 40   | 50   | 60   | C2814 | 30   | 35   | 40   | D896  | 2.20 | 2.60 | 2.90 |
| A509        | 35    | 40     | 45   | A909   | 7.90 | 8.20 | 8.60 | C1312  | 25   | 30   | 35   | C1915  | 50   | 60   | 70   | C2824 | 1.10 | 1.25 | 1.50 | D904  | 3.90 | 4.30 | 4.60 |
| A510        | 2.00  | 2.20   | 2.40 | A912   | 55   | 65   | 75   | C1313  | 25   | 30   | 35   | C1919  | 30   | 35   | 40   | C2837 | 5.40 | 5.60 | 5.90 | D947  | 5.00 | 6.00 | 7.00 |
| A525        | 50    | 60     | 70   | A913   | 70   | 70   | 80   | C1316  | 100  | 480  | 480  | C1921  | 50   | 60   | 70   | C2838 | 5.80 | 6.00 | 6.20 | D993  | 2.95 | 3.30 | 3.60 |
| A537        | 2.10  | 2.30   | 2.50 | A914   | 80   | 90   | 90   | C1317  | 25   | 30   | 35   | C1923  | 25   | 30   | 35   | C2839 | 30   | 35   | 40   | D994  | 4.30 | 4.60 | 4.90 |
| A539        | 35    | 40     | 45   | A915   | 50   | 60   | 70   | B621   | 30   | 35   | 40   | C1940  | 40   | 45   | 50   | C2921 | 8.40 | 8.60 | 8.90 | D995  | 4.80 | 5.20 | 5.60 |
| A545        | 50    | 60     | 70   | A916   | 90   | 1.10 | 1.30 | B622   | 1.80 | 1.80 | 2.00 | C1941  | 1.20 | 1.50 | 1.80 | C2922 | 8.60 | 8.90 | 9.40 | D1012 | 30   | 35   | 40   |
| A561        | 30    | 35     | 40   | A917   | 80   | 90   | 1.10 | B623   | 50   | 60   | 70   | C1942  | 2.80 | 3.10 | 3.30 | C2927 | 25   | 30   | 35   | D1029 | 55   | 65   | 75   |
| A562        | 30    | 35     | 40   | A918   | 40   | 50   | 60   | B624   | 6.40 | 6.50 | 1.00 | C1943  | 3.40 | 3.80 | 4.20 | C2930 | 1.80 | 1.80 | 2.00 | D1046 | 1.70 | 1.95 | 2.15 |
| A564        | 30    | 35     | 40   | A919   | 40   | 50   | 60   | B647A  | 50   | 60   | 70   | C1944  | 45   | 50   | 55   | C2931 | 6.00 | 7.0  | 8.0  | D1047 | 2.60 | 2.90 | 3.20 |
| A565        | 60    | 70     | 80   | A921   | 40   | 50   | 60   | B647B  | 40   | 45   | 50   | C1945  | 45   | 50   | 55   | C2932 | 2.20 | 2.35 | 2.45 | D1048 | 30   | 35   | 40   |
| A566        | 2.40  | 2.80   | 3.20 | A922   | 35   | 45   | 55   | B648   | 50   | 60   | 70   | C1946  | 55   | 65   | 75   | C2933 | 3.50 | 4.0  | 4.5  | D1060 | 1.10 | 1.30 | 1.50 |
| A606        | 1.30  | 1.50   | 1.70 | A923   | 35   | 45   | 55   | B649A  | 50   | 60   | 70   | C1947  | 1.60 | 1.70 | 1.80 | C2934 | 2.90 | 3.10 | 3.25 | D1062 | 1.40 | 1.60 | 1.90 |
| A607        | 1.60  | 1.80   | 2.00 | A924   | 1.20 | 1.60 | 1.90 | B649B  | 4.20 | 4.50 | 4.80 | C1973  | 80   | 90   | 1.00 | D290  | 2.40 | 2.55 | 2.95 | D1063 | 1.50 | 1.90 | 2.20 |
| A608        | 35    | 40     | 45   | A925   | 25   | 30   | 35   | B657   | 3.50 | 3.65 | 3.95 | C1974  | 1.50 | 1.70 | 1.90 | D291  | 1.55 | 1.75 | 1.95 | D1064 | 2.40 | 2.60 | 2.90 |
| A609        | 60    | 70     | 80   | A926   | 35   | 40   | 45   | B657A  | 1.20 | 1.50 | 1.90 | C1975  | 1.50 | 1.70 | 1.90 | D292  | 1.80 | 2.10 | 2.30 | D1067 | 65   | 70   | 80   |
| A610        | 3.20  | 3.40   | 3.80 | A927   | 25   | 30   | 35   | B661   | 4.20 | 4.40 | 4.60 | C1980  | 50   | 60   | 65   | D313  | 65   | 75   | 85   | D1111 | 80   | 100  | 1.20 |
| A611        | 3.20  | 3.40   | 3.80 | A928   | 35   | 40   | 45   | B662   | 1.20 | 1.30 | 1.50 | C1981  | 3.00 | 3.20 | 3.60 | D315  | 80   | 90   | 1.00 | D1138 | 80   | 95   | 1.10 |
| A620        | 70    | 80     | 1.10 | A929   | 40   | 45   | 50   | B666A  | 1.20 | 1.30 | 1.50 | C1982  | 1.60 | 1.80 | 2.00 | D322  | 30   | 35   | 40   | D2002 | 40   | 50   | 60   |
| A621        | 1.10  | 1.25   | 1.65 | A930   | 35   | 40   | 45   | B666B  | 1.25 | 1.40 | 1.60 | C1983  | 30   | 35   | 40   | D323  | 30   | 35   | 40   | D2003 | 70   | 80   | 90   |
| A627        | 3.10  | 3.30   | 3.60 | A931   | 30   | 35   | 40   | B669A  | 1.25 | 1.40 | 1.60 | C1984  | 40   | 50   | 60   | D324  | 30   | 35   | 40   | D2004 | 40   | 50   | 60   |
| A628        | 30    | 35     | 40   | A932   | 40   | 45   | 50   | B669B  | 2.30 | 2.60 | 2.90 | C1985  | 25   | 30   | 35   | D325  | 50   | 60   | 70   | D2005 | 70   | 80   | 90   |
| A634        | 45    | 55     | 65   | A933   | 1.60 | 1.70 | 1.80 | B669C  | 2.30 | 2.60 | 2.90 | C1986  | 45   | 50   | 55   | D326  | 30   | 35   | 40   | D2006 | 70   | 80   | 90   |
| A636        | 85    | 1.10   | 1.30 | A934   | 50   | 60   | 70   | B672   | 2.10 | 2.20 | 2.40 | C1987  | 30   | 35   | 40   | D327  | 30   | 35   | 40   | D2007 | 60   | 70   | 80   |
| A640        | 30    | 35     | 40   | A935   | 90   | 1.00 | 1.10 | B673   | 3.50 | 3.65 | 3.95 | C1988  | 30   | 35   | 40   | D328  | 30   | 35   | 40   | D2008 | 65   | 75   | 85   |
| A641        | 30    | 35     | 40   | A936   | 35   | 40   | 45   | B674   | 3.50 | 3.65 | 3.95 | C1989  | 45   | 50   | 55   | D329  | 30   | 35   | 40   | D2009 | 65   | 75   | 85   |
| A642        | 40    | 45     | 50   | A937   | 30   | 35   | 40   | B675   | 4.20 | 4.50 | 4.80 | C1990  | 45   | 50   | 55   | D330  | 30   | 35   | 40   | D2010 | 65   | 75   | 85   |
| A643        | 45    | 50     | 55   | A938   | 30   | 35   | 40   | B700   | 2.75 | 3.45 | 3.95 | C1991  | 30   | 35   | 40   | D331  | 30   | 35   | 40   | D2011 | 30   | 35   | 40   |
| A649        | 5.00  | 5.25   | 5.50 | A939   | 35   | 40   | 45   | B702   | 4.00 | 4.50 | 4.90 | C1992  | 30   | 35   | 40   | D332  | 30   | 35   | 40   | D2012 | 30   | 35   | 40   |
| A653        | 2.70  | 2.90   | 3.10 | A940   | 35   | 40   | 45   | B703   | 3.00 | 3.40 | 3.90 | C1993  | 30   | 35   | 40   | D333  | 30   | 35   | 40   | D2013 | 30   | 35   | 40   |
| A659        | 35    | 45     | 55   | A1000B | 1.20 | 1.40 | 1.60 | B704   | 2.50 | 3.00 | 3.40 | C1994  | 30   | 35   | 40   | D334  | 30   | 35   | 40   | D2014 | 30   | 35   | 40   |
| A661        | 60    | 65     | 70   | A1001  | 3.00 | 3.90 | 4.20 | B705   | 1.10 | 1.30 | 1.50 | C1995  | 30   | 35   | 40   | D335  | 30   | 35   | 40   | D2015 | 30   | 35   | 40   |
| A663        | 3.70  | 3.90   | 4.10 | A1011  | 75   | 80   | 90   | B706   | 2.80 | 3.10 | 3.40 | C1996  | 30   | 35   | 40   | D336  | 30   | 35   | 40   | D2016 | 30   | 35   | 40   |
| A666        | 35    | 40     | 45   | A1012  | 40   | 50   | 60   | B707   | 1.20 | 1.40 | 1.60 | C1997  | 30   | 35   | 40   | D337  | 30   | 35   | 40   | D2017 | 30   | 35   | 40   |
| A670        | 90    | 1.00   | 1.20 | A1013  | 60   | 70   | 80   | B708   | 1.20 | 1.40 | 1.60 | C1998  | 30   | 35   | 40   | D338  | 30   | 35   | 40   | D2018 | 30   | 35   | 40   |
| A671        | 80    | 90     | 1.00 | A1014  | 55   | 70   | 80   | B709   | 3.25 | 3.50 | 3.80 | C1999  | 30   | 35   | 40   | D339  | 30   | 35   | 40   | D2019 | 30   | 35   | 40   |
| A672        | 30    | 35     | 40   | A1015  | 1.10 | 1.30 | 1.50 | B710   | 3.25 | 3.50 | 3.80 | C2000  | 30   | 35   | 40   | D340  | 30   | 35   | 40   | D2020 | 30   | 35   | 40   |
| A673        | 35    | 40     | 45   | A1016  | 55   | 70   | 80   | B711   | 1.10 | 1.30 | 1.50 | C2001  | 30   | 35   | 40   | D341  | 30   | 35   | 40   | D2021 | 30   | 35   | 40   |
| A678        | 35    | 45     | 55   | A1017  | 55   | 70   | 80   | B712   | 1.10 | 1.30 | 1.50 | C2002  | 30   | 35   | 40   | D342  | 30   | 35   | 40   | D2022 | 30   | 35   | 40   |
| A679        | 3.75  | 4.00   | 4.25 | A1018  | 35   | 40   | 45   | B713   | 1.10 | 1.30 | 1.50 | C2003  | 30   | 35   | 40   | D343  | 30   | 35   | 40   | D2023 | 30   | 35   | 40   |
| A682        | 70    | 80     | 90   | A1019  | 45   | 50   | 55   | B714   | 1.10 | 1.30 | 1.50 | C2004  | 30   | 35   | 40   | D344  | 30   | 35   | 40   | D2024 | 30   | 35   | 40   |
| A683        | 40    | 45     | 50   | A1020  | 45   | 50   | 55   | B715   | 1.10 | 1.30 | 1.50 | C2005  | 30   | 35   | 40   | D345  | 30   | 35   | 40   | D2025 | 30   | 35   | 40   |
| A684        | 40    | 45     | 50   | A1021  | 45   | 50   | 55   | B716   | 1.10 | 1.30 | 1.50 | C2006  | 30   | 35   | 40   | D346  | 30   | 35   | 40   | D2026 | 30   | 35   | 40   |
| A685        | 25    | 30     | 35   | A1022  | 45   | 50   | 55   | B717   | 1.10 | 1.30 | 1.50 | C2007  | 30   | 35   | 40   | D347  | 30   | 35   | 40   | D2027 | 30   | 35   | 40   |
| A689K       | 35    | 40     | 45   | A1023  | 45   | 50   | 55   | B718   | 1.10 | 1.30 | 1.50 | C2008  | 30   | 35   | 40   | D348  | 30   | 35   | 40   | D2028 | 30   | 35   | 40   |
| A705        | 45    | 55     | 65   | A1024  | 45   | 50   | 55   | B719   | 1.10 | 1.30 | 1.50 | C2009  | 30   | 35   | 40   | D349  | 30   | 35   | 40   | D2029 | 30   | 35   | 40   |
| A706        | 1.10  | 1.30   | 1.40 | A1025  | 45   | 50   | 55   | B720   | 1.10 | 1.30 | 1.50 | C2010  | 30   | 35   | 40   | D350  | 30   | 35   | 40   | D2030 | 30   | 35   | 40   |
| A711        | 50    | 60     | 70   | A1026  | 45   | 50   | 55   | B721   | 1.10 | 1.30 | 1.50 | C2011  | 30   | 35   | 40   | D351  | 30   | 35   | 40   | D2031 | 30   | 35   | 40   |
| A719        | 25    | 30     | 35   | A1027  | 45   | 50   | 55   | B722   | 1.10 | 1.30 | 1.50 | C2012  | 30   | 35   | 40   | D352  | 30   | 35   | 40   | D2032 | 30   | 35   | 40   |
| A720        | 25    | 30     | 35   | A1028  | 45   | 50   | 55   | B723   | 1.10 | 1.30 | 1.50 | C2013  | 30   | 35   | 40   | D353  | 30   | 35   | 40   | D2033 | 30   | 35   | 40   |
| A721        | 25    | 30     | 35   | A1029  | 45   | 50   | 55   | B724   | 1.10 | 1.30 | 1.50 | C2014  | 30   | 35   | 40   | D354  | 30   | 35   | 40   | D2034 | 30   | 35   | 40   |
| A722        | 25    | 30     | 35   | A1030  | 45   | 50   | 55   | B725   | 1.10 | 1.   |      |        |      |      |      |       |      |      |      |       |      |      |      |

**PLANS & KITS**

**FREE** catalog 99 cent kits. Buy 2 get 1 free. Parts, bargains galore. ALLKIT, 434 West 4th St., West Islip, NY 11795

**PRINTED** circuit boards from sketch or artwork. Kit projects. Free details. DANOCINTHS INC., Box 261, Westland, MI 48185

**CABLE** TV converters and equipment. Plans and parts. Build or buy. For information send \$2.00. C & D ELECTRONICS, PO Box 21, Jenison, MI 49428

**LIGHTING** display sequencers and controllers. Send SASE for information on plans, parts and consulting services. DESIGN SPECIALTY, 15802 Spingdale St. #80, Huntington Beach, CA 92649

**SAVE** steps, money. Use your telephones as an intercom. Plans \$5.00. dB Enterprises, Box 453R, Westwood, NJ 07675

**SPIES** like our antennas, so do HAMS and SWLs. SDRE, Box 242, Blacksburg, VA 24060 (703) 951-9030

**CONVERT** your \$2000.00 oscilloscope into a \$69.99 T.V. monitor. Super simple, fun, more practical than it sounds. Complete plans \$2.95. Random Access, Box 4177OR, Phoenix, AZ. 85080

**MICROWAVE** downconverter new 4 stage design outperforms all the others. Kit \$59.95. Assembled \$89.95. 6 month warranty. Bogner antenna \$31.95. System gainover 45 dB. \$2.00 for information. MINIATURE COMMUNICATION, P.O. Box 114, Cudahy, WI 53110

**APPLE II** compatible. Highly advanced MMS burglar alarm kit. Includes mil spec sensor, floppy software, interface PC boards, parts list, schematic, and instructions. \$199.50 introductory order CK/MO/COD. RIGEL SYSTEMS, 2974-R Scott Blvd., Santa Clara, CA 95050. (408) 727-3628


**FREE** 1982 catalog; components, kits, P.C. board materials, enclosures. HAUCK ELECTRONICS, 1928 Fairacres Ave., Pittsburgh, PA 15216

**8085 SBC** COMPUTER. Bare board with manual \$40.00, monitor ROM \$20.00, both \$55.00, manual

\$7.50. Requires terminal, power supply. Send SASE for brochure. MINIMAL SYSTEMS, P.O. Box 1064-R, Acton, MA 01720

**36 CHANNEL CABLE CONVERTER FOR TV & VTR**

**\$29.95**  
6 or more 24.95 ea.

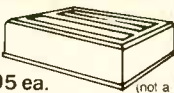

Call for free catalog 800-523-0721  
Spectrum Electronics, 5932 Market St., Phila., PA 19139

**MICROWAVE HORN ANTENNA KIT**

1.7-26 GHz Frequency Range 17-19 lb Gain Kit w/Assembly Instructions \$39.95\*  
Down Converter Board \$19.95\* (w/Antenna Kit \$14.95)  
Parts Kit for Board \$29.95\* (w/Antenna or Board \$24.95)  
COMPLETELY ASSEMBLED AND TESTED SYSTEM \$129.95 (including power supply and cabling)  
2.1 to 2.6 GHz Ant. - 34 db Gain (or greater)



**MICROTESSA ASSOCIATES**  
2335 South 2300 West, Salt Lake City, Utah 84119  
Check or M.O. only — Allow 2-4 Weeks Delivery (Cost includes shipping)  
\*Utah Residents Please Add 5% Sales Tax

**U.H.F.** TV descrambler—cheapest, most superior design on market. Approximately \$20 worth of readily available parts, your old B&W TV and a basic knowledge of electronics necessary. Plans \$5.00. RAMP ELECTRONICS, 1500 Venera Ave., Suite 2-D, Coral Gables, FL 33146

**SINE** wave decoder problems? Solve them with essential information including trouble shooting, alignment, antenna hook-up, improvements. Manual; \$15.00. SIGNAL PRESS, Box 25 12-R, Culver City, CA 90230

**TV educational** book. Most complete book available. Theory of encoding and decoding, schematics, parts layout, construction tips, trouble shooting, alignment, etc. Retro-fit, sine-wave, bandpass filter circuit. Audio output through your TV circuit. Much more. \$50 value, just \$19.95 plus \$2.50 shipping. Internal and external **EDUCATIONAL KITS** AVAILABLE. JIMCO, Box 40443RE, Cincinnati, OH 45240

**BRAINWAVE** kits control electronic speech. Music. Robots. Newsletter. Catalog \$3.00. ROSE AIRCRAFT, 269 Dahlia, I.B., CA 92032

**PROJECTION TV**...Convert your TV to project 7 foot picture. Results equal to \$2,500.00 projector. Total cost less than \$200.00. Plans & lens \$16.00. Illustrated information free. Credit card orders 24 hours. (215) 736-3979. MACROMGA, Washington Crossing, PA 18977

**MICROWAVE** television "downconverters." Introducing powerful new 5-stage design. Easily assembled. Catalog: \$2.00 (refundable). NDS, Box 12652-R, Dallas, 75225

**SUBSCRIPTION TV KITS**

**UHF Gated Pulse Kit**...\$39.00  
**UHF Sinewave Kit**...\$37.00

Kits include parts, manual and etched pc board.

**Informative Catalog**...\$2.00

**J & W ELECTRONICS**  
**P. O. BOX 61-B**  
**CUMBERLAND, RI. 02864**

**THEY TALK - YOU LISTEN!**

Improve your monitoring receivers with unique accessories. Preamps, descramblers, notch filters, active antennas, preselectors, multi-couplers, frequency lists, beam antennas and more.

**FREE CATALOG FREE**

GROVE ENTERPRISES, INC. Dept. J Brasstown, NC 28902

**74LS SERIES**

|       |     |       |      |       |      |
|-------|-----|-------|------|-------|------|
| LS00  | .24 | LS125 | .95  | LS243 | 1.79 |
| LS02  | .24 | LS138 | .75  | LS244 | .95  |
| LS04  | .24 | LS139 | .75  | LS245 | 1.89 |
| LS05  | .24 | LS151 | .75  | LS257 | .80  |
| LS08  | .24 | LS153 | .75  | LS266 | .49  |
| LS10  | .24 | LS154 | 1.75 | LS283 | .95  |
| LS14  | .89 | LS157 | .75  | LS290 | 1.20 |
| LS20  | .24 | LS161 | .95  | LS293 | 1.79 |
| LS27  | .24 | LS164 | .95  | LS298 | .99  |
| LS30  | .24 | LS166 | 1.95 | LS367 | .69  |
| LS32  | .36 | LS175 | .89  | LS368 | .69  |
| LS42  | .49 | LS181 | 1.99 | LS373 | .99  |
| LS74  | .44 | LS192 | .89  | LS374 | 1.69 |
| LS85  | .95 | LS193 | .89  | LS377 | 1.40 |
| LS86  | .39 | LS221 | 1.10 | LS390 | 1.79 |
| LS90  | .65 | LS240 | .95  | LS393 | 1.79 |
| LS109 | .39 | LS241 | .95  | LS399 | 1.59 |
| LS123 | .95 | LS242 | 1.79 | LS670 | 2.10 |

**ORDER TOLL FREE**

**(800) 538-8800**

**UPGRADE YOUR APPLE or TRS-80**  
4116 200ns  
8/12.95

**MICROPROCESSOR REAL-TIME CLOCK MSM 5832**  
7.25

|            |     |      |
|------------|-----|------|
| IC Sockets | ST  | W/W  |
| 8 PIN      | .10 | .49  |
| 14 PIN     | .12 | .50  |
| 16 PIN     | .15 | .57  |
| 18 PIN     | .20 | .85  |
| 20 PIN     | .25 | .99  |
| 22 PIN     | .25 | 1.30 |
| 24 PIN     | .25 | 1.40 |
| 28 PIN     | .35 | 1.50 |
| 40 PIN     | .40 | 1.80 |

ST = Solder tail  
W/W = Wirewrap

**Z80**  
Z80 A CPU 5.45  
Z80 A PIO 5.45  
Z80 A CTC 7.00

Call for Complete List

**6500**  
6502 6.90  
6502A 9.45  
6504 6.90  
6505 7.65  
6507 9.90  
6520 4.35  
6522 9.90  
6532 13.95  
6551 11.75

**DISKETTES 5 1/4"**  
ANTHANA SS SD Soft 23.95  
WABASH SS SD Soft 23.95  
VERBATIM SS SD Soft 28.95

**MISC.**

**Disc Controller**  
1771 20.95  
1791 34.95  
1793 34.95  
1797 49.95

**Uarts**

AY3-1014 5.85  
AY5-1013 3.90  
AY5-2376 12.00  
TR 1602 4.25

**Interface**

8T26 1.65  
8T28 1.95  
8T95 .95  
8T96 .95  
8T97 .95  
8T98 .95  
DM8131 2.90  
DS8836 1.25

**16K APPLE RAM CARD**

Upgrade your 48K Apple II to full 64K

BARE BOARD 29.95  
KIT 59.95  
ASSEMBLED & TESTED 79.95

**VISIT OUR RETAIL STORE AND RECEIVE A 5% DISCOUNT!**

**CRYSTALS**

|            |      |         |      |
|------------|------|---------|------|
| 32.768 KHZ | 3.75 | 5.185   | 3.90 |
| 1.0 MHZ    | 4.50 | 5.7143  | 3.90 |
| 1.8432     | 4.50 | 6.5536  | 3.90 |
| 2.0        | 3.90 | 8.0     | 3.90 |
| 2.097152   | 3.90 | 10.0    | 3.90 |
| 2.4576     | 3.90 | 14.3188 | 3.90 |
| 3.2768     | 3.90 | 18.0    | 3.90 |
| 3.579545   | 3.00 | 18.432  | 3.00 |
| 4.0        | 3.00 | 20.0    | 3.00 |
| 5.0        | 3.00 | 22.1184 | 3.00 |
| 5.0688     | 3.90 | 32.0    | 3.90 |

**CONNECTORS**

|        |        |      |
|--------|--------|------|
| RS 232 | Male   | 3.00 |
| RS 232 | Female | 3.50 |
| RS 232 | Hood   | 1.20 |

Call or write for prices on  
**8000, 6800, CMOS, Crystal, Linear, TTL, 74's.**

**ALL MERCHANDISE IS 100% GUARANTEED**

**EPROMS**

|        |            |      |
|--------|------------|------|
| 1702   | (1ns)      | 3.00 |
| 2708   | (45ns)     | 2.99 |
| 2716   | (5v 450ns) | 3.95 |
| 2716-1 | (5v 350ns) | 8.50 |
| 2532   | (5v 450ns) | 8.95 |
| 2732   | (5v 450ns) | 8.95 |
| 2764   | (5v 450ns) | Call |

**STATIC RAMS**

|         |            |       |
|---------|------------|-------|
| 2101    | (450ns)    | 1.85  |
| 21L02   | (250ns LP) | 1.55  |
| 2111    | (450ns)    | 2.49  |
| 2114    | (450ns)    | 1.95  |
| 2114L-3 | (300ns LP) | 2.25  |
| 2114L-2 | (200ns LP) | 2.30  |
| TMM2016 | (200ns)    | 9.00  |
| TMM2016 | (150ns)    | 11.00 |
| HM6116  | (200ns)    | Call  |
| HM6116  | (150ns)    | Call  |
| HM6116  | (120ns)    | Call  |

LP = Low Power

**DoKau** Computer Products, Inc.  
3250 Keller Street, #9  
Santa Clara, CA 95050  
(800) 538-8800  
Calif. Residents (408) 988-0697




**TERMS:** For shipping include \$2.00 for UPS Ground, \$3.00 for UPS Blue Label Air. \$10.00 minimum order. Bay Area residents add 6% Sales Tax. California residents add 6% Sales Tax. We reserve the right to limit quantities and substitute manufacturer. Prices subject to change without notice. Send SASE for complete list.

# ADVANCED COMPUTER PRODUCTS

SEND \$2.00 FOR 104 PAGE CATALOG

## 16K Apple™ Ramcard

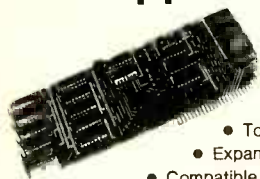

LIST 195 ACP \$74.95

- Full 1 year warranty
- Top quality — gold fingers
- Expand Apple II 48K to 64K
- Compatible with Z-80 Softcard™
- Allows system to run with CP/M™, PASCAL, DOS 3.3, COBAL, Visicalc, etc.
- Supplied with extra 16K RAM & has (2) LED's

## 32K STATIC RAM

2 or 4 MHz Expandable Uses 2114's

16K 4 MHz Kit \$159.95  
16K 4 MHz A&T \$217.95  
32K 4 MHz Kit \$199.95  
32K 4 MHz A&T \$289.95  
208/2716 EPROM \$339.00  
BARE BOARD \$39.95  
BareBrd/w/all parts less mem. \$9.95

## Astec RF Modulator

for COLOR & B/W

P/N 1082 Channel 3 or 4 \$6.95  
P/N 4151 UHF Channel 33 \$9.95

## BARE BOARDS

S-100 Sound Board \$34.95  
8080A CPU \$34.95  
32K Static RAM (2114) \$34.95  
9K EPROM (2708) \$24.95  
2708/2716 EPROM \$24.95  
ACP Proto Board \$22.95  
Vector 8800 Proto \$22.20  
Vector 8803 11 slot MB \$29.95  
ACP Extender w/connector \$18.95  
13 Slot Mother Board (WMC) \$32.95  
9 Slot Mother Board (WMC) \$29.95  
8 Slot Mother Bd (Expandable) \$34.95  
Floppy PCB (B) SHUGART \$39.95  
S-100 (A75-8910) Sound Board \$41.95  
Apple Sound Board \$24.95

## MOSTEK 4K RAMS

200,000 pieces in stock — priced to move.  
Same as MK402T except TMS retre-ih. MK4015 4Kx1 RAM. \$29¢ ea.

## PMI "Super Beta" LOW POWER AMPLIFIER

INTERNALLY COMPENSATED P/N OP12GJ

Voffset = 1.0 mV  
Ibias = 5.0mA  
Gain = 40V/mV  
(quantity limited)

## 4K STATIC RAM SELL-OFF

Same as TMS4044 but designed specifically for Z-80 based systems. This is a full-spec 4Kx1 RAM, 450ns On-Chip P/N Zig6104-4 while supply lasts.

8703 8 bit \$35.00  
8703 8 bit 12V \$35.00  
8703 8 bit 15V \$35.00  
8703 8 bit 18V \$35.00  
8703 8 bit 24V \$35.00  
8703 8 bit 30V \$35.00  
8703 8 bit 36V \$35.00  
8703 8 bit 42V \$35.00  
8703 8 bit 48V \$35.00  
8703 8 bit 54V \$35.00  
8703 8 bit 60V \$35.00  
8703 8 bit 66V \$35.00  
8703 8 bit 72V \$35.00  
8703 8 bit 78V \$35.00  
8703 8 bit 84V \$35.00  
8703 8 bit 90V \$35.00  
8703 8 bit 96V \$35.00  
8703 8 bit 102V \$35.00  
8703 8 bit 108V \$35.00  
8703 8 bit 114V \$35.00  
8703 8 bit 120V \$35.00  
8703 8 bit 126V \$35.00  
8703 8 bit 132V \$35.00  
8703 8 bit 138V \$35.00  
8703 8 bit 144V \$35.00  
8703 8 bit 150V \$35.00  
8703 8 bit 156V \$35.00  
8703 8 bit 162V \$35.00  
8703 8 bit 168V \$35.00  
8703 8 bit 174V \$35.00  
8703 8 bit 180V \$35.00  
8703 8 bit 186V \$35.00  
8703 8 bit 192V \$35.00  
8703 8 bit 198V \$35.00  
8703 8 bit 204V \$35.00  
8703 8 bit 210V \$35.00  
8703 8 bit 216V \$35.00  
8703 8 bit 222V \$35.00  
8703 8 bit 228V \$35.00  
8703 8 bit 234V \$35.00  
8703 8 bit 240V \$35.00  
8703 8 bit 246V \$35.00  
8703 8 bit 252V \$35.00  
8703 8 bit 258V \$35.00  
8703 8 bit 264V \$35.00  
8703 8 bit 270V \$35.00  
8703 8 bit 276V \$35.00  
8703 8 bit 282V \$35.00  
8703 8 bit 288V \$35.00  
8703 8 bit 294V \$35.00  
8703 8 bit 300V \$35.00  
8703 8 bit 306V \$35.00  
8703 8 bit 312V \$35.00  
8703 8 bit 318V \$35.00  
8703 8 bit 324V \$35.00  
8703 8 bit 330V \$35.00  
8703 8 bit 336V \$35.00  
8703 8 bit 342V \$35.00  
8703 8 bit 348V \$35.00  
8703 8 bit 354V \$35.00  
8703 8 bit 360V \$35.00

## UV "EPROM" ERASER

Model UVs-11E \$79.95  
Holds 4 EPROMs at a time.  
Model S-52T \$325.00

## 16K Memory Expansion Kits for Apple/TRS-80

8 pcs 4116 16K 200/250nS \$12.95  
Specify counter. CALL FOR VOLUME PRICING

## "D" SUB CONNECTORS

Unreal price. DB37 male, DB25 female. Gold PC mount with mounting holes. Mig AMP. Specify 25 or 37 pins.

BD37 \$2.50 DB25 \$1.95

## Stepper Motor

USED IN DATA PRODUCTS PRINTER \$19.95 ea.

## 12 VOLT BUZZER/HORN

2" DIAMETER ALL METAL \$2/\$1.99

## GE D43C3

PNP power HFE = 40-120 VCEO = 30 IC = 3A 6,000 pcs available \$69¢ ea.

## CONNECTORS

DB25P (RS232) \$3.25  
DB25S Female \$3.75  
Hood \$1.25  
Set with Hood, Sale \$7.50  
22/44 S/T, KIM \$2.95  
43/86 S/T, MOT \$6.50  
50/100 S-100 Connector W/W \$4.95  
50/100 S-100 Connector S/T \$3.95

## Full ASCII Encoded Keyboards

RCA 128-Character, 58-Key Typewriter Format for Alphabetic Entry \$99.00  
VP-806 Async serial output. Reg. \$99.00  
ACP SALE ... \$69.95

## MICROPROCESSORS

|       |         |        |         |       |        |
|-------|---------|--------|---------|-------|--------|
| Z8001 | \$39.00 | 8008-1 | \$14.95 | 8802P | 14.85  |
| Z8002 | 69.00   | 2901   | 9.90    | 8035  | 14.85  |
| Z80   | 9.95    | 2901A  | 14.95   | 8039  | 12.95  |
| Z80A  | 11.35   | 99001A | 48.95   | 4073N | 34.95  |
| 2650  | 8502    | 9.95   | 9.95    | 8785  | 48.85  |
| 2650  | 16.95   | 6502A  | 16.95   | 8748  | 49.95  |
| 1802  | 9.75    | IM6100 | 29.95   | 6809  | 30.00  |
| 8080A | 4.75    | 8000   | 19.95   | 8800  | 129.95 |
| 8085  | 14.95   | 8803S  | 9.95    | 8805  | 48.95  |

## RAMS

CALL FOR QTY PRICING

|           |         |      |        |       |        |
|-----------|---------|------|--------|-------|--------|
| 6116/2016 | \$7.95  | 2147 | \$5.99 | 5290  | \$1.99 |
| 8254-64K  | 8.50    | 411  | 5.99   | 5298  | 1.48   |
| 4116-2    | 1.99    | 414  | 4.63   | 6308  | 4.50   |
| 4116-2    | 8/12.95 | 1101 | 9.99   | 6518  | 6.79   |
| 2101      | 3.99    | 1103 | 9.99   | 6561  | 3.79   |
| 2102      | .79     | 4027 | 4.69   | 6604  | 3.99   |
| 21L02-2   | 1.49    | 4044 | 3.99   | 6605  | 7.99   |
| 21L02-4   | 1.29    | 4050 | 4.69   | 9140  | 8.99   |
| 2111      | 3.49    | 4050 | 4.69   | 9140  | 8.99   |
| 2112      | 3.49    | 4056 | 3.99   | 93415 | 6.99   |
| 2114      | 1.99    | 4115 | 1.49   | 93425 | 9.99   |
| 2114L-2   | 3.25    | 4200 | 7.95   |       |        |
| 2114L-4   | 2.29    | 4402 | 1.99   |       |        |
| 2125      | 6.99    | 5260 | 4.80   |       |        |

## UNIQUE

64K only \$8.50

|      |        |      |        |          |         |
|------|--------|------|--------|----------|---------|
| 8155 | \$9.95 | 8259 | \$8.95 | 68047    | \$22.95 |
| 8156 | 9.95   | 8275 | 19.95  | 68488    | 19.95   |
| 8202 | 29.95  | 8279 | 9.50   | 46505    | 22.95   |
| 8205 | 2.69   | 6810 | 4.75   | 65220    | 6.95    |
| 8213 | 4.95   | 6812 | 6.50   | 65222    | 8.95    |
| 8214 | 4.95   | 6821 | 6.50   | 6530-X   | 24.95   |
| 8216 | 2.75   | 6828 | 10.50  | 6532     | 17.95   |
| 8224 | 2.95   | 6834 | 16.95  | 6551     | 19.95   |
| 8226 | 2.95   | 6845 | 22.95  | Z80-PIO  | 6.50    |
| 8228 | 3.95   | 6847 | 27.95  | Z80-PIO  | 6.50    |
| 8243 | 6.95   | 6850 | 6.50   | Z80-CTC  | 6.50    |
| 8250 | 14.95  | 6852 | 5.25   | Z80A-CTC | 9.50    |
| 8251 | 6.50   | 6860 | 10.95  | Z80-DMA  | 19.95   |
| 8253 | 11.95  | 6862 | 10.95  | Z80-DMA  | 27.95   |
| 8255 | 4.50   | 8875 | 9.95   | Z80-SIO  | 24.95   |
| 8257 | 9.50   | 6880 | 2.49   | Z80A-SIO | 29.95   |

## MOS PROMS

|                   |         |              |        |
|-------------------|---------|--------------|--------|
| 2764 (8Kx8) TS    | \$69.95 | 2708 (450nS) | \$5.75 |
| 2732 (4Kx8) TS    | 12.95   | 2708 (60nS)  | 5.25   |
| 2716/2516, 6V     | 17.02A  | 5.75         |        |
| (28Kx8) TS        | 7.95    | MM5203AQ     | 14.50  |
| TMS52716, 6V, 12V | 17.95   | MM5204Q      | 9.95   |
| 2758, 5V, (450nS) | 3.50    |              |        |

## HI-TECH

|                         |        |                           |        |
|-------------------------|--------|---------------------------|--------|
| 2513-001 (5V) Upper     | \$9.50 | DAC08                     | \$9.95 |
| 2513-005 (5V) Lower     | 10.95  | DAC10                     | 9.95   |
| 2513-040 (5V) Lower     | 38.95  | 8038 Function Generator   | 4.50   |
| MCM65710 ASCII Shifted  | 12.95  | MC4024 VCO                | 2.95   |
| MCM66740 Math Symbol    | 13.95  | LM566 VCO                 | 1.95   |
| MCM66750 Alpha Counter  | 13.45  | XR2206 Function Generator | 5.25   |
| 1771-01 8" x MiniRoxy   | 24.95  | TR16028 (5V, 12V)         | 3.95   |
| 1781 Dual Floppy        | 29.95  | AT1510 (5V, 12V)          | 4.95   |
| 1791-01 Dual Floppy     | 38.95  | AV1014 (5V, 12V)          | 9.50   |
| 1791-02 Dual Floppy     | 44.95  | AV1014 (5V, 12V)          | 9.50   |
| 1793 DS Floppy          | 44.95  | IM6402                    | 7.95   |
| 1797 DS Floppy          | 54.95  | IM6403                    | 9.95   |
| 1691 Data Separator     | 18.95  | 2350 USRT                 | 8.95   |
| 2143 Control Generator  | 18.95  | 18718 Astable             | 24.95  |
| 8703 8 bit Binary       | 13.50  | MC4114                    | 11.95  |
| 8701 10 bit Binary      | 22.00  | 4702                      | 14.85  |
| 8703 8 bit TS           | 13.50  | WD1941                    | 19.95  |
| 9400 Volt to Freq Conv. | 7.25   | CD50516                   | 6.95   |
| 8750 3.5V Digi BCD      | 13.95  | IN82250                   | 15.95  |
| 14088 8 bit             | 3.95   | 18718 Astable             | 13.75  |
| 14088 8 bit             | 5.95   | AV5-3600                  | 10.95  |
| DA001 D to A            | 5.95   | MM570AAC                  | 8.95   |

## SOCKETS

|           |       |        |     |
|-----------|-------|--------|-----|
| 1-24      | 25-49 | 50-100 |     |
| 8 pin LP  | .16   | .15    | .14 |
| 14 pin LP | .22   | .21    | .20 |
| 18 pin LP | .29   | .28    | .27 |
| 20 pin LP | .34   | .32    | .31 |
| 22 pin LP | .39   | .37    | .36 |
| 24 pin LP | .48   | .47    | .46 |
| 28 pin LP | .65   | .64    | .63 |
| 40 pin LP | .80   | .79    | .78 |

## 3L WIREWRAP SOCKETS (GOLD)

|                 |      |      |      |
|-----------------|------|------|------|
| 8 pin WW        | .55  | .54  | .49  |
| 10 pin WW (Tin) | .65  | .63  | .58  |
| 14 pin WW       | .75  | .73  | .67  |
| 18 pin WW       | .90  | .77  | .70  |
| 18 pin WW       | .95  | .90  | .81  |
| 20 pin WW       | 1.15 | 1.08 | .99  |
| 22 pin WW       | 1.45 | 1.35 | 1.23 |
| 24 pin WW       | 1.35 | 1.28 | 1.14 |
| 28 pin WW       | 1.60 | 1.53 | 1.38 |
| 40 pin WW       | 2.20 | 2.09 | 1.89 |

## SUPER IC CLOSEOUT SPECIALS

|          |          |            |          |            |         |          |         |
|----------|----------|------------|----------|------------|---------|----------|---------|
| ULN2003  | 2/\$1.99 | 2N6121     | 3/\$1.00 | 8080A CPU  | 2.95    | 5027 CRT | \$9.95  |
| 74LS668  | 3/1.99   | SIG 2652   | 3.95     | 2102 RAM   | 7.75    | 11C74    | 6.95    |
| 74LS377  | 2/1.99   | 74S267     | 1.95     | 4060 RAM   | 1.45    | 9503     | 2.88    |
| 74ALS11  | 2/1.99   | 2758 EPROM | 2.95     | 8X300 CPU  | 14.95   | MM5320   | 5.99    |
| 8259     | 6.95     | 74173/81T0 | 5/1.99   | 74AS387    | 1.96    | 9131 RAM | 1.99    |
| 6861 RAM | 2.95     | Z80A CPU   | 4.95     | 2708 EPROM | 8/29.95 | EMM4402  | 1.99    |
| LM733CN  | 3/1.99   | 6522       | 6.95     | 74LS93     | 3/1.00  | 1103 RAM | 3/1.50  |
| MC1414   | 3/1.99   | 8502 CPU   | 5.95     | 2114       | 8/14.50 | 8700 A/D | 2/16.95 |

CP/M trademark of Digital Research. Apple trademark of Apple Computer.

TOLL FREE 800-854-8230 TWX 910-595-1565

## LINEAR

|            |        |           |        |
|------------|--------|-----------|--------|
| 78H05      | \$5.95 | LM1414N   | \$1.90 |
| 78M06      | 1.49   | LM1458C/N | 4.49   |
| 78M06      | 1.49   | MC1488N   | .99    |
| LM108AH    | 2.95   | MC1489N   | .39    |
| LM3001C    | .99    | LM1496N   | .89    |
| LM3041H    | .35    | LM1556N   | 1.50   |
| LM3055H    | 1.89   | LM1820N   | .95    |
| LM3055H    | 1.89   | LM1850N   | .95    |
| LM3058     | 3.25   | LM1899N   | 3.10   |
| LM3070N    | .29    | LM2111N   | 1.75   |
| LM308C     | .98    | LM2300N   | .98    |
| LM309K     | 1.49   | LM2901N   | 2.50   |
| LM310CN    | 1.25   | LM2917N   | 2.95   |
| LM312H/CN  | .89    | CA3013T   | 2.19   |
| LM312H     | 1.75   | CA3018T   | 1.86   |
| LM317T     | 1.70   | CA3021T   | 3.49   |
| LM318CN    | 1.49   | CA3023T   | 2.99   |
| LM319N/H   | 1.25   | CA3035T   | 2.75   |
| LM320K-XX* | 1.35   | CA3039T   | 1.29   |
| LM320T-XX* | 1.39   | CA3046N   | 1.29   |
| LM320H-XX* | 1.25   | LM3053N   | 1.49   |
| LM323K     | 4.95   | CA3059N   | 3.19   |
| LM324N     | .95    | CA3060N   | 3.19   |
| LM337K     | 6.95   | CA3062N   | 4.95   |
| LM338K     | 5.95   | LM3065N   | 1.49   |
| LM339N     | .95    | CA3080T   | 1.29   |
| LM340K-XX* | 1.75   | CA3081N   | 1.69   |
| LM342K-XX* | 1.25   | LM3082N   | 1.49   |
| LM344H     | 1.95   | CA3083N   | 1.55   |
| LM348N     | 1.20   | CA3086N   | .80    |
| LM350K     | 5.60   | CA3089N   | 2.99   |
| LM358CN    | 1.95   | CA3097N   | 1.99   |
| LM358N     | 1.49   | LM3101N   | 1.19   |
| LM372N     | 1.95   | CA3140T   | 1.19   |
| LM376N     | 3.75   | CA3146N   | 2.49   |
| LM377N     | 2.75   | CA3160T   | 1.19   |
| LM380C/N   | 1.25   | CA3190N   | 1.95   |
| LM381N     | 1.79   | CA3140N   | 5.99   |
| LM382N     | 1.95   | MC3429N   | 1.49   |
| LM386N     | 1.25   | MC3460N   | 3.95   |
| LM387N     | 1.40   | SG3524N   | 3.95   |
| LM390N     | 1.95   | CA3600N   | 3.39   |
| NE531T     | 3.75   | LM3900N   | .59    |
| NE555V     | .39    | LM3950N   | 1.19   |
| NE568N     | .98    | LM3908N   | .98    |
| NE561T     | 1.95   | LM3914N   | 3.75   |
| NE568H/V   | 1.25   | LM3915N   | 3.95   |
| NE567/V    | 1.50   | RC4131N   | 2.95   |
| NE582N     | 2.75   | RC4136N   | 2.95   |
| LM7070N    | 1.99   | RC4151N   | 3.70   |
| LM709N/H   | .29    | RC4194TK  | 4.95   |
| LM710N/H   | .75    | RC4195TK  | 5.40   |
| LM711N/H   | .39    | ULN2001   | 1.25   |
| LM715N     | 1.95   | ULN2003   | 1.50   |
| LM723N/H   | .65    | SN75450N  | .59    |
| LM733N/H   | .98    | SN75451N  | .35    |
| LM737N     | 1.15   | SN75452N  | .49    |
| LM741CN/H  | .33    | SN75453N  | .49    |
| LM741CN-14 | .19    | SN75454N  | .49    |

Latest microstrip model of the "original"  
**MICROWAVE TV SYSTEM KIT**

- LT-13 Down Converter with Preamp
- 16 dBi Slotted Antenna
- Deluxe Power Supply Kit
- All Coaxial Cables Included
- 2000 - 2600 MHz Tuning Range

**\$164.95**  
+ \$4.00 shipping



**LAB-TRONICS, INC.**  
P. O. Box 171  
Rogers, MN 55374  
612-428-4226

WRITE FOR  
**McGEE'S**  
**SPEAKER & ELECTRONICS CATALOG**

**1001 BARGAINS IN SPEAKERS**

Tel.: 1 (816) 842 5092  
1901 MCGEE STREET KANSAS CITY, MO. 64108

**FOR SALE**

**MICROWAVE receiver system.** Write: "Dealers Wanted," Dept. RE, POB 4181, Scottsdale, AZ 85258 (602) 941-9395.

**THE Intelligence Library.** Restricted technical secrets—books on electronic surveillance, lock-picking, demolitions, investigation, etc. Free brochures: MENTOR, Dept. Z, 135-53 No. Blvd., Flushing, NY 11354

**RESISTORS** 1/4W, 1/2W 5% carbon films 3¢ ea. **NO MINIMUMS.** Cabinet assortments, 1% metal films. Request details. Bulk pricing available. **JR INDUSTRIES** 5834-C Swancreek, Toledo, OH 43614

**SAVE up to 50% on name brand test equipment.** Free catalog and price list. **SALEN ELECTRONICS**, Box 82-G, Skokie, IL 60077

**CABLE TV converters, microwave antennas, cable parts, plans, parts and assembled units.** For information send \$2.00. **SAT-TECH P.O.** Box 10026, Cleveland, OH 44110

**32K color computers \$499.95.** Extended BASIC ROM's \$85.00. **SPECTRUM PROJECTS**, 93-15 86 Drive, Woodhaven, NY 11421

**UHF TV Yagi antennas.** Channels 14 to 70. MATV MFR's discount. Catalog 50 cents. **C.E.D.**, 24, High Range Rd., Londonderry, NH 03053

**PICTURE tube rebuilding equipment—we sell and buy new and used equipment.** Free training. **ATOLL TELEVISION**, 6425 Irving Park, Chicago, IL 60634, phone (312) 545-6667

**FREE KIT Catalog**

FUNCTION GENERATOR KIT \$59.95 contains TEST & EQUIP.  
Auto-Ranging Cap-meter kit \$79.95

Phone 415-447-3433  
Write or Phone for FREE CATALOG. MENTOR'S Average 1 minute Saturday call is 21¢.

**DAGE SCIENTIFIC INSTRUMENTS**  
BOX 1054R LIVERMORE CA 94550

**PROFESSIONAL** electronic devices, plans, kits, P.C. circuitry, famous drop in microphone cartridge, debugging equipment, more items available. For information send \$2.00: **MOUNTAIN ELECTRONICS**, R. 2, Box 186A, Charlotte, TN 37036

**OCTOPUS** circuit tester and oscilloscope with horizontal input troubleshoot circuits fast. Schematic \$1.50. **ADAMS G.F.**, 1070 Easton Rd. #6, Roslyn, PA 19001

**SUBSCRIPTION** television educational manual. Complete theory and circuits, \$9.95. Parts and kits available. **D & S ENTERPRISES**, PO Box 110901RE, Nashville, TN 37210

**PORTABLE** digital capacitor meter with 1% accuracy range 1 pf to 10,000 µF. Uses readily available CMOS IC's etched and drilled. PCB and plans \$14.95, calibration components included. **DRISCOLL ELECTRONICS**, 57 Scofield Ave., Bpt, CT 06605

**TESLA** coils: 100" arcs! Five plan manual \$15.00. Catalog \$1.00. **B&L SCIENTIFIC**, 215 West First, Suite 105-47RE, Tustin, CA 92680


**EDUCATION & INSTRUCTION**

**DISCOUNT** technical books, Sams, Hayden, TAB, and others, 15-30%, write **COMPUTERWARE**, Box 10070, San Jose, CA 95157

**UNIVERSITY** degrees by mail! Bachelors, Masters, Ph.D.'s...Free revealing details. **COUNSELING**, Box 317-RE9, Tustin, CA 92680

**ATTENTION ELECTRONIC TECHNICIANS**

Highly Effective Home Study BSEE Degree Program for Experienced Electronic Technicians  
Our New Advanced Placement Program grants Credit for previous Schooling & Professional Experience. Advance Rapidly! Our 36th Year!  
FREE DESCRIPTIVE LITERATURE!  
Cook's Institute of Electronics Engineering  
DESK 15, P.O. BOX 20345, JACKSON, MS 39209



**Be an FCC LICENSED Electronic Technician**

Earn up to \$600 a Week & More!  
No costly school — The Original FCC Tests  
Answers exam manual that prepares you at home for FCC General Radiotelephone License  
Newly revised multiple-choice exams cover all areas tested on the actual FCC Govt exam!  
No previous experience required. \$12.95 post-paid. Moneyback Guarantee.  
**COMMAND PRODUCTIONS**  
Dept. E P.O. Box 26348, San Francisco, CA 94126



**39.95** ADD \$2.50 FOR POSTAGE  
**30 CHANNEL CABLE TV CONVERTER**

**FREE!** UNUSUAL 96 PAGE ELECTRONIC PARTS & IDEAS CATALOG!

ORDER No. 171AE047  
**ETCO** ROUTE 9N, PLATTSBURGH, N.Y. 12901  
Tel.: (518) 561-8700



# VIDEO DISCOUNTS

**TEKNIKA WIRELESS REMOTE CONTROL TV TUNER**  
**\$110.00** ea.  
Model 6301



**REMOTE TV CONVERTER**  
Wireless Remote Control 40 Channels  
4 or more  
**139.95** ea. **125.00** ea.  
Model CTC5R



**36 CHANNEL UP CONVERTER FOR TV & VTR** Cable VHF to UHF  
Model V5736  
1-3 pieces **\$29.95** ea.  
4 pieces & up **\$24.95** ea.



**VIDEO SWITCHER**  
Model V 4801 **\$29.95** ea.  
Flip a switch to watch a program on any channel, while simultaneously recording a program on any cable or pay TV channel - or vice versa. Plus, you can use your recorder's programming feature to record TV programs while you're away.




**VIDEO CONTROL CENTER**  
ModelV 4802 **\$39.95** ea.  
Provides remote control access of all your Video, TV or Cable inputs to your TV set or Big Screen TV from one convenient location by merely flipping a switch.



**COAXIAL SWITCHING FOR TV VIDEO CASSETTE RECORDERS**  
Model AB-370 **\$6.95** ea.  
3-position coaxial push-button switch.



**COAX AB SWITCHES**  
Model AB-27 **\$2.95** ea.  
● Input: 75 ohm. ● Output: 75 ohm.



Model AB-28 **\$2.95** ea. Model AB-29 **\$2.95**  
● Input: 75 ohm. ● Input: 75 & 300 ohm.  
● Output: 300 ohm.

**ANTENNA/CABLE TV SWITCH**  
Model AB-400 **\$10.95** ea.



**ANTENNA/CABLE TV SWITCH**  
Model AB-410 **\$9.95** ea.  
● Switches from cable to antenna system instantly. ● Accepts 75 or 300 ohm inputs.




**TV GAME SWITCH**  
ModelV 450 **\$2.95**  
300 ohm in and out with RCA plug.



**COAXIAL SWITCH**  
Model DCS-A/B **\$7.95**  
A versatile product, with a range of consumer and MATV applications.




**VHF/FM AMPLIFIERS**  
Model 7002 **\$9.95** ea.  
● All solid state signal amplifier boosts weak signals. For 2 sets.




Model 7004 **\$12.95** ea.  
● For up to 4 sets ● Signal gain 3 dB



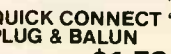**DISTRIBUTION AMPLIFIER VHF/UHF FM** With FM Trap  
Model DA-425 **\$29.95** ea.  
● Designed for TV/VCR multiple-set installations.



**QUICK CONNECT "F" PLUG & BALUN**  
ModelV 400 **\$1.50** ea.  
10 for \$12.50




**QUICK CONNECT "F" PLUG**  
ModelV 403 **.75**  
10 for \$6.00  
For 75 ohm cable. No wiring necessary.



**QUICK CONNECT "F" PLUG RG 59U**  
ModelV 4036 **\$2.50** ea.  
6 ft.



**VHF/UHF MATCHING TRANSFORMERS**  
Model MT-1 **\$.75** ea.  
10 for \$6.00  
VHF/UHF 75-300 ohm matching unit. Miniature size completely shielded and balanced for reduction of direct pick-up.



Model MT-2 **\$1.10** ea.  
10 for \$9.00  
Completely plastic molded construction for weather-proofing. Supplied with rubber boot.



**FORDHAM**  
855 Conklin St. Farmingdale, N.Y. 11735

Master Charge  
VISA  
COD  
Money Order  
Check  
\$25.00 minimum order  
COD's extra (requires 25% deposit)

N.Y. State residents add appropriate sales tax.

ADD FOR SHIPPING AND INSURANCE TO \$250.00 ..... \$ 4.50  
\$251.00 to 500.00 ..... 6.00  
501.00 to 750.00 ..... 8.50  
751.00 to 1000.00 ..... 12.00  
over 1000.00 ..... 12.50

**TOLL FREE (800) 645-9518**  
in N.Y. State call (516) 752-0050

RADIO-ELECTRONICS

### TTL 74LS SERIES

|         |     |          |     |          |      |           |      |          |      |
|---------|-----|----------|-----|----------|------|-----------|------|----------|------|
| 74LS00N | .21 | 74LS42N  | .44 | 74LS138N | .55  | 74LS191N  | .85  | 74LS283N | 84   |
| 74LS01N | .22 | 74LS47N  | .72 | 74LS139N | .79  | 74LS192N  | .74  | 74LS296N | 96   |
| 74LS02N | .24 | 74LS73N  | .35 | 74LS148N | 1.39 | 74LS193N  | .74  | 74LS348N | 1.65 |
| 74LS03N | .24 | 74LS74N  | .32 | 74LS151N | .43  | 74LS194N  | .74  | 74LS362N | 9.95 |
| 74LS04N | .25 | 74LS75N  | .45 | 74LS153N | .42  | 74LS192IN | .89  | 74LS365N | 5.9  |
| 74LS05N | .25 | 74LS112N | .66 | 74LS156N | .87  | 74LS240N  | 1.19 | 74LS366N | 5.9  |
| 74LS08N | .24 | 74LS85N  | .89 | 74LS157N | .48  | 74LS241N  | 1.19 | 74LS367N | 5.9  |
| 74LS09N | .25 | 74LS86N  | .35 | 74LS158N | .48  | 74LS242N  | 1.19 | 74LS368N | 5.9  |
| 74LS10N | .24 | 74LS90N  | .42 | 74LS160N | .79  | 74LS243N  | 1.19 | 74LS373N | 1.96 |
| 74LS11N | .28 | 74LS93N  | .58 | 74LS161N | .81  | 74LS244N  | 1.25 | 74LS374N | 1.36 |
| 74LS12N | .24 | 74LS93N  | .54 | 74LS163N | .69  | 74LS245N  | 1.95 | 74LS375N | .64  |
| 74LS13N | .36 | 74LS96N  | .72 | 74LS164N | .58  | 74LS251N  | .69  | 74LS377N | 1.25 |
| 74LS14N | .48 | 74LS107N | .42 | 74LS165N | .89  | 74LS252N  | .69  | 74LS378N | .96  |
| 74LS15N | .29 | 74LS117N | .96 | 74LS167N | .81  | 74LS254N  | .79  | 74LS380N | 1.36 |
| 74LS21N | .27 | 74LS122N | .45 | 74LS170N | 1.59 | 74LS255N  | 1.49 | 74LS393N | 1.44 |
| 74LS26N | .25 | 74LS123N | .69 | 74LS173N | .72  | 74LS266N  | .42  | 74LS447N | 8.9  |
| 74LS30N | .34 | 74LS125N | .49 | 74LS174N | .44  | 74LS273N  | 1.19 | 74LS862N | 1.68 |
| 74LS32N | .27 | 74LS132N | .45 | 74LS176N | .81  | 74LS279N  | .74  | 74LS670N | 1.36 |
| 74LS38N | .28 | 74LS133N | .49 | 74LS189N | 4.45 | 74LS280N  | 1.96 |          |      |

### MICRO COMPUTER SUPPORT CENTER STATIC RAM'S

|           |              |                               |       |
|-----------|--------------|-------------------------------|-------|
| P2016-20  | 16K (2K x 8) | 200NS 24 PIN                  | 9.95  |
| P2101-25  | 1K (256 x 4) | 250NS 22 PIN                  | 2.65  |
| P2102-25L | 1K (1K x 1)  | 250NS 16 PIN Low Power        | 1.59  |
| P2112-25  | 1K (256 x 4) | 250NS 16 PIN                  | 2.75  |
| P2114-20L | 4K (1K x 4)  | 200NS 18 PIN Low Power        | 2.45  |
| P2114-30L | 4K (1K x 4)  | 300NS 18 PIN Low Power        | 2.20  |
| P2147-055 | 4K (4K x 1)  | 55NS 18 PIN VERY SPECIAL      | 3.95  |
| P2149-045 | 4K (1K x 4)  | 45NS 18 PIN Ceramic           | 9.95  |
| P4315-45L | 4K (4K x 1)  | 45NS 18 PIN (CMOS) Low Power  | 4.95  |
| P5516-25L | 16K (2K x 8) | 250NS 24 PIN (CMOS) Low Power | 19.95 |
| P6116-15  | 16K (2K x 8) | 150NS 24 PIN (CMOS)           | 17.95 |
| P6116-20  | 16K (2K x 8) | 200NS 24 PIN (CMOS)           | 15.95 |
| P6514-45  | 4K (1K x 4)  | 45NS 18 PIN (CMOS)            | 4.65  |
| P6504-20  | 4K (4K x 1)  | 200NS 18 PIN (CMOS)           | 2.95  |

—SPECIAL—  
THE SIMPLE SOLUTION  
TO I.C. SELECTION  
1982 I.C. MASTER

- Deluxe 3500 Page 2-Volume Set
- 55,000 I.C. Devices
- 150 Manufacturers
- 2400 Complete Data Sheets from 62 Manufacturers

Regularly \$82.50  
Active's Super Low Price  
**\$49.95**

ACT NOW WHILE QUANTITIES LAST

### TTL 74F SERIES FAIRCHILD ADVANCED SCHOTTKY

The competition may be in short supply but ACTIVE HAS THE STOCK!

|         |      |          |      |          |      |          |      |
|---------|------|----------|------|----------|------|----------|------|
| 74F00PC | .96  | 74F109PC | 1.20 | 74F158PC | 2.36 | 74F258PC | 2.34 |
| 74F00N  | .96  | 74F111PC | .96  | 74F182PC | 3.20 | 74F352PC | 2.34 |
| 74F04PC | 1.11 | 74F138PC | 2.16 | 74F241PC | 4.30 | 74F353PC | 2.34 |
| 74F08PC | .96  | 74F139PC | 2.16 | 74F242PC | 5.25 | 74F373PC | 3.85 |
| 74F10PC | .96  | 74F157PC | 2.16 | 74F257PC | 2.34 | 74F534PC | 5.85 |

ACT NOW WHILE QUANTITIES LAST

### DYNAMIC RAM'S

|          |               |                            |       |
|----------|---------------|----------------------------|-------|
| P4050-30 | 4K (4K x 1)   | 300 NS 18 PIN              | 3.65  |
| P4060-30 | 4K (4K x 1)   | 300 NS 22 PIN              | 3.65  |
| C4116-20 | 16K (16K x 1) | 200 NS 16 PIN Ceramic      | 2.95  |
| P4116-20 | 16K (16K x 1) | 200 NS 16 PIN              | 1.95  |
| P4116-25 | 16K (16K x 1) | 250 NS 16 PIN VERY SPECIAL | 1.49  |
| P4164-15 | 64K (64K x 1) | 150 NS 16 PIN SPECIAL      | 15.95 |
| P4164-20 | 64K (64K x 1) | 200 NS 16 PIN              | 14.95 |

### OPTOELECTRONICS

#### L.E.D. Lamps

|         |                    |    |
|---------|--------------------|----|
| LED 209 | T-1 3mm Red        | 10 |
| LED 211 | T-1 3mm Green      | 19 |
| LED 212 | T-1 3mm Yellow     | 14 |
| LED 220 | T-1-3/4 5mm Red    | 11 |
| LED 222 | T-1-3/4 5mm Green  | 19 |
| LED 224 | T-1-3/4 5mm Yellow | 19 |

#### Displays

|  |       |
|--|-------|
| FND 357                                  | 1.29  |
| FND 500/TIL 322                          | 1.19  |
| FND 507/TIL 321A                         | 1.19  |
| DL 707/MAN 72                            | 1.05  |
| DL 1416 (4 Digit, 16 Segment Alpha Num.) | 24.95 |
| DL 2416 (4 Digit, 17 Segment Alpha Num.) | 27.95 |

#### Isolators

|             |           |
|-------------|-----------|
| ILD 74 1.49 | TL 111 51 |
| ILD 74 2.60 | 4N 26 51  |
| ILCT 2 1.85 | 4N 33 69  |
| MCT 2 .52   |           |

Refer to our previous AUGUST ad for other devices not listed here.

Active is your one stop source for the widest variety of electronic components. Contact us for devices not listed and for volume quotes.

Unless superceded next month, the prices will remain valid for 60 days.

### CMOS — CD4000 SERIES —

OVER 2 MILLION IN UNITS IN STOCK!  
PLASTIC AND CERAMIC AVAILABLE  
CHECK ACTIVE'S JULY AD FOR PRICES  
WE WON'T BE UNDERSOLD.

### EPROM'S

|                 |              |  |       |
|-----------------|--------------|--|-------|
| C2708-45        | 8K (1K x 8)  | 450NS 24 PIN                                     | 5.95  |
| C2716 / TMS2516 | 16K (2K x 8) | 450NS 24 PIN Single 5 Volt Supply, Intel Pin Out | 5.95  |
| C2516-35        | 16K (2K x 8) | 350NS 24 PIN Single 5V Supply, Intel Pin Out     | 6.95  |
| TMS2716         | 16K (2K x 8) | 450NS 24 PIN 3 Power Supply, T1 Pin Out          | 9.95  |
| C2532           | 32K (2K x 8) | 450NS 24 PIN T1 Pin Out                          | 12.80 |
| C2732           | 32K (4K x 8) | 450NS 24 PIN Intel Pin Out                       | 12.80 |

### UNGAR-PRINCESS LINE FOR MICRO SOLDERING

|      |                         |       |      |                         |       |
|------|-------------------------|-------|------|-------------------------|-------|
| 6976 | 10W, 3 Wire Iron        | 27.25 | 6960 | Pencil Nib, Plated      | 2.04  |
| 6990 | Solder Iron Holder      | 9.82  | 6961 | Screwdriver Nib, Plated | 2.04  |
| 6991 | Retil Sponge for Holder | 1.52  | 6962 | Spare Nib, Plated       | 2.04  |
| 6910 | 10W Heat Unit           | 12.58 | 6939 | Desolder Kit, 3 Tips    | 35.99 |
| 6915 | 15W Heat Unit           | 12.58 | 6943 | Desolder Tip, 60 DIA    | 6.05  |
| 6903 | 3-Wire Handle           | 15.05 | 6944 | Desolder Tip, 50 DIA    | 6.05  |
| 6950 | Pencil Nib, Copper      | 1.10  | 6945 | Desolder Tip, 375 DIA   | 6.05  |
| 6951 | Screwdriver Nib, Copper | 1.10  | 6946 | Desolder Tip, 180 DIA   | 6.05  |
| 6952 | Spade Nib, Copper       | 1.10  | 6947 | Desolder Tip, Slotted   | 4.40  |
| 6953 | Precision Nib, Plated   | 2.04  | 6982 | Dual-In-Line Extractor  | 5.40  |
|      |                         |       | 6983 | TDS Extractor           | 5.00  |

### LINEAR IC'S

|        |      |       |      |         |      |           |      |
|--------|------|-------|------|---------|------|-----------|------|
| 301ATC | .34  | 348PC | .99  | 7411C   | .28  | 3900PC    | 5.9  |
| 307TC  | .49  | 358TC | .49  | 7477PC  | .50  | 4138PC    | 8.8  |
| 308TC  | .59  | 380PC | 1.25 | 1458TC  | .29  | 4558TC    | .44  |
| 309KC  | 1.35 | 393TC | .49  | 1488PC  | .64  | N8726N    | 1.09 |
| 311TC  | .49  | 411PC | .27  | 1489APC | .64  | SN75477N  | 2.75 |
| 317KC  | 2.59 | 556PC | .58  | 2211PC  | 2.89 | SN76489N  | 7.39 |
| 317JC  | 1.59 | 567TC | .89  | 2240PC  | 1.89 | SN76489AN | 5.29 |
| 318TC  | 1.39 | 723PC | .45  | 308PC   | 1.29 | ULN2003AN | .99  |
| 323KC  | 4.50 | 725TC | 1.60 | 308APC  | .59  | ZX2100N   | 4.99 |
| 324PC  | .48  | 733PC | .79  | 330PC   | .69  | XR2206PC  | 3.75 |
| 339PC  | .48  | 741HC | .56  | 3403PC  | 1.79 |           |      |

KC = T03, UC = T020, HC = T05, TC = 8 PIN MINI DIP, N or PC = DUAL IN LINE IC

### BIPOLAR PROM'S

|              |          |                |        |       |
|--------------|----------|----------------|--------|-------|
| 6330/82S23   | 32 x 8   | Open Collector | 16 PIN | 2.45  |
| 6331/82S123  | 32 x 8   | Tristate       | 16 PIN | 2.45  |
| 93417/82S126 | 256 x 4  | Open Collector | 16 PIN | 2.45  |
| 93427/82S129 | 256 x 4  | Tristate       | 16 PIN | 2.45  |
| 27S29/28S42  | 512 x 8  | Tristate       | 20 PIN | 6.95  |
| 93453/82S137 | 1024 x 4 | Tristate       | 18 PIN | 5.95  |
| 93451/82S181 | 1024 x 8 | Tristate       | 24 PIN | 10.95 |
| 7128/27S185  | 2048 x 4 | Tristate       | 18 PIN | 13.95 |

### PLASTIC ENCLOSURES

by PAC TEC

| HEIGHT   | WIDTH | DEPTH | PRICE |
|----------|-------|-------|-------|
| CM5-125K | 1.50" | 5.08" | 18.90 |
| CM5-200K | 2.25" | 5.08" | 10.80 |
| CM6-225K | 2.50" | 6.06" | 12.30 |
| CM6-300K | 3.25" | 6.06" | 13.00 |

Available Colors: Black, Grey, Tan and Blue

### DIODES AND RECTIFIERS

| ZENER DIODES      | SWITCHING DIODES | RECTIFIERS |      |        |      |
|-------------------|------------------|------------|------|--------|------|
| IN746A - IN759A   | .12              | IN918A     | .035 | IN4001 | .05  |
| 400 MW            |                  | IN4148     | .035 | IN4002 | .06  |
| IN5224B - IN5252B | .13              | IN4149     | .035 | IN4003 | .07  |
| (500 MW)          |                  | IN4150     | .035 | IN4004 | .08  |
| IN4752A - IN4752A | .17              | IN4151     | .05  | IN4005 | .085 |
| (1 WATT)          |                  | IN4152     | .05  | IN4006 | .09  |
| IN4753A - IN4754A | .32              | IN4153     | .05  | IN4009 | .10  |
| (1 WATT)          |                  | IN4448     | .05  | IN4933 | 32   |
| IN5338B - IN5369B | .47              | IN4449     | .05  | IN4934 | 32   |
| (5 WATT)          |                  | IN4454     | .05  | IN4935 | 34   |
| IN5370B - IN5388B | .89              |            |      | IN4937 | 36   |
| (5 WATT)          |                  |            |      |        |      |

SPECIFY EXACT P/N OR VOLTAGE

### MICROPROCESSOR CHIP SETS

|             |                 |       |       |      |
|-------------|-----------------|-------|-------|------|
| 6500 FAMILY | 8080 FAMILY     |       |       |      |
| 6502 CPU    | 8035            | 5.45  | 8224  | 2.95 |
| 6520 CPU    | 8080A           | 4.65  | 8226  | 2.25 |
| 6522 VIA    | 8085A           | 6.95  | 8228  | 4.65 |
| 6532 RIOT   | 8086            | 34.95 | 8251  | 5.95 |
| 6551        | 8083 CPU (CMOS) | 11.25 | 8253  | 8.50 |
|             | 8155            | 9.00  | 8255  | 5.05 |
|             | 8212            | 2.25  | 8257  | 8.00 |
|             |                 |       | 8259A | 7.50 |

### 5% CARBON FILM RESISTORS

Available stock on all 5% standard values between 1 OHM and 9.1 MEG OHM. Multiples of 200 pcs. per value

|                      |         |
|----------------------|---------|
| 1/4 WATT             |         |
| Below 1000 pieces    | .05 ea. |
| 1000 pieces and more | .03 ea. |
| 1/2 WATT             |         |
| Below 1000 pieces    | .06 ea. |
| 1000 pieces and more | .04 ea. |

### D-SUBMINIATURE RS232 TYPE CONNECTORS AT MINIATURE PRICES

| NO. OF CONTACTS |         |
|-----------------|---------|
| 49-1109P        | 9 2.75  |
| 49-1109S        | 9 3.22  |
| 49-1115P        | 15 3.67 |
| 49-1115S        | 15 4.40 |
| 49-1125P        | 25 5.05 |
| 49-1125S        | 25 5.75 |
| 49-1137P        | 37 7.25 |
| 49-1137S        | 37 8.25 |

S = SOCKET, P = PLUG

### SCR'S and TRIAC'S

|         |                   |      |
|---------|-------------------|------|
| TIC45   | SCR 6 AMP 60V     | .54  |
| TIC47   | SCR 6 AMP 200V    | .69  |
| 2N5054  | SCR 8 AMP 200V    | .29  |
| TIC106D | SCR 5 AMP 400V    | 1.15 |
| TIC116D | SCR 8 AMP 400V    | 1.29 |
| TIC116E | SCR 8 AMP 500V    | 1.89 |
| TIC116M | SCR 8 AMP 600V    | 2.39 |
| TIC126D | SCR 12 AMP 400V   | 1.48 |
| TIC206D | Triac 3 AMP 400V  | .99  |
| TIC216E | Triac 6 AMP 200V  | 1.65 |
| TIC216D | Triac 6 AMP 400V  | 1.96 |
| TIC226D | Triac 8 AMP 400V  | 1.33 |
| TIC226E | Triac 8 AMP 500V  | 1.55 |
| TIC236D | Triac 12 AMP 400V | 1.95 |
| TIC246D | Triac 16 AMP 400V | 1.84 |
| TIC253D | Triac 25 AMP 400V | 2.79 |

### 6800 FAMILY

|           |       |
|-----------|-------|
| 6800 CPU  | 4.65  |
| 6802 CPU  | 7.95  |
| 6808 CPU  | 8.45  |
| 6809 CPU  | 13.95 |
| 6810 RAM  | 2.65  |
| 6821 PIA  | 2.65  |
| 6840      | 7.95  |
| 6845      | 16.50 |
| 6850 ACIA | 3.15  |
| 6852      | 4.85  |

### SPEECH EVALUATION BOARD LIMITED QUANTITY

PLUG IN YOUR OWN EPROM AND IT SAYS WHAT YOU WANT IT TO SAY

SPSB1001-01 \$159.95

### TELEDYNE 3 1/2 DIGIT A/D CONVERTERS

|         |                                |       |
|---------|--------------------------------|-------|
| 7106CPL | Interfaces with an LCD         | 12.95 |
| 7107CPL | Directly Drives an LED Display | 12.95 |
| 7116CPL | Auto Zero, Auto Polarity       | 13.75 |
| 7117CPL | Drives LED Display             | 13.75 |
| 7126CPL | Direct LCD Display Drive       | 12.95 |

### 8080 FAMILY

|           |       |
|-----------|-------|
| 6800 CPU  | 4.65  |
| 6802 CPU  | 7.95  |
| 6808 CPU  | 8.45  |
| 6809 CPU  | 13.95 |
| 6810 RAM  | 2.65  |
| 6821 PIA  | 2.65  |
| 6840      | 7.95  |
| 6845      | 16.50 |
| 6850 ACIA | 3.15  |
| 6852      | 4.85  |

### — SWITCHES —

|           |  |      |
|-----------|--|------|
| MTA-1060  | 6 AMP Toggle Switch, SPDT, ON NONE ON            | 1.30 |
| SLS-220   | Miniature Slide Switch, DPDT                     | 1.30 |
| DSS-10    | DIP Switch, 10 Position                          | 1.65 |
| MSPS-103C | Miniature Pushbutton Switch, Normally Open       | .65  |
| MSPS-103B | Miniature Pushbutton Switch, Normally Closed     | .65  |
| 35-375    | Rotary Switch, 6 Position, Shorting, 2 Poles     | 2.30 |
| 35-376    | Rotary Switch, 12 Position, Shorting, 1 Pole     | 2.30 |
| 35-377    | Rotary Switch, 5 Position, Non Shorting, 2 Poles | 2.30 |
| 35-378    | Rotary Switch, 3 Position, Non Shorting, 3 Poles | 2.30 |
| 35-379    | Rotary Switch, 4 Position, Shorting, 3 Poles     | 2.30 |
| 35-380    | Rotary Switch, 3 Position, Shorting, 4 Poles     | 2.30 |

### VOLTAGE REGULATORS

1 Amp Positive

|                        |      |
|------------------------|------|
| 78XXKC Series (T0-3)   | 1.29 |
| 78XXUC Series (T0-220) | .69  |

1 Amp Negative

|                        |      |
|------------------------|------|
| 79XXKC Series (T0-3)   | 1.49 |
| 79XXUC Series (T0-220) | .79  |

Available Voltages 5, 6, 8, 12, 15, 18, 24.

5 Amp Positive

|         |                   |      |
|---------|-------------------|------|
| 78H05SC | 5 Volts (T0-3)    | 6.95 |
| 78H125C | 12 Volts (T0-3)   | 7.95 |
| 78H65C  | Adjustable (T0-3) | 6.95 |

10 Amp Positive

|         |                |      |
|---------|----------------|------|
| 78P05SC | 5 Volts (T0-3) | 9.95 |
|---------|----------------|------|

### 6800 FAMILY

|           |       |
|-----------|-------|
| 6800 CPU  | 4.65  |
| 6802 CPU  | 7.95  |
| 6808 CPU  | 8.45  |
| 6809 CPU  | 13.95 |
| 6810 RAM  | 2.65  |
| 6821 PIA  | 2.65  |
| 6840      | 7.95  |
| 6845      | 16.50 |
| 6850 ACIA | 3.15  |
| 6852      | 4.85  |

“6800 SALE” - 10% DISCOUNT on \$100.00 or more order of 6800 Product

### ZILOG

|                |       |
|----------------|-------|
| Z80A-CPU(4MHZ) | 6.25  |
| Z80A-PIU       | 6.10  |
| Z80A-CTC       | 6.10  |
| Z80A-DMA       | 15.95 |

# KITS KITS KITS KITS KITS KITS

**ELECTRONIC KITS**  
We have one of the largest selections of inexpensive electronic kits (over 60 available!) and we have been providing quality kits for over 10 years to thousands of schools, hobbyists and engineers worldwide. Remember, all of our kits contain all parts and quality PC board (no need to buy the PC board extra). Compare our prices, extra features and complete parts. You just won't find any other kits that compare!

**ATTENTION DEALERS**  
We are looking for dealers to sell our line of kits. We provide liberal discounts and prices that beat any competition. Less than \$100 gets you started! Write or call for more information.

**NEW** **120VAC LIGHT SEQUENCER KIT**  
Great for discos, billboards, special effects, roof top Christmas displays, etc. This reliable IC and SCR kit sequences 10 outputs. The board has 10 output pads and each output pad can light up to 150 watts of 120VAC lamps (your choice) connected to it. Features variable speed and fused input. Kit comes with all parts, PC board and instructions. Size of board: 4" x 8". Operates from 120 VAC. C4725 \$19.95

**NEW** **10 NOTE SOUND SYNTHESIZER KIT**  
Very unique simple music synthesizer features 10 adjustable notes, variable pitch, variable speed, flashing LED and individual or flowing notes. Make "robot" sounds, space war computer effects, etc. One of the most unusual kits. Circuit features 3 IC's and 12 trimmer resistors. Complete with all parts, PC board and instructions. Size of board: 2.8" x 4". Operates from 9V battery (not included). C4723 \$19.95

**NEW** **ELECTRONIC SLOT MACHINE KIT**  
Realistic action slot machine features sound effects, digital readouts and flashing LED. Has 3 different symbols that "roll" and "come up" one at a time. When all symbols are the same a special winner note sounds. Circuit uses 7 IC's and 12 resistors. Kit comes complete with all parts, PC board and instructions. Size of board: 5.5" x 7". Operates from 9V battery (not included). C4723 \$29.95

**NEW** **ELECTRONIC DIGITAL DICE KIT**  
Fun and exciting—this kit replaces conventional dice. Features bright jumbo LEDs and "roll" sound. Speed of roll is fully adjustable and dice stop individually! Circuit uses 4 IC's and 10 resistors. Kit comes complete with all parts, PC board and instructions. Size of board: 4" x 4.8". Operates from 9V battery (not included). C4724 \$15.95

**CHANEY electronics inc.**  
P.O. BOX 27038  
DENVER, COLORADO 80227  
303-781-5750

Phone Orders: 303-781-575C  
Minimum AD Order \$9.00  
Please include \$1.50 for postage (UPS)  
VISA, MC accepted  
Phone orders are welcome  
Send for our free catalog of unique items

CIRCLE 101 ON FREE INFORMATION CARD

**Microwave TV antennas.** Best in the West! Rod disc type. Complete with cable, accessories, warranty, 52 dB \$125.00. Dealers wanted. GALAXY ELECTRONICS, 6007 N. 61st Ave., Glendale, AZ 85301 (602) 247-1151

**STAGGERED resistor assortment** 1/4W 5% common values 40 each. Less common 10 each. 500 total \$10.00 CI ELECTRONICS, P.O. Box 3034, Camarillo, CA 93010

**MAGIC TV machine.** Amateur microwave receivers, 1 yr. warranty, \$99.95. MICRO, Box 3123, Temple, AZ 85281. We repair most brands of amateur microwave receivers.

**MICROWAVE downconverters.** Also UHF subscription TV kits. Catalog 20c. TROJAN ENTERPRISES, 2920 Shelby, Indianapolis, IN 46203

**SCANNER/monitor accessories—kits and factory assembled.** Free catalog. CAPRI ELECTRONICS, Route 1R, Canon, GA 30520

**FREE speaker catalog!** Woofers, mids, tweeters, hardware, crossovers, grille cloth, plans, kits, information, much more. Discount prices. UNIVERSAL SOUND, Dept. RE, 2253 Ringling Blvd., Sarasota, FL 33577 (813) 953-5363

**POLICE fire scanners, scanner crystals, antennas, radar detectors.** HPR, Box 19224, Denver, CO 80219

**TRS-80 mod 3 cassette programs** 16K mail-list and inventory list. \$14.00 each, \$20.00 both. Write SUN MERCHANDISE COMPANY, Dept. RE-1, 1739 Embassy Drive, Jacksonville, FL 32207

**CABLE TV Secrets—the outlaw publication** the cable companies tried to ban. HBO, Movie Channel, Showtime, descramblers, converters, etc. Suppliers list included. Send \$7.95 to CABLE FACTS, Box 711-R Pataskala, OH 43062

**LIQUIDATING \$100,000 inventory:** speaker comes, gaskets, voice coils, spiders; also finished speakers, 50% - 75% below cost. Free list: ISE, 355 Cowan Terrace W, Brownsville, TX 78521

**ANYTHING electronic located fast.** Reliable service, details \$1.00 SASE. W.K.M. 212 N. Milford Ave., Baltimore, MD 21224

## SUPER SALE

**EPROM's**

|                  |        |        |      |
|------------------|--------|--------|------|
| 2716 (5V, 450ns) | \$3.95 | \$3.55 | CALL |
| 2732 (5V, 450ns) | 7.85   | 6.95   | CALL |
| 2532 (5V, 450ns) | 11.20  | 9.25   | CALL |

**STATIC RAM**

|                 |      |      |      |
|-----------------|------|------|------|
| 6116P-3 (150ns) | 7.50 | 7.20 | CALL |
| 2114L-2 (200ns) | 2.10 | 1.70 | CALL |

**DYNAMIC RAM**

|              |      |      |      |
|--------------|------|------|------|
| 4164 (200ns) | 7.90 | 7.49 | CALL |
|--------------|------|------|------|

**MISC**

CPU Z80A ..... \$5.29 ea.  
CDP-1854ACE (UART) ..... \$4.80 ea.  
16K RAM Expansion Kit  
for TRS-80 Mod III ..... \$12.95/8

**SUNTRONCS CO., INC.**  
12621 CRENSHAW BOULEVARD  
HAWTHORNE, CALIFORNIA 90250

STORE HOURS: Mon-Fri, 10am to 6:30pm - Sat 10am to 5pm  
IN CALIFORNIA OUTSIDE CALIFORNIA TOLL FREE  
(213) 644-1149 1-800-421-5775  
Min Order: \$10, P/H: \$2, Accept VISA, Mastercard, Check or M.O.

**LATEST in video accessories!!** Free shipping in U.S.A. Catalog \$1.00. ELECTRONICS ET-CETERA, P.O. Box 826-L, Solvang, CA 93463

**MINI FM MIC**  
Compact size, only 2" x 1" x 3/4". Transmit to FM radio 88-108 MHz. Exceptional audio quality. Transmits stable signal up to 900 ft. Complete kit incl. case, battery & instructions. Only \$13.95. Assembled \$18.95. Add \$1.55 S&H ea. Send 20c stamp for brochure.

S.E. Corp., Box 1132-RE  
Yorba Linda, CA 92686

### COMPUTERS ATARI® 800™ COMPUTER SYSTEM

400w/16K \$350.00  
800w/16K \$699.00

\*800 Computer w/48K  
★BEST BUY★ \$825.00

**ATARI PERIPHERALS:**

|                       |                      |         |
|-----------------------|----------------------|---------|
| Printer '82E - 6500*  | Asteroids            |         |
| Disk Dr '81E - 4850** | Missile Com          | > 32.50 |
| Record '41C - 8200*   | Sup. Brk. Out        |         |
| Paddle (pr) > 16.95   | Assem. Edit - 4900   |         |
| Joystick (pr) > 16.95 | Star Raiders - 4500* |         |
| 32K RAM - 179.95      | Basketball - 2800*   |         |
| Basic Cart - 4900*    | Chess - 3200*        |         |

Pac-Man → \$36.95

**Diskette Storage BOX**  
→ HARD PLASTIC ←

5 1/4 inch → \$2.95ea. (SRW)

8 inch → \$4.75ea. ☆

**Bare Bones APPLE II**

w/o Keyboard = 48K RAM = \$450.  
w/o Pwr. Supply

|              |               |                 |
|--------------|---------------|-----------------|
| Microswitch: | Power Supply: | APPLE           |
| Keyboard:    | 5amp.:        | Reference Manl. |
| \$79.95      | \$124.00      | \$18.00         |

**\* SPECIALS**

3inch Mini FAN → \$8.95

2111 → \$2.45  
8155 → \$11.50  
ER2501 → \$4.95  
AY5 1013A → \$2.95

8202 → \$29.95  
6522 → \$5.25

2716(+5V) → \$4.50  
2732 → \$8.95

8255 → \$5.95  
8748-8 → \$31.00  
MC6800 → \$7.75  
MC6802 → \$14.95  
MC6850 → \$4.50  
MC6821 → \$4.95

8 Pos. DIP SWITCH \$1.35ea.  
'1982' IC MASTER 2 Vois. \$59.95

**Diskette SALE!!**  
"Wabash"

|               |         |
|---------------|---------|
| 5 1/4         | 8inch   |
| SS/SD \$22.00 | \$25.00 |
| SS/DD 27.40   | 30.40   |
| DS/SD 0       | 34.90   |
| DS/DD 32.40   | 37.40   |

## CONCORD COMPUTER PRODUCTS

1971 SO STATE COLLEGE ANAHEIM, CALIF. 92806  
(714) 937-0637  
CHECK - M/O  
NO COD  
\$10. MIN. ORDER. CA RES ADD 6%

**FREIGHT MONITORS**

**ZENITH # ZVM-121**  
12in. 15MHz./GREEN Phos. \$113.00

**J.C.S.#KG-12**  
12in. 19MHz./GREEN Phos. Non-Glare Screen \$134.50

**BMC#BM-12A**  
12in. 15MHz./GREEN Phos. \$95.00

**AMDEK#CM-13 (COLOR I)**  
13in./COLOR!! \$375.00

### COMPONENTS

|            |             |              |             |
|------------|-------------|--------------|-------------|
| 74LS00 .24 | 74LS83 .70  | 74LS165 .85  | 8126 1.20   |
| 74LS02 .24 | 74LS86 .38  | 74LS174 .85  | 8128 1.20   |
| 74LS03 .24 | 74LS90 .60  | 74LS190 1.25 | 8130 2.75   |
| 74LS04 .24 | 74LS91 .85  | 74LS192 .85  | 8080A 3.75  |
| 74LS05 .24 | 74LS92 .85  | 74LS193 .85  | 8155 10.50  |
| 74LS06 .30 | 74LS93 .60  | 74LS194 .85  | MC1300 1.50 |
| 74LS08 .24 | 74LS95 .80  | 74LS195 .85  | MC1350 1.15 |
| 74LS10 .24 | 74LS96 .38  | 74LS196 .85  | MC1386 1.40 |
| 74LS11 .33 | 74LS97 .38  | 74LS197 .85  | MC1458 .55  |
| 74LS12 .24 | 74LS98 .38  | 74LS198 .85  | LM380 1.10  |
| 74LS13 .24 | 74LS99 .38  | 74LS200 .85  | MC1488 1.00 |
| 74LS14 .89 | 74LS100 .40 | 74LS201 .85  | MC1489 .95  |
| 74LS15 .24 | 74LS101 .40 | 74LS202 .85  | 8212 1.95   |
| 74LS16 .24 | 74LS102 .40 | 74LS203 .85  | 8216 1.80   |
| 74LS17 .24 | 74LS103 .40 | 74LS204 .85  | 1103A .95   |
| 74LS18 .24 | 74LS104 .40 | 74LS205 .85  |             |
| 74LS19 .24 | 74LS105 .40 | 74LS206 .85  |             |
| 74LS20 .30 | 74LS106 .40 | 74LS207 .85  |             |
| 74LS21 .24 | 74LS107 .40 | 74LS208 .85  |             |
| 74LS22 .30 | 74LS108 .40 | 74LS209 .85  |             |
| 74LS23 .30 | 74LS109 .40 | 74LS210 .85  |             |
| 74LS24 .30 | 74LS110 .40 | 74LS211 .85  |             |
| 74LS25 .30 | 74LS111 .40 | 74LS212 .85  |             |
| 74LS26 .30 | 74LS112 .40 | 74LS213 .85  |             |
| 74LS27 .30 | 74LS113 .40 | 74LS214 .85  |             |
| 74LS28 .30 | 74LS114 .40 | 74LS215 .85  |             |
| 74LS29 .30 | 74LS115 .40 | 74LS216 .85  |             |
| 74LS30 .30 | 74LS116 .40 | 74LS217 .85  |             |
| 74LS31 .30 | 74LS117 .40 | 74LS218 .85  |             |
| 74LS32 .30 | 74LS118 .40 | 74LS219 .85  |             |
| 74LS33 .30 | 74LS119 .40 | 74LS220 .85  |             |
| 74LS34 .30 | 74LS120 .40 | 74LS221 .85  |             |
| 74LS35 .30 | 74LS121 .40 | 74LS222 .85  |             |
| 74LS36 .30 | 74LS122 .40 | 74LS223 .85  |             |
| 74LS37 .30 | 74LS123 .40 | 74LS224 .85  |             |
| 74LS38 .30 | 74LS124 .40 | 74LS225 .85  |             |
| 74LS39 .30 | 74LS125 .40 | 74LS226 .85  |             |
| 74LS40 .30 | 74LS126 .40 | 74LS227 .85  |             |
| 74LS41 .30 | 74LS127 .40 | 74LS228 .85  |             |
| 74LS42 .30 | 74LS128 .40 | 74LS229 .85  |             |
| 74LS43 .30 | 74LS129 .40 | 74LS230 .85  |             |
| 74LS44 .30 | 74LS130 .40 | 74LS231 .85  |             |
| 74LS45 .30 | 74LS131 .40 | 74LS232 .85  |             |
| 74LS46 .30 | 74LS132 .40 | 74LS233 .85  |             |
| 74LS47 .30 | 74LS133 .40 | 74LS234 .85  |             |
| 74LS48 .30 | 74LS134 .40 | 74LS235 .85  |             |
| 74LS49 .30 | 74LS135 .40 | 74LS236 .85  |             |
| 74LS50 .30 | 74LS136 .40 | 74LS237 .85  |             |

**74S SERIES**

|          |             |
|----------|-------------|
| 74S00 35 | 74S86 1.10  |
| 74S02 38 | 74S128 1.45 |
| 74S03 38 | 74S132 1.10 |
| 74S04 45 | 74S138 .96  |
| 74S05 65 | 74S140 1.25 |
| 74S06 38 | 74S148 1.25 |
| 74S07 55 | 74S174 .95  |
| 74S08 55 | 74S175 .95  |
| 74S09 55 | 74S181 4.00 |
| 74S10 55 | 74S182 2.75 |
| 74S11 55 | 74S186 3.50 |
| 74S12 55 | 74S190 3.50 |
| 74S13 55 | 74S200 3.50 |
| 74S14 55 | 74S201 3.50 |
| 74S15 55 | 74S202 3.50 |
| 74S16 55 | 74S203 3.50 |
| 74S17 55 | 74S204 3.50 |
| 74S18 55 | 74S205 3.50 |
| 74S19 55 | 74S206 3.50 |
| 74S20 55 | 74S207 3.50 |
| 74S21 55 | 74S208 3.50 |
| 74S22 55 | 74S209 3.50 |
| 74S23 55 | 74S210 3.50 |
| 74S24 55 | 74S211 3.50 |
| 74S25 55 | 74S212 3.50 |
| 74S26 55 | 74S213 3.50 |
| 74S27 55 | 74S214 3.50 |
| 74S28 55 | 74S215 3.50 |
| 74S29 55 | 74S216 3.50 |
| 74S30 55 | 74S217 3.50 |

**EPROMS**

|           |       |             |
|-----------|-------|-------------|
| 1702      | 2.25  | 8/3 95 ea.  |
| 2708      | 2.95  | 8/2 65 ea.  |
| 2716 (5V) | 5.00  | 8/4 50 ea.  |
| 2732 (5V) | 11.50 | 8/8 20 ea.  |
| 2732 (5V) | 10.50 | 8/8 25 ea.  |
| 2732 (5V) | 11.50 | 8/10 25 ea. |

**VOLTAGE REGULATORS**

|      |       |      |            |      |      |      |      |      |      |
|------|-------|------|------------|------|------|------|------|------|------|
| 7805 | 7808  | 7812 | 7818       | 7824 | 7828 | 7830 | 7836 | 7840 | 7845 |
| 4027 | 200ns | 2.00 | 8/175 ea.  |      |      |      |      |      |      |
| 4184 | 200ns | 9.50 | 8/1300 ea. |      |      |      |      |      |      |

**STATIC RAMS**

|        |       |             |             |
|--------|-------|-------------|-------------|
| 2111   | 2.85  | 8/2 50 ea.  |             |
| 2112   | 2.85  | 8/2 50 ea.  |             |
| 2114   | 2.00  | 4/14 00 ea. |             |
| 2114L  | 200ns | 2.25        | 4/2 00 ea.  |
| 4M6116 | 200ns | 11.50       | 4/10 50 ea. |

**NO P.O. BOX SHIPMENTS**

RADIO-ELECTRONICS

CIRCLE 81 ON FREE INFORMATION CARD



**ramsey**

# the first name in Counters!



## 9 DIGITS 600 MHz \$129<sup>95</sup> WIRED

**PRICES:**

|                                      |          |
|--------------------------------------|----------|
| CT-90 wired, 1 year warranty         | \$129.95 |
| CT-90 Kit, 90 day parts warranty     | 109.95   |
| AC-1 AC adapter                      | 3.95     |
| BP-1 Nicad pack + AC Adapter/Charger | 12.95    |
| OV-1, Micro-power Oven time base     | 49.95    |
| External time base input             | 14.95    |

The CT-90 is the most versatile, feature packed counter available for less than \$300.00! Advanced design features include: three selectable gate times, nine digits, gate indicator and a unique display hold function which holds the displayed count after the input signal is removed! Also, a 10MHz TCXO time base is used which enables easy zero beat calibration checks against WWV. Optionally, an internal nicad battery pack, external time base input and Micro-power high stability crystal oven time base are available. The CT-90, performance you can count on!

**SPECIFICATIONS:**

Range: 20 Hz to 600 MHz  
 Sensitivity: Less than 10 MV to 150 MHz  
 Less than 50 MV to 500 MHz  
 Resolution: 0.1 Hz (10 MHz range)  
 1.0 Hz (60 MHz range)  
 10.0 Hz (600 MHz range)  
 Display: 9 digits 0.4" LED  
 Time base: Standard-10.000 mHz, 1.0 ppm 20-40°C  
 Optional Micro-power oven-0.1 ppm 20-40°C  
 Power: 8-15 VAC @ 250 ma

## 7 DIGITS 525 MHz \$99<sup>95</sup> WIRED



**SPECIFICATIONS:**

Range: 20 Hz to 525 MHz  
 Sensitivity: Less than 50 MV to 150 MHz  
 Less than 150 MV to 500 MHz  
 Resolution: 1.0 Hz (5 MHz range)  
 10.0 Hz (50 MHz range)  
 100.0 Hz (500 MHz range)  
 Display: 7 digits 0.4" LED  
 Time base: 1.0 ppm TCXO 20-40°C  
 Power: 12 VAC @ 250 ma

The CT-70 breaks the price barrier on lab quality frequency counters. Deluxe features such as, three frequency ranges - each with pre-amplification, dual selectable gate times, and gate activity indication make measurements a snap. The wide frequency range enables you to accurately measure signals from audio thru UHF with 1.0 ppm accuracy - that's .0001%! The CT-70 is the answer to all your measurement needs, in the field, lab or ham shack.

**PRICES:**

|                                      |         |
|--------------------------------------|---------|
| CT-70 wired, 1 year warranty         | \$99.95 |
| CT-70 Kit, 90 day parts warranty     | 84.95   |
| AC-1 AC adapter                      | 3.95    |
| BP-1 Nicad pack + AC adapter/charger | 12.95   |

## 7 DIGITS 500 MHz \$79<sup>95</sup> WIRED



**PRICES:**

|  |         |
|--|---------|
| MINI-100 wired, 1 year warranty        | \$79.95 |
| AC-Z Ac adapter for MINI-100           | 3.95    |
| BP-Z Nicad pack and AC adapter/charger | 12.95   |

Here's a handy, general purpose counter that provides most counter functions at an unbelievable price. The MINI-100 doesn't have the full frequency range or input impedance qualities found in higher price units, but for basic RF signal measurements, it can't be beat! Accurate measurements can be made from 1 MHz all the way up to 500 MHz with excellent sensitivity throughout the range, and the two gate times let you select the resolution desired. Add the nicad pack option and the MINI-100 makes an ideal addition to your tool box for "in-the-field" frequency checks and repairs.

**SPECIFICATIONS:**

Range: 1 MHz to 500 MHz  
 Sensitivity: Less than 25 MV  
 Resolution: 100 Hz (slow gate)  
 1.0 KHz (fast gate)  
 Display: 7 digits, 0.4" LED  
 Time base: 2.0 ppm 20-40°C  
 Power: 5 VDC @ 200 ma

## 8 DIGITS 600 MHz \$159<sup>95</sup> WIRED



**SPECIFICATIONS:**

Range: 20 Hz to 600 MHz  
 Sensitivity: Less than 25 mv to 150 MHz  
 Less than 150 mv to 600 MHz  
 Resolution: 1.0 Hz (60 MHz range)  
 10.0 Hz (600 MHz range)  
 Display: 8 digits 0.4" LED  
 Time base: 2.0 ppm 20-40°C  
 Power: 110 VAC or 12 VDC

The CT-50 is a versatile lab bench counter that will measure up to 600 MHz with 8 digit precision. And, one of its best features is the Receive Frequency Adapter, which turns the CT-50 into a digital readout for any receiver. The adapter is easily programmed for any receiver and a simple connection to the receiver's VFO is all that is required for use. Adding the receiver adapter in no way limits the operation of the CT-50, the adapter can be conveniently switched on or off. The CT-50, a counter that can work double-duty!

**PRICES:**

|   |          |
|---|----------|
| CT-50 wired, 1 year warranty                                    | \$159.95 |
| CT-50 Kit, 90 day parts warranty                                | 119.95   |
| RA-1, receiver adapter kit                                      | 14.95    |
| RA-1 wired and pre-programmed (send copy of receiver schematic) | 29.95    |



## DIGITAL MULTIMETER \$99<sup>95</sup> WIRED

**PRICES:**

|                                       |         |
|---------------------------------------|---------|
| DM-700 wired, 1 year warranty         | \$99.95 |
| DM-700 Kit, 90 day parts warranty     | 79.95   |
| AC-1, AC adaptor                      | 3.95    |
| BP-3, Nicad pack + AC adapter/charger | 19.95   |
| MP-1, Probe kit                       | 2.95    |

The DM-700 offers professional quality performance at a hobbyist price. Features include: 26 different ranges and 5 functions, all arranged in a convenient, easy to use format. Measurements are displayed on a large 3 1/2 digit, 1/2 inch LED readout with automatic decimal placement, automatic polarity, overrange indication and overload protection up to 1250 volts on all ranges, making it virtually fool-proof! The DM-700 looks great, a handsome, jet black, rugged ABS case with convenient retractable tilt bail makes it an ideal addition to any shop.

**SPECIFICATIONS:**

DC/AC volts: 100uV to 1 KV, 5 ranges  
 DC/AC current: 0.1 uA to 2.0 Amps, 5 ranges  
 Resistance: 0.1 ohms to 20 Megohms, 6 ranges  
 Input impedance: 10 Megohms, DC/AC volts  
 Accuracy: 0.1% basic DC volts  
 Power: 4°C cells

### AUDIO SCALER

For high resolution audio measurements, multiplies UP in frequency.

- Great for PL tones
- Multiplies by 10 or 100
- 0.01 Hz resolution!

\$29.95 Kit \$39.95 Wired

### ACCESSORIES

|  |         |
|--|---------|
| Telescopic whip antenna - BNC plug                                       | \$ 7.95 |
| High impedance probe, light loading                                      | 15.95   |
| Low pass probe, for audio measurements                                   | 15.95   |
| Direct probe, general purpose usage                                      | 12.95   |
| Tilt bail, for CT 70, 90, MINI-100                                       | 3.95    |
| Color burst calibration unit, calibrates counter against color TV signal | 14.95   |

### COUNTER PREAMP

For measuring extremely weak signals from 10 to 1,000 MHz. Small size, powered by plug transformer-included.

- Flat 25 db gain
- BNC Connectors
- Great for sniffing RF with pick-up loop

\$34.95 Kit \$44.95 Wired

**ramsey electronics, inc.**

2575 BAIRD RD. • PENFIELD, NY 14526

PHONE ORDERS  
 CALL 716-586-3950

**TERMS**

Satisfaction guaranteed - examine for 10 days, if not pleased return in original form for refund. Add 5% for shipping insurance to a maximum of \$10. Overseas add 15%. COD add \$2. Orders under \$10. add \$1.50. NY residents, add 7% tax.

CIRCLE 72 ON FREE INFORMATION CARD

**CUSTOM** electronic manufacturing, prototype, short production run. **DAUS ELECTRONICS**, P.O. Box 831, Angier, NC 27501

**RECORDS**—tapes! Discounts to 73%; all labels; no purchase obligations; newsletter; discount dividend certificates; 100% guarantees. Free details. **DISCOUNT MUSIC CLUB**, 650 Main Street, PO Box 2000, Dept. 3-0782, New Rochelle, NY 10801

**DESCRAMBLERS** gated pulse sinewave, transmitters, sniffers, bugfoiler, lineals, scramblers, schematics, boards, kits. Catalog \$2.00. **M&M ELECTRONICS**, Box 252, Crompond, NY 10517

**SUPER-buy:** microwave receiving systems, converters, satellite TVRO. Large selection of best quality products. Lowest prices anywhere. Free information. Catalog \$3.00. Satisfaction guaranteed. **TCE**, Box 343, Dept. R, Brooklyn, NY 11230

**USA** subscription—TV stations (MDS) brochure. Latest and most complete information: exact tower locations, programming, equipment, ownership and more. Send \$10.00 to **TCE**, Box 343, Dept. R, Brooklyn, NY 11230

**TEKTRONIX** and HP 30 MHz used oscilloscope \$200.00. (714) 985-9967.

**POWER-AMP** sub-assemblies, 100 watts rms. .05% distortion, completely assembled and tested, quantity pricing available, free brochure. **CLAXTON AUDIO**, 3174 Periwinkle, Memphis, TN 38127

### WANTED

Ideas, inventions, new products wanted for presentation to industry. Call free 1-800-528-6050. Arizona 1-800-352-0458. X831.

### UHF CONVERTERS

**DELUXE** sine wave UHF converter. Sound out of TV like normal with only antenna connection to TV or VCR. Kits \$175.00 (312) 267-3455. **LSR ENGINEERING**, Box 6075, Chicago, IL 60680

### REEL TO REEL TAPES

**TRUCKLOAD** sale, Ampex high quality open reel tape, 1800' or 2400' on 7" reels, used once, unboxed. Case of 40, \$45.00. Cassettes available. **VALTECH ELECTRONICS**, Box 6-RE, Richboro, PA 18954

### COMMUNICATIONS EQUIPMENT

**DECODE** Morse, radioteletype signals from airwaves with CODE\*STAR reader. Kit \$169.95, wired \$229.95. Shipping \$5.00. **MICROCRAFT**, Box 513R, Thiensville, WI 53092 (414) 241-4654

### POWER SUPPLIES

**LABORATORY** quality 5-volt, 12-volt, tri-voltage supply for Op-Amps, IC's, Microprocessors. Kit \$69.95. Wired \$89.95. Shipping \$4.00. **MICROCRAFT**, Box 513R, Thiensville, WI 53092. (414) 241-8144

### FIBEROPTICS

**ANALOG** photo receiver. Beautiful sine, square, triangle reproduction. 10 μs response (2.0 kHz). Complete manual including analog LEDxmttr schematic. \$27.50 + \$2.25 P&H. Req. case and P.S. C. **CLEARWATERS**, 2074 Wallace Ave., #604, Bronx, NY 10462

### ARTWORK

**ARTWORK**, professional quality, fast turn around. Call or write today for more information or quote: **ELECTRONIC COMMUNICATION ENG.**, PO Box 18725, Greensboro, NC 27419. Phone (919) 299-9772

### COMPUTER PROGRAMS

**WIN \$**, dog race program. TRS-80 M/III, color, pocket specify \$25.00. **PAUL PICKS**, PO Box 244, Lutz, FL 33549

### PROGRAMS


**INFINITE TAX TABLE** for handheld computers. TRS-80, Sharp, etc. Fit & Fica any amount of wages, dependants or pay periods. Well documented, including options. Send \$5.95. **ENERGY CONTROL SYSTEMS**, Box 1396, Gretna, LA 70053 (504) 362-2090

### CB RADIO

**GET** more CB channels and range! Frequency expanders, boosters, speech processors, FM converters, PLL/slider tricks, how-to books, plans, modifications. Catalog \$2.00. **CB CITY**, Box 31500RE, Phoenix, AZ 85046

**Help Prevent Birth Defects – The Nation's Number One Child Health Problem.**

Support the

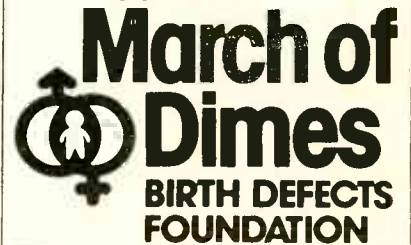

# SURPLUS ITEMS!

We're closing out our parts business to concentrate on the **CompuPro** line of high performance computers. Remaining parts listed below are limited quantity, first come/first served. Counts approximate (+5%). No phone orders, no partial orders. Use this ad as order blank, or photocopy ad.

### DELUXE 12V CLOCK NOW ON SPECIAL!

For cars, vans, planes, boats, or houses using alternate DC power, National's MA1003 is the finest looking, most readable 12V DC clock module we've ever seen. Includes four blue/green fluorescent 0.3" readouts that are more pleasing to the eye, and more readable, than LEDs or LCDs; brightness control option; "dim-when-headlights-on" option for automotive applications; and sample application note.

These have sold elsewhere for up to \$19.95. Our price: \$8.95 each, 2/\$17.95, or if you're looking for real value, 10/\$59.95! Take advantage now of the one of the best clock module deals on the market.

### CAPACITORS

|                      |        |
|----------------------|--------|
| 1000 uF/35V, axial   | 40/\$5 |
| 500 uF/15V, axial    | 50/\$5 |
| 2200 uF/16V pc mount | 35/\$5 |
| 1000 uF/16V          | 50/\$5 |
| 220 uF/25V pc mount  | 50/\$5 |
| 1000 uF/150V         | 25/\$5 |
| 10,000 uF/10V axial  | 25/\$5 |

### TRANSISTORS

|                       |           |
|-----------------------|-----------|
| MPS3694 NPN           | 1000/\$35 |
| 2N4400 NPN 1/4" leads | 2000/\$70 |
| 2N5227 PNP            | 1000/\$35 |
| 2N4917 PNP            | 2000/\$70 |
| FPQ3725 quad xistors  | 50/\$5    |

### LOW PROFILE SOCKETS

|        |        |
|--------|--------|
| 8 pin  | 50/\$5 |
| 14 pin | 50/\$5 |
| 16 pin | 50/\$5 |
| 18 pin | 40/\$5 |
| 20 pin | 35/\$5 |

### LINEAR ICs

|                  |        |
|------------------|--------|
| LM301            | 30/\$5 |
| LM741            | 50/\$5 |
| LM733            | 50/\$5 |
| LM380            | 30/\$5 |
| LM556            | 25/\$5 |
| LM703            | 25/\$5 |
| uA706            | 20/\$5 |
| uA723            | 25/\$5 |
| Lm1458           | 20/\$5 |
| CA3080           | 10/\$5 |
| 4195TK           | 20/\$5 |
| LM7806 + 6 reg   | 10/\$5 |
| LM7808 + 8V reg  | 10/\$5 |
| LM7815 + 15V reg | 10/\$5 |
| LM7818 + 18V reg | 10/\$5 |
| LM7824 + 24V reg | 10/\$5 |
| LM7906 -6V reg   | 10/\$5 |
| LM7908 -8V reg   | 10/\$5 |
| LM7915 -15V reg  | 10/\$5 |
| LM7918 -18V reg  | 10/\$5 |
| LM7924 -24V reg  | 10/\$5 |

### CMOS

|      |        |
|------|--------|
| 4010 | 40/\$4 |
| 4015 | 40/\$5 |
| 4016 | 50/\$5 |
| 4019 | 40/\$5 |
| 4022 | 40/\$5 |
| 4023 | 60/\$6 |
| 4025 | 50/\$5 |
| 4028 | 60/\$5 |
| 4030 | 50/\$5 |
| 4040 | 20/\$5 |
| 4069 | 50/\$5 |
| 4071 | 50/\$5 |
| 4073 | 50/\$5 |
| 4075 | 50/\$5 |
| 4093 | 50/\$5 |
| 4116 | 50/\$5 |
| 4507 | 50/\$5 |
| 4512 | 50/\$5 |

### ODDS AND ENDS

|   |        |
|---|--------|
| Misc. pots - some funny shafts, some duals, some singles, no time to select                                   | 35/\$5 |
| 250 Ohm trim pots   | 50/\$5 |
| 500 Ohm   | 50/\$5 |
| 25A/50V diode bridges   | 5/\$5  |
| Dynamic mic originally designed for Cartrivision with extension cable (miniplug male and female); stereo pair | 5/\$5  |
| Extension cable as above  | 5/\$5  |
| Stereo amps with LM380s and pots. May even work!  | 2/\$5  |
| 15 MHz crystal oscillator in small can  | 2/\$5  |
| Colorburst crystal 3.58 MHz   |        |
| 1 MHz HC-6 crystal  | 5/\$5  |

**GODBOUT**  
ELECTRONICS

OAKLAND AIRPORT, CA 94614-0355

Send the coupon below to **Bill Godbout Electronics**, RE Parts Sale, PO Box 2355 Oakland Airport, CA 94614-0355.

Please send the parts circled above to (PLEASE PRINT OR TYPE):

Name \_\_\_\_\_

Street Address (necessary for UPS delivery) \_\_\_\_\_

Town \_\_\_\_\_ State \_\_\_\_\_ ZIP \_\_\_\_\_

Subtotal for parts: \_\_\_\_\_

Californians add tax \$ \_\_\_\_\_

Handling (strike out for orders over \$25) \$ 2.00

Postage (allow 5%, excess refunded) \$ \_\_\_\_\_

TOTAL \$ \_\_\_\_\_

CIRCLE 82 ON FREE INFORMATION CARD

# DIGI-KEY CORPORATION

In. M., Ak., Hi. Call 218-681-6674

**NATIONAL SEMICONDUCTOR • PANASONIC • QUALITY - Name brand products from nationally recognized manufacturers.**  
**ARIES • PLESSEY • MOLEX • AAYD • BISHOP GRAPHICS • J. OK MACHINE • LINGAR • GC CHEMICALS • SERVICE - Computerized order processing and inventory control.**  
**WISA • MICONDUCTOR • PANASONIC • SAVINGS - Volume Discounts • OEM Quantity Pricing • Toll Free 800 Number.**  
**CHEMICALS • ARIES • PLESSEY • MOLEX • E MACHINE • DIAMOND TOOL • LINGAR • GC CH INSTRUMENTS • ITI • A PRODUCTS • DIA IND TOOL • LINGAR • GC CHEMICALS • ARIES** **master charge**  
**CHEMICALS • ARIES • PLESSEY • MOLEX • E**

## INTEGRATED CIRCUITS

| Part No. | 15 Pin TTL | 28 Pin TTL | 40 Pin TTL | 84 Pin TTL |
|----------|------------|------------|------------|------------|
| 7400     | 25         | 150        | 250        | 1500       |
| 7401     | 25         | 150        | 250        | 1500       |
| 7402     | 25         | 150        | 250        | 1500       |
| 7500     | 25         | 150        | 250        | 1500       |

## TEXAS INSTRUMENTS I.C. SOCKETS

| Part No. | 15 Pin TTL | 28 Pin TTL | 40 Pin TTL | 84 Pin TTL |
|----------|------------|------------|------------|------------|
| 2834     | 25         | 150        | 250        | 1500       |
| 2835     | 25         | 150        | 250        | 1500       |
| 2836     | 25         | 150        | 250        | 1500       |
| 2837     | 25         | 150        | 250        | 1500       |
| 2838     | 25         | 150        | 250        | 1500       |
| 2839     | 25         | 150        | 250        | 1500       |
| 2840     | 25         | 150        | 250        | 1500       |
| 2841     | 25         | 150        | 250        | 1500       |
| 2842     | 25         | 150        | 250        | 1500       |
| 2843     | 25         | 150        | 250        | 1500       |
| 2844     | 25         | 150        | 250        | 1500       |
| 2845     | 25         | 150        | 250        | 1500       |
| 2846     | 25         | 150        | 250        | 1500       |
| 2847     | 25         | 150        | 250        | 1500       |
| 2848     | 25         | 150        | 250        | 1500       |
| 2849     | 25         | 150        | 250        | 1500       |
| 2850     | 25         | 150        | 250        | 1500       |
| 2851     | 25         | 150        | 250        | 1500       |
| 2852     | 25         | 150        | 250        | 1500       |
| 2853     | 25         | 150        | 250        | 1500       |
| 2854     | 25         | 150        | 250        | 1500       |
| 2855     | 25         | 150        | 250        | 1500       |
| 2856     | 25         | 150        | 250        | 1500       |
| 2857     | 25         | 150        | 250        | 1500       |
| 2858     | 25         | 150        | 250        | 1500       |
| 2859     | 25         | 150        | 250        | 1500       |
| 2860     | 25         | 150        | 250        | 1500       |
| 2861     | 25         | 150        | 250        | 1500       |
| 2862     | 25         | 150        | 250        | 1500       |
| 2863     | 25         | 150        | 250        | 1500       |
| 2864     | 25         | 150        | 250        | 1500       |
| 2865     | 25         | 150        | 250        | 1500       |
| 2866     | 25         | 150        | 250        | 1500       |
| 2867     | 25         | 150        | 250        | 1500       |
| 2868     | 25         | 150        | 250        | 1500       |
| 2869     | 25         | 150        | 250        | 1500       |
| 2870     | 25         | 150        | 250        | 1500       |
| 2871     | 25         | 150        | 250        | 1500       |
| 2872     | 25         | 150        | 250        | 1500       |
| 2873     | 25         | 150        | 250        | 1500       |
| 2874     | 25         | 150        | 250        | 1500       |
| 2875     | 25         | 150        | 250        | 1500       |
| 2876     | 25         | 150        | 250        | 1500       |
| 2877     | 25         | 150        | 250        | 1500       |
| 2878     | 25         | 150        | 250        | 1500       |
| 2879     | 25         | 150        | 250        | 1500       |
| 2880     | 25         | 150        | 250        | 1500       |
| 2881     | 25         | 150        | 250        | 1500       |
| 2882     | 25         | 150        | 250        | 1500       |
| 2883     | 25         | 150        | 250        | 1500       |
| 2884     | 25         | 150        | 250        | 1500       |
| 2885     | 25         | 150        | 250        | 1500       |
| 2886     | 25         | 150        | 250        | 1500       |
| 2887     | 25         | 150        | 250        | 1500       |
| 2888     | 25         | 150        | 250        | 1500       |
| 2889     | 25         | 150        | 250        | 1500       |
| 2890     | 25         | 150        | 250        | 1500       |
| 2891     | 25         | 150        | 250        | 1500       |
| 2892     | 25         | 150        | 250        | 1500       |
| 2893     | 25         | 150        | 250        | 1500       |
| 2894     | 25         | 150        | 250        | 1500       |
| 2895     | 25         | 150        | 250        | 1500       |
| 2896     | 25         | 150        | 250        | 1500       |
| 2897     | 25         | 150        | 250        | 1500       |
| 2898     | 25         | 150        | 250        | 1500       |
| 2899     | 25         | 150        | 250        | 1500       |
| 2900     | 25         | 150        | 250        | 1500       |

## 3 AMP SILICON RECTIFIER




Price includes container and shipping. See our catalog for more information.

## IT RECTIFIERS



Price includes container and shipping. See our catalog for more information.

## IT SILICON ZENER DIODES

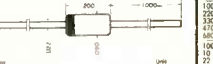

Price includes container and shipping. See our catalog for more information.

## 150 CAPACITORS

Price includes container and shipping. See our catalog for more information.

## PANASONIC LS Series Miniature Aluminum Electrolytic CAPACITORS

| Value  | Part No. | Price |
|--------|----------|-------|
| 1000µF | 1000     | 1.00  |
| 500µF  | 500      | 0.75  |
| 220µF  | 220      | 0.50  |
| 100µF  | 100      | 0.35  |
| 50µF   | 50       | 0.25  |
| 22µF   | 22       | 0.18  |
| 10µF   | 10       | 0.13  |
| 5µF    | 5        | 0.09  |
| 2.2µF  | 2.2      | 0.06  |
| 1µF    | 1        | 0.04  |
| 0.5µF  | 0.5      | 0.03  |
| 0.22µF | 0.22     | 0.02  |
| 0.1µF  | 0.1      | 0.01  |

## NEW! KIT

Price includes container and shipping. See our catalog for more information.

## PANASONIC POLYESTER CAPACITORS

| Value  | Part No. | Price |
|--------|----------|-------|
| 1000µF | 1000     | 1.00  |
| 500µF  | 500      | 0.75  |
| 220µF  | 220      | 0.50  |
| 100µF  | 100      | 0.35  |
| 50µF   | 50       | 0.25  |
| 22µF   | 22       | 0.18  |
| 10µF   | 10       | 0.13  |
| 5µF    | 5        | 0.09  |
| 2.2µF  | 2.2      | 0.06  |
| 1µF    | 1        | 0.04  |
| 0.5µF  | 0.5      | 0.03  |
| 0.22µF | 0.22     | 0.02  |
| 0.1µF  | 0.1      | 0.01  |

## NEW! KIT

Price includes container and shipping. See our catalog for more information.

## PANASONIC METALLIZED POLYESTER CAPACITORS

| Value  | Part No. | Price |
|--------|----------|-------|
| 1000µF | 1000     | 1.00  |
| 500µF  | 500      | 0.75  |
| 220µF  | 220      | 0.50  |
| 100µF  | 100      | 0.35  |
| 50µF   | 50       | 0.25  |
| 22µF   | 22       | 0.18  |
| 10µF   | 10       | 0.13  |
| 5µF    | 5        | 0.09  |
| 2.2µF  | 2.2      | 0.06  |
| 1µF    | 1        | 0.04  |
| 0.5µF  | 0.5      | 0.03  |
| 0.22µF | 0.22     | 0.02  |
| 0.1µF  | 0.1      | 0.01  |

## MOLEX I.C. SOCKET PINS

| Part No. | Price |
|----------|-------|
| MOX100   | 1.00  |
| MOX200   | 2.00  |
| MOX300   | 3.00  |
| MOX400   | 4.00  |
| MOX500   | 5.00  |
| MOX600   | 6.00  |
| MOX700   | 7.00  |
| MOX800   | 8.00  |
| MOX900   | 9.00  |
| MOX1000  | 10.00 |
| MOX1100  | 11.00 |
| MOX1200  | 12.00 |
| MOX1300  | 13.00 |
| MOX1400  | 14.00 |
| MOX1500  | 15.00 |
| MOX1600  | 16.00 |
| MOX1700  | 17.00 |
| MOX1800  | 18.00 |
| MOX1900  | 19.00 |
| MOX2000  | 20.00 |

## TEXAS INSTRUMENTS GOLD EDGEBOARD CONNECTORS

| Part No. | Price |
|----------|-------|
| TEI100   | 1.00  |
| TEI200   | 2.00  |
| TEI300   | 3.00  |
| TEI400   | 4.00  |
| TEI500   | 5.00  |
| TEI600   | 6.00  |
| TEI700   | 7.00  |
| TEI800   | 8.00  |
| TEI900   | 9.00  |
| TEI1000  | 10.00 |
| TEI1100  | 11.00 |
| TEI1200  | 12.00 |
| TEI1300  | 13.00 |
| TEI1400  | 14.00 |
| TEI1500  | 15.00 |
| TEI1600  | 16.00 |
| TEI1700  | 17.00 |
| TEI1800  | 18.00 |
| TEI1900  | 19.00 |
| TEI2000  | 20.00 |

## SILICON TRANSISTORS

| Part No. | Price |
|----------|-------|
| 2N3638   | 0.25  |
| 2N3639   | 0.25  |
| 2N3640   | 0.25  |
| 2N3641   | 0.25  |
| 2N3642   | 0.25  |
| 2N3643   | 0.25  |
| 2N3644   | 0.25  |
| 2N3645   | 0.25  |
| 2N3646   | 0.25  |
| 2N3647   | 0.25  |



7400

\*Number of Pins of each I.C. for easy Socket purchase

MICROPROCESSOR COMPONENTS

\*Evaluation Kits



Table with columns: Part No., Price, Part No., Price, Part No., Price. Lists various microprocessors like SN7400N, SN7401N, SN7402N, etc.

STATIC RAMS

Table with columns: Part No., Price, Part No., Price, Part No., Price. Lists static RAMs like 1101, 2101, 2102, etc.

DYNAMIC RAMS

Table with columns: Part No., Price, Part No., Price, Part No., Price. Lists dynamic RAMs like 1103, 4103, 4104, etc.

FUNCTION

Table with columns: Part No., Price, Part No., Price, Part No., Price. Lists various functional ICs like 70A51PI, 70A52V, etc.

74LS

Table with columns: Part No., Price, Part No., Price, Part No., Price. Lists 74LS series components like 74LS00, 74LS01, etc.

EPROMS

Table with columns: Part No., Price, Part No., Price, Part No., Price. Lists EPROMs like 1702A, 2708, etc.

PROMS

Table with columns: Part No., Price, Part No., Price, Part No., Price. Lists PROMs like 74S18, 74S19, etc.

ROM'S

Table with columns: Part No., Price, Part No., Price, Part No., Price. Lists ROMs like 2513 (2140), 2513 (3071), etc.

MICROPROCESSOR CHIPS

Table with columns: Part No., Price, Part No., Price, Part No., Price. Lists microprocessor chips like Z80 (7803), 80C86, etc.

NMOS LOGIC MEMORY

Table with columns: Part No., Price, Part No., Price, Part No., Price. Lists NMOS logic memory like MC66107P, MC66107, etc.

DATA ACQUISITION

Table with columns: Part No., Price, Part No., Price, Part No., Price. Lists data acquisition components like DC10, MC3470, etc.

MICROPROCESSOR MANUALS

Table with columns: Part No., Price, Part No., Price, Part No., Price. Lists microprocessor manuals like M-282, M-CDP1802, etc.

6800/6800 SUPPORT DEVICES

Table with columns: Part No., Price, Part No., Price, Part No., Price. Lists 6800/6800 support devices like MC6802CP, MC6801AP, etc.

74C-C/MOS

Table with columns: Part No., Price, Part No., Price, Part No., Price. Lists 74C-C/MOS components like 74C02, 74C03, etc.

8080/8080A SUPPORT DEVICES

Table with columns: Part No., Price, Part No., Price, Part No., Price. Lists 8080/8080A support devices like INS8081, DR214, etc.

SPECIAL FUNCTION

Table with columns: Part No., Price, Part No., Price, Part No., Price. Lists special function components like DS90C02CN, DS90C02CN, etc.

LINEAR

Table with columns: Part No., Price, Part No., Price, Part No., Price. Lists linear components like LM0002CN, LM1001L, etc.

TELEPHONE/KEYBOARD CHIPS

Table with columns: Part No., Price, Part No., Price, Part No., Price. Lists telephone/keyboard chips like AV-59200, AV-59200, etc.

TELEPHONE/KEYBOARD CHIPS

Table with columns: Part No., Price, Part No., Price, Part No., Price. Lists telephone/keyboard chips like AV-59200, AV-59200, etc.

50 VOLT CERAMIC DISC CAPACITORS

Table with columns: Value, Price, Value, Price. Lists 50V ceramic disc capacitors like 22pF, 47pF, etc.

74S/PROM'S

Table with columns: Part No., Price, Part No., Price, Part No., Price. Lists 74S/PROM'S components like 74S02, 74S03, etc.

25 Pin - D Subminiature (meets RS232)

Table with columns: Part No., Price, Part No., Price, Part No., Price. Lists 25-pin D subminiature components like DR25P, DR25P, etc.

Solder Eylet/Wire Wrap Edge Card

Table with columns: Part No., Price, Part No., Price, Part No., Price. Lists solder eyelet/wire wrap edge cards like AV-59200, AV-59200, etc.

CAPACITOR CORNER

Table with columns: Value, Price, Value, Price. Lists capacitor corner components like 100V MYLAR film capacitors, 50V tantalum capacitors, etc.

CA-LINEAR

Table with columns: Part No., Price, Part No., Price, Part No., Price. Lists CA-linear components like CA3010H, CA3010H, etc.

IC SOCKETS

Table with columns: Part No., Price, Part No., Price, Part No., Price. Lists IC sockets like 25 Pin - D Subminiature, etc.

CD-CMOS

Table with columns: Part No., Price, Part No., Price, Part No., Price. Lists CD-CMOS components like CD4000, CD4001, etc.

WIRE WRAP (IC) SOCKETS

Table with columns: Part No., Price, Part No., Price, Part No., Price. Lists wire wrap (IC) sockets like 8 pin LP, 14 pin LP, etc.

MINI ALUMINUM ELECTROLYTIC CAPACITORS

Table with columns: Value, Price, Value, Price. Lists mini aluminum electrolytic capacitors like 100µF, 220µF, etc.

LOW PROFILE (TIN) SOCKETS

Table with columns: Part No., Price, Part No., Price, Part No., Price. Lists low profile (tin) sockets like 8 pin LP, 14 pin LP, etc.

Spec Sheets - 25c each

Spec Sheets - 25c each. FREE 88c Postage for your FREE 1982 JAMECO CATALOG. Prices Subject to Change.

\$10.00 Minimum Order - U.S. Funds Only

\$10.00 Minimum Order - U.S. Funds Only. California Residents Add 6 1/2% Sales Tax. Postage - Add 5% plus \$1.00 Insurance. Send S.A.S.E. for Monthly Sale Flyer!

Jameco Electronics logo and address: 1355 SHOREWAY ROAD, BELLMONT, CA 94002. PHONE ORDERS WELCOME - (415) 592-8097

CIRCLE 69 ON FREE INFORMATION CARD

### JE600 Hexadecimal Encoder Kit

FULL 8-BIT LATCHED OUTPUT 19-KEY KEYBOARD

The JE600 Encoder Keyboard Kit provides two separate hexadecimal digits produced from sequential key entries to allow direct programming for 8-bit microprocessor or 8-bit memory circuits. Three additional keys are provided for user operations with one having a bistable output available. The outputs are latched and monitored with 9 LED readouts. Also included is a key entry strobe. Features: Full 8-bit latched output for microprocessor use. Three user-define keys with one being bistable operation. Debounce circuit provided for all 19 keys. 9 LED readouts to verify entries. Easy interfacing with standard 16-pin IC connector. Only +5VDC required for operation. Size: 3 1/4" H x 8 1/4" W x 8 3/4" D.

**JE600/DTE-HK** (After assembled as pictured above) ... \$99.95

**JE600 Kit** (19-Key Hexadec. Keyboard, PC Board & Cmpnts. (no case)) ... \$59.95

**K19 19-Key Keyboard** (Keyboard only) ... \$14.95

**DTE-HK** (case only - 3 1/4" H x 8 1/4" W x 8 3/4" D) ... \$44.95

### JE610 ASCII Encoded Keyboard Kit

The JE610 ASCII Keyboard Kit can be interfaced into most any computer system. The kit comes complete with an industrial grade keyboard switch assembly (62-keys), IC's, sockets, connector, electronic components and a double-sided printed wiring board. The keyboard assembly requires +5V @ 150mA and -12V @ 10 mA for operation. Features: 60 keys generate the 126 characters, upper and lower case ASCII set. Fully buffered. Two user-define keys provided for custom applications. Caps lock for upper-case only alpha characters. Utilizes a 2376 (40 pin) encode-read-only memory chip. Outputs directly compatible with TTL/CMOS or MOS logic array. Easy interfacing with a 16-pin dip or 18-pin edge connector. Size: 3 1/4" H x 14 1/2" W x 8 3/4" D.

**JE610/DTE-AK** (After assembled as pictured above) ... \$124.95

**JE610 Kit** (62-Key Keyboard, PC Board, & Components (no case)) ... \$79.95

**K62 62-Key Keyboard** (Keyboard only) ... \$34.95

**DTE-AK** (case only - 3 1/4" H x 14 1/2" W x 8 3/4" D) ... \$49.95

### JE212 - Negative 12VDC Adapter Board Kit for JE610 ASCII KEYBOARD KIT

Provides -12V DC from Incoming 5VDC ... \$9.95

### JE215 Adjustable Dual Power Supply

General Description: The JE215 is a Dual Power Supply with independent adjustable positive and negative output voltages. A separate adjustment for each of the supplies provides the user unlimited applications for IC current voltage requirements. The supply can also be used as a general all-purpose variable power supply.

**FEATURES:**

- Adjustable regulated power supplies, pos. and neg. 1.2VDC to 15VDC.
- Power Output (each supply) 5VDC @ 500mA, 10VDC @ 750mA, 12VDC @ 500mA, and 15VDC @ 175mA.
- Two, 3-terminal adj. IC regulators with thermal overload protection.
- Heat sink regulator cooling.
- LED "on" indicator.
- Printed Board Construction.
- 120VAC Input.
- Size: 3-1/2" W x 5-1/16" L x 2-1/4" H

**JE215 Adj. Dual Power Supply Kit** (as shown) ... \$24.95

(Picture not shown but similar in construction to above)

**JE200 Reg. Power Supply Kit** (5VDC, 1 amp) ... \$14.95

**JE205 Adapter Brd.** (to JE200) 5V @ 9 & 12V ... \$12.95

**JE210 Var. Pwr. Sply. Kit**, 5-15VDC, to 1.5amp ... \$19.95

### HP-Display Sale-National

5082 Series - 0.43 Inch - 7-Segment

| Part Number | Color      | Description    | 1-3 Price | SALE PRICE |
|-------------|------------|----------------|-----------|------------|
| 5082-7650   | Hi Eff Red | CA - LHD       | 99        | \$4.29/49  |
| 5082-7651   | Hi Eff Red | CA - RHD       | 99        | \$4.29/49  |
| 5082-7653   | Hi Eff Red | CC - RHD       | 99        | \$4.29/49  |
| 5082-7656   | Hi Eff Red | Overflow ±1RHD | 99        | \$4.29/49  |
| 5082-7660   | Yellow     | CA - LHD       | 99        | \$4.29/49  |
| 5082-7661   | Yellow     | CA - RHD       | 99        | \$4.29/49  |
| 5082-7663   | Yellow     | CC - RHD       | 99        | \$4.29/49  |
| 5082-7670   | Green      | CA - LHD       | 99        | \$4.29/49  |
| 5082-7671   | Green      | CA - RHD       | 99        | \$4.29/49  |
| 5082-7673   | Green      | CC - RHD       | 99        | \$4.29/49  |
| 5082-7676   | Green      | Overflow ±1RHD | 99        | \$4.29/49  |
| 5082-7750   | Red        | CA - LHD       | 99        | \$4.29/49  |
| 5082-7751   | Red        | CA - RHD       | 99        | \$4.29/49  |
| 5082-7761   | Red        | Overflow ±1RHD | 99        | \$4.29/49  |
| 5082-7760   | Red        | CC - RHD       | 99        | \$4.29/49  |

CA-Comm. Anode CC-Comm. Cathode LHD/RHD/Left/Right hand dec.

### Mini Stereo AM/FM Receiver

Model 2830 ... \$29.95

WITH HEADPHONES For Joggers, Cyclists, Skaters & Sports Events

**FEATURES:** Lightweight headphones. Left/right balance control. Full fidelity stereo sound. Additional black soft carrying case & shoulder strap. Belt clip (hands free). Operates on 3 AA cell batteries (not incl.). Compact size: 3 1/4" x 4 1/4" x 1". Wt. 6 oz.

## KEYBOARDS — POWER SUPPLIES

### ALPS 26-KEY CALCULATOR KEYBOARD

Features: 7 Position, 3 Position and 2 Position Switching (ON/OFF). These are from Olivetti's Top of the Line. Mechanical SPST Switching; 22-pin Edge Card Connection.

Part No. KB26 ... \$1.95 each or 2/\$3.49

### MICRO SWITCH 69-KEY KEYBOARD

Data Entry Keyboard. Encoded Output: 5-bit Parallel EBC DIC. Switching: Hall Effect. 24-pin Edge Card Connection. Complete with Pin Connector.

Part No. KB69SD12-2 ... \$1.95 each

### DATANETICS 74-KEY KEYBOARD

ASCII Encoded Keyboard. Output: 5-bit Parity ASCII. Supply voltage +5, -12 volt. Switching: Mechanical SPST - 50-pin Connection. Complete with Pin Connector.

Part No. KB8354 ... \$29.95 each

### MICRO SWITCH 85-KEY KEYBOARD

Data Entry Keyboard. Encoded Output: 5-bit Parallel EBC DIC. Supply Voltage: +5VDC. Main Keyboard is QWERTY. Additional Key Pads for cursor and word processing functions.

Part No. KB85D18-1 ... \$29.95 each

### MICRO SWITCH 88-KEY KEYBOARD (PARALLEL ASCII)

Data Entry Keyboard used in a Diablo 1640 Terminal. Supply Voltage: +5V, -12V. Switching: Hall Effect - 18-pin Edge Card Connection. Schematic included. Uses 8048 Encoder Chip.

Part No. BBS22 ... \$69.95 each

### POWER SUPPLY - 5VDC @ 1 AMP REGULATED

Transaction Tech Output: +5VDC @ 1 amp (plus ±30VDC reg. input 115VAC 60Hz). Two-terminal (black/white) self-contained case. R. 3 cond. block pack cord. Size: 6 1/4" W x 7 1/2" D x 2 1/4" H. Wt. 4.0 lbs.

Part No. PSS1194 ... \$19.95 each

### POWER SUPPLY - 5VDC @ 1 AMP REGULATED

B Industries Output: +5VDC @ 1 amp, +36-42VDC adj. 400mA or less, 30VAC (isol.) @ 1.5 amp. Input 115VAC 60Hz. Case: 5 1/2" x 7 1/2" x 1 1/2" H. Self-contained case w/ rubber feet. 5 ft. 3 cond. blk. pow. cord. On/off switch. 6 1/4" W x 7 1/2" D x 2 1/4" H. Wt. 7 lbs.

Part No. PS407D ... \$24.95 each

### POWER SUPPLY - 5VDC @ 7.5 AMP, 12VDC @ 1.5 AMP SWITCHING

Input: 115VAC, 50-60Hz @ 3 amp/230VAC, 50Hz @ 1.5 amp. Fan w/low power supply silent self-cooled. (115/230VAC) Output: 5VDC @ 7.5 amp, 12VDC @ 1.5 amp. 5 ft. blk. pow. cord. 11 1/4" W x 13 1/2" D x 3 1/4" H. Wt. 8 lbs.

Part No. PS94V0 ... \$49.95 each

### POWER PAC - Heavy Duty Multi-Voltage Power Supply - 5VDC, 12VDC, 24VDC

Output: +5VDC @ 30A, +12VDC @ 2A, -12VDC @ 4A & +24VDC @ 3A. Input: 115VAC, 7A, 220VAC, 3.5A. Reg. ±. 15% line & load cond. Ripple: 10mV peak to peak (5mV RMS). Overvolt protect. 5V, +12V, -12V. Overcurr. protect. incl. 15% "L" x 6" H x 11 7/8" D. Wt. 40 lbs.

Part No. 285-D16 ... \$89.95 each

### SORENSEN Regulated Power Supplies

Sorensen's open construction (SOC) power supplies are series-regulated solid-state systems, designed to provide reg. DC voltages at 6 levels (2-28 vrange). These units are open-framed on sturdy black anodized aluminum for excellent mounting.

**FEATURES:** 115/208/230VAC input @ 50-63Hz. Low Ripple: 1.5mVrms, 5mV P-P maximum. Adjustable current limit. Voltage adjustment control. All schematics and specifications supplied with unit. Series A,S,E,C have three mounting styles (Series F, bottom mounting only).

| Part No.  | Series | Output Voltage Adjustment (volts) | Output Current (amps) | Size (inches) | Weight | Price |         |
|-----------|--------|-----------------------------------|-----------------------|---------------|--------|-------|---------|
| SOC 3-5   | B      | 1.9                               | 2.1                   | 6.1           | 4.1    | 2.8   | \$18.95 |
| SOC 3-6   | F      | 1.8                               | 25.0                  | 5.0           | 11.5   | 17.5  | \$82.4  |
| SOC 3-7   | A      | 4.75                              | 5.25                  | 3.0           | 2.4    | 1.8   | \$4.00  |
| SOC 3-8   | E      | 4.25                              | 5.75                  | 18.0          | 15.0   | 17.0  | \$24.95 |
| SOC 3-9   | F      | 4.75                              | 5.25                  | 20.0          | 21.0   | 17.5  | \$36.95 |
| SOC 10-11 | E      | 11.4                              | 12.6                  | 11.0          | 9.2    | 6.8   | \$16.00 |
| SOC 10-12 | F      | 11.4                              | 12.6                  | 11.0          | 9.2    | 6.8   | \$16.00 |
| SOC 10-13 | F      | 11.4                              | 12.6                  | 11.0          | 9.2    | 6.8   | \$16.00 |
| SOC 18-A  | C      | 14.25                             | 15.75                 | 5.0           | 4.2    | 3.6   | \$9.00  |
| SOC 18-B  | E      | 14.25                             | 15.75                 | 9.5           | 7.8    | 5.8   | \$14.00 |
| SOC 18-C  | F      | 14.25                             | 15.75                 | 10.0          | 10.0   | 9.0   | \$18.00 |
| SOC 28-A  | A      | 28.0                              | 29.0                  | 9.8           | 9.8    | 9.5   | \$4.00  |

### Powertec Sub-Modular DC Power Supplies

SM Series power supplies include rectifying, filtering, regulating, overload and overvoltage protection functions. You need only connect the sub-module to the appropriate secondary transformer tap and bolt the unit to a heatsink.

**REGULATION LINE:** 10% for a change from -10% to +10% input voltage. LOAD: 15% for a 0-100% load change (units below 5V output maintain 5V regulation). OUTPUT RIPPLE: 1mV RMS, 3mV P-P typical. 5mV P-P maximum. INPUT CHARACTERISTICS: Requires low-level AC input. Operate output current 15% for operations at 50Hz.

| Part Number | Input Voltage | Output Voltage | Output Current | Size (inches)      | Wt.                | Price   |         |
|-------------|---------------|----------------|----------------|--------------------|--------------------|---------|---------|
| 22AA-300    | 100V          | 3.0V           | 3.0A           | 2.50 x 3.00 x 0.90 | 4.3 lbs.           | \$18.95 |         |
| 22B-200     | 220V          | 2.2A           | 115-120VAC     | 2.2VAC 3A w/CT     | 3.00 x 3.06 x 1.18 | 8 oz.   | \$14.95 |
| 22B-300     | 220V          | 1.7A           | 115-120VAC     | 28VAC 2.5A w/CT    | 2.75 x 5.75 x 1.15 | 8 oz.   | \$19.95 |
| 22C-100     | 6.0A          | 1.1A           | 115-120VAC     | 18VAC 6A w/CT      | 2.80 x 7.50 x 1.15 | 8 oz.   | \$49.95 |
| 22C-300     | 6.8A          | 2.5A           | 115-120VAC     | 48VAC 3A w/CT      | 2.90 x 7.50 x 1.18 | 8 oz.   | \$49.95 |
| 22E-100     | 18.00A        | 1.1A           | 115-120VAC     | 28VAC 10A w/CT     | 3.00 x 7.00 x 3.30 | 2 lbs.  | \$49.95 |
| 22E-100     | 18.00A        | 1.1A           | 115-120VAC     | 16VAC 24A w/CT     | 2.90 x 7.00 x 3.30 | 2 lbs.  | \$29.95 |

### MOORECOSTER Regulated Power Supplies

MOORECOSTER Regulated Power Supplies are series-regulated solid-state systems, designed to provide reg. DC voltages at 6 levels (2-28 vrange). These units are open-framed on sturdy black anodized aluminum for excellent mounting.

**FEATURES:** 115/208/230VAC input @ 50-63Hz. Low Ripple: 1.5mVrms, 5mV P-P maximum. Adjustable current limit. Voltage adjustment control. All schematics and specifications supplied with unit. Series A,S,E,C have three mounting styles (Series F, bottom mounting only).

| Part No.  | Series | Output Voltage Adjustment (volts) | Output Current (amps) | Size (inches) | Weight | Price |         |
|-----------|--------|-----------------------------------|-----------------------|---------------|--------|-------|---------|
| MOC 3-5   | B      | 1.9                               | 2.1                   | 6.1           | 4.1    | 2.8   | \$18.95 |
| MOC 3-6   | F      | 1.8                               | 25.0                  | 5.0           | 11.5   | 17.5  | \$82.4  |
| MOC 3-7   | A      | 4.75                              | 5.25                  | 3.0           | 2.4    | 1.8   | \$4.00  |
| MOC 3-8   | E      | 4.25                              | 5.75                  | 18.0          | 15.0   | 17.0  | \$24.95 |
| MOC 3-9   | F      | 4.75                              | 5.25                  | 20.0          | 21.0   | 17.5  | \$36.95 |
| MOC 10-11 | E      | 11.4                              | 12.6                  | 11.0          | 9.2    | 6.8   | \$16.00 |
| MOC 10-12 | F      | 11.4                              | 12.6                  | 11.0          | 9.2    | 6.8   | \$16.00 |
| MOC 10-13 | F      | 11.4                              | 12.6                  | 11.0          | 9.2    | 6.8   | \$16.00 |
| MOC 18-A  | C      | 14.25                             | 15.75                 | 5.0           | 4.2    | 3.6   | \$9.00  |
| MOC 18-B  | E      | 14.25                             | 15.75                 | 9.5           | 7.8    | 5.8   | \$14.00 |
| MOC 18-C  | F      | 14.25                             | 15.75                 | 10.0          | 10.0   | 9.0   | \$18.00 |
| MOC 28-A  | A      | 28.0                              | 29.0                  | 9.8           | 9.8    | 9.5   | \$4.00  |

### SHIPMENT IN 24 HOURS

## 6:00 AM to 6:00 PM (PST)

# Call: (415) 592-8097

### JUMPER AND CABLE ASSEMBLIES

Standard Jumper Jumper Kits

All jumpers use low profile dip plugs with heavy duty pins for repeated disconnect applications.

| JUMPER KIT | Part No.   | Size (inches) | Wt.             | Price |
|------------|------------|---------------|-----------------|-------|
| JUMPER KIT | 924102-12  | 14            | single end 12"  | 3.79  |
| JUMPER KIT | 924102-24  | 14            | single end 24"  | 7.99  |
| JUMPER KIT | 924102-36  | 14            | single end 36"  | 11.99 |
| JUMPER KIT | 924102-48  | 14            | single end 48"  | 15.99 |
| JUMPER KIT | 924102-60  | 14            | single end 60"  | 19.99 |
| JUMPER KIT | 924102-72  | 14            | single end 72"  | 23.99 |
| JUMPER KIT | 924102-84  | 14            | single end 84"  | 27.99 |
| JUMPER KIT | 924102-96  | 14            | single end 96"  | 31.99 |
| JUMPER KIT | 924102-108 | 14            | single end 108" | 35.99 |
| JUMPER KIT | 924102-120 | 14            | single end 120" | 39.99 |
| JUMPER KIT | 924102-132 | 14            | single end 132" | 43.99 |
| JUMPER KIT | 924102-144 | 14            | single end 144" | 47.99 |
| JUMPER KIT | 924102-156 | 14            | single end 156" | 51.99 |
| JUMPER KIT | 924102-168 | 14            | single end 168" | 55.99 |
| JUMPER KIT | 924102-180 | 14            | single end 180" | 59.99 |
| JUMPER KIT | 924102-192 | 14            | single end 192" | 63.99 |
| JUMPER KIT | 924102-204 | 14            | single end 204" | 67.99 |
| JUMPER KIT | 924102-216 | 14            | single end 216" | 71.99 |
| JUMPER KIT | 924102-228 | 14            | single end 228" | 75.99 |
| JUMPER KIT | 924102-240 | 14            | single end 240" | 79.99 |
| JUMPER KIT | 924102-252 | 14            | single end 252" | 83.99 |
| JUMPER KIT | 924102-264 | 14            | single end 264" | 87.99 |
| JUMPER KIT | 924102-276 | 14            | single end 276" | 91.99 |
| JUMPER KIT | 924102-288 | 14            | single end 288" | 95.99 |
| JUMPER KIT | 924102-300 | 14            | single end 300" | 99.99 |

### Standard DB25 Series Cables

Now you can order DB25 P or S connectors with the cable necessary to fit your application. Choose from our standard flat cable in 4-foot lengths. Call today.

| Part No. | Cable Length | Connector       | Price     |
|----------|--------------|-----------------|-----------|
| DB25P-4  | 4 feet       | 1-DB25P         | 9.95 ea.  |
| DB25S-4  | 4 feet       | 1-DB25S         | 10.95 ea. |
| DB25P-4P | 4 feet       | 2-DB25P         | 16.95 ea. |
| DB25S-4S | 4 feet       | 1-DB25P/1-DB25S | 17.95 ea. |
| DB25S-4S | 4 feet       | 2-DB25S         | 18.95 ea. |

Spec Sheets - 25¢ each  
Send 8¢ Postage for your FREE 1982 JAMECO CATALOG  
Prices Subject to Change

### 5 1/4" Mini-Floppy Disc Drive

FOR TRS-80 MODEL I, III (Industry Standard)

Features: single or double density. Recording mode: FM single, MFM double density. Power: +12VDC (±0.6V) 1.6 amp max. 5VDC (±0.25V) 0.8 amp max. Unit as pictured at left (does not incl. case, power supply or cables). 30 page data book included. Weighs 3 1/2 lbs. Size: 5 1/4" W x 8 1/4" D x 3 1/4" H.

Part No. Limited Quantity! Price

**FD200** Single sided, 40 tracks, 250K bytes capacity ... \$179.95

**FD250** Double sided, 35 tracks, 438K bytes capacity ... \$199.95

### EXPAND YOUR TRS-80 TO 16K, 32K OR 48K

\*Model 1 - From 4K to 16K Requires (1) One Kit  
Model 3 - From 4K to 48K Requires (3) Three Kits  
Color - From 4K to 16K Requires (1) One Kit  
\*\*Model 1 equipped w/Expansion Board up to 48K (2) Two Kits Req'd.

TRS-80 16K Conversion Kit - Kit comes complete with 8 each MM5290 (UP14116) 16K Dynamic RAM (+ns) & documentation for conversion. TRS-16K2 150ns ... \$149.95

TRS-16K3 200ns ... \$149.95

TRS-16K4 250ns ... \$109.95

### Pee Wee Boxer Fan

36cm free air delivery  
3.125" sq. x 1.665" depth  
10 yrs. cont. duty at 20°C ambient to 70°C  
For Apple users

**PWS2107** Cleaned & tested (used) ... \$ 7.95 ea.

**PWS2107U** New ... \$12.95 ea.

### Muffin Fan

105cm free air delivery  
4.68" sq. x 1.50" depth  
10 yrs. cont. duty at 20°C ambient to 70°C  
115V 50/60Hz 14W Wt. 17 oz.

**MU2A1-U** Cleaned & tested (used) ... \$ 7.95 ea.

**MU2A1-N** New ... \$12.95 ea.

### COMPUTER GRADE CAPACITORS

| 1/4 Price Sale! | 1/2 Price Sale! | 1/4 Price Sale! | 1/2 Price Sale! |      |       |        |      |       |         |      |       |
|-----------------|-----------------|-----------------|-----------------|------|-------|--------|------|-------|---------|------|-------|
| mfd             | wvdc            | price           | mfd             | wvdc | price | mfd    | wvdc | price | mfd     | wvdc | price |
| 250             | 150             | 1.95            | 4,500           | 50   | 3.95  | 20,000 | 20   | 2.95  | 43,000  | 10   | 5.95  |
| 500             | 200             | 2.49            | 9,000           | 25   | 4.49  | 21,000 | 15   | 3.95  | 45,000  | 5    | 5.95  |
| 1,250           | 3               | 3.99            | 6,100           | 40   | 4.99  | 22,000 | 15   | 4.88  | 52,000  | 20   | 5.95  |
| 1,500           | 25              | 1.95            | 7,000           | 60   | 2.49  | 23,000 | 7    | 1.95  | 55,000  | 15   | 5.95  |
| 1,500           | 50              | 2.95            | 10,000          | 15   | 2.95  | 10,000 | 20   | 2.95  | 58,000  | 20   | 5.95  |
| 2,000           | 10              | 2.95            | 10,000          | 16   | 3.95  | 23,000 | 20   | 3.95  | 65,000  | 10   | 7.95  |
| 2,100           | 200             | 2.95            | 11,000          | 19   | 4.95  | 24,000 | 20   | 2.95  | 73,000  | 7.95 |       |
| 2,250           | 100             | 3.95            | 13,000          | 16   | 3.95  | 27,000 | 10   | 2.95  | 80,000  | 15   | 9.95  |
| 2,300           | 33              | 3.95            | 14,000          | 13   | 3.95  | 32,000 | 26   | 4.95  | 90,000  | 10   | 8.95  |
| 2,500           | 15              | 2.95            | 15,000          | 10   | 2.95  | 40,000 | 25   | 3.95  | 120,000 | 15   | 10.95 |
| 3,000           | 25              | 1.95            | 18,000          | 10   | 3.95  | 45,000 | 10   | 4.95  | 160,000 | 10   | 8.95  |
| 3,600           | 40              | 3.95            |                 |      |       |        |      |       |         |      |       |

OVER 200 OTHER VALUES AVAILABLE!  
SALE! Just deduct 50% of price listed above!

### JOYSTICKS

**JS-5K** 5K Linear Taper Pots ... \$5.25

**JS-100K** 100K Linear Taper Pots ... \$4.95

**JS-150K** 150K Linear Taper Pots ... \$4.75

**JS-5K** (Pictured) 40K (2) Video Controller in Case ... \$4.95

### UV-EPROM Eraser

8 Chips - 51 Minutes

1 Chip - 37 Minutes

Erase 2708, 2716, 2732, 2764, 2516, 2532, 2564. Erases up to 8 chips within 51 minutes (1 chip in 37 minutes). Maintains constant exposure distance of one inch. Special conductive foam liner eliminates static build-up. Built-in safety lock to prevent UV exposure. Compact - only 9"00" x 3"75" x 2"50". Complete with holding tray for 8 chips.

### UVS-11EL Replacement Bulb

DE-4 uv-EPROM Eraser ... \$79.95

### MOTOROLA AM/FM Stereo Push Button Car Radio

Model 5VW3901 ... \$49.95

FOR VOLKSWAGEN SCIROCCO, RABBIT, AUDI 5000 AND FOX (with minor adjustments, can be used in any automobile)

Includes bezel trim & everything pictured. Two ea. 4 x 6 speakers & grille (1 1/4" deep). All cables & leads for hook-up. Incl. all instruction Manuals for easy installation. Cut-out dim: 7" W x 1 1/4" H x 6 1/4" D.

CIRCLE 69 ON FREE INFORMATION CARD



# AMAZING DEVICES

**PHASORS**

**PHASOR PAIN FIELD** — Patented and recently developed in our labs is being tested by Gov't for riot control. Soon to come under weapons restrictions as an internal machine. Easily hand-held. Hazardous if NOT USED WITH DISCRETION.  
PPF-1 PLANS (sold for animal control) ..... \$15.00

**INVISIBLE PAIN FIELD GENERATOR** — Produces a directional field of moderately intense pain to back of head up to 50'. Cigarette pack size enclosure is easily hidden.  
IPG-3 PLANS ..... \$7.00 IPG-3K KIT & PLANS ..... \$44.50  
IPG-30 (assembled for animal control) ..... \$59.50

**PHASOR STUN/BURNING WAND** — Produces sufficient electrical energy capable of burning flesh. Intended as a personal defense device.  
PSW-3 PLANS ..... \$8.00 PSW-3K KIT & PLANS ..... \$59.50

**LASERS**

**RUBY LASER RAY PISTOL** — Intense visible red, burns, hazardous, with parts sources.  
RUBY PLANS (includes all part sources) ..... \$15.00

**CARBON DIOXIDE LASER** — Generates 20-40 watts of continuous power capable of burning, cutting, hazardous. (with all part sources) ..... \$15.00

**LASER RIFLE** — Produces 200-3000 pulses of 30 watt optical energy. Portable and easily hand-held.  
LRG-3 PLANS ..... \$10.00  
LRG-3K KIT PLANS (minus diode) ..... \$129.50

**POCKET LASER** — For the beginner, visible red "optical version", non-hazardous.  
LHC-2 ..... \$5.00 LHC-2K KIT & PLANS ..... \$24.50

**HIGH POWERED PORTABLE ENERGY SOURCE FOR LASERS AND MAGNETIC WEAPONS** — Exploding wires, shockwave, etc. Miniature size.  
HPS-1 PLANS ..... \$8.00 HPS-1K KIT & PLANS ..... \$49.50

**PARTICLE BEAM WEAPON** — PLANS ..... \$15.00

**SECURITY**

**INFINITY XMTR** — Uses telephone lines for selective home or office listening while away on business or vacation.  
INF-1 PLANS ..... \$15.00

**SEE IN DARK** — Long range, total darkness.  
SD-4 PLANS ..... \$10.00

**LONG RANGE WIRELESS MIKE** — Crystal clear quality — miniature.  
FBT-7 PLANS ..... \$7.00 FBT-7K PLANS & KIT ..... \$34.50

**WIRELESS TELEPHONE TRANSMITTER** — Long range, automatic.  
VWPM-5 PLANS ..... \$10.00 VWPM-5K PLANS & KIT ..... \$34.50

Send for FREE catalog description of above plus hundreds more plans, kits and completed items. We accept MC or Visa or when ordering, send check or money order. We pay shipping charges on orders over \$50.00, otherwise include 10% with remittance.

SEND TO: **SCIENTIFIC SYSTEMS**  
DEPT. R8, BOX 716, AMHERST, N.H. 03031

CIRCLE 98 ON FREE INFORMATION CARD

## ELECTRONIC KITS FROM HAL-TRONIX

2304 MHZ DOWN CONVERTERS. TUNES IN ON CHANNELS 2 TO 7 ON YOUR OWN HOME T.V. HAS FREQUENCY RANGE FROM 2000 MHZ TO 2500 MHZ. EASY TO CONSTRUCT AND COMES COMPLETE WITH ALL PARTS INCLUDING A DIE-CAST ALUM CASE AND COAX FITTINGS, REQUIRE A VARIABLE POWER SUPPLY AND ANTENNA (Antenna can be a dish type or coffee can type depending on the signal strength in your area.)

2304 MOD 1 (Basic Kit) ..... \$49.95  
(Less case & fittings)

2304 MOD 2 (Basic / Pre-amp) ..... \$59.95  
(Includes case & fittings)

2304 MOD 3 (Hi-Gain Pre-amp) ..... \$69.95  
(Includes case & fittings)

POWER SUPPLY FOR EITHER MODEL ABOVE IS AVAILABLE. COMES COMPLETE WITH ALL PARTS, CASE, TRANSFORMER, ANTENNA SWITCH AND CONNECTORS (Kit) \$24.95  
Assembled ..... \$34.95  
Slotted Microwave Antenna For Above Downverters ..... \$39.95

**PREAMPLIFIERS**

HAL PA-19 — 1.5 mhz to 150 mhz. 19db gain operates on 8 to 18 volts at 10ma. Complete unit \$8.95

HAL PA-1.4 — 3 mhz to 1.4 ghz. 10 to 12 db gain operates on 8 to 18 volts at 10ma. Complete unit \$12.95  
(The above units are ideal for receivers, counters, etc.)

16 LINE TOUCH TONE DECODER KIT WITH P.C. BOARD AND PARTS ..... \$69.95

12 LINE TOUCH TONE DECODER KIT WITH P.C. BOARD AND PARTS ..... \$39.95

16 LINE ENCODER KIT, COMPLETE WITH CASE, PAD AND COMPONENTS ..... \$39.95

12 LINE ENCODER KIT, COMPLETE WITH CASE, PAD AND COMPONENTS ..... \$29.95

MANY, MANY OTHER KITS AVAILABLE

Send 20 cents stamp or S.A.S.E. for information and flyer on other HAL-TRONIX products. To order by phone: 1-313-285-1782.



**HAL-TRONIX**  
P.O. Box 1401  
Southgate, MI 48195


SHIPPING INFORMATION:

ORDERS OVER \$25.00 WILL BE SHIPPED POSTPAID EXCEPT ON ITEMS WHERE ADDITIONAL CHARGES ARE REQUESTED ON ORDERS LESS THAN \$25.00 PLEASE INCLUDE ADDITIONAL \$2.00 FOR HANDLING AND MAILING CHARGES.

CIRCLE 99 ON FREE INFORMATION CARD

# QUALITY parts at DISCOUNT PRICES

## 4 CHANNEL 8 TRACK HOME UNIT

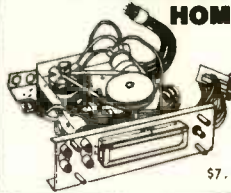

\$7.25 PER ASSEMBLY

BRAND NEW UNITS... ASSEMBLY INCLUDES; TAPE HEAD, MOTOR BELT, 110VAC MOTOR, PRE-AMP, LIGHTS, SWITCHES, SOLENOID AND OTHER EXCEPTIONAL PARTS... AN UNUSUAL BUY!

## MINI BSR



\$17.50 each

## AUTOMATIC RECORD CHANGER

\* B.S.R. MODEL C136R/C/3  
\* PLAYS 33/45/78 RECORDS  
\* MINI SIZE: 8 1/4" X 12"  
INCLUDES DUST COVER AND PLASTIC CASE (NOT PICTURED) WITH FRONT CUT OUT TO FIT STEREO UNIT (NOT INCLUDED).

## JOYSTICK



PRECISION DEVICE... CONTAINS 4 50K CENTER TAPPED ALPS POT'S. \$4.75 ea

## BLACK PLASTIC CASE




PAC-TEC SERIES C  
BLACK PLASTIC ENCLOSURE ADJUSTABLE HEIGHT FROM 1.63" TO 2.93", WIDTH 6.85", DEPTH 8". BUILT-IN STAND OFFS FOR P.C. BOARDS... FRONT AND BACK PANELS NOT INCLUDED... \$5.25 PER CASE

## VARACTOR DIODES


BB-103 3 FOR \$1.00  
100 FOR \$30.00  
MV2205 3 FOR \$1.00  
100 FOR \$30.00
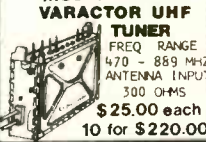
## MITSUMI MODEL UE5-A55 VARACTOR UHF TUNER



\$25.00 each  
10 for \$220.00

## MINI SIZE BUZZERS

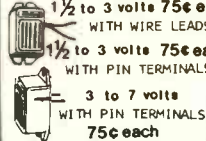

1 1/2 to 3 volts 75c ea WITH WIRE LEADS  
1/2 to 3 volts 75c ea WITH PIN TERMINALS  
3 to 7 volts WITH PIN TERMINALS 75c each

## PHOTO FLASH CAPACITORS

170 MFD 330 VOLT  
1 1/2" X 7/8" 2 FOR \$1.50  
10 FOR \$7.00  
600 MFD 360 VOLT 3 3/4" HIGH X 1" DIA. \$1.00 EA. 10 FOR \$9.00  
750 MFD 330 VOLT 2" HIGH X 1 3/4" \$1.25 EACH 10 FOR \$11.00

## SLIDE POTS

500K linear taper  
2 7/8" LG. 75c EACH  
1 3/4" TRAVEL 75c EACH

## COMPUTER GRADE CAPACITOR

1700 mfd. 150VDC \$2.00  
2 1/2" DIA X 4 3/4" HIGH  
3,600 mfd. 40VDC \$1.00  
1 3/8" DIA. X 3" HI  
6,400 mfd. 60VDC \$2.50  
1 3/8" DIA X 4 1/4"  
12,000 mfd. 40 VDC \$3.00  
2" DIA X 4 1/4" HIGH  
18,000 mfd. 75 VDC \$4.00  
2 1/2" DIA X 4 1/2" HIGH  
22,000 mfd. 15VDC 2" DIA X 2 1/2" HIGH \$2.00  
22,000 mfd. 40VDC 2" DIA. X 6" HIGH \$3.00  
25,000 mfd. 75 VDC \$4.50  
3" DIA X 4 3/8" HIGH  
45,000 mfd. 25 VDC 2" DIA. X 4" HIGH \$3.50  
72,000 mfd. 15VDC 2" DIA. X 4" HIGH \$3.50

## COMPUTER GRADE CAPACITOR SPECIAL

180,000 mfd. at 6V  
2 1/4" DIA X 4 1/2" HIGH \$1.50  
CLAMPS TO FIT CAPACITORS 50c ea.

## DC WALL TRANSFORMER

ALL ARE 115 VAC PLUG IN  
4 VDC at 70 MA \$2.50  
5.8 VDC at 125 MA \$2.50  
9 VDC at 100 MA \$2.00  
9 VDC at 225 MA \$3.00

## TRANSFORMERS

120 volt primaries  
5.6 VOLTS at 750 MA \$3.00  
6 VOLTS at 150 MA \$1.25  
12 V.C.T. at 500 MA \$2.50  
16.5 V. at 3 AMPS \$6.50  
18 VOLTS at 350 MA \$2.00  
18 VOLTS at 1 AMP \$4.50  
18 V.C.T. at 2 AMP \$5.50  
25.2 V.C.T. at 2.8 AMP \$5.50  
35 V.C.T. at 1 AMP \$3.50  
42 V.C.T. at 1.2 AMP \$4.50  
65 V.C.T. at 2 AMP \$5.50

## L.E.D.'s STANDARD JUMBO DIFFUSED

RED 10 FOR \$1.50  
GREEN 10 FOR \$2.00  
YELLOW 10 FOR \$2.00

## FLASHER LED 5 VOLT OPERATION RED JUMBO SIZE

2 FOR \$1.70

## BI POLAR LED SUB MINI LED

2 FOR \$1.70  
.079" X .098" RED  
20mA at 1.75v  
10 FOR \$1.00  
200 FOR \$18.00  
QUANTITY PRICES AVAILABLE

## BLACK LIGHT (ULTRAVIOLET)

# E. # F6T5BL \$2.50 each

# FREE! SEND FOR OUR NEW 40 PAGE CATALOG FREE!

## CONNECTORS WEATHERPROOF 2 CONDUCTOR

POLARIZED SET, 18 GA. WIRE. \$1.00 / SET

## 4 CONDUCTOR

\$1.50 PER SET  
WEATHER-PROOF SOCKET AND CONNECTOR SET...

## EDGE CONNECTOR

ALL ARE .156" SPACING

## 15/30 GOLD

SOLDER EYELET \$2.00 EACH

## 18/36 GOLD

SOLDER EYELET \$2.00 EACH

## 22/44 GOLD

SOLDERTAIL (P.C. STYLE) \$2.50 EA 10 FOR \$22.50

## 22/44 TIN

SOLDERTAIL (P.C. STYLE) \$1.35 EA 10 FOR \$12.50

## 42/84 GOLD

SOLDER EYELET \$4.00 EACH

## 4PDT RELAY

14 pin style  
3 amp contacts  
24 volt d.c. coil  
120 volt a.c. coil  
Used but fully tested  
\$1.70 EACH  
specify coil voltage  
LARGE QUANTITIES AVAILABLE  
SOCKETS FOR RELAY 50c each

## 6 VDC RELAY

MINIATURE D.P.D.T.  
3 AMP CONTACTS  
FUJITSU # FBR321D006  
\$1.75 EA 10 / 16.00

## 2 CHANNEL LIGHT ORGAN



EASILY HOOKS INTO STEREO SPEAKERS AND ALLOWS 110 V.A.C. LIGHTS TO DANCE WITH MUSIC. \$6.50 PER UNIT STRING OF 20 LIGHTS TO CONNECT TO EITHER CHANNEL-- \$1.75 FOR LIGHTS  
ORGAN WILL ACCEPT TWO LIGHT STRINGS

## L-PAD

STANDARD 8 OHM  
50 DB L-PAD... \$1.50 EACH

## 8 LINE CORD

SUT M/E 18 - 3  
ROUND GRAY  
\$2.00 EACH 10 FOR \$18.50

## MICROWAVE TRANSISTORS

N.P.N. SILICON SPECIAL PRICE \$2.50 EACH

## CANNON XLRA-3-13 CONNECTOR

3 PRONG CHASSIS MOUNT CONNECTOR \$2.00 EACH  
10 for \$19.00

## 75 ohm CO-AX

12 FOOT R.C.A. PLUGS BOTH ENDS... USED FOR VIDEO GAMES... \$1.25 EA

## 0-10 MINUTE TIMER

ADJ. TIMING MOTOR FROM 0 - 10 MIN. RATED 10 AMPS. 125 VAC MOUNTS ON 1" CENTERS... \$4.75 EACH

## MULTI-SWITCH 8 STATION

INTERLOCKING ASSEMBLY 4-D.P.D.T. 7-4-P.D.T. 6 1/2" MOUNTING CENTERS \$3.00 PER ASSEMBLY

## 5 STATION

INTERLOCKING ASSEMBLY 3-4-P.D.T. 2-D.P.D.T. 4 1/8" MOUNTING CENTERS \$2.50 PER ASSEMBLY

## 3 STATION

NON-INTERLOCKING 2-D.P.D.T. 7-4-P.D.T. PUSH ON/PUSH OFF STYLE 1 1/2" MOUNTING CENTERS \$1.50 PER ASSEMBLY

## LIGHTED PUSH BUTTON

RED LIGHTED 120 VAC 10 AMP. S.P.S.T. "POWER" PRINTED ON FACE. MOUNTS IN 7/8" SQUARE HOLE... \$1.50 EA 10 / \$13.50

## 6volt 9amp/hr RECHARGEABLE

ELPOWER # EP690 SOLID GEL CELL 5 1/2" X 4 1/4" X 2 3/4"..... \$15.00 EACH

**MANUFACTURERS - WE WILL PURCHASE YOUR EXCESS INVENTORY (213) 380-8000**

## ALL ELECTRONICS CORP.

905 S. Vermont Ave.  
P.O. BOX 20406  
Los Angeles, Calif. 90006  
TOLL FREE ORDER NO.  
800-876-5432  
AK-HI-CA (213) 380-8000  
Mon. Fri. Saturday  
9 AM - 5 PM 10 AM - 3 PM

TERMS  
• Quantities Lim. to  
• Min Order: \$10.00  
• Add \$2.50  
Shipping USA  
• Calif. Res. Add.  
• Prompt Sh. pping  
NO COD

CIRCLE 79 ON FREE INFORMATION CARD



# FORMULA INTERNATIONAL INC.

12603 CRENSHAW BOULEVARD • HAWTHORNE, CALIFORNIA 90250 • (213) 973-1921



## Introducing THE Pineapple™



### 48K Color Computer Kit


Easy to assembly! All components are clearly silk screened on the circuit board. Kit includes predrilled double sided PC Board, all integrated circuits, sockets, professional high-impact plastic casing, keyboards, connectors and switching power supply.

#### Features

- Numeric key pad
- Game paddle jacks on both sides
- Speaker volume control on the back.

Dealer inquiries invited.

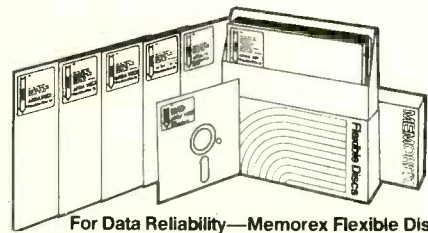**\$645<sup>00</sup>** per kit  
No C.O.D. orders




For Data Reliability—Memorex Flexible Discs

### 5 1/4" Flexible Disc Sale

Why buy other brands when you can buy MEMOREX disc for much less and backed by 1 year factory warranty.
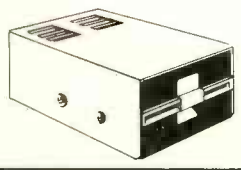
#### PRICE BREAK-THRU ON APPLE® DRIVE!

100% APPLE Compatible  
5 1/4" Floppy Disc Drive



**\$295.00** Each  
**\$375.00** Each  
(with controller)

| PART # | DESCRIPTION                                 | PRICE              |
|--------|---|--------------------|
| 3481   | 5 1/4"SSDD Soft Sector w/Hub Ring           | 1-9 ..... \$2.45   |
| 3483   | 5 1/4"SSDD 10 Hard Sector w/Hub Ring        | 10-99 ..... \$2.15 |
| 3485   | 5 1/4"SSDD16 Hard Sector w/Hub Ring         | 100-499... \$2.00  |
|        |   | 500 & up... call   |
|        |   | 10pcs. 100pcs.     |
| 3062   | 8"SSDD IBM Compatible (128 B/S, 26 sectors) | \$2.15 .... \$2.00 |
| 3015   | 8"SSDD Shugart Compatible (32 Hard Sector)  | \$2.15 .... \$2.00 |
| 3090   | 8"SSDD IBM Compatible (128 B/S 26 Sectors)  | \$2.85 .... \$2.65 |
| 3102   | 8"DSDD Soft Sector (Unformatted)            | \$3.30 .... \$3.05 |
| 3115   | 8"DSDD Soft Sector (128 B/S, 26 sectors)    | \$3.50 .... \$3.25 |
| 3491   | 5 1/4"DSDD Soft Sector w/Hub Ring           | \$3.25 .... \$3.00 |
| 3493   | 5 1/4"DSDD 10 Hard Sector w/Hub Ring        | \$3.25 .... \$3.00 |
| 3495   | 5 1/4"DSDD 16 Hard Sector w/Hub Ring        | \$3.25 .... \$3.00 |

#### MICROPROCESSOR COMPONENTS

|                   |                  |                 |
|-------------------|------------------|-----------------|
| Z80..... 8.75     | Z80A-DMA . 28.50 | 2708..... 5.95  |
| Z80A ..... 9.25   | 2102..... 1.50   | 2716..... 9.60  |
| 8080A..... 5.50   | 21L02..... 1.50  | 2516..... 11.95 |
| Z80-PIO .... 7.50 | 2114..... 2.95   | 2732..... 15.95 |
| Z80A-PIO... 8.50  | 2114L..... 2.95  | 2532..... 16.95 |
| Z80A-SIO... 29.50 | 4116..... 3.00   | 2764..... 49.95 |
| Z80A-CTC... 8.50  | 1702A..... 4.95  |                 |

#### SANYO MONITORS

| MODEL NO. | DESCRIPTION      | LIST     | SALE     |
|-----------|------------------|----------|----------|
| VM 4509   | 9" B&W, 10 MHz   | \$190.00 | \$169.00 |
| DM 5109   | 9" Green, 10 MHz | \$200.00 | \$180.00 |
| DM 8012   | 12" B&W, 18MHz   | \$250.00 | \$225.00 |
| DM 8112   | 12" Green, 18MHz | \$260.00 | \$235.00 |
| DMC 6013  | 13" Color        | \$470.00 | \$425.00 |
| DMC 6113  | 13" RGB Color    | \$995.00 | \$895.00 |

#### IC SOCKETS

|        | LP     | WW     | LP     | WW     |
|--------|--------|--------|--------|--------|
| 8-pin  | 5/ .75 | 5/1.91 | 22-pin | 5/1.62 |
| 14-pin | 5/1.00 | 5/2.40 | 24-pin | 5/1.80 |
| 16-pin | 5/1.20 | 5/2.65 | 28-pin | 5/2.10 |
| 18-pin | 5/1.35 | 5/2.98 | 40-pin | 5/3.02 |
|        |        |        | 20-pin | 5/1.52 |
|        |        |        |        | 5/4.55 |

#### SPECIAL OF THE MONTH

|                  |                      |            |
|------------------|----------------------|------------|
| 2532 EPROM       | 4116 (200nS)         | 2732 EPROM |
| \$9.95 ea.       | 8/\$13.50 32/\$43.20 | \$8.95 ea. |
| LIMITED QUANTITY |                      |            |

CIRCLE 70 ON FREE INFORMATION CARD



# FORMULA INTERNATIONAL INC.

12603 CRENSHAW BOULEVARD • HAWTHORNE, CALIFORNIA 90250 • (213) 973-1921



## MATCHED PAIR MOTOR TRANSISTORS BY MOTOROLA

|            |     |           |         |          |
|------------|-----|-----------|---------|----------|
| A. MJ2955  | PNP | 150 Watts | BV=60V  | \$3.50   |
| 2N23055    | NPN | 150 Watts | IC=15A  | per pair |
| B. NJE2955 | PNP | 90 Watts  | BV=60V  | \$3.00   |
| MJE3055    | NPN | 90 Watts  | IC=10A  | per pair |
| C. MJ15003 | NPN | 250 Watts | BV=140V | \$12.00  |
| MJ15004    | PNP | 250 Watts | IC=20A  | per pair |

All above parts guaranteed prime and include data sheets.



## HYBRID AUDIO POWER AMPLIFIER IC's

Typical ratings: Operating case temp. 85°C. T<sub>H</sub>D=0.5% (20Hz-20KHz). Input resistance 10K-100KΩ. Power band width 20Hz-20KHz. Freq. response 10-100KHz. Output resistance =8Ω. With built-in protection circuit. All units come with data sheet.

| Part No. | Output  | Vcc  | Unit Price |
|----------|---------|------|------------|
| STK040   | 10W+10W | ±18V | \$14.50    |
| STK041   | 15W+15W | ±20V | \$18.50    |
| STK050   | 50W     | ±35V | \$26.50    |
| STK054   | 23W     | ±19V | \$13.50    |
| STK056   | 30W     | ±22V | \$18.50    |
| STK070   | 70W     | ±42V | \$32.50    |
| STK415   | 7W+7W   | 30V  | \$ 8.50    |
| STK439   | 15W+15W | 39V  | \$16.50    |
| STK465   | 30W+30W | ±28V | \$22.50    |
| STK0105  | 100W    | ±50V | \$36.50    |

## SANYO ANTENNA SIGNAL BOOSTER

This Booster is specially designed for UHF Channels (14-83). After installing (between the antenna input cable, and the UHF tuner), this unit will provide a minimum of 10dB gain, that is approximately 2 times better than you are seeing now. Ideal for those who live in apartments that can not put an outdoor antenna. Small in size, only 2" x 1 1/2" x 1". Supply voltage is 15 VDC. Back in Stock



## SANYO UHF VARACTOR TUNER

FOR UHF CHANNEL 14-83

Tuning voltage +1~+28VDC. Input impedance 75Ω. IF band width 7-16MHz. Noise figure 11.5dB Max. Size 2 3/4" x 1 1/2" x 1/2". Supply voltage 15VDC. Sound IF=58.0MHz.

Model 115-B-403A. Video IF 45.0MHz

Model 115-B-405A. Video IF 62.5MHz

\$35.00 ea.

Tuner is the most important part of the circuit. Don't let those \$19.00 tuners fool you. All units are brand new from Sanyo. When ordering please specify model number.

## CRYSTAL CONTROLLED WIRELESS MICROPHONE SYSTEM

Transmitter FET mic for flat 30-18 KHz response. Xtal controlled 49 MHz AM Band for drift-free performance. 100 MW output (range approx 1/2 mile) for reliable long range transmission. Powered by a 9V radio battery (included).

Receiver: Xtal controlled locks on 49 MHz transmitter signal. On panel VU meter, monitors the signal strength from the microphone. Standard phone jack outlet connection to a PA, or other phone input. 9V battery included. This professional set is ideal for on stage, in field, church, in house or outdoor use.

## WHISTLE ACTIVATED SWITCH BOARD

All boards are pre-assembled and tested. Your whistle to its FET condenser microphone from a distance, as far as 30 feet away (sensitivity can be easily adjusted), will turn the switch on and if you whistle again, it will turn off. Ideal for remote control toys, electrical appliance such as lights, coffee pots, TV, Hi-Fi, radio or other projects. Unit works on 9VDC.

MODEL 968 ..... \$4.50 ea.



## PROFESSIONAL REGULATED VARIABLE DC POWER SUPPLY KIT

All solid state circuitry with high efficiency power transistor 2SD388 and IC voltage regulator, MC733. Output voltage can be adjusted from 0-30V at 1A. Current limited or 0-15V at 2A. Current limited. Internal resistance is less than 0.005Ω. Ripple and noise less than 1mV. Dual on panel meters for voltage and amp reading, also with on board LED and audible over load indicator. Kit comes with pre-drilled PC Board, instructions, all necessary electronic components, transformer and a professional locking metal cabinet. The best projector for school and the most useful instrument for repairmen. Build one today!

MODEL TR88A 0-15VDC @ 2A  
MODEL TR88B 0-30VDC @ 1A

\$59.50 Per Kit



## TA-800 120W PURE DC POWER STEREO AMP KIT

Getting power hungry from your small amp? Have to watch your budget? Here's a good solution! The TA-800 is a pure DC amplifier with a built in pre-amp. All coupling capacitors are eliminated to give you a true reproduction of the music. On board tone and volume controls combined with built in power supply make the TA-800 the most compact stereo amp available. Specifications: 60W x 2 into 8Ω. Freq. range 0-100KHz ±3dB. THD 0.1% or better. S/N ratio 80dB. Sensitivity: 3mV into 47K. Power Requirement: ±24-40 Volts.

A GOOD BUY!

at \$65.00

## SUPER FM WIRELESS MIC KIT — MARK III

This new designed circuit uses high FREQ. FET transistors with 2 stage pre-amp. Transmits FM range (88-120MHz) up to 2 blocks away and with the ultra sensitive condenser microphone, that comes with the kit, allows you to pick up any sound within 15 ft. away. Kit includes all electronic parts, OSC coils, and PC Board. Power supply 9VDC.

FMC-105

\$11.50 Per Kit

## ULTRASONIC SWITCH KIT

Kit includes the Ultra Sonic Transducers, 2 PC Boards for transmitter and receiver, all electronic parts and instructions. Easy to build and a lot of uses such as remote control for TV, garage door, alarm system or counter. Unit operates by 9-12VDC.

\$15.50 ea.

## ELECTRONIC SWITCH KIT

CONDENSER TYPE. Touch On - Touch Off. Uses 7473 IC and 12V relay

\$5.50



## LOW TIM DC STEREO PRE-AMP KIT TA-1020


Incorporates brand-new DC design that gives a frequency response from 0-100KHz ±0.5dB. Added features like tone defat and loudness control let you tailor your own frequency supplies to eliminate power fluctuation!

Specifications: • THD/TIM less than .005% • Frequency response DC to 100KHz ±0.5dB • RIAA deviation ±0.2dB • S/N ratio better than 70dB • Sensitivity Phono 2mV/47K/Aux 100mV/100K • Output level 1.3V • Max output 15V • Tone controls Bass ±10dB @ 50Hz/Treble ±10dB @ 15Hz • Power supply ±24VDC @ 0.5A. Kit comes with regulated power supply, all you need is a 48VCT transformer @ 0.5A.

Only \$44.50

X'tormer:

\$4.50 ea.

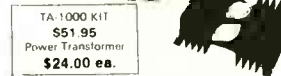

## 100W CLASS A POWER AMP KIT

Dynamic Bias Class "A" circuit design makes this unit unique in its class. Crystal clear, 100 watts power output will satisfy the most picky fans. A perfect combination with the TA-1020 low TIM stereo pre-amp.

Specifications: • Output power 100W RMS into 8Ω, 125W RMS into 4Ω • Frequency response 10Hz-100KHz • THD less than 0.008% • S/N ratio better than 80dB • Input sensitivity 1V max. • Power supply ±40V @ 5A

## 1 WATT AUDIO AMP

All parts are pre-assembled on a mini PC Board. Supply Voltage 6-9VDC

SPECIAL PRICE \$1.95

## 6W AUDIO AMP KIT

2 LM380 with Volume Control. Power Supply 6-18VDC

Only \$7.50

## TA-323 60 WATTS TOTAL 30W + 30W STEREO AMP KIT

This is a solid state all transistor circuitry with on board stereo pre-amp for most microphone or phone input. Power output employs 2 pairs matching Darlington Transistors driven by the popular 2N3053 Driver Transistors. Four built on board controls for volume, balance, treble and bass. Power supply requires 48VCT 2.5A transformer. THD of less than 0.1% between 100Hz-10KHz at full power. (30 Watts + 30 Watts loaded into 8Ω).

## SPECIAL EXCELLENT PRICE!

MODEL 001-0034

\$29.50 Per Kit

Transformer

\$10.50 ea.

## ELECTRONIC DUAL SPEAKER PROTECTOR

Cuts off when circuit is shorted or over loaded to protect your amplifier as well as your speakers. A must for OCL circuits.

KIT FORM \$8.75 ea.

## "FISHER" 30 WATT STEREO AMP

MAIN AMP (15W x 2). Kit includes 2 pcs. Fisher PA 301 Hybrid IC, all electronic parts with PC Board. Power supply ±18VDC (not included). Power band with (KF 1%±3dB). Voltage gain 33dB. 20Hz-20KHz.

Super Buy

Only \$18.50

## FLUORESCENT AUDIO LEVEL MONITOR

This is the kind of VU monitor that is being used by most amplifier manufacturers. IC's are used to simplify circuit layout. Easy to assemble and can be used with all power level amplifiers. Power requirement 12VDC.

TE-221 KIT

For Just \$28.50

(Limited Stock)

## MARK IV — 15 STEP

### LED POWER LEVEL INDICATOR KIT

This new stereo level indicator kit consists of 36 4-color LED's (15 per channel) to indicate the sound level output of your amplifier from -36dB to +3dB. Comes with a well designed silk screen printed plastic panel and has a selector switch to allow floating or gradual output indicating. Power supply is 6-12VDC with THG on board input sensitivity controls. This unit can work with any amplifier from 1W to 200W. Kit includes 70 pcs driver transistors, 38 pcs matched 4-color LED's, all other electronic components, PC Board and front panel.

MARK IV KIT

\$31.50

## REGULATED DUAL VOLTAGE SUPPLY KIT

± 10-30 VDC @ 250 ma adjustable, fully regulated. Kit includes all electronic parts, filter capacitors, IC's, heat sinks and PC Board.

\$12.50 per kit



## AUDIO FREQUENCY SPECTRUM ANALYSER KIT TA-2900

This Audio Frequency Spectrum Analyser analyses audio signals in 10 octaves over a dynamic range of 30 dB. The technique allows the sound "coloration" introduced by unwanted room and speaker resonances to be substantially eliminated.

The TA-2900 provides a visual presentation of the changing spectrum thru 100 red LED displays. So you can actually see proof of the equalized sound you've achieved. The TA-2900 kit comes with all the electronic components. I.C., predrilled PC board, the instructions and a 19" Rack Mount type metal cabinet with professional silkscreen printed front panel.

- Input Sensitivity Tape Monitor/10mV - 1.8mV 50K Ohms Speaker Terminal/0.2W - 100W 8 Ohms
- Display Level Range (all octaves) 20B per step—14dB to 40B
- Delay Time (1 KHz) Fast/18dB/s Slow/60dB/s
- Power Input: 117V or 220V AC 50-60 Hz
- Power Consumption: 36W
- Dimensions: 482(W) x 102(H) x 250(D) mm

\$99.50 per kit

## POWER SUPPLY KIT

0-30VDC REGULATED. Uses UA723 and 2N3055 power transistor. Output can be adjusted from 0-30V @ 2A. Complete with PC Board and all electronic parts.

TRANSFORMER \$9.50 ea.

POWER SUPPLY KIT \$10.50 ea.

## PROFESSIONAL FM WIRELESS MICROPHONE

Made by one of the leading Japanese manufacturers. This factory assembled FM wireless microphone is powered by two AA size batteries. It transmits in the range of 88-108 MHz. Element is built in a plastic tube type case with an omnidirectional electronic condenser microphone unit. By using a standard FM radio, signal can be heard anywhere on a one-acre lot. Sound quality was judged "very good." MODEL WEM-36.

WAS \$16.50

ON SALE

\$12.50 each



Never worry about battery, because it has none! Easy to carry in pocket and handy to use. Ideal for emergency light. It generates its own electricity by squeezing grip lever. Put one in your car, boat, camper or home. You may need it some time!

EXCLUSIVE \$3.95 ea.

## FLUORESCENT LIGHT DRIVER KIT

12V DC POWERED. Lights up 8-15 Watt Fluorescent Light Tubes. Ideal for camper, outdoor, auto or boat. Kit includes high voltage coil, power transistor, heat sink, all other electronic parts and PC Board. Light tube not included.

\$6.50 Per Kit

## SOLAR CELLS

0.5V 200MA. Ideal for all kinds of solar projects, cells can be put in series to double voltage or parallel to double current.

\$1.99 ea.

## FOR COMMERCIAL FREE TV BOX BUILDERS

|        |                  |                           |                  |
|--------|------------------|---------------------------|------------------|
| MC1358 | ..... \$3.00 ea. | LM380                     | ..... \$2.00 ea. |
| MC1350 | ..... \$2.25 ea. | LM7815                    | ..... \$1.20 ea. |
| MC1330 | ..... \$3.00 ea. | LM7818                    | ..... \$1.20 ea. |
| MC1406 | ..... \$2.50 ea. | 10K10T P.C. Mount         | ..... \$3.00 ea. |
| MC1458 | ..... \$1.00 ea. | 10K11T P.C. Mount         | ..... \$1.75 ea. |
| LM1889 | ..... \$3.75 ea. | Toroid Coils (set of 4)   | ..... \$3.00 ea. |
| NE565  | ..... \$2.19 ea. | 5-35pF (Trimmer Cap)      | ..... .85 ea.    |
| NE564  | ..... \$3.45 ea. | Power Transformer 18V, 8A | ..... \$3.50 ea. |

## NEW ARRIVALS

### 6-WAY A/C ADAPTOR

Input: 110V A/C Output: 3v, 4.5v, 6v, 7.5v & 12VDC Current: 300mA

OUR LOW PRICE

\$5.50 each

## 19" RACK MOUNT CABINETS

Black anodized front panel with black textured case.

| WIDTH | DEPTH   | HEIGHT | PRICE   |
|-------|---------|--------|---------|
| 17"   | 11 1/2" | 3"     | \$25.50 |
| 17"   | 11 1/2" | 5"     | \$31.50 |
| 17"   | 11 1/2" | 7"     | \$39.50 |

PHONE ORDERS ONLY  
CALL TOLL FREE  
1-800-672-8758

## SHIPPING AND HANDLING CHARGES


|                        |                       |
|------------------------|-----------------------|
| Under \$50.00 Purchase | Over \$50.00 Purchase |
| 10%                    | 5%                    |
| 15%                    | 10%                   |
| 25%                    | 20%                   |

Minimum Order \$10.00 / Calif. Residents add 6.5% Sales Tax. Phone Orders Accepted on VISA or MC ONLY. NO C.O.D.'s. Prices subject to change without notice.

CIRCLE 70 ON FREE INFORMATION CARD
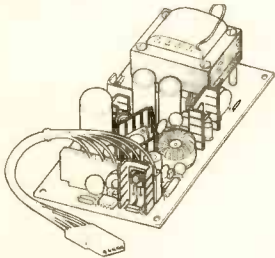
## Brand New Micro Computer Power Supply

- \* Switching regulation
- \* Multiple DC outputs:
  - +5V 4A -12V 1A
  - +12V 1A -2.2 to 15V 0.5A
- \* Fiberglass PCB
- \* Over-voltage protection with IC monitor
- \* 110/220 V input
- \* Factory assembled
- \* Circuit diagram available (for a copy, send self-addressed stamped envelope)
- \* \$49.00 each, freight prepaid (Calif residents pls add \$3 sales tax)



## FUJITECH AUDIO KITS

### LATEST AUDIO TECHNOLOGY FROM JAPAN

Send \$5.00 for each assembly manual, refundable with order.

Monarchy Engineering, Inc.  
380 Swift Avenue, Unit 21  
South San Francisco, CA 94080

Visa or Mastercharge acceptable.

- Model A501 Power Amp**
- \* Pure Class A 25W + 25W
  - \* Switchable to Class AB 100W + 100W
  - \* Switchable to Bridge Class A 100W mono
  - \* Switchable to Bridge Class AB 300W mono
  - \* Frequency Response 5-200KHz (-1dB)
  - \* Signal-to-Noise Ratio 120dB
  - \* Non-magnetic Chassis
  - \* "Out-board" comprehensive protection circuitry
  - \* DC circuitry with limited use of NFB
  - \* High Efficiency Fluid Convection Cooling
  - \* THD under 0.007%



KIT ONLY  
\$299.00

\$299.00

- Model A502 DC Stereo Control Center**
- \* Direct DC coupling from Input to Output
  - \* DC servo circuitry
  - \* Cascade FET Input in all stages
  - \* Separate Moving Coil RIAA amplifier
  - \* Distortion below 0.005% (3V)
  - \* Max Output 15V
  - \* Frequency Response 20Hz-20KHz ±0.2 dB
  - \* Maximum Phono Input
    - MC = 16mv RMS (1KHz)
    - MM = 270mv RMS (1KHz)
  - \* Built-in Headphone amplifier
  - \* Relay Output Muting

KIT ONLY  
\$349.00



\$349.00

# CABLE TV

## CONVERTERS DESCRAMBLERS

Largest Selection  
of Equipment Available  
\$ Buy Warehouse Direct & Save \$



36 channel  
converter  
\$45.95

36 channel  
wired remote  
converter  
only  
\$88.95



Send \$2 for complete catalog  
of converters and unscramblers

Quantity Discounts • Visa • Master Charge  
Add 5% shipping — Mich. residents add 4% sales tax

**C&D Electronics, Inc.**  
P. O. Box 21, Jenison, MI 49428  
(616) 669-2440

# B. G. MICRO

P. O. Box 280298 Dallas, Texas 75228  
(214) 271-5546

Visa • MasterCard • American Express

### STATIC RAM

|   |              |
|---|--------------|
| 21L02-1KX1 250 n.s.<br>Low Power  | .95          |
| 21L4L-3 1KX4 300 n.s.<br>Low Power  | 2.75 8/17.50 |
| HM6116P-4-2KX8 + 5v-200 n.s.<br>CMOS Low Power 2716<br>Style Pin Out                          | 8/59.95      |
| TMM2016-2KX8 +5v-NMOS<br>200 n.s. - 2716 Style<br>Pin Out                                     | 8/59.95      |
| 6501-5 256X4 - CMOS - Data<br>Retention 2 Volts - 22 Pin - 200 n.s.<br>Typ. 5V Very Low Power | 1.50         |
| 6514 J-5 1KX4-CMOS Super Low<br>Power 350 n.s. Similar to 2114<br>Same Pin Out                | 2.95         |
| 8108-5 1KX8 NMOS 5V 500 NS<br>22 Pin  | 2.50         |

4K STATIC RAMS  
LESS THAN 94c EACH  
MK4104J-4 - 250 N.S. 18 Pin Ceramic  
Computer Mfg. Surplus. PRIME. Fully  
static easy to Use. Has Same Pin Out as  
TMS4044, but slightly different timing.  
With Specs. (Mostek)

8 for 8.95 32 for 29.95  
**VERY LOW POWER!**

### DYNAMIC RAM

|  |               |
|--|---------------|
| 5280N-5 (2107B-4 - TMS4060)<br>4KX1 22 Pin | 8/3.95        |
| 4027-4KX1-250 n.s.                         | 1.75          |
| 4116-16KX1-200 n.s.                        | 8/14.95       |
| 4164+ +5v 64K                              | 12.95 8/79.95 |

### PRECISION HYBRID OSCILLATOR MODULE

Has both 1 MHz and 2 MHz TTL - outputs  
Hermetically sealed - Ultra high stability over  
wide temp. range - originally cost over \$40.00  
each - we made a super purchase from a major  
computer manufacturer - 5 Volt operation - fits  
standard 24 pin socket - Manufactured by  
Motorola oscillator division 7.50 (w/data)  
MC6871A 3/20.00

### SOCKETS

|                    |         |
|--------------------|---------|
| Low Profile Solder |         |
| 8 Pin              | 13/1.00 |
| 14 Pin             | 10/1.00 |
| 16 Pin             | 8/1.00  |
| 18 Pin             | 8/1.00  |
| 20 Pin             | 7/1.00  |
| 24 Pin             | 6/1.00  |
| 28 Pin             | 6/1.00  |
| 40 Pin             | 5/1.00  |

Buy \$10 Get \$1.00  
FREE CHOICE

### CPU

|            |       |
|------------|-------|
| 8035       | 6.95  |
| 8039       | 7.95  |
| 8748 Intel | 15.95 |

### 74LS

|           |            |            |
|-----------|------------|------------|
| LS00 .24  | LS125 .95  | LS243 1.49 |
| LS02 .24  | LS138 .79  | LS244 .99  |
| LS04 .24  | LS139 .79  | LS245 1.95 |
| LS05 .24  | LS151 .79  | LS257 .79  |
| LS08 .24  | LS153 .79  | LS266 .59  |
| LS10 .24  | LS154 1.75 | LS283 .99  |
| LS14 .89  | LS157 .79  | LS290 .99  |
| LS20 .24  | LS161 .99  | LS293 1.75 |
| LS27 .24  | LS164 .99  | LS298 .89  |
| LS30 .24  | LS166 .99  | LS367 .79  |
| LS32 .36  | LS175 .89  | LS368 .79  |
| LS42 .49  | LS181 1.99 | LS373 .99  |
| LS74 .44  | LS192 .89  | LS374 1.49 |
| LS85 .95  | LS193 .89  | LS375 1.49 |
| LS86 .39  | LS221 1.10 | LS377 1.19 |
| LS90 .69  | LS240 .99  | LS390 1.19 |
| LS109 .39 | LS241 .99  | LS393 1.19 |
| LS123 .99 | LS242 1.49 | LS399 .99  |

### MISCELLANEOUS

|   |        |
|---|--------|
| AY3-8910-Sound Chip with 60<br>page data manual | 12.95  |
| DM8131 6 Bit Unfilled Bus<br>Comparator         | 2.99   |
| 8 Pin Dip Shunt                                 | 3/1.00 |
| TR1602-UART same as<br>AY5-1013                 | 1.99   |
| IM6402-+5v High speed<br>UART-AY5-1013 pin out  | 2.00   |
| MC1408L6 D to A Converter<br>8 Bit              | 1.79   |
| AD551J D to A Converter<br>10 Bit               | 1.79   |
| 1771 Single Density FDC                         | 22.50  |
| 1791 Double Density FDC                         | 29.95  |
| 5027-CRT Controller -<br>Programmable - 24 x 80 | 14.95  |
| 68845 - Motorola (HD46505SP)<br>CRT Controller  | 17.59  |
| 82S123-32X8 Tri State Bi polar<br>PROM          | 1.99   |
| 82S129 Tri State Bi Polar Prom                  | 1.99   |

### EPROM

|  |       |
|--|-------|
| 1702A 256X8 1 us                                   | 2.50  |
| 2708 1KX8 450 n.s.                                 | 2.95  |
| 27A08 1KX8 350 n.s.                                | 3.95  |
| 2716 2KX8+5v 450 n.s.<br>(Buy 2 Get 1 FREE.)       | 5.95  |
| 2716-1 2KX8+5v 350 n.s.                            | 7.95  |
| 2732 4KX8 450 n.s. Intel Pin Out                   | 9.95  |
| 2732A-3 4K x 8 350 n.s.<br>Intel Pin Out Low Power | 11.95 |
| 2532 4KX8 450 n.s. T.I. Pin Out                    | 9.95  |

### Z80

|                       |       |
|-----------------------|-------|
| Z80 2.5 MHz CPU       | 4.95  |
| Z80DMA-DMA Controller | 9.95  |
| Z80PIO - Parallel     | 5.95  |
| Z80SIO/O Chan. Ser.   | 16.95 |
| Z80A-4MHz CPU         | 8.95  |
| Z80A SIO/O            | 19.95 |

CALL OR WRITE FOR PRICES ON CMOS-8080 - BIT SLICE - TTL - 74S - CRYSTALS - DIP SWITCHES  
TERMS: Add \$1.50 postage, we pay balance. Orders over \$50.00 add 85c for insurance. No C.O.D. Texas Res. add 5% Tax. 90 Day Money Back Guarantee on  
all items. All items subject to prior sale. Prices subject to change without notice. Foreign order - U.S. funds only. We cannot ship to Mexico. Countries other  
than Canada, add \$3.50 shipping and handling.

### MICROWAVE EQUIPMENT

HI-GAIN, LOW NOISE, 2.1-2.4GHz.  
MICROWAVE RECEIVING SYSTEM  
COMPLETE ---READY TO INSTALL.  
INCLUDES 20" PARABOLIC ANTENNA,  
DOWN CONVERTER, POWER SUPPLY,  
ALL CABLES AND CONNECTORS WITH  
COMPLETE INSTRUCTIONS FOR EASY  
INSTALLATION.  
COMPLETE SYSTEM - U.S. SHIPPING FREE - \$119  
BUY 5 SYSTEMS at \$104 each  
(six month limited warranty)

**SUPER LED's**  
2 amp. rating w/heat sink  
ME2 IR (a) 25A pulse  
ME5 IR (b)  
MV4 RED (a) \$ 4.95 each  
6-32 stud

**RESISTOR SALE**  
.25W 5% carbon film - \$1.50 per 100 (one value)  
all standard values from \$ 12 per 1000  
2.7 to 4.7M ohms

|          |  |        |
|----------|--|--------|
| 8085     | NEC CERAMIC 40 PIN MICROPROCESSOR  | \$6.95 |
| HM5290J  | NSC 16Kx1 DYNAMIC RAM (4116) CERAMIC   | 2.95   |
| 92758    | INTEL EPROM 1Kx8 24 PIN CERAMIC  | 3.95   |
| TR1AC    | RCA 8 AMP 60DY TO-220 TAB CASE   | .75    |
| VOY      | VOICE ACTUATED SW. (SCR, MIC, AMP.)  | .95    |
| H1A-2    | G.E. OPTO ISOLATOR 6 PIN DIP   | .25    |
| 5101     | 256X4 CMOS RANDOM ACCESS MEMORY DIP  | .95    |
| TR1AC    | 25 AMP 40DY ON 3"x6" ALUMINUM HS   | 2.95   |
| 7402     | TTL QUAD 2 IN NOR GATE DIP   | .10    |
| 7430     | TTL 8 INPUT NAND GATE DIP  | .10    |
| 7440     | TTL DUAL 4 INPUT BUFFER DIP  | .10    |
| 70-92    | PNP TRANSISTOR PAK 100 PRIME FOR   | 5.00   |
| LM747    | DUAL 741 OPERATIONAL AMPLIFIER DIP   | .50    |
| LH0021   | NSC 1 AMP OPERATIONAL AMPLIFIER TO3  | 5.00   |
| 2504T    | 1024 BIT DYNAMIC SHIFT REGISTER TO-5   | 1.00   |
| 2416     | INTEL 256x24 CHARGE COUPLED MEMORY   | 2.50   |
| 5244     | INTEL DRIVER FOR ABOVE MEMORY  | 3.50   |
| 12P15/15 | DC TO DC CONVERTER - 12VDC TO DUAL<br>15V AT 40MA OUTPUT, CAN BE PLUS<br>OR MINUS 15 OR 30V 24 PIN DIP | 7.95   |

4811 MYRTLE AVE  
PO BOX 41778  
Sacramento, Ca.  
95841  
we pay post on orders for \$10 or more  
orders must include in post BAC, MC are  
not prepaid and shipping is added.  
916 334 2161

**BABYLON  
ELECTRONICS**

CIRCLE 102 ON FREE INFORMATION CARD


# Poly Paks<sup>INC</sup>

Quality Electronics For Less!

BRAND NEW!  
FIRST TIME ANYWHERE!
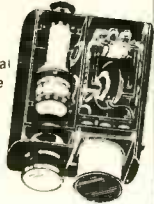
## IR SCIENTIFIC INFRARED VIEWER KIT

- An Easy To Assemble Kit
- Everything You Need Including Comprehensive Instruction Manual
- Lightweight, Binocular-Type Case
- Factory Preselected & Pretested Components
- For: Night Surveillance, IR Communications & Control, Document Authentication, Thermal Viewing, & More



See in the Dark!

Special Introductory Price **\$169.95**

Shipping & Handling add \$4 per unit (\$6 outside U.S.)  
MASS. RES. ADD 5% SALES TAX.

### SPECIFICATIONS:

- Image Converter — type 6032
- Spectral Response — 500 to 1200 nanometers (800 max)
- Resolution — 50 lines/mm
- Magnification — 3X
- Focus Range — 3 ft. to infinity
- Lens — 150mm, 1.3-10° field infrared telephoto and 10 X Ramsden Eyepiece
- Infrared Source — 900 nanometer, 4500 max. candlepower
- Case Size — 7 3/4" X 6 1/2" X 2 3/4"
- Power Requirement — 6 V DC (4 "D" cells or equiv.)

Ask for FREE POLY PAKS CATALOG

Order by Mail or Call TOLL FREE

**800-343-3086**

Mass. Res. Call 617-245-3828

ORDER SHIPPED IN 24 HRS.

Poly Paks  
P.O. Box 942, RE-9  
S. Lynnfield, MA 01940



CIRCLE 87 ON FREE INFORMATION CARD

over 1600 products!

includes technical tips & information

## FREE CATALOG

### Burglar/Fire Alarms Security Products



- Alarm Controls • Remote Stations
- Infrared • Motion Detectors • Sirens
- Microwave • CCTV • Fire Detectors
- Vehicle Alarms • Phone Dialers
- Key Locks • Wireless Components
- Magnetic Contacts • Glass Protection
- Lights • System Parts • Tools • Books
- Bells • Ionization Smoke Detectors

**mountain west**

4215 N. 16th Street Dept. RE-9  
Phoenix, AZ 85016  
1-800-528-6169

CIRCLE 97 ON FREE INFORMATION CARD

(602) 266-9758 (602) 234-3026



ARIZONA ELECTRONIC  
SURPLUS



6835 N. 16th St. • Phoenix, AZ 85016

### MICRO WAVE DOWN CONVERTER KIT (HMR II type)



\$39.95

- PC Bd, 3-MRF901's, 2-MBD 101's,
- 1 Thermistor, 1 Choke, 3-Chip Caps,
- 1 "F" Connector, 8 Resistors
- + Instructions

### POWER SUPPLY

12-18v


D.C.

\$19.90



BUY BOTH FOR ONLY **\$53.99**

### SPEAKER BOX

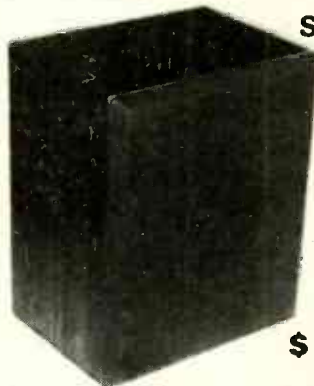

w/5" SPEAKER

\$11.95

### PULSE RATE INDICATORS

USED FOR HEART MONITORS  
100% Functional

\$19.95



- Includes:
- 5" LCD Readout
- ICL 7106 CPL A-D Decoder Driver
- MC 14016
- MC 14013

- MC 14584
- LM 32 YN
- TL 064 CN
- Piezo Buzzer
- 9 V. Batt. Clip
- Misc. Elect. Components

### NEW PLASTIC CASE

Made for Heart Monitor above.

\$1.55

- Includes:
- 9 V. Batt. Holder
- Front Bezel

Excellent for Frequency Counter.



### 4" LINE CORD



45¢

ALL ORDERS SHIPPED SAME DAY VIA UPS

Postage & Handling Not Included

(602) 266-9758 (602) 234-3026

CIRCLE 92 ON FREE INFORMATION CARD

DON'T FORGET



USE YOUR READER SERVICE CARD

## Summer Sale!!

### I/O "SELECTRIC" TYPEWRITER

REDUCED!!! (This Month Only)

Regularly \$399.00



SAVE \$50!!!

**\$349.00** EA.

- Fully Operational
- TTL Input/Output Level
- USE AS A TYPEWRITER
- Software or Hardware Driven
- Spare Parts Available, Too
- Full 15" Platen
- IBM Model 745

These fabulous typewriter/printers originally cost over \$1000.00 each!! Each machine is fully tested and operational and only requires 5 VDC and 24 VDC for I/O capability. Electronic Repeat (when activated) is capable of repeating ANY character or key. Soon we will be offering software, then hardware interfaces for these terrific machines, meanwhile SAVE 50 BUCKS.

Only \$349.00 ea.



### DIGITAL MUSICAL KEYBOARDS

Only **\$69.00** Each

Built to specifications for ARP, the world famous Synthesizer Maker. Features 3 octaves (36 keys) with TTL Decoded 6-bit output which determines the note and octave of a pressed key. Excellent for keyboard inputs to Micro-computer & Digital Synthesizers and more. NEW, UNUSED, keyboard with Electronics.

Write or Call for Our FREE Exciting NEW FLYER!!!

Computer Products & Peripherals Unlimited

WAREHOUSE:  
18 Granite St. Waverhill, Mass. 01830

MAIL ORDERS:  
Box 204, Newton, New Hampshire 03858

TELEPHONE ORDERS:  
617/372-8637  
Sorry, No Collect Calls  
Mastercard & VISA Accepted

CIRCLE 103 ON FREE INFORMATION CARD


# SPARTAN Electronics Inc.



CALL (516) 499-9500  
MAIL

6094 Jericho Tpke.  
Commack, N.Y. 11725

## Remote T.V. Converter

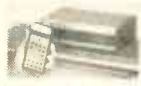

PHILIPS 139.95 Ea.  
4 & up 125.00  
60 Channel  
Wireless Control

## Commodore Color-Sound-Graphics



VIC-20  
\$259.


Cassette Player \$69.00

## Logic Probe

## Global Specialties #LP-2

\$28.49

DTL/TTL/CMOS

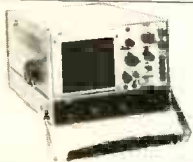

BK PRECISION

\$991

## DELUXE 40 CHANNEL VHF to UHF Block Converter

\$38.95 ea.  
Features accessible fine tuning knob included: matching X former and two cables

## Surge Stopper Brooks

4 Outlet w/circuit bkr. led/sw \$59.79  
1 Outlet \$43.50

Now you can have Maximum Protection for your sensitive electronic equipment.



## Refurbished Monitors 12" diagonal 39.95



## Atari 800 w/16K RAM \$659



## Atari 400 w/16K \$289

## 42 Channel CATV Converter

w/on/off Fine Tuning \$94.95



## 40 Channel VHF to UHF Block Converter



28.95 Ea.  
24.95 4 & up

## Volume Discounts


|  |                   |         |
|--|-------------------|---------|
| Min. Order \$10.00                       | to 75.00          | \$2.50  |
| International shipping Add'l.            | 76.00 to 250.00   | \$4.50  |
| Prices subject to change without notice. | 251.00 to 500.00  | \$8.00  |
| COD 2.00 Extra                           | 501.00 to 750.00  | \$8.50  |
|  | 751.00 to 1000.00 | \$12.00 |
|  | Over 1000.00      | \$12.50 |

(516) 499-9500  
Mon Th 9-8  
Tu W F 9-6  
Sa 9:30-5

# BEC BULLET ELECTRONICS

P.O. BOX 401244R GARLAND, TX. 75040 (214) 278-3553

## Sound Effects Kit \$18.50

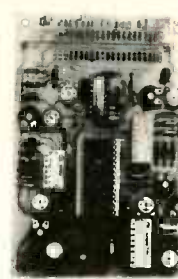

The SE-01 is a complete kit that contains all the parts to build a programmable sound effects generator. Designed around the new Texas Instruments SN76477 Sound Chip, the board provides banks of MINI DIP switches and pots to program the various combinations of the SIF Oscillator, VCO, Noise, One Shot, and Envelope Controls. A Quad Op Amp IC is used to implement an Adjustable Pulse Generator, Level Comparator and Multiplex Oscillator for even more versatility. The 3 1/2 x 5 PC Board features a prototype area to allow for user added circuitry. Easily programmed to duplicate Explosions, Phasor Guns, Steam Trains, or almost an infinite number of other sounds. The unit has multiple applications. The low price includes all parts.

assembly manual, programming charts, and detailed 76477 chip specifications. It runs on a 9V battery (not included). On board 100mW amp will drive a small speaker directly, or the unit can be connected to your stereo with incredible results! (Speaker not included) 76477 is included. Available separately for \$3.15 each.

## The Super Music Maker

REVISION 2 \$24.95 (Basic Kit)

SEE SPECIAL OFFER BELOW



- Comes with 25 pre-programmed tunes.
- On board 7 watt amplifier drives 8 ohm speaker directly.
- Works on 12VAC or 12 VDC.
- Uses either 2708 or 2716 EPROM for expanded tune playing capability. Listing available pre-programmed ROMs.

A true electronic music maker based on a microprocessor chip. The Super Music Maker is the only kit that allows easy addition of pre-programmed tunes by plugging in one memory chip (ROM). Over 20 different ROM's with over 500 tunes are available. Use the kit for a Car Horn, Doorbell, Door Announcer, etc. If you have an EPROM programmer our manual tells you how to program your own tunes. Kit includes quality plated and drilled PC Board and all components.

### OPTIONAL ACCESSORIES

|  |          |
|--|----------|
| DIP SWITCHES One 8 pos., one 5 pos., for tune address  | 2.00/set |
| WALL PLUG TRANSFORMER For operation on 117VAC house current  | 3.00     |
| INJECTION MOLDED PLASTIC CASE w/custom front & rear panels, hardware and 2 five pos. rotary switches (replaces DIP switches) | 8.00     |
| HORN SPEAKER 8 watt, 8 Ohm with mounting bracket   | 6.25     |

### SPECIAL OFFER

Buy a Super Music Maker kit for \$24.95 and get FREE, a 2708 ROM pre-programmed with 35 popular tunes. This offer gives you over 60 songs to choose from!


## 7 Watt Audio Amp Kit \$6.95

SMALL, SINGLE HYBRID IC AND COMPONENTS FIT ON A 2" x 3" PC BOARD (INCLUDED). RUNS ON 12VDC. GREAT FOR ANY PROJECT THAT NEEDS AN INEXPENSIVE AMP. LESS THAN 3% THD @ 5 WATTS. COMPATIBLE WITH SE-01 SOUND KIT.
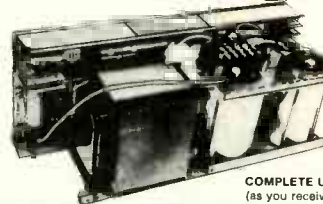
## THE PRESIDENT SAYS: "HOGWASH!!"

After taking one look at the TRIPUT POWER SUPPLY our engineer declared that the units were worth several hundred dollars each. He pointed out the engineering, high quality construction and state-of-the-art integrated design in support of his position. The President of BEC more pragmatically pointed out the already full warehouse and the two trailer truck loads of power supplies waiting in the parking lot, and set the price to move them QUICKLY!

3 OUTPUTS  
12V @ 8A (12A Int.)  
5V @ 10A  
-12V @ 5A  
INPUT 105 - 125VAC



COMPLETE UNIT (as you receive it)

62.50

Plus \$5.00 Freight

21 lbs. 6 x 5 1/2 x 12

ONE TIME OFFER! LIMIT TWO (2) SUPPLIES PER CUSTOMER

- UNIT IS COMPLETELY ASSEMBLED!
- Fused primary and DC sections
- HUGE SHIELDED TRANSFORMER
- 2% Load & Line Regulation
- Low Ripple < 100mv
- Short Circuit Protection
- Overvoltage Protection on all three outputs
- 25A Bridge Rectifier
- Over 60,000 mfd of filter
- High Efficiency Switching Regulator reduces heatsink area
- Schematics and service guide included
- Thermal Shutdown
- Status LED's (3)

- COD MINIMUM \$20.00 • ADD \$2.50 FOR COD'S
- UPS DELIVERY ADDRESS MUST ACCOMPANY ALL COD ORDERS
- \$1.00 HANDLING ON ORDERS UNDER \$10.00
- VISA, MC CARDS OR CHECK
- ADD 6% FOR SHIPPING
- TEXAS RESIDENTS ADD 5% STATE SALES TAX
- ALL FOREIGN ORDERS ADD 25% FOR SHIPPING (CANADA 15%) NO FOREIGN COD'S
- CALL (214) 278-3553 TO PLACE CREDIT CARD OR COD ORDER

# Macro PROFITS! MICROWAVE ANTENNAS at micro \$19<sup>95</sup> to \$169<sup>95</sup>

## Amateur 32-Element Yagi Antenna

- Not a kit, so it's easier to sell • 1.9-2.5 Ghz
- 38 1/2" long • Die-cast waterproof aluminum housing • Withstands temps -40° to +140°F. • 50-ohm type "N" connector • Mounting hardware included.

Only \$19<sup>95</sup>

## 2 Ghz MICROWAVE ANTENNA

with 52 dB Overall Gain

- Built-in down converters • Tune 1.9-2.5 Ghz • Operates on channels 2-6 • 22 dB gain resonant disc antenna • Standard 12-16 vdc power supply • Mounting bracket for horizontal or vertical polarity • Comes with: 60' coax with connectors, 3' jumper cable, 75-300 ohm and 300-75 ohm adapters, complete instruction.

\$129<sup>95</sup>

## LONG-RANGE MICROWAVE ANTENNAS with Separate Down Converters FULL-YEAR WARRANTIES!

58 dB Gain

Just \$144<sup>95</sup>

62 dB Gain

Only \$169<sup>95</sup>

- Tuneable temp-compensated L.O. • Power supply with built-in A-B switch
- High gain, low noise figures • Convenient mounting tabs • Weather-resistant housings • For distant or low signal areas • Two microwave pre-amp stages • 2.1-2.3 Ghz • 20 Mhz input band-width • Noise figure: 5 dB
- TV channels 2-6 • 75-ohm type "F" output • 50-ohm type "N" input impedance • Aluminum housing • Withstands temps from -40° to +140°F.

Dealer inquiries invited.

## East Coast: N.C.I. INC.

79-59 264th St.  
Floral Park, N.Y. 11004  
212-929-3505/212-544-5990

## West Coast: Galaxy Electronics


600 N. 61st Ave.  
Glendale, Arizona 85301  
602-247-1151

# KNAPCO

|   |  |  |
|---|--|--|
| <b>G.E. MOV Spike Eliminators</b><br>10/9.90 <b>\$1.29</b><br> | <b>2 1/2" Meters</b><br>0-15 VDC<br>0-20 VDC<br>0-150 VAC<br>30-0-30 DCA<br>Any 1<br><b>\$5.95</b>   | <b>BROAD BAND AMPS.</b><br>TUSA # DAT 25<br>25 DB. GAIN<br>75 OHM<br>50 TO 890 MHZ.<br><b>\$23.50</b>  |
| <b>Transformer</b><br>Dual bobbin<br>30V.<br>-14V. 1.5 AMP<br>3" Mount Centers 2" high<br><b>\$3.00</b>   | <b>Tri-Color LEDS</b><br>Red/Green reverse volt.<br>Yellow A.C.<br>2/1.50  | <b>Voltage Regulators</b><br>-5V. 7805<br>-5V. 79M05<br>+6V. 7806<br>+12V. 7812<br><b>5/5.50 10/9.95</b>   |
| <b>Chassis (H.D.)</b><br>Fantastic!<br>4" x 8" x 2 1/4" H.<br><b>79¢</b>  | <b>Infrared Emitter and Photo Diode Detector</b><br>XC880-A<br>TIL413 short leads 1 pr.<br><b>\$2.00</b><br><b>Mura Cordless Telephone</b><br>As is Complete with schematics<br><b>\$43.50</b>   | <b>MOTOROLA PIEZO SPEAKERS</b><br>3/4" SPECIAL RESPONSE<br>60 TO 30,000 Hz<br><b>\$6.95</b>  |
| <b>115 V. BLOCK FANS</b><br>4 1/2" SQ. # FAN 41<br>3" SQ. # FAN 31<br><b>\$6.95</b>   | <b>C &amp; K Sub Mini</b><br>N.O. Pushbutton Switch<br>10/3.00 #8631   | <b>KEMET CHIP CAPS</b><br>.018 / 100 V.<br>MATCH PAIRS<br>MIL. SPEC.<br>1.49 PR.   |
| <b>ASSORTED LEECRAFT INDICATORS</b><br>#31 (SNAP-IN) RED, AMBER, DUALS 115V.<br><b>10/3.95</b>  | <b>General Instrument Varactor Tuners</b><br>Your Choice<br>VHF - UHF<br><b>\$22.50</b><br><b>Mini Switches</b><br>Micro Switch<br>SPDT w/long blue paddle<br><b>79¢</b><br><b>Compu-Lite</b><br>red push (Illuminated)<br>mom #849-1191<br><b>69¢</b> | <b>Voltage Regulator Boards</b><br>Just hook up to transformer<br>12V. or 9V.1.5A<br><b>\$1.29</b><br><b>RFI FILTERS</b><br>2 AMP. HOPKINS # F-85010<br><b>\$1.95</b><br>6 AMP. CORCOM # 6EF1<br><b>\$2.95</b><br><b>Dip Tantalum Caps</b><br>6.8, 10, 15, 22, 33, 47, @ 63V<br>22, 68 @ 10V<br>1.5, 3.3, 4.7, 6.8 @ 16V<br>15 @ 20V.<br>.47, .68, 1.5, 2.2, 3.3, 4.7, 6.8 @ 35V<br>22, 68, 1 @ 50V dipped and solid<br><b>29¢</b> |
| <b>TRANSFORMER</b><br>36V. 200 MA.<br><b>99¢</b><br><b>SEND FOR FREE 1982 CATALOG</b><br>or call us at<br>(813) 392-0406                        | FOREIGN CATALOGS SEND \$1.00<br><b>H.J. Knapp of Florida, Inc.</b><br>4750 96th St. N. St. Petersburg, Florida 33708   | <b>Piezo Elements</b><br>Fantastic Mike-Speaker<br><b>39¢</b><br><b>Audio Amplifier</b><br>8 watt<br><b>\$5.95</b>   |

CIRCLE 90 ON FREE INFORMATION CARD
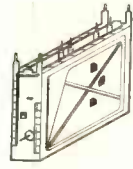
## MORE GAIN Than a Mitsumi Tuner PHILIPS VARACTOR TUNER — \$23.95




MODEL ELC 1045  
 FREQ. RANGE UHF 470-889 MHZ  
 CHANNEL 14-83  
 OUTPUT CHANNEL 3  
 75 OHM INPUT

|          |   |         |
|----------|---|---------|
| Part No. | Philips UHF Tuner ELC 1045                                | \$23.95 |
| DSW10    | Printed Circuit Board, Pre-drilled                        | \$15.00 |
| DSW30    | Glass Epoxy   | \$4.95  |
| DSW30    | P.C.B. Potentiometers 5-10K, 1-5K                         | \$5.95  |
| DSW40    | Resistor Kit 1/4 watt 5%                                  | \$4.95  |
| DSW50    | Carbon Resistors 32 pcs.                                  | \$4.95  |
| DSW50    | Panel Mount Potentiometers                                | \$2.95  |
| DSW60    | 2-10K and Knobs   | \$2.95  |
| DSW70    | IC's 7 pcs., 1 Rectifier,                                 | \$15.95 |
| DSW70    | 2 Regulators & 1 Heat Sink                                | \$4.95  |
| DSW80    | Electrolytic Cap Kit, 8 pcs.                              | \$4.95  |
| DSW90    | Ceramic Cap Kit, 33 pcs.                                  | \$6.95  |
| DSW90    | Power Transformer   | \$3.95  |
| DSW100   | Variable Trimmer Kit, 4 pcs.                              | \$3.95  |
| DSW100   | Coil Kit, 2-18 uh, 1 variable 33 uh                       | \$1.95  |
| DSW110   | +1 - +37-12 Toroid + 26 wire                              | \$4.95  |
| DSW120   | I.C. Sockets 5-8 pins, 2-14 pin                           | \$4.95  |
| DSW130   | PRI-117Vac, SEC 24Vac, 1 amp                              | \$5.95  |
| DSW140   | Speaker, Oval 8 ohm                                       | \$3.00  |
| DSW140   | Misc. Parts, Hardware & Hookwire                          | \$7.95  |
| DSW140   | Ant. Term, Switch Dpdt, Fuse, Fuseholder, Line Cord, etc. | \$7.95  |

When Ordering All Items  
 DSW10-D140 Total Price \$99.95


## R.F. Modulator

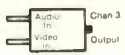

Combine both audio and video output onto channel 3 or 4 of your T.V. set. Single I.C. chip (MC 1374) makes for quick and easy assembly. Single adjustment control! A must for every video recording or computer enthusiast.

VH-0 Kit ..... \$19.95

## UHF T.V. Preamp

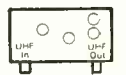

Features:  
 • 25 dB gain!  
 • Kit

Your reception will dramatically improve! This unit will enable you to pull in signals you never knew were there!

For both indoor and outdoor use. Input and output impedance 75 ohm. No adjustment! Easy assembly.

JH-0 Kit ..... \$22.95

## Microwave Receiver 1.9-2.5 GHz



PS-1 Assembled 32 element antenna ..... \$19.95  
 PS-2 20 dB gain microwave receiver kit with variable power supply kit ..... \$50.00  
 PS-3 Complete package PS-1 & PS-2 ..... \$65.00

Mounting Hardware Included

Available by Mail Order only  
 Send check or money order to

### STAVIS ELECTRONICS, INC.

912 W. Touhy Avenue  
 Park Ridge, Illinois 60068  
 (312) 692-5223

Minimum order \$15.00. Add 10% shipping on orders under \$35.00. Orders over \$35.00, add 5%.  
 Catalog - \$1.00. Visa & Mastercharge acceptable

CIRCLE 93 ON FREE INFORMATION CARD

|  |  |   |
|--|--|---|
| <b>\$6.95</b><br>8-1020<br>8 OZ<br> <b>UHF TUNER</b><br>TOP QUALITY, UHF TUNERS ARE BRAND NEW, TESTED, TOP PERFORMERS! GREAT FOR REPLACEMENT USE, CABLE CONVERTERS, DECRYPTERS, HAM BAND CONVERTERS, ETC. ETC.  | <b>DIP SOCKETS</b><br>8 PIN 16¢<br>S-0800<br>14 PIN 18¢<br>S-1400<br>16 PIN 20¢<br>S-1600<br>18 PIN 25¢<br>S-1800<br>24 PIN 38¢<br>S-2400<br>28 PIN 45¢<br>S-2800<br>40 PIN 55¢<br>S-4000  | <b>\$15.95</b><br> <b>POWER SUPPLIES</b><br>±15 VDC 100 MA POWER MODULE<br>PC MOUNT, 120 VAC IN, ±15 VDC WELL REGULATED OUT.<br>2-1/2" X 3-1/2" X 7/8" CARBON MODEL # D-15-100                         |
| <b>\$1.75</b><br>C-7030<br>50 PIN<br>C-7035<br>20 PIN<br><b>SOCKET JUMPER CONNECTORS</b><br>ACCEPT RIBBON CABLE, CLINCH TO PERMANENTLY CONNECT. BOTH HAVE GOLD CONTACTS.   | <b>12 VDC RELAY</b><br>20 AMP 3/4 HP CONTACTS<br>P B B AMF TYPE<br>KRP 3 DH WITH ONE LARGE SPST N.O. CONTACT - GREAT FOR MOTORS, AUTOMOTIVE, HEAVY EQUIPMENT<br>OCTAL BASE<br>4 OZ<br>R-1208<br><b>\$2.25</b>  | <b>WIRE TIES</b><br>7-1/4" LOCKING WHITE NYLON<br>3 LB/1000<br>100/\$1.50<br>1000/\$10<br>10,000/\$90   |
| <b>Brand New 115 VAC 8 Track TAPE DECK WITH PLAYBACK AMP</b><br> COMPLETE 8 TRACK TRANSPORT<br><b>\$6.95</b><br>QUALITY BUILT BY MOTOROLA WITH AUTO TURN ON, END OF TAPE SENSOR, AUTO TRACK CHANGE, 115 VAC CAPACITOR START MOTOR, STEREO R/P HEAD AND ±12 VDC PLAY BACK ELECTRONICS GREAT FOR HOME/PHONE ANSWERS, ROBOTS, ETC. | <b>BCD Thumbwheel SWITCH</b><br>WITH COMPLIMENT 0-9<br>B-2124<br>GOLD CONTACTS STD SIZE CAN BE STACKED TO ANY WIDTH OUTPUT IS 1-2-4-8 WITH COMPLIMENT<br><b>\$1.25</b>   | <b>Wire Wrap WIRE</b><br>SILVER PLATED KYNAR 30 AWG BLACK<br>10,000 FT SPOOL \$150.00<br>15,000 FT SPOOL \$205.00<br>20,000 FT SPOOL \$265.00   |
| <b>Stepping MOTORS</b><br>SIGMA MODEL NO. 20-2230200<br>FEATURES A STEP ANGLE OF 1.8°, MAX SPEED OF 4000 STEPS/SEC, 40 OZ-IN OF TORQUE, 9 WATTS DISSIPATION, ABSOLUTE ERROR OF 0.06%, NON-CUMULATIVE BRING YOUR ROBOTS TO LIFE, BUILD X-Y PLOTTERS, HAVE POSITIONAL FUN! THESE ARE NEW, CURRENT PRODUCTION, WITH A LIST PRICE OVER \$100.00!<br>M-2140 (1.3 LB)<br><b>\$10.00</b><br><b>FREE CATALOG</b>           | <b>ILLUMINATED INTERLOCKING 7-POSITION PUSH-BUTTON SWITCH</b><br>B-3017<br>SWITCHCRAFT ASSEMBLY ORIGINALLY COST OVER \$30. FEATURES DPDT EACH POSITION, WITH SILVER CONTACT LEAF SWITCHES THAT WILL OUTLIVE BOTH OF US! SOCKETS ACCEPT ANY T-3/4 PLATE GLASS BULB, FRONT REPLACEABLE. BUTTONS ARE 9" HI, 0.6 W, 4.4" WIDE OVERALL<br><b>\$4.95</b> | <b>ETCHANT Ammonium Persulfate</b><br>FAST AND EASY TO USE, MUCH CHEAPER THAN THE "OTHER" STUFF!! JUST MIX 1/2 POUND TO A GALLON OF WATER (1 OZ TO 1 PINT) AND ETCH!<br>THE WHITE CRYSTALS MAKE A CLEAR SOLUTION THAT TURNS BLUE WHEN 1 LB (MAKES 2 GAL.) FULL OF COPPER<br><b>\$1.95</b> |
| <b>Ribbon Cable</b><br>26 AWG<br>50 CONDUCTOR<br>1-9 FEET \$1.00/FT<br>10-24 FT 90/FT<br>25-99 FT 85/FT<br>100 & UP 80/FT<br>C-7C45  | <b>DIAMONDBACK ELECTRONICS COMPANY</b><br>PO BOX 12095<br>SARASOTA, FL. 33578<br>Phone Orders 813-953-2829<br>CONTINENTAL US ADD \$1.60 FOR THE FIRST LB & 50¢ FOR EACH EXTRA LB. WEST COAST ADD \$1.80 FOR THE FIRST LB & 50¢ FOR EACH ADDITIONAL LB.<br>*7 MINIMUM ORDER \$15 CREDIT CARD  | <b>ETCHANT Ammonium Persulfate</b><br>FAST AND EASY TO USE, MUCH CHEAPER THAN THE "OTHER" STUFF!! JUST MIX 1/2 POUND TO A GALLON OF WATER (1 OZ TO 1 PINT) AND ETCH!<br>THE WHITE CRYSTALS MAKE A CLEAR SOLUTION THAT TURNS BLUE WHEN 1 LB (MAKES 2 GAL.) FULL OF COPPER<br><b>\$1.95</b> |

CIRCLE 91 ON FREE INFORMATION CARD

SEPTEMBER 1982

133



ELECTRONICS CO., INC.

SEND OR CALL for your

# FREE Catalog

1982  
A 48 page handbook with 48 SUPER exciting, low cost, electronic projects.  
(Some projects as low as \$2.50).

CALL Toll-Free  
1-800-453-1708

Utah residents 1-801-628-3627

## NEW

These PPG Electronic Kits are available at your local electronic store.

### Kit #

- 801 POCKET DICE
- 802 SIGNAL INJECTOR
- 803 SPACE WAR GUN
- 804 METAL DETECTOR
- 805 LOGIC PROBE
- 806 BURGLAR ALARM
- 808 DECISION MAKER
- 809 LED PENDULUM METRONOME
- 811 DOUBLE DECISION MAKER
- 812 SIREN OSCILLATOR
- 814 ROBOT BLINKER
- 816 MINI-WINK
- 818 FISH CALLER
- 820 SHIMMER LIGHTS
- 821 CHRISTMAS TREE
- 822 ONE CHANNEL COLOR ORGAN
- 824 AUTOMATIC SIREN
- 826 FUZZ BOX
- 828 9-VOLT POWER SUPPLY
- 830 0-15 VOLT POWER SUPPLY
- 834 COLOR ORGAN 3-CHANNEL, 1-CONTROL
- 836 3-CHANNEL, 4-CONTROL COLOR ORGAN
- 838 12-VOLT POWER SUPPLY
- 840 VARIABLE STROBE LIGHT
- 842 12-VOLT COLOR ORGAN
- 844 T.V. JAMMER
- 846 12-VOLT SAFETY STROBE FLASHER
- 850 WHOOPER ALARM
- 852 COMBINATION LOCK/ALARM CONTROL
- 856 ELECTRONIC TENNIS
- 858 DIGITAL ROULETTE
- 860 5-30 VOLT REGULATED POWER SUPPLY
- 861 BIG SOUND PORTABLE ORGAN
- 862 FULL-WAVE MOTOR SPEED CONTROL
- 866 DIGITAL SLOT MACHINE
- 868 DIGITAL OICE
- 870 NERVE TESTER
- 876 8-DIGIT DIGITAL CLOCK
- 878 DIGITAL BIRD
- 880 12-VOLT, 2-AMP REGULATED POWER SUPPLY
- 882 MUSICAL HORN
- 884 SOUND ACTIVATED COLOR ORGAN, 1-CHANNEL
- 886 AUDIO AMP/INTERCOM
- 888 LIBRARIAN TORMENTOR
- 890 STOP-ACTION TIMING TESTER
- 892 TELEPHONE HOLD BUTTON
- 894 PHASOR GUN/SOUND GENERATOR
- 898 BINARY CLOCK

Also available, complete Basic Electronics Course

## Build Some TODAY!

PPG Electronics Co., Inc.  
791 Red Rock Road,  
St. George, Utah, 84770

Special Prices For Educators

## FREE CATALOG



- Precision Hand Tools
- Breadboarding Kits
- Digital Multimeters
- Oscilloscopes
- Test Probes
- Tool Kits
- Soldering Supplies
- Solder Suckers

Features 84 pages of hard-to-find products for building, testing, and repairing electronics equipment. These are quality, brand name products used by big electronics companies. Contains hundreds of photos, detailed descriptions, and pricing. Most items are discounted at big savings. Everything is easy to order by phone or mail, ready for immediate delivery, and fully guaranteed. VISA and Master Card accepted.


Contact East, Dept. 0158  
7 Cypress Drive, P.O. Box 160  
Burlington, MA 01803

In a hurry to receive your catalog?  
Call (617) 272-5051

# We need your support. Your gift is the gift of love.

 **American Heart Association**  
WE'RE FIGHTING FOR YOUR LIFE

## MORE GAIN THAN A VARACTOR UHF TUNER

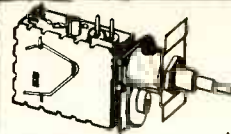

**SATISFACTION GUARANTEED**

**\$15.00**

Freq. Range UHF470-889MHz Channels 14-83 Output Channel 3.

Available on request: Ch 2 or 4.

Part No. B20  
Modified High Gain Tuner. . . . . **\$15.00**

1. The first thing we do is change the standard diode found in every tuner to a Hot Carrier Diode.
2. The tuners output is then measured and compared to our computer derived chart from which we determine the correct value coil to add across the IF output for maximum Pre-Peaked gain.
3. The tuner is fed a standard 10db antenna input, and while monitoring the output on our Spectrum Analyzer, the tuner is tuned to the desired channel and its oscillator is offset for the desired output frequency as follows:  
Ch. 2:58Mhz Ch. 3: 63Mhz Ch. 4: 68Mhz  
We call this step peaking because the tuners output looks like a peak on our spectrum analyzer and the highest point of that peak is actually adjusted for the desired output.
4. Finally, we measure the tuners output one more time which is again compared to our computer derived performance chart to ascertain the correct value of the second coil which is added to the tuners internal connections.

This procedure was developed by GILCO and its our computer derived performance charts that make our tuner better. That's because almost every tuner gets a different value coil before it's peaked and then a different value coil after it's peaked. The combinations are endless and the way we determine the values is our secret.

### PRINTED CIRCUIT BOARDS

Part No. B21 Printed Circuit Board. . . . . **\$17.00**

1. This Printed Circuit Board uses only one jumper, others use 9.
2. The component layout is screen printed on the Component side of the pre-drilled P/C Board.
3. The solder side of the P/C Board is covered with High Temperature Solder Resist for ease of assembly.
4. This P/C board was designed to take advantage of the Gilco High Gain Tuner which means its circuitry is simpler and more efficient than those circuits that require inferior Varactor Tuners.

### ELECTRONIC PARTS KITS

Part No. B22 Complete Parts Kit. . . . . **\$80.00**

All resistors (30), Potentiometers (1-5K, 3-10K), Panel Mount Potentiometer (10K), Electrolytic Capacitors (6), Ceramic and Mylar Disc Capacitors (35), Variable Capacitors (4), All Integrated Circuits (7), Voltage Regulator, Heat Sink, Diodes (4), IC Sockets (4-8 pin, 3-14 pin), Power Transformer (24V/1A), Coil Kit with No. 26 wire (4), Speaker (4" 3 Oz.), Standoffs, Coaxial cable, All misc. Hardware, etc. All parts are individually packaged and labeled.

All components including the wire, Hardware, Coaxial Cable and heat sinks are included in the parts kit. This means your assembly time from start to finish is only 4 hours.

Order all 3, B20, B21, B22. . . . . **110.00**

Order 5 each, B20, B21, B22. . . . . **95.00/set**

### ACCESSORIES: AMPLIFIERS

- Part No.
- |     |   |                    |
|-----|---|--------------------|
| A02 | New 2 Stage Low Noise 28db gain RF Amplifier. Specially designed for kit builders | <b>Kit \$18.00</b> |
| A03 | New 1 Stage Low Noise 14db gain Amplifier   | <b>Kit \$10.50</b> |
| A04 | 75-300 OHM matching Transformer.  | <b>\$1.00</b>      |
| F59 | Coaxial Connectors. . . . .   | <b>.30</b>         |

Mail order only. Send check or money order to:

**GILCO INTERNATIONAL, INC.**

P. O. Box 8817, Coral Gables, FL 33124


Tel. (305) 823-5891 For CDD orders add 10% shipping and handling or for orders over \$50, add 5%.

FL residents add 5% sales tax. Please write for more information

# Make Radio Shack Your Parts Place™

• No Minimum Order! • No Waiting! • Great Low Prices!


## Full-Spec Microwave Devices

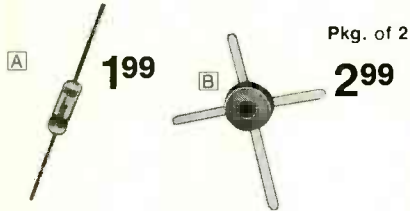

**A** 5082-2835. Low-noise Schottky barrier diodes. Ideal for UHF and microwave stripline mixers. Maximum capacitance: 1 pF. 276-1124 ..... Pkg. of 2/1.99

**B** MRF-901. Low-noise NPN transistor for use to beyond 2000 MHz. Beamlead-style macro-X case. 300 mW. 276-2044 ..... 2.99

## Computer Connectors

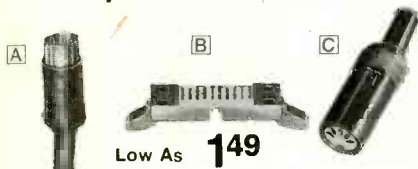

**A** 4-Pin DIN-Type Plug. For audio and micro-computer use. 274-007 ..... 1.49

**B** 40-Position Card Edge Connector. Highest quality, reusable. For ribbon cable. 276-1558 ..... 4.95

**C** 5-Pin Inline Jack. Accepts 3 or 5-pin plugs. Solder terminals. Strain relief. Shielded. 274-006 ..... 1.49

## PC Board Kit and Supplies




**895**

Two 4 1/2 x 3" boards, resist-ink pen, solvent, etchant, layout strips and circles, tank, 1/16" drill bit, instructions. 276-1576 ..... 8.95

Extra Resist-Ink Pen. 276-1530 ..... 1.39

Extra Etchant. 16 oz. 276-1535 ..... 2.49

## Direct-Etch Dry Transfers

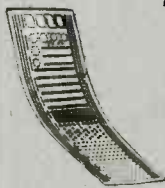

**Easy to Use!**

**259**

Set of 4

Transparent sheets with rub-on circles, strips, component pads and more. Press on to a copper clad PC board and you're ready to etch—with "pro-quality" results. 276-1577 ..... Set/2.59


## Adjustable PC Board Holder



**695**

Frees hands for easier soldering and repair. Mounts on bench or in a vice. Holds board securely, yet is fully adjustable. 276-1568 ..... 6.95

## V to F, F to V IC

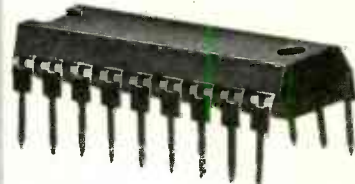

14-Pin With Data

**High Accuracy**  
**Great for FSK, Modems**

**349**

9400. This bipolar/CMOS device accepts an analog voltage and generates a proportional frequency, or provides an output voltage in proportion to input frequency. Operates up to 100 kHz. See our *Engineer's Notebook II* for circuit ideas. Single/split supply. 276-1790 ..... 3.49

## Miniature DPDT Relay With 12VDC Coil



Socket included

**469**

Top quality! Long-life contacts rated 3 amps at 125VAC. Coil: 75 milliamps, 160 ohms. Relay, 1 1/4 x 1 x 3/4". Includes chassis or PC-mount socket with clip for relay. 275-206 ..... 4.69


## Panel Lettering

**NEW FOR '83** **259**

4 sheets with rub-on letters, symbols, numbers and more. 270-201 ..... 2.59




## Mike Element

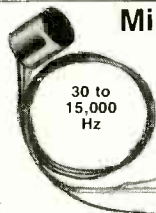

**299**

Omnidirectional Electret. 3/8" dia. 4-10VDC. 270-092 ..... 2.99

## DC Buzzer

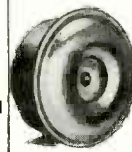

**Cut 42%**  
Reg. 1.19 **69¢**

Super loud! 1.5-3VDC with low current. 273-004 ..... Sale 69¢

## Versatile Solenoid



**NEW FOR '83** **399**

Ideal for robots, model railroads, opening valves, door latches and more. Spring return plunger. 31 ohms, 430 milliamps at 12VDC. 273-251 ..... 3.99

1 1/8 x 1 1/16 x 1 1/16"

## SPDT Lever Switch



**149**

Submini, 3/4" roller lever. 5 amps at 250VAC. 275-017 ..... 1.49

## Motorola-Type Jack



**NEW FOR '83** **99¢**

With 4 1/2-inch shielded cable. For scanners, car radio hookups. 274-713 ..... 99¢

## "Battery" Clips




**119** Set. of 2

One Red One Black

Fit car battery posts. Crimp or solder. 270-344 ..... Set 1.19

## Dress Up and Protect Your Project!

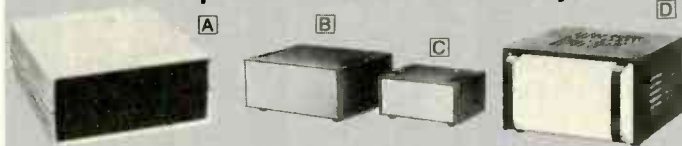

**795** **995** **695** **1095**

**A** Deluxe Two-Tone Enclosure. ABS plastic end panels for easy drilling, internal slots and standoffs for PC boards, self-stick feet. 2 1/4 x 5 x 5 1/4". 270-218 ..... 7.95

"Silver-Look." Both feature vented steel tops, easy-to-work aluminum chassis, rubber feet and very classy "silver" finish.

**B** 3 1/4 x 7 1/2 x 5 7/8". 270-229 ..... 9.95

**C** 2 1/2 x 5 1/16 x 4 7/16". 270-228 ..... 6.95

**D** "Handle" Box. Easy to carry. Vented steel top with black finish, aluminum front and bottom, rubber feet. 5 1/4 x 9 1/2 x 6 1/4". 270-270 ..... 10.95

## Panel Meter Sale!

**Save \$207**



Reg. 8.95 **688** Each

Micronta® precision at 23% off! Jeweled movements. Large, easy-to-read faces.

0 to 50 Microamps DC. 270-1751 ..... Sale 6.88

0 to 1 Milliamps DC. 270-1752 ..... Sale 6.88

0 to 15 Volts DC. 270-1754 ..... Sale 6.88

## Low-Cost Light Ups!



**NEW FOR '83**

**A** Micro 12V Lamps. One red, one green, 60 mA. Metal panel recommended. 272-334 ..... Pkg. of 2/1.69

**B** Push-In Neon Panel Lamps. One red, one green. Built-in dropping resistors for 120V use. 272-709 ..... Pkg. of 2/1.99

**C** Yellow LEDs in Chromed Holders. 276-073 ..... Pkg. of 2/1.69

**D** Orange Rectangular LEDs. Hi brightness. 276-074 ..... Pkg. of 2/99¢

# Radio Shack®

A DIVISION OF TANDY CORPORATION • OVER 8400 LOCATIONS IN 80 COUNTRIES

Retail prices may vary at individual stores and dealers  
CIRCLE 75 ON FREE INFORMATION CARD

**4116** 16K DYNAMIC 250NS **8/\$11<sup>95</sup>** SET

**2114** 1KX4 STATIC **8/\$15<sup>95</sup>** SET

**ALL MERCHANDISE 100% GUARANTEED!**

**CALL US FOR VOLUME QUOTES**

**STATIC RAMS**

|            |          |                     | Each    | 100 pcs |
|------------|----------|---------------------|---------|---------|
| 2101       | 256 x 4  | (450ns)             | 1.95    | 1.85    |
| 5101       | 256 x 4  | (cmos) (450ns)      | 4.95    | 3.95    |
| 2102-1     | 1024 x 1 | (450ns)             | .89     | .85     |
| 2102L-2    | 1024 x 1 | (LP) (250ns)        | 1.69    | 1.55    |
| 2102L-4    | 1024 x 1 | (LP) (450ns)        | 1.29    | 1.15    |
| 2111       | 256 x 4  | (450ns)             | 2.99    | 2.49    |
| 2112       | 256 x 4  | (450ns)             | 2.99    | 2.79    |
| 2114       | 1024 x 4 | (450ns)             | 8/16.95 | 1.95    |
| 2114L-2    | 1024 x 4 | (LP) (200ns)        | 8/15.95 | 1.90    |
| 2114L-3    | 1024 x 4 | (LP) (300ns)        | 8/18.95 | 2.25    |
| 2114L-4    | 1024 x 4 | (LP) (450ns)        | 8/17.95 | 2.10    |
| 2147       | 4096 x 1 | (55ns)              | 9.95    | call    |
| TMS4044-4  | 4096 x 1 | (450ns)             | 3.49    | 3.25    |
| TMS4044-3  | 4096 x 1 | (300ns)             | 3.99    | 3.75    |
| TMS4044-2  | 4096 x 1 | (200ns)             | 4.49    | 4.25    |
| MK4118     | 1024 x 8 | (250ns)             | 9.95    | call    |
| TMM2016    | 2048 x 8 | (150ns)             | call    | call    |
| HM6116-4   | 2048 x 8 | (cmos) (200ns)      | call    | call    |
| HM6116-3   | 2048 x 8 | (cmos) (150ns)      | call    | call    |
| HM6116-2   | 2048 x 8 | (cmos) (120ns)      | call    | call    |
| HM6116LP-4 | 2048 x 8 | (LP) (cmos) (200ns) | call    | call    |
| HM6116LP-3 | 2048 x 8 | (LP) (cmos) (150ns) | call    | call    |
| HM6116LP-2 | 2048 x 8 | (LP) (cmos) (120ns) | call    | call    |
| Z-6132     | 4096 x 8 | (Qstat) (300ns)     | 34.95   | call    |

LP = Low Power Qstat = Quasi-Static

**Z-80**  
2.5 Mhz

|           |       |
|-----------|-------|
| Z80-CPU   | 6.00  |
| Z80-CTC   | 5.95  |
| Z80-DART  | 15.25 |
| Z80-DMA   | 17.50 |
| Z80-PIO   | 6.00  |
| Z80-SIO/0 | 18.50 |
| Z80-SIO/1 | 18.50 |
| Z80-SIO/2 | 18.50 |
| Z80-SIO/9 | 16.95 |

**4.0 Mhz**

|            |       |
|------------|-------|
| Z80A-CPU   | 6.00  |
| Z80A-CTC   | 8.65  |
| Z80A-DART  | 18.75 |
| Z80A-DMA   | 27.50 |
| Z80A-PIO   | 6.00  |
| Z80A-SIO/0 | 22.50 |
| Z80A-SIO/1 | 22.50 |
| Z80A-SIO/2 | 22.50 |
| Z80A-SIO/9 | 19.95 |

**6.0 Mhz**

|          |       |
|----------|-------|
| Z80B-CPU | 17.95 |
| Z80B-CTC | 15.50 |
| Z80B-PIO | 15.50 |

**ZILOG**

|       |       |
|-------|-------|
| Z6132 | 34.95 |
| Z8671 | 39.95 |

**8200**

|        |       |
|--------|-------|
| 8202   | 34.95 |
| 8205   | 3.50  |
| 8212   | 1.85  |
| 8214   | 3.85  |
| 8216   | 1.80  |
| 8224   | 2.50  |
| 8226   | 1.80  |
| 8228   | 4.90  |
| 8237   | 19.95 |
| 8238   | 4.95  |
| 8243   | 4.45  |
| 8250   | 14.95 |
| 8251   | 4.75  |
| 8253   | 9.25  |
| 8253-5 | 9.85  |
| 8255   | 4.75  |
| 8255-5 | 5.25  |
| 8257   | 8.50  |
| 8257-5 | 8.95  |
| 8259   | 6.90  |
| 8259-5 | 7.50  |
| 8272   | 39.95 |
| 8275   | 29.95 |
| 8279   | 9.50  |
| 8279-5 | 10.00 |
| 8282   | 6.65  |
| 8283   | 6.65  |
| 8284   | 5.70  |
| 8286   | 6.65  |
| 8287   | 6.50  |
| 8288   | 25.00 |
| 8289   | 49.95 |

**8000**

|          |       |
|----------|-------|
| 8035     | 7.25  |
| 8039     | 7.95  |
| INS-8060 | 17.95 |
| INS-8073 | 29.95 |
| 8080     | 3.95  |
| 8085     | 7.95  |
| 8085A-2  | 11.95 |
| 8086     | 59.95 |
| 8088     | 39.95 |
| 8089     | 89.95 |
| 8155     | 7.95  |
| 8156     | 8.95  |
| 8185     | 29.95 |
| 8185-2   | 39.95 |
| 8741     | 39.95 |
| 8748     | 29.95 |
| 8755     | 32.00 |

**6800**

|               |       |
|---------------|-------|
| 68000         | call  |
| 6800          | 4.95  |
| 6802          | 10.95 |
| 6808          | 13.90 |
| 6809E         | 19.95 |
| 6809          | 19.95 |
| 6810          | 2.95  |
| 6820          | 4.95  |
| 6821          | 4.95  |
| 6828          | 14.95 |
| 6840          | 12.95 |
| 6843          | 34.95 |
| 6844          | 25.95 |
| 6845          | 16.95 |
| 6847          | 12.25 |
| 6850          | 3.45  |
| 6852          | 5.75  |
| 6860          | 10.95 |
| 6862          | 11.95 |
| 6875          | 6.95  |
| 6880          | 2.95  |
| 6883          | 24.95 |
| 68047         | 24.95 |
| 68488         | 19.95 |
| 6800 = 1MHZ   |       |
| 68B00         | 10.95 |
| 68B02         | 22.25 |
| 68B09E        | 29.95 |
| 68B09         | 29.95 |
| 68B10         | 7.95  |
| 68B21         | 12.95 |
| 68B45         | 35.95 |
| 68B50         | 12.95 |
| 68B00 = 2 MHZ |       |

**DISC CONTROLLERS**

|        |       |
|--------|-------|
| 1771   | 21.95 |
| 1791   | 29.95 |
| 1793   | 38.95 |
| 1795   | 54.95 |
| 1797   | 54.95 |
| 6843   | 34.95 |
| 8272   | 39.95 |
| UPD765 | 39.95 |
| 1691   | 18.95 |
| 2143   | 18.95 |

**INTERFACE**

|        |      |
|--------|------|
| 8T26   | 1.69 |
| 8T28   | 2.49 |
| 8T95   | .99  |
| 8T96   | .99  |
| 8T97   | .99  |
| 8T98   | .99  |
| DM8131 | 2.95 |
| DP8304 | 2.29 |

**MISC**

|          |       |
|----------|-------|
| 3341     | 4.95  |
| 76477    | 3.95  |
| AY3-8910 | 12.95 |
| MC3340   | 1.49  |
| 95H90    | 7.99  |
| 11C90    | 13.95 |
| 8202A    | 34.95 |
| 3242     | 7.95  |
| MC3480   | 9.00  |
| MC4024   | 3.95  |
| MC4044   | 4.50  |
| 3205     | 3.50  |

**BIT-RATE GENERATORS**

|         |       |
|---------|-------|
| 14411   | 11.95 |
| BR1941  | 11.95 |
| 4702    | 12.95 |
| COM5016 | 16.95 |
| MM5307  | 10.95 |

**UARTS**

|          |       |
|----------|-------|
| AY3-1014 | 6.95  |
| AY5-1013 | 3.95  |
| PT1472   | 9.95  |
| TR1602   | 3.95  |
| 2350     | 9.95  |
| TMS6011  | 5.95  |
| IM6402   | 7.95  |
| IM6403   | 8.95  |
| INS8250  | 14.95 |

**KEYBOARD CHIPS**

|          |       |
|----------|-------|
| AY5-2376 | 11.95 |
| AY5-3600 | 11.95 |
| 74C922   | 5.25  |
| 74C923   | 5.50  |

**CLOCK CIRCUITS**

|         |       |
|---------|-------|
| MM5314  | 4.95  |
| MM5369  | 3.95  |
| MM5375  | 4.95  |
| MM58167 | 8.95  |
| MM58174 | 11.95 |
| MSM5832 | 6.95  |

**CRYSTALS**

|            |      |
|------------|------|
| 32.768 khz | 1.95 |
| 1.0 mhz    | 4.95 |
| 1.8432     | 4.95 |
| 2.0        | 3.95 |
| 2.097152   | 3.95 |
| 2.4576     | 3.95 |
| 3.2768     | 3.95 |
| 3.579535   | 3.95 |
| 4.0        | 3.95 |
| 5.0        | 3.95 |
| 5.0688     | 3.95 |
| 5.185      | 3.95 |
| 5.7143     | 3.95 |
| 6.0        | 3.95 |
| 6.144      | 3.95 |
| 6.5536     | 3.95 |
| 8.0        | 3.95 |
| 10.0       | 3.95 |
| 14.31818   | 3.95 |
| 15.0       | 3.95 |
| 16.0       | 3.95 |
| 18.0       | 3.95 |
| 18.432     | 3.95 |
| 20.0       | 3.95 |
| 22.1184    | 3.95 |
| 32.0       | 3.95 |

**DYNAMIC RAMS**

|          |           |              | Each    | 100 pcs |
|----------|-----------|--------------|---------|---------|
| TMS4027  | 4096 x 1  | (250ns)      | 2.50    | 2.00    |
| MK4108   | 8192 x 1  | (200ns)      | 1.95    | call    |
| MM5298   | 8192 x 1  | (250ns)      | 1.85    | call    |
| 4116-120 | 16384 x 1 | (120ns)      | 8/29.95 | call    |
| 4116-150 | 16384 x 1 | (150ns)      | 8/18.95 | 1.95    |
| 4116-200 | 16384 x 1 | (200ns)      | 8/13.95 | call    |
| 4116-250 | 16384 x 1 | (250ns)      | 8/11.95 | call    |
| 4116-300 | 16384 x 1 | (300ns)      | 8/13.80 | call    |
| 2118     | 16384 x 1 | (5v) (150ns) | 4.95    | call    |
| MK4816   | 2048 x 8  | (5v) (300ns) | 24.95   | call    |
| 4164-200 | 65536 x 1 | (5v) (200ns) | call    | call    |
| 4164-150 | 65536 x 1 | (5v) (150ns) | call    | call    |

**EPROMS**

|         |          |              | Each | 8 pcs |
|---------|----------|--------------|------|-------|
| 1702    | 256 x 8  | (1us)        | 4.95 | 4.50  |
| 2708    | 1024 x 8 | (450ns)      | 3.75 | 3.50  |
| 2758    | 1024 x 8 | (5v) (450ns) | 9.95 | 8.95  |
| TMS2516 | 2048 x 8 | (5v) (450ns) | 6.95 | 5.95  |
| 2716    | 2048 x 8 | (5v) (450ns) | 4.95 | 3.95  |
| 2716-1  | 2048 x 8 | (5v) (350ns) | 9.00 | 8.50  |
| TMS2716 | 2048 x 8 | (450ns)      | 9.95 | 8.95  |
| TMS2532 | 4096 x 8 | (5v) (450ns) | 9.95 | 7.95  |
| 2732    | 4096 x 8 | (5v) (450ns) | 9.95 | 7.95  |
| 2732A-2 | 4096 x 8 | (5v) (200ns) | call | call  |
| 2764    | 8192 x 8 | (5v) (450ns) | call | call  |
| TMS2564 | 8192 x 8 | (5v) (450ns) | call | call  |

5v = Single 5 Volt Supply

**EPROM ERASERS**

| Timer   | Capacity Chip | Intensity (uW/V <sup>2</sup> ) |        |
|---------|---------------|--------------------------------|--------|
| PE-14   | 6             | 5,200                          | 83.00  |
| PE-14T  | X 6           | 5,200                          | 119.00 |
| PE-24T  | X 9           | 6,700                          | 175.00 |
| PL-265T | X 20          | 6,700                          | 255.00 |
| PR-125T | X 16          | 15,000                         | 349.00 |
| PR-320T | X 32          | 15,000                         | 595.00 |

**ORDER TOLL FREE**  
**800-538-5000**  
**800-662-6279**  
(CALIFORNIA RESIDENTS)

*IF YOU CAN FIND A PRICE LOWER ELSEWHERE, LET US KNOW AND WE WILL BEAT THEIR PRICE.*

- ★ Computer managed inventory—virtually no back orders.
- ★ Guaranteed lowest prices!
- ★ Fast service — most orders shipped within 24 hours!

**MONTHLY SPECIALS**  
**CPU SALE**

|                 |                       |
|-----------------|-----------------------|
| Z-80 CPU 2MHZ   | \$3.95 (10/ 3.75 EA)  |
| 6502 1 MHZ      | \$5.95 (10/ 5.75 EA)  |
| 6809 INT. CLOCK | \$12.95 (10/11.25 EA) |

**16 BIT**

|                   |                |
|-------------------|----------------|
| <b>8086</b>       | <b>\$29.95</b> |
| <b>68000 8MHZ</b> | <b>\$99.95</b> |

SALE ENDS SEPT. 30, 1982. PLEASE STATE "SEPTEMBER SPECIALS" WHEN ORDERING

HOURS:  
M-F, 9-5; Sat. 11-3

**VISIT OUR**  
**RETAIL STORE**



**JDR MICRODEVICES, INC.**

1224 S. Bascom Avenue  
San Jose, CA 95128

800-538-5000 • 800-662-6279 (CA)  
(408) 995-5430 • Telex 171-110

PLEASE USE YOUR CUSTOMER NUMBER WHEN ORDERING

TERMS: For shipping include \$2 for UPS Ground or \$3 for UPS Blue Label Air. Items over 5 pounds require additional shipping charges. Foreign orders, include sufficient amount for shipping. There is a \$10 minimum order. Bay Area and Los Angeles Counties add 6½% Sales Tax. Other California residents add 6% Sales Tax. We reserve the right to substitute manufacturer. Not responsible for typographical errors. Prices are subject to change without notice. We will match or beat any competitor's price provided it is not below our cost.



2716 16K EPROMS 8/\$3<sup>95</sup> EACH

2732 32K EPROMS 8/\$7<sup>95</sup> EACH

ALL MERCHANDISE 100% GUARANTEED!

CALL US FOR VOLUME QUOTES

74LS00

Table listing various 74LS00 logic chips with prices. Includes items like 74LS00, 74LS01, 74LS02, etc.

LINEAR

Table listing various linear ICs with prices. Includes items like LM301V, LM308V, LM309K, etc.

IC SOCKETS

Table listing various IC socket types and prices. Includes items like 8 pin ST, 14 pin ST, etc.

CMOS

Table listing various CMOS ICs with prices. Includes items like 4000, 4001, 4002, etc.

BI FET

Table listing various Bi FET transistors with prices. Includes items like TL071, TL072, etc.

EXAR

Table listing various EXAR ICs with prices. Includes items like XR 2206, XR 2207, etc.

VOLTAGE REGULATORS

Table listing various voltage regulators with prices. Includes items like 7805T, 7808T, 7812T, etc.

CONNECTORS

Table listing various connector types and prices. Includes items like RS232 MALE, RS232 FEMALE, etc.

DIP SWITCHES

Table listing various DIP switch configurations and prices. Includes items like 4 POSITION, 5 POSITION, etc.

LED LAMPS

Table listing various LED lamp types and prices. Includes items like Jumbo Red, Jumbo Green, etc.

CALL US FOR YOUR 74C00 REQUIREMENTS

WE HAVE

- ★ 74C00 ★ 74S00 ★ TRANSISTORS
★ 7400 ★ LINEAR ★ ... and much more!

DISKETTES

5 1/4"

Table listing 5 1/4" floppy diskette types and prices.

8"

Table listing 8" floppy diskette types and prices.

APPLE FAN \$69.00

- ★ Outlet on rear.
★ Simply snap over air vents.
★ Quiet motor.

MONITORS ZENITH ZVM-121

\$119.95

NEC JB-1201M

\$169.00

EPSON PRINTERS

- MX-80
MX-80FT
MX-100

CALL FOR PRICE

ADD ON DISK DRIVE FOR Apple\* II

- ★ Includes metal cabinet
★ Color matches Apple\*
★ 35 Tracks/single side
★ Includes cable
★ Use with Apple\* II Controller

\$375.00

\*Apple is a trademark of APPLE COMPUTER INC.

16K APPLE\* RAM CARD

- ★ Upgrade your 48K Apple\* II to full 64K of RAM.
★ Fully software and hardware compatible with the Apple language card and microsoft Z80 card.
★ Eliminates the need for the Apple-soft or Integer Basic ROM card when used in conjunction with DOS 3.3.
★ Allows you to run Apple Fortran or Pascal with no difficulty.
★ Available as bare board, kit, or assembled and tested board.

BARE BOARD ..... \$40.00

KIT ..... 69.96

ASSEMBLED & TESTED ... 74.95

\*Apple is a trademark of APPLE COMPUTER INC.


JDR MICRODEVICES, INC.

1224 S. Bascom Avenue San Jose, CA 95128

800-538-500J • 800-662-6279 (CA) (408) 995-5430 • Telex 171-110

PLEASE USE YOUR CUSTOMER NUMBER WHEN ORDERING
TERMS: For shipping include \$2 for UPS Ground or \$3 for UPS Blue Label Air. Items over 5 pounds require additional shipping charges.

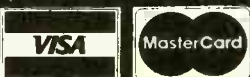HOURS: M-F, 9-5; Sat. 11-3
VISIT OUR RETAIL STORE



# ETCO

## CABLE TV CONVERTERS AND OTHER GOOD STUFF!

**SMASHING ALL SALES RECORDS — OUR NEW 30 CHANNEL CABLE TV CONVERTER!**



Converts mid & super band cable channels for viewing on your TV set!  
No. 349AE047

**39<sup>95</sup>** \$34.95 ea. / 5

**HOT NEW IMPORT! REMOTE CONTROL 30 CHANNEL CABLE TV CONVERTER!**



Includes remote TV on/off switch and fine tuning control!  
No. 349VA275

**89<sup>95</sup>** \$79.95 ea. / 5  
**574.95** ea. / 10

**ETCO MKII WIRELESS — THE ULTIMATE CABLE TV CONVERTER!**



Set TV to channel 3, and the hand held remote control does it all!  
No. 349ZA008

**189<sup>00</sup>**

**VIDCOR 2000 CONVERTER ELIMINATES PROBLEMS WHEN VIDEOTAPEING FROM CABLE TV**



Restores your VCR's capability for programming. Restores remote channel control. Enables videotaping of one cable program while watching another.  
No. 349VA950

**89<sup>95</sup>** \$89.95 ea. / 5


**UNUSUAL FACTORY SURPLUS MID-BAND — SUPER-BAND CABLE TV TUNER**



Converts cable channels to a common IF frequency. Experimenters — build cable converters, decoders, etc. With schematic. No. 349VA342

**19<sup>95</sup>** \$17.50 ea. / 10

**FACTORY SURPLUS UHF TUNERS**



Brand new production surplus. All solid state. Ideal for experimental work building cable TV converters, etc. No. 349SU099

**4<sup>95</sup>** \$3.95 ea. / 10

**MINIATURE FM WIRELESS MICROPHONE**



Hides in the palm of your hand. Reception on any standard FM radio or receiver.  
No. 349VA482

**29<sup>95</sup>** \$27.50 ea. / 5  
\$24.95 ea. / 10

**QUARTER-MILE WIRELESS MICROPHONE & RECEIVER SYSTEM**



FCC approved crystal controlled wireless mike & receiver. All battery operated. Electret wide-range response. VU meter.  
No. 349VA093

**69<sup>95</sup>** \$49.95 ea. / 5

**FACTORY SURPLUS VHF / UHF "TWIN" VARACTOR TUNERS!**



Admiral No. NC 3143-1. BRAND NEW! Ideal for building or repairing electronically tuned TV "FRONT ENDS". A hard to find item at a sensational price!  
No. 349VC308

**39<sup>95</sup>** \$34.95 ea. / 5

**DUMPING! NORELCO ENDLESS LOOP CASSETTES!**



Impossible to find at any price!  
3 minutes — No. 349VA605  
6 minutes — No. 349VA606

**4<sup>95</sup>** \$4.49 ea. / 10


**IN STOCK — THE MURA CORDLESS TELEPHONE SYSTEM!**



Answer & originate calls with this wireless push-button 400 ft. range re-chargeable! Last number recall! Paging feature! Use with rotary, touch systems!  
No. 349VA274

**144<sup>88</sup>** \$129.95 ea. / 5


**SALE OF QUARTZ BATTERY OPERATED CLOCK MOVEMENTS!**



Accuracy of 1/1000 year up to 4 years operation on 1.5kV line "C" cell. Imported from West Germany. No. 349VA561

**9<sup>95</sup>** \$8.95 ea. / 5

**20 AMP REGULATED 12VDC POWER SUPPLY!**



13.8 vdc no load, 12.5 vdc full load! Easily handles ham station, marine radio, SSB lineups up to 400w P.E.P. Brand new, factory sealed! 110 VAC. No. 349VA394

**69<sup>88</sup>** \$59.88 ea. / 5

**FREE FASCINATING CATALOG**

— rich packed with unique items, electronic bargains and unusual offers. Write or circle the information card number below.

**ETCO ELECTRONICS NORTH COUNTRY SHOPPING CENTER PLATTSBURGH, N.Y. 12901**

Check with order, please. Visa & Mastercard OK. (Sorry, no C.O.D.'s. Add 15% for UPS & Handling (Excess refunded). N.Y. State residents add 7% sales tax. Dealer & Export inquiries invited. Our telephone order desk never closes.

Call 1-518-561-8700.

# ADVERTISING INDEX


RADIO-ELECTRONICS does not assume any responsibility for errors that may appear in the index below.

## Free Information Number Page

|            |   |                      |
|------------|---|----------------------|
| 50         | AMC Sales                                 | 91                   |
| 26         | AP Products, Inc.                         | 30                   |
| —          | Aaron Gavin                               | 76                   |
| 65         | Abex                                      | 104                  |
| 74         | Active Electronics                        | 119                  |
| 77         | Advance Computer Products                 | 117                  |
| —          | Advance Electronics                       | 28-29, 32, 77        |
| 79         | All Electronics                           | 127                  |
| 22         | William B. Allen Supply                   | 111                  |
| 52         | Anders Precision Instruments Co., Inc.    | 110                  |
| 20         | Antenna Specialists                       | 79                   |
| 92         | Arizona Electronics                       | 131                  |
| 89         | B.G. Micro                                | 130                  |
| 40         | B&K Precision Dynascan Corp.              | 94                   |
| 102        | Babylon Electronics                       | 130                  |
| 34         | Barker & Williamson                       | 90                   |
| —          | Karel Barta                               | 114                  |
| 10         | Bishop Graphics, Inc.                     | 31                   |
| —          | Bullet Electronics                        | 132                  |
| —          | C & D Electronics, Inc.                   | 130                  |
| —          | CIE, Cleveland Institute of Electronics   | 18-21                |
| 67         | CRT                                       | 105                  |
| 24         | Cambridge Learning                        | 103                  |
| 101        | Chaney Electronics                        | 120                  |
| —          | Command Productions                       | 118, 138             |
| 16         | Communications Electronics                | 2                    |
| —          | Components Express                        | 106                  |
| 103        | Computer Products & Peripherals Unlimited | 131                  |
| 81         | Concord Electronics                       | 120                  |
| —          | Contact East                              | 134                  |
| —          | Cook's Institute                          | 118                  |
| —          | Dage Scientific                           | 118                  |
| —          | Data Services Co.                         | 118                  |
| —          | Devtronix/Organ Products                  | 114                  |
| 91         | Diamondback                               | 133                  |
| —          | Digatek Corp.                             | 114                  |
| 100        | DigiCom Engineering, Inc.                 | 114                  |
| 73         | Digi-Key Corp.                            | 123                  |
| 80         | Dokay                                     | 116                  |
| 31         | Edsyn                                     | 112                  |
| 19         | Electra Company                           | 25, 114              |
| 25         | Electronic Rainbow, Inc.                  | 95                   |
| —          | Electronic Specialists, Inc.              | 108                  |
| —          | Eto Electronics                           | 118, 138             |
| 57         | Etronix                                   | 110                  |
| 58         | Firestone Tarp. Mfg.                      | 110                  |
| 15         | Fluke Mfg. Co., Inc.                      | 5                    |
| —          | Fordham Radio                             | 118                  |
| 70         | Formula International                     | 128-129              |
| —          | Gilco International, Inc.                 | 134                  |
| 53, 54     | Gladstone Electronics                     | 94                   |
| 11         | Global Specialties Corp.                  | 81                   |
| —          | Global TV Electronics                     | 114                  |
| 82         | Godbout Electronics                       | 122                  |
| —          | Grantham College of Engineering           | 109                  |
| —          | Grove Enterprises, Inc.                   | 116                  |
| 23         | Hal Communications Corp.                  | 34                   |
| 99         | Hal-Tronix                                | 127                  |
| —          | Heath                                     | Cover III, 15, 87-89 |
| 35, 36, 37 | Hickok Electrical Instruments             | 86, 90, 108          |
| 14         | Hitachi Denshi America, Ltd.              | 44                   |
| 95         | Hitek Electronics                         | 126                  |
| 98         | Information Unlimited                     | 127                  |
| 49         | International Crystal                     | 107                  |
| 71         | JDR, Microdevices                         | 136-137              |
| —          | J&W Electronics                           | 116                  |
| 69         | Jameco Electronics                        | 124-125              |
| 56         | Jan Crystal                               | 109                  |
| 90         | H.J. Knapp                                | 133                  |
| 4, 5       | Leader Instruments Corp.                  | Cover II             |
| —          | McGee's Radio                             | 118                  |
| —          | McGraw-Hill Book Co.                      | 36-39                |
| —          | McKay Co.                                 | 114                  |
| 76         | MCM Audio                                 | 115                  |
| 63         | Masco Electronics                         | 104                  |
| 42         | Micro Management Systems, Inc.            | 113                  |
| —          | Microtenna Associates                     | 116                  |
| —          | Monarchy Engineering, Inc.                | 130                  |
| 97         | Mountain West/Alarm                       | 131                  |
| 9          | Multitech Electronics, Inc.               | 27                   |
| —          | NRI Schools                               | 8-11                 |
| —          | NTS Schools                               | 96-99                |
| —          | Nabih's, Inc.                             | 110                  |

|        |                                      |          |
|--------|--------------------------------------|----------|
| 94     | Neptune Communications, Inc.         | 132      |
| —      | Netronics                            | 75, 82   |
| 32     | North American Soar                  | 82       |
| 17     | O.K. Machine & Tool                  | 13       |
| 28     | Omnitron Electronics                 | 102      |
| 84     | P.P.G. Electronics Co., Inc.         | 134      |
| 43     | Pac-Tec Corp.                        | 107      |
| 55     | Paia Electronics                     | 107      |
| 7      | Panasonic                            | 1        |
| 39     | Panavise                             | 76       |
| —      | Philips ECG                          | 33       |
| 13     | Philips Test & Measuring Instruments | 41       |
| 41     | Platt Luggage                        | 112      |
| 87     | Poly Paks                            | 131      |
| 38     | Protecto Enterprises                 | 76       |
| —      | RCA                                  | 26       |
| 75     | Radio Shack                          | 135      |
| 72     | Ramsey Electronics                   | 121      |
| 96     | SCR Electronics, Inc.                | 126      |
| 62     | SMP, Inc.                            | 104      |
| 66     | SRS                                  | 105      |
| —      | Sabadia Exports Corp.                | 120      |
| 33     | H.W. Sams                            | 93       |
| 104    | Satellite TV                         | 114      |
| —      | Shure Brothers                       | 109      |
| —      | Simple Simon Electronics             | 85       |
| 21     | Simpson Electronics Co.              | 24       |
| —      | Sinclair Research, Ltd.              | 16-17    |
| —      | Sintec Co.                           | 91       |
| 78     | Solid State Sales                    | 126      |
| —      | Spartan Electronics                  | 132      |
| 59     | Spectrum Electronics                 | 104, 116 |
| 93     | Stavis Electronics, Inc.             | 133      |
| —      | Suntronics Co., Inc.                 | 120      |
| 61     | Symmetric Sound Systems              | 105      |
| 18     | TAB Books                            | 83       |
| —      | Tektronix                            | 7, 22-23 |
| 46, 47 | Triplett Corp.                       | 100      |
| 44, 45 | Triton Marketing Corp.               | 113      |
| 6, 68  | Ungar-Division of Eldon Industries   | 35, 105  |
| 64     | Universal Enterprises                | 105      |
| 29     | Vaco                                 | 101      |
| 48     | Vector Electronics Co.               | 107      |
| 60     | Video Control                        | 105      |
| 8      | VIZ Mfg. Co.                         | 43       |
| 51     | Wersi Electronics                    | 91       |
| —      | Zenith Radio Co.                     | Cover IV |
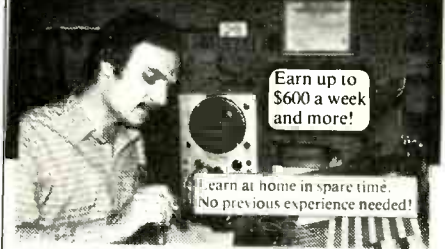
# Be an FCC LICENSED ELECTRONIC TECHNICIAN!



No costly School. No commuting to class. The Original Home-Study course that prepares you for the FCC Radio-telephone license exam in your spare time! Passing the exam is your "ticket" to thousands of exciting opportunities in Communications, Broadcasting, Mobile two-way systems, Microwave stations, Radar installations, Aerospace and more.

**NO NEED TO QUIT YOUR JOB OR GO TO SCHOOL**

You learn how to pass the FCC License exam at home at your own pace with this easy-to-understand, proven course. Within a few short weeks you could be on your way to being one of the highest paid workers in the electronics field. It's that easy! U.S. Federal law requires you to have an FCC License if you want to operate and maintain virtually any communications system — you don't need a College degree to qualify, but you DO need an FCC License. With this Home-Study course, you'll be ready to pass the FCC Government licensing exam in a remarkably short time. Send for FREE facts now. No obligation. No salesman will call. MAIL COUPON TODAY!

## COMMAND PRODUCTIONS

FCC LICENSE TRAINING, Dept. E  
P.O. Box 2223, San Francisco, CA 94126

Rush FREE facts on how I can prepare for my FCC License at home in my spare time.

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

# Let's get personal...

try out the in-stock selection of Heath/Zenith microcomputers, peripherals, accessories and software.

Now available at your nearby Heathkit Electronic Center, or through the Heathkit mail order catalog.

You get more with a Heath/Zenith personal microcomputer system! We offer:

**1. Proven high-performance hardware:** Thousands of our microcomputers prove themselves daily, in the field.

**2. Vast software library:** Three operating systems (including CP/M), languages, word processors, an electronic spreadsheet, versatile utilities and the 500-program Heath Users' Group software library.

**3. Self-instruction courses:** Evaluation and programming courses from Heathkit/Zenith Educational Systems.


**4. Service support:** Before and after the sale - consultation by phone, carry-in service by trained technicians.

**Test run one of our microcomputers at any of the more than 60 convenient Heathkit Electronic Centers in the U.S.**
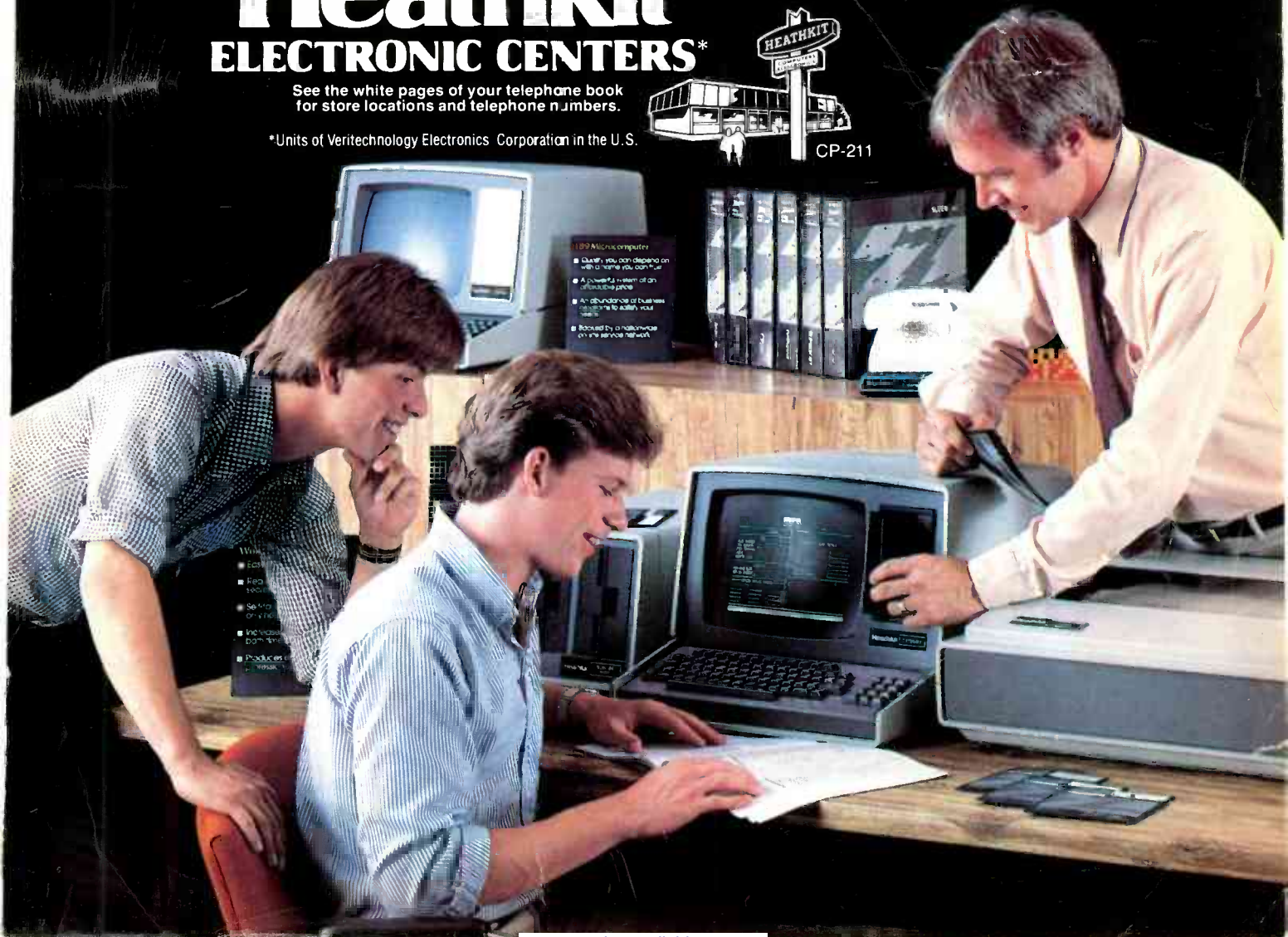
## Heathkit<sup>®</sup> ELECTRONIC CENTERS\*

See the white pages of your telephone book for store locations and telephone numbers.

\*Units of Veritechnology Electronics Corporation in the U.S.



1987 Microcomputer  
■ Great! You can depend on  
with a "name you don't"  
■ A powerful system at an  
affordable price.  
■ An abundance of business  
software to help you  
succeed.  
■ Backed by a nationwide  
service network.

What's  
■ Easy  
■ High  
■ Speed  
■ Dependable  
■ Backed  
■ Product



New from Zenith!

# Two-way protection from high voltage surges for the appliances and electronics you sell or service!

A brief, high voltage surge – or spike – can occur in any electrical system and, at amplitudes lower than 600V, cause little or no damage.

But at greater amplitudes, a spike can do real damage. And the greater the high voltage surge – resulting from nearby lightning, for example – the greater the risk of harm, especially to solid-state devices.

That's why Zenith now introduces the Spike Suppressor: to protect the susceptible TV receivers and household appliances you sell or service from damaging high voltage surges!


And the Zenith Spike Suppressor

protects not one, but two ways.

First, the new Zenith Spike Suppressor absorbs most line voltage spikes so only a safe voltage level reaches the protected equipment.

Second, heavy or prolonged voltage surges cause the Zenith Spike Suppressor to cut off power completely for added protection and to signal the need for a replacement.

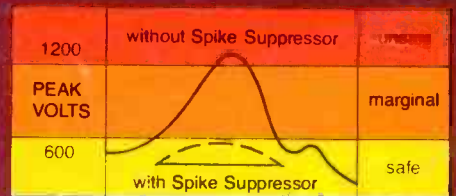That's double-duty protection against spikes and reason enough for you to stock and sell the Zenith Spike Suppressor. Your bottom line's another. So call your Zenith distributor now!



In this graph, the solid curve represents the excess voltage or "spike" imposed on an electric system and, represented by the dotted line, the protection provided household appliances as the Zenith Spike Suppressor absorbs the excess voltage and prevents it from surging thru the system.

## ZENITH

The quality goes in before the name goes on.®