

PRACTICAL

ELECTRONICS

SEPTEMBER 1971

209

...BURST-FIRE...

POWER CONTROLLER



Also inside...

TIMER
with **DIGITAL READOUT**

ADCOLA Soldering Instruments add to your efficiency

THE NEW 'INVADER'

ADCOLA L.646

for Factory Bench Line Assembly

A precision instrument—supplied with standard 3/16" (4.75 mm) diameter, detachable copper chisel-face bit*.

Standard temp. 360°C at 23 watts.

Special temps. from 250°C—410°C.

*Additional Stock Bits (illustrated) available

COPPER

B 38 $\frac{1}{8}$ " — 3.2 mm CHISEL FACE

B 14 $\frac{1}{4}$ " — 2.4 mm CHISEL FACE

B 24 $\frac{1}{8}$ " — 4.75 mm SCREWDRIVER FACE

B 12 $\frac{1}{8}$ " — 4.75 mm EYELET BIT

B 58 $\frac{1}{2}$ " — 6.34 mm CHISEL FACE

LONG LIFE

B 42 LL $\frac{1}{8}$ " — 4.75 mm CHISEL FACE

B 38 LL $\frac{1}{8}$ " — 3.2 mm CHISEL FACE

B 14 LL $\frac{1}{4}$ " — 2.4 mm CHISEL FACE

B 44 LL $\frac{1}{8}$ " — 4.75 mm SCREWDRIVER FACE

PRICE
£1.85



Don't take chances. We don't. All our ADCOLA Soldering Instruments are of impeccable quality. You can depend on ADCOLA day after day. That's why they're so popular. You get consistent good service... reliability... from our famous thermally controlled ADCOLA Element and the tough steel construction of this ideal production tool.

* Write for price list and catalogue

ADCOLA

Regd. Trade Mark

ADCOLA PRODUCTS LTD.,

(Dept. L), ADCOLA HOUSE, GAUDEN RD., LONDON, S.W.4.

Telephone: 01-622 0291/3 • Telegrams: Soljoint London Telex • Telex: Adcola London 21851



EX RENTAL TV'S

19" — £29.95

23" — £39.95

All Channels 405/625

2 Years Guarantee.

Free List by return.

19" Slim line TV's £14.95. Guaranteed 2 years. Send for List. Carr. & Ins. all sets £1.95. Daily demonstrations to personal shoppers.

TEAK HI-FI STEREO CABINETS £14.95

Brand New 44" wide x 16" deep x 18" high with Legs. A superb piece of furniture. Carr. £1.00.

TRANSISTOR GANG CONDENSERS 30p. MINIATURE AM POST 5p. PRECISION TAPE MOTORS £1.95. 200/240V. POST 20p.

Transistor Radio Cases: 25p each. Size 9 1/2" x 6 1/2" x 3 1/2". P. & P. 15p. SPEAKERS 50p 2 1/2" 8Ω BRAND NEW. P. & P. 5p.

TRANSISTORS Post Free

AC 126 AF 179 OC 81D

AC 128 OC 45

AF 114 OC 71

AF 117 OC 81 15p each

POTENTIOMETERS 23p each

Double & Switched 500 KΩ/500 KΩ 3 1/2" shaft

Double & Switched 500 KΩ/100 KΩ 2" shaft

Double & Switched 1 MEG/100 KΩ 1 1/2" shaft

Post. & Pack. 5p.—4 for 10p

KNOBS 100,000 to clear (Brand New)

100 assorted Radio & T.V. knobs 50p.

Postage 25p. (If you require sets 2 to 6 just ask)

TV TUBES REBUILT GUARANTEED 2 YEARS



14"—£3.95, 17" & 19"—£5.95,

21" & 23"—£6.45.

Exchanged Bowls. Carr. 53p.


DUKE & CO. (LONDON) LTD.

621/3 Romford Road, Manor Park, E.12

Phone 01-478 6001-2-3 Stamp for Free List

PHOTOELECTRIC KIT

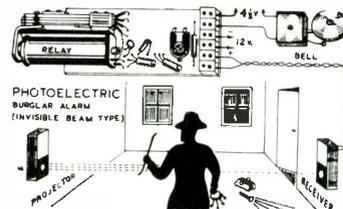CONTENTS: 2 P.C. Chassis Boards, Chemicals, Etching Manual, Infra-Red Phototransistor, Latching Relay, 2 Transistors, 3 Diodes, Resistors, Gain Control, Terminal Block, Elegant Case, Screws, etc. In fact everything you need to build a Steady-Light Photo-Switch/Counter/Burglar Alarm, etc. (Project No. 1) which can be modified for modulated-light operation.



PHOTOELECTRIC KIT £1.95

Postage and Pack. 15p (UK)

Commonwealth: SURFACE MAIL 20p

AIR MAIL £1.00

Australia, New Zealand, S. Africa, Canada and U.S.A.

Also Essential Data Circuits and Plans for Building

10 Advanced Designs

INVISIBLE BEAM OPTICAL KIT

Everything needed (except plywood) for building: 1 Invisible-Beam Projector and 1 Photocell Receiver (as illustrated). Suitable for all Photoelectric Burglar Alarms, Counters, Door Openers, etc.

CONTENTS: 2 lenses, 2 mirrors, 2 45-degree wooden blocks. Infra-red filter, projector lamp holder, building plans, etc. Price £1.00 Postage and Pack. 5p (U.K.). Commonwealth: Surface Mail 10p, Air Mail 30p.

LONG RANGE INVISIBLE BEAM OPTICAL KIT

CONTENTS: As above. Twice the range of standard kit. Larger Lenses, Filter, etc. Price £1.50. Postage and Pack. 5p (U.K.). Commonwealth: Surface Mail 15p, Air Mail 50p.

JUNIOR PHOTOELECTRIC KIT

Versatile invisible-beam, Relay-less, Steady-light Photo-Switch, Burglar Alarm, Door Opener, Counter, etc., for the Experimenter.

CONTENTS: Infra-Red Sensitive Phototransistor, 3 Transistors, Chassis, Plastic Case, Resistors, Screws, etc. Full Size Plans, Instructions, Data Sheet "10 Advanced Photoelectric Designs". Price £1.00. Postage and Pack. 5p (U.K.). Commonwealth: 10p; Airmail 20p.

JUNIOR OPTICAL KIT

CONTENTS: 2 Lenses, Infra-red Filter, Lampholder, Bracket, Plans, etc. Everything (except plywood) to build 1 miniature invisible beam projector and photocell receiver for use with Junior Photoelectric Kit.

Price 50p. Post and Pack. 5p (U.K.). Commonwealth: Surface Mail 10p; Air Mail 20p.


YORK ELECTRICS Mail Order Dept.

335 BATTERSEA PARK ROAD, LONDON, S.W.11

Send S.A.E. for full details, a brief description of all Kits and Projects

"guid gear in sma' buik" from NKT

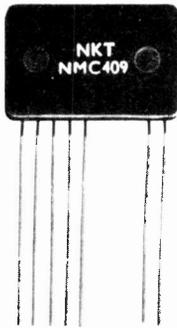With a range of thick film hybrid microcircuits off the shelf, Newmarket brings alive for you the old Scottish proverb quoted above—
"Good things come in small packages."



NMC409 Slow Speed Eccles-Jordan "Divide-by-two"

This RST flip-flop is designed specifically for slow speed switching in industrial controls where standard monolithic TTL/DTL finds it difficult to cope with the large voltage transients arising and where the precise stabilised 5-1V d.c. supply needed for TTL/DTL is difficult to provide (and costly). The NMC409 can work on any unregulated supply of 6-24V, and is immune to fast voltage spikes because it is designed not to switch faster than 10 kHz. Size: 1.1in × 0.7in × 0.23in. One-off price £2.50

NMC396 Precision 6V Regulator d.c. Supply

This self-contained d.c. voltage regulator provides a precise 6V, 150mA d.c. output from a 7-15V d.c. input. The hybrid assembly technique allows the output voltage to be set during manufacture

typically to within 25mV of 6V (in contrast to the wider absolute tolerances unavoidable in monolithics). The NMC396 has all the electrical robustness and stability of a discrete-component assembly and incorporates overload protection. Ideal for deriving a precise 6V from a 9 or 12V battery, it can also be fed from a standard d.c. power pack such as the NKT PC101.

Size: 0.60in × 0.60in × 0.25in. One-off price £2.50



NMC426 Optoelectronic Solid State Logic Indicator


This microcircuit is designed primarily to indicate visually the state of a binary logic circuit but can be used in any circuit calling for a visual indication of the existence or absence of a d.c. voltage at a test point. Completely self-contained it only requires three connections to a nominal 5V d.c. supply, to earth and to the test point. The light display is a gallium arsenide phosphide solid state diode lamp with virtually unlimited life. The NMC426 incorporates an internal d.c. amplifier enabling the light to switch on with an input drive of only 1µA or 2V, and it takes a current of only a few µA from standard TTL/DTL logic gates. Size: 0.42in × 0.31in × 0.13in. One-off price £2.83



NMC809A Wide Band Amplifier

This wide band amplifier is a self-contained d.c. feedback pair (with output buffer stage) with access to the internal feedback loop for response tailoring. The hybrid assembly technique enables the low frequency gain to be set in manufacture to precisely 22dB and gives a narrow gain spread difficult to achieve by monolithic techniques. Usable for bandwidths up to 50MHz, the NMC809A employs the easily handled standard dual-in-line package. Its thick film hybrid assembly eliminates the parasitic stray capacitances to earth unavoidable with monolithics and gives it the electrical stability and robustness of discrete component designs.

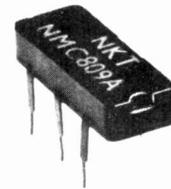Size: 0.71in × 0.28in × 0.15in. One-off price £3.34



distributors

For further details contact one of the distributors listed below. (In the case of large scale requirements you can save time by referring direct to Newmarket.)

Coventry Factors Ltd.,
Coronet House,
Upper Well Street,
Coventry,
Warwickshire CV1 4AF
Tel. 0203-21051/5
Telex 311243

G.S.P.K. (Sales) Ltd.,
Hookstone Park,
Harrogate,
Yorkshire.
Tel.: Harrogate 86258
Telex 57962

I.T.T. Electronic Services Ltd.,
Edinburgh Way,
Harlow, Essex.
Tel. 02796-26777
Telex 81146

S.D.S. (Portsmouth) Ltd.,
Hilsea Industrial Estate,
Portsmouth PO3 5JW.
Tel.: 0715/65311
Telex 86114

Eastern Aero Electrical Services Ltd.,
Building 202,
Enfield Road,
Hounslow, Middlesex.
Tel. 01-759 1314

Hird-Brown Electronics Ltd.,
Lever Street,
Bolton,
BL3 6BJ, Lancashire.
Tel.: Bolton 27311
Telex 63478

L.S.T. Electronic Components Ltd.,
7 Coptfold Road,
Brentwood,
Essex.
Tel.: Brentwood 226470
Telex 99443

NKT Newmarket
Transistors
Ltd.
Exning Rd., Newmarket, Suffolk
Tel.: Newmarket (0638) 3381
Telex 81358

IMPORTANT. THIS LATEST 1971 MODEL INCORPORATES ALL THE LATEST TECHNOLOGICAL IMPROVEMENTS AND SUPERSEDES ALL EARLIER MODELS! YES, THIS SENSATIONAL BRAND NEW VEF 204 RUSSIAN 8 WAVEBAND PORTABLE RADIO, DESIGNED FOR WORLD WIDE RECEPTION, will probably make your present radio seem like a "crystal set"! It's far better than any other 8 wave radio that even they have produced before! It even incorporates a special **MARINE WAVEBAND** to receive spoken communications from ship-to-shore! Complete with optional battery eliminator for both battery and mains use! It represents the finest value we have ever offered! We're almost giving them away at only £13.97—a mere fraction of even today's Russian miracle price! In fact we challenge you to compare the performance and value with that of £42.00 radios! *You just can't lose, we'll refund your money instantly if you are not astounded! Purer and sweeter tone than ever! Much wider band spread than hitherto, for absolutely "pin-point" station selection! Yes, the Russians have really surpassed themselves this time, proving once again their fantastic ability in the field of electronics and brilliantly reflecting their advanced micro-circuitry techniques in the field of spaceship and satellite communications. YOU GET THIS AMAZING SET FROM US AT A PRICE THAT BEARS NO RELATION TO ITS TRUE VALUE! Yes, 8 separate wavebands, including Standard Long, Medium and Short Waves to cover the world. PLUS special "ship-to-shore" **MARINE BAND**: Unique side control waveband selection unit gives incredible ease of station tuning! Thousands of different transmissions, and stations at your fingertips 24 hours a day, including ships at sea, etc. and messages from all over the world—truly nothing is secret! The radio enthusiast can have the world in the palm of his hand! You must hear it to believe it! Superb, sweet tone—controlled from a whisper to a roar that will fill a hall! Genuine push-pull output! Separate ON/OFF volume and Treble/Bass tone controls! **Pres-bution dial illumination!** Take it anywhere—runs economically on standard batteries (obtainable everywhere) or direct through battery eliminator from 220/240V AC mains supply. Internal ferrite rod aerial plus built-in telescopic aerial extending to full 31in. length. It's also a fabulous **CAR RADIO**—any speed, requires no additional aerial, **UNIQUE!** Elegant Black and Chrome finish case. **SIZE 11ins. x 9ins. x 3ins.** overall approx. Magnificently designed and superbly made to give years of perfect service. Complete with **WRITTEN GUARANTEE**, manual with simple operating instructions and circuit diagram. **ONLY £13.97** (with mains/battery eliminator £1.38 extra). **BOX, POST, ETC. 50p.** Standard batteries 38p extra. Can also be used through extension amplifier, tape recorder or public address system. Send today or call at either store, but **HURRY!** It's the chance of a lifetime. (Sorry—we cannot change these new radios for any earlier model already purchased.) Send quickly or call. Refund guaranteed.

RUSSIAN WORLD BEATER!

JUST ARRIVED!

The Fabulous BRAND NEW 1971

WORLD WIDE RECEPTION
THOUSANDS OF TRANSMISSIONS AND STATIONS THE WORLD OVER!

NOT JUST A RADIO—BUT TECHNOLOGICAL MAGIC!

THIS OFFER ONLY FROM US!

VEF 204 8 WAVEBAND

10 TRANSISTOR PLUS 2 DIODES PORTABLE RADIO

AND NOW WITH 'SHIP-TO-SHORE' MARINE BAND

BATTERY MODEL £13.97p
BOX POST ETC. 50p

WE COULDN'T EVEN MAKE THEM FOR OUR FANTASTIC PRICE!

***COMPARE IT'S PERFORMANCE with £42 RADIOS!**



SHOPERTUNITIES LTD. SL

Dept. PE/8, 164 UXBRIDGE ROAD, LONDON W12 8AQ (facing Shepherd's Bush Green). (Thursday 1 p.m., Friday 7 p.m.)

ALSO AT 37/39 HIGH HOLBORN, LONDON, W.C.1 (opposite Chancery Lane). (Wed. 1, Thurs. 7). Both stores open from Monday to Saturday from 9 a.m. until 6 p.m.

G. F. MILWARD 369 Alum Rock Road, Birmingham B8 3DR. Tel. 021-327 2339

VEROBOARD
2 1/2in x 1in x 0.15in 6p 5in x 3 1/2in x 0.15in 28p 3 1/2in x 3 1/2in x 0.1in 24p
3 1/2in x 2 1/2in x 0.15in 16p 17in x 2 1/2in x 0.15in 55p 5in x 0.15in 23p
3 1/2in x 3 1/2in x 0.15in 20p 17in x 3 1/2in x 0.15in 74p 5in x 3 1/2in x 0.1in 28p
5in x 2 1/2in x 0.15in 20p 3 1/2in x 2 1/2in x 0.1in 21p
Spot Face Cutter 38p. Pin Insert Tool 48p. Terminal Pins (0.1 or 0.15) 36 for 18p. Special Offer Pack consisting of 5 2 1/2in x 1in boards and a Spot Face Cutter—50p.

RECORD PLAYER CARTRIDGES. Well below normal prices!
G90 Magnetic Stereo Cartridges, Diamond Needle, 6mV output, £4. ACOS GP 67/2 (Mono, Crystal) 75p. ACOS GP 91/3 (Compatible, Crystal) £1. ACOS GP 93/1 (Stereo, Crystal, Sapphire) £1.25. ACOS GP 93/1D (Stereo, Crystal, Diamond) £1.63. ACOS GP 94/1 (Stereo, Ceramic, Sapphire) £1.50. ACOS GP 94/1D (Stereo, Ceramic, Diamond) £1.88. ACOS GP 95/1 (Stereo, Crystal with two L.P./Stereo needles) £1.25.

TRANSISTORISED FLUORESCENT LIGHTS, 12 volt. All with reversed polarity protection. 8 watt type with reflector suitable for tents, etc. £3. Postage/Packing 25p. 15 watt type, batten fitting for caravans £4. Postage/Packing 25p. 13 watt type, batten with switch. 22in x 2in. x 1in £5. Postage/Packing 25p. THESE CAN BE SENT ON APPROVAL AGAINST FULL PAYMENT.

MULLARD POLYESTER CONDENSERS
1,000pF, 1,200pF, 1,500pF, 1,800pF, 2,200pF, 15p per dozen (all 400V working). 0.15µF, 0.22µF, 0.27µF, 30p per dozen (all 160V working). 25% discount for lots of 100 of any one type.

RESISTORS
1/2 and 1 watt. Most values in stock. 50p per 100. 10p per dozen of any one value. **WIRE WOUND MAINS DROPPERS.** Hundreds of values from 0.7 ohm upwards. 1 watt to 50 watts. A large percentage of these are multi-tapped droppers for radio/television. Owing to the huge variety these can only be offered "assorted" at 50p per dozen.

SILVER MICA/CERAMIC/POLYSTYRENE CONDENSERS
Large range in stock, 75p per 100 of any one value. 15p per dozen.
RECORDING TAPE BARGAIN! The very best British Made low-noise high-quality Tape! 5in Standard 38p. Long-play 45p. 5 1/2in Standard 45p. Long-play 60p. 7in Standard 60p. Long-play 82p. We are getting a fantastic number of repeat orders for this tape. Might we suggest that you order now whilst we still have a good stock at these low prices?

STOCKTAKING CLEARANCE! IMPOSSIBLE TO REPEAT!
We have huge numbers of components in quantities too small to advertise individually. In order to "clear the decks" we have made up parcels containing a mixture of carbon and wire-wound resistors, electrolytic and paper condensers, controls, transistors, diodes etc., for a tiny fraction of normal price. It is emphasised that these are mixed parcels only—contents cannot be stipulated! Sold only by weight.
Gross weight 2 lb. £1 (postage 20p)
Gross weight 5 lb. £2 (postage 30p)

NEW! NEW! NEW! NEW!

An aerosol spray providing a convenient means of producing any number of copies of a printed circuit both simply and quickly.

Method: Spray copper laminate board with light sensitive spray. Cover with transparent film upon which circuit has been drawn. Expose to light. (No need to use ultra-violet.) Spray with developer, rinse and etch in normal manner.

Light sensitive aerosol spray £1.00
Developer spray 50p

SPECIAL 50p PACKS. ORDER 10 PACKS AND WE WILL INCLUDE AN EXTRA ONE FREE ! ! !

RESISTORS, 1/2 watt		TRANSISTORS	
assorted	100 50p	P.N.P. Untested but mainly O.K.	50 50p
Wire-wound 1 to 3 watt	20 50p	N.P.N. Untested but mainly O.K.	50 50p
5 to 7 watt	15 50p	OC71 equivalent	5 50p
10 watts	10 50p	Light-sensitive Diodes	10 50p
Multi-tapped	12 50p	(These produce up to 1mA from light)	
PAPER CONDENSERS		BY 127 Rectifiers	4 50p
Tv types	50 50p	IN4007 Rectifiers	4 50p
Miniature	100 50p	(1200V peak)	
ELECTROLYTIC CONDENSERS		STC 3/4 Rectifiers	6 50p
Suitable for Mains		WIRE	
Radio/Tv	10 50p	Solid Core. Insulated	100yd 50p
Transistor types	20 50p	Stranded ditto	50yd 50p
Mixed (both types)	15 50p	SOLAR CELLS	
POLYSTYRENE CONDENSERS	100 50p	Large Selenium	2 50p
MULLARD POLYESTER CONDENSERS		Small	3 50p
50 50p		(6 cells will power a Micromatic radio)	
100 50p		CRYSTAL TAPE RECORDER	
SILVER MICA NUTS AND BOLTS. Mixed length/type		MIKES	1 50p
8 B.A.	100 50p	CRYSTAL EARPIECES	
6 B.A.	100 50p	3.5mm Plug 2 50p	
4 B.A.	100 50p	TRANSISTORISED Signal Injector Kit	1 50p
2 B.A.	100 50p	TRANSISTORISED Signal Tracer Kit	1 50p
EARPIECES, MAGNETIC		TRANSISTORISED CAR REV. COUNTER KIT (Needs 1 mA meter as indicator)	AI 50p
No Plug	6 50p		
2.5mm Plug	4 50p		
3.5mm Plug	4 50p		
500 MICRO-AMP LEVEL METERS	1 50p		

G. F. MILWARD, Drayton Bassett, Tamworth, Staffs. Postage (minimum) per order 15p.

DISCOUNTS UP TO 60% ON BRANDED GOODS

ALL BRAND NEW in manufacturer's sealed cartons. GUARANTEED 12 MONTHS.

SONY · LEAK · SINCLAIR · TELETON · ARMSTRONG · THORENS · PHILIPS · K.E.F. · TEAC · ROGERS · PIONEER

SPECIAL OFFER

Garrard SP25 Mk.III
Goldring G800H
Teak plinth and tinted cover. Ready wired for immediate use.

£19.50

Please add £1.15 for post and packing

TURNTABLES

Please add 50p for post and packing

*Garrard SP25 Mk. III	£10.75
*Garrard 2025TC with stereo cart.	£8.00
*Garrard 2025TC with Sonotone 9TAHC	£8.95
*Garrard 3000 with Sonotone 9TAHC	£10.25
*Garrard SL65B	£13.25
*Garrard AP76	£18.75
*Garrard SL72B	£24.00
*Garrard SL75B	£26.00
*Garrard SL95B	£35.50
Garrard 401	£27.00
*B.S.R. MP60	£11.50
Pioneer PL12AC	£29.00
Thorens TD125	£64.50
Thorens TD125AB	£98.50
Thorens IS0A B11	£42.50
Goldring GL69/2	£21.50
Goldring GL69P2	£29.50

* Items marked can be mounted in plinth and cover, ready wired for £4.50 extra plus 25p for post and packing

AMPLIFIERS

Please add 50p for post and packing

Armstrong 521 (cased)	£41.95
Amstrad 8000	£17.70
Europhon 10 + 10	£14.50
Leak 30 Chassis	£42.95
Leak 70 Chassis	£51.50
Leak 30 Cased	£49.00
Leak 70 Cased	£59.00
Metrosound ST20	£25.25
Philips R580	£20.50
Pioneer SA500	£41.50
Pioneer SA700	£68.00
Pioneer SA900	£94.50
Rogers Ravensbrook Chassis	£36.00
Rogers Ravensbrook Cased	£41.00
Rogers Ravensbourne Chassis	£45.00
Rogers Ravensbourne Cased	£48.50
Sinclair 2000 Mk. I	£21.00
Sinclair 2000 Mk. II	£24.50
Sinclair 3000	£32.50
Sinclair PRO60/2 < Z30/PZ5	£16.00
Sinclair PRO60/2 < Z30/PZ6	£18.00
Sinclair PRO60/2 < Z50/PZ8/Trans.	£22.95
Teleton SAQ206	£18.00

TUNERS

Please add 50p for post and packing

Armstrong 523 AM/FM	£41.00
Armstrong 524 FM	£32.00
Dulci FMT7	£20.00
Dulci FMT7 Stereo	£27.50
Teleton GT101 MPLX	£31.50
Rogers Ravensbourne FET 2 Chassis	£47.00
Rogers Ravensbourne FET 2 Cased	£51.00
Rogers Ravensbrook FET 4 Chassis	£34.00
Rogers Ravensbrook FET 4 Cased	£39.00

PICK-UP ARMS

Please add 35p for post and packing

SME 3009/S2	£26.00
SME 3012/S2	£27.50

TUNER AMPLIFIERS

Please add 75p for post and packing

Armstrong 525 FM	£70.75
Armstrong 526 AM/FM	£80.75
Teleton CR10T with speakers	£28.25
Teleton F2300 (new product)	£39.75
Teleton CR55	£37.00
Teleton TSP50	£53.00
Teleton F2000	£31.50
Wharfedale 100-1	£114.00

SPEAKERS

Please add £1.25 for post and packing

Wharfedale Denton	(PRICE PER PAIR) £31.25
Wharfedale Melton	£49.90
Wharfedale Triton	£45.75
Wharfedale S110ton	£40.75
Keletron KN500	£16.50
Keletron KN700	£19.50
Keletron KNI23/3	£31.50
Keletron KNI1000	£27.50
Keletron KNI500	£37.00
Keletron KN2000	£41.50
K.E.F. by letter	
Celestion Ditton 120	£35.50
Celestion Ditton 15	£49.50
Celestion Ditton 25	£101.00
Celestion Ditton 10	£67.50
Ste-Ma 400	£34.00
Ste-Ma 300	£48.50
Hi-Fi 4	£78.00
Hi-Fi 115	£17.50
Hi-Fi 3	£63.50

GLOBAL CONTRACT SERIES

Contract 8 3-way 7 watts R.M.S.	£16.00
Contract 6 3-way 5 watts R.M.S.	£10.75

SPEAKER KITS

Wharfedale Unit 3	£20.50
Wharfedale Unit 4	£27.00
Wharfedale Unit 5	£39.00

CARTRIDGES

Please add 10p for post and packing

Goldring G850	£4.15
Goldring G800H	£5.75
Goldring G800	£6.95
Goldring G800E	£10.95
Goldring G800SE	£15.95
Sonotone 9TAHC Diamond	£1.75
Shure M3DM	£4.95
Shure M445/7/C	£7.20
Shure M55	£9.20
Shure M75E	£14.50
Shure V15 Type 2	£29.00
Shure M44E	£8.25
Shure M31E	£8.75
Shure M32E	£8.15
Audio-Technica AT66	£4.95
Audio-Technica AT35	£14.95
SMC 101	£3.15
MC15	£5.75

TAPE DECKS & RECORDERS

Please add 75p for post and packing

Teleton FXB 5100	£46.50
Teleton TCR130	£28.75

PERSONAL CALLERS VERY WELCOME!


Come and browse through our multi 1,000 foot warehouse/showroom. **NO PARKING PROBLEM**

The following branded names are not allowed to be advertised at Discount Rates—SONY, SANYO, BANG & OLUFSEN, TRIO, RAOFORD, SONAB, NIKKO, CHILTON, FERROGRAPH, LUXOR, CELESTION, AKAI, TANNON, TANOBERG, TEAC, CAMBRIDGE, ARENA, ROTEL. Send a stamped addressed envelope for a GUARANTEED DISCOUNT PRICE.

PLINTHS & COVERS

(as illustrated)

£3.25

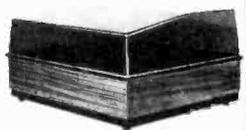

plus 35p post and packing

Finished in real teak veneer with tinted dustcover. Ready to use (fully assembled). Suitable for Garrard SP25, 2025TC, 3000, AT60, 2000, 2500, 3500, 5100, 1025, SL65B.

Also for B.S.R. McDONALD MP60 and others

Plinths and Covers for AP76, AP75, SL72B, SL75B, SL95B. £4.25 plus 35p post and packing.

Also finished in walnut to match Japanese equipment—no extra charge.

GLOBAL TRANSEUROPEAN COMBO

Made by world famous European manufacturer

COMPLETE HI-FI STEREO SYSTEM

VHF/MEDIUM/LONG WAVE Tuner Amplifier 4 watt per channel, separate tone and balance controls. Two neat speakers with wooden slatted front. Single play deck in plinth and cover. Finished in teak. Fully guaranteed 12 months. On constant demonstration.

£38.50

plus £1.25 carriage



GLOBAL AUDIO DISCOUNT WAREHOUSES

Dept. (PE1) 174 Pentonville Road, London, N1. Telephone 01-278 1769

Open Monday to Saturday 9.30 a.m. to 6 p.m. LATE NIGHT FRIDAY 7 p.m.

2 minutes from KING'S CROSS, EUSTON & ST. PANCRAS on main road leading to the East and West Country

MAIL ORDERS. Order with confidence. Send Postal Order, Cheque, Money Order, Bank Draft, Giro or Cash by Registered Mail. **CALLERS:** Please note that cheques can only be accepted together with cheque cards (not Barclay Card).



High Salary A Dream House A New Car And A Secure Future


Get into the Computer Industry the fast and easy way.

Now for the first time, anybody (no special qualifications are needed) can train outside the computer industry for an exciting career as a **computer operator in only 4 weeks** — and can earn £2,000 ++ p.a.

How? We are the only commercial training organisation in the U.K. permitted to use the famous 'Eduputer'.

JOBS GALORE! 144,000 new operators will be needed over the next five years alone. And the moment you qualify our exclusive computer appointments bureau introduces you to computer users everywhere.

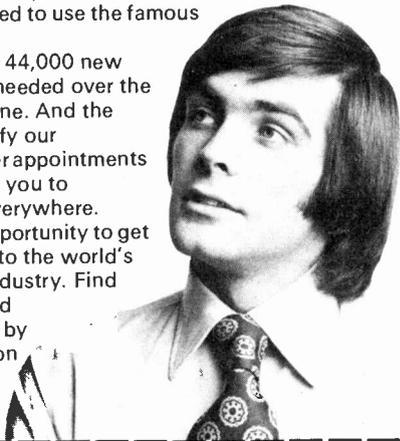This is your big opportunity to get out of a rut and into the world's fastest growing industry. Find out more **FREE** and without obligation by posting this coupon **TO-DAY.**



London Computer Operators Training Centre

C25 Oxford House, 9/15 Oxford Street, London, W.1
Telephone 01-734 2874
127/131 The Piazza, Dept. C25, Piccadilly Plaza, Manchester 1. Telephone 061-236 2935.

Please send me your **FREE** illustrated brochure on exclusive Eduputer 'hands on' training for computer operating.

Name _____

Address _____

Tel _____

MARSHALL'S INTEGRATED CIRCUITS

NEW LOW PRICES LARGEST RANGE
BRAND NEW FULLY GUARANTEED
SPECIAL OFFER 5% DISCOUNT
TO SATURDAY CALLERS
JULY AND AUGUST ONLY

MOTOROLA

We can now offer a vast range of Motorola IC's at industrial distributor prices.

Examples	£p	Data Sheets
MC724P	0-66	
MC790P	1-24	£0-12½
MC1303L	2-70	extra

FAIRCHILD (RTL)

	1-5	6-11	12+
L900	40p	37p	35p
L914	40p	37p	35p
L923	40p	37p	35p

Data sheet 12½p

LINEAR

Op. Amps.	1-5	6-11	11 24
UA702A T05	£p	£p	£p
UA702C T05	2-80	2-70	2-75
UA703C T05	1-77	0-75	0-72
UA709A T05	1-25	1-17	1-12
UA709C D1L	0-65	0-55	0-50
UA709C T05	0-55	0-52	0-46
UA710C T05	1-25	1-17	1-12
UA710C T05	0-70	0-65	0-60
UA716 T05	1-87	1-75	1-70
UA728C T05	1-62	1-50	1-42
UA730C T05	1-80	1-45	1-37
UA741C T05	0-87	0-80	0-70
UA741C D1L	0-87	0-80	0-70
LM741CN D1L	0-75	0-65	0-60

MULLARD PLESSEY

TTL	£p	SL403D	2-12½
FJH101	0-87½	SL701C	1-45
FJH121	0-87½		
FJH141	0-87½		
FJH161	0-87½		
FJH171	0-91		
FJH221	0-87½		
FJH101	1-37½		
FJH121	1-87½		
FJH141	3-12½		
FJH161	1-87½		
FJH221	3-12½		
FJK101	2-25		
FJY101	0-80		

TOSHIBA

	£p
TH9013P	£4-57
20 WATT AMP	
TH9014P	£1-50
PRE-AMP	

MULLARD DTL

	£p	MULLARD LINEAR	£p
FCH101	0-87½	TAA241	1-62½
FCH121	1-05		
FCH201	1-32½		
FCH231	1-50		
FCJ101	1-62½		
FCJ111	1-55	2-42	4-25
FCJ201	1-80	2-43	1-50
FCJ211	2-75	2-63	0-77½
FCK101	4-7½		
FCY101	1-05	2-93	0-97½
		3-00	1-75
		3-10	1-25
		3-20	0-72½
		3-50	1-75
PA222	2-60	4-35	1-47½
PA230	1-40	5-21	1-32½
PA234	0-98	5-22	3-60
PA237	2-10	5-30	4-95
PA239	2-10	5-30	1-97½
PA246	1-60	5-70	1-97½
PA264	1-90	8-11	4-45
PA265	2-00		
PA424	2-05	TAB101	0-97½
PA436	1-90	TAD100	1-97½
PA494	2-05	TAD110	1-97½

GENERAL ELECTRIC

	£p
PA222	2-60
PA230	1-40
PA234	0-98
PA237	2-10
PA239	2-10
PA246	1-60
PA264	1-90
PA265	2-00
PA424	2-05
PA436	1-90
PA494	2-05

SGS

	£1-92½	£3-75
TAA661B	£1-92½	TAA700
TAA621	£2-15	

100 or more gates may be mixed to qualify for the 100+ price. This concession also applies to MSU's.

8 Pin TO-5 I.C. Holders, £0-35
 10 Pin TO-5 I.C. Holders, £0-57½
 12 Pin TO-5 I.C. Holders, £0-62½
 14 Pin Dual-in-Line I.C. Holders, £0-20
 16 Pin Dual-in-Line I.C. Holders, £0-25

TTL LOGICS

	1-11	12-24	1-11	12-24
SN7400	0-20	0-18	SN7474	0-43
SN7401	0-20	0-18	SN7475	0-45
SN7402	0-20	0-18	SN7476	0-45
SN7403	0-20	0-18	SN7480	0-70
SN7404	0-20	0-18	SN7481	1-40
SN7405	0-20	0-18	SN7482	0-87
SN7406	0-80	0-75	SN7483	0-87
SN7407	0-20	0-18	SN7484	2-00
SN7408	0-20	0-18	SN7485	3-62
SN7409	0-20	0-18	SN7486	0-33
SN7410	0-20	0-18	SN7489	0-87
SN7411	0-23	0-21	SN7491A	1-21
SN7412	0-48	0-48	SN7492	0-87
SN7413	0-40	0-38	SN7493	0-87
SN7416	0-84	0-78	SN7494	0-87
SN7417	0-84	0-78	SN7495	0-87
SN7420	0-20	0-18	SN7496	0-87
SN7423	0-51	0-47	SN7497	6-40
SN7425	0-48	0-45	SN74100	1-65
SN7427	0-48	0-45	SN74104	1-52
SN7428	0-80	0-75	SN74105	1-52
SN7430	0-23	0-21	SN74107	0-52
SN7432	0-48	0-45	SN74110	0-80
SN7433	0-80	0-75	SN74111	1-57
SN7437	0-84	0-80	SN74118	1-30
SN7438	0-84	0-80	SN74119	1-92
SN7440	0-23	0-21	SN74121	2-00
SN7442	0-85	0-81	SN74123	2-85
SN7443	2-88	2-70	SN74145	1-80
SN7444	2-88	2-70	SN74150	3-52
SN7445	2-80	2-40	SN74151	1-40
SN7446	1-00	0-95	SN74153	1-40
SN7447	1-00	0-95	SN74154	2-20
SN7448	1-00	0-95	SN74155	1-68
SN7449	1-00	0-95	SN74156	1-68
SN7450	0-20	0-18	SN74157	1-92
SN7451	0-20	0-18	SN74160	1-80
SN7453	0-20	0-18	SN74161	2-60
SN7454	0-20	0-18	SN74162	4-26
SN7456	0-20	0-18	SN74163	4-26
SN7470	0-40	0-38	SN74164	2-20
SN7472	0-32	0-30	SN74165	2-25
SN7473	0-43	0-41	SN74166	4-45

RCA

Type	1-24	25-99	Type	1-24	25-99
CA3000	1-80	1-60	CA3033A	4-28	3-80
CA3000V1	1-80	1-60	CA3035	1-28	1-10
CA3001	2-68	2-40	CA3035V1	1-23	1-10
CA3001V1	2-68	2-40	CA3036	0-78	0-65
CA3002	1-80	1-60	CA3037	1-85	1-47
CA3002V1	1-80	1-60	CA3037A	2-53	2-25
CA3004	1-80	1-60	CA3038	2-53	2-25
CA3005	1-17	1-05	CA3038A	3-40	3-03
CA3006	2-80	2-50	CA3039	0-84	0-75
CA3007	2-63	2-34	CA3040	2-40	2-14
CA3008	1-80	1-60	CA3041	1-37	1-27
CA3008A	2-96	2-64	CA3042	0-99	0-97
CA3010	1-37	1-23	CA3043	1-37	1-23
CA3010A	2-53	2-25	CA3044	1-20	1-07
CA3011	0-74	0-65	CA3044V1	1-20	1-07
CA3011PRP			CA3045	1-23	1-09
CA3012	0-74	0-65	CA3046	0-69	0-60
CA3012V1	0-89	0-79	CA3047	1-37	1-25
CA3013	1-05	0-94	CA3047A	2-53	2-25
CA3014	1-24	1-10	CA3048	2-04	1-81
CA3014V1	1-24	1-10	CA3050	1-84	1-64
CA3015	2-09	1-86	CA3051	1-34	1-20
CA3015A	3-40	3-03	CA3052	0-68	0-47
CA3016	2-48	2-19	CA3053	0-60	0-41
CA3016A	3-73	3-33	CA3054	1-09	0-97
CA3018	0-84	0-75	CA3055	1-69	1-51
CA3018A	1-10	0-99	CA3056	1-20	1-07
CA3019	0-84	0-75	CA3056A	3-19	2-85
CA3020	1-28	1-13	CA3059	1-65	1-46
CA3020A	1-60	1-43	CA3060	1-71	1-37
CA3021	1-56	1-39	CA3062	2-55	2-27
CA3021V1	1-56	1-39	CA3064	1-20	1-07
CA3022	1-30	1-18	CA3065	1-20	1-07
CA3023	1-28	1-13	CA3066	2-11	1-84
CA3026	1-00	0-90	CA3067	2-18	1-94
CA3026PRP			CA3068	2-43	2-16
CA3028A	1-00	0-90	CA3070	1-71	1-37
CA3028B	1-05	0-94	CA3072	1-66	1-48
CA3029	0-87	0-77	CA3075	1-13	1-00
CA3029A	1-65	1-47	CA3076	1-30	1-18
CA3030	1-37	1-23	CA3078	3-19	2-85
CA3030A	2-53	2-25	CA3080	0-75	0-70
CA3033	2-53	2-25	CA3080A	3-19	2-85

See our ad. on opposite page for transistors, diodes and passive components and P. & P. charges. Many more types in stock and arriving daily. Please inquire.

LARGEST STOCKS WIDEST RANGE

SEMICONDUCTORS & COMPONENTS

BRAND NEW GUARANTEED

TRANSISTORS

2G301	20p	2N3405	45p	40311	35p	BC172	15p	BSW70	27p	NKT238	25p
2G302	20p	2N3414	22p	40312	47p	BC175	22p	BSX19	17p	NKT240	27p
2G303	20p	2N3415	27p	40314	37p	BC182	12p	BSX20	17p	NKT241	27p
2G306	42p	2N3417	37p	40320	47p	BC189	12p	BSX21	37p	NKT242	20p
2G308	20p	2N3417	37p	40324	32p	BC184	12p	BSX22	45p	NKT243	20p
2G309	30p	2N3570	11-25	40323	32p	BC121L	12p	BSX26	45p	NKT244	17p
2G371	15p	2N3572	97p	40326	37p	BCY30	27p	BSX28	35p	NKT245	20p
2G374	20p	2N3605	27p	40329	30p	BCY31	30p	BSX60	82p	NKT261	20p
2G381	22p	2N3606	27p	40344	27p	BCY32	50p	BSX61	82p	NKT262	30p
2N404	22p	2N3607	22p	40347	57p	BCY33	25p	BSX76	22p	NKT264	20p
2N696	20p	2N3754	12p	40348	57p	BCY34	30p	BSX77	27p	NKT271	20p
2N697	20p	2N3763	12p	40360	42p	BCY39	80p	BSX78	27p	NKT274	20p
2N698	25p	2N3704	17p	40361	47p	BCY40	50p	BSX79	27p	NKT275	20p
2N706	12p	2N3705	15p	40362	57p	BCY42	15p	BSY10	27p	NKT281	27p
2N708	15p	2N3707	15p	40370	57p	BCY43	15p	BSY11	27p	NKT401	87p
2N709	62p	2N3708	9p	40407	40p	BCY54	32p	BSY25	15p	NKT402	90p
2N718	25p	2N3709	10p	40408	52p	BCY58	22p	BSY26	17p	NKT403	75p
2N726	30p	2N3710	12p	40410	57p	BCY60	97p	BSY27	17p	NKT404	62p
2N727	30p	2N3711	12p	40410	57p	BCY70	20p	BSY28	17p	NKT405	62p
2N914	17p	2N3715	22-20	40467A	35p	BCY71	42p	BSY29	17p	NKT451	62p
2N916	17p	2N3716	22-20	40468A	35p	BCY72	17p	BSY32	25p	NKT452	62p
2N918	30p	2N3791	22-75	40600	57p	BCZ10	27p	BSY36	25p	NKT459	47p
2N929	22p	2N3819	37p	40673	11-25	BCZ11	27p	BSY37	25p	NKT460	47p
2N930	27p	2N3823	37p	AC107	30p	BCZ12	27p	BSY38	25p	NKT613F	32p
2N1090	20p	2N3824	12p	AC126	20p	BCY39	22p	BSY40	32p	NKT674F	30p
2N1091	22p	2N3854A	27p	AC127	25p	RD121	65p	BSY41	32p	NKT677F	30p
2N1131	25p	2N3855	27p	AC128	25p	RD123	82p	BSY42	32p	NKT713	25p
2N1132	25p	2N3855A	30p	AC129	22p	BD124	72p	BSY43	32p	NKT718	30p
2N1302	17p	2N3856	30p	AC176	25p	BD131	85p	BSY44	32p	NKT10439	30p
2N1303	17p	2N3856A	30p	AC187	82p	BD132	85p	BSY45	37p	NKT10439	37p
2N1304	22p	2N3858	35p	AC188	37p	BDY10	21-37p	BSY54	40p	NKT10519	32p
2N1305	22p	2N3858A	35p	AC188	37p	BDY11	21-37p	BSY56	90p	NKT20329	47p
2N1306	25p	2N3859	27p	ACY14	27p	BDY17	1-75	BSY78	47p	NKT26339	47p
2N1307	25p	2N3859A	32p	ACY19	25p	BDY18	1-75	BSY82	52p	NKT80111	97p
2N1308	30p	2N3860	30p	ACY20	25p	BDY19	1-97p	BSY90	12p	NKT80113	12p
2N1309	30p	2N3866	11-50	ACY21	25p	BDY20	1-12p	BSY95A	12p	C111	75p
2N1507	17p	2N3877	40p	ACY22	20p	BDY38	97p	C1424	27p	C425	25p
2N1613	25p	2N3877A	40p	ACY28	20p	BDY60	82p	C426	40p	C428	37p
2N1621	32p	2N3881	40p	ACY31	25p	BDY61	82p	C441	30p	C442	30p
2N1632	30p	2N3900A	40p	ACY40	20p	BDY62	21-25	C425	25p	C428	37p
2N1637	30p	2N3901	47p	ACY41	25p	BF115	25p	C426	40p	C441	30p
2N1638	27p	2N3903	35p	ACY44	40p	BF117	47p	C428	37p	C442	30p
2N1671B	11	2N3904	35p	AD140	52p	BF163	37p	C744	30p	D16P1	37p
2N1711	25p	2N3905	37p	AD143	57p	BF167	32p	D16P2	40p	D16P3	40p
2N1889	32p	2N3906	37p	AD150	62p	BF173	32p	D16P4	40p	D16P5	40p
2N1893	27p	2N3907	37p	AD161	37p	BF177	30p	D16P6	40p	D16P7	40p
2N2147	27p	2N4059	11p	AD162	37p	BF178	30p	D16P8	40p	D16P9	40p
2N2148	57p	2N4060	12p	AF106	42p	BF179	30p	D16P10	40p	D16P11	40p
2N2160	57p	2N4061	12p	AF114	25p	BF180	35p	D16P12	40p	D16P13	40p
2N2193	40p	2N4062	12p	AF115	25p	BF181	32p	D16P14	40p	D16P15	40p
2N2193A	42p	2N4244	47p	AF116	25p	BF184	25p	D16P16	40p	D16P17	40p
2N2194A	30p	2N4282	17p	AF117	25p	BF187	25p	D16P18	40p	D16P19	40p
2N2211	27p	2N4303	47p	AF118	82p	BF188	17p	D16P20	40p	D16P21	40p
2N2218	32p	2N4287	17p	AF119	20p	BF195	20p	D16P22	40p	D16P23	40p
2N2219	32p	2N4288	17p	AF124	20p	BF196	42p	D16P24	40p	D16P25	40p
2N2220	25p	2N4289	17p	AF125	20p	BF197	42p	D16P26	40p	D16P27	40p
2N2221	25p	2N4290	17p	AF126	20p	BF198	42p	D16P28	40p	D16P29	40p
2N2222	30p	2N4291	17p	AF127	17p	BF200	52p	D16P30	40p	D16P31	40p
2N2287	11-07	2N4292	17p	AF139	37p	BF224	20p	D16P32	40p	D16P33	40p
2N2297	30p	2N4303	47p	AF178	42p	BF225	20p	D16P34	40p	D16P35	40p
2N2368	17p	2N5027	62p	AF179	72p	BF237	22p	D16P36	40p	D16P37	40p
2N2369	17p	2N5028	57p	AF179	72p	BF238	22p	D16P38	40p	D16P39	40p
2N2369A	17p	2N5029	47p	AF180	32p	BF244	32p	D16P40	40p	D16P41	40p
2N2410	42p	2N5030	42p	AF239	27p	BFW58	27p	D16P42	40p	D16P43	40p
2N2484	27p	2N5172	12p	AF279	47p	BFW59	25p	D16P44	40p	D16P45	40p
2N2484A	32p	2N5174	62p	AF280	47p	BFW60	25p	D16P46	40p	D16P47	40p
2N2539	22p	2N5175	52p	AF280	62p	BFW61	47p	D16P48	40p	D16P49	40p
2N2540	22p	2N5176	40p	AFZ11	32p	BFX12	22p	D16P50	40p	D16P51	40p
2N2613	35p	2N5232A	30p	ASY26	25p	BFX13	22p	D16P52	40p	D16P53	40p
2N2614	30p	2N5245	45p	ASY27	37p	BFX29	30p	D16P54	40p	D16P55	40p
2N2646	52p	2N5246	42p	ASY28	27p	BFX30	30p	D16P56	40p	D16P57	40p
2N2696	32p	2N5249	67p	ASY30	27p	BFX33	37p	D16P58	40p	D16P59	40p
2N2711	25p	2N5265	25-25	ASY36	25p	BFX44	37p	D16P60	40p	D16P61	40p
2N2712	25p	2N5266	22-75	ASY50	25p	BFX68	67p	D16P62	40p	D16P63	40p
2N2713	27p	2N5267	62-62	ASY51	32p	BFX84	25p	D16P64	40p	D16P65	40p
2N2714	30p	2N5305	37p	ASY54	32p	BFX85	25p	D16P66	40p	D16P67	40p
2N2865	62p	2N5306	40p	ASY76	25p	BFX86	25p	D16P68	40p	D16P69	40p
2N2904	30p	2N5307	37p	ASZ21	42p	BFX87	27p	D16P70	40p	D16P71	40p
2N2904A	32p	2N5308	37p	ASZ21	42p	BFX88	27p	D16P72	40p	D16P73	40p
2N2905	37p	2N5309	62p	AI103	11-25	BFX89	62p	D16P74	40p	D16P75	40p
2N2905A	40p	2N5310	42p	BC107	12p	BFX93A	62p	D16P76	40p	D16P77	40p
2N2906	25p	2N5354	27p	BC107	12p	BFY10	32p	D16P78	40p	D16P79	40p
2N2906A	27p	2N5355	27p	BC108	12p	BFY11	42p	D16P80	40p	D16P81	40p
2N2907	30p	2N5356	32p	BC109	12p	BFY17	22p	D16P82	40p	D16P83	40p
2N2929	15p	2N5363	47p	BC119	30p	BFY18	32p	D16P84	40p	D16P85	40p
2N2924	15p	2N5366	32p	BC115	27p	BFY19	32p	D16P86	40p	D16P87	40p
2N2925	15p	2N5367	57p	BC116A	27p	BFY20	11-60	D16P88	40p	D16P89	40p
2N2926	15p	2N5457	37p	BC118	32p	BFY21	42p	D16P90	40p	D16P91	40p
Green	14p	28005	75p	BC121	20p	BFY24	45p	D16P92	40p	D16P93	40p
Yellow	12p	28020	82	BC122	20p	BFY25	45p	D16P94	40p	D16P95	40p
Orange	12p	28102	82	BC123	25p	BFY26	45p	D16P96	40p	D16P97	40p
2N3013	32p	28103	25p	BC126	35p	BFY29	50p	D16P98	40p	D16P99	40p
2N3014	32p	28104	25p	BC140	30p	BFY30	50p	D16P100	40p	D16P101	40p
2N3053	25p	28501	32p	BC147	17p	BFY41	47p	D16P102	40p	D16P103	40p
2N3054	50p	28502	30p	BC148	12p	BFY43	50p	D16P104	40p	D16P105	40p
2N3055	75p	28503	27p	BC149	17p	BFY50	22p	D16P106	40p	D16P107	40p
2N3133	30p	3N128	70p	BC152	17p	BFY51	22p	D16P108	40p	D16P109	40p
2N3134	30p	3N139	11-25	BC157	17p	BFY52	17p	D16P110	40p	D16P111	40p
2N3135	25p	3N140	72p	BC157	20p	BFY53	17p	D16P112	40p	D16P113	40p
2N3136	25p	3N141	72p	BC158	17p	BFY36A	17p	D16P114	40p	D16P115	40p
2N3390	25p	3N142	55p	BC159	20p	BFY75	30p	D16P116	40p	D16P117	40p
2N3391	20p	3N143	67p	BC180	62p	BFY76	42p	D16P118	40p	D16P119	40p
2N3391A	30p	3N152	87p	BC167	15p	BFY77	47p	D16P120	40p	D16P121	40p
2N3392	17p	3N153	87p	BC168B	15p	BFY90	15p	D16P122	40p	D16P123	40p
2N3393	15p	40055	87p	BC168C	15p	BPX25	57p	D16P124	40p	D16P125	40p
2N3394	15p	40244	22p	BC169B	14p	BPX29	41-80	D16P126	40p	D16P127	40p
2N3402	22p	40251	87p	BC169C	15p	BPY10	11-80	D16P128	40p	D16P129	40p

SP25 Mk III SPECIAL!



Garrard SP25 Mk. III Single Record Player. Fitted Goldring G850 or AT68 Magnetic Stereo Cartridge as available Complete in Teak Plinth with Rigid Perspex Cover.
Total list Price over £29.
PREMIER PRICE £19.90
P. & P. 50p.



TAPE CASSETTES
C60 (60 min.) 37p 3 for £1.05
C90 (90 min.) 62p 3 for £1.80
C120 (120 min.) 87p 3 for £2.55
P. & P. 5p

All cassettes can be supplied with library cases at 3p extra each.

PREMIER QUALITY MICROPHONES

Precision made, beautifully designed and offering reliability at a reasonable price.



FANON MKO47 MINIATURE DYNAMIC
Frequency response 60-13,000Hz Impedance 50k Ω (-50dB). (Can be used with stand, hand held or around neck. Die cast body satin chrome finish. Features removable windscreen. Complete with 8ft cable, stand adaptor and Lavalier cord. **PREMIER PRICE £5.97.** P. & P. 20p.

FANON MKO45 3-WAY DYNAMIC
Frequency response 60-12,000Hz. High impedance. Complete with 8ft cable, table stand and Lavalier cord. **PREMIER PRICE £2.87.** P. & P. 20p.

FANON MKC54 DYNAMIC
Frequency response 60-12,000Hz. Impedance 50k Ω (-60dB) and 150 ohms (-71dB). On/off switch. Complete with 20ft cable and stand adaptor. **PREMIER PRICE £8.97.** P. & P. 20p.

E.M.I. 13x8in. HI-FI SPEAKERS



Fitted two 2in tweeters and crossover network. Available with 8 or 15 ohm impedance. Handling capacity 10W. Brand new.

£3.47 P. & P. 40p

METER BARGAINS

MODEL GT800 MULTIMETER

A precision made pocket sized test meter, ideally suited for testing electronic circuits or electronic appliances. Supplied complete with test lead and batteries.
Ranges—D.C. voltages: 10, 50, 250, 1,000V (1,000 O.P.V.). A.C. voltages: 10, 50, 250, 1,000V (1,000 O.P.V.). D.C. current: 1mA, 100mA. Resistance: 0-150 Kohms. Decibels: -10 to +22dB (at a.c. 10V range).

£2.47. P. & P. 17p.



MULTIMETER 20,000 O.P.V. MULTIMETER

Features large easy-to-read meter, wide choice of ranges. With test leads, batteries and manual. Size: 4 1/2in x 3 1/2in x 1in.
Ranges: D.C. voltages: 0-5-25-50-250-500-2,500V. A.C. voltages: 0-10-50-100-500-1,000V. D.C. current: 0-50 μ A-2.5mA-250mA. Resistance: 0-6,000 ohms, 0-8 meg ohms (300 ohms and 30 Kohms at centre scale) Capacity: 10 uuf to 600uf, 0.01uf to 1uf. Decibels: -20 to +22dB.

£4.90. P. & P. 17p.



MODEL CT620 MULTITESTER

Ranges: D.C. voltages: 0, 5, 25, 100, 500/1,000V (20,000 ohms/V). A.C. voltages: 0, 5, 25, 100, 500, 1,000V (10,000 ohms/V). D.C. current: 0, 50 μ A, 0mA, 5mA, 50mA, 500mA. Resistance: 0, 6k Ω , 600k Ω , 6M Ω , 60M Ω . Decibels: -20 to +22dB in 5 ranges.

£5.62. P. & P. 17p.

"VERITONE" RECORDING TAPE

SPECIALLY MANUFACTURED IN U.S.A. FROM EXTRA STRONG PRE-STRETCHED MATERIAL. THE QUALITY IS UNEQUALLED.

TENSILISED to ensure the most permanent base. Highly resistant to breakage, moisture, heat, cold or humidity. High polished splice free finish. Smooth output throughout the entire audio range. Double wrapped—attractively boxed.

LPS 3'	250'	P.V.C.	28p	DT6 5 1/2'	1800'	POLYESTER	£1.12
TT8 3'	450'	POLYESTER	37p	TT6 5 1/2'	2400'	POLYESTER	£1.87
DT3 3 1/2'	600'	POLYESTER	57p	DT5 7'	1200'	P.V.C.	82p
SP5 5'	600'	P.V.C.	42p	LP7 7'	1800'	ACETATE	75p
LP6 5'	900'	P.V.C.	50p	DT7 7'	2400'	POLYESTER	£1.25
DT5 5'	1200'	POLYESTER	75p	TT7 7'	3600'	POLYESTER	£2.50

TAPE SPOOLS 3' 5p, 5', 5 1/2', 7' 9p.
Post and Packing 3' 5p, 5', 5 1/2' 8p, 7' 10p. (3 reels and over Post Free.)



PREMIER RADIO

10 & 23, TOTTENHAM COURT ROAD, LONDON, W.1 TEL: 01-636 3451/2639
HEAD OFFICE & MAIL ORDER DEPT. 23, TOTTENHAM CT. RD. TEL: 01-636 3451



The Unique MULTI-MINI TWIN-VICE



An extra "Pair of hands" for those tricky jobs

ASSEMBLY—SOLDERING—GLUING—WIRING—DRILLING ETC.

- INDEPENDENT ADJUSTMENT OF THE TWO VICE HEADS TO ANY ANGLE WITH POSITIVE LOCKING.
- JAWS WILL FIRMLY GRIP, ROUND, FLAT, SQUARE, OR HEXAGONAL PARTS.

TWIN VICE: £5.90 (24p P & P)

ALSO AVAILABLE
SINGLE VICE: £3.37 (20p P & P)
COVENTRY MOVEMENT CO. LTD.
DEPT. PE4, BURNSALL ROAD
COVENTRY CV5 6BU STD 0203 - 74363

** OPPORTUNITY KNOCKS ** SAVE £ £ £ £'s

Low cost guaranteed full spec. components from leading manufacturers.
SN74N TTL (Plastic DIL)

7400, 10, 20, 30—Gates	1-24	25-99	100+
7401, 02, 03, 04, 40, 50, 51, 53, 54, 60—Gates	21p	18p	14p
7413, 70, 72—Dual Schmitt and Single F/F's	33p	31p	27p
7442, 141—BCD/DEC Decode and Driver	86p	76p	65p
7446, 47—30V and 15V BCD/7 Seg. Dec. Dr.	£1.40	£1.30	£1.20
7473, 74, 76—Dual F/F's	42p	38p	35p
7480, 83—Adders	86p	76p	65p
7475—Quad Latch	45p	43p	41p
7481—16-bit Memory	£1.33	£1.23	£1.13
7482—Binary Adder	£1.28	£1.18	98p
7486—Excl. OR Gate	78p	68p	58p
7490, 92, 93, 94, 95—Cntrs. and Rgstrs.	86p	76p	65p
74121—Monostable	86p	76p	65p
74122—Retrig. Mono	£1.35	£1.30	£1.28
74123—Dual Retrig. Monostable	£2.30	£2.20	£2.10
7445, 145—30V and 15V 80mA BCD/DEC Driv.	£1.78	£1.68	£1.59
74190, 191—Reversible Counters	£3.30	£3.00	£2.80

*SPECIAL OFFER—7400, 10, 20, 30. Quantities of 25 or more, mixed. ALL ONE PRICE 12p

*Mix Devices for quantity price
*Free 74N wall chart with every TTL order
Op. Amps—709/741—8 and 14 lead DIL and TO5 53p 45p 40p
Dual Op's—709DN 741DN, 747DN £1.30 £1.20 99p


*Free report on audio amp design using Op Amps with every Op Amp order over £1.50. Report alone, 15p inc. p. & p.

1N4148/914/916 Diodes 4p 3p 2.5p
BC107/108/109/182/183/184 —G.P. NPN's 11p 10p 9p
BC212/213/214—PNP Complementaries 15p 14p 13p
TIS 43—Unijunction 40p 38p 37p
2N3819—F.E.T. 40p 38p 37p

Terms: C.V.O. 50p min. ord. P. & P. 10p U.K. 25p Europe, 60p Overseas. Delivery subject to stock. Overseas orders welcome.

ELMTEX LTD. (COMPONENTS DIV.)
83 HIGH STREET, DUNMOW, ESSEX
Tel.: Great Dunmow 2202

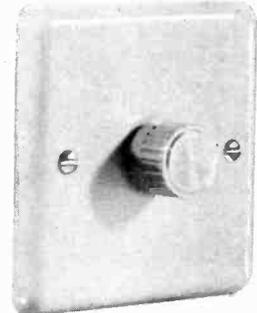Vary the strength of your lighting with a DIMMASWITCH





The DIMMASWITCH is an attractive and efficient dimmer unit which fits in place of the normal light switch and is connected up in exactly the same way. The ivory mounting plate of the DIMMASWITCH matches modern electric fittings. Two models are available, with the bright chrome knob controlling up to 300 w or 600 w of all lights except fluorescents at mains voltages from 200-250 v, 50Hz. The DIMMASWITCH has built-in radiator: 600—£3.20 Kit Form £2.70
300—£2.70 Kit Form £2.20

All plus 10p post and packing.
Please send C.W.O. to:—

DEXTER & COMPANY
1 ULVER HOUSE, 19 KING STREET
CHESTER CH1 2AH Tel. 0244-25883
As supplied to H.M. Government Departments

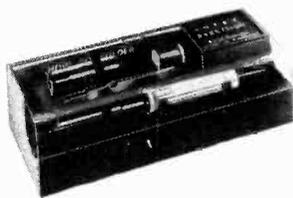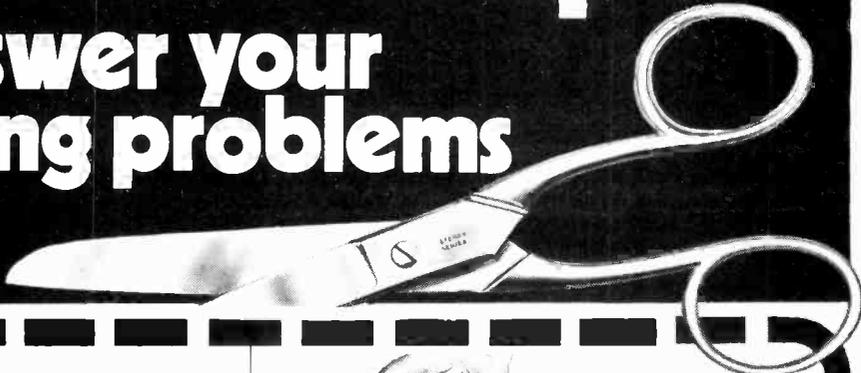cut out this coupon and answer your soldering problems




SK1 SOLDERING KIT

In rigid plastic "tool box" containing Model CN - 15 watts - 240 volts miniature iron fitted $\frac{3}{16}$ " bit. Spare bits $\frac{5}{32}$ " and $\frac{3}{32}$ ". Reel of resin-cored solder, heat sink, cleaning pad, stand and booklet "How to Solder".

Send me

kit(s) **£2.75**

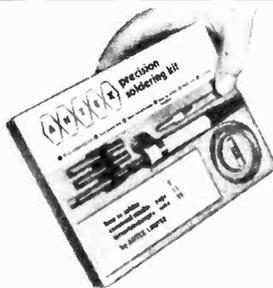

SK2 SOLDERING KIT

In polystyrene pack, containing 15 watt miniature soldering iron, 240 volts fitted with $\frac{3}{16}$ " bit, 2 spare bits $\frac{5}{32}$ " and $\frac{3}{32}$ ". Coil of resin-cored solder, heat sink, 1A fuse and booklet "How to Solder".

Send me

kit(s) **£2.40**




Model CN 240/2
- 15 watts
- 240 volts

Fitted with nickel plated $\frac{3}{32}$ " bit and packed in handy transparent box.

Send me

pack(s) **£1.70**

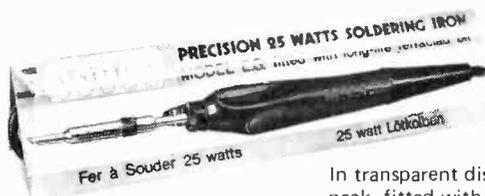

ES240 D 25 watt
soldering iron

In transparent display pack, fitted with long life iron-coated bit $\frac{1}{8}$ " diam. Interchangeable spare bits $\frac{3}{32}$ ", $\frac{1}{16}$ ", $\frac{1}{4}$ " (extra) available. Improved design to ensure strong and reliable high speed iron. Heats up in 2 minutes.

Send me

pack(s) **£1.83**



M.E.S.
Battery-operated
12 volt
soldering iron

Complete with 15 ft (4.50m) lead, 2 heavy gauge clips for instant

connection to car battery and a guide 'How to Solder'. Packed in strong plastic wallet.

Send me

kit(s) **£1.95**



from electrical and radio shops or by Free Post (No stamp required) from ANTEX Ltd. FREE POST PLYMOUTH, PL1 1BR
Tel: (0752) 67377/8

● Please send the ANTEX colour catalogue.

● Please send the following:

I enclose cheque /P.O./Cash (Giro No. 2581001)

NAME

ADDRESS

LOW COST ELECTRONIC AND SCIENTIFIC EQUIPMENT AND COMPONENTS

DIGITAL INDICATORS KGM TYPE M3

A neat compact indicator providing selective display 0-9. Fig. Ht. 18mm. Panel mounting. 6mm tubular midjet flange lamps. Supplied with 28V bulbs. Finished matt black anodized. W. 1in, H. 2in. Wt. 4oz. £3-25. Post free.



OVERHAULED AVOMETERS

Models 40, 47A, 48A. (Models 47A and 48A are Admiralty pattern.)
D.C. volts: 0-12, 1-2, 12, 120, 480, 1,200.
Amps: 0-012, 0-12, 1-2, 12.
A.C. volts: 12, 120, 480, 1,200.
Amps: 0-012, 0-12, 1-2, 12.
Ohms: 1,000, 10,000, 1,000,000 (external voltage source).
Sensitivity: 166.6 Ohms/Volt, 333.3 Ohms/Volt when divided by two button is pressed on both a.c. and d.c. ranges. £16. P. & P. 70p.



Complete with voltage multiplier for 480V and 3,600V. Current shunts for 120A and 480A. A.C. current transformer for 20A and 60A. In special wooden box. £18-50. P. & P. £1.
Due to demand it may not always be possible to supply a particular model, and a different type to that ordered may be dispatched. These models are electrically identical.

MUMICATOR PRICE LIST

END READING (16mm Fig. Height)	
B13 base	
GR10M/U Clear	0-9 Display
GR10M Amber filter	0-9 Display
Quantity	Price each (less base)
1-3	£1-40
4-10	£1-35
11-25	£1-30
26-100	£1-20

Bases 20p each

SIDE READING (14mm Fig. Height)	
0-9 Display	
XN3F/A	38mm leads Amber Filter
XN3F	38mm leads Red Filter
XN3A/F	6mm leads Red Filter
XN3A	6mm leads Clear Filter
XN11/F	38mm leads Red Filter
XN23/FA	38mm leads Amber Filter

SPECIAL DISPLAYS	
XN9	38mm leads Clear Filter
NX10/C	6mm leads Clear Filter
NX22	38mm leads Clear Filter

Displays Fig. "1"	
Displays "+, - and ~"	
Displays "X, A, Ω, Vmv"	
Quantity	Price each
1-3	£1-15
4-10	£1-10
11-25	£1-05
26-100	95p

All Post free.

TELESCOPIC CABINET LID STAYS



Lift lid once stays open. Lift twice catch releases and allows lid to close. Closed length 7 1/2in, open length 10 1/2in. Finished dull plating brand new. 4 for £1. Post free.

SLIDING CABINET LID STAYS



Similar principle to above closed length 1 1/2in, open length 5 1/2in. Finished dull plating brand new. 5 for £1. Post free.

NEW MICROSWITCHES—HONEYWELL

1 PL 900 6 contacts. 15 Amp. 125/250 volts. Single pole. ON/OFF. Plunger operated. L 1 7/8", W. 5/8", H. 3/4". Price 5 for £1-25. Post free.

NEW FRACTIONAL H.P. CAPACITOR MAINS MOTORS

230V, 50Hz, 0.65A, 1/20 h.p., 2,850 r.p.m. Cont. rated. Shaft 3/16in dia. x 1/2in long. Circular clamp mounting. £3-50. Post free.

DELAY LINE LEXOR MDN 2484D


Miniature resin encapsulated module. Total delay 50msec to 10msec. Tapped at 10% intervals. Impedance 75 ohms to 10 kΩ. 30V wkg. Attention 0.5 dB/msec. Also available MDN 2484C 3 micro-sec 600 ohm impedance. 2 1/2in x 1 1/2in x 1 1/2in. £1-50. Post free.

MIDGET POWER RELAY OMRON Mk I

230V, 50Hz. 1PDT new. Faulty plating on frame. 5 for £1-50. Post free.


MEMORY CORE STORES

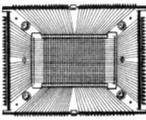42 x 52, 2kΩ bit ferrite core store. C/W quantity OAI/O load diodes. Ideal for building computer store, holding information, teaching experiments, demonstrations, etc. Price £25-25. P. & P. 38p.



BRAND NEW CAPACITOR REVERSIBLE SINGLE PHASE PARVALUX MOTORS

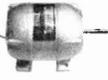230/250V, 50Hz, 2,800 r.p.m.; 130 h.p. cont. rated; 3/16in dia. shaft; 3/16in long foot mounting; wt. 6lb. C/W capacitor. £3-50. Post free.



CONSTRUCT YOUR OWN FRUIT MACHINE

1inch coloured displays (ex fruit machines). Operate on rear lamp projection principle. Displaying 12 pictures as follows: 3 cherries, pistol, lemon, barrel, bell, orange, plum, rugby ball, 5 pointed star, man holding glass of ale, BAR and HELD in words. 2 screw panel mounting W 1 1/2" H 2 1/2". Uses 10mm tubular MCC bulbs. Offered at bargain price to clear stocks. 3 units for £1 (less bulbs). P. & P. 30p.

VOLTMETER "AS NEW"


Ex-Factory Superior quality 5" Moving Coil 200 ohms/Volt. A.C./D.C. 0-150 & 0-300 volts. Mirror Scale. Ernest Turner Model 32 in teak carrying case. 10 1/2" x 8 1/2" x 4". £5-50 (Post free).

TELEPHONE DIALS

Clear Perspex, very good condition. No markings. 75p each. P. & P. 25p.

OSCILSCOPE TYPE CT 52

A very handy miniature portable instrument for general purpose applications. W 1 1/2" H 2 1/2" D 5 1/2". 2 1/2in diam. tube. Wave form investigation from 10Hz-20MHz. Pulse monitoring duration 50 microseconds to 0.1 microsecond. Time base free running 10Hz-40kHz. Also single sweep facility from 50 microseconds to 3 microseconds. "Y" Amplifier. Delay Line Calibration Voltage. Power supply 110-250V. 40/60Hz, 50W. Supplied with metal carrying case. L. 13in. H. 8in. W. 5 1/2in. Weight 14 1/2lb (less Graticule, assembly and Viewing Hood). Price £22. P. & P. £1-50.

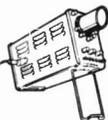

GOOD QUALITY INSTRUMENTS TAKEN IN PART EXCHANGE OR PURCHASED FOR CASH

Electronic Brokers Ltd. (Dept. P.E.) 49-53 Pancras Road London NW1 Tel. 01-837 7781 Telex 267307

Open Mon.-Fri. 9-6 p.m.

VALVES SAME DAY SERVICE NEW! TESTED! GUARANTEED!

SETS 1R5, 1S5, 1T4, 8S4, 3V4, DAF91, DF91, DK91, DL92, DL94. Set of 4 for £1-02, DAF96, DP96, DK96, DL96, 4 for £1-48

	5p	10p	15p	20p	25p	30p	35p	40p	45p	50p	55p	60p	65p	70p	75p	80p	85p	90p	95p	1.00
1R5	0-28	25U4GT	0-57	DL96	0-38	EL500	0-62	PCL82	0-36	UABC80	0-38									
1R5	0-22	30C1	0-30	DY86	0-28	EM80	0-41	PCL83	0-30	UAF42	0-31									
1T4	0-16	30C15	0-63	DY87	0-28	EM81	0-41	PCL84	0-37	UBC41	0-32									
3S4	0-28	30C17	0-80	DY802	0-40	EM84	0-33	PCL85	0-45	UBF80	0-34									
3S4	0-37	30C18	0-87	EAF80	0-39	EM87	0-37	PCL86	0-41	UBF80	0-35									
5U4G	0-28	30F3	0-76	EAF42	0-50	FY81	0-38	PCL88	0-39	UCB84	0-36									
5V4G	0-37	30FL1	0-63	EB41	0-40	EY86	0-32	PCL800	0-77	UCB85	0-38									
5Y3GT	0-30	30FL12	0-72	EB91	0-11	EZ40	0-43	PEN4A	0-42	UCF80	0-36									
5Z4G	0-37	30FL14	0-72	EB33	0-40	EZ41	0-43	PEN36C	0-70	UCH42	0-32									
6J30L2	0-58	30L1	0-32	EBC41	0-54	EZ80	0-23	PPL200	0-58	UCH81	0-32									
6AL5	0-11	30L15	0-62	EBC90	0-22	EZ81	0-24	PL36	0-49	UCH82	0-35									
6AM6	0-13	30L17	0-73	EBF80	0-33	EZ82	0-37	PL81	0-46	UCB83	0-35									
6AQ5	0-28	30F4	0-85	EBF89	0-31	GZ92	0-43	PL8A	0-51	UF41	0-36									
6AT6	0-22	30F12	0-77	ECC81	0-18	GZ34	0-50	PL82	0-33	UF89	0-33									
6AT6	0-22	30F19	0-65	ECC82	0-23	KT41	0-77	PL83	0-35	UL41	0-30									
6BA6	0-22	30PL1	0-63	ECC83	0-35	KT61	0-55	PL84	0-33	UL44	1-00									
6BE6	0-23	30PL13	0-85	ECC85	0-28	KT66	0-33	PL500	0-65	UL84	0-35									
6B6	0-42	30PL14	0-70	ECC804	0-60	LN319	0-63	PL504	0-67	UM84	0-22									
6B7G	0-60	30PL15	0-90	ECC80	0-30	LN329	0-72	PM84	0-37	UY41	0-41									
6BD6G	1-10	35L8T	0-45	ECC89	0-36	LN339	0-63	PX25	1-17	UY85	0-28									
6F14	0-45	35W4	0-28	ECH35	0-30	N78	0-37	PY82	0-55	VP48	0-77									
6F23	0-71	35Z4GT	0-25	ECH42	0-63	P61	0-50	PY33	0-55	Z77	0-22									
6F25	0-62	807	0-45	ECH81	0-29	PABC80	0-35	PY81	0-27	Transistors										
6K7G	0-12	6063	0-62	ECH83	0-41	PC86	0-51	PY82	0-27	AC107	0-17									
6K8G	0-17	AC/V P2	0-77	ECH84	0-37	PC88	0-51	PY83	0-28	AC127	0-18									
6Q7G	0-28	B349	0-65	ECL80	0-35	PC96	0-42	PY88	0-35	AD140	0-37									
68L7GT	0-37	EB29	0-62	ECL82	0-33	PC97	0-40	PY80	0-37	AF115	0-20									
6V6G	0-23	CCH35	0-85	ECC89	0-40	PC900	0-37	PY801	0-27	AF116	0-20									
6V6GT	0-32	CL31	1-25	EF39	0-35	PC84	0-32	R19	0-32	AF117	0-20									
6X4	0-28	CY31	0-33	EF41	0-40	PC85	0-30	R20	0-65	AF118	0-48									
6XGT	0-28	DAF91	0-22	EF80	0-24	PC88	0-45	U25	0-68	AF125	0-17									
10P13	0-60	DAF96	0-38	FF85	0-31	PC89	0-47	U26	0-65	AF127	0-17									
12AH8	2-25	DF33	0-38	FF86	0-31	PC8189	0-51	U47	0-68	OC26	0-25									
12AU6	0-28	DF96	0-38	FF81	0-13	PC878	0-30	U50	0-65	OC44	0-12									
12AU7	0-28	DH77	0-22	EF183	0-29	PC82	0-32	U2	0-31	OC71	0-12									
12AX7	0-28	DK32	0-37	EF184	0-32	PC86	0-47	U78	0-24	OC72	0-12									
19BG6G	0-87	DK91	0-28	EH90	0-42	PC800	0-67	U191	0-62	OC75	0-12									
20F2	0-67	DK92	0-42	EL33	0-55	PCF801	0-33	U193	0-42	OC81	0-12									
20P3	0-85	DL96	0-38	EL34	0-49	PCF802	0-45	U231	0-72	OC8D	0-12									
20P4	0-92	DL92	0-28	EL84	0-24	PCF805	0-67	U301	0-52	OC82	0-12									
25L6GT	0-25	DL94	0-37	EL90	0-26	PCF806	0-60	U259	0-51	OC8D	0-12									
						PCF808	0-72	U801	0-96	OC170	0-22									

READERS RADIO

85 TORQUAY GARDENS, REDBRIDGE, ILFORD ESSEX Tel. 01-550 7441

Postage on 1 valve 5p, on 2 or more valves 3p per valve extra. Any parcel insured against damage in transit 3p extra.

PARKERS SHEET

METAL FOLDING MACHINES

HEAVY VICE MODELS

With Bevelled Former Bars

Carr. free

No. 1. Capacity 18 gauge mild steel > 36in. wide ... £15

No. 2. Capacity 18 gauge mild steel > 24in. wide ... £10

No. 3. Capacity 16 gauge mild steel > 18in. wide ... £10


Also new bench models. Capacities 36in. > 1

Discosound

P. A. AND DISCOTHEQUE EQUIPMENT

— A COMPREHENSIVE RANGE COVERING EVERY REQUIREMENT

AMPLIFIERS, MIXERS, LIGHT CONTROL UNITS.

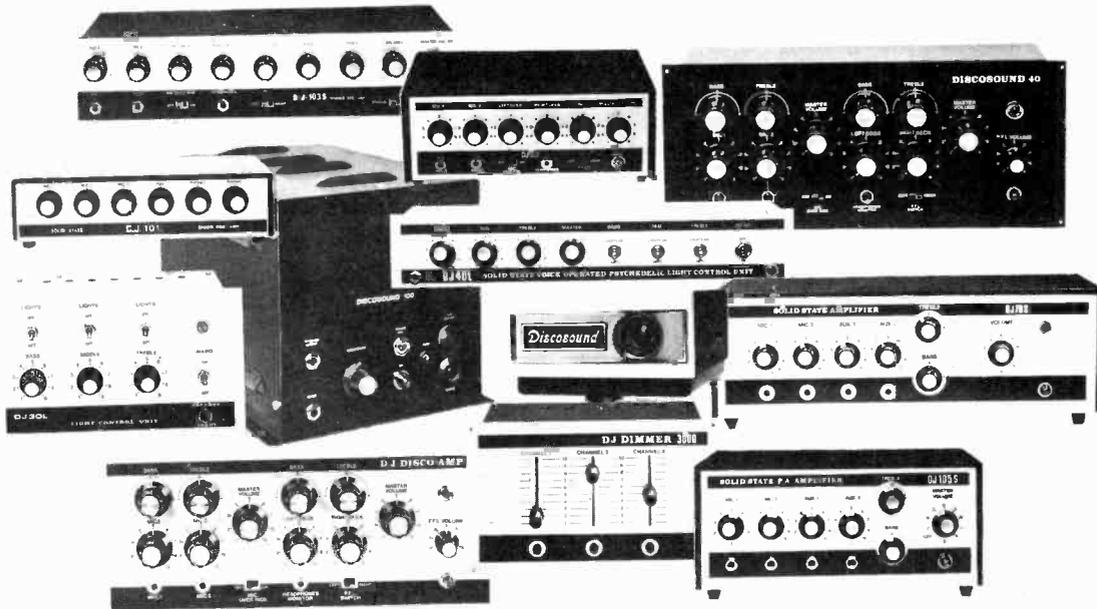

D.J.101 Mixer Pre-Amplifier

Six inputs allow full mixing facilities for all types of equipment. 9V battery operation. Size: 10½in x 2½in x 4½in. Suggested Retail Price £14

D.J.102 Discotheque Mixer Pre-Amplifier

Four inputs each with its own volume control plus master volume control, PFL monitoring and mic. override switches. Size: 10½in x 4in x 4in. Suggested Retail Price £25

D.J.105S P.A. Amplifier

4-channel mixing facilities each with separate inputs and volume controls. 30W r.m.s. power output: a.c. mains 200/250V a.c. Size: 11½in x 5in x 6in. Suggested Retail Price £41

D.J.70S Integrated Mixer Amplifier

Power output 70W r.m.s. 4-channel mixer with separate inputs and volume controls, plus master volume and separate bass and treble controls. Size: 15½in x 6in x 6in. Suggested Retail Price £68

D.J. Disco-Amp.

Designed specifically for use with discotheques. Power output 100W r.m.s. Two mic. inputs and two gram inputs, with independent volume controls plus bass and treble controls. Incorporates many exclusive features. Front panel size: 16½in x 7in. Suggested Retail Price £85

Discosound 40 Discotheque Pre-Amplifier

Features independent inputs and volume controls for two microphones and two turntables plus separate bass, treble and master volume controls. Self-powered and ideal for use with Discosound 100 Power Amplifier (is capable of running 10 of these power amplifiers—total 1,000W). Front panel size: 16½in x 7in. Suggested Retail Price £40

Discosound 100 Power Amplifier

100W r.m.s. power amplifier (at 8 ohms) utilising all silicon transistors and features full automatic overload against short or open circuits. Frequency response 20–20,000Hz ±3dB. Distortion less than 1% at 70W r.m.s. ±1dB. Size: 10½in x 8in x 7in. Suggested Retail Price £49.50

D.J.103S Stereo Pre-Amplifier

A high quality stereo discotheque pre-amp unit. Incorporating two microphone and two turntable inputs each with independent volume control, plus bass, treble, balance and master volume control. Offers full mixing and monitoring facilities. Front panel size: 16½in x 3½in. Suggested Retail Price £49.50

D.J.30L Psychedelic Light Control Unit

3-channel light unit enabling bass, middle and treble frequencies from the amplifier to be operated individually. Handles 1,000W per channel. Front panel size: 10in x 6in. Suggested Retail Price £37.50

D.J.40L Sound Operated 3-channel light unit

Features built-in microphone which eliminates the need for connections to any amplifier or sound source. Handles 1,000W per channel. Front panel size: 16½in x 3in. Suggested Retail Price £56.25

D.J. DIMMER 3000

3-channel light dimmer unit offered in two versions: Dimmer 3000—a straight 3-channel dimmer unit with mains input and three light outputs. Dimmer 3000S—for use in conjunction with D.J.30L Light Control unit only and has three mains inputs and three light outputs. Front Panel size: 10in x 6in. Suggested Retail Price £32.50

Discosound Disco-Wheel

A projector designed to project a range of liquid wheels and colour change wheels for special lighting effects, adding colour and variety to any form of entertainment. Size: 7½in x 10½in x 5½in. Suggested Retail Price £50

A range of complete Discotheques with matching Speakers also available.

DISCOSOUND PRODUCTS ARE GUARANTEED FOR 12 MONTHS

For full details of the Discosound range of products call at or write to your nearest Discotheque Centre — Demonstrations given at any time.

DISCOSOUND

122 Balls Pond Road, London N.1. Tel: 01-254 5779

HENRY'S RADIO LTD.,

309 Edgware Road, London W.2. Tel: 01-723 6963

CRESCENT RADIO LTD.

11 & 40 MAYES ROAD, LONDON N22 6TL 888 3206

MAIL ORDER DEPT.
No. 11
MAYES RD.
LONDON
N22 6TL

COMPONENTS AND HI FI FOR THE HOME CONSTRUCTOR

OUR SHOPS ARE OPEN ALL DAY FROM 9 A.M. TO 6 P.M. 6.30 P.M. ON FRIDAY (WE CLOSE ALL DAY THURSDAY)
13 SOUTH MALL, EDMONTON, N.9 803 1685

"CRESCENT" D.J. PARTY AMPLIFIER "P100"



A completely new style 100W Amplifier especially designed for the D.J. who expects his equipment to look and sound really good, and still keep a moderate price.
10-30,000Hz response.
All loudspeaker systems suitable.
Full output into 4 ohm.

All silicon transistors. F.E.T. at front end. Real value at £42 plus £1 P. & P. and insurance.

★ £2 DISCOUNT ★

If purchased at the same time as the Psychedelic Light Control Unit. If you require more information please send a S.A.E.

STEREO HEADSET

8 ohm impedance, complete with plug and 5ft lead. A very comfortable phone set. Listen to stereo without noise interrupting the pleasure. Wonderful value. £2-50 plus 10p P. & P.



STEREO JUNCTION BOX

For stereo amplifiers without stereo jack socket. £1-25 plus 8p P. & P.

PSYCHEDELIC LIGHT CONTROL UNIT



Three Channel: Base—Middle—Trebble. Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier, and connect three 250V up to 500W lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed).
£18-50 plus 38p P. & P.

If you require more information please send S.A.E.

CRESCENT CASSETTES



Top quality cassettes at unbeatable prices (complete with standard storage case): C60 38p, C90 63p, C120 88p plus 5p P. & P.

S. G. BROWN HEADPHONES

Used! But in good working condition. These Type "F" phones are 4,000Ω imp. and a bargain at



50p Plus 10p. P. & P. per pair

CHROME TV STAND



28in x 8 1/2in x 16in high. This modern design TV stand would make an ideal base for a coffee table and is a bargain at:

£1-63 plus 25p P. & P.

EA1000 3 WATT AUDIO AMPLIFIER MODULE

An Audio Amplifier designed around the TAA621 Linear I.C.:
Supply Voltage 8-24V
Speaker Imp. 8-16 ohm
Frequency 50Hz-20kHz
Overall Size 2in. x 3in. x 1in.
Ideal Amplifier for radios, record players, stereo units, etc.
Full technical data and diagrams with each module. All guaranteed and a bargain at



BRIGHTNESS CONTROL

Full control over 300 watts of incandescent lighting. Thyristor light dimmer mounted on a standard switch block ready to fit into a MK. Box. Enjoy the pleasure of having the precise amount of light you require at any time. Our Price £2-75 plus 8p P. & P. each.



BATTERY ELIMINATOR

Plug your Transistor Radio, Amplifier, Cassette, etc., into the a.c. mains through this compact eliminator. 2 1/2in x 2in x 3in approx. 41V £1-50. 6V £1-50. 9V £1-50. 7 1/2V complete with cable and plug for Philips Cassette.



£2 plus 8p P. & P. each.

MAINS KEYNECTOR

Keynector connects any Electrical Equipment to the mains supply in seconds. Ideal for bench, garage, demonstrations, etc. Multi connections can be made (max load 13A fused).
ONLY £2-75 P. & P. 6p.



£2-63 + 5p P. & P.

MIDGET FLEX CONNECTOR

Approx. 2 amp rating. Two-pin non-reversible midget flex connector. Approx. size: 2in x 3in. Ideal for loudspeaker connections, etc. 8p plus 2p P. & P.


MAINS TRANSFORMER

Fused Primary 240V. Secondary 220V @ 50M/A. 6.3V @ 1A. This transformer is made to a very high standard and is a small size: 2in x 2 1/2in x 2 1/2in. 65p plus 15p P. & P.



BARGAIN BOARDS

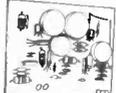Components galore for the experimenter. Ex computer boards with: Resistors, Capacitors and useful Transistors—at least 4 transistors per board.




BARGAIN PRICE 30p per board
5 BOARDS £1-20. P. & P. Free on this item.

YOURS FREE FOR 7 DAYS

The 'New Picture-Book' way of learning BASIC ELECTRICITY (5 VOLS.) BASIC ELECTRONICS (6 VOLS.)

You'll find it easy to learn with this outstandingly successful NEW PICTORIAL METHOD—the essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate, cartoon-type drawing. The books are based on the latest research into simplified learning techniques. This has proved that the PICTORIAL APPROACH to learning is the quickest and soundest way of gaining mastery over these subjects.

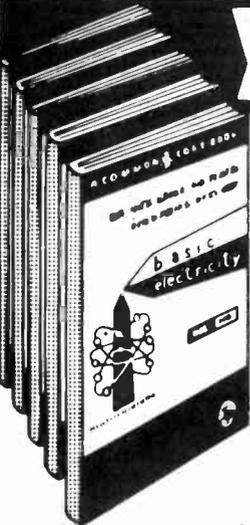

WHAT READERS SAY

"SIMPLE AND EASILY EXPLAINED"
"I have never come across or read anything so simple and easily explained."
P.L., Wood Green

"COMPLETELY SATISFIED"
"I would like to say I am completely satisfied with the wonderful manuals."
A.L.P., Buckingham

"PERFECT DETAIL"
"I find these books are exactly what I have been looking for: they explain everything in perfect detail."
H.W.R., Pontefract

A TECH-PRESS PUBLICATION

POST NOW FOR THIS OFFER !!

The series will be of exceptional value in training mechanics and technicians in Electricity, Radio and Electronics.

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT BR2 7HP

Please send me WITHOUT OBLIGATION TO PURCHASE, one of the above sets on 7 DAYS FREE TRIAL, I will either return set, carriage paid, in good condition within 7 days or send the following amounts. BASIC ELECTRICITY £4.50. Cash Price on Down Payment of £1 followed by 4 fortnightly payments of £1 each (Total £5). BASIC ELECTRONICS £5.40. Cash Price on Down Payment of £1 followed by 5 fortnightly payments of £1 each (Total £6). This offer applies to UNITED KINGDOM ONLY. Overseas customers cash with order, prices as above.

Tick Set required (Only one set allowed on free trial)

BASIC ELECTRICITY BASIC ELECTRONICS

Prices include Postage and Packing.

Signature _____
(If under 18 signature required of parent or guardian)

NAME _____
BLOCK LETTERS
FULL POSTAL ADDRESS _____

SEMI-CONDUCTORS/VALVES

ALL DEVICES BRAND NEW AND FULLY GUARANTEED

Transistors		2N3415		2N3458		BC114		15p		BFW90		2N219		30p	
2C301	20p	2N3416	27p	2N3459	48p	BC115	15p	BFW91	20p	NK723	27p				
2C302	10p	2N3439	13p	2B103	25p	BC116	15p	BFX12	22p	NK724	22p				
2C303	20p	2N3440	17p	2B104	25p	BC119	15p	BFX13	22p	NK725	22p				
2C306	30p	2N3664	17p	2B301	47p	BC121	20p	BFX30	30p	NK727	20p				
2C308	30p	2N3665	15p	2B302	47p	BC122	20p	BFX37	30p	NK728	25p				
2C309	30p	2N3666	22p	2B303	57p	BC125	15p	BFX44	37p	NK729	27p				
2C371	15p	2N3668	22p	2B304	72p	BC126	20p	BFX66	67p	NK721	27p				
2C374	20p	2N3669	25p	2B501	35p	BC134	15p	BFX84	25p	NK722	20p				
2C374	20p	2N3670	15p	2B502	35p	BC135	15p	BFX85	32p	NK723	20p				
2N388A	48p	2N3752	17p	2B503	35p	BC136	15p	BFX86	25p	NK724	17p				
2N404	20p	2N3805	27p	2B583	40p	BC137	15p	BFX87	25p	NK725	25p				
2N696	15p	2N3806	27p	3N128	70p	BC138	15p	BFX88	25p	NK726	25p				
2N697	15p	2N3807	22p	3N140	77p	BC140	35p	BFX89	62p	NK726	30p				
2N698	25p	2N3838	18p	3N141	72p	BC141	35p	BFX92A	70p	NK726	20p				
2N699	42p	2N3839A	18p	3N142	67p	BC147	15p	BFY11	42p	NK727	10p				
2N706A	11p	2N3842	10p	3N143	67p	BC148	15p	BFY18	25p	NK728	50p				
2N708	15p	2N3843	20p	40C00	50p	BC152	15p	BFY21	15p	NK729	20p				
2N709	45p	2N3844	25p	40C05	50p	BC153	15p	BFY24	40p	NK728	20p				
2N718	30p	2N3845	25p	40C11	35p	BC154	35p	BFY29	40p	NK728	20p				
2N726	25p	2N3892	18p	40C13	35p	BC157	15p	BFY30	40p	NK740	87p				
2N727	25p	2N3893	15p	40C14	35p	BC158	15p	BFY35	62p	NK740	75p				
2N914	17p	2N3702	10p	40C14	35p	BC159	15p	BFY37	25p	NK741	62p				
2N918	30p	2N3703	10p	40C15	37p	BC168B	15p	BFY52	25p	NK741	62p				
2N929	25p	2N3704	10p	40C16	37p	BC168C	15p	BFY53	17p	NK741	62p				
2N930	24p	2N3705	10p	40C17	37p	BC169A	15p	BFY56A	57p	NK742	62p				
2N937	52p	2N3706	10p	40C19	55p	BC169C	15p	BFY76	42p	NK743	47p				
2N1090	25p	2N3707	12p	40C20	47p	BC170	15p	BFY77	57p	NK743	47p				
2N1091	25p	2N3708	10p	40C23	35p	BC171	15p	BFY90	65p	NK747	42p				
2N1131	25p	2N3710	10p	40C26	37p	BC172	15p	BKX19	17p	NK778	27p				
2N1132	25p	2N3710	10p	40C26	37p	BC172	15p	BKX19	17p	NK778	27p				
2N1302	17p	2N3711	10p	40C29	47p	BC177	25p	BKX21	20p	NK778	27p				
2N1303	17p	2N3713	187p	40C34	27p	BC178	20p	BKX26	45p	NK778	30p				
2N1304	22p	2N3714	200p	40C37	47p	BC179	25p	BKX27	47p	OC16	50p				
2N1305	22p	2N3715	222p	40C38	42p	BC182	15p	BKX28	32p	OC19	37p				
2N1306	24p	2N3716	222p	40C40	42p	BC182L	10p	BKX60	82p	OC20	75p				
2N1307	24p	2N3717	222p	40C42	30p	BC183	10p	BKX61	62p	OC22	60p				
2N1308	25p	2N3791	272p	40C42	30p	BC183L	10p	BKX76	62p	OC23	60p				
2N1309	24p	2N3819	34p	40C43	30p	BC184	15p	BKX77	20p	OC23	60p				
2N1507	17p	2N3820	57p	40C46	57p	BC184L	15p	BKX78	25p	OC25	37p				
2N1613	21p	2N3823	75p	40C47	40p	BC186	25p	BKX24	15p	OC26	25p				
2N1631	35p	2N3854	27p	40C48	62p	BC187	27p	BKX26	15p	OC28	60p				
2N1632	40p	2N3854A	27p	40C49	62p	BC212L	12p	BKX26	15p	OC29	60p				
2N1637	38p	2N3854B	27p	40C50	62p	BC212L	12p	BKX27	15p	OC35	60p				
2N1638	27p	2N3855A	30p	40A12	50p	BC214L	10p	BKX27	15p	OC36	60p				
2N1639	27p	2N3856	30p	40A47A	57p	BCY10	27p	BKX29	17p	OC41	25p				
2N1701	110p	2N3856A	35p	40A68A	35p	BCY30	24p	BKX32	25p	OC42	25p				
2N1711	24p	2N3858	25p	40C28	72p	BCY31	30p	BKX36	25p	OC44	17p				
2N1889	32p	2N3858A	30p	40C60	57p	BCY32	30p	BKX37	25p	OC46	12p				
2N1893	87p	2N3859	27p	40C63	50p	BCY33	20p	BKX38	20p	OC46	15p				
2N1947	72p	2N3859A	27p	40C64	50p	BCY34	25p	BKX39	32p	OC70	15p				
2N2160	67p	2N3860	30p	AC126	20p	BCY35	20p	BKX40	32p	OC72	12p				
2N2193	40p	2N3866	150p	AC127	24p	BCY39	30p	BKX61	32p	OC72	12p				
2N2193A	42p	2N3877	40p	AC128	20p	BCY40	50p	BKX62	32p	OC73	30p				
2N2194	27p	2N3877A	40p	AC151	18p	BCY41	15p	BKX63	37p	OC74	30p				
2N2194A	30p	2N3900	37p	AC152	22p	BCY42	15p	BKX64	40p	OC75	22p				
2N2217	27p	2N3900A	40p	AC154	22p	BCY43	15p	BKX66	40p	OC76	22p				
2N2218	30p	2N3901	37p	AC157	22p	BCY44	32p	BKX79	45p	OC77	20p				
2N2219	20p	2N3903	25p	AC187	25p	BCY52	25p	BKX95A	12p	OC81	20p				
2N2220	25p	2N3904	25p	AC188	27p	BCY59	22p	BKX95A	12p	OC81	20p				
2N2221	25p	2N3905	30p	AC177	27p	BCY60	97p	C424	15p	OC81D	20p				
2N2222	20p	2N3906	30p	ACY18	24p	BCY70	15p	C460	15p	OC82	25p				
2N2222A	20p	2N4008	15p	ACY19	24p	BCY71	20p	GET102	30p	OC82D	15p				
2N2297	40p	2N4020	10p	ACY20	20p	BCY72	15p	GET113	30p	OC83	25p				
2N2368	15p	2N4060	15p	ACY21	20p	BCY73	15p	GET114	15p	OC84	25p				
2N2369	17p	2N4061	12p	ACY22	10p	BCY79	30p	GET115	20p	OC89	25p				
2N2369A	17p	2N4062	12p	ACY28	17p	BCZ10	27p	GET120	25p	OC140	25p				
2N2410	42p	2N4244	47p	ACY39	47p	BCZ11	40p	GET873	12p	OC170	25p				
2N2483	27p	2N4248	15p	ACY40	14p	BD112	50p	GET880	30p	OC171	30p				
2N2484	32p	2N4249	15p	ACY41	25p	BD116	112p	GET887	15p	OC200	40p				
2N2539	25p	2N4250	18p	ACY44	40p	BD121	62p	GET889	22p	OC201	60p				
2N2540	25p	2N4251	18p	ACY45	40p	BD122	62p	GET890	22p	OC202	75p				
2N2613	27p	2N4255	42p	AD149	47p	BD124	47p	GET896	32p	OC203	80p				
2N2614	30p	2N4256	42p	AD150	42p	BD131	75p	GET897	22p	OC204	40p				
2N2646	47p	2N4285	17p	AD161	35p	BD132	82p	GET898	22p	OC205	75p				
2N2711	25p	2N4286	17p	AD162	35p	BDY10	125p	MAT100	25p	OC206	90p				
2N2712	25p	2N4287	17p	AF109	45p	BDY20	105p	MAT110	30p	OC207	75p				
2N2713	25p	2N4289	15p	AF114	25p	BDY61	125p	MAT120	35p	OCPT1	42p				
2N2714	25p	2N4290	15p	AF115	25p	BDY62	100p	MAT121	30p	OCPT2	50p				
2N2904	20p	2N4290	15p	AF116	25p	BF117	47p	MJ400	107p	ORP61	40p				
2N2904A	25p	2N4291	15p	AF117	25p	BF117	47p	MJ420	112p	ORP61	40p				
2N2905	25p	2N4292	15p	AF118	44p	BF152	28p	MJ430	112p	P346A	22p				
2N2906	20p	2N4293	15p	AF121	30p	BF154	38p	MJ430	102p	ST140	15p				
2N2906A	25p	2N4303	47p	AF124	32p	BF158	28p	MJ440	95p	ST141	40p				
2N2907	25p	2N4304	47p	AF125	19p	BF159	57p								

HI-FI EQUIPMENT

SAVE UP TO
33 1/3% OR MORE
SEND S.A.E. FOR
DISCOUNT PRICE LISTS
AND PACKAGE OFFERS!



RECORD DECKS

B.S.R.	
Mini Mono	£4-97
CU29*	£6-70
MP60	£11-30
610	£15-15
510	£12-47
310	£10-85
MP60 T.P.D.1.	£18-75
MP60 T.P.D.2	£17-55
610 T.P.D.1.	£22-12
510 T.P.D.1.	£20-19
210 Package*	
	£11-30
H.T.70	£16-60
H.T.70 Package	



GARRARD

A40 II*	£28-40
2095 T/C*	£29-75
3500*	£29-75
8P25 III	£11-30
A70 II	£11-97
8L65B	£14-40
AP76	£20-20
8L72B	£25-00
8L75B	£27-50
8L95B	£27-00
401	£28-40

THORENS

TD 125	£59-85
TD125A B	£94-25
TX25	£6-70
TD150A II	£41-95
TD150A B II	£41-95
TX11	£3-77

!Mono *Stereo Cartridge
All other models less Cartridge
Carriage 50p extra any model.

RECORD DECK PACKAGES

Decks supplied ready wired in plinth and cover fitted with cartridge.
Garrard 2025 T/C with Sonotone
9TAHCD £13-95
Garrard 8P25 III with Goldring G800 £18-95
Garrard AP76 with Goldring G800 £30-95
BBR MP60 with Audio Technica AT-55 £21-00
Goldring GL69/2 with Goldring G800 £27-80
Goldring GL75 with Goldring G800 £45-50
Goldring GL75 with Goldring G800E £50-00
Carriage 50p extra any model.



TE-1035 STEREO HEADPHONES

Low cost high performance stereo headphones. Foam rubber ear cups. Adjustable headband. No hum impedance.
25-18,000Hz. With lead and stereo jack plug.
ONLY £1-97. P. & P. 124p.



SINCLAIR EQUIPMENT



Project 60. Package offers 2 x Z30 amplifier, stereo 60 pre-amp. P25 power supply, £18-75. Carr. 374p. Or with P26 power supply, £18-95. Carr. 374p. 2 x Z50 amplifier, stereo 60 pre-amp. P25 power supply, £20-25. Carr. 374p. Transformer for P25, £2-97; extra. Add to any of the above £2-87; for active filter unit and £16 for a pair of Q16 speakers. Project 60 FM Tuner £20-97. Carr. 374p.
All Sinclair products in stock. IC10/IC12 £2-50. 2,000 amplifier, £25. Carr. 374p. 3000 Amplifier £24-50. Carr. 374p. Neoteric amplifier £45-97. Carr. 374p.


LATEST CATALOGUE



SEND NOW—
STILL ONLY
374p
P. & P.
10p


Our new 6th edition gives full details of a comprehensive range of HI-FI EQUIPMENT COMPONENTS, TEST EQUIPMENT AND COMMUNICATIONS EQUIPMENT. FREE DISCOUNT COUPONS VALUE 50p. 272 pages, fully illustrated and detailing thousands of items at bargain prices.

TELETON SAQ-206 STEREO AMPLIFIER

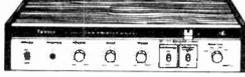

Latest exciting release. Beautifully styled with walnut case. 6 + 6 watts r.m.s. Switched inputs for Mag, Xtal, aux, tape. Incorporates volume, bass, treble, sliding balance, scratch filter and loudness controls. Rec. List £32-50. Our price £18-50. Carr. 374p.

TELETON SPECIAL OFFER!

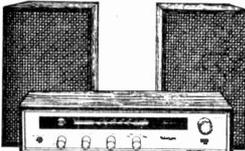

CR107 AM/FM STEREO TUNER AMPLIFIER WITH MATCHING PAIR SA1003 SPEAKER SYSTEMS
Output 4 watts per channel. Excellent reception AFC, built-in MPX. Cer/XTAL Input. Total List £50-25. Our PRICE £29-95. Carr. 624p.
Also available with Garrard 2025/T Record Changer, Plinth, cover and stereo cartridge. Ready wired. £42-50. Carr. £1.

★ TRANSISTORISED FM TUNER ★

6 TRANSISTOR HIGH QUALITY TUNER. SIZE ONLY 6.4 x 24in. 3 I.F. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Coverage 88-108 MHz. Ready built ready for use. Fantastic value for money. £8-374. P. & P. 124p. Stereo multiplex adaptors £4-974.

RUSSIAN CI-16 DOUBLE BEAM OSCILLOSCOPES
5MHz Pass Band. Separate Y1, Y2 amplifiers. Calibrated triggered sweep from 0.2µsec to 100msec/cm. Supplied complete with all accessories and instructions. £87. Carr. paid.

BELGO DA-20 SOLID STATE DECADE AUDIO OSCILLATOR

New high quality portable instrument. Sine 1Hz to 100kHz. Square 20Hz to 20kHz. Output max. +10dB (10kΩ). Operation 220/240V a.c. Size 215mm x 150mm x 120mm. Price £27-50. Carr. 25p.


TE-20RF SIGNAL GENERATOR

Accurate wide range signal generator covering 120 kc/s-260 Mc/s on 6 bands. Directly calibrated variable R.F. attenuator. Operation 200/240V a.c. Brand new with instructions. £15. P. & P. 374p. S.A.E. for details.

TE22 SINE SQUARE WAVE AUDIO GENERATORS

Sine: 20kc/s to 200 kc/s on 4 bands. Square: 20kc/s to 30 kc/s. Output impedance 3,000 ohms. 200/250V. A.C. Supplied brand new and guaranteed with instructions manual and leads. £16-50. Carr. 374p.

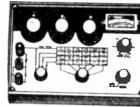TRANSISTORISED L.C.R. A.C. MEASURING BRIDGE



A new portable bridge offering excellent range and accuracy at low cost. Ranges: R. 1Ω-11.1 megΩ. G. Ranges ±1%. L. 1µH ±1.1 HENRY'S 6 Ranges -2%. C. 10pF ±1110mF d. 6 Ranges ±2%. TURNS RATIO 1:1/1000-1:1100. 6 Ranges ±1%. Bridge voltage at 1,000 cps. Operated from 9 volts. 100µA. Meter indication. Attractive 2 tone metal case. Size 7 1/2 x 5 x 2in. £20. P. & P. 25p.

TE-16A Transistorised Signal Generator, 5 ranges 400 kHz-30 MHz. An inexpensive instrument for the handyman. Operates on 9V battery. Wide, easy to read scale. 800 kHz modulation. 5 1/2 x 5 1/2 x 3 1/2. Complete with instructions and leads. £7-97. P. & P. 20p.



LAFAYETTE TE46 RESISTANCE CAPACITY ANALYSER

2pF-2,000 mfd 2 ohms-200 megohms. Also checks impedance, turns ratio, insulation. 200/250V a.c. Brand New £17-50. Carr. 374p.



RUSSIAN 22 RANGE MULTIMETER

Model U437 20,000 o.p.v. A first class versatile instrument manufactured in U.S.S.R. to the highest standards. Ranges: 2.5/10/50/250/500/1000V d.c., 2.5/10/50/250/500/1000V a.c. D.C. current 100 mA/1/10/100mA/1A. Resistance 300 ohms/30/300kΩ/3MΩ. Complete with batteries, test leads, instructions and sturdy steel carrying case. OUB PRICE £5-97 P. & P. 25p



TE11 DECADE RESISTANCE ATTENUATOR

Variable range 0-11dB. Connections. Unbalanced T and Bridge T. Impedance 600Ω range (0-1dB x 10) + (1dB x 10) + 10 + 20 + 30 + 40dB. Frequency: d.c. to 200kHz (-3dB). Accuracy: ±0.5dB. 4-indication ±0.1. Maximum input less than 4W (50V). Built in 600Ω load resistance with internal/external switch. Brand new £27-50. P. & P. 25p.



ROUND SCALE TYPE PENCIL TESTER MODEL TS.68


Completely portable, simple to use pocket sized tester. Ranges 0/3/30/300V a.c. and d.c. at 2,000 o.p.v. Resistance 0-20kΩ. ONLY £1-97. P. & P. 13p.



UR-1A SOLID STATE 4 BANDS RECEIVER
4 Bands covering 35kHz-30MHz. FET, 4 Meter, Variable BFO for SSB. Built in Speaker, Bandspread, Sensitivity Control. 220/240V a.c. or 12V d.c. 12in x 4 1/2in x 7in. Brand new with instructions. £25. Carr. 374p.



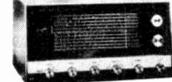UNR-30 RECEIVER
4 Bands covering 550kHz-30MHz. B.F.O. Built in Speaker 220/240V a.c. Brand new with instructions. £16-75. Carr. 374p.



LAFAYETTE HA-600 RECEIVER

General coverage 150-400kHz, 550kHz-30MHz. FET front end, 2 mech. filters, product detector, variable B.F.O., noise limiter, S Meter, Bandspread, RF Gain. 15in x 9 1/2in x 8 1/2in. 18B. 220/240V a.c. or 12V d.c. Brand new with instructions £45. Carr. 50p.

CRYSTAL CALIBRATORS No. 10

Small portable crystal controlled wavemeter. Size 7" x 7" x 4". Frequency range 500 Kc/s. 10 Mc/s (up to 30 Mc/s on harmonics). Calibrated dial. Power requirements 300 V.D.C. 15mA and 12 V.D.C. 0.3A. Excellent condition. £3-474. Carr. 374p.



B.C. 221 FREQUENCY METERS
latest release 125kHz to 20MHz. Excellent condition. Fully tested and checked and complete with calibrator charts. £27-50 each. Carr. 50p.

SOLID STATE VARIABLE A.C. VOLTAGE REGULATORS

Compact and panel mounting. Ideal for control of lamps, drills, electrical appliances, etc. Input 230/240V a.c. Output continuously variable from 20V to 230V. Model MR2305 5A 68 x 46 x 43mm, £8-374. Model MR2310 10A 90 x 68 x 43mm, £11-974. Postage 124p.

AUTO TRANSFORMERS
0/115/230V. Step up or step down. Fully shrouded.
150W. £2-374. P. & P. 174p.
300W. £3-25. P. & P. 224p.
500W. £4-974. P. & P. 324p.
1,000W. £7-25. P. & P. 374p.
1,500W. £8-974. P. & P. 424p.
5,000W. £38-90. P. & P. £1.

Completely portable, simple to use pocket sized tester. Ranges 0/3/30/300V a.c. and d.c. at 2,000 o.p.v. Resistance 0-20kΩ. ONLY £1-97. P. & P. 13p.

POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range ex-stock. Single hole fixing, tin. dia. shafts. Bulk quantities available.
25 WATT. 10/25/50/100/250/500/1,000/1,500/2,500 or 5,000 ohms. 724p. P. & P. 74p.
50 WATT. 10/25/50/100/250/500/1,000/1,500 or 5,000 ohms. £1-05. P. & P. 74p.
100 WATT. 1/5/10/25/50/100/250/500/1,000 or 2,500 ohms. £1-374. P. & P. 74p.

"YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS

Excellent quality - Low price - Immediate delivery

S-260 General Purpose Bench Mounting		S-260B Panel Mounting	
1A	£5-50	1A	£5-50
2.5A	£6-75	2.5A	£6-624
5A	£9-75	Please add postage	
8A	£14-50		
10A	£18-50		
12A	£21-00		
20A	£37-00		



G.W.SMITH & CO. (RADIO) LTD

27 TOTTENHAM CT. RD. LONDON, W1 Tel: 01-636 3715
3 LISLE STREET, LONDON, W.C.2 Tel: 01-437 8204
34 LISLE STREET, LONDON, W.C.2 Tel: 01-437 9155
311 EDGWARE ROAD, LONDON, W.2 Tel: 01-262 0387
OPEN 9-6 MONDAY TO SATURDAY

All Mail Orders to -
11-12, Paddington Green,
London W.2
Tel: 01-262 0562
(Trade supplied)

Now! A FAST EASY WAY TO LEARN BASIC RADIO & ELECTRONICS



Build as you learn with the exciting new **TECHNATRON** Outfit! No mathematics. No soldering—you learn the practical way.

Learn basic Radio and Electronics at home—the fast, modern way. Give yourself essential technical "know-how"—like reading circuits, assembling standard components, experimenting, building—quickly and without effort, and enjoy every moment. B.I.E.T.'s Simplified Study Method and the remarkable **TECHNATRON** Self-Built Outfit take the mystery out of the subject, making learning easy and interesting.

Even if you don't know the first thing about Radio now, you'll build your own Radio set within a month or so!

... and what's more, you will understand exactly what you are doing. The **TECHNATRON** Outfit contains everything you need, from tools to transistors—even a versatile Multimeter which we teach you to use. All you need give is a little of your spare time and the surprisingly low fee, payable monthly if you wish. And the equipment remains yours, so you can use it again and again.

You LEARN—but it's as fascinating as a hobby.

Among many other interesting experiments, the Radio set you build—and it's a good one—is really a bonus. This is first and last a teaching course, but the training is as fascinating as any hobby and it could be the springboard for a career in Radio and Electronics.

A 14-year-old could understand and benefit from this Course—but it teaches the real thing. The easy to understand, practical projects—from a burglar-alarm to a sophisticated Radio set—help you master basic Radio and Electronics—even if you are a "non-technical" type. And, if you want to make it a career, B.I.E.T. has a fine range of Courses up to City and Guilds standards.

New Specialist Booklet

If you wish to make a career in Electronics, send for your FREE copy of "OPPORTUNITIES IN TELECOMMUNICATIONS / TV AND RADIO". This brand new booklet—just out—tells you all about **TECHNATRON** and B.I.E.T.'s full range of courses.



FREE

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept. B12, ALDERMASTON COURT, READING RG7 4PF

POST THIS COUPON FOR FREE BOOK

To B.I.E.T. Dept. B12, Aldermaston Court, Reading RG7 4PF
Please send books and full information — free and without obligation.



NAME AGE

ADDRESS

OCCUPATION

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY



for fast, easy, reliable soldering

Contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux required.

SAVBIT ALLOY ALSO REDUCES COPPER BIT WEAR.

Economically packed for general electrical and electronic soldering. 75 ft. 18 gauge on plastic reel. Recommended retail price 75p
Size 12



THIN GAUGE SOLDER, ESSENTIAL FOR

soldering small components and thin wires. High tin content, low melting point, 60/40 alloy, 170 ft. 22 gauge on plastic reel. Recommended retail price 75p
Size 10



A RANGE OF SOLDERS IN HANDY DISPENSERS.

REF. ALLOY SWG

19A 60/40 18 18p *

Size 5 (Illustrated) Savbit 18 18p *

15 60/40 22 22p *

*Recommended Price



INVALUABLE FOR STRIPPING FLEX, THE NEW AUTOMATIC OPENING BIB WIRE STRIPPER AND CUTTER,

adjustable for all standard diameters. Plastic covered handles can also be used as wire cutter. Recommended retail price 50p



From Electrical and Hardware shops. If unobtainable, write to: **Multicore Solders Ltd., Hemel Hempstead, Herts.**

INTERCOMS

OUTSTANDING VALUE

ONLY £2.95

P. & P. 25p INC. BATTERY, 65ft LEAD, etc.



Superb quality two way transistorised intercom. Call, talk, listen. Amazingly sensitive—will amplify the quietest whisper. Hundreds of uses—baby alarm, invalids, home, office, shop, workshop, playroom, etc. Absolutely complete, ready to use. One of the best intercoms, at a remarkably low price. Ideal gift!!

- Also available—all complete as above with battery, leads, etc.—
- 3 STATION intercom (1 master 2 subs) £5.55 (P. & P. 35p)
- 4 STATION intercom (1 master 3 subs) £6.65 (P. & P. 40p)
- TELEPHONE AMPLIFIER with suction pickup. £2.95 (P. & P. 20p)
- EASIPHONE two way telephone amplifier. Just place receiver onto Easiphone—it switches on automatically—for a "no hands" conversation. Modern styling, quality construction. ONLY .. £7.55 (P. & P. 30p)

EAGLE

PRODUCTS —the name you can trust
SUPERB VALUE AT OUR DISCOUNT PRICES

HIGH QUALITY MICROPHONES

CO.92 .. £10.25	DM.82 .. £2.49
CO.96 .. £12.54	DM.94 .. £7.88
DM.16HL .. £6.07	DM.614 .. £2.13
DM.18HL .. £7.08	UD.50HL .. £7.49
DM.31C .. £7.08	UD.53S .. £11.16
DM.34C .. £6.07	UD.76HL .. £17.18
DM.58HL .. £9.47	200C .. £2.41
DM.73 .. £5.63	300C .. £2.22

STEREO HEADPHONES

SE.1 .. £4.38	SE.40 .. £5.28
SE.5 .. £2.62	SE.60 .. £7.57
SE.21 .. £8.97	SE.80 .. £13.34
SE.28 .. £9.88	SE.100 .. £14.27
SE.30 .. £6.53	

INTERCOMS

IN.2 .. £3.10	IN.505 .. £14.05
IN.302 .. £7.99	IN.500 .. £7.99
IN.404 .. £11.38	WI.2 .. £14.48

C.W.O. Please. Post, Packing and Insurance. 25p on all Eagle Products. (Mail Order only at present).

DORSET ELECTRONICS (PE)

Bransgore, Christchurch, Hants BH23 8AQ

TRANSISTOR RADIOS TO BUILD YOURSELF


Backed by after sales service

NEW! roamer eight mk 1 WITH VARIABLE TONE CONTROL

7 Tunable Wavebands: Medium Wave 1, Medium Wave 2, Long Wave, S.W.1, S.W.2, S.W.3, and Trawler Band. Built-in ferrite rod aerial for Medium and Long Waves. 4 section 24in. retractable chrome plated telescopic aerial for Short Waves for maximum performance. Push-pull output using 600mW type transistors. Socket for car aerial. Tape record socket. Selectivity switch. Switched earpiece socket complete with earpiece for private listening. 8 transistors plus 3 diodes. Famous make 7 x 4in speaker. Air spaced ganged tuning condenser. On/off switch volume control. Wave change switch and tuning control. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in approx. Easy to follow instructions and diagrams make the Roamer Eight a pleasure to build. Parts price list and easy build plans 25p (FREE with parts).

Total building costs **£6-98**
Post, packing and insurance 41p

Overseas
P. & P.
90p

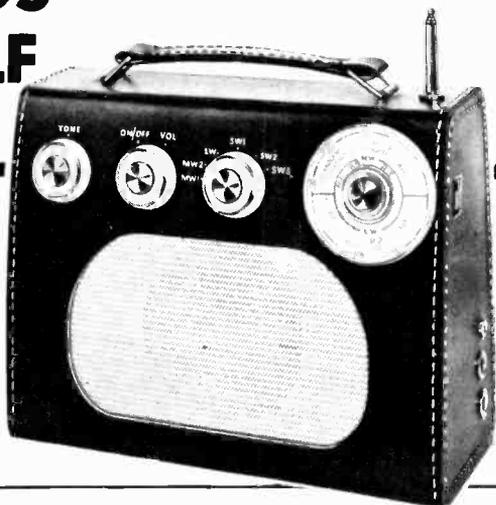

roamer seven mk IV

7 FULLY TUNABLE WAVEBANDS—M.W.1, M.W.2, L.W., S.W.1, S.W.2, S.W.3 and Trawler Band. Extra Medium waveband provides easier tuning of Radio Luxembourg, etc. Built in ferrite rod aerial for Medium and Long Waves. Retractable 4 section 24in chrome plated telescopic aerial for peak Short Wave listening. Socket for Car Aerial. Powerful push-pull output. 7 transistors and two diodes including Micro-Alloy R.F. Transistors. Famous make 7 x 4in P.M. speaker. Air spaced ganged tuning condenser. Volume/on/off control, wave change switches and tuning control. Attractive case with carrying handle. Size 9 x 7 x 4in approx. Easy to follow instructions and diagrams make the Roamer 7 a pleasure to build. Parts price list and easy build plans 15p (FREE with parts).



Total building costs
£5-98


Personal Earpiece with plug and switched socket for private listening, 30p extra.

Post, packing and insurance 41p
Overseas P. & P. 90p

NEW!

transeight SIX WAVEBAND PORTABLE WITH 3in. SPEAKER

Attractive case in black with red grille and black knobs and dial with spun brass inserts. Size 9 x 5 1/2 x 2 1/2 in. approx. Tunable on Medium and Long Waves, 3 Short Waves and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 8 improved type transistors plus 3 diodes. Push-pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 25p (FREE with parts).

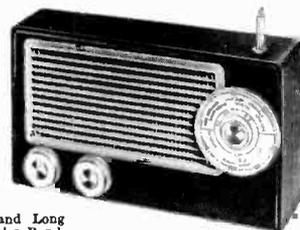

Total building costs
£4-48


Earpiece with plug and switched socket for private listening, 30p extra.

Post, packing and insurance 31p
Overseas P. & P. 70p

pocket five

MEDIUM WAVE, LONG WAVE AND TRAWLER BAND PORTABLE WITH SPEAKER

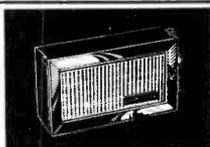Attractive black and gold case. Size 5 1/2 x 1 1/4 x 3 1/2 in. Tunable over both Medium and Long Waves with extended M.W. band for easier tuning of Luxembourg, etc. 7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker. Easy build plans and parts price list 8p (FREE with parts). Earpiece with plug and switched socket for private listening, 30p extra.



Total building costs
£2-23 Post,
packing
and insurance 21p
Overseas P. & P. 55p

transona five NOW WITH 3" SPEAKER

MEDIUM WAVE, LONG WAVE AND TRAWLER BAND PORTABLE

Attractive case with red speaker grille. Size 6 1/2 x 4 1/2 in x 1 1/2 in. 7 stages—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser, volume control, fine tone moving coil speaker. Easy build plans and parts price list 8p (FREE with parts). Earpiece with plug and switched socket for private listening, 30p extra.




Total building costs
£2-50 Post,
packing
and insurance 22p
Overseas P. & P. 55p

IMPROVED MODEL !

roamer six SIX WAVEBAND PORTABLE WITH 3in. SPEAKER

Attractive black case with red grille and black knobs and dial with spun brass inserts. Size 9 x 5 1/2 x 2 1/2 in. approx. Tunable on Medium and Long Waves, two Short Waves, Trawler Band plus an extra M.W. band for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and latest telescopic aerial for Short Waves. Improved circuit. 8 stages—6 transistors and 2 diodes including Micro-Alloy R.F. Transistors, etc. Easy build plans and parts price list 10p (FREE with parts). Earpiece with plug and switched socket for private listening, 30p extra.

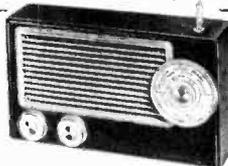

Total building costs
£3-98 Post,
packing
and insurance 26p
Overseas P. & P. 70p

RADIO EXCHANGE LTD

61a, HIGH STREET, BEDFORD. Tel. 0234 52367

I enclose £..... please send items marked

ROAMER EIGHT	<input type="checkbox"/>	ROAMER SEVEN	<input type="checkbox"/>
TRANSEIGHT	<input type="checkbox"/>	POCKET FIVE	<input type="checkbox"/>
TRANSONA FIVE	<input type="checkbox"/>	ROAMER SIX	<input type="checkbox"/>

Parts price list and plans for.....

Name.....

Address.....

* Calls side entrance Barratts Shoe Shop

* Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

PE 33

28watts, r.m.s. 40Hz to 40kHz ± 3 dB

There are two stereo amplifiers — the RT100 for ceramic cartridges, the RT101 for magnetic. Both incorporate FETs (FIELD EFFECT TRANSISTORS), just like top-priced units. FETs give you more of the signal you want, and almost none of the background hiss you don't. Both units have a jack socket to plug in headphones and there's a separate output for tape recorder. Filters (an unusual feature in this price range) and tone controls give a wide range of bass and treble adjustment which compensate for input deficiencies and domestic acoustic conditions.



Viscount III Audio Suite complete **£49**

PRICES SYSTEM 1

Viscount III RT101 amplifier £22.00 + 90p p&p
 2 x Duo Type II speakers, £14.00 + £2 p&p
 Garrard SP25 Mk. III with
 MAG. cartridge, plinth
 and cover £23.00 + £1 p&p
Total £59.00

Available complete for only **£52.00 + £3.50 p&p.**

SPECIFICATION

14 watts per channel into 3 to 4 ohms. Total distortion @ 10W @ 1kHz 0.1%, P.U.1 (for ceramic cartridges) 150mV into 3 Meg. P.U.2 (for magnetic cartridges) 4mV @ 1kHz into 47K equalised within ± 1 dB R.I.A.A. Radio 150mV into 220K. (Sensitivities given at full power.) Tape out facilities; headphone socket, power out 250 mV per channel. Tone controls and filter characteristics: Bass +12 dB to -17 dB @ 60 Hz. Bass filter: 6 dB per octave cut. Treble control: treble +12 dB to -12 dB @ 15 kHz. Treble filter: 12 dB per octave. Signal to noise ratio: (all controls at max) RT101 - P.U.1 and radio -65 dB. P.U.2 - 58 dB. RT100 same as RT101 but P.U.2 (for crystal cartridges) 450 mV into 3 Meg. Cross talk better than -35 dB on all inputs. Overload characteristics 26 dB on all inputs. Size 13½" x 9" x 3½"

SYSTEM 2

As System 1, but with 2 x Duo Type III speakers at pair £32.00 + £3 p&p
Available complete for £69 + £4 p&p

SYSTEM 3

Viscount III Amplifier RT100 £17.00 + 90p p&p
 2 x Duo Type II speakers, pair £14.00 + £2 p&p
 Garrard SP25 Mk. III with CER. diamond
 cartridge, plinth and cover £21.00 + £1 p&p
Total £52.00

Available complete for only **£49.00 + £3.50 p&p**

SPEAKERS Duo Type II

Size 17" x 10½" x 6½". Drive unit 13" x 8" with parasitic tweeter. Max. power 10 watts. 3 ohms
 Teak veneer cabinet. £14 pair + £2 p&p.
 Duo Type III Size 23½" x 11½" x 9½". Drive unit 13½" x 8½" with H.F. speaker. Max. power 20 watts at 3 ohms. Frequency range 20Hz to 20kHz.
 Teak veneer cabinet. £32 pair + £3 p&p.

Radio and TV Components (Acton) Ltd, 21d High Street., Acton, London, W3 6NG
 323 Edgware Road, London, W.2. Mail orders to Acton. Terms C.W.O. All enquiries S.A.E.
 Goods not dispatched outside U.K.

R+TV

XCELITE

Precision made hand tools
for the professional



PLIERS

69CG Radio-TV Pliers
70CG Flat Nose Pliers
71CG Round Nose Pliers

72CG Chain Nose Pliers
73CG Tip Cutting Pliers
74CG Diagonal Close Cutting Pliers

A complete range of miniature lightweight pliers specially designed for holding, bending, shaping and cutting of fine wires in electronic, Radio/T.V., electrical and jewellery work. Precision made for the expert with miniatures in mind. Cushion grip handle, coil spring openers.



SEIZERS

32H 5" Straight Nose Junior 5" Seizer
33H 5" Curved Nose Junior 5" Seizer

42H 6" Straight Nose Seizer
43H 6" Curved Nose Seizer

Box joint construction, two position snap on lock. Precision machined from perfectly tempered stainless steel. Holds like surgical clamp and acts as heat sink. Straight or curved nose, in 5" and 6" sizes.

Distributed by

Special Products Distributors Limited
81 Piccadilly, London, W.1

Tel. 01-629 9556

Cables: SPECIPROD, London, W.1

Full details on request

Made in U.S.A.

JERMYN 50p BARGAIN PACKS

All fully coded, all from well-known manufacturers and now available, while stocks last, at better than bulk-buyer's prices! Cash with order only.

THIS MONTH:

1N4148	Signal Diode (= 1N914)	18 for 50p
1N5060	1 Amp Rectifier 400V (= A14D) avalanche protected	7 for 50p
2N2926	NPN Silicon Transistor (Red) hfe 55-110	8 for 50p
2N2923	NPN Silicon Transistor hfe 90-180	7 for 50p
2N2646	Versatile Unijunction	3 for 100p

Post and packing 10p for 1 or 2 packs;
3 packs or more post free.

Order and quantity, till sold (but we regret packs cannot be subdivided).



P.O. or Cheque payable Jermyn Industries,
Vestry Estate, Sevenoaks, Kent.

TOURIST

MARK 3
CAR RADIO

ALL TRANSISTOR

Beautifully designed to blend with the interiors of all cars. Permeability tuning and long wave loading coils ensure excellent tracking, sensitivity and selectivity on both wave bands. R.F. sensitivity at 1MHz is better than 8 micro volts. Power output into 3 ohm speaker is 3 watts. Pre-aligned I.F. module and tuner together with comprehensive instructions guarantees success first time. 12 volts negative or positive earth. Size 7in x 2in x 4 1/2in deep.



Circuit diagram 13p, free with parts. Speaker, baffle and fixing kit £1.25 extra plus P. & P. 25p

SET OF PARTS

£6.30 Plus P. & P. 50p

Speaker postage free when ordered with parts

SOUND 50

50 WATT AMPLIFIER & SPEAKER SYSTEM



Output Power: 45 watts R.M.S. (Sine wave drive).
Frequency response: -3dB points 30Hz at 18KHz. Total distortion: less than 2% at rated output. Signal to noise ratio: better than 60dB.
Speaker Impedance: 3, 8 or 15 ohms. Bass Control Range: ±13dB at 60Hz. Treble Control Range: ±12dB at 10KHz.
Inputs: 4 inputs at 5mV into 470K. Each pair of inputs controlled by separate volume control. 2 inputs at 200mV into 470K.

To protect the output valves, the incorporated fail safe circuit will enable the amplifier to be used at half power.

SPEAKERS! Size 20in x 20in x 10in incorporating 12in heavy duty 25 watt high flux, quality loudspeaker with cast frame. Cabinets attractively finished in two tone colour scheme—Black and grey.

COMPLETE SYSTEM £50 Plus P. & P. or available separately
Amplifier: £28.50 plus £1.50 P. & P.
Speaker: £12.50 each plus £2.25 P. & P.

ELEGANT SEVEN Mk. III (350mW Output)



7-transistor fully tunable M.W.-L.W. Superhet portable. Set of parts. Complete with all components, including ready etched and drilled printed circuit board —back printed for foolproof construction. MAINS POWER PACK KIT: 75p extra.

£5.25 Plus P. & P. 50p. Circuit 13p Free with parts.


THE DORSET (600mW Output)

7-transistor fully tunable M.W.-L.W. Superhet portable. Set of parts. The latest modulated and pre-alignment techniques makes this simple to build. Sizes: 12in x 8in x 3in.

£5.25 Plus P. & P. 50p. Circuit 13p. Free with parts.



CONTINENTAL 4-TRACK, 3-SPEED TAPE DECK

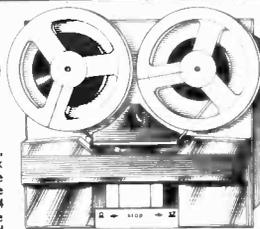

R.C. 74 tape deck. Three speeds—7 1/2, 3 1/2 and 1 1/2 i.p.s. 4-track record/playback head. Plus 4-track erase head. Positive pressure pad system. Takes any tape spool up to and including 7in. The R.C. 74 is driven by a powerful 200/250V 50-cycle a.c. motor. A heavy, accurately balanced flywheel brings wow and flutter levels down to approx. 0.3% total at 3 1/2 and 7 1/2 i.p.s. Fast rewind in both directions. Controls couldn't be simpler! Just five push buttons that interlock to cut out accidental tape damage. Efficient servo-action type braking. Easy drop-in tape loading.

The R.C. 74 comes with an attractive moulded deck cover, which has positions for tone and volume controls. The unit is built into a rigid die-cast frame, and overall size of the whole unit is 12 1/2 x 11 1/2 x 6in. Every single deck fully tested before dispatch. Spools not supplied. Price complete £15. Plus 75p P. & P.

R+TV RADIO & TV COMPONENTS (ACTON) LIMITED

See opposite page for addresses

RST

VALVE MAIL ORDER CO.
BLACKWOOD HALL
16A WELLFIELD ROAD, LONDON SW16 2BS
SPECIAL EXPRESS MAIL ORDER SERVICE
 Express postage 1p per transistor, over ten post free

Sp	Sp	Sp	Sp	Sp	Sp
IN21	0-18	AC127	0-25	BF173	0-30
IN23	0-20	AC128	0-25	BF181	0-38
IN85	0-88	AC187	0-30	BF184	0-25
IN253	0-50	AC188	0-30	BF185	0-25
IN256	0-50	ACY17	0-30	BF194	0-18
IN645	0-25	ACY18	0-25	BF195	0-16
IN725A	0-20	ACY19	0-25	BF196	0-28
IN914	0-06	ACY20	0-25	BF197	0-25
IN4007	0-23	ACY21	0-25	BF861	0-28
19021	0-20	ACY22	0-18	BF898	0-28
18113	0-15	ACY27	0-25	BFX12	0-28
18130	0-13	ACY28	0-18	BFX13	0-25
18131	0-13	ACY39	0-55	BFX29	0-30
18202	0-23	ACY40	0-15	BFX30	0-33
28240	1-99	ACY41	0-25	BFX31	0-28
28301	0-20	ACY44	0-38	BFX63	0-50
28302	0-23	AD140	0-50	BFX84	0-30
28306	0-30	AD149	0-50	BFX85	0-40
28371	0-23	AD161	0-38	BFX86	0-38
28381	0-25	AD162	0-38	BFX87	0-38
28414	0-30	AF106	0-30	BFX88	0-25
28417	0-25	AF114	0-25	BFY10	1-00
28214	0-43	AF115	0-30	BFY11	1-25
28247	0-25	AF116	0-33	BFY17	0-25
28250	0-50	AF117	0-25	BFY18	0-25
28404	0-23	AF118	0-38	BFY19	0-25
28697	0-18	AF119	0-20	BFY24	0-46
28698	0-43	AF124	0-25	BFY41	1-00
28706	0-25	AF125	0-18	BFY50	1-05
28706A	0-13	AF126	0-18	BFY51	0-20
28708	0-16	AF127	0-18	BFY52	0-28
28709	0-63	AF139	0-30	BFY53	0-18
28711	0-38	AF178	0-48	BFY64	0-43
28987	0-53	AF179	0-48	BFY90	0-68
281090	0-30	AF180	0-30	BFY92A	0-50
281091	0-33	AF181	0-43	BX860	0-85
281131	0-30	AF186	0-40	BX876	0-15
281132	0-30	AFY19	1-18	BSY26	0-18
281302	0-20	AFZ11	0-63	BSY27	0-20
281303	0-28	AFZ12	0-75	BSY51	0-50
281304	0-25	AFZ26	0-25	BSY93A	0-15
281305	0-25	AFY27	0-33	BSY95	0-15
281306	0-25	AFY28	0-25	BT102/500R	0-75
281307	0-25	AFY29	0-30	OA70	0-10
281308	0-30	AFY36	0-25	OA71	0-10
281309	0-28	AFY50	0-18	BT Y79/100R	0-75
281420	0-98	AFY51	0-40	BT Y79/400R	0-75
281507	0-28	AFY53	0-20	OA79	0-10
281508	0-28	AFY54	0-20	OA81	0-10
281909	0-25	AFY62	0-25	OA85	0-13
282147	0-75	AFY86	0-33	OA86	0-12
282148	0-60	ASZ21	0-43	OA90	0-10
282160	0-63	ASZ23	0-75	OA91	0-08
282218	0-30	AC Y30	0-88	OA95	0-08
282219	0-38	AC Y31	0-50	OA99	0-06
282297	0-03	BC107	0-13	BY210	0-40
282297	0-30	BC108	0-13	BY211	0-35
282369A	0-20	BC109	0-18	BY212	0-30
282613	0-28	BC113	0-25	BY213	0-25
282646	0-53	BC115	0-33	BY215	1-00
282712	0-25	BC116	0-40	BY215	0-63
282784	0-50	BC116A	0-38	BY216	0-13
282846	0-25	BC118	0-30	BY288CV3	0-18
282848	0-43	BC121	0-20	CI11	0-65
282904	0-30	BC122	0-20	CRS1/40	0-48
282904A	0-33	BC125	0-68	CS43	2-50
282906	0-30	BC126	0-65	CS410	0-13
282907	0-38	BC140	0-45	CS410	0-13
282924	0-23	BC147	0-18	DD000	0-15
282925	0-18	BC148	0-13	DD003	0-15
282926	0-13	BC149	0-20	DD006	0-18
283054	0-50	BC157	0-20	DD007	0-40
283055	0-75	BC158	0-20	DD008	0-38
283072	0-13	BC159	0-23	GD3	0-33
283073	0-13	BC160	0-23	GD4	0-30
283706	0-23	BC168	0-13	GD5	0-33
283707	0-16	BCY31	0-30	GD8	0-25
283709	0-13	BCY32	0-50	GD12	0-05
283710	0-13	BCY33	0-25	GET102	0-30
283819	0-35	BCY34	0-30	GET103	0-23
283820	0-88	BCY38	0-40	GET113	0-20
283823	0-75	BCY39	0-60	GET114	0-15
285027	0-53	BCY40	0-50	GET115	0-45
285088	0-33	BCY42	0-15	GET116	0-50
28605	1-00	BCY70	0-20	GET120	0-25
28591	0-50	BCY71	0-30	GET872	0-30
28594	0-75	BCY10	0-50	GET873	0-25
28501	0-38	GD211	0-40	GET880	0-33
28703	0-63	BD121	0-65	GET881	0-25
AA129	0-20	BD123	0-83	GET882	0-25
AA212	0-30	BD124	0-80	GET885	0-25
AA213	0-13	BDY11	1-63	GEX44	0-08
AC107	0-38	BF115	0-25	GEX43/1	0-08
AC126	0-25	BF167	0-25	GEX941	0-15
				GJ3M	0-25
				GJ4M	0-38
				GJ5M	0-25
				GJ7M	0-38
				HG1005	0-60
				HS100A	0-20
				MAT100	0-25
				MAT101	0-30
				MAT121	0-80
				MAT122	0-25
				MAT123	0-25
				MAT124	0-25
				MAT125	0-25
				MAT126	0-25
				MAT127	0-25
				MAT128	0-25
				MAT129	0-30
				MAT131	0-30
				MAT133	0-25
				MAT134	0-25
				MAT135	0-25
				MAT280	0-25

Send for Heathkit – and send for the best

The best in hi-fi; the best in short-wave;
the best in domestic, marine and auto equipment;
the best in everything electronic.



Heathkit comes direct from the world's leading suppliers of top-quality electronic equipment. You assemble your components using the unique Heathkit 'step-and-check' method and there's a team of experts ready to help and advise you on any problem. But you won't need them. Hardly anyone does!

Send for your FREE catalogue – NOW.

Practical Electronics September 1971

Please send me details of your complete range of kits.

Name

Address

Heath (Gloucester) Limited,
Gloucester, GL2 6EE.
A Schenker Company
PE09

3 WAYS

HOME RADIO (Components) Ltd.
Dept. PE, 234-240 London Road,
Mitcham CR4 3HD. 01-648 8422

of obtaining components *quickly & easily*

1 CALL AT No. 240 London Rd., Mitcham

If you live within easy reach of Mitcham or are in the area at any time do call on us. We are almost opposite Mitcham Baths. We open 9 a.m. every weekday. On Wednesdays we close 1 p.m. and all other days, including Saturdays, 5.30 p.m. On Saturdays we have extra staff to deal with queries. We carry a vast stock of components, and 999 times out of a 1,000 we can immediately lay our hands on the particular item required.

2 JOIN OUR CREDIT ACCOUNT SERVICE

We began our Credit Account Service about 18 months ago and it has proved extremely popular. Little wonder! Our customers find it a very simple and convenient way of purchasing all their radio and electronic needs. We supply pre-paid envelopes and order forms and no matter how many orders you send us you make only one payment per month. There are several other advantages with our Credit Account Service. Please write or phone for details.

The price of 70p applies only to catalogues purchased by customers in the U.K. and to BFPO addresses.

3 and ORDER BY MAIL OR TELEPHONE

Although we are kept busy selling "over the counter" we supply even more by Mail Order. You can telephone any time of day or night, Sundays included. If you ring out of office hours a recording machine takes your message for us to deal with as soon as we open shop again. Our number is 01-648 8422. If you wish to order by post our address is in the panel at the top of the page. We deal with all orders promptly.

WHICHEVER WAY YOU CHOOSE you need the Home Radio Catalogue

In its 315 pages are listed over 8,000 components, over 1,500 of them illustrated. Each copy contains 10 vouchers, each worth 5p when used as instructed. Free Supplements are supplied regularly to keep you up-to-date. The Catalogue costs 50p over the counter, or 70p including postage and packing.



Post this Coupon with
Cheque or P.O. for 70p

Please write your Name and Address in block capitals

Name.....

Address.....



HOME RADIO (Components) LTD.
Dept. PE, 234-240 London Road, Mitcham CR4 3HD

Editor F. E. BENNETT Assistant Editor M. A. COLWELL Editorial Assistants D. BARRINGTON G. GODBOLD M. KENWARD
Art Editor J. D. POUNTNEY Technical Illustrators J. A. HADLEY P. A. LOATES
Advertisement Manager D. W. B. TILLEARD

ON THE ROAD

THE motor car is a wonderful vehicle for electronics. Solid state technology never had a happier hunting ground. Consider that reliable easy-to-tap d.c. supply at 12 volts: just what the transistor ordered. No wonder so many interesting and useful aids for the motorist have appeared in recent times. Many owe their origin to private electronics enthusiasts, their imagination stirred to new heights during long solo drives, no doubt; or, perhaps, during enforced idling caused by holiday season snarl-ups.

The majority of such devices represent electronics in a comparatively simple form. Whether as self-sufficient gadgets or systems, or as ancillary units for coupling to standard car accessories for control purposes, their function is to aid the motorist rather than his vehicle. Useful as they are, such appendages do not represent the limit of electronics involvement in motor cars. This is far from the case. Electronics is destined to become a vital and intrinsic part of the vehicle itself.

The increasing concern over road safety and environmental matters like atmosphere pollution, will bring about more stringent regulations. In order to meet these tough requirements the car manufacturers will have no alternative but to look beyond their own industry and traditional methods. They are already fairly familiar with the possibilities of electronics in the internal combustion engine field. For example, the advantages of electronic ignition and fuel injection have long been known. It is only the initial cost that deters car manufacturers from incorporating such systems in their mass produced models.

Coming now to more life-or-death matters, car designers in the future will have little option but to incorporate more refined and sensitive control systems. Present systems largely dependent upon electro-mechanical and hydraulic linkages will undergo drastic change, if not entire replacement, as electronic control systems are developed. Methods of preventing wheel slide by use of electronic sensing and computing techniques to control the brake have already been perfected. This is a foretaste of the future in motoring.

This revitalizing of the traditional vehicle is all to the good, though even the magic of electronics cannot save the internal combustion engine from ultimate extinction. Indeed, how far on the road towards fully automated driving will we have journeyed before the electric powered vehicle overtakes us? Commercial interests are very reticent about the current state of development in this exciting area, but there have been some ominous (or rather, welcome) rumblings from Detroit, of late. Perhaps the long awaited motoring revolution is nearer than we think.

F.E.B.

THIS MONTH

CONSTRUCTIONAL PROJECTS

BURST-FIRE POWER CONTROLLER	710
TIMER WITH DIGITAL READOUT	722
SEISMOGRAPH	736
WAR GAMES COMPUTER	748

SPECIAL SERIES

RADIO ASTRONOMY TECHNIQUES—4	730
------------------------------	-----

GENERAL FEATURES

MICROWAVE SEMICONDUCTORS	716
--------------------------	-----

NEWS AND COMMENT

EDITORIAL	709
BOOK REVIEWS	729
NEWS BRIEFS	746
MARKET PLACE	747
SPACEWATCH	757
READOUT	758

Our October issue will be published on Friday, September 17

© IPC Magazines Limited 1971. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press. Subscription Rates including postage for one year, to any part of the world, £2.65 (£2 13s. 0d).
Practical Electronics, Fleetway House, Farringdon St., London, E.C.4. Phone: Editorial 01-634 4452; Advertisements 01-634 4202

THE simple control of power has for a long time been desirable, but it was not until the introduction of thyristors, or silicon controlled rectifiers that such control became convenient in the home constructor field.

The unit to be described here is capable of controlling power levels of up to 1kW and makes use of the "burst fire" system to achieve this. Any attempt to control elements in excess of this rating will result in damage to the controller.

Although the handling of greater power levels might seem to be desirable, it should be borne in mind that most heaters of a greater power output have the facility of switching in and out 1kW at a time. Thus fine control of 1kW will cover most situations; larger power handling would call for a larger unit than that described here.

In order to understand the advantages of the burst-fire system and why it is used in this controller, a brief outline of the alternative method is given. There are, of course, advantages and disadvantages in both systems, as will be seen.

PHASE SHIFT CONTROL DISADVANTAGES

The simplest form of control of power, using a thyristor, is that known as "phase shift". Fig. 1 shows a typical waveform of load current controlled in this way, where switch-on is delayed in each half-cycle, so causing the power level, averaged over a number of cycles, to be less than when no delay is included. Variation of the length of the delay varies the average power level.

Controllers based on the phase-shift principle have been described previously in this magazine. While they are quite satisfactory in enabling the power level to be controlled, there are two disadvantages.

Since the current switch-on is sudden and is repeated at the rate of 50Hz, a large level of radio frequency is generated and careful screening and filtering are called for if interference to radio and television is to be avoided. Loads consisting of motors, such as electric drills, tend to give much lower levels of interference due to the inductance of the windings acting as a built-in filter. In general, the greater the power level being controlled, the greater level of interference generated.

Distortion of the mains supply also occurs as can be seen from Fig. 1, and large scale use of phase-shift control at high power levels—say greater than a few hundred watts—can give rise to difficulties. The Electrical Supply Authorities accordingly discourage the use of phase-shift control for space heaters.

BURST FIRE COMPARED

The burst-fire system causes very little or no interference, even without filtering, and no distortion of the supply voltage occurs. This is because complete half-cycles of current are permitted to flow to the load in controllable trains as in Fig. 2. Alteration of the ratio of "on" time to "off" time, while still maintaining complete half-cycles in the power supplied to the load, varies the average output power.

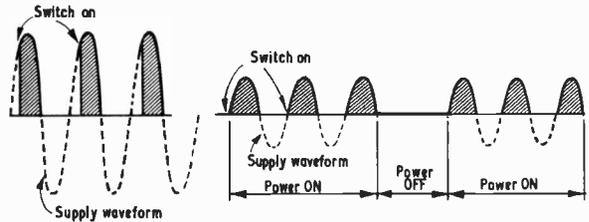


Fig. 1 (left). Phase shift control of thyristor load current. Power supplied can be varied by altering switch-on point

Fig. 2 (right). Current half cycles supplied to load with burst fire control. Note that switch-on occurs at zero point

CHOICE OF PULSE PERIODS

The actual lengths of time employed for "on" and "off" require choosing with care. Both periods should not be too short, for if, for example, the current period was to consist of two half-cycles, then only a slight change in component values, due to load or temperature changes, could alter this to either one or three half-cycles. This represents a large percentage change and smooth stable control would be impossible.

Conversely, too long a period of time in either the "on" or "off" mode would permit a heater element to alternately cool down and heat up. Continuous temperature cycling of this kind might give rise to a shorter life for the element. In any case, it is easily avoided, for with correct timing, the thermal inertia of the element overcomes this.

The unit described here has been arranged to have its output pulsed on and off once per second, that is "on" time plus "off" time is equal to about 1 second. As the ratio of "on" and "off" is varied, to effect a change in average power supplied, this time of 1 second remains virtually constant, due to the circuit configuration employed.

Control of power from 10 per cent to 90 per cent of full is possible; a by-pass switch (which may be omitted if desired) enables full power to be supplied when required.



— — — provides smooth power.

APPLICATIONS FOR THE BURST FIRE CONTROLLER

From the foregoing it will readily be seen that while the Burst Fire Controller is eminently suitable for control of heaters—such as electric fires, aquaria heaters and photographic processing bath heaters—it is not suitable for the dimming of lights, nor the slowing of motor speeds.

However, as was noted earlier, phase-shift control of electric motors is appropriate; the self suppression of interference in motors and the generally lower power levels present in lamp circuits avoid the difficulties mentioned in that system.

Uses for the Burst Fire Controller involving lamps is in those cases where flashing is required. Christmas tree and similar displays are examples; perhaps a cycling period of about 5 to 10 seconds would be more suitable and possible modifications will be given later.

Having thus outlined the need for burst fire control, we can now turn to practical details.

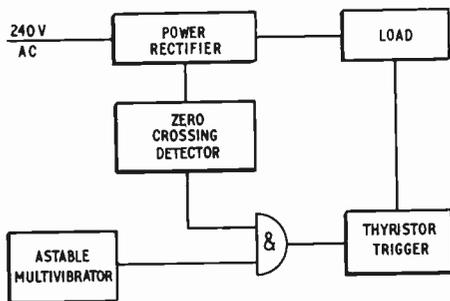


Fig. 3. Block diagram of controller

BLOCK DIAGRAM

In Fig. 3 is given the block diagram of the unit. Here the astable multivibrator has an almost constant frequency, but its on-off ratio can be altered. The output of the multivibrator, together with information from the zero crossing detector, is fed to the AND gate, the output of which turns on the thyristor, and so applies power to the load.

The incorporation of the AND gate in this way ensures that switch-on of the thyristor occurs only at the start of each mains half-cycle, so causing no high frequency radiation.

CIRCUIT ACTION

Full circuit details are given in Fig. 4. In the circuit diagram, transistors TR2 and TR3 form the astable multivibrator, which has two points of interest.

Potentiometer VR1 enables the on-off ratio of the multivibrator to be changed but with a constant repetition rate. This is because while varying amounts of resistance can be included between each base and the positive supply rail, the total amount of such resistance is constant, one base circuit having more resistance included as the other has less.

The inclusion of the diode D7 and resistor R9 to supply rail, isolates the timing capacitor C6 from the collector of TR3 so allowing the voltage at that collector to rise sharply when the transistor ceases to conduct. Consequently, a good square wave is available for passing to the AND gate comprising D8, D9 and R11.

ZERO CROSSING DETECTOR

The second input to the AND gate is derived from the zero crossing detector circuitry.

Inspection of the circuit will show that the upper side of C3 has D3 connected to negative rail; similarly, C4 has D1 connected to the positive rail. This means that the waveforms at the upper sides of C3 and C4 are 90 degrees out of phase with the waveform across D6, this acting as a positive clamp to the negative line and providing positive half-cycles, as shown in Fig. 5.

These provide positive switching of TR1, so giving positive signals, coinciding with zero mains crossing, at the emitter of TR1.

The capacitors C3 and C4 are connected to the mains, and so must withstand full mains potential. For this reason, 750 volts should be considered the minimum working voltage for these components, with 1,000 volt working desirable.

GATE CONTROL

The AND gate comprising D8 and D9 controls the switching of TR4. Suppose TR3, in one of its

--- **BURST-FIRE** ---

POWER CONTROLLER

control up to 1kW

By J. N. Watt

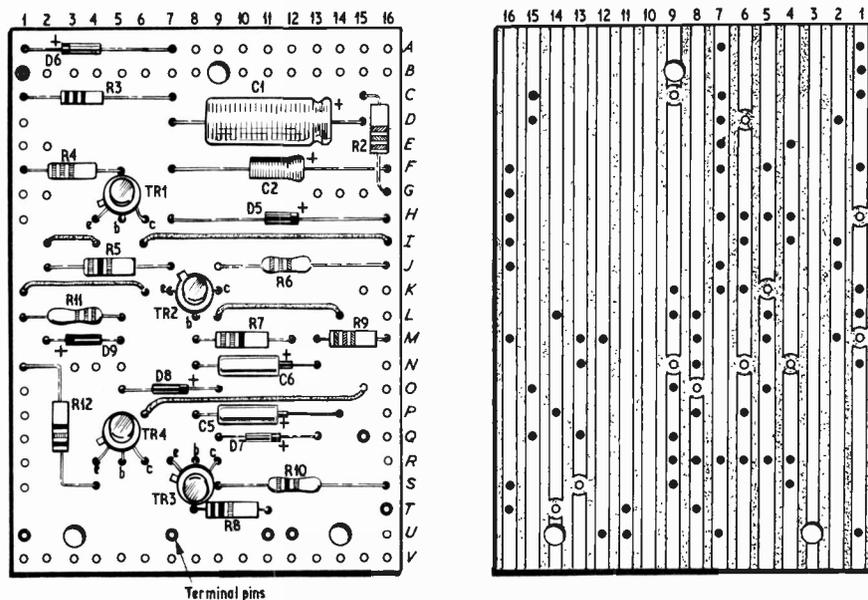


Fig. 7. Assembly and wiring layout of control board

BEWARE OF HIGH VOLTAGES

Practical construction raises some important safety points and it would be as well to mention them first.

All parts of the circuitry are at high voltage, due to direct connection to the mains and under no circumstances should any part be handled directly when live. Disconnect the unit from the mains supply by un-plugging it when making any adjustments or modifications to it.

Since most oscilloscopes are grounded via mains earth at one input terminal, it is essential that any waveform inspection is made through a 1 : 1 isolating transformer. Any direct oscilloscope connections will certainly result in considerable damage to the controller circuitry.

Where control of an electric fire is intended, avoid low mark-space ratio settings of VR1, since short period bursts of power are not sufficient to make a 1kW element glow. This could be dangerous to children with inquisitive fingers who might think the fire is off.

For insulation, the piece of Veroboard carrying most of the components in Fig. 7 is secured by means of 4B.A. nylon screws and nuts, with nylon nuts used as insulated spacers. The heat sinks themselves are earthed, although the components they carry are of course at high potential, with the appropriate insulation.

The need for care, when the cover of the box is removed and the unit is connected to the mains, cannot be too strongly emphasised. Of course, in normal use, no danger should arise.

A strong die-cast box is used to house the controller, and this should be earthed. Such boxes are readily available, easy to drill and, rather important in this case, provide good protection.

COMPONENTS . . .

Resistors

R1	15k Ω	6W wire wound	R7	47k Ω
R2	390 Ω	$\frac{1}{2}$ watt	R8	47k Ω
R3	68k Ω		R9	15k Ω
R4	2.2k Ω		R10	10k Ω
R5	2.2k Ω		R11	10k Ω
R6	10k Ω		R12	120 Ω

All 10% $\frac{1}{2}$ watt except where otherwise stated

Potentiometers

VR1 250k Ω carbon linear

Capacitors

C1 40 μ F elect. 16V
 C2 47 μ F elect. 6V
 C3, C4 1000pF 750V (2 off)
 C5, C6 2.2 μ F elect. 6V (2 off)

Transistors

TR1—TR4 BC107 (4 off)

Diodes

D1—D4 BYZ12 (4 off)
 D6—D9 IN914 (4 off)
 D5 5.6V 400mW Zener

Thyristor

SCR1 BTY79-400R

Switch

S1 D.P.D.T. 5A contact rating

Miscellaneous

LPI-Mains neon, heat sinks and insulating mica for rectifiers, nylon screws and nuts (4 B.A.). Eight way insulated tag strip, 13A mains socket, Die-cast box 7 $\frac{1}{2}$ in \times 4 $\frac{3}{4}$ in \times 2 $\frac{1}{2}$ in.

A high degree of polish can be imparted to the box by rubbing with successively finer grades of emery paper, followed by toothpaste (in lieu of jewellers' rouge) and then metal polish. Alternatively, a painted finish, obtained by making use of one of the many spray aerosols on the market, enables a choice of colour to be made.

MOUNTING THE RECTIFIERS

The four power rectifiers, D1 to D4, and the thyristor are mounted on heat sinks as shown in the wiring diagram of Fig. 8.

These sinks are earthed, and this can be done because mica washers, with insulating bushes, are employed on the diode and thyristor mounting studs as in Fig. 9.

Each of the sinks is painted matt black, to assist with heat dissipation, as are the inside surfaces of

the box. A light smear of silicon grease, if available, should be applied to the surfaces of the sinks that joint with the box.

When fitting the washers, ensure that no burrs are present that could puncture the mica insulation. After fixing, check that the mica washers are still insulating, with an ohmmeter.

FULL POWER SWITCHING

A mains voltage neon lamp across the load indicates when power is actually being applied to it, while the double pole change-over switch S1 enables full power to be applied direct to the load when required.

This switch must be capable of handling the full load current, and for this reason has a rating of 5A or greater.

When wiring up, remember that all leads passing load current can be called upon to carry 4A, so use

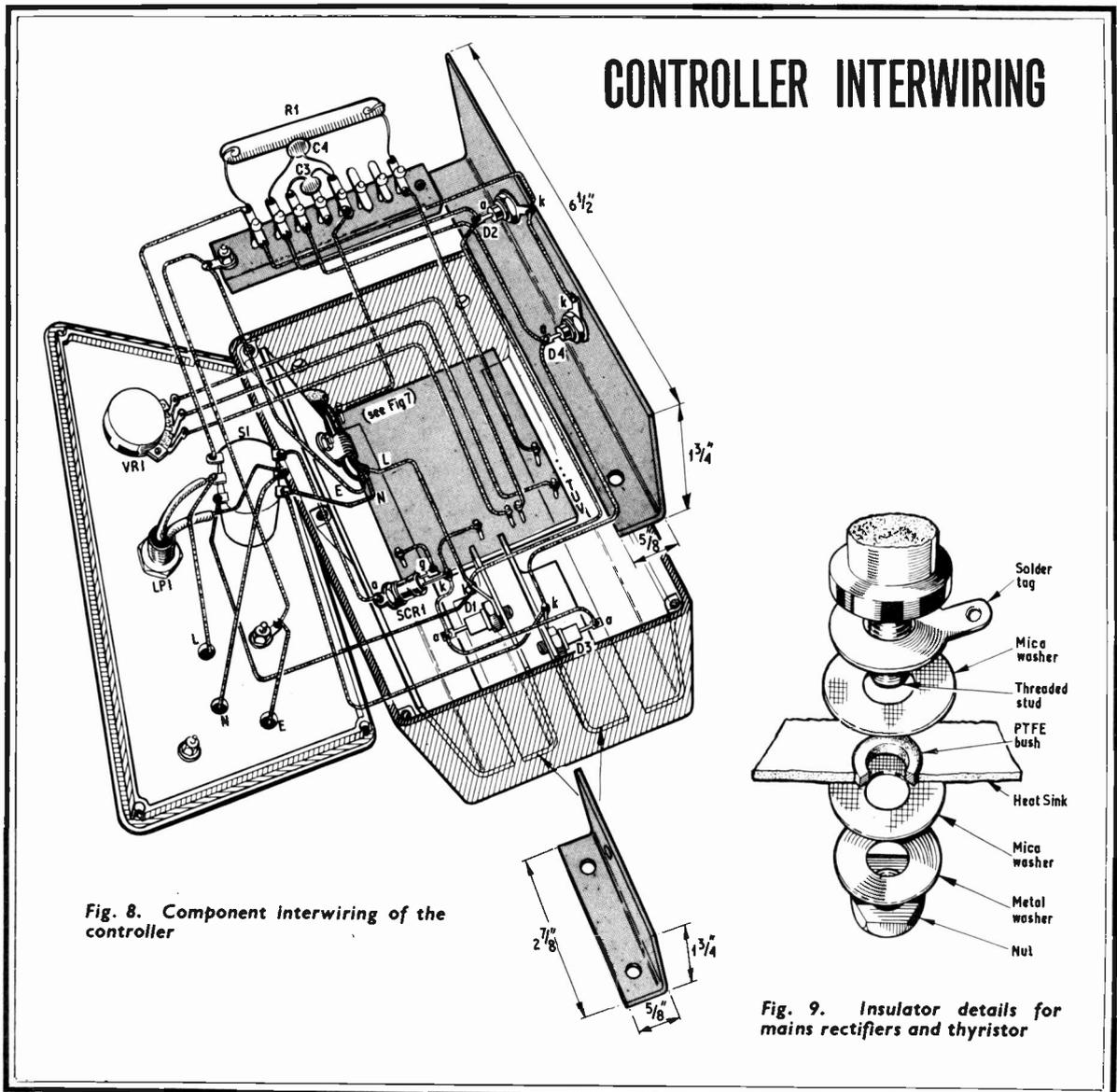


Fig. 8. Component interwiring of the controller

Fig. 9. Insulator details for mains rectifiers and thyristor

wire of an appropriate rating. Leads such as those running to the Veroboard can be of a lighter gauge.

When it has been ensured that all components and connections have been made correctly, power can be applied.

CHECK OUT

A voltmeter should be used to monitor the d.c. voltages present—those given in Fig. 4 are with respect to the thyristor cathode. At the collector of TR3 the voltage will change as the multivibrator oscillates, it depending on the setting of VR1.

A 100 watt lamp is a good load to check the operation of the unit; it will easily be seen that variation of the setting of VR1 results in a short flash at intervals of about one per second at one end of the range, with almost continuous light, punctuated by short term extinguishing of the lamp, at the other end. Settings of VR1 in between give smooth control of average power.

After a few minutes, withdraw the plug of the unit from the mains, and test the running temperature of the diodes and thyristor. With the 100 watt load suggested, they should not be in any way warm to the touch.

At this stage, it would be as well to ensure that the zero crossing circuits and AND gate are working correctly. To do this, disconnect one end of C3. The lamp should continue to flash, but at reduced brilliance. Disconnection of C4 also will give no output at all.

The explanation for this is that with C3 removed, only alternate half-cycles of the mains can be switched through to the load. Removal of both C3 and C4 means that no pulses are fed to TR1 and, with the AND gate working correctly, the output of the multivibrator is unable to switch on the thyristor.

NO INTERFERENCE

Correct functioning of this part of the circuit is essential if no interference is to be caused, for if the thyristor could apply voltage to the load starting at

any time but zero crossing, the resultant sudden flow of a large current would generate considerable r.f. energy.

Switch off of load current at zero crossing is automatic, for the current through the thyristor falls to zero at the end of each half-cycle.

With C3 and C4 replaced and a larger load connected, such as a 1kW fire, there will be a warming of the heat sinks and the box at the higher power settings. This is quite in order. It should be borne in mind that about 30 watts is to be dissipated at the highest setting, and in case this seems excessive, remember that it is only 3 per cent of the total power controlled.

At lower power settings, only slight warming should occur.

Depending on the relative values of the capacitors employed for C5 and C6—remember that electrolytics have a wide tolerance—it will be found that average power levels of from 10 per cent to 90 per cent of full power can be delivered.

SUBSTITUTE COMPONENTS

The question of substitute components will no doubt arise in connection with the Burst Fire Controller.

The transistors specified are BC107, but in fact unmarked *npn* transistors, quoted as being "similar to BC107" worked well, provided those found to be leaky or of low gain were not used.

As for the diodes D6 to D9, germanium or silicon devices can be used, although D8 and D9 should be of a similar type.

The thyristor employed in the prototype was a Mullard BTY79-400R; a BT102-500R also functioned satisfactorily. Unmarked thyristors, of a sufficiently high current rating may require more gate current than this circuit can generate and consequently may not prove to be suitable.

The power diodes are type BYZ12, with cathode stud. Alternatives, provided that they are at least of 400 volt 4A rating, but preferably of a somewhat higher current carrying capability, can be employed.

FLASHING DISPLAYS

As already described, the repetition rate is about one burst per second. An increase in the value of C5 and C6 to say, 4.7 μ F, or 6.8 μ F will slow down the rate of flashing to a suitable rate, while unequal values of these capacitors will enable the relative lengths of "on" and "off" time to be varied over a very wide range, particularly useful for lamp flashing displays.

Should the use of the Burst Fire Controller be confined to such uses, with upper power limits of, say, 200 watts, then some economies in the construction can be made. A 3A thyristor, on a smaller heat sink, and 1A wire ended rectifiers should enable the unit to be constructed in a smaller die-cast box, so making a very compact unit.

Apart from the obvious use of controlling room heaters, constructors may find the Controller useful to run a soldering iron, when on stand-by, at a reduced temperature, with switching to full power for actual soldering. These will increase the life of the iron bit. Other uses will doubtless occur to the home experimenter.

★



Microwave semiconductors

By M. FLETCHER (Mullard Ltd)

MICROWAVE frequencies occupy that part of the spectrum where the circuitry used is comparable in size to the wavelength. In practice this usually means frequencies from 1GHz to 100GHz or possibly higher. Originally exploited for radar at the beginning of World War II, microwaves now have a multitude of applications.

The wide bandwidths possible are utilised in communications, both overland and by satellite. Microwaves form a valuable research tool for performing various physical measurements and the use of high power microwaves is now being applied to cooking.

Until comparatively recent times microwave electronics has been largely the domain of thermionic devices. Within the last decade however a host of microwave semiconductor components have become available. Many of these, because of their simplicity and low power consumption compared to thermionic devices, are stimulating new applications for microwaves not previously considered practical.

POINT CONTACT

In the early development work on radar principles, a sensitive detector was required for the receiver to respond to the high frequencies being used. The

technique adopted was to use a point contact diode either as a detector or as a mixer in a superhet receiver.

The diodes used were really a refined form of the simple cat's whisker semiconductor rectifier used in early radio receivers. The form of construction is shown in Fig. 1. The noise figures obtained were poor by modern standards but sufficed for the purpose. No basic change in technology took place for many years although a steady improvement in materials and techniques brought about improvements in noise performance (Fig. 2).

Although still widely used today the point contact diode remained the only semiconductor element available to microwave engineers for nearly two decades. In the early 1960s, however, the gathering pace of semiconductor technology began to have application in the microwave area. One of the first of these devices was the variable capacitance diode or varactor.

VARACTOR DIODES

The varactor diode depends on the phenomenon of capacitance change under varying reverse bias due to the variation in the width of the depletion region in a *pn* junction. See Fig. 3.

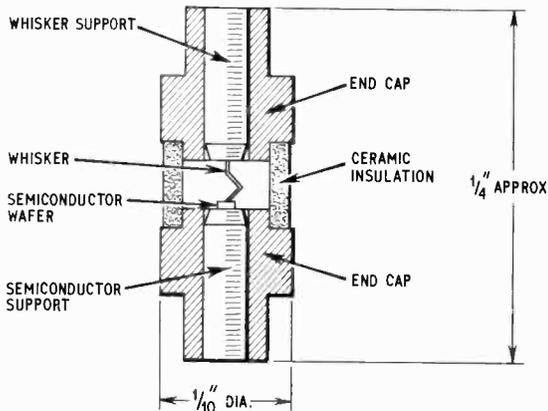


Fig. 1. Construction of a modern point contact mixer diode

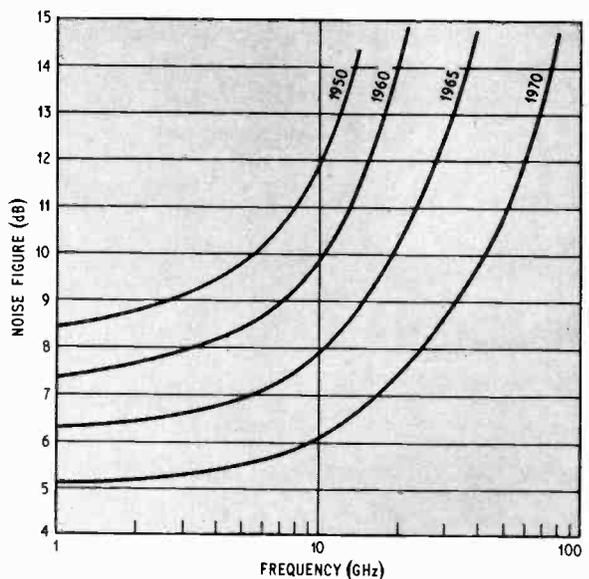


Fig. 2. Improvement in the noise figures of mixer diodes

The capacitance voltage relationship is $C \propto V^{-n}$. The value of n depends on the impurity profiles in the pn junction. It is typically 0.5 (as shown in Fig. 3) but the important point is that the relationship is non-linear.

The junction capacitance of a microwave varactor is normally specified at $V = 6V$ and might be from 0.2pF to 20pF, depending on the application. Various methods are used for fabricating pn junction varactors, two important ones being shown in Fig. 4.

The diodes are usually made with silicon although gallium arsenide is used for some special applications. The manufacturing problem is to define the required area of diffused pn junction since this affects the capacitance value.

In the case of the mesa diode this is done by etching away the unwanted area. In the case of the planar diode areas are defined by making holes in the oxide window of required size prior to diffusion. The holes are made by photolithography and the whole process is similar to that used for making planar transistors.

The advantage with planar construction is that a large number of diodes may be fabricated with one series of operations. When the varactor chip is made it must be mounted in an envelope suitable for use at microwave frequencies.

The varactor diode has numerous applications, not all of them confined to microwaves. Clearly it may be used as a circuit tuning element which is voltage controlled. In this respect it is used for tuning microwave oscillators, T.V. tuners, automatic frequency control systems and so on.

The other applications of the varactor depend on the fact that it is a non-linear circuit element whose response to a large signal differs from that of a small one. The change of impedance at high signal levels may be applied to limiter type circuits.

Under conditions of high signal level the varactor will generate harmonics. If resonant circuits are coupled, tuned to the harmonic frequencies, substantial amounts of power may be extracted at the higher frequency. Using the second or third harmonic, a chain of varactor multipliers may be built up capable of giving powers in the order of 1-2 watts at 8GHz (see Fig. 5).

Of course, losses are present in this system both in the circuits and the varactors and a great deal more power must be supplied at the lower frequencies from, say, power transistors. However it is a useful technique for generating power with solid state devices and is widely used in communications transmitters. Obtainable output powers are shown in Fig. 6.

SCHOTTKY BARRIER DIODES

Another new type of microwave diode to appear in recent years is the Schottky barrier diode. Basically a Schottky barrier is a junction diode with the junction formed between the semiconductor and a metal contact rather than between dissimilar semiconductor materials, as in the case of an ordinary pn diode.

The construction of a Schottky diode is shown in Fig. 7. The manufacturing processes used are very similar to those for planar diodes and many of the same advantages accrue, for example the uniformity arising from making a large number of diodes with a single process.

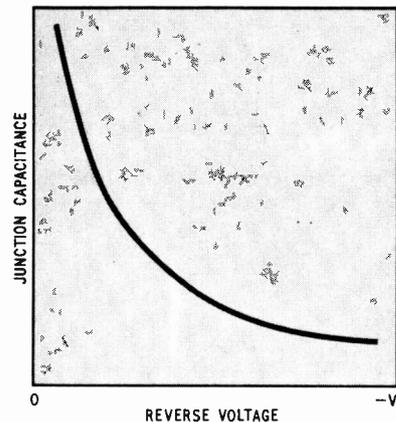


Fig. 3. Relationship of capacitance with voltage $C \propto V^{-n}$

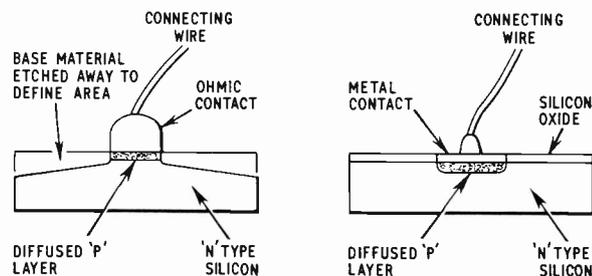


Fig. 4. Construction of (left) Mesa and (right) planar pn diodes. The chips are typically $0.25mm \times 0.25mm$

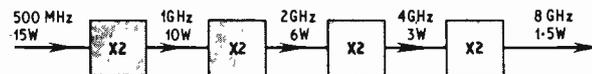


Fig. 5. Chain of varactor doublers producing 1.5W at 8GHz

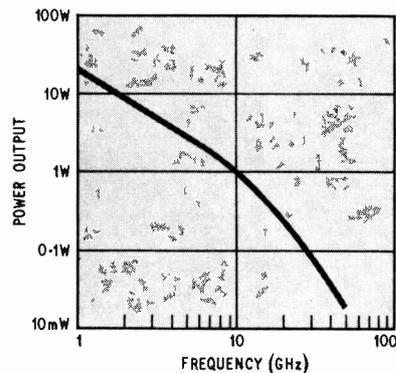


Fig. 6. Output power obtainable from varactor chains

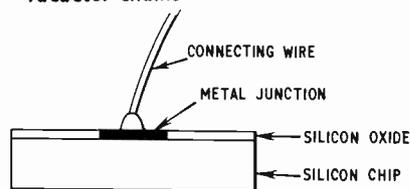


Fig. 7. Construction of Schottky barrier diode. The metal junction may be as small as 0.01mm across

The Schottky diode has the advantage that minority carrier storage effects (present in normal *pn* junction diodes) cannot take place. These limit the switching speed and hence rectification efficiency and are the main reason why *pn* diodes are not suitable for detection or mixing of microwave frequencies.

Thus Schottky diodes are finding application as microwave mixer diodes and have noise figures equal to the best point contact diodes. They are also

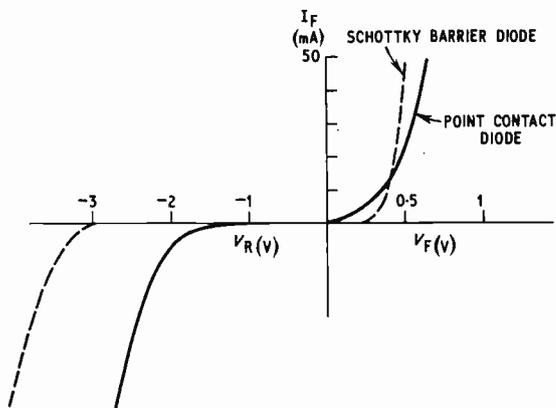


Fig. 8. Voltage/current characteristic of the Schottky barrier diode (dotted) compared with that of a point contact diode

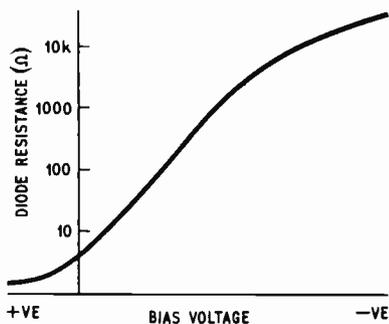


Fig. 9. Variable resistance characteristic of a pin diode

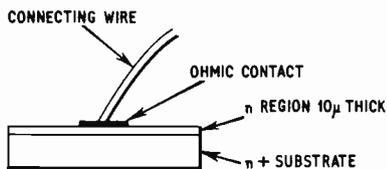


Fig. 10. Construction of a Gunn diode

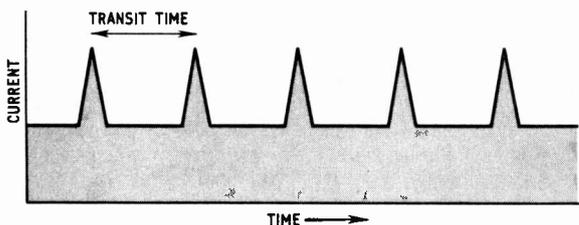


Fig. 11. Current/time waveform in a Gunn diode

mechanically more robust and have several other advantages so that in time they are likely to displace the long standing point contact microwave diode. The absence of minority carrier storage also makes the Schottky diode useful in high speed switching circuitry. The d.c. characteristics of silicon point contact and Schottky diodes are compared in Fig. 8.

THE PIN DIODE

Another new and very useful device is the *pin* diode. These consist of a *pn* silicon junction with a layer of intrinsic or high sensitivity silicon between the *p* and *n* regions. When forward biased the *pin* diode behaves as a resistance from d.c. to microwave frequencies. The value of the resistance depends on the forward current (see Fig. 9). Under reverse bias the resistance is very high.

Thus the *pin* diode may be used as an electrically variable resistance or attenuator. It uses at microwave frequencies are for switching and modulating microwave signals as well as an electrically variable attenuator. It can perform switching in a few nano-seconds and handle peak powers of hundreds of watts.

GUNN DIODE

The Gunn diode is one of the most important forms of a new family of microwave semiconductors which are used for directly generating microwave power from d.c. In view of their simplicity of operation and simple power supply requirements, Gunn diodes present an attractive alternative to the klystron valve.

The Gunn diode requires a power supply of a few volts d.c. which can be obtained from a battery as opposed to the reflex klystron which requires (typically) $-150V$ d.c. for the reflector, $+300V$ for the resonator, and $6.3V$ for the heater. At present Gunn diodes are rather expensive but already a Gunn diode transmitter with its battery can cost less than a klystron with its special power supply. Gunn diodes are available which can give up to $100mW$ of output power.

Gunn diodes are already being used in "mini-radar" systems for small boats, in burglar alarms, for counting, for measuring the speed of road traffic, and for many other applications where small size, simplicity of design and portability are important. Although simple in operation the mechanism of the Gunn diode requires some explanation.

The device is named after J. B. Gunn who discovered the phenomenon now called the "Gunn Effect" at the Watson Research Centre of I.B.M. in 1963.

GUNN DIODE CONSTRUCTION

Gunn diodes contain a tiny wafer of *n*-type gallium arsenide of thickness about $100\mu m$ mounted in a standard microwave diode encapsulation. The faces of the wafer constitute the two electrodes of the device, Fig. 10.

The wafer consists of a thin active layer of *n*-type gallium arsenide grown on a low resistivity substrate of the same material. The substrate is bonded to the anode terminal of the encapsulation and the other face of the wafer has an evaporated cathode contact connected by a bonded gold wire.

The Gunn diode has two terminals called the cathode and the anode. However, it is misleading to

ILP ELECTRONICS

present

the

HY40

for perfection

in stereo



Output Power: British rating, 40 watts peak, 20 watts RMS continuous.

Load Impedance: 8–16 ohms

Input Impedance: 22K Ω at 1KHz.

Voltage Gain: at 1KHz 30 dB.

Frequency Response: 5Hz to 60 KHz \pm 1dB.

Total Distortion: less than 1% (typical 0-1%) at all output powers.

Supply Voltage: 45 or \pm 22.5 volts.

Price: including comprehensive manual and P.C. board, Mono £3.98. Stereo £7.96. All post free.

Two HY40's each with five inexpensive extra components require only the addition of a simple power supply and tone network to produce a Hi-Fi stereo amplifier of excellent quality for modest cost.

The FREE MANUAL supplied with each HY40 gives clear "easy-build" instructions for a suitable power supply and tone network incorporating Volume, Bass, Treble and Balance controls, together with inputs for Ceramic and Magnetic Pick-ups, Tape, Tuner and Auxiliary Functions. Internally the HY40 is based on conventional and proven circuit techniques developed over recent years and will prove ideal not only for Hi-Fi but also for public address, organs, groups, etc.

ILP Electronics Ltd. Crossland House · Nackington · Canterbury

THIS MONTH'S NEW BARGAINS

T03 Heat Sink. Suitable for most power transistors OC26, etc. This is aluminium, anodised black for maximum heat dissipation. Supplied complete with mounting nuts and washers. Price 10p each or 10 for 90p. Size approx. 2 1/2 x 1 1/2 in.

12 Volt 500 M.A. Mains Transformers. Miniature type now available, price 55p each or 10 for £5.

3 Core Flex, New Colours. (Brown for live, blue for neutral, yellow/green for earth.) This is completely p.v.c. covered and ribbed, virtually non-kinkable. Suitable for washing machines (without heaters) and all portable tools, lawn mowers, etc. Conductor size 23/36. 1 p. per dozen yards £10 per 100yd coil.

MOTOR by A.E.I. 1/20 hp, 1.275 r.p.m. Self-starting for normal a.c. mains, a well made enclosed motor with standard 3/16in dia. shaft 1in long. Suitable for light power operation. Continuous rating. £1.50 plus 20p post.

Instrument Motor by Evershed. Hysteresis motor—makers type No. FEK25-4G30—this is a capacitor start motor for 110V a.c. working double ended shaft—£3.50 plus 20p post and insurance.

Cut and Prepared 3 Core Leads. 2yds long, p.v.c. covered and ribbed, virtually non-kinkable—23/36 conductors. Old colour scheme, 5p each, 10 for 70p. New colour scheme 15p each or 10 for £1.35.

Hearing Aid Amplifiers (Ex behind ear deaf aids). 3 transistors on tiny P.C. board with volume control—whole thing about half as big as Oto cube. £1.75 or with sub-miniature microphone and L.S. attached £3.50.

Totally Enclosed Mains Transformers with Primary for normal 230/240V 50Hz mains and secondary rated at 4A 80V tapped at 75V and 70V. This is a very well made transformer totally enclosed in metal case. Size 4 1/2 in x 3 1/2 in x 6 1/2 in high. Made to be mounted above chassis with terminations all on bottom. £3.50 each plus 65p post.

8 AMP Variacs. 0-260V—panel mounting type—ex-unused equipment, fully guaranteed. £10 each. (Carriage: England £1; Wales and Scotland: £1.20.)

Water Switches. Standard Size (1) wafer built to Post Office spec, good contacts and generally very reliable. 9 pole 3 way on 3 wafers, 45—10 for £4. ditto 2 pole 3 way, 20p—10 for £1.80.

P.C. Edge Connector. 18 contact switch with 2 mounting/earthing lugs—50p each, 10 for £2.70. **Pointer Knobs.** Bulgin brass insert type ref. No. K.357, black with white line down pointer grub screw fixing, 5p each—10 for 45p.

Jack-Socket Bulgin. Catalogue No. J14. This is a standard size panel mounting jack, with two leaf contact circuit switches incorporated. Makers recommended price 41p. Our price 30p or 10 for £2.70.

Miniature Water Switch, 1 Pole 8-Way. This has a short spindle and is therefore suitable only for mounting through a metal panel. Price 12p or 10 for £1.08.

24-Way Rotary Switch. Single pole, £1.25; double pole, £1.95.

Double pole, Double Throw Toggle Switch. Suitable for mains voltage and up to 10A. 15p or 10 for £1.35.

Pre-Recorded Tapes. Very Special Offer. Regular speed (3 1/2 i.p.s.) Mono tape recordings of popular long playing records. Each tape plays for approximately 15 minutes per track. These are on 5in spools but can easily be joined together to make a long tape for background music. We are offering these at less than 1/3 of the regular price.

Classical Recordings Offer. 32 recordings all "Nutcracker pieces," "Pomp and Circumstance Marches" "Nutcracker Suite" etc. Made by famous composers. Total of 32 different recordings (giving a playing time of approx. 16 hours). Price £20.

Popular Recordings Offer. 36 recordings of popular music by Frank Sinatra, Dean Martin, Cliff Richards, Nat King Cole, etc. (giving a total time of approx. 18 hours). Price £22.

Miniature Switch, 1 pole 6 way—Ex-unused equipment, 6p each, 10 for 54p.

Battery Model, Ballour Auto-changer. As mains model but for 24V operation also these are new ex-factory stock, not returned export. Less cartridge, 55 each plus 50p post and insurance. **Waterproof Floodlights.** Made by G.E.C. to take up to 500W lamp—ideal for garden lighting, etc. Price £2 each plus 65p carriage.

CAR ELECTRIC PLUG

Fits in place of cigarette lighter. Useful method for making a quick connection into the car electrical system. 38p each or 10 for £3.42.

ROCKER SWITCH

13A self-fixing into an oblong hole, size approximately 1 1/2 x 1/2 in 6p each, 10 for 54p.

MAINS RELAY BARGAIN

Special this month are some single, double and treble pole changeover relays. Contacts rated at 15A. Operating coil wound for 240V a.c. Good British make Unusud. Size approx. 1 1/2 x 1 1/2 in. Open construction.

Single pole 25p each 10 for £2.25
Treble pole 40p each 10 for £3.60

HORSTMANN "TIME AND SET" SWITCH

(A 15A Switch) Just the thing if you want to come home to a warm house without it costing you a fortune. You can beat the switch on time of your electric fire, etc., up to 14 hours from setting time or you can use the switch to give a boost period of up to 3 hours. Equally suitable to control processing. Regular price probably around £5. Special snip price £1.50, p. & ins. 25p.



OUT OF SEASON BARGAIN

TANGENTIAL HEATERS



Once again we are able to make a special bargain offer of these very popular heating units. Tangential heaters although brought out a few years ago are still the latest and best type as nothing has yet been made which could be called an improvement on them. The tangential unit is still the only one used in good quality heaters made by Hoover, G.E.C. and all the famous names. The unit comprises quiet running a.c. induction motor with special bearings, the tangential impeller and a 2 section heater element which allows switching half and full heat in the case of the 2 kW and one-third—two-thirds and full heat in the case of the 3 kW. These heaters are also fitted with a safety cutout to cut the heaters should the impeller stop or the air with flow be impeded. They are free standing and need only the simplest of cases, even a wooden cabinet is suitable or the plinth of the kitchen cabinet. Lots of customers missed our special Summer offer of these heaters last year so order early. 200/240 V 2 kW model £2.50. 200/240 3 kW model £3.50. Control switch heaters only 25p or two-heat, cold-blow and off switch. Postage and insurance 35p on heaters.

AMPLIFIER MAINS TRANSFORMER



50V 1 1/2 A. Upright mounting with fixing brackets and metal shrouds to contain magnetic field, 50 c/s primary, tapped 100V, 117V, 210V, 230V and 250V. 2 secondaries, one 50V 1 1/2 A, other 6V 1A for pilot light, etc. £1.95, postage 30p.

THIS MONTH'S SNIP

LIGHT DIMMER



For any lamp up to 200W. Mounted on switch plate to fit in place of standard switch. Virtually no radio interference. Price £1.99 plus 20p post & ins.

CAPACITOR DISCHARGE CAR IGNITION

This system which has proved to be amazingly efficient and reliable was first described in the *Wireless World* about a year ago. We can supply kit of parts for improved and even more efficient version, price £4.95 + 30p post. When ordering please state whether for positive or negative systems.

ELECTRONIC IGNITION


STANDARD WAFER SWITCHES



Standard size 1" wafer—silver-plated 5-amp contact, standard 1" spindle 2" long—with locking washer and nut.

No. of Poles	2	3	4	5	6	8	9	10	12
1 pole	40p	40p	40p	40p	40p	40p	40p	40p	40p
2 poles	40p	40p	40p	40p	40p	40p	40p	40p	40p
3 poles	40p	40p	40p	40p	70p	70p	70p	95p	95p
4 poles	40p	40p	40p	70p	70p	70p	70p	£1.20	£1.20
5 poles	40p	40p	70p	70p	95p	95p	95p	£1.45	£1.45
6 poles	40p	70p	70p	95p	95p	95p	95p	£1.70	£1.70
7 poles	70p	70p	70p	95p	£1.20	£1.20	£1.20	£1.95	£1.95
8 poles	70p	70p	70p	95p	£1.20	£1.20	£1.20	£2.20	£2.20
9 poles	70p	70p	95p	95p	£1.45	£1.45	£1.45	£2.45	£2.45
10 poles	70p	70p	95p	£1.20	£1.45	£1.45	£1.45	£2.70	£2.70
11 poles	70p	95p	95p	£1.20	£1.70	£1.70	£1.70	£2.95	£2.95
12 poles	70p	95p	95p	£1.20	£1.70	£1.70	£1.70	£3.20	£3.20

INSTRUMENT SWITCHES

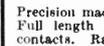

Precision made with diecast indexing mechanism. Full length 1/2 in spindle 5A and silver plated contacts. Range except for 8 way is as standard wafer switches. Prices obviously higher. For 40p read 60p, for 70p read £1, for 95p read £1.40, for £1.20 read £1.80, for £1.45 read £2.20. Note also 2 way types available up to 36 poles, 3 way 30 poles, 4 way 24 poles, 5 way 19 poles, but 10 and 12 way only available up to 6 poles.

3 STAGE PERMEABILITY TUNER



This Tuner is a precision instrument made for the famous Radionobile Car Radio. It is a medium wave tuner (but set of longwave coils available as an extra if required with a frequency coverage 1620kHz-25kHz and intended to operate with an I.F. value of 470kHz. Extremely accurate. The two small dial enable switch on/off times to be accurately set. Ideal for switching on tape recorders. Offered at only a fraction of the regular price—new and unused only £2.50, less than the value of the clock alone—post and insurance 15p.

ELECTRIC CLOCK WITH 25 AMP SWITCH



Made by Smith's, these units are as fitted to many top quality cookers to control the oven. The clock is mains driven and frequency controlled so it is extremely accurate. The two small dial enable switch on/off times to be accurately set. Ideal for switching on tape recorders. Offered at only a fraction of the regular price—new and unused only £2.50, less than the value of the clock alone—post and insurance 15p.

DISTRIBUTION PANELS

Just what you need for work bench or lab. 4 x 13A sockets in metal box to take standard 13A fused plugs and on/off switch with neon warning light. Supplied complete with 7ft of heavy cable. Wired up ready to work. £2.25 less plug, £2.50 with fitted 13A plug; £2.65 with fitted 1 1/2 A plug plus 25p P. & I.

Where postage is not stated then orders over £5 are post free. Below £5 add 20p. Semiconductor add 5p post. Over £1 post free. S.A.E. with enquiries please.

MAINS OPERATED SOLENOIDS




Model 778—small but powerful 1in pull—approx. size 1 1/2 x 1 1/2 x 1 1/2 in 60p.
Model 400/1 1in pull. Size 2 1/2 x 2 x 1 1/2 in 75p.
Model FT10 1 1/2 in pull. Size 3 1/2 x 2 1/2 x 2 1/2 in £1.80 plus 20p post and ins.

XEE 1/c, relays and most parts available. Send for list

MAINS CONNECTOR

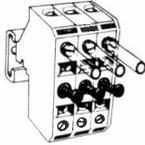A quick way to connect equipment to the mains safely and firmly—L, N, and E, coded to new colour scheme; disconnection by plugs prevents accidental switching on; has sockets which allow insertion of meter (without disconnection); cable inlets firmly hold one hair wire on up to four 7-029 cables. 85p each.



MINIATURE WAFER SWITCHES

2 pole, 2 way—4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole, 6 way—1 pole, 12 way. All at 18p.



WATERPROOF HEATING ELEMENT

26 yards length 70W. Self-regulating temperature control. 50p post free.

COMPUTER TAPE

2,400ft of the Best Magnetic Tape money can buy—users claim good results with Video and sound. 1in wide £1.45 plus 33p post and insurance, with cassette. 1/2 in wide £1.25 plus 30p post and insurance with cassette. 1in wide £1 plus 25p post and insurance with cassette. Spare spools and cassettes—1in 1 1/2, 1in 85p, 1/2 in 75p each plus 20p post and insurance.




BALANCED ARMATURE UNITS

These capsules are 1/2 in dia. and 1/2 in thick. They will operate as a microphone or loudspeaker so can be used in intercom and similar circuits. 35p, 10 for £3.

MULTI-SPEED MOTOR

Replacement in many well-known food mixers. Six speeds are available 500, 850 and 1,100 r.p.m. from either or both of the nylon sockets (where the beaters of the food mixers normally go) and 8,000, 12,000 and 15,500 r.p.m. (ideal polishing speeds) from the main drive shaft. This drive shaft is 1/2 in dia. and approximately 1in long. A further point about this motor is that being 230/240V a.c.-d.c. series wound its speed may be further controlled with the use of our Thyristor controller. This is a very powerful and useful motor size approx. 2in dia. x 5in long, mains 230/240V. Price 85p plus postage and insurance. 12 or more post free.

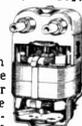

MAINS OPERATED CONTACTOR

220/240V 50 cycle solenoid with laminated core so very silent in operation. Closes 4 circuits each rated at 10A. Extremely well made by a German Electrical Company. Overall size 2 1/2 x 2 x 2in. £1 each.



QUICK CUPPA

Mini Immersion Heater, 350W, 200/240V. Boils full cup in about two minutes. Use any socket or lamp holder. Have at bedside for tea, baby's food, etc. £1.25, post and insurance 14p. 12V car model also available same price. Jug heater £1.50 plus p. & p. 14p.



TREASURE TRACER

Complete Kit (except wooden battens) to make the metal detector as described editorially in Practical Wireless, August issue. £2.50 plus 20p post and insurance.

A New Service to Readers. A bulletin bringing news of new lines, special snips and "too few to advertise" lines will be posted to subscribers during first week of each month. The bulletin will be called "Advance Advert News" and the Subscription is 60p per year. Subscribers will also receive our completed 1971 catalogue when this is published.

J. BULL (ELECTRICAL) LTD.

Dept. P.E. 7, Park Street, Croydon CRO 1YD

think of it as a diode as it has no *pn* junction and cannot be used for rectification. When a few volts d.c. are applied to make the anode positive with respect to the cathode, the current which flows is d.c. with superimposed pulses as illustrated in Fig. 11.

In the case of a diode designed to work at 10GHz, the current pulses occur at 10^{-10} second intervals and can be used to induce oscillations in a cavity or waveguide resonator.

GUNN EFFECT

The Gunn effect is caused by high field regions called "domains" passing between the cathode and the anode. When the supply is connected a high field domain builds up at the cathode and drifts rapidly through the crystal to the anode. As the domain reaches the anode, a new domain forms at the cathode.

The transit time of the domains through the active layer determines the frequency of the pulses. The velocity of the domains has been measured experimentally and is known to be about 10^{11} $\mu\text{m/s}$ and so a frequency of 10GHz ($\lambda = 3\text{cm}$) is obtained with a $10\mu\text{m}$ thickness.

As is well known, in the energy band diagram for semiconductor materials the valence and conduction bands are separated by an energy gap called the "forbidden gap". Electrons can be excited from the valence band to the conduction band by the application of energy, for example by heating the crystal or by the addition of donor atoms. However, this well-known concept does not explain the Gunn effect.

To explain the effect we must look more closely at the conduction band. This can in fact be divided into two regions—the normal conduction band and a higher energy "satellite" band. In the satellite band the effective mass of the electrons is higher and their mobility lower than in the normal conduction band, Fig. 12.

In *n*-type gallium arsenide the majority of the conduction band electrons can be excited into the satellite band by the application of a field of about 350V/mm. As this critical field is reached the electrons in the crystal become heavier and slow down.

This reduction in average velocity results in a negative resistance characteristic. For this phenomenon to occur, the energy gap between the normal conduction and satellite bands must be considerably smaller than the forbidden gap between valence and conduction bands, otherwise the application of the critical field would result in the transfer of electrons across the forbidden gap, and an increase rather than a decrease in the average velocity would result. Only a few known materials, notably gallium arsenide and gallium phosphide, have a suitable band structure.

ELECTRON MOBILITY

In an ordinary conductor under normal conditions the electron velocity increases linearly with the applied field (Ohm's law). In *n*-type gallium arsenide, however, the average velocity increases at first linearly with the field, Fig. 13 A to B and then, as the critical field of 350V/mm is reached and electrons begin to move into the low mobility satellite band, the average velocity begins to fall (point B). Eventually, as the field continues to increase and all the available electrons have moved into the satellite band, the velocity increases linearly again (C to D).

Clearly the region BC is one of negative resistance. However, the result of applying such a bias field to the wafer is not the same as for conventional negative resistance devices.

In practice the wafer is biased in the negative differential resistance region above the threshold value of 350V/mm. Many of the electrons coming into the crystal at the cathode are excited to the lower mobility satellite band and slow down. The situation where two types of carrier exist simultaneously is unstable and the lighter electrons flow away leaving a concentration of heavy ones behind.

It follows that there is a local increase in the field since, in the negative resistance region BC, a fall in average velocity is associated with an increase in field. Moreover the effect is cumulative since an increase in the field causes a further decrease in average velocity.

Hence a high field E_H builds up at the cathode whereas the field throughout the rest of the crystal falls to a low value E_L . The high field domain (E_H) drifts rapidly across the wafer to the anode.

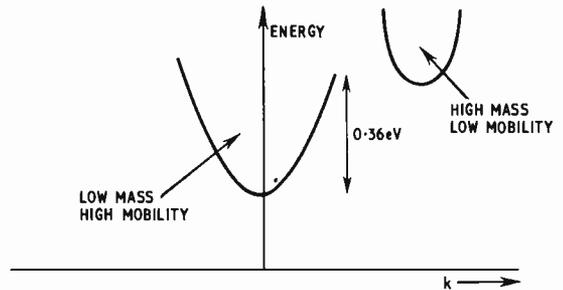


Fig. 12. Energy band diagram for gallium arsenide

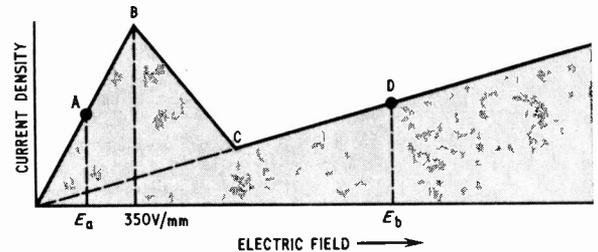


Fig. 13. Current density/electric field characteristic of an *n*-type gallium arsenide diode

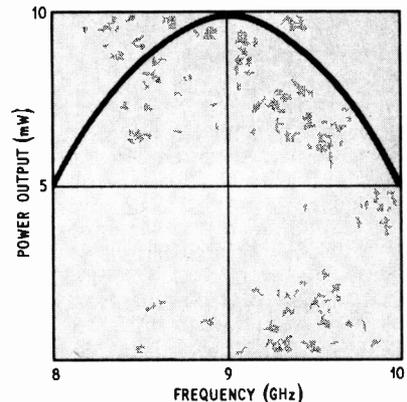


Fig. 14. Tuning characteristic for a Gunn oscillator

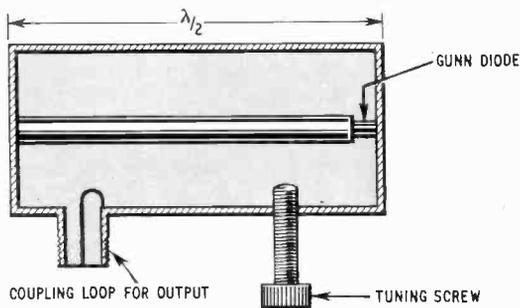


Fig. 15. Sectional view of a coaxial cavity Gunn oscillator

As the domain reaches the anode the bias supply again causes the field at the cathode to exceed the threshold of 350V/mm and a new domain is established. The action repeats continuously.

CHARACTERISTICS OF GUNN DIODES

From the above explanation of the Gunn Effect it is apparent that the frequency of oscillation depends on the thickness of the active layer of gallium arsenide (10 μ m at 10GHz). Whilst this is true, the device must be used in a cavity and the effect of the r.f. voltage in the cavity is to modify the transit time of the current pulses through the diode.

In practice it is found that a Gunn diode oscillator may be tuned up to one octave by tuning the cavity. Maximum power output occurs at or near the "normal" transit time frequency however (Fig. 14). Cavities may be constructed in either coaxial or waveguide form. A simple coaxial cavity is shown in Fig. 15.

By introducing a varactor diode into the cavity electronic tuning of the Gunn oscillator is possible up to a few per cent by varying the d.c. bias applied to the varactor. Such a combination of Gunn diode, cavity and varactor form a solid state equivalent of the klystron with the inherent advantages of modest power supply requirements and solid state reliability.

Gunn diodes are now commercially available from 4GHz to nearly 40GHz with power outputs from a few milliwatts to 100 milliwatts. Apart from being used in the traditional forms of microwave equipment the Gunn diode is already opening new fields of application for microwaves as mentioned above. Although the diodes are currently somewhat expensive for amateur construction projects the possibilities are many.

FUTURE FOR MICROWAVE SEMICONDUCTORS

So much innovation has occurred in this field during the last 10 years that it seems unlikely to be repeated in the 1970s. Although other new forms of device may be introduced there is bound to be an overriding trend to lower cost microwave semiconductors stimulating new microwave applications.


One way of producing cheaper microwave circuits is to eliminate the traditional "plumbing" required and substitute a thin film circuit. Transmission line components may be deposited onto a thin film substrate and microwave semiconductors bonded to this in chip form.

Already being introduced to professional systems, this technique is likely to have considerable impact in microwave applications in the years to come. ★

FOR SPORTS EVENTS
PHOTOGRAPHIC PROCESSING

MACHINE MEASUREMENT
BATCH COUNTING

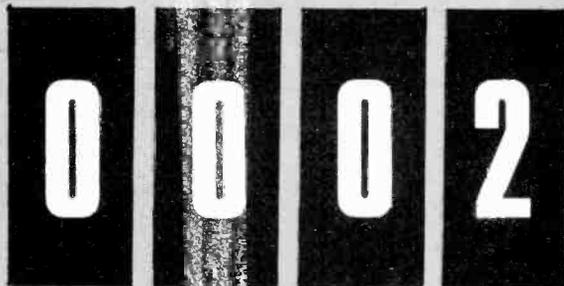Range 1/10 second to 16 minutes, or possibly 2 1/2 hours with a digital meter



●
TIMER
with **DIGITAL**
READOUT

THERE are many situations in both recreational pursuits and in engineering, where it is necessary to measure a time interval to one-tenth of a second without employing expensive and complex equipment. The suggested design in this article gives a direct digital reading with tenths of a second and keeps the cost to a reasonably small figure.

MEASUREMENT READOUT

In most digital timers, the designs are based on the accurate generation of a basic frequency; then, with suitable gating circuits, the counting of the number of cycles passed whilst the gate is open. The accuracy of these timers is therefore mainly dependent on the frequency generator.

Although some of the cost is determined by the frequency generator accuracy, the major proportion of the cost is usually involved in the readout system. An inexpensive digital readout device is the electromagnetic counter, several versions being readily available on the surplus market.

The use of this counter does place a limitation on the smallest measurable time interval and hence the number of decimal figures, since the maximum speed of operation is 10Hz. Accepting this limitation allows an inexpensive design based on a minimum time measurement of 0.1 second to be constructed.

Fig. 1 shows the system block diagram. A simple astable or multivibrator circuit generates a square wave of 10Hz. When the gate is opened this square wave supply drives the counter at the same speed. If the gate is held open for 10.8 seconds, the counter will have counted 10 units for each second, i.e. a reading of 108. Marking in the decimal point gives a direct readout of 10.8 seconds.

DRIVE CIRCUIT

The multivibrator circuit is given in Fig. 2. The transistors can be any germanium types such as OC71 or OC72. Potentiometer VR1 controls the frequency of oscillation, and the square wave generated may be taken from the collector of either TR1 or TR2.

Fig. 3 shows a suitable drive circuit for the counter. The additional relay is necessary since the majority of low voltage counters available on the surplus market take currents that are too high for the OC72.

If it is required to eliminate the additional counter battery and relay, then it is often possible to remove the counter coil and replace it with a more suitable coil taken from a Post Office 600 type relay, as was done in the prototype.

CALIBRATION

The unit should be calibrated with the multivibrator driving the counter, so that any loading presented by the relay/counter unit is accounted for. This may be achieved by comparing the collector voltage waveform with that of a signal generator, producing a signal of 10Hz, on a double beam oscilloscope, or a direct reading frequency meter.

An alternative method is to measure the time taken for the counter reading to change from, say 0 to 3,000 (which should take five minutes) with a stop watch. In this case an accuracy of at least 6 counts in 3,000, i.e. 0.2% or better should be obtainable.

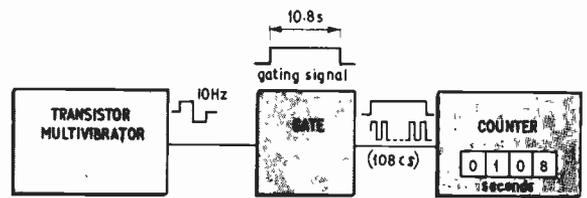


Fig. 1. Block diagram of the basic timing system

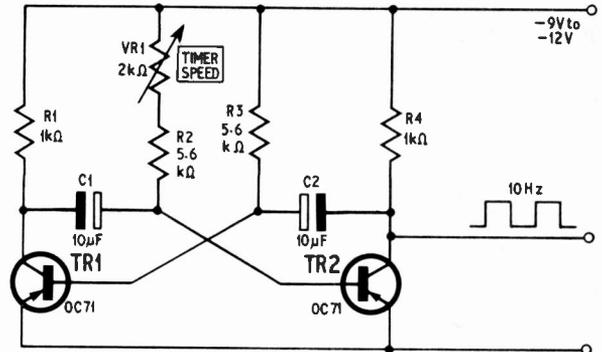


Fig. 2. Multivibrator oscillator used for providing clock pulses


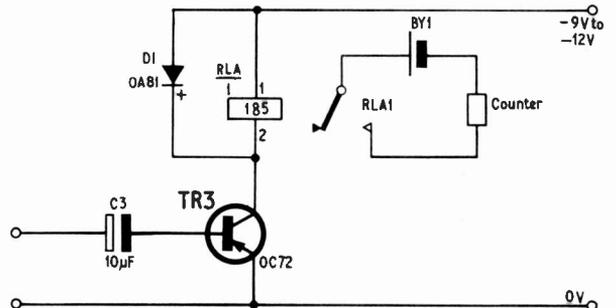


Fig. 3. Relay driver for operating the counter readout

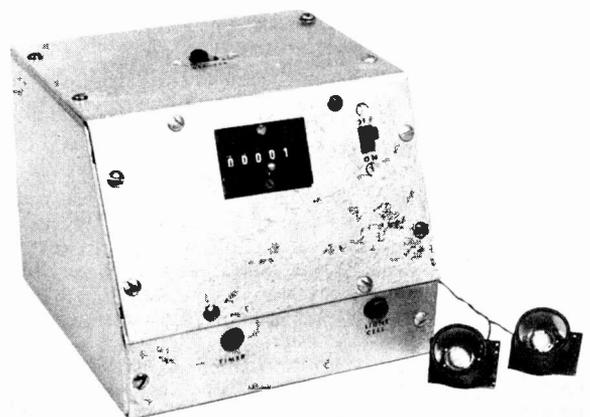

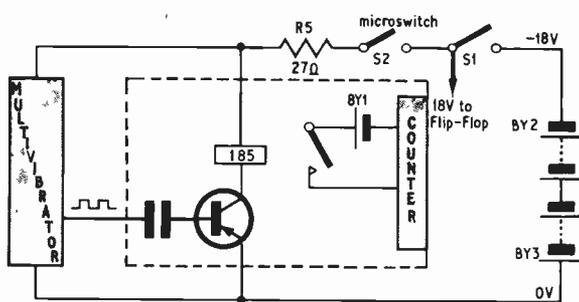
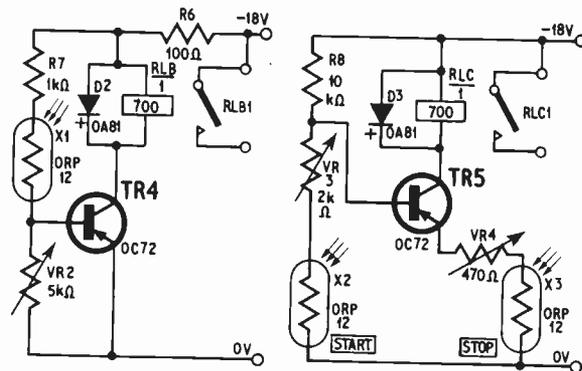
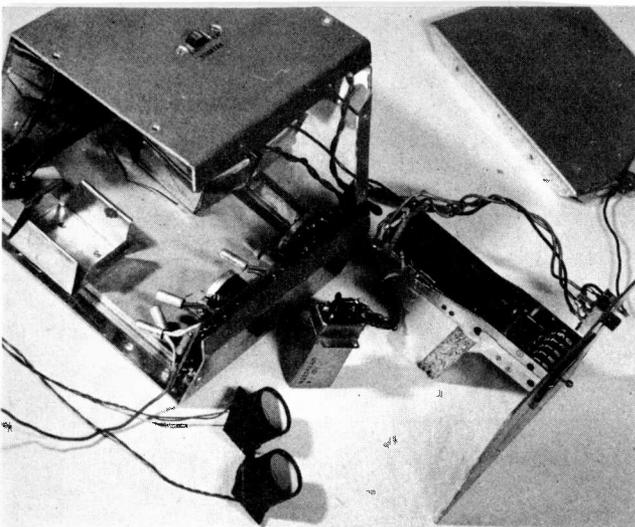


Fig. 4a. Multivibrator system using a microswitch to gate the clock pulses to the driver. The circuit for the multivibrator is in Fig. 2 and the relay driver in Fig. 3

COMPONENTS . . .

MULTIVIBRATOR AND RELAY DRIVER (Fig. 4a)

Resistors

- R1 1kΩ
- R2 5.6kΩ
- R3 5.6kΩ
- R4 1kΩ
- R5 27Ω
- All ± 10%, ¼W carbon

Potentiometer

- VR1 2kΩ linear preset spindle type

Capacitors

- C1, C2, C3 10μF elect. 15V (3 off)

Transistors

- TR1, TR2 OC71 (2 off)
- TR3 OC72

Diode

- D1 OA81

Relay

- RLA 185Ω, 6V operate

Batteries

- BY1 Battery to operate counter
- BY2, BY3 9V type PP9 (2 off)

Switches

- S1 Single pole on/off toggle switch
- S2 Single pole on/off microswitch

Miscellaneous

- Digital Counter (ex-G.P.O. telephone charge meter) (see text)
- Veroboard, 0.15in matrix, 12 copper strips by 38 holes for whole project

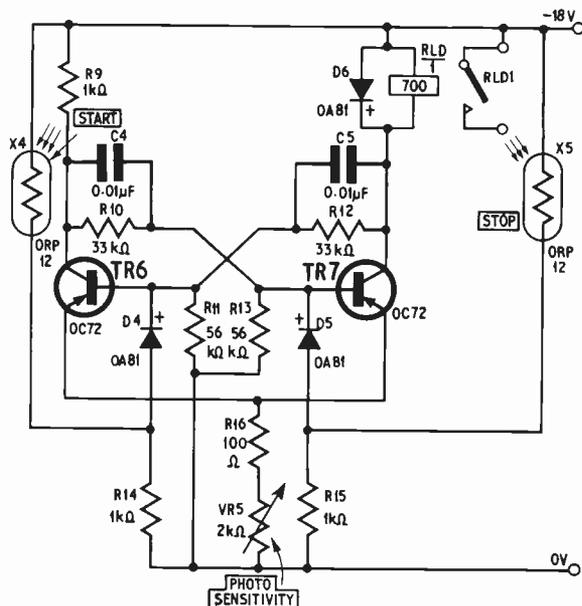


Fig. 4d. An improved stop start light sensitive circuit in the form of a flip-flop. Relay RLD1 is used in place of S2 in Fig. 4a

COMPONENTS . . .

LIGHT-SENSITIVE FLIP-FLOP (Fig. 4d)

Resistors

- R9 1kΩ
- R10 33kΩ
- R11 56kΩ
- R12 33kΩ
- R13 56kΩ
- R14 1kΩ
- R15 1kΩ
- R16 100Ω
- All ± 10%, ¼W carbon

Potentiometer

- VR5 2kΩ linear preset spindle type

Capacitors

- C4, C5 0.01μF

Transistors

- TR6, TR7 OC72 (2 off)

Diodes

- D4, D5, D6 OA81 (3 off)

Relay

- RLD 700Ω, 12V operate

Light sensitive cells

- X4, X5 ORP12 light dependent resistors 2 off)

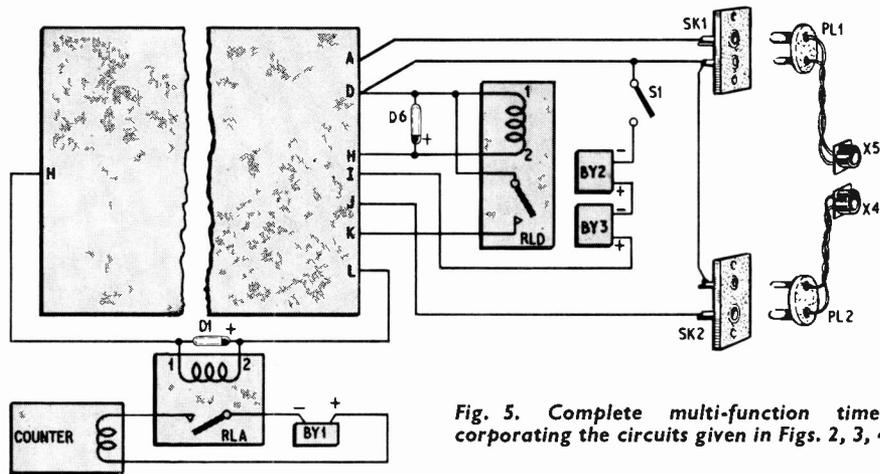


Fig. 5. Complete multi-function timer incorporating the circuits given in Figs. 2, 3, 4a, 4d

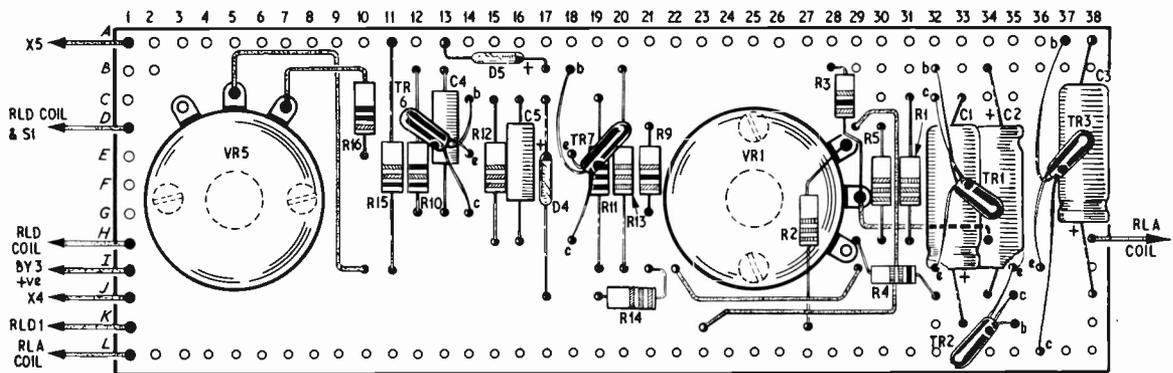


Fig. 6. Layout of components on Veroboard of system shown in Fig. 5. The copper strips must be cut at holes 25A, 25B, 25C, 24D, 25D, 25H, 24I, 25I, 25J, 25K

GATING CIRCUITS

To gate the unit, several methods are possible depending on the application of the timer. Basically, two alternatives are available: firstly, the d.c. supply line to the oscillator may be interrupted; secondly the output from the multi-vibrator may be interrupted. Both methods may have particular advantages, but in the prototype design the negative supply line was switched on and off by a relay.

Four possible gating methods are shown in Fig. 4. The first method (Fig. 4a) is the simplest, and is a single pole on/off switch such as a microswitch. This circuit could be employed for measuring the time taken for a moving object to pass a given point, so that the microswitch is held closed by the object. Alternatively, the switch could be held closed manually when the time for the object to pass between two points could be measured.

Fig. 4b indicates a photoresistor operated gate for a similar situation to that outlined above, the contacts on the relay replace the microswitch contacts. These methods could be used for sports events, photographic processing, machine speed measurement, batch counting and so on.

Fig. 4c shows a circuit whereby the passage of an object in front of the first cell X2 starts the timer, and the passage of an object in front of the second cell X3 stops the timer. This method was found to be satisfactory with the first model constructed, but the setting of VR3 and VR4 was found to be very critical.

Because of this, the more conventional bistable circuit (Fig. 4d) was adopted. Due to the additional transistor, diodes and other components, the circuit is more expensive, but the added reliability justifies its use in the majority of applications.

RESET CONTROL

An improvement may be to use a counter with a reset control, so that all the time reading will commence from zero readout. Unfortunately these units are much more costly, and some applications may not justify this additional expenditure. Resettable counters are obtainable but can cost a few pounds to buy. Further accuracy is possible by modifying the multivibrator to operate at 50Hz and to utilise a high speed counter.

CONSTRUCTION

A complete operational system using the basic system shown in Fig. 4a employs the following circuits for reliability, and the construction of the timer is based on these three: the multivibrator (Fig. 2); a gate unit (Fig. 4d); the drive unit (Fig. 3).

A Veroboard layout for this system is given in Fig. 6 and uses a board that has twelve copper strips each 38 holes long. The preset-potentiometers are fitted directly to the board, so that the only components not attached are the relays, with their associated diodes, the counter and miscellaneous

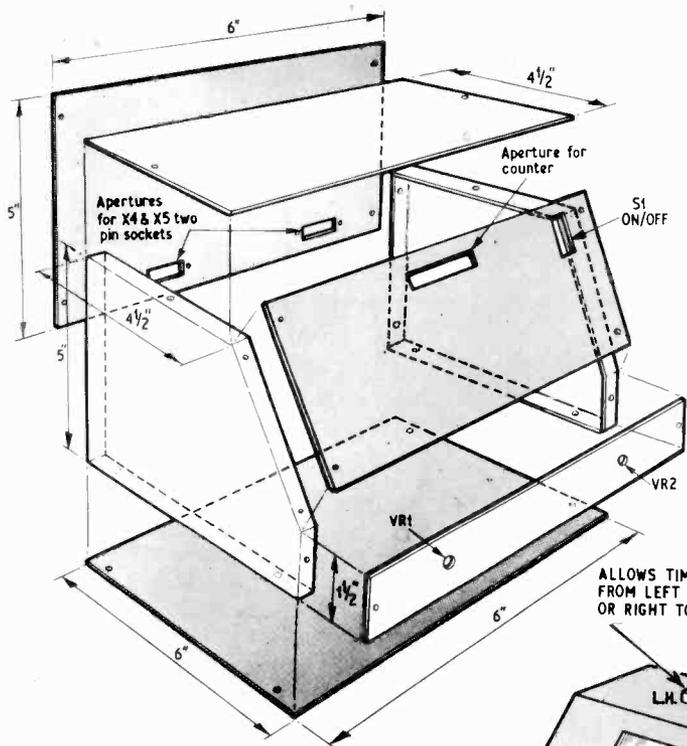


Fig. 7. Exploded view of the case showing drilling and assembly details


hardware such as switches, batteries, plugs and sockets. The use of "skeleton" or miniature potentiometers would enable a shorter length of Veroboard to be used.

The inter-unit wiring diagram is given in Fig. 5. This assumes that the counter requires the additional relay in the drive unit, and the extra battery. The counter used in the prototype had a coil which took only a few milliamperes, so that this directly replaced the relay RLA.

One suitable form of case (Fig. 7) is constructed from 18 s.w.g. or 20 s.w.g. aluminium sheet. Two end pieces are folded as indicated, and the flat top panel, rear, base, lower front and instrument panels fastened to the end pieces with self tapping screws. Alternatively, if bending proves too difficult, the end pieces may be cut from $\frac{3}{8}$ inch thick plywood, and the panels screwed to them.

A slide switch S1 is used to isolate the batteries when the timer is not in use. One refinement on the prototype was to use a two-pole, two-way slide switch in conjunction with the two cells, so that the triggering sequence of the cells could be reversed. For example, switch position 1: cell 1 starts the timer, cell 2 stops the timer; switch position 2 reverses the operation. See Fig. 8.

Fig. 8. Set-up of timer with two light sensitive cells for timing a moving object

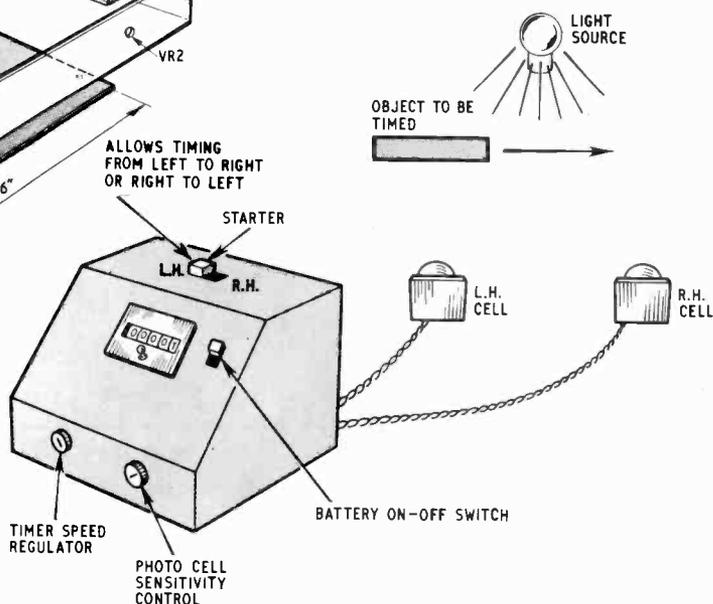

LIGHT SENSORS

Each l.d.r. is soldered to a small piece of Veroboard. Light shields for these may be made from small cardboard tubes (such as is found for containing sweets) and glued to the cells, to keep out unwanted stray light. The leads are fitted with miniature two-pin plugs to fit the sockets on the rear panel of the case.

Penlight torches are used as light projectors for the cells, as they produce a narrow concentrated beam of light, and are easily fitted in the required positions with adhesive tape.

OPERATION

Connect the two photo-sensitive l.d.r.s into the sockets on the rear of the case. Place the cells in bright daylight or average (not brilliant) artificial lighting. Switch on the supply. With the "starter" switch selecting "L.H.", and the right-hand cell covered with the hand or a piece of card, the counter should stop. If it does not, adjust the sensitivity control until it does. This should now be set for normal operation. Normally, when the L.H. cell is covered the timer should start; when covering the R.H. cell it should stop. Moving the "starter" switch to R.H. will reverse the cell effects.



TRANSISTORS

NEW LIST - NEW PRICES
SEND FOR FREE COPY TODAY

Brand New	Fully Guaranteed		
2N404	20p	BC107	12p
2N896	15p	BC108	12p
2N097	15p	BC109	12p
2N306	15p	BC113	15p
2N706A	12p	BC114	25p
2N930	25p	BC115	20p
2N131	25p	BC116	25p
2N132	25p	BC116A	30p
2N1302	20p	BC118	25p
2N1303	20p	BC119	35p
2N1304	25p	BC121	20p
2N1305	25p	BC135	20p
2N1306	25p	BC136	22p
2N1307	25p	BC137	25p
2N1308	25p	BC138	25p
2N1309	25p	BC147	17p
2N1613	22p	BC148	12p
2N1711	25p	BC149	17p
2N2147	25p	BC154	37p
2N2160	60p	BC157	20p
2N2218	20p	BC168	17p
2N2219	20p	BC159	20p
2N2222	20p	BC169	15p
2N2222A	25p	BC177	25p
2N2369	20p	BC178	25p
2N2484	25p	BC179	27p
2N2646	60p	BC182L	12p
2N2904	20p	BC183L	12p
2N2904A	25p	BC184L	15p
2N2905	25p	BC212	12p
2N2906	20p	BCY30	25p
2N2906A	25p	BCY31	30p
2N2907	25p	BCY32	30p
2N2926	10p	BCY33	25p
2N3011	25p	BCY34	30p
2N3055	20p	BCY38	40p
2N3054	50p	BCY39	85p
2N3055	75p	BCY40	50p
2N3252	10p	BCY58	25p
2N3702	10p	BCY70	15p
2N3703	10p	BCY71	20p
2N3704	15p	BCY72	15p
2N3705	15p	BCY78	30p
2N3707	15p	BCY79	30p
2N3709	10p	BCZ10	35p
2N3710	10p	BCZ11	35p
2N3819	35p	BD112	50p
2N3820	60p	BD121	65p
2N4058	15p	BD123	80p
2N4061	15p	BD124	75p
2N4547	35p	BD125	50p
2N4549	50p	BD131	75p
2N4550	50p	BD132	50p
2N4551	50p	BD133	62p
2N4552	50p	BD156	57p
2N4553	50p	BDY102L	25p
2N4554	75p	BDY112L	82p
40250	50p	BDY172L	50p
40361	50p	BDY182L	75p
40362	55p	BDY192L	75p
AA430	10p	BDY61L	25p
AA432	15p	BDY62L	25p
AA433	12p	BF115	25p
AA437	10p	BF152	30p
AC107	37p	BF154	40p
AC126	25p	BF158	30p
AC127	25p	BF160	30p
AC128	25p	BF167	25p
AC176	25p	BF170	35p
AC187	30p	BF173	30p
AC188	30p	BF177	40p
ACY17	30p	BF178	25p
ACY18	25p	BF179	25p
ACY19	25p	BF180	35p
ACY20	20p	BF181	35p
ACY21	20p	BF182	30p
ACY22	16p	BF184	20p
ACY39	60p	BF185	20p
ACY40	15p	BF194	17p
AD140	50p	BF195	15p
AD149	50p	BF196	15p
AD161	37p	BF197	15p
AD162	37p	BF200	37p
AF114	25p	BF274	37p
AF116	25p	BFX13	25p
AF117	25p	BFX20	25p
AF118	62p	BFX37	35p
AF124	25p	BFX44	25p
AF125	20p	BFX85	35p
AF126	17p	BFX86	25p
AF127	17p	BFX87	25p
AF128	30p	BFX89	20p
AF178	47p	BFY18	30p
AF179	65p	BFY50	20p
AF180	62p	BFY51	20p
AF181	42p	BFY52	22p
AF186	40p	BFY53	17p
AF239	40p	BFY90	65p
AS236	25p	BFX39	20p
AS272	82p	BFX21	20p
AS278	25p	BFX76	15p
AS279	30p	BFX95	15p
AS276	47p	BFX95A	15p
AS221	42p	BY100	15p
BA115	7p	BY126	15p
BA164	10p	BY127	15p
BAX13	6p	BY182	85p
BAX16	7p	BYZ10	40p
BAY31	7p	BYZ11	35p
BAY38	17p	BYZ12	30p

HENRY'S LOW COST INTEGRATED CIRCUITS

WE OFFER FROM STOCK AN EXCLUSIVE RANGE OF BRAND NEW FULL SPECIFICATION LOW COST TTL 7400 RANGE OF INTEGRATED CIRCUITS

Part No.	Ceramic	Description	Price and Qty.
7400	Quadruple 2-input NAND Gate	23p	20p 10p 15p 13p
7401	Quadruple 2-input Positive NAND Gate (with open collector output)	23p	20p 15p 13p
7402	Quadruple 2-input Positive NAND Gates (with open collector output)	23p	20p 15p 13p
7403	Quadruple 2-input Positive NAND Gates (with open collector output)	23p	20p 15p 13p
7404	Hex Inverters	23p	20p 15p 13p
7405	Hex Inverter with open collector	23p	20p 15p 13p
7410	Triple 3-input Positive NAND Gates	23p	20p 15p 13p
7413	Dual 4-input Schmitt Trigger	35p	32p 29p 25p
7420	Dual 4-input Positive NAND Gates	23p	20p 15p 13p
7423	8-input Positive NAND Gates	23p	20p 15p 13p
7420	Dual 4-input Positive NAND Buffers	23p	20p 15p 13p
7441	BCD to decimal nixie driver	87p	77p 69p 60p
7442	BCD to decimal decoder (4-10 lines, 1 of 10)	87p	77p 69p 60p
7447	BCD-Seven-Segment Decoder/Drivers (15-V Outputs)	£1.40	£1.30 £1.20 £1.05
7450	Expandable dual 2-input AND-OR-INVERT	23p	20p 15p 13p
7451	Dual 2-wide 2-input AND-OR-INVERT GATES	23p	20p 15p 13p
7452	Quad 2-input Expandable AND-OR-INVERT	23p	20p 15p 13p
7454	4-wide 2-input AND-OR-INVERT Gates	23p	20p 15p 13p
7460	Dual 4-input Expander	23p	20p 15p 13p
7470	Master-slave J-K Flip-Flop	35p	32p 29p 25p
7472	Master-slave J-K Flip-Flop	35p	32p 29p 25p
7473	Dual 0 Master slave J-K Flip-Flop	43p	40p 37p 33p
7474	Dual 0 Master slave J-K Flip-Flop	43p	40p 37p 33p
7475	Quad J-K Flip-Flop	47p	45p 43p 40p
7476	Dual J-K with pre-set and clear	47p	45p 43p 40p
7480	Gated Full Adders	87p	77p 69p 60p
7481	16-bit read/write memory	£1.35	£1.25 £1.15 £1.00
7482	2-bit Binary Full Adders	£1.30	£1.20 £1.00 86p
7483	Quad Full Adder	87p	77p 69p 60p
7486	Quad 2-input Exclusive OR Gates	80p	70p 67p 60p
7489	BCD decade counter	77p	77p 69p 60p
7491	8-bit Shift Registers	£1.21	£1.00 87p 75p
7492	Divide-by-Twelve Counters	87p	77p 69p 60p
7493	4-bit Binary Counters	87p	77p 69p 60p
7494	Dual entry 4-bit shift register	87p	77p 69p 60p
7495	4-bit up-down shift register	87p	77p 69p 60p
7496	5-bit Parallel in parallel out Shift Register	87p	77p 69p 60p
7497	8-bit Bistable Latches	£1.75	£1.65 £1.35
7411	Hex Set-Reset Latches	£1.30	£1.20 £1.00 85p
7412	Monostable Multivibrators	87p	77p 69p 60p
7414	BCD-to-Decimal Decoder/Driver	87p	77p 69p 60p
7415	BCD-to-Decimal Decoder/Drivers	£1.80	£1.70 £1.60 £1.50
7415	8-bit Data Selectors (with Strobes)	£1.40	£1.30 £1.20 £1.05
74153	Dual 4-Line-to-1-Line Data Selectors/Multiplexers	£1.40	£1.30 £1.20 £1.05
74191	Binary Counter reversible	£3.50	£3.25 £3.00 £2.50

Prices may be mixed to qualify for quantity price. Dates available for above series in booklet form, price 10p. (Ref. No. 30). Larger quantity prices Extn. 4, Dual Inline 14 Pin Socket 30p each 16 Pin 35p each.

SILICON RECTIFIERS

1 AMP MINIATURE WIRE ENDED PLASTIC RECTIFIERS

Type	P.I.V.	1-49	50+	100+	500+	1000+
IN4001	50	8p	7p	8p	5p	4p
IN4002	100	8p	7p	8p	5p	4p
IN4003	200	10p	9p	7p	6p	5p
IN4004	400	10p	9p	8p	7p	6p
IN4005	600	12p	10p	9p	7p	6p
IN4006	800	12p	14p	12p	11p	9p
IN4007	1000	20p	16p	13p	12p	10p

1.5 AMP MINIATURE WIRE ENDED PLASTIC RECTIFIERS

Type	P.I.V.	1-49	50+	100+	500+	1000+
PL4001	50	10p	8p	8p	7p	6p
PL4002	100	11p	10p	9p	8p	7p
PL4003	200	12p	11p	10p	9p	8p
PL4004	400	12p	11p	10p	9p	8p
PL4005	600	15p	13p	11p	10p	9p
PL4006	800	17p	15p	13p	12p	10p
PL4007	1000	20p	17p	16p	13p	11p

INTEGRATED CIRCUITS

IC	Price	IC	Price
MCFC4000P	£1.18	LA709C	85p
I.C. 12	£2.75	MC1304	£2.76
PA246	£2.45	MC724P	65p
TA263	75p	741C (70S)	85p
TAD100	£1.97	709C (DIL)	85p
TAD110	£1.97	709C (DIL)	65p
MC1303	£2.60	Toshiba 20 watt	
UL900	40p	Amp	£4.47
UL914	40p	Toshiba	
UL923	40p	PreAmp	£1.50

ZENER DIODES

400 mW 5% Miniature
BZY Range. All voltages 3-33 Volt 16p each.

Voltage	Price
25 + 12p; 100 + 10p; 500 + 8p; 1000 + 6p. Any one type.	
1 Watt 5% Metal case. Wire Ends. 6-8V. all voltages to 100V. 25p each.	
25 + 22p; 100 + 19p; 500 + 17p; 1000 + 15p. Any one type.	
3 Watt Plastic Wire Ends 5% All voltages 6-8-100V. 30p each.	
25 + 27p; 100 + 25p; 500 + 23p; 1000 + 21p. Any one type.	
10 Watt 81ud Mounting 5% All voltages 5-100V. 40p each.	
25 + 87p; 100 + 85p. Any one type.	

TRIACS

Type	P.I.	Cur.	(All stud mounting)
SC35A	100	3 amps	90p
SC35B	200	3 amps	85p
SC35C	400	3 amps	80p
SC40A	100	6 amps	£1.00
SC40B	200	6 amps	£1.20
SC40C	400	6 amps	£1.25
SC45A	100	10 amps	£1.25
SC45B	200	10 amps	£1.35
SC45C	400	10 amps	£1.50
SC50A	100	15 amps	£1.65
SC50B	200	15 amps	£1.75
SC50C	400	15 amps	£2.00
SC50D	500	15 amps	£2.10
SC50E	500	15 amps	£2.25
DIAC ST2	20p		

Larger quantity prices E. tn. 4

SEMI-CONDUCTORS

LOOK AT THESE PRICES FOR QUANTITIES FROM STOCK

AFI14 Mullard 25p 25 + 20p 100 + 17p 500 + 15p	AFI15 Mullard 25p 25 + 20p 100 + 17p 500 + 15p
AFI16 Mullard 25p 25 + 20p 100 + 17p 500 + 15p	AFI17 Mullard 25p 25 + 20p 100 + 17p 500 + 15p
2N3055 75p Mullard 115watt Silicon Power 25 + 65p 100 + 50p	2N3819 Texas 35p 25 + 30p 100 + 25p 500 + 20p 1000 + 18p
BFY90 65p 1000 MC/S 25 + 60p 100 + 55p 500 + 50p	2N2646 40p Motorola Unijunction 25 + 35p 100 + 30p 500 + 25p
AFI39 30p Siemens V.H.F.	AFI86 40p Mullard V.H.F. 25 + 35p 100 + 30p 500 + 25p
OC170 Mullard 25p 25 + 21p 100 + 17p 500 + 15p	BYZ13 25p Mullard 6a 200v 25 + 20p 100 + 17p 500 + 15p
OC171 Mullard 30p 100 + 22p	BC107, BC108, BC109 12p each I.T.T. Plaps 25 + 11p 100 + 10p 500 + 8p
BY127 Mullard 20p 1000v 1 amp Plastic 25 + 17p 100 + 15p 500 + 13p	OC71 97p Mullard Photo 25 + 85p 100 + 80p 500 + 75p
BCI13 SGS 15p 25 + 13p 100 + 11p 500 + 9p	OA202 10p SILICON Diodes 25 + 8p 100 + 6p 500 + 5p 1000 + 4p
OC28 62p Mullard Power 25 + 55p 100 + 50p 500 + 42p	OC42 Mullard 30p 25 + 25p 100 + 23p 500 + 21p 1000 + 18p
OC45 Mullard 15p 25 + 13p 100 + 12p 500 + 10p 1000 + 8p	OC71 Mullard 15p 25 + 12p 100 + 10p 500 + 8p
OC75 Mullard 25p 25 + 21p 100 + 17p 500 + 15p 1000 + 13p	ORP12 Mullard 50p 25 + 45p 100 + 42p 500 + 40p
OC20 97p Mullard 100v 25 + 85p 100 + 80p 500 + 75p	2N930 25p 25 + 33p 100 + 20p 500 + 17p 1000 + 15p
OC44 Mullard 17p 25 + 15p 100 + 13p 500 + 11p 1000 + 10p	OC72 Mullard 25p 25 + 20p 100 + 17p 500 + 15p 1000 + 13p
OC139 Mullard 25p 25 + 20p 100 + 17p 500 + 15p	OC84 25p 25 + 20p 100 + 17p 500 + 15p
OC81 Mullard 25p 25 + 20p 100 + 17p 500 + 15p	AF239 42p 25 + 35p 100 + 30p 500 + 25p 1000 + 20p

HENRY'S SEMI-CONDUCTOR DEPARTMENT

303 EDGWARE RD., LONDON, W. TEL: 01-723 1008/9
RADIO LTD. CALLERS 356 EDGWARE ROAD W2.

NEW LIST - NEW PRICES
1971 TRANSISTOR
LIST 1500 +
SEND FOR YOUR FREE
COPY TODAY.

VARIABLE VOLTAGE TRANSFORMERS

BODINE TYPE N.C.I. GEARED MOTOR



(Type 1) 71 r.p.m. Torque 10lb. inch. Reversible, 1/70th h.p., 50 cycle, 0.38 amp. (Type 2) 28 r.p.m. Torque 20lb. inch. Reversible, 1/80th h.p., 50 cycle, 0.28 amp. "As new" condition. Input voltage of motor 115V a.c. Supplied complete with transformer for 230/240V a.c. input. Price, either type £3.15 plus 35p P. & P. or less transformer £2.13 plus 27p P. & P.

12 VOLT DC MOTOR

Powerful 1 amp. REVERSIBLE motor. Speed 3,750 RPM complete with external gear train (removable) giving final speed of 125 RPM. Size: 4 1/2" x 2 1/2" dia. Price 95p inc. post.



230V/240V COMPACT SYNCHRONOUS GEARED MOTORS

Manufactured by either Sangamo, Haydon or Smith. Built-in gearbox. 1 rev. per hour. Clockwise rotation. 1 rev. per hour. Anti-clockwise rotation. 2 revs. per hour. Clockwise rotation. 3 revs. per hour. Anti-clockwise rotation. 5 revs. per hour. Anti-clockwise rotation. 60 revs. per hour. Clockwise rotation. Fraction of makers' price. All at 75p incl. P. & P.



ALARM BELL

Mfg. by GENTS. 6 inch bell, 3/6 volt D.C. operation. As NEW. Only £1.50 plus 45p P. & P.

200-250V A.C.

NEON INDICATOR

Available in red or amber at 20p each. Or in green at 32p each. Minimum order 3 units. P. & P. 5p.



ELECTRONIC ORGAN KIT

Easy to build, Solid State. Two full octave (less sharps and flats). Fitted hardwood case. Powered by two penlite 1.5V batteries. Complete set of parts including speaker, etc. together with full instructions and 10 tunes. Price £3.00. P. & P. 22p.

50 in 1 ELECTRONIC PROJECT KIT

50 easy to build Projects. No soldering, no special tools required. The kit includes Speaker, Meter, Relay, Transformer, plus a host of other components and a 56-page instruction leaflet. Some examples of the 50 possible Projects are: Sound Level Meter, 2 Transistor Radio, Amplifier, etc. Price £7.75. P. & P. 30p.

CRYSTAL RADIO KIT

Complete set of parts, including: Crystal Diode, Ferrite Antenna, Drilled Chassis, and Personal Ear Piece. No soldering, easy to build, full step by step instructions. £1.75 inc. post.

230V AC SOLENOID

Extremely powerful with approx. 14lb. pull, 1" travel. Fitted with mounting feet. Size: 4" long, 2 1/2" wide, 3" high. £2.00 incl. P. & P.



230-250V SOLENOID

Mfg. by Westool, approx. 1 1/2 lb pull (similar in appearance to above illustration). Size of feet 1 1/2" x 1 1/2". Price 85p incl. Post.

VENNER Electric Time Switch

200/250V Ex. G.P.O. Tested. Manually set, 2 on, 2 off every 24h. Override switch: 10A £3.75, 15A £3.25, 20A £3.75. P. & P. 20p. Also available with solar dial ON dusk, OFF dawn. Price as above.



INPUT 230/240V a.c. 50/60 OUTPUT VARIABLE 0-260V.

All Types (and Spares) from 1/2 to 50 amp from stock.

SHROUDED TYPE

1 amp, £5.50. 2.5 amp, £6.75.

5 amp, £9.75. 8 amp, £14.50.

10 amp, £18.50. 12 amp, £37.50.

15 amp, £25.00. 20 amp, £37.00.

37.5 amp, £72.00. 50 amp, £92.00. Carr. extra.

OPEN TYPE (Panel Mounting) 1/2 amp, £3.93.

1 amp, £5.50. 2 1/2 amp, £6.63. Carr. 40p on open types.



2.5 AMP

Superior Quality Precision Made NEW POWER RHEOSTATS

100 WATT. 1 ohm, 10A; 5 ohm, 4.7A; 10 ohm, 3A; 25 ohm, 2A; 50 ohm, 1.4A; 100 ohm, 1A; 250 ohm, 0.7A; 500 ohm, 0.45A. 1 kΩ, 280 mA; 1.5 kΩ, 230 mA; 2.5 kΩ, 2A; 5 kΩ, 140 mA. Diameter 3 1/2" Shaft length 3 1/2" dia. 1 1/2" in. All at £1.50 each. P. & P. 5p.

50 WATT. 1/5, 10/25, 50/100, 250/500, 1/1.1-5/2-5/kΩ. All at £1.12 each. P. & P. 11p.

25 WATT. 10/25/50/100/250/500/1/1.1-5/2-5/kΩ. All at 78p each. P. & P. 15p.



STROBE! STROBE! STROBE!

Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/250V a.c. operation.

EXPERIMENTERS' ECONOMY KIT

Speed adjustable 1 to 36 Flash per sec. All electronic components including Veroboard S.C.R. Unijunction Xenon Tube, and instructions £6.30 plus 25p P. & P.

NEW INDUSTRIAL KIT

Ideally suitable for schools, laboratories, etc. Roller tin printed circuit. New trigger coil, plastic thyristor. Speed adjustable 1-80 f.p.s. Price £10.50. P. & P. 50p.

HY-LYGT STROBE MK III

This strobe has been designed and produced for use in large rooms, halls and the photographic field, and utilizes a silica plug-in tube for longer life expectancy, printed circuit for easy assembly, also a special trigger coil and output capacitor. Speed adjustable 0-30 f.p.s. Light output approx. 4 joules. Price £12.00. P. & P. 50p.

AND NOW! THE 'SUPER' HY-LYGT KIT

Approx. four times the light output of our well proven Hy-Lyght strobe.

- Heavy duty power supply.
- Variable speed from 1-23 flash per sec.
- Fantastic Octal based tube with massive electrodes.
- Reactor control circuit producing an intense white light.

The brilliant light output of the "SUPER" HY-LYGT gives fabulous effects with colour filters. Never before a Strobe Kit with so HIGH an output as LOW a price. ONLY £20 plus 75p P. & P.

7-inch POLISHED REFLECTOR. Ideally suited for above Strobe kits. Price 53p. P. & P. 13p or post paid with kits.

RELAYS SIEMENS, PLESSEY, Etc.

MINIATURE RELAYS - COMPETITIVE PRICES

1	2	3	4	1	2	3	4
45	6-9	2 HD M	50p	700	12-24	2 c/o	63p*
185	6-12	2 c/o	63p*	700	15-35	2 c/o HD	73p*
185	6-12	4 c/o	73p*	700	16-24	6M	63p*
230	9-12	4 c/o	78p*	1,250	24-36	4 c/o	63p*
280	9-12	2 c/o	73p*	2,500	36-45	6M	63p*
600	18-32	4 c/o	78p*	2,400	30-48	4 c/o	30p
700	16-24	4M 2B	63p*	9,000	40-70	2 c/o	50p*
700	16-24	4 c/o	78p*	15k	85-110	6M	50p*

(1) Coil ohms; (2) Working d.c. volts; (3) Contacts; (4) Price (HD) Heavy Duty. All Post Paid. *Including Base.

MAINS RELAY

230V a.c. coil 3 c/o. 10 amp a.c. contacts, 50p plus 8p P. & P.

MOTOROLA MAC II/6 PLASTIC TRIAC 400 PIV. 8 AMP

Now available EX STOCK. Supplied with full data and applications sheet. Price £1.05. P. & P. 7p. Suitable DIAC (RCA 40583) 30p each.

COLOUR TELEVISION PICTURE FAULTS

There are over 120 illustrations, including 88 colour photographs by K. J. Bohlman. £2.50. Postage 10p.

RCA SOLID-STATE HOBBY CIRCUITS MANUAL, by R.C.A. £1.05. Postage 10p.

ABC'S OF INTEGRATED CIRCUITS, by R. P. Turner. £1.25. Postage 10p.

TRANSISTOR AUDIO & RADIO CIRCUITS, by Mullard. £1.50. Postage 10p.

TAPE RECORDERS, by H. W. Hellyer. £2.25. Postage 10p.

BASIC THEORY & APPLICATION OF TRANSISTORS, by Dover. 90p. Postage 10p.

TRANSISTOR MANUAL, by G.E. £1.05. Postage 10p.

RADIO VALVE & TRANSISTOR DATA, by A. M. Ball. 75p. Postage 10p.

ELECTRONICS POCKET BOOK, by J. P. Hawker. £1.40. Postage 10p.

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST of British and American Technical Books
19-21 PRAED STREET
LONDON W2 1NP

Phone: PADdington 4185

Closed Saturday 1 p.m.

OSMABET LTD.

We make transformers amongst other things

MAINS TRANSFORMERS

Prim. 200/240V a.c. TX6, 425-0-425V, 500 mA, 8.3V, 6A CT, 0-5-6-3V, 3A, £12.75; TX1, 425-0-425V, 250mA, 6.3V/4A CT, 0-5-6-3V, 3A, £17.80; TX2, 250-0-250V, 150mA, 6.3V/4A CT, 0-5-6-3V, 3A, £4.05; TX3, 300-0-300V, 120mA, 6.3V/2A CT, 6.3V, 2A, 8.3V, 1A, £4.05; TX8, 250-0-250V, 65mA, 6.3V, 1.5A, £2.10; MT1, 200V, 30mA, 6.3V, 1A, £1.20; MT2, 230V, 45mA, 6.3V, 1.5A, £1.50; MT2A, 250V, 60mA, 6.3V, 2A, £1.85; MT3 Prim. 110/240V, Sec. 250V, 100mA, 6.3V, 2A, £2.25.

AUTO TRANSFORMERS

30 to 4kVA, up to 10kVA to order.

MULTIVOLT TRANSFORMERS

Prim. 200/240V a.c. OMT4/1. One tapped sec. 5-20-30-40-60V giving 5-10-15-20-25-30-40-45-50-60, 10-0-10, 20-0-20; 30-0-30V a.c., 1A, £2.25; OMT4/2 ditto, 2A, £3.45; OMT5/1 one tapped sec. 40-50-60-80-90-100-110V a.c., 1A, £3.45. Duo 12V 4A-12V 4A £3.60; Duo 0-10-20-25V 2A-0-10-20-25V 2A £3.60.

LOW VOLTAGE TRANSFORMERS

Prim. 200/240V a.c. 6.3V, 1.5A, 85p; 3A, £1.13; 6A CT, £1.80; 12V, 1.5A, £1.13; 3A CT, £1.80; 6A CT, £2.70; 18V, 1.5A CT, £1.80; 24V, 1.5A CT, £1.80; 3A CT, £2.70; 3A, £2.75; 8A, 85p; 12A, 85p; 40, 3A CT, £3.45.

MIDGET RECTIFIER TRANSFORMERS

For FW rect., size 1 1/2 x 2 x 1 1/2 in. Prim. 200/240V a.c. output, PPT1 9-0-9V, 0.3A, PPT2 12-0-12V, 0.25A, PPT3 20-0-20V, 0.15A, £1.20 each; ditto, size 2 x 2 1/2 x 1 1/2 in. MTV1 9-0-9V, 1A, 98p; MTV2 12-0-12V, 1A, 100p; MTV3 20-0-20V, 0.75A, £1.20 each.

O/P TRANSFORMERS FOR POWER AMPLIFIERS

P.P. sec. tapped 3-7.5-15 ohms, A-A 6.8kΩ, 30W (KT66, etc.), £4.05; 50W, 3kΩ, A-A, £6.75; 100W, 3kΩ, A-A, EL34 (KT88, etc.), £11.40 with and to 400V.

LOUDSPEAKERS, HI-FI, P.A., GUITAR, ETC.

New boxed famous makes, 25W, £5.60; 35W £7.20; 50W, £9.45; 60W, £11.80; 100W, £19.90; E.M.I. 131 x 8in, 10W, 8 and 15 ohms, £2.25; fitted two tweeter Hi-Fi, 3, 8 and 15 ohms, £4; Horn tweeter 2-16kHz, 8 or 15 ohms, 10W, £1.80; 6in, 8in, 9in, 6in, 12in, 8in, 12in, 10in, £1.95, 7 x 4in, £1.25, 8 x 6in, £1.35, 10 x 6in, £1.90, 3, 8 or 15 ohms. MATCHING AUTO SPEAKER TRANSFORMER Match speaker impedance to amplifier from 3 to 8 or 15 ohms, step up or down 10V, 75p.

12V LT FLUORESCENT LIGHTING

Complete 8 watt 12 in fitting with tube, £3.75; 12V inverter for 20 watt tube, £5.75.

PRINTED CIRCUIT ETCHING KITS

Comprehensive factory pack, with all solutions, and equipment to make your own P.C. boards, instructions, £1.25.

Carrriage extra all orders.

S.A.E. INQUIRIES-LISTS, MAIL ORDER ONLY

46 Kenilworth Road, Edgware, Middx. HA8 8YG

Tel. 01-958 9314

SERVICE TRADING CO

All Mail Orders—Also Callers—Ample Parking Space
Dept. P.E. 57 BRIDGMAN ROAD, LONDON W4 5BB
Phone 01-995 1560 SHOWROOM NOW OPEN MON.-FRI.

Personal callers only. Open Sat.
9 LITTLE NEWPORT ST.
LONDON WC2H 7JJ 01-437 0576



BOOK REVIEWS

A DICTIONARY OF ELECTRONICS—Third Edition

Compiled by S. Handel

Published by Penguin Reference Books

413 pages, 6½in × 4½in. Price 45p

TO COMPILE a dictionary of any kind is no small task and of those currently available in the electronics field, this Penguin paperback gives by far the best value for money. To add to the data given above, there are 185 designated diagrams plus numerous "thumb-nail" drawings of circuit symbols against appropriate references. All the descriptions and diagrams are concise and easy to understand; cross-references are also given to related expressions in a distinctive type face.

Whilst Mr Handel readily admits in the Preface that omissions are inevitable due either to oversight or the need for avoiding over complication, one must give full credit for keeping up-to-date with such a useful work. Since the second edition was first published five years ago, a great many changes in electronics have brought to light several new entries.

On the subject of acronyms, many have had to be left out; the author feels that he needs a RED PENCIL—a Reliable Electronic Device for Printing Every Name Composed of Initial Letters.

M.A.C.

TEST YOUR KNOWLEDGE OF PHYSICAL ELECTRONICS

By T. Wilmore

88 pages. Price 80p

TEST YOUR KNOWLEDGE OF APPLIED ELECTRONICS

By R. W. J. Barker

92 pages. Price 80p

TEST YOUR KNOWLEDGE OF TELECOMMUNICATIONS

By L. Ibbotson

92 pages. Price 80p

Published by the Butterworth Group.

All 7½in × 4½in.

THREE titles in a series of revision texts designed to cover a first degree course in electrical engineering and HNC, HND and CEI examinations. The books are based on a series of question and answer tests which have appeared over a period of years in *Wireless World*.

The first in the series deals with electron physics and poses questions on electron dynamics, atomic theory and spectra, semiconductor physics electron emission and valves. It concludes with sections on gas discharge processes, devices and lasers and masers.

The second book, probably more pertinent for readers of this magazine, covers rectifiers and regulator diodes, load lines, small signal amplifiers, feed-

back, power amplifiers, oscillator, switching theory and waveshaping.

The final volume in Telecommunications includes principles, Fourier analysis, noise, two part networks, transmission lines, waveguides, radio propagation, aerials and modulation theory.

In each of the books the questions are set on each right hand page with the solutions overleaf. This certainly speeds the learning process.

Since most of the questions require calculations, to work through these texts will undoubtedly reinforce any weaknesses or knowledge of specific matter for examination purposes.

G.G.

INTEGRATED CIRCUIT SYSTEMS

By D. J. Walter, B.Sc.(Eng.), C.Eng.

Published by Iliffe Books (Butterworth Group)

228 pages, 9in × 6in. Price £3.50

FIRST of all let me qualify this title a little because first impressions might assume a complete dossier on all types of integrated circuit. The primary aim of the book is to assist students in the final stages of HND or degree courses in engineering and computer science. The emphasis is on logic systems using monolithic integrated circuits, although operational amplifiers and d-to-a and a-to-d converters are brought in at the end to relate the arithmetic logic to real time and on-line applications.

Having established these details it comes somewhat as a surprise to find Chapter 1 extolling the ins and outs of reliability assessment and statistical analysis of quality control procedures. Chapter 2 goes into manufacturing procedures, and it is not until page 59 that we start to come to terms with the theory and application of logic systems and Boolean algebra in relation to integrated circuits. This, as they say, is the meat, and the book progresses through flip flops and counting circuits to binary calculation, correction and coding in Chapter 5.

Armed with the information gained in these three chapters, the reader can then make an intelligent assessment of the advanced techniques using MOS (Chapter 6) which will undoubtedly figure more prominently in the near future.

Converters (mentioned previously) provide a means of assessing the characteristics of analogue or digital techniques and interrelating both of these to the task in hand.

Generally, this book has been carefully prepared and the author provides a great deal of useful material, assuming that the reader has some mathematical background experience.

M.A.C.

PRICES !!!

Due to recent Government purchase tax changes, all prices quoted in the magazine may be subject to alteration

RADIO ASTRONOMY TECHNIQUES

BY F.W.HYDE · PART 4

*Image of the Sun projected by an optical telescope.
First sunspots ever transmitted over BBC television*



THE first project that will be undertaken will be a Simple Full Power Radio Telescope for the study of Solar Radiation. This project has been chosen because it will be possible to record the sun quite satisfactorily with a minimum of apparatus. Furthermore, it will be possible to use the system for the amateur bands and for the observation of satellites. The design of the aerial system will also be applicable to a more advanced telescope in the form of a simple interferometer and later to the near professional set-up of a complete phase-switching system. All the apparatus of the simple full power telescope will be absorbed as the project advances.

NATURAL PROGRESSION

Those who undertake this programme will be going step by step from the simplest type of radio telescope to the most advanced form that can be attempted by the private enthusiast.

There is a considerable advantage in taking this course, because in moving from the simple to the complex a better understanding of the final results will emerge. It also means that each unit that is constructed or adapted will remain in the project. There will be no redundant parts. This perhaps will be most helpful to the younger group who may have to improvise more.

In the construction of the telescope only common or garden "bits" will be essential, but of course those who wish to put their mechanical engineering skill to work can do so provided the basic parameters are kept in mind. The aerial system can normally be of wood or angle iron, whether the latter be the wrought iron type or drilled constructional angle of which there are a number of proprietary makes. The life of an aerial system constructed of wire and rough sawn timber, even unpainted, is of the order of ten years. In fact the writer has one unit which is still in operation after twelve years.

Perhaps it would be right here to set out the objects of the Project and what is required to implement them.

THE PROJECT

The purpose of this project is the study of solar radiations at a frequency of 137MHz. Time of observations:

- (1) Sunrise to two hours after sunrise
- (2) Two hours before noon (G.M.T.) until two hours after noon
- (3) Two hours before sunset until sunset

Conditions of locality will determine whether the first and last items are practicable. It will add valuable data about the propagation of radio waves if these two periods of observation can be put into operation.

THE TELESCOPE

Aerial System

Ninety degrees Corner Reflector Steerable in azimuth and altitude, or fixed in azimuth but steerable in altitude.

Pre-Amplifier

Valve or transistor, gain preferably 16dB plus, noise level as low as possible, bandwidth about 5-10MHz.

Receiver

A standard communications receiver preceded by a convertor for the operating frequency. A two-position time constant circuit may be added.

Recording

For recording purposes a pen recorder and/or tape recorder will be required. The pen recorder should preferably have two speeds, one inch and three inches per hour. The tape recorder should have speeds sufficient to cover the period of observation and ideally this will be $\frac{1}{8}$ inches per second. If the recorder can accommodate large reels then $1\frac{7}{8}$ inches per second could be used.

Power Supply

The power supply should be stabilised. The preferred form would be a stabilised mains transformer. Some of these are still available on the surplus market. If this is not possible then a voltage stabilised power pack can be employed. Many of the communications units already have in-built stabilisation.

D.C. Amplifier

This will offer a higher sensitivity than the direct recording from the output of the receiving unit. Where the pen recorder is of a low current type then this will be an advantage. If the pen recorder is of the potentiometer type it will have an in-built amplifier.

DATA RECORDING

The manner in which data recordings are stored is most important. It may take the form of an album for the pen recordings or, alternatively, the whole record may be kept on the paper roll and a simple table with spindles used to scan the paper by rolling from one spindle to the other. The advantage of this is that later scrutiny may reveal other items of regular change which may be worth a special study. This is in fact how many new sources of radiation were discovered.

Cassettes are useful to store the tape recordings.

The log book should be arranged in columns so that it contains a record of the times of starting and finishing an observation. The background level of radiation at the start of the observation period and also at the end of the period should be noted. The maximum level that was recorded should also be included. Finally, a column for special remarks which should include a note of the weather conditions at the time of observations.

AUTOMATED OPERATIONS

It should be noted here that in radio astronomy it is not always necessary for the operator to be present. This is perhaps one of its advantages over optical astronomy. Provided certain precautions are taken anyone can be taught the simple methods of setting up and switching on the equipment and merely returning to check at the time the observation ends.

If no help like this is available then the whole operation can be automated so far as the start and stop times are concerned. A time clock arranged to cut in for a sufficiently adequate time for the

equipment to warm up and become stabilised, and then to cut out at the end of the observation time would work out quite well.

Such a procedure will result in a considerable saving in paper and tape, and in the general project that is being used to start the hobby, will not materially affect the results. The day to day variations of local conditions will be known since there will be a preliminary trial period of observation before starting the observations in earnest.

THE CORNER REFLECTOR AERIAL

The corner reflector has been chosen for two main reasons. Firstly, it has a front-to-back ratio which is superior to the ordinary dipole and reflector. Unwanted signals from the rear of the array are at a minimum and the best use of the forward gain can be made.

Setting the size for the lowest frequency that is to be used will allow for even greater efficiency when other projects involving higher frequencies are attempted—this is the second reason for the choice of this type of aerial.

REASON FOR HIGH GAIN

The corner reflector can be regarded as a development of the flat sheet in that it is folded so that single elements may be used for the same effective gain. An analysis of this aerial is not an easy task but some clue as to the reason for the high gain in such a simple aerial can be understood from the diagram in Fig. 4.1.

Angles other than 90 degrees may be used but each has certain individual characteristics. For example, had 60 deg. been chosen instead of 90 deg. there would have been a greater reduction in bandwidth for little advantage in forward gain.

If the diagram in Fig. 4.1 is studied it will be seen that there are three images of the dipole in addition to the dipole itself. The nett result of this configuration is to provide a forward gain of some 10dB over a single dipole. It can be viewed as though the images reinforce the real dipole and add to the gain.

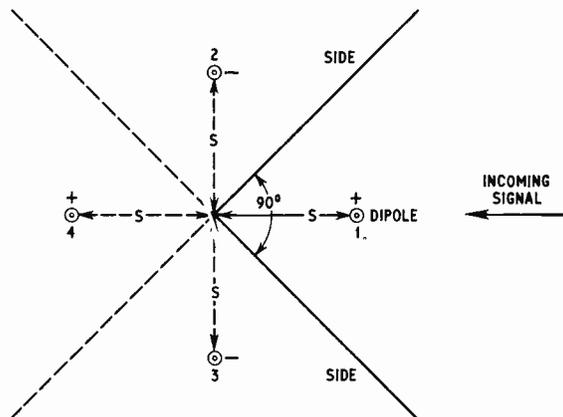


Fig. 4.1. The corner reflector aerial: an analysis diagram showing the reflections of the real dipole. If the reflector was not present the configuration would behave as though there were four separate dipoles. The presence of the reflector can be regarded as the means by which the gain is increased over a half-wave dipole in free space. The result is an increased gain in the forward direction

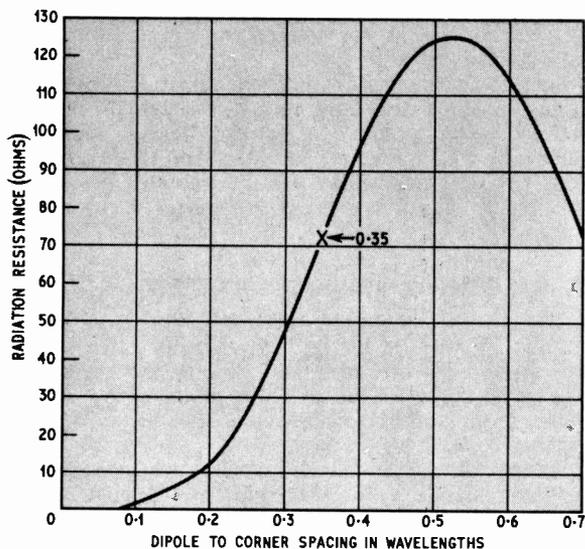


Fig. 4.2. Chart of terminal radiation resistance of a half wavelength dipole in relation to the distance of the dipole from the apex of a 90 degree corner reflector

It is possible to set up an extensive mathematical analysis of the corner reflector but no useful purpose would be served at this time by doing this. The empirical measurements which have been made of this type of aerial yield consistent results and these data will be used for the purpose of this design. The system is quite tolerant in that the gain over a reasonable variation of dimensions remains constant.

AERIAL IMPEDANCE

The chart in Fig. 4.2 shows the variation of the impedance of the dipole at various distances from the apex of the reflector. It will be seen that the optimum value is a spacing from the apex to the centre of 0.35 wavelengths for an impedance of 72 ohms.

If a single dipole is used then standard 75 ohm coaxial cable will be suitable for conveying the signals from the aerial to the receiving system.

PRACTICAL DIMENSIONS

Having chosen a frequency of 137MHz for the project the practical aerial will need to conform to the following dimensions.

The frequency of 137MHz is a wavelength of approximately 2.2 metres. This is about 7ft 2in. The length of the reflector according to the dimensions laid down in Part 1 should not be less than 1.5 wavelengths at the lowest frequency to be used. At the frequency chosen this will be 10ft 9in, but for convenience this can be rounded up to 11ft.

The width of the side of the reflector was given as not less than 0.7 of a wavelength. This works out at approximately 5ft, but as it would be beneficial to exceed this dimension this will be rounded up to 6ft.

With these dimensions it will be possible to use two half-wavelength dipoles in the reflector with the benefit of gain increase by a factor of 2.

AERIAL CONSTRUCTION

The diagrams in Fig. 4.3 show the constructional details for the aerial reflector assembly.

Work begins with the construction of the reflector. This consists of two frames each 11ft by 6ft, see "A". These should be finished with a coat of aluminium paint. Next the reflecting surface is added to each frame. This can consist of either wire mesh or single wires.

WIRE MESH REFLECTOR

If mesh is to be used, then it must be of good quality with a mesh size of not less than one inch. This refers to the normal twisted galvanised wire type. There is another popular type of welded mesh and this is better than the ordinary type previously mentioned. Both types of mesh do however, suffer from certain mechanical drawbacks. This particular type of reflector requires to be pulled very tightly up on the frames and it is doubtful if a really flat surface will be achieved with mesh. A certain amount of buckling is tolerable—say up to one and a half inches—however, it does not look very elegant though the performance of this aerial will not be impaired.

SINGLE WIRES

A more simple and easy method of making the reflector is to use single wires. This can result in a successful unit which is also of satisfying appearance. The single wires may be of standard insulated telephone wire or fencing wire (16 s.w.g.) which should be "half-hard" to hold tension.

The wires should be arranged in parallel rows at one inch spacing. They will run longitudinally and be secured at each end of the frame. If insulated wire is used then on the wooden frames ordinary staples should be used.

Starting at one end the wire is made off with two turns round the staple and a tail of 2 inches or so left, see inset diagram "A". The staple is then driven home tightly. The other end of the wire is dealt with in the same way after tensioning. The intermediate fixings are made with staples driven in far enough to hold the wire but leaving room for movement to take care of expansion and contraction.

If bare wire is used then it would be better to use insulated staples for the intermediate positions since movement in the wire in the supporting staples may give rise to unwanted noise in the aerial system.

CONNECTING THE TAILS

After a frame is completed the tails should be soldered so that there is a continuous connection between all elements of the reflector. It is not good enough to merely twist the ends together for there will be corrosion which could also add to noise in the aerial. The rule again here as with wiring connections is use *no flux other than resin*.

Fig. 4.3a shows how the two frames are bolted together. The accompanying photograph of one type of corner unit shows some of the details of construction. (The supports at the sides of the particular unit shown in this photograph will help to give some alternative ideas for use in cases where the aerial is to be fixed in azimuth.)

The reflector itself has side members bolted on, see "B". The centre strut serves to support the dipole units and also provide the suspension points for the reflector on the main frame support.

It will be necessary to check the centre of gravity of the completed unit so that it is balanced. This will ensure easy adjustment of position in altitude.

RADIO TELESCOPE CORNER REFLECTOR AERIAL Constructional Details

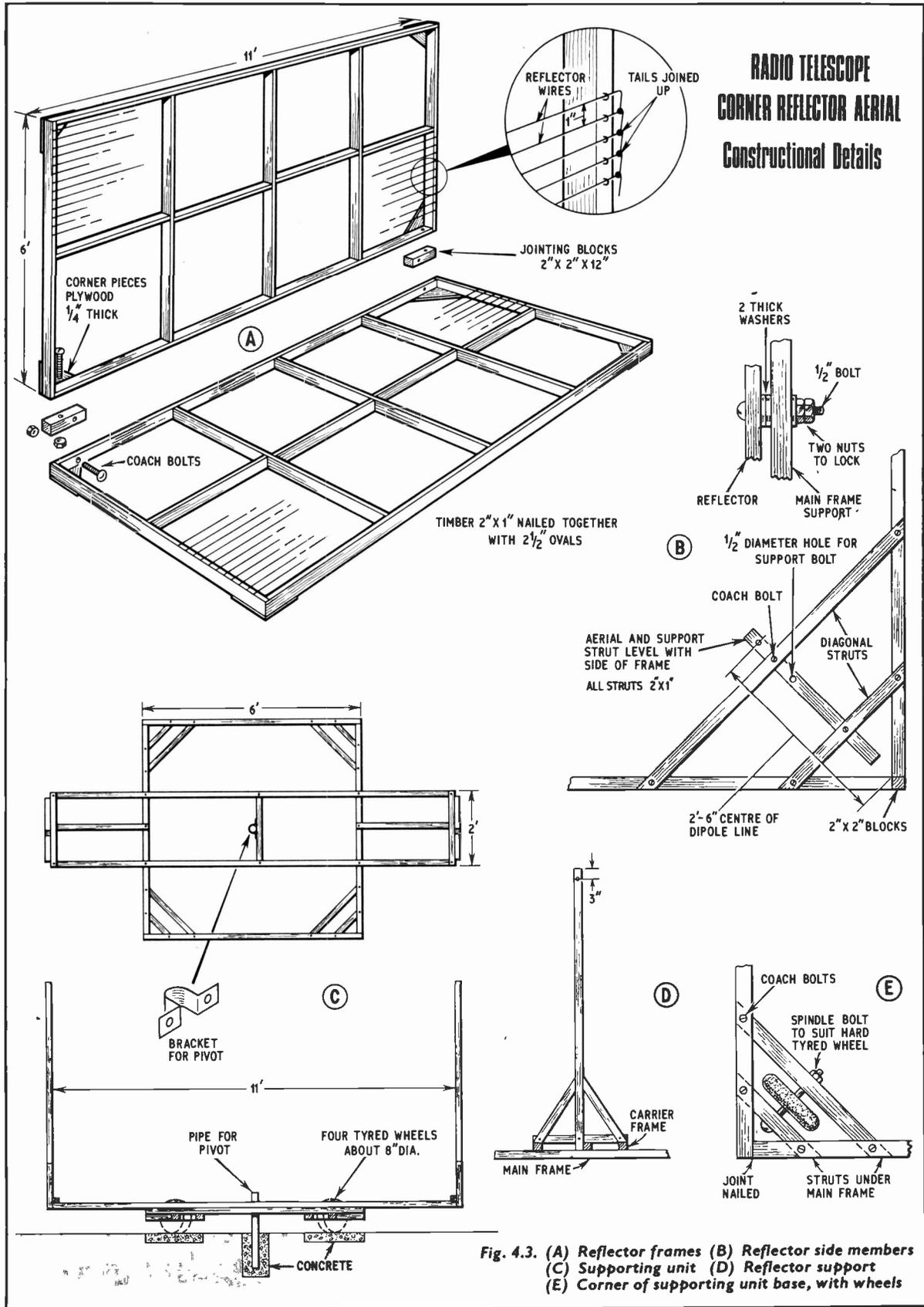


Fig. 4.3. (A) Reflector frames (B) Reflector side members (C) Supporting unit (D) Reflector support (E) Corner of supporting unit base, with wheels

SUPPORTING UNIT

The next task is to make the supporting unit which can be made in either of two forms—fixed or steerable. The basic construction is the same in both cases and is shown in "C". The material used is 2in by 2in timber and the assembly consists of a base and frame-support system. The base is made 6ft by 6ft with corner diagonal members which will serve as supports for the wheels (see "E") as well as providing rigidity for the base frame. If the unit is not to be steerable in azimuth then the wheels can be omitted.

On this base is mounted the aerial support system which is a sub-frame with vertical supports for the reflector, see "D". Again the material used is 2in by 2in timber. Detailed measurements are given in the diagrams.

For main assembly work coach bolts are used as far as possible since these will weather well, make for easy assembly, or if necessary allow easy dismantling for future modification.

If the aerial is to be steerable it is preferable that the wheels should run on a solid surface. Ideally this would be of concrete about 2in thick or, alternatively, concrete paving units could be used provided the base on which they are laid is carefully prepared, see "C". Cost-wise concrete would be the better choice.

If it is decided to make a permanent base and the project is to be carried through to the later developments of the interferometer where a second aerial unit will be required, then place the first unit on the east-to-west base line at one end of the line.

An alternative method of mounting the reflector, which again can be fixed or steerable, is shown in the photograph on page 467 (Part 1 of this series). This arrangement will provide scope for those who prefer to work in materials other than wood. The foundation for the steerable unit is much simpler than for the four wheel system of the first design, described above.

FOLDED DIPOLES

The frequency chosen will enable two dipoles to be used and in order to make the system as efficient as possible folded dipoles will be used. It was stated that the optimum distance from the apex would be 0.35 wavelengths and that this would give an impedance of 72 ohms. As two aerials are to be used

it will be better to make these folded dipoles to take advantage of the increase in impedance that these will provide. By doing this the system can be properly matched and balanced.

A dipole is naturally a balanced system, and the use of coaxial cable to make connections makes it unbalanced. It might be thought that because it is common practice to use coaxial cable for connection between the television aerial and the receiver, that this is also a satisfactory arrangement for radio astronomy. This is not so because the level of signal that is available for television is much greater than that which is received from extra terrestrial sources.

BALUN TRANSFORMER

It is however possible to use coaxial cable for part of the system. In order to do this a balance to unbalance transformer known as a "balun" is used to connect an unbalanced system to a balanced system and vice versa.

To connect the folded dipole to standard 75 ohm cable the "balun" shown in diagrammatic form in Fig. 4.4 will be used. This is a 4-1 step down in impedance and provides a balanced connection at the dipole. Details of the construction are given in Fig. 4.5. The centre core of the coaxial feeder is connected to a half-wave length of cable in a special way. The outer braid of the cable ends are all connected together as closely as possible.

The inner of the main cable and inner of the nearest end of the half-wave section are connected together and to one side of the dipole. The inner of the other end of the half-way section is connected to the other side of the dipole. No connection is required to the outer of the coaxial cable at the dipole end of the system. The other end of the main coaxial lead matches the unbalanced termination at 75 ohms.


CONNECTING THE DIPOLES

The dipoles can be either of the following types.

They can be made up from copper wire of about 14 s.w.g. The wire should be hard drawn copper, or cadmium copper. This is necessary because there will be considerable strain on the dipoles if they are to remain in the focal line of the reflector without sagging.

Alternatively, the standard commercial folded dipole as used for television can be employed. In this case the dipole can be supported by an aluminium tube of about 0.5in diameter, from the apex of the reflector.

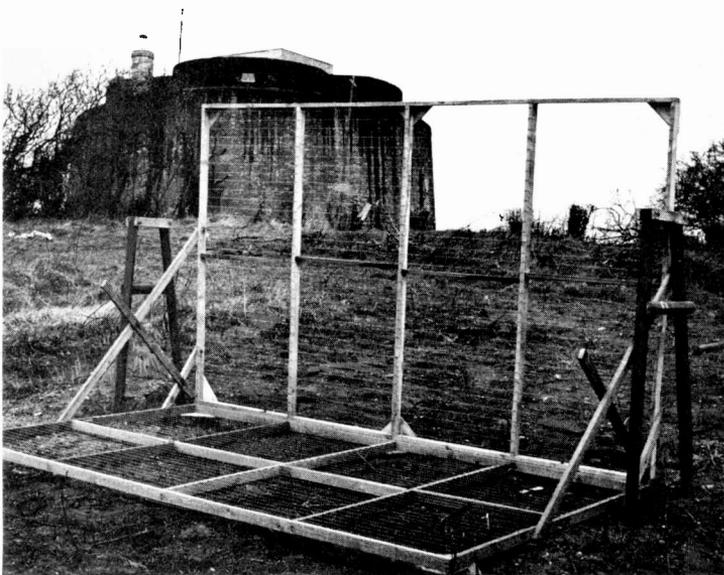The "balun" on each dipole and the coaxial lead should go straight to the apex of the reflector and the lead taken through without touching the wires of the reflector screen. The free ends of the two cables will be matched to the 50 ohm quarter-wave section which will, in turn, be plugged into the preamplifier. See Fig. 4.6.



A corner reflector aerial built by the author. Note that the side supports are of a different style to those in the described design


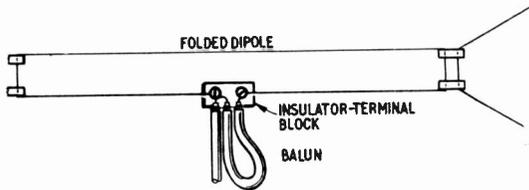



Fig. 4.4. A balance to unbalance transformer or "balun" connected to a dipole

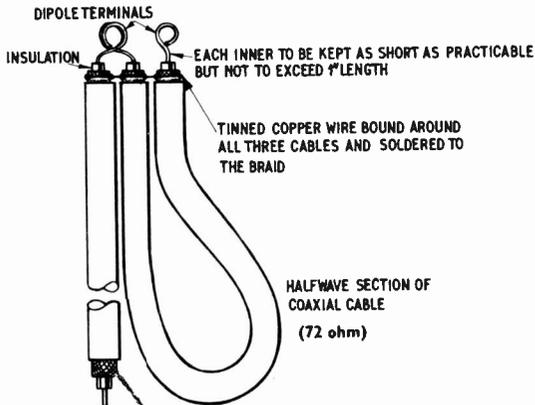

NOTE: The length of the halfwave section will depend on the type of cable insulation :

$$\begin{aligned} \text{Solid polythene} &= \frac{\text{wavelength} \times 0.65}{2} \\ \text{Cellular polythene} &= \frac{\text{wavelength} \times 0.86}{2} \\ \text{Air-spaced} &= \frac{\text{wavelength} \times 0.9}{2} \end{aligned}$$

Fig. 4.5. Constructional details of the balun

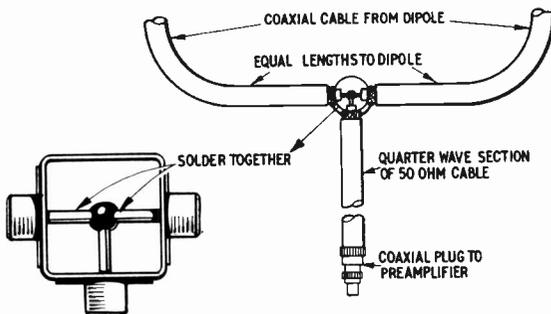

CONNECTING BOX SUFFICIENTLY SMALL TO ALLOW COAXIAL SOCKET TAILS TO MEET

Fig. 4.6. Connector of two dipoles to the 50 ohm cable

If wire dipoles are used then a wood support reaching nearly to the dipoles will help to support the balun and cable. The dipoles themselves are supported in the reflector framework between the diagonal struts by means of nylon cords. The assembly of the two dipoles is shown in Fig. 4.7.

If the commercial type of dipole is used then balun and cable can be taped to the tube support.

ASTRONOMICAL TERMS

During this article the terms azimuth and altitude have been used. Though no doubt many will be familiar with these terms it may be of interest to give a short summary of the use of them. They are the coordinates by which the position of a celestial object may be indicated. A diagram of the system is shown in Fig. 4.8.

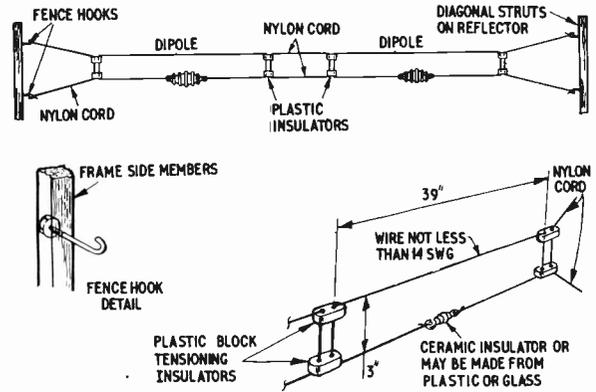


Fig. 4.7. Details of the dipole assembly and mounting

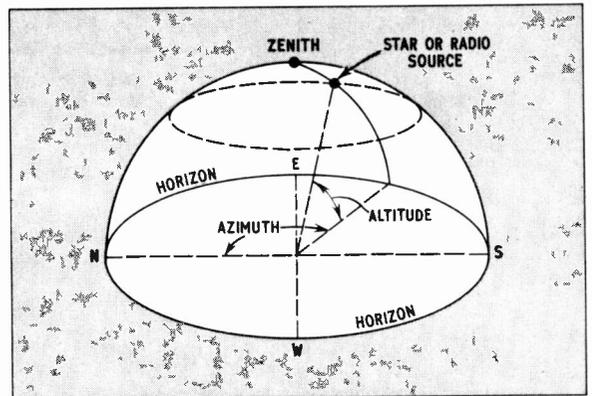


Fig. 4.8. Illustrating the meaning of the terms Azimuth and Altitude

AZIMUTH

This is the distance measured on a horizontal circle which coincides with the visible horizon. It is measured usually from North in degrees through East (90°), South (180°), West (270°), thence up to North again (360°). The logging of a position, for example, would read "Azimuth 202°."

ALTITUDE

This is the distance from the horizon up to the position of the object observed. The greatest altitude is 90° therefore the logging in this case might be "Altitude 52°". This greatest altitude is called the Zenith.

The altazimuth system is known as the Horizon System of Coordinates. It is used where the aerial system in radioastronomy is steerable in these terms and the position so obtained is translated into other celestial coordinates such as equatorial or galactic. Where large radio telescopes are involved it is usual to have direct computerised conversion of altazimuth to the other system of equatorial coordinates, in order that the telescope is kept continuously pointing to the correct position.

Altazimuth coordinates are used mostly for the location of artificial satellites where it is necessary to follow their path.

Next month: The receiver set-up and recording methods will be described, and some elementary Solar Astronomy will be discussed.



PART TWO

SEISMOGRAPH

BY D. BOLLEN

An instrument for the detection and graphing of earth tremors

THIS month constructional details for a 1Hz vertical seismograph are given together with installation and operating instructions.

A 1HZ VERTICAL SEISMOMETER

The spring pendulum seismometer of Fig. 9 is based on a welded mild steel frame. It might be possible to persuade a garage proprietor to weld the frame and also tap threaded holes in the baseplate, but if not, the frame could be built of well seasoned oak. Compared with many other seismometers, the spring pendulum type is one of the easiest to set up and operate.

Any old spring will not do for the seismometer as it must be near zero length. If the turns of a zero length spring were without thickness it would shrink to nothing when untensioned. Of course, an actual spring will only contract to the position where the wire turns touch. Some springs can have a theoretical negative length, depending on how they are wound.

To determine the spring length, tension it with various weights, measure the extension given by each weight, and then plot weight against extension on a graph. When the resulting straight line is projected it should pass through, or close to, the zero co-ordinates.

A spring of the dimensions specified in Fig. 9 can be obtained from most large ironmongers, but it is advised that several should be purchased so that one may be selected which has a zero or negative length.

A negative length spring can be converted to zero length by altering the spring adjuster.

Magnets for the transducer are taken from dismantled loudspeakers. The small bar magnet taped to the seismometer boom, above the calibrating coil, will impart a small force to the boom when the calibrating coil is energised by a 1Hz sine wave input. Approximately 1 millivolt r.m.s. in the coil will produce a zero-peak deflection of 50 nanometers.

The thin leads from the transducer coils are threaded through the hollow boom, and can be terminated by soldering them to a tag strip mounted on the upright section of the frame. Coil the transducer wires so that they do not interfere with the free movement of the seismometer boom.

To make up the seismometer mass, obtain a length of 2in inside diameter cardboard tube and glue this to a cardboard base. Insert and glue in position a dowel of the same diameter as the boom tube, then melt down 2lb of lead and pour this into the mould.

WINDING TRANSDUCER AND CALIBRATING COILS

A bobbin for the transducer coil, shown in Fig. 10, is made up from two 2½in square thin sheets of s.r.b.p., and a 1in × 1in × ¼in plywood former. Make sure that the corners of the former are rounded off, and edges smoothed, before glueing on the s.r.b.p. sides.

Drill a hole in the centre of the bobbin for mounting on a mandril in the chuck of a hand drill. With a sharp spike, make a hole in one s.r.b.p. side to admit L1 start lead. Solder some thin red insulated wire to the 40 s.w.g. enamelled wire and push through the spiked hole. Secure and insulate the joint with a layer of plastics insulating tape.

Wind on 2,000 turns of 40 s.w.g. wire for L1 then make another spiked hole and terminate this winding with a short length of green insulated wire. Insert the wire through the hole and insulate and secure with plastics tape.

A similar procedure is followed for the L2 winding, except that this consists of 500 turns of 40 s.w.g. wire, and has a blue start lead and a green finish lead. Finally, use more plastics tape to protect the windings and transducer bobbin.

A piece of s.r.b.p. or gummed paper tube is glued to one edge of the transducer bobbin to make a push fit mount on the end of the seismometer boom. A hole is drilled to admit the transducer leads.

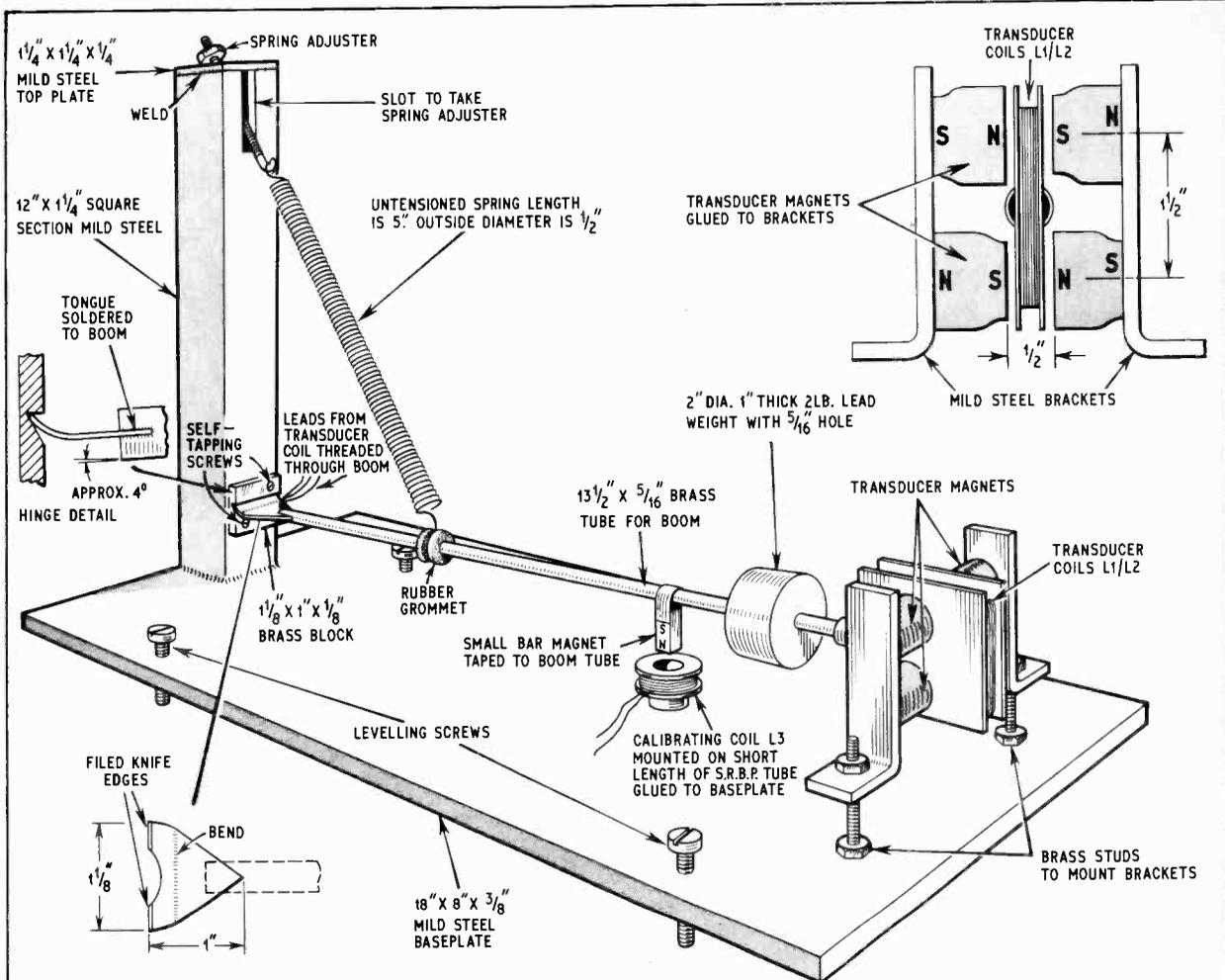


Fig. 9. Constructional details of 1Hz vertical seismometer


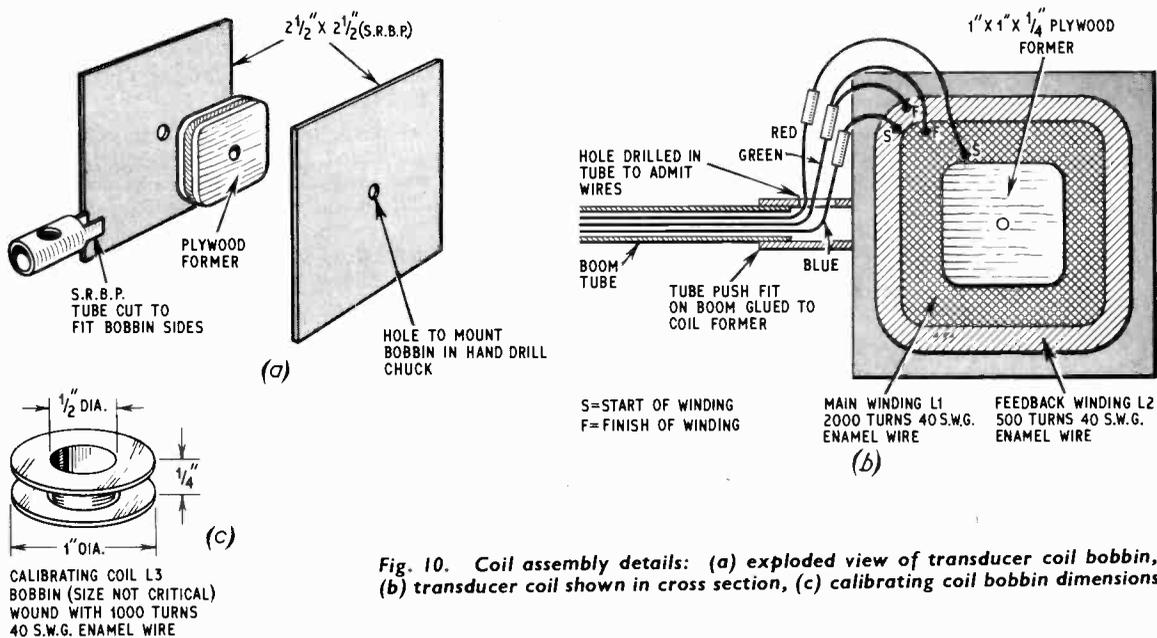


Fig. 10. Coil assembly details: (a) exploded view of transducer coil bobbin, (b) transducer coil shown in cross section, (c) calibrating coil bobbin dimensions

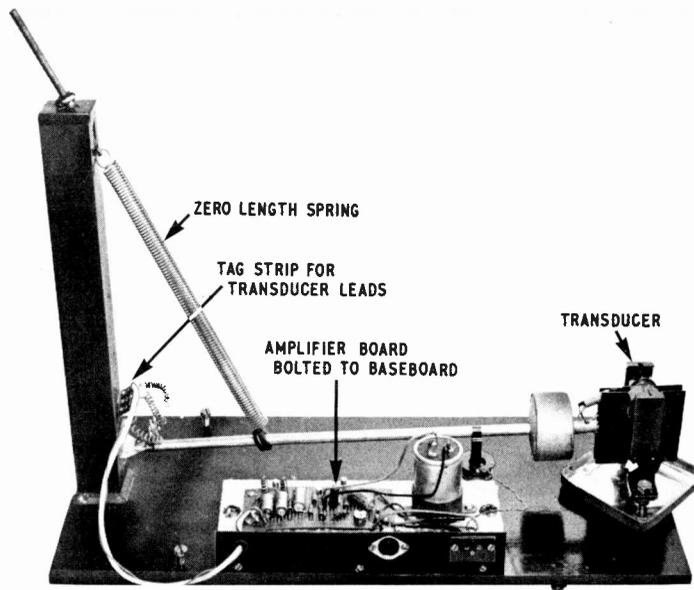

The calibrating coil dimensions are not critical, and the small bar magnet does not have to enter the hole in the centre of the calibrating coil. An LA5 pot core bobbin, or a former of approximately the same shape and size, can be wound with approximately 1,000 turns of 40 s.w.g. enamelled wire to make the transducer coil L3.

CONSTRUCTING THE SEISMOMETER AMPLIFIER

For the seismometer amplifier, prepare a piece of 0.1in matrix Veroboard 19 holes wide by 43 holes long, with copper strips running parallel to the longest side. Drill holes to take panel mounting screws, enlarge the holes for VR1 tabs, and make breaks in the copper strips, see caption Fig. 11.

Insert and solder all terminal pins and proceed with mounting all components, except R2. Take particular care not to overheat transistors TR1 and TR2.

TESTING

To test the seismometer amplifier module for wiring or component faults, solder a 470 ohm resistor temporarily across the terminal pins to which the red and green leads from the transducer coil will later be attached.

Connect the orange and black leads to the module panel as in Fig. 11, and ignore the remaining terminal pins.

Wire the orange lead to the positive terminal of a 12V battery, and the black lead to the negative terminal.

Check the potential between the collector and emitter of TR1 using a 20 kilohm/volt meter. If significantly lower than 0.9V, disconnect the battery and add resistor R2; this should increase the TR1 collector emitter voltage to near the required value. If necessary experiment with the value of R2.

Where the TR1 voltage is found to be much higher than 0.9V, when R2 is absent, the transistor may be faulty.

Now check the voltage between the collector of TR2 and the negative battery terminal. Any serious departure from five volts will probably indicate either a faulty transistor, a wiring error, or abnormally high leakage in C3.

PEN AMPLIFIER CONSTRUCTION AND TESTING

The pen amplifier module is based on a 0.1in matrix Veroboard 19 holes wide by 57 holes long, with copper strips running parallel to the longest side. Drill holes to take the panel mounting screws,

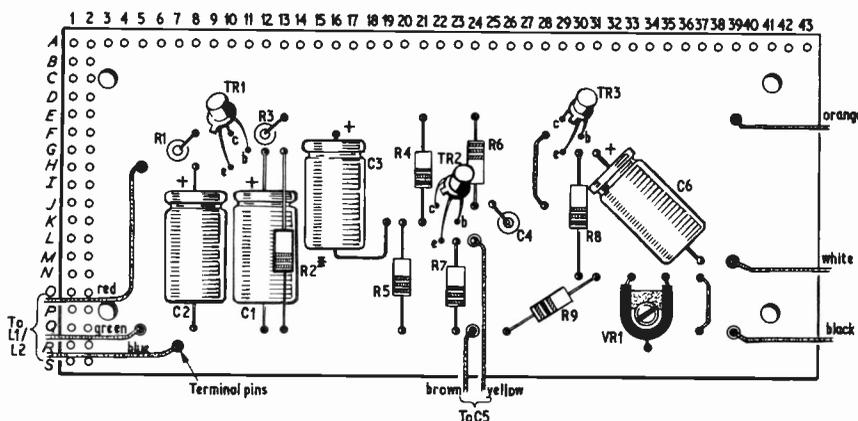


Fig. 11. Assembly and wiring details of seismometer amplifier. Cut copper strips at the following: B4; B40; C4; C40; D4; D40; F18; G14; H14; N34; O5; O40; P5; P40; R5; R40

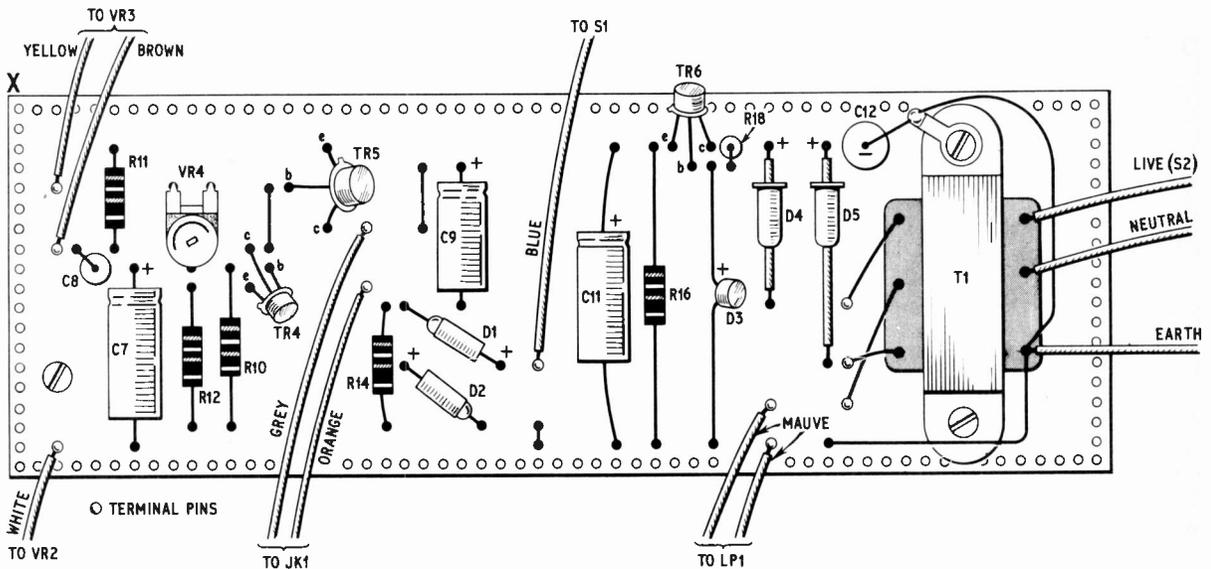


Fig. 12. Assembly and wiring details of pen amplifier. Cut copper strip at following holes: B48; C36; C48; D27; D48; E10; E11; E48; K27; M6; N6; N30; O6; O48; P6; P48; Q48; R9; R48

the miniature mains transformer mounting screws, and enlarge holes for VR4 tabs.

Make breaks in the copper strips as listed in the caption of Fig. 12, and insert all terminal pins before wiring up other components.

Make a preliminary check on the pen amplifier module as follows. Temporarily wire a six volt, 60mA bulb across the terminal pins identified by mauve leads in Fig. 12. Connect a mains lead to the appropriate pins on the miniature mains transformer T1.

Solder a one kilohm resistor across the grey and orange lead terminal pins, and connect a shorting link across the brown and yellow lead terminal pins.

When the mains input to T1 is switched on, look for a dull red glow from the lamp LP1. With the testmeter, check that the voltage across C11 is between 11V and 12V.

Apply the positive voltmeter lead to the grey wire terminal pin, and the negative lead to module earth. Adjust VR4 for a reading of around 6V.

If it is impossible to obtain a reading of 6V, there may be a wiring fault, or something wrong with TR4 or TR5.

INSTALLING THE SEISMOMETER AMPLIFIER

Although insensitive to slow changes of ambient temperature, the seismometer amplifier should be screened against thermal variations which lie within the frequency range of the seismograph, otherwise there will be an addition to the apparent overall noise level. Draughts can similarly produce spurious noise.

Thermal screening is achieved by placing the amplifier module inside a draught proof box which is lined with expanded polystyrene. In Fig. 13, board mounting and interwiring details are shown. Here the aluminium base plate provides a support for the polystyrene lined s.r.b.p. cover. Only the socket panel is shown. SK1 and SK2 are mounted by means of an 8in x 1½in s.r.b.p. panel attached to the side of the 8in x 3in x 1½in aluminium chassis.

A layer of expanded polystyrene is interposed between the top of the chassis, and the amplifier module and C5, to minimise thermal gradients. Leads from the seismometer transducer are taken through a grommet in the s.r.b.p. panel, to appropriate terminal pins on the module panel.


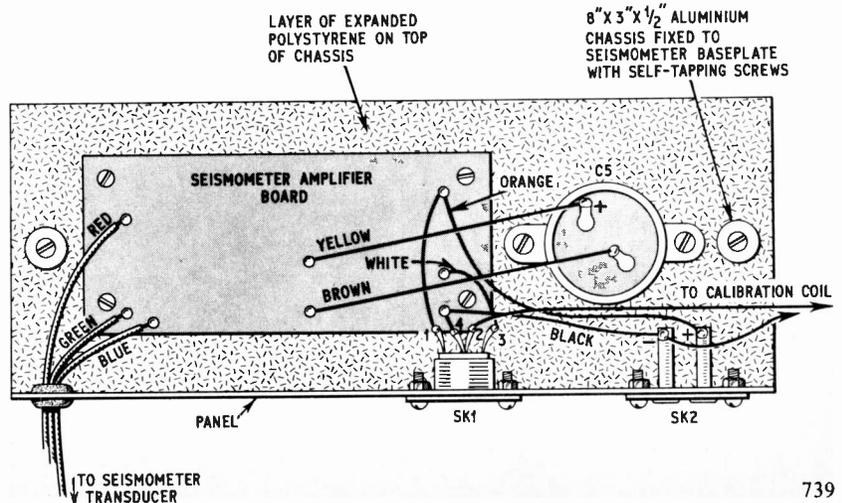


Fig. 13. Seismometer amplifier unit. After assembling the unit should be enclosed in hardboard lined with polythene to exclude draughts, and short term temperature changes

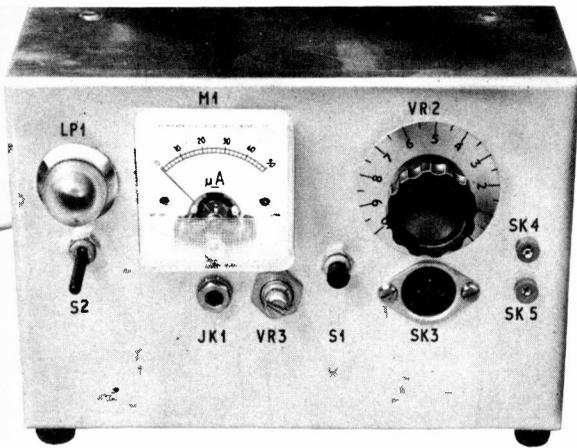

There is sufficient room on the baseplate of the seismometer to accommodate the complete seismometer amplifier and batteries on either side of the boom. The amplifier unit chassis can be fixed with two self-tapping screws. If desired, a battery box can be made up for BY1 and BY2.

CONTROL UNIT CONSTRUCTION

A 6in × 4in × 2½in aluminium chassis placed on its side will serve as a box for the control unit components, and can house the pen amplifier module.

After drilling the box front to take those components shown in Fig. 14, drill holes in the sides of the box to accept the pen amplifier module mounting screws, and mains lead grommet. Install all controls, sockets, and the amplifier module, then proceed with wiring up as shown.

CONSTRUCTING A DISC RECORDER

A prototype disc recorder which incorporates a bell warning circuit and a pen vibrator is shown in Figs. 15a and b. Disc recorder layout will depend on the types of turn-table motor used and on additional facilities.

A start can be made by selecting a suitable motor for one revolution per 24 hour operation. It is essential to have a slipping clutch drive of the type found in mechanisms taken from alarm clocks, electric wall clocks, or time switches.

Most time switches have a spindle with a threaded hole which can be easily adapted to take a turntable, but in the case of a converted clock, a threaded bush must be soldered to the hour hand cog as in Fig. 16a. If difficulty is experienced in making a suitable turntable and fixing it to the motor, try using an old gramophone turntable with a friction drive on the rim; this will also allow a bigger paper disc to be employed, and will give greater trace detail.

Mount the turntable assembly on a baseboard made of plywood or thick s.r.b.p., with space to spare for the pen relay RLA, and RLB and RLC if used (see Fig. 8).

RELAYS

All relays specified for the disc recorder are of the G.P.O. type 3000, with 1,000 ohm windings, operating on 6–12V. Modification details for RLA are given in Fig. 16b.

The pen arm is soldered to a 4B.A. solder tag which is held against the armature by a small pressure spring. The arm is free to move up and down, with the pen counterbalanced by a lead weight, but is driven horizontally by the movement of the armature; in this way the pen is free to follow surface irregularities of the paper and maintains a constant but light contact.


Remove RLA armature and glue two small squares of foam plastic, approximately ¼in × ¼in × ¼in thick, to the relay frame and polepiece, then replace the armature and mount the pen arm. If necessary, bend the relay contacts so that they are just open when the armature is naturally biased by the foam inserts.

Fix RLA to the baseboard beside the turntable and bend the pen arm until the resulting ink trace is in line with the turntable radius. The disc recorder in its basic form will now be ready for use.

EXTRA FACILITIES

It is useful to have some warning of the onset of a tremor when the seismograph is left operating

Fig. 14. Interwiring of control unit

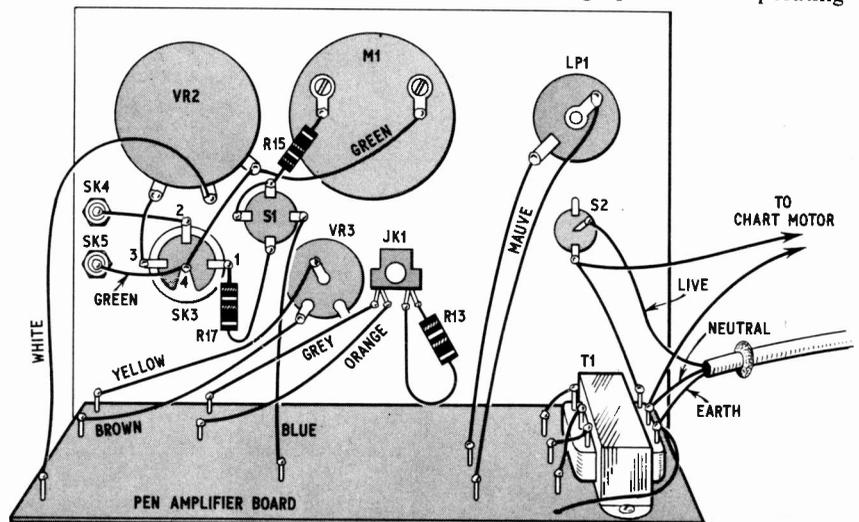

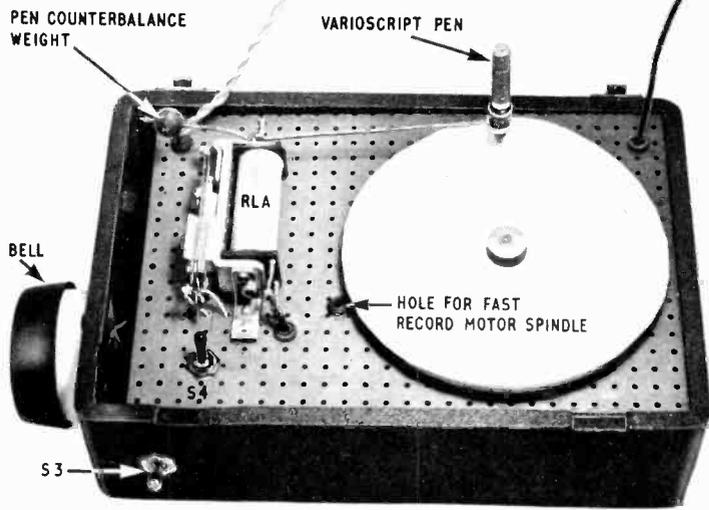


Fig. 15a. Top view of prototype disc recorder

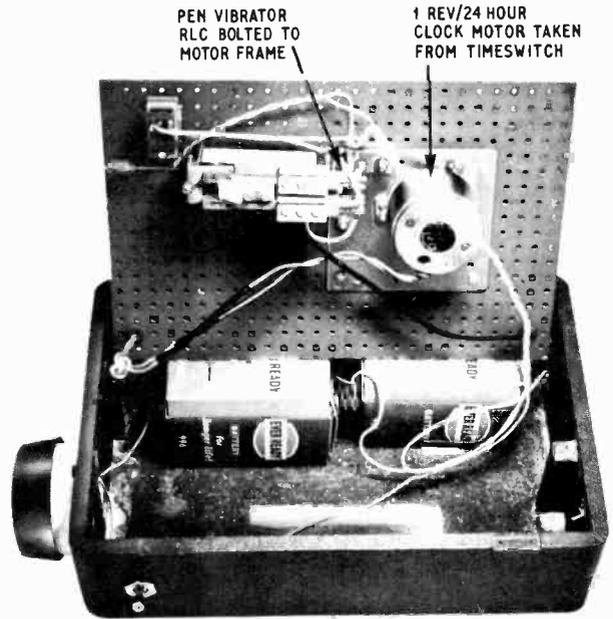
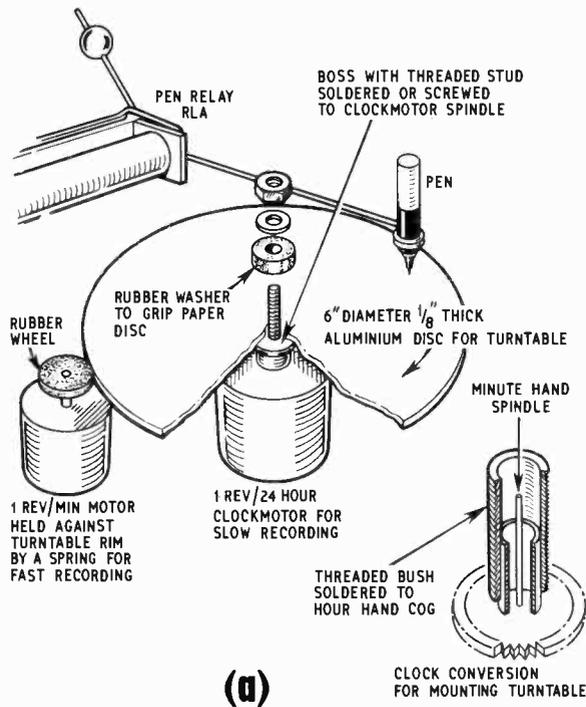


Fig. 15b. Underside of motor board

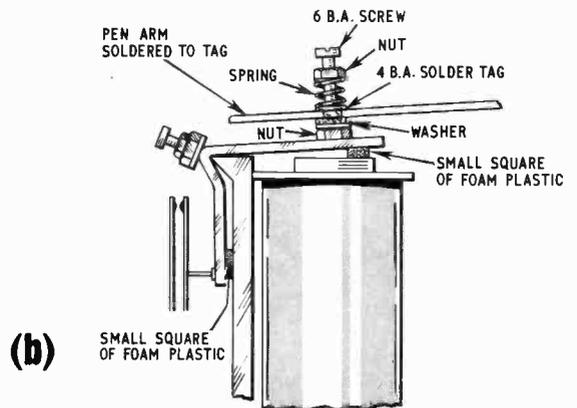
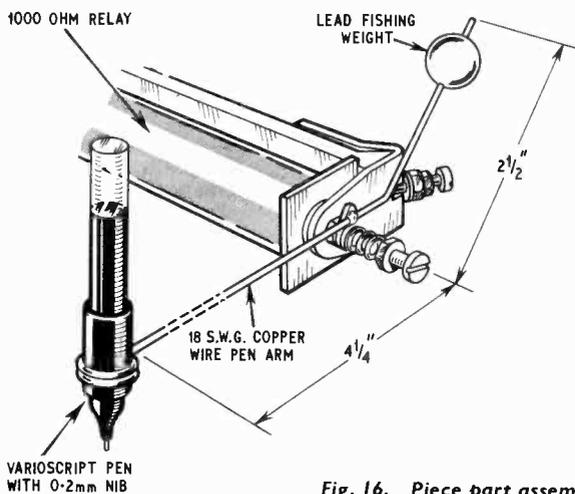


Fig. 16. Piece part assembly details for disc recorder

unattended, perhaps in a separate room. The simple bell circuit wired to the relay RLA contacts as in Fig. 8 can be quickly added to the basic recorder.

One of the bugbears of most pen recorders is unreliable inking. There is nothing more infuriating than finding that the pen has dried up just before the onset of an interesting event. To improve matters, the pen can be filled with watered down ink, but this gives a grey trace.

Further improvement results if the detachable nib is cleaned at the end of each 24 hour recording period, but this is a nuisance, and uses up valuable recording time.

The remedy is to employ a vibrator to keep the point of the nib bouncing up and down on the paper, and maintain a tiny pool of wet ink under the nib, without appreciably thickening the trace. A description of the vibrator has already been given, see also Fig. 8 and Fig. 15.

For triggered, expanded trace recording, a one revolution per minute synchronous motor can be arranged to rim drive the turntable approximately one revolution in every 36 minutes by means of a spring loaded $\frac{1}{2}$ in diameter rubber wheel.

A choice of motor speeds and friction wheel sizes will allow a wide range of recording speeds to be covered.

INSTALLING THE SEISMOMETER

An ideal seismometer site would be a deep pit excavated down to bedrock, somewhere in the middle of a large, unpopulated area of open countryside, devoid of trees, and at least one hundred miles from the nearest seashore. Of course, the ideal site is not available in the United Kingdom, and the best use must be made of available terrain.

In the centre of large towns built on chalk or clay, the "cultural" noise level will almost certainly mask all but the strongest tremors from distant events, but advantage can be taken of reduced human activity in the early hours of the morning. The seismograph will anyway be left running for 24 hours under normal circumstances.

The seismometer can be placed on a large concrete block which is let into the floor of a cellar, as this serves to couple it efficiently to the ground.

A suburban site could be based on a pit—or seismometer "vault" to use the correct term—dug in a garden. See that the pit is either well drained, or rendered completely waterproof with a lining of impervious concrete.

Although rural seismometer sites are obviously the best, the presence of trees can multiply the micro-seismic background noise at least three or four times when a high wind is blowing, and quarry shots have a perverse habit of turning up right in the middle of an interesting recording.

Training areas for the Armed Services are also situated in rural areas. Guns, bombs, depth charges, and sonic booms are all recorded faithfully by the seismograph.

Having decided upon and prepared a seismometer site, the instrument is installed and levelled with the aid of a spirit gauge. Make sure that the transducer coil is correctly aligned, completely free to move, and cannot touch the magnets.

A sharp increase in resonant frequency can be caused by minute whiskers of ferrous metal bridging the gap between magnets and coil. The remedy is to clean the magnets by wiping them with a piece of foam plastic.

A tin can placed over the transducer assembly, with a cut-away to clear the seismometer boom, will prevent dirt collecting on the magnets. It is advisable to protect and shield the seismometer with a heavy box cover of wood or metal, which is in turn covered by an old blanket to keep out drafts and loud noises.

TESTING THE SEISMOGRAPH

Connect the seismometer amplifier to the control unit. Adjust VR1 for minimum damping (slider earthed, and plug in the batteries. With gain control CR2 at zero, switch on the control unit, and wait for a minute or two for the circuits to settle down.

Advance VR2 while watching the zero-peak meter; the pointer should be seen to rise and fall rhythmically at the resonant frequency of the seismometer. If instead the pointer persistently goes to full scale, at low settings of VR2, and the panel lamp LP1 flashes, this will indicate instability.

The instability might have been caused by switch-on surges, in which case a 1.5V d.c. voltage injected into SK4 sockets should kill the unwanted oscillation, and return the seismometer amplifier to normal working.

To check the amplifier noise level, set VR2 to zero and clamp the seismometer transducer by inserting a thickness of cardboard between the coil and the magnets. Turn VR2 to maximum gain and observe the peak meter deflection, this should not exceed $4\mu\text{A}$ on the existing meter scale.

CALIBRATION

The seismologist is not necessarily concerned with the accurate measurement of ground motion amplitudes. Often it is enough to time the tremors, and merely compare relative trace amplitudes. Nevertheless, it is instructive to see how the seismometer responds to a well defined mechanical displacement and there are several methods of attempting this.

Perhaps the best technique is to place the seismometer on a special "shaking table", a precision engineered platform capable of being moved with great accuracy through small distances.

A simpler alternative more suited to the amateur is to impart a small motion to the seismometer boom by applying a known electromagnetic force.


An item of equipment needed for calibration is a sub-audio oscillator, tunable from about 0.5Hz–5Hz, with an output of at least 10V r.m.s., and having a switched attenuator covering 100dB or more.

An ordinary audio signal generator can sometimes be converted for sub-audio use by adding extra large capacitors to the frequency determining network, while at the same time increasing the value of all coupling, de-coupling, and smoothing capacitors to prevent distortion and loss of output at the lowest attainable frequencies.

The Heathkit AG-9U, for example, will work down to 0.1Hz after suitable modification.

To calibrate the 1Hz spring pendulum seismometer, attach a small pointer to the seismometer mass, arranged so that it moves up and down a millimetre scale. Temporarily short-circuit the red and green leads from the transducer coil L1 at the seismometer amplifier input, and make sure that the supply is disconnected.

electronics mastered!*

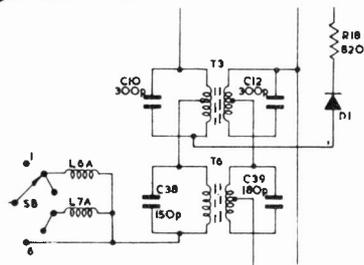

by our highly practical
BUILD, SEE & LEARN system

Step by step we take you through the apparent intricacies of electronics and show you how easily you can master the subject. Write for the brochure which shows, in full detail, how you can do it.

1

We provide a full range of components and sub-assemblies, with details of what they do, so that you learn to recognise all the 'bits and pieces'. Using some of these you are instructed in how to build this oscilloscope, simply and quickly.


2

You are shown how to read and understand circuit diagrams so that you can later build more advanced equipment or draw your own diagrams.


3

You can construct over 40 kits, including:—

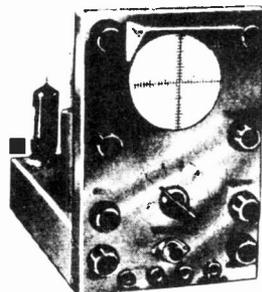- Valve experiments
- Transistor experiments
- Amplifiers
- Oscillators
- Signal tracer
- Photo electric circuit
- Computer circuit
- Basic radio receiver
- Electronic switch
- Simple transmitter
- a.c. experiments
- d.c. experiments
- Simple counter
- Time delay circuit
- Servicing procedures



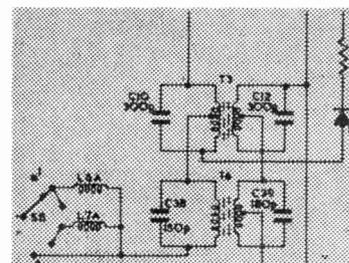This course has been designed to help even those who are complete newcomers to electronics. No Maths needed!



**POST NOW
FOR
FREE BROCHURE**

BLOCK CAPITALS PLEASE

To: British National Radio School, Reading, Berks.
Please send your free Brochure, without obligation, to:

NAME

ADDRESS

P.E.9

FREE

**SPECIAL ELECTRONIC GIFT
to all our Students POST COUPON NOW!**

SPECIAL PURCHASE!


BRAND NEW FM MULTIPLEX STEREO DECODER UNITS. Manufactured by PHILIPS. Size 2" x 3" x 1". All transistor 24V. at 6mA. Supplied pre-wired with full circuit diagram and connection details. £4 each. Post free.

FEW ONLY—LEAK MK I TRANSCRIPTION PICK-UP ARMS. Using the world famous gimbal pivot system. Complete but less pick-up head. £2-50. P. & P. 20p.

INPUT MATCHING TRANSFORMER. Beautifully made in heavy Mu-metal cylindrical case for minimum hum pick-up. Size 1 1/2" high x 1 1/4" dia. Ratio 150:1 approx. Especially suitable for matching dynamic or ribbon mikes or pick-up from low to high impedance or vice versa. 75p each. Post Free.

BLACK ANODISED 16g. ALUMINIUM HEAT SINKS. For TO3, complete with mica's and bushes. Size 2 1/2" x 3". 25p pair. P. & P. 5p.

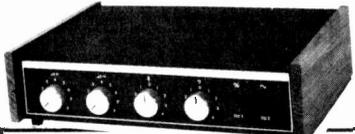HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



NEW IMPROVED MODEL WITH HIGHER OUTPUT AND INCORPORATING HIGH QUALITY READY DRILLED PRINTED CIRCUIT BOARD FOR EASY CONSTRUCTION

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Output stage for any speakers from 5 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled printed circuit board, attractive front panel, knobs, wires, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output 14W r.m.s. per channel into 8 ohms. Frequency response +3dB 12-30,000Hz. Sensitivity better than 80mV into 1MΩ. Full power bandwidth +3dB 12-15,000Hz. Bass boost approx. to -12dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 35V at 1.0 amp. Overall size 7 1/2" wide x 6 1/2" deep.


Fully detailed stage construction manual and parts list free with kit or send 18p plus large S.A.E. **PRICES AMPLIFIER KIT £10-50 P. & P. 15p. POWER PACK KIT £3 P. & P. 30p. CABINET £3 P. & P. 30p.**

(Post Free if all units purchased at same time). Full after sales service. Also available ready built and tested, £20-50. Post Free.

Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc.) and will then perform mixing and fading facilities for medium powered Hi-Fi Discosqueue use, etc.

SPECIAL PURCHASE OF MANUFACTURER'S SURPLUS

All Transistor P.M. tuner head with twin A.M. Gang incorporated. Beautifully engineered with precision geared reduction drive. F.M. R.F. Transistor, oscillator/Mixer and first I.F. stage (10.7 Mc/s output) with optional AFC connection. Built on printed circuit panel and fully screened. Extremely stable over range 65-108 Mc/s. Brand new and pre-aligned. Size 2 1/2" H. x 1 1/2" W. x 2 1/2" D. For 6V D.C. at 2.8mA. A.M. Gang fitted with trimmers which can be connected to standard A.M. aerial and oscillator circuits if required. **LIMITED NUMBER. Only £2-25 post free.** Connection details supplied.

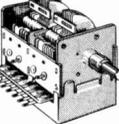

HIGH GRADE COPPER LAMINATE BOARDS 8 x 6 x 1/4 in. FIVE for 50p. P. & P. 13p.

TELESCOPIC AERIALS WITH SWIVEL JOINT. Can be angled and rotated in any direction. 6 section Lacquered Brass. Extends from 6in. to approx. 22 1/2 in. Maximum diameter 1/4 in. 25p each. P. & P. 5p.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-240V. Secondary combinations: 0-6-10-15-20-25-30-35-40-60V half wave at 1 amp or 10-0-10, 20-0-20, 30-0-30V, at 2 amps full wave. Size 3inL x 3 1/2inW x 3inD. Price £1-75. P. & P. 30p.

MAINS TRANSFORMER. For transistor power supplies. Pri. 200/240V. Sec. 0-5-9 at 300mA. 70p. P. & P. 13p. Pri. 200/240V. Sec. 12-0-12 at 1 amp. 85p. P. & P. 13p. Pri. 200/240V. Sec. 10-0-10 at 2 amp. £1-38. P. & P. 30p. Tapped Primary 200-220-240V. Sec. 21-3V at 300mA. 65p. P. & P. 13p.

Open 9-5.30 Monday to Saturday
Early closing Wed. 1 p.m.
A few minutes from South Wimbledon Tube Station

SPECIAL OFFER!! HI-FI LOUDSPEAKER SYSTEM

Beautifully made teak finish enclosure with most attractive Tygan-Vynair front. Size 16 1/2 in high x 10 1/2 in wide x 3 1/2" deep. Fitted with E.M.I. Ceramic Magnet 13in x 8in bass unit, two H.F. tweeter units and crossover. Power handling 10W. Available 3, 8 or 15 ohm impedance.

Our Price £8-40 Carr. 65p.
CABINET AVAILABLE SEPARATELY £4-50. Carr. 60p.

Also available in 8 ohm with EMI 13in x 8in. bass speaker with parasitic tweeter. £6-50. Carr. 65p.

LOUDSPEAKER BARGAINS

3in 4 ohm 50p. P. & P. 15p. 5in 3 ohm 80p. P. & P. 15p. 7 x 4in 3 ohm £1-05. P. & P. 20p. 10 x 6in 3 or 15 ohm £1-90. P. & P. 30p. E.M.I. 8 x 5in 3 ohm with high flux magnet £1-62. P. & P. 20p. E.M.I. 13 1/2 x 8in 3 ohm with high flux ceramic magnet £2-10 (15 ohm £2-25). P. & P. 30p. E.M.I. 13 x 8in, 3 or 8 or 15 ohm with two inbuilt tweeters and crossover network £4-20. P. & P. 30p. E.M.I. 13" x 8" twin cone (parasitic tweeter) 8 ohm £2-25. P. & P. 30p.

BRAND NEW. 12in 15w H/D Speakers, 3 or 15 ohm. Current production by well-known British maker. Now with HiLux ceramic ferrobat magnet assembly. £5-50. Guitar models: 25w £6-50, 35w £8-50. P. & P. 35p each.

E.M.I. 3 1/4in HEAVY DUTY TWEETERS. Powerful ceramic magnet. Available in 3, 8 or 15 ohm 88p each. P. & P. 13p.

12in "RA" TWIN CONE LOUDSPEAKER 10 watts peak handling, 3 or 15 ohm, £2-20. P. & P. 30p. 35 ohm SPEAKERS 3". £1-05. P. & P. 13p.

VYNAIR & REKINE SPEAKERS & CABINET FABRICS app. 5 1/2 in. wide. Usually £1-75 yd., our price 75p yd. length. P. & P. 15p (min. 1 yd.). S.A.E. for samples.

HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexifoam earmuffs. Wired and fitted with standard stereo 1/4 in jack plug. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. **PRICE £2-95.** P. & P. 15p.

SINGLE HEADPHONE. With aluminium headband. Approx. 200 ohm. 25p. P. & P. 8p.

CRYSTAL MIKES. High imp. for desk or hand use. High sensitivity. 95p. P. & P. 8p.

HIGH IMPEDANCE CRYSTAL STICK MIKES. OUR PRICE £1-05. P. & P. 8p.

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER. For P.U. Tape, Mike, Guitar, etc., and suitable for use with valve or transistor equipment. 9-18V. Battery or from H.T. line 200/300V. Frequency response 15Hz-25KHz. Gain 20dB. Solid encapsulation size 1 1/2 x 1 1/2 in. Brand new—complete with instructions. Price 88p. P. & P. 13p.

BRAND NEW E.M.I. LIGHTWEIGHT PICK-UP ARM WITH ARM REST. Fitted mono to stylus and cartridge for LP/78, ONLY £1. P. & P. 8p.


QUALITY RECORD PLAYER AMPLIFIER MK II

A top quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. w. x 3 1/2 in. h. 6h. Ready built and tested. **PRICE £3-75.** P. & P. 40p. **ALSO AVAILABLE** mounted on board with output transformer and speaker ready to fit cabinet below. **PRICE £4-88.** P. & P. 60p.

DE LUXE QUALITY PORTABLE R/C CABINET MK II 1/2 cut motor board size 14 1/2 in. clearance 2 1/2 in. below. 5 1/2 in. above. Will take above amplifier and any B.S.R. or GARRARD changer or Single Player (except AT60 and SP25). Size 18 x 15 x 8in. **PRICE £3-98.** P. & P. 60p.

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements with output transformer and speaker to follow each other. Fully shrouded section wound output transformer to match 3-15Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and E280 rectifier. Simple instruction booklet 15p (Free with parts). All parts sold separately. ONLY £7-97. P. & P. 55p. Also available ready built and tested complete with std. input sockets, £9-97. P. & P. 65p.

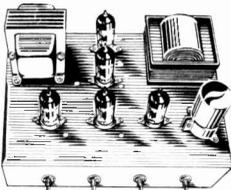

BRAND NEW TRANSISTOR BARGAINS. GET 15 (Matched pair) 75p; V15/10p, 50p; OC71 25p; OC76 30p; AF17 15p; 3C539 (NPN) 15p. Set of Mullard's sold separately. ONLY £7-97. P. & P. 55p. Also available ready built and tested complete with std. input sockets, £9-97. P. & P. 65p.


SPECIAL PURCHASE!

SPEAKER CABINET FROM FAMOUS MAKER!

Beautifully made all-wooden construction cabinet with medium walnut finish front, gold anodised expanded aluminium grille and dark sides. Approx. size overall 11 1/2" high x 5" deep x 13 1/2" wide at base. Easily removable handle cut out for 6 1/2" speaker. Fibre board back. Could accommodate amplifier or radio together with speaker. An expensively made cabinet at a give-away price.

LIMITED NUMBER ONLY £1-38 Post Free.

DE LUXE STEREO AMPLIFIER

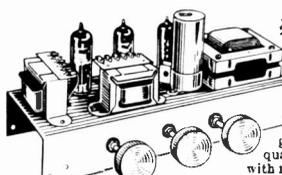

a.c. mains 200-240 volts. Using heavy duty fully isolated mains transformer with full wave rectification giving adequate smoothing with negligible hum. Valve line up—2 x ECL86 Triode Pentodes. 1 x E280 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate "balance" control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume level to be used with negligible distortion. Supplied complete with knobs, chassis size 11in. w x 4in. x 6in. Overall height including valves 5in. Ready built and tested to a high standard. **Price £2-92.** P. & P. 45p.

4-SPEED RECORD PLAYER BARGAINS

Mains models. All brand new in maker's packing. **LATEST B.S.R. C109/A21 4-SPEED AUTOCHANGER.** With latest mono compatible cartridge £6-87. Carr. 50p. With stereo cartridge £7-97. Carr. 50p. **SUITABLE PLINTH UNIT FOR ABOVE** with rigid plastic cover. £5-75 complete. P. & P. 50p.

LATEST GARRARD MODELS. All types available 1025, 2025, SP25, 3000, AT60, etc. S.A.E. for Latest Prices! **FLINTH UNITS** cut out for Garrard Models 1025, 2025, 2000, 3000, 3500, etc. With rigid transparent plastic cover. Special design enables above models to be used with cover in position. Also suitable for housing AT60 and SP25. **OUR PRICE £5-75 complete.** P. & P. 50p.


LATEST ACOG GP91/13C Mono Compatible Cartridge with 1/4" stylus for 1/4" EP/78. Universal mounting bracket. £1-50. P. & P. 5p.

SONOTONE STAHC COMPATIBLE STEREO CARTRIDGE T/O stylus. Diamond Stereo LP and Sapphire 78. ONLY £2-50. P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. £3. P. & P. 10p.

LATEST RONETTE T/O Stereo Compatible Cartridge for EP/LP/Stereo/78. £1-65. P. & P. 10p.
LATEST RONETTE T/O Mono Compatible Cartridge for EP/LP/78 mono or stereo records on mono equipment. £1-50. P. & P. 10p.

3-VALVE AUDIO AMPLIFIER HA34 MK II

Designed for Hi-Fi reproduction of records, A.C. line operation. Ready built on plated heavy gauge metal chassis, size 7 1/2 in. x 4 1/2 in. x 4 1/2 in. Incorporates ECC83, EL84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £4-75. P. & P. 35p.

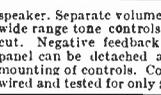

H/L "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. £3-98. P. & P. 40p.

HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. AC mains 200/240V. Supplied absolutely Brand New, completely wired and tested with good quality output transformer. **FEW ONLY.**

OUR ROCK BOTTOM BARGAIN PRICE £2-75 P. & P. 35p.

HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES

A must for servicemen and home constructors, 1971 edition including many 1000's of British, U.S.A., European and Japanese transistors. ONLY 40p. Post 5p.

HARVERSON SURPLUS CO. LTD.

170 HIGH ST., MERTON, LONDON, S.W.19 Tel. 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

Inject a 1Hz sinusoidal signal of about 5V r.m.s. into the calibration coil L3, via sockets SK4 and SK5 on the control unit front panel.

With the help of another person, tune the oscillator for maximum deflection of the seismometer boom, and then adjust the oscillator output voltage until the seismometer mass is swinging through a vertical distance of 1 millimetre. Carefully note the exact oscillator voltage required to give the above deflection, then switch off the oscillator.

Remove the short circuit from the transducer leads and re-connect the supply. Advance VR2 to make sure that the seismometer is now responding correctly to microseisms, with VR1 set for minimum damping.

With VR2 turned down low, attenuate the previous oscillator output voltage by 80dB and inject this signal into SK5. Adjust the oscillator frequency control for maximum deflection of the zero-peak meter; this is because the seismometer may not have the same point of resonance for very large and very small displacements. Since the original deflection was 1 millimetre peak-to-peak, or 0.5 millimetre zero-peak, the new seismometer deflection should be $0.5\text{mm} \times 10^{-4}$, or 50 nanometres.

Adjust VR2 for a full scale deflection of $50\mu\text{A}$ on the zero-peak meter, and make a note of the VR2 setting for future reference. The calibration obtained will be dependent on the amount of damping applied.

For other settings of VR1, re-calibrate, or prepare a response graph similar to Fig. 2 so that known settings of VR1 can be related to amplitude.

Another factor to be taken into account is that the calibration will only apply at the particular frequency used to deflect the seismometer boom, because the transducer is of the velocity type. It is a reasonable assumption that output will be related to amplitude in the undamped mode when the seismometer can only respond to a narrow band of frequencies centred at resonance.

OBTAINING RECORDINGS

Set VR2 to zero and insert the disc recorder jack plug into socket JK1 on the control unit front panel. Wait for a few minutes for the pen amplifier to settle down, and then adjust VR4 to position the armature of relay RLA at the mid-point of its travel.

Set up the pen, paper disc, and turntable rotation. Advance VR2 until the pen just moves in response to microseisms, and gives a slightly thickened trace. If necessary, re-adjust the pen zero by means of fine control VR3.

Leave the disc recorder running for several hours to check for reliable inking and pen deflection. At the same time, try injecting a range of frequencies from the test oscillator via SK5, to see how the complete seismograph responds to displacements of the seismometer mass.

SEISMOGRAMS

Four seismograms obtained with a simple disc recorder are given in Fig. 17.

A tremor from an epicentre a few hundred miles from the seismograph is depicted in Fig. 17a, recorded at a speed of one revolution every 24 hours. Seismogram Fig. 17b is the result of a rapid succession of small quarry shots at a distance of 6 miles (also clearly audible at the recording station); turntable speed one revolution every 36 minutes.

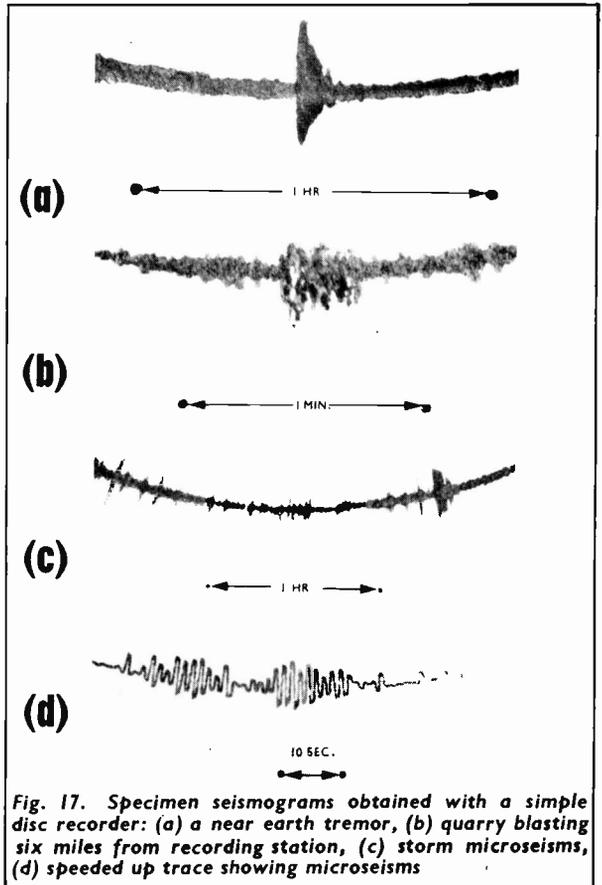


Fig. 17. Specimen seismograms obtained with a simple disc recorder: (a) a near earth tremor, (b) quarry blasting six miles from recording station, (c) storm microseisms, (d) speeded up trace showing microseisms

An approaching area of low pressure, accompanied by high winds produced the seismogram of Fig. 17c; the large amplitude deflections were caused by trees in the vicinity of the seismometer. The recording speed for this was the same as for Fig. 17a seismogram.

Finally, in Fig. 17d, a turntable rate of one revolution per minute gives a detailed record of microseisms, and shows the modulation effect which is sometimes referred to as "string of sausages".

Although not certain, the modulation may be caused by long period oscillations from the continental shelf being added to more local microseisms.

If a strip or helical chart recorder is available, having paper speeds of 10sec/cm or more, it can be connected to the seismograph control unit as shown in Fig. 18, to obtain more detailed recordings.

Serious seismological work demands the use of fast paper speeds with precise timing marks, to fix the arrival times of subsidiary waves reflected from crustal layers.

STRIP CHART RECORDINGS

The two seismograms in Fig. 19 are representative of traces given by a strip chart servo recorder.



Fig. 18. Circuit for feeding output from pen amplifier into an advanced recorder

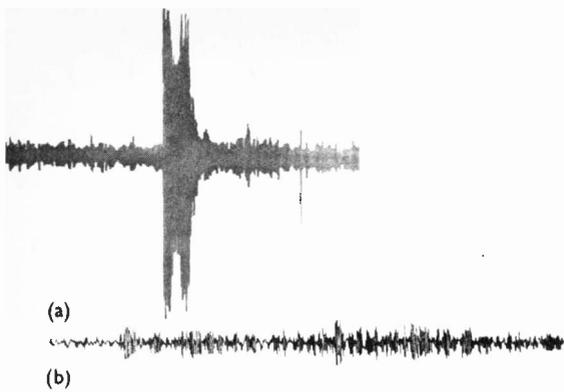


Fig. 19. Seismograms obtained with a strip recorder, (a) earthquake in the North Atlantic Ocean, (b) depth charge recorded at a distance of 250 miles

Fig. 19a is of a confirmed earthquake centred under the North Atlantic ridge, with minimum damping applied to the seismometer, and a fairly slow paper speed of 5.5min/cm.

Clearly shown here are the two peaks produced by the difference in arrival times of major P and S waves.

Fig. 19b gives a good general impression of seismograph sensitivity, and also shows the increase in detail resulting from a faster paper speed of 10sec/cm. To obtain this seismogram, frequencies below 1Hz were filtered out by reducing the value of C14 coupling capacitor (Fig. 18) to one microfarad. The input impedance of the chart recorder was ten kilohms

For this, the response of the seismometer was set to wide-band with near maximum damping, and the major recorded frequencies were in the region of 5Hz.

FILTERING

The seismograph response characteristic can, of course, be tailored to suit a particular situation.

If the main interest is the recording of teleseisms, that is events occurring some thousands of miles away, integrating capacitor C10 in Fig. 7 can be added to attenuate signals above 1Hz; this also partly corrects the inherent transducer response to yield an output more nearly related to amplitude over the full frequency range of the instrument, instead of velocity.

Quarry shots and other explosions can form a study in themselves, as seismic signals revealing something of the structure of the Earth's crust.

For all but explosions approaching nuclear magnitude, the frequencies generally encountered will lie above 1Hz. It will pay, therefore, to improve the signal to microseismic noise ratio by attenuating unwanted frequencies below 1Hz; simply achieved by reducing the value of C14, as was done for seismogram Fig. 19b.

To conclude this short introduction to the subject, the serious experimenter can find plenty of opportunity in the field of seismology for circuit development. Good sub-audio amplifiers, filters, and oscillators are scarce items. Equally, there are few seismological stations run by amateurs in the British Isles, despite the new impetus given to the subject by nuclear explosion detection and Moon quake recording. ★

NEWS BRIEFS

Sub Trainer

A NEW era in the training of Royal Naval submarine crews was signalled by the recent opening of a computer-based Submarine Command Team Trainer (SCTT) at HMS Neptune, the R.N. training establishment.

The SCTT system was developed jointly by the Ministry of Defence and the Electronic & Display Equipment Division of Ferranti Ltd. in Manchester, and is based on two Ferranti Argus computers.

The equipment is designed to train the submarine command team and crew in tactics and operations, and the various degrees of training available in the simulator system range from simple operator training to complex tactical exercises involving a number of target and escort vessels. Realistic simulations of sonar, radar, periscope, fire control and navigation systems are provided.

Lucas Looks Ahead

WITH the formation of an Electronics Product Group under Dr. John E. Maund, Lucas Electrical Limited intend to marry their undisputed engineering skill in automotive electrical systems with the more recent electronics and semiconductor technology and production capacity of their former Semiconductor Division.

This move was considered desirable in the face of a rapidly changing electronics market where integration in both i.c. and hybrid module form are foreseen as major expansion areas, and in particular the acceleration of automotive electronics technology, an area in which Lucas has made a significant contribution. This company sees a greatly expanded market in the future since electronic-based systems will become essential parts of modern cars as a move to meet the new safety and environmental requirements.

Apart from the automotive market, Lucas intends to increase its activities in other areas, including consumer electronics. To this end their recent distributor agreements with two large U.S. component manufacturers, Centralab Semiconductor and Quantrol Electronics, are significant. The optoelectronics market in particular is seen as a major expansion area in the future.

It is of interest to note that the entry of Lucas into the field of semiconductor manufacture started originally in 1955 when, faced with the difficulty of obtaining silicon semiconductors, they decided to develop and manufacture their own.

They achieved fame as the creators of the world's first 500V transistor.

A JOB WITH P.E.?

An unusual opportunity for an electronics enthusiast to enter technical journalism. There is a vacancy for an editorial assistant, age 20 to 30, on the staff of Practical Electronics. Keeness and ability to learn more important than previous experience in publishing.

Write, with brief details of career, to the Editor, Practical Electronics, Fleetway House, Farringdon Street, London, E.C.4.

MARKET PLACE

Items mentioned in this feature are usually available from electronic equipment and component retailers advertising in this magazine. However, where a full address is given, enquiries and orders should then be made direct to the firm concerned.

INSTRUMENT CASES

Keeping up with the range of instrument cases available on the market is becoming increasingly difficult for the designer and constructor of equipment.

Adding to this large selection of instrument cases available at present are three new ranges from **West Hyde Developments, Vero Electronics and McArdle and Brainsby**.

With the increase in popularity of anodised aluminium finishes, West Hyde have developed the "Brightcase" instrument case which can be either free standing or rack mounting. The external construction is of aluminium with the exception of the top and bottom panels which are made of black PVC coated steel.

The anodised side panels are held with button head socket screws, which can also be used to carry the rack mounting brackets.

All units come complete with front and back panels in anodised aluminium in either full, half or quarter width. These panels are held by stainless steel Pozidriv screws on to the anodised main rails. Inside there are four aluminium slides on which the equipment can rest.

Details of case sizes and prices can be obtained from West Hyde Developments Ltd., Ryefield Crescent, Northwood Hills, Northwood, Middx. HA6 1NN.

As an addition to their "D" series instrument cases Vero Electronics introduce a 17½in deep series. The cases accept standard 19in front panels or frames and incorporate flush fitting side handles, for ease of carrying.

The cases incorporate all the usual features of the "D" series, such as tilt feet, front trim, and handles and a vinyl paint finish. Ventilation is provided by slots in the bottom and rear panels which are both detachable for easy access to the interior.

Further details of all the Vero cases are available from Vero Electronics Ltd., Chandlers Ford, Hampshire, SO5 3ZR.

The Impex range of cases from McArdle and Brainsby covers 36 different sizes. The case bodies are made from 20 s.w.g. steel coated with stove enamel in green hammer finish.

The detachable front and back panels are 18 s.w.g. satin anodised aluminium and the base is made from 18 s.w.g. passivated zinc plated steel.


Further information on the Impex range of cases is obtainable from McArdle and Brainsby (Import and Export) Ltd., P.O. Box 2BB, Newcastle-upon-Tyne, NE99 2BB.

SWITCH KIT

Constructors will be delighted to learn that a contender to the famous Maka Switch, which many readers seem to have difficulty in obtaining, is now being marketed through **Home Radio (Components) Ltd.**, by **A.B. Electronic Components Ltd.**

The switch is available in kit form and practically any multiple arrangement of rotary switching can be set-up. The switch consists of a shafting unit with a 6in shaft, wafers, screens, spacers, studding and a mains switch.

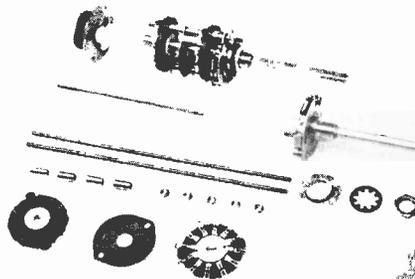Addresses of local stockists and details of wafers available can be obtained from A.B. Electronic Components Ltd., Sutherland House, 5/6 Argyll Street, London, W1V 1AD.



Switch kit made by
A.B. Electronics Components

TREASURE HUNTER


Hunting for buried treasure appears to be one of the popular outdoor pastimes, and the electronic metal detector is an essential part of the equipment of every serious treasure hunter.

A useful little handbook "A Fortune Under Your Feet" by Edward Fletcher has been brought to our attention. Its value is in the lesser known facts it contains about where and how to search. One chapter gives a broad outline of metal locators and suggests the kind of performance one should look for. Available from **Joan Allen & Co.**, Biggin Hill, Kent, price 45p plus 6p post and packing.


METALS TO ORDER

Happy to meet even the smallest order and advise which metal is best suited for a particular job, **Henry Righton & Co. Ltd.**, of Brookvale Road, Witton, Birmingham 6, have opened a "Cash & Carry" counter for the do-it-yourself enthusiast and model builders in the Birmingham area.

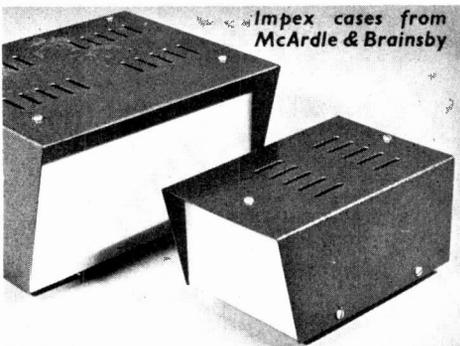
The counter, open from 9.0 a.m. to 5.0 p.m. and 8.30 a.m. to 12 noon Saturdays, is able to supply aluminium, brass, copper, bronze and stainless steel in rod, bar tube, sheet or strips cut to any size, shape or length.



Impex cases from
McArdle & Brainsby

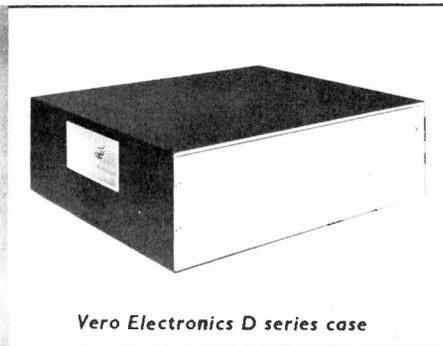

Vero Electronics D series case

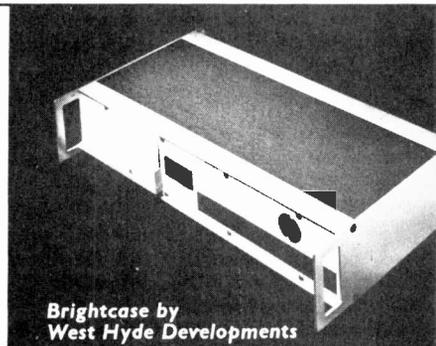

Brightcase by
West Hyde Developments

WAR GAMES COMPUTER

PART TWO

By D. R. Daines

IT SHOULD have been possible with last month's article to play in a very limited game using the primary parameter controls in Fig. 8. The SPEED controls would be "slowest" at the higher voltage end of the potentiometers VR4 and VR5; while TARGET SIZE would be smallest when S4 is switched to (d) line and largest on R22, although the labels for these switch positions have no direct importance to circuit function—only to strategy.

SECOND STAGE—PANEL 'A'

Panel A contains the three multivibrators and the gate. The circuit is shown in Fig. 9. TR1 and TR2 form the first "CHANCE" multivibrator, with TR3 added to speed up the rise time.

The frequency of a multivibrator can be changed by altering the voltage applied to the bases of the transistors, which is what is done here. VR1 alters the voltage, while VR2 alters the distribution of that voltage between TR1 and TR2, thereby altering the mark/space ratio (Fig. 8). The large CR combinations result in a slow change-over rate, and can be as low as once in every six or seven seconds.

The RATE OF FIRE multivibrator is formed by TR4 and TR5, with TR6 speeding up the output. Applying a variable voltage to the base of both transistors TR4 and TR5 would result in a varying frequency, but the mark/space ratio would remain the same; what is required is a fixed time pulse output with a variable delay between pulses. To this end TR4 is provided with a fixed base bias, but the voltage to TR5 is varied.

Exactly the same configuration is applied to the PROBABILITY multivibrator formed by TR7 and TR8, but the components are chosen to give a repetition rate somewhere between those of MV1 and MV2. TR9 speeds up the output. In practice TR6 provides a very good square wave, but because of the slow repetition rates of MV1 and MV3, TR3 and TR9 switch on and off very slowly, but the result is good enough for our purpose.

The outputs of the three multivibrators are applied to the gate formed by D5, D6, D7 and R41 (D8 is described later). Any small glass diodes will do for this purpose. If an oscilloscope is available, R41 may be adjusted to give the best output, but a meter may

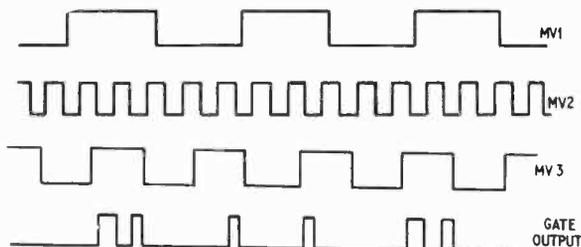


Fig. 9a. The waveforms into each gate diode D5, D6, D7 and the gate output waveform

COMPONENTS . . .

STAGE TWO (Panel "A" Fig. 9)

Resistors

R23	56k Ω	R30	100k Ω	R37	1M Ω
R24	1k Ω	R31	1M Ω	R38	22k Ω
R25	1k Ω	R32	470k Ω	R39	330k Ω
R26	22k Ω	R33	22k Ω	R40	56k Ω
R27	10k Ω	R34	330k Ω	R41	100k Ω
R28	56k Ω	R35	56k Ω		(see text)
R29	22k Ω	R36	22k Ω		

All $\pm 10\%$, $\frac{1}{4}$ W carbon

Capacitors

C3	25 μ F elect. 50V
C4	50 μ F elect. 50V
C5	0.05 μ F polyester
C6	0.05 μ F polyester
C7	4 μ F elect. 50V
C8	10 μ F elect. 50V
C9	0.25 μ F polyester

Transistors and Diodes

TR1 to TR9 any general purpose germanium types (e.g. OC71) all same (9 off)
D4 to D8 any general purpose diodes (e.g. OA81) all same (4 off)

Miscellaneous

Copper strip Veroboard 8in \times 3 $\frac{1}{2}$ in
Dial (ex-P.O. type) with all contacts or components for Alternative Firing Element (Fig. 10)

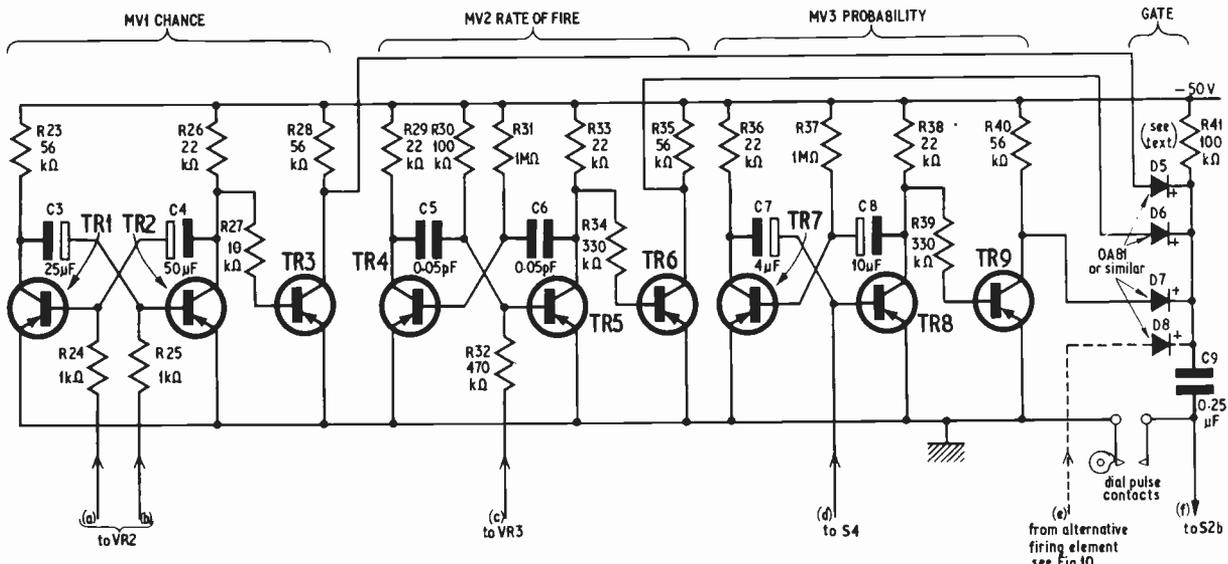


Fig. 9b. Circuit diagram of the multivibrators and gate (stage one) with waveforms (Fig. 9a) showing how coincidence gating is achieved

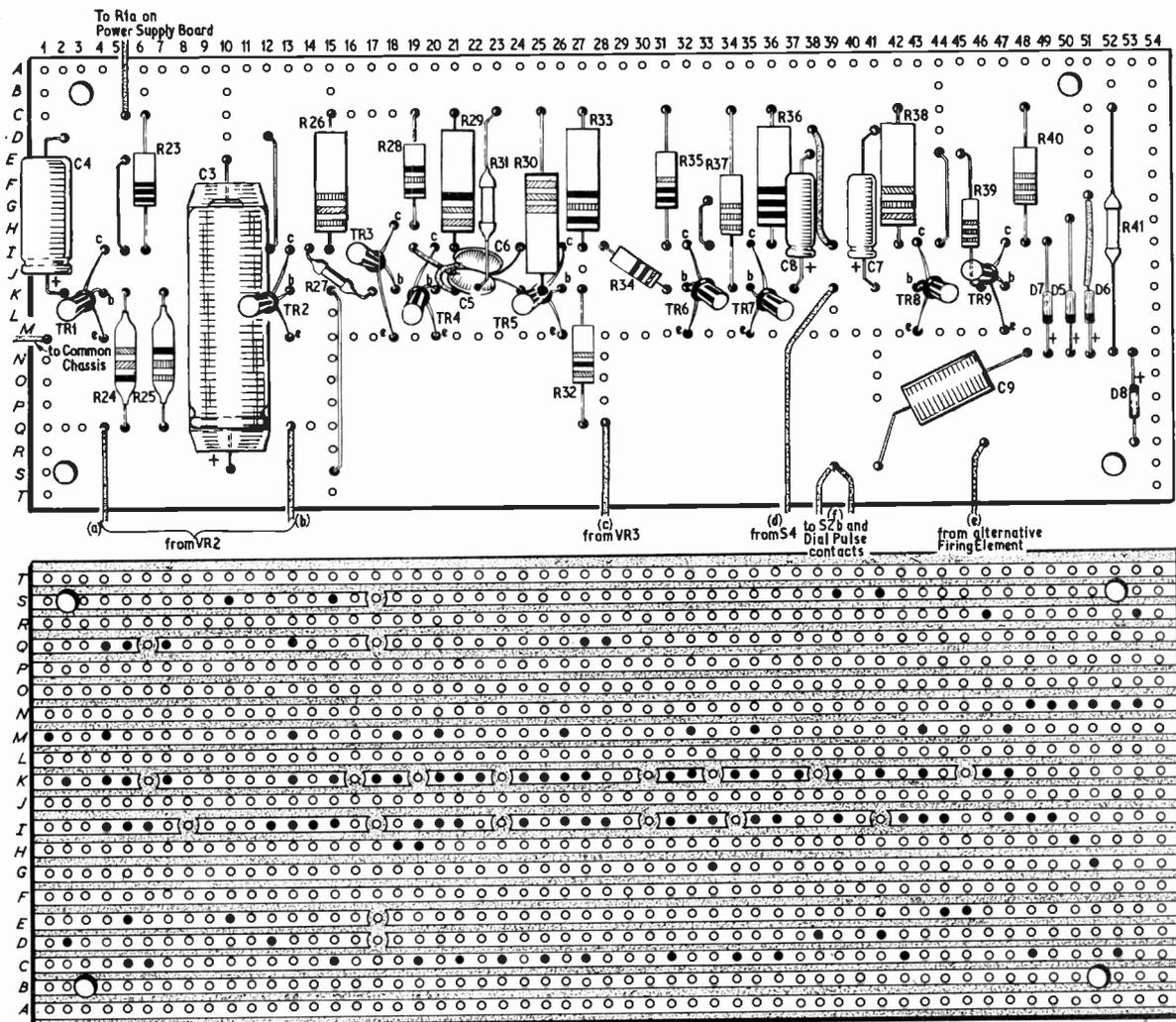


Fig. 9c. Layout of components on Panel A with underside view showing the breaks in the copper strips

ELECTROVALUE

EVERYTHING BRAND NEW TO SPEC • LARGE STOCKS • NO SURPLUS

BARGAINS IN NEW SEMI-CONDUCTORS

MANY AT NEW REDUCED PRICES • ALL POWER TYPES WITH FREE INSULATING SETS

40361	55p	2N2905	44p	2N4291	15p	BC148	9p	BFX87	29p
40362	67p	2N2905A	47p	2N4292	15p	BC149	10p	BFX88	26p
2N696	17p	2N2924	20p	AC107	46p	BC153	19p	BFY50	23p
2N697	18p	2N2925	22p	AC126	20p	BC154	20p	BFY51	20p
2N706	12p	2N2926	11p	AC127	20p	BC157	12p	BFY52	23p
2N930	29p	2N3053	27p	AC128	20p	BC158	11p	BXS20	16p
2N1131	29p	2N3055	60p	AC153K	22p	8C159	12p	C407	17p
2N1132	29p	2N3702	13p	AC176	16p	BC167	11p	MC140	25p
2N1302	19p	2N3703	13p	ACV20	20p	BC168	10p	MPS6534	35p
2N1303	19p	2N3704	13p	ACV22	16p	BC169	11p	MPS6534	30p
2N1304	26p	2N3705	13p	AD140	63p	BC177	14p	NKT211	25p
2N1305	26p	2N3706	13p	AD142	50p	BC178	13p	NKT212	25p
2N1306	33p	2N3707	13p	AD149	58p	BC179	14p	NKT214	23p
2N1307	33p	2N3708	10p	AD161	33p	BC182L	11p	NKT274	18p
2N1308	36p	2N3709	11p	AD162	36p	BC183L	10p	NKT403	65p
2N1309	36p	2N3710	13p	AF114	24p	BC184L	11p	NKT405	79p
2N1613	23p	2N3711	13p	AF115	24p	BC212L	16p	OC71	38p
2N1711	36p	2N3819	23p	AF120	24p	BC213L	16p	OC81	25p
2N1893	54p	2N3904	35p	AF124	24p	BC214L	16p	OC81D	25p
2N2147	95p	2N3906	35p	AF127	22p	BCY70	18p	ZTX300	14p
2N2218	34p	2N4058	13p	AF139	33p	BCY71	33p	ZTX301	16p
2N2218A	44p	2N4059	10p	AF239	36p	BCY72	15p	ZTX302	22p
2N2219	38p	2N4060	11p	ASV26	27p	BF115	23p	ZTX303	22p
2N2219A	53p	2N4061	11p	ASV28	27p	BF167	18p	ZTX304	27p
2N2270	62p	2N4062	11p	BC107	12p	BF173	16p	ZTX500	18p
2N2369A	19p	2N4124	18p	BC108	11p	BF194	14p	ZTX501	21p
2N2483	35p	2N4126	27p	BC109	12p	BF195	15p	ZTX502	21p
2N2484	42p	2N4284	15p	BC125	15p	BFX29	31p	ZTX503	22p
2N2646	47p	2N4286	15p	BC126	22p	BFX84	25p	ZTX504	22p
2N2904A	42p	2N4289	15p	BC147	10p	BFX85	52p		

Appointed distributors for
SIEMENS (U.K.) LTD.

Appointed stockists
NEWMARKET TRANSISTORS
RADIOHM POTENTIOMETERS

SAVE £6.25 ON THE NEW ENGLEFIELD 840 AMPLIFIER

This latest Peak Sound high fidelity amplifier incorporates many strikingly original features including facility for adding in stereo FM tuner. Superb performance characteristics and luxurious styling. Electrovalve choice of simulated soft leather covering in black, blue, red or dark green. As advertised at £45. Our price, net... **£38.75**

MAINLINE AMPLIFIER KITS

70W. power amplifier, £12.60 nett.

30 WATT BAILEY AMPLIFIER PARTS

Transistors and PCB for one channel £6.46
Capacitors, resistors (metal oxide), and transistors, one channel. £8.41.
Complete unregulated power supply pack, £4.75
Suitable heatsink 10DN 400C, 55p

RESISTORS

Code	Power	Tolerance	Range	Values available	1 to 9 (see note below)	10 to 99	100 up
C	1/20W	5%	82Ω-220KΩ	E12	9	8	7
C	1/8W	5%	4.7Ω-470KΩ	E24	1	0.8	0.7
C	1/4W	10%	4.7Ω-10MΩ	E12	1	0.8	0.7
C	1/2W	5%	4.7Ω-10MΩ	E24	1.2	1	0.9
C	1W	10%	4.7Ω-10MΩ	E12	2.5	2	1.9
MO	1/2W	2%	10Ω-1MΩ	E24	4	3.5	3
WW	1W	10% ± 1/20Ω	0.22Ω-3.9Ω	E12	7	7	6
WW	3W	5%	12Ω-10KΩ	E12	7	7	6
WW	7W	5%	12Ω-10KΩ	E12	9	9	8

Codes: C = carbon film, high stability, low noise.
MO = metal oxide, Electroasil TR5, ultra low noise.
WW = wire wound, Plessey.

Values:
E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades.
E24 denotes series: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

ZENER DIODES 5% full range E24 values:
400mW: 2.7V to 30V, 15p each; 1W: 6.8V to 82V, 27p each; 1.5W: 4.7V to 75V, 60p each.
Clip to increase 1.5W rating to 3 watts (type 266F), 4p.

CARBON TRACK POTENTIOMETERS, long spindles. Double wiper ensures minimum noise level.
Single gang linear 100Ω to 2.2MΩ, 12p; Single gang log, 4.7KΩ to 2.2MΩ, 12p; Dual gang linear 4.7KΩ to 2.2MΩ, 42p; Dual gang log, 4.7KΩ to 2.2MΩ, 42p; Log/antilog, 10K, 47K, 1MΩ only 42p; Dual antilog, 10K only, 42p. Any type with ±A D.P. mains switch, 12p extra.
Only decades of 10, 22 and 47 available in ranges quoted.

CARBON SKELETON PRE-SETS
Small high quality, type PR, linear only: 100Ω, 220Ω, 470Ω, 1K, 2K2, 4K7, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M2, 4M7, 10MΩ. Vertical or horizontal mounting, 5p each.

COLVERN 3 watt Wire-wound Potentiometers.
10Ω, 15Ω, 25Ω, 50Ω, 100Ω, 150Ω, 250Ω, 500Ω, 1K, 1.5K, 2.5K, 5K, 10K, 15K, 25K, 50K, 32p each.

Handbook of transistor equivalent and substitutes, 40p. (Postage 3p if ordered alone).

Prices are in pence each for quantities of the same ohmic value and power rating. NOT mixed values. (Ignore fractions on total value of resistor order.)

MULLARD polyester C280 series
250V 20%: 0.01, 0.022, 0.033, 0.047 3p each; 0.068, 0.1, 4p each; 0.15, 4p; 0.22, 5p, 10%: 0.33, 7p; 0.47, 8p; 0.68, 11p; 1μF, 14p; 1.5μF, 21p; 2.2μF, 24p.

MULLARD SUB-MIN. ELECTROLYTICS
C246 range, axial lead 6p each
Values (μF/V): 0.64/64; 1/40; 1.6/25; 2.5/16; 2.5/64; 4/10; 4/40; 5/64; 6.4/64; 6.4/25; 8/4; 8/40; 10/2.5; 10/16; 10/64; 12.5/25; 16/40; 20/64; 20/64; 25/6.4; 25/25; 32/4; 32/10; 32/40; 40/16; 40/2.5; 50/6.4; 50/25; 50/40; 64/4; 64/10; 80/2.5; 80/16; 80/25; 100/6.4; 125/4; 125/10; 125/16; 160/2.5; 200/6.4; 200/10; 250/4; 320/2.5; 320/6.4; 400/4; 500/2.5.

LARGE CAPACITORS
High ripple current types: 1000/25, 28p; 1000/50, 41p; 1000/100, 82p; 2000/25, 37p; 2000/50, 57p; 2000/100, £1.44; 2500/64, 77p; 2500/70, 98p; 5000/25, 62p; 5000/50, £1.10; 5000/100, £2.91; 10000/50, £2.40.

● ● ● COMPONENT DISCOUNTS
10% on orders for components for £5 or more.
15% on orders for components for £15 or more.
(No discount on nett items.)

POSTAGE AND PACKING
Free on orders over £2. Please add 10p if orders under £2.
Overseas orders welcome: carriage and insurance charged at cost.
Send S.A.E. for latest list. All items in stock at time of going to press. Prices subject to alteration without notice.

SIEMENS TTL INTEGRATED CIRCUITS

We stock full range of all Siemens types for a very wide range of applications. For full details, see our latest catalogue described below.
PLESSEY I.C. SL403D 7.5 ohms. £2.10 nett. Applications table 10p.

S-DeCs put an end to birds nesting
Components just plug in—saves time—allows re-use of components. S-Dec (70 points), £1.00
T-Dec. may be temperature-cycled (208 points), £2.50 Also μ-DeCs and IC carriers.

INDICATOR LAMPS
NEON chrome bezel, round red NR/R, 24p; chrome bezel, round amber NR/A, 24p; chrome bezel, round clear NR/C, 24p. Neon, square red type L55C/R, 18p; amber type L55C/A, 18p; clear type L55C/C, 18p. All above are for 240V mains operation. Filament types: 6V, 0.04A square red type L55C/R-6V, 30p; 6V, 0.04A amber type L55C/A-6V, 30p; 6V, 0.04A clear type L55C/C-6V, 30p; 6V, 0.04A green type L55C/G-6V, 30p; 12V, 0.04A L55C/R-12V, 34p; 34V, 0.04A L55C/R-28V, 45p.

SIEMENS 5% TOLERANCE POLYCARBONATE CAPACITORS

250V up to 0.1mF; 100V 0.1mF and above
0.01, 0.012, 0.015, 0.018, 0.022, 0.027 5p
0.033, 0.039, 0.047, 0.056, 0.068, 0.082, 0.1, 0.12, 0.15, 0.18, 0.22 6p
0.27 8p
7p 0.33 8p

DIN CONNECTORS

	2-pole	3-pole	4-pole	5-pole	6-pole
Loudspeaker	12p	13p	14p	15p	15p
Audio	12p	13p	14p	15p	15p
Audio	12p	13p	14p	15p	15p
Audio	12p	13p	14p	15p	15p
Audio	12p	13p	14p	15p	15p

NOW READY—1971 ELECTROVALUE CATALOGUE

64 pages plus covers. Thousands of items plus classified information and illustrations.
Post free **10p**

ELECTROVALUE DEPT. P.E.971, 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY
Hours: 9-5.30, 1.0 p.m. Saturdays. Phone: Egham 5533 (STD 0784-3) Telex 264475

TECHNICAL TRAINING

*in radio television
and electronics*

Whether you are a newcomer to radio and electronics, or are engaged in the industry and wish to prepare for a recognized examination, ICS can further your technical knowledge and provide the specialized training so essential to success. ICS have helped thousands of ambitious men to move up into higher paid jobs—they can help you too! Why not fill in the coupon below and find out how?

Many diploma and examination courses available, including expert coaching for:

- C. & G. Telecommunication Techns'. Certs.
 - C. & G. Electronic Servicing
 - R.T.E.B. Radio/T.V. Servicing Certificate
 - Radio Amateurs' Examination
 - Radio Operators' Certs.
 - General Certificate of Education, etc.
- Now available, Colour T.V. Servicing

Examination Students coached until successful

NEW SELF-BUILD RADIO COURSES

Learn as you build. You can learn both the theory and practice of valve and transistor circuits, and servicing work while building your own 5-valve receiver, transistor portable, and high-grade test instruments, all under expert tuition. Transistor Portable available as separate course.

POST THIS COUPON TODAY

for full details of ICS courses in Radio, T.V. and Electronics



INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 151, Intertext House, Stewarts Rd., London, S.W.8

Please send me the ICS prospectus—free and without obligation.

(state Subject or Exam.)

NAME
(Block Capitals Please)
ADDRESS

AGE

9/71

INTERNATIONAL CORRESPONDENCE SCHOOLS

OCTOBER 71



SERVO CHART RECORDER

The rate of change of some electrical signals is often too slow to provide convenient monitoring with a test meter. This Chart Recorder makes a continuous assessment in graphical form on slow moving paper of such changing signals.

Suitable for use with currently running P.E. Radio Telescope project and other applications involving long-term observation and monitoring.

ENGINE TEMPERATURE CONTROLLER

The fan used in the motor car is unnecessarily wasteful when driven from the engine. This controller operates a fan independently from engine drive according to the temperature of the water in the radiator.

WATER LEVEL AND RAIN ALARM

A simple audible alarm is triggered when rain falls or when the level of water in a vessel reaches a set point.

PRACTICAL ELECTRONICS

ON SALE SEPTEMBER 17

Practical Electronics September 1971

two poles of a pushbutton. It should be red and marked "Firing". Depressing the button discharges C11 completely and at the same time turns TR10 off and TR11 on.

The collector of TR11 becomes approximately 3 volts negative with respect to earth, and 6 volts with respect to the negative rail. C11 begins to charge through R47 and as it charges the base of TR12 lowers.

There comes a point (after about five seconds) when TR12 switches off. The voltage at the collector rises towards the negative rail, and this rise is transmitted through R51 to turn TR10 on. TR10 and TR11 together form a bistable and they now assume a stable state in which TR10 is on and TR11 off. The cycle cannot resume until S5 is again depressed, hence the whole circuit is a five-second timer, determined by R47, R48, R50, R51 and C11.

While TR10 is in the off position during the cycling process, the voltage at the collector rises to the negative rail and this is taken out to prime the gate

via D8 (Fig. 9a). Since nothing can pass the gate until all inputs have a 1 (positive), no rate of fire pulses can go forward until the firing button is pressed.

This substitution for the dial would leave the constructor no method of feeding the computer with information regarding the number of guns firing and so it would be necessary to introduce another VR arranged as a voltage divider, and it may be necessary to adjust the gate resistor.

Fig. 10b shows the connections to the dial and lamps on the upper part of the control panel.

THIRD STAGE WIRING

Pulses are now routed and attenuated according to the positions of the remaining controls, S6, S7 and S8 (Fig. 11). Notice that first they go through the second wafer of the CALIBRE switch, S2b. Heaviest calibre pulses pass unattenuated, while others pass through voltage divider networks, for example that formed by R48 and R49.

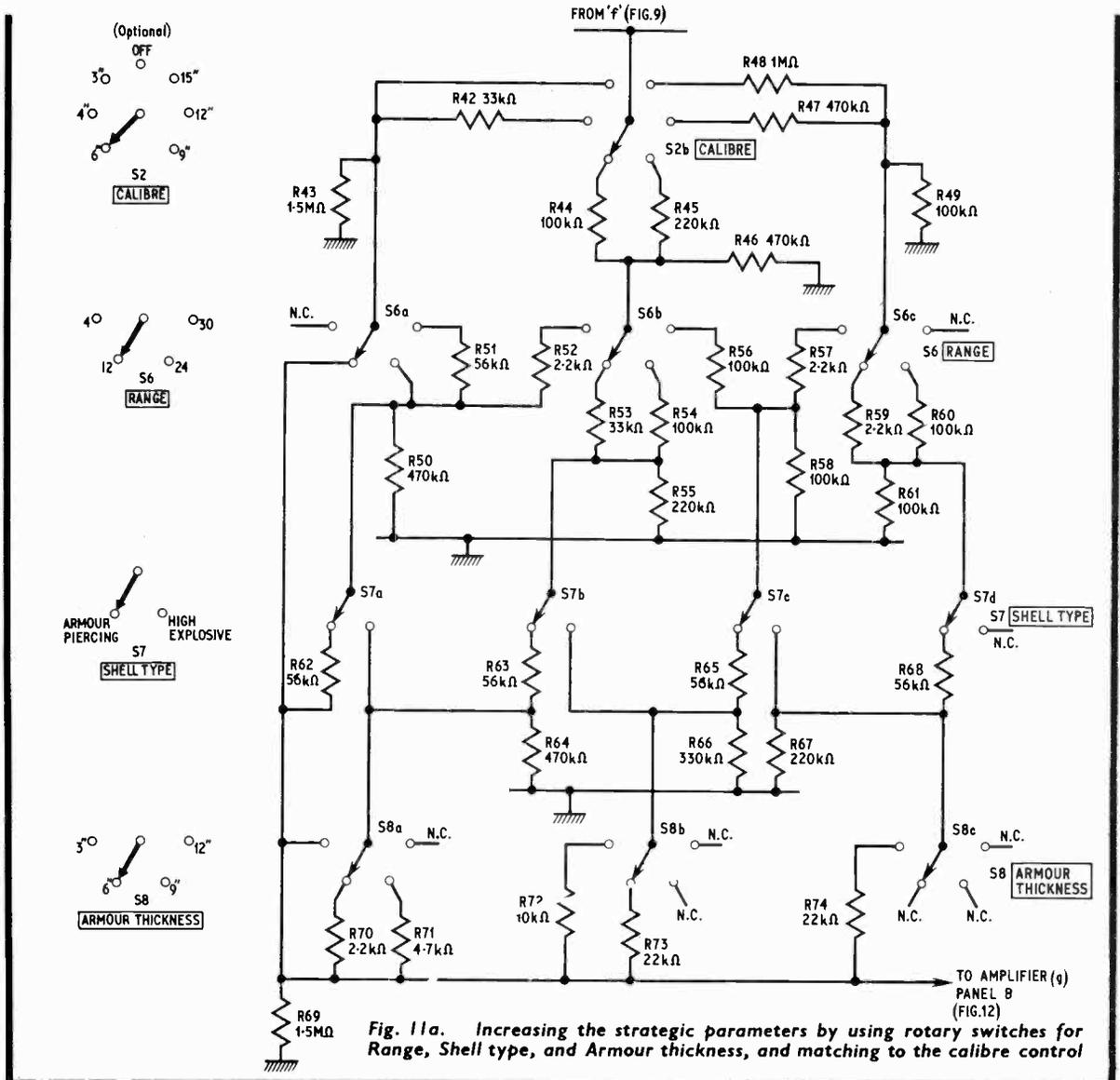


Fig. 11a. Increasing the strategic parameters by using rotary switches for Range, Shell type, and Armour thickness, and matching to the calibre control

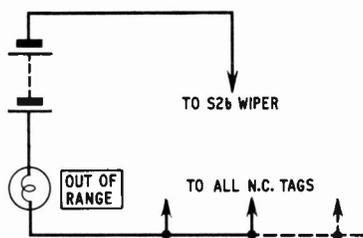


Fig. 11b. How to use n.c. positions to indicate "out of range"

COMPONENTS . . .

STAGE THREE (Fig. 11)

Resistors

R42	33k Ω	R53	33k Ω	R64	470k Ω
R43	1.5M Ω	R54	100k Ω	R65	56k Ω
R44	100k Ω	R55	220k Ω	R66	330k Ω
R45	220k Ω	R56	100k Ω	R67	220k Ω
R46	470k Ω	R57	2.2k Ω	R68	56k Ω
R47	470k Ω	R58	100k Ω	R69	1.5M Ω
R48	1M Ω	R59	2.2k Ω	R70	2.2k Ω
R49	100k Ω	R60	100k Ω	R71	4.7k Ω
R50	470k Ω	R61	100k Ω	R72	10k Ω
R51	56k Ω	R62	56k Ω	R73	22k Ω
R52	2.2k Ω	R63	56k Ω	R74	22k Ω

Switches

- S6 3-pole, 4-way rotary wafer
- S7 6-pole, 2-way rotary wafer (only 4 poles are used)
- S8 3-pole, 4-way rotary wafer

Optional (see Fig. 11b and text)

- Lamp and battery (any voltage) to show "out of range"

The other dividers will readily be discerned. At S6, the RANGE control, lightest calibres are blocked at long range, while heaviest calibres are blocked at short range, it being assumed that such guns will fire over their targets.

If desired, the outputs marked N.C. (no connection) may be taken to illuminate an out-of-range bulb (Fig. 11b). A separate supply will be necessary; four 1.5 volt batteries in series would feed a six volt bulb for months, at the rate of use found here.

The SHELL TYPE switch S7 is unusual in that the player is required to make a conscious choice that is not governed by conditions on the playing board. There are two positions, marked "Armour piercing" and "High explosive", the point being that AP shells pierce thicker armour, but HE shells do more damage.

On the AP side the pulses pass through a divider network such as R63 and R64, but are routed to the left of the diagram to pierce thicker armour, whereas HE pulses pass unattenuated to the right.

The ARMOUR switch S8 is set for armour thickness and again the pulses are blocked if the shells that they represent cannot pierce that thickness at that range. Others are attenuated by voltage dividers as before. Notice that R69 may form a divider with R62 as well as R70 to R74. The clear unattenuated signal path down the left of the diagram means that at optimum range the very heaviest shells whether HE or AP can pierce any armour. At a little longer range the heaviest AP can do so.

TESTING AND USING

Disconnect the chassis wire from the telephone dial (Figs. 9b and 10b), allowing pulses to pass unrestricted, and apply an oscilloscope to the output. There should be a very wide variation in the amplitude and frequency of pulses, and since we now have 12 controls (without the dial), the total number of combinations becomes $6^3 \times 10^3 \times 12 \times 4^2 \times 3 \times 2$ —which is over 60 million combinations. It is obviously impossible to check all these and it becomes necessary to sample in order to satisfy ourselves that all is well.

First repeat the tests of the second stage, ensuring that the sequence pattern alters with the movement of the previous controls. Then set the RANGE switch to position two (short) and ARMOUR to minimum. Under these conditions all calibre settings will produce pulses.

Check that heavy calibres produce large amplitude pulses, and not vice-versa. Switching RANGE to position 1 should block the two heaviest calibres, while switching to position 4 will block the lightest.

Check that pulses are progressively attenuated with range, also in the AP position. Check the progressive blocking of lighter calibres as armour is thickened.

It is really a matter of checking step by step, keeping a clear idea of the principles involved. When all is satisfactory, replace the chassis lead to the dial.

The computer can be used with a voltmeter as before, if necessary with an amplifier stage. Deflection of the needle indicates damage, but it is difficult, to be any more precise about this without becoming complicated. The amount of deflection is not a very good guide to the amount of damage because of the time lag in meter response.

A single heavy pulse of short duration may pass unnoticed by the observer, whereas a longer train of weaker pulses would produce a deflection proportionate to their amplitude and frequency. It is much better at this stage to say that if there is a needle deflection there is damage and to roll a dice to ascertain the extent of the damage.

Next month : Stage four — the start of showing how much damage is made to equipment.

P. E. GEMINI

REPRINTS AVAILABLE

Because of the continuing interest in the "P.E. Gemini" Dual Purpose Stereo Amplifier it has been decided to reprint all articles (together with any appropriate amendments) in booklet form.

The price of this 32-page booklet is 55p, including postage. Orders for copies, with P.O. or cheque made payable to IPC Magazines Ltd., should be addressed as follows:

The Receiving Cashier (P.E. Gemini)
IPC Magazines Ltd.,
Tower House,
Southampton Street,
London, W.C.2.

MAIL ORDER DIVISION

distronic

THE POWER HOUSE LTD

28 BURNT MILL
ELIZABETH WAY
HARLOW ESSEX
HARLOW 32947

**Why wait weeks? — ALL OUR ORDERS
DISPATCHED BY RETURN OF POST!**
Transistors, Diodes and Integrated Circuits

A) DIODES & RECTIFIERS

IN4001	7p
IN4002	8p
IN4003	9p
IN4004	10p
IN4005	12p
IN4006	14p
IN4007	20p

AC187K	} Matched pr. 50p
AC188K	
AC191	15p
AC192	15p
AC193	20p
AC193K	} Matched pr. 60p
AC194K	
AC194	20p
AD143	50p
AD262	} Matched pr. 90p
BD162	
AD262	35p
AD263	40p
AF106	25p
AF109	35p
AF139	31p
AF166	20p
AF170	18p
AF172	18p
AF200	25p
AF201	30p
AF239	40p
AF239S	45p
AL102	60p
AL103	50p
AU103	£1

BC109	11p
BC113	20p
BC114	20p
BC115	25p
BC116A	30p
BC117	30p
BC125	20p
BC126	30p
BC132	20p
BC134	20p
BC137	30p
BC142	35p
BC143	40p
BC144	40p
BC145	35p
BC147	15p
BC148	11p

BFX86	30p
BFX87	30p
BFX88	25p
BFY34	30p

Please note minimum order 50p

Compare our prices

WO05	40p
WO1	45p
WO4	48p
WO6	50p

Send 10p for price list or free with order

B) TRANSISTORS

2N696	15p
2N930	25p
2N930A	30p
2N1613	22p
2N1711	25p
2N2369	20p
2N2484	34p
2N2605	45p
2N2904	36p
2N2904A	41p
2N2905	46p
2N2905A	60p
2N3053	22p
2N3055	70p
2N3442	£2
2N3638	25p
2N3866	£1-50
2N4347	£1-50
2N4356	35p
40411	£2-50
AC138	15p
AC141	20p
AC141H	25p
AC142	15p

**Component Discounts
10% on orders over £5**

AU106	95p
AU107	70p
AU108	65p
AU110	£1
AU111	70p
AUY21A	60p
AUY22A	70p
AUY35	45p
AUY37	60p
BC107	11p
BC108	11p

BC149	15p
BC153	30p
BC154	35p
BCY70	26p
BCY71	26p
BCY72	26p
BF152	25p
BF153	25p
BF158	25p
BF159	35p
BF160	28p
BF177	25p
BF178	35p
BF179C	40p

BFY50	22p
BFY51	20p
BFY52	20p
ME0404-1	12p
ME0404-2	13p
ME1001	10p
ME1002	11p
ME2001	10p
ME2002	11p
ME3001	20p
ME3002	25p
ME4001	10p
ME4002	11p
ME6001	15p
ME6002	18p
ME8001	20p
ME8002	30p
ME8003	30p
ME9001	15p
ME9002	15p
MEL11	40p
MEL12	50p
MEU21	40p
MEU22	50p
OC25	37p

C) INTEGRATED CIRCUITS

709C (TO-99)	95p
709C (DIP)	95p
741C (TO-99)	£1-25
741C (DIP)	£1-25

2N3055	70p
115 Watt 15 Amp	
2N3053	22p
1 Amp TO-5	
BC107	11p
Also BC108 and BC109	
AF239	40p
UHF: 5 DB at 800 MHz	
WO1	45p
1 Amp, 100 V Bridge Rectifier	
AD262	} PNP Matched 90p
BD162	
10 Watts, AUDIO OUTPUT PAIR	
AD142	50p
80 Volts, 10 Amp TO-3	
AU103	£1
155 Volts, 10 Amp TO-3	
AU106	95p
320 Volts, 10 Amps	
BC147/8/9	15p
High gain LOCKFIT	
ME1001	10p
45 Volt high gain	
40411	£2-50
30 Amp, 150 Volts	
IN4001	7p
1 Amp, 100 Volts	
BF179C	40p
250 Volts TO-5	
BFY51/2	20p
2N3866	£1-50
1 Watt output at 400MHz	
BC114	20p
High gain: 200 at 1mA	
741C	£1-25
DIP or TO-99	
High gain operational amp. S/C proof	

POSTAGE & PACKING PLEASE ADD 10p TO YOUR ORDER

**SEND FOR
BONUS VOUCHER*
FREE WITH EVERY
£1 ORDER**

*Redeemable upon receipt of subsequent order value £5 or more, received before Dec. 31, 1971

BONUS VOUCHER

Save money on electronic components, books, magazines, and more. Redeemable on orders of £5 or more. Valid until 31st Dec 1971.

distronic LTD

28 BURNT MILL, ELIZABETH WAY, HARLOW, ESSEX



PHILIPS STEREO & MONO AUTOCHANGER

£9.75 Post 85p.
Precision hi-fi quality at bargain price. Silver and grey deck enamelled finish. 10 1/2 in. dia. turntable. 4 speeds, 16, 33 1/3, 45 and 78 r.p.m. Plays 7, 10, 12 in. discs which can be mixed. Fitted renowned Philips plug-in pick-up with stylus LP STEREO EP and 78. Sensitivity 100mV. Frequency response 30cps-16Kcs. Lightweight stylus pressure 3-6 grammes. Board size required 14 x 12 1/2 in. Above 4 in. Below 2 1/2 in.



PHILIPS PORTABLE PLAYER CABINET

Size 18 x 15 1/2 x 7 1/2 in. Cut out above deck. Amplifier space 14 x 5 x 3 1/2 in. Satin aluminium front grille. Really smart appearance. Black/White or Green/Grey. **£4** Post Chrome fittings. 25p

BSR C.109 SUPERSLIM STEREO & MONO CHANGER

Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. AC 200/250V. Size 13 1/2 x 11 in. Above motor board 3 1/2 in. below motor board 2 1/2 in. with STEREO and MONO XTAL **£7.75** Post 25p.



GARRARD PLAYERS with Sonotone 9TA Cartridges. Stereo Diamond and Mono Sapphire. RP25 Mk II £15. Model 9500 Stereo and Mono Autochanger £14. Post 25p.
RECORD PLAYER PORTABLE CABINET £3.75 Space for amplifier and autochanger. Post 25p.
RGCS DE-LUXE 3 WATT AMPLIFIER. Ready made tested. 8-stage with triode pentode valve, 3 watts output. Tone and volume controls. Isolated mains transformer. Knobs, loudspeaker, valves ECL82, E230. Response 50-12,000 cps. Sensitivity 200mV. Post 25p. **£4**
RGCS 2 WATT AMPLIFIER with loudspeaker and valves UCL82 and UV85. Post 25p. **£3**

R.C.S. TEAKWOOD BASE. Ready cut out for mounting (state player make and model). **£2.75**
R.C.S. PLASTIC COVERS FOR ABOVE BASE. Durable plated finish, attractive appearance. **£2.75**

EMI PICK-UP ARM. With mono xtal and stylus £1.25.
EMI JUNIOR 4 SPEED RECORD PLAYER. Mains £3.00 Hi-Fi motor, turntable and pick up. Post 25p.
HI-FI PICK UP CARTRIDGES. Diamond Stereo/Mono 9TA £2.90; GP24 £2.75; GP25 £2.25; Mono GP21 £1.50; GC2 £1.25; GP27 85p; ACOS LP. only 50p. All standard fixing complete with stylus.

WEYRAD P50 - TRANSISTOR COILS

RA2W Ferrite Aerial... Spare Cores... 3p
AC. P50/1AC... Driver Trans. LFTD4... 50p
L.F. P50/200 470 kc/s... Printed Circuit, PCA1... 50p
M.F. P50/300... J.B. Tuning Gang... 65p
P51/1 or P51/2... Weyrad Booklet... 10p
P50/3V... OPT1... 55p
Mullard Ferrite Rod 8 x 1/2 in. 20p. 6 x 1/2 in. 25p.

VOLUME CONTROLS

Long spindles. Midget Size 5 K ohms to 2 Meg. LOG or LIN. L/S 15p. D.P. 25p. STEREO L/S 55p. D.F. 75p. Edge 5K. S.F. Transistor 25p. **80ohm Coax 4p** yd.

WIRE-WOUND 3-WATT POTS. Small type with small knob. Values 10Ω to 30K. **25p**
WIRE-WOUND 3-WATT STANDARD SIZE POTS. LONG SPINDLE **40p**
10 OHMS to 100 K.

VEROBOARD 0-15 MATRIX
2 1/2 x 5 in. 19p. 3 1/2 x 3 1/2 in. 16p. 3 1/2 x 3 1/2 in. 15p. 3 1/2 x 5 in. 20p.
EDGE CONNECTORS 16 way 25p. 24 way 35p.
PINS 38 per packet 17p. FACE CUTTERS 88p.
S.R.B.F. Board 0-15 MATRIX 2 1/2 in. wide 3p per lin., 3 1/2 in. wide 4p per lin., 5 in. wide 5p per lin. (up to 17 in.).
S.R.B.F. undrilled 1 in. Board 10 x 8 in. 15p.

BLANK ALUMINIUM CHASSIS. 18 s.w.g. 2 in. sides 7 x 4 in. 45p; 9 x 7 in. 50p; 11 x 7 in. 70p; 13 x 9 in. 75p; 14 x 11 in. 80p; 15 x 14 in. 85p; 11 x 3 in. 50p.
ALUMINIUM PANELS 18 s.w.g. 6 x 4 in. 8p; 8 x 6 in. 15p; 10 x 7 in. 17p; 12 x 8 in. 23p; 14 x 9 in. 27p; 12 x 12 in. 32p.

1 1/2 in. DIAMETER WAVECHANCE SWITCHES. 25p.
2 p. 2-way, or 2 p. 3-way, or 3 p. 4-way 25p each.
1 p. 1. 2-way, or 4 p. 2-way, or 4 p. 3-way 25p
1 inch DIAMETER Wavechange "MAKITS" 1 p. 12-way, 2 p. 6-way, 3 p. 4-way, 4 p. 3-way, 6 p. 2-way, 1 water 80p, 2 water 95p. Extra waters up to six 80p each.
TOGGLE SWITCHES, sp. 14p; dp. 18p; dp. dt. 23p.

ALL PURPOSE HEADPHONES

H.R. HEADPHONES 2000 ohms Super Sensitive... **£1.75**
LOW RESISTANCE HEADPHONES 3-5 ohms... **2p**
DE LUXE STEREO HEADPHONES 8 ohms... **£3.25**



"THE INSTANT" BULK TAPE ERASER AND RECORDING HEAD DEMAGNETISER **£2.35** Post 15p

GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

For Mike, Tape, P.U. Guitar, etc. operation. Size 1 1/2 x 1 1/2 x 1 1/2 in. 200-300V. E.C. operation. Mace 25 c.p.s. to 25 Kcs. 26 db gain. For use with valve or transistor equipment. Full instructions supplied. Brand new. **90p** Post 10p
Guaranteed. Details S.A.E.

NEW TUBULAR ELECTROLYTICS
2/350V... 14p 100/25V... 10p 16+16/500V... 55p
4/350V... 14p 250/25V... 14p 50+50/350V... 55p
8/450V... 14p 500/25V... 20p 80+100/350V... 58p
16/450V... 15p 8+8/450V... 18p 32+32/250V... 15p
32/450V... 20p 8+16/450V... 20p 32+32/450V... 33p
50/25V... 10p 16+16/450V... 25p 32+32+32/350V... 43p
50/50V... 10p 32+32/350V... 25p 100+50+50/350V... 48p

CAN TYPES
SUB-MIN. ELECTROLYTICS 1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p; 500, 1000mF 12V 15p; 2000mF 25V 35p.
CERAMIC. 1pF to 0.01mF, 4p. Silver Mica 2 to 5000pF, 4p. PAPER 350V-0.1 4p, 0.5 13p; 1mF 15p; 2mF 150V 15p. 500V-0.001 to 0.05 4p; 0.1 5p; 0.25 5p; 0.47 25p. 1.00V 0.001, 0.00047, 0.01, 0.02, 0.05, 0.047, 0.1, 14p. SILVER MICA. Close tolerance 1%. 2.2-500pF 8p; 560-2.200pF 10p; 2.700-5.600pF 20p; 6.800pF-0.01, mid 30p each. TWIN GANG. "0-0" 208pF+178pF, 65p; Slow motion drive 365pF+385pF with 25pF+25pF, 50p; 500pF slow motion, standard 45p; small 3-gang 50p 5F-11.0. SHORT WAVE SINGLE. 25V, 50p, 55p.
CERAMIC THERMISTOR. 250, 300, 500, 50p.
TUNING. Solid dielectric. 100pF, 500pF, 35p each.
TRIMMERS. Compression 30, 50, 70pF, 5p; 100pF, 150pF, 8p; 200pF, 8p; 800pF, 750pF, 10p; 1000pF, 10p. RECTIFIERS CONTACT COOLED half wave 60mA 38p; 85mA 48p. SILICON BYZ13 30p; BY100 30p; BY127 30p. Full wave Bridge Rectifiers 75mA, 150mA, 150mA 88p. DIODES. RECT. 250V 200mA 30p. NEON PANEL INDICATORS 250V AC/Dc Red or Amber 20p. RESISTORS. 1 w., 1 w., 1 w., 20% 1p; 2 w. 5p. HIGH STABILITY. 1 w., 2 w., 10 ohms to 1 meg., 10p. Dkto 50. Preferred values 10 ohms to 10 meg., 4p. WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt, 100ohms to 100K 10p each; 2 1/2 watt, 1 ohm to 8.2 ohms 10p.

Q MAX CHASSIS CUTTER

Complete: a die, a punch, an Allen screw and key
1 in. 88p 1 in. 88p 1 1/2 in. 98p 1 1/2 in. £2.20 2 1/2 in. £2.21
1 in. 88p 1 in. 88p 1 1/2 in. £1.03 1 1/2 in. £1.45 2 1/2 in. £2.86
2 in. 88p 1 1/2 in. 88p 1 1/2 in. £1.08 2 in. £1.90 1 in. 88p

AM - FM/VHF TUNING GANG

Super quality small size 1 1/2 x 1 1/2 x 1 1/2 in. spin spindle 1/4 in. 385+365 pF with 25+25 pF. British made. Geared slow motion drive 6:1. Plastic dust cover. 6BA tapped front fixing. Cast aluminium frame. **50p** POST FREE

MAINS TRANSFORMERS

All post 25p each
250-0-250 50 mA. 6.3 v. 2 amp. centre tapped... £1.10
250-0-250 80 mA. 6.3 v. 4 amp. ... £1.40
250-0-250 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a. £2
350-0-350 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a. £2
300-0-300 v. 120 mA. 6.3 v. 4 a. CT. 6.3 v. 2 a. £2.50
MINIATURE 200 v. 20 mA. 6.3 v. 1 a. 2 1/2 x 2 1/2 in. 75p
MIDGET 230 v. 45 mA. 6.3 v. 2 a. 2 1/2 x 2 1/2 in. 90p
P.E. AURORA TRANS. 12+12V. 500mA £1.50
MINI-MAINS 20V. 100mA. 1 1/2 x 1 1/2 in. 50p
HEATER TRANS. 6.3 v. 3a. 70p
Dkto tapped sec. 1.4 v., 2.3, 4, 5, 6.3 v. 1 1/2 amp. 80p
GENERAL PURPOSE LOW VOLTAGE. Tapped outputs at 2 amp., 3, 4, 5, 6, 8, 9, 10, 15, 18, 24 and 30 v. £2
1 amp., 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60. £2
2 amp., 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60. £3
AUTO TRANSFORMERS. 115v to 230V or 230v to 115v. Input/Output, 150w. £2; 500w. 55p; 1000w. £12
CHARGER TRANSFORMERS. Input 200/250V. for 6 or 12v. 1 amp. £1.20; 2 amp. £1.60; 4 amp. £1.90
FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12v. outputs. 1 amp. 40p; 2 amp. 55p; 4 amp. 85p.
All Transformers Postage 25p each

E.M.I. 13 1/2 x 8 in. LOUSPEAKERS


With flared tweeter cone and ceramic magnet. 10 watt.
Bass res. 45-60 cps. **£2.25**
Fix 10,000 gauss.
State 3 or 8 or 15 ohm. Post 15p
And with twin tweeters. **£4**
And crossover. 10 watt. **£4**
State 3 or 8 or 15 ohm. Post 15p
As illustrated.
Recommended Teak Cabinet **£5**
Size 16 x 10 x 9 in. Post 25p.

10W MINI-MODULE £3.25 LOUSPEAKER KIT

Post 25p
Triple speaker system combining on ready cut baffle: 1 in. chipboard 15 1/2 x 8 1/2 in. 272ba Bass, Middle and Treble loudspeakers and crossover condenser. The heavy duty 5 in. Bass Woofer unit has a low resonance cone. The Mid-Range unit is specially designed to add drive to the middle register and the tweeter recreates the top end of the musical spectrum. Total response 20-15,000 cps. Full instructions for 3 or 15 ohm.
TEAK VENEERED BOOKSHELF ENCLOSURE. 16 1/2 x 10 1/2 x 6 in. Modern design, dark grey Teak covered baffle. **£5** Post 25p

ALL MODELS "BAKER SPEAKERS" IN STOCK

BAKER 12in MAJOR £9

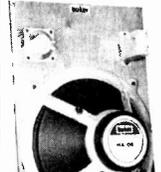

30-14,500 c.p.s., 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwell. Bass resonance 40 c.p.s. Rated 20 watts. State 3 or 8 or 15 ohm. Post Free.

Module kit, 30-17,000 c.p.s. with tweeter, crossover, baffle and instructions. **£11.50**

'GROUP 25' 'GROUP 35' 'GROUP 50'

12 inch **£7** 12 inch **£9** 15 inch **£19**
25 watt 8 or 8 or 15 ohm 35 watt 3 or 8 or 15 ohm 50 watt 8 or 15 ohm

BAKER "BIG-SOUND" SPEAKERS
TEAK HI-FI SPEAKER CABINETS. Fluted wood front. For 12 in. round Loudspeakers... £9 Post 25p
For 13 in. Loudspeaker... £9 Post 25p
For 10 x 6 in. Loudspeaker... £4 Post 25p
LOUDSPEAKER CABINET WADDING 18in. wide, 15p lb

THIS LACONIC NETWEETER IS THE VERY LATEST DESIGN AND GIVES A HIGHER STANDARD OF PERFORMANCE THAN MORE EXPENSIVE UNITS



The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 cps to 12,000 cps. Size 3 1/2 x 3 1/2 in. deep. Rating 10 watt. 3 ohm or 15 ohm models. **£1.90** Post 10p

TWO-WAY XOVER NETWORK 3000 c/s.

With variable tweeter attenuator giving accurate high/low frequency balance. Mounted on panel 6 1/2 in. with control knob, tweeter and woofer leads and 1/4 in. Post input terminals. Suitable for 3 to 8 ohm imp. **£1.90** Post 10p

GOODMANS HEAVY DUTY 10in. WOOFER

10w. Large ceramic magnet. 30-12,000 cps. Ideal **£4** P.A., Columns, Hi-Fi Enclosures, etc.

Horn Tweeters 2-16Kcs, 10W 8 ohm or 15 ohm £1.50.
De Luxe Horn Tweeters 2-18 Kcs, 15W, 8 ohm £3.
TWO-WAY 3,000 c.p.s. CROSSOVERS 3 or 6 or 15 ohm 95p.
SPECIAL OFFER: 80 ohm, 2 1/2 in. dia., 35 ohm, 3 in. 25 ohm, 3 in. dia.; 6-4 in; 8-5 in. **£1** EACH TYPE
15 ohm, 3 1/2 in. dia.; 7-4 in; 8-5 in.
3 ohm, 2 1/2 in. 3 in. 5 in. 5 in. 3 in. 7 x 4 in.
Loudspeakers P.M. 3 OHMS. 6 in. £1.10; 8 x 5 in. £1.25; 8 x 2 1/2 in. 60p; 8 in. £1.75; 16 in. £1.90.
5 in. WOOFER. 8 w. max. 20-10,000 cps. 8 or 15 ohm £1.80.
ELAC 8 in. De Luxe Ceramic 3 ohm or 15 ohm £2.50.
RICHARD ALLAN TWIN CONE LOUSPEAKERS 8 in. dia. 4 watt; 10 in. dia. 5 watt; 12 in. dia. 6 watt, 3 or 8 or 15 ohm models £1.95 each. Post 15p.
OUTPUT TRANS. EL84, etc. 25p. MIKE TRANS. 50:1 25p.
SPEAKER COVERING MATERIALS. Samples Large 8 A.S.E. GOODMANS OUTPUT TRANSFORMER 5 watt push pull for valves EL84, etc., 3, 8 and 15 ohms 85p. Post 20p.

100 WATT ALL PURPOSE POWER AMPLIFIER

4 inputs speech and music. Response 10-30,000 cps. Matches all loudspeakers. A.C. 200/250V. Treble **£36** Post and Bass controls. Guaranteed. Details S.A.E. Free

ALL EAGLE PRODUCTS

SUPPLIED AT LOWEST PRICES.
ILLUSTRATED EAGLE CATALOGUE 20p. Post free
BARGAIN AM TUNER. Medium Wave. Transistor Superhet. Ferrite aerial. 9 volt. **£4**

BARGAIN 4 CHANNEL TRANSISTOR MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt. **£3**

BARGAIN FM TUNER 88-108 Mc/s Six Transistor. 9 volt. Printed Circuit. Calibrated slide dial tuning. Walnut Cabinet. Size 7 x 6 x 4 inch **£10**


BARGAIN FM TUNER as above. **£7.50**

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built, with volume control. 9v. **£3.50**

COAXIAL PLUG 6p. PANEL SOCKETS 6p. LINE 18p. **OUTLET BOXES.** SURFACE OR FLUSH 25p. **BALANCED TWIN FEEDERS** 5p yd. 80 ohms or 300 ohms. **JACK SOCKET** Side, open-circuit 14p, closed circuit 23p; Chrome Lead Socket 45p. **Phono Plug** 5p. **Phono Socket** 6p. **JACK PLUGS** Sid. Chrome 15p. 3 mm Chrome 14p. **DIN SOCKETS** Chassis 3-pin 11p. 5-pin 19p. **DIN SOCKETS** Lead 3-pin 15p; 5-pin 15p. **DIN PLUGS** 3-pin 18p; 5-pin 25p. **V-LINE HOLDERS.** 8p; CERAMIC 3p; CANS 5p.

E.M.I. TAPE MOTORS. 120v. or 240v. AC. 1,200 r.p.m. 4 pole 135mA Spindle 0.187 x 0.75 in. Size 3 1/2 x 2 1/2 in. (Illustrated). Post 15p. **£1.25**
BALFOUR GRAM MOTORS. 120v. or 240v. AC. 1,200 r.p.m. 4 pole 100mA. Spindle 1 x 3/20. Size. 2 1/2 x 2 1/2 in. Post 15p. **85p**

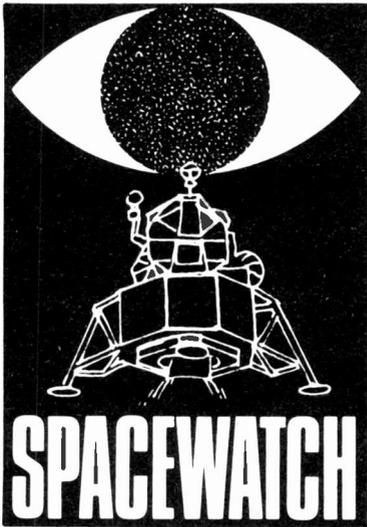Minimum Post and Packing 15p. RETURN OF POST DESPATCH. HI-FI STOCKISTS. CUSTOMERS FREE CAR PARK. CALLERS WELCOME
RADIO COMPONENT SPECIALISTS 337 WHITEHORSE ROAD, CROYDON
Open 9-6 p.m. (Wednesdays 9-1 p.m., Saturdays 9-5 p.m.)
List 5p. Written guarantee with every purchase. (Export: Remit cash and extra postage.) Buses 133, 68 pass door. S.R. Stn. Selhurst. Tel. 01-684-1665



BY FRANK W. HYDE

SOVIET PROBE TO MARS

One of the experiments being carried out on the Soviet probe to Mars, which began with the launching of the Russian *Mars 3* on May 28, indicates extensive Russo-Franco co-operation. This is the first time that a Western European country has been able to "thumb a lift" on an interplanetary probe.

The originators of the new experiment J. L. Steinberg and C. Carubalos of the Observatoire de Meudon are studying solar bursts at metre wavelengths.

The particular study of sudden bursts of radiation from the sun is being carried out because the mechanism of their appearance is not fully understood. The bursts which may last from a few milliseconds to a few seconds are not adequately explained by the thermal motions of electrons. There must be some additional mechanism involving energetic electrons interacting with the magnetic field, and the plasma in the corona.

SOLAR RADIATIONS

Solar radiations are classified into different type groups. The two types involved in this study are Type 1 which last for less than half a second and are strongly polarised, indicating interaction with the coronal field; and Type 3 which are indicated by solar flares, terrestrial magnetic disturbances and auroral effects.

Type 3 bursts last for seconds and the particles that are involved move at very high speeds through the corona. Typically the velocity of the particles may be as high as 100,000 km/second. Type 3 bursts are confined to a cone of direction with an axis that lines up with direction of maximum variation of electron density.

From the earth these can be studied only in two dimensions but with the instrumentation on a probe it will be possible to obtain simultaneous observations from earth and a position in distant space. A partial 3D effect can then be secured. For this reason the French have called this a "stereo experiment". It is hoped that the experiment will reveal how the energy of the bursts is distributed in space and also the total amount of energy that is radiated.

The earth based station will be installed at Nancay in France where the 1,500 metre long radio heliograph is in operation. This radio telescope can provide 50 high resolution radio images of the Sun every second.

On *Mars 3* there is a radio telescope mounted on the solar panels of the spacecraft so that it is always pointing at the Sun. Two identical receivers will be in operation, one on *Mars 3* and one connected to the aerials at Nancay. From the probe data will be telemetered to the USSR where it will be processed and then passed on to France for comparison with their data.

MARINER NINE

The ninth of the *Mariner* series on its way to Mars alone, since *Mariner 8* aborted on May 8 for the reasons given in August *SPACEWATCH*, has been modified to give a compromise survey of the planet. It will go into a 65 degree orbit with periaips at 750 miles.

Under the new scheme less than 70 per cent of the planet will be mapped but with the same resolution as was originally intended. The slant range will be greater for some of the photography and some loss of detail will ensue.

Instead of the original plan of looking at six selected areas every five days it will look at several small areas once every seventeen days. Also, two tapes of data per day will be relayed back to earth instead of three as would have been the case with both vehicles operating. The scheduled programme remains the same at 90 days.

INTERSTELLAR MOLECULES

Using the 300 foot radio telescope at Kitt Peak to observe the emission lines in the millimetre-wave spectrum of the object Sgr B2, which is near the galactic centre, Dr. L. E. Snyder and Dr. D. Buhl have identified the molecules methylacetylene ($\text{CH}_3\text{C}_2\text{H}$) and isocyanic acid (HNCO).

They also found another line in the spectra of two other galactic sources W51 and DR21 though identification was difficult. It is thought that the molecule is isocyanide (HNC) but this opinion is based on laboratory work.

Dr. Snyder is from The University of Virginia and Dr. Buhl from the National Radio Astronomy Observatory.

ARTIFICIAL MARS CHAMBER

At the Institute of Microbiology in Moscow a chamber has been set up to simulate Martian conditions in order to examine the behaviour of different types of micro-organisms. The chamber with a pressure of 7mm of mercury and sharp temperature variations ranging from minus 60 degrees to plus 30 degrees Centigrade, with a minimum amount of moisture, represents the conditions that are as near to that which exists on the planet.

Soil bacteria from the Pamirs, the Kara-Kum desert and Dixon Island in the Arctic Ocean was obtained for the experiment. During the experiments it turned out that microbes and bacteria from Dixon Island had the highest survival factor.

It is thought that the main reason for the survival of terrestrial forms in a Martian environment was the low humidity. Also, it turned out that coloured organisms were able to endure the conditions better.

It seems that pigment is a good protection against the effect of ultra violet rays. There are some workers who think that the changing colour observed on Mars is linked with the activity of micro-organisms.

If there is life on Mars then the cycle involving micro-organisms is a necessary part of any organic process.

TELESCOPES IN SATELLITES

The object of the design of telescopes to be carried by satellites above the turbulent and murky parts of the earth's atmosphere is to obtain improved viewing.

Such instruments are costly and tend to be of relatively large size if they are to exceed the performance of the 200 inch reflector at Mount Palomar. Hopes of any unit of suitable size being put into space seemed to be linked to the advent of the space shuttle since the greatest single weight unit is the mirror.

A solution to the problem has been offered by J. Wilczynski of IBM. He suggests that two mirrors 20 inches in diameter could be put into orbit in such a way that the resolution of the 200 inch telescope could be achieved.

The new telescope would consist of two mirrors arranged to have a common focus by mounting them on a common arm which could be rotated with great precision. The image through the two mirrors would be photographed and the position changed. This would continue until the whole area was covered. By this means any point on any picture would be mathematically related to any other.

Readout—

A SELECTION FROM OUR POSTBAG

Correspondents wishing to have a reply must enclose a stamped addressed envelope. We regret we are unable to guarantee a reply on matters not relating to articles published in the magazine. Technical queries cannot be dealt with on the telephone.

Prior notice please!

Sir—Referring to the correspondence published in your July issue, one of the answers to the general problem of constructors being unable to obtain components, is for the authors of the articles in your magazine and others, to ensure that all components are currently obtainable at the time of issue. The name of the manufacturer of specialised components, including semiconductors should be mentioned, as also sources of supply.

In agreement with Mr P. F. Clarke, prior notice to suppliers would ensure that specialised components could be available within a reasonable time from the date of publication of a constructional article.

My firm is able to supply any component manufactured by Mullard Ltd., on a one-off basis, and this covers many thousands of individual items.

For Mr A. J. Sanders, the components he requires in the way of ferrites and associated hardware, can be supplied off the shelf.

I sympathise with Mr H. Boys of Weedon regarding the Mullard LA 2103 which is obsolete, the number having been changed twice since 1968.

I cannot understand Mr Easterfield's difficulties in obtaining Radiospares components, as all items in their catalogue (available to the trade only) can be supplied to retailers generally throughout the country on the day after an order is placed.

A. F. Trinder,
Gurney's (Radio) Ltd.

Reckless design

Sir—We agree that the points you have raised constitute real problems to the amateur constructor. We would, however, like to make the following comments:

Amateurs often obtain components for their circuits from unusual sources, i.e. cannibalising surplus equipment and by buying from surplus dealers. This means that very often the manufacturer is approached for components which are either obsolete or have been made for a specific purpose against a specific contract.

We as a company are in the process of appointing distributors for our components and would suggest that prior to publishing circuits the designer contacts either ourselves or one of our distributors so as to ascertain the availability.

We would mention that we would expect our distributors to deal not only with industrial customers but with amateur customers as well. It is probable, however, that there would be minimum order charges.

If this kind of liaison could be built up, it should in theory then be possible to arrange for our distributors to hold stocks of particular items, and in fact we see no reason why there should not be some reference at the end of the article as to where the components could be obtained.

We are sympathetic towards amateurs as very often amateur designed circuits eventually become professional circuits, but we do consider that some amateurs are reckless in the extreme by designing circuits without having made sure that the components are available.

The other point we would like to make, is that as manufacturers it is really not a practical proposition for us to deal direct with amateurs, as they only usually require very small quantities and the cost of processing their orders costs more than the goods. This of course emphasises the need for distributors.

J. N. Shipton,
Siemens (United Kingdom) Ltd.

Inadequate details

Sir—I refer to the letter published in the May issue concerning the supply of components to electronic enthusiasts.

In my experience the main problems encountered when dealing with private individuals are exactly those outlined by Mr Hughes. Firstly, ascertaining the exact component required and secondly arranging payment. Often orders give inadequate details and describe the application instead of the component which, rather than enter into correspondence, we tend to reject.

The remedy is for anyone requiring our components to detail accurately the unit required, preferably the type number, but if this is

unknown, the value, working voltage, tolerance, size, etc., and; if the price is also unknown to request a Pro Forma Invoice.

On receiving an order in this form, our Distributor Division will be pleased to supply anyone subject to the following conditions which are necessary to cover the cost of non-standard clerical routines and to protect against the unfavourable economics of special small quantity manufacture:—

1. The order has a minimum value of £3.

2. The component required is in stock or available from Work-in-Progress.

Our Distributor Division carries a broad selection of Eric products, manufactured both in the U.K. and overseas, including ceramic, monolithic and trimmer capacitors, r.f.i. suppression filters, semiconductors and integrated circuits, and is able to provide on request full details of its stock programme.

While appreciating that we can only satisfy in part the demand for specialised, new or non-standard items, we can, if given a business-like order, extend considerably the variety of Eric products previously available to the enthusiast.

R. D. Hurrell,
Distribution Manager,
Eric Electronics Ltd.

Good relations

Sir—I hope I am not too late in replying to your editorial in PRACTICAL ELECTRONICS May issue, which at the same time was related to a letter in *Readout* from M. J. Hughes.

On behalf of our company we would be very pleased to help those electronic enthusiasts who are having trouble in obtaining semiconductors. As stockists for many components we may well be able to offer some of those rather special parts which people need from time to time.

In Worcester we have already served a number of amateur radio enthusiasts with their "ones and twos" requirements and we see no reason why this should not be extended to those other branches of electronics which need similar parts.

As a licensed "ham" I appreciate the feelings of those unable to complete a project for the want of a small part. If readers care to send us their "wants lists", particularly for all types of semiconductors, integrated circuits, capacitors, miniature transformers and so on, we should be glad to do our best to help. What we value most is a satisfied customer whether he buys one part or one thousand, and we have no minimum order charge on those goods we actually hold in stock.

R. C. Evans, G3LQC,
Thorp Electronic Components Ltd.

TTCC-1051 Meter

Miniaturised version of Model C-1052 employing similar ultra compact slimline impact resistant cabinet. Features—large easy to read 1 1/2 in meter with mirror scale, D'Arsonval movement. Overload protection circuit. Fine calibration gives extremely high standard of accuracy on all ranges. Ohms zero adjustment. Click-stop range selection switch. Colour coded scales.

- DC/V: 0.3 15 150 300 1.2kV at 20k/ohms/V
- AC/V: 0.6 30 300 1.3kV at 10k/ohms/V
- DC current: 0-60μA - 300mA
- Resistance: 0-60k - 6M/ohms
- Decibels: -20dB to +17dB
- Complete with battery and test leads



LASKY'S PRICE £4.25 POST 18p


EXCLUSIVE TM-1

MODEL TM-1 MINI-TESTER

The first of Lasky's new-look top value meters, the TM-1 is a really tiny pocket multimeter providing "big" meter accuracy and performance. Precision movement calibrated to 3 in of full scale. Click stop range selection switch. Beautifully designed and made impact resistant black case with white and metallic red/green figuring. Ohms zero adjustment.

Size Only

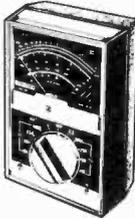- DC/V: 0-100-250-1,000 at 1k OPV
- AC/V: 0-10-50-250-1,000 at 1k OPV
- DC CURRENT: 0-1mA, 100mA
- Resistance: 0-150k
- Decibels: -10dB to 22dB
- Complete with test leads, battery and instructions



LASKY'S PRICE £1.95 POST 13p

TM-5 5K ohms/V POCKET MULTIMETER

Another new look pocket multimeter from Lasky's providing top quality and value. The "slimline" impact resistant case, size 4 1/2 in X 2 1/2 in X 1 1/2 in, fitted with extra large 2 1/2 in square meter. Readability is superior on all low ranges; making this an excellent instrument for servicing transistorised equipment. Recessed click stop selection switch. Ohms zero adjustment. Buff finish with crystal clear meter cover.

- DC/V: 3-15-150-300-1,200 at 5k OPV
- AC/V: 6-30-300-600 at 2.5k OPV
- DC Current 0-300μA, 0-300mA
- Resistance: 0-10k/ohms, 0-1M ohm
- Decibels: -10dB to +16dB
- Complete with test leads, battery and instructions.

LASKY'S PRICE £2.95 POST 13p

BSR McDONALD MP60

High precision low-mass counterbalanced pick-up arm, heavy balanced turntable, simple to operate controls, viscous cueing device, slide in cartridge carrier, 4 pole motor.

BSR McDONALD MP60 UNITS & PACKS.

A. Chassis only. B. Complete with Lasky's plinth and cover. C. Complete with Lasky's plinth, cover and AD76K cartridge. D. Comp. wired on BSR plinth with cover. E. as D, plus AD76K cartridge.

MODEL	A	B	C	D	E
610	£15.45	£18.75	£22.50	£24.50	£28.50
510	£13.45	£16.95	£20.75	£22.00	£26.00
310	£9.95	£13.45	£17.25	£21.00	£23.50
MP60	£12.50	£15.75	£19.50	£21.50	£25.50

GARRARD UNITS AND PACKAGES MODEL SL55B

Four speed auto changer

LASKY'S PRICE £10.50 POST 35p

Garrard SP25 Mk. III	£11.50	Garrard AP76 without cart.	£20.95
Garrard SP25 Mk. III wired	£12.00	Garrard 3,000 with 9TA cart.	£10.50
Garrard SP25 Mk. II with 9TA cart.	£13.95	Garrard 2025TC with 9TA cart.	£9.85
Garrard AP76 with AD76K cart. and Lasky's plinth and cover.	£35		
Garrard AP76 with Shure M44E cart. and Lasky's plinth and cover.	£40		
Garrard SP25 Mk. III. AD76K cart. and Lasky's plinth and cover.	£20		
Garrard SP25 Mk. III. Micro M2100/c cart. and Lasky's plinth and cover	£25		

POST FOR ALL PACKAGES 50p

Lasky's Radio Limited

Branches

207 EDGWARE ROAD, LONDON, W.2 Tel: 01-723 3271

33 TOTTENHAM CT. RD., LONDON, W.1 Tel: 01-636 2605

Open all day, 9 a.m. - 6 p.m. Monday to Saturday

152/3 FLEET STREET, LONDON, E.C.4 Tel: 01-353 2833

Open all day Thursday, early closing 1p.m. Saturday

The Home of High Fidelity

42-45 TOTTENHAM CT. RD., LONDON, W.1 Tel: 01-580 2573

Open all day, 9 a.m. - 6 p.m. Monday to Saturday


NEW CITY BRANCH NOW OPEN

109 FLEET STREET, LONDON, E.C.4 Tel: 01-353 5812

Open all day Thursday, early closing 1p.m. Saturday

ALL MAIL ORDERS AND CORRESPONDENCE TO: 3-15 CAVELL ST. TOWER HAMLETS, LONDON, E.1 Tel.: 01-790 4821

DIGITAL CLOCK SCOOP

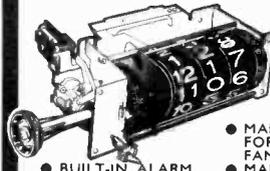

- SHOCK AND VIBRATION PROOF
- 12-HOUR ALARM
- AUTO "SLEEP" SWITCH
- HOURS, MINUTES AND SECONDS READ-OFF
- FORWARD AND BACKWARD TIME ADJUSTMENT
- SILENT OPERATION SYNCHRONOUS MOTOR
- MADE ESPECIALLY FOR LASKY'S BY FAMOUS MAKER
- MAINS OPERATION

EXCLUSIVELY FROM LASKY'S in chassis form for you to mount in any housing. The clock measures 4 1/2 W x 1 1/2 H x 3 1/2 D (overall from front of drum to back of switch). SPEC.: 210/240V AC, 50Hz operation; switch rating 250V, 3A. Complete with instructions.


HUNDREDS OF APPLICATIONS. COMPLETE WITH KNOBS

LASKY'S PRICE £6.95 POST 18p

SPECIAL QUOTATIONS FOR QUANTITIES

TMK LAB 100

A highly accurate yet rugged Multitester using a 10μA meter hand calibrated to a DC accuracy of 3% of full scale. Special features—ultra large meter scale 6 1/2 x 3 1/2 in incorporating an entirely new type of range selection panel which gives instant range identification without taking your eyes from the meter. An audible buzzer is provided for easy short testing. SPEC.: DC/V ranges: 0-5, 2.5, 10, 50, 250, 500, 1,000V at 100k/ohms. AC/V ranges: 3, 10, 50, 250, 500, 1,000V at 5k/ohms. DC current: 0-10, 100μA, 0-10, 100mA, 0-2.5, 10A. Resistance: 0-1k, 10k, 100k, 10M, 100M/ohms. Decibels: 10 to 49dB. Continuity test. Audible buzzer. Operates on 11-5V U2 and 1 1/2 15V 154 type batteries. Cabinet size 7 1/2 x 6 1/2 x 3 1/2 in. Weight 4lb.

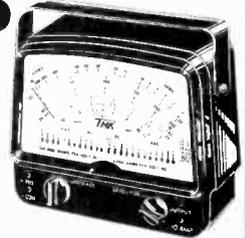

LASKY'S PRICE £17.75 POST 25p

TMK MODEL 200 METER KIT

TMK offer the unique opportunity of building a really first-class precision multimeter at a worthwhile saving in cost. The cabinets are supplied with the meter scale and movement mounted in position. The highest quality components and 1% tolerance resistors are used throughout. Supplied complete with full constructional circuit and operating instructions.


Specification
20,000 P.O.V. Multimeter. Features 24 measurement ranges with mirror scale accuracy. DC/V and current: 2%. A.C./V: 3%. Resistance 3%. Special 0-6V DC range for transistor circuit measurements.



ONLY

LASKY'S PRICE £4.60 POST 13p

TTC Model A-1005 FM TUNER CHASSIS

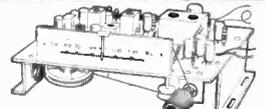

1,000's sold of this highly sensitive FM tuner—fully tunable—range 88 to 108 Mc/s. Completely wired on printed circuit 10.3 Mc/s IF. 6 transistors and 3 diodes. Slow motion tuning drive. Size 6 1/2 x 4 x 2 1/2 in. Operates from any 9V DC source. Full data and circuit supplied.

LASKY'S PRICE £6.50 POST 18p

ADD MULTIPLEX to the MODEL A-1005

You can enjoy stereo sound with the Model A-1005 FM Tuner above by adding the TTC Model A-1005M Multiplex Adaptor. Brief specification: MPX input sensitivity 100mV. Output 150mV. Self-powered by a 9V battery. 4 transistor and 6 diode circuit. Size 5 1/2 x 2 x 2 1/2 in. Also suitable for use with other FM tuners with MPX input.

LASKY'S PRICE £4.95 POST 18p



Great new OFFER from **DIOTRAN** TRANSISTORS

BRAND NEW FULLY GUARANTEED DEVICES

AC107	15p	AF115	17p	BC140	35p	BCY31	22p	BF272	80p	EC403	15p	ORP60	40p	2N918	30p	2N2714	25p	2N3704	15p
AC113	20p	AF116	17p	BC141	35p	BCY32	25p	BF273	30p	GET880	27p	ORP61	40p	2N929	22p	2N2904	25p	2N3705	12p
AC115	23p	AF117	17p	BC142	45p	BCY33	17p	BF274	30p	MAT100	15p	ST140	12p	2N930	25p	2N2904A	30p	2N3706	12p
AC125	17p	AF118	30p	BC143	40p	BCY34	20p	BF308	35p	MAT101	17p	ST141	17p	2N931	20p	2N2905	30p	2N3707	12p
AC126	17p	AF124	21p	BC145	45p	BCY70	17p	BF309	37p	MAT120	15p	T1543	40p	2N932	22p	2N2905A	30p	2N3708	8p
AC127	17p	AF125	20p	BC147	17p	BCY71	30p	BF316	30p	BF316	30p	MAT121	17p	2N933	27p	2N2906	25p	2N3709	8p
AC128	17p	AF126	20p	BC148	12p	BCY72	15p	BFV10	15p	MPF102	43p	V405A	25p	2N934	20p	2N2906A	27p	2N3710	10p
AC141K	17p	AF127	20p	BC149	17p	BCZ11	20p	BFX29	27p	MPF105	30p	OC19	30p	2N935	20p	2N2907	25p	2N3711	10p
AC142K	17p	AF139	33p	BC150	17p	BD121	85p	BFX84	20p	OC19	30p	2G301	19p	2N936	22p	2N2907A	30p	2N3711A	10p
AC151	15p	AF178	50p	BC151	20p	BD123	85p	BFX85	27p	OC20	50p	2G302	19p	2N937	20p	2N2908	25p	2N3712	10p
AC154	15p	AF179	50p	BC152	17p	BD124	75p	BFX86	22p	OC22	30p	2G303	19p	2N938	20p	2N2909	25p	2N3713	10p
AC155	17p	AF180	50p	BC153	27p	BD131	80p	BFX87	25p	OC23	33p	2G304	20p	2N939	20p	2N2910	25p	2N3714	10p
AC156	17p	AF191	50p	BC134	30p	BD132	80p	BFX88	22p	OC24	45p	2G306	35p	2N940	20p	2N2911	25p	2N3715	10p
AC157	17p	AF186	45p	BC137	20p	BDY20	£1	BFY50	20p	OC25	25p	2G308	35p	2N941	20p	2N2912	25p	2N3716	10p
AC165	17p	AF239	37p	BC158	17p	BF115	22p	BFY51	20p	OC26	25p	2G309	35p	2N942	20p	2N2913	25p	2N3717	10p
AC166	17p	AF211	37p	BC159	20p	BF117	45p	BFY52	20p	OC28	40p	2G339	40p	2N943	20p	2N2914	25p	2N3718	10p
AC167	20p	AFZ12	45p	BC167	13p	BF118	60p	BFY53	17p	OC29	40p	2G339A	15p	2N944	20p	2N2915	25p	2N3719	10p
AC168	20p	AL102	85p	BC168	13p	BF119	70p	BSX19	15p	OC35	33p	2G344	15p	2N945	20p	2N2916	25p	2N3720	10p
AC169	14p	AL103	85p	BC169	13p	BF152	35p	BSX20	15p	OC36	40p	2G345	15p	2N946	20p	2N2917	25p	2N3721	10p
AC176	23p	ASV26	30p	BC170	13p	BF153	35p	BSY25	15p	OC41	20p	2G371	13p	2N947	20p	2N2918	25p	2N3722	10p
AC177	20p	ASV27	30p	BC171	13p	BF154	35p	BSY26	15p	OC42	22p	2G371B	10p	2N948	20p	2N2919	25p	2N3723	10p
AC187	30p	ASV28	25p	BC172	13p	BF157	45p	BSY27	15p	OC44	15p	2G374	17p	2N949	20p	2N2920	25p	2N3724	10p
AC188	30p	ASV29	25p	BC173	13p	BF158	25p	BSY28	15p	OC45	12p	2G377	17p	2N950	20p	2N2921	25p	2N3725	10p
ACY17	25p	ASV50	25p	BC174	13p	BF159	30p	BSY29	15p	OC70	15p	2G378	15p	2N951	20p	2N2922	25p	2N3726	10p
ACY18	20p	ASV51	25p	BC175	22p	BF160	30p	BSY38	15p	OC71	9p	2G382	15p	2N952	20p	2N2923	25p	2N3727	10p
ACY19	22p	ASV52	25p	BC177	17p	BF162	30p	BSY39	15p	OC72	13p	2G401	30p	2N953	20p	2N2924	25p	2N3728	10p
ACY20	20p	ASV54	25p	BC178	17p	BF163	35p	BSY40	15p	OC74	12p	2G414	30p	2N954	20p	2N2925	25p	2N3729	10p
ACY21	18p	ASV55	25p	BC179	17p	BF164	35p	BSY41	15p	OC75	15p	2G417	25p	2N955	20p	2N2926	25p	2N3730	10p
ACY22	19p	ASV56	25p	BC180	20p	BF165	35p	BSY95	12p	OC76	15p	2N388	30p	2N956	20p	2N2927	25p	2N3731	10p
ACY27	18p	ASV57	25p	BC181	22p	BF167	22p	BSY95A	12p	OC77	25p	2N388A	30p	2N957	20p	2N2928	25p	2N3732	10p
ACY28	19p	ASV58	25p	BC182	10p	BF173	22p	BU105	£3.90	OC81	15p	2N404	30p	2N958	20p	2N2929	25p	2N3733	10p
ACY29	30p	ASV58	25p	BC182L	10p	BF176	35p	CI11E	60p	OC81D	15p	2N404A	30p	2N959	20p	2N2930	25p	2N3734	10p
ACY30	25p	ASZ21	40p	BC183	10p	BF177	35p	C400	30p	OC82	15p	2N404A	30p	2N960	20p	2N2931	25p	2N3735	10p
ACY31	25p	BC107	10p	BC183L	10p	BF178	45p	C407	25p	OC82D	15p	2N527	60p	2N961	20p	2N2932	25p	2N3736	10p
ACY34	18p	BC108	10p	BC184	13p	BF179	50p	C424	17p	OC83	20p	2N696	12p	2N962	20p	2N2933	25p	2N3737	10p
ACY35	18p	BC109	11p	BC184L	13p	BF180	30p	C425	40p	OC84	20p	2N697	15p	2N963	20p	2N2934	25p	2N3738	10p
ACY36	30p	BC113	25p	BC186	27p	BF181	30p	C426	30p	OC139	15p	2N698	24p	2N964	20p	2N2935	25p	2N3739	10p
ACY40	15p	BC114	30p	BC187	27p	BF182	30p	C428	20p	OC140	17p	2N699	55p	2N965	20p	2N2936	25p	2N3740	10p
ACY41	18p	BC115	30p	BC207	11p	BF183	30p	C441	27p	OC170	15p	2N706	7p	2N966	20p	2N2937	25p	2N3741	10p
ACY44	35p	BC116	35p	BC209	11p	BF184	30p	C442	35p	OC171	15p	2N706A	7p	2N967	20p	2N2938	25p	2N3742	10p
AD140	40p	BC117	35p	BC209	11p	BF185	30p	C444	37p	OC200	25p	2N708	45p	2N968	20p	2N2939	25p	2N3743	10p
AD142	40p	BC118	25p	BC212L	11p	BF188	30p	C450	17p	OC201	27p	2N709	40p	2N969	20p	2N2940	25p	2N3744	10p
AD149	43p	BC119	45p	BC213L	11p	BF194	23p	C720	12p	OC202	27p	2N711	40p	2N970	20p	2N2941	25p	2N3745	10p
AD161	35p	BC125	35p	BC213L	11p	BF195	24p	C722	25p	OC203	25p	2N717	42p	2N971	20p	2N2942	25p	2N3746	10p
AD162	35p	BC126	35p	BC214L	12p	BF196	30p	C740	25p	OC204	25p	2N718	24p	2N972	20p	2N2943	25p	2N3747	10p
AD161		BC132	25p	BC225	25p	BF197	35p	C742	17p	OC205	35p	2N718A	50p	2N973	20p	2N2944	25p	2N3748	10p
16Z(HP)	63p	BC134	30p	BC226	35p	BF200	45p	C744	17p	OC309	35p	2N726	27p	2N974	20p	2N2945	25p	2N3749	10p
ADT140	50p	BC135	30p	BC317	12p	BF222	80p	C760	17p	P346A	17p	2N727	27p	2N975	20p	2N2946	25p	2N3750	10p
ADZ11	£2	BC136	30p	BC318	12p	BF257	35p	C762	17p	P397	45p	2N743	17p	2N976	20p	2N2947	25p	2N3751	10p
ADZ12	£2.10	BC137	35p	BC319	12p	BF270	25p	C764	60p	OCP71	43p	2N744	17p	2N977	20p	2N2948	25p	2N3752	10p
AF114	17p	BC139	45p	BCY30	20p	BF271	17p	CE401	15p	ORP12	43p	2N914	17p	2N978	20p	2N2949	25p	2N3753	10p

DIODES & RECTIFIERS

8p	AA119	8p	BYZ11	32p	OAB1	7p
12p	AA120	8p	BYZ12	30p	OAB5	7p
45p	BA116	22p	BYZ13	25p	OAG0	6p
40p	BA126	22p	BYZ16	35p	OAG1	7p
42p	BY100	15p	BYZ17	35p	OAG5	7p
15p	BY101	12p	BYZ18	30p	OA200	6p
50p	BY105	15p	BYZ19	25p	OA202	7p
27p	BY114	12p	OA5	17p	SO10	4p
27p	BY126	15p	OA10	22p	SO19	4p
17p	BY127	15p	OA47	7p	IN914	6p
17p	BY130	15p	OA70	7p	IN916	6p
17p	BYZ10	35p	OA79	8p	IN418	6p

1,000,000

NP-NPN PLASTIC AND METAL CAN TYPES

Clearance of manufacturers' seconds, selected in types and guaranteed no open or short circuit units. Ideal cheap transistors for radio enthusiasts, manufacturers, schools and colleges.

TYPE STN18. Silicon Planar Transistors npn TO-18 Metal Can. Types similar to: 2N706, 2N2238, BSY27-95A, BSX44-76-77. Price: 500 £9, 1,000 £15

TYPE STP18. Silicon Planar Transistors npn TO-18 Metal Can. Types similar to: BCY70-72, 2N2906-7, 2N2411 and BC186-7. Also used as complementary to the above npn type device type STN18. Price: 500 £9, 1,000 £15

TYPE STNL. Silicon Planar Epitaxial Planar Transistors TO-92 case. I.C. 200mA, 300mW medium to high gain, available in npn or pnp and types similar to: NPN2N2926-2N2711-2N3391-2N3707-2N3711-BC167-8-9. Price: 500 £7.50, 1,000 £13

TYPE STPL. As above but in pnp and similar to types 2N5354-56, 2N4058-2N4061 and 2N3702-3. Also used as complementary to the above npn devices type STNL. Price: 500 £7.50, 1,000 £13

TYPE STNK. Silicon Planar Plastic Transistor npn with TO-18 pin circular lead configuration, I.C. 200mA, 300mW and similar to BC107-8-9, BC170, BC173, BC182-184, BC237-8-9 and BC337-8. Price: 500 £9.50, 1,000 £16

When ordering, please state type required, i.e., STNK or STN18, etc.

1,000,000

SILICON TRANSISTORS FOR SALE

Clearance of npn Silicon Transistors from the 2S300 (TO-5) and 2S320 (SO-2) range and similar to the GC200-205 and BCY30-34 series. Ideal for Amateur Electronics, Radio Hams and for experimental use in Schools, Colleges and Industry.

Approximate count by weight:
100 off—75p (plus p. & p. 10p)
300 off—£1.75 (plus p. & p. 15p)
500 off—£2.50 (plus p. & p. 17p)
1,000 off—£4 (plus p. & p. 25p)
10,000 off—£35 (plus p. & p. 55p)

Large quantities quoted for on request. EXPORT INQUIRIES WELCOME

DIOTRAN

SALES

PO BOX 5, WARE, HERTS

Full Money-Back Guarantee

POSTAGE & PACKING 7p

10 MILLION DIODES

Silicon or Germanium

State which when ordering

200	50p	10,000	£10.00
1,000	£2.00	50,000	£30.00
5,000	£7.00	100,000	£50.00

2,000,000 SILICON

PLANAR TRANSISTORS

TO18 P.N.P. & N.P.N. TYPES

State which when ordering

100	£1.50	10,000
-----	-------	--------

Duty bound

Sir—I am following with considerable interest the correspondence and your remarks in P.E. relating to supplies of special electronic components to the amateur.

It may be of interest to your readers to know that the British Amateur Electronics Club appears to anticipate the demand by amateurs in some cases. This is probably because we are an amateur organisation, and the problems relating to minimum economical orders do not apply.

As an example, when the British Amateur Electronics Club started in 1966, silicon controlled rectifiers available in this country were very expensive. However, the B.A.E.C. was able to obtain good quality SCR's in America at very low prices, even after paying duty and additional postage.

Members of the B.A.E.C. are able to obtain specialised electronic components either at cost or, if they are required for experimental purposes and the member undertakes to write an article on his experiments for the B.A.E.C. Newsletter, they are provided free of charge.

The B.A.E.C. has recently been able to obtain very cheap but perfect voltage regulator integrated circuits and also inexpensive infrared and visible-light semiconductor generators (L.E.D.) and receivers (photo-transistors).

These, as you know, are available in this country at relatively high prices, but I think that if any supplier in this country, who is interested in the amateur market, were to study the advertisements in amateur electronic magazines published in America, they, too, would be able to supply sophisticated and up-to-date electronic devices at reasonable prices to the amateur.

However, this does not apply to the well-known SN74 TTL integrated circuits which are in fact cheaper in this country than in America.

C. Bogod,
British Amateur Electronics Club

Opposite view

Sir—Having been a home constructor for a number of years, I would like to present the opposite view in your correspondence on the subject of components, and their availability.

I have rarely, if ever, experienced difficulty in obtaining components I require, even by mail order. Having lived in an area close to the majority of component retailers, I received, with few exceptions, courteous assistance and good service during personal buying of parts.

As I am no longer able to shop personally, due to a change of resi-

dence to another area of the country, I have, for the past year been buying by mail. Parcels received have been well packed, again with few exceptions, and refunds for out of stock items cheerfully and promptly given. In the case of the exceptions, a simple, well worded letter of complaint direct to the sales manager has usually cleared matters in a fortnight or less.

Considering the amount of business done by mail order, it is surprising that the service of most retailers is as good as it is, indeed, it could be far worse.

While I would also concur with the view that "one-offs" and highly specialised components are a loss maker for the firm who are prepared to deal with them, I would express surprise that the people who complain about being unable to obtain them, while deeming themselves capable of constructing, testing and setting to work a piece of often complex equipment, are unable to write to suppliers for their catalogues and find a replacement.

The one possible exception to the last paragraph is the amateur radio enthusiast, who, following the demise of the only manufacturer (Electroniques) in the country supplying r.f. coils to tune the amateur bands, has the dubious choice between bodging commercially available coils or winding his own.

To conclude, if components cannot be bought, begged or borrowed for the special project, there is a solution—set up in business and supply your own components!

P. J. Brent,
Helensburgh,
Scotland.

Final tip

Sir—I have just received PRACTICAL ELECTRONICS magazine July issue, and after reading *Readout* I cannot understand why a number of your readers have such a problem trying to obtain parts for various circuits.

For instance, a 6-pole 5-way switch (letter on page 585), an advertisement for this appears on the opposite page 584, I think that a lot of readers do not take enough trouble to read the various advertisement pages for items wanted.

I have always found most manufacturing companies or large distributors very helpful regarding where to obtain special parts providing you keep your request brief, enclose an s.a.e. and make sure that your letter can be read.

A final tip, always keep by your side a number of catalogues from various companies, this can make life a lot easier.

D. J. Brown,
Coventry.



CLAIM!

I have information which may help Sheriff Maynes-Humm, our lively guardian of the peace. Last night I was standing on the Wheatstone Bridge on the Newton by-pass near to the p-n junction. I had been to the "Silicon" chip shop to bring some feedback when Current passed me at some speed. He showed no sign of stopping and in the minority carrier on his megacycle I noticed the mentioned joules.

May I say that the frequency of this type of crime committed by Current is something that, socially, Hertz. I recall that not long ago the same thing happened to two other pretty dynes, the lovely Cath Ode and her cooler sister An Ode.

It is to be hoped that all who know the much loved Milli will help to get back to health, transformer situation, and insulator from any future attacks. Watts more, I trust that Current will be put on charge and if not given the potential drop then made to walk the Planck.

I am sorry if my reaction seems unusually strong but the core of the matter is that Eddy Current is one of my two ill-begotten sons who have always wasted energy. I could never control them and many are the times that I have had to cover up for them. But to no avail, and matters that for Eddy and his equally heated brother I squared no losses. This has always peaked me and as far as I am concerned both are transients.

R. M. S. Current,
Waverley.

YATES ELECTRONICS

(FLITWICK) LTD.

RESISTORS

1/4W Iskra high stability carbon film—very low noise—capless construction. 1/4W Mullard CR25 carbon film—very small body size 7.5 x 2.5mm. 4W Erie wire wound.

Power	Tolerance	Range	Valves available	1-99	100+
1/4	5%	4.7Ω-2.2MΩ	E24	1.0p	0.8p
1/4	10%	3.3MΩ-10MΩ	E12	1.0p	0.8p
1/4	10%	1Ω-3.9Ω	E12	1.0p	0.8p
1/4	5%	4.7Ω-1MΩ	E12	1.0p	0.8p
4	10%	1Ω-10Ω	E12	7.5p	7.5p

Quantity price applies for any selection. Ignore fractions on total order.

DEVELOPMENT PACK

0.5 watt 5% Iskra resistors 5 off each value 4.7Ω to 1MΩ.
E12 pack 325 resistors £2.50.
E24 pack 650 resistors £4.80.

MULLARD POLYESTER CAPACITORS C296 SERIES

400V: 0.001μF, 0.0015μF, 0.0022μF, 0.0033μF, 0.0047μF, 2.2p, 0.0068μF, 0.01μF, 0.015μF, 0.022μF, 0.033μF, 3p, 0.047μF, 0.068μF, 0.1μF, 4p, 0.15μF, 6p, 0.22μF, 7.5p, 0.33μF, 11p, 0.47μF, 13p.
160V: 0.01μF, 0.015μF, 0.022μF, 0.033μF, 0.047μF, 0.068μF, 3p, 0.1μF, 0.15μF, 0.22μF, 4p, 0.33μF, 6p, 0.47μF, 7.5p, 0.68μF, 11p, 1.0μF, 12.5p.

MULLARD POLYESTER CAPACITORS C280 SERIES

250V P.C. mounting: 0.01μF, 0.015μF, 0.022μF, 3p, 0.033μF, 0.047μF, 0.068μF, 3.5p, 0.1μF, 4p, 0.15μF, 0.22μF, 5p, 0.33μF, 6.5p, 0.47μF, 8.5p, 0.68μF, 11p, 1.0μF, 13p.

MYLAR FILM CAPACITORS

100V: 0.001μF, 0.002μF, 0.005μF, 0.01μF, 0.02μF, 2.5p, 0.04μF, 0.05μF, 0.068μF, 0.1μF, 3.5p.

CERAMIC DISC CAPACITORS

100pF to 10,000pF, 2p each.

CAPACITOR DEVELOPMENT PACK

Selection of 100 ceramic and polyester capacitors, 100pF to 1.0μF, £2.90.

ELECTROLYTIC CAPACITORS—One Price—5p Each

Mullard C426 series (μF/V): 25/6.4, 50/6.4, 100/6.4, 200/6.4, 320/6.4, 16/10, 32/10, 64/10, 125/10, 200/10, 10/16, 20/16, 40/16, 80/16, 125/16, 6.4/25, 12.5/25, 25/25, 50/25, 80/25, 4/40, 8/40, 16/40, 32/40, 50/40, 2.5/64, 5/64, 10/64, 32/64.
Miniature P.C. mounting (μF/V): 10/12, 50/12, 100/12, 200/12, 5/25, 10/25, 25/25, 100/25.

POTENTIOMETERS

Carbon track 5kΩ to 1MΩ, log or linear (log 1/4W, lin 1/4W). Single, 12p. Dual gang (stereo), 40p.

SKELETON PRESET POTENTIOMETERS

Linear: 100, 250, 500Ω and decades to 5MΩ. Horizontal or vertical P.C. mounting (0.1 matrix). Sub-miniature 0.1 watt, 4p each. Miniature 0.25 watt, 5p each.

SEMICONDUCTORS

AC126	15p	BFY52	22p	OC81	15p	2N3055	72p
AC127	15p	BSY56	30p	OC82	15p	2N3702	15p
AC128	15p	BSX21	25p	ORP12	47p	2N3703	14p
AD140	40p	BY124	7.5p	IN4001	7.5p	2N3704	17.5p
AF115	17.5p	BY210	30p	IN4002	10p	2N3705	15p
AF117	17.5p	BY213	20p	IN4003	11p	2N3706	12p
BC107	14p	OA95	7.5p	IN4004	12.5p	2N3707	18.5p
BC108	10p	OA91	7.5p	IN4005	14p	2N3708	10p
BC109	10p	OA202	7.5p	IN4006	15p	2N3709	11p
BFY50	22p	OC71	15p	IN4007	16p	2N3710	12p
BFY51	19p	OC72	15p	2N2926	11p	2N3711	14p

ZENER DIODES

400mW 5% 3.3V to 30V, 17p.

VEROBOARD

	0.1	0.15		0.15	0.1
2 1/2 x 3 1/2	22p	16p	17 x 3 1/2 (plain)	52 1/2p	—
2 1/2 x 5	24p	24p	17 x 2 1/2 (plain)	37 1/2p	—
3 1/2 x 3 1/2	24p	24p	2 1/2 x 5 (plain)	17 1/2p	—
3 1/2 x 5	27p	27p	2 1/2 x 3 1/2 (plain)	15p	—
17 x 2 1/2	75p	57 1/2p	Pin insertion tool	47 1/2p	47 1/2p
17 x 3 1/2	100p	75p	Spot face cutter	37 1/2p	37 1/2p
17 x 5 (plain)	—	75p	Pkt. 50 pins	20p	20p

ROTARY SWITCHES

2P2W, 1P12W, 2P6W, 3P4W, 4P3W, 22.5p.

PLUGS AND SOCKETS

Standard 1/4 in screened	17 1/2p	2.5mm insulated	7 1/2p
Standard 1/4 in insulated	14p	3.5mm insulated	7 1/2p
Stereo 1/4 in screened	35p	3.5mm screened	12 1/2p
Standard 1/4 in socket	15p	2.5mm socket	7 1/2p
Stereo 1/4 in socket	17 1/2p	3.5mm socket	7 1/2p

BRUSHED ALUMINIUM PANELS

12" x 6" = 25p; 12" x 2 1/2" = 10p; 9" x 2" = 7p.

C.W.O. please. Post and packing, please add 10p to orders under £2. Data sheets are available for most of the components listed, and will be sent free on request.

BE39 ELSTOW STORAGE DEPOT, KEMPSTON HARDWICK, BEDFORD

THE MOTORIST WHO CARES FOR HIS CAR...



READS PRACTICAL motorist

the most widely read motoring monthly published on the 15th of the month — 15p

IN 15 MINUTES YOU COULD HAVE CAPACITIVE DISCHARGE ELECTRONIC IGNITION FITTED TO YOUR CAR

Capacitive Discharge Ignition is recognised as being the most efficient ignition system and will give you:

- CONTINUAL PEAK PERFORMANCE
- UP TO 20% REDUCED FUEL CONSUMPTION
- EASIER ALL-WEATHER STARTING
- INCREASED ACCELERATION & TOP SPEED
- LONGER SPARK PLUG LIFE
- INCREASED BATTERY LIFE
- CONTACT BURN ELIMINATED
- PURER EXHAUST GAS EMISSION
- RADIO INTERFERENCE SUPPRESSED



For all petrol engines—cars, boats, etc. Guaranteed for 5 yrs.

Complete Installation Kit for 12-volt vehicles £12.95 + 35p P. & P. State earth polarity of vehicle POSITIVE or NEGATIVE earth. Unit Construction Kit also available for the radio electronics constructor £9.95 + 35p P. & P. The construction kit includes instructions and all components for wiring as positive or negative earth, and is complete with the stove enamelled steel case and aluminium base. All components are available separately.

ELECTRONIC DESIGN ASSOCIATES 82 BATH STREET, WALSALL WS1 3DE

BUILD THIS WAH-WAH PEDAL KIT



AND SAVE £££'s

- Please send me
- Selective amplifier module £1.75
- Foot Volume control pedal £5.13
- COMPLETE KIT £6.50
- add 38p for assembly of module
- Send 15p for latest catalogue


Name _____
Address _____

*Tick as required
WILSIC ELECTRONICS LTD.
6 COPLEY RD. DONCASTER, YORKS.

The Wilsic Wah-Wah pedal comprises a SELECTIVE AMPLIFIER MODULE KIT, containing all the components to build a two transistor circuit module, which may be used by the constructor for his own design or fitted to the FOOT VOLUME CONTROL PEDAL (as photo) converting it to Wah-Wah operation. This pedal is in strong fawn plastic and fitted with output lead and screened plug.

new

Super IC-12

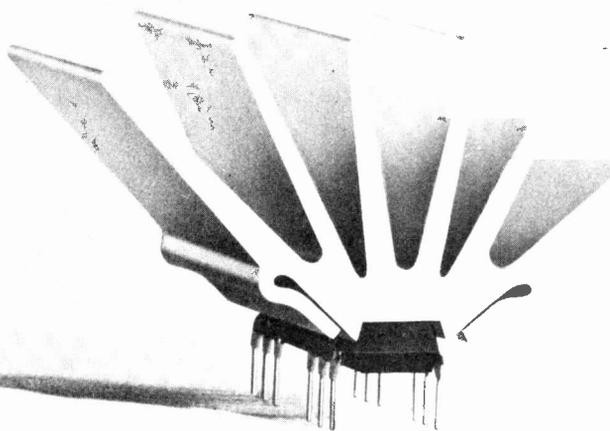

High fidelity Monolithic Integrated Circuit Amplifier

Two years ago Sinclair Radionics announced the World's first monolithic integrated circuit Hi-Fi amplifier, the IC.10. Now we are delighted to be able to introduce its successor, the Super IC.12. This 22 transistor unit has all the virtues of the original IC.10 plus the following advantages:

1. Higher power.
2. Fewer external components.
3. Lower quiescent consumption.
4. Compatible with Project 60 modules.
5. Specially designed built-in heat sink. No other heat sink needed.
6. Full output into 3, 4, 5 or 8 ohms.
7. Works on any voltage from 6 to 28 volts without adjustment.
8. NEW 22 transistor circuit.

Output power 6 watts RMS continuous (12 watts peak).

Frequency Response 5 Hz to 100KHz \pm 1 dB.

Total Harmonic Distortion Less than 1%. (Typical 0.1%) at all output powers and all frequencies in the audio band.

Load Impedance 3 to 15 ohms.

Power Gain 90dB (1,000,000,000 times) after feedback.


Supply Voltage 6 to 28 volts (Sinclair PZ-5 or PZ-6 power supplies ideal).

Size 22 x 45 x 28 mm including pins and heat sink.

Input Impedance 250 Kohms nominal.

Quiescent current 8mA at 28 volts.

With the addition of only a very few external resistors and capacitors the Super IC.12 makes a complete high fidelity audio amplifier suitable for use with pick-up, F.M. tuner etc. Alternatively, for more elaborate systems, modules in the Project-60 range such as the Stereo 60 and A.F.U. may be added. The comprehensive manual supplied with each unit gives full circuit and wiring diagrams for a large number of applications in addition to high fidelity. These include car radios, oscillators etc. The very low quiescent consumption makes the Super IC.12 ideal for battery operation.

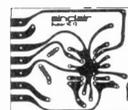

Price, inc. FREE printed circuit board for mounting.

£2.98 Post free



SINCLAIR GENERAL GUARANTEE
Should you not be completely satisfied with your purchase when you receive it from us, return the goods without delay and your money will be refunded in full, including cost of return postage, at once and without question. Full service facilities are available to all Sinclair customers.

Sinclair Radionics Ltd, London Rd, St. Ives Huntingdonshire PE17 4HJ
Telephone St Ives (048 06) 4311

sinclair

Sinclair Project 60

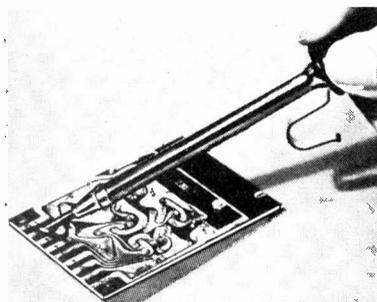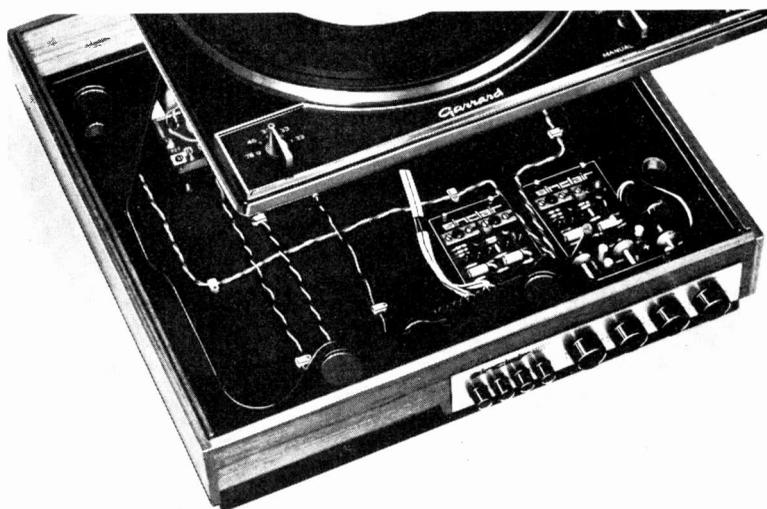The World's leading range of high fidelity modules



Project 60 offers more advantage to the constructor and user of high fidelity equipment than any other system in the world.

Performance characteristics are so good they hold their own with any other available system irrespective of price or size.

Project 60 modules are more versatile – using them you can have anything from a simple record player or car radio amplifier to a sophisticated and powerful stereo tuner-amplifier. Either power amplifier can be used in a wide variety of applications as well as high fidelity. The Stereo 60 pre-amplifier control unit may also be used with any other power amplifier system, as can the AFU filter unit. The stereo FM tuner operates on the unique phase lock loop principle to provide the best ever standards of sensitivity and audio quality. Project 60 modules are very easily connected together by following the 48 page manual supplied free with all Project 60 equipment. The modules are great space savers too and are sold individually boxed in distinctive white and black cartons. With all these wonderful advantages, there remains the most attractive of all – price. When you choose Project 60 you know you are going to get the best high fidelity in the world, yet thanks to Sinclair's vast manufacturing resources (the largest in Europe) prices are fantastically low and everything you buy is covered by the famous Sinclair guarantee of reliability and satisfaction.

Typical Project 60 applications

System	The Units to use	together with	Cost of Units
Simple battery record player	Z.30	Crystal P.U., 12V battery volume control	£4.48
Mains powered record player	Z.30, PZ.5	Crystal or ceramic P.U. volume control etc.	£9.45
20 + 20 W. stereo amplifier for most needs	2 x Z.30s, Stereo 60, PZ.5	Crystal, ceramic or mag. P.U., F.M. Tuner, etc.	£23.90
20 + 20 W. stereo amplifier with high performance spkrs.	2 x Z.30s, Stereo 60, PZ.6	High quality ceramic or magnetic P.U., F.M. Tuner, Tape Deck, etc.	£26.90
40 + 40 W. R.M.S. de-luxe stereo amplifier	2 x Z.50s, Stereo 60 PZ.8, mains trsfrmr	As above	£34.88
Indoor P.A.	Z.50, PZ.8, mains transformer	Mic., guitar, speakers, etc., controls	£19.43


*F.M. Stereo Tuner (£25) & A.F.U. Filter Unit (£5.98) may be added as required.

Sinclair Radionics Limited, London Road,
St. Ives, Huntingdonshire PE17 4HJ.
Tel: St. Ives (048 06) 4311

sinclair

from a simple amplifier to a complete stereo tuner amplifier with Project 60 modules

Z.30 & Z.50 power amplifiers

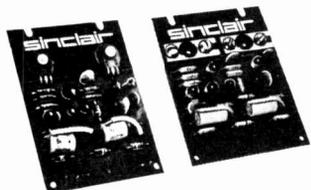

The Z.30 and Z.50 are of advanced design using silicon epitaxial planar transistors to achieve unsurpassed standards of performance. Total harmonic distortion is an incredibly low 0.02% at full output and all lower outputs. Whether you use Z.30 or Z.50 amplifiers in your Project 60 system will depend on personal preference, but they are the same size and may be used with other units in the Project 60 range equally well.

SPECIFICATIONS (Z.50 units are interchangeable with Z.30s in all applications).

Power Outputs

Z.30 15 watts R.M.S. into 8 ohms using 35 volts; 20 watts R.M.S. into 3 ohms using 30 volts.

Z.50 40 watts R.M.S. into 3 ohms using 40 volts; 30 watts R.M.S. into 8 ohms using 50 volts.

Frequency response: 30 to 300,000Hz \pm 1dB.

Distortion: 0.02% into 8 ohms.

Signal to noise ratio: better than 70dB unweighted.

Input sensitivity: 250mV into 100 Kohms.

For speakers from 3 to 15 ohms impedance.

Size: 14 x 80 x 57 mm.

Z.30

Built, tested and guaranteed with circuits and instructions manual. **£4.48**

Z.50

Built, tested and guaranteed with circuits and instructions manual. **£5.48**

Power Supply Units

Designed special for use with the Project 60 system of your choice. Use PZ.5 for normal Z.30 assemblies and PZ.6 where a stabilised supply is essential.


PZ.5 30 volts un stabilised **£4.98**

PZ.6 35 volts stabilised **£7.98**

PZ.8 45 volts stabilised

(less mains transformer) **£7.98**

PZ.8 mains transformer **£5.98**

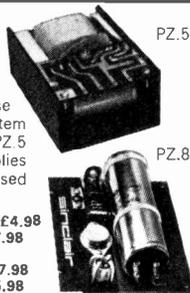

Project 60 Stereo F.M. Tuner



First in the world to use the phase lock loop principle

The phase lock loop principle was used for receiving signals from space craft because of its vastly improved signal to noise ratio. Now, Sinclair have applied the principle to an F.M. tuner with fantastically good results. Other original features include varicap diode tuning, printed circuit coils, an I.C. in the specially designed stereo decoder and squelch circuit for silent tuning between stations. Good reception is possible in difficult areas, and often a few inches of wire are enough for an aerial. In terms of a high fidelity this tuner has a lower level of distortion than any other tuner we know. Stereo broadcasts are received automatically as the tuning control is rotated, a panel indicator lighting up as the stereo signal is tuned in. This tuner can also be used to advantage with any other high fidelity system.

SPECIFICATIONS—Number of transistors: 16 plus 20 in I.C. **Tuning range:** 87.5 to 108 MHz. **Capture ratio:** 1.5dB. **Sensitivity:** 2 μ V for 30dB quieting; 7 μ V for full limiting. **Squelch level:** 20 μ V. **A.F.C. range:** \pm 200 KHz. **Signal to noise ratio:** > 65dB. **Audio frequency response:** 10 Hz—15 KHz (\pm 1dB). **Total harmonic distortion:** 0.15% for 30% modulation. **Stereo decoder operating level:** 2 μ V. **Cross talk:** 40dB. **Output voltage:** 2 x 150mV R.M.S.


Operating voltage: 25-30 VDC. **Indicators:** Mains on; Stereo on; tuning.

Size: 93 x 40 x 207 mm.

Built and tested. Post free.

£25

Stereo 60 Pre-amp/control unit

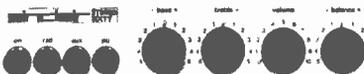

Designed for Project 60 range but suitable for use with any high quality power amplifier. Again silicon epitaxial planar transistors are used throughout, achieving a really high signal-to-noise ratio and excellent tracking between channels. Input selection is by means of push buttons and accurate equalisation is provided for all the usual inputs.


SPECIFICATIONS—Input sensitivities: Radio—up to 3mV. Mag. p.u. 3mV: correct to R.I.A.A curve \pm 1dB: 20 to 25,000 Hz. Ceramic p.u.—up to 3mV; Aux—up to 3mV. **Output:** 250mV. **Signal to noise ratio:** better than 70dB. **Channel matching:** within 1dB. **Tone controls:** TREBLE + 15 to -15dB at 10 KHz; BASS + 15 to -15dB at 100Hz.

Front panel: brushed aluminium with black knobs and controls. **Size:** 66 x 40 x 207 mm.

Built tested and guaranteed.

£9.98

A.F.U. High & Low Pass Filter Unit

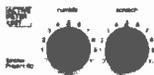

For use between Stereo 60 unit and two Z.30s or Z.50s, and is easily mounted. It is unique in that the cut-off frequencies are continuously variable, and as attenuation in the rejected band is rapid (12dB/octave), there is less

loss of the wanted signal than has previously been possible. Amplitude and phase distortion are negligible. The A.F.U. is suitable for use with any other amplifier system. Two filter stages—rumble (high pass) and scratch (low pass). Supply voltage—15 to 35V. Current—3mA. H.F. cut-off (-3dB) variable from 28KHz to 5KHz. L.F. cut-off (-3dB) variable from 25Hz to 100Hz. Distortion at 1 KHz (35V supply) 0.02% at rated output. **Size:** 66 x 40 x 90 mm.

Built tested and guaranteed.

£5.98

The Sinclair Guarantee

If within 3 months of purchasing Project 60 modules directly from us, you are dissatisfied with them, we will refund your money at once. Each module is guaranteed to work perfectly and should any defect arise in normal use we will service it at once and without any cost to you whatsoever provided that it is returned to us within 2 years of the purchase date. There will be a small charge for service thereafter. No charge for postage by surface mail. Air-mail charged at cost.

To: SINCLAIR RADIONICS LTD LONDON ROAD ST. IVES HUNTINGDONSHIRE PE17 4HJ

Please send

Name

Address

I enclose cash/cheque/money order.

PE 971

SPECIALIST ELECTRONICS COMPANY

SPECIAL OFFER:

Sinclair project 60 kit complete with power supply, two Z30's and stereo 60. **£18.95** post free

CLEARANCE ITEMS:

Garrard plinth and cover for 2025TC £6.00.
Plessey electrolytics 50 uf, 50 volt, 5p each.

BRAND NEW FULL SPEC. COMPONENTS

100 uf electrolytics 25 volt. 20p each.
500 uf @ 25 volts, 25p each.
Plessey SL403A £2.20 each. SL702C £1.10 each.

List 5p. P. & P. on all orders under £2.00, 5p.

24 KINGSWAY, WATERLOO, LIVERPOOL 22
(Mail order only)

Joan E. Allen & Company

offers a comprehensive range of

COIN & METAL DETECTORS

THE HUNTER

High sensitivity combined with marked stability to give a simple-to-use detector which is a must for the professional man such as tree surgeon, electrical contractor or serious treasure hunter **£24.00**

THE EXPLORER

Inexpensive but sensitive. Will give hours of treasure hunting fun for the whole family on the beach, whilst walking or at home in the garden. A useful robust general purpose detector. **£19.50**

THE DISCOVERER

1. The Do-It-Yourself kit entails a minimum capital outlay and can be easily assembled in a few hours. The kit is complete except for a standard portable transistor radio as most families have one of these available. As sensitive and stable as the more expensive detectors but a fraction of the cost **£5.40**

2. The "Discoverer" Metal Detector fully assembled and ready for use (transistor radio not included) **£7.50**

3. Portable transistor radio ideal for use with the "Discoverer" Metal Detector **£1.95**

TREASURE HUNTER'S HANDBOOK

"A Fortune Under Your Feet". This new publication answers all your questions on treasure hunting. Find out the How, Where, When and Why of this fascinating new hobby **45p** plus 6p post and packing

PLEASE ADD 30p TO DETECTOR ORDERS TOWARDS COST OF POST, PACKING AND INSURANCE.

ALL DETECTORS ARE GUARANTEED FOR ONE YEAR.

SHOWROOM DEMONSTRATIONS: MONDAY-FRIDAY 10-5 p.m.
SATURDAY 9-11 p.m.

FURTHER DETAILS OF ALL DETECTORS AVAILABLE ON REQUEST (A 3p stamp would be appreciated).

184 Main Road, Biggin Hill, Kent. Telephone: Biggin Hill 4234


If you have difficulty in obtaining PRACTICAL ELECTRONICS

Please place a regular order with your newsagent or send 1 year's subscription (£2.65) to Subscription Department, Practical Electronics, Fleetway House, Farringdon St., London, E.C.4.

LST FOR SIEMENS, NEWMARKET, IR, RCA MULLARD, TEXAS, FERRANTI, GE

AC107	37p	BY100	20p	NKT10339	25p	IN4005	12p
AC126	25p	BYX10	15p	NKT10419	19p	IN4006	15p
AC127	25p	BYZ10	40p	NKT10439	27p	IN4007	20p
AC128	20p	BYZ12	30p	NKT10519	22p	IN4148	7p
AC151	12p	BYZ13	20p	NKT20329		2G302	19p
AC176	25p	BZ2788/		0013	31p	2G371	15p
AC187	30p	C23	15p	NKT80111	67p	2G374	25p
AC188	30p	C3V6	15p	NKT80112	83p	2N174	80p
AC177	29p	C3V9	15p	NKT80131	£1.00	2N385A/	
AC188	30p	C3V6	15p	NKT80111	67p	2N388A	75p
AC188	30p	C3V6	15p	NKT80112	83p	2N404	23p
AC188	30p	C3V6	15p	NKT80113	83p	2N404	23p
AC188	30p	C3V6	15p	NKT80114	83p	2N404	23p
AC188	30p	C3V6	15p	NKT80241	83p	2N404	23p

4-STATION INTERCOM

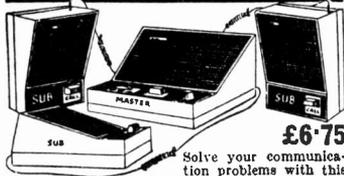

£6.75

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. and other accessories. P. & P. 40p.

MAINS INTERCOM

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On/off switch and volume control with lock system. Price £13.95. P. & P. 55p extra.

INTERCOM/BABY ALARM



£3.15

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 66ft. connecting wire. Battery 18p. P. & P. 25p.

Transistor TELEPHONE AMPLIFIER



£2.98

Why not boost business efficiency with this incredible De-Luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume control. Battery 18p extra. P. & P. 20p. Full price refunded if not satisfied in 7 days.

WEST LONDON DIRECT SUPPLIES (PE/9)
169 KENSINGTON HIGH STREET, LONDON, W.8

DABAR audio mixer modules



A range of audio Pre-amplifier Modules is now available enabling the construction of custom-built audio mixers for studio, P.A. and discotheque installations; at reasonable cost and with many facilities usually available only on expensive systems. The Modules, constructed on glass fibre printed-circuit boards, are complete with anodised aluminium black fascia plates and four control knobs identified: L.F., H.F., Echo Send and P.F.L. The modules are designed for use with external faders or volume controls and fulfil most requirements in the audio field. Up to ten input modules may be mixed into the combined Mixer/Line Amplifier Type MX/LNTA which is available on a matching fascia plate with V.U. meter. The line amp will deliver +20dBm. All mixing may be effected with 10k log faders. The modules are fixed with four screws and dimensions are 7½in × 2½in.

Input modules available:

- UM1 200-600 ohm MIC
- UM2 50k ohm MIC
- UM3 Mag P/U 1.5mV R.I.A.A.
- UM4 Mag P/U 5mV R.I.A.A.
- UM5 Crystal P/U 500mV
- UM6 High Level Tape/Tuner 500mV

Mixer/Line amp MX/LNTA: 10 inputs plus expander input; 600 ohm line out with preset for V.U. adjustment.

Power Unit for above Modules: Type PU11/30, 30V, 500mA. 100W slave amplifier—100W into 4 ohm load 13½in × 10½in 7½in.

Prices: UM1-6, £9 each. MX/LNTA, £12. PU11/30, £8. 100W Slave Amp £60.

Manual showing mixing arrangements, connection data, etc., 25p. S.A.E. all inquiries. Trade inquiries welcome.

DABAR ELECTRONIC PRODUCTS

98a LICHFIELD STREET
WALSALL, STAFFS WS1 1UZ
WALSALL 34365

NEW RANGE U.H.F. TV AERIALS

All U.H.F. aerials now fitted with tilting bracket and 4 element grid reflectors.

Loft Mounting Arrays, 7 element, 45-; 11 element, 52.6; 14 element, 60.-; 18 element, 70.-; Wall Mounting with Cranked Arm, 7 element, 65.-; 11 element, 75.-; 14 element, 82.6; 18 element, 90.-; Chimney Mounting Arrays—Complete, 7 element, 90.-; 11 element, 87.6; 14 element, 95.-; 18 element, 105.- Complete assembly instructions with every aerial. Low Loss Co-axial Cable, 18 yd. King Teleboosters—Labgear U.H.F. Boosters from 75.-; Belling Lee "Concord" all Band V.H.F. U.H.F. channels operated pre-amp £7.10.0. State clearly channel number required on all orders. P. Aerials 8.-; Accessories 3.-; C.W.O. or C.O.D.

BBC · ITV · FM AERIALS



B.B.C. (Band 1), Loft, 25.-; Wall S.D. 32.6, "H" array, 60.-; I.T.V. (Band 3), 5 element loft array, 45.-; 7 element, 55.-; Wall mounting 5 element, 65.-; Combined BBC ITV loft 1 + 5, 55.-; 1 + 7, 67.6. Wall mounting 1 + 5, 77.6. Chimney mounting 1 + 5, 90.-; Pre-amps from 75.-.

Combined BBC/ITV. BBC Aerials, 1 + 5 + 9, 80.-; 1 + 5 + 14, 90.-; 1 + 7 + 14, 100.-; Available loft only.

F.M. Radio Loft S.D. 19.6. "H", 38.6. 3 element array, 57.6. Standard co-axial cable, 1-yd. Coax plugs, 1.8. Outlet boxes, 6. Diplexer crossover boxes, 17.6. pp. Aerials, 8.-; accessories, 3.-; C.W.O. or C.O.D. (min. C.O.D. charge 3.6.) 1 - for fully illustrated Lists.

CALLERS WELCOMED

OPEN ALL DAY SATURDAY

K.V.A. ELECTRONICS (Dept. P.E.)
40-41 Monarch Parade
London Road, Mitcham, Surrey
01-648 4884

THE RADIO SHOP

16 Cherry Lane, Bristol BS1 3NG
Tel.: Bristol 421196. STD Code 0272

Your West Country shop for electronic components and solid state devices

TTL IC'S SERIES 74N

7400N 25p (12)	7473N 45p (8)
7401N 25p (12)	7474N 45p (8)
7404N 25p (12)	7475N £1 (8)
7410N 25p (12)	7476N 53p (8)
7420N 25p (12)	7483N £1.05
7430N 25p (12)	7490N £1.05 (5)
7440N 25p (12)	7492N £1.05 (5)
7441N £1.05 (5)	7493N £1.05 (5)
7442N £1.05 (5)	7494N £1.05 (5)
7450N 25p (12)	7495N £1.05 (5)
7453N 25p (12)	7496N £1.05 (5)
7460N 25p (12)	74121 £1
7470N 38p (8)	P. & P. 5p
7472N 38p (8)	

Full Outs

Quantity in Bkts. 50p Pkt. P. & P. 5p.
Series 74N, Data booklet 13p Post free
900, 914, 923, Data booklet 12p Post free
930 Series, Data booklet 14p Post free

TRANSISTOR EQUIVALENTS BOOK
Feb. 1971. 78 pages, 40p P. & P. 3p

DUAL IN LINE SKTS.

14 pin, 30p; 16 pin, 37p. R. & P. 3p

R.T.L. IC'S

µL 900 Buffer, 40p; µL 914, 40p; µL 923, 45p. P. & P. 5p

LINEAR IC'S

µA 703, 45p (TO-5); µA 709, 55p (DIL.). P. & P. 5p

Experimental I.C. with circuits for Morse code osc. variable timer wiper speed control, etc. Aircraft band converter. Circuit instructions and components. All you need is a tobacco tin 50p P. & P. 5p

Tape recorder level meters. 500 micro amp. Size 1in × 1in × ½in 50p P. & P. 5p

3-digit tape recorder counters 32p P. & P. 5p


B.F.O. for any radio. Circuit instructions and components. All you need is a tobacco tin £1.05 P. & P. 5p

NEW CATALOGUE

Includes two 5p vouchers, 10p post paid.

INTER-LOCKING PLASTIC STORAGE DRAWERS

NEAT!
HANDY!
TIDY!

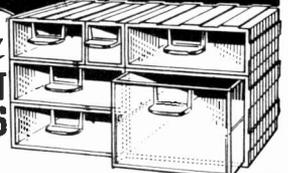

DISCOUNT PRICES

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots/removable space dividers. Build up any size cabinet for wall, bench or table top.

5 SIZES ALL INTERLOCK

BUY AT TRADE PRICES!

SINGLE UNITS (1D) (5ins × 2½ins × 2½ins) £1.35 DOZEN.

DOUBLE UNITS (2D) (5ins × 4½ins × 2½ins) £2.25 DOZEN.

TREBLE (3D) £2.35 for 8.

DOUBLE TREBLE 2, draws, in one outer case (6D2), £3.65 for 8, EXTRA LARGE SIZE (6D1) £3.30 for 8.

PLUS QUANTITY DISCOUNTS!

Orders £5 and over DEDUCT 5% in the £. Orders £10 and over DEDUCT 7½% in the £. Orders £20 and over DEDUCT 10% in the £. PACKING/POSTAGE/CARRIAGE: Add 35p to all orders under £5. Orders £5 and over, packing/postage/carriage free.

QUOTATIONS FOR LARGER QUANTITIES ALL PRICES TAX PAID


IVORYET LIMITED

(Dept. PE9) 124 Cricklewood Broadway, London, N.W.2
Tel. 01-450 4844

FIND BURIED TREASURE WITH THIS
READY BUILT & TESTED

Treasure Locator Module


Only
£4-95
(99/-)

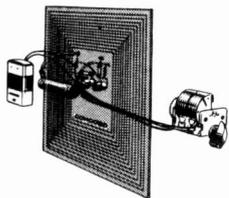

BRAND NEW FULLY TRANSISTORISED PRINTED CIRCUIT METAL DETECTOR MODULE. Ready built and tested—just plug in a PP3 battery and it's working. Put it in a case, screw a handle on and YOU HAVE A PORTABLE TREASURE LOCATOR EASILY WORTH ABOUT £80! Extremely sensitive—penetrates through earth, sand, rock, wood, dirt, water, etc.—EASILY LOCATES COINS, GOLD, SILVER, WATCHES, JEWELLERY, NUGGETS, METALLIC ORE, HISTORICAL RELICS, BURIED PIPES, KEYS, NAIL-IN-TREES, ETC., ETC. Signals exact location by "beep" pitch increasing as you near buried metallic objects. PRINTED CIRCUIT SEARCH COIL so stable and sensitive it will detect certain objects buried SEVERAL FEET BELOW GROUND! GIVES CLEAR SIGNAL ON ONE COIN! You could even pay for your holidays with two or three days electronic beachcombing—it's almost like having a licence to print money! Unclaimed treasure now exceeds the combined wealth of all nations. ORDER NOW WHILE PRESENT STOCKS LAST—TREMENDOUS DEMAND EXPECTED AT THIS REMARKABLY LOW PRICE. DEMONSTRATIONS DAILY. ORDERS DEPARTED IN STRICT ROTATION. SEND NOW £4-95 + 30p carr. (99/- + 6/-) etc. (High quality Danish Stethoscope headphones £2-75 (55/-) extra if required).

SOOTHE YOUR NERVES, RELAX WITH THIS AMAZING RELAXATRON

CUTS OUT NOISE POLLUTION—SOOTHS YOUR NERVES! Don't underestimate the uses of this fantastic new design—the RELAXATRON is basically a pink noise generator based on avalanche operated transistors. Besides being able to mask out extraneous unwanted sounds, it has other very interesting properties. For instance, many people find a rainstorm mysteriously relaxing, a large part of this feeling of well-being can be directly traced to the sound of falling raindrops!—a well known type of pink noise. A group of Dentists have experimented on patients with this pink noise—NO ANAESTHETICS WERE USED! The noise ostensibly created a most definite reaction on these patients' nervous systems with the results that their pain systems were blocked. IF YOU WORK IN NOISY OR DISTRACTING SURROUNDINGS, IF YOU HAVE TROUBLE CONCENTRATING, IF YOU FEEL TENSED, UNABLE TO RELAX—then build this fantastic Relaxatron. Once used it will be without it—use this amazing pink noise generator whenever you feel uneasy, can't relax or wish to concentrate. TAKE IT ANYWHERE, pocket sized. Uses standard PP3 batteries (current used so small that battery life is almost shelf-life) CAN BE EASILY BUILT BY ANYONE OVER 12 YEARS OF AGE using our unique, step-by-step, fully illustrated plans. No soldering necessary. All parts including case, a pair of crystal phones, Components, Nuts, Screws, Wire, etc. etc. no soldering. Send only £2-25 + 25p (45/- + 5/-) p. & p. parts available separately.)

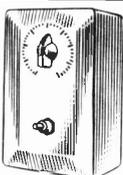


ONLY
£2-37
(47/6)

only
£2-25
(45/-)

EAVESDROP ON THE EXCITING WORLD OF AIRCRAFT COMMUNICATIONS—JUST OUT V.H.F. AIRCRAFT BAND CONVERTER

Many thousands of v.h.f. Aircraft Band Converters now selling in U.S.A. Listen in to AIRLINES, PRIVATE PLANES, JETPLANES. Eavesdrop on exciting cross-talk between pilots, ground approach control, airport tower. Hear for yourself the disciplined voices hiding tenseness on talk downs. Be with them when they have to take nerve ripping decisions in emergencies—Tune into the international distress frequency. Covers the aircraft frequency band including HEATHROW, GATWICK, LUTON, RINGWAY, PRESTWICK, ETC. CLEAR AS A BELL. This fantastic fully transistorised instrument can be built by anyone nine to ninety in under two hours. (Our design team built four—everyone worked first time). No knowledge of radio or electronics required. No soldering necessary. Fully illustrated simply worded instructions take you step-by-step. Uses standard PP3 battery. Size only 4 1/2" x 3" x 1 1/2". All you do is extend rod aerial, place close to any ordinary medium-wave radio—(even tiny portables) NO CONNECTIONS WHATSOEVER NEEDED. Use indoors or outdoors. THERE WILL BE ENORMOUS DEMAND FOR THIS NEW DESIGN. SEND NOW, ONLY £2-37 (47/6) + 23p (4/6) p. & p. for all parts, including cases, nuts, screws, wire, etc., etc. (parts available separately)

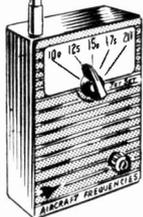

GET A GOOD NIGHT'S SLEEP—EVERY NIGHT! INGENIOUS ELECTRONIC SLEEP INDUCER

only
£2-75
(55/-)



CAN'T SLEEP AT NIGHTS? DO YOU WAKE UP IN THE NIGHT AND CAN'T GET OFF TO SLEEP AGAIN? WOULD YOU LIKE TO BE GENTLY SOOTHED OFF TO SATISFYING SLEEP EVERY NIGHT? Then build this ingenious electronic sleep inducer. It even stops by itself so you don't have to worry about it being on all night! The loudspeaker produces soothing audio-frequency sounds, continuously repeated—but as time goes on the sounds gradually become less and less—until they eventually cease altogether, the effect it has on people is amazingly very similar to hypnosis. A control is provided for adjusting the length of times etc., all transistor, can be built by anyone over 12 years of age in about two hours. No knowledge of electronics or radio needed. Extremely simple, easy-to-follow, step-by-step, fully illustrated instructions included. No soldering necessary. Works off standard batteries—extremely economical. Size only 3" x 4 1/2" x 1 1/2"—take it anywhere. All parts including case, loudspeaker, components, nuts, wire, screws, etc. etc. THERE WILL BE A GREAT DEMAND FOR THIS UNIQUE NEW DESIGN—SEND NOW £2-75 + 25p (55/- + 5/-) p. & p. (parts available separately).

REAL WORKING ELECTRONIC ORGAN



ONLY
£2-75
(65/-)

Anyone from nine years onwards can build it easily in one short evening following the fully illustrated, step-by-step, simply worded instructions. BIG DEMAND ANTICIPATED FOR THIS UNIQUE INSTRUMENT! MEET at our low, low building price. ONLY £2-75 (65/-) + 23p (4/6) p. & p. for all parts, including case, loudspeaker, transistors, condensers, resistors, knobs, transformer, volume control, wire, nuts, screws, simple (but full) instructions, etc. etc. Use standard battery (parts available separately). Have all the pleasure of making it yourself, finish with an exciting gift for someone.

Don't confuse with ordinary electric organs that simply blow air over mouth-organ type reeds etc. Eight months were spent in creating and testing this superb, revolutionary electronic organ. Fully transistorised—no valves. Proper self-contained loudspeaker. Fifteen separate keys open two full octaves—play the "Yellow Rose of Texas", play "Silent Night", play "Auld Lang Syne", play lots and lots of similar tunes on this real working electronic organ. Although it's no theatre organ it's certainly no tiny thing, it measures 13" x 10" x 2 1/2". You have the thrill and excitement of building it together with the pleasure of playing a real, live, throbbing electronic organ. Take it anywhere—play it anywhere. NO PREVIOUS KNOWLEDGE OF ELECTRONICS NEEDED—NONE WHATSOEVER. No soldering necessary. It really is as simple as a.b.c. to make, assemble and play.

SHORTWAVE TRANSISTOR RADIO Can be built in one evening



ONLY
£2-25
(45/-)

At last! After trying countless circuits searching for easy build, work first-time short wave. Giving advanced world-wide performance, we chose this "Sky Roma". Anyone from 9 years up can follow the step-by-step, easy-as-ABC, fully illustrated instructions. (We built ten prototypes and every one worked first time) no soldering necessary. 76 stations logged on rod aerial in 30 mins.—Russia, Africa, USA, Switzerland, etc. Experience thrills of world wide news, sport, music, etc. Eavesdrop on unusual broadcasts. Uses PP3 battery. Transistorised (no valves). Size only 3" x 4 1/2" x 1 1/2". As tremendous demand anticipated price held to only £2-25 (45/-) + 17p (3/6) p. & p. for all parts incl. Cabinet, screws, instructions etc. (Part available separately).

BUILD 5 RADIO AND ELECTRONIC PROJECTS

TOTAL BUILDING PRICE
£1-97
(39/6)



Amazing Radio Construction set! Become a radio expert for £1-97 (39/6). A complete Home Radio Course. No experience needed. Parts including simple instructions for each design. Illustrated Step-by-step plans, all Transistors, loudspeaker, personal phone, knobs, screws, etc., all you need. Presentation Box 27p (7/6) extra as illus. (if required) (extra parts available separately) no soldering necessary. Send only £1-97 (39/6) + 23p (4/6) p. & p.

FIND BURIED TREASURE! TREASURE LOCATOR TRANSISTORISED

NOW IT'S HERE AT LAST, after experimenting for four and a half months with a multitude of different circuits and carrying out actual field tests with prototypes, our design team have come up with this real winner. This fully portable transistorised metal locator detects and tracks down buried metal objects—it signals exact location with low audible sound (no phones used)—uses any transistor radio which fits inside—no connections needed. FINDS GOLD, SILVER, LOOT COINS, JEWELLERY, KEYS, WAR SOUVENIRS, ARCHAEOLOGICAL PIECES, METALLIC ORE, NUGGETS ETC. ETC. Outdoors or indoors. Extremely sensitive, will signal presence of certain objects buried several feet below ground! No knowledge of radio or electronics required. Can be built with ease in one short evening by anybody from nine years of age upwards, with the wonderfully clear, easy to follow, step-by-step, fully illustrated instructions—it really is as easy as A.B.C. transistorised—no valves. Uses standard PP3 battery. No soldering necessary. Size of detector head 13 1/2" x 10" x 2 1/2". Great demand expected at this remarkably low price.



ONLY
£2-37
(47/6)

ORDER WHILE PRESENT STOCKS LAST. All parts including detector head case, nuts, screws, wire, simple instructions etc., etc. ONLY £2-37 (47/6) + 27p (5/6) p. & p. (Sectional handle as illustrated 75p (15/-) extra). Parts available separately. Made up looks worth £15!

EXAMINE AT HOME FOR 7 DAYS. YOUR MONEY REFUNDED IN FULL IF NOT 100% DELIGHTED.

CONCORD ELECTRONICS LTD (Dept. PE22) 8 Westbourne Grove, London W.2.
(STAFF WANTED FOR ALL DEPARTMENTS) (Nr Bayswater & Queensway Tubes. 1 minute ABC Cinema) Callers Welcome 9 a.m.-6 p.m. inc. Saturday

The largest selection

NEW LOW PRICE TESTED S.C.R.'s

PIV	1A	3A	7A	10A	16A	30A
	TO-5	TO-66	TO-66	TO-48	TO-48	TO-48
50	0.23	0.25	0.47	0.50	0.53	1.15
100	0.25	0.33	0.53	0.58	0.63	1.40
200	0.36	0.37	0.57	0.61	0.75	1.60
400	0.43	0.47	0.67	0.75	0.93	1.75
600	0.53	0.57	0.77	0.97	1.25	
800	0.63	0.70	0.90	1.20	1.50	4.00

SIL. RECTS. TESTED

PIV	300mA	750mA	1A	1.5A	3A	10A	30A
	2A	6A	10A	TO-1	TO-66	TO-88	
50	0.04	0.05	0.05	0.07	0.14	0.21	0.47
100	0.04	0.06	0.05	0.13	0.16	0.23	0.75
200	0.05	0.09	0.06	0.14	0.20	0.24	1.00
400	0.06	0.13	0.07	0.20	0.27	0.37	1.25
600	0.07	0.18	0.10	0.23	0.34	0.45	1.85
800	0.10	0.17	0.13	0.25	0.37	0.55	2.00
1000	0.11	0.25	0.15	0.30	0.46	0.63	2.50
1200	—	0.33	—	0.33	0.57	0.75	

TRIACS

VMBM	2A	6A	10A
	TO-1	TO-66	TO-88
100	0.50	0.63	1.00
200	0.70	0.90	1.25
400	0.90	1.00	1.60

SILICON HIGH VOLT. AGE RECTIFIERS

10-Amp 3-KV. (3000 P.L.V.) Stud Type with Flying Leads, 80p each.

DIACS

FOR USE WITH TRIACS BR100 37p each

2A POTTED BRIDGE RECTIFIERS 200V 50p

UNIJUNCTION

UT46, Evt. 2N2646, Evt. T1843, 2N2600 27p each, 25-99 25p 100 UP 20p.

NPN SILICON PLANAR BC107/8/9, 10p each; 50-99, 8p; 100 up, 8p each, 1.00 off, 7p each, 1.00 tested and coded TO-18 case.

FREE

One 50p Pak of your own choice free with orders valued \$4 or over.

AF239 PNP GERM. SIEMENS VHF TRANSISTORS, RF MIXER & OSC. UP TO 900 MHZ. USE AS REPLACEMENT FOR AF139-AF186 & 100% OF OTHER USES IN VHF. OUR SPECIAL LOW PRICE—1.24 37p each, 25-99 34p each 100 + 30p each.

FET'S

2N 3819 35p
2N 3820 35p
MPF105 40p

CADMIUM CELLS

ORP12 43p
ORP60, ORP61 40p each

PHOTO TRANS.

OCF71 Type, 43p

SIL. G.P. DIODES 5p

300mW 30... 0.50
40PIV (Min.) 100... 1.50
Sub-Min. 500... 5.00
Full Tested 1,000... 9.00
Ideal for Organ Builders.

D13D1 Silicon Unilateral switch 50p each.

A Silicon Planar, monolithic integrated circuit having thyristor electrical characteristics, but with an anode gate and a built-in "Zener" diode between gate and cathode. Full data and application circuits available on request.

ADI61 NPN

ADI62 PNP

MATCHED COMPLEMENTARY PAIRS OF GERM. POWER TRANSISTORS

For mains driven output stage of Amplifiers and Radio receivers. OUR LOWEST PRICE OF 83p PER PAIR

2N3055 115 WATT SIL. POWER NPN

OUR PRICE 83p EACH

FULL RANGE OF ZENER DIODES

VOLTAGE RANGE 2-33V. 400mW (DO-7 Case) 13p ea. 11W (Top-Hat) 18p ea. 10W (80-10 Stud) 25p ea. All fully tested 5% tol. and marked. State voltage required.

BRAND NEW TEXAS GERM. TRANSISTORS

Coded and Guaranteed

Pak No.	EQVT
T1	8 2G371A OC71
T2	8 2G374 OC75
T3	8 2G374A OC81D
T4	8 2G381A OC81
T5	8 2G382T OC82
T6	8 2G344A OC44
T7	8 2G345A OC45
T8	8 2G378 OC78
T9	8 2G399A 2N1302
T10	8 2G417 AF117

All 50p each pak

2N2060 NPN SIL. DUAL TRANS.

CODE D1699 TEXAS. Our price 25p each.

120 VCB NIXIE DRIVER TRANSISTOR.

Sim. BSX21 & C407, 2N1893 FULLY TESTED AND CODED ND120. 1-24 17p each. TO-5 N.P.N. 25 up 15p each.

Sil. trans. suitable for P.E. Organ Metal TO-18

Eqvt. ZTX300 5p each. Any Qty.

EX-EQUIPMENT MULLARD

AF117 transistors. Large can 4 leads type. Leads cut short but still usable. real value at 15 for 50p.

KING OF THE PAKS Unequalled Value and Quality

SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Satisfaction GUARANTEED in Every Pak, or money back.

Pak No.	Description	Price
U1	120 Glass sub-min. general purpose germanium diodes	50p
U2	60 Mixed germanium transistors AF1RF	0.50
U3	75 Germanium gold bonded diodes sim. OA5, OA47	0.50
U4	40 Germanium transistors like OC81, AC128	0.50
U5	60 200mA sub-min. Sil. diodes	0.50
U6	30 Silicon planar transistors NPN sim. BSY95A, 2N706	0.50
U7	16 Silicon rectifiers Top-Hat 750mA up to 1,000V	0.50
U8	50 Sil. planar diodes 250mA, OA/200/202	0.50
U9	20 Mixed volts 1 watt Zener diodes	0.50
U11	30 PNP silicon planar transistors TO-5 sim. 2N1132	0.50
U13	30 PNP-NPN sil. transistors OC200 & 2B104	0.50
U14	150 Mixed silicon and germanium diodes	0.50
U15	25 NPN Silicon planar transistors TO-5 sim. 2N697	0.50
U16	10 3-Amp silicon rectifiers stud type up to 1000 PIV	0.50
U17	30 Germanium PNP AF transistors TO-5 like ACY 17-22	0.50
U18	8 6-Amp silicon rectifiers BYZ13 type up to 600 PIV	0.50
U19	25 Silicon NPN transistors like BC108	0.50
U20	12 1.5-Amp silicon rectifiers Top-Hat up to 1,000 PIV	0.50
U21	30 A.F. germanium alloy transistors 2G300 series & OC71	0.50
U22	30 Mat's like MAT series PNP transistors	0.50
U24	20 Germanium 1-Amp rectifiers GJM up to 300 PIV	0.50
U25	25 300Mc/s NPN silicon transistors 2N708, BSY27	0.50
U26	30 Fast switching silicon diodes like 1N914 micro-min	0.50
U28	Experimenters' assortment of integrated circuits, untested. Gates, flip-flops, registers, etc. 8 assorted pieces	1.00
U29	10 1-Amp SCR's TO-5 can up to 600 PIV CR81/25-600	1.00
U31	20 Sil. Planar NPN trans. low noise amp 2N3707	0.50
U32	25 Zener diodes 400mW D07 case mixed volts, 3-18	0.50
U33	15 Plastic case 1 amp silicon rectifiers 1N4000 series	0.50
U34	30 Sil. PNP alloy trans. TO-5 BCY26, 2B302/4	0.50
U35	25 Sil. planar trans. PNP TO-18 2N3906	0.50
U36	25 Sil. planar NPN trans. TO-5 BFY50/51/52	0.50
U37	30 Sil. alloy trans. SO-2 PNP, OC200 2B322	0.50
U38	20 Fast switching sil. trans. NPN, 400Mc/s 2N3011	0.50
U39	30 RF germ. PNP trans. 2N1303/5 TO-5	0.50
U40	10 Dual trans. 6 lead TO-5 2N2060	0.50
U41	25 RF germ. trans. TO-1 OC45 NKT72	0.50
U42	10 VHF germ. PNP trans. TO-1 NKT687 AF117	0.50

Code Nos. mentioned above are given as a guide to the type of device in the Pak. The devices themselves are normally unmarked.

GENERAL PURPOSE GERM. PNP POWER TRANSISTORS

Coded GP100. BRAND NEW TO-3 CASE. POSS. REPLACEMENTS FOR—OC25-28-29-30-35-36, NKT401-403-404-405-406-451-452-453, T13027-3028, 2N250A, 2N456A-457A-458A, 2N511 A & B, 2G220-222, ETC.

SPECIFICATION VCB0 80V VCE0 50V IC 10A PT. 30 WATTS HFE 30-170. PRICE 1-24 25-99 100 up 43p each 40p each 30p each

GENERAL PURPOSE SILICON NPN POWER TRANSISTORS

Coded GP300. BRAND NEW TO-3 CASE. POSSIBLE REPLACEMENT FOR—2N3055, BDY20, BDY11.

SPECIFICATION VCB0 100V, VCE0 60V, IC 15AMPS, PT. 115 WATTS. Hfe 20-100. FTI MHZ. PRICE 1-24 25-99 100 up 55p each 50p each 47p each

GENERAL PURPOSE NPN SILICON SWITCHING TRANS. TO-18 SIM. TO 2N706/8. BSY27/28/95A. All usable devices no open or short circuits. ALSO AVAILABLE IN PNP Sim. to 2N2906, BCY70. When ordering please state preference NPN or PNP.

	5p	100	For	7-50
20	For	0.50	For	1.00
50	For	1.00	For	13.00

HIGH POWER SILICON PLANAR TRANSISTORS TO-3.

FERRANTI ZT1487 NPN VCB60 1c 6A 1T, 1M/es VCE40 Pct. 75W VEB8 HFE15-45 PRICE 30p EACH

RTL MICROLOGIC CIRCUITS

Eopxy TO-5 case 1-24 25-99 100 up
uL900 Buffer 35p 33p 27p
uL914 Dual 2/p 100 For 1.75
uL923 3-K flip-flop 50p 47p 45p
Data and Circuits Booklet for 1.50 Price 7p.

NEW QUALITY TESTED PAKS

Pak	Description	Price
Q1	20 Red spot trans. PNP AF	0.50
Q2	16 White spot R.F. trans. PNP	0.50
Q3	4 OC77 type trans.	0.50
Q4	6 Matched trans. OC44/45/81/81D	0.50
Q5	4 OC75 transistors	0.50
Q6	4 OC72 transistors A.P.	0.50
Q7	4 AC126 trans. PNP high gain	0.50
Q8	7 OC81 type trans.	0.50
Q9	7 OC71 type trans.	0.50
Q10	2 AC127/128 comp. pairs PNP/NPN	0.50
Q12	3 AF116 type trans.	0.50
Q13	3 AF117 type trans.	0.50
Q14	3 OC111 H.F. type trans.	0.50
Q15	5 2N2926 sil. epoxy trans.	0.50
Q16	2 GCT860 low noise germ. trans.	0.50
Q17	3 PNP 1 8T141 & 2 8T140	0.50
Q18	4 Mat's 2 MAT 100 & 2 MAT 120	0.50
Q19	3 Mat's 2 MAT 101 & 1 MAT 121	0.50
Q20	4 OC137 NPN germ. trans.	0.50
Q22	20 NKT trans. A.F. R.F. coded	0.50
Q23	10 OA202 sil. diodes sub-min.	0.50
Q24	8 OA81 diodes	0.50
Q25	6 1N914 sil. diodes 75PIV 75mA	0.50
Q26	8 OA80 germ. diodes sub-min. 1N697	0.50
Q27	2 10A 600PIV sil. rect. 1S45B	0.50
Q28	2 Sil. power rect. BYZ13	0.50
Q29	4 Sil. trans. 2 x 2N896, 1 x 2N897, 1 x 2N698	0.50
Q30	7 Sil. switch trans. 2N706 NPN	0.50
Q31	6 Sil. switch trans. 2N708 NPN	0.50
Q32	3 PNP sil. trans. 2 x 2N1131, 1 x 2N1132	0.50
Q33	3 Sil. NPN trans. 2N1711	0.50
Q34	7 Sil. NPN trans. 2N2369, 500MHZ.	0.50
Q35	3 Sil. PNP TO-5 2 x 2N2904 & 1 x 2905	0.50
Q36	7 2N3646 TO-18 plastic 300MHZ NPN	0.50
Q37	3 2N3905 NPN sil. trans.	0.50
Q38	7 PNP trans. 4 x 2N3703, 3 x 2N3702	0.50
Q39	7 NPN trans. 4 x 2N3704, 3 x 2N3705	0.50
Q40	7 PNP amp. 4 x 2N3707, 3 x 2N3708	0.50
Q41	3 NPN trans. TO-18 2N3904	0.50
Q42	6 NPN trans. 2N5172	0.50
Q43	7 BC107 NPN trans.	0.50
Q44	4 NPN trans. 4 x BC108, 3 x BC109	0.50
Q45	3 BC113 NPN TO-18 trans.	0.50
Q46	3 BC115 NPN TO-5 trans.	0.50
Q47	4 NPN high gain 3 x BC167, 3 x BC168	0.50
Q48	4 BCY70 NPN trans. TO-18	0.50
Q49	4 NPN trans. 2 x BFY51, 2 x BFY52	0.50
Q50	7 BSY28 NPN switch TO-18	0.50
Q51	7 BSY85A NPN trans. 300MHZ.	0.50
Q52	8 BY100 type sil. rect.	1.00
Q53	25 Sil. & germ. trans. mixed all marked new	1.50

PRINTED CIRCUITS—EX-COMPUTER

Packed with semiconductors and components, 10 boards give a guaranteed 30 trans and 30 diodes. Our price 10 boards, 50p. Plus 10p P. & P. 100 Boards £3, P. & P. 30p.

TRANSISTOR EQUIVALENTS BOOK.

A complete cross reference and equivalents book for European, American and Japanese Transistors. Exclusive to BI-PAK 75p each.

GERM. POWER TRANS.

Type	Price each	Type	Price each
OC20	50p	OC29	40p
OC22	30p	OC35	33p
OC23	33p	OC36	40p
OC25	25p	AD140	40p
OC26	25p	AD142	40p
OC28	40p	AD149	43p

OUR STOCKS of individual devices

are now too numerous to mention in this Advertisement. Send S.A.E. for our listing of over 1,000 Semiconductors. All available Ex-Stock at very competitive prices.

Dual-in-Line Low Profile Sockets

14 and 16 Lead Sockets for use with Dual-in-Line Integrated Circuits

Order No.	1-24	25-99	100 up
TSR 14 pin type	30p	27p	25p
TSR 16 pin type	35p	32p	30p

-the lowest prices!

74 series T.T.L. I.C's

**NOW LOWER THAN EVER PRICES
—GREATER RANGE**

BI-PAK Semiconductors offer you the largest and most popular range of I.C.'s available at these **EXCLUSIVE LOW PRICES**. TTL Digital 74N Series fully coded, brand new. Dual in-line plastic 14 and 16 pin packages.



BI-PAK Order No.	Similar Types to: Description	Price and qty. prices		
		1-24 \$p	25-99 \$p	100 up \$p
BF00 = 7400	Quadruple 2-input NAND gate	0-23	0-20	0-15
BF01 = 7401	Quadruple 2-input positive NAND gate (with open collector output)	0-23	0-20	0-15
BF02 = 7402	Quadruple 2-input positive NOR gates	0-23	0-20	0-15
BF03 = 7403	Quadruple 2-input positive NAND gates (with open-collector output)	0-23	0-20	0-15
BF04 = 7404	Hex Inverters	0-23	0-20	0-15
BF10 = 7410	Triple 3-input positive NAND gates	0-23	0-20	0-15
BF13 = 7413	Dual 4-input Schmitt trigger	0-35	0-32	0-29
BF20 = 7420	Dual 4-input positive NAND gates	0-23	0-20	0-15
BF30 = 7430	8-input positive NAND gates	0-23	0-20	0-15
BF40 = 7440	Dual 4-input positive NAND buffers	0-23	0-20	0-15
BF41 = 7441	BCD to decimal hex driver	0-87	0-77	0-67
BF42 = 7442	BCD to decimal decoder (4-10 lines, 1 of 10)	0-87	0-77	0-67
BF47 = 7447	BCD seven-segment decoder/drivers (15V outputs)	1-40	1-30	1-20
BF50 = 7450	Expandable dual 2-input and/or invert	0-23	0-20	0-15
BF51 = 7451	Dual 2-wide 2-input and/or invert gates	0-23	0-20	0-15
BF53 = 7453	Quad 2-input expandable and/or invert	0-23	0-20	0-15
BF54 = 7454	4-wide 2-input and/or invert gates	0-23	0-20	0-15
BF60 = 7460	Dual 4-input expander	0-23	0-20	0-15
BF70 = 7470	Single-phase J-K flip-flop	0-35	0-32	0-29
BF72 = 7472	Master-slave J-K flip-flop	0-35	0-32	0-29
BF73 = 7473	Dual master-slave J-K flip-flop	0-43	0-40	0-37
BF74 = 7474	Dual D type flip-flop	0-43	0-40	0-37
BF75 = 7475	Quad latch	0-47	0-45	0-43
BF76 = 7476	Dual J-K with pre-set and clear	0-47	0-45	0-43
BF80 = 7480	Gated full adders	0-87	0-77	0-67
BF81 = 7481	16-bit read/write memory	1-35	1-25	1-15
BF82 = 7482	2-bit binary full adders	1-30	1-20	1-00
BF83 = 7483	Quad full adder	0-87	0-77	0-67
BF86 = 7486	Quad 2-input exclusive or gates	0-80	0-70	0-60
BP90 = 7490	BCD decade counter	0-87	0-77	0-67
BP91 = 7491	8-bit shift registers	1-21	1-00	0-87
BP92 = 7492	Divide-by-twelve counters	0-87	0-77	0-67
BP93 = 7493	4-bit binary counters	0-87	0-77	0-67
BP94 = 7494	Dual entry 4-bit shift register	0-87	0-77	0-67
BP95 = 7495	4-bit up-down shift register	0-87	0-77	0-67
BP96 = 7496	3-bit parallel in parallel out shift register	1-10	1-00	0-90
BF100 = 74100	8-bit bistable latches	1-75	1-65	1-55
BF118 = 74118	Hex set-reset latches	1-30	1-20	1-00
BF121 = 74121	Monostable multivibrators	0-87	0-77	0-67
BF141 = 74141	BCD-to-decimal decoder/driver	0-87	0-77	0-67
BF145 = 74145	BCD-to-decimal decoder/drivers	1-80	1-70	1-60
BF151 = 74151	8-bit data selectors (with strobe)	1-40	1-30	1-20
BF153 = 74153	Dual 4-line-to-1-line data selector/multiplexers	1-40	1-30	1-20
BP191 = 74191	Binary counter reversible	3-50	3-25	3-00

PRICE-MIX. Devices may be mixed to qualify for quantity prices.
PRICES for quantities in excess of 500 pieces mixed, on application.
Data is available for the above Series of Integrated Circuits in booklet form, price 13p.

TTL INTEGRATED CIRCUITS

Manufacturers' "Fall outs" - out of spec. devices including functional units and part function but classed as out of spec. from the manufacturers' very rigid specifications. Ideal for learning about I.C.'s and experimental work.


PAK No.	PAK No.	PAK No.
UIC00 = 12 x 7400N 50p	UIC42 = 5 x 7450N 50p	UIC80 = 5 x 7480N 50p
UIC01 = 12 x 7401N 50p	UIC50 = 12 x 7450N 50p	UIC82 = 5 x 7482N 50p
UIC02 = 12 x 7402N 50p	UIC51 = 12 x 7451N 50p	UIC83 = 5 x 7483N 50p
UIC03 = 12 x 7403N 50p	UIC60 = 12 x 7460N 50p	UIC86 = 5 x 7486N 50p
UIC04 = 12 x 7404N 50p	UIC70 = 8 x 7470N 50p	UIC90 = 5 x 7490N 50p
UIC05 = 12 x 7405N 50p	UIC72 = 8 x 7472N 50p	UIC92 = 5 x 7492N 50p
UIC10 = 12 x 7410N 50p	UIC73 = 8 x 7473N 50p	UIC93 = 5 x 7493N 50p
UIC20 = 12 x 7420N 50p	UIC74 = 8 x 7474N 50p	UIC94 = 5 x 7494N 50p
UIC40 = 12 x 7440N 50p	UIC75 = 8 x 7475N 50p	UIC95 = 5 x 7495N 50p
UIC41 = 5 x 7441AN 50p	UIC76 = 8 x 7476N 50p	UIC96 = 5 x 7496N 50p
	UICX1 = 25 x Ass'd 74's £1.50	

Paks cannot be split but 20 assorted pieces (our mix) is available as PAK UICX1. Every PAK carries our BI-PAK Satisfaction or money back GUARANTEE.

BRAND NEW LINEAR I.C.'s—FULL SPEC.

Type No.	Case	Leads	Description	Price
BP 201C—SL201C	TO-5	8	G.P. Amp	63p 50p 45p
BP 701C—SL701C	TO-5	8	OP Amp	63p 50p 45p
BP 702C—SL702C	TO-5	8	OP Amp Direct OP	63p 50p 45p
BP 702—72702	D.I.L.	14	G.P. OP Amp (Wide Band)	53p 45p 40p
BP 709—72709	D.I.L.	14	High OP Amp	53p 45p 40p
BP 709P— μ A709C	TO-3	8	High Gain OP Amp	53p 45p 40p
BP 711— μ A711	TO-5	10	Dual comparator	58p 50p 45p
BP 741—72741	D.I.L.	14	High Gain OP Amp (Protected)	75p 60p 50p
μ A 703C— μ A703C	TO-5	6	R.F.—I.F. Amp	43p 35p 27p
TAA 263—	TO-72	4	A.F. Amp	70p 60p 55p
TAA 293—	TO-74	10	G.P. Amp	80p 75p 70p

ANOTHER BI-PAK FIRST!

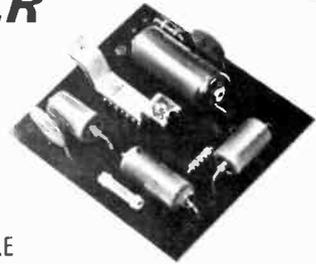

THE NEW S.G.S.
EA 1000 AUDIO
AMPLIFIER MODULE

***GUARANTEED NOT LESS THAN 3 WATTS RMS**

Especially designed by S.G.S. incorporating their proven Linear I.C. Audio Amp. TA/621 providing unlimited applications for the enthusiast in the construction of radios, record players, Audio and Stereo units. Also ideal for intercom systems, monitoring applications and phone answering machines. **OTHER USES:** portable applications where supply rails as low as 9V are of prime importance.

- Sensitivity 40 mV for 1 watt
- Overall Size 2" 3" 1/2"
- Voltage GAIN 40dB but can be varied up to 73dB for some applications.
- Typical Total Harmonic Distortion at 1 watt less than 1%.
- Signal to Noise Ratio 86dB.
- *Supply voltage (Vs) = 24V 15ohm load.
- Frequency response better than 50 Hz to 25 KHz for -3dB.
- Module Tested and Guaranteed
- Normal supply Voltage 9-24V.
- Quantity 1-9 10-25
- Suitable for 8-16 OHM Loads.
- Price each £2.63 £2.28
- Larger quantities quoted on request

Full hook-up diagrams and complete technical data supplied free with each module or available separately at 10p each.

NOTE THESE PRICES!

IC's	DTL 930 SERIES	LOGIC
Type No.	Function	Price
BP930	Expandable dual 4-input NAND	1-24 23p 20p 15p
BP932	Expandable dual 4-input NAND buffer	25p 23p 20p
BP933	Dual 4-input expander	25p 23p 20p
BP935	Expandable Hex Inverter	25p 23p 20p
BP936	Hex Inverter	25p 23p 20p
BP944	Dual 4-input NAND expandable buffer without pull-up	25p 23p 20p
BP945	Master-slave JK or RS	35p 32p 29p
BP946	Quad, 2-input NAND	23p 20p 15p
BP948	Master-slave JK or RS	35p 32p 29p
BP954	Monostable	80p 85p 80p
BP955	Triple 3-input NAND	23p 20p 15p
BP9093	Dual Master-slave JK with separate clock	80p 75p 70p
BP9094	Dual Master-slave JK with separate clock	80p 75p 70p
BP9097	Dual Master-slave JK with Common Clock	80p 75p 70p
BP9099	Dual Master-slave JK Common Clock	80p 75p 70p

Devices may be mixed to qualify for quantity price. Larger quantity prices on application. (DTL 930 Series only).

DTL (Diode Transistor Logic) INTEGRATED CIRCUITS manufacturers' "Fall outs" - out of spec. devices including functional units and part functional but classed as out of spec. from the manufacturers' very rigid specifications. Ideal for learning about I.C.'s and experimental work.

Pak No.	Pak No.	Pak No.
UIC930 = 12 x μ A 930 50p	UIC948 = 8 x μ A 948 50p	
UIC932 = 12 x μ A 932 50p	UIC951 = 5 x μ A 951 50p	
UIC933 = 12 x μ A 933 50p	UIC961 = 12 x μ A 961 50p	
UIC935 = 12 x μ A 935 50p	UIC963 = 5 x μ A 963 50p	
UIC936 = 12 x μ A 936 50p	UIC964 = 5 x μ A 964 50p	
UIC944 = 12 x μ A 944 50p	UIC967 = 5 x μ A 967 50p	
UIC945 = 8 x μ A 945 50p	UIC969 = 5 x μ A 969 50p	
UIC946 = 12 x μ A 946 50p	UIC X 925 Assorted 930 Series £1.50	

Paks cannot be split but 20 Assorted Pieces (our mix) is available as Pak UICX9. Every Pak carries our BI-PAK Satisfaction or money back guarantee. Data Booklet available for the BP930 Series. PRICE 13p.

All prices quoted in new pence Giro No. 388-7006
Please send all orders direct to warehouse and despatch department

BI-PAK

P.O. BOX 6, WARE, HERTS

Postage and packing add 7p. Overseas add extra for airmail.
Minimum order 50p. Cash with order please.

Guaranteed Satisfaction or Money Back

Practical Electronics Classified Advertisements

RATES: 7p per word (minimum 12 words). Box No. 7p extra. Advertisements must be prepaid and addressed to Classified Advertisement Manager, "Practical Electronics" IPC MAGAZINES LTD., Fleetway House, Farringdon Street, London EC4A 4AD

MISCELLANEOUS

NO NEED TO WORRY ABOUT A TRANSMITTING LICENCE

because this GPO approved transmitter/receiver kit does not use R.F. and you can get one easily. Your transmissions will be virtually SECRET since they won't be heard by conventional means. Actually it's TWO KITS IN ONE because you get all the printed-circuit boards and components for both the transmitter AND receiver. You're going to find this project REALLY FUN-TO-BUILD with the EASY-TO-FOLLOW instructions. An extremely flexible design with quite an AMAZING RANGE—has obvious applications for HOUSE-TO-HOUSE USE, SCHOOL PROJECTS, LANGUAGE LABORATORIES, SCOUT CAMPS, etc.

GET YOURS! SEND £5.20 NOW

TO: 'BOFFIN PROJECTS'
DEPT. KE2010
4 CUNLIFFE ROAD
STONELEIGH, EWELL, SURREY

TOP MANUFACTURERS' PRODUCTS AT TRADE PRICES!!!

ADCOLA SOLDERING IRONS AND ACCESSORIES: 60/40 SOLDER

ELECTROBIL RESISTORS: TR4, TR5, TR6, TR8, CS

T.M.C. RELAYS, PUSH BUTTON KEYS AND LEVER KEYS

B.I.C.C. P.V.C. EQUIPMENT WIRE—ALL COLOURS

Send large s.a.e. for price lists

SPEEDY COMPONENTS SUPPLY LTD.

High Street · Handcross
Haywards Heath · Sussex RH17 6BW

Handcross 671/2
CALLERS WELCOME

CLEARING LABORATORY, scopes, V.T.V.M.'s, V.O.M.'s, H.S. recorders, transcription turntables, electronic testmeters, calibration units, P.S.U.'s, pulse generators, D.C. null-potentiometers, bridges, spectrum analysers, voltage regulators, sig-gens, M/C relays, components, etc. Lower Beeding 236.

JOHN SAYS ...

RING MODULATOR by Dewtron is professional, transformerless, 5-transistor, has adjustable F1/F2 rejection. Module £7. Unit £8.90. WAA-WAA Pedal kit of all parts, including all mechanics and instructions ONLY £2.45. **AUTO RHYTHM** from Dewtron modules. Simple unit for waltz, fox-trot, etc. Costs £16.35 in modules. **ORGAN PERCUSSION** and other fascinating effects. Send 15p for illustrated list. D.E.W. LTD., 254 Ringwood Road, Ferndown, Dorset

PRINTED CIRCUITS. Capacity now available for prototype or production runs, Artworks. Photographs, Etched Boards, and Assembly. Fast turn round. Send S.A.E. for quotations. Also copper laminated fibreglass board. Single sided 1p per sq. inch. Double sided 2p per sq. inch. Any size out. Minimum order 50p. P.P. plus 10%. **SYSTEMATICS**, 18 Pennine Road, Millbrook, Southampton, Hants.

PROFESSIONAL CONTROL PANELS

with **FASCIA KIT**

MAKE YOUR OWN PANELS IN PERMANENT, ANODISED, SELF-ADHESIVE ALUMINIUM. NO SPECIAL EQUIPMENT NEEDED. EASY TO FOLLOW INSTRUCTIONS. CHOICE OF SILVER ON BLACK, GOLD, RED, BLUE, GREEN.

TRIAL KIT (Approx. 50 sq. in.) 98p + p.p. 30p
No. 2 KIT (Approx. 100 sq. in.) £1.58 + p.p. 30p
M.P.E. Ltd., BRIDGE ST., CLAY CROSS, DERBYS.

MISCELLANEOUS (continued)

TOP TRANSISTORS

Brand New and Individually Tested Transistors supplied unmarked, but packed separately for identification and guaranteed to be within their correct specification or money refunded. All at 9p. each or Any 12 transistors for only £1

ACY22	BFY51	OC72	2N3702
BC108	BFY52	OC202	2N3703
BC109	BSY27	ZTX300	2N3705
BC168	OC45	2N706	2N3706
BC169	OC71	2N2926	2N3708

Money back guarantee. P & P. 10p.

J. M. KING (L)

17 Buckridge, Portpool Lane, London, E.C.1

12 VOLT FLUORESCENT LIGHTS



Beat Power Cuts, 12 ins 8 watt Tube, ideal for Caravan, Tent, Emergency Lighting, etc. Fully Transistorised, Low Battery Drain. With ON/OFF Switch and 12V Socket to run other Lights or 12V Equipment.

Unbeatable at **£3.30**

or in kit form **£2.90** post paid

SALOP ELECTRONICS
23 Wyle Cop
Shrewsbury, Shropshire

Callers welcome
S.A.E. for lists

We stock all those components and materials required by the home Hi-Fi constructor, including speaker grille fabrics, BAF wadding, speaker kits, cabinets, crossover networks, inductors, etc. AT TOP DISCOUNTS. Price list free of charge. Send 2 x 3p stamps for pattern card of speaker grille fabrics. Mail order ONLY. No callers please.

Dept. P.E.9

AUDIOSCAN
4, PRINCES SQUARE
HARROGATE, YORKS.

LOUDSPEAKERS for P.E. intercom. 15Ω, 3in. Two for £1, post free. CROWBOROUGH ELECTRONICS, Eridge Road, Crowborough, Sussex.

COMPLETE SYSTEM of 8 telephones, automatic dialling distribution board and 200yd connecting cable. All working, £25 o.n.o. Buyer collects. Also Radionic Set No. 4 plus Pre-amp Kit and Educational E parts, £15 o.n.o. Telephone (Manchester) 061-973 4646.

VERITONE POLYESTER recording tape, 5½in 1200 £1, 1800 £1; 7in 2400 £1.70. Cassettes: C80 60p, C90 80p, C120 £1. All post free. C.W.O. SBC TAPES, 16 Bishops Road, Sutton Coldfield, Warwickshire.


CHEMICALS. Wide range. Send S.A.E. for list. KEMCO, 22 Kemerton Road, London, S.E.5. Mail Order only.

WRITING a constructional article for P.E.? Drop us a line, and we will tell you how we may be able to help. Nestra Electronics Ltd., 97 Felpham Way, Bognor Regis, Sussex, atten. Mr. N. Strange.

MISCELLANEOUS (continued)

MAINS KEYNECTOR

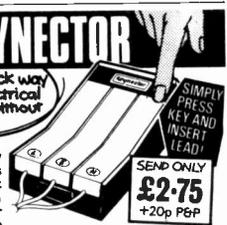The safe quick way to connect electrical equipment without a plug!



SEND ONLY **£2.75** +20p P&P

Revolutionary new Keynector connects electrical equipment to mains supply in seconds. Ideal for high-speed bench testing, shop demonstrations or do-it-yourself experts. Keynector can take multi-parallel connections up to 13 amp. maximum loading off one mains point, is easy to operate, and pays for itself by saving time. Safety features include wall or bench fixing, built-in safety switch with 13 amp. fuse, no protruding parts eliminates accidental shocks, special neon safety light shows Keynector is working. As selected for the Design Centre.

MARKTYME (MAIL ORDER) LTD Dept. PE2
72 Willaeden Lane
London, N.W.6
01-624 4633

BUILD IT in a DEWBOX quality cabinet 2in x 2½in x any length. DEW LTD., Ringwood Road, Ferndown, Dorset. S.A.E. for leaflet. Write now—right now.

FASCIA PANELS, hi-fi equipment, etc., etched aluminium to individual specifications, S.A.E. details. R. MARSH, 29 Shelbourne Road, Stratford on Avon, Warwick.

RECORD T.V. SOUND using our loudspeaker isolating transformer. Provides safe connection to recorder. Instructions included, 70p + 10p P. & P. CROWBOROUGH ELECTRONICS (P.E.), Eridge Road, Crowborough, Sussex.

PSYCHEDELIC LUMINOPHONICS

Or is this just another way of referring to FANTASY? Either way, our Projects 24 and 1014 probably come within this category—THINK OF THE FUN YOU WOULD HAVE WITH SOMETHING LIKE THIS AT A PARTY! There are MANY OTHER UNUSUAL PROJECTS TOO—how about an ELECTRONIC STETHOSCOPE for LISTENING THROUGH WALLS, etc., or a TRANSMITTER/RECEIVER that doesn't use RF, SO LICENCE WORRIES ARE OVER! Then there's another project for a "LEARNING" MACHINE—imagine one of these in YOUR BACKROOM; YOUR FRIENDS WOULD BE AMAZED! IF REALLY UNUSUAL projects interest you, then WE'VE GOT WHAT YOU WANT. In a few days from now YOU COULD BE IN THE "SCIENCE-FICTION" WORLD OF "BOFFIN"!

DON'T PUT IT OFF! SEND 15p for your list—NOW

BOFFIN PROJECTS

4 CUNLIFFE RD., STONELEIGH, EWELL, SURREY
Designs by GERRY BROWN and JOHN SALMON
and presented on TV

LADDERS

VARNISHED TIMBER LADDERS from manufacturer, LOWEST PRICES anywhere: 15ft ext., £6.20; 17ft ext., £6.50; 20ft ext., £7; 21ft ext., £7.75; 24ft ext., £8.90; 29ft ext., £10.25; 31ft triple ext., £12.25; 36ft triple ext., £16. Carr. 80p. Free Lists. Also Aluminium Ext. and Loft Ladders. Callers welcome. Dept. PEE, HOME SALES, Baldwin Road, Stourport, Worcs. Phone: 02-993 2574. Placing order on C.O.D.

TEST EQUIPMENT

SIGNAL GENERATOR 9 to 300MHz output 1 Microvolt to 100 Millivolts. 1,000Hz internal sinewave and squarewave modulation £15. SECO, 61 Arragon Road, Twickenham, Middlesex. 01-892 1217.



TELEVISION TRAINING (MONOCHROME AND COLOUR)

This private College provides theoretical and practical training in Radio and TV Servicing. Courses of 16 months' duration, with daily attendance, are available for beginners and shorter courses for men with previous training in Electronics and Radio. Training courses in Marine Radiocommunication and Radar are also available. Write for prospectus to: London Electronics College, Dept. B/3, 20 Penywern Road, Earls Court, London SW5 9SU. Tel. 01-373 8721.

EDUCATIONAL

EDUCATIONAL

Young men (and women) trained as Radio Officers on liners and other ships. Salaries rising to £2,500 per year (all found). Immediate vacancies. Grants available for Day full time course. For details of training write to: The Radio College, 91 Lancaster Road, Preston, Lancs., stating if interested in Day or Postal course.

GET INTO ELECTRONICS—big opportunities for trained men. Learn the practical way with low-cost Postal Training, complete with equipment. R.T.E.B., City & Guilds, Radio, TV, Telecoms, etc. For free informative Guide, write CHAMBERS COLLEGE (Dept. 856K), Aldermaston Court, Reading, RG7 4PF.

MEN! You can earn £50 p.w. Learn Computer Operating. Send for FREE brochure—LONDON COMPUTER OPERATORS TRAINING CENTRE, C95 Oxford House, 9-15 Oxford Street, London, W.1.

Courses for ELECTRONICS COMMUNICATIONS AND ELECTRICAL TECHNICIANS

at

SOUTH-EAST LONDON TECHNICAL COLLEGE

Day, evening, day and evening courses
Also full-time, sandwich and block courses

CITY AND GUILDS OF LONDON INSTITUTE COURSES

ORDINARY AND HIGHER NATIONAL CERTIFICATE COURSES

ORDINARY AND HIGHER NATIONAL DIPLOMA COURSES

Enrolment 13th to 16th September, 1971
Earlier application is desirable for Diploma courses

Particulars from Department
of Electrical Engineering and
Applied Physics, South-East
London Technical College,
Lewisham Way, SE4 1UT
Tel. 01-692 7296 Ex. 27

ENGINEERS—get a technical certificate. Exam and Certificate Postal Courses in all branches of Engineering, Electronics, Radio and TV, Computers, Draftings, Building, etc. Write for helpful Free Book—BIET (Dept. H.4), Aldermaston Court, Reading, RG7 4PF.

SERVICE SHEETS

RADIO TELEVISION, over 8,000 Models. JOHN GILBERT TELEVISION, 1b Shepherds Bush Rd., London, W.6 (01-743 8441).

SERVICE SHEETS. Radio, TV, etc., 8,000 models. List 10p. S.A.E. enquiries. TELRAY, 11 Maudland Bank, Preston.

SERVICE SHEETS (1925-1971) for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., by return post, with free Fault-Finding Guide. Prices from 5p. Over 8,000 models available. Catalogue 13p. Please send S.A.E. with all orders/enquiries. HAMILTON RADIO, 54 London Road, Bexhill, Sussex. Telephone, Bexhill 7097.

SITUATIONS VACANT

EAGLE INTERNATIONAL require Audio Engineers. Excellent prospects. Must be fully conversant with Stereo Amplifiers, Tuners, Multiplex, etc. Contact MR. MORROW 01-903 0144.

ELECTRONIC/ELECTRICAL TECHNICIAN required for duties in Teaching Laboratories. Interest in servicing electronic equipment an advantage. Excellent prospects. Salary range £1,041 to £1,410 plus £125 London Weighting. Application forms from Personnel Officer (Technical Staff EE1), UNIVERSITY COLLEGE LONDON, Gower Street, London, WC1E 6BT.

FOR SALE

SEEN MY CAT? 5,000 items. Mechanical and Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PE, New Mills, Stockport.

CATALOGUE NO. 18, Electronic and Mechanical Components, new and manufacturers' surplus. Credit vouchers value 50p. Price 23p, including post. ARTHUR SALLIS RADIO CONTROL LTD., 28 Gardner Street, Brighton, Sussex.

MORSE MADE !! EASY

FACT NOT FICTION. If you start RIGHT you will be reading amateur and commercial Morse within a month (normal progress to be expected).

Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it, it's as easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed.

For details and course C.O.D. ring S.T.D. 01-660 2896 or send 4p stamp for explanatory booklet to:

GSHC (Box 19), 45 GREEN LANE, PURLEY, SURREY

P.E. Nov. '64 (No. 1) to Dec. '69 except Jan. '65, Aug. '67. Any offers for these 59 copies? GORRETT, "Anton", West Beeches Road, Crowborough, Sussex.

DELCO ROTARY TRANSFORMERS, 12/24 volt input, 265/540 volts output at 0-12 amps. (new) £2-25 each, carriage paid. A. C. SUMMERS, Dallas Works, New Milton, Hampshire.



TECHNICAL TRAINING IN RADIO, TELEVISION AND ELECTRONIC ENGINEERING

First-class opportunities in Radio and Electronics await the ICS trained man. Let ICS train YOU for a well-paid post in this expanding field.

ICS courses offer the keen, ambitious man the opportunity to acquire, quickly and easily, the specialized training so essential to success. Diploma courses in Radio/TV Engineering and Servicing, Colour TV Servicing, also Electronics, Computers, etc.

Expert coaching for:

- C. & G. TELECOMMUNICATION TECHNICIANS' CERTIFICATES.
- C. & G. ELECTRONIC SERVICING.
- R.T.E.B. RADIO AND TV SERVICING CERTIFICATE.
- RADIO AMATEURS' EXAMINATION.
- RADIO OPERATOR CERTIFICATES.

Examination Students coached until successful.

NEW SELF-BUILD RADIO AND ELECTRONIC COURSES

Build your own 5-valve receiver, transistor portable, signal generator and multi-meter. All under expert guidance.

POST THIS COUPON TODAY and find out how ICS can help YOU in your career. Full details of ICS courses in Radio, Television and Electronics will be sent to you by return mail.

MEMBER OF THE ASSOCIATION OF BRITISH CORRESPONDENCE COLLEGES

INTERNATIONAL CORRESPONDENCE SCHOOLS

A WHOLE WORLD
OF KNOWLEDGE
AWAITS YOU!

International Correspondence Schools
(Dept. 152), Intertext House, Stewarts Road,
London SW8 4UJ

NAME.....
Block Capitals Please

ADDRESS.....

AGE..... OCCUPATION..... 9/71

WANTED

CASH PAID for New Valves. Payment by return. WILLOW VALE ELECTRONICS, 4 The Broadway, Hanwell, London, W.7. 01-567 5400/2971.

HIGHEST POSSIBLE CASH prices for Revox, Ferrograph, Brenell, Vortexion, Tandberg. 9.30 - 5.00. 01-837 8200.

WE PAY THE HIGHEST PRICES for new valves. Cash sent by return. A.D.A. MANUFACTURING CO., 116 Alfreton Road, Nottingham.

TOP PRICES PAID.

for new valves and components

Popular T.V. and Radio types
KENSINGTON SUPPLIES

(B) 367 Kensington Street
Bradford 8, Yorks.

DECEMBER '69, MARCH '70 issues of *Practical Electronics*. Offer 50p per copy or will pay by arrangement to borrow for few days. Phone 01-579 1036.

RECEIVERS AND COMPONENTS

BRAND NEW COMPONENTS BY RETURN.

Electrolytics 15 or 25 volts, 1, 2, 5, 10 mfd, 3½p; 25, 50, 4p; 100, 5p. Mylar Film 100V 0-001, 0-002, 0-005, 0-01, 0-02, 2p; 0-04, 0-05, 0-1, 2-5p. Mullard miniature carbon film resistors, third watt E.12 series. 1Ω-10MΩ, 8 for 5p. Postage 5p. THE C.R. SUPPLY CO., 127, Chesterfield Road, Sheffield, S8 0RN.

P. E. AURORA. Complete sets of electronic components for assembly on Vero board. We also have specially designed printed circuit cards for a combined controller/filter system readily available. (S.A.E. for lists).

OPTELMEC LTD.
1, 2 & 3 Nelson Works
Back Road, SIDCUP, Kent

I.C. STEREO AMPLIFIER

3W per channel, internal overvoltage, short circuit and polarity protection. Input required, 250mV for 3W output into 8 ohm speakers. Distortion at max. output 0.5%. Controls, volume, bass, treble and balance. Supply, 18V @ 1A d.c. Size 7in x 8½in x 1½in, will fit into the lower part of most plinths. **Built and tested complete with instructions, £14-75.** P. & P. 25p.

POWER SUPPLY for I.C. Stereo Amplifier, unregulated. Input 230/250V a.c. Output 18V @ 1A d.c. Insulated case size 4in x 4in x 3in. **Built and tested, £4-75.** P. & P. 25p. Amplifier and power supply on one order P. & P. 25p only.


HEATSINKS

5DN Plain undrilled 4in x 4½in x ½in finned one side only, 28p each.
5DN Plain drilled 2 x TO-3 (OC28), 38p each.
10DN Plain undrilled 4in x 4½in x 1½in finned both sides, 38p each.
10DN Plain drilled 2 x TO-3 (OC28), 38p each.
Accessory kits TO-3 (OC28), 1 set 5p; 2 or more sets 4p each.
80-55 (AD161) 1 set 5p; 2 or more sets 4p each.
P. & P. on Heatsinks and Accessory kits 10p under £1.

SEPTON ELECTRONICS

P.O. Box 15, Aldershot, Hants
Mail order only please.

DRY REED INSERTS

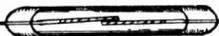

Overall length 1.85" (Body length 1.1"). Diameter 0.14" to switch up to 500 mA at up to 250V D.C. Gold clad contacts. 62p per doz.; £3-75 per 100; £27-50 per 1,000; £250 per 10,000. All carriage paid.

G.W.M. RADIO LTD.

40/42 Portland Road, Worthing, Sussex BN9 34897

RECEIVERS AND COMPONENTS

(continued)

Microcircuits

709 40p; 741 73p; PA230 97p; PA234 87p; PA237 £1-63; 5L402A £1-75; MEL11 35p; D40C1 55p; 7400 21p; 7410 21p; 7430 21p; 7473 42p; 7474 42p; 7486 62p; DIL Conn 25p.

Transistors

2N3055 60p; 2N5172 7p; BCY70 18p; BD124 80p; BFX86 15p; ME0402 21p; ME0412 20p; ME0413 15p; ME1002 12p; ME4101 11p; ME4102 12p; ME6001 13p; ME6101 15p; MEF104 45p; MPB111 35p.

1A Rectifiers

50V 7p; 400V 10p; 600V 14p; 1000V 19p.

Bridges—50V 37p; 100V 40p; 200V 40p.

Printed Circuit Resist Pen, 80p.

JEF ELECTRONICS (P.E.9)

York House, 12 York Drive, Grappenhall, Warrington, Lancs. Mail Order Only. C.V.O. P. & P. 5p per order. Overseas 40p. Money back if not satisfied. List free on application.

RADIO SPARES EQUIPMENT

now available for enthusiasts and amateurs. Callers by appointment. S.A.E. must accompany all enquiries.

SONAR GROUP (Dept. P.E.)

24 Fordway Ave., Blackpool, Lancs.
Telephone 0253 (Blackpool) 32819

COMPUTER PANELS 5-BC108 diodes 15p, post 5p,

4-50p, post 10p. AMERICAN PANELS. Total at least 30 transistors, first grade components, details provided, 3-55p, post 10p. 8-OC170, DIODES, 35p, post 8p each. 8-OC72/73/42, 8-OA10 DIODES, 40p, post 10p each. 4-MDS34, 5-100mF ELECTROLYTICS, 12V potcore, etc., 30p, post 8p each. NEW COIL PACKS: LON4, MED, S.W. piano key. No choke, 80p, post 10p each. ORP18 in panel ex-equipment, 38p c.p. MICRO SWITCHES on or off, 15p c.p., discount for quantities. FERRITE ROD 7" x 1", 12p, post 8p each. LA2 POT CORES. 20 in AL1 box with 20 1% caps, £1-50, post 27p. Singles, 15p c.p. COMPUTER RELAYS. D.P.D.T., 700 ohm coil, weigh 1oz, 55p with base, 65p post free. SMALL SYNCHRONOUS MOTORS with train of gears, 200-250V, 30p post free.

POLYSTYRENE CAPACITORS. 125V, 150, 180, 220, 330, 390, 560, 680, 820, 1,200, 1,500, 1,800, 2,200, 2,700, 3,300, 3,900, 5,600, 6,800, 8,200, 0-01, 0-012, 0-015, 15p dozen, post 10p.

Assorted. 1" leads, 100 for 30p, post 10p.

ASSORTED COMPONENTS. 7lb. £1-25 c.p.

ASSORTED COMPUTER PANELS. 2lb. £1-25 c.p.

J.W.B. RADIO

75 HAYFIELD ROAD, SALFORD 6, LANCs.

MAIL ORDER ONLY

PE GEMINI

STEREO AMPLIFIER

(Dual purpose, 30W per channel)

All the components to build this high quality amplifier, as featured in "Practical Electronics," Nov. 1970—Feb. 1971, are now available from one source.

ALL PARTS CAN BE PURCHASED SEPARATELY.

Please send foolscap size S.A.E. for free complete lists. Return post service.

MAIL ORDER ONLY

ELECTROSPARES

21 BROOKSIDE BAR
CHESTERFIELD, DERBYSHIRE

QUALITY • VALUE • SERVICE

PRINTED CIRCUIT BOARDS FOR P.E. PROJECTS

All boards drilled and roller tinned complete with layout drawing.

EXAMPLES

Marine Tachometer (May 1970) 25p ea. Musical Stave (May 1970) 40p ea.
Waa-Waa pedal Vol. 4 No. 7 14p ea. Audio Sig. Gen. (Sine and Square on one board) Vol. 5 No. 10 42p ea.

S.A.E. for List. Now available from: HENRY'S RADIO LTD., Edgware Road, London, W.2
P.H. ELECTRONICS, Industrial Estate, Sandwich, Kent. Tel. 2517

RECEIVERS AND COMPONENTS

(continued)

TO66 HEAT RADIATORS

Anodised, 2in high, 14°C/W. 12½p (25 + 10p).

Min. S.P. REED RELAYS N/O

12V coil, 10W reed, p.c.b. Mtg. 70p (25 + 60p).

Min. S.P. REED RELAYS C/O

12V coil, 3W reed, p.c.b. Mtg. £1-35 (25 + £1-25).

D.I.L. SOCKETS

14 lead, 40p (25 + 35p); 16 lead, 45p (25 + 40p); also 24 and 40 lead.

Needing semiconductors and components? Let us quote for your "shopping list". Our min. order only £1. Please add 10p for P. & P. Orders over £5 paid. Mail Order only. Strictly C.W.O.

KONTAX ELECTRONICS (Sheerness) Ltd., 115 Barton Hill Drive, Minster-on-Sea, Sheerness, Kent

NEW SILICON TRANSISTORS

Texas markings. NOT seconds, etc., or rejects. Both are for general-purpose, low-level, high-gain applications. Both have hfe 45-800 and max dissipation 250 mw.

2N3708 7p each. (N-P-N, coll-emitter 30v max, coll current 30ma max).

2N4059 9p each. (P-N-P, coll-emitter -30v max, coll current -30ma max).

Ratings at 25°C free-air temp. Data sheets 1p ea. Mail order only. Post etc. 6p per order.

K. M. GRAPHIC (Components Dept.) Ref. D1

8 Gower Street, Derby DE1 1SB

MAGNETIC RECORDING TAPE. Fully Guaranteed.

5in L.P., 60p. 5in D.P., £1. 5in T.P., £1-50. 7in L.P., £1. 7in D.P., £1-55. 7in T.P., £3. Inverter, 15 W 12 to 240 V, £1-50. Postage, 15p. Send 10p for full lists of electronic components. MFJ ELECTRONICS, 495 Alum Rock Road, Birmingham, 8.

CHROMASONIC ELECTRONICS

supply only 1st grade branded goods
subject to makers' guarantees

SN7400N, 1, 2, 4, 5, 10, 20, 26, 30, 40, 50, 51, 54
SN7460N all 25p ea.
SN7441AN, 42, 75, 81, 82, 90, 92, 93, 94, 95 all £1 ea

PA230 82p	PA246 82-45	TAA310 61-25
PA234 87p	TAA263 70p	TAA320 62-5p
PA237 81-57	TAA293 90p	TAD100 61-95
PA239 82-50	TAA300 21-90	TAD110 61-95

LOW NOISE HI-STABS

½ watt 5%, all E24 values 3 for 2p plus p. & p. up to 50 resistors + 1p for each additional 50.

FREE CATALOGUE p. & p. 3p

p. & p. on all orders other than resistors 6p.

56 Fortis Green Road, London
N10 3HN

TELERADIO SPECIAL PRODUCTS

Hi-Fi Amplifier Systems by Texas, Linsley Hood & Bailey. In kit form with P.C. Board.

Digital Clock Kit.

Radio Control Systems.

Details gladly sent on request from

325/7 L. Fore Street, Edmonton, N.9

BATTERY ELIMINATORS

The ideal way of running your TRANSISTOR RADIO, RECORD PLAYER, TAPE RECORDER, AMPLIFIER, etc. Types available: 6v, 9v, 12v, 18v (single output) £2 each. P. & P. 15p. 9v + 9v; 6v + 6v; or 4½v + 4½v (two separate outputs) £2.50 each. P. & P. 15p. Please state output required. All the above units are completely isolated from mains by double wound transformer ensuring 100% safety.

R.C.S. PRODUCTS (RADIO) LTD.
(Dept. P.E.), 31 Oliver Road, London, E.17

BI-PRE-PAK LIMITED

FULLY TESTED AND MARKED

	£p		£p
AC107	0-15	OC170	0-23
AC126	0-13	OC171	0-23
AC127	0-17	OC200	0-25
AC128	0-13	OC201	0-25
AC176	0-25	2G301	0-13
AC177	0-15	2G303	0-13
AF239	0-37	BC113	0-10
AF186	0-50	2N1302-3	0-20
AF139	0-37	2N1304-5	0-25
BC154	0-25	2N1306-7	0-30
BC171 = BC107	0-13	2N1308-9	0-35
BC172 = BC108	0-13	2N3819FET	0-45
BF194	0-15		
BF274	0-15	Power Transistors	
BFY50	0-20	OC20	0-50
BSY25	0-57	OC23	0-30
BSY26	0-13	OC25	0-25
BSY27	0-13	OC26	0-25
BSY28	0-13	OC28	0-30
BSY29	0-13	OC35	0-25
BSY95A	0-13	OC36	0-37
OC41	0-13	AD149	0-30
OC44	0-13	AUJ10	0-25
OC45	0-13	2S034	0-25
OC71	0-13	2N3055	0-63
OC72	0-13		
OC73	0-17	Diodes	
OC81	0-13	AA42	0-10
OC81D	0-13	OA95	0-10
OC83	0-20	OA79	0-09
OC139	0-13	OA81	0-09
OC140	0-17	IN9114	0-07

FREE!

PACKS OF YOUR OWN CHOICE UP TO THE VALUE OF 50p WITH ORDERS OVER £4

CLEARANCE LINES

	1-10	10-50	50+
SL403D Audio amp.	£2	£1.95	£1.80
1C 709C Linear Opp. amp	50p	40p	35p
A.E.I. fully marked and tested gates	25p	22p	20p
A.E.I. fully marked and tested flip-flops	50p	40p	30p
OC71/72 fully tested unmarked	5p	5p	4p
Matched sets 1-OC44, 2-OC45 per set	25p	20p	15p
Matched sets OC45's 1st and 2nd IF per set	15p	12p	10p
TIC 45 Thyristors—			
6 amp 60V Texas	15p	15p	12p
OA47 gold bonded diodes	3p	3p	2p
1W Zener diodes 6-8, 7-5, 24, 27, 30 and 43V	5p	4p	3p
10W Zener diodes 7-5, 11, 13, 20 and 100V	20p	17p	15p
Micro switches, S/P, C/O	25p	20p	15p
1 amp bridge rec. 25V	25p	22p	20p
1 amp plastic rectifiers. These are voltage, reversed polarity and other rejects from the BY127 range. Ideal for low voltage power units etc. Price £1 per 100.			

COLOUR T.V. LINE OUTPUT TRANSFORMERS

Designed to give 25kV when used with PL509 and PY500 valves. As removed from colour receivers at the factory. **ONLY £1 each** post and packing 23p.

BUMPER BUNDLES

These parcels contain all types of surplus electronic components, printed panels, switches, potentiometers, transistors and diodes, etc.

2 LBS IN WEIGHT FOR £1
Post and packing 25p.

NEW TESTED AND GUARANTEED PAKS

B2	4	Photo Cells, Sun Batteries. 0.3 to 0.5V, 0.5 to 2mA.	50p
B79	4	IN4007 Sil. Rec. diodes, 1,000 PIV lamp plastic	50p
B81	10	Reed Switches, mixed types large and small	50p
B99	200	Mixed Capacitors. Postage 13p. Approx. quantity, counted by weight	50p
H4	250	Mixed Resistors. Postage 10p. Approx. quantity, counted by weight	50p
H7	40	Wirewound Resistors. Mixed types and values. Postage 8p	50p
H8	4	BY127 Sil. Recs. 1000 PIV. 1 amp. plastic	50p
H9	2	OCPT1 Light Sensitive Photo Transistor	50p
H12	20	NKT155/259 Germ. diodes, brand new stock clearance	50p
H18	10	OC71/75 uncodded black glass type PNP Germ.	50p
H19	10	OC81/81D uncodded white glass type PNP Germ.	50p
H28	20	OC200/1/2/3 PNP Silicon uncodded TO-5 can	50p
H29	20	OA47 gold bonded diodes coded MCS2	50p

OUR VERY POPULAR 3p TRANSISTORS

FULLY TESTED & GUARANTEED

- TYPE "A" PNP Silicon alloy, metal TO-5 can. 2S300 type, direct replacement for the OC200/203 range.
- TYPE "B" PNP Silicon, plastic encapsulation, low voltage but good gain, these are of the 2N3702/3 and 2N4059/62 range.
- TYPE "E" PNP Germanium AF or RF—please state on order. Fully marked and tested.
- TYPE "F" NPN Silicon plastic encapsulation, low noise amplifier of the 2N3708, 9, 10, 11.

BULK BUYING CORNER

NPN/PNP Silicon Planar Transistors, mixed, untested, similar to 2N706/6A/B, BSY26-29, BSY95A, BCY70, etc. £4-25 per 500; £8 per 1,000.

Silicon Planar NPN Plastic Transistors, untested, similar to 2N3707-11, etc., £4-25 per 500; £8 per 1,000.

Silicon Planar Diodes, DO-7 Glass, similar to OA200/202, BAY31-36, £4-50 per 1,000.

NPN/PNP Silicon Planar Transistors, Plastic TO-18, similar to BC113/4, BC153/4, BF153/160, etc., £4-25 per 500; £8 per 1,000.

OC44, OC55 Transistors fully marked and tested, 500+ at 8p each; 1,000+ at 6p each.

OC71 Transistors, fully marked and tested, 500+ at 6p each; 1,000+ at 5p each.

3823E Field effect Transistors. This is the 2N3823 in Plastic Case, 500+ 13p each; 1,000+ 10p each.

1 amp Miniature Plastic Diodes:
IN4001, 500+ 3p each; 1,000+ 3p each.
IN4004, 500+ at 5p each, 1,000+ at 4p each.
IN4006, 500+ at 6p each, 1,000+ at 5p each.
IN4007, 500+ at 8p each, 1,000+ at 7p each.

NEW UNMARKED UNTESTED PAKS

B66	150	Germanium Diodes Min. glass type	50p
B83	200	Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ.	50p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	50p
B86	50	Sil. Diodes sub. min. IN914 and IN916 types	50p
B88	50	Sil. Trans. NPN, PNP, equiv. to OC200/1, 2N706A, BSY95A, etc.	50p
B60	10	7 Watt Zener Diodes Mixed Voltages	50p
H6	40	250mW. Zener Diodes DO-7 Min. Glass Type	50p
H10	25	Mixed volts, 1½ watt Zeners. Top hat type	50p
H11	30	MAT Series " alloy " npn Transistors	50p
H15	30	Top Hat Silicon Rectifiers, 750mA. Mixed volts	50p
H16	8	Experimenters' Pak of Integrated Circuits. Data supplied	50p
H20	20	BY126/7 Type Silicon Rectifiers, 1 amp plastic. Mixed volts.	50p

F.E.T. PRICE BREAKTHROUGH!!!

This field effect transistor is the 2N3823 in a plastic encapsulation, coded as 3823E. It is also an excellent replacement for the 2N3819.

Data sheet supplied with device.

1-10 30p each, 10-50 25p each, 50+ 20p each.

Make a Rev. Counter for your Car. The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car. **£1 each**

FREE CATALOGUE AND LISTS for:—

ZENER DIODES TRANSISTORS, RECTIFIERS FULL PRE-PAK LISTS & SUBSTITUTION CHART

MINIMUM ORDER 50p CASH WITH ORDER PLEASE. Add 10p post and packing per order. OVERSEAS ADD EXTRA FOR AIRMAIL.

P.O. RELAYS 8 FOR

Various Contacts and Coil Resistances. No individual selection. Post & Packing 25p **£1**

FREE! A WRITTEN GUARANTEE WITH ALL OUR TESTED SEMICONDUCTORS

BI-PRE-PAK LTD

DEPT. A, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX
TELEPHONE: SOUTHEND (0702) 46344

STEREO - NOW YOU CAN BUILD YOUR OWN

Mullard Unilex modules need no soldering, no knowledge of electronics. They make the stereo amplifier so simple that anyone can build it in an hour, for around £16. Connect the record deck and speakers and you've built your stereo system. For the comprehensive instruction book 'Do-it-yourself Stereo' and stockist list post this coupon today with a 25p P.O.



Mullard UNILEX

Room 512,
Mullard House,
Torrington Place,
London WC1E 7HD.

Name _____

Address _____

PE9.71

CED 136A

BRUNEL TECHNICAL COLLEGE, BRISTOL

DEPARTMENT OF MARINE AND
AERO-ELECTRONICS

MARINE RADIO OFFICERS

The Department offers the following courses for prospective Radio Officers in the Merchant Navy—2 years' full-time course leading to the Ministry of Posts and Telecommunications General Certificate in Radiocommunications. 1 term full-time course leading to the Department of Trade and Industry Radar Maintenance Certificate. Conversion Course from 1st or 2nd class MPT R/T Licences (Full and Restricted). Marine Electronics Diploma. Advanced Marine Electronics Diploma.

LICENSED AIRCRAFT RADIO ENGINEERS (Civil Aviation)

A full-time course of two years' duration commences in September of each year. This leads to the award of the Aircraft Maintenance Engineers Category R Licence issued by the Air Registration Board.

All instruction and practice is carried out with modern equipment and test instruments, in well-equipped laboratories and workshops at the College and on the Department's own aircraft at Bristol Airport.

The Department also offers a course for the Board of Trade Civil Aeronautical RT Licence.

For further information apply to — Head of Department of Marine and Aero-Electronics,

Brunel Technical College, Ashley Down

BRISTOL BS7 9BU

Telescopic Aerials 47in	Each	10	100
Capacitors 400-200-50-10mF	45p	£4	£36
16-16mF 450V	30p	£2-60	£23
Dubilier 0-1 500V	21p	£1-80	£18
TCC 0-1 400V	30p	30p	£2-50
Hunts 0-04mF 500V	21p	20p	£1-80
TCC 0-001 and 0-005	2p	18p	£1-60
100pF Feed through Ceramics	3p	25p	£2-20
Plugs Jack Standard	10p	85p	£5-50
.. 3.5mm	7p	80p	£4
.. 2.5mm Shielded	8p	70p	£6
Sockets Jack Standard	7p	50p	£4-50
.. 3.5mm	5p	35p	£2-50
Electrolytic Transistor Type			
5mf 10V	21p	20p	£1-80
10mf 10V	21p	20p	£1-80
30mf 10V	3p	25p	£2-20
50mf 10V	4p	35p	£3-10
25mf 50V	6p	55p	£5
50mf 50V	7p	65p	£6
500mf 12V	9p	88p	£8-10
250mf 12V	7p	85p	
6400mf 25V	50p		
Switches, Rotary D.P. 250V 2A	8p	80p	
Skeleton Presets 2K	8p	70p	
Microphones, Lapel	37p	£3-20	
Acos MIC 4	92p	£8-75	
.. MIC 60	94p	£9	
UD130 Dual Impedance 600 ohm and 50K	£4-50	£40	
8 Watt Transistor Amplifier	£3-45	£28-50	
Crystal Ear piece	20p	£1-80	
2 Way Intercoms, OHTDEN	£2-50	£21	
5K Potentiometers with Switch	18p	£1-40	
Co-ax. Sockets on Isolation Panel	8p	50p	
Balance and Tuning Meters 500µA	38p	£3-40	
100 Mixed Resistors	45p		
Rectifiers Battery Charging 11A	18p		
.. .. 2A Contact Cooling	27p	£2-50	
.. .. 4A	42p	£3-80	
Valve Bases B7G and B9A	3p	28p	
Miniature Indicator Lamps	11p	£1	
6V or 12V Bulbs for above	4p	35p	
Add 10p on orders under £5.			

For Items not listed or prices for large quantity please enquire:

M. DZIUBAS
158 Bradshawgate
Bolton, Lancs.

FERRANTI

SEMICONDUCTORS AT LOWEST PRICES

ZTX107	10p	ZTX501	11p	Z8142	30p	K8036A	17p
ZTX108	9p	ZTX502	15p	Z8170	9p	K8039A	17p
ZTX109	10p	ZTX503	18p	Z8171	11p	K8043A	17p
ZTX300	10p	ZTX504	38p	Z8172	14p	K8047A	17p
ZTX301	11p	ZTX510	18p	Z8174	15p	K8051A	17p
ZTX302	15p	ZTX530	18p	Z8176	21p	K8056A	17p
ZTX303	12p	ZTX631	20p	Z8178	34p	K8062A	17p
ZTX304	19p	BFS59	15p	Z8270	10p	K8068A	17p
ZTX310	7p	BFS60	19p	Z8271	14p	K8075A	17p
ZTX311	9p	BFS61	19p	Z8272	16p	K8082A	17p
ZTX312	9p	BFS96	16p	Z8274	17p	K8091A	17p
ZTX313	10p	BFS97	21p	Z8276	28p	K8100A	17p
ZTX314	11p	BFS98	21p	Z8278	33p	K8110A	17p
ZTX320	25p					K8120A	17p
ZTX330	13p	Diodes		Zeners		K8130A	17p
ZTX331	14p	Z8140	22p	K8030A	17p	K8130A	17p
ZTX500	10p	Z8141	39p	K8033A	17p	K8150A	17p

Postage and Packing 10p. Free above £2. Send S.A.E. for data.

DAVIAN ELECTRONICS
P.O. Box 38, Oldham, Lancs.

BAKER 15in. AUDITORIUM

A high wattage loudspeaker of exceptional quality with a level response to above 8,000 cps. Ideal for Public Address, Discotheques, Electronic instruments and the home.

Maximum Power 35 watts
Bass Resonance 35 c.p.s.
Flux Density 15,000 gauss
Voice coil impedance 8 or 15 ohms models
Useful response 20-14,000 c.p.s.
Nett weight 15 lbs.

£19

POST
FREE

GUITAR MODEL "GROUP 50" 50 watt £19
Latest catalogue 5p with enclosure plans

Baker Reproducers Ltd

Bensham Manor Road Passage, Thornton Heath, Surrey. 01-684-1665



In just 2 minutes, find out how you can qualify for promotion or a better job in Engineering ...

That's how long it will take you to fill in the coupon below. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. Home Study Course gets results fast - makes learning easier and something you look forward to. There are no books to buy and you can pay-as-you-learn on 'SATISFACTION - OR REFUND OF FEE' terms. If you'd like to know how just a few hours a week of your spare time, doing something constructive and enjoyable, could put you out in front, post the coupon today. No obligation.

WHICH SUBJECT WOULD INTEREST YOU?

Mechanical

A.M.S.E. (Mech.)
Inst. of Engineers
Mechanical Eng.
Maintenance Eng.
Welding
General Diesel Eng.
Sheet Metal Work
Eng. Inspection
Eng. Metallurgy
C. & G. Eng. Crafts
C. & G. Fabrication

Draughtsmanship

A.M.I.E.D.
Gen. Draughtsmanship
Die & Press Tools
Elec. Draughtsmanship
Jig & Tool Design
Design of Elec. Machines
Technical Drawing
Building

Electrical & Electronic

A.M.S.E. (Elec.)
C. & G. Elec. Eng.
General Elec. Eng.
Installations & Wiring
Electrical Maths.
Electrical Science
Computer Electronics
Electronic Eng.

Radio & Telecomms.

C. & G. Telecomms.
C. & G. Radio Servicing
Radio Amateurs' Exam.
Radio Operators' Cert.
Radio & TV Engineering
Radio Servicing
Practical Television
TV Servicing
Colour TV
Practical Radio & Electronics (with kit)

Auto & Aero

A.M.I.M.I.
MAA IMI Diploma
C. & G. Auto Eng.
General Auto Eng.
Motor Mechanics
A.R.B. Certs.
Gen. Aero Eng.

Management & Production

Computer Programming
Inst. of Marketing
A.C.W.A.
Works Management
Work Study
Production Eng.
Storekeeping
Estimating
Personnel Management
Quality Control
Electronic Data Processing
Numerical Control
Planning Engineering
Materials Handling
Operational Research
Metrication

Constructional

A.M.S.E. (Civ.)
C. & G. Structural
Road Engineering
Civil Engineering
Building
Air Conditioning
Heating & Ventilating
Carpentry & Joinery
Clerk of Works
Building Drawing
Surveying
Painting and Decorating.
Architecture
Builders' Quantities

General

C.E.I.
Petroleum Tech.
Practical Maths.
Refrigerator Servicing
Rubber Technology
Sales Engineer
Timber Trade
Farm Science
Agricultural Eng.
General Plastics

General Certificate of Education

Choose from 42 'O' and 'A' Level subjects including:
English
Chemistry
General Science
Geology
Physics
Mathematics
Technical Drawing
French
German
Russian
Spanish
Biology
B.I.E.T. and its associated schools have a recorded success over 10,000 G.C.E. successes at 'O' and 'A' level.
WE COVER A WIDE RANGE OF TECHNICAL AND PROFESSIONAL EXAMINATIONS.

Over 3,000 of our Students have obtained City & Guilds Certificates. Thousands of other exam successes.

THEY DID IT— SO COULD YOU

"My income has almost trebled... my life is fuller and happier."—Case History G/321.

"In addition to having my salary doubled, my future is assured."—Case History H/493.

"Completing your Course meant going from a job I detested to a job I love."—Case History B/461.

FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you.

Free!

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). We'll send you full details and a FREE illustrated book. No obligation and nobody will call on you... but it could be the best thing you ever did.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept B4, Aldermaston Court, Reading RG7 4PF.

POST THIS COUPON TODAY

(Write if you prefer not to cut this page)



To: B.I.E.T., Dept B4, Aldermaston Court, Reading RG7 4PF
Please send me book and details of your Courses in

Name Age

Address

Occupation

B.I.E.T. - IN ASSOCIATION WITH THE SCHOOL OF CAREERS - ALDERMASTON COURT, BERKSHIRE

Published approximately on the 15th of each month by IPC Magazines Ltd., Fleetway House, Farringdon Street, London, E.C.4. Printed in England by Chapel River Press, Andover, Hants. Sole Agents for Australia and New Zealand - Gordon & Gotch (A/asia) Ltd.; South Africa - Central News Agency Ltd.; Rhodesia and Zambia - Kingstons Ltd.; East Africa - Stationery and Office Supplies Ltd. Subscription Rate (including postage): For one year to any part of the world £2.50 (42.13.0.). Practical Electronics is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.


HENRY'S RADIO LIMITED



ENGLAND'S LEADING ELECTRONIC CENTRES

HI-FI · COMPONENTS · TEST · PA · DISCOTHEQUE · ELECTRONIC ORGANS · MAIL ORDER

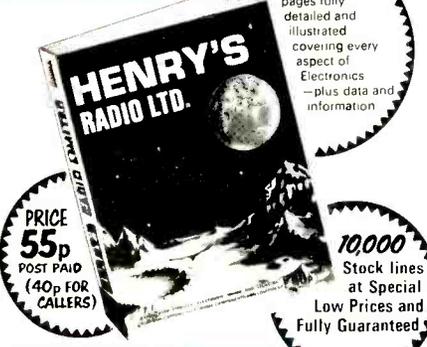**COMPLETELY NEW
10th EDITION
CATALOGUE**



350 pages fully detailed and illustrated covering every aspect of Electronics —plus data and information

PRICE 55p
POST PAID
(40p FOR CALLERS)

10,000 Stock lines at Special Low Prices and Fully Guaranteed

PLUS! FIVE 10p VOUCHERS FOR USE WITH PURCHASES

FREE to Industry, Educational or any Organisation, including Schools and Colleges, etc. Apply on Official heading to our "303" address.

A NEW HENRY'S CATALOGUE IS A MUST FOR ELECTRONICS TODAY!

To Henry's Radio Ltd. (Dept. PE)
3 Albemarle Way, London, E.C.1.

Please send.....copies at 55p each Post Paid.

I enclose Cheque/PO for

(Use **BLOCK CAPITALS**—cut out and send with Cheque or Postal Order (No cash please). Use only for ordering catalogue).

Name

Address

..... (PE)

Allow 7-10 days from date of posting.

MORE OF EVERYTHING AT LOW PRICES ALWAYS FROM HENRY'S

*Components from stock for almost all published designs.

TRANSISTOR AMPLIFIERS

NEW RANGES NOW IN STOCK

(Leaflets Ref. Nos. 6 and 8).

Post, etc. 20p.

4-300 4TR 9V 300mW	£1-75
104 4TR 9V 1W	£2-12
304 4TR 9V 3W	£2-47
555 6TR 12V 3W	£2-75
PA7 6TR 16V 7W	£3-62
608 6TR 24V 10W	£4-12
410 4TR 28V 10W	£4-97
MPA12/3 6TR 18V 12W	£4-50
MPA12/15 6TR 36V 12W	£5-25
Z30 9TR 30V 20W	£3-75
PA25 10TR (Special) 25W	£7-50
Z50 30V 40W	£5-47
PA50 12TR (Special) 50W	£9-50
100 100W with power supply	£45

post 45p

OPTIONAL POWER SUPPLIES

Post, etc., 20p


PS00 (One or Two) for 104, 304	£2-62
PS20 (One or Two) for PA7	£3-47
MU24/40 (One or Two) for MPA12/3 or MPA12/15	£4-50
PZ5 for Z30 or PZ6 for Z30	£6-97
PZ8 for Z50	£2-25
P11 for 608	£2-87
MU442 for 1 or 2 PA25 or 1 only PA50	£6-50

Post, etc., 20p

NEW MINIATURE LOW COST AMPLIFIER MODEL 4-300

9V operated or mains unit optional transformer (MT98 70p), 1-10mV adjustable sensitivity. P/P output for 3-8 ohms. Fitted volume control and leads. Size 5½in x 1½in x ¾in. Thousands of uses—takes magnetic, dynamic and crystal inputs direct. Output 300mW—very high gain—built in rectifier circuit.

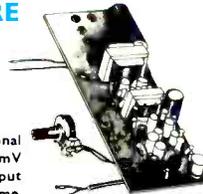Price £1-75
P.P. 15p. Complete with FREE leaflet No. 8.



HI-FI TO SUIT EVERY POCKET



CHOOSE 100 STEREO SYSTEMS FROM

and a complete range of individual units in stock—Demonstrations all day—visit our new Hi-Fi Store. **LOW CASH OR CREDIT/HP TERMS** (Credit terms from £30 purchase—callers only). **FREE**—Stock Lists Nos. 16/17 on request. **BEST VALUE IN U.K.**

GARRARD TAPE DECK



9V operated 2-speed tape deck fitted Record/Replay track and Erase/Bias Osc. Head. Complete with Oscillator/Record head circuit. Unit size 9in x 6½in x 1½in and 2½in below motor board. Takes up to 4in spools. Supplied Brand New.

Price £9-97
P.P. 33p (¾in. tape 300ft.) and spool 40p.

BUILD YOURSELF A QUALITY RADIO



HENELEC EQUIPMENT

(as previously advertised)

SELF-POWERED SILICON PRE-AMPLIFIERS
FET154 Stereo £16-50, post 25p.
FET9/4 Mono with mike mixer £12-50, post 20p.

SILICON POWER AMPLIFIERS FOR USE WITH ABOVE
PA25 25W into 8Ω £7-50, post 20p.
PA50 50W into 4Ω £9-50, post 20p.
MU442 power supply for 1 or 2 PA25's or 1 only PA50 £6, post 20p.

PACKAGE DEALS
FET9/4 plus PA25 plus MU442 £25, post 40p.
FET9/4 plus PA50 plus MU442 £27, post 40p.
FET154 plus 2 x PA25 plus MU442 £36, post 50p.
FET154 plus 2 x PA50 plus 2 x MU442 £40, post 50p.

No soldering—just edge connectors and din plugs/sockets.
Free Brochure No. 25.



Total cost £6-98, p.p. 35p. All parts sold separately. Ask for Leaflet No. 1.

PROJECT 60 PACKAGE DEALS
2 x Z30 amplifier, stereo 60 pre-amp. PZ5 power supply, £16-75. Carr. 40p. Or with PZ6 power supply, £18-25. Carr. 40p. 2 x Z50 amplifier, stereo 60 pre-amplifier PZ8 power supply, £20-25, p.p. 40p. Transformer for PZ8 £2-25 extra. Any of the above with Active Filter unit add £4-75 or with pair Q16 speakers add £15. Also **NEW FM TUNER, £21.**

BUILD THIS YHF FM TUNER

5 MULLARD TRANSISTORS 300kc/s BANDWIDTH. PRINTED CIRCUIT, HIGH FIDELITY REPRODUCTION. MONO AND STEREO. A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately. Free Leaflet Nos. 3 and 7. **TOTAL £6-97**, p.p. 20p. Cabinet £1, Decoder Kit £5-97. Tuning meter £1-75. Mains unit (optional) Model PS900 £2-47. Mains unit for Tuner and Decoder PS1200 £2-62.



Electronic Components,
Audio and Test Gear Centre
**356 EDGWARE ROAD,
LONDON, W.2.**
Tel: 01-402 4736

High Fidelity Sales &
Demonstrations Centre
**354 EDGWARE ROAD,
LONDON, W.2.**
Tel: 01-402 5854

Electronic Organs,
P.A. & Discotheque Centre
**309 EDGWARE ROAD,
LONDON, W.2.**
Tel: 01-723 6963

Mail Orders, Special Bargain
Shop, Industrial Sales
**303 EDGWARE ROAD,
LONDON, W.2.**
Tel: 01-723 1008/9

"354" & "356" OPEN SIX FULL DAYS A WEEK 9 am to 6 pm MONDAY TO SATURDAY