

PRACTICAL

ELECTRONICS

MAY 1976

35p

FREE!

ADD-ON CAPACITANCE UNIT



...this PRINTED WIRING BOARD

ideal for this



ALSO INSIDE...



DIGITAL FREQUENCY METER

Plus

AUDIO



COMPASS

PRACTICAL ELECTRONICS

VOLUME 12 No. 5 MAY 1976

CONSTRUCTIONAL PROJECTS

- DIGITAL FREQUENCYMETER** *by A. J. Buxton*
Gives digital readout of frequency measurement of up to 500MHz 376
- ADD-ON CAPACITANCE UNIT** *by R. W. Lawrence*
Direct measurement of capacitance on your multimeter.
Can be built on the free printed wiring board provided with this issue.* 390
- AUDIO COMPASS** *by M. Kenward*
An off-course alarm for use on self-steered yachts and power craft. Allows ears to replace eyes
when steering a compass course at night 394
- COMPUTER VOICE** *by E. A. Parr*
Generates those "Dalek"-type voice effects 406

GENERAL FEATURES

- USING CMOS DIGITAL I.C.s—5** *by D. B. Johnson-Davies & A. M. Marshall*
Electronic switches and oscillators 384
- SEMICONDUCTOR UPDATE** *by R. W. Coles*
A look at some recently released devices 404
- HELLS, BELLS AND DECIBELS** *by D. Maynard*
Ever get confused about dB's? This article helps clarify the subject 411
- INGENUITY UNLIMITED**
Multiple Octave Organ—Time Switch—Burglar Alarm—Frequency Divider—Indicator for
Discotheque PFL System—Light-on Indicator—Courtesy Light Timer—Dual Fade for Slide
Presentation—Low Voltage Indicator—Car Alarm—Recording Level Indicator—Touch Keyboard 413

NEWS AND COMMENT

- EDITORIAL—Under-Sold?** 375
- NEWS BRIEFS**
Summer School 382
- BOOK REVIEWS**
Selected books we have received 382
- POINTS ARISING**
How Inventive Competition—Digi-Probe—Opto-Coupled R.P.M. Meter 382
- SPACEWATCH** *by Frank W. Hyde*
Soviet Venus Probes—Powersat—Set Backs 383
- MARKET PLACE**
Interesting new products 410
- INDUSTRY NOTEBOOK** *by Nexus*
What's happening inside industry 412
- PATENTS REVIEW**
Latest patent information including price increase 424

*** FREE WITH THIS ISSUE — PRINTED WIRING BOARD**

Our June issue will be published on Friday, May 14, 1976
(for details of contents, see page 405)

© IPC Magazines Limited 1976. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

ERSIN

Multicore

5 CORE SOLDER

for fast easy reliable soldering EASY TO USE DISPENSERS AND REELS IDEAL FOR HOME CONSTRUCTORS

Ersin Multicore Solder contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux is required.

SAVBIT handy solder dispenser



A coil of Ersin Multicore Savbit Solder in a dispenser 7ft 6in of 18 s.w.g. (2.2 metres of 1.22mm). The Solder that reduces the wear of soldering iron bits.

Size 5
32p

SAVBIT solder for general purpose work

A handy plastic reel of SAVBIT alloy. 63ft of 18 s.w.g. (19.2 metres of 1.22mm)

Size 12 £1.80



ALU-SOL for soldering aluminium

New Multicore Alu-sol flux-cored solder in 16 s.w.g. No extra flux needed. Plastic reel holds 36ft. Supplied with full instructions. Also available in solder dispenser.

Size 4 £2.32



Fine gauge solder for soldering small components

Fine gauge solder for soldering small components 138ft of 22 s.w.g. (42.0 metres of 0.71mm) Ersin Multicore 5 core solder wound on a plastic reel. Suitable for intricate work and small components.

Size 10 £1.44



For soldering fine joints




Dispensers of Ersin Multicore Solder make those small jobs easier. 21ft of 22 s.w.g. (6.4 metres of 0.71mm) solder, specially suitable for soldering fine wires, small components and for repairing printed circuits.

Size 15 40p

Or size 19A for kit wiring or Radio and T.V. repairs 7ft. (2.1 metres) of 18 s.w.g. (1.22mm) Ersin Multicore Solder.

Size 19A 34p

NEW BIB WIRE STRIPPER & CUTTER

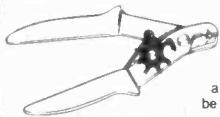

Fitted with unique 8 gauge selector with handle locking device and easy grip handles. Spring incorporated for automatic opening. Strips insulation from flex and cables in seconds and can also be used as a cutter.

Model 8B.80p

NEW SOLDER WICK



Absorbs solder instantly, from tags and printed circuits. Only needs 40 to 50 Watt soldering iron. Quick and easy to use. Does not need flux and is non-corrosive.

Size 18 90p

Bib Hi-Fi Accessories Limited,

Sole U.K. Sales Concessionaires, P.O. Box 78 Hemel Hempstead, Herts. HP2 4RH

Prices shown are recommended retail excluding VAT. From Electrical and Hardware Shops. If unobtainable, send 20p P & P plus VAT at 8p in the £1. Prices and specifications subject to change without notice.


Vero Electronics Ltd. manufacture cases to give your projects a *professional* finish. Cases are available in plastic, extruded aluminium and PVC coated steel. A new catalogue describing these cases, Veroboard, pins, tools, card frame etc. is available (price 10p + S.A.E. 7" x 9")

vero

THE CASE OF THE PROFESSIONAL FINISH...



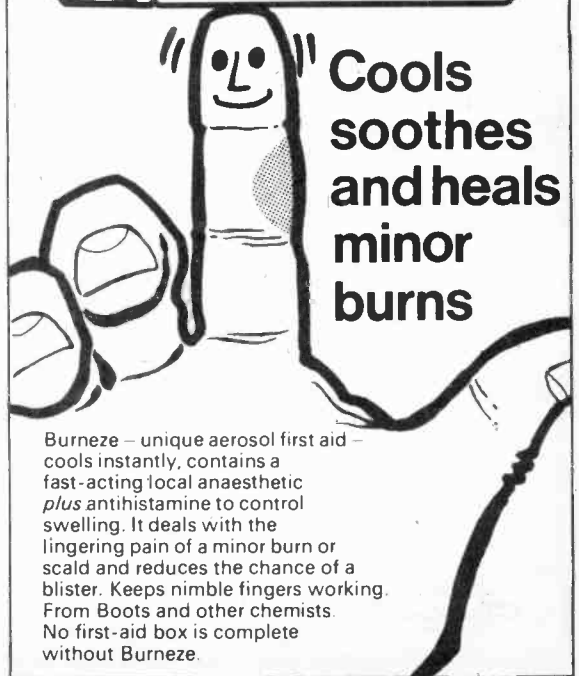Vero Electronics Limited, Retail Dept., Industrial Estate, Chandler's Ford, Hants., SO5 3ZR
Telephone: Chandler's Ford 2956 (STD 04125)



Cools soothes and heals minor burns

Burneze - unique aerosol first aid - cools instantly, contains a fast-acting local anaesthetic plus antihistamine to control swelling. It deals with the lingering pain of a minor burn or scald and reduces the chance of a blister. Keeps nimble fingers working. From Boots and other chemists. No first-aid box is complete without Burneze.

SAXON

ENTERTAINMENTS LTD.


SYSTEM 7000

professional standards · realistic prices

SA1208D—120 WATTS RMS POWER AMP USES 150W 16A RCA DEVICES

All three types include

- 10 Transistors 4 Diodes—Fibre Glass P.C.B.
- Typical Distortion—0.4% Noise—80dB
- Short, Open Circuit proof—Load line limiting
- Only FOUR Connections—Simplicity!
- High sensitivity (240mV) suits most mixers
- 30H—40kHz \pm 1dB frequency response
- Single supply line—No output capacitor needed (95V)
- Standard 8 Ω output—will operate on other impedances
- Compact—6" x 3" x 1½" (15 x 8 x 4cm)
- All units individually tested and guaranteed

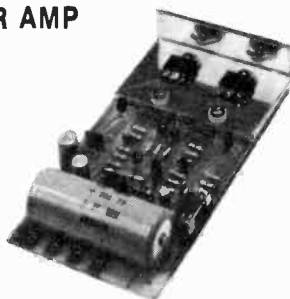

Large S.A.E. brings leaflet

In the same series

SA608
60W RMS
INTO 8 Ω (65V)
£12.50

SA308
30W RMS
into 8 Ω (48V)
£9.50

SA1208D £19.50

POWER SUPPLIES

On glass-fibre P.C.B., high grade transformer, fully fused and ready to wire:

PM1201 for one SA1208D **£11.60**

PM1202 for two SA1208D **£15.30**

PM601/2 for one or two SA608 **£10.50**

PM301/2 for one or two SA308 **£8.80**

SYSTEM 7000 DISCO CONTROL UNIT



- Complete and ready to plug in
- Totally encased—no soldering at all
- Tough, bold, two tone stainless panel—for panel mounting or freestanding
- Inputs for 2 ceramic cartridges/tape/microphone
- Individual deck controls AND left/right fader
- Low noise (-80 dB) 20Hz—50kHz \pm 1dB
- Suits all Saxon amplifiers and most other makes
- ½ watt headphone monitor—five position switch with mute positions

- CONTROLS—L. to R.: Mic Vol/Treble/Bass, Autofade depth, L/Deck Vol, R/Deck Volume, Tape Volume, Treble, Bass, Master, Monitor Volume, Monitor Selector-On-Off

Mono **£34.50**

Stereo **£49.50**

IN MODULAR FORM


Printed circuit sub-assembly version of disco control unit. All electronics included. Only plugs, socket and one switch required.

Mono **£18.50** Stereo **£27.50**

Front panel for either version **£3.50**

SYSTEM 7000 LIGHTING CONTROL UNIT

- Full control of 3kW of lights (1kW/channel)
- Audio control plus sequence plus override
- Variable speed sequence with slider function control
- Stainless steel two tone panel—matches mixer
- 13 transistors 8 diodes—advanced control circuitry
- High audio sensitivity—operates from any amplifier
- Attractive Bondene case—free standing or panel mounting
- Individual tone controls plus master audio control

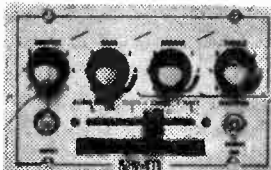

SUPERFECT MODULE

On P.C.B. Requires only plug/socket/panel for mounting as desired **£27.75**

£38.00 Inc. case and plug—ready to use

SOUNDLITE 3KW CONVERTER MODULE

O/p up to 1kW/channel: Individual tone and master controls: RCA 8A triacs: SCINTILLATING LIGHT DISPLAY: Operates from any amplifier: glass-fibre PCB: Unbeatable value at

£15.50

SYSTEM 7000 MODULAR MIXING

- COMPLETELY WIRED WITH STAINLESS PANEL:
- UP TO 20 CHANNELS MONO, STEREO OR MIXED

- Inputs for all sources inc. mag. cartridge
- Wide range bass and treble controls
- Only one mixing module required
- ½W monitor power outlet
- Feeds most amplifiers
- Modern low noise circuitry
- 20Hz—30kHz \pm 1dB
- Echo send/return facility
- Complete—ready to plug in or solder
- 5cm matrix—bold panel
- Individual monitor buttons
- Send for details

with panels as illustrated



INPUT Mono **£8.50** Stereo **£12.00**

MIXER Mono **£8.50** Stereo **£12.00**

IN PCB MODULAR FORM

With same facilities and performance as complete units with panels as illustrated. Up to 20 input modules may be used with one mixer. On glass-fibre PCBs. Soldered or edge connections.

IM7001/M mono input **£5.50**

IM7001/S stereo input **£9.00**

IM7002/M mono mixing **£5.50**

IM7002/S stereo mixing **£9.00**

SAXON STROBES

- SUPERSTROBE
- 1 flash/2 sec up to 20 flashes/sec
- Compact black Bondene case
- Ideal for the mobile disco or smaller club

£24.75

- PRO-STROBE
- Giant 80 watt tube. Discharge energy up to 8 Joules
- External trigger—audio up to 240V
- Use with Soundlite for rainbow strobe effect
- Smart, tough Bondene case 8in x 8in x 5in approx.

£38.50

150 WATT LIQUID WHEEL PROJECTOR

- Complete with wheel and 150 watt tungsten lamp
- Wide range of extra effects may be attached
- Adjustable feet
- A valuable acquisition in any modern set-up

£29.20 Spare wheels **£4.90**



LOUDSPEAKERS 12"/50W high grade chassis units, 14000 gauss: presence dome: **£14.50**

CABINETS

Attractive range of speaker and other cabinets at our showroom. Enquiries welcomed

ACCESSORIES

Mics: Headphones: Special Lamps.

PRICES include carr. and packing ● V.A.T. must be added to value of all U.K. orders at 8% ● C.O.D. 65p extra ● S.A.E. all enquiries please

Send or phone your ACCESS or BARCLAY CARD No. for prompt attention. After 5pm leave your message on our Answer-phone

Orders by post. Please make cheques or crossed P.O. s payable to
SAXON ENTERTAINMENTS LTD.

327-333 Whitehorse Road, Croydon, Surrey CR0 2HS

Telephone: 01-684 6385/0098

Shop Hours 9am-5pm (Lunch 12.30-1.70); Sat. 9.30am-5pm ● Prices and specifications subject to alteration without notice ● Mail Order desk 10am-4pm Mon-Fri

TRADE ENQUIRIES

Send for name and address of your nearest wholesale supplier

Sinclair SCIENTIFIC KIT




ONLY £6.50
+50p p&p

LASKYS now offer this Sinclair Scientific Calculator for a fraction of the original cost. All parts are supplied - all you need provide is a soldering iron and a pair of cutters, complete step-by-step instructions. Assembly time is about 3 hours. The Sinclair Scientific performs logs, trig and arithmetic at the touch of a button.

FEATURES OF THE SINCLAIR SCIENTIFIC

Functions summary Four arithmetic functions: (+, -, ×, ÷). Sin and Arcsin, Cos and Arccos, Tan and Arctan, Automatic squaring, Automatic doubling, Log10 and Antilog10, giving quick access to xy (including square and other roots). Scientific notation. Display shows 5-digit mantissa and 2-digit exponent, both signable. 200 decade range. 9,9999 x 10⁹⁹. Post-fixed operators. Post-fixed operators (reverse Polish notation): allow chain calculations of unlimited length. *Upper and lower case* operation. Basic arithmetic keys each have two extra functions. Pocket-sized. 4½" x 2" x ½". Weight: 4oz. Trim-fit plastic carrying case.

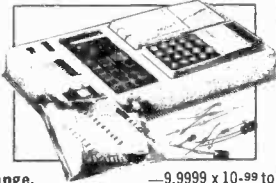

—9,9999 x 10⁻⁹⁹ to 9,9999 x 10⁹⁹.

LONDON 481 Oxford Street, W1. 01-493 8641
10 Tottenham Court Road, W1. 01-637 2232
33 Tottenham Court Road, W1. 01-636 2605
42 Tottenham Court Road, W1. 01-636 0845
257 Tottenham Court Road, W1. 01-580 0670
3 Lisle Street, WC2. 01-437 8204
118 Edgware Road, W2. 01-723 9789
153 Edgware Road, W2. 01-723 6211
311 Edgware Road, W2. 01-262 0387
346 Edgware Road, W2. 01-723 4453
382 Edgware Road, W2. 01-723 4194
109 Fleet Street, EC4. 01-353 5812
152 Fleet Street, EC4. 01-353 2833
BIRMINGHAM 116 Corporation St. 236 3503
BRENT CROSS Unit D19 Brent Cross Shopping Centre, Now open
BRISTOL 16-18 20 Penn Street. 20421
CHATHAM The Pentagon Centre. 407104

CROYDON 1046 Whitgift Centre. 681 3027
COLCHESTER Unit AS Lion Walk Shopping Centre, opening FEBRUARY
DARTFORD The Arndale Centre. 32 73481
KINGSTON 38/40 Eden Street. 546 1271
LEICESTER 45 Market Place. 537678
LEWISHAM 29 Riverside, The Centre. 318 2297
NORTHAMPTON 78 Abington St. 35753
NOTTINGHAM 5-7 Lower Parliament St. 48987
OXFORD 16 Westgate Centre. 722870
READING 6 Friars Walk, Friar St. 595459
RICHMOND 32 Hill Street. 948 1441
ROWFORD 86 South Street. 20218
SOUTHEND 205/206 Churchill West. 612241
SLOUGH 65 Queensmere Centre. 7524401
SWINDON 12 Brunel Plaza
TUNBRIDGE WELLS 53/57 Camden Rd. 23242
WOLVERHAMPTON 30 Wulfrum Way. 23384



To LASKYS CUSTOMER SERVICES DIVISION (Dept. K)
Audiotronic House, The Hyde, London NW9 6JJ. Tel: 01-200 1321

Please send me Sinclair Scientific Calculator Kits at £6.50 plus 50p p&p

NAME

ADDRESS

SIGNATURE

TOTAL PURCHASE PRICE (inc. p/p & Ins.)

Please send me FREE Hi-Fi catalogue price list

I enclose cheque postal order money order

I wish to pay by Barclaycard/Access/Diners Club and my number is

Registered in England No. 347947 at Lower Grosvenor Place, London SW1 0EX

Random FLASHER UNIT




Wired ready for use
Complete with three
100 watt coloured lamps
that flash independently
at random
£18.95

TWIN BANK 6 LIGHT UNIT



(less lamps) LENGTH 14½ inches
B.C. Fitting **£9.55**
E.S. Fitting **£10.35**

Sound to Light MASTER UNIT

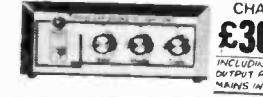

600 WATTS PER CHANNEL
£30.95
INCLUDING CHANNEL OUTPUT PLUGS AND MAINS INPUT SOCKET.

TYPE A SPOT



(less lamp)
B.C. Fitting **£1.95** EACH
E.S. Fitting **£2.12** EACH


TYPE B 3 BANK UNIT



(Less Lamps)
B.C. Fitting **£6.90** EACH
E.S. Fitting **£7.26** EACH

100 WATT SPOT LAMPS
RED, YELLOW, GREEN, BLUE, CLEAR
£1.18 each
Maximum 3 lamps
B.C. or E.S. Fitting

TWIN BANK 12 LIGHT UNIT

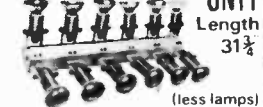

(less lamps) Length 31½
B.C. Fitting **£15.60** EACH
E.S. Fitting **£17.00** EACH

ALL PRICES INCLUDE V.A.T. AND POST & PACKING (These prices apply to the United Kingdom only)

Send 20p for illustrated leaflet & price list

ALBEN ENGINEERING CO. LTD.
DEPT. PE THE CRESCENT, WORSTHORNE,
BURNLEY, LANCs. Tel Burnley 20940

12in LONG PERSISTENCE CRT. Full spec. Price £6.50 to include V.A.T. and Carriage.
MAKE YOUR SINGLE BEAM SCOPE INTO A DOUBLE WITH OUR NEW LOW PRICED SOLID STATE SWITCH. 2Hz to 8MHz. Hook up to a 9 volt battery and connect to your scope and have two traces for ONLY £8.25, P. & P. 25p. (Not cased, not calibrated.)
WIDE RANGE WOBBLATOR. 5MHz to 150MHz up to 15MHz sweep width. Only 3 controls, preset RF level, sweep width and frequency. Ideal for 10-7 or TV IF alignment, filters, receivers. Can be used with any general purpose scope. Full instructions supplied. Connect 6-9V a.c. and use within minutes of receiving. All this for ONLY £8.75, P. & P. 35p. (Not cased, not calibrated.)
20Hz to 200kHz WB, SINE and SQUARE GENERATOR. Four ranges. Independent amplitude controls, thermostat stabilised. Ready to use. 9V supply required. £8.85 each. SINE WAVE only £8.85 each. P. & P. 35p. (Not cased, not calibrated.)
GRATICULES 12cm x 14cm high quality plastic 15p each. P. & P. 8p.

*Large quantity of good quality components—NO PASSING TRADE—so we offer 3lb of **ELECTRONIC GOODIES** for £1.70. Post paid

*METER PACK—3 different meters for £2. P. & P. 55p.
MIN TRANSFORMER. 240V input, 3V 1A output. Brand new 85p each, P. & P. 20p.
P.C.B. PACKS. S & D. Quantity 2 sq. ft.—no tiny pieces. 50p, P. & P. 37p.
*CAPACITOR PACK—50 brand new components. only 50p, P. & P. 37p
SOME OSCILLOSCOPES ALWAYS AVAILABLE. S.A.E. stating specification and price range.

*TRIMMER PACK. 2 twin 50/200pF ceramic, 2 twin 10/80pF ceramic, 2 min strip with 4 preset 5/20pF on each, 3 air spaced preset 30/100pF on ceramic base. ALL BRAND NEW. 25p the lot, P. & P. 15p.
*PHOTOCELL equ. OCP71, 13p each.
*MULLARD OCP70, 10p each.
LISTS OF EQUIPMENT, etc., now available. S.A.E. please. Callers always welcome.

*MODERN TELEPHONES. Type 706: two tone grey or black, £3.75 each. Style similar to Type 746: grey, or black, £3 each. As above but discoloured, grey only, £2 each. P. & P. all types 45p each.
*HANDSETS. Complete with 2 inserts and lead. £1.25 each, P. & P. 37p.
*DIALS. ONLY 50p each, P. & P. 25p.
*HIGH VALUE—PRINTED BOARD PACK. Hundreds of components, transistors, etc.—No 2 boards the same. No short leaded transistor computer boards. £1.75, post paid.


*CRYSTALS. 4-43MHz. Brand new. £1.25 each. P. & P. 15p.
RESETTABLE COUNTERS—4 digit by Sodeco/Stonebridge. 1,000 ohm coil. £2 each. P. & P. 35p.
*BEEHIVE TRIMMER 3/30 pF. Brand new. Qty 1-9 13p each, P. & P. 15p; 10-99 10p each, P. & P. 25p; 100-999 7p each, P. & P. free.
HE CRYSTAL DRIVE UNIT. 19in rack mount. Standard 240V input with superb crystal oven by Labgear (no crystals) £5 each Carr. £2
*1,000pF FEED THRU CAPACITORS. Only sold in packs of 10, 30p, P. & P. 15p.

VAT NOT INCLUDED IN PRICE
Goods marked * 25% VAT, otherwise 8%
OPEN 9 a.m. to 5.30 p.m. ANY DAY

CHILTHEAD LTD
7/9 ARTHUR ROAD, READING, BERKS.
(rear Tech. College) Tel. Reading 582605

ELECTRONIC DIGITAL CLOCK

with alarm and snooze features

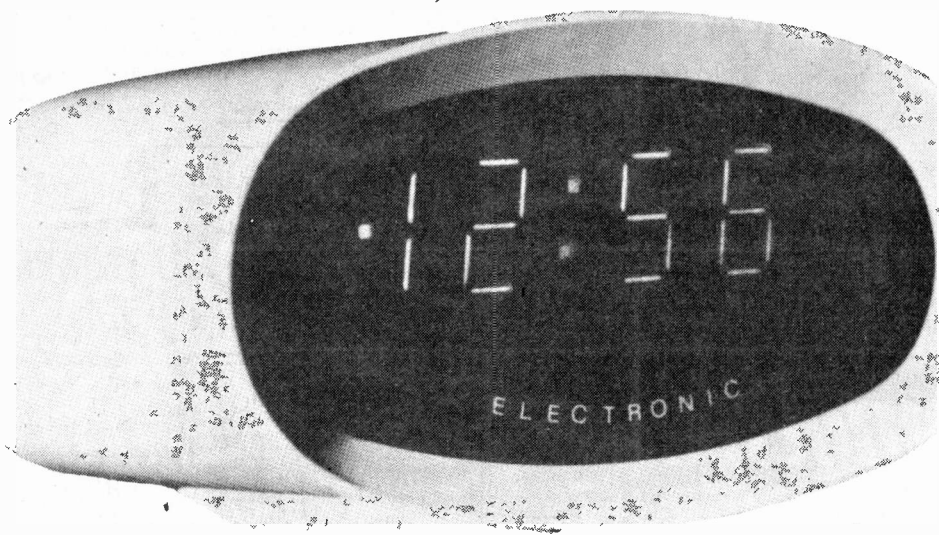

Features:

- 0.7 INCH HIGH DIGITS
- VARIABLE INTENSITY
- 24-HOUR ALARM
- 5-MINUTE REPEATING, SNOOZE ALARM
- ALARM SET INDICATOR
- SNOOZE INDICATOR

Size: 130mm x 90mm x 95mm
Weight: 10oz

- PULSING SECOND INDICATOR
- POWER INTERRUPT INDICATOR
- ALARM CANCEL FEATURES—TILT OPERATION
- ALARM TONE OUTPUT
- A.M.—P.M. INDICATOR

Power supply: 110V a.c. $\pm 10\%$ 60Hz
230V a.c. $\pm 10\%$ 50Hz

Manufactured to high standards by a major American electronics corporation, this superbly styled solid-state timepiece is made available to all readers fully guaranteed.

Mail order customers: Please enclose 55p for postage and packing.

SPECIAL OFFER

£12.48

Plus 99p VAT

Free trial in your home—Try out the clock in your home. If digital time is not for you return it in original condition within 10 days and we'll refund your money without question.

TM TIME MICROELECTRONICS

33 Wateridge Road, Basingstoke, Hants
RG21 2RA. Tel. (0256) 66961

Please send electronic clocks as illustrated. I enclose cheque postal order money order

Name

Address

Signature



Rising to the occasion at High Fidelity 1976

Room 1006 at the Heathrow International Hotel gives London another opportunity to see the New BD3 in action, alongside the rest of the Connoisseur range.

Connoisseur

BD3 transcription unit

Down to the last detail the Connoisseur BD3 transcription turntable is a must for the serious audiophile, all present day requirements being met with an ease only the finest products can maintain, with accuracy as the keynote. The BD3 incorporates a studio-style rising turntable principle giving accurate cueing; the turntable rising to the pickup height on quick start, with run-up time being almost immediate - a fraction of a second. Plus a pickup arm without drift. Other interesting features include the electronically controlled variable speed DC motor. The power source which converts mains to a stabilised 9v. DC supply is external, and consequently there is no hum field. Three speeds: 33, 45 and 78 rpm, all with variable control. The belt driven 11 1/2 diameter turntable with a neon illuminated stroboscopic disc, complete on wood plinth and a hinged acrylic dust cover.

The BD3 arm is an ideal companion to the turntable, being constructed from lightweight aluminium tubing, incorporating unipivot with a unique method of magnetic stabilisation for the horizontal bearings, and knife edges for the vertical, adjustable magnetic bias and an inter-changeable lightweight head shell which will accept the majority of cartridges, and enabling tracking weights in the region of 0.6 gms. to be used.

For further details of the BD3 or the BD1 Kit, SAU2 arm, the BD2 integrated assembly and SCU1 ceramic cartridge, please contact your dealer or send a stamp for brochure.

Manufactured by:-

A. R. Sugden & Co. (Engineers) Ltd.,
Atlas Mill Road, Brighouse,
Yorkshire, HD6 1ES.

Telephone: Brighouse (04847) 2142.

Telegrams & Cables: Connoisseur, Brighouse.

B. BAMBER ELECTRONICS

Dept PE, 5 STATION ROAD, LITTLEPORT, CAMBS., CB6 1QE
Telephone: ELY (0353) 860185 (2 lines) Tuesday to Saturday

PLEASE ADD 8% VAT UNLESS OTHERWISE STATED

BARGAIN OFFER
MIXED COMPONENT PACKS, containing resistors, capacitors, switches, pots, etc. All new (random sample bag revealed approx. 700 items), £2 per pack, while stocks last.
TUNED COILS, 2 section coils, around 1MHz, with a black smart tuning knob, which moves an internal core to vary the inductance, many uses, easily rewound, 3 for 50p.
TWIN I.F. CANS, approx. 1in x 1/2in x 1in high, around 3.5-5MHz, 2 separate transformers in 1 can, internally screened, 5 for 50p + 25% VAT.
SMALL MAINS SUPPRESSORS (small chokes, ideal for radio, Hi-Fi inputs, etc.) approx. 1/2in x 1 1/2in, 3 for 50p.
PERISPEX TUNER PANELS (for FM Band 2 tuners) marked 88-108 MHz and Channels 0-70, clear numbers, rest blacked out, smart modern appearance, size approx. 3 1/2in x 1 1/2in, 2 for 35p.
Multiturn Pots, 10 turn, 1/2in spindle (ex-equip), following values available, 2kohm, 5kohm, 400kohm, £1 each.
Lead suppressors (10kohm) for mobile plug leads, 4 for 50p.
1mA Meters, 2 in square, plastic fronts (these have a paper scale stuck over the original marked 0-1mA which is easily peeled off and an internal 10K resistor which is easily removed), £1-75 each or 2 for £3.
R/S Midget 3 pole 4 way, rotary switches, 40p each.

SPECIAL OFFER
Miniature 500hm Coax, high quality, PTFE insulation and blue PTFE cover, solid silver plated inner, and silver plated braid, approx 3m, overall diameter (ideal for unit wiring of RF stages up to 23cm), 4 metres for 80p.

TRANSISTOR HEATSINKS, to take 2 x TO18 transistors, screw in clamps, block size 1 x 1 1/2in, with holes for mounting, 3 for 50p.

HIGH QUALITY SPEAKERS, 8 1/2in x 6in elliptical, only 2in deep, inverse magnet, 4ohms, rated up to 10W, £1-50 each, or 2 for £2-75 (qty. discount available), + 25% VAT.

TV PLUGS AND SOCKETS
TV Plug (metal type), 5 for 80p.
TV Sockets (metal type), 4 for 80p.
TV Line Connectors (back-to-back sockets), 5 for 50p. Please add 25% VAT.

2-9pF, 10mm circular ceramic trimmers (for VHF/UHF work) 3 pin mounting, 5 for 50p.
TO3 transistor insulator sets, 10 for 80p.
PC Board Withdrawal handles, mixed coils, 8 for 50p.
Solder, 20 SWG, 60/40 alloy, approx 8 yds for 25p.
MINIATURE 2 PIN PLUGS AND SOCKETS (fit into 1/2in hole, pins enclosed, with covers for chassis mounting, or can be used for in-line connectors). Bargain pack of 3 plugs + 3 sockets + covers, 50p.
PROGRAMMERS (magnetic devices). Contain 9 microswitches (suitable for mains operation) with 9 rotating cams, all individually adjustable, ideal for switching disco lights, displays, etc., or industrial machine programming. (Need slow motion motor to drive cams, not supplied) 9 switch version £1-50, or 15 switch version £2.
HEAVY DUTY HEATSINK BLOCKS, undrilled, base area 2 1/2in x 2 1/2in, with 6 fins, total height 2 1/2in 50p each.
SV RELAYS, Continental type, 2 pole change over, 35p.
RUBBER MAGNETS 1/2in square, with mounting hole, 20 for 50p.
SPERRY 7-SEGMENT P.O.D. DISPLAYS, digit height 0.3in red, with decimal points, 150V to 200V (nominal 180V) operation. These are high-volt industrial type and therefore brighter than normal displays. All brand new. AT THE BARGAIN PRICE OF 50p PER DIGIT. TYPE 332 (two digits in one mount) £1 each, TYPE 333 (three digits in one mount) £1-50. (Sorry, no single digit available.) Dats supplied.

BSX20 (VHF Osc/Mult), 3 for 50p.
BC108 (metal can), 4 for 50p.
PBC 108 (plastic BC108), 5 for 50p.
OC200 Transistors, 6 for 50p.
BFY51 Transistors, 4 for 80p.
BCY72 Transistors, 4 for 80p.
PNP audio type TO5 Transistors, 12 for 25p.
BF152 (UHF amp/mixer), 3 for 50p.
BA121 Varicap Diodes, 4 for 50p.

1 1/2in polythene chassis mounting fuseholders, 6 for 30p.
Mullard Tubular ceramic trimmers, 1-18pF, 6 for 50p.
I.C. is some coded, 14 DIL type, untested, mixed, 20 for 25p.

PLEASE ADD 8% VAT UNLESS OTHERWISE STATED

PLUGS AND SOCKETS
BNC Socket (Single-hole mounting type) Ex-equipment (special offer) 3 for 50p.
BNC Plugs (ex-equipment), 5 for £1.
N-Type Plugs 50 ohm, 80p each, 3 for £1-50.
N-Type Sockets (4-hole chassis mounting, 50 ohm (a small coax lead type), 80p each.
PL250 Plugs (PTFE), brand new, packed with reducers, 80p or 5 for £3.
SO239 Sockets (PTFE), brand new (4-hole fixing type), 80p each or 5 for £2-25.
25-way ISEP Plugs and Sockets, 40p set (1 plug + 1 socket).
Plugs and sockets sold separately at 25p each.
Bulgin Round Free Sckt. 3 pin, for mains input on test equipment, etc., 25p each.
Bulgin Flat 2-pin Flex Connectors non-reversible 40p each.
Mobile Converters, 24V DC input 13-8V at approx 3-4A DC output, fully stabilised, £3-50 each (ideal for running 12V car radio from 24V lorry battery).
Pkts. of 25A Nuts (the self-locking ones with the nylon insert) 100 for 50p.

We now stock Spiratux Tools for the electronic enthusiast. Screwdrivers, Nut Spanners, BA and Metric sizes, pop rivet guns, etc. S.A.E. for list.
I.F. Cans, 1/2in square, suitable for rewind, 6 for 50p + 25% VAT.
Miniature earphones with min. jack plug, 2 for 50p + 25% VAT.

Duobiler Electrolytics, 500uF, 450V, 2 for 80p.
Duobiler Electrolytics, 100uF, 275V, 2 for 80p.
Plessey Electrolytics, 470uF, 63V, 3 for 80p.
TCC Electrolytics, 1000uF, 30V, 3 for 80p.
Plessey Electrolytics, 1000uF, 180V, 40p each (3 for £1).
Duobiler Electrolytics, 5000uF, 35V, 50p each.
Duobiler Electrolytics, 5000uF, 50V, 80p each.
Duobiler Electrolytics, 5000uF, 70V, 85p each.
ITT Electrolytics, 6800uF, 25V, high grade, screw terminals, with mounting clips, 80p each.
Plessey Electrolytics, 10,000uF at 65V, 75p each.
Plessey Cathodray Capacitors, 0-0.4uF at 12-5kV DC, Screw terminals, £1-50 each.

PLEASE ADD 25% VAT TO ALL CAPACITORS
A LARGE RANGE OF CAPACITORS AVAILABLE AT BARGAIN PRICES. S.A.E. FOR LIST.

SPECIAL OFFER!
MAINS TRANSFORMER, TYPE 14/4, 14V at 4A, £2-50.
Diecast Boxes (approx size in inches)
4-3 x 2-3 x 1-2 85p
4-8 x 2-3 x 1-5 75p
4-8 x 3-8 x 1 85p
4-8 x 3-8 x 2 £1-00
4-8 x 4-8 x 2 £1-45
4-8 x 3-8 x 3 £1-55
6-8 x 4-8 x 2 £2-25
8-8 x 5-8 x 2 £1-85
10-6 x 6-8 x 2 £2-25


Please add 8% VAT

WELER SOLDERING IRONS
EXPERT. Built-in-applight illuminates work. Pistol grip with fingertip trigger. High efficiency copper soldering tip.
EXPERT SOLDER GUN. £8-80 + VAT (54p)
EXPERT SOLDER GUN KIT (apart bits case, etc.), £9-80 + VAT (78p)
SPARE BITS, PAIR, 25p + VAT (2p)
MARKSMAN SOLDERING IRONS
SP150 15W £2-85 + VAT (20p)
SP250 25W £2-53 + VAT (20p)
SP25DK 25W + bits, etc, kit £3-12 + VAT (25p)
BENCH STAND with spring for Marksmen Irons, £1-80 + VAT (14p)
SPARE BITS
MT8 for 15W, 42p + VAT (3p).
MT4 for 25W, 35p + VAT (3p).
TCPI TEMPERATURE CONTROLLED IRON. Temperature controlled iron & PSU, £18-43 + VAT (£1-47).
SPARE TIPS
Type CC single flat. Type K double flat fine tip. 80p each + VAT (8p).
ALL SPARES AVAILABLE

MULTICORE SOLDER
Size 5 Savbit 18 s.w.g. in alloy dispenser, 32p + VAT (3p).
Size 12 SAVBIT 18s.w.g. on plastic reel £1-80 + VAT (15p).

MINIATURE PLIERS High quality "Crescent" made in USA. £4-35 + VAT (36p).
BIDE CUTTERS, high quality "Crescent", made in USA. £3-45 + VAT (44p).

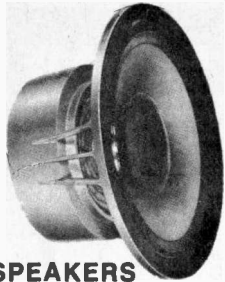Terms of Business: CASH WITH ORDER. MINIMUM ORDER £1. ALL PRICES INCLUDE POST & PACKING (UK ONLY). SAE with ALL ENQUIRIES Please. PLEASE ADD VAT AS SHOWN. ALL GOODS IN STOCK DESPATCHED BY RETURN.



WILMSLOW AUDIO

THE Firm for speakers!

SPEAKERS

Baker Group 25, 3, 8 or 15 ohm	£8-84
Baker Group 35, 3, 8 or 15 ohm	£10-25
Baker Group 50/12 8 or 15 ohm	£14-00
Baker Group 50/15 8 or 15 ohm	£18-82
Baker Deluxe 124 8 or 15 ohm	£13-75
Baker Major 3, 8 or 15 ohm	£11-87
Baker Superb 8 or 15 ohm	£18-12
Baker Regent 12in 8 or 15 ohm	£10-00
Baker Auditorium 12in 8 or 15 ohm	£18-25
Baker Auditorium 15in 8 or 15 ohm	£21-56
Castle 8RS/DD 4 or 8 ohm	£9-95
Celestion G12M 8 or 15 ohm	£12-95
Celestion G12H 8 or 15 ohm	£15-95
Celestion G12/50 8 or 15 ohm	£16-50
Celestion G12/50TC 8 or 15 ohm	£18-00
Celestion G12/50 2236 s/cone	£16-50
Celestion G12/50 2239 s/cone, alum. dome	£17-00
Celestion G15C 8 or 15 ohm	£26-95
Celestion G18C 8 or 15 ohm	£34-50
Celestion HF1300 8 or 15 ohm	£7-75
Celestion HF2000 8 ohm	£9-50
Celestion MH1000 8 or 15 ohm	£13-50
Celestion C03K	£4-95
Decca London ribbon horn	£32-00
Decca London CO/1000/8 crossover	£7-50
Decca DK30 ribbon horn	£19-06
Decca CO/1/8 crossover (DK30)	£5-00
EMI 150 13 x 8in d/cone 8 ohm	£2-84
EMI 13 x 8in 20W bass 8 ohm	£9-00
EMI 14 x 9in bass 8 ohms, 14A770	£13-25
EMI 8 x 5in, 10W, d/cone, roll surr.	£3-95
EMI 8 1/2in d/cone, roll surr., 8 ohm	£4-37
EMI 8in roll surr. bass	£8-37
EMI 5in mid range	£3-50
Elac 59RM109 (15 ohm), 59RM114 (8 ohm)	£3-75
Elac 8 1/2in d/cone, roll surr., 8 ohm	£4-25
Elac 10in 10RM239, 8 ohm	£4-25
Eagle Crossover 3000Hz 3, 8 or 15 ohm	£1-75
Eagle FR4	£8-12
Eagle FR85	£9-82
Eagle FR8	£12-31
Eagle FR10	£15-82
Eagle HT15	£4-40
Eagle HT21	£8-81
Eagle MHT10	£4-44
Eagle FF28 Multicell, horn	£9-00
Fane Pop 15, 8 or 16 ohm	£5-25
Fane Pop 25T, 8 or 16 ohm	£7-50
Fane Pop 33T, 8 or 16 ohm	£9-25
Fane Pop 50, 8 or 16 ohm	£12-50
Fane Pop 55, 8 or 16 ohm	£15-50
Fane Pop 60, 8 or 16 ohm	£17-95
Fane Pop 70, 8 or 16 ohm	£18-75
Fane Pop 100, 8 or 16 ohm	£27-95
Fane Crescendo 12A, 8 or 16 ohm	£37-85
Fane Crescendo 12BL, 8 or 16 ohm	£36-95
Fane Crescendo 15/100A, 8 or 16 ohm	£49-95
Fane Crescendo 15/125, 8 or 16 ohm	£59-95

SPEAKERS

Fane Crescendo 18, 8 or 16 ohm	£67-95
Fane 910 Mk II horn	£15-75
Fane 920 Mk II horn	£36-95
Fane HPX1 crossover 200W	£2-50
Fane 13 x 8in, 15W dual cone	£5-50
Fane 801T 8in d/c, roll surr.	£9-95
Gauss 12in 200W	£84-00
Gauss 15in 200W	£96-00
Gauss 18in 200W	£129-00
Goodmans Axent 100	£8-44
Goodmans Axent 200 8 ohm	£14-95
Goodmans Axent 402 8 or 15 ohm	£22-00
Goodmans Twinaxiom 8, 8 or 15 ohm	£19-55
Goodmans Twinaxiom 10, 8 or 15 ohm	£18-00
Goodmans 8P 8 or 15 ohm	£5-95
Goodmans 10P 8 or 15 ohm	£8-25
Goodmans 12P 8 or 15 ohm	£14-95
Goodmans 12PG 8 or 15 ohm	£16-50
Goodmans 12PD 8 or 15 ohm	£16-95
Goodmans 12AX 8 or 15 ohm	£39-00
Goodmans 15AX 8 or 15 ohm	£45-00
Goodmans 15P 8 or 15 ohm	£22-50
Goodmans 18P 8 or 15 ohm	£39-00
Goodmans Hifax 750P	£18-00
Goodmans 5in midrange 8 ohm	£4-50
Jordan Watts Module, 4, 8 or 15 ohm	£17-08
Kef T27	£5-75
Kef T15	£8-94
Kef B110	£7-50
Kef B200	£8-70
Kef B139	£16-75
Kef DN8	£2-31
Kef DN12	£5-99
Kef DN13 SP1015 or SP1017	£4-50
Lowther PM8	£34-00
Lowther PM8 Mk I	£36-50
Lowther PM7	£54-00
Peerless KO10DT 4 or 8 ohm	£8-08
Peerless DT10HFC 8 ohm	£9-18
Peerless KO40MRF 8 ohm	£10-31
Peerless MT225HFC 8 ohm	£3-12
Richard Allan CA12 12in bass	£22-00
Richard Allan HP8B	£13-25
Richard Allan LP8B	£9-25
Richard Allan DT20	£8-75
Richard Allan CN8280	£15-00
Richard Allan CN820	£3-50
Richard Allan Super Disco 60W 12in	£16-95
Richard Allen CG15 15in bass	£27-95
Richard Allen Super Disco 12in 60 watt	£15-95
Richard Allen Super Disco 10in 50 watt	£9-95
Richard Allen Super Disco 8in 50 watt	£11-95
Radford BD25	£18-44
Radford MD9	£11-50
Radford MD8	£11-50
Radford TD3	£8-08
Radford Cross Over Network	£14-25

STC 4001G	£8-56
Tannoy 10in HPD	£75-00
Tannoy 12in HPD	£81-95
Tannoy 15in HPD	£97-95
Wharfedale Super 10 RS/DD 8 ohm	£15-00

SPEAKER KITS

Baker Major Module 3, 8 or 15 ohm	each	£14-75
Fane Mode One Mk II 15W	each	£11-50
Goodmans DIN 20 4 or 8 ohm	each	£14-75
Goodmans Mezzo Twin kit	pair	£47-19
Heime XLK 30	pair	£19-00
Heime XLK 35	pair	£24-00
Heime XLK 40	pair	£35-00
Heime XLK 50	pair	£56-00
Kefkit 1	pair	£49-00
Kefkit III	each	£43-75
Peerless 20-2	each	£17-44
Peerless 30-28	each	£24-38
Peerless 20-3	each	£26-56
Peerless 50-4	each	£40-50
Peerless 3-15	each	£17-19
Peerless 1080	pair	£58-00
Peerless 1070	each	£48-00
Peerless 1120	each	£50-00
Richard Allan Twin assembly	each	£14-95
Richard Allan Triple 8	each	£22-50
Richard Allan Triple 12	each	£27-95
Richard Allan Super Triple	each	£32-50
Richard Allan RA8 Kit	pair	£42-00
Richard Allan RA82 Kit	pair	£96-00
Richard Allan RA82L Kit	pair	£73-00
Wharfedale Linton II kit	pair	£23-12
Wharfedale Glendaie 3XP kit	pair	£53-00
Wharfedale Dovedale III kit	pair	£86-00

HI-FI ON DEMONSTRATION In our showrooms:

Akal, Armstrong, Bowers & Wilkins, Castle, Celestion, Dual, Goodmans, Kef, Leak, Pioneer, Radford, Richard Allan, Rotel, Tandberg, Trio, Videotone, Wharfedale, etc.—ask for our Hi-Fi discount price list.

ALL PRICES INCLUDE VAT
(PRICES CORRECT AT 28.2.78)
Send stamp for free 32 page booklet "Choosing a Speaker"

ALL UNITS GUARANTEED NEW AND PERFECT
Carriage and Insurance: Speakers 50p each (12in and up 75p each); Kite 80p each (£1.60 per pair); Tweeters and Crossovers 30p each.

WILMSLOW AUDIO

Dept HFA

Loudspeakers, mail order and export:
Swan Works, Bank Square, Wilmslow.

Hi-Fi, Radio and TV: Swift of Wilmslow,
5 Swan Street, Wilmslow, Cheshire.

PA, Hi-Fi and Accessories: Wilmslow
Audio, 10 Swan Street, Wilmslow,
Cheshire.

Telephone: Loudspeakers, mail order and
export—Wilmslow 29599; Hi-Fi, Radio,
etc.—Wilmslow 28213.

Complete kits in stock for Radford Studio 90, Radford Monitor 180, Radford Studio 270, Radford Studio 360, Hi-Fi Answers Monitor (Rogers), Hi-Fi News No Compromise (Frisby), Wireless World Transmission Line (Bailey), Practical Hi-Fi and Audio Monitor (Giles), Practical Hi-Fi and Audio Triangle (Giles), Popular Hi-Fi (Colloms), etc.


Construction leaflets for Radford, Kef, Jordan Watts, Tannoy, Hi-Fi Answers Monitor, free on request.

P.A. amplifiers, microphones, etc., by Shure, Linear, Eagle, Beyer, AKG, etc.

FREE with orders over £10—"Hi-Fi Loudspeaker Enclosures" book.

ENGINEERS

FREE

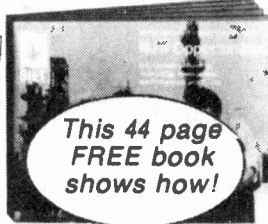

This 44 page
FREE book
shows how!

YOURSELF FOR A BETTER JOB WITH MORE PAY!

Do you want promotion, a better job, higher pay? "New opportunities" shows you how to get them through a low-cost, Home Study Course. There are no books to buy and you can pay as you learn.

This easy to follow GUIDE TO SUCCESS should be read by every ambitious engineer. Send for this helpful 44 page free book NOW! No obligation, nobody will call on you. It could be the best thing you ever did.

CHOOSE A BRAND NEW FUTURE HERE

CUT OUT THIS COUPON

Tick or state subject of interest.
Post to address below.

- | | | |
|---|--|--------------------------|
| <input type="checkbox"/> ELECTRICAL & ELECTRONICS | <input type="checkbox"/> Air Registration Board Certs. | <input type="checkbox"/> |
| <input type="checkbox"/> Practical Radio & Electronics (with kit) | <input type="checkbox"/> MAA/IMI Dip. | <input type="checkbox"/> |
| <input type="checkbox"/> Electronic Engineering Certificate | <input type="checkbox"/> CONSTRUCTIONAL Heating Ventilating & Air Conditioning | <input type="checkbox"/> |
| <input type="checkbox"/> General Elect. Eng. Certificate | <input type="checkbox"/> Architectural Draughtsmanship & Design | <input type="checkbox"/> |
| <input type="checkbox"/> C. & G. Elect. Installations | <input type="checkbox"/> L.I.O.B. | <input type="checkbox"/> |
| <input type="checkbox"/> Elect. Install. & Work | <input type="checkbox"/> Carpentry & Joinery | <input type="checkbox"/> |
| <input type="checkbox"/> C. & G. Elect. Technicians | <input type="checkbox"/> Plumbing Technology | <input type="checkbox"/> |
| <input type="checkbox"/> | <input type="checkbox"/> General Building | <input type="checkbox"/> |
| <input type="checkbox"/> | <input type="checkbox"/> Painting & Decorating | <input type="checkbox"/> |
| <input type="checkbox"/> | <input type="checkbox"/> MECHANICAL | <input type="checkbox"/> |
| <input type="checkbox"/> | <input type="checkbox"/> A.M.S.E. (Mech.) | <input type="checkbox"/> |
| <input type="checkbox"/> | <input type="checkbox"/> General Mech. Eng. | <input type="checkbox"/> |
| <input type="checkbox"/> | <input type="checkbox"/> Inst. Engineers & Technicians | <input type="checkbox"/> |
| <input type="checkbox"/> | <input type="checkbox"/> Maintenance Engineering | <input type="checkbox"/> |
| <input type="checkbox"/> | <input type="checkbox"/> Welding | <input type="checkbox"/> |
| <input type="checkbox"/> | <input type="checkbox"/> MANAGEMENT & PRODUCTION | <input type="checkbox"/> |
| <input type="checkbox"/> | <input type="checkbox"/> Computer Programming | <input type="checkbox"/> |
| <input type="checkbox"/> | <input type="checkbox"/> Inst. of Cost & Managements Accts. | <input type="checkbox"/> |
| <input type="checkbox"/> | <input type="checkbox"/> DRAUGHTSMANSHIP & DESIGN | <input type="checkbox"/> |
| <input type="checkbox"/> | <input type="checkbox"/> General Draughtsmanship | <input type="checkbox"/> |
| <input type="checkbox"/> | <input type="checkbox"/> A.M.I.E.D. | <input type="checkbox"/> |
| <input type="checkbox"/> | <input type="checkbox"/> Electrical Draughtsmanship | <input type="checkbox"/> |

POST NOW

G.C.E.

—58 'O' & 'A' Level Subjects
—over 10,000 Group Passes!

Aldermaston College

Dept. TPE 17, Reading RG7 4PF

also at our London Advisory Office, 4 Fore Street Avenue, Moorgate, London EC2Y 5EJ. Tel. 01-628 2721.

NAME (Block Capitals)

ADDRESS

Postcode


Other subjects of interest Age

Accredited by C.A.C.C. Member of A.B.C.C.

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

REVERSIBLE ASSEMBLY FRAME FOR PRINTED CIRCUITS

Simply assemble, turn over and solder

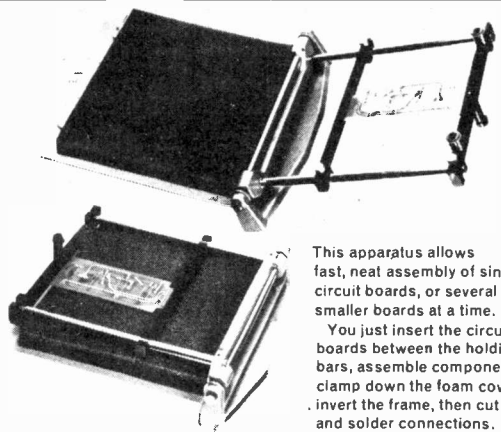

- ★ Takes one or more circuit boards
- ★ Fully adjustable foam cover
- ★ Also ideal for repairs and retouching

This apparatus allows fast, neat assembly of single circuit boards, or several smaller boards at a time.

You just insert the circuit boards between the holding bars, assemble components, clamp down the foam cover, invert the frame, then cut and solder connections. Our special magnetic locking system ensures that components stay firmly in place.

Indispensable for any circuitry laboratory, repair shop, or production line use. Available in two sizes:

Max. JA 500 - 220 x 170 mm.
area JA 1000 - 370 x 170 mm.

For full details, please contact:
Special Products Distributors Ltd.,
81 Piccadilly, London W1V 0HL.
Telephone: 01-629 9556.

CRESCENT RADIO LTD.

11-15 & 17 MAYES ROAD, LONDON N22 6TL
(also) 13 SOUTH MALL, EDMONTON, N.9

MAIL ORDER DEPT.
1 ST. MICHAELS TERRACE, WOOD GREEN, LONDON N22 4JZ
Phone: 888-4474


3 KILOWATTS PSYCHEDELIC LIGHT CONTROL UNIT
Three Channel: Bass, Middle, Treble. Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier, and connect three 250V up to 1000W lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed.)
£18.50 plus 75p. P. & P. + 8%.

CABLE LESS SOLDERING IRON WAHL "ISO-TIP"

- ★ Completely portable.
 - ★ Solders up to 150 joints per charge.
 - ★ Recharges in its own stand.
 - ★ Fine tip for all types of soldering.
 - ★ Only 8in long and weighs just 6 ozs.
- OUR PRICE **£9.75** + 8%.
(Spare bits are available)

BARGAIN PROJECT BOX

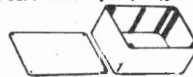A plastic box with moulded extrusion rails for PC or Chassis panels with metal front plate fitted with four screws (all supplied).
An ideal box to give a small project a professional finish.
SIZE (internal) 81mm x 51mm x 28mm.
OUR PRICE **40p.** + 8%.



"CRESCENT" 100 WATT R.M.S. ALL PURPOSE AMPLIFIER U. BUILD. IT

We supply the three modules for you to build this Disco-Group-P.A. amplifier into the cabinet of your choice.

★ **THE POWER AMP MODULE**
170W r.m.s. sq. wave 300W instantaneous peak into 8 ohm (60W into 16 ohm).

★ **THE PRE-AMP MODULE**
Four control pre-amp, Vol. Bass, Treble. Middle controls. Designed to drive most amplifiers using F.E.T. first stage.

★ **THE POWER SUPPLY**
Is supplied complete with the mains transformer. Complete fixing instructions are supplied and no technical knowledge is required to connect the three ready wired modules. A fantastic bargain. **£27.50**, carr. £1.20. Send S.A.E. for further details on this or our ready built amplifiers. + 8%.

12-0-12V 500M/A

240V primary transformer bargain. Approx. size: 60mm x 40mm x 50mm; fixing centres: 75mm. Our price **£1.20.** + 8%.

TELESCOPIC AERIAL

Nine section fully swivelling telescopic aerial with 4BA single bolt fixing or two hole fixing bracket. Fully extended 43". Fully closed 7". Our Price **50p** + P/P + VAT @ 25%.

Low Voltage Stereo Amplifier

8 transistor stereo amplifier with volume, bass, balance and tone controls. Approx. 3W into 8 ohm per channel. Needs a 9/12V d.c. supply and is complete on a 2 1/2in x 7 1/2in P/c board. Ideal for domestic record players, etc.


A BARGAIN AT 45 + 25% VAT

U.K. CARRIAGE 50p UNLESS OTHERWISE STATED
VAT—All prices are excluding VAT. Please add to each item the VAT rate indicated.

RTVC

ELIZABETHAN STEREO TUNER AMPLIFIER

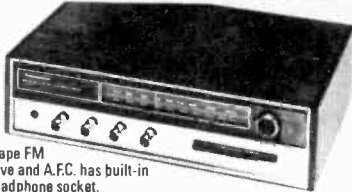This compact Tuner Amplifier gives you full medium wave and V.H.F. coverage and FM stereo. With inputs for your turntable and tape recorder. It has rotary tuning, Volume, Balance, Bass and Treble controls and push button selection switches for Phono/tape FM Stereo, FM mono, Medium wave and A.F.C. has built-in stereo beacon and switched headphone socket.




Technical Specifications 15 transistors, 11 diodes, integrated circuit. Power output 8 watts. Size of tuner amplifier: 4" x 10" x 15 1/2" approx. Finished in selected rosewood veneer with brushed aluminium front panel and matching controls. Output into 15 ohms speakers only.

£29.00
+ p&p £1.50

*STEREO 21

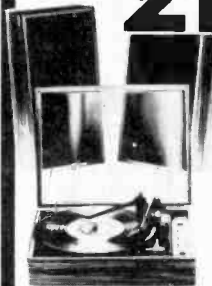INCORPORATING A GARRARD DECK
Garrard 3 speed Deck automatic, manual facilities together with stereo cartridge and cueing device.



Stereo 21, easy to assemble audio system kit. No soldering required. The unit is finished in Sim Teak, and the acrylic top presents an unusually interesting variation on the modern deck plinth.

Includes - 3 speed deck, automatic manual facilities together with stereo cartridge and cueing device.

Two speakers with cabinets.

Amplifier module. Ready built with control panel, speaker leads and full, easy to follow assembly instructions.

Specifications - For the technically minded.

Input sensitivity, 600mV. Aux. input sensitivity 120mV. Power output 2.7 watts per channel. Output impedance 8-15 ohms. Stereo headphone socket with automatic speaker cutout. Provision for auxiliary inputs - radio, tape, etc., and outputs for taping discs.

Overall Dimensions. Speakers approx 12" x 9" x 5". Complete deck and cover in closed position approx. 15 1/2" x 12" x 6".

Extras if required. Optional Diamond Stylus £1.60. Specially selected pair of stereo headphones with individual level controls and padded earpieces to give optimum performance £5.80.

COMPLETE ONLY
£23.20 + p&p £4.00

BSR DECKS WITH PLINTHS AT FANTASTIC REDUCTIONS



MP 60 Type (illustrated) £16.00
Less Cartridge p&p £2.00

C141 (not illustrated) £12.00
Auto, with Cue p&p £1.50
Fitted Stereo Cartridge

All plinths finished in matching Teak veneer.

EASY TO BUILD SPEAKER KITS

These superb simulated teak-finished speaker kits have been specially designed by RTVC for the cost-conscious hi-fi enthusiast who wants top quality speakers but doesn't want to spend the earth. Built to EMI's exacting specification, these new RTVC speaker kits (350 type kit) incorporate 13" x 8" woofer, 3 1/2" tweeter and matching crossover.


Easily put together with just a few basic tools. Specification (each speaker): Impedance 8 ohms. Power handling 15 watts RMS (30 watts peak). Response 20-20,000 Hz. Size 20" x 11" x 9 1/2" approx. Comparable built units (EMI LE3) sold elsewhere for over £45 pair.

£22.00 pair complete Complete with crossover Components and circuit diagram.

THE 'COMPACT' EASY BUILD SPEAKER KIT

A compact bookshelf speaker system giving a high electro acoustic efficiency for the low powered amplifier. The professional finish can be obtained with the minimum of tools, the infinite baffle type enclosures come ready mitered and professionally finished, and fix together with masking tape till glue dries.

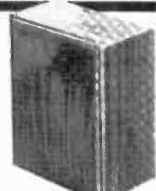The cabinet measures 12" x 9" x 5" deep approx finished in simulated teak, incorporating a quality 7" x 4" elliptical speaker, power handling 4 watts, flux density 30,000 maxwells, impedance 8-15 ohms nominal, voice coil dia 3/8" magnet size 2 1/2" approx.



£6.00 + p&p £1.70
PAIR INCLUSIVE

EMI 350 KIT

£7.25 + £1.20 p & p.

Complete with crossover Components and circuit diagram

System consists of a 13" x 8" approx. woofer with a 3" tweeter, crossover components and circuit diagram. Frequency response: 20 Hz to 20 KHz. Power handling 15 watts RMS into 8 ohms. (Peak 30 watts.)

VISCOUNT IV STEREO AMP

NOW AVAILABLE IN KIT FORM! **30x30**
WATTS RMS

COMPLETE 20x20 SYSTEMS

SYSTEM 1A **£69.00**

The new 20 + 20 watt Stereo Amplifier incorporating the latest silicon transistor solid state circuitry, the RTVC VISCOUNT IV gives you a powerful 20 watts RMS per channel into 8 ohms. Superb teak-finished cabinet, with anodised fascia to harmonise with any decor. Polished trim and knobs.

The VISCOUNT IV has a comprehensive range of controls - volume, bass, treble, balance mono/stereo, mode selector, and scratch filter.

Front panel socket for stereo headphones. And a host of sockets at the rear - for left and right speakers, tape recorder, auxiliary, tuner, disc and microphone.

SPECIFICATION: 20 watts RMS per channel 40 watts peak. Suitable 8-15 ohms speakers. Total distortion at 10 watts better than 0.2%. Six switched inputs: 1. Magnetic PU. - 3 millivolts at 47 K ohms (R.I.A.A.); 2. Crystal/ceramic PU. - 50 millivolts at 50 K ohms (R.I.A.A.); 3, 4, 6. Tape Tuner/Aux. - 140 millivolts at 50 K ohms (flat frequency response); 5. Microphone - 3 millivolts at 50 K ohms (flat frequency response).

CONTROLS: Push button ON/OFF, stereo/mono, scratch filter, 6 position rotary selector. Individual rotary controls for treble, bass, balance and volume. Headphone socket, tape out socket, Aux. mains output. Frequency response: 25 Hz to 25 kHz at full rated output. Signal to noise ratio: better than -50 dB on all inputs. Tone control range: Bass ±15 dB at 50 Hz; Treble ±12 dB at 10 KHz. Power requirements: 250V A.C. mains at 60 watts.

Approx size: 15 1/2" x 3" x 10". **MP60 type deck** with magnetic cartridge, de luxe plinth and cover. **Two Duo Type 11a matched speakers** - Enclosure size approx. 19 1/2" x 10 1/2" x 7 1/2" in simulated teak. Drive unit 13" x 8" with 3" tweeter. 15 watts handling, 30 watts peak.

SYSTEM 2 **£85.00**

Viscount IV amplifier (As System 1a)
MP60 type deck (As System 1a)

Two Duo Type III matched speakers

- Enclosure size approx. 27" x 13"

x 11 1/2". Finished in teak simulate.

Drive units 13" x 8" bass driver, and

two 3" (approx.) tweeters. 20 watts

RMS, 8 ohms frequency range -

20 Hz to 18,000 Hz.

Complete System with these

speakers **£85.00** + £7.60 p & p.

PRICES: SYSTEM 1a

Viscount IV R103

amplifier £27.50 + £1.90 p & p.

2 Duo Type 11a

speakers £30.00 + £6.50 p & p.

MP60 type deck with Mag. cartridge

de luxe plinth

and cover £22.00 + £3.30 p & p.

Total if purchased

separately: £79.50

Available complete for only: **£69.00**

+ £6.50 p & p.

PRICES: SYSTEM 2

Viscount IV R103

amplifier £27.50 + £1.90 p & p

2 Duo Type III

speakers £46.00 + £7.50 p & p.

MP60 type deck with Mag. cartridge

de luxe plinth

and cover £22.00 + £3.30 p & p.

Total if purchased

separately: £95.50

Available complete for only **£85.00**

+ £7.60 p & p.



Scotland and the Orkneys P & P Surcharge
System 1a £1.75 System 2 £3.50

Note: 30x30 kit available only as a separate item.

PUSH BUTTON CAR RADIO KIT- THE TOURIST TT*



NO SOLDERING REQUIRED

NOW BUILD YOUR OWN PUSH BUTTON CAR RADIO +£1.05 p & p.
Easy to assemble construction kit comprising fully completed and tested printed circuit board on which no soldering is required. All connections are simple push fit type making for easy assembly. Fine tuning push button mechanism is fully built and tested to mate with printed circuit board.

TECHNICAL SPECIFICATION: (1) Output 4 watts RMS output. For 12 volt operation on negative or positive earth. (2) Integrated circuit output stage, pre-built three stage IF Module. Controls volume manual tuning and five push buttons for station selection, illuminated tuning scale covering full, medium and long wave bands. Size chassis 7" wide 2" high and 4 1/2" deep approx.


Speaker including baffle and fixing strip £2.00 +45p p & p. Car Aerial Recommended - fully retractable £1.60+40p p & p.
The Tourist I Kit For the experienced constructor. If you can solder on a printed circuit board you can build this model. Same technical specification as Tourist TT. **Price £8.20+£1.05 p & p.**

SPECIAL OFFER

The Tourist I Kit, same specification as Tourist TT complete with speakers, fixing kit and fully retractable aerial **£10.50** + p & p £1.50

STEREO CASSETTE TAPE DECK KIT*

Kit comprises of ready built cassette tape transport mechanism. Featuring pause control, solenoid assisted auto-stop, 3 digit tape counter, belt-driven balanced fly wheel, DC motor with electronic speed control, ready built and mounted record/replay PC board, and two VU meters, power supply, PC board, mains transformer. Input and output sockets and two level controls. Specification power source 240 AC 50Hz. Output more than 0.5v input mike -65dB. 10KΩ. DIN -47dB. 100KΩ. Track system 2 channel stereo record play-back. Tape speed 4.8CM/SEC. Frequency response 50-12,000Hz signal to noise ratio -42dB. Recording system AC Bias. Erasing system AC erase. Bias frequency 57KHz. Size of mechanism 8" x 5" x 3 1/2" approx. unit easy to mount into your cabinet 3" required to clear base of mechanism approx.

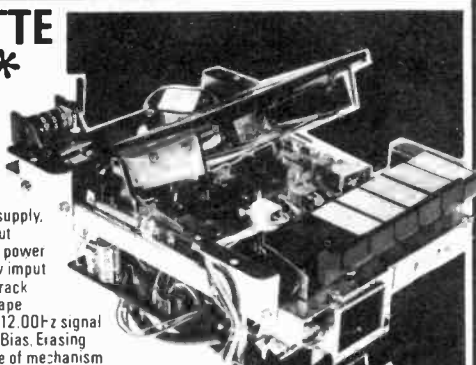


This is an advanced kit not suitable for those without electrical knowledge and those unable to solder.



£32.50
+ p & p £1.50
or send SAE for complete details.

NEW!


*DISCO AMPLIFIER

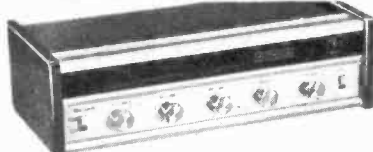

Reliant Mk IV Mono Amplifier, ideal for the small disco or house parties. Output 20 watts RMS into 8 ohms (suitable for 15 ohms). Inputs *4 electrically mixed inputs. *3 individual mixing controls. *Separate bass and treble controls common to all 4 inputs. *Mixer employing F.E.T. (Field Effect Transistors). *Solid State circuitry. *Attractive styling.

INPUT SENSITIVITIES - Input - 1). Crystal mic. guitar or moving coil mic, 2 and 10mV. (Selector switch for desired sensitivity.) - Inputs - 2), 3), 4). Medium output equipment - ceramic cartridge, tuner, tape recorder, organs, etc. - all 250mV sensitivity. AC Mains, 240V operation. Size approx: 12 1/2" x 6" x 3 1/2" **£20.00** +£1.35 p & p.

8 TRACK HOME CARTRIDGE PLAYER

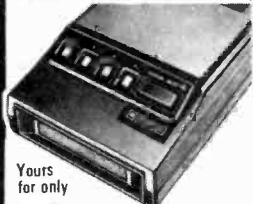

Yours for only


£14.00 +£1.70 p & p.

Elegant self selector push button player for use with your stereo system. Compatible with Viscount IV system, Unisound module and the Stereo 21. Technical specification Mains input, 240V, Output sensitivity 125mV.

SPECIAL OFFER

As above but complete with build yourself Unisound Amplifier Kit (see opposite panel) + 2 'Compact' easy to build speaker kits (see opposite page) **£25.00** + p & p £2.00

BUILD YOUR OWN STEREO AMPLIFIER*

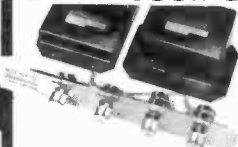


For the man who wants to design his own stereo - here's your chance to start, with Unisound - pre-amp, power amplifier and control panel. No soldering - just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum. 240V. AC only.

Also available with 2 speakers (7"x4") **£10** + £1.75 p & p. **£8.95** +£1.05 p & p.
Also available with the 'Compact' (see opposite page) easy build speaker kit **£13.50** + £2 p & p

INCORPORATES: Pre-Amp with full mixing facilities, including switched input for mic with volume control, switched input for auxiliary with volume control, bass and treble controls, volume control and blend control for turntables. Two B.S.R. MP80 type single play professional series decks, fitted with crystal cartridges.

PORTABLE DISCO CONSOLE*

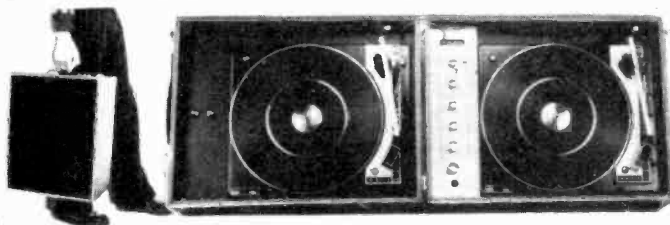

TECHNICAL SPECIFICATION:
Pre-amp - Output - 200mV.
Auxiliary inputs - 200mV and 750mV into 1 meg. Mic input - 6mV into 100K. 240 volt operation. Turntables capacity - 7", 10" or 12" records. Rumble, wow and flutter Rumble Better than -35dB. Wow Better than 0.2%. Flutter Better than 0.06% (Gaumont kalee meter).
Finish - Satin black mainplate with black turntable mat inlaid with brushed aluminium trim. Tonearm and controls in black and brushed aluminium.

Console size -
Unit Closed - 17 1/2" x 13 1/2" x 8 1/2" (app.)
Unit Open - 35 1/2" x 13 1/2" x 4 1/2" (app.)
This disco console is ideally matched for the Reliant IV and Disco 50 or any other quality amplifier.
The unit is finished in black PVC with contrasting simulated teak edging, diamond spun control knobs with matching control panel.

Yours for only **£49.00** +£6.50 p & p.

All prices include VAT at current rates



DO NOT SEND CARD

Just write your order giving your credit card number

Mail orders to Acton. Terms C.W.D. All enquiries stamped addressed envelope. Goods not despatched outside U.K.

Leaflets available for all items listed thus * Send stamped addressed envelope. All items subject to availability. Prices correct at 1st Mar. 1976 and subject to change without notice.

Minimum order on ACCESS/BARCLAYCARD-£11.



21D HIGH STREET, ACTON, LONDON W3 6NG
323 EDGWARE ROAD, LONDON W2

Personal Shoppers EDGWARE RD: 9 a.m.-5.30p.m. Half day Thurs
ACTON: 9.30a.m.-5p.m. Closed all day Wed.

It's here!

The Minisonic Mk. 2 has arrived—available NOW for the first time in kit form, the Minisonic 2 probably represents the best value for money in electronic music today.


Kits are available for complete instruments or individual sections, or for the conversion of Mk. 1 Minisonics to Mk. 2 specification. (Conversion details apply to Eaton Audio P.C.B.s, but may be adapted to suit others.)

In order to ensure that the appearance of the complete instrument enhances its performance, a complete cabinet kit is available, incorporating a fully finished black enamelled, silk-screened front panel, with matching back and base, and solid Afromosa end-cheeks. This kit also includes all switches, knobs, sockets, screws and panel indicators, keyboard and contact assemblies.

Cabinet Kit, including end cheeks, panels, switches, knobs, sockets, LED indicators, keyboard, set of GB (double pole) contacts
Kit MS/2-1 £192.64
Keyboard Controller—incorporating long duration 'Hold' circuit
Kit MS/2-3 £8.67
Voltage Controlled Oscillator (including temperature stabilization)
Kit MS/2-4 £16.96
Note: 2 off MS/2-4 are required.
Synchronisation Components (required for one VCO only)
Sync. Kit 34p
Envelope Shaper/VCA
Kit MS/2-5 £6.88
Note: 2 off MS/2-5 are required.
H.F. Oscillator/Detector
Kit MS/2-6 £1.84

Hold Isolator (including relay)
Kit MS/2-7 £3.24
Voltage Controlled Filter
Kit MS/2-8 £7.54
Ring Modulator
Kit MS/2-9 £3.75
Noise Generator
Kit MS/2-10 £2.00
Output Amplifiers (including panning, mixer and headphone amplifiers—2 channels)
Kit MS/2-11 £6.93
Control Envelope Inverter
Kit MS/2-12 91p
Stabilised Power Supply (includes reference supply and the transformer)
Kit MS/2-13 £9.00
Send large S.A.E. for further details of contents of kits.

Conversion Kits
Ancillary Functions Kit—for conversion of kbd. control, H.F. osc., detector, envelope shapers, V.C. filter, ring modulator, inverter, power supply, reference rails, output stages
Kit MS/2-14C £11.67
Oscillator Conversion Kit (for one V.C.O. only)
Kit MS/2-15C £11.04
SEPARATE ITEMS
P.C. Boards—Main Board (all modules except power supply, hold isolator, reference supply)
Board EA014 £3.80
Power Supply Board
Board EA015 £1.80
MD 8001 Dual Transistor £1.20
LM318N high speed op. amp. £2.14
2N5459 Field Effect Transistor 48p
Multiturn Preset Pots—1k, 10k or 20k (Cermet) 96p

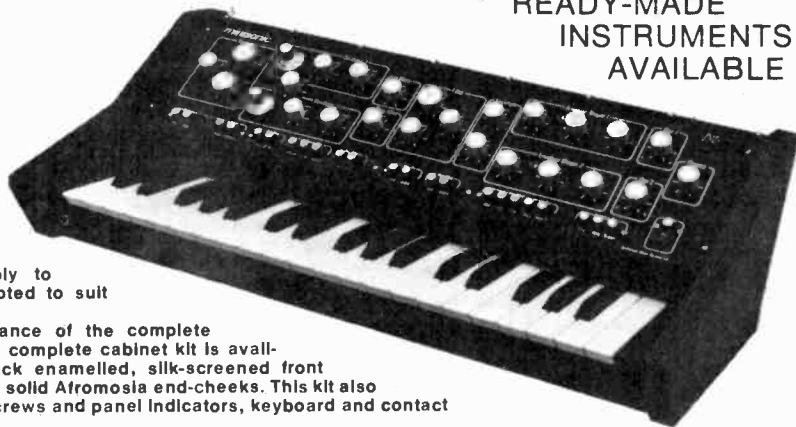


READY-MADE
INSTRUMENTS
AVAILABLE

EATON AUDIO

DEPT. PE, P.O. BOX 3
ST. NEOTS, CAMBS.
PE19 3JB

TERMS: MAIL ORDER ONLY C.W.O. MINIMUM ORDER £1 V.A.T. Please add 25% to value of order inc. P. & P. unless otherwise stated. Cheques or P.O.s payable to Eaton Audio. Orders over £5 free of P. & P. otherwise please add 10p in the £1.

INTER-LOCKING PLASTIC STORAGE DRAWERS

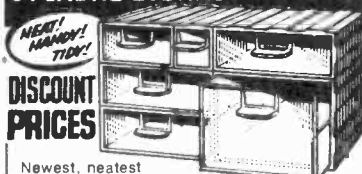

Neatest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. 1D and 2D have space dividers. Build up any size cabinet for wall, bench or table top.

As supplied to Post Office, Industry and Government Depts.

SINGLE UNITS (1D) (5in x 2½in x 2½in). £2.40 DOZEN.

DOUBLE UNITS (2D) (5in x 4½in x 2½in). £4.20 DOZEN.

TREBLE (3D) £4.20 for 8

DOUBLE TREBLE 2 drawers, in one outer case (6D2), £5.90 for 8.

EXTRA LARGE SIZE (6D1) £5.40 for 8.

PLUS QUANTITY DISCOUNTS

Orders over £20, less 5%.
Orders over £60, less 7½%.

PACKING/POSTAGE/CARRIAGE: Add 75p to all orders under £10. Orders £10 and over, please add 10% carriage.

QUOTATIONS FOR LARGER QUANTITIES
Please add 8% V.A.T. to total remittance

FLAIRLINE SUPPLIES

(Dept. PE5)
24 Cricklewood Broadway, London NW2
Tel. 01-450 4844

THE WORLD RADIO T.V. HANDBOOK 1976

Price £5.00

ACTIVE-FILTER COOKBOOK by D. Lancaster. Price £9.30.

99 WAYS TO KNOW AND USE YOUR ELECTRONIC CALCULATOR by L. E. Frezel. Price £3.95.

TRANSISTOR SUBSTITUTION HANDBOOK No. 15. Price £2.50.

EXPERIMENTS WITH OPERATIONAL AMPLIFIERS LEARNING BY DOING by G. B. Clayton. Price £3.35.

UNDERSTANDING IC OPERATIONAL AMPLIFIERS by R. Melen. Price £2.45.

SEMICONDUCTOR CIRCUIT ELEMENTS by T. D. Towers. Price £5.90.

THE RADIO AMATEUR'S HANDBOOK 1976 by A.R.R.L. Price £4.85.

SERVICING WITH THE OSCILLOSCOPE by G. J. King. Price £4.80.

FOUNDATIONS OF WIRELESS AND ELECTRONICS by M. G. Scroggie. Price £4.25.

★ TOTAL PRICE INCLUDE POSTAGE ★

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST
of British and American Technical Books

19-21 PRAED STREET
LONDON W2 1NP


Phone 01-723 4185
Closed Saturday 1 p.m.

BRIDGE ELECTRONICS COMPONENTS

£	£	£
AC126 0-13	BD138 0-28	2N2218A 0-18
AC127 0-13	BD139 0-29	2N2219 0-17½
AC128 0-11	BD140 0-32	2N2219A 0-18
AC151 0-18	BDY56 1-00	2N2221 0-17½
AC152 0-25	BF115 0-20	2N2221A 0-18
AC153 0-27	BF200 0-25	2N2222 0-17½
AC176 0-14	BF194 0-09	2N2646 0-30
AC187K 0-27	BF195 0-09	2N2904 0-18
AC188K 0-27	BF198 0-12	2N2905 0-18
AD161 0-35	BF199 0-12	2N2906 0-18
AD162 0-35	BF257 0-24	2N2907 0-18
BA102 0-10	BF258 0-24	2N2926G 0-09
BAX13 0-03	BF259 0-24	2N3053 0-20
BAX16 0-04	BFX29 0-22	2N3054 0-40
BC107 0-09	BFX30 0-22	2N3055 0-45
BC108 0-09	BFX84 0-20	2N3393 0-12
BC109 0-09	BFX85 0-27	2N3441 0-56
BC147 0-09	BFY50 0-19	2N3442 0-96
BC148 0-09	BFY51 0-19	2N3638 0-10
BC149 0-09	BFY52 0-19	2N3638A 0-10
BC167 0-10	BY126 0-11	2N3702 0-10
BC168 0-10	BY127 0-11	2N3704 0-10
BC169 0-10	QA47 0-06	2N3706 0-10
BC182 0-09	QA90 0-04	2N3708 0-10
BC183 0-09	QA91 0-04	2N3771 1-25
BC184 0-09	QA200 0-05	2N3772 1-35
BC212 0-09½	QA202 0-06	2N3773 2-00
BC213 0-09½	IN914 0-04	2N3904 0-11
BC214 0-9½	IN4004 0-05	2N3906 0-12
BC237 0-08	IN4007 0-08	2N5294 0-35
BC238 0-08	IN4308 0-05	2N5296 0-35
BC239 0-08	IS920 0-05	2N5784 0-20
BC307 0-09	2N697 0-15	2N3819 0-30
BC308 0-09	2N698 0-14	2N4036 0-55
BC309 0-09	2N706 0-10	2N4037 0-40
BC327 0-12	2N708 0-10	2N4921 0-80
BC328 0-12	2N916 0-23	2N5060 0-25
BCY70 0-13	2N1305 0-25	2N4289 0-25
BCY71 0-13	2N1307 0-25	2N5447 0-12
BCY72 0-12	2N1308 0-25	2N5448 0-12
BD135 0-25	2N1613 0-15	2N5457 0-30
BD136 0-26	2N1711 0-15	2N5458 0-27
BD137 0-27	2N2218 0-17½	2N6027 0-40

FULLY GUARANTEED

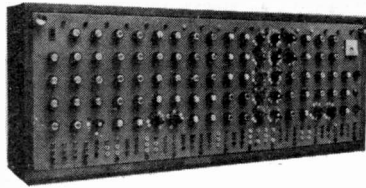Mail order only VAT extra p6p 20p
Bridge Electronics
PO Box No. 10 Fishponds Bristol BS16 2LX



P.E. SYNTHESISER

(P.E. Feb. 1973 to Feb. 1974)

The well acclaimed and highly versatile large-scale mains-operated Sound Synthesiser complete with keyboard circuits. All function circuits may be used independently, or interconnected. The greater the number of circuits, the greater the versatility. Other circuits in our lists may be used with the Synthesiser to good advantage.

THE MAIN SYNTHESISER

- Stabilised Power Supply £12-05
- Two Linear Voltage Controlled Oscillators and one Inverter—all 3 circuits: £16-38
- PCB (2 are required)—each £1-48
- Two Ramp Generators and Two Input Amplifiers—all 4 circuits £5-62
- PCB (holds all 4 circuits) £1-38
- Sample-and-Hold and Noise Generator—PCB (holds both circuits) £6-64
- Tone Control, £2-43; PCB, 80p £1-70
- Reverberation Amplifier £6-36
- Spring Line unit for Reverb Amp £4-95
- Ring Modulator £3-75
- Peak Level Meter Circuit £1-50
- 100µA Panel Meter £3-75
- PCB for Rev., R-Mod. & Meter Ccts. £1-94
- Envelope Shaper, £5-35; PCB, £1-46
- Voltage Controlled Amp. and Diff. Amp. £6-86
- PCB (holds both circuits) £1-32
- THE SYNTHESISER KEYBOARD CIRCUITS**
- Can be used without the Main Synthesiser to make an independent musical instrument) £14-55
- 2 Log. Voltage Controlled Oscillators for both log VCO's £2-40
- Divider, 2 Hold Circuits, 2 Modulation Amplifiers, Mixer and 2 Envelope Shapers £19-64
- PCB (Holds the first 6 circuits) £1-80
- PCB for both Envelope Shapers £1-55
- Keyboard Stabilised Power Supply £7-30
- Printed Circuit Board 94p

SYNTHESISERS AND KEYBOARDS

P.E. JOANNA

(P.E. May to Aug. 1975)

The new electronic piano that has switchable alternative voicing of Piano Honky-Tonk and Harpsichord. All PCB's are "as published".

- Power Supply £7-96
- Tone Generator and Top C Envelope Shaper £9-25
- PCB for above £1-30
- Envelope Shapers 12 sets (full requirement) £32-16
- Set of 12 PCB's (full requirement) £15-00
- Voicing and Pre-Amplifier Circuits £8-37
- PCB for above circuits £1-84
- Power Amplifier £14-50
- PCB for power amp .95p

KEYBOARDS

Kimber-Allen Keyboards as required for many published circuits, including the P.E. Joanna, P.E. Minisonic and P.E. Synthesiser. The manufacturers claim that these are the finest moulded plastic keyboards made.

- 3 Octave Keyboard (37 notes C to C) £20-50
- 4 Octave Keyboard (49 notes C to C) £23-50
- 5 Octave Keyboard (61 notes C to C) £27-00
- Contact Assemblies for use with above keyboards: Single-pole change-over (SP) as for P.E. Joanna and P.E. Minisonic. Two-pole normally-open make-break (2P) as for P.E. Synthesiser. Special contact assembly (4PS) having 4 poles, 3 of which are normally-open make-break contacts and the fourth is a change-over contact—this special assembly enables the same keyboard to be used with the P.E. Synthesiser, P.E. Minisonic, and P.E. Synthesiser simultaneously thus avoiding the cost of more than one keyboard.

Contact	Each Set	3 Octave	4 Octave	5 Octave
SP	20p	£7-40	£9-80	£12-20
2P	24p	£8-88	£11-76	£14-64
4PS	48p	£17-76	£23-52	£29-28

Printed Circuit Boards for use with the above contacts and thus eliminating most of the inter-wiring required, are available—details in our lists.



P.E. MINISONIC

(P.E. Nov. 1974 to March 1975)


A portable, battery or mains operated, miniature sound synthesiser, with keyboard circuits. Although having slightly fewer facilities than the large P.E. Synthesiser, the functions offered by this design give it great scope and versatility.

- Two Voltage Controlled Oscillators £5-22
- Voltage Controlled Filter and Voltage Reference Circuit £3-41
- Two Envelope Shapers and Two Voltage Controlled Amplifiers £7-25
- Keyboard Controller and Hold Circuits £2-66
- Keyboard Divider Resistors (select type to suit keyboard used, all are 2% tolerance). 2 Octave, £1; 3 Oct., £1-48; 4 Oct., £1-96; 5 Oct., £2-44.
- H.F. Oscillator and Detector £1-66
- Ring Mod., Noise Gen. & Env. Inverter £5-27
- Two Power Amplifiers and Two Mixers £3-55
- Battery Eliminator £5-88
- Temperature Stabiliser £1-47
- PCB to hold 2 VCOs, VCF and V-Ref £2-02
- PCB to hold 2 ESs, 2 VCAs, 2 Mixers, Ring Mod, Keyboard Control and Hold £2-20
- PCB to hold 2 Power Amps, Noise Gen, Envelope Inverter, HF Osc. and Detector £1-45
- PCB for Battery Elim. & Temp. Stab. £1-35

FOR ADDRESS, INFORMATION REGARDING POST AND PACKING, VAT, LISTS, AND EXPORT TERMS SEE OUR OTHER ADVERTISEMENT ON OPPOSITE PAGE

Photos: 2 of our units containing some of the P.E. projects built from our kits and PCBs. (The cases were built by ourselves and are not for sale.)

PHONOSONICS

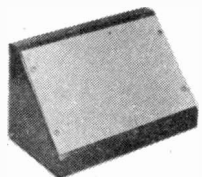

New sloping cases from OLSON

Type	Panel Dim	Depth	Height	Price
1	150mm x 100mm	95mm	95mm	£1-55
2	200mm x 100mm	95mm	95mm	£1-75
3	250mm x 100mm	95mm	95mm	£1-95

PLEASE ADD 40p P. & P. and VAT


New range of cases at 45° sloping panels. Attractively designed, of robust construction, and finished in two tone colour. supplied complete with four rubber feet. Available from stock in three different widths.

MATERIALS

Cases made from 20g steel. Front panels made from 20g aluminium.

COLOURS

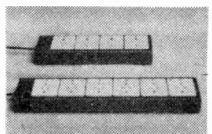Cases sprayed in light brown hammer finish. Front panels sprayed in light grey semi gloss enamel.



PORTABLE POWER DISTRIBUTION

- Complete with 8ft cable and 13A plug.
- 4 sockets 13A £8-00
- 6 sockets 13A £9-50
- 4 sockets 13A + 5W £9-15
- 8 sockets 13A + 5W £10-10

Please add VAT and 50p post and packaging

Trade counter is open for personal callers from 9 a.m.-5 p.m., Monday-Friday

OLSON ELECTRONICS LTD.

5-7 LONG STREET, LONDON E2

Tel. 01-739 2343

ELECTROVALUE

The good components service

In relatively few years, Electrovalue has risen to a position of pre-eminence as mail-order (and industrial) suppliers of semi-conductors, components, accessories, etc. There are wide ranges and large stocks to choose from as well as many worthwhile advantages to enjoy when you order from Electrovalue.

CATALOGUE 8 ISSUE 2 READY NOW!

Second printing (Green cover) with up-dated information, 144 pages. New items. Opto-electronics. Diagram of components, applications, I.C. circuits, etc. Post free 40p, including voucher for 40p for use on order over £5-00 list value. A must for careful buyers.

DISCOUNTS

On all C.W.O. mail orders, except for some items marked NETT.
 5% on orders list value £5 or more 10% £15 or more

FREE POST AND PACKING

On all C.W.O. mail orders in U.K. over £2 list value. If under, add 15p handling charge.

PRICE STABILIZATION POLICY

Prices are held and then reviewed over minimum periods of 3 months. Next review period effective from April 1st.

QUALITY GUARANTEE

On everything in our Catalogue—No manufacturers rejects, seconds or sub-standards merchandise.

ELECTROVALUE LTD


All communications to Dept. 5/2, 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB. Telephone Egham 3803, Telex 284475. Shop hours 9-5.30 daily, 9-1 pm Sat.

NORTHERN BRANCH: 680 Burnage Lane, Burnage, Manchester M19 1NA. Telephone (061) 432 4845. Shop hours Daily 9-5.30 pm; 9-1 pm Sat.

Join the Digital Revolution

Understand the latest developments in calculators, computers, watches, telephones, television, automotive instrumentation. . .

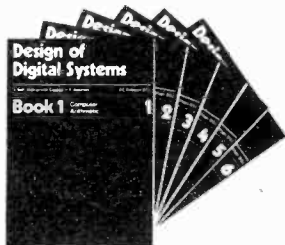Each of the 6 volumes of this self-instruction course measures 11½" x 8½" and contains 60 pages packed with information, diagrams and questions designed to lead you step-by-step through number systems and Boolean algebra, to memories, counters and simple arithmetic circuits, and on to a complete understanding of the design and operation of calculators and computers. Design of Digital Systems.



£5.95

plus 50p packing and surface post anywhere in the world.

Payments may be made in foreign currencies.

Quantity discounts available on request.

VAT zero rated.

Also available—a more elementary course assuming no prior knowledge except simple arithmetic. Digital Computer Logic and Electronics

In 4 volumes:

1. Basic Computer Logic
2. Logical Circuit Elements
3. Designing Circuits to Carry Out Logical Functions
4. Flipflops and Registers

£3.95

plus 50p P. & P.

Offer Order both courses for the bargain price £9.25, plus 50p P. & P.

**Designer
Manager
Enthusiast
Scientist
Engineer
Student**

These courses were written so that you could teach yourself the theory and application of digital logic. Learning by self instruction has the advantages of being quicker and more thorough than classroom learning. You work at your own speed and must respond by answering questions on each new piece of information before proceeding to the next.

Guarantee—no risk to you

If you are not entirely satisfied with Design of Digital Systems or Digital Computer Logic and Electronics, you may return them to us and your money will be refunded in full, no questions asked.

To: Cambridge Learning Enterprises (Dept. ENG)
FREEPOST, St. Ives, Huntingdon, Cambs. PE17 4BR

*Please send me . . . set(s) of Design of Digital Systems at £6.45 each, p & p included

*or . . . set(s) of Digital Computer Logic and Electronics at £4.45 each, p & p included

*or . . . combined set(s) at £9.75 each, p & p included

Name

Address

*delete as applicable
No need to use a stamp—just print FREEPOST on the envelope. PE5

orchard electronics

TRANSISTORS

AC125 20p	ASY67 70p	BC147A 9p*	BC205A 16p*	BC309B 16p*
AC126 20p	BA145 15p*	BC147B 10p*	BC206A 16p*	BC317A 12p*
AC127 20p	BA154 10p*	BC148 9p*	BC207A 11p*	BC312B 12p*
AC128 20p	BA155 15p*	BC148B 10p*	BC208A 11p*	BC322B 15p*
AC132 36p	BAX12 10p	BC149B 11p*	BC209B 13p*	BC327 16p*
AC141 20p	BAX13 4p	BC149C 11p*	BC212A 13p*	BC328 18p*
AC142 17p	BAX16 6p	BC153 18p*	BC212L 16p*	BC337 18p*
AC151 24p	BC107 11p	BC154 18p*	BC213B 12p*	BC338 16p*
AC153 27p	BC107A 12p	BC157B 12p*	BC213L 14p*	BC461 36p*
AC176 20p	BC108 10p	BC168A 12p*	BC214 16p*	BC557 8p
AC188 20p	BC108B 11p	BC169A 12p*	BC214L 17p*	BC668 8p
AD161 42p	BC109 11p	BC167A 11p*	BC237A 16p*	BC559 16p*
AD162 42p	BC109B 12p	BC168B 14p*	BC238A 15p*	BCY70 18p*
AF114 24p	BC109C 13p	BC171A 14p*	BC239B 16p*	BCY71 18p*
AF115 24p	BC116 16p*	BC172A 16p*	BC261A 16p	BCY72 14p
AF116 24p	BC118 16p*	BC173B 16p*	BC262A 16p	BD115 60p
AF117 24p	BC117 18p*	BC177 17p	BC266A 18p	BD121 90p
AF118 47p	BC118 10p*	BC178B 18p	BC267A 17p	BD123 90p
AF124 30p	BC119 25p	BC179B 18p	BC268B 18p	BD124 88p
AF125 30p	BC125 14p*	BC182B 10p*	BC269 15p	BD151 36p
AF128 28p	BC132 11p*	BC182L 11p*	BC287 20p	BD132 38p
AF139 34p	BC135 12p*	BC183B 10p*	BC300 27p	BD133 65p
AF186 60p	BC136 16p*	BC183L 10p*	BC301 26p	BD135 37p*
AF239 37p	BC137 16p*	BC184B 12p*	BC302 26p	BD136 38p*
AS126 30p	BC138 16p*	BC184L 11p*	BC303 30p	BD137 44p*
AS127 34p	BC139 36p	BC186 25p	BC304 27p	BD138 47p*
AS128 30p	BC142 22p	BC187 26p	BC307A 16p*	BD139 54p*
AS129 34p	BC143 24p	BC204A 16p*	BC308A 14p*	BD155 76p*

INTEGRATED CIRCUITS LINEAR

709 (8 pin DIL) 40p	ZENERS (400 mW)	VOLTAGE REGULATORS (TO3)	DIL Sockets	INTEGRATED CIRCUITS
741 (8 pin DIL) 33p	BZX83/BZY88	5V 1A £1.75	8 pin 15p	TTL Digital
NE555 60p	3V3, 3V6, 3V9, 5V 1A	12V 1A £1.75	16 pin 17p	7400 18p
	4V3, 4V7, 5V1, 12V 1A	15V 1A £1.75		7401 20p
	5V6, 6V2, 6V5, 7V5, 8V2, 9V1, 10V, 12V, 13V, All at 12p each*			7402 18p
				7403 18p
				7404 28p
				7405 28p
				7406 40p
				7407 40p
				7408 24p
				7409 28p
				7410 18p
				7411 24p
				7412 25p
				7413 28p

VAT—Items marked * add 25%, remainder at 8%.

Flint House, High Street, Wallingford, Oxon OX10 0DE
Tel.: Wallingford (0491) 35529 Telex 4SPWALFRD 849349



FREE Brochure on New KITS

Whether professional, student, teacher or amateur, the field of electronics can open up a new world for you.

Send 15p S.A.E. (10In x 12In) to cover postage

PLEASE NOTE OUR NEW ADDRESS




CROFTON don't just sell kits, we offer you a technical back up service to ensure your success

The following is a selection of some of the more popular kits—

- ★ Mullard CCTV Camera
- ★ PE CCTV Camera
- ★ "Mistral" Digital Clock Kit £12.50 (inc. VAT + 50p P. & P.); Built £18 + 50p P. & P.
- ★ Electronic Ignition
- ★ Sound Operated Flash
- ★ PW Tele-Tennis Game
- ★ UHF Modulator
- ★ Bench Power Supply
- ★ Wobulator
- ★ All ETI Top Projects
- ★ Many of the Elektor Projects

NOTE PCBs for most published projects available to order

CROFTON ELECTRONICS LTD

Dept E, 35 Grosvenor Road, Twickenham, Middx. 01-891 1923

barclay

ELECTRONICS

TECHNOLOGICAL
PRECISION PRODUCTS

DECIMO

VATMAN SCIENTIFIC—Large green display, 8-digits, 2 exponents, 4 trig log functions, 10⁹⁹ radian degrees, exchange, memory, π, reciprocal, X², etc. Single function keyboard. 20 hr battery life. **£27.50**



MINI-VATMAN—Similar to above but slimmer. Green display, 8-digits, % key, √. **£9.50**

MINI-VATMAN M—As above but with % and full-function memory. **£11.50**

VATMAN (illus.)—8-digit, % key, green display. **£9.50**

SUPER-VATMAN—Similar to above but with full-function memory, X², reciprocal, π, √. **£12.45**

ROCKWELL

63R (illus.)—8-digit, 2 exponent, 10⁹⁹ memory, 2-level parentheses, all trig and log functions, degree radian, factorial, reciprocal, π, √, etc. Rechargeable. **£32.95** (inc. recharger)



61R—Green display, 8-digits, all trig and log functions. **£21.95**

51R—8-digits, metric and currency converter. **£21.95**

8R—8-digits, % key. **£8.95**

20R (illus.)—8-digits, % key, full-function memory. **£11**



31R—√, memory, memory exchange, reciprocal, X², Rechargeable. **£15.75** (incl. recharger)

24RD—Green display, √, 8-digit. **£13.75**

24K (illus.)—Stainless-steel slimline, green display, beautiful leatherette wallet to hold pen, note-pad (all included) and credit cards. Full memory, √, click-buttons. Rechargeable. (inc. recharger) **£21.95**



CASIO

FX-20 (illus.)—Full trig and log functions; 8-digit mantissa or 6-digit mantissa and 2-digit exponents; 10⁹⁹ to 10⁻⁹⁹ bright green display; full sin, cos, tan, inverse sin, inverse cos, inverse tan, log X and ln x, e^x, X², √, reciprocal degree radian conversion; memory and exponent key. **ONLY £19.45**



FX-15—As above but larger and including a larger display, X² key, π key, reciprocal key. **ONLY £25.70**

FX-101—De Luxe model with similar functions to the FX-15 but 8-digits + 2 exponents 10⁹⁹ to 10⁻⁹⁹.

OUR PRICE £29.75

8R—Memory, % key. **£8.95**

POCKET 8s—% key. **£7.95**

POCKET MINI-MEMORY—% key, bright green display. **£9.95**

ALL ITEMS CARRY A FULL YEAR'S GUARANTEE
British Standard Adaptor for all non-rechargeable calculators **ONLY £2.50**

NOVOUS

4520—8-digit, 2 exponent, 10⁹⁹ RPN logic, full trig and log functions, 4-roll stack, memory, memory exchange, √, degree and radian. Rechargeable. (inc. recharger) **£22.75**



4525 (illus.)—Rechargeable. Programmable version of 4520. (inc. recharger) **£45.90**

4510—8-digits, 3 level stack, all trig and log function, √, π, reciprocal, memory, etc. **£14.50**

4515—100-step programmable version. **£37.75**

6020—Financier. **£17.95**

6025—Financier 100-step programmable. Rechargeable. (inc. recharger) **£45.90**

2030—Statistician. **£17.80**

6035—100-step programmable Statistician. Rechargeable. (inc. recharger) **£45.90**

TEXAS

SR50A (illus.)—10-digit, 2 exponent, all trig and log functions, hyperbolic, X to the root of Y, radian and degree, factorial, memory, etc. Rechargeable. (inc. recharger) **£37.75**



SR51A—As above but with 3 independent memories, linear regression, mean, variance, standard deviation, permutation, random number generation plus 20 basic conversions and their inverse. Rechargeable. (inc. recharger) **£49.75**

T1200 (illus.)—8-digit, % key. **£8.50**



T1250—As above with memory. **£8.95**

sinclair

NEW SCIENTIFIC—Only 1/2 in x 2 1/2 in x 1/2 in, yet has 8-digits or 5+2 exponents. Using the NEW chip, it has full algebraic logic and many more functions. Algebraic logic is constant on all four arithmetic functions.



Functions: C & CE key • sin • cos • tan • arcsin • arccos and tan • reciprocal • E to the X • natural log • antilog • √ • memory + • memory - • memory exchange • memory cancel • EE exponent • change notation • PLUS a degree radian switch! **ONLY £14.60**

OXFORD 300—Larger version of above. **£17.95**

SCIENTIFIC PROGRAMMABLE

CAMBRIDGE £8 £29.50

CAMBRIDGE MEMORY £10.75

OXFORD 150 £8.95

CBM

4148R (illus.)—10-digits, 2 exponents. Full log and trig functions. X² Reciprocal, π, X root of Y, Polar rectangular co-ordinates. 2-store memory. Rechargeable. Mean and Standard deviation. (inc. recharger) **£32.50**



SR1800—Similar to the 4148R. Green display. Battery operated. **£27.50**

796D—8-digits, % and store. **£6.75**

997R—Rechargeable % and full memory. (inc. recharger) **£12.50**

7919D—Full trig and logs. 8-digit or 5+2 exponents. Reciprocal, π, √, memory. **£13.50**

ALL PRICES INCLUDE VAT. Please add 55p P. & P.

Digital Wrist Watches

ARNOS

5 - Function digital watch in stainless steel finish with matching bracelet. Shows hrs, mins, date, a.m. and fad-out hold and indicator. **£21.90**



Gold finish **£23.90**

ASTRA

3-Functions. Shows hrs, mins and secs. Single button operation. Limited supplies at this low, low price. **ONLY £13.95 with strap. Gold finish £15.95**



THE SUPERB 10-function PULSTRONIC

Shows date and month in correct order! Single button control. Display visible in pitch dark. Hrs, Mins, Secs, Date + Month, Day of Week, self-adjusting calendar, Auto hold and fade-out, A.M. setting indicator, P.M. setting indicator. Undoubtedly one of the most sophisticated watches available at this unbeatable price! Styled in finest solid Stainless-steel, satin finished with polished bevelled edges. Complete with adjustable matching stainless-steel bracelet and a FREE presentation box.

LIMITED SUPPLIES ONLY £37.40

ORDER FORM

PHONE CALLS AND PERSONAL CALLERS WELCOME MONS-THURS BETWEEN 2 and 5 p.m. 01-458 4755.

To: BARCLAY ELECTRONICS Dept. PE68, STANLEY HOUSE, 1115 FINCHLEY ROAD, LONDON N.W.11

Please send me with/without optional mains adaptor. I enclose cheque/money order total value £ including 55p to cover P. & P.

NAME

ADDRESS

barclay

DIGITAL : CLOCKS : KITS : CALCULATORS

"ALPHA": 4 GREEN 0.5in HIGH DIGITS

Alpha Module (excl. case)	Kit	Alarm	Std
Alpha Module (excl. case)	Built	£13.00	£10.00
Alpha complete: Perspex Case	Kit	£14.00	£11.00
Alpha Clock: Perspex Case	Built	£15.50	£12.50
		£21.50	£17.50

ALARM ● Tilt Snooze ● AM/PM ● Mains failure
 Ind. ●
 ● Auto-Control Brightness by Photocell ●

"DELTA": 4 RED 0.5in HIGH LEDs

Delta Module (excl. case)	Kit	Alarm	Std
Delta Module (excl. case)	Built	£11.00	£9.00
Delta complete: Perspex Case	Kit	£11.50	£9.50
Delta Clock: Perspex Case	Built	£15.00	£12.00
Delta complete: Teak Case	Kit	£21.00	£17.00
Delta Clock: Teak Case	Built	£15.70	£12.70
		£21.70	£17.70

Perspex Case Colours: Black, White, Red, Green, Blue, Orange.
 Built Modules and Clocks: 12 or 24 hour.
 Complete Clocks: 2 year guarantee.

"NOVUS" CALCULATORS

650 Mathbox	£5.40	850 Mathbox	£6.75
4510 Mathematician	£16.20	6020 Statistician	£21.60

C.W.O. **PULSE ELECTRONICS**

(PE12), 202 Shefford Road, Clifton, Shefford, Beds.
 S.A.E. complete range


Module kits
 from
£900

INCL. VAT. P & P

SATISFACTION GUARANTEED

- Modern 2 Part Case
- Drilled P.C.B.
- 4 Digit Display 0.5 inch high
- All components included
- Even Mains lead included
- Full Instructions
- Assembly Drawing
- Circuit Diagram

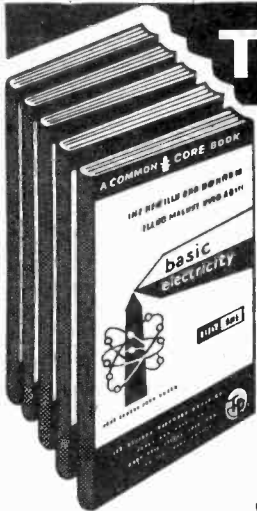You supply only mains plug and standard tools. Easy!



The Pictorial Method

BASIC ELECTRICITY(5vols)
 ELECTRONICS(6vols)
 TELEVISION(3vols)

You'll find it easy to learn with this outstandingly successful PICTORIAL METHOD. The essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate cartoon-type drawing. These clear and concise illustrations make study a real pleasure. The books are based on the latest research into simplified learning techniques. This easy-approach-to-learning method has proved beyond doubt that acquiring knowledge can be an enjoyable experience.

YOUR 100% GUARANTEE

Should you be, in any way dissatisfied with the MANUALS your money will be refunded by return of post.

The series will be of exceptional value in training mechanics and technicians in Electricity, Radio and Electronics.

WHAT READERS SAY

- I didn't know this subject could be so easily presented. *J.K., Earlsfield*
 Pleased to say how understandable your books are—I now have a sound knowledge of the subject. *A.K., Hull*
 Invaluable for my training as a Technician. *W.J., Stockport*
 They have an easy approach to learning that a mathematical idiot like myself can easily understand. *K.L.Y., Ashton-u-Lyme*
 Thank you for the excellent publication: the best in form and type I have ever come across. *T.L.O., Shanklin*
 I find the Basic Manuals the best in their class and a real help in my work in phototype electronics. *C.L.P., Cardiff*

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT. BR2 7HP

Please find enclosed P.O./Cheque value £.....

- BASIC ELECTRICITY 5 parts £8.00
- BASIC ELECTRONICS 6 parts £9.50
- BASIC TELEVISION 3 parts £5.00

Tick Set(s) required. Prices include Postage

YOUR 100% GUARANTEE. If after 10 days examination you decide to return the Manuals your money will be refunded in full.

NAME
 BLOCK LETTERS
 FULL POSTAL.....
 ADDRESS

POST NOW FOR THIS OFFER!

15-240 WATTS!

HY5 Pre-amplifier


The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (mag Cartridge, tuner, etc.) are catered for internally, the desired function is achieved either by a multi-way switch or direct connection to the appropriate pins. The internal volume and tone circuits merely require connecting to external potentiometers (not included). The HY5 is compatible with all I.L.P. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre-amplifier.

FEATURES: complete pre-amplifier in single pack; multi-function equalisation; low noise; low distortion; high overload; two simply combined for stereo.

APPLICATIONS: hi-fi; mixers; disco; guitar and organ; public address.

SPECIFICATION: inputs—magnetic pick-up 3mV; ceramic pick-up 30mV; tuner 100mV; microphone 10mV; auxiliary 3–100mV; input impedance 47k Ω at 1kHz. Outputs—tape 100mV; main output 500mV R.M.S. Active Tone Controls—treble \pm 12dB at 10kHz; bass \pm 12dB at 100Hz. Distortion—0.1% at 1kHz; signal/noise ratio 88dB. Overload—38dB on magnetic pick-up. Supply Voltage— \pm 16–50V.

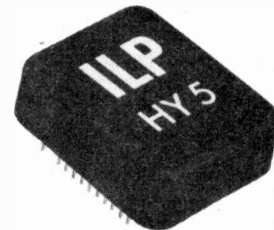Price \pounds 4.75 + \pounds 1.19 VAT. P. & P. free



HY30 15W into 8 Ω

The HY30 is an exciting New kit from I.L.P. It features a virtually indestructible I.C. with short circuit and thermal protection. The kit consists of: I.C., heatsink, P.C. board, 4 resistors, 6 capacitors, mounting kit, together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up to date technology available.

FEATURES: complete kit; low distortion; short, open and thermal protection; easy to build.

APPLICATIONS: updating audio equipment; guitar practice amplifier; test amplifier; audio oscillator.

SPECIFICATION: Output Power—15W R.M.S. into 8 Ω . Distortion—0.1% at 15W. Input Sensitivity—500mV. Frequency Response—10Hz–18kHz—3dB.

Price \pounds 4.75 + \pounds 1.19 VAT. P. & P. free

AVAILABLE
JUNE 1976

HY50 25W into 8 Ω

The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most reliable and robust High Fidelity modules in the World.

FEATURES: low distortion; integral heatsink; only five connections; 7 amp output transistors; no external components.

APPLICATIONS: medium power hi-fi systems; low power disco; guitar amplifier.

SPECIFICATION: Input Sensitivity—500mV. Output Power—25W R.M.S. into 8 Ω . Load Impedance—4–16 Ω . Distortion—0.04% at 25W at 1kHz. Signal/Noise Ratio—75dB. Frequency Response—10Hz–45kHz—3dB. Supply Voltage— \pm 25V. Size—105 x 50 x 25mm.

Price \pounds 6.20 + \pounds 1.55 VAT. P. & P. free



HY120 60W into 8 Ω


The HY120 is the baby of I.L.P.'s new high power range, designed to meet the most exacting requirements including load line and thermal protection this amplifier sets a new standard in modular design.

FEATURES: very low distortion; integral heatsink; load line protection; thermal protection; five connections; no external components.

APPLICATIONS: hi-fi; high quality disco; public address; monitor amplifier; guitar and organ.

SPECIFICATION: Input Sensitivity—500mV. Output Power—60W R.M.S. into 8 Ω . Load Impedance—4–16 Ω . Distortion—0.04% at 60W at 1kHz. Signal/Noise Ratio—90dB. Frequency Response—10Hz–45kHz—3dB. Supply Voltage— \pm 35V. Size—114 x 50 x 85mm.

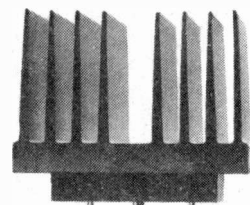Price \pounds 14.40 + \pounds 1.16 VAT. P. & P. free



HY200 120W into 8 Ω


The HY200 (now improved to give an output of 120 watts) has been designed to stand the most rugged conditions such as disco or group while still retaining true hi-fi performance.

FEATURES: thermal shutdown; very low distortion; load line protection; integral heatsink, no external components.

APPLICATIONS: hi-fi; disco; monitor; power slave; industrial; public address.

SPECIFICATION: Input Sensitivity—500mV. Output Power—120W R.M.S. into 8 Ω . Load Impedance—4–16 Ω . Distortion—0.05% at 100W at 1kHz. Signal/Noise Ratio—96dB. Frequency Response—10Hz–45kHz—3dB. Supply Voltage— \pm 45V. Size—114 x 100 x 85mm.

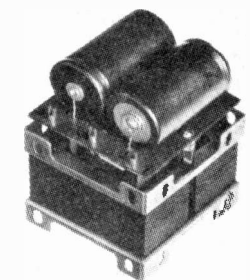Price \pounds 21.20 + \pounds 1.70 VAT. P. & P. free



HY400 240W into 4 Ω

The HY400 is I.L.P.'s "Big Daddy" of the range producing 240W into 4 Ω ! It has been designed for high power disco or public address applications. If the amplifier is to be used at continuous high power levels a cooling fan is recommended. The amplifier includes all the qualities of the rest of the family to lead the market as a true high power hi-fidelity power module.

FEATURES: thermal shutdown; very low distortion; load line protection; no external components.

APPLICATIONS: public address; disco; power slave; industrial.

SPECIFICATION: Output Power—240W R.M.S. into 4 Ω . Load Impedance—4–16 Ω . Distortion—0.1% at 240W at 1kHz. Signal/Noise Ratio—94dB. Frequency Response—10Hz–45kHz—3dB. Supply Voltage— \pm 45V. Input Sensitivity—500mV. Size—114 x 100 x 85mm.

Price \pounds 29.25 + \pounds 2.34 VAT. P. & P. free

POWER SUPPLIES: PSU36—suitable for two HY30s \pounds 4.75 + \pounds 1.19 VAT. P. & P. free. PSU50—suitable for two HY50s \pounds 6.25 + \pounds 1.58 VAT. P. & P. free. PSU70—suitable for two HY120s \pounds 12.50 + \pounds 1.00 VAT. P. & P. free. PSU90—suitable for one HY200 \pounds 11.50 + 92p VAT. P. & P. free. PSU100—suitable for two HY200s or one HY400 \pounds 21 + \pounds 1.88 VAT. P. & P. free.

TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS

I.L.P. Electronics Ltd.
Crossland House,
Nackington, Canterbury
Kent CT4 7AD
Tel (0227) 63218

Please supply

Total Purchase price

I Enclose: Cheque Postal Orders Money Order

Please debit my Access account Barclaycard account

Account number

Name and Address

Signature

BI-PAK High quality audio

NEW

STEREO FM TUNER

Fitted with Phase Lock-loop Decoder

- ★ FET Input Stage
- ★ VARI-CAP diode tuning
- ★ Switched AFC
- ★ Multi turn pre-sets
- ★ LED Stereo Indicator

Typical Specification:
 Sensitivity 3µ volts
 Stereo separation 30dB
 Supply required 20-30V
 at 90 Ma max.

OUR PRICE ONLY

£19.95

The 450 Tuner provides instant programme selection at the touch of a button ensuring accurate tuning of 4 pre-selected stations, any of which may be altered as often as you choose, by simply changing the settings of the pre-set controls. Used with your existing audio equipment or with the BI-KITS STEREO 30 or the MK60 Kit etc. Alternatively the PS12 can be used if no suitable supply is available, together with the Transformer T461. The S450 is supplied fully built, tested and aligned. The unit is easily installed using the simple instructions supplied.

STEREO PRE-AMPLIFIER PA 100



A top quality stereo pre-amplifier and tone control unit. The six push-button selector switch provides a choice of inputs together with two really effective filters for high and low frequencies, plus tape output.

Frequency Response +1dB 20Hz-20kHz.
 Sensitivity of Inputs:
 1. Tape Input 100mV into 100k ohms
 2. Radio Tuner 100mV into 100k ohms
 3. Magnetic P.U. 3mV into 50k ohms
 P.U. Input equalises to R1AA curve within 1dB from 20Hz to 20kHz.
 Supply 20-35V at 20mA. Dimensions — 299 x 89 x 35mm.

£13.50 P. & P. 45p


MK60 AUDIO KIT:
 Comprising: 2 x AL60's, 1 x SPM80, 1 x BTM80, 1 x PA100, 1 front panel and knobs.
 1 Kit of parts to include on/off switch, neon indicator, stereo headphone sockets plus instruction booklet. COMPLETE PRICE £27.55 plus 62p postage.

TEAK 50 AUDIO KIT:
 Comprising: Teak veneered cabinet size 16½ x 11½ x 3½in, other parts include aluminium chassis, heatsink and front panel bracket plus back panel and appropriate sockets etc. KIT PRICE £9.20 plus 62p postage.

AL 60

VAT ADD 25%

25 Watts (RMS)

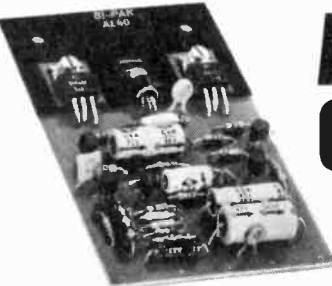

- Max Heat Sink temp. 90°C.
- Frequency response 20Hz.
- Distortion better than 0.1 at 1kHz.
- Supply voltage 15-50V.
- Thermal Feedback.
- Latest Design Improvements.
- Load—3, 4, 5 or 16 ohms.
- Signal to noise ratio 80dB.
- Overall size 63 x 13mm.

Especially designed to a strict specification. Only the finest components have been used and the latest solid-state circuitry incorporated in this powerful little amplifier which should satisfy the most critical A.F. enthusiast.

ONLY **£3.95**

Stabilised Power Supply Type SPM80

SPM80 is especially designed to power 2 of the AL60 Amplifiers, up to 15 watts (r.m.s.) per channel simultaneously. With the addition of the Mains Transformer BMT80, the unit will provide outputs of up to 1.5A at 35V. Size: 63 x 105 x 30mm. Incorporating short circuit protection.

INPUT VOLTAGE 33-40V A.C.
 OUTPUT VOLTAGE 33V D.C. Nominal
 OUTPUT CURRENT 10mA-1.5 amps
 OVERLOAD CURRENT 1.7 amps approx.
 DIMENSIONS 105 x 63 x 30mm
 TRANSFORMER BMT80 £2.60 + 62p postage

£3.00

STEREO 30 COMPLETE AUDIO CHASSIS



7 + 7 WATTS R.M.S.
 The Stereo 30 comprises a complete stereo pre-amplifier, power amplifiers and power supply. This, with only the addition of a transformer or overwind will produce a high quality audio unit suitable for use with a wide range of inputs i.e. high quality ceramic pick-up, stereo tuner, stereo tape deck etc. Simple to install, capable of producing really first class results, this unit is supplied with full instructions, black front panel, knobs, mains switch, fuse and fuse holder and universal mounting brackets enabling it to be installed in a record plinth, cabinets of your own construction or the cabinet available, ideal for the beginner or the advanced constructor who requires Hi-Fi performance with a minimum of installation difficulty (can be installed in 30 mins).

TRANSFORMER **£2.45** plus 62p P. & P.
 TEAK CASE **£3.65** plus 62p P. & P. **£15.75** P. & P. 45p


equipment mono and other modules for Stereo

IT'S NEW!

IT'S POWERFUL

IT'S THE AL250

125 watts
R.M.S.

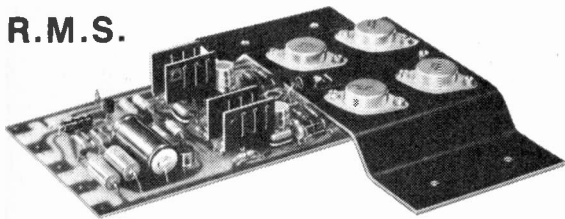

POWER AMPLIFIER

Specially designed for use in—
Disco Units, P.A. Systems, high power
Hi-Fi, Sound reinforcement systems

The module has a sensitivity of 450mV and a frequency response extending from 25Hz to 20kHz whilst distortion levels are typically below 0.1%. The use of 4, 115W transistors in the output stage makes the unit extremely rugged while damage resulting from incorrect or short-circuit loads is prevented by a four transistor protection circuit.


The unit is intended for use in many applications such as disco units, sound reinforcement systems, background music players, etc.

SPECIFICATION:

Output Power: 125 watt RMS
Continuous
Operating voltage: 50-80
Loads: 4-16 ohms
Frequency response: 25Hz-20kHz
Measured at 100 watts
Sensitivity for 100 watts output at
1kHz: 450mV
Input impedance: 33k ohms

Total harmonic distortion
50 watts into 4 ohms: 0.1%
50 watts into 8 ohms: 0.06%
S/N ratio: better than 80dBs
Damping factor: 9 ohms: 65
Semiconductor complement: 13
transistors 5 diodes
Overall size: Heatsink width
190mm, length 205mm, height
40mm

MPA 30

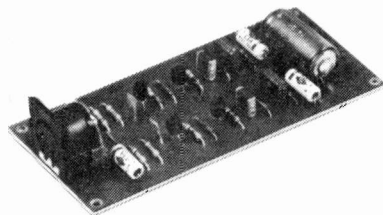

Enjoy the quality of a magnetic cartridge with your existing ceramic equipment using the new Bi-Pak M.P.A. 30 which is a high quality pre-amplifier enabling magnetic cartridges to be used where facilities exist for the use of ceramic cartridges only. Used in conjunction are 4 low noise, high gain silicon transistors. It is provided with a standard DIN input socket for ease of connection. Supplied with full, easy-to-follow instructions.

£2.65


**VAT
ADD
25%**

**POSTAGE &
PACKING**

Postage & Packing add 25p unless otherwise shown. Add extra for airmail. Min. £1-00

AL10-20-30

AUDIO AMPLIFIER MODULES

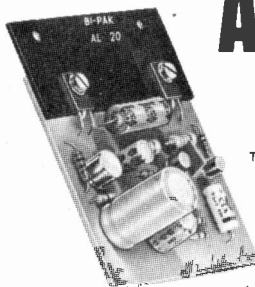

The AL10, AL20 and AL30 units are similar in their appearance and in their general specification.

However, careful selection of the plastic power devices has resulted in a range of output powers from 3 to 10 watts R.M.S. The versatility of their design makes them ideal for use in record players, tape recorders, stereo amplifiers and cassette and cartridge tape players in the home. Harmonic Distortion $P_o = 3$ watts $f = 0.25\%$ Load

Impedance 8-16 ohm

Frequency response $\pm 3dB$ $P_o = 2$ watts 50Hz-25kHz
Sensitivity for Rated $O/P - V_a = 25V$, $R_L = 80$ ohm
 $f = 1kHz$ 75mV. RMS. Size: 75 x 63 x 25mm.

AL10 3W R.M.S. **£2.30** AL2 5W R.M.S. **£2.65** AL30 10W R.M.S. **£2.95**

NEW

PA 12

£6.50

NEW PA12 Stereo Pre-Amplifier completely redesigned for use with AL10 20 30 Amplifier Modules. Features include on/off volume, Balance, Bass and Treble controls. Complete with tape output.

Frequency Response 20Hz-20kHz ($\pm 3dB$)
Bass and Treble range $\pm 12dB$
Input impedance 1 meg ohm
Input Sensitivity 300mV
Supply requirements 24V, 5mA
Size 152 x 84 x 33mm

PS 12

Power supply for AL10/20/30, PA12, S450 etc. Input voltage 15-20V a.c. Output voltage 22-30V d.c. Output Current 800mA Max
Size 60 x 43 x 26mm.

Transformer T538 £2.30


£1.20

BI-PAK


P.O. BOX 6, WARE, HERTS

ONLY £15.95 + 8% VAT


VERO

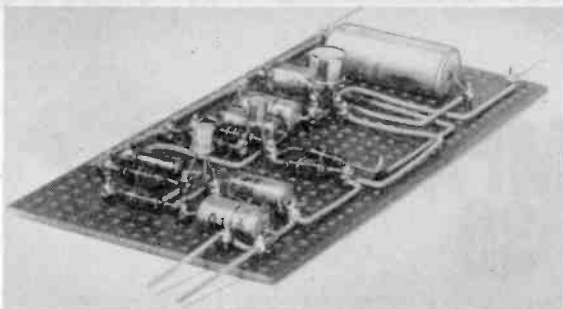

Veroboard® Universal Wiring Boards

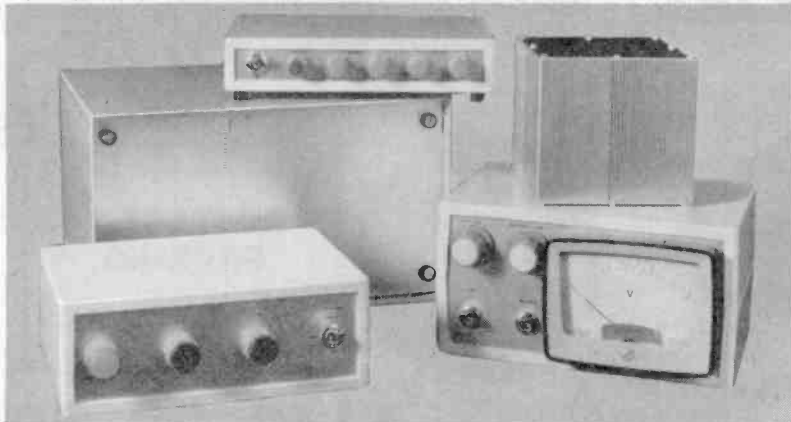

Plastic and Metal Verobox®

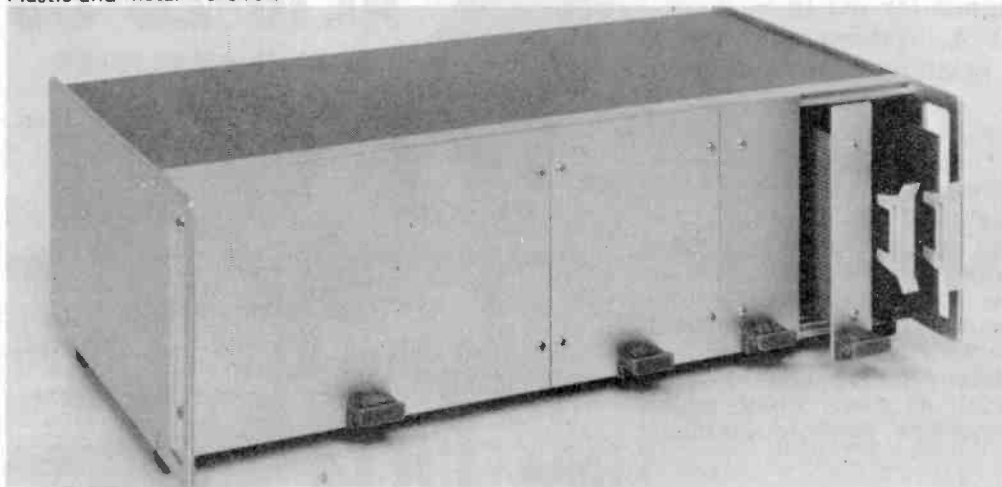

19" Card Frame/Case

Vero Products for the HOME CONSTRUCTOR

Vero Electronics Limited, Retail Dept.,
Industrial Estate, Chandler's Ford, Hants., SO5 3ZR
Telephone: Chandler's Ford 2956 (STD 04215)

UNDER-SOLD?

MANY of the great achievements and commercial successes of electronics are due to the amazing cheapness of semiconductor devices, no less than to their technical versatility. But the first of these attributes could well prove an embarrassment or liability when considering its effect upon the popular image of electronics, and this is especially important now when the whole question of salaries and status of technical employees in the industry has come to the fore, as discussed by Nexus in this month's Industry Notebook.

Cheapness of components has helped reduce certain consumer type products to the expendable grade. Cheap transistor radios provided the first examples of modern electronic products which are sometimes deemed not worth repairing but are discarded when trouble appears. With the arrival of the digital watch, this custom could be carried to its ultimate absurdity. For if prices continue to fall as confidently predicted, it could eventually become more economical and certainly more convenient to throw away the cheaper type digital watch when the batteries expire and buy another.

There is a further interesting aspect well illustrated by this product, since the digital watch is also invading the fine jewellery market. These up-market models owe everything to their external appearance—to the case—since the electronic assembly might be identical to that used in a cheaper version. Cheap, common, and expendable plastics versus expensive, exclusive, and indestructible fine metals. Micro-electronics has made it all possible, but the case designers and makers seem likely to skim off the cream.

The digital watch thus offers an illuminating but disturbing example of highly advanced technology selling for a song, and the packaging alone determining whether the final product be a cheap and expendable item or a lasting and valuable possession. Moreover, in more general terms, as the ordinary constructor knows only too well, it is not unusual for the major cost of an electronic project to be taken up by non-active components and also items such as the hardware used in the assembly of the components and to encase the completed project. We all welcome and enjoy low cost active devices, but to the technically-appreciative, values must seem somehow to have become reversed.

Almost too late it seems semiconductor makers sense that they have been blinded by their own technological success and have been unwise in waging price wars on one another in order to acquire a bigger portion of the cake. The short term gains have been considerable, but what of the future? Has then electronics sold itself short? Any cheapening of the technology, any equating of its products with, say, easy-come easy-go plastics commodities must in the long term be detrimental to the status and financial well-being of those employed in electronics. Perhaps the semiconductor industry should recall that charity begins at home, and that cut-price technology is not really in everyone's best interests, and that it often leaves the biggest plums for outsiders to gather.

F.E.B.

Editor
F. E. BENNETT

Editorial
D. BARRINGTON *Production Editor*
G. GOBOLD *Technical Editor*
R. W. LAWRENCE, B.Sc.

Art Dept.
J. D. POUNTNEY *Art Editor*
D. J. GOODING
R. J. GOODMAN
K. A. WOODRUFF


Editorial Offices:
Fleetway House, Farringdon St.
London EC4A 4AD
Phone: 01-634 4452

Advertisement Manager
D. W. B. TILLEARD
Phone: 01-261 5148

P. J. MEW
Phone: 01-261 5190

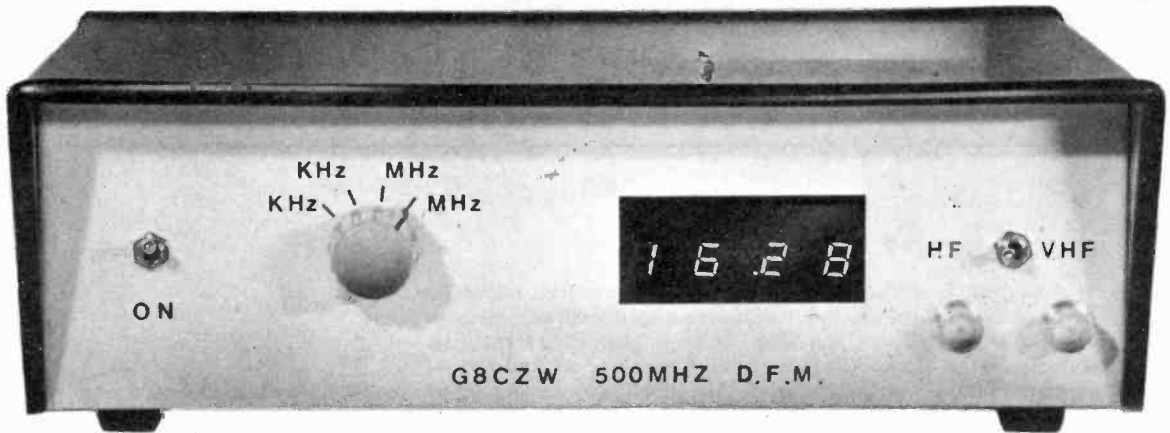C. R. BROWN *Classified*
Phone: 01-261 5000

Advertising Offices:
King's Reach Tower, Stamford St.
London SE1 9LS
Phone: 01-261 5000



DIGITAL FREQUENCY METER

By A.J. BUXTON

THIS article describes the design, construction and testing of a digital frequency meter (D.F.M.). This particular instrument has been designed as a radio society construction project and with this in mind it was necessary to use straightforward, logical design.

Ease of fault-finding has been one of the main considerations and to this end a design has been produced which can be tested and maintained using simple test gear.

The entire logic is contained on a single printed circuit board, and the four-digit display (in this case seven-segment light emitting diodes) is on another board. The power supply and the range switching are the only items that need free wiring.

The basic unit to be described has a 50 ohm input impedance and can measure up to at least 50MHz. Modifications will be described to extend

the frequency range to 500MHz and to give a high input impedance.

A major innovation in this instrument is the use of a large scale integrated (l.s.i.) circuit to replace the majority of the logic. The Ferranti ZN1040E counts, stores, decodes and drives up to four seven-segment displays.

THE ZN1040E

The ZN1040E is a large scale integrated circuit fabricated using the "collector diffusion isolation" (c.d.i.) process. Fig. 1 shows the internal functions contained within this device together with the pin connections.

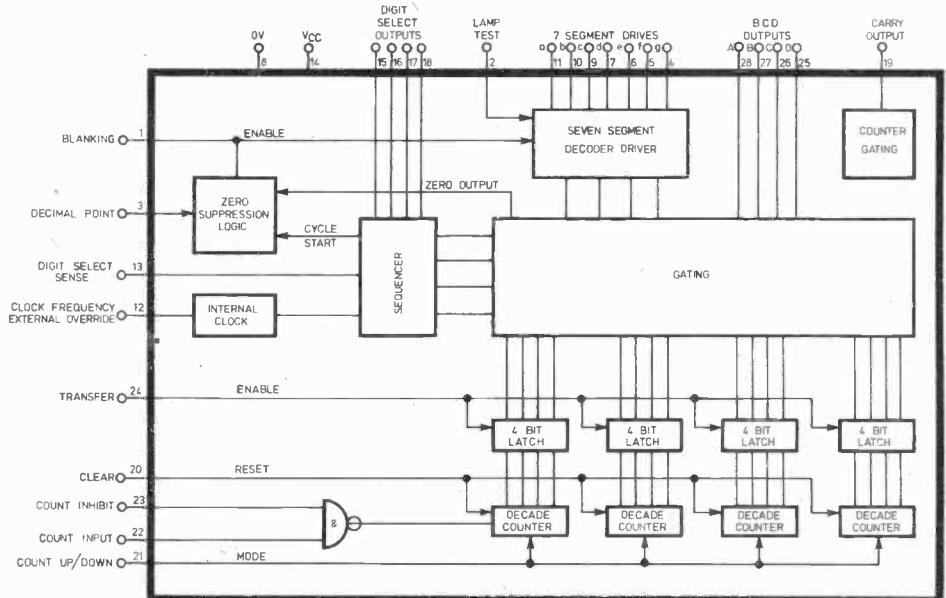


Fig. 1. The internal functions and pin connections of the Ferranti ZN1040E integrated circuit

SPECIFICATION . . .

Frequency Ranges	10.00 to 99.99kHz 100.0 to 999.9kHz 1.000 to 9.999MHz 10.00 to 99.99MHz
Input Resistance	50 ohm
Sensitivity	40mV
Input Voltage d.c. bias (max)	400V
Frequency Resolution	10Hz on Range 1
Timebase Frequency	5MHz
Timebase Ageing Rate	± 10p.p.m. per year
Timebase Temperature Stability	± 10p.p.m. (10°C to 55°C)

The device is contained in a 28-lead plastic encapsulated package. By directly driving from the multiplexed, seven-segment outputs or by decoding the binary coded decimal (b.c.d.) outputs, any contemporary display can be used.

The seven-segment drivers can sink a current of 80mA, which results in an average current of 20mA per segment when multiplexed.

When free-running, the internal multiplex clock oscillator gives a frequency of about 500kHz. This frequency can be lowered by the addition of a capacitor to pin 12. In this instrument a 0.01µF capacitor is used to give a frequency of 3kHz.

A direct drive at TTL logic levels will override the multiplexing to the driven frequency.

The ZN1040E requires a single 5V supply and consumes an internal current of 90mA. It is fully compatible with TTL devices.

CIRCUIT DESCRIPTION

A circuit diagram of the complete unit minus the power supply is shown in Fig. 2. This circuit shows the basic unit with a 50 ohm input impedance. All the circuitry is contained on two printed circuit boards: one for the logic and input circuits and one for the display. The two boards are shown as dotted lines in Fig. 2.

The circuit is more easily understood if considered in sections.

THE OSCILLATOR

The oscillator is the single most important function within a digital frequency meter as the accuracy depends almost entirely on the crystal oscillator.

Variations in temperature, crystal age and supply voltage all affect crystal frequency. Adding all the effects together, one can be faced with an error of 30Hz in 1MHz or 0.003 per cent.

Initial crystal frequency inaccuracy can be trimmed out using a capacitor (VC1). This can also be used to trim out the effects of ageing. There is admittedly room for improvement of the oscillator used in this design but it is simple and in line with the basic design concept.

A 5MHz crystal (X1) is used, this frequency being useful as temperature and mechanical stability are optimised at this frequency.

COMPONENTS . . .

MAIN UNIT

Resistors

R1-R5	270Ω (5 off)	R25	2.2kΩ
R6-R15	100Ω (10 off)	R26	470Ω
R16	2.2kΩ	R27	1kΩ
R17	100Ω	R28	3.3kΩ
R18	150Ω	R29	2.2kΩ
R19, R20	5.6kΩ (2 off)	R30	470Ω
R21	15kΩ	R31	10kΩ
R22	10kΩ	R32	1kΩ
R23	1kΩ	R33-R36	470Ω (4 off)
R24	100Ω		
All ±5% $\frac{1}{4}$ or $\frac{1}{2}$ W			

Capacitors

C1	6,800pF
C2-C4	0.05µF 6V disc (3 off)
C5	10pF mica
C6	0.01µF disc
C7	0.05µF disc
C8	50µF 10V elect
C9	0.05µF disc
C10	30pF mica
C11	0.05µF disc
C12	0.1µF 6V disc
C13	100µF 10V elect
C14	30pF mica
C15	10pF mica
C16, C17	330pF mica (2 off)
C18	0.05µF disc
C19	470pF disc
C20	0.05µF disc
C21	1,000pF 6V disc
C22-C28	0.05µF disc (7 off)
C29	2,200µF 25V elect
C30	330µF 16V elect
C31	0.1µF 6V disc
C32	100µF 6V elect
VC1	3-60pF trimmer

Transistors and Diodes

TR1-TR4	ZTX4403 (4 off)
TR5, TR6	ZTX300 (2 off)
TR7	ZTX312
TR8, TR9	ZTX500 (2 off)
TR10-TR12	ZTX312 (3 off)
D1	4.7V 400mW Zener
D2-D4	ZS170 (3 off)

Integrated Circuits

IC1	NE592	IC6	ZN7400
IC2	ZN74196	IC7	ZN7403
IC3	ZN1040E	IC8-IC14	ZN7490 (7 off)
IC4	ZN7474	IC15	78M05
IC5	ZN74123		

Display


LED1-LED4	DL707 (4 off)
-----------	---------------

Switches

S1	2 pole 4 way rotary
S2	Single pole on/off toggle
S3	D.p.d.t. mains toggle

Miscellaneous

T1	Mains primary, 8-0-8V 500mA secondary (Douglas MT207CT)
X1	5MHz crystal
SK1	BNC socket
FS1	2A 20mm fuse and holder
9-way tag strip	
Filter for display, p.c.b.s, sockets for i.c.s if required, case, nuts and bolts, standoffs, etc.	

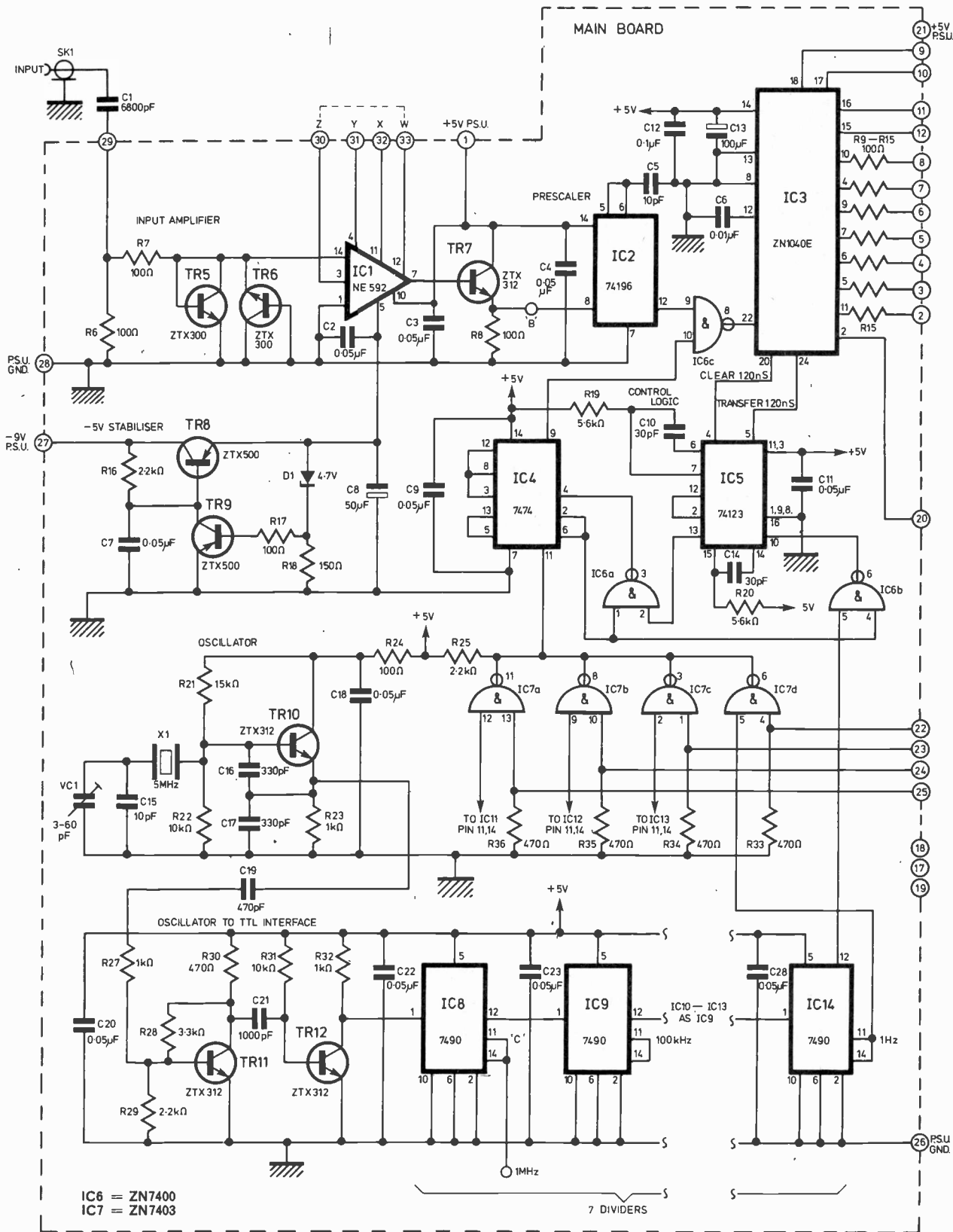

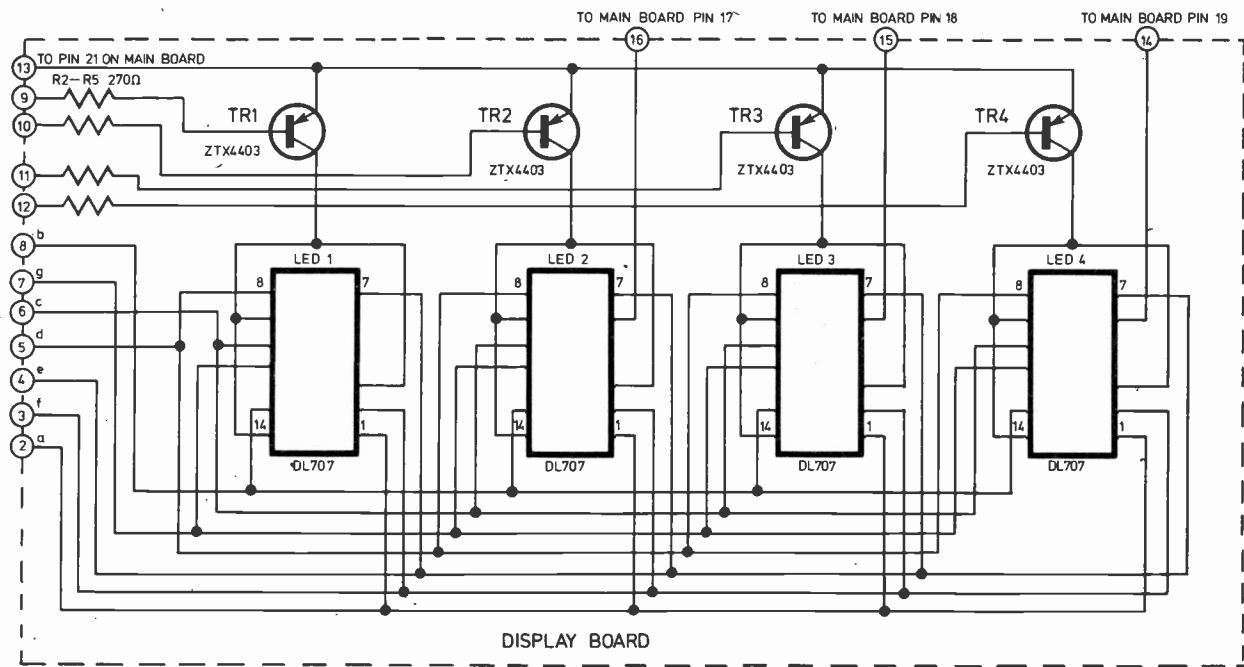


Fig. 2. Circuit diagram of the Digital Frequency Meter (50 ohm version). The dotted lines indicate the boundaries of the two printed circuit boards. The circles with numbers inside refer to the pads on the circuit boards to which wires are connected

Transistor TR10 and associated components form the basic oscillator whose output is fed to the amplifier TR11 and then to TR12 which interfaces the signal to TTL logic levels. As mentioned earlier, the frequency of this clock oscillator is set by trimming the 3 to 60pF capacitor VC1.

THE CLOCK DIVIDER CHAIN

The clock oscillator frequency is divided down to generate logic control pulses. These pulses determine the time for which the main signal gate (IC6c) is open. They also control the transfer of information to the displays and the clearing of the counters in the ZN1040E.

This four-range, four-digit counter has four orders of magnitude of full scale display, so four lengths of timing pulse are needed to cover them.

Full scale ranges are 99.99MHz (in practice limited to 50MHz by the limitations of the ZN1040E), 9.999MHz, 999.9kHz and 99.99kHz.

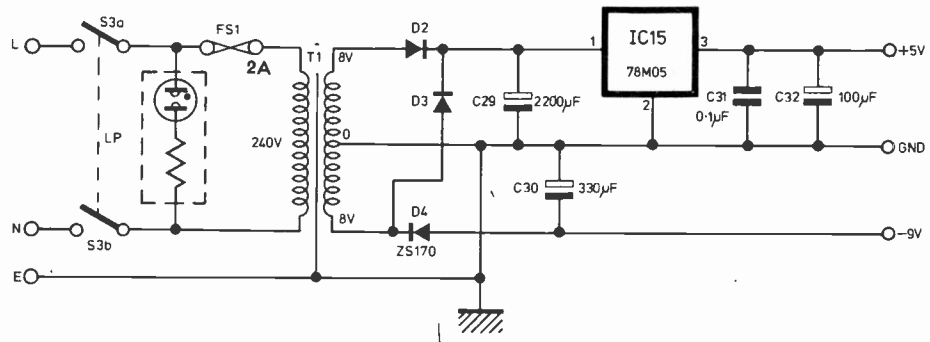
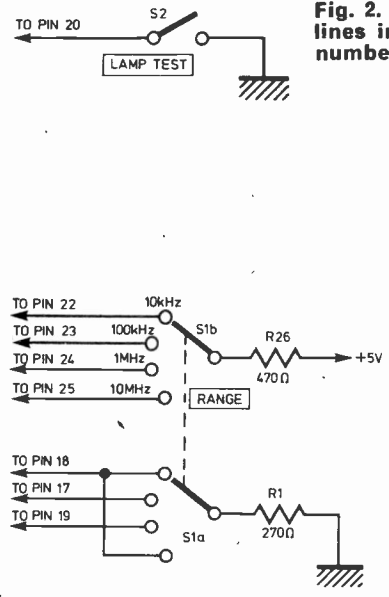


Fig. 6. Circuit diagram of the power supply which produces the 5V and -9V lines to the main board

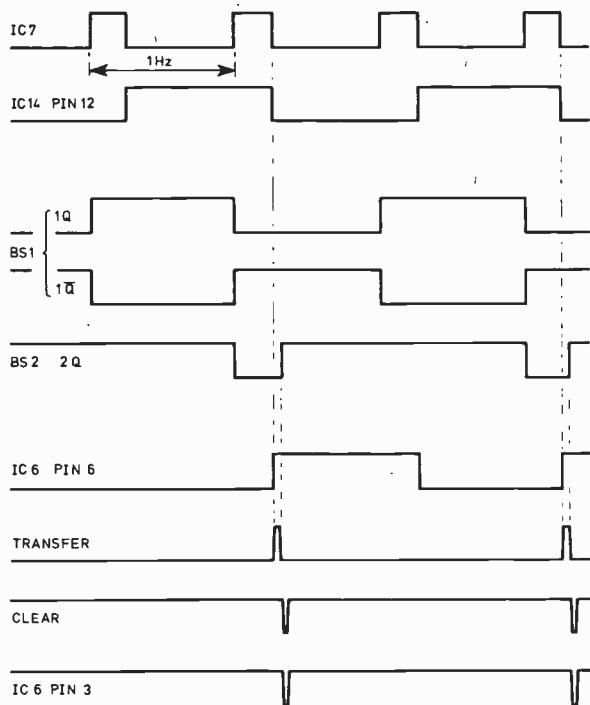


Fig. 3. The timing of the control pulses at various points in the circuit

If the counter is to display, say, 6.800MHz, then 6,800 pulses must pass to the counters. A decade divider connected to the input (IC2) divides the input frequency by ten, giving a frequency of 680.0kHz at the signal gate input (IC6c pin 9). This means that to let 6,800 pulses through, gate IC6c must be open for 1/100th of a second (10ms). The figure "6.800" will then be displayed, the range switch S1 inserting the decimal point to compensate for the prescaler.

The four ranges thus require the following gate times:

Frequency Range	Time gate open (secs)
10.00 to 99.99kHz	1
100.0 to 999.9kHz	0.1 (100ms)
1.000 to 9.999MHz	0.01 (10ms)
10.00 to 99.99MHz	0.001 (1ms)

To obtain these length pulses the 5MHz clock is divided by six and a half decade counters (IC8 to IC14). The remaining divide-by-two is used to start the transfer, clear and reset logic.

Control pulse selection is effected by selecting one of the open collector NAND gates in IC7 using switch S1b. Each of the four gates is connected to a different point in the divider chain. The non-selected gate inputs are held low by the resistors R33 to R36. The outputs of the four NAND gates are WIRED-OR connected via resistor R25.


THE CONTROL LOGIC

The control logic determines when a transfer or clear pulse is required and when the signal gate can be opened, thus ensuring a correct sequence of events. The timing diagram (Fig. 3) shows the sequence when the fastest range is selected and the circuit of Fig. 4 shows the control logic in more detail.

The output from the end of the divider chain (IC4, pin 12) is a one second high, one second low series of pulses.

Consider the state when the two bistables of IC4 have been set by a pulse from IC7, so that $2\bar{Q}$ is high and output 1Q is high. The next negative edge from the divider chain will produce a positive edge at the output of IC6b. This will trigger monostable MS2, producing a 120ns positive "transfer" pulse at

Fig. 4. The control pulse generation circuitry in more detail. The logic shown here produces the clear and transfer pulses required by the ZN1040E and the signal gate control pulses

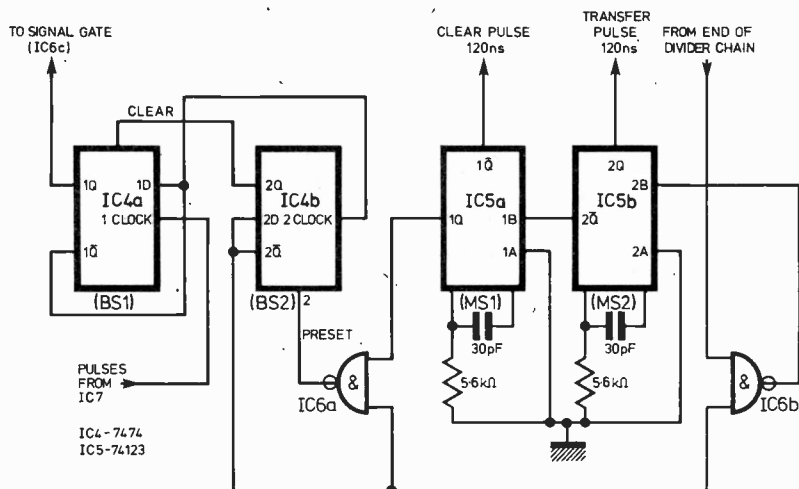

its 2Q output. This pulse transfers the information from the counters to the latches and hence to the display in the ZN1040E.

When the 2Q output of MS2 returns to low, its $\overline{2Q}$ output goes high, triggering monostable MS1 which also produces a 120ns "low" pulse. This pulse is used to clear the counters to 0000. Meanwhile the 1Q output is high for 120ns, taking the output of IC6a low which sets BS2's 2Q output high, clearing BS1 whose 1Q output goes low, thus closing the signal gate IC6c. The logic is now set for the timing period.

TIMING SEQUENCE

The 7474 is a positive edge triggered bistable. On receiving the first positive edge from IC7 after being set, BS1 is triggered. 1Q goes high thus opening gate IC6c. $\overline{1Q}$ goes low which has no effect on 2 CLOCK input as a positive edge is required.

The pulse from IC7 goes low, this having no effect on 1 CLOCK. However, when it goes high again (after the required timing period of one second) 1Q will go low thus closing the signal gate. At the same time $\overline{1Q}$ goes high which triggers BS2, setting 2Q low and clearing BS1. $\overline{2Q}$ remains high in readiness for the next negative edge which starts the whole sequence.

The action of the bistable BS1 divides the pulses from IC7 by two. A 100Hz frequency, with 2.5ms high and 7.5ms low pulses, causes the gate to be open for 10ms.

COUNTING AND DISPLAY

After the counters of the ZN1040E are cleared, the signal gate will be opened for a fixed period. The frequency of the pulses entering the count input (pin 22) will be a tenth of the frequency to be displayed. The ZN1040E has a minimum count rate of 5MHz so the measured frequency can be as high as 50MHz or greater.

The pulses at the count input are counted on the four cascaded decade counters (Fig. 1). When the signal gate is closed the control logic generates a pulse to transfer the counter information to the latches. The clear pulse then sets the counter to zero. Should there be more than 9,999 pulses, the most significant digits will be lost, only the four least significant digits of the number of pulses being retained.

This feature is most useful when measuring a frequency with more than four significant digits. If, say, 29.215MHz is to be measured, the instrument can be deliberately over-ranged to read 9.215MHz, the "2" being remembered from the measurement on the next range.

An internal clock generates the multiplexing signals which control the gating that scans the latches, and addresses the digit select output.

When any particular digit is addressed, the latch information relevant to that digit is presented at the seven-segment decoder/driver output. As each display is addressed with a one-in-four time slot, the average power supplied to each segment is 0.25 the peak power.

Resistors R9 to R15 are used to limit the output current to about 25mA peak, 6mA per segment average is adequate for most applications.

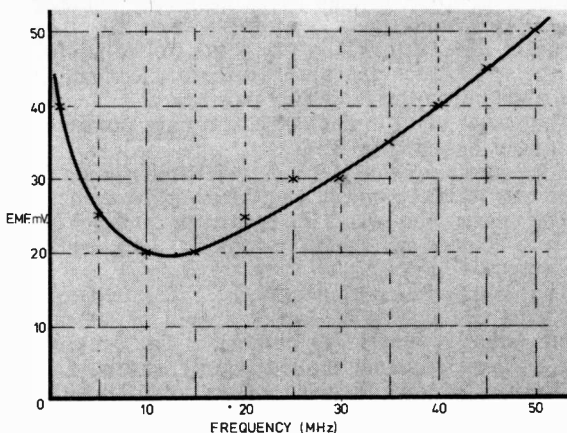


Fig. 5. Frequency plotted against sensitivity for the NE592 integrated circuit amplifier

The frequency of the internal clock can be lowered by the addition of a capacitor or overridden by driving pin 12 with an external TTL clock. A capacitor of $0.01\mu\text{F}$ has been used in this design to give a multiplex frequency of 2.8kHz.

The displays used in this meter are four DL707 (LED1 to 4). Being common anode i.e.d. displays, they are suitable for driving directly from the ZN1040E, i.e. without interface circuitry. The anode pull-up transistors TR1 to TR4 are used because of the high currents that are required if an "8" is to be displayed (all segments used). A current of 200mA peak can flow in this case. Resistors R2 to R5 limit the current flowing into the bases of these transistors.

Decimal point selection is carried out using the same switch as is used for the gate period selection (S1).

PRESALER CIRCUIT

In order to measure frequencies higher than the 5MHz limit imposed by the ZN1040E, it is necessary to pre-divide the input frequency. IC2 is a 74196 decade divider capable of operating at 50MHz. It is wired as a divide-by-two then a divide-by-five. The 10pF capacitor C5 connected to the divide-by-two output (pins 5 and 6) acts as a load to prevent instability under no-signal conditions.

Though the frequency capability of the ZN1040E is 5MHz and of the 74196 50MHz, these are minimum figures; a typical pair of i.c.s will operate above this range.

INPUT AMPLIFIER

The input impedance of the instrument as shown in Fig. 2 is 50 ohm. If a high input impedance is required, then the buffer board to be described next month will be required.

A capacitor at the input (C1) protects the input from d.c. bias potential up to 400V. Two transistors (TR5, TR6) connected as diodes are used to limit the input voltage to IC1. Transistors are used as a

cheap alternative to high speed switching diodes. If diodes are used here they must have a reverse recovery time of less than 6ns if the full capabilities of the instrument are to be realised. Resistor R7 limits the current in these two transistors.

The power input to the instrument must not exceed the power handling of R6.

The input amplifier IC1 is a wideband video amplifier type NE592 connected in the inverting mode.

The emitter follower TR7 is used to interface IC1 to IC2. Under no signal conditions, 2.1V will be measured at "B".

The i.c. has four outputs (W, X, Y, Z) used to set the gain. By linking X and Y a gain of 400 at a bandwidth of 40MHz is obtained. The graph of Fig. 5 shows frequency plotted against sensitivity.

Shorting W and Z gives a gain of 100 with a 90MHz bandwidth. A 10k Ω variable resistor between X and Y allows a variable gain of unity to 400.

The -5V line required by the NE592 is supplied by the simple stabiliser (TR8 and TR9) fed with -9V.

THE POWER SUPPLY

The power requirements of the instrument are 5V at 500mA, and -5V at 30mA. The power supply and stabiliser for the +5V line is shown in Fig. 6. The -9V line is fed to the stabiliser on the main printed circuit board which produces the -5V for IC1.

The current drain is 350mA with no-signal input and 500mA with all eights displayed.

Next month: Constructional details, high impedance buffer and v.h.f. prescaler



BOOK REVIEWS

INTRODUCTION TO QUANTUM ELECTRONICS

By P. A. Lindsay

Published by Pitman

202 pages, 240mm \times 160mm. Price £6.00

QUANTUM Electronics is no longer confined to the scientific laboratory. An important and growing technology has emerged based on the practical utilisation of electromagnetic radiation interaction with matter on the atomic scale through the medium of devices such as lasers. The applications of lasers are likely to increase in the future and already they play an important part in industry and in the medical field.

Thus the subject covered by this book could be a very rewarding one for the engineering student to pursue. The term "Introduction" might be misleading. This is an advanced level textbook and it explores the subject in a rigorous analytical manner with extensive use of maths. The author is Professor of Physical Electronics at King's College, University of London.

D.D.R.

MULLARD DATA BOOK 1976

176 pages, 134 \times 96mm. Price \$50p.

THIS is a handy pocket reference containing abridged data on the Mullard range of components for use in consumer applications, including valves, semiconductor devices, TV tubes, capacitors and resistors. Equivalents and comparables are also listed.

For easy reference different coloured pages are used for each of the main sections; blue for semiconductors, yellow for picture tubes and receiving valves and green for capacitors and resistors.

The book is obtainable from specialist components stockists or direct from Technical Press Ltd., Freeland, Oxford, OX7 2AP.

NEWS BRIEFS

Summer School for Teachers

THE Department of Electrical Engineering Science at Essex University will be holding its annual Electronics Summer School for teachers during the week July 12-16 and, this year, three courses *Linear Circuit Design*, *Digital Circuit Design* and *Small Computer Systems* will be run simultaneously.

The Linear Circuit Design course is concerned with the use of transistors and operational amplifiers in analogue applications and the basic circuits of a hi-fi amplifier are investigated in detail.

The Digital Circuit Design course concentrates on the use of the transistor as a switch and develops a design using integrated logic circuits; a digital patchboard is used to introduce the concepts of combinational and sequential logic design.

Small Computer Systems is a new course which should be of interest to mathematics teachers as well as those interested in electronics; the aims of the course are to introduce a typical small computer, the PDP-8, to investigate how it is used and to discuss its function in schools.

Further information on the Summer School can be obtained from Mr R. J. Mack at the Department of Electrical Engineering Science, University of Essex, Wivenhoe Park, Colchester CO4 3SQ.

POINTS ARISING

HOW INVENTIVE ARE YOU COMPETITION

Full results will appear next month. Unfortunately it was not possible to include them in this issue, as originally hoped.

DIGI-PROBE (April 1976)

In Fig. 7 (p. 292) the resistor on the left-hand edge of the top board should be annotated R16. Also the lead from the junction of R15, R16 and R17 should go to IC2 pin 12 and not as shown to pin "e" on the DL704 display. The lead from pin "e" of the display should be connected to the other side of R16.

OPTO-COUPLED R.P.M. METER (February 1976)

Some constructors have had difficulty in obtaining the MS4A photo-cell specified. This can be obtained from: Davian Electronics, PO Box 38, Oldham, Lancs, OL2 6XJ.

This is an error on the p.c.b. master (page 146). The track in the top left-hand portion of Fig. 2 which connects the collector of TR1 to the positive supply line (shorting out R2) should be removed.



BY FRANK W. HYDE

SOVIET VENUS PROBES

The Soviet satellites *Venera 9* and *Venera 10*, continuing their orbiting studies of Venus, have measured the temperature of the clouds near their upper boundary. This was at a level of -35 degrees centigrade. Records of the glow on the night side of the planet indicate that the spectrum differs from that of the Earth glow.

The electron density on the day side is much higher than the night side and about 90 per cent less than that of the Earth. Another feature is that the ionosphere of Venus appears to be closer to the planet and much thinner than that of the Earth.

The pictures that have been sent back so far have encouraged the Soviet investigators to examine the radio method of exploring through the cloud layer. Although some five years ago Yuri Spiridinov had devised a system of measuring relief using data sent back by *Mariner 5*, this was not pursued because the general consensus of opinion was that the surface of the planet would be mainly smooth.

The technique involves the critical refraction layer of the Venusian atmosphere about 30 kilometres or so above the surface. The angle of refraction of the radio beam is so great that it must also be reflected by the surface. Using the split beam technique, similar holography in the visible spectrum, one half of the beam passes below the critical level and the other half above the critical level.

A signal sent from Earth will be received by a space probe on the dark side, and will be the sum of the direct and reflected wave. Thus, a picture can be built up from the

recordings and the result is, when computerised, a picture of the surface in the radio frequency spectrum. More than one line scan is needed of course, but since Venus moves very slowly on its axis, 243 terrestrial days, and the probe needs to be in radio shadow, a line by line scan is easily obtained.

Although the original data received from *Mariner 5* was insufficient to produce a full picture, nevertheless the contour was shown at two frequencies. The indicated variation of height ranged from 0.3 to 2.7 metres. This agreed very well with the pictures that were received from the probes landed on the surface. This technique could be applied in a number of other cases and may prove a very useful tool of the future.

OUTER BOUNDARY

Spacecraft *Pioneer 10* crossed the orbit of Saturn on February 10 and headed out to the boundary of the solar system. On that date it was some 1,000 million miles from the Earth. Its velocity was about 26,000mph.

The equipment has continued to function normally and data continues to be sent back. It is considered that with the sensitivity of the Deep Space Network, *Mariner 10* will be in communication until it reaches the orbit of Uranus and maybe further. The orbit of Uranus is about 2,000 million miles from the Earth.

POWERSAT

The American Congress now has the results of Boeing's power generation satellite proposals. This will require some 30 spacecraft, each of which will have a system of converting solar energy to microwaves which are beamed to Earth. The system has been described in detail in an earlier Spacewatch.

The Earth stations will be situated on the equator in desert areas such as Nevada in America. Provision will have to be made for heavy lifting transporters to raise some of the structures. These transporters will be about 90ft high with a cluster of 21 engines around a 100ft diameter base. The cost, if the pilot experiments are successful, would be something of the order of 60,000 million dollars over a period of 30 years.

SET BACKS

A number of casualties have resulted from the new American finance cuts in the space budget. Some of the cuts mean that decades may pass before missions can be set up again.

It is the Space Science area that has suffered most. A Jupiter orbiter probe for launch in 1981 has been deferred. The Moon orbiter and the fly-by for Comet Encke have also been abandoned. Although, here there is a possibility that *Helios* could be diverted so that the opportunity is not lost.

A tragic loss to astronomy is the withholding of further finance for the 94in orbiting telescope. It will not be possible to advance this project for at least 18 months.

The Venus *Pioneer* programme which will release probes for different depths of penetration into the Venusian atmosphere will still go ahead.

The mission which was planned for a journey via Jupiter, Saturn, Uranus has been postponed and this is the one which means decades in terms of delay because the astronomical positions will not be suitable. This was the "sling-shot" mission where the precise position of the trajectories would have enabled the gravitational effects to help the vehicle on its way.

FUTURE PLANS


However, some good news is available and the studies planned for the next 11-year period of solar activity will go ahead. The mission will cost 85 million dollars using a 3,000lb satellite which will be known as the Solar Maximum Mission. This will be the first modular design to carry instrumentation retrievable by Shuttle.

At the time of going to press, four launchings have taken place this year. They are: *Helios B*, the second of the German Solar probes; Communications Technology Satellite, a joint effort of NASA and Canada; *Intelstat IV-A-B*, owned by International Telecommunications Organisation and *Marisat*, launched for Comsat General Corporation. *Marisat-B* will follow in May and *Marisat-C* later in the year.

The RCA *Satcom*, second of the domestic communications satellites, was due for launch in March. A NATO satellite *3-A* will be in geostationary orbit in April for North Atlantic Treaty Organisation Relay. LAGEOS, which is Laser Geodynamic Satellite for predicting ocean surface conditions and circulating patterns. It will also be concerned with earthquake hazards and is due for launch in April. *Comstar 1-A* and *Comstar 1-B* will be launched in May and August.

Finally, the *Tiros* Operational Satellite for the National Oceanic and Atmospheric Administration will be placed in orbit in September.

Using CMOS digital I.C.s

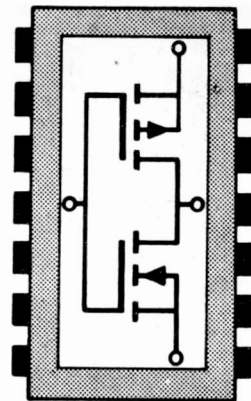

By D.B. JOHNSON-DAVIES & A.M. MARSHALL B.A.

PART 5

THIS part concerns electronic switches and oscillators with practical circuit examples.

MONOSTABLES

The monostable is basically a single-shot oscillator. It produces an output pulse of constant width independent of the duration of the input pulse, thus curtailing long pulses and extending short ones. The simple differentiating circuit of Fig. 5.1 performs the first function, as shown by the waveforms in (a). The period of the output pulse depends on the transfer voltage V_T of the inverter as the time constant RC charges from V_{SS} to V_{DD} , and will vary between devices from about 0.4RC seconds with $V_T = 30$ per cent of V_{DD} to 1.2RC seconds with $V_T = 70$ per cent of V_{DD} . If, however, the input pulse is shorter than this period, as in the waveforms (b), the capacitor does not charge fully to V_T and the output pulse will be constrained to the length of the input pulse. In other words this circuit will only act as a pulse shortener.

This differentiating circuit can be used as a simple delay unit, and Fig. 5.4 shows a frequency doubler using two such circuits, one triggering on each edge of the clock pulse.

For the circuit of Fig. 5.1 to function as a monostable, it must be made to latch on until the full output pulse has been delivered. This is achieved in Fig. 5.2 by using a NOR gate to hold the input to the differentiating circuit "high" until the capacitor has charged to V_T . This excellent monostable does however suffer from the variation in period between devices, mentioned above.

The circuit of Fig. 5.3 can be used if a more predictable period is needed. Two gates fabricated on the same chip will have closely matched transfer voltages, and by using two identical RC time constants, the between device variations are effectively cancelled out.

SCHMITT TRIGGERS

At the interface between analogue and digital circuits comes the Schmitt trigger, which gives a snappy "yes" or "no" for an undecided analogue input signal. The perfect Schmitt has a characteristic as represented in Fig. 5.5. The Schmitt, if presented with a slowly rising input voltage, will switch sharply

off at V_{UT} (the upper threshold voltage) and will not switch back on again until the voltage has fallen below V_{LT} (the lower threshold voltage). This difference $V_{UT} - V_{LT}$, is called the hysteresis, and it prevents the circuit from going into oscillation when the input is held at one of the thresholds.

One way of obtaining hysteresis is to make the transfer point unstable by applying positive feedback, as in Fig. 5.6. The feedback is equal to R_1/R_2 , and this should be less than the combined gain of the inverters for switching to occur. The average threshold voltage V_T can be varied, if required, by connecting a resistor R_3 to V_{DD} for V_T of greater than $V_{DD}/2$, and to V_{SS} for V_T less than $V_{DD}/2$.

Another type of Schmitt trigger, unique to CMOS, makes use of the variation of the transfer characteristic of multi-input gates described earlier. Fig. 5.7 shows a circuit with a hysteresis of about 30 per cent of V_{DD} . This can be reduced to 15 per cent of V_{DD} if required by taking one of the three inputs of gate A to V_{DD} . The other two gates are arranged as a familiar R-S latch.

TRANSFER CURVE

If one of the inputs of a two-input gate is held at somewhere between the two logic levels (i.e. between 3 and 7 volts with a 10 volt supply) the transfer curve for the other input is altered as shown in Fig. 5.8. The Schmitt triggers of Fig. 5.9 make use of this property of CMOS gates. The circuit in (a) using NAND gates triggers at above $V_{DD}/2$, whereas using NOR gates as in (b) gives trigger levels below $V_{DD}/2$. In both circuits the hysteresis can be varied from 0 to 40 per cent of V_{DD} by altering V_X .

SCHMITT PACKAGES.

As an alternative to constructing Schmitt triggers from discrete gates, the CMOS family contains a few ready-made Schmitt packages. The 4093 contains four 2-input NAND gates each with Schmitt circuits on both inputs. The 40106 is a hex-inverter with Schmitt inputs, and the package outline is the same as the 4069. In both these devices V_T is approximately $V_{DD}/2$, and the hysteresis is 2V with a 10V supply.


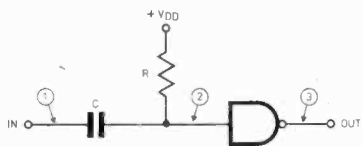
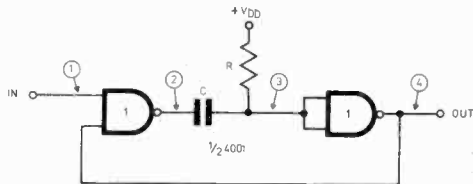


Fig. 5.1. Simple differentiating circuit. The period of the output pulse depends on the transfer voltage V_T of the inverter. For explanation of waveshapes below, see text

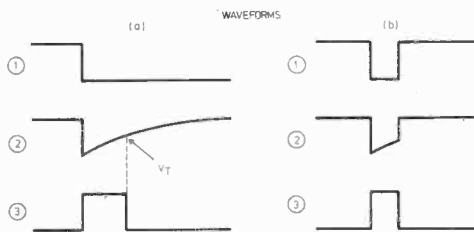

WAVEFORMS

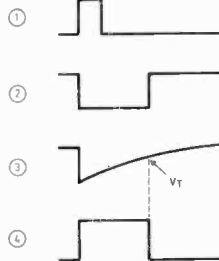


Fig. 5.2. Monostable circuit achieved by connecting a NOR gate to hold "up" the input to the differentiating circuit until the capacitor has charged to V_T

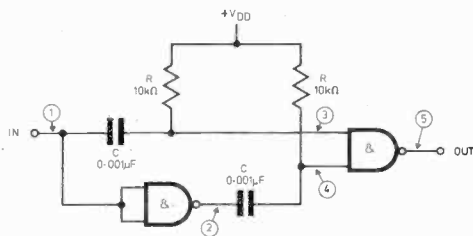


Fig. 5.4. Frequency doubler using two differentiating circuits, one triggering on each edge of the clock pulse, as can be seen from the waveshapes

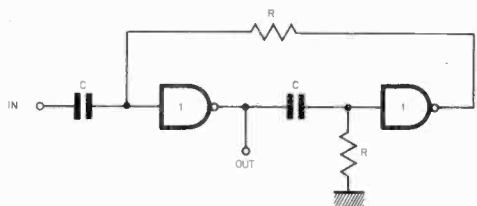
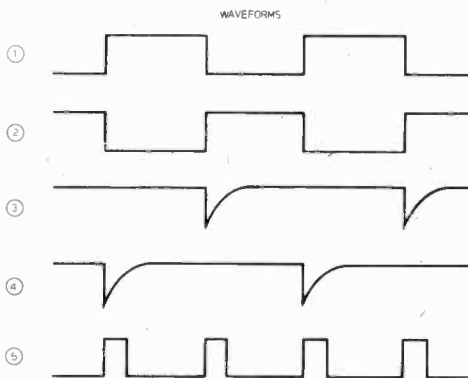


Fig. 5.3. With gates fabricated on the same chip and identical RC time constants output pulse periods can be more accurately predicted

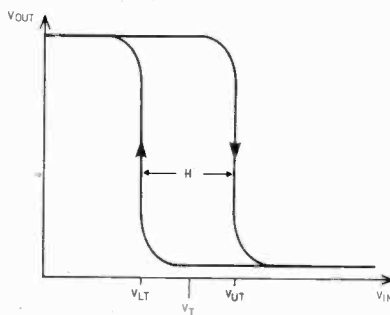


Fig. 5.5. The ideal Schmitt trigger characteristic. It can be defined either in terms of V_{LT} and V_{UT} (the lower and upper thresholds) or in terms of V_T and H (the average threshold voltage and hysteresis)

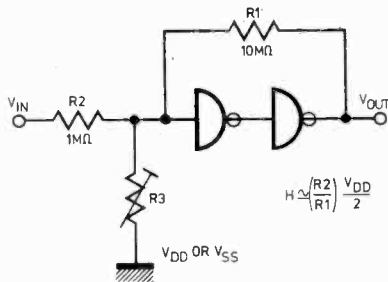


Fig. 5.6. Schmitt trigger formed from two inverters with positive feedback. R1 can be from 1 to 100 times R2. With the values shown (R3 not connected) and a supply of 10V, $V_{LT} = 5.0V$ and $V_{UT} = 5.8V$ approximately

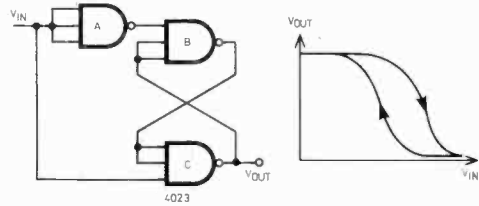


Fig. 5.7. Schmitt trigger using three-input gates

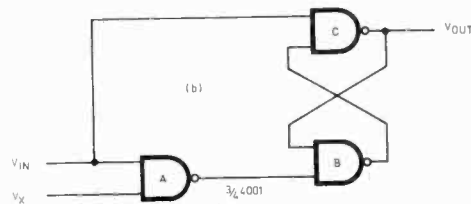
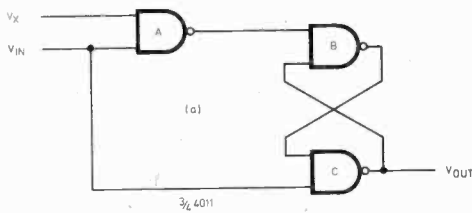


Fig. 5.9. Schmitt trigger circuits with hysteresis determined by the voltage V_X . (a) With NAND gates the circuit triggers at a voltage greater than $V_{DD}/2$. (b) Equivalent circuit with NOR gates triggers at below $V_{DD}/2$

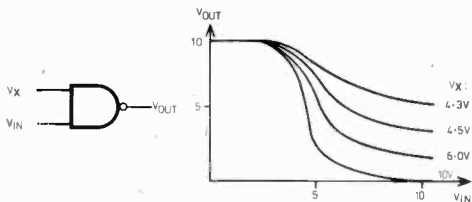


Fig. 5.8. Transfer curve variations for non-logic levels V_X at one input of a two-input NAND gate. The supply is 10V

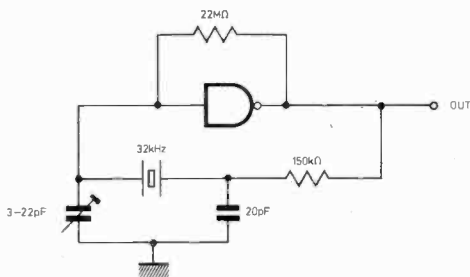


Fig. 5.10. Crystal oscillator


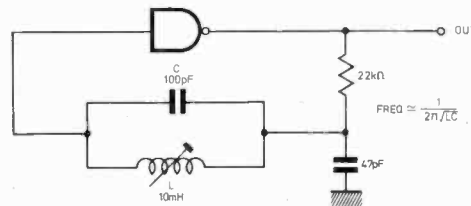


Fig. 5.11. Showing an L/C oscillator the frequency of which being stable to within about 0.001 per cent for a 2V change in the supply voltage

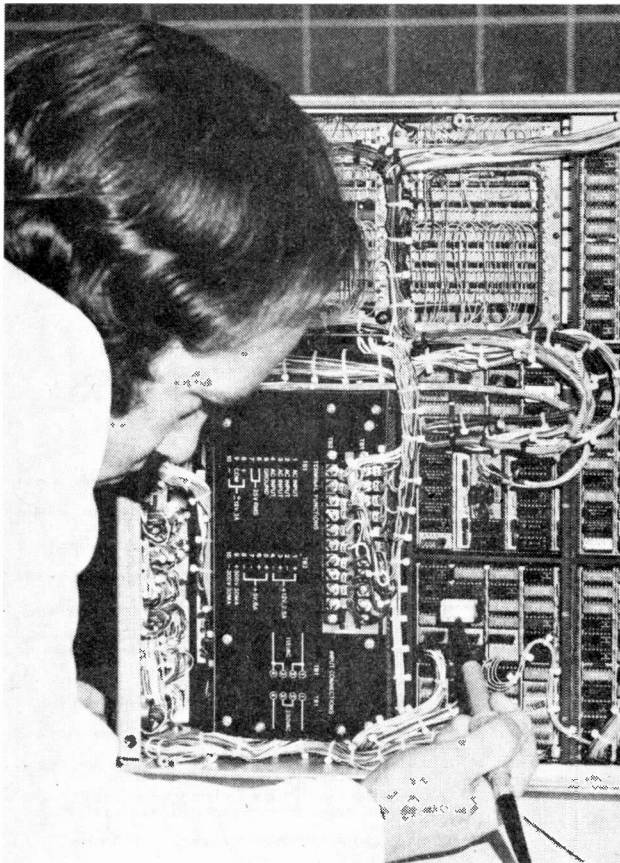

This hobby brings big rewards.

A soldering iron and a screwdriver. If you know how to use them, or at least know one end from the other, you know enough to enrol in our unique home electronics course.

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.


You build, see and learn as, step by step, we take you through all the fundamentals of electronics and show you how easily the subject can be mastered and add a new dimension not only to your hobby but also to your earning capacity.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write, at any time, for advice or help during your work. A Certificate is given at the end of every course.


1

Build an oscilloscope.

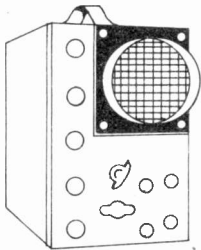As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.




2

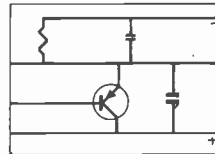

Read, draw and understand circuit diagrams.

In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.

3

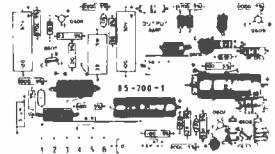

Carry out over 40 experiments on basic circuits.

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

To find out more about how to learn electronics in a new, exciting and absorbing way, just clip the coupon for a free colour brochure and full details of enrolment.

PLUS FREE GIFT!



ALL STUDENTS ENROLLING IN OUR COURSES RECEIVE A FREE CIRCUIT BOARD ORIGINATING FROM A COMPUTER AND CONTAINING MANY DIFFERENT COMPONENTS THAT CAN BE USED IN EXPERIMENTS AND PROVIDE AN EXCELLENT EXAMPLE OF CURRENT ELECTRONIC PRACTICE


Brochure without obligation to:
**BRITISH NATIONAL RADIO
 & ELECTRONICS SCHOOL, Dept. EL56**
 P.O. Box 156, Jersey, Channel Islands

NAME _____

ADDRESS _____

(Block caps please)

Greenbank Electronics Established 1970

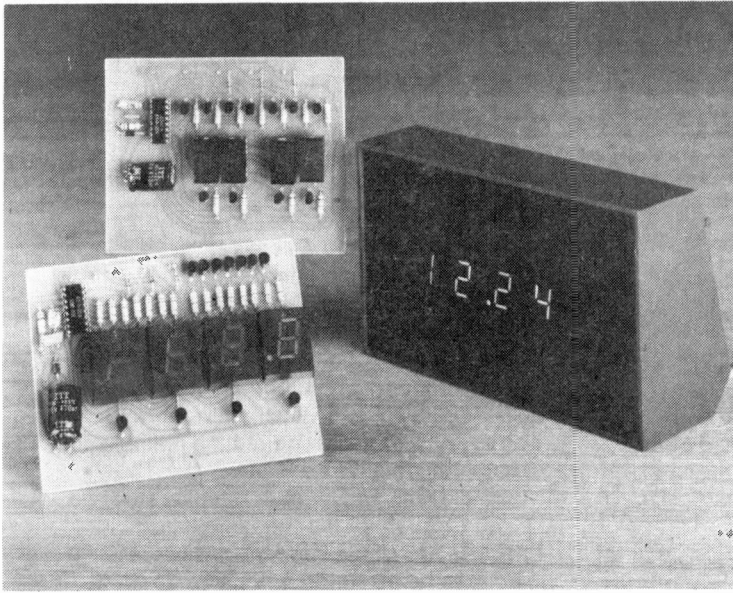

The illustration shows the two P.C.B. module kits already assembled, one has 8mm high digits, the other has 16mm high digits. Also shown is an example of a completed clock.
Free on request: Data on AY-5-1224 and MK50253 clock chips, 4 and 6 digit alarm clock suggested circuits, quartz crystal timebase, and L.E.D. displays (if you can send an S.A.E., it makes things a little easier for us).

CLOCK CHIPS

AY-5-1224A 4 digit basic clock £3.50 MK 50253 4/6 digit alarm/snooze £5.50

ECONOMY RED LED DISPLAYS ('Class II' quality, but guaranteed by us, fully returnable if not satisfied).
 DL-707E/DL-704E 8mm (0-3") 70p. DL-727E/DL-728E 12mm (0-5") Double Digit £1.80. DL-747E/DL-750E 16mm (0-6") —£1.50.

CMOS WITH DISCOUNTS! (Any mix: disc. 10% 25+, 25% 100+)

4000/14000	0-15	4023/14023	0-15	4043/14043	0-80	4066/14066	0-55	4096/—	0-85	14515/4515	2-55	14543/—	1-50
4001/14001	0-15	4024/14024	0-80	4044/14044	0-75	4067/—	2-95	4097/—	2-95	14516/4516	1-10	14549/—	2-95
4002/14002	0-15	4025/14025	0-15	4045/—	1-15	4068/14068	0-15	4099/—	1-50	14517/—	5-40	14552/—	8-05
4006/14006	0-95	4026/—	1-40	4046/14046	1-10	4069/14069	0-15	—	—	14518/4518	1-00	14553/—	3-50
4007/14007	0-15	4027/14027	0-45	4047/—	0-70	4070/14070	0-15	—	—	14520/4520	1-00	14554/—	1-20
4008/14008	0-75	4028/14028	0-70	4048/—	0-45	4071/14071	0-15	—	—	14521/—	2-00	14555/4555	0-70
4009/14009	N/S	4029/—	0-90	4049/14049	0-45	4072/14072	0-15	4700/—	1-50	14522/—	1-50	14556/4556	0-70
4010/14010	N/S	4030/14030	0-45	4050/14050	0-45	4073/14073	0-15	7083/—	4-25	14524/—	N/S	14557/—	3-20
4011/14011	0-15	4031/—	1-80	4051/14051	0-75	4075/14075	0-15	—	—	14526/—	1-50	14558/—	0-90
4012/14012	0-15	4032/14032	0-85	4052/14052	0-75	4078/14078	1-25	—	—	14527/4527	1-20	14559/—	2-85
4013/14013	0-45	4033/—	1-10	4053/14053	0-75	4077/14077	0-15	—	—	14528/4089	0-85	14560/—	1-55
4014/14014	0-80	4034/14034	1-55	4054/—	0-95	4078/14078	0-15	14501/—	0-15	14529/—	1-30	14561/—	0-45
4015/14015	0-80	4035/14035	0-95	4055/—	1-05	4081/14081	0-15	14502/4502	1-00	14530/—	0-65	14562/—	5-25
4016/14016	0-45	4036/—	1-80	4056/—	1-05	4082/14082	0-15	14505/—	3-30	14531/—	1-25	14566/—	1-20
4017/14017	0-80	4037/—	0-75	4057/—	20-35	4085/—	0-55	14506/—	0-35	14532/4532	1-80	14572/—	0-35
4018/—	0-80	4038/14038	0-85	4059/—	10-60	4086/—	0-55	14508/4508	2-35	14534/—	6-00	14580/40180	6-00
4019/14519	0-45	4039/—	2-85	4060/—	0-90	4089/—	0-85	14510/4510	1-10	14536/—	2-85	14581/40181	3-05
4020/14020	0-90	4040/14040	0-85	4061/—	18-40	4093/14093	0-65	14511/4511	1-25	14537/—	15-25	14582/40182	1-15
4021/14021	0-80	4041/—	0-65	4062/—	N/S	4094/—	1-50	14512/—	1-05	14539/—	1-05	14583/—	0-71
4022/14022	0-75	4042/14042	0-85	4063/—	0-90	4095/—	0-85	14514/4515	2-55	14541/—	1-80	14585/—	1-45

Terms: C.W.O. Add VAT to all prices at 8%. Post etc., U.K. 10p per order, export 75p (no VAT). All orders processed on day of receipt

GREENBANK ELECTRONICS (Dept. W4P)
 94 New Chester Road, New Ferry, Wirral, Merseyside, L62 5AG, England.
 Tel:—051-645 3391

CJL

CJL LTD. P.O. BOX 34, CANTERBURY, CT11 1YT
 ALL PRICES INCLUDE P&P AND V.A.T.


ANTEX SOLDERING IRONS

(with slide on & off bits)	
15W 'C' miniature irons	£2.30
3/32" 1/8" 3/16" bits—each	£0.45
'C' Elements	£1.10
18W 'G' miniature irons	£2.50
3/32" 1/8" 3/16" bits—each	£0.45
'G' Elements	£1.30
15W 'CCN' Low leakage irons	£2.75
3/32" 1/8" 3/16" bits—each	£0.45
'CCN' Elements	£1.50
25W 'X25' Low leakage irons	£2.30
3/32" 1/8" 3/16" bits—each	£0.47
'X25' Elements	£1.15
'SK1', 'SK2', Soldering Kits	£3.85
ST3 Stands for all models	£1.10
SOLDER in Bib dispenser	£0.45

WIRE STRIPPER & CUTTER

£0.85	
HAND DRILLS Leytool precision, compact, 5/16" chuck	£3.99
AERIALS Extend 15-120cm	£1.50
CASSETTE 'Head Demagnetisers' Shaped pole—saves time	£3.65
EARPHONES Stethoscope	£1.25
Crystal earphone, lead & plug	£0.65
Headphone, 2, 000 n.	£3.20
INTERCOMS 2-station	£6.35
MICROPHONES Dynamic	£2.15
PRINTED CIRCUIT KITS -All items for producing p.c.'s	£3.99
SIGNAL INJECTOR -Audio through video signals, self contained	£4.25
STEREO HEADPHONES 8n	£4.85
SPEAKERS -75mm dia. 8n	£1.00

TIDY TRAY TOOL BOX

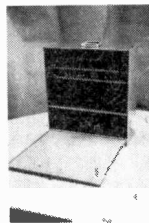

Detachable tool box lid, hardboard line, doubles as a portable working surface. 18 transparent standard size "A" component drawers. Extension plug and socket for Soldering iron or small portable tools. Substantial steel construction, finished in blue hammer enamel. Overall size: 18in high x 16 1/2in deep x 7in wide.

Price: £8.75 including VAT
 Postage and package: £1.25 extra.

WOOD-JEFFREYS LTD.

North Road, Kirkburton, Huddersfield HD8 0RJ
 Telephone: Kirkburton 3323

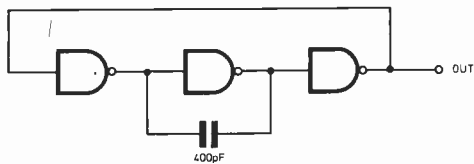


Fig. 5.12. Ring oscillator which uses only one capacitor which is charged and discharged through the inverters

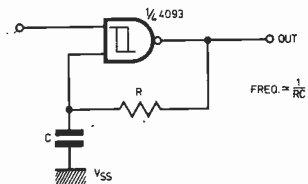


Fig. 5.13. Schmitt used as an oscillator

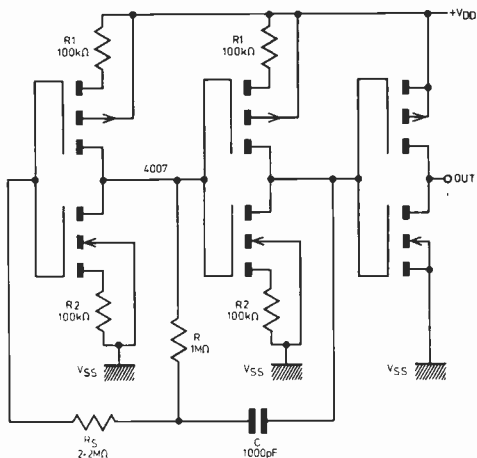


Fig. 5.14. Low-power astable with current limiting resistors R₁ and R₂. These can be any value up to about 470kΩ. With the values given the frequency is about 450kHz

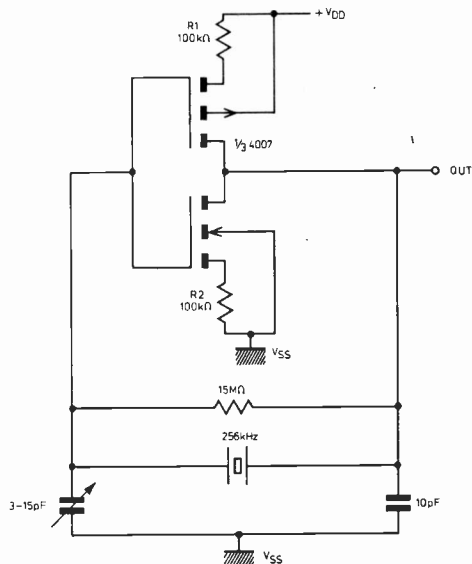


Fig. 5.15. Low-power crystal oscillator. Frequencies of up to 10MHz are possible with a supply of 15V

STABLE OSCILLATORS

For more critical applications, stable oscillators can be made by connecting a crystal or L-C network as a feedback network across an inverter. A crystal oscillator circuit is shown in Fig. 5.10, and crystals resonating at up to several megahertz can be accommodated by altering the values of the two capacitors. Fig. 5.11 shows an L-C oscillator, the frequency being stable to within about 0.001 per cent for a 2V change in the supply voltage.

The ring oscillator of Fig. 5.12 uses only one external capacitor which is charged and discharged through the MOSFETs of the inverters. It will oscillate at between 1kHz and 10MHz for values of C from 1μF to 1pF.

The Schmitt trigger will operate as an oscillator giving a range of 1Hz to 1MHz with suitable values of R and C (Fig. 5.13). Six discrete oscillators can be built with one 40106 package.

LOW POWER

Where power consumption is critical, as in battery-powered circuits, it may be worth modifying these simple oscillator circuits given in the previous part in order to conserve a few milliwatts.

The quiescent current drawn by a gate is negligible; of the order of nanoamps. The major part of the dissipation of a CMOS oscillator occurs during the transition between states, due to the charging and discharging of circuit capacitances, and therefore increases with frequency. This dissipation can be reduced at the expense of decreased output drive capability by the addition of resistors between the source and V_{SS}, and the drain and V_{DD} of the MOSFET pair, thus decreasing the current that flows during conduction. The 4007 dual complementary pair plus inverter provides access to the individual MOSFETs and so can be used in such circuits.

Fig. 5.14 shows a low-power oscillator constructed from a 4007 package, with a frequency of about $1/2.7RC$. The power consumption at 10 volts falls from about 5mW with R₁ and R₂ shorted as in the simple oscillator circuit, to about 200μW with R₁ = R₂ = 100kΩ. Due to the increased output impedance the oscillator is very sensitive to loading, and so an inverter is added as an output stage.

The crystal oscillator of Fig. 5.15 requires only about 30μW with a supply of 5 volts, and the presence of R₁ and R₂ has the added effect of stabilising the frequency against variations in supply voltage.

continued on page 408

**FREE
BOARD
PROJECT**

ADD-ON CAPACITANCE UNIT

By R.W. LAWRENCE B.Sc.



THE measurement of capacitance has always been more difficult than the measurement of resistance, voltage, etc.

The traditional method of performing the operation is with some form of impedance bridge, but this can involve a lengthy ritual of balancing and adjustment to obtain a final reliable reading.

The circuit to be described will allow instant measurement of capacitance from less than 1pF to greater than 10 μ F, displaying the result on an ordinary multimeter.

THEORY OF OPERATION

The add-on capacitance unit uses simple, conventional techniques and relatively few components. Referring to the block diagram (Fig. 1) it will be seen that there are three basic sections: an oscillator, a virtual earth amplifier, and a precision rectifier arrangement whose output feeds a voltmeter (a multimeter set to a range whose f.s.d. lies between 1-3V).

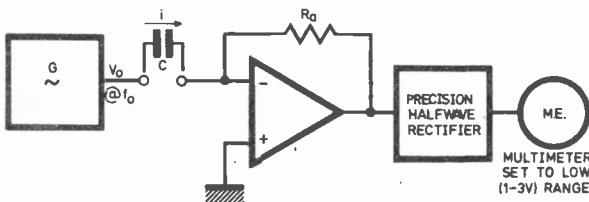


Fig. 1. Block diagram of the Add-on capacitance unit

If we assume the sinewave oscillator is set to a frequency f_0 , its output voltage is V_0 , and the unknown capacitance value is C , then simple theory yields the current flowing into the virtual earth as being:

$$i = \frac{V}{Z} = \frac{V_0}{1/2\pi f_0 C}$$

This current is directly proportional to the admittance (the reciprocal of impedance) of the capacitor which, in turn, is proportional to the value of the capacitance and the frequency.

VIRTUAL EARTH

Since the current cannot flow into the inverting input of the operational amplifier, an equal and opposite current from the output will flow via the feedback resistor R_a such that the two cancel out at the inverting input providing the so-called "virtual earth".

The voltage appearing at the output of the op. amp. will thus be $i \times R_a$. However, since i itself is proportional to capacitance and frequency (of the oscillator) and the output of the virtual earth amplifier is proportional to i , it follows that this output voltage will also be proportional to the feedback resistor R_a as well as the capacitance and frequency.

In practice R_a and the frequency f_0 are switched to allow a very wide range of capacitors to be measured (less than 1pF to well over 10 μ F) with good accuracy (dependent on the quality of the meter and components, but can be as good as 1-2 per cent).

The output from the virtual earth amplifier is then rectified with a precision rectifier and presented to the voltmeter (multimeter) for display. The precision

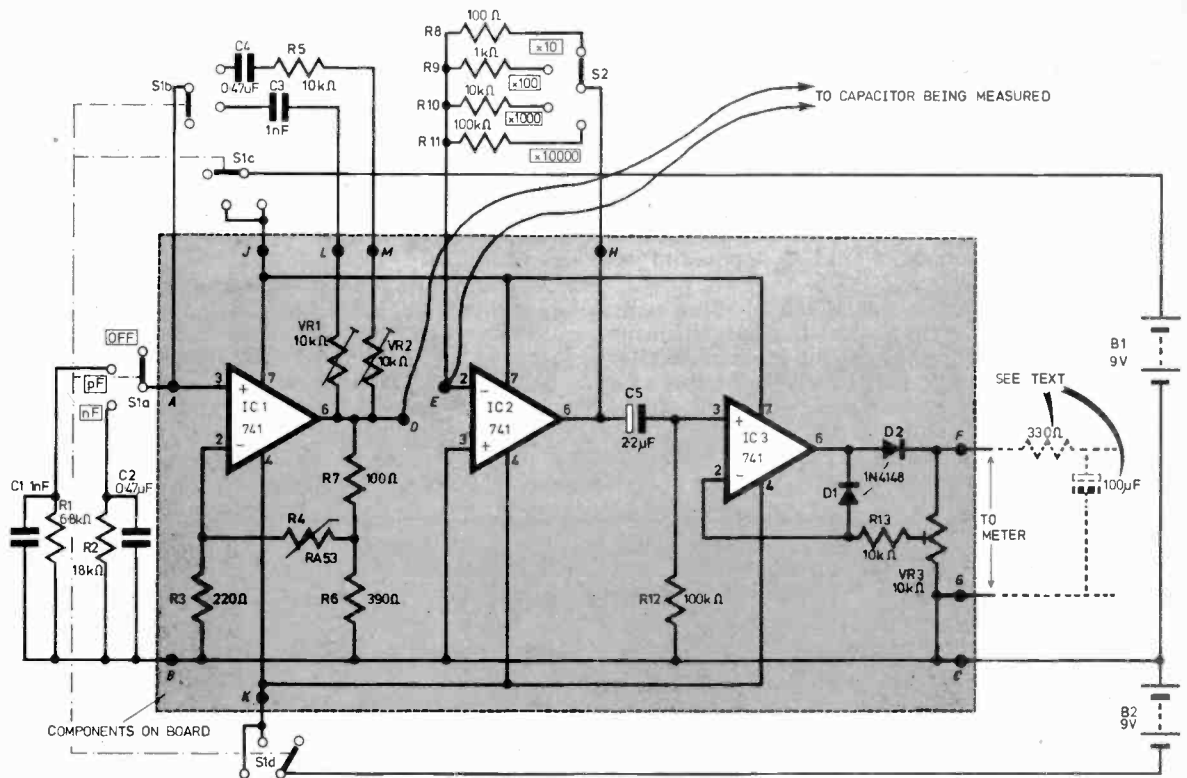


Fig. 2. Full circuit diagram

rectifier merely uses a further op. amp. to overcome diode forward voltage drops and thus obtain accurate rectification down to low output levels.

The circuit diagram is shown in Fig. 2.

INTEGRATION

The output from the unit consists of half sine-waves, and it is left to the meter to integrate these and provide a continuous reading. No problems were encountered with the larger type of meters (AVOs, etc.), but with smaller ones needle "judder" may cause annoyance. If this arises the effect can be alleviated with the simple addition of two extra components.

If a $100\mu\text{F}$ capacitor is connected across the output of the unit via a 330Ω resistor and the meter output is taken across the capacitor, the integration process is greatly improved and the judder cut down considerably. The addition of these components increases the meter reading a certain amount and therefore the gain of the rectifier stage must be reduced to maintain accurate calibration.

COMPONENTS

The only components that are required to be of any appreciable accuracy or stability are the range resistors R8 to R11. If possible these should be 1 per cent types, otherwise 5 per cent types can be used if they are "hand-picked" with an accurate ohm-meter.

The integrated circuits are all 741s. Although it was initially suspected that bandwidth/slew rate limitations would prohibit their use this was not found to be the case in practice, and high accuracy was maintained throughout all ranges. This obviously keeps the price down and maintains appeal to the economy-minded constructor.

Resistors mounted on the Veroboard have to be small if they are to be mounted horizontally. There is no reason why slightly larger resistors should not be used provided they are end-mounted.



STABILISATION

The thermistor specified is the popular R53 type. When used in Wien bridge oscillators of conventional design these have the property of stabilising the output at a little less than 1V r.m.s. This was found to be rather low for this application and hence a potential divider has been inserted between the output of the 741 and the thermistor.

This causes the thermistor to think that the output level is lower than it is and the circuit stabilises at an output level of around 2V r.m.s. as opposed to the original 700–800mV.

One of the unfortunate side effects of using some types of thermistors as amplitude stabilising elements is the time required for the output to stabilise after range switching. This is particularly so in this case where a large frequency change is performed. If it is felt that the settling time is too long (it in fact

then be checked to be at approximately at earth potential (this is a good test as it is a quick method of checking all is well throughout the complete circuit). Solder bridging, missing Vero breaks and components not properly soldered in are the sort of faults usually found to be at the root of any problems encountered.

The oscillator section should begin to oscillate within a few seconds of switching on; checking and re-checking once again being necessary if no output is obtained.

Calibration should commence with the rectifier gain potentiometer VR3 being set to minimum gain (slider nearest to D2 cathode). The two operating frequencies 20Hz and 20kHz should then be set as accurately as possible with a scope. If one is not available then VR1 and VR2 should be adjusted to their mid-positions.

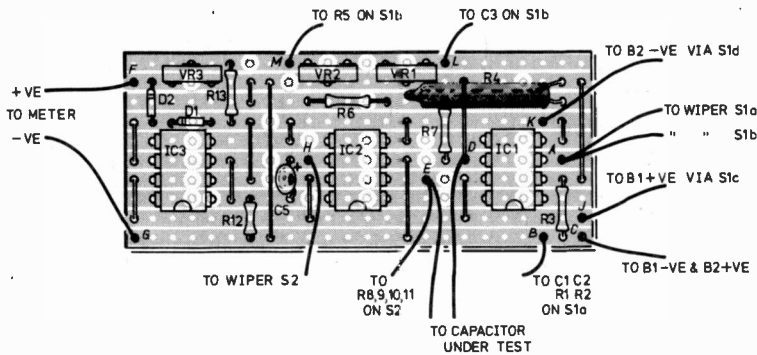


Fig. 3. Component layout and board-cutting details

amounts to about 3 or 4 seconds) an alternative f.e.t. stabilised arrangement can be substituted (see "Modifications").

CONSTRUCTION

A certain amount of dexterity is required in the construction of the Veroboard as space is very much at a premium. If the specified components are used no great problems should be encountered, and the unit can easily be built on the free board provided.

Construction should commence by cutting the breaks on the Veroboard with either a proper Vero spot-face cutter or a drill of correct size. Components should then be soldered in with care to avoid bridging of parallel tracks. Wire links can be made from stripping ordinary single cored connecting wire or using greater than 22 s.w.g. tinned copper wire from other sources.

C1, R1, C2, R2 and R5–9 are mounted on their respective switches to lessen the number of components on the Veroboard. Obviously, if a larger piece of board is available they can be mounted adjacent to the other components.

CALIBRATION AND TESTING

Firstly, it is worthwhile mentioning that initial setting up and testing of the device is made easier by having an oscilloscope at hand.

As a precautionary measure the current supplied to the unit should be measured when the unit is first tested. This should be in the region of 5–10mA using 9V supplies. The outputs of the 741s (pin 6) should

COMPONENTS . . .

Resistors

R1 6.8k Ω	R9 1k Ω 1%
R2 18k Ω	R10 10k Ω 1%
R3 220 Ω	R11 100k Ω 1%
R4 RA53 bead type thermistor (R.S. Components—access via Doram)	
R5 10k Ω	R12 100k Ω
R6 390 Ω	R13 10k Ω
R7 100 Ω	*R14 330 Ω (270 Ω –1k Ω , see text)
R8 100 Ω 1%	*R15 100k Ω

All resistors $\frac{1}{10}$ W 5% unless otherwise specified

Capacitors

C1, 3 1nF plastic or ceramic
C2, 4 0.47 μ F plastic or ceramic (pref. type C280)
C5 2.2 μ F tantalum 10V
*C6 2.2 μ F elect. 10V

Potentiometers

VR1–3 10k Ω min. vertical


Semiconductors

D1–3 1N4148
*D4 1N4148
*TR1 2N3819
IC1–3 741

Miscellaneous

R.S. Components "midget" wafer switches, 3-pole 4-way, and 4-pole 3-way. Case: Vero plastic box 120 × 65 × 40mm code no. 65-2518. Knobs and hardware, crocodile clips, two PP3 batteries

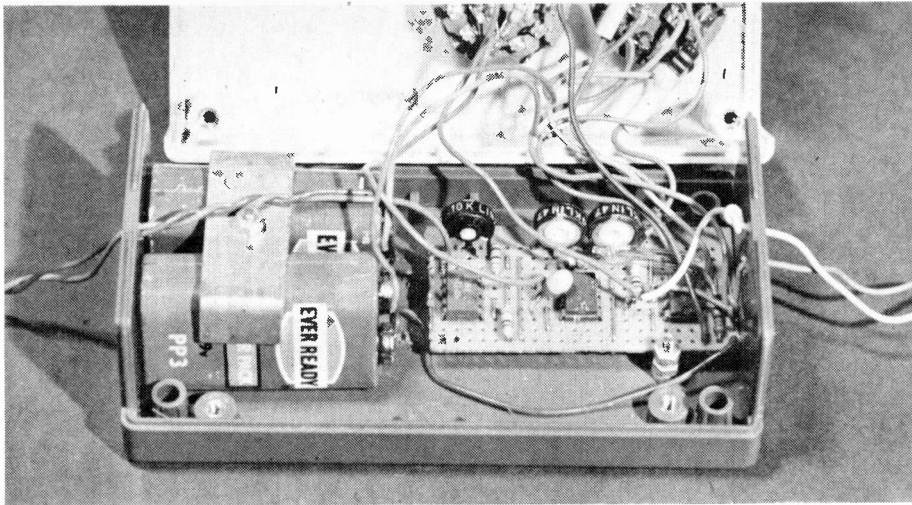* Components marked with an asterisk required for optional modification only—see text



Internal layout of the add-on unit. The batteries are held in place with an aluminium bracket and a 30mm CSK 6BA bolt. There is enough room either side of the free board to allow it to be held in place with the 6BA bolt/nut arrangement as shown

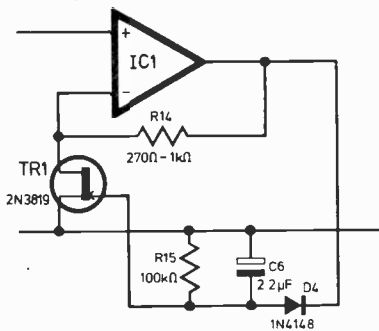


Fig. 4. Alternative f.e.t. stabilising network around oscillator section

PRECISION CAPACITORS

At some stage in the calibration procedure it is necessary to refer to either one, or (preferably), a range of accurate capacitors. These can often be found on ex-equipment circuit boards which are generally on sale at many electronics stores. An ideal range would contain such values as 10pF, 100pF, 1nF, 1μF, 10μF, all within 20 per cent tolerance. Obviously it may prove difficult for some constructors to obtain such capacitors, in which case less accurate ones will have to be resorted to. The majority of the above mentioned capacitors are in fact used for checking and it is possible to calibrate the capacitance unit successfully with only one 10,000pF, exploiting the fact that two ranges overlap (10,000pF and 10nF). It may therefore be considered worthwhile to invest in one precision 10,000pF capacitor and use standard types for spot checks throughout the other ranges.

Set the nF/pF switch to nF and check that the oscillator output is about 1.5–2V r.m.s. Set the multiplier switch to $\times 10$. Connect the 10,000pF capacitor to the test leads and the "meter output" to

an appropriately adjusted multimeter (a low voltage d.c. range with an f.s.d. between 1 and 3V). The capacitance unit is designed to give 1V output for "full-scale" reading on each range; hence, if a 1V range is available this would do best.


The rectifier gain control should now be increased with VR3, and if all is well it should be possible to adjust the output level such that the meter is reading 1V. The nF/pF switch should now be set to the pF position and the multiplier switch to 10,000 (corresponding to 10,000pF f.s.d.). The meter should read in the region of 1V and any discrepancy adjusted out with the 20kHz trimmer VR1.

If this cannot be done, and no scope was initially available to set the two operating frequencies reasonably accurately, VR1 should be adjusted to give as near 1V output as possible and VR3 then used to set it exactly. In doing this the nF range will be misaligned, and therefore, with the 10,000pF capacitor still connected, and the range and multiplier switches once again set to read 10nF, VR2 should be used to adjust the output to read 1V once more. It is a question of juggling with the three calibration potentiometers (VR1–3) as outlined above until the unit is satisfactorily calibrated, although it is worth stressing that an oscilloscope can save quite a lot of time in this process.

MODIFICATIONS

Earlier it was mentioned that the response time of the thermistor was rather long and that it could be reduced by inserting an f.e.t. stabilising arrangement in place of it. The modified section is shown in Fig. 4. The output of the oscillator is rectified and then used to bias the gate of an *n*-channel f.e.t. If the output level reduces the f.e.t. is turned on which increases the gain of the amplifier and stabilises the level. In practice the value of the feedback resistor R14 is a little critical; if it is too large the output level will not be held stable, and if too small, no output will result. A value of between 270Ω and 1kΩ was found to be suitable.



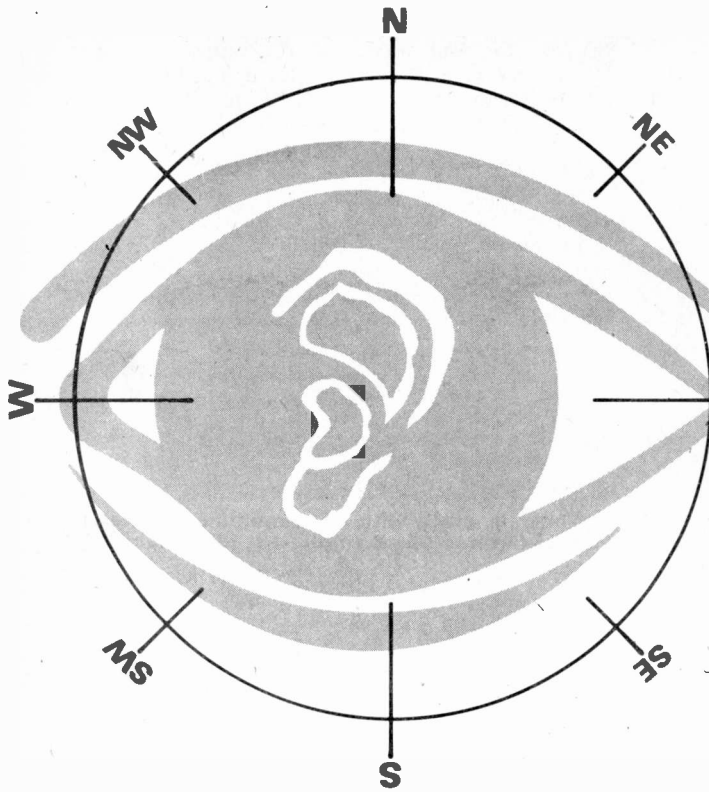

AUDIO COMPASS

By M. KENWARD

SOME time ago we were asked to design and construct an inexpensive unit to enable a blind man to steer a yacht on a straight course. The design, which is a direct result of that request, is fully described in this article.

In addition to being of immense help to blind sailors, the design will also assist those sailors who use wind vane steering, as it can provide an off course alarm, and also power boat enthusiasts, as it can be used to steer a straight course without the need to look away from the water ahead. It could also prove very useful on a long passage where a compass course must be sailed, particularly at night, as it allows the use of ears rather than eyes, which can become tired.

The audible output from the unit is provided through a crystal earpiece and can be a high frequency, no output or a low frequency. The no output indicates that the yacht is on course and the high or low frequency that the yacht has gone off course in one direction or the other. The width of the no output (or dead) band can be varied from about 5 degrees (2.5 degrees off course on either side) up to about 50 degrees (25 degrees off course either side) this is to suit the conditions and the response of the boat/helmsman and is adjusted by the helmsman with a sensitivity control.

In use the boat is put on course, the compass is revolved until the unit gives no output at maximum sensitivity and the helmsman then steers to keep no output, adjusting the volume and sensitivity to suit himself. When used as an on off course alarm a relay switches on a loud alarm to indicate that the boat has gone off course by more than the amount previously set.


CIRCUIT OPERATION

Two Hall effect probes are mounted on a suitable compass to detect the position of the magnet inside that compass. The Hall effect probes (H1 and H2) are fed with a constant voltage by TR1 (Fig. 1), the voltage being derived from the forward voltage drop of D1 and D2 in series (about 1.4V). The output from each probe is fed to an input of the 741 op. amp. IC1, one to the inverting input and one to the non-inverting input. Provided both inputs are at the same level the output at pin 6 will be zero (comparator arrangement) this can be corrected by adjustment of the offset control VR1.

If the pole of the compass magnet is between the two probes the output from them will be similar. If the pole moves towards one probe the output from that probe will increase (see section on Hall effect later) and from the other decrease—this will cause the output of IC1 at pin 6 to rise or fall at a rate dependent on the setting of the sensitivity control VR2 (this provides a variable degree of negative feedback to IC1).

The output from pin 6 is fed directly to the bases of TR2 and TR3 which act simply as switches to prevent the relays from loading the output of IC1. If the output goes high, TR2 is turned on, thus connecting the two relays across the 0V and +9V lines. Relay RLA will be turned on, thus connecting the supply to the unijunction oscillator formed by TR4 and its associated components and producing an audible output in the crystal earpiece connected to SK1. Relay RLB will not turn on due to the presence of D3.

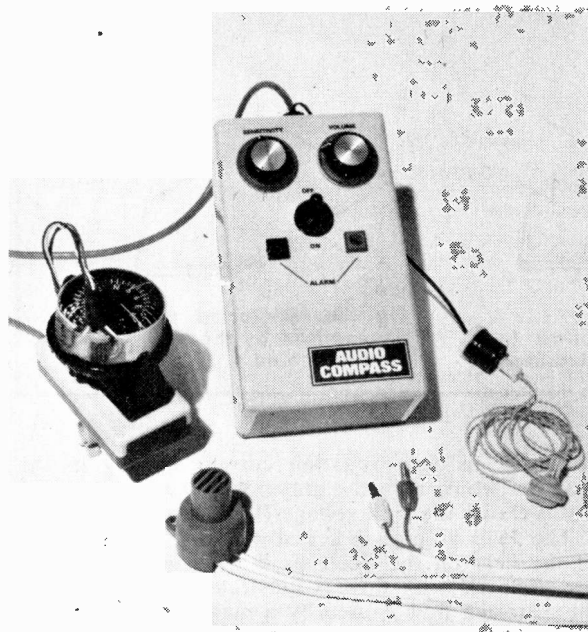If however the output at pin 6 goes low TR3 will be turned on thus operating RLA and RLB, this



The complete Audio Compass also showing the audible warning device used as the off course alarm

not only connects the oscillator but also shorts out R5, thus greatly increasing the frequency of the oscillator and hence of the output at SK1. The audible note thus indicates towards which probe the compass magnetic pole has moved.

The sockets SK2 and SK3 across RLA1 may be used to trigger an audible alarm, powered by the yacht's or other supply, to give an audible off course alarm. This facility can be set to trigger from about 2.5 degrees off, to about 25 degrees off by means of VR2 but does not indicate which way off course the yacht has gone (more about this later), and when in operation prevents the use of the normal audible output. The facility is added for those who use some form of wind vane self steering. It will provide an audible alarm if the yacht has been steered off its original course by the preset amount. The alarm recommended is the RS type audible warning device 12V or 24V, as required.

COMPONENT NOTES

One or two further points concerning the circuit operation should be made clear before we proceed, these concern the components used and their siting in the unit. It was found necessary to provide a stabilised supply for the two probes as their output varies considerably with the current flowing through them. The simple supply formed by TR1, R1, D1

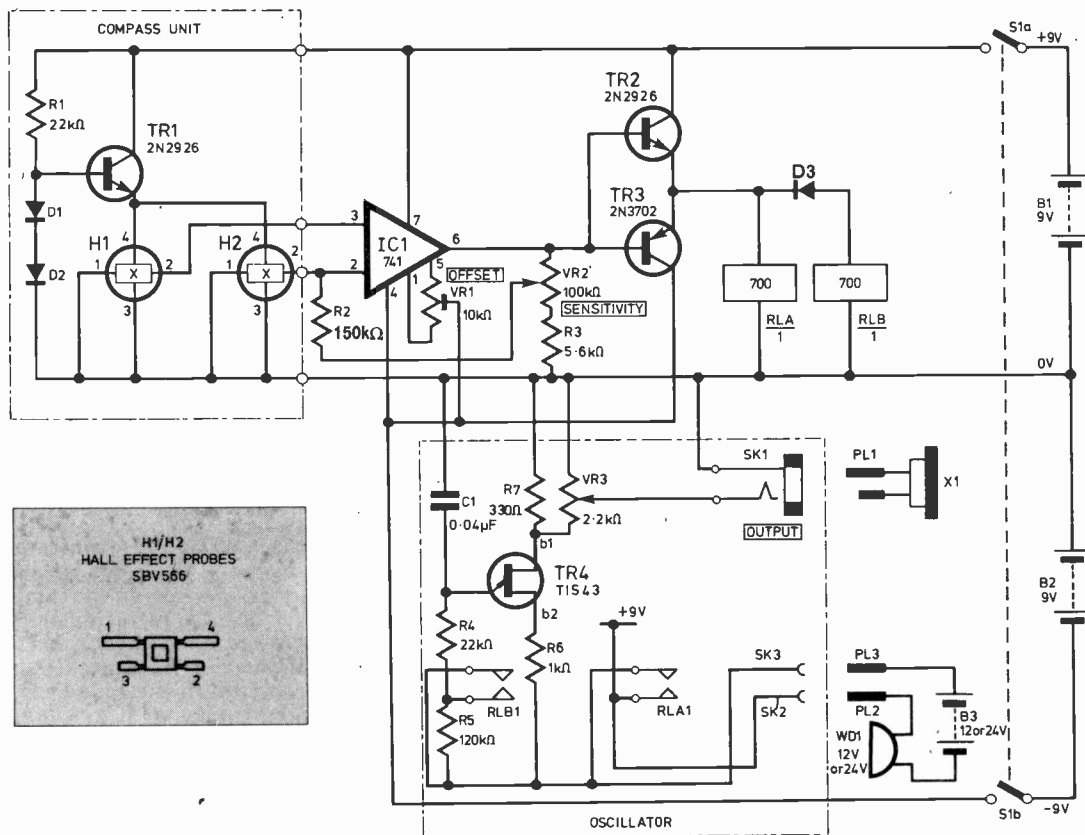


Fig. 1. The complete circuit diagram of the Audio Compass

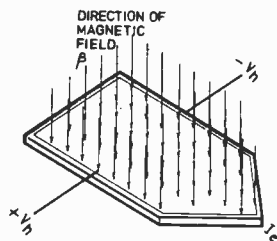


Fig. 2. Generation of Hall voltage

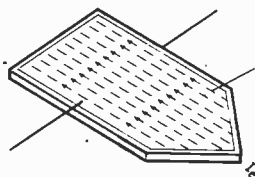


Fig. 3a. Electron flow in a conductor or semiconductor

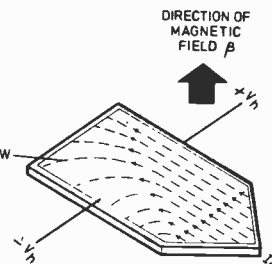


Fig. 3b. Distorted electron flow caused by the magnetic field indicated

and D2 was found to be perfectly adequate, provided internal cells are used and the unit is not connected to the boats supply. The components forming this stabiliser are sited as near the two probes as possible in order to negate any lead resistance which may prove troublesome.

The values of resistors R2 and R3 set the limits to the sensitivity of the unit and those shown were found to be most suitable. Reduction of R3 will decrease the minimum dead band, but if this is taken too far the unit will be difficult to set up and it would become impossible to keep within the dead band when in use.

Similarly, reduction of R2 will increase the dead band, but if this is taken too far, the limits of the sensing probes will be reached and either no output will result or only one note may sound. Experimentation with these values, either up or down, will not harm the unit and some constructors may find it helpful to do this. It is not recommended that preset resistors are permanently employed as their value could easily be altered with a knob.

It should be fairly obvious from the circuit description above that relay RLB must operate at the same instant or preferably before RLA. If this is not the case the output will always start at a low frequency and then go high if the voltage at TR2/TR3 emitters goes low.

To prevent this, the working voltage of both relays must be checked and that which operates at the lowest voltage used for RLB; the operating voltage will probably be around 3V. For this same reason a germanium diode must be used for D3 since the voltage drop across this will only be about 0.2V, instead of 0.7V for a silicon diode.

The two diodes used in the stabiliser circuit must be silicon diodes and are used to provide a "Zener" voltage of about 1.4V.

HALL EFFECT

The Hall Effect was discovered by E. H. Hall about 90 years ago and the principle involved accounts for the deflection of cathode ray beams in magnetically deflected tubes, so it has been employed for some considerable time, although many readers may not be aware of it.

Basically the effect causes a voltage (the Hall voltage) to be set up in a conductor or semiconductor in the presence of a magnetic field when an excitation current flows through the conductor or semiconductor. The effect is illustrated by Fig. 2. The

current I_e is the excitation current flowing in the material which is in the presence of a magnetic field β this causes the Hall voltage V_h to be set up.

The Hall voltage is actually caused by the effect of the field on the electrons flowing in the conductor. The electron flow is illustrated in Fig. 3a and the distorted flow caused by a magnetic field in Fig. 3b.

The electrons tend to build up along the edge of the conductor and, since they are negatively charged give rise to the Hall voltage as indicated. The maximum Hall voltage is limited because the abundance of negatively charged electrons tends to repel further electrons (like charges repel), hence a state of equilibrium is reached when the magnetic force equals the repulsion of further electrons. This state is reached in much less than a microsecond and the Hall voltage will therefore quickly follow any variations in magnetic field. If the excitation current is varied, a greater number of electrons are introduced and hence V_h increases.

It is thus easy to see why V_h is directly proportional to both I_e and β .

PRACTICAL CONSIDERATION

In the application described the Hall voltage is minute since the field around the compass magnet is also very small. In addition to this an offset voltage is set up in the device which causes a continuous voltage of about 1.5V per ampere (excitation current) to appear in addition to the Hall voltage. This offset voltage can be greatly reduced by the design and material of the probe—of the order of 2mV or less per ampere—but such probes are expensive (about £30 each—as opposed to about £1 each for those used).

The effect of the offset voltage is taken care of in the circuit of Fig. 1 by using the 741 a comparator so that it only senses the difference in the input voltage and not its level. Since two similar probes are used the offset voltage on each will be similar and any slight variations can be cancelled by the offset control VR1 (a multivibrator preset) which varies the bias on the two input circuits of IC1.

We have shown that variations in the excitation current will provide variations in the Hall voltage. To provide stability both probes are fed by the stabiliser. Although this does not hold the current through each probe constant it has been found to be perfectly adequate since the probes are similar and therefore have a similar resistance/temperature

characteristic. They are also mounted relatively close to each other.

The current through each probe has been set to about 15mA to provide enough sensitivity, consistent with reasonable battery life when using a PP9 battery. This current could, if required, be increased—by increasing the Zener voltage set by D1–D2—up to a maximum of 75mA for each device. If this maximum is approached, steps must be taken to ensure that no one probe is exceeding that current.

HOUSING

The construction of the unit has been kept as simple and straightforward as possible. It was decided that to be of use to the blind yachtsman it

COMPONENTS . . .

Resistors

R1 22k Ω	R4 22k Ω
R2 150k Ω	R5 120k Ω
R3 5.6k Ω	R6 1k Ω
All $\pm 10\%$ $\frac{1}{4}$ W carbon	

Capacitor

C1 0.039 μ F

Potentiometers

VR1 10k Ω multiturn preset
 VR2 100k Ω lin. carbon
 VR3 2.2k Ω log carbon

Semiconductors


H1, H2 SBV 566 Hall effect probes (2 off—Electro-value)
 D1, 2 any small silicon diodes (2 off)
 D3 any small germanium diode
 TR1, 2 2N2926
 TR3 2N3702
 TR4 TIS43
 IC1 741 op amp

Miscellaneous

RLA1, 2 6–9V d.c. 700 coil reed relay (348-970 Doram 2 off)
 SK1 Line jack socket and plug (PL1) to suit X1
 SK2, 3 Plastic encapsulated banana sockets and plugs (PL2, 3) to suit (2 off each)
 S1 D.p.d.t. switch with thread to match dolly cover—see miscellaneous
 B1 PP9 9V battery and clips
 B2 PP3 9V battery and clips
 X1 Crystal earpiece with plug and lead at least 1 metre long.
 WD1 Audible warning device 12V or 24V as required (Doram). Only required for off course alarm function.
 Cases 188 \times 110 \times 60mm and 100 \times 50 \times 25mm Vero or Bocon (West Hyde Developments) plastic boxes with interlocking lid; cable gland ENCGQ (West Hyde Developments); plastic dolly cover for S1 (WS234 Home Radio Components); knobs pointer (2 off—see text); Veroboard 0.1in matrix approx. 100 \times 100mm; connecting wire; 4B.A. fixings; 4 way cable at least 2 metres (see text); three suction pads, two terry clips for 25mm diameter tube (stern pulpit).

Compass

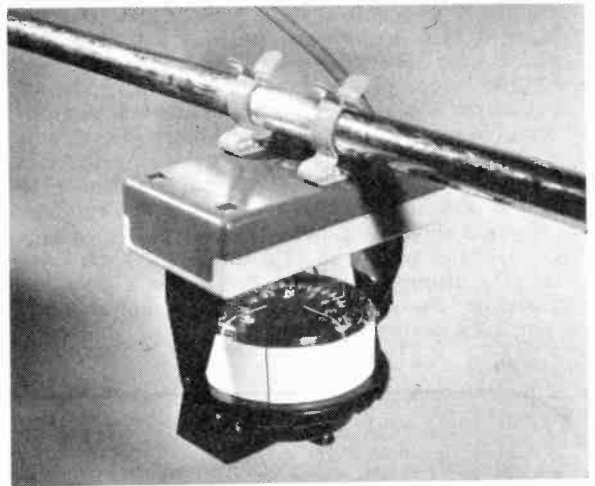Sestrel Junior dingy compass with gimballed mount (see text).



One way of mounting the compass unit on the rail. It could also be inverted so that the compass is more easily accessible

would not only need to be portable but also easily able to be fixed and used on any yacht, as few blind people own their own boats.

It is necessary to mount the compass where it can be adjusted to set the course and where it is free from knocks. To this end the compass unit has been equipped with two Terry clips so that it can be fitted to the stern pulpit of most yachts.

Similarly, the control unit which measures about 190 \times 110 \times 65mm is fitted with rubber suction pads so that it can be attached to any smooth flat surface near the helmsman. The two units are linked by a single four-way lead. This lead must be long enough to cover most situations (about 2 metres).

The control unit carries the batteries and has an output for the earpiece as well as sockets for an audible alarm. Both boxes carrying circuitry should be fairly splash proof and all metal work must be able to stand up to salt water type environment.

The control box of the Audio Compass, this is fitted with three suction pads for mounting purposes



Obviously if the unit is to be used only on one craft or if it is to be used only as an off course alarm, it could be permanently fixed and in the latter case could be completely housed below deck. The off course alarm only application allows certain sections of the circuitry to be omitted, more about this later, however, since the cost of these sections is relatively low we would advise the constructor to build the complete unit so that the audio compass can be used should the need arise. This also means that the owner would be able to offer a blind crew a useful position and, from the author's own experience, this could prove to be valuable and interesting for both parties.

CONSTRUCTION

Construction of the two units is shown in Figs. 4 and 5. There are no special precautions other than saying it is probably safer to use a holder for IC1. This is useful when changing i.c.s as we have found that there are a number of duff ones about. It is also necessary to take the usual precautions when soldering D3, since this is a germanium device and thus easily damaged by excess heat.

The output socket for the crystal earpiece is mounted on a 300mm length of twin-cable which passes out of the case through the cable gland. This adds extra length to the lead and allows the box to remain sealed (it is difficult to get a sealed jack

CONTROL UNIT


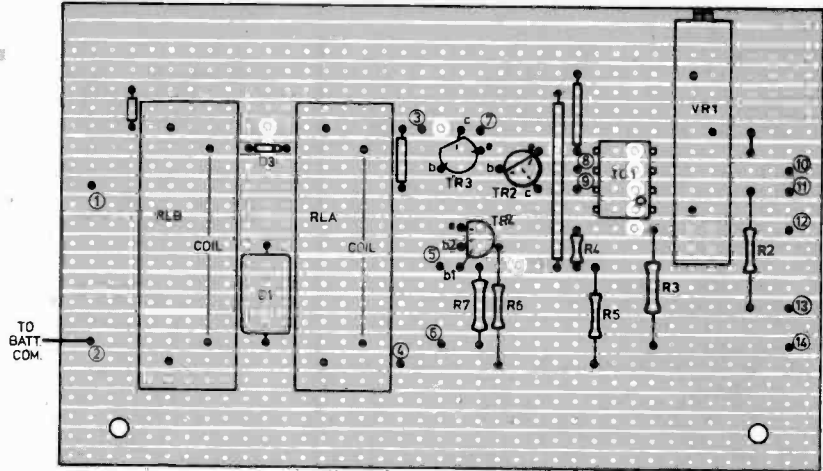


Fig. 4. Construction and wiring of the control unit. Veroboard layout is shown above with connecting points indicated by numbers which tie up with the lower diagram and Figs. 5 and 6

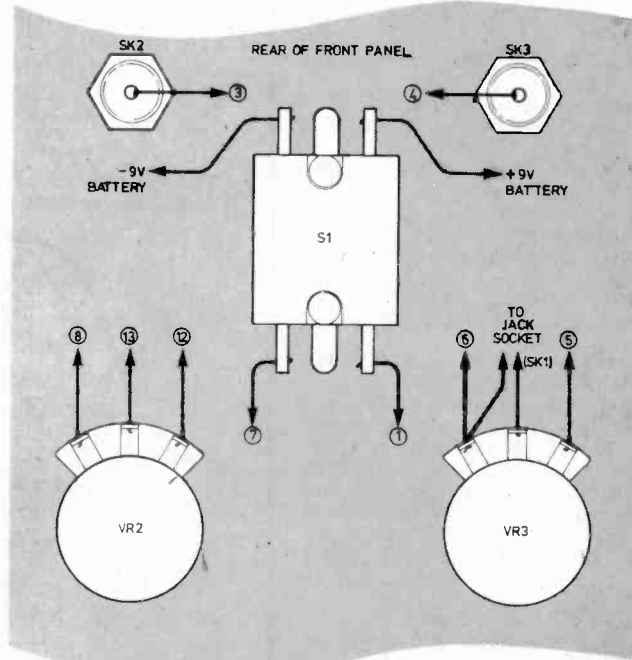

socket). The socket can be a "line" type or can be mounted in any suitable small container and may be easily changed if it becomes badly corroded.

The fitting and wiring of the two probes is shown in Fig. 6. These probes are very small and **must be handled and soldered with great care in order not to damage the leads**. They do not seem to be particularly heat sensitive but excess heat should be avoided. The probes are eventually covered with Araldite to protect them and fitted—square marked side inwards—against the plastic ring which is fitted over the compass, in line vertically with the magnet.

Construction of the compass unit is shown in Fig. 6. The materials used should be plastic or brass as

indicated, because these are non magnetic and corrosion resistant. The revolving ring is made of Contiboard white iron-on edging which is used glue side inwards with the ends overlapped and "ironed" together to form a ring.

INITIAL TESTING

Before testing the unit the supply current on the positive line should be checked to ensure the probes are not consuming too much current. Supply current should be about 30 to 50mA (depending on the output of IC1) and definitely not more than 60mA. If all is in order the unit can be tested for correct operation.

COMPASS UNIT

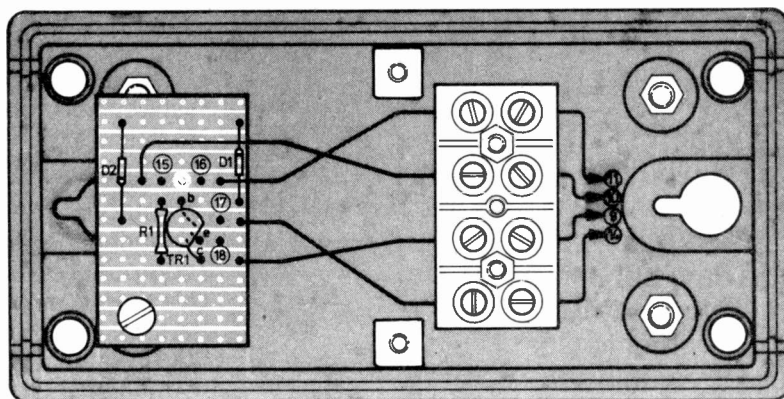


Fig. 5. Layout and wiring of the compass unit. The lead outlets can be sealed with silicon compound


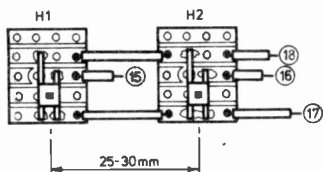


Fig. 6. Fitting and wiring of the two Hall effect probes. Basic arrangement of the compass unit is also shown, the wires to the probes should be extra-flexible to allow the compass to swing freely

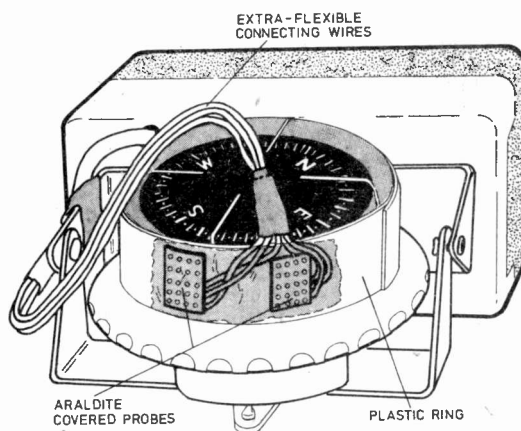


The Black Watch kit

£14.95!

★ **Practical**—easily built by anyone in an evening's straightforward assembly.

★ **Complete**—right down to strap and batteries.

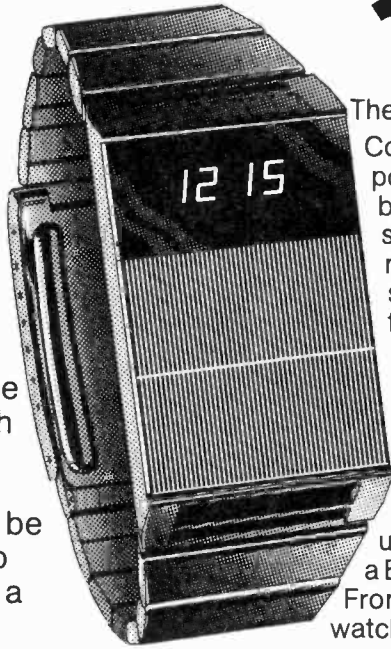★ **Guaranteed.** A correctly-assembled watch is guaranteed for a year. It works as soon as you put the batteries in. On a built watch we guarantee an accuracy within a second a day—but building it yourself you may be able to adjust the trimmer to achieve an accuracy within a second a week.





The Black Watch by Sinclair is unique. Controlled by a quartz crystal, and powered by two hearing aid batteries, it uses bright red LEDs to show hours and minutes, and minutes and seconds. And it's styled in the cool prestige Sinclair fashion: no knobs, no buttons, no flash.


The Black Watch kit is unique, too. It's rational—Sinclair have reduced the separate components to just four—and it's simple: anybody who can use a soldering iron can assemble a Black Watch without difficulty. From opening the kit to wearing the watch is a couple of hours' work.

Touch and tell

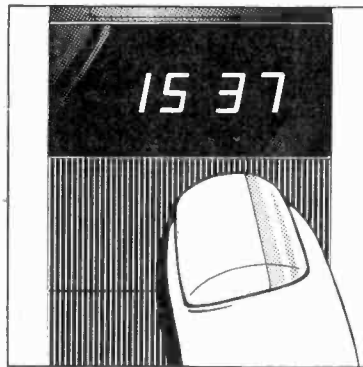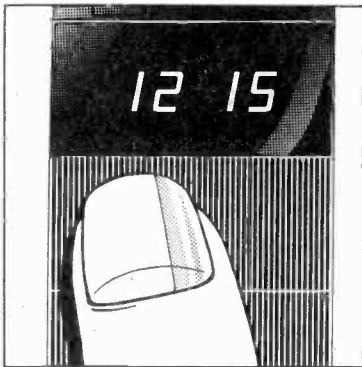Press here for hours and minutes... here for minutes and seconds.



Batteries easily replaced at home.

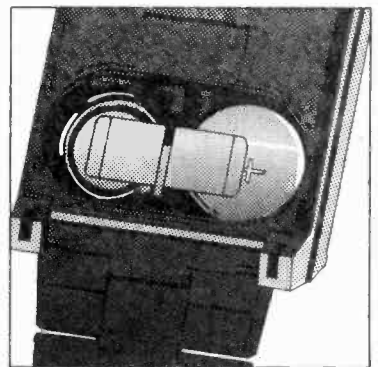

The specialist features of the Black Watch

Smooth, chunky, matt-black case, with black strap. (Black stainless-steel bracelet available as extra—see order form.)

Large, bright, red display—easily read at night. Touch-and-see case—no unprofessional buttons.

Runs on two hearing-aid batteries (supplied). Easily re-set using special button—no expensive jeweller's service.

The Black Watch – using the unique Sinclair-designed state-of-the-art IC.

The chip ...

The heart of the Black Watch is a unique IC designed by Sinclair and custom-built for them using state-of-the-art technology – integrated injection logic.


This chip of silicon measures only 3 mm x 3 mm and contains over 2000 transistors. The circuit includes

- a) reference oscillator
- b) divider chain
- c) decoder circuits
- d) display inhibit circuits
- e) display driving circuits.

The chip is totally designed and manufactured in the UK, and is the first design to incorporate all circuitry for a digital watch on a single chip.

... and how it works

A crystal-controlled reference is used to drive a chain of 15 binary dividers which reduce the frequency from 32,768 Hz to 1 Hz. This accurate signal is then counted into units of seconds, minutes, and hours, and on request the stored information is processed by the decoders and display drivers to feed the four 7-segment LED displays. When the display is not in operation, special power-saving circuits on the chip reduce current consumption to only a few microamps.

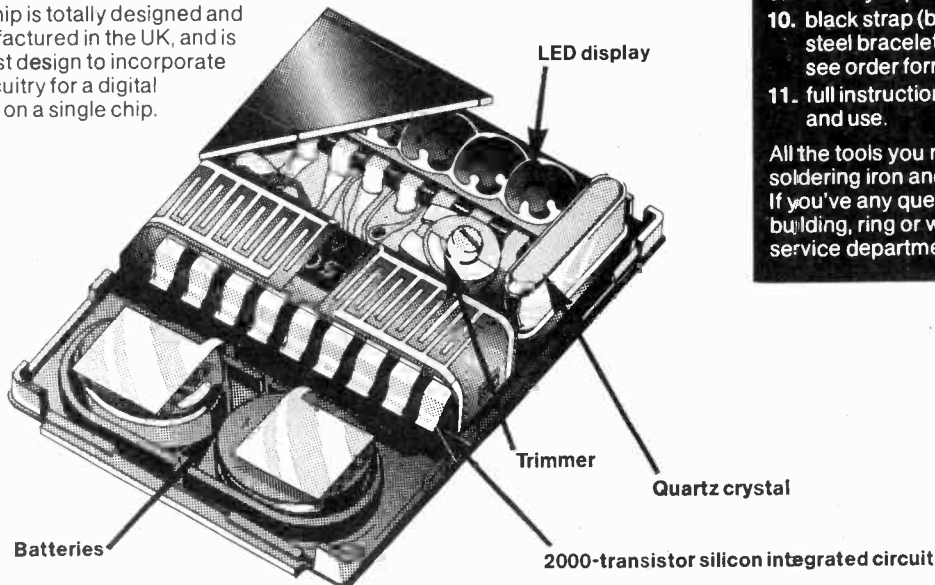

Complete kit £14.95!

The kit contains

1. printed circuit board
2. unique Sinclair-designed IC
3. encapsulated quartz crystal
4. trimmer
5. capacitor
6. LED display
7. 2-part case with window in position
8. batteries
9. battery-clip
10. black strap (black stainless-steel bracelet optional extra – see order form)
11. full instructions for building and use.

All the tools you need are a fine soldering iron and a pair of cutters. If you've any queries or problems in building, ring or write to Sinclair service department for help.

Take advantage of this no-risks, money-back offer today!

The Sinclair Black Watch is fully guaranteed. Return your kit in original condition within 10 days and we'll refund your money without question. All parts are tested and checked before despatch – and correctly-assembled watches are guaranteed for one year. Simply fill in the FREEPOST order form and post it – today!

Price in kit form: £14.95 (inc. black strap, VAT, p & p).

Price in built form: £24.95 (inc. black strap, VAT, p&p).

sinclair

**Sinclair Radionics Ltd,
London Road, St Ives,
Huntingdon, Cambs., PE17 4HJ.
Tel: St Ives (0480) 64646.**

Reg. no: 699483 England. VAT Reg. no: 213 8170 88.

To: Sinclair Radionics Ltd, FREEPOST, St Ives, Huntingdon, Cambs., PE17 4BR.

Please send me

Total £

..... (qty) Sinclair Black Watch kit(s) at £14.95 (inc. black strap, VAT, p&p).

* I enclose cheque for £..... made out to Sinclair Radionics Ltd and crossed.

..... (qty) Sinclair Black Watch(es) built at £24.95 (inc. black strap, VAT, p&p).

* Please debit my *Barclaycard/Access/ American Express account number

..... (qty) black stainless-steel bracelet(s) at £2.00 (inc. VAT, p&p).

Name (please print) _____


Address _____

Signature _____

PE/5

FREEPOST – no stamp required.

* Delete as required

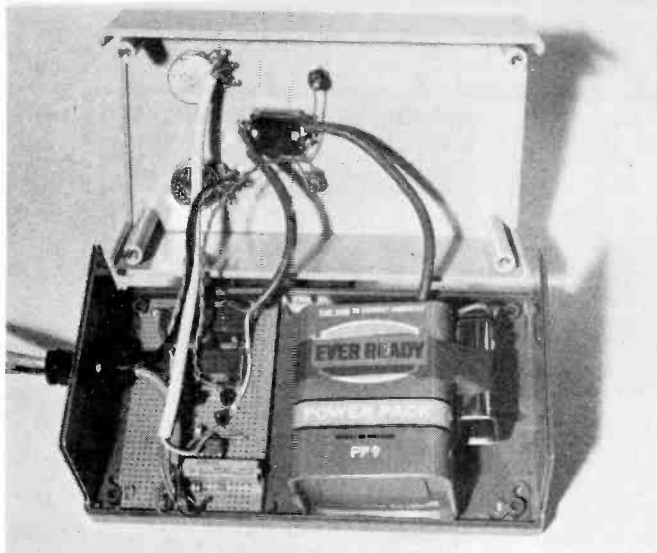


Internal view of the control box showing general layout. Foam rubber can be used to hold the batteries in place

To do this switch on and, with the sensitivity control turned fully up and the probes away from the compass, adjust the offset control VR1 until no output results or until the output frequency is just on the point of changing. Next introduce a metal screwdriver between the two probes and move it between the probes. The magnetism usually contained in the screwdriver should be enough to cause the two output signals to be produced, depending on which probe is approached.

If the unit does not function correctly the output of the i.c. can be checked, it should vary from +7 to -7 volts with variation of magnetic field at the probes. Once this is established a similar voltage should appear at the emitters of TR2 and TR3 and this should cause RLA and RLB to operate. Check this by measuring the resistance across RLA1 and RLB1. If all is well but no output results the fault must be in the unijunction oscillator, check the wiring and test for faulty components.

Volts on IC1 pins 2 and 3—the Hall voltage

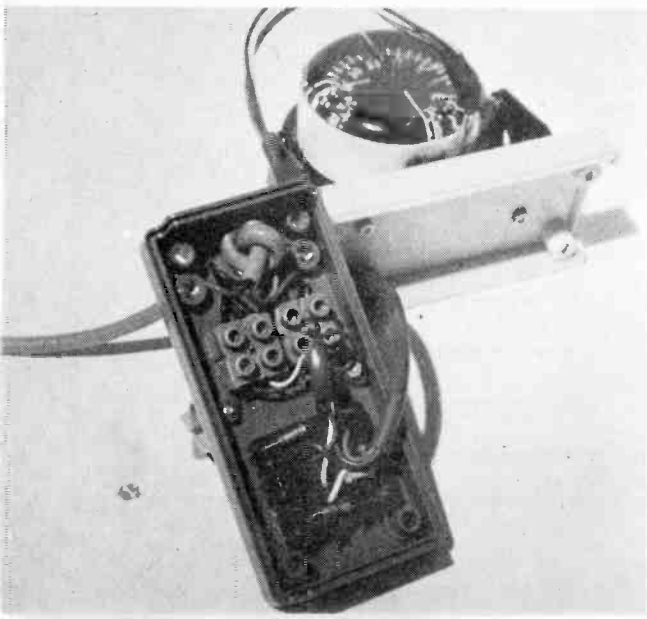Construction of the compass unit. Use of a connecting block allows the two units to be separated



plus offset—should be about 0.3V and it may be possible to see slight variation of this on a high impedance voltmeter (20,000Ω/V plus) if one pole of a magnet is brought close to the relevant probe.

ALARM ONLY

Should it be decided to construct only an off course alarm the unijunction oscillator, relay RLB and D3 may be omitted. The contacts of RLA1 then go only to SK2 and SK3 and are wired to the alarm and external supply as shown in Fig. 1.

The omission of these parts will save very little current and make little difference to the duration of the battery supply. With the above omissions the alarm will sound whichever way off course the craft has gone and thus no indication of direction is provided. If direction indication is deemed necessary for the alarm function, two different alarms should be employed e.g. that specified and a bell. The second alarm being wired to RLB1—which, together with D3 must be retained—in the same way as indicated for WD1 and RLA1. In addition to this a second germanium diode must be inserted in series with RLA, in the opposite polarity to D3. Thus when the output voltage of TR2/3 goes positive RLA will operate and when negative RLB will operate.

If as suggested earlier, the complete unit is constructed although only to be used as an alarm, the output earpiece can be left disconnected while in use—this will not affect operation of the unit or do any harm.

FINAL ASSEMBLY

The compass is gimballed in one direction only to take care of the heel of the craft, the floating card and magnet can move to overcome any pitching. The probes must be covered in Araldite and fixed to the ring on the compass housing in line with the magnet. A course setting line can be drawn between the probes.


It has been found that Araldite will not produce a good bond on the plastic ring and this is all to the good as it means that the probes and their Araldite covering may be prised off if necessary.

The possibility of using compasses other than that specified can be investigated simply by affixing the probes in the most suitable position (as near to, and on the same plane as the magnet) with insulation tape and trying the unit. The compass should be of good enough quality to function correctly without violent swings when in use.

Once in place the probes and their wiring can be protected by a couple of layers of plastic insulation tape. It must be noted that the ring should not be continually rotated on one direction as this will eventually break the leads. If this is thought to be a problem a stop should be fitted to the rotating section to prevent it going past 360 degrees.

When complete the unit can be set up by arranging the compass so that the north pole lines up with the line between the probes. Preset VR1 should then be adjusted with VR2 at maximum sensitivity, until no output results or the frequency just changes. The unit is then ready for use.

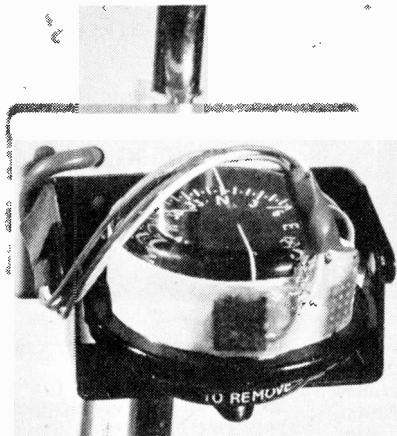The complete unit is intended to be reasonably water resistant and to this end a cable gland is used where the wires enter the main case. Also a flexible plastic dolly cover is used to protect S1 from the influx of water.



Another method of mounting the compass unit. It should be remembered that the gimbal takes care of yacht heel

The simplest method of sealing the two potentiometers is to employ knobs with a fairly large diameter and flat underside. Two cut-down babies' teats are then glued to the case so that when the knobs are fitted they push down on the rubber ring forming a reasonable seal. The teats can be easily and cheaply replaced when worn.

The cable entries to the compass unit can be sealed with silicon bath sealing compound and this could also be used around the joint on the smaller case once final testing is complete. The larger case must be easily taken apart to facilitate battery charging.

IN USE

Due to the design of the unit similar output notes and dead band are produced with respect to both the north and south poles of the compass. This is not a problem once the boat is on course but should none the less be noted.

The off course signal will continue to sound, should a correction not be made, until the craft has passed through 180 degrees. Because of this action it is always best to set the probes to sense one pole,

A happy man. The Audio Compass allows Jeff Bull, who is totally blind, to take full control of the helm without any directional assistance from other crew members



say north, as this then provides a standard output with variation in course, e.g. if going off course in an easterly direction a high note would sound if in a westerly direction a low note. Should the other pole be sensed, these notes would reverse.

Due to the fact that the compass specified cannot be corrected and that its environment will change, it should not be used as an accurate course indicator. It is better to put the craft on the correct heading and set the audible compass (at maximum sensitivity) to suit. It is possible to make up a normal deviation chart for the compass, if it is mounted in a fixed position, to enable accurate setting should this be required.

The prototype compass has been successfully tested in various yachts and it has been found that in most sea conditions the movement of the craft gives rise to bleeps from the unit before a continuous note sounds, these bleeps gradually increasing in length as the craft goes off course until a continuous note sounds. This provides a good indication of the rate of change of heading, of how far off course one has gone, and therefore of the amount of correction required. This also provides good indication when coming back on course, since the reverse then happens with the bleeps getting shorter until silence prevails.

A similar output will result when an off course alarm is employed—if the first few bleeps do not arouse the crew the continuous note soon would.

COST

The complete unit can be constructed for approximately £20, about half of this being the cost of the compass specified. The audible alarm, if required, will add approximately £1.50 to the overall cost. Please note that the above prices are only estimates and do not include V.A.T.

ACKNOWLEDGEMENT

The author wishes to thank Des Sleightholme, editor of *Yachting Monthly*, who put forward the original idea, for his assistance in testing the unit and Jeff Bull who acted as a "guinea pig" and provided valuable criticism from the blind helmsman's point of view. ★

SEMICONDUCTOR UPDATE

By R.W. COLES

A8400 S1-1020G
FX205 S1-1030G
S1-1010G, S1-1050G,

V-F-V BREAKTHROUGH

There has been available for a number of years, an extremely useful and versatile class of circuit modules known as V to F's or F to V's, to those professional engineers fortunate enough to be able to justify their expense. Yes, you guessed it, the reason why V to F's and F to V's have not been seen in these pages before is because they have been much too expensive for amateur use. I am very pleased to report that this situation has now changed with the introduction by Teknis Electronics of a monolithic V-F-V which knocks spots off the expensive hand-made modules on the grounds of cost, size and performance!

The abbreviation V to F stands for "voltage-to-frequency" and F to V stands for "frequency to voltage" and the new device from Teknis, the **A8400**, will do both, unlike some of its more expensive predecessors which were often just single-function devices.

The usefulness of a device which can convert a d.c. input voltage into a directly related output frequency of between 0 and 100kHz, and vice versa, is really quite mind boggling. Fancy turning your frequency counter into a digital voltmeter with 0.05 per cent linearity and 5 digit resolution? Just hook up an A8400 as a V to F and feed the output into your counter and you've done it—just like that...

Or, do you want to record slowly changing d.c. signals on a tape recorder with simple replay? Use an A8400 connected as a V to F to turn those d.c. signals into audio tones, then replay them later through an A8400 connected as an F to V—it's that easy. The possible applications go on and on, and are limited only by your imagination, the availability of a cheap monolithic device brings to amateurs the advantages enjoyed by instrumentation engineers for years.

The A8400 does cost rather more than a 741, in fact about £12 in small quantities, but this is about a third of the cost of its nearest rival, and a bargain in my book!

PSEUDO-SINE

Consumer Microcircuits Ltd. are a British firm who make a very useful range of m.o.s. integrated circuits

intended for use in audio-tone signalling and control system applications. Their range already includes tone transceivers, frequency sensitive switches and tone triggered timers, and has recently been extended with a fascinating little device known as the **FX205 sinewave oscillator**. As expected the FX205 is as unique as the other circuits in the Consumer Microcircuits range, and could well be useful for use in a wide range of amateur projects, from radio control systems to intercoms.

The FX205 generates a stable audio tone of between 25Hz and 5kHz using only a single external resistor and capacitor, the output signal being of a "pseudo-sinewave" shape generated entirely by the digital circuitry of the chip. Internal circuitry includes an astable oscillator, a monostable, a digital to analogue converter and a four bit binary counter.

In operation the astable is timed by the external RC network and the resulting output is divided down by the counter, the outputs of which drive the D to A converter which is weighted so as to produce the "pseudo-sine" output signal which is sufficiently pure for use as a signalling tone. The internal monostable can be used, if desired, to produce "tone bursts" up to ten seconds in length under the control of an external trigger signal, which could be just a push switch closure.

A "tone enable" input is also provided for use when gated operation is required, and the option is available of using an external synchronising signal instead of the internal oscillator. Where multiple-tone signals are required, the outputs of several FX205s can be "WIRE-OR'd" together.

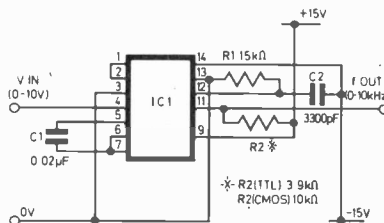


Fig. 1. A8400 as a V to F converter

PAINLESS POWER

Monolithic audio power amplifiers are limited in power dissipation due to chip size constraints, so if you want to make those woofers throb with a bit more than the paltry 10 watts afforded by even the sturdiest monolithic devices, you'll have to either use a discrete design or go in for a pre-packaged hybrid.

A new series of hybrid amplifiers with output powers of 10, 20, 30 and 50 watts is now available from Rastra Electronics Ltd., and you may find that one of these is more cost-effective than a conventional discrete design, especially if you are suffering from the dreaded "wiring-up-itis" (wiring-up-itis, has of course been known to make expensive woofers disappear up their own infinite baffles, to make 2N3055's glow like beam tetrodes, and make grown men cry!)

The new hybrids from Rastra the **S1-1010G, S1-1020G, S1-1030G** and **S1-1050G** are made in Japan by Sanken and are complete power amplifiers suitable for Hi-Fi, musical instruments and public address applications. The output stage is a quasi-complementary class B type using passivated power transistors with good "second-breakdown" resistance, and built-in current limiting on the S1-1030G and S1-1050G. The performance specification seems quite good, for the S1-1050G for example, full power bandwidth is from 20Hz to 20kHz while delivering 20V r.m.s. to an 8 ohm load with a 66 volt supply. Full power t.h.d. is 0.5 per cent maximum, and the signal to noise ratio is typically 90dB.

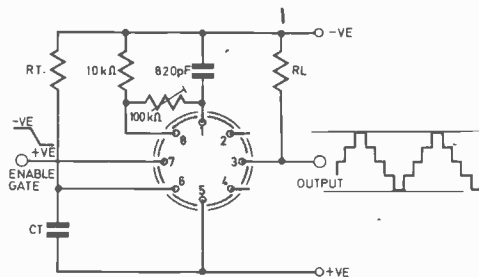


Fig. 2. FX205 as a tone-burst generator. The burst length is determined by R_T and C_T

NEXT MONTH!

OUT AND ABOUT with PE

**NEW
SERIES**

for RADIO CONTROL ENTHUSIASTS...

PROPORTIONAL CONTROL

Incorporating a 9-channel control unit for use with all types of models, this system features 7 channels with full proportional control and 2 channels which provide basic "on-off" control. The system operates on a time-division multiplex principle, and compares very favourably with the more expensive commercial units on the market at the moment.

PLUS

for the MOTORING ENTHUSIAST...


DIGITAL MILOMETER

Designed for use on car rallies or for applications where accurate map reading and navigation from a car are essential, or merely as an accurate elapsed distance indicator.

The use of 7-segment displays allows easy reading Day or Night

AUDIO MILLIVOLTMETER

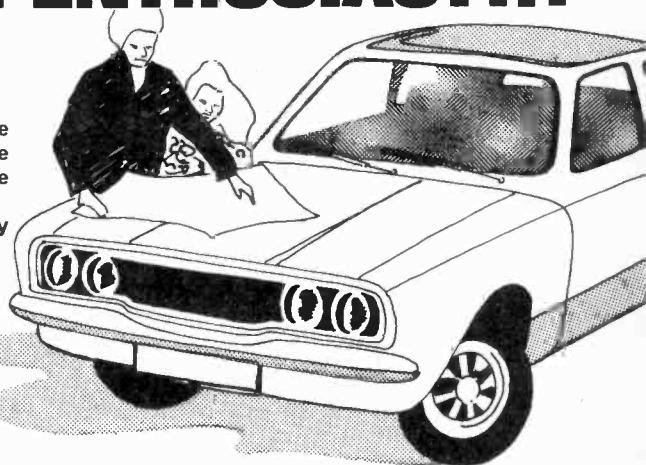With a frequency response extending from below 20Hz to above 200kHz and a sensitivity which allows a f.s.d. of 1mV to be obtained, the Audio Millivoltmeter will no doubt find a ready home on many an audiophile's test bench



PRACTICAL ELECTRONICS

Our June issue will be published on Friday, May 14, 1976

PLEASE NOTE:
It is in your interest to place a firm order with your newsagent—in advance. Back numbers are not available, so make sure of your copy now!

Simple

COMPUTER VOICE

By E.A. PARR B.Sc.

ORIGINALLY intended to generate a computer sounding voice for an amateur dramatic society, this device can be used to make "Dalek" type voices, and as such can provide hours of entertainment for children.

The circuit is simple, easy to set up, uses little current, can be battery operated, and is suitable for fitting into a child's space suit or Dalek outfit, as well as its original application.

The output level is 500mV, hence it is compatible with both the AUX input on most amplifiers (for stage use) and the many available i.c. power amplifiers for battery operation in a child's toy.

CIRCUIT DESCRIPTION

The usual way of producing a mechanical voice is by synthesiser techniques such as ring modulation. An oscillator giving a sine wave output is used to amplitude modulate the audio signal.

A circuit similar to this was tried, but whilst it worked and gave good results, it was somewhat tricky to set up, and there were doubts about its long term stability.

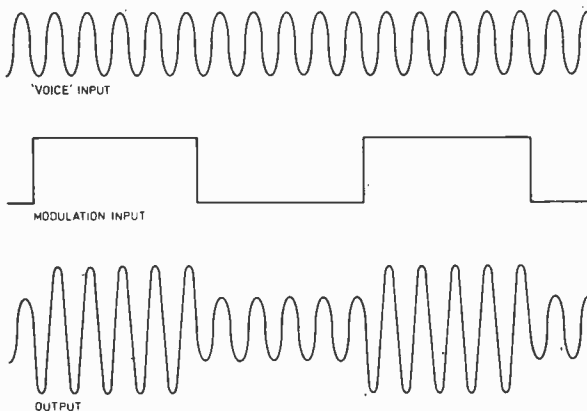


Fig. 1. Voice input before and after modulation

The final circuit behaves in a similar way to a conventional amplitude modulator, but the modulating waveform is a square wave (Fig. 1).

The circuit diagram of the final circuit is shown in Fig. 2. IC1 is a 741 operational amplifier arranged as an inverting amplifier. The circuit is designed for a single power supply, hence R3, R4 provide a mid rail voltage at their junction. The gain of the amplifier is determined by the ratio R5/R2. The microphone used has an output of 15mV so the gain is set to 30 to give the required 500mV output.

COMPONENTS . . .

Resistors

- R1 10k Ω (100k Ω for high output microphone)
- R2 1k Ω (39k Ω for high output microphone)
- R3 1k Ω
- R4 1k Ω
- R5 39k Ω
- R6 1k Ω
- R7 100k Ω
- R8 22k Ω

All resistors 10% $\frac{1}{4}$ W carbon

Potentiometers

- VR1 50k Ω lin.
 - VR2 50k Ω lin.
 - VR3 500k Ω lin.
- All horiz. min. presets

Capacitors

- C1 0.1 μ F plastic or ceramic
- C2 25 μ F 16V elect.
- C3 1 μ F 16V elect.
- C4 0.1 μ F plastic or ceramic

Integrated circuits, diodes

- IC1 741
- IC2 555
- D1 Any general purpose silicon diode (1N914, 1N4148, etc.)

Miscellaneous

- Relay RLA R.S. Components (access through Doram) type: D.I.L. reed relay, Form A (for 6-12V supplies)
- Veroboard 2 $\frac{1}{2}$ in \times 3in (65mm \times 80mm), case and hardware to suit

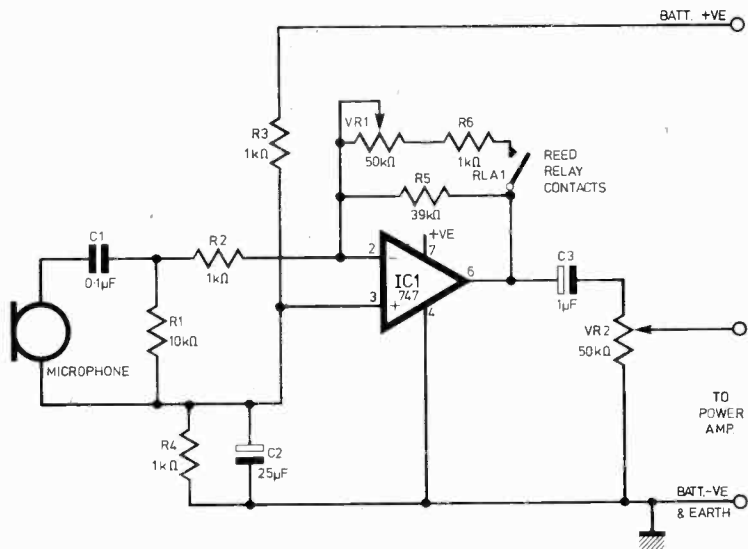


Fig. 2. Circuit diagram of the modulator

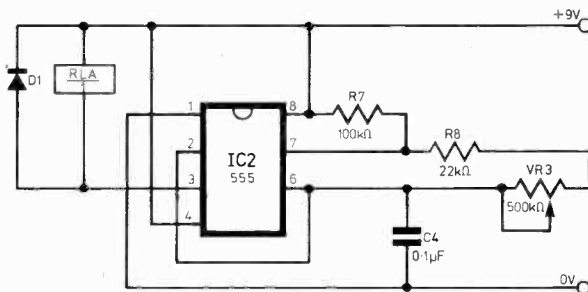


Fig. 3. Details of the modulation oscillator

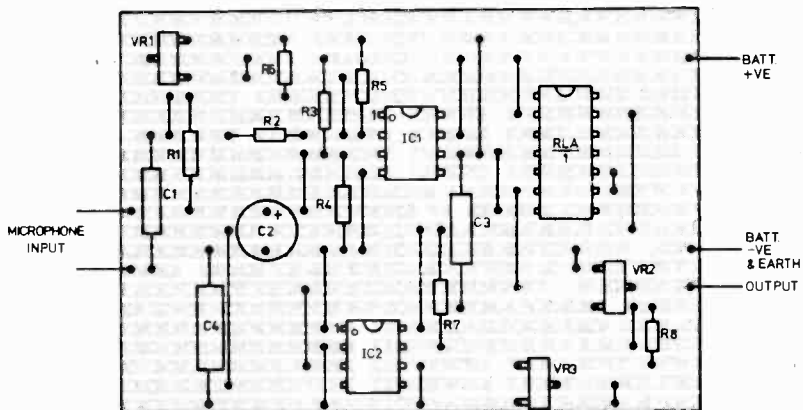


Fig. 4. Component layout and Veroboard cutting details

When relay RL1 contact closes, the gain is reduced and is given by the ratio $(VR1 + R6 \text{ in parallel with } R5)/R2$.

RV1 therefore controls the "depth" of the modulation and thus the amount of distortion.

MICROPHONE

The moving coil microphone used was somewhat bassy, so capacitor C1 was included to give a certain amount of bass cut. As the gain of the amplifier is determined by negative feedback, it is very easy to add shaping should such features as bandpass filtering be required.

If a ceramic or other high output microphone is used, resistors R1 and R2 should be increased in value to reduce the gain of the amplifier.

CONSTRUCTIONAL DETAILS

The circuit is constructed on 0.1in Veroboard, and layout and track cutting diagrams are given in Figs. 3 and 4. These are straightforward and should present no problems.

Trim pots are used on the circuit although there is no reason why the pots should not be mounted remotely.

To sum up: VR1 controls the depth of the distortion, VR2 the volume, VR3 the rate of distortion. In theory VR1 should affect the volume, but in practice at the levels of distortion necessary, the effect is not unduly noticeable.

MODULATION OSCILLATOR

The relay is "buzzed" by an oscillator (shown in Fig. 3) constructed from the ubiquitous 555 timer. The frequency of oscillation is controlled by R7, R8, C4 and VR3.

VR3 controls the "rate" of the modulation. The relay can be driven up to 250Hz but it was found that the best results were given in the range 20-60Hz.

Diode D1 clips any inductive spikes generated as the relay coil de-energises. This is included in the reed relay used in the prototype.

It might be thought that the life of the relay would be very short being maltreated in this manner, but as the relay used (and most reeds) have a mechanical life in excess of 10 million operations the author did not feel this posed any problem.

Contact life is not so easy to assess as it is determined by two conflicting factors. A large switched current causes contact burn, conversely a small arc helps to clean oxidation off the contacts. The current being switched in this circuit is infinitesimal, so the contact life will be determined by the dirt on the contacts. It is impossible to say when failure will occur, but the prototype has been working for several months without showing any signs of imminent death.

The supply can be anywhere in the range 6 to 15 volts (with suitable choice of reed relay). The prototype was built for 9 volts operation.

With a 9 volt supply, the current consumption is about 12mA. ★

CMOS DIGITAL I.C.s

continued from page 389

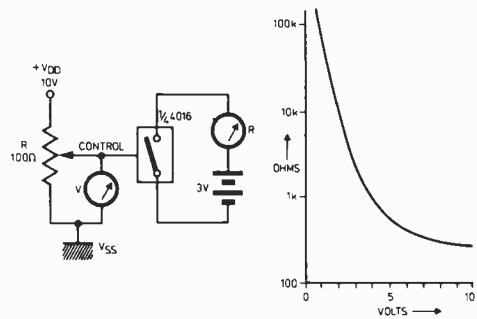


Fig. 5.16. The bilateral switch as a voltage-controlled variable resistor. The curve shows the variation in resistance with control voltage. The measuring arrangement is also shown.

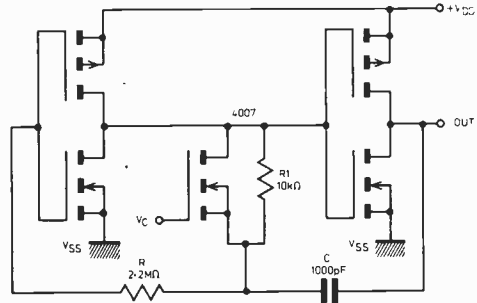


Fig. 5.17. Voltage-controlled oscillator. The voltage V_C determines the frequency, and with a 10V supply a range of between 10 and 15kHz is obtained with the values shown

VOLTAGE CONTROLLED CIRCUITS

The bilateral switch has so far been considered as an almost perfect switch; its resistance changes from about 300 ohms with the control pin at V_{DD} to several megohms with the control grounded. However, it can also operate as a voltage-controlled variable resistor (VVR) if non logic-level voltages are applied to the control input (Fig. 5.16).


The resistance depends somewhat on the voltage levels at the terminals of the bilateral switch, and this causes slight distortion of the transmitted signal. The voltage at either terminal should not go above V_{DD} or below V_{SS} . This simple VVR features extremely good isolation between the control input and the terminals, the resistance being greater than 10^{12} ohms, and can be used as the basis for voltage controlled filters, amplifiers and oscillators. A single n -channel device can also act as a VVR, and a similar curve is obtained although the minimum "on" resistance may be as high as 1,000 ohms. A simple VCO (voltage controlled oscillator) based on this and built from a single 4007 package (one device is not used) is shown in Fig. 5.17. The paralleled resistance of the n -channel MOSFET and R1 varies between approximately 1,000 ohms with the MOSFET "on", and R1 with MOSFET "off". A range of between 10 and 15kHz is obtained with the values shown for V_C of between 0 and 10 volts.

Next month: Retriggerable monostable and digital low pass filters

SOUND DESIGN

A PRACTICAL ELECTRONICS PUBLICATION

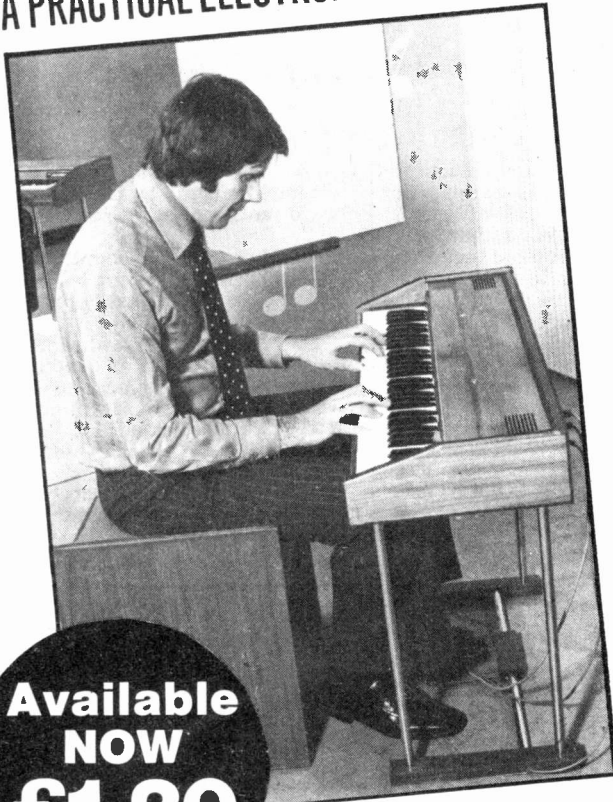A SPECIAL SELECTION OF MUSICAL PROJECTS FROM PE



Available
NOW
£1.20

by post only

(Please allow at least 2 weeks for delivery)

THE JOANNA ELECTRONIC PIANO

has realistic piano effect with touch-sensitive keyboard and additional choice of harpsichord or honky-tonk voicing.

THE ORION STEREO AMPLIFIER

A hi-fi amplifier with output of over 20+20 watts. Compact and complete in one unit, it measures only 14" x 6" x 2".

THE MINISONIC MK2 SOUND SYNTHESISER

An up-dated version of the published Mk 1, the Mk 2 has an integral keyboard, two 250 mW monitoring channels and loudspeakers, and facilities for amplitude, frequency and harmonic modulation.

PLUS Some great sound effects units for guitars, keyboard instruments and general recording.

If you do not wish to mutilate your copy of the magazine, please send your order on a separate sheet.

To: Practical Electronics, Post Sales Dept.,
IPC Magazines Ltd., Carlton House,
66-68 Great Queen Street, London WC2.

Please send me copy(ies)
of "Sound Design". I enclose a Postal
Order/Cheque for £1.20 (£1 + 20p post.
& pack.) or (state amount for more than
one copy)
(p & p 35p for 2 copies).

PLEASE WRITE IN BLOCK LETTERS

Name

Address

..... Post code.....

Remittances with overseas orders must be sufficient to cover despatch by sea or air mail as required.

Company registered in England. Regd. No. 53626. A subsidiary of Reed International Limited

MARKET PLACE

Items mentioned in this feature are usually available from electronic equipment and component retailers advertising in this magazine. However, where a full address is given, enquiries and orders should then be made direct to the firm concerned. All quoted prices are those at the time of going to press.

CASES

To complement their range of Minicases, **Olson Electronics** have just introduced a new range of robust, sloping front instrument cases.

Ideal for housing many of the constructional projects published in this magazine, particularly test gear, the cases are made from 20g mild steel and the 45 degree sloping front panel from 20g aluminium. The cases are only 95mm high by 95mm deep and supplied in three width sizes: 150mm, 200mm and 250mm. The front panel is 100mm by the required width.

Supplied with four rubber feet they are sprayed in light brown hammer finish and the front panels are finished in light grey semi-gloss enamel.

Full particulars of these excellent cases can be obtained from **Olson Electronics Ltd., Factory No. 8, 5-7 Long Street, London, E2 8HJ.**

WORK HOLDER

A unit which allows the constructor a free hand when soldering components into small circuit boards is the latest product from **Special Product Distributors.**

Called the **JA500 Reversible Assembly Frame**, a small board is clamped in position and a foam pad, in a covering lid, holds the components to be soldered firmly in position which allows the work piece to be turned over for soldering.

The frame will handle circuit boards up to 220mm x 170mm and the overall dimensions of the assembly is 250mm x 280mm.

Further details and price of the Reversible Assembly Frame can be obtained from **Special Product Distributors Ltd., 81 Piccadilly, London, W1V 0HL.**

CERAMIC SOUNDERS

There are very many practical applications for audible warning or indicating devices, some of which include paging, systems failure, etc. where the sound output requirement, whilst being less than, say, an intruder alarm, has the composite advantages of reliability and efficiency.

ITT are marketing a range of five piezo ceramic sounders of sound outputs varying below 93dB. The tones available are continuous or pulsed.

Details are available from **ITT Components Group Europe, Materials Division, Edinburgh Way, Harlow, Essex.**

NEW TOOLS

A new range of high quality American tools for electronics are being offered by **West Hyde Developments.** These consist of 4½in curved needle pliers, 5½in long-nosed pliers, 4½in side-cutters and 4in face-cutters.

Made from finest alloy steels, they have p.v.c. handles and are supplied in strong p.v.c. pockets which can be easily hung up.

As well as the tools, there are two mirrors with useful features; one has a magnetic base, the other a variable angle head that can be remotely controlled.

Further details are available from **West Hyde Developments Ltd., Ryefield Crescent, Northwood, Middlesex.**


CATALOGUE

The new 100-page **Electronics Catalogue** from **Tandy** now lists a very large range of components from light emitting diodes and integrated circuits to calculator keyboard and printed circuit etchant kits.


Although the semiconductors seem rather expensive they are all guaranteed to be first quality and not rejects or "fall-outs".

The catalogue is devoted mainly to their vast range of audio hi-fi equipment and includes complete systems. Test gear, car radios and aerials are also included.

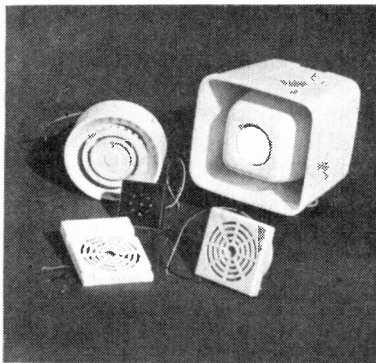
Copies of the 1975/76 **Electronics Catalogue** can be obtained from **Tandy Corporation (Branch UK), Bilston Road, Holyhead Road, Wednesbury, Staffs.**




Ceramic sounders from ITT

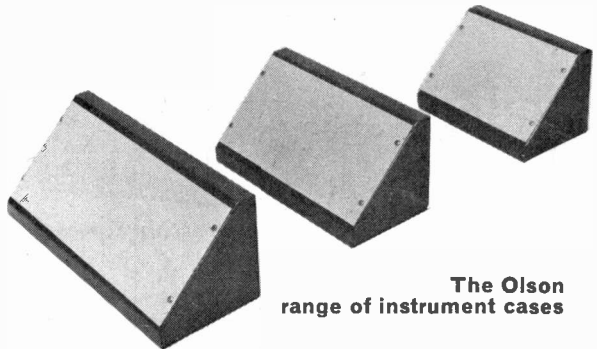

The Olson range of instrument cases

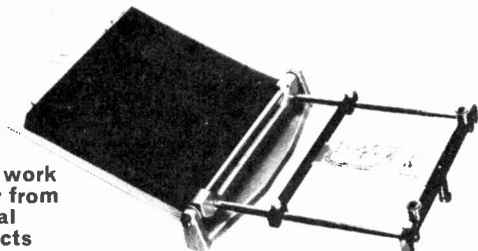

JA500 work holder from Special Products

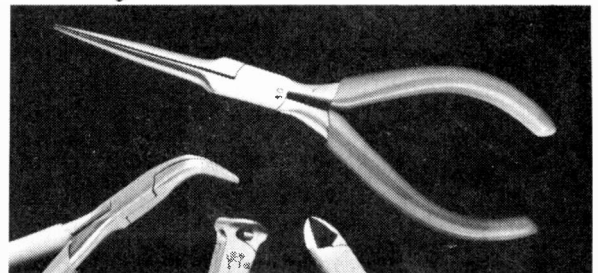

Quality tools from West Hyde

HELPS BELLS AND

DECIBELS

By D. MAYNARD

ONE of the things which usually causes students problems is the use of the decibel. In specifications it is quite common to find it used as the unit for gain. Sometimes the decibel is used for the power gain of an amplifier and sometimes for the voltage gain. Often the unit is used erroneously, and we must be sure of the meaning presented to us.

THE DECIBEL DEFINED

First, let us look at the definition of the decibel. The "deci" means "one tenth of" and the bel is a logarithmic unit of the ratio of two powers. Normally we use the unit when measuring gains or losses. Consider Fig. 1 which shows an amplifier of input impedance Z_1 with a load impedance Z_2 . I_1 and I_2 represent input and output currents, while V_1 and V_2 are input and output voltages respectively.

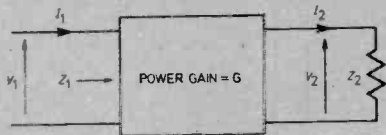


Fig. 1 Loaded power block from which equations are derived

Let us assume that V_1 is 10mV, Z_1 is 10k Ω , V_2 is 10 volts and Z_2 is 10 Ω . Then by Ohm's Law:

$$I_1 = \frac{V_1}{Z_1} = 0.1 \mu\text{A}$$

and

$$I_2 = \frac{V_2}{Z_2} = 1\text{A}$$

Voltages and currents are all r.m.s. Numerically, the power gain (G) is therefore:

$$G = \frac{V_2 \cdot I_2}{V_1 \cdot I_1} = \frac{10 \cdot 1}{10^{-2} \cdot 10^{-7}} = 10^{10}$$

Note that this is a number. It means that the output power is ten thousand million times greater than the input power. The voltage and current gains are respectively:

$$\frac{V_2}{V_1} = 10^3 \text{ and } \frac{I_2}{I_1} = 10^7$$

Obviously the voltage gain multiplied by the current gain is equal to the power gain.

So far we have made no mention in our calculations of decibels. If the input power is P_1 , and the output power P_2 , then the gain in bels is:

$$G = \log_{10} \frac{P_2}{P_1} = 10 \text{ bels}$$

The decibel is only one tenth of a bel and therefore there are ten times more decibels than bels for a given gain.

$$G = 10 \log_{10} \frac{P_2}{P_1} = 100 \text{ decibels}$$

VOLTAGE GAIN IN DECIBELS

We sometimes find voltage gains expressed in decibels, and this is where the error and confusion arise. The definition we used said that the decibel contains a power ratio. We can rewrite our expression for gain as follows:

$$G = 10 \log \frac{V_2^2 \cdot Z_1}{Z_2 \cdot V_1^2} \text{ dB}$$


When, and only when, $Z_1 = Z_2$ we can say that:

$$G = 10 \log \left[\frac{V_2}{V_1} \right]^2 \text{ db which in turn gives us:}$$

$$G = 20 \log \frac{V_2}{V_1} \text{ dB}$$

Students find difficulty in remembering when to use 10 log and when to use 20 log. If in doubt, always use 10 log and always consider power. Having said that we are then faced with information that gives voltage gains in decibels when the input and output impedances of the device are different. Theoretically, the figures are meaningless but in practice the person specifying the gain has used $20 \log V_2/V_1$ regardless of the fact that it does not apply. In our example, the voltage gain would be incorrectly stated as 60dB.

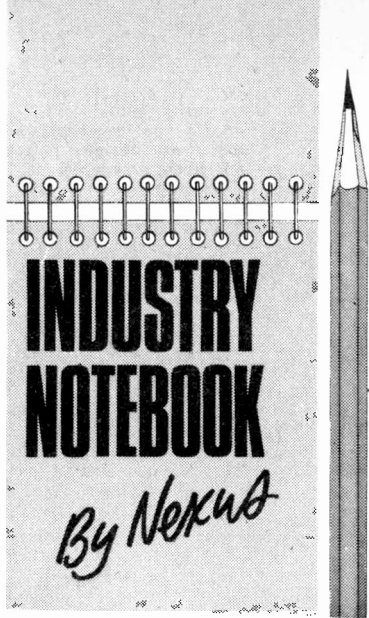Finally, may I appeal to writers of specifications to either stick to power gain figures or else to quote the maximum sensitivity of the amplifier. We would then have the figures we are really interested in. That is the input voltage (and impedance) required to produce the quoted maximum output power. ★



INDUSTRY NOTEBOOK

By Nexus

SALARY AND STATUS

Looking through the situations vacant columns in the professional electronics press it is clear that experienced engineers are still in demand both at home and overseas. But it is equally clear that the salaries offered to professional engineers have increased only relatively marginally during the past three years while unqualified people have enjoyed unprecedented increases in income.

Registered dock workers, for example, now enjoy a guaranteed minimum of £3,000 a year whether they work or not. Coal face workers are in sight of £5,000 a year. Shift workers on London Transport are in the £3,000 to £4,000 bracket, and complaining assembly-line workers in automobile plants are not nearly as bankrupt as their employers. There are even well-authenticated examples of unemployed people drawing up to £5,000 a year from the State, providing they have enough children and hire-purchase commitments.

Now and again one spots what looks, from the salary point of view, a winner. Up to £8,000, for example, was recently offered for a product planning manager in communications technology which, in this instance, meant satellite communications. Candidates were required to have "the maturity, standing and personality to negotiate at all levels from Director downwards and the necessary drive to lead a team in expanding the company's capability in the microwave field and particularly space".

But that was only the beginning. A candidate also needed to have had practical field experience,

have developed hardware, and preferably have commercial experience in the preparation of tenders. He must have knowledge of the national and international agencies concerned with space communications and, of course, all the technical standards in force. It would also be helpful if the candidate had some knowledge of line transmission and analogue and digital modems, multiplexing and switching equipment, data programs and video circuits.

The job entails forecasting the forthcoming market and defining the hardware needed, and producing in collaboration with development engineers, a programme to ensure that hardware is available at the right time at the right price. Quite rightly, the advertisement states that "This is possibly one of the most important appointments to be made in the Company for some time."

Clearly then, this is a key job which was no doubt keenly contested and ably filled. But it seems strange that such an important position, central to the company's future prosperity and that of possibly hundreds of work people should, in gross money terms, be worth no more than two bus drivers or one and a half hewers of coal, however worthy the drivers and hewers may be. After tax, of course, the differential becomes even less attractive.

MAINSTREAM

If we now drop our sights a little and look at the mainstream of engineers we find experienced chartered engineers attracting salaries in the range £3,000 to £4,000 and technician engineers from £2,000 to a little over £3,000 for the best people.

Generally, the best payers are the Civil Service and the nationalised corporations. But, even here, salaries tend to be low. A communications technician for a gas board with at least five years' experience of u.h.f./v.h.f. mobile radio and a sound knowledge of the principles of microwave/multiplex links and digital systems can start with as little as £2,361.

At an armed services resettlement briefing for electronics tradesmen earlier this year, people soon to leave the services were surprised and dismayed to learn that their service pay and allowances were superior to the salaries they could command in "civvy street". They were mostly mature people, many with family responsibilities, to whom a salary of £2,500 and the need to find accommodation represented a major fall in standard of living and probably quality of life as well. They'd be better off to stay on.

WORK OF LOVE

From a strictly financial point of view electronic engineers, be they of chartered or technician status or even totally unqualified academically, are their own worst enemies. They tend to love their work and regard it as a vocation more than a job. If they need to have employment to live, then there is nothing they'd rather be in than electronics with its ever-changing technology and novelty, and its intellectual challenge. Provided they were receiving a reasonable reward they were contented.

Unhappily, 25 per cent per annum inflation has overtaken the professional electronics engineer, and those in the lower pay brackets are now barely above the poverty line. With inflation currently at 15 per cent and scheduled not to drop to single figures before the end of the year, the more poorly paid will soon be in distress and the better-off still steadily sinking in real terms.

POINT OF CONFLICT

The Council of Engineering Institutes has now come out firmly with the proposal that professional engineers should join a trade union. By the Government sanctioning and even encouraging the widespread introduction of the closed shop, this move was perhaps inevitable. A great number of engineers will discover that if they are not union members they will have no job. A second compelling reason for the recommendation is that union muscle, ruthlessly applied, always achieves its objective. This is an established fact of which there are many recent examples.

The professional engineers are now in a dilemma. Professionally they have one code of conduct and as union members they will have another and these will often be in conflict. In a universally closed shop, to defy union instruction can mean expulsion from the union and thus expulsion from employment for the remainder of a working life. But equally, to comply with union instruction may involve both agonies of conscience and breaches of professional codes of conduct.

How this muddle of loyalties will be resolved remains to be seen. Perhaps there is no solution except to emigrate to the United States or West Germany where industrial affairs are conducted more logically and where real merit is rewarded realistically.

MULTIPLE OCTAVE ORGAN

THIS is my original circuit for a simple organ, using the NE555V, which can play through several musical octaves on a limited keyboard of eight keys in two different ways.

The circuit (Fig. 1a) uses a NE555V operated in its astable mode, frequency of oscillation being given

$$\text{as } f_1 = \frac{1}{T} = \frac{1.44}{(R_{in} 8 + 2R_B)C}$$

$$\text{Thus } \frac{f_2}{f_1} = \frac{R_{A1} + 2R_{B1}}{R_{A2} + 2R_{B2}}$$

The musical notes are in the ratio of 9/8 : 10/9 : 16/15 : 9/8 : 10/9 : 9/8 : 16/15.

This also shows that the musical ratio depends only on the ratio of the resistors R1 to R8, R_B being kept constant; also the capacitor between pin 6 and pin 1 of IC1 kept constant.

From eqn 1, with the note C at 262Hz, S1 at 2:

R1=53kΩ (i.e. 33kΩ + 20kΩ)

R2=47kΩ

R3=42kΩ (i.e. 20kΩ + 22kΩ)

R4=39kΩ


R5=34.5kΩ (i.e. 33kΩ + 1.5 kΩ)

R6=30kΩ

R7=27kΩ

R8=25.8kΩ (i.e. 24kΩ + 1.8kΩ).

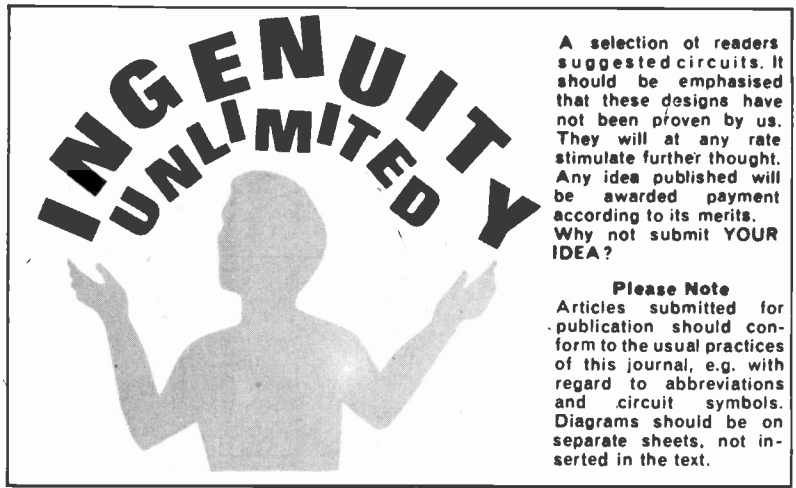S1 is a single pole, 3-way switch used for octave selection. At position 1 the notes range from C₁ to C₁'', i.e. 131Hz to 262Hz. Similarly at position 2, the range is C' to C'' (262-524Hz) and position 3 covers C'''-C''' (524Hz-1,024Hz).



A selection of readers suggested circuits. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought. Any idea published will be awarded payment according to its merits. Why not submit YOUR IDEA?

Please Note

Articles submitted for publication should conform to the usual practices of this journal, e.g. with regard to abbreviations and circuit symbols. Diagrams should be on separate sheets, not inserted in the text.

As the organ notes consist of a pulse of fixed duration (determined by R_B and capacitor selected by S1) repeated at musical frequencies, it is desirable to clamp the output pulses to a fixed duration to produce a "smooth" octave selection. A suitable monostable circuit using a NE555V is shown in Fig. 1b.

One of the inherent disadvantages of a simple organ is that the pressing of two or more keys will give only a note. However, this is exploited here to play two musical octaves on the eight keys without using the octave selection switch S1. It can be shown from eqn 1 that pressing key c' and key d' will produce note of C'' and that this occurs systematically as shown in Fig. 1c below.

This method will enable one to play notes in the upper octave without bothering to operate S1.

The output is melodious as it consists of a pulse of short duration repeated at musical frequencies; a tweeter is recommended at the amplifier output to reproduce these short pulses more clearly. For simplicity the semitone keys are omitted but can easily be added by calculating the required resistor from eqn 1. With the semitone keys added, there will be 13 keys and the corresponding ratio of each frequency to the one before it is 1.0595. Since the musical ratio is virtually dependent on R1 to R8, they should be preferably better than ±5 per cent. Close tolerance capacitors should be used for S1 for octave selection as they maintain musical ratios of the musical octaves.

Pek Yaw Kee,
Sarawak, E. Malaysia.

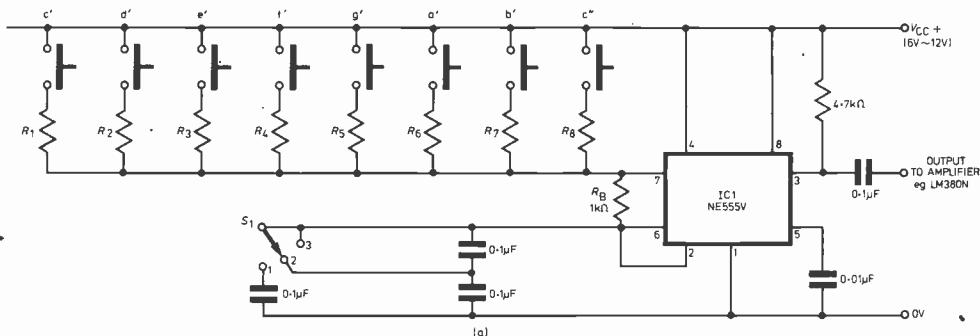


Fig. 1a

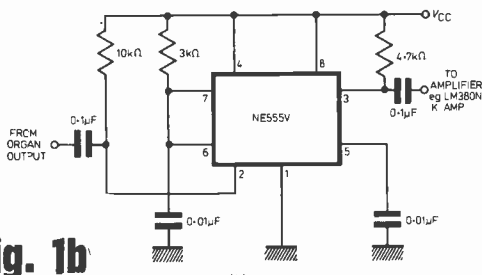


Fig. 1b

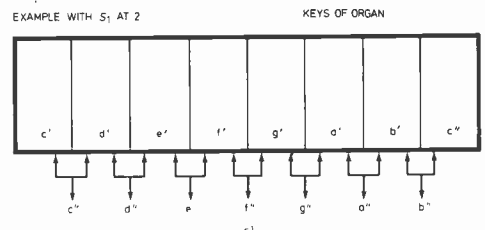


Fig. 1c

AUTOMATIC TIME SWITCH

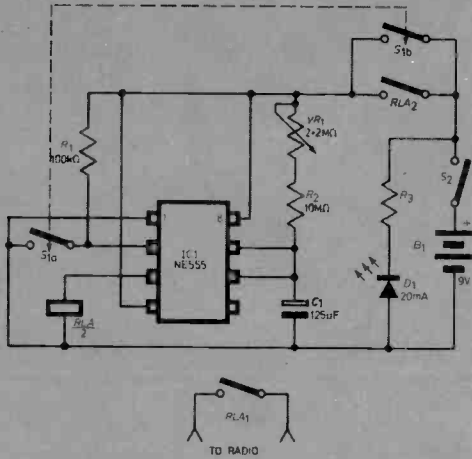


Fig. 1

THIS automatic time switch was designed to switch a radio and itself off after about half-an-hour, so that I could leave the radio on and go to sleep. The tuner has a start/reset switch which is illuminated by an l.e.d., see Fig. 1.

The circuit uses a NE555 timer as a monostable. The delay period is adjusted by VR1 which compensates for the tolerances of R2 and C1. The relay is a 6V 2-pole make type, with as high a coil resistance as possible. S1 is a 2-pole make switch and K3 is selected to suit the l.e.d. The relay contacts RLA1 interrupt the positive supply line to the radio.

P. Levey,
London, S.E.26.

FURTHER USES FOR UNIJUNCTIONS

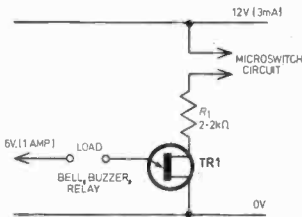


Fig. 1. Burglar Alarm

RARELY does one see the Unijunction transistor being put to any use other than as a relaxation oscillator. It can of course be put to many diverse uses.

In Fig. 1 it is used as a Burglar Alarm. Even if the microswitch circuit is remade after it is broken the bell, buzzer, etc. will stay on. Most common unijunction transistors will sink up to one amp. and so relatively heavy loads can be used without resorting to a relay. To reset the alarm, one of the load leads is broken.

In Fig. 2 the Unijunction transistor is used as a Frequency Divider.

If half-wave rectified a.c. from the mains is put in the input, the first stage divides by five, as with the second, and the third divides by two. Surplus unijunctions and transistors can be used, but the capacitor charging resistors may have to be changed. Generally if each stage is disconnected from the previous one, it should run at a slightly lower frequency than its expected working frequency. The circuit can be adapted readily for other applications as it is cheaper than TTL dividers.

A. F. Rabagliati,
Oundle, Northants.

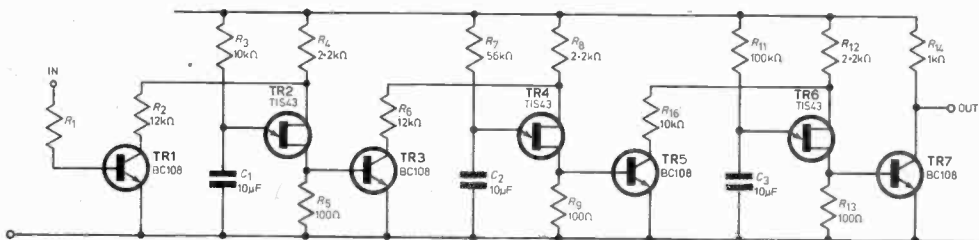


Fig. 2. Frequency Divider

DORAM


A PROFESSIONAL DEAL FOR AMATEURS

*ORDERS BY RETURN OF POST *NO QUIBBLE REPLACEMENT PART SERVICE
*QUALITY BRANDED PRODUCTS *FREE UP-DATE INFORMATION SERVICE

TOOLS

The handy EXPO 12V d.c. drill is supplied complete with drill kit containing 4 small drills, two spare collets, two cutters, wire brush, soft buffer, grindstone and 9 various milling and reaming tools.

Drill & kit £9.50 + s
Kit only £4.75 + s

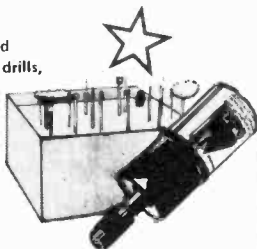

ORYX 50W SOLDERING IRON



Temperature can be altered between 200-400°C.

Iron 240V £6.90 + s
Stand £2.80 + s

ISO-TIP CORDLESS IRON

Mains and 12V d.c. versions available
£11.50 + s



DE-SOLDER TOOLS

Three high-suction models available

SR2 £6.20 + s
SR3 £5.20 + s
SR3AS £4.80 + s

Spare nozzle 60p ea. + s
Please state type



NICKEL - CADMIUM RECHARGEABLE CELLS

	Sim. to dry cell	nom. capacity	charge cur. (mA)	
HP7	0.5Ah	50	£1.10 s	
None	1-2Ah	100	£1.24 s	
HP11	2.0Ah	200	£1.80 s	
HP2	4.0Ah	400	£2.70 s	

ELECTRONIC IGNITION UNIT

- High performance
- For 2 & 4 stroke engines
- Improved start/running
- 'Crisper' throttle response
- Reduce battery drain

Neg. earth or pos. earth


£15.00 + s

Please state type required



BATTERY ELIMINATOR

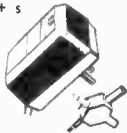Switched output 6, 7.5 or 9V at 250mA.
D.C. pos. or neg. earth
£3.15 + s



SEMI-CONDUCTOR DEVICES

RECTIFIERS


IN 4001 - 5p ea.)
IN 4002 - 6p ea.) + s
IN 4003 - 6p ea.)

1-0A bridge (400V) - 32p + H
1.6A " (200V) - 48p + H
1.6A " (800V) - 70p + H
2.0A " (200V) - 72p + H
2.0A " (600V) - 90p + H



MULLARD MODULES

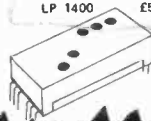LP 1173 - £6.10 + H
LP 1184/2 - £6.58 + H
LP 1185 - £4.50 + H
LP 1186 - £6.22 + H
LP 1400 - £5.15 + H



BIG PRICE REDUCTIONS

TRANSISTORS

BC 107 - 12p s
BC 108 - 11p s
BC 109 - 12p s
BFY 50 - 20p s
BFY 51 - 19p s
BFY 52 - 20p s
2N 3055 - 62p s
2N 2646 - 94p s
TIP 2955 £1.14 s
TIP 3055 - 61p s
BC 237B - 11p H
BC 238C - 10p H
BC 239C - 12p H
ZTX 107 - 10p H
ZTX 108 - 9p H
ZTX 109 - 12p H
ZTX 300 - 13p H
ZTX 500 - 14p H
MJE 340 - 62p H
TIP 31A - 36p H
TIP 32A - 40p H
2N 3819 - 27p H
3N 141 - 65p s
CS 715 - 18p H
10 for £1.50 H

(Similar to 2N 3819)
BF 180 - 40p s
BRY39 - 72p s

I.C.'s

T05 Reg - £1.10 s
MVR 5 - £1.55 s
MVR 12 - £1.55 s
MVR 15 - £1.55 s
LM 309K - £1.95 s
7805 - £1.50 s
7812 - £1.50 s
7815 - £1.50 s
7824 - £1.50 s
±15V D.I.L. - £2.82 s
TBA 231 - £1.50 H
TBA 800 - £1.20 H
TBA 810S - £1.30 H
TBA 820 - £1.00 H
ZN 414 - £1.30 H
ZN 424 - £1.25 H
741 Op-amp - 36p s
747 Op-amp (Dual 7411) - 95p s
748 Op-amp - 48p s
555 TIMER - 56p s
556 (dual 555) - £1.10 s
HA 1156 (similar to MC1310P) - £1.60 H
ORP12 - 72p s
8A Triac - £1.18 s
ZN 1034E - £4.70 s



'INTERNATIONAL 25'

Build yourself a **BIG SOUND amp** at a budget price



As featured in 'ETI' Oct. 75 edition

- #### FEATURES
- Triple Op-amp pre-amplifier
 - Power 'Darlington's'
 - Modern styling
 - 25W per channel into 8 ohms.

Complete kit with assembly instructions
Overseas orders £34.50
S.A.E. for full spec.

£29-95
+ £7.48 VAT

BOOKS (z)

Hi-fi hints and tips - 38p ea.
Towers international transistor selector - £2.95 ea.
Electronic circuit design handbook - a must for electronic enthusiasts - £4.50 ea.

CONDITIONS OF SALE

All prices are ex-VAT
If affixed with s add 8%
If affixed with H add 25%
Z = Zero rated
Package & posting free for orders over £3.00
Overseas orders add 15%
Cash with order. Cheques/Postal Orders to Doram Electronics Limited, P.O. Box TR8, Leeds, LS12 2UF
Small order handling charge of 40p for orders under £3.00

DORAM'S NEW CATALOGUE - THE AMATEURS GOOD COMPANION




ONLY 60p

inc. post & packing.
Free up-date service until Aug. 1976.

'SAMOS' CASES

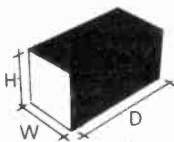Low-cost blue cover and white base PVC steel cases



S1 50W x 50H x 100D £1.03 + s
S2 100W x 50H x 100D £1.17 + s
S3 150W x 50H x 100D £1.31 + s
S4 50W x 75H x 125D £1.47 + s
S5 100W x 75H x 125D £1.68 + s
S6 150W x 75H x 125D £1.97 + s
S7 200W x 75H x 125D £2.19 + s

SPECIAL OFFER!!

If catalogue ordered simultaneously with order for SAMOS cases - case price less 25%

DORAM "The Doorway to Amateur Electronics"
An Electrocomponents Group Company

NAME


ADDRESS

POST CODE


I enclose 60p. Please send me by return my Doram Catalogue.
(Overseas orders except B.F.P.O. please add 30p for post and packing surface only).

PRECISION PETITE LTD. Dept. P.E.
119A HIGH STREET,
TEDDINGTON TW11 8HG
Tel. 01-977 0878

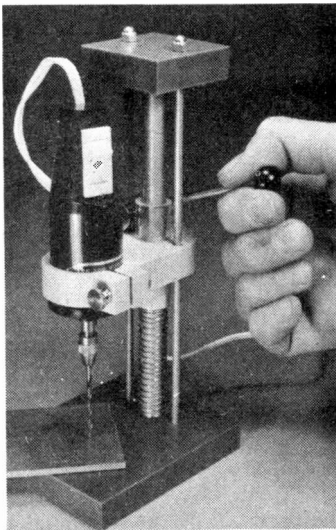**INTRODUCING A
MINIATURE
PRECISION 12V. D.C.
DRILL DESIGNED FOR
THE ELECTRONIC
ENGINEER**



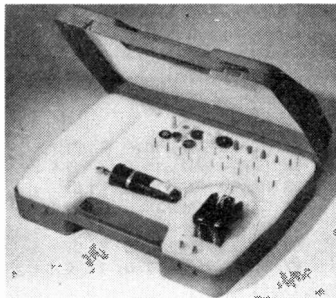Mk. II Drill only
£8.00 p.p. 35p
Stand
£3.76 p.p. 58p



Complete kit as illustrated (less batts.)
with a variety of 30 tools. Space for
Stand and Transformer.

KIT 30 TOOLS £16.00 p.p. 75p
STAND £3.76 p.p. 35p
TRANSFORMER £5.50 p.p. 75p

**S.A.E. FOR
DETAILS**

**P.E. JOANNA
Electronic
Piano**



**ALL PARTS CAN BE
SUPPLIED**

Keyboard, Keyswitch, P.C.B.s,
Hardware, Semiconductors,
Resistors, Capacitors, Cabinets
Complete kits or easy stages

Send S.A.E. for details

Clef Products

31 Mountfield Road, Bramhall
Stockport, Cheshire SK7 1LY

**HB ELECTRONICS
Mini
Bulk Offers**

All devices brand new and full spec. All
prices include VAT.

IN4001/2	30p/10	BC108	75p/10
IN4003/4/5	45p/10	BC109	75p/10
IN4006/7	50p/10	741 8 diil	£1.95/10
IN4148	20p/10	NE555	£1.80/4
BC107	75p/10	Red LED	£1.00/10

Mini or sub-mini slide switches £1.50/10
Micro switches £1.50/5

74 SERIES TTL

Type	Price	Type	Price	Type	Price
7401	12p	7441	62p	7482	45p
7402	12p	7442	55p	7483	40p
7403	12p	7445	71p	74100	89p
7404	13p	7447	79p	74121	28p
7405	15p	7474	26p	74122	39p
7406	30p	7476	25p	74141	83p
7408	15p	7483	75p	74145	58p
7410	13p	7486	26p	74174	83p
7413	31p	7409	40p	74177	£1.00
7432	25p	7491	55p	74196	£1.34

10% discount may be deducted from TTL prices for
orders of 25 pieces or more.
400mV Zener 3 to 30V 12p each. Wafer switches 50p
each. Submin. presets 10p each. 80 ohm 3 n speakers
65p each. 10W impedance earphones 20p each. $\frac{1}{2}$ W
(E12 values) resistors 2p each. Veroboard 0-1 and 0-15
2 1/2in x 5in 45p each. Car radio supra. 0-05uF 150V 20p
each. 35 ohm 3in speakers £1.55 each. C80 35p each.
C90 55p each.
Please send S.A.E. for enquiries or full component
lists. Please add 30p P. & P. on all orders under £5,
otherwise post free.
All above prices are mail order only. Shop prices may
differ.

HB ELECTRONICS

54 MONTAGU STREET, KETTERING
NORTHANTS. Phone Kettering 83922

SHOP OPEN DAILY 9:00-6:00
Access and Barclaycard orders welcome for
orders over £2.

GIRO NO 331 7056 Access and Barclay
card accepted
C.W.O. only Terms of business as in
our Catalogue
Export Order enquiries welcome (15 min.)
E & OE

1976 ISSUE 86 PAGES—3,000 ITEMS
FULLY ILLUSTRATED
*20p CREDIT
VOUCHERS
*ALL NEW STOCK
*SATISFACTION
GUARANTEED
*DISCOUNTS
*NEW PRICE LIST
FOR CAT. 4a S.A.E.

20p
plus 10p
postage

**TRONIC
COMPONENTS
Catalogue 5**

ATORS LTD.


Boxes — Cases —
Kits — PC Materials —
Tools — Resistors — Test
Meters — Capacitors —
Hardware — Semiconduc-
tors — Books — Post — Coils
— Audio Accessories — Screws
Connectors — Audio — Modules
— Veroboard — Transformers—
Knobs — Calculators — Audio Leads
— Batteries — S dec Storage Units —
Heatinks, etc., etc.

SPECIAL CAPACITOR KITS
C280 Kit—PC Mounting polyester 250V 5 of each
value: 0.01, 0.022, 0.047, 0.1, 0.22uF. 2 of 0.47, 1uF.
£1.88 net
C296 Kit—Tubular polyester. 400V. 5 of each value
0.01, 0.022, 0.047, 0.1, 0.22uF. 2 of 0.47uF. £2.67 net
Ceramic Kit—square plaque. 50V 5 of each value.
22, 33, 47, 100, 220, 330, 470, 1000pF. 220, 470pF.
0.01uF. £1.88 net.

SPECIAL RESISTOR KITS (CARBON FILM 5%) (Prices
include post & packing) 10E12 $\frac{1}{2}$ W or $\frac{1}{4}$ W KIT. 10 of
each E12 value, 22 ohms—1M. a total of 570 £5.29 net
25E12 $\frac{1}{2}$ W or $\frac{1}{4}$ W KIT. 25 of each E12 value, 22ohms—
1M. a total of 1425 £12.84 net

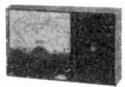
B. H. COMPONENT FACTORS LTD.

MULTIMETER U4323
22 Ranges plus AF/IF Oscilla-
tor 20,000V/Volt.
Vdc—0.5—1000V in 7 ranges
Vac—2.5—1000V in 6 ranges
Idc—0.05—500mA in 5 ranges
Resistance—3 Ω —1M Ω in 4
ranges
Accuracy—5% of F.S.D.
OSCILLATOR—1KHz and
485KHz (A.M.) at approx. 1 Volt.
Size—160 x 97 x 40mm.
Supplied complete with carrying
case, test leads and battery.
PRICE £9.95 net P. & P. 75p




U4323

MULTIMETER U4324
34 Ranges. High sensitivity.
20,000V/Volt.
Vdc—0.5—1200V in 9 ranges.
Vac—3—900V in 8 ranges.
Idc—0.06—3A in 6 ranges.
Iac—0.3—3A in 5 ranges.
Resistance—25 Ω —5M Ω in 5 ranges
Accuracy—dc and R—2 1/2% of F.S.D.
ac and db—4% of F.S.D.
Size—167 x 98 x 63mm.
Supplied complete with storage case,
test leads, spare diode and battery
PRICE £11.72 net P. & P. 75p




U4324

MULTIMETER U4341
27 Ranges plus Transistor Tester
16,700V/Volt.
Vdc—0.3—900V in 8 ranges
Vac—1.5—750V in 6 ranges
Idc—0.06—800mA in 5 ranges
Iac—0.3—300mA in 4 ranges.
Resistance—2K Ω —2M Ω in
4 ranges. Accuracy—dc—2 1/2%
ac—4% of F.S.D.
Ife—10—350 in 2 ranges.
Size—115 x 215 x 90mm.
Complete with carrying
case, test leads, and battery
PRICE £12.10 net P. & P. 75p



U4341

MULTIMETER U4313
33 ranges. Knife edge with mirror scale.
20,000V/Volt. High accuracy. mVdc—75mV.
Vdc—1.5—600V in 9 ranges
Vac—1.5—600V in 9 ranges
Idc—80—120 microamps in 2
Idc—0.6—1500mA in 6 ranges
Iac—0.6—1500mA in 6 ranges
Resistance—1K Ω —1M Ω in 4 ranges
db scale—10 to +12db
Accuracy—dc—1 1/2%, ac—2 1/2%
Size—115 x 215 x 90mm
Complete with carrying case,
test leads, and battery
PRICE £16.09 net P. & P. 75p



U4313

(P.E.), LEIGHTON ELECTRONICS CENTRE,
59 NORTH STREET, LEIGHTON BUZZARD, LU7 7EG.
Tel. Leighton Buzzard 2316 (Std. Code 05253)

VISUAL INDICATOR FOR DISCOTHEQUE PFL SYSTEMS

READERS who run mobile discotheques, like myself, may be interested in this simple yet effective visual cueing device to be used in place of headphones on existing equipment with PFL (Pre-fade-listen) facilities. For those readers not familiar with PFL, it is a system which allows the operator or DJ to locate the start of a second record whilst a first is playing, and so eliminate the time gap between one record and the next.

This device described, gives the operator a visual indication of the start of a record by means of an l.e.d. modulated in brightness by the music signal.

The circuit, see Fig. 1, consists of an REC70 bridge rectifier D1 and a small red l.e.d. type TIL209, D2, connected as shown. The music signal is rectified by the bridge and produces a varying d.c. voltage across the l.e.d.

The prototype was constructed inside a standard jack plug, of the type with a long plastic barrel, see Fig. 2.

The system has been tested with several makes of disc mixer, and found very successful. In most cases a gain control for the PFL is incor-

Fig. 1


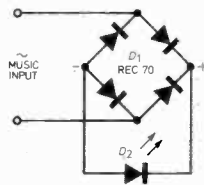


Fig. 2

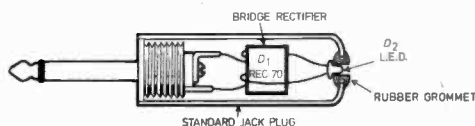

porated in the mixer, and when using the visual cueing light, this invariably needs to be set at maximum for highest sensitivity. In this case the d.c. peak voltage is unlikely to exceed 3V and result in any damage to the l.e.d. With this setting, it may be found that once

the record is playing the l.e.d. appears continuously on, but this is no disadvantage as the cueing light has only to indicate the start of the record.

S. E. Grist,
Guildford,
Surrey.

"LIGHTS ON" INDICATOR

THIS is a useful aid for motorists in that it gives a warning that the car lights are still on when attempting to get out of it.

The circuit (Fig. 1) is a simple unijunction transistor oscillator which gives a continuous note for about five seconds when the door is opened, that is, when the door switch is closed. The period setting can be changed by altering the value of C2.

When power is removed from the circuit it will reset in five minutes.

As the audible warning is for negative earth vehicles, for positive earth interchange connections at A and B.

R. A. Sudron,
Shadwell.

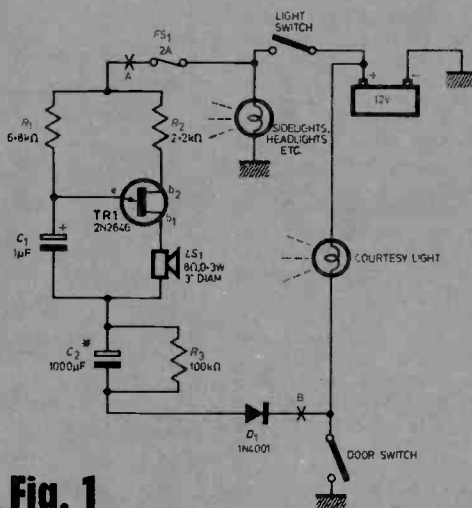


Fig. 1

COURTESY LIGHT TIMER

THE circuit in Fig. 1 is designed to extinguish a car interior light approximately 20 seconds after the car door is closed, allowing time to fasten seat belts, etc. The timer starts when the switch contacts open, and the light is extinguished automatically after the delay period has elapsed.

TR3 and Darlington pair TR4 and TR5 form a complementary bistable which is triggered on when TR5 collector is earthed by the switch S1, whose contacts carry the current for the interior lamp, LP1.

When S1 contacts open, the lamp current flows through TR5. About 1.5V is dropped across this, turning on TR1 via R3; C1 then charges through TR1 and R1. When C1 has charged to about 5V, TR2 conducts and diverts base current from TR3. The bistable then turns rapidly into the off state, discharging C1 via D1 and R2 ready for the next operation. Battery drain in the off state is about 1mA, which is taken by R3.

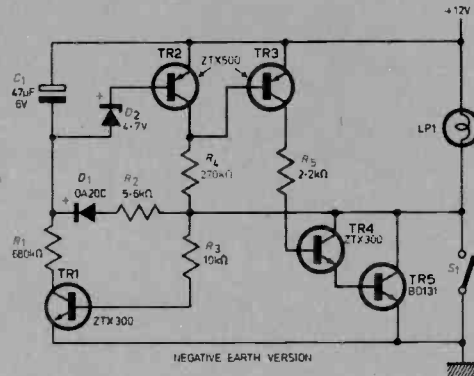


Fig. 1

For loads of up to 6W no heat-sink is needed for TR5 and a very compact unit can be built, possibly in the lamp housing itself. Loads of up to 36W can be switched with a heatsink. If the load is shorted the bistable should switch off without damage.

The circuit shown is for negative earth vehicles. A positive earth version can be made using a BD132 for TR5, transposing ZTX300 and ZTX500 transistors and reversing the polarities of C1, D1 and D2.

P. Albericci,
Stockport

THE following might be of interest to some of your photographically minded readers.

The latest fashion for Dual Fade Slide Presentation seemed a natural subject for solid state control, so triac circuitry came to mind. Most modern slide projectors use a low voltage halogen lamp and the low voltages necessitated a slightly different approach to circuitry.

Fig. 1 shows the basic interface circuitry which was built into a projector. This had spare pins available on its standard 6-pin DIN socket (pin 3 to earth, pin 2 is the slide change solenoid). The triac is simply wired in parallel with the existing lamp on/off switch.

Fig. 2 shows the simple manual control used to fade the projector lamp. Zeners D1, D2 take the place of the diac used in mains voltage circuits. The high value of capacitance is required to provide the relatively large gate current to the triac which is sluggish in the low voltage conditions. VR1 is a slider potentiometer for ease of use during a show, and VR2 is a pre-set which enables the full scale of the slider to be used.

A pair of projectors using this circuitry has been used for several successful slide-tape shows and the

DUAL FADE FOR SLIDE PRESENTATION

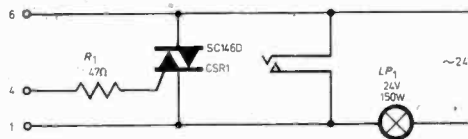


Fig. 1

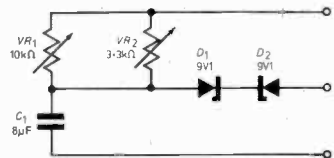


Fig. 2


colour change of the lamps during dimming has not been found to be objectionable.

A simple remote control of the lamp can be provided by a switch between pins 4 and 6. A tape con-

trol system is being developed using circuitry similar to the voltage controlled dimmer in *Ingenuity Unlimited* page 320, April 75.

P. Woods,
Meanor, Derbys.

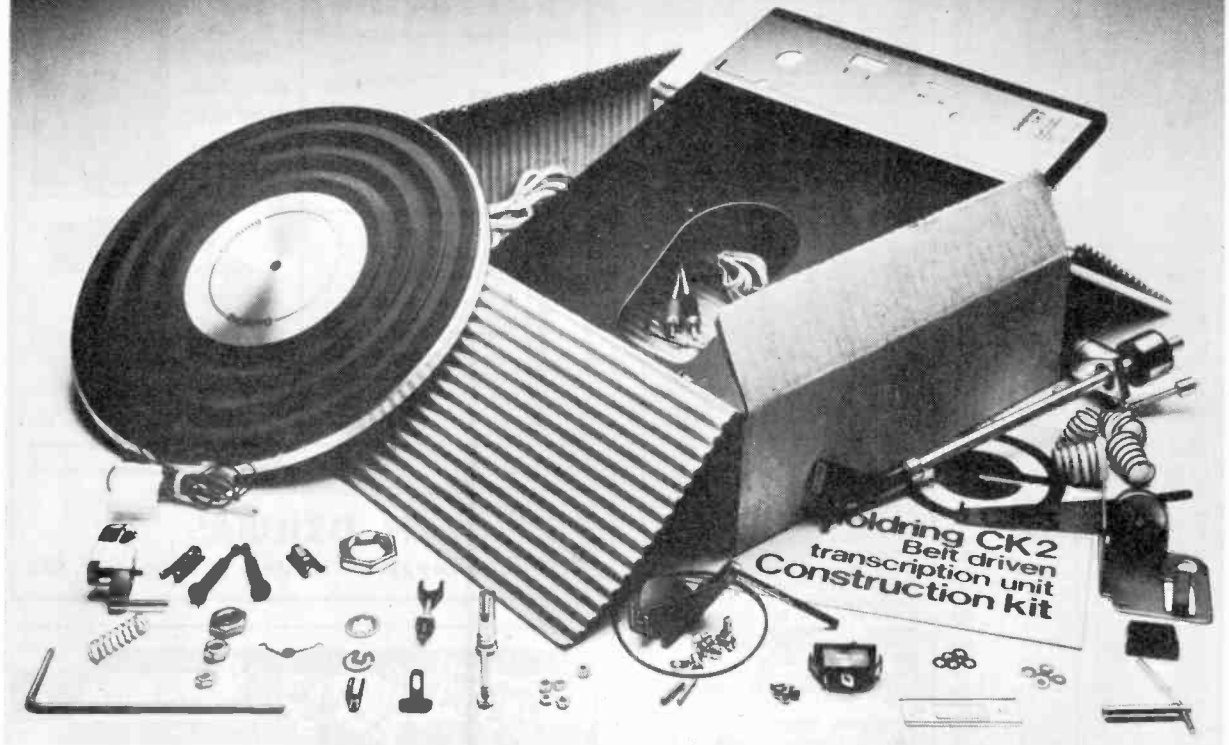How to get a reputation overnight for making Hi Fi equipment as good as ours.



To be perfectly honest, it's not that difficult.

Simply go out and buy a Goldring CK2 turntable construction kit. Follow the simple step by step instructions.

And in no time at all you'll be the proud owner of a superb, hand built, precision engineered deck.

Which can hardly fail to make your reputation amongst those who know about HiFi. And all achieved with the minimum capital outlay: around £28.00.

The Goldring CK2 kit is, in fact, based around the rather more widely known G102 turntable.

Which means it's belt driven, to reduce wow, flutter and rumble to an absolute minimum. (The same system most really expensive decks employ.)

The pick-up arm features a viscously damped raising and lowering device.

For the protection of your records, there's an anti-skate mechanism. And with an

easily adjustable playing weight, the arm will accept a wide range of cartridges, such as the Goldring G800.

A final touch is that both the on-off function and speed selection are via neat rocker switches.

If you fill in the coupon, we'll send you our free colour brochure, which describes the CK2 construction unit in detail.

And if you're serious about HiFi, you couldn't hope to ask for a better start than that.



To: Goldring Limited, 10 Bayford Street, Hackney, London E8 3SE.
Please tell me more about the Goldring CK2 Construction unit.

Name _____

Address _____

PE.5.76



THIS circuit (Fig. 1) was designed for use with an electronic voltmeter to indicate when the battery voltage falls below 7.5V where the accuracy of the meter begins to deteriorate.

The circuit can be made to switch at any voltage by altering R1, R2, D1, and by swapping pins 2 and 3 there is a choice of either normally on or normally off operation. The normally off arrangement is shown as in this state the circuit only takes 1.4mA.

P. Boscott,
Banbury

LOW VOLTAGE INDICATOR

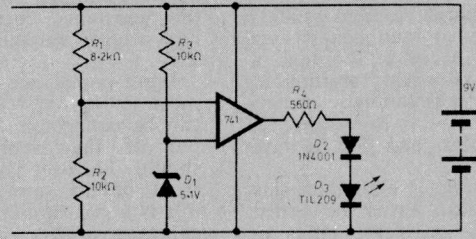


Fig. 1

CAR ALARM

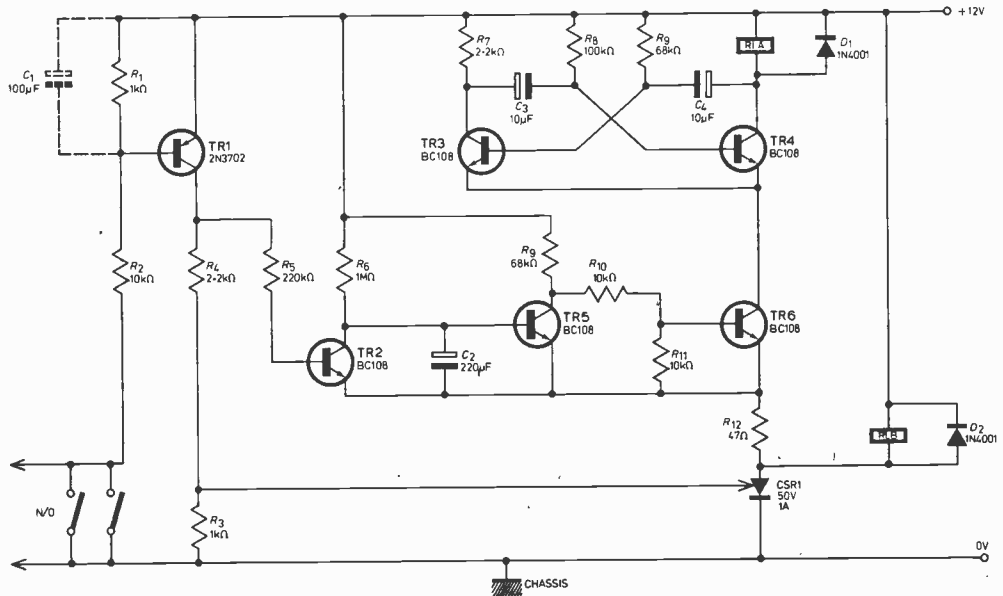


Fig. 1

THE requirements to be met for the car alarm were that it should give an audible/visual alarm for a preset interval and then reset to a "ready" state, the car meanwhile being immobilised. The quiescent power consumption must also be low.

The following circuit was devised which gives an alarm lasting about 20 seconds (bleeps horn and/or flashes headlamps) and breaks the ignition circuit, after which it resets ready to be triggered again. The methods used to trigger the alarm are door courtesy switches and/or a trembler switch. This alarm has the advantage over other types that it attracts attention and immobilises the car, but does so without being a public nuisance and without draining the battery (the alarm might be set off by an innocent party accidentally).

With power applied, in the quiescent state, the CSR1 is switched off and current is only drawn through

TR2, this being about 20 microamps.

If any of the alarm switches are earthed TR1 conducts, both causing TR2 to conduct and switching on the CSR. TR2 thus shorts the timing capacitor each time a switch is made and the timing period starts from this point. The CSR supplies power to the Schmitt trigger and, as TR6 is conducting initially, to the multivibrator. RLA contacts then open and close periodically to give the alarm. These contacts can be connected to the horn or headlamps but must therefore be of suitable rating. The writer used a miniature 700 ohm relay which closed at 20 milliamps and fitted heavier 5 amp contacts salvaged from defunct microswitches so obtaining a 10 amp capacity relay at low cost.

As the timing capacitor charges up, TR5 base voltage is raised until the Schmitt switches, TR6 being cut off and TR5 conducting. TR5's current is less than the hold-

ing current of the CSR which switches off, leaving the circuit in its quiescent state again.

Relay RLB is enabled when the CSR is on, and must be a latching type, either electrically or mechanically. The latter is probably preferable as the ignition reset switch can be hidden away.

If trouble is experienced by spurious triggering of the alarm, this should be cured by connecting a capacitor across TR1 base as shown and decoupling the supply if required.

Layout is completely non-critical, as are components. BC108's were used because they were to hand, but lower gain types are suitable. Note that TR1 is *pnp*, the rest are *nnp*. The CSR was a surplus item. The time delay can be altered by varying the values of R6 and C2.

D. W. Bickley,
Wolverhampton.

RECORDING LEVEL INDICATOR

ORDINARY tape recorder VU meters cannot respond quickly enough to sudden loud peaks. One can therefore record at too high a level without knowing, resulting in distortion. Peak-reading meters solve this problem to some degree, but are complex and not always totally successful.

The circuit (Fig. 1) eliminates this problem, and can easily be added to almost any transistor tape recorder. If the peak level of the input a.c. signal exceeds a certain level,

the 555 timer wired as a monostable is triggered, illuminating the l.e.d. for about 0.4 sec, as a warning that the recording level is too high. VR1 sets the trigger level, low resistance corresponding to a high trigger voltage, between 0 and 2.5V.

Input impedance is over 10k Ω for most settings of VR1, and the unit can be connected direct to the output of the record amplifier. It should however be connected in front of the tape head driver, as this is a constant-current driver, not constant-voltage.

D1 may be any l.e.d. D2, C3 and R4 stabilise the trigger level against

changes of V_{cc} . If V_{cc} is stabilised, these components can be omitted, connecting point X to V_{cc} and leaving pin 5 of the NE555 unconnected. VR1 should now be 100k Ω . This circuit will work for any V_{cc} from 6 to 15V, although R2 may need reducing to 680 Ω at low voltages. The maximum current demand with l.e.d. on, is 20mA, and less than 5mA with it off. In use, it is best to set it to trigger at a level corresponding to +2-3dB record level.

N. R. Arnot,
Welwyn Garden City,
Herts.

TOUCH KEYBOARD

FOR those not wishing to spend £20 on keyboard mechanics for their synthesiser, I have devised an electronic alternative.

The complete circuit is shown in Fig. 1. The contacts are made by etching a keyboard on fibreglass p.c.b. The circuit marked A is dupli-

cated for as many keys as required. A finger pressed on the contacts switches the transistor pair, producing about 5.3V across the resistor. The diodes "code" the key position into a 6-bit binary signal passing on to circuit B. (The key shown is the 13th.)

This circuit is a sampling digital-analogue convertor, which takes an input from the keyboard when a key is pressed.

The output may be taken to a

buffer stage as shown, allowing the keyboard to be compressed, expanded or offset up and down the spectrum. An integrator would produce a portamento effect.

A typical key design is shown in Fig. 2. If single plate operation is required the circuit of Fig. 3 could replace the two transistor circuit of Fig. 1, but it may be found unreliable.

N. B. Sargeant,
Fleet.

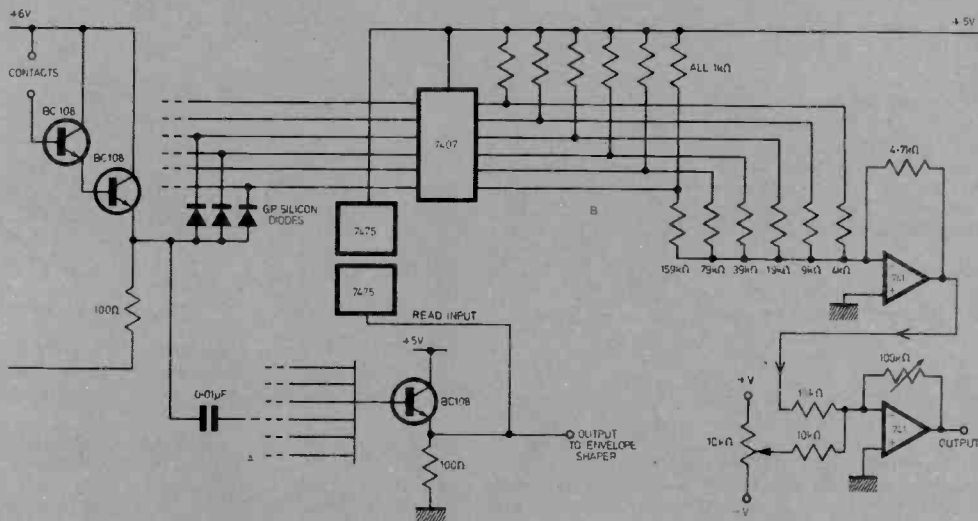


Fig. 1

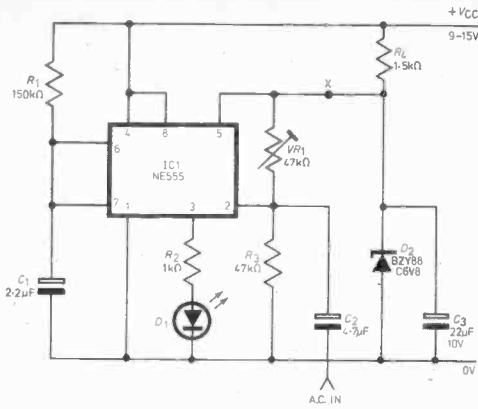


Fig. 1

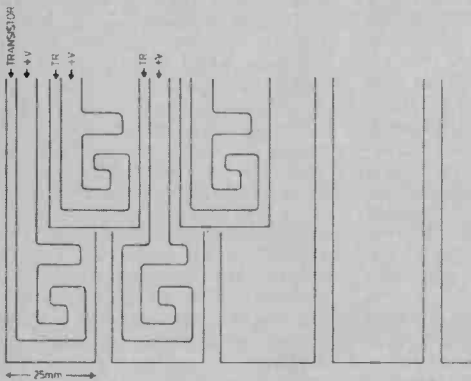


Fig. 2

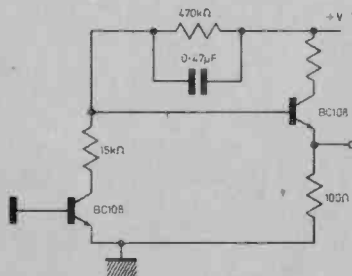


Fig. 3

TRANSFORMERS

ALL EX-STOCK - SAME DAY DESPATCH. VAT 8%

MAINS ISOLATING				12 AND OR 24 VOLT PRIMARY 240-250 VOLTS			
Ref.	VA (Watts)	£	P & P	Ref.	12V Amps.	24V Amps.	£ P & P
Prim. 120/240V. Sec. 120/240V Centre tap with screen				No.			
07*	20	3-77	58	111	0.5	0.25	1-54
149	60	4-69	72	213	1.0	0.5	1-86
150	100	5-33	85	71	2	1	2-41
151	200	8-54	1-12	18	4	2	2-97
152	250	10-32	1-41	70	6	3	4-43
153	350	12-47	1-41	108	8	4	5-09
154	500	14-33	1-61	72	10	5	5-50
155	750	21-94	BRS	116	12	6	5-80
156	1000	30-57	BRS	17	16	8	7-48
157	1500	34-89	BRS	115	20	10	10-10
158	2000	38-92	BRS	187	30	15	14-20
159	3000	61-48	BRS	226	60	30	17-87
115V or 240V sec. only*				50 VOLT RANGE			
30 VOLT RANGE				Prim. 200/240V. Sec. 0-19-25-33-40-50V			
Ref.	Amps.	£	P & P	Ref.	Amps.	£	P & P
No.				No.			
112	0.5	1-90	58	102	0.5	2-71	58
79	1.0	2-52	72	103	1.0	3-55	72
3	2.0	3-77	72	104	2.0	4-95	85
20	3.0	4-70	85	105	3.0	8-10	97
21	4.0	5-56	85	106	4.0	7-98	1-12
51	5.0	6-75	97	107	6.0	12-71	1-25
117	6.0	7-52	1-12	118	8.0	13-63	1-61
68	8.0	10-26	1-25	119	10.0	17-75	BRS
89	10.0	10-36	1-41	AUTO TRANSFORMERS			
60 VOLT RANGE				Ref. VA Auto Taps			
Prim. 200/240V. Sec. 0-24-30-40-48-60V				Ref. VA	£	P	P & P
No.	Amps.	£	P	No. (Watts)			
124	0.5	2-48	72	113	20	0-115-210-240	1-75 51
126	1.0	3-68	72	64	75	0-115-210-240	3-05 72
127	2.0	5-33	85	4	150	0-115-200-220-240	4-33 72
125	3.0	7-90	97	68	300	0-115-200-220-240	6-11 85
123	4.0	9-19	1-41	67	500	0-115-200-220-240	9-36 1-25
40	5.0	10-24	1-25	64	1000	0-115-200-220-240	14-36 1-61
120	6.0	12-07	1-41	93	1500	0-115-200-220-240	19-02 BRS
121	8.0	15-75	BRS	95	2000	0-115-200-220-240	25-41 BRS
122	10.0	19-40	BRS	73	3000	0-115-200-220-240	36-84 BRS
189	12.0	20-25	BRS	CASED AUTO TRANSFORMERS			
SCREENED MINIATURES				240V mains lead input and U.S.A. 2-PIN outlets:			
Ref. mA	Volts	£	P & P	20VA	£3-29	P. & P. 72p	113W
No.				150VA	£8-37	P. & P. 85p	4W
238	200	3-03	1-62	500VA	£10-97	P. & P. £1-25	67W
212	1A, 1A	0-6, 0-6	1-93	1000VA	£18-39	P. & P. BRS	84W
13	100	0-0-9	1-56	2000VA	£28-71	P. & P. BRS	95W
225	330, 330	0-6, 0-6	1-64	HIGH VOLTAGE MAINS ISOLATING			
207	500, 500	0-8-9, 0-8-9	2-02	Prim. 200/220V or 400/400V			
208	1A, 1A	0-8-9, 0-8-9	3-07	Sec. 100/120V or 200/240V	Ref.	£	P & P
236	200, 200	0-15, 0-15	1-56	60	243	4-37	97
214	300, 300	0-20, 0-20	2-03	350	247	10-93	1-41
221	700 (d.c.)	20-12-0-12-20	2-38	1000	250	26-31	BRS
206	1A, 1A	0-15-20-0-15-20	3-83	2000	252	44-12	BRS
203	500, 500	0-15-27-0-15-27	3-15	PLUS			
204	1A, 1A	0-15-27-0-15-27	4-14	POWER UNIT			
S112	500	12-15-20-24-30	1-97	CC12-05 Output Switched			
BRIDGE RECTIFIERS				3-4-5-6-7-8-9-12V at 500mA, £4-08. P & P 48p. VAT 25%			
50V	2A	35p		HIGH QUALITY MODULES			
100V	2A	40p		3 W RMS Amplifier £2-30			
200V	1A	45p		5W RMS Amplifier £2-65			
400V	4A	65p		10W RMS Amplifier £2-95			
500V	2A	60p		25W RMS Amplifier £3-45			
500V	10A(PM TAG)	£2-35		Pre-Amp for 3-5-10W £4-03			
TEST METERS				Pre-Amp for 25W £13-20			
AVO 8 MK5		£55-88		Power Supplies 3-5-10W 88p			
AVO 72		£21-72		Power Supplies 25W £3-00			
U4313*		£13-85		Transformer 3W £1-48			
U4315*		£11-80		Transformer 5-10W £2-13			
* (USSR) Inc. steel carrying case				Transformer 25W £2-60			
P. & P. £7-10. VAT 8%				P. & P. Amps/Pre-Amps/Power Supplies 18p			
ANTEX SOLDERING IRONS				P. & P. Transformers 37p. VAT 25%			
15W	£2-68, 18W	£2-45, 25W	£2-26,	ELECTROSIL METAL OXIDE RESISTORS			
Soldering Iron Kit £3-61, Stand for above £1-13. P. & P. 25p. VAT 8%				Style Tol. Ohmic Range Price/per 100			
MAGNETIC TO CERAMIC CARTRIDGE CONVERTOR				TR4 2% 10Ω-300kΩ £10-50			
Operating voltage 20-45V only £2-65 P. & P. 18p. VAT 25%				5% 10Ω-300kΩ £6-00			
BSR MINI-DECK				TR5 2% 10Ω-470kΩ £2-50			
4 Speed Autochanger £8-00 P. & P. 72p. VAT 25%				2% 510kΩ-1MΩ £2-60			
NEW STEREO 30 COMPLETE STEREO CHASSIS INC. 7 + 7W RMS AMP. Pre-amp, power supply, front panel, knobs (needs mains trans.). Stereo 30. £15-75. Mains trans. £2-45. Teak veneered cab. £3-65. P. & P. 85p. VAT 25%				TR6 2% 10Ω-47Ω £16-50			
				2% 51Ω-510kΩ £7-50			
				2% 560k-2MΩ £18-50			
				TR8 2% 10Ω-91Ω £18-50			
				2% 100Ω-100kΩ £10-50			
				2% 110k-1MΩ £11-50			
				QTY-P.O.A. P. & P. 25p/100			

PLEASE ADD VAT AFTER P & P
Audio Accessories and Bargain Component Paks.
Semi-Conductor stockists.
Callers welcome (Mon-Fri) or send stamp for lists

Barrie Electronics Ltd.

3, THE MINORIES, LONDON EC3N 1BJ

TELEPHONE: 01-488 3316/8

NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST.

PATENTS REVIEW...

PATENT INCREASE

On January 1, 1976, the price of a printed copy of a British Patent rose, by more than 100 per cent, to 75p. This is still cheap for a fact-packed specification of a hundred-or-so pages, accompanied by a dozen-or-so sheets of drawings, and is tolerable for the more average length of a dozen pages. But it makes any patent of brief content rather expensive.

For this reason, readers should remember that most of the official publications of the British Patents Office can be consulted free of charge at over two dozen libraries dotted around the United Kingdom. Fortunately, this situation is unlikely to change, because it would undermine the basic principle of patenting, whereby an inventor is awarded a monopoly in return for disclosing details of his invention to the public in a Patent Office publication.

Free access to any patent mentioned in this column should currently be available through the public, commercial or central library in the following towns:

Aberdeen; Aberystwyth; Belfast; Birmingham; Bradford; Bristol; Coventry; Edinburgh; Glasgow; Huddersfield; Hull; Leeds; Leicester; Liverpool; London (British Museum; Science Museum; Science Reference Library attached to the Patent Office); Loughborough (University of Technology); Manchester; Middlesbrough; Newcastle upon Tyne; Norwich; Nottingham; Plymouth; Portsmouth; Preston; Sheffield; Swindon; Wolverhampton.

LICENSING GUIDE

The British Library recently published another of its extremely useful "Guides to Literature". These are available free by post from the Bayswater Branch of the Science Reference Library (10 Porchester Gardens, Queensway, London W2 4DE), or on personal request from the SRL attached to the Patent Office at Southampton Buildings, Chancery Lane, London WC2.

Each guide has the same general format; a background to the subject and clear references to all the most useful literature that is available to the public in the SRL.

So far there have been no publications specifically on electronics topics (subjects covered have been artificial polymers, automotive fuels and odd protein sources), but news of any guideline on a selected area of electronics will be reported if and when it is published.

The latest guideline relates to "Patent Licensing Opportunities", and could be of considerable interest to both inventors and manufacturers working in the electronics field. Some of the source references given relate to regular publications which publicise both inventions available for licence and potential licensees seeking inventions; other references relate to the legal aspects of licensing, both here and abroad.

In the latter context, it is important to bear in mind that since we have joined the EEC the situation in Europe has become somewhat confused. Briefly, the Treaty of Rome forbids any restriction or distortion of competition within the EEC and thus would appear to ban any exclusive licence, i.e. any licence that gives any one manufacturer in a territory the right to corner a market without fear of competition from other manufacturers.

In 1962 the Common Market Commission issued its now famous, so-called "Christmas message" which appeared to condone exclusive licences if tied to a patent. But this 1962 exemption has been steadily confused and eroded. Currently, to the publicly admitted dismay of the CBI, inventors and manufacturers must realistically regard any straightforward exclusive licence in Europe as void under the Treaty of Rome.

There is legal machinery for asking the Commission in Brussels to give its advance opinion on a draft licence, but this is a lengthy procedure, riddled with red tape. Thus anyone with an electronic invention to license and hopes of profit without problems, is best advised to steer clear of licensing any one manufacturer to the

exclusion of others. Likewise firms are best advised to avoid entering into exclusive licences if humanly and commercially possible.

REMOVING DENTS

A simple but allegedly previously ignored approach to straightening out dents in car bodywork is claimed by Erwin Schill, of Switzerland, in BP 1 403 164.

According to the inventor, it is well known that to use a welding tool to soften the damaged metal leaves stresses in the sheet after removal of the dent. The proposed solution is to use a welding tool in the manner of a hammer, so that a multitude of tiny spots are heated briefly to a high temperature, rather than a whole area.

The necessary tool is shown in Fig. 1; the handle incorporates a hammer head with a central copper electrode which is surrounded by a safety sheath. The dent is flattened using short tapping movements so that the electrode briefly contacts the metal and heats spots of around 1mm square to 1,000°C for a fraction of a second at a time. The material surrounding each contact point draws in and if the spots are peppered over the surface to be treated (Fig. 2) the result is an overall flattening without undesirable stressing of the metal.

BP 1 403 164


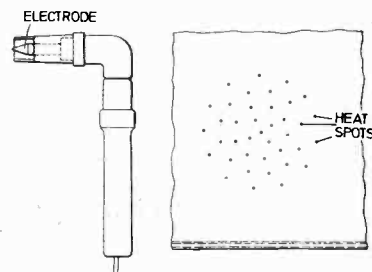


Fig. 1

Fig. 2

THE 'MISTRAL' 1 DIGITAL CLOCK

★ COMPLETE KIT ★

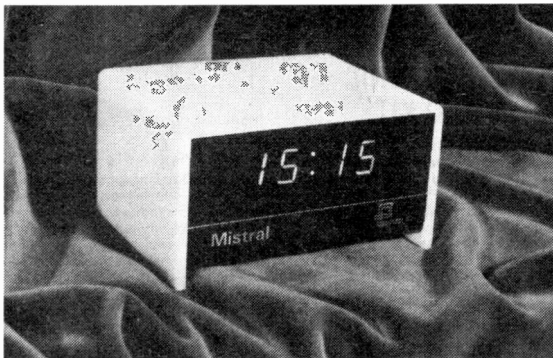

- Pleasant green display · 12/24 Hour readout
- Silent Synchronous Accuracy · Fully electronic
- Pulsating colon · Push-button setting
- Building time 1 hr · Attractive acrylic case
- Easy to follow instructions · Size 10.5 × 5.7 × 8cm
- Ready drilled PCB to accept components

KIT PRICE £11.57

Inc. P. & P. + £0.93 VAT

THE 'MISTRAL' 2 DIGITAL ALARM CLOCK

WITH SLEEP-OVER FEATURE




- Soft Green Display
- 24 Hour Alarm
- 10 Minute Repetition
- Alarm Set Indicator
- Accurate Silent Timekeeping
- British Designed and Built

COMPLETE PRICE £14.35

Inc. P. & P. + £1.15 VAT

1419 — ADVANCED

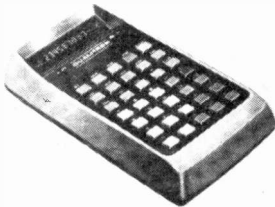

SPECIFICATION

- 14 digit LED display
- 10 digit mantissa with sign and 2 digit exponent with sign for data entry or results ($10^{-99} \sim 10^{99}$)
- Automatic selection of correct notation for result display (scientific or floating point)
- Dome keyboard for excellent response and preventing double entry input

BASIC FUNCTION (+, -, ×, ÷) AND MEMORY

- Algebraic mode operation
- Constant operations
- Chain operations
- Repeat operations
- Change sign operation
- Display and Y register exchangeable
- One accumulating memory
- Display and memory exchangeable

SPECIAL FUNCTION


- Trigonometric functions (sin, cos, tan)
- Inverse trigonometric functions (\sin^{-1} , \cos^{-1} , \tan^{-1})
- Hyperbolic functions (sinh, cosh, tanh)
- Inverse hyperbolic functions (\sinh^{-1} , \cosh^{-1} , \tanh^{-1})
- Radian or degree selectable
- π constant
- Logarithms (ln, log)
- Anti-logarithms (e^x , 10^x)
- Power function (y^x)
- Reciprocal ($1/x$)
- Square root (\sqrt{x})

PRICE £25.89

P. & P. 75p + VAT £2.13

1420 — SENIOR

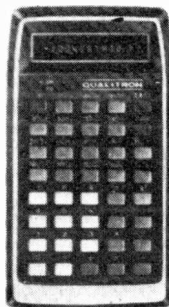- 14 digit LED display
- 10 digit mantissa with sign and 2 digit exponent with sign for data entry or results ($10^{-99} \sim 10^{99}$)




- Automatic selection of correct notation for result display (scientific or floating point)
- Dome keyboard for excellent response and preventing double entry input
- Algebraic mode operation
- Chain operations
- Change sign operation
- Three memories
- Display and memory exchangeable
- Trigonometric functions (sin, cos, tan)
- Inverse trigonometric functions (\sin^{-1} , \cos^{-1} , \tan^{-1})
- Radian or degree selectable
- π constant
- Logarithms (ln, log)

- Anti-logarithms (e^x , 10^x)
- Combinatorial functions ($n!$, $\binom{n}{r}$, $(n)_r$)
- Normal distribution function ($P(x)$)
- Gamma function ($\Gamma(x)$)
- Group operations (\sum , \prod , σ , \bar{x} , s , s_x)
- Group controls (K, K+, Σ , Δ , Δ , CL, CLR)
- Power function (y^x)
- Reciprocal ($1/x$)
- Square root (\sqrt{x})
- Square (x^2)
- Sum of squares ($\sum x^2$)
- Summation ($\sum x$)
- Item count (n)
- Mean value (\bar{x})
- Mixed chain operations with parentheses approach (up to two levels)

PRICE £55.63

P. & P. 75p + VAT £4.51

1421 — PROGRAMMABLE

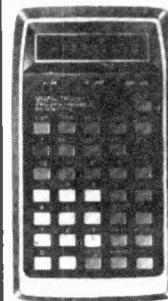

BESIDES HAVING THE CAPABILITY OF A SCIENTIFIC CALCULATOR:

- 9 digit LED display
- 8 digits capacity for data entry or results ($10^{-99} \sim 10^{99}$)
- Full floating point
- Automatic display blanking
- Three register operational stack
- Change sign operation
- Reverse polish notation
- Display and Y register exchangeable
- One accumulating memory (Memory store, Memory recall, M + X, M - X and M × X)
- Trigonometric functions (sin, cos, tan)
- Inverse trigonometric functions (\sin^{-1} , \cos^{-1} , \tan^{-1})
- Radians and degrees exchangeable
- π constant
- Logarithms (ln, log)
- Anti-logarithms (e^x)
- Power function (y^x)
- Reciprocal ($1/x$)
- Square root (\sqrt{x})
- Square (x^2)

IT CAN LOAD ANY 102 STEPS PROGRAM TO HELP YOU SOLVE THE REPEATED, ENORMOUS, COMPLEX PROBLEMS:


The Quiltron Programmable calculator can be used to memorize any combination of key entries while in the LOAD mode, then automatically plays back the programmed sequences as often as desired in the RUN mode. Up to 102 steps can be stored in multiprogram sequence blocks. Each block or program can be executed individually or you can make the decision to branch to specific program, run each in series or perform intermediate calculations from the keyboard.

PRICE £40.80

P. & P. 75p + VAT £3.32



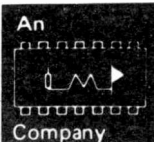Cash, Cheque or Postal Order or if you wish to use Barclaycard or Access, simply quote name, address and card number when ordering.



IMTECH PRODUCTS LTD

IMP HOUSE, ASHFORD ROAD
ASHFORD, MIDDX. TW15 1XB
Telephone: ASHFORD 44211 (4 lines)
Telex: 936291 WESSIMP ASHFORD

Sparkrite mk2

Capacitive discharge electronic ignition

VOTED BEST OF 8 SYSTEMS TESTED BY 'POPULAR MOTORING' MAGAZINE



- * Smoother running
- * Instant all-weather starting
- * Continual peak performance
- * Longer coil/battery/plug life
- * Improved acceleration/top speeds
- * Up to 20% better fuel consumption

Sparkrite Mk. 2 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 15/30 mins.

Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISES EVERYTHING NEEDED

Ready drilled pressed steel case coated in matt black epoxy resin, ready drilled base and heat-sink, top quality 5 year guaranteed transformer and components, cables, coil connectors, printed circuit board, nuts, bolts, silicon grease, full instructions to make the kit negative or positive earth, and 10 page installation instructions.

OPTIONAL EXTRAS

Electronic/conventional ignition switch. Gives instant changeover from "Sparkrite" ignition to conventional ignition for performance comparisons, static timing etc., and will also switch the ignition off completely as a security device, includes: switch connectors, mounting bracket and instructions. Cables excluded. Also available RPM limiting control for dashboard mounting (fitted in case on ready built unit).

CALLERS WELCOME. For Crypton tuning and fitting service - phone (0922) 33008.

PRICES INCLUDE VAT, POST AND PACKING.

Improve performance & economy NOW

POST TODAY!

Quick installation
No engine modification required

Electronics Design Associates, Dept. PE5,
82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 33652

Name
Address

Mk. 2 DIY Ass. Kit @ £11.80	QUANTITY REQD.
Mk. 2 Ready Built Negative Earth @ £14.97	
Mk. 2 Ready Built Positive Earth @ £14.97	
Ignition Changeover switches @ £4.30	
R.P.M. Limit systems in above units @ £2.42	

I enclose cheque/PO's for £


Cheque No.

Send SAE if brochure only required.

SAVE SAVE SAVE

Save your money on:

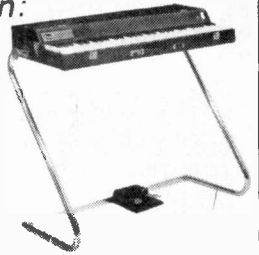- ★ TOUCH SENSITIVE PIANO KIT
- ★ SYNTHESISER KIT
- ★ ELECTRONIC PIANO KIT



★ Portable Organ kit with 4-Octave keyboard 2 pitches, external tuning, 10 Voices Vibrato. Plywood cabinet and cover finished in black rexine. Price £99-00
★ Portable Organ kit with 4-Octave keyboard, 3 pitches, external tuning, 10 Voices Vibrato. Plywood cabinet and cover finished in black rexine. Price £145-20
★ Portable Piano kit with touch-sensitive 5-Octave keyboard. Plywood cabinet and cover finished in black rexine. Price £145-00
★ Console Organ kit with 5-Octave keyboard 3 pitches, external tuning, 10 Voices, Sustain, Delay Vibrato, Piano Marimba and Wah Wah effects. Console finished in walnut. Price £250-93
★ Console Organ kit with 2 x 4-Octave keyboards and 13 note pedal board, 4 pitches external tuning, 15 Voices on upper keyboard, 5 pitches and 10 Voices on lower keyboard, 2 Voices on pedal, Sustain Reverberation Delay Vibrato, Snare Drum and Cymbal on Pedal, Piano Marimba and Wah Wah effects, 4 Drum Unit buttons. Console finished in Teak or Walnut. Price £470-65
★ Console Organ kit with 2 x 5-Octave keyboards and 32 note R.C.O. Pedal Board, 6 pitches all effects and finish as above. Price £680-00
★ Console Organ kit with 3 x 5-Octave keyboards and 32 note polyphonic R.C.O. Pedal Board, 8 pitches, magnificent range of voices. Price £960-00.

★ Components: 4-Octave keyboard C-C £15-50, 5-Octave keyboard C-C and F-F £20-00. Top octave tone generator, complete with external tuning capacitor, GU500, £12-95. Top octave tone generator and divider unit complete with external tuning capacitor, GD500 £50-00. Construction Manual for Portable Organ, using discrete components £2-25. Catalogue 80p.

ELVINS ELECTRONIC MUSICAL INSTRUMENTS

Organ Centre: 12, Brett Rd., Hackney, London E8 1JP. 01-986 8455
Component Shops: 8, Putney Bridge Rd., London SW18 1HU, 01-870 4949. 40/42a, Dalston Lane, Hackney, London E8 2AZ, 01-249 5624.

All prices are exclusive of VAT.

ELECTROLYTIC CAPACITOR OFFER

10000/63 £1-88	2200/40 30p	220/63 18p
10000/50 £1-50	1000/180 83p	180/25 9p
5000/70 78p	1000/40 25p	100/40 15p
5000/50 75p	1000/30 25p	100/12 7p
5000/35 50p	1000/25 25p	8/450 16p
5000/12 25p	470/63 23p	16/450 25p
3000/25 30p	470/35 20p	50/450 30p
2500/70 63p	330/100 30p	32 x 32/450 38p
2200/6-3 20p	250/64 20p	50/50 8p

Micro Switches (make or break) 33p

Cable Ties 3p

TOS Heat Sinks 13p

Pot cores (14mm or 18mm), complete 40p

18" Plastic Din Sockets 13p

DIGITAL I.C.s

Large range of 7400 series in stock. Prices from 18p.

INTEGRATED AUDIO POWER AMPS.

20W RMS, 1 off £8-38, Stereo pair £11-95.

30W RMS 1 off £7-95, Stereo pair £14-80.

50W RMS 1 off £12-38, Stereo pair £22-78.

50W RMS (40) amp. kits complete with building and application details. Suitable for instruments, disco, hi-fi, etc. £8-95.

S.A.E. FOR DETAILS

ZN414 IC Radio, £1-20.

741 54p.

IC sockets DIL, all 26p.

Complete range of components held in stock.

Resistors C.F. 0-5W and 0-25W.

all 2p.

Metal Oxide 0-5W. 5p.

MYLAR Caps:

1nF, 2nF, 5nF, 6p, 10nF, 20nF, 30nF, 40nF, 47nF, 8p, 0-1uF.

0-2uF, 12p.

C280, Polyester 250V:

10nF, 22nF, 4p, 33nF, 47nF, 4p,

68nF, 5p, 0-1uF, 0-15uF, 5p,

0-22uF, 6p, 0-33uF, 9p, 0-47uF,

10p, 0-88uF, 14p, 1-0uF, 17p,

1-5uF, 25p, 2-2uF, 29p.

1N4004 7p

1N4007 9p

1N4148 5p

0A90 8p

0A91 8p

CRS1/40 89p

CRS3/40 11-00

CRS7/40 £1-38

CRS1/60 £1-25

CRS7/60 £1-80

40669 £1-18

ZENER DIODES

400mW 16p

1 watt 19p

SEMICONDUCTORS

AC141 57p	BC157 14p	BD115 87p	MJ3000 £2-88	2N3053 26p
AC142 42p	BC158 12p	BD121 £1-48	MJ3001 £2-80	2N3054 66p
AC187 30p	BC159 12p	BD124 97p	MJ4200 £5-06	2N3055 59p
AC188 30p	BC167 14p	BD131 52p	MJE2955 £1-48	2N3702-
AC187K 41p	BC168 14p	BD132 84p	MJE3055 75p	2N3711 14p
AC188K 41p	BC189 15p	BD135 56p	TIP29A 89p	
AD161 62p	BC182 13p	BD136 83p	TIP30A 95p	40361 55p
AD162 62p	BC212 18p	BFY50 23p	TIP31A 87p	40362 60p
BC107 13p	BC301 32p	BFY51 22p	TIP32A 89p	40407 40p
BC108 12p	BC302 56p	BFY52 24p	TIP41A 72p	40408 55p
BC109 18p	BC303 37p	MJ481 £1-36	TIP42A £1-27	40409 63p
BC147 14p	BCY70 18p	MJ491 £1-52	TIP2855 £1-38	40499-
BC148 12p	BCY71 50p	MJ2500 £2-75	TIP3055 75p	40410 65p
BC149 14p	BCY72 18p	MJ2501 £2-85		

ALL PRICES INCLUDE VAT

P. & P. 25p on all orders. Hundreds of other types of semiconductors held in stock. S.A.E. with all inquiries.

EBA

Elliott Blunt Audio Ltd

40 YORK STREET, TWICKENHAM, MIDDX.

Tel. 01-891 1692

Opening hours 9.30 a.m. to 6 p.m. Tuesday to Saturday

constructors guides

This exciting new series, provides clear and easily understood descriptions, advice and general help for amateur constructors, students and technicians aimed at breaking down the barriers that often deter beginners in electronics.

Available Now...

ELECTRONIC DIAGRAMS

M. A. Colwell

One of the first things that newcomers to radio and electronics need to come to terms with is the language used. This book, which is aimed primarily at beginners, attempts to break down the barriers which so often deter students from taking up the subject. It takes the reader through the logical steps of building up circuit diagrams from elementary circuit symbols to complex systems.

112 pages 216 x 138mm Illustrated
0 408 00201 8 £1.80

PRINTED CIRCUIT ASSEMBLY

M. J. Hughes, MA, AMIERE and M. A. Colwell

This Guide describes the characteristics of the various bases used in printed circuit systems and guides the reader through the stages of translating circuit diagrams into printed circuit layouts. Image transference, etching, milling and trimming methods are described. Some special techniques such as through-hole plating, edge connector tabs and multi-layer assembly are also outlined, and reliability and maintenance procedures are discussed. The merits of alternative ready-made proprietary assembly systems are reviewed and tabular comparisons made.

96 pages 216 x 138mm Illustrated
0 408 00203 4 £1.80

ELECTRONIC COMPONENTS

M. A. Colwell

This book forms an introduction to electronic components, what they are and what they do, and provides guidance on recognition and

choice of component for particular applications. Included are resistors, capacitors, transformers, chokes, coils and tuned circuit components, semiconductors and electromechanical and electromagnetic devices. It also shows how to recognise faults and prevent breakdowns.

112 pages 216 x 138mm Illustrated
0 408 00202 6 £1.80

Available June...

PROJECT PLANNING AND BUILDING

Morris A. Colwell

This guide will help the constructor to plan, design and lay out his electronic projects. The book explains planning, use of tools, component board layout, the design and layout of chassis and cases, and assembly and wiring. There is also an extremely useful Appendix.

SIMPLE CIRCUIT BUILDING

P. C. Graham

This Guide provides a logical introduction to general purpose circuits for the home constructor and to converting theoretical circuits into practical layouts. The book covers a wide range of easy to assemble circuits, including switching and logic circuits and their layouts, operational amplifiers, a.c. amplifiers and d.c. power supplies.

PRACTICAL ELECTRONIC PROJECT BUILDING

Alan Ainslie and Morris A. Colwell

A concise but informative guide to some of the current popular methods of construction and techniques employed in home construction. Contains hints on finishing and fault-finding methods.

For details of all Newnes Technical Books please write for a free catalogue and watch for announcements in following issues of Practical Electronics.




Newnes Technical Books



BOROUGH GREEN, SEVENOAKS, KENT TN15 8PH

Build it yourself!

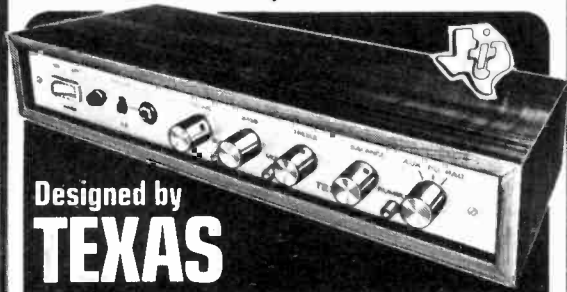

Designed by
TEXAS

Featured by **PRACTICAL WIRELESS**
SOLE U.K. DISTRIBUTORS - HENRY'S

Build the Texan stereo amplifier, then you can be doubly proud! For a start, you'll own a superb home entertainment unit. And have had all the pleasure of doing it yourself, with the Henry's kit.

Look at the Texan specification

Incorporating fully integrated stereo preamp and power amp, with 6 IC's, 10 transistors, 6 rectifiers and zener diodes. Plus stabilised, protected circuitry, glass fib pcb; Gardener's low-field low-line mains transformer; all facilities and controls. SLM design, chassis 14 1/2" x 6" x 2" overall; 20 watts per channel RMS, less than 0.1% distortion at 1 kHz.

- ★ Can be built Stage by stage Ask for leaflet 20.
- ★ Everything necessary supplied. Full after sales service and guarantees.

KIT PRICE
£35.00
inc. VAT + £1 p.p.p.

Built and tested
£45.00 inc. VAT
+ £1.00 p.p.p.

THE NATURAL FOLLOW-ON - THE TEXAN FM TUNER KIT!

KIT PRICE
£25.95
inc. VAT +
50p p.p.p.

Build the matching Texan stereo tuner! Features advanced varicap tuning. Phase lock loop decoder. Professionally designed circuit. Everything you need is in the kit. From the glass fibre pcb to the cabinet itself. Excellent spec: 2.5 uV aerial sensitivity. 500 mV output (adjustable). Tuning range 87-102 MHz. Mains powered.

Built and tested £30.95 inc. VAT + 50p p.p.p.

VIDEO SPORT

... all the electronic excitement
you could wish for!

★ OVER
10,000
ALREADY SOLD
★ IDEAL
GIFT

An up-to-the-minute game. Plugs into your own TV aerial socket. Switch on. And you're away! Choose your game - football, tennis or hole-in-the-wall. Absolutely safe. For you. Your children. And your TV. Mains powered.
List Price £42.50

inc. VAT +
50p p.p.p.

WHATEVER YOU DO, DON'T FORGET
YOUR LATEST **HENRY'S CATALOGUE!**



For this new edition, we have made hundreds of changes and additions. It has over 200 pages, containing virtually everything for amateurs and professionals. And you'll have no bother at all finding everything you want, because there's a complete alphabetical index as well as a section index. Together, they put you right on course for the items you need. From Sinclair projects to educational kits. Oscilloscopes to panel meters. Coils to capacitors. Transistors to valves. Loudspeakers to microphones - all at competitive prices. Over 200 pages of vital statistics - just for you! So send now for your copy.

ONLY 50p

20p Carri/Pack

FREE to Educational Establishments when ordered on official headed notepaper.

- Over 5000 items inside!
- Every copy contains a free 50p voucher.
- Many new items.
- Over 200 pages.

Henry's

SELF-SERVICE CENTRES 404 and
309 EDGWARE ROAD, LONDON W2
Bargains galore - Call in and see for yourself!

404/6 EDGWARE ROAD, LONDON W2 01-402 8381
LOWER SALES FLOOR, 231, TOTTENHAM CT. RD., LONDON W1 01-636 6687

NEW MIDLANDS STORE
94/96 UPPER PARLIAMENT STREET, NOTTINGHAM, 0602-40403
ALL MAIL TO HENRY'S RADIO, 303 EDGWARE ROAD, LONDON W2

FND500 Jumbo 0.5" C.C. Red LED display now only £1.02

ADVANCED CLOCK KIT

(P.E. Mains Clock Feb./Mar. 76)

Complete kit including attractive slim case for 8 digit alarm clock with sleep alarm, snooze, high brightness driving of Jumbo LED displays, automatic intensity control—with optional add-ons of touch switch snooze control and crystal control/battery back-up. **£26.80**

P.E. CAR CLOCK with Journey Timer

6 digit clock for use in any car with 12V battery, with an independent journey timer incorporated. Bright Jumbo LED display comes on with ignition—automatic intensity control. Complete kit of all parts needed including case, PCB's and all components. Full instructions. **£39.50**

Easy to Build E.E. DIGITAL CLOCK (Jan. issue). Kit of all components, including case etc., for this attractive clock with 12mm green display. Full instructions. **£15.70**

50 Hz Xtal Timebase Kit for clocks (incl. advanced kit above). **£6.28**

CMOS ICs	CD4029	0.94	CD4059	3.64	CD4510	1.12	Displays
RCA MOT	CD4030	0.46	CD4060	0.92	CD4511	1.28	SLT-01
ONLY	CD4031	1.82	CD4061	16.43	CD4514	2.56	DL704E
	CD4000	0.17	CD4032	0.88	CD4515	2.56	FND500
	CD4001	0.17	CD4033	1.14	CD4063	0.90	CD4516
	CD4002	0.17	CD4034	1.56	CD4066	0.58	CD4518
	CD4006	0.97	CD4035	0.97	CD4067	2.95	CD4520
	CD4007	0.17	CD4036	1.82	CD4068	0.18	CD4527
	CD4008	0.79	CD4037	0.78	CD4069	0.18	CD4532
	CD4009	0.46	CD4038	0.88	CD4070	0.18	CD4535
	CD4010	0.46	CD4039	2.86	CD4071	0.18	CD4556
	CD4011	0.17	CD4040	0.88	CD4072	0.18	MC14528
	CD4012	0.17	CD4041	0.89	CD4073	0.18	MC14534
	CD4013	0.46	CD4042	0.89	CD4075	0.18	MC14553
	CD4014	0.83	CD4043	0.83	CD4076	1.27	MC14566
	CD4015	0.83	CD4044	0.77	CD4077	0.18	MCM14552
	CD4016	0.46	CD4045	1.15	CD4078	0.18	MCM14555
	CD4017	0.83	CD4046	1.10	CD4081	0.18	Clock Chips
	CD4018	0.83	CD4047	0.74	CD4082	0.18	MK50253
	CD4019	0.46	CD4048	0.46	CD4085	0.59	MMS314
	CD4020	0.92	CD4049	0.46	CD4086	0.59	AY51224
	CD4021	0.83	CD4050	0.46	CD4089	1.27	AY51202
	CD4022	0.79	CD4051	0.77	CD4093	0.66	MK50250
	CD4023	0.17	CD4052	0.77	CD4094	1.53	CMOS
	CD4024	0.84	CD4053	0.77	CD4095	0.86	Books
	CD4025	0.17	CD4054	0.95	CD4096	0.86	No VAT or
	CD4026	1.42	CD4055	1.08	CD4097	2.95	P & P
	CD4027	0.46	CD4056	1.08	CD4099	1.50	P & P
	CD4028	0.74	CD4057	20.35	CD4502	0.98	MCMOS 2-77

ADD VAT at 8% (Higher rate does not apply to any of above).

25p P & P on all orders. Despatch is by 1st Class Post.

Price list and data sent FREE with an order, or on request (an SAE helps). Official orders welcomed (written or phoned)—Univs, Polys, Govt, Cos, etc. Export orders: No VAT, add 50p (Europe) £1 (overseas) for Airmail P & P. (No Export outside Europe for databooks and transformers).

SINTEL, 53b Aston Street, Oxford. Tel. 0865 49791

Test Equipment



Multimeters


The Eagle range of multimeters covers every possible need of the electrical or electronic engineer. They cost from about £6 to £58 (inc V.A.T.). There's at least one which suits your job precisely.

We have a lot of other test equipment too. Send the coupon and we'll send you our complete catalogue.

Please send me details of all your test equipment

NAME

ADDRESS

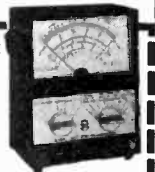

Eagle International Ltd., Precision Centre, Heather Park Drive, Wembley HA0 1SU
Tel(01)-902 8832

Eagle

PE

BI-PRE-PAK

Bargains in Semi-Conductors, components, modules & equipment.

B-P-P Packs

Originated in 1959 by the company's managing director, his were the first semi-conductor and component packs to be marketed in this country, and indeed, the company's name grew out of "British Industrial Pre-Packed Components". Today, Bi-Pre-Pak continues to occupy a position of pre-eminence in the supply of packs as well as a vastly extended range of products detailed in our latest 24 page A4 size free catalogue. Send 10p stamped large self-addressed envelope for your copy by return.

IT'S ALL IN OUR FREE CATALOGUE

Component Packs

CP1 150 Capacitors, mixed bag of paper, silver mica, electrolytics, etc. Approx quantity, counted by weight. (post & packing)60p
 CP2 200 Resistors, mixed bag of different types, values, wattages, etc. Approx. quantity, counted by weight60p
 CP3 40 Wirewound resistors, mixed types, values and wattages60p
 CP4 12 Potentiometers, pre-sets, w/wound, carbon, etc. Mixed types and values60p
 CP5 5 Earphones, single low impedance for transistor radio, cassettes, etc. Less plugs, for suitable plugs see PAKs CP9 and CP1060p
 CP6 50 TO-5 mounting pads, fits between transistor and board, for that pro. finish60p
 CP8 500 Cable clips for G.P.O. jin dia. cable. Nylon with hardened steel pin (probably tungsten) per sealed box of 50060p
 CP9 5 3-5mm plugs, miniature jack, to fit earphones in PAK CP560p
 CP10 5 2-5mm sub miniature jack, to fit earphones in PAK CP560p
 CP11 6 Screwdrivers, 1 x mains neon tester, 5 x grub screw-drivers60p
 CP12 10 Reed relay inserts, 1in long jin dia. These will operate from an external magnet or coil. For Magneta see PAK CP1360p
 CP13 10 magnets of various sizes for operating reed-switches in PAK CP12. Ideal for burglar alarms on doors and windows etc60p
 CP14 40 Potentiometers, pre-sets, carbons, dualgangs, with and without switches, etc. Mixed values and wattages £1-20
 CP15 12 Standard crocodile clips, screw fixing, good quality60p
 CP16 5 P.C. boards each containing a BF180 UHF amplifier transistor. A good basis for building a TV aerial pre-amp as various parts Inc.60p
 CP17 25 Electrolytic Capacitors, various values and wattages, many useful types, from TV to transistor radio and Hi-Fi (post and packing 23p)60p
 CP18 1 Light activated SCR-50 volt 1-6 amps type L3F. Ready mounted on PC board with gate resistor and leads fitted. Full data and circuit diagrams for 14 projects, include: slave photo flash unit, burglar alarm, etc.60p
 CP19 3 Micro switches 1 pole change over, standard model 1jin x jin60p
 CP20 10 Relays, assorted types, ex-GPO and others, mixed voltages£1-20
 CP21 200 Square inches of copper laminate P.C. board, in approx. 8 pieces60p
 CP22 3 Fibreglass plain printed circuit boards, approx 2jin x 14in60p
 CP23 4 Switches, miniature push to make single pole60p

Semi-Conductors

TESTED AND GUARANTEED

TP4 3 SN7490 integrated circuits, 14 pin dual in line TTL type. Decade counter. Get one FREE these are 60p each in singles£1-20*

All the following are at 60p each pack

TP9* 5 SN7400 integrated circuits, 14 pin dual in line TTL type. Quad 2-input NAND gate. Get one FREE, these are 15p each.
 TP10 2 light dependant resistors, 400 ohms light 1 megohm dark, jin dia.
 TP11 10 Transistors XB102 and XB112 equiv. to AC126, AC156, OC81/2, OC72, etc.
 TP12* 4 127 Silicon rectifiers 1000 piv 1 amp. Plastic TV rectifier.
 TP13* 5 OCP71 Light sensitive transistors.
 TP14 20 OC71 germanium PNP audio pre-amp transistor, black glass type.
 TP15 20 OC81 germanium PNP audio output transistor, white glass type.
 TP16 20 OC200/1/2/3 transistors, PNP silicon TO-5, unmarked.
 TP17 20 1 watt zener diodes, mixed voltages, 6-8 to 43 volts.
 TP18 20 2N3707/8/9/10 transistors, NPN silicon plastic, unmarked.
 TP19 100 Diodes, mixture of germanium, gold bonded, silicon, etc., a useful selection of many types, marked and unmarked.
 TP20 10 Mullard OC45 transistors, I.F. amp PNP germanium.
 TP21 20 BFY50/1/2, 2N696/7, 2N1613, etc. NPN silicon TO-5 uncodded. Complementary to PAK TP24.
 TP24 20 BFY64, 2N2904/5, etc., PNP silicon TO-5 uncodded. Complementary to PAK TP23.
 TP30 20 NPN silicon planar transistors, TO-18 similar to BC108 etc. uncodded.
 TP31 20 PNP silicon planar transistors, TO-18 similar to BC178 etc. uncodded.
 TP32 20 2N2928 Silicon Plastic transistors, uncodded and ungraded for colours.

UNTESTED PACKS - 60p EACH

Specialty for keen bargain hunters

UT1 50 PNP germanium transistors, AF and RF. Very good yield.
 UT2 150 Germanium diodes, miniature glass type.
 UT3 40 Zener diodes, 250mW OAZ240 range, average 50% good.

SINGLES

Bridge Rectifiers, Plastic encapsulated
 PIV = 50V 100V
 1 amp 25p* 35p* 400V 45p*
 2 amp 35p* 45p*
 4 amp 45p* 60p*
 6 amp 50p* 80p*
 BY164 equiv. SKB2/02 400V 1-5 amp45p*

F.E.T.s:
 2N3919 18p; 2N4416 20p
 Mos F.E.T.s:
 3N141/MEM61650p
 Uni-Junction Transistors:
 2N2160 85p* 2N2646 48p*
 TIS 43 31p*
 P.U.T.s: 2N2602750p
 L.E.D.s: TIL209, Red18p*
 YIL211, Green33p*

Also:
 POWER DIODES,
 THYRISTORS,
 TRIACS,
 DIAC,
 ZENER DIODES,
 OPTO-ELECTRONICS,
 Etc.

EXCITING NEW
 STIRLING SOUND
 AUDIO MODULES
 SEE NEXT
 MONTH'S ISSUE

POWER TRANSISTORS

	Vce	Watts	1c Amps	Price
40P1	15	20	3	20p*
40P2	40	40	4	30p*
40P2	40	40	4	30p*
90N1	15	45	4	25p*
90P1	15	45	4	25p*
90N2	40	90	8	35p*
90P2	40	90	8	35p*

Many other types available from 3 to 115 watts

Integrated Circuits: MM5314 Dual in line clock chips £3-00*
 LMS 380/SL 60745 Dual in line 2W audio amp. with data, etc50p
 Dual in line IC sockets 8-pin-14p; 14-pin-15p*; 16-pin-18p*

Sundry

Signal Generator: For MW and IF covers 550kHz to 1-6 MHz for MW and 400 to 550kHz for IF: Fully portable (p & p 40p)£4-25*
 Pocket Signal Injector: Fountain-pen type. Invaluable for finding fault£2-00*
 Ex-GPO 5in 5in Sliccutters: Not new, but in perfect order, per pair50p*
 Ex-GPO 6in Long Nose Pliers: Not new, but in perfect order, per pair60p*
 Mains Transformers:
 MT5 6V 0 6V 100mA£1-22*
 MT12 12V 0 12V 50mA£1-22*
 SST9/1 9V lamp£1-67*
 SST12/1 12V lamp£2-05*
 SST18/1 18V lamp£2-50*
 SST25/2 25V 2amp£3-00*
 SST30/2 30V 2amp£4-25*
 SST35/4 35V 4amp£5-50*

PC EDGE CONNECTORS

Type	Size	Pitch	Price
SSEC 6 way	1jin	0-156in	32p
SSEC 10 way	1jin	0-156in	50p
SSEC 12 way	2in	0-156in	60p
SSEC 16 way	2jin	0-156in	75p
SSEC 18 way	3in	0-156in	85p
SSEC 22 way	3jin	0-156in	100p

OTHER UNTESTED PACKS

60p ea.
 UT10 15 power transistors, PNP germanium and NPN silicon, mostly TO-3 but some plastic and some marked.
 UT13 15 integrated circuits, experimenters pak, dual in line, TO-5, TTL, DTL, marked and unmarked, some definitely good but old types.

For full ranges - See Catalogue

All free of VAT - We carry very large stocks of technical books by Babani & Bernard Publishers, by Newnes and Butterworth as well as reference books from the Common Market in English/German/Italian. All detailed in our catalogue.

B-P-P SECURITY CHECK POINT

- Write your own name and address clearly in block capital letters.
- Check that your order is correct for description, quantity and price.
- Don't forget VAT at 25% of total value of order unless otherwise stated.
- MAKE SURE YOU GET OUR NAME AND ADDRESS RIGHT WHEN ORDERING
- Cash (cheque, money or postal order) with your please
- Mention this journal when ordering if you don't want to cut out the coupon.

TERMS OF BUSINESS:

VAT at 25% must be added to total value of orders except for items marked * or (%), when VAT is to be added at 8%. No VAT on overseas orders. POST and PACKING add 25p for UK orders unless marked otherwise. Minimum mail order acceptable—£1. Overseas orders, add £1 for postage. Any difference will be credited or charged. PRICES subject to alteration, without notice. AVAILABILITY: All items available at time of going to press when every effort is made to ensure correctness of information.

To BI-PRE-PAK, 224-226 WEST RD., WESTCLIFF-ON-SEA, ESSEX

Please send

for which I encloseinc VAT

Name

Address

PE3A



BI-PRE-PAK LTD

Co. Reg. No R20919

222 224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SS0 9DF.


TELEPHONE: SOUTHEND (0702) 46344.

WRITE ORDER SEPARATELY AND ATTACH COUPON IF REQUIRED

SINCLAIR IC20
IC20 10W + 10W stereo IC amplifier kit with free booklet and printed circuit, £8.95.
PS20 Power supply kit for the above, £4.95.
VP20 Volume, tone-control and preamp kit, £7.95.
SP20 10W 4 ohm speaker for IC20, £2.95.

Send S.A.E. for free leaflet.

JC12 AMPLIFIER
6W IC audio amp. with free data and printed circuit, £1.95*



DELUXE KIT FOR JC12
Includes extra parts for the pcb and vol., bass and treble controls for mono version, £2.29. Stereo model with balance control, £4.95.

JC12 POWER KIT
Supplies 25V lamp, £2.95.

JC12 PREAMP KITS
Type 1 for magnetic pickups, mics and tuners. Mono £1.55. Stereo £3.10. Type 2 for ceramic or crystal pickups. Mono £5p. Stereo £1.70.

LOUDSPEAKERS FOR JC12
8in. x 5in. 8 ohms 5W £2.50.


Send S.A.E. for free leaflet on kits.

SINCLAIR PROJECT 80
FM tuner £13.25. PZ5 £3.95. Q16 £10.95. PZ6 £8.70. PZ8 £8.10. Trans for PZ8 £5.40. Z40 £5.75. Stereo 80 £11.95. Project 805 £28.95. Project 805Q £18.95. Quad decoder £14.95. Z80 discontinued but we stock 30W equivalent amp, £10.30.

PRINTED CIRCUIT KIT £3.95*
Make your own printed circuits. Contains etching dish, 200 sq.ins. of copper clad board, 1 lb ferric chloride, etch resist pen, small drill bit, laminate cutter and instructions.

MAINS TRANSFORMERS
6-0-6V 100mA 85p. 0-0-9V 100mA 85p. 18V 1A £1.95*. 0, 12, 15, 20, 24, 30V 1A £2.95*. 12-0-12V 1A £1.95*. 0, 12, 15, 20, 24, 30V 2A £4.29*. 20V 2½A £2.20. 6V and 9V trans are d.c. rated, others are a.c. volts.

SINCLAIR BLACK WATCH
Fully assembled with black strap, £20.95*. Bracelet, £2*.



SINCLAIR CALCULATORS*
Cambridge £7.95. Cambridge Memory £11.20. Scientific £11.95. Oxford 100 £2.95. Cam. Sci. £14.95. Oxford 300 £16.95. Programmable scientific £25.95. Mains adaptor for programmable and Oxfords £3.19. Mains adaptor for Cambridge and Scientific £3.15.

CBM CALCULATORS*
789MD £8.45. 867D £7.80. SR1900 £23.25. 778MD 7 digit %/memory £5.95. SR7919D 8 digit/memory/trig/log/pl/powers/scientific notation, £13.20. SR4148R with mains unit, £34.95. Mains unit for other machines, £2.95.


CASIO CALCULATORS*
Personal mini 8+6 digits £5.95. Pocket 8S 8 digits %/const. £8.25. Memory 8R 8 digits %/memory/const. £9.25. FX20 £19.95. Mains adaptor for all models £3.95.

24-HR. DIGITAL CLOCK KIT*
Includes pcb, mains power supply, attractive case, 0-5in. jumbo green display, clock chip, and all other parts. Displays hours and minutes separated by a pulsating colon. Kit £12.50. Built £15.50. Send S.A.E. for free leaflet.

S-DECS AND T-DECS*
Special Offer: 25p or 50p off orders accompanied by 25p or 50p PB Electronics advert.

S-DeC £2.24
T-DeC £4.05
u-DeC A £4.45
u-DeC B £7.85

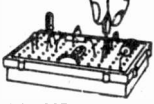
IC carriers—
16 dll: plain £1.07, with socket £2.21.
10 TOS: plain 99p, with socket £1.95. SST1 80p, SSU1 60p, SSN1 60p.



SWANLEY ELECTRONICS
Dept. PE, PO Box 68, Swanley, Kent

Battery Eliminator Bargains

55 WAY SUPER
New switched model. 3 to 30V in ½V steps. Fully stabilized. 1A output. Kit £7.95. Assembled £10.95. 2 Amp model. Kit £8.95. Built £12.95.



G-WAY SPECIAL
Switched output of 3/4V/6.7V/9.12V at 500mA with 4-way multi-jack plug and free matching socket, £5.80.

6-WAY DOUBLE RADIO MODEL £6.80
Similar to above, but with press-stud battery connectors. 3 + 3/4 + 4/8 + 6/7 + 7/9 + 9/12 + 12V at 250mA. Also gives 15/18/24V single.

3-WAY MODEL
Switched output of 6.7/9V at 250mA with 4-way multi-jack plug and free matching socket, £2.95*.

RADIO MODELS
50mA with press-stud battery connectors for radios, etc. 6V £2.95. 9V £2.95. 4 + 4V £4.45. 6 + 6V £4.45. 9 + 9V £4.45.

CASSETTE MAINS UNITS
7½V output to run cassette recorders from the mains. Complete with 5 pin DIN plug, £3.45.

CAR CONVERTERS
Input 12V DC. Output 6.7/9V DC 1A regulated, £3.95*.

BATTERY ELIMINATOR KITS
Send S.A.E. for free leaflet on range.

100mA radio type with press stud battery terminals. 4½V £1.95. 6V £1.95. 9V £1.95.
50mA double radio type with press stud terminals. 4½V + 4½V £2.75. 6V + 6V £2.75. 9V + 9V £2.75.
100mA cassette type with 5 pin DIN plug. 7½V £1.95.
Stabilized 8-way type with voltage stabilizer to give low hum. 3/4/6/7/9/12/15/18V 50mA. £2.95.
Heavy duty 12-way types 4/6/7/8/11/13/14/17/21/28/34/42V. 1 Amp £3.95. 2 Amp £5.95.

Post 30p on orders under £2, otherwise free. Prices include VAT (Overseas customers deduct 7% on items marked *, otherwise 20%). Official orders from schools, government labs., etc., welcome.

New Clock Chips and Clocks

In addition to National, Mostek and Caltex clock chips, we are now selling a range of General Instrument chips.

AY-5-1202
12 or 24 hour. 50 or 60Hz. Interfaces directly with Futaba 5LT01 £4.78

AY-5-1230
Similar to 1202. ON/OFF programmable alarm. In 7 segment mode can drive 5LT01, or BCD to drive logic or TV display chips £5.25

MISTRAL CLOCK KIT
Uses AY-5-1202 + Futaba 5LT01. Complete kit including case £11.58

CHEVIOT ALARM CLOCK
24 hour 4 digit alarm clock, 0-5in green display, tilt to snooze. Finished clock—not kit £21.85

5LT01. Green Phosphor Diode
Futaba 5LT01 display has 4 digits with AM/PM. Seconds indication on colon. Requires multiplexed input £5.80

5LT02
Similar to 5LT01. Requires non-multiplexed input, e.g. MM5316 £5.80

5LT03
5 digit multiplexed for use as counter or DVM module £5.80

Terms: CWO. Access, Barclaycard (simply quote your number and sign). Credit facilities to accredited account holders.
VAT—All prices exclude VAT (8%). P. & P. 15p

BYWOOD

68 Ebbens Road, Hemel Hempstead
Herts. HP3 9QR
Tel. 0442 62757

4-STATION INTERCOM



£15.95 + VAT £1.28

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs). In robust plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospitals, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft and other accessories. P. & P. 75p.

MAINS INTERCOM NEW MODEL
No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On off switch and volume control. Price £31.84 per pair. P. & P. 75p.

NEW! AMERICAN TYPE CRADLE TELEPHONE AMPLIFIER



ONLY £12.95 + VAT £1.04

Latest transistorised Telephone Amplifier with detached plug-in speaker. Placing the receiver on to the cradle activates on/off switch for immediate two-way conversation without holding the handset. Many people can listen at a time. Increase efficiency calls: leaves the user's hands free to make notes, consult files. No long waiting, saves time with long-distance calls. Volume. Direct tape recording model at £18.95 + VAT £1.12. P. & P. 70p. 10-day price refund guarantee.

WEST LONDON DIRECT SUPPLIES (PE5)
169 KENSINGTON HIGH STREET, LONDON, W.8

OSMABET LTD We make transformers amongst other things

LOW VOLTAGE TRANSFORMERS
Prim. 200/240V a.c., 5V 1A 50p; 6-3V 1-5A £1.85; 3A £2.10; 5A CT £3.75; 12V 1.5A 15p; 0-12-15-20-24-30V 2A, £4.50; 4A, £8.75. 0-5-20-30-40-60V 1A, £4.85; 2A, £8.75. 0-40-50-60-80-100-110V 1A, £7.

MIDGET RECTIFIER TRANSFORMERS
For FW rect. 200/240V a.c., 0-0-8V 1-5A or 0-0-9V 1A £1.90 each; 12-0-12V 1A, or 20-0-20V 0-75A, or 0-0-9V 0-3A, or 12-0-12V 0-25A, or 20-0-20V 0-15A, or 0V 0-5A + 6V 0-5A, or 9V 0-35A + 9V 0-35A, or 12V 0-25A + 12V 0-25A, or 20V 0-15A + 20V 0-15A, all at £2 each.

LOUDSPEAKERS
2½in 6 or 75Ω, 2½in 8 or 25Ω, 3in 3, 8 or 35Ω, 3½in 8, 15 or 80Ω, 85p each; 8 x 5in 3, 8, 15 or 25Ω, £1.75; Goodman speakers, 8in full throw 8Ω 10W, £4.25; 6½in double cone 4Ω, 3; 12in 25W 4 or 15Ω, £8.

"INSTANT" BULK TAPE/CASSETTE ERASER
Instant erasure any diameter tape spool or cassette, demagnetises tape heads. 200/240V a.c., £3.75.

TAPE RECORDER MOTORS
New, blowers, fans, etc., 110V a.c., 50p (75p pair).

SYNCHRONOUS GEARED MOTORS 200/240V a.c.
Brand new Smiths, built in gearbox, 6 r.p.m., 75p each.

PAPER TUBULAR CONDENSERS
4-7mf, 160V, 30 x 20mm, 20p (100 for £10).

SPEAKER MATCHING AUTO TRANSFORMER
12W, 3 to 8 or 15Ω, up or down, £1.85.

G.E.C. MANUAL OF POWER AMPLIFIER COVERING VALVE AMPLIFIERS OF 30W TO 400W 35p.

CABLES — CABLES — CABLES
MICROPHONE TWIN H/DUTY, BRAIDED SCREEN
Professional cable for stag studio, outdoor. PVC covered, grey, 20p per metre. Grey: Single cable, black, 10p per metre.

MULTI WAY SCREENED, PVC COVERED
3 way £1; 2 way 75p; 14 way 50p; 6 way 20p; 4 way 14p; 2 way 10p; 1 way 6p per metre.

FLEXIBLE PVC MINI 3-CORE CABLE
19/010 100 metres 3-core for speakers, intercoms, etc., £3.

TWIN FIG. 8 CABLE
Polarised, £2-50 100 metres.

ALL TYPES DOMESTIC AND COMMERCIAL CABLES, ALL SIZES AND COLOURS CONNECTING WIRES, MULTI SCREENED AND UNSCREENED CABLE.
TRADE ENQUIRIES INVITED
Carriage and VAT extra on all orders
S.A.E. ENQUIRIES. LISTS. MAIL ORDER ONLY
46 Kenilworth Road, Edgware, Middx. HA8 5YG
Tel. 01-958 8314

RETURN OF POST MAIL ORDER SERVICE


R.C.S. 10 WATT AMPLIFIER KIT



This kit is suitable for record players, tape play back, guitars, electronic instruments or small P.A. systems. Two versions are available. A mono kit or a stereo kit. The mono kit uses 13 semiconductors. The stereo kit uses 22 semiconductors with printed front panel and volume, bass and treble controls. Spec. 10 watts output into 8 ohm. 7 watts into 15 ohms. Response 20 CPS to 30 K/CS. input 100 M.V. high imp. Size 9 1/2 in. x 3 in. x 2 in.

Mono kit **£12.50** Stereo kit **£20** Post 45p.
Easy to build. Full instructions supplied.

ELAC 10 inch



Dual cone plasticized roll surround. Large ceramic magnet. 50-18,000 cps. Bass resonance 55 cps. 8 ohm impedance. 10 watts

£4.95

TEAK VENEER HI-FI SPEAKER CABINETS

MODEL "A". 20 x 13 x 12 in. For 12 in. dia. **£12.50** Post 75p Baker speaker.

MODEL "B". 16 x 10 x 9 in. For 8 x 8 in. **£6.95** Post 45p EMI speaker.

LOUDSPEAKER CABINET WADDING 18 in. wide, 20p ft.

BAKER RECOMMENDED 12 inch Enclosure 4 cubic ft. HI-FI CABINET £21.50. Carr. £2 each. Fint only. Size 30 x 20 x 12 in. Teak Finished Front.

TEAKWOOD LOUDSPEAKER FRONT GRILL
Modernise your cabinets with the Grooved look. 10 1/2" x 7 1/2" 45p.

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER
Will mix Microphone, records, tape and tuner with separate controls into single output 9 volt battery operated. **£5.20**

STEREO VERSION OF ABOVE £6.85.

R.C.S. STEREO FM TUNER



This completely cased mains powered Hi-Fi Tuner with brushed aluminium fascia is British made using the latest circuitry. Bargain **£30** Post 45p.


BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built with volume, treble and bass controls. 18 volt battery operated. **£3.95**

WAFER HEATING ELEMENTS
Type H
Size 10 1/2 x 8 1/2 x 1/2 in. Operating voltage 200/250V. a.c. 250 watts approx. Suitable for Heating Pads, Food Warmers, Convector Heaters, etc. Must be clamped between two sheets of metal or asbestos.
ONLY 40p EACH (FOUR FOR £1.50)
ALL POST PAID—Discounts for quantity.


E.M.I. 13 1/2 x 8 in. SPEAKER SALE!

With flared tweeter cone and ceramic magnet, 10 watt, 8 ohm. **£3.45** Post 45p.
Bass res. 45-50 cps. Flux 10,000 gauss.

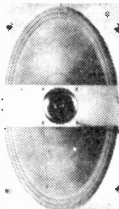With tweeter. **£5.25** Post 45p.
And crossover. 10 watt. State 3 or 8 ohm. As illustrated. 15 watt model 8 or 15 ohm £8.



BAKER MAJOR 12" £11.50



30-14,500 c/s. 12 in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s. Rated 25 watts. NOTE: 3 or 8 or 15 ohms must be stated.

Module kit, 20-17,000 c/s with tweeter, crossover, baffle and instructions. **£14.50** As illustrated. Post 80p

Please state 3 or 8 or 15 ohms. Post 80p

"BIG SOUND" BAKER SPEAKERS

Robustly constructed to stand up to long periods of electronic power. As used by leading groups and discos

Useful response 30-13,000 cps. Bass Resonance 55 cps.

GROUP "25" **£8.95** Post 40p
12 in. 30 watt
3, 8 or 15 ohms.

GROUP "35" **£10.50** Post 40p
12 in. 40 watt
3, 8 or 15 ohms.

GROUP 50/12 in. **£14.50** Post 80p
80 watt 8 or 15 ohms

GROUP "50" **£19.50** Post 80p
16 in. 75 watt
8 or 15 ohms.

Group + PA Cabinets in stock Send for Leaflet.



BAKER 50 WATT ALL PURPOSE TRANSISTOR AMPLIFIER

All purpose transistorised. Ideal for Groups, Disco and P.A. 4 inputs speech and music. 2 way mixing. Output 8/15 ohm. A.C. Mains. Separate treble and bass controls.

£49 Carr. £1.00



NEW 'DISCO 100 WATT' £52
ALL PURPOSE AMPLIFIER CHASSIS Carr. £1
2 inputs. 4 outputs separate volume treble and bass controls. Ideal disco or slave amplifier chassis.


PW SOUND TO LIGHT DISPLAY

Complete kit of parts with R.C.S. printed circuit. Three 1000 watt channels. As featured in December Practical Wireless. **£12.50** CABINET extra £3.

GOODMANS CONE TWEETER

18,000 cps. 25 watts 8 ohm. Price **£3.60**

R.C.S. 100 WATT VALVE AMPLIFIER CHASSIS

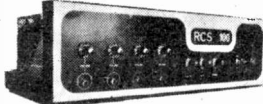

Professional model. Four inputs. Treble, Bass, Master, Volume Controls. Ideal disco, P.A. or groups. S.A.E. for details. 5 speaker outputs, very robust job. Suitable carrying case **£16.50** **£85** plus £1.50 carr.

E.M.I. GRAM MOTOR £1.25 Post 80p
180v. or 240v. A.C. 2,400 rpm. 2-pole 70mA. Size 2 1/2 x 2 1/2 in.

E.M.I. TAPE MOTOR £2.00 Post 30p
4 pole, 240v. 185 mA. 1400 rpm Spindle 1/4 in. diameter. 180v version £1. (Illustrated). Size 3 1/2 x 2 1/2 x 1 in.



NEW BSR HI-FI AUTOCHANGER STEREO AND MONO


Plays 12", 10" or 7" records Auto or Manual. A high quality unit backed by BSE reliability with 12 months' guarantee. AC 200/250v. Size 13 1/2 x 11 1/2 in. Above motor board 2 in. Below motor board 2 in.



With STEREO/MONO CARTRIDGE **£10.95** Post 75p

PORTABLE PLAYER CABINET £4.50

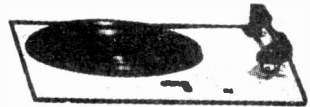Modern design. Size 16" x 15" x 7" rexine Post 50p. covered. Large front grille. Hinged Lid. Chrome fittings. Motor board out for Garrard or BSE deck. Few only, in red and black.



R.C.S. DISCO DECK SINGLE RECORD PLAYER

Fitted with auto stop, stereo/compat. cartridge. Base-plate. Size 11 in. x 8 1/2 in. Turntable. Size 7 in. diameter A/C mains. £20/250V.

3 speeds plays all size records. **£6.95** Post 45p
Two for **£13.** Post 75p

HEAVY METAL PLINTHS

With P.V.C. Cover. Cut out for most B.S.R. or Garrard decks. Silver grey finish. Model "A". Size 12 1/2 x 14 1/2 x 7 1/2 in. Model "B". Size 16 x 13 1/2 x 7 in. **£5.95** Post 75p

TINTED PLASTIC COVERS ONLY


Sizes: 'A'—14 1/2" x 18 1/2" x 4 1/2". 'B'—20 1/2" x 12 1/2" x 4 1/2". 'C'—17 1/2" x 13 1/2" x 4 1/2". 'D'—19 1/2" x 14 1/2" x 4 1/2". 'E'—23.50. Ideal for record decks, tape decks, etc. Post 45p.

BAKER HI-FI SPEAKERS HIGH QUALITY — BRITISH MADE SUPERB

12 in. 25 watts

A high quality loudspeaker, its remarkable low cone resonance ensures clear reproduction of the deepest bass. Fitted with a special copper drive and concave tweeter cone resulting in full range reproduction with remarkable efficiency in the upper register.
Bass Resonance 25cps
Flux Density 16,500 gauss
Useful response 20-17,000cps
8 or 15 ohms models.

£17.00 Post 80p

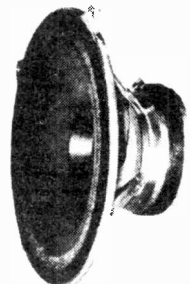


AUDITORIUM

12 in. 35 watts

A full range reproducer for high power, Electric Guitars, public address, multi-speaker systems, electric organs. Ideal for Hi-Fi and Disco-theques.
Bass Resonance 35cps
Flux Density 15,000 gauss
Useful response 25-16,000cps
8 or 15 ohms models.

£15.50 Post 80p

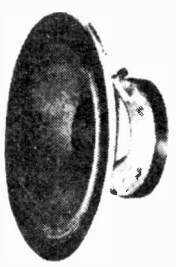

AUDITORIUM

15 in. 45 watts

Bass Resonance 35cps
Flux Density 15,000 gauss
Useful response 20-14,000 cps
8 or 15 ohms models.

£19.50 Post 80p

RADIO COMPONENT SPECIALISTS

Minimum post 30p. Access and Barclaycard Welcome. Radio Books & Components Lists 10p.

337 WHITEHORSE ROAD, CROYDON

Open 9—6 Wed. 9—1 Sat. 9—5 (Closed for lunch 1.15—2.30)
Rail Selhurst. Tel. 01-684 1665

FULL SPEC. NEW DEVICES, BY RETURN

BC107	18p	TIP42A	75p	1N4004	5p
BC108	18p	TIP2855	65p	1N4007	5p
BC109	18p	TIP3055	45p	3A/800V Rec.	15p
BC122L	18p	T1843 (LJLT)	25p		
BC123L	18p	ZTX320	15p	BRIDGES	
BC184L	18p	ZTX304	25p	1A/200V	25p
BC212L	14p	ZTX500	15p	2A/800V	33p
BC213L	14p	ZTX504	25p	DIL. I.C.s	
BC214L	14p	2N3905	65p	741 8 pin	25p
TIP29A	45p	2N3819	35p	555 Timer	45p
TIP30A	45p	1N914	4p	DISPLAYS LED	
TIP31A	51p	1N4148	4p	7-seg.	
TIP32A	55p	1N4002	4p	0-375in	£1-15
TIP41A	73p	1N4003	4p	0-5in	£1-40

REGULATORS TO-ZEE	CAPACITORS	
7805 (5V)	£1-50	10mF/12V
7812 (12V)	£1-50	100µF/1
7815 (15V)	£1-50	1000mF/5V
7824 (24V)	£1-50	100µF/1-50

VAT Included. P. & P. 20p.
Display Data—S.A.E. please

AUDIO-OPTICS

19 Middletway, Chirhor, Oxon.
Tel. Kingston Blount 52683

BRAND NEW COMPONENTS BY RETURN.

Electrolytics 16V, 25V, 50V, 0-47, 1-0, 2-2, 4-7, 10mfd, 5p; 22, 47, 51p (50V, 8p); 100, 7p (50V, 8p); 220, 8p (50V, 10p); 500, 11p (50V, 10p); 1000/25V, 18p. Subminiature bead-type tantalums. 0-1/35V, 0-22/35V, 0-47/35V, 1-0/35V, 2-2/35V, 4-7/35V, 10/20V, 22/16V, 47/6V, 100/3V, 11p. Mylar Film 100V, 0-001, 0-002, 0-005, 0-01, 0-02, 3p; 0-04, 0-05, 3½p. Mullard tubular polyester 400V E6 series, 0-001-0-022, 3½p; 0-033-0-1, 4½p. Mullard polyester 100V tubular or 250V miniature for vertical mounting E6 series, 0-01-0-047, 3½p; 0-068, 0-1, 4½p; 0-15, 0-22, 6p; 0-33, 7p; 0-47, 9p; 0-68, 11p; 1-0, 14p; 1-5/250V, 18p; 2-2/250V, 22p. Mullard miniature C333 ceramics 63V E12 series 2% 1-8pF-47pF, 3p; 50pF-330pF, 3½p. Plate ceramics 50V E6 series 470pF-47,000pF, 2p. Polystyrene 63V. E12 series 10pF-1,000pF, 3p; 1,200pF-10,000pF, 4p. Miniature highstab carbon film resistors ½W E12 series 5% (10% over 1MΩ) 1Ω-10MΩ, 1-2p; 1N4002, 6p; 1N4006, 8p; 1N4148, 4p. Postage 10p. Prices VAT inclusive. THE C.R. SUPPLY CO., 127 Chesterfield Road, Sheffield, S8 0RN.

Yes, still the same JUMBO bottle
Beware of imitations

175cc P.C.B. Ink £1.50

Quick drying ferric chloride etch
resist ink, applied by pen or brush.

MAWSON ASSOC.

64 Brookbank Road, London, SE13

FOR SALE

PE, PW since 1967 and EE, 75p. S.a.e. for availability. Mr. J. GILKESON, 34a, Chevet Lane, Wakefield.

PRACTICAL ELECTRONICS. Indexed bound volumes 1967-1975, offers? Mr. MORAN, 53 Betenson Avenue, Sevenoaks, Kent.

TWO FIVE OCTAVE KEYBOARDS. One set of four pole contacts. All unused. Bargain Price. Tel. 01-949 1654.

P.E. JOANNA KIT. Incomplete. Contains 90% components, P.C.B.s, keyboard, contacts, instructions. Worth £100 New. Offers. Phone Dorking 2668.

PRACTICAL ELECTRONICS Magazines 1965 to 1974. Mint condition. Offers. MANSFIELD, 97 Spencefield Lane, Leicester. Tel. Thurnby 3646.

P.E. SYNTHESISER KEYBOARD, pair log V.C.O.s, assembled, working, +48 note divider and contracts, £20. Chester 41707.

ELECTRICAL

STYLI AND CARTRIDGES. For the best at keenest prices send SAE for free illus. list to FELSTEAD ELECTRONICS (PE), Longley Lane, Gatley, Cheshire, SK8 4EE.

EDUCATIONAL

COLOUR TV SERVICING.

Learn the techniques of servicing Colour TV sets through new homestudy course approved by leading manufacturers. Covers principles, practice and alignment with numerous illustrations and diagrams. Other courses for radio and audio servicing. Full details from: ICS SCHOOL OF ELECTRONICS, Dept. 771S, Intertext House, London, SW8 4UJ. Tel. 01-622 9911 (all hours).

TAPETALK

The CLEVER way to LEARN
TWO C60 Cassettes entitled
INTRODUCING ELECTRONICS

£5-44 plus 55p VAT/P. & P.

TAPETALK, P.O. Box 99 (PE)
Milton Keynes MK3 5BR
Tel.: Milton Keynes (0908) 77710

TECHNICAL TRAINING.

Get the training you need to move up into a higher paid job. Take the first step now—write or phone ICS for details of ICS specialist homestudy courses on Radio, TV, Audio Eng. and Servicing, Electronics, Computers; also self-build radio kits. Full details from: ICS SCHOOL OF ELECTRONICS, Dept. 771S, Intertext House, London, SW8 4UJ. Tel. 01-622 9911 (all hours).

TELEVISION TRAINING

16 MONTHS' full-time practical and theoretical training course in Radio and TV Servicing (Mono and Colour) for beginners, with GCE (or equivalent) in Maths & English.

13 WEEKS' full-time Colour TV Servicing course. Includes 100 hours practical training. Mono revision if necessary. Good electronics background essential.

NEXT SESSION commences on April 20th.

Prospectus from London Electronics College, Dept. A5, 20 Pennywern Road, London SW5 9SU. Tel. 01-373 8721.

CITY & GUILDS EXAMS.

Study for success with ICS. An ICS homestudy course will ensure that you pass your C. & G. exams. Special courses for: Telecoms Technicians, Electrical Installations, Radio, TV & Electronics Technicians, Radio Amateurs. Full details from: ICS SCHOOL OF ELECTRONICS, Dept. 771S, Intertext House, London, SW8 4UJ. Tel. 01-622 9911 (all hours).

LADDERS

LADDERS, varnished 20' 9" extd. £19-82. Carr. £1-40. Leaflet. Also aluminium ext. and loft ladders. Tel. Telford 586644.

WANTED

WANTED—FLUKE 8000A, Advance DMM3 or similar Digital Multimeter. Also "X-Y" recorder any make or condition considered. Cash waiting. Tel. Brighton 684286.

TOP PRICES PAID
NEW VALVES AND TRANSISTORS
Popular T.V. and Radio types
KENSINGTON SUPPLIES (B)
367 Kensington Street
Bradford 8, Yorks.

BOOKS AND PUBLICATIONS

START YOUR OWN BUSINESS
REWINDING ELECTRIC MOTORS

This unique instruction manual shows step by step how to rewind motors, working part or full time, without previous experience. Everything you need to know easily explained, including where to obtain materials, how to get all the work you need, etc., etc. A goldmine of information and knowledge. Only £3.65 plus 25p P. & P. From: **MAGNUM PUBLICATIONS, Dept. PE5** Brinksway Trading Estate, Brinksway Stockport SK3 0BZ Overseas Distributors wanted.

SERVICE SHEETS

SERVICE SHEETS for radio, TV, tape recorders, stereo, etc., with free fault-finding guide, 50p and S.A.E. HAMILTON RADIO, 47 Bohemia Road, St. Leonards, Sussex.

BELL'S TELEVISION SERVICES for service sheets, manuals and books on Radio/TV, etc. Service sheets 50p plus S.A.E. Service sheet catalogue 25p. Back issues of magazines from April, '74 onwards. Cover price plus 12p post. Free booklists on request. S.A.E. with enquiries please to: B.T.S. 190 Kings Road, Harrogate, Yorkshire. Tel. Harrogate (0423) 55885.

SERVICE SHEETS, radio, TV, etc. 10,000 models. Catalogue 24p plus S.A.E. with orders-enquiries. TELRAY, 154 Brook Street, Preston, PR1 7HP.

TAPES

TAPETALK

THE NATURAL WAY TO LEARN

Two C60 cassettes entitled
THE SCIENCE OF SOLDERING
£5-44 plus 55p VAT/P. & P.

TAPETALK, P.O. Box 99 (PE)
Milton Keynes MK3 5BR
Tel.: Milton Keynes (0908) 77710

MISCELLANEOUS

HELME
DO-IT-YOURSELF
HI-FI STEREO
SPEAKER KITS
The best value around!
Send for details
HELME AUDIO PRODUCTS LTD.
Dept. P.E.
SUMMERBRIDGE
HARROGATE YORKS
Tel. Darley 279 (Std Code 0423 72)

MISCELLANEOUS

BUILD THE TREASURE TRACER
MK III Metal Locator



- Varicap tuning
- Britain's best selling metal locator kit
- Fitted with Faraday shield
- Speaker and earphone operation
- 4,000 already sold
- Prebuilt search coil assembly
- Five transistor circuit
- Thoroughly professional finish
- You only need soldering iron, screw driver, pliers and snips
- As seen on BBC-1 and BBC-2 TV

Send stamped, addressed envelope for leaflet

Complete Kit **£12-50** Post 85p + £1 00 VAT (8%)
Built and tested **£17-50** Post 85p + £1 40 VAT (8%)

MINIKITS ELECTRONICS, 6g CLEVELAND ROAD
LONDON E18 2AN (Mail Order Only)

LOW COST I.C. MOUNTING for any size DIL package. 100 Solderon sockets 60p, 7 and 8 hole plastic supports 5p pair. Quantity rates, S.A.E. details and sample. Trial pack 60p. (P. & P. 10p order). P.K.G. ELECTRONICS, Oak Lodge, Tansley, Derbyshire, DE4 5FE.

ENAMELLED COPPER WIRE

S.W.G.	1lb reel	1lb reel
10 to 19	£2-40	£1-35
20 to 29	£2-45	£1-40
30 to 34	£2-60	£1-50
35 to 40	£2-85	£1-60

All the above prices are inclusive of postage and packing in the U.K.

COPPER SUPPLIES

102 Parrswood Road, Withington, Manchester 20
Telephone 061-445 8753

DO-IT-YOURSELF LOUDSPEAKERS for hi-fi are our speciality. Full range of components and accessories including chassis speakers, cross-overs, sound absorbent, grille fabrics, etc., always available. We stock the fabulous value Helme speaker kits (complete with full and easy instructions), also Peerless and Wharfedale kits. Just about the lowest prices anywhere! Send 8p stamp for bargain list to: AUDIOSCAN, Dept. PE575, 4 Princes Square, Harrogate, North Yorkshire.

BUILD YOUR OWN

YOU ARE INVITED TO SEND S.A.E. FOR LISTS ON OUR VERY EXTENSIVE RANGE OF HIGH QUALITY AMPLIFIERS, PRE-AMPS, F.M. TUNERS, INSTRUMENTS, RADIO CONTROL, IGNITION UNITS AND MANY OTHER KITS. STATE REQUIREMENTS.

TELERADIO ELECTRONICS

325 Fore St., Edmonton, London N9

SUPERB INSTRUMENT CASES by Bazell, manufactured from heavy duty PVC faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range, competitive prices start at a low 75p. Examples, Width, Depth, Height, 8" x 5" x 3" **£1-55**; 10" x 6" x 3" **£2-20**; 12" x 8" x 3" **£2-70**; 14" x 6" x 3" **£2-95**; 10" x 8" x 3" **£2-75**; 12" x 8" x 3" **£3-20**; 14" x 8" x 3" **£3-60**; 12" x 10" x 3" **£3-60**; 8" x 4" x 4" **£1-80**; 10" x 6" x 4" **£2-70**; 12" x 6" x 4" **£2-85**; 14" x 6" x 4" **£3-25**; 12" x 8" x 4" **£3-60**; 14" x 8" x 4" **£3-80**; 7" x 7" x 5" **£2-65**; 8" x 10" x 6" **£3-60**; 12" x 8" x 7" **£4**; 14" x 8" x 7" **£4-80**; 12" x 10" x 7" **£4-25**; 12" x 12" x 7" **£4-40**; 14" x 10" x 7" **£5**; 12" x 10" x 8" **£5**; 14" x 10" x 8" **£5-30**; 14" x 12" x 7" **£5-20**; 12" x 12" x 8" **£5-50**; 14" x 12" x 8" **£5-80**. Plus 72p Carriage and 8% VAT. 16" x 8" x 8" **£7-60**; 18" x 10" x 8" **£8-40**; 18" x 8" x 8" **£9-50**; 18" x 10" x 8" **£10-30**; 19½" x 8" x 8" **£11-50**; 19½" x 10" x 8" **£12-30**. Plus £1-25 Carriage and 8% VAT. Over 400 models to choose from. Prompt despatch. Free literature (stamp would be appreciated). BAZELLI, Dept. No. 23, St. Wilfrid's, Foundry Lane, Halton, Lancaster LA2 6LT.

I.C. EXPERIMENTER'S KITS

Learn about modern electronics with our new series of Kits on digital logic techniques. Each Kit contains specially selected I.C.s, Holders, Veroboard, L.E.D.s, and Instructions. Available at **£3-50** each (including P. & P.)
Kit One—Gates Kit Two—Flip-Flops
Kit Three—Shift Registers
Kit Four—Counters Kit Five—Displays
S.A.E. for further details to:
AUTOMATED HOMES
69 High Street, Ryton, Coventry CV8 3FJ
(Mail Order Only)

NICKEL CADMIUM fully sealed rechargeable batteries. Equivalent dry cell sizes. Discount. S.A.E. brings full details by return. Charges available. SANDWELL PLANT LTD., 1 Denholm Road, Sutton Coldfield, West Midlands, B73 6PP. Tel. 021-354 9764.

PHOTOTECH (EUROPE)

New Optoelectronic Detectors
Type 1: Photodiode, 2 pin Configuration: Photosensitive area 0.85 x 10⁻³ square inches.
Type 2: Photoswitch, 4 pin Configuration, 20V-30V supply. Switching threshold set by external R.C.
Type 3: Photoswitch with automatic threshold adjustment. 6 pin Configuration 20V-30V supply.
LED: Gallium Arsenide Phosphide red emitting diode.
Data and operating notes sent with each order. Prices: (including VAT, packaging and carriage)
Type 1: 75p each Type 2: £1.00 each
Type 3: £1.50 each
LED: 17p each, or free with each optoelectronic detector ordered.
Please send C.W.O. or S.A.E. for data only to:
Phototech (Europe), 23a Upper Elmers End Road, Beckenham, Kent

PRINTED CIRCUIT BOARDS, all epoxy/glass-fibre. Roll tinned, ready for immediate assembly. Prices include post and pack, no extras. P.C.B.s available by return for Practical Electronic Amplifiers: 1C50 (Dec. '75) **£3-80** per set (3 P.C.B.s); Orion Jan. '75 **£3-98**; others: Scorpio Mk. 2 **£1-40**; Joanna **£15** per set (14 P.C.B.s S.R.B.P.). Practical Wireless: Disco Amplifiers **£4-28** each. Production space available for: P.C.B. production, silk screen printing, tinning, P.C.B. design and modifications, electroplating full art/graphic, photographic and design facilities. Production estimates by return upon submission of "Roughs". Full masters existing units or circuit diagram to: W.K.F. ELECTRONICS, Welbeck Street, Whitwell, Worksop, Notts. S80 4TW. Callers by appointment to 1-3 Station Road, Whitwell. Tel. Whitwell (Derbyshire) 695 or 544 (STD Code 090974).

CABINET FITTINGS

FOR

Stage Loudspeakers and Amplifier Cabs
Fretcloths, Coverings, Recess Handles, Strap Handles, Feet, Castors, Locks and Hinges, Corners, Trims, Speaker Bolts, etc. etc.
Send 2 x 8p Stamps for samples and list.

ADAM HALL (P.E. SUPPLIES)

Unit Q, Starline Works, Grainger Road
Southend-on-Sea, Essex.

TRANSMIT!

★ **Unique TRANSMITTER RECEIVER** Kit. No licence examinations or tests required to operate this transistorised equipment. Easy to build. Get transmitting. Send **£7-95** for yours now!

★ **Psychedelic MINI-STROBE** Kit. Take a pocket-sized lightning storm to Disco's and parties. "Brain-freeze" 'em with vari-speed stop-motion flashes. Includes super case too. Send **£3-50** now!


(All prices include V.A.T., packing and postage.)

Send remittance to:

BOFFIN PROJECTS
4 CUNLIFF ROAD
STONELEIGH, EWELL, SURREY
(Mail order U.K. only)
Or for more details, send 20p for lists

DIG THIS! Already over £500,000 worth of treasures have been uncovered with electronic metal detectors. C. SCOPE offer the best in BFO, IB and TR machines at competitive prices. Tel. Ashford 29141 for details.

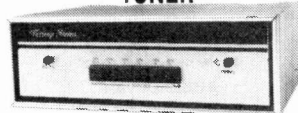THE P.E. "VARICAP" STEREO PUSH BUTTON TUNER



Using the latest Mullard modules for R.F. and I.F. circuits—pre-aligned for ease of construction—this KIT has an F.M. tuner with stereo decoder, push button tuning, self regulated power supply, etc., etc. for highest quality reproduction.

Price **£43-50** inc. VAT, P. & P.
S.A.E. for FREE brochure

We also still supply ALL components for the P.E. "GEMINI" STEREO AMPLIFIER. Send 55p + 12p P. & P. for a full constructional booklet containing performance details, specification assembly instruction and fault finding guide.

ELECTRO SPARES

Dept. P.E. 288 Ecclesall Road,
Sheffield, S11 8PE

CLEARING LABORATORY, scopes, recorders, testmeters, bridges, audio, R.F. generators, turntables, tapeheads, stabilised P.S.U.s, sweep generators, test equipment, etc. Lower Beeding 236.

12 VOLT 21in 13 watt FLUORESCENT LIGHTING (by THORN/AEI)

with diffuser and on/off switch.
Ideal. caravan, boat, emergency lighting, etc.
Guaranteed

£5-50
inc. VAT and post
List price £7-02 inc. VAT.

SALOP ELECTRONICS Tel. 53296
23 Wyle Cop, Shrewsbury, Shropshire

DRY TRANSFER LETTERING for that one-off panel. "BEC" cabinets. Orion case still available. Send for leaflets 15p (refundable): H.M. ELECTRONICS, 275a Fulwood Road, Sheffield, S10 3BD.

PRINTED CIRCUITS and HARDWARE

Readily available supplies of Constructors' hardware, Aluminium sheet and sections. Printed circuit boards, top quality for individual or published designs.

Prompt service.

Send 15p for catalogue.

RAMAR CONSTRUCTOR SERVICES

Masons Road, Stratford on Avon
Warwicks. Tel. 4879

GLASS FIBRE P.C.B.s: 1:1 master and 7p per square inch tinned or 9p per square inch drilled and tinned Plus 30p per board. Send for quotation on double sided boards. Discount for quantity. PROTO DESIGN, 4 Highelife Way, Wickford, Essex SS11 8LA.

RADIO EXCHANGE LTD.

ALL PRICES INCLUDE VAT

NEW EDU-KIT MAJOR

COMPLETELY SOLDERLESS
ELECTRONIC CONSTRUCTION KIT
BUILD THESE PROJECTS WITHOUT SOLDERING IRON OR SOLDER



- 4 Transistor Earpiece Radio
- Signal Tracer
- Signal Injector
- Transistor Tester NPN —PNP
- 4 Transistor Push Pull Amplifier
- 24 Resistors
- 21 Capacitors
- 10 Transistors
- 3 1/2-way Connectors
- 2 Volume Controls
- Ready Wound MW/LW/SW Coils
- 5 Transistor Push Pull Amplifier
- 7 Transistor Loudspeaker Radio MW/LW.
- 5 Transistor Short Wave Radio
- Electronic Metronome
- Electronic Noise Generator
- 3 1/2" Loudspeaker
- 2 Slider Switches
- Ferrite Rod
- 6 1/2 yards of wire
- 1 yard of sleeving, etc.
- Batteryless Crystal Radio
- One Transistor Radio
- 2 Transistor Regenerative Radio
- 3 Transistor Regenerative Radio
- Audible Continuity Tester
- Sensitive Pre-Amplifier
- Earpiece
- Mica Baseboard
- 3 Knobs

Complete kit of parts including construction plans
Total building costs **£9.99**
P.P. and Ins. 65p
(Overseas Seamail P. & P. £3.50)

V.H.F. AIR CONVERTER KIT

Build this converter kit and receive the aircraft band by placing it by the side of a radio tuned to medium wave or the long wave band and operating as shown in the instructions supplied free with all parts.

Uses a retractable chrome plated telescopic aerial, gain control, V.H.F. tuning capacitor, transistor, etc.

All parts including case and plans

£4.35 P.P. & Ins. 40p



POCKET FIVE

Now with 3in Loudspeaker, 3 tunable wavebands, MW, LW and Trawler Band. 7 stages, 5 transistors and 2 diodes, super-sensitive ferrite rod aerial, attractive black and gold case. Size 5 1/2in x 1 1/2in x 3in approx.

Complete kit of parts including construction plans.

Total Building Costs: **£3.99** P.P. and Ins. 50p



NEW Everyday Series

Build this exciting new series of designs.

E.V.5. 5 Transistors and 2 diodes. MW/LW. Powered by 4 1/2V battery. Ferrite rod aerial, tuning condenser, volume control, and now with 3in. loudspeaker. Attractive case with red speaker grille. Size 9in. x 5 1/2in. x 2 1/2in. approx. All parts including Case and Plans.

Total Building costs **£4.75** P. & P. + Ins. 50p

E.V.6. Case and looks as above. 6 Transistors 3 diodes. Powered by 9V battery. Ferrite rod aerial, 3in. loudspeaker, etc. MW/LW coverage. Push/Pull output.

All parts including Case and Plans.

Total Building costs **£5.50** P. & P. + Ins. 50p

E.V.7. Case and looks as above, 7 Transistors and 3 diodes. Six wavebands, MW/LW, Trawler Band SW1, SW2, SW3, powered by 9V battery. Push pull output. Telescopic aerial for short waves. 3in. Loudspeaker.

All parts including Case and Plans.

Total Building Costs **£7.05** P. & P. + Ins. 50p



ROAMER TEN MARK 2

WITH VHF INCLUDING AIRCRAFT

Now with free earpiece and switched socket. 10 transistors. Latest 5" x 3" loudspeaker. 9 tunable wavebands MW1, MW2, LW, SW1, SW2, SW3, Trawler band, VHF and local stations, also aircraft band. Built in ferrite rod aerial for MW/LW. Chrome plated, 6 section telescope aerial, can be angled and rotated for peak short wave and VHF listening. Push pull output using 600mW transistors. Car aerial socket. 10 transistors plus 3 diodes. Ganged tuning condenser with VHF section. Separate coil for aircraft band.

Volume on/off. Wave change and tone controls. Attractive Case in rich chestnut shade with gold blocking. 9in. x 7in. x 4in. Easy to follow instructions and diagrams. Total build: **£11.87** P.P. and Ins. 65p costs:



EDU-KIT
Build Radios, Amplifiers, etc., from easy stage diagrams

Five unit including master unit to construct

Components include: Tuning condenser, 2 volume controls, 2 slider switches, fine tone 3in moving coil speaker, terminal strip, ferrite rod aerial, battery clips, 4 tag boards, 10 transistors, 4 diodes, resistors, capacitors, 3 1/2in knobs. Units once constructed are detachable from master unit, enabling them to be stored for future use. Ideal for schools, educational authorities and all those interested in radio construction.

All parts including case and plans. **£6.99** P.P. and Ins. 55p

JIFFY TESTER

Easy to build and operate, fits in the pocket. A quick checker for continuity of resistors, chokes, diodes, transistors, circuit wiring (not mains) and loudspeakers. Complete with earpiece, jack plug and socket resistors, capacitors, components, etc.

Complete kit of parts including construction plans **£3.15** P. & P. + Ins. 30p



ELECTRONIC CONSTRUCTION KITS

E.C.K. 2 Self Contained Multi-Band V.H.F. Receiver Kit.

9 transistors and 3 diodes. Push pull output. 3in loudspeaker, gain control, superb 9 section swivel ratchet and retractable chrome plated telescopic aerial, V.H.F. tuning capacitor, resistors, capacitors, transistors, etc. Will receive T.V. sound, public service band, aircraft, V.H.F. local stations, etc. Operates from a 9 volt P.P. 7 battery (not supplied with kit).

Complete kit of parts **£7.95** P.P. and Ins. 55p



Including Construction Plans

E.C.K. 4

7 Transistors, 6 tunable wavebands, MW, LW, Trawler Band. 3 Short Wave Bands, Receiver Kit.

With 5in x 3in loudspeaker. Push pull output stage, gain control, and rotary switch. 7 transistors and 4 diodes. 6 section chrome-plated telescopic aerial. 8 in sensitive ready wound ferrite rod aerial, tuning capacitor, resistors, capacitors, etc. Operates from a 9 volt P.P. 7 battery (not supplied with kit).

Complete kit of parts **£7.25** P.P. and Ins. 55p



Including Construction Plans


EDU-KIT JUNIOR

Completely Solderless Electronic Construction Kit. Build these projects without Soldering Iron or Solder.

- ★ Crystal Radio Medium Wave Coverage—No Battery necessary
- ★ One Transistor Radio
- ★ 2 Transistor Regenerative Radio
- ★ 3 Transistor Earpiece Radio Medium Wave Coverage
- ★ 4 Transistor Medium Wave Loudspeaker Radio
- ★ Electronic Noise Generator
- ★ Electronic Metronome
- ★ 4 Transistor Push/Pull Amplifier

All parts including loudspeaker, earpiece, MW ferrite rod aerial, capacitors, resistors, transistors, etc.

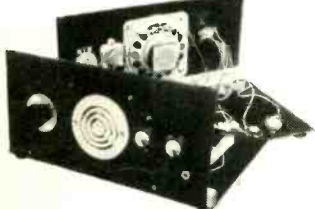Complete kit of parts including construction plans **£7.25** P. & P. + Ins. 50p



To: RADIO EXCHANGE LTD.

61A High Street
Bedford MK40 1SA

Tel.: 0234 52387, REG NO. 788372

- Callers side entrance "Lavelis" Shop.
- Open 10-1. 2.30-4.30 Mon. Fri. 9-12 Sat

Enclose £..... for

Name

Address

PE576

More than just a catalogue

Projects for you to build

Bohndase

**MAPLIN
ELECTRONIC
SUPPLIES**
SUPERSONIC
SAME-DAY-SERVICE
QUALITY COMPONENTS
-FAST!

**READY MADE
ALARM
CLOCK
MODULE!**
* CAN CONTROL
A RADIO, TOO!

**ONLY
£8-60**
INC. V.A.T. & P.I.P.

Just add transformer
and switches!



This is a fully constructed and tested electronic clock module as illustrated. Data sheet supplied with module shows how simple it is to connect an audible alarm, and your battery or mains radio. A data sheet available separately. Please send s.a.e.


Please note: Details not in our catalogue.

- * BRIGHT 4 DIGIT 0.5 INCH INCH DISPLAY
- * FLASHING COLON (1Hz)
- * SWITCH-FOR-DISPLAY SECONDS
- * ALARM SET INDICATOR
- * P.M. INDICATOR
- * POWER FAILURE INDICATION
- * SLEEP TIMER
- * SNOOZE TIMER
- * AUTOMATIC DISPLAY BRIGHTNESS (NEEDS CDS CELL)
- * TIME CAN BE SET ACCURATELY TO WITHIN ONE SECOND
- * LEADING ZERO BLANKING



132 pages!
**REALLY GOOD VALUE
FOR MONEY AT JUST 40p.**

ELECTRONIC ORGAN

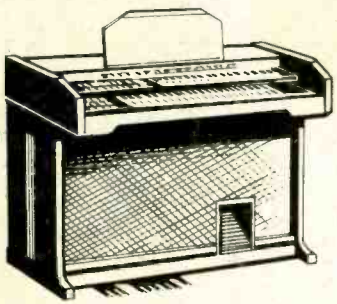

Build yourself an exciting Electronic Organ. Our leaflet MESS1, price 15p, deals with the basic theory of electronic organs and describes the construction of a simple 49-note Instrument with a single keyboard and a limited number of stops.

Leaflet MESS2, price 15p, describes the extension of the organ to two keyboards each with five voices and the extension by an octave of the organ's range.

Solid-state switching and new footages along with a pedal board and a further extension of the organ's range are shown in leaflet MESS3, priced at 35p.

No more doubts about prices

Now our prices are GUARANTEED (changes in VAT excluded) for two month periods—and we'll tell you about price changes in advance for just 30p a year (refunded on purchases). If you already have our catalogue send us an S.A.E. and we'll send you our latest list of GUARANTEED prices. Send us 30p and we'll put you on our mailing list—you'll receive immediately our latest price list then every two months from the starting date shown on that list you'll receive details of our prices for the next GUARANTEED period before the prices are implemented!—plus details of any new lines, special offers, interesting projects—and clip-off coupons to spend on components to repay your 30p when used as directed.

NOTE: The price list is based on the Order Codes shown in our catalogue so an investment in our super catalogue is an essential first step.

Call in at our shop, 284 London Road, Westcliff-on-Sea, Essex. Please address all mail to P.O. Box 3, Rayleigh, Essex, SS6 8LR.

SYNTHESISER



A reprint of the complete article giving full construction details published by "Electronics Today International" between January-

September '74 of the International Voltage Controlled Synthesiser, developed as a "state of the art", now available, price £1.50. S.A.E. please for detailed price list.

GRAPHIC EQUALISER



A really superior high quality stereo graphic equaliser as described in the January edition of "Electronics Today International". We stock all the parts (except wood-

work) including the metalwork drilled and printed. 15p brings you a reprint of the article.

**MAPLIN
ELECTRONIC
SUPPLIES**

P.O. Box 3 Rayleigh Essex SS6 8LR.
Telephone: Southend-on-Sea (0702) 44101