

PRACTICAL

ELECTRONICS

JUNE 1979

50p

CINE SPEED CONTROLLER



**SPECIAL
WATCH
OFFER!**


Plus...

OHIO SUPERBOARD II REVIEW



OHIO SUPERBOARD II NEW — FIRST IN UK — ON DEMO

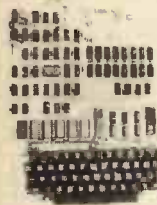For electronic buffs. Fully assembled and tested. Requires +5V at 3 Amps and a video monitor or TV with RF converter to be up and running.



STANDARD FEATURES

- Uses the ultra powerful 6502 microprocessor
- 8K Microsoft BASIC-in-ROM
- Full feature BASIC runs faster than currently available personal computers and all 8080-based business computers.
- 4K static RAM on board expandable to 8K
- Full 53-keyboard with upper/lower case and user programmability
- Kansas City standard audio cassette interface for high reliability
- Full machine code monitor and I/O utilities in ROM

Direct access video display has 1K of dedicated memory (besides 4K user memory), features upper case, lower case, graphics and gaming characters for an effective screen resolution of up to 256 by 256 points. Normal TV's with overscan display about 24 rows of 24 characters; without overscan up to 30 x 30 characters.

EX-STOCK — £263

Please phone to check availability or send £10 to reserve one and pay the balance on delivery

INTERESTED IN HOME COMPUTING?

Start now and don't get left behind THE NASCOM 1 is here Ex-stock with full technical services

Plus the opportunity to join the fastest moving club of personal computer users enabling you to get the most out of your computer. You can OBTAIN and EXCHANGE programs and other software — many now available.

- The Powerful Z80 Microprocessor
- Professional Keyboard
- 1 Kbyte Monitor in EPROM
- 2 Kbyte RAM (expandable)
- Audio Cassette interface
- Plugs into your domestic TV
- Easy construction for straightforward instructions
- no drilling or special tools
- Just neat soldering required.



SAVE £60

FREE B BUG valued at £23.00 plus 10 x C12 cassettes valued at £4.00 plus Standard Modulator valued at £2.25 **WITH EVERY NASCOM**

Only ~~£197.50~~ + 8% VAT (includes p & p + insurance)

- Manuals seperately 2.95
- Z80 programming Manual 6.90
- Z80 Technical Manual 2.95
- PIO Technical Manual 2.95

NEW LOW PRICE
£165
Power supply suitable for NASCOM 19.90

NASCOM AD ONS — Nascom improved monitor B Bug (2K) featuring — *Four times tape speed *Direct text entry without ASCII *Extended keyboard facility *Additional useful subroutines £23.00

- Nascom Vero Case £22.50
- Nascom Joy Stick Kit £14.90
- Nascom Music Box Kit £9.90 (write your own tunes and play them on your Nascom. Complete with full documentation).

GRAPHICS ADD ON BOARD £9.90
Complete kit to upgrade your NASCOM for graphics capability includes full documentation and demonstration program.

SHORT C12 CASSETTES 10 for £4.00 FOR COMPUTER PROGRAMMES

All prices include VAT except where shown. Orders over £5 post and packing free otherwise add 20p. Please make cheques and postal orders payable to COMP, or phone your order quoting BARCLAYCARD or ACCESS number.

COMP COMPUTER COMPONENTS

14 STATION ROAD, NEW BARNET, HERTFORDSHIRE TEL: 01-441 2922 (Sales) 01-449 6596
CLOSE TO NEW BARNET BR STATION — MOORGATE LINE TELEX: 298755
OPEN — 10am to 7pm — Monday to Saturday CONTINUOUS DEMONSTRATIONS
£6 EXTRA FOR SECURICOR DELIVERY

THE TRS-80 (SPECIAL SCOOP) Low Priced, Ready to Go!



Use your own cassette

Level-II with 4K RAM
Improved graphics, print formatting, and a faster cassette transfer rate are features of Level-II BASIC.

£399 + VAT

PLUGS INTO YOUR OWN TV

Level-II with 16K RAM
A combination of 16K RAM and the powerful Level-II BASIC produces a system capable of handling most demands.

£499 + VAT

KEY BOARD ONLY

COMPLETE WITH UHF MODULATOR

UK POWER SUPPLY — £9.90 + VAT

MODULATORS UHF Channel 36

Standard 6 meg band width £2.25
High Quality 8 meg band width £4.90

Teleplay presents the PROGRAMAGAME of all time!

TELEPLAY have produced a product of a strange game for you and your family that will not go out of date as it becomes available, and your colour video centre will be up to date the Teleplay way. You will state the Teleplay way. Works OK on Black and White TV

save points in the long run

EX STOCK IMMEDIATE DELIVERY

REALISTIC SOUND EFFECTS

We offer all this to you for ONLY **£28.90** + £2.31 VAT (Total £31.21)

The Teleplay consists of a Professional Finished Inner Monitor Box Joystick & Hand Controls one cartridge which consists of 10 games Football, Tennis, Solo Soccer, H & Z, Hockey, Hockey, Mania, Accusator, Shoot 'em, Mania, Accusator

TELEPLAY GIVES YOU TWICE THE FUN BUILDING AND PLAYING THE MOST PROFESSIONAL TV GAME KIT EVER OFFERED

SAVE £10

Main Console has 3 Facility Handing Switches

Every 3 months a NEW game will become available to you and those already under production include Superheroes, Shark 'n' Hot, Wide Out and many more. The price of these will vary from £12 to £19 depending upon the complexity of the game.

Additional Cartridges NOW available in four Cartridges and Hand Controls £14.90
Stunt Cycle 4 games Cartridge and Hand Controls £18.90
Tank Battle 2 games Cartridge Controls already with basic kit £12.90
Road Race 2 games

NEW — WIPE OUT cartridge — 6 games £13.90

Cartridges come complete with printed case and map to help you play

All parts fully guaranteed



PRACTICAL ELECTRONICS

VOLUME 15 No. 6 JUNE 1979

CONSTRUCTIONAL PROJECTS

SOUND TO LIGHT—2 CONCLUSION <i>By Ben J. Duncan</i> Construction and lighting displays	26
CINE SPEED CONTROLLER <i>by M. Yeomans</i> Projector speed stabilisation	34
MICROPROCESSOR EVALUATION SYSTEM—2 <i>by D. S. Coutts</i> Construction and testing	42
ULTRASONIC REMOTE CONTROL <i>by M. Plant and G. Hallam</i> Universal 40kHz system	50
WORKSHOP P.S.U. <i>by S. Hoare</i> 60V–1A ranges—meterless test gear	56

GENERAL FEATURES

OHIO SUPERBOARD II REVIEW <i>by A. A. Berk, B.Sc., Ph.D.</i> First good look at this long awaited system	18
SEMICONDUCTOR UPDATE <i>by R. W. Coles</i> A look at some recently released devices	25
R.F.I. SUPPRESSION IN P.S.U.s <i>by B. E. Taylor</i> Guidelines to successful design	54
INGENUITY UNLIMITED Low Cost Thermometer—Guitar Fuzz/Sustain Unit—Lamp Dimmer— Stereo Peak Detecting PPM—Boat Speed Controller	65
MICROBUS <i>by D.J.D.</i> A bi-monthly focus on micro's for the home constructor	68

NEWS AND COMMENT

EDITORIAL	17
PATENTS REVIEW Thought provoking ideas on file at the British Patents Office	31
SPACEWATCH <i>by Frank W. Hyde</i> Venus 11 and Venus 12, Trouble for Scatha, UK-6 Britain's special stargazer	32
WATCH OFFER	33
NEWS BRIEFS Countdown	38
British Satellite—Marshall's Bristol Move	39
Frequency by Time—Teachers to Study—Cut Price Watches—David Cohen	55
POINTS ARISING TRS 80 Review—Metronome—Phaser—Champ-Prog	39
MARKET PLACE New products	40
INDUSTRY NOTEBOOK <i>by Nexus</i> What's happening inside industry	48
BOOK REVIEWS	55

OUR JULY ISSUE WILL BE ON SALE FRIDAY, 8 JUNE 1979

(for details of contents see page 49)

© IPC Magazines Limited 1979. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

TRAIN FOR SUCCESS

in Radio, Television & Electronics

ICS have helped thousands of ambitious people to move up into higher paid more secure jobs in the field of electronics - now it can be your turn. Whether you are a newcomer to the field or already working in the industry, ICS can provide you with the specialised training so essential to success.

Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful, is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

- Telecommunications Technicians
- Radio, T.V. Electronics Technicians
- Technical Communications
- Radio Servicing Theory
- Radio Amateurs
- Electrical Installation Work
- Also MPT Radio Communications Certificate

Diploma Courses

Colour T.V. Servicing
Electronic Engineering & Maintenance
Computer Engineering and Programming
Radio, T.V. and Audio, Engineering & Servicing
Electrical Engineering, Installations & Contracting

Other Career Courses

A wide range of other technical and professional courses are available including GCE.

FREE BOOK

Post this coupon or 'phone today for free ICS careers guide.

Name _____

Address _____

Age _____

ICS

To ICS, Dept. H273, Intertext House,
London SW8 4UJ
or telephone 01-622 9911 (all hours)

TOUCH CONTROLLED LIGHTING KITS (300W)

A Lightdimmer with NO knob. Dimming and on/off functions are controlled by touch. Features include:

- ★ No mains wiring.
- ★ Easy to build - uses one MOS 1C.
- ★ Switches on to preset brightness.
- ★ Can be switched and dimmed from many locations using TDE/K kit making 2-way switching easy.

★★ PRICE TD300K £9.67
TDE/K £1.62

TSD300K TOUCH-SWITCH & DIMMER combined. One touchplate for on/off. Small knob controls brightness. £5.62
TS300K TOUCHSWITCH. Two touchplates. ON/OFF £4.64
TSA300K AUTOMATIC. One touchplate. Preset time delay of variable 2 secs to 3½ mins. £4.64
LO300K LIGHTDIMMER. £3.24
SPECIAL OFFER
10% Discount on any 4 lighting control kits.


DIGITAL VOLTMETER/THERMOMETER KIT



Based on the 7106 single IC 3½ digit D.V.M. the Kit contains a PCB, resistors, capacitors, presets, I.C. and 0.5" liquid crystal display. Components are also included to enable the basic D.V.M. kit to be modified to a Digital Thermometer using a single transistor as the sensor. Requires a 2mA 9V supply (PP3 battery).

ONLY £23.75

24HR CLOCK/APPLIANCE TIMER KIT

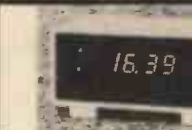

Switches any appliance of up to 1KW on and off at preset times once a day. KIT contains: AV-5-1230 Clock/Appliance Timer IC, 0.5" LED display, mains supply, display drivers, switches, LEDs, triac, complete with PCBs and full instructions. £16.09
White box (56 x 131 x 71mm) - drilled £2.70
- undrilled £2.38
Ready built £24.30

ABOVE PRICES INCLUDE V.A.T.

Quantity discounts on request. Add 25p postage and packing. Callers by appointment only:

T.K. ELECTRONICS (PE) 106 Studley Grange Road, London, W7 2LX.
01-579 9794

TRIACS

400V Plastic Case	16A	97p
3A	53p	
8A	67p	10A 178p
12A	76p	25A 205p
6A with trigger		86p
SCR (IC106D) 5A/400V		41p
Diac		19p

LEDs/DISPLAYS

0.2" Red 13p	(£1.08/10)
Green or Yellow	18p
DL727 Dual 0.5" CA	£1.62
	(two for £3.00)
LCD 3½ digit 0.5" dit	£8.75

SUPER SAVERS

5 x 741 97p	4 x 555	97p
LM3911 Thermometer IC		£1.08p
ZN1034E Timer IC		£1.34p
10 x BC108 Transistors		68p

RESISTORS

¼W (CR25 size) E12 series	
Values 22 ohm to 10 Mohm	
Pack 10 (one value)	11p
10 packs (mixed values)	84p

TRANSFORMERS

Standard 240V mains primary	
100mA secondary (miniature)	
6-0-6V 92p	9-0-9V 97p
12-0-12V	102p

TEMPERATURE CONTROL KIT

Uses LM3911 IC to sense temperature (80°C max) and triac to switch heater. PCB (4 cm. sq.), potentiometer, plus all other components included with instructions. 500W - £3.46 1KW - £3.78

Now, complete your system!



Citronic MM313 Mixer

Ideal for the DIY enthusiast building up a complete disco system 4/6 ch mono. inc. LED indicators, connections via phono sockets at rear. Bargain price, including PSU £84.24.

The ultimate range of speakers

We carry a good selection of high quality chassis for the DIY speaker constructor: 12" or 15" Bass speakers and Dual Concentrics. Exponential horns from £13.77, or our fabulous Piezo Horns which handle a 5K-20K frequency range in any PA system up to 100W (No X over required) and cost only £6.18. each



Projectors

Come and see our specially selected projectors from £42.12 (Squire Multiflect 150) to £94.50 (Tutor 11E) plus the widest array of projector attachment and effects that you'll ever see on continuous demonstration.



Turntables

Our unsurpassed Disco experience has enabled us to select the best turntables for your requirements. For example the new BSR P200 belt drive. ONLY £28.12.



Ropelights

Great effect at discos. 7 metres long. Multiway connectors. 4 channel. £43.20 (inc. pack of spare bulbs)

Bulgian Octal plugs and sockets

There's always hundreds of Bulgian Octal multiway plugs and sockets in stock at Roger Squire's. Each pin rated 6A. Perfect for your Sound to Light System. P552 SOCKET £0.65. P551 PLUG £1.94.



Multiway Cables
4 core (6A) 59p/metre
5 core (6A) 73p/metre
6 core (6A) 86p/metre

Many disco accessories

All Roger Squire's shops have a service department which carries large stocks of DISCO SPARES & ACCESSORIES.

PERSONAL CALLERS ONLY

Roger Squire's
DISCO CENTRES

ALL SHOPS OPEN TUE-SAT
LATE NIGHT WED.
(UP TO 8 PM)

LONDON 176 Junction Road, N19. 50Yds Turnell Park Tube Station. Tel: 01 272 7474
BRISTOL 125 Church Road, Redfield (Near St. George) 1 mile from end of M32
MANCHESTER Tel: 0272 550550
GLASGOW 251 Deansgate 3, 15 mins from City Centre
Tel: 061 831 7676
Margaret Drive Kelvinside 20, just behind the BBC.
Tel: 041 946 3303

WATFORD ELECTRONICS

35 CARDIFF ROAD, WATFORD, HERTS., ENGLAND
MAIL ORDER, CREDITORS WELCOME. Tel. Watford 40588/9

ALL DEVICES BRAND NEW, FULL SPEC. AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O. OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS' OFFICIAL ORDERS ACCEPTED. TRADE AND EXPORT INQUIRY WELCOME. P&P Add 30p to ALL ORDERS UNDER £10.00. OVERSEAS ORDERS POSTAGE AT COST. AIR/SURFACE.

SEND 50p (plus 25p P&P) FOR OUR CATALOGUE

VAT Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 8% to devices marked * to the rest add 12%.

We stock many more items. It pays to visit us. We are situated behind Watford Football Ground. Nearest Underground/BR Station: Watford High Street. Open Monday to Saturday 9.00 am - 6.00 pm. Ample Free Car Parking space available.

ELECTROLYTIC CAPACITORS: Axial lead type (Values are in μ F) 500V: 10.40; 47.68p; 250V: 100.65p; 63V: 0.47, 1.0, 1.5, 2.2, 3.3, 4.7, 5.6, 8.2, 10, 15, 22, 33, 47, 52, 50, 11p; 63, 100, 27p; 50V: 50.11p; 100, 220, 25p; 470, 32p; 1000, 50p; 40V: 22, 33, 8p; 100, 12p; 2200, 3300, 62p; 4700, 85p; 35V: 10, 33, 9p; 330, 47, 32p; 1000, 49p; 25V: 10, 22, 47, 6p; 80, 100, 160, 8p; 220, 250, 13p; 470, 640, 25p; 1000, 27p; 1500, 30p; 2200, 45p; 3300, 62p; 4700, 88p; 16V: 10, 40, 47, 68, 7p; 100, 125, 8p; 330, 14p; 470, 16p; 1000, 1500, 20p; 2200, 34p; 10V: 4, 10, 6p; 640, 10p; 1000, 14p.

Tag End 70V: 2000, 89p; 4700, 135p; 640, 3300, 99p; 50V: 10,000, 255p; 40V: 2500, 65p; 3300, 470, 70p; 15,000, 450p; 25V: 4700, 68p; 2200, 48p; 325V: 32 + 32, 175p.

POLYESTER CAPACITORS: Axial lead type. (Values are in μ F) 400V: 0.001, 0.0015, 0.0022, 0.0033, 9p; 0.0047, 0.0068, 0.01, 0.015, 0.018, 10p; 0.022, 0.033, 10p; 0.047, 0.068, 14p; 0.10, 15p; 0.15, 0.22, 22p; 0.33, 0.47, 39p; 0.68, 45p. 160V: 0.039, 0.15, 0.22, 11p; 0.33, 0.47, 19p; 0.68, 1.10, 27p; 1.5, 29p; 2.2, 32p. **DUBILIER:** 1000V: 0.01, 0.015, 20p; 0.022, 22p; 0.047, 26p; 0.1, 38p; 0.4, 47p.

POLYESTER RADIAL LEAD (Values are in μ F) 250V: 0.01, 0.015, 0.022, 0.027, 6p; 0.033, 0.047, 0.068, 0.1, 7p; 0.15, 11p; 0.22, 0.33, 13p; 0.47, 15p; 0.68, 18p; 1.0, 24p; 1.5, 27p; 2.2, 31p.

TANTALUM BEAD CAPACITORS 35V: 0.1 μ F, 0.22, 0.33, 0.47, 0.68, 1.0, 2.2 μ F; 3.3, 4.7, 6.8, 25V: 1.5, 10, 20V: 1.5, 15V: 10 μ F, 13p each; 47, 100, 40p; 100V: 22 μ F, 33, 6V: 47, 68, 100, 3V: 68, 100 μ F, 20p each.

MYLAR FILM CAPACITORS 100V: 0.001, 0.002, 0.005, 0.01, 0.1 μ F 6p; 0.015, 0.02, 0.04, 0.05, 0.05 μ F 7p; 0.01 μ F, 0.2, 9p; 50V: 0.47 μ F, 11p.

CERAMIC CAPACITORS: 50V 5pF to 10nF; 22nF, 33nF, 47nF; 0.1 μ F, 0.1 μ F; 6p; 0.2 μ F, 7p.

POLYSTYRENE CAPACITORS 10pF to 1nF; 1.5nF to 47nF, 10p.

SILVER MICRA (Values in pF) 3-3, 4-7, 6-8, 10, 12, 18, 22, 33, 47, 50, 68, 75, 82, 85, 100, 120, 150, 220, 250, 9p ea; 300, 330, 360, 390, 600, 820, 18p ea; 1000, 1200, 1800, 2000, 2200, 20p ea.

MINIATURE TYPE TRIMMERS 2.5 5pF, 3 10pF, 10 40pF, 22p, 5 25pF, 5 45pF, 50pF, 88pF.

COMPRESSION TRIMMERS 3-40p, 10-80p, 25-190pF, 30p, 100-500pF, 45p; 1250V, 60p.

SOLDERING PINS* 100 pins 50p; 500 pins 200p.

JACK PLUGS		SOCKETS	
Screened chrome	Plastic body	open metal	moulded with break
2.5mm 13p	10p	8p	11p
3.5mm 18p	14p	13p	contacts 12p
MONO 26p	14p	13p	20p
STEREO 32p	18p	15p	24p

DIN	PLUGS	SOCKETS	In Line
2 PIN Loudspeaker	10p	8p	20p
3 4 5 PIN Audio	13p	10p	20p

Co-axial (plastic/metal)	10p	12p	18p	22p
PHONO assorted colours Metal Screened	10p	8p angle 8p double	15p	20p

BANANA	4mm	11p	12p
2mm <td>11p <td>12p</td> <td>12p</td> </td>	11p <td>12p</td> <td>12p</td>	12p	12p
1mm <td>6p</td> <td>7p</td> <td>7p</td>	6p	7p	7p
WANDER <td>3mm <td>7p</td> <td>7p</td> </td>	3mm <td>7p</td> <td>7p</td>	7p	7p

TTL 74LS (TEXAS)

LS00	13	LS63	150	LS153	76	LS240	236	LS246	185
LS01	13	LS73	46	LS155	96	LS241	231	LS247	48
LS02	14	LS74	46	LS156	96	LS242	232	LS248	186
LS03	14	LS75	48	LS157	76	LS243	233	LS252	228
LS04	14	LS76	40	LS158	96	LS244	155	LS353	228
LS05	23	LS78	40	LS160	128	LS245	270	LS365	65
LS08	23	LS83	115	LS161	98	LS247	190	LS366	65
LS08	22	LS85	118	LS162	38	LS248	10	LS367	65
LS10	23	LS86	43	LS163	102	LS249	190	LS368	66
LS11	22	LS90	38	LS164	114	LS251	134	LS373	180
LS12	23	LS91	104	LS165	75	LS252	142	LS375	160
LS13	38	LS92	89	LS166	226	LS257	110	LS374	
LS14	75	LS93	89	LS168	155	LS258	110	LS377	212
LS15	30	LS95	116	LS169	150	LS259	160	LS378	184
LS20	20	LS96	46	LS170	288	LS260	450	LS379	215
LS21	22	LS107	44	LS173	105	LS266	52	LS384	86
LS22	22	LS109	55	LS174	106	LS273	244	LS385	155
LS26	48	LS112	55	LS175	110	LS275	250	LS386	86
LS27	28	LS113	50	LS181	398	LS279	66	LS390	230
LS28	48	LS114	50	LS183	298	LS280	250	LS393	230
LS30	22	LS122	70	LS189	108	LS283	192	LS396	215
LS32	27	LS127	70	LS190	140	LS290	128	LS396	215
LS33	39	LS124	180	LS191	140	LS293	128	LS398	276
LS37	39	LS125	60	LS192	132	LS295	185	LS399	230
LS38	39	LS126	60	LS193	130	LS298	68	LS445	150
LS40	28	LS132	95	LS194	166	LS299	458	LS447	144
LS42	98	LS136	55	LS195	136	LS300	175	LS490	180
LS47	138	LS138	85	LS196	100	LS302	175	LS498	180
LS48	120	LS139	85	LS197	140	LS303	468	LS498	180
LS49	120	LS145	108	LS199	140	LS324	240	LS670	248
LS51	24	LS147	170	LS200	348	LS325	290	LS673	1050
LS54	28	LS148	173	LS202	345	LS326	294	LS674	1450
LS55	30	LS151	96	LS221	96	LS327	286	LS677	1050

TTL 74*

7400	11	7494	78	74194	98	4056	134
7401	11	7496	57	74195	93	4059	80
7402	11	7497	189	74197	80	4060	115
7403	12	74100	119	74198	160	4061	1425
7404	12	74105	62	74199	175	4062	999
7405	18	74107	29	74200	92	4063	1110
7406	18	74109	54	74201	92	4066	380
7407	38	74111	65	74202	92	4068	22
7408	17	74112	128	74203	115	4068E	20
7409	17	74116	198	74204	115	4069E	20
7410	11	74118	83	74205	15	4070	32
7411	20	74119	144	74206	15	4071	21
7412	20	74120	144	74207	21	4072	21
7413	30	74121	25	74208	115	4073	23
7414	45	74122	46	74209	115	4075	23
7416	30	74123	48	74210	115	4076	85
7417	30	74125	38	74211	115	4078	85
7420	16	74126	57	74212	115	4081	20
7421	29	74128	74	74213	115	4082	21
7422	17	74132	73	74214	115	4085	74
7423	27	74136	65	74215	115	4086	73
7425	27	74141	56	74216	115	4088	150
7426	36	74142	209	74217	115	4089	150
7427	27	74143	314	74218	115	4090	150
7428	30	74144	314	74219	115	4091	150
7430	30	74145	65	74220	115	4092	150
7432	25	74147	175	74221	115	4093	150
7433	40	74148	109	74222	115	4094	150
7437	30	74150	99	74223	115	4095	150
7438	33	74151	64	74224	115	4096	150
7440	15	74153	64	74225	115	4097	150
7442	68	74155	53	74226	115	4098	150
7443	115	74156	80	74227	115	4099	150
7444	112	74157	67	74228	115	4100	150
7445	94	74159	85	74229	115	4101	150
7446	94	74160	82	74230	115	4102	150
7447	94	74161	82	74231	115	4103	150
7448	51	74162	92	74232	115	4104	150
7450	17	74163	92	74233	115	4105	150
7451	17	74164	105	74234	115	4106	150
7453	17	74165	105	74235	115	4107	150
7454	17	74166	140	74236	115	4108	150
7460	17	74167	200	74237	115	4109	150
7469	40	74168	200	74238	115	4110	150
7472	25	74172	625	74239	115	4111	150
7473	32	74173	120	74240	115	4112	150
7474	25	74174	87	74241	115	4113	150
7475	38	74175	87	74242	115	4114	150
7476	38	74176	75	74243	115	4115	150
7478	48	74178	155	74244	115	4116	150
7481	86	74178	155	74245	115	4117	150
7482	69	74180	85	74246	115	4118	150
7483	72	74181	165	74247	115	4119	150
7484	95	74182	88	74248	115	4120	150
7485	75	74184	135	74249	115	4121	150
7486	31	74185	135	74250	115	4122	150
7490	30	74190	95	74251	115	4123	150
7491	75	74191	95	74252	115	4124	150
7492	38	74192	98	74253	115	4125	150
7493	32	74193	98	74254	115	4126	150

CMOS*

4000	15	4070	32	4096	150
4001	17	4071	21	4097	150
4002	17	4072	21	4098	150
4003	17	4073	23	4099	150
4005	23	4075	23	4100	150
4008	85	4076	85	4101	150
4009	38	4077	40	4102	150
4010	38	4078	21	4103	150
4011	18	4081	20	4104	150
4012	18	4082	21	4105	150
4013	45	4085	74	4106	150
4014	80	4086	73	4107	150
4015	82	4088	150	4108	150
4016	85	4093	85	4109	150
4017	82	4094	190	4110	150
4018	30	4095	190	4111	150
4019	48	4096	110	4112	150
4020	99	4097	372	4113	150
4021	95	4098	110	4114	150
4022	85	4099	145	4115	150
4023	22	4160	109	4116	150

+ BATTERY FLUORESCENT LIGHTING —



White Enamel cases as shown above, including lampholders. Type "A" or "B" £1.50 + 12p VAT. Case only, £1.00 + 8p VAT. Plastic Lampholders to suit 50p + 4p VAT pair. Ceramic (adaptable) 40p + 4p VAT pair. Tubes to fit (21 in.) £1.00 + 8p VAT. (These can only be supplied when cases are ordered due to risk of postal damage.) Case type "C" (18 in.) or Case type "D" (12 in.) including lampholders £1.25 + 10p VAT.

INVERTED TRANSFORMERS, special design for maximum efficiency £1.00 each + 8p VAT
 Transistor, Heat Sink, Circuit board cut to size, Resistor, Capacitors etc. £1.00 pack + 8p VAT
 21 in. Fittings built and tested £4.95 + 40p VAT
 12 in. ditto (Batten type) £4.95 + 40p VAT

THIS IS ABOUT HALF THE PRICE THAT A SIMILAR FITTING WOULD COST YOU ELSEWHERE!!!!

WHY NOT DO AS MANY OTHERS ARE DOING, BUILD THEM AND SELL THEM TO YOUR CAMPING FRIENDS?

PRINTED CIRCUITS. WHY NOT MAKE YOUR OWN WITH FOTOLAK POSITIVE LIGHT SENSITIVE LACQUER

Now you can produce perfect printed circuits in minutes! Method: Spray cleaned board lightly with lacquer. When dry, place positive master of required circuit on now sensitised surface. Expose to daylight, develop and etch. Any number of exact copies can of course be made from one master. Widely used in industry for prototype work.

FOTOLAK Aerosol	£1.50 + 12p VAT	Pre-coated 1/16" Fibre-glass board:	Plain Copper-clad Fibre-glass	Single-sided	Double
Developer	30 + 3p VAT	204mm x 114mm	Approx. 3-18mm thick, sq. ft.	£1.25 + 10p VAT	£1.50 + 12p VAT
Ferric Chloride	40 + 4p VAT	204mm x 228mm	Approx. 2-00mm thick, sq. ft.	£2.00 + 16p VAT	£2.25 + 18p VAT
Clear Acetate Sheet	12	408mm x 228mm	Approx. 1-00mm thick, sq. ft.	£1.50 + 12p VAT	£1.75 + 14p VAT
Daylo Pens	75 + 6p VAT	467mm x 305mm	Approx. .79mm thick, sq. ft.	£1.25 + 10p VAT	

Giant packs of unused mixed components! Weight 4lbs., these contain an assortment of resistors (carbon and wire-wound); capacitors, (electrolytic, paper, silver-mica, polyester and polystyrene); transistors, diodes, volume and pre-set controls and hosts of other 'bits and pieces'. No two bags are the same, but all contain a jolly good mixture of parts. Ideal for the odds and ends box!!! Per bag..... £3.00 + 38p VAT

Brand new printed circuit boards containing I.C.'s., transistors, diodes, resistors, capacitors etc. etc. It is quite impossible to list these so we are selling by weight at £1.00 + 8p VAT per lb. This could include upwards of 100 integrated circuits! Send as many £1's as you wish, we will weigh as varied a parcel as possible and refund your change!

SPECIAL OFFER! Few only 3-channel (each 750 watts) Sound-to-light units. Fantastic value for money! Plug into any loud-speaker socket and create your-own disco-type light show! Any mains lamps may be used £17.95 + £1.44 VAT

PLEASE NOTE: Prices + VAT as shown. No VAT on overseas orders. Postage **INLAND** 65p per order. Overseas include extra to cover. We will refund any excess paid. Any enquiries for further details **MUST** include stamped addressed envelope!

G. F. MILWARD (ELECTRONIC COMPONENTS LTD.), 369 Alum Rock Road, B'Ham B8 3DR. 021-327 2339

INTRODUCING

the Crofton
**ASCII Encoded
 Keyboard**
 in kit form **£38.40** inc. VAT and p/p

ORDER ALL YOUR ELECTRONIC REQUIREMENTS FROM ONE SOURCE

Whether for your computer or any other project. We stock a wide range of components, P.E. P.C.B's Calscope Oscilloscopes. Television Camera Kits, Lens, Tubes and Monitors.

AS WELL AS THE UNBEATABLE CROFTON 6800 MICRO which is probably the best value for money today.

Write or telephone for full details of our products

CROFTON
Electronics Limited
 35 Grosvenor Road, Twickenham
 Middlesex • Tel: 01-891 1923

RADIO EXCHANGE LIMITED

NEW ROAMER TEN R.K.3.

Multiband V.H.F. and A.M. Receiver. 13 Transistors and Six Diodes. Quality 6" x 3" Loudspeaker.

With Multiband V.H.F. section covering Mobiles, Aircraft, TV. Sound, Public Service Band, Local V.H.F. Stations etc. and Multiband A.M. section with Airspaced Tuning Capacitor for easier and accurate tuning, covering M.W.1, M.W.2, L.W. Three Short Wave Bands S.W.1, S.W.2, S.W.3 and Trawler Band. Built-in Ferrite Rod Aerial for Medium Wave, Long Wave and Trawler Band, etc., Chrome-plated 7 section Telescopic Aerial, angled and rotatable for peak Short Wave and V.H.F. reception, Push-Pull output using 600mW Transistors. Gain, Wave-Change and Tone Controls. Plus two Slider Switches. Powered by P.P.9-9 volt Battery.

Complete kit of parts including carrying strap. Building Instructions and operating Manuals.



£14.79 + £1.10 P & P

For further details of our other kits please write, enclosing S.A.E., to:

Radio Exchange Ltd
 61A High Street
 Bedford MK40 1SA

Callers welcome. Reg. No. 788372


Clef Kits —

Designer approved quality kits for Electronic Musical Instrument Construction.

JOANNA 72 & 88 PIANOS
 Six and 7½ Octave Electronic Pianos with unique Touch Sensitive Action, as used in the P.E. JOANNA, which electronically simulates piano key inertia — a feature not available in any other design. A new physical layout has been adopted to simplify construction.

P.E. STRING ENSEMBLE
 The only kit available to the proven A. J. Boothman Design for this versatile String Machine.

Send S.A.E. to —

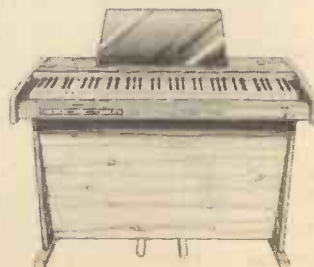

Clef Products (Dept P.E.) 16, Mayfield Road, Bramhall, Cheshire SK7 1JU

Measure Resistance to 0.01Ω ... At a Price that has no resistance at all


New **ELENCO PRECISION** Digital Multimeter M1200B
USA

ONLY £55 (+£3 p&p + VAT £4.64 = £62.64)

***FULLY GUARANTEED
FOR 2 YEARS**

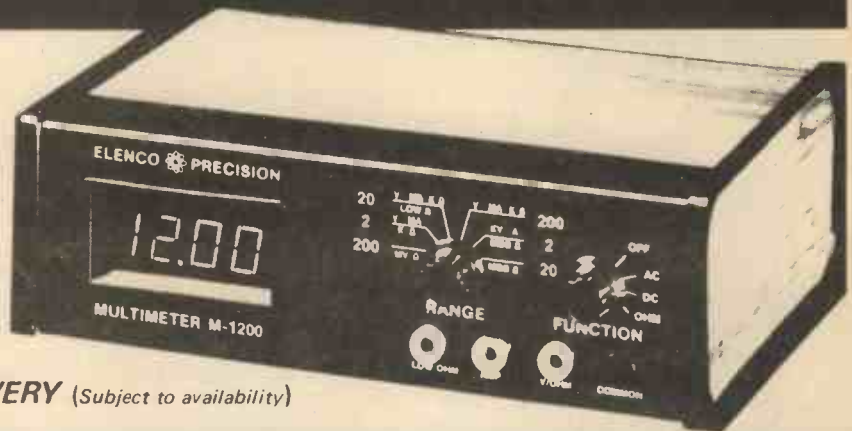***METAL CASE**

***EX STOCK DELIVERY** (Subject to availability)



THE ULTIMATE IN PERFORMANCE - MEASURES RESISTANCE TO 0.01 OHMS, VOLTAGE TO 100 MICROVOLTS, CURRENT TO 1 MICROAMPS AT LOWEST EVER PRICE!

FEATURES

- 3½ digits 0.56" high LED for easy reading
- 100μV, 1μA, 0.01Ω resolution
- High input impedance 10 Megohm
- High accuracy achieved with precision resistors, not unstable trimpots
- Input overload protected to 1000V (except 200mV scale to 600V)
- Auto zeroing, autopolarity
- Mains (with adaptors not supplied) or battery operation-built-in charging circuitry for NiCads
- Overrange indication
- Hi Low power ohms, Lo for resistors in circuit, Hi for diodes

SPECIFICATIONS:

DC Volts	Range 200mV, 2V, 20V, 200V, 1000V Accuracy 1% ± 1 digit, Resolution .1mV Overload protection 1,000 volts max
AC Volts	Range 200mV, 2V, 20V, 200V, 1000V (Response 45Hz to 5KHz) Accuracy 1.5% ± 2 digits, Resolution .1mV Overload protection 1000V max, 200mV scale 600V
DC Current	Range 2mA, 20mA, 200mA, 2amp. Accuracy 1% ± 1 digit, Resolution 1 Microamp Overload protection -- 2 amp fuse and diodes
AC Current	Range 2mA, 20mA, 200mA, 2 amp Accuracy 1.5% ± 2 digits, Resolution 1 Microamp Overload protection -- 2 amp fuse and diodes
Resistance	Range 20, 200, 2K, 200K, 2 Meg, 20 Meg. Accuracy 1% ± 1 digit, Resolution .01 ohms
Environmental	Temp coefficient 0° to 30°C ± .025% °C Operating Temp 0° to 50° C Storage - 20° to 60° C
General	Mains adaptor: 6 - 9 Volts @ 200mA (not supplied) 4C size batteries (not supplied) Size 8¼ x 5¼ x 2¼ Weight 2½ lbs.

At £55, M1200B is the best buy among DMM's currently available. Its 0.01 ohms resolution allows you to detect shorted windings in coils, transformers or motors. It is also useful in checking low contact resistance in switches, relays or connectors. Poor solder connections can also be spotted. The low power ohms function permits accurate measurements of in circuit resistance without forward biasing semiconductor junctions.

You have been waiting a long time for a digital multimeter with all these features at a price like this. Now its yours.

Also available from retail shops:

Audio Electronics, 301 Edgware Rd, London W2
Z & I Aero Services, 85 Tottenham Court Road
London W.1

***AGENTS WANTED**

ELENCO PRECISION Sole UK Distributor

ME Maclin-Zand Electronics Ltd
38 Mount Pleasant, London WC1XOAP
Tel. 01-837 1165 or Hemel Hempstead
(0442) 832 966
Telex. 8953684 MACLIN G

© N Zand PE for further information

To: Maclin-Zand Electronics Ltd PE6
1st Floor, Unit 10, East Block
38 Mount Pleasant, London WC1X OAP

Please send me _____ DMM M1200B
@ £62.64 inc. p & p + VAT (overseas £60).

I enclose cheque/P.O./Bank Draft for £ _____

Name _____ (BLOCK
Address _____ LETTERS
PLEASE)

ALPHA OR BETA. BOTH BETTER.



Alpha IV



Beta

A glance at the front panel of the Gould Advance Alpha IV reveals much of its story. An intelligent use of technology – but at a down-to-earth price of only £105.*

A second look shows a big and beautiful, '2000 count', L.C.D. for displaying 25 ranges of AC/DC voltage and current and resistance.

A third, the snug compartment for the throw-away batteries which can give over 400 hours' operation.

But would you, perhaps, rather buy a Beta?

It has 28 ranges of AC/DC current, resistance and AC/DC volts – plus optional temperature measurement (–20 °C to +120 °C).

Within either you notice our very special CMOS chip (with an on-chip oscillator) and a simple lay-out that exudes longlife.

But, apart from the fact that both Alpha IV and Beta carry a 'Made-in-Britain' label, they sport another important parameter.

A two-year, seldom called-upon, guarantee.

Exercise your options and ask for data from Gould on both.

You'd better!

* Price exclusive of VAT, and effective only at time of writing.



GOULD

Gould Instruments Division,
Roebuck Road, Hainault, Essex IG6 3UE
Telex: 263785
TELEPHONE: 01-500 1000



Wilmslow Audio

THE firm for speakers!

SEND 15p STAMP FOR THE WORLD'S BEST CATALOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS, ETC. AND DISCOUNT PRICE LIST

AUDAX ● AUDIOMASTER ● BAKER
BOWERS & WILKINS ● CASTLE ● CELESTION
CHARTWELL ● COLES ● DALESFORD
DECCA ● EMI ● EAGLE ● ELAC ● FANE
GAUSS ● GOODMAN'S ● I.M.F. ● ISOPHON
JR ● JORDON WATTS ● KEF ● LEAK ● LOWTHER
McKENZIE ● MONITOR AUDIO ● PEERLESS
RADFORD ● RAM ● RICHARD ALLAN ● SEAS
SHACKMAN ● STAG ● TANGENT ● TANNOY
VIDEOTONE ● WHARFEDALE ● YAMAHA

WILMSLOW AUDIO (Dept. P.E.)
SWAN WORKS, BANK SQUARE, WILMSLOW,
CHESHIRE SK9 1HF

Discount Hi-Fi, etc. at 5 Swan Street and 10 Swan Street
Tel.: Wilmslow 529599 for Speakers Tel.: Wilmslow 526213 for Hi-Fi

FLADAR DUAL VOLTAGE TRANSFORMERS

PRIMARY 220-240 50HZ.
ALTERNATIVE SECONDARY VOLTAGE AND CURRENT
AVAILABLE BY SERIES OR PARALLEL CONNECTION

Type	Voltage	Current	£	p/p	Type	Voltage	Current	£	p/p
06FE06	6+6	0.5A EACH	1.71	54p	12FE24	24+24	0.2A EACH	2.27	65p
08FE06	6+6	0.6A EACH	2.05	64p	60FE24	24+24	1.2A EACH	4.30	92p
12FE06	6+6	1A EACH	2.27	65p	80FE24	24+24	1.5A EACH	5.10	1.08p
20FE06	6+6	1.6A EACH	2.96	76p	50FE28	28+28	0.75A EACH	3.51	76p
50FE06	6+6	3A EACH	3.51	76p	60FE28	28+28	1.1A EACH	4.30	92p
80FE06	6+6	4A EACH	4.30	92p	80FE28	28+28	1.4A EACH	5.10	1.08p
08FE09	9+9	0.3A EACH	1.71	54p	20FE30	30+30	0.35A EACH	2.96	76p
08FE09	9+9	0.5A EACH	2.05	64p	50FE30	30+30	0.75A EACH	3.51	76p
12FE09	9+9	0.75A EACH	2.27	65p	60FE30	30+30	1A EACH	4.30	92p
20FE09	9+9	1A EACH	2.96	76p	80FE30	30+30	1.2A EACH	5.10	1.08p
50FE09	9+9	2.5A EACH	3.51	76p					
80FE09	9+9	3A EACH	4.30	92p					
06FE12	12+12	0.25A EACH	1.71	54p					
08FE12	12+12	0.3A EACH	2.05	64p					
12FE12	12+12	0.5A EACH	2.27	65p					
20FE12	12+12	0.8A EACH	2.96	76p					
50FE12	12+12	2A EACH	3.51	76p					
80FE12	12+12	2.5A EACH	4.30	92p					
80FE12	12+12	3A EACH	5.10	1.08p					
06FE15	15+15	0.2A EACH	1.71	54p					
08FE15	15+15	0.25A EACH	2.05	64p					
12FE15	15+15	0.4A EACH	2.27	65p					
20FE15	15+15	0.6A EACH	2.96	76p					
50FE15	15+15	1.6A EACH	3.51	76p					
60FE15	15+15	2A EACH	4.30	92p					
80FE15	15+15	3A EACH	5.10	1.08p					
06FE20	20+20	0.15A EACH	1.71	54p					
12FE20	20+20	0.25A EACH	2.27	65p					
20FE20	20+20	0.5A EACH	2.96	76p					
50FE20	20+20	1.2A EACH	3.51	76p					
60FE20	20+20	1.5A EACH	4.30	92p					
80FE20	20+20	2A EACH	5.10	1.08p					
CHARGER TRANSFORMER									
48FE12	0-6-12	4A	3.51	76p					
66FE12	0-6-12	5A	4.32	92p					
70FE12	0-6-12	6A	5.50	1.08p					
MULTI TAP RANGE									
VOLTAGES AVAILABLE 12-0-12 or 15-0-15 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30									
30FE30		1A	3.83	76p					
60FE36		2A	5.16	92p					
80FE36		3A	6.48	1.08p					
CENTRE TAP SECONDARY									
06FE30	6-0-6	1A	1.66	54p					
08FE40	8-0-8	1A	2.00	54p					
12FE50	12-0-12	1A	2.21	65p					
20FE80	15-0-15	1A	2.89	76p					
50FE80	20-0-20	2A	3.43	76p					
60FE100	28-0-28	2.2A	4.06	92p					
80FE70	24-0-24	3A	4.97	1.08p					
90FE60	20-0-20	4A	5.24	1.24p					
100FE26	26-0-26	3.5A	5.40	1.24p					
100FE28	28-0-28	3.5A	5.40	1.24p					
100FE30	30-0-30	3A	5.40	1.24p					
100FE36	36-0-36	3A	5.40	1.24p					
150FE26	26-0-26	5A	7.02	1.40p					
150FE30	30-0-30	4A	7.02	1.40p					
150FE36	36-0-36	4A	7.02	1.40p					
150FE42	42-0-42	3A	7.02	1.40p					

FLADAR ELECTRIC
P.O. BOX 19
WESTCLIFF-ON-SEA
ESSEX. 0702-613314

TRADE ENQUIRIES
WELCOME

PLEASE ENQUIRE
FOR OTHER TYPES
NOT SHOWN

PAYMENT TERMS:
C.W.O. Cheques,
Postal Orders
All Prices
include V.A.T.

RELAYS SIEMENS, PLESSEY, etc. MINIATURE RELAYS

RELAYS. WIDE RANGE OF A.C. and D.C. RELAYS AVAILABLE from stock. phone or write in your enquiries

FT3 NEON FLASH TUBE

High intensity multi turn high voltage neon glow discharge flash tube. Design for ignition timing etc. £1.50. P & P 25p (£1.75 inc. VAT). 3 for £3. P & P 50p (£3.75 inc. VAT & P.)

RODENE UNISEIT TYPE 71 TIMER

0-60 sec. 230V a.c. operation. Incorporating a lapsed time indicator and repeat facilities. A precision motorised timer ideal for process timing photography, welding, mixing, etc. Price £6. P & P 60p. £7.13 inc. VAT & P. & P.

N.M.S.



WHY PAY MORE?

MULTI RANGE METER TYPE MF15A a.c. d.c. volts 10 - 50, 250, 500, 1000. Ma 0-5, 0-10, 0-100. Sensitivity 2000V. 24 range diameter 133 by 93 by 46mm including test leads. Price £7.00 plus 50p P. & P. (£8.10 inc. VAT & P.)

N.M.S.



METERS (New) - 90 mm DIAMETER

A.C. Amp. Type 6272. 0-1A. 0-5A. 0-20A. A.C. Volt. 0-150V. 0-300V. D.C. Amp. Type 65C5. 0-2A. 0-10A. 0-20A. D.C. Volt. 0-15V. 0-30V. All types £3.50 ea. + P. & P. 50p (£4.32 inc. VAT), except 0-50A. 0-100A. D.C. price £5.00 + 50p. P. & P. (£5.94 inc. VAT).



NEW HEAVY DUTY SOLENOID. mfg

by Magnetic Devices. 240V a.c. operation approx. 10lbs pull (intermittent rating) at 1/2 in. Price £4.00 P. & P. 60p. (£4.95 inc. VAT & P.). N.M.S.



A.C. SOLENOID pvc ether type 176/2

240 V. A.C. Approx. 1lb. at 1/2 in. intermittent rating. Price £1 p&p 20p (£1.30 inc. VAT & P.).

WESTOOL TYPE MM8 Model 2, 240V AC. Approx 1 1/2 lb pull at 1/2 inch. Rating 1. Price £1.50 p&p 20p. (£1.84 inc. VAT & P.) N.M.S.

MINIATURE UNISELECTOR

12 volt. 11-way. 4 bank (3 non-bridging 1 homing). £2.50. P. & P. 35p (£3.08 inc. VAT & P.). N.M.S.



240 A.C. SOLENOID OPERATED FLUID VALVE

Rated 1 p.s.i. will handle up to 7 p.s.i. Forged brass body, stainless steel core and spring 1/2 in. b.s.p. inlet outlet. Precision made. British mfg. PRICE £3.50 Post 50p (£4.32 inc. VAT & P.)



MICRO SWITCHES

Sub min Honeywell roller m/s type 3115m 9061. 10 for £2.50 post paid. LEVER OPERATED 20 amp. C/O. Mfg. by Unimax USA. 10 for £4. P. & P. 50p (min. order 10) £4.86 inc. VAT. D.P. C/O lever m/s switch mfg. by Cherry Co. USA. Precious metal low resistance contacts. 10 for £2.25 P. & P. 30p. Total inc. VAT £3.02 (min 10).



MERCURY SWITCH

Size 27mm x 5mm, 10 for £5.00 (inc. VAT £5.72) min quantity 10. Heavy duty type, size 38 x 16 x 10mm, minimum quantity 10. £7.50 post paid (£8.10 inc. VAT & P.).



VORTEX BLOWER AND VACUUM UNIT

Dynamically balanced totally enclosed 9in rotor with max. air delivery of 1.5 cubic metres per min. Max. static pressure 600mm W.G. Suction or blow from 2 side-by-side 37mm I.D. circular apertures fitted to base of unit. Powerful continuously rated 115V a.c. motor mounted on alloy base with fixing facilities. Dimensions: length 32cm x width 25cm x height 25cm. These units are ex equipment but have had minimum use. Fully tested prior to despatch. Price £12 + £1.50 P. & P. (£14.50 inc. VAT & P.). Suitable transformer for 230/240V a.c. £6 + £1 P. & P. (£7.56 inc. VAT & P.).



CENTRIFUGAL BLOWER

Smith type FFB 16 x .022 220/240V A.C. Aperture 10 x 4 cm overall size 16 x 14cm. Price £3.75 P. & P. 75p. (inc. VAT £4.86). Other types available. S.A.E. for details



24 volt. D.C. BLOWER UNIT

Precision 24 volt. D.C. 0.8 amp Blower that works well on 12V 0.4 amp D.C. Producing 30 cu.ft. min at normal air pressure. £4.50 P. & P. 75p (inc. VAT £5.61). N.M.S.

INSULATION TESTERS NEW!

Test to I.E.E. Spec Rugged metal construction suitable for bench or field work constant speed clutch Size L 8in W 4in H 6in weight 6lb. 500V. 500 megohms. £49. Post 80p (£53.78 inc. VAT & P.). 1,000V 1,000MΩ. £55. Post 80p (£60.26 inc. VAT & P.) SAE for leaflet



All Mail Orders—Callers—Ample Parking

Dept. PE, 57 BRIDGMAN ROAD
CHISWICK, LONDON W4 5BB
Phone 01-995 1560

Showroom open Mon.-Fri.

VARIABLE VOLTAGE TRANSFORMERS

INPUT 230/240V a.c. 50/60 OUTPUT

VARIABLE 0-260V All Types SHROUDED TYPE

200 watt (1 amp inc. a.c. voltmeter) £14.50
0.5 KVA (2 amp MAX) £17.00
1 KVA (5 amp MAX) £22.50
2 KVA (10 amp MAX) £37.00
3 KVA (15 amp MAX) £45.50
5 KVA (25 amp MAX) £74.00
10 KVA (50 amp MAX) £168.00
15 KVA (75 amp MAX) £260.00



CARRIAGE AND PACKING EXTRA

LT TRANSFORMERS

0-10-15V at 3 amp (ex new equip) £2.50 P. & P. 50p (£3.24 inc. VAT)
13-0-13V at 1 amp £2.50 P. & P. 50p (£3.24 inc. VAT)
25-0-25V at 2 amp £4.50 P. & P. 75p (£5.67 inc. VAT & P.)
0-4V/6V/24V/32V at 12 amp £18.50 P. & P. £1.90 (£22.03 inc. VAT & P.)
0-6V/12V at 20 amp £14.70 P. & P. £1.50 (£17.50 inc. VAT)
0-12V at 20 amp or 0-24V at 10 amp £12.00 P. & P. £1.50 (£14.58 inc. VAT & P.)
0-6V/12V at 10 amp £8.25 P. & P. £1.25 (£10.26 inc. VAT)
0-6V/12V/17V/18V/20V at 20 amp £19.00 P. & P. £1.50 (£22.10 inc. VAT & P.)
0-10V/17V/18V at 10 amp £10.50 P. & P. £1.50 (£12.96 inc. VAT)
Other types in stock; phone for enquiries or send sae for leaflet.

HY-LIGHT STROBE KIT MK IV

Latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/240V a.c. operation. Designed for larger rooms, halls, etc. Speed adjustable 1-20 f.p.s. Light output greater than many (so called 4 Joule) strobes. Price £19.00. Post £1 (£21.60 inc. VAT & P.). Specially designed case and reflector for Hy-Light £8.80. Post £1 (£10.58 inc. VAT & P.).

XENON FLASHGUN TUBES

Range available from stock SAE for details



ULTRA VIOLET BLACK LIGHT FLUORESCENT TUBES

4ft. 40 watt £8.70 (callers only) 2ft. 20 watt £6.20. Post 75p. (£7.51 inc. VAT & P.) (For use in stan. bi-pin fittings) Mir 1 1/2 in. 8 watt £2.80. Post 35p. (£3.40 inc. VAT & P.) 9 in. 6 watt £2.25. Post 35p. (£2.81 inc. VAT & P.). 6 in. 4 watt £2.25. Post 35p. (£2.81 inc. VAT & P.). Complete ballast unit, for either 6", 9" or 12" tube 230V AC or DC or £3.50. Post 45p. (£4.27 inc. VAT & P.). 400 watt UV lamp and ballast complete £31.50. Post £3. (£37.26 inc. VAT & P.). 400 watt UV lamp only £11.25. Post £1.20 (£13.45 inc. VAT & P.).

SQUAD LIGHT

A new conception in light control. Four channels each capable of handling 750 watts of spotlights, floodlights or dozens of small mains lamps. Seven programs all speed controlled plus flash modulation, effectively giving 14 different displays. Makes sound-to-light obsolete. Completely electrically and mechanically noise free. S.A.E. (foolscap) for further details. Price £60.00 p&p 70p (£65.61 inc. VAT & P.).



WIDE RANGE OF DISCO LIGHTING EQUIPMENT

S.A.E. (foolscap) for details

Superior Quality Precision Made NEW POWER RHEOSTATS

New ceramic construction, embedded winding heavy duty brush assembly, continuously rated.
25 WATT 10/25/50/100/250/500/1kΩ/1.5kΩ, £2.40. Post 20p (£2.81 inc. VAT & P.)
50 WATT 2500 £2.90. Post 25p (£3.40 inc. VAT & P.)
100 WATT 1/5/10/25/50/100/250/500/1kΩ/1.5kΩ/2.5kΩ/3.5kΩ £5.90 p & p 35p (£6.75 inc. VAT)
Black, Silver, Skirted knob calibrated in Nos. 1-9 1/4 in. dia. brass bush. Ideal for above Rheostats 24p each.



SPECIAL OFFER

BERCO type L RHEOSTAT 85 ohm 300 watt 1.86 amp. £7.50 p. & p. 50p. (Total: £8.64 inc. V.A.T.). N.M.S.

RELAYS

Wide range of AC and DC relays available from stock. Phone or write in your enquiries

230/240V A.C. Relays: Arrow 2 c/o. 15 amp £1.50 (£1.84 inc. VAT & P.). T.E.C. open type 3 c/o. 10 amp £1.10 (£1.40 inc. VAT & P.). Omoron or Keyswitch 1 c/o. 7 amp £1.00 (£1.30 inc. VAT & P.). D.C. Relays: Open type 9/12V 3 c/o 7 amp £1.00 (£1.30 inc. VAT & P.). Sealed 12V 1 c/o 7 amp octal base. £1.00 (£1.30 inc. VAT & P.). Sealed 12V 2 c/o 7 amp octal base. £1.25 (£1.56 inc. VAT & P.). Sealed 12V 3 c/o 7 amp 11-pin. £1.35 (£1.67 inc. VAT & P.). 24V. Sealed 3 c/o 7 amp 11-pin £1.35 (£1.67 inc. VAT & P.). (amps = contact rating). P & P on any Relay 20p. Other types available — phone for details. N.M.S.

Diamond H heavy duty A.C. relay 230/240V a.c., two C/O contacts 25 amps res at 250 c. £2.50 p&p 50p. (£3.24 inc. VAT & p&p) Special base 50p. N.M.S.

GEARED MOTORS

4 1/2 rpm. 115V. a.c. 50 cycle, mf. SIGMA Inst. Ltd. U.S.A. Price: £7.50 + 75p. P. & P. (£8.91 inc. VAT). supplied with transformer, N.M.S.

7 1/2 rpm. 115V. a.c. 50 cycle approx. 25lb. mf. KLAXON. 28 rpm. 115V. a.c. 20lb. in. reversible. 71 rpm. 115V. a.c. 10lb. in. reversible. all approximately similar to drawing. Price of above 3 Motors: £4.75 + 75p. P. & P. (£5.95 inc. VAT). N.M.S. Any of above 3, supplied with Transformer for 240V. operation: £7.25 + £1.00 P. & P. (£8.91 inc. VAT).



19 rpm FHP 220/240V. a.c. reversible, torque 14.5kg. Gear ratio 144-1. Brand new including capacitors. mf. CITENCO. Price: £14.25 + £1.25 P. & P. (£16.20 inc. VAT). N.M.S.



30 rpm. 230/240V. a.c. 50lb. in. mf. PARVALUX. Price: £15.00 + £1.50 P. & P. (£17.82 inc. VAT). N.M.S.

56 rpm. 240V. a.c. 50lb. in. 50Hz 0.7 amp. Shaft length 35mm. Dia. 16mm. Wt. 6kg. 600g. mf. FRACMO. Price: £15.00 + £1.50 P. & P. (£17.82 inc. VAT). N.M.S.



100 rpm. 110V. a.c. 115lb. in. 50Hz 2.8 amp. single phase split capacitor. Immense power. Continuously rated. Totally enclosed. Fan-cooled. In-line gearbox. Length 250mm. Dia. 135mm. Spindle dia. 15.5mm. length 145mm. Tested. Price: £12.00 + £1.50 P. & P. (£14.58 inc. VAT). R. & T. Suitable Transformer for 230/240V. operation. Price: £8.00 + 75p. P. & P. (£8.45 inc. VAT).



200 rpm. 35 lbs. in. 115V. 50Hz. Price: £11.00 + £1.50 P. & P. (£18.90 inc. VAT). N.M.S. Suitable Transformer for 230/240V. a.c. Price: £8.00 + £1.00 P. & P. (£9.72 inc. VAT). N.M.S.

500 rpm. 230/250V a.c. 3 1/2 in. 2 right-angled spindles. Mf. PARVALUX. Price £11.00 + £1.00 P. & P. (£12.96 inc. VAT). N.M.S.

6/9V. D.C. Miniature Geared Motor, precision built, incredibly powerful for size — approx speed @ 6V - 60 rpm 40 ma. approx. speed @ 9V - 80 rpm 50 ma. Size: 27mm dia, 38mm length, 55gr. weight, drive spindle 5 x 3mm dia. Price: £2.50 post paid (£2.70 inc. VAT). N.M.S.

12V. D.C. type S02. Shunt 1/2 hp continuously rated 4000 rpm. Mf. PARVALUX. Price: £10.00 + 75p. P. & P. (£11.61 inc. VAT). N.M.S.

230/240V. a.c. 1 rpm Synchronous geared motor, mf. HAYDON. 230/240V. a.c. 2 rpm Synchronous geared motor, mf. CROUZET. Price above 2 Motors: £2.90 + 30p. P. & P. (£3.46 inc. VAT). N.M.S.

1,400 rpm 115V. a.c. Motor, HP 1/2 continuously rated. Fitted with anti-vibration cradle mounting. Mf. FRACMO. Supplied complete with Transformer for 230/240V. a.c. operation. Price: £10.00 + £1.00 P. & P. (£11.88 inc. VAT). N.M.S.

1,600 rpm. 230V. a.c. reversible Motor, 0.25 a. complete with anti-vibration mounting bracket and capacitor. O/a size: 110 x 90mm. Spindle 3/8 dia. reversing. Mf. GENERAL ELECTRIC. R. & T. Price: £3.00 + 50p. P. & P. (£3.78 inclusive).

ROTARY VACUUM AIR COMPRESSOR & PUMP



Carbon Vane oil-less. 100/115V. A.C. 1/12 h.p. motor 50/60 cycle 2875/3450 rpm. 20" vacuum 1.25 c.f.m. 10 p.s.i. (approx. figures) mft. by Gast Co. Fraction of maker's price. £14.00 p. & p. £1.00 (Total: £16.20 inc. VAT). Suitable Transformer. £3.50 p. & p. 50p. (Total, £4.32 inc. VAT). N.M.S.

BLOWER VACUUM PUMP

English Electric 3 phase AC. motor 220/250V. Or 380/440V. 1.425 c.f.m. 1/2 h.p. continuously rated. Direct coupled to William Allday & Co Alcosa carbon vane blower/vacuum pump 0.9 cfm B.H.G. Price £22 p&p £2 (25.92 inc. VAT & p) N.M.S.

Time Switch

Venner Type ERD Time switch 200/250V a.c. 30 amp contact 2 on/2 off every 24 hrs. at any manually pre-set time. 36 hour Spring Reserve and day omitting device. Built to highest Electrical Board specification. Price £7.75. P. & P. 75p (£9.18).



SANGAMO WESTON TIME SWITCH

Type S251 200/250V. a.c. 2 on/2 off every 24 hours. 20 amps contacts with override switch dia. 4 x 3 price £6.50 P. & P. 50p inc. VAT £7.56. Also available with Solar dial. R. & T.

Yet another outstanding offer.

IMFD 600V Dobilier wire ended capacitors. 10 for £1.50 p&p 50p. (£2.16 inc. VAT & p&p) (Min 10) N.M.S.

230V a.c. FAN ASSEMBLY

Powerful continuously rated a.c. motor complete with 5 blade 6 1/2 in. or 4 blade 5 in. aluminium fan. Price £3.00. P. & P. 65p. (£3.94 inc. VAT & P.).



KEY:
N.M.S. New Manufacturers Supply
R. & T. Reconditioned and Tested

Personal callers only Open Saturdays

9 LITTLE NEWPORT STREET
LONDON WC2H 7JJ
Phone 01-437 0576

SERVICE TRADING CO.
ACCOUNT CUSTOMERS MIN. ORDER £10.00

KITS FOR SYNTHESISERS, SOUND EFFECTS



PHONOSONICS

MAIL ORDER SUPPLIERS OF QUALITY PRINTED CIRCUIT BOARDS, KITS AND COMPONENTS TO A WORLD-WIDE MARKET

P.E. MINISONIC Mk. 2 SYNTHESIZER

A portable mains-operated Miniature Sound Synthesiser, with keyboard circuits. Although having slightly fewer facilities than the large P.E. Synthesiser the functions offered by this design give it great scope and versatility. Consists of 2 log VCOs, VCF, 2 envelope shapers, 2 voltage controlled amps, keyboard hold and control circuits, HF oscillator and detector, ring modulator, noise generator, mixer, power supply.

Set of basic component kits (excl. KBD R's and tuning pots - see list for options available). from £61.00
Set of printed circuit boards £8.99

P.E. SYNTHESIZER (P.E. Feb. 73 to Feb. 74)

The well acclaimed and highly versatile large-scale mains-operated Sound Synthesiser complete with keyboard circuits. Other circuits in our lists may be used with the Synthesiser to good advantage. Details in our lists.

FORMANT SYNTHESIZER (Elektor 1977/78)

Very sophisticated music synthesiser for the advanced constructor who puts performance before price. Details in our lists.

128-NOTE TUNE-PROGRAMMABLE SEQUENCER

(P.E. Nov/Dec 77)

Enables a voltage controlled synthesiser to automatically play pre-programmed tunes of up to 32 pitches and 128 notes long. Programs are keyboard initiated and note length and rhythmic pattern are externally variable. (Please use order codes quoted in brackets.)

Main Circuit (Nov) excl. sw's (KIT 76-1) £18.03
Power Supply (KIT 76-3) £4.72
Trigger Inverter and Alt. Output (KIT 76-2) £1.15
LED Counter (KIT 76-4) £2.10
PCB (as published) for KITS 76-1 & 3 (PCB 76A) £2.61
PCB for KITS 76-2 & 4 (PCB 76B) £2.54

P.E. STRING ENSEMBLE (PE Mar-July 78)

The new keyboard string-instrument synthesiser.

Basic component sets:

Power Supply (KIT 77-1) £8.77
Tone Generator (KIT 77-2) £14.66
Diode Gates (KIT 77-3) £18.81
Chorus Generator (KIT 77-4) £19.08
Voicing System (KIT 77-5) £7.38

Printed Circuit Boards:

Double-sided PCB for Power Supply, Tone Generator & Diode Gates with most of the Matrix wiring as printed tracking (PCB 77L/R) £18.40
PCB for Chorus Generator (PCB 77C) £2.65
PCB for Voicing System (PCB 77D) £2.62

Fuller details of kits & PCBs are in our lists.

P.E. JOANNA PLUS ORGAN VOICING

The basic five octave electronic piano (P.E. May/Sept 75 and Sound Design) has switchable alternative voicings for Honky-Tonk, ordinary piano, and Harpsichord or a mixture of any of these three, together with facilities including fast and slow tremolo, loud and soft pedal switching, and sustain pedal switching. The modification retains all the circuitry associated with the piano but in addition provides an organ-voice envelope facility with 5 switchable pitches, variable attack and sustain, phasing and vibrato.

Set of components (excl switches) for PSU, Frequency generator, Pitch and Note Divider, Envelope Shapers, Voicings, and Control circuitries. (Order as KIT 71-5) £99.25
Set of PCBs (Order as PCB SET 71-6) £29.18

GUITAR EFFECTS PEDAL (P.E. July 75)

Modulates the attack, decay and filter characteristics of an audio signal not only from a guitar but from any audio source, producing 8 different switchable effects that can be further modified by manual controls. Possibly the most interesting of all the low-priced sound effects units in our range. Circuit does not duplicate effects from the Guitar Overdrive Unit.

Component set with special foot operated switches £7.69
Alternative component set with panel switches £5.05
Printed circuit board £11.43

COMPONENTS SETS include all necessary resistors, capacitors, semiconductors, potentiometers and transformers. Hardware such as cases, sockets, knobs, keyboards, etc. are not included but most of these may be bought separately. Fuller details of kits, PCBs and parts are shown in our lists.

CIRCUIT AND LAYOUT DIAGRAMS are supplied free with all PCBs unless "as published".

PHOTOCOPIES of P.E. texts for most of the kits are available—prices in our lists.

ELEKTOR ELECTRONIC PIANO (Elektor Sept 78)

A touch-sensitive, multiple-voicing 5 octave piano using the latest integrated-circuit techniques for the keying and envelope shaping and virtually eliminating "bee-hive" noise hitherto inherent in previous electronic pianos. Details in our lists.

DIGITAL REVERBERATION UNIT (Elektor May 78)

A very advanced unit using sophisticated i.c. techniques instead of mechanical spring-lines. The basic delay range of 24 to 90mS can be extended up to 450mS using the extension unit. Further delays can be obtained using more extensions.

Main component set (KIT 78-1) £45.45
Extension component set (KIT 78-2) £43.36
PCB for KIT 78-1 (PCB 78A) £2.86
PCB for KIT 78-2 (PCB 78B) £1.06

ANALOGUE REVERBERATION UNIT (Elektor Oct 78)

Using i.c.s instead of spring-lines, the main unit has a maximum delay of up to 100mS, and the additional set extends this up to 200mS. May be used in either mono or stereo mode.

Main component set (KIT 83-1) £26.18
Additional Delay Set (KIT 83-2) £18.25
PCB (as published) to hold both above kits (PCB 9873) £4.31

RESONANCE FILTER (Elektor Oct 78)

This filter module has been designed to allow a synthesiser to produce a more realistic simulation of natural musical instruments.

Basic component set (KIT 82-1) £15.10
PCB (as published) (PCB 9951) £3.29

SYNTHESIZER EXTERNAL INPUT INTERFACE

(P.E. Oct 78)

This unit allows external inputs, such as guitars, microphones etc. to be processed by the circuits within a synthesiser.

Basic component set (incl PCB) (KIT 81-1) £2.94

GUITAR MULTIPROCESSOR (P.E. Dec/Feb 78)

An extremely versatile sound processing unit capable of producing, for example, Flanging, Vibrato, Reverb, Fuzz and Tremolo as well as other fascinating sounds. May be used with most electronic instruments. Details in our lists.

RHYTHM GENERATOR KITS

Several available - details in our lists.

GUITAR FREQUENCY DOUBLER (P.E. Aug. 77)

A modified and extended version of the circuit published. Component set and PCB £4.52

GUITAR SUSTAIN (P.E. Oct 77)

Maintains the natural attack whilst extending note duration. Component set, PCB and foot switches £5.13
Component set, PCB and panel switches £3.71

WIND AND RAIN UNIT

A manually controlled unit for producing the above-named sounds. Component set (Incl. PCB) £4.26

GUITAR OVERDRIVE UNIT (P.E. Aug. 76)

Sophisticated, versatile Fuzz unit, including variable and switchable controls affecting the fuzz quality whilst retaining the attack and decay, and also providing filtering. Does not duplicate the effects from the Guitar Effects Pedal and can be used with it and with other electronic instruments.

Component set using dual slider pot £7.58
Component set using dual rotary pot £6.89
Printed circuit board £1.62

FUZZ UNIT

Simple Fuzz unit based upon P.E. "Sound Design" circuit. Component set (incl. PCB) £2.05

TREMOLO UNIT

Based upon P.E. "Sound Design" circuit. Component set (incl. PCB) £2.94

TREBLE BOOST UNIT (P.E. Apr. 76)

Gives a much shriller quality to audio signals fed through it. The depth of boost is manually adjustable. Component set (incl. PCB) £2.51

WAVEFORM CONVERTER

Slightly modified from a circuit published in "Elektor". Converts a saw-tooth waveform into four different waveforms: sine-wave, mark-space saw-tooth, regular triangle form, and squarewave with an externally variable mark-space ratio.

Component set (incl. PCB but excl. sw's) £8.40

VOLTAGE CONTROLLED FILTER (P.E. Dec. 74)

Part of the P.E. Minisonic now released as an independent kit for use with other synthesisers.

Component set (Incl. PCB) (Order as Kit 65-1) £7.17

RING MODULATOR (P.E. Jan. 75)

Part of the P.E. Minisonic now released as an independent kit for use with other synthesisers.

Component set (incl. PCB) (Order as Kit 59-1) £5.50

NOISE GENERATOR (P.E. Jan. 75)

Part of the P.E. Minisonic now released as an independent kit for use with other synthesisers.

Component set (incl. PCB) (Order as Kit 60-1) £3.84

ENVELOPE SHAPER WITHOUT VCA (P.E. Oct. 75)

Provides full manual control over attack, decay, sustain and release functions, and is for use with an existing voltage controlled amplifier.

Component set (incl. PCB) £4.77

ENVELOPE SHAPER WITH VCA (P.E. Apr. 76)

This unit has its own voltage controlled amplifier and has full manual control over attack, decay, sustain and release functions.

Component set (incl. PCB) £6.68

TRANSIENT GENERATOR (P.E. Apr. 77)

An envelope shaper, without VCA, having the usual attack, decay, sustain and release functions, and in addition it also provides a "Repeat Effect" enabling a synthesiser to be programmed to imitate such instruments as a mandolin or banjo.

Component set £4.87
Printed circuit board £1.82

SOPHISTICATED PHASING AND VIBRATO UNIT

A slightly modified version of the circuit published in "Elektor", December 1976, and includes manual and automatic control over the rate of phasing and vibrato.

Component set £17.38
Printed circuit board £2.33

PHASING UNIT (P.E. Sept. 73)

A simple but effective manually controlled unit for introducing the "phasing" sound into live or recorded music.

Component set (incl. PCB) £3.20

PHASING CONTROL UNIT (P.E. Oct. 74)

For use with the above Phasing Unit to automatically control the rate of phasing.

Component set (incl. PCB) £4.74

WAH-WAH UNIT (P.E. Apr. 76)

The Wah-Wah effect produced by this unit can be controlled manually or by the integral automatic controller.

Component set (incl. PCB) £3.63

AUTOWAH UNIT (P.E. Mar. 77)

Automatically produces Wah-pedal and Swell-pedal sounds each time a new note is played.

Component set, PCB, special foot switches £7.67
Component set and PCB, with panel switches £4.83

VOICE OPERATED FADER (P.E. Dec. 73)

For automatically reducing music volume during "talk-over"—particularly useful for Disco work or for home-movie shows.

Component set (incl. PCB) £3.97

10% DISCOUNT VOUCHER (PE 74)

TERMS: Goods in current adverts & lists over £50 goods value (excl P&P & VAT). Correctly costed, C.W.O., U.K. orders only. This voucher must accompany order. Valid until end of month on cover of P.E.

ADD: POST & HANDLING

U.K. orders - Keyboards add £2.00 each plus VAT. Other goods: under £15 add 25p plus VAT, over £15 add 50p plus VAT. Recommended: optional insurance against postal mishaps, add 50p for cover up to £50, £1.00 for £100 cover, etc. pro-rata. N.B. Eire, C.I., B.F.P.O. and other countries are subject to higher export postage rates.

ADD 12% VAT

(or current rate if changed). Must be added to full total of goods, discount, post & handling, on all U.K. orders. Does not apply to Exports.

EXPORT ORDERS ARE WELCOME but to avoid delay we advise you to see our list for postage rates. All payments must be cash-with-order, in Sterling by International Money Order or through an English Bank. To obtain list - Europe send 20p, other countries send 50p.

PHONOSONICS · DEPT PE74 · 22 HIGH STREET · SIDCUP · KENT DA14 6EH

TERMS: C.W.O., MAIL ORDER OR COLLECTION BY APPOINTMENT (TEL 01-302 6184)

AND OTHER PROJECTS

PHOTOGRAPHS In this advertisement show two of our units containing some of the P.E. projects built from our kits and PCBs. The cases were built by ourselves and are not for sale, though a small selection of other cases is available.



LIST—Send stamped addressed envelope with all U.K. requests for free list giving fuller details of PCBs, kits and other components.

OVERSEAS enquiries for list: Europe—send 20p; other countries—send 50p.

KIMBER-ALLEN KEYBOARDS AND CONTACTS

Kimber-Allen Keyboards as required for many published circuits. The manufacturers claim that these are the finest moulded plastic keyboards available. All octaves are C to C, the keys are plastic, spring-loaded, fitted with actuators, and mounted on a robust aluminium frame.

- 3 Octave (37 notes) £25.50
- 4 Octave (49 notes) £32.25
- 5 Octave (61 notes) £39.75

Contact Assemblies (gold-clad wire) for use with the above KBDS (1 for each note):

- Type GJ: Single-pole change-over each 25½p
- Type GA: 1 pair of contacts, normally open each 24p
- Type GB: 2 pairs of contacts, each pair normally open each 28½p
- Type GC: 3 pairs of contacts, each pair normally open each 37½p
- Type GE: 4 pairs of contacts, each pair normally open each 46½p
- Type GH: 5 pairs of contacts, each pair normally open each 58½p
- Type 4PS: 3 pairs of contacts plus single-pole changeover each 57p

Printed Circuit Boards for use with most contacts (thus eliminating much interwiring) are available. Details in our lists.

P.E. TUNING FORK (P.E. Nov. 75)

Produces 84 switch-selected frequency-accurate tones. A LED monitor clearly displays all beat note adjustments. Ideal for tuning acoustic or electronic musical instruments.

- Main component set (incl. PCB) £14.93
- Power supply set (incl. PCB) £6.28

SYNTHESISER TUNING INDICATOR (P.E. July 77)

A simple 4-octave frequency comparator for use with synthesisers and other instruments where the full versatility of the P.E. Tuning Fork is not required.

- Component and PCB (but excl sw.) £7.45

CONSTANT DISPLAY FREQUENCY METER (PE AUG 78)

A 5-digit frequency counter for 1Hz to 99999Hz with a 1Hz sampling rate. Readout does not count visibly or flicker due to display blanking.

- Component set £24.05*
- Printed circuit board £3.03*

*This kit & PCB are at 8% VAT (all others are 12½%)

TAPE NOISE LIMITER

Very effective circuit for reducing the hiss found in most tape recordings. All kits include PCBs

- Standard tolerance set of components £2.96
- Superior tolerance set of components £3.76
- Regulated power supply (will drive 2 sets) £4.69

DYNAMIC RANGE LIMITER (P.E. Apr. 77)

Automatically controls sound output to within a preset level.

- Component set (incl. PCB) £4.58

DISCOSTROBE (P.E. Nov. 76)

4-channel light-show controller giving a choice of sequential, random, or full strobe mode of operation.

- Basic component set £18.19
- Printed circuit board £3.45

BIOLOGICAL AMPLIFIER (P.E. Jan./Feb. 73)

Multi-function circuits that, with the use of other external equipment, can serve as lie-detector, alphaphone, cardiophone etc.

- Pre-Amp Module Components set (incl. PCB) £3.95
- Basic Output Circuits—combined component set with PCBs, for alphaphone, cardiophone, frequency meter and visual feed-back lampdriver circuits. £6.59
- Audio Amplifier Module Type PC7 £7.75

SOUND BENDER (P.E. May 74)

A multi-purpose sound controller, the functions of which include envelope shaper, tremolo, voice-operated fader, automatic fader and frequency-doubler.

Details in lists.

SOPHISTICATED POWER SUPPLIES

A wide range of highly stabilised low noise power supply kits is available—details in our lists.

NEW PCB SERVICE

PCBS FOR ALL NEW P.E. & E.E. PROJECTS FOR WHICH PCB LAYOUTS HAVE BEEN PUBLISHED AND FOR WHICH FULL COPY-RIGHT CLEARANCE IS AVAILABLE.

LIMITED QUANTITIES ONLY FOR AN EXPERIMENTAL PERIOD.

LET US KNOW YOUR NEEDS AND WE WILL ADVISE YOU OF AVAILABILITY AND PRICES.

INTEGRATED CIRCUITS

- 301 8-pin DIL 48p
- 318 8-pin DIL 220p
- 320-15 --- 195p
- 324 14-pin DIL 87p
- 341-15 --- 87p
- 709 8-pin DIL 48p
- 723 T05 87p
- 723 14-pin DIL 51p
- 726 T05 1005p
- 741 8-pin DIL 24p
- 748 8-pin DIL 57p
- 4007 14-pin DIL 174p
- 4011 14-pin DIL 174p
- 4024 14-pin DIL 464p
- 4069 14-pin DIL 18p
- 4136 14-pin DIL 126p
- AM2833 8-pin DIL 380p
- AY10212 16-pin DIL 617p
- AY16721/6 188p
- CA3046 14-pin DIL 71p
- CA3080 8-pin DIL 63p
- CA3084 14-pin DIL 209p
- FX209 16-pin DIL 729p
- LM323 --- 582p
- M252 16-pin DIL 680p
- MC3340 8-pin DIL 150p
- MCM6810 24-pin DIL 670p
- SG3402N 14-pin DIL 262p
- STK025 --- 595p
- TDA1022 16-pin DIL 582p
- XR2207 14-pin DIL 420p
- ZN425E 16-pin DIL 375p

TRANSISTORS

- AC128 32p
- AC178 28p
- BC107 13p
- BC108 13p
- BC109 15p
- BC109C 18p
- BC177 18p
- BC184 11p
- BC187 18p
- BC204 10p
- BC209C 10p
- BC213 13p
- BC219 11p

PHONONICS

PRICES ARE CORRECT AT TIME OF PRESS. E. & O. E. DELIVERY SUBJECT TO AVAILABILITY.

GREENWELD

443c Millbrook Road Southampton
SO1 0HX Tel: (0703) 772501

All prices quoted include VAT. Add 25p UK/BFPO Postage. Most orders despatched on day of receipt. SAE with enquiries please. **MINIMUM ORDER VALUE £1.** Official orders accepted

from schools, etc. (Minimum invoice charge £5). Export/Wholesale enquiries welcome. Wholesale list now available for bona-fide traders. Surplus components always wanted.

OSCILLOSCOPES

We have available from stock the following SCOPEX models: 4D10A — DC-10MHz; 10mV sensitivity; Stab Power supplies; Dual beam; 3% accuracy; Excellent value at £214 inc VAT and Carr.
4S6 — DC-6MHz; 10mV sensitivity. Ideal portable scope. Solid state circuitry. All for £150 inc VAT and Carr.

RELAYS

- W847 Low profile PC mntg 10x33x20mm 6V coil, SPCO 3A contacts. 93p
- W817 11 pin plug in relay, rated 24V ac, but works well on 6V DC. Contacts, 3 pole c/o rated 10A. 95p
- W839 50V ac (24V DC) coil. 11 pin plug in type, 3 pole c/o 10A contacts Only 85p
- W846 Open construction mains relay. 3 sets 10A c/o contacts. £1.20
- W877 675R 12-27V DPCO 23x20x10mm sealed can 88p
- W880 230V ac DPCO 10A contacts, enclosed case £1.30
- W830 200R 6-12V DPCO 23x20x10mm sealed can 88p

Send SAE for our relay list — 84 types listed and illustrated.

AMPLIFIER KIT £1.75

Mono gen. purpose amp with tone and Vol/on-off controls. Utilises sim. circuitry to above amp. Output 2W into 8 ohms. Input matched for crystal cartridge, 4 transistor circuit. Simple to build on PCB provided. Can be either battery or mains operated. (For mains powered version add £2.20 for suitable transformer.) Blue vinyl covered aluminium case to suit (W372) £1.30

STEREO V.U. METER

2 meters 40 x 40mm plus driver board supplied with full data and circuit £3.50

DIN SOCKET OFFER

2 pin switched speaker socket. PC mounting; 5 pin 180° PC mntg or chassis mntg (clip fix). All the same price, any mix: 10 for 70p 25 for £1.60 100 for £5.50.

TMS4030 RAM

4096 bit dynamic RAM with 300ns access time; 470ns cycle time; single low capacitance high level clock ip; Fully TTL compatible; Low power dissipation. Supplied with data £2.75

MISCELLANEOUS IC's

Supplied with data if requested. MC3302 quad comp. 120p; 710 diff comp. (T099) 40p; ZN1034E precision timer £2.25; LM711 Dual diff comp 65p; LM1303 dual stereo pre-amp 75p; MC1469R voltage reg £1.50; UPC1025H audio £3.50; 575C2 audio £2.88; TDA2640 audio £2.92; SN75110 dual line driver 70p; MC8500 CRCC gen POA

EDGE CONNECTORS

Special purchase of these 0.1" pitch double-sided gold-plated connectors enables us to offer them at less than one-third of their original list price! 40 way 90p

HEAT SINK OFFER

Copper T05 sink 17mm dia x 20mm. 10 for 40p; 100 for £3; 1000 for £25

74 SERIES PACK

Selection of boards containing many different 74 series IC's. 20 for £1; 50 for £2.20; 100 for £4.

THE NEW 1978-9 GREENWELD CATALOGUE

FEATURES INCLUDE:

- 50p Discount Vouchers
 - Quantity prices for bulk buyers
 - Bargain List Supplement
 - Reply Paid Envelope
 - Priority Order Form
 - VAT inclusive prices
- PRICE 30p + 15p POST

KITS! KITS!

Send SAE for list of kits from a single Amplifier to a Reaction Tester, etc.

NIXIE TUBES

ITT Type GN77AH. Supplied with data 60p each
7-seg display, wire ended tube NEC type LD8012 ¼" high, with data 65p
7-seg display, (as above) Futaba type DG-10Q1 0.3" char. 70p with data

PUSH BUTTON BANKS

Illustrated list of types from 30p in our Bargain List No 6 — Send SAE.

BC182B OFFER

Special Offer for quantity users 1k .035+VAT; 5k .032+VAT. Price negotiable on 10k. Approx 70k available.

DIODE SCOOP!!!

We have been fortunate to obtain a large quantity of untested, mostly unmarked glass silicon diodes. Testing a sample batch revealed about 70% useable devices — signal diodes, high voltage rectifiers and zeners may all be included. These are being offered at the incredibly low price of £1.25/1000 — or a bag of 2500 for £2.25. Bag of 10,000 £8. Box of 25,000 £17.50. Box of 100,000 £60.

Disc Ceramic Caps = big variety of values and voltages from a few pF to 2.2uF; 3V to 3kV. 200 for £1; 1000 £4.

PC ETCHING KIT MK III

Now contains 200 sq. ins. copper clad board, 1lb. Ferric Chloride, D.A.L.C. etch-resist pen, abrasive cleaner, two miniature drill bits, etching dish and instructions. £4.25

BUY A COMPLETE RANGE OF COMPONENTS AND THESE PACKS WILL HELP YOU

- ★ **SAVE ON TIME**—No delays in waiting for parts to come or shops to open!
- ★ **SAVE ON MONEY**—Bulk buying means lowest prices—just compare with others!
- ★ **HAVE THE RIGHT PART**—No guesswork or substitution necessary!

ALL PACKS CONTAIN FULL SPEC. BRAND NEW, MARKED DEVICES—SENT BY RETURN OF POST. VAT INCLUSIVE PRICES.

- K001 50V ceramic plate capacitors, 5%, 10 of each value 22pF to 1000pF. Total 210, £3.60
- K002 Extended range, 22pF to 0.1uF. 330 values £5.40
- K003 Polyester capacitors, 10 each of these values: 0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1, 0.15, 0.22, 0.33, 0.47uF. 110 altogether for £4.95
- K004 Mylar capacitors, min 100V type. 10 each all values from 1000pF to 10,000pF. Total 130 for £3.75
- K005 Polystyrene capacitors, 10 each value from 10pF to 10,000pF. E12 series 5% 160V. Total 370 for £12.30
- K006 Tantulum bead capacitors, 10 each of the following: 0.1, 0.15, 0.22, 0.33, 0.47, 0.68, 1, 2, 3, 4.7, 6.8, all 35V; 10/25 15/16 22/16 33/10 47/6 100/3. Total 170 tants for £14.20
- K007 Electrolytic capacitors 25V working, small physical size. 10 each of these popular values: 1, 2, 2.2, 4.7, 10, 22, 47, 100uF. Total 70 for £3.50
- K008 Extended range, as above, also including 220, 470 and 1000uF. Total 100 for £5.90
- K021 Miniature carbon film 5% resistors, CR25 or similar. 10 of each value from 10R to 1M; E12 series. Total 610 resistors, £8.00
- K022 Extended range, total 850 resistors from 1R to 10M; £8.30
- K041 Zener diodes, 400mW 5% 82Y88, etc. 10 of each value from 2.7V to 36V. E24 series. Total 280 for £15.30.
- K042 As above but 5 of each value £8.70

TRANSFORMERS

All mains primary: 12-0-12V 50mA 85p; 100mA 95p; 1A £2.50, 6-0-6V 100mA 85p; 1A £2.40, 9-0-9V 75mA 85p; 1A £2.70, Multi-tapped type 0-12-15-20-24-30V, 1A £3.95; 2A £5.35; 3A £6.90, 20V 2A £3.90, 25V 1A £2.25; 12V 8A £4; 24V 5A £7.50; 0-22-34-41V 4A £7.50; 20V @ 300mA twice £2.50;

SEMICONDUCTORS POTS & IRONS

SOCKETS

1611 8 pin DIL	£0-11
1612 14 pin DIL	£0-12
1613 16 pin DIL	£0-13
1614 24 pin DIL	£0-25
1615 28 pin DIL	£0-30
1616 TO18 Transistor	£0-12
1617 TU3 Transistor	£0-35
16117 TO5 Transistor	£0-12

VOLTAGE REGULATORS

Positive	
MVR7805 v.a. 7805 TO220	£0-70
MVR7812 v.a. 7812 TO220	£0-70
MVR7815 v.a. 7815 TO220	£0-70
MVR7818 v.a. 7818 TO220	£0-70
MVR7824 v.a. 7824 TO220	£0-70
Negative	
MVR7905 v.a. 7905 TO220	£0-80
MVR7912 v.a. 7912 TO220	£0-80
MVR7915 v.a. 7915 TO220	£0-80
MVR7918 v.a. 7918 TO220	£0-80
MVR7924 v.a. 7924 TO220	£0-80
v.a. 723C TO99	£0-45
72723 14 pin DN	£0-45
LM309K TO3	£1-50

ZENER DIODES

400mw (Bz88) DO7 Glass encapsulated range of voltages available. 1-3v, 2-2v, 2-7v, 3-3v, 3-9v, 4-3v, 4-7v, 5-1v, 5-6v, 6-2v, 6-8v, 7-5v, 8-2v, 9-1v, 10v, 11v, 12v, 13v, 15v, 16v, 18v, 20v, 22v, 24v, 27v, 30v, 33v, 39v.

No. Z4 8p ea.
1w-1.5w Plastic and metal encapsulated range of voltages available. 1-3v, 2-2v, 2-7v, 3-3v, 3-9v, 4-3v, 4-7v, 5-1v, 5-6v, 6-2v, 6-8v, 7-5v, 8-2v, 9-1v, 10v, 11v, 12v, 13v, 15v, 16v, 18v, 20v, 22v, 24v, 27v, 30v, 33v, 39v, 47v, 51v, 68v, 72v, 75v, 82v, 91v, 100v.

No. Z13 15p ea.
10w Metal stud type SOT0 case. Range of voltages available. 1-3v, 2-2v, 2-7v, 3-3v, 3-9v, 4-3v, 4-7v, 5-1v, 5-6v, 6-2v, 6-8v, 7-5v, 8-2v, 9-1v, 10v, 11v, 12v, 13v, 15v, 16v, 18v, 20v, 22v, 24v, 27v, 30v, 33v, 39v, 47v, 51v, 68v, 72v, 75v, 82v, 91v, 100v.

No. Z10 35p ea.

SILICON RECTIFIERS

200mA	
IS920 50v	£0-06
IS921 100v	£0-07
IS922 150v	£0-08
IS923 200v	£0-09
IS924 300v	£0-10
1 Amp	
IN4001 50v	£0-04
IN4002 100v	£0-05
IN4003 200v	£0-06
IN4004 400v	£0-07
IN4005 600v	£0-08
IN4006 800v	£0-09
IN4007 1000v	£0-10
1.5 Amp	
IS015 50v	£0-09
IS020 100v	£0-10
IS021 200v	£0-11
IS023 400v	£0-13
IS025 600v	£0-14
IS027 800v	£0-16
IS029 1000v	£0-20
IS031 1200v	£0-25

3 Amp	
IN5400 50v	£0-14
IN5401 100v	£0-15
IN5402 200v	£0-16
IN5404 400v	£0-17
IN5405 600v	£0-21
IN5407 800v	£0-25
IN5408 1000v	£0-30

10 Amp	
IS10/50 50v	£0-19
IS10/100 100v	£0-21
IS10/200 200v	£0-23
IS10/400 400v	£0-35
IS10/600 600v	£0-42
IS10/800 800v	£0-51
IS10/1000 1000v	£0-60
IS10/1200 1200v	£0-69

30 Amp	
IS30/50 50v	£0-56
IS30/100 100v	£0-69
IS30/200 200v	£0-93
IS30/400 400v	£1-25
IS30/600 600v	£1-76
IS30/800 800v	£1-94
IS30/1000 1000v	£2-31
IS30/1200 1200v	£2-88

60 Amp	
IS70/50 50v	£0-75
IS70/100 100v	£0-84
IS70/200 200v	£1-20
IS70/400 400v	£2-15
IS70/600 600v	£2-25
IS70/800 800v	£2-50
IS70 1000 1000v	£3-00
BYX38/300 6A 300v	£0-45
BYX38/600 6A 600v	£0-60
BYX38/300 Rev 6A 300v	£0-45
BYX38/600 Rev 6A 600v	£0-60

POTENTIOMETERS

CARBON POTS (Linear Track)

Single gang with wire end terminations, 6mm x 50mm plastic shaft 10mm bushes supplied with shake proof washer & nut. Tolerance $\pm 20\%$ of resistance.

1831 1k ohms £0-26*	1836 47kohms £0-26*
1832 2k2ohms £0-26*	1837 100kohms £0-26*
1833 4k7ohms £0-26*	1838 220kohms £0-26*
1834 10kohms £0-26*	1839 470kohms £0-26*
1835 22kohms £0-26*	1840 1Meg £0-26*
1841 2M2 £0-26*	

CARBON POTS (Log Track)

1842 4k7ohms £0-26*	1846 100kohms £0-26*
1843 10kohms £0-26*	1847 220kohms £0-26*
1844 22kohms £0-26*	1848 470kohms £0-26*
1845 47kohms £0-26*	1849 1Meg £0-26*
1850 2M2 £0-26*	

DUAL CARBON POTS (Lin Track)

These high quality dual gang pots are fitted with wire end terminations and 6mm x 50mm plastic shaft 10mm, bush and supplied with shake proof washer & nut track tolerance $\pm 20\%$ but matched to within 2db of each other. VC3

1851 4k7 £0-86*	1856 100kohms £0-86*
1852 10kohms £0-86*	1856 220kohms £0-86*
1853 22kohms £0-86*	1857 470kohms £0-86*
1854 100kohms £0-86*	1858 1Meg £0-86*
1859 2M2 £0-86*	

DUAL CARBON POTS (Log Law)

1860 4k7ohms £0-86*	1864 100kohms £0-86*
1861 10kohms £0-86*	1865 220kohms £0-86*
1862 22kohms £0-86*	1866 470kohms £0-86*
1863 47kohms £0-86*	1867 1Meg £0-86*
1868 2M2 £0-86*	

SINGLE GANG SWITCHED (Lin Law)

These potentiometers are fitted with double pole on-off switches. The switch is incorporated within the rotary action of the pot. Specification of pot is as VC1. Switch rating 1-5amps at 250v AC.

1870 4k7ohms £0-65*	1874 100kohms £0-65*
1871 10kohms £0-65*	1875 220kohms £0-65*
1872 22kohms £0-65*	1876 470kohms £0-65*
1873 47kohms £0-65*	1877 1Meg £0-65*
1878 2M2 £0-65*	

SWITCHED POT (Log Track)


Specification as VC2 but track having (log) law.

1879 4k7ohms £0-65*	1883 100kohms £0-65*
1880 10kohms £0-65*	1884 220kohms £0-65*
1881 22kohms £0-65*	1885 470kohms £0-65*
1882 47kohms £0-65*	1886 1Meg £0-65*
1887 2M2 £0-65*	

ANTEX IRONS

O/No. 1943. 15 watt high quality soldering iron totally enclosed element in a ceramic shaft fitted with 3/32" bit. £3-80
O/No. 1947. Replacement element for 1943 iron. £1-90
O/No. 1944. Iron coated bit 3/32" for 1943 iron. £0-46
O/No. 1945. Iron coated bit 1/8" for 1943 iron. £0-46
O/No. 1946. Iron coated bit 3/16" for 1943 iron. £0-46
O/No. 1948. General purpose 18 watt iron fitted with iron coated bit. £3-60
O/No. 1952. Replacement element for 1948 iron. £1-90
O/No. 1949. Iron coated bit 3/32" for 1948 iron. £0-46
O/No. 1950. Iron coated bit 1/8" for 1948 iron. £0-46
O/No. 1951. Iron coated bit 3/16" for 1948 iron. £0-46

PRINTED CIRCUIT BOARD TRANSFERS

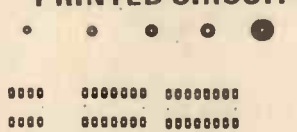

Draw your own boards with the new BI-PAK etch-resist transfers. Lay the symbols on the board, rub over with a soft pencil. The transfer will adhere to the board. Then complete the circuit with your BI-PAK

DUAL GANG LOG-ANTI-LOG POT

1888 Track specification as dual gang pots VC3 but tracks mounted to log-anti-log action 100kohms £0-75*

SPECIAL VOLUME CONTROLS

A miniature 16mm type replacement volume control incorporating single pole on-off switch. Resistance value 5kohms. Tolerance $\pm 20\%$ 1/watt rating. 1889 £0-27* VC8

MINIATURE ROTARY VOL

5kohms log law with on/off switch. 20mm grooved spindle. Tag connections 17mm dia. Supplied with fixing nut. Used mainly for replacement. 1890 £0-54* VC9

WIRE WOUND POTS

A range of wire wound single gang pots with linear tracks of 1 watt rating, fitted with 10mm bush and supplied with shake-proof washer and nut.

1891 10ohms £0-80	1895 220ohms £0-80
1892 22ohms £0-80	1896 470ohms £0-80
1893 47ohms £0-80	1897 1kohms £0-80
1894 2kohms £0-80	1898 2kohms £0-80
1899 4k7ohms £0-80	

PRE-SET POTS

Miniature type for transistor circuits. The wiper of the preset is provided with a slot for screw driver adjustment. The tags of the preset will fit printed wiring boards with a pitch of 2.54mm. All tracks are linear law.

1801 10ohms £0-09*	1808 22kohms £0-09*
1802 22ohms £0-09*	1809 47kohms £0-09*
1803 47ohms £0-09*	1810 100kohms £0-09*
1804 1kohms £0-09*	1811 220kohms £0-09*
1805 2kohms £0-09*	1812 470kohms £0-09*
1806 4k7ohms £0-09*	1813 1Mohms £0-09*
1807 10kohms £0-09*	1814 2Mohms £0-09*
1815 4M7ohms £0-09*	

PRE-SET POTS

Miniature type for transistor circuits. Wiper adjustment is made by a screw driver slot. Designed to fit 2.54mm pitch board. All tracks are linear law.

1816 10ohms £0-09*	1823 22kohms £0-09*
1817 22ohms £0-09*	1824 47kohms £0-09*
1818 47ohms £0-09*	1825 100kohms £0-09*
1819 1kohms £0-09*	1826 220kohms £0-09*
1820 2kohms £0-09*	1827 470kohms £0-09*
1821 4k7ohms £0-09*	1828 1Megohms £0-09*
1822 10kohms £0-09*	1829 2Mohms £0-09*
1830 4M7ohms £0-09*	

OPTOELECTRONICS

NEW INCREASED RANGE - ALL 1ST QUALITY LED'S (diffused)

O/no.	Type	Size	Colour	Price
1501	ARL209(TIL209)	.3mm (1.25)	RED	£0-10
1502	MIL323(TIL211)	.3mm (1.25)	GREEN	£0-15
1503	MIL331(OPL212A)	.3mm (1.25)	YELLOW	£0-15
1504	ARL490(FLV117)	.5mm (2)	RED	£0-10
1505	MIL525(TIL222)	.5mm (2)	GREEN	£0-16
1506	MIL535(MV535)	.5mm (2)	YELLOW	£0-16
1509	FLV111	.5mm (2)	CLEAR	£0-11

SUPER 'Hi-Brite' Type

1521	MIL32	.3mm (1.25)	RED	£0-10
1522	MIL52	.5mm (2)	RED	£0-10
1514	ORP12	Light dependent resistor		£0-55
1520	OCPT1	Photo transistor		£0-35

LEO CLIPS

1508/125	pack of 5	125 clips		£0-18
1508/2	pack of 5	2 clips		£0-16
ALL @ 8% V.A.T.				

DISPLAYS

DL303 7 segment O.P. left (.30" height)	Common Anode	O/NO: 1523	£0-70	
RED Single Digit				
DL707 7 segment O.P. left (.0.3" height)	Common Anode	O/NO: 1510	£0-95	
RED Single Digit				
DL527 7 segment D.P. left (.50" height)	Common Anode	O/NO: 1524	£1-70	
RED Two-Digit Reflector				
DL727 7 segment D.P. right (.510" height)	Common Anode	O/NO: 1521	£2-20	
RED Two-Digit Light Pipe				
DL747 7 segment D.P. Left (.630" height)	Common Anode	O/NO: 1511	£1-70	
RED Single-Digit Light Pipe				
ALL @ 8% V.A.T.				

OPTO-ISOLATORS

Isolation Breakdown - Voltage 1500 - continuous fwd current 100mA			
CIL74 Single-Channel 6 pin DIP standard type - optically coupled pair with infra-red LED Emitter and NPN Silicon Photo Transistor.	O/NO: 1497	£0-50	
CILD74 Multi-Channel 8 pin DIP Two Isolated Channels.	O/NO: 1498	£1-00	
CILQ74 Multi-Channel 16 pin DIP Four Isolated Channels.	O/NO: 1499	£2-20	
ALL @ 8% V.A.T.			

2nd GRADE LED PACK

A pack of 10 standard sizes and colours which fail to perform to their very rigid specification, but which are ideal for amateurs who do not require the full spec. O/NO 107 £1-50

THYRISTORS

600ma	TO 18 Case	7 Amp	TO 48 Case
Volts No.	Price	Volts No.	Price
10 THY600/10	£0-15	50 THY7A/50	£0-48
20 THY600/20	£0-16	100 THY7A/100	£0-51
30 THY600/30	£0-20	200 THY7A/200	£0-57
50 THY600/50	£0-22	400 THY7A/400	£0-62
100 THY600/100	£0-25	600 THY7A/600	£0-78
200 THY600/200	£0-38	800 THY7A/800	£0-92
400 THY600/400	£0-44		

1 amp	TO 5 Case	10 Amp	TO 48 Case
Volts No.	Price	Volts No.	Price
50 THY1A/50	£0-28	50 THY10A/50	£0-51
100 THY1A/100	£0-28	100 THY10A/100	£0-57
200 THY1A/200	£0-32	200 THY10A/200	£0-52
400 THY1A/400	£0-38	400 THY10A/400	£0-71
600 THY1A/600	£0-45	600 THY10A/600	£0-99
800 THY1A/800	£0-58	800 THY10A/800	£1-22

3 amp	TO 66 Case	16 Amp	TO 48 Case
Volts No.	Price	Volts No.	Price
50 THY3A/50	£0-28	50 THY16A/50	£0-54
100 THY3A/100	£0-30	100 THY16A/100	£0-58
200 THY3A/200	£0-33	200 THY16A/200	£0-62
400 THY3A/400	£0-42	400 THY16A/400	£0-90
600 THY3A/600	£0-50	600 THY16A/600	£1-39
800 THY3A/800	£0-65		

5 Amp	TO 66 Case	30 Amp	TO 94 Case
Volts No.	Price	Volts No.	Price
50 THY5A/50	£0-36	50 THY30A/50	£1-18
100 THY5A/100	£0-45	100 THY30A/100	£1-43
200 THY5A/200	£0-50	200 THY30A/200	£1-93
400 THY5A/400	£0-57	400 THY30A/400	£1-79
600 THY5A/600	£0-69	600 THY30A/600	£1-50
800 THY5A/800	£0-81		

No.	Price
BT101/500R	£0-80
BT102/500R	£0-80
BT106	£1-25
BT107	£0-93
BT108	£0-98
2N3228	£0-70
2N3535	£0-77
BTX30/50L	£0-33
BT	

BOOKS AND COMPONENTS

BOOKS BY BABANI

BP6	Equipment & Mechanists Ref. Tables	40p
BP14	2nd Book Transistor Equivs & Subs	£1.10
BP22	79 Electronic Novelty Circuits	75p
BP24	52 Projects Using IC741 (for Equiv)	75p
BP26	Radio Antenna Book Long Distance Reception and Transmission	85p
BP27	Giant Chart of Radio Electronic Semiconductor and Logic Symbols	60p
BP32	Build Metal and Treasure Locators	85p
BP34	Practical Repair/Renovation C/TV	95p
BP35	Handbook of IC Audio Preamplifier and Power Amplifier Construction	95p
BP36	50 Diets use Germ/Sil/Zener Diodes	75p
BP37	50 Projs Using Relays/SCR/Triacs	£1.10
BP39	50 Field Effect Trans Projects	£1.25
BP40	Digital IC Equivs and Pin Connection	£2.50
BP41	Linear IC Equivs and Pin Connection	£2.75
BP42	50 Simple LED Circuits	75p
BP43	How to make Walkie-Talkies	£1.25
BP44	IC 555 Timer Projects	£1.45
RF45	Projects on Opto-electronics	£1.25
BP46	Radio Circuits Using IC's	£1.35
BP47	Mobile Discoteque Handbook	£1.35
BP48	Electronics Projects for Beginners	£1.38
BP49	Popular Electronic Projects	£1.45
BP50	IC LM3900 Projects	£1.35
BP55	Radio Stations Guide	£1.45
BP160	Coil Design and Construction Manual	85p
BP202	Handbook of Integrated Circuits Equivalents and Substitutes	75p
BP205	1st Book Hi-Fi Speaker Enclosures	75p
BP213	Circuits for Model Railways	85p
BP215	Shortwave Circuits and Gear for Experimenters and Radio Hams	85p
BP216	Electronic Cardsets and Games	85p
BP217	Solid State Power Supply Handbook	85p
BP221	28 Tested Transistor Projects	95p
BP222	Short wave Receivers for Beginners	95p
BP223	50 Projects using IC CA3130	95p
BP224	50 CMOS IC Projects	95p
BP225	A Practical Intro to Digital IC's	95p
BP226	Build Advanced Short-wave Receivers	£1.20
BP227	Beginners Guide to Building Electronic Projects	£1.25

NEWNES BOOKS — NEW V.A.T. Zero Rated

ORDER NO.	DESCRIPTION	PRICE
216	QUESTIONS & ANSWERS: Transistors 3rd Ed.	£1.00
217	Integrated Circuits	£1.00
218	Radio and Television	£1.25
219	Electronics	£1.15
220	Colour TV 2nd Ed.	£1.15
221	Hi Fi	£1.15
222	20 Solid State Proj. for Car	£1.95
223	20 Solid State Proj. for Home	£1.95
224	110 Int. Circ. Proj. for Home	£2.95
225	110 Thyristor Projects	£2.50
226	Operational Amp. Proj. for Home	£2.50
227	110 Practical IC Proj. for Home	£2.75
228	Electricity	£1.15
229	Beginners Guide to Electronics	£2.25
230	Beginners Guide to Television	£2.25
231	Beginners Guide to Transistors	£2.25
232	Beginners Guide to Electric Wiring	£2.25
233	Beginners Guide to Radio	£2.75
234	Guide to Colour TV	£2.25
235	Electronic Diagrams	£1.80
236	Electronic Components	£1.80
237	Printed Circuit Assembly	£1.80
238	Transistor Pocket Book	£3.90
239	50 Semiconductor Circuits	£1.80
240	Semiconductor Handbook Part 1	£5.25
241	Semiconductor Handbook Part 2	£4.28
242	Electronics Pocket Book	£3.90
243	Radio Value & Semiconductor Data	£2.40
244	Beginners Guide to Integrated Circuits	£2.75
249	HI PAK TTL Data Book	£0.50
	HI PAK CMOS Data Book	£0.45

P.C.B. BOARDS

C26	4 pieces 8" x 3 1/4" (approx.) Single-sided fibreglass	80p
C27	3 pieces 7" x 3 1/4" (approx.) Double-sided fibreglass	60p

SWITCHES

Description	No.	Price
DPDT miniature slide	1973	£0.14*
DPDT standard slide	1974	£0.15*
Toggle switch SPST 1 amp 250V a.c.	1975	£0.33*
Toggle switch DPDT 1 amp 250V a.c.	1976	£0.42*
Rotary on-off mains switch	1977	£0.50*
Push switch - Push to make	1978	£0.14*
Push switch - Push to break	1979	£0.18*

ROCKER SWITCH	Colour	No.	Price
A range of rocker switches SPST - moulded in high insulation. Material available in a choice of colours ideal for small appliances	RED	1980	£0.30*
	BLACK	1981	£0.30*
	WHITE	1982	£0.30*
	BLUE	1983	£0.30*
	YELLOW	1984	£0.30*
	LUMINOUS	1985	£0.30*

Description	No.	Price
Miniature SPST toggle, 2 amp 250V a.c.	1958	£0.70*
Miniature SPST toggle, 2 amp 250V a.c.	1959	£0.75*
Miniature DPDT toggle, 2 amp 250V a.c.	1960	£0.80*
Miniature DPDT toggle, centre off, 2 amp 250V a.c.	1961	£0.95*
Push button SPST, 2 amp 250V a.c.	1962	£0.90*
Push button SPST, 2 amp 250V a.c.	1963	£0.95*
Push button DPDT, 2 amp 250V a.c.	1964	£1.20*

MIDGET WAFER SWITCHES	Description	Order No.	Price
Single-bank wafer type - suitable for switching at 250V a.c. 100mA or 150V d.c. in non-reactive loads make-before-break contacts. These switches have a spindle 0.25in dia. and 30° indexing.	1 pole 12 way	1985	£0.48*
	2 pole 6 way	1966	£0.48*
	3 pole 4 way	1967	£0.48*
	4 pole 3 way	1968	£0.48*

MICRO SWITCHES	Description	Order No.	Price
Plastic button gives simple 1 pole change over action	Rating 10 amp 250V a.c.	1970	£0.25

FUSE HOLDERS AND FUSES

Description	Order No.	Price
20mm x 5mm chassis mounting	506	£0.16*
1 1/2" x 1/2" chassis mounting	507	£0.12*
1 1/2" car inline type	508	£0.16*
Panel mounting 20mm	509	£0.20*
Panel mounting 1 1/2"	510	£0.32

QUICK BLOW 20mm	Type	No.	Type	No.	Type	No.
	150mA	611	6p	1A	615	5p
	250mA	612	5p	1.5A	616	8p
	550mA	613	5p	2A	617	5p
	800mA	614	7p	2.5A	618	6p

ANTI-SURGE 20mm	Type	No.	Type	No.	Type	No.
	100mA	622	1A	625	2.5A	628
	250mA	623	2A	626	3.15A	629
	500mA	624	1.6A	627	5A	630
			All 7p each			

QUICK BLOW 1 1/2"	Type	No.	Type	No.	Type	No.
	250mA	631	500mA	632	800mA	634
	1A	635	2.5A	638	4A	641
	2A	637	3A	639	5A	642
			All 6p each			

NUTS AND BOLTS

8A BOLTS - packs of 8A threaded cadmium plated screws slotted cheese head. Supplied in multiples of 50.

Type	No.	Price	Type	No.	Price
1in OBA	839	£1.20	1in 4BA	846	£0.32
1in OBA	840	£0.75	1in 4BA	847	£0.25
1in 2BA	842	£0.65	1in 6BA	848	£0.40
1in 2BA	843	£0.45	1in 6BA	849	£0.21
1in 2BA	844	£0.52	1in 6BA	850	£0.25
1in 4BA	845	£0.44			

8A NUTS - packs of cadmium plated full nuts in multiples of 50.

Type	No.	Price	Type	No.	Price
OBA	855	£0.72	4BA	857	£0.30
2BA	856	£0.48	6BA	858	£0.24

8A WASHERS - flat cadmium plated plain stamped washers supplied in multiples of 50.

Type	No.	Price	Type	No.	Price
OBA	859	£0.14	4BA	861	£0.12
2BA	860	£0.12	6BA	862	£0.12

SOLDER TAGS - hot tinned supplied in multiples of 50.

Type	No.	Price	Type	No.	Price
OBA	851	£0.40	4BA	853	£0.22
2BA	852	£0.28	6BA	854	£0.22

TRANSFORMERS

MINIATURE MAINS Primary 240V			Price
No.	Secondary		
2021	6V-0-6V	100mA	90p*
2022	9V-0-9V	100mA	90p*
2023	12V-0-12V	100mA	£1.12

MINIATURE MAINS Primary 240V with two independent secondary windings			Price
No.	Type		
2024	M1280-0-6V, 0-6V RMS		£1.60*
2025	M1150-0-12V, 0-12V RMS		£1.60*

1 AMP MAINS Primary 240V			Price
No.	Secondary		
2026	6V-0-6V 1 amp		£2.50*
2027	9V-0-9V 1 amp		£2.00*
2028	12V-0-12V 1 amp		£2.60*
2029	15V-0-15V 1 amp		£2.75*
2030	30V-0-30V 1 amp		£3.45*

STANDARD MAINS Primary 240V Multi-tapped secondary mains transformers available in 1 amp, 1 amp and 2 amp current rating Secondary taps are 0-19-25-33-40-50V.

Voltages available by use of taps:			Price
4, 7, 8, 10, 14, 15, 17, 19, 25, 31, 33, 40, 25-0-25V.	No.	Rating	
	2031	1 amp	£3.40*
	2032	1 amp	£4.40*
	2033	2 amp	£5.45*

AUDIO LEADS

107	FM Indoor Ribbon Aerial	£0.60*
113	3.5mm Jack plug to 3.5mm jack plug. Length 1.5m	£0.75*
114	5 pin DIN plug to 3.5mm Jack connected to pins 3&5. Length 1.5m	£0.85*
115	5 pin DIN plug to 3.5mm Jack connected to pins 1&4. Length 1.5m	£0.85*
116	Car aerial extension. Screened insulated lead. Fitted plug & skt.	£1.25*
117	AC mains connecting lead for cassette recorders & radios. 2 metres	£0.68*
118	5 pin DIN phono plug to stereo headphone jack socket	£1.06*
119	2+2 pin DIN plugs to stereo jack socket with attenuation network for stereo headphones. Length 0.2m	£0.90*
120	Car stereo connector. Variable geometry plug to fit most car cassette. 8 track cartridge & combination units. Supplied with inline fused power lead and instructions.	£0.60*
123	6.6m Coiled Guitar Lead Mono Jack Plug to Mono Jack Plug BLACK	£1.80*
124	3 pin DIN plug to 3 pin DIN plug. Length 1.5m	£0.75*
125	5 pin DIN plug to 5 pin DIN plug. Length 1.5m	£0.75*
126	5 pin DIN plug to Tinned open end. Length 1.5m	£0.75*
127	5 pin Din plug to 4 Phono Plugs.	£1.30*
128	All colour coded. Length 1.5m	£0.80*
129	5 pin DIN plug to 5 pin DIN socket. Length 1.5m	£1.05*
130	2 pin DIN plug to 2 pin DIN inline socket. Length 5m	£0.88*
131	5 pin DIN plug to 3 pin DIN plug. 1 & 4 and 3&5. Length 1.5m	£0.83*
132	2 pin DIN plug to 2 pin DIN socket. Length 10m	£0.98*
133	5 pin DIN plug to 2 phono plugs. Connected pins 3&5. Length 1.5m	£0.75*
134	5 pin DIN plug to 2 phono sockets. Connected pins 3&5. Length 23cm	£0.68*
135	5 pin DIN socket to 2 phono plugs. Connected pins 3&5. Length 23cm	£0.68*
136	Coiled stereo headphone extension lead. Black. Length 6m	£1.75*
178	AC mains lead for calculators etc.	£0.45*

CASES AND BOXES

INSTRUMENT CASES. In two sections vinyl covered top and sides, aluminium bottom, front and back.

No.	Length	Width	Height	Price
156	8 1/2"	5 1/2"	1 1/2"	£1.25
156	11"	6"	3"	£2.12
157	6"	4 1/2"	1 1/2"	£1.30
158	9"	5 1/2"	2 1/2"	£1.78

ALUMINIUM BOXES. Made from bright ali. folded construction each box complete with half inch deep lid and screws.

No.	Length	Width	Height	Price
159	5 1/2"	2 1/2"	1 1/2"	62p
160	4"	4"	1 1/2"	62p
161	4"	2 1/2"	1 1/2"	62p
162	5 1/2"	4"	1 1/2"	70p
163	4"	2 1/2"	2"	64p
164	3"	2"	2 1/2"	44p
165	7"	5"	2 1/2"	£1.04
166	8"	6"	3"	£1.32
167	6"	4"	2"	86p

V.A.T. Add 12 1/2% to prices marked* 8% to those unmarked. Items marked † are zero rated.

P.&P. 35p unless otherwise shown. Giro Acc No. 338-7006

BI-PAK

DEPT. PE6, P.O. Box 6, Ware, Herts
COMPONENTS SHOP: 18 BALDOCK STREET, WARE, HERTS.

Kontite remote control switch

—Simple to install
even simpler to use



The Receiver: contains input and output cables which are connected to the appliance to be controlled.

The Transmitter:

is light and cordless and housing the battery. Simply, point the transmitter at the receiver to turn on or off



Now available in the U.K. the 'Kontite' Remote Control unit switches electrical appliances and equipment on or off safely from distances of up to 35 feet.

Televisions, radios, hi-fi equipment, lighting, model trains etc. electric fans, electric fires (up to 2kw) and many other appliances are within its scope, providing that they have a power supply of 240/250 AC single phase, 50/60 Hz and a maximum 10 amp rating and also that the relevant safety regulations are applied.

The unit is ideal for use in the home, office, factory and hospital. Particularly useful as an aid to the disabled and invalid—wherever an electrical appliance is difficult to reach in the normal manner.

The Kontite Remote Control Switch available now through Electrical Component Retailers.



If you have difficulty in locating a stockist please contact:

Kay & Co (Engineers) Ltd.

Acresfield House, 15 Exchange Street, Bolton, Lancashire.
Telephone: Bolton 21041 Telex: 63186

ALCON

BRING YOU THE NEW CHINAGLIA



MINOR POCKET MULTIMETER

THE
PROFESSIONAL
SOLUTION
TO
GENERAL
MEASUREMENT
PROBLEMS

£32.50 inc. VAT.

The best instrument for the workshop, school, toolbox, T.V. shop and anywhere accurate information is needed quickly and simply.

IT OFFERS:

- ★ Single-knob range selection
- ★ 110° Full-view mirror scale and fine line pointer
- ★ Clear unambiguous scales
- ★ A well-damped cylindrical magnet movement with resilient bearings
- ★ 31 ranges providing coverage from 150mV to 1.5kV d.c.; 7.5V to 1.5kV a.c.; 50µA to 2.5A d.c.; 25mA to 12.5A a.c.; 10kΩ and 10MΩ resistance and six signal level ranges.
- ★ Accuracy ±2.5% d.c., ±3% a.c. and 2% resistance.

For details of this and other exciting Alcon Instruments please write or phone—

ALCON Instruments Ltd.

19 MULBERRY WALK. LONDON SW3 6DZ TEL: 01-352 1897

PE SUSTAIN UNIT

(P.E. OCTOBER 1977)



BUILD A SUSTAIN UNIT EQUAL TO THE BEST COMMERCIAL MODELS.

COMPLETE KIT — £7.95*

ALL HIGH QUALITY COMPONENTS AS SPECIFIED.

DESIGNER APPROVED.

FERRANTI Semiconductors
BUY FROM THE SPECIALISTS!

We can supply any Ferranti semiconductor device at the lowest prices. Send S.A.E. for our data sheet & price list.

ZNA116E	£3.75*	ZNA134J	£21.00*	BC415P	16p	ZTX109	12p
ZN1040E	£7.50*	ZN425E	£3.50*	ZTX107	11p	ZTX213	11p
ZN1034E	£1.65*	ZN424E	£1.20	ZTX108	10p	ZTX384W	24p

TO CLEAR: P.C.B.'s for ZNA116 D.V.M. £1.00* the pair, while stocks last.

ORION Complete set of semiconductors £9.75
Glass fibre PCB, printed with component locations £3.50
amplifier

PE PHASER UNIT

Give your guitar lift-off with this superb phaser unit. Performance equal to the best commercial models. Uses latest FET operational amplifiers for low noise and low battery drain.

COMPLETE KIT OF TOP QUALITY PARTS, AS SPECIFIED..... £15.95 + 8% VAT

Pack 1. Resistors, capacitors and preset pot..... £3.75 + 8% VAT

Pack 2. All semiconductors and I.C.'s..... £6.00 + 8% VAT

Pack 3. Pots, Footswitch, Jacks & glassfibre p.c.b..... £4.25 + 8% VAT

Pack 4. Case and feet..... £2.00 + 8% VAT

Individual parts: TLO62CP 80p*, Printed Circuit £1.50*, BF245B 50p*, Footswitch £1.50*.

PE TV SOUND SEPARATOR

Complete set of semiconductors £2.30. High quality glass fibre p.c.b. £1.50.
Murata filters: SFE6.0MA 50p. CDA6.0MC 50p.

P & P 15p per order. Orders over £5 past free.

All devices are top grade, brand new and to full manufacturer's spec. We do not sell seconds or rejects. Send S.A.E. for our data sheet and price list.
Prices do not include VAT—add 8% to items marked*, and 12½% to all others.

DAVIAN ELECTRONICS (Mail order, callers by appointment only)
13 Deepdale Avenue, Royton, Oldham OL2 6XD

Marshall's

Head Office and Mail Order to Dept. P.E.

A. Marshall (London) Ltd.

Kingsgate House, Kingsgate Place, London NW6 4TA

Tel: 01-624-0805 Telex 21492

Retail Sales: London: 40 Cricklewood Broadway, NW2 3ET. Tel: 01-452 0161/2 ALSO 325 Edgware Road, W2. Tel: 01-723 4242

Glasgow: 85 West Regent Street, G2 2QD. Tel: 041-332 4133 AND Bristol: 108A Stokes Croft, Bristol, BS16 2LX. Tel: 0272 654201.

LEDS - OPTO BY SIEMENS

Displays 7 seg		LEDS	Red	Gr	Yell
Com anode or cath <td>5mm 3mm</td> <td>15</td> <td>19</td> <td>19</td>		5mm 3mm	15	19	19
Rear view		5mm 20	20	20	20
8mm HT	£1-50	Extra			
10mm HT	£1 55	Bright	40	40	40
14mm HT	£1-57	I/red LD271		£0-55	
18mm HT	£1-85	I/red receiver		£1-45	
		Opto coupler	£1-55		

Full range + data in our '79 catalogue

RAACO STORAGE BOXES

Strong durable high impact polystyrene boxes with brass hinge pins.

B9 £1-82 B18 £1-78

LINEAR (See catalogue for full range)

LM339N	0-80	LM1828N	1-90	CA3026	0-70
LM340T-5	0-88	LM1830N	1-90	CA3028A	0-90
LM340T-12	0-88	LM1845N	1-50	CA3028B	1-25
LM340T-15	0-88	LM1848N	1-38	CA3029	0-75
LM340T-24	0-88	LM1850N	1-90	CA3029A	0-90
LM341P-5	0-58	LM1859N	0-58	CA3030	0-70
LM341P-12	0-56	LM1890N	P.O.A.	CA3030A	2-70
LM341P-15	0-56	LM2907N-8	1-80	CA3031	3-70
LM341P-24	0-56	LM2917N-8	0-60	CA3034	2-75
LM345K	6-97	LM3301N	1-60	CA3035	1-95
LM348N	0-95	LM3302N	0-55	CA3036	1-21
LM350K	6-50	LM3401N	0-55	CA3038	2-90
LM358N	0-60	LM3900N	0-48	CA3038A	4-16
LM360N	3-00	LM3905N	1-15	CA3039	0-77
LM370N	3-30	LM3909N	0-78	CA3040	3-75
LM371H	2-35	LM3911N	1-10	CA3041	1-65
LM373N	3-35	LM3913N	P.O.A.	CA3042	1-65
LM374N	3-35	LM3914N	2-70	CA3043	1-25
LM377N	1-80	LM7850CN	1-58	CA3045	1-50
LM378N	2-40	LM78105CH	0-85	CA3052	0-77
LM379S	4-25	LM7812CH	0-85	CA3047	2-20
LM380N-8	0-96	LM7815C5H	0-85	CA3047A	3-70
LM380N-14	2-08	LM78124CH	0-85	CA3048	2-45
LM381AN	1-70	LM7805KC	1-56	CA3049	1-98
LM381N	1-69	LM7812KC	1-56	CA3050	2-86
LM382N	1-32	LM7815KC	1-56	CA3051	1-62
LM384N	1-55	LM7824KC	1-56	CA3052	1-78
LM386N	0-88	LM78105CZ	0-30	CA3053	0-77
LM387N	1-10	LM7812CZ	0-30	CA3054	1-10
LM388N	1-00	LM7815CZ	0-30	CA3059	2-10
LM389N	1-00	LM78124CZ	0-30	CA3060	2-50
LM392N	0-87	MC667P	2-75	CA3062	3-75
LM701B	2-99	MC671P	1-75	CA3064	1-10
LM701C	2-99	MC672P	1-75	CA3065	1-10
LM702C	0-81	MC724P	1-80	CA3068	3-80
LM703LN	1-15	MC789P	2-10	CA3070	1-90
LM709CH	0-70	MC790P	3-10	CA3071	1-90
LM709-8	0-49	MC796P	2-20	CA3072	1-90
LM709-14	0-49	MC799P	2-20	CA3075	1-70
LM710CH	0-87	MC830P	0-70	CA3080	0-85
LM710-14	0-48	MC833P	0-70	CA3080	0-85
LM711CN	0-48	MC836P	0-82	CA3080A	2-10
LM716	1-00	MC837P	0-82	CA3086	0-50
LM723CH	0-62	MC838P	2-35	CA3088F	1-87
LM723C-14	0-55	MC840P	0-65	CA3089E	2-80
LM741CH	0-50	MC844P	0-70	CA3090Q	4-40
LM741C-8	0-30	MC846P	0-60	CA3130	1-06
LM741C-14	0-30	MC848P	1-10	CA3140	1-04
LM747CN	0-78	MC849P	0-70	LO05T1	2-25
LM748-8	0-50	MC857P	0-85	LF365N	0-80
LM748-14	0-50	MC861P	0-85	LF356N	0-80
LM900	0-50	MC1033P	0-50	LF357N	0-80
LM911	0-50	CA3000	1-30	LF1320N	3-00
LM921	0-50	CA3001	4-25	LF1333N	3-00
LM923	0-50	CA3002	3-35	LF1374H	0-49
LM1303N	1-15	CA3006	4-68	LF1374N	0-38
LM1304N	1-32	CA3007	4-15	LM114H	2-75
LM1305N	1-12	CA3008	2-55	LM301AH	0-48
LM1307N	1-22	CA3012	1-65	LM301-8	1-50
LM1310N	2-10	CA3013	1-85	LM804H	1-50
LM1315N	1-30	CA3014	2-20	LM307N	0-50
LM1458N	0-40	CA3018	0-75	LM308H	0-95
LM1496N	0-97	CA3018A	1-16	LM308N	0-35
LM1800N	1-14	CA3020	1-54	LM309KC	1-85
LM1801N	2-25	CA3020A	2-26	LM317K	1-30
LM1808N	2-10	CA3021	2-40	LM317MP	1-35
LM1812N	0-20	CA3022	2-20	LM317T	2-20
LM1820N	1-18	CA3023	2-20	LM318N	2-48

MEMORIES (see catalogue for full range)

MM2708Q	0-00	MM88C30N	2-08	TMS4043-2NL	2-98	TMS9903NL	13-74
MM5204Q	9-90	MM5314N	4-47	TMS4044-20NL	8-85	TMS9904	P.O.A.
MM5303N	0-83	MM57105N	10-43	TMS4045-20NL	8-88	TMS9905	P.O.A.
MM5307AA/N13	4-5	MM57109N	13-41	TMS4050-2NL	0-48	ADC0871CCN	
MM5314	4-60	MM57160N	0-71	TMS4051-2NL	0-48		15-63
MM5318	4-60	MM57161N	0-71	TMS4060-2NL	0-48	ADC3511CCN	0-30
MM5330N	4-20	TMS2715JL	19-50	TMS4116-25JL		ADC3711CCN	0-35
MM80C95N	0-58				20-00	ADD3501CCN	0-30
MM80C96N	0-68		0-10	TMS4164NL	P.O.A.	ADD3701CCN	0-35
MM80C97N	0-58	TMS4033NL	1-75	TMS6011NC	5-36	A2Y513	0-75
MM80C98N	0-64	TMS4036-2NL	3-28	TMS9900JL	44-41	A3-8500	6-50
MM82C19N	2-90	TMS4039-2NL	2-78	TMS9901NL	10-66	A3-8710	12-75
MM88C29N	2-08	TMS4042-2NL	2-98	TMS9902NL	9-16	SFF7301A	0-95
				TMS9909NL	9-16	SFF96364	16-00

CMOS (see catalogue for full range)

74C00N	0-24	74C48N	1-38	74C95N	1-04	CD4000	0-20	CD4013B	0-52
74C02N	0-24	74C73N	0-54	74C107N	1-22	CD4001B	0-20	CD4014	1-00
74C04N	0-24	74C74N	0-56	74C150N	4-14	CD4002	0-18	CD4015	0-75
74C08N	0-24	74C76N	0-54	74C151N	2-47	CD4006	1-25	CD4016	0-92
74C10N	0-24	74C83N	1-30	74C154N	3-68	CD4007	0-18	CD4017B	1-05
74C14N	0-24	74C85N	1-30	74C157N	2-21	CD4008B	0-98	CD4018B	1-05
74C20N	0-24	74C86N	0-64	74C160N	1-11	CD4009	0-58	CD4019B	0-52
74C30N	0-24	74C89N	4-39	74C161N	1-11	CD4010	0-58	CD4020B	1-15
74C32N	0-24	74C90N	0-85	74C162N	1-11	CD4011B	0-20	CD4021	1-05
74C42N	0-92	74C93N	0-85	74C163N	1-11	CD4012	0-20	CD4022B	1-00

NEW 1979 CATALOGUE

48 page catalogue — new enlarged micro section — largest range of quality components from franchised suppliers available in UK. All VAT inclusive prices. Over 8,000 line items plus lots more. 50p post paid or 40p to callers at any of our four branches.



* MAIL ORDER *

Please add 40p for p/p to all orders. Telephone orders on credit cards £10.00 minimum.



NEW TELETEXT CHIPS

from Mullard — available now from Marshall's — Sole UK distributor to the hobbyist market.

SAA Series, for the reception, display and control of television based text display systems Suitable for 'CEE-FAX' and 'ORACLE' Remote Control	
SAA5000 Infrared / Ultrasonic	£3.48
SAA 5010 Station selector / DICS	£8.13
SAA5012 Binary Input Tuners	P.O.A.
TELETEXT (Dedicated I.C. s)	
SAA5020 TIC (Timing Chain)	£8.71
SAA5030 VIP (Video Input Processor)	£11.61
SAA5040 TAC (Teletext Data Acquisition and Control)	£31.82
SAA5060 TROM (Teletext Read-Only Memory)	£18.86

TIC, TAC & TROM are NMOS — VIP is linear bipolar
We recommend using DIL sockets with these chips

TRIACS


POWER PRICES AT UNBEATABLE		P.T.C.20E5		P.T.C.22E5		P.T.C.26E5		P.T.C.24E6		P.T.C.25E6		P.T.C.23E6			
0-5A	25v	TO18	£0-32	0-5A	25v	TO18	£0-32	0-5A	25v	TO18	£0-32	0-5A	25v	TO18	£0-32
0-5A	50v	TO18	£0-33	0-5A	50v	TO18	£0-33	0-5A	50v	TO18	£0-33	0-5A	50v	TO18	£0-33
0-5A	100v	TO18	£0-40	0-5A	100v	TO18	£0-40	0-5A	100v	TO18	£0-40	0-5A	100v	TO18	£0-40
0-5A	150v	TO18	£0-43	0-5A	150v	TO18	£0-43	0-5A	150v	TO18	£0-43	0-5A	150v	TO18	£0-43
0-5A	200v	TO18	£0-45	0-5A	200v	TO18	£0-45	0-5A	200v	TO18	£0-45	0-5A	200v	TO18	£0-45
0-5A	250v	TO18	£0-48	0-5A	250v	TO18	£0-48	0-5A	250v	TO18	£0-48	0-5A	250v	TO18	£0-48
0-5A	300v	TO18	£0-50	0-5A	300v	TO18	£0-50	0-5A	300v	TO18	£0-50	0-5A	300v	TO18	£0-50
0-5A	350v	TO18	£0-52	0-5A	350v	TO18	£0-52	0-5A	350v	TO18	£0-52	0-5A	350v	TO18	£0-52
0-5A	400v	TO18	£0-54	0-5A	400v	TO18	£0-54	0-5A	400v	TO18	£0-54	0-5A	400v	TO18	£0-54
0-5A	450v	TO18	£0-56	0-5A	450v	TO18	£0-56	0-5A	450v	TO18	£0-56	0-5A	450v	TO18	£0-56
0-5A	500v	TO18	£0-58	0-5A	500v	TO18	£0-58	0-5A	500v	TO18	£0-58	0-5A	500v	TO18	£0-58
0-5A	550v	TO18	£0-60	0-5A	550v	TO18	£0-60	0-5A	550v	TO18	£0-60	0-5A	550v	TO18	£0-60
0-5A	600v	TO18	£0-62	0-5A	600v	TO18	£0-62	0-5A	600v	TO18	£0-62	0-5A	600v	TO18	£0-62
0-5A	650v	TO18	£0-64	0-5A	650v	TO18	£0-64	0-5A	650v	TO18	£0-64	0-5A	650v	TO18	£0-64
0-5A	700v	TO18	£0-66	0-5A	700v	TO18	£0-66	0-5A	700v	TO18	£0-66	0-5A	700v	TO18	£0-66
0-5A	750v	TO18	£0-68	0-5A	750v	TO18	£0-68	0-5A	750v	TO18	£0-68	0-5A	750v	TO18	£0-68
0-5A	800v	TO18	£0-70	0-5A	800v	TO18	£0-70	0-5A	800v	TO18	£0-70	0-5A	800v	TO18	£0-70
0-5A	850v	TO18	£0-72	0-5A	850v	TO18	£0-72	0-5A	850v	TO18	£0-72	0-5A	850v	TO18	£0-72
0-5A	900v	TO18	£0-74	0-5A	900v	TO18	£0-74	0-5A	900v	TO18	£0-74	0-5A	900v	TO18	£0-74
0-5A	950v	TO18	£0-76	0-5A	950v	TO18	£0-76	0-5A	950v	TO18	£0-76	0-5A	950v	TO18	£0-76
0-5A	1000v	TO18	£0-78	0-5A	1000v	TO18	£0-78	0-5A	1000v	TO18	£0-78	0-5A	1000v	TO18	£0-78

THYRISTORS

TYPE	RATING	CASE	PRICE
TIC44T	0-6A 30v	TD18	£0-30

ELF II

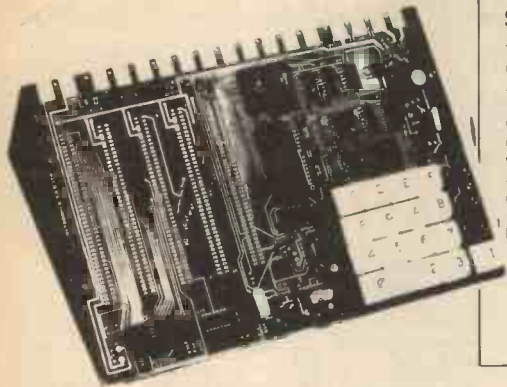FEATURING THE AMAZING RCA COSMAC 1802 MICROPROCESSOR



SPECIFICATIONS

The £99.95 ELF II computer features an RCA COSMAC COS/MOS 1802 8-bit microprocessor addressable to 64K bytes with DMA, interrupt, 16 registers, ALU, 256 byte RAM expandable to 64K bytes, professional hex keyboard fully decoded so there's no need to waste memory with keyboard scanning circuits, built-in power regulator, 5 slot plug-in expansion bus (less connectors), stable crystal clock for timing purposes and a double-sided, plated-through pc board plus RCA 1861 video IC to display any segment of memory on a video monitor or TV screen along with all the logic and support circuitry you need to learn every one of the RCA 1802's capabilities.

£99⁹⁵

PLUS £7.99 V.A.T.

YOU can own an ELF II personal computer for just £99.95.

STOP reading about computers and get your "hands on" an ELF II and Tom Pittman's Short Course. ELF II demonstrates all the 91 commands which an RCA 1802 can execute, and the Short Course speedily instructs you how to use them.

ELF II's VIDEO OUTPUT makes it unique among computers selling at such a modest price. Attached to your Video/Monitor ELF II allows you to display alphanumeric readout, graphics or video games.

ELF II EXPLODES INTO A GIANT

ELF II's 5-Card expansion buses allows you to expand as your need for POWER grows. Plug in the GIANT MONITOR BOARD for I/O with cassette, ASC II Keyboard, TTY, RS232-C etc. ADD up to 16K RAM onboard or more. Build your own circuits with a KLUGE prototype board.

Expanded ELF II is perfect for engineers, business, industry, scientific and educational purposes.

TINY BASIC cassette tape makes programming the ELF II even easier. Use with your ELF II; Commands include: SAVE: LOAD: +, -, * (j); LET: IF/THEN: PRINT: GOTO: GOSUB: RETURN: END: REM: CLEAR: LIST: RUN: PLOT: PEEK AND POKE: 26 variables (A-Z) comes fully documented and includes alphanumeric character generator for direct display on your TV.

ELF-BUG MONITOR cassette lets you debug programmes at lightning speed. It displays contents of all registers on your TV at any point in your programme. Also displays 24 bytes with full addresses, blinking cursor and auto-scrolling. A must for the serious programmer.

AVAILABLE SHORTLY
TEXT EDITOR, ASSEMBLER, DISASSEMBLER AND
NEW VIDEO DISPLAY BOARD
TELEPHONE ORDERS ACCEPTED.



138 KINGSLAND ROAD, LONDON E2 8BY. Tel: 01-739 1582.

PLEASE SEND ME TICK. COMPLETE AND POST TO ABOVE ADDRESS

- RCA COSMAC ELF II Kit, complete with instruction and operating manual.... £107.95
- ELF II Wired & Tested complete with power supply, RCA 1802 Users manual and T. Pittman's "Short Course"..... £161.15
- Power Supply for ELF II..... £5.40
- GIANT BOARD KIT for cassette I/O: TTY, RS232-C I/O, 8 bit P I/O, decoders for 14 separate I/O instructions and systems monitor..... £39.96
- GIANT BOARD Wired & Tested..... £64.75
- 4K RAM BOARD Kit addressable to any page to 64K..... £97.15
- 4K RAM BOARD Wired & Tested..... £124.15
- KLUGE Prototype board accepts up to 36 IC's..... £15.95
- 86 pin Gold Plated Connectors (1 required for each add on cards)..... £5.40
- RF Modulator to use with TV..... £3.00
- ASC II Professional Keyboard Kit with 128 ASC II upper/lower case, 96 printable characters. Onboard regulator, parity logic selection and choice of 4 handshaking signals to mate with most computers..... £63.33
- ASC II Keyboard Wired & Tested..... £98.15
- DE-LUXE METAL & PERSPEX CABINET for ELF II..... £29.82

- DE-LUXE METAL CABINET for ASC II KEYBOARD..... £19.83
- EXPANDED POWER SUPPLY, required when using 4K RAM..... £19.78
- TINY BASIC cassette Tape..... £14.68
- ELF-BUG monitor cassette Tape..... £14.68
- Tom Pittman's "Short course on Microp & Comp" Programme Manual..... £5.00
- Tom Pittman's "Short course on Tiny Basic"..... £5.00
- RCA 1802 Users manual..... £5.00

ALL PRICES QUOTED INCLUDE VAT
all items ex-stock
ADD £2.00 P & P for orders over £15.00

I enclose Cheque/PONO:.....
Barclaycard No:..... or phone.....
Access Card No:..... or phone.....
Name.....
Address.....

DEALERS' INQUIRIES WELCOME

SUPERIOR WATCHES

A well known consumer magazine has published a report on watches which supports our opinion that CASIO and SEIKO are the best watches in the world with CASIO offering unbeatable value for money.

★ THIS YEAR'S STAR BUY

CASIO 46CS-27B
46CS-29B
(29B slightly different case style)

Almost certainly the slimmest and most sophisticated ALARM CHRONOGRAPHS available today.

- LC Display of hours, minutes, seconds, day; And with day, date, month and year calendar.
- Optional 12 hour with am/pm or 24 hour clock display.
- 24 hour alarm setting.
- Optional hourly chimes.
- Chrono measures from 1/10 second to 6 hours.
- Net, lap 1st & 2nd place.
- 7.8mm Stainless Steel case.
- Real mineral glass face.
- Water resistant to 100 feet.
- Less than ± 10 seconds per month.
- S/S bracelet, removable links. Backlight.



£39.95

CASIO ALARM WATCHES



25CR-16B

Left, 9.1mm

£24.95

25CS-16B

Right, 9.25mm

£34.95

LC Display of hours, minutes, seconds (or date), day, am/pm; And with day, month and year. 24 hour alarm setting. Nightlight. 15 months battery life. Stainless Steel case and Mineral Glass face, Water Resistant to 100 feet. Matching fully adjustable bracelets.

CASIO CHRONOGRAPHS

52QS-14B

Left, 8mm

£22.95

45CS-22B

Right

34.95



Net, lap and 1st and 2nd place timing to 1/10 second. Stainless Steel cases with Mineral Glass faces. Water Resistant to 66 and 100 feet. Both have night-lights. 52QS Displays hours, minutes, seconds, am/pm; And with day, date and month. Chrono times to 1 hr, with rollover 45CS Displays hours, minutes, seconds, day; And with day, date, month & year. Selectable 12 hour (with am/pm) or 24 hour clock display, Dual Time facility. Fully adjustable S/S bracelets & removable links.

NEW THE AMAZING MELODY 80 Musical calculating diary watch



ADVANCE SPECIFICATION. Two separate Alarm Tunes. Calculator with keys 1-8 playing individual notes - a mini synthesizer! Complete calendar Watch, Stopwatch, - measuring net and lap times to 1/10 second - Alarm Timer and Calculator with %, 1/10 full memory, date calculations. CASIO RRP £31.95.

£25.95

Other CASIO Calculating Diary Alarm Watches
AQ-2000 £24.95, MQ-10 £35.95, MQ-11 £29.95.
CASIO LCD scientific calculators
FX-48 £14.95; FX-80 £16.95; FX-2500 £19.95; FX-3100 £23.95; FX-58 (alarm clock, stopwatch) £24.95

Most CASIO products available from stock. Send 25p for illustrated brochures of this superb range of watches or calculators (both on request).

Prices include VAT, P & P. Send cheque, PO or phone your ACCESS or BARCLAYCARD number to:-

TIMETRON

Dept PE., Beaumont Suite, 164-167 East Road,
Cambridge CB1 1DB. Telephone 0223 67503

Callers welcome by appointment

AITKEN BROS.

35, High Bridge, Newcastle upon Tyne

Tel: 0632 26729



TMK 500 MULTIMETER 30,000 o.p.v. AC volts 2.5, 10, 25, 100, 250, 500, 1000. DC volts. 0.25, 1, 2.5, 10, 25, 100, 250, 1000. DC current 50µa, 5mA, 50mA, 12 amp. Resistance 0-6K, 60K, 6MEG, 60MEG. Decibels. -20 to + 56 db. Buzzer continuity test size, 160 x 110 x 55MM. Batteries & leads included. **PRICE £24.95.**



SINCLAIR PDM35 DIGITAL POCKET MULTIMETER DC volts (4 ranges) 1MV to 1000V AC volts 1V to 500V DC current (6 ranges) 1nA to 200MA. Resistance (5 ranges) 1Ω to 20 MEGΩ. **PRICE £32.95.** AC Adaptor £3.75 de luxe padded carrying case £3.50 MN 1604 Battery. 99p.



SINCLAIR DM235 BENCH-PORTABLE DIGITAL MULTIMETER. DC volts (4 ranges) 1MV to 1000V AC volts (4 ranges) 1MV to 750V AC & DC current 1µa to 1000MA Resistance (5 ranges) 1Ω to 20 MEGΩ. **PRICE £54.75** Carrying case £9.50. AC adaptor/charger. £3.98 Rechargeable Battery Pack. £9.14.



PANEL METERS DIMS 60MM x 45MM. 50µ amp, 100µ amp 1MA, 5MA, 10MA, 50MA, 100MA, 500MA, 1 amp, 2 amp, 25V dc, 30V dc, 50v AC, 300V ac, "S", "VU" 50-0-50µa, 100-0-100µa, 500-0-500µa. **PRICE £4.95.**



DESOLDERING TOOL SUCTION PUMP. £5.95



PHONE OR SEND YOUR ACCESS OR BARCLAYCARD NUMBER FOR SALES OVER £10. ALL PRICES INCLUDE POSTAGE AND VAT. CATALOGUE 50p. DEDUCTIBLE ON FIRST ORDER OF £5.00 OR MORE.

PNP VERSION OF 2N 3055 BDX 94 @ 75p each.
 100 MINIATURE DIODES CV 9637 with preformed leads @ 50p.
 POLYSTYRENE CAPACITORS sufflex type 12, 15, 20, 25, 30, 50, 56, 100, 120, 1000pf. All at 20p doz.
 WIRE ENDED CRYSTALS 28KHz, 28.5KHz, 31.5KHz. All at 50p each.
 TRANSISTORS 10xAJ CRYSTALS BC 548, BC 549. All 10p, 6 for 50p.
 McMURDO 8 PIN PLUG @ 20p, 8 PIN SOCKET @ 20p, COVER @ 15p.
 3 GANG VARIABLE CAPACITOR 25 + 25 + 25pf @ 75p.
 10 Amp S.C.R.'s 100 PIV @ 25p, 400 PIV @ 50p, 800 PIV @ 60p.
 400mW ZENERS unmarked Good 3.6v, 6.8v, 10v, 11v, 12v, 13v, 16v, 18v, 24v, 30v, 33v, 36 volt. All at 10 for 40p.
 GLASS WIRE ENDED MERCURY SWITCHES @ 25p.
 MC 3340 ATTENUATOR i.c. with data @ 50p.
 X BAND GUNN DIODES with data @ £1.65 each.
 MINIATURE ROTARY SWITCHES 3 Pole 3 way @ 40p, 2 Pole 4 way @ 20p, 1 Pole 10 way 2 Bank @ 40p.
 10 WATT ZENERS 18v, 33v, 57v, 100 volt. All 30p each.
 DIE CAST ALLOY BOXES 6" x 4" x 2" @ £1.15.
 TUBULAR TANTALUM CAPACITORS 2.2uf 20v.w., 68uf 15v.w., 100uf 20v.w., 150uf 20v.w. All at 5p each.
 10 MULTI-TURN TRIM-POTS Assorted for 60p.
 50 BC 107-8-9 TRANSISTORS assorted untested @ 57p.
 ELECTROLYTIC CAPACITORS 2240uf 40v.w. @ 40p, 3,300uf 63v.w. @ 50p, 4500uf 25v.w., 6400uf 25v.w. @ 25p.
 UNIUNION TRANSISTORS 2N 4871 @ 22p, 22N 6028 @ 25p, 2N 6029 @ 25p, MEU 21 @ 22p, MU 4894 @ 22p, 4JDSE29 @ 22p, TIS 43 Type @ 22p.
 30 ASSORTED 10xAJ CRYSTALS @ £1.10, 20 FT 243 CRYSTALS assorted @ £1.50, 20 FT 241A CRYSTALS assorted @ £1.10.
 MULLARD TAA 320 M.O.S.T. PRE-AMPLIFIERS i.c. with circuits @ 35p.
 PLASTIC BC 107, BC 108, BC 177 TRANSISTORS 8p, 10 for 60p.
 MULLARD STRIPLINE 800 MHz NPN BF 362 @ 25p.
 200 ASSORTED 1/4 watt RESISTORS for 75p.
 50 2 WATT ASSORTED ZENERS untested @ 57p.
 600 MHz 8 DIGIT FREQUENCY COUNTER @ £115.
 MAINS TRANSFORMERS 240 volt input. Type 1. 24 volt tapped at 14 volt 1 amp @ £1.30 (P&P 25p), Type 2. 22-0-22 volt 500mA @ £1.60 (P&P 25p), Type 3. 45 volt 6 amp @ £4.50 (P&P 95p), Type 4. 20 volt 1 amp twice 10 volt 1 amp twice @ £4.50 (P&P 95p), Type 5. 45 volt 2 amp 45 volt 500 mA @ £3.50 (P&P 95p), Type 6. 16 volt 2 amp @ £1.60 (P&P 25p), Type 7. 24 volt 1.75 amp @ £1.60 (P&P 25p), Type 8. 30 volt 1 amp @ £1.60 (P&P 25p), Type 9. 13-0-13 volt 1 amp @ £1.60 (P&P 25p), Type 10. 22 volt 500 mA @ 95p (P&P 20p), Type 11. 12 volt 100 mA @ 85p (P&P 20p), Type 12. 22 volt 1 amp, 7.5 volt 500 mA, 6v 1 amp @ £1.60 (P&P 25p), Type 13. 16.5 volt 1 amp @ £1.60 (P&P 25p), Type 14. 12 volt 1 amp @ £1.60 (P&P 25p), Type 15. 32-0-32 volt 500 mA @ £1.60 (P&P 25p).

Please add 20p for post and packing, on U.K. orders under £2, unless stated otherwise. Overseas post at cost.


J. BIRKETT
RADIO COMPONENT SUPPLIES
 25 The Strait, Lincoln LN2 1JF Tel. 20767

Celestion



Retail & Trade from:

ADAM HALL

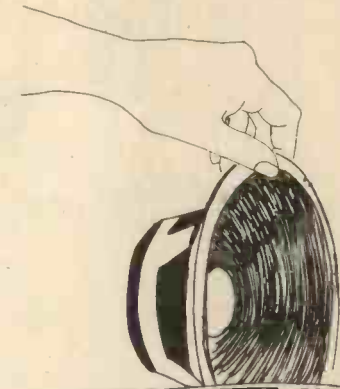

Whatever Your Cabinet Fitting Requirements

ADAM HALL SUPPLIES

Can Pull It Out Of The Bag

Celestions new Power Range Loudspeakers from 10" up to 18" including Powercells & Horns plus our own full range of cabinet fittings which include cabinet covering cloths, fret cloths, trims, locks & catches, hinges, handles, corners, castors, feet & lots of other specialised hardware, most of it impossible to get anywhere else.

Send 30p in stamps for both catalogues to:
 ADAM HALL PE SUPPLIES LTD.
 Unit 3, Carlton Court, Granger Rd,
 Southend on Sea, Essex

RST

VALVE MAIL ORDER CO.

Climax House
Fallsbrook Road, London SW16 6ED

**SPECIAL EXPRESS
MAIL ORDER SERVICE**

AA119	0.11	BCY70	0.18	MPSU01	0.41	1N914	0.06	7405	0.17
AA132	0.45	BCY72	0.14	MPSU06	0.52	1N916	0.08	7406	0.43
AA213	0.19	BC211	1.62	NE55	0.59	1N4001	0.07	7407	0.43
AA215	0.37	BD115	0.49	NKT401	1.16	1N4003	0.08	7409	0.22
AA217	0.29	BD121	1.30	NKT403	1.87	1N4004	0.08	7410	0.17
AC107	0.65	BD123	1.30	NKT404	1.87	1N4005	0.09	7412	0.28
AC125	0.22	BD124	1.40	OA5	1.03	1N4006	0.09	7413	0.35
AC126	0.22	BD131	0.38	OA7	0.59	1N4007	0.10	7416	0.35
AC127	0.27	BD132	0.43	OA10	0.65	1N4009	0.17	7417	0.18
AC128	0.22	BD135	0.37	OA47	0.15	1N4148	0.07	7420	0.18
AC141	0.27	BD136	0.37	OA70	0.32	1N5400	0.14	7422	0.22
AC141K	0.38	BD137	0.38	OA79	0.32	1N5401	0.14	7423	0.35
AC142	0.22	BD138	0.43	OA81	0.32	1S44	0.05	7425	0.32
AC142K	0.32	BD139	0.46	OA85	0.32	1S920	0.08	7427	0.32
AC176	0.22	BD140	0.48	OA90	0.09	1S921	0.09	7428	0.46
AC187	0.22	BD144	2.16	OA91	0.09	2G301	1.08	7430	0.18
AC188	0.22	BD181	1.19	OA95	0.09	2G302	1.08	7432	0.32
AC17	0.92	BD182	1.27	OA200	0.10	2G306	1.19	7433	0.39
AC18	0.86	BD237	0.43	OA202	0.10	2N404	1.08	7437	0.35
AC19	0.81	BD238	0.59	OA211	1.08	2N696	0.27	7438	0.35
AC20	0.76	BDX10	0.98	OA220	1.08	2N897	0.27	7440	0.19
AC21	0.81	BDX32	2.16	OA2201	1.08	2N698	0.32	7441AN	0.39
AC139	1.62	BDY20	1.35	OA2206	1.08	2N705	1.30	7442	0.78
AD149	0.76	BDY60	1.62	OA2207	1.08	2N706	0.16	7447AN	0.97
AD161	0.49	BF115	0.27	OC16	2.16	2N708	0.22	7450	0.19
AD162	0.49	BF152	0.19	OC20	2.70	2N930	0.22	7451	0.19
AF106	0.81	BF153	0.22	OC22	2.70	2N1131	0.28	7453	0.19
AF114	0.81	BF154	0.27	OC23	2.97	2N132	0.38	7454	0.19
AF115	0.81	BF159	0.25	OC24	3.24	2N1302	0.38	7460	0.19
AF116	0.81	BF160	0.17	OC25	0.97	2N1303	0.38	7470	0.38
AF117	0.81	BF167	0.22	OC26	0.97	2N1304	0.49	7472	0.36
AF139	1.43	BF173	0.22	OC28	2.16	2N1305	0.49	7473	0.39
AF186	1.30	BF177	0.26	OC29	2.16	2N1306	0.54	7474	0.43
AF239	0.49	BF178	0.28	OC35	1.62	2N1307	0.54	7475	0.58
AF211	2.97	BF179	0.27	OC36	1.52	2N1308	0.59	7476	0.43
AF212	2.97	BF180	0.32	OC41	0.86	2N1309	0.59	7480	0.59
ASV26	0.43	BF181	0.32	OC42	0.81	2N1613	0.27	7482	0.81
ASV27	0.43	BF182	0.32	OC43	2.43	2N1671	1.62	7483	0.97
AS215	1.35	BF183	0.27	OC44	0.65	2N1893	0.27	7484	1.08
AS216	1.35	BF184	0.28	OC45	0.59	2N1897	1.89	7486	0.38
AS217	1.35	BF185	0.27	OC71	0.59	2N2148	1.78	7490	0.86
AS220	1.62	BF194	0.10	OC72	0.59	2N2218	0.27	7491AN	0.86
AS221	2.16	BF195	0.10	OC73	1.08	2N2219	0.26	7492	0.65
AU110	1.84	BF196	0.11	OC74	0.70	2N2220	0.19	7493	0.65
AU113	1.84	BF197	0.14	OC75	0.70	2N2221	0.19	7494	0.36
AU170	1.84	BF200	0.29	OC76	0.59	2N2222	0.19	7495	0.78
BA145	0.15	BF242	0.23	OC77	1.30	2N2223	0.97	7496	0.36
BA148	0.15	BF244	0.30	OC81	0.70	2N2368	0.18	7494	3.24
BA154	0.10	BF257	0.26	OC81Z	1.30	2N2369A	0.23	74100	1.62
BA155	0.11	BF258	0.28	OC82	0.70	2N2484	0.22	74107	0.49
BA156	0.10	BF259	0.35	OC83	0.70	2N2646	0.59	74109	0.76
BAW52	0.06	BF336	0.32	OC84	0.70	2N2904	0.27	74110	0.54
BAX13	0.07	BF337	0.32	OC122	1.62	2N3055	0.27	74111	0.76
BAX16	0.10	BF338	0.33	OC123	1.89	2N3068	0.23	74115	1.89
BC107	0.13	BFS21	4.28	OC139	2.43	2N2907	0.23	74118	1.08
BC108	0.13	BFS28	2.41	OC140	2.97	2N2924	0.23	74119	1.62
BC109	0.14	BFS61	0.23	OC141	3.51	2N2925	0.25	74120	0.90
BC113	0.14	BFS98	0.23	OC170	1.08	2N2926	0.16	74121	0.43
BC114	0.15	BFW10	0.70	OC171	1.08	2N3053	0.27	74122	0.65
BC115	0.17	BFW11	0.70	OC200	1.62	2N3054	0.54	74123	1.08
BC116	0.17	BFX84	0.24	OC201	1.89	2N3055	0.76	74125	0.59
BC117	0.19	BFX85	0.25	OC202	1.89	2N3440	0.65	74126	0.59
BC118	0.11	BFX87	0.23	OC203	1.89	2N3441	0.86	74128	0.65
BC125	0.18	BFX88	0.23	OC204	2.70	2N3442	1.19	74132	0.76
BC126	0.23	BFY80	0.28	OC205	2.70	2N3525	0.86	74136	0.59
BC136	0.17	BFY81	0.28	OC206	0.42	2N3614	1.62	74141	1.89
BC136	0.17	BFY52	0.28	OC207	1.89	2N3702	1.12	74142	2.48
BC137	0.17	BFY64	0.28	OC208	1.35	2N3703	0.15	74143	2.70
BC147	0.10	BFY90	1.35	ORP12	0.81	2N3704	0.15	74144	2.70
BC148	0.09	BSX19	0.23	R2008B	1.97	2N3705	0.15	74145	0.97
BC149	0.10	BSX20	0.22	R2009	2.43	2N3706	0.15	74147	2.16
BC157	0.16	BSX21	0.22	R2010B	1.97	2N3707	0.15	74148	1.89
BC158	0.09	BT106	1.35	TC144	0.32	2N3708	0.11	74150	1.73
BC159	0.11	BTY79/4	3.45	TC226D	1.30	2N3709	0.15	74151	0.92
BC167	0.14	BU205	1.97	TL1209	0.22	2N3710	0.11	74154	1.89
BC170	0.12	BU206	2.53	TP129A	0.46	2N3711	0.11	74155	0.92
BC171	0.11	BU208	2.25	TP130A	0.50	2N3712	1.87	74156	0.92
BC172	0.13	BY100	0.15	TP131A	0.46	2N3713	2.18	74157	0.81
BC173	0.13	BY126	0.15	TP132A	0.52	2N3713	3.24	74159	2.27
BC177	0.16	BY127	0.16	TP133A	0.75	2N3819	0.41	74170	2.48
BC178	0.15	BZX61	0.19	TP134A	0.79	2N3820	0.51	74172	4.75
BC179	0.17	Series		TP141A	0.68	2N3823	0.62	74173	1.51
BC182	0.12	BYZ88	0.14	TP142A	0.76	2N3866	0.81	74174	1.82
BC183	0.11	BZ185		TP1295B	0.72	2N3904	0.15	74175	0.97
BC184	0.12	CRS1/05	0.49	TP1305S	0.60	2N3905	0.15	74176	1.19
BC212	0.14	CRS1/40	0.65	TS143	0.51	2N3906	0.15	74178	1.35
BC213	0.14	CRS3/40	0.81	ZS140	0.28	2N4058	0.16	74179	1.35
BC214	0.17	CRS3/60	0.97	ZS170	0.24	2N4058	0.11	74180	1.28
BC237	0.10	GEX56	1.62	ZS178	0.81	2N4060	0.14	74190	1.62
BC238	0.14	GEX541	1.89	ZS271	0.26	2N4061	0.14	74191	1.62
BC301	0.27	GJ3M	0.81	ZS278	0.64	2N4062	0.15	74192	1.46
BC303	0.26	GJ5M	0.81	ZTX107	0.12	2N4124	0.18	74193	1.46
BC307	0.11	GL7M	0.81	ZTX108	0.11	2N4126	0.18	74194	1.35
BC308	0.11	GM0378A	1.89	ZTX109	0.14	2N4286	0.23	74195	1.08
BC327	0.23	KS10A	0.32	ZTX300	0.17	2N4287	0.25	74196	1.30
BC328	0.21	MJE340	0.86	ZTX301	0.15	2N4289	0.27	74197	1.19
BC337	0.21	MJE370	1.26	ZTX302	0.17	2N5457	0.39	74198	2.43
BC338	0.19	MJE371	0.66	ZTX303	0.19	2N5458	0.39	74199	2.43
BCY30	1.08	MJE520	0.56	ZTX304	0.21	2N5459	0.39	78013N	1.87
BCY31	1.08	MJE521	0.59	ZTX311	0.14				
BCY32	1.08	MJE295S	1.35	ZTX314	0.23				
BCY33	0.97	MJE305S	0.81	ZTX500	0.16				
BCY34	0.97	MPE102	0.34	ZTX501	0.16				
BCY39	3.24	MPE103	0.34	ZTX502	0.18	7400	0.17	Plugs in socket	
BCY40	1.08	MPE104	0.34	ZTX503	0.19	7401	0.17	- low profile	
BCY42	0.27	MPE105	0.34	ZTX504	0.23	7402	0.17	8 pin DIL	0.16
BCY43	0.27	MPSA08	0.26	ZTX531	0.23	7403	0.17	14 pin DIL	0.16
BCY58	0.17	MPSA56	0.29	ZTX580	0.18	7404	0.18	16 pin DIL	0.18

Open daily to callers: Mon.-Fri. 9 a.m.-5 p.m.
Valves, Tubes and Transistors - Closed Saturday
Terms C.W.O. only - Tel. 01-677 2424-7
Quotations for any types not listed S.A.E.
Post and Packing 30p per order
All prices include V.A.T.

Prices correct when going to press

ADAMIN miniature SOLDERING IRONS

£3.90

by LITESOLD
(INC P & P)



They are ideal for fine electronics work of all kinds and their high performance and range of bits gives them great flexibility.

Features include:

Fully enclosed heating elements - non-seize bits
Unbreakable nylon handle - Detachable hook
Fully insulated to withstand 1000V AC.

Specification:

- Wattage: 12W.
- Temperature: 360C.
- Weight: 1/2 oz (14.9g) less flex.
- Bit size: 1/16" supplied.

Full range of 14 bits available - details of these and other soldering products sent with order.

Future Electronics

Dept. MA1 Unit B1 Parkhall Trading Estate,
Martell Road, London SE21.

CRESCENT RADIO LTD.

1 ST. MICHAELS TERRACE,
WOOD GREEN, LONDON,
N22 4SJ (MAIL ORDER DEPT.) 888-3206

FLIP
Push Button
Heads or Tails.

Complete kit and full instructions supplied.
A pocket game. Easy to build and great to play. Kit price £5.25 + 42p VAT.
Post free.

3 KILOWATT PSYCHEDELIC LIGHT CONTROL UNIT
1000W lighting per channel, max.
A 3 channel sound to light unit housed in a robust metal case, with a sensitivity control for each channel i.e. Bass, middle and treble. Full instructions make this unit easy to connect to your present amplifier.
S.A.E. for spec. sheet.
Still only £20.00 + 1.60 VAT.

PANEL METERS.
Dims:- 60 x 47 x 33mm.
Require 38mm dia. cut out

T22	0-100µA
T23	0-500µA
T24	0-1 M/A
T25	0-5 M/A
T26	0-10 M/A
T27	0-50 M/A
T28	0-100 M/A
T30	0-1 AMP
T31	0-2 AMP
T36	VU Meter
T43	0-30 V.DC
T36	"S" Meter

£5.50 + 44p VAT.

STEREO CONDENSER MICROPHONE

SPECIAL STEREO 600 ohms
Sensitivity deviation within 3dB between right and left microphone. In carrying case. Fitted TWQ 3.5mm JACK PLUGS.
£13.00 + 1.62 VAT.

CR. 100 MONO AMPLIFIER MODULE
Output power:- 1

THE BIG GUNS!

LAST month in the leader we looked at one aspect of the manufacturers and industrial distributors involvement in component supply. Although many companies are not interested in supplying one-off components on a mail order retail basis they are now becoming more interested in encouraging hobbyist use of their products and in making the hobbyist aware of their company name.

The fact that a good percentage of our readers are employed in industry, does, of course, not escape them and they also realise that the spending power of the hobbyists as a collective unit is considerable. We are gradually finding more companies that are willing to spend some time and effort wooing the hobbyist.

This issue carries the second part of our *Microprocessor Evaluation System*, it will have been noted by many readers that this system is based on a General Instruments device and the article is written by one of their engineers. G.I. actively encourage their employees to develop ideas for publication and it is likely that more projects will come from this stable. We are also in contact with Ferranti, Mul-

lard and Texas and expect these contacts to also bear fruit.

It is true to say that this is not something new and we have had similar tie-ups in the past. What is interesting is that at the present time, more large organisations are becoming aware of the potential in this market, and, because of this, we should all benefit. Obviously the knowledge and industrial backup that such companies provide can lead to the best possible projects, often developed by the very engineers involved in the design of the i.c.s. employed. We can thus offer readers projects developed with the aid of test gear and facilities that are out of reach of a small company, let alone most hobbyists.

This factor is probably not significant when related to a sound to light system or remote control but when a high quality amplifier is to be described, immense benefit in the performance of a project constructed at home can result. We believe that this involvement by such companies can only do good to our hobby, however, we will not overlook the fact that it is often possible to improve on commercial equipment.

COMPUTER

If you read the review of Superboard II in this issue, that long awaited product of Ohio Scientific Industries, you will realise that it is possible to improve on the design and, even for its extremely competitive price, the Superboard, although very versatile, is not the best possible product. It follows that although a great deal of time and company effort has been expended in the design of this product, the final result could still be improved on; fantastic though that may sound when related to such an excellent computer for less than £300.

As we have noted at the end of the review, improvements are being incorporated in a design based on Superboard and we expect a full series to be published in P.E., starting in the August issue, describing what we honestly believe will be a computer to outstrip all others in the price range — kit or complete.

EAR PLUGS?

It seems that the bit of trumpet blowing we did a couple of months ago has had no effect on any readers as, to date, we have not received a single comment on it!

Mike Kenward

EDITOR

Mike Kenward

Gordon Godbold ASSISTANT EDITOR

Mike Abbott TECHNICAL EDITOR

Alan Turpin PRODUCTION EDITOR

David Shortland PROJECTS EDITOR

ADVERTISEMENT MANAGER

SECRETARY

REPRESENTATIVE

CLASSIFIED MANAGER

Jack Pountney ART EDITOR

Keith Woodruff ASSISTANT ART EDITOR

John Pickering SEN. TECH. ILLUSTRATOR

Isabelle Greenaway TECH. ILLUSTRATOR

Judith Kerley SECRETARY

D. W. B. Tilleard

Christine Pocknell

Peter Mew 01-261 6819

Colin Brown 01-261 5762

01-261 6676

Editorial Offices:

Westover House,
West Quay Road, Poole,
Dorset BH15 1JG
Phone: Editorial Poole 71191

We regret that lengthy technical enquiries cannot be answered over the telephone (see below).

Advertising Offices:

King's Reach Tower,
King's Reach, Stamford Street, SE1 9LS
Telex: 915748 MAGDIV-G

Make Up/Copy Dept.: 01-261 6601

Technical Queries

We are unable to offer any advice on the use or purchase of commercial equipment or the incorporation or modification of designs published in Practical Electronics.

All letters requiring a reply should be accompanied by a stamped, self addressed envelope and each letter should relate to one published project only.

Components are usually available from advertisers; where we anticipate supply difficulties a source will be suggested.

Back Numbers

Copies of most of our recent issues are available from: Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF, at 75p each including Inland/Overseas p&p.

Binders

Binders for PE are available from the same address as back numbers at £2.85 each to UK addresses, £3.45 overseas, including postage and packing, and VAT where appropriate.

Orders should state the year and volume required.

Subscriptions

Copies of PE are available by post, inland or overseas, for £10.60 per 12 issues, from: Practical Electronics, Subscription Department, Oakfield House, Perrymount Road, Haywards Heath, West Sussex RH16 3DH.

Cheques and postal orders should be made payable to IPC Magazines Limited.

It is not often, even in the lightning-fast field of Microcomputers, that we have a chance to review a system quite as up-to-the-minute as the one described below. The machine lent to us by COMP Components (14 Station Road, New Barnet, Herts. Tel: 01-441 2922) was perhaps one of the only two in the country at that time. Supply problems have been immense for Ohio Scientific Industries who make the machine. It can only be hoped that, by the time this review appears, the Superboard will be available ex-stock, or on very short delivery, not only from COMP but from the many stockists who started taking orders before Xmas on a full cash basis from the hundreds of hobbyists who have shown interest in this remarkable machine.

The photographs in this article show the compact form the Superboard takes—along with the type of video output which can be expected. Prices range from just over £260 to around £280—see current adverts in this issue for the latest information.

THE machine comes as a single p.c.b. which includes the keyboard section, plus a set of manuals and cassette-based demonstration programmes.

P.C.B. LAYOUT

The p.c.b. is extremely well laid-out, as the photograph shows, with the keyboard deciding the total width of the board which is approximately 370 by 305mm (14½in. x 12in.) in size. The quantity of room and uncramped nature of the assembly would make this a very acceptable kit with few of the usual problems associated with highly dense component layouts. Plenty of high frequency by-passing is also provided as can be seen from the number of disc-ceramic capacitors dotted about the board.

Referring to the p.c.b. photograph: just above, and to the left of the keyboard, is a line of six 24-pin d.i.l. sockets holding, from left to right, one ACIA (6850) for serial communication devices such as cassette and teletype, the monitor ROM (2K Bytes) and four BASIC ROMs (2K Bytes each). These are followed by the 6502 MPU which is at the heart of this machine. Further to the right is a pair of two-way data bus buffers—using 8T28 chips—and some logic for running the keyboard. Finally, at extreme right, is a 40-pin d.i.l. expansion socket labelled J1. The 8T28's are used purely for expansion via J1.

The next couple of rows of i.c.s are for various logic functions and include some unoccupied i.c. pads labelled PROTO on the circuit diagram in the manual and not connected to any p.c.b. tracks. The two rows above these form the next two main blocks

of the system—VDU and RAM sections. The RAM is seen implemented by two half-rows of 2114 (1K by 4 BITS) RAM i.c.s over to the right. Eight of these sockets contain i.c.s in the basic system giving 4K bytes of memory and eight more are provided for 4K of expansion simply by plugging in the extra chips.

Only 7K of memory is shown in the photograph. Further to the left is another pair of 2114s forming a further 1K of RAM for the VDU. Next to these is the 24-pin character-generator chip and switching i.c.s for the VDU which is of the memory-mapped type for speed and complete flexibility of use. Over to the extreme left is the crystal-controlled clock generator from which the whole computer, from MPU to cassette interface, derives its timing information.


At the top of the board is the remaining support logic and cassette interface (over to the left), along with various unoccupied holes and pads—the components for which may be added later to complete an asynchronous communications interface including RS232. The top right of the board has provision for power supply unit components, and in the photograph houses an efficient little u.h.f. modulator (ASTECC) which allows direct connection to the aerial socket of a TV (tuning around Channel 36) and gives the excellent results shown in the photographs in this article.

- ★ 8K High Speed BASIC + 2K Monitor
- ★ Up to 8K RAM On Board
- ★ Cassette interface at 300 BAUD (CUTS)
- ★ VDU—With its Own Dedicated RAM
- ★ Full ASCII Keyboard
- ★ Fully Expandable Via On-Board Sockets
- ★ Less than £300

OHIO SUPERBOARD II REVIEW

A.A. BERK B.Sc. Ph.D.



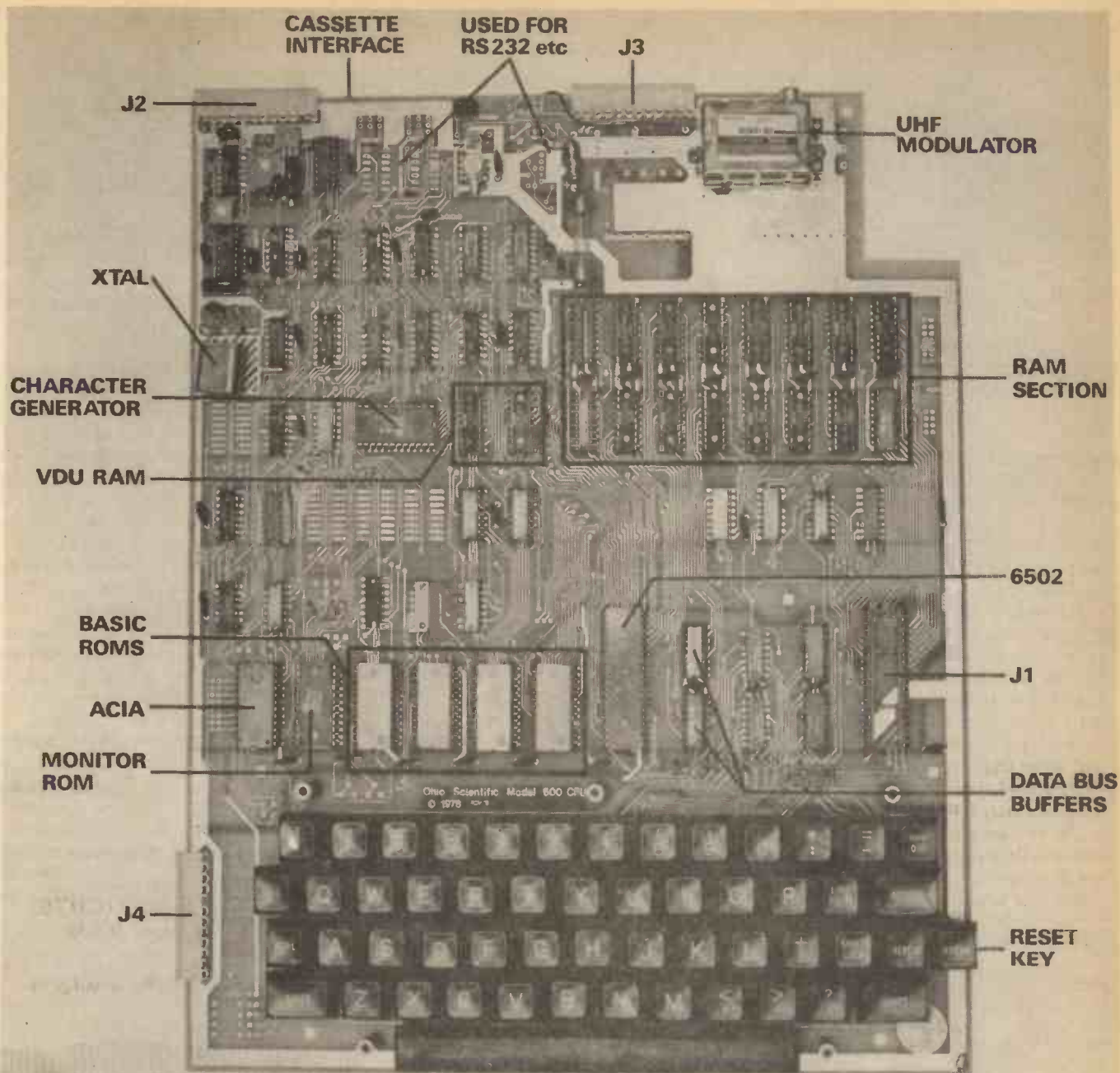

SUPPLY

The Superboard is a single supply device requiring a regulated +5 volt source. The current depends heavily on the number and type of 2114 employed on the board. OHIO supplies the low-power versions, and with the full 8K the p.s.u. will have to deliver 2.5 to 3 amps. There are also two sockets (with plugs included!) on the top edge of the board. The most important of these is J2—to the left—as this supplies inputs and outputs to cassette and video monitor (or u.h.f. modulator). The other, J3, is for asynchronous communications.

The various "links" printed on the p.c.b. may be cut and connected differently for a variety of uses, and a further edge connector, J4, next to the keyboard (left) may be used to expand the key-functions for a separate programmable application.

The ambitious user will certainly find the p.c.b. construction and layout more flexible than most single-board computers on the market, not least for the reason of spaciousness of design.

KEYBOARD

The integral keyboard gains its best "touch" when the whole p.c.b. is screwed firmly to a base-board of some rigid material such as chip-board. It is pleasant to operate and apparently instantaneous in use. There are 53 keys which form a familiarly spaced type-writer format with legends properly moulded-in for durability and excellent readability.

One's unconscious emotional reaction to any computer is almost certainly heavily dependent upon three things:

- (a) The keyboard.
- (b) The display.
- (c) The software monitor and programming language employed.

These three areas are described overleaf.

To the computer, the keyboard is an array of 8 rows and 8 columns occupying a single address location (DFOO). One location is enough as the 8 rows are write-only and the columns read-only. The keyboard routine, stored in the monitor ROM, constantly sends "walking-bit" information to the rows—latched by two 4-bit latches (74LS75s)—and reads the columns looking for the result of a key-closure. The keyboard is thus read for information and decoded by the monitor—this obviates the necessity for a hardware keyboard-encoder chip and ensures speed and accuracy with a low (and hence cheap) chip count. Multiple key readings are prevented by carefully written software and, indeed, this keyboard was considerably less prone to "doubling" than that of some other personal computers.

One or two idiosyncrasies of the keyboard are worth mentioning. The BREAK key to the far right of the keyboard, is simply a RESET button and will be described later. RUBOUT and ESC seem to have no effect for normal operation and the REPEAT key appears to do the exact opposite. If any key is pressed for more than about half a second, that character or function starts repeating continuously (a very useful feature) until the key is released—pressing REPEAT stops this process!

The character generator in the VDU section contains upper and lower case letters plus all the necessary special characters in the ASCII set. These are accessible via the keyboard but not all are indicated. For instance, "UP ARROW"—here implemented by \wedge —is an essential part of BASIC programming and is given by SHIFT N, a fact which the experienced programmer will already know, but not so the first time user. There are several other "hidden" special characters, and the complete list, which I discovered, is shown in Table 1 along with any function they perform.

Table 1

Shifted Character	Special Character	Function
P	@	deletes current line
O	—	deletes last character typed
S	C	none
K	[none
L	\	none
M]	none
N	\wedge	"up arrow" in BASIC

Normal operation of the keyboard is in upper-case mode and for this, the SHIFT LOCK must be set in its "down" or "locked" position. My first mistake was to miss this point in an initial enthusiasm to see the BASIC working! Here the manual has its own poignant, if ungrammatical, reminder to the user not to be guilty of the adage about—"reading the instructions when all else fails".

As BASIC text is entered into the machine each line may be corrected or deleted before the computer reads the line for execution or filing. When such a line is complete, RETURN is pressed to transfer the line into the machine.

Two control characters are used on the keyboard: CONTROL O and CONTROL C. The first suspends the VDU display during command and program entry, the second suspends program execution. CONTROL O is very useful, for instance, for running from a clear screen—the command RUN, typed after CONTROL O, will not appear.

DISPLAY

As explained above, the VDU section is of the memory mapped type and hence each character on the screen occupies a specific memory location. The Hex address of the "screen" can be found on the memory map diagram (Table 2) and will be seen

to occupy 1024 (1K) locations. These are arranged as 32 characters by 32 lines on the screen, but many of them remain undisplayed by the majority of TV sets. The reason for this is quite simple and rests on the fact that a 4MHz (approx.) crystal is employed to generate the "dot" frequency for the characters. Each character is formed from an 8 x 8 dot matrix and the width of a dot on a TV screen is inversely proportional to the dot frequency; 4MHz is simply too low (and hence the dots are too large) to accommodate much more than 24 characters on a horizontal line.

I could only fit 23 on the Philips set illustrated. It is possible to adjust some sets to accommodate more characters per line, but the machine is meant for the average domestic TV, and the majority of rental companies will show a remarkable lack of enthusiasm for your rearrangement of the internals of their £300 colour sets.

In setting up the machine for initial use, the SHIFT LOCK is pressed to lock it into the "down" position and then the BREAK key operated. BREAK may be pressed at any time during use causing the display to clear and present the letters D/C/W/M? on the lowest line used by the monitor. These letters, as with all entries to the machine under monitor control, scroll upwards on the display as new entries take their place on the lowest line. BREAK places the machine in its command mode and only one of the above four command letters will be accepted at this point.

The letter D is for disk operation and is not applicable here. C clears the memory of the machine and causes the words MEMORY SIZE? to appear. At this point the user may reserve memory space to hold machine code routines or binary data blocks. Typing just RETURN reserves no memory space, while typing any number greater than 769 (the minimum number of memory bytes needed as workspace for the monitor and BASIC interpreter) will restrict the RAM available for writing in BASIC. This prevents subsequent programming from using the reserved space and destroying its contents.

The next message to appear is TERMINAL WIDTH? Typing RETURN assumes the number 24, while typing any number from 16 to 23 restricts the use by the BASIC interpreter to that number of characters per line VDU display. Any number greater than 24 is assumed to mean 24, and any number less than 16 is ignored causing TERMINAL WIDTH? to reappear. When other output devices are used, the width may be specified up to 72 characters.

After terminal width has been specified, the Superboard enters its BASIC function by printing up a quick advert for itself and giving the number of free bytes of RAM available, which it determines using a memory test. Any RAM malfunction may be noted at this point.

Table 2. Memory Map of the Superboard II

Hex Address	Function
0000 - 02FF	This block of RAM is used by the monitor and BASIC ROMs as scratch-pad—included here is the stack and all necessary vectors and flags
0300 - 0FFF	Rest of basic 4K system RAM
2000 - 1FFF	Optional extra on-board 4K RAM
A000 - BFFF	BASIC ROMs (8K)
D000 - D3FF	Video RAM
DFOO	Keyboard
F000 - F001	ACIA for serial communications
F800 - FFFF	Monitor ROM including: floppy disk bootstrap, keyboard routine, 65V machine code monitor, BASIC support and hardware vectors for NMI, RESET and IRQ



TUAC

TRANSISTOR UNIVERSAL AMPLIFICATION CO. LTD.
PHONE 01-672 3137/672 9080
MANUFACTURERS OF QUALITY AMPLIFICATION AND LIGHTING
CONTROL SYSTEMS

PRICES INCLUDE VAT, P & P FREE
correct at 1.5.79
TO ORDER BY POST


Make cheques/P.O.s payable to TUAC LTD. (PE479) or quote
Access/Barclaycard No. and post to TUAC LTD. (PE479) 119
Charimont Road, London SW17 9AB. We accept phone orders from
Access/Barclaycard Holders. Phone 01-672 9080.

NEW FROM TUAC ULTRA QUALITY HIGH POWER New D.C. Coupled Design AMPLIFIERS



T.H.D. at full power 0.1%
T.D. 500 300W into 2 Ohms
220W into 4 Ohms
140W into 8 Ohms
Power supply P.S. 300
T.D. 150 150W into 4 Ohms
100W into 8 Ohms
Power supply P.S. 150
T.D. 150. 60 Version 60W into 8 Ohms
40W into 15 Ohms.
Power supply P.S. 60
Note P.S. 300 will drive 2 T.D. 150 amplifiers

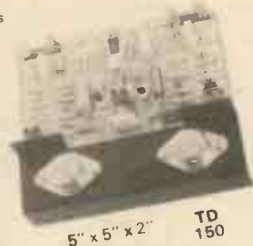Featuring
Electronic Short Open & Thermal Overload Protection.
Brief Spec.
Input Sensitivity 0.775.v. R.M.S. (O.D.B.) at 25 K Ohms
Frequency Response 20 Hz-20 KHz
Hum & Noise - 100 dB Relative full output



£45.00
£30.00
£28.25
£19.75
£19.75
£15.50

All output ratings are R.M.S. continuous sine wave output.

AMPLIFIER MODULES



SPEC. INPUT
SENSITIVITY 60 mV
for full output
Frequency response
20 Hz-20 KHz
HUM & NOISE - 70 dB

TL30 5" x 5" x 2"
* 35 watt 10 amp output transistors £14.75
TL60 5" x 5" x 3"
* 60 watt R.M.S. continuous sine wave output
* 2 R.C.A. 110 watt 15 amp output transistors £18.50
TL100 5" x 5" x 3"
* 100 watt R.M.S. continuous sine wave output
* 2 R.C.A. 150 watt 15 amp output transistors £21.50
TP125 7" x 6 1/2" x 3"
* 125 watt R.M.S. continuous sine wave output
* 4 R.C.A. 150 watt 15 amp output transistors £27.50


4 CHANNEL SOUND TO LIGHT SEQUENCE CHASER - 4LSMI

- Full wave control
- RCA 8A Triacs
- 1000W per channel
- Fully suppressed and fused
- Switched master control for sound operation from 1/2W to 125W
- Speed control for fixed rate sequence from 8 per minute to 50 per second
- Full logic integrated circuitry with optical isolation for amplifier protection

£21.50

Model 501 500W per channel as above without sound triggering

£14.00

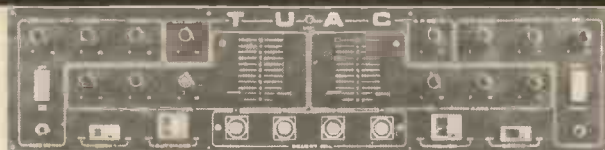

STEREO DISCO MIXER

With touch sensitive switching and auto fade

INPUTS: Four identical stereo inputs available with any equalisation. Two magnetic and two flat supplied as standard. High quality slider control on each channel. Volume, treble and bass controls for each pair of sliders. Sensitivity mag. .3mV (R.I.A. comp.). Flat 50mV at 1kHz. Bass controls ±18dB at 60Hz. Treble controls ±18dB at 15kHz
OUTPUT: Up to 3 volts (+12dB) available. Attenuated output for TUAC Power Modules, Rotary master and balance controls. Band width 15Hz - 25kHz ± dB.
P.F.L.: Output 250mV into 8 ohms. Rotary volume control. Monitoring facility for all 4 channels. Selection via touch sensitive illuminated switches. Switched visual cue indicator.
Miscellaneous Facilities: Two illuminated deck on/off switches. Mains illuminated on/off switches. Auto fade illuminated on/off switch. Mains powered with integral screen and back cover. Complete with full instructions
Size 25in long x 6in high x 3in deep
Mono Disco Mixer with autofade £52.00 £189.00

3 CHANNEL LIGHT MODULATOR SILMB

- RCA 8A Triacs
- 1000W per channel
- Each channel fully suppressed and fused
- Master control to operate from 1W to 125W
- Full wave control

£21.50



FRONT PANEL FOR LIGHTING EFFECT MODULES

(complete with switches, neons and knobs)
as illustrated



For S1LMB £8.30
Size 8" x 4 1/2"



4LSM1 £7.25
Size 6 1/2" x 4 1/2"



S1LMB £9.50
(Combined with 3SDM1
Size 9" x 4 1/2"

POWER SUPPLIES



Vacuum varnish impregnated. Transformers
with supply board incorporating pre-amp supply:


PS250 for supplying 2 TP125s £30.00
PS200 for supplying to TL100s £30.00
PS60/60 for supplying 2 TL60s £30.00
PS125 ± 45 volts for TP125 £19.75
PS100 ± 43 volts for TL100 £18.25
PS60 ± 38 volts for TL60 £15.50
PS30 ± 25 volts for TL30 £12.50
PSU 2 for supplying disco mixer £7.50

STOCKISTS - CALLERS ONLY

A1 Music, 88, Oxford Street, Manchester (Tel 061 236 0340)
Geo Mathews, 85/87, Hurst Street, Birmingham (Tel 021-622 1941)
Soccodi, 9, The Friars (Tel Canterbury 60948)
Cookies Disco Centre, 126/128, West Street (Tel Crewe 4739)
Garland Bros. Ltd., Deptford Broadway, London 01-692 4412
Luton Disco Centre, 88, Wellington Street, Luton (Tel Luton 411733)
Session Music, 163, Mitcham Road, Tooting (Tel 01-672 3413)
Mon-Sat 10am to 6pm, Closed Wed.
Electra Centre, 58, Lancaster Road, Preston (Tel Preston 58488)
Electrosure Ltd., Fore Street (Tel Exeter 56687)
Salcoglen Ltd., 43, Borough Road (Tel Middlesbrough 242851)
Menhouse Ltd., 82, St. Mary Street (Tel Southampton 28028)

TRADE & EXPORT ENQUIRIES 01-672 3137

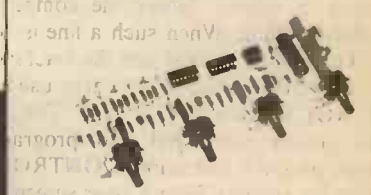ADD SEQUENCE CHASING + DIMMING EFFECTS FOR TUAC 3 CHANNEL LIGHT MODULATOR




- Speed Control 3 per min. to 10 per sec.
- Full logic integrated circuitry
- Dimmer control to each channel

3SDM1 £16.50

SUPPLIERS TO H.M. GOVT. DEPTS. MANUFACTURED AND ASSEMBLED IN GT. BRITAIN FULLY TESTED AND GUARANTEED
SEND NOW FOR OUR FREE 28 PAGE ILLUSTRATED CATALOGUE: SEND STAMP PLEASE

SUPERSOUND 13 HI-FI MONO AMPLIFIER

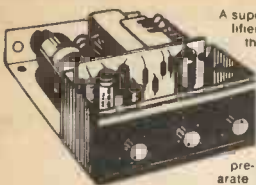

A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz-30KHz \pm 3db. Fully integrated pre-amplifier stage with separate Volume, Bass, Treble and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3in high \times 6in wide \times 7in deep. AC 200-250V.

PRICE £18.00 P. & P. £1.20.

HARVERSONIC MODEL P.A. TWO ZERO

An advanced solid state general purpose mono amplifier suitable for Public Address system, Disco, Guitar, Gram., etc. Features 3 individually controlled inputs (each input has a separate 2 stage pre-amp.). Input 1, 15mV into 47k. Input 2, 15mV into 47k (suitable for use with mic. or guitar etc.). Input 3, 200mV into 1 meg. suitable for gram, tuner, or tape etc. Full mixing facilities with full range bass & treble controls. All inputs plug into standard jack sockets on front panel. Output socket on rear of chassis for an 8 ohm or 16 ohm speaker. Output in excess of 20 watts R.M.S. Very attractively finished purpose built cabinet made from black vinyl coated steel, with a brushed anodised aluminium front escutcheon. For ac mains operation 200-240 volts. Size approx. 12in wide \times 5in high \times 7in deep.



Special introductory price £28.00 \leftarrow £2.50 carriage and packing.

"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 11in \times 14in \times 1in deep. Weight 19oz. Power handling 20W R.M.S. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffles. Send S.A.E. for full details. Only £8.40 each + P. & P. (one 90p, two £1.10). Now available in 8in round version, 10 watts R.M.S. 60Hz-20KHz £5.25 + P. & P. (one 65p, two 75p.).

MAINS OPERATED SOLID STATE AM/FM STEREO TUNER



200/240V Mains operated Solid State F.M., A.M., Stereo Tuner. Covering M.W. A.M. 540-1505KHz V.H.F. F.M. 88-108MHz. Built-in Ferrite rod aerial for M.W. Full AFC and AGC on A.M. and F.M. Stereo Beacon Lamp Indicator. Built-in Pre-amps with variable output voltage adjustable by pre-set control. Max. o.p. Voltage 600mV R.M.S. into 20K. Simulated Teak finish cabinet. Will match almost any amplifier. Size 8in wide \times 4in high \times 9in deep approx.

Limited number only at £28.00 + £1.50 P. & P.

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-150 speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up, 2 EL84s, ECC83, EF86 and EZ80 rectifier. Simple instruction booklet 25p + S.A.E. (Free with parts). All parts sold separately. ONLY £18.00 P. & P. £1.40. Also available ready built and tested £22.00 P. & P. £1.40.

STEREO MAGNETIC PRE-AMP Sens. 3mV in for 100mV out. 15 to 35V neg. earth. Equ. \pm 1dB from 20Hz to 20KHz. Input impedance 47K. Size 1in \times 2in \times 5in H. £3.00 + 20p. P. & P.

Mullard LP1159 RF-IF module 470 kHz £2.25 + P. & P. 20p. Full specification and connection details supplied. Pye VHF FM Tuner Head covering 88-108 MHz 10.7 MHz I.F. output. 7-BV + earth. Supplied pre-aligned, with full circuit diagram with precision-ganged F.M. gang and 323PF + 323PF A.M. Tuning gang only £3.15 + P. & P. 35p.

SPECIAL OFFER

Slightly shop soiled radios by well-known manufacturer for AC Mains or battery use. MW and FM bands. Dynamic M/coil speakers, telescopic aerial and internal ferrite aerial. Earpiece socket for personal listening. Finished in attractive simulated leatherette.

Size 7H \times 9 3/4" W \times 4"D approx. Fully guaranteed. Bargain price of only £10.00 + £1.30 p&p.

SPECIAL OFFER LIMITED NUMBER ONLY

GOODMANS speakers, 6 1/2" 8 ohm, long throw, ceramic magnet, full range rated 10 watts R.M.S. (when fitted in enclosure). £4.00 each + 80p. P. & P. (P. & P. on two £1.20)

HARVERSONIC SUPERSOUND 10 + 10 STEREO AMPLIFIER KIT

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity integral pre-amp with Bass, Treble and two Volume controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for use with speakers from 8 to 15 ohms. Compact design, all parts supplied including drilled metalwork, high quality ready drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification. Power output: 14 watts R.M.S. per channel into 5 ohms. Frequency response \pm 3dB 12-30,000Hz. Sensitivity better than 80mV into 1 M Ω . Full power bandwidth \pm 3dB 12-15,000Hz. Bass boost approx. to \pm 12dB. Treble cut approx. to \pm 16dB. Negative feedback 18dB over main amp. Power requirements 35V at 1A.

Overall size 12in wide \times 8in deep \times 2 1/2in high. Fully detailed 7 page construction manual and parts list free with kit or send 25p plus large S.A.E.

AMPLIFIER KIT (Magnetic input components 33p extra) £14.50 P. & P. 80p

POWER PACK KIT £6.00 P. & P. 95p

CABINET £6.00 P. & P. 95p

SPECIAL OFFER—only £25.00 if all 3 items ordered at one time plus £1.25 P. & P.

Full after sales service. Also available ready built and tested £31.25 P. & P. £1.50

HARVERSONIC STEREO 44

A solid state stereo amplifier chassis, with an output of 3-4 watts per channel into 8 ohm speakers. Using the latest high technology integrated circuit amplifiers with built in short term thermal overload protection. All components including rectifier smoothing capacitor, fuse, tone control, volume controls, 2 pin din speaker sockets and 5 pin din tape rec./play socket are mounted on the printed circuit panel. Size approx. 9in \times 2in \times 1in max depth. Supplied brand new and tested, with knobs, brushed anodised aluminium 2 way escutcheon (to allow the amplifier to be mounted horizontally or vertically) at only £10.00 + 50p P. & P. Mains transformer with an output of 17V a.c. at 500mA can be supplied at £2.00 + 40p P. & P. if required. Full connection details supplied.

STEREO DECODER

SIZE 2" \times 3" \times 1" ready built. Pre-aligned and tested for 9-16V neg. earth operation. Can be fitted to almost any FM VHF radio or tuner. Stereo beacon light can be fitted if required. Full details and instructions (inclusive of hints and tips) supplied. £5.00 plus 20p P. & P. Stereo beacon light if required 40p extra.

Open 9.30-5.30 Monday to Friday, 9.30-5 Saturday Closed Wednesday. Prices and specifications correct at time of press. Subject to alteration without notice

HARVERSON SURPLUS CO. LTD.

(Dept. P.E.) 170 MERTON HIGH ST., MERTON, LONDON, S.W.19 Tel: 01-540 3985

A few minutes from South Wimbledon Tube Station

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

New Heathkit electronic test equipment course.

- Section 1. Analogue and digital meters.
- Section 2. Oscilloscopes.
- Section 3. Frequency generation and measurement.
- Section 4. Special measuring instruments.

New Heathkit car electrical systems course.

- Section 1. Electrical principles of the car.
- Section 2. Starting system fundamentals.
- Section 3. Car charging systems.
- Section 4. Accessories and body electrical.

Two new self-instruction courses from Heathkit. Based on step-by-step programmed instructions, they let you learn at your own pace in your own home.

Each course is complete and contains audio/visual material, text, and parts for 'hands on' experiments with the optional Heathkit experimenter trainer. So all you need is a cassette player and the will to learn.

Full details of Heathkit courses are available in the Heathkit catalogue, together with hundreds of kits you can build for yourself—computers, oscilloscopes, transceivers etc.... Send for your copy now.

There are Heathkit Electronics Centres at 233 Tottenham Court Road, London (01-636 7349) and at Bristol Road, Gloucester (0452 29451).

Registered in England, No. 606177.

Soldering Iron offer FREE



New Heathkit CI 1265 Digital Tach/Speedometer.

Push-button digital readout. Displays engine speed/rpm. Accurate to 1 mph or rpm variations of 100.

To: Heath (Gloucester) Limited, Dept. PE 6/79 Bristol Road, Gloucester, GL2 6EE. Please send a copy of the Heathkit catalogue. I enclose 20p in stamps. Please send a copy of the Computer Brochure. I enclose 20p in stamps.

Name _____

Address _____

N.B. If you are already on the Heathkit mailing list you will automatically receive a copy of the latest Heathkit catalogue without having to use this coupon.

When you receive your catalogue you will get details of this free offer.



The other two command letters are used in the following way. W allows a re-entry after the BREAK without clearing memory. A most thoughtful addition—if only for the reason that the BREAK key is placed far out to the right of the keyboard and very exposed. It is easy, after setting up a BASIC program to brush the BREAK key causing the screen to clear and D/C/W/M? to appear—pressing C at this point would delete the program completely. M is used to enter the machine code monitor and will be described later.

During text entry, the monitor moves a “dash” symbol (the cursor) across the screen to keep the user updated with his current writing position. “SHIFT O” may be used at any time to delete the previous character written—this causes a dash to appear permanently at that point to remind the user that, as far as the machine is concerned, the previous character has been deleted. Several such dashes imply the deletion of that number of previous characters; and SHIFT P deletes the whole line, writing an @ symbol and moving the cursor to a new line.

In this way editing may be performed on a line adequately but slightly awkwardly. A better way would be to actually remove the deleted character from the display and backstep the cursor.

As can be seen from the photographs, the display provides very large characters separated vertically by very little space; this tends to make the text less readable than the majority of VDU pictures. However, it allows a very cheap system of “character slot” graphics to be implemented on the system. 128 of the character-generator ROM's patterns are graphic characters—inaccessible from the keyboard, incidentally. This includes a rich variety of tanks, guns, gaming characters, playing-card suits, lines, blocks and many more, to be displayed during program execution. Due to the lack of space between the character rows, these join up vertically as well as horizontally to produce continuous patterns. Separate dots within the 8 × 8 matrix of each character slot cannot be lit separately, and hence the term “character slot” graphics as opposed to “point graphics”.

In addition, the top few TV lines of the top row of characters are rather indistinct as there is no delay and blanking at the start of each frame.

Most TVs find it easy to synchronise with the Superboard even though it produces 60Hz frame information for the US market: some adjustment of the vertical hold is often necessary. The 60Hz frame frequency (non-interlaced) provides one other slight drawback. Most TVs have badly smoothed d.c. rails, and a little 50Hz hum is always present—this tends to beat with the 60Hz frame frequency causing a constant jitter of the screen contents—more noticeable as the brightness control is increased.

As the display is memory mapped, the user may access it simply by “POKE”ing information into the RAM block (1K) dedicated to storing the screen's contents. As explained, many of these slots are undisplayed on an average TV screen. The monitor carefully starts each line of BASIC text 5 spaces in from the left on each line and uses only the top 26 lines in order to ensure that no information is lost during program development. The full screen is 32 characters by 32 lines, and most British TVs will show all the lines though not all the characters on each line. However, much of the software supplied for the Superboard uses all 32 lines of the display which actually covers less than the normal 625 lines of UK TVs.

It is clear that some considerable thought has been employed in providing a display capable of use in gaming and “animation” applications. This has been successful up to a point given the extremely low price of this powerful system—the designers have even included a monostable circuit to blank the video display each time the MPU accesses the VDU. This helps to prevent spurious noise from appearing on the screen during continuous use of the VDU.

SOFTWARE MONITOR AND PROGRAMMING

The above section contains a full description of the commands available to the user and below is described use of the two languages employed in programming the Superboard—BASIC and 6502 machine code.

The fact that the system offers the language BASIC to the user will undoubtedly be the prime reason for his buying this machine. It should be emphasised that this is no Tiny BASIC or in any sense a minimal version. It is a full 8K Microsoft BASIC and even includes the very useful DEF FN.

It was clear from the start that program execution was fast, but I was unprepared for the remarkable speed of calculation which became apparent. When reviewing the TRS80, I ran some standard (Benchmark) programs and carefully timed them for later comparison. Programs not concerned with arithmetic or scientific calculation ran in about 55 per cent of these times on the Superboard—not surprising as the TRS80 is known to have a slightly slow clock. However, the 6502 on the Superboard was clocked at 1MHz, and the 2MHz version would halve these times again. This is still interesting but unremarkable.

I then tried my scientific calculation program. A large number of intermediate results are required, and the TRS80 had run this program in 117 seconds. I typed RUN on the Superboard and pressed return. There was no time to notice the reading on my watch—it ran in 7 seconds! I tried re-running the program 20 times and even juggled it about—still 7 seconds. The original program had no print-out so I made it print all 500 intermediate results on the VDU—the time shot up to just on 15 seconds. At this point, I noticed that the actual chip on the board was the “A” version of the 6502—able to run at 2MHz.

Swapping a few wires around increased the MPU clock to 2MHz, and I was fascinated to watch the Benchmark program run in 3½ seconds—about 1½ seconds slower than the time quoted for its running on an IBM 370/115 mainframe computer. The speed of the Superboard rests entirely with the version of the BASIC interpreter included in its design, and not to any special feature of the 6502 for example—presumably Microsoft could do just as well on any other system, if they tried.

The BASIC statements may be typed in for immediate execution or, by giving them line numbers, may be written as part of a larger program for running later. In immediate mode, the computer acts like a super calculator—with responses to Sine and Cosine markedly faster than those of my Texas SR56 calculator. Any level of parenthesis is available along with all the usual BASIC scientific functions to a floating-point accuracy of 6½ digits and including the random number function.

The only omission I discovered in the repertoire worth noting was the PRINT USING statement. Otherwise, everything is there, including numeric and string arrays plus an excellent set of string-handling functions.

Memory efficiency and speedy programming are aided by omitting “LET” in assignments and using “?” for PRINT. Multiple statements are allowed on a single line by the use of a colon as separator. Variables may be two characters in length (the first must be alphabetic) and, with array variables, there are as many as could be wished for by the most voracious scientist.

The BASIC manual, as implied in the documentation, was not written as a primer. It is a quick-reference list for the knowledgeable user. In parts, it is a little too quick and even now I am unable to fathom out the use of the USR function which has the useful capability of being able to call machine code routines from a BASIC program.

LIST is one of the most important BASIC editing features. On the Superboard it is very versatile. “LIST 50-” and “LIST 50-100” will give a listing of a program from line 50 onwards and between 50 and 100 respectively; also, “LIST -50” gives the list up to line 50, and “LIST 50” gives line 50 alone. This is all very useful and appears nowhere in the manual!

The BASIC interpreter also supplies 17 stated error codes to assist in the debugging of programs. Each code is composed of a letter plus a graphic symbol for some reason. SYNTAX ERROR for instance, is denoted by S_ as opposed to the more usual SN. I also discovered one unlisted error code—B . This turned up after typing (in immediate mode) A(1000), among other things. Perhaps someone should run a competition to discover how many other codes, plus their access statements, exist—could be interesting!

It is certain that the first time user will find the documentation on BASIC, supplied with the kit, inadequate, and he is well advised to seek out one of the excellent primers on this subject best found from a local library or by browsing in the technical section of most sizeable bookshops. The language is easy to learn and will enable programming to quite a sophisticated level in an hour or two.

MACHINE CODE

The fact that the Superboard can also be programmed in machine code, via the machine code monitor, impresses me very strongly. It adds that touch of flexibility which is prevalent throughout the system's design. The machine code is accessed by typing "M" when D/C/W/M? appears on the screen after BREAK. This causes six characters to appear at top left of the screen—four hex characters for address, followed by a space, and two characters for the data contained at that location.

The commands available for program writing are rudimentary but adequate. Typing a full stop allows subsequent hex characters to load the address field of the display. The data field is kept updated during this process allowing the user to view the contents of any memory location. To load the data field, a "/" must be typed. "L" allows loading from the cassette and "G" causes execution of a machine code program starting at the current address displayed on the screen. The manual also gives the starting address, in the monitor, of several useful routines, thus allowing a very low level utilisation of the machine.

A user who wishes to write many machine code routines, perhaps for control purposes, would do well to write a sophisticated BASIC program, using PEEK and POKE, to aid the loading and construction of such routines.

CASSETTE INTERFACE

I had a little trouble loading both the standard and my own saved programs, at first—nothing serious, however, and a little experience with the tape-recorder's controls gave acceptable results most of the time. The cassette interface runs at about 300 BAUD and depends upon the constant crystal-controlled clock

of the whole system for both recording and retrieving data. This means that changes in tape speed will diminish performance more severely than would be the case if the retrieval clock were derived from the recorded data itself. Data is stored on the CUTS (Kansas City) standard of recording a low pitch tone for a logic zero and high for a one. Decoding one's and zero's from the tape depends upon the decay time of a monostable to distinguish between high and low tones—its time constant is adjustable, for setting up, by a subminiature pot on the board.

The software supplied with the board, on cassette, formed a strange mixture of games, educational programs, calculations and financial packages. Some of the tapes actually seemed to contain software errors—if the tape interface can be trusted—and one, at least, was complete rubbish. One or two of the games were good—particularly "New York Taxi" where the player has to hail a taxi without being run over; and "Hectic"—a game well outside my powers of speed and co-ordination—the display left me staring fascinated by the mayhem-like destruction implied by a spinning bomb which hurtles from random points in the sky and removes bits of the landscape.

There is also a Ratio Analysis program giving an idea of the machine's business capabilities, and one or two educationally useful teaching programs.

As a very rough guide to the speed of loading and size of programs, "New York Taxi" takes up about 2.7K of memory, occupies 81 lines of program and takes 2 minutes 20 seconds to load.

MANUAL AND EXPANSIONS

The user's manual is not bad but could do with re-writing in a more concise and logical form. Very complete circuit diagrams are included which appear, on the whole, accurate and well drawn; however, a little verbal explanation in this area would help the user to appreciate some of the finer points of design more easily.

The short section on BASIC and two pages describing the whole of microprocessor theory will leave the beginner mystified and the expert bored. Most of the facts appear somewhere in the quite lengthy text but are either laboured or under explained.

The final section is devoted to the 6500 series of MPU chips and their machine code. This is most useful for reference, but is entirely for the experienced.

The Superboard II, to give its full title, is the name given to the OSI 600 board, and may be incorporated into a special metal case with power supply to form the CHALLENGER 1P. The 610 board is an expansion p.c.b. containing 24K RAM and a floppy disk controller. Sockets are provided for dual mini floppy drives as well as a d.i.l.-plug terminated ribbon cable to plug into J1 on the Superboard. The 610 also interfaces to the 620 expansion board designed to run the OSI 48-line bus for the full range of OSI add-ons.

Expansion capabilities and flexibility of the basic p.c.b. are very varied—for instance, there is a link option on the board to enable the future use of a single 64K bit ROM for the BASIC interpreter instead of the four 16K bit ROMs supplied. This would free three 2716-pin-compatible sockets for other things. This type of detail will remain unused by the majority of users but tends to imply a high degree of thoughtful system design.

CONCLUSION

The machine described here is certainly one of the most exciting on the present market for both the hobbyist and anyone needing an introduction to computers in general and microcomputers in particular.

The video output is probably not fitted for business applications though the power of the machine may well be. The addition of an asynchronous video terminal and printer would, however, solve the problem quite quickly.



In a short time, the home computer man will learn the limitations of cassette storage in general and will begin to hanker after the yet largely unappreciated advantages of disk. Here again the Superboard provides the answer with a cheap plug-in floppy disk system.

The price of the Superboard puts it into a class of its own which is going to be very hard for the current purely machine-code systems to match. Its BASIC is nearly as powerful as, and faster than, that of the Tandy TRS80, for instance. It is, of

course, written by the same firm and takes up the same amount of ROM. The monitor on the other hand (half the size of the TRS80's) is less powerful in many ways but better in others—allowing machine code, for instance. The graphics and VDU, though more than adequate, are not up to the standard of the more expensive systems, however.

It is perhaps here, while discussing its comparison with a computer three times its price, that the finest compliment is to be found for this excellent innovation into the UK market.

As a consequence of the remarks in this article, COMP Components have designed and are producing a computer—The Compukit UK 101 (in kit form for £219 + VAT)—based on the Superboard but with many enhancements. These include up to 48 characters per line—with much clearer type and a superior character font with many useful technical symbols. The VDU will generate 50Hz frame information with a faster "dot" clock to produce a rock steady picture even through a modulator—which will be included on the board, as well as a regulated p.s.u. just requiring a transformer to make the system fully operational. Keyboard management will be much improved and include all the missing characters mentioned in Table 1.

Our contributor Dr. Berk will be writing a series of articles fully describing the design and construction of Compukit UK 101 and these should be published in P.E. commencing in the August issue, thus providing readers with a better Superboard at even lower cost.

Semiconductor UPDATE...

FEATURING : FRED IM 7224/5 DM 8678 R.W. Coles

FRED

To me, Fred will always be Fred Bennett, the previous Editor of our favourite electronics mag, and, incidentally, its founder. Well Fred, if you are reading this you'll be pleased to know that at long last your services to electronics have been officially recognised. They have named a series of semiconductor devices after you, so you can join the ranks of Hertz, Ohm, Ampere and all the rest!

Hang on a minute though, leafing through the FRED data sheet I find no unsolicited testimonial, only a bleak paragraph which informs me that **FRED** stands for Fast Recovery Epitaxial Diode.

Joking aside, the FRED is a device worth a second look. The name has been coined by Thomson-C.S.F., the French semiconductor house, and they have made a whole series of diodes available under the FRED banner. The diodes are intended for use as rectifiers in switching power supplies and the like, and they represent a big improvement on the traditional silicon diode design.

The need for these devices has been emphasised by the new power-supply-wonder-of-the-age, the D.O.L. (Direct-Off-Line) switcher. These power supplies get rid of the heavy iron transformer of traditional designs and make possible small, lightweight, regulated power packs in a fraction of the normal space.

The way they work is simple enough. Take a 230V a.c. input and half-wave rectify it to give a high d.c. voltage. Now chop up this d.c. supply into a high frequency . . . pulse train using transistors and then pass it through a small, lightweight, high frequency isolating and step down transformer. Finally, rectify in the traditional way, only use FREDs. To achieve voltage regulation, monitor the output voltage and use it to control the width of the pulses produced by the chopper transistors.

Easy isn't it, but as you can imagine the "high frequency" bit causes problems not only for the choppers, but also for the rectifiers. Old fashioned rectifiers are fine at 50Hz but at 20kHz? forget it. FREDs on the other hand have a low forward voltage drop, low conduction losses, high surge current rating, low reverse recovery time, low forward recovery time and are great at 20kHz. The range includes the BYW80 at 7 Amps, the BYW 81 at 12 Amps, the BYW 77 at 20 Amps, the BYW 92 at 35 Amps, and the BYW 78 at 50 Amps. Better luck next time Fred!

COUNT ON IT

You have probably seen the delectable Intersil D.V.M. chips, the ICM 7106 and 7107. Well now Intersil have done it again with a whole family of counters in the same image. Once again you can have a choice of l.e.d. or l.c.d. displays, but in addition you can choose either a 19999 full scale count or the 15959 timer variety. As usual, the chips drive their displays directly, and they'll run from five volt supplies too. CMOS technology is used, and so the **IM7224** l.c.d. version draws only 10 microamps at 1kHz and a miserly 1 milliamp at a full 10MHz! The **7225** l.e.d. version takes a lot more of course, or rather, the displays do. To get the 15959 versions, just add an "A" suffix. This new chip is going to be a big success, you can count on it!

DOTTY CHIP

Anyone who studied the excellent P.E. VDU SYSTEM series must have been impressed by the capabilities of the SFF 96364 TV controller chip which helped to make that low cost system possible. You may have noticed that in addition to the control chip, the system used NMOS RAMs, several TTL packages and a 24 pin

character generator ROM which contained the character dot matrix information for the raster scan display. If you are thinking of building this sort of system into, say, a home computer, you may be interested to learn that you can save quite a lot of board space and trade three packages for one if you substitute a National **DM 8678** for the existing 2513 ROM and two of its TTL support chips.

In the existing system, 6 bit ASCII character data from the screen RAM memory area is latched in a TTL 74174 register before being used to control the character select lines of the 2513 ROM. Output data from the ROM appears in parallel a row at a time, and has to be serialised in another TTL package, a 74165 parallel in/serial out shift register, before being applied to the modulator.

The DM8678 device replaces the two 16 pin TTL devices and the 24 pin ROM with a single 16 pin package. Not a bad trade! The pin reduction is possible because whereas the 2513 ROM had parallel inputs and outputs, the DM 8678 has parallel inputs but a serial output. The speed requirements of such a fast system can be met by the National device because it is a bipolar (not MOS) chip which is fully TTL compatible. The DM 8678 chip comes in a variety of optional forms which each contain a different character font. For compatibility with the P.E. system, the DM 8678 CAB is required because it has a 7 x 5 character dot matrix in upper case. Of course it would be very easy to add a lower case character facility to the system by using two DM 8678s, with some simple extra gating. In this case a DM 8678 CAH would be required.

If you really were cramped for space, another saving might be to substitute a single MK 4118 1K x 8 RAM for the eight 2102 S currently specified.



SOUND to LIGHT

BEN J. DUNCAN Pt.2

In this part constructional details will be given together with display techniques.

CONSTRUCTIONAL NOTES

If the PSU regulators' heatsink is mounted vertically, then the signal processing circuitry can be mounted on the rear, the heatsink then acting as a screen.

The inductors L1 and L2 consist of 500 turns of 19 s.w.g. enamelled copper wire, close wound in layers on a 200 x 10mm ferrite rod. Each layer should be covered with good quality p.v.c. tape, particularly the top layer. This reduces the likelihood of problems arising from damaged insulation.

The plastic regulators share a 2.1°C/W heatsink. The 7915 regulator must be isolated from the sink. The C106D thyristors are wired directly into the Zero Voltage Switch p.c.b., and are bolted to a 19°C/W sink, which should not be able to touch other components on the p.c.b.

The pulse transformers should be mounted so that their 2.5kV isolation is not negated (a good quality insulating base should be utilised).

The Triacs are individually mounted on isolated 2.1°C/W heatsinks. The holes should not be drilled until the size of the p.t.f.e. standoff washers is known. After drilling, carefully remove all burrs. It is most important that the stud nut is tightened slowly and not excessively, until the device is firmly held against the heatsink.

When mounting the above devices, there are three important considerations:

- (a) Use proper heatsink compound between mating surfaces, and use it in moderation. (b) Remove the anodisation from the heatsink where the device is to be mounted, but do this with great care in order to maintain a smooth mounting plane. (c) After drilling, remove all burrs and projections with a smooth cut file. The insulating properties of mica are easily destroyed by partial rupture and punctures resulting from rough metal surfaces. Great care must be taken to maintain a smooth heatsink surface for this reason.

The heatsink specified for the triacs will maintain their junction temperature at around 60°C at full load current. If very light loads are connected, the junction temperature will drop and this results in a decrease in gate sensitivity. To maintain reliable triggering, R5 and R6 may be reduced to

27 ohms. If further current is required, then additional pulse transformers could be wired in parallel. The load current at which triggering begins to fail cannot be predicted owing to the spread in triac sensitivities, but the prototype would drive a single 100W lamp. Gate insensitivity may also be corrected by judiciously increasing the junction temperature. This is achieved simply by adding more mica washers and/or omitting thermal mounting compound on one or more interfaces. The BTX 94 data sheet must be consulted and soak tests should be made to ensure that reliability is not reduced as a result of excessive temperature rise. If possible, the triacs should be selected for $I_{GT} < 90\text{mA}$, $V_{GT} < 2\text{V}$, hence avoiding the need for trial and error methods.

The low junction temperature achieved with the specified heatsink ensures reliability consistent with the adage "The cooler you keep the device, the longer it lives".

TRANSFORMER PHASING

Correct phasing of the pulse transformers is essential for reliable triggering. The gate pulse should be negative with respect to triac terminal MT1. Linking the anode and cathode of the C106 thyristor should cause the lamps to light. If this test fails, then either the zero voltage switch or the transformer phasing is in error. Prior to testing the unit, check that the pulse transformers are wired between the gate and MT1 triac terminals, and that terminal MT2 is wired to the live via the load. Also test the isolation between MT2 and the heatsink. Finally, thoroughly check the circuitry.

ALTERNATIVE VERSIONS

If power capacity is to be sacrificed for a lower cost, then the following substitutions may be made:

Component	Design Version (6.2A/channel)	Low Power Version (4.8A/channel)
Triac	BTX94-600	BTW37-600
Heatsink	2.1°C/W	4.0°C/W
High speed fuse	Ferraz 600.CP.AS.10.38-12	600.CP.AS.38-6
Slow fuse	5A, 1½ in. glass, 'quick blow'	3A, 1½ in. glass, 'quick blow'

A single channel version is another expedient economy. On the other hand more channels may be accommodated

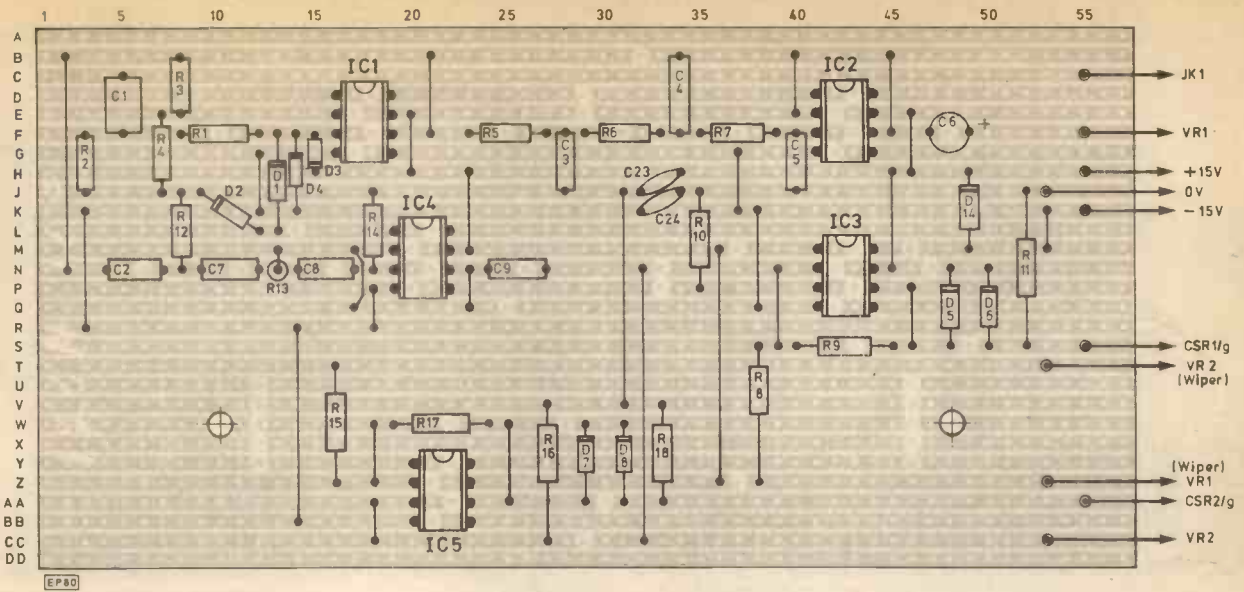


Fig. 6. Signal processing board

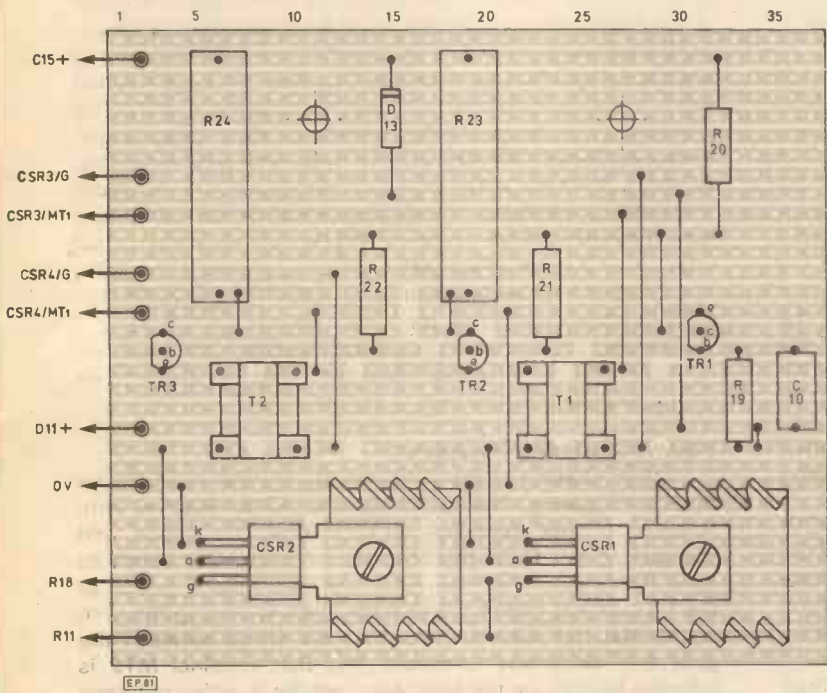


Fig. 7. Zero voltage switch board

with modifications to the signal processing circuitry. Steep bandpass filters, possibly based on cascaded low and high pass Chebyshev filters are required for an unambiguous display. In both cases, a pro-rata change in the rating of the power supply transformer and rectifiers is the only modification necessary to the remainder of the unit. The unit may be wired into 30A mains feeds with complete confidence. Higher current feeds are suitable provided the prospective short circuit current is under 900A. This value may be derived from the supply impedance. A simple method of measuring the latter parameter is to connect the largest allowable load to the feed. The difference between

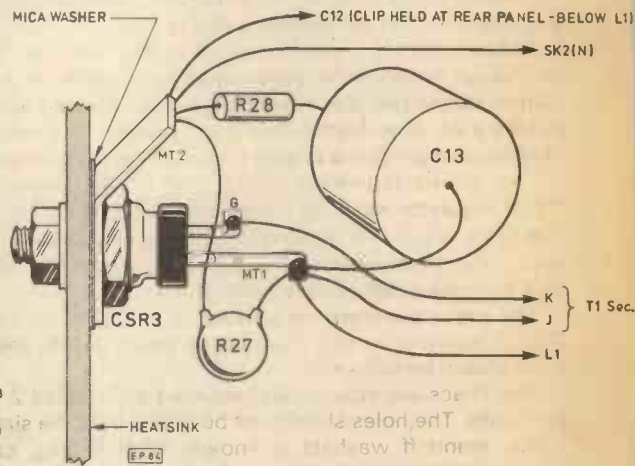


Fig. 8. Circuitry directly mounted to channel triac. Layout is similar for both channels

loaded and open circuit supply voltage will indicate the supply impedance reasonably accurately.

The use of loads in excess of 6.2A in the design version is limited primarily by lamp surge current. On certain mains supplies, where impedance is relatively high, one may well get away with greater loads. Under no circumstances however should the high speed fuses be subjected to currents in excess of 11.5A. This implies the use of a 7A fuse (If 1 1/4 in. glass) to protect the high speed fuse. As such a fuse is not available, and its use would significantly reduce triac protection it is recommended that the point where 5A 1 1/4 in. fuses start to go 'pop' is taken to be the safe limit.

Normally however, no problems will be experienced provided speaker cables are kept well away from mains cables connected to the SLM.

LAMPS

In order to minimise lamp filament failure rate and thereby avoid unnecessary loss of high speed fuses it is expedient to use single coil lamps, having longer life and more robust filaments. Inherently heavy duty lamps such as PAR 38 types are strongly recommended. Wherever possible, 240 or 250V lamps should be specified. If, say 230V lamps were used at a venue with a 250 volt supply, the 9 per cent increase in voltage over the nominal will shorten lamp life by 60 per cent. Using 250V lamps will of course entail a small loss in potential light output in most cases; 240V lamps are the best compromise.

Zero voltage switching, applying intermittent power (as in this application) and good ventilation also increase filament life expectancy. 100W lamps are the compromise between a large number of small lamps with low thermal inertia giving a responsive display but with high hardware costs, and a smaller number of high power lamps exhibiting a sluggish response. Thermal lag will significantly affect the character of a display, so experimentation is urged.

Stage lighting gelatines (Cinemoid) are a cheaper colour medium than coloured lamps and provide a wide range of colours of differing densities. No's 11, 18, 34, 41 and 46 are typically of optimum density for efficient projection. It has been stressed that good display technique is the crucial factor in successful discotheque lighting; operators who are seriously concerned with lighting display techniques should study stage lighting and carry out extensive experiments. Whilst the difference between theatrical (stage) and discotheque lighting in the applied sense is wide, the basic principles are similar.

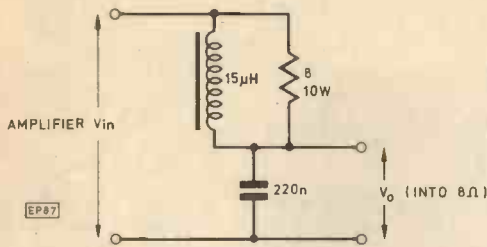


Fig. 9. Theile network

R.F.I. PROBLEMS

If r.f.i. is troublesome, assuming that the r.f.i. elimination routine has been dutifully followed, then the best course of action is to suppress at the point of pickup. This is usually sensitive audio circuitry. The use of a Theile network in power amplifiers prevents r.f.i. picked up in speaker cables being fed back to the input via feedback networks (Fig. 9). If unbalanced lines are used for interconnection, the use of balanced line cable is helpful. One of the inner cores is used for the return, and the screen is connected *at one end only*.

Earthing arrangements should be under suspicion, particularly mains earths. The SLM should ideally have its own, low impedance cable to the mains socket. In exceptionally difficult cases, copper screening may be employed. This should hermetically encase the power control circuitry. All mains cables should be screened with copper braid.

Audio circuitry power supplies should incorporate suppression chokes of the bifilar variety.


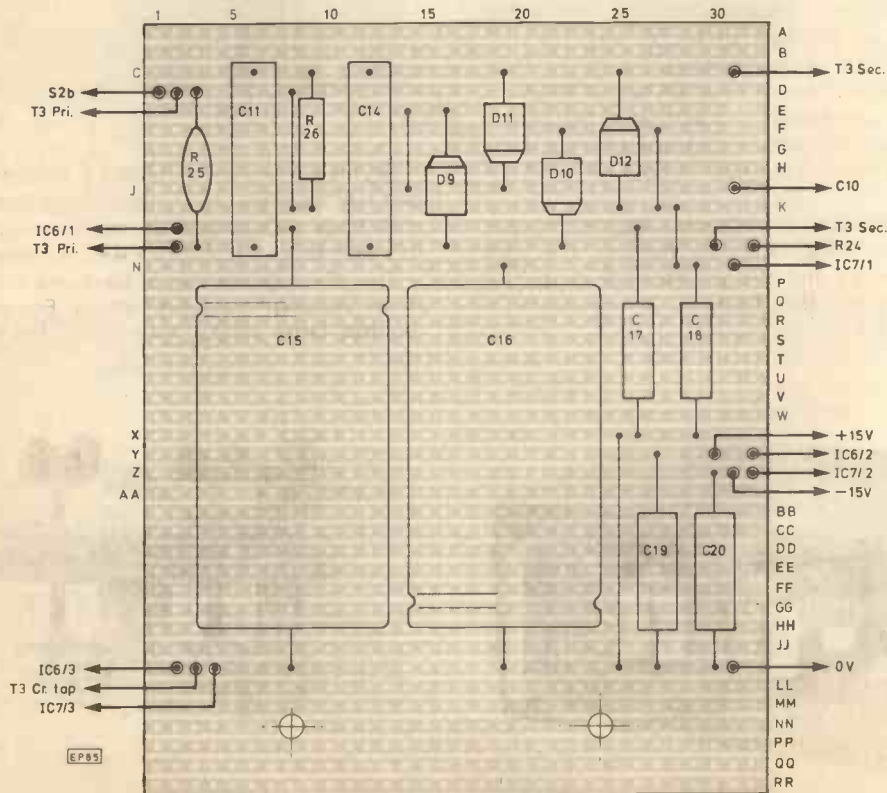
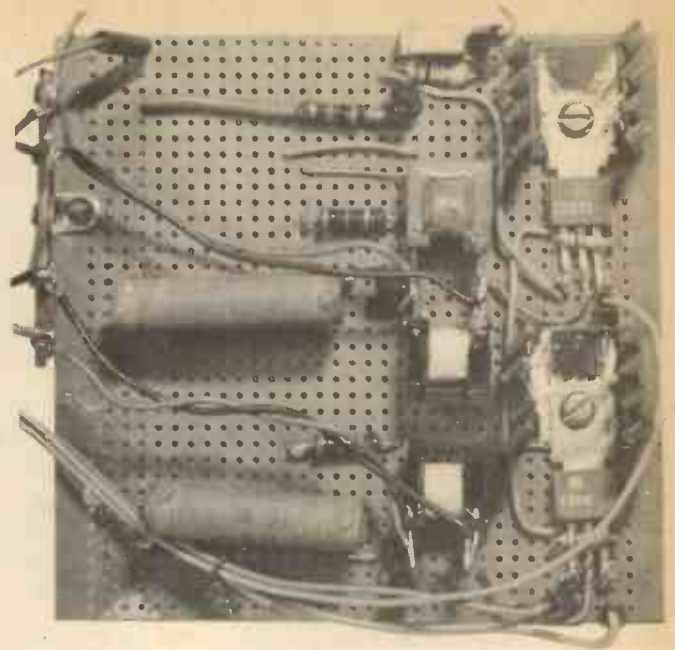


Fig. 10. Power supply board

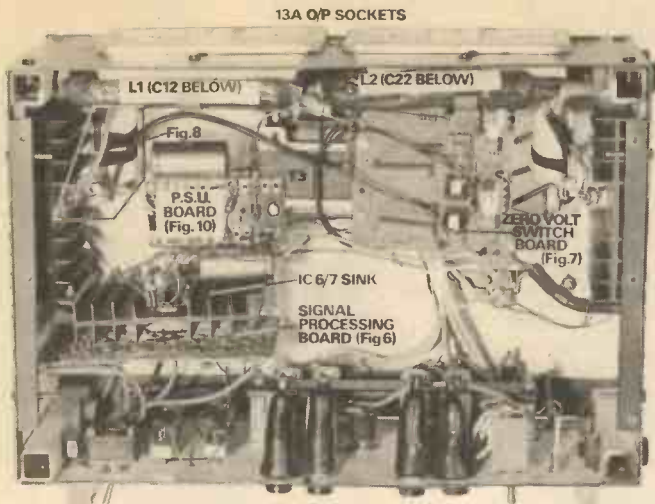


DISPLAYS

Displays are dichotomised by the two classes of music: those which are viewed and those which are experienced, appertaining to cerebral and physical music respectively. For the former, suitable "viewed" displays consist of lamps faced by coloured and patterned diffusion screens. Unfortunately, this display mode, in the form of "lightboxes" is common in discotheques, yet is *totally* unsuited to the enhancement of physical music.


A "physical display", in the same manner as physical music must "cry out for physical participation", hence a display which is "experienced". To achieve this, light must be projected. Of course, "lightboxes" project light, but the effect is weak and ineffectual, because they are not usually designed to act as an efficient projector they have a multiplicity of close seated colours project a mixed light which tends towards pale hues or even white and the light source is often in the line of sight and acts as a distraction, hence the rule of physical displays, (a) use efficient light projectors (b) project a minimal number of bold colours from discrete sources.

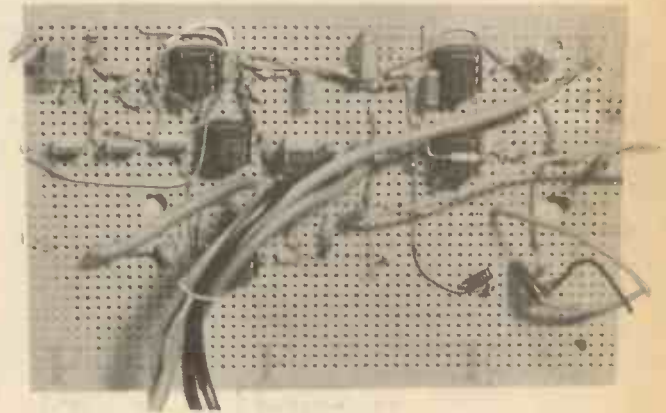Strategic placing of bass and treble displays causes violent oscillation which is stimulating. Remove the light source from the audience's line of sight. Ideally it should be overhead, but close to the floor is an acceptable compromise.



An idealised overhead display system based on rock concert techniques would consist of lighting units in steel boxes with hook clamps and parabolic reflector lamps, which in this case should be 100W PAR 38s instead of PAR 56s.

The direct opposition of bass and treble lamps gives rise to an exciting "cross-fire" effect. Equipment of this calibre requires large capital investment, but it is certainly worth

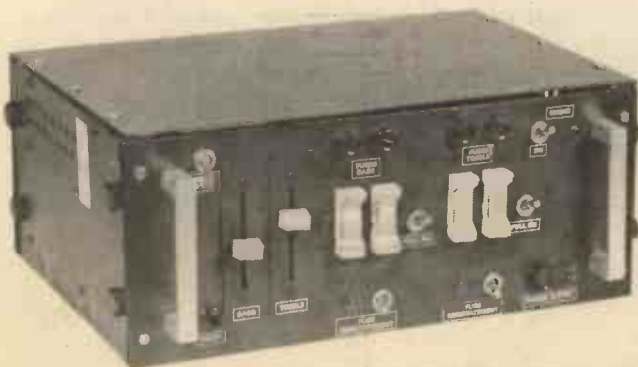

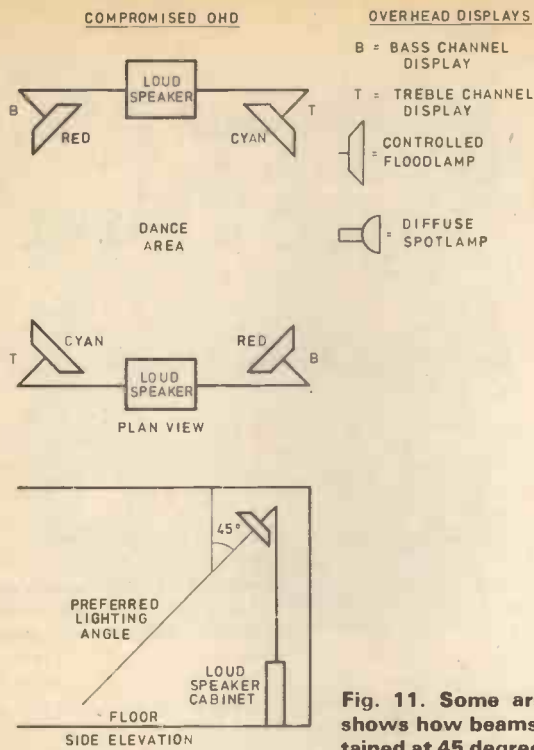


Fig. 11. Some arrangements for overhead displays (OHD). Directly above shows how beams from areas P and R will mutually interact. Lamps are maintained at 45 degrees and colours chosen to minimise this problem


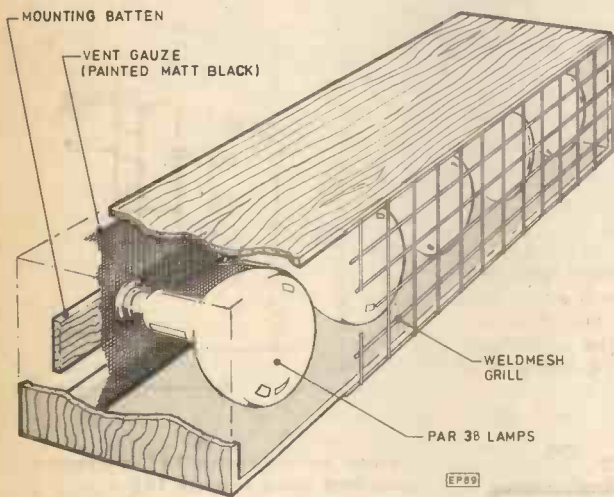


Fig. 12. Low cost projection box

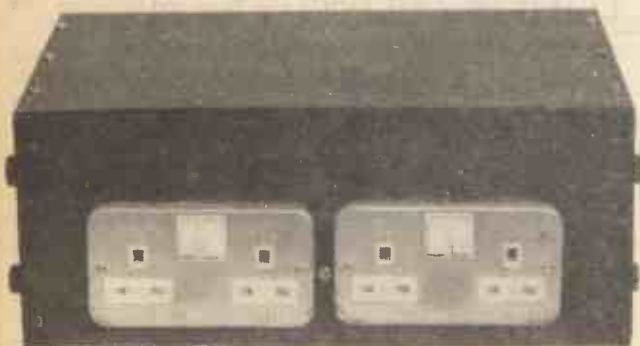

hiring it from PA hire contractors for special occasions.

A compromise arrangement suitable for small venues is shown in Fig. 11; setting up is rapid. Note again the arrangement of bass and treble lamps in order to give a cross-fire effect. The compromise between a large number of discrete sources which are costly and take a long time to set up and a small number which concentrate the light sources unduly is around 500W per box, made up of 5 x 100W PAR 38s.

PROJECTION BOX

The key details of a simple projection box are shown in Fig. 12 or 50mm grid x 8 or 12 gauge "Weldmesh" serves to protect the lamps and gelatine sheet which is pinned behind it; PAR 38s are however extremely tough and it may be omitted if desired. The lamps are mounted on a centre batten. Local power connection should be of butyl cable and brass holders should be used in order to ensure a long service life at high temperatures.

A fine zinc or aluminium mesh, matt black painted flush with the aforementioned batten will provide reasonable ventilation with minimal light leakage. When setting up an SLM or judging the aesthetic effect of a display, study the effect of the lighting on people rather than viewing the light source. The use of too many colours will only create an ambiguous, confusing pattern which defeats the object of using a two channel SLM. Stray white light can be troublesome and if elimination is impossible, exchanging the offending light source for a 60W "Fireglow" lamp is a reasonably diplomatic solution. Bear in mind that the location of floor mounted sources often defines the nucleus of the dance area in discotheque applications.

Finally, remember that the discotheque is primarily concerned with music and dancing. A good sound system is the first prerequisite; lighting is a secondary consideration, but lighting which stimulates dancing must be the foremost choice. ★

PATENTS REVIEW...


Copies of Patents can be obtained from :
the Patent Office Sales, St. Mary Cray, Orpington, Kent Price 95p each

TOUCH CONTROL

Fidelity Radio Ltd. of London NW10 in BP 1 513 562 propose a simple and cheap touch or tuning control for an amplifier or radio. It is suggested that the device can also be used to control lighting or power. The patent was applied for in early 1975 and is granted under the old laws.



A control panel carries two parallel strips, 2, 3, of conductive ink, which are printed by silk screen techniques. The strip 2 serves as a resistor and is connected at one end to a low voltage supply, e.g. 5 volts. The strip 3 offers negligible resistance. When a finger is placed as a bridge at any position along the length of the parallel strips, the potential at that position on strip 2 is applied to strip 3, i.e. the finger acts as the movable contact of a potential divider.

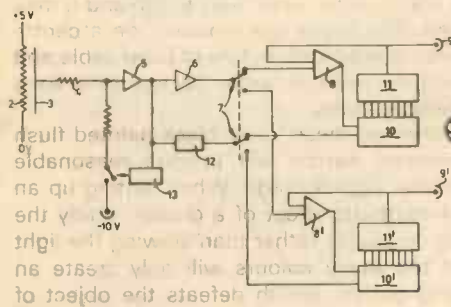

Strip 3 is connected to the circuit under control by resistor 4 which is incorporated to protect the circuit components against static discharge. Amplifier 5 connects to signal processing device 6 which removes any residual a.c. and supplies one input of a comparator 8.

The second comparator input is derived from output 9 and the comparator feeds an up-down signal to digital counter 10 so that the count changes as the potential at 6 varies with respect to the potential at 9.


Clock pulses for counter 10 are sourced from pulse generator 12.

When the potential at strip 3 is very low, i.e. when there is no finger contact, the output of amplifier 5 drops to a value which operates switching device 13 to connect the amplifier input to a fixed potential source (e.g. -10 volts). This drops the output of amplifier 5 further to establish a positive closed position of the switch 13 and de-activate the clock pulse generator 12. This ensures that spurious charges on strip 3 cannot achieve a control function. Counter 10 and an analogue converter 11 at the counter output together act as a store for the last sensed finger position on strip 3.

The output at 9 is used as a control signal, for instance to vary receiver tuning or amplifier volume.

ALARM HORN

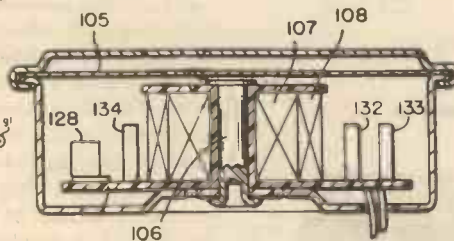General Signal Corporation of New York in BP 1 523 909 describes a simple but efficient horn design, suitable for generating an alarm tone. The patent was first applied for in late 1974 and thus is granted under the old laws.




The horn has a two part coil, inner or primary coil 107 being wound inside secondary coil 108 on the same core 106.

Primary coil 107 has five or six times the number of turns in coil 108 and the two coils are wound in opposite sense and in series. The magnetic fluxes generated by a common current are thus in opposition and the overall flux is equal to the difference between the two fluxes.

As the circuit shows the lower end of primary coil 107 is coupled to the collector

130 of a control transistor 128 and the upper end of coil 107 is coupled to the transistor base 129 via resistor 132.

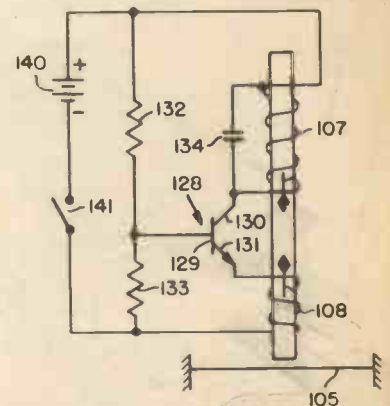The upper end of secondary coil 108 is coupled to the transistor emitter 131 and the lower end of coil 108 is coupled to transistor base 129 via resistor 133. Resistor 132 is approximately 10 times the value of resistor 133, the two resistors thus defining a potentiometer chain connected in parallel with the series connected coils. Capacitor 134 bridges coil 107.



When control switch 141 is closed d.c. flows from battery source 140 through the potentiometer chain to put transistor base 129 slightly positive with respect to the emitter. Transistor 128 turns on initiating conduction from collector 130 to emitter 131. Current now flows and capacitor 134 charges.

As a consequence of the turns ratio and sense of the coils a positive voltage is induced in coil 108 which reverse biases transistor 128. But current continues to circulate in the series RC circuit 107, 134 to dissipate stored energy. As the current and flux from coil 107 reduces, transistor 128 switches on and the whole cycle repeats.

A diaphragm 105 adjacent to the coils and core 106 will move with the flux to produce sound. The pitch of the sound produced will depend on the diaphragm resonance and component values. The patent suggests values suitable for generating a piercing tone of 2-2kHz.



VENUS 11 AND VENUS 12

The two Russian Probes released from Venus 11 and Venus 12 landed on the surface of the planet at points some 500 miles apart. Venus 11 was launched from Earth first and then four days later Venus 12 was also launched. However the flight path differed so that although Venus 11 was launched first it was sent along a different and rather longer path. Consequently Venus 12 was the first vehicle to arrive at Venus and release its probe. Four days later the second probe was on its way to the surface of the planet.

Both probes commenced a regular stream of data. The report of the temperature and pressure at the surface was to the effect that the pressure was of the order of 88 times that of the Earth's atmosphere, and the temperature in excess of 450°C. Each probe, during its descent, relayed information about the state of the Venusian atmosphere. Nine samples were taken and the result has enabled the profile to be modelled. There is close agreement with that of the American probes. The chromatographs have confirmed that the major constituents are carbon dioxide and nitrogen. The chromatographs at the surface have also detected carbon monoxide.

There is a significant point of interest about these chromatographs. Usually they are somewhat bulky pieces of equipment. In this case the "sigma" units were small and weighed only two pounds. With the data from the Russian units and that from the American mission the knowledge of the bright planet should be increased considerably.

TROUBLE FOR SCATHA

The United States Air Force satellite, which was designed for a project of special importance, the investigation of the electrical charges built up on spacecraft, has run into

difficulties. Since its launch on January 30 a power supply has malfunctioned and one of the transmitters gave trouble. A back-up instrument was brought into service but the data signals received back on Earth were not strong enough. The mission engineers felt that they could overcome the problem but this meant waiting for the period March/April when the vehicle was eclipsed. However this cannot help the "Light Ion" mass spectrometer which seems to have developed a short-circuit on one of the load resistors.

So far Scatha has had the experience of three charge conditions. One of these built up to -300V. These charges are thought to be related to geomagnetic storms stirred up by the Sun. The eclipse was not detected by Scatha. This was the total eclipse of February 26. The Field Detector experiment uses an antenna of 100 feet span. It consists of two fine wires attached at one end to the satellite and having a small mass at the other end. The rotation of the satellite, about 1 rpm, deploys the wires by "centrifugal" reaction.

The orbital characteristics are: apogee 43,225km., perigee 27,780km, an inclination of 8.3°. There is a drift rate of 6° east daily. The vehicle has a designed lifetime of one year.

UK-6 BRITAIN'S SPECIAL STARGAZER

UK-6 has the launch date of May 24 this year. A Scout vehicle will launch the satellite which will go into a high circular orbit. Originally it was intended that the altitude should be 550km. In fact the altitude will be 625km with an inclined orbit of 55°. This situation has been achieved by improvements in the Scout vehicle. In addition to the achieving of the greater height the lifetime of the satellite will be increased. It is expected that its life will be 3 years, but if the same nursing by the team who kept UK-5 in operation is available, the life will be extended.

It is predicted that there will be a period of intense solar activity at the end of this year resulting in the raising of the top limit of the Earth's atmosphere. There will therefore be the possibility of detecting particles which come from the Sun's corona. The inclination of the orbit was chosen in the interest of the cosmic ray detector. At the inclination of 55° the instrument will be able to scan through the Earth's magnetic field. This position however does reduce slightly the best achievable measurements by X-ray apparatus.

ALTITUDE CONTROL

The mass of the UK-6 is 155kg. The payload is about 40 per cent of the total, which is a high proportion. The satellite is spin stabilised. The altitude control is rather unusual, being based on a magnetic coil which encircles the base of the satellite body. When a current is passed through the coil a force is set up which enables the whole satellite to be precessed to another position. There is provision for passive thermal control and the solar array will be able to deliver 95W continuously to the end of its life. Batteries are available to provide power when the satellite is eclipsed.

The X-ray sensors are directed away from the Sun so that simultaneous observations may be made from Earth.

It is hoped that UK-6 will provide more data so that an even better assessment may be made of the manner in which stars are formed. There are three principal experiments on board and these will provide information on variable X-ray sources, low energy X-ray sources, such as the possible Black Hole Cygnus X-1 or the Crab nebula. There will also be information on the heavier nuclei of cosmic rays. These are suspected to come from the remnants of super-novae. These data will enable astrophysicists to understand more about how the radiation is produced and perhaps provide a clue as to formation or collapse of stars.

COSMIC-RAY DETECTOR ON UK-6

The cosmic-ray detector was supplied by a team from Bristol University. It is the largest of the experiments. It consists of a pair of concentric spheres 75cm in diameter. They are filled with a mixture of neon, helium and argon with traces of nitrogen. The mixture is maintained at a pressure of a little over one atmosphere. A battery of photomultiplier tubes surround the chamber and these observe any events taking place within. The outer sphere acts as a supporting structure. The inner which is made of plastic and contains a wavelength "shifter" is the working part of the detector. The designers believe that this will be the first instrument to accurately measure the rays formed from elements over a wide range, specifically from iron to uranium and possibly beyond. The action of the cosmic-ray detector is such that when a cosmic-ray, which is an atom that has lost its electrons, passes through the chamber it produces flashes of visible radiation, one each time it passes through the plastic sphere and one each time it passes through the gas mixture. This is the Cherekov effect which is observed by the photomultipliers. The detector is arranged so that several of the multipliers "see" each flash. The charge on the nuclei is measured as it passes through.

The second experiment which is designed for the investigation of low energy X-rays is a joint contribution by the University of Birmingham and the University College, London. The experiment has four gazing incidence X-ray reflectors which lead to proportional counters. These are intended to be pointed at possible X-ray sources, to allow detailed observations to be made. These studies will work in cooperation with ground based observation to ensure the accurate position fixing of the sources.

Leicester University supplied the third principal experiment and it is designed to observe the variable X-ray sources. The apparatus is similar to the University College and Bristol University experiment with the ability to observe rapidly varying sources.

Two minor experiments from the Royal Aircraft Establishment are aboard the satellite. One is a collection of new types of solar cells which are to be tested under space conditions and the other investigates how space effects metal oxide semiconductors.

SPECIAL OFFER!

L.C. DIGITAL ALARM CHRONO

£22.95

Including V.A.T. Postage and Packing

A quality watch at an unbelievable price.

This Lambda l.c.d. alarm chronograph comes with complete instructions, and a worldwide one year guarantee and service network booklet. It is shown full size on the front cover and this page and has the following functions.

Hours; minutes; seconds; date; day of the week; am/pm indication; stopwatch with 1/10 second readout, split time with automatic reset after six seconds and up to 13 hour capability; flashing stopwatch indication if time is displayed while stopwatch is running; bleeping 24 hour alarm which sounds for one minute unless previously cancelled, the display flashes while the alarm is sounding; alarm set indication; simple, "to the second", time and date setting; second watch including seconds, date, day of week and am/pm indication for displaying time in another zone; nightlight; screw section in back to enable quick, simple d.i.y. battery replacement; stainless case and black/stainless bracelet; fully adjustable bracelet to fit wrists from 130mm (5 1/8 in) to 200mm (7 7/8 in) circumference without removal of links.

The alarm is loud enough to wake most people and the dual time zone facility is very useful for foreign phone calls, whilst travelling or just on holiday.

We have been careful with the choice of this watch and have tested it for three months, since we anticipate heavy demand please allow a maximum of 21 days for delivery—more if you live outside the U.K.



Please complete both parts of the coupon in BLOCK CAPITALS

To: METAC Electronics and Time Centre (P.E. Offer)
67 High Street, Daventry, Northants. Tel. 032 72 76545.

Mail order only

Please send me watch/es at £22.95 each

I enclose P.O./Cheque No. Value

Name

Address


Please allow 21 days (maximum) for delivery (more for overseas orders)

OFFER CLOSES JULY 31, 1979

Name

Address

From: METAC Electronics and Time Centre (P.E. Offer)
67 High Street, Daventry, Northants.



EVEN the simplest form of sound track cannot be synchronised unless the projector speed can somehow be stabilised. This particular speed controller is designed to eliminate speed variations from any cause, and is entirely automatic in operation. It operates within very close limits and can be preset to run the projector at any desired speed. This version provides switching between 16 and 24 f.p.s. for a standard 8 mm projector. The 24 f.p.s. setting is used for showing silent versions of sound films.

The principle may be applied to any variable speed motor where some form of revolution detector can be fitted.

PRINCIPLE OF OPERATION

Pulses are derived from the projector using a photo-darlington and lamp, located on either side of the shutter blades (see Fig. 1). The pulses are fed to a Schmitt trigger to eliminate noise. The squared up pulses are then fed to a digital filter. The filter gives two low outputs if the frequency of the input pulses is within the passband. If the input frequency is above this band, point A goes high, and if the frequency is below the passband, point B goes high. The outputs A and B are used to drive an electronic switch which will charge or discharge a capacitor as appropriate. The voltage across the capacitor is amplified and used to drive an opto-isolator. The opto-isolator drives a triac switching circuit via a two transistor amplifier.

A digital filter is used, since it requires very few components and can provide a very narrow, sharply defined band width.

CIRCUIT OPERATION

Pulses from the photo-darlington are first cleaned up by the Schmitt trigger formed by TR2, TR3, R1, 2, 3, 4 and 5. Refer to Fig. 2. They then pass to the 4528 CMOS IC whose catalogue description is a *dual retriggerable-resettable monostable multivibrator!* In this application the two monostables contained within the i.c., are configured as a digital filter.

CINE SPEED CONTROLLER

M. YEOMANS

The pulses from the Schmitt trigger are fed into the two monostables via the leading edge trigger inputs. The time constants of the two monostables define the lower and upper limits of the passband. With the respective R set high, output pulses appear at Q for input pulses below the crossover frequency. For higher frequencies Q remains high. With R set low, the output at Q remains low.

IC1(a) defines the lower limit of the passband, so that below this band its Q output varies at the input frequency, setting R on the (b) circuit low for the leading edge of each new pulse, and therefore holding "Qb" low. Within the passband Qa remains high and Qb varies at the input frequency. Above the passband Qb remains high.

Components D1, D2, C3, C4, R8, R9 form low pass filters, so that the inputs to the switches can only be set high when Q and \bar{Q} are in steady states outside the passband.

The electronic switches are provided by one half of a 4016 CMOS quad bilateral switch i.c. The switches cause the capacitor C5 to charge or discharge according to the frequency of the input pulses, and the voltage is applied to the gate of the 2N3819 FET. The very high gate impedance ensures that the charge remains constant until the next operation of one of the switches. The i.e.d. is driven by TR5.

The LDR of the opto-isolator varies the current drawn by TR6 and TR7, and hence the current through the bridge rectifier. These components take the place of the variable resistor in the normal triac control circuit.

The control circuit is connected in series with the projector motor and its normal variable speed control resistor.

DESIGN PARAMETERS

For stable speed control and rapid response at switch-on without overshoot, an appropriate value for C5 must be selected. If C5 is too small, the motor speed will hunt about the desired value, since the effective time constant of the

speed controller is smaller than the reaction time of the motor. If C5 is too large the motor will take too long to reach the correct speed when switched on. The optimum value of C5 will depend upon the characteristics of the motor and the load presented by the projector, and is easily found by experiment.

CONSTRUCTION


The lamp and photo-darlington are mounted on a small piece of veroboard which is supported by a conveniently placed bracket adjacent to the projector shutter blades. The low voltage power supply is derived from the 8V a.c. projector lamp supply. All the leads, including those for the motor control circuit, are taken out of the base of the projector body to a separate box, mounted behind the projector on a common baseboard. This form of construction was chosen so that no physical modification of the projector would be necessary.

The low voltage circuits are mounted on two pieces of veroboard approximately 45 x 120mm. A third plain matrix board of the same size holds the a.c. circuitry and opto-isolator, and the three boards are mounted as a sandwich, using 6BA studding and spacing nuts, inside an aluminium box.

A single toggle switch provides switching for 16 and 24 f.p.s. Slower speeds may be obtained using the normal projector speed control. The control circuit is energised by switching on the projector and no other controls are necessary.

The layout and form of construction are not critical, apart from the need to ensure that the high voltage triac circuit is mounted separately from the rest of the components.

Using a variable speed cine projector can be very frustrating. Continuous adjustment may be necessary to keep the speed of the projector constant as the machine warms up, and the load on the take up spool varies.

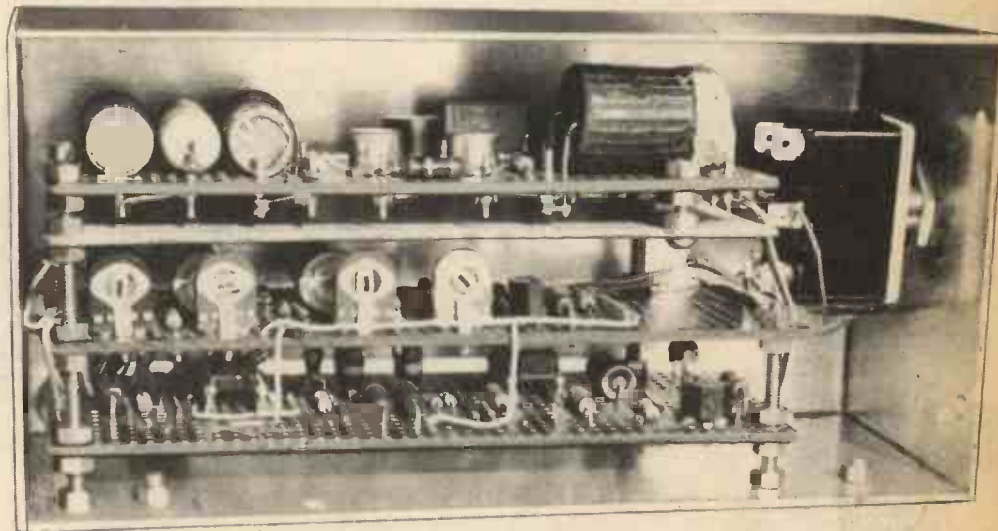

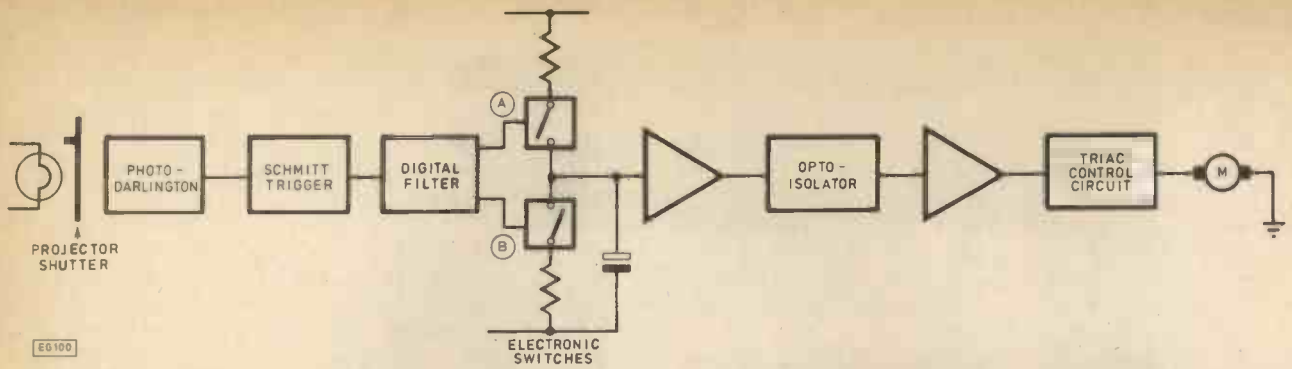


Fig. 1. Block diagram of Cine Speed Controller. Solid state switches are used to transfer the digital filter output to the integrating capacitor.

COMPONENTS ...

Resistors

R1	100k
R2	1k
R3	47k
R4	100k
R5	3k3
R6, R7	270k (2 off)
R8-R10	4M7 (3 off)
R11	2M
R12	3k9
R13	1k2
R14	22k
R15	390
R16	100k
R17	200k
R18	22
R19	1k5
R20	82
R21	47
R22	ORP12 LDR

Potentiometers

VR1-VR4 250k presets (4 off)

Capacitors

C1-C4	100n (4 off)
C5	4μ7
C6, C7	100n/400V (2 off)
C8, C9	100μ (2 off)

Transistors and Diodes

TR1	2N5777
TR2, TR3	BC147 (2 off)
TR4	2N3819
TR5	BC148
TR6, TR7	BF259 (2 off)
D1, D2	1N914 (2 off)
D3	TIL209
D4	BR100
D5-D8	full wave rectifier
D9-D12	400V p.i.v.
D13	BZY88C6V8
CSR1	T2800D


Integrated Circuits


IC1	4528
IC2	4016

Miscellaneous

L1, L2 55 Turns 28 s.w.g. 1½ x ¼ inch ferrite rod.
 LP1 miniature 5V incandescent bulb.
 S1 DPDT toggle switch.


Fig. 2. Full circuit diagram.

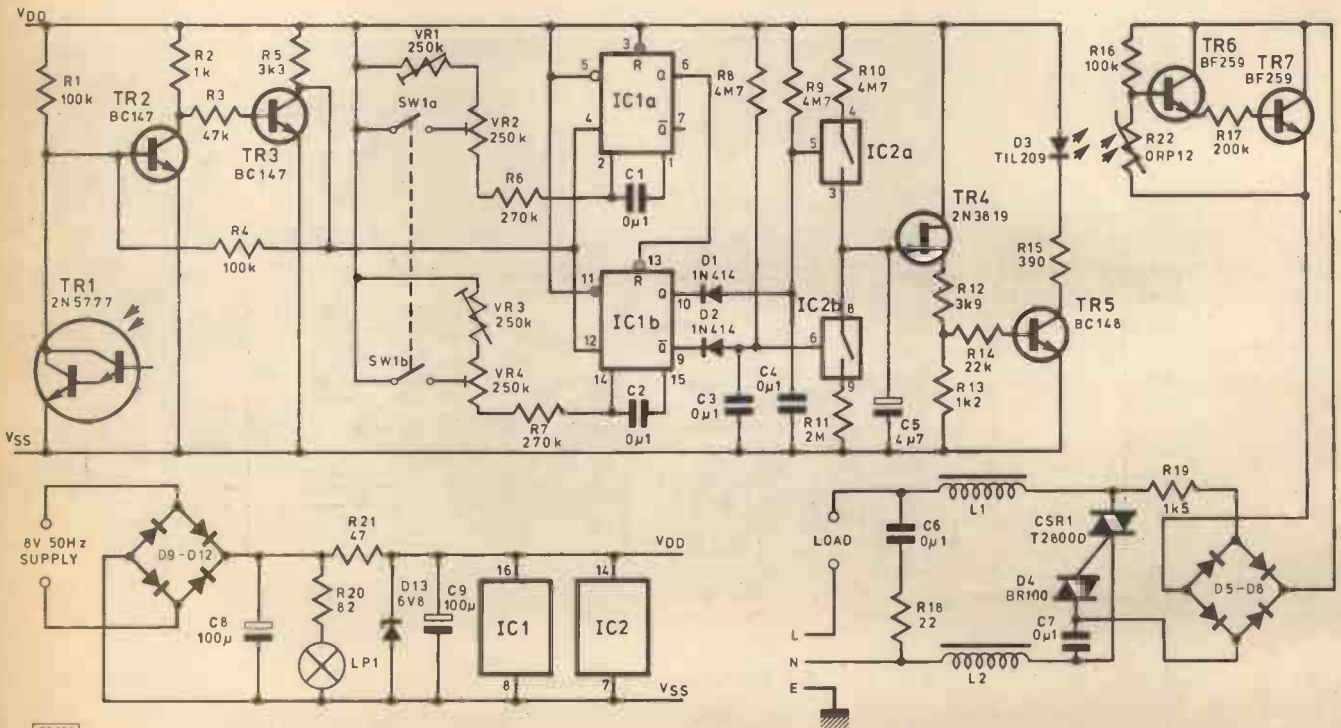

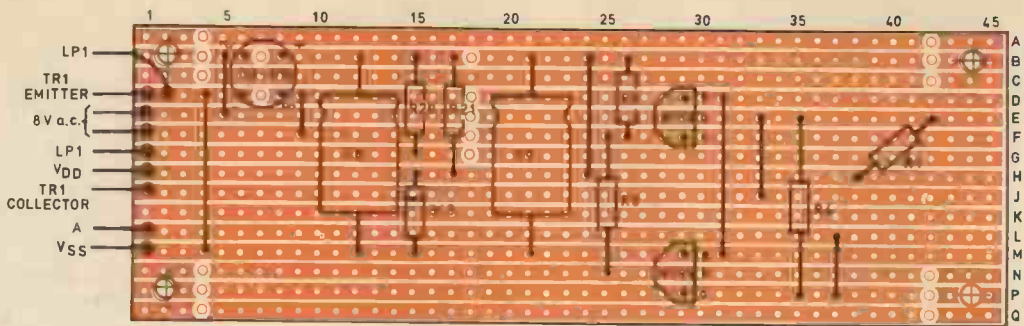


EG 113

Fig. 3. Supply Board.

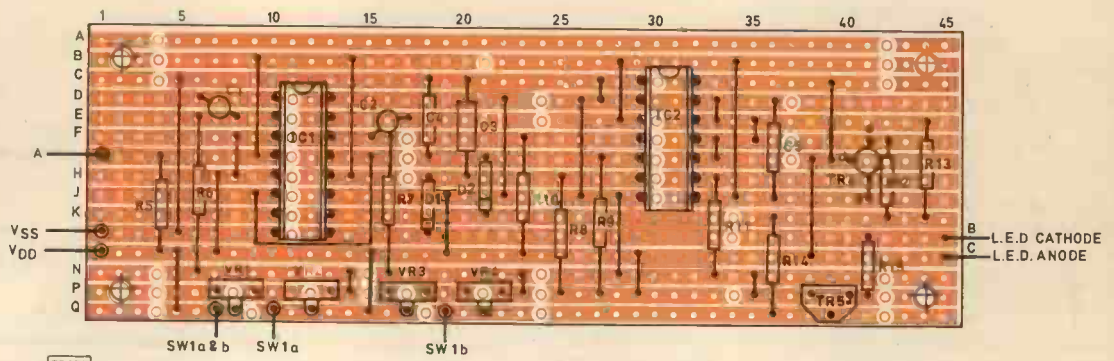


EG 114

Fig. 4. Main Board.

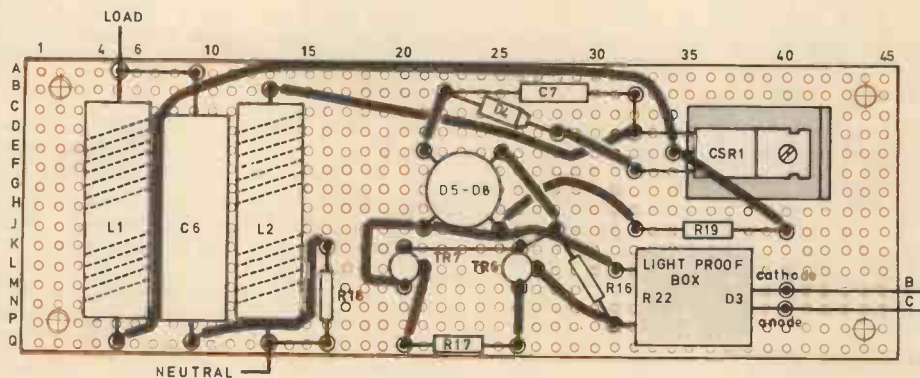

EG 115

Fig. 5. Mains Voltage Board.

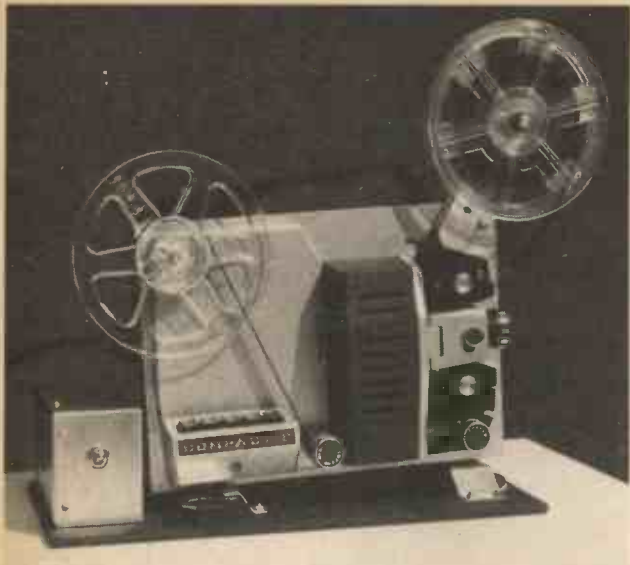

SETTING UP PROCEDURE

Apart from the selection of an appropriate value for C5, the only other adjustments required are the tuning of the digital filter. VR1 and VR3 have to be set to define the lower and upper limits of the passband respectively.

Some method must be used to indicate when the projector is running at the correct speed. A strobe disc on a convenient shaft provides a very accurate method of measurement.

With S1 set to 16 f.p.s., the passband of the digital filter is first set to its maximum by adjusting VR1 to its maximum, and VR3 to its minimum value. The normal speed control is set to *fast* and when the projector is switched on, C5 will be uncharged and the motor speed will rise to the top of the passband. VR3 is now increased, bringing down the motor speed until it reaches a value fractionally above 16 f.p.s. The



top of the passband is now set. If a load is now applied to the projector by grasping the take-up spindle, the speed will drop. VR1 is decreased until the motor speed has risen to a value fractionally below 16 f.p.s. The bottom of the passband is now set. Further fine adjustment of the two resistors may now be made as necessary to achieve the minimum passband. S1 is then set to 24 f.p.s. and the procedure repeated with VR2 and VR4.

CONCLUSIONS

There is no *simple* electronic solution to the accurate control of a variable speed motor, but with the right time constants and the band width correctly set up, this solution works extremely well! It provides a stable projector speed which is totally independent of motor temperature or load. No modification of the projector was necessary and no additional power supplies are required. With a common base board, the projector and speed control are completely portable. At last the projectionist can watch the film instead of the projector. ★

News Briefs

by Mike Abbott

COUNTDOWN

Muirhead '79—May 15-16. Muirhead is a company which specialises in communications technology and servo control systems, and the exhibition and symposium will take place at the Glaziers Hall in London. Further details: Mrs. P. Boreham on 01-650 4888.

The first All-Electronics Show/Seminex, Scotland, will take place on May 15-17, 1979, at Edinburgh's Assembly Rooms. Some 68 exhibitors were listed at the time of writing. Details: Saffron Walden 22612.

Welsh Amateur Radio, TV, Electronics and Computer Exhibition—Sunday, May 20. Barry Memorial Hall. There will be trade, and bring-and-buy stands. Further details: Reg Knowles on 0222-565656.

Midlands Breadboard—May 23-26. Bingley Hall, Birmingham. Details: Trident.

Intel Fair—June 11, 1979. Wembley Conference Centre. Details to be announced.

Tranducer 79 + Testmex 79—June 19-21. Wembley Conference Centre. Details: Trident.

Great British Electronics Bazaar—June 28-29, 1979. Alexandra Palace, London. Details: 0799-22612.

1979 Microcomputer Show (incorporating the DIY Computer Fair)—July 5-7. Bloomsbury Centre Hotel, London. Will include seminars. Further details: Online Conferences Ltd. Tel: Uxbridge (0895) 39262.

Consumer Electronics Symposium—July 8-11, 1979. University of Essex. Organised by the Society of Electronic and Radio Technicians. Details: The Symposium Office (CE), SERT, Faraday House, 8-10 Charing Cross Road, London, WC2 0HP.

The International Word Processing exhibition and conference will take place July 10-13, 1979, at the Wembley Conference Centre.

Word processing is having a dramatic effect on business procedures, and this event, which is claimed to be the largest in Europe, will display "virtually every available system and piece of equipment".

Details: BETA Exhibitions, Business Equipment Trade Association, 109 Kingsway, London WC2B 6PU.

Harrogate International Festival of Sound—August 18-19 (public), August 20-21 (trade) 1979. The Exhibition Centre + hotels. Details: Exhibition and Conference Services Ltd., Tel. 0423-62677.

Telecom '79—September 20-26. Palais des Expositions, Geneva. Details: Secretariat Telecom '79, Orgexpo, 18 Quai Ernest-Ansermet, Case Postale 65. CH-1211, Geneva 4 (Suisse).

Eltro Hobby '79—October 3-7. Killesberg Exhibition Grounds, Stuttgart. Details: 01-236 0911.

Compec—November 6-8, 1979. Grand Hall Olympia, London. Details: Iliffe Promotions Ltd. Tel: 01-261 8437/8.

Electronics 79—November 20-23. Olympia, London. Details: 021-705 6707.

Breadboard 79—December 4-8. Royal Horticultural Halls, Westminster. Details: Trident International Exhibitions. Tel 0822 4671.

IEA/Electrex—February 25-29, 1980. National Exhibition Centre, Birmingham. Details: Industrial and Trade Fairs Ltd. Tel: 021-705 6707.

All-Electronics Show (1980)—April 29-May 1. Grosvenor House, London. Details: 0799-22612.

News Briefs

BRITISH SATELLITE

by Mike Abbott

THE FIRST all British amateur satellite is to be built at the University of Surrey, co-ordinated by the Telecommunications Research Group within the Department of Electronics and Electrical Engineering. The satellite's purpose and proposed features are a departure from the international OSCAR series, in that it will provide practical experience in developing an inexpensive UK spacecraft programme, and will feature a series of high frequency beacons, enabling radio amateurs worldwide to study the changing effects of the ionosphere on radio signals.

Collaboration will involve the university's Electronics and Amateur Radio Society (EARS), the Amateur Satellite Corporation (AMSAT), AMSAT-UK, and the Radio Society of Great Britain. Many companies such as Racal are to give active support.

Priority will be given to telecommand and other fundamental services, but complex experiments are anticipated, to be undertaken either by the university or amateur groups in this country. With a possible launch opportunity in early 1981, the satellite is intended for a polar orbit at an altitude of 900km.

These satellites house VHF and UHF receiver/transmitters which allow radio amateurs to extend the range of their transmissions in the same way television programmes are relayed around the globe.

With the fault which developed in OSCAR-6 causing it to switch on and off unexpectedly, extra command stations were set up in Canada and Australia to control its use. Lacking in a similar facility, indiscriminate use by European radio enthusiasts threatened the satellite with drained batteries, and to counteract this EARS set up the only command station in the world, run (to this day) by students.

The EARS command station has since 1974 commanded successive OSCAR satellites while in orbit over Europe.

MARSHALL'S BRISTOL MOVE

DUE TO expansion, Marshall's have now moved from Fishponds Road, Bristol, to 108A Stoke's Croft, which is approximately five minutes' walk from the main shopping centre.

POINTS ARISING

TRS 80 REVIEW (April 1979)

Unfortunately some errors appeared in the programs given in the TRS 80 review. The programs should read:

```
PRINT((389*14.761)↑ 8.7)*SIN(0.87)
```

```
10 CLS
20 FOR X = 129 TO 191
30 PRINT X; " "; CHR$(X);
40 IF INT((X-128)/9) = (X-128)/9 THEN PRINT: PRINT
50 NEXT
```


METRONE (September 1978)

If the unit does not operate correctly, swap the two gates IC3d and IC1d so that IC3c is driven from IC3d. D3 should be 7-5V.



PHASER (April 1979)

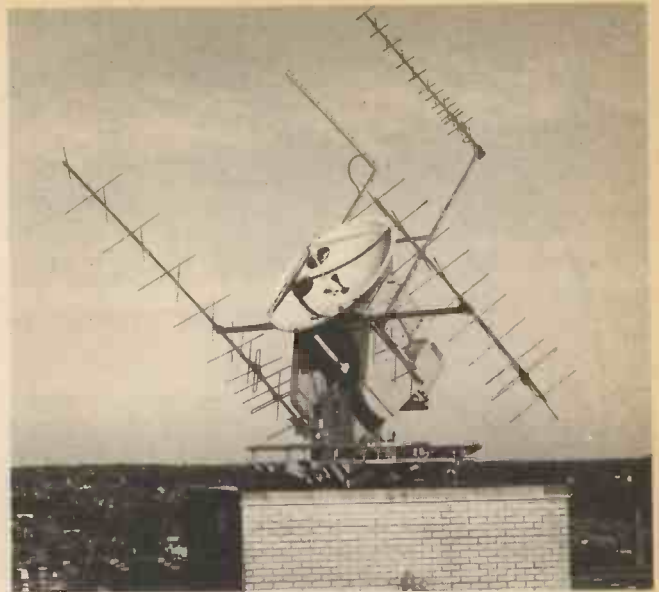The pin connections for the BF244B were incorrectly given in Fig. 2. The correct connections are shown above.



The command station at Surrey University has a steerable aerial complex capable of tracking to an accuracy of 0.5 deg, using an ex-Admiralty 2-metre paraboloid, and a tracking mount which was originally part of a Bofors anti-aircraft gun.



CHAMP-PROG (April 1978)

Fig. 8.2. D1 should go to pin 15 on IC1, and C2 should go to pin 14, IC1. Also, pin 2 should connect to pin 12 of IC1 and not pin 5. The timing capacitor of IC3 (C6) should be 47nF. TR20 configuration should conform to that of TR19-26. The connections to pins 1 and 3 of the PROM socket should be interchanged.

Fig. 8.5. These waveforms may seem to be upside-down, but are in fact correct. See Readout September 1978.


If the supply over-voltage protection circuit triggers unnecessarily due to the regulator's slow response at switch-on, reduce the unregulated input voltage to 72 volts.

The data bus should not be taken from the transistors of CHAMP, since they perform an inversion, but direct from the CHAMP data bus.

The circuit around D22 and S1 should be wired as below.

AUTORANGING MULTIMETER (May 1979)

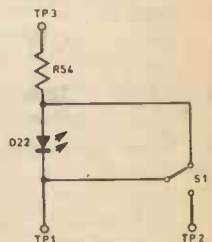A printing error has placed the green wiring overlays in Figs. 2.8 and 2.9 about 5mm "North West" of their intended positions. Correct registration can be recognised by noting that wires 1 to 5 should go to the wafer poles (below mounting lugs).



Market Place


Items mentioned are usually available from electronic equipment and component retailers advertising in this magazine. However, where a full address is given, enquiries and orders should then be made direct to the firm concerned. All quoted prices are those at the time of going to press.

by
**Alan
Turpin**

and
**David
Shortland**

STORING AND DISPENSING

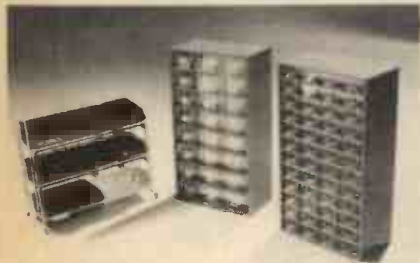If you are not a smoker who stores components in 2 oz. tobacco tins you may be interested in one of Verospeed's smart multi-drawer units. They are available in 24 and 48 drawer sizes. The drawers are easily labelled and dividers are available in packs of ten.



Also shown is a component dispenser for small production runs. It has three rows of picking bins of varying widths.

Multi-drawer units are £16.80, plus VAT, inc. p&p. The component dispenser is £5.52, plus VAT, inc. p&p. Bins, from 38p to 92p.

Verospeed, Barton Park Industrial Estate, Eastleigh, Hampshire, SO5 5RR. (0703 618525).

IRONS AT EXCLUSIVE PRICES


A company offering Litesold irons at reduced prices has just been set up. The company, called Future Electronics, is advertising the irons exclusively to P.E. readers.

The Litesold Model 15, 12W iron, fitted with a 1/16in. bit, operating at 360°C and weighing 14.9gms is available at £3.90 inc. VAT and p&p from Dept. MA1, Unit B1, Park Hall Trading Estate, Martell Road, London SE1. (01-761 3919).

MINI CASSETTE DECK

The CM600 miniature cassette system is a completely self contained unit measuring only 76 x 76 x 64mm and has been designed specifically for digital applications. With the drive motor, read/write amplifiers and control circuitry all included in the unit it only requires a 5V power supply for operation.

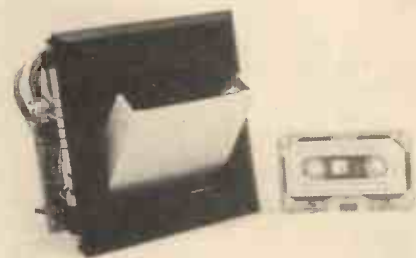The CM600 has a two track recording head which produces a maximum recording density of 800 bits per in. and a data rate of 2,400 baud. Data capacity on a standard 100ft miniature cassette is 1.6M bits. The reel to reel drive system has a forward search speed of 5 i.p.s. with a rewind speed of 15 i.p.s. and a stop/start time of 150ms.



Operation of the system is controlled entirely by external logic signals. Typically these represent tape direction (forward/release), tape motion (stop/go), tape speed (fast/slow), select read/write and data input. Output lines carry data and indicate which side of the cassette is being used.

The price of the CM600 is £110 plus VAT and p&p.

BFI Electronics Limited, 516 Walton Road, West Molesey, Surrey KT8 0QF. (01-941 4066).

DISPLAY CONSOLES

The new range of easy access display consoles from Boss Industrial Mouldings offers the option of either a satin black aluminium display panel or red, green or neutral grey, translucent filter windows if illuminated displays are to be used.

The contoured sides of the BIM7500 series are 12.7mm thick, solid oiled walnut, with textured sand finished exterior panels, the top one being 1.2mm thick steel and the keyboard panels being 1.6mm thick aluminium.




The consoles are available in nine sizes offering the combination of 4 keyboard panel widths and overall sizes ranging from 250 x 260 x 112mm high to 500 x 431 x 200mm high with the larger sizes having a fully hinged upper section.

The exterior panels of all models are quickly detachable on removal of two or three concealed screws to enable rapid component accessibility.

The consoles vary in price from £38.44 to £81.54 excluding VAT and p&p. For further information contact Boss Industrial Mouldings Ltd., Higgs Industrial Estate, 2 Herne Hill Road, London SE24 0AU.

P.C.B. TERMINAL BLOCKS

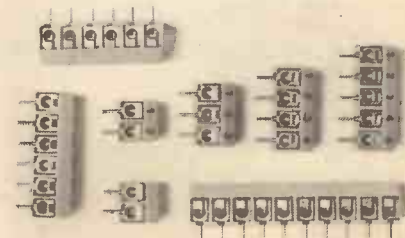A range of p.c.b. mountable terminal blocks from two to 12 ways is available from Carrier Electronics. The pins are on a 5mm pitch or two pitches of 0.1in matrix board. Wires up to 1.5mm² are accepted in a nickel plated brass bush with screws clamping on to captive phosphor bronze wire protectors. The terminals have a 13A continuous rating.




Prices range from 18p for two way to 74p for 12 way, plus, VAT at eight per cent, and postage.

Carrier Electronics Ltd., 48 Chester Street, Wrexham, Clwyd. (0978 56671).

ELF II

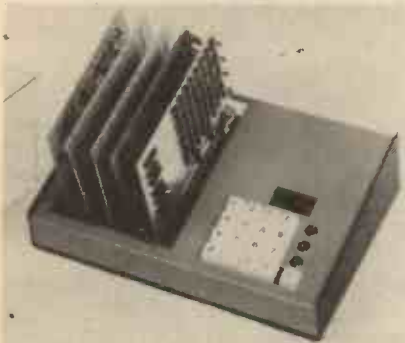The Elf II microcomputer kit is based on the RCA1802 8 bit microprocessor. The basic system includes a 256 bit RAM expandable up to 64K, a fully decoded hex keyboard and a 5 slot plug-in expansion bus (less the 86 pin connectors). The system is mounted on a double sided plated through p.c.b. A 1861 video i.c. is also supplied to enable segments of the memory to be displayed on a TV screen.



Also included in the basic kit is an owner's manual and complete instructions for assembly and testing. A power supply is available for £5.00 together with a complete range of expansion modules, including a fully encoded ASCII keyboard.

The basic Elf II kit is available from £99.95 with a steel cabinet and plexiglas dust cover for an extra £29.95. All prices are exc. VAT and p&p. *P.E. will soon be reviewing this kit.*

HL Audio, 138 Kingsland Road, London E2 8BY. (01-739 1582).

KEYBOARD KIT

This keyboard kit has a 7 bit parallel ASCII encoded output with dual polarity strobe edges and it can generate both upper and lower case ASCII codes. The unit has a power requirement of 5V 120mA and features long keystroke (3mm) keys throughout. All the keytops have removable transparent caps suitable for special legends if required.



The overall size of the keyboard is 290 x 140 x 25mm and it is priced at £28.50 plus VAT and p&p.

Video Terminals, 197 Hornbeams, Harlow, Essex. (0279 30132).

PSUs

The TPS range of precision bench power supplies consists six high accuracy dual and single output units from 0-30V, 1A up to 0-60V, 2A.



Although they are similar, the six units in the range offer different specific features: Three of the range are dual output units, with the facility to connect in series and parallel to effectively double the voltage or current ratings and all the outputs have a regulation of less than 0.5mV variation. With a ripple and noise figure of less than 0.5mV r.m.s.

Four of the units have an additional 5V (1 or 3A) output facility, allowing users to power logic circuits without connecting to the principal output terminals. The separate 5V feeds may be finely adjusted by an internally mounted trimpot.

Output voltage on all types is adjusted by a 10-turn potentiometer mounted on the front panel, and this allows setting to be carried out to within 5mV. Similarly, current trip adjustment is made using a single turn potentiometer. The moving-coil meters provide reading accuracy better than 2 per cent f.s.d., and on one model—the TPS 21D—these are replaced by l.e.d. digital readouts.

The prices of the TPS range are from £108.55 to £254.42 plus VAT and p&p.

Gresham Lion Limited, Gresham House, Twickenham Road, Feltham, Middlesex TW13 6HA. (01-894 5511).

CASIO CALENDAR

The Calendar 200 from Casio is a liquid crystal quartz digital wristwatch that displays the time, date or calendar page for any month of the year. The calendar display is a new idea from Casio whereby the information is presented like a conventional calendar page accompanied by a large digit representing the number of the month and an indicator showing the position of the Sundays. Automatic leap year conversion is programmed in.



Recommended retail price is £84.95 including VAT. For further information contact **Casio Electronics Co. Ltd., 28 Scrutton Street, London, EC2A 4TY. (01-377 9087).**

CHILTERN IMPACT PRINTER

The new type 150 Numeric Impact Printer has been specifically designed for the digital instrument market. The instrument has eight active columns as standard with facility to expand to 15 columns if required. Each column has 12 characters with 0 to 9 with a dash and dot format and two extra columns have assorted symbols.



The standard interface is parallel TTL CMOS DTL compatible with optional inverted logic by selection and manual or remote control of all functions. An optional bit parallel character serial interface is available as is a line buffer giving up to four lines of storage.

There are optional clock/calendar and serial event counter cards available with the unit and for specialised print functions an IEEE/488 interface.

For further information contact **Chiltern Data Systems Ltd., Stoke Row, Henley-on-Thames, Oxon, RG9 5RB. (049-17 549).**

PLAY IT AGAIN CASIO

What more could you want a calculator to do than calculate, tell the time and ring alarms? Casio think a tune playing function may fulfil a need. Their Melody Card, M-80, is just slightly larger than their recent credit-card size series.

Digits 1 to 8 are labelled Do to Dò, digit 9 gives one note above that octave, and the decimal and zero play the two notes below it. Thus you can play the one note samba and more.



A digit "key" will play its note as long as the key is pressed. Tunes of up to eight notes can be stored in memory. Even the timer alarms can be made melodious.

The recommended retail price of this threat to the Stylophone is £29.95. It can be bought by post at £25.95, inc. VAT and p&p. from **Timetron, The Beaumont Suite, 164-167 East Road, Cambridge CB1 1DB. (0223 67503).**

Microprocessor Evaluation System

PART TWO

D.S.COUTTS

THE complete development system was mounted into a 380 x 200 x 100mm case which was drilled as shown in Fig. 2.2. and then covered with fablon. The switches and l.e.d.s were fitted to the front panel taking care to place the anode pin of each l.e.d. at the top. The on/off switch, two DIN sockets, fuse holder and a grommet for the cable entry hole were fitted next with a 6BA earth tag fitted close to the grommet.

The outside positions of switches S4 to S19 were joined together using two 16 s.w.g. tinned copper wire bus bars with the anodes of D1 to D16 joined to the third bus bar via resistors R34 to R49. (Fig 2.1).

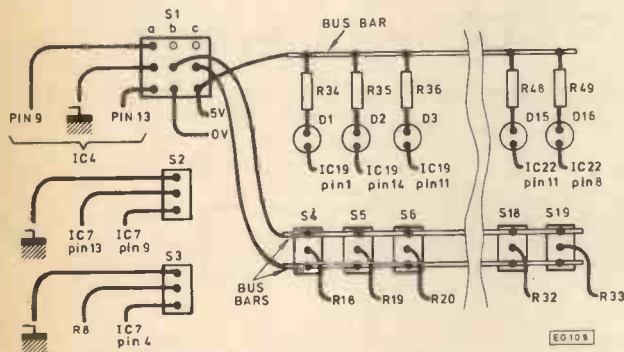


Fig. 2.1. Front panel wiring diagram

The track layouts for the double sided p.c.b. are shown in Figs. 2.3 and 2.4 with the component overlay in Fig. 2.5. After the board has been made it should be placed in the case along with the transformer. Check that the transformer is clear of the p.c.b. and then mark and drill the three p.c.b. mounting holes.

Extra holes should be drilled in the rear and bottom of the case for ventilation.

POWER SUPPLY UNIT

The circuit diagram of the p.s.u. is shown in Fig. 2.6 with the p.c.b. design and component overlay shown in Fig. 2.7 and 2.8. After the p.c.b. has been assembled and checked ensuring that the two regulators (IC25, IC26) are soldered with long leads, the p.c.b. should then be mounted on the rear of the case and the two regulators mounting holes drilled. Both regulators should then be mounted using the insulated mounting kits supplied with the devices.

An ohmmeter should be used to check that the regulators

are not shorted to the case and then the p.s.u. can be wired up to the secondary winding of the transformer. The earth lead from the 0V of the p.s.u. should also be connected to 6BA solder tag under one of the mounting screws of SK 1.

The mains cable to the primary of the transformer can be wired next via the fuse holder and mains switch. The mains earth lead should also be connected to the case.

Recheck the p.s.u. wiring and then switch on and monitor the output voltages. They should be approximately -3.3V, +5V and +11.2V. If the p.s.u. is functioning correctly switch off and disconnect the unit from the mains.


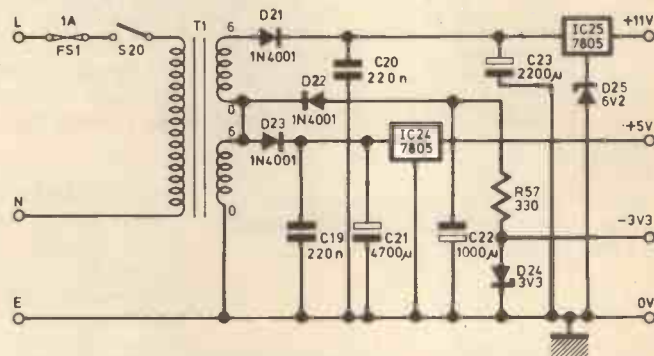
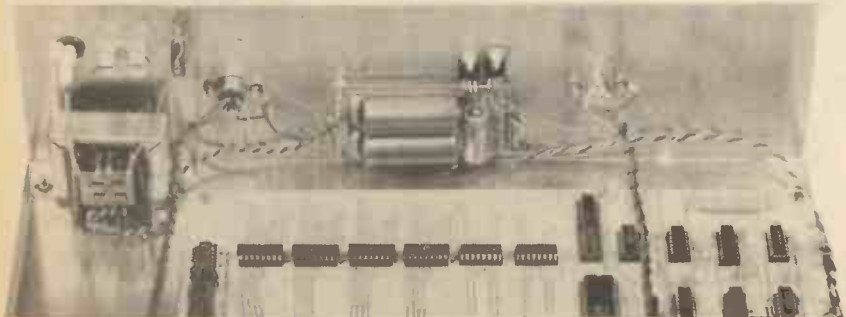
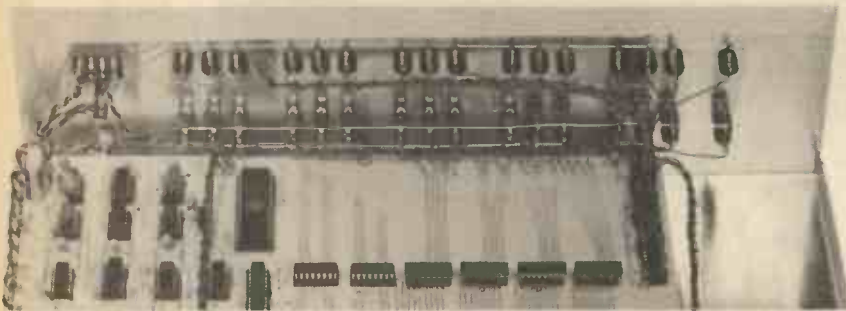


Fig. 2.6. Power supply circuit diagram

MAIN PRINTED CIRCUIT BOARD

The main processor board can be soldered next and it is strongly advised that i.c. sockets are used for all the integrated circuits. A suggested soldering sequence is to fit the i.c. sockets first, checking their orientation carefully, then the resistors and capacitors, TR1, TR2, D17, to D20 and 1MHz. crystal. Vero-pins can be used for the power input wires, S1-S19 and the l.e.d.s D1 to D16. Also fit pins for the five branch external output and input lines and fit pins for IC19 pins 9, 10, 15 and 16 (the 4 bottom Q lines of the output latches). Fit all the through board links, ensuring that they are soldered both sides. Also check that all capacitors and resistors are soldered both sides of the board where necessary. *Do not plug any i.c.s in yet.*

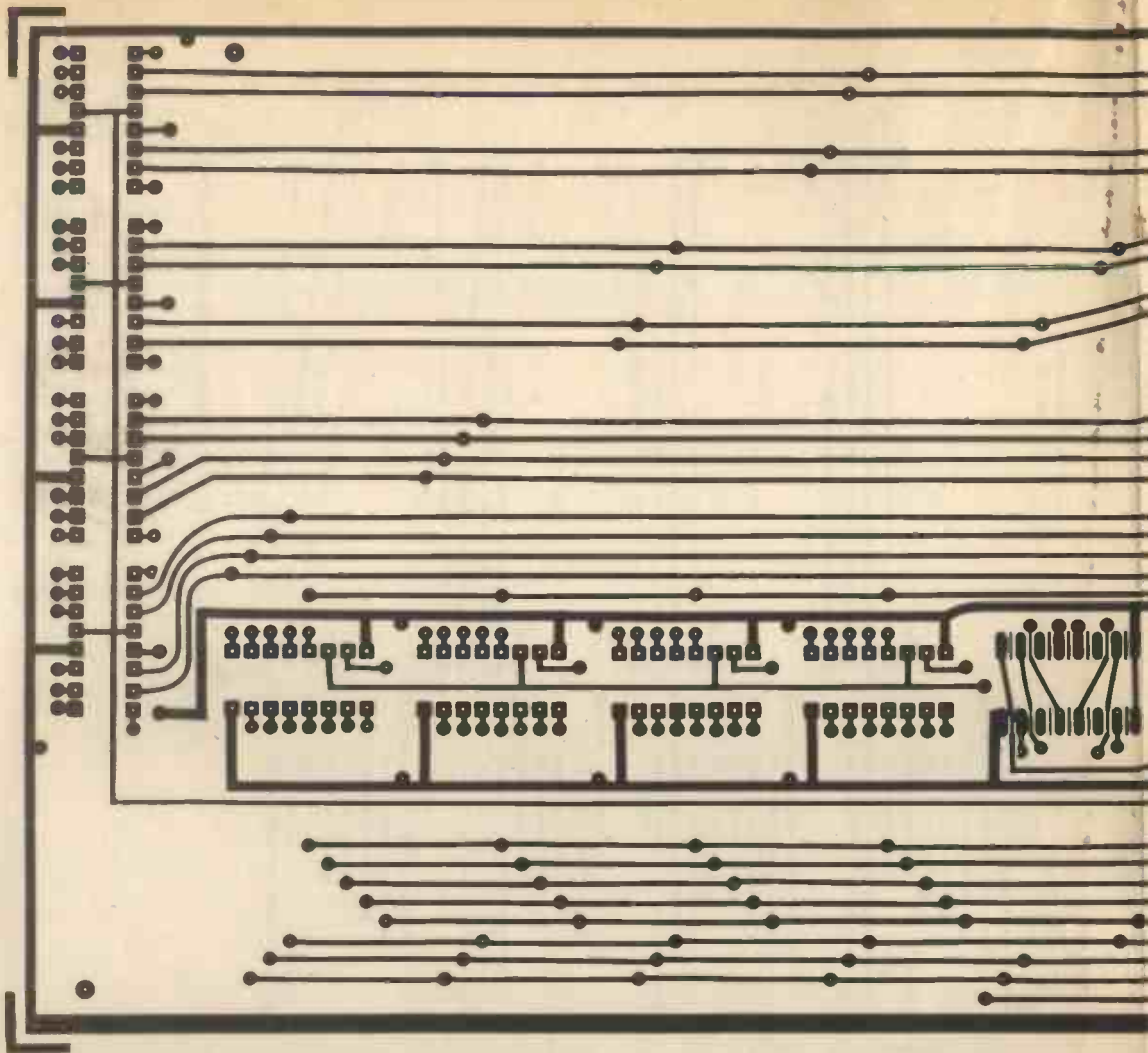Clean the flux from the board and examine it very carefully for bad joints and solder bridges between tracks. At this point take an ohmmeter and check the p.c.b. out against the circuit diagram. An hour spent doing this could save many hours later.



PL1 (Output)

Pin	From	Signal
1	IC19 pin 16	O/P latch 2 ^o
2	IC19 pin 15	O/P latch 2 ¹
3	IC19 pin 10	O/P latch 2 ²
4	IC19 pin 9	O/P latch 2 ³
5	n.c.	
6	PSU +5V	+5V
7	GND	0V

PL2 (Input)

Pin	From	Signal
1	IC23 pin 25	EBCA \emptyset
2	IC23 pin 24	EBCA1
3	IC23 pin 23	EBCA2
4	IC23 pin 22	EBCA3
5	IC6 pin 1	EBC1
6	PSU +5V	+5V
7	GND	0V

TABLE 1

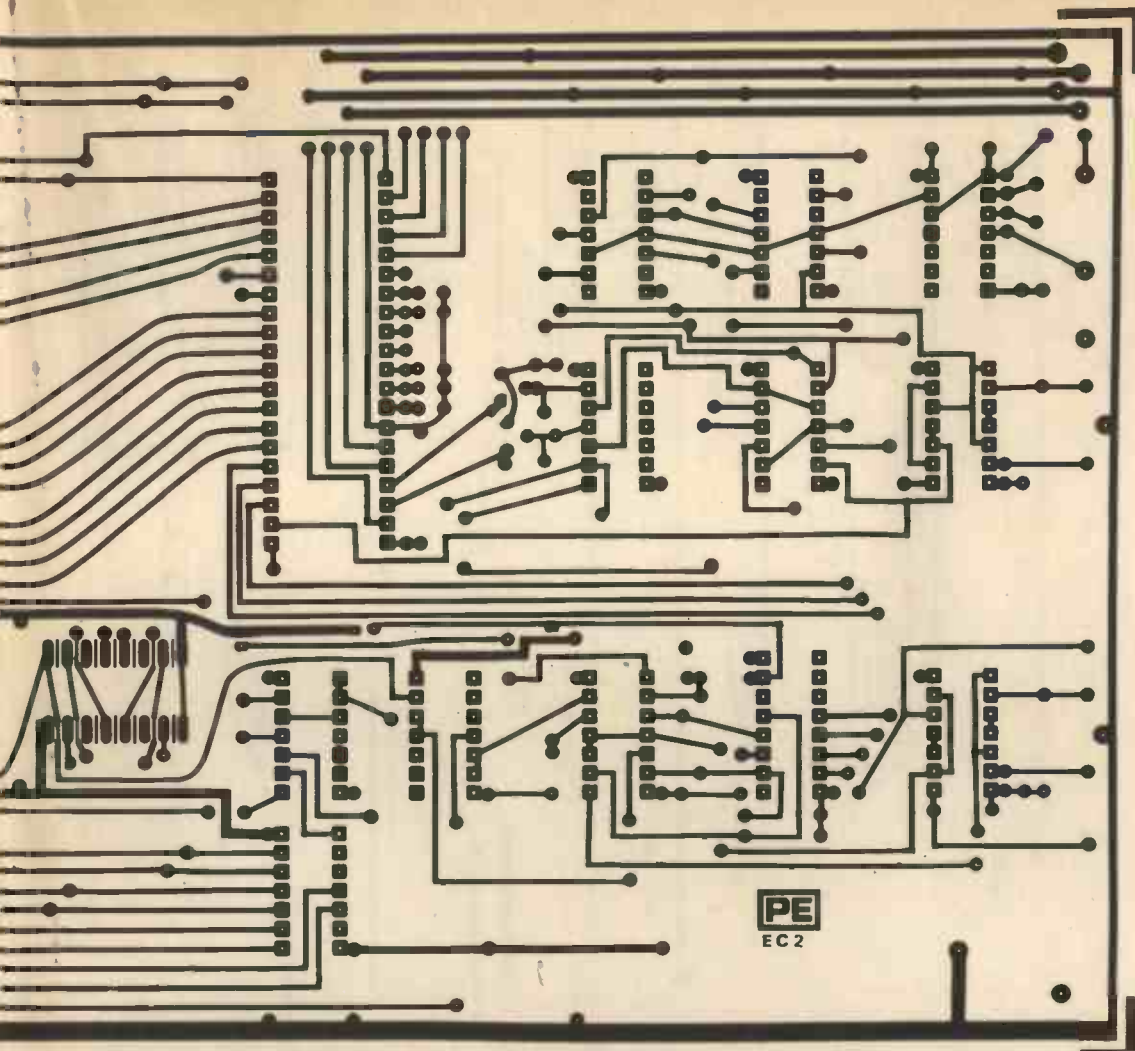


Fig. 2.3. Underside view of the main printed circuit board

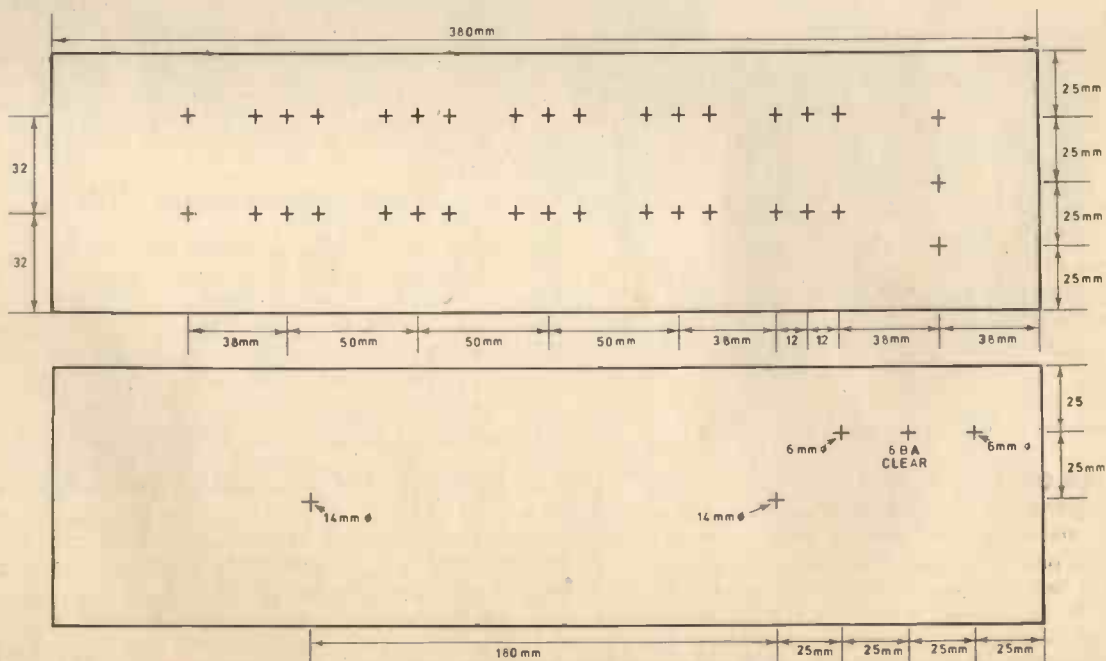


Fig. 2.2. Case drilling details. Front panel (top), rear panel (bottom)

EG107

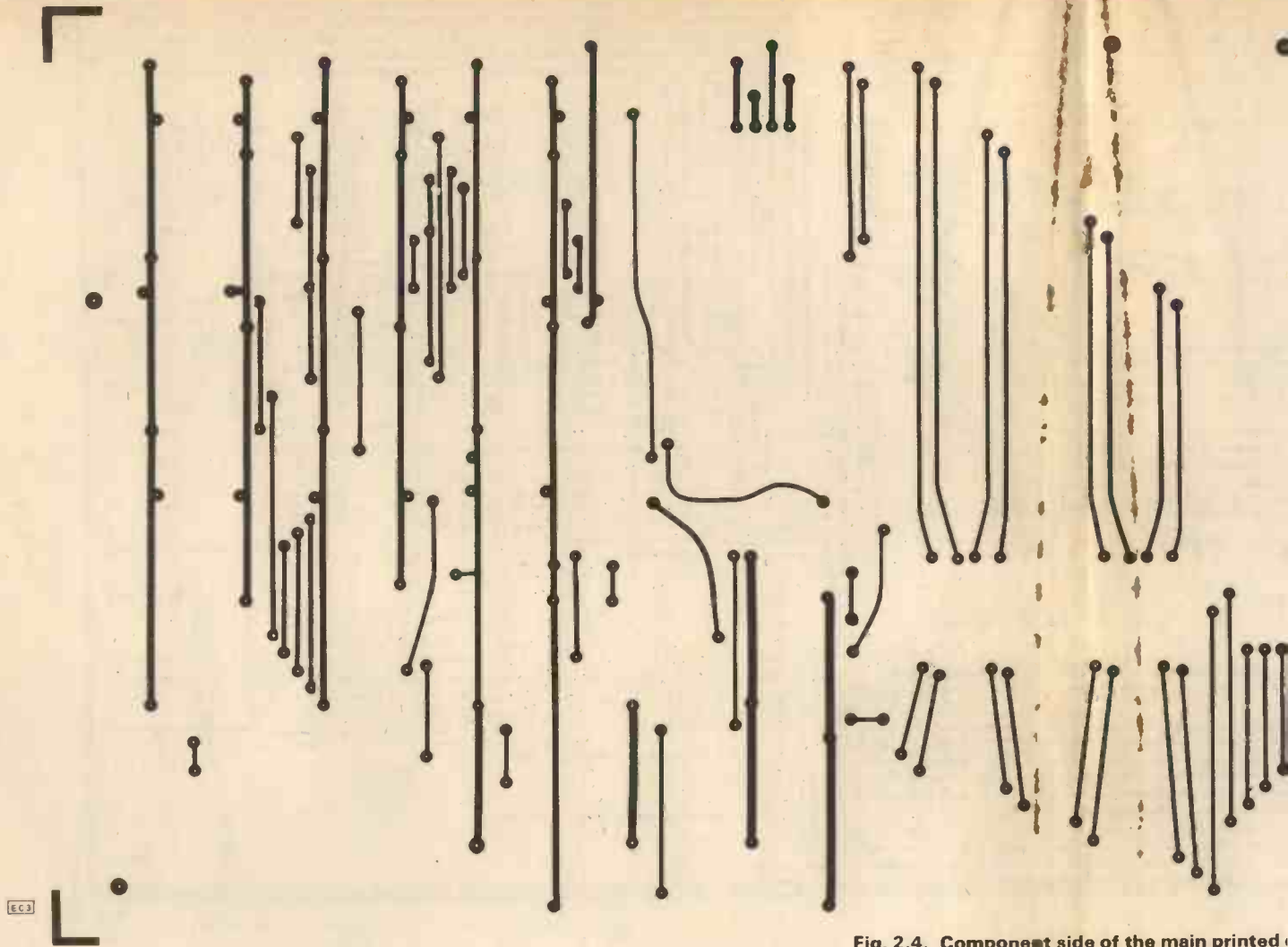


Fig. 2.4. Component side of the main printed



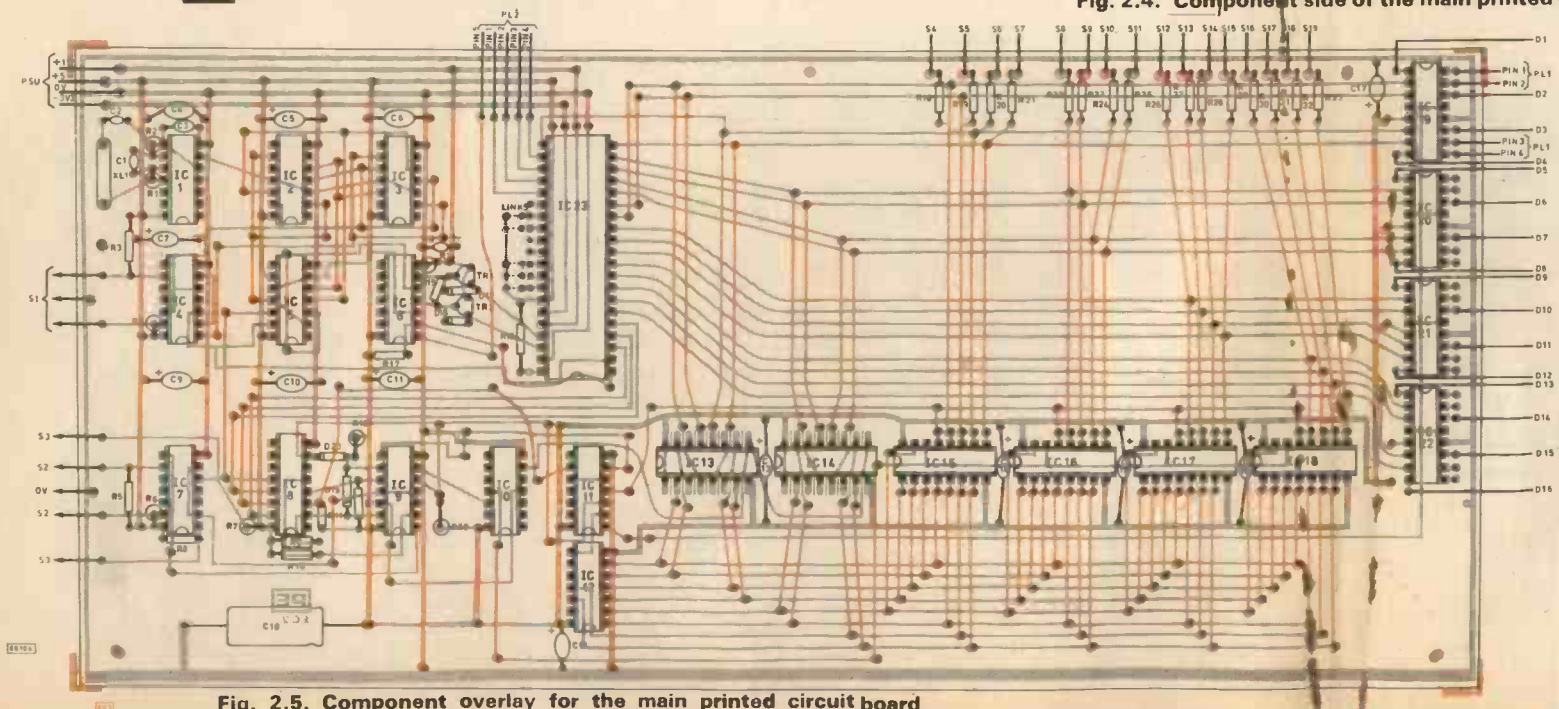


Fig. 2.5. Component overlay for the main printed circuit board

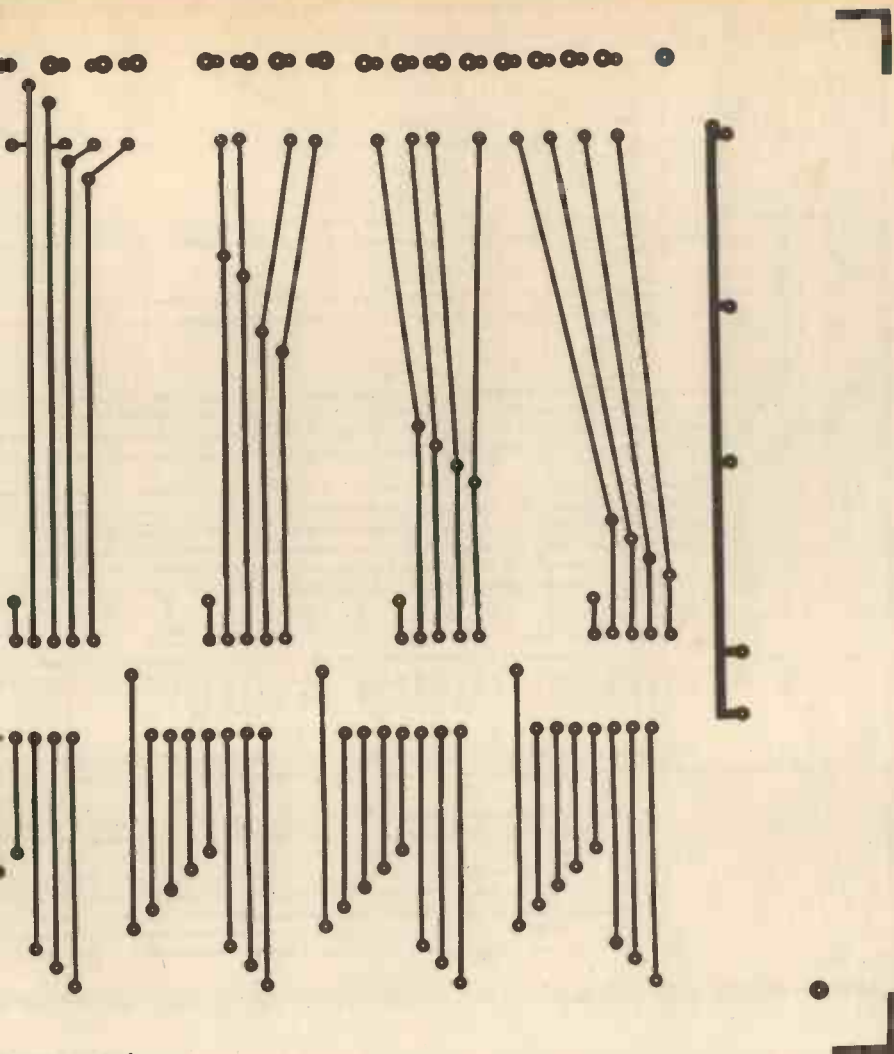

circuit board

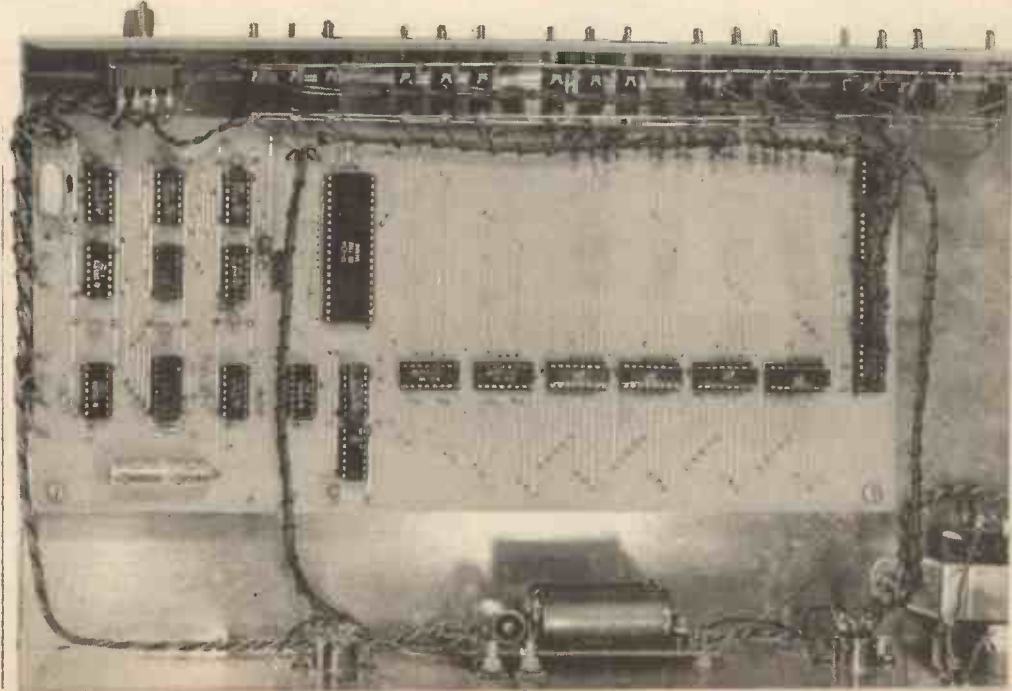

INSTALLATION OF MAIN P.C.B. AND TESTING

Mount the processor p.c.b. back into the case with the three self-tapping screws and connect the power supply outputs to the board. Connect the unit to the mains, switch on and monitor the voltages on the main p.c.b. If they are correct the switches can be wired to the board. *Always remember to switch off at the mains before inserting i.c.s or adding wires to the board.*

Wire switches S1, S2 and S3, wire the bus connected to R34 to the +5V rail. Insert IC1, switch on, and check that the 1MHz clock appears at IC1 pin 6. Insert IC4 and check that when the run load switch is in the load position IC4 pin 8 is low and when the switch is in the run position pin 8 goes high. Fit IC2 and 3 and check that when S1 is in the run position pulses appear at IC2 pins 9 and 5 and IC3 pins

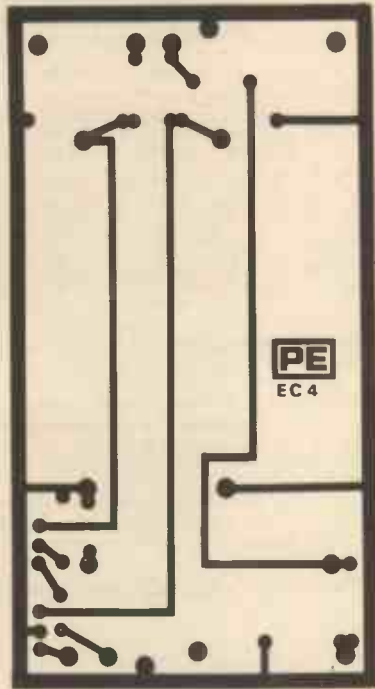


Fig. 2.7. P.c.b. design for the p.s.u

9 and 5. Fit IC5 and 6 and check that pulses appear at IC5 pins 6 and 8 when S1 is in the run position, at IC6 pins 4 and 6, and also at TR1 and TR2 emitters. When S1 is in the load position IC4 pin 3 should be low and when S1 is in the run position IC4 pin 3 should go high. Leave S1 in the load position.

Insert IC7. Check that IC7 pin 8 is high and goes low when S2 is pressed. Check that IC7 pin 6 is high and goes low when S3 is pressed. Insert IC8, 9, 10, 11, 13 and 14. IC13 pin 9 should go low and then high when S2 is pressed and released. IC11 pin 4 should be high and should go low when S3 is pressed. IC10 pin 11 should be high and should go low when S3 is pressed. Insert IC12, 19, 20, 21 and 22. Wire the centre connection of switches S4-S19 to the Veropins at the end of resistors R18 to R33, set all 16 switches to their centre off position and switch on the unit. Monitor IC19 pin 2 and check that it is floating (i.e. an open circuit TTL input). Check that when S4 is switched down ('O') the pin is switched to ground and when S4 is switched up ('O') the pin goes to +5V. Carry out this test on pins 2, 3, 6 and 7 of IC19, 20, 21 and 22 with switches S4 to S19, each switch control only one pin. Monitor IC11 pin 2, set the bottom eight switches S4 to S11 up at '1' and press S2.

Address 377 octal should be loaded into the address latches IC13 and 14 and IC11 pin 2 should go low. Put S4 to 'O' and press S2, IC11 pin 2 should go high. Put S4 to '1' and press S2, IC11 should go low again. Put S5 to 'O' and press S2, IC11 should again go high. Repeat the above test for all eight bottom switches, only when they are all at '1' should IC11 pin 2 go low.

If everything is alright, wire the cathodes of l.e.d.s D1 to D16 to p.c.b. D1 goes to IC19 pin 1, D16 to IC22 pin 8 (Fig. 1.3). Also wire up DIN sockets 1 and 2 as shown in Table 1. Insert IC15, 16, 17, 18 and 23, check that S1 is in the load position and S4 to S19 are in their centre off position and switch the unit on. Check all the p.s.u. voltages again to check that they are alright under full load.

The processor can be tested by the short program shown below.

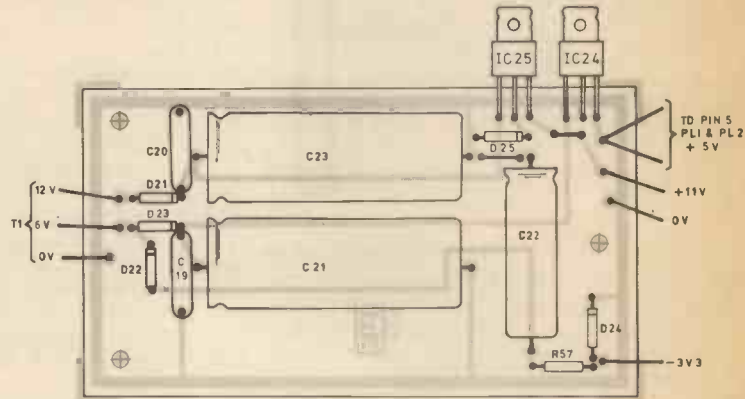


Fig. 2.8. Component overlay for the p.s.u

ENTERING A SIMPLE PROGRAM

Consider the following program to increment register 1 in the CPU and output its contents to the l.e.d.s:—

Octal Add	Binary Add	Octal Data	Binary Data	
0	0 000 000 000 000 000	711	0 000 000 111 001 001	Clear R1
1	0 000 000 000 000 001	11	0 000 000 000 001 001	
2	0 000 000 000 000 010	1101	0 000 001 001 000 001	Output R1 to
3	0 000 000 000 000 011	377	0 000 000 011 111 111	
4	0 000 000 000 000 100	4	0 000 000 000 000 100	Jump to
5	0 000 000 000 000 101	1400	0 000 001 100 000 000	
6	0 000 000 000 000 110	1	0 000 000 000 000 001	Write start add into location 376
376	0 000 000 011 111 110	0	0 000 000 000 000 000	

1. Select Load/Run switch S1 to Load.
2. Set switches S4 to S19 to octal 0.
3. Push Enter Add S2 to enter Add 0 into Add register.
4. Set switches S4 to S19 to octal 711.
5. Push Enter Data switch to enter 711 into 0 in RAM.
6. Set switches S4 to S19 to octal 1.
7. Push Enter Add switch to enter Add 1 into Add register.
8. Continue until the octal number 1 is entered into location octal 6 in the RAM.
9. Now select octal 376 on switches S4 to S19.
10. Push Enter Add switch, enter 376 into Add register.
11. Write octal 0 into this location using switches S4 to S19 and the Enter Data switch. This writes the start Add into location octal 376 (any spare location can be used for the start address).
12. Put switches S4 to S19 to centre (off) position.
13. Select Load/Run switch to RUN. The program should now commence and the l.e.d.s should increment.
14. It is important that the last entry into the Add register should be the start Add of the program.

NEXT MONTH: programming.



INDUSTRY NOTEBOOK

By Nexus

Training

Catch 'em while they're young seems to be the motto in France. I note with interest a press report that 10,000 microcomputers are being ordered for French schools and universities and that 150 teachers are to get a year's training on their use and another 1,500 teachers a shorter course. In parallel there is a big competition for ideas on how to use MPUs in which up to 1,000 young inventors are expected to submit entries. A similar scheme is in preparation for the UK with a funding of £12.5 million over five years, but is still in the paper and committee stage.

In the UK there are encouraging signs that science and engineering are regaining favour in schools and colleges as proper, even exciting, future careers. Salary structures have certainly improved over the past three years and the prospect, as seems certain, of a critical shortage of engineers over the next decade or so will at least give employment security and fine opportunities to all those who take the profession seriously. The latest salary survey shows that IEE members were averaging £7,240 p.a. in January this year compared with £6,210 p.a. in January 1978, an improvement well in advance of the cost of living. In the public sector electrical and electronic engineers' salaries on average were higher than in private industry so one assumes that public sector employees will keep quiet about comparability while those in the private sector might well start raising hell—a reverse of the general trend.

Results

The fickle wheel of fortune spares nobody. EMI's high-flyer, the EMI Scanner, so profitable in its early years is now almost a dirty word with losses this year estimated by City sources as £15 million or more, largely attributed to slumping sales in the USA and increasing competition in the market place. Budget-price brain scanners,

for example, are expected from two Japanese manufacturers this year, Toshiba and Hitachi. But EMI can take comfort in having sold two top-price whole-body scanners to China for £500,000 and is clearly making further efforts to diversify its market outside the USA.

Plessey, despite increased business looks like having a standstill year as far as profits are concerned. In Plessey's case the problems are in the loss-making Liverpool plant making telephone exchanges, and Garrard making record players. Industrial disruption has also eaten into Plessey profits, one estimate being £800,000. So wonderful performance in some areas of Plessey activities are masked in the overall results by difficulties elsewhere, and by no means always the fault of the company.

Plessey, however, remains fundamentally strong with a record order book of over £800 million and with exports and overseas sales accounting for over half total turnover and a market in 131 countries.

GEC is forecast as pushing up profits this year to over £370 million and topping easily the £400 million mark in 1979/80. Profit growth will be led by GEC's electronic divisions, spearheaded by Marconi. The formation of GEC-Fairchild in the UK has sparked off speculation that GEC has its sights on acquiring the whole of Fairchild Camera and Instruments in the United States.

The Racal Group, fastest growing in both turnover and profit in British electronics, is expected to have another good year. Recent tidying up operations include two name changes. Racal-Thermionic, the professional-quality tape-recording company in the Group has been re-named Racal Recorders Ltd and a base in the USA has been established as Racal Recorders Inc with sales and service initially from Rockville, Maryland, and Corona, near Los Angeles. These will be followed by other sales and service outlets later this year at Chicago and Houston. British Physical Laboratories, acquired by Racal in 1974 becomes Racal-BPL, the change coinciding with the entry of BPL into the digital panel meter field.

Among Racal's recent off-beat support activities are backing for Britain's first amateur scientific satellite being co-ordinated by the University of Surrey and the supply of radio equipment to the Trans-globe Expedition which sets off from Greenwich next September on a three-year circumnavigation of the world by its Polar axis over land, sea and pack-ice. The Racal equipment is said to be worth over £130,000.

Hire

Hiring rather than buying instruments often makes good sense, especially if you need them only to meet short-term needs such as a small production run or in field-commissioning of a new installation. The UK instrument hire business has hitherto been shared by two companies, Livingston Hire and Labhire. Now there is a third entrant in the field, Leasemetrix. Not much

of a threat, you might imagine, against two experienced and well-established companies. That is, until you look at the Leasemetrix management. At the top is David Rennie who set up Livingston Hire in the 1960s and was top man there until parting company in 1975. Rennie is joined by sales manager R. J. Mundy and laboratory manager Ray Keogan who both held the same positions at Livingston.

An intriguing situation for industry watchers. Will Leasemetrix come up from behind and scoop the pool? Will there be a price war? Rennie says there will be no price cutting. As for coming up from behind, Rennie thinks there will be a big expansion in instrument hire and there is room for a third company. Financial backing for Leasemetrix comes from the Small Business Capital Fund which is a venture capital operation of the Co-operative Insurance Society.

Show-Biz

Telecom 79, the giant telecommunications show to be held at Geneva in September will see Britain's biggest ever promotional exercise. Centre-piece will be a huge BPO/Industry joint stand covering 9,000 sq metres occupied by the Post Office, GEC, Plessey, STC, Marconi and Pye TMC. The commercial companies will also have their own individual stands as will 24 other British companies in the business. The operation is supported by the British Overseas Trade Board and the Electronic Engineering Association. Public Relations for the promotion on a day-to-day basis is headed by Peter Wymer, well-known in the industry for many years as publicity manager at Mullard and later as a publicity chief in the Post Office before becoming a private consultant.

Mini-LP

The shape of things to come in the hi-fi market could be the 4½ in diameter LP record recently demonstrated in experimental form by Philips. A laser beam is used as a "pick-up" thereby eliminating record wear and giving a ten-year life with normal useage. Philips would clearly like its audio disc to become a world standard, following the path of the Philips tape cassette. The Japanese, however, are all working towards audio systems which will be compatible with videotapes. It could be the start of another damaging war in consumer electronics ending in another muddle of incompatible equipment. Philips say they will adopt a liberal licensing policy towards other manufacturers. If it goes ahead the Philips system should be commercially available by the mid-1980s. A big plus-point for the 4½ in hi-fi disc is that it can be readily used in cars.

Automated Oven

In an attempt to capture a larger share of the microwave oven market, Toshiba has introduced an oven controlled by inserting a magnetic card which is encoded with the cooking instructions.

next month!



STROBOSCOPE...

Almost any rotating or vibrating system can be studied in motion using this strobe. Any irregularity is instantly revealed.


SWITCHED TONE TREBLE BOOST

Rapid click-free selection of four switched tones, each of subjectively balanced loudness level. Designed for the practising musician.

SPECIAL OFFER!

MULTIMETER

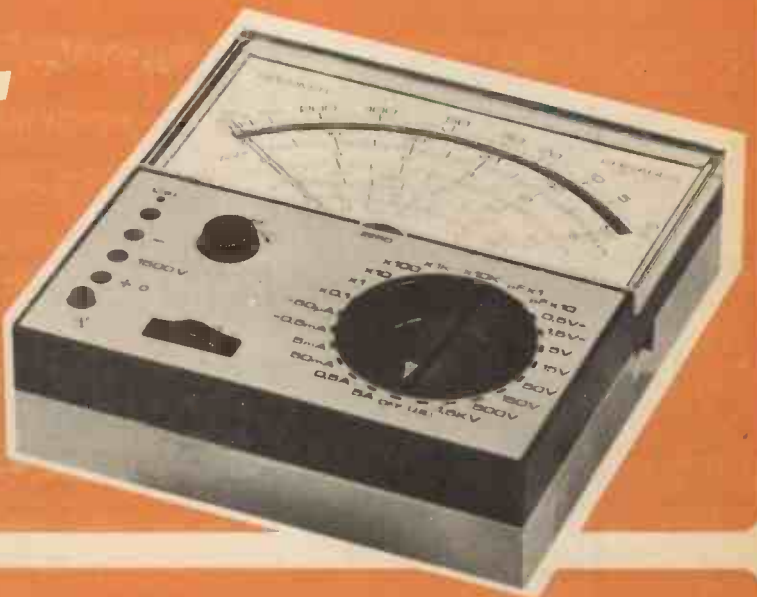SAVE £21. A Chinaglia Dolomiti US1 for £32.95 including postage and VAT. Features 39 ranges, 20 k Ω /V up to 5A and 1.5kV with electromechanical overload protection, signal injector, antiparallax mirror, case and 12 months guarantee.




PRACTICAL

ELECTRONICS

OUR JULY ISSUE WILL BE ON SALE FRIDAY, 8 JUNE 1979



ULTRASONIC REMOTE CONTROL

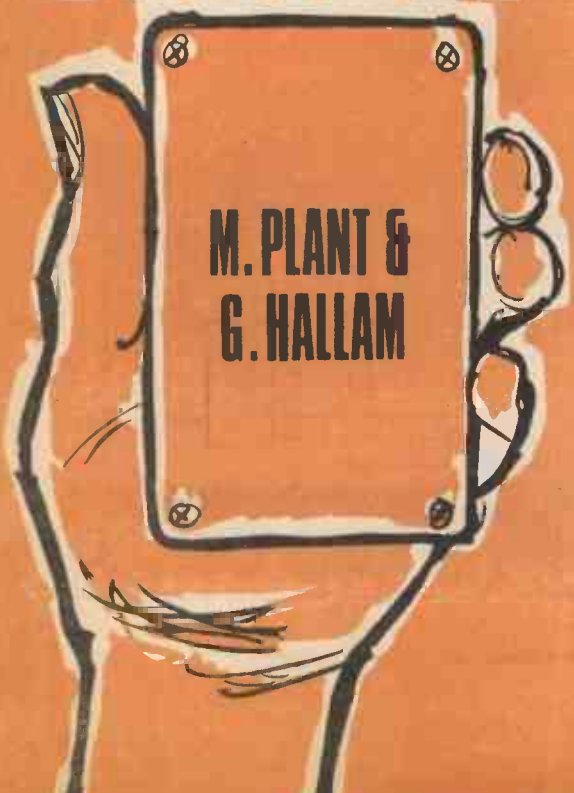

THIS project describes how ultrasonic transducers can be used in a control system for domestic use. Although this is not a novel application, TV manufacturers have used ultrasonic remote control systems for a number of years, many constructors should be able to find a number of interesting applications i.e. on/off control of mains operated appliances that might be of special interest to the aged or handicapped people. The control of garage doors and toys are two further possibilities. This system also has the facility for temporarily switching mains power on or off for a predetermined period of time which can be useful for lighting a path or porch light when returning home.

There are a number of methods that can be used when designing remote control systems and broadly these methods depend on either electromagnetic or sound waves.

The main problem in designing a system based on electromagnetic or sound waves as carriers of the control signal is to avoid the spurious triggering of the controlled element by artificial or natural signals having characteristics similar to the control signal.

One commonly used method is to modulate in a characteristic way the carrier signal from the control transmitter and to tune in the receiver to this characteristic. If infra-red is the carrier, an infra-red light emitting diode could be used to emit pulses of radiation at a frequency of say 20kHz, which the receiver detects via a photo diode rejecting all other frequencies. This same principle holds good for a radio control system.

TRANSDUCERS

In order to avoid having to build a tuned circuit when using electromagnetic waves, it has become popular to use ultrasonic transducers which are already "tuned in" to a fixed frequency (usually 40 kHz).


These transducers depend upon the piezoelectric effect for their action which means that if a periodically changing voltage of 40kHz is applied across their terminals they resonate at this frequency and emit a beam of ultrasonic sound. (Note that 16kHz is the highest frequency most of us can hear.) Since the receiver transducer is identical to that of the transmitter, upon receiving this beam it responds by producing a 40kHz voltage across its terminals. As the ultrasonic beam is of high frequency with a narrow band width it is reasonably insensitive to signals from other sources.

The transmitter is housed in a small plastic case and is activated by a push button switch.

The receiver has its own low voltage power supply derived from the mains supply or from an internal battery. The relay closes when the receiver detects 40kHz ultrasonic waves



Receiver and Transmitter

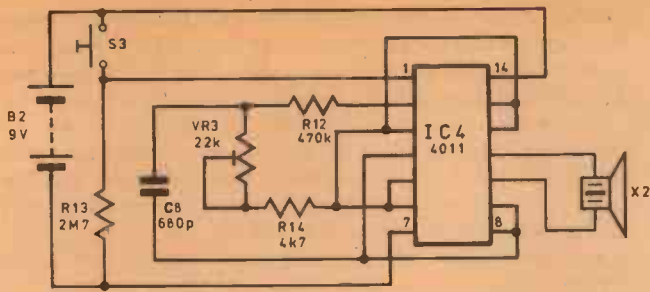

EG 111 Fig. 1. Circuit diagram of the Transmitter

and mains power is then available to the appliance plugged into the 13A socket. The wattage of the mains power which can be controlled depends largely on the choice of relay (750W is the maximum for the one specified in the components list). Switches are provided for bistable (on/off), monostable (temporary on) and mains/battery operation. The battery supply can easily be dispensed with for it merely provides an on/off action via another pair of the mains relay contacts available at two sockets. The range of the control system for domestic use depends greatly on the type of furnishings in a room, but you should expect from 5 to 8 metres.

TRANSMITTER


The circuit diagram of the transmitter is shown in Fig. 1. A CMOS 4011 i.c. is used as a square wave oscillator to drive the ultrasonic transducer at a frequency of 40kHz. The oscillator is inactive until S3 is closed taking the voltage at pin 1 high. The 4011 contains four NAND gates, two of which are wired as an oscillator using R12, VR3, R14 and C8. The other two NAND gates are used as buffers to switch power to the transducer. The outputs, pins 10 and 11, of the second two NAND gates go high and low in a complementary way at a frequency of 40kHz. The variable resistor VR3 enables the frequency of the oscillator to be adjusted to the resonant frequency of the transducer.

RECEIVER

A combination of bipolar devices and CMOS integrated circuits is used in the ultrasonic sensitive receiver shown in Fig. 2. The function of the circuit may be understood by dividing it into its basic elements. Remember that the overall function of the circuit is to close the relay contacts RLA1

when the ultrasonic transducer receives the 40kHz sound waves.

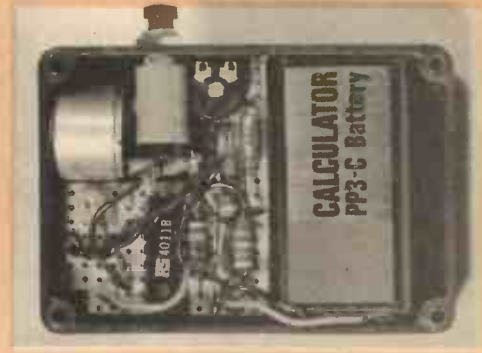Firstly the circuit operates from a nominal 10V d.c. supply derived from the mains via transformer T1, rectifier diodes D1 and D2, smoothing capacitor C1, and the series stabiliser components, TR1, R1 and Zener diode D4. For portable




Internal view of the Transmitter

operation of the circuit, S1 enables a 9V battery to be switched into the circuit.

Upon detecting an ultrasonic beam pulsed at around 40kHz, the ultrasonic receiver transducer generates a small sinusoidal voltage which the preamplifier, based on transistors TR2 and TR3, amplifies. The amplified signals at the collector of TR3 are rectified by D3 and appear as negative going pulses at pin 2 of IC1 which compares these voltage peaks with the voltage on pin 3. The latter voltage is set by R8 and the variable resistor VR1 which acts as a sensitivity control. Thus, when no signals appear at the collector of TR3, pin 2 is held high by R7 and the output voltage from the op amp is zero. When voltage pulses arrive at pin 2 and drive this voltage below that of pin 3, the output voltage suddenly switches positive, a condition which is made clear when D5 lights. Capacitor C4 provides a certain amount of integration of the pulses and avoids spurious operation of the op amp.

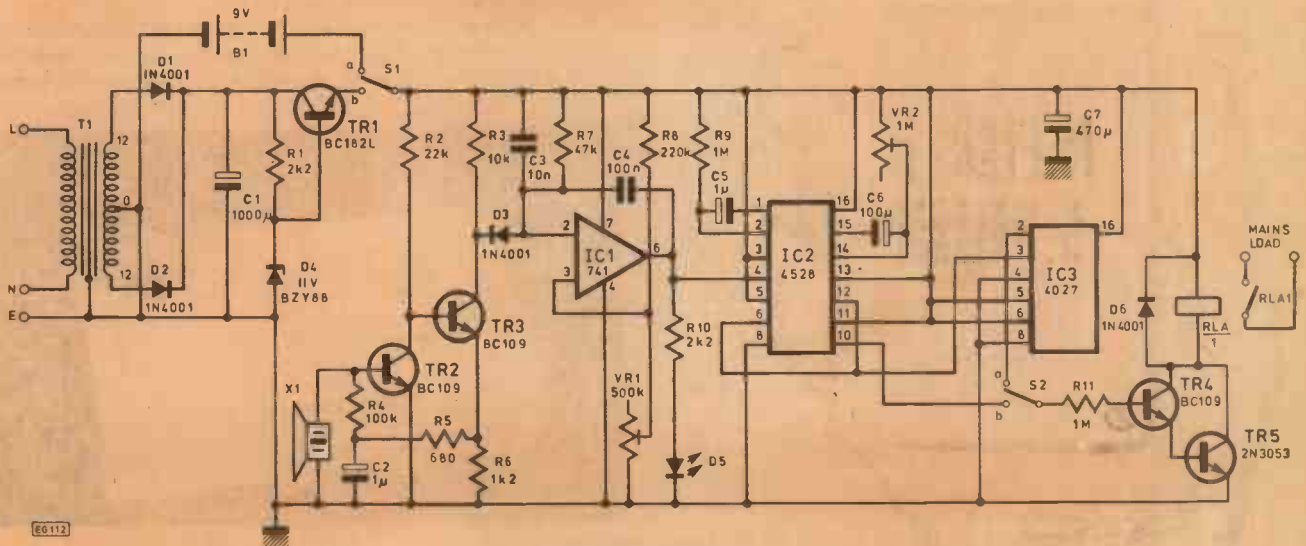The signal from the op amp passes to pin 4 of IC2, a dual monostable CMOS i.c. The rising voltage on pin 4 triggers the first of these monostables, IC2a, producing a pulse from pin 6 the duration of which is fixed by the product of the R9 and C5 values. This monostable acts as a pulse shaper to provide reliable operation of IC2b and the CMOS flip-flop IC3.




EG 112 Fig. 2. Circuit diagram of the Receiver

The second monostable is triggered via pin 12 and produces a positive output voltage at pin 10 for a duration determined by the product of the VR2 and C6 values. The same trigger pulse from pin 6 of IC2a switches the flip-flop IC3 via pin 3. Each pulse operates the flip-flop so that its voltage at pin 2 goes alternately high and low. Switch S2 selects in position 'a' the flip-flop output and in position 'b' the monostable output. Either pulse passes to the Darlington pair current buffer transistors TR4 and TR5 to drive the relay RLA. Thus the circuit provides a stable (on/off) or monostable (temporary on) control of the relay. The monostable period is set by VR2. The mains relay contact RLA1 determines the mains current which can be switched and hence the power of the mains appliance which can be controlled.

CONSTRUCTION

The transmitter components are assembled on a small piece of Veroboard as shown in Fig. 3. One mounting hole on the Veroboard firmly fixes the circuit by means of a 6BA

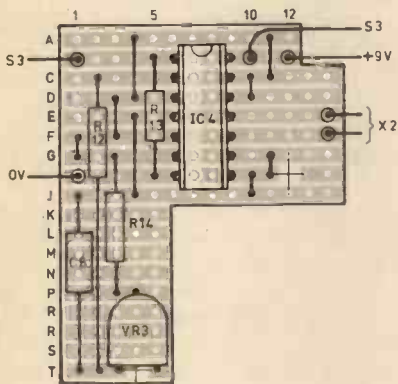

EG109

Fig. 3. Veroboard layout for the Transmitter

nut and screw to the inside of the plastic box shown in the photograph, in which the battery, transducer and switch are also fitted. Before screwing down the box lid, the variable resistor VR3 will need to be adjusted as explained under "setting up".

The receiver circuit is similarly assembled on the Veroboard as shown in Fig. 4. Note that this board also carries the rectifiers for the d.c. supply fed from the low voltage transformer windings. Decide if you want the battery facility. If not, S1a and S1b connections are not required. Double check all the spots where the Veroboard track needs to be cut away.

Note that diode D6 is wired directly across the relay contacts. One pair of the relay contacts (normally open) may be taken to a pair of 4mm sockets for control applications if the unit is to be operated from the internal battery.

SETTING UP

If a battery has been included in the design, switch to the battery mode using S1a position. Turn the sensitivity control VR1 fully clockwise and the red l.e.d. should light up. Turn back VR1 until the l.e.d. just goes out. As you do this, the relay may be heard to operate. Jangle some keys in front of the receiver transducer and the l.e.d. should momentarily light and the relay be heard to operate. This shows that the circuit is sensitive to ultrasonic noise from the keys. A similar procedure should be followed to check the circuit's operation from the mains.

Now check the function of the transmitter by pointing it towards the receiver from a distance of about one metre. Keep the button pressed and the l.e.d. on the receiver should light up. If it doesn't, use a small screwdriver to adjust VR3. The setting of VR3 is critical so take your time. The idea is to tune the transmitter to produce the maximum signal from the receiver transducer. If you have a multimeter, connect it across pin 6 to ground of the op amp and adjust VR3 in the transmitter until the maximum voltage is detected. Or an oscilloscope can be used connected across the receiver transducer to detect the maximum signal voltage swing. Plug in a table lamp to the receiver's 13A socket. Switch the

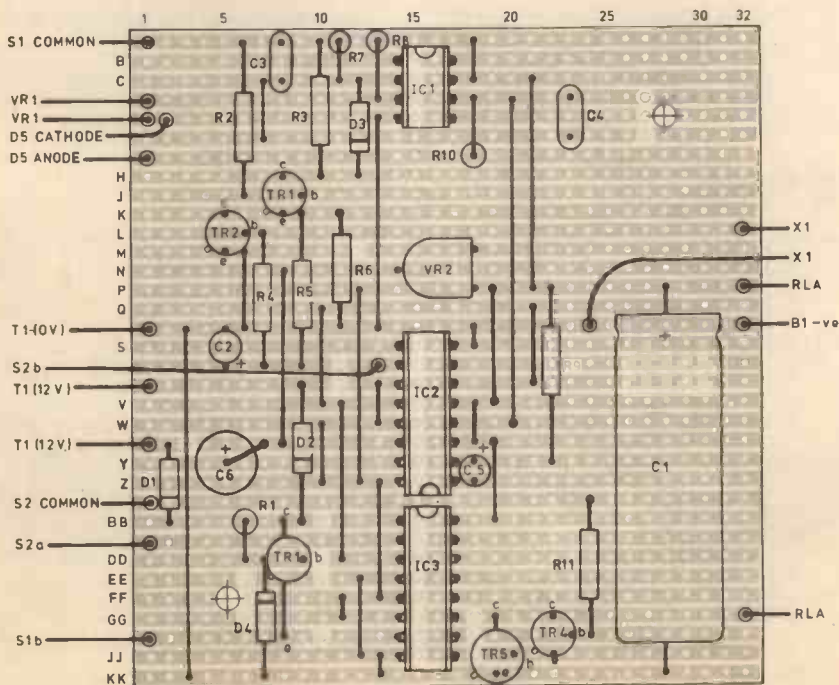


Fig. 4. Veroboard layout for the Receiver

EG110

COMPONENTS . . .

Resistors

R1, R10	2k2 (2 off)
R2	22k
R3	10k
R4	100k
R5	680
R6	1k2
R7	47k
R8	220k
R9, R11	1M (2 off)
R12	470k
R13	2M7
R14	4k7

All resistors $\frac{1}{2}$ W 5% carbon.

Potentiometers

VR1	500k lin
VR2	1M hor. preset
VR3	22k hor. preset

Capacitors

C1	1000 μ 25V elect
C2, C5	1 μ 16V elect (2 off)
C3	10n polyester
C4	100n polyester

C6	100 μ 16V elect
C7	470 μ 25V elect
C8	680p polystyrene

Semiconductors

D1, D2, D3, D6	1N4001 (4 off)
D4	11V BZY88 Zener
D5	TIL 209
TR1	BC182L
TR2, TR3, TR4	BC109 (3 off)
TR5	2N3053
IC1	741
IC2	4528
IC3	4027
IC4	4011B

Switches


S1, S2	s.p.d.t. min. toggle (2 off)
S3	push to make p.b. switch

Miscellaneous


X1	Receiver 40kHz
X2	Transmitter 40kHz
B1	PP6 battery
B2	PP3 battery
RLA	12V 2 pole changeover 3A contacts
Battery clips	
Mains 13A socket	
Case type 301 (70 x 50 x 25mm) Maplin.	
Case type 103 (188 x 110 x 60mm) Maplin.	

mode switch S2 to the bistable mode and press the transmitter button pointing the transmitter at the receiver from a distance of about 2 metres. Remember that the ultrasonic beam is quite narrow (about 10°). One operation of the push switch (not too brief) will bring on the l.e.d. and the relay will be heard to operate and the lamp will go on or off. Practice the operation until you can reliably control the lamp, one push for on and the next push for off. You should get control over a distance of at least 5 metres.

Now check the operation of the monostable by switching S2 to this mode. The lamp will normally come on and remain on for a period of time determined by the setting of VR2. Wait for the lamp to go off and then use the transmitter to bring it on. Set VR2 to give the delay required—up to about 50 seconds with the values of VR2 and C6 given. The duration can be increased by increasing the value of C6. This

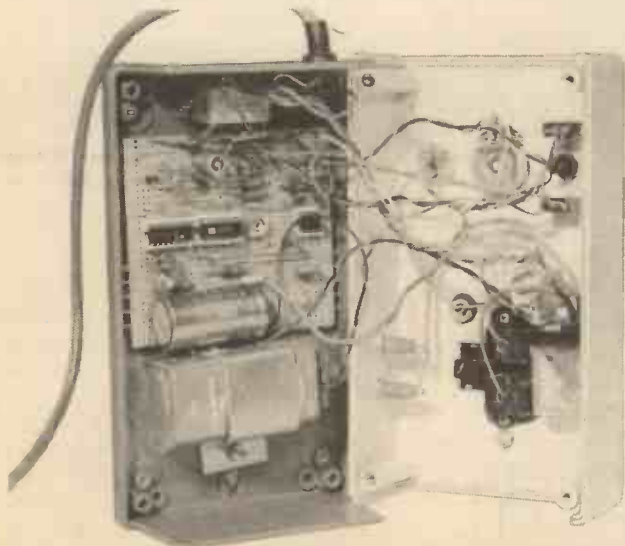

Internal view of the Receiver

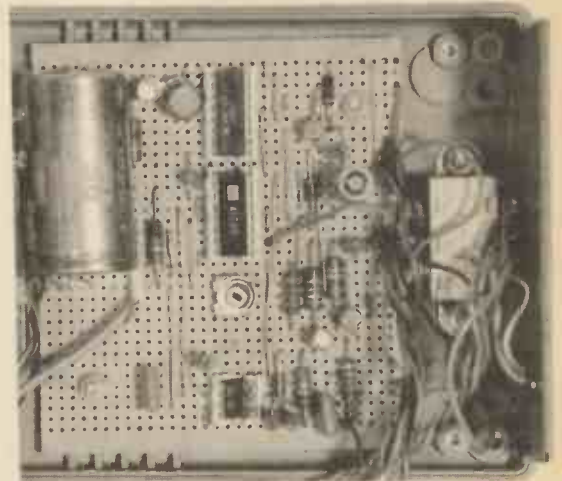

monostable facility is provided if you want to turn on appliances such as a porch light for a limited period of time. In all these adjustments take great care when the receiver is being operated from the mains not to inadvertently touch any bare mains connections within the unit. Note also that the maximum mains power which can be switched by the relay is determined by the current rating of the relay provided it is a 250V type, so check the wattage of the appliances.

If the receiver sensitivity control is set too high, the receiver might be triggered by noise which has an ultrasonic component. So beware of rustling papers, jangling keys, the click of a central heating thermostat and bats! You may have to turn down the sensitivity control to avoid unwanted triggering of the receiver circuit.

Finally, you might like to know that the ultrasonic beam from the transmitter can be reflected from objects in a room: the ceiling or the wall opposite the receiver, from a chair leg—or you. ★

R.F.I. SUPPRESSION for Power Supply Units

B.E. TAYLOR*

SCORES of very comprehensive articles have been written on the subject of suppressing (and filtering) conducted radio-frequency interference generated by switch-mode power supplies. Very few of these articles have been written with the non-specialist engineer in mind, and even fewer have been written that cover r.f.i. generated by linear regulators. This article attempts to show that the design of power supplies with good interference suppression can easily be achieved, provided that a few relatively simple rules are followed.

SOURCES OF RFI

The first, and most important rule, is to design the power supply with r.f.i. suppression as an integral part of the design. It is futile simply to try to filter the noise at the line input and/or output terminals after the noise has been generated. The interference should be reduced at source. To this end, one must first recognise these sources of interference, and all supplies—even linear ones—have one or more of these sources.

How can linear regulators be classed as generators of r.f.i.? It is only when the linear regulator is closely scrutinised that one recognises one of the first sources of r.f.i. for all supplies: that of large, line-pulse currents and their rates of change. One of the reasons for these large pulse currents is the line-frequency rectifier and the use of capacitor input filters. The reservoir capacitor forces the rectifier to conduct over very narrow conduction angles, and the sudden start and/or cessation of the resulting large current pulse that flows in line and neutral conductors—containing unwanted inductance (or the primary referred leakage inductance of the line transformer in a linear supply)—generates noise voltages that appear at the line and neutral terminals.

The effect of this rate of change of current is one of the major sources of

interference over the 10kHz to 100kHz band, and is also a factor up to a few megahertz. One of the remedies for this source of interference is to connect as large a value of capacitor (as large as the relevant safety specifications will allow) as near as possible to the a.c. terminals of the rectifier bridge.

Another source of r.f.i. (this time appearing at the output terminals) can be attributed directly to sudden changes in current flow, and is generated in the output rectifiers in switch-mode supplies—whether they be Schottky-barrier devices or plain fast-recovery rectifiers. The usual solution for these devices is to connect RC snubbers across the rectifiers or across the transformer secondary.

Yet another source of interference from currents and their rates of change is the emission of magnetic fields around conductors, chokes and transformers.

Not all r.f.i. is due to current. Many sources also arise from the capacitive coupling of rapid changes in voltage. Unfortunately, the 'dabbing' of the odd capacitor or resistor will have little or no effect. To eliminate these generators of interference, one must revert to the principles of good electrical and mechanical design.

IDENTIFICATION AND ELIMINATION

At this point, it is best to identify some of these sources, to tabulate them and to look at some of the available means of elimination that may be employed:

(1) The first source of noise due to sharp edges in voltage waveforms is the capacitance between the cases of switching transistors and their heatsinks. Since the case of the transistor is usually tied to the collector (the isolated-case TO-3 transistor is not yet readily available, so its use cannot be freely advocated), and the heatsink is usually at ground potential, it is easy to see the capacitor so created as forming

a potential divider with the capacitors to ground in the line input filter. Because the capacitors to ground in the input filter are limited to a maximum value (to minimise earth leakage currents) it is just not feasible to keep increasing their capacitances ad infinitum. The capacitance of transistor case to ground should be eliminated or at least drastically reduced. Reducing this capacitance is fairly easy; the use of aluminium oxide insulating washers in preference to mica or Melinex ones to increase dielectric constant is one method. The elimination of this capacitance, on the other hand, involves the use of one or other of the two most common ploys: the guard screen (the subject of a Gould patent) or the use of a heatsink electrically isolated from ground. The heatsink should be connected to the negative line rectified rail.

(2) One of the most easily recognised sources of noise is due to transformer inter-winding capacitance. The use of electrostatic screens should prove more than adequate in eliminating this source. On no account, though, should the screens be connected to ground, but to d.c. rails—one to each side of the transformer. The exception to this rule is the safety screen. Therefore, between primary and secondary, the screens should be in the following order:

(i) primary; (ii) guard screen connected to the positive line rectified d.c. rail; (iii) safety screen to ground; (iv) guard screen connected to the common output terminal; and (v) secondary.

(3) A third source associated with the transformer in switch-mode supplies, but one that is less easily recognised, is the capacitance between windings and the transformer core. The winding of greatest concern is the primary, which is usually found to be in close prox-

imity to the core (whether it is the innermost or outermost winding is largely immaterial). Once again, a guard screen between the winding and core may be used. On the other hand, it is easier simply to isolate the core electrically from ground. Whichever technique is used, care must be taken to ensure to connect either the guard screen or core electrically to the primary d.c. rail.

(4) A problem very similar to the transformer-winding/core capacitance is the capacitance between the winding and core of the output filter choke, especially if the 'hot' end of the winding happens to be nearest the core. A simple remedy is merely to transpose the connections if the current-carrying conductors are not made of copper strip. If transposition of connections is not possible, the measures described in the preceding paragraph are necessary.

THYRISTOR INTERFERENCE

One of the most insidious of sources of r.f.i. and one which covers both current and voltage generation, is the thyristor or triac used in many soft-start circuits to limit inrush current. Claims are made that zero-crossing triggering of thyristors virtually eliminates them as generators of interference. This most certainly is not the case; thyristors always generate interference. It is only the magnitude of the noise that varies. The lesson to be learned, therefore, is that, if they must be used, the devices must be inserted in one of the rectified lines and triggered by d.c.

ELECTROMAGNETIC FIELDS

Finally, it is worth looking, if only briefly, at r.f.i. generated by the emission of electric and magnetic fields. These fields emanate from devices and conductors handling pulse voltages and currents. The only viable approach to solving the problem is good layout. A few rules, if

applied diligently, will be repaid handsomely; these may be stated as:

- (a) Do keep cable lengths as short as possible.
- (b) Do lump together all pulse-carrying conductors.
- (c) Do not allow these conductors to come into close proximity to supply conductors.
- (d) Do not route cables carrying supplies or outputs near to transformers, chokes and switch transistors.

CONCLUSION

If, in the final analysis, all the foregoing rules are applied, a clean supply is almost certain to be the outcome. The application of a relatively simple filter should then be all that is necessary to make virtually any supply comply with most existing specifications. ★

* *Gould Electronic Power Supply Division*



HEAVY CURRENT ELECTRICITY IN THE UNITED KINGDOM

By Lord Hinton of Bankside,
Pergamon Press

79 pages, Price £5 Hard Cover; £2 Soft Cover

WHILST many of the readers of this magazine are probably aware of the salient milestones in the history and development of electronics throughout its various ramifications, beyond the power socket however, such knowledge is invariably lacking. This fascinating monograph will rectify any such deficiency as it provides a history of heavy current technology from its earliest development up to the time when the industry was nationalised in 1947.

The utilisation of electric power dates from Faraday's paper on electromagnetic induction in 1831 which precipitated the great change in world life style. Sadly, for this country, we lagged behind other industrial countries, both in the structure of an emerging electrical power industry and in the use of electricity.

We read of the stunting restrictions of central government that prevented a prosperous electrical manufacturing industry to be built up and which, no doubt, contributed to Edison's monopolistic incandescent light patent which funded a fortune for the inventor and spawned the giant General Electric corporation.

It was not until the 1926 Act had been passed that it became possible for Britain to have a forward looking electricity supply industry. That Act set up the Central Electricity Generating Board which had the job of creating and operating the national grid, the construction of which was not completed until 1933. However, although the C.E.B. had control over the grid retailing was still done by municipalities and by private companies. Nationalisation in 1947 established a new framework under the British Electricity Authority with ownership of all generating stations and subsequent rationalisation.

A pithy read that doesn't tax the mind. Highly recommended.

G.G.

April Fool? The 10-4 Newsletter is officially published *quarterly* but tends to appear every four months. So, the £1.50 subscription to C.B.A. entitles four issues. Apologies to all.

A.T.

News Briefs

FREQUENCY BY TIME

A HIGH resolution, fully autorange frequency meter, is available from Orbit Controls of Cheltenham, which uses the reciprocal of time period to compute frequency.

Using a central processor, the 75C 501 TIC meter can measure down to 0.0001Hz, and faster than is possible by the more conventional approach. It can display the digital reading in any engineering units required.

TEACHERS TO STUDY

A ONE week course organised by the Department of Electrical Engineering at the University of Salford, is aimed at providing teachers who have some basic knowledge of electronics, with the opportunity to extend that knowledge. Running from July 16-20, 1979, the material covered will be adequate for the electronics option of the JMB "A" level physics syllabus, or other syllabi of comparable standard. It will cover operational amplifiers and integrated logic circuit applications, with approximately half the time being spent on experimental work. Details: The Administrative Assistant (Short Courses), Room 110, Registrar's Dept., University of Salford M5 4WT.

CUT PRICE WATCHES

WE HAVE received from Timetron, a revised price list giving details of some very significant recommended retail price reductions in Casio watches. An example is the 46CS-27B Alarm/Chronograph which in the April/May '79 price list has come down in RRP from £89.95 to £49.95. Timetron are selling this watch for £39.95.

OBITUARY

IT is with regret that we report the death of David Cohen of RT-VC. A well known character in the electronic retail business, David was the sort of straight talking business man with whom you always knew where you stood—we liked him a lot!

RT-VC will continue under the guidance of his son. We offer our sympathy to his family and friends.

WORKSHOP P.S.U

S. HOARE

ONE of the most useful pieces of test equipment for the workshop is a variable output supply for use in testing and setting up new circuits. The design featured in this article was developed to meet the author's requirements. Firstly the power supply should cover a wide range, 0 to 50 or 60V, and to avoid the need for a built-in voltmeter it should be possible to dial up any required voltage. Secondly, the output would have switchable current limiting, and a high maximum current—1A. The current limiting should protect the circuit the power supply is feeding—in this case the power supply switches to standby after excess current. Thirdly, it should be as difficult as possible to get an excess voltage on the power supply output. The fourth requirement is that the power supply should be unharmed by misuse and protected against overheating.

PANEL INDICATORS

The front panel layout is shown in the photograph. Upon switching on the circuit comes on to standby. After setting output conditions the "Output Connect" switch is turned on, and the reset button pressed. If all is well the output comes on and stays on. If not, the output current limits at the value selected, and the supply reverts to standby when the button is released. When changing voltage or working on the equipment being tested the "Output Connect" switch is turned off, completely isolating the output and switching the power supply to standby. If the output voltage is increased with the output connected, the supply again reverts to standby. If the power supply should overheat the warning light comes on and the power supply cannot be reset until the temperature has dropped.

The idea is to make the system "fail-safe", as this is the only way to avoid expensive accidents when setting up new equipment. In practice this arrangement has proved very convenient to use for testing and fault finding.

CIRCUIT ACTION

With the increased availability of cheap i.c.s it seemed obvious that the circuit should be built around one, and the 723 voltage regulator was chosen. The normal way of connecting this is shown in simplified form in Fig. 1. A part of the output voltage is compared with the reference voltage. If the output tends to be low the error amplifier output goes up so the output is maintained. However the 723 will only stand 40V input, giving a maximum of about 36V out.


One way to get higher voltage outputs is shown in Fig. 2. There is a little fiddling to keep the error amplifier working in the correct range, but the only real complication is a separate power supply for the i.c. This, however can be very simple. In each case, the output can be reduced to zero by connecting the frequency compensation terminal to the i.c. negative line—this feature will be used for current limiting and overheating protection. Also, in each case the output voltage is proportional to the "Set Output" resistance, but in Fig. 1 the minimum output is the same as the reference voltage, whereas in Fig. 2 the minimum output is zero.

The V_z output on the i.c. is only provided on the 14 d.i.p. version of the 723, but a metal can 723 could be used with an external 8V Zener diode.

The complete circuit is shown in Fig. 4. Frequency compensation is provided by C1, and the emitter follower transistor (Figs. 1-2) becomes two transistors, TR4 and 5 to provide the required current gain.

As the reference voltage can vary between about 6.8 and 7.5V, preset potentiometers VR2 and 3 have to be provided.

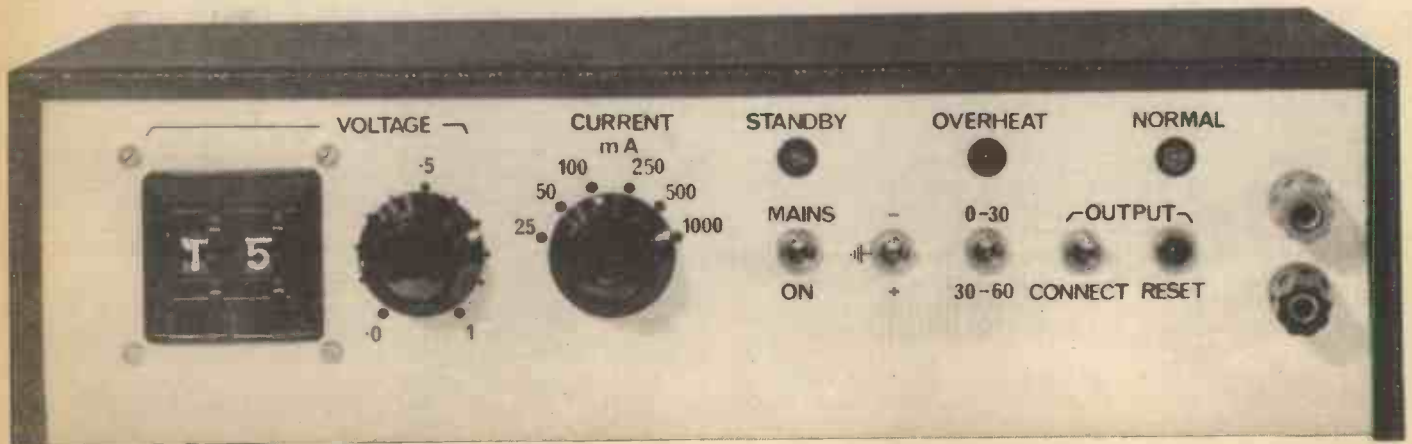Current limiting is provided by sensing the voltage drop across R12 and the resistor selected by the current limit switch, S3. To avoid wasting power, and to avoid an unnecessarily large heat sink on the output transistor a range switch, S8 is used to switch the input to the regulator to about 60 or 35V.



COMPONENTS . . .

Resistors

R1	1k
R2	4k7
R3	1k
R4	3k3
R5	3k
R6	270
R7	5k6
R8	5k6
R9	1k
R10	1k
R11	100
R12	47
R13	47
R14	15
R15	5.6
R16	4.7
R17	4.7
R18	1.2W
R19	220k
R20	47k
R21	2k2 2W
R22	22k
R23	100k
R24	100k
R25-R33	1k 2%
R34-R38	10k 2%

Unless otherwise specified all resistors $\frac{1}{4}$ or $\frac{1}{2}$ watt 5% high stability

Switches

S1	Push-button push to break
S2	2 decade thumbwheel edge switch (see text)
S3	2 pole 6 way rotary
S4	Single pole double throw toggle (EV Type S7101)
S5	Double pole double throw toggle (EV Type S7201)
S7	Double pole double throw toggle (EV Type S7201)
S8	Single pole double throw toggle (EV Type S7101)

Potentiometers

VR1	1k horizontal preset (Type PR15)
VR2	1k horizontal preset (Type PR15)
VR3	1k horizontal preset (Type PR15)
VR4	1k linear wirewound (see text)

Capacitors

C1	1n disc ceramic
C2	1 μ 63V electrolytic
C3	47 μ 63V electrolytic
C4	2,200 μ F 100V electrolytic
C5	470 μ F 25V electrolytic
C6	220p ceramic plate

Semiconductors

IC1	723, d.i.l. voltage regulator
TR1	OC81
TR2	BC184L
TR3	BC184L
TR4	2N5192
TR5	2N3055
TR6	BC184L
TR7	BC184L
D1	1N4148
D2	TIL209 Green
D3	TIL209 Red
D4	1N4002
D5	1N4002
D6	1N4002
D7	1N4148
D8	1N4148
D9	TIL209 Green
REC1	Diode bridge 2A 100V r.m.s.
REC2	Diode bridge 0.5A 40V r.m.s.
D10	33V 400mW Zener
D11	1N4148
D12	1N4148
D13	1N4002
R25	VA1100

Transformers

T1	0-25-40-50V 1A (EV Type GP501)	} Mains
T2	6-0-6V 100mA (EV Type 606/1)	

Heatsinks

(For TR4)	17°C/W (EV Type TV4)
(For TR5)	2°C/W (EV Type 10DN400)
(For TR1)	Clip type (EV Type A1031)

Fuses

FS1	500mA 20mm
FS2	1.5A 20mm

'EV Type' references refer to components available from Electrovalue Ltd., 28 St. Judes Rd., Englefield Green, Egham, Surrey, TW20 0HB. The cabinet is a 'Norman', Type WB4, size 280 x 150 x 75mm approx.

Normally the difference between the input and output is less than about 33V, so TR7 is not drawing current, and the voltage at the base/emitter junction of TR6 plus D8 has to reach about 1.2V before TR6 draws any current, and makes the output fall. If the input is much more than 33V higher than the output, because the supply is set to high range and is current limiting (or incorrectly set to high range when a low voltage is selected) there is a risk of excessive power being dissipated in TR5. To avoid this TR7 switches on and shorts out D8, so that current limiting occurs when TR6 base is +0.6V, and the maximum current is halved.

CONTACT RESISTANCE

R18 is shown as 1 ohm rather than 1.2 because the wiring and switch resistance of the prototype was about 0.2 ohms. As the contact resistance of the current limit switch could be a problem in time it is a good idea to wire two

switch sections in parallel on the 1A range as shown. (This is "fail-safe" as higher resistance will reduce the maximum current.)

Reference to the 723 published data will show that there is already a current limit transistor equivalent to TR6 provided to do the same job. However, the rating of this transistor is inadequate in this configuration so an external device is used.

STANDBY

In Figs. 1 and 4 the voltage at point "x" is 0 when the output is stabilised. This point is sensed in the circuit by TR3. If the output voltage drops, for example, due to the onset of current limiting the voltage at the base of TR3 goes positive. When it reaches 0.6V TR3 conducts and pulls down the output of the stabiliser, and D2 ("Standby") comes on.

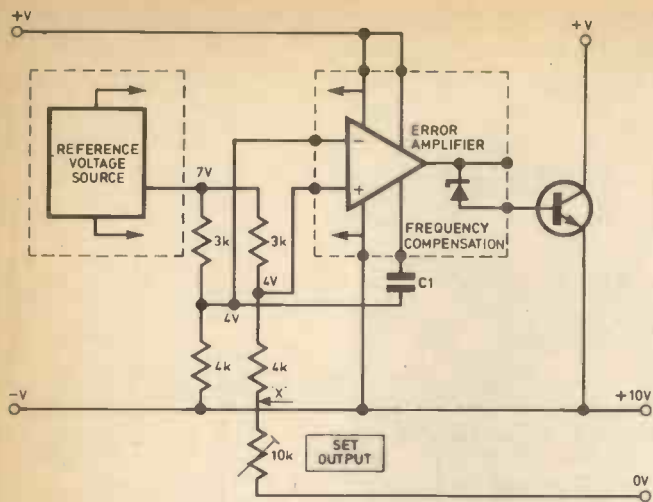


Fig. 1. Operation of the 723 voltage regulator. Area within dotted lines indicates i.c.

Once this has happened the output will stay low, and can only be reset by opening S1, the "Reset" button. In practice, R6 is included to make the normal voltage at "x" about 0.3V, so that the detection of lack of stabilisation is more sensitive. When S2 is operated it will often go open circuit as it switches. In this situation the voltage at "x" goes positive, and the stabiliser goes to "Standby", whereas in a conventional circuit the output would start to rise to full voltage. If the new setting is to a higher voltage "x" goes positive and the stabiliser goes to "Standby".

OVERHEAT

The "Overheat" circuit has a temperature sensor mounted on the heat sink of TR5. The author is not aware of any cheap universally available thermistor designed for this job, so a germanium output transistor, TR1, is used (OC81 in prototype).

The leakage current of a germanium transistor is enormously temperature sensitive, and in this case a vice can be turned into a virtue! Although transistors are obviously not designed for this job, general purpose germanium types should work in this circuit.

If in a given case the leakage is too low, the base can be

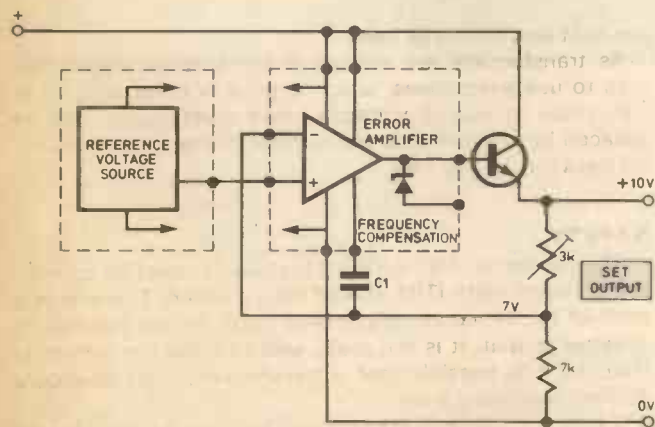


Fig. 2. High voltage operation of the 723 regulator

left open circuit. The output of the overheat circuit is connected to pin 13 of the i.c. after the "Reset" switch, so that in the event of overheating the output cannot be brought on.

NORMAL INDICATION

The "Normal" diode D9 is connected to indicate actual output voltage, so D5 and 6 are needed to make sure that it comes on at 1V. Although the l.e.d. is not very bright below about 5V this was thought to be a useful indication of correct operation, and the extra complication of constant current circuits does not seem worth while. Incidentally D5 and 6 also protect the power supply against reverse voltages.

With the component values shown the output is 1V for every kilohm selected by S2. As shown this is a two decade thumb wheel edge switch, plus a 1 kilohm linear wirewound potentiometer for fine control. However, any desired alternative may be used.

Possibilities that come to mind are a 10 turn potentiometer, or a 12-way switch giving 3V steps, and a +30V switch, which could be the same switch as the range switch. However, a reasonably good quality switch should be used, as should it go permanently open circuit the stabiliser output could be reset to maximum. (An intermittent open circuit, which is much more likely, would merely put the output to standby).

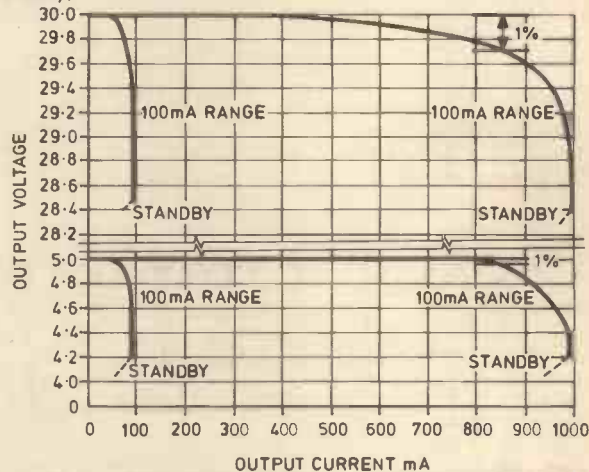


Fig. 3. Graphs showing workshop power supply unit's voltage regulation

The power dissipated by TR5 is the difference between input and output voltage, multiplied by the maximum current, and could be up to about 40W. To cope with this a heat sink with a thermal dissipation of about 2°C/W is indicated.

The maximum dissipation from the heat sink will only be achieved if the fins are mounted vertically in free air—that is, on the outside of the back panel.

It helps a little if the heat sink is painted matt black, and a smear of silicone grease must be used on both sides of the insulating washer for TR5. In practice the back panel of the case will dissipate some heat, and the prototype using the specified heat sink cut down from 4 to 3 inches runs quite cool, but it is not recommended to reduce the heat sink much more. TR4 runs at the power of TR5 divided by the h_{FE} of TR5—a maximum of about 2W. This power is comfortably dissipated by a small heat sink mounted on the circuit board.

The whole circuit depends on TR5 dissipating the necessary power with low leakage. The 2N3055 is not expensive, and to use a lesser transistor, or one of dubious origins, is asking for trouble.

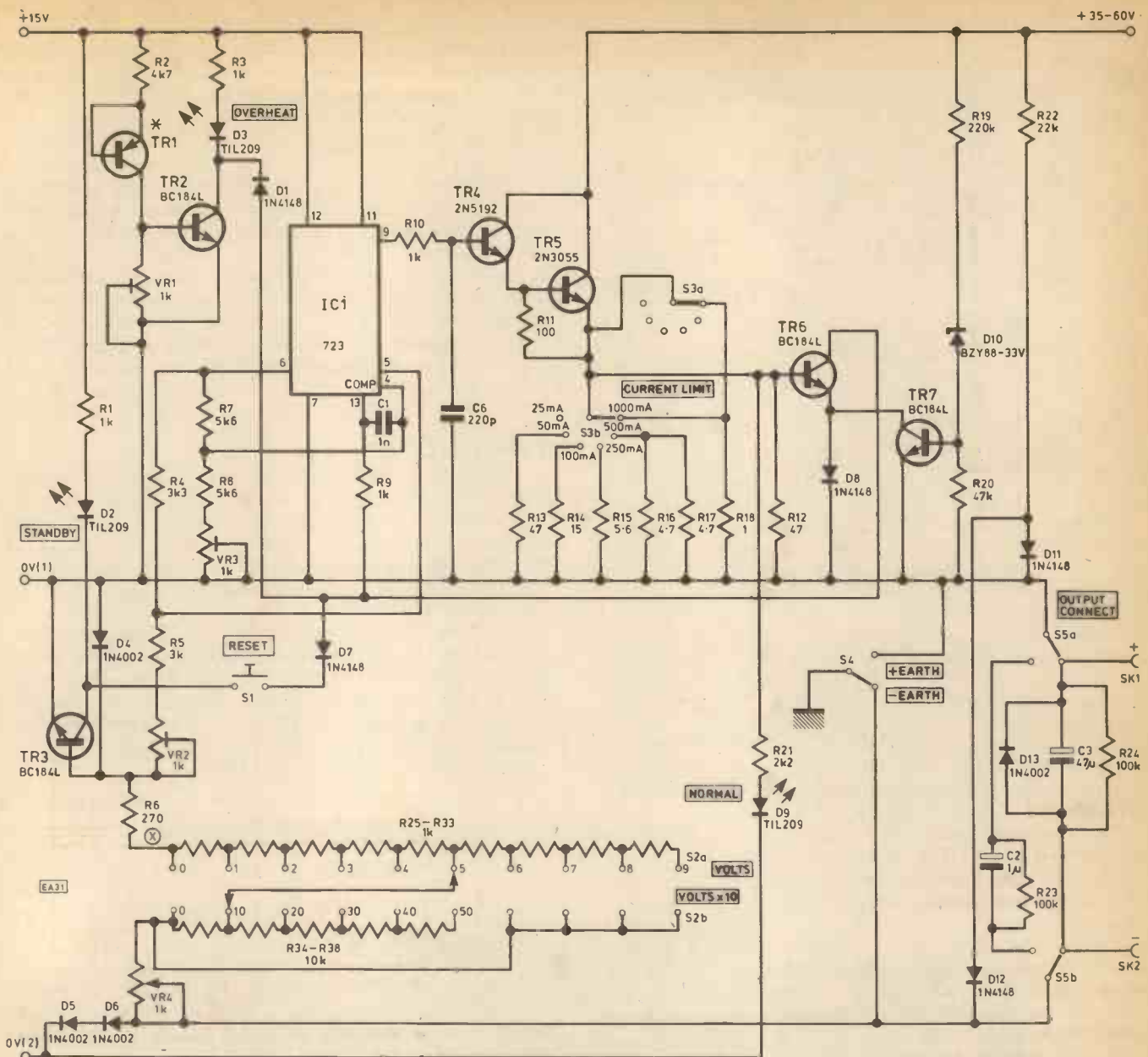


Fig. 4. P.s.u. circuit

RECTIFIER CIRCUIT

The stabiliser circuit is fed from the rectifier circuit of Fig. 5. Ironically, the compromises in the circuit have been made here, for the sake of specifying components that are universally available at a reasonable price. As the range switch is before the reservoir capacitor a thermistor is included to reduce the switching surge to reasonable proportions. However, this must increase the amount by which the power supply sags at high current.

The highest voltage rating of large electrolytic capacitors at a reasonable price is 63V, which is just above the 60V obtained at low loads using the 40V tapping of the specified transformer. However, at a continuous load of 100mA this drops to 56V, and at 1A to 45V. The maximum output voltage is about 3V less. As equipment to be tested will rarely demand continuous high current as well as high voltage, this compromise seems reasonable. However, for those who refuse to compromise, the alternative is to use a 2N3442 for TR5. Then the high range can use the 50V output of T1 which should be rated at 2A. In this case the full

size heat sink should be used.

As transformers are expensive some constructors may wish to use alternatives, which is quite in order as long as the actual measured voltages prove suitable. T2 can be replaced by any available transformer giving a rectified output between 14 and 18V.

SAFETY

The cabinet and all exposed metalwork must be connected to mains earth (TR5 should have a cover). The output is earthed by S4 connecting mains earth to the positive or negative output. It is not really safe to allow the output to float, as it is possible that a transformer could develop a primary/secondary short.

If both transformers are replaced by types having a screen between primary and secondary a floating output becomes permissible.

The fuses are not made accessible from the outside as their failure would indicate a fault within the power supply.

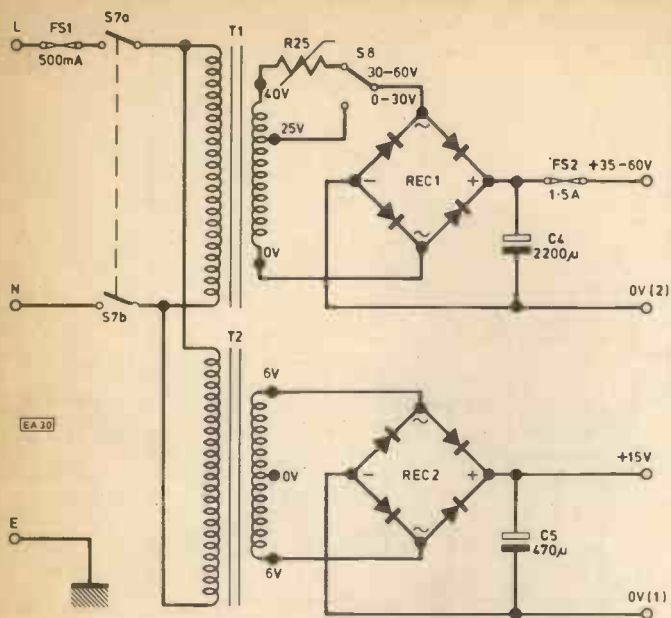


Fig. 5. Bridge supplies for main circuit

STABILITY

The inherent stability of the 723 regulator is very high (a fraction of 1% in most circumstances), so the accuracy achieved depends largely on the components used. The absolute value of R4-R8 is not important as long as they do not vary. Thus 5% high stability resistors are good enough for this application. The resistors R25-R33 for the 1V steps are critical, but a 5% error represents only 50mV, which is close enough for most purposes.

When a nine is dialled up, however, nine of these resistors are in series, giving a possible error of 450mV. Statistically the error in this case should be much less than 5%, but the extra expense of 2% resistors is probably worthwhile. The resistors R34-R38 for 10 volt steps should however normally be 2%.


The preset potentiometers VR2 and 3 are a potential weak link, but they only make up a small part of the total resistance. If preferred they could be replaced by multiturn preset potentiometers.

For the minimum thermal drift in the i.c. the resistances seen by the inverting and non-inverting inputs should be equal. This is achieved at about 15V, but the unbalance at other voltages is not great enough to cause difficulties, as the i.c. does not dissipate enough heat to run at all hot.

CONSTRUCTION

The general construction of the prototype can be seen from the photographs. The circuitry is mounted mostly on two pieces of Veroboard corresponding to Fig. 6 and Fig. 7. The layout for the rectifier circuit is given in Fig. 7. Layout for the stabiliser, Fig. 4, is given in Fig. 6. This uses rather a large number of links, and could probably be improved upon, but the extra expense of a printed circuit board does not seem warranted. It is recommended that Veropins should be used for external connections, as this makes assembly easier and reduces the likelihood of short circuits between tracks. The construction must be of a high standard if expensive disasters are to be avoided. In particular beware of whiskers of solder or removed copper getting between tracks.

The i.c. should be mounted in a holder.

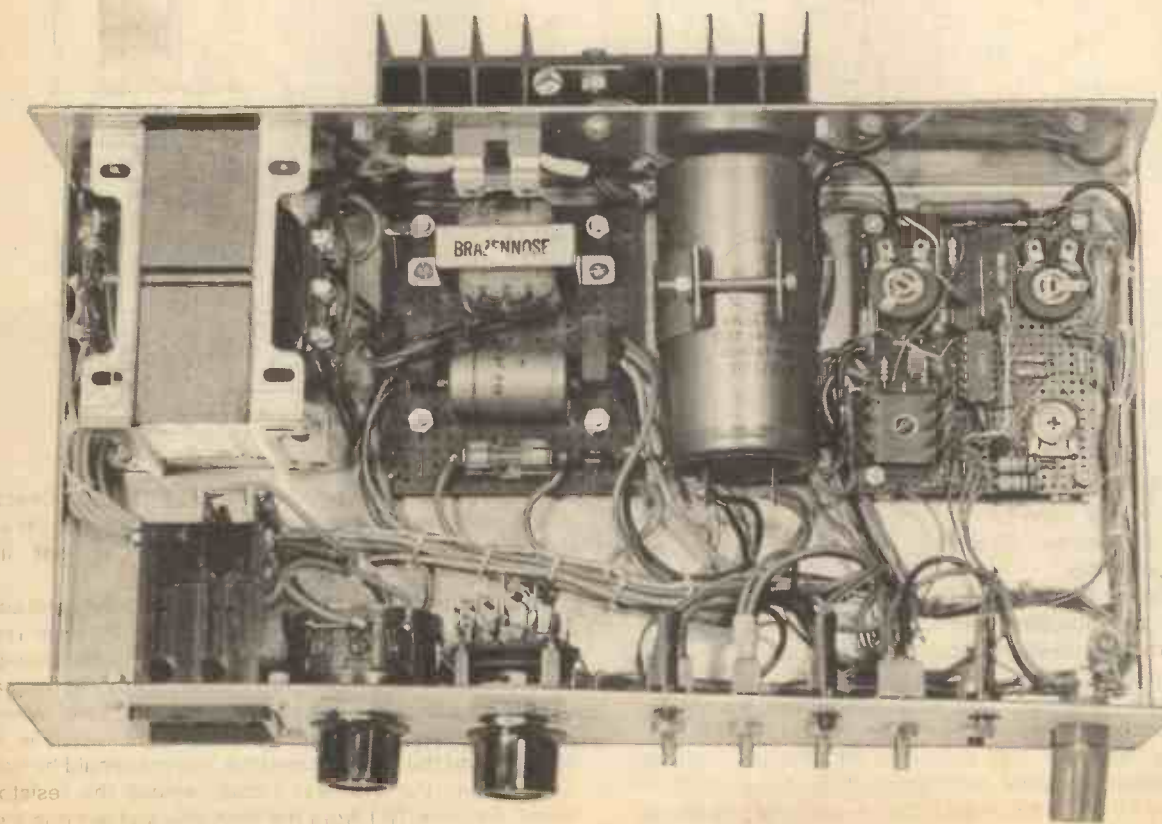

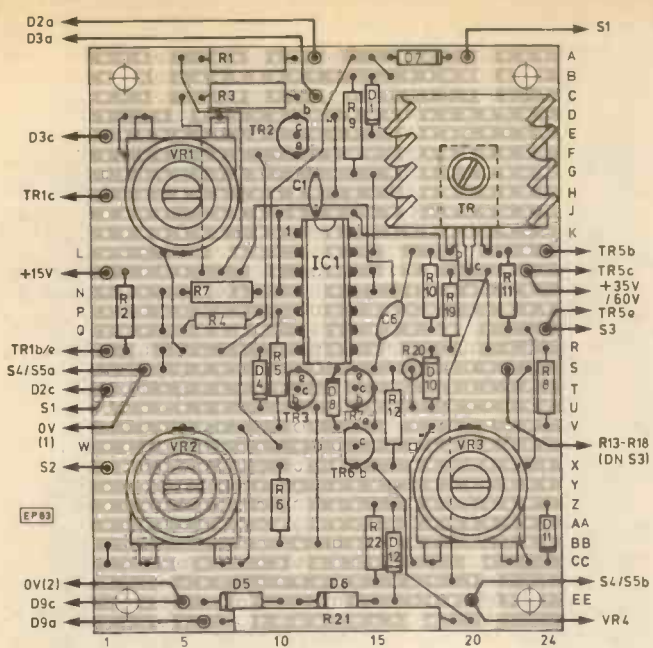


Fig. 6. Stabiliser circuit

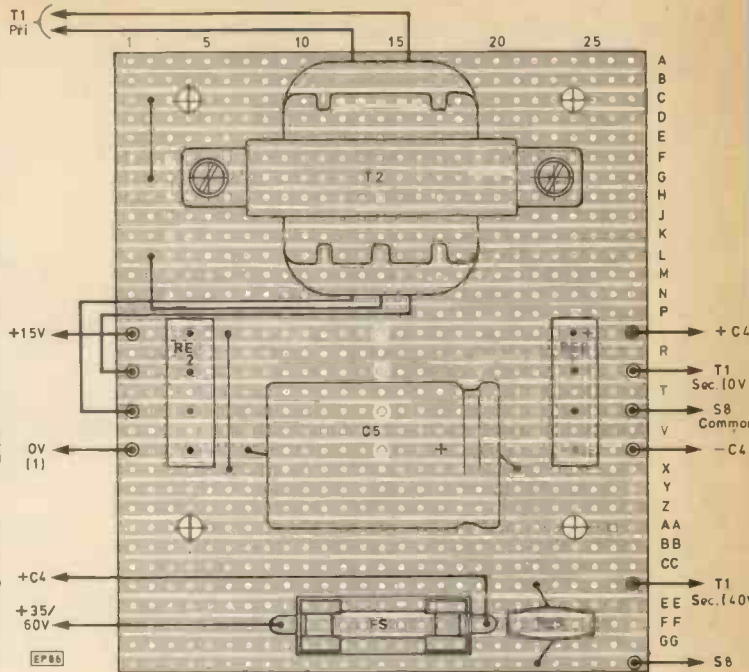


Fig. 7. Supply board T1 and C4 are elsewhere chassis mounted (see photograph)

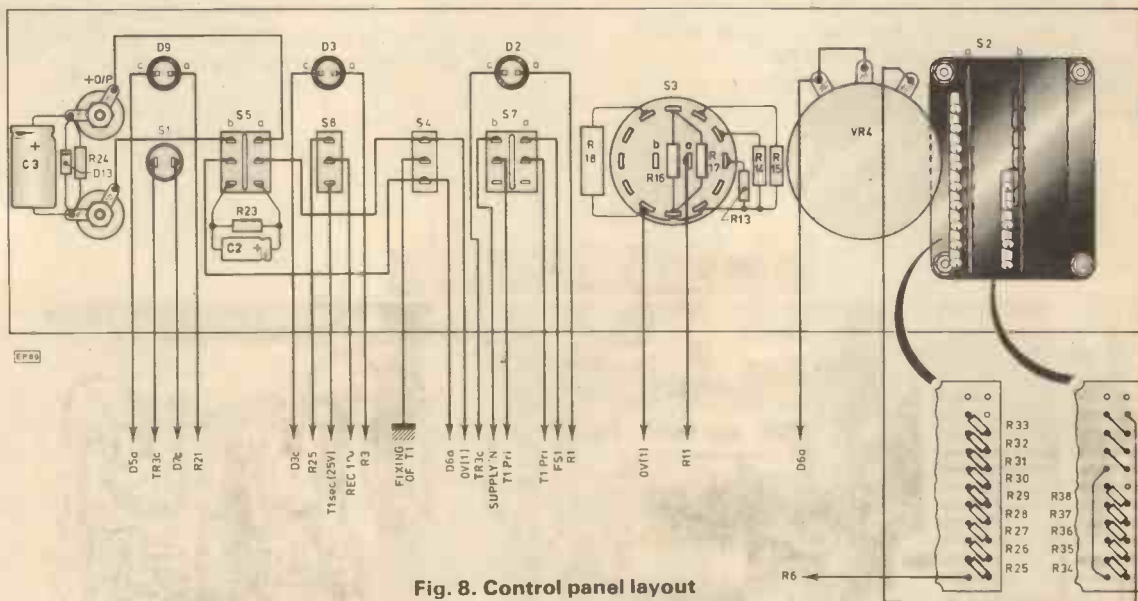


Fig. 8. Control panel layout

SETTING UP

If the unit has been built properly there should be no snags, but it is worthwhile testing methodically just in case something is wrong.

It is advisable to build and test the rectifier circuit before connecting the stabiliser circuit. Before connecting TR5 check that there is no short circuit to the heat sink.


Switch to 20V, 25mA, low range, "Connect" turned on, and connect a voltmeter to the output terminals. Switch on, and the standby light should come on. Press the reset button, and the "Standby" light should go off, "Normal" light on and the voltmeter should read about 20V. Adjust VR2 to correctly set 1V and VR3 to set 20V—repeat the process as

necessary as the two controls interact. Check for overheating (at this point the overheat circuit is not set up, so if necessary adjust VR1 so that the "Overheat" light is off).


To check the current limit select 10V, 25mA, and connect a meter set to 100mA in series with a 220 ohm resistor. Press the "Reset" button—the "Standby" light should stay on, and the meter should read 25mA approx., as long as the "Reset" button is pressed, dropping to zero when the "Reset" button is released. If the range switch is set to 30–60V and the test repeated the current should be halved.

To set up the overheat circuit remove the resistor and meter. Remove TR1 from the heat sink and put it in a cup of


VIEWS INSIDE . . .

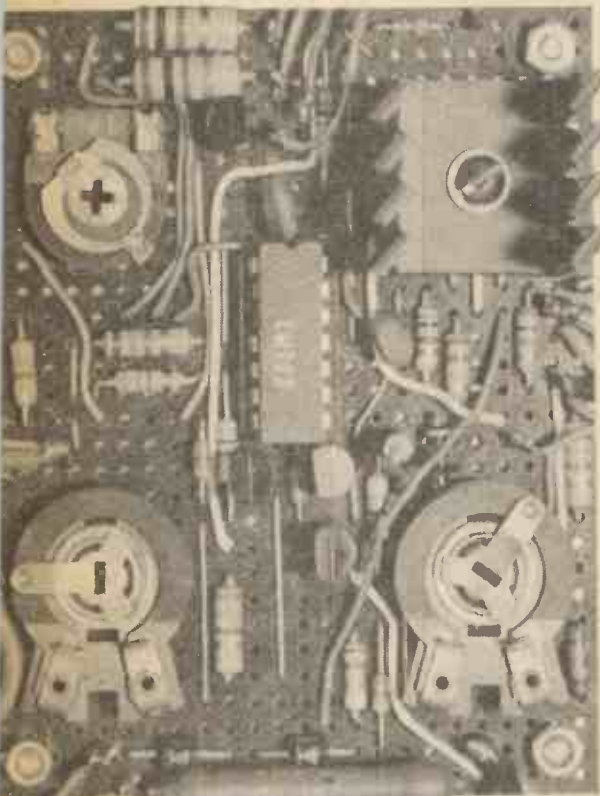

(a)

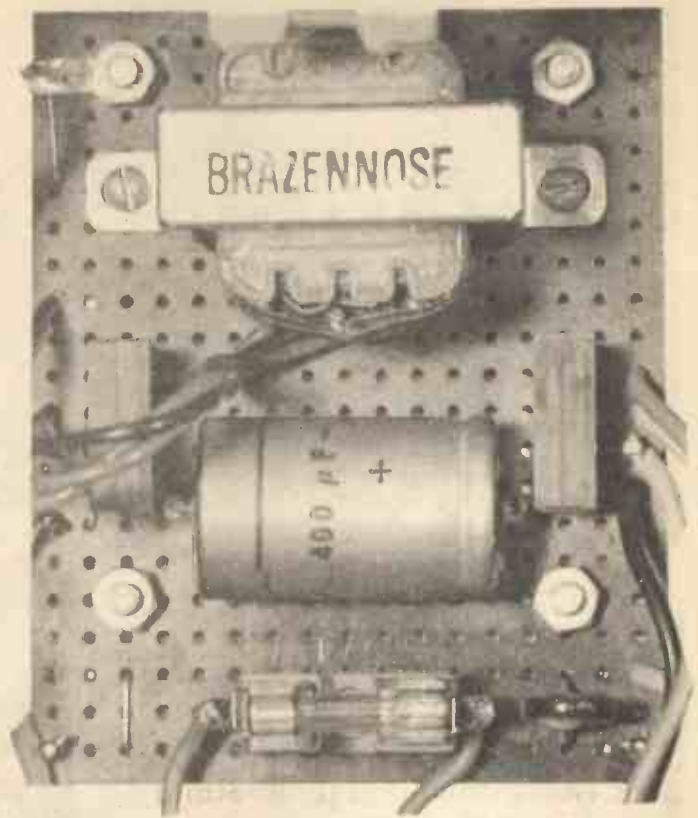

(b)

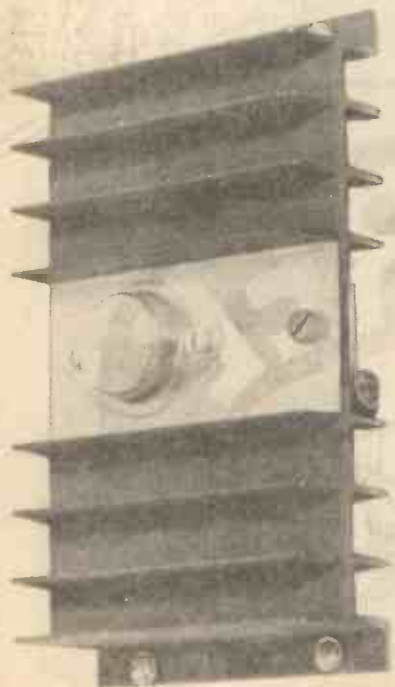

(c)

Fig. 9 (a) Stabiliser Veroboard (b) Supply Veroboard (c) Showing mounting of OC81 sensor below TR5's heatsink

almost boiling water (just dip the can of the transistor in the water, not the leads). Switch on and press the "Reset" button. Increase VR1 from minimum resistance until the "Overheat" light and the "Standby" light both come on. Check that the "Reset" button is inoperative. Switch off and reconnect TR1 to the heat sink.

If all is well the unit can be tested at higher current. The hardest test is low output voltage at maximum current. If all is still well set to high range, where the hardest test is about 30V at maximum current. Also check that TR4 and the i.c. are not overheating.

Now test for leakage in TR5, which is shown by a voltage on the output, and thus a slight glow in the "Normal" light when the circuit should be in "Standby", especially on the high range. If all is well get TR5 hot by running at low output voltage, high current for some time until it is on the verge of overheating. Turn off the "Connect" switch, and check that the "Normal" light is completely off.

Give the power supply a good soak test, and if necessary slightly adjust VR2 to correct the output at 1V and VR3 to correct the output at 50V. Check that the output is correct at other voltages, and check the current limit on all ranges. ★

LOOK!

Here's how you master electronics.

.... the **practical** way.

This new style course will enable anyone to have a real understanding by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to further your career in electronics or as a self-employed electronics engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write, at any time, for advice or help during your work. A Certificate is given at the end of every course.


1. Build an oscilloscope.

As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.



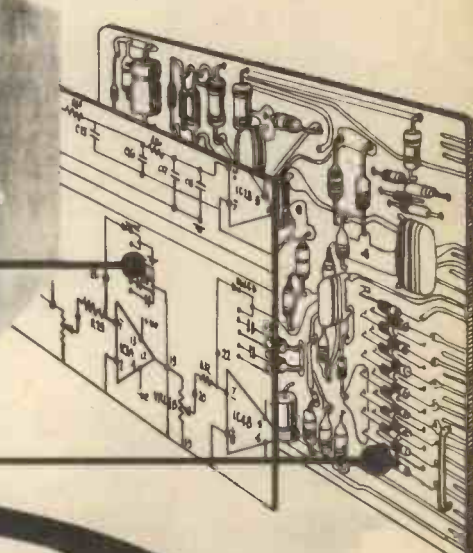2. Read, draw and understand circuit diagrams.

In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.



3. Carry out over 40 experiments on basic circuits.

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

4. Free Gift.

All students enrolling in our courses receive a free circuit board originating from a computer and containing many different components that can be used in experiments and provide an excellent example of current electronic practice.

FREE

Post now, without obligation, to:-

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL


P.O. Box 156, Jersey, Channel Islands.

NAME _____

ADDRESS _____

PEB 6/79

Block caps please

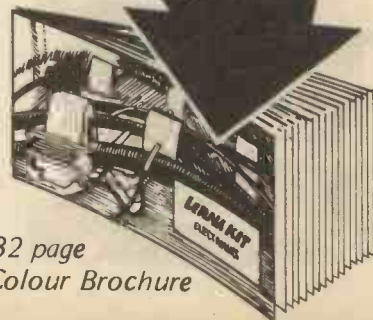

32 page
Colour Brochure

SAXON ENTERTAINMENTS

P.A. & DISCOTHEQUE
EQUIPMENT AT
INCOMPARABLE PRICES

STANDARD CENTAUR 100W

£249 +Carr £15 & VAT £21.12 Deposit **£57.12**
12 months @ £21.94 or 24 months @ £12.54

SUPER CENTAUR 200W

£299 +Carr £15 & VAT £25.12 Deposit **£68.12**
12 months @ £26.19 or 24 months @ £14.90

GXL 200W

With Twin 200 Watt Cabinets

£389 +Carr £15 & VAT £32.32 Deposit **£87.32**
12 months @ £33.64 or 24 months @ £14.90

GXL WITH PDF BINS (illus)

£417 +Carr £15 & VAT £34.56 Deposit **£93.56**
12 months @ £36.36 or 24 months @ £20.81

CUSTOM CENTAUR 400/600W WITH FOUR PDF 100A BINS

£699 +Carr & VAT £57.52 Deposit **£155.52**
12 months @ £60.54 or 24 months @ £34.66

CENTAUR

STEREO DISCOS
C/W LIGHT SHOW & DISPLAY
TWIN LOUDSPEAKERS & LEADS
100W-600W

20%
DEPOSIT
CREDIT
TERMS



6XL + PDF BINS

- ★ 2 Year warranty
- ★ Full Mixing + Crossfade + Mic/Tape Inputs
- ★ Headphone & Cue Light Monitoring
- ★ Full Range Bass/Treble Controls + Mic Tone
- ★ 4 Channel Soundlight + Display

JUST PLUG IN AND GO!!
SEND TODAY FOR YOUR FREE BROCHURE

MINI DISCO 100 WATT

MONO SYSTEM WITH LOUDSPEAKERS

£179.50 +Carr £15 & VAT £15.56 Deposit **£42.06**
12 months @ £16.22 or 24 months @ £9.24

P.A. SYSTEMS

2 YEAR GUARANTEE

100 WATT **£159.90**
+Carr £15 & VAT £13.99 Deposit
12 months @ £14.77 or **£37.89**
24 months @ £8.48

- ★ Four Mixing Inputs
- ★ Bass & Treble Controls
- ★ Twin Piezo Horn Columns

200 WATT **£249.00**
+Carr £15 & VAT £21.12 Deposit
12 months @ £22.23 or **£57.12**
24 months @ £12.73

AMPLIFIER UNITS ONLY

AP100 AMPLIFIER

£49.50 +Carr £1.50 & VAT £3.96

- ★ 4 Mixed Inputs
- ★ Bass/Treble Controls
- ★ Vynide Case
- ★ 100 Watts Output

AP200 AMPLIFIER

£89.50 +Carr £1.50 & VAT £7.16

- ★ Six Mixed Inputs
- ★ Three Sets Bass/Treble
- ★ 200 Watts Output
- ★ Slove Socket



NEW SAXON KLAXON

UK Police - Hawaii 50
US Police Destroyer

Four Sirens in one package **£17.50** + VAT £1.40

Individual Sirens **£7.50** + VAT 60p

NEW SAXON SMASH

ALIEN VOICE SIMULATOR

Add a new dimension to your disco with this press button effect unit
Insert between mic & amp **£7.50** + VAT 60p

PLUTO PROJECTORS

P140 **£38.50**
150 WATT
INC WHEEL

P5000 **£89.50** + VAT £7.16
250 watt Q.I. inc Cassette/Wheel
(Full range of wheels - ask for list)



ELECTRECT MIC DI501 **£18.50***
TOP QUALITY UNIT + VAT £2.31

ECM105 LOW COST ELECTRECT
CONDENSER MIC + VAT 62p **£5.00***

MELOS CASSETTE ECHO-
REVERB UNIT - Twin input
VARIABLE SPEED & DEPTH + VAT £5.20 **£65.00**


AMPLIFIER MODULES

- 30Hz-20kHz
- Short/open circuit proof
- Top grade components
- Suit most mixers



SA308 8 ohms 30W 45V **£10.75*** + £1.34
Supply for 2 modules **£11.90*** + £1.49
SA604 4 ohms 50V **£14.50** + £1.16
Supply for 1 or 2 modules **£14.95** + £1.20
SA608 8 ohms 60W 65V **£15.50** + £1.24
Supply for 1 or 2 modules **£14.95** + £1.20
SA1204 4 ohms 120W 75V **£17.50** + £1.40
Supply for 1 module **£14.95** + £1.20
SA1208 8 ohms 120W 95V **£21.00** + £1.68
Supply for 2 modules **£24.75** + £1.98

DISCO MIXERS - COMPLETE OR MODULAR

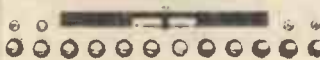

MONO OR STEREO WITH AUTOFADE

Available complete and ready to plug in or as an easy to connect module with all controls except monitor switch already fitted - full instructions supplied.

FEATURES INCLUDE:
Twin Deck - Mic & Tape Inputs - Wide range bass & treble controls - Full headphone monitoring - Crossfade - Professional standard performance.

COMPLETE MIXERS

(with case)
Mono mains **£45.75** + £3.66
Stereo mains **£63.75** + £5.10

MODULES

Mono module **£27.50** + £2.20
Stereo module **£37.50** + £3.00
Panel **£3.95** + 32p
Kit of knobs/sockets etc **£5.50** + 44p

D.I.Y. MODULES FOR P.A. SYSTEMS

MONO/STEREO


Input Modules
Mono PCB only **£6.50** + 52p
Stereo PCB only **£10.50** + 84p

Mono C/W
Front panel **£9.50** + 76p
Stereo C/W
Front panel **£13.75** + £1.10

Mixer/Monitor Modules
Mono PCB only **£6.50** + 52p
Stereo PCB only **£10.50** + 84p


Mono C/W
Front panel **£9.50** + 76p
Stereo C/W
Front panel **£13.75** + £1.10

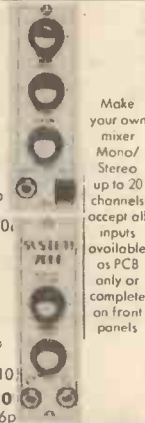Power supply to suit **£9.50**
send for full details. +VAT 76p



Make your own mixer Mono/ Stereo up to 20 channels accept all inputs available as PCB only or complete on front panels

SOUND-TO-LIGHT UNITS

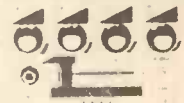

3 CHANNEL - 3kW **£29.50** + VAT £2.36

- Operates from 1W upwards
- Bass/middle/treble/master controls + £1 carr complete

Module only **£19.75** + VAT £1.58
Panel **£2.95** + VAT 24p

4 CHANNEL - 4 kW SOUND-LIGHT SEQUENCER (illus)
£39.50 Carr £1 + VAT £3.16

- Dimmer on each channel
- Automatic sound light level
- Logic circuitry throughout

Module only **£26.75** + VAT £2.14
Panel **£2.95** + VAT 24p

MOTOROLA PIEZO HORNS **£4.50. YES!!** + VAT 36p

FUZZ LIGHTS Red, Blue, Yellow, Green **£22.80** + VAT £1.82

HEAVY DUTY SPOT BANKS - MATCHES LOUDSPEAKERS
3 way 600W **£35.50** 4 way 800W **£39.50** Carr £2 + VAT £2.84 + VAT £3.16

100W SPOTS
Red - Blue - Amber - Green **£1.50 ea.** + VAT 12p

CABINET FITTINGS
ICI Vynide 50" wide **£3.50m** + VAT 28p
Kick-res grille 50" wide **£3.50m** + VAT 28p
Neflon kick proof 24" wide **£3.50m** + VAT 28p
Corners/feet/recess plates 15p ea. + VAT 1p
Recess handle 45p + VAT 3p
Bar handles **£2.50** + VAT 20p
Jack plugs/sockets 25p + VAT 2p

LOUDSPEAKER CABINETS - COMPLETE WITH LEADS

- Fitted with 100W 17,000 Gauss drivers
- Rugged cabinets with aluminium trim - black vynide etc
- Lifetime guarantee on main drive unit

Standard 100W 1 x 12 (48 x 41 x 24) **£39.00**
Carr £3 + VAT £3.12
Large 100W 1 x 12 (65 x 48 x 24) **£49.50**
Carr £3 + VAT £3.96
P.A. 1 x 12 (+ 2 Piezos) (80 x 38 x 24) **£66.50**
Carr £3 + VAT £5.32
P.A. 2 x 12 200W (100 x 38 x 24) **£99.00**
Carr £3 + VAT £7.92
Disco 2 x 12 200W (80 x 63 x 24) **£85.00**
Carr £3 + VAT £6.80
PDF reflex bin (80 x 40 x 41) **£95.00**
Carr £3 + VAT £7.60

PDF100 Reflex Bin - Twin Horns - Integrated Slave Amplifier - Accepts mono or stereo signals

- Use with all types of mixer
 - Pan and volume controls
 - Send for details
- £130** Carr £3 Deposit **£28.40** + VAT £10.64

All prices subject to 8% VAT except where asterisked (12 1/2%) Shop premises open Tues to Sat 9 am - 5 pm
Lunch 12.30 - 1.30 pm Mail order dept open Mon to Fri 10 am - 4 pm Ring 01-684 6385

TO ORDER

By Post Send your requirements with cheque crossed P.O. or 60p COD charge to address below or just send your Access or Barclaycard Number NOT THE CARD.


By Phone You may order COD, Access or Barclaycard. Post & Packing 50p on all orders except where stated.

SAXON ENTERTAINMENTS

327 Whitehorse Road, Croydon, Surrey.

All Enquiries Large SAE Please Brochures on request

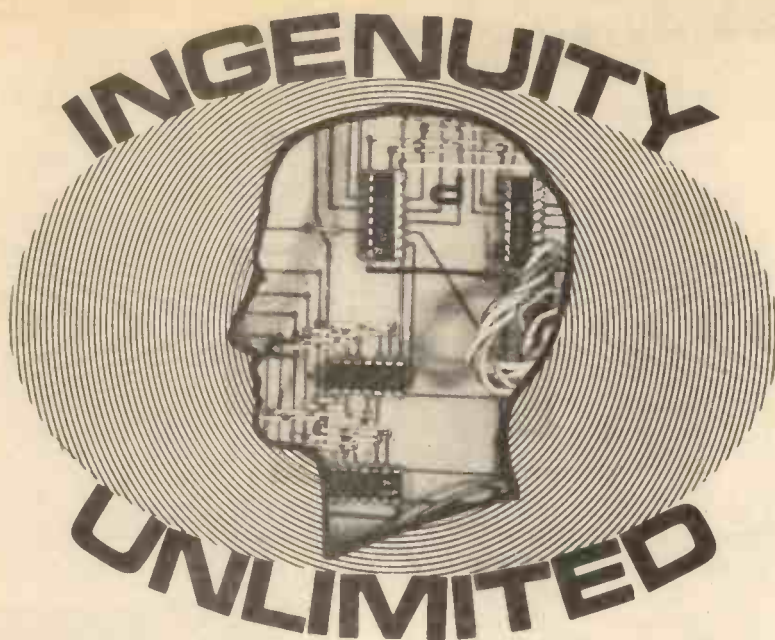MANCHESTER DISCO CENTRE, 237 DEANS GATE, MANCHESTER
CALLERS ONLY - (061) 832 8772 - COMPLETE UNITS ONLY




A selection of readers' original circuit ideas. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought.

Why not submit *your* idea? Any idea published will be awarded payment according to its merits.

Articles submitted for publication should conform to the usual practices of this journal, e.g. with regard to abbreviations and circuit symbols. Diagrams should be on separate sheets, not inserted in the text.

Each idea submitted must be accompanied by a declaration to the effect that it is the original work of the undersigned, and that it has not been accepted for publication elsewhere.

LOW COST THERMOMETER

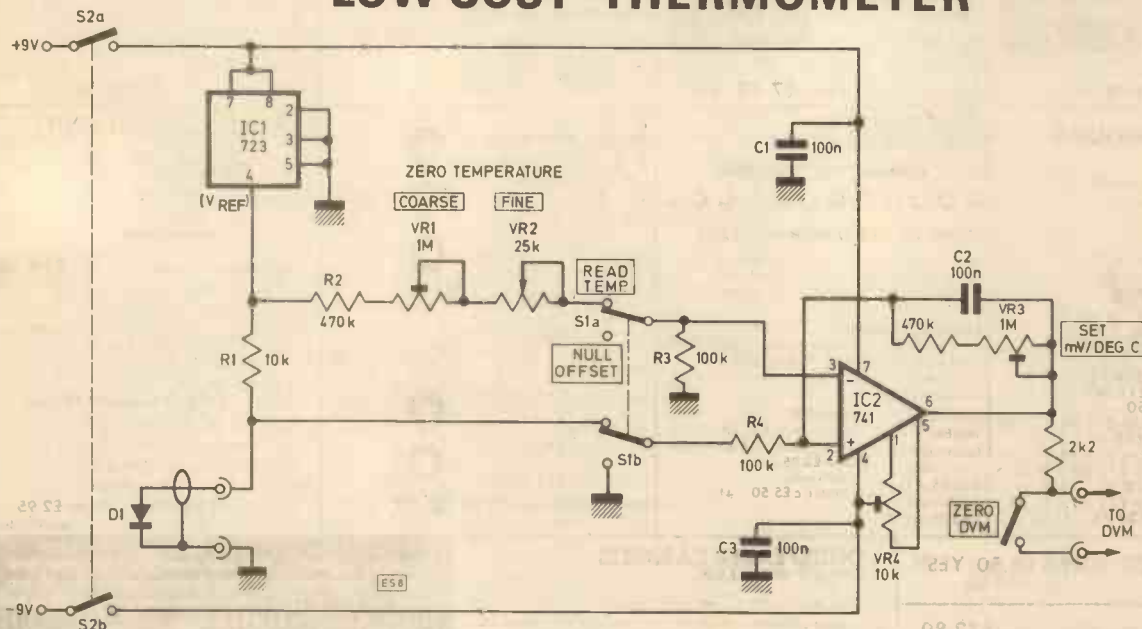

THIS circuit was designed as a cheap thermometer utilising an external $3\frac{1}{2}$ digit DVM providing readings of $20 \text{ mV}/^\circ\text{C}$. Whilst making no total claim for originality, I was impressed by the stability of a 741 used as a d.c. amplifier of fairly high sensitivity. The nearest commercial equivalent would have cost over £120, and would not have been very suitable (for an enzyme kinetics experiment).

On the basis of the success of this circuit, I might try extending the use of 741s

in laboratory applications where, commercially, chopper amplifiers are used. It would not be too difficult to make a chopper-stabilised amplifier with 741s and analogue gates. D1 (any small silicon diode) was minimally insulated with epoxy resin, for good thermal conductivity. Once the 741 offset had been nulled at the appropriate ambient temperature (R3 and R4 maintain approximate offset current balance), it drifted by $<1 \text{ mV}$ over several months.

The temperature was zeroed in

ice/water every few hours (drift $<\pm 3 \text{ mV}/5 \text{ hr}$). Response was very linear and repeatable over the operating range of $0\text{--}50^\circ\text{C}$, and accuracy was probably limited by the calibration (accurate to 0.1 deg C). D1 dissipates $300\text{--}400 \mu\text{W}$, and self-heating may not always be negligible. The $+9 \text{ V}$ supply is a minimum safe value for the 723 for a stable V_{ref} .

B. J. Fowler,
Dept of Biochemistry,
Liverpool Polytechnic.


GUITAR FUZZ/SUSTAIN UNIT

COMMERCIAL guitar effects are usually very highly priced and therefore a circuit which offers two useful effects cheaply must be very appealing to most guitarists. The circuit shown is cheap to build and gives the ever-popular fuzz effect as well as sustain.

This design can be built either as a separate unit or is small enough to be inserted directly inside the guitar body.

A standard pre-amp consisting of TR1 enables even very low output guitars to be used successfully. The amplified signal is then fed to an op-amp IC1 via C1. Because of the high gain the waveform will be severely clipped. With S1 in the "fuzz" position the signal will be attenuated by R10 and taken to the output.

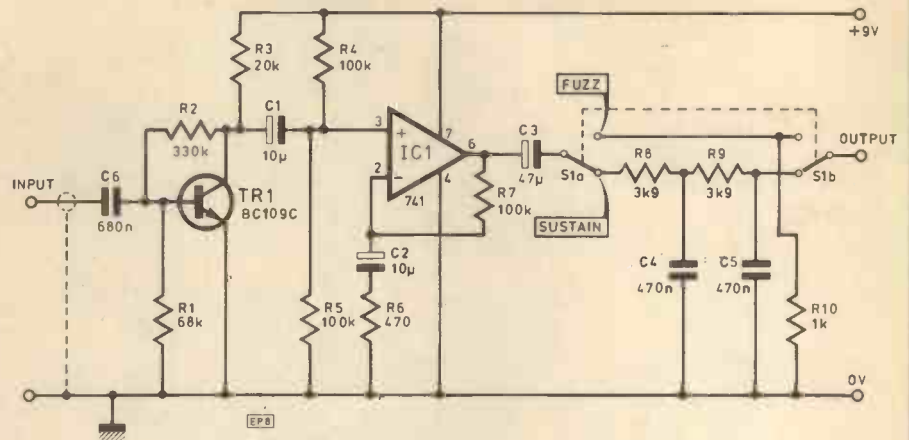With S1 in the "sustain" position the output from IC1 will be attenuated and modified by the two stage RC network R8 C4 and R9 C5. This will remove most of the high order harmonics formed by the clipping to leave a sound more like the original. Sustain will be present because during the time clipping occurs the output level will remain constant independent of the input.



Should any residual fuzz sound at output be a nuisance then adjustment of the amplifier tone controls for maximum bass and minimum treble will eliminate it.

Battery drain is below 1mA so a PP3 battery would make a compact power source. The high gain of the circuit may cause several problems: the circuit should be laid out in a logical manner to avoid instability and positive feedback.

The input lead should be screened to prevent hum and radio pickup. Owing to the increased sensitivity the guitarist should use his hand to damp the strings not being played. Guitar volume and tone controls should, of course, be left at maximum.

A. Niemiro,
Welwyn Garden City,
Herts.

LAMP DIMMER

MANY lamp dimmer circuits suffer from several drawbacks:

- (1) Power consumption is too high for operation in a sealed box.
- (2) High levels of r.f.i.
- (3) Failure of a component may have disastrous results.
- (4) Lamp flicker at very low light levels and hence the inability to turn the lamp off without a switch.

The circuit shown consumes a maximum of 0.25W and drives the lamp with a.c. using a thyristor and a bridge rectifier.


The lamp is wired in series with the circuit which enables r.f.i. to be reduced using only one capacitor across the mains input giving an effective RC filter with the lamp. Failure of any one component will at worst only turn the lamp fully on or off.

TR1 and TR2 form a switch which operates when the voltage across C1 exceeds that set by R1 and R2. The energy in C1 fires the thyristor after a delay set by VR1.


The 12V Zener provides a working voltage to the circuit which falls to zero at

the end of each half cycle reducing the base voltage of TR1 towards zero. The timing capacitor is thus discharged each half cycle which avoids lamp flicker due to charge being accumulated on C1 when VR1 is set for a delay longer than a half cycle. Triggering early in the following cycle is thus avoided enabling trouble free control at near zero light levels.

M. A. McCabe,
Bradford,
W. Yorks.

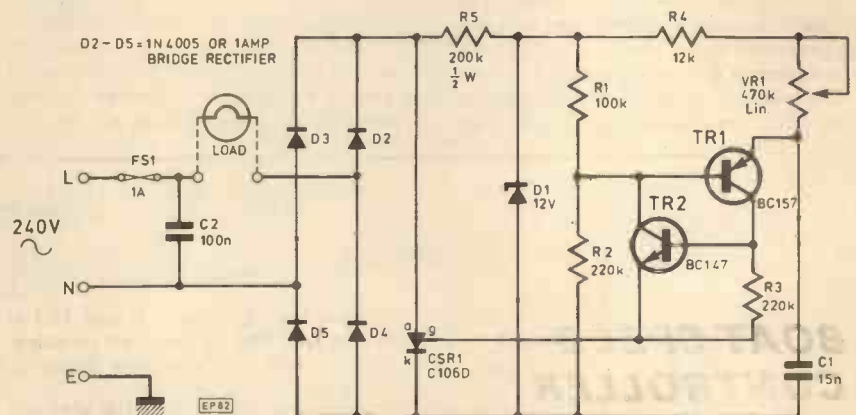

STEREO PEAK DETECTING PPM

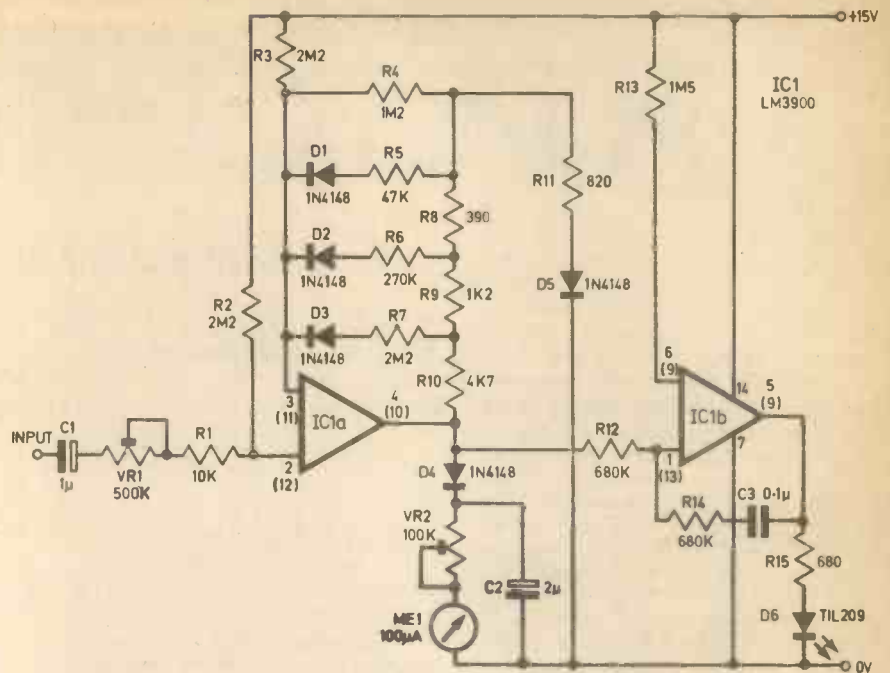

ONE disadvantage of peak program meters (PPMs), apart from their usual cost and complexity, is their ability of hiding serious overloads. This is because the logarithmic response makes a large overload look like an insignificant one. It is for this reason that this simple inexpensive circuit for a PPM was designed to include a peak detection circuit which can detect a +1dB overload.

The circuit shows for one channel. The figures in brackets indicate the IC1 pin connections for the other channel. IC1 is a quad current differencing amplifier (CDA). The incoming signal is half wave rectified by IC1a, the gain of which is controlled

as a function of the output voltage to give a logarithmic response. This response is tailored by switching in negative feedback as the output voltage increases. Four discrete linear slopes are combined to approximate the logarithmic response. Diodes D1, D2 and D3 are used as the switches. Diode D5 provides some temperature compensation. The output peaks charge C2 to give an attack time of about 1ms. The decay time is about 160ms. IC1b forms a comparator/monostable which will drive the i.e.d. overload indicator for 40ms periods if a +1dB signal persists for 1ms. A continuous overload will cause the i.e.d. to flash on and off.

The meter scale is linear and calibrated -35dB to +5dB. The meter zero is calibrated -35dB, although it is, of course, infinity, but this makes little difference.

Setting up is very simple, since the overload indicator provides a means of calibration. First, a signal is applied to the input which is just sufficient in amplitude to light the overload i.e.d. VR2 is then adjusted so that the meter reads +1dB. VR1 can then be adjusted so that a 0dB input deflects the meter to 0dB. This can be anywhere between 60mV and 2.8V r.m.s.

P. R. Williams,
Stevenage,
Herts.

BOAT SPEED CONTROLLER

A FRIEND wanted to control the speed of a model boat without wasting valuable power across a power rheostat. This design evolved.

The on time (o/p high) is when C1 is being charged via R1 and D1.

The off time (o/p low) is when C1 is being discharged through VR1 and R2 to pin 7. This off time can be varied by ranging VR1 but the on time is not altered due to D1 bypassing R2 and VR1 on charge.

When the o/p at pin 3 is high TR1 is switched on. The o/p pulses are smoothed by C2 which also eliminates damaging back e.m.f.



As the o/p transistor is a TIP 3055 and is saturated, no heatsink should be required.

C3 is to remove spikes from the supply line.

A 100 kilohm potentiometer was used as the servo which moves this had only limited movement. The variation of the resistance required to be about 10 kilohms. A resistor can obviously be put in parallel with VR1 if the movement is too great.

The speed can be varied from full to very slow, smoothly.

S. H. Allsop,
South Anston,
Sheffield.

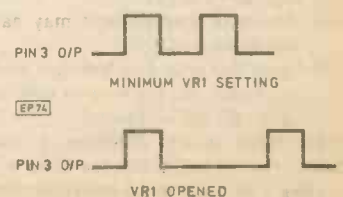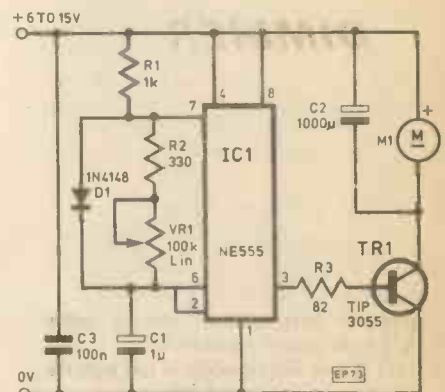

MICRO-BUS

Compiled by DJD.

Appearing every two months, Micro-Bus presents ideas, applications, and programs for the most popular microprocessors; ones that you are unlikely to find in the manufacturers' data books. The most original ideas often come from readers working on their own systems, and payment will be made for any contribution featured.

THIS month's Micro-Bus looks at two activities that are normally considered extremely difficult for computers. The first is speaking, and a board which will provide speech output for a microcomputer is reviewed here; a program for generating random limericks used to evaluate the system is given in full, together with details for using it without a speech system to print limericks. The second activity, on a less serious note, is self-replication, and self-replicating programs in BASIC and M6800 assembler are given here.

MICRO TALKS

The speech channel is, for humans, the most fundamental means of communication, but it is still largely neglected as a means of communicating with computers, and HAL in "2001 A Space Odyssey" remains a creation of science fiction. However electronically synthesised speech was generated as long ago as 1951 by Walter Lawrence's PAT, or Parametric Artificial Talker, and although it is still difficult to produce very high-quality speech there are now simplified systems available for use with microcomputers.

One such system is the USA-produced Computalker board, designed for the S-100 bus and sold here for around £310 with software. Another product, the British-designed Microspeech board, has recently become available and Micro-Bus obtained one to review.

MICROSPEECH REVIEWED

The Microspeech board, shown opposite, is designed for use with the SS-50 bus as used in the South-West Technical Products MP-68 microcomputer which is based on an M6800 micro. At £295 including software it may seem rather expensive, but the circuitry is fairly complex containing some 38 i.c.s. The hardware and software were designed by Tim Orr and Richard Monkhouse respectively, both of whom formerly worked at Electronic Music Studios.

SYNTHESIS BY RULE

The Microspeech system uses a method of generating speech known as "synthesis by rule". The speech is stored in the most economical form of phonetic text, in which

unique symbols are used to represent the different sounds from which the words are composed. Typically a minute of speech coded in this way can be stored in each 1K of memory.

Each speech sound is represented by an unambiguous one- or two-letter code; for example, "O" is the vowel sound in "hot" and "got", and "OO" is the vowel sound in "boot" or "true". The phrase "stupid computers" is rendered as "STYOOPIXD/KOMPYOOTETS". The "/" is used to separate words; a space gives a pause in the flow of speech. It is also possible to exert some control over the pitch of the voice, and this may be used to add intonation to make the speech sound more natural; for example "+" and "-" increase and decrease respectively the pitch of the voice by one unit, and these may be inserted between the phonetic codes at any point.

Two pieces of software provided with the system both convert the phonetic text into a series of parameter values which control the electronics of the synthesiser board. One, a stand-alone program, enables one to enter a piece of phonetic text and play it. The other

program is a patch to SWTP 8K BASIC which makes it possible for a BASIC program to produce speech output. The phonetic text is printed to port 3; the speech software buffers it until an up-arrow is received, whereupon the text is spoken.


BLOCK DIAGRAM

Microspeech's electronic vocal tract is shown in block form in Fig. 1. The nine parameters on the diagram which control the different sections of the model are:

Frequencies:	Amplitudes:
F1—formant 1	AH—aspired sounds
F2—formant 2	AV—vowel sounds
F3—formant 3	AF—fricative sounds
FF—fricative formant	AN—nasal sounds
FV—voice oscillator	

To specify these parameters, nine 8-bit numbers are output to the Microspeech board by the controlling software. Each number is converted to an analogue voltage by a D/A converter and then steered to one of nine

The Microspeech board which will provide speech output from a microprocessor system.

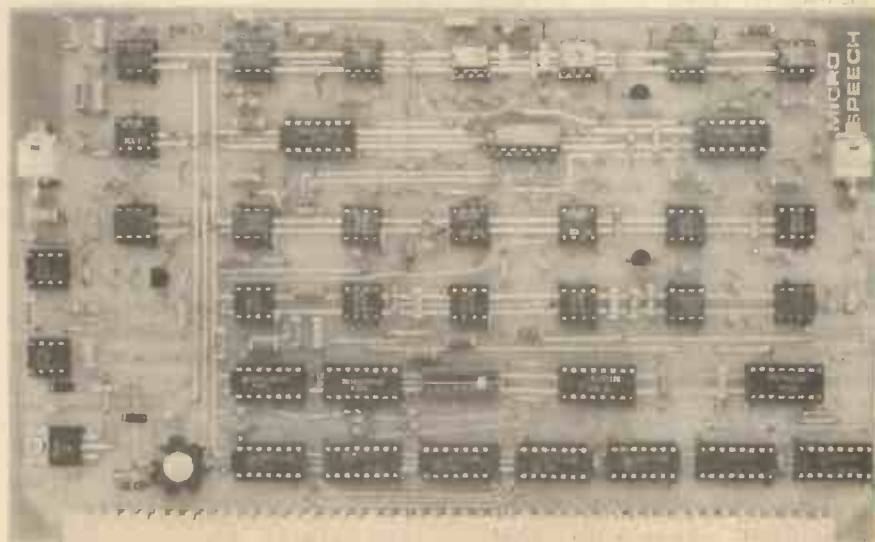

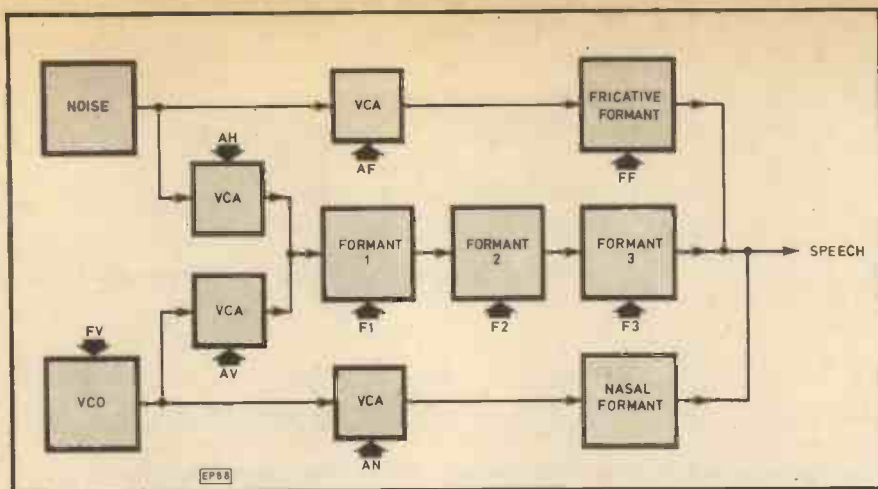


Fig. 1. Block diagram of the speech synthesiser electronics; the nine control voltages determine the speech sound produced.

sample-and-hold units by a multiplexer. The nine parameters are updated by the software at a rate of 50 times a second. The manipulation of these parameters enables the human speech sounds to be simulated as follows:

Vowels are generated by producing waveforms with maximum energies at certain specific frequencies known as the formants. The first three formant frequencies turn out to be the most important in determining the perceived vowel; for example, the "O" in "hot" has formants at 730Hz, 1kHz, and 2.4kHz, whereas the "OO" in "boot" has formants at 300Hz, 370Hz, and 2.2kHz.

Diphthongs, such as "AY" in "pay" and "OY" in "boy", are produced by gliding from one vowel sound to another. The vowel sounds are created electronically by passing the sawtooth waveform output from the VCO (Voltage Controlled Oscillator) through a line of three voltage-controlled bandpass filters, one for each formant (see Fig. 1).

A separate formant filter is used for nasals such as "M" in "man" and "NG" in "sing". Nasals, diphthongs, and vowels are all voiced sounds so that there is a pitch associated with them, and this pitch varies with the intonation of the voice. The unvoiced sounds, such as the fricatives "F" in "fat" and "SH" in "ship", are generated instead by passing the output of a noise generator through a bandpass filter.

The centre-frequency of the filter characteristic determines the speech sound heard; a frequency of about 4kHz will give an "F" sound whereas one of 2.5kHz will give an "SH" sound. If the sound includes some voicing these become the "V" in "vow" and the "ZH" in "azure" respectively.

Finally, stop consonants such as "D" in "dog" and "T" in "top" are generated by a period of silence followed by a gliding of the formants to the values determined by the vowel following the consonant. The difference between "D" and "T" is produced by the addition of a short burst of noise at the start of the latter sound.

RANDOM LIMERICKS

In order to try out the Microspeech system with the BASIC software a short BASIC

program was written to make the micro compose its own random limericks, and read them out! The program is given in Fig. 2. A typical limerick produced by the program might be:

A vicious bland grocer from Spain
Once demolished some cakes on a train
He demolished so slow
That he demolished some dough
This vicious bland grocer from Spain.

Fig. 2. BASIC program which composes random limericks and speaks them or, with modification, prints them.

```

0001 REM SPEAKING LIMERICKS
0010 GOTO 1000
0020 DATA SAURDIHD,GRATSFUHL
0025 DATA WIYLIH ,VIXSHETS
0030 DATA SPAHKLIHNG
0035 DATA GREEN,YUNG
0040 DATA VIYL ,BLAAND
0045 DATA IJWLD
0050 DATA DUCHEHS,GROWSER
0055 DATA GLUTEN,FLAOTIHST
0060 DATA LAONDREHS
0070 DATA WEHMBLIH,SPAYN
0075 DATA CHAAD,SPEEK
0080 DATA KIXNGS
0085 DATA KAWNTEHD,FJLLDWD
0090 DATA NQWTIXSD,DEHMILIXSHD
0095 DATA KILLEHKTED
0100 DATA SUM STAAMPS
0105 DATA ET/STQWT,ET/NYQJD
0110 DATA SUM KAYKS,ET/FRJG
0115 DATA AAND/FEHLT/TREHMBLIH
0120 DATA JN/ET TRAYN
0125 DATA AAND/WEHNT/MAAD
0130 DATA TWIYS ET WEEK
0135 DATA AAND/GRQD/WIXNGZ
0140 DATA SHEE,HEE,SHEE
0145 DATA HEE,SHEE
0150 DATA KWIXK,SLJW,FYUII
0155 DATA HAHRD,LAIT
0160 DATA ET BRIXX,SUM DQW
0165 DATA ET SKRUJ
0170 DATA SUM/LAHRD
0175 DATA ET PLAYT

```

Not up to Edward Lear perhaps, but with a cunning choice of words some of the limericks can turn out to be quite amusing.

The program of Fig. 2 works by choosing from among five alternatives at a particular point in the limerick; for example, the first adjective is chosen from : sordid, graceful, wily, vicious, and sparkling. These alternatives are specified, in phonetic form, in the DATA statements in lines 20 to 175 in the program. The subroutine at 7005 reads five strings from the DATA statements, chooses the one specified by the value of C (1 to 5), and prints it to the speech buffer.

If the subroutine is entered at 7000 the value of C is chosen at random, giving a random choice of one of the five strings. The subroutine at 6000 prints an up-arrow to the speech buffer, causing the strings to be vocalized. Rhyming is ensured by making the choice of the phrase at the end of the second line depend on the choice of word at the end of the first line; the same method ensures a rhyme between lines 3 and 4. The program would eventually be expanded with a greater number of alternative words at each point, but even with just five alternatives the results can be unexpected.

The program of Fig. 2 can just as well be made to produce printed limericks; the strings in the DATA statements should be changed to the written equivalents of the phonetic forms shown, and the PRINT statements should be altered to give printing at the terminal.

```

1000 DEF FNA(X)=INT(RND(0)*X)+1
1010 RESTORE
1020 PRINT #3,"A1 ";
1030 GOSUB 7000:X=C
1040 GOSUB 7000:Y=C
1050 GOSUB 7000:Z=C
1060 GOSUB 8000
1100 GOSUB 7000:Q=C
1110 GOSUB 6000
1120 PRINT #3,"WUNS ";
1130 GOSUB 7000
1131 G$=C$
1140 GOSUB 7000
1150 C=Q:GOSUB 7005
1160 GOSUB 6000
1180 C=Z:GOSUB 7005
1190 PRINT #3,G$;"S1W";
1191 G$=C$+G$
1200 GOSUB 7000:A=C
1210 PRINT #3,"DHAAT";G$;
1230 C=A:GOSUB 7005
1240 GOSUB 6000
1250 RESTORE
1270 PRINT #3,"DHIXS";
1280 C=X:GOSUB 7005
1290 C=Y:GOSUB 7005
1300 C=Z:GOSUB 7005
1310 GOSUB 8000
1320 C=Q:GOSUB 7005
1330 GOSUB 6000
1340 GOTO 1000
6000 PRINT #3,"  ";RETURN
7000 C=FNA(5)
7005 FOR M=1 TO 5:READ A$
7020 IF M=C THEN C$=A$
7030 NEXT M:PRINT#3,C$;
7050 RETURN
8000 PRINT #3,"FROM";RETURN

```

```

          *
          NAM COPY
0000 8D 00  HERE  BSR  *+2  PC ON STACK
0002 30          TSX
0003 31          INS
0004 31          INS
0005 EE 00          LDX  O,X  X=HERE+2
0007 09          DEX
0008 09          DEX
0009 C6 14          LDA  B  ELAST-HERE+1
000B A6 00  MOVE  LDA  A  O,X
000D BD EOCA        JSR  OUT2HS
0010 5A          DEC  B
0011 26 F8          BNE  MOVE
0013 39          LAST  RTS
          *
EOCA  OUT2HS EQU  $EOCA  IN MIKBUG
          END

```

```

1000 FOR N=1000 TO 1040 STEP 10
1005 DATA FOR N=1000 TO 1040 STEP 10
1010 READ A$
1015 DATA READ A$
1020 PRINT N;A$
1025 DATA PRINT N;A$
1030 PRINT N+5;"DATA ";A$
1035 DATA PRINT N+5;"DATA ";A$
1040 NEXT N

```

Fig. 4. Self-replicating BASIC program which lists itself.

INTELLIGIBILITY

Just how good is the speech produced by the Microspeech board? To evaluate the system a piece of phonetic text was typed in, and on replaying it we were pleasantly surprised at the result. However we were in for a shock; we played the same speech to an unsuspecting volunteer, and they did not even identify it as speech, let alone understand it.

It seems fair to say that the speech produced is perfectly intelligible provided that you know what it is saying! Perhaps the best way of describing it is to say that it is like listening to someone with a very unfamiliar accent; after about half-an-hour's practice the speech is almost perfectly understood, especially if the sense is fairly predictable. It seems that human speech is a very difficult thing to simulate electronically; using the most sophisticated synthesis-by-rule systems people typically identify only 50 per cent of the words correctly unless very careful attention is paid to producing perfect timing and intonation.

In conclusion, the Microspeech board is great fun for use in non-serious applications where perfect intelligibility is not important; for example, for producing spoken output

from games programs. It also has serious applications where experience with the speech it produces would overcome the problem of intelligibility; for example, dictation of the output from programs over the telephone, production of auditory alarms and warnings, and as a computer interface for the handicapped.

SELF-REPLICATING PROGRAMS

It is a fascinating, and by no means trivial, problem to write programs which will create an identical copy of themselves. Two examples are given here, but readers who find better solutions are urged to communicate these to Micro-Bus immediately. In assembler language for a particular micro the problem is fairly simple, even with the restriction that the program must work wherever it is placed in memory.

An example for the M6800 micro is shown in Fig. 3; when executed it prints a copy of itself to the terminal in hex. It assumes the existence of a subroutine, OUT2HS, which will print the byte pointed to by the X register as two hex characters, and then increment the X register. Alternatively the program can be

made to put a copy of itself into memory by changing the instruction at \$000D to A7, 14, 0B.

A feature of this program deserving mention is the dummy subroutine call at \$0000 which puts the program counter onto the stack so that it can be loaded into the X register. It is probably possible to write similar self-replicating programs for other micros; one for SC/MP appears in the Mk 14 programming manual.

Writing self-replicating programs in a high-level language such as BASIC poses a far trickier problem. One stumbling-block with BASIC is the difficulty of printing a quote character. Fortunately in SWTP BASIC, in which this problem was attempted, character strings in DATA statements may contain quotes provided that they do not contain commas or colons. The program in Fig. 4 when run, prints a copy of itself to the terminal. To put it more graphically, the effect of typing RUN is the same as the effect of typing LIST! It is probably not possible to write self-replicating programs in all dialects of BASIC, and successful attempts or impossibility proofs are welcomed.

News Briefs

MORE FOR YOUR PET

TO QUOTE Commodore: "The PET family is here!" The 8K PET (2001-8) computer is now cheaper, at £594 inclusive. An up-gradable 4K version (2001-4) is also available at £497.

Two new bigger memory PETs are scheduled for release in May, the 2001-6N and 2001-32N, each with beefier typewriter style keyboards as opposed to PETs earlier calculator type. For 16K of RAM you pay £729, and for 32K RAM you will pay £858, but remember, in these versions there is no cassette deck! This is to make room for the larger keyboard.

Two printers expected to be available from April, one of which is the 2023 which supercedes the previously announced 2020 printer. Capable of producing all PET graphics including reverse field and lower case, this 80 columns, 7 x 6 needle matrix impact printer can hammer along at an average of 93 chars/sec. It will also print double width capitals for document headings etc. For £594 you will be purchasing a software formattable microprocessor controlled hard-copy peripheral suitable for small business and engineering applications.




The 2022 is a higher quality tractor feed printer which can do everything the cheaper one can do, and naturally, more. How about up to four copies on 8½ inch plain paper? Mailing labels, customised forms and even cheques for salaries! £696.60 inclusive.

May 1979 will also see the release of Commodore's 2040 Dual Drive Floppy giving a total of 360K bytes on two standard 5¼ inch disks. This peripheral uses two microprocessors of its own, plus fifteen memory i.c.s. Commodore claim to have eliminated all problems of double-tracking or double-density. The floppy disk operating system uses none of PETs user memory. Suitable for all models of PET and priced at £799.20 inclusive. Commodore Systems Division, 360 Euston Road, London NW1.

From Science of Cambridge: the new MK 14. Simplest, most advanced, most flexible microcomputer – in kit form.

**only
£39.95
(+ 8% VAT)**

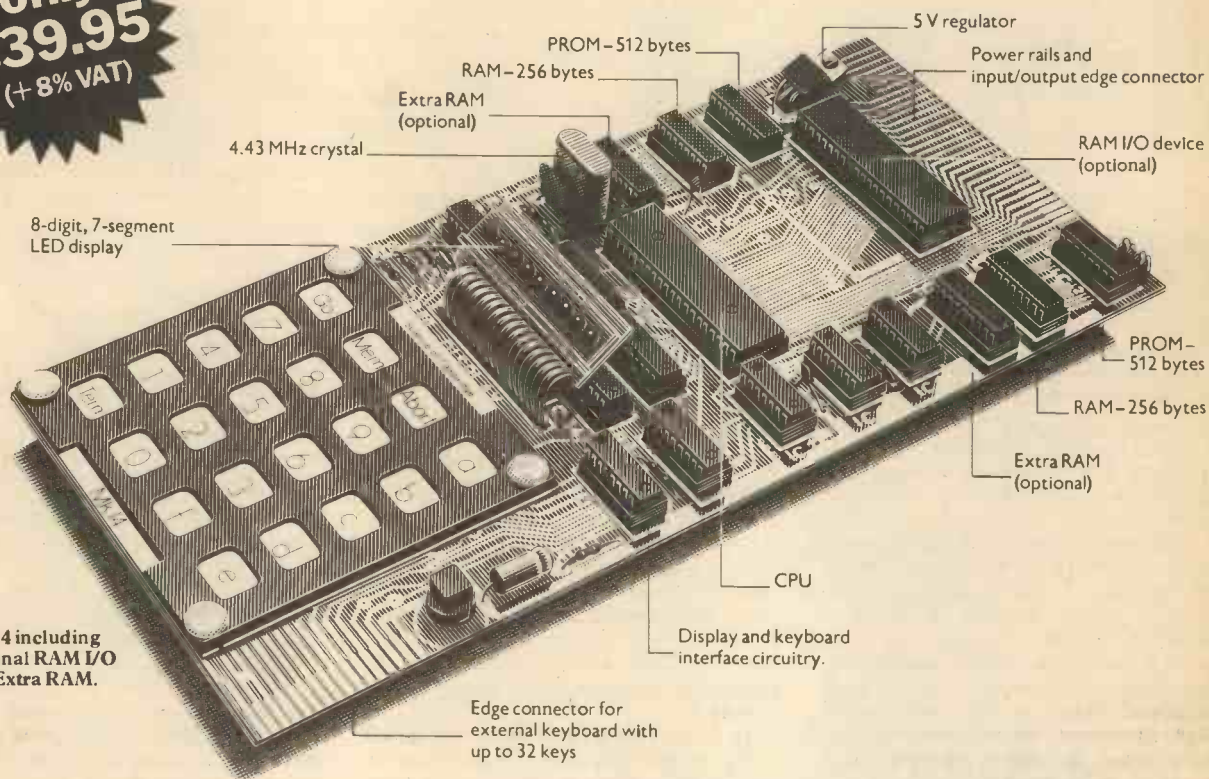

MK 14 including optional RAM I/O and Extra RAM.

The MK 14 is a complete microcomputer with a keyboard, a display, 8 x 512-byte pre-programmed PROMs, and a 256-byte RAM programmable through the keyboard.

As such the MK 14 can handle dozens of user-written programs through the hexadecimal keyboard.

Yet in kit form, the MK 14 costs only £39.95 (+ £3.20 VAT, and p&p).

More memory – and peripherals!

Optional extras include:

1. Extra RAM – 256 bytes.
 2. 16-line RAM I/O device (allowed for on the PCB) giving further 128 bytes of RAM.
 3. Low-cost cassette interface module – which means you can use ordinary tape cassettes/recorder for storage of data and programs.
 4. Revised monitor, to get the most from the cassette interface module. It consists of 2 replacement PROMs, pre-programmed with sub-routines for the interface, offset calculations and single step, and single-operation data entry.
 5. PROM programmer and blank PROMs to set up your own pre-programmed dedicated applications.
- All are available now to owners of MK 14.

A valuable tool – and a training aid

As a computer, it handles operations of all types – from complex games to digital alarm clock functioning, from basic maths to a pulse delay chain. Programs are in the Manual, together with instructions for creating your own genuinely valuable programs. And, of course, it's a superb education and training aid – providing an ideal introduction to computer technology.

SPECIFICATIONS

● Hexadecimal keyboard ● 8-digit, 7-segment LED display ● 8 x 512 PROM, containing monitor program and interface instructions ● 256 bytes of RAM ● 4 MHz crystal ● 5 V regulator ● Single 8 V power supply ● Space available for extra 256-byte RAM and 16 port I/O ● Edge connector access to all data lines and I/O ports

Free Manual

Every MK 14 kit includes a Manual which deals with procedures from soldering techniques to interfacing with complex external equipment. It includes 20 sample programs including math routines (square root, etc), digital alarm clock, single-step, music box, mastermind and moon landing games, self-replication, general purpose sequencing, etc.

Designed for fast, easy assembly

The MK 14 can be assembled by anyone with a fine-tip soldering iron and a few hours' spare time, using the illustrated step-by-step instructions provided.

How to get your MK 14

Getting your MK 14 kit is easy. Just fill in the coupon below, and post it to us today, with a cheque or PO made payable to Science of Cambridge. And, of course, it comes to you with a comprehensive guarantee. If for any reason, you're not completely satisfied with your MK 14, return it to us within 14 days for a full cash refund.

Science of Cambridge Ltd,
6 Kings Parade, Cambridge, Cambs., CB2 1SN.
Telephone: Cambridge (0223) 311488

To: Science of Cambridge Ltd, 6 Kings Parade, Cambridge, Cambs., CB2 1SN.

Please send me the following, plus details of other peripherals:

- MK 14 Standard Microcomputer Kit " £43.55 (inc 40p p&p.)
 Extra RAM " £3.88 (inc p&p.)
 RAM I/O device " £8.42 (inc p&p.)

I enclose cheque/money order/PO for £_____ (indicate total amount.)

Name _____

Address (please print) _____

Science of Cambridge

PE6


Allow 21 days for delivery.

TOTAL AMPLIFICATION FROM

CRIMSON ELEKTRIK

— WE NOW OFFER THE WIDEST RANGE OF SOUND PRODUCTS —

STEREO PRE-AMPLIFIERS

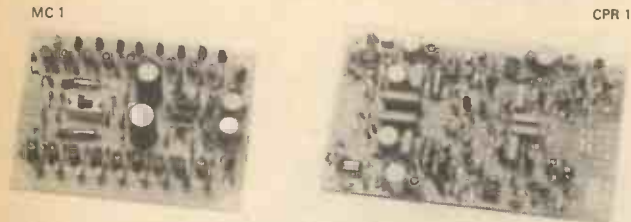

CPR 1 - THE ADVANCED PRE-AMPLIFIER

The best pre-amplifier in the U.K. The superiority of the CPR 1 is probably in the disc stage. The overload margin is a superb 40dB, this together with the high slewing rate ensures clean top, even with high output cartridges tracking heavily modulated records. Common-mode distortion is eliminated by an unusual design. R.I.A.A. is accurate to 1dB; signal to noise ratio is 70dB relative to 3.5mV distortion < .005% at 20kHz. Following this stage is the flat gain/balance stage to bring tape, tuner, etc. up to power amp, signal levels. Signal to noise ratio 86dB; slew-rate 3V/μs; T.H.D. 20Hz - 20kHz < .008% at any level. F.E.T. muting. No controls are fitted. There is no provision for tone controls. CPR 1 size is 130 x 80 x 20mm. Supply to be ± 15 volts.

MC 1 - PRE-AMPLIFIER

Suitable for nearly all moving-coil cartridges. Send for details.

X02: X03 - ACTIVE CROSSOVERS

X02 - two way, X03 - three way. Slope 24dB/Octave. Crossover points set to order within 10%.

REG 1 - POWER SUPPLY

The regulator module, REG 1 provides 15.0-15v to power the CPR 1 and MC 1. It can be used with any of our power amp supplies or our small transformer TR 6. The power amp kit will accommodate it.

POWER AMPLIFIERS


It would be pointless to list in so small a space the number of recording studios, educational and government establishments, etc. who have been using CRIMSON amps satisfactorily for quite some time. We have a reputation for the highest quality at the lowest prices. The power amp is available in five types, they all have the same specification: T.H.D. typically .01% any power 1kHz 8 ohms; T.I.D. insignificant; slew rate limit 25V/μs; signal to noise ratio 110dB; frequency response 10Hz-35kHz, -3dB; stability unconditional; protection drives any load safely; sensitivity 775mV (250mV or 100mV on request); size 120 x 80 x 25mm.

POWER SUPPLIES

We produce suitable power supplies which use our superb TOROIDAL transformers only 50mm high with a 120-240 primary and single bolt fixing (includes capacitors/bridge rectifier).

POWER AMPLIFIER KIT

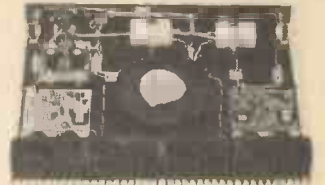The kit includes all metalwork, heatsinks and hardware to house any two of our power amp modules plus a power supply. It is contemporarily styled and its quality is consistent with that of our other products. Comprehensive instructions and full back-up service enables a novice to build it with confidence in a few hours.



ACTIVE CROSSOVERS

X02 £14.83
X03 £23.06

POWER AMPLIFIER MODULES

CE 608 60W/8 ohms 35.035v £16.30
CE 1004 100W/8 ohms 35.0-35v £19.22
CE 1008 100W/8 ohms 45.0-45v £23.22
CE 1704 170W/8 ohms 45.0-45v £29.12
CE 1708 170W/8 ohms 60.0-60v £31.90

TOROIDAL POWER SUPPLIES

CPS1 for 2 x CE 608 or 1 x CE 1004 £14.47
CPS2 for 2 x CE 1004 or 2/4 x CE 608 £16.82
CPS3 for 2 x CE 1008 or 1 x CE 1704 £17.66
CPS4 for 1 x CE 1008 £15.31
CPS5 for 1 x CE 1708 £22.68
CPS6 for 2 x CE 1704 or 2 x CE 1708 £23.98

HEATSINKS

Light duty, 50mm, 2°C/W £1.30
Medium power, 100mm, 1-4°C/W £2.20
Disc/group, 150mm, 1-1°C/W £2.85
Fan, 80mm, state 120 or 240v £18.50
Fan mounted on two drilled 100mm heatsinks, 2 x 4°C/W, 65°C max. with two 170W modules. £29.16

THERMAL CUT-OUT, 70°C

£1.38

POWER AMP KIT £32.40

PRE-AMPS: These are available in two versions - one uses standard components, and the other (the S) uses MO resistors where necessary and tantalum capacitors.

CPR1 £29.49 CPRIS £39.98
MC1 £18.50 MCIS £29.49
POWER SUPPLY:
REG £6.75 TR6 £1.75

BRIDGE DRIVER, 8DI

Obtain up to 340W using 2 x 170W amps and this module. £5.40

CRIMSON ELEKTRIK
1A STAMFORD STREET,
LEICESTER LE1 6NL
Tel. (0533) 537722

All prices shown are UK only and include VAT and post. COD 90p extra. £100 limit. Export is no problem, please write for specific quote. Send large SAE or 3 international Reply Coupons for detailed information. UK - please allow up to 21 days for delivery.

Distributor: Minic Teleprodukt, Box 12035, S-750 12 Uppsala 12, Sweden.

ASTRA-PAK			92 GODSTONE ROAD			WHYTELEAF SURREY CR3 0EB																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
7400	7401	7402	7999	8000

DIGITALLY SYNTHESIZED DOOR CHIME

24 tunes including "Rule Britannia", "Col. Bogie" etc.
Adjustable speed and tone.
In sturdy moulded case, taking internal PP3 batteries.
1 year guarantee. Special reduced price for PE readers only £14.95.

<p>Don't Let Your Environment Dehydrate You! Buy our Honeywell Humidity Controller. Membrane actuated, very sensitive. 1/2" shaft, 250V, 3.75A Contacts ideal for greenhouses, centrally heated homes, offices etc. Build your own humidifiers or alarms. Fraction of original cost 50p ea. 5 for £2.</p> <p>CASSETTE MOTORS Sell Regulating, will operate 8-12V. Ideal for models, mechanical switching etc. 2000 R.P.M. approx. 90p ea.</p> <p>ULTRASONIC TRANSDUCERS Transmitter and receiver. 40 kHz. 14 mm diam. £4.25 pair.</p> <p>6 x 6 POLE REED RELAYS ON BOARD 12V ideal for burglar alarms, model railways etc. £2.45</p> <p>100 MINIATURE REED SWITCHES We are the cheapest! £3.30</p> <p>EARPIECES Magnetic with plug and lead 25p ea. 5 for £1 Crystal with lead 40p ea. 3 for £1</p> <p>MAKE CHEAP BATTERY ELIMINATORS Fully shrouded mini mains transformers. 240V in 6-0-6V at 100 mA out. Complete with mains lead and plug, ex new equip. 90p</p> <p>DE LUXE FIBRE GLASS PRINTED CIRCUIT ETCHING KITS Includes 150 sq. ins. copper clad F/G. board, 1 lb ferric chloride, 1 data etch resist pen. Abrasive cleaner. Etch tray plus instructions. Special Price £4.95 1 lb FE. C1. To mil. spec £1.25 5 lb FE. C1. To mil. spec £5.00 150 sq. in. Single sided board £2.00 150 sq. in. Double sided board £3.00</p>	<p>SMOKE AND GAS DETECTOR Uses TGS 105 plug in sensor, housed in neat 3 1/2" dia cast box. led indicator. 24V, 112V by altering 3 component values). Will operate lamp or relay, with data and circuit. £6.95 Relays for above £1 ea. state voltage</p> <p>TRANSISTOR PACKS 100. Full spec, new and marked. Includes BC148, BC184L, ME0412, BF274, BC154 etc. £4.95 200 as above and includes AC128, 2N3055, BFY50, BD131, BF200 etc. £9.95 Buy bulk and save money, these packs are worth at least double</p> <p>P/B SWITCH BANKS These cost a fortune! Were made for various music centres. Includes independent and interdependent latching types multi pole c/o etc. Can be modified. Can't be repeated. 3 Banks for £1</p> <p>BULK BARGAINS, STOCK UP FOR WINTER 300 mixed 1/2 & 1/4 watt resistors £1.50 150 mixed 1 & 2 watt resistors £1.50 300 mixed capacitors, modern, most types £3.30 100 mixed ceramic and plate caps £1.20 25 pots and presets £1.50 25 presets, skeleton etc. £1.20 20 VDRs and thermistors £1.20 100 Hi-wattage resistors wirewound etc. £2.20 100 electrolytics, nice values £2.20 300 printed circuit resistors £1 300 printed circuit components £1.50</p> <p>100K MINIATURE THUMBWHEEL SLIDER POTS Very neat, can be banded side by side. Ideal for v. cap tuning, graphic equalizers etc. 10 for £1</p> <p>100K STEREO SLIDER POTS Good quality, 25p ea. 5 for £1</p> <p>MINIATURE LEVEL/BATT. METERS 200μA F.S.D. as fitted to many cassette recorders. 90p</p>
---	---

40p P & P on all above items. Cheque or P.D. with order to:

SENTINEL SUPPLY, DEPT. P.E.

149A BROOKMILL RD., DEPTFORD, LONDON, SE8



20 x 20 WATT STEREO AMPLIFIER
 Viscount IV unit in teak simulate cabinet. Silver finish rotary controls and pushbuttons with matching fascia. red mains indicator and stereo jack socket. Functions switch for mic, magnetic and crystal pickups, tape tuner and auxiliary. Rear panel features two mains outlets DIN speaker and input sockets plus fuse 20x20 watts RMS 40x40 watts peak. For use with 8 to 15 ohm speakers.
£29.90
 £2.50 p&p

30x30 WATT AMPLIFIER IN KIT FORM
 For the experienced constructor complete in every detail, same facilities as Viscount IV, but with 30x30 output 60x60 watts peak. For use with 4, 15 ohms speakers.
 + p&p
£29.00 £2.50

SPECIAL OFFER
30 x 30 WATT AMPLIFIER KIT
 with BSR P200 belt drive deck and Shure M75 cartridge.
£55.00
 + p&p £5.00

EMI SPEAKER BARGAIN
 Stereo pair 350 kit. System consists of 13" x 8" approx. woofer with rolled surround, 2 1/2" approx. Audax tweeter, crossover components and circuit diagram. Frequency response 20 Hz to 20 KHz. Power handling 15 watts RMS. 20 watts max. 8 ohm impedance.
£14.95
 Per stereo pair + £3.40 p&p

BSR P200
 Belt drive chassis turntable unit semi automatic, cueing device.
£24.95
 p&p £2.55
 A.D.C. QLM 30 Mk III Magnetic Cartridge to suit.
£7.75

BSR Manual single play record deck with auto return and cueing lever. Fitted with stereo ceramic cartridge 2 speeds with 45 r.p.m. spindle adaptor ideally suited from home or disco use.
 p&p
 OUR PRICE **£10.95** £2.55

GARRARD DECK MODEL CC 10A
 Record changer with cueing device fitted with stereo ceramic cartridge ready to fit into your own plinth.
£7.95 p&p £2.00 Size 12" x 8"

SANYO Nic/cad. battery, with mains charger equivalent in size and replaces 4 SP11 type batts. Size 3 3/4" x 1 1/4" x 2" approx.
£7.50 p&p £1.50p

BARGAIN FOR PERSONAL SHOPPERS ONLY
Altone UA4 Stereo System
 Features 8 watt total output. Full size BSR manual turntable with cueing and auto return. Socket for tape in and out and stereo headphones.
 complete with speakers. **£34.95**

Micro Cassette Recorder
 Pocket size—home or office use or when travelling.
£13.95

Battery operated fluorescent camping lamp.
 Runs off 8 U2 batteries.
£4.50

Mullard

AUDIO MODULES IN BARGAIN PACKS
CURRENT CATALOGUE

PRICE £ AT OVER 25 PER PACK


SEE OUR PRICES

1 PACK 1 2 x LP1173 10w. RMS output power audio amp modules. + 1 LP1182/2 Stereo pre amp for ceramic and auxiliary input.
 OUR PRICE **£4.95**
 p&p £1.00

2 PACK 2 2 x LP1173 10w. RMS output power audio amp modules + 1 LP1182/2 Stereo pre amp for magnetic, ceramic and auxiliary inputs
illus. OUR PRICE **£7.45**
 p&p £1.00

AVAILABLE ALSO TO PURCHASERS OF THE 10 + 10 AMPLIFIER KIT.

10 + 10 AMPLIFIER KIT
 An opportunity to buy a 10 watts per channel stereo amplifier kit which is suitable for use with a ceramic cartridge. The amplifier utilises proven Mullard modules and is available at a very competitive price. The amplifier kit comes complete with instructions and includes: a Mullard LP1183 stereo preamplifier module, two LP1173 power amplifiers with integral heatsinks, a power supply, Zobel networks, front and back mounting panels, a finished fascia panel, all control potentiometers (bass, treble, volume and balance), switches, input, output and headphone sockets, wire, and an easily assembled wrap around cabinet to house the finished unit.
 Size approximately "9 1/2" x 8 1/2" x 4"
 p&p £2.05 **£11.95**

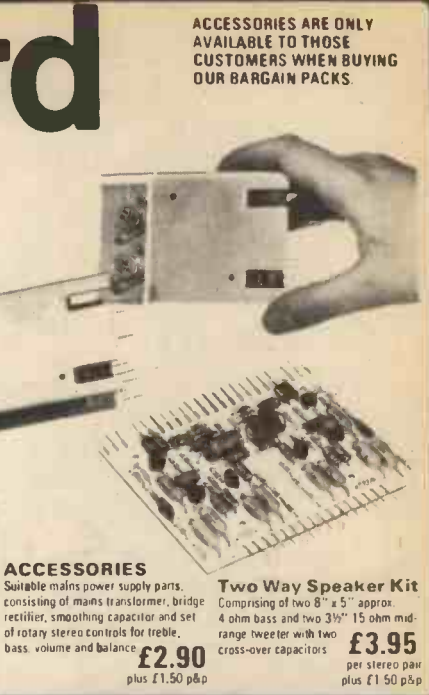

ACCESSORIES ARE ONLY AVAILABLE TO THOSE CUSTOMERS WHEN BUYING OUR BARGAIN PACKS.

ACCESSORIES
 Suitable mains power supply parts, consisting of mains transformer, bridge rectifier, smoothing capacitor and set of rotary stereo controls for treble, bass, volume and balance. **£2.90** plus £1.50 p&p

Two Way Speaker Kit
 Comprising of two 8" x 5" approx. 4 ohm bass and two 3 1/2" 15 ohm mid-range tweeter with two cross-over capacitors. **£3.95** per stereo pair plus £1.50 p&p

BARGAINS FOR PERSONAL SHOPPERS

LED 5 function men's digital watch stainless steel finish **£5.95**
 LCD 5 function men's digital watch stainless steel finish **£6.95**
 LCD 8 Function CHRONOGRAPH men's digital watch, stainless steel finish **£12.95**
POCKET CALCULATOR. With LED display, memory and percentage key **£2.95**
AM/FM DIGITAL CLOCK RADIO. Accurate 4 Digit Electronic Clock with 1/2" LED display. Buzzer and snooze timer **£11.95**

50 WATT MONO DISCO AMP
£29.95
 P&P £2.50
 Size approx. 13 3/4" x 5 1/4" x 6 1/2"

50 watts rms, 100 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and treble controls and master volume.

125 Watt Power Amp Module **£13.95**
 Mains power supply for above unit **£3.50**
MULLARD Built power supply **£1.50**
 DECCA 20w Stereo speaker kit comprising 2 8" approx. bass units + 2 3 1/2" approx. tweeter inc. crossovers **£20.00**
VIDEOMASTER Super Score TV Game with pistol mains operation **£14.95**

70 & 100 WATT MONO DISCO AMP
 Size approx. 14" x 4" x 10 1/4"
 Brushed aluminium fascia and rotary controls.
 Five vertical slide controls, master volume, tape level, mic level, deck level, PLUS INTER DECK FADER for perfect graduated change from record deck No 1 to No 2, or vice versa. Pre fade level control (PFL) lets YOU hear next disc before loading it in. VU meter monitors output level.
 Output 100 watts RMS 200 watts peak.
 70 watt **£57**
 140 watt peak p&p £4.00
 100 watt **£65**

PORTABLE RADIO/CASSETTE RECORDER. AM/FM with clock LW, MW, SW, VHF mains/battery operation **£41.95**
VIDEOMASTER COLOUR SHOT TV GAME
 Choice of three games—Football, Tennis and Squash. Ready to play—one or two players. MAINS OPERATED. OPPORTUNITY AT **£9.95** ONLY

DUO II SPEAKERS
 Attractive teak finish, modern design, incorporating 2 speaker units—8" approx. woofer and 2 1/2" approx. tweeter. 45 to 1800 Hz. Impedance 8 ohms. Power 15 watts RMS. 20 watts max. Per stereo pair
 For personal callers only. **£17.00**



323 EDGWARE ROAD, LONDON W2
 21B HIGH STREET, ACTON W3 6NG
 ACTON: Mail Order only. No callers
 ALL PRICES INCLUDE VAT AT 12 1/2%
 All items subject to availability. Price correct at 14/4/79 and subject to change without notice.

FOR PERSONAL SHOPPERS ONLY
STEREO RADIOGRAM CABINET
 Finished in a natural teak veneer with opening top. Easily modified to accommodate stereo equipment of your choice. Price **£10.95**
 Size approximately 47" x 15 1/2" x 15"

MICRO CHIMES

FROM THE INVENTORS
OF MICROPROCESSOR
MUSICAL CHIMES

New price for the
original

CHROMA- CHIME KIT

24 tune model!

Due to the fantastic
success of this product right
across the World we are able to offer it at

only **£9.95** + 75p p&p

Comes complete with:

- * TMS1000 Micro
- * Superb cabinet
- * All R's & C's
- * Switches & pots
- * Fully prepared PCB
- * All semiconductors
- * Loudspeaker
- * Socket & Hardware
- * Fully detailed kit manual

TMS 1000N - MP0027A Micro-computer chip available separately if required. Full 24 tune spec device supplied with data sheet and fully guaranteed.

New low price only **£4.95** inc. p&p
(Only present 24 tune repertoire currently available.)

A COMPLETE KIT FOR THE NEW MICRO CHIME

This easy to
build kit includes:

- * TMS1000 Custom MPU Chip
- * Special purpose designed case
- * Fully drilled and legended PCB
- * All transistors, Resistors and Capacitors
- * Full set of mechanical parts
- * Smart fascia labels
- * IC Socket and Loudspeaker
- * Really Low Price!

only **£8.95** + 55p p&p

CHROMATRONICS
RIVER WAY
HARLOW
ESSEX U.K.

ALL CHROMATRONICS PRODUCTS
SUPPLIED WITH MONEY BACK GUARANTEE
PLEASE ALLOW 7-21 DAYS FOR DELIVERY

Please send me: PE1
TO: CHROMATRONICS, RIVER WAY, HARLOW, ESSEX. UK.

NAME _____

ADDRESS _____

I enclose cheque/PO value £ _____
or debit my ACCESS/BARCLAYCARD account no. _____

Signature _____

CHROMATRONICS

BIG BARGAINS - NEW MODELS



VT07 LCD
Chronograph
hours, minutes,
seconds, day date
month, 1/100th sec
timing, lap times,
1st & 2nd place timing.

£12.95



VT04 LCD
Chronograph
as VT07 but with
solar assisted panel
(not rechargeable).

£13.95

VT10 LCD Alarm
2 button, 24 hour
alarm plus usual
time features.

£13.95



VT06 LCD Alarm-
Chronograph with
dual time zone
facility, 24 hour
alarm, 1/10th sec
chrono, lap time
plus usual time
features.

£22.95



VT12 LCD
Solar Alarm
Chronograph
same spec. as VT06.

£29.95

ALL WATCHES
CARRY 12 MONTHS'
GUARANTEE AND
ARE DESPATCHED
SAME DAY AS RECEIPT
OF ORDER (Subject to
availability)

ATARI VIDEO COMPUTER - £149.95

+ NEW CARTRIDGES COMING SOON
SKYDIVER BOWLING
MINI GOLF STREET RACER

CODE BREAKER
BRAIN GAMES
HUNT & SCORE

VAT, P & P inc. Send Cheque or PO or telephone card



VIDEOTIME PRODUCTS
56 Queens Rd., Basingstoke, Hants.,
RG21 1REC Tel: (0256) 56417.



PROGRESSIVE RADIO

31 CHEAPSIDE,
LIVERPOOL L2 2JO

SPECIAL OFFER SEMICONDUCTORS:-
TBA800 50p. LM3400 40p. 741 8 Pin 6 for £1. NE555 22p. ZN414 75p. LM380 80p. 741S 35p. IN4005 recs. 10 for 35p. 723 Regs 35p. LM340T (6v 1amp) 40p. AD161/2 matched pair 70p.

L.E.D.S. 0.2" Red 10p. 0.2" Green 12p. 0.2" Clear 15p.

MINIATURE MAINS TRANSFORMERS. 240v AC Primary. 6-0-6v 100ma, 9-0-9v 75ma, 12-0-12v 50ma all 73p each. 12-0-12v 100ma 92p. 0-6, 0-6v 280ma, £1.20. 12v 500ma 95p. **PULSE TRANSFORMERS.** Miniature P.C. board mounting 1:1 Plus 1 55p. Larger type 1:1 30p.

NEW LOW PRICED POCKET MULTIMETERS. KRT100 1,000 ohms per volt, 1,000 volts AC/DC, 100K resistance, 150ma DC current, mirror scale range selector switch £4.65. KRT101 As above but range selection via Prod Tip Insertion £3.75.

MINIATURE TOGGLE SWITCHES. SPST 8 x 5 x 7mm 49p. DPDT 8 x 7 x 7mm 53p. DPDT centre off 12 x 11 x 9mm 78p. **PUSH SWITCHES.** Push to make 16 x 6mm 14p, push to break version 15p.

TOOLS. Good quality side cutters 5" insulated handles £1.35. Matching snub nosed pliers also £1.35. Neon mains tester screwdriver 8" long 44p. **PRECISION TOOL KIT.** Supplied in plastic hinged case consists of 5 spanners 4 to 6mm, 5 Hex. nut drivers 3 to 5mm, 3 small screwdrivers, 2 Philips screwdrivers, 1 awl, 3 Alan Keys £3.35. **TEST LEAD JUMPER SET.** 10 leads with various coloured croc clips each end 80p.

CASSETTE HEAD REPLACEMENTS. Mono cassette £1.30. Stereo cassette £3.00. **TAPE HEAD DEMAGNETISERS.** 240v AC £2.00.

TERMS CASH WITH ORDER (OR OFFICIAL ORDERS FROM SCHOOLS ETC) POSTAGE 30p. (OVERSEAS POST AT COST) VAT INCLUSIVE, SAE FOR ILLUSTRATED LISTS.
PROGRESSIVE RADIO, 31 CHEAPSIDE, LIVERPOOL L2 2DY.



TOPS THE PACK!

- COMPONENTS** - Now over 1,000 types in stock!
- KITS** - See the new range of low-cost 'ELEKITS'.
- SERVICE QUALITY** - 1st Class same day despatch.
- PRICES** - All guaranteed products.
- MAGAZINE PROJECTS** - Many reductions!
- PROJECTS** - Trouble-free!

S.A.E. for list of PE projects

I enclose 30p*, please send catalogue.

Name _____

Address _____

*Refundable with future orders over £5.00.

STEVENSON

Electronic Components

REGULATORS

78L05 30p	7805 60p	79L05 70p	7912 80p
78L12 30p	7812 60p	79L12 70p	7915 80p
78L15 30p	7815 60p	7905 80p	LM723 35p

HARDWARE


MINIATURE TRANSFORMERS

240 Volt Primary

Secondary rated at 100mA.

Available with secondaries of:

6 - 0 - 6, 9 - 0 - 9 and	
12 - 0 - 12.	92p. each.

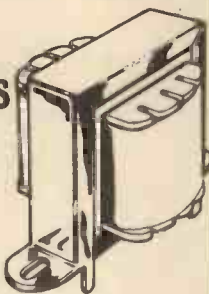

LOUDSPEAKERS

56mm dia. 8 ohms	70p
64mm dia. 8 ohms	75p
64mm dia. 64 ohms	75p
70mm dia. 8 ohms	100p
70mm dia. 80 ohms	110p



TERMINALS

Rated at 10A. Accepts 4mm plug, black, blue, green, brown and red 22p

SWITCHES

Subminiature toggle. Rated at 3A 250V.

SPDT 70p	SPDT centre off 75p
DPDT 80p	DPDT centre off 95p



Standard toggle

SPST 34p	DPDT 48p
----------	----------

Wavechange switches.

1P12W, 2P6W, 3P4W or 4P3W all 43p ea.

Miniature switches (non-locking)

Push to make 15p Push to break 20p

Slide switches (DPDT)

Miniature 14p	Standard 15p
---------------	--------------



CONTROL KNOBS

Ideal for use on mixers etc. Push on type with black base and marked position line. Cap available in red, blue, green, grey, yellow and black. 14p



TRANSISTORS

AC127 17p	8CY71 14p	ZTX109 14p
AC128 16p	8CY72 14p	ZTX300 16p
AC176 18p	8D131 35p	2N697 12p
AD161 38p	8D132 35p	3N1302 38p
AD162 38p	8D135 38p	2N2905 22p
BC107 8p	8D139 35p	2N2907 22p
BC108 8p	8D140 35p	2N3053 18p
BC109 8p	8F244B 36p	2N3055 50p
BC147 7p	8FY50 15p	2N3442 135p
BC148 7p	8FY51 15p	2N3702 8p
BC149 8p	8FY52 15p	2N3704 8p
BC148 9p	MJ2955 98p	2N3705 9p
BC177 14p	MPSA60 20p	2N3706 9p
BC178 14p	MPSA56 20p	2N3707 9p
BC179 14p	TIP29C 60p	2N3708 8p
BC182 10p	TIP30C 70p	2N3819 22p
BC182L 10p	TIP31C 65p	2N3904 8p
BC184 10p	TIP32C 80p	2N3905 8p
BC184L 10p	ZTX107 14p	2N3906 8p
BC212 10p	ZTX108 14p	2N3905 8p
BC212L 10p		2N3906 8p
BC214 10p		2N4058 12p
BC214L 10p		2N4547 32p
BC477 19p		2N4548 30p
BC478 19p		2N5459 32p
BC479 19p		2N5777 50p
BC548 10p		
BCY70 14p		

DIODES

1N914 3p	1N5401 13p
1N4001 4p	8ZY88ser. 8p
Full spec. product.	
1N4148. £1.40/100. £11/1000	

LINEAR

THIS IS ONLY A SELECTION!	CA3140 38p	NE555 21p
709 28p	LM301AN 26p	NE556 50p
741 16p	LM318N 85p	NE555 85p
747 40p	LM324 45p	NE567 170p
748 30p	LM380 75p	SN76003 200p
CA3046 55p	LM382 120p	SN76013 140p
CA3080 70p	LM1830 150p	SN76023 140p
CA3130 90p	LM3900 50p	SN76033 200p
	LM3909 65p	TBA800 70p
	MC1496 60p	TD1022 650p
	MC1458 32p	ZN414 75p

CAPACITORS

TANTALUM BEAD	each
0.1, 0.15, 0.22, 0.33, 0.47, 0.68, 1 & 2.2uF @ 35V	8p
4.7, 6.8, 10uF @ 25V	13p
22 @ 16V, 47 @ 6V, 100 @ 3V	16p

MYLAR FILM

0.001, 0.01, 0.022, 0.033, 0.047	3p
0.068, 0.1	4p

POLYESTER

Mullard C280 series	
0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1	5p
0.15, 0.22	7p
0.33, 0.47	10p
0.68	14p
1.0uF	17p

CERAMIC

Plate type 50V. Available in E12 series from 22pF to 1000pF and E6 series from 1500pF to 0.047uF 2p

RADIAL LEAD ELECTROLYTIC

63V	0.47	1.0	2.2	4.7	10	5p
						7p
						13p
						20p
25V	10	22	33	47		5p
						8p
						10p
						15p
						23p

CONNECTORS

JACK PLUGS AND SOCKETS

	screened	unscreened	socket
2.5mm	9p	13p	7p
3.5mm	9p	14p	8p
Standard	16p	30p	15p
Stereo	23p	36p	18p

DIN PLUGS AND SOCKETS

	plug	chassis socket	line socket
2pin	7p	7p	7p
3pin	11p	9p	14p
5pin 180°	11p	10p	14p
5pin 240°	11p	10p	16p

1mm PLUGS AND SOCKETS

Suitable for low voltage circuits, Red & black. Plugs: 6p each Sockets: 7p each.

4mm PLUGS AND SOCKETS

Available in blue, black, green, brown, red, white and yellow. Plugs: 11p each Sockets: 12p each

PHONO PLUGS AND SOCKETS

Insulated plug in red or black	9p
Screened plug	13p
Single socket	7p Double socket 10p

74LS

LS00 13p	LS73 25p	LS156 60p
LS01 13p	LS74 25p	LS157 48p
LS02 13p	LS75 30p	LS164 65p
LS03 13p	LS76 25p	LS174 48p
LS04 13p	LS78 35p	LS175 48p
LS08 15p	LS83 35p	LS190 62p
LS10 13p	LS85 70p	LS192 60p
LS13 28p	LS86 30p	LS193 60p
LS14 45p	LS90 36p	LS196 60p
LS20 13p	LS93 38p	LS251 50p
LS30 13p	LS95 45p	LS257 50p
LS32 16p	LS123 70p	LS258 50p
LS37 24p	LS125 38p	LS266 30p
LS40 17p	LS126 38p	LS283 60p
LS42 40p	LS132 60p	LS290 60p
LS47 90p	LS136 28p	LS365 40p
LS48 70p	LS138 50p	LS366 40p
LS54 15p	LS139 50p	LS367 40p
	LS151 50p	LS368 40p
	LS153 50p	LS386 35p
	LS155 55p	LS670 140p

TTL

7400 10p	7454 12p	74132 45p
7401 10p	7473 20p	74141 55p
7402 10p	7474 22p	74148 90p
7404 12p	7475 25p	74150 55p
7408 12p	7476 20p	74151 40p
7410 10p	7489 25p	74156 55p
7413 22p	7490 25p	74164 65p
7414 39p	7492 30p	74165 55p
7420 10p	7493 25p	74170 100p
7427 20p	7494 22p	74174 50p
7430 10p	7495 35p	74177 50p
7442 38p	7496 45p	74190 50p
7447 45p	7499 25p	74191 50p
7448 50p	74122 38p	74192 50p
	74123 38p	74193 50p
	74125 35p	74196 50p
	74126 35p	74197 50p


CMOS

4001 12p	4018 55p	4050 25p
4002 12p	4023 12p	4066 35p
4007 12p	4024 40p	4068 18p
4011 12p	4026 90p	4069 12p
4013 28p	4027 30p	4071 12p
4015 50p	4028 48p	4081 13p
4016 30p	4029 50p	4093 45p
4017 48p	4040 60p	4510 65p
	4042 50p	4511 65p
	4046 90p	4518 65p
	4049 25p	4520 60p

FULL DETAILS IN CATALOGUE!

SKTS

Low profile by Texas

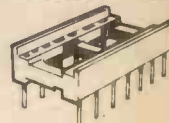

8 pin	8p	16 pin	11p	28 pin	22p
14 pin	10p	24 pin	18p	40 pin	32p

Soldercon pins: 100:50p. 1000:370p

OPTO

LED's	0.125in.	0.2in	each	100+
Red	TIL209	TIL220	9p	8p
Green	TIL211	TIL221	13p	12p
Yellow	TIL213	TIL223	13p	12p
Clips	3p			

DISPLAYS

DL704	0.3 in CC	130p	120p
DL707	0.3 in CA	130p	120p
FND500	0.5 in CC	100p	80p

RESISTORS

Carbon film resistors. High stability, low noise 5%.

E12 series. 4.7 ohms to 10M. Any mix:	
0.25W	each 100+ 1000+
0.5W	1p 0.9p 0.8p
	1.5p 1.2p 1p

Special development packs consisting of 10 of each value from 4.7 ohms to 1 Meg-ohm (650 res) 0.5W £7.50. 0.25W £5.70.

METAL FILM RESISTORS

Very high stability, low noise rated at 1/4W 1%. Available from 51ohms to 330k in E24 series. Any mix:

0.25W	each 100+ 1000+
	4p 3.5p 3.2p

PLEASE WRITE FOR YOUR FREE COPY OF OUR NEW 64 PAGE CATALOGUE OF COMPONENTS.


CONTAINS OVER 2500 STOCK ITEMS.



WHY NOT VISIT OUR NEW SHOP

We welcome callers at our new premises at the address below (5 mins. from High St.) We are open Mon - Sat, 9am - 6pm. Special offers available.

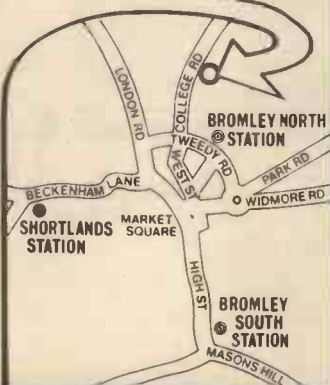Express telephone order service. Orders received before 5pm. are shipped first class on that day. Contact our Sales Office now! Tel: 01-464 2951/5770.



ORDERS DESPATCHED BY RETURN POST

Quantity discounts on any mix TTL, CMOS, 74LS and Linear circuits: 100+ 10%, 1000+ 15%. Prices VAT inclusive. Please add 30p for carriage. All prices valid to April 1980. Official orders welcome.

BARCLAYCARD & ACCESS WELCOME.



Mail orders to: STEVENSON (Dept PE)

76 College Road, Bromley, Kent, England

BAKER LOUDSPEAKER, 12 INCH, 60 WATT.
GROUP 50/12, 4 OR 8 OR 16 OHM HIGH POWER.
FULL RANGE PROFESSIONAL QUALITY.
RESPONSE 30-16,000 CFS
MASSIVE CERAMIC MAGNET
WITH ALUMINIUM PRESENCE CENTRE DOME.
£21
Post £1.60

BAKER "BIG-SOUND" SPEAKERS
Post £1 each

'Group 25'	'Group 35'	'Group 50/15'
12 inch	12 inch	15 inch
30 watt £12	40 watt £14	75 watt £33
4 or 8 or 16 ohm	4 or 8 or 16 ohm	8 or 16 ohm

10 WATT PER CHANNEL STEREO AMPLIFIER
Ready made in chassis form. Mains operated.
Volume balance, treble and bass slider controls.
Pick up and tape inputs. Recording output.
Front panel size: 16 1/2 x 1 1/2 in.
Chassis size: 13 x 15 in. Bargain **£18.50**

HEATING ELEMENTS WAFER THIN
Size 10 1/2 x 8 1/2 x 1/16 in. Operating voltage 200/250V a.c. 250W approx. Suitable for Heating Pads, Food Warmers, Convector Heaters, etc. Must be clamped between two sheets of metal or similar. ALL POST PAID - Discounts for quantity.
ONLY 40p EACH (FOUR FOR £1.50)

MINI MODULE BAFFLE KIT Post 75p
15 x B 1/2 in, 3-way Loudspeaker System EM1 5in, Bass 5in, Middle 3in Tweeter with 3-way Crossover & Ready Cut Baffle. Full assembly instructions supplied. Response=60 to 20 000 C.P.S. 12 watt RMS. 8 ohms. **£10.95** per kit. Two kits **£20.**



SINGLE RECORD PLAYER
Fitted with auto stop, stereo compatible cartridge. Baseplate. Size 11 x 6 1/2 in Turntable Size 7 in diameter a.c. mains 220 250V 3 speeds plays all size records **£7.95**
Post 45p
Two for **£15.** Post 75p.

NEW BSR SINGLE PLAYER £22.50
Model P182 3-speeds flared aluminium turntable. Post £1.
"S" shaped arm, cueing device, stereo ceramic cartridge.
B.S.R. De-Luxe Autchanger with stereo cartridge, plays all size records. **£18.00**

BAKER 150 WATT ALL PURPOSE TRANSISTOR MIXER AMPLIFIER



Ideal for Groups Disco P.A. and Musical Instruments 4 inputs speech and music. 4 way mixing.
Output 4/8/16 ohm. a.c. Mains 240V.
Separate treble and bass controls.
100 volt line model £14 extra. **£79** Carr 11 50

BAKER COMPACT 50 WATT AMPLIFIER



IDEAL FOR DISCOS, GROUPS AND P.A.
Two inputs with volume controls. Master treble bass and volume controls. Suitable for all loudspeakers. **£59** Post £1.

R.C.S. SOUND TO LIGHT DISPLAY MK II
Complete kit of parts with R.C.S. printed circuit. Three 1000W channels. Will operate from 200mV signal source. CABINET extra £4. **KIT = £17.00**

R.C.S. 10 WATT AMPLIFIER KIT

This kit is suitable for record players, tape play back, guitars, electronic instruments or small P.A. systems. Two versions are available. The mono kit uses 13 semiconductors. The stereo kit uses 22 semiconductors. Both kits have printed front panel and volume, bass and treble controls. Spec. 10W output into 8 ohms. 7W into 15 ohms. Response 20c to 30kc.
input 100mV. high imp. Size 9 1/2 x 3 x 2 1/2 in. A/C mains operated
Mono kit **£12.50** Stereo kit **£20** post 45p
Easy to build. Full instructions supplied.

LOW VOLTAGE ELECTROLYTICS
1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p, 500mF 12V 15p; 25V 20p; 50V 30p, 1000mF 12V 17p; 25V 35p; 50V 47p; 100V 70p, 2000mF 6V 25p; 25V 42p, 2500mF 50V 62p, 3000mF 25V 47p; 50V 65p, 3900mF 100V £1.60, 4700mF 63V £1.20, 5000mF 6V 25p; 12V 42p; 25V 75p; 35V 85p, 5600mF 76V £1.60, 1200mF 78V 80p

HIGH VOLTAGE ELECTROLYTICS
8/350V 22p 8+8/450V 50p 50+50/300V 50p
16/350V 30p 8+16/450V 50p 32+32/450V 75p
32/500V 75p 16+16/450V 50p 100+100/275V 85p
50/350V 50p 32+32/350V 50p 150+200/275V 70p

TINTED PLASTIC COVERS ONLY
Sizes: 1 1/2 x 1 1/2 x 4 1/2 in. £3, 16 x 14 x 3 1/2 in. £5, 15 1/2 x 13 x 4 in. £4, 17 1/2 x 9 1/2 x 3 1/2 in. £3, 14 1/2 x 14 1/2 x 2 1/2 in. Rosewood sides £4.
Ideal for record decks, tape decks, etc. Post £1.

R.C.S. LOW VOLTAGE STABILISED POWER PACK KITS

All parts and instructions with Zener diode, printed circuit rectifiers and double wound mains transformer. Input 200 240V a.c. Output voltages available 6 or 7.5 or 9 or 12V d.c. up to 100mA or less. Size 3 x 2 x 1 1/2 in. Please state voltage required. **£2.95** Post 45p

ELECTRO MAGNETIC PENDULUM MECHANISM **95p** Post 30p

1.5V d.c. operation over 300 hours continuous on SP2 battery. Fully adjustable swing and speed. Ideal displays teaching electro magnetism or for metronome strobe etc.

MAINS TRANSFORMERS ALL POST 75p each

250-0-250V 70mA	6 3V 2A	£1.45
250-0-250 80mA	6 3V 3 5A 6 3V 1A or 5V 2A	£1.60
300-0-300 80mA	6 3V 3 5A 6 3V 1A or 5V 2A	£1.80
300-0-300 120mA	2 x 6 3V 2A CT x 6 3V 2A	£1.50
220V 50mA 6 3V 2A		£1.00
HEATER TRANS	6 3V 3A £1.45 1 amp	£1.00

GENERAL PURPOSE LOW VOLTAGE Tapped outputs at 2A 3 4 5 6 8 9 10 12 15 16 24 and 30V
1A 6 8 10 12 15 16 20 24 30 36 40 48 60
2A 6 8 10 12 15 16 20 24 30 36 40 48 60
3A 6 8 10 12 15 16 20 24 30 36 40 48 60
5A 6 8 10 12 15 16 20 24 30 36 40 48 60
5 8 10 16V 1A £2. 12V 100mA £1. 12V 300mA £1.

12V 750mA **£1.30** 40V 2A tapped 10V or 30V **£2.95**
10-0-10V 2A **£2.50** 40V 2A **£2.95** 30V 5A 34V 2A **£1. £3.75**
2 x 15V 6A **£9.** 12-0-12V 2 amp **£2.95** 25-0-25V 2 amp **£4.**
20-0-20V 1A **£2.95** 30V 1A **£2.75** 20V 1A **£2.20**
9V 3 amp **£2.75** 60V 40V 20V or 20-0-20V 1A **£3.50**
30-0-30 2A **£7.** 9V 250mA **£1.30** 30V 2 amp **£3.**
AUTO TRANSFORMERS: 115V to 230V or 230V to 115V
150W **£7;** 250W **£8;** 400W **£9;** 500W **£10.**
CHARGER TRANSFORMERS: input 200/250V for 6 or 12V
1 1/2A **£7.5;** 3A **£9;** 4A **£10.**
FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12V outputs
1 1/2A **55p;** 4A **£1.25.** HALF WAVE 12V 1 1/2A **25p.**

BLANK ALUMINIUM CHASSIS, 18 s.w.g. 2 1/2 in. sides, 6 x 4 in. 95p; 8 x 6 in. £1.40; 10 x 7 in. £1.55; 14 x 9 in. £1.90; 16 x 6 in. £1.65; 12 x 9 in. £1.20; 16 x 10 in. £2.20; 12 x 8 in. £1.70.
ALUMINIUM PANELS, 18 s.w.g. 6 x 4 in. 24p; 8 x 6 in. 38p; 10 x 7 in. 54p; 12 x 9 in. 50p; 12 x 8 in. 70p; 16 x 6 in. 70p; 14 x 9 in. 94p; 12 x 12 in. £1; 16 x 10 in. £1.16.
ALUMINIUM ANGLE BRACKET, 8 x 8 x 1/2 in. 20p.
ALUMINIUM BOXES, MANY SIZES IN STOCK
4 x 2 x 2 in. 80p; 3 x 2 x 1 in. 85p; 6 x 4 x 2 in. 95p; 8 x 6 x 3 in. £1.50; 9 x 4 x 4 in. £1.70; 6 x 4 x 4 in. £1.30; 10 x 7 x 3 in. £2.20.

THE "INSTANT" BULK TAPE ERASER £5.50
Suitable for cassettes and all sizes of tape reels a.c. mains 200-240V Post
Leaflet S A E 50p
Head demagnetiser **£4.75**

RADIO COMPONENT SPECIALISTS 337 WHITEHORSE ROAD, CROYDON, U.K. Tel. 01-684 1665

Minimum post 30p. Access and Barclaycard/Visa. Same day despatch. Radio Books and Components Lists 20p. Open 9-8 Sat. 9-5 (Closed Wednesday all day).

Codespeed

PO Box 23, 34 Seafield Road, Copnor, Portsmouth, PO3 5BJ

ELECTRONIC MAIL ORDER SPECIALISTS

New, Full Spec. Devices

MM5314 CLOCK CHIP SNIP. A bulk purchase allows us to offer these digital clock chips at the unbelievable price of only **£1.99** each. With data. Cat. Number 207

CALCULATOR KEYBOARDS. Two multifunction calculator keyboards. Excellent key action. Only **£1.00** the pair. Cat. number 101

DIGITAL MULTIMETER CHIP. This MM5330 d.v.m. chip can be used to build a high accuracy d.v.m. or panel meter. Has auto polarity and over-range indication. Supplied with data and circuit. Requires some additional circuitry. Only **£3.95** Cat. number 404

9 DIGIT DISPLAY. A 9 digit, 7 segment gas discharge display. Super, bright 0.25" high digits. With data, only **75p** Cat. number 310

10 HYBRID CIRCUITS. Now miniaturise your home produced PCB's with these 10 hybrid circuits, each containing 8 resistors and 8 capacitors. Useful values. 10 hybrids for 50p Cat. number 801

P.U.T.'s. Four MEU21 Programmable Unijunction Transistors (electrically similar to 2N6027). Lots of uses, long delay times, oscillators, phase controllers and many more. With data and usage sheet. 4 for 50p Cat. number 402

LED CLOCK DISPLAY. A superb 24 hour LED clock display with 0.8" high digits. Display panel is common cathode and non-multiplexed. A snip at only **£3.95** Cat. number 204

2102 MEMORIES. Now at a new low price. These MM2102, 1024 bit static RAM's are offered for only 99p Supplied with data sheet. Cat. number 102

4 DIGIT LIQUID CRYSTAL DISPLAY. A super, high contrast 4 digit non-multiplexed display. Digit height is 0.5" and the display is supplied with data and a special, easy to solder, edge connector. **£6.95** Cat. number 206

6 DIGIT L.E.D. DISPLAY. A common cathode 6 digit 7 segment L.E.D. display from Texas Instruments. Multiplexed with built in bubble magnifiers. Digit height 0.1". **£1.00** Cat. number 206

DIGITAL ALARM CLOCK MODULE. A digital alarm clock module, complete with 0.5" LED display. Just add mini transformer and time setting switches for fully functional clock. With data and instructions, only **£6.50** Cat. number 205

5 DIGIT MICRO L.E.D. DISPLAY. Built on top of a 16 pin dual in line package this 7 segment display has 5 bright 0.09" high digits. Terrific value for only 75p Cat. number 308

Untested or Used Items

CALCULATOR TOPS (Untested - so no guarantees). The upper half of two hand held calculator cases with integral keyboard. Ex-equipment but believed to be o.k. Only 50p the pair. Cat. number 105

DEFECTIVE CALCULATORS. A production line reject calculator with lots of accessible goodies inside. Detachable keyboard, display, case and PCB with approx. 25 transistors and calculator chip. Not much wrong with some we tested. A bargain at only **£2.50** Cat. number 104

Postage and Packing please add 25p (Overseas orders add 60p)
Your satisfaction guaranteed on all items.
New spring catalogue now available. Send medium sized S.A.E. for your free copy.

EVERYBODY'S DOING IT!

Doing what? Sending for the latest Home Radio Catalogue. It's the most comprehensive components catalogue you can get. 128 pages, about 2,500 items listed, and profusely illustrated. Now only **£1.25**, with a free bargain list. Send your cheque or postal order now.

Home Radio Components Ltd.
Dept. PE, 234 London Road,
Mitcham, Surrey CR4 3HD

QUALITY REEL TO REEL & CASSETTE TAPE HEADS

SOME POPULAR UNIVERSAL CASSETTE TAPE HEADS

B12-01	MONO PLAYBACK	£1.80	E12-09	MONO/STEREO ERASE	£1.80
B12-02	MONO RECORD/PLAYBACK	£3.92	B22-02	TWIN HALF TRACK RECORD/PLBK	£5.82
B24-01	STEREO PLAYBACK	£3.22	C44RPS02	QUAD QUARTER TRACK REC/PLBK	£9.14
B24-02	STEREO RECORD/PLAYBACK	£6.50	C22ES02	TWIN HALF TRACK ERASE	£4.60
B24-PP	STEREO GLASS FERRITE REC/PLBK	£11.32			

AUDIO AND HI-FI CATALOGUE (80 PAGE FULL COLOUR) 50 PENCE

MONOLITH

THE MONOLITH ELECTRONICS CO. LTD.
5/7 CHURCH ST., CREWKERNE, SOMERSET, ENGLAND. (0460) 74321

PLEASE ENCLOSE 30p P&P WITH ORDER
ALL PRICES INCLUDE VAT

76 Practical Electronics June 1979

**QUARTZ LCD
5 Function**

Hours, mins., secs., month, date, auto calendar, back-light, quality metal bracelet.

£6.65

Guaranteed same day despatch.
Very slim, only 6mm thick.



M1

**QUARTZ LCD
7 Function**

Hours, mins., secs., month, date, auto calendar, back-light, seconds STOP WATCH.

£9.65

Guaranteed same day despatch.
Very slim, only 6mm thick.



M2

**QUARTZ LCD
11 Function SLIM CHRONO**

6 digit, 11 functions. Hours, mins., secs., day, date, day of week. 1/100th, 1/10th, secs., 10X secs., mins. Split and lap modes. Back-light, auto calendar. Only 8mm thick. Stainless steel bracelet and back. Adjustable bracelet. Metac Price

£12.65 Thousands sold!

Guaranteed same day despatch.



M3

**QUARTZ LCD
ALARM 6 Function**

Hours, mins., secs., month, date, back-light, 24 hour ALARM. Adjustable stainless steel bracelet. Only 9mm thick.

£12.65

Guaranteed same day despatch.



M4

**QUARTZ LCD
ALARM 7 Function**

Hours, mins., secs., day, date, alpha day, back-light, auto calendar. Adjustable stainless steel bracelet. Only 9mm thick.

£17.65

Guaranteed same day despatch.



M5

**QUARTZ LCD Alarm
Chronograph with Dual
Time Zone Facility**

Constant LCD display of hours and minutes (plus optional seconds or date display, plus day of the week and am/pm indication) Perpetual calendar, day, date, month and year. 24 hour alarm with on/off indication 1/10 second chronograph measuring net, lap and first and second place times. Dual time zone facility night light. Only 9mm thick.

£22.65



M6

**SOLAR QUARTZ LCD
Chronograph with Alarm
Time Zone Facility**

Constant LCD display of hours and minutes, plus optional seconds or date display, plus day of the week and am/pm indication Perpetual calendar, day, date, month and year 24 hour alarm with on/off indication 1/10 second chronograph measuring net, lap and first and second place times. Dual time zone facility night light. Only 9mm thick.

£25.65



M7

**QUARTZ LCD
Alarm Chrono**

22 function, 6 digit. Hours, mins., secs., date, day of week, stopwatch, split time, alarm, second watch (dual time), back-light. FRONT BUTTON OPERATION.

£22.65

Guaranteed same day despatch

METAC ★ PRICE



M8

**SOLAR QUARTZ LCD
Chronograph**

6 digit, 11 function. Hours, mins., secs. 1/100, 1/10 secs., mins. Split and lap modules. Auto calendar and back light. Powered from solar panel with battery back-up.

£13.95



M9

SEIKO Alarm Chrono

LCD, hours, mins., secs., day of week, month, day and date, 24 hour Alarm, 12 hour chronograph, 1/10th secs., and lap time. Back light, stainless steel, HARDLEX glass. List Price £130.00 METAC PRICE

£105.00



M10

SEIKO Chronograph

LCD, hours, mins., secs., day of week, month, day, date, 12 hour chronograph, 1/10th secs. and lap-time. Back light, stainless steel water resistant, HARDLEX glass.

List Price £85.00

METAC PRICE

£68.00



M11

**SOLAR QUARTZ LCD
5 Function**

Genuine Solar / Solar panel with battery back-up. Back light and auto calendar. Hours, mins., secs., day, date. Quality metal bracelet.


£8.95

Guaranteed same day despatch.



M12

**HANIMEX
Electronic
LED Alarm Clock**

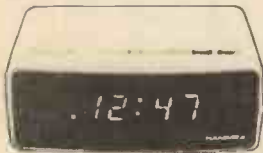

Features and Specification: Hour/minute display. Large LED display with p.m. and alarm on indicator. 24 Hours alarm with on/off control. Display flashing for power loss indication. Repeatable 9-minute snooze. Display bright/dim modes control. Size: 5.15" x 3.93" x 2.36" (131mm x 111mm x 60mm). Weight 1.43 lbs (0.65 kg). AC power 220V.

£8.65 Thousands sold!

Guaranteed same day despatch.

M13

**QUARTZ LCD
Ladies Slim Bracelet**

5 function. Hours, mins., secs., day, date and back light and auto calendar. Elegant metal bracelet in silver or gold. State preference. **£15.95** Guaranteed same day despatch.



M14


**QUARTZ LCD
Ladies 5 Function**

Only 25 x 20mm and 6mm thick. 5 function. Hours, mins., secs., day, date and back light and auto calendar. Elegant metal bracelet in silver or gold. State preference. **£9.95** Guaranteed same day despatch.



M15

**DIGITAL
LED CLOCK**

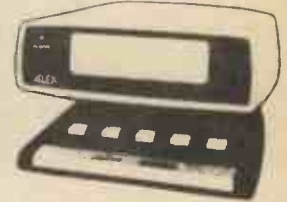

Automatic brightness control. Weekend alarm cancel.

Features and Specification: Hour/minute display. Large LED display with p.m. and alarm on indicator. 24 Hours alarm with on-off control. Display flashing for power loss indicator. Repeatable 9-minute snooze. Automatic brightness control. Weekend alarm cancel.

£10.95

Guaranteed same day despatch.

M16

HOW TO ORDER

Payment can be made by sending cheque, postal order, Barclay, Access or American Express card numbers. Write your name, address and the order details clearly, enclose 30p for post and packing or the amount stated. We do not wait to clear your cheque before sending the goods so this will not delay delivery. All products carry 1 year guarantee and full money back 10 day reassurance. Battery fitting service is available at our shops. All prices include VAT.

Trade enquiries: Send for a complete list of trade prices — minimum order value £100. Telephone Orders: Credit card customers can telephone orders direct to Daventry or Edgware Rd., 24 hour phone service at both shops: 01-723 4753 03272-76545.



CALLERS WELCOME
Shops open 9.30 - 6.00.

Metac

ELECTRONICS
& TIME CENTRES

North & Midlands
67 High Street, DAVENTRY
Northamptonshire
Telephone: 03272 76545


South of England
327 Edgware Road
LONDON W.2
Telephone: (01) 723 4753

The latest kit innovation!

from Sparkrite

*Sparkrite -
was featured by Shaw Taylor
in 'DRIVE IN'*

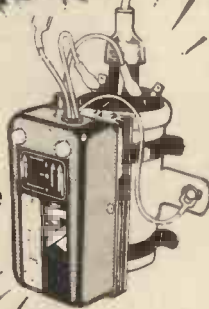the quickest fitting
CLIP ON
capacitive discharge
electronic ignition
in KIT FORM



- Smoother running
- Instant all-weather starting
- Continual peak performance
- Longer coil/battery/plug life
- Improved acceleration/top speeds
- Optimum fuel consumption

Sparkrite X4 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 1/3 mins.

Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). The circuit incorporates a voltage regulated output for greatly improved cold starting. The circuit includes built in static timing light, systems function light, and security changeover switch. All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISES EVERYTHING NEEDED

Die pressed epoxy coated case. Ready drilled, aluminium extruded base and heat sink, coil mounting clips, and accessories. Top quality 5 year guaranteed transformer and components, cables, connectors, P.C.B., nuts, bolts and silicon grease. Full instructions to assemble kit neg. or pos. earth and fully illustrated installation instructions.

NOTE — Vehicles with current impulse tachometers (Smiths code on dial RV1) will require a tachometer pulse slave unit. Price £3.85 inc. VAT, post & packing UK only.

Electronics Design Associates, Dept. PE 10, 82 Bath Street, Walsall, WS1 3DE. Phone: Walsall 614791

Electronics Design Associates, Dept. PE 6
82 Bath Street, Walsall, WS1 3DE. Phone: (9) 614791

Name

Address

Phone your order with Access or Barclaycard

Inc. V.A.T. and P.P.

QUANTITY REQD.

Send SAE if brochure only required.

X4 KIT £16.65

I enclose cheque/PO's for

TACHOPULSE SLAVE UNIT £3.85

£

Cheque No.

Please state polarity pos or neg earth.
Access or Barclaycard No.

ELECTROVALUE

Your leading direct suppliers for

nm

**NASCOM MICROCOMPUTERS
AND FULL SUPPORTING RANGE
OF ITEMS TO ENABLE YOU TO
WORK AT PROPER
PROFESSIONAL LEVELS**

- ★ At newest reduced prices.
- ★ Widest possible range stocked
- ★ Information on request
- ★ Enquiries from trade, industrial and educational users invited

**Appointed distributors for the
fine products of:**

**SIEMENS, ISKRA, RADIOHM,
VERO AND MANY OTHER
FAMOUS MANUFACTURERS**

It's a good deal better from

ELECTROVALUE LTD

Dept. PE6, 28 St. Judes Road, Englefield Green, Egham, Surrey TW20 0HB.

Phone: Egham 3603. Telex 264475.

Northern Branch (Personal shoppers only), 680 Burnage Lane,
Burnage, Manchester M19 1NA. Phone (061) 432 4945.

- We pay postage in U.K. on orders list value £5 or over. If under, add 27p handling charge.
- We give discounts on C.W.O. orders, except items marked Net or N in our catalogues.
 - on orders, list value **5%** £10 or more
 - on orders list value **10%** £25 or more.
 Not on Access or Barclay orders
- We stabilise prices. by keeping to our printed price lists which appear but three or four times a year.
- We guarantee all products brand new, clean and to maker's spec. No seconds, no surplus.
- WE WILL SEND YOU OUR 120-PAGE CATALOGUE No. 9 FREE ON REQUEST. Comprehensive, informative, very well produced. Write, phone or call for your free copy, together with latest price list.

JAYEN

BUILD THESE ADVANCED DESIGN INSTRUMENTS

DM-2



FG-1a



- DIGITAL MULTIMETER**
- DC Volts 1mV to 1000V
 - AC Volts 1V to 500V
 - DC Current ... 0.1mA to 0.2A
 - Resistance 1Ω to 20MΩ
 - Battery Test Point
 - Auto Polarity & Zero
 - Total cost less than £30 (incl. case)
- FUNCTION GENERATOR**
- 30mV to 10V pk-pk
 - 1Hz to 100kHz
 - DC coupled amplifier
 - Sine, Square & Triangle
 - Separate TTL output
 - Total cost less than £20 (case extra)

Jayen Developments, 21 Gladeside, Bar Hill, Cambridge CB3 8DY. Tel: (0954) 80285.

To: JAYEN Developments, 21 Gladeside, Bar Hill, Cambridge CB3 8DY
Tel: (0954) 80285

Please send a JAYEN

DM-2 @ £4.85

FG-1a @ £4.50

(Incl. VAT and P&P)

Name

Each kit comprising a PC board, punched and lettered Front Panel, Instructions and Component Shopping List.

Money to be refunded if the kit is returned within 10 days.

PE6

15-240 WATTS!

HY5 Preamplifier

The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (mag Cartridge, tuner, etc.) are catered for internally, the desired function is achieved either by a multi-way switch or direct connection to the appropriate pins. The internal volume and tone circuits merely require connecting to external potentiometers (not included). The HY5 is compatible with all I.L.P. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre-amplifier.

FEATURES: complete pre-amplifier in single pack, multi-function equalisation; low noise; low distortion; high overload; two simply combined for stereo.

APPLICATIONS: hi-fi; mixers; disco; guitar and organ; public address.

SPECIFICATION: Inputs—magnetic pick-up 3mV; ceramic pick-up 30mV; tuner 100mV; microphone 10mV; auxiliary 3-100mV; input impedance 47k Ω at 1kHz. Outputs—tape 100mV, main output 500mV R.M.S. Active Tone Controls—treble \pm 12dB at 10kHz; bass \pm 12dB at 100Hz. Distortion—0.1% at 1kHz, signal/noise ratio 68dB. Overload—38dB on magnetic pick-up. Supply Voltage— \pm 16-50V.

Price £6.27 + 78p VAT. P. & P. free

HY5 mounting board B.1. 48p + 6p VAT. P. & P. free



HY30 15W into 8 Ω

The HY30 is an exciting New kit from I.L.P. It features a virtually indestructible I.C. with short circuit and thermal protection. The kit consists of: I.C., heatsink, P.C. board, 4 resistors, 6 capacitors, mounting kit, together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up to date technology available.

FEATURES: complete kit, low distortion, short, open and thermal protection; easy to build.

APPLICATIONS: updating audio equipment; guitar practice amplifier; test amplifier; audio oscillator.

SPECIFICATION: Output Power—15W R.M.S. into 8 Ω . Distortion—0.1% at 15W. Input Sensitivity—500mV. Frequency Response—10Hz-16kHz -3dB.

Price £6.27 + 78p VAT. P. & P. free

HY50 25W into 8 Ω

The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most reliable and robust High Fidelity modules in the World.

FEATURES: low distortion; integral heatsink, only five connections; 7 amp output transistors; no external components.

APPLICATIONS: medium power hi-fi systems; low power disco; guitar amplifier.

SPECIFICATION: Input Sensitivity—500mV. Output Power—25W R.M.S. into 8 Ω . Load Impedance—4-16 Ω . Distortion—0.04% at 25W at 1kHz. Signal/Noise Ratio—75dB. Frequency Response—10Hz-45kHz -3dB. Supply Voltage— \pm 25V. Size—105 x 50 x 25mm.

Price £8.18 + £1.02 VAT. P. & P. free



HY120 60W into 8 Ω

The HY120 is the baby of I.L.P.'s new high power range, designed to meet the most exacting requirements including load line and thermal protection this amplifier sets a new standard in modular design.

FEATURES: very low distortion; Integral heatsink, load line protection; thermal protection, five connections; no external components.

APPLICATIONS: hi-fi; high quality disco; public address; monitor amplifier; guitar and organ.

SPECIFICATION: Input Sensitivity—500mV. Output Power—60W R.M.S. into 8 Ω . Load Impedance—4-16 Ω . Distortion—0.04% at 60W at 1kHz. Signal/Noise Ratio—90dB. Frequency Response—10Hz-45kHz -3dB. Supply Voltage— \pm 35V. Size—114 x 50 x 85mm.

Price £19.01 + £1.52 VAT. P. & P. free

HY200 120W into 8 Ω


The HY200 (now improved to give an output of 120 watts) has been designed to stand the most rugged conditions such as disco or group while still retaining true hi-fi performance.

FEATURES: thermal shutdown; very low distortion; load line protection; integral heatsink; no external components

APPLICATIONS: hi-fi; disco; monitor; power slave; industrial; public address

SPECIFICATION: Input Sensitivity—500mV. Output Power—120W R.M.S. into 8 Ω . Load Impedance—4-16 Ω . Distortion—0.05% at 100W at 1kHz. Signal/Noise Ratio—96dB. Frequency Response—10Hz-45kHz -3dB. Supply Voltage— \pm 45V. Size—114 x 50 x 85mm.

Price £27.99 + £2.24 VAT. P. & P. free

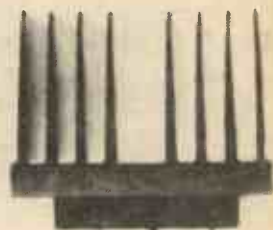

HY400 240W into 4 Ω


The HY400 is I.L.P.'s Big Daddy of the range producing 240W into 4 Ω ! It has been designed for high power disco or public address applications. If the amplifier is to be used at continuous high power levels a cooling fan is recommended. The amplifier includes all the qualities of the rest of the family to lead the market as a true high power hi-fidelity power module.

FEATURES: thermal shutdown; very low distortion; load line protection; no external components.

APPLICATIONS: public address; disco; power slave; industrial.

SPECIFICATION: Output Power—240W R.M.S. into 4 Ω . Load Impedance—4-16 Ω . Distortion—0.1% at 240W at 1kHz. Signal/Noise Ratio—94dB. Frequency Response—10Hz-45kHz -3dB. Supply Voltage— \pm 45V. Input Sensitivity—500mV. Size—114 x 100 x 85mm.

Price £38.61 + £3.09 VAT. P. & P. free

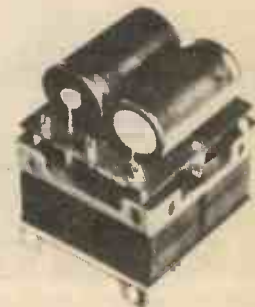

POWER SUPPLIES: PSU36—suitable for two HY30s £6.44 + 81p VAT. P. & P. free. PSU50—suitable for two HY50s £8.18 + £1.02 VAT. P. & P. free. PSU70—suitable for two HY120s £14.58 + £1.17 VAT. P. & P. free. PSU90—suitable for one HY200 £15.19 + £1.21 VAT. P. & P. free. PSU180—suitable for two HY200s or one HY400 £25.42 + £2.03 VAT. P. & P. free.

Free post + packing applicable to U.K. only.

TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS

I.L.P. Electronics Ltd.,
Graham Bell House,
Roper Close, Canterbury,
Kent CT2 7EP.
Tel: (0227) 54778

Please supply

Total Purchase price

I Enclose: Cheque Postal Orders Money Order

Please debit my Access account Barclaycard account

Account number

Name and Address

Signature

Registered office No. 1032630

TRANSFORMERS EX-STOCK

PRICES INCLUDE VAT. SAME DAY DESPATCH

12 OR 24 VOLT OR 12-0-12V PRIMARY 220-240V VOLTS

Ref	12V Amps	24V £	P & P
111	0.5	0.25	2.38
213	1.0	0.5	2.85
71	2	1	3.79
18	4	2	4.35
85	5	2.5	4.86
70	6	3	6.78
108	8	4	8.02
72	10	5	8.77
116	12	6	9.71
17	16	8	11.58
115	20	10	15.10
187	30	15	19.36
226	60	30	39.03

50 VOLT RANGE

Pri 220/240V Sec 0-20-25-33-40-50V. Voltages available 5, 7, 8, 10, 13, 15, 17, 20, 33, 40 or 20V-0-20V, 25V-0-25V.

Ref	Amps	£	P & P
102	0.5	3.68	0.84
103	1.0	4.94	1.04
104	2.0	7.73	1.23
105	3.0	9.24	1.43
106	4.0	12.32	1.62
107	6.0	16.26	1.77
118	8.0	21.88	2.25
119	10.0	26.98	2.25
109	12.0	31.21	2.25

MAINS ISOLATORS (SCREENED)

Pri 120/240V SEC 120/240V (C. Tapped)

Ref	VA (Watts)	£	P & P
07*	20	4.75	0.85
149	60	7.24	1.04
150	100	8.23	1.23
151	200	12.05	1.62
152	250	14.34	1.99
153	350	17.74	1.99
154	500	22.11	2.32
155	750	31.38	2.65
156	1000	40.18	2.65
157	1500	55.49	2.65
158	2000	66.75	2.65
159	3000	93.59	2.65

HIGH VOLTAGE ISOLATORS

Prim 200/220V or 400/440V Sec 110/120V CT or 200/240 CT

VA	Ref	£	P & P
60	243	7.24	1.43
350	247	17.74	1.99
1000	250	45.10	2.65

30 VOLT RANGE

Pri 220/240V Sec 0-12-15-20-24-30V. Voltages available 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30V or 12V-0-12V, 15V-0-15V.

Ref	Amps	£	P & P
112	0.5	2.85	0.84
79	1.0	3.88	1.04
3	2.0	6.23	1.04
20	3.0	6.70	1.23
21	4.0	8.63	1.23
51	5.0	10.66	1.43
117	6.0	12.06	1.57
88	8.0	18.15	1.77
89	10.0	18.63	1.99
90	12.0	20.70	2.11
91	15.0	23.72	2.25
92	20.0	31.81	2.65

60 VOLT RANGE

Pri 220/240V Sec 0-24-30-40-48-60V. Voltages available 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60V or 24V-0-24V, or 30V-0-30V.

Ref	Amps	£	P & P
124	0.5	4.19	1.04
126	1.0	6.38	1.04
127	2.0	8.21	1.23
125	3.0	11.88	1.43
123	4.0	13.52	1.62
40	5.0	17.11	1.99
120	6.0	19.50	1.99
121	8.0	27.80	2.25
122	10.0	31.91	2.65
189	12.0	36.78	2.65

AUTO TRANSFORMERS

Ref	VA (Watts)	£	P & P
113	15 0-115-210-240	2.68	0.77
64	75 0-115-210-240	4.33	1.04
4	150 0-115-200-220-240	5.78	1.04
69	250	7.60	1.23
67	500 0-115-200-220-240	11.87	1.77
84	1000 0-115-200-220-240	20.26	2.25
93	1500 0-115-200-220-240	25.14	2.65
95	2000 0-115-200-220-240	37.61	2.65
73	3000 0-115-200-220-240	63.95	2.65
80S	4000 0-115-200-220-240	83.01	2.65
57S	5000 0-115-200-220-240	96.66	2.65

CASED AUTO TRANSFORMERS

240V cable in & 115V USA 2 pin outlet

VA	Ref	£	P & P
20	6.43	1.04	56W
75	8.35	1.23	64W
150	10.81	1.23	4W
200	12.01	1.57	65W
250	12.15	1.57	69W
500	20.70	1.77	67W
1000	30.11	2.25	84W
1500	35.48	2.65	93W
2000	53.97	2.65	95W

SCREENED MINIATURES

Ref	mA	Volts	£	P & P
238	200	3-0-3	2.78	0.59
212	1A, 1A	0-6, 0-6	3.08	0.84
13	10A	0-9, 0-9	2.31	0.41
235	330, 330	0-9, 0-9	2.31	0.41
207	500, 500	0-8-9, 0-8-9	2.99	0.77
208	1A, 1A	0-8-9, 0-8-9	3.81	0.84
236	200, 200	0-15, 0-15	2.15	0.41
214	300, 300	0-20, 0-20	3.02	0.84
221	700 (DC)	20-12-0-12-20	3.68	0.84
206	1A, 1A	0-15-20-0-15-20	5.00	1.04
203	500, 500	0-15-27-0-15-27	6.31	1.04
204	1A, 1A	0-15-27-0-15-27	6.52	1.04
239	50	12-0-12	2.78	0.41

TEST METERS

U4315 Budget Meter 20,000 ohm/V Ranges 1000V AC/DC 2.5A AC/DC 500K resistance in steel robust case £17.12
AV08 Mk5 £95.15
AV071 £38.88
AV073 £52.60
EM272 £62.42
MM5 minor £35.59
DA116 AVO digital £117.61

MINI-MULTIMETER

DC-1000V AC-1000V DC-100mA Res 150KΩ 1000Ω/V Bargain £7.78 P & P 67p

20,000 ohm/V Multimeter, mirror scale. Ranges AC/DC to 1000V, DC currents to 250mA. Resistance to 3 Megs. 5" x 3 1/4" x 1 1/2". £14.44 P & P £1.13

ISOLATOR - Special Price

0-200-220-240V, 0-240V Centre Tap, 250VA. Ref. 62 £56.2 P & P £1.04

ELECTROSIL TR4 5% £2.15/100

ELECTRONIC CIRCUIT KIT

Home electronics teacher. Start simply and progress to a TRF radio or electronic organ. No soldering, all parts included in presentation box. Full instructions. Price £8.95 P & P £1.04

PANEL METERS

Ref.	Ref.	£	
0-50µA	6.70	0-50µA	7.24
0-500µA	6.43	0-500µA	7.24
0-1mA	6.43	0-1mA	7.24
0-30V	6.43	0-30V	7.24

SEND 15p STAMPS FOR CATALOGUE

Prices correct 1.12.78. PE1.

COMPONENT PACKS

65 1/2w Metal Oxide Resistors
65 1/2w Metal Oxide Resistors
150 Mixed Value Capacitors
10 Read Switch.
60 Wire Wound Resistors.
10 Caps 3000mf 30v.
25 assorted Presets.
50 Wire Wound Resistors.
Warders B.A. nuts, bolts, washers etc.
10 mixed value electrolytic capacitors from 32µf to 2,000µf

BE9 Miniature Transformer

Pri 0-240V Scr 28 x 26 x 20mm Sec. 12-0-12V
50MA 97p P & P 14p

NEW RANGE TRANSFORMERS

Pri 0-220-240V 2 Amp. 45-36-0-36-45 £12.14 P & P £1.40
Sec. 0-36-48 twice. To give 36 0 36 48 0 48 72V or 92V.
Pri 120 or 240V 2 Amp.
2 amp 13.11 P & P 1.51
3 amp 15.88 P & P 1.60
4 amp 20.27 P & P 1.99
5 amp 28.77 P & P 2.32
171 Centre 3.20 P & P 0.84
173 Tapped 3.88 P & P 0.84
174 4.05 P & P 0.93
175 6.19 P & P 1.04

S-DECS Solderless bread boarding

Ref. £
S Dec 3.35
T Dec 4.70 P & P 43p
U Dec A 4.86
U Dec B 7.55

ANTEX SOLDERING IRONS

Ref. £
15W 4.05 P & P 50p
25W 4.27 P & P 50p
Stand 1.71

BRIDGE RECTIFIERS

Ref. £
100V 25A 2.36
200V 2A 0.51 P & P 16p
400V 4A 0.96
400V 6A 1.41
500V 12A 3.08

AMPLIFIER MODULES

Ref.	£	P & P
10W (AL30)	4.58	0.38
25W (AL60)	5.57	0.38
35W (AL80)	8.76	0.38
125W (AL250)	21.08	0.38
PS12	2.18	0.38
SPM80	4.78	0.38
PA12	8.66	0.38
PA100	19.38	0.38

ABS Plastic Boxes inset brass nuts, slots to take PC cards, flush fitting lid.

Ref.	£	P & P
PB1 90mmx62x40	0.70	0.31
PB2 100mmx75x40	0.79	0.31
PB3 120mmx100x45	0.94	0.31
PB4 215mmx130x85	2.74	0.43

Plug in Saver Batteries

P126 - fits into 13A SKT 6, 7-5, 9V, 300MA multipoint outlet £4.50 P & P 0.59

TRANSFORMERS Special Offer

P.W. Purbeck oscilloscope transformer in stock 250-0-250
6-3V, 12-9V £7.51 P & P 97p
BE3 100V line to 4Q 7/10W £2.21 P & P 77p
BE4 0-120V x 2 (120V or 240) Screen sec 9-0-9V 1A £2.59 P & P 77p
BE5 15W matching trans. sec 150 volt EL84 £1.62 P & P 32p
BE6 Pri 0-220V sec 4500V, 10 MA £4.86 P & P £1.08
BE7 0-110-120 220V Pri 240V Sec 220V 1A £1.62 32p P & P
BE8 0-240 15-0-15V 2A £1.62 P & P 76p
Ref 30 240-240 isolator 200VA £4.54 P & P £1.04

Barrie Electronics Ltd.
3, THE MINORIES, LONDON EC3N 1BJ
TELEPHONE: 01-488 3316/7/8
NEAREST TV STATIONS: ALDGATE & LIVERPOOL ST

Put a Clamp on those small jobs with NODEX quick-grip vice



Adaptable to all drill supports. V-notch allows fixing of all profiles.

Dimensions	
Overall length	150mm
Overall width	130mm
Overall height	50mm
Jaw opening	70mm
Jaw height	35mm
Jaw width	70mm
Weight	850 grammes

The patented locking system of the Nodex vice allows for instantaneous locking or loosening for use as a vice or as a press. Usable horizontally or vertically on the bench top or on the bench edge.

Descriptive leaflet and general catalogue available from:

SPECIAL PRODUCTS DISTRIBUTORS LTD.

81 PICCADILLY, LONDON W1V 0HL

Tel: 01-629 9556

Cables: Speciproduct London W1

SINCLAIR PRODUCTS microvision tv world model £147.95, UK model £89.95, mains adaptor £6.73, PM35 £28.95, mains adaptor £3.19, case £3.19, DM350 £68.95, DM450 £97.95, DM235 £49.45, rechargeable batts £7.50, mains adaptor £3.70, case £8.45, enterprise prog calculator with accessories £22.95, cambridge prog calculator £12.13, prog library £4.45, mains adaptor £3.20.
CSC MAX100 freq meter £75.40.
CALSCOPE oscilloscopes send see for data or see the Calscope advert in this magazine. Super 6 £174, Super 10 £236.
COMPUTER GAMES chess challenger 10 £167, chess challenger 7 £79, checker challenger 4 £84, checker challenger 2 £50, Atari videocomputer £138, cartridges £13.45.
COMPONENTS send see for full list. 1N4148 1.4p, 1N4002 2.9p, 741 15p, bc182b, bc183b, bc184b, bc212b, bc213b, bc214c 4.5p, resistors 1W 5% £12 10R to 10M 1p, 0.8p for 50+ of one value. 16V electrolytics. 5/12/5/10/22uf 5p, 100uf 6p, 1000uf 10p, 1 lb FeCl 1.05, dabo pen 79p, 60sq ins pcb 55p.
IC AUDIO AMPS with pcb. JC12 6W £1.60, JC20 10W £2.95, send see for data.
BATTERY ELIMINATORS 3-way type 6/7 1/2V 300mA £2.95, 100mA radio type with press-studs 9V £3.35, 9V+9V £4.50, car converter 12V input, output 4 1/2 6/7 1/2V 800mA £2.50.

TV GAMES send see for data. AY-3-8500 + kit £8.95, rifle kit £4.95, AY-3-8600 + kit £12.50, stunt cycle chip + kit £12.10, tank battle kit £4.50.

TRANSFORMERS 6-0-6V 100mA 74p, 1 1/2 £2.35, 6.3V 1 1/2 £1.89, 9-0-9V 75mA 74p, 1A £2, 2A £2.80, 12-0-12V 100mA 90p, 1A £2.49.

BATTERY ELIMINATOR KITS send see for data. 100mA eliminator types with press-studs 4.3V £1.40, 6V £1.40, 9V £1.40, 4 1/2+4 1/2 £1.80, 6+6V £1.80, 9+9V £1.80, stabilized 8-way types 3/4 1/2 6/7 1/2 9/12/15/18V 100mA £2.80, 1amp £6.40, stabilized power kits 2-18V 100mA £3.60, 2-30V 1A £6.95, 2-30V 2A £10.95, 12V car converter 6/7 1/2 1A £1.35.

T-DEC AND CSC BREADBOARD S-DEC £3.17, t-dec £4.02, u-deca £4.40, u-decb £6.73, exp300 £6.21, exp350 £3.40, exp 325 £1.73, exp4b £2.48.


BI-PAK AUDIO MODULES s450 £23.51, AL80 £4.86, pa100 £16.95, spm80 £4.47, bmt60 £5.95, stereo 90 £29.12, AL30 £3.95, PA12 £7.60, PS12 £1.39, MA60 £35.44.

SWANLEY ELECTRONICS

(Dept. PE), 32 Goldsel Road, Swanley, Kent BR8 8EZ

Post 30p extra, prices include Vat. Official and overseas orders welcome.

STORAGE CABINETS

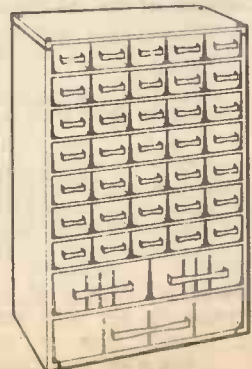


Metal Cabinets 12" wide x 5 3/4" deep, finished blue with transparent plastic drawers.

Type	H (ins)	No. of Drawers	Price
1118	11	15	2 £8-65

Understanding Digital Electronics

New teach-yourself courses

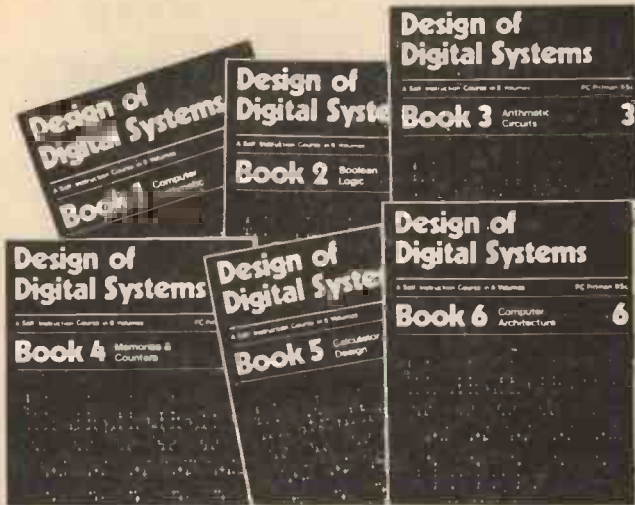

Design of Digital Systems is written for the engineer seeking to learn more about digital electronics. Its six volumes – each A4 size are packed with information, diagrams and questions designed to lead you step-by-step through number systems and Boolean algebra to memories, counters and simple arithmetic circuits, and finally to a complete understanding of the design and operation of calculators and computers.

The contents of Design of Digital Systems include:

Book 1 Octal, hexadecimal and binary number systems; conversion between number systems; representation of negative numbers; complementary systems; binary multiplication and division.


Book 2 OR and AND functions; logic gates; NOT, exclusive-OR, NAND, NOR and exclusive-NOR functions; multiple input gates; truth tables; De Morgans Laws; canonical forms; logic conventions; Karnaugh mapping; three-state and wired logic.

Book 3 Half adders and full adders; subtractors; serial and parallel adders; processors and arithmetic logic units (ALUs); multiplication and division systems.

Book 4 Flip flops; shift registers; asynchronous and synchronous counters; ring, Johnson and exclusive-OR feedback counters; random access memories (RAMs) and read only memories (ROMs).

Book 5 Structure of calculators; keyboard encoding; decoding display data; register systems; control unit; program ROM; address decoding; instruction sets; instruction decoding; control program structure.

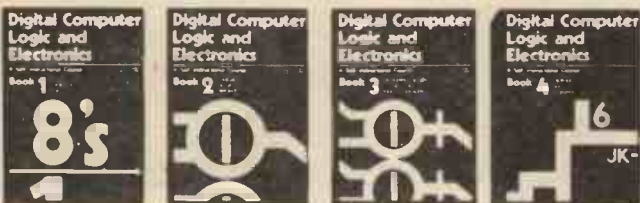Book 6 Central processing unit (CPU); memory organization; character representation; program storage; address modes; input/output systems; program interrupts; interrupt priorities; programming; assemblers; computers; executive programs; operating systems and time sharing.



Digital Computer Logic and Electronics is designed for the beginner. No mathematical knowledge other than simple arithmetic is assumed, though the student should have an aptitude for logical thought. It consists of four volumes – each A4 size – and serves as an introduction to the subject of digital electronics. Everyone can learn from it – designer, executive, scientist, student, engineer.

Contents include: Binary, octal and decimal number systems; conversion between number systems; AND, OR, NOR and NAND gates and inverters; Boolean algebra and truth tables; De Morgans Laws; design of logic circuits using NOR gates; R-S and J-K flip flops; binary counters, shift registers and half adders.

CAMBRIDGE LEARNING ENTERPRISES, Unit 29, Rivermill Site, FREEPOST, ST. IVES, HUNTINGDON, CAMBS. PE17 4BR, ENGLAND. TELEPHONE ST. IVES (0480) 67446. PROPRIETORS: DRAYRIDGE LTD. REG. OFFICE: RIVERMILL LODGE, ST. IVES. REGD. IN ENGLAND NO. 1328762

In the years ahead the products of digital electronics technology will play an important part in your life. Calculators and digital watches are already commonplace. Tomorrow a digital display could show your vehicle speed and fuel consumption; you could be calling people by entering their name into a telephone which would automatically look up their number and dial it for you.

These courses were written by experts in electronics and learning systems so that you could teach yourself the theory and application of digital logic. Learning by self-instruction has the advantages of being faster and more thorough than classroom learning. You work at your own pace and must respond by answering questions on each new piece of information before proceeding.

After completing these courses you will have broadened your career prospects and increased your fundamental understanding of the rapidly changing technological world around you.

The six volumes of Design of Digital Systems cost only: **£8.10** +90p post & packing

And the four volumes of Digital Computer Logic and Electronics cost only: **£4.60** +90p post & packing

But if you buy both courses, the total cost is only: **£12** +£1 post & packing

Price includes surface mail anywhere in the world: Airmail extra.

Flow Charts & Algorithms

HELP YOU PRESENT:

safety procedures, government legislation, office procedures, teaching materials and computer programs by means of YES and NO answers to questions.

THE ALGORITHM WRITER'S GUIDE explains how to: define the questions, put them in the best order and draw the flow chart, with numerous examples shown. All that students require is an aptitude for logical thought. Size: A5, 130 pages. This book is a MUST for those with things to say.

£2.95 + 45p post and packing by surface mail anywhere in the world. Airmail extra.

GUARANTEE

If you are not entirely satisfied your money will be refunded.

Please allow 21 days for delivery.

Cambridge Learning Enterprises, Unit 29, Rivermill Site, FREEPOST, St. Ives, Huntingdon, Cambs. PE17 4BR, England.

Please send me the following books:

-sets Digital Computer Logic & Electronics @ £5.50, p & p included
-sets Design of Digital Systems @ £9.00, p & p included
-Combined sets @ £13.00, p & p included
-The Algorithm Writer's guide @ £3.40, p & p included

Name.....

Address.....

I enclose a *cheque/PO payable to Cambridge Learning Enterprises for £.....

Please charge my *Access/Barclaycard/Visa/Eurocard/Mastercharge/Interbank account number.....

Signature.....*delete as appropriate.

Telephone orders from credit card holders accepted on 0480-67446 (Ansafone). Overseas customers should send a bank draft in sterling drawn on a London Bank, or quote credit card number.

PE29


BIMENCLOSURES



ALL METAL BIMCASES
Red, Grey or Orange 14swg Aluminium removable top and bottom covers. 18 swg black mild steel chassis with fixing support brackets.
BIM 3000
(250x167.5x68.5mm)
£14.58



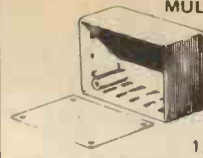MINI DESK BIMCONSOLES
Orange, Blue, Black or Grey ABS body incorporates 1.8mm pcb guides, stand-off bosses in base with 4 BIMFEET supplied. 1mm Grey Aluminium panel sits recessed with fixing screws into integral brass bushes.
BIM 1005 (161 x 96 x 58mm) £2.18
BIM 1006 (215 x 130 x 75mm) £3.05



MULTI PURPOSE BIMBOXES
Orange, Blue, Black or Grey ABS with 1mm Grey Aluminium recessed front cover held by screws into integral brass bushes. 1.8mm pcb guides incorporated and 4 BIMFEET supplied.
BIM 4003 (85x56x28.5mm) £1.18
BIM 4004 (111x71x41.5mm) £1.62
BIM 4005 (161x96x52.5mm) £2.19




ALL METAL BIMCONSOLES

All aluminium, 2 piece desk consoles with either 15° or 30° sloping fronts, sit on 4 self-adhesive non-slip rubber feet. Ventilation slots in base and rear panel for excellent cooling. See latest catalogue for new styles and sizes

Colour Code	Top Panel	Base
A	Off White	Blue
B	Sand	Green
C	Satin Black	Gold

15° Sloping Panel	30° Sloping Panel	
BIM7151 (102x140x51 [28] mm)	BIM7301 (102x140x76 [28] mm)	£10.67
BIM7152 (165x140x51 [28] mm)	BIM7302 (165x140x76 [28] mm)	£11.44
BIM7153 (165x216x51 [28] mm)	BIM7303 (165x183x102 [28] mm)	£12.61
BIM7154 (165x211x76 [33] mm)	BIM7304 (254x140x76 [28] mm)	£13.82
BIM7155 (254x211x76 [33] mm)	BIM7305 (254x183x102 [28] mm)	£15.36
BIM7156 (254x287x76 [33] mm)	BIM7306 (254x259x102 [28] mm)	£16.67
BIM7157 (356x211x76 [33] mm)	BIM7307 (356x183x102 [28] mm)	£17.58
BIM7158 (356x287x76 [33] mm)	BIM7308 (356x259x102 [28] mm)	£18.55

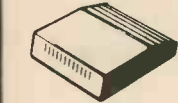


ABS & DIECAST BIMBOXES

6 sizes in ABS or Diecast Aluminium. ABS moulded in Orange, Blue, Black or Grey. Diecast Aluminium in Grey Hammetone or Natural. All boxes incorporate 1.8mm pcb guides, stand-off supports in base and have close fitting flanged lids held by screws into integral brass bushes (ABS) or tapped holes (Diecast).

	ABS	Diecast	Hammetone	Natural
(50x50x31mm)	N/A	BIM5001/11	TBA	£1.02
(100x50x25mm)	BIM2002/12	£0.96	BIM5002/12	£1.46
(112x62x31mm)	BIM2003/13	£1.13	BIM5003/13	£1.78
(120x65x40mm)	BIM2004/14	£1.35	BIM5004/14	£2.24
(150x80x50mm)	BIM2005/15	£1.52	BIM5005/15	£2.84
(190x110x60mm)	BIM2006/16	£2.37	BIM5006/16	£3.94

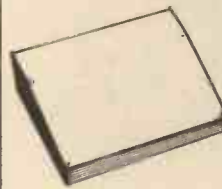
Also available in Grey Polystyrene with no slots and self-tapping screws
BIM 2007/17 (112x61x31mm) £1.00



LOW PROFILE BIMCONSOLES

Orange, Blue, Black or Grey ABS body has ventilation slots as well as 1.8mm pcb guides and stand-off bosses in base. Double angle recessed front panel with 4 fixing screws into integral brass bushes. 4 BIMFEET supplied.

BIM 6005 (143 x 105 x 55.5 [31.5] mm)	£2.37
BIM 6006 (143 x 170 x 55.5 [31.5] mm)	£3.08
BIM 6007 (214 x 170 x 82.0 [31.5] mm)	£4.12

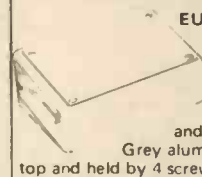

EUROCARD BIMCONSOLES

Orange, Blue, Black or Grey ABS body accepts full or 1/2 size Eurocards, with bosses in the base for direct fixing. 1.8mm wide pcb guides incorporated and 4 BIMFEET supplied. 1mm Grey aluminium lid sits flush with body top and held by 4 screws into integral brass bushes.

BIM 8005 (169x127x70 [45] mm)	£4.12
BIM 8007 (243x187x103 [66] mm)	£6.10

BIMTOOLS + BIMACCESSORIES



MAINS BIMDRILLS


Small, powerful 240V hand drill complete with 2 metres of cable and 2 pin DIN plug. Accepts all tools with 1mm, 2mm or .125" dia. shanks. Drills brass, steel, aluminium and pcb's. Under 250g, off load speed 7500 rpm. Orange ABS, high impact, fully insulated body with integral on/off switch £10.53

Mains Accessory Kit 1 includes 1mm, 2mm, .125" twist drills, 5 burs and 2.4mm collet £2.48

Mains Kit 2 includes Mains BIMDRILL as above, 20 assorted drills, mops, burs, grinding wheels and mounted points, 1mm, 2mm, 2.4mm and .125" collets. Complete in transparent case measuring 230x130x58mm £22.14

BIMDAPTORS

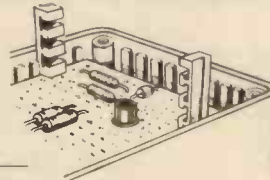Allows pcb's to be flat mounted sandwich fashion in BIMBOXES, BIMCONSOLES, and all other enclosures having 1.5mm wide vertical guide slots. One plastic BIMDAPTOR on each corner of pcb(s) enables assembly to be simply slid into place. 54mm long, 10 slots on 5mm spacing and can be simply snapped off to length. £1.08 per pack of 25.



BIMFEET

11mm dia. 3mm high, grey rubber self-adhesive enclosure feet. £0.77 per pack of 24




12 VOLT BIMDRILLS

2 small, powerful drills easily hand held or used with lathe/stand adaptor. Integral on/off switch and 1 metre cable.

Mini BIMDRILL with 3 collets up to 2.4mm dia. £ 8.10
Major BIMDRILL with 4 collets up to 3mm dia. £13.60

Accessory Kits 1 have appropriate drills and collets as above plus 20 assorted tools. Mini Kit 1 - £15.12, Major Kit 1 - £19.44. Accessory Kits 2 have appropriate drills, collets plus 40 tools and mains-12V dc adaptor. Mini Kit 2 - £34.02, Major Kit 2 - £39.42. Accessory Kits 3 as appropriate Kits 2 plus stand/lathe unit. Mini Kit 3 - £45.36, Major Kit 3 - £50.76.

BIMPUMPS

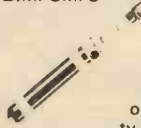

2 all metal desoldering tools provide high suction power and have easily replaceable screw in Teflon tips. Primed and released by thumb operation with in-built safety guard and anti-recoil system.

BIMPUMP Major (180mm long) £7.99
BIMPUMP Minor (150mm long) £6.80

BIMIRONS



Type 30 General Purpose 27 watt iron with long life, rapid change element, screw on tip, stainless steel shaft and clip on hook. Styled handle with neon. £4.05

Type M3 Precision 17 watt iron, quick change tip, long life element, styled handle with clip on hook. £4.43

BIMBOARDS



DIL COMPATIBLE BIMBOARDS



Accept all sizes (4-50 pin) of DIL IC packages as well as resistors, diodes, capacitors and LEDs. Integral Bus Strips up each side for power lines and Component Support Bracket for holding lamps, switches and fuses etc. Available as single or multiple units, the latter mounted on 1.5mm thick black aluminium back plate which stand on non slip rubber feet and have 4 screw terminals for incoming power.

BIMBOARD 1 has 550 sockets, multiple units utilising 2, 3 and 4 BIMBOARDS incorporate 1100, 1650 and 2200 sockets, all on 2.5mm (0.1") matrix.

BIMBOARD 1 £ 8.83

BIMBOARD 2 £21.01

BIMBOARD 3 £29.84

BIMBOARD 4 £38.79

DESIGNER PROTOTYPING SYSTEM

1, 2, or 3 BIMBOARDS mounted on BIM 6007 BIMCONSOLE with Integral Power Supply (± 5 to ± 15 Vdc @ 100mA and fixed +5Vdc @ 1A) All O/P's fully isolated. Short circuit and fast fold back protection. Power rails brought out to cable clamps that accept stripped wire or 4mm plug.

DESIGNER 1 £55.62

DESIGNER 2 £61.02

DESIGNER 3 £66.42

83

...FROM **BOSS**
INDUSTRIAL MOULDINGS LIMITED

All quoted prices are 1 off and include Postage, Packing and VAT. Terms are strictly cash with order unless you have authorised BOSS account. For individual data sheets or short form catalogue on all BOSS products send stamped, self addressed 4x 8 1/2" envelope.

2 Herne Hill Road, London SE24 0AU
Telephone: 01-737 2383
Telex: 919693 Answer Back: 'LITZEN G'
Cables & Telegrams: 'LITZEN LONDON SE24'



NOTICE TO READERS

When replying to Classified Advertisements please ensure:

- (A) That you have clearly stated your requirements.
- (B) That you have enclosed the right remittance.
- (C) That your name and address is written in block capitals, and
- (D) That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

RECEIVERS AND COMPONENTS

P.C.Bs PAXOLIN 10 1/2" x 4 1/4" - £1.25. 12" x 9" 70p. 17 1/2" x 9 1/2" £1.15. D.S. 10" x 8 1/2" 80p. Fibre Glass 9" x 8" £1.20. 18" x 8" £2.40. D.S. 13" x 6" £1.30. 11 1/2" x 7 1/2" £1.60. Panel with 42 assorted 74 series ICs £1.50. 20 wire ended neons £1.300 small components, trans, diodes £1.50. 7 lbs assorted components £3.60. 3 1/2 lbs £2.10. List 15p. Refundable. Post 20p under £1. Insurance add 15p.

J.W.B. RADIO

2 Barnfield Crescent, Sale, Cheshire M33 1NL

ALL PRICES PER 100 5% carbon film resistors 25p; C280 capacitors 50p; IC's from £3.00; Zenner's £3.00; W/W Resistors £3.00; Diodes from £2.00; Valves £20.00; Slider controls £10.00; Micro switches £8.50; Many other bargains. Lists s.a.e. Bardwell, 212 Stubley Lane, Dronfield-Woodhouse, Sheffield S18 5PY.

RIBBON MICROPHONES with 4/8 Pole Switch 95p; Microswitches, Capacitors, Receivers and Microphone Capsules 10p each; Bakelite Telephones £2.95; Handsets 50p; Magneto Generators £1.75. P & P £1.50. CONVERSATION PIECES, 55 Swindon Road, Cheltenham. (35707).

BRAND NEW COMPONENTS BY RETURN

Electrolytic Capacitors 16V, 25V, 50V. 0.47, 1.0, 2.2, 4.7 & 10 mfd. — 5p. 22, 47—5 1/2p. (50V—6p). 100—7p. (50V—8p). 220—8p. (50V—10p). 470—11p. (50V—16p). 1000/15V—15p. 1000/25V—18p. 1000/40V—35p. Subminiature bead tantalum electrolytics. 0.1—0.22, 0.47, 1.0 @ 35V & 4.7 @ 63V—8p. 2.2/35V & 4.7/25V—9p. 10/25V & 15/16V—12p. 22/16V, 33/10V, 47/6V, 68/3V, 100/3V—14p. Subminiature Ceramic Caps. E12 Series 100V. 2% 10 pf. to 47 pf.—3p. 56 pf. to 330 pf.—4p. 10% 390 pf. to 4700 pf.—4p. Vertical Mounting Ceramic Plate Caps. 50V. E12 22 pf.—1000 pf.—E6 1500 pf. to 47000 pf.—2p. Polystyrene E12 Series 63V. Horizontal Mtg. 10 pf. to 1000 pf.—3p. 1200 pf. to 10000 pf.—4p. Miniature Polyester 250V. Var. Mtg. E6 Series. .01 to 0.1—4p. .15 & .22—5p. .33 & .47—8p. 0.68—11p. 1.0—14p. 1.5—20p. 2.2—22p. Mylar (Polyester) Film 100V. Vertical Mtg. .001, .002, .005 3 1/2p. .01, .02 4 1/2p. .04, .05—5 1/2p. Miniature resistors Highstab. 5% E12 Series. 0.125W mixed metal/carbon film 100—2MΩ—1p. 0.25W carbon film 1Ω—10MΩ (10% over 1MΩ)—1p. (E24 series in 1/2W c.film 2.00—2MΩ only). 0.25W 0.5W & 1W metal film 100—2MΩ—2p. 1N4148—2p. 1N4002—4p. 1N4006—6p. 1N4007—7p. BC107/8/9, BC147/8/9, BC157/8/9, BF184/7—9p. B pin i.c.'s. 741 Op.amp.—18p. 555 timers—24p. 20mm. fuses .15, .25, .5, 1.0, 2.0, 3.0 & 5A—3p. 20mm. fuseholders P.C. or Chassis Mtg.—5p. 400 mW. zener diodes E24 series 2V—33V—8p. Prices VAT inclusive Post 10p. (Free over £4).

THE C. R. SUPPLY CO.

127, Chesterfield Rd., Sheffield S8 0RN

TUNBRIDGE WELLS COMPONENTS, Ballard's, 108 Camden Road, Tunbridge Wells, Phone 31803. No Lists. Enquiries S.A.E.

SMALL ADS

The prepaid rate for classified advertisements is 20 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £6.60 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Practical Electronics and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Practical Electronics, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

GUARANTEED ICs 7400/10p 7447/55p 7473/24p 74121/24p 4000/15p 4011/15p 4017/55p 4027/32p 709/22p 741/22p 7805/60p NE555/25p. Many more! SAE full list CP ICs 22 Oakfield Road, Croydon, Surrey.

COMPONENTS: 32 LEDs (12R, 10G, 10Y) £3, 10 packs £25; LM741 15p, 10 for £1.40; NE555 22p, 10 for £2; LM3900 40p, 10 for £3.50; LM380 65p, 10 for £6; CPU's Z80 £10, 6800 £7; 8080 £6; Z80A £14, TMS2708 £6.50, all Micros include socket-2102-1 (450n) 801 Trans. 2N222A 13p—Resistors 4p any mix; Ceramic Disc 27pF to 8n2 1p any mix; P&P 12p, CMOS, TTL, Micros free list. Tel (0506 632337) R. Machnik, 13 Hopefield Place, Blackburn, West Lothian.

COMPONENTS 365pF airspaced variable capacitors, £2.50 inclusive; 500pF dilexon variable capacitors, £1.55 inclusive; motors, relays, valves, and more. S.A.E. for details: D. E. Wood, Chestnut Cottage, Bentley, Hampshire, GU10 5HZ.

Resistors 0.5W 5% Carbon film E12 100-10M 1p. Ceramic Caps 68pF-6800pF E6 range 1 1/2p. Polyester 0.01-0.22 2 1/2p. 0.33-0.47 6p. 0.68, 1.0 9p. 2.2 20p. Electrolytic 25V 2-160uF 4 1/2p. 220, 500 9p. 1000 16p. 6800 60p. Red LED 0.125" 9p. Gr. yell. 0.2" 12p. 0.2" clips 3p. 1N4148 21p. 1N4001 3 1/2p. 400mV Zener 2.7-33V E24 7p. 3A 70V Bridge 40p. BC10 7/8/9, BC147, 148, 158, 182 8p. 2N3055 40p. 741 18p. LM3900 42p. 555 22p. Post 15p.

PROTON ELECTRONICS

DEPT A, 1A, 2 & 4 STOPES ROAD, RADCLIFFE, MANCHESTER M26 0TN

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact COLES-HARDING & CO., 103 South Brink, Wisbech, Cambs, 0945-4188. Immediate settlement.

SERVICE SHEETS

SERVICE SHEETS for Radio, Television, Tape Recorders, Stereo etc. With free Fault-finding guide, from 50p and S.A.E. Catalogue 25p and S.A.E. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex.

BELL'S TELEVISION SERVICES for Service Sheets on Radio, TV, etc £1.00 plus S.A.E. Colour TV Service Manuals on request. S.A.E. with enquiries to B.T.S. 190 Kings Road, Harrogate, N. Yorkshire, Tel: (0423) 55885.

BOOKS AND PUBLICATIONS

ALL SERVICE SHEETS and Manuals supplied - enquiries welcome - S.A.E. Please. Repair any T.V. easily, full individual instructions, any set (Circuit £1 extra) for £5. Send details of set to: T.I.S. (PE) 76 Church Street, Larkhall, Lanarks ML9 1HE.

RECORD ACCESSORIES

STYL Cartridges for MUSIC CENTRES, &c. FREE List No.29 for S.A.E. includes Leads, Mikes, Phones &c. FELSTEAD ELECTRONICS, (PE), Longley Lane, Gatley, Cheshire. Ches. SK8 4EF.

SITUATIONS VACANT

TEST TECHNICIAN

We are a small expanding electronics company looking for a self-motivated person who can utilise their initiative in a variety of interesting work. Formal qualifications are desirable, however candidates with a basic knowledge of electronics will be considered. The position offers a good salary and all the usual benefits of a small company.

Contact M. C. BIGGS on Erith 41933

CONDITIONS OF ACCEPTANCE OF CLASSIFIED ADVERTISEMENTS

1. Advertisements are accepted subject to the conditions appearing on our current advertisement rate card and on the express understanding that the Advertiser warrants that the advertisement does not contravene any Act of Parliament nor is it an infringement of the British Code of Advertising Practice.
2. The publishers reserve the right to refuse or withdraw any advertisement.
3. Although every care is taken, the Publishers shall not be liable for clerical or printers' errors or their consequences.

EDUCATIONAL

COLOUR TV SERVICING

Learn the techniques of servicing Colour TV sets through new homestudy course approved by leading manufacturers. Covers principles, practice and alignment with numerous illustrations and diagrams. Other courses for radio and audio servicing. Full details from:

ICS SCHOOL OF ELECTRONICS

Dept. H272 Intertext House, London SW8 4UJ

Tel. 01-622 9911 (all hours)

State if under 18

TECHNICAL TRAINING

Get the training you need to move up into a higher paid job. Take the first step now—write or phone ICS for details of ICS specialist homestudy courses on Radio, TV, Audio Eng. and Servicing, Electronics, Computers: also self-build radio kits. Full details from:

ICS SCHOOL OF ELECTRONICS

Dept. H272 Intertext House, London SW8 4UJ

Tel. 01-622 9911 (all hours)

State if under 18

CITY & GUILDS EXAMS

Study for success with ICS. An ICS homestudy course will ensure that you pass your C. & G. exams. Special courses for: Telecoms. Technicians, Electrical Installations, Radio, TV & Electronics Technicians, Radio Amateurs. Full details from:

ICS SCHOOL OF ELECTRONICS

Dept. H272 Intertext House, London SW8 4UJ

Tel. 01-622 9911 (all hours)

State if under 18

WHETHER SEA-GOING OR SHORE-BASED, an exciting life awaits you as a Marine Radio Officer. Full details from The Principal, Barking College of Technology, Dagenham Road, Romford. RM7 0XU. (Telephone Romford 66841).

OVERSEAS APPOINTMENTS

PRODUCTION TECHNICIAN

required in South Africa.

Excellent opportunity for skilled wireman with test experience.

The position is permanent and offers good salary, good working conditions, warm climate, subsidised house mortgage.

Write giving details of age, experience etc. to:

Klerkscale (Pty) Ltd,
P.O. Box 944, Klerksdorp 2570,
South Africa.

FOR SALE

PE MAGS May 69 to Mar 75 (6 missing) £30. ETI Top projects 1+2, 6. £2.75. Tel: Fisher 63930 (Evenings).

ELEKTOR SYNTHESISER IV. C.O. bargain £260. Digital sequencer parts £50. P.E. Synthesiser Keyboard Circuits, various amps. Needs attention. Magazines, lots of spares, offers. Birmingham. 707 4543.

COLOUR MODULATOR

Kit **£6-95** FOR ALL TV GRAPHICS!
 ● Red, Green & Blue inputs ● Switchable background colours ● FREE interface details for tank battles — lifelike effects

WILLIAM STUART SYSTEMS
 137, Billericay Road Herongate Brentwood Essex CM13 3SD
 Tel: 0277 810244 Barclay Card Access Accepted

NEW BACK ISSUES of "PRACTICAL ELECTRONICS" available 70p each Post Free. Open P.O./Cheque returned if not in stock — Bell's Television Services, 190 Kings Road, Harrogate, N. Yorks. Tel: (0423) 55885.

FOR SALE £65. PE Joanna i-built all major parts present including body and keyboard, plus original magazine articles. 33 Norman Stead Road, Tilehurst, Reading. Tel: Reading 23016.

ELECTRONIC ORGAN CONSTRUCTORS. Organ Cases and consoles. Units from Table Top Case to Three Manual Console with full Pedal Board. Write for details: Hi-Fi Enthusiast. Stackable Hi-Fi. Cabinets to hold Amp-Tuner, Player and Tape, plus storage for records and tapes. Box No. 79.

MK14 — Full working order. P.S.U. and extras. P.E. P.W. 1968 to 75 Unbound. Ring Coventry 468346.

MK14 microcomputer, built with cassette interface, extra RAM. O.J. 069, Ripley (Derbyshire) 873244.

ADVANCE QS25B Oscilloscope 5MHz, dual trace with manual, and accessories. Little used. £50 o.n.o. Tel: Hemel Hempstead 48784.

LADDERS

LADDERS. Varnished 25ft. extd. £35.70. Carr. £2.80 Leaflet. Callers welcome. Open Sat. Ladder Centre (PEE5), Halesfield (1) Telford 586644.

MISCELLANEOUS

PRACTICAL ELECTRONICS P.C.B.'s

in glass fibre tinned and drilled

Dec. 77 Car Burglar Alarm 1412-1 68p.
 May 78 Moving Light Display £2.75.
 Aug 78 Digital Thermometer, two boards £1.45.
 Oct. 78 High Performance Power Supply £2.18.
 Oct. 78 Analogue Computer:
 Overlord £3.31. Relay £2.41. Main £6.85.
 Dec. 78 RC Motor Control 67p. RC Fall Safe 39p.
 Guitler Sound, Main board £2.95.
 Jan. 79 Guitar Sound, clock £1.87.
 Low pass filter £1.95.
 Feb. 79 Guitar sound PSU £1.25. Pulse Generator £1.39.
 Mar. 79 Headlight Warning £1.12.
 April 79 Phaser 98p.
 For full list and current boards please send S.A.E. P.C.B.'s also produced from customer's own master — please send for quote.

Postage — On orders less than £10.00 please add 25p. postage. C.W.O. please.

PROTO DESIGN

14 Downham Road, Ramsden Heath, Billericay, Essex CM11 1PU

THE SCIENTIFIC WIRE COMPANY

PO Box 30, London E.4
 Reg. Office 22 Coningsby Gdns

ENAMELLED COPPER WIRE

SWG	1 lb	8 oz	4 oz	2 oz
10 to 19	2.85	1.45	.75	.60
20 to 29	2.85	1.65	.90	.70
30 to 34	3.05	1.75	1.00	.75
35 to 40	3.40	1.95	1.15	.84
41 to 43	4.55	2.55	1.95	1.30
44 to 46	5.05	3.05	2.15	1.70
47	8.00	6.00	3.00	1.80
48	15.00	9.00	6.00	3.30

SILVER PLATED COPPER WIRE

	4.50	2.25	1.44	.90
14 & 16	4.50	2.25	1.44	.90
20 & 22	5.00	2.85	1.74	1.06
24 & 26	5.70	3.31	2.00	1.22
28 & 30	6.67	3.86	2.36	1.44

Prices include P & P and VAT
 SAE brings list of copper & resistance Wires
 Dealer Enquiries Invited.

TRANSISTORISED IGNITION KIT

£4.85 incl. carr & VAT
 Complete pack of parts with p.c.b. to build our transistorised ignition system based on Dornington Power Transistors specially developed for auto ignition.

Send S.A.E. for FREE CIRCUIT diagram.

All components with p.c.b. (less case) £4.85.

SOLEC PRODUCTS,

68 Dale Street, Manchester, M1 2HS.

TIRRO's new mail order price list of electronic components now available on receipt of SAE. TIRRO ELECTRONICS, Grenfell Place, Maidenhead, Berks.



Readily available Hardware and Accessories for Home Constructors, Dev. Engineers, Modelmakers. Selected range of quality components. Drawing materials for p.c. boards. Reliable resist coated epoxy glass laminate, no unusual chemicals. Printed circuit boards, top quality to personal designs, prompt service. Photography for p.c.b. Solid tungsten carbide drills. All immediately available. Catalogue 15p stamps please to:

RAMAR CONSTRUCTOR SERVICES,
 Masons Rd. Stratford on Avon
 Warwks. CV37, 9NF 0789-4879

I.C. EXPERIMENTAL/EDUCATIONAL KITS

This popular series of Kits on Digital Logic techniques has now been further improved to include additional components, resulting in greater constructional flexibility and educational capacity. Each Kit contains selected I.C.'s, Holders, Veroboard, L.E.D.'s and Instructions. Available at £5.00 each (inc. p. & p.).

Kit One — Gates Kit Two — Flip-Flops
 Kit Three — Shift Registers Kit Four — Counters
 Kit Five — Displays

S.A.E. for further details to:

AUTOMATED HOMES

69 High Street, Ryton, Coventry CV8 3FJ (mail order)

GUITAR/PA/MUSIC AMPLIFIER

100 watt with superb treble/bass overdrive, 12 months guarantee. Unbeatable at £42; 60 watt £37; 200 watt £58; 100 watt twin channel sep. treble/bass per channel £55; 60 watt £48; 200 watt £72; 100 watt four channel sep. treble/bass per channel £75; 200 watt £92; slaves 100 watt £32; 200 watt £49; fuzz boxes, great sound, £8.50; bass fuzz £9.50; overdriver, fuzz with treble and bass boosters £14; 100 watt combo superb sound overdrive, sturdy construction, castors, unbeatable, £89; twin channel £99; bass combo £99; speakers 16 in. 100 watt £35; 12 in. 100 watt £22.50; 60 watt £14.50.

Send cheque or P.O. to:

WILLIAMSON AMPLIFICATION

62 Thorncliffe Avenue, Dukinfield, Cheshire
 Tel: 061-344 5007 or 061-308 2064

CLEARING LABORATORY. Scopes, recorders, testmeters, bridges, audio, R.F. generators, turntables, tapeheads, stabilised P.S.U.s, sweep generators, test equipment, etc. Lower Beeding 236.

RECHARGEABLE BATTERIES

TRADE ENQUIRIES WELCOME

FULL RANGE AVAILABLE. SAE FOR LISTS. £1.25 for Booklet "Nickel Cadmium Power" plus Catalogue. Write or call: Sandwell Plant Ltd., Union Drive, BOLDMERE, SUTTON COLDFIELD, WEST MIDLANDS. 021-354 9764; or see them at TLC, 32 Craven Street, Charing Cross, London WC2.

MICROCOMPUTER HIRE

ALSO OTHER EQUIPMENT
**NESCOM, HORIZON, APPLE II
 PET, CROMEMCO,
 + OTHERS MAY BE AVAILABLE
 ON REQUEST.**

**LESS THAN £12 A WEEK FOR
 SOME DELIVERY +
 COLLECTION FREE IN
 GREATER LONDON, SAME
 DAY DELIVERY WHEN
 AVAILABLE. ALL EQUIPMENT
 MAY BE BOUGHT.**

Telephone: 01-368 9002.

PROMGLOW LTD.,
 30 CITY ROAD, E.C.1.

NICKEL CADMIUM BATTERIES

Rechargeable and suitable for fast charge: HP7 (AA) £1-13, SUB C £1-47, HP 11 (C) £2-15, HP 2 (D) £3-27, PP3 £4-09, PP3 not suitable for fast charge, PP3 charger £5-81. All above Nickel Cadmium batteries are guaranteed EVER READY full spec, and are supplied complete with solder tags (except PP3). Just in stock — New rechargeable sealed lead acid maintenance free batteries suitable for burglar alarms etc. 1.2 amp hr 6v. £6-40 2-6 amp hr, 6v. £5-65. Quantity prices available on request. Date and charging circuits free on request with orders over £10 otherwise 30p post and handling (specify battery type), all prices include VAT. Please add 10% P & P on orders under £10. 5% over £10.

Cheques, postal orders, mail order to **SOLID STATE SECURITY DEPT PE, 10, Bradshaw Lane, Parbold, Wigan, Lancs. 02575-4726.**

SUPERB INSTRUMENT CASES BY BAZELLI, manufactured from P.V.C. faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range. Competitive prices start at a low 90p, chassis punching facilities at very competitive prices, 400 models to choose from, free literature (stamp would be appreciated). BAZELLI, Dept: No. 23, St Wilfred's, Foundry Lane, Halton, Lancaster. LA2 6LT.

NO SIG. GEN.?

10Hz-200Hz, logic and variable sine or square wave outputs, linear frequency scale, £10.80.

TIME? MSF 60KHz Receiver, built-in antenna, data out, £13.70. Sequential year, month, date, day, hours, minutes, seconds display parts (no case or pcb) for receiver, £10.70.

RADIO 4 GONE? 200KHz to Medium Wave Converter, inductive and coax outputs, £9.70.

Please write for overseas prices. Each easy-assembly kit includes all parts, printed circuit, case, instructions, postage etc, money back assurance so SEND off NOW.

CAMBRIDGE KITS

45 (FT) Old School Lane, Milton, Cambridge.

CENTURION ALARMS & ELECTRONIC SALES

DON'T BUY IN KITS — BUY CHEAPER IN BITS

Burglar alarm equipment at unbeatable prices. Just look!

Magnetic Reed Contacts, flush easy fitting.....£0.85
 Pressure Mat (Stair Size).....£1.30
 Pressure Mat (Large).....£1.90
 Bell Covers, best available. Don't confuse with cheaper decoy covers. Drilled & Tapped P.V.C. coated metal covers. Fully sign written. Only.....£9.95
 Two-Tone Police Sirens, weather-proof horns.....£12.95
 Control Panels Battery/ mains operation.....£29.95
 Ultra-Sonic Motion Detectors, adjustable range of approximately 30ft. Only.....£45.00
 Send S.A.E. for Full Lists.

NEW CHESS COMPUTERS

Chess Champlon 6 level.....£89.50
 Boris, the Talking Chess Computer.....£195.00

All Prices Inc. VAT and p&p.

Send C.W.O. to **CENTURION**
 265 Wakefield Road, Huddersfield,
 West Yorks. Tel: 663667

VIDEO MUSIC



Videograph II links to the aerial socket of your tv and provides a full colour **GIANT** oscilloscope display. A must for hi-fi, home entertainment, discos, organs etc.

New — signal invert control, integral square wave generator. Plus — full details for testing your audio system for transient distortion, crosstalk etc.

Complete **£19-95** Luxury cabinet and Kit only controls. £9-95

READY BUILT VIDEOGRAPH £39-95 + £1. Post & Packing.
WILLIAM STUART SYSTEMS Ltd
 Dover House, Billericay Road,
 Herongate, Brentwood,
 Essex CM13 3SD.
 Telephone: Brentwood (0277) 810244

CHORDGATE Ltd. SWINDON

Printed Circuit Boards. Add 27p post & packing for 1 to 3 boards. Larger quantities post & packing inclusive

Voltage Tripler P.C.B. contains 40.1 MFD 1000V, 2 pre-sets, 1 bridge rect., 4 IN4007, 9 resistors. 65p.

P.C.B. contains 2 TIP31 (or equiv.), MJE 340 and over 70 other resistors, diodes, zeners, transistors, bridge rect., and capacitors. 50p.

P.C.B. contains 2 x 741, 2N4921 and over 40 other components and multitrn 20k pot. 60p.

P.C.B. contains 2 IP 10W Wafer Switches, 2 x 7490 I/C, 2 x 74141 I/C, various Logic I/Cs, IN4148 and over 50 components. 60p.

P.C.B. with GEC, G424 Triac control IC, 2 SGS transistors, three 9 watt WW resistors and 12 other components. 70p.

P.C.B. with 8 x BC107, 8 x BCY70, 4 pre-set pot., and over 70 other components. 75p.

Parcel of 1 each of above, 6 P.C.B.'s. £3.30.

Post and packing inclusive.

Audio Amplifier Boards containing 2 x BFY50, IBFX29 and output pair of 2N5293 output transistors rated at 36 watts when heatsink mounted £1.75 or 2 for £3.00. Post and packing inclusive.

(Dept C.) 194 A DROVE ROAD, SWINDON, WILTS.

ALL OUR PRICES INCLUDE V.A.T.

FOR YOUR GUIDANCE VALUE ADDED TAX

Unless otherwise shown, all prices in advertisements are inclusive of VAT. Where prices are exclusive, readers should ensure that they have added the correct amount of VAT before ordering.

Export orders are not subject to the addition of Value Added Tax.

WORLD RADIO TV HANDBOOK

1979

Price: £9.16

1979 RADIO AMATEUR'S HANDBOOK
by ARRL Price: £7.86

HOW TO BUILD A COMPUTER CONTROLLED
ROBOT by T. Loofbourrow Price: £5.20

HOW TO REPAIR VIDEO GAMES
by R. Goodman Price: £6.35

TESTING METHODS & RELIABILITY
ELECTRONICS by A. Simpson Price: £4.50

CLOSED CIRCUIT T.V. FOR TECHNICIANS
VOL I by K. J. Bohlman Price: £5.00

AMATEUR RADIO TECHNIQUES
by P. Hawker Price: £3.70

SOME COMMON BASIC PROGRAMS
by L. Poole Price: £6.00

8080 8085 SOFTWARE DESIGN
by C. A. Titus Price: £7.50

MICROCOMPUTER ANALOG CONVERTER
SOFTWARE & HARDWARE INTERFACING
by C. A. Titus Price: £7.50

ALL PRICES INCLUDE POSTAGE

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST
of British and American Technical Books

19-21 PRAED STREET
LONDON W2 1NP

Phone 01-723 4185

Closed Saturday 1 p.m.

MICROPROCESSOR COURSE ANNOUNCEMENT

A two-day intensive course on the *Design of Microprocessor Systems* will be given at the Institution of Electrical Engineers, Savoy Place, London, by D. Zissos* on July 5 and 6, 1979. Full details will appear in the next issue of the *Practical Electronics*.

(*Author of System Design with Microprocessors, Academic Press, 1978).

INDEX TO ADVERTISERS

A.E. Supplies.....	86	Computer Components		I.C.S. Intertext.....	2, 84	Sandwell Plant Ltd.....	85
Ace Mailtronix.....	74	(Teleplay).....	cover li	I.L.P. Electronics.....	79	Saxon Entertainments.....	64
Adam Hall (P.E. Supplies).....	15, 85	Crescent Radio.....	16	Jayen Developments.....	78	Science of Cambridge.....	71
Aitken Bros.....	15	Crimson Elektrik.....	72	J.W.B. Radio.....	84	Scientific Wire Co.....	85
Alcon Instruments Ltd.....	12	Crofton Electronics.....	4	Kay & Co Ltd.....	12	Sentinel Supply.....	72
Astra-Pak.....	72	C.R. Supply Co.....	84	Maclin-Zand.....	5	Service Trading.....	7
Automated Homes.....	85	Davian Electronics.....	12	Maplin Electronic Supplies.....	cover iv	Solec Products.....	85
Barrie Electronics.....	80	E.D.A.....	78	Marshall, A. (London) Ltd.....	13	Solid State Security.....	85
Biggs, M. C.....	84	Electrovalue.....	78	Metac.....	77	Sparks Developments.....	82
Bi-Pak.....	10, 11	Fladar.....	6	Mill Hill Supplies.....	80	Special Products.....	80
Birkett, J.....	15	Flairlines Supplies.....	86	Milward, G. F.....	4	Squire, Roger.....	2
Boffin Projects.....	86	Furama Electronics.....	82	Modern Book Co. Ltd.....	87	Stevensons Electronic Components.....	75
Boss Industrial Mouldings.....	83	Future Electronics.....	16	Monolith.....	76	Swanley Electronics.....	80
British National Radio & Electronics School.....	63	Gould Instruments.....	6	P.A.W.K. & I. Yates.....	84	T.K. Electronics.....	2
Cambridge Kits.....	85	Greenweld Electronics.....	9	P.K.G. Electronics.....	86	T.U.A.C.....	21
Cambridge Learning.....	81	H.L. Audio.....	14	Phonosonics.....	8, 9	Technomatic.....	88
Centurion Alarms.....	85	Harversons.....	22	Progressive Radio.....	74	Timetron.....	14
Chordgate.....	87	Heathkit Ltd.....	22	Proto Design.....	85	Videotime Products.....	74
Chromasonic.....	82	Hiykon Ltd.....	86	Radio Component Specialists.....	76	Watford Electronics.....	3
Chromatronics.....	74	Home Radio.....	76	Radio Exchange.....	4	William Stuart Systems Ltd.....	85
Clef Products.....	4			Ramar Constructor Service.....	85	Williamson Amplification.....	85
Codespeed.....	76			R.S.T. Valve Mail Order.....	16	Wilmslow Audio.....	6
Colour Print Express.....	cover iii			Radio & T.V. Components.....	73		

TTL by TEXAS	74117 90p	4000 SERIES	93 SERIES	160p	VEROBOARD	TRANSISTORS	25p	BFX86/7 30p	TIP35A 225p	*2N3820 50p	DIODES	*ZENEERS
7400 13p	74181 160p	4001 15p	9302 175p	160p	0.15	AC126 25p	BFX88 30p	TIP35C 290p	*2N3820 50p	*BY127 12p	*2.7V 33V	
7401 14p	74180 93p	4002 17p	9308 316p	2x 3x 41p 33p	(copper clad)	AC127/20 25p	BFW10 90p	TIP35E 340p	2N3823 70p	*0A47 9p	400mW	9p
7402 14p	74181 200p	4006 95p	9310 275p	2x 5 49p 45p		AC176 25p	BFY50 22p	TIP35G 290p	2N3866 90p	*0A81 19p	1W	5p
7403 14p	74182 90p	4007 18p	9311 160p	3x 3x 49p 45p		AD149 70p	BFY51/2 22p	TIP41C 78p	*2N3903/4 18p	*0A85 15p		
7404 17p	74184A 150p	4008 80p	9312 160p	2x 1x 17 152p 121p		AD161/2 45p	BFY56 30p	TIP42C 82p	*2N3905/6 20p	*0A91 9p		
7405 90p	74185 150p	4009 40p	9316 225p	4x 1x 17 252p —		BC109 11p	BFY90 90p	TIP42E 82p	*2N4058/9 12p	*0A95 9p		
7406 32p	74186 100p	4010 50p	9322 150p	Part of 35 pins 30p		BC117 20p	BFY90 90p	TIP42E 82p	*2N4060 12p	*0A200 9p		
7407 32p	74191 100p	4011 17p	9322 150p	Pin. face cutter 85p		BC120 11p	BFY90 90p	TIP42E 82p	*2N4061/2 18p	*0A202 10p		
7408 19p	74192 100p	4012 18p	9334 225p	Spot face cutter 85p		BC121 20p	BFY90 90p	TIP42E 82p	*2N4123/4 22p	*IN914 4p		
7409 19p	74193 100p	4013 50p	9368 200p	Pin insertion		BC124 19p	BU104 225p	TIP42E 82p	*2N4125/6 22p	*IN916 4p		
7410 15p	74194 100p	4014 84p	9370 200p	tool		BC157/8 10p	BU108 225p	TIP42E 82p	*2N4289 20p	*IN916 4p		
7411 24p	74195 95p	4015 84p	9374 200p	VERO WIRING		BC159 11p	BU108 225p	TIP42E 82p	*2N4290 20p	*IN916 4p		
7412 30p	74197 80p	4017 80p		Plus spare 325p		BC189C 12p	BU205 200p	TIP42E 82p	*2N4291 20p	*IN916 4p		
7413 30p	74198 80p	4018 89p		Spare spool		BC172 12p	BU205 200p	TIP42E 82p	*2N4292 20p	*IN916 4p		
7414 60p	74199 150p	4019 45p		(wire) 80p		BC177/8 17p	BU208 200p	TIP42E 82p	*2N4293 20p	*IN916 4p		
7415 27p	74200 1000p	4020 100p		Combes 7p each		BC179 30p	BU208 200p	TIP42E 82p	*2N4294 20p	*IN916 4p		
7416 27p	74221 160p	4021 110p				BC182/3 13p	BU208 200p	TIP42E 82p	*2N4295 20p	*IN916 4p		
7417 27p	74221 160p	4022 100p				BC184 11p	BU208 200p	TIP42E 82p	*2N4296 20p	*IN916 4p		
7420 47p	74221 160p	4023 22p				BC184 11p	BU208 200p	TIP42E 82p	*2N4297 20p	*IN916 4p		
7421 47p	74221 160p	4024 50p				BC184 11p	BU208 200p	TIP42E 82p	*2N4298 20p	*IN916 4p		
7422 22p	74229 250p	4025 20p				BC184 11p	BU208 200p	TIP42E 82p	*2N4299 20p	*IN916 4p		
7423 34p	74265 90p	4026 130p				BC184 11p	BU208 200p	TIP42E 82p	*2N4300 20p	*IN916 4p		
7424 34p	74278 90p	4027 50p				BC184 11p	BU208 200p	TIP42E 82p	*2N4301 20p	*IN916 4p		
7425 30p	74278 90p	4028 84p				BC184 11p	BU208 200p	TIP42E 82p	*2N4302 20p	*IN916 4p		
7426 40p	74278 90p	4029 100p				BC184 11p	BU208 200p	TIP42E 82p	*2N4303 20p	*IN916 4p		
7427 34p	74283 190p	4030 55p				BC184 11p	BU208 200p	TIP42E 82p	*2N4304 20p	*IN916 4p		
7428 36p	74284 400p	4031 200p				BC184 11p	BU208 200p	TIP42E 82p	*2N4305 20p	*IN916 4p		
7429 30p	74289 90p	4032 22p				BC184 11p	BU208 200p	TIP42E 82p	*2N4306 20p	*IN916 4p		
7430 17p	74290 150p	4033 180p				BC184 11p	BU208 200p	TIP42E 82p	*2N4307 20p	*IN916 4p		
7431 30p	74291 150p	4034 200p				BC184 11p	BU208 200p	TIP42E 82p	*2N4308 20p	*IN916 4p		
7432 30p	74292 150p	4035 110p				BC184 11p	BU208 200p	TIP42E 82p	*2N4309 20p	*IN916 4p		
7433 40p	74293 150p	4036 110p				BC184 11p	BU208 200p	TIP42E 82p	*2N4310 20p	*IN916 4p		
7434 35p	74294 200p	4037 75p				BC184 11p	BU208 200p	TIP42E 82p	*2N4311 20p	*IN916 4p		
7435 35p	74298 200p	4038 84p				BC184 11p	BU208 200p	TIP42E 82p	*2N4312 20p	*IN916 4p		
7436 35p	74356 150p	4039 80p				BC184 11p	BU208 200p	TIP42E 82p	*2N4313 20p	*IN916 4p		
7437 35p	74356 150p	4040 80p				BC184 11p	BU208 200p	TIP42E 82p	*2N4314 20p	*IN916 4p		
7438 35p	74356 150p	4041 80p				BC184 11p	BU208 200p	TIP42E 82p	*2N4315 20p	*IN916 4p		
7439 35p	74356 150p	4042 80p				BC184 11p	BU208 200p	TIP42E 82p	*2N4316 20p	*IN916 4p		
7440 17p	74356 150p	4043 90p				BC184 11p	BU208 200p	TIP42E 82p	*2N4317 20p	*IN916 4p		
7441 17p	74356 150p	4044 90p				BC184 11p	BU208 200p	TIP42E 82p	*2N4318 20p	*IN916 4p		
7442 17p	74356 150p	4045 110p				BC184 11p	BU208 200p	TIP42E 82p	*2N4319 20p	*IN916 4p		
7443 112p	74368 150p	4046 110p				BC184 11p	BU208 200p	TIP42E 82p	*2N4320 20p	*IN916 4p		
7444 112p	74390 200p	4047 110p				BC184 11p	BU208 200p	TIP42E 82p	*2N4321 20p	*IN916 4p		
7445 100p	74393 200p	4048 55p				BC184 11p	BU208 200p	TIP42E 82p	*2N4322 20p	*IN916 4p		
7446 93p	74490 225p	4049 55p				BC184 11p	BU208 200p	TIP42E 82p	*2N4323 20p	*IN916 4p		
7447 60p	74490 225p	4050 49p				BC184 11p	BU208 200p	TIP42E 82p	*2N4324 20p	*IN916 4p		
7448 60p	74490 225p	4051 80p				BC184 11p	BU208 200p	TIP42E 82p	*2N4325 20p	*IN916 4p		
7449 17p	74500 14p	4052 80p				BC184 11p	BU208 200p	TIP42E 82p	*2N4326 20p	*IN916 4p		
7450 17p	74504 18p	4053 80p				BC184 11p	BU208 200p	TIP42E 82p	*2N4327 20p	*IN916 4p		
7451 17p	74504 18p	4054 150p				BC184 11p	BU208 200p	TIP42E 82p	*2N4328 20p	*IN916 4p		
7452 17p	74508 25p	4055 125p				BC184 11p	BU208 200p	TIP42E 82p	*2N4329 20p	*IN916 4p		
7453 17p	74510 20p	4056 135p				BC184 11p	BU208 200p	TIP42E 82p	*2N4330 20p	*IN916 4p		
7454 17p	74510 20p	4057 135p				BC184 11p	BU208 200p	TIP42E 82p	*2N4331 20p	*IN916 4p		
7455 17p	74510 20p	4058 115p				BC184 11p	BU208 200p	TIP42E 82p	*2N4332 20p	*IN916 4p		
7456 17p	74510 20p	4059 115p				BC184 11p	BU208 200p	TIP42E 82p	*2N4333 20p	*IN916 4p		
7457 36p	74522 28p	4060 55p				BC184 11p	BU208 200p	TIP42E 82p	*2N4334 20p	*IN916 4p		
7458 36p	74522 28p	4061 55p				BC184 11p	BU208 200p	TIP42E 82p	*2N4335 20p	*IN916 4p		
7459 36p	74522 28p	4062 55p				BC184 11p	BU208 200p	TIP42E 82p	*2N4336 20p	*IN916 4p		
7460 50p	74527 38p	4063 120p				BC184 11p	BU208 200p	TIP42E 82p	*2N4337 20p	*IN916 4p		
7461 100p	74530 20p	4064 22p				BC184 11p	BU208 200p	TIP42E 82p	*2N4338 20p	*IN916 4p		
7462 84p	74532 27p	4065 20p				BC184 11p	BU208 200p	TIP42E 82p	*2N4339 20p	*IN916 4p		
7463 100p	74547 90p	4066 22p				BC184 11p	BU208 200p	TIP42E 82p	*2N4340 20p	*IN916 4p		
7464 100p	74547 90p	4067 22p				BC184 11p	BU208 200p	TIP42E 82p	*2N4341 20p	*IN916 4p		
7465 110p	74555 30p	4068 22p				BC184 11p	BU208 200p	TIP42E 82p	*2N4342 20p	*IN916 4p		
7466 34p	74573 50p	4069 22p				BC184 11p	BU208 200p	TIP42E 82p	*2N4343 20p	*IN916 4p		
7467 34p	74574 50p	4070 30p				BC184 11p	BU208 200p	TIP42E 82p	*2N4344 20p	*IN916 4p		
7468 210p	74574 50p	4071 22p				BC184 11p	BU208 200p	TIP42E 82p	*2N4345 20p	*IN916 4p		
7469 33p	74575 45p	4072 22p				BC184 11p	BU208 200p	TIP42E 82p	*2N4346 20p	*IN916 4p		
7470 80p	74585 110p	4073 22p				BC184 11p	BU208 200p	TIP42E 82p	*2N4347 20p	*IN916 4p		
7471 80p	74585 110p	4074 107p				BC184 11p	BU208 200p	TIP42E 82p	*2N4348 20p	*IN916 4p		
7472 48p	74586 100p	4075 22p				BC184 11p	BU208 200p	TIP42E 82p	*2N4349 20p	*IN916 4p		
7473 48p	74586 100p	4076 107p				BC184 11p	BU208 200p	TIP42E 82p	*2N4350 20p	*IN916 4p		
7474 84p	74590 60p	4077 22p				BC184 11p	BU208 200p	TIP42E 82p	*2N4351 20p	*IN916 4p		
7475 84p	74590 60p	4078 107p				BC184 11p	BU208 200p	TIP42E 82p	*2N4352 20p	*IN916 4p		
7476 65p	745107 45p	4079 107p				BC184 11p	BU208 200p	TIP42E 82p	*2N4353 20p	*IN916 4p		
7477 130p	745112 100p	4080 22p				BC184 11p	BU208 200p	TIP42E 82p	*2N4354 20p	*IN916 4p		
7478 130p	745112 100p	4081 22p				BC184 11p	BU208 200p	TIP42E 82p	*2N4355 20p	*IN916 4p		
7479 130p	745112 100p	4082 22p				BC184 11p	BU208 200p	TIP42E 82p	*2N4356 20p	*IN916 4p		
7480 130p	745112 100p	4083 22p				BC184 11p	BU208 200p	TIP42E 82p	*2N4357 20p	*IN916 4p		
7481 130p	745112 100p	4084 22p				BC184 11p	BU208 200p	TIP42E 82p	*2N4358 20p	*IN916 4p		
7482												

Why buy colour films?

When you get a Kodak colour film

FREE

for every one you send in for processing by the Practical Electronics Colour Print Service!



Reliability at less cost

Photography can cost you a lot less these days. If you know how to go about it. Like the hundreds of thousands of magazine readers who are delighted with this reliable Colour Print Service – and the replacement films that come FREE to every customer! So why don't you give it a try? Here's what you do. Send us any make of colour print film inside the envelope enclosed in this issue. Or fill in the coupon below and send it with your film in a strong envelope to: The Practical Electronics Colour Print Service, Freepost, Teddington, Middlesex, TW11 8BR. No stamp is required.

Send no money

But don't send any money until you see the colour of your prints. We're so confident in the reliability of the service and the quality of our prints, every one of which is checked by professionals at our laboratories.

Luxury colour prints

You'll be amazed at the crisp, sharp, high-definition sheen finish of the prints we supply . . . borderless to give you maximum picture area. And coming with the prints will be your FREE Kodak colour film, worth around £1, the same size as the one you sent us for processing.

Unbeatable value

What about prices? Ours are certainly much less than those you would pay in most shops – quite apart from the free film you get every time we develop and print for you.

Our Colour Print Service charges you only 15p for each print, plus 85p towards developing, postage and packing. The minimum charge is 85p inc. VAT (that is, if no prints can be made). The offer is limited to the UK, Eire, CI and BFPO.

More benefits to you

You benefit in two additional ways. Firstly, you enjoy a personal service with every care taken over each individual order. And secondly, you pay only for what you get – with no credit vouchers as with many other companies. An invoice comes with your prints so it's a straight business transaction.

Use this label if you haven't got an envelope, or pass it to a friend who might like to take advantage of our offer. It is used to send your prints and free film.

(Offer Exc. Minolta & Sub-miniature. Roll Film 10p surcharge 400 ASA 20p surcharge).

**From: Practical Electronics Colour Print Service,
Freepost, Teddington, Middlesex TW11 8BR**

Mr/Ms _____

Address _____

Postcode _____



Speakers from 1 1/2 inch to 15 inch; megaphone, PA horns, crossovers etc. They're all in our catalogue. Send the coupon now!



A genuine 150W per channel stereo disco to build yourself. Full specification in our catalogue.



Our catalogue even includes some popular car accessories at marvellous prices.



Our catalogue describes a wide range of plugs and sockets, all at marvellous prices. See cat. pages 14 to 129 for details.



61-note touch-sensitive piano to build yourself. Full specification in our catalogue.



A very high quality 40W per channel stereo amplifier with a superb specification and lots of extras. Full construction details in our catalogue.



A digitally controlled stereo synthesiser the 5600S with more facilities than almost anything up to £3,000. Build it yourself for less than £700. Full specification in our catalogue.



A hi-fi stereo tuner with medium and long wave, FM stereo and UHF TV sound! Full construction details in our catalogue.



These are just some of the metal cases we stock. There are dozens of plastic ones to choose from as well. See pages 52 to 57 of our catalogue.

MAPLIN

ELECTRONIC SUPPLIES LTD

All mail to:-
P.O. Box 3, Rayleigh, Essex SS6 8LR.
Telephone: Southend (0702) 554155.

Shop: 284 London Road,
Westcliff-on-Sea, Essex.
(Closed on Monday).
Telephone: Southend (0702) 554155.



Multimeters, analogue and digital, frequency counter, oscilloscopes, and lots, lots more at excellent prices. See cat. pages 106 and 183 to 188 for details.



A 10-channel stereo graphic equaliser with a quality specification at an unbeatable price when you build it yourself. Full specification in our catalogue.



A massive new catalogue from Maplin that's even bigger and better than before. If you ever buy electronic components, this is the one catalogue you must not be without. Over 280 pages - some in full colour - it's a comprehensive guide to electronic components with hundreds of photographs and illustrations and page after page of invaluable data.

Our bi-monthly newsletter contains guaranteed prices, special offers and all the latest news from Maplin.



A superb range of microphones and accessories at really low prices. Take a look in our catalogue - send the coupon now!

Post this coupon now for your copy of our 1979-80 catalogue price 75p.

Please send me a copy of your 280 page catalogue as soon as it is published (8th Jan. 1979). I enclose 75p but understand that if I am not completely satisfied I may return the catalogue to you within 14 days and have my 75p refunded immediately. If you live outside U.K. send £1 or ten International Reply Coupons.

NAME _____

ADDRESS _____