

PRACTICAL WIRELESS

NOVEMBER
1970

316
(17½ new
2 pence)

PW 25/25 STEREO AMPLIFIER



**AUDIO * FAIR
PREVIEW**

**RESISTANCE
CAPACITANCE
BRIDGE**

**SHORT-WAVE
TRANSISTOR
PREAMP**

ADCOLA Soldering Instruments add to your efficiency

ADCOLA 64

for Factory Bench Line Assembly

A precision instrument—supplied with standard 3/16" (4.75 mm) diameter, detachable copper chisel-face bit*.

Standard temp. 360°C at 23 watts.

Special temps. from 250°C—410°C.

*Additional Stock Bits (illustrated) available

COPPER

B 38 $\frac{1}{4}$ " — 3.2 mm CHISEL FACE

B 14 $\frac{3}{16}$ " — 2.4 mm CHISEL FACE

B 24 $\frac{1}{4}$ " — 4.75 mm SCREWDRIVER FACE

B 12 $\frac{3}{16}$ " — 4.75 mm EYELET BIT

B 58 $\frac{1}{4}$ " — 6.34 mm CHISEL FACE

LONG LIFE

B 42 LL $\frac{1}{4}$ " — 4.75 mm CHISEL FACE

B 38 LL $\frac{1}{4}$ " — 3.2 mm CHISEL FACE

B 14 LL $\frac{3}{16}$ " — 2.4 mm CHISEL FACE

B 44 LL $\frac{1}{4}$ " — 4.75 mm SCREWDRIVER FACE



Don't take chances. We don't. All our ADCOLA Soldering Instruments are of impeccable quality. You can depend on ADCOLA day after day. That's why they're so popular. You get consistent good service . . . reliability . . . from our famous thermally controlled ADCOLA Element and the tough steel construction of this ideal production tool.

* Write for price list and catalogue



ADCOLA PRODUCTS LTD.,
(Dept. M), ADCOLA HOUSE, GAUDEN RD., LONDON, S.W.4.
Telephone: 01-622 0291/3 • Telegrams: Soljoint London Telex • Telex: Adcola London 21851

EX-RENTAL TELEVISIONS

TWO-YEAR GUARANTEE

17" SLIMLINE 405 only
£11 10 0


19" SLIMLINE 405/625
39 Gns.

Carriage and Insurance 30/-
FREE ILLUSTRATED LIST OF
TELEVISIONS

17"—19"—21"—23"

WIDE RANGE OF MODELS,
SIZES AND PRICES

DEMONSTRATIONS DAILY

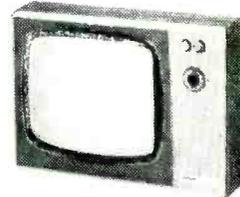

TWO-YEAR GUARANTEED TUBES 100% REGUNNED

Slim Line Tubes 110" 17" and 19" 109/6, 21" and 23" 129/6.

Normal Tubes 70" and 90" 17" 99/6, 21" 119/6, 14" and other sizes 79.6.

SPEAKERS 10/-, 2 1/2" 8Ω, 3 1/2" 25Ω, 4" 10Ω, 3" x 5" 8Ω, 7" x 4" 3Ω, 8" x 3" 3Ω. BRAND NEW. P. & P. 2/-.

RECORD PLAYER CABINET 49/6

Transistors: Mullard matched output kit 7/6, OCB1D—2 OCB1's. P. & P. FREE.

Transistor Radio Cases: 4 for £1. Size 9 1/2" x 6 1/2" x 3 1/2". P. & P. 9/6.

Ferrite Rods 3/6: 6" and 8" complete with LW/MW Coils. P. & P. FREE.

STRIP LIGHT TUBES 3/9 each. 11" (284mm). 230/240 volts, 30 watts. Ideal for cocktail cabinets, illuminating pictures, diffused lighting, etc. 6 for £1. P. & P. free.



Cloth covered. Size 16 1/2" x 14 1/2" x 7 1/2". Takes any modern auto-changer. P. & P. 7/6.

(DUKE & CO. LONDON) LTD.

£21/3 Romford Road, London, E12

Tel. 01-478 6001/2/3

PHOTOELECTRIC KIT

CONTENTS: 2 P.C. Chassis Boards, Chemicals, Etching Manual, Infra-Red Photo-transistor, Latching Relay, 2 Transistors, 3 Diodes, Resistors, Gain Control, Terminal Block, Elegant Case, Screws, etc. In fact everything you need to build a Steady-Light Photo-Switch/Counter/Burglar Alarm, etc. (Project No. 1) which can be modified for modulated-light operation.



PHOTOELECTRIC KIT 39/6

Postage and Pack 2/6 (UK)
Commonwealth:
SURFACE MAIL 3/6
AIR MAIL £1.00
Australia, New Zealand,
S. Africa, Canada and U.S.A.
Also Essential Data Circuits
and Plans for Building
10 Advanced Designs

INVISIBLE BEAM OPTICAL KIT

Everything needed (except plywood) for building: 1 Invisible-Beam Projector and 1 Photocell Receiver (as illustrated) Suitable for all Photoelectric Burglar Alarms, Counters, Door Openers, etc.

CONTENTS: 2 lenses, 2 mirrors, 2 45-degree wooden blocks, Infra-red filter, projector lamp holder, building plans, etc. Price 19/6. Postage and Pack. 1/6 (U.K.). Commonwealth. Surface Mail 2/-; Air Mail 8/-.

LONG RANGE INVISIBLE BEAM OPTICAL KIT

CONTENTS: As above. Twice the range of standard kit. Larger Lenses, Filter, etc. Price 29/6. Postage and Pack. 1/6 (U.K.). Commonwealth: Surface Mail 2/6; Air Mail 10/-.

JUNIOR PHOTOELECTRIC KIT

Versatile Invisible-beam, Relay-less, Steady-light Photo-Switch, Burglar Alarm, Door Opener, Counter, etc., for the Experimenters.

CONTENTS: Infra-Red Sensitive Phototransistor, 3 Transistors, Chassis, Plastic Case, Resistors, Screws, etc. Full Size Plans, Instructions, Data Sheet "10 Advanced Photoelectric Designs". Price 19/6. Postage and Pack. 1/6 (U.K.). Commonwealth 2/-; Air Mail 4/-.

JUNIOR OPTICAL KIT

CONTENTS: 2 Lenses, Infra-red Filter, Lampholder, Bracket, Plans, etc. Everything (except plywood) to build 1 miniature invisible beam projector and photocell receiver for use with Junior Photoelectric Kit.

Price 10/6. Post and Pack. 1/6 (U.K.). Commonwealth: Surface Mail 2/-; Air Mail 4/-.

YORK ELECTRICS

335 BATTERSEA PARK RD., LONDON S.W.11

Send a S.A.E. for full details, a brief description and Photographs of all Kits and all 52 Radio, Electronic and Photoelectric Projects Assembled.

knight-kits

FANTASTIC LOW PRICES!

Due to huge purchase these superb U.S.A. construction kits can be offered at 25%—50% off recommended list prices. Absolutely complete with most detailed construction and operating books. Available from all branches or by mail order for 7/6 CARRIAGE AND PACKING on each kit. Two kits or more carr. free.

KG-865 50 Watt Stereo Amplifier Kit

DELUXE FEATURES



All Silicon Transistors for Stability, Cleaner Sound ● Extremely Wide Power Bandwidth and Frequency Response ● 50W IEF Power Output ● Specially Selected Low-Noise Preamp Transistors ● Two Printed Circuit Boards for Fast Easy Assembly ● Convenient Front-Panel Stereo Headphone Jack ● Teak-finished Extruded Aluminium Front Panel ● Two AC Convenience Outlets

● Output: 50W I.F.H., 25W per channel; 34W continuous sine wave ● Response: $\pm 1dB$, 18 to 30,000Hz ● Output Impedance: 4 through 16ohms, plus stereo headphones ● I.M. Distortion: under 1% at 60Hz and 7,000Hz mixed 4:1 at rated power ● Input Sensitivity: Magnetic Phono, 5mV; Tuner and Auxiliary, 500mV ● Power Requirement: 230-250V, 50Hz a.c.

Recommended List Price £34.19.6: 24 GNS Assembled 89 GNS. Teak Case 85 extra

ALL SILICON TRANSISTORS

The NEW KG-980 Stereo FM Receiver Kit



Designed to Satisfy the Most Critical Listener

R.F. and I.F. Panels Assembled and Aligned ● Front Panel Stereo Headphone Jack and Speaker Muting Switch ● Full Controls including Tape Monitor ● 50W I.F.H. Output ● Usable I.E.F. Sensitivity: $3\mu V$ ● Frequency Response: $\pm 1dB$, 30 to 15,000Hz. ● Harmonic Distortion: less than 1.0% ● A.M. Suppression: more than 30dB ● Channel Separation: 30dB ● Complimentary Transformerless ● Power Output: 50W I.F.H. (25W per channel); 34W continuous sine wave ● Frequency Response: $\pm 1dB$, 18 to 30,000Hz ● Power Bandwidth: 20-20,000Hz at 1% harmonic distortion ● Two R.F. Stages ● Stereo Indicator Light. Recommended List Price £82.19.6: 89 GNS. Assembled 49 GNS. Teak Case 5 GNS. Extra.

KG-375A Deluxe Solid-State Auto Analyzer Kit

Tune-up and trouble-shoot any car, perform actual road tests

Its several testers in one . . . do all this



Set Engine Idle and Automatic Transmission Shift Points ● Detect Condition of Point Surfaces ● Detect Distributor Wear ● Check Voltage and Current Regulators ● Check Generators for both Current and Voltage Output ● Find Poor or Open Earth Circuits ● Detect Variation in Dwell Angle. Recommended List Price £23.17.6: 16 GNS. Assembled Price: 21 GNS.

KG-625 Deluxe 6in Vacuum Tube Volt Meter Kit

Huge 6in Meter Scale ● Ranges: a.c. 0-0.5-1.5-5-15-50-150-500-1,500V full scale. ● Accuracy: $\pm 3\%$ of full scale reading ● Input Resistance: 11M Ω to 1,500V ● Ranges: a.c. 0-1.5-5-15-50-150-500-1,500V full scale. 0-4-2-14-42-140-420-1,400-4,200V full scale ● Accuracy $\pm 5\%$ ● Frequency Response $\pm 1dB$, 30Hz to 3MHz; $\pm 3dB$, 30Hz to 5MHz ● Ohmmeter Ranges: 1-1,000-10,000 ohms; 0-1-10-100-1,000M Ω ● Battery 1½V Z. Recommended List Price £24.19.6: 12 GNS. Kit 620 as KG 625 (same Ranges) but 4in Scale: Recommended List Price £18.5.6 9½ GNS.



— WHY NOT BUY THE PAIR? —

KG-371 Deluxe Solid-State Timing Light


Performance surpasses assembled units costing much more



Helps Set Ignition Timing ● Checks Synchronisation of Double Breaker Arms ● Checks for Sticking Automatic Spark-Advance Mechanism ● Checks Distributor Cam Wear ● Built-in D.C. Power Supply ● Reliable Solid-State Circuit ● Your car gives more miles per gallon; Improved performance; Greater reliability. Recommended List Price £12.10.0: 9 GNS. Available Assembled Only.

STAR ROAMER 5-Band Shortwave Receiver Kit

Bandspread: electrical, calibrated 0-100 ● Sensitivity: 10 μV for 10dB signal-to-noise ratio ● I.F. Bandwidth: 3kHz at 6dB down ● Beat Frequency: variable, 0-5kHz ● Speaker: its permanent-magnet type ● Power Supply: fused, transformer operated ● Headphone Output: low impedance ● Valve Complement: 1-5BE6, 1-6X8, 1-12AX7, 1-6AK5 or 1-6AR5 ● Power Requirements: 230-250V, 50Hz a.c.; 15W ● Covers 200 to 400kHz and 550kHz to 30MHz in 5 Band-switched Ranges ● Superheterodyne Circuit includes controlled regenerative I.F. stage ● A.V.C. reduces fading and blasting; A.N.L. cuts noise to a minimum ● Aerial Trimmer effectively peaks incoming signals for best reception ● Illuminated "S" Meter; Large, Easy-to-Read 7½in Slide Rule Dial. Recommended List Price £21.19.0: 14 GNS. Assembled Price 19 GNS.

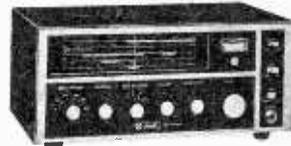


100-in-1 Electronic Science Lab

LOOK AT THE PROJECTS YOU CAN BUILD
Electronic Scale ● Electronic Timer ● Signal Generator ● Hybrid Light Meter ● Signal Injector ● Morse Code Buzzer ● Electronic Cat ● Metronome ● Code Flasher ● CW Monitor ● Ohmmeter ● Boat Horn ● Hybrid Radio ● Hybrid Voice Relay ● Air-Powered Radio ● Polarity Checker ● Valve Checker. Includes: ● Dual Headset ● Photocell ● Speaker ● Meter ● Aerial ● Transistors. Recommended List Price £16.8.0: 9½ GNS.



KG-640 20,000 ohms/Volt VOM Kit

BIG PROFESSIONAL SIZE 62 RANGE MULTIMETER ● A.C. Volts (12 Ranges): 0-2-4-8-16-40-80-200-400-800-1,600-2,000-4,000V ● D.C. Volts (12 Ranges): 0-0.8-1.6-8-16-40-80-400-800-1,600-2,000-4,000V ● Output Volts (8 Ranges): 0-2-4-8-16-40-80-200-400V ● Resistance (3 Ranges): 0-1,000-100,000 ohms-10 mega. Centre scales at 12, 1,200 and 120K Ω ● D.C. Current (10 Ranges): 0-0-100-400-800 μA , 8-16-200-400mA, 8-16A ● Decibels (12 Ranges): -12 to +74 ● D.C. Sensitivity: 20,000 ohms per volt or 10,000 ohms per volt (function of scale multiplier switch). ● Frequency Response: 80Hz to beyond 200kHz ● Accuracy: D.C. 3%, A.C. 5% ● Test Leads: one red, one black, each 48in long ● Multiplier Resistors: AU 1% carbon film. Recommended List Price £16.19.6: 9½ GNS. Assembled Price 12 GNS.

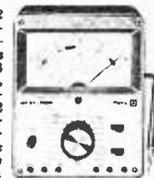

JASON TAPE

We offer you fully tenasilled polyester/mylar and P.V.C. tapes of identical quality hi-fi, wide range recording characteristics as top grade tapes. Quality control manufacture. They are truly worth a few more coppers than acetate, sub-standard, jointed or cheap imports. TRY ONE AND PROVE IT YOURSELF.

Postage 1/- reel. Post free less 5% on three reels. Quality and Trade enquiries invited. NOTE. Large tape stocks at all branches.

Standard	2/3	3in.	Long	2/3	3in.	Double	4/-	4in.	Triple	
3in. 1,500ft.	4in. 3,000ft.	4/8	4in. 4,800ft.	5in. 6,000ft.	7/6	5in. 9,000ft.	10/6	5in. 1,200ft.	15/-	5 1/2in. 2,400ft.
5in. 900ft.	10/6	5 1/2in. 1,200ft.	13/-	5 1/2in. 1,800ft.	19/-	7in. 3,600ft.	44/-	7in. 1,200ft.	18/6	7in. 1,800ft.
										7in. 2,400ft.
										8in. 600ft.
										8in. 600ft.

Stockists of Leak, Quad, Chapman, Goodman, Armstrong, Tripletone, Linear, Rodgers, Truvox, Ferrograph, Wharfedale, etc., etc.

TECHNICAL TRADING

- All Mail Orders:—
- ★ ARUNDEL 13-17 Queen Street Tel. 3280
 - ★ BRIGHTON 6 Queen's Road Tel. 23975
 - ★ LONDON 10 Tottenham Court Road Tel. MUSEUM 2639
 - ★ PORTSMOUTH 350-352 Fratton Road Tel. 22034
 - ★ SOUTHAMPTON 72 East Street Tel. 25851

PERSONAL CALLERS Welcomed at all Branches where there are large Hi-Fi and component stocks at the keenest prices including:

GARRARD 1025 Autochangers complete with GARRARD STEREO CARTRIDGE 7½ GNS.

MAGNETIC CARTRIDGES Goldring 800H 7½ GNS.

Shiro AT33 £7.10.0 (Both listed over £10)



Train for tomorrow's world in Radio and Television at The Pembridge College of Electronics.

The next full-time 2 year College Diploma Course which gives a thorough fundamental training for radio and television engineers starts on 5th January, 1971.

The course includes theoretical and practical instruction on Colour Television receivers and is designed to cover the syllabus of the new City and Guilds Radio, Television and Electronics Technicians' Course. Pembridge College diplomas are awarded to successful students.

The way to get ahead in this fast growing industry—an industry that gives you many far-reaching opportunities—is to enrol now. Minimum entrance requirements Senior Cambridge or 'O' Level, or equivalent in Mathematics and English.

To: The Pembridge College of Electronics (Dept. PW16), 34a Hereford Road, London, W2. 5AJ

Please send, without obligation, details of the Full-time Course in Radio, Television and Electronics.

NAME.....

ADDRESS.....

BUILD YOUR CIRCUITS ON VEROBOARD

—the Universal Wiring Board—
obtainable from your local Retailer

Trade enquiries to:
NORMAN ROSE (ELECTRICAL) LTD.
8 St. Chad's Place, Gray's Inn Road, London, W.C.1

Technical enquiries to:
VERO ELECTRONICS LTD.
Industrial Estate, Chandler's Ford, Hants

GOLDRING & GARRARD PRICES SLASHED

G.850 £4.17.6d p.p. 2/6. SP25 Mk 11 £10.15.0d p.p. 10/-
SEE BELOW FOR OTHER MODELS
Goldring 800/E Elliptical Transcription Arm Cart. £11.15.0d p.p. 4/-



PLINTHS AND COVERS

Suitable for AT60, SP25, 3000, 2500, 3500. Superbly finished Plinth, ready cut for use, complete with Tinted Perspex Cover. This unit is finished in Teak Polish and will blend in any modern home. 79/6 p.p. 7/6.

TURNTABLES

Garrard 2025 TC	Son 9 TAHC Diamond	£9.10.0d
Garrard 3000	Son 9 TAHC Diamond	£9.12.6d
Garrard A70	Mk 11 Less Cart.	£11.15.0d
Garrard SL65B	Less Cart.	£13.19.6d
Garrard AP75	Less Cart.	£15.19.6d
Garrard SL72B	Less Cart.	£24.0.0d
Garrard SL75	Less Cart.	£25.0.0d

10/- P.P. FOR DECKS, SPEAKERS, AMPS ETC.

MISCELLANEOUS

Teleton CR 10T £29.0.0d p.p. 10/-
Teleton F4200 £42.0.0d p.p. 10/-
Best Stereo Headphones Ω 52/6 p.p. 5/-
"Master" Magnetic Cart. Diamond Stylus 65/- p.p. 5/-
LL Nova Amp. 5 + 5 Mag and Cer-Input £15.10.0d p.p. 10/-
3-Way Speaker System Teak Cabinet, size 14½" x 8" x 6", 10 Watts Peak, each £5.19.6d p.p. 7/6
Nova 7500 VHF Tuner Plus 7 x 7 Amp. £39.0.0d p.p. 10/-
3-Way Speaker System Teak Cabinet, size 21" x 11½" x 9½" 20 Watts Peak, each £11.19.6d p.p. 10/-
Prices for good not listed, sent by return of post. S.A.E. please.

LEAK SANDWICH

Enclosure (26" x 15" x 12") oiled (matt) walnut 8 ohms—up to 35w handling capacity.
List price £45. 10. each.
Our price £32 each p. p. 10/-

GARRARD SP25 ON PLINTH WITH COVER

Complete, not wired, £14.12.8d p.p. 15/- Ready wired with 5-pin Din or Phono, 10/6 extra.
For any other Deck, 3000, 2025TC, add price of Plinth and Cover to Deck and add 15/- p.p.

Send P.O. Order. Cheques, etc., to:

AUDIO SUPPLIES

Callers welcome: 50 STAMFORD HILL, LONDON, N.16
Phone: 01-806 3611

Open Sun. 10 a.m. to 2 p.m. Mon. to Sat. 9.30 to 6 p.m. Thurs. 1 p.m.



AMAZING MINI-DRILL

FOR PRECISION
**MODEL
WORK**


Indispensable for precision drilling, grinding, polishing, etching, gouging, shaping. Precision power for the enthusiast. Shockproof. Completely portable power from 4½ volt external battery. So much more scope with MINI-DRILL. Super Kit (extra power, interchangeable chuck) 79/6, p.p. 2/6. De Luxe Professional Kit with 17 tools 130/- p.p. 4/6. Money ref. g'tee.

+ 6 TOOLS

MERLIN SUPPLY CO.

Dept. PW11D, Nailsea, Bristol BS19 2LP

New for Project 60

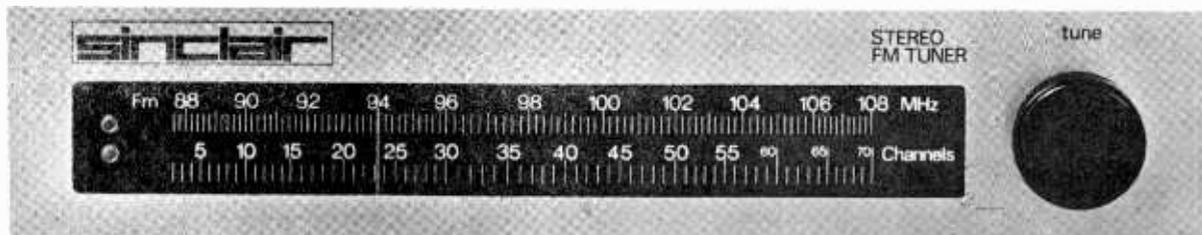

the world's first high fidelity *phase lock loop* FM tuner

It has always been our policy at Sinclair Radionics to employ new and highly advanced circuitry in our products so that we can offer better performance at competitive prices. Our new F.M. tuner is the first in the World to use the phase lock loop principle. We have also incorporated such advanced features as varicap diodes for the tuning, printed circuit coils for the tuner and I.F. strip, A.G.C., A.F.C., an excellent squelch circuit to silence the tuner between stations, an Integrated Circuit stereo decoder and the option of remote control and push button switching.

The phase lock loop principle was first applied to receivers for reception from satellites because of the important improvements in signal to noise ratio that could be obtained by this technique. In addition there were the benefits of greatly improved selectivity and sensitivity. The Project 60 tuner, as the specifications show, is unsurpassed by any tuner now available yet we are able, because of the new circuitry, to sell the product at a fraction of the price.

From the high fidelity point of view this new circuit has the very important advantage of very much lower distortion than any other tuner known to us.

A voltage controlled oscillator (V.C.O.) in a phase lock loop tuner is kept in phase with the incoming signal by a phase comparator or detector which compares the two and feeds a control voltage to the oscillator. This control voltage is the audio output in the case of an F.M. signal. Since it is possible to design a V.C.O. which has an extremely linear voltage to frequency transfer characteristic excellent audio fidelity can be readily achieved. Furthermore, the oscillator can track a signal whilst completely rejecting a nearby stronger signal which would cause interference in a conventional receiver.

In use the tuner is especially attractive because the squelch circuit gives complete silence between stations and because fine tuning is accomplished automatically by the tuner. Accurate tuning is therefore ensured.


The use of an integrated circuit for the stereo decoder part of the circuit helps to give improved performance as it enables us to use a far more sophisticated circuit than would otherwise be possible. In particular stereo separation is excellent. Switching from mono to stereo is automatic and is indicated by a bulb.

The Project 60 tuner is supplied completely built and tested and ready

to be mounted into any cabinet you choose. It may be used with any high fidelity amplifier including of course the Project 60 amplifier systems. The remarkable selectivity and sensitivity will make it possible to receive stereo transmissions in many more areas and foreign broadcasts will also be received far more readily. It is worth remembering that the Project 60 tuner will operate well on only a few inches of wire in most areas should this be necessary.

Project 60 F.M. tuner specifications

Number of transistors	16 plus 20 in I.C.
Tuning range	87.5 to 108 MHz.
Capture ratio	1.5dB
Sensitivity	2 μ V for 30dB quieting 7 μ V for full limiting
Squelch level	20 μ V
A.F.C. range	\pm 200 KHz.
Signal to noise ratio	>65dB
Total harmonic distortion	0.15% for 30% modulation
Stereo decoder operating level	2 μ V
Pilot tone suppression	30dB
Cross talk	40dB
I.F. frequency	10.7 MHz
Output voltage	2 x 150mV R.M.S.
Aerial Impedance	75 Ohms
Indicators	Mains on; Stereo on; tuning indicator

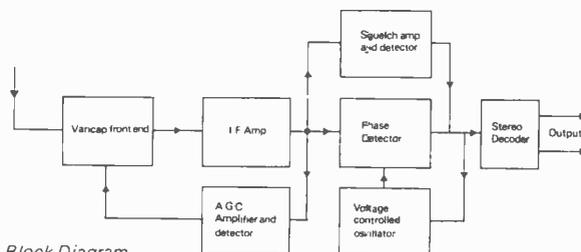

Block Diagram

Price: £25 built and tested. Post free.


sinclair

Sinclair Radionics Ltd.

at the International Audio
and Music Fair, Olympia, Stand

44

Project 60

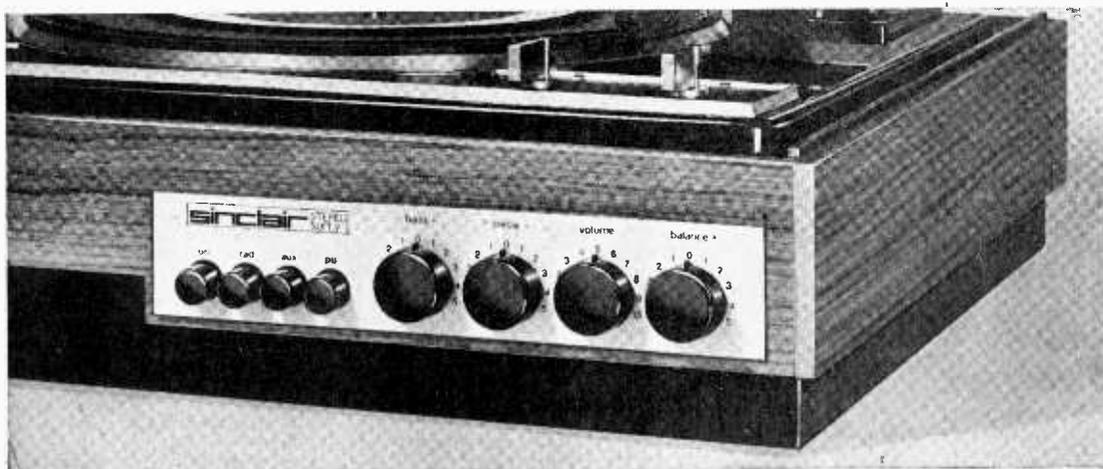

Laboratory standard modular high fidelity

Sinclair Project 60 comprises a range of modules which connect together simply to form a compact stereo amplifier with really excellent performance. So good, in fact, that only 2 or 3 amplifiers in the world can compare in overall performance and now the constructor has choice of assemblies with either 20 or 40 watts output per channel, with or without filter facilities.


The modules are: 1. The Z.30 and Z.50 high gain power amplifiers. 2. The Stereo 60 preamplifier and control unit. 3. The Active Filter Unit. 4. 4 supply units—PZ.5; PZ.6; PZ.7 and PZ.8. In a normal domestic application, there will be no significant difference between PZ.5 or PZ.6 unless loudspeakers of very low efficiency are being used, in which case the PZ.6 will be required. For assemblies using two Z.50's there is the PZ.8 supply unit to ensure maximum performance from these amplifiers. No skill or experience are needed to build your system and the Project 60 manual gives all the instructions you can possibly want, clearly and concisely. Perhaps the greatest beauty of the system is that it is not only flexible now but will remain so in the future as new additions are made to the range. A stereo F.M. tuner is next to come. These and all other modules introduced will be compatible with those already available and may be added to your system at any time. And because Sinclair are the largest producers of constructor modules in Europe, Project 60 prices are remarkably low.

System	The Units to use	In conjunction with	Your Project 60 Units will cost
A Car Radio	Z.30	Existing car radio, Sinclair Micromatic	89/6
B Simple battery powered record player	Z.30	Crystal pick-up, 12 V or more battery supply and volume control	89/6
C Mains powered record player	Z.30 and PZ.5	Crystal or ceramic P.U. Vol. control etc.	£9.9.0
D 20+20 watts RMS stereo amplifier for most needs	Two Z.30s, Stereo 60 and PZ.5	Crystal, ceramic or magnetic P.U., most dynamic speakers, FM tuner, etc.	£23.18.0
E 20+20 watts RMS stereo amplifier for use with low efficiency (high performance) speakers	Two Z.30s, Stereo 60 and PZ.6	High quality ceramic or mag. P.U., F.M. Tuner, Tape Deck, etc. All dynamit spkrs.	£26.18.0
F 40+40 watts RMS deluxe stereo amplifier	Two Z.50s, Stereo 60 PZ.8 and mains transformer	As for E	£32.17.6
G Outdoor public address system	Z.50	Microphone, up to 4 P.A. speakers, 12V car battery with converter, or 45V d.c. and controls	£5.9.6
H Indoor P.A.	One Z.50, PZ.8 and mains transformer	Mic., guitar, heavy duty speakers etc., controls	£17.8.6
J High pass and low pass filters	AFU	D, E or F as above	£5.19.6
K Stereo F.M. tuner		To be released shortly	

How to assemble and use Project 60 modules to best advantage in the above and other applications will be found in the fully descriptive Project 60 manual included with Project 60 systems. This 48 page manual is available separately, price 2/6d including postage.

sinclair SINCLAIR RADIONICS LTD., 22 NEWMARKET ROAD, CAMBRIDGE

Telephone 0223 52731

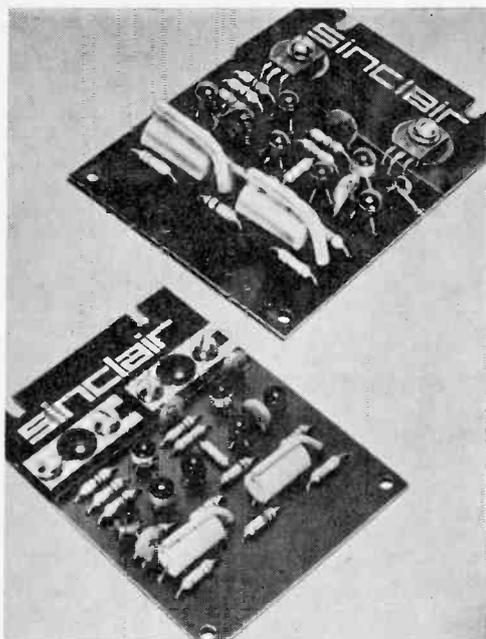

Z.30 & Z.50 Power amplifiers

The Z.30 together with the Z.50 are both of advanced design using silicon epitaxial planar transistors to achieve unsurpassed standards of performance. Total harmonic distortion is an incredibly low 0.02% at full output and all lower outputs. Whether you use the Z.30 or Z.50 power amplifiers in your Project 60 system will depend on personal preference, but they are the same physical size and may be used with other units in the Project 60 range equally well. For operating from mains, for the Z.30 use PZ.5 for most domestic requirements, or PZ.6 if you have very low efficiency loudspeakers. For Z.50, use the PZ.8 described below.

SPECIFICATIONS (Z.50 units are interchangeable with Z.30s in all applications.)

Power Outputs

Z.30 15 watts R.M.S. into 8 ohms, using 35V; 20 watts R.M.S. into 3 ohms using 30 volts.

Z.50 40 watts R.M.S. into 3 ohms from 40 volts; 30 watts R.M.S. into 8 ohms, using 50 volts.

Frequency response 30 to 300,000 Hz \pm 1dB

Distortion 0.02% into 8 ohms

Signal to noise ratio better than 70 dB unweighted


Input sensitivity 250mV into 100 Kohms.

For speakers from 3 to 15 ohms impedance

Size $3\frac{1}{2} \times 2\frac{1}{4} \times \frac{1}{2}$ ins. (90 x 58 x 13 mm)

Z.30 *Built, tested and guaranteed* **89/6**

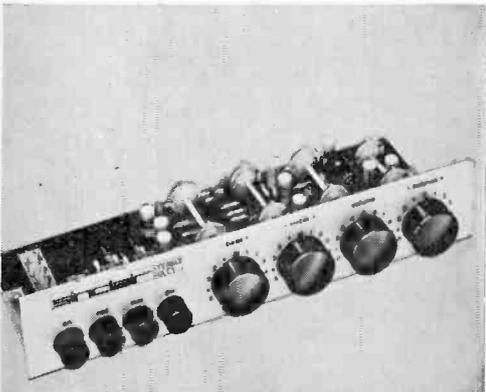Z.50 *Built, tested and guaranteed* **109/6**




Stereo 60 Pre-amp/Control unit

Designed for the Project 60 range but suitable for use with any high quality power amplifier. Silicon epitaxial planar transistors are used throughout, achieving a really high signal-to-noise ratio and excellent tracking between channels. Input selection is by means of push buttons and accurate equalisation is provided for all the usual inputs.

- Input sensitivities — Mag. p.u. — 3mV correct to R.I.A.A. curve \pm 1dB; 20 to 25,000Hz. Ceramic p.u., Radio and Aux, each up to 3mV.

- Output — 250mV.
- Signal-to-noise ratio — better than 70dB.
- Channel matching — within 1dB.
- Tone controls — TREBLE +15 to -15dB at 10kHz; BASS +15 to -15dB at 100Hz.
- Front panel — brushed aluminium with black knobs and controls.
- Size $8\frac{1}{2} \times 1\frac{1}{2} \times 4$ ins. (210 x 138 x 102 mm)

Built, tested and guaranteed **£9.19.6**

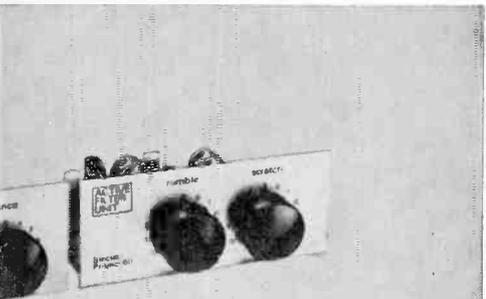


Active Filter unit

For use between Stereo 60 unit and two Z.30s or Z.50s, the Active Filter Unit matches the Stereo 60 in styling and is as easily mounted. It is unique in that the cut-off frequencies are continuously variable, and as attenuation in the rejected band is rapid (12dB/octave), there is less loss of the wanted signal than has previously been possible. Amplitude and phase distortion are negligible. The Sinclair A.F.U. is suitable also for use with

any other amplifier system. Two stages of filtering are incorporated—rumble (high pass) and scratch (low pass). H.F. cut-off (-3dB) variable from 28kHz to 5kHz. L.F. cut-off (-3dB) variable from 25Hz to 100Hz. Filter slope, both sections 12dB per octave. Distortion at 1kHz (35V supply) 0.02% at rated output.

Built, tested and guaranteed **£5.19.6**

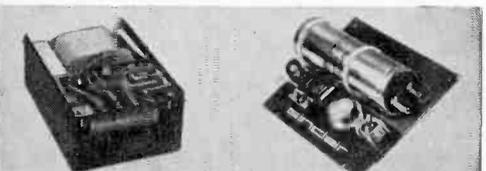

Power Supply units

Designed specially for use with the Project 60 system of your choice. Illustration shows PZ.5 power supply unit to left and PZ.8 (for use with Z.50s) to the right. Use PZ.5 for normal Z.30 assemblies and PZ.6 where stabilised supply is essential.

PZ-5 30 volts unstabilised £4.19.6

PZ6-35 volts stabilised £7.19.6

PZ-8 45 volts stabilised (less mains transformers) £5.19.6

PZ-8 mains transformer £5.19.6

GUARANTEE If within 3 months of purchasing Project 60 modules directly from us, you are dissatisfied with them, we will refund your money at once. Each module is guaranteed to work perfectly and should any defect arise in normal use we will service it at once and without any cost to you whatsoever provided that it is returned to us within 2 years of the purchase date. There will be a small charge for service thereafter. No charge for postage by surface mail, Air-mail charged at cost.

To: SINCLAIR RADIONICS LTD., 22 NEWMARKET RD., CAMBRIDGE
Please send

NAME

ADDRESS

For which I enclose cash/cheque/
money order



PW11

At the International
Audio & Music Fair, Stand

44

sinclair

Sinclair IC-10

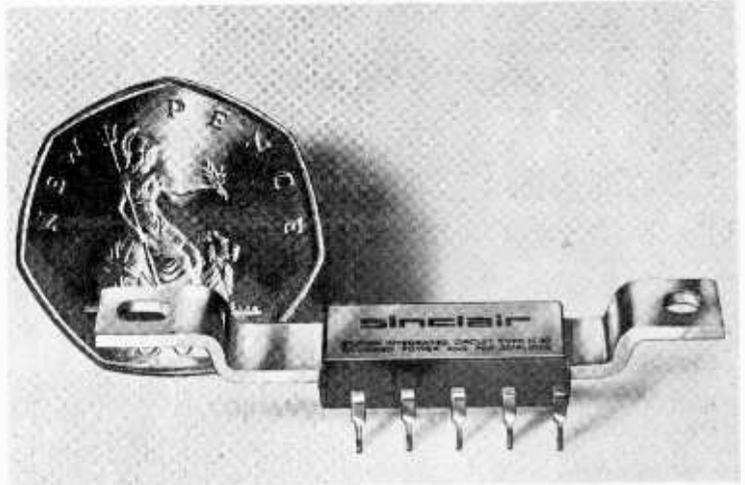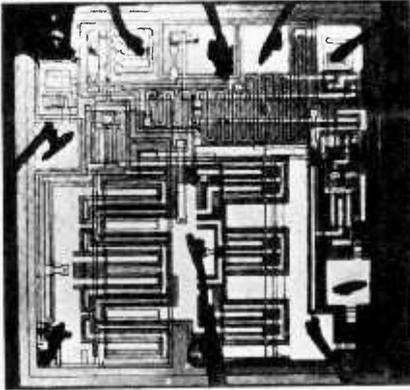

the world's most advanced high fidelity amplifier

Specifications

Output: 10 Watts peak, 5 Watts R.M.S. continuous
 Frequency response: 5 Hz to 100 KHz ± 1 dB
 Total harmonic distortion: Less than 1% at full output.
 Load impedance: 3 to 15 ohms.
 Power gain: 110dB (100,000,000,000 times) total.
 Supply voltage: 8 to 18 volts.
 Size: 1 x 0.4 x 0.2 inches.
 Sensitivity: 5mV.
 Input impedance: Adjustable externally up to 2.5 M ohms.

Circuit Description

The first three transistors are used in the pre-amp and the remaining 10 in the power amplifier. Class AB output is used with closely controlled quiescent current which is independent of temperature. Generous negative feedback is used round both sections and the amplifier is completely free from crossover distortion at all supply voltages, making battery operation eminently satisfactory.

Applications

Each IC-10 is sold with a very comprehensive manual giving circuit and wiring diagrams for a large number of applications in addition to high fidelity. These include stabilised power supplies, oscillators, etc. The pre-amp section can be used as an R.F. or I.F. amplifier without any additional transistors.

The Sinclair IC-10 is the world's first monolithic integrated circuit high fidelity power amplifier and pre-amplifier. The circuit itself, a chip of silicon only a twentieth of an inch square by one hundredth of an inch thick, has 5 watts R.M.S. output (10w. peak). It contains 13 transistors (including two power types), 2 diodes, 1 zener diode and 18 resistors, formed simultaneously in the silicon by a series of diffusions. The chip is encapsulated in a solid plastic package which holds the metal heat sink and connecting pins. This exciting device is not only more rugged and reliable than any previous amplifier, it also has considerable performance advantages. The most important are complete freedom from thermal runaway due to the close thermal coupling between the output transistors and the bias diodes and very low level of distortion.

The IC-10 is primarily intended as a full performance high fidelity power and pre-amplifier, for which application it only requires the addition of such components as tone and volume controls and a battery or mains power supply. However, it is so designed that it may be used simply in many other applications including car radios, electronic organs, servo amplifiers (it is d.c. coupled throughout), etc. Once proven, the circuits can be produced with complete uniformity which enables us to give a full guarantee on every IC-10, knowing that every unit will work as perfectly as the original and do so for a lifetime.

SINCLAIR
IC-10 with IC-10 manual
 Post free. **59/6**

To: SINCLAIR RADIONICS LTD., 22 NEWMARKET RD., CAMBRIDGE	
Please send	
.....	NAME
.....	ADDRESS
.....
.....
for which I enclose cash/cheque money order	PW 11

sinclair

At the International Audio
and Music Fair, Olympia, Stand

44


Q.16 High fidelity loudspeaker

Developed out of the revolutionary and much praised design of the original Sinclair Q.14 comes this more advanced version to meet the requirements of even greater numbers of high fidelity enthusiasts. The Q.16 employs the same well proven acoustic principles in which a special driver assembly is meticulously matched to the physical characteristics of the uniquely designed housing. In reviewing this exclusive Sinclair design, technical journals have been loud in their praise for it and it comfortably stands comparison with very much more expensive loudspeakers. The shape of the Q.16 enables it to be positioned and matched to its environment to much better effect than is the case with conventionally styled enclosures, and with its improved styling, the Q.16 presents an entirely new and attractive appearance. A solid teak surround is used with a special all-over cellular black foam front chosen as much for its appearance as for its ability to pass all audio frequencies unimpaired.

The Q.16 is compact and slim and is the ideal shelf-mounted speaker, and brings genuine high fidelity within reach of every music lover.

Specifications

Construction:	A sealed seamless sound or pressure chamber is used with internal baffle, all of materials carefully chosen to ensure freedom from spurious tone coloration.
Loading:	Up to 14 watts R.M.S.
Input impedance:	8 ohms.
Frequency response:	From 60 to 16,000Hz. as confirmed by independently plotted B & K curve.
Driver unit:	Specially designed high compliance unit having massive ceramic magnet of 11,000 gauss, aluminium speech coil and special cone suspension. Excellent transient response is achieved.
Size and styling:	9 $\frac{3}{4}$ " square on face \times 4 $\frac{3}{4}$ " deep with neat pedestal base. Black all-over cellular foam front with natural solid teak surround.
Price:	£8 19 6.

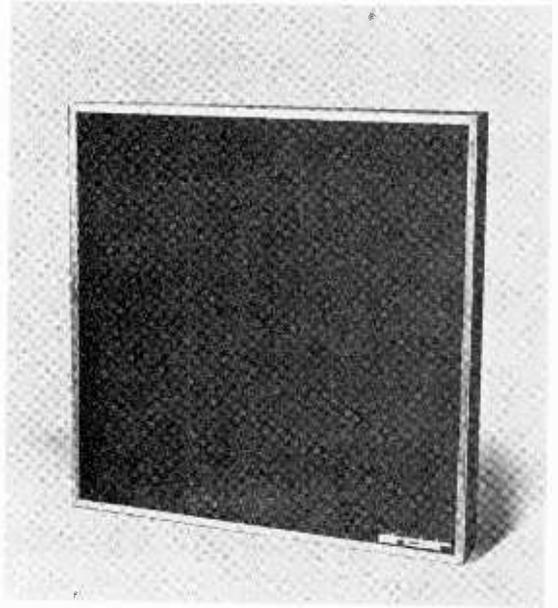

Micromatic Britain's smallest radio

Considerably smaller than an ordinary box of matches, this is a multi-stage A.M. receiver meticulously designed to provide remarkable standards of selectivity, power and quality. Powerful A.G.C. is incorporated to counteract fading from distant stations; bandspread at higher frequencies makes reception of Radio 1 easy at all times. Vernier type tuning plus the directional properties of the self-contained special ferrite rod aerial makes station separation very much easier than with many larger sets. The plug-in high fidelity type magnetic earpiece which matches exactly with the output of the Micromatic provides wonderful standards of reproduction both for speech and for music. Everything including the batteries is contained within the attractively designed case. Whether you build your Micromatic or buy it ready built and tested, you will find it as easy to take with you as your wristwatch, and dependable under the severest listening conditions.

Specifications

Size:	1 $\frac{1}{8}$ " \times 1 $\frac{7}{16}$ " \times $\frac{1}{2}$ " (46 \times 33 \times 13mm).
Weight including batteries:	1 oz. (28.35gm) approx.
Tuning:	Medium wave band with bandspread at higher frequency end.
Earpiece:	High-fidelity magnetic type.
Battery requirements:	Two Mallory Mercury Cells, type R.M. 675, for long working life.
Case:	Black plastic with anodised aluminium front panel, spun aluminium dial.
Controls:	Tuning dial, and on/off switching by means of earpiece plug.
Price:	Available in kit form complete with earpiece, case, instructions and supply of solder in fitted pack. 49/6. Ready built, tested and guaranteed. 59/6.



CRESCENT RADIO LTD.

11 & 40 MAYES RD. N.22 888-3206

MAIL ORDER DEPT.
No. 11
MAYES RD.
LONDON
N22
6TL




TRANSFORMER SCOOP

Primary 110, 220, 250 v. fused. Secondary 220 v. at 50mA, 6.3v. at 1 amp. Overall size 2 1/2" x 2" x 2 1/2" high. 12/6 P. & P. 3/-

2 x 3-15 volt, 1 amp. Secondary 250 volt Primary. Can be used as 6-8v. heater transformers. 7/6 each. P. & P. 3/-

SEND FOR FREE LISTS OF SEMI CONDUCTORS

MODEL MAKERS MOTOR

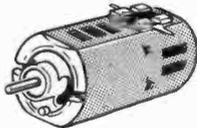

Rated up to 11.5 volt 400mA, torque 12g-cm. Size—1 1/4" long x 7/8" diam. Shaft—1/8" long x 1/16" diam. 4/6 P. & P. 1/8.

COMPONENT CENTRE

8" x 6" one sided printed circuit board	2/- each
BY100 type rectifier 800 piv 750mA	3/3 each
4-pin transistor holders	6d. each
2 1/2" 8 ohm loudspeaker	5/8 each
2 1/2" 8 ohm loudspeaker	6/8 each
2 1/2" 8 ohm loudspeaker	5/8 each
U2 battery holders (blue plastic)	1/- each
10 ohm w/w pots	2/8 each
OC81 double heat clips	6d. each
Tape recorder rev. counters	5/- each
Transistors, Diodes, S.C.R.s etc.	Send for list now

Please include P. & P.
Send 3/- for our Component Catalogue and Flog Lists.



SHELF UNIT

Two teak finish shelves on a black frame (overall size: 28in. x 25in. x 12in.). Ideal for hi fi equipment: amplifiers, speaker cabinets, etc. The perfect answer for housing unit audio and equipment. This unit is wall mounting

50/-

PLEASE NOTE P. & P. IS FREE



WESTON MILLIAMMETER

Modern clear plastic design. 1mA full scale, calibrated 0-100. 2 1/2" x 2 1/2" x 1 1/2" deep.

30/- Plus 2/6 P. & P.

IMPORTED PANEL METERS

KA-38C 1 1/2" x 1 1/2" 50µA, 100µA, 500µA, 1mA, 5mA. S meter 1mA, 300v. All at

KA-65C 3 1/4" x 3 1/4" 300v., S meter 500µA, 1mA. All at

29/6 Plus 1/- P. & P.

39/6 Plus 1/6 P. & P.

All modern design and made to high standards.

FLICK SWITCHES

250 volt 3A. Single Pole on-off. 1 1/2" nylon Toggle. 3/6 P. & P.



E.M.I. SET 450

3, 8 or 15 Ω, 10 watts. 65/- Plus 7/6 P. & P.

DWELL TIME UNIT




These small units contain the following components: 700 ohm DPDT relay with base, 1µF 250v. paper, 0.01µF 400v. paper, 50µF 35v. electrolytic, 3 diodes, OC200 transistor, a 2N2928 type transistor unmarked, a skeleton pre-set pot, 4 pin din plug & skt., 4 foot of 4 core screen. All housed in a small neat metal box. Can be made into many timing devices.

12/- Plus 1/6 P. & P.

CRESCENT CHROMOSONIC SOUND OPERATED LIGHT DISPLAY

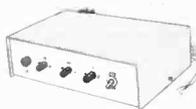The unit is connected directly across the speaker output of an amplifier, it will then convert audio signals into a spectacular three colour psychedelic light display. SEND S.A.E. FOR FURTHER DETAILS



Size 8 1/2" x 5 1/2" x 3" high. 500 watts each channel light output. A total of 15 x 100 watt lamps can be used! Input—jack socket. Controls vary the input to each channel.

£18-10-0 each

Plus P. & P. 7/6.

CHROME TV STAND

28 x 8 1/2 x 16in. high. This modern design TV Stand would make an ideal base for a coffee table and is a bargain at

32/6 Plus 6/- P. & P.

MAINS UNITS for all types of TRANSISTOR EQUIPMENT

PLUS-3 MAINS UNIT

Provides three separate switched output voltages 6v., 7 1/2v. and 9v. DC. attractive case with indicator light, mains lead output socket, plug and lead. Size 4 1/2" x 3 1/2" x 2 1/2" in.

57/6 P. & P. 2/6



(Extra lead with DIN plug for Cassette Recorders 7/6)

MAINS UNIT

for transistor equipment using 7 1/2v. Complete with DIN plug for power socket. Can also be supplied for a 6-volt output complete with suitable plug. (State make, model and voltage required.) 45/- P. & P. 2/6



UNIT FOR USE WITH 12v CAR BATTERY

Suitable for running transistor radios etc. (State output reqd. - 6v, 7 1/2v or 9v) Price 35/- including fused lead P. & P. 2/6

MAINS UNITS

For single outputs, 6v, 9v, 12v, 18v, 39/6. For two separate outputs, 4 1/2v + 4 1/2v, 6v + 6v., 9v + 9v. 42/6. P. & P. 2/6 per unit. (Please state outputs reqd.)

MAINS UNIT FOR ALL TRANSISTOR RADIOS ETC., USING PP3 TYPE BATTERY. (ALSO AVAILABLE FOR 6V.)


20/- P. & P. 2/-



All units are completely isolated from mains by double wound transformer ensuring 100% safety.

R.C.S. PRODUCTS (RADIO) LTD.
(Dept. P.W.), 31 Oliver Road, London, E.17

DIMMASWITCH

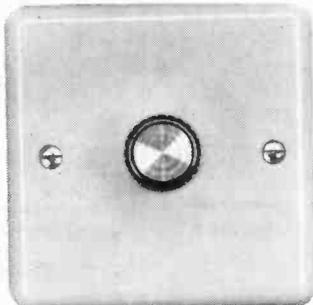

This is an attractive dimmer unit which fits in place of the normal modern light switch. The ivory mounting plate matches modern fittings and the control knob is bright chrome. An ON/OFF switch is incorporated to control 40-600 watts of all lights except fluorescents at mains voltages from 200-250V, 50 Hz.

Competitive products sell at £4.19.6d.—our price is £3 4s. We also offer at £2 14s. a complete kit of parts with instructions enabling you to build this dimmer yourself.

The circuit uses a miniature RCA triac and a diac triggering device to give complete reliability. Radio interference suppression is included.

Post and Packing 1/6d. extra.

Please send Cash with Order to:—

DEXTER & COMPANY
OLVER HOUSE, 19 KING STREET,
CHESTER CH1 2AH.

Tel: Chester 25883

As supplied to H.M. Govt. Departments, Hospitals
Local Authorities, etc.

NEW BOOKS

MAKING & REPAIRING TRANSISTOR RADIOS

by W. G. Oliver (G.3XT)
(Pub. by Foulsham Technical)

(Oct.) 21/-

SECURITY ELECTRONICS

by John E. Cunningham

(Oct.) 34/-

101 QUESTIONS AND ANSWERS ABOUT TRANSISTOR CIRCUITS

by Leo. G. Sands (Oct.) 26/-

HI-FI STEREO SERVICING GUIDE

by Robert G. Middleton

(Nov.) 35/-

101 EASY HAM RADIO PROJECTS

by Robert M. Brown and Tom Knettel


(Nov.) 30/-

FOULSHAM-SAMS TECHNICAL BOOKS
(W. FOULSHAM & CO. LTD.)
YEovil RD., SLOUGH, BUCKS, ENGLAND

ROC ELECTRONICS

CRYSTAL RADIO KIT Model R.125

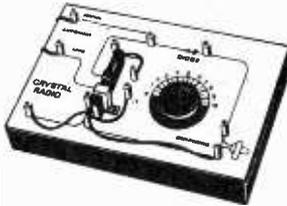
This easy to build Radio is based on the same circuit developed by Marconi for the very first radio transmission but uses a modern ferrite aerial for maximum efficiency.
A perfect introduction to Radio Theory.



PRICE £1.10.0.



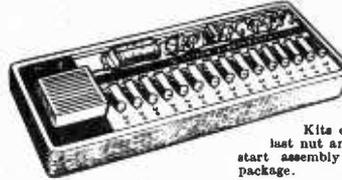2 OCTAVE ELECTRONIC ORGAN KIT Model R.129




Complete with a music book containing 10 easy to play songs the R.129 solid state organ kit covers 2 full octaves.
Slotting into a fitted hardwood case the top panel carries the key assemblies and all the components including the loud-speaker. Like all Roc Electronic

Kits every item is included down to the last nut and bolt so that the constructor can start assembly within minutes of opening the package.

PRICE £4.10.0.

2 TRANSISTOR SOLAR RADIO KIT Model R.126

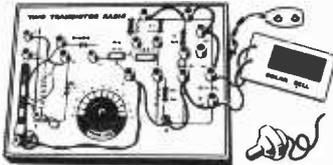

Like all Roc Electronic Kits the R.126 uses reliable no-solder connections to produce a complete 2 transistor radio in under 2 hours. As well as battery operation the kit is supplied complete with a solar cell to provide power from the Sun or any strong light source.


PRICE £2.10.0.



20 PROJECT SOLAR ELECTRONIC KIT Model R.128


This ultra modern Project Kit is shaped for the space age. Carried inside a transparent domed 4 1/2 in capsule the R.128 comes complete with a self-contained solar cell to power any one of 20 projects ranging from a one transistor radio to a Morse set complete with key and Morse training code. Supplied complete with easy to follow instructions and even the cement to assemble this unique electronic space capsule.

PRICE £4.10.0.

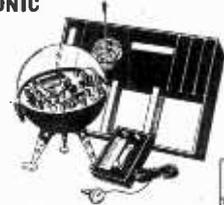

10 PROJECT INTEGRATED CIRCUIT KIT Model R.127

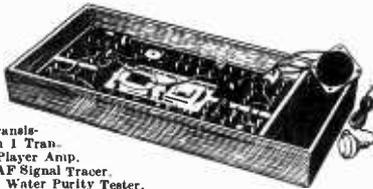Using a robust Solid State Integrated circuit the R.127 kits will build any one of these projects: (1) Germanium Radio. (2) Test Oscillator. (3) Morse Telegraph Training Set. (4) I.C.I. Transistor Radio. (5) Germanium 1 Transistor Radio. (6) Record Player Amp. (7) Continuity Tester. (8) AF Signal Tracer. (9) Radio Transmitter. (10) Water Purity Tester.



PRICE £3.10.0.

50 PROJECT ELECTRONIC KIT

Model R.130



King of the Roc Electronic Kits is the Giant R.130 which makes up into no less than 50 separate projects including Radio Receivers, Transmitters, Pachometer, Rain Alarm, Testers, Electronic Switches, Amplifiers and even an Electronic Target Game. As well as earphone, speaker, meter, relay, transformer, solar cell, buzzer, etc., etc., the R.130 is supplied complete with a fitted hardwood case and clear detailed instructions for all 50 projects.


PRICE £7.19.0.

5 WATT STEREO INTEGRATED AMPLIFIER CHASSIS Model R.123

Mounted on a heavy gauge chassis the fully transistorised R.123 stereo amplifier is completely self-contained even down to ganged volume and separate tone controls. For a simple stereo amplifier of excellent quality all you have to provide is the cabinet and control knobs.

SPECIFICATION:
Output: 5W total. 2.5W per channel.
Input sensitivity: 600mV at 2-2Mohms.

PRICE £4.19.0.

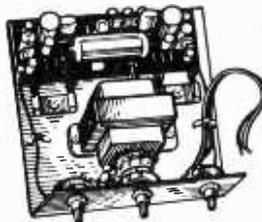

AM/FM/MPX STEREO TUNER

Model R.132



Matching the R.131 amplifier in both styling and performance the R.132 tuner covers AM and FM including stereo multiplex channels. A separate meter indicates signal strength and tuning on both AM and FM Bands. A usable FM sensitivity of 3µV means that the R.132 can be used anywhere, even in different stereo reception areas.

SPECIFICATION:
FM: frequency range: 87-108MHz.
Usable sensitivity: 3µV for 20dB quieting.
Stereo separation: 30dB at 1KHz.
Image rejection: 60dB.
AM: frequency range: 525-1605KHz.
Usable sensitivity: 250µV.

PRICE
£36.0.0.



5 WATT 8 TRACK CARTRIDGE STEREO AMPLIFIER Model R.133

Just slot in one of the many 8 track cartridge tapes available for a continuous programme of your favourite music. A manual programme override switch enables you to switch from one track to the next at the push of a button at the same time a numbered indicator lights up to show which track is playing. Beautifully finished in an oiled walnut cabinet the R.133 is mechanically engineered to provide long and reliable service. **SPECIFICATION**—Tape speed: 9.5 cm/sec (31 i.p.s.). Wow & flutter: better than 0.3%. Frequency range: 40-12,000Hz. Cross talk: better than 40dB at 1,000Hz. Output: 5W total. 2.5W per channel. Amplifier outputs: 200mV.

PRICE £36.0.0.



40 WATTS STEREO AMPLIFIER

Model R.131



Looking as good as it sounds the R.131 stereo amplifier offers excellent quality and value for money. Housed in a handsome wooden cabinet this new Roc Amplifier uses the latest solid state circuit techniques to give a specification second to none at the price.

SPECIFICATION—Output: 40W total 20W per channel. Frequency Range: 20-35000Hz. Input: Phone: Mag, 3-6mV R.I.A.A.; Xtal, 100mV; tape, 200mV; tuner, 200mV. Control: Bass, treble, volume left, volume right, selector main/remote speakers, power on/off, loudness and stereo/mono.

PRICE £25.0.0.



STEREO HEADPHONES Model R.328

Built up to a standard not down to a price, the R.328 stereo headphones represent a breakthrough in value for money.

A valuable addition to any stereo installation they will provide many hours of listening pleasure.

SPECIFICATION:
Matching impedance: 8-16 ohms.
Frequency range: 30-15,000Hz.

PRICE £2.8.0.



RETURN OF POST MAIL ORDER SERVICE

Orders under £10 please add 5/- post and packing. Orders over £10 sent post free.

ROC ELECTRONICS LIMITED
193 EDGWARE ROAD LONDON W2 1ET
TELEPHONE: 01-723 8211

Lasky's

Audio Tronics 70

Send your name and address now to receive immediately the new 1971 Edition of LASKY'S famous Audio-Tronics pictorial catalogue larger and more comprehensive than ever before. Packed with 1000's of items for the Radio and Hi-Fi enthusiast. Electronics Hobbles, Servicemen, and Communications Ham. Covers every aspect of Hi-Fi (Including Lasky's budget Stereo Systems, and Package Deals) plus Lasky's amazing money saving vouchers worth over £32. Send your name and address and 2/6 for post and inclusion on our regular mailing list.

THORN PYGMY PLUG-IN

A compact pygmy relay on an 8-pin base with D.P.D.T. contacts rated to 10A. (Some type are 3 P.D.T. on an 11-pin base).

RN TYPE	Contacts	Base	Coil Voltage
215048	D.P.D.T.	8 pin	48V AC/DC
235004	D.P.D.T.	8 pin	40V DC
215060	D.P.D.T.	8 pin	60V AC/DC
305030	3 P.D.T.	11 pin	60V DC
205024	D.P.D.T.	8 pin	24V DC
215042	D.P.D.T.	8 pin	42V DC

Others available in limited quantities.

LASKY'S PRICE 12/6 post 3/6



MODEL 5025 50,000 O.P.V. FEATURING 57 MEASUREMENT RANGES

Uses an entirely new range selection mechanism which permits the use of a really large meter in a more compact cabinet. The range selected is indicated on the meter face. High speed rotary range selection knob; polarity reversal switch, shielded meter movement with overload protection circuit; Special μ A and mA measurement ranges.

SPECIFICATION DCV: 0-0.25-2.5-10-50-250-1,000V at 25K/OPV. 0-0.125-1.25-5-0.25-125-500V at 50K/OPV. ACV: 0-3-10-50-250-1,000V at 2.5K/OPV. 0-1.5-5-25-125-500V at 5K/OPV. DC μ A: 0-25 μ A at 125mA; 0-50 μ A at 250mA. DCmA: 0-2.5-25-250mA at 125mV; 0-5-50-500mA at 250mV. DC Amps: 0-5A at 125mV; 0-10A at 250mV. Resistance: 0-10M/ohms. Output: Capacitor (0.1 μ F, 400V) in series with ACV ranges. Decibels: -20 to +81.5dB. Operates on two 1.5V batts. Black bakelite cabinet, size 5 1/2 x 6 1/2 x 2 1/2 in. Complete with test leads.



KIT £10.10.0 Post 5/-
ALSO AVAILABLE READY BUILT AND TESTED £12.10.0 Post 5/-

JUST ARRIVED

Lasky's C60, C90, C120.


Exclusively made for us in U.S.A. Great Savings!

	Each	Post	Five for	Ten for		
C 60	7/6	1/-	33/-	2/-	62/-	3/-
C 90	12/6	1/-	56/-	2/-	110/-	3/-
C 120	17/-	1/-	75/-	2/-	139/-	3/-

U.S.A. Cassette head cleaner, 10/6, Post 1/-
Post 1/- each, five for 2/-, ten for 3/-



SKYROVER Mk II

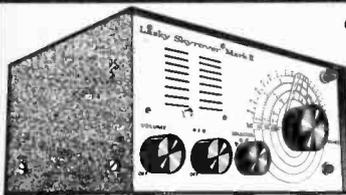

COMMUNICATION RECEIVER

A short wave receiver, exclusive to Lasky's, at a real economy price. Four valve line up using one each 6BE5, 6BA6, 6AV6 and 6AR5 valves, gives highly sensitive reception and powerful gain. Switch selected SW frequency range cover: 1.5 to 30MHz in three separate bandspread ranges and full AM medium wave-band cover in one range 550-

1,600kHz. Reduction drive tuning with hair line cursor. Controls include volume on/off BFO, Band selector. Power on indicator lamp. External antenna connections and mains fuse at rear. Internal speaker plus standard 5mm jack socket for phones on front. For 220/240V a.c. mains operation. Strong metal cabinet finished in grey crackle with anodised silver front panel. Size 9 1/2 x 5 1/2 x 5 1/2 in. Complete with mains lead and full instructions.

LASKY'S PRICE £13.13.0 Post 5/-

TMK METER KITS

This meter kit by TMK offers the unique opportunity of building a really first-class precision multimeter at a worthwhile saving in cost. The cabinet, movement and range selector mounted in position is supplied with the meter scale. The highest quality components and 1% tolerance resistors are used throughout. Supplied complete with full constructional, circuit and operating instructions.

MODEL 200 20,000 O.P.V. Multimeter. Features 24 measurement ranges with mirror scale. Large 3 x 2 in meter. Full scale accuracy: DCV and current: $\pm 2\%$. ACV: $\pm 3\%$. resistance $\pm 3\%$. Special 0.6V DC range for transistor circuit measurements.

SPECIFICATION
● DCV: 0-0.6-6-30-120-600-1,200V at 20K/OPV. ● ACV: 0-0.6-30-120-600-1,200V at 10K/OPV. ● DC Current: 0-0.6-6-600mA. ● Resistance: 0-10K 100K 1M-10M/ohms (58-580-5.8K-58K at mid-scale). ● Capacitance: 0-0.02-0.2 μ F (AC 6V range). ● Decibels -20 to +63dB. ● Output: 0.05 μ F blocking capacitor. Uses two 1.5V (U7 type) batteries. Black bakelite cabinet—Size 5 1/2 x 3 1/2 x 1 1/2 in. Complete with test leads.



KIT PRICE ONLY 92/- Post 3/6

EXCLUSIVE TMI & TM5

MODEL TM-1 MINI TESTER

The first of Lasky's new-look top value meters, the TM-1 is a really tiny pocket multimeter providing "big" meter accuracy and performance. Precision movement calibrated to $\pm 3\%$ of full scale. Click stop range selection switch. Beautifully designed and made impact resistant black case—with white and metallic red/green figuring. Ohms zero.

- DCV: 0-10-50-250-1,000 at 1K/OPV.
- ACV: 0-10-50-250-1,000 at 1K OPV.
- DC CURRENT: 0-1mA, 100mA.
- Resistance: 0-150k Ω .
- Decibels: -10dB to 22dB.
- Complete with test leads, battery and instructions.



Size Only 3 1/2 in. x 2 1/2 in. x 1 1/2 in.

LASKY'S PRICE 39/6 POST 2/6 MODEL TM-5 5K OHMS/V POCKET MULTIMETER

Another new look pocket multi-meter from Lasky's providing top quality and value. The "slimline" impact resistant case—size 4 1/2 in x 2 1/2 in x 1 in, fitted with extra large 2 1/2 in square meter. Readability is superior on all low ranges; making this an excellent instrument for servicing transistorised equipment. Recessed click stop selection switch. Ohms zero adjustment. Buff finish with crystal clear meter cover.

- DCV: 3-15-150-300-1,200 at 5K OPV.
- ACV: 6-30-300-600 at 2.5K OPV.
- DC Current 0-300 μ A, 0-300mA.
- Resistance: 0-10k Ω , 0-1M Ω .
- Decibels: -10dB to 16dB.
- Complete with test leads, battery and instructions.



LASKY'S PRICE 49/6 POST 2/6

Garrard

SL-55

OTHER GARRARD UNITS FROM STOCK

AUTOCHANGERS	
SL72B	£25 0 0
2025TC with stereo cartridge	£8 17 6
3000 complete with 9TAHC stereo cartridge	£9 19 6
SL65B	£15 10 0
SL95B	£35 0 0
SL75B	£28 0 0

SINGLE PLAYERS
AP 75, £18.10.0. AP75 with AD76K mag. cart., £21.10.0. 401 Transcription Unit, £20.0.0

BASES AND COVERS FOR GARRARD UNITS
Type WB1 and WB5 for models AT60 Mk II, 2025TC, 3000, SL65B, SL55, 1025, SP25 Mk. II. Price WB1 £3 16 6. WB5 £5 12 6. Type WB4 for models SL72B, SL75B, SL95B Price £5 12 6, Perspex covers: SP1C for WB1 £3 14 1, SP4C for WB4 and WB5 (allows unit to be played with the cover in place—Price £4 8 0.



SPECIAL SL-55 OFFER

One of the famous Garrard Synchro-Lab Series. Takes 8 L.P.s. Four-speed auto-changer; incorporating a tubular pickup arm and adjustable stylus force. Wired for Mono and Stereo. NOW AT LASKY'S SPECIAL PRICE. Complete with SONOTONE 9TA STEREO CARTRIDGE. £10.19.6

SCOOPMT-65 SPECIAL OFFER

EXCLUSIVE HI-FI STEREO TUNER AMP. OFFER THE MT-65 CHASSIS

Solid state AM/FM multiplex tuner with FET front-end/17 +17 watts stereo amplifier by world famous manufacturer. Frequency response 20-45KHz. Inputs—2.3mV mag. p/u and 140mV tape play. Tape record output. Controls: Left/right volume, bass, treble, loudness, monitor. Tuning meter and stereo beacon. Stereo 'phone jack. Machined stainless steel front panel. Overall size 20x34x16in. List Price £75.

SPECIAL PRICE £66.0.0

CARRIAGE 12/6

DE-LUXE "COMPACT" PACKAGE OFFER

MT-65 Chassis	£75 0 0
GARRARD AP-75 3-speed Single Player	£23 16 7
AUDIO DEVELOPMENT AD-36K Magnetic Cartridge	£5 18 6
2 WHARFEDALE DENTON Speaker Systems	£36 0 0
"Compact" Teak Cabinet (as shown)	£7 10 0
TOTAL RECOMMENDED LIST PRICE	£148.5.1


LASKY'S PACKAGE PRICE



£132.0.0

U.K.: carriage 40/-
All units available separately

Sinclair Project 60

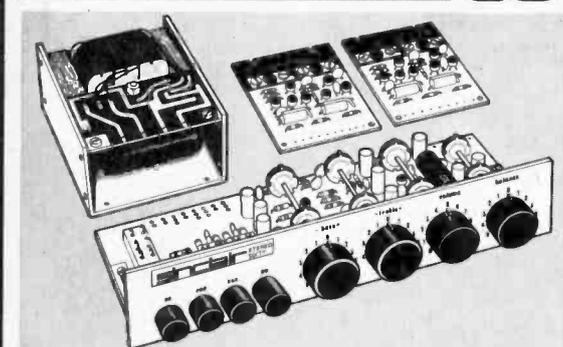

Project 60 is a range of modules which connect together to form a complete stereo amplifier. The modules are: 1. Z-30 high gain power amp. 2. Stereo-40 pre-amp. control unit. 3. The PZ-5 unbalanced and PZ-6 stabilised power supplies. A complete system comprises two Z-30's, one Stereo-40 and a PZ-5 or PZ-6.

STEREO 60 SPECIFICATION

Input sensitivities: Radio up to 3mV, Magnetic Pick-up 3mV, correct to R.I.A.A. curve -1dB; 20 to 25,000Hz. Ceramic Pick-up up to 3mV. Auxiliary up to 3mV. Output: 1 volt. Signal to noise: better than 70dB. Front panel: brushed aluminium with black knobs and controls. Size: 8¼ x 1½ x 4in.

£9.19.6

post 3/6

Z-30 SPECIFICATION

Power output: 15W R.M.S. into 8ohms using a 35 volt supply. Frequency response: 30 to 300,000Hz - 1dB. Distortion: 0.02%. Signal to noise: better than 70dB. Input sensitivity: 250mV into 100K ohms. Loudspeaker imp: 3 to 15 ohms. Power requirements: from 8 to 35V DC (The Z30 will operate from batteries if required) - Size: 3½ x 2¼ x 1½in.

89/6

post 3/6

PZ5

30V unbalanced - sufficient to drive two Z-30's and a Stereo 60 for domestic applications.

99/6

Post 2/6

PZ6

35V stabilised - ideal for driving two Z-30's and a Stereo 60 for low efficiency speakers.

£7.19.6


Post 2/6

PACKAGE PRICE For Stereo 60, two Z-30 and one PZ-5

£19.19.6

Post 10/-

EXCLUSIVE DIGITAL CLOCK SCOOP!

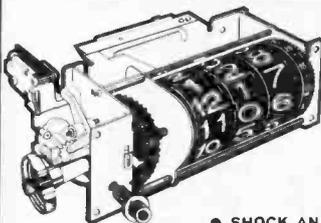

- SHOCK AND VIBRATION PROOF
- BUILT IN ALARM BUZZER

SPECIAL QUOTATIONS FOR QUANTITIES

- MADE ESPECIALLY FOR LASKY'S BY FAMOUS MAKER
- MAINS OPERATION
- 12 HOUR ALARM
- AUTO "SLEEP" SWITCH
- HOURS, MINUTES AND SECONDS READ-OFF
- FORWARD AND BACKWARD TIME ADJUSTMENT
- SILENT OPERATION SYNCHRONOUS MOTOR

This unique DIGITAL CLOCK is now available EXCLUSIVELY FROM LASKY'S in chassis form for you to mount in any housing that you choose. All settings are achieved by two dual-concentric controls at the front including: ON-OFF-AUTO and AUTO ALARM, "sleep" switch, 10 minute division "click" set alarm (up to 12 hour delay), time adjustment. Ultra simple mechanism and high quality manufacture guarantee reliable operation and long life. The sleep switch will automatically turn off any appliance—radio, TV, light, etc., at any pre-set time up to 60 min. and in conjunction with the AUTO setting will switch on the appliance again next morning.

The clock measures 4½ x 1½ x 3½ (overall from front of drum to back of switch). SPEC: 210/240V AC, 50Hz operation; switch rating 250V, 3A. Complete with instructions. HUNDREDS OF APPLICATIONS.

COMPLETE WITH KNOBS.

LASKY'S PRICE £6.19.6

Post 3/6

AUDIO DEVELOPMENT



AD-309K
PRECISION PICK-UP ARM COMPLETE WITH AD-76K MAGNETIC CARTRIDGE

The new AUDIO DEVELOPMENT precision counter-balanced pick-up arm—ready fitted with the outstanding AD-76K magnetic

cartridge is constructed of brass throughout, heavily chrome-plated; uses needle and miniature ballrace bearings; both coarse and fine balance adjustment is provided. The fixed head has standard ¼in. mounting centres and is finished in black enamel with chrome lifting spur. Completely wired, with all fixing nuts and washers. Arm rest also supplied. Tech. details: Overall length 285mm; needle to pivot length 223mm; offset angle 24°; overhang 10mm. Requires single 7/16in dia. mounting hole.

LASKY'S PRICE £9.19.6

Post 3/6

INTERNATIONAL

MAGNETIC RECORDING TAPE FROM THE U.S.A. AT LASKY'S RECORD LOW PRICES

3in. Message tape, 150ft.	2 8	5¼in. Long play, 1200ft. Mylar	15 0
3in. Message tape, 225ft.	3 9	5¼in. Triple play, 2400ft.	35 0
3in. Message tape, 300ft.	7 8	7in. Standard play, 1200ft. Acetate	12 6
3¼in. Triple play, 600ft. Mylar	10 0	7in. Standard play, 1200ft. Mylar	12 6
5in. Double play, 1200ft.	15 0	7in. Long play, 1800ft. Mylar	18 6
5in. Long play, 900ft. Acetate	10 0	7in. Double play, 2400ft. Mylar	25 0
5in. Standard play 600ft.	8 6	7in. Long play 1800ft. Acetate	15 0
5¼in. Double play, 1800ft. Mylar	22 6	7in. Triple play 3600ft. Mylar	50 0
5¼in. Long play 1200ft. Acetate	15 0		
5¼in. Standard play 900ft. PVC	12 6		

P. & P. 1/- extra per reel, 4 reels and over Post Free. Special quotes for quantities.

Lasky's Radio Limited

207 EDGWARE ROAD, LONDON, W.2. Tel: 01-723 3271

33 TOTTENHAM CT. RD. LONDON, W1P 9RB. Tel: 01-636 2605

Open all day, 9 a.m. - 6 p.m. Monday to Saturday

109 FLEET STREET, LONDON, E.C.4. Tel: 01-353 5812

152/3 FLEET STREET, LONDON, E.C.4. Tel: 01-353 2833

Open all day Thursday, early closing 1 p.m. Saturday

HIGH FIDELITY AUDIO CENTRES

42-45 TOTTENHAM CT. RD. LONDON, W1P 9RO. Tel: 01-580 2773

Open all day, 9 a.m. - 6 p.m. Monday to Saturday

118 EDGWARE ROAD, LONDON, W.2. Tel: 01-723 5789

Open all day Saturday early closing 1 p.m. Thursday

ALL MAIL ORDERS AND CORRESPONDENCE TO: 3-15 CAVELL STREET, TOWER HAMLETS, LONDON, E1 2BN Tel: 01-790 4821

Complete Stereo System £41

WITH VISCOUNT F.E.T. AMPLIFIER
 FIELD EFFECT TRANSISTORS



This superb stereo system is a real price break through. It comprises the VISCOUNT F.E.T. Mk I amplifier on which full details are given below, the famous Garrard SP 25 (including teak veneer base and transparent cover) with diamond cartridge or 2025 TC and the very successful DUO type 2 speakers. Measuring 17½in x 10½in x 6½in, the Duo type 2 speakers are beautifully finished in teak veneer with matching vynair grills. They incorporate a 10½in x 6½in drive unit and high frequency speaker, both of which are of 3 ohms impedance. The Duo speaker system is also available separately at £6.6.0 each, plus 15/- p. & p.

Complete stereo system £41 plus £2 10 p. & p. or with Mk II Amplifier and Magnetic Cartridge £45 & £2 10 p. & p.

The Viscount F.E.T. Mk I £14.5 plus 7/6 p. & p.

High fidelity transistor stereo amplifier employing field effect transistors. With this feature and accompanying guaranteed specifications below, the Viscount F.E.T. vastly surpasses amplifiers costing far more.

Specification—Output per channel 10 watts r.m.s. Frequency bandwidth 20 Hz to 20 kHz + 1db at 1 watt. Total distortion at 1 kHz at 9 watts 0.5%. Input sensitivities CER. P.U. 100mV into 3 meg ohms. Tuner 100mV into 100K ohms. Tape 100mV into 100K ohms. Overload Factor Better than 26db.

Signal to noise ratio—70db on all inputs (with vol. max). Controls—6 position selector switch (3 pos. stereo and 3 pos. mono). Separate volume controls for left and right channels. Bass ± 14db at 60 Hz. Treble (with D.P.S. on off) ± 12 db at 10 KHz. Tape recording output sockets on each channel. Size 12½in. 6in. 2½in. in simulated

teak case. BUILT & TESTED. MkII (MAG P.U.) £15.15 plus 10/- p. & p. Specification same as Mk. 1, but with the following inputs. Mag. P.U. CER. P.U. Tuner. Spec. on Mag. P.U. 3mV at 1 kHz input impedance 47K. Fully equalised to within ±1db RIAA. Signal to noise ratio—65db (vol. max).

The £29-10-0 Stereo system

The Duetto is a good quality stereo amplifier, attractively styled and finished. It gives superb reproduction previously associated with amplifiers costing far more.

SPECIFICATION—R.M.S. power output 3 watts per channel into 10 ohms speakers.

INPUT SENSITIVITY. Suitable for medium or high output crystal cartridges and tuners. Cross-talk better than 30dB at 1Kc/s.

CONTROLS: 4-position selector switch (2 pos. mono and 2 pos stereo) dual ganged volume control.

TONE CONTROL Treble lift and cut Separate on off switch. A preset balance control.




Duetto integrated transistor stereo Amp. Garrard Changer from Cover and teak finish plinth Duo Type 1 speakers (see opp. page) The above items purchased together

£9.10.0 + 7/6 p&p.
 £7.19.6 + 7/6 p&p.
 £4.15.0 + 7/6 p&p.
 ea. £4. 4.0 + 7/6 p&p.
 £29.10.0 + £1.10 p&p.

SOUND 50

50 WATT AMPLIFIER & SPEAKER SYSTEM

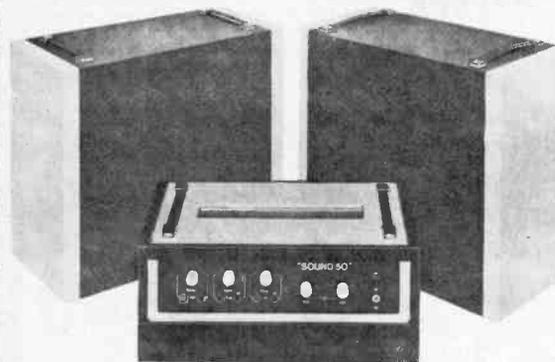

The Sound Fifty valve amplifier and speakers are sturdily constructed with smart housings and thoroughly tested electronics. They are designed to last—to withstand the knocks and bumps of life on the road. Built for the small and medium sized gig, they are easy to handle and quick to set up and can be relied upon to come over with all the quality and power you need.

Output Power: 45 watts R.M.S. (Sine wave drive). Frequency response: -3dB points 30Hz at 18KHz. Total distortion: less than 2% at rated output. Signal to noise ratio: better than 60dB.

Speaker Impedance: 3, 8 or 15 ohms. Bass Control Range: ± 13 dB at 60Hz. Treble Control Range: ± 12 dB at 10 KHz. Inputs: 4 inputs at 5mV into 470K. Each pair of inputs controlled by separate volume control. 2 inputs at 200mV into 470K.

To protect the output valves, the incorporated fail safe circuit will enable the amplifier to be used at half power.

SPEAKERS! Size 20" x 20" x 10" incorporating Baker's 12" heavy duty 25 watt high flux, quality loudspeaker with cast frame. Cabinets attractively finished in two tone colour scheme—Black and grey.

COMPLETE SYSTEM £45 Plus 60/- P. & P.
Sound 50 amp and 2 speakers

or available separately.

Amplifier £28.10.0 plus 20/- P. & P.

Speakers £12.10.0 each plus 30/- P. & P.

LIQUIDATED STOCK

DANSETTE

TOURISTE MK3

CAR RADIO


ALL TRANSISTOR

Beautifully designed to blend with the interiors of all cars. Permeability tuning and long wave loading coils ensure excellent tracking, sensitivity and selectivity on both wave bands. R.F. sensitivity at 1 MHz is better than 8 micro volts. Power output into 3 ohm speaker is 3 watts.

Originally sold complete for £154.6.

Pre-aligned I.F. module and tuner together with comprehensive instructions guarantees success first time. 12 volts negative or positive earth. Size 7in x 2in x 4½in deep.

See top of previous page for address

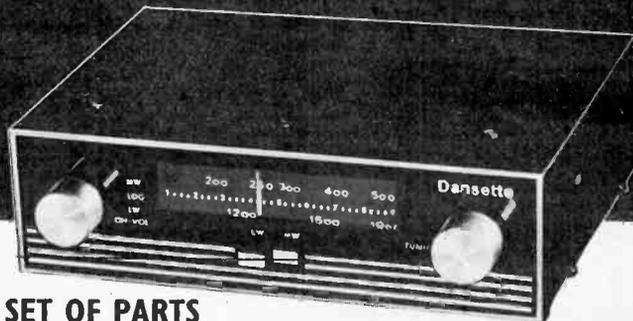

SET OF PARTS

£6.6.0


plus 7/6 P. & P.

Circuit diagram 2/6. Free with parts

Speaker, baffle and fixing kit 25/- extra plus 4/- p. & p. Postage free when ordered with parts.

The ELEGANT SEVEN Mk. III

(350mW Output)

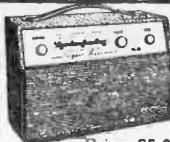

7 transistor fully-tunable M.W.—L.W. superb portable. Set of parts. Complete with all components, including ready etched and drilled printed circuit board—back printed for foolproof construction. MAINS POWER PACK KIT: 9/8 extra.

Price £5.0.0 plus 7/6 P. & P. Circuit 2/6 FREE WITH PARTS

The DORSET

(600mW Output)



7-transistor fully tunable M.W.—L.W. superb portable with baby alarm facility. Set of parts. The latest modular and pre-alignment techniques makes this simple to build. Sizes: 12 x 8 x 3in. MAINS POWER PACK KIT: 9/8 extra.

Price £5.5.0 plus 7/6 P. & P. Circuit 2/6 FREE WITH PARTS

The Classic


Simulated teak case

£9.10

Plus P. & P. 7/8



SPECIFICATION: Sensitivities for 10 watt output at 1KHz into 3 ohms. Tape Head: 2 mV (at 2.1 p.p.s.) Mag. P.U.: 2 mV. Cer. P.U.: 80mV. Tuner: 100mV. Aux. 100mV. Tape/Rec. Output. Equalisation for each input is correct to within ± 2 dB (E.I.A.A.) from 20Hz to 20KHz. Tone Control Range: Bass: 13dB at 60Hz. Treble: ± 14 dB at 16KHz. Total Distortion: (for 10 watt output) < 1.5%. Signal Noise: < -60dB. A.C. Mains 200-250V. Size 12½in long, 4½in deep, 2½in high. Built and tested

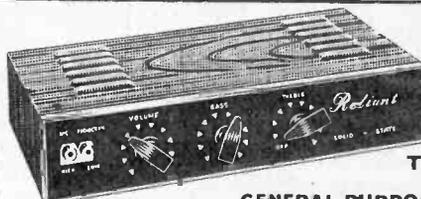

THE RELIANT

SOLID-STATE

GENERAL PURPOSE AMPLIFIER

SPECIFICATIONS
Output ± 10 watts. Output impedance—3 to 4 ohms. Inputs ± 1 .x-tal mic 10mV Tone Controls—Treble control range ± 12 dB at 10KHz. 2 .gram/radio 250mV. Bass control range ± 15 dB at 100Hz. Frequency Response—(with tone controls central) ± 15 dB points at 20Hz and 40KHz. Signal to Noise Ratio—better than -60dB. Transistors—4 silicon Planar type and 3 Germanium type. Mains input—220/250V. A.C. Size of chassis—10½in. x 4½in. x 2½in. For use with Std. or L.P. records, musical instruments, all makes of pick-ups and mikes. Separate bass and treble lift control. Two inputs with control from gram. and mike. Built and tested.

RELIANT Mk. II in simulated teak case £7.5 plus 7/6 P. & P.

THE DUO SPEAKER SYSTEM

Similar in design to those on the previous page the 2-way speaker system is beautifully finished in polished teak veneer, with matching vynair grille. It is ideal for wall or shelf mounting either upright or horizontally.

Type 1 SPECIFICATION—Impedance 3, 8 or 10 ohms (please state requirement). It incorporates Goodmans high flux 6in. x 4in. speaker and 2½in. speaker. Teak finish 12in. x 6½in. x 5½in. 4 guineas each. 7/6 P. & P.

RADIO & TV COMPONENTS

R+TV

(ACTON) LIMITED

Build working radio receivers and electronic circuits in an evening



Beginner or advanced student — you learn fast with Radionic kits

Circuits work first time with the Radionic 'no soldering' method. With the X30 kit, build 33 experiments: a printed circuit transistor radio, burglar alarm, morse code buzzer etc. The more advanced kits are suitable for G. C. E., City and Guilds, National Certificate and higher. Every set includes construction notes and all circuit diagrams. It's so easy for you to build *and* learn because you construct circuits that resemble the theoretical diagram. Re-use components easily, too — they're screw-in-mounted.

Send off this coupon today.

TO: RADIONIC PRODUCTS LTD., PW3
St. Lawrence House, Broad Street, Bristol BS1 2HF

Please send me full details of all Radionic Kits/please send me one Radionic Kit X30, for which I enclose £7 19s. 6d.

(delete where inapplicable)

Name _____

Address _____



BRAND NEW FULLY GUARANTEED TRANSISTORS

SEND FOR NEW LIST NEW PRICES

1N4001 1/6	AAZ12 4/-	BPY10 19/6	2N3819 15/-	2N3819 15/-	2N3819 15/-
1N4002 1/6	AAZ13 2/8	BKX20 3/6	2N3819 15/-	2N3819 15/-	2N3819 15/-
1N4003 2/-	AAZ17 2/-	BKX21 7/6	2N3819 15/-	2N3819 15/-	2N3819 15/-
1N4004 2/6	AC126 5/-	BKX76 3/6	2N3819 15/-	2N3819 15/-	2N3819 15/-
1N4005 2/6	AC127 5/-	BBY27 4/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
1N4006 3/-	AC127Z 10/-	BBY28 5/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
1N4007 4/-	AC128 5/-	BBY29 5/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
1N4009 1/6	AC153 4/-	BBY50 5/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
1N4148 1/6	AC154 3/-	BBY53 5/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
2G210 1/6	AC166 2/-	BBY58 5/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
2G240 4/6	AC176 5/-	BBY67 5/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
2G301 4/-	AC187 6/-	BBY95A 3/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
2G302 4/6	AC188 6/-	BBY95 3/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
2G303 5/-	AC17 6/-	BY100 3/6	2N3819 15/-	2N3819 15/-	2N3819 15/-
2G306 6/-	AC17 6/-	BY103 4/6	2N3819 15/-	2N3819 15/-	2N3819 15/-
2G308 6/-	AC19 5/-	BY126 3/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
2G309 6/-	AC19 5/-	BY127 4/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
2G371 4/6	ACV21 4/6	BY210 8/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
2G374 5/6	ACV22 3/6	BY211 7/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
2Q381 5/-	ACV28 3/6	BY212 6/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
2Q382 6/-	ACV34 4/-	BY213 5/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
2Q383 5/-	ACV36 5/-	BY215 20/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N404 4/6	ACV39 11/-	BY216 12/6	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N596 3/6	ACV40 10/-	GET102 8/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N697 3/6	AD140 10/-	GET103 4/6	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N698 8/6	AD149 10/-	MPP102 8/6	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N706 2/-	AD161 7/6	MPP103 7/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N706A 2/6	AD162 7/6	MPP104 7/6	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N707 9/6	AF102 12/6	MPP105 8/6	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N798 3/-	AF114 6/6	OA5 5/6	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N914 4/6	AF115 6/-	OA7 4/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N916 4/6	AF116 6/6	OA9 2/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N918 7/6	AF117 5/-	OA10 5/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N919 4/-	AF118 12/6	OA47 2/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N920 5/-	AF124 6/-	OA70 2/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N922 6/6	AF125 8/-	OA71 2/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N930 8/6	AF126 4/-	OA73 2/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N1131 6/-	AF127 4/-	OA74 2/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N1132 6/6	AF139 6/-	OA79 2/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N1303 4/6	AF178 9/6	OA81 2/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N1304 5/-	AF181 8/6	OA85 2/6	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N1305 5/-	AF186 8/6	OA86 2/6	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N1306 5/-	AF239 8/-	OA90 2/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N1307 5/-	AFY19 22/6	OA91 1/6	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N1308 6/-	AFZ11 12/6	OA95 1/6	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N1309 5/-	AFZ12 15/-	OA200 1/6	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N1613 4/6	ASV26 5/-	OA202 2/6	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N2147 15/-	ASV27 6/6	OA210 7/6	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N2160 12/6	ASV28 5/-	OA211 7/6	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N2287 25/-	ASV29 6/-	OA2225 7/6	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N2646 10/6	ASV67 9/6	OA2228 7/6	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N2904 6/-	ASZ21 8/6	OA2229 9/6	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N2905 7/6	AUY10 18/6	OA231 9/6	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N2925 4/-	B3M 18/6	OA232 9/6	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N2928 2/6	BA110 8/-	OA238 9/6	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N3011 5/-	BAY31 2/-	OC16 8/6	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N3063 5/-	BC107 2/6	OC19 7/6	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N3064 10/-	BC108 2/6	OC20 19/6	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N3055 15/-	BC109 2/6	OC22 8/6	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N3702 2/6	BC118 8/-	OC23 10/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N3703 2/6	BC118 8/-	OC24 10/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N3704 3/6	BC118 7/6	OC25 7/6	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N3705 3/6	BC134 7/6	OC26 5/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N3707 3/-	BC135 6/-	OC28 12/6	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N3709 2/6	BC136 7/-	OC29 12/6	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N3710 2/6	BC137 8/-	OC30 10/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N3711 2/6	BC138 8/-	OC36 12/6	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N3730 10/-	BCY30 5/6	OC41 6/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N3731 12/6	BCY31 6/-	OC42 6/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N3794 2/6	BCY32 10/-	OC43 8/6	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N3819 7/-	BCY33 4/-	OC44 4/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N3820 17/6	BCY34 6/-	OC45 8/6	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N3923 17/6	BCY38 8/6	OC46 8/6	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N4058 3/6	BCY39 9/6	OC70 2/6	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N4061 3/-	BCY40 8/6	OC71 3/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N4288 3/-	BCY42 5/-	OC72 5/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N4288 3/-	BCY43 5/-	OC73 6/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N4289 3/6	BCY70 4/-	OC74 6/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N4290 3/-	BCZ1 7/6	OC75 8/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N4291 3/-	BC147 3/6	OC76 5/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
2N4292 3/-	BC148 2/6	OC77 8/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
40361 11/-	BC149 4/-	OC78 5/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
40362 12/-	BF152 8/-	OC81 5/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
28001 10/-	BF194 3/6	OC81D 4/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
28002 10/6	BF195 3/-	OC82 5/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
28003 8/6	BD124 12/6	OC83 5/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
28004 9/6	BE3000 5/-	OC84 5/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
28006 14/-	BF115 6/-	OC122 10/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
28012 25/-	BF154 8/-	OC123 10/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
28013 20/-	BF158 8/-	OC139 5/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
28017 18/-	BF159 12/-	OC140 7/8	2N3819 15/-	2N3819 15/-	2N3819 15/-
28034 12/6	BF163 8/-	OC141 15/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
28038 25/-	BF167 5/-	OC169 4/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
28320 9/-	BF173 6/-	OC170 5/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
28321 8/-	BF180 7/6	OC171 6/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
28322 7/6	BF181 7/6	OC200 7/8	2N3819 15/-	2N3819 15/-	2N3819 15/-
28323 10/-	BFX30 8/-	OC201 9/6	2N3819 15/-	2N3819 15/-	2N3819 15/-
28324 12/6	BFY38 5/-	OC202 12/6	2N3819 15/-	2N3819 15/-	2N3819 15/-
28512 9/6	BFY20 12/6	OC203 7/8	2N3819 15/-	2N3819 15/-	2N3819 15/-
28701 8/6	BFY60 4/6	OC204 8/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
28702 11/-	BFY61 4/-	OC205 12/6	2N3819 15/-	2N3819 15/-	2N3819 15/-
28731 8/6	BFY62 4/6	OC206 12/6	2N3819 15/-	2N3819 15/-	2N3819 15/-
28732 8/6	BFY63 3/6	OC207 15/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
28733 9/6	BFY64 8/6	OC209 18/6	2N3819 15/-	2N3819 15/-	2N3819 15/-
AA178 8/6	BLY10 20/-	ORP12 10/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
AA178 8/6	BLY11 22/6	ORP60 8/-	2N3819 15/-	2N3819 15/-	2N3819 15/-
AA178 8/6	BLY11 22/6	ORP60 8/-	2N3819 15/-	2N3819 15/-	2N3819 15/-

PLEASE NOTE MINIMUM ORDER SHOULD BE 10/-

Quantity Prices 100 + Phone (01) New Autumn List. New devices, 723 0401 Ex. 4. All listed devices are from stock at time of going to press for free copy today! Please add 1/6 post packing to your order. Discounts 10% on 12 + any one type 15% on 25 + any one type

HENRY'S RADIO

Mail Order Dept. Components Origin Dept.
 303 EDGWARE ROAD, LONDON W 2
 Telephone 01-723 1008 9
 OPEN MON. SAT 9am-6pm THURS 9am-5pm

The FERROGRAPH SENSATION!


JUST LOOK AT THESE
FABULOUS LOW PRICES!

SERIES 7 RECORDERS


MODEL NO.	LIST PRICE	CASH PRICE
724/722	£242 10 9	£199 10 0
702/704	£207 7 0	£169 10 0
713	£188 10 0	£156 0 0

AVAILABLE ON NO DEPOSIT CREDIT TERMS.
CARRIAGE 30/- EXTRA.

PORTABLE OR WOOD CABINET.

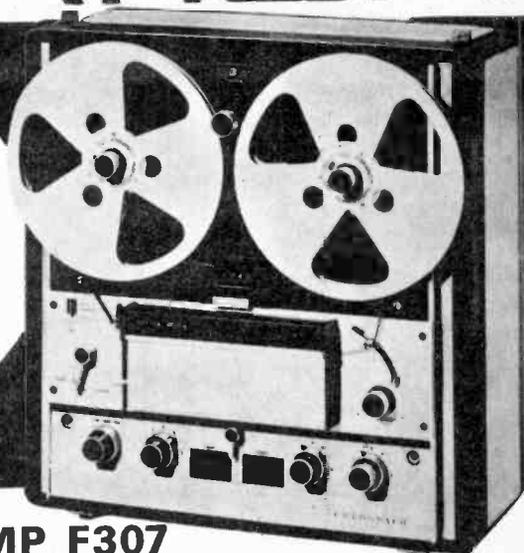

FERROGRAPH STEREO AMP F307

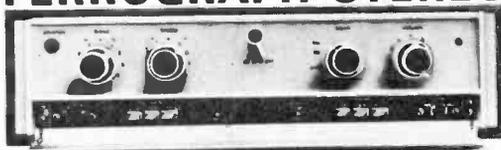

The famous 20 watt per channel amplifier from Britain's most respected manufacturer. A fabulous range of facilities rarely ever available in equipment at this price. Finished in wood veneered cabinet. Brand new with instructions and guarantee.

LIST PRICE £59

£47

CARRIAGE 10/-

AVAILABLE ON NO DEPOSIT INSTALMENT CREDIT.

SENT FREE!

THE KJ CATALOGUE
PACKED FULL OF ALL
THINGS AUDIO. BIG
MONEY SAVING OFFERS
FOR EVERYONE FROM A
REEL OF TAPE TO A
FERROGRAPH. OVER 200
ILLUSTRATED PAGES.



EXCLUSIVE TO

The **NATIONAL RS766 US 4 TRACK STEREO TAPE-DECK**. This superb unit contains pre-amplifiers suitable for feeding a Hi-Fi system or external amplifier ● Three tape speeds 7½, 3½, 1½ i.p.s. ● Takes up to 7" reels ● Freq. Response 30-18,000 cps at 7½ i.p.s. ● Wow and flutter less than 0.1% at 7½ i.p.s. ● 2 x Record level VU meters ● Monitoring through headphones ● DIN connection for record/playback ● Magnificent wood cabinet—Size 13½" (w) x 11" (h) x 5½" (d) ● Brand new with full instructions and Guarantee.

FANTASTIC
SPECIAL OFFER
SAVE £25

LIST PRICE £87/13/7

 PRICE
ONLY

59

GNS
CARRIAGE PAID

NO DEPOSIT INSTALMENT CREDIT AVAILABLE



PHILIPS STEREO TUNER BARGAINS!

GH 944 AM/FM STEREO TUNER
SAVE £23. LIST PRICE £72.18.4.
Receives LW/MW/SW/VHF, A.F.C. on
FM, Tuning meter. Sleek continental teak
veneer cabinet. Brand new and guaran-
teed.

CASH PRICE £49.18.0.

GH 927 FM STEREO TUNER
SAVE £15. LIST PRICE £44.19.6.
Receives VHF Stereo broadcasts, can
be used in conjunction with your
amplifier or tape recorder. A.F.C. on FM.
Tuning meter, and low line teak cabinet.
Brand new and guaranteed.

CASH PRICE £29.19.6.

AVAILABLE ON NO DEPOSIT
INSTALMENT CREDIT.

KJ ENTERPRISES (DEPT PWT11) 33 BRIDLE PATH WATFORD HERTS
Tel 25634 Showrooms 101 St ALBANS ROAD WATFORD (close to Watford Junction Station)

R.S.C HIGH FIDELITY STEREO 'PACKAGE' OFFERS

Four fully wired units ready to 'plug in.'
 ★ Super 30 Amplifier (15 + 15 watt) in veneered housing
 ★ Garrard SP25 mk II Turntable on Plinth with cover
 ★ Goldring CS90 Ceramic P.U. Cartridge with diamond stylus
 ★ Pair of Stanway II 'Speaker Units'
76 Gns. Carr. 30/-
 Special Total Price

Matching as recommended for optimum performance. Send S.A.E for coloured brochure showing other money-saving offers.

Package prices apply providing all individual units are purchased from any branch within 3 months. See leaflet.



ATTRACTIVE TEAK or AFORMOSIA VENEERED CABINETS and PLINTHS
 TERMS AVAILABLE ON ALL PACKAGE OFFERS

★ TA12 Amplifier 6.5 + 6.5 watt in veneered housing
 ★ Garrard SP25 mk II Player unit on Plinth
 ★ Goldring CS90 Ceramic P.U. Cartridge with diamond stylus
 ★ Pair of Dorchester Loudspeaker Units
54 Gns. Carr. 25/-
 Total Price

Or Deposit £6.19.6 and 9 monthly payments £6.4.6 (Total £57.6.0). Transparent Plastic Cover 3 gns. extra.

AS ABOVE BUT WITH GARRARD 3000 AUTOCHANGER AND SONOTONE 9TA Ceramic Cartridge in lieu of SP25 and CS90
49 Gns. Carr. 25/-

Or Deposit £6 and 9 monthly payments £5.14.0 (Total £57.6.0) Trans. Plastic cover 3 gns. extra.

LOW DEPOSIT CREDIT TERMS

Available on purchases over £8 KITS of parts excepted

INTEREST CHARGES REFUNDED

On Credit Sales settled in 3 months

AUDIOTRINE A55 HIGH QUALITY STEREO SYSTEM

5 + 5 WATT OUTPUT

GARRARD 5200 Changer with low mass pick-up arm and Stereo Cartridge. CONTROLS: TREBLE, BASS, VOLUME, STEREO BALANCE. Operation on standard 200-250v. A.C. mains. Output rating I.H.F.M.



Luxurious Teak Veneer Finished Cabinets. Transparent plastic (tinted) cover included for main unit. Silver finished fascia plate and matching control knobs.

PAIR OF LOUSPEAKER UNITS

incorporating high flux 8" x 5" speaker. Size approx. 13 x 7 1/4 x 8 1/2 ins.

Price complete **39 Gns.** Carr. 25/- ONLY

Terms: Deposit £5 and 9 monthly payments 4 gns (Total 44.18.0)

A REALLY SURPRISING STANDARD OF QUALITY IS OBTAINABLE FROM THIS COMPACT LOW PRICED SYSTEM

R.S.C G66 6+6 WATT high quality STEREO AMPLIFIER

Individual Ganged controls: Bass, Treble, Volume and Balance. Printed circuit construction employing 10 Transistors plus Diodes. Output rating I.H.F.M. Suitable for Crystal Pick-ups etc., and for loudspeaker output impedances of 3 to 15 ohms. For standard 200-250v. A.C. mains operation. Attractive silver finished metal fascia plate and matching control knobs.



Complete KIT of PARTS INCLUDING FULLY WIRED PRINTED CIRCUIT and comprehensive wiring diagram and instructions **£9.19.9**

Or FACTORY BUILT in Teak veneered cabinet. No leaflet supplied for this unit as illustrated **£12.10.0** carr. 7/9 Or dep. 37/6 and 9 monthly pymts. 29/6 (Total £15.3.0).

PACKAGE OFFER SAVE **£4** approx Above G66 assembled in cabinet.

plus pair DORCHESTER LOUSPEAKER UNITS **£27.10.0** Carr. £1 Or Deposit £5 and 9 monthly payments 57/8 (Total £30.17.6).

R.S.C. TFM1 SOLID STATE VHF/FM RADIO TUNER

★ High-sensitivity. ★ 200-250v. A.C. Mains operation. ★ Sharp A.M. Rejection ★ Drill-free reception. ★ Output ample for any amplifier (approx. 500 m.v.). ★ Output for feeding Stereo Multiplexer. ★ Tuner head using allison Planar Transistors. ★ Designed for standard 80 ohm co-axial input. Visually matching our Super 15 and 30 amplifiers and of the same high standard of performance and reliability. Printed circuitry. A quality product at considerably less than the cost of comparable units. FACTORY BUILT 18 gns. Or in Teak finished cabinet as illustrated **£1 gns.** Terms: Deposit **£6.1.0** and 9 monthly payments. 22s. Total **£24.18.0**. Stereo version. 23 1/2 gns. Carr. 10/6 extra.



HIGH FIDELITY LOUSPEAKER UNITS

Cabinets latest style Satin Teak or Afrormosia veneer. Acoustically lined or filled acoustic damping. Ported where appropriate. Credit terms available.

DORCHESTER Size 16 x 11 x 9in. appr. Range 45-15,000 c.p.s. Rating 8-10 watts. Fitted High flux 13 x 8in. Dual Conc speaker. Imp. 3 or 15 ohms. **9 Gns.** Carr. 7/6

STANWAY II Size 20 x 10 1/2 x 9 1/2in. appr. Rating 10 watts. Inc. 13 x 8in. speaker with highly flexible cone surround, long throw voice coil and 11,000 line magnet. High flux tweeter. Handsome Scandinavian design cabinet. Range 35-20,000 c.p.s. Imp. 15 ohms. Gives smooth realistic sound output. **16 Gns.** See top of page for illustration

R.S.C. TA12 MKIII 6.5 + 6.5 WATT STEREO AMPLIFIER FULLY TRANSISTORIZED, SOLID STATE CONSTRUCTION HIGH FIDELITY OUTPUT OF 6.5 WATTS PER CHANNEL

Designed for optimum performance with any crystal or ceramic Gram. P.U. cartridge, Radio tuner, Tape recorder, 'Mike' etc. ★ 3 separate switched input sockets on each channel ★ Separate Bass and Treble control ★ Slide switch for mono use ★ Speaker Output 3-15 ohms ★ For 200-250v. A.C. mains ★ Frequency Response 20-20,000 c.p.s. - 2dB ★ Harmonic Distortion 0.3% at 1,000 c.p.s. Hum and Noise - 70dB ★ Sensitivities (1) 50mV (2) 400mV (3) 100mV. Output rating I.H.F.M. ★ Handsome finish Facia plate and Knobs. Complete kit of parts with full wiring diagrams & instructions. Factory built with 12 months guarantee **17 gns.** or Deposit **£8.0.0** and 9 monthly pymts 39/- (Total £20.11.0). Or in Teak or Afrormosia Carr. 7/6 veneer housing **20 1/2 gns.** Dep. 3 Gns. and 9 monthly payments 47/- (Total £24.6.0).



R.S.C SUPER 30 Mk II HIGH FIDELITY STEREO AMPLIFIER

High Grade Components - Specifications - comparable with units costing considerably more.

TRANSISTORS 9 high quality types in each channel.

OUTPUT 10 Watts R.M.S. continuous into 15Ω (per channel). 15 Watts R.M.S. continuous into 3Ω.

INPUT SENSITIVITIES Mag. P.U. 4 mV. Ceramic P.U. 35 mV. Tape Amp. 400 mV. Aux. 100 mV. Mic. 5 mV. Tape Head 2.5mV.

FREQUENCY RESPONSE ± 2dB. 10-20,000 c.p.s.

TREBLE CONTROL +17 dB to -14 dB at 10 Kc/s.

BASS CONTROL +17 dB to -15 dB at 50 c/s.

HUM LEVEL -80 dB.

HARMONIC DISTORTION 0.1% at 10 watts 1,000 c.p.s.

Employing Twin Printed Circuits.

200/250v. A.C. mains operation.

CROSS TALK 52 dB at 1,000 c.p.s.



CONTROLS 5 Position Input Selector, Bass, Treble, Vol., Bal., Stereo/Mono Switch, Tape Monitor Switch, Mains Switch.

INPUT SOCKETS (1) P.U. (2) Tape Amp. (3) Radio, (4) Mic. or Tape Head. (Operation of Input Selector assures appropriate equalisation).

CHASSIS Strong Steel construction. Approx. 12 x 3 x 8in.

FACIA PLATE Attractive design in rigid plastic, silver background black lettering. Silver finish matching control knobs as available.

Eminently suitable for use with any make of pick-up or Mic. (Ceramic or Magnetic, Moving Coil, Ribbon or Crystal) currently available. Superb sound output quality can be obtained by use with first rate ancillary equipment.

COMPLETE KIT OF PARTS Point to point wiring diagrams and detailed instructions. **22 Gns.** Carr. 15/-

UNIT FACTORY BUILT **29 Gns.**

With 12 months guarantee. Or Deposit **£4** and 9 monthly payments 66/8 (Total £33.18.6 or in Teak or Afrormosia veneer housing Carr. 16/- Terms: Deposit **£4** and 9 monthly payments of 74/- (Total £37.6.0). Send S.A.E. for leaflet.

- BRADFORD 10 North Parade. (Half-day Wed.) Tel. 25349
- BLACKPOOL (Agent) O. & C. Electronics, 227 Church Street
- BIRMINGHAM 30/31 Gt. Western Arcade (Half-day Wed.) 021-236-1279
- DERBY 26 Osmaston Rd., The Spot (Half-day Wed.) Tel. 41361
- DARLINGTON 18 Priestgate (Half-day Wed.) Tel. 68043
- EDINBURGH 133 Leith St. (Half-day Wed.) Tel. Waverley 5766
- GLASGOW 326 Argyle St. (Half-day Tues.) Tel. CITY 4158
- HULL 91 Paragon Street (Half-day Thursday) Tel. 20505



MAIL ORDERS TO: Audio House, Henconner Lane, Leeds 13. No C.O.D. under £1. Terms C.W.O. or C.O.D. Postage 4/6 extra under £2. 5/9 extra under £5. Trade supplied. S.A.E. please with enquiries.

Branches open all day Sats. MAIL ORDERS MUST NOT BE SENT TO SHOPS

- 32 High Street (Half-day Thurs.) Tel. 56420
- LEICESTER 5-7 County (Mecca) Arcade, Briggate (Half-day Wed.) Tel. 28252
- LEEDS 73 Dale St. (Half-day Wed.) Tel. CENTRAL 3573
- LIVERPOOL 238 Edgware Road, W2 (Half-day Thurs.) Tel. PAD 1629
- LONDON 60A Oldham Street (Half-day Wed.) Tel. CENTRAL 2778
- MANCHESTER 106 Newport Rd. (Half-day Wed.) Tel. 47096
- MIDDLESBROUGH 41 Blackett Street (Opp Fenwicks Store) (Half-day Wed.) Tel. 21469
- NEWCASTLE UPON TYNE 13 Exchange Street (Castle Market Bldgs.) (Half-day Thursday) Tel. 20716
- SHEFFIELD

'YORK' HIGH-FIDELITY 3 SPEAKER SYSTEM

- ★ Moderate size only 25 x 14 x 10in. COMPLETE KIT 20 Gns
- ★ Response 30-20,000 c.p.s. Impedance 15 ohms
- ★ Performance comparable with units costing considerably more. Consists of (1) 12in. 15 watt Bass unit with cast chassis, Roll rubber cone surround for ultra low resonance, and ceramic magnet. (2) 3-way quarter section series cross-over system. (3) 8 x 5in. high flux middle range speaker. (4) High efficiency tweeter. (5) Appropriate quantity acoustic damping material (6) Teak veneered cabinet. (7) Circuit and full instructions. Terms: Dep. 3 Gns. and 9 monthly payments 45/6 (Total 22 1/2 Gns.). DEMONSTRATIONS AT ALL BRANCHES

AUDIOTRINE HI-FI SPEAKER SYSTEMS

Consisting of matched 12in. 11,000 line 15 Watt 15 ohm high quality speaker, cross-over unit and tweeter. Smooth response and extended frequency range ensure surprisingly realistic reproduction. **£5.15.0**

OR SENIOR 15 WATT INC. HF126 15,000 LINE SPEAKER £8.15.0. Carr. 5/9



AUDIOTRINE HIGH FIDELITY LOUSPEAKERS

Heavy construction. Latest high efficiency ceramic magnets. Treated Cone surround. "D" indicates Tweeter Cone providing extended frequency range up to 16,000 c.p.s. "L" indicates Roll Rubber cone surround. Impedance 3 or 8-15 ohms. Please state choice. Exceptional performance at low cost.

HF801D	8" SW	54/3	HF120D	12" 15W	89/9
HF102D	10" 10W	67/11	HF128	12" 15W	25.5.0
HF120	12" 16W	79/9	HF128D	12" 15W	25.15.0

HI-FI SPEAKER ENCLOSURES

Teak or Afrormosia veneer finish. Modern design. Acoustically lined. All sizes approx. Carr. 6/- per enclosure
JES Size 16 x 11 x 9in. Pressurised. Gives pleasing results with any 8in. HI-FI speaker. **£4.14.6**
SES For optimum performance with any 8in. HI-FI speaker. Size 22 x 15 x 9in. Forted **£5.15.0**
ES10 For outstanding results. ES12 For exdnt prfnce with 12in HI-FI speaker and Tweeter. **£6.19.9**
 Size 24x15x10in. P'd. **£5.19.9** Size 25 x 16 x 10 1/2in.



RECORD PLAYING UNITS

Money saving units. Mounted on Plinth. Supplied with transparent plastic cover. Ready to plug into Amplifier or Tape recorder.

RP2C Garrard SP25 Mk II (with heavy turntable) fitted Goldring CS90 high compliance ceramic Stereo/Mcno cartridge with diamond stylus. Carr. 9/6 **£24.12.6**

RP5C Garrard 2025 Auto Unit fitted Garrard GC8 23 Stereo Cartridge with diamond tip. Carr. 9/6 **15 Gns.**

Other types available with Magnetic cartridges and with alternative design plinths.

R.S.C. PLINTHS

Superior Solid Natural Wood Construction for Record Playing units, cut for Garrard 1025, 2025, 3000, AT60, SP25 etc. **3 gns. 6 gns. Carr. Free**



AVAILABLE WITH TRANSPARENT PLASTIC COVER Carr. Free

LEADING MAKES HI-FI EQUIPMENT AT CLEARANCE PRICES
 Available at branches only

LINEAR L10 HIGH FIDELITY 10W AMPLIFIER 10 Gns.

with separate Pre-amp Magnetic P.U. matching. To clear

SUPER 15 HIGH FIDELITY SOLID STATE AMPLIFIER

Approx. as Super 30 but single channel. Complete kit with full constructional details and point to point wiring diagrams. **12 1/2 gns.** Carr. 12/6

OR FACTORY BUILT 15 Gns. Carr. 12/6. Terms: Deposit 4 Gns. and 9 monthly payments 31/1 (Total £13.9) Available in Teak or Afrormosia veneered housing. 19Gns.

R.S.C. BATTERY/MAINS CONVERSION UNITS

TYPE BM1 An all-dry battery eliminator. Size 6 1/2 x 4 1/2 in. approx. Completely replaces batteries supplying 1.5v. and 90v. where A.C. mains 200/250v. 50c/s is available. Complete kit with diagram 59/9 or assembled 69/9.



OR FACTORY BUILT WITH 12 MONTHS' GUARANTEE **£33.19.9**

R.S.C. TA6 6 Watt HI-FI SOLID STATE AMPLIFIER

200-250v. AC mains operated. Frequency Response 30-20,000 c.p.s. -2dB. Harmonic Distortion 0.3% at 1,000 c.p.s. Separate Bass and Treble. 'hit' and 'cut' controls. 3 input sockets for Mike, Gram, Radio or Tape. Input selector switch. Output for 3-15 ohm spkrs. Max. sensitivity 5mV. Output rating I.H.F.M. Fully enclosed enamelled case, 9 1/2 x 2 1/2 x 4 1/2 in. Attractive brushed silver finish face plate 10 1/2 x 3 1/2 in. and matching knobs. Complete kit of parts with full wiring diagrams and instructions. **7 Gns.** Carr. 7/6

OR FACTORY BUILT WITH 12 MONTHS' GUARANTEE **£33.19.9**

R.S.C. A11 HI-FI 12-14 WATT AMPLIFIER

PUSH-PULL ULTRA LINEAR OUTPUT "BUILT-IN" TONE CONTROL PRE-AMP. Two input sockets with mixing facilities High sensitivity, 5 valves. Independent Bass and treble controls. Frequency response ±3dB 30-20,000 c/s. Hum level -60dB. Sensitivity 40 millivolts. For Crystal or Ceramic P.U.s. High Impedance "mikes". For Musical Instruments etc. Std. A.C. mains. For 3 or 15 ohm spkrs. SAE for leaflet. Complete kit. Full instructions and point-to-point wiring diagrams. Carr. 11/6. Twin handled metal cover 35/-. Price Factory built 14 gns. or Deposit £3 and 9 monthly payments of 31/6 (Total £17.8.9). RSC A11 TRANSFORMERISED VERSION of above complete kit 9 Gns. (Assembled 13 Gns.).



R.S.C. COLUMN SPEAKERS

ALL TYPES 15 OHMS COVERED IN REXINE/VYNAIR, IDEAL FOR VOCALISTS AND PUBLIC ADDRESS.

TYPE C4100 also suitable for Bass Guitar or Electronic Organ.
TYPE C485 25-30 WATTS
 Fitted four 8" high flux 8 watt speakers.
 Overall size approx 48 x 10 x 5 in. Carr. 10/-
 Terms: Dep. £3 and 9 monthly payments 35/6 (Total £18-19-8) **16 Gns.**
TYPE C4100 100 watts inc. four 12" 50 watt speakers for conservative rating. Extra heavy construction. Acoustically filled and pressurised. Terms: Deposit £8 and 9 monthly payments 25-10-6 (Total £57-14-6) **48 Gns.** Carr. 21

30 WATT HI-FI AMPLIFIER

FOR GUITAR, VOCAL OR INSTRUMENTAL GROUP.
 A 2 or 4 input. 2 vol. control HI-FI unit with Separate Bass and Treble controls. Current valves. Peak output rating. Strong Rexine covered cabinet with handles. Attractive black/gold P.V.A. fascia. Neon indicator. For 200-250v. A.C. mains. For 3 or 15 ohm speakers. Send S.A.E. for leaflet. Terms: Deposit £3.14.0 and 9 monthly payments of 42/- (Total £22.12.0) Carr. 12/6 **19 Gns.**



HIGH QUALITY LOUSPEAKER UNITS

IN TEAK OR AFRORMOSIA VENEERED CABINETS

L125 50 WATT
 Two tone Rexine and vynair finish. Fitted pair of 12" 60 watt high flux speakers for conservative rating. Impedance 8-15 ohms. **28 Gns.**
L18 13" x 8" 10 WATT
 10,000 lines 3 or 15 ohms. State Impedance required. **15 ohms. Carr. 8/9**
5 Gns. £8-19-9
 Carr. 7/6

R.S.C. BASS REGENT 50 WATT AMPLIFIER

A powerful high quality all-purpose unit for lead, rhythm, bass guitar, vocalists, gram, radio, tape, Peak Output rating. Loudspeaker unit horizontal or vertical mounting. **55 Gns.**
 ★ Two extra heavy duty 12in. Loudspeakers. Carr. 30/-
 ★ Four Jack inputs and two Volume Controls for simultaneous use of up to four pick-ups or "mikes". Bass and Treble controls. Deposit £13.4.9 and 9 monthly payments of £5.11.9 (Total 60 1/2 gns.) Send S.A.E. for leaflet.



FAL PHASE 50 AMPLIFIER 50 Watt

Solid state 3 Separately controlled inputs Ind. Bass and Treble Controls. Output for Speaker/s 3-30 ohms. Size 17" x 7" x 7 1/2" 200-250 A.C. mains. Peak Output rating. For fuller details of Phase 29 Gns. Carr. Free 50 see Manufacturers advert. page 578 or send S.A.E. for leaflets.

FAL PHASE 100 AMPLIFIER

100 Watt Solid State 4 Separately controlled inputs Plus master volume Control. Ind. Bass and Treble Control. Output for speaker/s 3-30 ohms. Protective circuit to guard against damage from accidental shorts I.H.F.M. Output rating **59 Gns.**

FANE ULTRA HIGH POWER LOUSPEAKERS

All power ratings are R.M.S. continuous 3 years' guarantee. High flux ceramic magnets. Veneer cast chassis. All carr. free.

'POP' 100
 18" 100 Watt
 14,500 gauss
 8/150
21 gns.
 Dep: £6 and 9 monthly payments 22 (Total £24).
'POP' 60
 15" 60 Watt
 14,000 gauss
 8/150
£12.18.0.
 Dep: 3 gns. and 9 monthly payments 22/6 (Total £15.1.8)
'POP' 50
 12" 50 Watt
 10,000 gauss
10 GNS. 150
 Dep. £2 and 9 monthly payments 22/6 (Total £12.2.6)
 Pair suitable all purposes

FANE LOUSPEAKERS

'POP' 30C
 12in. 25 WATT
 Dual Cone 15Ω (For uses other than Bass Guitar or Elect. Organ)
£5-19-9 Carr. free
 or Dep. £1 and 9 monthly payments 13/- (Total £6.17.0).

R.S.C. A10 30 WATT ULTRA LINEAR HI-FI AMPLIFIER

Highly sensitive. Push-Pull high output, with Pre-amp/Tone Control Stages. Hum level-70dB. Frequency response ±3dB 30-20,000 c/s. All high grade components. Valves EF86, EF85, ECC83, 807, 807, GZ54. Separate Bass and Treble Controls. Sensitivity 30 millivolts. Suitable for High Impedance microphones. Designed for Clubs, Schools, Theatres, Dance Halls or Outdoor Functions, etc. For use with Electronic Organ, Guitar, String Bass, etc. Gram, Radio or Tape. Reserve L.T. and H.T. for Radio Tuner. Two inputs with associated volume controls so that two separate inputs such as Gram and "Mikes" can be mixed. 200-250 v. 50 c/s A.C. mains. For 3 and 15 ohm speakers. Complete Kit of parts with point to point wiring diagram and instructions. Twin handled perforated cover 35/-.

OR factory built with EL34 output valves and 12 months' guarantee for 18 Gns. Carr. 12/6
TERMS: Deposit £3.0.0 and 9 monthly payments of £2.8 (Total £21.0.0). Send S.A.E. for leaflet. **15 Gns.**

RSC TRANSFORMERS AND L.F. CHOKES

FULLY GUARANTEED. Impregnated and Interleaved where necessary


Primarys 200-250v. 50c/s. Screened		FILAMENT or TRANSFORMER POWER PACK	
MIDGET CLAMPED TYPE 2 1/2 x 2 1/2 in.		Types 6.3v. 1.5a. 8/9; 6.3v. 2a. 9/9; 6.3v. 3a. 13/9;	
250v., 60mA, 6.3v. 2a.	17/11	6.3v. 6a. 22/9; 12v. 1a. 9/11; 12v. 3a. or 24v. 1.5a. 28/9; 0.9 13v. 1.5a. 18/11; 0.12-25-42v. 2a. 31/9	
FULLY SHEATHED UPRIGHT MOUNTING		CHARGER TRANSFORMERS 0.9-15v. 1.1a. 18/9;	
250-0-250v. 60mA, 6.3v. 2a., 0-5-6.3v. 2a.	24/9	24a. 19/11; 3a. 21/11; 6a. 25/11; 6a. 29/9; 8a. 36/9;	
250-0-250v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a.	29/9	AUTO (Step Up/step Down) TRANSFORMERS	
300-0-300v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a.	39/9	150 watts, 34 1/8 250 watts 50, 80, 500 watts 105/-	
300-0-300v. 130mA, 6.3v. 4a., c.t., 6.3v. 1a.	47/11	OUTPUT TRANSFORMERS	
For Mullard 10A Amplifier	47/11	Standard Pentode 5,000 Ω or 7,000 Ω to 3 Ω	8/9
350-0-350v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a.	39/9	Push-Pull 8 watts EL84 to 3 Ω or 15 Ω	14/9
350-0-350v. 150mA, 6.3v. 4a., 0-5-6.3v. 3a.	47/9	Push-Pull 10 watts 6V6, ECL86 to 3, 5, 8 or 15 Ω	24/9
425-0-425v. 200mA, 6.3v. 4a., c.t., 5v. 3a.	89/9	Push-Pull EL84 to 3 or 15 Ω 10-12 watts	28/9
450-0-450v. 200mA, 6.3v. 4a., c.t., 6.3v. 3a., 5v. 3a.	93/9	Push-Pull Ultra Linear for Mullard 510, etc.	39/9
460-0-460v. 250mA, 6.3v. 4a., c.t., 5v. 3a.	99/9	Push-Pull 15-18 watts, sectionally wound G1G, KT66, etc., for 3 or 15 Ω	35/9
TOP SHEATHED DROP-THERM TYPE		Push-Pull 20 watt high quality sectionally wound EL84, 6L6, KT66 etc. to 3 or 15 Ω	59/9
250-0-250v. 100mA, 6.3v. 2a., 0-5-6.3v. 2a.	27/9	SMOOTHING CHOKES 100mA, 7-10H. 250 Ω	
250-0-250v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a.	39/9	12/9; 100mA, 10H. 200 Ω 10/9; 80mA, 10H. 350 Ω 9/9; 50mA, 10H, 400 Ω 7/11.	
300-0-300v. 150mA, 6.3v. 4a., 0-5-6.3v. 3a.	39/9	SELENIUM RECTIFIERS F. W. (Bridged)	
Suitable for Mullard 510 Amplifier	46/9	All 12v. D.G. output. Max. A.C. input 18v.	
350-0-350v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a.	39/9	1a. 4/3. 2a. 7/11. 3a. 9/9. 4a. 12/9. 6a. 15/9.	
350-0-350v. 150mA, 6.3v. 4a., 0-5-6.3v. 3a.	46/11		

LOOK!

PRACTICAL!

VISUAL!

EXCITING!

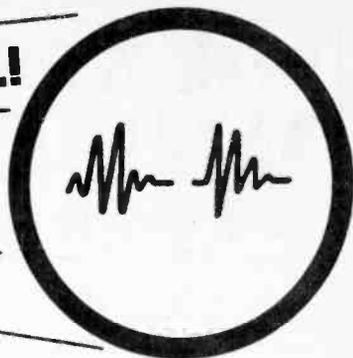


a new 4-way method of mastering

ELECTRONICS

by doing — and — seeing . . .


1 ▶ OWN and HANDLE a

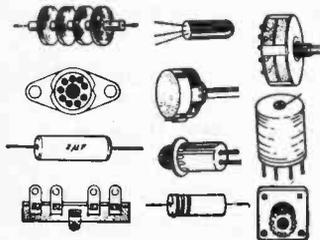complete range of present-day **ELECTRONIC PARTS and COMPONENTS**




2 ▶ BUILD and USE

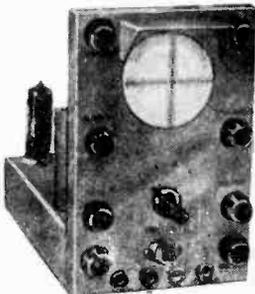a modern and professional **CATHODE RAY OSCILLOSCOPE**



3 ▶ READ and DRAW and

UNDERSTAND CIRCUIT DIAGRAMS

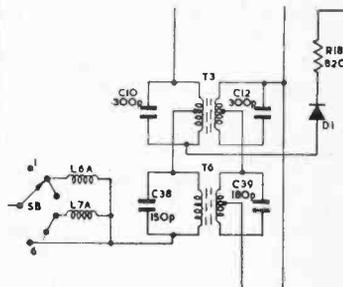

4 ▶ CARRY OUT OVER **40** EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS AND SEE HOW THEY WORK . . . INCLUDING . . .

- VALVE EXPERIMENTS
- TRANSISTOR EXPERIMENTS
- AMPLIFIERS
- OSCILLATORS
- SIGNAL TRACER
- PHOTO ELECTRIC CIRCUIT
- COMPUTER CIRCUIT
- BASIC RADIO RECEIVER
- ELECTRONIC SWITCH
- SIMPLE TRANSMITTER
- A.C. EXPERIMENTS
- D.C. EXPERIMENTS
- SIMPLE COUNTER
- TIME DELAY CIRCUIT
- SERVICING PROCEDURES

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of Electronic equipment, Radio and TV receivers, etc.

FREE POST NOW
for
BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO SCHOOL, READING, BERKS.** Please send your free Brochure, without obligation, to: *we do not employ representatives*

NAME BLOCK CAPS

ADDRESS PLEASE P.W. 11

PRACTICAL WIRELESS

VOL 46 NO 7

Issue 765

NOVEMBER 1970

TOPIC OF THE MONTH

Keep it Clean, Lads

SOMEWHAT belatedly, everyone is becoming concerned about pollution, and 'Conservation' is the new 'in' word. The atmosphere is being poisoned by industry and the internal combustion engine, the seas and rivers are being polluted by industrial waste, foodstuffs and livestock are being contaminated by insecticides and other toxics, the countryside is being despoiled by pylons, roadworks and lanes and woods being used as dumping tips for junk. The list is long and depressing, not only for homo sapiens but for the rest of the animal world too.

Although this is not the place to set up a platform for action against such obvious causes of pollution, it is worth remembering that we (meaning radio enthusiasts, broadcasters and users of electronic equipment) are by no means absolved from blame in adding certain contributions to the overall mess.

Relative to transmitting, how about all those international shortwave stations who have (with a few notable exceptions) evolved from goodwill broadcasters to blatant provocative propagation machines? How about those who retaliate by swamping the bands with jammers? How about pirate broadcasters and pirate amateur stations? These are only a few activities which can be classified as pollution of the airways.

Even the humble home constructor may (usually unconsciously) add his contribution. We like to think that readers of P.W. are not numbered among those who invade the peace of other individuals by playing radios or cassette tape recorders at full and gloriously distorted volume in public places, but a few may be unsuspectingly annoying neighbours by the incredible noises which emanate from the shed where a new piece of gear is being tested. Those without sheds to work in should sometimes pause to think if they are not causing domestic pollution by using the loudspeaker to listen to DX in the small hours, spilling solder on the Axminster, burning or drilling holes in the kitchen table, scattering the floor with dud capacitors and other such unsocial activities.

On the major scene, pollution can be nailed to the masthead of Irresponsibility. On the domestic front, perhaps Thoughtlessness is a fairer term. So, however ardent you may be in your chosen hobby, spare a thought for others and keep it clean, lads.

W. N. STEVENS—*Editor.*

**DECEMBER ISSUE WILL BE PUBLISHED
ON NOVEMBER 6**

NEWS AND COMMENT

Leader	515
News . . . News . . . News . . .	516
Practically Wireless <i>by Henry</i>	546
Showtime 1970	560
On the Short Waves <i>by Malcolm Connah and David Gibson, G3JDG</i>	565
MW Column <i>by Charles Molloy</i>	573

CONSTRUCTIONAL

P.W. 25/25 Stereo Amplifier, Part 1 <i>by F. C. Judd</i>	531
Tuning Facilitated <i>by F. G. Rayer</i>	540
I.C. of the Month (Mullard TAA320 Bi-fet Preamp) <i>by L. A. J. Ireland</i>	544
Capacitance and Resistance Bridge <i>by John Thornton Lawrence</i>	548
S.W. Transistor R.F. Preamp <i>by P. Cairns, G3ISP</i>	552
Vibrasonic 25-50 Guitar Amplifier, Part 3 <i>by F. C. Judd G2BCX</i>	555
Take 20—General Purpose Preamplifier <i>by Julian Anderson</i>	589
500kHz Crystal Calibrator <i>by R. W. Bunney</i>	570

SPECIAL FEATURES

Audio Fair Preview
by David Cameron 519

Win a DECCA 3000 Hi-Fi System
—Full details on page 525

©IPC Magazines Limited 1969. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected, and reproduction or imitations in whole or in part are expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices are those current as we go to press. All correspondence intended for the Editor should be addressed to Fleetway House, Farringdon Street, London, E.C.4. Address correspondence regarding advertisements to Advertisement Manager, Fleetway House, Farringdon Street, London, E.C.4. Orders for back numbers should be addressed to IPC Magazines Ltd., Back Numbers Department, Carlton House, Gt. Queen Street, London W.C.2.

NEWS... NEWS... NEWS...

Dolby and Kellar



One of the drawbacks of obtaining quality reproduction from the tape cassette has been the problem of background noise. Tape hiss increases as the tape speed is lowered and the track width decreased.

The Dolby system of noise reduction enables these problems to be overcome and full use to be made of the features of the tape cassette. By reducing the level of the background hiss by 10dB, the Dolby system gives the opportunity to use the wide frequency and dynamic range necessary to provide the serious listener with high quality reproduction of music.

The Dolby system works by boosting the strength of the signal (the subject being recorded) whenever it falls below a predetermined level, thus increasing the signal-to-noise ratio of the master tape. During playback of the master tape the circuits that increased the low level signals during the recording now lower them back to the correct value. As they do so, they automatically reduce the system background noise.

The Kellar DTA 50 (illustrated) uses the Dolby 'B' system. It has a continuous power output of 25W per channel, input for magnetic pickup cartridges or radio tuner, wide range tone controls with 12dB of boost and cut at 100Hz and 10kHz, a noise level of -70dB and the facility of recording from any source, including microphone, using the Dolby 'B' noise reduction system during the recording and replay process. The DTA 50 also gives the best possible reproduction from pre-recorded tape cassettes whether Dolby processed or not. Price of the DTA 50 is £150 including purchase tax. *Kellar Electronics Limited, Maryland Works, 9 Brydges Road, Stratford, London, E.15.*

Cassette case

The Bib Division of Multicore Solders Limited announce the introduction of their new Bib Cassette Case which has been specially designed to hold up to 12 tape cassettes in their containers in a way that they can be easily withdrawn and replaced. This case is a neat method of storing and carrying cassettes which is covered in black deer-skin PVC. The folding lid is held fast by two button fasteners and the overall appearance is most attractive. Price 17s. 7d., plus 7s. 3d. Purchase Tax.



Martin Audiokits

It is announced that after a period of reorganisation, these constructional units for building a high fidelity amplifier and f.m. tuner systems are again in production.


Martin Audiokits were probably the very first to exploit the advantages of using transistorised modular units for the constructor to assemble and they quickly gained a reputation for reliability, good performance and value.

The range is now to be extended and updated but owners of existing equipment will still be able to add any new items to what they already have. Full servicing facilities are available and enquiries should be addressed to *Martin Audiokits, 154 High Street, Brentford, Middlesex.* (Telephone 01-560 1161) which is now a division of *Louis and Lewis (Electronics) Ltd., The Boat House, 15 Thames Street, Hampton, Middlesex.*


The whole truth

Rank Audio Visual Ltd. are marketing in the U.K. the Empire Scientific Corporation (U.S.A.) range of stereo magnetic cartridges under the trade name of 'Empire'. These cartridges are manufactured in the U.S.A. and the range includes models for high-performance playback systems. In the popular 808 series for automatic record changers, there are two models the 808 at £9 and the 808E at £12 17s. The de-luxe 808 series includes four models ranging in price and specification.

The 999VE has a frequency response (within ± 2.2 dB) from 20-20,000Hz, elliptical stylus and a recommended tracking force of 0.5 to 1.5 grams. This retails at £44 10s. The 1000ZE (stereo calibration standard) is individually calibrated to have a flat frequency response within ± 1 dB from 20-20,000Hz (overall frequency response 4-40,000Hz) and has the ability to track effectively at stylus forces as low as 0.1 gram. The price is £63. For further technical details write to: *Rank Audio Visual Ltd., Great West Road, Brentwood, Middlesex.*

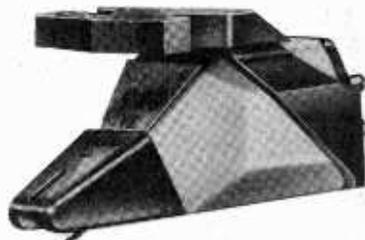

THE 999VE CARTRIDGE

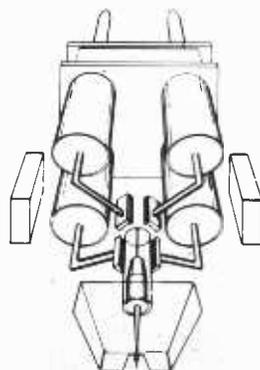

EXPLODED VIEW OF THE EMPIRE CARTRIDGE

Slant Polarization

At certain of the BBC's local radio stations, where it is feasible to do so, slant polarization will be used instead of the horizontal polarization which has been used previously for all the v.h.f. radio services. Slant polarization, with the electric field at 45° to the horizontal and perpendicular to the direction of propagation, will improve v.h.f. reception in cars and with portable receivers used in the open air.


Vertical and horizontal aeri- als are equally suitable for receiving signals with slant polarization and satisfactory reception, with the vertical rod aeri- als used on many cars and portable v.h.f. receivers, will be better maintained toward the limit of the nominal service area. The effect is equivalent to the use of 6dB or more additional transmitter power, thus doubling the signal strength. There will be substantially no effect on reception in the home with receivers using built-in aeri- als, because the passage of a signal through a building tends to mix the polarization. On an outdoor horizontal aerial at roof level, slant polarization will give slightly less pick-up (about 70 per cent or -3dB).

The Invaders



Shown for the first time on their stand at the recent "R.S.G.B." Exhibition was the Adcola 'Invader' soldering iron. The instrument is based on the Adcola thermally controlled heating element. The handle is made from a relatively new plastic which does not retain heat, so keeping the handle always cool. A handy hook is also another feature of the handle design. The heating element can be removed should it become damaged and replaced within 90 seconds. Seven stock voltages are available from 6V to 250V and in temperature ranges of 250°C-440°C. Price is 37s. plus 1s. p.p. *Adcola Products Limited, Adcola House, Gauden Road, London, S.W.4.*

Motorola Design Note

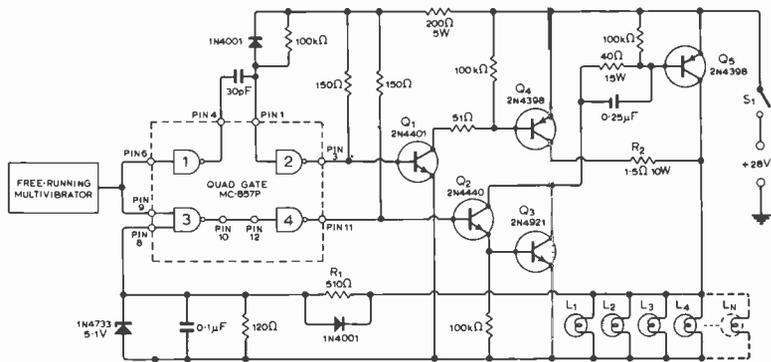

The commonest causes of failure in control circuits used to switch flashing indicator lamps on and off are overloads due to cold lamp filaments during starting, current surges during starting due to the charging of associated capacitive loads, and short-circuited lamps. Such failures can be eliminated with the use of this circuit.

The circuit holds the lamp driver transistor Q5 cut off until the lamps have heated enough so that the 28V supply voltage will not cause excessive current. When switch S1 is closed, the free-running multivibrator applies a square wave with a 1 sec period and a 50 per cent duty cycle to the quad gate pins 9 and 6. Gates 1 and 2 comprise a monostable multivibrator; when pin 6 goes high (+5V), the output of gate 2 at pin 3 will go high for about 75 millise- c, then return to the low state. When the output of gate 2 is high, Q1 and Q4 turn on, supplying current to the lamps through resistor R2. If the lamp circuit is not short-circuited, the voltage across the lamps continues rising as the filaments heat

and their resistances increase. When the lamp voltage increases to between 7.5 and 10.0V, gate 3 is driven on through R1, and the output of gate 4 goes high. This action turns Q2, Q3 and Q5 on, applying the full supply voltage to the lamps in 0.5 sec pulses, as triggered by the multivibrator, and causing the lamp to flash. If the lamp circuit is shorted, gate 3 will not be turned on to turn on Q5. Instead, Q4 will continue to cycle, sending a current pulse of 75 millise- c duration once each second through the short-circuit. The maximum pulse current is limited to about 20A by R2. Normal 1 sec flashing will be resumed when the short-circuit is removed. Second and subsequent pulses will not be delayed in supplying full power, because the lamp filaments will have been preheated by the first pulse.

The advantage of this circuit is that it automatically resets to normal operation once an overload or a short-circuit fault has been cleared. This aids in fault finding and maintenance and ensures that intermittent faults do not result in a disruption of operation.

Catalogue

A useful catalogue for the home constructor, the Electrovalue catalogue contains everything from aeri- als to washers. Also, it is a useful reference for semiconductor characteristics and connections. The catalogue retails at 2s post free from: *Electrovalue, 28 St Judes Road, Englefield Green, Egham, Surrey.*

Lothians Society

Meetings of the Lothians Radio Society are now held at Theatre Workshop, 66 Hanover Street, on the 2nd and 4th Thursdays of each month. The Society holds lectures, films, visits, etc. This year, it is hoped, talks will be included on neon signs, colour TV, and radar. *D. E. Ferguson, 1 Braidburn Crescent, Edinburgh, EH10.6EL.*

No-fuss stereo. For the very fussy.



Last year we introduced something new to the stereo scene: Deccasound simplicity.

Our new systems made it possible for *anyone* to enjoy good stereo sound – simply by plugging in and adjusting a few controls.

We made four Deccasound systems in all – two of 6 watts and two of 12, each with perfectly matched playing deck, amplifier and two speakers (plus FM Tuner and stereo decoder as optional extras).

So successful was our idea, that we've since made a console version, with an AM/FM tuner built in.

And this year we're extending the principle to hi-fi, with the result you see below.

Our Deccasound 3000 system gives you an impressive choice of decks, an amplifier of a hairy 30 watts per channel, plus two muscular speakers.

Plus a choice of FM or AM/FM Tuners, as an optional extra.

All perfectly matched for sound, as well as for appearance, to give you a lot of very high fidelity – without expertise or fuss.

See it at your Hi-fi stockist, or drop us a line for full details, Decca, Ingate Place, Queenstown Road, London, SW8.

DECCASOUND

No-fuss stereo. For the very fussy.

Now up to 60 watts. And looking good.

2 speaker enclosures each with 12" bass unit plus 2 x 1" tweeters. dimensions 27" x 18" x 14"

Deccasound 3000 stereo amplifier. Output 30 watts per channel; frequency response 20Hz to 30KHz; Full range of ancillary controls and input and output sockets.



Choice of decks; latest Garrard AP76 with special refinements to obtain best results from Decca C4E magnetic cartridge or BSR MA 75 using a Decca Deram cartridge.

AUDIO FAIR

PREVIEW



by David Cameron

This will be the second of the new-style Audio Fairs to be held at Olympia, London, occupying some 100,000 square feet of the National Hall and gallery. The organisers hope that it will be the most comprehensive hi-fi exhibition ever launched and they have certainly made great efforts to draw in the audio crowds. Most of the audio exhibitors (there are record companies and photographic exhibitors, too) will be running demonstrations in studios similar to those used last year but with various improvements—notably much better ventilation and construction materials more sympathetic audiowise. The International Audio Festival and Fair will be open from 10 a.m. to 9 p.m. each day from Tuesday, October 20th to Saturday, October 24th inclusive, with a special day (October 19th) set aside for press and trade only.

One of the attractions this year will be a series of lectures and presentations which will be running at 2, 4, 6 and 8 p.m. on each day (October 20–24th inc.) in a lounge seating about 400. Some of the highlights will be "Progression of Electric Music Synthesisers" by Dr. R. A. Moog; "How good is your Gramophone" by John Borwick; Sir Arthur Bliss discussing his new recording of Beethoven's Pastoral Symphony; "Types of Recorded Sound Quality" by John Crabbe; on Saturday at 8 p.m.—a Jazz Festival. There will also be a continuous film show running from noon to 6 p.m.

If you want to attend any of these activities, tickets will be available at the Olympia main entrance. No charge is made but owing to the limited seating accommodation seats for all performances must be obtained by ticket only. There will also be programmes for the entire 20 events—again available at the main entrance to the exhibition.

Owing to having to obtain information well before the opening of the exhibition, it has not been possible to provide details of what every audio exhibitor is showing. However, in the pages that follow, you will find the highlights from the exhibits of companies able to supply us with information before going to press. There may well, however, be last minute surprises. Companies are listed alphabetically with the stand number in parenthesis.

ALBA (47)

Newcomers to the Audio Fair, but by no means newcomers to the world of sound equipment, Alba have been around for 53 years, having started in the sound business in the days of the acoustic gramophone. Concentrating on the low- and medium-price range, they will be showing a number of interesting items.

In the lower price bracket is the 442 portable stereo "all-round-the-house" player, the second speaker fitting into the lid for transportation; price is £39 19s.

The audio units start off with the UA 552 which comprises a combined amplifier/record player (with Garrard C110 autochanger) feeding 3W r.m.s. per channel into two matched speaker units. Complete, the price is £45 10s. Another version, the UA662, sells at £59 19s. and features a 5W per channel amplifier, the latest BSR C137 autochanger with aueing device, and a pair of speaker enclosures each housing a 6½in. and 3in. unit. DIN sockets for radio unput and tape connections are fitted.

Another product is the UA 400 tuner-amplifier, covering l.w., m.w. and f.m. band, with switchable a.f.c. and incorporating a Garrard 2025TC autochanger. Price is £57 2s. plus £6 11s. extra if a decoder is required. Matching pair of speakers (UA500) are available at £17 18s. the pair.

The highlight of the Alba exhibit is their UA100 Series. The UA100 is a tuner-amplifier employing 30 transistors and covering l.w., m.w., s.w. and v.h.l./f.m. bands, and providing 15+15W r.m.s. at less than 0.3% distortion. Specification 2μV sensitivity for 500mW (f.m.), amplifier figures include frequency response 20Hz to 20kHz ±2dB (excluding bass compensated volume control), bass control ±12dB at 70Hz, treble control ±12dB at 12kHz, feedback factor of main amplifiers 40dB. Features include stereo beacon, switchable a.f.c., quiet tuning control. Input sockets are provided for pickup and tape and a tape output socket is fitted. Price, £65 8s. (decoder £6 11s. extra).

The second unit is the UA200 record player deck which incorporates a Garrard SP25 (2) player with high compliance magnetic cartridge, cueing device, wow less than 0.2% r.m.s. and flutter less than 0.08% r.m.s. Price is £30 10s. To match these units are the UA300 speaker enclosures, each housing a 6½in. main unit and a 3in. tweeter, which sell at £24 the pair.

There is also a new amplifier (UA700) which can be used as an alternative to the UA100. It employs 20 transistors, provides 15+15W output and sells at £34 10s.

ARMSTRONG (35)

We have no news of any brand new models, but Armstrong will be showing their well established and successful Series 500 range of amplifiers, tuner and tuner-amplifiers. A new demonstration of music with matching commentary has been specially prepared for this event and will be played through the 526 a.m.-f.m. stereo tuner-amplifier. This unit has been chosen as it represents the complete range, having the same performance and specification as the separate 50W amplifier and tuners. Figures include (f.m. tuner section) 5μV sensitivity for 30dB signal/noise ratio at 75kHz deviation, full limiting at 5μV, i.f. rejection 90dB, (decoder) 30-15,000Hz ±1dB frequency response, 30dB at 1kHz channel separation, hum and noise 60dB below full output, 40dB suppression (38kHz). Features include switchable loudness control (reduces overall gain by 20dB giving range of volume control for low level listening while at the same time increasing bass and treble), quieting control to suppress interstation noise while tuning on f.m., rumble filter, two treble filters (1, providing 3dB attenuation at 6.5kHz increasing to 25dB at 10kHz; 2, providing 3dB attenuation at 4.5kHz increasing very steeply to 40dB at 9kHz), tape monitor sockets, inputs for pickup 1, pickup 2, tape playback and radio, tuning meter with centre zero tuning on f.m. The 526 sells at £104 14s. 3d.

AEG (23)

The full range of current Telefunken products will be shown, in addition to the following new models.

The *Musikus* 108V is a portable domestic stereo record player/amplifier giving 6+6W output, the speakers being detached for playing or attached to the player unit for transportation. The 3-speed player unit has adjustable stylus pressure facilities and automatic end of disc cutout.

AUDIO FAIR PREVIEW 70

The Stereo Centre 2080K is another unit. Price, 63gns. domestic stereo ensemble, priced at 66gns.

The Stereo Compact 2080R is a novel flat stereo layout incorporating central record player unit with 6+6W amplifier on one end and a 4-band a.m.—f.m. tuner at the other end. Dimensions are only $26\frac{1}{2} \times 12 \times 5\frac{1}{2}$ in. The separate speaker enclosures are hexagonal.

AUDIX (24)

Main features on the Audix stand will be the Studio 80 laboratory/monitor power amplifier, the MXT/800 series of professional mixers and the new *Graphic Stereo* preamplifier which will be on show for the first time. The conventional treble and bass controls have been replaced by five-section graphic equalisers operating independently in each channel to permit correction or shaping of the whole audio spectrum and to obviate less flexible facilities such as presence and loudness controls. Each low level input has its own pre-amplifier section. Function switching is simpler than usual and both mono and mixing operation are provided, making further use of the separate channel gain controls. There is ample power to drive any high quality earphones or 600-ohm line.

BELL & HOWELL (48)

A new loudspeaker system, the AR-6, from Acoustical Research will make its first appearance at the Audio Fair. Weighing 20lb. and measuring only $19\frac{1}{2} \times 12 \times 7$ in., it is small enough for bookshelf fitting and light enough to hang on a wall. It is, however, claimed to have an extremely good bass response and will accept the output of virtually any hi-fi domestic amplifier up to 100W r.m.s.

The AR-6 is equipped with three drivers. One is a specially designed 8in. bass unit with urethane polymer suspension, mounted in an acoustically sealed enclosure, and the others are a special passive radiator and a $1\frac{1}{2}$ in. tweeter with a response to beyond 20kHz and exceptionally wide dispersion. Recommended retail price is £63 (in oiled teak) or £55 (in pine). The pine finish is ready sanded for painting or staining by the customer.

Denis Wratten, head of the Bell & Howell Audio Products Division says "the harmonic distortion of the AR-6 at 40Hz is less than that of most conventional loudspeaker systems of higher cost and vastly greater size." The enclosure itself has been designed to reduce interference patterns between the drivers and diffraction effects around the cabinet edges. These phenomena are inaudible in normal listening but they can have greater significance in small, acoustically dead rooms where the listener is very close to the speakers.

B & W ELECTRONICS (21)

Although B & W will be showing their complete range of high quality loudspeaker systems, interest will surely centre on the new release of the Continental Style Model 70 System. The concept of the Model 70 is based on six factors: (1) new thinking on the acoustical distribution pattern especially within the vitally important mid-frequency region on 400Hz to 5kHz, aiming towards exploring the advantages of a distribution pattern approximating to spherical, (2) a mid-frequency unit capable of handling input powers in the region of 35W r.m.s. with distortion factors in the order of 0.5% or lower, (3) a very low distortion bass radiator capable of truly complementing aspects (1) and (2) above without occupying an unduly large enclosure volume (4) exploration of the listening advantages by increasing reverberant to direct sound, (5) all units to be designed and built within the B & W factory, (6) styling and general appearance to be acceptable in the world market.

In the resultant system, the bass unit is of 12in. diameter

mounted in an infinite baffle type chamber with complex internal absorbents making it almost aperiodic. The system resonance is below 40Hz, with a free air resonance in the region of 18-22Hz. It will handle high powers at low distortion and covers frequencies up to 400Hz. Frequencies above 400Hz are covered entirely by an 11-module electrostatic mid- and high-frequency unit with a virtually circular distribution pattern in a vertical plane through mid-band frequencies, providing a wide and uniform arc in a frontal direction with a strong rear radiating pattern which can be controlled to vary the reverberation for ambient listening conditions and personal judgement.

New standards for distortion have been set. Although Model 70 is rated at 25W r.m.s., we understand that distortion figures of less than 0.5% are being obtained from production samples with 35W r.m.s. input. Frequency response of the system is better than ± 4 dB from 50Hz to 15kHz, ± 5 dB from 40Hz to 20kHz.

BRITISH RADIO CORPORATION (58)

Products under the BRC banner are Ultra, Ferguson, HMV and Marconiphone. The emphasis will be on audio unit systems. Among those shown will be the 2416 stereo amplifier integrated with an f.m. radio and record playing unit which, with two speaker enclosures, is priced at £129 14s. The amplifier delivers 15+15W r.m.s. at better than 0.5% total harmonic distortion and has a frequency response of 40Hz to 16kHz ± 0.5 dB, -1 dB. The radio section has five v.h.f. channels and record playing is taken care of by a Garrard type SP25 Mk II with Goldring 800H free field magnetic cartridge.

Ferguson will be represented by four separate unit systems ranging in price from £84 14s to £138 5s. Marconiphone will show the Unit 3 and Unit 4 systems and Ultra have two audio systems.

BSR (17)

As readers will know, the policy of BSR has recently been changed to enter into the field of more expensive record player units. These are to be known as the McDonald series of units and these will be seen for the first time at this Audio Fair.

The MP60 is a single player unit equipped with low mass pickup arm with calibrated stylus pressure adjustment, bias compensator, heavy large turntable and viscous cueing device. Similar in styling is the Model 610 which combines the functions of a stereo record changer, a fully automatic single record player and a repeating turntable. It has four speeds, an automatic stop, synchronous motor, tracking control, bias compensator, viscous cueing device.


The 510 is an autochange unit and the 310 is another auto-changer with similar features to the other models. All these units are available unmounted or mounted on an afromosia plinth with smoked styrene cover.

DECCA (59)

The new extended range of Deccasound unit audio equipment will be on display the philosophy being simplicity of installation and operation which Decca sum up as "no fuss stereo for the very fussy". In addition to 6W, 12W and 30W systems a newcomer to the range is the Compact 3 which combines a.m. and f.m. tuners with 6W amplifiers and record playing facilities in a free-standing unit. The speaker enclosures are detachable to obtain better stereo effect.


Deccasound 604 consists of four units—a 6+6W amplifier (A600), turntable unit (D1000) and two bookshelf speakers (L100). Deccasound 603 is similar except that the playing deck and amplifier are combined in one unit. Deccasound 1204 consists of a 12+12W amplifier (A1200), a turntable unit (D1000) and two free standing speakers (L200). The alternative 1203 system combined deck and amplifier.

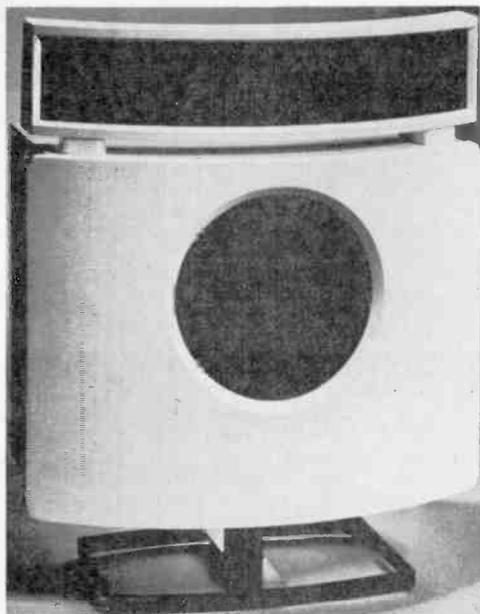The 3000 Series is the top system. It is a 30+30W system built around the Decca ffs pickup and employing a specially developed Garrard AP76 turntable. If you miss seeing this system at Decca's stand, you can see it in the Practical Wireless studio where it is being displayed as the prize in our special Audio Fair Competition (see page 525).




◀ The latest version of the Model 70 speaker system from B & W, setting new standards in low distortion.

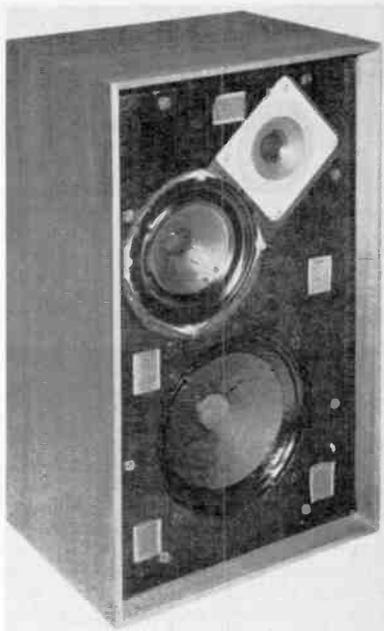
A view of the new Mordaunt Short MS 077 compact bookshelf speaker system with front grille removed to show the constituent units. ▶



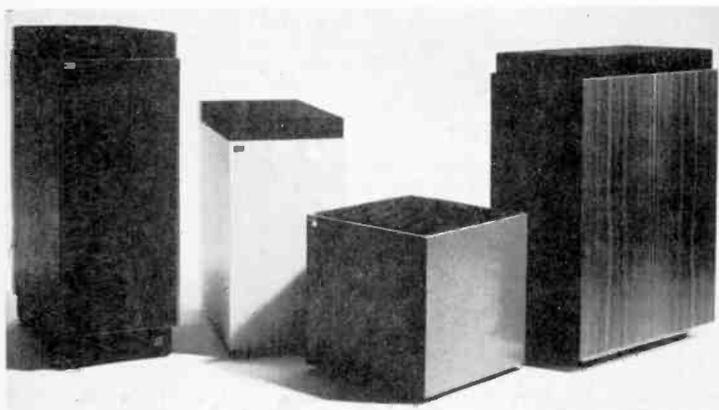A selection of the new loudspeaker systems from Sonab claimed to be the first to be truly omnidirectional. ▼





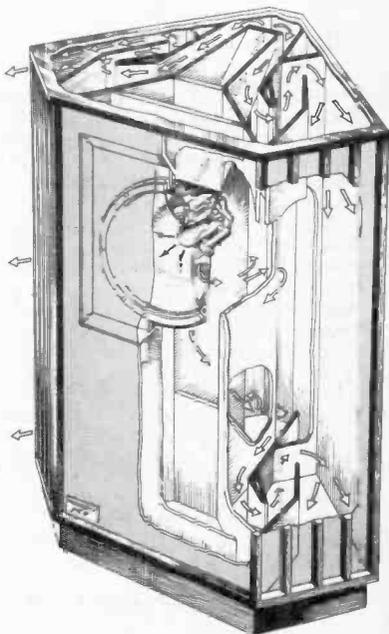A cross sectional view of the popular Monitor Gold dual concentric loudspeaker system from Tannoy. ▶



◀ One of the new bookshelf speaker systems by Leak, employing a Sandwich bass unit.

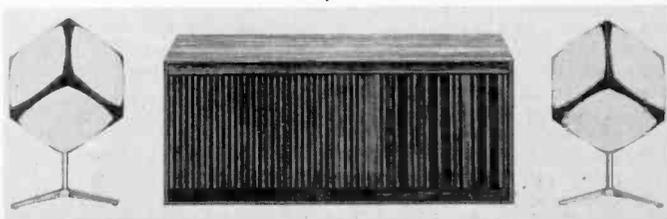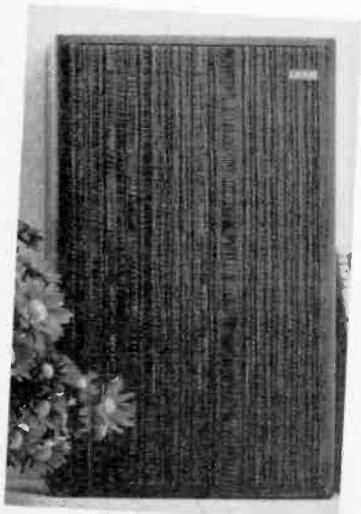Novel speaker system from Grundig—the Troika, designed to allow the maximum flexibility in the placing of the units. ▼



AUDIO FAIR PREVIEW

70

DIAMOND STYLUS CO (27)

All users of audio equipment will find something of interest in Diamond Stylus' display of accessories. For instance, the company have a range of diamond styli varying from unmounted points to a variety of nearly 300 types of cantilevers mounted with diamonds and individually packaged. Also on show is the *Record-Matic* automatic record selector which allows a choice of records at the touch of a finger tip while at the same time serving as a storage unit. Showing for the first time are two new products—a special cloth for cleaning record grooves which can be revitalised by sprinkling with water, and a sponge pad which cushions turntable to provide a quiet record drop when using autochangers, eliminates record slip, prevents damage to the stylus and decreases static pull from turntable to cartridge.

Other exhibits include a new stylus cleaner and a set of matched record/replay and erase heads made specifically for use with Philips stereo type cassettes.

DYNATRON (60)

Dynatron will be featuring their range of audio separates. The heart of the 1970 range is the SRX25A tuner-amplifier which covers l.w., m.w. and f.m. bands, employs 30 transistors and features a.f.c., tuning indicator on all wavebands, stereo beacon, built-in decoder, tone compensated volume control, switched scratch filter, loudness contour switch, stereo headphone socket and an output of 32W music rating. The audio units include a variety of designs from modern to period styling and takes in record storage units and stereo headphones.

Also being shown will be the new 90 Series range of audio separates comprising an amplifier, amplifier-player, tuner-amplifier and tuner-amplifier-player. The amplifiers each have an output of 45+45W r.m.s. and the record player unit in all cases is the Goldring-Lenco GL75 fitted with the Goldring G800 cartridge. The amplifier uses silicon transistors throughout and features high and low pass filters, tape monitor socket, channel reverse switching, A and B speaker switching and provision for crystal and magnetic pickups. The tuner has four preset v.h.f. channels in addition to manual tuning, all using varicap diodes. The v.h.f. front-end uses two dual gate FETs with crystal block filters in the i.f. stages. Five ICs are incorporated. Prices are £62 (SA90 amplifier), £122 (HFC90 amplifier-player), £165 (STA90 tuner-amplifier), £215 (HFC91 tuner-amplifier-player). Speaker enclosures for use with this equipment are LS1608 infinite baffle system (£50 pair), LS4008 bass reflex system (£84 pair).

FARNELL-TANDBERG (16)

The complete range of Tandberg tape recorders, tuner-amplifiers and loudspeakers will be on show. Of particular interest will be the new Tandberg Model 3000X four-head tape deck which will be demonstrated with the 15+15W f.m. tuner-amplifier and the Tandberg-Thorens turntable and Tandberg speakers.

The Professional Series II battery-operated tape recorder will also be shown in its new form as the Model II-12M, with complete synchronising units which enable the user to compile high quality lip synchronised sound tracks. This system will be demonstrated throughout the run of the exhibition.

A completely new tuner-amplifier will be shown (model S/S11) incorporating four wavebands, separate tuning for a.m. and f.m. and 15+15W r.m.s. output. Two new high performance mini loudspeakers will also be shown.

Of special interest to the travelling music lover will be the Tandberg TP4-1 portable radio, a compact and lightweight unit offering outstanding performance as an f.m. tuner or as a complete small tuner-amplifier system.

Although we had no firm information at going to press it is

understood that the company hope to mount a demonstration of four channel stereo sound from a completely new recorder.

GARRARD (7)

Although Garrard will be showing their complete range of record playing units, two new models will be on display for the first time. The first is the AP76, a transcription single record playing unit which features a 4-pole induction motor, slide-in cartridge carrier, bias compensator, calibrated stylus force adjustment, cue and pause facility and tab controls. The second is the SP25 Mk III, an updated version of the popular Mk II widely used in hi-fi ensembles.

GOLDRING (34)

From the established range will be the Goldring-Lenco transcription turntable units including the GL75 with its heavy, dynamically balanced turntable and precision pickup arm with knife-edge bearings, and the GL69 Mk II turntable unit which in common with the GL75 features infinitely variable speed adjustment, viscously damped pickup lowering device and bias compensation. A wide range of stereo magnetic cartridges will be shown, including the G800 Super E which is individually calibrated and supplied with its own frequency response curve and, at the other end of the price scale, the G850 cartridge which was designed for budget hi-fi systems.


Newcomers will be a stereo amplifier (ST3000) which has a hi-fi specification and delivers 15+15W r.m.s. A tuner-amplifier (ST4000), which has the same high quality audio section as the ST3000 is also on show. Finally, a new and inexpensive turntable unit (Model 705), which has belt drive and synchronous motor, will be introduced.

GRUNDIG (18)

As to be expected Grundig will be showing a big selection of tape recorders. Among the newcomers is the TK147, which at £96 4s. is designed for the more avid enthusiasts. It is a single speed (3 $\frac{3}{4}$ i.p.s.) four-track fully automatic recorder incorporating delayed auto-record level setting and two fully automatic recording amplifiers serving as preamplifiers on playback. This system, composed of an elaborate circuit arrangement, is claimed to keep distortion level, frequency response and dynamic range constant whatever the conditions, the composition or volume of the recording. Two of the four recording tracks can be played back together so that a commentary may be added to background music. Recording can also be monitored through headphones. The circuit employs 28 semiconductors and specification figures include frequency response of 40-12,500Hz, wow and flutter less than 0.2%, signal-to-noise ratio better than 47dB.

For the professional wanting a sophisticated portable, the new TK3200 will be interesting. It can be powered by batteries, rechargeable DEAC accumulators, car or boat batteries and mains supply with the aid of a power unit. It is a 2-track machine, operating at 1 $\frac{7}{8}$, 3 $\frac{3}{4}$, 7 $\frac{1}{2}$ i.p.s., and has a fully automatic recording level setting with manual override. Two separate automatic delay levels are provided for speech and music and there are individual controls for manual record level, volume, bass and treble. Features include steel chassis, moving coil meter recording level/battery level indicator, frequency response from 40Hz to 8kHz (1 $\frac{7}{8}$), 12,500Hz (3 $\frac{3}{4}$) or 16kHz (7 $\frac{1}{2}$), S/N ratio better than 48dB (7 $\frac{1}{2}$), two speakers (4 $\frac{1}{2}$ " x 2 $\frac{1}{2}$ " in. bass unit and 1 $\frac{1}{2}$ " in. tweeter). Price is £178 3s.

Also on show will be the new and unique *Troika* loudspeaker system, specially designed to allow greater flexibility in the placing of the units. The system consists of two 7in. cubes each containing six loudspeakers; these provide omnidirectional radiation of middle and treble frequencies and are said to give a remarkably wide stereo effect. The troika cubes are supplied with small tripod stands and a ceiling attachment ring so that they may be placed on a shelf, table or floor or hung from the ceiling or wall. The one bass speaker which completes the system may be placed in any convenient part of the room.

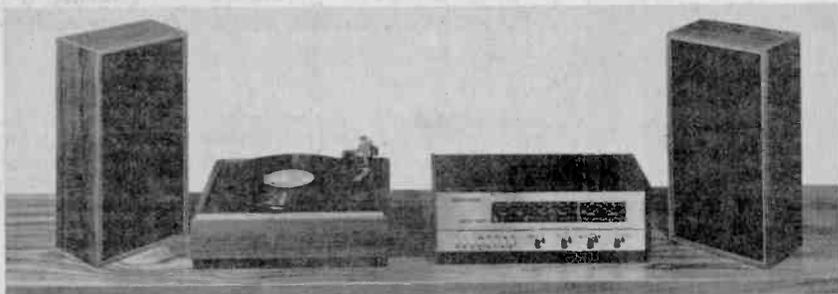


▲ Compact audio system from Alba, comprising UA100 tuner-amplifier, UA200 record player deck and matching loudspeakers.




▶ The MD3, a new miniature pencil microphone on desk base MSE00 from Reslosound.

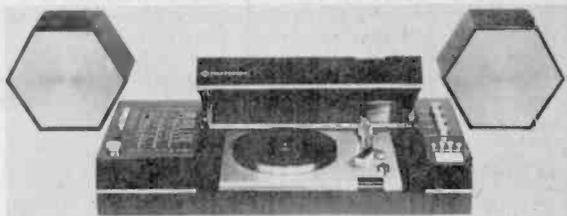▶ Telefunken 2080R Stereo Compact system presented in a novel flat layout and featuring hexagonal speaker enclosures.



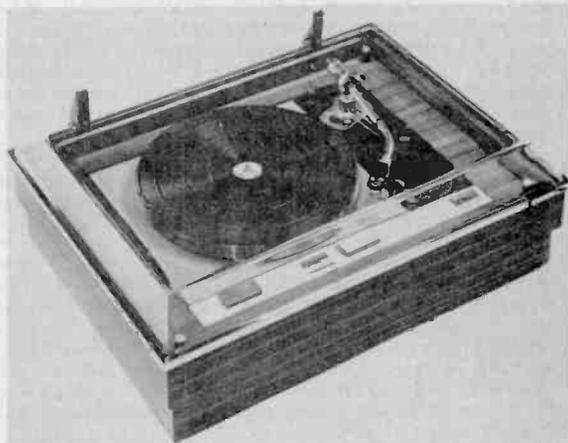▼ One of the new units from BSR under the McDonald marque—the 610 hi-fi autochanger.



▲ The SME model 2000 plinth system incorporating the well known Series II arm and a Thorens TD125 record player unit.

◀ Novel styling is a feature of the Ultra 6405 amplifier-tuner-record player, shown with matching speaker enclosures.

▼ A versatile hi-fi amplifier at a modest price—the SQ707 from Lux.



AUDIO FAIR

PREVIEW 70

The advantages of the system are that it takes up a minimum amount of space, there is little restriction on the placing of the speakers and the listener is not confined to one small area of the room to enjoy the full stereo image. Power handling is 30W per channel (40W peak). The bass unit handles frequencies from 40-400Hz and the cube units take over from 400-20,000Hz. Price is £97 5s. 6d.

HEATH (15)

All readers of P.W. will make sure they have a good look at the Heathkit exhibit. A selection of the audio models will be on show and will be demonstrated in the studio. Among the new models are two stereo tuner-amplifiers.

The AR-19 covers m.w. band and the f.m. band and its amplifier has a continuous power output of 20W per channel. Features include a new FET front end, four IC stages, electronically regulated power supply, less than 0.25% THD at full power, tuner sensitivity 2 μ V, f.m. stereo separation 35dB at middle frequencies, comprehensive key tab switching, linear slider controls for bass, treble, balance and volume. Price is £118 as a kit.

The AR-29 is in a similar type of presentation but has a more impressive performance, at a price of £168 for the kit. Output is 35W continuous power per channel at less than 0.25% THD. A new FET front end plus IC design gives the tuner 1.8 μ V sensitivity. Stereo separation (mid frequencies) is 40dB. Modular plug-in unit construction is used. Both this and the AR-19 features "black magic" panel lighting plus heavy chrome plated diecast front panels.

Also worth noting is the new Trent loudspeaker. The enclosure measures only 19 x 10 x 8 $\frac{1}{2}$ in. and houses an 8in. bass unit and a 4in. h.f. unit. The cabinet is provided ready assembled and finished in teak or walnut veneers to match other Heathkit equipment. Kit price is £14.

HOWLAND WEST (53)

Howland West will be showing their complete ranges of audio products from Dynaco, Lux, Nikko, Neat, JP, IMF and the company's own Scandinavian range of speaker systems and Clearview equipment cabinets.

New from the Japanese company of Nikko are three models. The FAM-10 is an a.m.—f.m. multiplex tuner selling at £48 10s. 7d. with sensitivities of (a.m.) 200mV/m for 20dB S/N and (f.m.) 2mV. Figures for the f.m. section include stereo separation of more than 32dB at 1kHz, image rejection of 50dB and a capture ratio of 4.5dB. Features include separation control (factory preset), rotating ferrite rod aerial, signal strength meter and stereo beacon.

The TRM-1200, which sells at £98, is described as a professional stereo amplifier. It employs two ICs, 29 semiconductors, and features circuit breaker protection, stereo headphone socket, output level meters for both channels, provision for driving two sets of stereo speakers simultaneously, high and low pass filters, loudness control, four input sockets and A/B speaker switching. Specification figures include frequency response (main input) 13-50kHz \pm 1dB, 40+40W r.m.s. output at 0.3% distortion (full power).

The third new Nikko item is the STA-1101 multiplex a.m.-f.m. tuner-amplifier which features all plug-in circuitry, four FETs, 12 ICs, separate a.m. and f.m. tuning controls, sliding light tuning indicators, separate volume control for remote speaker system, linear slide type volume, bass and treble controls, an i.f. section that includes two crystal filters and ceramic filter, extra tape recorder output socket, a triple circuit breaker protection system, speaker compensator to eliminate i.f. response loss in low efficiency speakers, separate amp/preamp output and two VU meters. The main amplifier frequency response is 10Hz to 70Hz \pm 1dB and the r.m.s. output per channel is 37W at 8 Ω with

a distortion figure of 0.3% at full power. The price is £246 5s. 7d.

Also on show is the interesting range of GG Control Units. These useful products are basically small control boxes to enable the user to switch amplifiers to various speaker and headphone outlets in a number of different ways, and the series includes Input/Output comparators used for dealer demonstrations or for use at exhibitions etc.

Another new Japanese product is the JP601 transcription turntable unit which incorporates a 4-pole synchronous motor and belt drive. Running at 33 $\frac{1}{3}$ or 45 r.p.m., the wow figure is less than 0.1% and the S/N ratio more than 40dB. The pickup arm is of a new design and the playing weight is set by means of coarse and fine adjustments. A lowering device is fitted. Price is £42 4s. 10d.

High performance amplifiers and tuners by Lux are also on show. These include the 507, which incorporates 48 semiconductors and gives an r.m.s. output of 60+60W into 8 Ω and features a 3-stage direct coupled preamplifier, automatic resetting protection circuit, high and low pass filters, a low boost switch to improve performance of bookshelf IB speaker systems, facilities for two separate speaker systems, monitor socket, tone controls which may be used coupled or separately. Frequency response is 20-50,000Hz -1dB, total harmonic distortion less than 0.2% at maximum output, residual noise less than 2mV. Price is £124.

For the budget conscious, the SQ707 amplifier fills the bill at £59. It uses 23 silicon semiconductors and features A/B speaker switching (with attenuator which cuts the gain by 18dB), tape monitor socket, headphone jack, power output of 17+17W r.m.s. into 8 Ω , frequency response of 30-30,000Hz \pm 1dB, distortion less than 1% at full power, residual noise level less than 2mV and S/N ratio more than 60dB at pickup socket.

KELLAR ELECTRONICS (69)

Readers will have their first opportunity to see the new cassette tape recorders from Kellar incorporating Dolby B noise reduction circuitry, details of which will be found on page 516 of this issue. There will also be two new products with the same theme. These are 'black boxes' for use with existing reel-to-reel tape recorders to convey the advantages of the Dolby system. Model 1 is for use with combined record/replay head type machines and Model 2 is for use with machines having separate record and replay heads, thus permitting monitoring from the tape via Dolby. Both models incorporate stabilised power supplies, VU meters and the necessary level controls for the correct setting up of the equipment.

LEAK (49)

The established Leak audio units such as the Stereo 70 amplifier, the Stereo 30 Plus amplifier and the Stereofetic f.m. tuner will need no introduction to keen audiophiles and they will be on show and demonstrated at the Fair. A new departure for Leak, however, is the range of sandwich loudspeakers.

The Model 200 is a three speaker system employing the Sandwich bass unit plus a mid-range and a treble unit. Power handling capacity is 18W r.m.s. Price is £23 each. The Model 300 is a similar system except that the cabinet is larger and the price is £29 10s. each. The Model 600 is the big brother of the series employing a Sandwich bass unit, a plastics coated mid-range unit and a new Leak tweeter. Power handling capacity is 40W r.m.s. and the price is £45 each.

LEE PRODUCTS (94)

Among the range of more conventional audio equipment, visitors can see a novel new product from the Lee stable—the Elizabethan Audio Chair. This is an apparently normal, though very comfortable, winged armchair, but inserted into the wings there are two concealed loudspeakers. These enable the occupant of the chair to listen in comfort and privacy to stereo sound without unduly disturbing other people in the same room. We tried one of these chairs at the recent trade exhibition and found it very effective.

The nylon covers, which zip off for easy washing, are available in a choice of four plain colours—turquoise, tan, gold

WIN! THIS DECCASOUND 3000 SERIES HI FI SYSTEM! WORTH OVER £200!!



A FREE competition organised by Practical Wireless in co-operation with Decca Radio and Television Ltd.

The 3000 System combines all the simplicity of the Deccasound philosophy with the best in sound reproduction. This 30-watt per channel system has been designed around Decca's *ffss* pick-up whose capabilities as a transducer are world-renowned. A specially developed version of the Garrard AP76 turntable matches the high quality potential of the

pick-up while the amplifier has such refinements as HF and LF filters and other facilities required in hi-fi equipment. Twin floor-standing speaker enclosures incorporating speaker units specially developed in Decca's hi-fi loudspeaker division have been designed to ensure optimum performance from the system.

HOW TO ENTER...

Listed below are eight features applying to the Decca 3000 Series audio unit system. All you have to do is to place these features in what you consider to be their order of importance for choosing the units as a hi-fi system. For example, if you think that *Good stereo separation* is most important of all, write E in the box marked 1st on the entry coupon. The key letter of your next choice goes into the box marked 2nd, and so on for all eight.

Complete the form, all in ink or ballpoint pen, with your full name and address, then post in a sealed envelope to: PRACTICAL WIRELESS HI-FI COMPETITION, 1-2 Bear Alley, Farringdon Street, London, EC4X 1AJ (Comp.), to arrive not later than the closing date: Monday, 16th November, 1970.

IMPORTANT Before sealing your envelope, copy out on the back of the envelope eight key letters in exactly the same order as they appear on your completed coupon. Do not enclose any correspondence or matter other than your entry form.

RULES

There is no entry fee, but each attempt must be fully completed in ink on the proper printed coupon cut from Practical Wireless, and bear the entrant's own full name and address.

- A. Ease of interconnection of units
- B. Low turntable rumble figure
- C. Bias compensator and arm lifting device
- D. Power handling and frequency response of speakers
- E. Good stereo separation
- J. Accurate matching between units
- K. Low distortion figures
- L. Low hum and noise figures of system

FREE ENTRY COUPON

1st	
2nd	
3rd	
4th	
5th	
6th	
7th	
8th	

PRACTICAL WIRELESS

Hi-Fi Competition

My order of importance for the eight points is given on the left. I agree to the rules as final and legally binding.

(Signed)
Mr./Mrs./Miss

Full
Address

Post to: PRACTICAL WIRELESS Hi-Fi Competition
1-2 Bear Alley, Farringdon Street,
London, EC4X 1AJ (Comp.).

Closing date: 16th November, 1970

please cut out along this line



AUDIO FAIR PREVIEW 70

or avocado green, as well as two floral patterns in blues or browns. Two or even three chairs can be connected to any stereo unit, a suitable choice from Elizabethan being the Windermere stereo unit, which is available with matching swivel pedestal. Prices for the units are £52 for the Audio Chair, £65 for the Windermere stereo unit and £10 for the swivel pedestal.

MORDAUNT SHORT (33)

A compact bookshelf loudspeaker system which makes its international debut at the exhibition can be seen on this stand. The cabinet measures $15\frac{3}{4} \times 9\frac{1}{2} \times 8$ in. and the complete unit weighs about 14½ lb. It comprises three drive units (6, 3 and 2 in.) with a power handling capacity of 15W music rating and a frequency range of 40-20,000Hz. The treble and mid-range units are virtually identical to the larger MS 100. Price is £27.

MULTICORE (51)

Great strides have been made in recent years by the Bib Division of Multicore in devising and making available all manner of very useful accessories and other aids—tape splicers, maintenance kits, cleaners, and so forth. A good deal of attention has also been directed towards the tidying up of enthusiasts collections of records and tapes, leading to the various packs of tape cassette and spool labels, etc. The latest development in this field will be seen for the first time at the Audio Fair—a new low cost system of indexing record collections.

The system is suitable for 1-100 records and costs 34s. It comprises a simulated pigskin finish padded PVC index book with 12 clear slip-in filing pockets into which pre-printed and colour-coded index pages can be slotted (and extracted, updated and refiled as further information is added when the record collection grows). Columns provided permit the compilation of such details as date, number of record, title, composer and artists etc. Also included in the pack are 100 pairs of self-adhesive labels numbered 1-100 and 40 general purpose self-adhesive labels so that works can be filed under appropriate headings such as classical, jazz, pop, etc.

NATIONAL RADIO (14)

One of the highspots here will be a demonstration of Panasonic quadrasonics (4-track stereo), the dem. unit being flown in from the USA where it has been on show at the New York Fair. Other tape equipment on show will be the RS-678US 8-track 3-head tape deck and, it is hoped, a new model—the RS-763US—which uses hot-pressed ferrite heads and incorporates a 4-pole hysteresis motor with wow and flutter of less than 0.09%.

There will also be various other audio units, including the SA-65 de-luxe tuner-amplifier which features FETs, ICs and silicon transistors, two r.f. stages, filter switching, 7-position input selector.

POWER JUDD (107)

This company is exhibiting record storage units under the name of Paddock.

The self-adjusting conical-spring-loaded mahogany support panels in a Paddock 'tidy' hold records upright and pressed together in a neat and tidy condition. Whether it holds 1 or 100 records, each one is held upright with the correct pressure applied, yet allowing easy removal or replacement of records. The unit is sturdily constructed in resin-bonded mahogany ply to prevent warping and is spray finished. Price is 59s.

RANK-WHARFEDALE (49)

Undoubtedly the highlight of exhibit will be the new 100.1 tuner-amplifier which boasts a most impressive specification at a competitive price. (£125 gns.). The tuner section includes FETs and ICs and covers l.w., m.w. bands in addition to f.m. Sensitivity on f.m. is $1\mu\text{V}$, to give 30dB signal/noise ratio at 75kHz deviation. Stereo crosstalk is better than 35dB at 1kHz. Tuning is by meter and a stereo beacon is fitted.

The amplifier, which delivers 35W per channel r.m.s., has impressive distortion figures—at any power up to 35W per channel into 8Ω it is less than 0.07%. Weighted noise level (gain at minimum) is -90dB; weighted noise level (disc input, gain at maximum) -75dB. The frequency response is 12.5Hz to 50Hz \pm 3dB. Facilities include low pass filter, v.h.f. muting switch, local and remote speaker switching, stereo headphone socket, tape socket, three separate input sockets.

Two new Wharfedale speakers make their debut. The Triton is a 3-speaker 3-way bookshelf system using an 8in. bass unit, 5in. mid-range unit and a 1in. dome treble unit, giving a system frequency range of 50-18,000Hz. Power handling is 18W r.m.s. Price £27 10s. The Aston is a slim line shelf or wall mounting unit incorporating an 8in. bass unit, 3in. treble unit and a 4-element crossover unit. Frequency range is 65-17,000Hz and power handling capacity 20W r.m.s. Price per pair is £42.

Audio enthusiasts will also be wise to have a look at the range of loudspeaker kits (Unit 3, Unit 4 and Unit 5) which are supplied boxed with full instructions for assembly.

RESLOSOUND (52)

A wide range of public address and associated equipment includes amplifiers up to 50W, line source loudspeakers, re-entrant horn speakers, floor stands, boom arms, table stands and desk bases, plus a wide selection of all types of microphones. Also on show, and being demonstrated, will be the Reslo-Audac range of radio microphones which have a range of 500 yards or more and eliminate the problems of trailing cables associated with the conventional type of microphone.

A new addition to the Reslo range is a highly portable PA system known as the ISR/10. Weighing only 30lb. and measuring $34 \times 12 \times 9$ in., it contains three 8in speaker units, 10W amplifier with three microphone inputs, together with a radio microphone receiver. Other new products which will be displayed include the SR530 30W amplifier, a new desk base, two new pencil microphones, a new ribbon microphone and a radio guitar. Further details were not available at time of going to press.


ROGERS (28)

On show will be the basic Rogers range comprising the Ravensbrook and Ravensbourne stereo amplifiers, together with their respective matching f.m. tuners. The tuners feature FET front ends, IC i.f. strips and a decoder with automatic electronic switching. Interesting constructional feature is the use of high grade fibreglass for virtually all the printed circuit boards, a Rogers exclusive.


In addition, Rogers will be showing the first three instruments in an entirely new range of audio test equipment, designed and developed by Sign Electronics. These comprise a low distortion oscillator, an a.f. millivoltmeter and a distortion factor meter.

SINCLAIR (44)


Two major additions to their range of products are being shown by Sinclair. The first is a new f.m. tuner claimed to be the first in the world to use the phase lock loop principle. This principle was first used in receivers for reception from satellites because of the improvements in signal/noise ratio and improved selectivity and sensitivity. A voltage controlled oscillator in a phase lock loop tuner is kept in phase with the

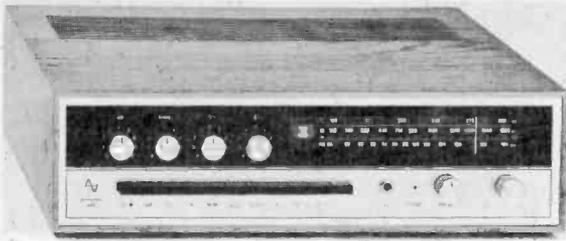

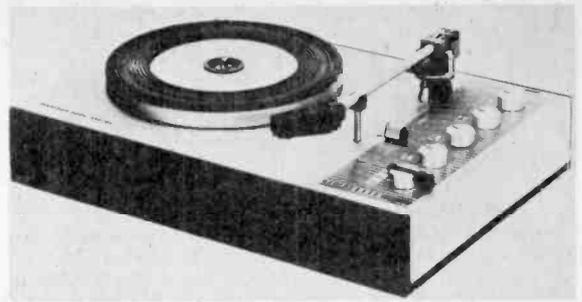One of the Armstrong 500 Series audio units—the Model 526 tuner-amplifier.



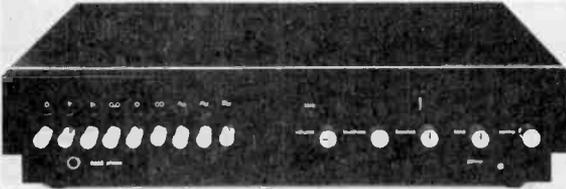The Musikus 108V, a portable domestic stereo record player/ amplifier from Telefunken.




The Sonab R7000 has only one tone control which lifts bass and cuts treble or lifts treble and cuts bass.




High grade tuner-amplifier by Wharfedale is the 100.1 which has an impressive performance at comparatively modest cost.



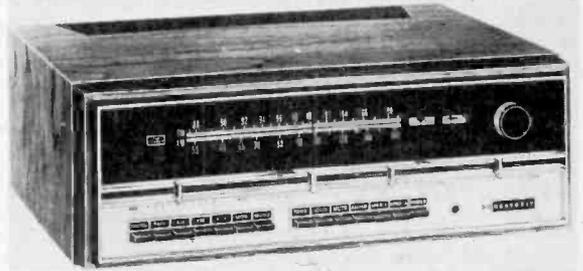Described as a "professional stereo amplifier", the Nikko TRM1200 is priced at under one hundred pounds.



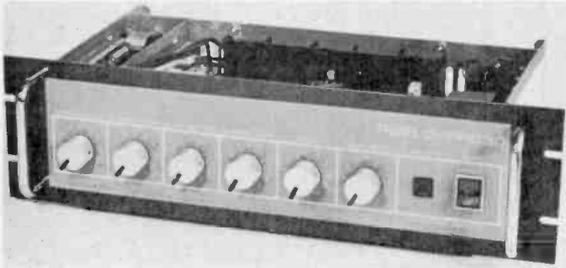One of the new tuner-amplifiers from Heathkit, the AF29 incorporates all the latest features.



The latest p.a. amplifier from Resosound, the SR530 has an output of 30 watts and flexible mixing facilities.

A novel product that may solve a domestic problem is the Elizabethan audio chair which contains two concealed loudspeakers in the chair wings.



◀ The TK147 is the latest tape recorder from Grundig and incorporates a number of new features and facilities.

AUDIO FAIR PREVIEW 70

incoming signal by a phase comparator or detector which compares the two and feeds a control voltage to the oscillator. This control voltage is the audio output in the case of an f.m. signal. Since it is possible to design a VCO which has an extremely linear voltage/frequency characteristic, excellent audio fidelity can be achieved. Also, the oscillator can track a signal while completely rejecting a nearby stronger signal which would cause interference in a conventional receiver. The tuner also features printed circuit coils for the tuned circuits, a squelch circuit to silence the tuner between stations, an i.c. stereo decoder and the option of remote control and push button switching. The price of the tuner, designated Project 60, is £25.

The other new product is the System 3000 amplifier which has a total harmonic distortion of less than 0.4% at full output (17W per channel r.m.s.) at 1kHz. It has a stabilised power supply with automatic overload protection and uses silicon transistors throughout. Price is £45.

SME (9)

Still going strong—the SME Series II arm, considered by many to be the ultimate in precision pickup arm design. Extremely low pivot friction is achieved by the use of high precision ball races protected against the entry of dust and the tone arm is carried on knife-edge bearings. Approximately 0.02 gramme applied at the stylus will deflect the arm vertically or laterally. Dynamic damping of the arm mass/stylus compliance resonance is obtained by dividing the arm mass into two portions joined by an elastic coupling which also effectively ejects rumble frequencies. It has, of course, all the required modern adjuncts such as lever operated hydraulic raising/lowering control, bias adjustor graduated to correspond with tracking force, and a base plate sliding through lin. on bed plate for precise tracking adjustment.

SONAB (61)

This will be a new name to many readers, but not for long for the company have some very interesting products. The Sonab range of hi-fi equipment is to initially comprise five loudspeaker systems (one in kit form), a turntable unit and a tuner-amplifier.

The loudspeakers are claimed to have been the first in the world to be truly omni-directional and they have their drive units mounted in the upper surface of the cabinet. The OA6 has a frequency range of 26-18,000Hz, the bass performance being attributed to the fact that the bass unit is driven by its own power amplifier incorporated within the speaker cabinet. This amplifier provides electronic compensation for the frequency response curve of the speaker and is used to extend the response down to the limits of human hearing.

The OA6 has six speaker elements (an 8½in. bass unit, an 8½in. mid-range unit and four 2in. tweeters, the latter being mounted in the top of the cabinet crosswise with the rear pair facing diagonally upwards and backwards). It is claimed that when the speaker unit stands on the floor with its back no further than 8in. from a wall, the response curve will be ±4dB within 29-15,000Hz. This superb system costs £137 5s.

The OA5 has five elements and dispenses with the built-in amplifier and thereby costs far less (£68 10s.). Response is 37-18,000Hz, and deviation from flat is ±4dB from 42-15,000Hz. This system is available as a kit at £49 10s.

The OA4 is a small version employing only one 8½in. unit plus the four tweeters. Frequency range is 44-18,000Hz, power handling is 35W and the price £45. The smallest of the range is the V-1 which although based on similar principles to the other models contains only a single drive unit of 8½in.

to cover the claimed frequency range of 40-17,000Hz. It differs from the other models in that it can be placed and directed in any position within a room like a conventional speaker. Price is £65 15s. 3d.

The tuner-amplifier, model R7000, has an output of 35+35W r.m.s. at 8Ω, with a frequency response of 25Hz to 25kHz ±0.5dB at a harmonic distortion of less than 0.1% at all levels up to rated power output. Signal-to-noise ratio is better than 70dB at the pickup socket and better than 80dB at the high level inputs. With volume control at minimum the noise level is 95dB. Features include full protection against short circuits and overload conditions, loudness and volume controls, rumble filter (5dB at 100Hz), choice of three high pass filter slopes, f.m. capture ratio of 1.5dB and outputs for tape, centre channel, two speakers and headphones. A novel feature is the provision of only one tone control based on a principle developed by Stig Carlsson. The adjustment range of the control at 100Hz is ±7dB and at 10kHz ±6dB, the control affecting both channels simultaneously, either lifting the bass and cutting the treble or lifting the treble and cutting the bass. This unit will retail around £200.

Also to be shown is the 75S turntable unit, all functions being controlled by two buttons. It has a synchronous motor and belt drive, with a wow and flutter figure of 0.08% and rumble of less than 60dB weighted. Sonab will additionally display a range of high quality stereo headphones from Clark, which are recommended for use with the Sonab equipment.

TANNOY (29)

Highlighted will be the established range of *Monitor Gold* loudspeaker systems which range in price from £41 to £170, together with separate units for mounting in the customers own cabinets. Also on display will be a range of pickups cartridges and spare styli.

TRANSCRIPTORS (54)

Apart from the well known precision Transcriptor turntables, one new model will be on show at the Audio Fair. Supplied complete with tone arm and moulded clear acrylic top, it features a synchronous motor driving a 6lb. non-ferrous turntable via a belt. The acoustic and mechanical feedback properties are such that the whole baseboard floats at a resonance below 5Hz and a fluid dashpot may be used to damp this movement. The tone arm is designed for use with the most advanced cartridges and the frictional characteristics of the stabilised jewelled unipivot are exceptionally good. All the expected facilities are included, such as hydraulic lowering and cueing device and bias compensator. The price of the new unit is £57 12s.

3M (3)

Visitors to the Scotch magnetic tape stand this year will be able to enter a free contest featuring mystery animal voices. Six Cybervox language laboratory booths will be used for the competition, which offers a portable cassette recorder and a supply of tape cassettes as first prize.


Entry forms will be available for the 3M wildlife sound recording contest, now in its third year, and there will be a bank of quality tape recorders from makers such as Tandberg, Ferrograph, Teac, Revox and Akai on which visitors will be able to compare, via headphones, identical musical excerpts pre-recorded on Scotch *Dynarange* tape.

The newly introduced Scotch 360/361 helical scan video tapes, which feature a unique textured backing for improved handling and cleaner performance, will also be demonstrated on VTR equipment.

DON'T FORGET TO VISIT STAND 68 WHERE PRACTICAL WIRELESS WILL BE PUTTING ON DEMONSTRATIONS OF AUDIO EQUIPMENT.

Just what is this ABR, that makes such a vital difference to the 'DITTON 15'?

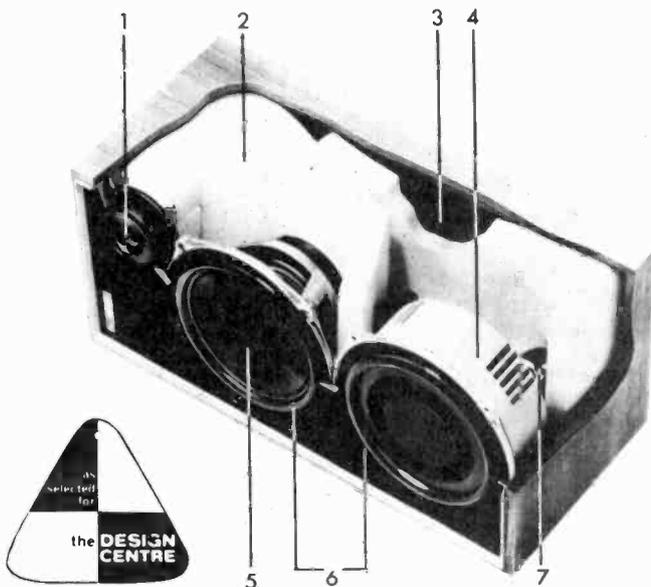1. Studio quality high frequency unit (HF1300 Mk. 2).
2. Anechoic cellular foam wedge and lining eliminates standing waves.
3. High hysteresis panel loading material to eliminate structural resonances.
4. Auxiliary Bass Radiator (ABR)—plastic foam diaphragm of high rigidity and low mass having a free air resonance of only 8 Hz, double roll suspension allowing excursions up to $\frac{3}{4}$ " with virtual absence of distortion.
5. 8" bass unit, with free air resonance of 25 Hz, and massive Ferroba II magnet structure for optimum magnetic damping and cone treated with viscous damping layer to suppress resonances.
6. Units mounted flush to eliminate diffraction effects and tunnel resonances; covered by acoustically transparent grille cloth for maximum presence.
7. Full L-C Crossover network.



VISIT US ON STAND No. 2

and listen to the acknowledged 'DITTON' Hi-Fi Speaker Systems, and hear the vital differences.

INTERNATIONAL

AUDIO FAIR

OLYMPIA 20-24 OCTOBER 1970

Please write for details.

HEAR CELESTION'S NEW SPEAKER!

Celestion

Studio
Series

**Loudspeakers for
the Perfectionist**

**ROLA CELESTION LTD., FOXHALL ROAD,
IPSWICH, SUFFOLK**

Goodmans Loudspeakers speak for themselves

This is a range which offers a truly superlative loudspeaker system for every requirement. From the tiny Maxim which offers true High Fidelity quality for the smallest of rooms, to the massive Magister easily capable of filling a concert hall with perfect sound, every one is outstanding in its class for design, for performance and for value. Your local Goodmans' dealer has full details, or write directly to us for the latest colour brochure.




Goodmans Loudspeakers Limited
Axiom Works, Wembley, Middlesex. Tel: 01 - 902 1200




Maxim

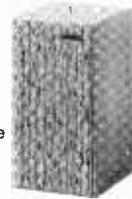The first miniature, truly High-Fidelity loudspeaker system. Only 10½" x 5½" x 7½" deep. Design Centre approved. Range: 45 - 20,000 Hz. Power: 12 watts. Impedance: 8 to 16 ohms. £16. 7. 0. plus £4. 0. 9. P. Tax. (£16.350 plus £4.038)





Minister

A superb system designed to meet the public demand. Using an 8" Bass unit and Goodmans Special 1" dome Tweeter. Size 19" x 10½" x 10" deep. Range: 45 - 22,000 Hz. Power: 20 watts. Impedance: 4 to 8 ohms. £18. 0. 0. plus £4. 9. 0. P. Tax. (£18,000 plus £4.450) Packed in pairs.

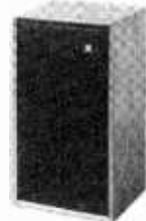



Mezzo 3

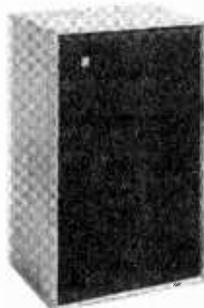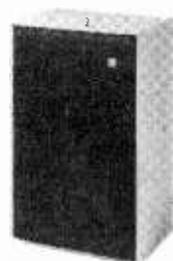The Goodmans bookshelf speaker system, it incorporates a 12" bass unit and Goodmans special 1" Dome Tweeter. Distinctive styling. 12" x 19½" x 9" deep. Range: 40 - 22,000 Hz. Power: 30 watts. Impedance: 4 to 8 ohms. Design Centre approved. £30.18. 0. nil P. Tax. (£30.900)




Magnum K-2

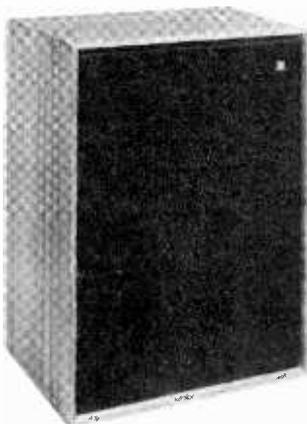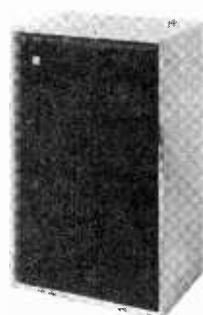Studio quality three speaker system, 12" bass unit, 4" mid range and 1" Dome Tweeter. Design Centre approved. 15" x 24" x 11½" deep. Range: 30 - 22,000 Hz. Power: 40 watts. Impedance: 4 to 8 ohms. £40. 2. 0. nil P. Tax. (£40.100)



Magister

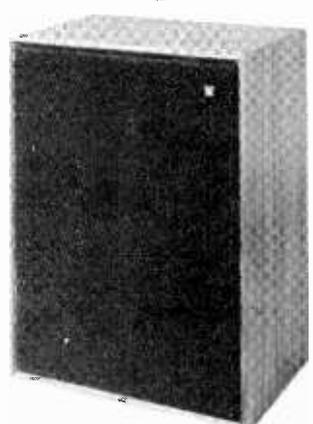This is the loudspeaker system for the perfectionist. Three speaker assembly incorporating a 15" bass unit, 4" mid range and Goodmans 1" Dome Tweeter. 27" x 20" x 14½" deep. Range: 26 - 22,000 Hz. Power: 50 watts. Impedance: 4 to 8 ohms. £57. 0. 0. nil P. Tax. (£57.000)



All these cabinets are available in Teak or Walnut to order.

PW7/70

pw 25/25



STEREO

AMPLIFIER

F.C. JUDD

PART 1

THE stereo amplifier to be described in this article is based on commercially made power amplifier modules and a suitable matching power supply chosen from the wide range now currently available.

The use of ready made power amplifier stages and a power supply does overcome certain technical problems for those with a very limited range of test equipment. For example, an oscilloscope as well as an audio signal generator would be necessary for checking a home constructed power output module for full power output i.e., to clipping point and there is of course the ever present risk of damaging or even completely destroying expensive power transistors in the event of a wiring error or accidental short circuit.

The Henelec PA-25 power modules chosen for the PW 25-25 stereo amplifier are fully protected against all but the most drastic treatment and have a high electrical performance. They require around 700mV for the development of full r.m.s. power output which is 25 watts per module.

Facilities

The pre-amplifier section employs fairly conventional hi-fi amplifier circuitry and provides for input signals from a radio tuner, magnetic or ceramic pick-up cartridges, tape head and tape replay from a tape recorder or tape record/replay unit. The controls cater for volume, stereo balance, bass and treble lift and cut, rumble filter and heterodyne whistle filter. The latter is useful for reducing surface noise from old records. At full gain, the pre-amplifier provides over 1V r.m.s. signal so that full output is produced from the power stage modules with a volume control setting at approximately three-quarters of its full rotation from zero. The stereo balance control reduces the signal level of either channel from maximum to zero and at midway travel equalizes the signal level from each channel to within ± 1 dB.

Performance

Performance shown in Table 1 should be readily obtainable providing the amplifier is constructed with the components specified and according to the layout described in this article.

TABLE 1

Power Output	
8 ohm load	25W r.m.s. per channel
15 ohm load	15W r.m.s. per channel
Distortion	
Less than 0.25% at rated power output	
Inputs	
Radio	90mV at 100k Ω
Mag pick-up (PU1) (RIAA)	4mV at 56k Ω
Ceramic pick-up (PU2)	80mV at 1.5M Ω
Tape Head (CCIR)	8mV at 10k Ω
Tape Replay	200mV at 220k Ω
Outputs	
Loudspeakers	8 or 15 ohms only
Tape record outlet	Up to 1V at 10k Ω
Frequency Response	
10-30,000Hz ± 1 dB	
Signal to Noise	
Radio and Tape	Better than -60dB
Pick-up inputs	Better than -56dB
Crosstalk	
All inputs	Better than -50dB
Bass Control	
± 15 dB lift or cut at 50Hz	
Treble Control	
± 15 dB lift or cut at 15,000Hz	
Rumble Filter	
-5 to 6dB at 40Hz	
Whistle Filter	
-20dB at 10,000Hz	

It is worth noting here that a polished wood cabinet finished in teak or walnut is available to constructors from Fircastle Limited, of Hockley, Essex. (see components list). The cabinet costs £3 6s. 0d. inclusive and has been designed to accommodate the PW 25-25 amplifier constructed to the dimensions given.

Circuit

The pre-amplifier circuits for each channel are identical, Fig. 1. The circuitry is conventional and each channel consists of an input stage (Tr1 and Tr2) which, with suitable input attenuation and a negative feedback network, provides frequency response equalization for magnetic pick-up and tape head and maintains matching input sensitivity and gain for the linear inputs i.e., ceramic pick-up, radio and tape replay.

This is followed by the stereo balance control VR1 formed by two 10kΩ potentiometers, one a log type and one an anti-log type, which equalize the signals through each channel. The range of balance control is from maximum to zero signal level through either channel.

The second section of the pre-amplifiers begins with the bass and treble control networks formed around VR3 (bass control) and VR2 (treble control). The tone control network is an "active" type and operates in conjunction with negative feedback between the collector and base of Tr3. Part of the feedback circuitry is used for the rumble filter (C15, R23, C16 and S3) and for the whistle filter (C17, R27, R28, C21 and S4). The final stage consists of a buffer amplifier (Tr4) the gain of which is attenuated by negative feedback at the emitter circuit. The output from Tr4 goes to the power modules via VR4 (volume control) and also to phono sockets for connection to a tape recorder. Recording can therefore, be carried out with the volume control turned off i.e., no signals from the loudspeakers.

The positive supply for the pre-amplifiers is derived from the MU442 power supply unit via R35 which brings the +35V rail from this unit down to approximately +22V. The pre-amplifier positive rail is decoupled by C24 (5000μF) to ensure the least possible mains ripple.

Construction

The layout for the pre-amplifiers, power output modules and power supply unit is shown in Fig. 2. The dimensions of the chassis and front panel are such that the finished amplifier will exactly fit the Fircastle cabinet mentioned earlier. The chassis itself is simply a flat sheet of 16 s.w.g. aluminium and the front panel is secured to it by means of $\frac{1}{8}$ x $\frac{3}{16}$ in. aluminium angle.

Note: Do not under any circumstances use duralumin for the construction of the chassis and front panel or the pre-amplifier screens. The oxidation that forms on Dural can produce high resistance earthing connections between the pre-amplifiers and power output modules resulting in both h.f. and l.f. instability. A prototype of this amplifier was in fact assembled on a Dural chassis with resultant h.f. and l.f. instability and hum loops.

Details of the front panel size and drilling are given in Fig. 3. Note, that the dimensions of the

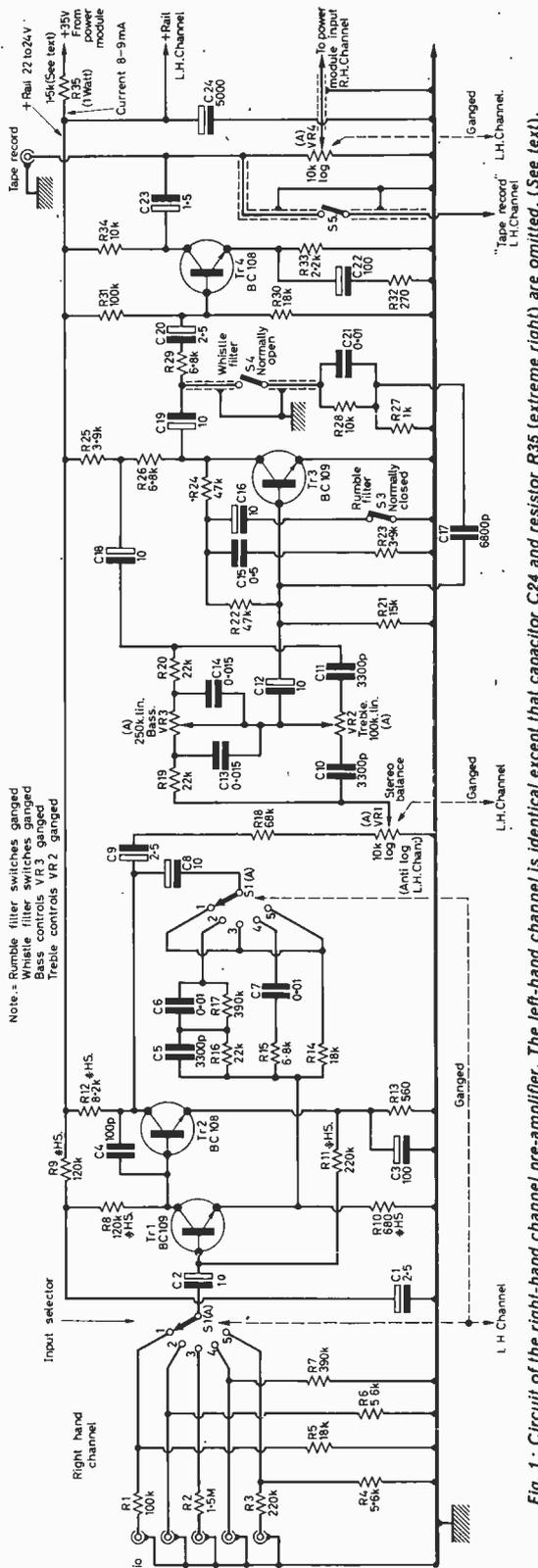


Fig. 1: Circuit of the right-hand channel pre-amplifier. The left-hand channel is identical except that capacitor C24 and resistor R35 (extreme right) are omitted. (See text).

Merry Christmas from Antex

Complete Soldering Kit 55/-

This contains the iron fitted with a $\frac{3}{16}$ " bit, interchangeable spare bits $\frac{5}{32}$ " and $\frac{3}{32}$ ", resin cored solder; felt cleaning pad; stand for soldering iron, and a booklet "How to solder." From Electrical and Radio Shops or send cash to Antex.

Model CN 240/2

15 watts - 240 volts 34/-

Fitted with nickel plated bit $\frac{3}{32}$ " and in handy transparent pack. From Electrical and Radio Shops or send cash to Antex.

PRECISION MINIATURE SOLDERING IRONS
 Antex, Mayflower House, Plymouth, Devon.
 Telephone: 45296. GPO No. 2581000.
 Telex: 45296. GPO No. 2581000.

Please send me the Soldering Kit

Please send me the Model CN 240/2 Pack

I enclose cheque/P.O./cash value

NAME

ADDRESS

BENTLEY ACOUSTIC CORPORATION LTD.

Suppliers to H.M. Government. 38 CHALCOT ROAD, LONDON, N.W.1 Telephone 01-722-9090

EXPRESS POSTAL SERVICE, SAME DAY DESPATCH BY FIRST CLASS MAIL
ALL GOODS ARE NEW, BEST QUALITY MANUFACTURE ONLY, AND SUBJECT TO MAKER'S GUARANTEE

OA2 5/8	6D6 3/8	10PL12 7/8	78	4/8	E180C0 8/8	E183 7/8	PC84 8/8	SP61 6/8	VT501 3/4	ASY27 8/8	OA9 2/8
OB2 6/8	6E5 7/8	12A6 12/6	85A2 4/8	8/8	E180F 10/8	E184 4/8	PC85 6/8	TH4B 10/8	VU111 7/8	ASY28 6/8	OA10 8/8
OZ4 4/8	6F1 12/6	12AC6 7/8	85A3 4/8	8/8	E182CC 22/6	E185 8/8	PC88 9/8	TH23 13/6	VU120 12/8	ASY29 10/8	OA47 2/8
LA3 4/8	6F8G 5/8	12AD6 7/8	90AG 6/7/8	6/8	E1184 10/6	E186 8/8	PC89 9/8	TP22 11/8	VU120A12/8	BI181 10/8	OA70 3/8
LA5 5/8	6F8M 12/6	12AE6 12/6	90AV 6/7/8	6/8	E450 1/6	E191 4/8	PC189 10/6	TP25 6/8	VU133 7/8	BA109 9/8	OA73 3/8
LA7GT 7/3	6F12 3/8	12AT7 3/8	90C3 24/8	8/8	E474 13/6	E192 5/8	PC630 13/6	TP26 10/8	W63 10/8	BA115 2/8	OA79 1/8
IC1 5/8	6F13 3/8	12A7T 3/8	90CV 3/8/6	6/8	EABC80 6/8	EM80 7/8	PC806 15/6	UABC80 6/8	W68 10/8	BA116 2/8	OA81 1/8
IC2 9/8	6F15 10/8	12AU6 4/8	90C1 1/6	6/8	EAC91 3/8	EM81 7/8	PC800 13/6	UAF42 10/8	W77 2/6	BA129 2/8	OA85 1/8
IC3 7/8	6F18 7/8	12AU7 4/8	150B2 14/6	6/8	EAF42 10/8	EM84 6/8	PCF80 6/8	UB41 6/8	W81M 13/6	BA130 2/8	OA86 4/8
IC5 4/8	6F23 14/8	12AV6 5/8	150CZ 5/8	5/8	EB34 3/8	EM87 7/8	PCF82 6/8	UBC41 9/8	W101 26/2	BCY10 5/8	OA90 2/8
ID5 7/8	6F24 13/8	12AV7 9/8	201 20/8	20/8	EB41 4/8	EY51 7/8	PCF84 8/8	UBC81 7/8	W107 8/8	BCY12 5/8	OA91 1/8
ID8 9/8	6F25 13/8	12AX7 4/8	302 15/6	6/8	EB91 2/8	EY81 7/8	PCF85 10/8	UBF80 5/8	W29 12/8	BCY33 5/8	OA95 1/8
IFD1 6/8	6F26 5/8	12AY7 9/8	303 15/6	6/8	EBC1 6/8	EY82 5/8	PCF87 13/6	UBF89 6/8	XF12 9/8	BCY34 4/8	OA200 1/8
IFD9 4/8	6F28 14/8	12BA6 6/8	305 16/6	6/8	EBC81 6/8	EY84 10/8	PCF90 13/6	UBL21 9/8	X24 18/6	BCY38 5/8	OA202 2/8
IG6 6/8	6F29 6/8	12BE6 5/8	306 13/8	6/8	EB90 4/8	EY86/87 6/8	PCF800 13/8	UC92 5/8	X41 10/8	BCY39 4/8	OA210 9/8
1H6GT 7/8	6F30 6/8	12BH7 6/8	807 11/8	6/8	EB91 5/8	EY88 8/8	PCF801 7/8	UC84 8/8	X61 5/8	BCZ11 6/8	OA211 13/6
ILA 2/8	6F32 3/8	12E1 17/8	956 2/8	6/8	EBF80 6/8	EY91 3/8	PCF802 9/8	UC85 7/8	X63 6/8	BCI07 4/8	OA2200 12/6
ILD5 6/8	6G6G 15/8	12J5GT 2/6	1821 10/8	10/8	EBF83 8/8	EZ35 5/8	PCF805 12/8	UCF80 8/8	X64 12/6	BCI08 3/8	OA2201 10/6
LN5 8/8	6H6GT 6/8	12J7GT 6/8	6763 6/8	6/8	EBF89 5/8	EZ40 7/8	PCF806 11/8	UCI21 8/8	X65 10/8	BCI13 5/8	OA2202 9/8
INSGT 7/8	6J5G 3/8	12K7GT 6/8	6980 5/8	5/8	EEL21 12/6	EZ41 6/8	PCF807 11/8	UCI22 12/8	X66 10/8	BCI15 3/8	OA2203 9/8
1PI 7/8	6K5G 3/8	12K7GT 6/8	7193 10/8	10/8	EBC1 12/6	EZ42 7/8	PCF808 11/8	UCI23 12/8	X67 10/8	BCI16 5/8	OA2204 9/8
1PI0 5/8	6J6 3/8	12Q7GT 5/8	7475 14/8	14/8	EC54 10/8	EZ81 4/8	PCL82 7/8	UCL82 7/8	X109 28/8	BCI18 4/8	OA2204 9/8
1PI1 6/8	6J7G 4/8	12SA7GT8/8	A1834 20/8	20/8	EC70 4/8	EZ90 4/8	PCL83 10/8	UCL83 10/8	X119 6/8	BD119 9/8	OA2205 9/8
1R5 5/8	6J7 6/8	12S7 6/8	A1234 19/8	19/8	EC86 12/6	FC4 12/6	PCL84 7/8	UF41 10/8	Z63 4/8	BFY50 4/8	OA2207 10/6
1R4 4/8	6K7G 2/8	12S7 6/8	A3042 15/6	15/6	EC88 12/6	FW4/500 15/8	PCL85/805 8/8	UF42 9/8	Z152 4/8	BFY51 4/8	OA2210 7/8
1S5 4/8	6K8 4/8	12S7 6/8	AC2PEN 19/8	19/8	EC91 6/8	FW4/800 15/8	PCL86 8/8	UF80 9/8	Z159 16/8	BFY52 4/8	OA2211 7/8
1T4 2/8	6K7 4/8	12S7 6/8	AC2PEN 19/8	19/8	EC92 4/8	FW4/800 15/8	PCL86 8/8	UF85 6/8	Z199 4/8	BFY53 4/8	OA2212 10/6
1U4 5/8	6K1 19/8	12S7 6/8	AC2PEN 19/8	19/8	EC93 4/8	FW4/800 15/8	PCL86 8/8	UF86 9/8	Z219 6/8	BFY54 5/8	OA2214 7/8
2A7 12/6	6L6GT 7/8	12S7GT8/8	DD 19/8	19/8	EC93 8/16	GZ30 17/8	PCL86 8/8	UF89 9/8	Z249 14/8	BFY55 4/8	OC19 25/8
2D13C 7/8	6L7 12/6	14H7 9/8	AC6PEN 7/8	7/8	EC94 11/8	GZ32 9/8	PCL86 8/8	UF10 10/8	Z259 50/8	BFY56 4/8	OC22 7/8
2D21 6/8	6L12 5/8	14H7 15/8	AC044 23/8	23/8	EC98 3/8	GZ33 12/6	PEN45 7/8	UL46 12/6	Z314 12/6	BFY57 4/8	OC23 7/8
2X2 4/8	6L18 8/8	18 12/6	AC044 23/8	23/8	EC98 3/8	GZ34 10/8	PEN45 7/8	UL46 12/6	Z314 12/6	BFY57 4/8	OC23 7/8
3A4 4/8	6L19 8/8	18A45 4/8	AC/TH11 19/8	19/8	EC98 3/8	GZ34 10/8	PEN45 7/8	UL46 12/6	Z314 12/6	BFY57 4/8	OC23 7/8
3A5 10/8	6L1D2 6/8	19H 40/8	AC/TH11 19/8	19/8	EC98 3/8	GZ34 10/8	PEN45 7/8	UL46 12/6	Z314 12/6	BFY57 4/8	OC23 7/8
3B7 5/8	6LD20 6/8	20D1 13/8	AC/TH11 19/8	19/8	EC98 3/8	GZ34 10/8	PEN45 7/8	UL46 12/6	Z314 12/6	BFY57 4/8	OC23 7/8
3D6 3/8	6N7GT 6/8	20D4 20/8	ARF3 7/8	7/8	EC98 3/8	GZ34 10/8	PEN45 7/8	UL46 12/6	Z314 12/6	BFY57 4/8	OC23 7/8
3Q4 7/8	6P15 4/8	20F2 14/8	ATP4 2/3	2/3	EC98 3/8	GZ34 10/8	PEN45 7/8	UL46 12/6	Z314 12/6	BFY57 4/8	OC23 7/8
3Q8GT 6/8	6P28 25/8	20L1 20/8	AZ1 8/8	8/8	EC98 3/8	GZ34 10/8	PEN45 7/8	UL46 12/6	Z314 12/6	BFY57 4/8	OC23 7/8
3B4 5/8	6PL12 6/8	20A5 17/8	AZ21 9/8	9/8	EC98 3/8	GZ34 10/8	PEN45 7/8	UL46 12/6	Z314 12/6	BFY57 4/8	OC23 7/8
3V4 6/8	6Q7G 6/8	20P3 18/8	AZ41 10/8	10/8	EC98 3/8	GZ34 10/8	PEN45 7/8	UL46 12/6	Z314 12/6	BFY57 4/8	OC23 7/8
4D1 3/8	6Q7GT 6/8	20P4 18/8	B36 6/8	6/8	EC98 3/8	GZ34 10/8	PEN45 7/8	UL46 12/6	Z314 12/6	BFY57 4/8	OC23 7/8
5R4GY 10/6	6R7G 7/8	20P5 20/8	B39 6/8	6/8	EC98 3/8	GZ34 10/8	PEN45 7/8	UL46 12/6	Z314 12/6	BFY57 4/8	OC23 7/8
5U4G 5/8	6R7 11/8	25A6G 5/8	B719 5/8	5/8	EC98 3/8	GZ34 10/8	PEN45 7/8	UL46 12/6	Z314 12/6	BFY57 4/8	OC23 7/8
5V4G 7/8	6R8A7GT 7/8	25L6G 5/8	B729 12/8	12/8	EC98 3/8	GZ34 10/8	PEN45 7/8	UL46 12/6	Z314 12/6	BFY57 4/8	OC23 7/8
6Y3GT 5/8	6R8A 7/8	25Y6G 8/8	BL63 10/8	10/8	EC98 3/8	GZ34 10/8	PEN45 7/8	UL46 12/6	Z314 12/6	BFY57 4/8	OC23 7/8
5Z3 9/8	6R8G 6/8	25ZAG 6/8	CL33 15/6	15/6	EC98 3/8	GZ34 10/8	PEN45 7/8	UL46 12/6	Z314 12/6	BFY57 4/8	OC23 7/8
5Z4G 7/8	6R8G 6/8	25ZAG 6/8	CV6 10/8	10/8	EC98 3/8	GZ34 10/8	PEN45 7/8	UL46 12/6	Z314 12/6	BFY57 4/8	OC23 7/8
6J30L2 12/6	6R87 3/8	25Z6G 3/8	CV63 10/8	10/8	EC98 3/8	GZ34 10/8	PEN45 7/8	UL46 12/6	Z314 12/6	BFY57 4/8	OC23 7/8
6A8G 6/8	6R87 6/8	30C1 6/8	CV271 12/6	12/6	EC98 3/8	GZ34 10/8	PEN45 7/8	UL46 12/6	Z314 12/6	BFY57 4/8	OC23 7/8
6A7 3/8	6R87GT 4/8	30C1 6/8	CV428 19/8	19/8	EC98 3/8	GZ34 10/8	PEN45 7/8	UL46 12/6	Z314 12/6	BFY57 4/8	OC23 7/8
6A65 4/8	6R87GT 4/8	30C15 13/8	CY1C 10/8	10/8	EC98 3/8	GZ34 10/8	PEN45 7/8	UL46 12/6	Z314 12/6	BFY57 4/8	OC23 7/8
6A35 9/8	6R87GT 7/8	30C17 18/8	CY31 7/8	7/8	EC98 3/8	GZ34 10/8	PEN45 7/8	UL46 12/6	Z314 12/6	BFY57 4/8	OC23 7/8
6A38 5/8	6R87GT 7/8	30C18 18/8	D1 12/6	12/6	EC98 3/8	GZ34 10/8	PEN45 7/8	UL46 12/6	Z314 12/6	BFY57 4/8	OC23 7/8
6AK5 5/8	6U4GT 12/8	30F5 16/8	D41 10/8	10/8	EC98 3/8	GZ34 10/8	PEN45 7/8	UL46 12/6	Z314 12/6	BFY57 4/8	OC23 7/8
6AK6 6/8	6U7G 10/8	30FL1 13/8	D63 5/8	5/8	EC98 3/8	GZ34 10/8	PEN45 7/8	UL46 12/6	Z314 12/6	BFY57 4/8	OC23 7/8
6AK8 6/8	6V6G 3/8	30FL2 15/8	DAC32 7/8	7/8	EC98 3/8	GZ34 10/8	PEN45 7/8	UL46 12/6	Z314 12/6	BFY57 4/8	OC23 7/8
6AL5 2/8	6V6GT 6/8	30FL12 16/8	DAF91 4/8	4/8	EC98 3/8	GZ34 10/8	PEN45 7/8	UL46 12/6	Z314 12/6	BFY57 4/8	OC23 7/8
6AM6 3/8	6X4 4/8	30FL13 8/8	DAP96 6/8	6/8	EC98 3/8	GZ34 10/8	PEN45 7/8	UL46 12/6	Z314 12/6	BFY57 4/8	OC23 7/8
6AQ5 5/8	6Y3GT 5/8	30FL14 14/8	DC390 10/8	10/8	EC98 3/8	GZ34 10/8	PEN45 7/8	UL46 12/6	Z314 12/6	BFY57 4/8	OC23 7/8
6AR6 20/8	6Y6G 8/8	30L1 13/8	D14 10/8	10/8	EC98 3/8	GZ34 10/8	PEN45 7/8	UL46 12/6	Z314 12/6	BFY57 4/8	OC23 7/8
6AT6 4/8	6Y7G 12/6	30L15 13/8	DF33 7/8	7/8	EC98 3/8	GZ34 10/8	PEN45 7/8	UL46 12/6	Z314 12/6	BFY57 4/8	OC23 7/8
6AU6 5/8	7A7 12/6	30L17 15/8	DF91 2/8	2/8	EC98 3/8	GZ34 10/8	PEN45 7/8	UL46 12/6	Z314 12/6	BFY57 4/8	OC23 7/8
6AV6 5/8	7AN7 6/8	30P4 12/8	DP96 6/8	6/8	EC98 3/8	GZ34 10/8	PEN45 7/8	UL46 12/6	Z314 12/6	BFY57 4/8	OC23 7/8
6B6G 2/8	7B6 10/8	30P4AMR17/6	DF97 10/8	10/8	EC98 3/8	GZ34 10/8	PEN45 7/8	UL46 12/6	Z314 12/6	BFY57 4/8	OC23 7/8
6B4 6/8	7B7 7/8	30P12 13/8	DE130 15/6	15/6	EC98 3/8	GZ34 10/8	PEN45 7/8	UL46 12/6	Z314 12/6	BFY57 4/8	OC23 7/8
6B6E 4/8	7C8 8/8	30P18 8/8	DF34 12/6	12/6	EC98 3/8	GZ34 10/8	PEN45 7/8	UL46 12/6	Z314 12/6	BFY57 4/8	OC23 7/8
6B6G 20/8	7D6 15/8	30P19 12/8	DIH76 5/8	5/8	EC98 3/8	GZ34 10/8	PEN45 7/8	UL46 12/6	Z314 12/6	BFY57 4/8	OC23 7/8
6B6E 7/8	7F8 12/6	30P11 13/8	DIH77 4/8	4/8	EC98 3/8	GZ34 10/8	PEN45 7/8	UL46 12/6	Z314 12/6	BFY57 4/8	OC23 7/8
6B6E 8/8	7H7 5/8	30PL13 15/8	DH81 10/8	10/8	EC98 3/8	GZ34 10/8	PEN45 7/8	UL46 12/6	Z314 12/6	BFY57 4/8	OC23 7/8
6BQ5 4/8	7H7 13/8	30PL14 15/8	DH101 25/8	25/8	EC98 3/8	GZ34 10/8	PEN45 7/8	UL46 12/6	Z314 12/6	BFY57 4/8	OC23 7/8
6BQ7A 7/8	7J7 7/8	30PL16 15/8	DH107 17/11	17/11	EC98 3/8	GZ34 10/8	PEN45 7/8	UL46 12/6	Z314 12/6	BFY57 4/8	OC23 7/8
6BR7 15/8	7Z4 6/8	30L1 13/8	DK2 10/8	10/8	EC98 3/8	GZ34 10/8	PEN45 7/8	UL46 12/6	Z314 12/6	BFY57 4/8	OC23 7/8
6BR8 12/6	9R6 7/8	30L15									

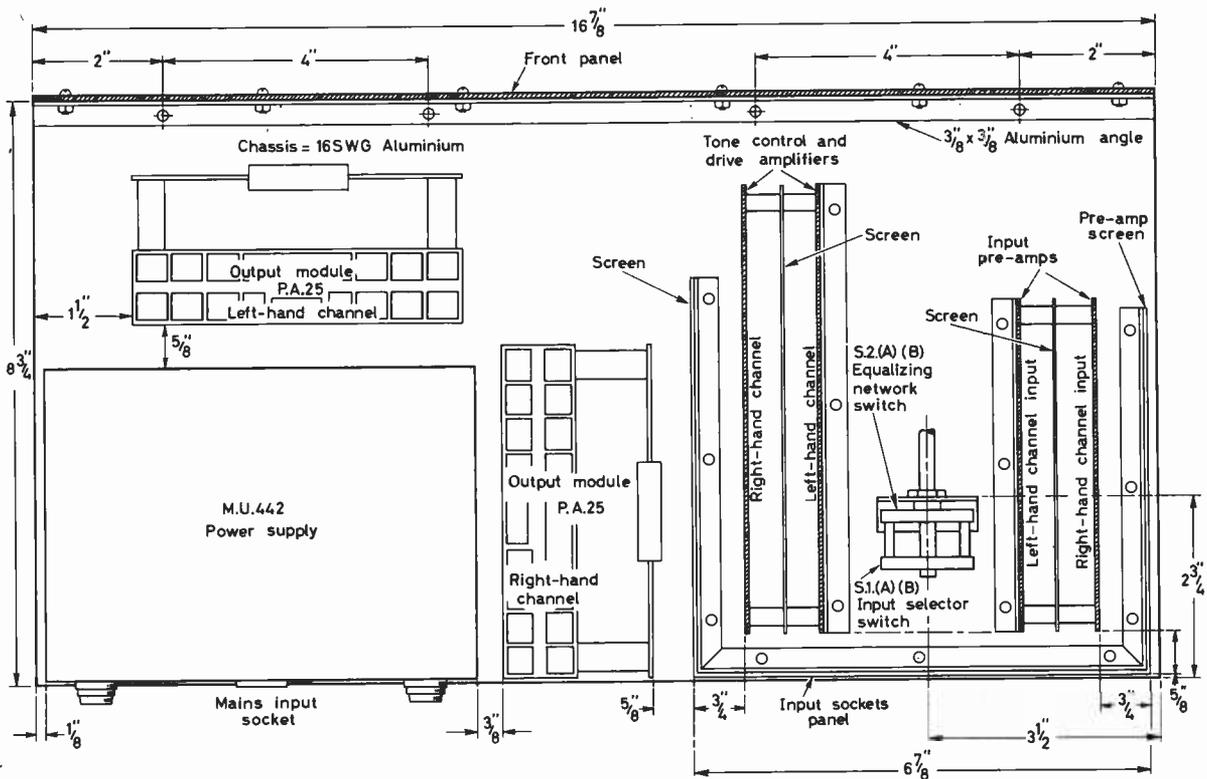


Fig. 2. Layout of units on chassis. Chassis dimensions must be adhered to if specified cabinet is to be used.

cut-outs for the mono/stereo switch (S5) the rumble filter switch (S3) and the whistle filter switch (S4) have not been given as these will depend on the physical size of the switches obtained. The front panel must be bolted to the chassis so that the lower edge is 1/4 in. below the chassis as shown in Fig. 4.

The next assembly, as shown in Fig. 5, is the U shaped screen the back section of which carries the five pairs of phono type input sockets and a pair for the tape recording outlet. No drilling details have been given for these as the fixing holes will depend on the type of sockets obtained. They should however, all be mounted centrally on the back of the screen as can be seen in the photograph. The actual mounting of the screen onto the chassis should be left until the pre-amplifiers have been

assembled, wired and secured in place.

The attenuator resistors for the inputs, which are wired directly to or across the sockets, should be fitted before the screen is secured into position. The remaining metalwork is that of making the mounting bracket for the selector switches S1 and S2. Details for this are given in Fig. 6.

Note, that all fixing screws for the power output modules, power supply, selector switch bracket and the large 'U' shaped pre-amplifier screen must be secured with counter-sunk screws with the heads beneath the chassis. The front panel must also be secured to the chassis angle piece with counter-sunk screws and with the heads on the front of the panel. These are covered with an aluminium strip as will be shown later.

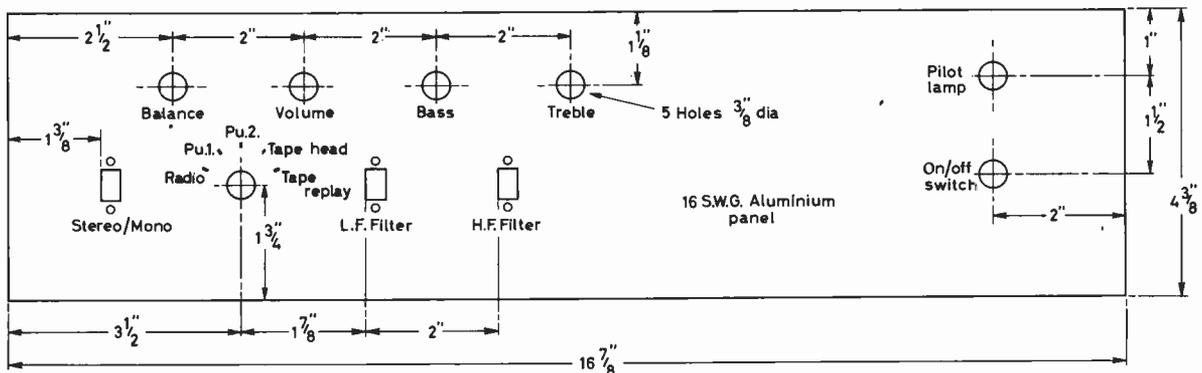


Fig. 3: Panel drilling information. Cut-outs for switches will depend on actual components used.

★ components list

Resistors:

R1 100kΩ	R5 18kΩ	R14 18kΩ	R18 68kΩ	R22 47kΩ	R26 6.8kΩ	R30 18kΩ	R34 10kΩ
R2 1.5MΩ	R6 56kΩ	R15 6.8kΩ	R19 22kΩ	R23 3.9kΩ	R27 1kΩ	R31 100kΩ	—
R3 220kΩ	R7 390kΩ	R16 22kΩ	R10 22kΩ	R24 47kΩ	R28 10kΩ	R32 270Ω	R35 1.5kΩ 1W
R4 5.6kΩ	R13 560Ω	R17 390kΩ	R21 15kΩ	R25 3.9kΩ	R29 6.8kΩ	R33 2.2kΩ	(one only)

All $\frac{1}{4}$ W 10%. Note: 2 of each required

R8 120kΩ R9 120kΩ R10 680Ω R11 220kΩ R12 8.2kΩ

All Hi-stability. Note: 2 of each required

VR1 (Balance control) 10kΩ anti-log + 10kΩ log (Henrys Radio)

VR2 (Treble control) 100kΩ + 100kΩ linear

VR3 (Bass control) 250kΩ + 250kΩ linear

VR4 (Volume control) 10kΩ + 10kΩ log.

Capacitors:

C1 2.5μF Elec.	C9 2.5μF Elec	C17 6800pF
C2 10μF Elec.	C10 3300pF	C18 10μF Elec.
C3 100μF Elec. 6VW	C11 3300pF	C19 10μF Elec.
C4 100pF S.M.	C12 10μF Elec.	C20 2.5μF Elec.
C5 3300pF	C13 0.015μF	C21 0.01μF
C6 0.01μF	C14 0.015μF	C22 100μF Elec. 6VW
C7 0.01μF	C15 0.5μF	C23 1.5μF Elec.
C8 10μF Elec.	C16 10μF Elec.	C24 5000μF 25VW

All electrolytics not less than 25V W except C3 and C22 (6V W). Two of each required except C24, 1 only.

Semi-conductors:

Tr 1 BC109 Mullard 2 off

Tr 2 BC108 Mullard 2 off

Tr 3 BC109 Mullard 2 off

Tr 4 BC108 Mullard 2 off

Power Modules and Supply:

2 Power Amplifier module Henelec Type PA25 (Henrys Radio)

1 Power Supply unit Henelec Type MU442 (Henrys Radio)

Miscellaneous:

3 Switches, DPDT, (S3, S4, S5) Slide type.

1 Switch, 2 pole 5 way with 2 wafers, ganged. (S1, S2) long spindle or use coupler.

1 Switch, SPST, mains toggle.

4 Control knobs (Eagle K30/3)

1 Control Knob (Eagle K30/4)

6 Pairs phono sockets (Henrys Radio)

1 Mains neon pilot lamp

2 Circuit boards plain s.r.b.p. $6\frac{1}{2}$ x $3\frac{1}{2}$ in. 0.15 matrix

1 Aluminium screen 20 s.w.g. same size.

2 Circuit boards plain s.r.b.p. 5 x $3\frac{1}{2}$ in. 0.15 matrix

1 Aluminium screen 20 s.w.g. same size

Note: Speaker plugs and mains input plug are supplied with the power unit Type MU442. Connecting cables and connectors ready for connection between the power amplifier modules and power supply are supplied with orders for the three units.

Chassis:

1 Chassis plate, $16\frac{7}{8}$ x $8\frac{1}{2}$ in. 16 s.w.g. aluminium.

1 Panel, $16\frac{7}{8}$ x $4\frac{1}{2}$ in. 16 s.w.g. aluminium.

1 Screen, $18\frac{7}{8}$ x $3\frac{1}{2}$ in. 16 s.w.g. aluminium (may be made from separate pieces, see Fig. 5).

4ft. Aluminium angle, $\frac{3}{8}$ x $\frac{3}{8}$ in.

Cabinet:

Amplifier cabinet, colour teak, PW1.

Amplifier cabinet, colour walnut, PW2.


Either of the above cabinets, to take a chassis to the dimensions given, can be obtained from Fircastle Ltd., 4 Eldon Way, Hockley Trading Estate, Hockley, Essex, at £3.6.0 inc. packing and postage, C.W.O. only. Cabinet includes chassis fixing screws and plastic feet.

**INTERNATIONAL AUDIO FESTIVAL & FAIR
OLYMPIA • OCTOBER 20-24**

Many New Models! in the FREE HEATHKIT 1971 Catalogue..



CONSUMER

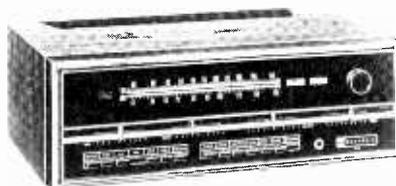

HI-FI & AUDIO



MODEL R/C CARS

Here's the bumper Heathkit catalogue for you. Read about the wonder and fascination of kit building . . . see in full colour the world's best values in Hi-Fi . . . Radio, and even model radio control. Get up to date with what's new in scientific instrumentation . . . instruments for test and service . . in fact there is a Heathkit for almost every purpose, in every walk of life. A wealth of information is all yours for the price of a postage stamp, in the Free Heathkit Catalogue.



MARINE



'TRENT' SPEAKER

- ★ No previous knowledge of electronics required.
- ★ The constructional manual supplied with every kit shows you how.
- ★ Building Heathkit models is so economic.
- ★ Save up to 50 % over factory built equipment.
- ★ Money saving direct from factory prices.
- ★ They make excellent Christmas gifts.



A Schlumberger Company

HEATH (Gloucester) LTD, GLOUCESTER GL2 6EE

Many other models in wide range . . .


**FILL IN THE COUPON FOR YOUR
FREE CATALOGUE TODAY.**

(In block capitals)

Name

Address

Post Code

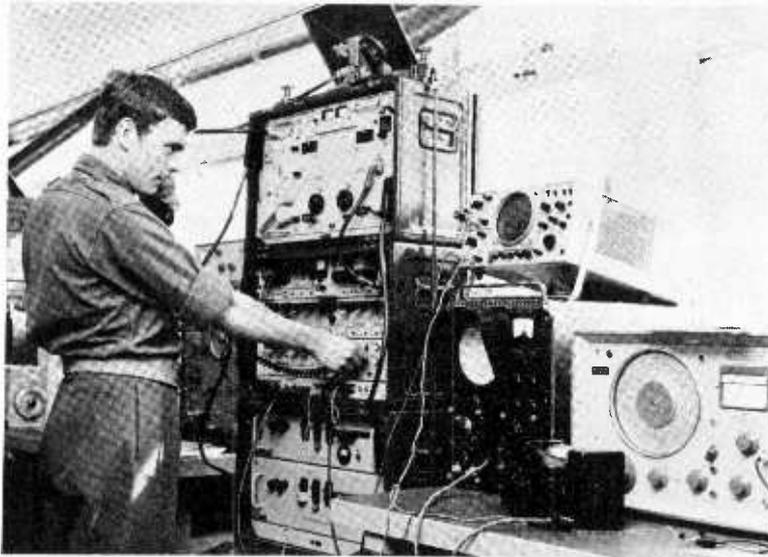

Radio Mechanics—read this now

£100 a year for a fortnight's camp plus 2 week ends

You are paid the above minimum amount for a fortnight's camp in the Summer, sometimes abroad, plus two week ends in the Winter by joining the ROYAL ELECTRICAL & MECHANICAL ENGINEERS, TERRITORIAL AND ARMY VOLUNTEER RESERVE as an Army Telecommunications Technician—Existing Volunteers find it great for a change from the same dull routine and faces. Adventure and comradeship as a member of an Army Unit are the keynotes, but full use is made of your trade skills and at least one year in every three you will be taught new techniques and new equipment as an individual at one of REME's Ultra Modern Technical Schools. As a Telecommunications Technician you will work on Army receivers and transmitters employing both valves, transistors, printed circuits and their ancillary equipment, using modern electronic test equipment. You are not expected to know it all on entry.

We are interested in men between 18 and 40 years of age with or WITHOUT former service. We want men with apprenticeships and several years' practical experience plus a good basic theoretical knowledge and are also interested in the enthusiastic amateur who does another job but spends much of his time working on (and not dreaming about) radio. We need practical men who can do a job of work.

If you are one of these tell us about your experience.

Let us send you details. Fill in the coupon and post it now.



Be a soldier, go abroad— and get paid for it

TO: CVHQ REME
BROXHEAD HOUSE, BORDON, HANTS.


Please send me details of the T & AVR REME:

Name..... Age.....

Address

Details of experience


.....
.....

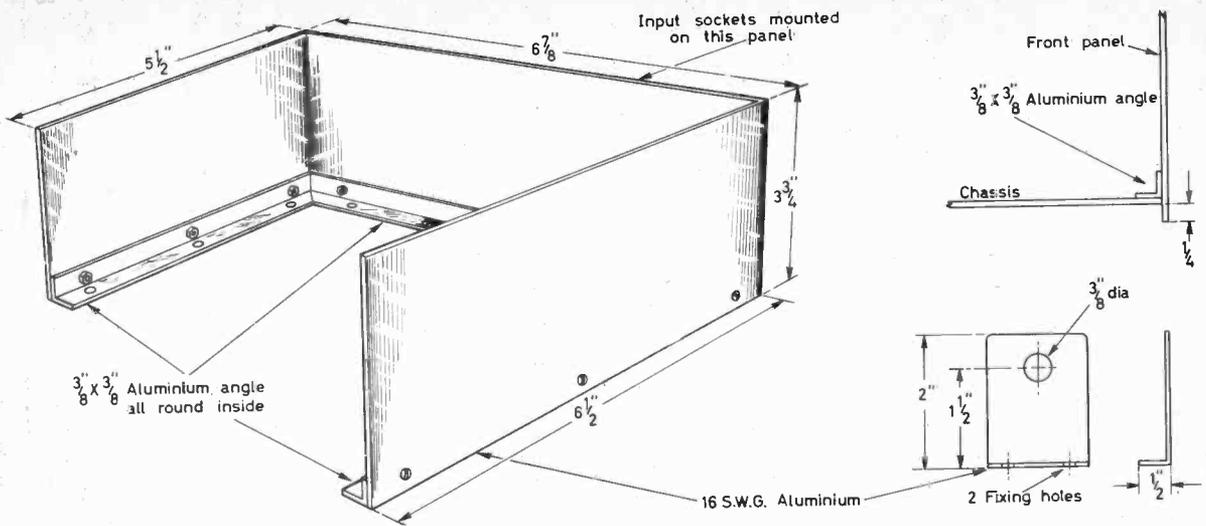

▲ Fig. 4: (top right) Fixing of panel to chassis.

Fig. 5: (above) Details of pre-amplifier screening.

Fig. 6: (bottom right) Mounting bracket for selector switches S1 and S2.

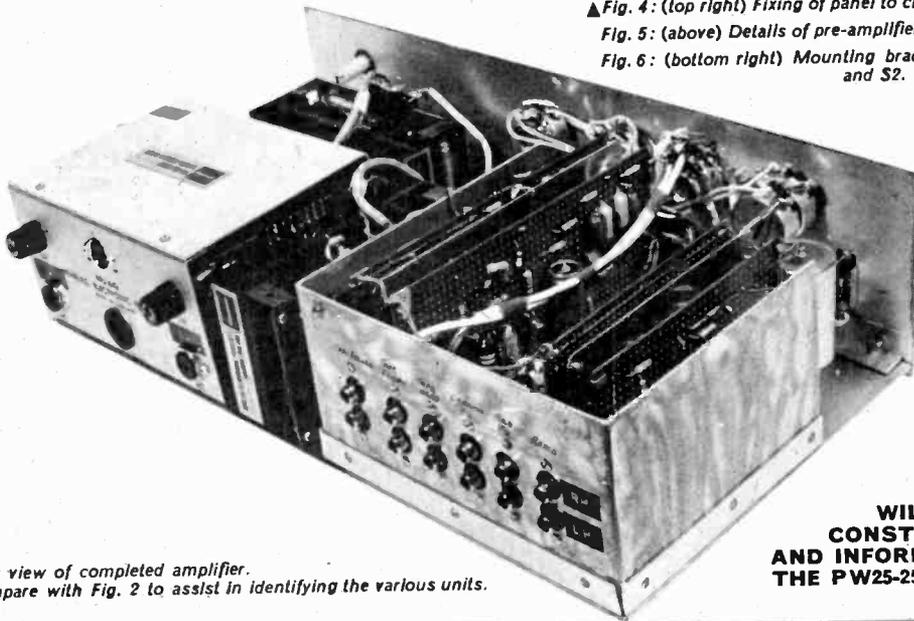

Rear view of completed amplifier.
Compare with Fig. 2 to assist in identifying the various units.

PART 2
NEXT MONTH
WILL INCLUDE FURTHER
CONSTRUCTIONAL DETAILS
AND INFORMATION ON TESTING
THE PW25-25 STEREO AMPLIFIER.

WELCOME !
TO OUR STAND

COME AND VISIT US

1970
INTERNATIONAL AUDIO
FESTIVAL & FAIR

OLYMPIA, LONDON W.14

OCTOBER 20th—24th (10 a.m.—9 p.m. each day)
The PRACTICAL WIRELESS stand will feature many
constructional features.

ORDER YOUR COPY NOW!


To (Name of Newsagent)

Please reserve/deliver the DECEMBER issue
of PRACTICAL WIRELESS (3s. 6d.), on sale
NOVEMBER 6th, and continue every month
until further notice.

NAME

ADDRESS

TUNING FACILITATED

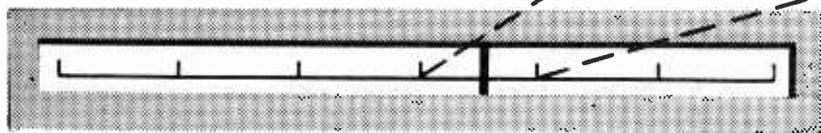

R. F. GRAHAM

THE ease of tuning and band coverage of home-constructed receivers can often be increased and extended without much difficulty. Some modifications, such as adding a fine tuning control, are very simple. Other changes, such as providing "Luxembourg bandspread" or adding an extra waveband, require more changes but can greatly increase the utility of a receiver.

Except for some points, miniature, pocket-size and commercially manufactured receivers do not usually lend themselves well to conversion.

Fine Tuner

This is a device found on certain commercial receivers, and has a vernier effect to ease the precise tuning of a transmission. Fig. 1 is a typical circuit. VC1/VC2 are the usual ganged tuning capacitor sections, with trimmers TC1 and TC2. The fine tuner VC3 is connected across the oscillator tuning capacitor VC2, and is of very small value—about 2.5pF to 4pF.

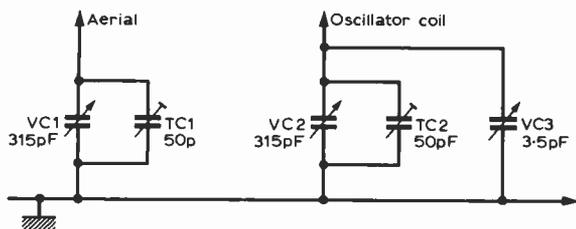


Fig. 1: The simplest form of bandspreading.

VC3 is connected to VC2 with reasonably short leads, and has a knob for panel operation. Because VC3 is so small, the practical loss of efficiency from possible mis-alignment with the circuit tuned by VC1 is ignored. With VC3 half closed, TC2 is slightly unscrewed to trim the circuits as usual (as at the h.f. end of the m.w. band). VC1/VC2 is then used as before, with VC3 as fine tuner when required.

Ganged Bandspreading

This is most appropriate in a receiver having one or more ranges, with perhaps a rather small or low-ratio drive. In Fig. 2 VC1/VC2 is the usual tuning capacitor, with trimmers TC1/2. VC3/VC4 is a 2-gang capacitor with its sections in parallel with VC1/VC2.

Since the ganged bandspreading capacitor places additional capacitance across both VC1 and VC2, it can be of larger value than VC3 in Fig. 1. About

15 to 20pF is generally best. Miniature 2-gang 17pF v.h.f. f.m. capacitors, available with built-in reduction drive if wanted, will do well. To maintain previous calibration of VC1/VC2, place VC3/VC4 half closed, and unscrew TC1 and TC2 a little to compensate.

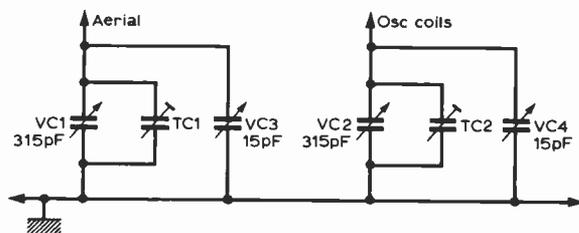


Fig. 2: Bandspreading applied to aerial and oscillator circuits.

Bandspreading in this way can be of enormous advantage when tuning s.w. signals, and also occasionally on other ranges, such as at the h.f. end of the m.w. band.

"Luxembourg Bandspread"

This is really a system which extends a small portion of the h.f. end of the m.w. band, so that it occupies the whole of the tuning capacitor swing. As an example, the usual m.w. band may be about 190-550m. Of this, the portion around 190-210m will occupy only an extremely small part of the tuning range, with the capacitor almost fully open. With "Luxembourg bandspread" a further range is obtained, about 185-210m, over the whole movement of the tuning capacitor.

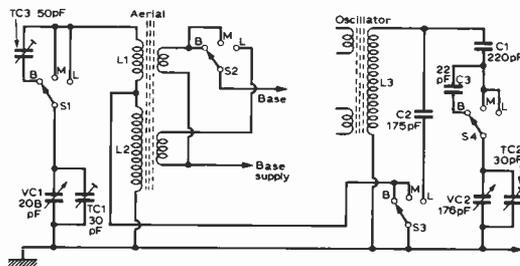


Fig. 3: Circuit providing bandspread over a part of a band.

Fig. 3 is a "Luxembourg bandspread" circuit for the usual m.w./l.w. receiver having a 208/176pF ganged tuning capacitor. A similar arrangement can be used with other receivers. The wavechange switch

WAY OUT- of the component finding maze




It may be fun finding your way out of the maze at Hampton Court, but it's not so funny trying to locate and obtain just the components you need for a particular job. In fact, the number of problems and frustrations you can meet is quite a-maze-ing!

There is an easy way out however. Simply get a copy of the Home Radio Catalogue and order whatever you need from the comfort of your easy chair. This famous radio and electronic constructor's "Bible" lists over 8,000 items, more than 1,500 of them illustrated. At only 12/6d. (8/6d plus 4/- post & packing) it's a gift—especially as each copy contains 6 vouchers, each worth 1/- when used as directed.

Once you have your Home Radio Catalogue you can make life even easier for yourself by joining our **Credit Account Service**. Then you can order by telephone any time of day or night, Sundays included! No need to bother with postal orders, cheques, registering envelopes every time you order. We send prepaid envelopes and you make only one payment each month. So simple! Write for details or telephone 01-648 8422.

YOUR FIRST STEP out of the maze—*Post the Coupon with your cheque or P.O. for 12/6d*

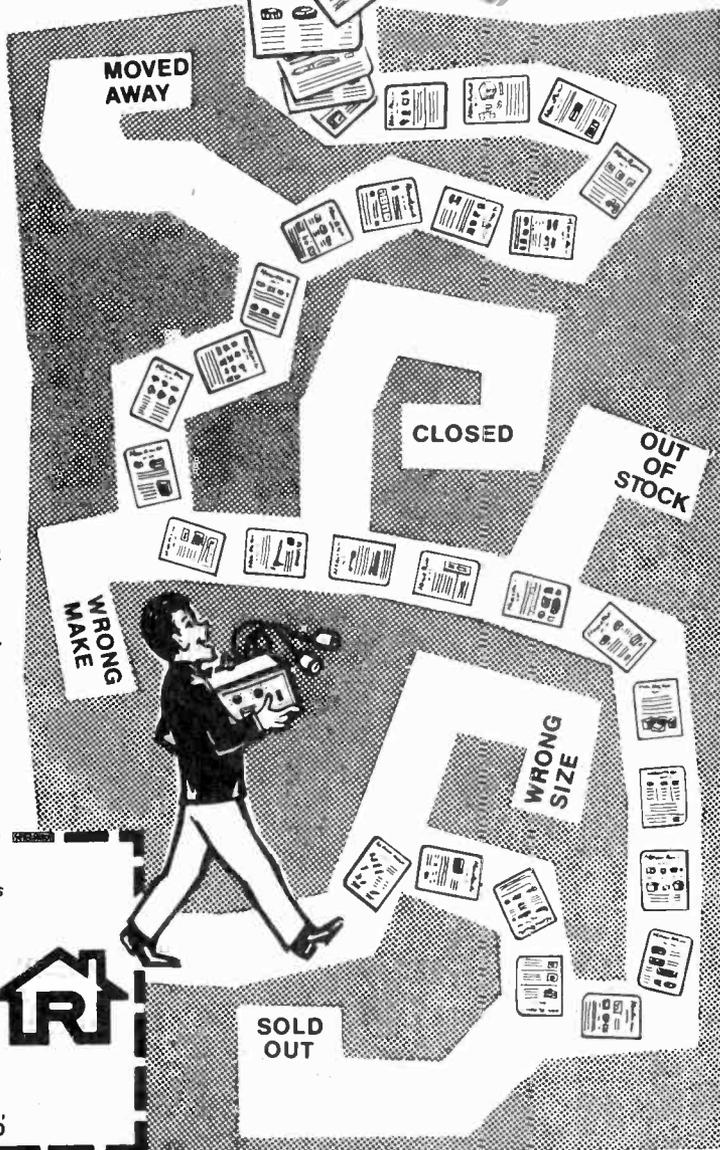The price of 12/6d applies only to catalogues purchased by customers residing in the U.K.



Please write your Name and Address in block capitals


NAME

ADDRESS



HOME RADIO (Components) LTD., Dept. PW,
234-240 London Road, Mitcham, Surrey, CR4 3HD

IN OCTOBER ISSUE

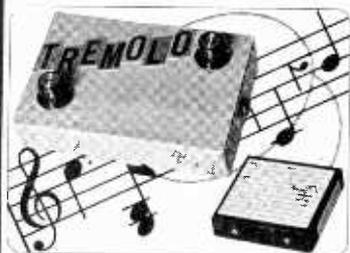

ULTRA-SIMPLE TREMOLO UNIT

Using very simple circuit techniques, this economic design is capable of providing tremolo modulation of an electric musical instrument which is controllable both in depth and speed.

FREE

A three-page art paper cut-out colour supplement featuring Circuit Diagram, Components List, Printed Board Details, Point-to-Point Wiring Diagram and Cabinet Details for this 2-transistor (ACY-19, OC44) unit.

*** SPECIAL WORKSHOP * EQUIPMENT OFFER**

PLUS

● **MANY OTHER PROJECTS AND FEATURES**

● **DATA SHEET No. 43**

ON SALE NOW 3/6

Copies may also be obtained direct from the Publishers 4/- including postage. Published by:

Data Publications Ltd.
57 Maida Vale, London, W.9

SHORTWAVE TRANSISTOR RADIO

Can be built in one evening



ONLY 45/-

At last! After trying countless circuits searching for easy build, work-first-time short waver, giving advanced world-wide performance, we chose this 'Sky Roma'. Anyone from 9 years up can follow the step-by-step, easy-as-ABC, fully illustrated instructions. (We built ten prototypes and everyone worked first time) no soldering necessary. 76 stations logged on rod aerial in 30 minutes—Russia, Africa, U.S.A., Switzerland, etc. Experience thrilled of world wide news, sport, music, etc. **Eavesdrop on annual broadcasts.** Uses PP3 battery. Transistorised (no valves!). Size only 3" x 4 1/2" x 1 1/2". **As tremendous demand anticipated price held in only 45/- + 3/6 p. & p.** for all parts including Cabinet, screws, instructions, etc. (Parts available separately). Money back guarantee.

MAKES 5 DIFFERENT TRANSISTOR RADIOS TOTAL BUILDING PRICE 39/6



Amazing Radio Construction set! Become a radio expert for 39/6. A complete Home Radio Course. No experience needed. Parts including instructions for each design. Step-by-step plan, all Transistors, condensers and resistors, knobs, screws, etc. all you need. Box size 14" x 10" x 2" (parts avail. sep.). Send only 39/6 + 4/6 P. & P. Money back guaranteed.

CONCORD ELECTRONICS LTD. (PW18)
8 Westbourne Grove, London, W.2
(near Baywater Tube) (Callers 9-6 inc. Sat.)

LOOK AT THESE PRICES

CARTRIDGES

Acos GP67-2, GP91-38C 22/6; Acos GP93-1 26/8; Acos GP94-1 22/6; Sonotone 9TAHC 29/6; All above in makers cartons; BSR X4H 30/-.

1 WATT AMPLIFIER

Complete with volume control, rectifier, smoothing cct, fully transistorised, **OUR PRICE 27/6**

PLUGS & SOCKETS

Phono plugs, red, white, yellow, green, grey, blue, black 11d 9/- per doz; Coaxial plugs, aluminium 1/6; Coaxial couplers 1/-; 2 pin DIN plugs 3/-; 3 pin DIN plugs 3/-; 5 pin DIN plugs 3/5; 2 pin, 3 pin DIN sockets 1/8; wander Plugs 6d; sockets 8d; Banana plugs 1/1, sockets 1/-; 3.5mm J/Plugs 1/6 & 2/6; Standard J/Plugs with solder terminals 2/-; Chrome 2/-; Side Entry J/Plugs black and chrome 4/9; Insulated j/sockets, o/cct 3/3, c/cct 3/6.

ELECTROLYTIC CAPACITORS

4uF, 150v 9d; 8uF 500v 3/-; 8uF 12v 10d; 8uF + 8uF 450v 4/3; 10uF 150v 9d; 12uF 25v 9d; 16uF 450v 2/9d; 16uF + 16uF 450v 4/8; 30uF 10v 9d; 50uF 10v 9d; 100uF 9v 9d; 100uF 12v 9d; 150uF 12v 9d; 320uF 9v 1/-; 1500uF 30v 3/9; 2.5uF 16v 6d; 10uF 16v 1/8; 5000uF 25v 10/-; 10,000uF 25v 15/-; 20,000uF 30v 21/-.

MICROPHONES

Acos Mic 45 22/6; Acos Mic 60 19/11; Planet CM70 30/-; Hand Mike 15/-; Shure 201 25; Shure 444 110.10.0.

VALVES

PY81 7/2; PCL82 7/9; EF183 9/-; EF184 9/-.

PLEASE NOTE CHANGE OF ADDRESS

GEORGE FRANCIS (Dept PW),

12-14, Middle Gate, Newark, Notts.
Telephone: Newark 4733.

WELBROOK HI-FI AMPLIFIER KIT

During last year Welbrook introduced to the Hi-Fi field their unique output stage which was a completely new break-through in high-fidelity Audio Design. It enabled us to produce an amplifier, giving a level of distortion at low output levels, normally associated with CLASS A or truly complimentary output stages, but still retaining the low relative cost and advantages of a CLASS B quasi-complimentary stage.

To maintain our position as a forerunner in the audio field, we now introduce this amplifier in kit form.

Consider the following brief specification and then note the price.

POWER OUTPUT:
10 watts R.M.S. per channel (8 ohms).

T.H.D.:
Typically less than 0.1% for all output levels up to 10 watts.

INPUTS:
Magnetic — ceramic — crystal P.U.
Tuner.
Tape.

OUTPUTS:
4 — 8 — 15 ohms.
Tape Output.

The kit consists of a fibreglass P.C.B., 20 silicon transistors, 12 silicon diodes, approximately 140 electronic components, and all materials required to complete a chassis mounted amplifier, including front panel and knobs.

PRICE: £32 0s. 0d.
(Cabinet Extra).

Further details and fully illustrated leaflets available.

Welbrook Engineering and

Electronics Limited

Brooks Street, Hr. Hillgate, Stockport, Ches.

Phone: 061-480 4268.

is removed, and replaced by a small 3-way, 4-pole rotary switch. This has three positions, Bandsread, Medium Waves and Long Waves.

VC1/VC2 tunes aerial and oscillator inductors, and has trimmers TC1 and TC2. For l.w. reception, L1 and L2 are in series, tuned by VC1. S2 switches the mixer transistor base to the coupling winding of the long wave section of the ferrite rod aerial, L2. S3 brings the capacitor C2 across L3, for oscillator tuning, while S4 connects VC2. For m.w. tuning, S3 shorts out L2 and S2 switches to L1 coupling winding. After fitting the 3-way switch, normal l.w. and m.w. reception should be obtained with the switch in its appropriate position.

With the switch at Bandsread, S2 and S3 are for m.w. coverage as before. S4 places C3 in series with VC2, so that the capacitance swing for the full rotation of VC2 is greatly reduced. S1 brings TC3 into series with VC1, for a similar limited frequency coverage here. This circuit is aligned in the usual way for m.w. reception. The switch is then put to Bandsread and a transmission tuned in with VC1/VC2 fairly well closed. TC3 is then carefully adjusted for best results. TC1 and TC2 may be adjusted, if necessary, for a coverage of about 185-210m.

Some circuits have separate trimmers for m.w. and l.w. If so, these can generally remain unchanged. Bandsread coverage can be changed by altering C3 which can be a pre-set trimmer. In some circuits both TC3 and C3 are fixed.

Manual Control

Many receivers have a 208/176pF capacitor with knob or dial directly on the shaft. Some capacitors of this kind are available with an integral ball drive, requiring no additional space. This will be found to ease manual adjustment of tuning.

In some home-built and other receivers it is possible to fit a 6:1 or other small ball drive to the capacitor spindle, setting the capacitor back a little on a bracket, or long bolts.

Adding 1,500m or Long Waves

Some receivers cover medium waves only, but in some parts of the country long wave coverage is extremely useful. This may tune a band around 1500m only, or give full l.w. coverage of about 1100-2000m.

Fig. 4 has the advantage that the aerial needs a m.w. winding only. This is L1, tuned by VC1 with trimmer TC1. L2 is the osc. coil, with usual padder Cp, and tuned by VC2. For 1500m, the switch places C1 across L1. Oscillator tuning is changed by C2, in a similar way to circuits with full l.w. coverage. This circuit does not give full l.w. band coverage, but allows VC1 to tune around 1500m.

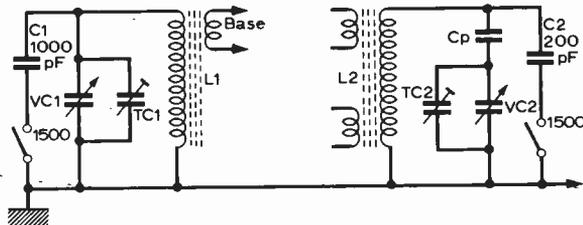


Fig. 4: Adding l.w. coverage to a receiver.

The values for C1 and C2 were suitable for an actual typical receiver, but should be checked by experiment first. C1 can be fixed and pre-set capacitors in parallel, adjusted until 1500m is reached with VC1 about half closed. A quite large trimmer (say 500pF) is required. C2 may also be a combination, such as 175pF fixed capacitor with 60pF parallel trimmer.

If the receiver is a midget design with no free space, a large variable ganged capacitor can be temporarily used at C1, and a smaller variable at C2. These are adjusted to tune 1500m, then disconnected. Their capacitances are measured, and suitable silver-mica fixed capacitors used in their place. With some simple t.r.f. receivers covering m.w. only, adding a suitable capacitor C1 will allow 1500m to be tuned with reasonable efficiency.

Two-band Tuning

When full medium wave and long wave coverage is required, a l.w. winding is used on the ferrite rod. Fig. 5 is a circuit which requires only a miniature 2-way slide switch.

VC1 tunes L1 for m.w. coverage, L3 being shorted out, and L2 being for base coupling. VC2 tunes the oscillator coil L4, with padder C1. M.W. trimming is by adjustment of TC1 and TC2 with alignment at the l.f. end of the band by moving L1 on the ferrite rod and adjusting the core of L4 in the usual way.

For l.w. coverage, the switch leaves L1 and L3 in series, and also brings in the additional capacitor C2, with trimmer TC3. L.W. alignment is by adjusting the position of L3 on the ferrite rod, and by TC3.

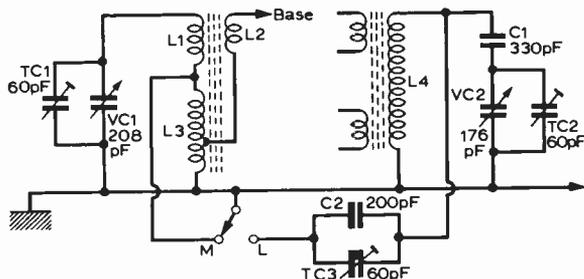


Fig. 5: Simple circuit for two-band coverage.


Ferrite rod aerials and oscillator coils for long and medium wave coverage are produced by several manufacturers. They are designed for particular capacitor values at C1 and C2, and some employ further switching, such as of base coupling windings. So the circuit and component values specified by the maker of the actual aerial fitted must be adhered to.

A Short Wave Band

A receiver may cover l.w. and m.w. only, and it is often possible to add a short wave band, if certain important points are not overlooked. Other receivers may have a s.w. band, but another range to cover other wanted frequencies may be required.

Fig. 6 is a typical multi-band circuit for which long, medium, and short wave coils are available (Denco) giving coverage up to 30MHz, or 10 metres.

—continued on page 573

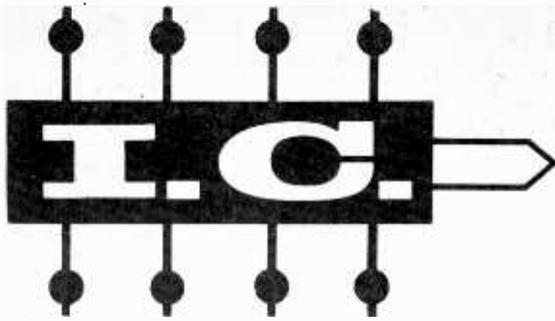

OF THE MONTH

L.A.J. IRELAND

Number 13

Mullard TAA320 Bi-fet Pre-amplifier

IT is difficult to decide whether to regard our topic this month as an i.c. or as a novel type of discrete circuit element developed and manufactured by the methods employed for integrated circuits. I am referring to the Mullard TAA320, which the supplier describes as an "Integrated metal oxide silicon l.f. preamplifier," or more imaginatively in the U.S.A. as a "bifet."

It is obvious by now that a few terms will have to be defined before designs and applications can be discussed. Readers will be familiar with the fact that as well as the now familiar transistor operating with two opposed p.n. junctions (and therefore properly described as a "bipolar" device) there exists also the more recent "field effect transistor" or f.e.t.

Description

This device, as the name implies, does not depend on the conduction characteristics of junctions, but is more nearly equivalent to the valve in its mode of operation, with a gate electrode controlling the current from source to drain. The gate is insulated from the conduction channel between source and drain by a very thin layer of a metallic oxide, and as would be expected, the standard modern f.e.t. is based on silicon technology. Hence the full title, metal oxide silicon field effect transistor, or *m.o.s.f.e.t.* (Just to add to the complexity, some references will indicate that the *m.o.s.f.e.t.* is a specialised form of the *i.g.f.e.t.* the name deriving from the fact that it has an insulated gate).


As is well known, the bipolar transistor is a current operated device, with the injection of charge carriers into the base from the emitter region. The f.e.t. is much more like the valve in its mode of operation, being a purely voltage controlled ("field") device. It therefore shares with the valve the high input impedance characteristic so useful in sensitive

low noise amplifiers, yet requiring some complicated feedback system in bipolar circuits. It is therefore a "natural" for use with crystal pick-ups, strain gauges, electrometers and similar signal sources with very low current levels but with voltages of the order of tens of millivolts.


Table 1: Ratings of TAA320

Drain to source volts	V_{DS}	20V max
Gate to source volts	V_{GS}	20V max
Gate to source max. non repeating surge		100V max
Drain Current	I_D	25mA max
Power dissipation		200mW max
Gate to source resistance		10^{11} ohms min.
Noise voltage (typical, 50Hz-15kHz $I_D=10mA., V_{DS}=10V$)		25 microvolts

The voltage gain of an f.e.t. alone is less than unity (typically 0.9) but the current gain is up to 1000, and therefore a good power amplification is associated with a very low noise figure. The advance which the TAA320 represents is that it associates the low output impedance and associated ease of matching to following circuits which is typical of the bipolar transistor with the input characteristics which give the f.e.t. its attractions. Finally, the price of around 13s. is strikingly less than an f.e.t. alone cost only a year or so ago.

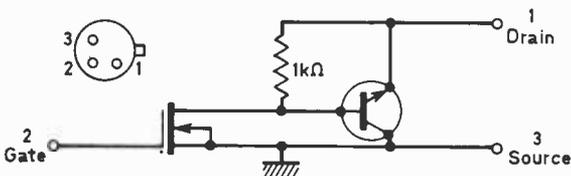

Circuit diagram of the TAA320.

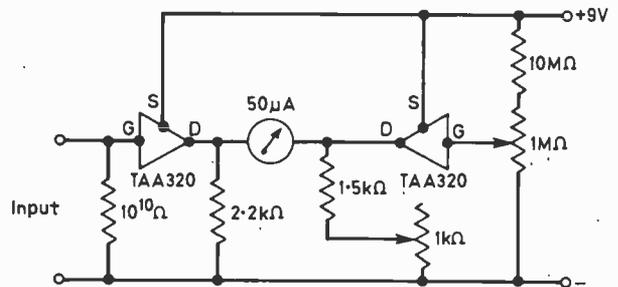


Electrometer or Instrumentation amplifier using two TAA320's.

Applications

Now for a few ideas on applications. The feature which will be noted first is the shorting clip with which the device is fitted when supplied. The reason is that the insulation of the gate, while inherently of a very high resistance, is subject to failure before the device is installed should it be subject to static charges, such as those workers may induce through friction with synthetic fabrics.

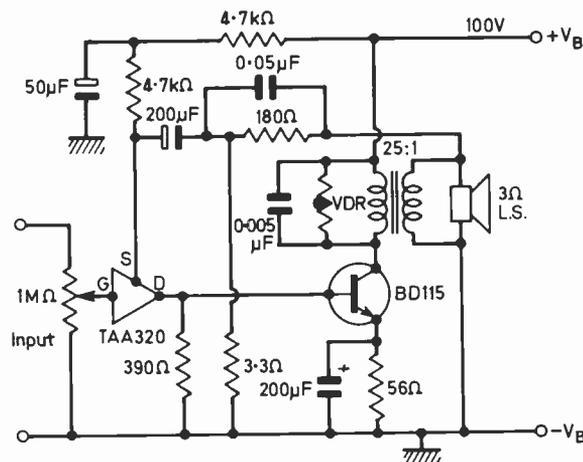These charges, though small, represent voltages much higher than the hundred or so which will "punch through" the gate insulation. After incorporation in equipment, however, the device is protected against such an event by the presence of the associated bias resistor and other external circuitry, and thereafter shares the reliability which is associated with modern silicon semiconductors.



2 watt audio amplifier for high-impedance microphone or pickup.

This should be taken as a warning, though, *not to accept units lacking this clip*, since they may have been damaged in transit, and further, not to remove the clip until the unit is safely soldered in place.

The application circuit diagram given shows a 2 watt silicon semiconductor amplifier designed to match a crystal pickup or microphone signal source; the BD115 stage may, of course, be replaced by any power amplifier of higher power at the discretion of the constructor. Further, a basic electrometer (microammeter) or instrumentation amplifier is also shown, which can be used for strain gauges, pH meters, or other devices in the amateur laboratory or for "science fair" projects. ■

"Project Autumn"

compete for the
Practical Wireless
"Designer's Trophy"



Readers of
Practical Wireless are
invited to submit articles for
publication and to compete
for the
Practical Wireless
"Designer's Trophy"

RULES.

1. Articles submitted for the competition should conform to the general style of material published in *Practical Wireless* and must describe the operation and construction of a piece of radio, audio or test equipment that has been designed and built by the author.
2. Articles should, preferably, be typed using double spacing, leaving wide margins, and on one side only of each sheet. Circuit diagrams and any other drawings should be on separate sheets and numbered to agree with the text. Author's roughs must be clear enough to permit re-drawing. Component lists must also be separate and laid out to the standard PW format.
3. Photographs of the equipment are desirable and should be in black and white, sharp and clear. Each photograph should be identified by sticking a piece of paper on the back rather than by writing on the photograph itself.
4. Components used in the design must be readily available from retail sources.
5. An entry form, properly completed, must accompany each article submitted. There is no limit to the number of articles submitted by any one author.
6. Articles must reach the Editor, *Practical Wireless*, Old Fleetway House, Farringdon Street, London, E.C.4. by the first post on Monday, November 2nd 1970 with the envelope and title sheet clearly marked "Project Autumn". A stamped, self-addressed envelope must accompany each entry.
7. All entries submitted will be considered by a panel of judges and the Editor's decision on all matters arising will be final. The Editor will require authors of winning entries to submit the equipment to him immediately on request for final assessment by the panel.
8. Employees and staff of *Practical Wireless* are not eligible for entry to this competition.
9. The winner of the competition will receive and retain outright the *Practical Wireless* "Designer's Trophy 1970". Other prizes will be awarded to the best runners-up. Any article published will be paid for at normal rates.

practically wireless

commentary by **HENRY**

Games
People play

IT was once again underlined at a recent IEA Exhibition at Olympia: engineers are children at heart.

Among the gleaming computers, the hardware and software of this electronic age, the queues could be seen forming for the Honeywell, Computer Technology and Electronic Associates stands. And why? because these lads had learned the secret of audience participation.

Hardworking electronic engineers had saved and scrimped—their energy if not their cash—towards this day's outing, and were not to be cheated. To heck with the hard facts, one could read those up tomorrow: let's have a go at some competitive pastime and try to win a week with a dolly-bird in remotest Canvey Island—or something.

More often than not it was less than nothing.

The sort of prize that the intellectual gentlemen on the computer stand tends to offer is merely the satisfaction of competing. Not, you will note, of having won. Like the Mullard "Grasp the Ball" gimmick that caught attention when the Radio Show was a one-piece exhibition (do you remember that far back, Joe?) the principle of electronic games is usually to demonstrate that frailty is human and the machine will always win.



A week with a dolly-bird in Canvey.

Of course, there is a serious purpose behind these games; the need to demonstrate the wide range of parameters the computer can handle, and the speed with which it churns out its solutions. But when Henry reads those wonderful "ten thousand decisions in only ten seconds" claims, he is sorely tempted to ask what was done with the minutes saved. Did some clever fellow find time to polish up a sonnet?

But let's not think that all was serious study at Olympia—although the concentration of some of those gamesters was in direct contrast to the open grins and carefree words of some of the fortune hunters on the peripheral stands. (Henry is no tipster, but if he had a few quid to spare, they would go into computer peripherals, where there seems to be no limit to development).

Some of the more rewarding games included a free holiday from MCP Electronics for the solution to a simple word game, and a free bottle of Scotch from the Marconi-Elliott Microelectronics stand. One does not easily obtain the products of Glenrothes, even by paying, so it is as well to mention that the prize was only offered to visitors who could pick a dud microcircuit in a batch of 10,000 randomly shipped from the factory.

Beauty of this competition was that it gave the trier a chance to do a spot of fault-finding with the Tetradyne. After seeing the recent Mullard film on microcircuit testing and reading about the RCA tester that vets a phenomenal number of ICs daily, Henry began to wish he could rig up a universal tester in his workshop into which all the tough dogs could be fed. But what would I do with the time I saved?

Oh yes, there was a treasure hunt. There had to be a treasure hunt. What would any electronics



What's done with the time saved?

exhibition be without its treasure hunt, I ask you?

This one had a serious portent. Beckman Instruments are rather proud of the fact that they introduced the first commercially available pH meter 35 years ago. They are celebrating their anniversary (thirty-fifth, what's that?) They hope that some hoarder will have an old instrument tucked away in the loft—or, to be even more satisfying, still in operation. The winner to be flown to the company headquarters at Fullerton, California, to receive his prize.

The irony is that the prize will be a new pH meter, a digital version, no less.

It is hard not to accuse Celdis of opportunism when one reads—one dared not participate—that their competitive venture was a chance to specify the design and equipment for their new application laboratory at Reading. The winner did not get the offer of the job of chief designer, but merely pocketed 100 guineas.

There, we fell to discussing the layout and design of wireless repair workshops.

It would not be a bad idea to start *PW* readers along those lines—Henry offers two guineas for the most fruitful and original idea towards the design and equipment of a small workshop. How's that for a game worth playing?

CAVE

TOP DISCOUNTS HI FI

5 Bridge Street
Richmond Surrey
01 948 1441 till 8pm

OPEN ALL DAY SATURDAYS
FIRST CLASS REPAIR SERVICE
UP TO 15% DISCOUNT ON
LP RECORDS
SEND FOR LISTS

Our demonstration rooms are equipped to enable you to listen to at least 40 different speakers and a large range of amplifiers, tuners, tuner-amplifiers, together with turntables, for you to compare the kind of sound you can get from both budget low-price systems and higher more sophisticated systems.

L.P. RECORDS—Up to 15% off. Send S.A.E. for lists. Our stock of new equipment is extensive and carries full manufacturer's guarantee. The above list is only representative of the equipment stocked by us. Equipment can be installed in any part of London, customers rarely being kept waiting. Overseas Customers welcome. Personal Export arranged.

P & C on most units 12/16. Insurance: 2/- per £10 value.
P & C on Tape Recorders is 17/6.

Prices quoted above are our selling prices at the time of going to press and are subject to alteration E. & O. E.

Special Carriage Charges for 48hr. Delivery Services.

	List Price	Cave's Cash Price
TURNTABLES		
MacDonald MP80	£15 0 0	£12 10 0
MacDonald 610	£18 19 0	£15 17 0
MacDonald 510	£16 0 0	£13 8 0
MacDonald 310	£12 19 0	£10 16 0
MacDonald Base & Cover	£7 12 0	£5 7 0
Dual 1219	£50 8 0	£4 6 0
Dual 1209	£42 12 0	£38 6 0
Transcriptor Reference	£98 2 0	£86 5 0
Transcriptor	£57 12 0	£50 19 0
Garrard 401	£31 14 0	£28 10 0
Garrard SL95B	£45 9 0	£38 19 0
Garrard SL75B	£35 12 0	£31 12 0
Garrard SL55B	£19 6 0	£16 12 0
Garrard AP75	£22 12 0	£18 12 0
Garrard SP25 Mk. II	£15 9 0	£11 12 6
Garrard AP76 Transcription Unit		Send for details
SPC1 & WB1	£7 11 0	£6 15 0
SPC4 & WB4	£10 2 0	£9 3 0
Goldring GL69 P & C	£39 17 1	£35 3 7
Goldring GL75 P & C	£49 2 8	£45 1 2
Goldring GL75 P & C and G800E	£68 9 11	£58 2 4
Goldring GL69 P & C and G800	£52 17 2	£44 18 11
Phillips 202	£64 0 0	£56 6 0
Thorens TD150A Mk. II	£43 13 0	£39 6 7
Thorens TD150AB Mk. II P & C	£51 11 0	£45 9 0
Thorens TD125	£75 17 0	£68 7 0
Thorens TD125 with P & C	£90 9 0	£79 16 0
Pioneer PL11AC	£48 17 7	£40 19 0

	List Price	Cave's Cash Price
SPEAKERS		
B & W DM3	£63 0 0	£53 11 0
B & W DM1	£32 0 0	£27 4 0
B & W 70 Monitor	£139 10 0	£118 10 0
EMIR Mk. 1	—	£15 19 0
EMIR Mk. 2	—	£19 10 0
Celestion Ditton 15	£29 0 0	£25 8 0
Celestion Ditton 25	£59 17 0	£50 17 0
Goodmans Magister	£57 0 0	£48 0 0
Goodmans Mezzo K	£40 2 0	£32 10 0
Goodmans Mezzo II Walnut	£30 18 0	£22 19 0
Goodmans Mamba's	£22 6 6	£18 5 0
KEF Celeste Mk. 2	£29 0 0	£23 19 0
KEF Concord	£43 10 0	£33 10 0
KEF Concerto	£53 19 0	£45 9 0
KEF Choral	£34 16 6	£30 17 0
Leak Mini—Sandwich Walnut	£29 15 0	£20 10 0
Leak Mini—Sandwich Rosewood	£29 15 0	£22 10 0
Leak Sandwich Teak	£45 10 0	£31 5 0
Leak Sandwich Rosewood	£45 10 0	£33 19 0
Wharfedale Denton	£19 0 0	£16 15 0
Wharfedale Super Lintons	£22 10 0	£19 19 0
Wharfedale Dovecote 3	£39 10 0	£32 10 0
Wharfedale Melton	£29 10 0	£23 19 0
Wharfedale Rosevale	£59 10 0	£49 18 0
Phillips GL5170 Enc.	£26 19 0	£22 19 0
Phillips RH482 pair	£36 0 0	£34 14 0
Quad Electrostatic	£66 0 0	£59 8 0
Radon SC/1 Amethyst	£13 17 11	£12 5 0
Radon SC/3 Opal	£24 0 0	£21 0 0
Rogers Ravensbrook	£47 10 0	£41 11 0

	List Price	Cave's Cash Price
Tannoy 12" Lancaster	£56 5 0	£49 5 0
Tannoy 15" Lancaster	£63 5 0	£55 7 0
Tannoy 111LZ	£41 0 0	£35 18 0
Tannoy Richmond 12"	£46 10 0	£39 11 0
Lowther PM6 Acousta	£58 0 0	£49 6 0
Pioneer CS53	£41 13 0	£35 8 0
Sansui SP30	£31 8 7	£27 13 0
Jordan Watts		Prices upon application

	List Price	Cave's Cash Price
CARTRIDGES		
Audio Technica AT-66	£6 4 8	£5 10 0
Audio Technica AT-66L/C	£6 4 8	£5 2 0
Audio Technica AT-21	£8 14 4	£7 13 0
Audio Technica AT-21X Elip.	£15 9 11	£12 19 0
Audio Technica AT-35X Elip.	£24 4 0	£14 19 0
Audio Technica VM3	£13 0 9	£11 10 0
Decca Deram Stereo	£5 5 0	£4 5 0
Orbit Magnetic	—	£4 5 0
Sonotone 9TAH/C Diam.	£4 0 6	£2 8 0
Sonotone 9TAH/C Sapp.	£7 8 3	£2 0 0
Shure M44-M	£11 2 4	£8 19 0
Shure M44-S	£10 3 10	£8 19 0
Shure M44 Elip.	£12 11 0	£9 19 0
Shure M55 Elip.	£12 19 5	£11 5 0
Shure M75-E	£16 13 6	£14 0 0
Shure M75-EI	£21 6 2	£17 17 0
Shure M75 Mk. 2	£40 15 3	£32 10 0
Shure V-15-7	£38 18 0	£27 10 0
Shure M75-G	£17 12 0	£14 15 0
Shure M91-E	—	£17 17 0
Goldring G800	£13 0 1	£8 19 0
Goldring G800E	£16 17 0	£13 12 0
Goldring G850	£6 10 0	£5 9 0
Goldring G800 Super E	£26 0 1	£19 19 0

	List Price	Cave's Cash Price
TUNERS		
Pioneer TX500	£79 5 3	£66 0 0
Pioneer TX900	£151 19 6	£126 15 0
Quad FM	£51 0 0	£46 0 0
Quad AM3	£48 0 0	£44 12 0
Rotel 120 ST	£49 17 8	£42 10 0
Teleton GT101	£45 10 0	£38 0 0
Wharfedale WFMT 1	£53 6 10	£37 10 0
Armstrong 524	£53 15 3	£47 19 0
Armstrong 523	£41 17 8	£37 14 0
Dual CT15	£81 15 6	£71 17 0
Dual CT16	£106 0 0	£93 3 0
Lux WL313	£143 14 7	£92 11 0
Lux WL515	£108 5 3	£75 15 0
Leak Stereofetic Chassis	£58 18 4	£53 19 0
Radford SMT3	£76 10 0	£64 19 0

	List Price	Cave's Cash Price
TUNER/AMPLIFIERS		
Pioneer SX440	£111 1 11	£92 15 0
Pioneer LX440	£116 9 11	£97 5 0
Pioneer LX800	£206 18 10	£181 16 0
Pioneer SX700	£156 0 3	£130 5 0
Pioneer SX900	£193 2 0	£161 5 0
Pioneer SX1500	£225 17 10	£188 13 0
Pioneer KX330	£78 15 11	£66 0 0
Lux 555	£168 0 0	£119 18 0
Rotel No. 130	£79 17 2	£67 12 0
Rotel FA X330	£95 0 5	£79 16 0
Rotel FA X660	£129 0 0	£99 19 0
Sansui 350	£129 2 0	£113 10 0
Sansui 400	£127 4 3	£99 0 0
Sansui 800	£145 19 7	£128 8 0
Sansui 2000	£162 3 0	£142 12 0
Teleton CR10T	£39 15 0	£26 19 0
Teleton TFS50	£74 0 0	£62 16 0
Wharfedale 100.1	£131 5 0	£112 13 0
Akal AA6600	£142 10 7	£125 9 0
Armstrong 525	£91 17 9	£81 19 0
Armstrong 526	£104 14 3	£93 19 0
Dual CR40	£178 1 3	£156 10 0

	List Price	Cave's Cash Price
HEADSETS		
Akal ASE9	£6 10 0	£5 14 0
Akal ASE20	£9 0 0	£7 18 0
Akal AEH10	£20 0 0	£17 0 0
Beyer DT48	£33 18 0	£27 19 0
Beyer DT48S	£33 14 0	£28 19 0
Beyer DT100	£13 18 6	£11 17 0
Beyer DT109	£23 18 6	£20 7 0
Beyer DT480	£29 5 0	£24 17 0
Pioneer SE50	£19 3 8	£16 6 0
Pioneer SE30	£12 12 0	£10 14 0
Pioneer SE20	£7 2 11	£2 2 0
Pioneer SE2P	£6 15 5	£5 15 0

	List Price	Cave's Cash Price
Rotel RH600	£5 10 0	£4 14 0
Rotel RH711	£9 0 0	£7 13 0
Sansui SS2	£7 14 6	£6 12 0
Sansui SS20	£16 10 0	£14 0 0
Secom 650	—	£3 12 0
A.K.G. & Eagle		Price upon application


	List Price	Cave's Cash Price
MICROPHONES		
Beyer M64	£10 7 0	£8 16 0
Beyer M64 SH	£14 7 0	£12 4 0
Beyer M67	£25 0 0	£21 5 0
Beyer M260	£29 6 0	£24 18 0
Beyer M260 SM	£29 6 0	£24 18 0
Beyer M81HL	£11 5 0	£9 11 0
Beyer M818HL	£22 18 6	£19 10 0
Beyer M55HL	£8 18 0	£7 11 0
Beyer Soundstar X1 'N'	£19 18 0	£16 18 0
Beyer Soundstar X1 'HLM'	£23 1 6	£19 12 0
Eagle DM 16HL	£6 12 4	£5 15 0
Eagle DM 58HL	£11 0 6	£9 13 0
Akal DM13	£7 10 0	£6 11 0
Akal ADM5	£4 15 0	£4 3 0
Akal ADM10	£5 10 0	£4 16 0
Akal ADM4	£3 17 6	£3 8 0
Gramplan, Shure, Reslowound, Grundig, A.K.G., Tandberg		Prices upon application

	List Price	Cave's Cash Price
TAPE RECORDERS		
Revox	£204 15 0	£180 10 0
Ferrograph 702/704	£207 7 0	£180 10 0
Ferrograph 722/724	£242 10 0	£202 19 0
Akal 4000D	£99 19 1	£74 9 0
Akal 1710/1	£29 0 0	£27 12 0
Akal 4000	£124 18 0	£103 19 0
Akal X5000L/W	£177 19 6	£156 13 0
Akal M-10L	£245 1 0	£215 13 0
Phillips 4302	£35 17 6	£30 16 0
Phillips 4307	£49 10 0	£42 10 0
Phillips 4308	£60 10 0	£51 19 0
Phillips 4404	£33 0 0	£27 5 0
Phillips EL3302	£28 7 0	£21 10 0
Grundig TK124	£44 18 0	£35 7 0
Grundig TK144	£49 19 0	£42 5 0
Grundig TK149	£57 12 8	£46 19 0
Grundig TK121	£54 15 7	£45 19 0
Grundig TK141	£59 8 0	£47 19 0
Grundig TK146	£68 2 10	£57 3 0
Truvox R44	—	£45 10 0
Teleton T710	£34 15 0	£30 10 0
Teleton 5L40	£37 10 0	£32 19 0
Teleton FXB 510D	£62 0 0	£52 15 0
Revox, Ferrograph, Tandberg, Uher, Teletunkon, Dual, Sansui, National, Pioneer—Prices upon application.		

	List Price	Cave's Cash Price
AMPLIFIERS		
Pioneer SA500	£61 19 7	£49 12 0
Pioneer SA700	£97 19 4	£78 7 0
Pioneer SA900	£133 16 7	£107 0 0
Pioneer SR202 Reverb.	£45 8 6	£36 7 0
Rogers Ravensbourne	£59 10 0	£47 10 0
Rogers Ravensbrook	£42 10 0	£36 19 0
Rotel 100AMP	£45 10 0	£37 10 0
Quad 303 & 33	£98 0 0	£87 19 0
Sansui AU222	£62 17 7	£53 10 0
Sansui AU555	£90 9 7	£68 8 0
Teleton SA Q203E	£27 5 0	£19 19 0
Teleton SA Q150/205	£26 5 0	£22 5 0
Teleton GA101	£33 1 5	£23 19 0
Armstrong 521	£56 0 0	£48 10 0
Dual CV80	£89 10 0	£76 0 0
Ferrograph F307	£59 0 0	£49 0 0
J. E. Sugden A21	£59 0 0	£49 0 0
Lux 1220	£124 10 0	£89 13 0
Lux 77T	£66 7 6	£52 10 0
Lux 505	£97 10 0	£69 12 0
Lux 606	£84 0 0	£59 19 0
Leak 30 Chassis	£53 0 0	£43 19 0
Leak 70 Chassis	£83 0 0	£53 11 0
Metrosound ST20	£36 0 0	£29 19 0
Sinclair 2.30	£4 9 6	£3 16 0
Sinclair 2.50	£5 9 6	£4 3 0
Sinclair Stereo 60 Pre-Amp	£9 19 6	£8 10 0
Sinclair S60 Filter Unit	£5 19 6	£5 2 0
Sinclair PZ-5	£7 19 6	£6 16 0
Sinclair PZ-6	£5 19 6	£5 2 0
Sinclair PZ-8	£5 19 6	£5 2 0
Sinclair IC10	£2 19 6	£2 15 0
Sinclair Z12	£4 9 6	£3 16 0
Sinclair PZ4	£4 19 6	£4 5 0
Sinclair Stereo 25	£2 19 6	£2 10 0
Sinclair 2000	£30 9 0	£22 19 0
Sinclair 2000 FM Tuner	£26 14 7	£23 10 0
Sinclair Decoder	£4 4 0	£3 19 0

it makes SOUND SENSE, buy from CAVES

A CAPACITANCE RESISTANCE BRIDGE

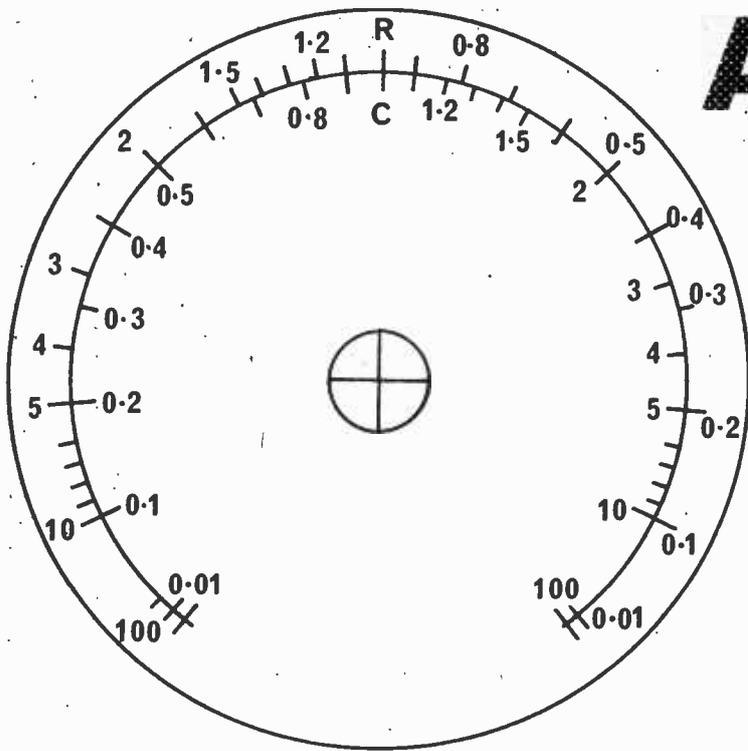

FOLLOWING THE TRANSISTOR AND DIODE TESTER OF LAST MONTH WE ARE PLEASED TO PRESENT THE SECOND PIECE OF TEST EQUIPMENT IN OUR NEW SERIES

THE Capacitance and Resistance Bridge, to be described, can be used to check capacitors in the range 10pF to about 100μF and resistors in the range 10 ohms to several megohms.


It consists of a transistor oscillator generating a sine wave voltage at 2kHz, the isolated output of this oscillator powering a Wheatstone bridge, where one side of the detector is earthed. The basic circuit is shown in Fig. 1.

The condition for balance of the bridge, that is when there is zero output to the detector, occurs

$$\text{when } \frac{Z_a}{Z_b} = \frac{VR1a}{VR1b}$$

The dial associated with VR1 is calibrated in terms of the ratio between the 'standard' and the unknown and is therefore direct reading in terms of capacitance and resistance.

Fig. 1: Basic circuit of CR bridge.

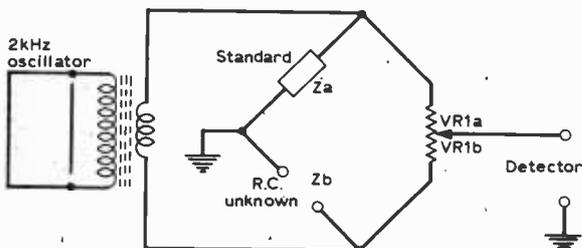

The accuracy of a simple CR bridge is dependent on the accuracy of the components used for the 'standards', and in keeping the stray capacitances and leakage to a minimum. The oscillator transformer, T1, has a secondary winding which has low stray capacity. This transformer is home made and for easy construction it uses a plastic slotted bobbin on a pair of Mullard 'Ferroxcube' 'E' cores.

The detector can conveniently be a small earphone of medium to high impedance. However, it is possible to improve the sensitivity by using a small audio amplifier feeding into a headphone or loudspeaker. A suitable Audio Monitor, for this purpose, will be described in a later article in this series.

Circuit Description

The complete circuit is shown in Fig. 2. The oscillator is a Hartley type employing a pnp transistor, OC72, operating in common emitter mode. Base biasing is provided by R1 and R2 and the operating current is determined by R3. This resistor also provides a measure of negative feedback to reduce the harmonic content of the oscillator output.

The oscillator transformer, T1, has a tapped primary winding, tuned to 2kHz by C2. The secondary winding has low stray capacity and relatively low output impedance which is suitable for powering the bridge circuit even when used on the low resistance and high capacitance ranges.

The bridge potentiometer, VR1, is a good quality wire-wound type which will give adequate resolution and accuracy. The dial, shown in the heading, full size, has been calibrated for this particular make and type of potentiometer and may not be correct if any other type of potentiometer is used.

The 'standards' built into the bridge determine

PRECISION AND ACCURACY BRIDGE

JOHN THORNTON LAWRENCE

the accuracy of the various ranges and these components specified have an accuracy of 1%, or better. Some relaxation of this ideal requirement may have to be accepted, on the grounds of cost and availability. A suggested compromise range of standards is given later.

Transformer Construction

Winding details:

Primary 800 turns of 42 s.w.g. enamelled copper wire tapped at 200 turns.

Secondary 15 turns of 42 s.w.g. enamelled copper wire.

The transformer consists of two Mullard FX1105 E-cores assembled face-to-face inside a plastic bobbin. The bobbin has four winding slots, the primary being wound in two slots at one end of the bobbin and the secondary winding wound in the slot at the opposite end, leaving an empty slot between the two windings.


The easiest way to wind the bobbin is by using a geared hand drill which has been clamped in a vice. Firstly, a small piece of wood, about two inches long is shaped so that it will just slide through the centre hole of the plastic bobbin, so forming a mandrel. A 2BA clearance hole is then drilled down the centre of the wood and a long 2BA screw or length of studding with two nuts is used to fit the wood block to the drill chuck.

The plastic bobbin is then slipped over the wood to the centre and wedged in place with a sliver of paper or card. By checking the gear ratio of the hand drill it will be possible to calculate how many revolu-

tions of the handle are required to produce the desired number of turns on the bobbin. The reel of winding wire should be fixed, at some convenient position above the drill, so that it will revolve freely, a pencil, large nail, or screwdriver blade can be used for this purpose.

Before commencing winding it is useful to have cutters or scissors and a few short (¼ in.) lengths of plastic tape ready cut and easily to hand. These can be used to anchor the winding ends as the job proceeds and will avoid the desire to have three hands for certain parts of the job!

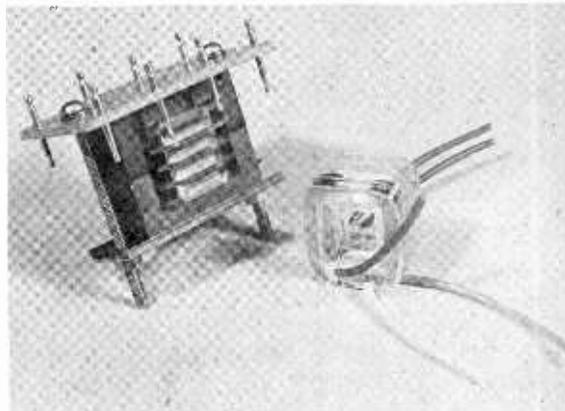The winding should be started by sticking the end of the wire to the wood mandrel with tape, leaving about three inches of spare end which is wrapped around the mandrel and again stuck with tape.



Completed transformer assembly with, right, a wound bobbin before insertion of the E-cores.


The wire is fed into the end slot through the gap in the end cheek and 200 turns are wound on. The wire should be guided into the slot with the fingers so as to keep a nice even winding. Winding at an even pace is best, as this avoids 'snatching' and the possibility of snapping the wire.

At the end of 200 turns, lead out a loop of wire about four inches long and fasten this to the mandrel with tape. Continue winding a further 200 turns in the end slot and then cross through the gap into the second slot and wind on 400 turns. Bring out the end of the winding for about four inches and stick down with tape as before.

The secondary winding of 15 turns can now be wound in the slot at the opposite end of the bobbin using the same method.

Having completed the winding it is advisable to fix the outside lead-out wires by putting a drop of 'Denfix' polystyrene solution on the top of the winding. When this has set, the winding may be taped over with 'Selltape' or similar tape. The lead-out wires may now be untaped from the mandrel

Fig. 2: Full circuit diagram of CR bridge.

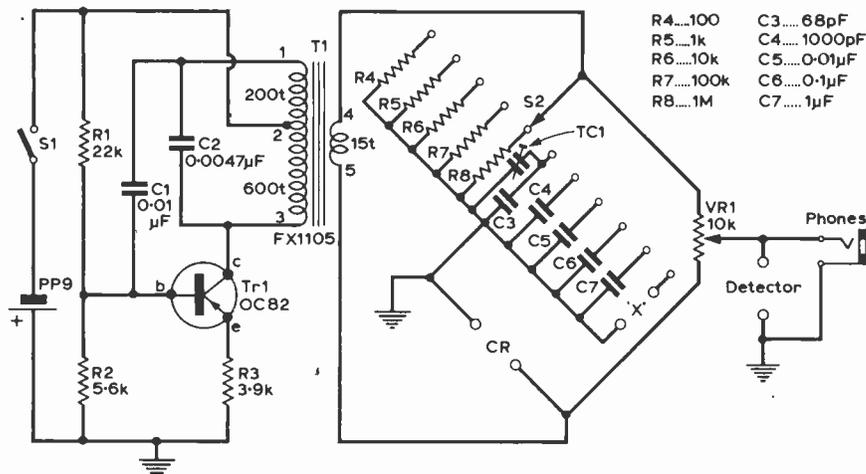

and sorted out, taking care not to damage them.

The wires then require cleaning and tinning with solder, an operation which requires reasonable care. It is advisable to practise with a spare piece of wire from the reel before attempting to clean the wires on the bobbin.

The tools required are a cigarette lighter or other source of a small flame, a small piece of very fine sandpaper, soldering iron, cored solder, cutters, etc.

The core and bobbin may now be clamped between the tag panel and the chassis, and the lead-out wires connected to the appropriate tags. Sleeving may be used on the lead-out wires if required.

If the connections to the tag panel, which are given in Fig. 3, are followed, then the oscillator circuit components may be mounted on top of the panel, as shown.

The phase of the secondary winding is unimportant and connection of the winding either way round will not affect the performance of the bridge.

Construction

The CR bridge is built in an Eddystone die-cast box, type 6357P. The controls and components are mounted on the lid of the box, which serves as the front panel of the instrument. The PP9 battery rests inside the box, which forms the main case of the instrument, and, as such, is fitted with plastic feet and a carrying handle.

The drillings for the front panel are given in Fig. 4. The size of hole D should be checked against the terminals used if these are different from those listed. The oscillator transformer is mounted on an aluminium bracket attached to the front panel, details are given in Fig. 5. The bracket is fixed to


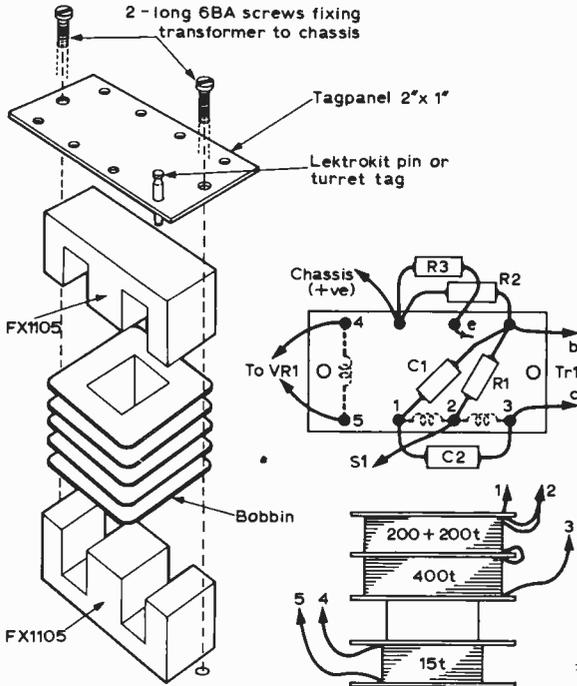


Fig. 3: Exploded view of transformer assembly with details of terminal board and bobbin windings.


The method is to hold the wire above the flame so that the enamel on the wire burns off but the wire remains undamaged, the correct amount of heat can be judged fairly easily after a little experimenting. The sooty copper wire is then cleaned by very gently drawing it through the sandpaper, which has been folded with the abrasive on the inside, remembering that 42 s.w.g. wire has a diameter of only four thousandths of an inch.

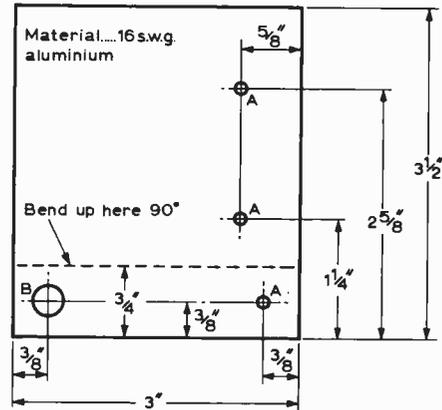The wire should be tinned by applying the cored solder and the iron at the same time so that the wire is in the centre of the active flux. A continuity test should be made of all the windings and if in order, the bobbin can be assembled in between the 'E' cores and a band of tape fixed around the edges of the cores to hold them together.



▲ Fig. 5: Details of transformer mounting bracket.

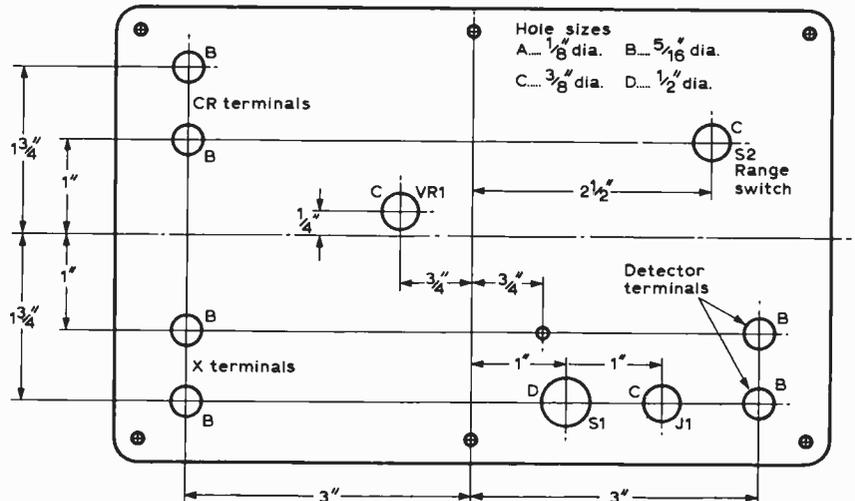▼ Fig. 4: Drilling plan of panel, viewed from the front. Note: The markings of the two pairs of terminals at the left side should be reversed.



★ components list

Resistors:

R1	22k Ω 5%	R5	1k Ω 2%
R2	5.6k Ω 5%	R6	10k Ω 2%
R3	3.9k Ω 5%	R7	100k Ω 2%
R4	100 Ω 2%	R8	1M Ω 2%

All resistors $\frac{1}{2}$ W

VR1 10k Ω 3W wirewound (Radiospares standard wirewound volume control)

Capacitors:

C1	0.01 μ F 250v 20% moulded tub. polyester
C2	0.0047 μ F 250v 20% moulded tub. polyester
C3	68pF 500V 1% silver mica
C4	0.001 μ F 1% (Home Radio Type 2FG25)
C5	0.01 μ F 1% (Home Radio Type 2FG29)
C6	0.1 μ F 1% (Home Radio Type 2FG33)
C7	1.0 μ F 1% (see text)
TC1	3-30pF concentric (beehive) trimmer

Transformer:

T1 'E' cores FX1105 (2 off) and bobbin (Henrys Radio)


Miscellaneous:

Transistor OC72 or similar. Die-cast box (Eddystone Type 6357P). Single pole toggle switch. Single pole 12 way wafer switch. Terminals, 6 off (Belling Lee, 4 mm type) Jack Socket, open type. Battery PP9 and connectors. Plastic feet and handle. Knobs (one modified by fitting pointer). Small quantity 42 s.w.g. enamelled wire. Material for bracket and tag panel.

the front panel by means of a 6BA screw and nut through the smaller hole and by the upper 'detector output' terminal, which passes through the larger hole and clamps the bracket to the front panel.

The oscillator components are mounted on a tag panel, on top of the oscillator transformer and the 'standard' components are mounted directly on the switch, S2, as shown in the photograph.

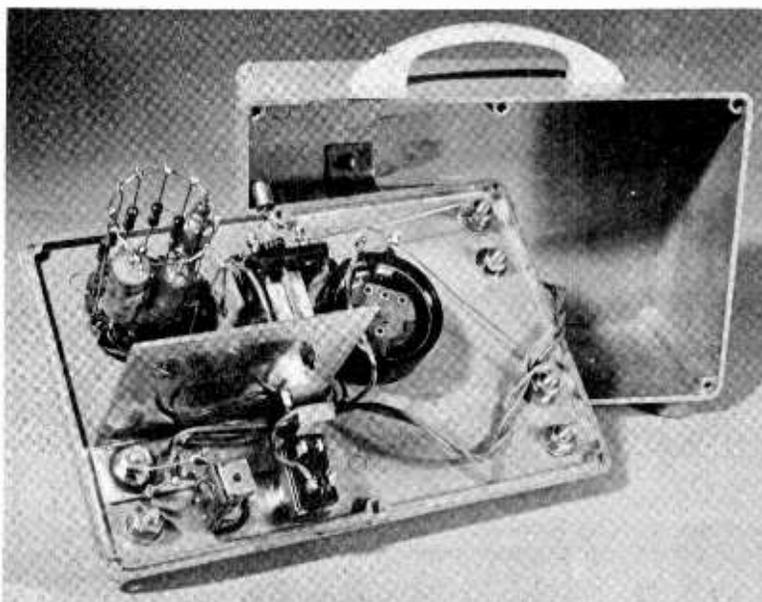The wiring from the range switch, S2, and VR1, to the CR terminals should be made in 18 or 20 s.w.g.



◀ View of the completed CR bridge mounted on the panel of the die-cast box. Note the method of mounting the various 'standard' components on the range switch, top left, to reduce stray capacitance.

tinned copper wire, dressed well clear of the panel, to keep stray capacitance to a minimum. The earthed outer cover of VR1 should be carefully removed, to reduce, still further, the stray capacitances from the bridge circuit to chassis.

The die-cast box may be sprayed with one of the usual car touch-up aerosol sprays, BMC Farina Grey was used on the prototype, and then lettered using Letraset, sheet 208.

The dial is fixed to the front panel using 'Cow Gum' adhesive, as this is very clean to work with. The whole front panel may then be protected by spraying with Letracote clear lacquer.

Calibration

The overall calibration depends on having the dial pointer set correctly with respect to the scale. To do this, the potentiometer should be slightly loosened from the front panel and the pointer knob fitted to the shaft and tightened up against the spindle flat.

The position of the potentiometer body is then set so that the pointer goes past each end of the scale by the same amount. The knob is then removed, the potentiometer is tightened and the knob re-fitted and checked again for the correct position.

The only range which requires individual calibration is the 100pF range and this is due to the unknown stray capacitances existing in S2 and the associated wiring. This range is calibrated by connecting a 100pF 1% silvered mica capacitor to the CR terminals, setting the dial to the 1:1 position, at the top of the scale, and adjusting TC1 for balance.


Accuracy

It is difficult to specify the overall accuracy as this varies with the scale reading, but the greatest accuracy will occur around the centre of the scale and will be about 1-2% worse than the accuracy of the standard. Measurement above about 5M Ω and below about 10pF are subject to greater errors due to the unavoidable stray capacitances.

It is somewhat difficult to find a source of 1 μ F close tolerance capacitors (for C7) and it may be necessary to accept a 20% type. Alternatively a number of 1 μ F capacitors could be checked on the 0.1 μ F range of the bridge and the most accurate one used. Occasionally surplus polystyrene capacitors become available and these are usually 5% or 2 $\frac{1}{2}$ % tolerance and therefore quite suitable.

—continued on page 574

S.W. transistor R.F. preamp

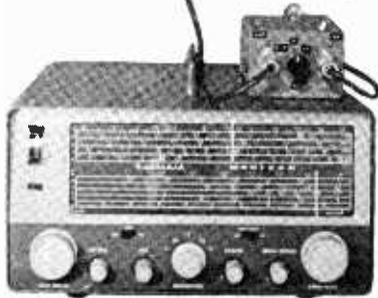

**P. CAIRNS
G3ISP**

THIS article describes a unit which can be used in conjunction with almost all types of short wave receiver. It should prove of particular value used with some of the older models or "surplus" receivers whose sensitivity is not always what one could wish. Basically the unit is a two stage r.f. transistor amplifier with switched broadband pretuned circuits to give a good measure of r.f. signal gain over the bandwidths quoted. In the unit described the three main amateur bands are selected, though the coils can be wound to allow for the selection of the broadcast bands instead, details of alternative channel selection will be given later. The amplifier has the advantage of small size and compact construction with standard 9V to 12V battery or power unit supply and low current drain. It is simple to operate, having only one switched control with input and output sockets, no tuning being required. The amplifier is simply connected between the incoming aerial lead and the receiver aerial socket, no internal connections or adjustments to the receiver are needed.

THE CIRCUIT

The circuit is shown in Fig. 1. The aerial is coupled via C1 directly into the emitter of Tr1, this being connected as a grounded base r.f. amplifier. The advantage of such a circuit is that it provides a very low input impedance with a high output impedance while giving a good measure of gain with optimum bandwidth. The very low input impedance allows direct matching with most types of receiving aerial while

the high output impedance allows a tuned circuit of reasonable Q to be used. R1 provides the d.c. return path for the emitter while the base is maintained at a constant voltage level by zener diode ZD1 the current bleed for this being via R3 and base decoupling by C5. The collector load is composed of a number of tuned circuits, these being selected by S1. Collector d.c. feed and decoupling is via R2 and C4. The Q of the tuned circuits allows a reasonable gain to be achieved over the required bandwidth. A higher gain, but narrower bandwidth, is obtained on the l.f. channels, the gain for each band decreasing by a factor of one third, while the bandwidth increases by a factor of three for increasing frequency. The output from the first stage is a.c. coupled to the second stage via C2.

The second stage, Tr2, is a normal emitter follower, R6 being the emitter load while d.c. base bias is obtained through R5. The series resistor R4 prevents parasitic oscillation and, while slightly reducing the input drive to Tr2, makes for a much more stable circuit. The purpose of the output stage is to provide a low impedance output suitable for matching into the receiver, this normally being low impedance. Thus, correct matching is achieved at both ends of the unit. The emitter follower input, having quite a high input impedance, imposes the minimum of damping across the tuned circuit. Tr2, therefore, besides providing the necessary impedance matching, also provides isolation between the r.f. amplifier circuit and the final signal output. C3 provides d.c. blocking to the output socket and load resistor R7. Decoupling of the supply is through C6.

The transistors chosen are both of the same type, being p-n-p germanium alloy diffused types, these having a good gain/frequency characteristic. They also allow for earthing of the outer shield, this proving an advantage at higher frequencies. The power supply can be either a 9V battery or 9-12V power unit. As the current drain at 9V is similar to the average transistor radio, about 10mA, any of the standard range of batteries are suitable.

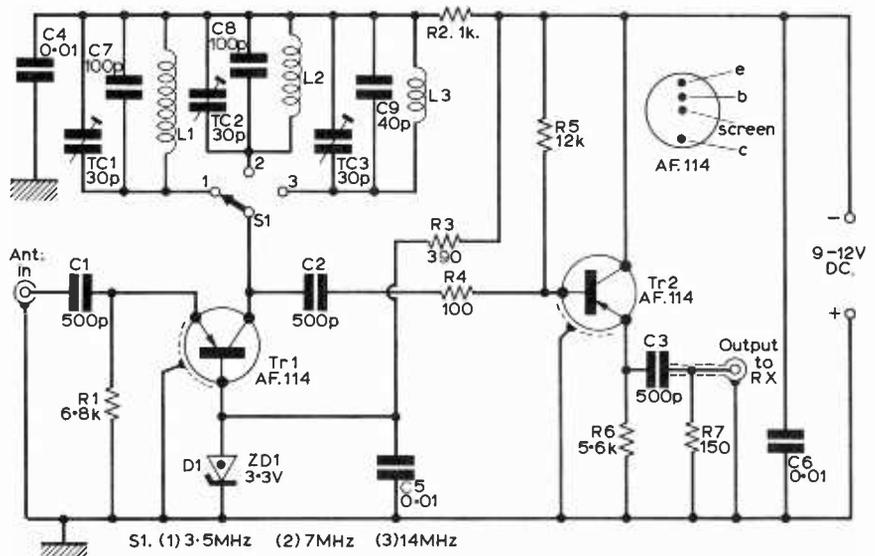


Fig. 1: The circuit of the switched r.f. preamplifier.

ALTERNATIVE COILS

The coils specified and used in the unit are for the 3.5, 7 and 14MHz amateur bands, the 14MHz tuned circuit giving a useable gain as high as the 21MHz amateur band. If the broadcast bands are required instead, however, the following data should prove useful, the coils specified being replaced by any other coils selected from the list; 49 metres—17 turns; 31 metres—11 turns; 25 metres—9 turns; 19 metres—6 turns. All $3\frac{1}{4}$ in. diameter and 18 s.w.g., close wound.

CONSTRUCTION

The construction is not particularly critical as it can be adapted to suit individual requirements. While the type of construction used by the writer is described, being about the minimum practical volume into which the circuit can be put, other forms of construction may be used. For those with no facilities for chassis work, a ready made case can be bought in one of the popular "Minibox" or "Diecast Box" ranges which are advertised in various sizes. If required, a larger case than specified may be used so as to contain the battery internally and also provide a little more "elbow room" for construction. Where, as with the writer, minimum size was of importance, the construction illustrated should prove of value. No matter what form of case or construction is used, the two basic sections described, Veroboard layout for components and coil pack assembly, should be adhered to. Also, wiring between coil pack, SI, and Veroboard, should be as short and direct as possible.

All components except the tuned circuit items and R7 are mounted on a piece of Veroboard $2\frac{1}{2}$ in. x $1\frac{1}{2}$ in. The layout of these components is shown in Fig. 2. This board should be completed first, including fly-leads for external connections, before mounting in the case. Next the coil pack is constructed as shown in Fig. 3. The base is made from paxolin sheet or similar material, six solder tags being fitted as shown.

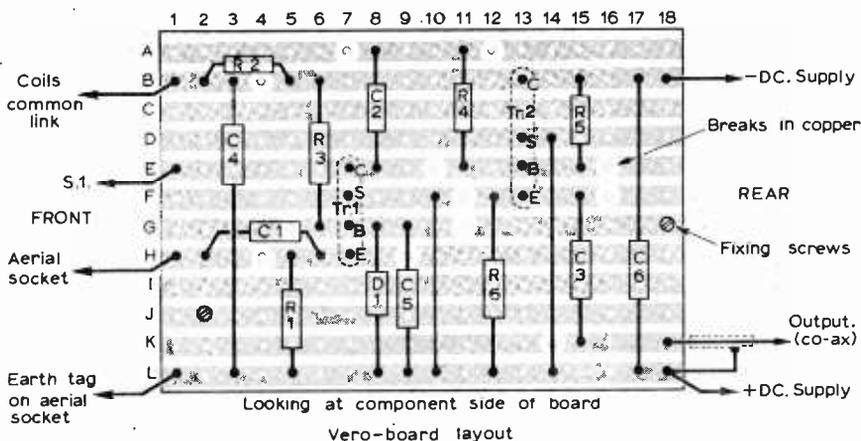


Fig. 2: The component layout on Veroboard.

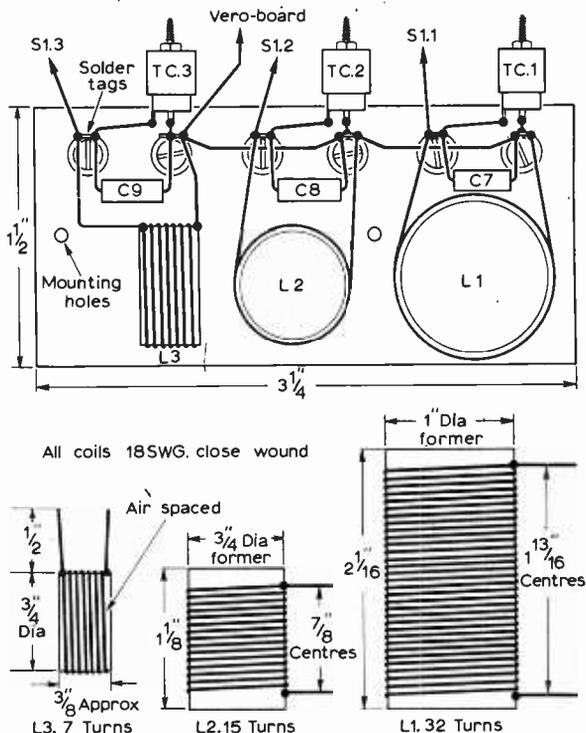



Fig. 3: The coil pack and coil winding details.

With the mechanical construction complete, mount switch and sockets on the front panel, an earth tag being placed under a fixing screw on each socket. The coil pack and Veroboard are now mounted on each side. The boards are stood off the sides by about $\frac{1}{2}$ in. by means of limiting nuts on the fixing screws. R7 is connected between the output socket and earth tag. The fly-leads previously soldered to the boards are now connected between the different points, being kept as short and direct as possible. The output from the Veroboard to the output socket is by means of a short length of co-axial cable. The d.c. supply leads are brought out from the rear

of the Veroboard, a hole with grommet being made in the rear of the case for this purpose. By splitting the unit into two circuit sections, both of which are completed before being mounted in the frame or case, only the minimum amount of wiring is required afterwards.

With the unit completed, alignment should take very little time. First set SI to select the 3.5MHz band, set the three trimmers to about mid-position and connect the d.c. supply. The simplest method of alignment is by means of a signal generator and oscilloscope or valve voltmeter. The gener-

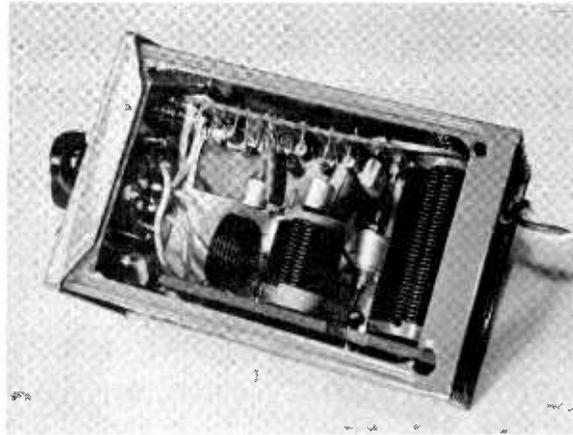ator is set to 3.5MHz (or about 3.7MHz if the phone band is of major importance) and a small level of signal applied to the aerial input socket. The valve-voltmeter or scope is connected across the output socket. The 3.5MHz trimmer is then adjusted for maximum output. As some hand capacity effect is



An inside view of the complete preamplifier.

almost inevitable, particularly at the higher frequencies, the trimmers should be adjusted in small steps, the trimmer being removed at each step to prevent false settings. With the first channel set up a similar procedure is carried out on the other channels, the signal generator being set to the appropriate frequency and the trimmer adjusted for

★ components list

Resistors:

R1	6.8kΩ	R5	12kΩ
R2	1kΩ	R6	5.6kΩ
R3	390Ω	R7	150Ω
R4	100Ω		

Capacitors:

C1	500pF	silver mica
C2	500pF	silver mica
C3	500pF	silver mica
C4	0.01μF	polyester
C5	0.01μF	polyester
C6	0.01μF	polyester
C7	100pF	silver mica
C8	100pF	silver mica or ceramic
C9	40pF	silver mica or ceramic

TC1, TC2, TC3 3-30pF concentric trimmers.

Semiconductors:

Tr1	AF114	ZD1	BZY88 C3V3 (3.3V) zener diode
Tr2	AF114		

Coils:

- L1 32 turns, 18 s.w.g. on 1in. diameter former, close wound.
- L2 15 turns, 18 s.w.g. on ½in. diameter former, close wound.
- L3 7 turns, 18 s.w.g. on ¾in. diameter former, air spaced.


Miscellaneous:

S1, 1-pole, 3-way rotary switch; Veroboard, 0.15in. matrix, 12 x 18 holes; pointer knob; 2 off co-ax sockets; chassis to specification.

maximum output.

If no instruments are available the unit can be aligned using the receiver itself. First tune in a quiet spot in the 3.5-3.6MHz range and reduce the r.f. gain until the background noise is just audible. Now connect up the unit, the 3.5MHz channel being selected. The background noise should be appreciatively louder. Now adjust the trimmer for maximum output. Again adjust it in steps to eliminate the effects of hand capacity. The effect of the unit can best be appreciated by reducing the r.f. gain to a very low level, first having taken the unit out of circuit. Tune across a selected portion of the band noting a number of stations and relative signal strengths. Then, without altering the r.f. gain, connect the unit in circuit, tune across the same portion of the band and note the difference in signal strength for the same stations.

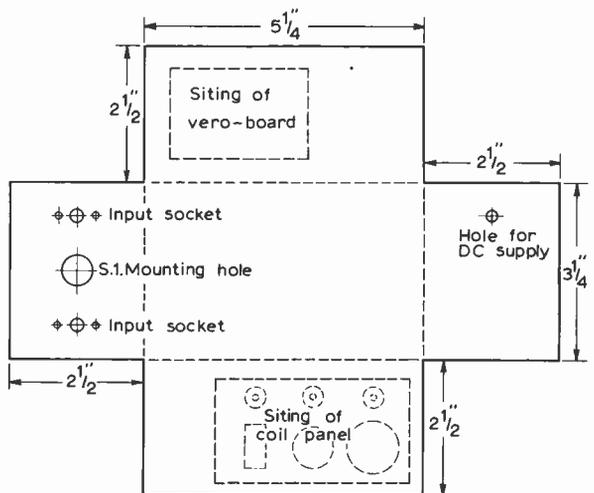The other channels are aligned in a similar manner. The audible differences in signal or noise level may not be quite so obvious on the 14MHz channel and exact trimming may be more difficult to achieve



A simple chassis to hold the Veroboard, the coil pack and the switch.

without the use of instruments. This is because of the greatly extended bandwidth and much flatter response at these frequencies. As the gain is constant over a much greater bandwidth, however, very accurate trimming is not vital, thus the problem tends to be self cancelling. When alignment is complete and the unit has been satisfactorily tried out on all bands, a spot of shellac on each of the trimmers will lock them in place.

In practice the amplifier should prove of value with most receivers. Its compact size and low power requirements make it extremely useful for field days, portable and mobile rigs, etc. Being small and robust it will withstand a great deal of rough usage without ill effect. A final point which may be mentioned is that like all such devices it amplifies all signals within the quoted bandwidth which appear at the aerial. Thus, both noise and signal are amplified equally and an acceptable signal-to-noise ratio is still required from the aerial to obtain acceptable results. Unfortunately, no one yet seems to have come up with a device which discriminates against unwanted noise in favour of wanted signal. ■



25-50

GUITAR AMPLIFIER

Part 3

THIS concluding article will deal with the electrical performance of the PW25-50 Amplifier, with testing for correct performance and with the optional extras: the tremulant on-off foot control and a foot controlled wah-wah effect.

The Henelec power amplifier module and its MU422 power supply require no adjustment and it is only necessary to ensure that they are correctly and securely positioned as shown in the layout diagrams in Part 2. Do not run the power amplifier unless the loudspeakers are connected and take great care not to short circuit the output whilst the amplifier is running at full power. The power unit and the module are both fuse protected.

Power Module

The specified performance of the Henelec PA50 amplifier module is as follows:

Power Output with 4Ω load (2-8Ω speakers).	50 watts r.m.s.
Power Output with 8Ω load (1-8Ω speaker).	25 watts r.m.s.
Power Bandwidth. 12Hz to 60kHz.	+3dB
Signal Input, for rated output.	max 600mV
Distortion, at full power.	not more than 1%
Hum and Noise.	-75dB

In order to drive fully the power module and to allow some reserve gain for low level input signals the pre-amplifier has been designed for a maximum output of 1.5V r.m.s. from an input of 40mV at the guitar inputs or 2mV at the microphone input. The guitar input sensitivities are more than sufficient for all standard guitar pick-ups of medium to high impedance.

Testing for performance

If test equipment, such as an audio frequency generator, a valve-voltmeter and an oscilloscope, is available the following tests can be carried out to ensure performance to specification. Constructors with only a multi-range meter can check the voltages and currents at various points which will be indicated. On initially testing the amplifier do not turn the master control to maximum. Ensure that the pre-amplifiers are operating properly before running the amplifier at full power.

The following table may assist in checking the function of the pre-amplifiers and tremulant circuit:

Total current drawn from pre-amplifier supply	28 to 30mA
Voltage at top of C28	20 to 22V
Current drawn by circuit Board 1	2.8 to 3mA
Current drawn by circuit Board 2	6 to 7mA
Voltage at junction R46 & R45 (circuit Board 2)	16 to 17V
Voltage at junction R29-C17 (circuit Board 2)	13 to 14V
Voltage at junction R8-C6 (circuit Board 1)	18V
Voltage at collector of Tr4 (AD161)	average 14V
Collector current Tr4 (AD161)	Average 18/20mA

If a sinewave audio signal generator and v.v.m. are available, the following signal level checks can be made. The master volume control VR8 should be set almost off, i.e., with just enough gain to make the signals audible.

1. Guitar input (guitar gain control max) 40mV in—signal at top of VR8 junction with C26 should be approx 1.5V r.m.s.
2. Microphone input (microphone gain max) 2mV—signal at top of VR8 junction with C26 should be approx 1.5V r.m.s.
3. Guitar input (gain max) 40mV in—signal at junction C16-R30 approx 800mV.
4. Guitar input (gain max) 40mV in—signal at mixing pre-amplifier input C22 approx 20mV.
5. Guitar input (gain max) 40mV in—signal at tremulant amplifier (Tr6) output junction C21-VR7 approx 1V r.m.s.

If an oscilloscope is available the sine wave output at the various points previously indicated can be checked as well. The output of the tremulant phase shift oscillator Tr3 and its amplifier Tr4 can be checked with an oscilloscope. The low frequency sine wave at Tr3 collector should be approximately 10V peak-to-peak and at Tr4 collector approximately 8V peak-to-peak.

It is most important that Tr4 runs at the specified collector current which in turn determines the correct brilliance of the l.d.r. and the panel tremulant

Fig. 17: (Right) Frequency response for guitar and microphone inputs.

Fig. 18: (Below) Responses obtainable with treble lift and tremulant tone control.

indicator lamp. With the tremulant turned off (S1 closed) both lamps should glow at about a quarter of their normal brilliance and the collector current of Tr4 should be a steady 18 to 20mA with the tremulant depth control at minimum (anti clockwise).

If the collector current is more than this the lamp will be brighter and the gain of the guitar pre-amplifier will be reduced. If the current is lower the l.d.r. will not produce the correct tremulant depth. Adjustment to the collector current of Tr4 can be made by changing the value of R18 (nominally 270 ohms) a little one way or the other.

When the tremulant circuit is switched on the lamps will flicker between extinction and the steady level of brilliance hitherto obtained. When the tremulant depth control is increased (clockwise) the lamps will glow slightly brighter and the collector current of Tr4 will rise by a milliamp or so.



Operational Notes

The treble control in the guitar pre-amplifier provides approximately 15dB lift at 10,000Hz and excessive treble lift could cause distortion if signals between about 6 and 10kHz are equal in amplitude to those in the mid frequency range. The treble control should therefore be used sparingly for signal sources such as a portable electronic organ. The 'tone tremulant' control can also cause severe distortion if used to excess particularly on signal sources other than an electric guitar.

For average use with a treble guitar and to obtain a distortion free tremulant, particularly on chord playing, the tremulant tone control and the treble control should both be set at about their midway position and the tremulant depth at minimum.

With guitar pick-ups of average sensitivity the master volume control should be set at about three quarters of its travel and the guitar input volume control adjusted accordingly. The same applies to the microphone input and as the microphone pre-amplifier is completely independent of the guitar circuitry it is not affected by the tremulant circuit.

The frequency response of the amplifier is more than adequate for guitar bass and whilst a single speaker and 25 watts output will provide good quality bass, the full 50 watts with two speakers will be much more suitable for group playing. The speakers are well within rating as a pair will in fact

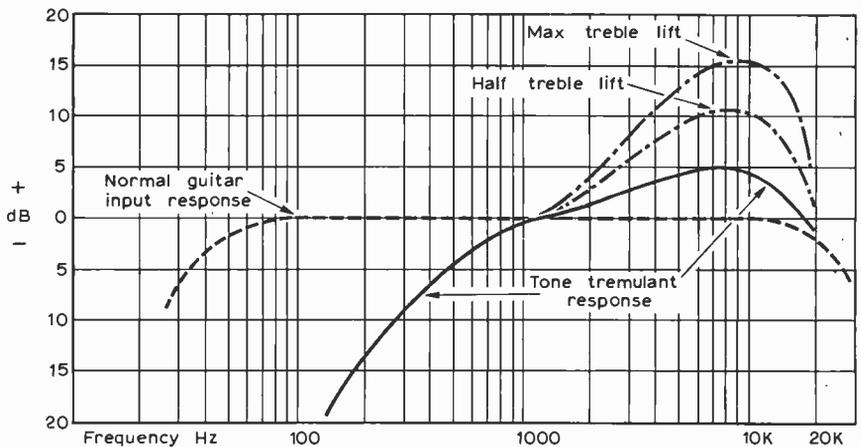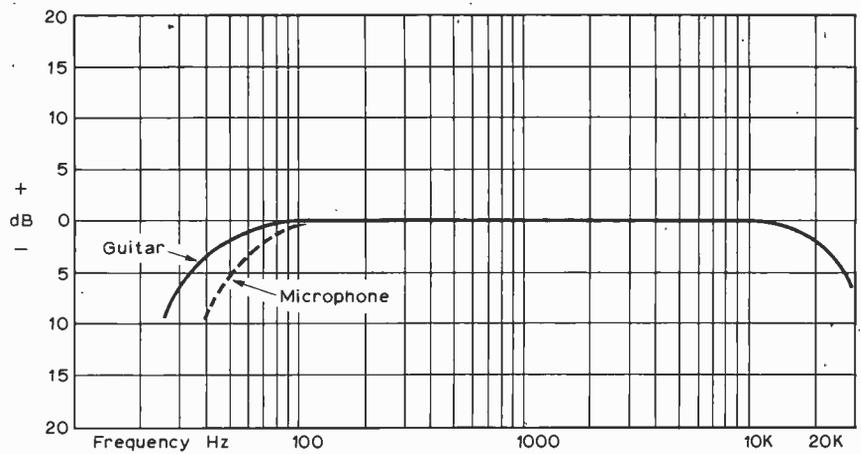

PW25-50 AMPLIFIER Overall performance specification

Max power output 4Ω load	50 watts (r.m.s.)
Max power output 8Ω load	25 watts (r.m.s.)
Input sensitivity (guitar)	Min 30 to 40mV (for rated output)
Input impedance (guitar)	100kΩ
Input sensitivity, (microphone)	2mV (without transformer)
Input impedance, (microphone)	100kΩ
Treble lift control	+15dB at 10kHz.
Frequency response (guitar)	-3dB at 35Hz to -3dB at 20,000Hz.
Frequency response (microphone)	-3dB at 45Hz to -3dB at 20,000Hz
Hum and noise level (guitar)	Better than 60dB below rated output
Hum and noise level (Microphone)	Better than 56dB below rated output
Distortion	Not greater than 1% at rated output
Tremulant speed	Approx. 5 to 10Hz
Tremulant depth	Variable between approx. 30 and 50% as a modulation function

COMET

HI-FI DISCOUNT WAREHOUSES

- All Items offered are brand new, latest models in manufacturers' sealed cartons. Fully guaranteed with after-sales service.
- Over 1000 Items in stock. Complete Free price list on request.



Customers Welcome

Open Daily to the public from 9 a.m. Closed Tuesday 1 p.m.
Mon. & Sat. 5-30 p.m. Open until 8 p.m. Wednesday, Thursday & Friday.

	Rec. Price	Retail Price	Comet Price
STEREO AMPLIFIERS			
ARMSTRONG 521	£56	0	£46 0 0
DULCI 207	£25	0	£17 0 0
DULCI 207M	£30	0	£20 19 6
GOODMANS Maxamp	£54	0	£39 19 6
HL.505	£23	2	£18 19 6
LEAK Stereo 30 Plus	£53	0	£42 19 6
LEAK Stereo 30 Plus in teak case	£59	10	£47 19 6
LEAK Stereo 70	£65	0	£52 0 0
LEAK Stereo 70 in teak case	£71	10	£56 19 6
LINEAR LT.66	£21	0	£16 19 6
LL. Stereo Amp	£23	10	£18 19 6
METRO SOUND ST 20	£36	0	£28 19 6
PHILIPS RH 521	£73	0	£58 19 6
PHILIPS RH 590	£49	0	£37 12 6
PHILIPS RH 580	£26	0	£19 19 6
PIONEER SA500	£62	1 11	£45 0 0
PIONEER SA700	£98	0	£74 19 6
PIONEER SA900	£134	2	£99 19 6
PIONEER Reverberation	£45	9 11	£35 19 6
QUAD 33 Pre-amplifier	£43	0	£38 19 6
QUAD 303 Main Amplifier	£55	0	£48 19 6
ROGERS Ravensbourne (case)	£59	10	£46 19 6
ROGERS Ravensbourne (case)	£64	0	£49 19 6
ROGERS Ravensbrook	£44	0	£38 19 6
ROGERS Ravensbrook (case)	£49	0	£39 19 6
SINCLAIR 2000	£30	9	£23 10 0
VOLTEX 100 watt stereo diacotheque 8 electronic-ally mixed inputs	£185	0	£139 0 0

	Rec. Price	Retail Price	Comet Price
TUNERS			
*ARMSTRONG 523 AM/FM	£53	15	£44 19 6
*ARMSTRONG 524 FM	£41	17 8	£34 19 6
ARMSTRONG M8 decoder	£9	10	£7 19 6
*DULCI FMT.7FM	£22	1	£17 19 6
DULCI FMT.75 Stereo	£31	0	£25 19 6
GOODMANS Stereomax	£82	10	£63 19 6
LEAK Stereofetic Chassis	£59	19	£52 19 6
LEAK Stereofetic in teak case	£67	3	£58 19 6
PHILIPS RH 690	£39	0	£31 19 6
PHILIPS RH691	£83	0	£70 10 0
PIONEER TX500 AM/FM	£77	18	£63 19 6
PIONEER TX900 AM/FM	£153	13	£125 0 0
QUAD Stereo FM	£51	0	£39 19 6
ROGERS Ravensbrook	£61	17	£49 19 6
ROGERS Ravensbrook (case)	£45	2	£39 19 6
*SINCLAIR 2000	£28	14	£19 4 6
TELETON 201X FM	£36	0	£29 19 6
TRUVOX FM 200/1C	£60	11	£39 19 6

All above tuners are complete with MPX stereo decoder except where starred.

	Rec. Price	Retail Price	Comet Price
TUNER/AMPLIFIERS			
ARENA 2400	£90	6	£71 19 6
ARENA 2600 Stereo AM/FM	£111	6	£94 0 0
ARENA 2700 Stereo	£105	0	£85 0 0
ARENA T1500F	£72	9	£59 19 6
ARENA T9000	£303	9	£258 0 0
*ARMSTRONG 525	£81	17	£67 19 6
*ARMSTRONG 526	£126	14	£102 19 6
ARMSTRONG M8 decoder	£9	10	£7 19 6
GOODMANS 3000	£77	14	£65 19 6
PHILIPS RH781	£74	19	£64 19 6
PHILIPS RH790	£125	0	£101 19 6
PIONEER KX330 AM/FM/SW	£78	12	£62 19 6
PIONEER SX770 AM/FM	£160	8	£129 19 6
PIONEER SX990 AM/FM	£194	14	£155 0 0
TELETON F.2000	£51	0	£34 19 6
TELETON 7AT1	£103	19	£85 0 0
TELETON R4200	£51	15	£39 19 6
TELETON CR/10T	£39	15	£29 19 6
TELETON TFS50	£75	10	£49 19 6
TELETON NX990 with speakers	£67	5	£48 19 6
TELETON R8000 with speakers	£63	5	£49 19 6
WHARFEDALE 1001	£131	5	£105 0 0

All above Tuner Amplifiers are complete with MPX stereo decoder except where starred.

CARTRIDGES ALL MAKES STOCKED AT DISCOUNT PRICES

	Rec. Price	Retail Price	Comet Price
PICKUP ARMS			
GOLDRING Lenco L75	£12	6	£10 10 0
GOLDRING Lenco L69	£9	5	£7 0 0

DELIVERY BY SECURICOR
WITHIN 72 HOURS
ALL IN-STOCK Items delivered by SECURICOR within 72 hrs. (Add 20/- only for Securicor delivery). All goods fully insured against loss or damage whilst in transit.

	Rec. Price	Retail Price	Comet Price
SME 3009 with S2 shell	£31	6 3	£25 19 6
SME 3012 with S2 shell	£33	7 3	£28 19 6

	Rec. Price	Retail Price	Comet Price
TURNTABLES			
ARENA SP25 with base, cover £22	1 0	£17 19 6	
B.S.R. McDONALD MP80	£15	0	£10 19 6
B.S.R. McDONALD 610	£18	9	£13 19 6
GARRARD SP25, fully wired with Goldring G600 magnetic cartridge, complete with base, plinth and cover	Special price	£20 19 6	
GARRARD SP.25 Mk II	£15	11 4	£10 10 0
GARRARD AP.75	£23	16 0	£17 10 0
GARRARD SL.55	£13	7 9	£11 12 6
GARRARD SL.65B	£19	6 5	£14 19 6
GARRARD SL.75B	£35	12 4	£28 19 6
GARRARD SL.95B	£45	9 1	£36 19 6
GARRARD 401	£31	14 2	£26 10 0
GARRARD SL.72B	£30	2 0	£24 19 6
GARRARD 3500 with GKS Cartridge	£15	15 0	£11 19 6
GARRARD base and cover to fit SP25, SL55, SL65B and 3500	Special price	£3 19 6	
GOLDRING GL69 Mk. II	£26	12 6	£21 10 0
GOLDRING GL69P Mk. II	£35	2 10	£27 19 6
GOLDRING GL.75	£36	8 2	£29 19 6
GOLDRING GL75P	£46	16 8	£39 19 6
GOLDRING Cartridges for 69P and 75P	£4	4 3	£3 8 0
GOODMANS 3025 complete with G800 cartridge	£37	14 9	£25 19 6
PHILIPS 228	£19	19 6	£16 19 6
PHILIPS GA146	£29	19 6	£24 19 6
PHILIPS 217	£6	0	£27 4 0
PHILIPS 202 Electronic	£64	0	£54 0 0
THORENS TD.125	£75	17 8	£61 19 6
THORENS 125AB	£120	3 11	£99 19 6
THORENS 150A Mk II	£43	12 7	£32 19 6
THORENS 150AB Mk II	£47	8 7	£40 19 6
THORENS TX11 Cover	£4	2 3	£3 13 6
THORENS TD.124/11	£46	15 10	£39 19 6

	Rec. Price	Retail Price	Comet Price
SPEAKERS			
ARENA HT 27	£18	18 0	£13 19 6
ARENA HT 28	£17	17 0	£12 19 6
ARENA HT 21	£10	10 0	£5 5 0
ARENA HT 7	£19	19 0	£17 0 0
ARENA HT 10	£22	1 0	£18 19 6
ARENA HT 20	£32	11 0	£26 19 6
ARENA HT 26	£78	15 0	£65 19 6
B & W DM3	£63	0	£53 6 0
B & W P2H	£94	10 0	£79 0 0
B & W DM1	£32	0	£25 19 6
CELESTION Dilton 10	£21	3 2	£16 19 6
CELESTION Dilton 15	£29	0	£22 19 6
CELESTION Dilton 25	£59	17 0	£46 19 6
DULCI AS 3	£8	8 0	£6 19 6
GOODMANS Majesta	£57	0	£44 19 6
GOODMANS Maxim	£20	7	£16 15 0
GOODMANS Mezzo II	£30	18 0	£22 19 6
GOODMANS Magnum-K	£40	2 0	£28 19 6
GOODMANS Marlamba	£24	0 1	£18 19 6
GOODMANS Mambo	£22	5 6	£17 19 6
GOODMANS 3005 (pair)	£25	0 0	£18 19 6
KEF Celesta	£29	0 0	£21 19 6
KEF Concord	£43	10 0	£32 19 6
KEF Concerto	£53	10 0	£41 19 6
KEF Cresta	£22	3 4	£17 19 6
LEAK Sandwich	£45	10 0	£29 19 6
LEAK Mini-Sandwich	£29	15 0	£21 19 6
LEAK 300	£27	10 0	£20 19 6
LEAK 200	£23	10 0	£17 19 6
LEAK 600	£45	0 0	£32 19 6
LOWTHER Acousta (with PM6)	£45	10 0	£38 7 6
LOWTHER Ideal Baffle	£35	10 0	£29 17 6
LOWTHER Acousta (with PM7)	£53	0 0	£45 19 6
QUAD Electrostatic	£66	0 0	£52 19 6
PHILIPS RH 481	£11	0 0	£9 2 6
PHILIPS RH 482	£18	0 0	£14 19 6

	Rec. Price	Retail Price	Comet Price
WHARFEDALE Speakers			
Alredale	£69	10 0	£55 19 6
Denton	£19	0 0	£14 19 6
Super Linton	£22	10 0	£18 10 0
Melton	£29	10 0	£22 19 6
Dovedale 3	£39	10 0	£24 19 6
Rosedale	£59	10 0	£46 19 6
UNIT 3 Speaker Kit	£11	19 6	£9 10 0
UNIT 4 Speaker Kit	£16	0 0	£13 5 0
UNIT 5 Speaker Kit	£23	10 0	£18 19 6

	Rec. Price	Retail Price	Comet Price
CHASSIS SPEAKERS			
GOODMANS Axlette 8	£7	9 6	£5 19 6
GOODMANS Twlnaxlette 8	£8	8 8	£6 19 6
GOODMANS Twlnaxiom 10	£9	8 5	£7 15 0
GOODMANS Axiom 10	£8	16 8	£6 19 6
GOODMANS Axiom 201	£13	9 0	£9 19 6
GOODMANS Axiom 301	£19	17 8	£14 19 6
GOODMANS Axidom 51	£12	3 0	£9 19 6
GOODMANS Audiom 61	£17	12 0	£12 19 6
GOODMANS Audiom 81	£29	13 0	£22 10 0
GOODMANS Audiom 91	£33	12 0	£25 19 6
GOODMANS Axiom 80	£26	1 4	£21 12 6
GOODMANS Audiom 91/100	£34	17 0	£26 2 9
GOODMANS ARU 180	£37	17 8	£28 19 6
GOODMANS ARU 280	£37	17 8	£28 19 6
GOODMANS ARU 480	£5	8 5	£4 1 3
GOODMANS ARU 172	£37	17 8	£28 19 6
GOODMANS Trebas 100	£7	9 0	£5 11 6
GOODMANS Trebas 5K/20KL	£8	8 0	£6 6 0
GOODMANS Midax	£11	4 0	£9 8 0
GOODMANS Attenuator	£3	1 4	£2 6 0
GOODMANS Crossover			
Networks XO/950/5000	£8	7 7	£6 6 0
GOODMANS Crossover			
Networks XO/950	£6	7 9	£4 15 9
GOODMANS Crossover			
Networks XO/5000	£2	6 0	£1 14 6
WHARFEDALE 8 inch Bronze/RS/DD	£4	8 0	£3 13 6
WHARFEDALE Super 8/RS/DD	£7	12 0	£6 6 0
WHARFEDALE Super 10/RS/DD	£12	14 0	£10 10 0
WHARFEDALE WMT 1 Matching Transformer	16	9	13 6

	Rec. Price	Retail Price	Comet Price
HI-FI STEREO TAPE DECKS AND TAPE RECORDERS			
AKAI X-360	£339	0 0	£284 0 0
AKAI X-360D deck	£290	0 0	£243 0 0
AKAI 1710L	£89	17 0	£69 19 6
AKAI 1800	£158	0 0	£133 0 0
AKAI 1800SD	£199	0 0	£167 0 0
AKAI 4000	£124	18 0	£99 19 6
AKAI 4000 D deck	£69	19 1	£69 19 6
ALBA R22 Battery/Mains	£50	5 0	£29 19 6
BUSH TP 60 Cassette Tape Recorder	£29	8 0	£24 19 6
BUSH TP 70 Cassette, 4-track	£29	19 0	£23 19 6
FERGUSON 3246	£43	0 0	£33 19 6
FERGUSON 3247 4-track	£48	9 0	£38 19 6
FERGUSON 3248 4-track	£54	6 0	£41 19 6
FERGUSON 3249 4-track	£64	6 0	£49 19 6
FERGUSON 3244 Stereo	£97	18 0	£79 19 6
GRUNDIG C200 Cassette	£37	19 10	£29 19 6
GRUNDIG TK 120 Continental	£39	5 0	£29 19 6
GRUNDIG TK 124	£44	18 0	£34 19 6
GRUNDIG TK 144	£49	19 6	£39 19 6
GRUNDIG TK 149	£57	12 8	£47 19 6
MARCONI TK 4218 Stereo tape Recorder	£89	11 2	£69 19 6
PHILIPS 290 Cassette Recorder with Radio	£34	0 0	£26 19 6
PHILIPS 3302 Cassette Tape Recorder	£28	7 0	£21 19 6
PHILIPS 4302 Twin Track	£35	17 6	£25 19 6
PHILIPS 4307 4-track	£49	10 0	£38 19 6
PHILIPS N4404 (4 track stereo)	£43	0 0	£69 19 6
PHILIPS N4407 Stereo	£105	0 0	£89 19 6
PHILIPS N4308	£60	10 0	£49 19 6</

This MONTH'S Best Buy . . .



8

AKG K50 Dynamic Stereo headphones

Complete with spare ear muffs.

Total (value £10/9/0d.) Our Price **£5.18.** + 4/6 p. & p.

Available only from us at this price. Due to entire purchase of manufacturer's remaining stock this fantastic offer is open only while stocks last.

- * High-fidelity reproduction due to broad frequency response (20-20,000Hz)
- * Substantially increased stereo effect
- * Headphones fit the head gently and do not shift
- * Earpieces fit ears snugly (Cardanic suspension)
- * Tone quality superior to conventional loudspeakers.
- * Only expensive studio loudspeakers can match the reproduction quality of the K50.
- * Music can be reproduced at concert hall volume (!), preserving the lower bass notes and brilliant treble tones without causing any strain to the listener.



GARRARD SP25

mk II **£10.19.6** Plus 10/- carriage
Normal price £15.11.4

Single record playing unit. Features include cue and pause and automatic pick-up return and switch off. Wired with mains cable and 5ft. twin screened stereo cable, 5 pin din plug. 10/6 extra. AP75 Complete with base and cover £25 plus 15/- carriage.

PLUGS?



- Pack 107 5-Pin Din 4/-
 - Pack 108 3-Pin Din 3/6
 - Pack 135 1/2" Jack 5/-
 - Pack 130 1/2" Jack Stereo 9/6
 - Pack 103 Loudspeaker Plug 3/-
 - Pack 100 Phono Plug 1/3
 - Pack 230 3-Pin Socket 4/6
 - Pack 236 5-Pin Socket 6/-
 - Pack 234 Loudspeaker Socket 6/-
 - Ready-made Leads
 - 3-pin to 3-pin Din 12/6
 - 3-pin to open end 10/6
 - 5-pin to 5-pin Din 16/-
 - 5-pin to open end 13/-
 - 5-pin to 4 phono plugs 18/6
- All leads approx. 6ft. in length. Post free, by return.

PLINTH & COVER £5.50

Unbeatable Value plus 10/- p. & p

Suitable for AT60; SP25; 3000; 2500; 3500. Superb finish. Spindle can be left in position with cover on. Cover of neutral smoke tint perspex. Also available for AP75; SL99; SL75 £6.17.6 plus 10/- carr.

Replacement Stereo DIAMOND STYLII

8TA 9TA 9TAHC GP91 ST4 ST9 EV26 GC8 **15/-** each others on request p. & p. 1/6

Countdown SPEAKER

Teak Cabinet

£12 insurance & carr. 7/6

A speaker of outstanding specifications and technical merit. Solid teak cabinet size: 14" x 10" x 6". Originally designed for use with our Countdown stereo budget system but now available separately.



EMI 10w matched loudspeaker set 450

Our Price **75/-** inc. 5/- p. & p.

13 1/2" x 8 1/2" elliptical loudspeaker and independent high frequency units with associated crossover network. Frequency range 55 to 13000Hz. The cone of the bass unit has a surround designed for high travel giving freedom from distortion when operated at low frequencies. Also 350 KIT 20W Frequency range: 20 to 20,000Hz. **£7.10.0.** Normal price £12.10.0 plus 8/- p & p. Also 150 KIT 10W 3, 8 or 15 ohms **50/-** plus 8/- p & p



SINCLAIR Project 60

SAVE nearly £5 Normal price £23.18.0d.

Designed for building into plinths etc., complete with two Z30 Output stages **£19** plus 10/- carr.

(20 watt) and power supply unit. Send S.A.E. for full technical brochure.

SINCLAIR 2000 AMPLIFIER SAVE 6ans. Our price 23gns.

Magnetic cartridges

Diamond **95/-** Styli

plus 2/6 p. & p.

Today's value £6.

Stylus replacement can be carried out without removing cartridge. Fully guaranteed.

Ronette 105 Stereo cartridge (Sapphire 78 Diamond LP) 25/- 2/6 p. & p.



SONOTONE Cartridges ...

(Filled Diamond Styli) (Ceramic) list price 82/-

Sensitivity: 9TA 80mV 9TAHC 55mV/cm/sec rms minimum at 45° at 1,000Hz measured on Decca SXL2057 **47/6** plus 2/6 p. & p.



who wants a **£2,000+p.a.** opportunity in the dynamic new computer industry?

In only **4 weeks** you're in – and only the incredible **Eduputer** can make it possible.

Now for the first time anybody can train **outside** the computer industry for a lucrative career as a computer operator, **with actual experience on an Eduputer.**

Who created Eduputer? The internationally famous company Programming Science International. They developed it to the specific requirements of the massive New York city training board and its practical results have been one amazing success story.

We are proud to have been selected as the only commercial training organisation permitted to use the Eduputer in the U.K. **Thanks to Eduputer, nine out of every ten can learn to operate the most advanced computers in only four weeks. Unlike Computer Programming, no special educational qualifications and no maths required. Just you and the incredible Eduputer!**

Jobs galore! The moment you qualify, our exclusive computer appointments bureau introduces you to computer users everywhere with good jobs to offer (up to £40 a week full-time, £50 a week as a temporary). More than enough to go round, too—because 144,000 new operators will be needed over the next five years alone.

This is your big opportunity to get out of a rut and into the world's fastest-growing industry. And remember—LCOT is the only commercial computer school to have Eduputer. It means a lot to employers.

Telephone: (01) 437 9906 NOW!

Or post the coupon today for full details FREE and without obligation.



London Computer Operators Training Centre,

B8 Oxford House, 9/15 Oxford Street, London W.1.

Telephone: (01) 437 9906.

127/131 The Piazza, Dept. B8, Piccadilly Plaza, Manchester 1.

Telephone: (061) 236 2935.

Please send me your free illustrated brochure on exclusive Eduputer "hands on" training for computer operating.

Name _____

Address _____

Tel: _____



J. J. FRANCIS
(WOOD GREEN) LTD
123 ALEXANDRA ROAD, HORNSEY,
LONDON, N.8. Tel: 01-888 1662

handle 100 watts r.m.s. In other words distortion through overloading would occur in the amplifier but never in the speakers.

The overall frequency response of the amplifier is shown in Fig. 17 and the effect of the treble lift and tremulant tone controls in Fig. 18. The reduction in bass response due to the tremulant tone control produces a considerable reduction in the level of lower frequency fundamental notes but ensures a strong build up of third and higher harmonics. The tremulant tone control should be used very little or not at all with bass guitar because of the effect on low frequencies.

Optional Extras

The tremulant control circuit can be switched on or off quite easily by means of a foot operated switch. It is only necessary to provide an extra jack socket on the front panel wired across the tremulant on/off switch (S1) as shown in the circuit (Fig. 5 Part 1). A suggested method of making a suitable foot switch is shown in Fig. 19. The switch must be a press on—press again-off type. Screened leads are not necessary for this, twin flex will do.

The 'wah-wah' effect can be produced by means of a foot controlled potentiometer and capacitor (VR9 and C29 in Fig. 5 part 1). When VR9 resistance

★ components list—optional extras

Tremulant Foot Control:

- 1—Panel jack socket and plug.
- 1—Press on/press off switch.
- Twin flex. Materials for foot control as in Fig. 19.

Wah-Wah Foot Control

- 1—Panel jack socket and plug.
- Screened cable.
- Materials for foot control as in Fig. 20.

is at minimum (foot pedal off) the capacitor C29 is shunted directly across the primary of T3 and severely attenuates the treble response of the tone tremulant amplifier. When the potentiometer is opened (foot pedal on) the shunt effect of C29 is reduced to zero.

The tremulant tone control must be on by about three quarters of its travel to produce the pronounced oom-wah effect when the foot control is operated. A suggested method of constructing a foot control is shown in Fig. 20. When the foot plate is pressed back the potentiometer should be at zero resistance. Screened lead must be used to connect the foot control to the amplifier the inner lead going to the junction C8-T3 IP.

Notes

When the amplifier is finally installed in the cabinet the main input socket panel is screwed to the beading at the rear of the amplifier compartment. The front panel can be secured all round with screws into the beading at the front and by means of two long self tapping screws at the rear as shown in Part 1 Fig. 2D.

The back panel of the speaker compartment must be a close fit and well secured with at least four screws on each side and top and bottom. Do not run the amplifier at full power unless the back panel is fitted and secured. The spaces each side of the mains input panel at the rear can be fitted with hardboard panels to prevent dust getting in and to protect the rear of the amplifier.

The performance of the PW25-50 amplifier has

been checked in every respect and has been used with satisfaction by a semi-professional guitarist with treble and bass guitar. It has been tested with microphone and music sources and with the direct signal level output from an electronic organ.

The writer strongly recommends that only the components, power module and loudspeakers etc. specified are used in order to obtain a performance equal to that specified and he is not prepared to provide modifications to the circuitry for use with other components or for other purposes. ■


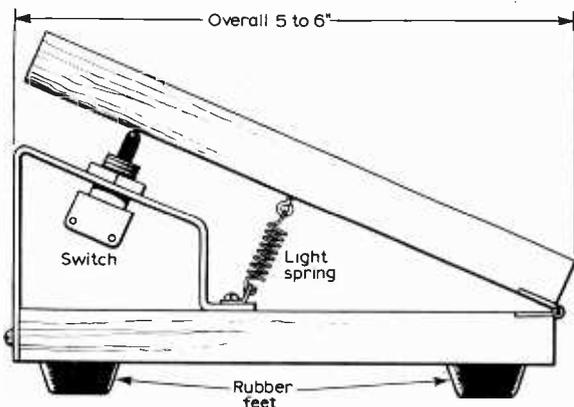


Fig. 19: Suggested construction of foot operated tremulant switch.

Fig. 20: (Below) Practical construction of foot operated wah-wah control.

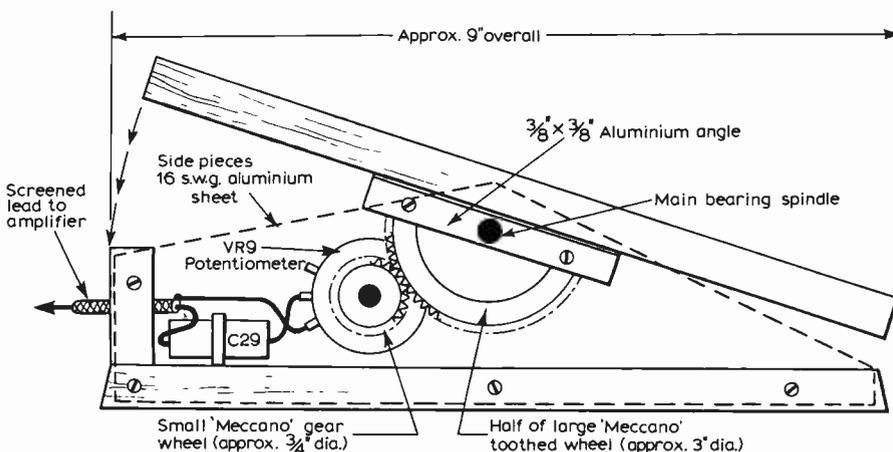

SHOWTIME 1970

A LOOK AT THE LONDON-BASED TRADE SHOWS

FOR the fourth year in succession, this year's radio-trade exhibitions took place in London at the end of August. Most companies showed their products in hotels, but one or two were "at home" to visitors. One enterprising firm ran cruises along the Thames from Westminster.

Altogether, some 40 firms exhibited their products with more than 50 brand-names being in evidence. Once again, the main emphasis was on television, particularly colour television, but one or two trends were apparent in radio.

(Details of new TV receivers and techniques are contained in a special report in the November issue of our companion magazine *Television*, on sale on 23rd October.)


Power Supplies

Although the majority of small portable radio receivers are battery-operated, several of the newly announced models feature internal mains-supply units, so that the sets will work from batteries or the mains supply as required. Two reasons are given for this trend—some firms say that the cost of batteries is now so high that the public is looking for mains-operated sets, and other firms say that most receivers, even very small portables, are used quite often in only one location, so mains operation is just as convenient as battery operation. Whatever the reason, battery/mains receivers are certainly making a come-back.

Readers with long memories will remember the old style battery/mains sets which used "all-dry" valves. Those receivers were not renowned for their reliability. Trouble often occurred in the mains-derived filament supply, and certain faults caused the filaments to burn out. However, running transistorised receivers from the mains is a comparatively simple matter, and the reliability of the modern mains/battery set should be high.

Local Radio

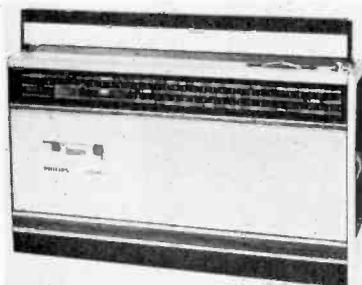The number of portable sets covering the v.h.f./f.m. band seems to be growing, and this may be due to the increasing popularity of local radio stations. The stations operate only on v.h.f./f.m.



Philips RR392 radio cassette recorder for mains/battery operation. Price is £56.



ITT-KB Junior Super v.h.f./f.m. and m.w. has 10 transistors and 400mW output.




Crown TRF-2900L 4-band portable (f.m., m.w., l.w., and 49m. bandspread) Ten transistors. Price is £44 15s. inc. tax.



The Sony TR 1300 5-band portable (medium wave plus four short waves.) Price is £45.

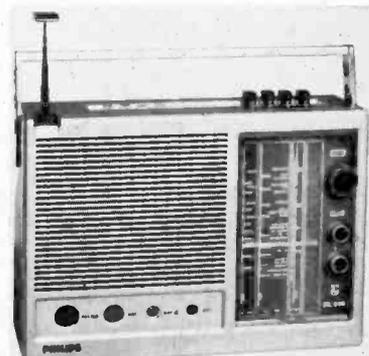
(Below) Philco T 240 13-transistor 5-band portable priced at £43 19s.



The Philips RL500 portable receiver with input/output sockets on the cabinet front. Price is £50.

at the moment, and the original 8 are now being supplemented by a further 20 (details of frequencies etc. are available from BBC Engineering Information Department, Broadcasting House, London, W.1).

Incidentally, certain local stations will use slant polarisation of signals instead of the horizontal polarisation used previously for all v.h.f./f.m. services. The stations involved are at Blackburn (96.4MHz), Derby (96.5MHz), and Manchester (95.1MHz). Leicester (95.05MHz, later 95.2MHz) and Nottingham (94.8MHz) will be converted to slant polarisation later. The use of s.p. should improve reception of v.h.f. in cars and in other circumstances where vertical receiving aerials are used (see News pages).

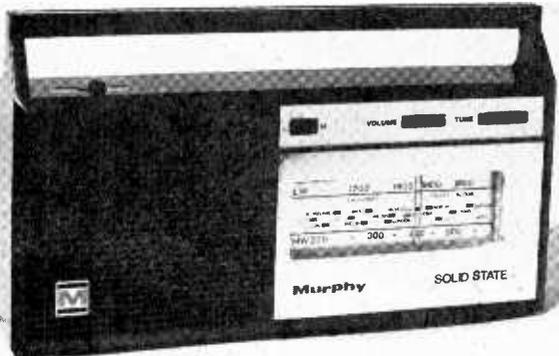

The Murphy B866 two-band l.w. and m.w. radio. Price, £11 10s.

The BBC states that it is not necessary or advisable to adjust outdoor v.h.f./f.m. aerials for slant polarisation. However, if for some reason such adjustment is made, the correct position is obtained by turning the aerial 45° from the horizontal, clockwise when looking towards the transmitter.


More v.h.f./f.m. receivers for cars made their appearance at the trade shows, and should be of particular use in the areas of local radio stations, since warnings of local traffic conditions will be featured in the programmes. The resulting increased awareness of v.h.f./f.m. radio should help manufacturers to sell their portable v.h.f. sets too.

Push-Button Tuning

While on the subject of v.h.f./f.m., we note another interesting development: pre-set selection



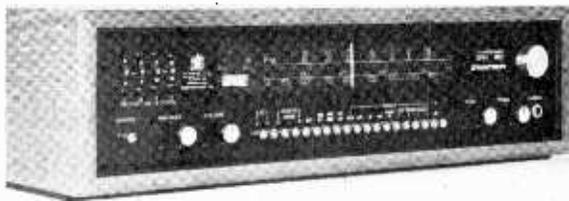
GEC2807 audio outfit with 15W music power per channel. Features Garrard deck and f.m. tuner. Price is £125.



The Dynatron STA 90 stereo tuner/amplifier priced at £165.

of programmes by push-button. Older readers will remember the days of a.m. radios with push-button tuning in which intricate mechanisms were employed to enable pressure on the buttons to rotate or position the ganged tuning capacitor in exactly the spot corresponding to the desired station. Many service engineers will remember the time spent trying to repair or set up the systems which often included gears, stranded-wire drives, and complicated detent mechanisms.

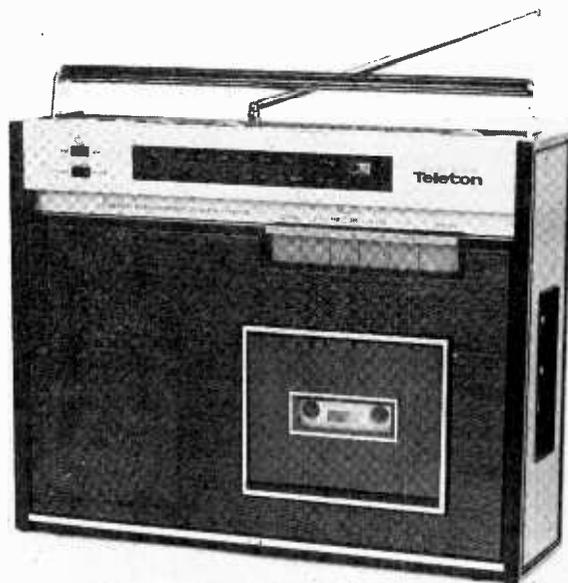The modern push-button set covers v.h.f./f.m. and if push-button selection of stations is held to be valuable on a.m., it is of even greater use on v.h.f./f.m., since most people seem to have difficulty in tuning in f.m. signals correctly, even when a tuning indicator is fitted.



The TRC 530M combined a.m./f.m. radio and cassette recorder from Teleton. Output is 1.6W and price is £47 10s.

The old mechanical system of push-button tuning is of course unsuitable for the high frequencies of the f.m. broadcast band, although no doubt a mechanical system could be made to operate if a very good a.f.c. circuit were included. The modern push-button system has been made possible by the variable capacity diode: a reverse-biased junction diode is connected in the signal circuits as part of the tuning capacitance, and variation of the reverse bias varies the thickness of the depletion layer of the diode, thus varying the effective capacitance. Tuning of the various circuits is carried out by varying the magnitude of the potential fed to the controlling diode or diodes. The push-buttons simply

actuate switches, and therefore need very little pressure to operate them. The "tuning" of each button is accomplished by adjusting a corresponding pre-set potentiometer.

Radio with Tape

Components continue to reduce in size, and many cassette tape recorders now feature an internal radio, the extra circuitry being accommodated with very little change in dimensions. These new recorders should be very popular since they enable radio programmes to be recorded without the use of a special tuner, and there is no longer the difficulty of connecting a portable set or mains receiver to the recorder.

Sockets

To enable receivers to be coupled to tape recorders, many of the new sets have special output sockets. This trend is to be welcomed especially as many of the new sets cover v.h.f./f.m., and are capable of delivering a high quality audio output. Many receivers have input sockets too, to be used to amplify the outputs from tape recorders, record-players, and, in some instances, microphones.

Semiconductors

Integrated circuits have now begun to make their appearance in domestic equipment, though their use is still on quite a small scale. Field-effect transistors are increasingly encountered in front-ends, and as a result, performances are steadily improving.

Crystal filters are used in i.f. strips in several receivers; they should be welcomed by service engineers since there are then fewer cores for customers to adjust!

Origins

Apart from equipment made in this country, most of the items shown were from Japan. However, there were receivers from Hong Kong, Germany and India. The Indian sets are being marketed here after a successful trial import of 10,000. The com-

pany concerned hopes to extend the range to include v.h.f./f.m. receivers.

Combination

The small size of modern components is continually having effects and is one of the reasons for the emergence of the combined tuners and amplifiers being shown by many firms. The old-style radiogram is less popular now, and the trend is to separate loudspeakers, record decks, and tuner/amplifiers. The radiogram will no doubt retain its popularity with the older generation, but younger ears seem to prefer the better standard of reproduction now obtainable from other types of equipment.

Cabinets

The square-cut cabinets of recent years were continued this year, but some makers introduced a rounded line, perhaps in the hope of starting a new trend. Novelty radios were seen again, with some sets made to resemble old fashioned telephones. Another set was housed in a fur poodle! On rather more sedate lines, a new receiver from another maker was designed to look like a cine camera.

Radios with built-in clocks (or clocks with built-in radios?) were seen at a number of the shows.

Summary

There were no really startling developments in the radio sets shown this year, but this is not to say that progress is not being made. The introduction of i.c.'s and the attention being paid to audio quality, power supplies, and ease of tuning, show that the radio market is still a healthy one. As local radio spreads, whether commercial or not, interest in radio should continue to revive, with radio no longer a poor relation of TV, but an entertainment and information medium in its own right.

Change of Date

By agreement among the various firms, next year's trade shows are scheduled for the end of May instead of the end of August.

CQ! CQ! CQ! CQ! CQ!

ISSUES FOR DISPOSAL

... all 1968 issues of P.W.—G. Taylor, 57 Woodlawn Road, Fulham, London, S.W.6.
... P.W. from June 1965 to September 1967 except for September 1965 and May 1967. S.A.E. for details.—D. Pearey, Matt Baker Hall, Parry's Lane, Bristol, BS9 1AD.
... copies of P.W. and W.W. from 1931 to 1939. The P.W.'s are 1946-47 and odd issues up to 1968.—L. Keyte, 31 Greenfields, Redditch, Worcs.
... a number of P.W.'s from 1955 to 1966. S.A.E. for details.—L. V. Thomas, 69 Haverstock Court, St. Paul's Cray, Kent.
... over 40 copies of P.W. (1967 complete) (1968 January to July) with blueprints. Sell or swap for stamp collection.—Cyril Timmins, 16 High Street North, West Mersea, Colchester, Essex.
... May 1965-April 1966, May 1966-August 1967, January 1968-March 1968.—S. L. Stanbridge, 45 Roman Road, Worting, Basingstoke, Hants.
... P.W. from December 1963 to February 1966. Will sell or exchange for transistor components.—A. Beveridge, The Schoolhouse, Tibbemor, Perth.
... issues of P.W. from 1951 to 1966.—L. Levell, Popes Hill, Newnham, Glos.
... 57 issues of P.W. from 1961-66 in excellent condition. 47 copies before 1961 in reasonable condition. S.A.E. please.—M. Pardoe, 3 Dunwell Avenue, Newby, Scarborough, Yorks.
... many issues of P.W. and P.T.V.—J. Foy, 101 Sandringham Road, Birmingham 22B.
... P.W. from January 1956-April 1968 inclusive. Will sell or swap for anything interesting electronic or otherwise.—I. R. W. Bram, 38 Muirfield, Perth, Scotland.
... 1968 issues January-November. Also Radio and Television Servicing 1966-67 models.—A. S. Holmwood, 8 Dock Street, Pembroke Dock, Pembro.
... copies of P.W. from 1959 to 1967 (42 copies).—E. D. May, 104 Northumberland Avenue, Hornchurch, Essex.
... P.W. July 1964 to April 1966, May 1966 to February 1969 and P.E. October 1965 to February 1969. S.A.E. for details.—I. P. Brockley, "Torbeth", New Road, Bignall End, Stoke-on-Trent, Staffs.
... 30 copies (1950-1953) of P.W., 60 copies (1963-1968) of P.W. and 48 copies (1948-1952) R.S.G.B. Bulletin.—W. H. Booker, 45 Annesley Road, Greenhill, Sheffield, 8.
... most copies of P.W. from 1961. S.A.E. please.—P. Barrow-Maudsley, 1a Well Street, Buckingham.

... large numbers of P.W.'s and a full set of P.E. from start to May 1969. Offers.—S. Heap, 29 Broadway, Helmsford, Rossendale, Lancs.
... all 1964, 1965 and 1966 issues. All 1967 except July and the full set of 1968. Can only dispose of in years.—J. Currie, 156 Hillhead Road, Kirkintilloch, Dunbartonshire, Scotland.
... copies of P.W., P.T.V. and P.E. and 400 service sheets. Large S.A.E.'s please.—D. W. Robson, 125 Atkinson Road, Newcastle-on-Tyne, NE4 8XX.
... numbers of P.W. in very good condition.—A. S. Davy, 123 Chapel Road, Brightlingsea, Essex.
... many issues of radio magazines going back to 1946.—A. G. W. Thompson, Thursley Cottage, Church Road, East Molesey, Surrey.
... May 1963, September and November 1964, November and December 1965 and January and February 1966.—D. P. Matthews, 18 Queen Anne's Gardens, Bush Hill Park, Enfield, Middx.
... P.W. issues January to December 1968, January to October 1969 and Radio & TV Servicing 1966-67. S.A.E.—A. S. Holmwood, 8 Dock Street, Pembroke Dock, Pembro.
... many issues of P.W., P.T.V., W.W., P.E. and R.C. Will dispose of in years (12 issues).—E. T. Bradford, 160 West Drayton Road, Colham Green, Uxbridge, Middx.
... most issues of P.W. from 1943 to 1967. Sell or exchange WHY.—W. J. Anderson 18 Stuart Road, Welwyn, Herts.
... an almost mint copy of No. 1, Volume 1 P.W. Offers?—T. E. Phelps, 143 Barn Mead, Harlow, Essex.

BOOKS WANTED

... radio and Television Servicing volumes 61-62, 62-63 and 64-65. Details to P. Hoyle, 95A Pimlico Road, London S.W.1.

CORRESPONDENTS WANTED

... someone of my own age (13) who is studying for the R.A.E.—Kenneth May, 71 West Street, Erith, Kent.
... any reader who has modified and HRO. Also any reader who would be willing to sell me coil packs for this set and anyone who can give me information on the QP166.—Ian Burr, The Hollands, Lower Icknield Way, Chinnor, Oxon.
... a shortwave listener who is also interested in radio and electricity in England.—G. Eveleigh, 28 Reigate Avenue, Sutton, Surrey.
... anyone of my own age (18) who is interested in amateur radio in general.—W. J. Cowell, 35 Bare Avenue, Bare, Morecambe, Lancashire.
... anyone of my own age (11) who is interested in semiconductors.—Paul Mallon, 522 Tay Street, Invercargill, New Zealand.

The 'KIT IDEA' by HEATHKIT

kit building is so easy the
Heathkit way.



TRY IT FOR YOURSELF

**START WITH A SMALL
BUT VERY USEFUL KIT**

**THE NEW HEATHKIT
BATTERY CHARGER**

**PRICE ONLY
£2.18.0. plus carr. 6/-**

**POWERFUL OUTPUT—UP TO 4 AMPS ● FULLY FUSED ● SOLID KNOCKABOUT CASE ●
SAFE DOUBLE WOUND TRANSFORMER ● FOR 6V OR 12V CARS ● ROBUST AMMETER**

Here's the easy to build, inexpensive kit to introduce you to kit building. As well as the fun and fascination of building it yourself you get Do-it-Yourself savings. The clear, simple, fully illustrated instructions make assembly foolproof. This is the battery charger to keep your car battery in top working condition.

Hurry, and make sure of your order today.

P.S. This also makes an excellent seasonal present . . .



A Schlumberger Company

HEATH (Gloucester) LTD GLOUCESTER GL2 6EE

(Block capitals please)

Name.....

Address.....

Post Code.....

Please send me a battery charger kit for
which I enclose £3.4.0, including carriage.

51/11A

BSR 4-SPEED SUPERSLIM AUTO RECORD CHANGER

Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 18 months' guarantee. Size 13 1/2" x 11 1/2" x 4 1/2". Above motor board 3 1/2". below 2 1/2". AC 200/250V.



with STEREO/MONO XTAL £7 Post 5/-
BSR UA70 Stereo/Mono Transcription Auto Changer. Calibrated Stylus Pressure. BSR Minichanger UA60 Stereo/Mono. Plays 12", 10" or 7" records. Size 12" x 8 1/2". AC 200/250V. Post 5/- £8

GARRARD PLAYERS with Sonotone 9TA Cartridges. Stereo Diamond/Mono Sapphire. SP25 Mk II 315 AT50 Mk II 215 Model 3000 213 Post 5/-
RECORD PLAYER PORTABLE CABINET Space for amplifier and autochanger. Post 5/- 75/-
RCS DE-LUXE 3 WATT AMPLIFIER. Ready made with 2-stage triode pentode valve, 3 watts output. Tone and volume controls. Isolated mains transformer, knobs, loudspeaker valves ECL82, EZ80. Response 50-12,000 cps. Sensitivity 200mV. Post 5/- £3
R50 2 WATT AMPLIFIER with loudspeakers and valves UCL82 and UY85 Post 5/- £3


E.C.S. TEAKWOOD BASE. Ready cut out for mounting (State plate make and model). E.C.S. PLASTIC COVERS FOR ABOVE BASE. Durable tinted plastic, attractive appearance. 7/6
EMI PICK-UP ARM. Complete with mono cartridge 29/6
EMI JUNIOR 4 SPEED RECORD PLAYER £3 Post 5/-
Mains operated motor, turntable and pick up HI-FI PICK UP CARTRIDGES GP94 55/-; GP93 45/-; GP91 30/-; GP67 19/6; ACOS L.P. only 10/6. All standard fixing complete with stylus.

CRYSTAL MIKE INSERTS

1 1/2" dia. 6/6. ACOS 1 1/2" dia. 12/6. BMS, 1" dia. 9/6.

PORTABLE AMPLIFIER

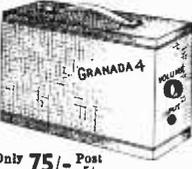Portable mini p.a. system. Many uses - ideal for Parties, or as a Baby Alarm, Intercom, Telephone or Record Player Amplifier, etc. Attractive resin covered cabinet, size 12 x 9 x 4 1/2", with powerful 7 x 4 in. speaker and four transistor one watt power amplifier. Uses 3 x 9 battery. Brand new with famous maker's guarantee. Only 75/- Post 5/-



WEYRAD P50-TRANSISTOR COILS
BA2W Ferrite Aerial .13/-
Osc. P50/LAC 6/-
I.F. P50/SC 470 kc/s. 6/7
3rd I.F. P50/SCC 6/7
P51/1 or P51/2 6/7
P50/SV 6/7
Ferrite Rod 8 x 1/4 in. 4/-, 6 x 1/4 in. 5/-

VOLUME CONTROLS
Long spindles, Midget Size 5 K. Ohms to 2 Meg. LOG or L.W. 1/8 3/1-. D.P. 5/-
STEREO L/S 11/-, D.P. 15/-
EDGE 5K. S.P. Transistor, 5/-
WIRE-WOUND 3-WATT POTS. Small type with small knob. Values 10Ω to 30 K. Carbon 20 K to 2 meg. 5/-
VEROBOARD 0.15 MATRIX 2 1/2 x 5 in. 3/8. 2 1/2 x 3 in. 3/2. 2 1/2 x 3 1/2 in. 3/2. 3 1/2 x 5 in. 5/2.
EDGE CONNECTORS 16 way 5/-. 24 way 7/6.
PINS 28 per packet 3/4. FACE CUTTERS 7/8.
S.E.R.P. Board 0.15 MATRIX 2 1/2 in. wide 6d. per lin., 3 1/2 in. wide 9d. per 1 in.: 5 in. side 1/- per lin. (up to 17 in.). S.E.R.P. undrilled 1/4 in. Board 10 x 5 in. 3/-.

BLANK ALUMINIUM CHASSIS. 18 s.w.g. 2 1/2 in. sides, 7 x 4 in., 6/-; 11 x 3 in., 7/8; 11 x 7 in. 9/8; 13 x 9 in., 10/6; 15 x 14 in., 15/-; 9 x 7 x 2 in., 8/6; 14 x 11 x 2 in., 14/6.
ALUMINIUM PANELS 18 s.w.g. 12 x 12 in. 6/6; 14 x 9 in. 5/6; 12 x 8 in. 4/6; 10 x 7 in. 3/6; 8 x 6 in. 2/6; 6 x 4 in. 1/6.
1-inch DIAMETER WAVE-CHANGE SWITCHES. 3 p. 6-way, or 2 p. 6-way, or 3 p. 4-way 4/6 each. 1 p. 12-way, or 4 p. 2-way, or 4 p. 3-way 4/6 each. 1 inch DIAMETER Wavechange "MAKITS" 1 p. 12-way, 2 p. 6-way, 3 p. 4-way, 4 p. 3-way, 6 p. 2-way, 1 waf. 12/-, 2 waf. 18/-, 3 waf. 24/-, 4 waf. 30/-, 5 waf. 38/-, 6 waf. 42/-.
TOGGLE SWITCHES. sp. 2/6; sp. dt. 3/6; sp. dt. 3/6; dp. dt. 4/6.

ALL PURPOSE HEADPHONES
H.R. HEADPHONES 2000 ohms Super Sensitive . . . 35/-
LOW RESISTANCE HEADPHONES 2-5 ohms . . . 39/6
DE LUXE STEREO HEADPHONES 8 ohms . . . 65/-



"THE INSTANT" BULK TAPE ERASER AND RECORDING HEAD DEMAGNETISER 200/250 v. A.C. Leadset S.A.E. 47/6 Post 2/6

Minimum Post and Packing 2/6 RETURN OF POST DESPATCH. HI-FI STOCKISTS. CUSTOMERS FREE CAR PARK. 337 WHITEHORN ROAD, CROYDON

564

★ GENERAL PURPOSE TRANSISTOR FRE AMPLIFIER BRITISH MADE ★

Battery 9-12v or H.T. line 200-300v D.C. operation. Size 1 1/2" x 1 1/2" x 1/2". Response 25 cps. to 25 K/s. 26db gain. For use with valve or transistor equipment. Full instructions supplied. Brand new. Guaranteed. Details S.A.E. 17/6 Post 2/6

NEW TUBULAR ELECTROLYTICS
2/350V . . . 2/8 100/25V . . . 2/- 16/1500V . . . 11/-
4/350V . . . 2/8 200/25V . . . 2/8 50/350V . . . 7/-
2/450V . . . 2/8 500/25V . . . 2/8 60+100/350V . . . 11/6
16/450V . . . 3/- 8+8/450V . . . 3/8 32+32/250V . . . 3/8
32/450V . . . 4/- 8+16/450V . . . 4/- 32+32/450V . . . 6/6
25/25V . . . 2/- 16+16/450V . . . 5/- 32+32+32/350V . . . 9/9
50/50V . . . 2/- 32+32/350V . . . 100-50+50/350V . . . 9/6

SUB-MIN. ELECTROLYTICS 1, 2, 4, 5, 6, 8, 16, 25, 30, 50, 100, 200mF 15V 2/-; 500, 1000mF 15V 3/6; 2000mF 25V 7/-
CERAMIC 1µF to 0.01 µF. 9d. 1µF Mica 2 to 5000pF, 9d. PAPER 350V-0.1 8d. 0.05 2/6; 1mF 3/-; 2mF 150V 3/-; 500V-0.001 to 0.05 9d. 0.1 1/-; 0.25 1/6; 0.47 5/-; 1.000V-0.001, 0.0025, 0.0047, 0.01, 0.02, 1/6; 0.047, 0.1, 2/6. SILVER MICA. Close tolerance 1% 2-500pF 1/8; 500-2,200 pF 2/-; 2,700-5,000pF 2/-; 6,800pF-0.01, mid 6/-; each. TWIN GANG. 40-0° 299pF 1/7; 130°; Slow motion drive 365+365 with 25+25pF 11/-; 500pF slow motion, standard 9/-; small 3-gang 500pF 25/-; SHORT WAVE. Single 25pF 11/-; CHROME TELESCOPIC AERIAL 23in. 5/-
TUNING. Solid dielectric. 100pF, 300pF, 500pF, 7/- each. TRIMMERS. Compression 30, 50, 70pF, 1/-; 100pF, 150pF, 1/8; 250pF, 1/6; 500pF, 750pF, 2/-; 1000 pF, 2/6. RECTIFIERS. COGNAC COOLERS. 100mA 60mA 7/6; 55mA 9/6. SILICON DIODES. BY100 10/-
Full wave Bridge Rectifiers 75mA 10/-; 150mA 19/6. EX-GOVERNMENT RECTIFIERS 250V, 200mA, 6/-
NEON PANEL INDICATORS 250V AC/DC Red, Amber 4/-
RESISTORS. Preferred values, 10 ohms to 10 meg. 1/6
1/2 w. 1 w. 2 w. 20% 3d. 1 1/2 w. 5d. 2 w. 1/-; 1 w. 10% 6d. HIGH STABILITY. 1 w. 2% 6 ohms 1 1/2 w. 2/-
Diode 500mA Preferred values 10 ohms to 22 meg. 9d. WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt, 10 ohms to 100K. 2/- each; 21 watt, 1 ohm to 3.2 ohms 2/-

Q MAX CHASSIS CUTTER

Complete a die, a punch, an Allen screw and key
1 in. 10/6 1 1/2 in. 17/6 1 3/4 in. 19/6 1 1/2 in. 24/- 2 1/2 in. 44/3
1 1/2 in. 16/6 1 in. 19/6 1 1/4 in. 20/6 1 1/2 in. 29/6 2 1/4 in. 57/3
1 in. 16/9 1 1/4 in. 19/6 1 1/2 in. 21/6 2 in. 39/9 1 in. sq. 38/6

TRANSISTOR MAINS POWER PACES. FULL WAVE 9 volt 500mA. Size 4 1/2 x 2 1/2 x 1 1/2 in. Metal case. 78/-
Crackle finish. Output terminals. On/Off switch.
Half Wave 9 volt 60mA. Size 2 1/2 x 1 1/2 in. Snap terminals 36/-

MAINS TRANSFORMERS

250-0-250 50 mA. 6.3 v. 2 amps. center tapped . . . 22/-
250-0-250 90 mA. 6.3 v. 4 amp. 28/-
250-0-250 80 mA. 6.3 v. 3.5 amp. 6.3 v. 1a. or 5 v. 2a. 38/-
350-0-350 90 mA. 6.3 v. 3.5 amp. 6.3 v. 1a. or 5 v. 2a. 38/-
300-0-300 120 mA. 6.3 v. 4 a. C.T. 6.3 v. 2 a. 50/-
MINIATURE 200 v. 20 mA. 6.3 v. 1 a. 2 1/2 x 2 1/2 in. 15/-
MIDGET 220 v. 45 mA. 6.3 v. 2 a. 2 1/2 x 2 1/2 in. 18/-
HEATER TRANS. 6.3 v. 1 1/2 a. 10/6
Ditto tapped sec. 1.4 v. 2, 3, 4, 5, 6.3 v. 1 1/2 amp. . . 15/6
GENERAL PURPOSE LOW VOLTAGE. Outputs 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30 v. at 2 amp. . . 38/-
1 amp. 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60, 38/-
AUTO TRANSFORMERS 0-115-230 v. Input/Output, 60 v. 18/6; 150v. 38/-; 500v. 25/-; 1000v. 21/2.
CHARGE TRANSFORMERS. Input 200/250V. for 6 or 12v. 1 1/2 amp. 24/-; 4 amp. 35/-
FULL WAVE BRIDGE CHARGE RECTIFIERS: 6 or 12 v. output, 1 1/2 amp. 8/-; 2 amp. 11/-; 4 amp. 17/-

COAXIAL PLUG 1/8, PANEL SOCKETS 1/8. LINE 3/6. OUTLET BOXES. SURFACE OR FLUSH 5/6.
BALANCED TWIN FEEDER 1/8 - 30 ohm or 800 ohms. JACK SOCKET 3/4 open-circuit 2/6, closed circuit 4/6; Chrome Lead Socket 7/8. Phone Plugs 1/-, Phone Socket 1/-, JACK PLUGS Std. Chrome 3/-; 3.5mm Chrome 2/6. DIN SOCKETS Chassis 3-pin 1/6; 5-pin 2/-. DIN SOCKETS Lead 3-pin 3/8; 5-pin 5/-. DIN PLUGS 3-pin 3/6; 5-pin 5/-. VALVE HOLDERS. 1/-; CERMAMIC 1/6; CARB 1/-.

E.M.I. 1 1/2 x 8 in. LOUDSPEAKERS

With flared tweeter cone and ceramic magnet. 10 watts. Bass res. 45-60 cps. Flux 10,000 gauss. State 3 or 8 or 15 ohm Post 2/6
Also with twin tweeters. With crossover, 10 watt. State 8 or 15 ohm. Post 2/6
Recommended Teak Cabinet Size 16 x 10 x 6 in. Post 2/6 £5

MINI-MODULE LOUDSPEAKER KIT

10 WATT 65/- CARRIAGE 5/-
Triple speaker system combining on ready cut baffle. In chipboard 15 in. x 8 1/2 in. Separate Bass, Middle and Treble loudspeakers and crossover condenser. The heavy duty 5 in. Bass Woofer unit has a low resonance cone. The mid-Range unit is specially designed to add drive to the middle register and the tweeter recreates the top end of the musical spectrum. Total response 30-15,000 cps. Full instructions for 3 or 8 ohms. TEAK VENERED BOOKSHELF ENCLOSURE. 16 x 10 x 9 in. Modern Scandinavian fluted front design for Mini-Module. £5 Post 2/6

ALL MODELS "BAKER SPEAKERS" IN STOCK

BAKER 12in. MAJOR £9

30-14,500 c.p.s., 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwell. Bass resonance 40 cps. Rated 30 watts. Voice coils 3 or 8 or 15 ohms. Post Free
Module kit, 30-17,000 c.p.s. with tweeter, crossover, baffle and instructions. £11.10.0

BAKER "GROUP SOUND" SPEAKERS - 8 or 15 ohm 'Group 25' 'Group 35' 'Group 50' 12in. 12in. 15in. 15in. 25 watt £7 25 watt £9 25 watt £19

TEAK HI-FI SPEAKER CABINETS. Fluted wood front. For 10 or 12in. round Loudspeaker £3.0.0
For 12 x 8in. or 8in. round Loudspeaker £5.0.0
For 10 x 6in. or 6in. round Loudspeaker £4.0.0
LOUDSPEAKER CABINET WADDING 18in. wide, 3/4 in.

TWO-WAY XOVER NETWORK 3000 c/s.

With variable tweeter attenuator giving accurate high/low frequency balance. Mounted on 2 1/2 in. x 4 in. with control knob, tweeter and woofer leads and input terminals. Suitable for 8 to 8 ohm impedance 38/-
Horn Tweeters 2-16k/s. 10W 8 ohm or 15 ohm 29/6
De Luxe Horn Tweeters 2-18 K/s. 15W, 18 ohm 59/6
ELAC MOVING COIL, Deluxe cone tweeter 8/8 ohm 55/-
TWO-WAY 3000cps CROSSOVERS 3 or 8 or 15 ohm 19/-
SPECIAL OFFER! 80 ohm 2 1/2 in. 2 1/2 in. dia.; 85 ohm 3in. 25 ohm 2in. dia.; 6 x 4 in.; 8 x 3 in.; 8 x 6 in. 15 ohm 3 1/2 in. dia.; 7 x 4 in.; 8 x 3 in.
8 ohm, 6 x 4 in., 3 ohm, 3 1/2 in. 5 in. 5 x 3 in. 7 x 4 in. 8 LOUDSPEAKERS P.M. 3 OHMS. 6 1/2 in. 22/6; 3 x 6 in. 25/-; 3 x 2 in. 18/-; 3 in. 35/-; 10 x 6 in. 38/-
3 in. WOOFER 3 watts max. 20-10,000 cps. 8 or 15 ohm 36/-
ELAC 8 in. De Luxe Ceramic 3 ohm or 15 ohm 50/-
SPECIAL OFFER - FAMOUS RICHARD ALLAN LOUDSPEAKERS 8 or 10 or 12in. Twin cone 3 or 15 ohm 39/6.
OUTPUT TRANS. EL84 etc. 5/-; MIKE TRANS. 50A 5/-
SPEAKER COVERING MATERIALS. Sampler Large S.A.E.

VHF-FM TUNER FRONT END

88-100 Mc/s
Transistor FM tuner oscillator and frequency changer printed circuit. Slow motion tuning gang condenser. Ready wired and tested including two transistors AP124 and AP125. A total of 39 components. Size 2 1/2 x 2 in. Requires I.F. and Detector stages 10.7 Mc/s. 9 Volt. Connection details supplied but we have no further information available. 45/- POST FREE

ALL EAGLE PRODUCTS

SUPPLIED AT LOWEST PRICES ILLUSTRATED EAGLE CATALOGUE 5/- Post Free.
BARGAIN AM TUNER. Medium Wave. Transistor Superhet. Ferrite aerial. 9 volt. £4
BARGAIN 4 CHANNEL TRANSISTOR MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt. £3
BARGAIN FM TUNER 88-103 Mc/s 8in. 3in. Transistor. 9 volt Printed Circuit. Calibrated slide dial tuner. Walnut Cabinet. Size 7 x 5 x 4 in. £10
BARGAIN FM TUNER as above less cabinet £7.10.0
FM STEREO MULTIPLEX ADAPTOR. For above or general use. Ready made with 4 transistors, 6 diodes. 99/6
BARGAIN 8 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built, with volume control. 9v. 69/6
★ RADIO BOOKS ★ (Postage 9d.)
Practical Radio Inside Out 4/6
Practical Stereo Handbook 3/8
Supersensitive Transistor Pocket Radio . . . 3/6
Radio Valve Guide, Books 1, 2, 3 or 4 ea. 5/- No. 5 ea. 6/8
T.V. Fault Finding 406/625 lines 8/6
Transistor Communication Sets 6/-
Wireless World Radio Valve Data 10/-
Transistor Circuits for Radio Controlled Models 7/6
Valves, Transistors and Diodes equivalents Manual . . 10/6
Coil design & construction 5/-
Hartley on Hi-Fi Radio Tuners 5/-
22 Transistor for Micro Alloy transistors 6/-
Practical Car Radio Installation 6/-

E.M.I. TAPE MOTORS

120V or 240V A.C. Heavy Duty Illustrated 1,200 r.p.m. 4 pole 135mA 25/- Post 3/6

BALFOUR GRAM MOTORS

120v. or 240v. A.C. Size 2 1/2 x 2 1/2 in. Clockwise 1,200 r.p.m. 4-pole 17/6 Post 50mA. Spindle 1 x 3/20

337 WHITEHORN ROAD, CROYDON Open 9-6 p.m. (Wednesdays 9-1 p.m., Saturdays 9-5 p.m.) Buses 133, 68 pass door. S.R. Stn. Selhurst. Tel. 01-604-1665

SHORT WAVES

MONTHLY NEWS FOR DX LISTENERS

DESPITE the warm weather I have received a record number of reports and I will start with one from:

C. R. S. Stacey of Tunbridge Wells who has a Lafayette HA-700 and a Joystick and an a.t.u. which enabled him to hear:

3306 Tentative logging of Rhodesia B.C. in English with much interference. 2000-2030, SINPO 21531

6175 *O.R.T.F.* relay of France Inter, 1920-1940, 45454

9520 *Kuwait B.S.* in Arabic from 1937 to 2024, 33533

9525 *Polish Radio* in English at 1931-1956, 33543

9625 *Israel B.A.* in English at 2052-2130, 33343

21535 *Radio RSA* to Africa in Eng., 1251-1550, 35232

Roderick Downes of Bournemouth does not have a communications receiver but he used his seven-valve domestic superhet. and 60ft. long-wire to hear some interesting stations including:

11652 *R. Pakistan*, Karachi in English at 2030, 55344

15018 *R. Hanoi*, in Eng. at 2000 and French at 2030

15265 *R. Afghanistan* to Europe, // to 17745, 1800

15345 *Kuwait B.S.* in English from 1830, 45344

17825 *NHK, Japan* also on 21535 in English at 0800

Richard Read of Portsmouth is only fourteen years old but this did not prevent him from using his Practical Wireless Modular Three-Band Short-Wave receiver and 17ft. vertical aerial to hear the following stations:

11710 *ABC, Australia*, English to Asia from 0900 to 1100

11720 *R. Trans Europe* in English, 0900-1000

15120 *Colombo B.S.*, Ceylon at 2000

17760 *Radio New York Worldwide* at 1900

21500 *Vatican Radio* in English from 1145 to 1205

Terry Gibbs of Swindon who is a regular reporter to this column has heard some very interesting stations recently including:

3338 *Radio Mozambique*, // with 4805 at 1500

3390 *Radio Rhodesia* in English at 2200

5985 *Radio Tangiers* at 1900-0300

6130 *Radio Halifax*, Nova Scotia at 0350-0400

9720 *Radio Haiti* at 1100-1500. (New freq. to me—MC)

Philip Batt of Littleborough in Lancashire has sent in another interesting report which included:

4865 *PRC5, R. Belem*, Brazil in Port. 0300, 32323

4920 *YVKR, R. Caracas*, Venezuela, Spanish at 0400

4980 *YVOC, Ecos del Torbes*, Venezuela in Sp. 0405

THE BROADCAST BANDS

Malcolm Connah

Frequencies in kHz ● Times in GMT

5095 *HJGG, R. Sutatenza*, Colombia, Indent. at 0300

17710 *R. Mali*, Bamako, French at 1745. (New freq?—MC)

C. J. Craven of Bexhill-on-Sea used his Eddystone EC10 and Joystick antenna to hear:

6125 *Voice of America*, 'The Breakfast Show' 0245

6230 *Radio Tirana*, Albania, Indent. at 0250

15165 *Damascus*, Syria in English at 1930

John Adams has recently moved to Cleethorpes where he has set up his Eddystone EC10 and 100ft. long-wire and managed to hear:

11765 *CBC, Canada*, Eng. to S. Africa at 0738

11825 *Radio Sofia*, with sign-off in English, 1930

17810 *R. Nederland*, Bonaire in Spanish at 2130

21640 *R. Nederland*, Bonaire in English at 1840

Regular reporter, **S. R. Wainwright** of St. Helens has again used his Skyrover Mk II and 100ft. long-wire to hear stations from all over the world:

4970 *YVLK, R. Rhumbos*, Venezuela in Spanish, 0400

4990 *YVMQ, R. Barquisimeto*, Ven. with 24 hour sched.

11865 *R. Trans Europe*, Portugal in Eng. 1345-1415

21545 *Radio Ghana* at 1445-1530 in // with 17870

S. J. Plant of Cwmbran in Monmouthshire has sent in another log which contained:

9515 *R. Ankara*, Turkey in Turkish at 2025

11765 *HCJB, Ecuador* in English from 2300 to 0000

11815 *Trans World Radio*, Bonaire, Eng. 0040-0130

15220 *R. Vilnius*, Lithuania in English, 2230-2300

Amongst those who sent in their reports in the form of news was **Roy Patrick** of Derby who contributed the following items:

KENYA The Voice of Kenya on 4915 now provides a good signal in the evening until sign-off at 2000. The programming is mainly pop and African music with commercials in Swahili.

GHANA Radio Ghana on 4915 is audible after Kenya signs-off on the same frequency. The signals are of fair strength and the programmes are in English.

LIBYA has been heard on the frequency of 9895 in the evenings and is at present providing a very strong signal.

UNITED ARAB REPUBLIC The Voice of Africa in Cairo has been heard in English at 2030 on 17725 with an excellent signal.

Robert Bruce of Angus in Scotland was amongst the many who sent in reports about *Radio Trans Europe*. The latest news of this station is that they are beaming test transmissions to the United Kingdom from 1345 to 1415 daily on 9625 and 11865.

SHORT WAVES

THE AMATEUR BANDS

David Gibson, G3JDG

Frequencies in kHz • Times in GMT

WHATEVER happened to all those l.f. lovers? More logs are coming in for 144MHz than 1.8, 3.5 and 7MHz put together. About 90% of the thuds on my doorstep were logs for 20 metres which must win the award of the most listened-to band this past month.

Things will doubtless change, but the propagation experts say that conditions should improve for the h.f. enthusiast so the 28MHz band might be worth a listen.

Regarding listening procedures. Many listeners switch straight to their favourite band (usually 14 or 21MHz) and prowl round with the dial logging everything which titivates the headphones. It is suggested that all serious listeners should check all bands before making a final selection. Many people will only switch to another band if their particular r.f. hero is dead.

John Moore (Leicester), queries ZA1AA who was asking for QSLs to be sent to P.O. Box 295, Tirana. John says he knows that there is no official amateur radio in Albania but thinks this one is legit, and probably operating underground. John is learning c.w. but says copy is difficult due to the hot weather making his b.f.o. drift. (How about negative temp. coefficient capacitors or perhaps a sun blind over the b.f.o.?)

Logs

Peter Baldwin (Peterborough), has a home-brew transistor receiver with 70ft. of wire round the attic. He reports 3.5MHz heavily laden with EU-type signals but managed to hook VS5RG.

John Moxham (Somerset), HRO5 plus a.t.u. and a 67ft. end-fed at 40ft., had a sniff around 80 metres. Best on s.s.b. were: UK9AAN, PY3BAD, PY4BLS, PY7BHW, while c.w. raised ZS1MH and ZD9BH.

A quick nip up the r.f. ladder brings us to 21MHz. **Tom Maxwell** (Lanarkshire), CR70A, 18ft. end-fed, is a man of few words. Amongst those few this month were: CR6MT, CX9CO, DK2WV/CN8, EA8GZ, EL2CB, ET3DS, HB9YC/4W1, HS1ACW, IT1SEZ/P1U (Ustica Is.), JA1SQI, JY1 (King Hussein of Jordan), KP4DAL, KV4FQ, KZ5AM, LU2ZE, MP4BHH, OA4LM, PY1JZ, SVOWY, VE7EL, VP2MM, W6MSM, XW8DM, 4N2HV, 4U1ITU, 4Z4AB, 5H3JR, 5K3LR, 6W8DY, 9H1BX, 9J2PV, 9Q5WF, 9X5PB. Type of emission not specified—probably s.s.b.

14MHz Happenings

Anderson strikes again! This time, Tim has an HRO MX of his own complete with 66ft. end-fed. Squeaks of s.s.b. on 14MHz from: AX6MK, CE3WN, CR6GA, HC6MJ, H1ISO, HK3CA, HK6AVR, HR2VFB, JY1, K6JW, KZ5KB, LI5K, LU2DAW, PY2EAL, TG7WT, T12JO, VE1TC, VK3XB, VP2VI, VP7CT, W6KH, WØCJZ, WA7CQA, WB6OC/MM/TG, XE1KV, YN1ZZ, YV1YC, ZC4MT, ZL1AJ1, ZM3QN, ZM4BO,

3A2CP, 4N2BR, 4X4RW, 5Z4MO, 6W8DY.

M. Cranage (Birmingham), P.W. superhet as per April 1967 plus "modifications" and a 50ft. end-fed. sends in some goodies gleaned from 14MHz. Among the s.s.b. was: AX2VK, AX3TG, AX5AZ, AX7IL, CE6GY, CO2FA, CR6CA, HK5AZ, HP1CU, HR1KRF, K2ALO/P/OHØ, K6UNT/KL7, OA4XN, SV1EC, TF3BV, VE1CF, VK3ZL, VK7IZ, VS5RG, WA1NGK/TF, W6CYU, WB6EZN, 5N2ABG.

Another son of sideband is **C. Smith** (Solihull), whose R1155 and 40ft. end-fed showed great affection for: CN8BG, CR5SP, CR6YS, CR7GJ, ET3DS, HK4MP, HR2WTA, HS4ADB, KP4CQB, PY1CAD, PZ5RK, SV1BV, TA1NC, TF3HS, UW9EA, XW8DK, YO4CT, 4N2KO, 4U1ITU, 4X4AE, 4Z4HE, 5Z4MO, 9H1CB, 9M6BA, 9N1MM.

L. Boucher (Glamorgan), describes his set up as 110ft longwire, home brew a.t.u. and one Virgin R1155. (Oah, ain't he bold!). Sideband sigs. from: AP2KS, AP5HQ, CR6MR, CR7LE, EA8HB, EL2K, EP2DA, JA1ITE, JA3DWA, JAØCJF, JH6OR, JY1, KR6EZ, KV4FA, LU3OAC, LU8ATB, MP4BIR, OX5AP, OY7JD, PY4FQ, PY6BP, PY7AEG, SM6ALJ/MM (Persian Gulf), TR8LB, VE1WZ, VK5NS, VP2AD, VQ9E, XW8DK, YV4WT, ZB2A, ZD7SD, ZS2H, 4N2SO, 4S7AB, 4X4HF, 5Z4MI/A, 6W8DY, 6Y5SR, 7X2SMA, 9H1CF, 9K2AG, 9Q5CO, 9V1QE. For all the technological revolution, you wonder if transistors could pull in very much more.

Award for persistence and courage this month must surely go to **H. Goodwin** who, despite attempts by a neighbour to stop him with a hedge clipper, carried on listening on 20 metres.

Higher Still

No brave soul has sent in a 70cm. log yet although threats to do so have been received. Nearest band to date is 144MHz which, it seems, is attracting quite a number of listeners.


Lurking near Canterbury at a place called Chilham is a two element yagi hidden in a loft. Tracing the feeder will lead you to a converter feeding an R107 tuning 14-16MHz. The enraptured creature listening to the signals will almost certainly be **Stephen Lloyd**. Observe the smile and squeaks of delight as the following are logged: F9UP/P, ON4FL, ON4HV, ON4RY, ON4VB, ON4ZN, ON5QW, PAØLCD, PAOPAL, PAOSWS.

Contests

Contests are appearing to go on ad infinitum. For October we've got: October 3-4, I.A.R.U. Region 1 u.h.f./s.h.f. listeners contest (gen. from the R.S.G.B.); 10-11, ten metre phone contest (should be interesting); 24-25, 40 metre c.w. contest (this one really separates the men from the boys); 24-25, CQ WW d.x. contest; November 7-8, 40 metre phone contest; 7-8, 2 metre c.w. contest.



LIND-AIR AUDIO

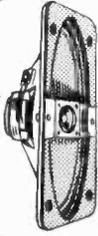

E.M.I. LOUDSPEAKERS
MODEL 450 13 1/2" x 8" elliptical with twin tweeters. 8 ohm impedance. 10 watts. Brand New, guaranteed. Lind-Air Price 89/6 P. & P. 4/6.
MODEL 150 13 1/2" x 8" elliptical. 3 and 15 ohm impedance. 10 watts. Lind-Air Price 59/6 P. & P. 4/6.
TEAK FINISH SPEAKER CABINETS
 Size 16" x 10" x 9". Ideal for above units £5.19.6

HI-TONE RECORDING TAPE

BRITISH MADE TOP QUALITY

J1001	3"	L.P. PVC	225ft.	5/6	P & P 1/2
J1002	3"	T.P. Poly	600ft.	10/6	P & P 1/2
J1003	5"	L.P. PVC	900ft.	10/-	P & P 1/8
J1004	5"	D.P. Poly	1200ft.	15/-	P & P 1/8
J1005	5 1/2"	L.P. PVC	1200ft.	12/6	P & P 2/-
J1006	5 1/2"	D.P. Poly	1800ft.	22/6	P & P 2/-
J1007	7"	S.P. PVC	1200ft.	12/6	P & P 2/6
J1008	7"	L.P. PVC	1800ft.	17/6	P & P 2/6
J1009	7"	D.P. Poly	2400ft.	25/-	P & P 2/6
J1010	7"	T.P. Poly	3600ft.	50/-	P & P 2/6
C60	Cassette	(Library cased)		8/6	P & P 1/-
C90	Cassette	(Library cased)		13/-	P & P 1/-
C120	Cassette	(Library cased)		18/-	P & P 1/-




DE-LUXE STEREO HEADPHONES
 With soft rubber earpieces. Impedance 8-16 ohms. Frequency response 23-13,000 cps. With lead and stereo plug.
59/6 P. & P. 3/6.

SOLDERING GUN



Comfortable grip with trigger control. "U" shaped 3 1/2" bit to minimise wear. Light beam is automatically directed on to end of bit when ON/OFF trigger is in use 230-250 volts. 85 watt element 49/6 P. & P. 3/6.

C.1001 MULTI-TESTER

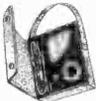

Size of meter 4 1/2 x 3 1/2 x 1 1/2 in. Complete with leather case. 85/- P. & P. 3/6.

Overload protection 20,000 ohm. AC volts 10, 50, 250, 1,000v. DC volts 5-25, 125, 500, 2500v. D.C. Current 0-50 uA, 0-250 mA. Resistance 0-80K, 0-6 Meg ohm. Decibels -20 to +22dB.

FIRST TIME EVER! SOLID STATE RADIO HEADPHONES

• STEREO EFFECT RADIO
 • POWERFUL TRANSISTOR RADIO BUILT INTO HEADPHONE WITH TUNING AND VOLUME CONTROL
 • TWIN TELESCOPIC AERIAL RODS
 • TWIN MAGNETIC SPEAKERS—ONE IN EACH EARPIECE

Listen to all your favourite radio programmes anywhere and anytime. Lightweight and comfortable to wear. Covers full medium waveband, supersensitive tuning control and variable volume control. Ideal for outdoors and indoors.
ONLY £10.19.6. P. & P. 4/6.

600 WATT LIGHT DIMMER SWITCH


Same size as standard wall switch and will dim incandescent lighting from full on to off. Heavy plastic box with control knob. LIND-AIR PRICE £4.10.0. P. & P. 3/6.

62D. MULTI-TESTER




20,000 p.p.v. DC voltage 5-25-50-250-500-2.5 K (20,000 ohms per volt). AC voltage: 10-50-100-500-1000 volts (10,000 ohms per volt). DC Current: 0-50 uA, 0-2.5 mA, 0-250 mA. Resistance: 0-8K, 0-6 Mg (300 ohm and 30K at centre scale). Capacitance: 10f to .001 mfd. .001 uf to 1 uf. Decibels: -20 to +22dB. Size 4 1/2 x 3 1/2 x 1 1/2 in. 71/- P. & P. 3/6.

S-DEC BREADBOARD

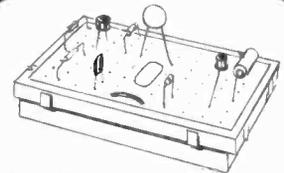

British Made
 Solderless breadboard panels, for fast reliable component connections. Single DeCs. One S-DEC with Control Panel, Jigs and Accessories for solderless connections to controls, etc., with booklet "Projects on S-DEC" giving construction details for a variety of circuits. 29/6. P. & P. 2/6.
 4-DeC KIT. Four S-DeCs with two Control Panels, Jigs and Accessories and the booklet "Projects on S-DEC" all contained in a strong attractive plastic case. Ideal for the professional user. £5.17.6. P. & P. 3/6.
 T-DeC KIT £2.10.0. P. & P. 3/6.

SINCLAIR PROJECT 60

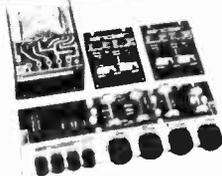

An attractive alternative for the enthusiast prepared to assemble these excellent modules to make a stereo assembly. 7.50 24 watt Power Amplifier 89/6 (2 required). Stereo Sixty Control/Pre-amplifier £9.19.6. PZ.5 Power Supply Unit £4.19.6. SINCLAIR PROJECT 60 Package deal price 18 GNS. P. & P. 12/6. Project 60 is supplied complete with instruction manual and templates for blind mounting.

SINCLAIR IC-10 INTEGRATED CIRCUIT

10 watt Amplifier. Size only 1 x 0.4 x 0.2in. A true hi-fi amplifier complete with manual giving details of a wide range of applications and instructions. Guaranteed 5 years.
ONLY 59/6 P. & P. 1/6.
 SPECIAL TRANSFORMER FOR OPERATING SINCLAIR IC-10 from A.C. mains 230/250v. Output 13v. at 0.5 amp. 16/6 P. & P. 2/6.

NEW from Mullard! UNILEX Audio Modules

Now you can build your own stereo units as you want them, and entirely in your own home.

A good quality stereo amplifier can be built with no electrical knowledge. All solid state—Baxendall tone control circuit—no soldering—terminal block connections throughout.



Everything you need to know about UNILEX SYSTEMS is in the Mullard book "Do it yourself stereo". Superb designs, detailed plans, simple instructions in non-technical language covering 4 systems in 4 price ranges.

Send for your copy now 5/- Post Free.

UNILEX Audio Modules

Amplifier Module EP9000	£2.18.0 each
Pre Amplifier Module EP9001	£3. 2.0 "
Power Supply Module EP9002	£4.12.0 "
Control Panel Assembly and Escutcheon Plate	£3. 5.0

BUILD A STEREO AMPLIFIER FOR ONLY

£16.15.0 P. & P. 7/6



Garrard HI-FI TURNTABLES



2025 T/C with stereo cartridge	£8.19.6
3000 with Sonotone	
9TAHCD stereo cartridge	£10.19.6
SP25 Mk II	£15.19.6
SL65B	£15.19.6
Base and cover for above	£5.19.6
AP75	£18.10.0
SL72B	£24.19.6
SL75B	£28. 7.0
SL85B	£39. 9.0
401	£28.10.0
Base and cover for above	£8.19.6
P. & P. Decks 12/6. Base & Cover 10/- Deck/Base/Cover 17/6.	
SPECIAL OFFERS!	
SP25 MkII with base £14.10.0. P. & P. 15/-.	
SP25 Mk II with Sonotone 9TAHCD cartridge and base £15.15.0. P. & P. 15/-.	
Sonotone 9TAHCD cartridge £2.15.0 P. & P. 1/6.	

18/19,25 & 53 TOTTENHAM CT. ROAD, LONDON W.1.

Telephone: 01-580 2255/4532/7679

Open 9-6 pm. Monday to Saturday. Thursday until 7 pm.

All Mail Orders and correspondence to Dept L5/11, Kirkman House, 54a Tottenham Court Road, London, W.1. Tel: 01-580 7041/2.

LOW PRICE, HIGH QUALITY SPEAKER SYSTEMS

All cabinets are new and carefully designed acoustically with speakers mounted on 3/4 in. chipboard baffles. All speakers are ex-TV high quality with hi-flux magnets carefully matched and tested.




COWDREY FIVE. Specially designed Corner Cabinet 20 1/2 x 13 x 7 1/2 in. deep. Finished in natural teak veneers with Vynair front. Fitted rubber feet. Five speaker units 15 ohms. impedance handles 15 watts. £6.0 P. & P. 9/6.



ADASTRA DOUBLE 5 stereo solid state amplifier housed in handsome cabinet veneered in natural teak. Size 11 1/2 x 6 x 5 1/2 in. 10 Transistors—power output 5 watts peak per channel. 220-240V A.C. Output impedance 12 to 15 ohms (our Cowdrey speaker system eminently suitable). Smart blue escutcheon. £14.14.0. P. & P. 10/6.

SCOTT. This elegant tapered cabinet 10 1/2 x 16 x 5 1/2 in. deep is attractively finished in black cloth with striped grey Vynair front. Suitable for table or for wall mounting. Fitted with 13 1/2 x 8 in. speaker unit and volume control, 3 or 15 ohms impedance—please state impedance required. £4.5.0. P. & P. 7/6d each. Fitted with E.M.I. 13 x 8 in. speaker unit and twin tweeters, 15 ohms impedance, capacity 10 watts. 35/- extra.

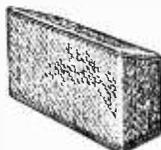

CAXTON COLUMN. This is a column cabinet 23 1/2 x 5 1/2 x 5 1/2 in. deep finished in black or wood grain cloth with blue Vynair front. Keyhole slot for wall mounting. Fitted with three speaker units, 9 ohms impedance. Handles 8 watts. Makes all the difference in quality and volume of tape recorders and record players. Real bargain at 59/6d. P. & P. 11/- each.

smart gold and brown Vynair front trimmed with white. Fitted re-coned 5 in. 3 ohm speaker. The baffle is half inch thick. A real bargain at 37/6. P. & P. 4/9.



IMP. Wedge shaped extension speaker 7 1/2 x 6 1/2 x 4 in. (max.). Covered in walnut wood grain cloth with foam Vynair front. Keyhole slot at back. Fitted with 3 ohm speaker unit. Only 25/6d. P. & P. 5/- each.



EARPIECES WITH CORD and 3.5mm. plug, 8 ohm magnetic, 3/-, 250 ohm 4/-, 180 ohm with clip, 8/6. Xtal. P. & P. 6d.

PIANO KEY PUSH BUTTON SWITCHES. 7 button inc. mains on off. 6 banks of 6 P.C.O., 8/6. P. & P. 2/-.

CARTRIDGES. Stereo: Sonotone 9TA H/C Diamond 47/6. Ronette S105 Medium Output, 28/6. S106 High Output 28/6. Acos GP93 1 Sapphire, 37/6. GP94 1 Sapphire, 39/6. GP91 Stereo Compatible (High, Medium or Low Output), 25/-, TA700 equivalent to B.S.R. SX1M, 35/-, Japanese equivalent to B.S.R. TC8s, 35/-, P. & P. 1/6.

Mono: Acos GP67/2 will replace Collaro and Garrard Mono cartridges, 18/6. T.T.C. Crystal High Gain, 15/-, B.S.R. TC8H Jap. equivalent, 25/-, P. & P. 1/6.

The **SHELLEY.** Size 21 x 11 x 6 1/2 in. An extremely elegant speaker system made of 12 mm. chipboard covered with teak leathercloth with dark Vynair front (send S.A.E. for cloth samples). This unique system uses three ex T.V. speaker 6 1/2 in. round for the Bass, 7" x 3" for the Middle and 5 in. round for Treble. Carefully matched and tested. Will handle 10-12 watts and will match 8 ohms impedance. If preferred the speakers can be wired in series parallel to match 3 ohms impedance. A real bargain at £4.19.6 plus 12/9 P. & P. **MATCHING TRANSFORMER** for 15 ohms 16/- post free



THE FIESTA 59/6

P. & P. 5/6
Brit. Isles.



Speaker and Volume control. Teak veneered with Black Vynair and Gold Fleck. 10" x 7 1/2" x 3 1/2" deep. 3 ohm ex TV Speaker.

Telephone Pick-up, 10/6. P. & P. 1/-, Xtal. label Mike, 7/6. Guitar Mike, 12/6 P. & P. 1/-.
FERROX RODS: 6 x 1 1/2 in., 2/6; 4 1/2 x 1 1/2 in., 2/-, P. & P. 1/- each.
FERROX RODS WITH COILS, 4 1/2 x 1 1/2 in., 3/6; 8 x 1 1/2 in., 5/6. P. & P. 1/- each.
ROTARY SWITCHES: 2 Pole Mains Switch, 3/-; 1 pole 12 way, 2 pole 2 way, 3 pole 3 way, 3 pole 4 way, 4 pole 3 way, 3/8 each. P. & P. 1/-.
TRANSISTOR SPEAKERS 3 ohm 2 in., 8/6, 3 in., 10/6. P. & P. 1/6.
SPEAKERS: E.M.I. 13 1/2 x 8 in., 3 ohm, 50/-, 15 ohm 00/00, P. & P. 5/6. E.M.I. 3 in. tweeter 17/6. P. & P. 2/6. E.M.I. 13 1/2 x 8 in. fitted two 2 1/2 in. tweeters, 15 ohm 90/-, P. & P. 5/6. E.M.I. 13 1/2 x 8 in. (15 ohm) Hi-Fi quality £5.19.6. P. & P. 5/6. E.M.I. Woofers, 6 1/2 x 6 1/2 in. square, 8 ohm, 59/6. P. & P. 4/6. E.M.I. Crossover 16/6. P. & P. 1/-, EAGLE Crossover units 3 or 16 ohms 17/4. P. & P. 1/6. Bakers 12 in. 25 watt 8 & 15 ohms £7. P. & P. 5/6. 9x6 in. ELAC 15 ohm, £3.0.0 59 RM 109.

BROADWAY ELECTRONICS

(Nr. Tooting Broadway Underground Station)

92 MITCHAM ROAD, TOOTING BROADWAY, LONDON S.W.17 01-672 3984

(Closed all day Wednesday)

AMATEUR RADIO TECHNIQUES

By Pat Hawker, G3VA

Third edition just published. Revised and enlarged. Now contains 208 pages and nearly 500 diagrams. 22s post paid

THE VHF-UHF MANUAL

By George Jessop, G6JP

A complete manual for frequencies above 30 MHz. Covers aerials, receivers, transmitters and test equipment. The first book of its kind outside the USA. 23s post paid

RADIO COMMUNICATION HANDBOOK

RADIO COMMUNICATION HANDBOOK



over 22,000 copies sold

Now in its second printing

The standard work in its field

832 pages of everything in the science of radio communication. The handbook's UK origin ensures easy availability of components. 69s post paid

Obtainable from:

RADIO SOCIETY OF GREAT BRITAIN
35 DOUGHTY STREET, LONDON, WC1N 2AE

WRITE NOW FOR YOUR


FREE CATALOGUE

CONTAINING

THOUSANDS OF COMPONENTS

From:

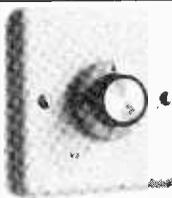W.E.C. LTD., 74, THE STREET, ASHTEAD, SURREY



The Nite-Lite dimmer switch will dim up to 400 watts of incandescent lighting from zero to full brilliance. This unit simply replaces the normal light switch, and is supplied with MK mounting frame for use where more depth is required.

Price built and tested 63/-
complete kit 55/-

All orders C.W.O. + 1/6 p & p Trade enquiries welcome

DIATHANE LTD.

111, Sheffield Rd., Wymondham, NORFOLK.

PRINTED CIRCUIT PROBLEMS ?

Prototype circuits produced from your artwork: 2/- per sq. in. + 2/6 p & p.
Small to medium batch production at reasonable rates!
Complete design and manufacture from circuit diagrams!

Fairchild

μL **914 sssss!** X STOCK 8/-

Quadrac 400v 4A (as used in our lamp dimmer) 29/6
Untested SCR's 300v 1A T05 case 2/- SAE for full list.

TAKE 20

JULIAN ANDERSON

A series of simple transistor projects, each using less than twenty components and costing less than twenty shillings to build.

THE circuit shown in Fig. 1 is one that I have used on a number of occasions for boosting low level audio signals; the gain is high—about 40dB—and the input and output impedances nicely match most transistor equipment. It can be used to boost the output from a crystal set or tuner with inadequate output or raise the output of a microphone, tape head or magnetic pick-up for feeding into an insensitive amplifier. Note that no frequency correction is incorporated and so, although this little signal booster will provide a much higher level, correction is still necessary when used with tape heads or magnetic pick-ups.

The Take 20 series is aimed mainly at the beginner and, since this month's circuit is extremely simple, we are going to go into the circuit in great detail and discuss why the circuit is so designed, why certain choices are made and discuss the function of every component.

TRANSISTOR CHOICE

First of all we decide that we want a preamplifier with high gain for audio frequency usage and that we want to use a readily available power source—namely a 9V battery.

Transistors can be used in three modes—common emitter, common base and common collector. Since we want to match normal transistor impedances for input and output and we want the highest overall gain we shall settle for the common emitter mode. Now for the choice of transistor; we already know that we want a high gain one which will operate well at 9V. In any early stages (which is where this stage will be used) we want to keep the noise as low as possible so the choice of a low noise type would be best. We then look through manufacturer's or supplier's lists and we find quite a variety which will fit the bill, so we go for the cheapest which is a BC169C, which happens to be a silicon NPN type.

Since we are unlikely to use the preamp in extremes of temperature and since silicon transistors are not greatly affected by temperature (at least compared to germanium) we need not worry about having a resistor and by-pass capacitor in the emitter circuit, this can be connected directly to the negative rail.

COLLECTOR LOAD

We know that we shall have to supply current to the collector through a load resistor. For efficient, low noise operation the collector current should be about 0.5mA in such a stage and the collector voltage half the supply volts—namely 4.5V.

No. 19 GENERAL PURPOSE PREAMPLIFIER

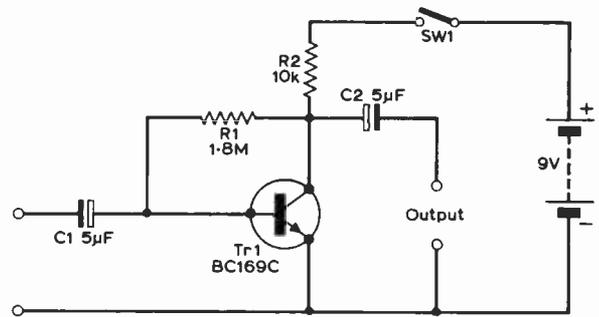


Fig. 1: The circuit of the preamplifier, the calculation of the values are shown in the text.

A simple application of Ohm's Law ($V=IR$) shows that the collector resistor should be 9,000Ω, we use the nearest preferred value, 10kΩ.

BASE BIAS

For the transistor to operate, a bias must be applied to the base. Now before we calculate its value, we must first decide where we get it from. We could take the supply from the 9V connection or from the nominal 4.5V at the collector of the transistor. If we take it from the collector we will be applying a measure of a.c. negative feedback and helping to maintain d.c. stability, so we take it from there.

Now the gain of a BC169C can vary from about 500 to 900, we shall take the lowest figure for the purpose of calculation and we know that the collector current has been set at 0.5mA or 500μA therefore the base current should be 1μA. The voltage at the base of the transistor should be 0.6V (typical value for silicon transistor and the collector voltage is 4.5V so the base bias resistor should drop $4.5-0.6=3.9V$ while passing 1μA. Reverting to our sums and Ohm's Law we find the value coming to 3.9MΩ. In fact this very high value should always be reduced slightly and we use a 1.8MΩ, though it will be found that there will be no noticeable difference between any value from 1.5MΩ to 3.9MΩ.

We have to couple the input to the base and to block the d.c. path this must be connected through a capacitor. The input impedance is about 10kΩ (the usual value for common emitter stages) and for good quality the time constant of the input capacitor and the input impedance should be five times lower than the lowest frequency we wish to amplify which we will assume to be 100Hz therefore the time constant should be 20Hz or 50mS. The time constant is the input impedance (10kΩ) times the input capacitor so this comes out at 5μF. If we wanted to amplify lower frequencies than 100Hz the value of this capacitor would have to go up.

The output capacitor is calculated in a similar way. As far as voltage ratings are concerned, we can see that no more than 9V will ever be applied to either so 9V capacitors are ideal. ■

500kHz CRYSTAL CALIBRATOR

R.W.Bunney

DUE to purchasing a new receiver, to replace an old B40/b unit, there was a need for a 500kHz crystal calibrator. (The B40/b has an internal 500kHz calibrator.) Accordingly the following very simple circuit was constructed, and over the past months has given reliable service. Pips are available up to and exceeding 30MHz. at good strengths.


Circuit

The circuit has an OC171 oscillator stage, followed by a second OC171 as a buffer amplifier. The current taken by the unit is in the order of 4mA at 9 volts.

The crystal obtained is an FT-241A type, marked 'Channel 70'. This is in fact a 54th harmonic type giving 27MHz, hence giving pips at 500kHz intervals. The advantage of using this type is that the price is about one-third that of a standard 500kHz crystal, and is considerably smaller than 10X types. In fact this crystal cost only 5/-.

Adjustment

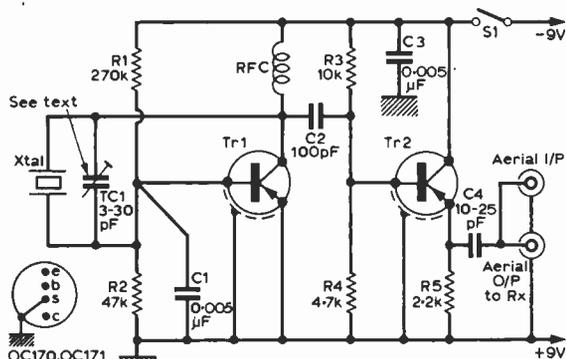In the event of the crystal oscillating slightly h.f., a 3-30pF concentric trimmer capacitor should be shunted across the crystal, and adjusted to obtain zero beat. If too l.f. in frequency, a series capacitor of the same value should be inserted, and adjusted accordingly. Zero beating with one of the standard frequency stations is the best method of setting up the oscillator.



Circuit of the crystal calibrator.

★ components list

Resistors:

R1	270kΩ	
R2	47kΩ	
R3	10kΩ	All ½W 10%
R4	4.7kΩ	
R5	2.2kΩ	

Capacitors:

C1	0.005µF
C2	100pF
C3	0.005µF
C4	10-25pF
TC1	3-30pF trimmer

Semi-conductors:

TR1/2 OC171 or OC170 or AF114

Miscellaneous:

R. F. Choke (Denco RFC10), Diecast box (Eddystone 6908P), SPST switch, 2 Co-axial sockets, Crystal holder and crystal Type FT-241A marked "Channel 70" (Henry's Radio).

The unit has been arranged to be in parallel with the aerial input to the receiver, simply switching it on to check calibration. Other crystals can of course be used in this position, but a 500kHz crystal seems to be the best frequency for broadcast station working.

Depending on the coupling required, a value of between 10pF and 25pF to connect with the aerial connection seems to be adequate. An Eddystone diecast box was used but if this seems extravagant any similar metal container will suffice. ■

QUERY COUPON

This coupon is available until 9th October and must accompany all queries in accordance with the rules of our Query Service.

PRACTICAL WIRELESS, NOVEMBER 1970

BINDERS AND INDEX

Don't let your copies of PRACTICAL WIRELESS become torn and dirty: hard-cover binders are available at 14s. 6d. from:

**BINDING SECTION,
IPC MAGAZINES, LTD.,
SOUTHAMPTON STREET,
LONDON, W.C.2.**

Indexes to Vol. 44, 1968-69, are also available at 1s. 6d. These prices include post and packing.

INCREASE YOUR KNOWLEDGE



Established 1891

MANY COURSES TO CHOOSE FROM incl.


RADIO & TV ENGINEERING & SERVICING,
TRANSISTOR & PRINTED CIRCUIT SERVICING,
COLOUR TV SERVICING, ELECTRONICS,
NUMERICAL CONTROL ELECTRONICS,
TELEMETRY TECHNIQUES, CONTROL SYSTEMS,
ELECTRONICS FOR AUTOMATION,
COMPUTERS, ETC.

ALSO EXAMINATION COURSES FOR

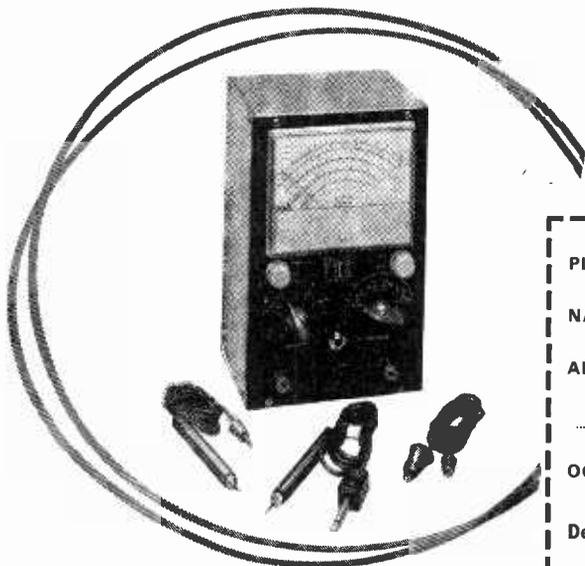C. & G. Telecommunication Technicians' Certificates
C. & G. Electronic Servicing
R.T.E.B. Radio/TV Servicing Certificate
Radio Operator Certificates
Radio Amateurs' Examination
General Certificate of Education, etc.

BUILD YOUR OWN RADIO AND INSTRUMENTS

With an ICS Practical Radio & Electronics Course you gain a sound knowledge of circuits and applications as you build your own 5-valve Superhet Receiver, Transistor Portable, and high-grade test instruments (shown below). Everything simply explained. All components and tools supplied. For illustrated brochure, post coupon below.



RADIO TELEVISION ELECTRONIC ENGINEERING

MEMBER OF THE ASSOCIATION
OF BRITISH CORRESPONDENCE COLLEGES

THERE IS AN ICS COURSE FOR YOU

Whether you need a basic grounding, tuition to complete your technical qualifications, or further specialized knowledge, ICS can help you with a course individually adapted to your requirements.

There is a place for you among the fully-trained men. They are the highly paid men—the men of the future. If you want to get to the top, or to succeed in your own business, put your technical training in our experienced hands.

ICS Courses are written in clear, simple and direct language, fully illustrated and specially edited to facilitate individual home study. You will learn in the comfort of your own home—at your own speed. The unique ICS teaching method embodies the teacher in the text; it combines expert practical experience with clearly explained theoretical training. Let ICS help you to develop your ambitions and ensure a successful future. Invest in your own capabilities.

FILL IN AND POST THIS COUPON TODAY

You will receive the FREE ICS Prospectus listing the examination and ICS technical courses in radio, television and electronics PLUS details of over 150 specialized subjects.

PLEASE SEND FREE BOOK ON.....

NAME

ADDRESS

OCCUPATION..... AGE.....

INTERNATIONAL CORRESPONDENCE SCHOOLS
Dept. 170, INTERTEXT HOUSE, STEWARTS ROAD, London, SW8

11/70

Coils for one band only are shown. L1 is the aerial coil, and L2 the oscillator coil.

The band-switch has six poles, and positions or "ways" for the number of ranges required. (E.g., 3-way, for three bands.) S1 switches aerial coupling windings and S2 base windings. S3 allows each coil to be tuned by VC1, and each coil has a trimmer TC1.

In the oscillator section, S4 and S5 switch collector and emitter circuits, and S6 the tuned winding. Cp is the coil padder, and each range has its own particular value here. For the coils mentioned, the padder is 110pF for long waves, 350pF for medium waves, 110pF for 180-57m, and 3000pF for 60-20m. The 28-9.5m coil requires no padder.

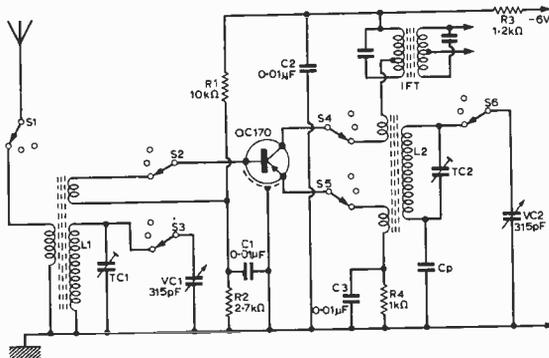


Fig. 6: Adding a s.w. band to a m.w./l.w. receiver.

The changes involved in such a modification depend on the receiver. With a l.w./m.w./s.w. receiver, substituting an additional s.w. range for the l.w. range could be a simple change. But other circuits may need more extensive modifications, and even a change of the mixer transistor, because the type fitted in a m.w./l.w. receiver may be unsuitable for s.w. With most ready-made receivers, conversion to a circuit like that in Fig. 6 will be too difficult. In the case of home-built equipment, it may be felt that it is worth while to retain the i.f. and audio sections, and re-build or modify the first stage so that an all-band circuit such as Fig. 6 can be incorporated. Provided wiring is short and direct, with a reasonably good layout, snags are not likely. Fig. 6 is for a 465kHz i.f. amplifier.

PRACTICAL WIRELESS QUERY SERVICE

Before using the query service it is important to read the following notes:

The PW Query Service is designed primarily to answer queries on articles published in the magazine and to deal with problems which cannot easily be solved by reference to standard textbooks. In order to prevent unnecessary disappointment, prospective users of the service should note that:

- We cannot undertake to design equipment or to supply wiring diagrams or circuits, to individual requirements.
- We cannot undertake to supply detailed information for converting war surplus equipment, or to supply circuitry.
- It is usually impossible to supply information on imported domestic equipment owing to the lack of details available.
- We regret we are unable to answer technical queries over the telephone.
- It helps us if queries are clear and concise.
- We cannot guarantee to answer any query not accompanied by the current query coupon and a stamped addressed envelope.

THE MW COLUMN

MEDIUM WAVE reception from South and East Asia starts in the autumn, the season extending right through until spring. Two times of the day are favourable for DXing; the first covering the period before close down (local time is 4½ to 9 hours ahead of GMT) while the second coincides with morning sign-on. Start about one hour before sunset and look for All India Radio Calcutta on 1130kHz. This 1000kW station signs-off at 1700 hrs GMT and has an English programme from 1530 to 1600 hrs. The Voice of America in Okinawa on 1178kHz is another megawatter. It broadcasts in Far Eastern languages but identifies in English on the hour and half hour and it can often be heard mixed with the Swedish station on the same frequency until 1700 hrs. KSBU 1360kHz is a gospel broadcaster in the Philippines which has programming in Chinese and Japanese until 1730 hrs but can be identified by its western style religious music. Look for Peking on 1000, 1230 and 1290kHz; Kabul Afghanistan on 1280 (until 1830 hrs); HLKX 1190 in Inchon South Korea; BED2 on 750 and BED88 on 1200kHz in Taiwan (Formosa). By mid-winter, DX can be heard as early as 1430 hrs GMT, Chinese stations often being prominent until they become submerged in European QRM as darkness approaches.

Chinese stations are also heard when they sign-on for the day. Lanchow 860; Anwei 940; Peking on 1090 and 1250; Urumchi 1525 along with Hanoi 1010kHz in North Vietnam were all logged after 2300 hrs GMT last winter. Indians are audible at this time too and some of them carry a news bulletin in English at 0110 hrs GMT. Try for Rajkot 1070; Calcutta 1130; Jabalpur 1180; Bibaker 1330. Western Asiatics are logged during the evenings, Bagdad 760 being a regular until 2230 hrs while from Iran there is Radio Irana Teheran on 895; Radio Kermanshah 985 and Radio Ahwaz 1390kHz.

CKGA 730kHz is a new 1kW station in Gander Newfoundland which was logged by the writer on the 12th August and belongs to the CBS network referred to last month. VOCM 590 St John's is the key station of the network and is often audible by 2300 hrs, while CKCM 620 in Grand Falls is usually strong at 0100 hrs when the Egyptian and RNE Tenerife on the same frequency have signed-off. North Americans are usually heard from 2300 hrs onwards once the band starts to clear of Europeans. The easiest is CBA in Moncton, New Brunswick, a 50kW main station of the Canadian Broadcasting Corporation on 1070kHz. CBA shares the channel with Paris 2 but can be logged after the latter goes off at 2300 hrs. Others logged regularly include CBN 640 St John's Newfoundland; WHDH 850 Boston; CJON 930 St John's; CHER 950 Sydney N.S.; WHN New York City on 1050kHz (after the BBC on 1052 closes down); WNEW 1130 also in NYC. Conditions are rather variable on the North American path so try again a few days later if you do not hear DX at the first attempt. When reception is good, many North Americans can be heard by 0100 hrs, an ordinary outdoor TV aerial being quite adequate.

Charles Molloy

Operation

A headphone is connected to the jack socket, or an audio amplifier and speaker to the detector terminals. The unknown capacitor or resistor is connected to the CR terminals and the bridge is switched on. The range switch and bridge potentiometer are then adjusted for balance (zero output), and the value read off the dial.

If the value of the component is completely unknown set the potentiometer to 1:1, centre scale, and turn the range switch to the position which appears nearest to a balance point and then adjust the potentiometer to give the final balance.

Test Voltages

Tr1. Emitter	-1.9V
Base	-2.1V
Collector	-9.0V

Transformer winding resistances

T1. Primary	1-2	25 ohms
"	2-3	80 ohms
Secondary	4-5	2 ohms

The terminals marked 'x' are included so that an external standard may be used, or two components may be compared. For example, if two matched resistors are required for some purpose, one resistor may be connected to the 'x' terminals and a number of resistors of nominally the same value tried in the CR terminals until a balance at 1:1 is obtained. The positions of balance which occur for each of the resistors can be read off as a ratio of their value to the one connected at 'x'. The same applies for capacitors, but on the 'C' range of the dial. ■

TELEVISION in the NOVEMBER issue

OSCILLOSCOPE PREAMPLIFIER

A further feature in our series on i.c.s for the constructor. This preamplifier uses two MC-1709CG i.c.s and is primarily intended for increasing the sensitivity of oscilloscopes though it can also be used as a general-purpose accessory, for example as an r.f./i.f./a.f. signal tracer. It provides stable voltage gain up to 200 and when used with the P.T.V. Videoscope MV3 boosts the basic sensitivity from 100 mV/cm. to a maximum of 0.5 mV/cm.

625 CONVERSION UNIT

Some well-built 625-line conversion units by the original Murphy firm are currently available on the surplus market. The kit includes valves and u.h.f. tuner and is therefore a complete u.h.f. receiver unit. David Robinson describes the unit and suggests ways in which the constructor can adapt it for his own purposes.

PLUS ALL THE REGULAR FEATURES

On Sale OCTOBER 23rd price 3s. 6d.

NEXT MONTH IN

PRACTICAL WIRELESS

FREE WALL CHART!!

In the December issue of PW we shall be presenting the first of two new free wall charts on AUDIO STANDARDS. Full details of the DIN audio specifications and test conditions for hi-fi systems and record/tape/tuner/amplifier combinations presented in a format convenient to both the professional engineer and the home constructor.

HF COMMUNICATION RECEIVER

All the amateur bands from 1.8 to 29.5 MHz are covered in this double-conversion all-transistor receiver. Adequate selectivity for good reception on s.s.b. is obtained using a special arrangement of standard i.f. transformers. Full details are given for the construction of all the tuning inductors together with precise alignment procedure.

AUDIO-VISUAL TESTER

A very useful little piece of equipment for the workshop allowing continuity testing to be carried out easily without the usual constant visual reference to a testmeter.

TELEPHONE AMPLIFIER

This device picks up the stray magnetic fields around a telephone and amplifies them to feed a loudspeaker which can be of great benefit in noisy locations.

PLUS THE REGULAR "TAKE 20" AND "I.C. OF THE MONTH" SERIES AND OTHER CONSTRUCTIONAL ARTICLES AND FEATURES

Don't miss your copy of the December issue of Practical Wireless—on sale 6th November—price 3s. 6d.

TYPE 13A DOUBLE BEAM OSCILLOSCOPES



An excellent general purpose 17" H. oscilloscope. T.B. 2 cps-750 Kc/s. Bandwidth 5.5 Mc/s. Sensitivity 33mV/C.M. Operating voltage 0/110/200/250V. A.C. Supplied in excellent working condition. £22.10.0. (Carriage 30/-).

AVO CT471A MULTIMETER

Battery operated. Fully transistorised. Sensitivity 100mΩ/v. Measures A.C./D.C. Voltages 12mV to 1,200V. A.C./D.C. Current 12mA to 1.2 Amp. Resistance 12 ohm to 120 mΩ. HF, VHF, UHF Voltage with multiplier 4V to 400V up to 50 Mc/s, 40mV to 4V up to 1,000 Mc/s. Offered in perfect condition. £55 each. Carr. 10/-.

CRYSTAL CALIBRATORS NO. 10



Small portable crystal controlled frequency meter. Size 7 x 7 1/2 x 4in. Frequency range 500 Kc/s-10 Mc/s (up to 30 Mc/s on harmonics). Calibrator dial. Power requirements 300V D.C. 15mA and 12V D.C. 0.3A. Excellent condition. 89/8. Carr. 7/6.

CLASS D WAVEMETERS



A crystal controlled heterodyne frequency meter covering 1-7.8 Mc/s. Operation on 6 volts D.C. Ideal for amateur use. Available in good used condition. £5.18.8. Carr. 7/6. Or brand new with accessories. £7.18.6. Carr. 7/6.

B.C. 221 FREQUENCY METERS

Latest release 125 KHz-20 MHz. Excellent condition. Fully tested and checked and complete with calibrator charts. £27.10.0 each. Carr. 10/-.

AM/FM SIGNAL GENERATORS



Oscillator Test No. 2. High quality precision instrument made for the industry by Alrmec. Frequency coverage 20-80 Mc/s. AM CW FM. Incorporates precision dial level meter, precision attenuator 1μV-100mV. Operation from 12 volt D.C. or 0/110/200/250 volt A.C. Size 12 x 8 1/2 x 9in. Supplied in brand new condition complete with all connectors fully tested. £45. Carr. 20/-.

AVO CT.38 ELECTRONIC MULTIMETERS


High quality 97 range instrument which measures A.C. and D.C. Voltage, Current, Resistance and Power Output. Ranges D.C. volts 250mV-10,000V. (10 meg Ω-110 meg Ω input). D.C. current 10μA-25 amps. Ohms. 0-1,000 meg Ω A.C. volt 100mV-250V (with R.F. measuring head up to 250 Mc/s). A.C. current 10μA-25 amps. Power output 50 micro-watts-5 watts. Operation 0/110/200/250V. A.C. Supplied in perfect condition complete with circuit lead and R.F. probe. £25. Carr. 15/-.

ADMIRALTY B.40 RECEIVERS

High quality 10 valve receiver manufactured by Murphy. Coverage in 5 bands 650 Kc/s-30 Mc/s. I.F. 500Kc/s. Incorporates 2 R.F. and 3 I.F. stages, bandpass filter, noise limiter, crystal controlled B.F.O. calibrator I.F. output, etc. Built-in speaker, output for phones. Operation 150/230 volt A.C. 230mA. Weight 114lb. Offered in good working condition. £22.3.0. Carr. 30/-.

TO-2 PORTABLE OSCILLOSCOPE

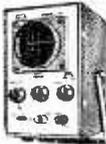A general purpose low cost economy oscilloscope for everyday use. Y amp. Bandwidth 2 CUPS-1 MHz. Input imp. 2 meg Ω 25 P.P. Illuminated scale. 2in. tube. 115 x 160 x 230mm. Weight 8lb. 220/240 V a.c. Supplied brand new with handbook. £22.10.0. Carr. 10/-.



SEW PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES, ETC.
● LOW COST ● QUICK DELIVERY ● OVER 200 RANGES IN STOCK ● OTHER RANGES TO ORDER

NEW "SEW" DESIGNS!

CLEAR PLASTIC METERS



TYPESW.100
100 x 80 mm.

30μA	69/6	20V. D.C.	59/6
50-0-50μA	67/6	50V. D.C.	59/6
100μA	67/6	300V. D.C.	59/6
100-0-100μA	65/-	1 amp. D.C.	59/6
500μA	62/6	5 amp. D.C.	59/6
1mA	59/6	300V. A.C.	59/6
		VU Meter	75/-

BAKELITE PANEL METERS

TYPE S-80
80 mm.
square fronts

50μA	62/6	50V. D.C.	49/6
50-0-50μA	59/6	300V. D.C.	49/6
100μA	57/6	1 amp. D.C.	49/6
100-0-100μA	57/6	5 amp. D.C.	49/6
500μA	52/6	300V. A.C.	52/6
1mA	49/6	20V. D.C.	49/6
		VU Meter	67/6

"SEW" CLEAR PLASTIC METERS

Type MR.85P. 4 1/2in. x 4 1/2in. fronts.



30μA	72/-	50μA	52/-
50-0-50μA	62/-	100μA	52/-
100μA	62/-	500μA	52/-
100-0-100μA	62/-	1 amp.	52/-
500μA	57/8	5 amp.	52/-
500-0-500μA	55/-	15 amp.	52/-
1mA	52/-	30 amp.	52/-
1-0-1mA	52/-	20V. D.C.	52/-
5mA	52/-	50V. D.C.	52/-
10mA	52/-	150V. D.C.	52/-
		300V. D.C.	52/-
		15V. A.C.	52/-
		300V. A.C.	52/-
		8 Meter Ima	52/8
		VU Meter	72/-
		1 amp. A.C.*	52/-
		5 amp. A.C.*	52/-
		10 amp. A.C.*	52/-
		20 amp. A.C.*	52/-
		30 amp. A.C.*	52/-

Type MR.52P. 2 1/2in. square fronts.

50μA	42/-	10V. D.C.	40/-
50-0-50μA	52/-	20V. D.C.	40/-
100μA	52/-	50V. D.C.	40/-
100-0-100μA	47/8	300V. D.C.	40/-
500μA	45/-	15V. A.C.	40/-
1mA	40/-	300V. A.C.	40/-
10μA	40/-	8 Meter Ima	42/-
50μA	40/-	VU Meter	42/-
100μA	40/-	1 amp. A.C.*	40/-
500μA	40/-	5 amp. A.C.*	40/-
1 amp.	40/-	10 amp. A.C.*	40/-
5 amp.	40/-	20 amp. A.C.*	40/-
10 amp.	40/-	30 amp. A.C.*	40/-

Type MR.65P. 3 1/2in. x 3 1/2in. fronts.

50μA	67/6	10V. D.C.	42/-
50-0-50μA	55/-	20V. D.C.	42/-
100μA	55/-	50V. D.C.	42/-
100-0-100μA	52/-	150V. D.C.	42/-
200μA	52/-	300V. D.C.	42/-
500μA	47/8	15V. A.C.	42/-
500-0-500μA	42/-	50V. A.C.	42/-
1mA	42/-	150V. A.C.	42/-
5mA	42/-	300V. A.C.	42/-
10mA	42/-	500V. A.C.	42/-
50mA	42/-	8 Meter Ima	47/6
100mA	42/-	VU meter	67/6
500mA	42/-	50mA A.C.I.	42/-
1 amp.	42/-	100mA A.C.*	42/-
5 amp.	42/-	200mA A.C.*	42/-
10 amp.	42/-	500mA A.C.*	42/-
15 amp.	42/-	1 amp. A.C.*	42/-
20 amp.	42/-	5 amp. A.C.*	42/-
30 amp.	42/-	10 amp. A.C.*	42/-
50 amp.	47/8	20 amp. A.C.*	42/-
5V. D.C.	42/-	30 amp. A.C.*	42/-

MARCONI TF885 VIDEO OSCILLATORS
0-5 mc/s Sine Square Wave £45. Carr. 20/-.

*MOVING IRON-
ALL OTHERS MOVING COIL
Please add postage



SEND FOR ILLUSTRATED BROCHURE ON SEW PANEL METERS—DISCOUNTS FOR QUANTITIES

Type MR.38P. 1 21/32in. square fronts.



50μA	40/-	200mA	27/6
50-0-50μA	37/6	300mA	27/6
100μA	37/6	500mA	27/6
100-0-100μA	35/-	750mA	27/6
200μA	35/-	1 amp.	27/6
500μA	30/-	2 amp.	27/6
500-0-500μA	27/6	5 amp.	27/6
1mA	27/6	10 amp.	27/6
1-0-1mA	27/6	3V. D.C.	27/6
2mA	27/6	10V. D.C.	27/6
5mA	27/6	15V. D.C.	27/6
10mA	27/6	20V. D.C.	27/6
20mA	27/6	100V. D.C.	27/6
50mA	27/6	150V. D.C.	27/6
100mA	27/6	300V. D.C.	27/6
150mA	27/6	300V. A.C.	27/6
		8 Meter Ima	42/-
		VU meter	42/-

Type MR.45P. 2in. square fronts.

50μA	45/-	5 amp.	30/-
50-0-50μA	42/-	15V. D.C.	30/-
100μA	42/-	20V. D.C.	30/-
100-0-100μA	37/6	50V. D.C.	30/-
200μA	37/6	300V. D.C.	30/-
500μA	32/-	15V. A.C.	30/-
500-0-500μA	30/-	300V. A.C.	30/-
1mA	30/-	8 Meter Ima	37/6
10mA	30/-	VU meter	45/-
50mA	30/-	1 amp. A.C.*	30/-
100mA	30/-	5 amp. A.C.*	30/-
500mA	30/-	10 amp. A.C.*	30/-
1 amp.	30/-	20 amp. A.C.*	30/-
		30 amp. A.C.*	30/-

"SEW" BAKELITE PANEL METERS

Type MR.65. 3 1/2in. square fronts.

500μA	35/-	500mA	35/-
1 amp.	35/-	1 amp.	35/-
5 amp.	35/-	5 amp.	35/-
15 amp.	35/-	15 amp.	35/-
30 amp.	35/-	30 amp.	35/-
50 amp.	35/-	50 amp.	35/-
5V. D.C.	35/-	5V. D.C.	35/-
10V. D.C.	35/-	10V. D.C.	35/-
20V. D.C.	35/-	20V. D.C.	35/-
50V. D.C.	35/-	50V. D.C.	35/-
150V. D.C.	35/-	150V. D.C.	35/-
300V. D.C.	35/-	300V. D.C.	35/-
50V. A.C.*	35/-	50V. A.C.*	35/-
150V. A.C.*	35/-	150V. A.C.*	35/-
300V. A.C.*	35/-	300V. A.C.*	35/-
500mA A.C.*	35/-	500mA A.C.*	35/-
1 amp. A.C.*	35/-	1 amp. A.C.*	35/-
5 amp. A.C.*	35/-	5 amp. A.C.*	35/-
10 amp. A.C.*	35/-	10 amp. A.C.*	35/-
20 amp. A.C.*	35/-	20 amp. A.C.*	35/-
30 amp. A.C.*	35/-	30 amp. A.C.*	35/-
50 amp. A.C.*	35/-	50 amp. A.C.*	35/-
VU meter	62/-	VU meter	62/-

EDGWISSE METERS

Type PE.70. 8 1/8in. x 1 1/8in. x 2 1/2in. deep.	80/-	500μA	52/6
50-0-50μA	47/6	1mA	49/6
50-0-50μA	45/-	50V. A.C.*	35/-
100μA	45/-	150V. A.C.*	35/-
100-0-100μA	45/-	300V. A.C.*	35/-
500μA	42/-	500mA A.C.*	35/-
1mA	42/-	1 amp. A.C.*	35/-
5mA	42/-	5 amp. A.C.*	35/-
10-0-10mA	35/-	10 amp. A.C.*	35/-
10mA	35/-	20 amp. A.C.*	35/-
50mA	35/-	30 amp. A.C.*	35/-
100mA	35/-	50 amp. A.C.*	35/-
		VU meter	67/6

POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush gear. Continuous running. Wide range available ex-stock. Single hole fixing. 3/16in. dia. shafts. Bulk quantities available.

25 WATT. 10/25/50/100/250/500/1000/1500/2500 or 5000 ohms. 14/6. P. & P. 1/6.
50 WATT. 10/25/50/100/250/500/1000/2500 or 5000 ohms. 21/- P. & P. 1/6.
100 WATT. 1/5/10/25/50/100/200/500/1000 or 2500 ohms. 27/6 P. & P. 1/6.


FTC-401 TRANSISTOR TESTER

Full capabilities for measuring A, B and ICO. NPN or PNP. Equally adaptable for checking diodes. Supplied complete with instructions, at battery and leads. £8.18.6 P. & P. 3/-.



MARCONI TF142E DISTORTION FACTOR METERS. Excellent condition. Fully tested. £20. Carr. 15/-.

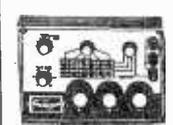TRANSISTORISED L.C.R. A.C. MEASURING BRIDGE



A new portable bridge offering excellent range and accuracy at low cost. Ranges: R. 1Ω-111 meg Ω. C. Ranges ± 1% L.T. 1μH-111 HENRYS 6 Ranges -2% C. 10pF-1110mF. 4

Ranges ± 0%. TURNS RATIO 1:1/1000-1:11000. 6 Ranges ± 1%. 10V. Voltage at 1,000 cps. Operated from 9 volts. 100μA. Meter indicator. Attractive 2 tone metal case. Size 7 1/2 x 5 x 2in. £20. P. & P. 5/-.

COSSOR 1049 DOUBLE BEAM OSCILLOSCOPES

D.C. coupled. Band width 1Kc/s. Perfect order. £25. Carr. 30/-.

TE-20 RF SIGNAL GENERATOR

Accurate wide range signal generator covering 120 Kc/s-290 Mc/s on 6 bands. Directly calibrated variable R.F. attenuator. Operation 200/240V a.c. Brand new with instructions. P. & P. £15.0.0. P. & P. 7/6. S.A.E. for details.

LELAND MODEL 27 BEAT FREQUENCY OSCILLATORS

Frequency 0-20 Kc/s. on 2 ranges. Output 500 Ω or 5k Ω. Operation 200/250V. A.C. Supplied in perfect order. £12.10.0 Carr. 10/-.

TE22 SINE SQUARE WAVE AUDIO GENERATORS

Sine: 20c/s to 200 Kc/s on 4 bands. Square: 20c/s to 30 Kc/s. Output impedance 500 ohms, 200/250V. A.C. Supplied brand new and guaranteed with instruction manual and leads. £18.10.0. Carr. 7/6.

LAFAYETTE TE-46 RESISTANCE CAPACITY ANALYSER

2 pF-2000 mF 2 ohms 200 meg-ohms. Also checks impedance, turns ratio, insulation. 200/250V. A.C. Brand New £17.10.0 Carr. 7/6.

270° 500 MICROAMP METER

Incorporated in Radio Altmeter Indicator 1D-14APN. Ideal for rev. counter etc. 15/6. P. & P. 3/-.

ADVANCE TEST EQUIPMENT

Brand new and boxed in original sealed cartons
TB5. AUDIO SIGNAL GENERATOR. 15 c/s to 50 Kc/s. Sine wave. Output 600 ohms or 5 ohms £30.0.0.
VM79. UHF MILLIVOLT METER. 100 Kc/s up to 1,000 Mc/s. A.C. 10mV to 3V. D.C. 10 mV to 3V. Current 0.01 uA to 0.3 mA. Resistance 1 ohm to 10 megohm. £25.0.0.
TT15. TRANSISTOR TESTER. Full range of facilities for testing PNP or NPN transistors in or out of circuit. £37.10.0. Carriage 10/- per item.

MARCONI TF195M BEAT FREQUENCY OSCILLATORS

0-40 Kc/s. £20. Carr. 30/-.

G. W. SMITH & CO (RADIO) LTD.
Also see next two pages

SEMI-CONDUCTORS/VALVES

BRAND NEW & FULLY GUARANTEED

TRANSISTORS

IN914	1/8	AC176	5/8	BSY95A	2/8	OA2	6/6	30C15	15/-	EY51	8/-
IN4001	2/8	AC187	12/8	BY100	3/8	OB2	6/6	30C17	18/-	EY86	8/-
IN4002	2/8	AC188	7/8	BY124	3/-	OA4	6/-	30C18	15/-	EY87	8/8
IN4003	2/8	AC177	5/8	BY126	4/-	IL4	2/6	30F5	17/-	EZ40	7/8
IN4004	3/8	AC185	7/8	BY127	4/8	IR5	7/-	30FL1	15/-	EZ41	9/-
IN4005	3/8	AC189	5/8	BY210	7/8	IK5	6/-	30FL2	18/-	EZ80	5/8
IN4006	3/8	AC191	5/8	BY211	6/8	IT4	4/8	30FL4	16/8	EZ81	5/8
IN4007	4/8	AC192	5/8	BY212	8/-	IU4	6/8	30L15	17/-	GZ32	9/8
IN4148	1/8	ACY22	4/8	BY213	5/8	IU5	9/8	30L17	17/-	GZ34	11/-
IN6054	4/8	ACY28	4/8	MJ480	19/8	2D21	6/8	30P12	16/-	KT66	27/8
2G301	4/8	ACY40	4/8	MJ481	25/-	3Q4	4/8	30P19	15/-	KT88	33/8
2G302	4/8	AD140	8/8	MFP102	8/8	3S4	7/8	30P1L	15/8	MU14	8/-
2G303	4/8	AD149	11/8	MFP103	7/8	3V6	6/-	30P1L3	18/-	PCB80	9/-
2G306	7/8	AD161	7/8	MFP104	7/8	5B4	11/-	30PL14	17/-	PC86	11/8
2G308	6/8	AD162	7/8	MFP105	7/8	5U4	6/-	35L6	9/8	PC88	13/-
2G309	6/8	AF114	5/8	NKT213	5/8	5V4	8/-	35W4	9/8	PC97	8/8
2G371	3/8	AF115	6/8	NKT214	4/8	5Y3	6/-	35Z4	5/8	PC900	9/8
2G374	4/8	AF116	5/8	NKT216	7/8	5Z4G	7/8	35Z5	7/8	PC84	7/8
2G381	4/8	AF117	5/8	NKT217	7/8	6/30L2	15/-	50B5	7/8	PC85	8/8
2G696	4/8	AF118	5/8	NKT222	8/8	6A7	4/8	50C5	7/8	PC86	12/8
2N697	4/8	AF119	4/8	NKT241	5/8	6AG7	7/8	80	9/8	PC89	10/8
2N698	5/8	AF124	4/8	NKT261	4/8	6AK5	6/-	85A2	7/8	PC189	11/-
2N706	2/8	AF126	4/8	NKT271	4/8	6AK6	11/8	802	9/8	PC80	6/8
2N706A	2/8	AF127	4/8	NKT272	4/8	6AL5	3/8	1625	6/8	PC82	6/8
2N708	3/8	AF139	6/8	NKT274	4/8	6AM6	4/8	5783	13/-	PCF84	9/8
2N714	3/8	AF178	11/8	NKT275	4/8	6AQ5	6/8	6146	30/-	PCF86	11/-
2N916	3/8	AF180	8/8	NKT282	8/8	6B6	11/8	6149	10/8	PCF80	10/8
2N918	6/8	AF181	8/8	NKT281	5/8	6AT6	5/8	CY31	7/8	PCF80	10/8
2N929	4/8	AF186	9/8	NKT403	15/-	6AU6	5/8	DAF91	5/8	PCF801	10/8
2N930	5/8	AF239	8/8	NKT404	15/-	6AV6	6/8	DAF96	7/8	PCF802	10/8
2N1131	5/8	ASV26	5/8	NKT405	12/8	6BA6	4/8	DF91	4/8	PCF805	15/-
2N1132	6/8	ASV77	7/8	NKT406	12/8	6BE6	5/8	DF96	7/8	PCF806	15/8
2N1302	3/8	ASV78	7/8	NKT407	15/-	6BES	6/8	DF97	7/8	PCF806	15/8
2N1303	3/8	ASV77	8/8	NKT408	15/-	6B6	8/8	DK92	9/8	PC82	7/8
2N1304	4/8	ASU10	30/8	NKT775	5/8	6B7A	7/8	DK96	8/8	PCL83	13/8
2N1305	4/8	BAV31	1/8	NKT10439	7/8	6BR7	17/-	DL92	7/8	PCL84	8/8
2N1306	5/8	BC107	3/8	OA5	2/8	6BR8	13/8	DL94	8/8	PCL85	9/8
2N1307	5/8	BC109	3/8	OA47	1/8	6BW6	18/-	DL96	7/8	PCL86	9/8
2N1308	5/8	BC113	5/8	OA47	1/8	6BW7	13/8	DM70	6/8	PCF80	11/8
2N1613	5/8	BC116	12/8	OA70	1/8	6C4	6/8	DY87	7/8	PL1	9/8
2N1711	5/8	BC125	11/8	OA79	1/8	6CD6	23/-	E88CC	12/8	PL82	9/8
2N1889	6/8	BC126	11/8	OA81	1/8	6CL6	10/8	E180F	15/8	PL83	8/8
2N1893	6/8	BC147	3/8	OA85	1/8	6CW4	12/8	EABC80	6/8	PL84	7/8
2N2147	14/8	BC148	3/8	OA90	1/8	6EAF	12/8	EAF42	10/8	PL500	12/8
2N2160	11/8	BC149	3/8	OA91	1/8	6F6G	6/8	EB01	3/8	PL404	18/-
2N2193	9/8	BC167	3/8	OA95	1/8	6F13	7/8	EBC41	10/8	PY32	11/8
2N2217	5/8	BC172	3/8	OA200	2/8	6F14	12/8	EBC81	6/8	PY33	12/8
2N2218	5/8	BC177	7/8	OA202	1/8	6F15	11/8	EBF80	8/8	PY80	6/8
2N2219	5/8	BC186	7/8	OA210	3/8	6F18	8/8	EBF83	8/8	PY81	6/8
2N2268	5/8	BC192L	4/8	OC20	15/8	6F23	18/8	EBF89	8/8	PY82	6/8
2N2369	3/8	BC184L	4/8	OC20	15/8	6G6	3/8	EJL21	15/8	PY83	7/8
2N2369A	4/8	BC122L	4/8	OC22	10/8	6J4	4/8	EC86	12/8	PY88	8/8
2N2444	6/8	BCY30	5/8	OC23	10/8	6J5	4/8	EC88	12/8	PY800	10/8
2N2613	7/8	BCY31	5/8	OC24	11/8	6J5GT	6/8	EOC40	11/8	PY801	10/8
2N2646	11/8	BCY32	7/8	OC25	10/8	6J6	3/8	EOC84	6/8	U25	15/8
2N2920	2/8	BCY33	4/8	OC26	6/8	6J7	8/8	EOC85	5/8	U26	15/8
2N2923	2/8	BCY34	4/8	OC27	10/8	6K8G	6/8	EOC88	8/8	U50	6/8
2N2924	3/8	BCY38	4/8	OC29	12/8	6L6GT	6/8	EU92	6/8	U92	6/8
2N2925	3/8	BCY42	3/8	OC35	8/8	6LD20	6/8	ECF82	7/8	UI91	14/8
2N2926	2/8	BCY43	3/8	OC36	12/8	6Q2	7/8	ECF86	12/8	U281	8/8
2N2926A	2/8	BCY71	8/8	OC41	4/8	68A7	7/8	ECH21	11/8	U282	8/8
2N2926B	2/8	BCY72	3/8	OC42	4/8	6807	6/8	ECH35	12/8	U301	11/8
2N3053	4/8	BC211	7/8	OC45	2/8	6837	7/8	ECH42	13/8	U302	20/8
2N3054	11/8	BD121	13/8	OC45	2/8	6847	6/8	ECH81	8/8	UABC80	6/8
2N3055	15/8	BD123	16/8	OC46	3/8	68L7	6/8	ECH83	8/8	UAF42	10/8
2N3391A	6/8	BD124	12/8	OC70	3/8	68N7	5/8	ECL80	9/8	UBC41	9/8
2N3416	7/8	BF115	5/8	OC71	3/8	68Q7	8/8	ECL82	6/8	UBC81	9/8
2N3470	17/8	BF117	9/8	OC72	2/8	6U4	12/8	ECL83	12/8	UBF80	7/8
2N3702	3/8	BF147	6/8	OC73	5/8	6V6G	5/8	ECL86	8/8	UBF89	7/8
2N3703	4/8	BF173	6/8	OC74	6/8	6X4	5/8	UCF7A	8/8	UCF7B	9/8
2N3704	4/8	BF180	7/8	OC75	4/8	6X4	5/8	EY85	8/8	UCY85	8/8
2N3705	4/8	BF181	6/8	OC76	4/8	6X6G	5/8	EF40	10/8	UCF80	10/8
2N3706	4/8	BF182	6/8	OC77	6/8	6X6GT	5/8	EF41	12/8	UCH21	11/8
2N3707	4/8	BF184	6/8	OC78	7/8	10C2	10/8	EF42	14/8	UCH42	13/8
2N3708	3/8	BF185	6/8	OC79	5/8	10P1	18/8	EF80	5/8	UCH81	8/8
2N3709	3/8	BF194	4/8	OC81D	5/8	10P1	18/8	EF86	4/8	UCL82	7/8
2N3710	4/8	BF195	5/8	OC83	5/8	10P14	20/8	EF88	4/8	UCL83	12/8
2N3711	4/8	BF200	10/8	OC84	5/8	12A16	5/8	EF89	5/8	UF41	10/8
2N3819	7/8	BF224	6/8	OC139	6/8	12A17	4/8	EP91	4/8	UF80	7/8
2N3903	7/8	BF225	6/8	OC140	6/8	12A17	5/8	EP92	7/8	UF85	7/8
2N3904	7/8	BF146	9/8	OC149	4/8	12A17	5/8	EP183	6/8	UF89	7/8
2N3905	7/8	BF152	8/8	OC170	6/8	12A16	6/8	EP184	7/8	UL41	12/8
2N3906	7/8	BF153	4/8	OC171	6/8	12B16	6/8	EL84	10/8	UL84	6/8
2N4058	5/8	BFX29	7/8	OC200	6/8	12B16	6/8	EL80	8/8	UY41	8/8
2N4059	5/8	BFX30	9/8	OC201	9/8	12BH7	6/8	EL33	17/8	UY85	6/8
2N4061	4/8	BFX44	7/8	OC292	12/8	19AQ5	6/8	EL41	11/8	VR105/30	5/8
2N4062	4/8	BFX45	7/8	OC293	8/8	20D1	9/8	EL42	11/8	VR105/30	5/8
2N4286	3/8	BFX86	6/8	OC296	8/8	20P2	15/8	EL81	10/8	VR105/30	5/8
2N4287	3/8	BFX87	6/8	OC295	8/8	20P1	10/8	EL84	5/8	VR105/30	5/8
2N4288	3/8	BFX88	5/8	OC207	12/8	20P1	10/8	EL85	3/8	VR105/30	5/8
2N4289	3/8	BFY18	6/8	OC71	8/8	20P3	12/8	EL91	5/8	VR105/30	5/8
2N4290	3/8	BFY20	12/8	ORP12	10/8	20P4	20/8	EL95	7/8	VR105/30	5/8
2N4291	3/8	BFY21	4/8	ORP60	10/8	20P5	20/8	EM80	8/8	VR105/30	5/8
2N4292	2/8	BFY81	4/8	P846A	4/8	25L6	7/8	EM81	8/8	VR105/30	5/8
2N5354	5/8	BFY52	4/8	PL4001	2/8	25Z4	6/8	EM84	7/8	VR105/30	5/8
2N5355	5/8	BFY90	13/8	PL4002	3/8	25Z5	6/8	EM85	11/8	VR105/30	5/8
28102	6/8	B8X19	3/8	PL4003	3/8	25Z6	11/8	EM87	11/8	VR105/30	5/8
28103	6/8	B8X20	3/8	PL4004	3/8						
28194	6/8	B8X21	7/8	PL4005	3/8						
40250	10/8	B8Y78	3/8	PL4006	4/8						
40381	12/8	B8Y28	3/8	P1007	4/8						
40382	12/8	B8Y27	3/8	T1843	4/8						
AC107	6/8	B8Y28	3/8	T1844	2/8						
AC126	4/8	B8Y38	4/8	T1845	3/8						
AC127	5/8	B8Y39	4/8	T1846	3/8						
AC128	5/8	B8Y39	4/8								
AC154	4/8	B8Y36	15/8								

THYRISTORS

PIV	50	100	200	300	350	400
1A	5/8	8/8	7/8	8/8	—	9/8
3A	6/8	7/8	8/8	—	—	9/8
5A	—	11/8	13/8	—	—	15/8
7A	—	11/8	13/8	—	—	19/8
100A	—	—	—	50/8	55/8	—

VALVES

OA2	6/6	30C15	15/-	EY51	8/-
OB2	6/6	30C17	18/-	EY86	8/-
OA4	6/-	30C18	15/-	EY87	8/8
IL4	2/6	30F5	17/-	EZ40	7/8
IR5	7/-	30FL1	15/-	EZ41	9/-
IK5	6/-	30FL2	18/-	EZ80	5/8
IT4	4/8	30FL4	16/8	EZ81	5/8
IU4	6/8	30L15	17		

RUSSIAN C1-16 DOUBLE BEAM OSCILLOSCOPES

5 MHz Pass Band. Separate Y1, Y2 amplifiers. Calibrated triggered sweep from -2 sec to 100 mill sec/cm. Supplied complete with all accessories and instructions £87. Carr. paid.



MARCONI T/44/TF956

AF Absorption Wattmeter
1 μ/watt to 6 watts.
£20. Carr. 10/-.

TEIII. DECADE RESISTANCE ATTENUATOR



Variable range 0-11dB. Connections. Unbalanced T and Bridge T. Impedance 600 Ω range (0.1dB x 10) + (1dB x 10) + 10 + 20 + 30 + 40dB. Frequency: d.c. to 200KHz (-3dB). Accuracy: 0.05dB. + Indication ±B x 0.01. Maximum input less than 4W (50V). Built in 600 Ω load resistance with internal/external switch. Brand new £27.10.0. P. & P. 5/-.

BELCO AF-5A SOLID STATE SINE SQUARE WAVE C.R. OSCILLATOR

Sine 18-200,000 Hz; Square 18-50,000 Hz Output max. + 10 dB (10 K ohms) Operation internal batteries Attractive 2-ton case 7 1/2" x 5" x 2". Price £17.10.0. Carr. 3/6.



TE-18A Transistorised Signal Generator

5 ranges 400Hz-30MHz. An inexpensive instrument for the handyman. Operates on 9v battery. Wide easy to read scale. 800kHz modulation. 5 1/2" x 5 1/2" x 3 1/2". Complete with instructions and leads. £7.18.8. P. & P. 4/-.



BELCO DA-20 SOLID STATE DECADE AUDIO OSCILLATOR

New high quality portable instrument. Sine 1 Hz to 100 KHz. Square 20 Hz to 20 KHz. Output max + 10 dB (10 K ohms). Operation 220/240v. A.C. Size 215mm x 150mm x 120mm. Price £27.10.0. Carr. 5/-.



TE-40 HIGH SENSITIVITY A.C. VOLT METER

10 meg. input 10 ranges: 01/003/1/3/1/3/10/30/100/300V. R.M.S. 4eps.-1.2 Mc/s. Decibels -40 to +50dB. Supplied brand new complete with leads and instructions. Operation 230V. A.C. £17.10.0 Carr. 5/-.



TE-65 VALVE VOLT METER

High quality instrument with 28 ranges. D.C. volts 1.5-1,500V. A.C. volts 1.5-1,500V. Resistance up to 1,000 megohms. 200/240v. A.C. operation. Complete with probe and instructions. £7.10.0. P. & P. 6/- Additional probes available: R.F. £2/6. H.V. 50/-



AUTO TRANSFORMERS

0/115/230V. Step up or step down. Fully shrouded.
150 W. £2. 2.6. P. & P. 3/6.
300 W. £3. 5.0. P. & P. 4/6.
500 W. £4.10.0. P. & P. 6/6.
1,000 W. £8.10.0. P. & P. 7/6.
1,500 W. £8.18.8. P. & P. 8/6.
7,500 W. £15.10.0. P. & P. 20/-.

SOLID STATE VARIABLE A.C. VOLTAGE REGULATORS

Compact and panel mounting. Ideal for control of lamps, drills, electrical appliances etc. Input 230/240v. A.C. Output continuously variable from 20V-230V. Model MR 2305 5 amp 68 x 46 x 48mm £8.7.6 Model MR 2310 10 amp 90 x 68 x 60mm £11.19.8 Postage 2/6



MULTIMETERS for EVERY purpose!

TECH FT-34. 1,000 O.P.V. 0/10/50/250/500/1,000V. A.C. and D.C. 0/1/100/500mA. D.C. 0/100K 39/6. P. & P. 2/6.

HONOR TE.10A. 20k Ω/Volt 5/25/50/250/500/2,500 v. D.C. 10/50/100/500/1,000 v. A.C. 0/50uA/2.5mA/250mA D.C. 0/6K/6 meg. ohm. -20 to +22 dB. 10-100 mfd. 0.100-0.1 mfd. 69/6. P. & P. 3/-.

MODEL TE-300. 30,000 O.P.V. Mirror scale, overload protection 0/8/3/15/60/300/1,200V. D.C. 0/6/30/120/600/1,200V. A.C. 0/80uA/6mA/60mA/300mA/600mA. 0/8K/80K/800K/8 meg. ohm. -20 to +63 db. £5.19.8. P. & P. 3/-.

MODEL TE-70. 30,000 O.P.V. 0/3/15/60/300/600/1,200V. D.C. 0/6/30/120/600/1,200V. A.C. 0/30uA/3/30/300mA. 0/16K/160K/1.6M/16 MegΩ. £5.10.0. P. & P. 3/-.

MODEL TE-90 50,000 O.P.V. Mirror scale, overload protection. 0/3/12/60/300/600/1,200 v. D.C. 0/6/30/120/300/1,200 v. D.C. 0/6/60/600/600mA. D.C. 16K/160K/1.6/16 MEGΩ. -20 to +63 db. £7.10.0. P. & P. 3/-.

TMK MODEL TW-50K 48 ranges, mirror scale. 50K/Volt. D.C. 5K/Volt A.C. D.C. Volts: 125, 25, 1.25, 2.5, 5, 10, 25, 50, 125, 250, 500, 1000V. A.C. Volts: 1.5, 3, 5, 10, 25, 50, 125, 250, 500, 1000V. D.C. Current: 25, 50mA, 2.5, 5, 25, 50, 250, 500mA, 5, 10 amp. Resistance: 10K, 100K, 1 MEG, 10 MEGΩ. Decibels: -20 to +81.5 dB. £8.17.6. P. & P. 3/6.

TE-900 20,000 Ω/VOLT GIANT MULTIMETER. Mirror scale and overload protection. 6in. full view meter. 2 colour scale. 0/2.5/10/250/1,000/5,000 v. A.C. 0/25/12.5/10/50/250/1,000/5,000 v. D.C. 0/50uA/110/100/500mA/10 amp. D.C. 0/2K/200K/20 MEG. OHM. £15.0.0. P. & P. 5/-.

MODEL AS-100D. 100K Ω/Volt. 5in. mirror scale. Built-in meter protection 0/3/12/60/120/300/600/1,200 v. D.C. 0/5/30/120/300/600 v. A.C. 0/10uA/6/60/300mA/12 Amp. 0/2K/200K/2M/200MΩ. -20 to +17 db. £12.10.0. P. & P. 3/6.

TMK LAB TESTER. 100,000 O.P.V. 6 1/2in. Scale Buzzer Short Circuit Check. Sensitivity: 100,000 O.P.V. D.C. 5K Ω/Volt A.C. D.C. Volts: 5, 10, 50, 250, 1,000 V. A.C. Volts: 3, 10, 50, 50, 250, 500, 1,000V. D.C. Current: 10, 100mA, 2.5, 10 amp. Resistance: 1K, 10K, 100K, 10MEGΩ, 100 MEGΩ. Decibels: -10 to 49 db. Plastic Case with Carrying Handle. Size 7 1/2in. x 6 1/2in. x 3 1/2in. £18.18.0. P. & P. 6/-.

LAFAYETTE HA-600 SOLID STATE RECEIVER
General coverage 150-400kc/s, 550 kc/s - 30mc/s. FET front end, 3 mech. filters, product detector, variable B.F.O., noise limiter, 8 Meter, Bandspread, RF Gain. 15" x 8 1/2" x 8 1/2". 18 lbs, 220/240v. A.C. or 12v. D.C. Brand new with instructions. £45. Carr. 10/-.

RCA COMMUNICATIONS AR88D RECEIVER
Brand new. 6 bands 630kc/s-32mc/s. Fully tested and checked. 110-250V. A.C. £85. Carr. £2.

"YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS
Excellent quality. Low price. Immediate delivery

MODEL S-280	General Purpose Bench Mounting	MODEL S-280 B	Panel Mounting
1 Amp	£5.10.0	1 Amp	£5.10.0
2.5 Amp	£6.15.0	2.5 Amp	£6.12.6
5 Amp	£9.15.0	Please add postage	
8 Amp	£14.10.0	ALL MODELS	
10 Amp	£18.10.0	INPUT 230 VOLTS,	
12 Amp	£21.0.0	60/80 CYCLES,	
20 Amp	£37.0.0	OUTPUT VARIABLE	
		0-250 VOLTS.	

Special discounts for quantity

UNE-30 RECEIVER
4 Bands covering 550kc/s-30mc/s. B.F.O. Built-in Speaker 220/240v. A.C. Brand new with instructions. £13.13.0. Carr. 7/6.

WS62 TRANCEIVERS
Large quantity available for EXPORT! Excellent condition. Enquiries invited.

UR-1A SOLID STATE COMMUNICATION RECEIVER
4 Bands covering 550kc/s-30mc/s. FET, 8 Meter, Variable BFO for 8SB, Built-in Speaker, Telescopic Aerial, Bandspread, Sensitivity Control. 220/240v. A.C. or 12v. D.C. 12 1/2" x 4 1/2" x 7". Brand new with instructions. £24. Carr. 7/6.

FULL RANGE OF CODAR AMATEUR EQUIPMENT IN STOCK

LAFAYETTE LA-324 STEREO AMPLIFIER
Solid State. 12.5w rms per channel. 20-20,000 Hz ±1db. Inputs Mag/Cer/Tuner/Aux. Output 4-16. Headphone Socket, Tape Output. Black and Brushed Aluminium Front Panel. 10 1/2" x 3 1/2" x 8 1/2". £24. Carr. 7/6.

FULL RANGE OF PARTRIDGE JOYSTICK RECEIVERS IN STOCK

TRIO 9R59DE COMMUNICATION RECEIVER

4 bands 500kc/s-30mc/s. 8 Meter. Variable B.F.O. Bandspread, 7" x 15" x 10". 115/250V. A.C. Brand new with instructions. £42. Carr. Paid. Full Range of other Trio Products in stock.	£55.0.0
JR.5008E Amateur Receiver	£77.10.0
JR.310 Amateur Receiver	£180.0.0
TS 610 Amateur Transceiver	£47.6
SP5D Matching Speaker	£25.19.6
HS4 Headphones	

VOLTAGE STABILISER TRANSFORMER S
180-280v. Input. Output 230v. Available 150w or 225w. £12.10.0. Carr. 5/-.

EDDYSTONE VHF RECEIVERS Model 770R.
19-185 Mc/s. Excellent condition. £150.

TRANSISTORISED TWO-WAY TELEPHONE INTERCOM
Operative over amazingly long distances. Separate call and press to talk buttons, 2-wire connection. 1000's of applications. Beautifully finished in ebony. Supplied complete with batteries and wall brackets. £6.19.8. P. & P. 3/6.

G.W.SMITH & CO. (RADIO) LTD

3, LISLE STREET, LONDON, W.C.2 Tel: 01-437 8204
34, LISLE STREET, LONDON, W.C.2 Tel: 01-437 9155
311, EDGWARE ROAD, LONDON, W.2 Tel: 01-262 0387
OPEN 9-6 MONDAY TO SATURDAY (EDGWARE ROAD 1/2 DAY THURSDAY)

All Mail Orders to -
147, Church Street, London, W.2
Tel: 01-262 6582
(Trade supplied)

NO



I'D RATHER HAVE A MINITEST™

The SEI MINITEST has made a remarkable impact in the pocket-sized multi-range meter market, by making itself a firm favourite with discerning people in the industry. Let's look into the reasons why.

First, the appearance. Diminutive, neat, wipe-clean cyclac case with shock and magnetic field proof steel liner. Controls are simple and easy to use.

Second, the range. The Minitest measures a.c. and d.c. voltages d.c. current and resistance over 20 ranges to a sensitivity of 20,000 and 2,000 ohms per volt d.c. and a.c. respectively. Third, high voltage probes. These extend the range to 25 or 30kV d.c. Little wonder the Minitest is preferred!



SALFORD ELECTRICAL INSTRUMENTS LTD
Peel Works, Barton Lane, Eccles,
Manchester M30 0HL
Telephone 061-789 5081 Telex 66711
A Member Company of GEC Electrical Components Ltd.


SEI S&C

FAL

AMPLIFIERS OF QUALITY AND RELIABILITY
at the right price

'PHASE 12'

An extremely attractive all silicon stereo amplifier Ideal for unit audio use. Facilities include MAGNETIC and CERAMIC P.U. RADIO, TAPE etc. Output 6 watts per channel Freq. Response 40-40,000 c.p.s.—3 dB. Hum level—74 dB. Controls include Input Selector, Volume, Balance, Bass, Treble and Stereo/Mono Switch. Black and silver facia panel with satin silver control knobs. Slimline finish enhanced by good quality Teak cabinet housing

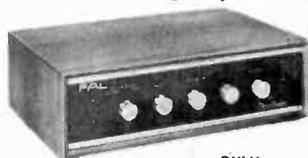

ONLY **24 Gns.**

Recommended Retail Price



'PHASE 50' P.A. AMPLIFIER

A solid state A.C. mains unit for Vocal and Instrumental Groups and General Public Address use.

29 GNS.

- ★ 50 watts output (Peak)
- ★ High sensitivity
- ★ 3-30 ohms matching
- ★ 3 separately controlled inputs
- ★ Freq. Response 22 c.p.s.—30 Kcs

Recommended Retail Price

For heavy demands on power, 'Phase 100' will provide 100 watts at music rating. 4 Inputs. Master volume etc.

59 GNS.

For leaflets on the above and other models in the FAL range please send SAE to:—

FUTURISTIC AIDS LTD, 104 Henconner Lane, Leeds 13

ERSIN



for fast, easy, reliable soldering

Contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux required.

SAVBIT ALLOY ALSO REDUCES COPPER BIT WEAR.

Economically packed for general electrical and electronic soldering. 75ft. 18 gauge on plastic reel. Recommended retail price 15/-



THIN GAUGE SOLDER, ESSENTIAL FOR

soldering small components and thin wires. High tin content, low melting point, 60/40 alloy, 170ft. 22 gauge on plastic reel. Recommended retail price 15/-



A RANGE OF SOLDERS IN HANDY DISPENSERS.

REF. ALLOY SWG

4A	60/40	18	3/.*
Size 5 (ultra-thin)	Savbit	18	3/.*
15	60/40	22	4/.*

*Recommended Price



INVALUABLE FOR STRIPPING FLEX, THE NEW AUTOMATIC OPENING BIB WIRE STRIPPER AND CUTTER,

adjustable for all standard diameters. Plastic covered handles can also be used as wire cutter. Recommended retail price 8/6



From Electrical and Hardware shops. If unobtainable, write to: Multicore Solders Ltd., Hemel Hempstead, Herts.

TRANSISTOR RADIOS TO BUILD YOURSELF

Backed by after sales service

NEW! roamer eight mk 1 WITH VARIABLE TONE CONTROL

7 Tunable Wavebands: Medium Wave 1, Medium Wave 2, Long Wave, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for Medium and Long Waves. Five section 22in. chrome plated Telescopic aerial for Short Waves can be angled and rotated for maximum performance. Push pull output using 600 mW transistors. Socket for car aerial. Tape record socket. Selectivity switch. Switched earpiece socket complete with earpiece for private listening. Eight transistors plus 3 diodes. Famous make 7in. x 4in. Speaker. Air spaced ganged tuning condenser. On/Off switch volume control. Wave change switch and tuning control. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams make the Roamer Eight a pleasure to build. Total Building Costs **£6.19.6**


Parts Price List and Easy Build Plans 5/- (FREE with parts).

P. & P. 7/6



roamer seven mk IV

SEVEN FULLY TUNABLE WAVEBANDS—MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Extra Medium waveband provides easier tuning of Radio Luxembourg, etc. Built in ferrite rod aerial for Medium and Long Waves. Retractable 4 section 24in. chrome plated telescopic aerial for peak Short Wave listening. Socket for Car Aerial. Powerful push-pull output. Seven transistors and two diodes including Micro-Alloy R.F. Transistors. Famous make 7 x 4in. P.M. speaker. Air spaced ganged tuning condenser. Volume/on/off control, wave change switches and tuning control. Attractive case with carrying handle. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams make the Roamer 7 a pleasure to build. Parts price list and easy build plans 3/- (FREE with parts). Personal Earpiece with switched socket for private listening, 5/- extra.

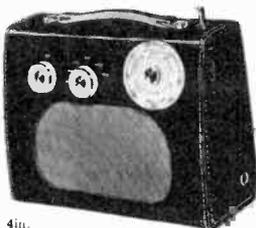

Total building costs


£5.19.6

P. & P. 7/6

pocket five

MEDIUM WAVE, LONG WAVE AND TRAWLER BAND PORTABLE WITH SPEAKER

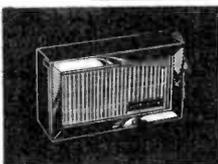Attractive black and gold case. Size 5½ x 1½ x 3½in. Tunable over both Medium and Long Waves with extended M.W. band for easier tuning of Luxembourg, etc. 7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker. Easy build plans and parts price list 1/6 (FREE with parts).



Total building costs

44/6


P. & P. 3/6

IMPROVED MODEL!

roamer six

SIX WAVEBAND PORTABLE WITH 3in. SPEAKER

Attractive black case with red grille and cream knobs and dial polished brass inserts. Size 9 x 5½ x 2½in. approx. Tunable on Medium and Long Waves, two Short Waves, Trawler Band plus an extra M.W. ferrite rod aerial and latest telescopic aerial for Short Waves. Improved circuit. 8 stages—6 transistors and 2 diodes including Micro-Alloy R.F. Transistors, etc. (Carrying strap 2/6 extra). Easy build plans and parts price list 2/- (FREE with parts).

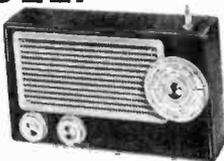

Total building costs

79/6

P. & P. 4/6

NEW!

trans eight

SIX WAVEBAND PORTABLE WITH 3in. SPEAKER

Attractive case in black with red grille and cream knobs and dial with polished brass inserts. Size 9 x 5½ x 2½in. approx. Tunable on Medium and Long Waves, three Short Waves and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. Eight improved type transistors plus 3 diodes. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 5/- (FREE with parts). Earpiece with switched socket for private listening 5/- extra.



Total building costs **89/6**

P. & P. 5/6

transona five

MEDIUM WAVE, LONG WAVE AND TRAWLER BAND PORTABLE WITH SPEAKER

Attractive case with red speaker grille. Size 6½ x 4½ x 1½in. 7 stage—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser, volume control, fine tone moving coil speaker. Easy build plans and parts price list 1/6 (FREE with parts).



Total building costs

47/6

P. & P. 3/6

RADIO EXCHANGE CO

61 HIGH STREET, BEDFORD. Tel. 0234 52367

I enclose £..... please send items marked

- | | | | |
|---------------|--------------------------|--------------|--------------------------|
| ROAMER EIGHT | <input type="checkbox"/> | ROAMER SEVEN | <input type="checkbox"/> |
| TRANSONA FIVE | <input type="checkbox"/> | TRANS EIGHT | <input type="checkbox"/> |
| POCKET FIVE | <input type="checkbox"/> | ROAMER SIX | <input type="checkbox"/> |

Parts price list and plans for

Name


Address

PW.23

★ Callers side entrance Stylo Shoe Shop

★ Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

YOURS FOR 7 DAYS FREE!

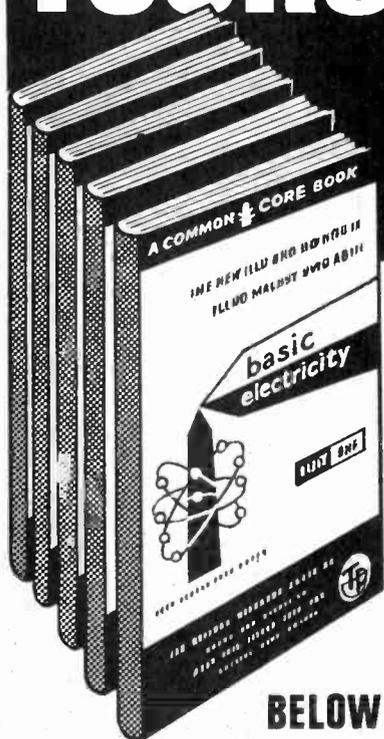

The 'PICTURE BOOK' way of learning **BASIC ELECTRICITY** (5 VOLUMES) **BASIC ELECTRONICS** (6 VOLUMES)

You'll find it easy to learn with this outstandingly successful PICTORIAL METHOD—the essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate, cartoon-type drawing. The books are based on the latest research into simplified learning techniques. This has proved that the PICTORIAL APPROACH to learning is the quickest and soundest way of gaining mastery over these subjects, TO TRY IT, IS TO PROVE IT

BELOW ARE EXTRACTS FROM THE MANY LETTERS RECEIVED

What readers say...

"TERRIFIC TECHNICAL EDUCATIONAL MANUALS"
 "As you know I have had from you both sets of Basic Electronics and Basic Electricity, these are terrific technical educational manuals, the best I have ever read." *K.F.H., Ilford.*

"IDEAL TEACHING AGENTS"
 "The books are ideal teaching agents. Thank you." *C.J.M., London, S.E.1.*

"ASTONISHED AT THE EASE OF LEARNING"
 "I am astounded at the ease of learning and understanding they provide." *B.M., London, E.5.*

"KEY TO LEARNING"
 "I cannot say enough in praise of these Manuals, I shall recommend them to anybody interested in electricity and wireless that I know. They are the key to learning." *D.F., Leeds 14.*

"ABSOLUTELY DELIGHTED"
 "I am absolutely delighted with the books and hope to learn quite a lot from them." *H.A.H., Rhyminney.*

"HELPED ME TO UNDERSTAND"
 "I am a qualified electrician. Your set of excellent books has helped me to understand matters in the field of electronics which I thought previously were above me. Indeed these books are well worth the money." *T.E.D., Abergavenny.*

"MOST PERFECT BOOKS"
 "I have decided to send you the full payment for the books you mailed to me, in my mind they are the most perfect books for any beginner to Electronics." *G.G., London, S.W. 8.*

"BEST BOOKS IN THIS COUNTRY"
 "On going through these books I have found they are the best books I have ever had in this country." *S.K.A., London, N.W.2.*

"KEY TO THE KNOWLEDGE"
 "Your books have been the 'key' to the knowledge I have needed." *J.M., Horsham.*

"UNDERSTAND THE BASIC FACTS"
 "This is the first time I have been able to understand the basic facts as all other books are too complicated." *L.W., Sheffield.*

"T.V. ENGINEER"

"So in two years I have come from a labourer on a building site to a T.V. Engineer, with the help of your books." *C.G., Sheppey.*

"SIMPLE, CLEAR AND CONCISE"

"I would like to endorse the feelings of many purchasers that they are a simple, clear and concise introduction to the study of electronics." *E.P.Y., London, S.E.9.*

"MONEY WELL SPENT"

"I consider this as money well spent. Thank you." *F.A., Burton-on-Trent.*

The series will be of exceptional value in training mechanics and technicians in Electricity and Electronics.

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT BR2 7HP

Please send me WITHOUT OBLIGATION TO PURCHASE, one of the above sets on 7 DAYS FREE TRIAL, I will either return set, carriage paid, in good condition within 7 days or send the following amounts. BASIC ELECTRICITY 75/- Cash Price or Down Payment of 20/- followed by 3 fortnightly payments of 20/- each. BASIC ELECTRONICS 90/- Cash Price or Down Payment of 20/- followed by 4 fortnightly payments of 20/- each. This offer applies to UNITED KINGDOM ONLY. Overseas customers cash with order, prices as above.

Tick Set required (Only one set allowed on free trial)

BASIC ELECTRICITY BASIC ELECTRONICS
 Prices include Postage and Packing.

Signature
 (If under 21 signature required of parent or guardian)

NAME
 BLOCK LETTERS
 FULL POSTAL ADDRESS

PW

DON'T MISS THIS OFFER! POST NOW!

MW/LW TRANSISTOR RADIO




Complete set of parts for this MW/LW Transistor Radio. Originally sold by world-famous company as a set for more than £17. Coverage 192-555m + 1070-1870m. 4 1/2" loudspeaker. Transistors 3 x AF117, OC81D + 2 OC81. Also works off car-aerial. Full instruction book 2/6, free with parts. State preference red, blue or tan and give alternative. Requires PPT battery, price 4/6 extra. All parts £6.17.6 + 4/6 post or £10.10.0 fully built + 4/6 post.

A few left of Super Six Kit (see previous issues) at £4.5.0 (+ 4/6 post).

9 volt 6 transistor superhet using 3HF AA17 in RF and IF stages powered by a two stage AF amplifier using OC81D. 2 x OC81. Output approx. 500MW.

6 PUSH-BUTTON STEREOGRAM CHASSIS

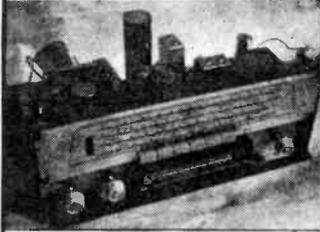

M.W.: S.W.1; S.W.2; V.H.F.; Gram: Stereo Gram Two separate channels for Stereogram with balance control. Also operates with two speakers on Radio. Chassis size: 15 x 7 x 6 1/2 in. high. Dial silver and black 15 x 3 in. 190-550M; 18-51M; 60-187M; VHF 86-100 Mc/s. Valves: ECC85, ECH81, EF89, 2x ECL86, EM84 and Rect. Price £19.19.0. carr. paid With Stereo Decoder fitted £27.10.0 extra.

STEREO AMPLIFIER type HV— 2 x 3 Watts

Fully built. On off sep. vol. and tone each channel 12 x 4 1/2 x 6 in. high. EZ80, 2 x ECL86; for 3 ohm speakers, double wound main trans: fixing flanges and base plate, suitable for crystal cart, tuner etc. £8.10.0 (8/- p. & p., 200-250V. A.C. Superior version — separate base. treble & vol. each channel with mono/stereo switch 15/- extra.



STEREO AMPLIFIER type RC— 2 x 3 Watts for 200-250V. A.C.

Fully built. 2 x UCL82, metal rect: ganged vol. and tone. cont: on-off balance. 11 x 3 1/2 x 4 in. high. Double wound mains trans. with supporting brackets. For 3-ohm speakers. £8 (8/- p. & p.)



MONO GRAM CHASSIS 3 WATT

3 Wave band long-med-short. Gram. 200-250V A.C. Ferrite aerial. Chassis 13 x 7 x 5 in. Dial 13 x 4 in. Double wound mains transformer 5 valves ECH81, EF89, EBC81, EL84, EZ80. Price £10.12.6. (7/6 p. & p.) Output trans. for 3-ohm speaker



NEW TAPE AMPLIFIER for 4 track B.S.R. Deck TD2. Mains and output Trans. 10" x 6" x 4" overall. Rect: ECC83, EL84. Mike and Gram Inputs. £7.5.0. (10/- p. & p.) For 3-ohm speaker. (For 200-250V. A.C.)

1 1/2 W MAINS GRAMOPHONE AMPLIFIERS

EZ80, ECL82, O.P. Transformer (3 ohm). Vol./On-off and Tone Control. Double wound mains transformer. 2 1/2 x 2 1/2 x 2 1/2 in. separate but wired to chassis, 4 x 2 1/2 x 4 1/2 in. over valves 67/6 including 5 in. Speaker (55/- less speaker). (Post paid.) (Two less 10%)

ECL82 with metal rect. O.P. Transformer for 3-ohm speaker. Size 8 x 5 1/2 x 4 in. overall. Bass, treble & vol./on-off on separate panel, 6 x 1 1/2 in. with fixing holes. Price 67/6 (+ 3/6 p. & p.). Not for low output cartridge. (Two less 10%).

MAINS TRANSFORMERS (200-250V AC INPUT)

Postage. Postage in brackets.
Out 250V at 50mA and 6.3V at 1 1/4. 10/- (2/8).
22V at 1A + 6.3V at 2A and 250V at 50mA 15/- (3/6).
250V at 40mA, 24V at 1A and 6.3V at 1 1/4 12/6 (2/8).
250V at 50mA, 22V at 1A and 6.3V at 1 1/4 17/6 (3/6).

USEFUL BOX 3 1/2" x 3 1/2" x 1 1/4" with fixing bracket 2/6 (Postage 2/-). 25/- per dozen post free.

NEW F.M. TUNER

Range 87 to 107 MHz Attractively finished metal container with cast front escutcheon. Case size 13 in. x 7 in. x 3 1/2 in. high. Mains transformer. Metal Rectifier and Valves ECC85, EF89, EF80, ECC82 as cathode follower. EM84 tuning indicator, 2 x AF117 and 2 diodes. A really fantastic performer. Price £16, tax paid and carr. paid or with Stereo Decoder, £24.



GLADSTONE RADIO

66 ELMS ROAD, ALDERSHOT, Hants.
(2 mins. from Station and Buses). FULL GUARANTEE. Aldershot 22240
CLOSED WEDNESDAY. S.A.E. for enquiries please.

BI-PRE-PAK LTD

DEPT. D, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX
TELEPHONE: SOUTHEND (0702) 46344

FULLY TESTED AND MARKED

AC107	3/-	OC170	4/6
AC126	2/6	OC171	4/6
AC127	3/6	OC200	3/6
AC128	2/6	OC201	7/-
AC178	5/-	2G301	2/6
ACY17	3/-	2G303	2/6
AF239	7/6	2N1302-3	4/-
AF186	10/-	2N1304-5	5/-
AF139	7/6	2N1306-7	6/-
BC184	5/-	2N1308-9	7/-
BC171 = BC107	2/6	2N3819 FET.	9/-
BC172 = BC108	2/6	2N3844A	5/-
BF194	3/-	Power	
BF274	3/-	Transistors	
BFY50	4/6	OC20	10/-
BBY25	7/6	OC23	10/-
BBY26	3/-	OC25	8/-
BBY27	3/-	OC26	5/-
BBY28	8/-	OC28	7/6
BBY29	3/-	OC35	5/-
BBY95A	3/-	OC36	7/6
OC41	2/6	AD149	10/-
OC44	2/6	AU Y 10	30/-
OC45	2/6	2N3055	15/-
OC71	2/6	28034	10/-
OC72	2/6	Diodes	
OC73	3/6	AA Y42	2/-
OC81	2/6	OA91	2/-
OC81D	2/6	OA79	1/9
OC139	2/6	OA81	1/9
OC140	3/6	IN914	1/6

FREE! Packs of your own choice up to the value of 10/- with orders over £4.

RETURN OF THE UNBEATABLE P.I. PAK. NOW GREATER VALUE THAN EVER

Full of short lead semiconductors and electronic components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP and NPN, and a host of diodes and rectifiers. Mounted on printed circuit panels. Identification chart supplied to give some information on the transistors.

PI PLEASE ASK FOR PAK P.I. ONLY 10/-
2/- P. & P. on this Pak

NEW UNMARKED UNTESTED PAKS

H10 25	Mixed volts 1 1/2 watt Zeners Top Hat type.	10/-
B80 8	Dual Trans. Matched O/P pairs NPN. Sil. in TO-5 can.	10/-
H11 30	Mat series "Alloy" PNP Transistors.	10/-
B83 200	Trans. Makers rejects. NPN/PNP. Sil. and Germ.	10/-
B84 100	Silicon Diodes DO-7 glass equiv. to OA200, OA202.	10/-
H15 30	Top Hat Silicon Rectifiers 750 mA. Mixed volts.	10/-
B86 50	Sil. Diodes sub. min. IN914 and IN916 types.	10/-
H16 8	Experimenters' Pak of Integrated circuits. Data supplied.	10/-
B88 50	Sil. Trans. NPN, PNP. equivalent to OC200/1, 2N706A, BSY95A. etc.	10/-
B60 10	7 Watt Zener Diodes. Mixed voltages.	10/-
H20 20	BY126/7 type Silicon Rectifiers 1 amp plastic. Up to 1,000 volts.	10/-
H6 40	250mW. Zener Diodes DO-7 min. Glass Type. AV.40% Good.	10/-

Complimentary Set.
NPN/PNP Germ.
Trans., Pak F.3. **2/6 PAIR**

NEW TESTED & GUARANTEED PAKS

B2 4	Photo Cells, Sun Batteries .3 to .5 volt, .5 to 2 ma	10/-
H8 4	BY127 Silicon Recs. 1000 P.I.V. 1 amp. Plastic. Replaces the BY100	10/-
B79 4	1N4007 Sil. Rec. Diodes. 1,000 P.I.V. 1 amp. Plastic.	10/-
B81 10	Reed Switches, mixed types, large and small.	10/-
B89 2	58P5 Light Sensitive Cells. Light Res. 400 Ohm Dark 1M Ohm	10/-
B91 8	NKT163/164 PNP Germ. TO-5 equivalent to OC44, OC45.	10/-
B92 4	NPN. Sil. Trans. A06 B8X20 2N2369 500 MHz, 360mW.	10/-
B93 5	GET113 Trans. equiv. to ACY17 to ACY21 PNP Germ.	10/-
B96 5	2N3136 PNP Sil Trans. TO-18, HFE 100-300 I.C. 600mA. 200MHz.	10/-
B88 10	XB112 and XB102 equiv. to AC126, AC156, OC81/2, OC71/2, NK271, etc.	10/-
H4 250	Mixed Resistors, Post and packing 2/-.	10/-
H7 40	Wirewound Resistors. Mixed Values. Postage 1/6.	10/-
H9 2	OCPT1 Light Sensitive Photo Transistors.	10/-

P.O. RELAYS 8 FOR
Various Contacts and Coil **20/-**
Resistances.
Post & Packaging 5/-

★ ALL OUR TESTED SEMICONDUCTORS HAVE A WRITTEN GUARANTEE ★

SEND FOR OUR FREE LISTS AND CATALOGUE OF ALL OUR PRODUCTS. CHECK YOUR OWN EQUIVALENT WITH OUR FREE SUBSTITUTION CHART.

NO CONNECTION WITH ANY OTHER FIRM. MINIMUM ORDER 10/-. CASH WITH ORDER PLEASE. Add 1/- post and packing per order. OVERSEAS ADD EXTRA POSTAGE.

MICRO SWITCH

5 amp. changeover contacts, 1/9 each, 18/- doz. 15 amp Model 2/- each or 21/- doz.



TOGGLE SWITCH

3 amp 250v. with fixing ring, 1/6 each, 15/- doz.

CONSTRUCTORS PARCEL

1. Plessey miniature 2 gang tuning condenser with built in trimmers and wave gang switch. 2. Ferrite slab aerial with coils to suit the above tuning condenser. 3. Circuit diagram giving all component values for 6 transistor circuit covering full medium wave and the long wave band around Radio 2. The three items for only 7/6d which is half of the price of the tuning condenser alone.

SLOW MOTION DRIVES

For coupling to tuning condensers etc. One end in. shaft, the other end fits to a 1/2 in. shaft with grub screws. Price 4/6 each 48/- dozen.

LARGE PANEL MOUNTING MOVING COIL METERS

Size 5in. x 4in. Centre zero 200-0-200 micro amp made by Sangamo Weston. Regular price probably 28. Our price 59/6, ditto but 100-0-100 79/6.

A.C. AMMETER

0-5 amps. flush mounting—moving iron. Ex equipment but guaranteed perfect 29/6.

CIRCUIT BOARDS

Heavy copper on 3/32 paxolin sheet ideal for making power packs etc. as sheet is very strong and thick enough to allow copper to be cut away with hacksaw blade. 5in. x 5in. 1/6 each, 15in. x 5in. 4/6d. each.

6KV A.C. TRANSFORMER

In ventilated sheet steel case—tapped 110v-140v-170v-200v-230v. Ex equipment but guaranteed perfect 119.10.0. carriage at cost.

PP3 BATTERY ELIMINATOR

Run your small transistor radio from the mains—full wave circuit—made up ready to wire into your set and adjustable high or low current. 8/6 each.



REED SWITCHES

Glass encased, switches operated by external magnet—gold welded contacts. We can now offer 3 types:

Miniature. 1in. long x approximately 1/4 in. diameter. Will make and break up to 1/4 A up to 300 volts. Price 2/6 each, 24/- dozen.
Standard. 2in. long x 3/16in. diameter. This will break currents of up to 1A, voltages up to 250 volts. Price 2/- each, 18/- per dozen.
Flat. Flat type, 2in. long, just over 1/16in. thick, approximately 1/4 in. wide. The standard type flattened out, so that it can be fitted into a smaller space or a larger quantity may be packed into a square solenoid. Rating 1 amp 200 volts. Price 6/- each, 23 per dozen.
 Small ceramic magnets to operate these reed switches 1/6 each, 18/- dozen.

0.005mFd TUNING CONDENSER

Proved design, ideal for straight or reflex circuits 2/6 each, 24/- doz.



SUB-MINIATURE MOVING COIL MICROPHONE

as used in behind the ear deaf aids
 A.C. also as earphone size only 1in. x 1in. x 1/4 in. Regular price probably 23 or more. Our price 19/6. Note these are ex-equipment but if not in perfect working order they will be exchanged.



CHART RECORDER MOTOR

Small 2" diameter (approx) instrument motor with fixing flange and spindle (1/4" long, 1/4" diameter) integral gear box gives 1 rev per 24 hours. 19/6

IGNITION (E.H.T.) TRANSFORMER

made by Parmeko Ltd., Primary 240V 50 cps. Secondary 5KV at 25 mA. Size approx. 4 1/2" x 3 1/2" x 2 1/2" thick. 22V each 4/6 p. & p.

12V EXTRACTOR FAN BY DELCO

Ideal for ventilation in Caravan, Car or Boat. 6 Bladed 5" diameter fan inside heavy duty cylinder with 3 point fixing flange. 5 1/2" diameter fixing hole. Length approx. 8 1/2". Exceptional bargain 27/6 plus 5/6 post and insurance.

NEED A SPECIAL SWITCH


Double Leaf Contact. Very slight pressure closes both contacts 1/8 each, 12/- doz. Plastic pusher suitable for operating, 1/- each, 9/- doz.

COMPUTER MULTI-CORE CABLES

12, 14/0076 copper cores, each one insulated by coloured P.V.C. then separately screened, the 12 metal braided cores laid together and P.V.C. covered overall making a cable just under 1/2 in. dia. but quite pliable. Price 7/6 per ft. Any length cut. Other sizes available 7 core 5/- ft., 6 core 4/- ft., 4 core 3/6 ft.

25 AMP ELECTRICAL PROGRAMMER

Learn in your sleep! Have Radio playing and kettle boiling as you awake—switch-on-lights to ward off intruders—have warm house to come home to. All these and many other things you can do if you invest in an Electrical Programmer. Made by the famous Smiths Instrument Company. This is essentially a 230/240 volt mains operated Clock and a 20 amp Switch, the switch-off time of which can be delayed up to 12 hours (continuously variable not Stepped). Similarly the switch-on-time can be delayed. This is a beautiful unit, size 5 1/2" x 3 1/2" x 2 1/2" deep. Metal encased, glass fronted with chrome surround. Offered at 47/6 plus 3/6 postage and insurance.

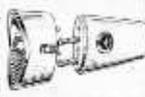

HI-FI SPEAKERS (15, 30, 40 & 100W)

FULL FI 12 INCH LOUDSPEAKER. This is undoubtedly one of the finest loudspeakers that we have ever offered, produced by one of the country's most famous makers. It has a die-cast metal frame and is strongly recommended for Hi-Fi load and Rhythm Guitar as public address. Flux Density 11,000 gauss—Total Flux 44,900 Maxwells—Power Handling 15 watts R.M.S. Cone Moulded fibre—Freq. response 30-10,000 c.p.s.—Specify 3 or 15 ohms—Mains resonance 60 c.p.s.—Chassis Diam. 12in.—12in. off mounting lugs—Baffle hole 11in. Diam.—Mounting holes 4, holes—1/4 in. diam. on pitch circle 11in. diam.—Overall height 5 1/2 in. A 25 speaker offered for only 23.18 plus 7/6 p. & p. 12in. 40watt 25.19.6. carr. 8/8. 15in. 25 watt 27.18.6. carr. 10/6. 18in. 100 watt 219.10.0. carr. 30/-.



INTEGRATED CIRCUIT BARGAIN

A parcel of integrated circuits made by the famous Plessey Company. A once-in-a-lifetime offer of Micro-electronic devices well below cost of manufacture. The parcel contains 5 ICs all new and perfect, first-grade device, definitely not sub-standard or seconds. The ICs are all single silicon chip General Purpose Amplifiers. Regular price of which is well over 21 each. Full circuit details of the ICs are included and in addition you will receive a list of 50 different ICs available at bargain prices 5/- upwards with circuits and technical data of each. Complete parcel only 21 post free; or List and all data 10/- post free. Credited when your order IC's value of 30/- and upwards.

MOTORIZED SWITCH For Animated signs etc.

This is motorised programmer switch, mains operated, with six 15 amp changeover contacts operated by triggers on a rotating drum. Six triggers will put switches up and another six triggers will put switches down. Also simple on/off operation or changeovers are possible. The triggers are exactly set to any position around the drum which is rotated by a one rev. per hour motor. (Motors with other speeds available). A beautifully made precision switch which probably cost in excess of 20. Limited quantity only 29.15. each post free.



DISTRIBUTION PANELS

Just what you need for work bench or lab. 4 x 13 amp sockets and on/off switch with neon warning light (in metal box). Takes standard 13 amp fused plugs. Supplied complete with 7 feet of heavy cable. 39/6 wired up, ready to work plus 4/6 post & insurance. 5 amp 3 pin model 35/-, 15 amp 3 pin model 45/-

BARGAIN OF THE YEAR

MICROSONIC KEYCHAIN RADIO

7 transistor Keychain Radio in very pretty case, size 2 1/2 x 2 1/4 x 1 1/4 in.—complete with soft leather zipped bag. Specification—
 Circuit: 7 transistor superheterodyne.
 Frequency range: 530 to 1600 Kc/s. Selectivity: 5 mv/m. Intermediate frequency: 465 Kc/s or 455 Kc/s. Power output: 40mW. Antenna: ferrite rod. Loudspeaker: Permanent magnet type.
 In transit from the East, these sets suffered slight corrosion as the batteries are left in them but when this corrosion is cleared away they should work perfectly—offered without guarantee except that they are new. Price only 24/6 less batteries plus 2/6 post 6 for 27 post free. Rechargeable batteries 8/6 pair.



24-HOUR TIME SWITCH

Mains operated. Adjustable contacts give 2 on/off per 24 hours. Contracts rated 15 amps. repeating mechanism so ideal for shop window control, or to switch hall lights (anti-burglar precaution) while you are on holiday. Made by the famous Smiths Company. This month only 49/6 with perspex cover, plus 3/6 postage and insurance, a real snip which should not be missed.


MOST AMAZING BARGAIN

PRINCESS AUTO CHANGER

The most amazing bargain ever! A brand new Auto change record player for less than the price of a single player... due to a frustrated export order we are able to offer the Balfour Princess 4 speed Autochanger—a really fine machine at about one third of its regular price.

The Balfour has two unique features (1) A patented brush system which automatically cleans styus after each record playing and (2) at shut off the pick-up locks itself into its recess—other features include pick-up height and styus pressure adjustments, and motor suitable for our 230/240 or for 115v. continental mains.

Beautifully styled—this is a high class expensive instrument but you can purchase one this month for only 59/6 plus 8/6 post and packing. One point, these changers have been to France and back and the vibrations of the journey, etc., may have loosened screws or otherwise put them out of adjustment. However, with each we supply a 16 page service manual and fault finding chart which is so detailed that if necessary you could completely re-build the changer. So this is truly a bargain that you will not want to miss so order today.

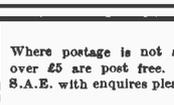

Where postage is not stated then orders over 25 are post free. Below 25 add 2/9. S.A.E. with enquires please.

MAINS TRANSFORMERS

Note all these are first grade Transformers and all have normal 200/240 volt 50 cycle primary. Mains Transformer Type No. 56786

Upright mounting, size 3 x 2 1/2 x 2 1/2 in. approximately, 2 secondaries one 230 volt 1 amp and the other 0.5 volt 1.5 amp. Earth screen between primary and secondaries—this transformer will power a 5.5 watt stereo amplifier (circuit diagram available, price 2/6). Suitable output transformer is type 56787 described below. Our price 17/6. Plus 4/6 post.

Mains Transformer Type No. 56783
 Chassis mounting type, size approximately 3 x 2 1/2 x 3in., 2 secondaries one 230 volt at 60 ma and other 6.3 volts 1.5 amp. Earth screen between primary and secondaries. This will power a 5 watt amplifier (circuit available 2/6). Matching OPT. 56734 described below. Price 18/6 plus 4/6 post. Mains Transformer Type No. 56896

Upright mounting, size approximately 4 x 3 x 2 1/2 in. 2 secondaries 275-0-275 at 90 ma and 6.4 volts at 3.1 ma. There is a screen between primary and secondaries. This is a partner to output transformer 56694 described below. Price 19/6 plus 4/6 post.

OUTPUT TRANSFORMERS

OPT. ref. 56684
 Chassis mounting—size 2 x 2 x 2 1/2 in. approximately 7 watts. A push pull transformer for matching 2/EL84 or similar valves to 15 ohm Loud Speaker. 14/6 no extra for post if ordered with Transformer 56695. Circuit diagram of amplifier available, price 2/6.

OPT. ref. 56787
 Upright mounting, size approximately 3 1/2 x 2 x 2 1/2 in. Matching impedance 60 ohms to 15 ohms. 5 watts output using transistor type AD140 (Circuit diagram available price 2/6). Price 8/6 each, no extra for postage if ordered with mains transformer type 56786.

OPT. ref. 56504
 Upright mounting, size approximately 2 x 2 1/2 x 2 1/2 in. Primary impedance 60 ohm, secondary impedance 3 ohm, otherwise this is as 56787. Price 8/6.

OPT. ref. 56784
 Chassis mounting, size approximately 2 1/2 x 2 x 1 1/2 in. Primary 500 ohm centre tapped. Ratio 271.5 watts output using twin ELL80 or similar. Price 12/6. No extra for postage if ordered with 56733.

HEAVY DUTY MAINS TRANSFORMER

30V. 37A. Primary tapped 200/240 in 10v. steps. A really beautiful "C" core transformer. Made by Parmeko, Impregnated and varnished. Weight approx. 50 lb., size approx. 8in. wide 4 1/2 in. deep and 8 1/2 in. high. Metal framed for free standing and fitted with E.S. screen. Probably priced 240-250 from Parmeko. Ex equipment, but perfect, 217.10 each, plus carriage at cost.

50 CYCLE TO 60 CYCLE INVERTERS

For operating American instruments and other equipment made for 60 cycles 115 v. from 230/240 50 cycle mains. These units have an output of 115 volts A.C. and will handle a load of up to 100 watts. These are precision made and have a reed type frequency meter which vibrates when the frequency is exactly 60 c.p.s. Adjustment of the frequency is by a knob on control panel. Input by 3 core output from 3 pin socket. Original cost of this in excess of 250. A limited quantity available 217/10 each.

MINIATURE WAFER SWITCHES

2 pole, 2 way—4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole 6 way—1 pole, 12 way. All at 3/6 each, 36/- dozen, your assortment.



WATERPROOF HEATING ELEMENT

26 yards length 70W. Self-regulating temperature control. 10/- post free.

MAINS OPERATED CONTACTOR

220/240v. 50 cycle solenoid with laminated core so very silent in operation. Closes 4 circuits each rated at 10 amps. Extremely well made by a German Electrical Company. Overall size 2 1/2 x 2 x 2 1/2 in. 19/6 each.



AUTO ELECTRIC CAR AERIAL

With dash board control switch—fully extendable to 40" or fully retracted. Suitable for 12V positive or Neg. earth supplied complete with fitting instructions and ready wired dash board switch 25.18.6 plus 5/- p. & p.



MAINS MOTOR

Precision made— as used in record decks and tape recorders— ideal also for extractor fan, blower, heaters etc. New and perfect. Snip at 9/6. Postage 3/- for first one then 1/- for each one ordered, 12 and over post free.

ELECTRONICS (CROYDON) LTD
 Dept. PW, 266 London Rd., Croydon CRO 2TH
 Also 102/3 Tamworth Road, Croydon

TECHNICAL TRAINING

in radio television and electronics

Whether you are a newcomer to radio and electronics, or are engaged in the industry and wish to prepare for a recognized examination, ICS can further your technical knowledge and provide the specialized training so essential to success. ICS have helped thousands of ambitious men to move up into higher paid jobs—they can help you too! Why not fill in the coupon below and find out how?

Many diploma and examination courses available, including expert coaching for:

- C. & G. Telecommunication Techns'. Certs.
- C. & G. Electronic Servicing
- R.T.E.B. Radio/T.V. Servicing Certificate
- Colour T.V. Servicing
- Radio Amateurs' Examination
- Radio operator Certs
- General Certificate of Education, etc.
- Now available Colour T.V. Servicing

Examination Students coached until successful

NEW SELF-BUILD RADIO COURSES

Learn as you build. You can learn both the theory and practice of valve and transistor circuits, and servicing work while building your own 5-valve receiver, transistor portable, and high-grade test instruments—all under expert tuition. Transistor Portable available as separate course.

POST THIS COUPON TODAY

for full details of ICS courses in Radio, T.V. and Electronics.



EST. 1891

INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 171, Intertext House, Stewart's Road, London, S.W.8.
Please send me the ICS prospectus—free and without obligation.
(state Subject or Exam).....

NAME

ADDRESS.....

11/70


INTERNATIONAL CORRESPONDENCE SCHOOLS

Stabilised P.U. 200/250v I/P, made by Solartron O/Ps 250 or 350v stab at 100 Ma also 6.3v 3 times, use 7 valves on chassis size 7 x 10 x 6" ex equip 65/-. Amplifier Units for 200/250v uses 7 valves as P.P. 6BW6 in O/P as int monitor speaker and current meter, O/P is 600 ohm in table cabinet size 19 x 12 x 10" used condition limited number £4.10s. Rack Cabinets 19" size overhaul 33" high, 22" wide 12½" deep hammer grey finish good cond. £3, Transformers 230v pria Sec 490-400-0-400-490 at 200 Ma, 5v 3a, 6.8 4a, 6.3 1.6a, 12v la C core ex equip 51/L.T. type sec 12v 1.5a 10/6, Osc Unit contains valves 12AT7 x 3, EF91 x 2, LA2 pot core, jack sk, coax sk, 10 & 500K pots, misc parts new cond 14/6, Metal Rect 12v 3a F.W. bridge new ex equip 10/6, Conds 8uf 750v Wk Dubiler 2 for 15/-, LA66 Pot Cores 3/6 ea 4 for 10/;, Coax cable H.D. 80 ohm 3/8th dia approx 30Ft new 14/6, Plugs & Sks miniature type 14 way 2/6 18 way 3/-. Meters 270' scale approx 1.5 Ma basic calibrated in altitude front 3½" sq. new cond 19/6. Helipots 500 ohm, 2.5K & 50K 16/6 ea, Helipot dials 10tr 16/6. Circuits 1475 & 1392 Rx 5/- ea.

Prices include post, S.A.E. with enquiry

A. H. Supplies

57, Main Road, Sheffield. S9. 5HL.

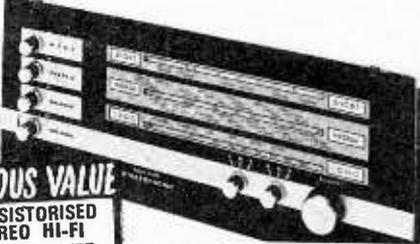

FABULOUS VALUE

TRANSISTORISED STEREO HI-FI RECORD PLAYER

Build your own Hi-Fi Record Player with the Sirenade fully transistorised amplifier which comes complete with 2-10" x 6" speakers and the latest BSR 4 Speed Stereo/Mono Record Changer.

Advanced solid state amplifier only 4½" deep, 14 transistors plus 4 diodes, separate Bass and Treble—10 watts total power. Frequency response 50-15,000 c/s.

EASY TO INSTALL
NO TECHNICAL KNOWLEDGE REQUIRED

Only **28 Gns.** + P&P 17/6
Credit terms available, first monthly payment £3.62 followed by 9 monthly payments of £3.62. (Total "Credit Sale" Price £33.18).
Send £4.38 today.

FANTASTIC BARGAIN OFFER!
"TRANSCONTINENTAL"
FULLY TRANSISTORISED STEREOGRAPHIC RADIOGRAM CHASSIS

Complete with 2-10" x 6" speakers and the latest BSR Mono/Stereo Record Changer—a complete radiogram at half normal price **ONLY**
10 Watts Total output
17 Transistors & 10 diodes
38 Gns. P&P 17/6

EASILY FITTED NO TECHNICAL KNOWLEDGE NECESSARY
Credit Terms available. First monthly payment £4.9.10 followed by 9 monthly payments of £4.9.10. (Total "Credit Sale" Price £44.18.4.) Send £5.74 today.

Callers Welcome

POST THIS COUPON NOW!

PLEASE SEND ME FREE DETAILS OF YOUR RANGE


Name

Address

LEWIS radio 100 CHASE SIDE, SOUTHGATE Dep. P1170 LONDON, N.14. TELEPHONE 886 3733/9686.

CODAR CR.70A

Communications Receiver 540-10 metres

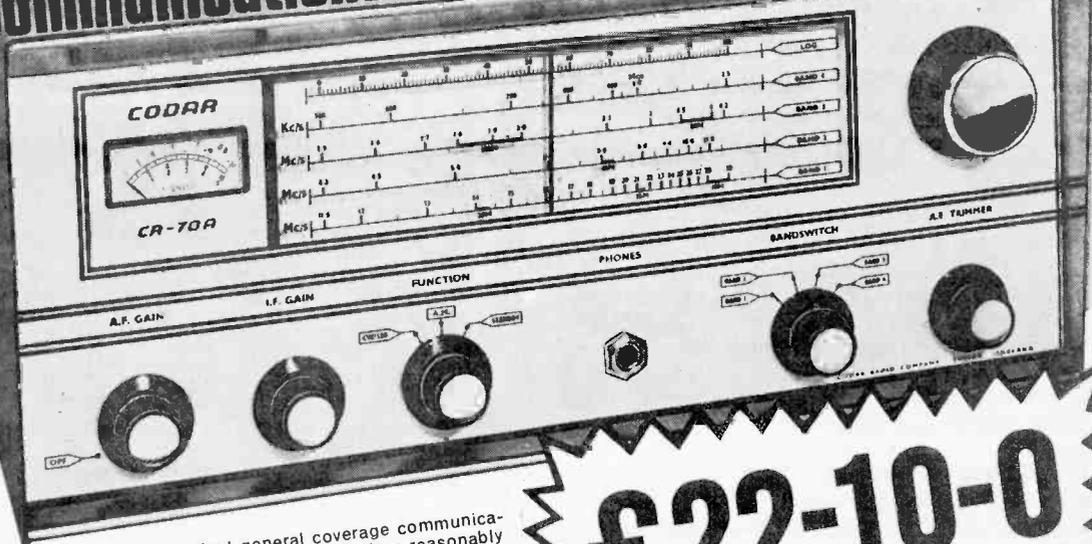

The Codar CR.70A is an excellent general coverage communications receiver for the keen short wave listener. Very reasonably priced at just £22.10.0 the CR.70A is outstanding value for money. In four stable ranges, the receiver covers from 540 metres medium wave, right through the shipping and coastguard frequencies all the short wave and international amateur bands up to and including 10 metres.

The CR.70A has a high 'Q' aerial input stage using exclusive CODAR COIL air space inductor. Double tuned, iron cored I.F. transformers produce high selectivity. Ready to plug into 200-250 volt AC mains, the CR.70A needs only your aerial and a 2-3 ohm loudspeaker. The cabinet measures only 13" x 5½" x 7½" and the control panel is finished in black and white with chrome trim knobs. Fully guaranteed for 12 months!

New model has separate direct output socket for feeding tape recorder, Hi-Fi equipment, etc.

£22-10-0

Carriage 13/- extra

- *Ideal for SWLs *5 valves (inc. two twin triodes) giving 7 valve line-up
- *Excellent on amateur and shipping frequencies
- *Calibrated signal strength meter (illuminated)
- *Automatic volume control
- *Separate B.F. oscillator for morse and S.S.B. signals
- *Two speed vernier tuning
- *Separate output for recording etc.

TRADE DESCRIPTION ACT 1968

Under the Trade Description Act 1968, it is illegal to give a misleading description or claim. We quote a few extracts from the hundreds of letters from satisfied customers and we claim that every testimonial letter is genuine, unsolicited and can be inspected at our offices.

Mr. J. Nicholson, Elphinstone Road, HASTINGS, Sussex.
I am delighted with the CR70A, at present I am working on an indoor aerial, and getting really fine results, as you rightly say this receiver has a high standard with a brilliant performance.

Mr. J. Walker, Biscoe Drive, ABINGDON, Berks.
I received the CR70A quite safely. I must say I am very pleased with it indeed. I have used other communication receivers in my time, and the CR70A is beyond my expectation and was well worth waiting for. My friends are amazed at its performance.

Mr. F. Rose, Oak Lane, HIGH WYCOMBE, Bucks.
You can be proud of your equipment, your name is held in great esteem by Radio Amateurs.

Mr. A. Sherwood, Norfolk Road, MAIDENHEAD, Berks.
I have recently purchased from you a CODAR CR70A. May I at this moment congratulate you on a first class piece of equipment and will certainly buy from you again. I remain a very satisfied customer.

Mr. W. Morris, Berch Avenue, ROMILEY, Cheshire.
May I take the opportunity to congratulate you upon the excellent quality and performance of CODAR Products.

Mr. D. Foster, Wansford Road, DRIFFIELD, Yorkshire.
I am very pleased with the quality of the parts and consider this fine set excellent value for money.

More extracts next month. Send 10d stamps for literature on CODAR COMMUNICATION EQUIPMENT. Start your own Short Wave Station now, and listen to world-wide commercial and amateur stations, shipping, trawlers, Ship to shore telephone, Lifeboat Services, Met stations, etc., etc.

CODAR UNIT 1 - MEADOW ROAD INDUSTRIAL ESTATE - EAST WORTHING - SUSSEX

WEYRAD

COILS & TRANSFORMERS FOR CONSTRUCTORS

Special versions of our P50 Series are now available for AF117 or OC45 Transistors. They can be used in the standard superhet circuit with slight changes in component values.

Oscillator Coil	P50/1AC (For OC45)	P50/1AC (For AF117).....	5/4
1st I.F. Transformer	P50/2CC (For OC45)	P51/1 (For AF117)	5/7
2nd I.F. Transformer.....	P50/2CC (For OC45)	P51/2 (For AF117)	5/7
3rd I.F. Transformer	P50/3CC (For OC45)	P50/3V (For AF117)	6/-
Rod Aerial	RA2W		12/6
Driver Transformer	LFD4/1		9/6
Output Transformer	OPT1		10/6
Printed Circuit	PCA1		9/6

I.F. TRANSFORMERS FOR "PRACTICAL WIRELESS" CIRCUITS

Components for several receivers are available, including the following for the "Clubman".

T41/1E	1st I.F. Transformer	7/6
* T41/2E	2nd I.F. Transformer	7/6
T41/3T	3rd I.F. Transformer	10/6
T41/3T	B.F.O. Coil	10/6

Details of these and our other components are given in an illustrated folder which will be supplied on request with 4d. postage please.

WEYRAD (ELECTRONICS) LIMITED

SCHOOL STREET, WEYMOUTH, DORSET

VALVES

SAME DAY SERVICE
NEW! TESTED! GUARANTEED

SETS 1R5, 1R5, 1T4, 3R4, 3V4, DAF91, DF91, DK91, DL92, DL94.
Set of 4 for 18/6, DAF96, DF 96, DK96, DL96, 4 FOR 29/-.

1A7GT 7/6	25U4GT11/6	DL94 6/9	EM34 14/6	PCL85 9/-	UBF80 5/9
1H5GT 7/3	30C1 6/6	DL96 7/3	EM80 8/3	PCL86 8/6	UBF89 6/9
1N5GT 7/9	30C15 13/-	DY86 5/9	EM81 8/3	PCL88 14/6	UCC84 7/-
1R5 5/9	30C17 18/-	DY87 6/9	EM84 6/9	PCL800 15/6	UCB85 7/3
1R5 4/3	30C18 13/6	EAB80 6/6	EM87 7/6	PEN44 8/6	UCF80 7/3
1T4 3/9	30F5 15/9	RAF42 10/-	EY31 7/3	PFL20011/9	UCH42 12/6
3R4 5/9	30FL1 12/9	EB91 2/3	EY86 6/6	PL36 9/9	UCH81 6/6
3V4 6/9	30FL12 14/6	EBC33 8/-	EZ40 8/-	PL81 9/3	UCR2 7/-
5Y3GT 5/9	30FL14 14/6	EBC41 10/6	EZ41 8/-	PL81A 10/3	UCL83 11/-
5Z4G 7/6	30L1 6/6	EBF80 6/9	EZ80 4/6	PL82 6/-	UF41 10/6
6/30L2 12/-	30L15 13/-	EBF89 6/3	EZ81 4/9	PL83 6/6	UP85 6/9
6AL5 2/3	30L17 15/6	ECC81 3/9	GZ32 8/9	PL84 6/6	UF89 6/9
6AM6 2/9	30P4 13/-	ECC82 4/9	GZ34 9/9	PL500 13/-	UL41 12/-
6AQ5 5/3	30P12 13/9	ECC83 7/-	KT41 15/6	PL504 13/6	UL44 20/-
6AT6 4/6	30P19 13/-	ECC85 5/9	KT61 9/9	PL508 23/6	UL84 7/-
6BA6 4/6	30PL1 12/9	ECC80A 12/-	KT66 16/9	PM84 7/6	UM80 5/-
6BE6 4/9	30PL13 14/6	ECP80 6/-	LN929 14/6	PX25 22/6	UM84 4/6
6B16 8/6	30PL14 14/-	ECP82 6/-	N78 17/6	PY32 10/-	UY41 7/6
6C5G 4/9	35L6GT 8/9	ECH35 6/-	P61 10/-	PY33 10/-	UY85 5/9
6CD8G 22/-	35W4 4/6	ECH42 12/9	PABC80 7/-	PY81 5/3	VP4B 15/6
6F14 9/-	35Z4GT 5/-	ECH81 5/9	PC86 10/3	PY82 5/3	W77 3/6
6F23 14/3	807 9/-	ECH83 8/3	PC88 10/3	PY83 5/9	W119 7/-
6F25 12/3	6083 12/6	ECH84 7/6	PC89 8/6	PY88 6/9	Z77 4/6
6J5G 4/9	AC/VP215/6	ECL80 8/-	PC97 8/-	PY400 7/6	Transistors
6K7G 2/6	AZ31 9/6	ECL82 6/9	PC900 7/6	PY801 7/6	AC107 3/6
6K8G 3/-	B349 13/-	ECL86 8/-	PC884 6/6	R19 6/6	AC127 2/6
6SN7GT 4/3	B729 12/6	EF37A 6/6	PCC85 6/-	R20 12/-	AD140 7/6
6V6G 3/3	OCH35 13/6	EF39 4/9	PCC88 9/-	SU2150A	AF115 3/-
6V6GT 6/6	CL33 18/6	EF41 11/9	PC889 9/6	U25 12/6	AF118 3/-
6X4 4/6	CY31 6/9	EF80 4/6	PC8189 9/9	U25 13/-	AF117 4/-
6X5GT 5/9	DAC32 7/3	EF85 6/3	PC8205 13/-	U26 12/-	AF125 3/6
10P18 7/-	DAF91 4/3	EF86 6/3	PCF80 6/6	U47 13/6	AF127 3/6
10P13 12/-	DAF96 7/3	EF89 5/3	PCF82 6/6	U49 12/-	OC26 5/-
12AT7 3/9	DF33 7/9	EF91 2/9	PCF86 9/6	U78 4/6	OC44 2/6
12AU6 4/9	DF91 2/9	EF183 5/9	PCF800 13/6	U191 12/6	OC45 2/6
12AU7 4/9	DF96 7/3	EF184 6/6	PCF801 6/6	U193 8/6	OC71 2/6
12AX7 4/9	DH77 4/6	EH90 8/6	PCF802 9/-	U251 14/6	OC72 2/6
12K8GT 7/3	DK32 7/6	EL33 9/6	PCF805 13/6	U301 10/6	OC75 2/6
19B6G617/6	DK91 5/9	EL34 6/6	PCF806 11/3	U329 14/6	OC81 2/6
20P2 13/6	DK92 8/6	EL41 11/-	PCF808 14/6	U801 19/6	OC81D 3/6
20P3 11/9	DK96 7/3	EL84 4/9	PCL82 7/3	UABC80 6/6	OC82 2/6
20P4 18/6	DL35 6/-	EL90 5/3	PCL83 10/3	UA42 10/3	OC82D 2/6
25L6GT 6/-	DL92 5/9	EL500 13/6	PCL84 7/6	UBC41 10/6	OC170 4/6

READERS RADIO

85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX. Tel. 01-550 7441.

Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra. Any Parcel Insured against Damage in Transit 6d. extra

When in LUTON, BEDS, you must visit the . . .

SELF-SERVICE RADIO COMPONENTS SHOP

Serve yourself from a selection of 1,200 boxes of Manufacturer's surplus stocks and save money.

9 a.m. to 5.30 p.m. every day.
Closed all day Wednesday.

SURPLECTRONICS

216 LEAGRAVE ROAD, LUTON, BEDS



BAKER 12in. MAJOR £9

The remarkable quality and performance of the "Major" makes possible truly brilliant and rich sound from a single loudspeaker. It recreates the entire musical spectrum from 30 to 14,500 c.p.s. The unit consists of the latest double cone, woofer and tweeter cone together with a special Baker CERAMIC magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c.p.s. For Hi-Fi or P.A. Rated 20 watts. Voice coils available 3 or 8 or 15 ohms.

Major Module 30-17,000 cps with tweeter, crossover, baffle 19 x 12 1/2 in. and instructions. £11.10.0


Send 4d Stamp for New Catalogue

Baker Reproducers Ltd

Bensham Manor Road Passage, Thornton Heath, Surrey. Telephone 01-684-1665

MONO TRANSISTOR AMPLIFIER HSL 700

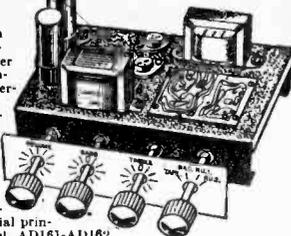A really high fidelity monaural amplifier with performance characteristics to suit the most discriminating listener.



6 transistor circuit with integrated pre-amplifier assembled on special printed sub panel. AD161-AD162 operating in symmetrical complementary pair. Output transformer coupled to 3 ohm and 15 ohm speaker sockets. Standard phono input sockets. Full wave bridge rectifier power supply for AC mains 200-240v. Controls: Bass, Treble, Volume/on/off. Function selector for P.U1, P.U2, Tape, Radio. The HSL 700 is strongly constructed on rigid steel chassis bronze hammer enamel finish, size 8 1/2 x 5 x 4 1/2 in. high.

Construction: P.U1-50m/v. 56K input impedance. P.U2-110m/v. 1 meg input impedance. Tape-110m/v. 1 meg input impedance. Radio-110m/v. 1 meg input impedance. Power measured at 1Kc. 4.5 watts RMS into 3 ohms. 1.58 watts RMS into 15 ohm. Overall frequency response 30 c/s-18 Kc/s. Continuously variable tone controls: Bass, +8db to -12db at 100c/s. Treble, +10db to -10db at 10Kc/s. The HSL 700 has been designed for true high fidelity reproduction from Radio Tuner, Gramophone deck and Tape Recorder preamp. Supplied ready built and tested, complete with knobs, attractive anodised aluminium front escutcheon panel, long spindles (can be cut to suit your housing requirements) full circuit diagram and operating instructions.

Our Special Price **£7.19.6** P & P 7/6

LOUDSPEAKER BARGAINS

3" x 4in 10/- P. & P. 1/6. 5in. 3 ohm 16/- P. & P. 3/- P. & P. 4/- E.M.I. 8 x 5in. 3 ohm with high flux magnet 26/- P. & P. 4/- E.M.I. 13 x 8in. 3 ohm with high flux ceramic magnet 42/- (15 ohm 45/-) P. & P. 6/- E.M.I. 13 x 8in. 3 or 15 ohm with two built tweeters and crossover network 4 gns. P. & P. 6/-

BRAND NEW. 12in. 15w. H/D Speakers, 3 or 15 ohms. Current production by well-known British maker. Now with Hifix ceramic ferrobar magnet assembly £5.10.0. P. & P. 7/6 Guitar models: 25w. £6.10.0, 30w. £8.10.0. E.M.I. 5in. HEAVY DUTY TWEETERS. Powerful ceramic magnet. Available in 3 or 8 or 15 ohms 18/6 each. P. & P. 2/6.

12in. "H.A." TWIN CONE LOUDSPEAKER. 10 watts peak handling, 3 or 15 ohm 37/6. P. & P. 6/8. 85 OHM SPEAKERS 3in. 14/- P. & P. 2/6;

MAGNAVOX DESK TYPE MOVING COIL MICROPHONE. Medium imp. Brand New. Special Price 42/- P. & P. 2/- SINGLE HEADPHONE

With aluminium headband. Approx 900 ohm 5/- P. & P. 1/6

BALANCED ARMATURE EARPHONE

Approx 70 ohm impedance. Can be used as ultra sensitive mike or speaker. ONLY 3/6. P. & P. 1/6.

CRYSTAL MIKES. High imp. for desk or hand use. High sensitivity, 18/6. P. & P. 1/8.

HIGH IMPEDANCE CRYSTAL STICK MIKES. OUR PRICE 21/- P. & P. 1/6

HIGH IMPEDANCE DYNAMIC STICK MIKES. High sensitivity, 38/6. P. & P. 2/6.

HONEYWELL MICROSWITCHES. 8/P. C/O. Push button action. Rating 250v. AC at 15 amps. Size approx. 1 1/2 x 1/2 x 1/2 in. 5/- each. P. & P. 1/- (6 or more post free).

SPECIAL OFFER! PLESSEY TYPE 29 TWIN TUNING GANG. 400pF + 146pF. Fitted with trimmers and 6:1 integral slow motion. Suitable for nominal 470 k/c I.F. Size approx. 2 x 1 x 1 1/2. Only 8/6. P. & P. 2/6.

TELESCOPIC AERIALS WITH SWIVEL JOINT. Can be angled and rotated in any direction. 6 section lacquered brass. Extends from 6in. to 22 1/2 in. approx. Maximum diameter 1/2 in. 6/- each. P. & P. 1/-

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-240v. Secondary combinations 0-6-10-15-20-25-30-35-40-60v. half wave at 1 amp, 10-0-10, 20-0-20, 30-0-30v. at 2 amps full wave. Size 3in. long x 3 1/2 in. wide x 3in. deep. Price 35/- P. & P. 2/6

MAINS TRANSFORMER. For transistor power supplies. Pri. 200/240v. Sec. 9-0-9 at 500mA. 14/- P. & P. 2/6. Pri. 200/240v. Sec. 12-0-12 at 1 amp. 17/6. P. & P. 2/6. Pri. 200/240v. Sec. 10-0-10 at 2 amp. 27/6. P. & P. 3/6. Tapped Primary 200-220-240v. Sec. 21.5v. at 500mA. 22/6. P. & P. 2/6

BATTERY CHARGER TRANSFORMERS. 200/240v. input. Nominal output for 6 or 12v. batteries 3 amps. Size approx. 3" x 2 1/2" x 2 1/2". Brand New. Price 21/- P. & P. 5/-

HIGH GRADE COPPER LAMINATE BOARDS. 8 x 6 x 1/4 in. FIVE for 10/- P. & P. 2/-

Open 9-5.30 Monday to Saturday
Early closing Wed. 1 p.m.
A few minutes from South Wimbledon Tube Station.

HARVERSON SURPLUS CO. LTD.

170 HIGH ST., MERTON, LONDON, S.W.19 Tel.: 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

STOCKISTS OF SINCLAIR EQUIPMENT

SPECIAL OFFER !! HI-FI LOUDSPEAKER SYSTEM

Beautifully made teak finish enclosure with most attractive Tygan-Uynair front. Size 16 1/2" high x 10 1/2" wide x 8" deep. Fitted with E.M.I. Ceramic Magnet 13" x 8" bass unit, two E.F. tweeter units and crossover. Power handling 40 watts. 8 Gns. 10/- Available in 3 or 15 ohm impedances. Also available in 8 ohm with EMI 13" x 8" bass speaker with parasitic tweeter £6 10 0 Carr 10/-

TRANSISTOR STEREO 8 + 8 MK II

Now using Silicon Transistors in first five stages on each channel resulting in even lower noise level with improved sensitivity. A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors giving 8 watts push pull output per channel (16W mono). Integrated pre-amp with Bass, Treble and Volume controls. Suitable for use with Ceramic or Crystal cartridges. Output stage for any speakers from 3 to 15 ohms. Compact design, all parts supplied including drilled metal work. Cir-Kit board, attractive front panel, knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Freq. response ±3db. 20-20,000 c/s. Bass boost approx. to +12db. Treble cut approx. to -16db. Negative feedback 18db over main amp. Power requirements 25V at 6 amp.

PRICES: AMPLIFIER KIT £10.10.0; POWER PACK KIT £3.0.0; CABINET £5.0.0. All Post Free. Carr. Also available STEREO 14 + 10. As above but 10 watts per channel. PRICES: AMPLIFIER KIT £12; POWER PACK KIT £3.10.0 Circuit diagram, construction details and parts list (free with kit) 1/6 (S.A.E.).

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P.U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-18v. battery or from H.T. line 200/300v. Frequency response 15Hz-25KHz. Gain 26dB. Solid encapsulation size 1 1/2" x 1 1/2" x 1/2". Brand new complete with instructions. Price 17/6 P. & P. 2/6.



BRAND NEW E.M.I. LIGHTWEIGHT PICK-UP ARM WITH ARM BEST, (as above). Fitted mono t/o stylus and cartridge for LP/78. ONLY 20/- P. & P. 1/6.

QUALITY RECORD PLAYER AMPLIFIER MK II A top quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. wide x 3in. deep x 6in. high. Ready built and tested. PRICE 75/- P. & P. 6/-

ALSO AVAILABLE mounted on board with output transformer and speaker ready to fit into cabinet below. PRICE 97/6. P. & P. 7/6.

DELUXE QUALITY PORTABLE R/P CABINET MK II. Uncut motor board size 14 x 12in. clearance 2in. below, 5 1/2 in. above. Will take above amplifier and any B.S.R. or GARRARD changer or Single Player (except AT60 and SP25). Size 18 x 15 x 8in. PRICE 79/6. P. & P. 9/6.


10/14 WATT HI-FI AMPLIFIER KIT A stylish finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other.

Fully controlled section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls, and separate base and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and EZ80 rectifier. Simple instruction booklet 2/6 (Free with parts). All parts sold separately. ONLY 27.19.6. P. & P. 8/6. Also available ready built and tested complete with std. input sockets, £9.19.6. P. & P. 8/6.

BRAND NEW TRANSISTOR BARGAINS. GET 15 (Matched pair) 15/-; V15/10p 10/-; OC71 5/-; OC76 6/-; A 117 3/6; 20330 (NPN) 3/-; Set of Mullard 6 transistors OC44, 2-OC45, AC128d matched pair AC128 25/-; ORP12 Cadmium Sulphide Cells 10/6. All post free.

VERY POWERFUL COMPACT MOTOR For 12v. D.C. operation. Off load consumption approx. 100mA. Totally enclosed. Quiet in operation with high starting torque. Overall size approx. 1 1/2" x 1 1/2" dia. Free shaft 3/8" dia. x 1/2". Ideal for Model Makers, etc. ONLY 7/6 each P. & P. 1/- 3 or more post free (A few 6v. versions also available)

DE LUXE STEREO AMPLIFIER

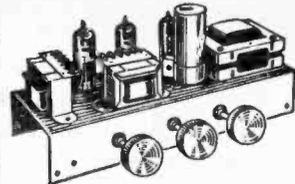

Valve line up: -2 x ECL86 Triode Pentodes, 1 x EZ80 as full wave rectifier. Two dual pentodes are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 30mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" w x 4" d. Overall height including valves 5". Ready built and tested to a high standard. PRICE 28.18.6 P. & P. 8/-

4-SPEED RECORD PLAYER BARGAINS Mains models. All brand new in maker's packing. SPECIAL OFFER! Famous GARRARD 3500 fitted Sonotone 9TAHCD Diamond Stereo Cartridge. List price over £16. Limited Number at £10. Carr. 5/6. LATEST B.S.R. C109/AB1 4-SPEED AUTOCHANGER. With latest mono compatible cartridge £6.19.6. Carr. 6/6. With stereo cartridge £7.19.6. Carr. 6/6. LATEST GARRARD MODELS. All types available 1025, 2025, SP25, 3000, AT90 etc. S.A.E. for latest Prices! PLINTH UNITS cut out for Garrard Model, 1025, 2025, 2000, 3000, 3500 etc. With rigid transparent plastic cover. Special design enables above models to be used with cover in position. Also suitable for housing AT60 and SP25. OUR PRICE £5.15.0 complete. P. & P. 8/6.

LATEST ACOS GP91/1SC mono compatible cartridge with t/o stylus LP/EP/78. Universal mounting bracket. 30/- P. & P. 1/6.

SONOTONE 9TAHC compatible Stereo Cartridge with diamond stylus 60/- P. & P. 2/-

LATEST RONETTE T/O STEREO COMPATIBLE CARTRIDGE for EP/LP/Stereo/78. 32/6. P. & P. 2/-

LATEST RONETTE T/O MONO COMPATIBLE CARTRIDGE for playing EP/LP/78 mono or stereo records on mono equipment. Only 30/- P. & P. 2/-

HIGH GAIN 4 TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT

Type T17 Peak output in excess of 1 1/2 watts. All standard British components. Built on a printed circuit panel size 6 x 3in. Generous size Driver and Output Transformers. Output transformer tapped for 3 ohm and 15 ohm speakers. Transistors (GET114 or 81, Mullard AC128 and matched pair of AC128) 9v. operation. Everything supplied, wire, battery clips, solder, etc. Comprehensive easy to follow instructions and circuit diagram 2/6 (Free with Kit). All parts sold separately. SPECIAL PRICE 49/6. P. & P. 3/-

Also ready built and tested, 55/- P. & P. 3/-

3-VALVE AUDIO AMPLIFIER HA3 MK II

Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" w x 4 1/2" d. x 4 1/2" h. Incorporates ECC83, EL84, EZ80 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only 24.15.0. P. & P. 6/-

HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. 79/6. P. & P. 6/-

HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL86 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. AC mains 200/240v. Supplied absolutely Brand New completely wired and tested with good quality output transformer.

FEW ONLY. BARGAIN PRICE **55/-** P. & P. 6/-

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

BI-PAK SEMICONDUCTORS

NEW LOW PRICED TESTED S.C.R.'s.

1A	3A	7A	16A	30A
(TO-5)	(TO-66)	(TO-48)	(TO-48)	
case	case	case	case	
PIV	each	each	each	PIV each
50	4/6	5/-	9/6	10/6
100	5/-	6/6	10/6	12/6
200	7/-	7/6	11/6	15/-
400	8/6	9/6	13/6	18/6
600	10/6	11/6	15/6	20/6
800	12/6	14/-	18/-	30/-

PRINTED CIRCUITS EX-COMPUTER
Packed with semiconductors and components. 10 boards give a guaranteed 30 trans. and 30 diodes. Our price 10 boards 10/- Plus 2/- p. & p.

TRANSISTOR EQUIVANT BOOK
A complete cross reference and equivalent book for European, American and Japanese Transistors. Exclusive to BI-PAK. 15/- each.

2N9060 NPN SIL. DUAL TRANS. CODD D1699 TEXAS. Our price 5/- ea.

120V8 NIXIE DRIVER TRANSISTOR. Sil. Metal TO-18. Fully tested and coded ND120, 1-24, 8/6 each. TO-5 NPN 25 up 8/- each.

MULLARD I.C. AMPLIFIERS
TAA243, Operational amplifier, 70/- each.
TAA263, Linear AF amplifier, 18/6 each.
TAA293, General purpose amplifier, 21/- each.

CA3020 RCA (U.S.A.) LINEAR INTEGRATED CIRCUITS
Audio Power Amplifier, 30/- each.

SIL. RECTS. TESTED

PIV	750mA	3A	10A	30A
50	1/-	2/9	4/3	9/6
100	1/3	3/3	4/6	15/-
200	1/9	4/-	4/9	20/-
300	2/3	4/6	6/6	22/-
400	2/6	5/6	7/6	25/-
500	3/-	6/-	8/6	30/-
600	3/3	6/9	9/-	37/-
800	3/6	7/6	11/-	40/-
1000	5/-	9/3	12/6	50/-
1200	6/6	11/6	15/-	

TRIACS

VBOM	2A	6A	10A
(TO-1)	(TO-66)	(TO-88)	
100	14/-	15/-	22/6
200	17/6	20/-	28/-
400	20/-	25/-	35/-

VBOM = Blocking voltage in either direction.

2N3055 115 WATT SIL. POWER. NPN. OUR PRICE 12/6 EACH

FULL RANGE OF ZENER DIODES
VOLTAGE RANGE 2-18V. 400mV (DO-7 Case)
2/8 ea. 1-5W (T. op-Hat)
3/6 ea. 10W. (80-10 Stud)
5/- ea. All fully tested 5% tol. and marked. State voltage required.

BRAND NEW TEXAS GERM. TRANSISTORS
Coded and Guaranteed.

PAK No.	EQVT
T1	8 2G371A
T2	8 2G374A
T3	8 2G374A
T4	8 2G381A
T5	8 2G382T
T6	8 2G344A
T7	8 2G345A
T8	8 2G378
T9	8 2G389A
T10	8 2G417

All 10/- each pack

SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Unequaled Value and Quality
Satisfaction GUARANTEED in Every Pak, or money back.

Pak No.

U1	120 Glass Sub-min. General Purpose Germanium Diodes	10/-
U2	60 Mixed Germanium Transistors AF/RF	10/-
U3	75 Germanium Gold Bonded Diodes sim. OA5. OA47	10/-
U4	40 Germanium Transistors like OC31, AC128	10/-
U5	60 200mA Sub-min. Sil. Diodes	10/-
U6	30 Silicon Planar Transistors NPN sim. B8Y96A, 2N706	10/-
U7	15 Silicon Rectifiers Top-Hat 760mA up to 1,000V	10/-
U8	50 Sil. Planar Diodes 250mA OA/200/202	10/-
U9	20 Mixed Volts 1 watt Zener Diodes	10/-
U11	30 PNP Silicon Planar Transistors TO-5 sim. 2N1132	10/-
U13	30 PNP-NPN Sil. Transistors OC200 & 28104	10/-
U14	150 Mixed Silicon and Germanium Diodes	10/-
U15	25 NPN Silicon Planar Transistors TO-5 sim. 2N697	10/-
U16	10 3-amp Silicon Rectifiers Stud Type up to 1,000 PIV	10/-
U17	30 Germanium PNP AF Transistors TO-5 like ACY17-22	10/-
U18	8 6-Amp Silicon Rectifiers BZY13 Type up to 600 PIV	10/-
U19	25 Silicon NPN Transistors like BC108	10/-
U20	12 1-5 amp Silicon Rectifiers Top-Hat up to 1,000 PIV	10/-
U21	30 AF Germanium alloy Transistors ZG300 Ser. & OC71	10/-
U23	30 Madt's like MAT Series PNP Transistors	10/-
U24	20 Germanium 1-amp Rectifiers GJM up to 300 PIV	10/-
U25	25 300Mc/s NPN Silicon Transistors 2N708, B8Y27	10/-
U26	30 Fast Switching Silicon Diodes like 1N914 Micro-min.	10/-
U28	Experimenters' Assortment of Integrated Circuits, untested. Gates, Flip-Flops, Registers, etc. 8 Assorted Pieces	20/-
U29	10 1-amp SCR's TO-5 can up to 600 PIV CR31/25-600	20/-
U31	20 Sil. Planar NPN trans. low noise Amp 2N3707	10/-
U32	25 Zener diodes 400mW D07 case mixed Volts, 3-18	10/-
U33	16 Plastic case 1 amp Silicon Rectifiers 1N4000 series	10/-
U34	30 Sil. PNP alloy trans. TO-5 BCY26, 28302/4	10/-
U35	25 Sil. Planar trans. PNP TO-18 2N2906	10/-
U36	25 Sil. Planar NPN trans. TO-5 BFY 50/51/52	10/-
U37	30 Sil. alloy trans. 80-2 PNP, OC200 28322	10/-
U38	20 Fast Switching Sil. trans. NPN. 400 Mc/s 2N3011	10/-
U39	30 RF Germ. PNP trans. 2N1303/5 TO-5	10/-
U40	10 Dual trans. 6 lead TO-5 2N2060	10/-
U41	25 RF Germ. trans. TO-1 OC45 NKT72	10/-
U42	10 VHF Germ. PNP trans. TO-1 NKT667 AF117	10/-

Code Nos. mentioned above are given as a guide to the type of device in the Pak. The devices themselves are normally unmarked.

I.C. AMPLIFIER

Identical encapsulation and pin configuration to the following: SL402-3, IC10 and IC403. Each circuit incorporates a pre-amp and class A.B. Power amp stage capable of delivering up to 3 watts RMS. Fully tested and guaranteed. Supplied complete with circuit details and data. CODED BP1010. OUR LOWEST PRICE 30/- each. 10 up 25/- each.

AD161 NPN AD162 PNP
MATCHED COMPLEMENTARY PAIRS OF GERM-POWER TRANSISTORS. For mains driven output stages of amplifiers and Radio receivers. OUR LOWEST PRICE OF 12/6 PER PAIR.

UNIUNCTION
UT46. Eqt. 2N2646 Eqt. TIS43. BEN3000 5/6 EACH 25-99 5/- 100 UP 4/-

NPN SILICON PLANAR
BC107/8 21/- each 50-99 1/10 100 up, 1/8 each, 1,000 off, 1/6 each. Fully tested and coded TO-18 case.

NPNDIFFUSED SILICON PHOTO-DUODIODE
TYPE 15701 (2N2175) for Tape Readout, high switching and measurement indicators. 50V, 250mV. OUR PRICE 10/- EACH 50 OR OVER 8/6 EACH. FULL DETAILS.

FET'S
2N 3819 8/-
2N 3820 20/-
MPP105 8/6

BI-PAK = LOW COST I.C.'s

BI-PAK Semiconductors now offer you the largest and most popular range of I.C.'s available at these EXCLUSIVE LOW PRICES. TTL Digital 74N Series fully coded, brand new. Dual in-line plastic 14 and 16 pin packages.

BI-PAK Order No.	SIM-TYPE.	Description	Price and qty. prices
			1-24 25-99 100 up
BP00	7400N	Quad 2-Input NAND Gate	6/6 5/6 4/6
BP01	7401N	Quad 2-Input NAND Gate - OPEN COLLECTOR	6/6 5/6 4/6
BP04	7404N	HEX INVERTER	6/6 5/6 4/6
BP10	7410N	Triple 3-Input NAND GATE	6/6 5/6 4/6
BP20	7420N	Dual 4-Input NAND GATE	6/6 5/6 4/6
BP30	7430N	Single 8-Input NAND GATE	6/6 5/6 4/6
BP40	7440N	Dual 4-Input BUFFER GATE	6/6 5/6 4/6
BP41	7441AN	BCD to decimal decoder and NIT Driver	22/6 20/- 17/6
BP42	7442N	BCD to decimal decode (TTL 0/1)	22/6 20/- 17/6
BP60	7450N	Dual 2-Input AND/OR/NOT GATE - expandable	6/6 5/6 4/6
BP63	7453N	Expandable 4-wide 2 input and/or nor gate.	6/6 5/6 4/6
BP60	7460N	Dual 4-Input - expandable	6/6 5/6 4/6
BP70	7470N	Single JK Flip-flop - edge triggered	9/- 8/- 7/-
BP72	7472N	Single Master Slave JK Flip-flop	9/- 8/- 7/-
BP73	7473N	Dual Master Slave JK Flip-flop	10/- 9/- 8/6
BP74	7474N	Dual D Flip-flop	10/- 9/- 8/6
BP76	7476N	Quad Bistable Latch	11/- 10/- 9/6
BP76	7476N	Dual Master Slave Flip-flop with preset and clear	11/- 10/- 9/6
BP83	7483N	Four Bit Binary Adder	26/- 22/6 20/-
BP90	7490N	BCD Decode Counter	22/6 20/- 17/6
BP92	7492N	Divide by 12 4 Bit binary counter	22/6 20/- 17/6
BP93	7493N	Divide by 16 4 Bit binary counter	22/6 20/- 17/6
BP94	7494N	Dual Entry 4 Bit Shift Register	22/6 20/- 17/6
BP95	7495N	4 Bit Up-Down Shift Register	22/6 20/- 17/6
BP96	7496N	5 Bit shift register	24/- 21/- 18/6

Data is available for the above Series of Integrated circuits in booklet form, price 2/6

BRAND NEW FULL TO MANUFACTURERS' SPECIFICATION

BP709 Operational Amplifier, dual-in-line 14 pin package = BN72709 and similar to MIC709 and ZLD709C 10/6 9/- 8/-

This is a high performance operational amplifier with high impedance differential inputs and low impedance output.

TTL INTEGRATED CIRCUITS

Manufacturers' "Fall outs" - out of spec. devices including functional units and part functional but classed as out of spec. from the manufacturers very rigid specifications. Ideal for learning about I.C.'s and experimental work, on testing some will be found perfect.

PAK No.	PAK No.	PAK No.
UIC00 = 5 x 7400N .10/-	UIC42 = 5 x 7442N .10/-	UIC80 = 5 x 7480N .10/-
UIC01 = 5 x 7401N .10/-	UIC50 = 5 x 7450N .10/-	UIC82 = 5 x 7482N .10/-
UIC02 = 5 x 7402N .10/-	UIC61 = 5 x 7461N .10/-	UIC83 = 5 x 7483N .10/-
UIC03 = 5 x 7403N .10/-	UIC60 = 5 x 7460N .10/-	UIC86 = 5 x 7486N .10/-
UIC04 = 5 x 7404N .10/-	UIC70 = 5 x 7470N .10/-	UIC90 = 5 x 7490N .10/-
UIC05 = 5 x 7405N .10/-	UIC72 = 5 x 7472N .10/-	UIC92 = 5 x 7492N .10/-
UIC10 = 5 x 7410N .10/-	UIC73 = 5 x 7473N .10/-	UIC93 = 5 x 7493N .10/-
UIC20 = 5 x 7420N .10/-	UIC74 = 5 x 7474N .10/-	UIC94 = 5 x 7494N .10/-
UIC40 = 5 x 7440N .10/-	UIC75 = 5 x 7475N .10/-	UIC95 = 5 x 7495N .10/-
UIC41 = 5 x 7441AN .10/-	UIC76 = 5 x 7476N .10/-	UIC96 = 5 x 7496N .10/-

UICX1 = 20 x asst'd 74's .30/-

Packs cannot be split but 20 assorted pieces (our mix) is available as PAK UICX1. Every PAK carries our BI-PAK Satisfaction or money back GUARANTEE.

DUAL-IN-LINE LOW PROFILE SOCKETS

14 AND 16 Lead Sockets for use with Dual-in-Line Integrated Circuits.

Order No.	Price each
TS014 14 pin type	1-24 25-99 100up
TS016 16 pin type	7/8 8/6 7/8

RTL FAIRCHILD (U.S.A.) I.C.'s

RTL Micrologic Circuits

Qty. prices each	1-11	12-24	25-99	100 +
Ep 900 Buffer, To-5 temp range 15°C to 55°C.	8/-	7/-	6/6	6/6
μL 914 Dual two-input GATE	8/-	7/-	6/6	5/6
μL 923 J-K Flip-flop	10/6	10/-	9/6	9/-

Full data and circuits for ICS in Booklet form price 1/6 each.
μA709C Linear RF-IF AMPLIFIER 11/- 10/- 9/- 8/8
PLASTIC CASE TO-6 lead up to 100 m/c.

DTL DIGITAL I.C.'s

DTL dual in-line package.

Price	10/- each	15/- each	10/- each
Type MC844P expandable dual 4-input NAND Power Gate			
Type MC845P Clocked Flip-flop			
Type 882 Triple 3-input NAND/NOR Gate			


FULL DATA SUPPLIED WITH UNITS

Please send all orders direct to our warehouse and despatch department.

BI-PAK SEMICONDUCTORS
P.O. BOX 6, WARE, HERTS.

Postage and packing add 1/- Overseas add extra for Airmail. Minimum order 10/- Cash with order please.

DISCOSOUND

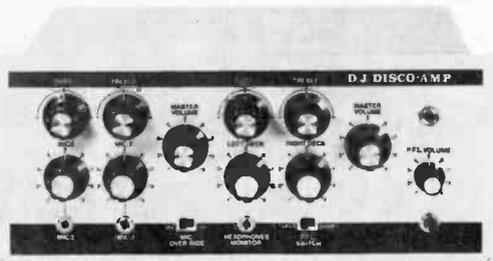

D.J. DISCO-AMP

Designed specifically for use with discotheques and has many exclusive features not normally found on P.A. amplifiers. The unit will be of use to the professional D.J. as well as in clubs and mobile discotheques.

A complete Pre-fade listen (P.F.L.) cueing monitor section is featured with separate input for headphones (either stereo or mono) with an independent volume control for headphone monitoring, and a P.F.L. switch, so that either turntable can be monitored for accurate cueing up of records. A mic over-ride switch is also added which cuts the music volume by half.

Specification: Output power 70 watts R.M.S. \pm 1db at 8 ohms. Frequency response: 30-20,000 Hz \pm 3db. Harmonic distortion: Less than 1% at full output. Signal/noise ratio: Better than -65db. Inputs: Mic 1 & 2 5 mV at 50 K ohms. Turntable 1 & 2 100mV at 1 meg ohm.

50 ohm or 600 ohm mic inputs may be ordered at extra cost. Size: Front Panel 16 $\frac{1}{2}$ in x 7in. Cut out 15 $\frac{1}{2}$ in x 6in. Fuses A.C. 1.5 amp (B.S.) mounted on back panel.

PRICE £85.0.0 inc. P & P.



D.J. 102 DISCOTHEQUE MIXER PRE-AMPLIFIER

Consists of a 4 channel mixer each with its own volume control and a complete P.F.L. monitoring system. Also features a mike cut down switch. For use with amplifiers having tone controls but not having the above facilities. Frequency response 20-20,000 Hz \pm 2db. Distortion less than 1%. Signal to noise ratio better than -65db. Size 10 $\frac{1}{2}$ in x 4in x 4in. Self Powered.

PRICE £25.0.0 inc. P & P.

DJ 30L PSYCHEDELIC LIGHT CONTROL UNIT

3 channel light control unit that handles up to 1,000 watts per channel. Separate bass, middle and treble controls for full frequency separation. Completely built and tested



PRICE £37.10.0 inc. P & P.

For full details of these and all Discosound Products write direct to:-

DISCOSOUND,

122 BALLS POND ROAD, LONDON, N.1.
Telephone: 01-254 5779

Full money back guarantee if returned within 10 days.
All Discosound Products are guaranteed for 12 months.
Demonstrations given at any time.

Mullard TECHNICAL BOOKS

Power Engineering using Thyristors

Part 1. Techniques of Thyristor Power Control

A new book to bridge the gap between electrical power engineering and electronics.

Including postage 32/-

Data Book 1970

Gives Mullard abridged data on valves, picture tubes, semiconductors and components used in consumer electronics.

Paper bound. Including postage 4/9

Transistor Audio and Radio Circuits

For radio receivers, radiograms, record players, tape recorders, hi-fi equipment.

Over 200 pages packed with the most up to date information.

Bound in cloth. Including postage 32/-

Electronic Counting Circuits. Techniques. Devices.

The increasing use of mechanization and automation in factories has given rise to an increased interest in counting. This present book is intended to help engineers to use electronics to solve their counting problems as simply or as cheaply as possible.

220 pages fully illustrated. With diagrams.

Including postage 29/-

Semiconductor Devices

This book is an introduction to Semiconductor Electronics and its contents should be readily understood. The subject is treated non-mathematically. Numerous illustrations and diagrams. Including postage 8/6.

A programmed book on Semiconductor Devices

This book is an integral programme which is a form of self instructional text.

Size 12ins. x 8ins. Numerous illustrations and diagrams. Including postage 14/-

Magnadur magnets for dc motors

Magnadur is a ceramic magnetic material characterised by an exceptionally high coercive force and extremely high resistivity. The book deals solely with the use of permanent magnets in D.C. motors. Bound in board. Numerous illustrations and diagrams. Including postage 16/6.

Post now to: Dept. M
SELRAY BOOK COMPANY
60 Hayes Hill Bromley BR2 7HP

BRAND NEW

SEMICONDUCTORS & COMPONENTS

SOLE AGENTS FOR SOLID STATES DEVICES INC., (USA), IN U.K.

GUARANTEED

TRANSISTORS

Table listing various transistor models (e.g., 2G301, 2G302) with their specifications and part numbers.

PANEL METERS

38 Series—FACE SIZE 42 x 42mm. All prices for 1-9 pieces. 50µA, 37/6; 100µA, 35/-; 200µA, 32/6; 500µA, 27/6; 50-0-50µA, 35/-; 100-0-100µA, 32/6; 500-0-500µA, 25/-; 1MA, 25/-; 5MA, 25/-; 10MA, 25/-; 50MA, 25/-; 100MA, 25/-; 500MA, 25/-; 1A, 25/-; 5A, 25/-; 10V 25/-; 20V, 25/-; 50V, 25/-; 300V, 25/-; 500V, 25/-.

SILICON RECTIFIERS

Table listing silicon rectifier specifications including PIV, IA, 3A, 6A, 10A, 17A and their corresponding prices.

DIODES & RECTIFIERS

Table listing diode and rectifier models (e.g., IN461, IN914, 1N4007) and their prices.

INTEGRATED CIRCUITS

Table listing integrated circuit models (e.g., CA3000, CA3005, CA3007) and their prices.

Data and application sheets 2/- per type. Motorola MC724P 13/3, MC799P 13/3, MC780P 49/5, MC838P 109/9, MC788P 16/6, MC1303P 54/-, MC789P 13/3, MC1304P 72/-, MC750P 24/9, MC1552G 92/2, MC792P 18/-.

Can now offer the whole range of Motorola I.C.'s and most of the RCA, Mullard, Siemens and G.E. I.C.'s at Industrial Consumer prices.

Our stocks and range of I.C.s are continually expanding and we invite queries for types not show from Enthusiasts and Industrial users.

Table listing TRIACS models (e.g., TAA241, TAA243, TAA263) and their prices.

THYRISTORS

Table listing thyristor specifications including PIV, IA, 3A, 6A, 7A, 25A and their prices.

VEROBOARD

Table listing Vero Board specifications including Matrix and prices.

HEAT SINKS

4-8 x 4 x 1in Finned for Two TO-3 Trans, 9/6; 4-8 x 2 x 1in Finned for One TO-3 Trans, 6/6; For 80-64 for TO-5, 1/-; Finned, For TO-18, 1/-; Finned, For TO-18, 1/-; Finned.

RESISTORS

Carbon Film 1 watt 5%, 3d; 1 watt 5%, 4d; 1 watt 5%, 5d; 1 watt 10%, 6d; 2 watt 10%, 1/3.

CAPACITORS

A large and comprehensive range available: Electrolytic, Polyester, Ceramic, Polystyrene, Silver Mica, Tantalum, Trimmers, Tuners. Examples: 2,000mF 25V, 8/6; 2,500mF 50V, 13/6; 3,000mF 25V, 10/6; 5,000mF 50V, 19/6.

POTENTIOMETERS

Carbon: Log. and Lin., less switch, 3/-; Log. and Lin., with switch, 4/6; Wire-wound, Pots (3W), 5/6; Twin Ganged Stereo Pots, Log. and Lin., 7/6.

PRESETS (CARBON)

0.1 Watt 1/-; 0.2 Watt 1/3; 0.3 Watt 1/6.

THERMISTORS

R53 (STC) 25/6; VA3705 17/6; K151 (1k) 2/6; Mullard Thermistors also in stock. Please enquire.

Post & Packing 1/6d per order. Europe 5/-. Commonwealth (Air) 13/- Send 6d. stamp for price list.

Send 2/6 for our New Comprehensive Catalogue containing Vouchers worth 6/- CALLERS WELCOME HRS. 9-5.30 Mon-Sat

Tel. 01-452 0161/2/3 A. MARSHALL & SON Telex 21492 28 CRICKLEWOOD BROADWAY, LONDON, N.W.2

BRAND NEW ARSDD COMMUNICATIONS RECEIVERS. AC mains input 110 volts or 250 volts. Frequency in 6 bands 835 kc/s up to 32 mc/s, output impedance 2.5-400 ohms. Complete with crystal filter noise limiter B.F.O. HF tone controls. Price £80 including spare set of valves, headphones and manual.

COMPUTER BOARDS Min 30 transistors and diodes and res. etc. 10 boards at 10/- plus 2/6 p.p.; 25 boards at £2/6 plus 4/6 p.p.

BARGAIN PARCELS 14lb at 2/- plus 6/6 p.p.; 28lb at 5/- plus 12/6 p.p.; 56lb at 9/- plus 25/- p.p. Contain pots, Res., Valves, Diodes, Tackboards, Chassis, Valveholders, etc. Good value save £25. Lucky Dip Service.

FURZHILL BEAT FREQUENCY OSCILLATOR 0-10 kc/s. 110/250 volt. Good condition complete with spares. £5.10.0 plus 25/- p.p.

VHF Receiver. Type 715, less crystal 60-100 Mc/s can be operated on 2 or 4 meters or made tunable 12 volt input, not tested; complete with valves and speaker. £3.0.0 plus £1 p.p.

VHF AERIAL TUNING UNITS consisting of the following: 1-1 1/2" 500 micro/ampmeter. 1 small 2-gang 75 PF capacitor. 1 various large wattage resistors for dummy load. Part gear R.N.C. type sockets. Will tune 10 mtrs. with 25/30 watts R.F. input. Size only 3 1/2" x 4 1/2" x 3 1/2". Sealed. Price 27/6 p.p. 5/-.

CRYSTALS AS NEW: Hc 6n, 5,340; 5,000; 5,005; 4,945; 4,875; 4,840; 4,795; 4,580; 4,660; 4,520; 4,510; 2,300; 2,295 Kc/s and 10 x J465 Kc/s. 10/- each plus 1/6 p.p.

SCOOP PURCHASE OF BRAND NEW CARBON RESISTORS. 10% tolerance 1/2 & 1 watt. Preferred values in packets of 10. Our price 10/- per 100, 19/- per 200, 27/- per 300, 50/- at 42/8. Our selection. p.p. 1/6 per 100 and 6d. per extra 100.

TRIMMER BARGAINS. These are 10PF sub-min. air-spaced trimmers on board with min. wire ended Xtal. Brand new. No details: Contents 3RD trimmers, some ceramic caps. Xtal frequency CR12 overtones 248 mc/s-250 Mc/s, 255 Mc/s. No choice.

Trimmers without Xtal — 12/- per doz. plus 3/6 p.p.
Trimmers with Xtal — 15/- per doz. plus 3/6 p.p.
Also 20 PF min. brand new air spaced.

NEW TOGGLE SWITCHES. 250 volt 3-5 amps. 2 pole 2 way. 12/6 dozen, 2/6 post and packing.

SIGNAL GENERATORS OSCILLATOR No. 2. Size 12in. x 8 1/2in. x 9in. Ideal for VHF work. 20-80 Mc/s. Functions are AM/CW. Deviation up to 40 Kc/s RF meter. Measuring levels. RF output 1 microvolt to 100 microvolts set. Mod-set carrier controls. Good condition with accessories. 230V AC 12V DC. £20.0.0 plus 15/- p.p.

TF 144 G Signal Generators 85 Kc/s to 25 Mc/s. Good condition and complete with accessories. £22.0.0 plus 30/- p.p.

AERIALS. New Condition. Whelp type lift 12/6 each. Used condition 12ft 10/- each. All collapsible type. Post and packing 3/6. Bases for the above 5/-, post and packing 2/6.

TELESCOPIC MASTS. New condition, 20ft closes to 5ft 9in. 90/-, carriage 15/-; 34ft closes to 5ft 9in 120/-, carr. 15/-; Used condition, 20ft 70/-, 34ft 80/-, carr. 15/-; Base for same 20/-, carr. 7/6.

New lengths 50ft Coaxial cable 70 ohms (approx.), coax plus each end. price 20/- each post and packing 2/6.

Magnetic Transducers new. price 7/6 post and packing 2/-.

New Aerial Wire on boards 7/22 uncovered. Length 75ft 8/- post and packing 2/6.

New small fuse boxes 250 volts 15 amps. 17/6 each post and packing 3/-.

Meters, moving coil ex equipment, good condition. Also 15 Amp DC, 20 Amp DC, 40 Amp DC. And R.F. Thermo Couple Meters 0-1 Amp, 2in diameter 10/-, post and packing 5/-.

C.W.O. CARRIAGE CHARGES MAINLAND ONLY.

A. H. THACKER,
Radio Dept.,
HIGH STREET, CHESLYN N.,
Nr. Walsall, Staffs.

NEW RANGE U.H.F. TV AERIALS

All U.H.F. aerials now fitted with tilting bracket and 4 element grid reflectors.
Loft Mounting Arrays. 7 element 45/-, 11 element 52/6, 14 element 60/-, 18 element 70/-, Wall Mounting with Cranked Arm. 7 element 65/-, 11 element 75/-, 14 element 82/6, 18 element 90/- Chimney Mounting Arrays complete. 7 element 80/-, 11 element 87/6, 14 element 95/-, 18 element 105/-.
Complete assembly instructions with every aerial. Low Loss co-axial cable 1/8 yd. King Teleboosters—Labreg U.H.F. Boosters from 75/-, Belling Lee 'Concord' All Band V.H.F./U.H.F. mains operated pre-amp £7.10.0. State clearly channel number required on all orders. p.p. Aerials 8/-, Accessories 3/-, C.W.O. or C.O.D.

BBC - ITV - FM AERIALS



B.B.C. (Band 1) Loft. 25/-, Wall S/D. 32/6. 'H' array 60/-, I.T.V. (Band 3) 5 element loft array 45/-, 7 element 55/-, Wall mounting 5 element 65/-, Combined BBC/ITV loft 1 + 5 55/-, 1 + 7 67/6, Wall mounting 1 + 5 77/6, Chimney mounting 1 + 5 90/-, Preamps from 75/-, Combined BBC/ITV/BBC2 Aerials. 1 + 5 + 9 80/-, 1 + 5 + 14 90/-, 1 + 7 + 14 100/-, Available loft only. F.M. Radio Loft S/D 19/6. 'H' 38/6, 3 element array 57/6. Standard co-axial cable 1/- yd. Coax plus 1/8. Outlet boxes 6/-, Diplexer crossover boxes 17/6, p.p. Aerials 8/-, accessories 3/-, C.W.O. or C.O.D. (min. C.O.D. charge 3/6). 1/- for fully illustrated Lists.

Callers welcomed—open all day Saturday.

K.V.A. ELECTRONICS (Dept. P.W.)
40-41 MONARCH PARADE,
LONDON ROAD, MITCHAM,
SURREY 01-648 4884

REC. PRICE £42.
OUR PRICE 36 gns.
(CASH ONLY) plus 9/- p.p.
Complete with standard
batteries and earpiece
BFO (OPTIONAL EXTRA)
ADD 35/-

THE NEW "JULIETTE" MPR 3065 (replaces the NA 5018A) IS A HIGH QUALITY COMMUNICATIONS RECEIVER



It NOT ONLY receives Aircraft, Shipping (VHF & SW), Taxis, Ambulances, Fire Service, T.V. Sound, Hama, Gas and Electricity Boards, Public Services and many other Radio Telephone Mobiles. BUT ALSO Classical Music, and all that Jazz.

TURN ON AND TUNE IN!!!
The MPR 3065 is a communications receiver and entertainment source in one neat, transistorised, portable package. It keeps Aircraft, Shipping, RT Mobiles, FM & AM Broadcasts at your fingertips.

Features a colour coded illuminated tuning dial and band selector, AFC, squeeze, BFO (optional extra) Large Speaker, Works off Mains or Batteries. Size: 10 1/2 x 7 1/4 x 4 inches.

FREQUENCIES: Medium Wave 540-1800 Kcs; Marine 1.6-4.6 Mcs; FM/VHF 88-108 Mcs; Aircraft 109-138 Mcs (Military, Civil & Ground Control); High VHF/PB 146-176 Mcs (Commercial & Industrial RT Mobiles). Availability of Mobile transmissions depend on operators in each area.

STOCKTON PARTNERS (DEPT. PW)
BRIGHOWGATE, GRIMSBY, Lincs.
Tel: 0472 64196/58815
Importers & Distributors

AUDIO EFFECTS

5 SHAW LANE, HALIFAX YORKS

Buy with confidence and obtain the right results. Refunds without question if any of our products fail to give 100% satisfaction.
AMATEUR BANDS ALL TRANSISTOR SUPERHET RECEIVER KIT. No fuss, no drilling. Just fit the components on our printed circuit. Slow Motion tuning. Simple IF alignment. Perspex front panel. Push pull AF amp drives your 8-15 ohm speaker. Amp can be used separately. Designed to accept a BFO signal. Uses Denco valves in coils 2T, 0.5 to 1.54 Mhz ST, 1.67 to 5.3 Mhz 4T; 5.0 to 15 Mhz ST, 10.5 to 31.5 Mhz Range 3T normally supplied with kit. Uses 9 volt battery. Easy step by step instructions. Complete Kit. £8.19.6 plus 5/6 P. P. & Ins. Extra ranges 12/- per range.

POWER CONTROLLER. Power at your finger tips. Not merely half watt control but full watt. A single variable control gives zero to full power. Uses latest 15 amp 3KW triac and special triggering device. Ideal for all types of lighting, fires, motors, drills, etc. Complete with box, power socket, cables, etc. In kit form with easy to follow instructions £6.9.6. Ready built £9.4.6 plus 5/6 P. P. & Ins.
REVERBERATION AMPLIFIER. Self contained transistorised, battery operated. An entirely different approach to sound reproduction. Normally, sound reproduction from a single source, has a flat one dimensional effect. With this unit, proper sound delay through reverberation, tones, are created with a truly third dimension for concert hall originality. Two controls adjust volume and reverberation. Simply plug microphone, guitar, etc., in, and the output into your amplifier. Supplied in a beautiful walnut cabinet 7 1/2in x 3in x 4 1/2in. £10.4.0 plus 6/- P. P. & Ins.

VOX SWITCH. This sound operated switch is ideal for mobile TX work, tape recorder switching, etc. You speak, it switches. High and medium imp. inputs. AF take off point. Drives your 12 volt relay. In kit form with full instructions 47/6. Ready built, tested and guaranteed. 67/6, plus 2/6 P. P.

METRONOME UNIT. Variable beat. Listen while you play and keep in time. Easily built, pocket size with personal mini earphone. In kit form 27/6, post paid. Ready built in an attractive polythene case, 37/6 post paid.
MORSE OSCILLATOR. PC board, transistors, high stab. components, battery carrier, car piece. Adjustable tone. Just attach your key. Drives phones or speaker. In kit form 17/6 post paid. Ready built in similar case as above 25/- post paid.

STRAIGHT FROM THE PRESS. Latest Mullard manual: Audio Amps, FM tuners. Stereo decoder, Receiver circuits, Hi Fi Tape, etc. etc. 32/6 post paid.
Texas transistors. Complementary symmetry. Driver. NPN, PNP output. The set of three ONLY 6/6 post paid.

NEW VALVES!

Guaranteed and Tested
24-HOUR SERVICE

IR5	5/8	DL55	4/9	EL33	9/3	FL36	9/3
185	4/3	DL92	5/8	EL84	4/9	PL81	9/3
174	2/9	DL94	6/8	EM34	13/9	PL82	5/9
384	5/9	DL96	7/8	EY31	7/-	PL83	6/3
3V4	6/8	DY86	5/3	EY86	6/3	PL84	6/3
6/30L2	11/6	DY87	5/3	EZ80	4/8	PL500	12/9
6A4Q5	5/-	EAB80	6/3	EZ81	4/8	PL504	13/3
4P25	12/-	EB91	2/-	KT61	9/3	PY32	10/6
6SN7GT	4/-	EB33	7/9	KT66	16/6	PY33	10/6
25L6GT	4/6	EBF89	6/-	N78	17/6	PY81	5/6
30CL18	12/9	ECC81	3/6	PC86	9/9	PY82	5/6
30FL1	12/6	ECC82	4/-	PC88	9/9	PY800	7/6
30L15	12/9	ECC83	4/9	PC97	7/8	PY801	7/6
30P4	12/-	ECP80	5/9	PC900	7/-	R19	6/3
30P19	12/-	ECP82	5/9	PC84	6/3	UP5	12/9
30P11	12/3	ECH35	5/6	PC89	9/3	UP2	11/8
30PL14	14/-	ECH81	5/9	PC189	9/6	U191	12/6
30PL14/13/6	13/6	ECL80	7/6	PCF80	5/11	U251	14/-
CC135	13/-	ECL83	6/3	PCF86	9/7	U329	14/-
DAC2	6/9	ECL86	7/6	PCF801	6/6	UAC800	6/6
DAF91	4/3	EF39	4/6	PCF82	9/9	UBF99	6/3
DAF96	7/6	EF80	4/6	PCF805	12/9	UC085	7/3
DF33	7/6	EF85	5/9	PCF806	11/-	UC81	6/6
DF91	2/9	EF86	6/3	PCL82	6/9	UC82	6/9
DF96	7/-	EF89	4/9	PCL83	10/6	UF89	6/6
DK32	6/9	EF91	2/6	PCL84	7/-	UL84	6/8
DK91	5/6	EF183	5/6	PCL85	6/6	UL11	7/6
DK92	8/3	EF184	6/3	PC86	8/3	UY85	5/9
DK96	7/3	EH90	7/3	PFL20011/6	6/6	Z77	3/9

Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra. Any insured parcel against damage in transit 6d. extra. Office address, no callers.

GERALD BERNARD
83 OSBALDESTON ROAD
STOKE NEWINGTON
LONDON, N.16

ELECTROVALUE

EVERYTHING BRAND NEW & TO SPECIFICATION • LARGE STOCKS

BARGAINS IN NEW SEMICONDUCTORS all power types supplied with free insulating sets

1N914	1/3	2N3706	3/3	40512	45/8	BC147	3/6	BFY51	4/3
1N9754	4/-	2N3707	4/-	40802	9/8	BC148	3/3	BHX20	3/9
1N4148	1/9	2N3708	3/-	AC107	14/8	BC149	3/8	BY164	10/-
1N6054	4/-	2N3709	3/-	AC126	6/6	BC153	10/-	BY238	3/8
18940	1/2-	2N3710	3/6	AC127	6/-	BC154	11/-	C106B1	14/6
2N696	6/6	2N3711	3/11	AC128	6/-	BC157	3/9	MC140	5/-
2N697	5/8	2N3731	24/-	AC176	11/-	BC158	3/8	MJ480	21/-
2N706	2/9	2N3794	3/3	ACY22	3/9	BC159	3/9	MJ481	27/-
2N1302	4/-	2N3819	8/8	ACY40	4/-	BC167	2/8	MJ491	30/-
2N1303	4/-	2N3820	25/6	ACY41	5/-	BC168	2/3	MPP102	7/8
2N1304	4/6	2N3904	7/8	AD142	14/3	BC169	2/6	NKT403	15/8
2N1305	4/6	2N3906	7/8	AD149	17/8	BC177	6/3	NKT405	15/-
2N1306	6/9	2N4058	5/3	AD161/AD162		BC178	5/8	OA47	1/9
2N1307	6/9	2N4059	4/-	(matched) 16/-	pr	BC179	6/-	OA90	1/3
2N1308	8/9	2N4060	4/3	AF114	7/-	BC182L	4/3	OA91	1/3
2N1309	8/9	2N4061	4/3	AF115	7/-	BC183L	2/3	OA95	1/3
2N1613	6/-	2N4062	4/3	AF116	6/6	BC184L	2/6	OA99	3/-
2N1711	7/-	2N4284	3/3	AF117	6/8	BC186	8/8	OA900	1/11
2N2147	18/9	2N4286	3/3	AF124	7/8	BC212L	5/-	OA902	2/-
2N2218	9/3	2N4289	3/3	AF127	7/-	BC213L	6/-	OC71	5/6
2N2270	12/9	2N4291	3/3	AF130	9/6	BC214L	5/3	TIP31A	17/8
2N2484	13/8	2N4292	3/3	AF180	18/6	BCY70	5/8	TI132A	23/9
2N2646	10/9	2N4410	4/9	AF239	9/9	BD121	18/-	TI843	10/8
2N2904	11/-	2N5062	12/3	ABY26	6/8	BD123	24/3	ZTX300	3/6
2N2924	4/-	2N5163	5/-	ABY27	8/3	BD124	16/-	ZTX301	3/8
2N2925	4/6	2N5192	25/-	ABY28	6/8	BF167	8/6	ZTX302	4/6
2N2926	2/3	2N5195	28/3	B5041	15/-	BF178	10/6	ZTX303	4/8
2N2953	5/8	2N5457	9/9	BA102	9/-	BF180	12/-	ZTX304	6/9
2N3054	7/3	2N5458	9/9	BA156	4/-	BF194	7/3	ZTX500	5/-
2N3055	16/-	2N5459	9/9	BA130	4/8	BF195	10/9	ZTX501	5/-
2N3225	10/9	40250	14/3	BA145	5/6	BFX29	7/5	ZTX503	6/-
2N3663	11/8	40361	12/8	BC107	2/8	BFX64	8/3	ZTX504	5/-
2N3702	3/8	40362	16/-	BC108	2/8	BFX86	8/3	ZTX504	12/-
2N3703	3/3	40406	16/3	BC109	2/9	BFX87	8/6	ZTX530	5/5
2N3704	3/9	40408	14/6	BC125	12/-	BFX88	6/9	ZTX531	6/9
2N3705	3/5	40430	37/-	BC126	12/-	BFY50	4/8		

RESISTORS

Code	Power	Tolerance	Range	Values available	1 to 9	10 to 99 (see note below)	100 up
C	1/20W	5%	82 Ω-220K Ω	E12	15	16	15
C	1/8W	5%	4.7 Ω-330K Ω	E24	2.8	2	1.75
C	1/4W	10%	4.7 Ω-10M Ω	E12	2.5	2	1.75
C	1/2W	5%	4.7 Ω-10M Ω	E24	3	2.5	2.25
C	1W	10%	4.7 Ω-10M Ω	E12	6	5	4.5
MO	1/2W	2%	10 Ω-1M Ω	E24	9	8	7
WW	1W	10% ± 1/20 Ω	0.22 Ω-3.9 Ω	E12		15d all quantities	
WW	3W	5%	12 Ω-10K Ω	E12		15d all quantities	
WW	7W	5%	12 Ω-10K Ω	E12		15d all quantities	

Codes: C = carbon film high stability low noise
MO = metal oxide Electrolytic TR5 ultra low noise
WW = wire wound Plessey.

Values:
E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades.
E24 denotes series: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

INTEGRATED CIRCUIT AMPLIFIERS

SINCLAIR IC10 complete with instruction book giving amplifier circuit details and range of applications. 59/8 nett.

PLESSEY SL403A Now only 42/8 nett 3W into 7.5 Ω for 18V supply. Application data sent with two more.

WAVELENGTH SWITCHES LONG SPINDLES

1P 12W: 2P 6W: 3P 4W: 4P 3W 4/9 each
SLIDER SWITCHES D.P.D.T. 3/- each

NEON INDICATOR LAMPS

all 200/250V. Square bezel, red only 3/9
Round chrome bezel red, amber, clear 4/9 each

Toggle switches, 250V a.c. 1.5A.
chrome dolly and chrome milled nut S.P.S.T. 3/9; S.P.D.T. 4/8; D.P.D.T. 5/8; S.P.D.T. Centre off 5/-.

S-Dec's put an end to "birdnesting". Components just plain in. Saves valuable time. Use components again and again. S-Dec only 30/-, Compact T-Dec, increased capacity, may be temperature-cycled. T-Dec only 50/- post free. Full range stocked.

MULLARD polyester C280 series

250V 20%: 0.01; 0.022; 0.033; 0.047 8d ea. 0.068; 0.1 8d ea., 0.15 11d., 0.22 1/-, 10%: 0.33 1/5, 0.47 1/8, 0.68 2/3, 1µF 2/8, 1.5µF 4/2, 2.2µF 4/9.

MULLARD SUB-MIN ELECTROLYTIC

C428 range axial lead 1/3 each
Values (µF/V): 0.64/64; 1/40; 1.6/25; 2.5/16; 2.5/84; 4/10; 4/40; 5/64; 6.4/64; 6.4/25; 8/4; 8/40; 10/2.5; 10/16; 10/84; 12.5/25; 16/40; 20/16; 20/64; 25/64; 25/25; 32/4; 32/10; 32/40; 32/64; 40/16; 40/2.5; 50/6.4; 50/25; 50/40; 64/4; 64/10; 80/2.5; 80/16; 80/25; 100/8.4; 125/4; 125/10; 125/16; 160/2.5; 200/6.4; 200/10; 250/4; 320/2.5; 320/6.4; 400/4; 500/2.5.

LARGE CAPACITORS

High ripple current types: 1000/25 5/8; 1000/50 8/2; 1000/100 16/3; 2000/25 7/4; 2000/50 11/4; 2000/100 28/8; 2500/64 15/5; 2500/70 19/8; 5000/25 12/6; 5000/50 21/11; 5000/100 58/8; 10000/15 17/-; 10000/25 24/8; 10000/50 44/-; 10000/70 61/-.

MEDIUM RANGE ELECTROLYTICS

Axial leads: 50/50 2/-; 100/25 2/-; 100/50 2/8; 250/25 2/8; 330/25 2/8; 250/50 3/8; 500/25 3/8; 500/50 4/8; 1000/25 4/-; 1000/50 6/-; 2000/25 6/-.

SMALL ELECTROLYTICS

Axial leads: 4.7/10; 4.7/25; 5/50 1/- ea. 10/10; 10/25; 10/50, 33/10; 50/10 1/- ea. 22/25; 25/50; 47/25; 100/10; 220/10 1/3 ea.

THE NEW 1970 ELECTROVALUE CATALOGUE

48 pages—thousands of items—packed with information 2/- post free. Add 4/- if sent overseas by air mail.

PEAK SOUND PRODUCTS

ENGLEFIELD CABINET KITS

Build it 12 + 12 or 25 + 25



Stereo Amplifier in modular kit from 12 watts per channel £38/9/-; 25 watts £58/15/- Cabinet kit only £8. These prices nett.
As recently reviewed in Hi Fi Sound.

BAXANDALL SPEAKER SYSTEM

Designed by Peter Baxandall. Superb reproduction for its size. Handles 10 watts with ease. Uses ELAC 15 Ω 59RM109 speaker Unit Kit £13/12/- nett; built £19/8/8 nett.

STEREO AMPLIFIER S.A. 10-10.

Developed from the very successful SA.8-8 amplifier giving first class stereo amplification featuring separate volume controls for each channel, bass and treble controls. 10 watts per channel into 5 to 8 Ω. Kit £19/7/8 nett; built £24/13/8 nett. Suitable 8 Ω wide range speakers with woofer, tweeter & x-over in cabinet available £13/15/- nett.

MAINLINE AMPLIFIER KITS

RCA/808 designed main amplifier kits. Input sensitivity 500-700mV for full output into 8 Ω.
Power Kit price including components Suitable unreg. power supply
12W 188/- nett 92/-
25W 190/- nett N/A
40W 210/- nett 115/1
70W 252/- nett 138/10

30 WATT BAILEY AMP. PARTS

Special summer reduction (to Sept. 30th 1970 only)
Sensitivity 1.2V for full output into 8 Ω
Transistors for one channel £7/5/8 list. £6 only nett.
Transistors for two channels £14/11/- list £11 only nett.
Capacitors and resistors (metal oxide) 30/- per channel nett.
Complete unregulated power supply kit 87/6 nett.

ZENER DIODES

5% full range E24 values: 400mW: 2.7V to 30V 4/8 each
1W: 6.8V to 82V 9/- each 1.5W: 4.7V to 75V 12/- each
Clip to increase 1.5W rating to 3 watts (type 268P) 8d.

CARBON TRACK

POTENTIOMETERS, long spindles
Double wiper ensures minimum noise level.
Single gang linear 220 Ω to 2.2M Ω 2/6
Single gang log 4.7K Ω to 2.2M Ω 2/6
Dual gang linear 4.7K Ω to 2.2M Ω 8/6
Dual gang log 4.7K Ω to 2.2M Ω 8/6
Log/antilog 10K, 47K, 1M Ω only 8/6
Any type with 1A D.P. mains switch, extra 2/3
Please note: only decades of 10, 22 and 47 are available within ranges quoted.

CARBON SKELETON PRE-SETS

Small high quality, type PR, linear only 100 Ω, 250 Ω, 470 Ω, 1K, 2K, 4K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M, 5M, 10M Ω vertical or horizontal mounting 1/4 each.

COMPONENT DISCOUNTS

10% on orders for components for £5 or more. 15% on orders for components for £15 or more (No discount on nett items).

POSTAGE AND PACKING

Free on orders over £2. Please add 1/8 if under. Overseas orders welcome: carriage charged at cost.

ELECTROVALUE

(Dept. PW.10) 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY
Hours: 9—5.30. Sat. 1 p.m. Tel.: Egham 5533 (STD 0784-3) Telex 264475

**Fully guaranteed
Individually packed
VALVES**

Open 9-12.30, 1.30-5.30 p.m. Thursday 9-1 p.m.

MANY OTHERS IN STOCK include Cathode Ray Tubes and Special Valves. U.K. Orders up to 10/-, 1/-; 10/- to £1 2/-; over £1. 2/- per £1; over £3 post free. C.O.D. 4/- extra



**ALL valves
guaranteed**

TRANSISTORS, ZENER DIODES etc.				brand							
CY31 7/-	ECL86 8/-	PC97 8/-	OA5 2/8	OC29 15/-	OC172 7/6	3FR5 6/6	AF118 10/-	CR83/20 10/-	6P25 11/-	19AQ5 7/9	2051 10/-
DAF96 7/9	EF36 3/6	PC90 9/6	OA10 6/-	OC35 8/6	OC200 6/6	3N123 17/8	AF139 10/-	CR83/30 10/-	6BA7 7/-	19G3 70/-	5933 22/6
DF96 7/6	EF37A 7/-	PC94 6/6	OA70 2/-	OC38 8/6	OC201 7/6	3N139 35/-	AF178 12/6	CR825/025 15/-	68A7GT 6/6	19G8 20/-	6057 10/-
DK96 7/6	EF39 6/-	PCC89 9/-	OA71 2/-	OC44 4/-	OC206 10/-	3N140 19/6	AFY19 22/6	6/6	68C7 13/-	19H4 25/-	6060 7/6
DL92 6/6	EF40 10/-	PCC189 11/-	OA79 1/8	OC45 2/6	IN21 3/6	3N154 19/6	ASY26 5/6	CR83/40 12/6	68CTGT 6/6	20P4 15/-	6066 13/6
DL94 8/-	EF41 12/6	PC8800 18/-	OA81 1/8	OC70 3/6	IN21B 5/-	3N159 29/-	ASY28 5/6	GET103 4/6	68G7 6/6	25L6GT 7/6	6064 7/6
DL96 7/6	EF80 5/-	PCF80 6/6	OA200 1/8	OC71 2/6	IN25 12/-	3FR5 7/6	BAW19 5/6	GET115 9/6	68H7 6/6	30P14 15/-	6065 13/6
DM70 6/6	EF83 9/7	PCF82 6/6	OA202 4/-	OC72 4/-	IN43 4/-	12J60 14/6	BC107 3/6	GET116 3/6	68J7 7/6	30C15 15/-	6080 27/6
DM71 7/6	EF85 6/6	PCF84 9/3	OA210 7/6	OC73 11/-	IN70 4/-	10D1 3/6	BC108 4/-	BD918 5/6	68J7GT 6/6	30C17 16/-	6146 28/-
DY86 6/6	EF86 6/6	PCF86 11/6	OA211 9/6	OC75 4/6	IN702-72578 28303	10/-	BCY10 9/-	BD928 5/6	68K7 6/6	30C18 15/-	6020 35/-
DY87 6/6	EF89 5/3	PCF200 15/6	OA2200 11/-	OC76 5/-	IN746A 40594	27/6	BCY72 7/9	BD948 6/6	68L7GT 6/6	30F6 18/9	9001 3/-
DY92 9/9	EP91 3/8	PCF201 15/6	OA2201 10/-	OC81 4/-	series 5/3	40695 27/6	BFY51 4/6	BD968 7/6	68M7GT 6/6	30FL12 18/6	9003 10/-
EB80C/01 27/-	EP92 7/6	PCF801 9/9	OA2202 to 2/-	OC81D 3/-	IN821A 21/-	40636 29/-	BFY52 4/6	BD988 9/6	68Q7 7/9	30FL13 9/3	9004 2/6
EABC80 6/6	EP95 5/6	PCF802 9/9	OA2206 9/6	OC81DM 8/-	IN825A 25/-	40696 29/-	BB1 9/-	V405A 7/6	68Q7GT 7/9	30FL14 15/6	9006 2/6
EAF42 10/-	EP183 6/6	PCF805 14/6	OA2207 9/6	OC82 5/-	I2MT5 7/6	40699 29/-	BB2 9/-	Z Range 9/6	68Q7GT 7/9	30FL15 17/-	C.R. Tubes
EB91 2/-	EP184 7/6	PCF806 13/6	OA2208 to 2/-	OC82DM 3/-	I2MT10 6/6	AC126 4/6	BB2 9/6	Zener diodes 3/6 ea.	68Q7GT 7/9	30FL16 17/-	CR297 22/6
EB91 2/-	EP184 7/6	PCF806 13/6	OA2213 6/6	OC83 3/-	I2T10 12/9	AC128 6/-	BU100 26/-	BYZ13 5/-	68Q7GT 7/9	30FL17 17/-	VCR27 22/6
EB91 2/-	EP184 7/6	PCF806 13/6	OA2223 to 2/-	OC83B 3/-	I2T10 12/9	AC128 6/-	BYZ13 5/-	Z2A range 7/6 ea.	68Q7GT 7/9	30FL18 17/-	VCR517 50/-
EB91 2/-	EP184 7/6	PCF806 13/6	OA2225 to 2/-	OC84 5/-	IN1306 6/6	AC128 6/-	BYZ16 15/-	Z3B range 7/6 ea.	68Q7GT 7/9	30FL19 18/-	VCR517B55/-
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC122 10/-	IN1307 6/6	AC128 6/-	BYZ16 15/-	Z3B range 7/6 ea.	68Q7GT 7/9	30FL20 18/-	VCR517C45/-
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC139 6/6	2N3053 6/6	AD149 11/-	CR81/20 9/6	ZL range 5/- ea.	68Q7GT 7/9	30FL21 17/-	5FP7 26/7
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC140 11/-	2N3054 12/6	AD161 7/-	CR81/30 10/-	ZL range 5/- ea.	68Q7GT 7/9	30FL22 17/-	5FP7 26/7
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC141 11/-	2N3055 12/6	AD162 7/-	CR81/35 11/6	ZL range 5/- ea.	68Q7GT 7/9	30FL23 17/-	5FP7 26/7
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC142 11/-	2N3056 12/6	AD162 7/-	CR81/40 12/6	ZL range 5/- ea.	68Q7GT 7/9	30FL24 17/-	5FP7 26/7
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC143 11/-	2N3057 12/6	AD162 7/-	CR81/45 12/6	ZL range 5/- ea.	68Q7GT 7/9	30FL25 17/-	5FP7 26/7
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC144 11/-	2N3058 12/6	AD162 7/-	CR81/50 12/6	ZL range 5/- ea.	68Q7GT 7/9	30FL26 17/-	5FP7 26/7
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC145 11/-	2N3059 12/6	AD162 7/-	CR81/55 12/6	ZL range 5/- ea.	68Q7GT 7/9	30FL27 17/-	5FP7 26/7
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC146 11/-	2N3060 12/6	AD162 7/-	CR81/60 12/6	ZL range 5/- ea.	68Q7GT 7/9	30FL28 17/-	5FP7 26/7
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC147 11/-	2N3061 12/6	AD162 7/-	CR81/65 12/6	ZL range 5/- ea.	68Q7GT 7/9	30FL29 17/-	5FP7 26/7
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC148 11/-	2N3062 12/6	AD162 7/-	CR81/70 12/6	ZL range 5/- ea.	68Q7GT 7/9	30FL30 17/-	5FP7 26/7
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC149 11/-	2N3063 12/6	AD162 7/-	CR81/75 12/6	ZL range 5/- ea.	68Q7GT 7/9	30FL31 17/-	5FP7 26/7
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC150 11/-	2N3064 12/6	AD162 7/-	CR81/80 12/6	ZL range 5/- ea.	68Q7GT 7/9	30FL32 17/-	5FP7 26/7
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC151 11/-	2N3065 12/6	AD162 7/-	CR81/85 12/6	ZL range 5/- ea.	68Q7GT 7/9	30FL33 17/-	5FP7 26/7
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC152 11/-	2N3066 12/6	AD162 7/-	CR81/90 12/6	ZL range 5/- ea.	68Q7GT 7/9	30FL34 17/-	5FP7 26/7
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC153 11/-	2N3067 12/6	AD162 7/-	CR81/95 12/6	ZL range 5/- ea.	68Q7GT 7/9	30FL35 17/-	5FP7 26/7
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC154 11/-	2N3068 12/6	AD162 7/-	CR81/100 12/6	ZL range 5/- ea.	68Q7GT 7/9	30FL36 17/-	5FP7 26/7
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC155 11/-	2N3069 12/6	AD162 7/-	CR81/105 12/6	ZL range 5/- ea.	68Q7GT 7/9	30FL37 17/-	5FP7 26/7
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC156 11/-	2N3070 12/6	AD162 7/-	CR81/110 12/6	ZL range 5/- ea.	68Q7GT 7/9	30FL38 17/-	5FP7 26/7
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC157 11/-	2N3071 12/6	AD162 7/-	CR81/115 12/6	ZL range 5/- ea.	68Q7GT 7/9	30FL39 17/-	5FP7 26/7
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC158 11/-	2N3072 12/6	AD162 7/-	CR81/120 12/6	ZL range 5/- ea.	68Q7GT 7/9	30FL40 17/-	5FP7 26/7
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC159 11/-	2N3073 12/6	AD162 7/-	CR81/125 12/6	ZL range 5/- ea.	68Q7GT 7/9	30FL41 17/-	5FP7 26/7
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC160 11/-	2N3074 12/6	AD162 7/-	CR81/130 12/6	ZL range 5/- ea.	68Q7GT 7/9	30FL42 17/-	5FP7 26/7
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC161 11/-	2N3075 12/6	AD162 7/-	CR81/135 12/6	ZL range 5/- ea.	68Q7GT 7/9	30FL43 17/-	5FP7 26/7
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC162 11/-	2N3076 12/6	AD162 7/-	CR81/140 12/6	ZL range 5/- ea.	68Q7GT 7/9	30FL44 17/-	5FP7 26/7
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC163 11/-	2N3077 12/6	AD162 7/-	CR81/145 12/6	ZL range 5/- ea.	68Q7GT 7/9	30FL45 17/-	5FP7 26/7
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC164 11/-	2N3078 12/6	AD162 7/-	CR81/150 12/6	ZL range 5/- ea.	68Q7GT 7/9	30FL46 17/-	5FP7 26/7
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC165 11/-	2N3079 12/6	AD162 7/-	CR81/155 12/6	ZL range 5/- ea.	68Q7GT 7/9	30FL47 17/-	5FP7 26/7
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC166 11/-	2N3080 12/6	AD162 7/-	CR81/160 12/6	ZL range 5/- ea.	68Q7GT 7/9	30FL48 17/-	5FP7 26/7
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC167 11/-	2N3081 12/6	AD162 7/-	CR81/165 12/6	ZL range 5/- ea.	68Q7GT 7/9	30FL49 17/-	5FP7 26/7
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC168 11/-	2N3082 12/6	AD162 7/-	CR81/170 12/6	ZL range 5/- ea.	68Q7GT 7/9	30FL50 17/-	5FP7 26/7
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC169 11/-	2N3083 12/6	AD162 7/-	CR81/175 12/6	ZL range 5/- ea.	68Q7GT 7/9	30FL51 17/-	5FP7 26/7
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC170 11/-	2N3084 12/6	AD162 7/-	CR81/180 12/6	ZL range 5/- ea.	68Q7GT 7/9	30FL52 17/-	5FP7 26/7
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC171 11/-	2N3085 12/6	AD162 7/-	CR81/185 12/6	ZL range 5/- ea.	68Q7GT 7/9	30FL53 17/-	5FP7 26/7
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC172 11/-	2N3086 12/6	AD162 7/-	CR81/190 12/6	ZL range 5/- ea.	68Q7GT 7/9	30FL54 17/-	5FP7 26/7
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC173 11/-	2N3087 12/6	AD162 7/-	CR81/195 12/6	ZL range 5/- ea.	68Q7GT 7/9	30FL55 17/-	5FP7 26/7
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC174 11/-	2N3088 12/6	AD162 7/-	CR81/200 12/6	ZL range 5/- ea.	68Q7GT 7/9	30FL56 17/-	5FP7 26/7
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC175 11/-	2N3089 12/6	AD162 7/-	CR81/205 12/6	ZL range 5/- ea.	68Q7GT 7/9	30FL57 17/-	5FP7 26/7
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC176 11/-	2N3090 12/6	AD162 7/-	CR81/210 12/6	ZL range 5/- ea.	68Q7GT 7/9	30FL58 17/-	5FP7 26/7
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC177 11/-	2N3091 12/6	AD162 7/-	CR81/215 12/6	ZL range 5/- ea.	68Q7GT 7/9	30FL59 17/-	5FP7 26/7
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC178 11/-	2N3092 12/6	AD162 7/-	CR81/220 12/6	ZL range 5/- ea.	68Q7GT 7/9	30FL60 17/-	5FP7 26/7
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC179 11/-	2N3093 12/6	AD162 7/-	CR81/225 12/6	ZL range 5/- ea.	68Q7GT 7/9	30FL61 17/-	5FP7 26/7
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC180 11/-	2N3094 12/6	AD162 7/-	CR81/230 12/6	ZL range 5/- ea.	68Q7GT 7/9	30FL62 17/-	5FP7 26/7
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC181 11/-	2N3095 12/6	AD162 7/-	CR81/235 12/6	ZL range 5/- ea.	68Q7GT 7/9	30FL63 17/-	5FP7 26/7
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC182 11/-	2N3096 12/6	AD162 7/-	CR81/240 12/6	ZL range 5/- ea.	68Q7GT 7/9	30FL64 17/-	5FP7 26/7
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC183 11/-	2N3097 12/6	AD162 7/-	CR81/245 12/6	ZL range 5/- ea.	68Q7GT 7/9	30FL65 17/-	5FP7 26/7
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC184 11/-	2N3098 12/6	AD162 7/-	CR81/250 12/6	ZL range 5/- ea.	68Q7GT 7/9	30FL66 17/-	5FP7 26/7
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC185 11/-	2N3099 12/6	AD162 7/-	CR81/255 12/6	ZL range 5/- ea.	68Q7GT 7/9	30FL67 17/-	5FP7 26/7
EB91 2/-	EP184 7/6	PCF806 13/6	OC16 18/-	OC186 11/-	2N3100 12/6						

give your car a present

The 1971 edition of the **PRACTICAL MOTORIST ANNUAL** is on sale Wednesday, October 14. Its 136 pages of authoritative and lavishly illustrated articles cover every aspect of car maintenance, overhauls, preservation, accessories and holiday motoring—as well as advice on driving safely through adverse conditions such as fog and floods.

PRACTICAL MOTORIST ANNUAL 1971 is an ideal reference book for every family motorist—and truly excellent value for only 5/- (25p)

PRACTICAL MOTORIST ANNUAL

1971

AN UNIQUE REFERENCE BOOK
FOR EVERY CAR OWNER
ON SALE 12th OCTOBER 5/- (25p)

Now! A FAST EASY WAY TO LEARN BASIC RADIO AND ELECTRONICS



Build as you learn with the exciting new **TECHNATRON** Outfit! No mathematics.

No soldering—but you learn the *practical* way.

Now you can learn basic Radio and Electronics at home—the *fast*, modern way. You can give yourself the essential technical 'know-how' sooner than you would have thought possible—read circuits, assemble standard components, experiment, build . . . and enjoy every moment of it. B.I.E.T.'s Simplified Study Method and the remarkable new **TECHNATRON** Self-Build Outfit take the mystery out of the subject—make learning *easy and interesting*.

Even if you don't know the first thing about Radio now, you'll build your own Radio set within a month or so!

. . . and what's more, **YOU'LL UNDERSTAND EXACTLY WHAT YOU ARE DOING**. The Technatron Outfit contains everything you need, from tools to transistors . . . even a versatile Multimeter which we teach you how to use. You need only a little of your spare time, the cost is surprisingly low and the fee may be paid by convenient monthly instalments. You can use the equipment again and again—and it remains your own property.

You LEARN—but it's as fascinating as a hobby.

Among many other interesting experiments, the Radio set you build—and it's a good one—is really a bonus; this is first and last a *teaching* Course. But the training is as rewarding and interesting as any hobby. It could be the springboard for a career in Radio and Electronics or provide a great new, spare-time interest.

A 14-year-old could understand and benefit from this Course—but it teaches the real thing. Bite-size lessons—wonderfully clear and easy to understand, practical projects from a burglar-alarm to a sophisticated Radio set . . . here's your chance to master basic Radio and Electronics, even if you think you're a 'non-technical' type. And, if you want to carry on to more advanced work, B.I.E.T. has a fine range of Courses up to A.M.I.E.R.E. and City and Guilds standards.

Send now for free 164-page book. Like to know more about this intriguing new way to learn Radio and Electronics? Fill in the coupon and post it today. We'll send you full details and a 164-page book —'ENGINEERING OPPORTUNITIES'—Free and without any obligation.



**BRITISH INSTITUTE OF
ENGINEERING TECHNOLOGY**
Dept, 372B, Aldermaston Court,
Aldermaston, Reading, RG7 4PF

To: B.I.E.T., Dept. 372B Aldermaston Court,
Aldermaston, Reading, RG7 4PF

I would like to know more about your
Practical Radio & Electronics Course. Please
send me full details and FREE 164-page book.

name.....

address.....

.....age.....



Practical Wireless Classified Advertisements

The pre-paid rate for classified advertisements is 1/8d. per word (minimum order 20/-), box number 1/6d. extra. Semi-displayed setting £5 10s. 0d. per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent *registered post*. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd., Fleetway House, Farringdon Street, London, E.C.4 for insertion in the next available issue.

MISCELLANEOUS

PARAPHYSICAL LABORATORY, Down-ton, Wilts. Fascinating international magazines. S.A.E. for list. Parcel 20s.

ALL THOSE LITTLE ITEMS which you can never find are available from our stock. Also speaker fabrics, BAF wadding, Peerless speakers, cabinet kits, cross-overs. For full details send 9d in stamps to **Audioscan**, Dept. P.W., 4 Princes Square, Harrogate, Yorks.

SOCKETS TO YOU will be a thing of the past, and also plugs and bare wires when you make a quick electrical connection with the revolutionary new Keynerector. Ideal for bench and high speed testing of electrical equipment. . . . a must for the do-it-yourself fan. Send for a leaflet to E.B. Instruments, Dept. PW, 49/53 Pancras Road, London N.W.1. (837 7781). Only 46/6 plus postage.

2 WATT TRANSISTOR AMPLIFIERS (not a kit). Standard 3 ohm output. Frequency response ± 2 db from 12 to 12000 cps, on board measuring $2\frac{1}{2}$ x $3\frac{1}{2}$ in. Ideal record players, etc., 22s 6d each, pp 1s 6d. A. Manley, 13 Randisbourne Gardens, Bromley Road, London, S.E.6.

TOP TRANSISTORS

ACY22 1/9	OC72 1/9	2N2926 1/9
BC168 1/9	OC200 1/9	2N3702 1/9
BC169 1/9	OC201 1/9	2N3703 1/9
BSY27 1/9	OC202 1/9	2N3705 1/9
OC45 1/9	ZTX300 1/9	2N3706 1/9
OC71 1/9	2N706 1/9	2N3708 1/9

All the above types are available at 16 for £1. Brand New. Individually Tested, unmarked but guaranteed to be within their correct specification, or money refunded.

ANTEX SOLDER IRON

A lightweight iron with a 15 watt nickel plated bit. Designed to enable you to weld reliable joints accurately. Model CN240 volts. Special low price. Act Now, Only 29/11

MONEY BACK GUARANTEE. P. & P. 1/-

J. M. KING (N)

17 Buckridge, Portpool Lane, London, E.C.1

ENAMELLED COPPER WIRE

S.W.G.	Per 1/2 lb reel	Per 1 lb reel
18-22.	11/3d	16/6d
23-30.	11/9d	17/6d
31-35.	12/3d	18/6d
36-40.	15/-	24/-
41-44.	17/9d	29/6d

Orders despatched by return of post. Please add 1/- per item P. & P.

Supplied by: Banner Transformers, 84 Old Lansdowne Rd, West Didsbury, Manchester, 20.

TRADE ENQUIRIES INVITED

VICTORIA STREET'S unique magazine and paperback centre, Hills Westminster. "Practical Wireless" always in stock. **HILLS WESTMINSTER LTD.**, 5 Artillery Row, Victoria Street, S.W.1 (01-222 6165).

MISCELLANEOUS

(continued)

BUILD IT in a DEWBOX quality cabinet. 2in. x 2 1/2in. x any length. D.E.W. Ltd., Ringwood Road, FERNDOWN, Dorset. S.A.E. for leaflet. Write now—Right now.

BIG BARGAIN PARCEL 13/- POST PAID

Containing multi-contact relay, transistors, resistors (some high stab), rectifiers, diodes, capacitors, pots, knobs, etc.

6 OR 12 VOLT FLUORESCENT LIGHTS

12 ins. 8 Watt tube ample light for caravan, tent etc. Fully transistorised, low battery drain. Unbeatable at **65/6**

or in kit form **57/6** post paid.

4 WATT GRAM AMPS.

Volume and tone controls, mains operation, 3 Ω output, new and boxed **72/6** POST PAID

SALOP ELECTRONICS Callers welcome
23 Wyle Cop, Shrewsbury, Shropshire S.A.E. for lists

THE NEW

ELECTRONIC MUSIC FOR YOU

Then how about making yourself an electric organ? Constructional data available—full circuits, drawings and notes! It has 5 octaves, 2 manuals and pedals with 24 stops—uses 41 valves. With its variable attack you can play Classics and Swing. Write NOW for free leaflet and further details to C. & S., 20 Maude Street, Darlington, Durham. Send 4d. stamp.

SERVICE MANUALS for Pre 1958 H.M.V. and E.M.I. MODELS. Radio and Record Player Manuals 5/- each. Television Manuals 7/6 each. Send C.W.O. stating model required. Also limited range of components and spares. Send details of your requirements. R.D.I. Ltd., Chilton Works, Garden Road, Richmond, Surrey.

MUSICAL MIRACLES! Drum, Cymbals, Waa-Waa and Fuzz modules. New unique effects units, Percussion etc. Good waa-waa kits 49/-. Famous "Mister Bassman" bass pedal unit. Also bargain components list of reed switches etc. Send S.A.E. NOW!—D.E.W. Ltd., 254 Ringwood Road, Fern-down, Dorset.

CONCRETE SPEAKER CABINETS

For those constructors who want to get the best from their speaker, in the form of unsurpassed crispness, and clarity of bass, a seamless precision-cast reflex cabinet in high-grade concrete has now been designed.

S.A.E. for details to:

R. J. COOPER,

120 Castle Lane, Solihull, Warks.

MISCELLANEOUS

(continued)

TV NOTES FOR UFO DETECTION, and 2 Optical Detector circuits, 9/6. All-night Optical/Radiation circuit with electronic "memory," 9/6. Radar & Electronic Publications, "Highlands," Needham Market, Suffolk.

WANTED

WANTED—Radio and Television Servicing, volumes 1960/61, 1961/62, 1962/63, 1963/64, 1964/65—Green, 34 Mendip Grove, Peterborough.

WANTED—copies of Radio Amateur Handbook before 1945. Magrath, 40 Mount Hermon Road, Woking, Surrey.

CASH PAID for New Valves. Payment by return. **WILLOW VALE, ELECTRONICS**, 4 The Broadway, Hanwell, London, W.7. 01-567/5400-2971.

WE BUY New Valves and Transistors. State price: **A.D.A. MANUFACTURING CO.**, 116 Alfreton Road, Nottingham.

WANTED NEW VALVES ONLY

Must be new and boxed
Payment by return

WILLIAM CARVIS LTD.
103 North Street, Leeds 7

WANTED NEW VALVES, televisions, radiograms, transistors, etc. **STAN WILL-ETTS**, 37 High Street, West Bromwich. Staffs. Tel.: WES 0186.

WE BUY New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. **WALTON'S WIRELESS STORES**, 55 Worcester Street, Wolverhampton.

WANTED EARLY WIRELESS ITEMS 1900-1920. Outside Horn, Hand-operated, Springless, Gramophones. Please describe and price wanted. T. Christen, 12 Princess Terrace, Brighton 7, Sussex BN2-5JS.

HI-FI EQUIPMENT

SHURE GOLDRING Cartridges Post Free. G800, M44/5/7 £7.17.6. M3D £5.5.0. M44E £8.19.6. M55E £9.19.6. M75E/2 £16.10.0. **GARRARD SP25/2** £10.17.6. AP 75 £16.17.6. p. & p. 7/6. Ultimate Electronics, 38 Achilles Road, London, N.W.6. Mail Order Only.

METAL WORK

METAL WORK: All types cabinets, chassis, racks etc., to your specifications. **PHIL-POTTS METAL WORKS LTD.**, Chapman Street, Loughborough.

FOR SALE

YUKAN SELF-SPRAY 30 PROFESSIONAL THE HUMAN ACCESSORY WAY

Get these **air drying GREY HAMMER** NOW! OR **BLACK WRINKLE (CRACKLE) Finishes**

Yukan Aerosol spraykit contains 16 ozs. fine quality durable easy instant spray. No stove baking required. Hammers available in grey, blue, gold, bronze. Modern Eggshell Black Wrinkle (Crackle) all at 15/6 at our counter or 16/6 carriage paid per push-button self-spray can. Also Durable, heat and water resistant. Black Matt finish (12 ozs. self-spray cans only) 15/6 carriage paid.

SPECIAL OFFER: I can plus optional transferable snap-on trigger handle (value 5/-) for 16/6, carriage paid. Choice of 13 self-spray plain colours and primer (Motor car quality) also available. Please enclose cheque or crossed P.O. for total amount direct to:

Dept. M **YUKAN, 307a, EDGWARE ROAD, LONDON, W.2.**

We supply many Government Departments, Municipal Authorities, Institutes and Leading Industrial Organisations—We can supply you too.

Open all day Saturday. Closed Thursday afternoons

SEEN MY CAT? 5,000 items. Mechanical & Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PW, NEW MILLS, Stockport.

MORSE MADE EASY !!

FACT NOT FICTION. If you start **RIGHT** you will be reading amateur and commercial Morse within a month. (Normal progress to be expected.)

Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it, it's easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed.

For details and course C.O.D. ring, s.t.d. 01-660 2896 send 8d. stamp for explanatory booklet to:

68088 (BOX 11), 45 GREEN LANE, PURLEY, SURREY

EDDYSTONE EC 10, new. £50.— Garton, 24 Park Drive, Sandiacre, tel. Long Eaton 4753.

SERVICE SHEETS

LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS, CAR RADIOS)

Only 5/- each, Manuals from 10/- plus large S.A.E.

(Uncrossed P.O.'s please, original returned if service sheets not available.)

C. CARANNA
71 BEAUFORT PARK
LONDON, N.W.11

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number alternative.

Free TV fault tracing chart or TV list on request with order.

Mail order only.

RADIO & TV SERVICE SHEETS 4/- S.A.E. Service manuals 12/6d each, P.&P. 1/6d. State make and model No. to: Bell's Television Service, Albert Place, Starbeck, Harrogate, Yorks.

SERVICE SHEETS: Radio, TV etc. 8,000 models. List 2/-. S.A.E. enquiries. TEL-RAY, 11 Maudland Bank, Preston.

SERVICE SHEETS (continued)

TRADER SERVICE SHEETS

5/- each plus postage

We can supply Trader Service Sheets for most makes and types of Radios, Tape Recorders and Televisions—Manuals for some.

Cheques and open P.O.s returned if sheets not available.

OAKFIELD ENTERPRISES LIMITED

30 CRAVEN STREET, STRAND
LONDON WC2

Make	Model	Radio/TV

1970 List now available at 2/- plus postage

If list is required indicate with X

From

Address

enclose remittance of.....
(and a stamped addressed envelope)
s.a.e. with enquiries please

MAIL ORDER ONLY (February PW)

SERVICE SHEETS (1925-1970) for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., by return post, with free Fault-Finding Guide. Prices from 1/-. Over 8,000 models available. Catalogue 2/6. Please send S.A.F. with all orders/enquiries. Hamilton Radio, 54 London Road, Bexhill, Sussex.

RADIO, TELEVISION over 3,000 models. JOHN GILBERT TELEVISION, 1b Shepherds Bush Rd., London W.6. SHE 8441.

EDUCATIONAL

TRAIN FOR SUCCESS WITH ICS

Study at home for a progressive post in Radio, TV and Electronics. Expert tuition for City & Guilds (Telecoms Techn's Cert. and Radio Amateurs') R.T.E.B., etc. Many non-exam courses incl. Colour TV Servicing, Numerical control & Computers. Also self-build kit courses—valve and transistor.

Write for **FREE prospectus** and find out how ICS can help you in your career.

ICS, DEPT. 541 INTERTEXT HOUSE, STEWARTS ROAD, LONDON, SW8

RADIO OFFICER training courses. Write: Principal, Newport and Monmouthshire College of Technology, Newport, Mon.

EDUCATIONAL (continued)

CITY & GUILDS (electrical, etc.) on "Satisfaction or Refund of Fee" terms. Thousands of passes. For details of modern courses in all branches of electrical engineering, electronics, radio, TV, automation, etc., send for 132-page Handbook—FREE. B.I.E.T. (Dept. 168K), Aldermaston Court, Aldermaston, Berks.

BECOME "Technically qualified" in your spare time, guaranteed diploma and exam. home-study courses in radio, T/V servicing and maintenance, T.T.E.B., City & Guilds, etc.: highly informative 120-page Guide—free. **CHAMBERS COLLEGE** (Dept. 857K), Aldermaston Court, Reading, RG7 4PF.

SITUATIONS VACANT

TV and Radio, A.M.I.E.R.E., City & Guilds, R.T.E.B. Certs., etc on "Satisfaction or Refund of Fee" terms. Thousands of passes. For full details of exams and home training Courses (including practical equipment) in all branches of Radio, TV, Electronics, etc. Write for 132 page Handbook—FREE. Please state subject. **BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY** (Dept 137K), Aldermaston Court, Aldermaston, Berks.

Radio Operators

There will be a number of vacancies in the Composite Signals Organisation for experienced Radio Operators in 1971 and subsequent years.

Specialist training courses lasting approximately 2 months are held at intervals. Applications are now invited for the course starting in September 1971.

Salary Scales
During training with free accommodation provided at the Training School:—

Age 21	£848 per annum
22	£906 " "
23	£943 " "
24	£981 " "
25 and over	£1,023 " "

On successful completion of course:—

Age 21	£1,023 per annum
22	£1,087 " "
23	£1,150 " "
24	£1,214 " "
25 (highest age point)	£1,288 " "

then by 6 annual increments to a maximum of £1,749 per annum.

Excellent conditions and good prospects of promotion. Opportunities for service abroad.

Applicants must be United Kingdom residents, normally under 35 years of age at start of training course, and must have at least 2 years operating experience or PMG qualifications. Preference given to those who also have GCE 'O' level or similar qualification.

Interviews will be arranged throughout 1971. Application forms and further particulars from:—

RECRUITMENT OFFICER (TR 37)
Government Communications Headquarters,
Oakley, Priors Road,
CHELTENHAM, Glos. GL52 5AJ
Tel: No. Cheltenham 21491 Ext 2270

RECEIVERS & COMPONENTS

A CORNUCOPIA OF COMPONENTS! Scarce valve, selected T.V. components, Speakers, Cabinets. Computer panels—long leads NOT printed circuits. Transistors, resistors—new and recovered. State requirements. S.A.E. (F.S.) for details. **MAIL-MART, 6 Eastbourne Road, Pevensey Bay, Sussex.**

RECEIVERS & COMPONENTS

(continued)

AERIAL BOOSTERS

We make four types of r.f. high gain transistorized pre-amplifiers

Wideband Radio Type L10 39/-
This covers the Medium and Short Wave.
V.H.F. F.M. Radio Type L11 59/-
This covers the V.H.F. radio band.
V.H.F. Television Type L12 59/-
Please state Band and I and III.
U.H.F. Television Type L45 59/-
Tunable over the U.H.F. band.
S.A.E. for Details. P. and P. 1/-

VALVE BARGAINS

Any 5—9/-; 10—14/-; 100—E5 10s: ECC82, ECL80, EF80, EF85, EF183, EBF89, EB91, EY86, PCC84, PCC89, PC97, PCF80, PCF86, PCL82, PCL83, PCL84, PCL85, PL36, PY33, PY81, PY82, PY801, PY800, 30L15.

7 day Money Back Guarantee.

VELCO ELECTRONICS

62 Bridle St, Ramsbottom, via Bury, Lancs.

EX-GOVT. COMMUNICATIONS RECEIVERS, calibrators, signal generators, components, etc., with money back guarantee. SAE list. Callers welcome, please phone first.—P. R. Gollidge, G3EDW, Glen Tor, Torrington, Devon. (STD 08-052) 2411.

CONSTRUCTOR UNITS

R.F. Generator. Supplied with coils, tuning cap., switch and details for wiring and calibration. Covers 150KH/z to 30MH/z. 89/6+3/6 pp.

A.F. Unit. Osc. operates at 2 freq's. for A.F., R.F. checks, connects as amp. for continuity checks. Dual freq. square wave o/p for audio/HIFI tests. Provides modulation for R.F. unit. 39/6+3/6 pp.

S.A.E. for Details. Tweed Electronics (PW), 9 The Green, Hatfield Peveril, Chelmsford, Essex.

BRAND NEW ELECTROLYTICS, 15/16V. 0.5, 1, 2, 5, 10, 20, 30, 40, 50, 100 mfd. 8.5d. E12 series 5% resistors. Carbon Film 1/4W 1Ω to 1MΩ, 1.5d. Wirewound 5W 15Ω to 15KΩ, 10d., postage 1/-. The C. R. Supply Co., 127 Chesterfield Rd., Sheffield 8.

E.M.I. LOUDSPEAKERS, 13" x 8" bass, 2" tweeters, crossover, 3, 8, 15 ohms, 75/-. 5" bass, special suspension, 8 ohms, 37/6. 3 1/2" tweeters, 8 ohms, 16/6. Transistors, 2N5172, BC 213L, 2/-, £1 doz. All post free. "Sontel," Dept. X, 183 Clapham Manor St., London, S.W.4. Tel: 01-720 3559.

JEF FOR VALUE

NEW BRANDED FULL SPEC. DEVICES

SL402A	35/-	PA234	17/6	PA237	31/6
N5709A	13/6	MEL11	9/6	D40C1	13/6
40669	24/-	40583	5/3	2N3055	14/-
2N5172	1/9	W005	7/6	1N4001	1/5
1N4002	2/-	1N4003	2/2	1N4004	2/5
1N4005	2/9	1N4006	3/5	1N4007	4/-

P. & P. 1/- per order. Overseas 7/6. Cash with order. Mail order only.

JEF ELECTRONICS (P.W.11)

York House, 12 York Drive, Grappenhall, Warrington, Lancs.

Money back if not satisfied.

NEW MODEL V.H.F. KIT MK2

Our latest Kit, improved design and performance plus extra Amplifier Stage, receives Aircraft, Amateurs, Mobile, Radio 2, 3, 4, etc. This novel little set will give you endless hours of pleasure and can be built in one evening. Powered by 9 Volt battery, complete with easy to follow instructions and built in Jack Socket for use with Earphones or Amplifier.

Only 68/-, P.&P. Free U.K. only
Postal Orders, Cheques to:

Dept. P.W.
Galleon Trading Co., 25 Avelon Road,
Romford, Essex

Stella Nine Range Cases

Manufactured in Black, Grey, or Blue Stelvetite and finished in Plastic-coated Steel, Morocco Finish with Aluminium end plates. Rubber feet are attached and there is a removable back plate. There is also a removable front panel in 18 s.w.g Alloy.

Now all Aluminium surfaces are coated with a strippable plastic for protection during manufacture and transit. All edges are polished.

LIST OF PRICES AND SIZES

Width	Depth	4" Height	6" Height	7 1/2" Height
		£ s. d.	£ s. d.	£ s. d.
6 1/2"	3 3/4"	15 0	18 0	1 1 6
6 1/2"	4 1/4"	16 3	1 1 6	1 5 0
8 1/2"	3 3/4"	18 0	1 5 0	1 5 0
8 1/2"	6 1/4"	1 5 0	1 11 9	1 17 0
10 1/2"	7 1/4"	1 14 6	2 2 6	2 6 0
12 1/2"	3 3/4"	1 5 0	1 11 9	1 17 6
12 1/2"	5 1/4"	1 14 0	2 2 0	2 5 6
12 1/2"	8 1/4"	2 3 0	2 11 6	2 15 6
14 1/2"	3 3/4"	1 10 0	1 17 6	2 2 0
14 1/2"	9 1/4"	2 11 6	3 7 0	3 10 0
16 1/2"	6 1/4"	2 6 0	2 15 6	3 1 9
16 1/2"	10 1/4"	3 0 0	3 18 0	4 6 0

Cases—Post 4s. 6d. per order.
Discounts available on quantities.

CHASSIS in Aluminium, Standard Sizes, with Gusset Plates

Sizes to fit Cases. All 2 1/4" Walls		
	s. d.	s. d.
6" x 3"	6 6	10" x 7" 10 3
6" x 4"	6 9	12" x 3" 8 0
8" x 3"	7 9	12" x 5" 9 0
8" x 6"	9 3	12" x 8" 12 9
		16" x 10" 19 0

Chassis—Post 3s. 0d. per order.
Discounts available on quantities.

E. R. NICHOLLS

Manufacturer of Electronic Instrument Cases

46 LOWFIELD ROAD
STOCKPORT - CHESHIRE
Tel: 061-480 2179

COMPLETE RANGE of receivers by Trio, Lafayette, Hallicrafters, etc. Chassis, panels, cabinets. S.a.e. for lists. Stephens-James Ltd., 70 Priory Road, Liverpool 4. Tel. 051-263-7829.

BOOKS & PUBLICATIONS

SURPLUS HANDBOOKS

19 set Circuit and Notes ..	7/0 p/p 6d.
1155 set Circuit and Notes ..	7/0 p/p 6d.
H.R.O. Technical Instructions ..	6/0 p/p 6d.
38 set Technical Instructions ..	6/0 p/p 6d.
46 set Working Instructions ..	6/0 p/p 6d.
88 set Technical Instructions ..	7/6 p/p 6d.
BC.221 Circuit and Notes ..	6/0 p/p 6d.
Wavemeter Class D Tech. Instr. ..	6/0 p/p 6d.
18 set Circuit and Notes ..	6/0 p/p 6d.
BC.1000 (31 set) Circuit and Notes ..	6/0 p/p 6d.
CR.100/B.28 Circuit and Notes ..	10/6 p/p 1/-
R.107 Circuit and Notes ..	7/6 p/p 6d.
AR.88D Instruction Manual ..	18/6 p/p 6d.
62 set Circuit and Notes ..	7/0 p/p 6d.
Circuit Diagram 5/6 each post free, R.1116/A, R.1224/A, R.1355, R.F. 24, 25 and 26, A.1134, T.1154, CR.300, BC.312, BC.342, BC.348J BC.348 (E.M.P.), BC.624, 22, 1475 (88), 1392.	
Colour Code Indicator ..	2/6 p/p 6d.
52 set Sender and Receiver circuits 8/- post free	

S.A.E. with all enquiries please.
Postage rates apply to U.K. only.

Mail order only to:

INSTRUCTIONAL HANDBOOK SUPPLIES

DEPT. PW, TALBOT HOUSE,
28 TALBOT GARDENS, LEEDS 8

ELECTRICAL

240 VOLT
ELECTRICITY ANYWHERE



BEST EVER 200/240 VOLS "MAINS" SUPPLY FROM 12 VOLT CAR BATTERY
Exclusive World Scoop Purchase. The fabulous Mk. 12D American Heavy Duty Dynamotor Unit with a Massive 220 watt output and giving the most brilliant 200/240 volt performance of all time. Marvellous for Television, Drills, Power Tools, Mains Lighting, AC Fluorescent Lighting and all 200/240 volt Universal AC/DC mains equipment. Made at tremendous cost for U.S.A. Govt. by Delco-Remy. This magnificent machine is unobtainable elsewhere. Brand New and Fully Tested, only £4.19.6, plus 10/6 postage. C.O.D. with pleasure. Money back if not delighted. Please send s.a.e. for interesting illus. details.
Dept. PW, STANFORD ELECTRONICS
Rear Derby Road, North Promenade,
Blackpool, Lancashire.

AERIALS

BAKER AND BAINES

UHF Aerials

BBC and ITV 625 Colour

10 ele, 42/-; 14 ele, 47/-; 18 ele, 65/-; 22 ele, 75/-; Double 22 ele, 160/-.
BBC Aerials: Dipole 35/-; X 43/-; H 48/-.
ITA Aerials: 5 ele, 39/-; 8 ele, 54/-; 11 ele, 66/-; double 5 array, 98/-.
Combined Aerials: Dipole plus 5, 54/-; H plus 5, 82/-; X plus 5, 90/-.
Special Loft Dipole plus 5, 42/-.
Diplexers - Triplexers - Matched Diplexers
UHF - VHF
Poles, Lashings, Clamps, Couplers, etc..
Co-Ax 1/3 and 2/3
Postage paid inland on Aerials only.
Please state channels when ordering.
SAE for full lists.

11 DALE CRESCENT, TUPTON, CHESTERFIELD

Est. 1943 **JOHNSONS** Tel: 24864

New! CV2—a unique triple-purpose VHF kit for the Amateur enthusiast. Integrated converter, receiver, and tuner-feeder. Fantastic single transistor performance! Comprehensive kit of high grade parts with three coils covering 80-178MHz, 9v battery, etc., together with simplified diagrams and instructions. Price complete, £4, post, packing and insurance paid, direct from makers. S.A.E. for literature.

JOHNSONS (RADIO) St. Martin's Gate, Worcester WR1 2DT

KEYNECTOR

The safe quick way to connect electrical equipment to the mains



Send for full details
EB INSTRUMENTS
49-53 PANCRAS ROAD, LONDON NW1
Tel: 01-837 7781

DOOR INTERCOM

Know who is calling and speak to them without leaving bed, or chair. Outfit comprises microphone with coil push button, connectors and master inter-com. Simply plugs together. Originally sold at £10. Special snip price 49/8, plus 3/8 postage.



5A, 3 PIN SWITCH SOCKETS

An excellent opportunity to make that bench die board you have needed or to stock up for future jobs. This month we offer 6 British made (Hicraft) bakelite flush mounting shuttered 5A switch sockets for only 10/- plus 3/8 post and insurance. (20 boxes post free).

TELESCOPIC AERIAL

For portable, car radio or transmitter. Chrome plated—six sections, extends from 7 1/2 to 47in. Hole in bottom for 6BA screw. 7/6 KNUCKLED MODEL FOR F.M. 8/6.

PHILIPS TRIMMER

0-30pf an old design but one which has never been bettered. 1/- each. 10/- doz. 24/0 per 100.



MINIATURE WAFER SWITCHES

2 pole, 2 way—4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole, 6 way—1 pole, 12 way. All at 3/6 each. 38/- dozen, your assortment.



WATERPROOF HEATING ELEMENT

26 yards length 70W. Self-regulating temperature control. 10/- post free.

BLANKET SWITCH

Double pole with neon let into side so luminous in dark. Ideal for dark room light or for use with waterproof element, new plastic case 5/6 each, 3 heat model 7/8.



COPPER CLAD ELEMENT

1250 wattle—4ft. long but bent to U shape, ideal for overhead heater—just mount reflector above. 12/6 each, plus 4/6 post. 26 doz. post paid.

ERGOTROL UNITS

These units made by the Mullard Group are for operating and controlling d.c. Motors and equipment from A.C. mains. Thyristors are used and these supply a variable d.c. resulting in motor speed control and operating efficiency far superior to most other methods. The units are contained in wall mounting cabinets with front control panel on which are fuses—push buttons for on/off and the variable thyristor firing control.



4 models are available—all are brand new in makers cases: £17.10.0
Model 2410 for up to 5 amps £27.10.0
Model 2411 for up to 10 amps £47.10.0
Model 2413 for up to 45 amps 295. 0.0
Model 2415 for up to 80 amps
Note: 2415 is a floor mounting unit.

'GLADIATOR' 2 WAVE BAND TRANSISTOR RADIO

7 transistor, 2 wave band (medium and long) pocket radio with carrying handle and ear-plug. These radios use a ferrite slab aerial and a conventional superhet circuit with built in moving coil speaker. Completely built up, ready to play. Offered at less than importers price due to bankrupt purchase. A remarkable bargain. 59/6 plus 3/8 post and insurance.



COMPONENT SNIP


Wire Wound Controls by Welwyn
Standard size approximately 1" (dia) with integral Bakelite control knob. Suitable for preset or variable circuits. Following values available: 15 Ohms, 22 Ohms, 33 Ohms, 100 Ohms, 300 Ohms. Normal retail price about 6/- each. Special snip price 2/- each or £1 per dozen.

THE FULL-FI STEREO SIX

The amplifier sensation of the year. You will be amazed at the fullness of reproduction and at the added qualities your records or tuner will reproduce. Built into metal cabinet elegantly styled in simulated teak finished to blend with modern furnishings, this amplifier uses an integrated solid state circuit with an output power of 6 watts R.M.S. split over the two channels. The amplifier is ideal for use with normal pick-ups and tuners, it has a double wound mains transformer and ganged volume and tone controls—also switching for Mono to Stereo, tuner or pick-up. Other controls include "treble lift and cut", "balance" and separate mains on/off switch. UNREPEATABLE PRICE is £28.18 plus 7/6 post and insurance.



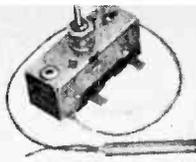Where postage is not stated then orders over £5 are post free. Below £5 add 2/9. S.A.E. with enquires please.



THERMOSTAT WITH PROBE

This is a sensor attached to a 16A switch by a 14in. length of flexible capillary tubing—control range is 20°F to 150°F so it is suitable to control soil heating and liquid heating especially when in buckets or portable vessels as the sensor can be raised out and lowered into the vessel. This thermostat could also be used to sound a bell or other alarm when critical temp. is reached in stack or heap subject to spontaneous combustion or if liquid is being heated by gas or other means not controllable by the switch. Made by the famous Teddington Co., we offer these at 12/6 each. Postage and insurance 2/9.

'CORONET' CAMERA

at a fraction of maker's price. Plus this FREE ever-ready drop-front case and shoulder strap. British made with precision auto-focus lens. Perfect pictures in colour and B & W. 12 pictures on Kodak 127 film. Extremely strong and robust. 14 days' free trial. We guarantee to return your money in full if you can't take perfect pictures. 19/6+2/6 p. & p.



Neon Mains Tester, 1/3 each. 12/- doz. Flood Lamp Control. Our dim and full switch is ideal for controlling photo flood lamps; it gives two lamps in series, two lamps full brilliance and lamps off. Similar control of other appliances can be arranged where used in pair or where circuit can be split exactly in half. Technically the switch is known as a double-pole change over with off. Our price 8/6. Sub-Miniature Silicon Diodes. General purpose type with gold-plated leads, 1/- each or 7/6 1/2 dozen. Message Tapes. 225ft. Tape on 3in. spools, normally 4/6 each, we offer 4 tapes for 12/6. Circular Flex. Non-kink. Ideal for vacuum cleaners etc., twin made by BIOC. Usually 8d. yd., 100 yd. coil for 30/-, plus 6/- postage.

ELECTRONICS (CROYDON) LTD

Dept. PW, 266 London Rd., Croydon CR0 2TH
Also 102/3 Tamworth Road, Croydon

multi-drawer storage units

NEW! HANDY! TIDY! I-N-T-E-R-L-O-C-K-I-N-G

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units, interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots—removable space dividers. Build up any size cabinet for wall, bench or table top.

BUY AT TRADE PRICES!

SINGLE UNITS (5ins x 2 1/2ins x 2 1/2ins) Usually 2/6 each. Our Price 24/- dozen

DOUBLE UNITS (5ins x 4 1/2ins x 2 1/2ins) Usually 4/6 each. Our Price: 40/- dozen

PLUS QUANTITY DISCOUNTS!


Orders £5 and over Deduct 1/- in the £

Orders £10 and over Deduct 1/6 in the £

Orders £20 and over Deduct 2/- in the £

Packing/Postage/Carriage: Add 6/- to all orders under £3. Orders £3 and over, Packing/postage/carriage free

Quotations for Larger Quantities

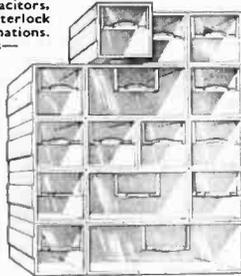

(Dept. PW10) 31 ALBERT RD. HENDON - LONDON NW4

A place for everything
Everything in its place!

If you have difficulty in obtaining PRACTICAL WIRELESS

Please place a regular order with your newsagent or send 1 year's subscription (£2-5-0) to Subscription Department, Practical Wireless, Tower House, Southampton St., London, W.C.2.

PADGETTS RADIO STORE

OLD TOWN HALL, LIVERSEDGE, YORKS.

Tel. Heckmondwike 4285

Amplifier Units Type A1413. Complete with Valves Type 5Z4 and 6V6GT. 230/250 Volt 50 cycles Transformer. Clean Condition. Untested 25/- Carriage B.R.S. 15/-.

Airmileage Units. Complete with 24 Volt Motor, and Gears, etc. Less Relay. Clean Condition. Untested 15/- Carriage B.R.S. 15/-.

New Chassis in Metal Case. 5 1/2 x 5 1/2 x 4". Complete with McMurdo Micronetron 18 way Plug and Socket, also 1000 Ohms Relay. 5/- P/P 4/6.

Amplifier and Diode Bridge Unit. Type 17626. Complete with Miniature sealed Relay and miniature Plug and Socket. Ex Units Bargain Price 7/6 Post Paid.

SPECIAL OFFER. Bush 17" T.V. Sets Series 75. 12 Channels Complete and Tested with good Tube £6/10/0. Cabinet Fair. Carriage and Insurance Passenger Train G.B. only 35/-. Untested 17" T.V. Complete 12 Channel 50/- Carriage £1.

Speakers Removed from T.V. Sets. All P.M. 3 Ohms. 5" round 3/- each 6 x 4 3/4" each. 7 x 4 5/8" each. Slot Speakers 8 x 2 1/2 5/- each Post on any Speaker 4/-.

8" P.M. Speakers in Cabinet with Volume Control 3 Ohm. Cabinet Condition Poor. Speaker First Class, 10/- Post and Packing 10/- Reclaimed T.V. Tubes with 6 month Guarantee 17" AW 43/80 AW 43/88 40/- MW 43/69 30/- each. All Tubes 15/- Carriage.

VALVE LIST—Ex Equipment. 3 months' guarantee. Single Valves Post 7d., over 3 Valves p. & p. paid.

ARP12	1/6	EY86	5/-	PY33	5/-	6U4	5/-
EB91	9d.	PCC84	2/-	PY81	1/6	6P28	5/-
EF85	3/-	PCF80	2/-	PY82	1/6	10P13	2/6
EBF80	3/-	PCL84	4/-	PZ30	5/-	185BT	8/6
ECC81	3/-	PCL85	4/-	U191	5/-	20D1	3/-
ECC82	3/-	EF183	4/-	U281	5/-	20P1	5/-
ECC83	4/-	EF184	4/-	U282	5/-	20P3	2/6
ECL80	1/6	PCL82	4/-	U251	5/-	30PL1	5/-
EF50	1/-	PCL83	5/-	6B8	1/8	30P12	5/-
EF80	1/6	PL36	5/-	6BW7	2/6	30F5	2/6
EF91	9d.	PL81	4/-	6K7	1/9	40FL1	5/-
						6/30L2	5/-

Head Office and Warehouse
44A WESTBOURNE GROVE
LONDON W2
Tel. PARK 5641/2/3

Z & I AERO SERVICES LTD.

Retail Shop
85 TOTTENHAM COURT ROAD
LONDON W1
Tel. LANGHAM 8403
Open all day Saturday

Please send all correspondence and Mail-Orders to the Head Office
When sending cash with order, please include 2/6 in £ for postage and handling
MINIMUM CHARGE 2/6. No C.O.D. orders accepted
PLEASE NOTE THAT THE VALVES OFFERED BELOW ARE NOT NECESSARILY OF U.K. ORIGIN
PLEASE NOTE THAT ALL PRICES ARE IN DECIMAL PARTS OF £, I.E. IN NEW PENCE

OA2	0.38	6AR5	0.35	6EJ7	0.35	6Y6G	0.60		
OA3	0.45	6AR6	0.40	6EW6	0.65	7Y4	0.85		
OB2	0.35	6AS5	0.35	6F1	0.70	9BW6	0.50		
OB3	0.60	6AS7G	0.80	6F5	0.60	10C2	0.50		
OC3	0.38	6AT6	0.30	6F6G	0.30	10D1	0.50		
OD3	0.35	6AB3	0.35	6F7	0.35	10P2	0.40		
1B3GT	0.38	6AV6	0.30	6F13	0.38	10F1	0.90		
1L4	0.20	6AW8A	0.55	6F14	0.65	10F9	0.50		
1R4	0.35	6BA6	0.25	6F15	0.65	10F18	0.45		
1R5	0.35	6BE6	0.30	6F18	0.45	10L1	0.45		
1R4	0.27	6BF5	0.80	6F23	0.80	10LD11	0.60		
1R5	0.25	6BF6	0.50	6F24	0.75	10P13	0.55		
1U4	0.25	6BH5	0.45	6F25	0.75	10P14	1.10		
1U4	0.27	6BJ6	0.45	6F26	0.38	12AB5	0.60		
1U5	0.50	6BK7A	0.55	6F28	0.60	12AC8	0.40		
1V2	0.45	6BL7GA	0.45	6J4	0.50	12AD6	0.40		
1X2B	0.40	0.85	6J5GT	0.30	12AL5	0.45	30A5	0.45	
2D21	0.35	6BN5	0.40	6J7	0.45	12AL5	0.45	30A3	0.40
3A4	0.35	6BN6	0.40	6K6GT	0.55	12AT9	0.30	30C1	0.30
3B28	2.15	6BQ5	0.25	6K7	0.35	12AT7	0.33	30C15	0.50
3BP1	2.75	6BR8	0.65	6K8G	0.35	12AU6	0.30	30C17	0.85
3Q4	0.40	6B8T	1.30	6K23	0.55	12AU7	0.30	30C18	0.75
3S4	0.35	6BW6	0.85	6K25	0.75	12AV6	0.33	30F5	0.65
3V4	0.46	6BW7	0.70	6L6GT	0.45	12AV7	0.50	30FL1	0.70
6R4GY	0.60	6BX6	0.25	6L7	0.40	12AX7	0.30	30FL12	0.33
6U4G	0.33	6BQ5	0.25	6L8	0.40	12AY7	0.55	30FL14	0.75
6U4GB	0.42	6C4	0.33	6LD20	0.40	12BA4	A0.55	30L1	0.40
6V4G	0.42	6C9GT	0.40	6N7GT	0.40	12BA6	0.35	30L15	0.85
6Y3GT	0.32	6CA4	0.28	6P1	0.60	12B7	0.35	30L17	0.70
6Z3	0.50	6CA7	0.50	6P28	0.68	12BE6	0.35	30P12	0.80
6Z4G	0.40	6CB6	0.30	6Q7	0.40	12BH7	0.40	30P19	0.50
6Z6/30L2	0.75	6CD6G	0.45	6S47	0.40	12B17	0.55	30P11	0.70
6B4	0.35	6C4	1.15	6H7G	0.85	12K5	0.55	30PL13	0.83
6B4F4	0.50	6C67	0.70	6H8K	0.85	12K7GT0.35	0.30	30PL14	0.90
6A07	0.40	6CH6	0.55	6LLGT0.35	0.30	12Q7G	0.30	35A3	0.55
6A1H	0.50	6CL6	0.50	6N8GT0.35	0.35	12R87	0.35	35A5	0.75
6A78	0.30	6CV4	0.93	6H87	0.40	14H7	0.80	35B5	0.65
6AK3	0.30	6D3	0.65	6H7	0.40	15B7	0.45	35C5	0.40
6AK6	0.57	6D3	0.45	6T8	0.35	20L1	1.10	35D5	0.70
6AL3	0.43	6D6	0.75	6U4GT	0.80	20P1	0.50	35L6GT	0.60
6AL5	0.20	6DK6	0.48	6V8A	0.40	20P4	1.10	35W4	0.30
6AM6	0.32	6DQ6B	0.83	6V8GT	0.38	20P5	1.20	35Z3	0.60
6AM6	0.33	6DR4	0.75	6X4	0.40	25C3	0.50	35Z4G	0.30
6AQ6	0.35	6E4	0.58	6L8GT	0.45	28D7	0.40	35ZGT	0.40
6AQ6	0.55	6EH7	0.30	6X4	0.55	25Z4G	0.70	50A5	0.70
								50A5	0.70

First Quality Fully Guaranteed



ELECTRONIC VALVES

28Z6GT	0.85	50B5	0.45	CY31	0.35	ECC81	0.33
30A3	0.40	50C4	0.40	DAF96	0.42	ECC82	0.30
30A3	0.40	50C6	0.40	DF96	0.42	ECC83	0.30
30C1	0.30	50D0G0.15	0.15	DK40	0.55	ECC84	0.30
30C15	0.50	50LGGT0.50	0.50	DK92	0.50	ECC85	0.60
30C17	0.85	83A1	1.50	DK92	0.50	ECC85	0.60
30C18	0.75	85A2	0.40	DK96	0.42	ECC88	0.40
30F5	0.65	90A1	2.50	DY86	0.33	ECC89	0.60
30FL1	0.70	90C1	0.60	DY87	0.35	ECC89	0.60
30FL12	0.33	90C2	1.25	DY87	0.35	ECC89	0.60
30FL14	0.75	90C3	0.70	DY87	0.35	ECC89	0.60
30L1	0.40	90C4	1.50	DY87	0.35	ECC89	0.60
30L15	0.85	90C5	0.60	DY87	0.35	ECC89	0.60
30L17	0.70	90C6	1.25	DY87	0.35	ECC89	0.60
30L18	0.75	90C7	0.60	DY87	0.35	ECC89	0.60
30L19	0.50	90C8	0.60	DY87	0.35	ECC89	0.60
30L20	0.40	90C9	1.50	DY87	0.35	ECC89	0.60
30L21	0.70	90C10	0.60	DY87	0.35	ECC89	0.60
30L22	0.80	90C11	0.60	DY87	0.35	ECC89	0.60
30L23	0.80	90C12	0.60	DY87	0.35	ECC89	0.60
30L24	0.80	90C13	0.60	DY87	0.35	ECC89	0.60
30L105	0.80	90C94	0.60	DY87	0.35	ECC89	0.60

In just 2 minutes, find out how you can qualify for promotion or a better job in Engineering . . .

That's how long it will take you to fill in the coupon below. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. Home Study Course gets results fast - makes learning easier and something you look forward to. There are no books to buy and you can pay-as-you-learn on 'SATISFACTION - OR REFUND OF FEE' terms. If you'd like to know how just a few hours a week of your spare time, doing something constructive and enjoyable, could put you out in front, post the coupon today. No obligation.

WHICH SUBJECT WOULD INTEREST YOU?

Mechanical

A.M.S.E. (Mech.)
Inst. of Engineers
Mechanical Eng.
Maintenance Eng.
Welding
General Diesel Eng.
Sheet Metal Work
Eng. Inspection
Eng. Metallurgy
C. & G. Eng. Crafts
C. & G. Fabrication

Draughtsmanship

A.M.I.E.D.
Gen. Draughtsmanship
Die & Press Tools
Elec. Draughtsmanship
Jig & Tool Design
Design of Elec. Machines
Technical Drawing
Building

Electrical & Electronic

A.M.S.E. (Elec.)
C. & G. Elec. Eng.
General Elec. Eng.
Installations & Wiring
Electrical Maths.
Electrical Science
Computer Electronics
Electronic Eng.

Radio & Telecomms.

C. & G. Telecomms.
C. & G. Radio Servicing
Radio Amateurs' Exam.
Radio Operators' Cert.
Radio & TV Engineering
Radio Servicing
Practical Television
TV Servicing
Colour TV
Practical Radio & Electronics (with kit)

Auto & Aero

A.M.I.M.I.
MAA IMI Diploma
C. & G. Auto Eng.
General Auto Eng.
Motor Mechanics
A.R.B. Certs.
Gen. Aero Eng.

Management & Production

Computer Programming
Inst. of Marketing
A.C.W.A.
Works Management
Work Study
Production Eng.
Storekeeping
Estimating
Personnel Management
Quality Control
Electronic Data Processing
Numerical Control
Planning Engineering
Materials Handling
Operational Research
Metrication

Constructional

A.M.S.E. (Civ.)
C. & G. Structural
Road Engineering
Civil Engineering
Building
Air Conditioning
Heating & Ventilating
Carpentry & Joinery
Clerk of Works
Building Drawing
Surveying
Painting and Decorating
Architecture
Builders' Quantities

General

C.E.I.
Petroleum Tech.
Practical Maths.
Refrigerator Servicing
Rubber Technology
Sales Engineer
Timber Trade
Farm Science
Agricultural Eng.
General Plastics

General Certificate of Education

Choose from 42 'O' and 'A' Level subjects including:
English
Chemistry
General Science
Geology
Physics
Mathematics
Technical Drawing
French
German
Russian
Spanish
Biology
B.I.E.T. and its associated schools have recorded well over 10,000 G.C.E. successes at 'O' and 'A' level.

WE COVER A WIDE RANGE OF TECHNICAL AND PROFESSIONAL EXAMINATIONS.

Over 3,000 of our Students have obtained City & Guilds Certificates. Thousands of other exam successes.

THEY DID IT—SO COULD YOU

"My income has almost trebled . . . my life is fuller and happier." - Case History G/321.

"In addition to having my salary doubled, my future is assured." - Case History H/493.

"A turning point in my career - you have almost doubled my standard of living." - Case History K/662.

"Completing your Course meant going from a job I detested to a job I love." - Case History B/461.

FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you.

Free!

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). We'll send you full details and a FREE illustrated book. No obligation and nobody will call on you . . . but it could be the best thing you ever did.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept D258, Aldermaston Court, Reading RG7 4PF.

(Write if you prefer not to cut this page)



BIET

POST THIS COUPON TODAY

To: B.I.E.T., Dept D258, Aldermaston Court, Reading RG7 4PF
Please send me book and details of your Courses in

Name Age

Address

Occupation

B.I.E.T. - IN ASSOCIATION WITH THE SCHOOL OF CAREERS - ALDERMASTON COURT, BERKSHIRE

Published approximately on the 7th of each month by IPC Magazines Limited, Fleetway House, Farringdon Street, London, E.C.4. Tel: 01-236 8080. Printed in England by Index Printers Dunstable, Beds. Sole Agents for Australia and New Zealand—Gordon and Gotch (A/asia) Ltd.; South Africa—Central News Agency Ltd.; Rhodesia and Zambia—Klugton Ltd.; East Africa—Stationery and Office Supplies Ltd. Subscription rate (including postage): For one year to any part of the world £2 5s 0d. PRACTICAL WIRELESS is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or any unauthorised cover by way of Trade, or affixed to as part of any publication, or advertising, literary or pictorial matter whatsoever.

HENRY'S RADIO LTD • MAIL ORDER AND INDUSTRIAL SALES DEPT. 303, EDGWARE ROAD LONDON W.2 01 723 1008 9

● **ELECTRONIC COMPONENTS AND EQUIPMENT**
AUDIO AND TEST GEAR
 356 EDGWARE ROAD LONDON W.2
 TEL. 01-402 4736


● **ELECTRONIC ORGANS, PUBLIC ADDRESS**
DISCOTHEQUE EQUIPMENT
 309 EDGWARE ROAD LONDON W.2
 TEL. 01-723 6963

● **HIGH FIDELITY SALES**
AND DEMONSTRATIONS
 354 EDGWARE ROAD LONDON W.2
 TEL. 01-402 5854

OPEN MONDAY TO SATURDAY 9AM TO 6PM. THURS 9AM TO 1PM. OPEN ALL DAY SATURDAY

COMPLETE STEREO SYSTEM FOR £39-10-0

HENELEC 5-5 STEREO AMPLIFIER. Inputs for ceramic cartridge. Aux/Tuner. Output for 8 to 15 ohms speakers. Silver with black and wood finish. British made. Size 12½ x 3½ x 6½. Fitted headphone socket. Complete system comprises 5-5 amplifier, Garrard 3000 or model 50 with 9TAHC diamond cartridge. Pair E.M.I. 10watt speakers, twin tweeters and crossover with polished wood cabinets 18" x 11" x 7". Also plinth and cover.

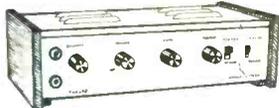

- **COMPLETE STEREO SYSTEM** (Rec. Price £50), **£39-10-0** p.p. 20/-
- **AMPLIFIER ONLY** £13-19-6, p.p. 7/6
- **TE1035 RECOMMENDED STEREO PHONES** 39/6

UNBEATABLE VALUE !!

BUILD THIS VHF FM TUNER

5 MULLARD TRANSISTORS 300 kc/s BANDWIDTH. PRINTED CIRCUIT. HIGH FIDELITY REPRODUCTION. MONO AND STEREO. A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately.



PARTS TOTAL COST £6.19.6, p.p. 3/6
DECODER £5.19.6, (FOR STEREO) p.p. 3/-
ASK FOR BROCHURE No. 3.

New printed circuit design with full power output. Fully tuneable on both MW/LW bands. 7 Mullard transistors. Fitted 5in. speaker. Room filling power. Easy to build with terrific results. Two colour leather-cloth cabinet with silvered front. All local and continental stations. Complete detailed instructions.

BUILD YOURSELF A QUALITY RADIO



Total cost £6.19.6, p.p. 6/6

Ask for Leaflet No. 1.

SINCLAIR EQUIPMENT Z30 75/- each, stereo 60 £8-10-0, PZ5 79/6, PZ6 £6-19-6, Z50 £5-9-6, PZ8 £5-19-6.

SPECIAL OFFER 2 of Z30, stereo 60, PZ5 (usually £23-10) or with PZ6 in place of PZ5 **£19**

WHEN IN LONDON visit the new Disco Centre at "354" and component shop at "356" Edgware Road, W.2.

TEST EQUIPMENT FOR YOUR HOME



AF105 50k/v multimeter (illus.), price £8-10, p.p. 3/6, leather case 28/6
200H 20k/v multimeter price £3-17-6, p.p. 3/-, case 12/6
TE200 RF Generator (illus.), price £15, p.p. 7/6
TE22D Matching Audio Generator, price £17, p.p. 7/6
TE65 Valve Voltmeter, price £17-10-0, p.p. 7/6
 Full details and complete range in catalogue



SLIM POCKET TEST GEAR

- **SIGNAL INJECTOR** 35/- p.p. 1/6
- **SIGNAL TRACER** 29/6 p.p. 1/6

NEW WORLD'S LOWEST COST STEREO MAGNETIC CARTRIDGE O/P 7mV, 20 c/s-20 Kc/s. Diamond Stylus. Fits most decks. Recommended for Quality and Performance
 Price 79/6 Model 940



FREE Stock List No. 16/17 on request
BEST VALUE IN U.K.

Choose from 100 complete stereo systems—Complete range of individual units also in stock. Demonstrations all day. Visit the new Hi-Fi Store

100 STEREO SYSTEMS
LOW CASH AND CREDIT/HP PRICES (Credit terms from £30 purchase-callers only).



HENRY'S LATEST CATALOGUE

New print. Now 350 pages. 6th Impression

- ★ **COMPONENTS, TEST GEAR**
- ★ **EQUIPMENT, MODULES**
- ★ **SPECIAL OFFERS ETC. ETC.**

Everything for the constructor
 Complete with 10/- value discount voucher for use with purchase. Price 7/6, p.p. 2/-

WHY NOT SEND AWAY TODAY?

NEW. 8 page SEMICONDUCTOR LIST FREE no: 36 new ranges and a few circuits.




YOU CAN SAVE 25% brand new GARRARD

(Post 7/6) **COMPLETE LIST FREE ON REQUEST AND GOLDRING**
 SP25mkII £10-19-6, AP75 £16-19-6, SL65B £14-19-6, SL72B £25 GL69 £22

SPECIAL OFFER Above with Sonotone 9talc diam. Add £2, with magnetic add 70/-, with Goldring G800 add £7-10-0

Also Fitted with 9talc diamond 2025TC £9-15-0, 3000LM £9-15-0, Model 50 £9-15-0
 Plinths/Covers: Standard 99/6, p.p. 4/6. De Luxe £8-10-0, p.p. 6/-, SL72B type £8-10-0, p.p. 6/-, GL69 Type £9-15-0 p.p. 6/6.

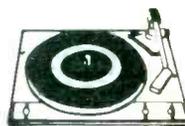● Goldring **GL69** with plinth and cover and G800 cartridge (usually £51) £39.10.0, p.p. 12/6.



NEW 25watt and 50watt RMS SILICON AMPLIFIERS


LOOK AT THE SPECIFICATIONS!

- 0.3% Distortion at full power
- -1db 11c/s to 40kc/s at full power
- Response -1db 11c/s to 100kc/s

PA25 10 Silicon Transistors Differential input, 25watts rms into Bohms, 700mV input. Size only 5" x 3" x 2". 4-hole fixing. 12watts into 15ohms. Supplied with edge connector and harness.

PA50 12-Transistor Version. 50watt rms into 3 to 4ohms
 MU442 Power supply for one or two PA25 or one PA50

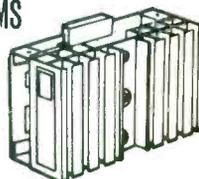● PA25 £7-10-0, ● PA50 £9-10-0, ● MU442 £6



NEW SELF POWERED PREAMPLIFIERS

Mains operated slim design Pre-amplifiers for use with any Power Amplifier. All Silicon FET/Transistor designs. Capable of driving up to 4-PA50 Amplifiers. Push Button selection. All facilities.

MODEL FET154 STEREO PREAMPLIFIER

Inputs for mag. Pickup, Tuner/Aux., Tape in and out. Response 20 c/s to 30kc/s. Output adjustable up to 1 volt. ±20dB Boost or Cutout Controls. Stim design. Size 12" x 5½" x 1½". Price £16-10-0

MODEL FET 9/4

Mono Preamplifier with built-in MIC MC XEC. Inputs for all Crystal and Ceramic cartridges, Tuner, Tape in and out. O/P and Response as FET154. Size 10½" x 4½" x 1½". Price £12-10-0

NO SOLDERING. JUST PLUG-IN CONNECTORS

ELECTRONIC ORGANS

COMPLETE RANGE OF COMPONENTS IN STOCK FOR ALL PURPOSES

- ★ **MODERN ALL BRITISH TRANSISTORISED DESIGNS AVAILABLE AS KITS OR READY BUILT VENEERED CABINETS FOR ALL MODELS**
- ★ **49 NOTE, 61 NOTE SINGLE MANUAL DESIGNS ALSO TWO MANUAL 49 NOTE**
- ★ **KITS AVAILABLE IN SECTIONS AS REQUIRED**
- ★ **NEW PAX DISCOTHEQUE CENTRE AT "309"**



HENRY'S RADIO LTD **FOUR ELECTRONICS CENTRES** ALL WITHIN 100 YARDS
 303 · 309 · 354 · 356 EDGWARE ROAD LONDON W.2