

**SPECIAL COLLECTOR'S EDITION**

# **electronics today**

ISSN. 0142-7229

INTERNATIONAL

APRIL 1982 85p

# 10<sup>th</sup>

**BIRTHDAY ISSUE!**

## **A Decade of Electronics**

**10 Projects ★ Over 50 circuits**

**Free to Enter Competitions**

**★ Over £500 in Prizes ★**

**★ WIN ★**

**A Digital Multimeter**

**A Hi-Fi Amplifier • A Computer**

**Plus Much More .....**

**24** Page  
**inside** Supplement

**AUDIO.... COMPUTING.... MUSIC.... RADIO.... ROBOTICS....**

# POWER PACKED — by POWERTRAN

Powertran's black boxes are packed with punch. Not only are they superb kits to buy and build they really do the job! Imaginative and ingenious design goes hand in hand with top quality materials and outstanding performance capability. With their smart black styling the kits harmonise visually as well as musically.

You can build each unit independently for its set task and then gradually increase your array until you have a complete bank of formidable controllable power.



Complete Kit — £49.90 + VAT

**MPA 200** is a low price, high power 100W amplifier. Its smart styling, professional appearance and performance, make it one of our most popular designs. With adaptable inputs the mixer accepts a variety of sources yet straightforward construction makes it ideal for the first-time builder.



Complete Kit — £49.50 + VAT

**CHROMATHEQUE 5000** — a 5-channel lighting system powerful enough for professional discos yet controllable for home-effects. Sound to light, strobe to music level, random or sequential effects — each channel can handle up to 500W yet minimal wiring is needed with our unique single-board design.



Complete Kit — £175.00 + VAT

**ETI VOCODER** — 14 channels, each with independent level control, for maximum versatility and intelligibility; Two input amplifiers — for speech/excitation — each with level control and tone control. The Vocoder is a powerful yet flexible machine that is interesting to build and thanks to our easy to follow construction manual, is within the capability of most enthusiasts.



Complete Kit — £64.90 + VAT

**SP2 200** twice the power with two of the reliable, durable and economic amps from the MPA200; fed by separate power supplies from a common toroidal transformer. Superb finish and quality components throughout — up to (even over!) the standard of high priced factory-built units.



**DJ90 Stereo Mixer** — this is a really versatile new mixer that enables the constructor DJ to produce a professional performance every time. There are two stereo inputs for magnetic cartridges, a stereo auxiliary input and mike input. Other 'plus' features are auto-panning for fast or slow, slider controls, multi-mixing, ducking, interrupt, input modulation, in short everything... the whole works — AND — under £100 complete! (We have illustrated the DJ90 teamed in our own console with the Chromatheque and an SP2 200 and speakers.

Complete Kit — £97.50 + VAT



THE FIRST WORDS AND THE LAST WORD IN ELECTRONIC KITS — SEE OUTSIDE BACK COVER OF THIS ISSUE!



**Digital Delay Line** — our latest kit! With its ability to give delay times from 1.6 mSecs to up to 1.6 secs. Many powerful effects including phasing, flanging, A.D.T., chorus, echo & vibrato are obtained. The basic kit is extended in 400 mS steps up to 1.6 secs. Simply by adding more parts to the PCB. Compare with units costing over £1,000! Complete kit (400 mS delay) **£135**. Parts for extra 400 mS delay £9.50p.

..... Quite simply the best way to make music



PORTWAY INDUSTRIAL ESTATE, ANDOVER, HANTS SP10 3NM. (0264) 64455.

## WORLD LEADERS IN ELECTRONIC KITS

- **Money Back Guarantee** — If you are not completely satisfied with your Powertran Kit return it in original condition within 10 days for full refund.
- **Free Soldering Practice Kit** — To assist the beginner we will supply, on request with your first kit order, a free soldering practice kit with useful tips and illustrations.
- **Component Packs** — Most kits are available as separate packs (e.g. PCB component sets, hardware sets etc). Prices in our FREE catalogue.
- **Ordering** — Full ordering details, delivery service, and sales counter opening — outside back of this issue.

ORDER BY PHONE  
(0264) 64455  
Simply telephone us with your order and quote  
Your Access or Barclaycard number.  
40 PAGE CATALOGUE FREE — CONTAINS  
FULL LISTINGS OF ALL OUR KITS

# electronics today

INTERNATIONAL APRIL 1982 VOL 11 NO 4



**Ron Harris B.Sc:** Editor  
**Peter Green:** Assistant Editor  
**Tina Boylan:** Editorial Assistant  
**Rory Holmes:** Project Editors  
**Phil Walker:**  
**Alan Griffiths:** Advertisement Manager  
**Paul Wilson-Patterson:** Group Art Editor  
**T.J. Connell:** Managing Director

**PUBLISHED BY:**  
 Argus Specialist Publications Ltd.,  
 145 Charing Cross Road, London WC2H 0EE.  
**DISTRIBUTED BY:**  
 Argus Press Sales & Distribution Ltd.,  
 12-18 Paul Street, London EC2A 4JS  
 (British Isles)  
**PRINTED BY:**  
 QB Limited, Colchester.  
**COVERS PRINTED BY:**  
 Alabaster Passmore.

**OVERSEAS EDITIONS and their EDITORS**  
 AUSTRALIA — Roger Harrison  
 CANADA — Halvor Moorshead  
 GERMANY — Udo Wittig  
 HOLLAND — Anton Kriegsman



Member of the  
 Audit Bureau  
 of Circulation

Electronics Today is normally published on the first Friday in the month preceding cover date. © Argus Specialist Publications Ltd 1982. All material is subject to worldwide copyright protection. All reasonable care is taken in the preparation of the magazine contents, but the publishers cannot be held legally responsible for errors. Where mistakes do occur, a correction will normally be published as soon as possible afterwards. All prices and data contained in advertisements are accepted by us in good faith as correct at time of going to press. Neither the advertisers nor the publishers can be held responsible, however, for any variations affecting price or availability which may occur after the publication has closed for press.

□ Subscription Rates. UK £11.95 including postage. Airmail and other rates upon application to ETI Subscriptions Department, 513 London Road, Thornton Heath, Surrey CR4 6AR.



## EDITORIAL AND ADVERTISEMENT OFFICE

145 Charing Cross Road, London WC2H 0EE. Telephone 01-437 1002/3/4/5.  
 Telex 8811896.

## FEATURES

<b>DIGEST</b> . . . . .	9	<b>READ/WRITE</b> . . . . .	54
News at nine		Get it off your chest	
<b>ELECTROMUSIC TECHNIQUES</b> . . . . .	17	<b>IGNITION COMPETITION</b> . . . . .	61
Circuits to experiment with		Bright sparks might win it	
<b>CRIMSON COMPETITION</b> . . . . .	33	<b>10th BIRTHDAY SUPPLEMENT</b> . . . . .	63
Win yourself a hi-fi . . . . .		Happy birthday to us	
<b>KITREVIEW</b> . . . . .	35	<b>BIRTHDAY COMPETITION</b> . . . . .	64
. . . and build some speakers for it		Win a decade's subscription	
		<b>AUDIOPHILE</b> . . . . .	88
<b>DESIGNER'S NOTEBOOK</b> . . . . .	45	Putting on the stylus	
Sample our delights		<b>VERO COMPETITION</b> . . . . .	111
		Some prize boxes	
		<b>TECH TIPS</b> . . . . .	113
		A smattering of readers' circuits	
		<b>CASIO COMPETITION</b> . . . . .	117
		For cool, calculating types	
		<b>ENTRY FORMS</b> . . . . .	133
		Only one cut required	

## PROJECTS

<b>ACCURATE VOLTAGE MONITOR</b> . . . . .	23	<b>ROBOT CONTROLLER PART 2</b> . . . . .	94
Check out your battery		For producing PWM	
<b>COMPUTER EXPANSION</b> . . . . .	26		
This'll blow your EPROM		<b>SOLID STATE REVERB</b> . . . . .	101
<b>AUTOMATIC CONTRAST METER</b> . . . . .	39	It's great-eat-eat-eat	
Something unusual		<b>CAPACITANCE METER PART 2</b> . . . . .	108
for photographers		We conclude with the construction	
		<b>SOUNDEFFECTS 2</b> . . . . .	118
<b>SOUNDEFFECTS 1</b> . . . . .	50	Steam train and whistle	
Bomb drop and explosion		<b>GUITAR PRACTICE AMP</b> . . . . .	121
<b>HIGH IMPEDANCE 100 MHz PROBE</b> . . . . .	57	Cheap, and keeps your neighbours cheerful	
Top flight test gear		<b>FOIL PATTERNS</b> . . . . .	136
		This is where our boards find lodging	

## INFORMATION

<b>NEXT MONTH'S ETI</b> . . . . .	15	<b>PCB SERVICE</b> . . . . .	44
Ever onward, ever better		Why mess with ferric chloride?	
<b>BOOK SERVICE</b> . . . . .	31	<b>SUBSCRIPTIONS</b> . . . . .	125
Read all about it		Advance booking	

# WATFORD ELECTRONICS

33/35 CARDIFF ROAD, WATFORD, HERTS, ENGLAND  
 MAIL ORDER, CALLERS WELCOME  
 Tel. Watford (0923) 40588. Telex: 8956095

**ALL DEVICES BRAND NEW, FULL SPEC. AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O.s OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS' OFFICIAL ORDERS ACCEPTED. TRADE AND EXPORT INQUIRY WELCOME. P.P. ADD 50p TO ALL ORDERS UNDER £10 NETT. OVERSEAS ORDERS POSTAGE AT COST. AIRSURFACE. ACCESS ORDERS WELCOME.**

**VAT** Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 15% to the total cost including P&P.  
 We stock thousands more items. It pays to visit us. We are situated behind Watford Football Ground, Nearest Underground/BR Station: Watford High Street.  
 Open Monday to Saturday: 9.00am to 6.00pm. Ample Free Car Parking space available.

**ELECTROLYTIC CAPACITORS:** (Values are in µF) 500V: 10 52p; 4778p; 63V: 0.47, 1.0, 1.5, 2.2, 3.3 3p; 4.7 3p; 6.8, 10 10p; 15, 22, 33, 47 12p; 60, 100, 150, 220, 330, 470 15p; 680, 1000, 1500, 2200, 3300, 4700 20p; 220V: 10 52p; 47 7p; 68, 100, 150, 220, 330, 470 10p; 680, 1000, 1500, 2200, 3300, 4700 15p; 50V: 1.0, 1.5, 2.2, 3.3, 4.7, 6.8, 10, 15, 22, 33, 47, 68, 100, 150, 220, 330, 470, 680, 1000, 1500, 2200, 3300, 4700 7p; 100V: 1.0, 1.5, 2.2, 3.3, 4.7, 6.8, 10, 15, 22, 33, 47, 68, 100, 150, 220, 330, 470, 680, 1000, 1500, 2200, 3300, 4700 7p.

**TAG-END TYPE:** 450V: 100uf 85p; 70V: 470u, 245p; 64V: 3300 198p; 2200 135p; 50V: 3300 145p; 2200 110p; 40V: 4700 160p; 25V: 10,000 320p, 15,000 345p.

**POLYESTER CAPACITORS:** Axial Lead Type  
 400V: 1nf, 1.5nf, 2nf, 3nf, 4nf, 5nf, 6nf, 7nf, 10nf, 15nf, 18nf, 22nf 12p; 33nf, 47nf, 68nf, 100nf, 150nf 20p; 220nf 30p; 330nf 42p; 470nf 52p; 680nf 1uF 68p; 2uF 82p.  
 160V: 10nf, 12nf, 33nf, 100nf 11p; 150nf, 220nf 17p; 330nf, 470nf 30p; 580nf 38p; 1uF 42p; 1.5 45p; 2uF 48p, 4uF 58p  
 1000V: 1nf 17p; 10nf 30p; 15nf 40p; 22nf 38p; 33nf 42p; 47nf 100n 42p

**POLYESTER RADIAL LEAD CAPACITORS:** 250V  
 10nf, 15nf, 22nf, 33nf, 47nf, 68nf, 100nf 7p; 150nf, 220nf 10p; 330nf, 470nf 13p; 680nf, 1uF 23p; 1u5 24p; 2uF 24p.

**TANTALUM BEAD CAPACITORS**  
 35V: 0.1uf, 0.2, 0.3 15p; 0.47, 0.68, 1.0, 1.5 16p; 2.2, 3.3 18p; 4.7, 6.8 22p; 10 28p; 15 33p; 22, 33 35p; 47, 6.8, 10 18p; 15, 33p, 22 30p; 33, 47 40p; 100 15p; 10V: 1.5 22, 2.2 26p; 3.3 47 35p; 100 55p; 6V: 100 42p.

**MYLAR FILM CAPACITORS**  
 100V: 1nf, 2, 4, 4nf, 10 6p; 15nf, 22nf, 30nf, 40nf, 47nf 7p; 55nf, 100nf, 200nf 9p; 50V: 470nf 12p.

**CERAMIC CAPACITORS 50V:**  
 Range: 0.5pF to 10nf 4p; 15nf: 22nf; 33nf: 47nf 5p; 100nf/30V 7p; 200nf/6V 8p

**SILVER MIC (Values in pF) 2, 3.3, 4.7, 6.8, 8, 10, 12, 15, 18, 22, 27, 33, 39, 47, 50, 56, 68, 75, 82, 85, 100, 120, 150, 180pF  
 \*200, 220, 250, 270, 300, 330, 360, 390, 470, 800, 800, 820 21p each  
 1000, 1000, 1800, 2200 30p each  
 3300, 4700pF 60p each**

**POLYSTYRENE CAPACITORS**  
 100V to 10kV: 1nf to 12nf 10p

**MINIATURE TYPE TRIMMERS**  
 2-66F, 2-100F 22p; 2-25pF, 5-56pF 30p; 10-88pF 35p

**COMPRESSION TRIMMERS**  
 3-40pF, 10-80pF 20p; 20-250pF 28p; 100-500pF 35p; 400-1250pF 48p

**RESISTORS Carbon Film High Stability, Low Noise Miniature, Tolerance 5%**

RANGE	VAL	1-99	100
1/4W	2.2k	4M7	E24 2p 1p
1/2W	2.2k	4M7	E12 2p 1p
1W	2.2k	1M1k	E12 5p 4p
2"	Metal Film 10k-1M	1M	6p 4p
1"	Metal Film 0.5W 511k-1M	1M	8p 6p

100 - price applies to Resistors of each value not mixed.

**DIODES**  
 AA119 15  
 BA100 15  
 BY100 24  
 BY126 15  
 BY127 12  
 CR033 250  
 OA9 40  
 OA47 12  
 OA70 12  
 OA79 15  
 OA85 15  
 OA90 15  
 CA91 8  
 CA95 8  
 OA200 8  
 CA202 8  
 IN314 15  
 IN1916 15  
 IN4001/2 6  
 IN4003 6  
 IN4007 7  
 IN4148 4  
 IN5401 4  
 IN5404 16  
 IN5406 17  
 IN5408 17  
 IN5409 17  
 IS44 9  
 IS921 9  
 6A/100V 40  
 6A/400V 50  
 6A/800V 65

**BRIDGE RECTIFIERS (plastic case) p**  
 1A/50V 20  
 1A/100V 22  
 1A/200V 24  
 2A/50V 35  
 2A/100V 39  
 2A/200V 40  
 2A/400V 46  
 2A/600V 55  
 6A/100V 83  
 6A/200V 95  
 6A/500V 125  
 10A/200V 125  
 10A/500V 130  
 25A/200V 240  
 25A/500V 395  
 5V 16A/DIL 56  
 5V 16A/DIL 50

**ZENERS**  
 Range: 2Vt to 39V 400mW  
 Range: 3V to 33V 1.3W  
 1.3W 1p each

**TRIACS**  
 3A/200V 54  
 3A/300V 56  
 6A/100V 80  
 6A/400V 69  
 6A/800V 115  
 12A/100V 78  
 12A/400V 95  
 12A/800V 188  
 BT 106 38  
 TIC44 24  
 TIC45 29  
 TIC46 29  
 TIC47 35  
 TIC48 32  
 TIC49 32  
 TIC50 32  
 TIC51 32  
 TIC52 32  
 TIC53 32  
 TIC54 32  
 TIC55 32  
 TIC56 32  
 TIC57 32  
 TIC58 32  
 TIC59 32  
 TIC60 32  
 TIC61 32  
 TIC62 32  
 TIC63 32  
 TIC64 32  
 TIC65 32  
 TIC66 32  
 TIC67 32  
 TIC68 32  
 TIC69 32  
 TIC70 32  
 TIC71 32  
 TIC72 32  
 TIC73 32  
 TIC74 32  
 TIC75 32  
 TIC76 32  
 TIC77 32  
 TIC78 32  
 TIC79 32  
 TIC80 32  
 TIC81 32  
 TIC82 32  
 TIC83 32  
 TIC84 32  
 TIC85 32  
 TIC86 32  
 TIC87 32  
 TIC88 32  
 TIC89 32  
 TIC90 32  
 TIC91 32  
 TIC92 32  
 TIC93 32  
 TIC94 32  
 TIC95 32  
 TIC96 32  
 TIC97 32  
 TIC98 32  
 TIC99 32  
 TIC100 32

**NOISE**  
 Z5J 195p

**VARIACAPS**  
 BA102 50  
 BB105B 40  
 BB108 40  
 BB110 40  
 MVAM2 165  
 MVAM115 158

**DIAC**  
 ST2 25  
 AM25LS31C 125

TRANSISTORS		SIEMENS Pcb Type Miniature poly. Capacitors	
AC125	35	BC212	10
AC126/7	35	BC213	10
AC128	30	BC214	10
AC141/2	30	BC215	10
AC176	28	BC216	10
AC187	32	BC217	10
AC188	32	BC218	10
AC191/17/18	75	BC219	10
AC192/20	75	BC220	10
AC193	75	BC221	10
AC194	75	BC222	10
AC195	75	BC223	10
AC378	75	BC406	10
AC379			

**SWITCHES**

TOGGLE: 2A, 250V  
 SPST 33p  
 DPDT 44p

**SUB-MIN TOGGLE**  
 SPST on/off 54p  
 SPDT c/w/over 80p  
 SPDT centre off 85p  
 SPDT centre both 85p  
 DPDT 6 taged 75p  
 DPDT centre off 80p  
 DPDT biased both ways 105p  
 DPDT 6 taged 75p  
 DPDT centre off 80p  
 DPDT 3 positions on/off 185p  
 3-pole 2 way 205p

**SLIDE 250V:**  
 DPDT 1A 14p  
 DPDT 1A c/off 15p  
 DPDT 1/2A 15p

**PUSHBUTTON 6A**  
 with 10mm Button  
 SPDT latching 99p  
 DPDT latching 145p  
 SPDT moment 99p  
 DPDT moment 145p

Mini Non Locking  
 Push to Make 15p  
 Push to Break 25p

**DIL PLUGS**  
 Length  
 4pin 44p  
 16pin 49p  
 24pin 80p  
 40pin 250p

Ribbon Cable ft  
 10 way 20p  
 20 way 40p  
 24 way 50p

**AMPHENOL PLUGS**

**DIL SWITCHES**

(SPST) 4 way 70p; 6 way 85p;  
 8 way 90p; 10 way 145p.  
 (SPDT) 4 way 190p.

**ROTARY SWITCHES:**  
 1 Adjustable Stop type  
 1 pole/2 to 12 way; 2p/2 to 6 way;  
 3 pole/2 to 4 way; 4p/2 to 3 way 45p

**ROTARY:** Mains DP 250V 4 Amp on/off 56p

**ROTARY (Mak-a-switch)**  
 Make a multiway switch. Shafting assembly has adjustable stop. Accommodates up to 6 wafers  
 (max. 6 pole/12 way + DP switch). Mechanism only 90p

**WAFERS:** (make before break) to fit the above switch mechanism.  
 1 pole/12 way; 2 pole/6 way; 3 pole/4 way; 4 pole/3 way; 5p/2 way 56p  
 Mains DP 4A Switch to fit 45p  
 Spacers 4p. Screen 6p

**ROCKER:** 5A/250V SPST 28p  
 ROCKER: 10A/250V SPDT 38p  
 ROCKER: 10A/250V DPDT c/w 96p  
 ROCKER: 10A/250V DPST with neon 85p

**VEROBOARD 0.1in**

VO Board 150p  
 DIP Board 330p  
 Vero Strip 144p

Proto DECS Veroblock 375p  
 S-Dec Eurobreadboard 350p  
 Limbo! 1 786p  
 Superstrip SS2 1350p

**PEN WIRING**  
 PEN + Spool 310p  
 Spare Spool 75p  
 Combs 80p

**FERRIC CHLORIDE**  
 1 lb bag Anhydrous 195p + 50p P&P

**HALO ETCH RESIST**  
 - Spare tip 90p

**ULTRASONIC TRANSDUCER**  
 40KHz 385p pr

**COPPER CLAD BOARDS**

Fibre glass	Single-sided	Double-sided	S.R.B.P.
5" x 6"	90p	110p	95p
6" x 12"	150p	195p	

**DIL SOCKETS (TEXAS)**

Length	Pin	Wire	Wrap
8pin	10p	25p	
14pin	10p	35p	
16pin	10p	42p	
18pin	10p	52p	
20pin	22p	60p	
22pin	25p	70p	
24pin	25p	70p	
28pin	28p	80p	
36pin	30p	105p	
40pin	30p	99p	

**PLUGS & SOCKETS**

JACK	Plug	Socket	In-line
2.5mm (plastic)	8p	16p	10p
3.5mm (plastic)	10p	15p	12p
1/4in Mono	16p	10p	18p
1/4in Stereo	15p	20p	15p
2pin	22p	24p	22p
3pin	26p	20p	39p
4pin	8p	6p	14p
5pin	13p	10p	15p
	16p	12p	15p
	13p	12p	15p

**PANEL METERS**

**FSD**  
 50-250x35mm  
 0.50uA 120p  
 0-100uA 120p  
 0-100uA 120p  
 0.50mA 295p  
 0-1mA 295p  
 0-50mA 295p  
 0-100mA 295p  
 0-500mA 295p  
 0-1A 295p  
 0-2A 295p  
 0-2.5V 295p  
 0-50V AC 295p  
 0-300V AC 295p  
 "S" 496p each

**CRYSTALS**  
 32.768KHz 150  
 100KHz 270  
 200KHz 295  
 455KHz 370  
 1MHz 290  
 1.008M 290  
 1.2MHz 385  
 1.6MHz 385  
 1.8MHz 385  
 1.8432M 290  
 2.0MHz 240  
 2.4678M 220  
 3.2768M 220  
 5.7194M 300  
 3.5850M 300  
 4.0MHz 290  
 4.032MHz 290  
 4.80MHz 290  
 4.194304M 200  
 4.433619M 200  
 5.0MHz 200  
 6.186MHz 300  
 6.242MHz 300  
 6.144MHz 240  
 6.5536MHz 200  
 7.168MHz 250  
 7.68MHz 200  
 8.0MHz 200  
 8.88732M 240  
 9.00MHz 200  
 10.0MHz 200  
 10.24MHz 200  
 10.7 220  
 12.0MHz 220  
 14.31814M 320  
 16.0MHz 250  
 18.0MHz 240  
 18.432M 240  
 19.3888M 325  
 24.0MHz 200  
 28.8MHz 200  
 27.648M 330  
 27.145M 290  
 38.86987M 240  
 48.0MHz 290  
 100.0MHz 375  
 116.0MHz 300

**RELAYS**

REED, Encapsulated, Single Pole, SW Normally Open, 200mA, 50V DC

RL12	7001 6V to 9V	120p
RL13	1K11 9V to 12V	120p
RL14	1K11 12V to 18V	120p
RL15	3K11 18V to 30V	135p

Single Pole, Change Over  
 RL16 1K11 4V to 10V 295p  
 RL17 1K11 9V to 12V 295p

Double Pole, Normally Open  
 RL18 3501 9V to 12V 200p

Miniature, enclosed, PCB mount. Our RL8 series  
 S.P.C.O.  
 RL6-91 17011 coil, 7V5 to 12V DC 380V/6A AC, 1300VA/50W 210p  
 D.P.C.O.  
 4311 coil, 4V2-7V DC, 250V AC; 5A; 1100VA/150W 218p  
 RL6-111 17011 coil, 8V-14V; 250V AC 5A 220p  
 RL6-114 74011 coil, 17V5-29V 250V 5A 11A 222p

CONTINENTAL Credia Type Relays. Miniature Plug-in relays. 110V DC; 1 2V AC; 2 A/D C; 2.5 A AC 30W/100VA  
 2 pole c/wover 1851; 6V-18V RL201 180p  
 RL202 180p  
 4 pole c/wover 9V to 18V; 1851L RL211 220p  
 High Power "Heavy Duty" PCB Mounting, Credia type  
 S.P.C.O. Power Gain: 1:8000 380V AC/16A; 3.5K VA. 8 to 19V; 190M 296p

**TRANSFORMERS**

Prim. 240V  
 6.0-6V; 9.0-9V; 12.0-12V 100mA 98p  
 pcb mounting, Miniature, Split Bobbin  
 3VA: 2x6V-0.25A, 2x9V-0.15A; 2x12V-0.12A;  
 2x15V-0.1A 290p  
 6VA: 2x6V-0.5A; 2x9V-0.3A; 2x12V-0.25A;  
 2x15V-0.2A 270p  
 Standard Split Bobbin type:  
 6VA: 2x6V-0.5A; 2x9V-0.4A; 2x12V-0.3A;  
 2x15V-0.25A 220p  
 12VA: 2x4.5V-1.3A; 2x6V-1A; 2x9V-0.6A;  
 2x12V-0.5A; 2x15V-0.4A; 2x20V-0.3A 285p (35p p&P)  
 24VA: 2x6V-1.5A; 2x9V-1.2A; 2x12V-1A;  
 2x15V-0.8A; 2x20V-0.6A 330p (60p p&P)  
 50VA: 2x6V-4A; 2x9V-2.5A; 2x12V-2A; 2x15V-1.5A; 2x20V-1.2A; 2x25V-1A; 2x30V-0.8A 440p (150p p&P)  
 100VA: 2x12V-2A; 2x15V-3A; 2x20V-2.5A;  
 2x25V-2A; 2x30V-1.5A; 2x50V-1A 820p (75p p&P charge to be added over and above our normal postal charge).

**JUMPER LEADS (Ribbon Cable Assembly)**

Length	14 pin	16 pin	24 pin	40 pin
24 inches	145p	185p	240p	390p
	Double ended DIP Jumper			
6 inches	185p	305p	300p	485p
12 inches	185p	216p	316p	480p
24 inches	210p	236p	346p	540p
30 inches	230p	250p	376p	590p

IEEE 124 (2 way) 675p  
 Centronic parallel (36 way) 850p

**VOLTAGE REGULATORS**

+ve	metal case	-ve
1A TD3	7805	7905
5V	7805	7905
12V	7812	7912
15V	7815	7915
18V	7818	7918

1A TO220 Plastic Casing  
 5V 7805 46p  
 12V 7812 50p  
 15V 7815 50p  
 18V 7818 50p  
 24V 7824 50p

100mA TO92 Plastic Casing  
 5V 78L05 30p  
 6V 78L62 30p  
 8V 78L82 30p  
 12V 78L12 30p  
 15V 78L15 30p

**D CONNECTORS**

Plugs	Sockets	Covers
3way 95p	125p	145p
15way 135p	195p	150p
25way 170p	230p	190p
37way 220p	290p	185p

Soldercon Pins  
 100 pins 70p  
 500 pins 325p

**25 way D CONNECTORS**

PCB Pins 200p  
 RT, angle 210p  
 275p

We stock many more Plugs, Sockets and Jumper Leads.

**25way D CONNECTOR**  
 Jumper Lead Cable Assembly  
 18" long, Single End, Male 500p  
 18" long, Single End, Female 870p  
 36" long, Double Ended, M/M 1325p  
 36" long, Double Ended, F/F 1315p  
 36" long, Double Ended, M/F 1275p

**ANTEX SOLDERING IRON**

C-15W 430p  
 CCN-15W 440p  
 CX17W 430p  
 CX25W 445p

Spare tips, assorted sizes 80p  
 Spare Elements 210p  
 Iron stand with sponge 160p

**ASTEC UHF MODULATORS**

Standard 6MHz 280p  
 Wideband 8MHz 425p

**BUZZERS, miniature, solid-state**

5V; 9V & 12V 70p

**LOUDSPEAKERS**  
 Miniature, 0.3W; 8Ω:  
 Zn, 3 1/2in, 2 1/2in 80p  
 2 1/2in 4011, 6411 or 8011 80p

**GAS BUBBLE DETECTORS**  
 For the detection of combustible and Toxic Gases like: Propane, Butane, Methane, Ammonia, Carbon Monoxide, Sulphur and Organic solvents vapours like Alcohol, Benzene, etc. Ideal for use in Booths, Caravans etc.  
 Type: TG812 & 813 525p  
 Socket for above 40p

**CMOS**

4000	14	4073	20	4532	110
4001	14	4075	20	4534	500
4002	14	4076	60	4536	295
4006	08	4077	28	4538	115
4007	18	4078	28	4539	115
4008	02	4081	28	4541	140
4009	26	4082	21	4543	135
4010	40	4085	65	4547	35
4011	15	4086	70	4549	395
4012	18	4089	140	4553	299
4013	34	4093	43	4554	190
4014	75	4094	168	4555	50
4015	68	4095	90	4556	55
4016	32	4096	90	4557	320
4017	48	4101	39	4561	320
4018	08	4098	08	4559	395
4019	42	4099	95	4560	180
4020	61	4100	95	4561	104
4021	70	4161	99	4562	485
4022	06	4162	99	4566	175
4023	20	4163	99	4568	260
4024	45	4174	99	4569	175
4025	19	4175	106	4569	175
4026	130	4192	001	4560	460
4027	38	4194	106	4581	250
4028	58	4408	780	4582	99
4029	77	4409	780	4583	99
4030	90	4410	725	4584	48
4031	170	4411	895	4685	99
4032	125	4412	895	4686	330
4033	185	4415	480	4598	290
4034	185	4419	280	4599	595
4035	95	4422	770	4097	88
4036	275	4428	00	40098	183
4037	115	4433	770	40100	215
4038	110	4435	860	40101	130
4039	220	4436	895	40102	180
4040	59	4450	395	40103	175
4041	78	4451	350	40104	95
4042	80	4490	350	40105	115
4043	70	4500	675	40106	75
4044	85	4501	28	40107	60
4045	170	4502	90	40108	450
4046	75	4503	895	40109	100
4047	75	4504	108	40110	300
4048	55	4506	65	40114	240
4049	30	4507	40	40116	194
4050	30	4508	265	40163	90
4051	78	4510	68	40174	85
4052	78	4511	68	40176	60
4053	78	4512	75	40181	220
4054	128	4513	895	40182	90
4055	125	4514	195	40192	80
4056	120	4515	198	40193	90
4057	1818	4516	75	40194	90
4059	480	4517	415	40257	195
4060	90	4518	42		
4061	1225	4519	29		
4062	895	4520	78		
4063	485	4521	200		
4064	38	4522	125		
4067	399	4526	95		
4068	22	4527	115		
4069	20	4528	80		
4070	26	4529	150		
4071	20	4530	90		
4072	20	4531	130		

**OPTO ELECTRONICS**

**LEDs with Clips**  
 TL1209 Red 13  
 TL1211 Grn. 17  
 TL1212 Yel. 18  
 TL1220 2" Red 14  
 2" Green, Yellow or Amber 18  
 0.2" Bi-colour  
 Red/Green 85p  
 Green/Yellow 78p  
 0.2" Tri colour  
 Red/Green/Yellow 85p

**Square LEDs, Red, Green, Yellow, 30**  
 Triangular LEDs,  
 Red 18  
 Green or yellow 22

**LD271 Infra Red 46**  
 SFH205 Detector 91  
 TL132 Infra Red 58  
 TL138 Detector 45  
 TL139 40  
 TL100 80  
 BARGRAPH, Red 10 segments 225

**ISOLATORS**  
 IL74 55  
 TIL111/2/4 90  
 #433 Photo Darlington 135

**7 Segment Displays**  
 TIL307 675  
 TIL312 3" CC 105  
 TIL313 3" CC 105  
 TIL321 5" CC 115  
 TIL322 3" CC 115  
 DL704 3" CC 99  
 DL707 3" CC 99  
 DL747 6" CC 180  
 8" Orange CA 280  
 FND357 Red 120  
 FND500 115  
 5" Green CA 190  
 5" Red CA 215  
 3" Red CA 150  
 3" Green CA 150  
 DVM178 1885  
 LCD 3 Digits 585  
 LCD 4 Digits 850  
 LCD 6 Digits 760

**NEON with resistor, push fit, 250V mains, Round:**  
 Red or Amber 30p  
 Rectangular, 100V: Red, Amber, Green 30p  
 TL139 170p  
 Reflective Optical Switch 295p

**COMPUTER CORNER**

**VIC 20** Micro Computer. Connects directly to a colour TV. Still only £185

- VIC Cassette Deck including a free 6 programme Cassette... £34
- EPSON MX80T 10" Tractor Feed, 9 x 9 matrix, 80 column, Speed 80 CPS, Bi-directional, Centronics interface, Baud rate 110-9600 (RS232C)... £316
- EPSON MX80FT Has Friction feed & Tractor feed plus all the MX80's facilities... £345
- EPSON MX80FT2 Has high resolution Graphics option plus all the MX80FT's facilities... £390
- EPSON MX100 132 Column Printer plus has all the facilities of MX80FT2. Value for money... £495
- SOFTY-2 As reviewed in PE Sept. '81 by Dr. A. Berk. The complete microprocessor development system for Engineers and beginners alike. New powerful Instructions. Accepts any 24 pin 5V single rail EPROM. Supplied fully built, tested. Enclosed in a black ABS case. Plug-in power supply included... £189
- VIDEO MONITOR 9", fully cased & guaranteed. B & W. Excellent value for money... £79
- TEX EPROM ERASER Erases up to 32 ICs in 15-30 minutes... £33
- SPARE 'UV' Lamp bulb... £9
- 5V/5A Power Supply Ready-built & tested... £25
- ABS CASE Attractive, Beige/Brown for Superboard, UK101 NASCOM, or Home brew... £25</

# Sinclair ZX81 Personal Comp the heart of a system that grows with you.

1980 saw a genuine breakthrough – the Sinclair ZX80, world's first complete personal computer for under £100. Not surprisingly, over 50,000 were sold.

In March 1981, the Sinclair lead increased dramatically. For just £69.95 the Sinclair ZX81 offers even more advanced facilities at an even lower price. Initially, even we were surprised by the demand – over 50,000 in the first 3 months!

Today, the Sinclair ZX81 is the heart of a computer system. You can add 16-times more memory with the ZX RAM pack. The ZX Printer offers an unbeatable combination of performance and price. And the ZX Software library is growing every day.

## Lower price: higher capability

With the ZX81, it's still very simple to teach yourself computing, but the ZX81 packs even greater working capability than the ZX80.

It uses the same micro-processor, but incorporates a new, more powerful 8K BASIC ROM – the 'trained intelligence' of the computer. This chip works in decimals, handles logs and trig, allows you to plot graphs, and builds up animated displays.

And the ZX81 incorporates other operation refinements – the facility to load and save named programs on cassette, for example, and to drive the new ZX Printer.



**New BASIC manual**

Every ZX81 comes with a comprehensive, specially-written manual – a complete course in BASIC programming, from first principles to complex programs.

## Kit: £49.<sup>95</sup>

### Higher specification, lower price – how's it done?

Quite simply, by design. The ZX80 reduced the chips in a working computer from 40 or so, to 21. The ZX81 reduces the 21 to 4!

The secret lies in a totally new master chip. Designed by Sinclair and custom-built in Britain, this unique chip replaces 18 chips from the ZX80!

### New, improved specification

- Z80A micro-processor – new faster version of the famous Z80 chip, widely recognised as the best ever made.
- Unique 'one-touch' key word entry: the ZX81 eliminates a great deal of tiresome typing. Key words (RUN, LIST, PRINT, etc.) have their own single-key entry.
- Unique syntax-check and report codes identify programming errors immediately.
- Full range of mathematical and scientific functions accurate to eight decimal places.
- Graph-drawing and animated-display facilities.
- Multi-dimensional string and numerical arrays.
- Up to 26 FOR/NEXT loops.
- Randomise function – useful for games as well as serious applications.
- Cassette LOAD and SAVE with named programs.
- 1K-byte RAM expandable to 16K bytes with Sinclair RAM pack.
- Able to drive the new Sinclair printer.
- Advanced 4-chip design: micro-processor, ROM, RAM, plus master chip – unique, custom-built chip replacing 18 ZX80 chips.



## Built: £69.<sup>95</sup>

### Kit or built – it's up to you!

You'll be surprised how easy the ZX81 kit is to build: just four chips to assemble (plus, of course the other discrete components) – a few hours' work with a fine-tipped soldering iron. And you may already have a suitable mains adaptor – 600 mA at 9 V DC nominal unregulated (supplied with built version).

Kit and built versions come complete with all leads to connect to your TV (colour or black and white) and cassette recorder.



uter-



## 16K-byte RAM pack for massive add-on memory.

Designed as a complete module to fit your Sinclair ZX80 or ZX81, the RAM pack simply plugs into the existing expansion port at the rear of the computer to multiply your data/program storage by 16!

Use it for long and complex programs or as a personal database. Yet it costs as little as half the price of competitive additional memory.

With the RAM pack, you can also run some of the more sophisticated ZX Software – the Business & Household management systems for example.

## Available now - the ZX Printer for only £49.<sup>95</sup>

Designed exclusively for use with the ZX81 (and ZX80 with 8K BASIC ROM), the printer offers full alpha-numerics and highly sophisticated graphics.

A special feature is COPY, which prints out exactly what is on the whole TV screen without the need for further instructions.

At last you can have a hard copy of your program listings – particularly

useful when writing or editing programs.

And of course you can print out your results for permanent records or sending to a friend.

Printing speed is 50 characters per second, with 32 characters per line and 9 lines per vertical inch.

The ZX Printer connects to the rear of your computer – using a stackable connector so you can plug in a RAM pack as well. A roll of paper (65 ft long x 4 in wide) is supplied, along with full instructions.

### How to order your ZX81

BY PHONE – Access, Barclaycard or Trustcard holders can call 01-200 0200 for personal attention 24 hours a day, every day.

BY FREEPOST – use the no-stamp-needed coupon below. You can pay

by cheque, postal order, Access, Barclaycard or Trustcard.

EITHER WAY – please allow up to 28 days for delivery. And there's a 14-day money-back option. We want you to be satisfied beyond doubt – and we have no doubt that you will be.

To: Sinclair Research Ltd, FREEPOST, Camberley, Surrey, GU15 3BR.				Order
Qty	Item	Code	Item price £	Total £
	Sinclair ZX81 Personal Computer kit(s). Price includes ZX81 BASIC manual, excludes mains adaptor.	12	49.95	
	Ready-assembled Sinclair ZX81 Personal Computer(s). Price includes ZX81 BASIC manual and mains adaptor.	11	69.95	
	Mains Adaptor(s) (600 mA at 9 V DC nominal unregulated).	10	8.95	
	16K-BYTE RAM pack.	18	49.95	
	Sinclair ZX Printer.	27	49.95	
	8K BASIC ROM to fit ZX80.	17	19.95	
	Post and Packing.			2.95

Please tick if you require a VAT receipt

TOTAL £

\*I enclose a cheque/postal order payable to Sinclair Research Ltd, for £

\*Please charge to my Access/Barclaycard/Trustcard account no.

\*Please delete/complete as applicable.

Please print

Name: Mr/Mrs/Miss

Address:

FREEPOST – no stamp needed. Offer applies to UK only.


ET1 04

# sinclair ZX81

6 Kings Parade, Cambridge, Cambs., CB2 1SN.  
Tel: (0276) 86104 & 21282.
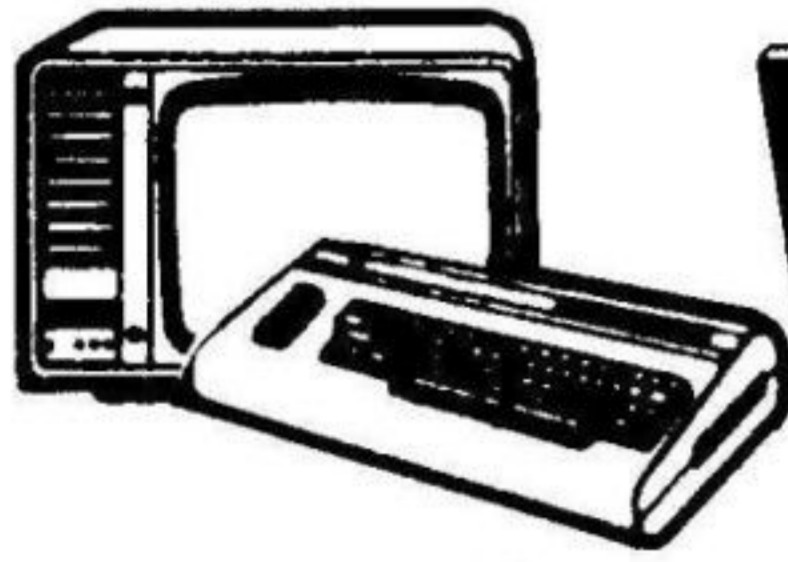
# COMBINED FORCES!

South East Computers PLUS Castle Electronics can now offer you Unequaled Service - at Supermarket Prices!




## VIC-20 COLOUR COMPUTER

- Graphics character set ●Plug-in programme/memory cartridges
- Colour ●Sound ●Programmable function keys ●5K memory expandable to 32K
- Standard PETBASIC ●Full-size typewriter keyboard
- Low-priced peripherals ●Joystick/paddles/lightpen
- Self teaching materials ●Cassette Deck now available £44.95

Only £189-95 INC. VAT

You won't find a Better Deal Anywhere in the South

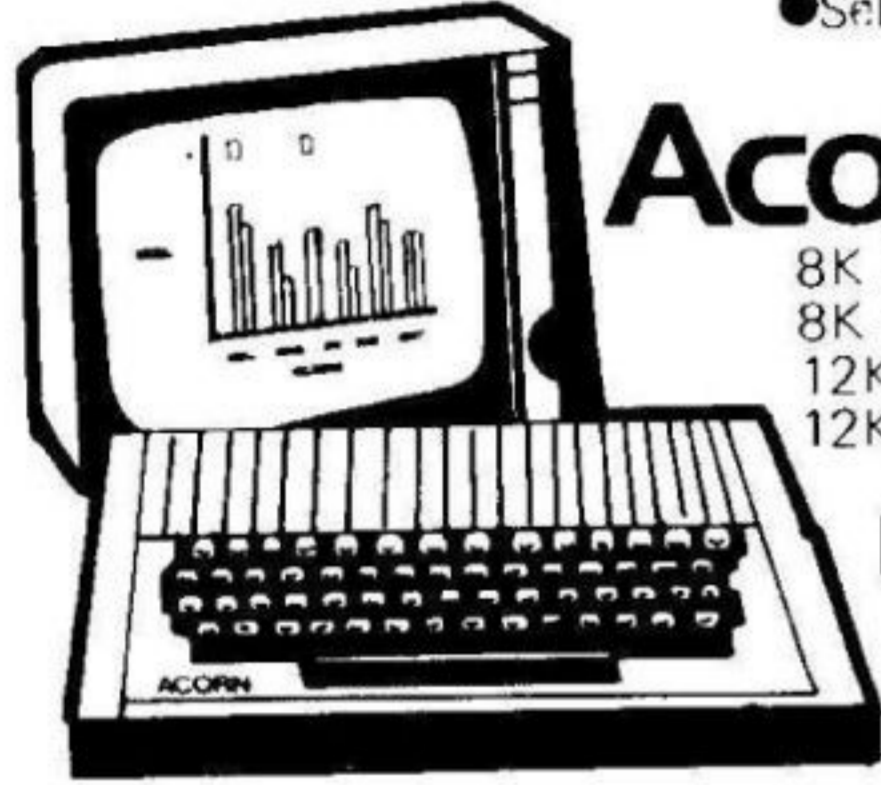BBC MICRO-COMPUTER NOW IN STOCK PLUS FULL RANGE OF ACCESSORIES



## Acorn Atom BRITISH DESIGNED PERSONAL COMPUTER

8K ROM + 2K RAM kit .....	£140.00	4K Floating Point ROM .....	£ 23.00
8K ROM + 2K RAM Ass. ....	£174.50	Colour Encoder .....	£ 21.85
12K ROM + 12K RAM kit .....	£255.00	Mains Power Supply .....	£ 9.20
12K ROM + 12K RAM Ass. ....	£289.50		

## TANGERINE microtan


Microtan 65 Kit .....	£79.35
Microtan 65 Built .....	£90.85
Tanex Min. Config. Kit.....	£49.45
20 way Keypad .....	£11.50

TANTEL PRESTEL ADAPTER - £199.00

We hold a complete stock of all the Tangerine equipment. Send SAE or Phone for details.



COMPUTERS FOR PEOPLE

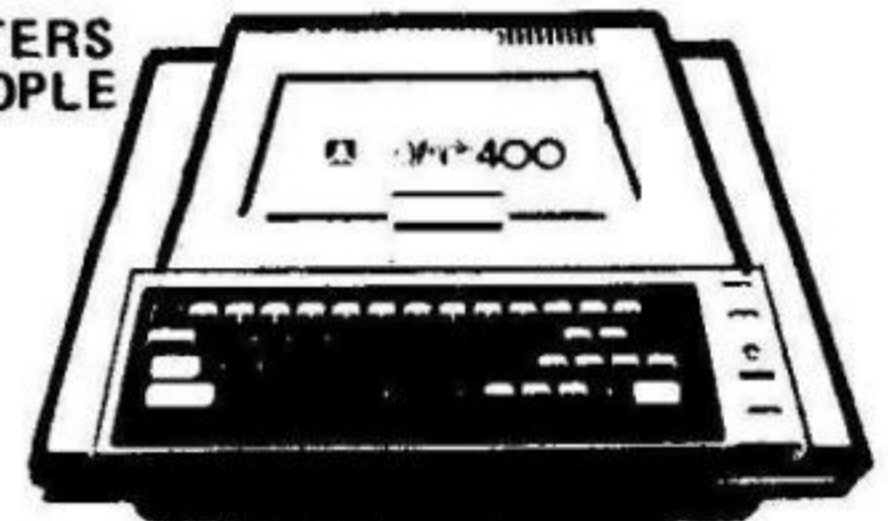

FROM £345.00 Plus All Accessories Available!

Model 400 16K .....	£345.00
Model 800 16K .....	£645.00
Cassette .....	£ 50.00
Disk Drive .....	£345.00
80 Col. Printer .....	£550.00



## COMMODORE PET

8K PET .....	£458.85
16K PET .....	£550.00
32K PET .....	£699.00
Dual Disk Drive .....	£799.00
Printer .....	£454.25
External Cassette .....	£ 44.95

Complete range of PET equipment in Stock

CASSETTE SOFTWARE: Strathclyde Basic Course, Basic Basic Course, Invaders, Treasure Trove of Games 1 to 10 (10 Selections of games), Basic Maths, Algebra, Statistical Packs and lots more!

Special Offer!


sinclair ZX81 FOR IMMEDIATE DESPATCH £69.99



BUILT-IN SOUND-HIGH RES. GRAPHICS'

Apple II Plus 48K .....	£790.00
Disk Drive + Controller .....	£383.00
D.D. without Cntrlr .....	£303.00
Pascal Card .....	£264.00
Eurocolour Card .....	£73.00
Hitachi 9" Monitor .....	£146.00

We Stock All the Goodies for Apple!

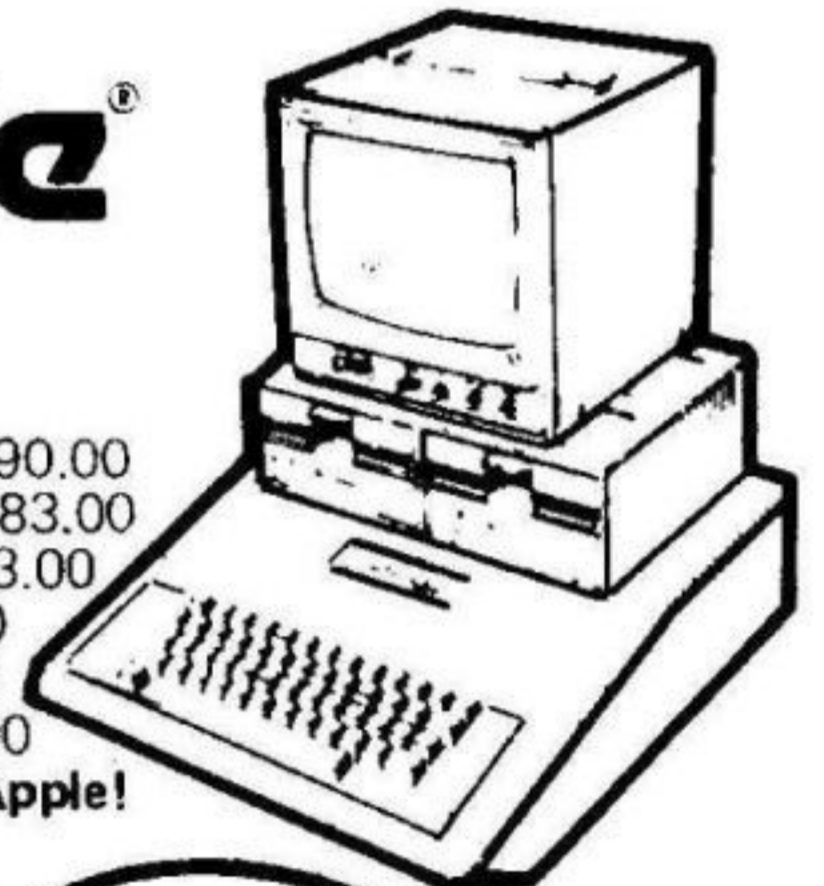

WE SPECIALISE IN COST EFFECTIVE SYSTEMS FOR SMALLER BUSINESSES

ALL PRICES INCLUDE VAT : ACCESS & BARCLAYCARD WELCOME ORDERS NORMALLY DESPATCHED DAY OF RECEIPT

## MicroComputers for Business

ASK FOR DETAILS OF OUR TOTAL SUPPORT OPTION

From Only £19 per week

### Package A

#### SILICON OFFICE SYSTEM

- 1 x CBM 8096 Computer
- 1 x CBM 8050 Dual Disk Drive
- 1 x CBM 8023 Matrix Printer
- Connecting cables, plus Silicon Software

From Only £43 per week

### Package B

#### ALTOS MULTI-USER HARD DISK SYSTEM

- 1 x ALTOS 8000/10 Computer with 10 Mbyte Hard Disk
- 208Kbyte Memory (4 users)
- 500Kbyte Floppy Disk Drive
- 2 x TVI 912C VDU's
- 1 x OKI Microline 83A Printer

ALL PERSONAL COMPUTER ENQUIRIES:- Contact Paul Brown or Sam Wright on Hastings (0424) 437875 (Formerly Castle Electronics)

FOR ALL BUSINESS SYSTEMS ENQUIRIES:- Phone Nick Rosenberg on Hastings (0424) 426844


SEC BUSINESS SYSTEMS SUPPLY A WIDE RANGE OF EASY-TO-OPERATE SYSTEMS AND PROGRAMMES TO MEET ALL OF TODAY'S BUSINESS NEEDS + FULL RANGE OF COMPUTER RELATED PRODUCTS + LEASING AGREEMENTS + FULL AFTER SALES SERVICE

**SEC** The Complete Computer Service!

15 CASTLE STREET, HASTINGS, EAST SUSSEX TN34 3DY DEPT. ET4



# DIGEST

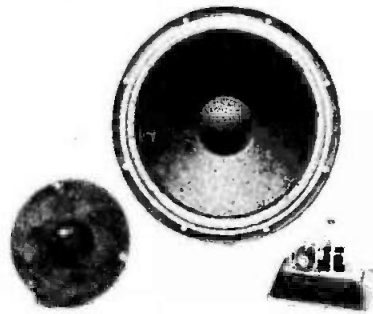

## ETI PRICE DECREASE

Readers will have no doubt noticed (painfully!) the cover price increase on this issue of ETI. We apologise for this, but are happy to say it is ONLY FOR THIS ISSUE and the price returns to 75p with the May issue.

The one-month jump was made necessary by the sheer size of this special issue. We hope you will agree it is worth it. If you could see the price of paper these days...(moan, moan).

Thank you for sticking with us through thick and thin... (and 10p!)

## Tempus Fugit

It's felt a little uncomfortable working in the ETI office this month; must be something to do with the sackcloth and ashes we're wearing. During the last few issues several of our reviews have featured Casio products, but we have consistently failed to credit the company which lent us the review models. The kindly folk in question are Tempus of 38 Burleigh Street, Cambridge CB1 1DG and we'd like to thank them for all the help they've been giving us. Tempus are leading Casio specialists and if there's something from Casio you're having problems obtaining, they will doubtless be as nice to customers as they are to us.

## Sun-Day Driving

A Volkswagen Dasher car is presently being tested carrying a roof-rack of AEG-Telefunken solar modules which convert solar energy directly into electric current. The small 160 W 'solar power plant' of the test car complements the dynamo and charges the battery. This means that fuel consumption can be reduced by approximately five percent. As yet the cost of manufacturing these solar panels makes them uneconomical to use, but with the rising prices of fuel, it is foreseeable that low-priced solar generators will enter the market. Not only that, future car generations will make increased use of electricity, for example with automatic start-stop devices and pollution-free electrical energy for air conditioning in cars in warm countries. Great idea — but where will you put the luggage?



## Tweeters That Go Cheap

Well, not just the tweeters, in fact. Mullard have a 40 W speaker system consisting of an 8" woofer as well as a high-power textile dome tweeter. They form part of a new low-price, two-way, self-build audio kit (whew!) being marketed by BK Electronics. The

BK Electronics crossover unit have been combined with spring-loaded terminals and recessed mounting panel. The complete system, when built into the 23 litre enclosure, is capable of handling 40 W comfortably. All this for the small outlay of £13.90 plus VAT and £1.50 carriage per kit! Get yours now from BK Electronics Ltd, 37 Whitehouse Meadows, Eastwood, Leigh-On-Sea, Essex SS9 5TY.



## Heading For The Top

Headphones seem to be getting lighter and smaller these days, so Sennheiser, that well-known manufacturer of headphones, has decided to launch a pair of their own lightweight 'phones. The new model HD40 is soon to be released in the UK and weighs only 60 grammes with extremely light contact pressure. They can be supplied with either a three or seven metre lead, the seven metre variety incorporating a volume control in the lead so that you don't have to march all that way back to the amp if it's too loud. Another feature is that each ear-piece can be revolved on the headband by 90 degrees if you have a funny shaped head or if you want to store them compactly (!). The Sennheiser HD40 will be launched in the UK with a suggested selling price, including VAT, of £16.55. For those of you interested in technical specs; frequency response is 22 to 18,000 Hz, impedance is 600 ohms, characteristic SPL is 90 dB and distortion factor < 1.2%.

## Electroware, OK?

OK Machine and Tool (UK) Ltd have launched a new division aimed at providing the electronics user with a really wide range of electronic hardware. All the products in the range will be available to everyone involved in building electronic equipment — that includes engineers, students, teaching staff, laboratory technicians and, not least, the hobbyist. The 40-page catalogue contains various products selected from OK's bench tool range — plus some new items — and includes soldering irons, wire-wrapping kits, IC tools, PCBs, cases, enclosures, connectors, sockets and test instruments to name just a few. Electroware is distributed throughout the UK by leading electronic and computer stores. Catalogues are free, but send 30p for postage and packing. If you want any further information or one of their catalogues contact OK Machine & Tool (UK) Ltd, Dutton Lane, Eastleigh, Hants SO5 4AA.

# Lack of ZX81 memory giving you headaches..?



## The Memotech 64K Memopak

The growth of interest in computer use caused by the introduction of the Sinclair ZX81 has made new and exciting demands on the ingenuity of electronic engineers. At Memotech we have focused our attention on the design of an inexpensive, reliable memory extension.

The Memopak is a 64K RAM pack which extends the memory of the ZX81 by a further 56K. Following the success of our 48K memory board the new memory extension is designed to be within the price range expected by Sinclair users. It plugs directly into the back of the ZX81 and does not inhibit the use of the printer or other add-on boards. There is no need for an additional power supply or for leads.

The Memopak together with the ZX81 gives a full 64K, which is neither switched nor paged, and is directly addressable. The unit is user transparent and accepts such basic commands as 10 DIM A(9000)

0-8K ...Sinclair ROM

8-16K...Memopak memory which can switch in or out in 4K blocks to leave space for memory mapping.


12-16K...Memopak memory which holds its contents during cassette loads and allows communication between programmes.

16-32K...This area can be used for basic programmes and assembly language routines.

32-64K...32K of RAM memory for basic variables and large arrays.

With the Memopak extension the ZX81 is transformed into a powerful computer, suitable for business, leisure and educational use, at a fraction of the cost of comparable systems.

**64K-£79**

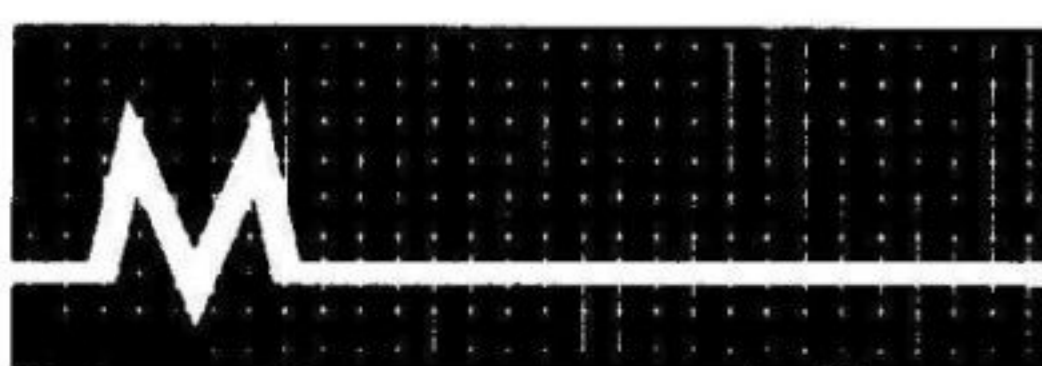

**MEMOTECH**

Memotech Ltd  
3 Collins Street  
Oxford · OX4 1XL  
Tel · 722102/3/4/5

Please debit my  
BARCLAYCARD/ACCESS\*  
account number:

\*Please delete  
whichever does not apply.

Signature



Date

NAME

ADDRESS

To: Memotech Ltd., 3 Collins Street, Oxford, OX4 1XL Telephone (0865) 722102

Please rush me:

	Quantity	Price	Total
64K RAM, Assembled		£68.69	
Stock Control Programme		£ 25.00	
Payroll Programme		£ 25.00	

VAT @ 15%


Postage £2.00

ETI TOTAL
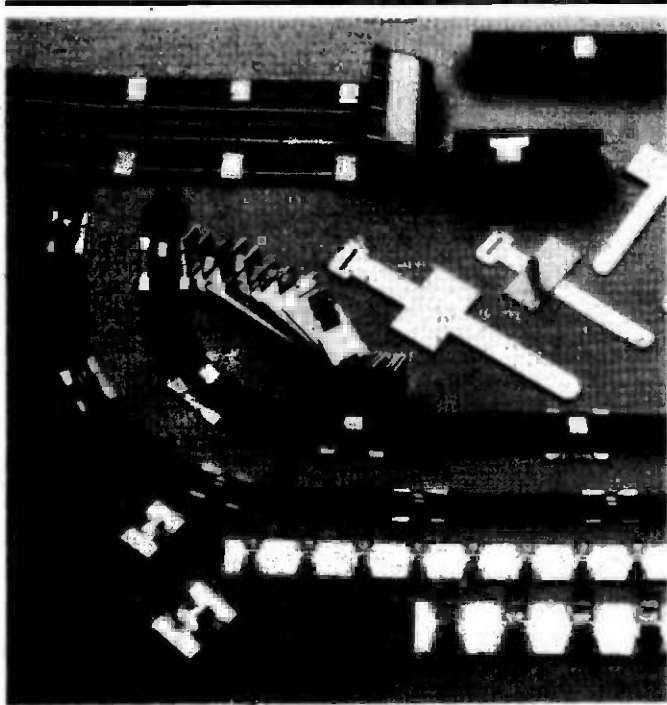
## High-res Printing

New from Hi-Tek is the Facit 4542, a high-speed, high-resolution printer which combines a new type of 'Flexhammer' print-head with advanced microprocessor control to make it equally suited to text printing, label or bar code production, and graphics output. Using 260-character-per-second bidirectional two-colour printing and a 14x9 dot-matrix format, the 4542 can produce a virtually unlimited range of characters as well as different grey scales in graphics applications. In normal text-printing applications, the 4542 features proportional spacing, justified right-hand margin and an extensive set of up to 512 characters in 11 national reper-toirs with red/black, elongated and underlining facilities. For label printing, a variable-size option is

available which allows characters or bar codes to be generated in 95 different sizes from 2.52 mm up to 240 mm. Selection of size and position is easily controlled by software commands. In the graphics mode, scanning, semi-graphics and 10 levels of grey/red scale are available to illustrate reports with histograms, curves and diagrams, as well as generating half-tone illustrations in applications such as tomography, process monitoring and computer-aided design. The key to the versatility of the 4542 is the print-head, which consists of a set of nine stored-force flexible metal hammers mounted directly on a magnet armature. No adjustment or lubrication is necessary, wear is minimal, and a 'floating' mount means that the correct paper/print-head distance is always maintained irrespective of the paper thickness or number of copies. Further information is available from Hi-Tek Distribution Limited, Trafalgar Way, Bar Hill, Cambridge, CB3 85Q.




## BT Bill Beater

Following the success of the Telcost TNA25 from the Ansafone Corporation, it was decided that a single line unit should be manufactured. The new machine offers a range of functions which are all designed to save money by monitoring telephone use. Ansafone's single line Telcost 1 has features including a 24-hour clock display, which instantly shows the cost of a call as soon as a user is connected with a number dialled. The unit also has a built-in printer which records details of the call including cost and number dialled. It also prints out the date, time, machine identification number and the duration of the call. Telcost 1 has a built-in memory which retains information even if the machine is disconnected from a power source. It also gives a special security midnight printout each night which frustrates any attempts to conceal the day's telephone costs by the destruction of the daily printout sheet. The machine is virtually tamper-proof as the printout will indicate if it has been disconnected from the line at any time, or if any information parameters have been changed. The machine has provision for it to be reprogrammed at any time to enable the user to keep in line with British Telecom unit rate charges and the date, time and identification number can be changed for any reason if the machine is moved to a new location. This desk-top unit is no bigger than a telephone and for an investment of around £249 could help to cut out the abuse of telephones in both large and small companies.
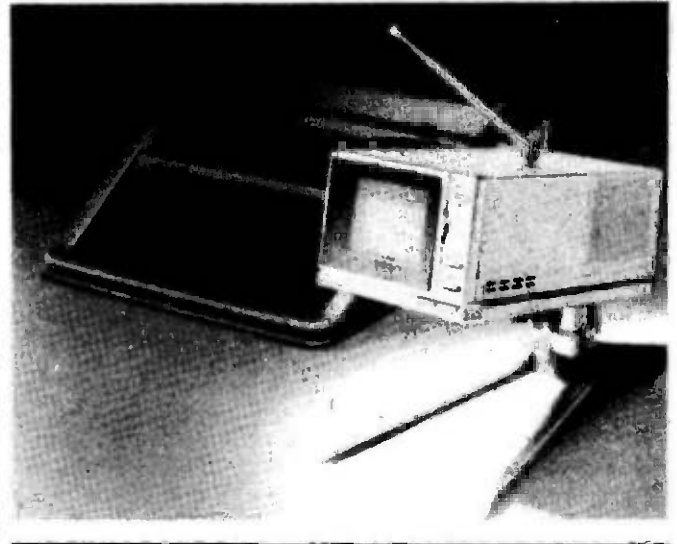
## Small And Beautiful

Hailed as 'the World's Smallest, Lightest and Lowest Power Consumption' television, the TH3-W3V from Matsushita certainly caught our editorial eye. Closer inspection revealed a colour TV set with a 3" colour picture tube, only 115 mm x 86 mm x 323.5 mm in size and 1.5 kg in weight. Power consumption is a mere 9.5 W and it operates on AC power, car batteries and on optionally available rechargeable batteries. Yet, despite its small size, it is equipped with video input/output terminals and operates as a colour monitor and a video tuner when connected to a video camera and a portable VTR, respectively. This 3" colour TV was launched on to the Japanese market in mid-December 1981 at the approximate price of £200. It is due for launch in the US in June this year and, hopefully, will be seen in this country shortly after. Further details will be supplied by National Panasonic (UK) Ltd, 300/313 Bath Road, Slough SL1 6JB.



## Sticky Clips

Brandauer adhesive cable clips from Stotron provide an inexpensive method of fixing round or ribbon cables to clean, dry surfaces. The range can handle round cables from just a few millimeters up to 19 mm and flat ribbon cables from 13 mm to 75 mm can be accommodated by a selection of clips with widths in stages of 6 mm. The adhesive is instant acting and polyethylene pads provide high levels of insulation, where necessary. Further information is available from Stotron Ltd, Unit 1, Haywood Way, Ivyhouse Lane, Hastings, East Sussex.

## Video Victory

Thorn EMI have just announced that agreements have been signed with Telefunken and JVC to form a holding company for the manufacture of video consumer electronics products in Europe. Thomson-Brandt was originally intended as a fourth partner, but this was not possible. However, the three other parties hope an opportunity will arise for Thomson-Brandt to join the venture.

Products manufactured by the joint venture will include VHS video cassette recorders, VHD video disc players and video cameras.



# Rapid Electronics

Tel: 0322 863494  
Hillcroft House  
Station Road  
Eynsford, Kent DA4 0EJ



LINEAR		CA3162E	450	LM377	150	LM3900	50	NE566	150	TAD1024	125
★709	25	CA3189E	290	★LM380	65	LM3909	70	NE567	100	TLO71	45
★741	14	ICL7106	790	★LM381	100	LM3911	120	NE571	425	TLO72	75
748	35	ICL8038	320	★LM382	120	★LM3914	200	RC4136	90	TLO84	90
AY-3-1270	840	ICM7555	80	★LM386	65	★LM3915	200	SN76018	150	XR2206	300
AY-3-8910	700	★LF351	40	★LM387	120	LM13600	120	SN76477	150	ZN414	100
★AY-3-8912		LF353	85	★LM393	100	MC1310	150	TBA641B11250	150	ZN423	195
	625	LF356	90	★LM709	25	MC3302	150	TBA800	80	ZN424	135
CA3046	60	LM10	395	LM710	50	MC3340	135	TBA810	95	ZN425E	390
CA3080	65	★LM301A	25	LM725	350	NE515	270	TBA820	80	ZN426E	330
CA3089	215	LM311	70	LM733	75	NE529	225	TBA950	290	ZN427E	650
CA3090AQ	375	LM318	85	★LM741	14	NE531	150	TCA940	170	ZN428E	480
CA3130E	90	★LM324	40	LM747	75	NE544	185	TDA1004	300	ZN1034E	200
CA3140E	45	★LM339	50	LM748	35	★NE555	16	TDA1008	320		
CA3160E	100	LM348	90	★LM1458	40	★NE556	45	TDA1010	225		
CA3161E	140	LM358	50	LM2917	200	NE565	120	TDA1022	560		

CMOS		★4017	43	4016	285	4055	115	4082	20	4502	70	4529	150
4000	14	4018	60	4039	295	4059	480	4085	65	4503	50	4532	95
★4001	12	4019	35	4040	55	4060	85	4086	65	4507	38	4534	495
4002	14	★4020	55	4041	75	4063	90	4089	140	4508	200	4538	110
4006	65	4021	65	4042	55	4066	35	★4093	33	4510	65	4543	110
4007	17	4022	70	4043	60	4067	395	4094	14	★4511	50	4549	380
4008	58	4023	18	4044	65	★4068	15	4095	90	4512	70	4553	295
4009	30	4024	40	4045	70	4069	18	4097	340	4514	180	4555	45
4010	35	★4026	96	4046	55	4071	18	4099	95	4516	75	4559	390
★4011	13	4027	30	★4049	28	4072	18	40106	50	★4518	45	4560	180
4012	17	4028	55	4050	28	4073	20	40109	100	4520	70	4584	45
★4011	22	4029	75	4051	60	4075	20	40163	100	4521	200	4585	99
4014	60	4030	35	4052	70	4076	60	40173	100	4526	80	4724	140
4015	60	4031	170	4053	60	4077	25	40175	100	4527	90		
★4016	22	4034	170	4054	110	4081	18	40193	120	★4528	75		

TTL		7413	24	7442	40	7480	45	74107	30	74155	60	74177	75
7400	11	7414	35	7444	85	7482	70	74109	32	74156	60	74179	65
7401	11	7415	25	7446	60	7483	50	74121	28	74157	43	74180	65
7402	12	7416	25	7447	48	7485	75	74122	45	74160	60	74181	135
7403	14	7417	20	7448	50	7486	25	74123	48	74161	60	74182	75
7404	14	7418	20	7449	16	7489	180	74125	40	74162	60	74190	70
7405	17	7419	20	7450	16	7490	28	74126	40	74163	60	74191	70
7406	26	7420	28	7451	16	7492	45	74127	40	74164	60	74192	70
7407	26	7421	28	7452	16	7493	45	74128	40	74165	60	74193	65
7408	15	7422	28	7453	16	7494	30	74129	40	74166	180	74194	70
7409	16	7423	25	7454	16	7495	35	74130	40	74167	180	74195	63
7410	14	7424	25	7455	16	7496	50	74131	40	74168	180	74196	63
7411	20	7425	27	7456	16	7497	120	74132	40	74169	180	74197	63
7412	20	7426	17	7457	30	7498	80	74133	40	74170	180	74198	95

LS TTL		LS21	15	LS76	20	LS125	30	LS161	42	LS221	60	LS365	38
LS00	13	LS22	16	LS77 <td>24</td> <td>LS126</td> <td>30</td> <td>LS162</td> <td>42</td> <td>LS240</td> <td>90</td> <td>LS366</td> <td>38</td>	24	LS126	30	LS162	42	LS240	90	LS366	38
LS01	14	LS27	18	LS81	50	LS132	45	LS163	42	LS241	80	LS367	38
LS02	14	LS28	18	LS82	50	LS133	45	LS164	50	LS242	80	LS368	50
LS03	14	LS31	16	LS86	25	LS138	35	LS165	120	LS243	85	LS373	80
LS04	15	LS32	16	LS90	35	LS139	35	LS166	85	LS244	80	LS374	80
LS05	15	LS37	16	LS92	38	LS145	75	LS170	170	LS245	120	LS375	50
LS06	16	LS38	16	LS93	35	LS147	160	LS171	70	LS247	75	LS377	90
LS07	16	LS40	16	LS95	45	LS148	95	LS174	60	LS251	40	LS378	70
LS08	16	LS42	38	LS96	110	LS151	40	LS175	60	LS257	48	LS390	75
LS09	16	LS47	40	LS107	45	LS153	40	LS190	55	LS258	45	LS393	75
LS10	16	LS48	80	LS109	30	LS154	120	LS191	55	LS259	95	LS399	220
LS11	16	LS51	16	LS112	30	LS155	45	LS192	55	LS266	25	LS541	135
LS12	15	LS55	30	LS113	30	LS156	45	LS193	60	LS273	90	LS670	175
LS13	25	LS73	25	LS114	30	LS157	35	LS195	50	LS279	50		
LS14	28	LS74	25	LS122	42	LS158	36	LS196	60	LS283	45		
LS15	15	LS75	27	LS123	55	LS160	42	LS197	68	LS353	100		

TRANSISTORS		BC157	10	BC558	10	BFX84	25	TIP30	45	★ZTX107	8	2N3054	55
AC125	35	★BC159 <td>8</td> <td>BCY71 <td>18</td> <td>BFX85 <td>25</td> <td>TIP30A <td>40</td> <td>★ZTX108 <td>8 <td>2N3055</td> <td>50</td> </td></td></td></td></td>	8	BCY71 <td>18</td> <td>BFX85 <td>25</td> <td>TIP30A <td>40</td> <td>★ZTX108 <td>8 <td>2N3055</td> <td>50</td> </td></td></td></td>	18	BFX85 <td>25</td> <td>TIP30A <td>40</td> <td>★ZTX108 <td>8 <td>2N3055</td> <td>50</td> </td></td></td>	25	TIP30A <td>40</td> <td>★ZTX108 <td>8 <td>2N3055</td> <td>50</td> </td></td>	40	★ZTX108 <td>8 <td>2N3055</td> <td>50</td> </td>	8 <td>2N3055</td> <td>50</td>	2N3055	50
AC126	25	BC160	45	BCY72 <td>18</td> <td>BFX87 <td>28</td> <td>TIP30B <td>50</td> <td>ZTX109</td> <td>12</td> <td>2N3442</td> <td>120</td> </td></td>	18	BFX87 <td>28</td> <td>TIP30B <td>50</td> <td>ZTX109</td> <td>12</td> <td>2N3442</td> <td>120</td> </td>	28	TIP30B <td>50</td> <td>ZTX109</td> <td>12</td> <td>2N3442</td> <td>120</td>	50	ZTX109	12	2N3442	120
AC127	20	★BC168C	10	BD115	80	BFX88	25	TIP30C	60	ZTX300	14	★2N3702	6
★AC128	20	BC169C	10	BD131	35	BFY50	23	TIP31A	45	ZTX301	16	2N3703	9
AC176	25	BC170	8	BD132	35	BFY51	23	TIP31B	45	ZTX302	15	★2N3704	6
AC187	22	BC171	10	BD133	50	BFY52	23	TIP31C	55	ZTX304	17	2N3705	9
AC188	22	BC172	8	BD135	50	BFY53	32	TIP32A	45	ZTX341	30	2N3706	9
AD142	120	BC177	18	BD136	30	BFY55	32	TIP32B	55	ZTX500	15	2N3707	10
AD149	80	BC178	18	BD137	30	BFY56	32	TIP32C	60	ZTX501	15	2N3708	10
AD161	40	BC179	18	BD138	30	BKY39	40	TIP33A	50	ZTX502	15	2N3709	10
AD162	40	BC182	10	BD139	35	BSX20	20	TIP33B	75	ZTX503	18	2N3772	190
AF124	60	★BC182L	8	BD140	35	BSX29	35	TIP34A	60	ZTX504	25	2N3773	210
AF126	50	BC183	10	BD204	110	BSY95A	25	TIP34C	85	2N697	20	★2N3819	15
AF139	40	BC183L	10	BD206	110	BU205	160	TIP35A	160	2N698	40	2N3820	40
AF186	70	BC184	10	BD222	85	BU206	200	TIP35C	180	2N706A	20	2N3823	65
AF239	75	★BC184L	7	BF180	35	BU208	170	TIP36A	170	2N708	20	2N3866	90
BC107	10	BC212	10	BF182	35	MJ2955	99	TIP36C	195	2N918	35	2N3903	10
BC107B	10	BC212L	10	BF184	25	MJE340	50	TIP41A	60	2N1132	22	2N3904	10
★BC108	8	BC213	10	BF185	25	MJE520	65	TIP42A	60	2N1613	30	★2N3905	6
BC108B	12	BC213L	10	BF194	12	MIF521	95	TIP120	90	2N2218A	45	2N3906	10
BC108C	12	BC214	10	BF195	12	MIF521	95	TIP121	90	2N2219A	25	2N4037	45
★BC109	8	★BC214L	8	BF196	12	MIF521	95	TIP122	90	2N2221A	25	2N4058	10
BC109C	12	BC217	8	BF197	12	MPI104	40	TIP141	120	2N2222A	20	2N4060	10
BC114	22	BC238	14	BF198	10	MPSA05	22	TIP142	120	2N2368	25	2N4061	10
BC115	22	BC308	15	BF199	18	MPSA06	25	TIP147	120	2N2369	11	2N4062	10
BC117	22	BC327	14	BF200	30	MPSA12	30	TIP2955	60	2N2484	25	2N5457	36
BC119	35	★BC328	14	★BF244B	18	MPSA55	30	TIP3055	55	2N2646	45	2N5458	36
BC137	40	BC337	14</										


## Grabbed By The Dooleys

Those tireless chappies down at Casio have taken time off from disguising BASIC computers and arcade games as pocket calculators and watches, and have turned their attention to the music scene. Although there is undoubtedly a market for top-flight organs and synthesisers amongst home musicians, many people will prefer something more modest — for financial reasons, because the living room is too small or because they can't figure out what all the knobs do. At the other end of the scale (sorry), the type of hand-held organ made notorious by Rolf Harris is a little too limiting. With the Casiotone 701, Casio have not just produced a solution to this problem but a radically new type of instrument.

The CT-701 is not just a 61-key polyphonic (eight voice) mini-synthesiser, but also contains an on-board computer that acts as a built-in sequencer; among other things. You can play along with the built-in rhythm unit, store your own music in memory and play it back automatically, or just load the machine with a Casio music score and let it get on with things by itself. The latter function is

quite extraordinary — Casio supply the music scores as bar codes and you read them into the machine using a light pen (like those at supermarket check-out desks). In melody guide mode you can even teach yourself to play the instrument, as LEDs above each key light up to tell you which note to play next.

Twenty preset sounds are available, such as pipe organ, flute, piano, oboe, bassoon etc, plus the synthesised drum sounds of the rhythm unit and the 'pneoom' sound so beloved by producers of disco records. Opinions of the preset sound quality vary from "beautiful" (Casio) through "very good" (an independent reviewer) to "too sharply filtered" (another independent reviewer). Since they can't agree and we haven't heard it (though, we're trying hard to get our mucky paws on one), you'll have to listen to one yourself before parting with any cash, but professional musicians seem to like it — the Dooleys use Casiotone mini-keyboards in their stage shows (fellow head-bangers may not see this as a compliment). With so much packed into such a compact case (only slightly larger than the actual keyboard) and such a low price (about £500), Casio would certainly seem to have done it again.

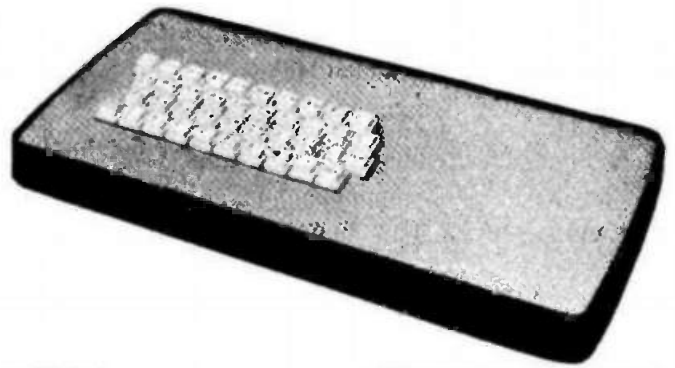

## ZX Revamp


For those of you who are serious ZX-81 owners (is there such an animal?) or would simply like to disguise the machine, there is a professional standard keyboard and enclosure now available from Protos Computer Systems. The keyboard is the first of a range of peripherals to make the computer suitable for more heavy-duty use. The 40-key Sinclair coded board uses top quality mechanical contact type key switches with relegendable tops. A steel mounting board holds the keys firmly in position and a high quality printed circuit board completes the board's electrical circuit. Connection to the Sinclair board is made by a flexible connector which is a

push fit to the sockets provided on the ZX81. Access to the edge board connector is via a side port on the Protos enclosure and tape in/out, power and UHF connections are made through the rear. To fit the Protos entails removing the Sinclair board from the black ABS case it comes in and fixing it inside the Protos enclosure with four Phillips type screws. No soldering is required and all electrical connections are plug/socket connections provided either on the Sinclair or the Protos. Further details on this and other forthcoming peripherals can be obtained from Protos Computer Systems, Frome Computing, 20 Ashtree Road, Frome, Somerset BA11 2AS. Please enclose a large SAE with any enquiries.
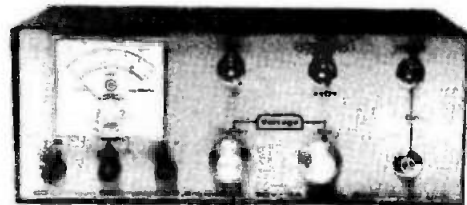
## Power For Peanuts

Grenson Electronics, designers and manufacturers of power supplies for the Nuclear Research Industry have come up with a series of bench power units. The first unit in the series is priced at


£59 and gives a variable stabilised output up to 30 V at 2 A in two ranges, has foldback re-entrant short circuit protection and current and voltage metering. This unit is also available in kit form at only £35 and further details are from Grenson Electronics Ltd, High March Road, Long March, Industrial Estate, Daventry, Northants NN11 4HQ.


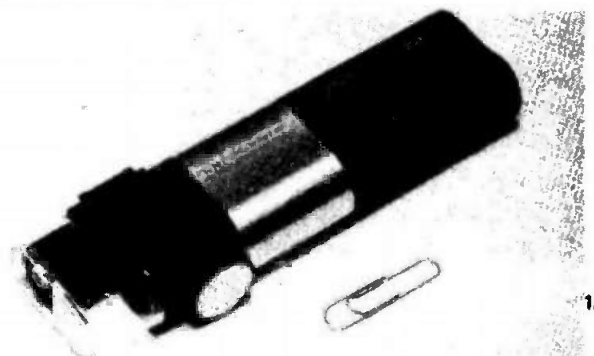
## Miniature Magnification

New from Stottron Ltd is the NScope Mark III pocket microscope. Priced at under £20 it is a useful tool for laboratories, schools, workshops, service engineers and the electronics, electrical, automotive, print and graphic trades, Uncle Tom Cobbley and all! It is 125 mm

long, with 20x magnification and a graticule showing linear and angular measurements. Illumination is powered by standard 1V5 'pen-light' batteries and a micro-stand (with spring clips for sample slides) is available as an option so that the device can be used like a conventional microscope. Further details on this device are available from Stottron Ltd, Unit 1, Haywood Way, Ivy House Lane, Hastings, East Sussex.





## Thin Meters

Sifam Ltd of Torquay in Devon are to market a range of very thin edgewise meters manufactured by General Electric of the USA. There are three sizes in the range with case widths of 38 mm, 63 mm and 89 mm and the units are scaled for vertical or horizontal presentation. The special feature of this design is the extreme thinness; the smallest has an overall depth of face of only 13 mm and the two larger sizes of about 17 mm. The smallest model has a rear-access zero set and a

simple spring-clip method of mounting. The two larger models have front access zero set at end of scale and a slide bracket form of mounting. They incorporate jewelled pivot movements with special high-torque magnets for reliable and accurate operation. The standard meters are available ex-stock from Sifam and have a maximum sensitivity of 50 microamperes. Scale markings can be produced to suit individual requirements. Further details of these and Sifam's own range of meters are available from: Sifam Limited, Woodland Road, Torquay, Devon TQ2 7AY.

# New Products

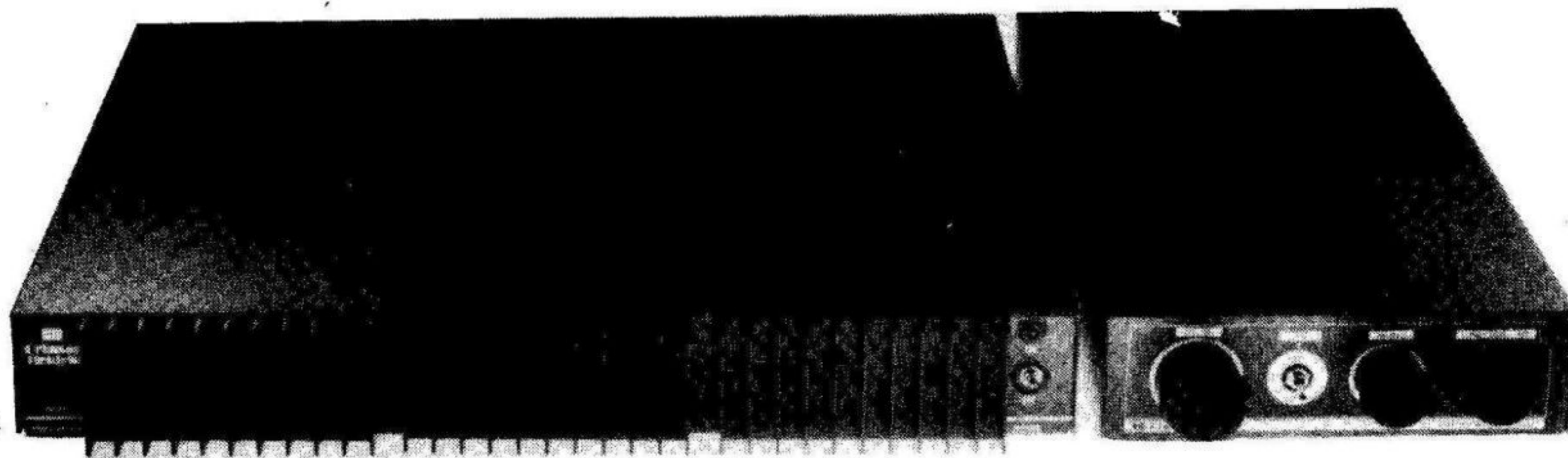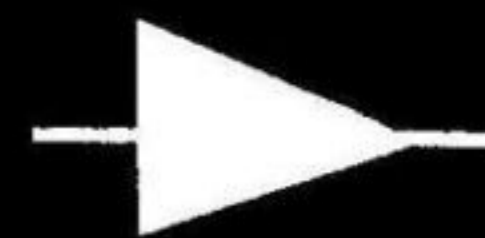

## HIFI STEREO AMPLIFIER KITS

From one of Britain's leading esoteric amplifier manufacturers comes an exciting new package of stereo amplifier kits, designed to offer all the advantages of true high fidelity but without the usual price penalty. These new kits offer the choice of moving magnet or moving coil inputs, 40 or 100 watts per channel, in fact, everything that made the previous models so popular is included but with added style, easier construction and a full two year warranty.

### The New Range Consists of

- The CK 1010 Stereo Pre Amplifier
- The CK 1040 WPC Power Amplifier
- The CK 1100 WPC Power Amplifier

## CK 1010

This kit contains all the necessary parts to build a complete pre-amp. The main PCB is ready assembled and tested therefore construction is simply a matter of point to point wiring and mechanical assembly of the connections and controls to the pre punched chassis.

The CK 1010 takes its DC supply from the CK 1040, 1100 or, if using a different power amplifier a PSK power supply kit. Inputs for disc, tuner and tape are provided and an optional add-on moving coil input can be fitted to extend its versatility. (MC2K)

## CK 1040

This is a nominal 40 watt per channel power amplifier kit which features our dual power supply and the DC output for the CK 1010. All components such as heatsinks, wire and connectors are included and protection is provided from short circuit outputs.

## CK 1100

Similar to the CK 1040 this model provides a nominal 100 watts per channel with extra heatsinking and thermal cutouts are provided as standard.

When correctly assembled these kits are guaranteed for two years.

"It would seem then that Crimson have maintained their position at the top of the commercial kit-build field. There is no oriental amplifier I know of that can better the sound of this combination overall at any price and only a few — such as the KA-1000 (500+) — are of comparable standard . . . I can say no more than that for £250 it (CK1010/MC2K/1100) is a bargain and one that becomes the reference point for kit amplifiers from now on."

ETI FEB 1982

## SPECIAL INTRODUCTORY OFFER 10-15% OFF!

As a special incentive to buy our new range of D.I.Y. Hifi Kits, we are offering the range for a limited period at silly discount prices

The offer closes on March 31st, with prices this low, demand is sure to be heavy, so order now and avoid delays at the same time save £££'s

CK 1010 — RRP £90.00 .....	<b>SPECIAL PRICE £79.20</b>
CK 1040 — RRP £119.00 .....	<b>SPECIAL PRICE £105.80</b>
CK 1100 — RRP £149.00 .....	<b>SPECIAL PRICE £130.80</b>
MC2K — RRP £25.00 .....	<b>SPECIAL PRICE £22.50</b>
PSK — RRP £20.00 .....	<b>SPECIAL PRICE £16.80</b>

Barclaycard or Access accepted, otherwise send C.W.O. C.O.D. £1.00 extra  
All prices include P&P to anywhere in the U.K. Export: Write for pro-forma




## Crimson Elektrik

FREEPOST, 9 CLAYMILL ROAD  
LEICESTER LE4 5ZD. ENGLAND  
TEL. 0533 761920, TLX 34694

# electronics today

INTERNATIONAL

NEXT  
MONTH

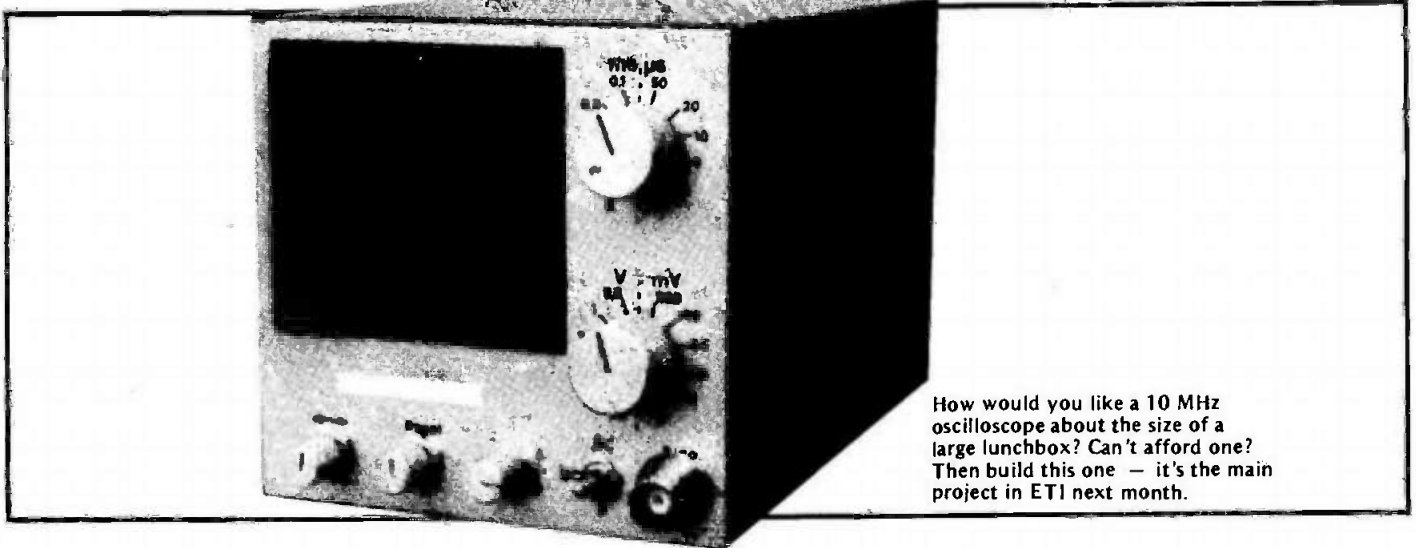

How would you like a 10 MHz oscilloscope about the size of a large lunchbox? Can't afford one? Then build this one — it's the main project in ETI next month.

## SLOT CAR CONTROLLER

Let's not beat about the bush. Slot cars are fun. If you're as keen on slot cars and electronics as we are, you'll be equally appalled at the crude control systems provided in the basic sets. Naturally we decided something should be done about the situation and came up with this project. You can have controlled acceleration with overshoot, dynamic braking, 'electronic' fuel tanks — and all from quite a simple circuit. There'll also be some advice on how to tune your cars to get the ultimate in performance from them. A must to read for kids of all ages.

## COLUMN LOUDSPEAKER DESIGN

Now this is good stuff. One of the bugbears of public address systems is acoustic feedback, which can be largely overcome by the use of a highly directional sound source. This directs the sound into the audience, where it's needed, and away from the microphone, where it isn't. This article describes the design of a novel column loudspeaker design that is cheap and highly effective.

## ROBOT CONTROLLER PART 3

In next month's ETI we continue this series with the construction information for this month's analogue pulse width modulation controller, plus full details and a PCB for a dual digital PWM controller. This will not only be of interest to roboticists but to anyone who needs to control the speed of DC motors.


Articles described here are in an advanced state of preparation. However, circumstances may dictate changes to the final contents.

## DVMEG


Any scholars out there will know that D is Roman for 500. Since V stands for volts, it will come as no surprise that this project generates 500 V to enable the leakage current through insulation to be tested using the built-in meter. In effect it is a high-voltage resistance meter for measuring values above about 1M $\Omega$  — hence the last part of the name. We don't just throw these things together, you know!
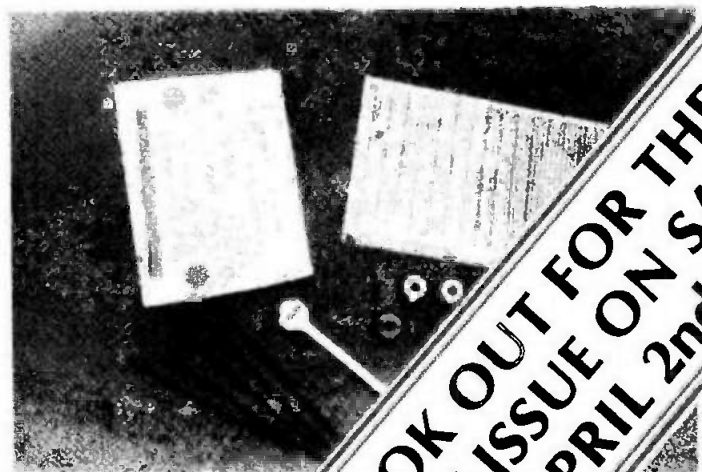
## BREADBOARDING SYSTEMS

There appears to have been a veritable explosion in the number of breadboarding and prototyping systems available to industry and the hobbyist; next month we'll be taking a look at some of them. Both solderwrap and insulation displacement techniques will be examined and we'll have an exclusive first review of a major new development from a leading manufacturer. Not to be missed!



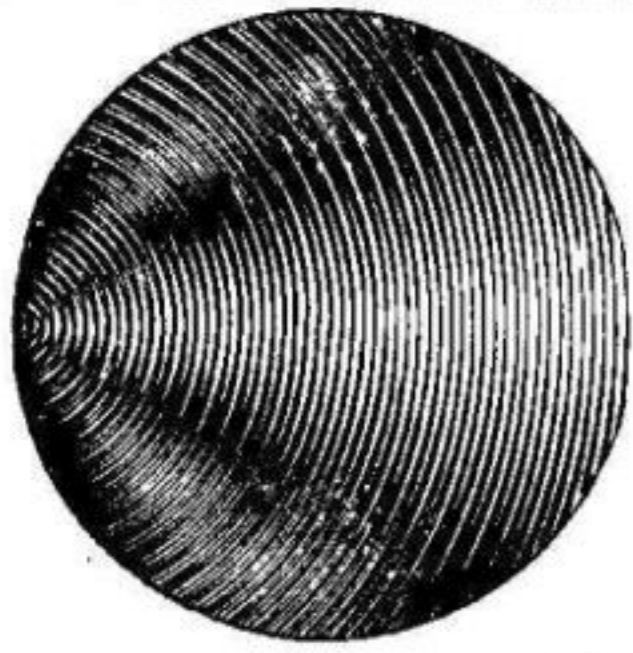LOOK OUT FOR THE  
MAY ISSUE ON SALE  
APRIL 2nd




APPROVED  
**thandar**  
STOCKIST

# B.K. ELECTRONICS
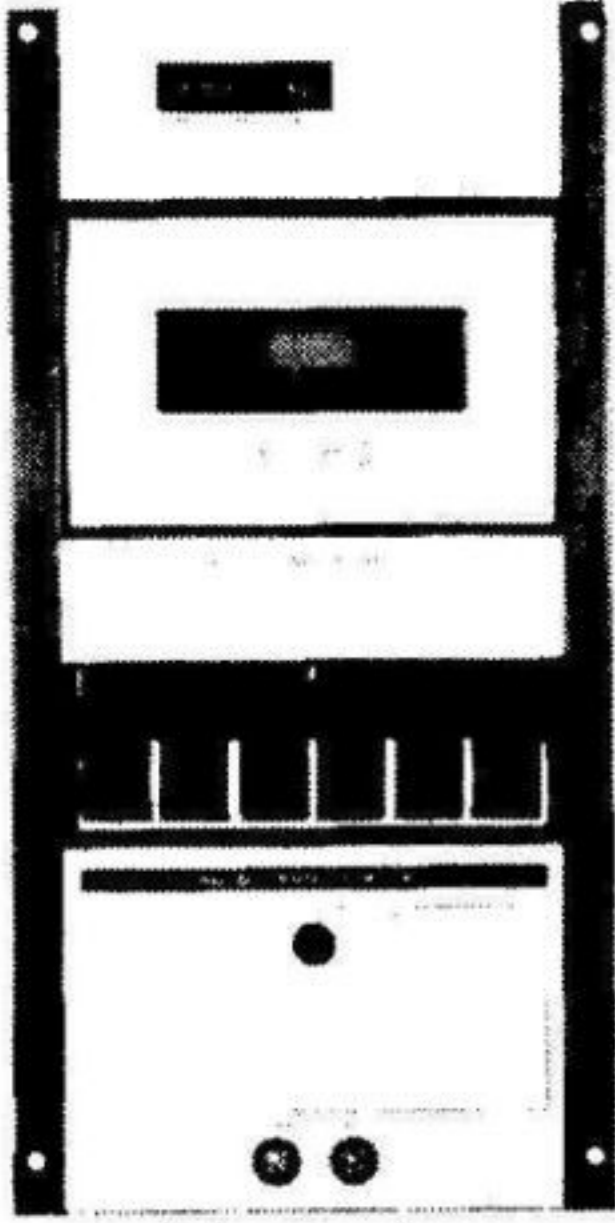
## A SOUND CHOICE

APPROVED  
**thandar**  
STOCKIST

★ PROMPT DELIVERY ★ PRICES INCLUDE V.A.T. ★ AMPLE STOCKS  
A PERSONAL SERVICE FROM A SMALL EXPANDING COMPANY



6 piano type keys

**STEREO CASSETTE TAPE DECK MODULE.**  
Comprising of a top panel and tape mechanism coupled to a record/play back printed board assembly. Supplied as one complete unit for horizontal installation into cabinet or console of own choice. These units are brand new, ready built and tested.

**Features:** Three digit tape counter. Auto-stop. Six piano type keys, record, rewind, fast forward, play, stop and eject. Automatic record level control. Main inputs plus secondary inputs for stereo microphones. **Input Sensitivity:** 100mV to 2V **Input Impedance:** 68K. **Output level:** 400mV to both left and right hand channels. **Output Impedance:** 10K. **Signal to noise ratio:** 45dB. **Wow and flutter:** 0.1%. **Power Supply requirements:** 18V DC at 300mA. **Connections:** The left and right hand stereo inputs and outputs are via individual screened leads, all terminated with phono plugs (phono sockets provided). **Dimensions:** Top panel 5 1/2in x 11 1/4in. Clearance required under top panel 2 1/4in. Supplied complete with circuit diagram and connecting diagram. Attractive black and silver finish.

**Price £26.70 + £2.50 postage and packing.**  
Supplementary parts for 18V D.C. power supply (transformer, bridge rectifier and smoothing capacitor) £3.50.

**NEW RANGE QUALITY POWER LOUD-SPEAKERS (15", 12" and 8").** These loudspeakers are ideal for both hi-fi and disco applications. Both the 12" and 15" units have heavy duty die-cast chassis and aluminium centre domes. All three units have white speaker cones and are fitted with attractive cast aluminium (ground finish) fixing escutcheons. Specification and Price:-


**15" 100 watt R.M.S.** Impedance 8ohm 59 oz. magnet, 2" aluminium voice coil. Resonant Frequency 20Hz. Frequency Response to 2.5KHz. Sensitivity 97dB. **Price £32 each.** £2.50 Packing and Carriage each.

**12" 100 watt R.M.S.** Impedance 8 ohm, 50 oz. magnet. 2" aluminium voice coil. Resonant Frequency 25Hz. Frequency Response to 4KHz. Sensitivity 95dB. **Price £23.70 each.** £2.50 Packing and Carriage each.

**8" 50 watt R.M.S.** Impedance 8 ohms, 20 oz. 1 1/2" aluminium voice coil, Resonant Frequency 40Hz, Frequency Response to 6KHz, Sensitivity 92dB. Also available with black cone fitted with black metal protective grill. **Price: White cone £8.90 each. Black cone/grill £9.50 each.** P & P £1.25 each.
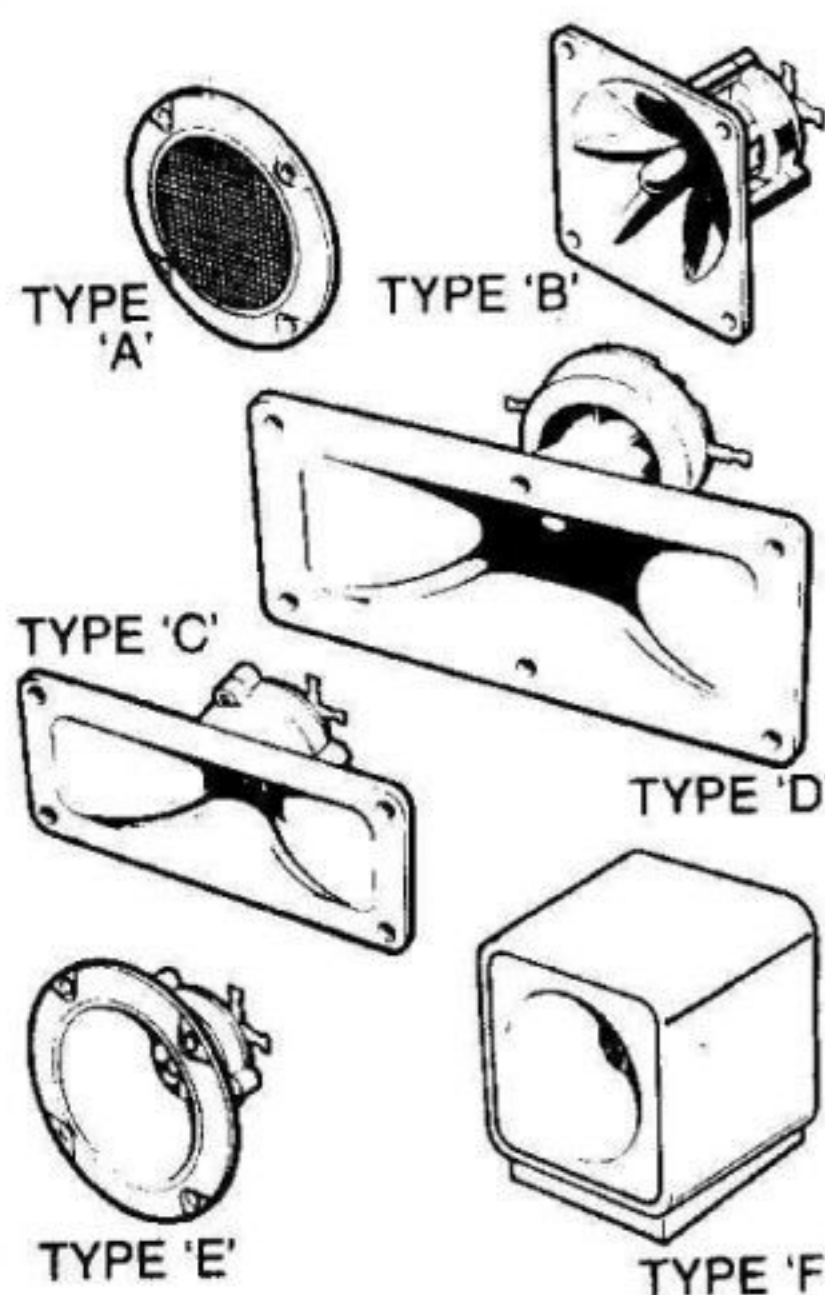
### PIEZO ELECTRIC TWEETERS - MOTOROLA

Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). **FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.**



**TYPE 'A' (KSN2036A)** 3" round with protective wire mesh, ideal for bookshelf and medium sized Hi-fi speakers. **Price £3.45 each.**

**TYPE 'B' (KSN1005A)** 3 1/2" super horn. For general purpose speakers, disco and P.A. systems etc. **Price £4.35 each.**

**TYPE 'C' (KSN6016A)** 2" x 5" wide dispersion horn. For quality Hi-fi systems and quality discos etc. **Price £5.45 each.**

**TYPE 'D' (KSN1025A)** 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-fi systems and quality discos. **Price £6.90 each.**

**TYPE 'E' (KSN1038A)** 1 1/4" horn tweeter with attractive silver finish trim. Suitable for Hi-fi monitor systems etc. **Price £4.35 each.**

**TYPE 'F' (KSN1057A)** Cased version of type 'E'. Free standing satellite tweeter. Perfect add on tweeter for conventional loudspeaker systems. **Price £10.75 each.**  
U.K. post free (or SAE for Piezo leaflets).

### 1K.WATT SLIDE DIMMER



- Controls loads up to 1KW
  - Compact size  
4 3/4" x 1 3/16" x 2 1/2"
  - Easy snap in fixing through panel/cabinet cut out
  - Insulated plastic case
  - Full wave control using 8amp triac
  - Conforms to BS800
  - Suitable for both resistance and inductive loads
- Innumerable applications in industry, the home, and discos/theatres etc.

**Price: £11.70 each + 50p P&P**  
(Any quantity)



### GENERAL PURPOSE 4 1/2" MINI SPEAKER

General purpose full range loudspeaker, ideal for mini systems etc.

- Rolled fabric surround
- Twin cone
- 8ohm impedance
- 15 watt RMS
- 1" voice coil
- 13oz magnet
- Frequency range 50/15000Hz

**Price: £6.90 each + 75p P&P**


### BSR P256 TURNTABLE

P256 turntable chassis ● S shaped tone arm ● Belt driven ● Aluminium platter ● Precision calibrated counter balance ● Anti-skate (bias device) ● Damped cueing lever ● 240 volt AC operation (Hz) ● Cut-out template supplied ● Completely manual arm. This deck has a completely manual arm and is designed primarily for disco and studio use where all the advantages of a manual arm are required.

**Price: £28.50 + £2.50 P&P**



### OMP | POWER AMPLIFIER MODULES

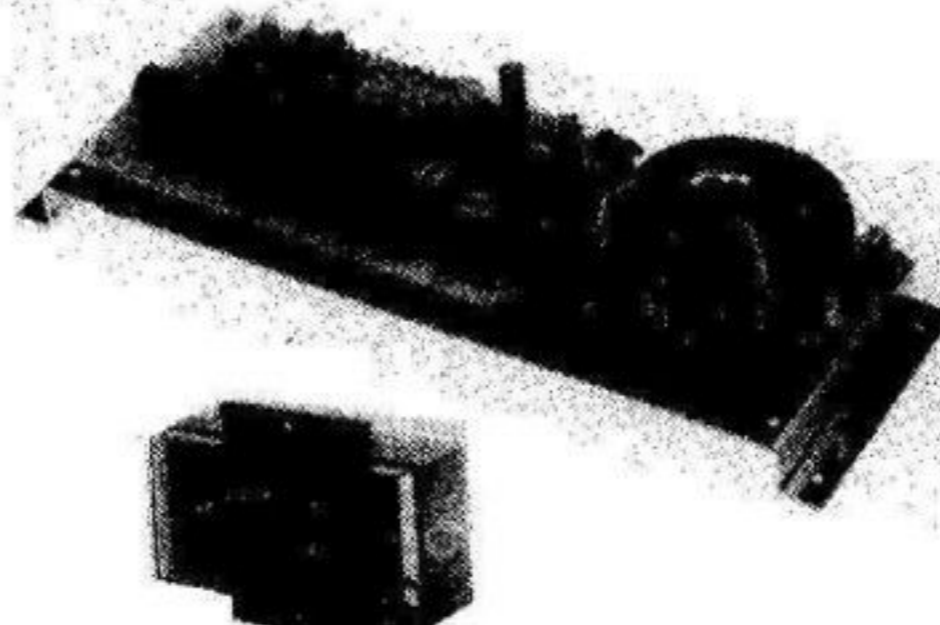

Vu Meter

### 100 WATT R.M.S.

Power Amplifier Modules with integral toroidal transformer power supply and heat sink. Supplied as one complete built and tested unit. Can be fitted in minutes. Auxilliary stabilised supply and drive circuit incorporated to power an L.E.D. V.u. meter, available as an optional extra.

#### SPECIFICATION:

Max. output power 100 watts R.M.S. (OMP100)  
Loads: (Open and short circuit proof) 4-16 ohms  
Frequency Response 20Hz-25KHz ± 3dB  
Sensitivity for 100 watts 500mV at 10K  
T.H.D. 00.1%

Size: 360 x 115 x 80mm  
Prices: OMP 100W £29.99 £2.00 P&P  
OMP 150W £39.99 £2.00  
V.u. Meter £6.50

### Matching 3-way loudspeakers and crossover

Build a quality 60watt RMS system Bohms

Build a quality 60 watt R.M.S. system.

- ★ 10" Woofer
- ★ 3" Tweeter
- ★ 5" Mid Range
- ★ 3-way crossover


Fitted with attractive cast aluminium fixing escutcheons and mesh protective grills which are removable enabling a unique choice of cabinet styling. Can be mounted directly on to baffle with or without conventional speaker fabrics. All three units have aluminium centre domes and rolled foam surround. Crossover combines spring-loaded loudspeaker terminals and recessed mounting panel.

**Price £22.00 per kit + £2.50 postage and packing.** Available separately, prices on request.

### 12" 80 watt R.M.S. loudspeaker.

A superb general purpose twin cone loudspeaker. 50 oz. magnet. 2" aluminium voice coil. Rolled surround. Resonant frequency 25Hz. Frequency response to 13KHz. Sensitivity 95dB. Impedance 8ohm. **Attractive blue cone with aluminium centre dome.**

**Price £17.99 each + £2.50 P&P.**

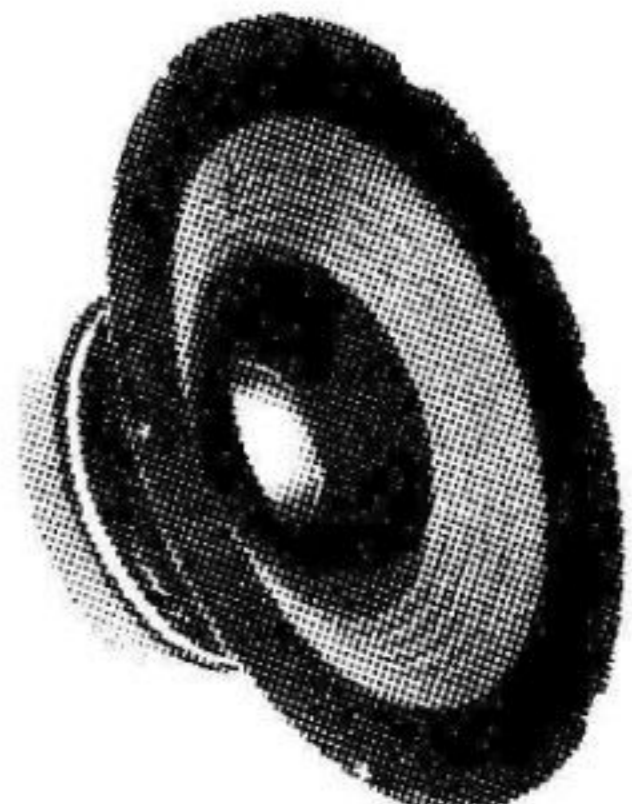

# B.K. ELECTRONICS

37 Whitehouse Meadows, Eastwood, Leigh-on-Sea, Essex SS9 5TY

★ SAE for current lists. ★ Official orders welcome. ★ All prices include VAT. ★ Mail order only. ★ All items packed (where applicable) in special energy absorbing PU foam. Callers welcome by prior appointment, please phone 0702-527572.





# ELECTROMUSIC TECHNIQUES

Tim Orr, our tame electronic designer, emerged from his workshop this month just long enough to hand over this bundle of circuits for the ardent build-it-yourself musician.

Virtually all of the electronic music synthesisers that have been produced to date employ analogue circuits to generate the synthesised sounds. The process is known as subtractive synthesis, and operates by dynamically filtering out parts of the spectrum of a signal that is often rich in harmonics. The results are instant, easy to modify and relatively inexpensive to implement. It is not possible to produce an arbitrary output spectrum, and so it is very difficult to synthesise realistic copies of naturally generated sounds. This can be done using a digital technique known as harmonic synthesis, whereby the sound is constructed by precisely defining the amplitude and phase of each of the harmonics. These are then added together to produce the output. However, natural sounds are constantly varying and so the data defining all the harmonics must also vary. Harmonic synthesis can produce very realistic sounds and is in itself a powerful technique for generating completely new sounds, but the hardware is a combination of sophisticated microprocessor and digital technology and so is outside the scope of this article.

When we hear a sound we unconsciously analyse it for useful information; "Who wants another drink?" for example. Nobody knows how the human brain analyses incoming sounds, but it does it with incredible speed and sophistication. It can extract precise information from sounds (speech perception), it can experience pleasure from a rich harmony, or it can even learn to ignore certain sounds, such as a ticking clock. The brain is very good at perceiving pitch (or at least it thinks it is; it is also a fairly good liar); see Fig. 1. When you hear a pure tone you

will get a strong impression of its pitch. You will not be able to define its frequency in Hertz, but you will be able to remember its pitch. A sawtooth has a strong harmonic structure but even so you will get the same pitch perception. The ringing tone has virtually no energy at the fundamental frequency and yet it is still possible to correctly perceive the pitch of the signal, although it is more difficult than for the pure tone.

Most musical instruments produce a range of notes. Some instruments, like violins, can produce a continuous range of frequencies; because, unlike the guitar, there are no frets along the neck of the instrument. Keyboard instruments have fixed tuning; the piano, for example. The keyboard is an excellent choice for controlling a synthesiser, as it is easily converted so that it generates suitable electrical signals and it is widely accepted by musicians. Equal temperament tuning is used, that is there are twelve notes per octave and they are spaced at intervals of the twelfth root of two (that is 1.0594631) along an exponential curve, as in Fig. 2.

## When You Hear The Tone . . .

The keyboard is used to define the fundamental pitch of a sound, but the actual shape of the waveform will determine its harmonic structure (Fig. 3). A sine wave is a pure tone and has no harmonics. A halfwave-rectified sine wave contains a fundamental plus a series of even harmonics. A fullwave-rectified sine wave is composed entirely of even harmonics. The squarewave and the triangle are both composed of a series of odd harmonics; in fact if you lowpass filter a square wave you can produce a triangle. The triangle is a fairly pure tone, with little of the energy in the waveform contained in its harmonics. The sawtooth is a rich waveform, having both odd and even harmonics.

The harmonic structure of all these waveforms extends to infinity, but the drawings only show the first 15 harmonics. If we call the harmonic number *n*, then the harmonic amplitude is easy to define. The rate at which the harmonic amplitude


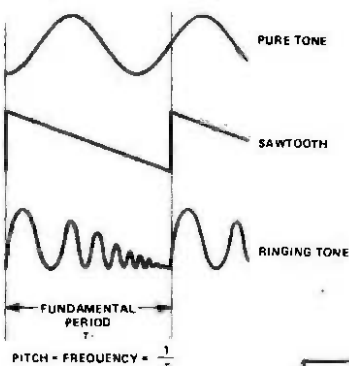


Fig. 1 Pitch perception.

NOTE	FREQUENCY (Hz)
A0	27.5
A1	56.0
A2	110.0
A3	220.0
A4	440.0
A5	880.0
A6	1760.0
A7	3520.0

NOTE	FREQUENCY (Hz)	RATIO
C4	261.6	1.0000
C4#	277.2	1.0595
D4	293.7	1.1225
D4#	311.1	1.1892
E4	329.7	1.2599
F4	349.2	1.3348
F4#	370.0	1.4142
G4	392.0	1.4983
G4#	415.3	1.5874
A4	440.0	1.6818
A4#	466.1	1.7818
B4	493.9	1.8877
C5	523.2	2.0000

Fig. 2 (below) Keyboard layout with table showing equal temperament tuning.

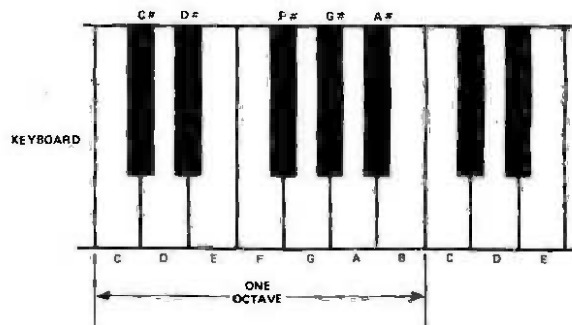

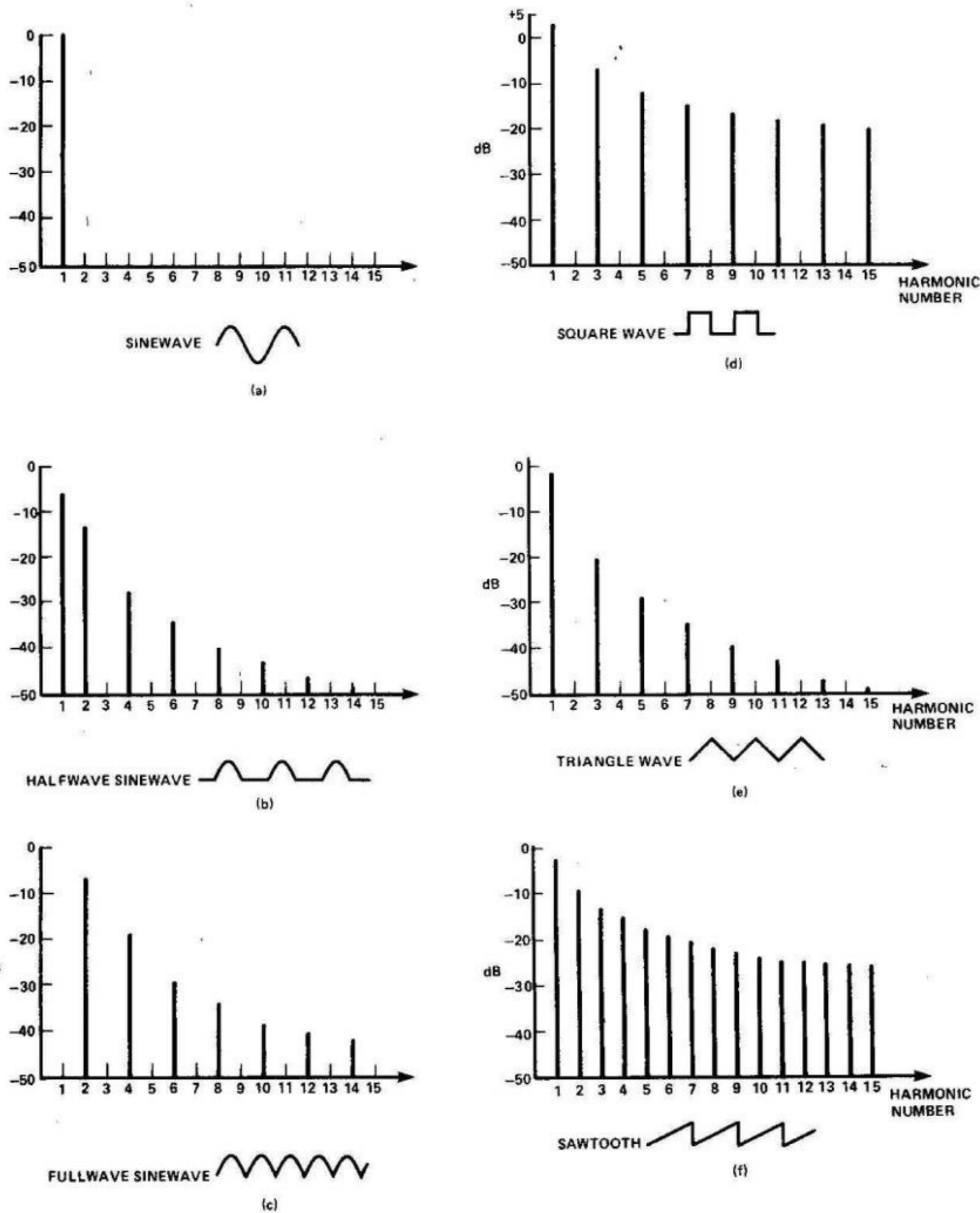


Fig. 3 Harmonic structure of various standard musical waveforms.

decreases is  $1/n$  for the sawtooth and square wave and  $1/n^2$  for the half and fullwave rectified sine wave and the triangle. Figure 4 shows a sawtooth being constructed from harmonics. The sum of the harmonics is beginning to look like a sawtooth. As more harmonics are added (with the correct phase and amplitude) the sum will converge upon the correct sawtooth shape. An interesting effect can be produced by changing the mark/space ratio of the square wave. This modifies the *odd* harmonic spectrum and introduces even harmonics. The mark/space ratio is often dynamically modified as a synthesis process.

Frequency modulation is often employed in synthesisers to produce vibrato and other dramatic pitch change effects. Figure 5 shows some of the effects of frequency modulation. As the modulation depth is increased, frequency sidebands are generated. Their spacing and amplitude are determined by the modulation depth and the modulation and carrier frequencies. To precisely calculate them involves some complex maths and Bessel functions (which I have forgotten all about). To make matters worse, synthesisers usually use voltage controlled oscillators with an exponential transfer function, which tends to exponentially distort the sideband positions. But so what! Music synthesisers are all about making music and not the calculation of sidebands. If a particular electronic device produces a useful musical effect, then use it, don't analyse it.

The output from an oscillator is known as an excitation signal. This defines the pitch of the signal, and to a certain extent the harmonic content of the final signal. It is common practice to filter the excitation signal (Fig. 6). The frequency response of the filter is referred to as a formant. The formant modifies the harmonic spectrum of the excitation, producing a colouration

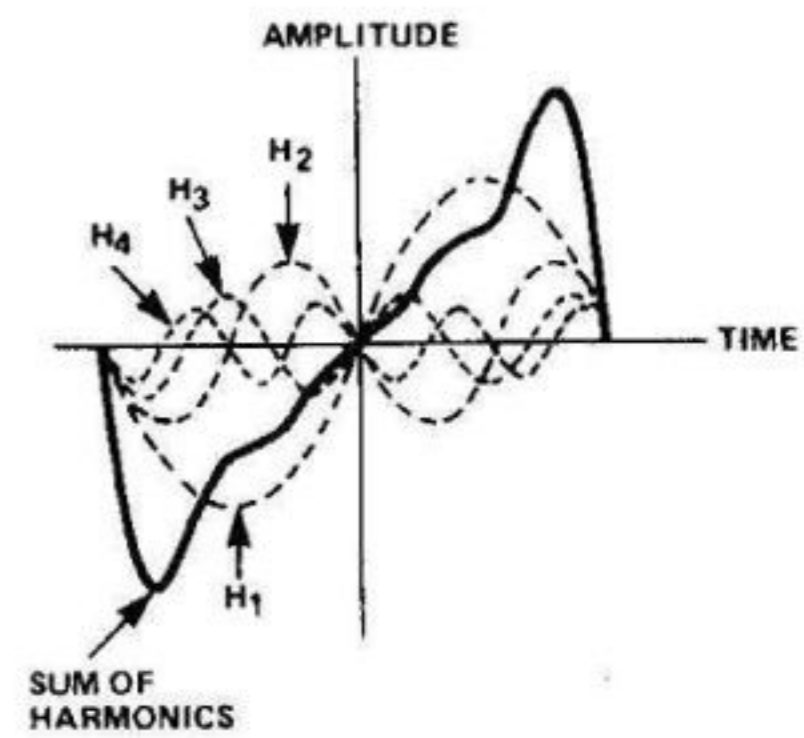


Fig. 4 Adding the first four harmonics to construct a sawtooth waveform.

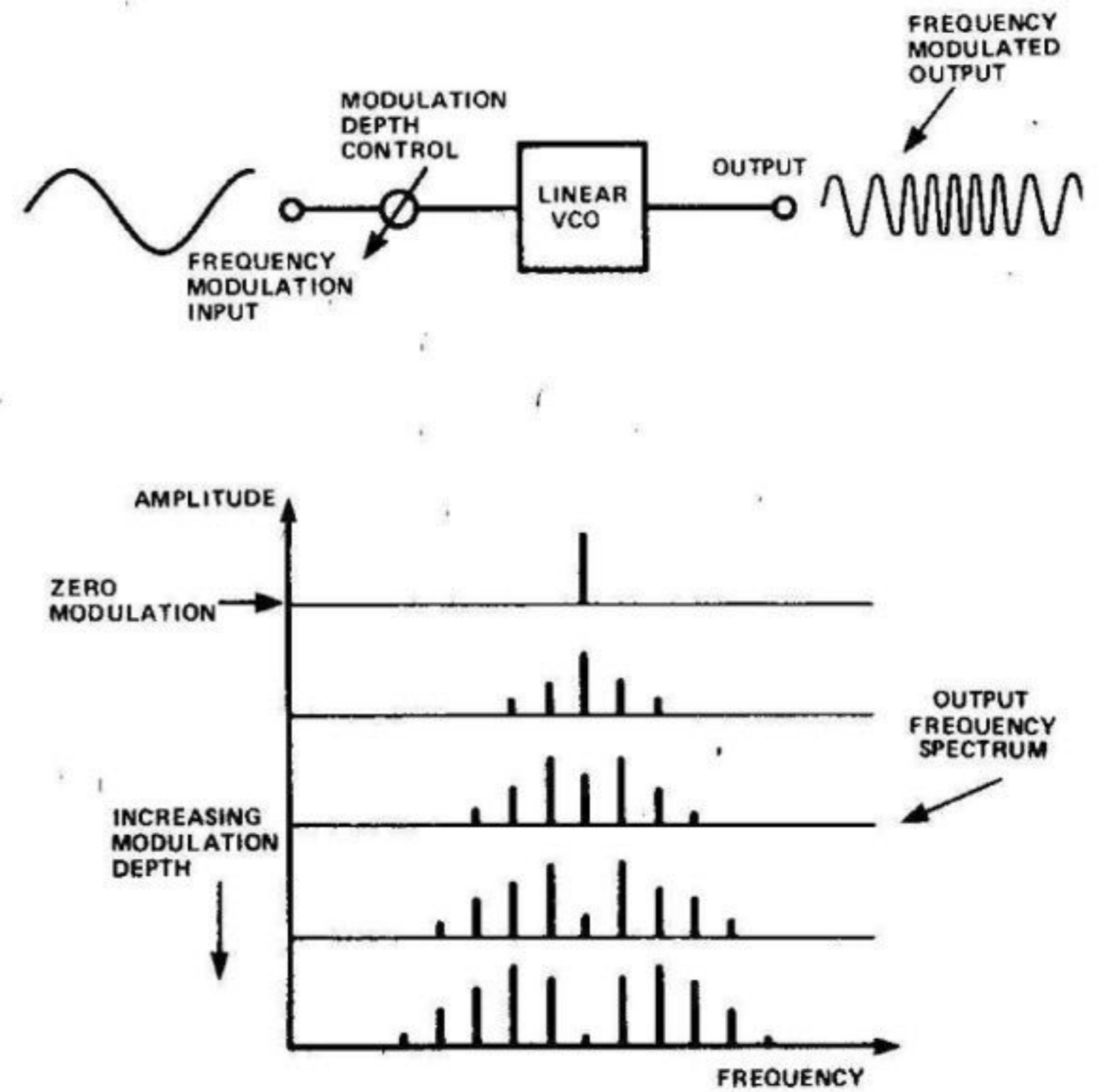


Fig. 5 The effects of frequency modulation.

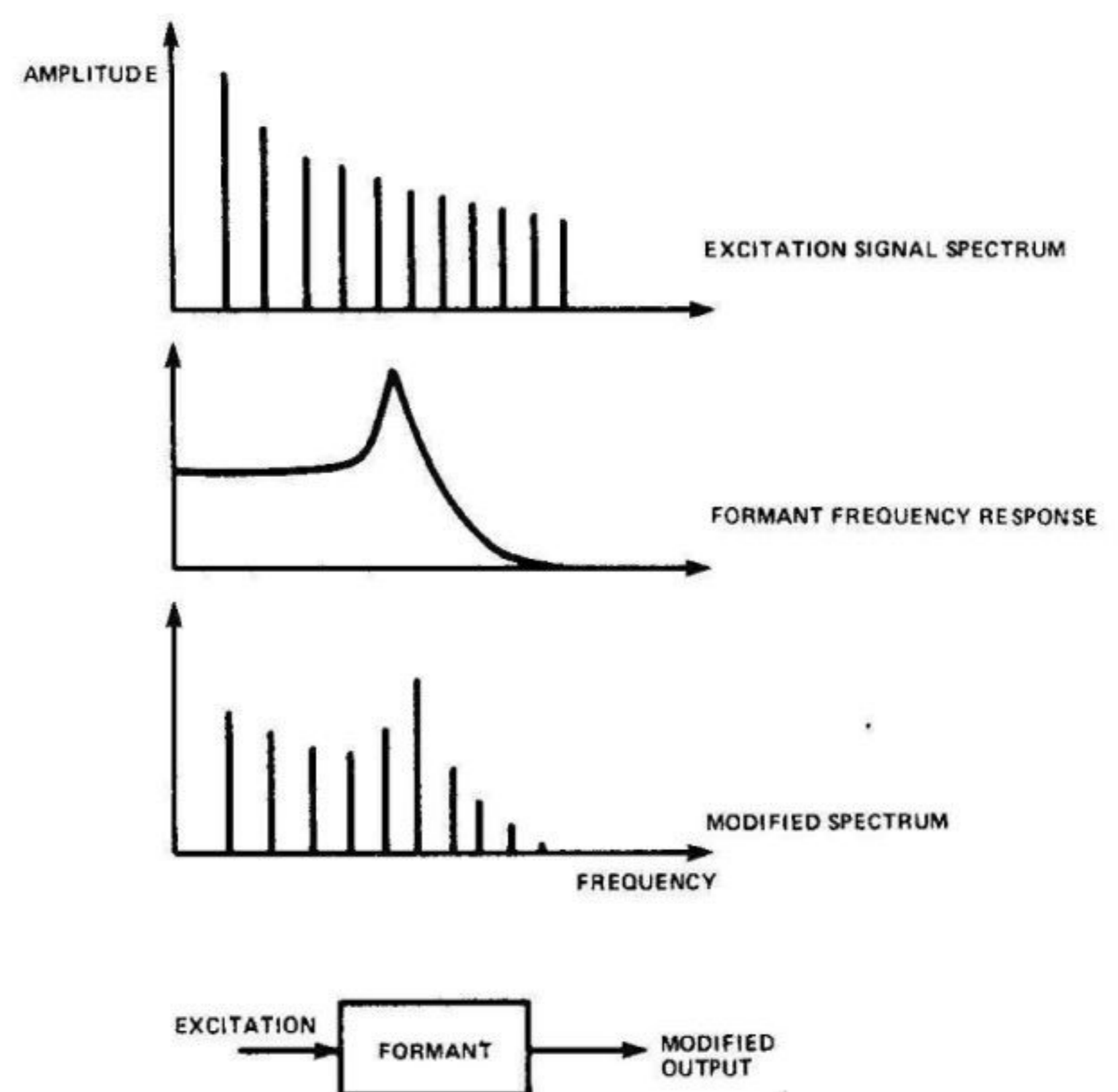


Fig. 6 The effect of filtering an excitation signal.

of the sound. The format is usually a mobile filter and this makes it possible to dynamically alter the sound colour. If the formant has a sharp resonant peak, then the output signal will ring as it passes the harmonics of the excitation.

Another parameter that characterises a sound is its

amplitude contour or envelope (Fig. 7). A sound that has a sharp attack and a slow release is similar to a plucked instrument. Other envelopes will make the sound seem like something else.

## Building Blocks

Most synthesizers are constructed from standard building blocks, and most of these blocks are voltage controlled. This is a very powerful concept, because it enables you to control a unit with a combination of control voltages and/or audio signals. Building blocks can be patched together in any arbitrary order to produce any system that is wanted. Some standard building blocks are detailed below.

**Voltage Controlled Oscillator** Used to generate the pitched excitation signals. Often a VCO will generate a wide range of waveforms. The control sensitivity is usually +1 V/octave. Therefore a one twelfth of a volt change will alter the oscillator pitch by one semitone. The exponential control law is a very powerful concept. If a VCO is being driven so that it produces a melody, then adding +1 V to the control input will transpose the melody up by one octave. Thus musical transpositions are very simple to produce. Often more than one VCO will be used, so that a rich chord is obtained.

**Voltage Controlled Filter** This is used as a formant for the excitation signal. The VCF is generally a lowpass filter, but it can often be a multi-mode device with lowpass, highpass, bandpass and notch responses. The VCF also has a Q (resonance) control. The control sensitivity is +1 V/octave for the frequency parameter, and undefined for the Q.

**Voltage Controlled Amplifier** The VCA controls the level of audio signals. The control law can be linear or logarithmic. The VCA is usually controlled by an ADSR unit and is employed to generate signal envelope contours. The device is a two quadrant multiplier.

**Attack, Decay, Sustain, Release unit** The ADSR is used to generate the signal envelope contour and also the VCF sweep waveform.

**Ring Modulator** This is a four quadrant multiplier or balanced multiplier. The output voltage is the product of the two input signals. It is often used to generate discordant or clangerous sounds.

**Noise source** Generates random noise, which can be used in the synthesis of non-pitched sounds such as explosions. Filtered or sampled noise can be used as a random control voltage.

**Low Frequency Oscillator** These oscillators are used to generate vibrato in the VCO or a filter sweep in the VCF.

**Keyboard** Musical control interface, generating pitch voltages of +1 V/octave and also a gate signal to indicate that a note is pressed. A monophonic keyboard only allows one note at a time to be pressed, but if more than one can be pressed simultaneously then the system is polyphonic.

There are several other building blocks such as flangers, sequencers, frequency shifters, and pitch detectors, but there isn't enough space to deal with them.

Polyphonic synthesizers tend to be voice-based, i.e. all the building blocks are pre-routed to form a voice (Fig. 8). Modular systems are not pre-routed and have to be patched, either with lots of jack-to-jack patch leads or via a matrix patch board using patch pins. Patch leads are relatively inexpensive, but the leads get in the way and it is often difficult to see just what you have patched. Matrix patch boards are easy to understand, but they suffer from crosstalk and a large board (60 by 60) might cost £500!


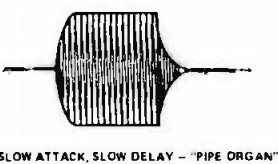
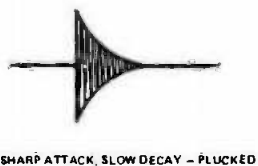
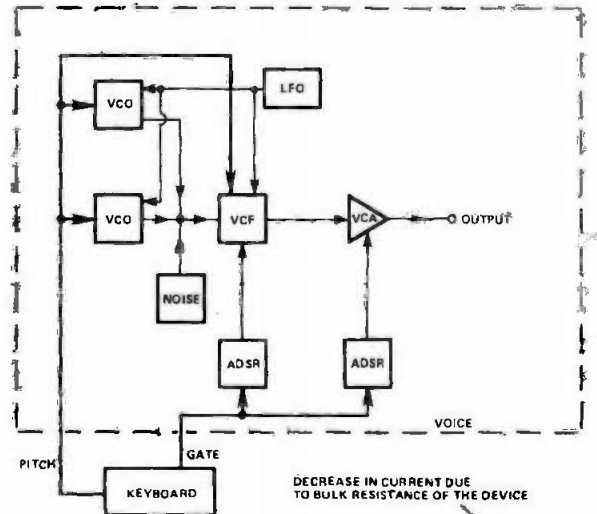


Fig. 7 (Above) Two typical amplitude contours, or envelopes.

Fig. 8 (Top right) The standard synthesiser voice.

Fig. 9 (Right) Silicon diode transfer characteristics.

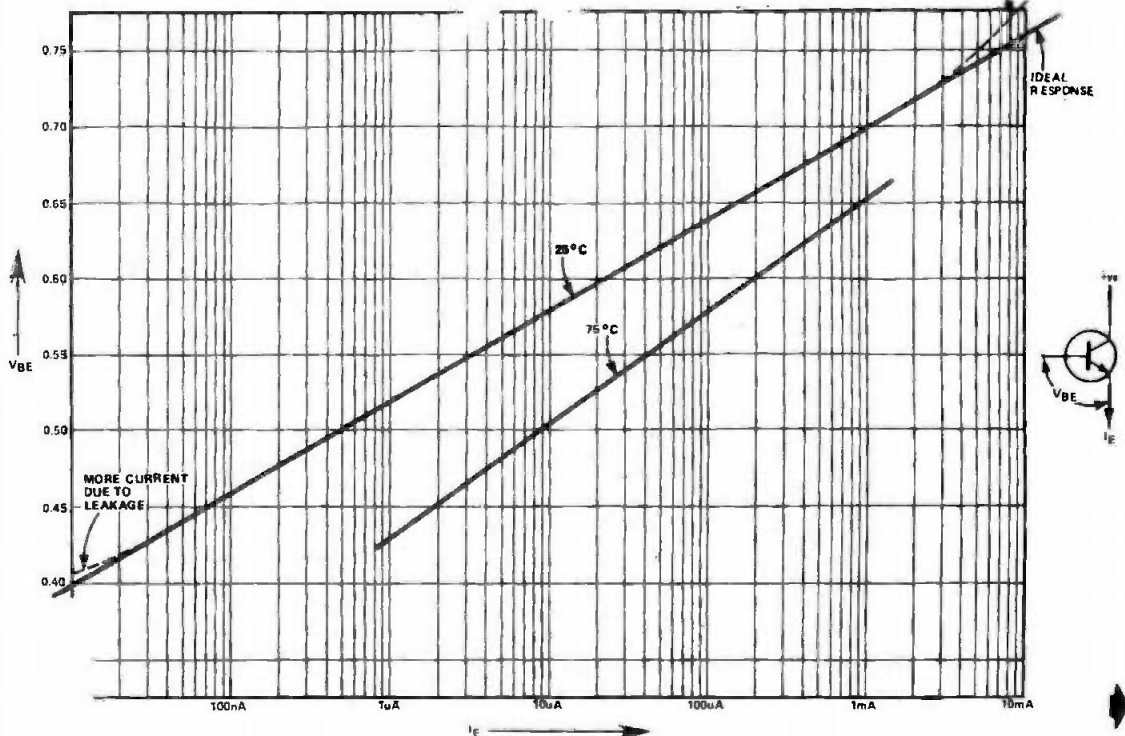


# Diode Data

The silicon diode has an exponential transfer function, that is the diode current increases exponentially for linear increments in the diode voltage (Fig. 9). This can be used to turn linear changes from, say, a keyboard into exponential or musical intervals in a VCO. The required musical range is probably no more than 200 to 1 and so a suitable operating current would be 0.5  $\mu$ A to 100  $\mu$ A, thus avoiding the non-exponential parts of the curve. The silicon diode is temperature dependent (it is often used as a thermometer) and so great care must be used to avoid thermal problems. The junction voltage changes by  $-1.9$  mV/ $^{\circ}$ C, but a semitone change is equivalent to 1.5 mV,

therefore a  $1^{\circ}$ C change could result in a 1.27 semitone change in pitch! Figure 9 shows two temperature effects in operation; there is a large shift and the slope of the line changes.

Figure 10 illustrates the equations that determine the diode operation. Two facts emerge from these equations. First, an 18 mV change in  $V_{BE}$  will double the current  $I_C$ , and second, this parameter has a temperature coefficient of  $-0.33\%/^{\circ}$ C. Both the temperature problems can be resolved by using a circuit similar to that shown in Fig. 11. Transistor Q1 is run at constant current (12  $\mu$ A) by the op-amp. Q2 is used as the exponentiator transistor. The emitter of Q2 is held at a voltage of about  $-0V6$ . Any voltage change at the base of Q2 will result in an exponen-

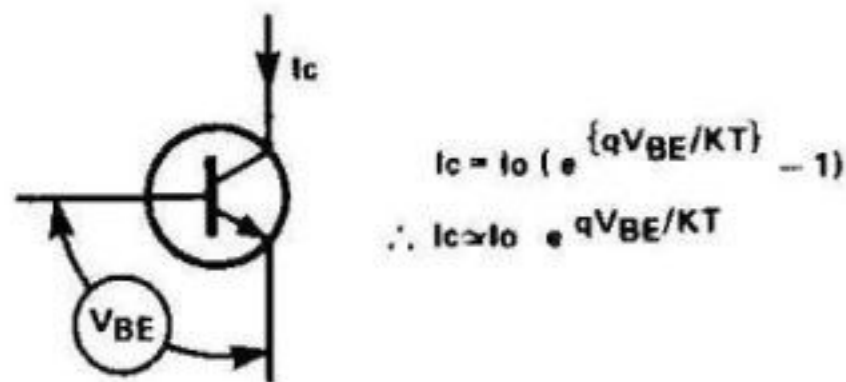

$$I_c = I_o (e^{(qV_{BE}/KT)} - 1)$$

$$\therefore I_c \approx I_o e^{qV_{BE}/KT}$$

WHERE  
 $I_o$  IS THE EMITTER SATURATION CURRENT  
 $K$  IS BOLTZMANN'S CONSTANT  
 $q$  IS THE CHARGE ON AN ELECTRON  
 $T$  IS THE TEMPERATURE IN  $^{\circ}$ K

HOWEVER,  $\frac{KT}{q}$  IS 26mV AT 28.58  $^{\circ}$ C (301.73  $^{\circ}$ K IS ROOM TEMPERATURE).  
 THEREFORE,  $I_c \approx I_o e^{V_{BE}/26}$

WHERE  $V_{BE}$  IS MEASURED IN mV  
 REARRANGING THE EQUATION,

$$26 \cdot \ln \left( \frac{I_c}{I_o} \right) = V_{BE}$$

THEREFORE, AN OCTAVE CHANGE IN  $I_c$  IS CAUSED BY A 18.021827mV CHANGE IN  $V_{BE}$  (AT 28.58  $^{\circ}$ C). HOWEVER, IF THE TEMPERATURE WERE  $+1^{\circ}$ C HIGHER, THEN  $V_{BE}$  WOULD HAVE TO BE INCREASED IN SIZE TO A NEW VALUE OF


$$26 \times \left( \frac{302.73}{301.73} \right)$$

SO, FOR AN OCTAVE CHANGE IN  $I_c$  AT THE NEW TEMPERATURE,  $V_{BE}$  MUST CHANGE BY 18.08155mV, AN INCREASE OF 0.059723mV. THIS CAN BE EXPRESSED AS A PERCENTAGE CHANGE PER  $^{\circ}$ C :-

$$\text{TEMPERATURE SENSITIVITY} = \frac{0.059723 \times 100}{18.021827} = 0.33139\%/^{\circ}\text{C}$$

Fig. 10 Exponential transistor characteristics.

Fig. 11 (Below) An exponential current sink.

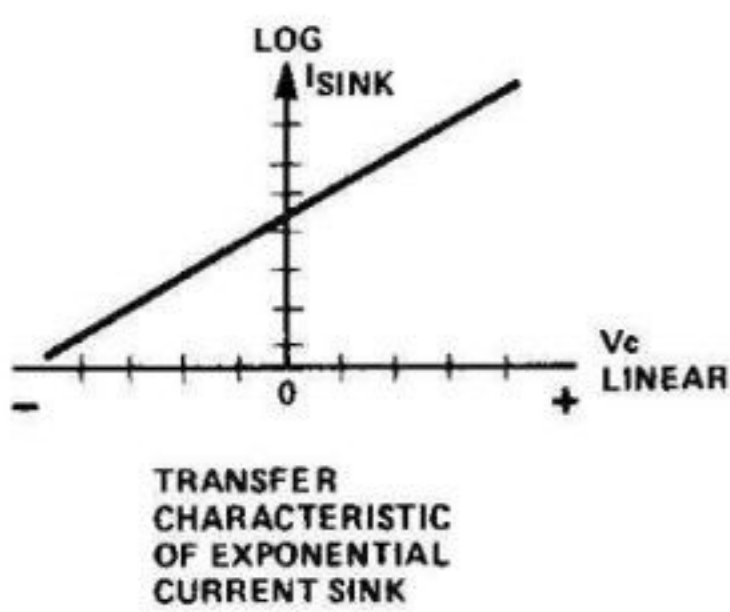

TRANSFER CHARACTERISTIC OF EXPONENTIAL CURRENT SINK

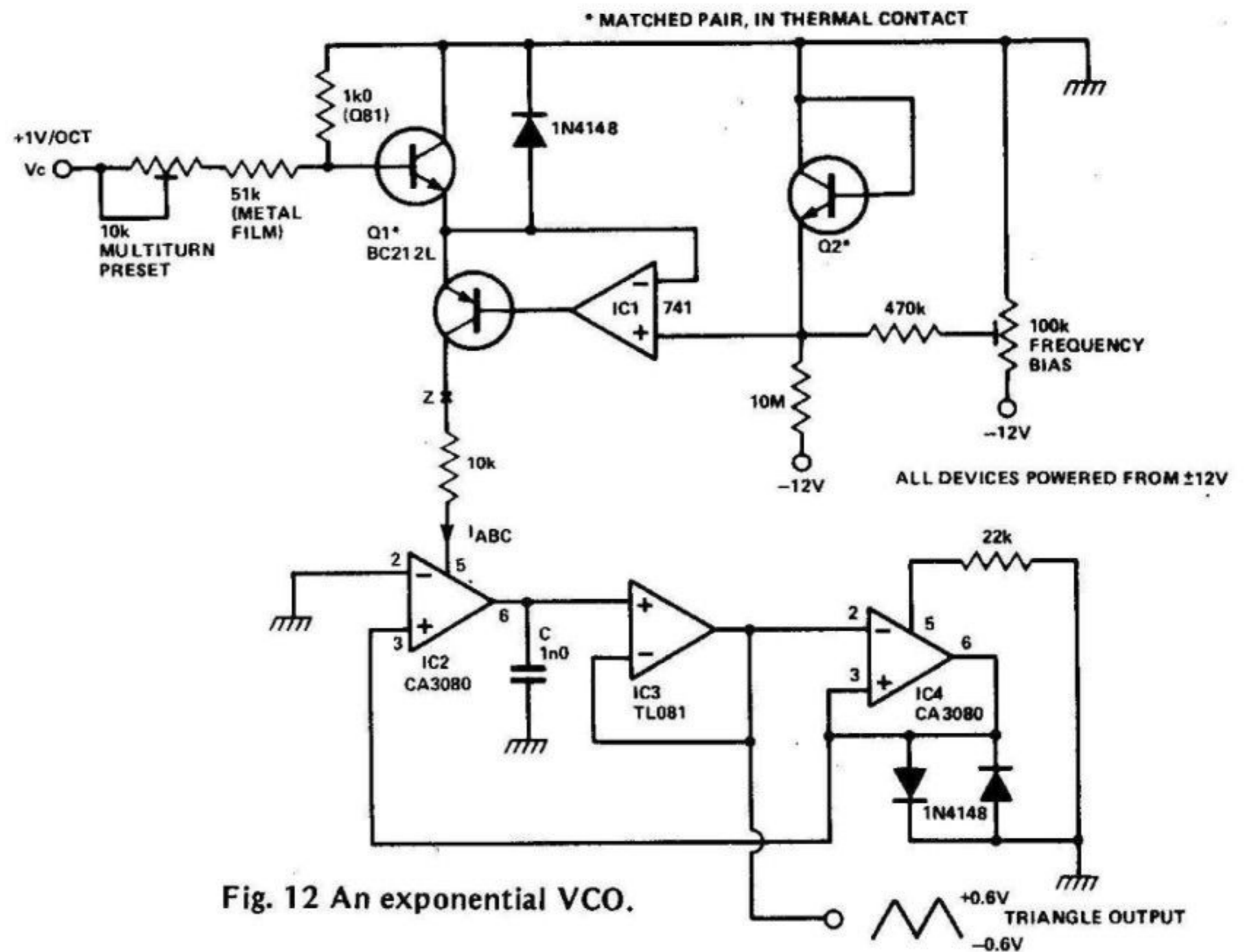
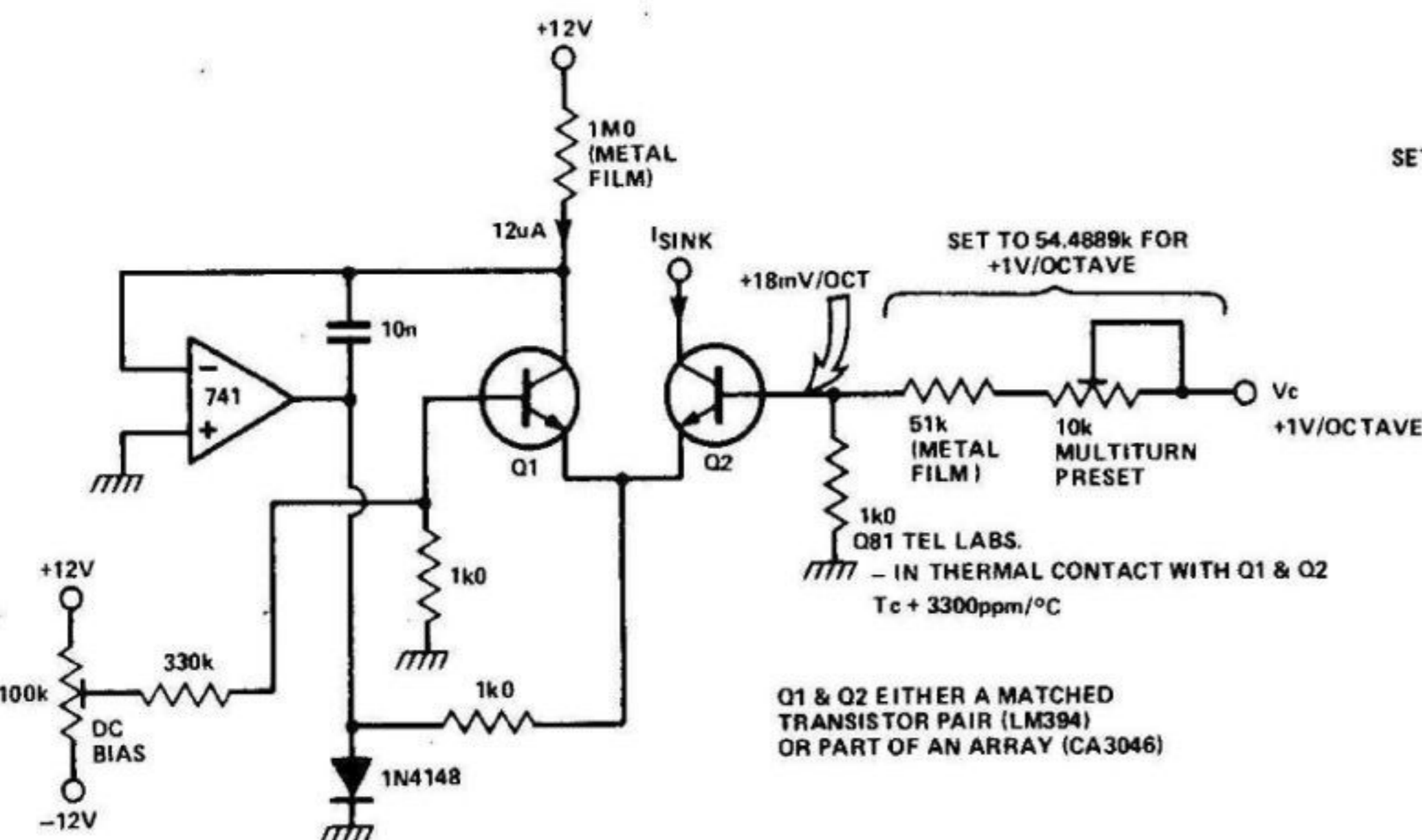


Fig. 12 An exponential VCO.

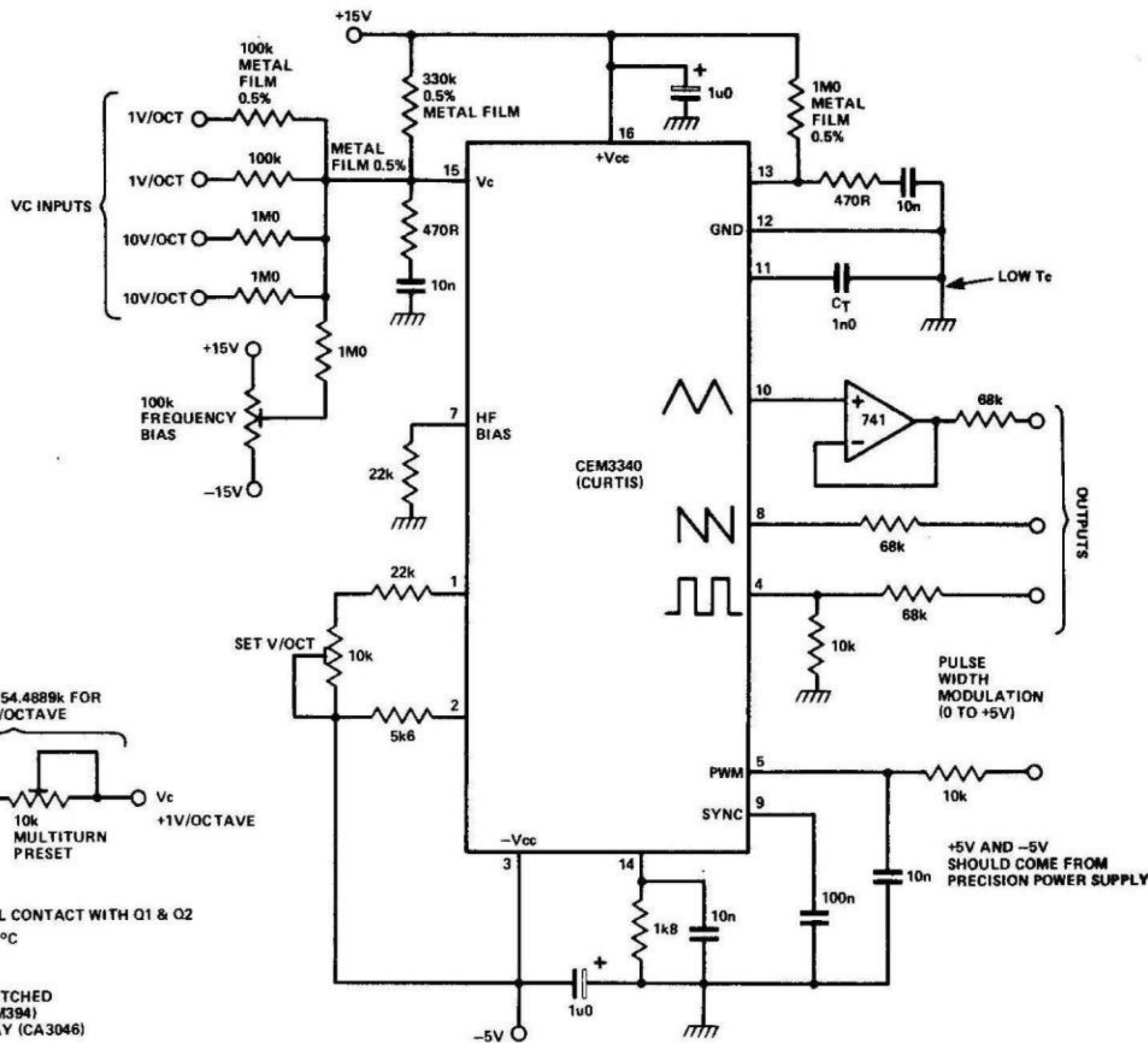


Fig. 13 A VCO using a monolithic device.

tial change in the collector current of Q2. Q1 and Q2 are in thermal contact and so any temperature change will effect both equally. Thus the  $-1.9 \text{ mV}/^\circ\text{C}$  factor is cancelled out by Q1 acting as a compensating thermometer for Q2. The slope change is removed by using a temperature sensitive resistance (Q81 — Tel Labs) which has an equal but opposite temperature coefficient to the diode junction. This resistor is often in thermal contact with the matched transistors. If this circuit is connected to a linear current controlled oscillator, a musical VCO is produced.

## VCO Circuits

Figure 12 is the circuit for an exponential VCO using an exponential current source. The oscillator is a standard triangle-square wave device. IC2 is a current-controlled integrator; the slow rate at its output is equal to  $I_{ABC}/C$ . This voltage is buffered by IC3 which drives a Schmitt trigger IC4. The output of IC2 ramps up and down between the two hysteresis levels which are determined by the two clamping diodes connected to the output of IC4. Any stray capacitance on the output of IC4 will slow down the Schmitt trigger and this will make the VCO go flat at high frequencies. Also the propagation time delay around the oscillator will cause a flattening out of the response at high frequencies. These effects can be nulled out but they may not even affect things if the VCO frequency is kept relatively low.

A very good VCO is shown in Fig. 13. It is a monolithic device, the CEM3340 from Curtis Electromusic Specialities Inc who make a range of electronic music devices. As can be seen, very few external parts are needed to implement the VCO. All the temperature compensation is performed inside the chip. Triangle, sawtooth and variable mark/space square wave outputs are simultaneously available. The mark/space ratio is a voltage controlled parameter. A sync input is also provided so that the VCO can be slaved to another oscillator.

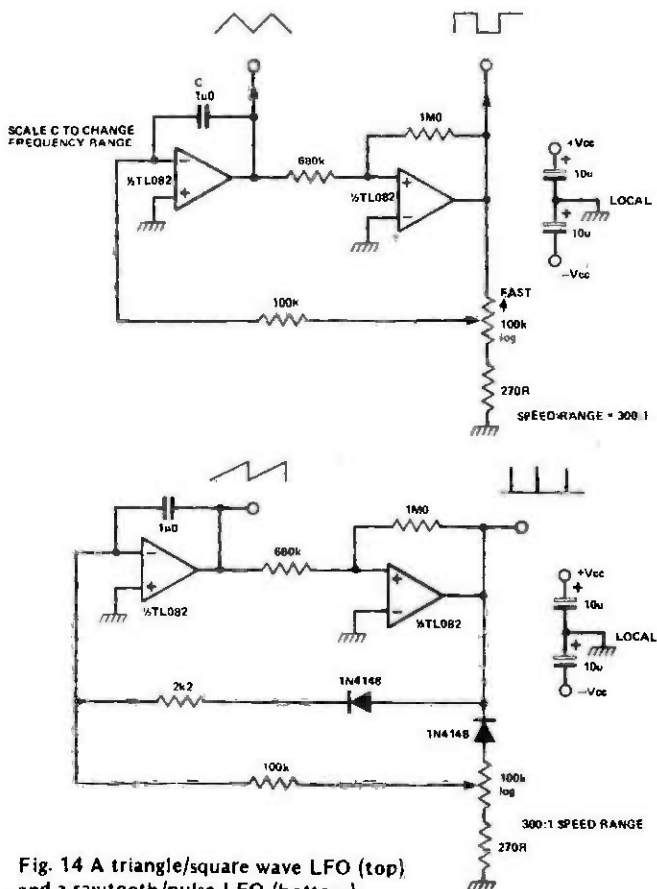


Fig. 14 A triangle/square wave LFO (top) and a sawtooth/pulse LFO (bottom).

## LFO Circuits

A couple of LFO units are shown in Fig. 14. All four output waveforms can be usefully employed to sweep VCOs and VCFs. Often the waveforms are mixed together to produce strange frequency modulations. When the sawtooth is fed into one side of a ring modulator and noise into the other, a beat track can be generated; it sounds a bit like a cymbal being hit.

## Noise Generators

In 'the old days' noise sources were made by amplifying the noise current of a diode junction that was zenering. These were a bit unreliable, and always involved selecting the device. However, noise can be generated digitally with a maximum length pseudorandom sequence generator (Fig. 15). The noise spectrum is relatively flat and always the same. If you slow down the clock rate you can get some interesting sounds; I think that this is used on some TV games. If a longer shift register is used, say 30 or 40 stages (the 4006 is 18 stages long), and the noise source is turned on, a tone is initially heard which gradually changes into noise as the sequence becomes more scrambled up. You can purchase a monolithic noise generator (pseudorandom); it is the MM5837 made by National Semiconductor, also sold by AMI with the part number S2688.

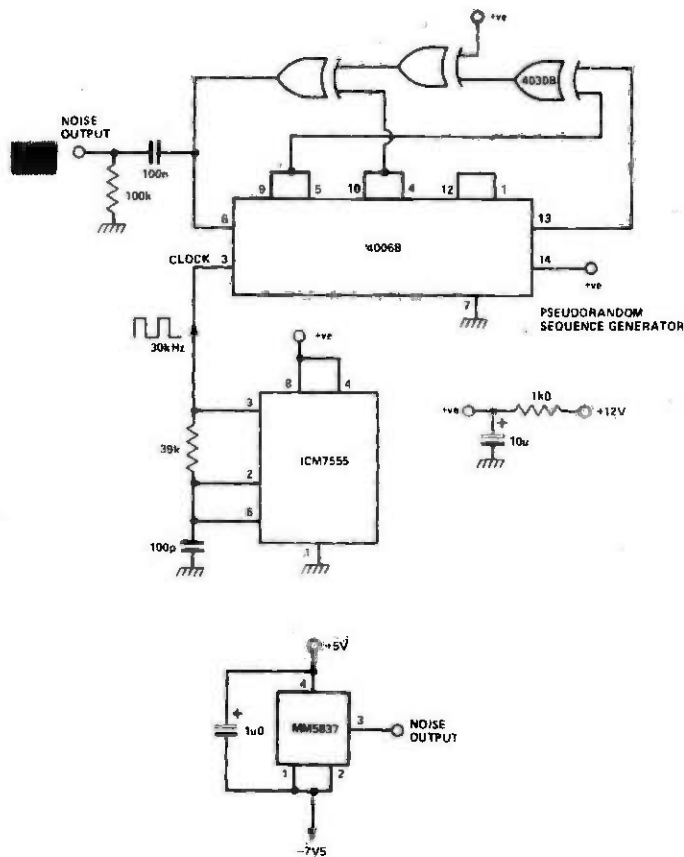


Fig. 15 A digital noise source (top) and a noise generator chip (bottom).

Five pages gone already, and we've still only scratched the surface of this fascinating subject. In part two next month, Tim Orr will continue his discussion of electro-music techniques with yet more circuit building blocks.

introducing

# The WERSI Comet



CLOSE UP OF COMET KEYBOARD

Aura Sounds have pleasure announcing the Comet, the "Band in One" organ, is now available through our branches. Once again the Comet achieves the optimum performance in its class.

It offers:—

- Numerous realistic and interesting tonal colours with guitar voices, synthesiser and other modern sounds together with the more traditional drawbar and orchestral sounds
- Playing aids include chord memory, WRS, Keyboard Selector, Wersi matic rhythm and automatic accompaniment section plus much, much more



THE COMET TRANSPORTABLE W10 T


- Comet can accept up to four satellite keyboards (in addition to the 2 keyboards on the organ — a five man band can play on one instrument.

- Wersi have simplified self assembly even more, with plug in circuits etc.

- Ergonomic playing table eases operation. The Comet is available in the elegant lines of the spinet (W10 S) and with chromed steel legs (W10 T) for transportability.

The Comet, the Organ to see us through the eighties — available now.

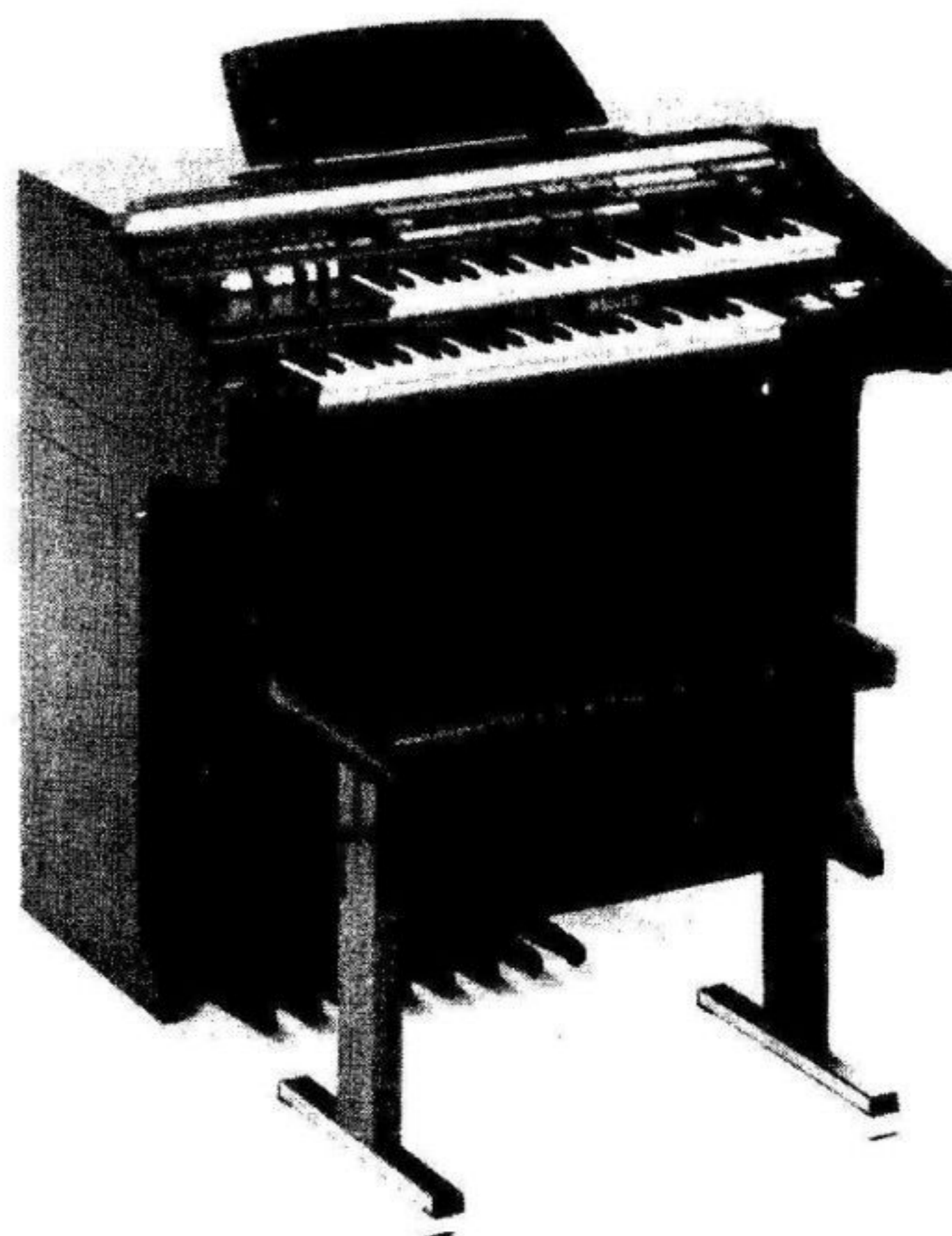For more details of this superb organ, ring us now on 01-668 9733 or write to Aura Sounds Ltd. at the Purley Branch.



THE COMET SPINET W10 S

**AURA SOUNDS LTD.**  
 are the first company to successfully market WERSI organs and kits in the U.K. We have modern show-rooms where we pride ourselves you will receive a friendly welcome Why not pop in and see the WERSI range for yourself — we can always arrange a free demonstration. We also offer a free technical telephone support service which is second to none.

Alternatively, fill in the coupon below for free details. For immediate action telephone 01-668 9733 24 hour answering service.

**AURA SOUNDS LTD.**  
 14-15 Royal Oak Centre, Brighton Road, Purley, Surrey.  
 Tel: 01-668 9733  
 17 Upper Charter Arcade, Barnsley, Yorkshire.  
 Tel: (0226) 5248  
 1729 Coventry Road, Sheldon, Birmingham.  
 Tel: 021-707 8244  
 Micro Centre, Albany Road, Newquay, Cornwall.  
 Tel: Newquay 5953

**WERSI and AURA — The Winning Combination**


Please send me FREE, all the details of The Comet and Wersi Range

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

Send to Aura Sounds Ltd., 14/15 Royal Oak Centre, Brighton Road, Purley, Surrey.

# ACCURATE VOLTAGE MONITOR

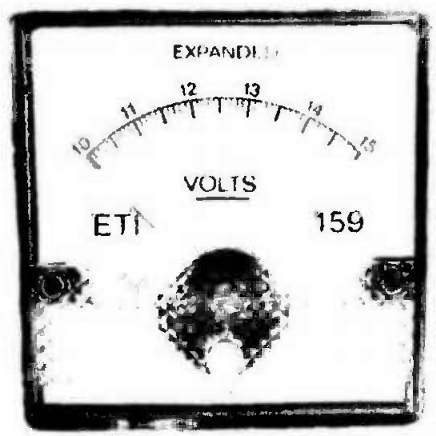

This simple, low-cost instrument can be built into power supplies or used as a portable or fixed 'battery condition' monitoring meter. Design by Simon Campbell and Roger Harrison.

Common storage batteries to power nominal 12 V DC electrical systems have a terminal voltage that ranges from a little over 10 V when discharged to around 15 V when fully charged, the operating voltage being somewhere in the range 11V5 to 13V8. Lead-acid batteries, for example, may have a terminal voltage under rated discharge that commences at around 14V2 and drops to about 11V8. A 12 V (nominal) nickel-cadmium battery may typically have a terminal voltage under rated discharge that starts at 13 V, dropping to 11 V when discharged.

Equipment designed to operate from a nominal 12 V DC supply may only deliver its specified performance at a supply voltage of 13V8 — mobile CB and amateur transceivers being a case in point. Other DC operated equipment may perform properly at 12V5 but 'complain' when the supply reaches 14V5.

To monitor the state of charge/discharge of a battery, a battery-operated system or the output of power supplies, chargers, etc, a voltmeter which can be easily read to 100 mV over the range of interest (10 to 15 V) is an invaluable asset. This project does just that.

## The Circuit

An LM723 variable voltage regulator is employed to set an accurate 'offset' voltage of 5 V, and the meter (M1) plus the trimpot RV2 and R3 make up a 5 V meter, with the trimpot allowing calibration. The negative terminal of the meter is connected to the output of the 723 so that it is always held at 5 V 'above' the circuit negative line. The positive end

of the meter goes to a zener which will not conduct until more than 5 V appears between the circuit +ve and -ve lines. Thus the meter will not have forward current flowing through it until the voltage between the +ve and -ve rails is greater than 10 V, and will read full scale when it reaches 15 V (after RV2 is set correctly).

The meter scale limits may be adjusted by setting the output of the 723 higher or lower (adjusted by RV1) and setting RV2 so that the meter has an increased or decreased full-scale deflection range.

A variety of meter makes and sizes may be used.

## Construction

Mechanical construction of this project has been arranged so that the PCB can be accommodated on the rear of any of the commonly available moving coil meter movements. We chose a meter with a 55 mm wide scale (overall panel width, 82 mm). A meter movement with a large scale is an advantage as it is considerably easier (and more accurate) to read than

## HOW IT WORKS

The meter, M1, is a 1 mA meter with series resistance — made up of R3 and RV2 — so that it becomes a 0.5V voltmeter. The negative end of the meter is maintained at 5 V above the circuit negative line by the output of IC1, a 723 adjustable regulator. The positive end of the meter is connected to the circuit positive line via ZD1, a 4V7 zener diode. Thus, no 'forward' current will flow in the meter until the voltage between the circuit negative line and the circuit positive line is greater than  $5 + 4.7 = 9V7$ . Bias current for the zener is provided by a FET, Q1, connected as a constant current source so that the zener current is accurately maintained over the range of circuit input voltage. This ensures the zener voltage remains essentially constant so that meter reading accuracy is maintained. The trimpot RV1 sets the output voltage of the 723. This determines the lower scale voltage. Trimpot RV2 sets the meter scale range, less resistance decreases it. Diode D1 protects the circuit against damage from reverse connection.

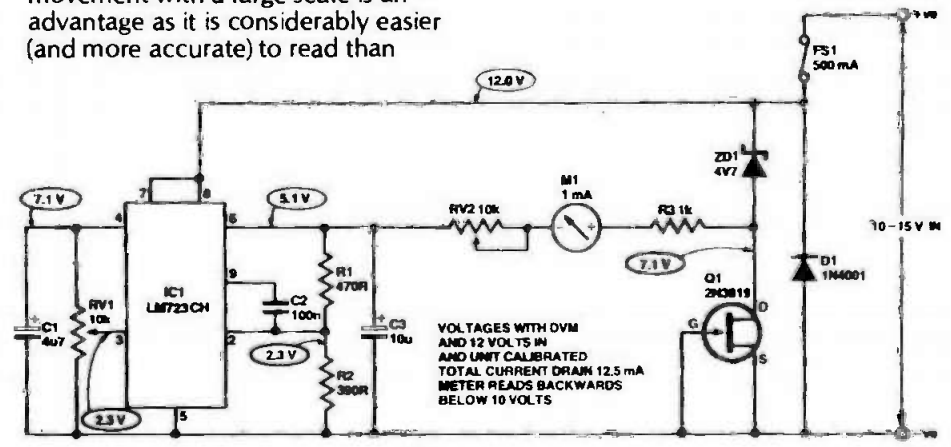


Fig. 1 Circuit diagram for the Voltage Monitor.

# PROJECT : Voltage Meter

Having chosen your meter, drill out the PCB to suit the meter terminal spacing first. The components may then be assembled to the board in any particular order that suits you. Watch the orientation of the 723, ZD1, the FET and particularly D1. The latter is an 'idiot diode'. That is, if you have a lapse of concentration or forethought and connect your project backwards across a battery, the fuse will blow and not the project. Fuses are generally found to be cheaper than this project!

Seat all the components right down on the PCB as the board may be positioned on the rear of the meter with the components facing the meter. The size of C2 may give you a little trouble. Polyesters are generally too large and therefore unsuitable. We used a ceramic type capacitor — as commonly used on computer PCBs as bypasses. Alternatively, a 100n tantalum capacitor (+ve to pin 2 of IC1) may be used. The actual value or type of capacitor is not all that critical.

We have used multiturn trimpots for RV1 and RV2 as they make the setting up a whole lot easier

## Calibration

For this you will need a variable power supply covering 10 to 15 V and a digital multimeter (borrow one for the occasion).

First set the 10 V point. Connect the digital multimeter across the power supply output and adjust the power supply to obtain 10.00 V. Set the mechanical zero on the meter movement to zero the meter's pointer. Connect the unit to the power supply output and adjust RV1 to zero the meter needle.

Next, set the power supply to obtain 15.00 V. Now adjust RV2 so that the meter needle sits on 15 V (full scale). Check the meter reading with the power supply output set at various voltages across the range. We were able to obtain readings across the full scale within  $\pm$  half a scale reading ( $\pm$  50 mV). With a 2% FSD accuracy meter the worst error may be about  $\pm$  one scale division.

## BUYLINES

Only one thing to comment on here; when you purchase your LM723 (or uA723 — same thing) make sure you get the version that comes in a T099 case, not the DIL version. The PCB is designed for the 10 pin version as shown in the overlay and the DIL type won't fit. Speaking of PCBs, as usual you can get it from us using the order form on page 44.

## PARTS LIST

Resistors (all  $\frac{1}{4}$  W, 5% metal film)  
 R1 470R  
 R2 390R  
 R3 1k0

Potentiometers  
 RV1,2 10k cermet multiturn horizontal trimpot

Capacitors  
 C1 4u7 10 V tantalum  
 C2 100n ceramic  
 C3 10u 10 V tantalum

### Semiconductors

IC1 LM723 (see Buylines)  
 Q1 2N3819  
 D1 1N4002 or similar  
 ZD1 4V7 400 mW or 1 W zener

### Miscellaneous

M1 1 mA meter (see text)  
 FS1 500 mA fuse and in-line fuse holder  
 PCB (see Buylines); meter scale to suit meter; red and black cable, etc.

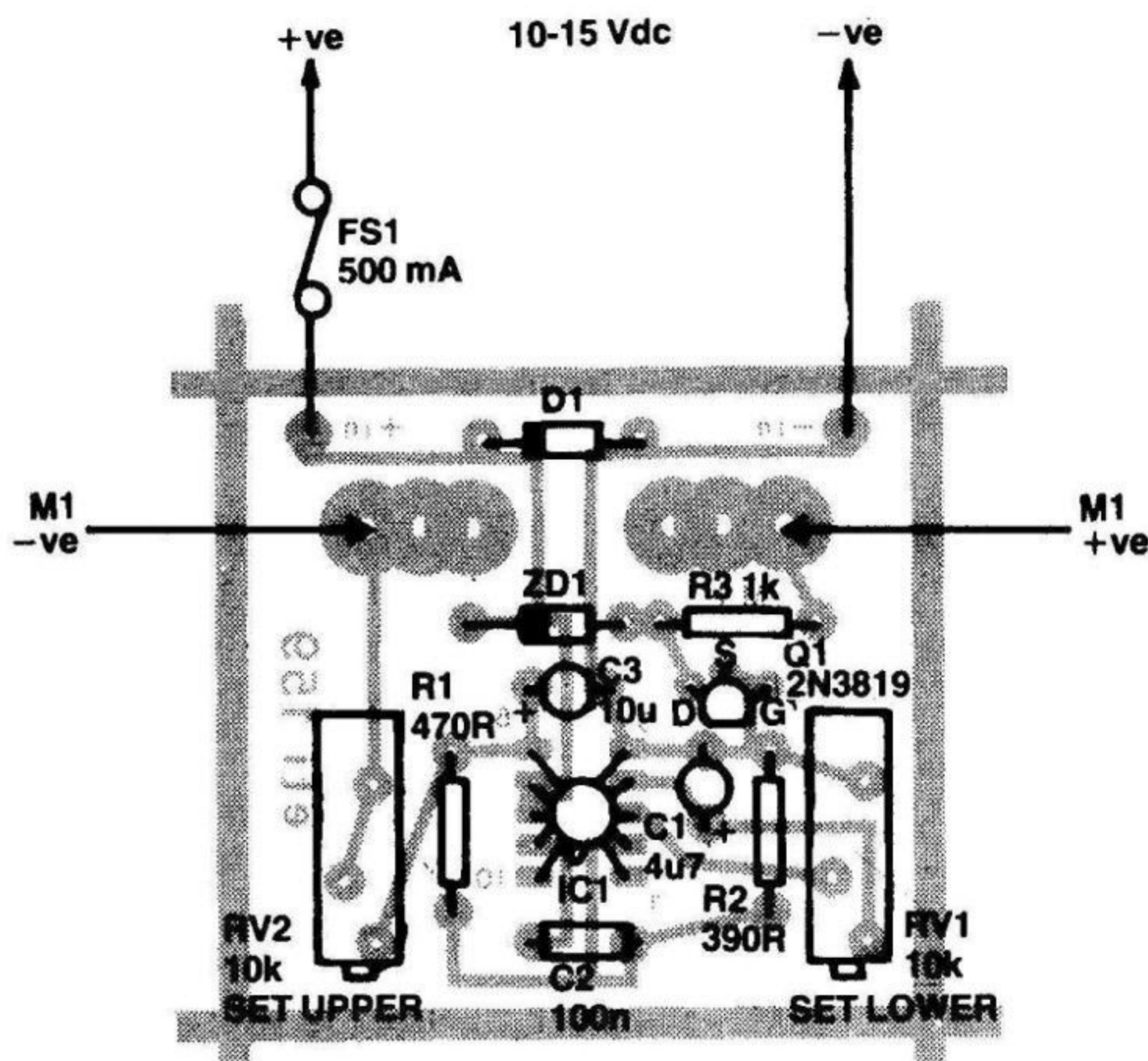


Fig. 2 Component overlay for the Voltage monitor. Note that IC1 is in a 10-pin T099 case.

## BATTERY CONDITION AND TERMINAL VOLTAGE

The 12 V battery, in its many forms, is a pretty well universal source of mobile or portable electric power. There are lead-acid wet cell types, lead-acid gel electrolyte (sealed) types, sealed and vented nickel cadmium types, and so on. They are to be found in cars, trucks, tractors, portable lighting plants, receivers, transceivers, aircraft, electric fences and microwave relay stations — to name but a few areas.

No matter what the application, the occasion arises when you need to reliably determine the battery's condition — its state of charge, or discharge. With wet cell lead-acid types, the specific gravity of the electrolyte is one reliable indicator. However, it gets a bit confusing as the recommended electrolyte can have a different S.G. depending on the intended use. For example, a low duty lead-acid battery intended for lighting applications may have a recommended electrolyte S.G. of 1.210, while a heavy-duty truck or tractor battery may have a recommended electrolyte S.G. of 1.275. Car batteries generally have a recommended S.G. of 1.260. That's all very well for common wet cell batteries, but

measuring the electrolyte S.G. of sealed lead-acid or nickel-cadmium batteries is out of the question.

With NiCads, the electrolyte doesn't change during charge or discharge.

Fortunately, the terminal voltage is a good indicator of the state of charge or discharge. In general, the terminal voltage of a battery will be at a defined minimum when discharged (generally between 10 and 11 V), and rise to a defined maximum when fully charged (generally around 15 V). Under load, the terminal voltage will vary between these limits, depending on the battery's condition.

Hence a voltmeter having a scale 'spread' to read between these two extremes is a very good and useful indicator of battery condition. It's a lot less messy and more convenient than wielding a hydrometer to measure specific gravity of the electrolyte!

The charge and discharge characteristics of typical lead-acid and sealed NiCad batteries are given in the accompanying figures.



# ELECTRONIC KITS

## Micro-processor universal Timer

This incredibly versatile programmable timer can control up to 20 functions at accurately timed intervals over a period of a week. Originally developed for industrial and laboratory use it offers many interesting and exciting possibilities for the amateur constructor.

Based on a pre-programmed TMS 1000 Microprocessor, the unit provides a 24 hour clock with four independent relay controlled outputs with a programmable period of one week. Up to 20 daily or weekly programmable functions can be set via a keyboard. Any of the timer functions can be assigned to control any one of the four relay outputs thus providing almost unlimited programming possibilities.

No previous experience of microprocessor programming is necessary since the manual explains all the possible operations, clearly and simply, enabling the inexperienced user to be fully conversant within one hour. Completed programme steps are indicated by LED's

The kit comes complete with printed panel and may be installed either as a 'built-in' or a 'free-standing' unit. A stabilised power supply mounted on a separate printed circuit board is supplied with the unit. It requires the addition of a 12V, 1A transformer. There is space on the board for up to four output control relays. One is supplied with the kit. Further relays may be ordered separately as required. Price: (excluding wooden housing as illustrated) **£48.37** inclusive of VAT and **DELIVERED FREE** on U.K. mainland.

### APPLICATIONS

The programmable timer can provide central control of domestic electrical cooking, heating and entertainment equipment.

The possibilities are limited only by the imagination of the user. Control of house lighting to discourage intruders; control of TV or audio equipment; sound or video recording control; automatic plant watering; automatic pet doors or feeding — are a few simple examples. For the professional or industrial user many uses in this area of process control will be found.

### TECHNICAL DATA:

**Power supply:**  
Mounted on separate pcb with space for up to four output control relays. Requires 12V/1A transformer.

### CONTROL SWITCHING:

Standard relays (one supplied with kit) will switch 2A.  
Additional relays may be ordered separately.  
National relay, order no. HT 12V.  
Siemens relay, order no. R1 INV12.

### MICROPROCESSOR:


TMS 1000

### DISPLAYS:

12mm 7 segment LED numerical display, LED programme function indicators.

### DIFFICULTY GRADE: 3

KIT NUMBER: K1682

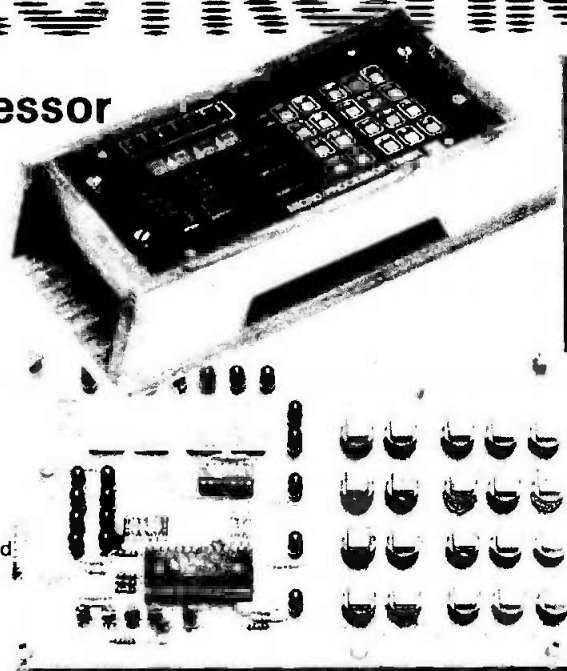

### THE VELLEMAN KIT RANGE

2.2 Watt mini amplifier  
Mono VU using LED's  
7 Watt amplifier  
Dimmer 1000 Watt  
Dimmer 1000 Watt (deparasite)  
High precision stopwatch  
Microprocessor Universal timer  
20 Watt monolithic amplifier  
FM oscillator  
Stereo VU using LED's  
Universal mono pre-amplifier  
60 Watt power amplifier  
Power supply 1 Amp  
Power supply for stereo 60 Watt amplifier  
Running light  
Digital panel meter  
Single digit counter  
Transistor ignition  
Complex sound generator  
50 Hz crystal base  
4 channel infra-red remote control (transmitter or receiver)  
Infra-red detection system (transmitter or receiver)  
Central alarm unit  
FM stereo decoder  
High quality FM tuner  
Digital frequency counter for receivers  
CB power supply 3.5 Amp 12V  
Digital thermometer  
FM stereo receiver (19 in. rack-mounting)  
2 channel infra-red remote control light dimmer (transmitter or receiver)  
Infra-red receiver for tuner K2558  
Infra-red transmitter for tuner K2558  
Tape/slide synchronizer  
3 channel coloured light organ  
20 cm display (common anode)  
20 cm display (common cathode)  
Three tone bell  
5-14V DC 1 Amp Universal power supply  
Light computer  
Universal stereo pre-amplifier  
Stereo RIAA corrector amplifier  
Universal 4 digit up/down counter with comparator  
Microprocessor doorbell with 25 tunes  
40 Watt audio amplifier  
Electric drill speed control  
Microprocessor-controlled EPROM programmer (kit form)  
Microprocessor-controlled EPROM programmer (built and tested)  
Universal start/stop timer

**Repair Service available (for a nominal charge) if your soldering technique is not quite what it should be!**

**Any technical enquiries welcomed —in writing—and will be answered promptly by letter.**

**TRADE ENQUIRIES WELCOME**



# VELLEMAN UK

P.O. Box 30, St. Leonards-on-Sea, East Sussex TN37 7NL Tel: Hastings (0424) 753246

Limited

Please send me your free catalogue of Velleman electronic kits:

ETI

Name .....

Address .....

# COMPUTER EXPANSION SYSTEM

How's your memory? If you're lacking EPROM and the ability to program it, the fourth of our expansion cards is just what you need. Design by Watford Electronics.

This month we present an EPROM programmer and associated EPROM cards suitable for the machine code freak to store away those beloved extra routines or the space invaders freak to capture his aliens in 0's and 1's for life.



The first major consideration when designing an EPROM programmer is just what EPROMs should it be capable of blowing. There is more than just a little confusion here. There are two basic types of EPROM currently available — those that run off a three rail supply and those that run from a

single +5 V rail. The two sizes of PROM most popular at the moment are 2K x 8 and 4K x 8. Aha! here manufacturers have had some fun. Intersil and others like calling their triple rail PROMs 2716 and 2732 whereas Intel make their 2716 and 2732 single rail; not to be missed out Texas try to settle the balance by nominating their EPROMs 2516 and 2532; both are single rail!

To clear up the matter our programmer will program single rail EPROMs only, these being the most popular. It will program the Texas 2516 2K x 8 EPROM and Intel 2716 2K x 8 EPROM as these are pin-for-pin compatible (see Fig. 1). However, 2532

and 2732 4K x 8 EPROMs are not compatible and we have stuck to the 2532, as this then allows for use of the new 2764 8K x 8 EPROMs with the minimum alteration (see Fig. 2). If you wish to program 2764's then you must make the alterations to correct the OE/V<sub>pp</sub> and CS lines. A12 has been brought to pin 1 and power (V<sub>cc</sub>) to pin 28.

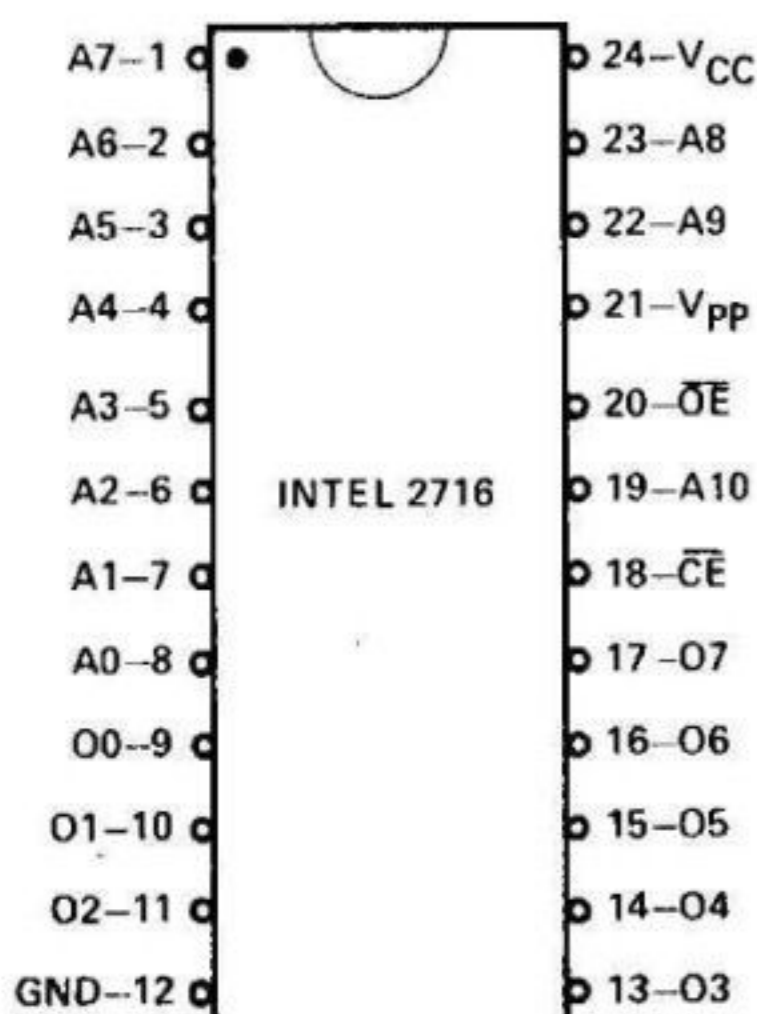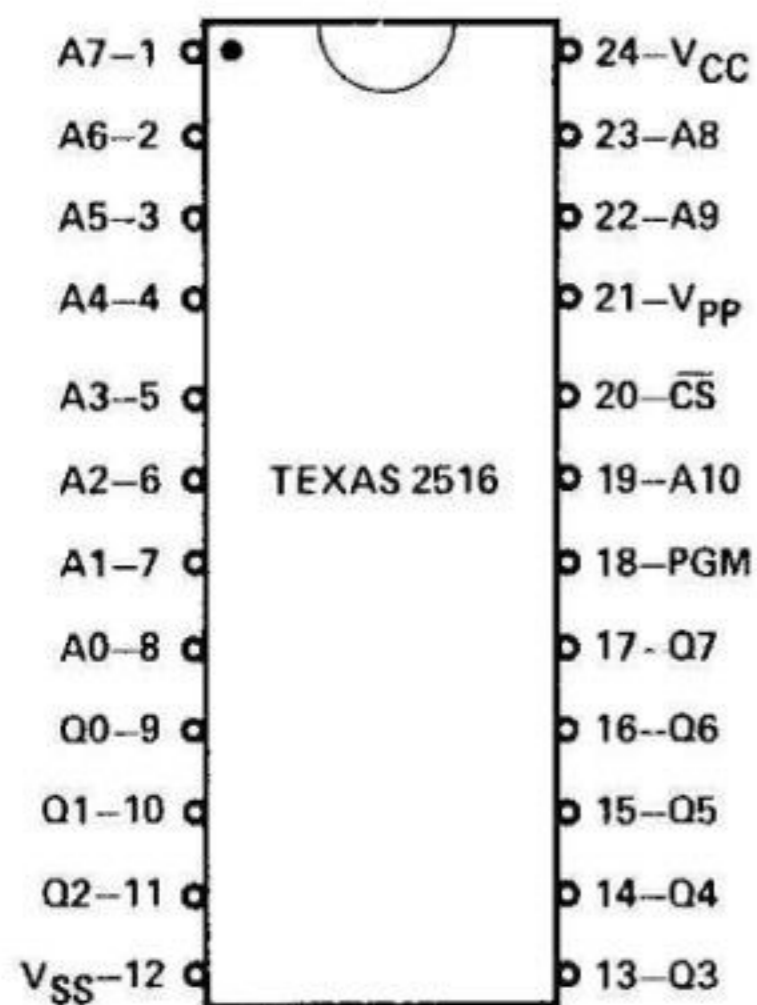Selection of the type of EPROM you want to program is made by means of a quad DIL switch. This switch is unusual in that each section operates two oppositely biased single pole switches — this means it can be



## HOW IT WORKS

### PROM PROGRAMMER

The heart of this board is two 6520 peripheral input-output chips — they serve to generate the address bus, the data and control signals for the chip being programmed.

R1 and C1 generate the power up reset; C4, 5 and 6 are included in for decoupling. The rather peculiar need of the V<sub>pp</sub> pin for 0, +5 V and +25 V is met by the PSU and switching circuit. Transformer T1 supplies 30 V AC to the bridge which rectifies it and feeds it to smoothing capacitor C3. IC3 and ZD1 regulate this to +25 V DC. C2 is included in the interests of stability. Transistors Q1 and Q2 handle the switching of V<sub>pp</sub> between 0, 5 and 25 V. This output is then fed to the DIL switch and then to the V<sub>pp</sub> pin of the EPROM to be programmed. Ports A and B of IC2 are used to generate the address bus — note A12 is connected to pin 1 of the EPROM (on a 28 pin basis) for use later with 2764 EPROMs. The data bus is generated by port A of IC1, while port B of IC1 generates the control for V<sub>pp</sub> and the CS and PGM lines which are switched with A11 to the correct pins of the EPROM by the DIL switch.

Inputs to the 6520s are straight from the expansion sockets —  $\phi$ 2 being used to enable the chips to reduce power consumption.

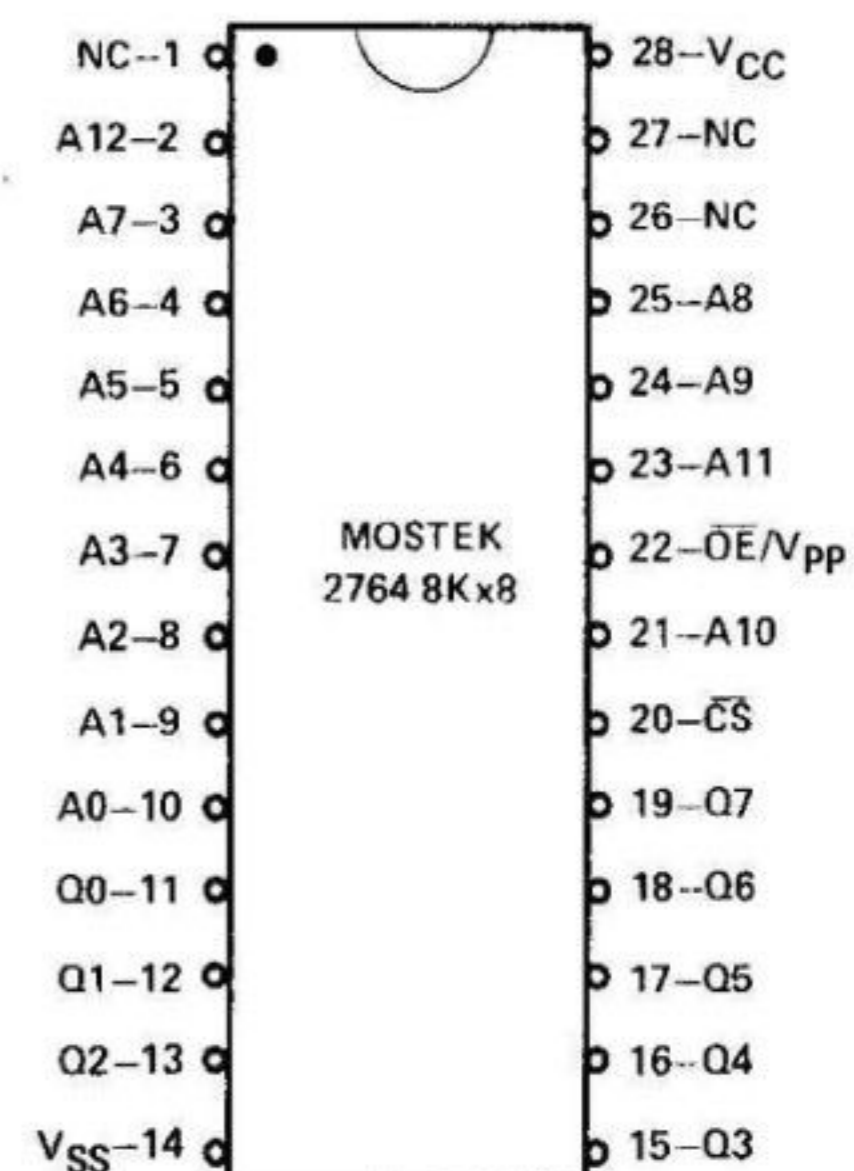
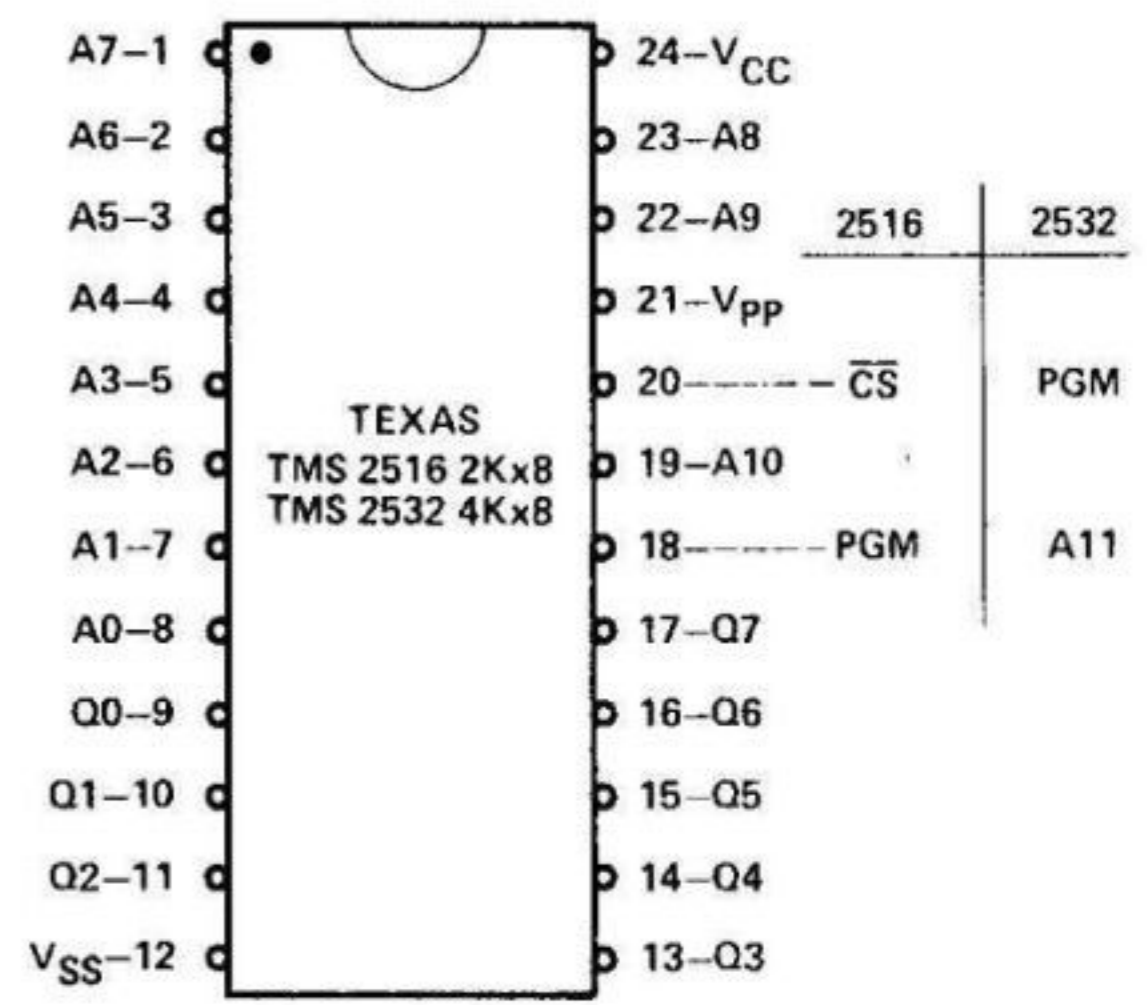


Fig. 1 You can program these EPROMs...

Fig. 2 ...or these ones.

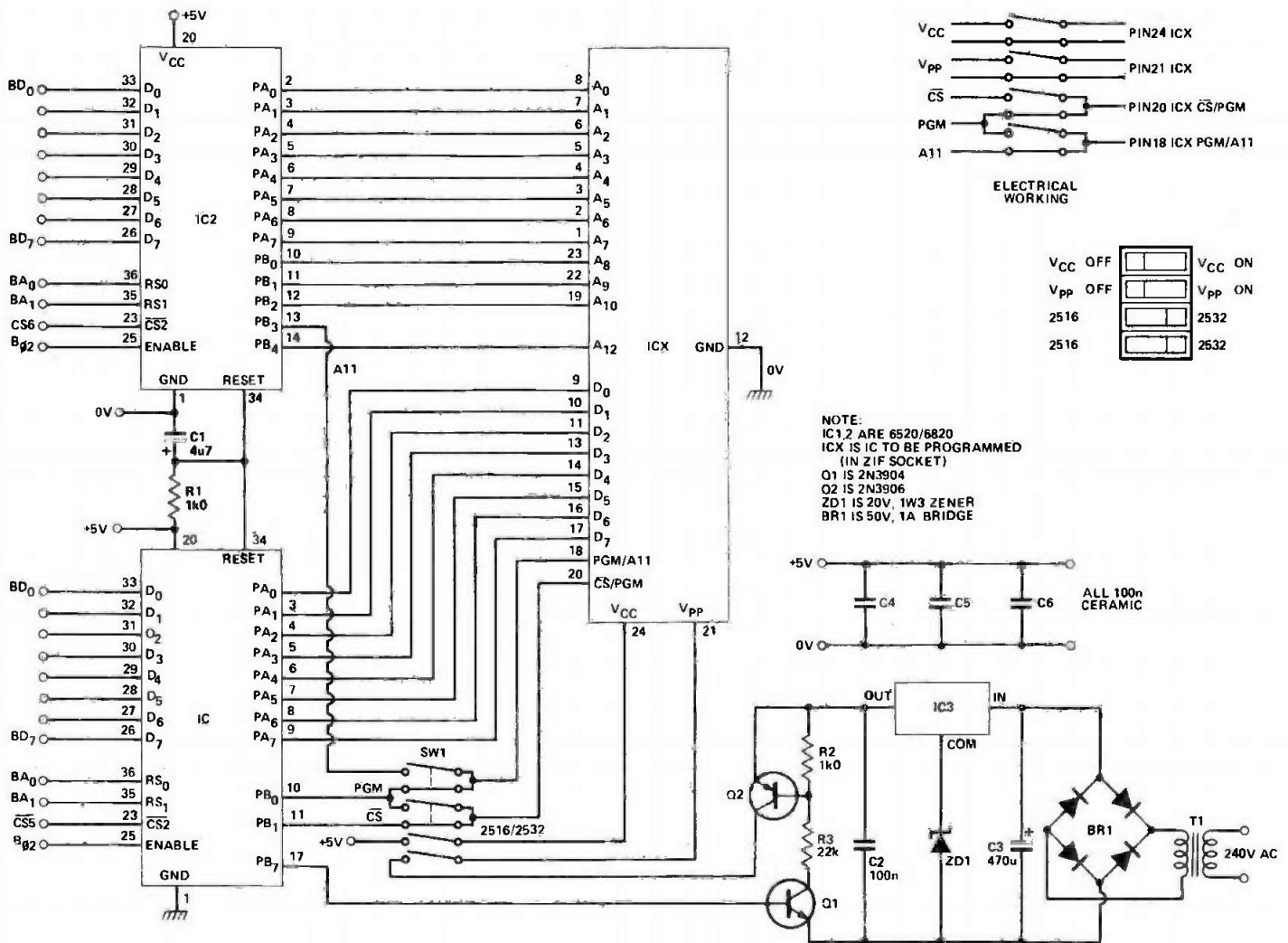


Fig. 3 Circuit diagram of the EPROM programmer, with details of SW1. ICX is the EPROM to be programmed.

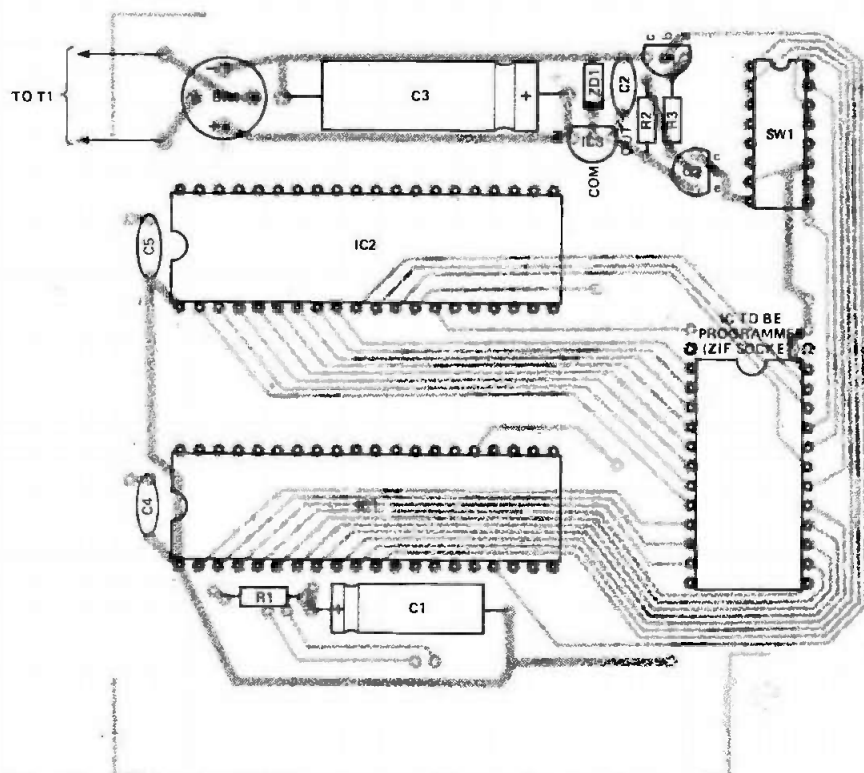


Fig. 4 Overlay for the EPROM programmer. The zero insertion force socket position has extra holes to allow for 2764s.

## PARTS LIST

PROM PROGRAMMER	
Resistors (all 1/4 W, 5%)	
R1,2	1k0
R3	22k
Capacitors	
C1	4u7 25 V axial electrolytic
C2,4,5,6	100n ceramic
C3	470u axial electrolytic
Semiconductors	
IC1,2	6520/6820
IC3	78L05
Q1	2N3904
Q2	2N3906
ZD1	20 V, 1W3 zener diode
BR1	1 A, 50 V bridge rectifier
Miscellaneous	
SW1	Quad DPST DIL switch
PCB (see Buylines); DIL sockets; transformer (6 VA, 0-15-0-15)	

used as a 4 pole changeover switch and makes it ideal for the job. Two of the four sections are used for chip power (+5 V) and the programming can be destroyed if V<sub>pp</sub> is applied with V<sub>cc</sub> disconnected. The other two sections are used to switch CS, PGM and A11 to the correct pins of the ZIF socket according to whether a 2516 or 2532 is to be used.

# PROJECT : Computer Expansion

## HOW IT WORKS

**PROM CARD**  
The PROM card is very straightforward as all the hard work is done by the motherboard. ICs 5 and 6 are used to generate A10 and A11 and the CS lines. The DIL header plug is used to set jumpers J1-J6 according to requirements (see text).

NOTE:  
IC1 IS 2516/2532/2764  
IC2 IS 2516  
IC3 IS 2516/2532  
IC4 IS 2516  
IC5,6 ARE 7408

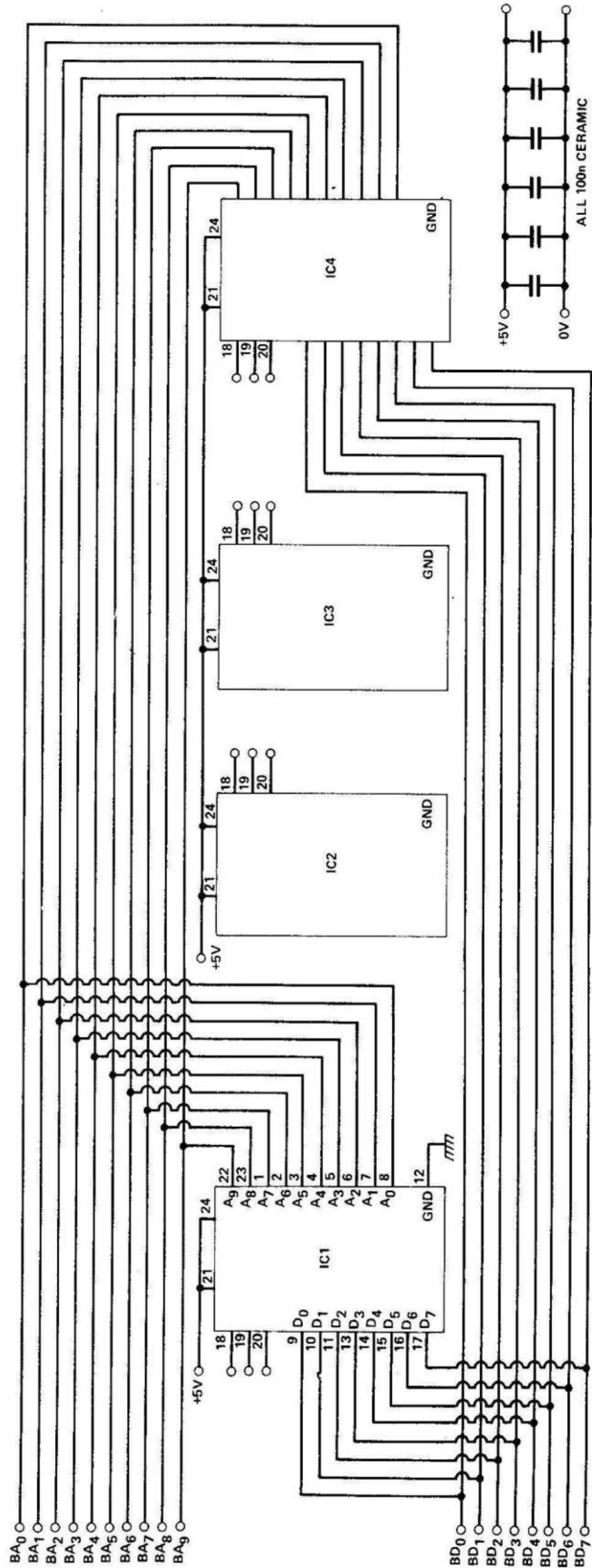
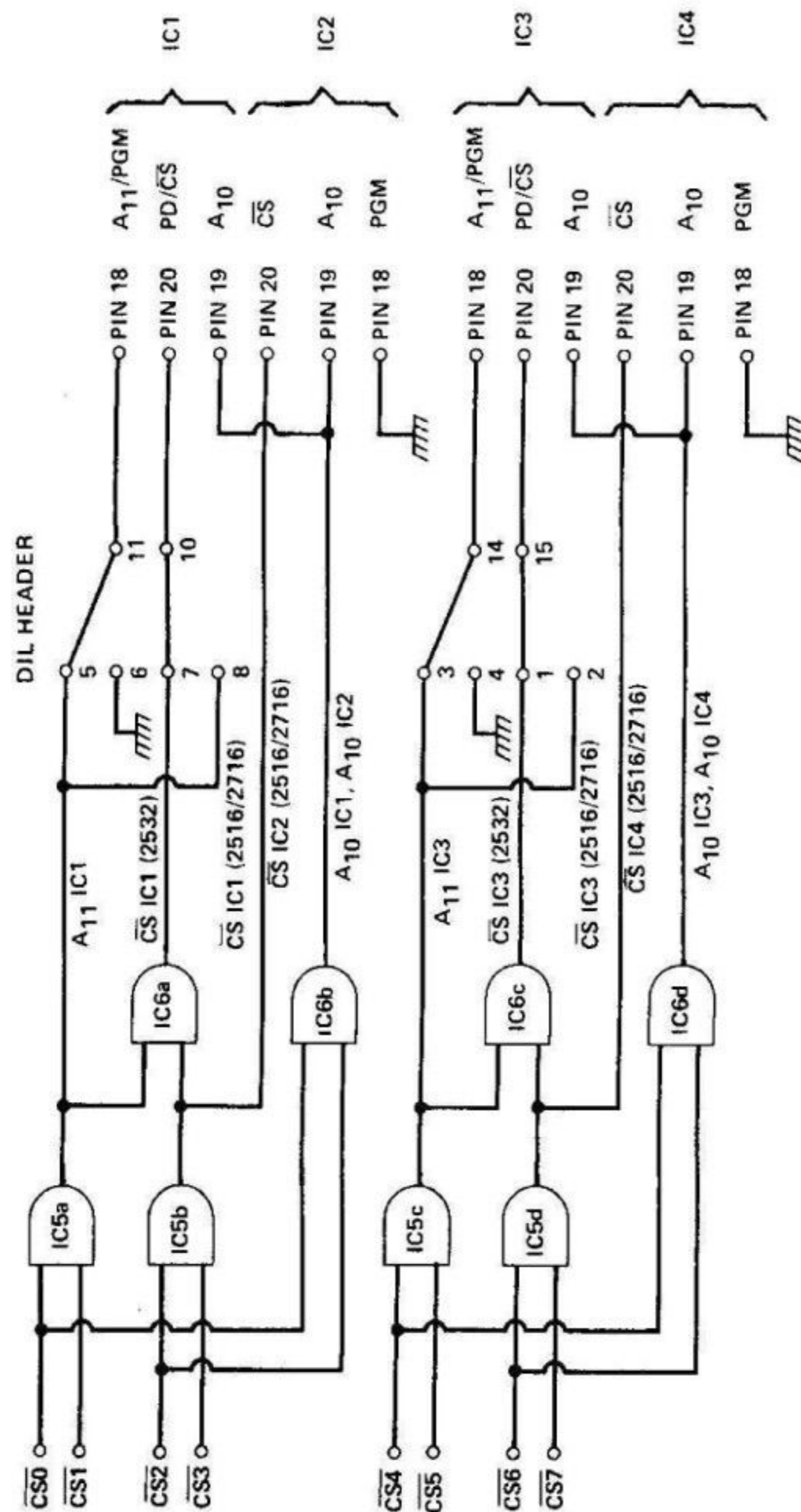


Fig. 5 Circuit diagram for the EPROM card. Links soldered to a DIL header select the correct signals for the various combinations of EPROMs — see Fig. 7 for details.

A similar method has been used on the EPROM card. As there are four sets of switches needed for four EPROMs a 16 pin header plug and socket have been used. You can make up a header for four 2516s and two 2532s and easily change the role of the board by simply exchanging header plugs. This retains better flexibility than jumper links and is cheaper than the method previously considered. The DIL header plug can be wired as in Fig. 3.

Refer to Fig. 7 for an explanation of how the header plug is wired.

## Construction

Construction of the two boards is very straightforward — follow the overlays given here. Note that if you want to move the card around in memory then simply break the connections CS5, CS6 to CS2 of the 6520 and re-make to the CS line you desire.

Use two Veropins or similar to bring the 30 V AC from the transformer to the board — unfortunate as it is using a transformer mounted off the PCB to generate the  $V_{pp}$  voltage, it is about the only practical way from a computer that has supply rails of 0 and 5V.

Fit the 28 pin DIL socket at the IC1 position on the EPROM board. This is to allow experimenters to fit a 2764-8K chip at a later date.

When you have finished you will have a very powerful means of customising your system to your own specifications. To mention one use: you could burn a renumber routine into ROM and then while writing a BASIC program simply renumber by calling the routine through the USR(X) function.

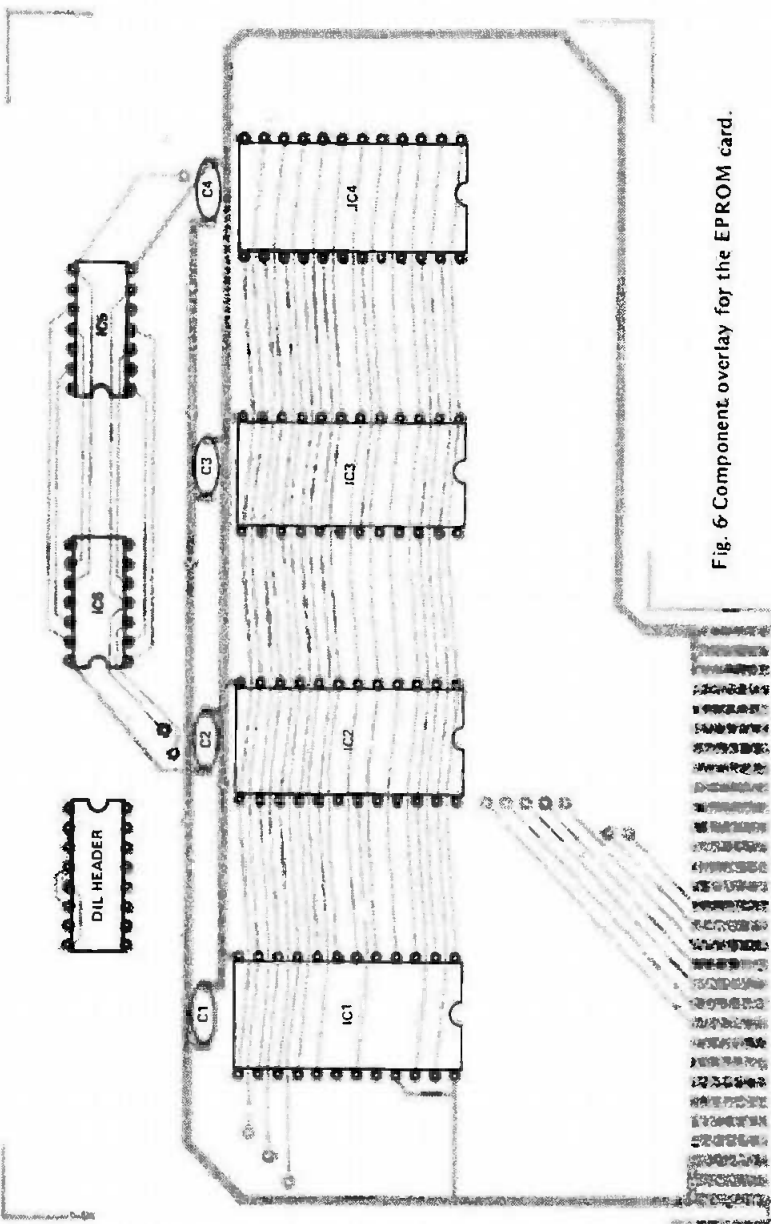


Fig. 6 Component overlay for the EPROM card.

## PARTS LIST

<b>PROM CARD</b>	
Capacitors	100n ceramic
C1-6	
<b>Semiconductors</b>	
IC1-4	2716, 2516, 2532 — PROMs
	as desired
IC5,6	7408
<b>Miscellaneous</b>	
PCB (see Buylines); DIL sockets as required; header plug (see text).	

## BUYLINES

A complete kit of parts for these expansion cards are available from Watford Electronics. The PROM programmer kit costs £26.95 (PCB only £9.75); the PROM card kit costs £11.95 (PCB only £9.75). All prices are subject to VAT at 15%.

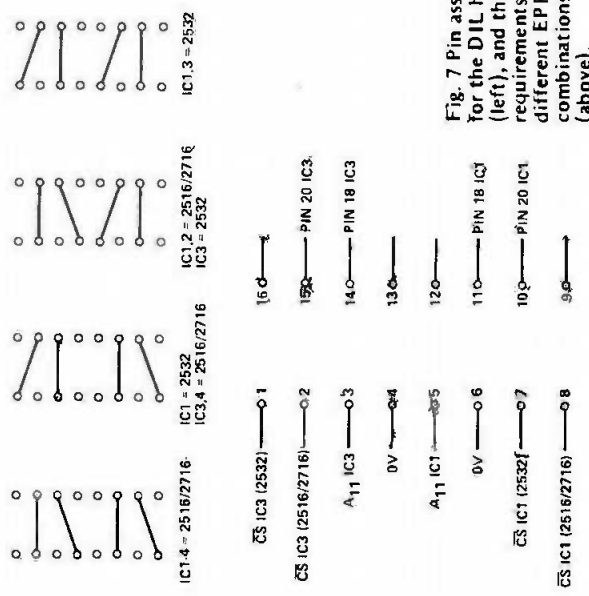



Fig. 7 Pin assignments for the DIL header (left), and the link requirements for the different EPROM combinations (above).

# MICROCOMPUTER COMPONENTS AND SYSTEMS

## LOWEST PRICES FASTEST DELIVERY
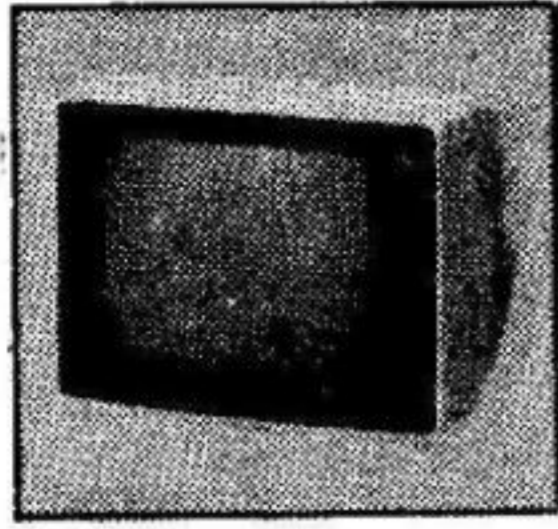
### NEC 12" MONITOR

- ★ GREEN DISPLAY
- ★ BUILT IN AMPLIFIER AND SPEAKER
- ★ £149.95 each excluding carriage (£10.00) and V.A.T. (15%)
- ★ EX-STOCK\*




The NEC JB1201M is a 12" Video Monitor optimised for use as a computer video display terminal (unlike most CCTV monitors available). The green phosphor CRT display greatly reduces eyestrain. The built in audio amplifier and speaker make it specially suitable for personal computers.

### EPROM PROGRAMMERS AND ERASER
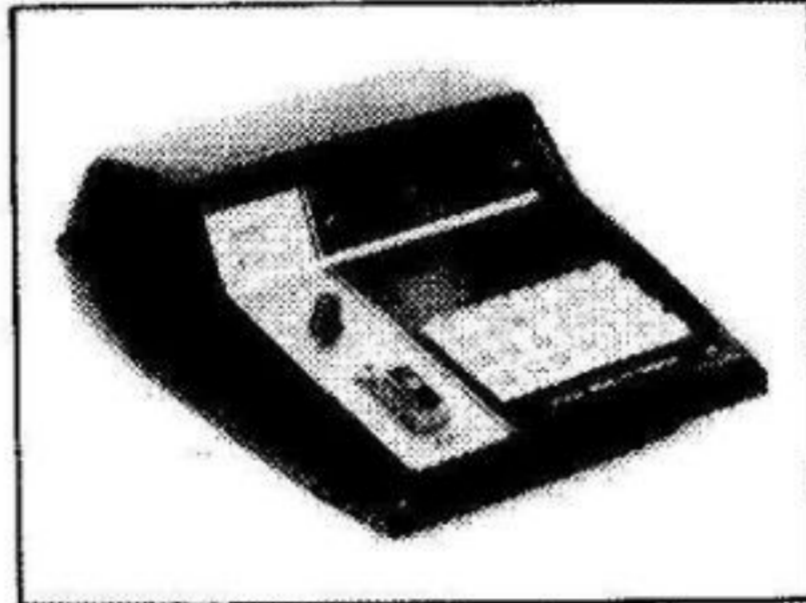
#### EP4000 EMULATING PROGRAMMER

- ★ COPY/PROGRAMME/EMULATE 2704/2708 2716/2508/2516/2532/2732 EPROMS
- ★ 4K x 8 STATIC RAM
- ★ VIDEO O/P AND 8 DIGIT LED DISPLAY
- ★ POWERFUL EDITING FACILITIES
- ★ COMPREHENSIVE I/O AS STD (RS232, TTL, 20mA PARALLEL, DMA)
- ★ £545.00 excluding carriage (£10.00) and V.A.T. (15%)
- ★ EX-STOCK\*




#### P4000 PRODUCTION PROGRAMMER

- ★ PROGRAMME UP TO 8 EPROMS SIMULTANEOUSLY
- ★ COVERS SAME EPROMS AS EP4000
- ★ INDEPENDANT BLANK CHECK/VERIFY PROGRAM MODES
- ★ SIMPLE TO USE
- ★ £545.00 excluding carriage (£10.00) and V.A.T. (15%)
- ★ EX-STOCK\*


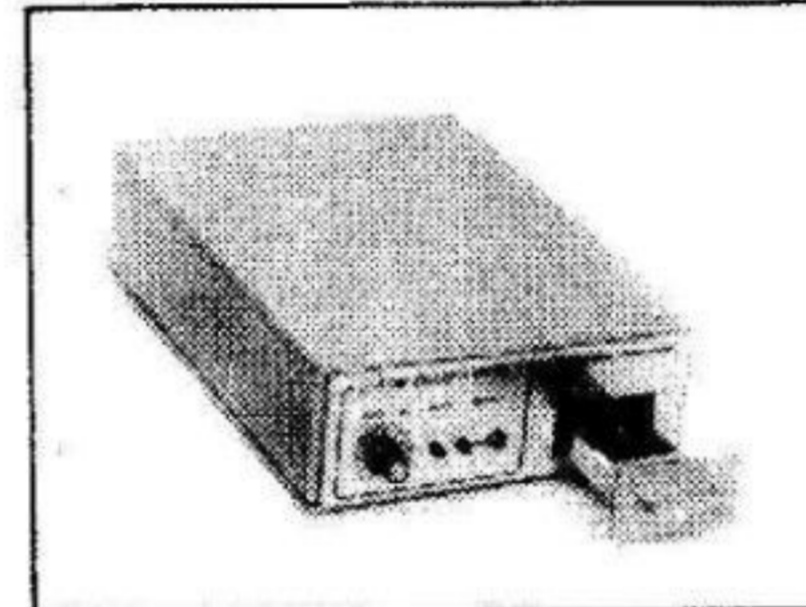
#### UV141 EPROM ERASER


- ★ 14 EPROM CAPACITY
- ★ SAFETY INTERLOCKED
- ★ ELECTRONIC TIMER
- ★ £78.00 excluding Carriage (£5.00) and V.A.T. (15%)
- ★ EX-STOCK\*


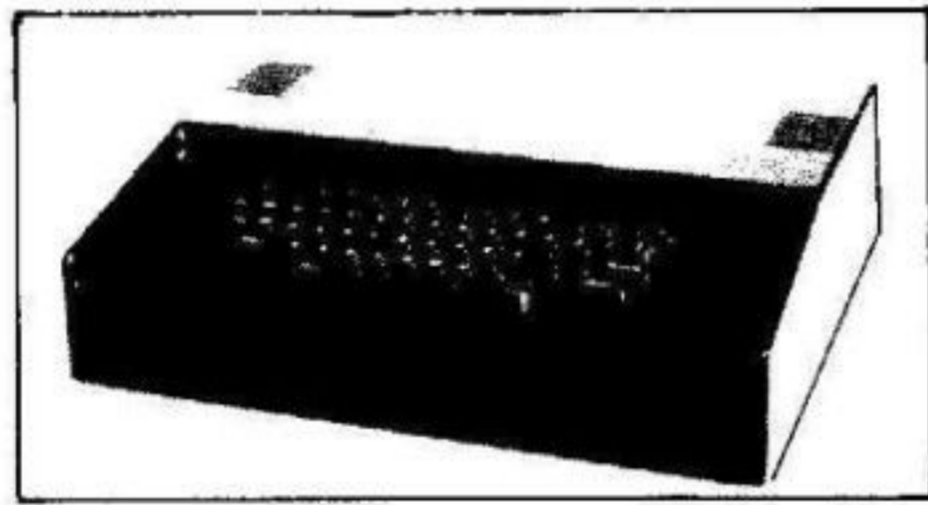
### KEYBOARD AND ENCLOSURE

**CASE** Attractively styled personal computer enclosure constructed of structured foam top and steel base (similar to the top selling Apple). Finished in charcoal and black.  
£49.95 excluding carriage (£10.00) and V.A.T. (15%)

**KEYBOARD** High quality electromechanical ASCII Encoded keyboard which can be fitted in above case or used separately. Full upper and lower case provided.  
£49.95 excluding carriage (£2.00) and V.A.T. (15%).



**TRANSFORMER** Mains transformer suitable for +5V at 2.5A and ±12V at 1A. Mounts on special lugs inside enclosure.  
£10.95 excluding carriage (£1.00) & V.A.T. (15%)

**HEATSINK** Heatsink for T03 Regulators which mounts inside rear of enclose.  
£2.50 excluding V.A.T. (15%)

**SPECIAL PRICE FOR CASE, KEYBOARD, TRANSFORMER & HEATSINK IF PURCHASED TOGETHER:**  
£99.95 excluding carriage (£15.00) & V.A.T. (15%)

Device	Price	Device	Price	Device	Price	Device	Price	Device	Price						
<b>MEMORIES</b>															
2114L-200ns	1+0.93	LM555CN	0.16	<b>CMOS 4000 'B' SERIES</b>						74LS190	0.48				
25+0.99		LM556CN	0.48	4553	2.90	74LS191	0.48	74LS192	0.48						
2114L-300ns GTE (FOR ACORN ATOM)	1.55	LM725CN	3.20	4555	0.39	74LS193	0.48	74LS194	0.39						
2708 450ns	1+2.25	LM741CN	0.14	4556	0.44	74LS195	0.39	74LS196	0.58						
25+1.99		LM747CN	0.70	4585	0.82	<b>74LS SERIES</b>									
2716 450ns (single +5V)	1+2.49	LM748CN	0.34	4000	0.11	74LS00	0.10	74LS01	0.11						
2716 350ns	25+2.25	<b>REGULATORS</b>								74LS02	0.12				
2532 450ns	1+4.50	7805	0.39	4001	0.11	74LS03	0.12	74LS04	0.12						
25+4.25		7812	0.39	4002	0.13	74LS05	0.13	74LS08	0.12						
2732 450ns	1+3.99	7815	0.39	4006	0.80	74LS09	0.12	74LS10	0.12						
25+3.80		78L05	0.29	4007	0.15	74LS11	0.12	74LS12	0.12						
2732 350ns	7.50	78L12	0.29	4008	0.55	74LS13	0.22	74LS14	0.39						
4116 200ns	1+0.74	78L15	0.29	4009	0.28	74LS15	0.12	74LS16	0.12						
25+0.70		7905	0.55	4010	0.35	74LS17	0.12	74LS18	0.12						
100+0.67		7912	0.55	4011	0.12	74LS19	0.12	74LS20	0.12						
4116 150ns	1+0.93	7915	0.55	4012	0.15	74LS21	0.12	74LS22	0.12						
25+0.89		<b>Z80 FAMILY</b>								74LS23	0.15				
4118 200ns	1+3.90	79L05	0.59	Z80 CPU	3.49	74LS24	0.12	74LS25	0.12						
25+3.45		79L12	0.59	Z80A CPU	3.99	74LS26	0.15	74LS27	0.12						
4118 150ns	6.00	79L15	0.59	Z80A CPU	3.99	74LS28	0.15	74LS29	0.15						
5516 200ns	12.50	LM309K	0.99	Z80A CPU	3.99	74LS30	0.12	74LS31	0.12						
6116 200ns	7.95	LM317K	3.20	Z80A CPU	3.99	74LS32	0.12	74LS33	0.18						
6116LP 200ns	10.00	LM323K	4.95	Z80A CPU	3.99	74LS34	0.15	74LS35	0.15						
6116LP 150ns	10.85	LM338K	4.75	Z80A CPU	3.99	74LS36	0.15	74LS37	0.15						
<b>CRT CONTROLLERS</b>															
EF6845P	9.50	<b>DATA CONVERTERS</b>								74LS38	0.15				
EF9364P	5.94	ZN425E-8	3.45	<b>NEW CATALOGUE NOW AVAILABLE</b>						74LS39	0.15				
EF9365P	82.90	ZN426E-8	3.00	Gives details of our full product range including price breaks and a voucher value £1. Please send SAE.						74LS40	0.15				
EF9366P	82.90	ZN427E-8	5.99	<b>SPECIAL OFFERS</b>						74LS41	0.15				
EF9365/6 DATA AND APPLICATIONS	2.00	ZN428E-8	4.75	1+	25+	100+	<b>DIL SOCKETS</b>								
<b>BUFFERS</b>															
81LS95	0.90	ZN429E-8	2.10	2114 Low Power 200 ns						0.84	0.79	0.74			
81LS96	0.90	ZN432CJ-10	28.09	6116 Low Power 200 ns						7.60	7.20	6.75			
81LS97	0.90	ZN433CJ-10	2.59	6116 Standard 200 ns						5.70	5.35	5.05			
81LS98	0.90	ZN440	56.63	<b>NEW FLOPPY DISC CONTROLLERS</b>						<b>LOW PROFILE - TIN</b>					
8T26A	0.99	ZN432E-10	14.75	FD1771	17.12	Z80A SIO-2	11.99	4050	0.26	74LS75	0.24	8 pin	0.07		
8T28A	1.40	ZN447	9.14	FD1791	32.61	MK 3886	11.00	4051	0.59	74LS76	0.20	14 pin	0.09		
8T95	1.35	ZN448	8.85	FD1793	32.61	MK 3886-4	14.47	4052	0.68	74LS78	0.19	16 pin	0.09		
8T97A	1.35	ZN449	3.20	FD1795	35.33	<b>6800 FAMILY</b>								18 pin	0.13
8T98	1.45	<b>MISCELLANEOUS SUPPORT CHIPS</b>										20 pin	0.14		
										22 pin	0.17				
										24 pin	0.19				
										28 pin	0.25				
										40 pin	0.29				
										<b>NEW LOW PROFILE - GOLD</b>		8 pin	0.22		
										14 pin	0.29				
										16 pin	0.31				
										18 pin	0.33				
										20 pin	0.35				
										22 pin	0.40				
										24 pin	0.42				
										28 pin	0.54				
										40 pin	0.81				
										<b>NEW ZERO - INSERTION FORCE DIL</b>		24 pin	6.30		
										28 pin	7.40				
										40 pin	8.80				
										<b>CRYSTALS</b>		1 MHz	2.90		
										1008 MHz	2.90				
										1.8432 MHz	2.20				
										3.6864 MHz	2.95				
										4 MHz	1.65				
										6 MHz	1.90				
										8 MHz	1.95				
										14 MHz	3.45				
										<b>NEW UNF MODULATORS</b>		6 MHz	2.75		
										8 MHz	4.40				
										<b>DATABOOKS</b>		THOMSON-EFCIS 6800 Data Book (inc p&p) 5.95			
												Data Converter Handbook (inc p&p) 1.58			
												<b>DATASHEETS</b>			
												Photocopied Data Sheets available for most product at 6p per page ex. p&p and V.A.T. Please telephone for details			

OFFICIAL ORDERS WELCOME

VISA

24 HOUR TELEPHONE SERVICE FOR CREDIT CARD USERS



QUANTITY DISCOUNTS AVAILABLE

PLEASE SEND S.A.E. (20P) FOR OUR NEW 1982 CATALOGUE. FREE REPLIED PAID ENVELOPE WITH EVERY ORDER. ALL PRICES EXCLUDE P & P ON ORDERS UNDER £10 (50p) AND V.A.T. (15%). ALL ORDERS DESPATCHED ON DAY OF RECEIPT WITH FULL REFUND FOR OUT OF STOCK ITEMS IF REQUESTED.

# MIDWICH COMPUTER COMPANY LIMITED

DEPT ET1, HEWITT HOUSE, NORTHGATE STREET, BURY ST. EDMUNDS, SUFFOLK IP33 1HQ  
TELEPHONE: (0284) 701321 TELEX: 817670

# electronics today international BOOK SERVICE

How to order: indicate the books required by ticking the boxes and send this page, together with your payment, to: ETI Book Service, Argus Specialist Publications Ltd, 145 Charing Cross Road, London WC2 0EE. Make cheques payable to ETI Book Service. Payment in sterling only please. All prices include P & P. Prices may be subject to change without notice.

## BEGINNERS

- Beginners Guide to Electronics** Squires £4.50
- Beginners Guide to Transistors** Reddihough £4.50
- Beginners Guide to Integrated Circuits** Sinclair £4.50
- Beginners Guide to Radio** King £4.50
- Beginners Guide to Audio** Sinclair £4.50
- Introducing Amateur Electronics** Sinclair £4.50
- Introducing Microprocessors** £5.20
- Understanding Electronic Circuits** Sinclair £5.30
- Understanding Electronic Components** Sinclair £5.30

## APPLICATIONS COOKBOOKS

- TV Typewriters Cookbook** £9.35
  - CMOS Cookbook** £9.85
  - Active Filter Cookbook** £11.30
  - IC Timer Cookbook** £8.65
  - IC Op-Amp Cookbook** £12.20
  - ITL Cookbook** £9.15
  - MC 6809 Cookbook** Carl D. Warren £5.30
  - PLL Synthesiser Cookbook** Kinley £5.85
  - 8085A Cookbook** Titus £10.75
- 
- How To Build Electronic Kits** Chapel £3.45
  - 110 Electronic Alarm Projects** Marston £5.25
  - 110 Semiconductor Projects for the Home Constructor** Marston £5.25
  - 110 Integrated Circuit Projects for the Home Constructor** Marston £5.25
  - 110 Thyristor Projects Using SCRs** Marston £5.25
  - 110 Waveform Generator Projects** Marston £5.25
  - 99 Practical Electronic Projects** Friedman £4.20

## COMPUTING & MICROPROCESSORS

- What is a Microprocessor?** 2 cassette tapes plus a 72-page book £10.00
- Beginners Guide to Computers and Microprocessors** with projects £6.05
- Basic Computer Games** Ahl £6.05
- Basic for Home Computers** Albrecht £6.60
- Illustrating Basic** Alcock £4.25
- Troubleshooting Microprocessors and Digital Logic** Goodman £6.10
- Z-80 Microcomputer Handbook** £9.35
- Microprocessors in Instruments and Control** Bibbero £15.30
- Basic Basic** Coan £9.95
- Advanced Basic** Coan £9.95
- 1001 Things to do with your Personal Computer** Sawusch £6.00
- Microcomputers, Microprocessors, Hardware, Software and Applications** Hilburn £17.40
- Microprocessor Systems Design** Klingman £21.95
- Introduction to Microprocessors** Leventhal £11.25
- Microprocessor Technology, Architecture and Applications** £11.30
- Basic with Style** Nagin £6.30
- Microcomputer Design** Ogdin £9.25
- Hands on Basic with a PET** Peckham £11.95
- 8800 Software Gourmet Guide and Cookbook** Scelbi £9.30
- 8080 Software Gourmet Guide and Cookbook** £9.30
- The 8080A Bugbook** Rony £10.05
- 8080/8085 Software Design** Titus £10.05
- How to Design, Build and Program your own Working Computer System** £7.10
- Your Own Computer** Waite £2.25
- Microcomputer Interfacing Handbook A/D & D/A** £6.35
- Crash Course in Microcomputers** Frenzel £14.95
- Musical Applications of Microprocessors** Chamberlain £20.95
- The Pascal Handbook** Tiberghien £12.45
- 50 Basic Exercises** Lamoitier £11.10
- Learning Basic with the Sinclair ZX80** £4.95
- Microprocessors for Hobbyists** Coles £4.25
- Introduction to Microcomputer Programming** Sanderson £5.25

- Microprocessors and Microcomputers for Engineering Students and Technicians** Woolland £5.95
- Using CP/M - Self Teaching Guide** Ashley Fernandez £6.95
- Digital Counter Handbook** Frenzel £8.65
- 33 Challenging Computer Games for TRS80-Apple-Pet** Chance £5.75
- How to Build Your Own Working Robot Pet** Dalesta £5.75
- Microprocessor and Digital Computer Technology** £16.00
- Guidebook to Small Computers** Barden £4.20
- How to Debug Your Personal Computer** Huffman £6.30
- How to Troubleshoot and Repair Microcomputers** Leuk £6.30
- 6809 Microcomputer Programmes and Interfacing with Experiments** Staugaard £11.45
- Wordprocessors Programmed. Training Guide with Practical Application** £
- Digital Circuits and Microcomputers** Johnson £9.75
- Experiments in Artificial Intelligence for Small Computers** £7.25

## TEST

- The Oscilloscope In Use** Sinclair NEW EDITION 1982
- How to Get More Out of Low-cost Electronic Test Equipment** Tobery £5.50

## THEORY

- Digital Signal Processing. Theory and Applications** Rabiner £26.40
- Electronic Communication Systems** Kennedy £8.95
- Principles of Communication Systems** Taub £8.40
- Introduction to Digital Filtering** Bognor £13.30
- Transistor Circuit Design** Texas Instruments £10.95
- Electronic Circuit Design Handbook** Design of active filters, with experiments: Berlin £6.80

## REFERENCE

- Electronic Engineers Reference Book** Turner £42.00
- Electronic Components** Colwell £4.00
- Electronic Diagrams** Colwell £4.00
- International Transistor Selector** Towers New £10.70
- International FET Selector** Towers £4.60
- International Op-Amp Linear IC Selector** Towers £8.00
- International Microprocessor Selector** Towers £16.00
- Dictionary of Audio - Radio and Video** Roberts £16.00
- Dictionary of Electronics** Amos £16.00
- Dictionary of Electrical Engineering** Amos £16.00
- Dictionary of Telecommunications** Amos £16.00
- Giant Book of Electronic Circuits** Collins £12.75
- World Radio/TV Handbook Vol. 35 1981** £10.50
- How to Build Electronic Projects** Malcolm £6.45
- Modern Electronic Circuit Reference Manual** Marcus £33.50

Please send me the books indicated. I enclose cheque/postal order for £.....

I wish to pay by Access/Barclaycard. Please debit my account.

5	2	2	4																	
4	9	2	8																	

Signed .....

Name .....


Address .....

.....

.....

# CALCULATORS

## CASIO

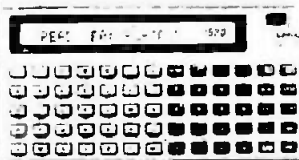

**FX702P** PROGRAM IN BASIC LANGUAGE 1800 STEPS/228 MEMORIES (MAX) 55 FUNCTIONS  
**£115.95**




**CA901** CALCULATOR, ALARM, INVADER GAME WATCH, 12/24 HOUR DISPLAY, 1/100 STOPWATCH, CHOICE OF ALARM TONE, STAINLESS STEEL CASE £27.95  
BLACK RESIN CASE £18.95



**W250** WATER RESISTANT TO 10 ATMOSPHERES, STOPWATCH, ALARM, DAY, DATE ETC. STAINLESS STEEL CASE AND STRAP £18.95  
BLACK RESIN CASE AND STRAP £16.95  
**AX210**


**AX210** Simultaneous analogue and digital display. Analogue display: Hours and minutes hands. Digital display: Hours, minutes, seconds, am/pm, year, month, date, day. Auto-calendar pre-programmed until 2023. Monthly calendar display, 12 or 24 hour time display. Daily alarm with 3 selectable melodies. Hourly time signal, Dual Time, Countdown alarm, 1/100 second stopwatch with lap and split timing. Accuracy: ± 15 sec/month. Battery life approx 18 months. Chrome plated case, stainless steel bracelet. Battery type: 1xBR2016 (Lithium battery), Module No 118

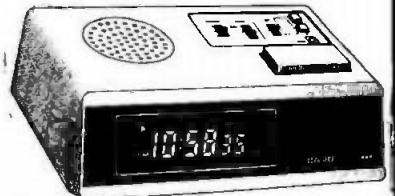


**CASIO MA1** Melody alarm clock with snooze  
**ONLY £11.95**



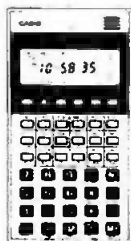**FX300P** 38 STEPS, 2 PROGRAMS, 61 FUNCTIONS, LITHIUM BATTERY



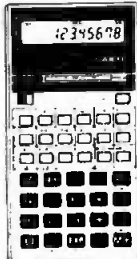**FX8160** 8+2 DIGIT 46 FUNCTIONS WITH CLOCK TIMER, ALARM AND 1/100 STOPWATCH ETC



**FX650** 10 DIGIT 50 FUNCTIONS STANDARD DEVIATION ETC


Take a Challenge? Try a Casio Game!



**BG 15**  
**£18.95**

**MG 880**  
**£11.95**


**MG 885**  
**£11.95**

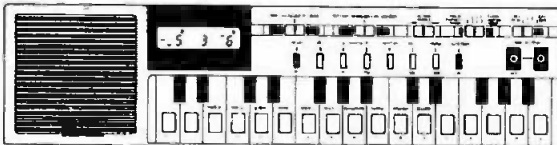

**CASIO VL1** MULTI VOICE ELECTRONIC MUSICAL INSTRUMENT & CALCULATOR. BUILT-IN RHYTHM BOX, AS SEEN ON TV.

**ONLY £31.95**

## TEXAS ELECTRONIC LEARNING AIDS

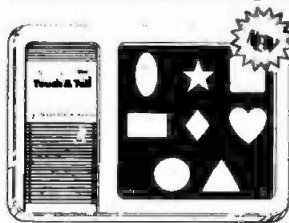


**TOUCH & TELL £31.95**

These two items are more than toys, the electronically synthesized voice guides and teaches at the child's own pace. Extra modules available for Touch & Tell - Animal Friends, Number Fun, All About Me, for Speak & Spell - Super Stumpers, Vowel Power, Mighty Verbs, Homonym Heroes, Magnificent Modifiers  
**ALL AT £11.95**



**SPEAK & SPELL £34.95**

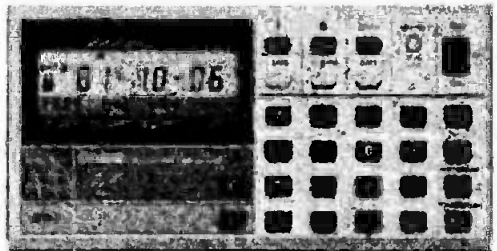

**CASIO FT7** FORTUNE TELLING CLOCK CALCULATOR WITH ALARM & CALENDAR  
**£16.95**


**512 (max.) Program Steps**  
**88 (max.) Memories,**  
**Alpha-numeric Clarity**

- 10 digit mantissa + 2 digit exponent
- Alphabetic dot matrix display (85 characters: upper/lower case letters of the alphabet, numbers, symbols and special characters).
- High utility variation of program steps and data memories with power back-up.

512 steps  
22 memories

32 steps  
88 memories

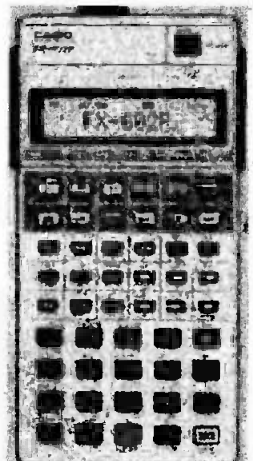- Program area divided into 10.
- Subroutines nestable up to 9 levels.
- True algebraic logic.
- 50 built in functions.
- Auto power off function.
- Connectable with the FP 10 optional mini printer.
- Connectable with the FA-2 optional adaptor for storing programs/data.
- 860 hours on two lithium batteries (CR2032).
- 9.6H x 7.1W x 14.2mmD, 100g (3.8"H x 2.34"W x 5-1/2"D, 3.5oz).



**FX-602P**



**EL5101**

**EL S100 24 DIGIT** £5.95  
**EL S101 16 DIGIT** £41.95  
**EL103** £25.95  
**PC 1211 POCKET COMPUTER** £91.95  
**CE 122 PRINTER/INTERFACE** £71.95

## SHARP

**HP41C/41CV**



## TEXAS INSTRUMENTS

**TI 51-111 32 KEY STROKES** £29.95  
**TI 57 150 KEY STROKES** £26.95  
**TI 58 & TI58C 480 STEPS/60 MEMORIES (MAX) 172 FUNCTIONS** £57.95  
**58C CONSTANT MEMORY** £68.95  
**TI 59 MAG CARD 960 STEPS/100 MEMORIES (MAX)** £121.95  
**PC 100C PRINTER FOR 58/59** £144.95  
**58/59 SOFTWARE, MATHS/UTILITIES, APPLIED STATS, ELECTRICAL ENGINEERING, BUSINESS DECISIONS, LEISURE, SURVEYING ALL AT** £35.95

## NEW FOR 1982 HEWLETT PACKARD

**HP32E WITH 15 REGISTERS** £37.95  
**HP34C 210 LINE PROGRAM** £102.95  
**HP38C PROGRAMMABLE FINANCIAL** £102.95  
**HP33C PROGRAMMABLE** £31.95  
**HP37E FINANCIAL** £51.95  
**HP67 MAG CARD** £247.95  
**HP41C COMPREHENSIVE SYSTEM, LCD DISPLAY, 318 REGISTERS, 2240 PROGRAM LINES, 10 PROGRAM LABELS, 84 USER DEFINABLE KEY FUNCTIONS, 58 FLAGS, 8 SUB ROUTINES, ACCESSORIES INCLUDE PRINTER, BAR CODE LIGHT PEN, MAGNETIC CARD READER, MEMORY MODULES, PROGRAM MODULES.**  
**HP41C** £184.95  
**HP41CV 5 TIMES MEMORY** £213.95

# C.S.S.

All prices include VAT, Post, and Packing. All goods new and fully guaranteed. Large S.A.E. with enquiries please  
**PO BOX 13 REDDITCH, WORCS B98 8NS Telephone (0527) 43169**



# WIN A CRIMSON ELEKTRIK CK1010/CK1100 100 W AMPLIFIER WORTH £230!



Below are 16 amplifier parameters. Choose the ten you think contribute most to a good quality sound and place them in order of importance. For example if you think that Flat Frequency Response is the most important factor determining good amplifier sound, place 'E' in the first box.

Fill in your name and address on the coupon and *list your ten letters (in order) on the outside back of the envelope*. Closing date is April 30th 1982, and you *must* use the coupon provided on page 133. Multiple entries are acceptable, but each must be on a separate coupon.

### RULES

1. Closing date is April 30th 1982, and all entries post-marked later than this date will be discounted.
2. The coupon provided in the magazine must be used. Photocopies are NOT acceptable.
3. Employees of ASP and their relatives are not eligible for entry.
4. The judges' decision is to be considered final and no correspondence will be entered into concerning the competition.

- |    |                                       |
|----|---------------------------------------|
| A. | Wide Bandwidth                        |
| B. | Precise RIAA Equalisation             |
| C. | Separate PSU for Each Channel         |
| D. | High Power Output                     |
| E. | Flat Frequency Response               |
| F. | Low Harmonic Distortion               |
| G. | Low Crosstalk                         |
| H. | Stability of output under any loading |
| J. | Ability to drive low impedance        |
| K. | Adequate heatsinking                  |
| L. | Conservatively-rated output stage     |
| M. | Provision of tone controls            |
| N. | DC Coupling                           |
| P. | Short Circuit Protection              |
| R. | Low Feedback                          |
| S. | Flat open-loop response.              |

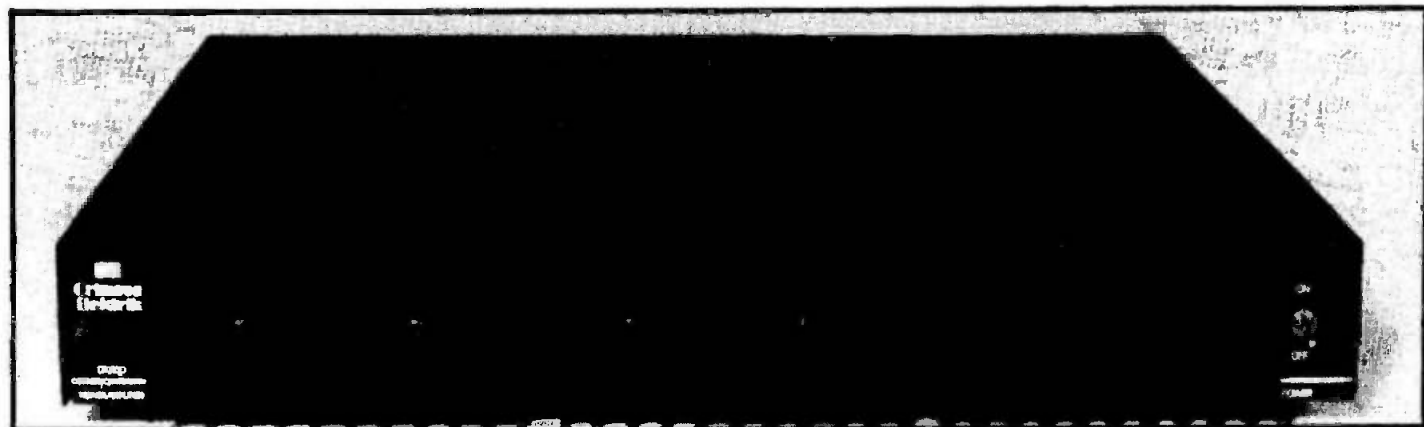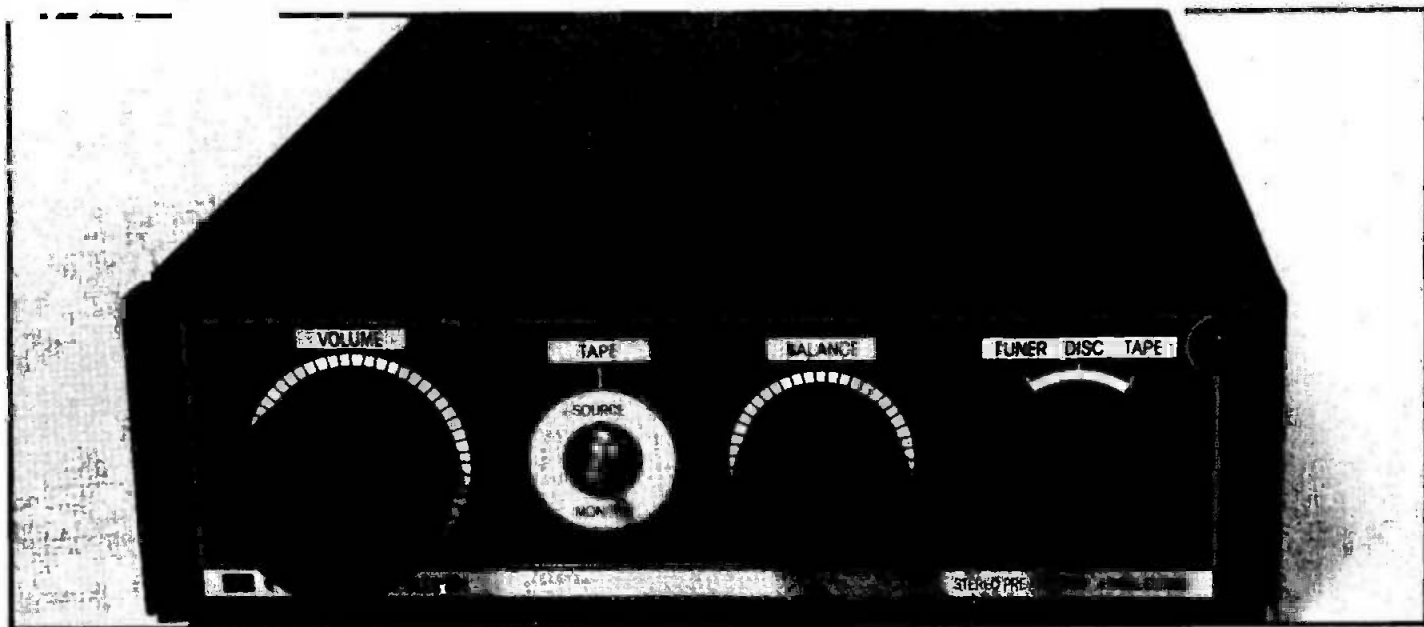

## OEM USERS

New amplifier boards to meet new needs

### New Signals

With digital audio now a reality and third generation noise reduction techniques with us already, the dynamic range of programme material is about to shoot up by a phenomenal 30dB. If the amp you work with at the moment can just cope, it's going to be in serious trouble when faced with the new signals. The clipping that will result will sound nasty and probably kill tweeters with its high frequency energy content.

J.W.R. have already solved the problem for you with their new high power PFAs. Designed to meet the exacting requirements of heavy duty P.A. and the even more exacting requirements of audiophile use, the ultra wide dynamic range modules can handle the most demanding of source signals.

### The PFA/HV

This four powerfet module is designed to run from supply rails up to  $\pm 100V$ . Rated at **300W continuous RMS** into 4 and 8 ohms and **250W** into 16 ohms, the module can sustain, for musically significant periods of time, **RMS powers of 500W** into 8 ohms and **900W** into 4 ohms. It also has the ability to drive 70V line distribution systems directly, obviating the need for expensive and quality compromising transformers.

This amp is designed particularly with music in mind. We anticipate usage often at only 50W to 100W average levels leaving 10dB of headroom.

### PFA 500

This module uses 8 H-PAK powerfets and is designed to produce a continuous RMS output current of **25 amps** and will run from a supply of up to  $\pm 70$  volts. The Unit will drive **250W** continuous RMS into 8 ohms, **450W** into 4 ohms, **600W** into 2 ohms and **700W** into 1 ohm.

Numerous features are included in the board to optimise efficiency. The H-Paks (thermally more efficient than TO3) are presented at ninety degrees to the P.C.B. so they can bolt directly onto the heatsink, instead of via the usual angle bracket. The resultant chip to heatsink thermal resistance is very low keeping junction temperatures down and efficiencies up. The Powerfet supply rails are kept separate from the rest of the amp. This enables the driver stage to be run from slightly higher rails resulting in larger undistorted output swings at little extra cost.

In addition a bridge mode input pin is available on board permitting instant bridge mode between any two boards without the need for separate inverting amps. Powers comfortably in excess of **1KW** can be delivered into 4 ohms in this configuration.

N.B. The new boards exhibit the same exemplary noise and distortion performance of the PFA80/120.

### OPTIONS

We are particularly sensitive to a manufacturers individual requirements, and all our boards come with many options (including higher slew rates, response tailoring etc.). The chances are we've got what you're looking for, and if not, we can probably do it for you by next week!

#### INTERESTED?

Phone Phil Rimmer on 01 800 6667 with your application requirement.


## THE POWERFET SPECIALISTS J. W. RIMMER

Mail order only to:  
Dept ETI/11, 148 Quarry Street, Liverpool L25 6HQ.

Telephone: 051-428 2651

Technical enquiries:  
367 Green Lanes, London N4 1DY. Tel: 01-800 6667

# THE POWERFET AMPLIFIER

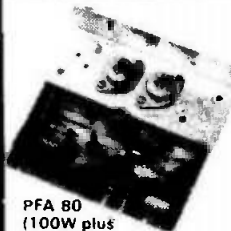


PFA 80  
(100W plus  
into 8!!)
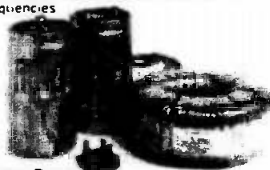
#### Powerfets

So far 29 semiconductor manufacturers have invested in this new technology. Clearly powerfets are something special.

Their enormous power gains eliminate conventional drive circuitry in power amps, permitting delightfully simple designs. Their freedom from secondary breakdown and their tendency to shutdown when thermally overstressed result in inherently stable and destruction proof output stages, not needing protection circuitry. And perhaps best of all, their lack of charge storage makes them fast and responsive, producing amplifiers of wide bandwidth and low distortion even at high frequencies.



Power Supply  
Components available

PFA 120  
(150W plus  
into 8!!  
300W INTO 4!!)

#### Elegant Simplicity

Advances in high technology should make life simpler. A cluttered power amplifier board may well perform superbly but its busy elaboration is an indication that its design is pushing the limit of its component technology.

There are now many first class bipolar power amp modules on the market. All of them are complex and consequently expensive. Any additional improvements in the areas where they are weak (e.g. H.F. distortion) can only be obtained with yet further complexity and cost.

Only a new technology can provide the sort of 'quantum jump' in component performance necessary to reduce the clutter on the board, reduce the cost and make the highest fi once more affordable.

The PFA is perhaps the perfect realisation of the classic powerfet amp design. The superb PCB allows the use of either one or two pairs of output devices, providing easy expandability for those starting with the smaller system. (The extra output pair of the PFA120 results in lower distortion and improved efficiency, particularly into low impedance loads).

The components used in the PFA have been chosen with extreme care. The lowest noise input devices and lowest distortion gain stage devices were selected regardless of cost. 140V powerfets were chosen against the more usual 120V to give improved safety margins.

Specification	PFA80	PFA120
Bandwidth	10Hz	100kHz 1dB
Output Power RMS into 8!!	80W $V_a = \pm 50V$	120W $V_a = \pm 55V$
THD (20Hz - 20kHz)	$\leq 0.008\%$	$\leq 0.005\%$
(kHz at rated output)	0.004 %/v	0.002 %/v
SNR		120dB
Slew Rate		>70V $\mu$ S
Gain		X22
Rin		30K
Vs max		$\pm 70V$
Cost (Built)	£17.46	£24.66 (P. & P. 75p)
(Kit)	£14.86	£21.86

#### Power Amp PAN 1397

A high quality 20W power amp board based on the HA1397. Easily modified for bridge operation providing high powers from low supply voltages.

#### Specification

Output power RMS	20W into 8!! at $\pm 22V$	
	20W into 4!! at $\pm 19V$	
THD	0.02% at 1kHz 1W to 12W	
SNR	90dB	
Input	100mV into 50K	
Cost (Built)	£9.80	(P. & P. 40p)

PSU  
101



PSU 101 Power Supply Board for 1 or 2 PAN 1397s. Provides  $\pm 22V$  at 3A AND  $\pm 27V$  with 2 second run-up for anti-thump circuit on PAN 1397. (Built) £3.86, P/P 75p

Mains transformer for above 17 0 17@ 50VA £3.95 (P. & P. £1)

#### Pre-amp PAN 20

The design is unique. Equalisation is applied after a flat gain stage, resulting in one of the best noise performances available. Superb overload figures are ensured by a front end incorporating a special gain attenuator control (volume control to you!). The inputs are uncommitted and can be used with any combination of signal sources in the 1mV to 10V range. RIAA equalisation is provided for mag PUs and space on the board is available for different equalisations.

Specification	
BW	20Hz-30kHz $\pm 1dB$
THD	0.003% typ.
at rated input	
SNR	85 dB (ref. 5mV RIAA)
	106 dB (ref. 100mV flat)
Vs	$\pm 20V$
Output	1V (clips at $\pm 20dB$ )
Cost (Built board less controls)	£8.78 2 needed for stereo (P. & P. 40p)

## THE POWERFET SPECIALISTS J. W. RIMMER


Mail order only to:  
Dept ETI/11, 148 Quarry Street, Liverpool L25 6HQ.

Telephone: 051-428 2651

Technical enquiries:  
367 Green Lanes, London N4 1DY. Tel: 01-800 6667

KIT  
REVIEW

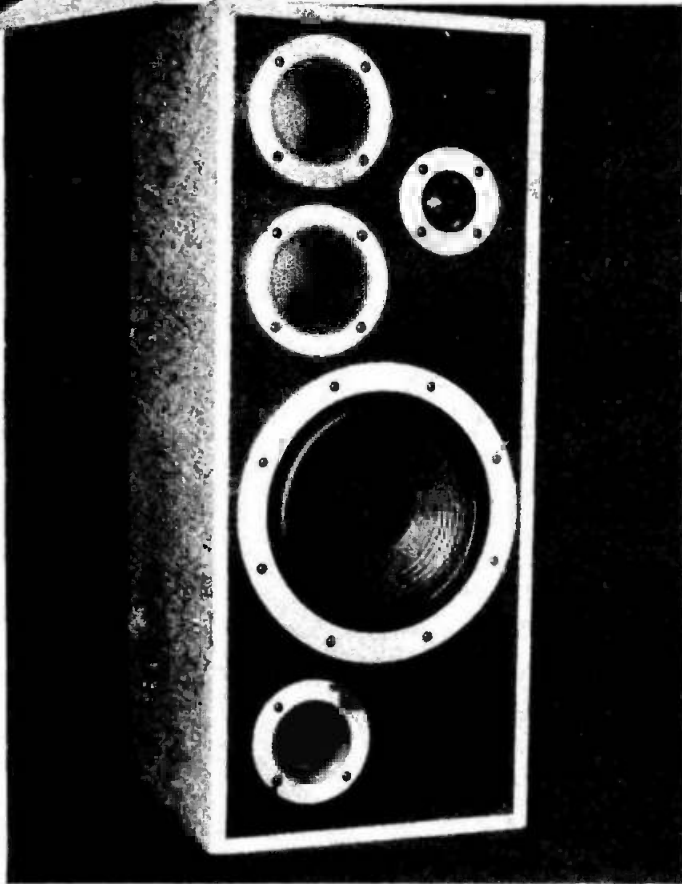**Fancy a pair of Wharfedale E70s? Can't afford them? Then why not build 'em yourself? Peter Freebrey underwent the mystic rites of woodworking and saved himself over £100.**



**F**or many years now there have been speaker manufacturers who have marketed kits for the 'do-it-yourself' audio enthusiast. At the present time there are several well known and respected firms supplying high quality kits. One such firm is Rank Hi Fi whom manufacture the Wharfedale range. Their approach to this market is the Wharfedale Speakercraft series of drive units and crossovers, together with the constructional information necessary to duplicate their ready-built units using these same components. If the demand is there someone will supply that demand... such is the case with Wilmslow Audio who sell kits of the cabinets to suit the Wharfedale units. This review follows the construction of the E70 system using the WE70 flat-pack cabinet kit.

Why build loudspeaker kits? Well, one obvious answer is to save money; often the cost of a kit is very much less than buying the completed unit. If you are reasonably competent at woodwork, it is perfectly feasible to start from scratch with just a large sheet of flooring grade  $\frac{3}{4}$ " chipboard. An electric power saw makes the job much easier and can also give a better edge to the cut. It is often the edges which concern people as they are going to be visible somewhere around the loudspeaker cabinet and it is easy to think that to get rid of the ugly sight of these will be difficult. This is not necessarily true; there are several ways in which unsightly edges may be hidden from view. The simplest answer is not only to buy a kit of speakers, crossovers, and so on, but perhaps to buy a ready-cut cabinet kit as well — this does not rid you of dealing with edges, but at least they are all cleanly cut!


I had heard that Wilmslow kits were of a very high standard — several people having commented upon the ease with which they went together. That sort of build-up sometimes takes a bit of living up to and I waited for the delivery of the WE70 kit with some uncertainty. When they arrived my initial reaction was favourable; all cuts were clean and the method of construction looked simple and sensible. The sides, top and base are rebated by about  $\frac{1}{8}$ ". This not only gives you a better mechanical joint, but also makes it almost impossible to get any voids or gaps — which is good, acoustically speaking. It also means that with the minimum of care the cabinet will slot together into its correct shape with no unsquare corners or leaning sides. Included with the kit were two cardboard transmission tubes for the mid-range units, acoustic damping material, grille material (both black plastic foam for the reflex port and cloth for the front), nylon grille plugs and sockets, 3 mm wander plugs and sockets for loudspeaker lead connections, and the screws to fix the speaker units themselves. Last but not least there are written instructions on how to assemble the kit.

## 16 Steps To Heaven

Step one in the instructions is to examine the panels for transit damage. Presumably if any damage is noticed, Wilmslow Audio should be contacted as soon as possible. Step two is to remove all dust, etc from the panels. Any excess of wood dust from the sawing operation can only do harm so vacuum all surfaces. If there were any build-up of sawdust at the surfaces to be glued that sawdust could conceivably impair any glue joints and also cause the fit of the joints to be out of true.

Step three is to assemble the cabinet without gluing to check the fit. It is also suggested that panels be swapped around to find the optimum results. This step proved to be most encouraging... I assembled one unit (panels only) and held it together with just one turn of linen tape (no string please — it can bite into the corners of the chipboard and cause you extra work later). The cabinet felt as firm as a rock. No glue, just well-fitting joints. Thus encouraged I rapidly got on to step four, which was to paint the face of the baffle board matt black. I gave it a couple of coats of sanding sealer — not so much to get a 'de luxe' finish but to seal the wood surface. Chipboard is pretty thirsty stuff and you can use up a lot of paint if you do not seal the surface first. Just be careful not to get any of the sealer or paint on the edges, as this may affect the glue joint you have to make later.

Step five is to glue the midrange enclosures (transmission tubes) to the baffle boards, using plenty of glue to ensure an airtight seal. The baffle boards are recessed to take the cardboard tubes so it is easy to line up for position. I used Evostik Resin W, which is a PVA wood-working adhesive for all glue joints. It is easy to apply and may be cleaned off the hands/clothes as it is water soluble. Just don't put your speakers out in the rain! Light pressure to a PVA glued joint gives a better joint so I placed one of the side panels across the top of the four tubes to ensure a light even pressure. Rather than apply liberal amounts of glue in one dose I used sufficient so that a *small* bead of glue was squeezed out all around the tube. This was smoothed around with a handy finger and when dry a further fillet of glue was applied all round the tube/baffle joint. Four pieces of approximately 1" thick polyurethane foam are supplied which must be

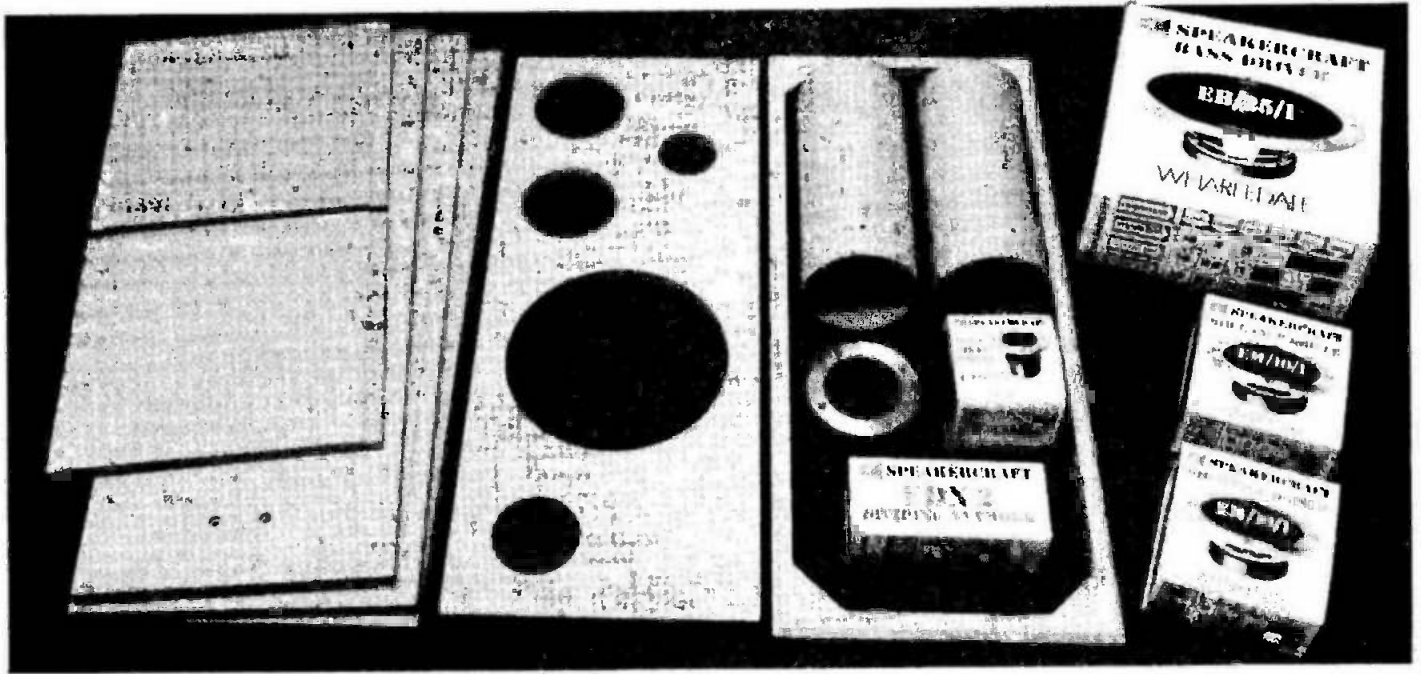

glued to the rear (outside) end of the baffle tubes. Wharfedale recommend a hard rubber pad at this position but as this 1" foam is to be compressed to about 3/16" it probably is just as good.

Step six is probably the most critical point in the whole construction procedure, for at this point the cabinet panels are glued together. This entails gluing five of the six panels; the sixth (the side furthest from the mid-range enclosures) is placed in its position while the glue is setting but is not glued. This enables you to work inside the cabinet; fitting the crossover, acoustic wadding etc.

Wharfedale suggest that the acoustic wadding be attached to the inside of the panels before you reach this step. Wilmslow Audio suggest that the wadding be fixed *after* the panels have been glued. Although I only learnt of Wharfedales' suggestion after I had completed step six, I favour the Wilmslow approach for several reasons.

If the wadding is stuck/tacked or stapled to the panels before they are fitted together two things may happen: 1) some of the wadding may inadvertently get caught between the panels and cause either an air gap or 2) force the cabinet to go together 'out of true'. Also, with the wadding in place you cannot inspect the inside corners to check that there is a continuous fillet of glue all along the joint.

If you choose the Wilmslow way you will have to cut the wadding to fit around the mid-range enclosures but in practice this proved to be a very simple task.

## Getting A Grip

Holding the whole thing together while the glue sets is quite a teaser. I was fortunate to have a set of excellent clamps known as Jet System Clamps made by TMT Design Ltd of Leamington Spa. They cost about £10 per clamp but are worth their weight in gold for this type of job. The problem comes from the 1" thick foam stuck to the rear of the mid-range enclosures; this tends to force the back panel out of position. Wilmslow suggest either that clamps be used or that the joints be held *firmly* together with masking tape. It is possible with masking tape but only just; remember that unlike your trial fitting in step three, the foam pads are being compressed to about 3/16" and all but one panel has glue all along the edges and is quite capable of sliding all over the place! I bought a wide webbing strap from a camping shop to assist the initial stages of holding the four vertical panels approximately in place while I set up the clamps. The cost of the strap was wasted as I could not get enough tension in it to over-

come the spring in the foam... a linen tape would have done just as well! If you are going to use masking tape then get someone to help apply the pressure to hold the front and back panels in position while you apply the tape. Lastly, cut up a thin polythene bag and place four pieces inside each corner of the panel that is not to be glued; it would be a shame if this stuck firmly to the rest of the panels by accident!

It is useful to have a rubber-faced hammer at this stage as, having clamped or taped the cabinet firmly together, you may wish to tap the panels firmly but lightly into position. A hammer and a block of wood do the trick just as well, but try not to mark or dent any edges. The places to look for out of true joints are the corners... remember once the glue has set there is nothing you can do, so a few light taps now can save the day. Wipe off excess glue with a damp cloth. Wipe from the centre of each panel *out* towards the edge; try not to get any glue smeared over the panels.

Having completed step six the rest of the construction is plain sailing. Step seven is simply to remove the loose side when the glue has set (leave for at least 24 hours). I then put a small fillet of glue all around the inside of all joints **BUT** not up to the edges where the last panel is to fit... we want it to go back from whence it came!

Step eight is to place the drive units and reflex port trims in the baffle board and mark accurately where pilot holes for the fixing screws are to be drilled. Although the chipboard is high density it has a fairly soft texture so it is well worth buying a new 1/8" drill bit. This ensures the pilot holes are clean and in the right place... worn bits tend to wander! Although I'm sure it is unnecessary I drilled all my pilot holes just deep enough for the screws by slipping a small rubber sleeve over the drill bit at the right depth. No-one could accuse me of having any extra holes or air gaps here!

Step nine is to position the grille frame on the front of the cabinet with the cabinet lying on its back. Use masking tape to hold it in position and carefully drill a pilot hole through the grille and into the baffle board. I used a 1/16" drill bit and drilled four holes, one in each corner section of the grille frame. These holes can now be drilled out to the correct size to accept the nylon plugs and sockets that hold the grille in place. Wilmslow supply eight plugs/sockets for each grille but as Wharfedale suggested that four would be sufficient I chose the latter. It is far easier to line up four holes than eight! For the socket in the baffle board I used a 7/16" bit and for the grille a 7/32" bit. Don't forget to drill only from the rear of the grille and only to a depth of 1/4-5/16". The 1/16" pilot hole may be filled with wood filler

but when the grille material is fitted I doubt that these holes can be seen. If you are happy with the finish on the baffle board then glue the sockets in now; if not, then wait until you have quite finished before fixing them in position. Do not stick the plugs in the grille until you have fixed the material in place. I used a quickset epoxy glue for these fittings.


Step 10 is to glue the black, acoustically transparent foam over the inside of the reflex port aperture. You can use either PVA glue or quickset epoxy, just be careful not to get any of the adhesive on the foam where it is over the port.

Step 11 is to position the crossover network inside the cabinet on the rear panel opposite the bass unit aperture. Before you screw it into position check that the leads from the drive units can reach their appropriate tags! Wharfedale recommend that the crossover has a piece of felt or foam between it and the panel to prevent any vibration rattles. Also in step 11 is the fitting of the input terminals through the rear panel. I smeared the threads on these sockets with some latex glue, again to ensure that there would be no air gaps. Solder the leads from the crossover to these terminals. . . . make sure they are connected correctly, red to red and black to black!

Step 12 is to cut three 5" discs of wadding and place these in the mid-range tubes. The Wharfedale instructions that come with every Speakercraft unit specify that the packing density of this wadding should increase towards the back of the tube and that the tube should be completely filled with wadding. In view of this I cut two extra discs and fluffed out those towards the front of the tube.
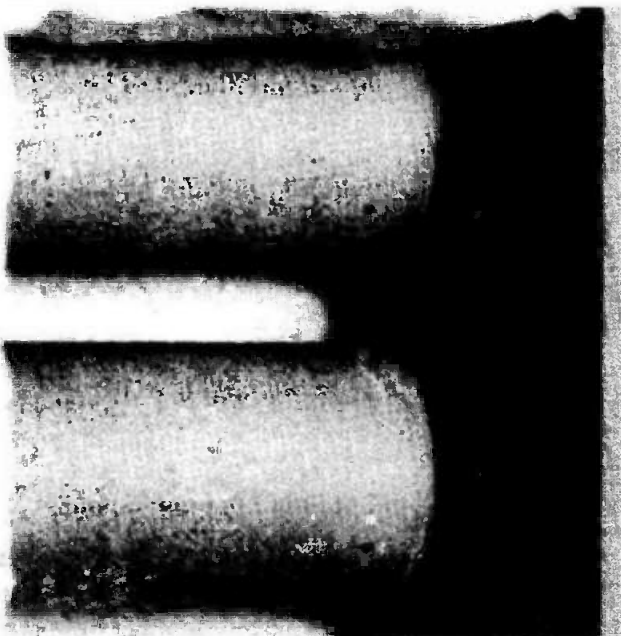
## It's In The Bag

Step 13 is to line the inside of the cabinet with the acoustic wadding and glue the remaining side into place. Now comes the tricky bit — how do you slide the wadding up behind the mid-range tubes? The wadding catches on the side panel and snags up behind the tubes! Easy — get a large polythene bag 12" or more wide and about 15" to 18" long, slide the wadding into the bag, slide the bag plus the wadding up behind the tubes and, lightly holding the wadding in place, pull out the bag. Cutting the wadding to fit round the tubes sounds fiddly but turned out to be quite easy. Cut the holes for the tubes smaller rather than larger as the wadding will easily stretch to fit comfortably in place. No wadding is required on the baffle board but don't forget to put wadding on the loose side panel before you glue it into place! The wadding may be tacked or stapled into place.



The wadding is tacked or stapled in place.

Step 14 is to attach the wires to the drive units — *observing the correct polarity* (if in doubt refer to the Speakercraft instructions and double-check every connection), and screw all units and ports to the cabinet. Wire up and fit the bass unit last as the bass aperture gives you ample room to work inside the cabinet connecting wires to the crossover. The wires from the mid-range units come through small holes in the tubes and these holes should be sealed after you have connected the wires to the crossover. The fitting of the drive units should only be started after the glue joints of the final side have thoroughly set and any glue fumes have completely cleared. The comment regarding fumes is highly pertinent if you are not using a water-based adhesive. There is a possibility that the fumes could affect certain plastics used in the construction of the drive units.

Step 15: You have two working loudspeaker systems, so connect them to your amplifier and sit back and enjoy your favourite record.

Step 16: The cabinets are now ready for their final cosmetic treatment. There are a number of options open to you: they may be:

- veneered either by you or a local cabinet-maker.
- covered in iron-on veneer or plastic laminate.
- sealed and then painted (preferably sprayed) in colour of your choice.
- Wilmslow Audio also suggest the use of a 'Contact' type covering as these can be obtained in very realistic wood-grain finishes.

Whichever method you opt for you will probably have to attend to the cabinet edges/joints before you can proceed. Due to the small but noticeable tolerances in the cutting of the panels, the amount of glue and the pressure used during the construction, there are likely to be a few panels that are slightly proud of the edges that butt up to them. There are several ways to solve these problems but the simplest is to use one of the proprietary wood fillers. Which choice depends upon your choice of finish.

If the cabinets are to be covered in plastic laminate you can afford to use one of the more easily worked fillers such as Fine Surface Polyfilla, Alabastine or Plaster of Paris. If, on the other hand, you are going to cover them with 'Contact' or simply spray-paint them then I would suggest a tougher type of filler that is less likely to crack or crumble. My choice here would be one of the car body fillers — they are easier to sand than some of the loaded general-purpose fillers from the DIY shop. So you are less likely to sand away the wood from the cabinet instead of the filler!

The grille material must be stretched over the grille frames and either tacked/stapled or glued (or both) to the inside of the frame. The material supplied by Wilmslow Audio stretched easily and evenly; I smeared PVA glue over the rear faces of the frames (having first painted them black) and stapled the material in place while the glue set. When set I trimmed off the excess material (having removed the 50-odd staples) and ran another bead of the adhesive over the edge of the material.

Looking back on the construction of this E70 loudspeaker system using the WE70 flat-packs, I can only say that I am very satisfied with the way they went together. There were one or two instructions that could have been a little clearer but they have been covered in this article. Common sense would probably have solved any uncertainties but I chose to phone Rank Hi Fi to confirm my conclusions. The people I spoke to did not know that I was writing this review and so it is a pleasure to say they could not have been more helpful. This entire project has been enjoyable from first to last.

## BUYLINES

Wilmslow Audio sell the complete WE70 package (flat pack, drivers and all components for two speakers) for £220 plus £8 carriage. Wilmslow Audio, 35/39 Church Street, Wilmslow, Cheshire SK9 1AS.

# AUDIO ELECTRONICS

ALL PRICES INCLUDE VAT

RETAIL-MAIL ORDER-EXPORT INDUSTRIAL-EDUCATIONAL

LONDON'S TEST EQUIPMENT CENTRES

CALL IN AND SEE FOR YOURSELF OPEN SIX DAYS A WEEK ALL MODELS ON DISPLAY



**CROTECH 3035 10 MHz Scope Plus Component Tester**

5" - 130mm Flat Face Tube DC - 10 MHz  
5mV/DIV 220/240V AC Trig. to 20 MHz

SAVE £21 PLUS

As advertised by us at £189.75 inc. VAT  
**NOW £168.50** inc. VAT  
(UK c/p £3.50) Exclusive to Audio Electronics

**PROFESSIONAL 100 K OHM/VOLT MULTIMETER**

30 ranges 15A AC/DC 1.5 KV, 200 meg ohms. Features mirror scale, polarity reverse, electronic overload protection, taut band suspension.

As advertised by us at £67.50 + case i.e. £84.00

SAVE £35

**NOW £49** Inc. VAT  
(UK c/p £1.50) with leather case Exclusive to Audio Electronics



**LCD LOW COST MULTIMETERS**

00001 3 1/2 digit LCD 26 range push button 2A AC/DC 20 meg ohm £36.50  
000011A/100m 3 1/2 digit LCD 15 range push button plus Mle Tester 10A DC (No AC) £43.50  
100m 3 1/2 digit LCD 30 range Rotary switch plus Mle Tester 10A AC/DC £69.95

Caters will always find a range of low cost test equipment accessories, tools, irons and boards in stock, also special offers for certain equipment which will vary from time to time

Price correct at time of preparation E&OE All prices include VAT

CHOOSE FROM UK'S LARGEST RANGE

**STOP PRESS** Few only 6110 23 range 10A AC/DC range hold, continuity buzzer plus much more. Rotary switch £59.95



**SABTRONICS EQUIPMENT NEW LOW PRICES!!**

New reliable range of DMM's and frequency computers with those extra facilities and competitive prices. All battery operated (supplied). Except 5020A mains. Optional mains eliminators available

**8 DIGIT COUNTERS** 0.1 HZ to 10 HZ Res. 10mV sensitivity to 100 MHz (UK c/p £1.00)

8110A 20 HZ-100 MHz in 2 ranges £77.00  
8610A 20 HZ-600 MHz in 3 ranges £94.00

**9 DIGIT COUNTERS** 30mV sensitivity to 1GHz. Resolution 0.1 HZ-10 HZ  
8610B 10 HZ-600 MHz in 3 ranges £113.85  
8000B 10 HZ-1GHz in 3 ranges £178.00

**FUNCTION GENERATOR** (UK c/p £1.00) with mains adaptor

5020A 1 HZ-200 KHZ Sine/Square/Triangle/TTC Freq. sweep. Low distortion £90.00

**DIGITAL MULTIMETERS** Two LCD hand held - one with temperature range. Also LCD and LED Bench models. 0.1% basic accuracy.

2035A 3 1/2 digit LCD hand 2A AC/DC 20Meg ohm ETC £71.00  
2037A As 2035A with -50°C to +150°C Temp. range 0.1°C resolution £77.00  
2010A 3 1/2 Digit LED. Auto decimal & minus. 10A AC/DC. 20Meg ohm etc. £81.50  
2015A LCD version of above £95.00

THP20 Touch and Hold Optional probe for DMM's £14.95

C/P 2935/37A 65p  
All others £1.00



**HAMEG OSCILLOSCOPES**

Range of top quality scopes for Amateur and Professional (UK c/p 307-£3.00, other £4.00)

307 Single trace 10 MHz, 5mV; 0.5 micro sec. Plus built in component tester 6 x 7cm display £158.70 (Optional carry case £18.40)

203 Dual 20 MHz. Trig to 30 MHz 5mV; 0.5 micro sec. 8 x 10cm display (replace model 312) £253.00

412-5 Dual 20 MHz delayed sweep; trig to 40 MHz; 5mV 0.1 micro sec. 8 x 10cm display £402.50

705 Dual 70MHz Delayed sweep; Single sweep; Delay line; Trig to 70MHz; 2mV; 0.1 micro sec. 8 x 10cm display £387.00

Options 203/412/705 Viewing hood £6.90  
Component tester 203, 412, 1206 £46.00  
Carry case (State model) £21.85


Optional Probes (All models) X1 £7.95; X10 £9.45  
X1 - X10 £10.50; X100 £16.95  
HZ65 Add on component tester - Any Scope £29.95



**RF AND AUDIO SIGNAL GENERATORS** Mains operated (UK c/p £1.00) Audio 20 HZ-200 KHZ 4 band. Sine/Square o/p

TE220 Distortion max 1% £69.95  
LA626 Distortion 0.5-1% leader £73.70  
LAG120A 5 range 10 HZ-1 MHz Size/sq. 0.05-0.8% DIS £146.00  
LA6125 Low distortion version of LAG120A 0.02% £273.00  
AG202A Distortion 0.5-1% Trio 78.20  
AG203 10HZ-1 MHz 5 band max distortion 0.1% Trio £126.50

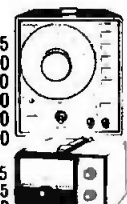
RF All feature Int/Ext. MDD. Variable output £59.95  
TE200 100 KHZ-100 MHz 6 band (300 MHz harmonics) £83.25  
LS616 100 KHZ-100 MHz 6 band (300 MHz harmonics) Leader £68.00  
SG602 100 KHZ-30 MHz 6 band professional trio



**VARIABLE AND FIXED POWER SUPPLIES** (UK c/p £1.00 any model).

**SPECIAL PURCHASE**  
1206 13.8v 6 to 8 amp £13.95

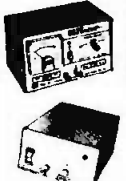\*PP241 0/12-12-24V 0/1 amp £35.00  
\*PP243 0/12-12/24V 0/3 amp £59.95  
\*RP154 5-15V 0/3 amp £49.95  
\*meter display



**THURLBY DIGITAL MODEL 1503 MULTIMETER**

4 1/2 Digit, 0.05% 7 Function LCD  
30 ranges: 1200V DC, 750V AC, 10A AC/DC, 32 Meg ohm. Also includes frequency measurement to 4MHz and 4kHz output. Made to exacting standards in the U.K.

Price is with batteries, test leads and mains adaptor.  
(optional carry case £20.45)

**£171.00**  
UK c/p £1.00



**AMATEUR/CB TESTING** - Full lists send SAE

KOM6 1.5 to 250 MHz 6 range DIP meter £47.95  
HM20 20K/VOLT multirange multimeter. Plus SWR/Power meter 150 MHz £28.95  
RC1000 0/10/100/1000 watts SWR etc. 150 MHz max £52.50  
MJ668A 10 ch. Pocket 2 metre scanner £69.00  
MJ668M Marine band version £69.00

UN74 SWR 0/10w Power. 0/50/144/430 MHz tester. £21.00  
FC100M 12V 100 MHz Freq Counter £69.95

**SPECIAL CB ACCESSORY PURCHASES** (Post 55p)

CB20 SWR/Power twin meter to 30 MHz 1kw £11.95  
175 SWR/Field strength/aerial matcher single m £11.95  
171 Twin meter SWR/Field strength 0/10/100w Power 144 MHz £11.95  
1206 13.8v 6 to 8 amp regulated power supply (post £1.00) £13.95

Just a selection of a huge range in stock - send for latest lists including professional ranges.



**PROFESSIONAL MULTIMETERS**

(UK c/p £1.50)  
All featuring AC/DC Volts/Current & Ohms ranges.


M1500 43 range 20K/Volt; AC/DC 10A 20 Meg ohm; 5kV AC/DC £57.50  
M1200 30 range 100K/Volt; AC/DC 15A 200 Meg ohm; £49.00

K1400 26 range large scale 20K/Volt; 10A AC/DC 20 Meg ohm; 5kV AC/DC £96.00  
K200 39 range 10 Meg ohm input. 25 HZ-1 MHz £105.00  
OPTIONS Cases: M 1500 & 1200 £16.50; K1400 £19.00  
Temperature Probe for: K1400 £18.00



**DIRECT READ HV PROBE** (UK c/p 65p)

0/40KV. 20K Volt £18.40




**SAFGAN PORTABLE OSCILLOSCOPES**

Range of low cost Dual Trace Scopes mains operated. Made in UK to exacting standards. Available as 10 MHz, 15 MHz or 20 MHz. All feature 5mV sensitivity, 0.5 micro sec. 6.4 x 8cm display (UK c/p £2.50)

DT410 Dual 10 MHz £184.35  
DT415 Dual 15 MHz £201.25  
DT420 Dual 20 MHz £216.20

OPTIONAL SCOPE PROBES - SEE HAMEG ABOVE


**MADE IN UK**

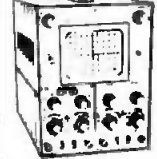

**LOGIC PROBES/MONITORS/PULSERS circuit powered** (UK c/p 60p)

LP1 DTL/TTL/CMOS. 10 MHz Pulse; Memory £35.50  
LP2 DTL/TTL/CMOS. 1.5 MHz; Pulse £19.95  
LP3 DTL/TTL/CMOS. 50 MHz; Pulse; Memory £55.95  
LM1 Logic monitor for 8 to 16 pin ICs £33.00  
DP1 Digital pulser. Single or 100pps. £58.50  
LOP076 50 MHz; 10Meg ohm; Logic Probe. with case £56.90

ALL PRICES INCLUDE VAT

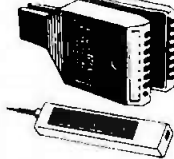

**AUDIO ELECTRONICS** CUBGATE LIMITED

301 EDGWARE ROAD, LONDON, W2 1BN, ENGLAND. TEL 01-724 3564  
ALSO AT HENRY'S RADIO, 404/406 EDGWARE ROAD, LONDON W2

WE ARE OPEN 6 DAYS A WEEK - CALL IN AND SEE FOR YOURSELF!

Order by Post with CHEQUES/ACCESS/VISA or Telephone your order

Allow up to 10 days for delivery

**FREE CATALOGUE**

Send large SAE (20p UK) Schools, Companies, etc. free on request.






# AUTOMATIC CONTRAST METER



What's black and white and read all over? Answer — a photographic negative, providing you've built this simple and useful device. Design and development by Rory Holmes.

Contrast ratio is a very important quality of photographic negatives that must be assessed during the printing process, in order to select the correct grade of photographic paper. The contrast of negatives depends on the type of film used, the lighting conditions and the developing process; consequently five grades of printing paper are available to enable the full range of tones from black to white to be reproduced from any negative. Grade 1 is termed the softest and it is used with the highest contrast negatives. At the other end of the scale, grade 5 is the hardest paper, which will enhance the tonal variations of poor contrast negatives.

During the design stage of this project we experimented initially with two separate photodetectors which measured the instantaneous light difference between two points. There are a number of problems with this approach, as the photodiodes and their associated amplifiers must be carefully matched in light sensitivity.

Secondly, the lightest and darkest points of the image must be known exactly, and the two photodetectors need to be simultaneously positioned on these points while the reading is taken. This is an awkward business at the best of times, but especially so in a darkroom!

We considered that a different

approach was required and developed the circuit of Fig. 1 to overcome some of these difficulties. Only one photodetector is used and the peak positive and negative voltages obtained from different light levels are followed and stored independently by sample and hold circuits.

Now, as long as the photodiode is scanned at some time through the lightest and darkest points of the image, the peak detectors will memorize the maximum and minimum voltages, and thus provide a contrast measurement.

The photodetector input stage of our meter is rather unusual in its configuration. Photodiodes are usually

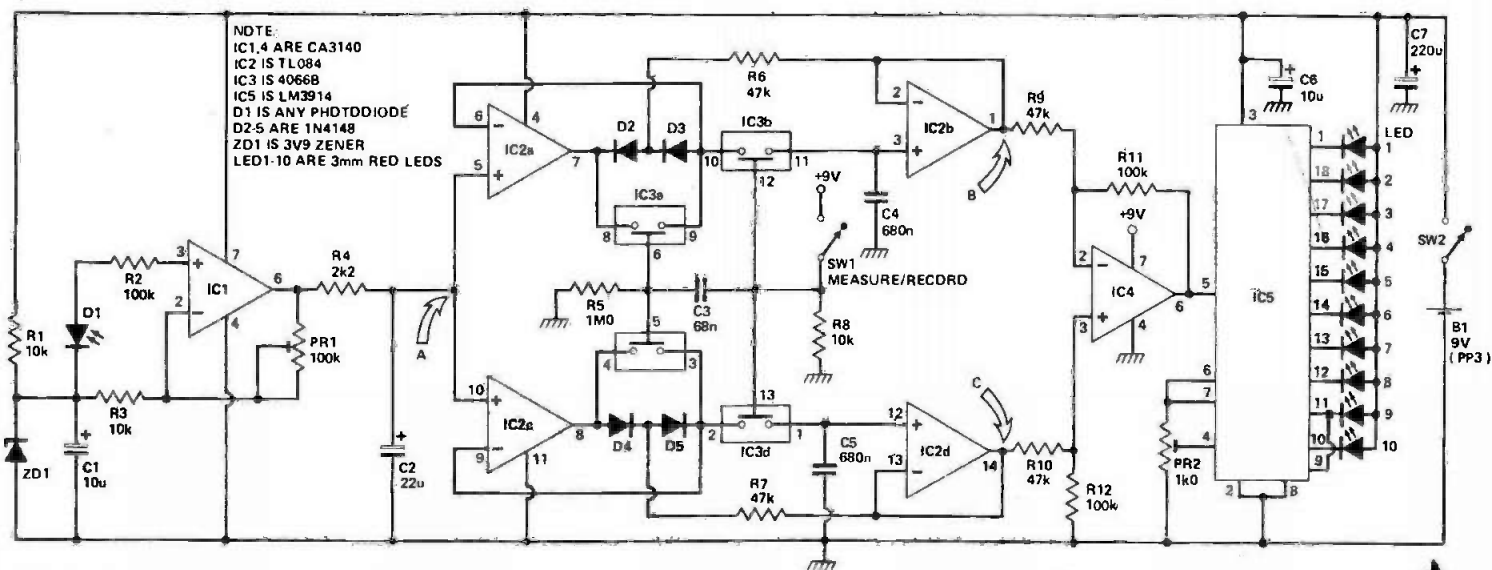


Fig. 1 Circuit diagram of the Contrast Meter.

used in the 'photovoltaic mode' where the photocurrent developed and measured is linearly proportional to the light intensity. Our input amplifier has an extremely high input impedance and thus measures the open circuit voltage generated by the photodiode. This voltage is logarithmically proportional to irradiance as the graph of Fig. 2 illustrates. This is a very convenient property since the sampling circuitry can now work on the log of the light level to provide maximum and minimum values. By simply subtracting these two values with a differential amplifier we obtain a voltage that is logarithmically proportional to the ratio of the maximum and minimum light levels, ie the contrast.

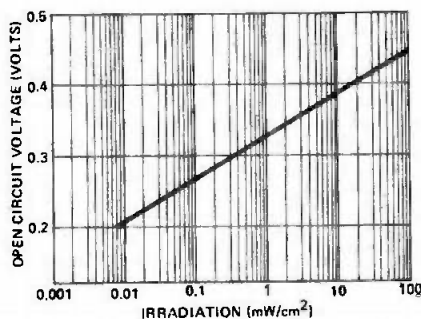


Fig. 2 Response of the photodiode used in this project.

## Meter Made

The ETI contrast meter was intended primarily to determine the paper grade for a well balanced print; consequently a 10 LED bargraph type meter is sufficiently accurate for calibrating the five grades of paper. At today's prices this also works out somewhat cheaper than a moving coil meter and is less prone to damage. After calibration, the meter will be found very easy to use. It is switched on with the 'sample/hold' switch in the 'hold' position and placed down flat on the enlarger base with the photodetector probe anywhere in the image area. (The photodiode has been mounted in a separate probe with its amplifier in order to keep it as close to the focused image plane as possible. If it were much higher than this the detecting element would pass through an unfocused image, giving a false contrast reading).

Any red safety lights should be switched off before the reading is taken to avoid error since the photodiode is responsive at this wavelength. The sample/hold switch should now be moved to the sample position; this will clear any previous reading and start measuring light variations. Now the photodiode may be moved across the image and through the areas that look the brightest and darkest. This can be

done quite slowly thanks to the peak detectors' long memory time; however, several areas should be scanned to ensure the recording of the true maximum and minimum. The eye can be deceived quite easily by those cunning optical illusions lurking among the shades of grey!

During the scanning process the reading on the LED scale will increase and finally level-off at the true contrast ratio when the black and white peaks have been covered. Before removing the meter from the image area the sample/hold switch should be set to 'hold'. The meter will now be immune to further light variations and will continue to display the contrast reading for a considerable time, thanks to the even longer memory of the sample/hold circuitry!

A true ratio is provided by the meter and thus the contrast reading for a given negative will be independent of the light source intensity and enlargement size (photographic aberrations known as "circles of confusion" may produce sources of error under certain conditions). Negatives may thus be compared or matched for contrast.

## Construction

The meter is built into a slim style plastic enclosure produced by OK Machine and Tool company. This houses the battery and main PCB on which all the parts are mounted. Since the light sensing element must be as close to the enlarger base plane as possible, we have mounted it externally on a separate small PCB with its associated amplifier. A probe to house the external sensor is made from a short length of aluminium channel extrusion. Figure 3 shows the

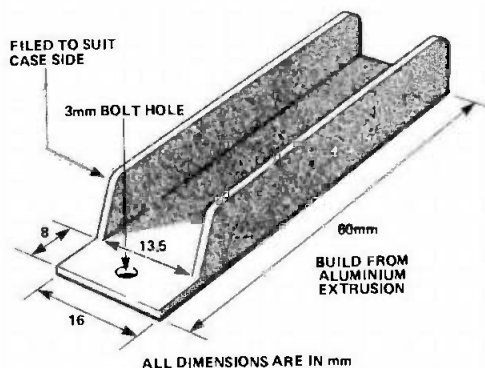


Fig. 3 Details for the aluminium extrusion that houses the photoprobe.

dimensions for the probe; if the aluminium channel proves difficult to obtain, a piece of the slotted aluminium extrusion used for commercial shelf-racking systems is ideal. This is available from most DIY

stores in short lengths with the required internal width. After filing or cutting to the right size, a piece of insulating tape should be stuck down on the inside to prevent shorting out the PCB. As shown in the diagram, a hole is drilled on the end for bolting it to the bottom of the case. This bolt should eventually be connected to circuit ground, thus providing screening for the photo-amplifier. The two PCBs for probe and main meter circuits are laid out as one board, and should be sawn apart along the lines shown on the foil patterns.

For other construction arrangements, the circuit can be left as a single board, since the interconnections are already made.

Three wires are used to connect the two boards together as indicated on the overlay; these should pass through a small hole drilled in the case side where the metal probe case is bolted on. When the probe board is mounted and stuck down in its channel, a piece of thin aluminium sheet is cut to form a lid with appropriate holes for the photodiode and preset. (The photodiode case is internally connected to the cathode, so it must not short against the lid).

## Calibration

Start with preset PR1 fully clockwise to set a gain of 1; also set PR2 fully anticlockwise, setting the voltage required to illuminate the lower end of the bargraph at zero. First, measure a high contrast negative that is known to require grade 1 paper for a good average contrast after developing. Initially a low contrast reading will be obtained, say about grade 4 or 5. Now, adjust PR1 anticlockwise to increase the gain of the photoamplifier. Take another measurement, when the contrast reading should be greater. Repeat this process until a grade 1 is consistently recorded.

Now select a negative with very poor contrast ratio, one known to require paper grade 5 for bringing out the contrast. Take measurements several times while adjusting only PR2 clockwise, until the bottom end of the scale illuminates at grade 5. The other contrast grades should now fall linearly between these points and can be checked for accuracy.

Although the bargraph display has a low resolution and accuracy, the rest of the metering circuit is obviously much better than this; consequently a moving coil meter could easily be added to measure the contrast voltage for those who may desire greater resolution.



# PROJECT : Contrast Meter

## HOW IT WORKS

The general circuit arrangement consists of a photo-amplifier which feeds a voltage derived from varying light levels in an enlarger, to a pair of peak detectors. One follows the peak positive voltage and the other the peak negative voltage. The capacitors used for storing the voltage peaks in the followers also form part of sample and hold circuits which are then switched to 'hold' after measurement. Their outputs represent the maximum and minimum values of light intensity. A differential amplifier then computes the ratio of these values and the result is displayed on an LED bargraph meter.

IC1, a CA3140 CMOS op-amp, is used as the photodetector amplifier. It is configured as a non-inverting DC amplifier with a gain variable from unity to about 10, set by PR1. Although IC1 can have input and output voltages all the way to ground, this facility is not used owing to the driving requirement of the TL084 quad op-amp. This requires inputs at least 1V above ground, and thus IC1's output is offset by a reference voltage of 3V9 provided by R1, ZD1 and C1. The anode of the photodiode is connected via R2 to the non-inverting terminal of IC1 which has an effectively infinite input impedance. Thus the open circuit voltage generated by the photodiode is amplified according to the gain set around IC1 and appears at the output on pin 6 added to the reference voltage.

The voltage at point A (ignoring the reference offset) will be logarithmically

proportional to the intensity of incident light, owing to the properties of the photodiode (see Fig. 2) R4 and C2 form a simple filter to remove 100 Hz ripple caused by AC mains bulbs. This voltage is fed directly to the peak detectors. These circuits are essentially the same, the difference being the polarity of the rectifier diodes. They operate in exactly the same way, and we shall deal only with the peak positive voltage follower.

Assume initially that the CMOS analogue switch IC3c is open and IC3d is closed. C5 will be connected to the output of op-amp IC2c via the rectifiers D4 and 5 (we can ignore the action of R7 for the moment). C5 will charge up via the rectifiers to the most positive voltage peak when the voltage at point A on the non-inverting terminal is greater than the capacitor voltage applied to the inverting terminal. The voltage held on C5 will drop over a period of time due to leakage current through the rectifiers D4 and 5 and the input bias current of IC2c. IC2c was chosen as a FET op-amp with a low input bias current and R7 is included to reduce the diode leakage current.

IC2d is connected to C5 as a straight forward high impedance voltage follower to buffer the stored voltage. When the input voltage to IC2c at point A drops below the peak value, IC2c's output will go negative, reverse biasing D4. However, IC2d applies the capacitor voltage via R7 to the anode of D5, effectively removing

leakage current through D5.

The peak positive value of the signal at A thus appears at point C, and likewise the peak negative value at point B. When the analogue switch IC3d is now opened, C5 is disconnected from the peak detector and acts in conjunction with IC2d as a sample and hold circuit thus isolating the measured values from further light variations.

When SW1 is open, R8 and R5 hold the control pins 13 and 5 of IC3 low, opening both analogue switches. This is the 'hold' mode. When SW1 is now closed, the control pin 13 is taken high, switching to the 'sample' mode. C3 and R5 produce a positive pulse (about 50 mS) on control pin 5 to briefly short out D4 and D5, so resetting the peak detector to the current voltage at point A. When C3 has charged the IC3c switch will open again, allowing the peak detector to function.

IC4 is wired as a differential amplifier with a gain of 2, to subtract the voltage at point C from point B. Since these voltages are the log of the light levels, the output on pin 6 will represent the contrast ratio of these light values.

IC5 is a standard LED bargraph driver, the LM3914. The input voltage on pin 5 is converted linearly to illuminate one LED on a scale of 10. Full scale deflection (LED 10) is set internally at 1V2; the zero scale deflection is set by PR2 anywhere between 0V and 1V2 during the calibration process. C6, a 10 uF tantalum, is required for IC5 to ensure stability from oscillation.

NOTE: k = CATHODE

0V +9V

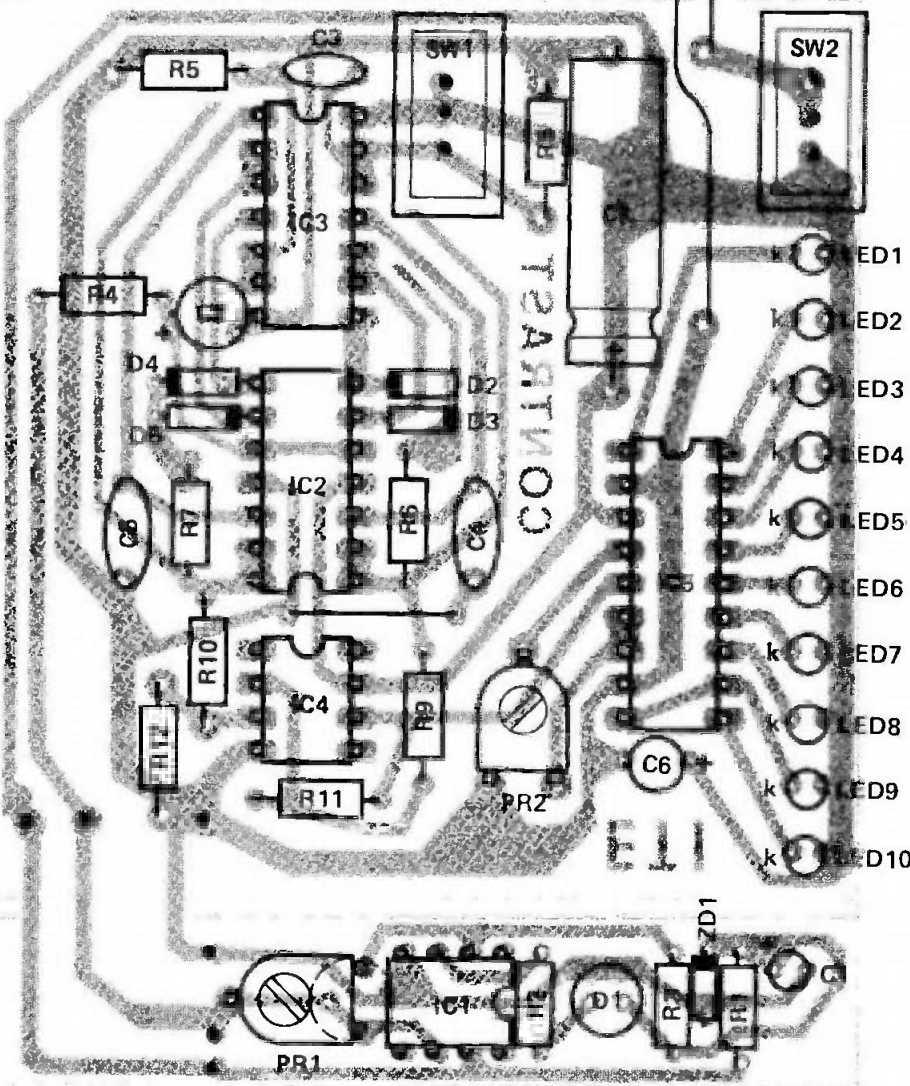


Fig. 4 (Left) Component overlay for the meter (showing the board uncut).

## PARTS LIST

Resistors (all 1/4 W, 5%)

R1, 3, 8	10k
R2, 11, 12	100k
R4	2k2
R5	1M0
R6, 7, 9, 10	47R

Presets

PR1	100k subminiature horizontal preset
PR2	1k0 miniature horizontal preset

Capacitors

C1	10u 35 V tantalum
C2	22u 25 V tantalum
C3	220u 16 V electrolytic
C4, 6	82n polycarbonate
C5	68 n ceramic

Semiconductors

IC 1, 4	CA3140
IC 2	TL084
IC 3	4066B
IC 5	LM3914
D1	BPX65
D2, 3, 4, 5	1N4148
LED1-10	3 mm red LED

Miscellaneous

SW1, 2	miniature slide switches
Case (see Buylines); PCB (see Buylines); B1	PP3 9 V battery (preferably alkaline type).

## BUYLINES

The photodiode specified in the Parts List is the one used in our prototype, but any general purpose type should do. The case we used is a Pactec type HP, size 146 x 91 x 28 mm. The PCB is available from us using the order form on page 44 — price is £2.12.

# BI-PAK BARGAINS




**5T21 SCREWDRIVER SET**  
6 precision screwdrivers in hinged plastic case. Sizes — 0.8, 1.4, 2, 2.4, 2.9 and 3.8mm. **£1.75**

**5T31 NUT DRIVER SET**  
5 precision nut drivers in hinged plastic case. With turning rod. Sizes: — 3, 3.5, 4, 4.5 and 5mm. **£1.75**

**5T41 TOOL SET**  
5 precision instruments in hinged plastic case. Crosspoint (Phillips) screw drivers: — H0 and H1 Hex key wrenches — 1.5, 2 and 2.5mm. **£1.75**

**5T51 WRENCH SET**  
5 precision wrenches in hinged plastic case. Sizes — 4, 4.5, 5, 5.5 and 6mm. **£1.75**

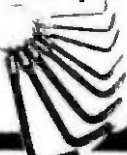BUY ALL FOUR SETS: 5T21-5T51 and get HEX KEY SET FREE  
HEX KEY SET ON RING  
Sizes: 1.5, 2, 2.5, 3, 4, 5, 5.5 and 6mm  
Made of hardened steel.  
HX/1 **£1.25**



## BI-PAK PCB ETCHANT AND DRILL KIT

Complete PCB Kit comprises  
1 Expo Mini Drill 10,000RPM 12v DC incl 3 collets & 1 x 1mm twist bit.  
1 Sheet PCB Transfers. 210mm x 150mm.  
1 Etch Resist Pen.  
1 1/2 pack FERRIC CHLORIDE crystals  
3 sheets copper clad board.  
2 sheets Fibreglass copper clad board.  
Full instructions for making your own PCB boards.  
Retail Value over **£15.00**  
OUR BI-PAK SPECIAL KIT PRICE **£9.75**  
ORDER NO. SX81



## BI-PAK SOLDER - DESOLDER KIT

Kit comprises ORDER NO. SX80  
1 High Quality 40 watt General Purpose Lightweight Soldering Iron 240v mains incl. 3/16" (4.7mm) bit.  
1 Quality Desoldering pump. High Suction with automatic ejection. Knurled, anti-corrosive casing and teflon nozzle.  
1.5 metres of De-soldering braid on plastic dispenser.  
2 yds (1.83m) Resin Cored Solder on Card.  
1 Heat Shunt tool tweezer Type.  
Total Retail Value over **£12.00**  
OUR SPECIAL KIT PRICE **£8.95**



## BRAND NEW LCD DISPLAY MULTITESTER.

RE 188m  
LCD 10 MEGOHM INPUT IMPEDANCE  
\*3 1/2 digit \*16 ranges plus hFE test facility for PNP and NPN transistors \*Auto zero, auto polarity \*Single handed, pushbutton operation \*Over range indication \*12.5mm (1/2-inch) large LCD readout \*Diode check \*Fused circuit protection \*Test leads, battery and instructions included.  
Max indication 1999 or — 1999  
Polarity indication Negative only  
Positive readings appear without + sign  
Input Impedance 10 Megohms  
Zero adjust Automatic  
Sampling time 250 milliseconds  
Temperature range — 5°C to 50°C  
Power Supply 1 x PP3 or equivalent 9V battery  
Consumption 20mW  
Size 155 x 88 x 31mm  
RANGES  
DC Voltage 0-200mV.  
0-2-20-200-1000V. Acc. 0.8%  
AC Voltage 0-200-1000V  
Acc. 1.2% DC Current 0-200uA.  
0-2-20-200mA 0-10A. Acc. 1.2%  
Resistance 0-2-20-200k ohms.  
0-2 Megohms. Acc. 1%  
BI-PAK VERY LOWEST POSS PRICE  
**£35.00** each



## SEMICONDUCTORS FROM AROUND THE WORLD

**100** A Collection of Transistors, Diodes, Rectifiers, Bridges, SCR's, Triacs, IC's both Logic and Linear plus Opto's all of which are current everyday usable devices. **100**

Guaranteed Value over £10 at Normal Retail Price

you're for only **£4.00** Data etc. in every pak. Order No. SX56



## EXPERIMENTER BOXES - ALUMINIUM - PLASTIC

**ALUMINIUM BOXES**  
Made with Bright Aluminium folded construction with deep lid and screws

SIZE * L	W	H	Order No	Price
5 1/4	2 1/4	1 1/2	159	<b>83p</b>
4	2 1/4	1 1/2	161	<b>83p</b>
4	2 1/2	2	163	<b>83p</b>
3	2	1	164	<b>57p</b>
8	6	3	166	<b>£1.68</b>
6	4	2	167	<b>£1.12</b>

All measurements for boxes are shown in inches. L = Length, W = Width, H = Height

## Plastic Boxes

Coloured. Black. Close fitting. Flanged Lid, fixing screws into brass bushes

SIZE * L	W	H	Order No.	Price
4	2	1	141	<b>£1.00</b>
4 1/2	2 1/2	1 1/2	143	<b>£1.30</b>
6	3 1/2	2	144	<b>£1.50</b>
Plastic as above but with aluminium top panel				
4	2 1/4	1	146	<b>£1.40</b>
Plastic sloping front				
5 1/2	4 1/4	2 1/2		
slope to				
		1 1/2	148	<b>£2.14</b>

## The Third and Fourth Hand...

... you always need but have never got until now  
This helpful unit with Rod mounted horizontally on Heavy Base. Crocodile clips attached to rod ends. Six ball & socket joints give infinite variation and positions through 360° also available attached to Rod a 2 1/2" diam magnifier giving 2 1/2 x magnification. Helping hand unit available with or without magnifier. Our Price with magnifier as illustrated ORDER NO. 1402 **£5.50**  
Without magnifier ORDER NO. 1400 **£4.75**



## "IRRESISTABLE RESISTOR BARGAINS"

Pak No.	Qty	Description	Price
SX10	400	Mixed "All Type" Resistors	£1
SX11	400	Pre-formed 1/2-watt Carbon Resistors	£1
SX12	200	1/4-watt Carbon Resistors	£1
SX13	200	1/4-watt Carbon Resistors	£1
SX14	150	1/2-watt Resistors 22 ohm	£1
SX15	100	2m2 Mixed 1 and 2 watt Resistors 22 ohm 2m2 Mixed	£1

Paks SX12-15 contain a range of Carbon Film Resistors of assorted values from 22 ohms to 2.2 meg. Save pounds on these resistor paks and have a full range to cover your projects.  
\*Quantities approximate, count by weight

## "CAPABLE CAPACITOR PAKS"

Pak No.	Qty	Description	Price
SX16	250	Capacitors Mixed Types	£1
SX17	200	Ceramic Capacitors Miniature	£1
SX18	100	Mixed Ceramics 1-pl-5-pl	£1
SX19	100	Mixed Ceramics 6-pl 0.5m	£1
SX20	100	Assorted Polyester/Polystyrene Capacitors	£1
SX21	60	Mixed C780 type capacitors metal foil	£1
SX22	100	Electrolytics, all sorts	£1
SX23	50	Quality Electrolytics 50 10000m	£1
SX24	20	Tantalum Beads, mixed	£1

\*Quantities approximate, count by weight.

## AUDIO PLUGS, SOCKETS AND ACCESSORIES

**25** pieces of Audio Plugs, Sockets and Connectors to include DIN 180°, 240°, In-line 3.6 Pin, Speakers, Phono Jack, Stereo and Mono, etc. etc. Valued at well over £3 normal. Order No. SX25. Our Price **£1.50** per pak. Guaranteed to save you money.  
SX26 3 Pcs. of 6 pin 240° DIN Plugs and Chassis Sockets **50p**  
SX28 100 Silicon NPN Transistors—all perfect. Coded mixed types with data and eqpt. sheet. No rejects. Real value. **£2.50**  
SX29 100 Silicon PNP Transistors—all perfect. Coded mixed types with data and eqpt. sheet. No rejects. Fantastic value. **£2.50**

## Silicon NPN 'L' Type Transistors

10-32 Plastic centre connector  
Like BC182 — 183L — 184L  
VC80 45 VCE0 30 IC200mA Hfe 100-400  
50 ohm 100 ohm 500 ohm 1000 ohm  
**£1.50 £2.50 £10.00 £17.00**

## PNP SILICON TRANSISTORS:

Similar ZTX500 — ZTX214 — E-Line  
VCE0 40 VCE0 35 IC 300mA Hfe 50-400  
Brand New — Uncoded — Petrol Devices  
50 ohm 100 ohm 500 ohm 1000 ohm  
**£2.00 £3.50 £15.00 £25.00**  
Order as ZTXPNP

## MOTOROLA PIEZO ELECTRIC TWEETER

Maximum Ratings:  
25 volts rms which is equal to:  
200 watts across 4 ohms  
100 watts across 8 ohms  
50 watts across 16 ohms  
BI-PAK SPECIAL OFFER PRICE **£4.88**  
ORDER NO. 1907


## DOME TWEETER

Dome tweeter for systems up to 50w.  
Impedance: 8 ohms  
Frequency Response: 2000-20,000Hz  
Dims: 98mm diam. x 31mm deep  
Our Price **£2.88** DM7200


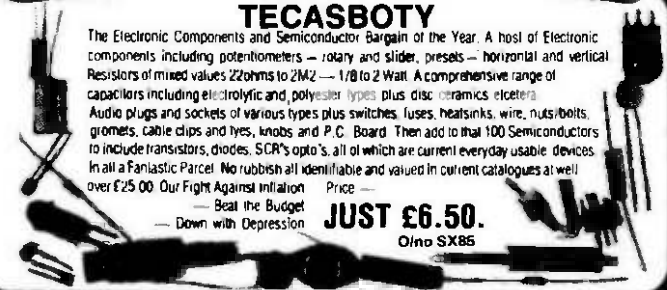
## TECASBOTY

The Electronic Components and Semiconductor Bargain of the Year. A host of Electronic components including potentiometers — rotary and slider, presets — horizontal and vertical. Resistors of mixed values 22ohms to 2M2 — 1/8 to 2 Watt. A comprehensive range of capacitors including electrolytic and polyester types plus disc ceramics etcetera. Audio plugs and sockets of various types plus switches, fuses, heatshinks, wire, nuts/bolts, gromets, cable clips and ties, knobs and P.C. Board. Then add to that 100 Semiconductors to include transistors, diodes, SCR's opto's, all of which are current everyday usable devices. In all a Fantastic Parcel. No rubbish all identifiable and valued in current catalogues at well over £25.00. Our Fight Against Inflation Price —  
— Beat the Budget  
— Down with Depression **JUST £6.50.**  
Oino SX85



# BI-PAK

Send your orders to Dept. ET14 BI-PAK PO BOX 6 WARE HERTS  
SHOP AT 3 BALDOCK ST, WARE HERTS  
TERMS: CASH WITH ORDER, SAME DAY DESPATCH, ACCESS  
BARCLAYCARD ALSO ACCEPTED. TEL (0920) 3182. GING 388 7006  
ADD 15% VAT AND 50p PER ORDER POSTAGE AND PACKING



Use your credit card. Ring us on Wate 3182 NOW and get your order even faster. Goods normally sent 2nd Class Mail.  
Remember you must add VAT at 15% to your order. Total Postage add 50p per total order.

# BI-PAK AUDIO

# THE PROFESSIONAL APPROACH

## HIGH QUALITY MODULES FOR STEREO MONO AND OTHER AUDIO EQUIPMENT

BI-PAK Audio Modules are famous for their variety, quality of design and ruggedness. For over 10 years BI-PAK have been suppliers to manufacturers of high quality audio equipment throughout the world - to date, well over 100,000 modules have been sold - this is why discerning amateur enthusiasts and professionals alike insist on using BI-PAK modules in their equipment.

They know that every item is designed and tested to do the job for which it is intended before it leaves the factory. Whatever you are building there is a lot of modules in the BI-PAK range to suit your every need.

### AUDIO AMPLIFIERS


5-10 watts (RMS)  
AL28 5 watt Audio Amp Module 22-30v supply £3.67  
AL30A 7-18 watt Audio Amp. Module 22-30v supply

£4.16.



### AUDIO AMPLIFIERS

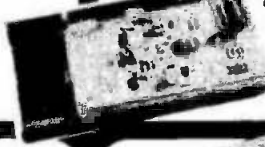15-25.35 watts (RMS)  
AL80 15-25 watt Audio Amp Module 30-50v supply £5.15.  
AL80 35 watt Audio Amp Module £8.07



£13.14.

### AUDIO AMPLIFIER

Audio Amplifier, 50W R.M.S., with integral heat sink and short circuit protection.

Introduced to fulfil the demand for a fully protected power amp, capable of driving high quality speaker systems at up to 50w with distortion levels below 05%. Ideal for domestic use. Discos, P.A. systems, electronic organs, etc. The generously rated components ensure continuous operation at high output levels. AL120 50 watt Audio Amp Module 50.70v supply

### AUDIO AMPLIFIER

125 watts (RMS), AL250.  
A power amplifier providing an output of up to 125w RMS into a 4 ohm load. Four 115w transistors in the output stage makes it extremely rugged while damage from incorrect or short circuit loads is prevented by a four transistor protection circuit. For use in many applications such as disco units, sound reinforcement systems, background music players etc.  
AL250 125 watt Audio Amp Module 50.80v supply

£19.60.

### POWER SUPPLIES

PS12 24v Supply Suit: 2 x AL10 2 x AL20 2 x AL30 & PA12/SA43 £1.86. SPM80 33v Stabilised supply Suit: 2 x AL80 PA100 to 15 watts £4.04. SPM12045 45v Stabilised supply Suit: 2 x AL80 PA100 to 25 watts £3.38. SPM12055 55v Stabilised supply Suit: 2 x AL80 PA200 £3.38. SPM12065 65v Stabilised supply Suit: 2 x AL120 PA200 1 x AL250 £3.38. SG30 150-15 Stabilised power supply for 2 x GE100 MKII £3.38

SPM120 is a fixed voltage stabiliser with an output voltage of either 45v, 55v, or 65v. Designed for use in audio applications, the stabiliser which provides output currents up to 2.5A operates direct from a mains transformer requiring only the addition of two electrolytic capacitors to complete the power supply.



### STEREO PRE-AMPLIFIERS

PA12 Supply voltage 22-30v input sensitivity 300mv Suit AL10/AL20/AL30 £3.56. PA100 Supply voltage 30-50v inputs. Tape Tuner Mag P.U. Suit: AL80/AL80 £17.85. PA200 Supply voltage 35-70v inputs. Tape Tuner Mag P.U. Suit: AL80/AL20/AL250 £18.24.

The PA200 is basically our popular PA100, modifications being made to make it compatible with the higher output amplifiers i.e. AL120 & AL250. The unit boasts six push button selectors giving a choice of 3 inputs, 2 filters, for both high and low frequencies and a stereo or mono button, all combining to give a top quality stereo pre-amplifier and tone control.

### MINIATURE FM TRANSMITTER MODULE

Freq 95-106 MHz Range: 4 mile Size: 45mm x 20mm Add 9v batt. Not licensed in UK  
Ideal for: 007-M19-FBI-CIA-KGB-etc. Price: £5.50

### MAGNETIC CARTRIDGE PRE-AMPLIFIER

Enjoy the quality of a magnetic cartridge with your ceramic equipment using the MPA30 which is a quality pre-amp, enabling magnetic cartridges to be used where factories exist for ceramic cartridges only. With a DIN input socket & full, easy to follow instructions. MPA30 Stereo Mag Cartridge, Pre-amp. - input 3.5mv Output 100mv £3.27.

### MONO PRE-AMPLIFIERS

MM100 suitable for disco mixer. MM100G suitable for guitar pre-amp mixer. The MM100 and MM100G mono pre-amplifiers are compatible with the AL80, AL80 AL120 and AL250 power amplifiers and their associated power supplies. MM100 Supply voltage 40-65v inputs. Tape Mag P.U. Microphone Max output 500mv £12.43. MM100G Supply voltage 40-65v inputs: 2 Guitars, Microphones Max output 500mv



£12.43.

### GE100 MKII

10 Channel Monographic Equaliser.  
Only 156mm x 65mm x 50mm including the 10 x 10K 45mm slider potentiometers and knobs which are mounted on a board above the circuitry. In the range of 31Hz to 16KHz you can cut and boost  $\pm 12dB$  with the 10 sliders, each with frequency marked on the circuit board. The GE100 uses include meters, P.A. systems and discos. It will also improve the sound reproduction of your existing audio equipment. Power supply for GE100 old SG30. Together with Transformer no: 2043. GE100 MKII 10 Channel monographic Equaliser with sliders & Knobs £20.00.

### PUSH BUTTON STEREO FM TUNER

Fitted with Phase locked loop decoder S453 Provides instant programme selection at the touch of a button ensuring accurate tuning of 4 pre-selected stations, any of which may be altered as often as you choose, simply by changing the settings of the preset controls. Features include FET input stage, Var-cap diode tuning.



£19.00.

Transformers are not included with power supplies. SPM120 Range also require reservoir and output capacitors

### TRANSFORMERS

2034 1.7 amp 25v suit SPM80 £4.88. 2035 2 amp 55v £4.86. 2036 750mA 17v Suit PS12 £2.85. 2040 1.5 amp 0-45v 55v Suit SPM12045 SPM12055v £8.46. 2041 2 amp 0-55v 65v Suit SPM12055 SPM12065v £8.46. 2038 1 amp 0-20v Suit Stereo 30 £3.58. 2043 150mA 150-15v Suit SG30 £1.88.

### ACCESSORIES

138 Teak Cabinet Suit Stereo 30 320 x 235 x 81mm £7.88. 140 Teak Cabinet Suit STA15 425 x 290 x 95mm £8.88. FP100 Front Panel for PA100 & PA200 £1.88. BP100 Back Panel for PA100 & PA200 £1.88. GE100FP Front Panel for one GE100MKII £1.76. TC880 Kit of Parts including Teak Cabinet chassis, sockets & knobs etc. 80 house STA15 Amplifier £17.66. PS250 Connects - 1 capacitor & 4 diodes for constructing unregulated power supply for AL250 to 125 watts £2.88.

### BI-PAK'S COMPLETELY NEW CATALOGUE

Completely re-designed. Full of the type of components you require, plus some very interesting ones you will soon be using and of course, the largest range of semiconductors for the Amateur and Professional you could hope to find. There are no wasted pages of useless information so often included in catalogues published nowadays. Just solid facts i.e. price, description and individual features of what we have available. But remember, Bi-Pak's policy has always been to sell quality components at competitive prices and THAT WE STILL DO.

BI-PAK'S COMPLETELY NEW CATALOGUE is now available to you. You will be amazed how much you can save when you shop for Electronic Components with a Bi-Pak Catalogue. Have one by you all the time - it pays to buy BI-PAK.

To receive your copy send **75p** plus 25p p&p

### BI-KITS

STAS 5 watts per channel Stereo Amplifier Kit consisting of 2 x AL20 amplifiers 1 x PA12 pre-amplifier 1 x PS12 power supply 1 x 2038 transformer and necessary wiring diagram £18.82. STA10 10 watts per channel Stereo Amplifier Kit consisting of 2 x AL30 amplifiers 1 x PA12 pre-amplifier 1 x PS12 power supply 1 x 2038 transformer and necessary wiring diagrams £28.83.

STA15 15 watts per channel Stereo Amplifier Kit consisting of 2 x AL60 amplifiers 1 x PA100 pre-amplifier 1 x SPM80 power supply 1 x 2034 transformer 2 x coupling capacitors for 8 ohms 470 mfd 50v and necessary wiring diagrams £38.78. STA25 25 watts per channel Stereo Amplifier Kit consisting of 2 x AL80 amplifiers 1 x PA100 pre-amplifier 1 x SPM12045 power

supply 1 x 2040 transformer 2 x coupling capacitors for 8 ohms 470 mfd 45v 1 x reservoir capacitor 2200 mfd 100v and necessary wiring diagram £46.78. STA35 35 watts per channel Stereo Amplifier Kit consisting of 2 x AL80 amplifiers 1 x SPM12055 power supply 1 x PA200 pre-amplifier 1 x 2035 transformer 2 x coupling capacitors 470 mfd at 50v for 8 ohms 1 x reservoir capacitor 2200 mfd 100v and necessary wiring diagram £46.78.

### REGULATED VARIABLE STABILISED POWER SUPPLY

Variable from 230 volts and 0.2 Amps Kit includes - 1 - VPS30 Module, 1 - 25 volt 2 amp transformer, 1 - 0.50v 2" Panel Meter, 1 - 0.2 amp 2" Panel Meter, 1 - 470 ohm wirewound potentiometer, 1 - 4K7 ohm wirewound potentiometer Wiring Diagram included VPS30 KIT £20.

### SIREN ALARM MODULE

American Police type siren powered from any 12 volt supply into 4 or 8 ohm speaker. Ideal for car burglar alarm, freezer break-down and other security purposes. BP124 5 watt 12v max - Siren Alarm Module £3.85.

# BI-PAK

Send your orders to Dept. E114 BI-PAK PO BOX 6 WARE HERTS SHOP AT 3 BALDWIN ST. WARE HERTS. TERMS: CASH WITH ORDER. SAME DAY DESPATCH. ADDRESS: HARCLEY ROAD ALSO ACCEPTED TEL: 04720 3187. CIRD 388 7096. ADD 15% VAT AND 50% PER ORDER POSTAGE AND PACKING.



Use your credit card. Ring us on Ware 3182 NOW and get your order even faster. Goods normally sent 2nd Class Mail. Remember you must add VAT at 15% to your order. Total Postage add 50p per Total order.

# ETI PCB SERVICE

Up until now PCBs were always the hardest component to obtain for a project. Of course you could make your own, but why bother anymore?

Now you can buy your boards straight from the designers — us! As of this issue all (non-copyright) PCBs will be available automatically from the ETI PCB Service. Each board is produced from the same master used to build our prototypes, so you can be sure it's accurate, and will be finished to the high standard you would expect from ETI.

In addition to the PCBs for this month's projects, we are making available some of the more popular designs from our recent past. See the list below for details. Please note that **NO OTHER BOARDS ARE AVAILABLE**. If it's not listed, we don't have it!

<b>APRIL 79</b>	<input type="checkbox"/> Guitar Effects Unit	£1.98	<b>MARCH 81</b>	<input type="checkbox"/> Engineer's Stethoscope	£1.99	<b>NOVEMBER 81</b>	<input type="checkbox"/> Music Processor	£5.51
	<input type="checkbox"/> Click Eliminator	£4.98					<input type="checkbox"/> Voice-Over Unit	£2.98
<b>JUNE 79</b>	<input type="checkbox"/> Accentuated Beat Metronome	£2.70	<b>APRIL 81</b>	<input type="checkbox"/> Musical Box	£1.98		<input type="checkbox"/> Car Alarm	£2.11
<b>FEBRUARY 80</b>	<input type="checkbox"/> Tuning Fork	£1.98		<input type="checkbox"/> Drum Machine (two boards)	£4.20		<input type="checkbox"/> Phone Bell Shifter*	£2.22
<b>MARCH 80</b>	<input type="checkbox"/> Signal Tracer	£1.70		<input type="checkbox"/> Guitar Note Expander	£2.40	<b>DECEMBER 81</b>	<input type="checkbox"/> Alcohometer (two boards)	£3.99
<b>AUGUST 80</b>	<input type="checkbox"/> CMOS Logic Tester	£1.98	<b>JUNE 81</b>	<input type="checkbox"/> Mini-drill Speed Controller	£2.20		<input type="checkbox"/> Bodywork Checker	£1.48
	<input type="checkbox"/> Capacitance Meter	£2.20		<input type="checkbox"/> Antenna Extender	£2.40		<input type="checkbox"/> Component Tester	£1.12
	<input type="checkbox"/> Ultrasonic Burglar Alarm	£2.15		<input type="checkbox"/> Alien Attack	£1.98	<b>JANUARY 82</b>	<input type="checkbox"/> Parking Meter Timer	£1.78
<b>OCTOBER 80</b>	<input type="checkbox"/> Cassette Interface	£2.20		<input type="checkbox"/> LED Jewellery: Cross	£1.10		<input type="checkbox"/> Infant Guard	£1.35
	<input type="checkbox"/> Fuzz/Sustain Box	£2.45		<input type="checkbox"/> Spiral (two boards)	£1.98		<input type="checkbox"/> Guitar Tuner (two boards)	£4.48
<b>NOVEMBER 80</b>	<input type="checkbox"/> Touch Buzzer	£1.45		<input type="checkbox"/> Star (two boards)	£1.99	<b>FEBRUARY 82</b>	<input type="checkbox"/> Ripple Monitor	£1.56
	<input type="checkbox"/> Light Switch	£1.45	<b>JULY 80</b>	<input type="checkbox"/> Waa-phase	£1.15		<input type="checkbox"/> Pest Monitor	£1.39
	<input type="checkbox"/> Metronome	£1.45		<input type="checkbox"/> System A A-MM/A-MC	£1.99		<input type="checkbox"/> I Ching Computer (two boards)	£3.98
	<input type="checkbox"/> 2W Power Amp	£1.45		<input type="checkbox"/> System A A-PR	£3.88		<input type="checkbox"/> Moving-magnet stage	£2.85
	<input type="checkbox"/> RIAA Preamplifier	£1.45		<input type="checkbox"/> Smart Battery Charger	£1.48		<input type="checkbox"/> Moving-coil stage	£2.85
	<input type="checkbox"/> Audio Test Oscillator	£2.35	<b>AUGUST 81</b>	<input type="checkbox"/> System A Power Amp (A-PA)	£3.58	<b>MARCH 82</b>	<input type="checkbox"/> Infinite Improbability Detector	£2.53
<b>DECEMBER 80</b>	<input type="checkbox"/> Musical Doorbell	£2.10		<input type="checkbox"/> Flash Sequencer	£2.58		<input type="checkbox"/> Capacitance Meter (two boards)	£10.64
	<input type="checkbox"/> Bench Amplifier	£1.90		<input type="checkbox"/> Hand-clap Synthesiser	£2.98		<input type="checkbox"/> Robot Motor Controller	£2.85
	<input type="checkbox"/> Four Input Mixer	£1.98		<input type="checkbox"/> Heartbeat Monitor	£1.37		<input type="checkbox"/> Light Wand	£1.40
<b>JANUARY 81</b>	<input type="checkbox"/> LED Tacho	£3.10		<input type="checkbox"/> Watchdog Home Security (two boards)	£3.98	<b>APRIL 82</b>	<input type="checkbox"/> Wattmeter	£3.39
	<input type="checkbox"/> Multi-Option Siren	£2.40	<b>SEPTEMBER 81</b>	<input type="checkbox"/> Mains Audio Link (three boards)	£5.51		<input type="checkbox"/> Contrast Meter	£2.12
	<input type="checkbox"/> Universal Timer	£2.48		<input type="checkbox"/> Laboratory PSU	£3.40		<input type="checkbox"/> Sound Effects board	£1.80
<b>FEBRUARY 81</b>	<input type="checkbox"/> Infra-red Alarm (four boards)	£4.98	<b>OCTOBER 81</b>	<input type="checkbox"/> Enlarger Timer	£2.55		<input type="checkbox"/> High Impedance Probe	£1.48
	<input type="checkbox"/> Pulse Generator	£2.68		<input type="checkbox"/> Sound Bender	£1.99		<input type="checkbox"/> Guitar Practice Amp	£5.68
				<input type="checkbox"/> Thermal Alarm	£1.97		<input type="checkbox"/> Accurate Voltage Monitor	£1.54
				<input type="checkbox"/> Micropower Pendulum	£1.66			

**How to order:** indicate the boards required by ticking the boxes and send this page, together with your payment, to: ETI PCB Service, Argus Specialist Publications Ltd, 145 Charing Cross Road, London WC2H 0EE. Make cheques payable to ETI PCB Service. Payment in sterling only please. Prices may be subject to change without notice.

Total for boards     £ .....  
 Add 40p p&p             0.40  
 Total enclosed         £ .....

I wish to pay by Access/Barclaycard. Please debit my account

BARCLAYCARD

VISA

5 2 2 4

4 9 2 9



Signed .....

Name .....

Address .....

# DESIGNER'S NOTEBOOK

Five into one does go. This month Don Keighley explains all about sampling and time-division multiplex systems, and looks closely at the advantages of pulse-width modulated telecommunications networks.

Sampling is a process we can undertake if we want to combine many different signals on to a single transmission line. The transmission line can be of any type such as wire, radio, or optical. Combining several signals into one is called 'multiplexing' and can save the expense of having many separate lines. Sampling is used in a specific type of multiplexing called time-division multiplexing (TDM) which I'll explain later. The other form of multiplexing — frequency-division multiplexing (FDM) — is the basis of all standard radio transmissions. Each signal to be transmitted is mixed with a carrier wave (or radio frequency) on to a set frequency within the radio spectrum. Thus many signals can be transmitted and received by radio link — one on each defined frequency of the radio spectrum.

Figure 1 shows an illustration of sampling. In the figure, a sinusoidal signal (known as the message signal) has a series of values taken at regular intervals. These sample values can be used to represent the message signal. For instance, we can pass the actual DC values of the samples, ie their voltages, along the line. At the other end of the line the sample values, or pulses as they are usually called, are converted back into the message signal, simply by passing them through a lowpass filter. The filter removes the high frequency pulses and thus re-creates the envelope of the original message signal — as shown by the sinewave of Fig. 2.

One of the most important questions arising is — How often do we need to sample the message signal? It is obvious that if the signal is sampled too few times we won't be able to

reconvert the pulses into the message signal at the receiving end of the transmission line.

The minimum number of samples is given by the sampling theorem, which states that a message signal of bandwidth  $B$  Hz can be represented by a set of sample values taken at a frequency of  $2B$  Hz. For example, an audio system has a frequency response of 20 Hz to 20 kHz. Its bandwidth is thus  $20,000 - 20 = 19,980$  Hz. The audio signal of the system can thus be represented if samples are taken at  $2 \times 19,980$  Hz = 39,960 Hz.

But the *minimum* number of representative samples ( $2B$  Hz) isn't the *easiest* number of samples to convert back into the message signal. It's usual to take a greater number of samples because doing so makes the reversion easier. To see why this is so we've got to take a look at the spectra of the transmitted samples and see how they differ when different sample frequencies are used. Figure 3 shows the possible spectrum of a message signal such as an audio signal. It's the sort of result you would see on the screen of a spectrum analyser. Frequency  $f_m$  is the maximum frequency contained in the signal. The lowest frequency contained is 0 Hz (the signal extends down to DC), so the bandwidth of the message signal is  $f_m - 0 = f_m$  Hz.

When the message signal is sampled at a frequency  $f_s$  the overall spectrum looks something like that shown in Fig. 4 and consists of components at harmonics of the sampling frequency, with upper and lower sidebands around them, as well as the original spectrum of the message signal. In Fig. 4 you can see the sampling frequency,  $f_s$  is more than twice  $f_m$  — hence there is a gap between the highest frequency of the higher sideband of a

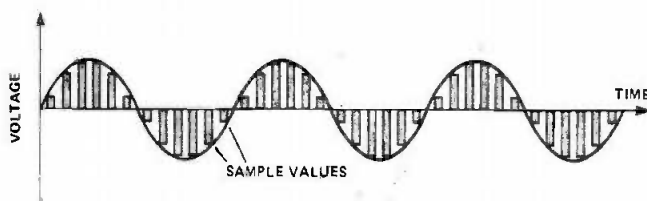


Fig. 1 A message signal can be represented by a series of sample values of the signal.

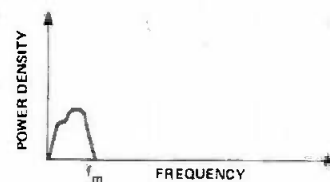


Fig. 3 Power density spectrum of typical audio signal. The higher frequency component in the signal is  $f_m$ . The signal extends down to 0 Hz, so the bandwidth of the signal is  $f_m$  Hz.

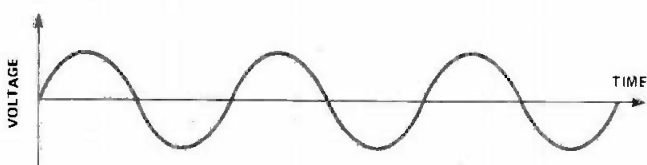


Fig. 2 If the series of sample values is passed through a lowpass filter the original message signal is recreated.

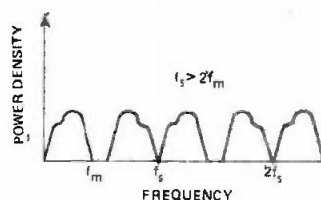


Fig. 4 Power density spectrum of an audio signal, sampled at a frequency of  $f_s$ . In this example,  $f_s$  is greater than  $2f_m$ .

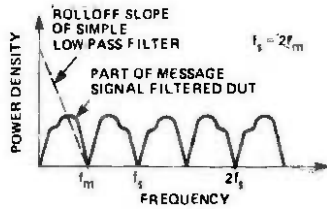


Fig. 5 Sampling frequency  $f_s$  equals  $2f_m$ . A simple lowpass filter may filter out some of the wanted message signal.

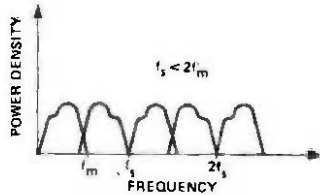


Fig. 6 Sampling frequency less than  $2f_m$ . A lowpass filter cannot be used to recreate the original message signal.

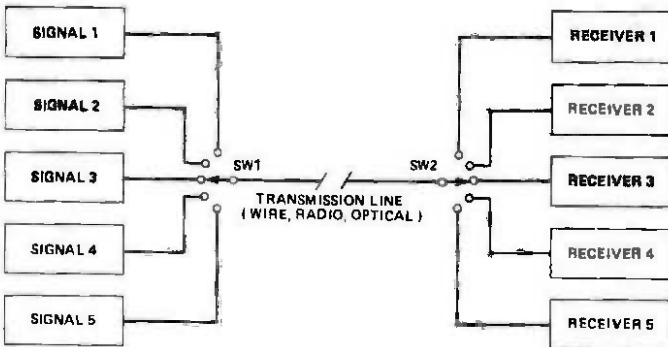


Fig. 7 A simple time-division multiplex (TDM) system.

component and the lowest frequency in the lower sideband of the next component. This gap between bands means that a simple lowpass filter can be used at the receiver to pass only the message signal and not the higher components: so the message signal is recreated.

With a sampling frequency of only  $2f_m$  (Fig. 5) the highest frequency of one band and the lowest frequency of the next occur at the same point. A simple lowpass filter would filter out some of the message signal, as shown in the figure. A more complex lowpass filter (with a steeper roll-off slope) could be used to correctly recreate the message signal.

In Fig. 6,  $f_s$  is less than  $2f_m$  and, as you would expect, the spectrum shows how message signal and sidebands overlap. A lowpass filter cannot be used to recover the whole of the message signal without letting through part of the next sideband.

## TDM Tricks

A simple TDM system is shown in Fig. 7, in block diagram form. Each signal to be transmitted is connected to an input of switch SW1. This switch, although shown in the diagram as a mechanical-type switch, will be of electronic construction in a real TDM system, so that a high switching speed can be obtained. The output signal from the switch is transmitted along the transmission line to switch SW2, which connects each receiver, in turn, to the line. Providing the switches are operating fast enough so that the sampling theorem is fulfilled ( $f_s \geq 2f_m$ ) for all the message signals, everything is fine and we have five signals passing down one line.

The whole process of sampling and TDM is a form of modulation because only a representation of the message signal is transmitted, not the actual signal. And because pulsed samples of the message signal are transmitted, we call the process pulse modulation.

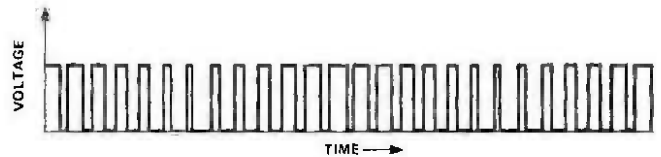


Fig. 8 Pulse-width modulation. The width of each pulse varies in accordance with the amplitude of the message signal.

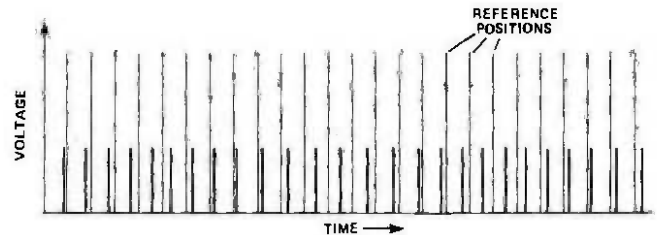


Fig. 9 Pulse-position modulation. Each pulse's position, with respect to a reference point, varies in accordance with the message signal amplitude.

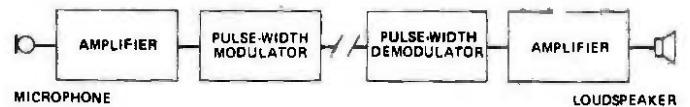


Fig. 10 A pulse-width modulation microphone/loudspeaker system.

There are various forms of pulse modulation which can be used in a TDM system, all relying on the fact that the original sample values control some property of corresponding pulses. The one just described uses the DC value (ie amplitude) of the pulses and is therefore known as pulse-amplitude modulation. Other forms of pulse modulation are: pulse-width modulation (where the width of the pulses is varied according to the sampled value) and pulse-position modulation (the position of the pulse, relative to a reference position, is proportional to the sample value). Figures 8 and 9 show examples of these pulse modulation systems and the sampling frequencies of both must follow the sampling theorem — the sampling frequency must be at least twice that of the message signal bandwidth. There is a final pulsed system, in which each sampled value is converted into a train of binary digits. This is, strictly speaking, a digital system and doesn't concern us here; however the system must still follow the sampling theorem.

## Practical Matters

With careful design all the pulse modulation systems can give good results in TDM but perhaps the best — because it's easy to use, has a high immunity to interference and yet needs a minimum of component hardware — is pulse-width modulation (PWM). Figure 10 shows a block diagram of a PWM microphone/loudspeaker set-up — such as you might have in a multi-station intercom system or similar.

We can investigate the modulation and demodulation blocks in more detail, as in Fig. 11 and 12. Figure 11 shows a simplified pulse-width modulator. It consists of an oscillator to provide sampling pulses at a rate of over  $2f_m$ , so that the sampling theorem is fulfilled. In a good quality audio modulator, the sampling rate is therefore over 40 kHz and the time between pulses must be  $1/f_s = 25 \mu\text{s}$ .

The pulse duration is less than this, say 1  $\mu\text{s}$ , and each pulse charges the capacitor C1 to full voltage. After charging, the capacitor is linearly discharged via the constant current source. The cycle repeats itself at every pulse. The capacitor's discharge rate is a product of the capacitor/constant current time constant, which should be about 2  $\mu\text{s}$ . Comparator IC1 compares the ramp discharge with the incoming audio signal — when the non-inverting input voltage is above that of the inverting input

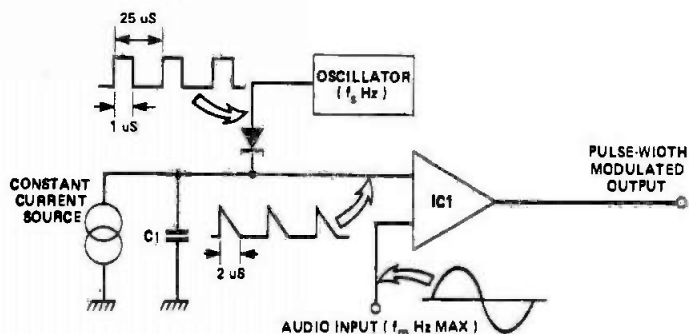


Fig. 11 A pulse-width modulator in detail.

the comparator output is high; when the non-inverting input is below the inverting input the output is low. Thus the output is high the instant of every sampling pulse, but falls low again after a time which is linearly related to the amplitude of the audio signal. In other words, the width of the pulse is modulated by the audio signal.

A pulse-width demodulator is shown in Fig. 12. A capacitor with a parallel constant current source is again used and the incoming width-modulated pulses cause a charge/discharge cycle similar to that in the modulator. The average DC level of charge across the capacitor is dependent on the width of the pulses — the wider the pulse, the higher the DC level. Buffer IC1 prevents loading of the voltage across the capacitor and the output is lowpass filtered by capacitor C2 to remove the sharp spikes of the sampling pulses, thus re-creating the original audio message signal.

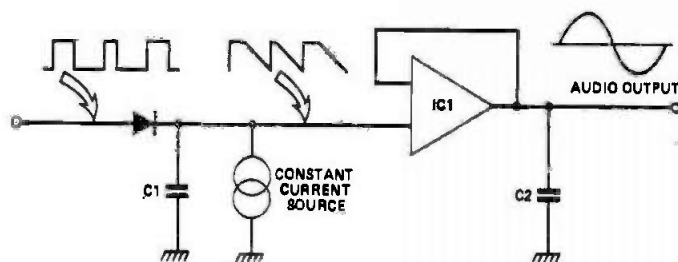


Fig. 12 A pulse-width demodulator can be built using the same basic components used in a pulse-width modulator.

The advantages of such a system aren't always immediately obvious, but you must remember that the audio signal is being represented by a pulse of nominal width 2  $\mu$ s in a cycling time of 25  $\mu$ s. This means that 12 different, high-quality audio signals can be time-division multiplexed down that transmission line simultaneously and without interference — and this is just a simple system. With a shorter nominal pulse width and more accurate modulators and demodulators, many more signals can be multiplexed on to a single transmission line.

It's all down to economics really. When you look at a large telecommunications system like the telephone network, there are literally thousands upon thousands of miles of expensive copper cable. By putting 100 telephone conversations down one line the overall cable cost is only 1/100th of that of a non-multiplexed system. Makes sense, doesn't it!

ETI

## Lost in the Hi-Fi Jungle?

Phone Wilmslow 526213

for an expert guide to the territories of:

**A&R** **Dual** **NAD** **MISSION** **PIONEER**

**AIWA** **HITACHI** **OPTONICA** **Sansui**

Plus

ARISTON • ACOUSTIC RESEARCH • P & W • CJ 55 • CELESTION  
GRADO • HITACHI • JR • KEF • M SHORT • MONITOR AUDIO  
ORTOFON • ROGERS • THORENS • VIDOTONE

### HI-FI MARKETS

*Sensible advice from expert staff*

**2 years guarantee on Hi-Fi**

*Service Department on Premises*

**Very competitive prices**

**SWIFT OF WILMSLOW** 5 Swan Street, Wilmslow, Cheshire Telephone 0625 526213

7 HUGHENDEN ROAD, HASTINGS, SUSSEX. TN34 3TG  
Telephone: HASTINGS (0424) 438004

LTD  
ELECTRONIC KITS

KS100 MINI VHF SUPER-REGENERATIVE RECEIVER 88-108MHZ 9V D.C. £5.34 inc VAT

KS272 6 CHAN HIGH POWER VU DISPLAY, 300W PER CHAN, 240V A.C. £21.29 inc VAT

KS200 MINI F.M. TRANSMITTER 88-108 MHZ 9V D.C. (NOT LICENCEABLE IN UK) £7.39 inc VAT

KS238 3 CHANNEL MICROPHONE OPERATED SOUND TO LIGHT, 300W PER CHAN 240V A.C. £14.43 inc VAT

KS240 3 CHAN SOUND TO LIGHT, OUTPUT 3 X 1KW 240V £13.70 inc VAT

UK564 LOGIC PROBE, SUITABLE FOR TTL OTL-SMOS CIRCUITS, 5V D.C. £9.46 inc VAT

KS260 3 CHAN CHASE LIGHT, 1KW PER CHAN, 240V A.C. £11.27 inc VAT

UK993 CROSS HATCH GENERATOR R.F. OUTPUT, U.H.F. INTERNAL 9V D.C. SUPPLY £22.94 inc VAT

Post & Packing, 50p per KS kit, 75p per UK kit. Send 20p S.A.E. for catalogue of our extensive range of kits & cabinets. Trade, Educational & Export enquiries welcomed.

BARCLAYCARD VISA

# KITS, COMPONENTS MICROS & PARTS

## THE GARAGE DOOR AT YOUR COMMAND

At last, a kit to enable your motorised garage door to be opened without setting foot from your car, and also enable the lights in your garage and drive to be switched on or off at the touch of a button. A momentary relay output operating the door control circuits (relay closes only while a valid code is transmitted) is indicated by LED. It features two latched outputs with common reset for switching 240V a.c. mains loads via remote opto-isolated solid state switches (1kW maximum). A hand-held transmitter for 9V PP3 battery operation constituting 4 function keys: Open/Close, on 1, on 2, Off, giving a range of approximately 40 feet is included. As a general purpose remote control in the home for switching lights, television and other appliances. This unit is ideal for the aged or disabled.

AS FEATURED IN PE FEB & MAR  
**£23.75**

ALL PRICES  
EXCLUDE VAT

### DISCO LIGHTING KITS

**DL1000K**  
This value-for-money kit features a bi-directional sequence, speed of sequence and frequency of direction change, being variable by means of potentiometers and incorporates a master dimming control. Only £14.80



**DLZ1000K**  
A lower cost version of the above, featuring unidirectional channel sequence with speed variable by means of a pre-set pot. Outputs switched only at mains zero crossing points to reduce radio interference to a minimum. Only £8.00

Optional opto input DL A1 ..... 60p  
Allowing audio ("beat")—light response.

### DO YOU LONG TO HEAR YOUR DOORBELL RING?

Our latest kit gives you a pleasing three-note harmonically related tone sequence (not a microprocessor controlled buzz or the same old ding dong) at a touch of a button.

This kit, based on a new integrated circuit, is supplied complete with a printed circuit board, loudspeaker and drilled box and requires only 9V battery and push button common to most households.

It may also be switched by logic in such applications as car alarms, clocks, toys, P.A. systems, etc. The unit produces a 150mW output and draws less than one 1uA from a PP3 battery when the tone ceases. Supplied complete with circuit and assembly instructions.

**IDEAL PROJECT FOR BEGINNERS—  
ONLY £5.00**



### DVM/ULTRA SENSITIVE THERMOMETER KIT

This new design is based on the ICL7126 1/2 lower power version of the ICL7106 chip and a 3 1/2 digit liquid crystal display. This kit will form the basis of a digital multimeter (only a few additional resistors and switches are required—details supplied), or a sensitive digital thermometer (-50°C to +150°C) reading to 0.1°C. The basic kit has a sensitivity of 200mV for a full scale reading, automatic polarity indication and an ultra low power requirement—giving a 2 year typical battery life from a standard 9V PP3 when used 8 hours a day, 7 days a week.  
Price £15.50



**WE ALSO STOCK:  
VERO PRODUCTS  
ANTEX SOLDERING IRONS  
BABANI BOOKS**

### EDUCATIONAL EXPANSION WITH SOFTY 2

Plug SOFTY 2 into the EPROM socket of your micro (Z80, 6800, 8035, etc.) prototype system and SOFTY 2 will operate as the ROM in your system but enable you to write data into any location, observe memory contents on any black & white TV and store the programme on a cassette recorder if required.


Various editing facilities are also available, permitting bytes or blocks of code to be changed, inserted, deleted, etc., enabling the programme to be developed and run on the host computer.

After "debugging" SOFTY 2 may be used to programme an EPROM (2716 or 2732). You can also use it as an intelligent EPROM programmer to copy EPROM's from a master to/from tape.

Housed in a black ABS case SOFTY 2 comes complete with a mains supply cable and 24-pin d.i.l. plug for connection to your prototype system and TV lead.

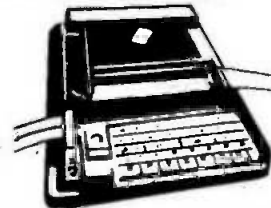**FULLY BUILT AND TESTED—ONLY £169.00**

For further details of SOFTY 2 and the new Z80 Assembler/Micro Controller-Menta available at just £115.00 please send stamped addressed envelope



### THE KEY TO YOUR SECURITY IS IN OUR LOCK

If the thought of car thieves, house breakers or people tampering with your electrical and electronic equipment upsets you, we have just the kit for you.

Our **ELECTRONIC LOCK KIT** includes a 10-way keyboard and a special IC which provides a 750mA output to drive a solenoid or relay (not supplied) when four keys are depressed in the correct sequence. This gives over 5,000 possible combinations! The sequence is prewired and may be easily changed by means of a small plug and socket. A "SAVE" function is also available enabling the open code to be stored (especially useful in a car when it is left in a garage for servicing as the open code need not be disclosed). Size: 7x6x3 cms. Power Consumption is 40uA at 5V to 15V d.c.

At only £10.50 + VAT, it will make a smaller hole in your pocket than a bunch of keys!

Electric Lock Mechanism ..... £12.50  
Suitable for use with existing door locks and above electronic lock kit.

### THE MULTI-PURPOSE TIMER HAS ARRIVED

Now you can run your central heating, lighting, hi-fi system and lots more with just one programmable timer. At your selection it is designed to control four mains outputs independently, switching on and off at pre-set times over a 7 day cycle, e.g. to control your central heating (including different switching times for weekends), just connect it to your system programme and set it and forget it—the clock will do the rest.



**FEATURES INCLUDE—**

- 0.5" LED 12 hour display.
- Day of week, am/pm and output status indicators.
- 4 zero voltage switched mains outputs.
- 50/60Hz mains operation.
- Battery backup saves stored programmes and continues time keeping during power failures. (Battery not supplied).
- Display blanking during power failure to conserve battery power.
- 18 programme time sets.
- Powerful "Everyday" function enabling output to switch every day but use only one time set.
- Useful "sleep" function—turns on output for one hour.
- Direct switch control enabling output to be turned on immediately or after a specified time interval.
- 20 function keypad for programme entry.
- Programme verification at the touch of a button.


**THERE HAS NEVER BEEN A CLOCK CAPABLE OF SO MUCH AT SUCH A LOW PRICE—  
ONLY £45.00**  
(including components, assembly and programme instructions in an attractive case).
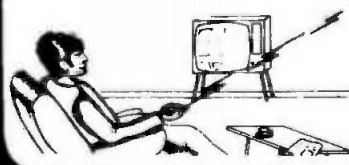
### THE PERFECT AID FOR "LAZYITIS"

Our Lamp Dimmer Kit with **INFRA RED REMOTE CONTROL** will enable you to switch the lights on or off, and set the brightness, at a push of a button without leaving your armchair, water-bed, etc. Not only will you save time but it has also been estimated that the savings in shoe leather and carpet wear alone would pay for this unit in approximately 1,3697 years or more!




This unit has considerable practical uses, especially for the old, infirm and disabled. It works like a conventional dimmer, enabling you to switch the lights on or off, or to dim them to whatever brightness you require, by touch or using the hand-held infra red transmitter. When assembled, it fits into a plaster depth box to replace your conventional switch or dimmer with no rewiring.



**TD300K Dimmer Kit ..... £14.30**  
**MKS Transmitter Kit ..... £4.20**  
We also still sell our highly popular **TD300K Touch Dimmer Kit at £7.00** and the **LD300K rotary controlled Dimmer Kit at ..... only £3.50**  
All kits contain all necessary components and full instructions. You only need a soldering iron and cutters.
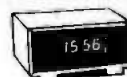
### 24 HOUR CLOCK/APPLIANCE TIMER KIT

Switches any appliance up to 1kW on and off at present times once per day. Kit contains: AY-5-1230 IC, 0.5" LED display, mains supply, display drivers, switches, LEDs, tracs, PCBs and full instructions.



**CT1000K Basic Kit ..... £14.80**  
**CT1000K with white box (56/131 x 71mm) ..... £17.40**  
(Ready Built) ..... £22.50


Add 55p postage & packing + 16% VAT to total.

Overseas Customers:  
Add £1.75 (Europe), £4.50 (elsewhere) for p&p.  
Send S.A.E. for further STOCK DETAILS.  
Goods by return subject to availability.

**OPEN** 9am to 5pm (Mon to Fri)  
10am to 4pm (Sat)

## FAST SERVICE - TOP QUALITY - LOW LOW PRICES

No circuit is complete without a call to

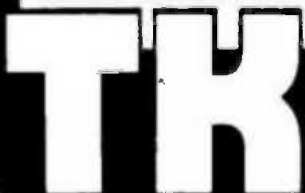

# ELECTRONICS ETI

11 Boston Road  
London W7 3SJ



Telephone: 01 579 9794/2842





# TK COMPONENT CITY

ALL GOODS SUPPLIED ARE GUARANTEED BRAND NEW AND TO MAKER'S SPECIFICATION.

## IF YOU CAN'T (REMOTE) CONTROL YOURSELF

Published remote control systems tend to be quite complex, requiring difficult-to-get components and a well-equipped lab to get them to work. If this has put you off making your own system we have just the kits for you. Using infrared, our K115 range from simple on/off controllers to coded transmitter/receivers with 16 on/off outputs or three analogue outputs for controlling, e.g., TV or Hi-Fi systems. The kits are easy to build and simple to set up, and they are extremely versatile, controlling anything from garage doors to room lighting just by adding the required output circuits, i.e. relays, triacs, etc.

**MK8 - Coded Infra Red Transmitter**  
Based on the SL490, the kit includes 2 IR LEDs, needs only 9x2x13 cm, and requires a 9V (PP3) battery. £5.80

**MK9 - 4 Way Keyboard**  
For use with the MK8 kit, to make a 4-channel remote control transmitter. £1.80

**MK10 - 16 Way Keyboard**  
For use with the MK8 kit, to generate 16 different codes for decoding by the ML928 or ML926 receiver (MK12) kit. £5.40

**MK11 - 10 On-Off channel IR Receiver with 3 analogue outputs (0-10V)** for controlling such functions as lamp brightness, volume, tone, etc. Other functions include an on/standby output and a toggle output, which may be used for sound muting. Based on ML922 decoder IC. Includes its own mains supply. £12.00

**MK12 - 16 Channel IR Receiver**  
For use with the MK8 kit with 16 on/off outputs which with further interfacing, such as relays or triacs, will switch up to 16 items of equipment on or off remotely. Outputs may be latched or momentary, depending on whether the ML926 or ML928 is specified. Includes its own mains supply. £11.95

**MK13 - 11-Way Keyboard**  
For use with MK8 and MK11 kits. Transmits programme step - and analogue - and -131, mute normalise analogue output, and on/standby. £4.35

## DISPLAYS

**COX87A 0.5" dual c.c. Red** 1.80  
**DL340M 0.1" 4-digit c.c.** 4.50  
**FND 500 0.5" c.c.** .85  
**FND 507 0.5" c.c.** .85  
**MF463 4 digit 0.5" multiplexed c.c.** 2.20  
**RGB 1000 10 elements Bar/Graph display, 25 x 8mm.** 1.30  
**Liquid Crystal Display, 3 1/2 digit, 0.5 digit, d.i.l. package.** 6.00

**KL9011 9-digit, 7-seg 0.1" cc LED calculator display with red filter.** .55

## CAPACITORS

**Polyester**  
250V d.c. £ £ £  
0.01 06 01 07 0.58 18  
0.02 06 11 12 1.0 24  
0.033 07 0.22 12 1.5 27  
0.047 07 0.33 12 2.7 31  
0.068 07 0.47 15

400V d.c.  
0.1 15 0.47 24 1.0 35  
0.22 17

**Ceramic - 50V**  
100pF 04 2.200F 04  
220pF 04 4.700F 06  
470pF 04 10.000F 06  
1000pF 04 100.000F 07

**Polystyrene 160V d.c.**  
10pF 15pF 22pF 47pF 68pF 07  
22pF 100pF 220pF 330pF 470pF 08  
1.000pF 2.200pF 3.300pF 4700pF 08  
4.700pF 6.800pF 12

## MEMORIES & MICROS

**PRICES SLASHED**

2114. . . . . 95  
2708. . . . . 2.25  
2716. . . . . 2.45  
2732. . . . . 4.80  
6810. . . . . 1.25  
6821P. . . . . 1.25  
6850P. . . . . 1.50  
6852P. . . . . 2.55  
8035L. . . . . 5.50  
M6802P(CPU). . . . . 3.85  
Z80ACP. . . . . 3.30  
Z80ACTC. . . . . 2.90  
Z80APIO. . . . . 2.90

## INTEGRATED CIRCUITS

555 Timer. . . . . 21  
558 Dual 555 Timer. . . . . 40  
741 Op. Amp. . . . . 19

AD590 Constant Current Temperature Sensor. . . . . 2.75  
AY-5-1224 Clock. . . . . 2.60  
AY-5-1230 Clock/7-mtr. . . . . 4.50  
AY-5-1270 Thermometer. . . . . 8.20  
CA1080 Transconductance Op Amp. . . . . 7.72  
CA3140 CMOS Op. Amp. . . . . 7.75  
CA3140 CMOS Op. Amp. . . . . 4.3  
ICL7106 DVM (LCD Drive). . . . . 7.00  
ICM555 CMOS 555 Timer. . . . . 78  
LM317 3-Term. Reg. . . . . 1.45  
LM3795 Dual SW Amp. . . . . 3.50  
LM380 2W Audio Amp. . . . . .80  
LM3832 Dual low noise pre-amp. . . . . 1.00  
LM386 250mW low voltage amp. . . . . 75  
LM1830 Fluid Level Detector. . . . . 1.50  
LM2917 F-V converter (14 pin). . . . . 1.80  
LM3909 LED Flasher/Oscillator. . . . . .80  
LM3911 Thermometer. . . . . 1.20  
LM3914 Dot/Bdr driver (linear). . . . . 2.10  
LM3915 Dot/Bdr driver (log). . . . . 2.20  
LS720 Electronic Combination Lock with "Smart" feature. . . . . 2.75  
LS725 Electronic Combination Lock with tempo output. . . . . 2.80  
MM74C011 4-digit display controller. . . . . 8.50  
MM74C015 7-segment BCD converter. . . . . 98  
MM74C222 Keyboard Encoder. . . . . 2.80  
MM74C926 counter/7-seg output. . . . . 4.50  
S5688 Touchammer. . . . . 2.50  
SA8000D Door Chime. . . . . 2.00  
SL440 A.C. Power Control. . . . . 1.75  
SL441 Burst Fire Controller. . . . . 1.38  
SN76477 Complex Sound Generator. . . . . 1.75  
TBAB00 5W Audio Amp. . . . . .85  
TBAB105 7W Audio Amp. . . . . 1.20  
TMS1121 Clock/7 day Timer. . . . . 8.60  
Data for TMS1121. . . . . .80  
TDA1024 Zero Voltage Switch. . . . . 1.20  
TDA2020 20W Audio Amp. . . . . 2.85  
TDA290 DC controlled, Base, Treble & Volume Pre Amp. . . . . 1.80  
TL081 J-FET Op. Amp. . . . . .37  
TL082 J-FET Op. Amp. . . . . .80  
TL084 Quad J-FET Op. Amp. . . . . 1.00  
ZNE14 AM Radio. . . . . .98  
ZN1024 E-Timer. . . . . 1.80  
Most ICs supplied with Data Sheet  
Data Sheets only - per device. . . . . 10  
ICL 7126 Ultra Low Power DVM. . . . . 8.00

## LEDs

3mm & 5mm Round Red.....09p Green.....12p  
Clips 3mm & 5mm.....03p Yellow.....12p

**(Shaped LEDs)** Red Green Yellow  
Rectangular (Gravestone) 16p 16p 16p  
Rectangular 2.5x5mm 17p 20p 20p  
Square 5x5mm 17p 20p 20p  
Triangular 5mm 17p 20p  
Arrowhead 2.5x5mm 17p 20p

**(Flashing LEDs)**  
5mm diameter Red.....39p Flashing/Continuous.....42p

**(Tri Colour LEDs)**  
5mm round.....30p 5mm Rectangular.....32p

## OPTO DEVICES

TL114 Opto-isolator. . . . . 38  
MEL11 Photodiode transistor. . . . . 35  
MEL31 Photo transistor. . . . . 26  
Neon 90V, wire-ended. . . . . 09  
ORP12 Light Dependent Register. . . . . 55

## ELECTROLYTIC

1/63 05 10/16 05  
2/63 05 22/16 05  
4/763 06 33/16 05  
10/63 07 47/16 06  
47/63 12 220/16 11  
22/25 08 470/16 14  
47/25 10 1000/16 20  
100/25 14 470/10 08  
220/25 14 1000/10 08  
470/25 24 1000/10 08  
1000/25 34 220/10 12  
2200/25 40

**Tantalum (Bead)**

0.1/35 09 10/25 20  
0.2/25 09 22/10 20  
0.4/35 09 20 20  
1.0/35 09 33/6 20  
7.7/25 10 47/6 3 27  
4.7/25 14 100/3 27

**VOLTAGE REGULATORS**

78L 100mA Positive 5, 12, 15V. . . . . 26  
79L 100mA Negative 5, 12, 15V. . . . . 60  
78 Series 1A positive 5, 12, 15V. . . . . 52  
79 Series 1A negative 5V. . . . . 35  
LM317T 1.2-3.7V adjustable 1.5A 1.80

## REMOTE CONTROL COMPONENTS

If you can design your own system, we stock a wide range of remote control components at very competitive prices.

LD271 IR Emitting Diode. . . . . 38  
SF205 Photo diode Detector. . . . . 70  
SL480 IC Pulse Amp. . . . . 1.80  
SL490 32 Command Encoder/Transmitter. . . . . 2.40  
ML927 10-channel receiver + 3 analogue outputs. . . . . 4.20

ML924 Programmable RC Receiver. . . . . 1.95  
ML925 A decoder designed for modularity control, providing a 2-speed drive motor and three position latched steering system or a vehicle with momentary action steering and a third motor, eg gun turret, switch, etc. Outputs also available for other facilities such as horn, turn indicators, headlights, etc. £2.10  
ML926 16-channel receiver, 4 momentary binary outputs. . . . . 1.40  
ML927 16-channel receiver, 4 momentary binary outputs. . . . . 1.40  
ML928 16-channel receiver, 4 latched binary outputs. . . . . 1.40  
ML929 16-channel receiver, 4 latched binary outputs. . . . . 1.40  
Chip-on plastic reflector for IR LEDs, increases range. . . . . .20

We have compiled a booklet on remote control, containing circuits, hints, data sheets and details of our remote control kits and components. So don't control yourself! - Send us 30p and a stamped addressed envelope for your copy TODAY!

## TRANSISTORS

BC108 npn .08 BC137 npn .13  
BC109 npn .15 RFV56 npn .20  
BC182 npn .08 TP131A npn .40  
BC183 npn .08 TP132A npn .40  
BC212 npn .09 2N1055 .45  
BC212L npn .09 2N1442 115W .90  
140V .140  
BC237 npn .12 2N3819 Nch fet .20

**V MOS Power Fets**  
VN10KM 0.5A/60V .52  
VN66AF 2A/60V .88

## DIODES & RECTIFIERS

1N4001 1A/50V. . . . . 04  
1N4004 1A/400V. . . . . 07  
1N4007 1A/1000V. . . . . 06  
1N4148 Si Diode 75mA/75V. . . . . 02  
1N5401 3A/50V. . . . . 10  
1N5404 3A/400V. . . . . 10  
OA9 Ge Diode 20mA/100V. . . . . 07

W05 1A/50V Bridge. . . . . 19  
W04 1A/400V Bridge. . . . . 22  
3A/50V Bridge. . . . . 38  
2A/400V Bridge. . . . . 58

**Zener Diodes**  
400mw 3.3V, 3.9, 4.3, 4.7, 5.1, 5.6, 6.2, 6.8, 7.5, 8.2, 9.1, 10, 12, 15, 18, 24, 27V. . . . . 08  
1.3W 7.5V, 8.2, 9.1, 10, 12, 15, 18, 24, 27V. . . . . 10

## RESISTORS

1/4W 5% E12 Series 10 ohm-10 Mohm Per pack of 10  
10 packs 110 values. . . . . 10

**Presets**

100 ohm h .08 47K h/v .08  
470 ohm h .08 100 h .08  
1K ohm h .08 470K h/v .08  
4.7K ohm h .08 1 Mohm v .08  
10 Kohm/h v .08  
22 Kohm v .08

**POTENTIOMETERS**

1K, 4.7K, 10K, 22K, 47K 100K, 470K. . . . . 30  
1M, 2.2M. . . . . 30  
Log No Switch 10K. . . . . 30

With DPST Switch  
Lin 2.5K, 5K, 10K, 100K, 250K. . . . . 60  
Log 5K, 10K, 50K, 100K, 500K. . . . . 60

Dual Gang  
Lin 1K, 10K, 100K. . . . . 60  
Log 5K, 10K. . . . . 60

## BOXES

Boxes with lid, ABS Black  
B1 75 x 56 x 35mm .88  
B2 95 x 71 x 35mm .85  
B3 115 x 95 x 37mm .95  
B4 150 x 100 x 60mm .110  
Porting Boxes (Grey)  
PB1 28 x 48 x 23mm .18  
PB2 38 x 51 x 25mm .34  
PB3 60 x 80 x 43mm .220  
Dipole Enclosure. . . . . 1.75  
Hand held control box with battery compartment ideal for remote control transmitter. (MK8) Colour Black. . . . . 3.80  
Mounting case for housing power supplies for calculators, radios, etc. Plug into 13A mains socket Colour Black  
MPI 51 72x58mm. . . . . 1.20  
MP2 56 5.92x72.5 1.50

**IC SOCKETS**

Low Profile  
Tape & Scribe etc.  
8 pin .08 22 pin .18  
14 pin .12 24 pin .20  
16 pin .14 28 pin .25  
18 pin .17 40 pin .36  
16 pin d.i.l. Plug  
Solderless Pins per 100 .50

**MINI KITS**

MK1 Temperature Controller/Thermostat. . . . . £2.60  
Uses LM3911 IC to sense temperature 180°C max and triac to switch heater. 1 KW E4  
MK2 Solid State Relay. . . . . £4.50  
Ideal for switching motors, lights, heaters, etc from logic. Opto-isolated with zero voltage switching. Supplied without triac.  
MK3 Bar/Graph Display. . . . . £2.60  
Displays an analogue voltage on a linear 10 element LED display as a bar or single dot. Ideal for thermometers, level indicators, etc. May be latched to obtain 20 to 100 element displays. Requires 5.70V supply.  
MK4 Precision Temperature Controller. . . . . £4.50  
Based on the ST 4411 Zero voltage switch, this kit may be wired to form a "burnt live" power controller enabling the temperature of an enclosure to be maintained to within 0.5°C. Max load 3 KW. . . . . £5.55

MKS Mains Timer  
Based on the ZN 1034E Timer IC this kit will switch a mains load on for 60% of a preset time from 20 minutes to 35 hours. Lower duty cycle periods may be required by minor component change. Maximum load 1 KW. . . . . £4.50

## 74 LS TTL

LS00 .12 LS14 .48 LS42 .40  
LS01 .12 LS15 .15 LS47 .42  
LS02 .13 LS20 .14 LS51 .15  
LSB3 .13 LS21 .15 LS54 .15  
LS04 .14 LS22 .15 LS55 .15  
LS05 .15 LS26 .18 LS73 .20  
LS08 .15 LS27 .15 LS74 .18  
LS09 .15 LS30 .14 LS75 .27  
LS10 .14 LS32 .15 LS76 .21  
LS11 .15 LS37 .17 LS85 .64  
LS12 .15 LS38 .16 LS86 .18  
LS13 .27 LS40 .14 LS90 .32

## TRIACS

400V Plastic Case (18x8x5) 3A TIC206D .80  
BA TIC226D .58  
12A TIC236D .85  
16A TIC246D .90  
25A TIC263D 1.00

6A with trigger O400B1 .85  
6A isolated triac TXAL226B .16  
Disc  
Opto-isolated triac MOC3020 0.1A / 400V 110p .10

## CMOS

4000 .14 4026 1.05 4093 .45  
4027 .40 4051 .24  
4001 .14 4028 .50 4511 .85  
4002 .14 4040 .68 4514 1.80  
4007 .14 4049 .30  
4011 .15 4050 .30  
4012 .17 4050 .30  
4013 .35 4060 .90  
4015 .70 4069 .18  
4016 .30 4070 .24  
4017 .65 4071 .22  
4019 .38 4072 .24  
4023 .22 4081 .22  
4025 .18 4043 .58

AND MANY MORE ITEMS INC PLUGS & SOCKETS, TRANSFORMERS, SPEAKERS, RELAYS, SWITCHES ETC. FOR PRICE LIST SEND SAE.

# TK ELECTRONICS

11 Boston Road London W7 3SJ Telephone: 01 579 9794/2842

# SOUND EFFECTS 1: BOMB DROP

One of the attractions of the more sophisticated video games seen in 'fun' arcades these days is the realistic array of sound effects that go with the action — gunshots, bomb whistles and explosions, etc. Make some yourself with just one IC. Design by Phil Wait.

Those 'cannon shots' and explosions that go with the popular 'Space Invaders' video games and its variants add a measure of interest, feedback and stimulation to the action in which you participate on screen. Those sounds are electronically synthesised — that is, they consist of a complex mixture of waveforms that make up the required sound.

A 'bomb drop and explosion' is a remarkably complex sound when analysed carefully. Looking at it simply, there is a descending tone followed by a burst of noise that dies away in intensity. The descending tone starts at quite a high pitch and is not a 'pure' tone (ie a sine wave). The explosion is a burst of noise that commences suddenly and dies away slowly in a recognisable way (usually exponentially). While it is possible to electronically produce very nearly an exact replica of a bomb drop and explosion, some compromises are acceptable to reduce the complexity and cost of the task and yet produce a recognisable replica of the sound.

To produce such sound using conventional components — transistors, diodes, op-amps, resistors and capacitors — would require a whole legion of components. Fortunately, the IC manufacturers can come to our rescue here and much of the circuitry can be incorporated into a complex integrated circuit requiring the addition of a minimum of external components and the appropriate interconnections to synthesise the required sound. Generating a wide variety of sounds fortunately requires only a limited number of functional blocks, such as: a noise generator, voltage controlled oscillators, multivibrators, envelope generators (a sort of modulator), mixers and amplifiers. Tim Orr discusses such circuitry elsewhere in this issue.

Texas Instruments, the giant US-based component and equipment

manufacturer, have designed a series of complex function ICs for various applications and among them is the SN76488 Complex Sound Generator. This chip contains both linear and digital circuitry and is intended for use in applications requiring audio feedback to the user — video games, pinball, alarms, toys, etc, or industrial indicators, feedback controls and the like. Power consumption is quite low, allowing battery operation, and only a single supply rail is required.

The SN76488 is contained in a 28-pin package and can be purchased for less than £5. It is quite a versatile chip, but we have chosen to describe how to obtain only two sound effects, these being a bomb drop and explosion, and a steam train and whistle. The former is described here; the latter appears on page 118.

## Construction

Both the projects described use the one PCB design. Only the required components are assembled into the board according to each overlay diagram to obtain the required sound generator. Naturally enough, the polarity of the IC should be noted as well as the polarity of electrolytic and tantalum capacitors used. Commence construction by assembling the passive components, followed by the IC. This is not a CMOS device and no special care is required, apart from being careful not to bend any pins under the device when inserting it. If you wish, a socket may be used for the IC. This way, you can assemble both projects and purchase only one IC, swapping between the boards as you need to use them!

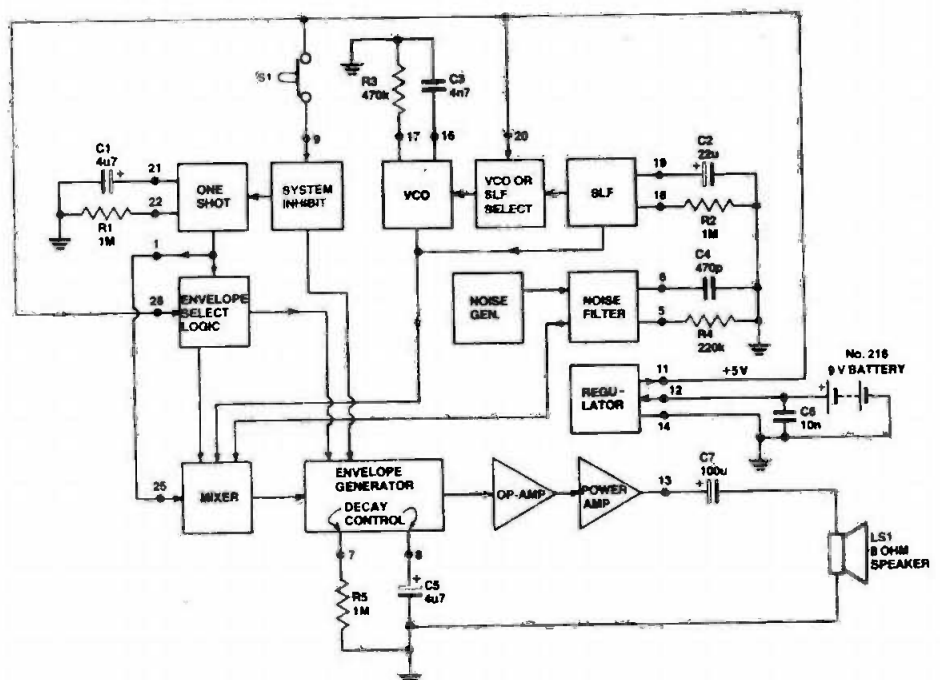


Fig. 1 Circuit diagram of the Bomb Drop and Explosion sound effects board.

Wiring to the switches, the speaker and the supply should be attached last.

The unit may be mounted in any convenient-sized box and the speaker mounted on the front. Alternatively, it may be wired into an existing piece of equipment. We'll have to leave these arrangements up to you.

## Projectile Project

This produces a 'bomb drop and explosion' sound at the press of a button. Alternatively, the push-button PB1 could be replaced by a pair of relay contacts operated by a piece of equipment or a transistor (emitter to pin 9, collector to other side of PB1) that is turned on by a logic high applied to its base via a resistor.

This project is one of the most complex, using almost every functional block within the SN76488. Varying R3 and C3 a little will vary the pitch range of the 'bomb drop' (descending whistle), while varying R4 or C4 a little will alter the characteristics of the explosion. Note that it is generally easier to 'fine tune' things by varying the resistor values. The duration of the event can be varied by changing the value of either C1 or R1 and the decay of the explosion can be changed by varying R5 (varying C5 produces quite gross changes in the decay period).

Watch that you insert the link on the PCB in this one, located at the 'notch' end of the IC.


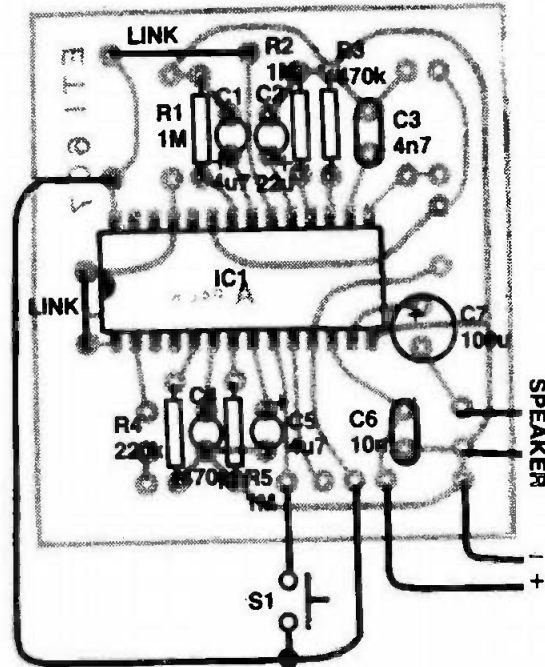


Fig. 2 Component overlay for the Bomb Drop board.

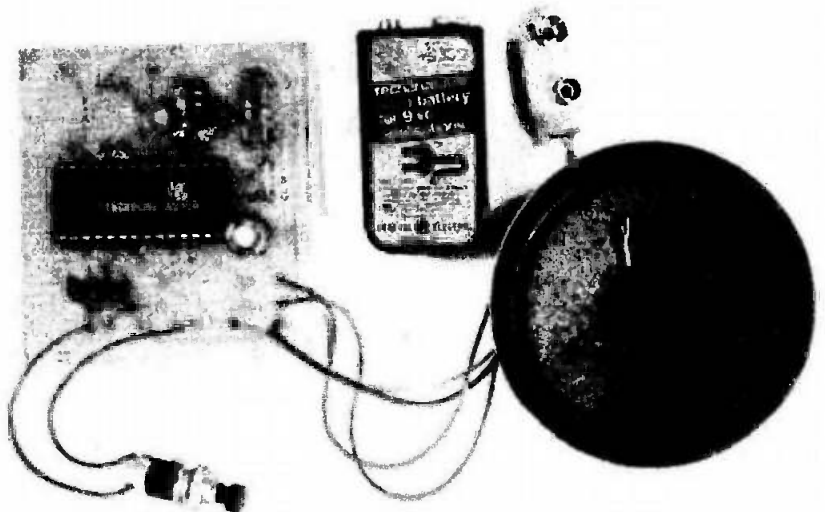

## PARTS LIST

### Resistors (all 1/4 W, 5%)

R1,2,5	1M0
R3	470k
R4	20k

### Capacitors

C1,5	4u7 16 V PCB electrolytic
C2	22u 16 V tantalum
C3	4n7 ceramic
C4	470p ceramic
C6	10n ceramic
C7	100u 16 V PCB electrolytic

### Semiconductors

IC1	SN76488 (see Buylines)
-----	------------------------

### Miscellaneous

PB1	SPST push-button switch
PCB (see Buylines);	50 mm diameter 8 ohm speaker; PP3 battery and clip.

## BUYLINES

Very few components and very few supply problems with this one. The SN76488 is an improved version of the Texas SN76477 and can be obtained from Technomatic. The PCB will cost you £1.80 from our PCB Service; see page 44 for details.

## HOW IT WORKS

This unit employs most of the function blocks in the SN76488. The SLF provides a linearly increasing voltage waveform, or ramp, to the VCO, taking several seconds for the ramp voltage to rise from zero to maximum value. The causes the VCO to produce a tone which 'glides' down in pitch, making the 'bomb drop' effect. The explosion is generated by the Noise Generator/Filter and the Envelope Generator. It starts with a burst of noise, which dies away in intensity exponentially in a few seconds.

The whole sequence is triggered by operating the pushbutton, PB1. This applies a high (+5 V) to the input of the System Inhibit block, pin 9. This in turn triggers the One Shot and the Envelope Generator. At the commencement of the One Shot timing period, the One Shot triggers the SLF H/L Sync, starting the SLF, and the VCO does its things. At the end of the One Shot timing period the Envelope Select Logic becomes operative, the SLF is disabled and the

Envelope Generator commences to do its thing. The Mixer selects the VCO output at the start of the One Shot timing period and the Noise Generator/Filter output at the end of the One Shot timing period. Thus the two sounds are switched through to the audio output stage in sequence, the Envelope Generator modifying the noise so that it dies away, the time it takes to do so being controlled by the time constant of R5, C5.

The starting pitch of the VCO is determined by R3 and C3, the rate of rise of the voltage ramp produced by the SLF is determined by C2 and R2, while the One Shot timing period is determined by the time constant of C1 and R1. The frequency characteristics of the broad-band noise produced by the Noise Generator are modified by R4 and C4 connected to the noise filter control pins (5 and 6).

Audio output is coupled to the loudspeaker via C7, a 100uF electrolytic capacitor.

THE 1982

# CASIO WORLD BEATERS

AND

**PRICE BEATERS**

BY TEMPUS

Our prices are the lowest authorised dealers are allowed to advertise; lower prices = no Casio guarantee (E&OE). Nevertheless we can beat any lower price by 5%\*. We have scanned last month's magazine for you and marked the lowest price we could find against a star ★.

### WATER RESISTANT WATCHES

With Alarm, Hourly Time Signal, Stopwatch and Calendar  
100 METRE WATER RESISTANT



**W-100**  
Resin case/strap  
£19.95



**W-150C**  
S/S case, resin strap  
£21.95



**W-150**  
All S/S  
£24.95

Time and auto calendar. Alarm and hourly chimes. Countdown alarm timer with repeat memory function. Professional 1/100 second stopwatch. Time is always on display, regardless of display mode. Amazing 5 year lithium battery life. Superior to the W-250.

### 50 METRE WATER RESISTANT



**AA-92W**  
(left)  
All S/S  
£25.95



**W-51**  
(right)  
All S/S  
£22.95

**AA-92W.** LCD Analog display of hours and minutes, with sync. digital seconds. Dual time. Digital display of time and calendar. Alarm, with "carousel" display. Countdown alarm timer with amazing "Starburst" display. Half hourly chimes. Long life lithium battery. **W-51.** The same module and functions as the W-150.



**W-20**  
Resin case/strap  
£12.95



**W-21**  
Resin S/S trim  
£14.95



**W-30**  
All S/S  
£19.95

12/24 hour time and auto calendar. Alarm and hourly chimes. Professional 1/100 second stopwatch to 12 hrs. Compact and slim cases, approx. 8mm thick. Lithium.

### OTHER MODELS



**CA-85**  
Resin  
Usually £19.95  
Price elsewhere  
★£18.95



**CA-901**  
Chrome  
Usually £29.95  
Price elsewhere  
★£27.95



**J-100**  
Resin  
£19.95

**CA 85/901.** Time and auto calendar. Calculator. Alarm and hourly chimes. Stopwatch. Dual time. **DIGITAL SPACE INVADER** game.

**J-100.** Similar to the CA-85 but without dual time and with a **JOGGING COMPUTER** instead of the game function.

**GM-10.** Alarm chrono with **SPACE INTERCEPTOR** game £19.95

**AA-85.** As AA-92W but in chrome, non W/R case £22.95

**F-82.** Alarm chronograph. Resin case and strap £10.95

**Ladies models**

**LM-3.** Melody alarm, stopwatch. Resin, S/S trim... £14.95

**LW-5.** Time/date/stopwatch. 50m W/R resin case £8.95

**LW-800C.** 6 digits. Time, date, 1/100 second stopwatch. £18.95

**100m Water Resistant S/S case with resin strap** £18.95

\*Providing the advertiser has stocks and we do not sell at a loss.

### AX-210. The world's most versatile watch?

Analog Display  
LC Display of hours and minutes  
Digital display

- Local time, 12 or 24 hour
- Full calendar display
- Dual time, 12 or 24 hour
- Alarm time display
- Countdown alarm timer with memory function.
- Professional 1/100 second stopwatch.

Hourly time signal. Daily alarm-electronic buzzer or 3 selectable melodies. Rapid forward/back setting 9.4 x 35.4 x 38mm.

Usual Price £29.95  
Lowest price elsewhere

★ £27.95



### SYMPHONIC ALARM CLOCK

MA-1  
£9.95

Mozart No. 40 or Buzzer.  
Hourly chimes.  
Snooze facility  
1 1/2 x 4 1/2 x 3 in.



### VIVID REALISM

Sound is the criterion when judging a musical instrument. Our CASIOTONE keyboards are out-selling all others because of their superb reproduction, quality and legendary reliability.

### GENERAL SPECIFICATION

All Casiotone keyboards (except VL-Tone) are polyphonic - up to 8 notes can be played simultaneously. They all have an integral amplifier and loudspeaker, plus an output jack for headphones and external amplifier or recorder.

### CALCULATORS

#### OUR BEST SELLING SCIENTIFIC

FX-3600P

10 digits, 61 scientific functions including Integrals and Regression analysis. Up to 38 program steps, 2 programs and 7 memories, all non-volatile. Wallet size. 1,300 hour battery.

Usual Price £22.95

Price elsewhere

★ £21.95



FX-3600P

FX-180P. Hand held version without hyperbolics £19.95




FX-180P

**FX-8100 Scientific with Clock, Alarms and Stopwatch**

8 digits, 49 scientific functions. Clock, hourly chimes, alarm. 2 countdown alarm timers. Auto calendar. 1/100 second pro stopwatch. Complete with wallet.

Usual Price £24.95

Price elsewhere ★£23.95

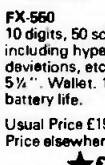

FX-8100

**FX-560**  
10 digits, 50 scientific functions including hyperbolics, standard deviations, etc. 5/16 x 2 7/8 x 5 1/2". Wallet. 1,300 hour lithium battery life.

Usual Price £19.95

Price elsewhere


★ £18.95

FX-5 £8.95; FX-7 £10.95; FX-82 £12.95; FX-100 £18.95



FX-560

### CALCULATING ALARM CLOCKS

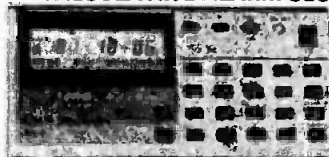

FT-7

FT-7 Fortune Teller and Matchmaker

Clock, alarm, hourly chimes, calendar. Predictions of individual fortunes (health, gambling/investment, business and love), or the compatibility between two persons on any given day. Usual Price £16.95

Price elsewhere ★ £16.95

BG-15. Boxing game, alarm clock, calculator. Usual Price £16.95. Price elsewhere £15.95

ML-76. 12 melody alarms, clock, calculator £14.95

ML-120. Wallet version of above £14.95

ML-2000 £22.95. UC-3000 £27.95. UC-360/365 £19.95

### BASIC CALCULATORS

MG-77 Compendium of Games

A game of chance, a game to test your reactions and a game to tax your intelligence. Plus a very useful clock as well and, of course, a wallet sized calculator.

ONLY £14.95



SL-801 Solar £8.95. HQ-25 Time calculations £9.95.

### CT-403



RRP £325  
ONLY £275.00

25 instruments over 4 octaves. Four voice memory function with push button selection. Vibrato and sustain switches. 16 rhythm accompaniments with fill-in variation Casio Auto Chord for one finger or auto playing of major, minor and 7th chords with bass. Ten functional controls including pitch. AC only. 4 3/8 x 30 3/8 x 11 3/4". Weight 17.6lbs.

### CT-202



RRP £325  
ONLY £275

"Son of success... The two harpsichords demonstrate the Casiotone's talent for sparkling crystal clear tones. Even more impressive is the clav..."

(Melody Maker)

49 instruments over 4 octaves. 4 voice memory function with push button selection. 3 vibrato settings and sustain. Pitch control. O/P jacks. AC only. 3 1/2 x 34 1/2 x 11 1/2". 16.8lbs.

### CT-101



RRP £255  
ONLY £225

25 instruments over 4 octaves. Four voice memory function with push button selection. Built in vibrato and sustain. Pitch control. AC only. 30 3/8 x 11 3/4 x 4 5/8". Weight 16.8lbs.

### VL-TONE (VL-1) Monophonic



RRP £39.95  
ONLY £35.95

VL-1 records and plays back up to 100 notes as a melody, with memory break-in. ONE KEY PLAY or AUTO PLAY of 5 instruments, or create your own unique sounds with A.D.S.R. 10 built-in AUTO RHYTHMS and TEMPO CONTROL. LCD digital readout of notes and tempo. Also a calculator. Battery powered with memory retention. With song book. 1 1/2 x 11 1/2 x 3".

DELIVERY NORMALLY BY RETURN OF POST

Price includes VAT and P&P. Send cheques, PO, or phone your ACCESS, VISA or B'CARD number to:

# TEMPUS

LEADING CASIO SPECIALISTS  
Dept. ET1  
38 Burleigh Street, Cambridge CBI IDG  
Telephone: 0223 312866

CATALOGUE  
ON REQUEST  
15 1/2 p stamp  
appreciated

# THE SENSATION OF THE JAPANESE MUSIC FAIR

Designed by a genius. Controlled by a computer. Programmed by a laser. Played by amateurs professionally and by professionals superbly.

## THE NEW CASIOTONE 701

"... what is going to become THE instrument of 1982 ... probably the best instructive keyboard I have come across. But it is also a top line musical instrument capable of satisfying even the most proficient musician ... I suggest you place your orders now." (Keyboard & Music Player).

"... opens up home music making for all the family ... one of the most advanced music teaching aids so far developed ... this instrument is going to be one of the biggest sellers of 1982." (Electronics & Music Maker).



### Complete Programmable Polyphonic Keyboard (RRP £555) ONLY £495


- \* Input an entire piece of music, specially scored in bar code and read by a light pen attached to the instrument.
- \* Alternatively, program your own melodies (max. 345 steps), chords (max. 201 steps) and tempo, via the keyboard, into the extensive memory, (up to 5 minutes playing or more) with full editing facilities.
- \* 3-WAY PLAYBACK.
  1. Automatic playback of the entire piece: melody, chord, bass and rhythm with arpeggio. Follow the melody as it plays via lamps above each individual key.
  2. Manual melody playing, guided by the keyboard lamps, with automatic bass and rhythm accompaniment.
- \* ONE KEY PLAY facility, allows the melody line to be played, simply by stroking one key. Non-players can become Instant Musicians!
- \* The 5 octave, 8 note polyphonic keyboard can be split into 2 & 3 octaves and a different voice can be selected for the accompaniment.
- \* 20 "breathakingly clear and bright" pre-set instruments and voices.
- \* 3-way chord section: — Fingered, Memory and Casiochord auto accompaniment.
- \* 16 rhythm accompaniments with "fill in" variation and two percussion effect buttons. Start/Stop, Synchro, Tempo and Balance controls. Variable Vibrato and Sustain. I/p & o/p jacks. Integral amplifier/speaker. Music book. AC only. Dims: 5 x 37 3/4 x 13 4/16". Optional extras: Foot pedals. Hard case.

**FREE**

CREDIT. 0% interest, 1/3 deposit, 12 monthly repayments. (Not MT-31, MT-40 or VL-1), or reduced rates for longer period. INTEREST (0%) on ACCESS, B'CARD or VISA for first 9 months, for any keyboard purchase over £90.

## NEW PORTABLE KEYBOARDS


### CASIOTONE MT-40

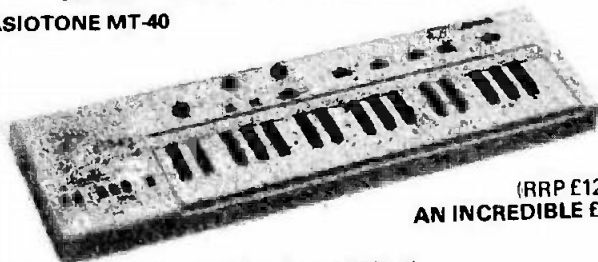

(RRP £125)  
AN INCREDIBLE £99

- \* 8-note polyphonic playing of this 37 key, 3 octave keyboard.
- \* 15 key bass keyboard with automatic synchronised bass function.
- \* 22 lively and realistic built-in instrument sounds and voices.
- \* 6 built-in auto rhythms, with dual "Fill-in" rhythmic interludes.
- \* Sustain, Vibrato and Pitch controls. Line out and Headphone jacks.
- \* Integral amplifier and speaker. Battery powered, or optional AC adaptor. Dims: 61.6 x 584 x 178mm (2 7/16" x 23" x 7"). Weight: 2.2kg (4.9lb).

### CASIOTONE MT-31

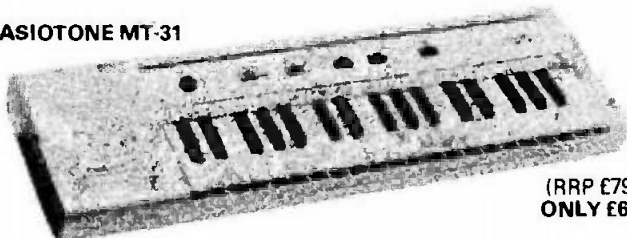


(RRP £79)  
ONLY £69

"... basically a revision of the MT-30 (one of my all time favourite electronic keyboards)." Electronics & Music Maker. Similar to the MT-40 but without the rhythm box, bass and auto functions. Dimensions: As MT-40. Weight: 2.0kg (4.4lb) including batteries.

## £100 COMPUTER

"Can do the job of a micro costing four times as much!"  
Personal Computer World

### CASIO FX-702P POCKET COMPUTER

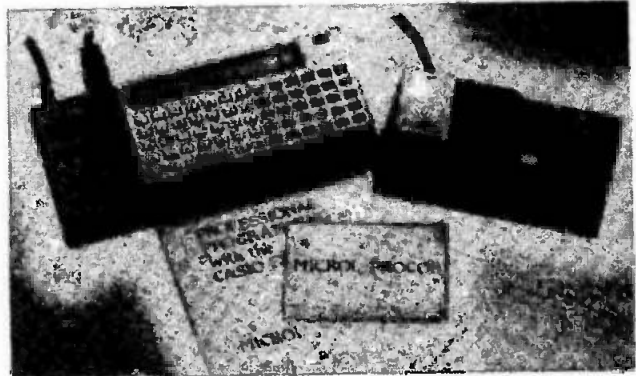

ONLY £99.95 Manufacturer's price reduction 1/2/82)

Plus FREE MICROL Professional Programming Pack (RRP £9.95)  
Or we will beat any lower advertised price by 5%

#### Eat your hearts out, H-P, Sharp and Texas!

The Casio FX-702P features: The biggest program storage capacity (up to 1680 steps), the biggest data storage capacity (up to 226 memories), and the widest range of math, science and statistics functions (55 in all, including Regression and Correlation), the most powerful English-like BASIC program-writing language and the fastest operation, for results without waiting! Subroutines: 10 levels, FOR: NEXT looping; 8 levels. Comprehensive edit, debug and trace modes. 240 hours battery life. 17 x 165 x 82mm.

FA-2. Cassette adaptor for bulk storage of programs and data, with powerful file name and remote control options. ONLY £19.95.

FP-10. Permanent hard copy printer; full 20 character line width, fast 40 character per second print speed. 2,600 lines per roll. (Low cost replacement rolls, £2.50 for five). 6,000 to 9,600 lines battery life. Rechargeable battery pack, NP-4M, prints 13,000 lines (£6.90). Mains adaptor, AD-4150, £5.

FP-10 Printer ONLY £44.95

Plus FREE Pack worth £5, or we will beat any lower price by 5%


#### SYSTEM PRICES — Save up to £50 on RRP

PACK A: FX-702P + MICROL Professional Programming Pack	£99.95
PACK B: FX-702P + FA-2cassette interface + PPP + PROCOS	£139.95
PACK C: FX-702P + FP-702P + FP-10 Printer + FA-2 + PPP + PROCOS	£179.95

#### MICROL PROCOS for the 702P. Exclusive to TEMPUS

Now you can create powerful, reliable programs in just minutes with this advanced integrated operating system, even if you have never programmed a computer before! "Visicalc-type" system answers "what if" questions and analyses trends. On ready-to-run cassette, with user manual.
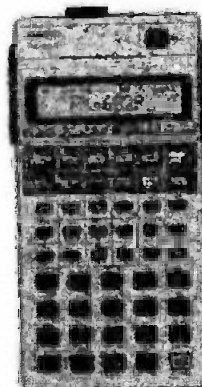
#### CASIO FX-602P The World's Fastest Programmable?



- \* LCD alpha/numeric (dot matrix) scrolling display.
- \* Variable input from 32 program steps with 88 memories, to 512 steps with 22 memories.
- \* Memory and program retention when switched off.
- \* Up to 10 pairs unconditional jumps (GOTO).
- \* Conditional jumps and count jumps. Indirect addressing. Manual jump.
- \* Up to 9 subroutines, up to 9 levels.
- \* 50 scientific functions, all usable in programs.
- \* PAM (Algebraic) with 33 brackets at 11 levels.
- \* Program and data storage on cassette tape using optional FA-2 remote control adaptor, £19.95.
- \* Compatible with the FX-501P and FX-502P.
- \* 9.6 x 71 x 141.2mm. 100g.

ONLY £74.95

Plus FREE MICROL Professional Programming Pack (RRP £9.95)  
Or we will beat any lower advertised price by 5%

# TEMPUS

# READ/WRITE

Dear Mr. Ron Harris Sir,

We seem to have been hearing quite a bit about System A recently; technically it looks a rather nice amplifier. However, it's difficult to tell how good commercially-produced units are with only limited information available about them. So what about the other end of the problem — what does System A sound like, compared with other amplifiers? Unfortunately, I can't see any of the hi-fi mags doing a review of it, so — how about you doing one (totally unbiased, of course) please, pretty please? Come on, put your reputation on the line!

Yours grovellingly,  
M.R. Barrett,  
Hove.

Certainly not. Someone might chop it off!

System A has a comparable sound to any of the more highly regarded

commercial units. Listening tests we have conducted over the months since the creature's completion, have shown it (the power amps) to have a more detailed and open midrange/top than ANY we have compared it to. The top commercial boxes — Threshold, Monogram, Carver, etc can exhibit a better bass control than the System A however, but as to whether or not that is important for your particular application (ie loudspeaker), I could not say (because you haven't told me what speakers you've got, have you?).


Anyone contemplating building a System A is welcome to write to us for advice on speaker matching.

Dear Sir,

I read with interest the articles in the July and August editions of ETI describing the construction of the System A Audio Amplifier, as I have been on the lookout for a high-quality

class A amplifier design for some time. My particular interest in class A stems from the fact that I own a pair of Lowther loudspeakers — these units are almost ridiculously sensitive, requiring only some 10 W or so of input to produce the equivalent sound output of a conventional 100 W system. Given this sensitivity, most high quality class AB amps are only ticking over when driving a pair of Lowthers, and hence are working at the highest distortion end of their operating range. Hence the interest in class A, where no penalty is paid for operating the amplifier at low levels of power output. However, before going ahead and building the System A, I would like the answers to a couple of questions. Firstly, the July article heralds System A as "quite simply the best, designed to out-perform even commercial equipment." There is, however, no objective assessment or comparison to back up this claim, and before laying out the not insignificant construction cost, I would like to see the amplifier reviewed, preferably alongside its "competition" in the commercial amplifier field. Is this a possibility?

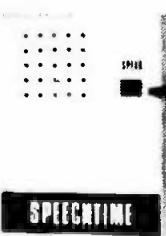Secondly, the high power output of the System A seems more than a slight degree of overkill in the context of my



**If you haven't bought me yet — it's high 'time' You did! . . . I'm only £24.50**

**SPEECHTIME**

Speech Speech Systems Ltd., P.O. Box 111, Andover, Hants. SP10 3NM

It's true! Continuing our special offer (while stocks last) means there's still nearly £5.00 off the price of 'Speech-time' — the first ever easy-to-build speaking clock kit. 'Speechtime's combination of electronics and quartz technology plus clear instruction manual make it fun to build and fun to own — equally suitable for beginner or expert.

Speechtime also makes a great gift to build for someone else. Look at these 'plus' features:

- Accurate to a minute a year
- Adjustable voice pitch
- Pocket size — approx. 5in. x 2½in. x 1in.
- Grained stainless-steel case
- Useful in the home or office

**SPECIAL OFFER PRICE**  
£24.50  
incl. of VAT and P&P

**Silicon Speech Systems**  
(A Powertran Subsidiary)

**PORTWAY INDUSTRIAL ESTATE, ANDOVER, HANTS., SP10 3NM**

**EASY ORDERING BY TELEPHONE**  
— RING ANDOVER (0264) 64455  
AND GIVE YOUR ACCESS OR BARCLAYCARD NUMBER




 <p><b>RELAYS BY KEYSWITCH</b> 10A 2-Pole C/O 240V Coil <b>ONLY 80p</b> 2 for £1.50 5 for £3.50</p>	<p><b>LOW-COST, RUGGED TEMPERATURE CONTROL</b></p>  <p><b>HIGH QUALITY TEMP. GAUGE 0° - 120°C</b> Remote sensor on 38" capillary, panel mounting dial 55mm. dia. <b>ONLY £1.85</b></p>
<p><b>RUBBER GROMMETS ¼" 10 for 20p</b> <b>STRAIN RELIEF SLEEVE 10 for 30p</b></p>	<p><b>USED EQUIPMENT</b></p> <p>Ex-P.O. Multimeters in leather case. AC/DC Volts, DC current, ohms. Absolute Bargain <b>£5</b></p>
<p>Recent Style P.O. Telephones <b>£4.75 + £1.80 P&amp;P</b> 2 for <b>£9 + £2.50</b>. 5 for <b>£20 + £5</b></p>	<p><b>16A 240V RANCO THERMOSTAT</b> Wide control range (low room temp. to over boiling point) Sensor on 22" capillary. <b>£2.30</b>, including control knob</p> <p><b>RANCO THERMAL CUT-OUT 100°C</b> 15A 240V. Sensing coil on 41in. capillary panel mounting with reset button <b>£1.20</b></p>
<p>Robust Metal Cabinets approx. 12" x 6" x 5" <b>£3.50 + £1.80 P&amp;P</b></p>	<p><b>BUY ONE EACH OF ABOVE FOR £4.85</b></p> <p><b>LATCHING RELAY WITH MANUAL RESET</b></p>  <p><b>3 POLES BREAK WHEN ENERGISED ONLY £1.00</b></p>
<p>10 Assorted P.O. Relays <b>£3.00 + £1.50 P&amp;P</b></p>	<p>Hubber Cabinet Feet 4 lge &amp; 4 small for 10p High quality plated metal terminal posts only 20p</p>
<p>5 Digit Counters 48V coil. Non resetable <b>75p</b></p>	<p>Belling Lee 4mm plugs with circular spring contact 10p</p>
<p><b>FREE</b> on request — Leaflet 'D.J.Y. Telephone Systems and Automatic Exchange Design'.</p>	<p><b>VERY SPECIAL OFFERS</b> Rotary Wafer switches 5p 8W — <b>£1.10</b> 2p 9W — 50p Spring-return lever 5p switch SDT 50p Tag-ended electrolytic 4700. 63V 75p</p>
 <p><b>L.E.M. SERVICES</b> 239 RUGBY ROAD LEAMINGTON SPA CV32 6DY WARWICKSHIRE</p> <p>TEL: 0926 30622 FOR QUANTITY DISCOUNTS ETC. ALL ITEMS — MONEY BACK IF NOT DELIGHTED.</p>	<p><b>ADD 50p P&amp;P ORDERS OVER £7.50 POST FREE</b> unless stated otherwise</p>

Lowthers. Is it reasonable, therefore, to construct a lower power version of the power amp section? If so, what modifications should be made to the present design?  
Yours sincerely,  
T. Jeffree,  
Milton Keynes

Taking the two points you raise, in order; first we feel it is inappropriate for us to review our own product against anyone else's. (Would you believe us anyway?) 'Objective' would not be an appropriate word to apply to such a test.

System A has aroused a great deal of interest and we know that a large number of sets have been completed. There is probably, however, a larger number of people still who would tackle the project, if only they could get to hear one first! Accordingly any owners of a System A who would be prepared to let a fellow ETI reader have a listen, can write to us and we'll run the letters herein. Secondly the high power output of the amp will not be wasted, even on your Lowthers, it will simply provide you with more headroom — and hence a cleaner sound with better bass output on transients.

Dear Mr Harris,

I am writing for advice on the purchase of an amplifier and speakers combination. I list my present system below:

Home-brew 10 W amp  
Ferguson (?) 3-way speakers  
(actually 2-way, 3-cone)  
Realistic 31-987 Graphic Equaliser  
Hitachi D-225 Cassette Deck  
Pioneer PL-300 turntable (the latest addition!)

The amplifier now ceases to be of any great use in terms of power, although quality is more than adequate (based on Bi-Pak AL30A). I have considered NAD3020, Pioneer SA410, and also the "Audiophile" amp, the MOSFET amps from JW Rimmer, and the Linsley-Hood kit from Powertran. The last three give me extra headroom, and I would like to feed them into AR18 speakers from Acoustic Research.

Basically, I would like your opinion on the Linsley Hood 75 De Luxe/AR18 combination, plus any comments on the other "possibles".

Also, the Pioneer PL300 I have just bought is certainly the best turntable I

have heard at the price (£79.95), and I can't help wondering why it gets so little attention. Perhaps you can fill me in?

Thank you for your valuable time,  
D. Cray,  
Ilford, Essex

PS When is Felicity Kendall to return to our screens?

The AR18 is a fine unit and if you like the sound of them, go ahead and buy yourself a pair. You haven't named your cartridge so I've no idea if it matches.

Ditch the equaliser, with decent speakers and amp, you won't need it!

As to amplifiers, from the units you mention the Linsley Hood power amps are the best bet, but the preamp of that unit is getting a bit long in the tooth now, although the sound quality is still very good by any standards. Have a listen to the Crimson CK1010/1100 set-up before you decide, however, as it is in your price range and offers a high-quality alternative.

The Pioneer PL300 I have not been able to listen to at any length and must thus refrain from commenting upon!

## EXCITING OFFERS!

### DIGITAL VOLTMETER MODULE

Fully built & tested



- Positive and negative voltages with an FSD of 999mV which is easily extended.
- Requires only single supply 7 - 12V.
- High overall accuracy  $\pm 0.1\%$  + 1 digit.
- Large bright 0.43" (11mm) LED displays.
- Supplied with full data and applications information.

ONLY £11.95 +VAT

Using this fully built and calibrated module as a basis now means that you can easily build a wide range of accurate equipment such as multimeters, thermometers, battery indicators, etc. etc. at a fraction of the cost of ready-made equipment. Full details are supplied with each module showing how to easily extend the voltage range and measure current, resistance and temperature. Fully guaranteed, the unit has been supplied to electricity authorities, Government departments, universities, the P.O. and many companies.

### Temperature Measurement

£2.15 +VAT

An easily constructed kit using an I.C. probe providing a linear output of 10mV/°C over the temperature range from -10°C to +100°C. The unit is ideal for use in conjunction with the above DVM module providing an accurate digital thermometer suitable for a wide range of applications.

### Power Supply

£4.95 +VAT

This fully built mains power supply provides two stabilised isolated outputs of 9V providing current levels of up to 250mA each. The unit is ideally suited for powering the DVM and the Temperature Measurement module.

### ULTRASONIC ALARM MODULE

Fully built & tested

ONLY £10.95 +VAT

### Power Supply & Relay Unit

£3.95 +VAT

Incorporating a stabilised 12V supply and a s.p.c.o. relay with 3A contacts, this unit is designed to operate in conjunction with the above ultrasonic unit. Fully built and tested, its compact size makes it ideal for constructing the smallest of units.



Range adjustable from 5' - 25'

A really effective fully built module which contains both ultrasonic transmitter and receiver, together with the necessary circuitry for providing the appropriate delays and false alarm suppression. Using this module with a suitable 12V power supply and relay unit such as that shown, a really effective though inexpensive intruder alarm may be constructed. The module, which is supplied with a comprehensive data sheet, is easily mounted in a wide range of enclosures. A ready drilled case, together with all the necessary hardware, is available below.

### Siren Module

£2.57 +VAT

Producing a very loud and penetrating wailing sound, this module operates from 9 - 15V. Capable of driving one or two 8 ohm speakers. Suitable horn speakers available at £4.30 each +VAT.

### Hardware Kit

£3.95 +VAT

A suitable ready drilled case together with the various mounting pillars, nuts and bolts, and including a rotary switch and 2mm sockets designed to house the ultrasonic alarm module, together with its associated power supply. Size 153mm x 120mm x 45mm.

In addition to the above a wide range of competitively priced electronic components is stocked. Please telephone your specific requirements.



## RISCOMP LIMITED

Dept. E.T.I.5.  
21 Duke Street,  
Princes Risborough, Bucks.  
Tel: Princes Risborough (084 44) 6326

- V.A.T. must be added on all items.
- Shop hours 9 - 5.30 (Weds. 9 - 1)
- ex-stock delivery on all items.
- Units on demonstration, callers welcome.
- Post and packing charge 50p per order.
- S.A.E. with all enquiries please.

# TECHNOMATIC

"TECHNOMATIC" compliments "ETI" on its 10th anniversary and takes this opportunity to announce some facts about "TECHNOMATIC". ETI readers and our customers, have seen, over a number of years, our advertisements containing product listings etc., but no details on our policies or capabilities. We now rectify this situation for sake of completeness.

Our aim is to supply prime grade components which are fully guaranteed and backed by manufacturer/distributor. We stress the fact that we are totally quality and value conscious and handle components from major manufacturers.

Our volume buying enables us to obtain preferential prices and the savings are passed onto the customers in the form of low prices — sometimes lower than trade!

As a matter of routine, we provide "by return of post" service, and all orders received by 3.30 pm are despatched on the same day. Our in depth stock holdings enable us to do this. Why not test us on your next order?

*And some more facts:*

## LONDON'S No 1

We stock the widest range  
of micro processors in  
LONDON

We are fully authorised distributors to the hobbyist market for TEXAS INSTRUMENTS, World's No 1 semi conductor manufacturer.

We are a major distributor of ACORN COMPUTERS who manufacture ATOM, ECONET and BBC microcomputers. Other dealerships include VERO, OK Machine Tool, GSC, ILP, and AP PRODUCTS.

We carry large stocks of MICROS, MEMORIES, TTLs, CMOS, LINEARS, OPTO-Devices, TRANSISTORS and other semi-conductors. We can normally offer ex-stock deliveries to volume buyers at special prices.

Our connector range includes: TI Sockets, IDC connectors, Euro connectors, Min-D connectors, Juniper Leads and a variety of Edge connectors.

We also carry in stock EPROM programming equipment including Softys, ganged programmers, erasers etc.

***GET THE BEST VALUE FOR YOUR MONEY***

## TECHNOMATIC LIMITED

15/17 BURNLEY ROAD  
LONDON NW10 1ED  
Tel 01-452 1500/450 6597  
Telex 922800

305 EDGEWARE ROAD  
LONDON W2  
Tel 01-723 0233

### LONDON'S No 1 RETAIL COMPONENT OUTLET




# INSTRUMENT PROBE

This probe will allow you to make CRO or frequency meter/timer measurements on high impedance circuits with waveforms having rise times as fast as three or four nanoseconds. Cost is well below commercial equivalents. Design by Jonathan Scott.

Most readers would be aware that, when taking a measurement on electronic circuitry, the input impedance of the measuring instrument must be much greater than the impedance of the circuit to which it is attached, otherwise the accuracy of the measurement suffers. The input impedance of the majority of oscilloscopes is generally 1M $\Omega$  with a parallel capacitance of between 20pF and 40pF. For a wide variety of applications this is perfectly adequate and will suffice for measurements of frequencies up to 5 MHz or so. The input impedance of the CRO falls with increasing frequency owing to the falling reactance of the input capacitance. For example, a capacitance of 30pF — which may be made up of direct input capacitance plus cable capacitance — has a reactance of only 500 ohms at 10 MHz. The input capacitance also affects the rise time of the input — that is, the speed at which a 'step' input will rise from the 10% amplitude value to the 90% amplitude value.

The input impedance of an oscilloscope can be effectively raised, and the capacitance decreased, by using a 'stepdown' probe. For example, a 'x10' probe will generally have an input impedance of 10M $\Omega$  and a parallel capacitance of between 5pF and 15pF. While this improves the input impedance there are two trade-offs. Firstly, unless elaborate (and expensive) compensation is employed, the rise time is degraded, and secondly, maximum sensitivity is decreased by a factor of 10. As Murphy's law would have it, your CRO will run out of grunt just when you need it most.

Taking the situation with digital counter/timers, we find similar problems. Those that operate beyond 30 MHz or 50 MHz generally employ a prescaler with an input impedance of 50 ohms — which is perfectly all right if you're working on low impedance circuits and/or with high signal levels. But there are those occasions when you need a high impedance input and a fast (high frequency) rise time. As with the CRO, this is where your

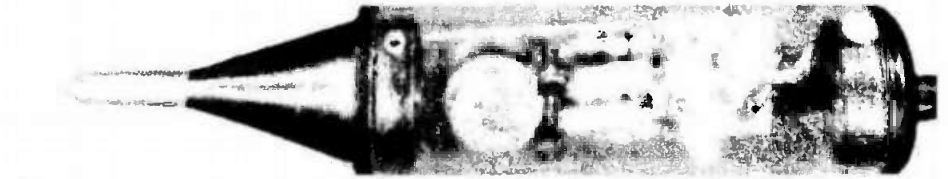

counter/timer runs out of grunt.

It's times like these you need this project; a x1 active instrument probe using a special buffer IC with an input impedance of typically 100,000 megohms! — that's 10<sup>11</sup> ohms — a very low input capacitance of around four to five picofarads, a fast rise time (around three nanoseconds) and a bandwidth of 100 MHz. Output impedance is around 50 ohms and the device is capable of driving capacitive loads up to several thousand picofarads. Thus it is eminently suited for use with high speed, wide bandwidth oscilloscopes and digital frequency meter/timers at frequencies up to 100 MHz. Output impedance is close to 50 ohms and it is thus suited to drive both high impedance instrument inputs and low impedance inputs (which are generally 50 ohms).

## Design

It's all done inside a special IC — an LH0033CG from National Semiconductors. This is described as a 'fast buffer amplifier'. (It has a companion designated LH0063, described as a 'damn fast buffer amplifier!'). The LH0033 is a direct-coupled FET-input voltage follower/buffer (gain  $\approx 1$ ) designed to provide high current drive at frequencies from DC to over 100 MHz. It will provide  $\pm 10$  mA into 1k $\Omega$  loads ( $\pm 100$  mA peak) at slow rates up to 1500 V/ $\mu$ S, and the chip exhibits excellent phase linearity up to 20 MHz. No offset voltage adjustment is required as the unit is constructed using specially selected FETs and is laser-trimmed during construction. Input is directly to the gate of a

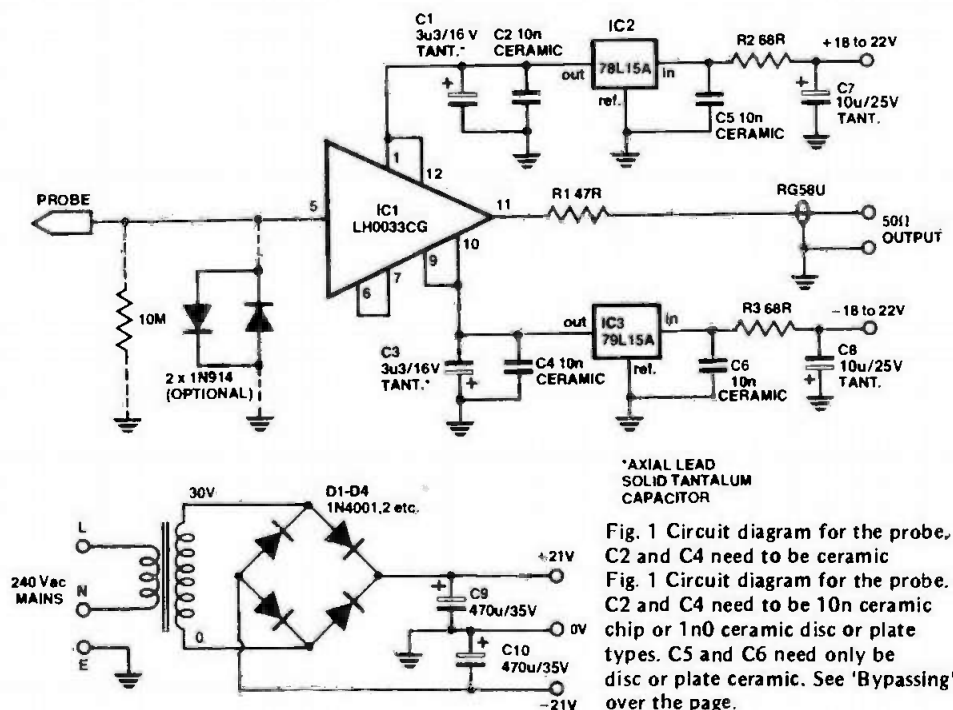


Fig. 1 Circuit diagram for the probe. C2 and C4 need to be ceramic. Fig. 2 Circuit diagram for the probe. C2 and C4 need to be 10n ceramic chip or 1n0 ceramic disc or plate types. C5 and C6 need only be disc or plate ceramic. See 'Bypassing' over the page.

## BYPASSING

junction FET, operated as a source follower, driving a complementary output pair of bipolar transistors.

Regulated plus and minus supplies of 15 V each provide power to the IC. Low-power three-terminal regulators are used to keep the unit compact. An external unregulated supply of between 18 and 22 V at around 50 mA is required to power the probe.

The supply pins on the IC need to be well bypassed over a wide frequency range so that the IC can maintain its characteristics, and the construction has been specially arranged to achieve this. Axial lead solid tantalum capacitors are used to bypass the IC's supply pins at the lower frequencies, while low inductance ceramic capacitors are employed as bypasses for the higher frequencies. A double-sided fibreglass PCB is used to preserve the high frequency response and the high input impedance, and the layout is arranged to permit direct connection to the probe tip and provide low input capacitance.

However, the presence of the PCB substrate will degrade the input impedance, surprisingly enough, and you can drill out the area of board immediately beneath pin 5 of the IC and solder the pin directly to the probe tip. For those who wish to go 'all the way' (as Frank Sinatra sings), the plastic insulation of the probe tip can be replaced with a similar piece of Teflon — if you can afford it and have access to a lathe.

The maximum input voltage permissible, when driving a high impedance load, is plus or minus 15 V. When driving a 50 ohm load, maximum input voltage permissible is only plus or minus 10 V (limited by maximum output current). No input protection has been included. However, if you are only working with circuits where voltages are no greater than about 1 V peak-to-peak, protection can be added by putting two diodes back-to-back in parallel with the input, along with a 10M resistor. The maximum input voltage figures include any DC voltages present, *plus* the superimposed signal voltage.

At this stage it is only fair to tell you that the LH0033CG is an expensive device (by comparison). But — compare the total cost of this probe to a similar commercially-made type and you won't catch your breath a second time!

### Construction

The project is constructed on a small double-sided fibreglass PCB with

Supply lead bypassing is important in order that the LH0033 can operate correctly over the full bandwidth from DC to 100 MHz. To ensure this, the bypassing has been specially arranged and the techniques employed are probably unfamiliar to many readers.

The output circuit signal return path for the IC is via the ground and the two supply rails. Any significant impedance in series with this path (or paths) will subtract signal from the output load. Thus, the supply rail bypassing has to present an impedance which is a *fraction* (like one-tenth or better) that of the minimum output load impedance. Here, the minimum output load is about 100 ohms ( $R1 + 50$  ohms instrument input impedance) and the supply bypassing impedance should ideally be less than 10 ohms across the frequency range.

The bypassing on each supply rail to the IC leads here takes advantage of the characteristics of three separate components to cover three sections of the frequency range.

From DC to around 100 kHz, each three-terminal regulator (IC2, IC3) has an output impedance well below one ohm, rising to four or five ohms at 1 MHz, as shown in Fig. 1. The two tantalum capacitors, C1 and C3, then take over.

Solid tantalum capacitors have a characteristic impedance that falls with frequency according to its value, which then 'flattens out' in the region around 500 kHz — 1 MHz, rising to a few ohms around 10 MHz, as can be seen in Fig. 2. Thus, C1 and C3 serve as effective bypasses across the range from around 100 kHz to around 10 MHz. Axial lead tantalum capacitors were chosen as their construction exhibits the slowest impedance rise following the minimum impedance value.

To provide bypassing over the decade from 10 MHz to 100 MHz, capacitors C2 and C4 have been specially chosen and positioned on the PCB. For the prototype, 'chip' ceramic capacitors were used. These tiny, 'naked' chips of ceramic with a capacitor embedded in them are probably the most effective bypass capacitors made. The leads and physical construction of all capacitors form an inductance which is

effectively in series with the capacitance of the component. The combined effect forms a series resonant circuit, the frequency of which (that is, the self-resonant frequency of the component) is mainly dependent on the length of the connecting leads, the particular construction of the capacitor and the way in which it is mounted. Ceramic chip capacitors, being a tiny block with connecting pads or surfaces on each end, have extremely low values of series inductance and thus very high self-resonant frequencies — see Fig. 4. Now, any value of chip capacitor between 1n0 and 10n can be used for C2 and C4. The self-resonant frequency of a 1n0 chip capacitor is somewhat above 100 MHz (as per Fig. 4), but that of a 10n chip is between 40 MHz and 50 MHz. Now, this isn't a problem, for the chip's impedance falls with frequency as usual until near the self-resonant frequency where it falls rapidly, reaching a minimum at the self-resonant frequency. Above that frequency its impedance rises again, but is still low enough for effective bypassing.

Ordinary ceramic disc and plate capacitors behave in much the same way. The self-resonant frequency of a typical 5 mm diameter disc or 5 mm square plate capacitor depends on the lead length, as shown in Fig. 5. Thus, you could use 470pF or 1000pF (1n0) capacitors of this type for C2 and C4, provided you installed them on the underside of the board with *absolute minimum lead length*.



Fig. 3 Ceramic chip capacitors shown about actual size.

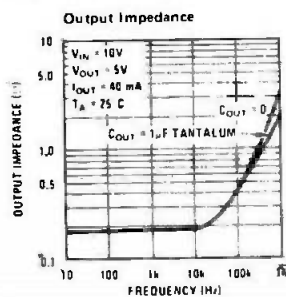


Fig. 1.

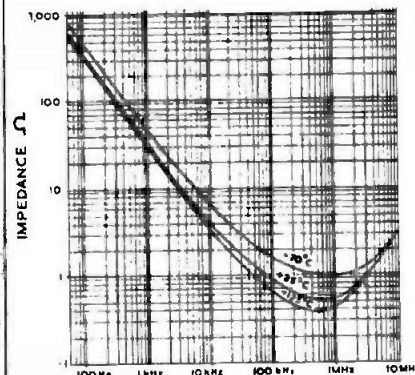


Fig. 2.

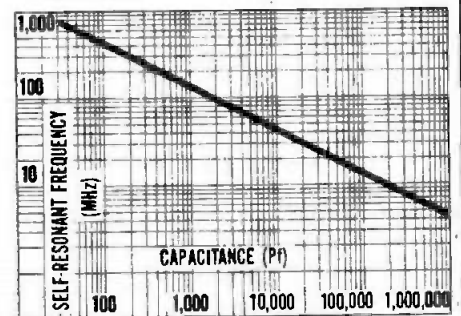


Fig. 4.

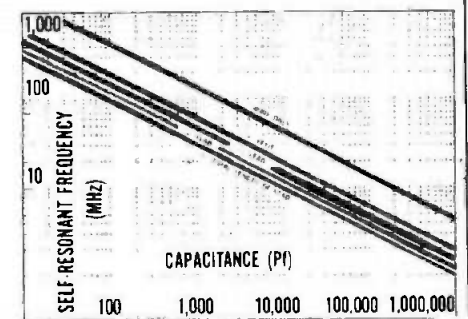


Fig. 5.

# PROJECT : Instrument Probe

components mounted on both sides of the board. Commence by soldering in place the components that go on the top side of the board, leaving IC1 until last. Note that the positive leads of both C3 and C8 are soldered to the groundplane areas on both the top and the bottom sides of the board. Take care with the orientation of the tantalum capacitor, as well as IC2 and IC3. Having done that, solder C2, C4, C5 and C6 to the bottom side of the board. Now you can install IC1. You will have to juggle the legs a little. Push the can as far down on the board as you're able; its base should sit no more than 3 mm from the board.

Now that you have everything in place, check it all. It seems pretty simple, but Murphy's law will ensure that the simplest things have the highest stuff-up rates!

All's well? — now you attach the output coax cable to the underside of the board, plus the DC input and ground (0 V) wires. But — before you do, slip the output end piece of the probe case over the cable and supply wires, push it down about 150 mm or so and then slip the case of the probe case down the wires. This saves slipping them over the other end of the whole business and sliding them all the way to the probe.

The probe tip can be attached and soldered in place last of all. Now you can screw it all together and attach the appropriate plugs to the other end of the cable and supply wires.

With the construction completed, you can power up and try it out. Note that the transformer suggested in our power supply is but one of many suitable types. Any transformer that will deliver at least 26 V AC at a load of about 50 mA will suffice. Alternatively, any dual polarity DC supply having an output between 18 and 22 V at 250 mA will power the probe.

## Note

Always take care that you don't exceed the input voltage limitation; LH0033s are expensive.

## BUYLINES

Ceramic chip capacitors and solid tantalum axial capacitors are a trifle unusual; however, they are stocked by C.T. Electronics (Action) Ltd, 267 & 270 Acton Lane, London W4 5DG. (They also stock the BNC plug should you have any problems there). We will be selling the double-sided board through out PCB Service — the order form is on page 44.

## PARTS LIST

### Resistors (all ¼ W, 5%)

R1 47R  
R2, R3 68R

### Capacitors

C1, C3 3u3 16 V solid tantalum axial leads  
C2, 4, 5, 6 10n ceramic block  
C7, C8 10u 25 V tantalum  
C9, C10 470u 35 V electrolytic (if required)

### Semiconductors

IC1 LH0033CG  
IC2 78L15A  
IC3 79L15A  
D1-D4 1N4001,2,etc. (if required)

### Miscellaneous

PCB (double-sided fibreglass); RG58U coax cable and BNC plug; T1 — (if required) 240 V to 30 V transformer or similar; optional 10M/¼ W 5% resistor and 2 x 1N914 diodes; wire; probe housing.

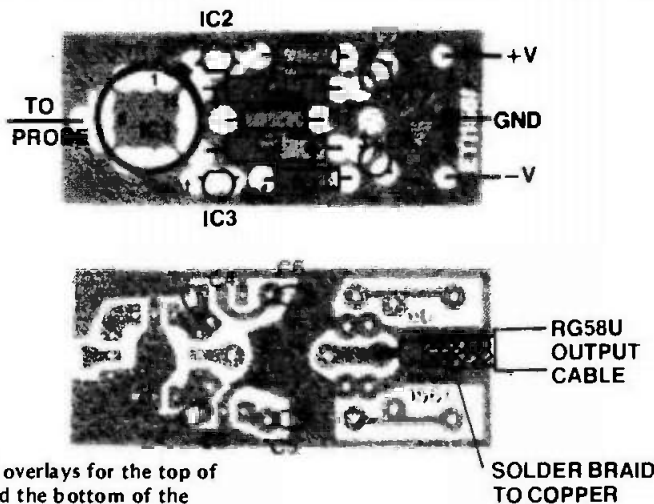


Fig. 2 Component overlays for the top of the board (top) and the bottom of the board (bottom!).

## HOW IT WORKS

This instrument probe employs a wideband hybrid voltage follower/buffer IC, the LH0033, with very close to unity gain, that features a very high input impedance and a low output impedance. It requires regulated, well-bypassed supply rails. Two three-terminal low power regulators provide plus-and-minus 15 V supplies from an unregulated input.

The internal circuit of the LH0033 is shown below. Basically, it consists of a FET input stage (Q1), operated as a source follower. The other FET, Q4, provides a constant current source for the source bias of Q1, while Q2 and Q3 are connected as diodes and provide bias for the bases of Q5 and Q6. Resistors R1 and R2 are laser trimmed in manufacture so that the IC meets the offset voltage specification. As Q1 has a constant current source load, the input impedance at the gate of Q1 is very low. The output of the source follower drives a complementary pair output stage, Q5-Q6. Thus the IC will have a very high input impedance and a gain very close to unity. With appropriate construction employed for the internal devices, the bandwidth over which the device will operate can be made very wide indeed. The -3dB point for the LH0033 is 100 MHz.


As the device is direct-coupled, DC levels will be maintained between input and output.

Bypassing requirements for the IC's supply leads are explained elsewhere in the article.

To provide regulated plus-and-minus 15 V rails for the IC, two three-terminal regulators are employed, a 78L15A for the positive rail and a 79L15A for the negative rail. These can supply up to 100 mA and have a very low output impedance up to

several hundred kilohertz, which is exploited for low frequency bypassing. Each supply rail requires an unregulated input of between 18 V and 22 V. Decoupling of the supply leads provided by R2/C7 on the positive rail and R3/C8 on the negative rail. The input terminal of each regulator is bypassed to prevent instability.

As the input voltage is limited to a maximum equal to the supply rails (high impedance load), input protection may be added in applications where only low level signals are being examined. As shown in the main circuit, this protection consists of two 1N914 diodes connected back-to-back in parallel with a 10 M resistor across the input. Signals above 1 V peak-to-peak will be clipped, preventing any damage to the IC. If very fast rise time signals are to be examined then better protection for the IC can be obtained by using hot-carrier diodes such as the HP 5082-2800 instead of the 1N914s.

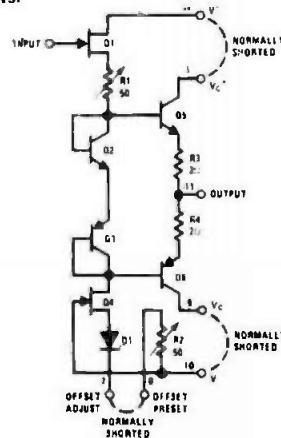

# LOOK

Kit includes tape transport mechanism, ready punched and back printed quality circuit board and all electronic parts i.e. semiconductors, resistors, capacitors, hardware, top cover, printed scale and mains transformer. You only supply solder & hook-up wire.

Self assembly simulated wood cabinet. £4.50 + £1.50 p+p.

INTRODUCTORY OFFER - ONLY  
**£32-95**  
+ £2.75 p&p.

Featured in April issue Practical Electronics, reprint 50p. Free with Kit.



## P.E. STEREO CASSETTE RECORDER KIT

- NOISE REDUCTION SYSTEM
- AUTO STOP ● TAPE COUNTER
- SWITCHABLE E.O.
- INDEPENDENT LEVEL CONTROLS
- TWIN V.U. METER
- WOW & FLUTTER 0.1%
- RECORD PLAYBACK I.C. WITH ELECTRONIC SWITCHING
- FULLY VARIABLE RECORDING BIAS FOR ACCURATE MATCHING OF ALL TAPES

## STEREO AMPLIFIER KIT



- Featuring latest SGS/ATES TDA 2006 10 watt output IC's with in-built thermal and short circuit protection.
- Mullard Stereo Pre-amplifier Module.
- Attractive black vinyl finish cabinet, 9" x 8 1/4" x 3 3/4" (approx).
- 10+10 Stereo converts to a 20 watt Disco amplifier.

To complete you just supply connecting wire and solder. Features include din input sockets for ceramic cartridge, microphone, tape or tuner. Outputs - tape, speakers and headphones. By the press of a button it transforms into a 20 watt mono disco amplifier with twin deck mixing. The kit incorporates a Mullard LP1183 pre-amp module, plus power amp assembly kit and mains power supply. Also features 4 slider level controls, rotary bass and treble controls and 6 push button switches. Silver finish fascia with matching knobs and contrasting cabinet. Instructions available, price 50p. Supplied FREE with kit.

**£16-50**

+ £2.90 p&p.

### SPECIFICATIONS:

Frequency response  
Input sensitivity

Suitable for 4 to 8 ohm speakers  
40Hz - 20KHz  
P.U. 150mV, Aux. 200mV.  
Mic. 1.5mV.  
Bass  $\pm 12$ db @ 60Hz  
Treble  $\pm 12$ db @ 10KHz  
0.1% typically @ 8 watts  
220 - 250 volts 50Hz.

Tone controls  
Distortion  
Mains supply

**8" SPEAKER KIT** Two 8" twin cone domestic speakers. £4.75 per stereo pair plus £1.70 p&p, when purchased with amplifier. Available separately £6.75 & £1.70 p+p.

## 125W HIGH POWER AMP MODULE

KIT: **£10-50** BUILT: **£14-25**  
+ £1.15 p&p + £1.15 p&p.

The power amp kit is a module for high power applications - disco units, guitar amplifiers, public address systems and even high power domestic systems. The unit is protected against short circuiting of the load and is safe in an open circuit condition. A large safety margin exists by use of generously rated components, result, a high powered rugged unit. The PC board is back printed, etched and ready to drill for ease of construction and the aluminum chassis is preformed and ready to use. Supplied with all parts, circuit diagrams and instructions.

**ACCESSORIES:** Suitable mains power supply kit with transformer: £7.50 plus £3.15 p&p.  
Suitable LS coupling electrolytic: £1.00 plus 25p p&p.



### SPECIFICATIONS:

Max. output power (RMS): 125W.  
Operating voltage (DC): 50 - 80 max.  
Loads: 4 - 16 ohms.  
Frequency response measured @ 100 watts: 25Hz - 20KHz.  
Sensitivity for 100 watts: 400mV @ 47K.  
Typical T.H.D. @ 50 watts, 4 ohms: 0.1%.  
Dimensions: 205 x 90 and 190 x 36 mm.

## HI-FI SPEAKERS AT BARGAIN PRICES

### GOODMANS TWEETERS

Bohm soft dome radiator tweeter (3 1/2" sq.) for use in up to 40W systems; with 2 element crossover.

**£3.50 each (p&p £1) or £5.95 pair (p&p £2).**



### 35 WATT MICRO 2-WAY SPEAKER SYSTEM

Unit comprises one 50w (4" app.) Audax soft dome tweeter HD100. And one 5" Audax bass/midrange 35w driver HIFI1JSM. Complete with 2 element crossover. Total impedance of system 4 ohms.

**£7.95**

PER SET + £2.70 p&p.



## P.E. STEREO TUNER KIT

This easy to build 3 band stereo AM/FM tuner kit is designed in conjunction with Practical Electronics (July 81 issue). For ease of construction and alignment it incorporates three Mullard modules and an I.C. IF. System.

**FEATURES:** VHF, MW, LW Bands, interstation muting and AFC on VHF. Tuning meter. Two back printed PCB's. Ready made chassis and scale. Aerial: AM - ferrite rod, FM - 75 or 300 ohms. Stabilised power supply with 'C' core mains transformer. All components supplied are to P.E. strict specification. Front scale size: 10 1/2" x 2 1/2" approx. Complete with diagram and instructions.

**£17-95**

Plus £2.50 p&p.

Self assembly simulated wood cabinet sleeve to suit tuner only. Finish size: 11 1/2" x 8 1/4" x 3 3/4".  
**£3.50** Plus £1.50 p&p.



### SPECIAL OFFER! TUNER KIT PLUS:

• Matching I.C. 10 watt per channel Power amp kit. • Mullard LP1183 built pre-amp, suitable for ceramic pick-up and aux. inputs. • Matching power supply kit with transformer. • Matching set of 4 slider £21.95 controls for bass, treble and volumes. + £3.80 P&P.

## PRACTICAL ELECTRONICS CAR RADIO KIT SERIES II



### 2 WAVE BAND, MW - LW

• Easy to build. • 5 push button tuning. • Modern design. • 6 watt output. • Ready etched and punched PCB. • Incorporates suppression circuits.

All the electronic components to build the radio, you supply only the wire and the solder, featured in Practical Electronics. Features: pre-set tuning with 5 push button options, black illuminated tuning scale. The P.E. Traveller has a 6 watt output neg. ground and incorporates an integrated circuit output stage, a Mullard 1F Module LP1181 ceramic filter type pre-aligned and assembled, and a Bird pre-aligned push button tuning unit.

Suitable stainless steel fully retractable aerial (locking) and speaker (6" x 4" app.) available as a complete kit. £2.50/pack + £1.50 p&p.

**£12-95**

+ £2.00 p&p.

## TV SOUND TUNER KIT



**£11-45**

+ £1.50 p&p.

As featured in E.T.J. December '81 issue. Kit of parts including PCB, UHF tuner and selector switch with all components excluding case.

• Transformer £1.50 + £1.50 p&p (p&p free on transformer if ordered with kit). • Ready built LP1183 Module for simulated stereo operation. £1.95 + 75p p&p.

## MONO MIXER AMP



**£39-95**

+ £3.70 p&p.

50 WATT Six individually mixed inputs for two pick ups (Cer. or mag.), two moving coil microphones and two auxiliary for tape, tuner, organs, etc. Eight slider controls - six for level and two for master bass and treble, four extra treble controls for mic. and aux inputs. Size: 13 1/2" x 6 1/2" x 3 3/4" app. Power output 50 watts R.M.S. (continuous) for use with 4 to 8 ohm speakers. Attractive black vinyl case with matching fascia and knobs. Ready to use.

## BIRD AUDIO STEREO CAR RADIO BOOSTER



To boost your car radio or radio cassette to 15W r.m.s. per channel.

**£9-95** + £1.50 p&p.

### ALL MAIL TO:

21E HIGH STREET, ACTON, W3 6NG.  
Note: Goods despatched to UK postal addresses only. For further information send for instructions 20p plus stamped addressed envelope. All items subject to availability. Prices correct at 31/1/82 and subject to change without notice. Please allow 7 working days from receipt of order for despatch.

ALL PRICES INCLUDE VAT AT 15%.

ALL CALLERS TO: 323 Edgware Rd, London W2. Telephone: 01-723 8432.  
Open 9.30 - 5.30pm. Closed all day Thursday.  
RTVC Limited reserve the right to update their products without notice.





# WIN AN ELECTRONIC IGNITION!

Hands up all those who had trouble starting their cars during the recent appalling weather. Don't you wish your car was fitted with an electronic ignition to make the most of your battery, as well as increasing the life of your contact breaker and giving you more miles to the gallon into the bargain?

The prize in this competition is a Total Energy Discharge ignition unit designed by Electronize Design, a company with a great deal of experience in

the field. The unit is supplied as a kit of parts and is easy to assemble.

To win this kit you have to answer these two questions:—

(1) The standard ignition circuit, using a coil and contact breaker, has been fitted to virtually all mass produced cars for 60 years. Who designed it? (We'll accept surname only).

(2) In a four-cylinder engine, firing the cylinders in the order 1-2-3-4 would lead to excessive engine vibration. Give one

firing sequence commonly used to overcome this problem.

Write your name, address and answers on the form on page 133 (there's no need to cut up this page) and send it to us by April 30th, 1982. (All right, you can put your hands down now!)

## RULES

1. Closing date is April 30th 1982, and all entries post-marked later than this date will be discounted.
2. The coupon provided in the magazine must be used. Photocopies are NOT acceptable.
3. Employees of ASP and their relatives are not eligible for entry.
4. The judges' decision is to be considered final and no correspondence will be entered into concerning the competition.

### ACORN ATOM

8K rom + 2K ram Kit £120, built £150. 12K rom + 12K ram kit £160, built £190. 4K expansion rom £26. Power supply £10.20

### UK101 AND SUPERBOARD

UK101 with 1K and free power supply and modulator kit £120, built £149. The below accessories suit both the UK101 and superboard: Extra ram £2.10 per K. 16K memory expansion complete kit £60, built £58. 32K memory expansion kit £74, built £82. Cassette recorder £13. Cegmon £22.50. Wemon £19.95. Word processor program £10. Centronics interface kit £10. 610 expansion board £179. Caset mini floppy disc drive with DOS £276. The below suit only superboard: Colour adaptor board built £46. Assembler/Editor tape £25. Guard band kit £10. Series 1 only 30 lines + 50 characters display expansion kit £14. UK101 display expansion kit £14.

### NEW GENIE 1 £299

EG3014 Expansion box with 16K/32K ram £199/£213. Disk drive £220. Ldos £88. Newdos + £49. Ajedit disk word processor £44. Colour board £36. Parallel printer interface £36. Monitors: EG100 white £69. OVM9PGR green £99. Colour Genie pos. Genie 3 pos.



### PRINTERS



Buy any of the below and get a free interface kit and word processor program for UK101 or Superboard: Epson MX70 £259. Epson MX80 £359. Epson MX80F/T1 £395. Epson MX80F/T7 £449. OKI Microline 80 £295. OKI Microline 82A £399. Centronics 737 £335. Seikosha GP80A £199.

### SWANLEY ELECTRONICS

Dept ET1, 32 Golds Rd., Swanley  
Kent BR8 8EZ  
Tel Swanley (0322) 64851

### SINCLAIR PRODUCTS\*

ZX81 built + mains adaptor £69.95 IPost £2.95 extnl. SC110 Oscilloscope £139. PDM35 £32.95 DM450 £116.

### BATTERY ELIMINATORS\*

3 way type 6/7.5/8V 300ma £3.50. 100ma radio types with press studs 9V £4.95. 9 - 8V £6.25. Car converter 12V input, output 3/4.5/6/7.5/9V 800ma £3.04.

### BATTERY ELIMINATOR KITS\*

100ma radio types with press studs 9V £1.79. 9 - 8V £2.50. Stabilized 8 way types 3/4.5/6/7.5/9/12/15/18V 100ma £3.12. 1 Amp £8.50. Stabilized power kits 2-18V 100ma £3.12. 1-30V 1A £8.50. 1-30V 2A £15.30. TTI and computer supplies 5V stabilized 1.5A £9.3A £14.6A £22.12V car converters 6/7.5/9V 1A £1.62.

### TV GAMES\*


AY-3-8600 + kit £12.98. AY-3-8550 + kit £9.26.

### BI-PAK AUDIO MODULES\*

AL30A £4.35. PA12 £9.31. PS12 £1.75. T538 £2.90. S450 £27.90. AL80 £5.62. PA100 £19.24. SPM80 £5.26. BMT80 £6.36. Stereo 30 £21.00. AL80 £8.56.
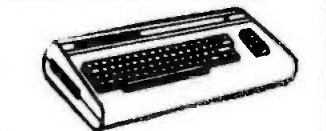
### VIC 20 COMPUTER

VIC 20 with free kit to allow use of a normal cassette recorder £165. Kit by itself £5. New low cost memory board. No need for a mother-board. Comes with 3K high resolution area + socket for a rom + sockets for 24K of ultra low current Nmos ram (Just plug in chips to expand memory) £49. Extra memory chips £39 per BK. VIC printer £199. Joystick £6.52.



### COMPONENTS\*


1N4148 1.5p. 1N4002 3.7p. NE555 8 pin 22p. 741 8 pin 22p. 741 8 pin 16p. 2N14 low current 300ns £1.35. BC102. BC194. BC212. BC214. BC547. BC548 6p. Resistors 5%. 1/4 watt £12. 100 to 10M 1p. 0.0p for 50 + of one value. Polystyrene capacitors £12.63V 10 to 1000pF 4p. 1n2 to 10n 5p. Ceramic capacitors 50V £6.22pF to 47n 2.5p. Electrolytic capacitors 50V .5. 1. 2mF 6p. 25V .5. 10mF 6p. 16V 22. 33mF 6p. 47mF 4p. 100mF 7p. 330. Zeners 400mw £24. 2v7 to 33v 7p. Preset pots subminiature 0.1W horiz or vert 100 to 2m2 8p. IC sockets 8 pin 8.7p. 14 pin 10.7p. 16 pin 12p.

Postage £3.50 computers, £4.50 on Printers and 45p on other orders. Lists 27p Post free. Please add VAT to all Prices except those sections marked with a \* which already include it. Overseas and official credit orders welcome.

## B.K. ELECTRONICS

The quality THANDAR range of equipment includes:  
●Function and pulse generators ●Digital frequency meters ●Digital thermometer ●Logic analyser  
Send **LARGE SAE** for complete lists.
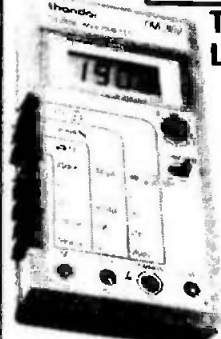
### The very latest TM352 HAND LCD DIGITAL MULTIMETER




- ★ 1 1/2 digit display
  - ★ DC and AC volts
  - ★ DC current
  - ★ Resistance and diode check
  - ★ Audible continuity check
  - ★ hrf measurements
  - ★ Latest push-button controls for ease of operation
- DC voltage 200mV 2V 20V 200V 1000V  
AC voltage 200V and 1000V  
DC current 200µA 2mA 20mA 200mA 10A  
Resistance, diode check and continuity test 20KΩ 200KΩ 2000KΩ  
hFE measurement 0 1000  
Power requirement 9V (PP3) battery  
Price £49.95 (including test leads and battery)  
Carry case £3.45.

### SC110 FULLY PORTABLE OSCILLOSCOPE

The new Thandar SC110 represents a breakthrough in oscilloscope development. The full-sized performance SC110 is less than 2" thick and weighs under 2lb, yet it retains the standard features of a bench oscilloscope.

- ★ 10MHz bandwidth
- ★ 10mV per div. sensitivity
- ★ Full trigger facilities are provided including brightness and auto with TV line and frame filtering
- ★ Runs on ordinary HP11 (four) batteries. Basic Price £139.00

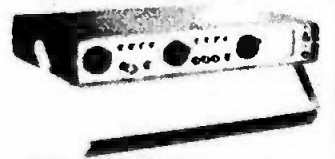Optional Extras: AC Adapter £5.69. Rechargeable Batteries £8.63. X1 probe £8.05. X10 probe £9.20. X1/X10 switched probe £10.90. Carry case £8.86.



All prices include V.A.T. Official orders welcome. Mail order only, or callers by prior appointment. Barclaycard/Access welcome. Cash/cheque, etc., with order. Large s.a.e. for complete Thandar list. Government and Educational Establishments official orders welcome.

**B.K. ELECTRONICS**  
37 Whitehouse Meadows, Eastwood, Leigh-on-Sea, Essex. SS9 5TY  
Tel. Southend 527572

# MASTER ELECTRONICS NOW!

## The PRACTICAL way!


This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to start or further a career in electronics or as a self-employed servicing engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write personally at any time, for advice or help during your work. A Certificate is given at the end of every course.

You will do the following:

- Build a modern oscilloscope
- Recognise and handle current electronic components
- Read, draw and understand circuit diagrams
- Carry out 40 experiments on basic electronic circuits used in modern equipment
- Build and use digital electronic circuits and current solid state 'chips'
- Learn how to test and service every type of electronic device used in industry and commerce today. Servicing of radio, T.V., Hi-Fi and microprocessor/computer equipment.

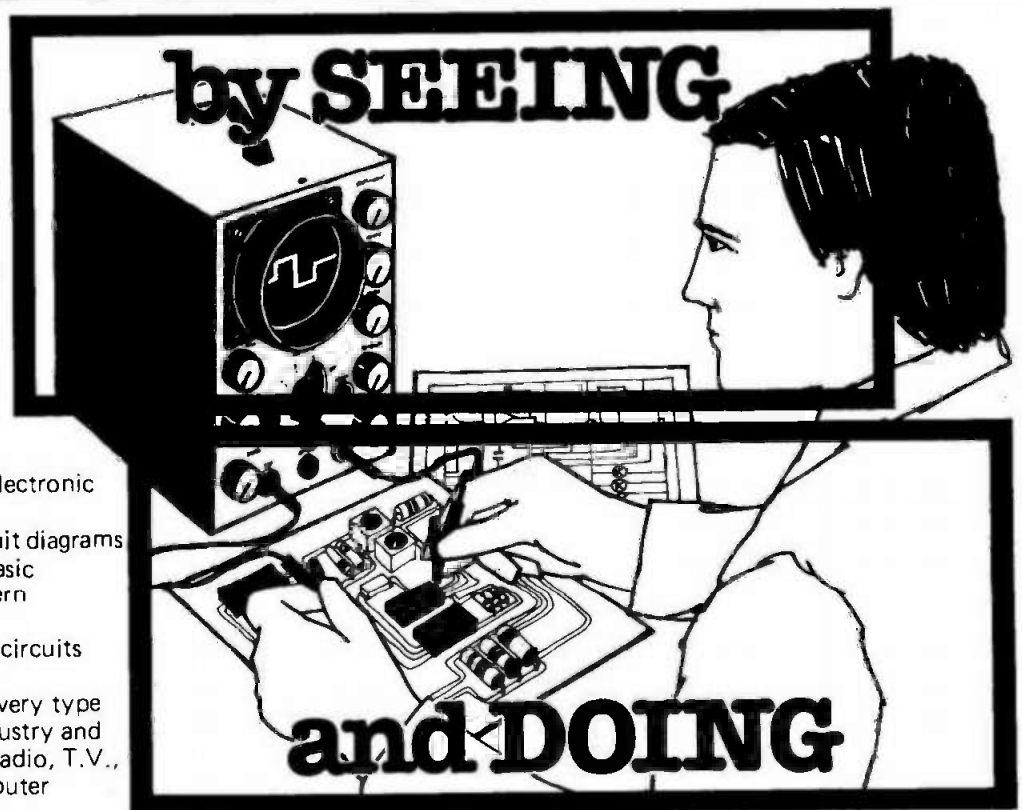

New Job? New Career? New Hobby? Get into **Electronics** Now!

**FREE!**

COLOUR BROCHURE



Please send your brochure without any obligation to

I am interested in:

ETI/4/820

- COURSE IN ELECTRONICS as described above
- RADIO AMATEUR LICENCE
- MICROPROCESSORS
- LOGIC COURSE

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

OTHER SUBJECTS \_\_\_\_\_


POST NOW TO:

BLOCK CAPS PLEASE

**British National Radio & Electronics School Reading, Berks. RG1 1BR.**

# electronics today

INTERNATIONAL

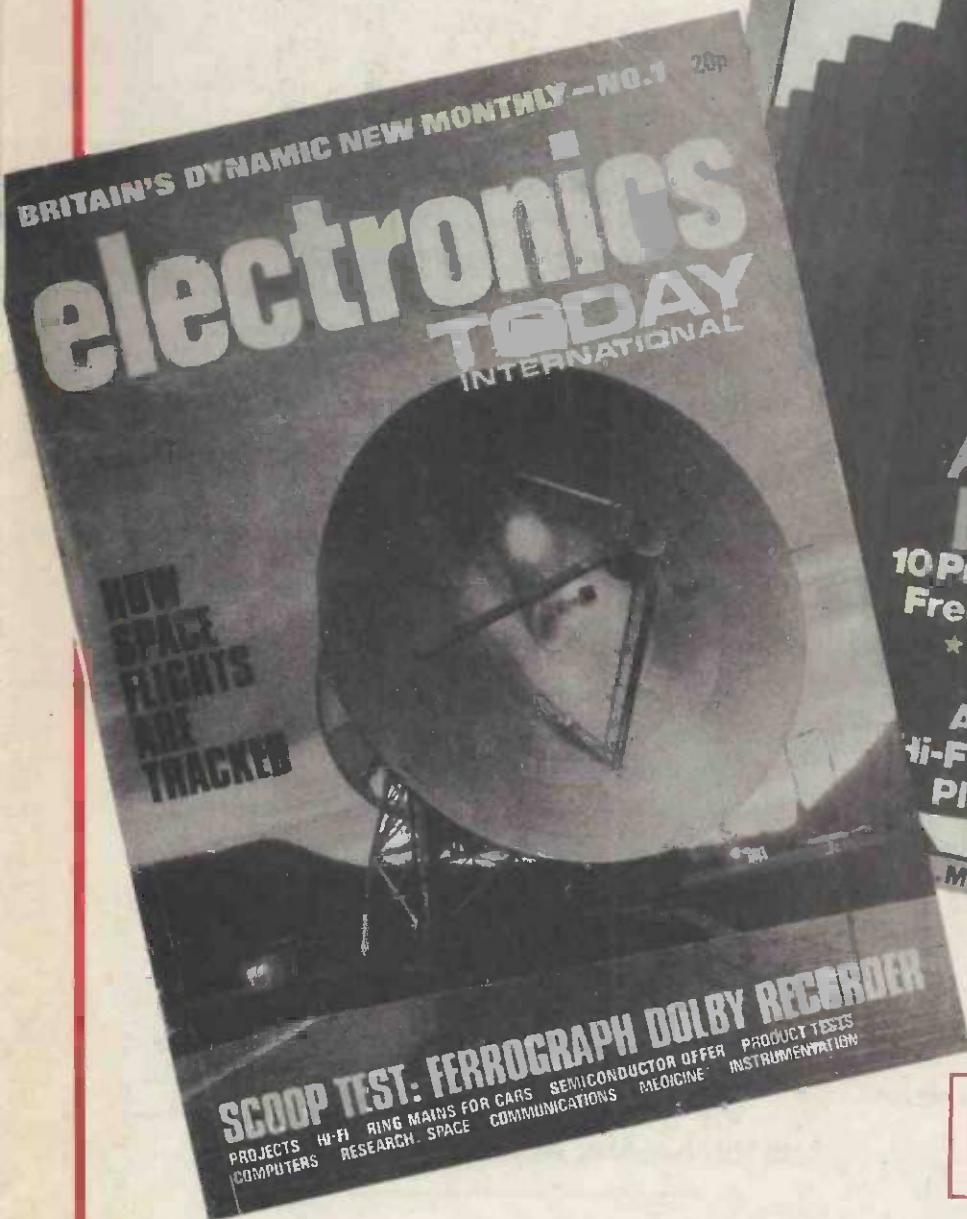

# A Decade of Electronics

..AUDIO....COMPUTING....MUSIC....RADIO....ROBOTICS..

## IF YOU'VE READ THE LAST TEN YEARS OF ETI WIN THE NEXT 10 FREE!



This is a special competition for our regular readers. We're offering a ten year subscription to ETI as a 'thank you' prize for supporting us this far. All the questions refer to back copies of our magazine and will be easy if you've kept the issues! (Surveys tell us that over 90% of readers keep ETI for longer than a year!) Index issues will be particularly useful, but will not give you *all* the answers. Fill in the coupon on page 133 — you don't need to ruin this issue — and don't forget your *name and address!* In the event that no one gets *all* the answers correct, the highest number of right answers will win. In the event of a tie, it will be the earliest postmark that takes the ten year subscription.

Read the questions carefully before answering.

1. Which issue was designated a "4 Channel Sound Special Issue"? \_\_\_\_\_
2. Who edited the May 1973 issue of ETI?  
\_\_\_\_\_
3. What month did the first issue of ETI appear in Britain?  
\_\_\_\_\_
4. What makes March 1979 good theatre?  
\_\_\_\_\_
5. ETI published the first-ever TV games project. In which issue? \_\_\_\_\_
6. Which IC is featured in the July 1976 "Data Sheet"?  
\_\_\_\_\_
7. The amplifier on the cover of the February 1982 issue has also appeared on a previous cover of ETI. Which one?  
\_\_\_\_\_

8. In 1979 who reviewed Star Chess for ETI?  
\_\_\_\_\_
9. Who first wrote the series "Electronics Tomorrow"?  
\_\_\_\_\_
10. The 100 W Guitar Amplifier (the first one!) appeared when? \_\_\_\_\_
11. Microfile is the title of ETI's regular computing hardware section. In which issue did it first appear?  
\_\_\_\_\_
12. In what year did we publish a synthesiser, an LED multimeter and an FM tuner in successive months?  
\_\_\_\_\_
13. What was "The Beast"? \_\_\_\_\_
14. How many parts of the popular "Electronics — It's Easy" series were published in ETI? \_\_\_\_\_
15. How many editors has ETI had in the past years?  
\_\_\_\_\_
16. In October 1976, who was ETI's Assistant Editor?  
\_\_\_\_\_
17. Who designed the Transcendent DPX?  
\_\_\_\_\_
18. Which issue began "Project 80"? \_\_\_\_\_
19. The 4600 synthesiser is one of our all-time most popular projects. In which issue did the series begin? \_\_\_\_\_
20. DIY Polyphonic keyboards came to ETI when?  
\_\_\_\_\_

### RULES

1. Closing date is April 30th 1982, and all entries post-marked later than this date will be discounted.
2. The coupon provided in the magazine must be used. Photocopies are NOT acceptable.
3. Employees of ASP and their relatives are not eligible for entry.
4. The judges' decision is to be considered final and no correspondence will be entered into concerning the competition.



LKRAM

+5V R8 1k0

R9 1k0

+5V IC19a 8

19 22 23 1 2  
A10 A9 A8 A7A

# electronics today

INTERNATIONAL 1972 - 1982

ISSN. 0142-7229

D7 D6 D5  
17 16 15

## 10 YEARS ON

The last ten years have been the most dramatic in the history of electronics. Tracing back, you can chart the explosive growth of the "consumer electronics product" from the first — highly expensive — calculators, through digital watches and the like — to the fully-equipped home computer.

When compiling this issue — ETI's 10th Birthday, as I'm sure you've noticed by now — it occurred to us that we had the entire course of electronics charted out for us — within the news pages of ETI! News Digest has always figured very highly in our readers surveys and companies mentioned therein have often commented upon the interest the feature generates.

Accordingly we went back and read every single news page from April 1972 through to April 1982. (Yes, it did take a long time). Lo and behold! History unfolded!

It was all there — the first calculators, the first watches, the beginnings of LCD, the first MPU chips, cheap memory, the Space Shuttle tests, bubble storage announced — and failed, CB radio underway, FETs on the hobbyist market, CMOS finally becoming cheaper than TTL — and the lunacies! We found quite a few of those, in fact. Witness the Queen's speech that wasn't and the TV game with ball-bearing scoreboard.

You will find them all in the following pages, the successes, the failures, the achievements...and the gaffs. We have gone through the mountain of material available and put together what we think is a truly historic collection. (Sounds good that doesn't it — should be in the British Museum.)

Reading through you will be presented with the fascinating and surprising history of electronics, 1972-1982. Check the dates each item appeared. Some of them will astound you. When was the first TV game on sale? The first LED watch? When could you buy a home computer in the UK? As to the ladies who crop up all the way through, we've no idea how they got there — they've nothing to do with us and they are most certainly not included just because we thought you would enjoy seeing them again. Enjoyment has got nothing to do with it.

It is an interesting conjecture as to what we will be able to include in our 21st Birthday Issue. Any guesses?

5 A9 3 13

G2

+5V

R14 1k0

13 14 15 1 2 3  
IC18  
CLR OE ADL LD LC CK  
5 11

+5V D4

IC10c

65

# AUDIO ELECTRONICS

ALL PRICES INCLUDE VAT

RETAIL-MAIL ORDER-EXPORT  
INDUSTRIAL-EDUCATIONAL

LONDON'S TEST EQUIPMENT CENTRES

CALL IN AND SEE FOR YOURSELF  
OPEN SIX DAYS A WEEK ALL MODELS ON DISPLAY



## CROTECH 3035 10 MHz Scope Plus Component Tester

5" - 130mm Flat Face  
Tube DC - 10 MHz  
5mV/DIV 220/240V AC Trig. to 20 MHz

SAVE £21 PLUS

As advertised by us at £189.75 inc. VAT  
**NOW £168.50** inc. VAT  
(UK c/p £3.50) Exclusive to Audio Electronics


## PROFESSIONAL 100 K OHM/VOLT MULTIMETER

30 ranges 15A AC/DC  
1.5 KV, 200 meg ohms.  
Features mirror scale,  
polarity reverse, electronic  
overload protection, taut band  
suspension.

As advertised by us at £67.50  
+ case i.e. £84.00

**NOW £49** inc. VAT  
(UK c/p £1.50) with leather case  
Exclusive to Audio Electronics

SAVE £35

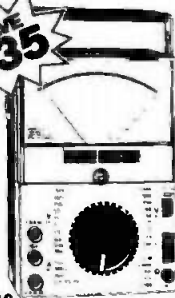


## LCD LOW COST MULTIMETERS

- 00001 3 1/2 digit LCD 26 range push button 2A £38.50
- AC/DC 20 meg ohm
- 000011A/1000 3 1/2 digit LCD 15 range push button plus Hfe Tester 10A DC (No AC A) £43.50
- 100m 3 1/2 digit LCD 30 range Rotary switch plus Hfe Tester 10A AC/DC £69.95

Customers will always find a range of low cost test equipment, accessories, tools, irons and boards in stock, also special offers for certain equipment which will vary from time to time. Price correct at time of preparation E&OE. All prices include VAT.

CHOOSE FROM UK'S LARGEST RANGE

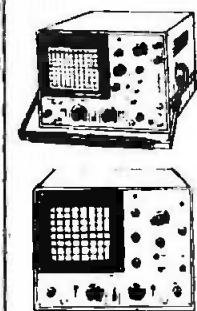STOP PRESS Few only 8110 23 range 10A AC/DC range hold continuity buzzer plus much more. Rotary switch £59.95



## TRIO OSCILLOSCOPES

Range of mains operated Scopes with 5" displays, triggered sweep (UK c/p £3.50)


- DUAL TRACE**
- CS1502A 10 MHz, 10mV, 1 micro sec. £267.95
  - CS1500A 11.15 MHz, 10mV, 0.5 micro sec. £341.55
  - CS1506A 20 MHz, 5mV, 0.5 micro sec. £363.40
  - CS1577A 35 MHz, 2mV, 0.1 micro sec. £523.25
  - CS1820 20 MHz, 2.5mV, 1 micro delay sweep £483.00
  - CS1830 Mk II 300 MHz, 2mV, 0.2 micro sec (filled delay line) £626.75
  - CS1575 5 MHz, 1mV, 0.5 micro sec. Multi display Audio scope. £312.80
- SINGLE TRACE**
- CS13030 5 MHz, 10mV, low sweep for observation below 1 Hz and up to 450 MHz, 75mm display (UK c/p £2.00) £124.20

## CROTECH OSCILLOSCOPES

Range of Portable Scopes mains and battery operated. Plus special features (UK c/p £3.00)

- 3030 Single trace 15 MHz, 5mV, 0.5 micro secs. Plus built in component tester, 95mm tube £168.75
  - 3131 Dual trace 15 MHz, trig to 35 MHz, 5mV, 0.5 micro sec. 130mm tube, plus component tester. £264.50
  - 3034 Battery-mains dual trace 15 MHz, Trig to 20 MHz built in Nicads, 5mV, 0.5 micro secs. (Eliminator charger optional £28.75) £356.50
- Also Available 3033, single trace 3034 3337, dual MHz, 130mm

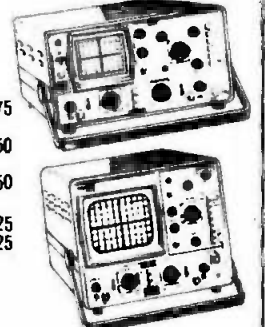STOP PRESS Model 3035 was £189.75 - Special Offer **£168.50**



### DIRECT READ HV PROBE (UK c/p 65p)

0/40KV, 20K Volt £18.40

### OSCILLOSCOPE PROBE KITS

(UK c/p 50p per 1 to 3) Available BNC plug or Banana X1 £7.95 X10 £9.45 X1-X10 £10.50 Also X100 (BNC only) £16.95

### MULTIMETERS

(UK c/p 65p or £1.00 for two)  
CHOOSE FROM UK'S LARGEST RANGE

- KRT101 10 range pocket 1K/Volt £4.95
- KRT100 12 range pocket 1K/Volt £5.50
- T10L 12 range 1K/Volt + overload £5.75
- MH55 10 range pocket 2K/Volt £6.50
- ST5 11 range pocket 4K/Volt £7.50
- AT1 12 range pocket Deluxe 2K/Volt £8.95
- MH56R 22 range pocket 20K/Volt £11.50
- YK300TR 19 range plus Hfe test 20K/Volt £14.95
- KRT5001 16 range - range double 50K/Volt £17.95
- ST303TR 21 range plus Hfe Test 20K/Volt £18.95
- AT1020 19 range Deluxe plus Hfe Test 20K/Volt £18.95
- ECT5000 As KRT5001 plus colour scales 50K/Volt £18.95

### CLAMP-ON-METERS INSULATION TESTERS

Multi-range clamps all with resistance range, carry case & leads. Also digital and DC clamp in stock (UK c/p 75p)

- ST300 300A, 600V 9 ranges £25.95
- ST310 300A, 600V 9 ranges £28.95
- K2602 150A, 600V, AC 7 ranges £35.95
- \*K2606 300A, 600V, AC 8 ranges £49.50
- K2803 300A, 600V, AC 9 ranges £58.95
- K2903 900A, 750V, AC 9 ranges £77.50
- K2103 1000A, 750V, AC 9 ranges £95.00
- \*Optional temperature probe £13.80

### SCOPE ADD ON UNITS

SUITABLE FOR ALL SCOPES

- LTC905 Semiconductor Curve tracer £95.45 (post 85p)
- KZ65 Component Tester £29.95 (Post 55p)

### ELECTRONIC INSULATION TESTERS

Battery operated complete with carry case (UK c/p £1.00)

- YF500L 500V/100Meg. Plus 0-100 ohm £85.00
- K3103 600V/100Meg Plus 0-2.6K ohm £109.00
- K3106 500V & 1000V 1000 & 2000Meg. £119.00
- K4101 Earth resistance tester £149.00
- M500 Hand cranked insulation tester 500V/100Meg. £79.50

### LOGIC PROBE (UK c/p 45p)

Leader LDP076 50 MHz, 10MEG ohm, 10n Sec with carry case £56.90

### THANDAR - SINCLAIR

Reliable low cost portable instruments, bench models all 25.5 x 15 x 15cm. Generators mains operated rest battery (supplied). UK c/p Hand models 65p, bench £1.15)

**DIGITAL MULTIMETERS (3 1/2 digit LCD)**

- TM354 Hand held, DC 2A, 2m ohm, 1mV - 1000V DC, 500V AC. £45.94
- TM352 Hand held, DC 10A, Hfe test, Continuity test £57.44
- TM353 Bench 2A AC/DC 1000V AC/DC 20M ohm, Typical 0.25% NEW LOW PRICE £86.25

**TM351 Bench, 10A AC/DC, 1000V AC/DC, 20M ohm Typical 0.1% £113.85**

**FREQUENCY COUNTERS (8 Digit)**

- M200A Hand held LED 200 MHz 10mV (600 MHz with TP600) £67.50
- New Model fitted BNC sockets
- TF040 Bench LCD 40 MHz, 40mV (400 MHz with TP600) £126.50
- TF200 Bench LCD, 200 MHz, 10-30mV (600 MHz with TP600) £166.75
- TP600 600MHz + 10 Prescaler 10mV £43.13

**GENERATORS (All bench models) mains operated**

- TG100 Function 1Hz-100 KHz, Sine/SO/Triangle/TTL £90.85
- TG102 Function 0.2Hz-2 MHz Sine/SO/Triangle/TTL £166.75
- TG105 Pulse, 5 MHz-5Hz (200ns-200ms) various outputs £87.75

**OSCILLOSCOPE (Bench model low power portable)**

- 10 MHz Z" trace, 10mV, 0.1 micro sec. All facilities. Model SC 110 £159.85
- Rechargeable battery pack £8.63, AC adaptor/charger £5.69

**OPTIONAL ITEMS**

- Carry case (bench only) £8.84 AC Adaptors (state model) £5.69

### KEITHLEY PROFESSIONAL DIGITAL MULTIMETER

Model 130, 25 range, Easy to hold and use LCD DMM, Size 7 x 3.1 x 1.5

Ranges

- DC Volts 200mV-1000V 0.5% 100 micro volt
- AC Volts 200mV-750V 1% 100 micro volt
- DC current 2mA-10AMP 1.2% 1 micro amp
- AC current 2mA-10AMP 2% 1 micro amp
- Resistance 200 ohm-20 Meg 0.5% 0.1 ohm

£102.35

### TV COLOUR GENERATORS

- PAL UHF and VHF Models
- LCG393 VHF 6 pattern £143.75
- LCG392u UHF 15 pattern £228.85
- LCG392v VHF 15 pattern £231.15
- LCG399 VHF/UHF 13 pattern £572.70
- MC101 UHF pocket colour } £162.50
- Fitted NICADS

# AUDIO ELECTRONICS

CUBEGATE LIMITED

301 EDGWARE ROAD, LONDON, W2 1BN, ENGLAND. TEL 01-724 3564  
ALSO AT HENRYS RADIO, 404/406 EDGWARE ROAD, LONDON W2

WE ARE OPEN 6 DAYS A WEEK - CALL IN AND SEE FOR YOURSELF!

Order by Post with CHEQUES/ ACCESS/VISA or Telephone your order

Allow up to 10 days for delivery

FREE CATALOGUE

Send large SAE (20p UK) Schools, Companies, etc. free on request.

ALL PRICES INCLUDE VAT

**TV GAMES COME OF AGE**

It is just over two years since the first TV games started to appear in pubs - since then a lot has happened in this field with a large number of small companies marketing various units by a variety of methods. Although the TV games have received a considerable

amount of publicity they have not yet caught on in a big way.

"No one who has ever played TV games has ever said anything derogatory about the concept", Richard Fairhurst of Videomaster Ltd., told ETI, "they may not like the price or the packaging but they always like the idea".

ETI NEWS NOV 1975



**bbc get it taped**

The BBC and 3M have collaborated to develop a new tape recording system claimed to provide 90 dB noise figure. The system will accommodate 32 tracks on one-inch tape at an undisclosed tape speed.

ETI NEWS JULY 1973

**PIEZOELECTRIC HEADPHONES**


The Pioneer SE-700 are the first high fidelity headphones to use the piezo-electric effect. As the audio signals reach the headphones, the driver elements of ultra-thin aluminium-coated high-polymer film expand and contract accordingly, creating "breathing" motion. Tonal characteristics are comparable to those of the electrostatic type headphones, but the SE-700 require no matching transformer.

ETI NEWS MAY 1975

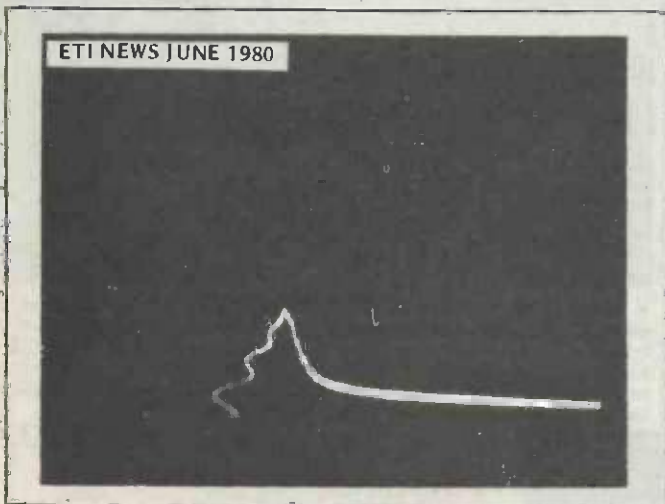**Doctor Who**

One of our readers, Mr. S. Knowles of Hampshire, sent us a scope picture he took whilst

designing with a Textronix 7403 on 500 nS/div with x10 expand. It seems he was looking for a pulse, but he may well have discovered the secret of time travel!



**Pet Chip**

This should appeal to those of you who spent your hard-earned pennies on a 'pet rock,'

We recently received a letter from an anonymous dad who made an apparently trivial Christmas present for his daughter. However, since then he has been inundated with orders.

Mr A. Nonymous painted a face on one end of an IC (pet IC, you see) and made a matchstick cage for it complete with watch battery feeding bowl.

The chip should quickly LATCH on to its new OHM. As for feeding, a few BITS of CURRENTS a day should be AMPLE. Just let it NOR away to its heart's content. You can teach it tricks.

Ta, Mr Nonymous. We haven't had a good groan in ages.

ETI NEWS MARCH 1980

**its a wide word**

Intel, Zilog and Motorola are taking their places in the front rank on the grid for this years expected race to 16 bit MPU sales. All three have completed development, and will probably show the nature of

their teeth at next months US Solid State Circuits Conference. The pause between this and letting loose of the hounds as it were will almost certainly mean late autumn production.

On yer marks .....

ETI NEWS MARCH 1978


**SHORTS**

● Every Ready - now called Berec - have released four rechargable consumer batteries, in the HP2, HP11, HP7 and PP3 varieties. Chargers are also available. An undoubted reaction to the phenomenal loss of dry cell power these days.

● Direct drive turntables yes. But direct drive MPUS? Also yes - now. The S2000 is a new release from AMI which can drive fluorescent displays directly, with HT drive and 7-segment decoding on chip. Also on board 64 x 4 RAM and 1K ROM. Intended for low cost applications.


● Ingersoll - the tick tick people - are into electronics. They have released three TV games, three clock radios, two Door Chimes, and a portable micro cassette player. Photo shows one of their new TV games. It must be Christmas.

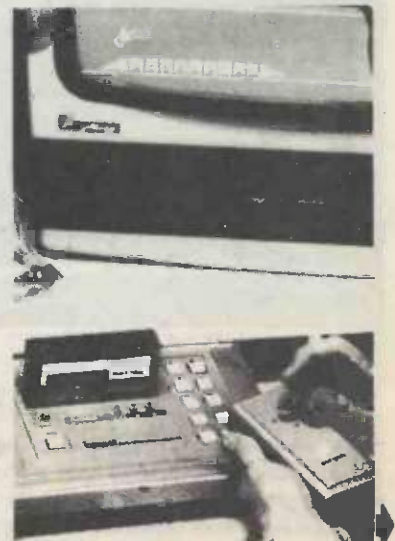● Fairchild are making a big fuss about having their F16K Dynamic 16K RAMs available at last. Access times vary from 150 ns to 300 ns.



ETI NEWS JAN 1979

## TALKING IN TRAINS

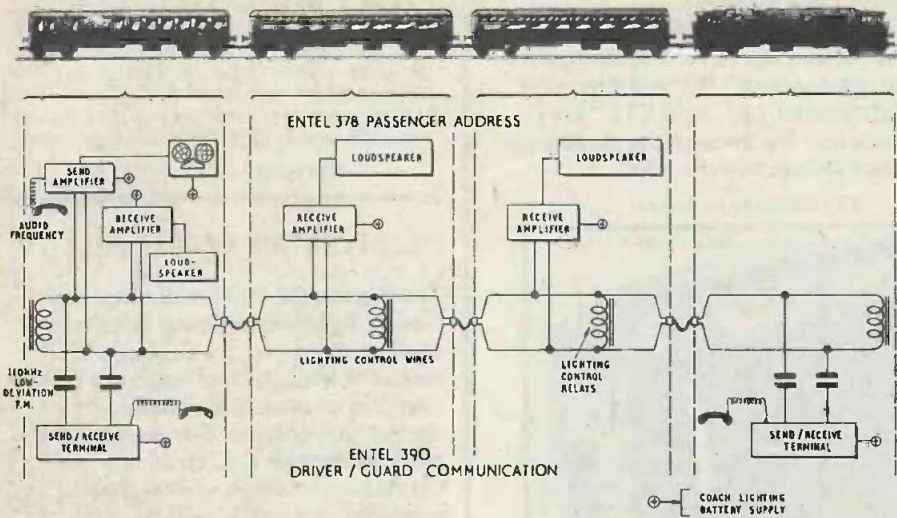

British Rail's plans for 150 mph trains include improved communication systems between drivers and guards. Also planned are passenger address systems.

A range of equipment – known as EMTL – has been designed specifically for this task by Britain's Nelson Tansley Ltd.

The main problem to be overcome was the impossibility of providing a special cable, running the length of the train, on which to carry the signals.

The equipment was therefore designed to accommodate any continuous circuit, for example, the control wires for the lighting relays which (in British Rail), are the only conductors always connected throughout any passenger train. In this case, departure from the ideal of a 600 ohm noise-free line is caused by the connexion across the wires of many relay solenoids, the impedance of which is not only complex, but variable.

ETI NEWS JULY 1972

## LASER MISSILE INTERCEPTOR

The US armed forces may soon have a laser missile interceptor. Air Force reports state that prototype deuterium fluoride lasers have been successfully tested at 'very very high' power outputs.

Power output is apparently so high that the laser beam burns straight through heavy gauge stainless nickel steel plate.

ETI NEWS JULY 1975


## BIAS – AUTOSELECTION

Cassette tape recorders that have been designed specifically for use with chromium dioxide tapes require special bias switching facilities.

At present this is done manually. However the latest BASF 'SM' chromium dioxide cassettes have a notch on the rear of the cassette (in addition to the tab now used to prevent erasure of recorded material) and, hope BASF – and Philips who are backing the system – future cassette players will have a switch mechanism actuated by this tab to bring in the necessary bias circuitry.

ETI NEWS APRIL 1972

ETI NEWS APRIL 1974

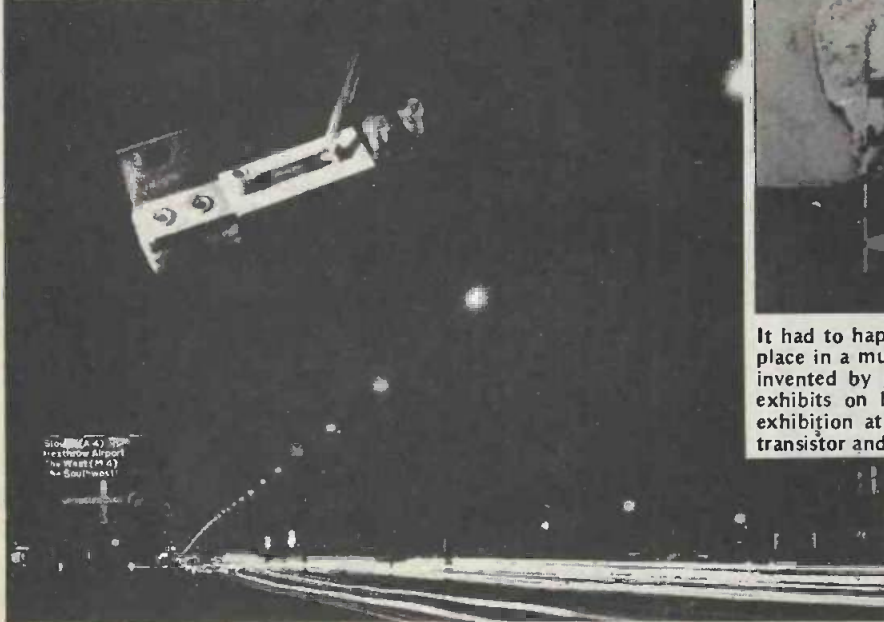

## LIGHTING THE WAY

Many local authorities are now using a street lighting control system in which a photoelectric cell measures the light level and varies the input to

a thick film heating element controlling a temperature sensitive switch. The street lights are therefore automatically switched on at dusk and off at dawn, which means that light is provided only when it is needed and ensures that electricity is not wasted.

1958



It had to happen. The integrated circuit is so old that it has earned its place in a museum. Doesn't it make you feel old? The world's first IC, invented by Jack Kilby of Texas Instruments in 1958, is one of three exhibits on loan from TI in Dallas for the 'Challenge of the Chip' exhibition at the Science Museum. The other two are the first silicon transistor and the first single chip microcomputer.

ETI NEWS MAY 1980

## GETTING READY FOR COMMERCIAL RADIO

Commercial radio is on its way; anyone doubting this should tune around the medium wave band where tests transmissions are already being conducted. Contracts for the supply of the transmitters and the aerials have been placed with EMI, the value of the order is put at £160,000.

ETI NEWS MAY 1973

shorts

- Tandy is doing well with its home computer in the USA, and is expanding, both physically and financially, that side of the business.
- New from GI — the Cricket chip. The AY-3-8910 is a programmable sound generator and is software controlled, needing only a power supply and clock to begin chirping or hooting or ...

Hong Kong King

Some numbers to tick off on your fingers. In the first six months of the year Hong Kong exported 16 million watches (worth £77m). These break down as 61% mechanical, 29% LCD and only 10% LED and quartz analogue com-

bined. Surprising LED figures eh? Germany developed a sudden lust for these non-tockers and their imports leapt up by 287%, putting them as the second largest consumers — behind the US and ahead of us!  
ETI NEWS NOV 1978

ETI NEWS OCT 1978

BE WARNED (IN A SMALL WAY!)

The Mini-Bleepitone 525 is a unit which provides a choice of two continuous signals of up to 80dBa with current consumption ranging from 3-15mA.



ETI NEWS JULY 1976

Its applications are wide, being ideally suited as a fault indicator mounted onto portable equipment and instrument panels, or for localised warning of such things as intruders and/or fire.

NEW LC DISPLAYS FOR WATCHES

A new series of Liquid Crystal displays have been announced by Beckman for digital watches. These display hours and minutes continually with either date or seconds, selected by a push-button. Contrast ratio is



20:1. power requirement is 1 micro-watt so that even with constant read-out battery life is over a year. LC modules are available for both 3V and 6V models and a CMOS compatible.  
Beckman Instruments Ltd.,  
Queensway, Glenrothes, Fife, Scotland.  
ETI NEWS OCT 1978

forget who not?

You know we've quite forgotten why we used this photo at all. Now let's see something to do with TV games? Anyway the editorial desks have been bereft of nice lady photos lately — so this one appeared as an oasis amid the dusty filing trays.  
P.S. Binatone the people who make the box in front — don't ask what box or in front of what or we won't



speak to you again — claim to now taken over half the TV game market — the magic 51% in fact.

ETI NEWS NOV 1978

Pocket Companion

Not just an electronic dictionary or a translator or an appointments diary or an encyclopedia, but something of all these rolled into one, the 'Brainbank' is hailed as the world's first pocket information centre and language laboratory.

Brainbank is programmed via a series of interchangeable, plug-in memory cells, so you have virtually unlimited information storage possibilities (armed with a bucket full of memory cells).

Each language cell, which contains 32K of ROM holds about 1200 of the most common

words, stored individually and in groups of up to fifty in categories such as travelling and food. The program also includes short phrases, automatically corrects spelling errors and explains words with double meanings (with its double entendre chip?).

The information centre's heart is a Mostek 3870 micro-processor. Memory cells are currently available on diet and nutrition, first aid, taxation and a thesaurus. New cells will become available every month. A custom cell service is also available.

Brainbank will cost around £150 plus £20 or less for each additional cell. We will tell you more about this little marvel, when we can get hold of one to play with.



ETI NEWS JAN 1980

## 300 MPH HOVERTRAIN - PUBLIC SHOWING


Computerised control and data recording equipment that can handle information from up to 413 different sources will be used in the development of Britain's tracked hovertrain - during its period of full-scale development.

From this console, commands will be transmitted by radio to the hovertrain and radioed signals from the measuring instruments inside the vehicle will be received, recorded and analysed.

The 25-ton vehicle straddles the track and is supported approximately an inch above it by a system of fans employing the hovercraft principle. The linear motor consists of an aluminium strip set into the top of the track as the motor's "stator", and a complex set of electrical windings mounted inside the body shell. Power is picked up from a trackside rail.

The train made its first run over a mile of the track recently, watched by visiting experts and the press from several countries. It performed perfectly during the slow-speed run and is now expected to reach speeds of up to 90 mph during the next two months.

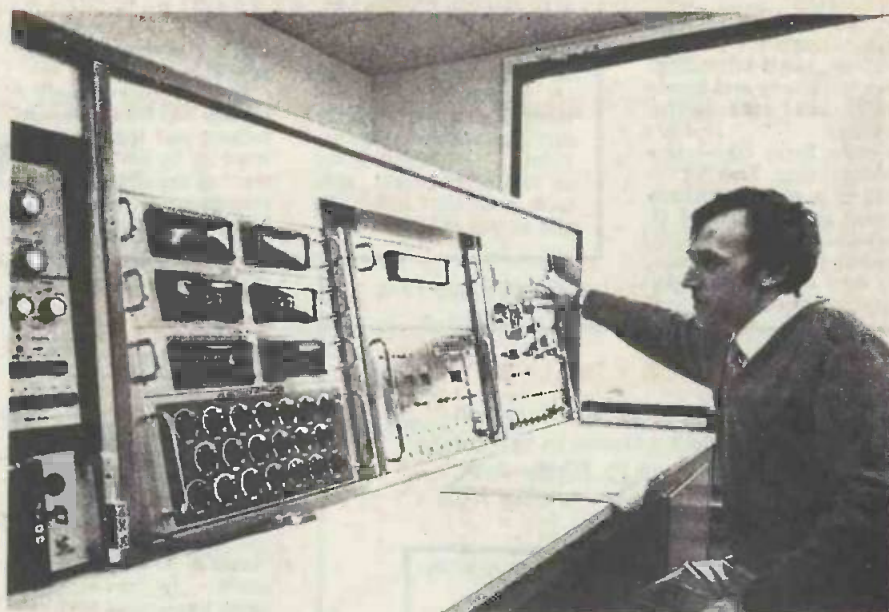The hovertrain has been designed and constructed by Tracked Hovercraft



ETI NEWS APRIL 1972 (OUR FIRST EVER NEWS ITEM!)

Ltd., a company set up by Britain's National Research Development Council, and would be capable of providing a link between central

London and the airport planned for Foulness, its passengers completing the journey in quiet pollution-free comfort in about 20 minutes.

## RED TAPE GAGS THE QUEEN!

In the wee small hours of January 19th 1903, Marconi established the first two-way communication across the Atlantic. Messages were exchanged between the American president Theodore Roosevelt and the British King Edward VII. To mark the 75th anniversary of this event, the Cornish Radio Amateur Club have organised a team of sixty local amateurs to run GB3 MSA (Marconi's Seventy-fifth Anniversary). The station was run 24 hours a day, from the

14th to the 22nd January, from the lounge of the Poldhu Hotel in sunny Cornwall - only metres away from the spot Marconi used.

Transmitting on 80m, 20m and 2m the team had already made 1 100 contacts in 51 countries when ETI contacted them on the 16th! All the equipment was owned by the club and its members and set up for the week specially. On the American side was another station, KM1 CC, based in Cape Cod. KM1 CC was run by

the local Barnstaple, Mass. radio club with the help of the Radio Club of America.

Now for the red tape... President Carter sent a message via KM1 CC and the Queen wanted to send a reply via GB3 MSA, just like Edward VII did back in 1903. The Home Office said that if she did, it would break a condition in all British amateurs licences - namely the one about not passing on messages from 3rd parties! So after 2 years preparation the Cornish Amateurs and the Queen were denied permission to reply to President Carter.

ETI NEWS MARCH 1978

## Something Bugging You?



With the increase in telephone tapping and boardroom bugging, Audiotel International have developed a simple to use, yet sophisticated successor to their Scanlock radio surveillance receiver. It is called the Scanlock Mark V8 and is a fast, easy means of detecting and locating an eavesdropping transmitter as well as being capable of routine 'sweep' searches of high level meetings rooms. Carried in a vehicle it can also locate any bleeper bug used for 'trailing'.

The Scanlock is not limited to the conventional radio receiver's range of 88-108 MHz. It covers the wider frequency spectrum of 10-1800 MHz and its automatic 'sweep' mode scans this range four times a minute. Finally all that is necessary is to press the 'Locate' button and use the hand-held wand to guide you to where the bug is located. The kit is the size of a small briefcase, weighing 6.3 Kg, complete with spare battery pack. There is also provision for mains usage. For further information contact Audiotel International Ltd at Saddlers Court, Yately, Surrey, GU177RX.

## CONCORDE BAN?

Whilst we are currently bombarded with PR material extolling the 'virtues' of the Concorde supersonic airliner it is interesting to note that in the USA Senator Alan Cranston has introduced a bill, co-sponsored by Senators Edward Muskie and Calborne Pell, to prohibit overseas supersonic transports from landing at any US airports or flying over US territory at supersonic speeds.

The SSTs which carry less than half the passenger load of a 747 make ten times as much noise on take-off and landing. ETI NEWS JULY 1972

## RICE LOGIC?

Later this summer - about June - National Semiconductor and Kellogg's are to hook-up on a promotional deal. All Kellogg cereal packets will carry coupons for reductions on National calculators. Barley credible is it not? ETI NEWS JULY 1976

**breadboard 78**  
At long last a show for the electronics enthusiast - Breadboard 78 will be held at Seymour Hall in London from the 21st to 25th of November - mark it in your diary now 'cos ETI will be exhibiting! If you are a firm and would like more details contact: Breadboard 78, Abbey Mead House, 23a Plymouth Road, Tavistock Devon PL19 8AU.  
ETI NEWS JUNE 1978

Step-by-step fully illustrated assembly and fitting instructions are included together with circuit descriptions. Highest quality components are used throughout.

# Sparkrite


BRANDEADING ELECTRONICS

NOW AVAILABLE IN KIT FORM



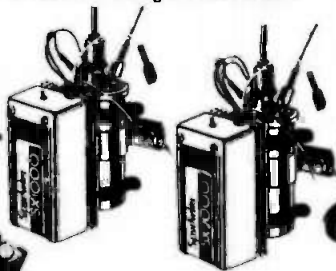
## SX1000 Electronic Ignition

- Inductive Discharge
- Extended coil energy storage circuit
- Contact breaker driven
- Three position changeover switch
- Over 65 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg. earth vehicles


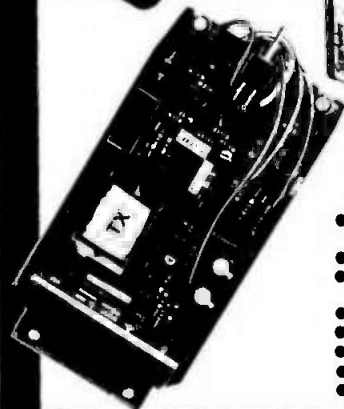
## SX2000 Electronic Ignition

- The brandleading system on the market today
- Unique Reactive Discharge
- Combined Inductive and Capacitive Discharge
- Contact breaker driven
- Three position changeover switch
- Over 130 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg. earth vehicles






## TX2002 Electronic Ignition

- The ultimate system ● Switchable contactless. ● Three position switch with Auxiliary back-up inductive circuit.
- Reactive Discharge. Combined capacitive and inductive. ● Extended coil energy storage circuit. ● Magnetic contactless distributor triggerhead. ● Distributor triggerhead adaptors included.
- Can also be triggered by existing contact breakers.
- Die cast waterproof case with clip-to-coil fitting ● Fits majority of 4 and 6 cylinder 12v neg. earth vehicles.
- Over 150 components to assemble
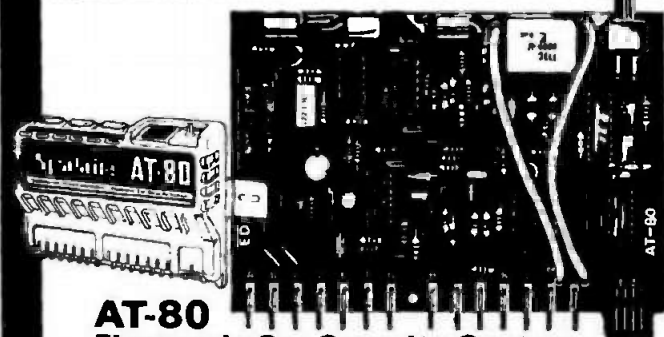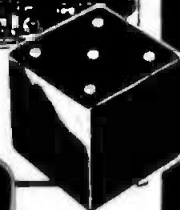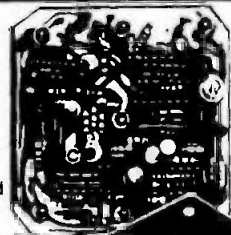
## MAGIDICE Electronic Dice

- Not an auto item but great fun for the family
- Total random selection
- Triggered by waving of hand over dice
- Bleeps and flashes during a 4 second tumble sequence
- Throw displayed for 10 seconds
- Auto display of last throw 1 second in 5
- Muting and Off switch on base
- Hours of continuous use from PP7 battery
- Over 100 components to assemble
- Supplied in superb presentation gift box



## AT-80 Electronic Car Security System

- Arms doors, boot, bonnet and has security loop to protect fog/spot lamps, radio/tape, CB equipment
- Programmable personal code entry system
- Armed and disarmed from outside vehicle using a special magnetic key fob against a windscreen sensor pad adhered to the inside of the screen ● Fits all 12V neg earth vehicles
- Over 250 components to assemble

## VOYAGER Car Drive Computer

- A most sophisticated accessory. ● Utilises a single chip mask programmed microprocessor incorporating a unique programme designed by EDA Sparkrite Ltd. ● Affords 12 functions centred on Fuel, Speed, Distance and Time. ● Visual and Audible alarms warning of Excess Speed, Frost/Ice, Lights-left-on. ● Facility to operate LOG and TRIP functions independently or synchronously.
- Large 10mm high 400ft-L fluorescent display with auto intensity. ● Unique speed and fuel transducers giving a programmed accuracy of + or - 1%. ● Large LOG & TRIP memories. 2,000 miles. 180 gallons. 100 hours. ● Full Imperial and Metric calibrations. ● Over 300 components to assemble. A real challenge for the electronics enthusiast!



All EDA SPARKRITE products and designs are fully covered by one or more World Patents

EDA SPARKRITE LIMITED 82 Bath Street, Walsall, West Midlands, WS 1 3DE England. Tel: (0922) 614791

	SELF ASSEMBLY KIT	READY BUILT UNITS
SX 1000	£12.95	£25.90
SX 2000	£19.95	£39.90
TX 2002	£29.95	£59.90
AT. 80	£29.95	£59.90
VOYAGER	£59.95	£119.90
MAGIDICE	£9.95	£19.90

PRICES INC. VAT. POSTAGE & PACKING

Allow 28 days for delivery

NAME \_\_\_\_\_ ET1.4.82

ADDRESS \_\_\_\_\_

I ENCLOSE CHEQUE(S)/POSTAL ORDERS FOR

£ \_\_\_\_\_ KIT REF \_\_\_\_\_

CHEQUE NO. \_\_\_\_\_  
24 hr. Answerphone  
PHONE YOUR ORDER WITH ACCESS/BARCLAYCARD  
SEND ONLY SAE IF BROCHURE IS REQUIRED

BRANDEADING BRITISH ELECTRONICS

CUT OUT THE COUPON NOW!

# ELECTRONIC GAMES

## COLOUR CARTRIDGE T.V. GAME



SEMI-PROGRAMMABLE T.V. GAME  
+ 4 Cartridges + Mains Adaptor  
Normal Price £73  
NOW REDUCED TO: **£39.50** inc VAT

## DATABASE T.V. GAME




FULLY PROGRAMMABLE CARTRIDGE T.V. GAME  
14 Cartridges available  
Normal Price £87.86  
NOW REDUCED TO: **£59** inc VAT

## ATARI T.V. GAME



The most popular T.V. Game on the market with a range of over 40 cartridges including SPACE INVADERS with over 112 games on one cartridge  
Normal Price £105.00  
NOW REDUCED TO: **£95.45** inc VAT

## SPACE INVADERS

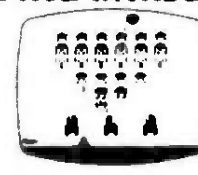

Hand-held Invaders Games available £19.95  
Invaders Cartridges available to fit ATARI RADOFIN ACETRONIC PHILIPS G7000  
Cartridges also available for MATTEL TELENG ROWTRON DATABASE INTERTON

## CHESS COMPUTERS



MANY UNITS ARE COVERED BY THE EXCLUSIVE SILICA SHOP 2 YEAR GUARANTEE

We carry a range of over 15 different Chess computers:  
Electronic Chess £29.95  
Chess Traveller £39.95  
Chess Challenger 7 £119.00  
Sensory 8 £119.00  
Sensory Voice £259.00  
**SPECIAL OFFERS:**  
VOICE CHESS CHALLENGER  
Normal Price £245 NOW £135.00  
SARGON 25/BORIS 25  
Normal Price £273.70 NOW £199.95  
All prices include V A T

## TELETEXT



## ADD-ON ADAPTOR £199


THE RADOFIN TELETEXT ADD-ON ADAPTOR

Plug the adaptor into the aerial socket of your colour TV and receive the CEEFAX and ORACLE television information services

### THIS NEW MODEL INCORPORATES:

- Double height character facility
- True PAL Colour
- Mains latest BBC & IBA broadcast specifications
- Push button channel change
- Unnecessary to remove the unit at switch normal TV programmes
- Gold plated circuit board for reliability
- New SUPERIMPOSE News Flash facility

## SPEAK & SPELL

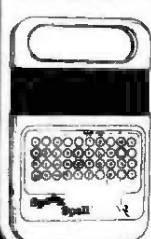

Normal Price £49.95  
NOW REDUCED TO:

**£39.50** inc VAT

Teach your child to spell properly with this unique learning aid Fully automatic features and scoring. Additional word modules available to extend the range of words.

## ADDING MACHINE

### OLYMPIA HHP 1010

Normal Price £57.21  
NOW REDUCED TO:

**£34** inc VAT

Uses ordinary paper! No need to buy expensive thermal paper!  
Fast adding PRINTER CALCULATOR 2 lines per second, 10 digit capacity. Uses normal adding machine rolls. Battery or mains operated. Size 9" x 4 1/2" x 2 1/2"  
*(Mains adaptor extra)*


## 24 TUNE ELECTRONIC DOOR BELL

Normal Price £18.70  
NOW REDUCED TO:

**£12.70** inc VAT

Plays 24 different tunes with separate speed control and volume control. Select the most appropriate tune for your visitor, with appropriate tunes for different times of the year!

## MATTEL T.V. GAME

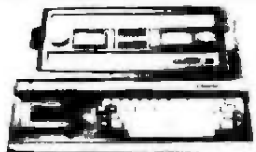

The most advanced T.V. game on the market 20 cartridges available. And now on KEYBOARD controls. **£199.95** inc VAT  
MATEL to a home computer with 16K RAM fully expandable and programmable in Microsoft Basic. Other accessories will be available later in the year.

## HAND HELD GAMES


### EARTH INVADERS



These invaders are a breed of creature hitherto unknown to man. They cannot be killed by traditional methods - they must be buried. The battle is conducted in a maze where squads of aliens chase home troops. The only way of eliminating them is by digging holes and burying them.  
Normal Price £29.95  
NOW REDUCED TO: **£23.95** inc VAT
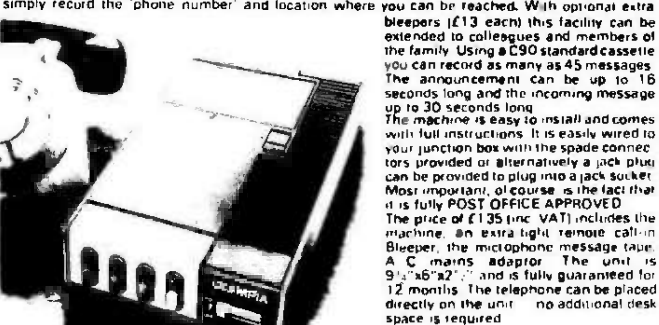
## THE OLYMPIA — POST OFFICE APPROVED TELEPHONE ANSWERING MACHINE WITH REMOTE CALL-IN BLEEPER

This telephone answering machine is manufactured by Olympia Business Machines, one of the largest Office Equipment manufacturers in the U.K. It is fully POST OFFICE APPROVED and will answer and record messages for 24 hours a day. With your remote call in bleeper you can receive these messages by telephone wherever you are in the world. The remote call-in bleeper activates the Answer/Record Unit, which will at your command repeat messages, keep or erase them, and is activated from anywhere in the world, or on your return to your home or office. The machine can also be used for message referral, if you have an urgent appointment, but are expecting an important call.



Extra bleepers (£13 each) this facility can be extended to colleagues and members of the family. Using a C90 standard cassette you can record as many as 45 messages. The announcement can be up to 16 seconds long and the incoming message up to 30 seconds long. The machine is easy to install and comes with full instructions. It is easily wired to your junction box with the spade connectors provided or alternatively a jack plug can be provided to plug into a jack socket. Most important, of course, is the fact that it is fully POST OFFICE APPROVED.  
The price of £135 (inc VAT) includes the machine, an extra light remote call-in bleeper, the microphone message tape, A C mains adaptor. The unit is 9 1/2" x 6 1/2" x 2 1/2" and is fully guaranteed for 12 months. The telephone can be placed directly on the unit - no additional desk space is required.  
**£135** inc VAT

## PRESTEL VIEWDATA




The ACE TELCOM VOX1000 Prestel Viewdata adaptor simply plugs into the aerial socket of your television and enables you to receive the Prestel Viewdata service in colour or black & white.

- Features:
- Simulated controls for easy, ready operation
  - Special graphics feature for high resolution
  - State of the art microprocessor controller
  - Standard remote telephone keypad with Prestel keys
  - Auto dialler incorporated for easy Prestel acquisition
  - True PAL colour encoder using reliable IC
  - Plasma filter and data line incorporated for minimum picture interference maximum fidelity
  - Includes convenient TV Prestel switchbox
  - Easily connected to standard home or office telephone lines
  - Fully Post Office approved

**SPECIAL PRICE £228.85** inc VAT

## HAND HELD GAMES

### GALAXY 1000

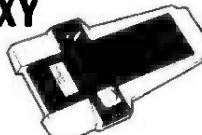

The 2nd generation Galaxy Invader. The invaders have re-grouped and have a seemingly endless supply of spacecraft whilst the player's arsenal is limited to just 250 missiles to be launched from 3 missile stations. You have to prevent the invaders landing or from destroying your home defences.  
Normal Price £24.95  
NOW REDUCED TO: **£19.95** inc VAT


**FOR FREE BROCHURES - TEL: 01-301 1111**



For free information brochures and samples, fill in and return to: Silica Shop, 1.4 The Mews, Hatherley Road, Sidcup, Kent DA14 4DX. Tel: 01-301 1111. Fax: 01-301 1111. E-mail: silica@silica.co.uk

For free information brochures and samples, fill in and return to: Silica Shop, 1.4 The Mews, Hatherley Road, Sidcup, Kent DA14 4DX. Tel: 01-301 1111. Fax: 01-301 1111. E-mail: silica@silica.co.uk

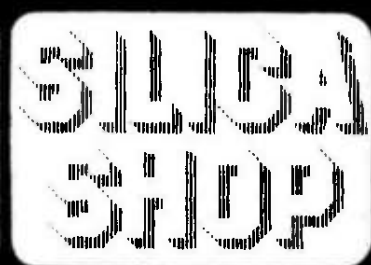**SILICA SHOP LIMITED** ETJ0482  
1.4 The Mews, Hatherley Road, Sidcup, Kent DA14 4DX  
Telephone: 01-301 1111 or 01-309 1111






## hammer fet-ish

A new range of low cost VMOS power FETs in plastic have been introduced by Siliconix. These devices are aimed at replacing conventional bipolar transistors in a great many applications. This development in VMOS technology has cut the price of such devices by a third enabling them to compete directly with bipolar devices.

ETI NEWS APRIL 1978

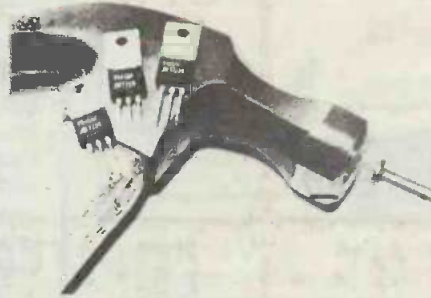

## CALCULATOR CHIPS NOW LESS THAN £1

Calculator chips prices continue their inexorable fall in price. Latest prices in the USA for four function eight digit MOS chips are now as low as 40p

ETI NEWS JULY 1975

to 80p. Even the complex scientific calculator chips are down to £6 or less compared to £20 this time last year.

MOS Technology Corporation for instance are selling a single chip scientific unit for £7.

ETI NEWS DEC 1977

## sailing into space.....

A 12 bladed solar sail spacecraft is a new candidate for mankind's first interplanetary shuttle. Designed to be employed in the 1980s its first use might well be a rendezvous with Halley's Comet in 1986.

The 'heliogyro' sail uses a helicopter type design with 12 'blades' composed of reflective aluminium plastic film, and deployed in two tiers of six each. After launch from the space shuttle, centrifugal force

would open the blades to their 4½ MILE length. (They're 28ft. wide). The craft sits in the centre of the array.

The craft would be slowly spun by the sun's photon radiation, and complete a rotation every three minutes. A square sail, and hence windjamming to the stars, was rejected in favour of the blades, which now fight it out with an ion stream propulsion system for NASA consideration.

## ACC AFTER ONE YEAR

Now moving into its second year of existence the Amateur Computer Club has now formulised its activities into a constitution and has a membership of over 200.

ETI NEWS AUG 1974

## Power Cuts On The Way

In 1968 your 20 inch colour telly using 90° deflection would have consumed over 200 W. Now, the figure is around 65 W. A new development from Finland will further reduce that to about 40 W.

The system, which results in a reduction of about 40% in power consumption, has been incorporated in the Salora G Series of portable colour sets. The design is basically a 90% efficient couple between the power supply and picture tube using an induction transfer system. The resultant cool running improves reliability and extends operational life.

● Bowmar has Texas's range and is homing in. Texas are being sued for \$3 million by Bowmar who allege the supply of a large number of defective calculator keyboards.

● XR4741 to you. Nothing to do with sci-fi but a new quad op-amp. Very low noise and better than a 741 in all respects. Available from RASTRA at 275 King St, Hammersmith, London W6. Ideal for audio projects where the hissing of summer circuits is not required.

● The Government's hi-fi firm, Strathem are to launch their new SM2000 turntable in the autumn, which will replace the SMA2 model. Once again the unit looks technically sound — maybe success at last for nationalised-fi?

ETI NEWS OCT 1978

## ANTI-SKID CONTROL

The first standard i.c.'s designed specifically for the automotive market have been announced by Fairchild. Both are complex linear circuits developed over the past two years as 'custom' circuits before being added to the standard product line.

ETI NEWS OCT 1973

## ELECTRONIC CHEQUEBOOK CALCULATOR

A pocket calculator that will hold and display bank cheque account balances for a year or more is shortly to be announced by the US Mostek Corporation.

During the times that the calculator is 'off' data is stored in a static shift register (drawing a mere 100 microamps). This data is then clocked solely when access is required.

The unit is expected to retail for less than £16 and will be built into a plastic chequebook holder.

ETI NEWS JULY 1975

## BUBBLING OVER

Next year Rockwell are hoping to launch their now developed one-megabit bubble memory price? One millicent per bit!

Their device can operate up to 300kHz and measures 10 x 9.5mm and is designed for a 1.8 micron bubble diameter. ETI NEWS SEPT 1977



The G Series, with its 16, 20 and 22 inch models, will operate from a standard 60A/hour 12 V battery for 15 hours, or from mains for as long as you pay your bills.

All the models feature automatic electronic tuning, fine

tuning and memory plus add-on options for remoted control, 12 V battery and video frequency interface unit.

Salora products are available in the UK from Salora (UK) Ltd, 25A Techno Trading Estate, Swindon SN2 6EZ.

## SPACE SHUTTLE ON THE TILES



Extremely pure silica glass has been manufactured for at least 40 years - longer than jet aircraft have been around. Now it is to aid and abet the

ultimate aircraft - the U.S. Space Shuttle. Made into tiles (composed of 96% silica glass) of which 34,000 are used, the material covers well over 70% of the surface of the Shuttle.

These tiles are incredible heat 'shedding' devices (see photo) and will be expected to withstand temperatures of up to 1260°C for 100 re-entries into the atmosphere. Previous heat shields were destroyed on re-entry.

Each tile is precisely milled to fit exactly against the curvature of the Shuttle body, thus making the composite craft as light as possible, and as aerodynamic as is feasible. This does however mean that no two of those 34,000 tiles are alike! Imagine the little man in a white coat with the job of fitting them to the aircraft - a huge 3-D jigsaw puzzle with only one solution out of 34,000 (i.e. 34,000 x 33,999 x 33,998...x 1) possibilities! Rather him than me.



ETI NEWS MARCH 1977

## solid state speech



If the latest goodie from Texas Instruments is as successful as we think it will be, the next generation will speak with an American accent! Called "Speak & Spell" it is a box that talks to the kids (with a 'standard' American accent),

and theoretically helps them pronounce new words correctly - it also compares how the kids spell the word with the correct (American) spelling, and indicates whether they gave the right answer.

ETI NEWS AUG 1978

## ORACLE ON AIR

ORACLE, ITV's Teletext system (see ETI, July 1975) began an on-air experiment on the ITV network on 30th June. Operating the experiment are two editorial teams and three computer systems. At ITN there is an editorial team (plus computer) for news and associated information. At London Weekend Television there will be an editorial team preparing public service and similar information pages, and the second computer. At Thames Television the third computer will be used to insert data into the network during the Monday to Friday broadcasting period with LWT taking over for the weekend transmissions. It is hoped that there will soon be sets with decoders in the main entrance lobbies of ITN House, London Weekend Television's South Bank Studios and Thames Television's Euston Studios, so that visitors can interrogate the system and see how ORACLE works.

ETI NEWS SEPT 1975

## WATCHES FACE COLLAPSE!

Five companies have dropped production of digital watches, due entirely to the price war raging around the product. Gruen, Benrus, Armin Litronix and Gillette have decided the wrist borne digit is not for them. Those still there are sufferin too. Bulova are expected to make a loss this year. Gillette in fact pulled out before they pulled in, scraping well laid plans to burst into the 'marketplace' at the eleventh hour.

ETI NEWS SEPT 1977

## £15 DOLBY RADIOS SOON?

Even the cheapest of domestic radio receivers may soon have Dolby circuitry inbuilt according to Alan Gregory of the Signetics Corporation, manufacturers of the NE545 Dolby IC chip.

Gregory believes that the inclusion of the chip (which will be sold to manufacturers for less than a dollar) will increase the price of domestic receivers by a pound at the most.

ETI NEWS APRIL 1975

## SCREEN TEST

The UK is now Hong Kong's largest market for TV games. We absorbed 26% of their export in the field, some 523,506 items if you please, in the first eight months of this year. Germany finished second

on 22% and the USA came third with 13%.

Somewhat of a surprise, and a shame, that we take more than the States of these items. I always thought we had more taste.

ETI NEWS JAN 1979

## A POCKET CALCULATOR IN EVERY HOUSEHOLD

"By the mid-70's the pocket electronic calculator will be as much an essential part of the household as the transistor radio is now". This is the prediction made by Sinclair Radionics.

Recent market research confirms that increasing numbers of the population are becoming aware of the possible applications of pocket electronic calculators. This is most marked in the educational field, at school and college levels although considerable interest is also being shown on the domestic front by husbands and wives who are able to use a calculator to help control the family budget.

ETI NEWS DEC 1973

## THE END OF THE AMP?

A British invention (three cheers!) could well mark the end of the amplifier as a circuit block. A new device called a 'voltage-to-current transactor' can do everything an op-amp can — but better. Invented by Professor Gosling and Carl Brinker, the device contains no passive components at all, and consists of a network of transistors.

The advantages are that it integrates smoothly rather than as a series of steps, follows an input quicker and with a wider dynamic range, is smaller in chip form and uses less external components. A VCT can also double as a transformer!

ETI NEWS OCT 1976

## Blonde Bombshell

Now be honest with yourself — aren't there times during those long cold winter days when you could do with one of these in your office. No, unfortunately I don't mean Blondie in the white pants. The blonde bombshells here are the brushed aluminium boxes of ITT Terryphone's new solid state intercom units.

The intercom, which doubles as a security and alarm system, consists of a master unit and from one to nine sub-units. The system is easily installed in many configurations.

Simple press-button-to-talk operation is featured on the master and sub-units. Each sub-unit can be called independently from the master unit, or all sub-units can be called simultaneously. Pressing the self-latching security button allows noises from children, equipment, burglars, etc to be picked up and transmitted to other parts of the premises. So, the intercom can be used as a security system in small businesses of a baby alarm at home.

Each sub-unit comes complete with cable and cable fixing pads for £20 each. The master unit costs £85 and comes with a mains plug and a screwdriver. Talking of Blondie — she can install an intercom in my office any time.

Further details of this system is available from ITT Terryphone, Station Approach, London Road, Bicester, Oxon OX6 7BZ.

ETI NEWS JAN 1980



## FIELD EFFECT LC DISPLAYS

Siemens incorporate the field effect principle in their new liquid crystal displays with low operating voltages.

10:28

All the liquid crystal displays in field effect technology have dark symbols on a light background and are suitable for reflection operation, all with high contrast ratios, low operating voltage and low power draw. Such features allow the displays to be driven by CMOS and other ICs.

ETI NEWS MARCH 1975

## BANDING TOGETHER

The Editor,  
Electronics Today International,  
36 Ebury Street,  
London SW1W 0LW.

Dear Sir,

We were most pleased to read the article "C.B. for Britain" in your July issue. The Citizens' Band Association is campaigning for the establishment of a VHF Citizens' Band in the UK and agrees with nearly all the points you make.

We have prepared a technical proposal for a VHF FM Citizens' Band which is being sent to the Home Office for discussion and contains a number of proposals to ensure that a British Citizens' Band suffers from few of the disadvantages of the American one. These proposals include:

1. Modulation shall be FM which avoids many problems of TVI, BCI and audio equipment break-in.
2. Each transceiver should contain an automatic identifying signal which is transmitted every time the transmit key is depressed. This means that anyone misusing Citizens' Band can easily be identified.
3. Transmission time should be limited to 75 seconds to prevent channels being monopolised.

Apart from the above, and a few purely technical proposals concerning standards which should be high enough to prevent interference to other services but not so unnecessarily high as to price Citizens' Band equipment out of the market, we believe that a British Citizens' Band should have a minimum of regulations.


Membership of the CBA is £1.50 p.a. for individuals and £5 for clubs.

Yours faithfully,

James M. Bryant,  
President, Citizens Band Association.

ETI NEWS OCT 1976

STEERING WHEEL? WOT STEERING WHEEL?

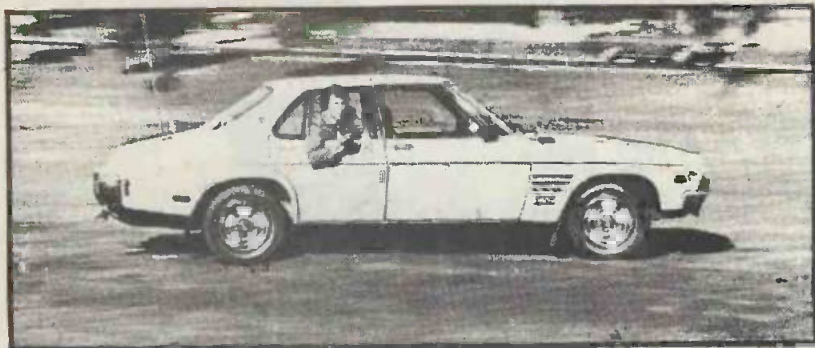

We had a very careful second look at this photograph, vowed to give up wine, women, and especially song, (for at least five minutes) then decided yes he was in the back seat, and yes the car was moving. Visions of a huge hoax flashed to the editorial mind — frenzied navvies rushing about with the backdrop to simulate movement — tiny men crammed into the wing mirrors steering via cunning Chinese arrangements of levers and gears. The mind boggled.

Alas the answer is nought so scandalous. Quite simply an Australian electronics enthusiast has packed his car full of voice recognition and MPU circuitry to the end that it will now

obey verbal commands — even by walkie-talkie up to a range of 12 miles (Naturally it obeys only its owners voice).

The car has a CCTV system installed which enables the driver to see behind him — very useful in injon country. Infra red sensors pick up red traffic lights and brake the car automatically — no we're not joking. Radar ranging maintains a constant distance with respect to the car in front, and sensors apply the brakes should the car come too close to any object — even people.

All this makes it a better driver than most of us.

ETI NEWS NOV 1976

right hook

In a historic ruling, the US Supreme Court has confirmed that private individuals have the right to buy or make their own telephone equipment and connect it to the US telephone network.

Under the ruling it will be legal to hook

ETI NEWS APRIL 1978

up as many devices as the user wishes — computer controlled systems, phone diverters, memory diallers, picturephones etc. etc. The only restriction is that the various bits must meet the relevant FCC requirements.

DIGITAL RECORDING

Japan's Nippon Columbia company have developed a digital recording technique. The new equipment, said to cost over £125,000 uses pulse code modulation.

Advantage of this technique is its virtual imperviousness to noise and distortion. Further details will be published as they come to hand.

ETI NEWS JAN 1973


LASER STICK FOR THE BLIND

A stick specially designed for blind persons gives the bearer a loud sonic signal in the event of impediment in his path at wrist height or above. The new device was commissioned by the Swedish Institute for the Handicapped and work on the project was initially financed by the Swedish Board for Technical Development (STU). The prototype stick comprises a 1.3-metre-long tube made of glassfibre-reinforced plastic. To it is attached a gallium-arsenide laser, a midget transmitter and receiver, and an amplifier. The power source is a tiny nickel-cadium accumulator. The laser beam's trajectory is almost at right-angles to the stick's length, and as such sticks are normally held forward at an angle of about 45 degrees to the ground, the beam is directed both upward and forward. The laser sends about 1000 pulses per second and when one of these meets an object — such as a lorry, car or a road sign — it is reflected back to the stick, where it is electronically transformed into a sonic warning signal to alert the bearer. ETI NEWS NOV 1972

Dynachem

ETI NEWS SEPT 1973

New Dimensions in Chemistry

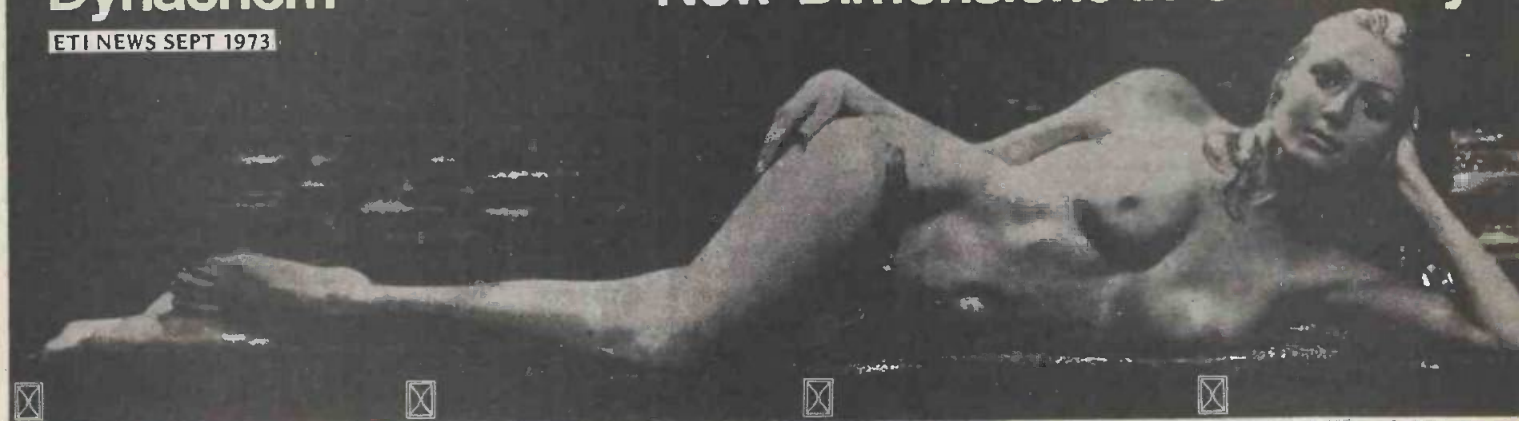

GIRL BY INSTALMENTS!

Electronics manufacturers throughout Europe are receiving a series of unusual sales leaflets from a manufacturer of specialist chemicals used in the making of

printed circuit boards.


Dynachem are sending out four leaflets spaced at regular intervals. On the front of each will be printed a tantalising part of the company's DYNAGIRL, an exquisite young lady well worth a second look. By keeping

the leaflets, the recipient will be able to build up a complete picture.


On the reverse sides will be information about the company's range of photo-resists, plating solutions, brighteners, cleaners and ancillary chemicals.
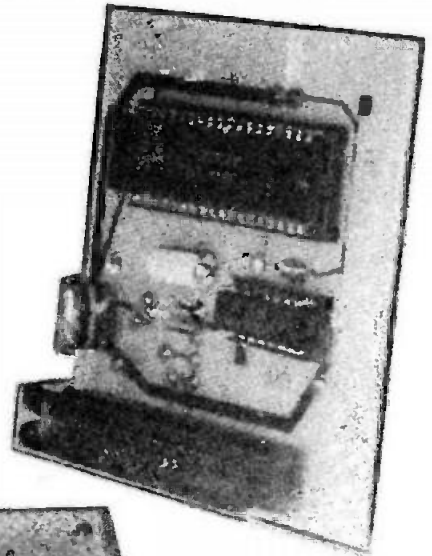
# ZX81 HARDWARE

- KEYBOARD KIT 20.75
- BUILT 25.50
- CASE 10.30
- BUILT & FITTED IN CASE 36.15



**EX STOCK!**

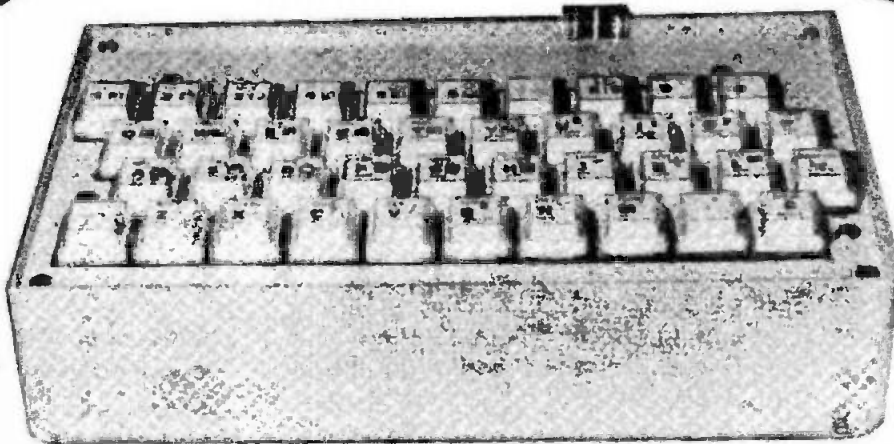


## IN/OUT PORT

- KIT 16.95
- BUILT 18.95

24 lines, in or out.  
Programmed by BASIC.

Spare switch  
48p

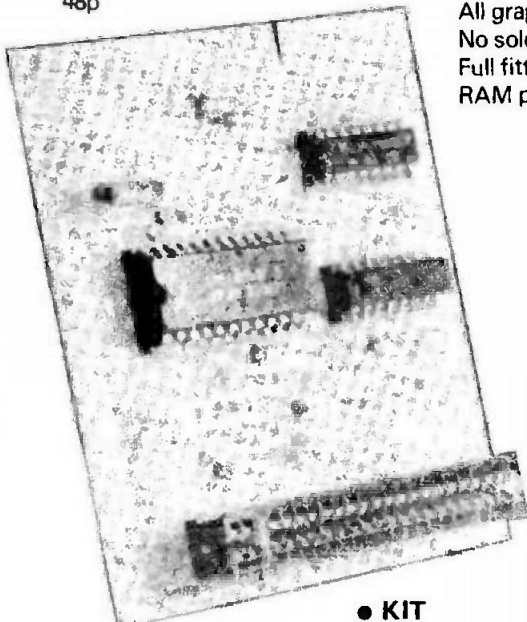40 typewriter keys.  
All graphics etc shown.  
No soldering (built version) just plug in.  
Full fitting and assembly instructions supplied.  
RAM pack operation not effected.





## MUSIC BOARD

3 outputs.  
.01Hz to 2Mhz.  
Programme by BASIC.

- KIT 16.95
- BUILT 18.95
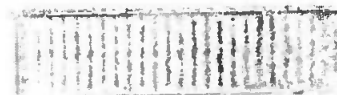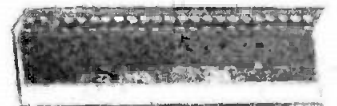
## CASE

Ready punched top.  
All screws supplied.  
Feet supplied.  
(For keyboard only, ZX81 does not fit inside).



## CONNECTORS

- ZX81 23 WAY 2.95
- MALE CONN 1.30
- IN-OUT/MUSIC BD 3.00
- 24 WAY RIBBON CABLE 1.40
- RAM PACK CONN 6.95

(Allows RAM pack to be mounted away from ZX81).

# REDDITCH ELECTRONICS

DEPT ET1  
21 FERNEY HILL AVE  
REDDITCH  
WORCESTERSHIRE  
B97 4RU

Prices include postage and VAT.  
Send SAE for free catalogue. Orders under £10 add 49p.

# ELECTROVALUE

MAIN DISTRIBUTORS FOR SIEMENS CAPACITORS, FERRITES, SEMI-CONDUCTORS, ETC. AND PRODUCTS OF OTHER LEADING HOUSES.

QUICK REF  
TTL I.C.  
SELECTION

## BOXES

VERO ALUMINIUM  
BIMBOX

DESCRIPTION	L	W	D	PRICE
<b>VERO INSTRUMENT CASES</b>				
21034	205	140	40	426p
21035	205	140	75	474p
21036	205	140	110	617p
21037	180	120	39	388p
21038	180	120	65	416p
21039	180	120	90	443p
21040	155	85	39	312p
21041	155	85	60	341p
21042	155	85	80	407p
21047	125	65	30	222p
21048	125	65	39	252p
21049	125	65	50	318p
<b>VEROPLASTIC</b>				
General purpose				
(black) 21024	72	47	25	50p
(white) 21025	72	47	25	50p
21390	120	80	36	78p
21391	180	110	65	146p
<b>ALUMINIUM</b>				
*pressed, with two IPK screws				
Ø7	70	133	38	85p
AB8	101	101	38	85p
AB9	101	70	38	85p
Ø10	101	133	38	85p
AB11	101	64	51	85p
AB12	75	51	25	85p
AB13	152	101	51	87p
AB14/2	127	89	64	99p
<b>BIMBOXES</b>				
*plastic ABS				
20002	100	50	25	87p
2004	121	66	40	105p
2005	152	82	50	123p
2006	192	113	61	216p
Plain Diecast				
5001P	50	50	25	88p
5002P	100	50	25	110p
5003P	113	63	31	130p
5004P	121	66	40	150p
5005P	152	82	50	195p
5006P	192	113	61	305p
Grey painted Diecast				
5001	50	50	25	115p
5002	100	50	25	145p
5003	113	63	31	190p
5004	121	66	40	145p
5005	152	82	50	322p
5006	192	113	61	425p

## SWITCHES

A selection of popular best-sellers from our great assortment of different types

MINIATURE TOGGLE		DUAL IN LINE (D.I.L.)			ROTARY TYPE	
250V AC/2A Chrome dolly		Single Throw	54p	Changeover	81p	One pole/12 way, Two pole/6 way, Three pole/4 way, Four pole/3 way all 40p each
Made in U.S.A.		Single Pole	85p	Single Pole	21p	
S7181 Single throw/Double pole	57p	4 Pole	125p	8 Pole	187p	
S7183 SP DT/Centre OFF	71p	8 Pole	187p	10 Pole	252p	
S7281 DPDT	85p	10 Pole	210p			
S7281 Single Pole/Three way	145p					
S7301 Three pole/DT	185p					

## CONNECTORS

We stock connectors from highly specialised types to the everyday kind that you must be sure of being able to get when you want them. Here are some examples. See also Catalogue 82.

AUDIO DIN			D-TYPE		
Ways	Plug	Socket	Ways	Sock	Plug
2	8p	8p	9	104p	78p 130p
3	14p	8p	15	147p	106p 139p
4	15p	14p	25	218p	150p 152p
5(180°C)	14p		37	315p	210p 160p
6	18p	20p			
7	19p	19p			

## PANEL MOUNTING METERS

**SPECIAL OFFER TO MARCH 31st**  
Panel mounting meters offered in the following F.S.D. ranges:—  
0-50µA, 0-100µA, 0-500µA, 0-1mA, 0-5mA, 0-10mA, 0-50mA, 0-100mA, 0-500mA, 0-1A  
Normal price, each **£2.69** Special offer price to Mar. 31 **£2.20**

## SABTRONICS

**FREQUENCY METERS**  
Model 8000B: 9-digit 1GHz Frequency Meter.  
Professional specification: £160.00  
2015A Bench DMM (LCD) £83.00  
2035A Hand-Held DMM (LCD) £52.00  
8110A 3 digit 100MHz DFM £57.00  
8610A 8 digit 600MHz DFM £82.00  
5020A 1.200KHz Function Generator, Sine, Squarer, Triangle and separate TTL Square wave outputs £79.00  
S.a.E. brings full details

## TRANSFORMERS

**BUDGET RANGE All primaries 240V**

SECONDARIES	5VA	15VA	24VA
0.6, 0-6	£2.85	£3.40	£4.40
0-12, 0-12	£2.85	£3.40	£4.40
0-15, 0-15	£2.85	£3.40	£4.40
0-20, 0-20	£2.85	£3.40	£4.40

**CHARGER TYPES Secondaries**

0.9-17V 1A	£3.15
0.9-17V 2A	£3.70
0.9-17V 4A	£4.70

(giving about 14V on full load)

## TOROIDAL RANGE

For details of secondary outputs, please see current I.L.P. Advertisements  
All primaries — 240 Volts  
30VA — £5.25; 50VA — £6.40; 80VA — £6.80; 120VA — £7.75; 160VA — £10.10;  
225VA — £11.65; 300VA — £13.50; 500VA — £17.25  
Remember — C.W.O. Orders (UK) are sent post paid if value £6.00 or over

## HANDY PACKS

Save you time, trouble and money

**RESISTORS**  
Each pack contains 100 in one decade quantities of each value according to popularity — ideal for general stock.  
RD1 (1-8.2Ω) RD2 (10-82Ω) RD3 (100-820Ω) RD4 (1K-8K2) RD5 (10K-82K) RD6 (100K-820K) RD7 (1M-10M) Price £1.50 each  
CAPACITORS Type CP1 Price £4.20  
Contains 100 ceramic capacitors, most values 1.8pF to 0.1µF, quantities of each according to popularity.

## Heat Sinks

Types 5F2, 5F, 18F2, 18F, 224F, 266F 14p each  
2Y-T066 £1.23  
2Y-T03 96p  
TV3 29p  
TV35 10DN £1.98  
6W4 (Drilled) £4.30  
Many other types and sizes in stock

## ANALOGUE IC SELECTION

741CB	18p
748CB	36p
7555	85p
CA3290E	95p
CA3130E	95p
CA3140E	55p
LM380N	99p
LM381	£1.51
LM3914N	£2.68
NE555V	23p
NE566A	79p
TDA2030	£1.45
TL071CP	46p
TL072CP	75p
TL074CN	£1.20
UAA170	£1.52
XR2205	£4.80
ZN414	£1.22
ZN425E	£3.90

## MORE POWER TO YOUR £

Start with CATALOGUE 82 and our newest price list (effective to June 1st) and see how much you save on ordering — and see too how Electrovalue service gives you confidence and satisfaction no matter what the size of your order. Send 70p for your Catalogue (A4 68 pages) by return. It includes a free voucher for 70p spendable on orders for £10 or more.

SEND FOR YOUR COPY AND START SAVING NOW!

## ORDERING DISCOUNTS & VAT

V.A.T. — PLEASE NOTE ALL PRICES IN THIS ADVERTISEMENT ARE EXCLUDING V.A.T. 16% MUST BE ADDED TO THE TOTAL VALUE OF YOUR ORDER WHEN PAYING.  
DISCOUNTS 5% allowed on orders £23.00 and over; 10% on orders £57.50 and over except for a small number of items with prices showing Net or N.  
POSTAGE — Free on C.W.O. orders in U.K. over £6.00 in value. Under — please add 50p handling charge.

## COMPUTER CUSTOMERS

Are invited to contact our associates EV COMPUTING LTD.  
700 Burnage Lane, Burnage, Manchester M19 1MA  
Telephone 061 432 4945

7400	.15
7401	.15
7402	.15
7403	.16
7404	.16
7405	.15
7406	.25
7407	.24
7408	.21
7409	.18
7410	.15
7413	.15
7414	.63
7420	.15
7430	.15
7440	.13
7442	.45
7443	.90
7444	.50
7447	.73
7448	.67
7450	.13
7451	.13
7453	.13
7454	.13
7460	.13
7470	.24
7472	.26
7473	.26
7474	.23
7475	.42
7476	.30
7480	.35
7482	.73
7483	.52
7486	.74
7488	1.59
7489	.28
7491	.71
7482	.43
7493	.40
7494	.55
7495	.54
7496	.54
7497	.85
74100	.42
74104	.27
74107	.47
74121	.27
74123	.47
74125	.46
74126	.45
74141	.54
74151	.43
74164	.75
74155	.46
74156	.46
74157	.48
74190	.70
74192	.70
74193	.70
74833	.95
741S00	.14
741S02	.14
741S04	.16
741S05	.23
741S06	.20
741S10	.19
741S11	.20
741S14	.58
741S20	.18
741S30	.21
741S323	.22
741S37	.24
741S38	.35
741S42	.58
741S47	.89
741S51	.25
741S73	.30
741S74	.30
741S75	.44
741S76	.30
741S85	.80
741S86	.38
741S90	.44
741S92	.58
741S93	.57
741S107	.40
741S112	.38
741S123	.82
741S125	.45
741S126	.42
741S132	.80
741S136	.40
741S137	1.10
741S138	.45
741S139	.70
741S145	1.20
741S148	1.65
741S151	.77
741S153	.77
741S155	.94
741S156	.94
741S157	.50
741S161	.78
741S163	.90
741S169	.90
741S165	.75
741S166	1.85
741S173	1.00
741S174	.85
741S175	.94

More still in Cat 82 as well as semi-conductors in great variety

## ELECTROVALUE LTD

Head Office and Shop (ALL mail order and correspondence) Dept ET14, 28 St Jude's Road, Englefield Green, Egham, Surrey TW20 0HB Telephone — Egham 33603 (STD 0784; London 87) Telex 264475  
NORTHERN BRANCH (Personal shoppers only) 680 Burnage Lane, Burnage, Manchester M19 1MA Telephone (061) 432 4945

ETI NEWS SEPT 1981


## Mini Discs

Philips, Sony and PolyGram have declared the Compact Disc Digital Audio System ripe for production. These companies are unanimous in the belief that this new

system will eventually replace the LP as we know it. PolyGram Records Operations and CBS/Sony have now put their productions on Compact Disc. It is not expected that the CD will be on the market before the autumn of next year.
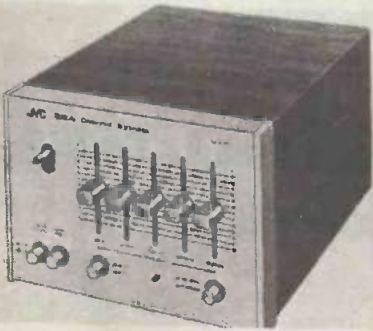
## STEREO CONTROL UNIT

Connect this unit to your existing power amplifier, and at your fingertips you will have a degree of control over the audio spectrum previously unattainable with conventional tone control systems. JVC's unique Model SEA-10 takes the full audio range of 20 to 20,000Hz and divides it up into five discrete frequency bands centred at 40, 250, 1000, 5000, and 15,000Hz. Each band can then be varied independently by  $\pm 12$ dB using the professional type slider controls with 2dB click stops.



ETI NEWS JULY 1973




ETI NEWS MAY 1975

## CARTRIDGE PERCUSSION UNIT

Bandmaster Limited of Gloucester Street, Glasgow, have designed a rhythm unit called the Powerhouse

which uses multi-track continuous tape loop to produce multi bar synchronised "live" percussion rhythms.

## DIGITAL MULTIMETER FROM ADVANCE

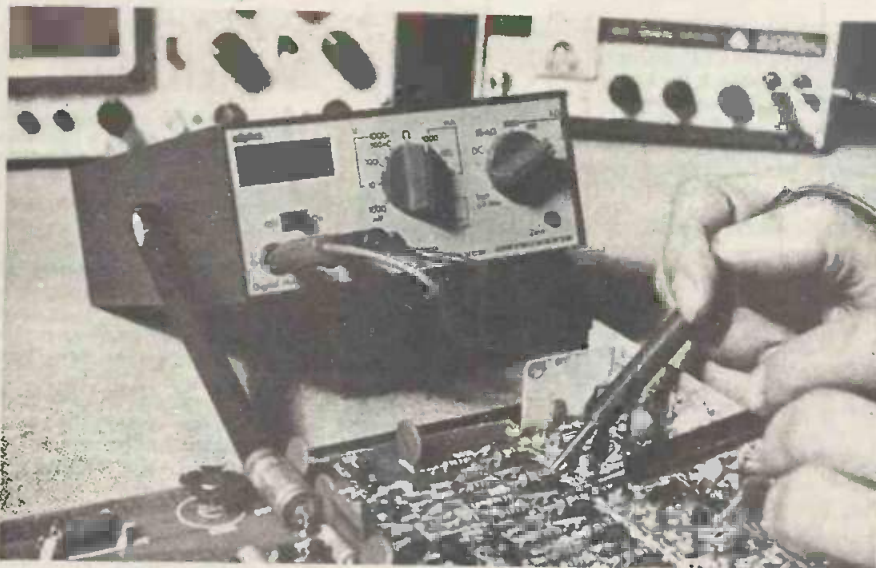

The way things are going, the adjective 'digital' will soon be dropped when talking about test gear. The advantages of digital readout are overwhelming compared to the standard meter (which has of course an analogue readout) and most new quality

test equipment utilises direct digital readout. One of the recently introduced DMM's is the Alpha from Advance Electronics; amongst the many attractive features is the price of £55.

ETI NEWS JUNE 1973

## MPG meter.....

A device called a Mileage Computer (what else?) from the Young Corporation in America is designed to produce a digital readout of miles per gallon being obtained from a vehicle at any given instant.

The device is composed of speed and distance sensors, fuel level indicator and calculator circuit. A sensor attached to the speedo picks up pulses every revolution to provide some of the info needed.

The MPG meter will sell at around \$20 in the USA. ETI NEWS DEC 1977

## COLOUR PREJUDICE?

Official figures for the number of homes with colour TV's, i.e. those with a license, have just exceeded 50% of the total. Some lesser mortals might well be tempted to conjecture how high the total would be if the un-licensed felons in our midst could be stood up and counted. Naturally we refrain from any such thoughts.

ETI NEWS DEC 1976

## TELEPHONE COMPONENTS

High-standard telephony today relies on components and function elements whose design and properties render them equally suitable for use in completely different fields. Read-only memories, MT components, keylock connectors and automatic cutouts are some examples of such components.

The MT (magnetic-core transistor) component developed detection of switching criteria in dc signalling systems, has a magnetic core with a rectangular hysteresis loop to detect signals which are amplified by the transistor. The core and transistor circuits are operated at the same potential and the defined Yes/No statements can be evaluated electronically or via relay circuits.

ETI NEWS APRIL 1973



## CMOS IN PLASTIC PACKAGES

Motorola Semiconductors have just announced that 39 devices from their standard CMOS logic family are now available in plastic packages. In the past, ceramic packages have been used for all CMOS devices

ETI NEWS SEPT 1973

## FAIRCHILD TO MAKE CONSUMER PRODUCTS

The USA's Fairchild group are actively planning to enter the consumer products market, according to a usually reliable source.

Fairchild's first products are believed to be a low-end of the market one-chip hand-held calculator with 8-12 digits. However several industry commentators query Fairchild's ability to produce the necessary MOS chips, quoting Lester Hogan's (president of Fairchild) own description of his company's performance in the MOS field as 'disappointing'.

ETI NEWS JUNE 1974

## PLASTIC BOXES

Vero Electronics Limited have recently become distributors for the Odenwaller Kunststoffwerk range of plastic products which include a range of plastic boxes. These are manufactured from high impact polystyrene, which is suitable for machining, engraving and silk screen printing. The upper portion of the box is coloured light grey and the lower portion, dark grey. The latter is provided with integral fixing points for circuit boards. The boxes can be free standing or wall mounting and should provide an attractive enclosure for reader's projects.

Vero Electronics Limited, Industrial Estate, Chandler's Ford, Eastleigh, Hants.

ETI NEWS JAN 1974



## SOVIET RADAR BLAMED FOR HIGH HEART DISEASE

A Russian radar tracking station near the Finnish town of Ilomaritsi may be responsible for a sharp increase in heart disease and cancer according to Dr. Milton Zaret, an American microwave expert.

The Finnish border towns have the highest rate of heart disease in the world and cancer has increased inexplicably.

ETI NEWS JULY 1975

## BLUE RESEARCH

Your choice of LED colours might include blue in the not so distant future. The new devices, being developed by Siemens, use silicon carbide and are predicted to have a forward voltage drop of 4 V at 50 mA.

ETI NEWS OCT 1979

\* Polaroid are about to release an automatic focusing camera that uses an ultra-sonic transducer to measure distance.

\* Computers stores in the US are opening up literally every day — we have just heard that 700 have been identified by someone preparing an exhibition! In addition to those dedicated to Home computers, office equipment suppliers and camera shops are at the forefront when it comes to jumping on the bandwagon; even Macey's stores have now got a computer department in some of their stores.

\* Sanyo have demonstrated a 6 mm thin solid state green and black television. The display is made out of 6,144 green LEDs in an area only 50 mm by 75 mm. They hope to have a commercial set by 1981.

\* A radar based overspeed detector is in use in the U.S. of A, the unit measures your speed and lights up a neon sign saying YOUR SPEED IS ... REDUCE SPEED. The unit is very effective, only problem was the local hot-rodders using it to check their top speed! Problem solved by limiting display to 75 instead of 99.

ETI NEWS SEPT 1978

## the little cb that santa forgot

Citizen Band radio manufacturers around the world are crying into their transceivers after Xmas. They expected a boost to sales to revive their drooping business, and it didn't materialise. Seems no-one wanted to contact anyone else — not even the reindeer.

ETI NEWS MARCH 1978

## Watch This!

If you're sick of digital watches, how about taking a look at this watch from Casio. It's all analogue, but with a difference. It's fully electronic and has no moving parts. It uses LCD and has conventional hours, minutes and sweep seconds hands. The Model AN8GL is designed to be attractive and fashionable, face colour matches the synthetic strap. Hour positions are marked by standard Roman numerals and all the time settings and adjustments are handled by two buttons, keeping the compact gold-plated watch case simple and uncluttered. The display shows hour and minute hands, and seconds indication is by a third sweep hand or as a series of marks on the face edge to show accumulated seconds. Accuracy is to within 15 seconds a month. RRP is £27.95, but products of this type are often sold cheaper. Further information can be obtained from Casio Electronics Co Ltd, 28 Scrutton Street, London EC2A 4TY.

ETI NEWS NOV 1981





# GREENWELD

443A Millbrook Road Southampton SO1 0HX


All prices include VAT at 15% — just add 50p post

## CONGRATULATIONS TO ETI ON THEIR 10TH ANNIVERSARY

Here are some special Bargains to celebrate!!!

ET1 Electrolytic Pack — 10 each of these PC mntg types: (uF/V) .47/50, 1/50, 2.2/50, 4.7/40, 10/40, 22/50, 33/25, 47/16, 47/40, 100/16, 100/35, 220/63, 330/25, 1000/16. Total 150 caps for £6.95  
 ET2 1A rects — 25 each 1N4001, 3, 5 & 7. Total 100 for £3.95  
 ET3 Minibox polyester caps — 10 each of .01/630, .022/250, .047/400, .068/250, .1/100, .22/100, .33/100, 47/100, 1/100. Total 90 caps for £3.50  
 ET4 TTL pack — 5 each of: 7400, 02, 05, 10, 13, 20, 30, 47, 73, 74, 86, 90, 93, 96, 107, 121. Total 80 chips for £14.95  
 ET5 100V 12A stud mntg diodes — 10 for £2  
 ET6 1/2 in 8R speakers — 2 for £1  
 ET7 200V 4A Triacs — 6 for £1  
 ET8 1500uF 40V PC mntg caps. 5 for £1  
 ET9 750uF 16V axial caps — 12 for £1  
 ET10 1/2W 5% CF resistors, 20 each of these values: 2R2, 4R7, 6R8, 22R, 33R, 47R, 68R, 150R, 270R, 560R, 820R, 1k2, 1k5, 2k2, 3k3, 12k, 68k, 82k, 120k, 180k, 750k, 3M9, 6M6, 6M8, 10M. Total 500 for just £3.50  
 ET11 Mains transformer, 12—0—12V 50mA. 2 for just £1  
 ET12 100 1N4148 diodes £2

### STABILIZED PSU PANEL

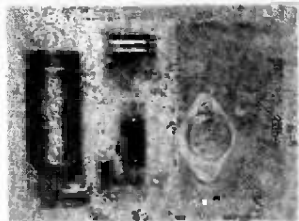

A199 A versatile stabilized power supply with both voltage (10—30V) and current (20mA—2A) fully variable. Many uses inc bench PSU, Nicad charger, gen. purpose testing. Panel ready built, tested and calibrated. £7.75. Suitable transformer and pots £6.00. Full data supplied.

### SPECIAL ETI BIRTHDAY OFFER (Aren't we nice!!!!)

The above PSU, transformer, pots, heat-sink, 0—30V and 0—2A meters, switch, terminals, neon and smart cabinet to mount it all in, plus wiring diagram & info.

JUST £24.95

### MIXED LED PACK

All new full spec by Micro, Fairchild, etc. Red, Yellow, Green, Amber, Clear, 3mm & 5mm. Pack of 50 asstd £3.95; 250 £15

### 1W AMP PANELS

A011 Compact audio amp intended for record player on panel 95 x 65mm including vol control and switch, complete with knobs. Apart from amp circuitry built around LM380N or TBA820M, there is a speed control circuit using 5 transistors. 9V operation, connexion data supplied. ONLY £1.50.

### OP—AMP PSU KIT

A198 All parts + instructions to make a 50mA + 15, 0, —15V supply from mains input. Only £1.95

### P.C. ETCHING KIT MkV

The best value in etching kits on the market — contains 100 sq ins copper clad board, Ferric Chloride, Etch resist pen, abrasive cleaner, two miniature drill bits, etching dish and instructions. All for £4.95.

### PANELS

Z521 Panel with 16236 (2N3442) on small heat sink, 2N2223 dual transistor, 2 BC108, diodes, caps, resistors, etc. 60p.  
 Z527 Raed relay panel — contains 2 x 6V reeds, 6 x 2S030 or 2S230, 6 x 400V reeds + Ra. 60p.  
 Z529 Pack of ex-computer panels containing 74 series ICs. Lots of different gates and complex logic. All ICs are marked with type

no. or code for which an identification sheet is supplied. 20 ICs £1.00; 100 ICs £4.00  
 A504 Black case 50 x 50 x 78mm with octal base. PCB inside has 24V reed relay, 200V 7A SCR, 4 x 5A 200V reeds, etc. 60p.

### CHEAP CHIPS

78477 Sound IC £1.25  
 2102A RAM 8 for £3  
 MK4027 shift reg. 8 for £6  
 uA78MG + volt reg £1.00  
 uA79MG — volt reg £1.20  
 74LS112 Dual Flip-Flop 8 for £1  
 TIL311 Hexadecimal display with decode 0—9 and A—F. With data £3.50.

### DEVELOPMENT PACKS

These packs of brand new top quality components are designed to give the constructor a complete range so the right value is to hand whenever required. They also give a substantial saving over buying individual parts.

K001 50V ceramic plate capacitors, 5%, 10 of each value 22pF to 1,000pF, total 210 £4.80.  
 K002 Extended range 22pF to 0.1. Values over 1000pF are of a greater tolerance. 10 of each value 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820, 1000, 1500, 2200, 3300, 4700, 6800, 01, 015, 022, 033, 047, 01. PRICE £7.66

K003 C280 or similar Polyester capacitors, 10 each of the following: .01, .015, .022, .033, .047, .068, .1, .15, .22, .33 and .47uF PRICE £5.40

K004 Mylar capacitors. Small size, vertical mounting 100V, 10 each of the following: .001, .0012, .0015, .0018, .0022, .0027, .0033, .0039, .0047, .0056, .0068, .0082, .01. Total 130 capacitors PRICE £4.70

K007 Electrolytic capacitors 25V working small physical size axial or radial leads. 10 each of the following: 1, 2.2, 4.7, 10, 22, 47, 100uF. Total 70 capacitors. PRICE £3.59

K008 Extended range, as above, also including 220, 470 and 1000uF all at 25V. Total of 100 capacitors. PRICE £6.35

K021 CR25 resistors or similar, miniature 1/4 watt carbon film 5%, as used in nearly all projects. 10 of each value from 10 ohms to 1M. E12 series. Total 610 resistors. PRICE £5.95

K041 Zener diodes 400mW 5%. 10 each of all the values from 2V7 to 36V. Total 280 zeners. PRICE £15.95

K051 LEDs. Pack of 60 comprising 10 each red, green and yellow 3mm and 5mm together with clips. PRICE £8.95

### UHF TUNERS

GJE Sylvania F4720 Channels 21—69. Brand new, no data £3.00.


### VHF TUNERS

Type F3720 (CCIR) by Sylvania. Bargain at only £3.00.

### RELAY/TRIAC PANEL MKII

Z537A PCB 100 x 75mm containing a wealth of components: 2 x 12V DPCO min relays, 5C146E 10A 400V triac, 555 timer, 10 x 1N4001 diodes, 2N5061 SCR, 2 x 3mm LED's 3 x 2N3704, R's & C's — Amazing value — if bought separately, parts would cost around £8!! Our price for the panel, just £1.50

### LIE DETECTOR

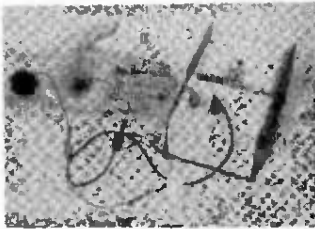

Not a toy, this precision instrument was originally part of an "Open University" course, used to measure a change in emotional balance, or as a lie detector. Full details of how to use it are given, and a circuit diagram. Supplied complete with probes, leads and conductive jelly. Needs 2 x 1.5V cells. Overall size 155 x 100 x 100mm. Only £7.95 — worth that for the case and meter alone!!

### 1000 RESISTORS £2.50

We've just purchased another 5 million preformed resistors, and can make a similar offer to that made two years ago, at the same price!! K523 — 1000 mixed 1/2 and 1/4W 5% carbon film resistors, preformed for PCB mntg. Enormous range of preferred values. 1000 for £2.50; 6000 £10; 20k £36

### 200 ELECTROLYTICS £4.00

K524 Large variety of values/voltages, mostly crooped leads for PCB mntg, 1—1000uF, 6—63V. All new full spec components, not chuck-outs!! 200 £4; 1000 £17.50

### CAPACITOR BARGAINS

2200uF 100V cans 80 x 40mm dia 75p; 10/£5.90;  
 220uF 10V axial 5p; 100 £2.30; 1000 £16; 400 + 100uF 275V 102 x 44mm dia. 75p; 10 £5.50;  
 200uF 350V, 100 + 100 + 50uF 300V can 75 x 44mm dia. 40p; 10/£3; 100/£20; 100uF 25V Axial £3/100;  
 0.33uF 50V rad. £1.50/100, £12/1000  
 0.47uF 50V rad. £1.50/100, £12/1000  
 22uF 50V rad £3/100, £24/1000  
 Electrolytics: 10u40V PC mntg 25/£1.25 100/£3; 4.7u/63V PC mntg same price  
 1250u/25V can 10/£1.60 100/£10  
 1500u/40V can 10/£2.20 100/£15  
 800u/250V can 10/£5.50 100/£44  
 400u/400V can 10/£8 100/£56  
 100u/350V, 100 + 100 + 50/300V (all in one can) 10/£5.00 100/£36.00

### TOROIDAL TRANSFORMER

110mm dia x 40mm deep. 100/240V pri. Sec 18V 4A, 6.3V 1A, 240V 0.3A. Ideal for scopes, monitors, VDU's etc. Special low price £5.95

### TRANSFORMERS

Mains primary, 50V 20A sec. £20.00  
 Mains pri. 110V 15A sec £30; 20A £40.00

### DISC CERAMICS

0.22uF 12V 9mm dia. Ideal for decoupling. 100 for £2.75; 1000 £28.00  
 0.05uF 12V 15mm dia. 100 £1.50; 1000 £12.00  
 Pack of disc ceramics, assorted values and voltages — 200 for £1.00

### 1N4006 DIODES

Special purchase of 1A rects, Russian made. Packed in boxes of 300, £8.50 per box; 4 boxes £30.00; 10 boxes £75

### AUDIBLE WARNING DEVICE

Solid state circuit drives high efficiency transducer to give high output. Voltage reqd 6—18V. Can also be driven direct from TTL or CMOS. Module size 45 x 21 x 12mm. Comprehensive data supplied £2.00

### NICAD CHARGER

Versatile unit for charging AA, C, D and PP3 batteries. Charge/boost switch. LED indicators at each of the 8 charging points. Mains powered. 210 x 100 x 80mm. £7.95

### ULTRASONIC ALARM — £14.95

Originally made to retail at over £50, these neat units housed in a 120 x 100 x 45mm case are brand new and boxed. They work by transmission of a 40kHz beam which responds to movement by detecting the Doppler freq. shift. Mains operated with internal buzzer and provided with date, these units are excellent value at only £14.95

### SOLENOIDS AND RELAYS

W921 Solenoid rated 48V at 25% duty cycle, but work well on 24V 1700gsm pull, 10mm travel) push or pull 27 x 18 x 15mm 55p  
 W922 Mains 240V ac solenoid, 10% duty cycle, push or pull, 16mm travel. 50 x 20 x 16mm. Only £1.50  
 W895 9V DC relay 500R SPCO 28 x 24 x 19, 50p  
 W733 11 pin plug in relay, 240V ac, 3PCO 5A contacts £2.50. Base £36p  
 W838 700R 24V 4PCO "continental" relay 35 x 30 x 18, only 84p; 10/£7.00  
 W847 37R 5—10V relay, SP 3A contact, PCB mntg 11 x 33 x 20, 95p; 10/£7.50  
 W893 Omron LY4 mains relay, 4PCO 5A contacts £2.60  
 W886 24V ac coil, but works well on 6V DC. 2 x 10A c/o contacts. Ex-equip, only 60p

### AMAZING! COMPUTER GAMES PCB's for PEANUTS!!

A bulk purchase of PCB's from several well known computer games including Battleships, Simon, Logic 5 and Starbird enable us to offer these at incredibly low prices:

#### 'STARBIRD'

Gives realistic engine sounds and flashing laser blasts — accelerating engine noise when module is pointed up, decelerating noise when pointed down. Press contact to see flash and hear blast of lasers shooting. PCB tested and working complete with speaker and batt. clip (needs PP3). PCB size 130 x 60mm. Only £2.95

#### 'SIMON'

The object of this game is to repeat correctly a longer and longer sequence of signals in 3 different games. (Instructions included). PCB contains chips, switches, lampholders and lamps, and is tested working, complete with speaker. Needs PP3 and 2 x HP11. PCB size 130 x 130mm. Only £3.95

#### 'COMPUTER BATTLESHIPS'

Probably one of the most popular electronic games on the market. Unfortunately the design makes it impractical to test the PCB as a working model, although it may well function perfectly. Instead we have tested the sound chip, and sell the board for its component value: SN76477 sound IC; TMS1000 u-processor; hat clips, R's, C's etc. Size 160 x 140mm. Only £1.50. Instruction book and circuit 30p extra

#### 'MICROVISION' Cartridges


These are a small PCB with a micro-processor chip, designed to plug in to the microvision console. Only snag is we don't have any consoles! However, they can be used as an oscillator with 4 different freq. outputs simply by connecting a battery and speaker. Tested and working (as an osc) with pin out data. PCB size 72 x 60mm.

ONLY 25p each!!

### LOGIC 5 PANEL

Tested Logic 5 now sold out — but we have some PCB's with 10 LED's and chip on, but no keyboard. Not tested. 50p

### ELECTRO-DIAL

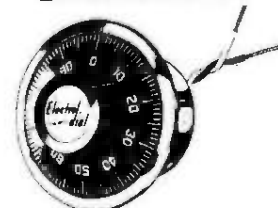

Electrical combination lock — for maximum security — pick proof. 1 million combinations!! Dial is turned to the right to one number, left to a second number, then right again to a third number. Only when this has been completed in the correct sequence will the electrical contacts close. These can be used to operate a relay or solenoid. Overall dia. 65mm x 60mm deep. Only £9.95  
 Also available without combination — Only £3.95

### 1982 CATALOGUE

... is not ready yet!! 1981 edition is now out of print, but the big new 1982/3 edition should be ready by late March '82 — Send 75p for your copy now!!

### WHOLESALE LIST

We have in stock many millions of components — we supply shops, M/O companies, Schools, Industrial Users etc. Can we supply you, too? Our quantity (100+) prices for new full-spec components is very competitive. Ask for our free bulk-buyers list.

**NEW CONTROL SYSTEM FOR SLR CAMERAS**

Electronic shutter speed and exposure controls can now be built into single lens reflex cameras without mechanically modifying the camera bodies or lenses.


A new control system, developed by Matsushita Electrical Industrial Corporation, measures the light at a preset aperture (in less than two

milliseconds) and then sets exposure time accordingly. Control range varies from 0.0005 seconds to four seconds — dependent upon lens aperture and film speed.

Prior to the Matsushita development, it was necessary to have a light measuring device accommodated behind the main lens — calculating light intensity with the lens held wide open. ETI NEWS JULY 1975

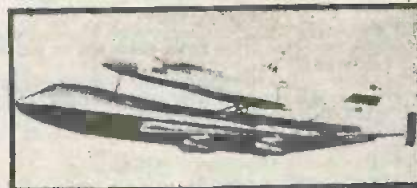**RIDING HIGH**

The next step in America's space programme is the testing of NASA's space shuttle. Landing tests are to be carried out in mid 1977. Amazingly the machine will be launched 'piggy-back' from a Jumbo 747! Several



flights will be made to ensure stability before the shuttle is actually released. Trust Americans to build the world's largest airliner and then carry people outside it! ETI NEWS AUG 1976

Elrad: ETI Germany.....

A new edition of ETI starts this month — Elrad in Germany. The name Elrad itself means nothing and is simply an amalgamation of electronics and radio. It is being published by Heinz Heise in Hanover and is edited by Udo Wittig  
ETI NEWS JAN 1978

**COSMOS NOW CHEAPER THAN TTL FOR MAJORITY OF DIGITAL SYSTEMS**

RCA has announced further price reductions in its CD4000 range of COS/MOS integrated circuits: The reductions range from 35% to 50%. The biggest price reductions have affected the more established MSI devices of the CD4000 range, with many types being reduced by over 50%.

As a result of the price cuts, many of the popular TTL devices are currently more expensive than the equivalent COS/MOS functions.

ETI NEWS SEPT 1975

**CB2B**

At long last a specification has been published by the Home Office for the legalisation of Citizen's Band radio. Two frequencies will be allocated: 934.025 to 934.975 MHz and 27.60125 to 27.99125 MHz. For the 934 MHz (AM) frequencies the maximum power is 8 W (25 W ERP), 20 channels at 50 kHz channel spacing. Hand-held units are restricted to 3 W PEP. On the 27 MHz (FM) frequencies the maximum power is 4 W (2 W ERP), 40 channels at 10 kHz spacing. Frequency tolerance: ±1.5 kHz. Maximum frequency deviation: ±2.5 kHz. Adjacent channel power: -60 dB to 2 uW, spurious emission less than 50 nW.

ETI NEWS JULY 1981

**CBM AGAIN!**



Right — now you've stopped staring at the picture can we proceed with this month's news. Thank you. Once again our old friends CBM have managed to get in on the act. The above watches — yes **watches** — represent their

long-awaited entry into the digital watch market — with the 5,000 series. All three use a common module, with the casings making for a price range of £17.50-£21.00.

ETI NEWS JAN 1977

**PLAY-ALONG-WITH-RCA**

Single chip I/O for video games is the laudible aim of messers. RCA. To be introduced in January the device is primarily a vertical and horizontal synching circuit designed for use with RCA's 1802 MPU. Price could well be around £12 when and if introduced into this country.

ETI NEWS DEC 1976



## CZECH ON CALCULATOR PRICES

ETI NEWS MAY 1976

A typical dour Czech day. The rain sleet across Prague. Somewhere in the back streets well away from the patrols and the populace, Ivan scuttles into a dingy corner shop.

There, amid the Western papers and naughty mags, he spots the object of his desires.

Eyes alight he lifts the proscribed machine from the rack, and carries it reverently to the counter, behind which stands the owner.

"How much?" he stammers, hands shaking.

"Novus 650 comrade? To you, £172. Crossed the border this morning right under the army's noses," he looks around furtively, and leans across the counter, whispering.

"Interested in the REAL thing eh comrade?" Ivan nods. The man reaches below the counter and produces a battered show box. Ivan's eyes are wide by now, riveted to the lid as it lifts. Inside lies a full frontal scientific, a HP 45.

Ivan faints.

Now before you dismiss this as merely the alcoholic follies of the ETI staff, following a party, let us inform you dear reader, that whilst we may be guilty of slight embroidery, our flight of fancy is based on fact.

It seems our Eastern friends consider pocket calculators to be highly prized items, and will pay vast sums to acquire them. What would cost you or 1 £7, our Ivan would need £172 to own. For that HP 45 you could possibly get a weekend with Siberian Sue, belle of the Balkans.

The reason behind this black marketing and smuggling is that calculator ships are not produced behind the ferric curtain and the machines are banned from importers lists by the governments, to preserve foreign exchange as their value is so high.

I wonder how they count it?

## FOUR CHANNEL DISCS

In the UK the EMI group have announced plans to release quadraphonic discs — using the CBS developed 'SQ Matrix' system — in April.

The company claims that the new discs will be fully compatible with existing stereo equipment.

ETI NEWS APRIL 1972

## COMPUTER 'ON A CHIP' WITH CASSETTE TAPE

A new byte-orientated micro-computer with its own in-built cassette tape backing storage has been produced by Computer Electronics Ltd, of Saffron Walden, Essex, as part of its range of cassette tape data systems.



Believed to be one of the first 'processors on a chip' computers to be developed in this country, the complete computer fits on one of the company's standard printed circuit cards. ETI NEWS AUG 1973

CALLING ALL K9s,  
R202s, ROBBIES,  
C3POs, MICROMICE  
etc, etc.....

ETI is very keen in getting a robot dialogue going.

Anyone out there on the other side of the printers ink interested in robotics, especially anyone actually building robots - of WHATEVER complexity - should contact us here at ETI.

If possible how about some photographs of your machines? They may well be in line for an appearance in ETI. So come on, lets be hearing from you - ALL of you - take pen in hand (or get the robot to do it) and write to

The Editor,  
ETI Magazine,  
145 Charing Cross Road,  
London WC2.

Mark your envelope  
"ROBOTS"

So we can deal with it  
with our usual  
machine-like efficiency.

ETI NEWS NOV 1979

## TV GAMES LSI CHIP AVAILABLE SOON

Rumours have been abounding for about a year now that an LSI chip for television games was being developed.

We now have definite news that Logic Leisure, a British Company, have produced a chip which will produce four TV games, with two variations on each, giving eight permutations. There is score and sound facility. Type number is not yet known but the chip is suitable for both 625-line, 50Hz and 525-line, 60Hz.

It is hoped that the chip will be on sale in October and the price tag is going to be in the £10-£12 range (plus VAT). U.K. distributorship is in the hands of Television Sports Co. Ltd., 6 Half Moon Street, Mayfair, London, W1Y 7RA.

ETI NEWS AUG 1975

## brief news


NASA have received weak signals from Skylab for the first time in four years. The possibility of sending it deeper into space is being considered...

★ A study by the American National Institute for Occupational Safety and Health (NIOSH) has concluded that VDUs in use in the offices of the New York Times are not responsible for cataracts developed by two copy editors working there...

ETI NEWS SEPT 1978
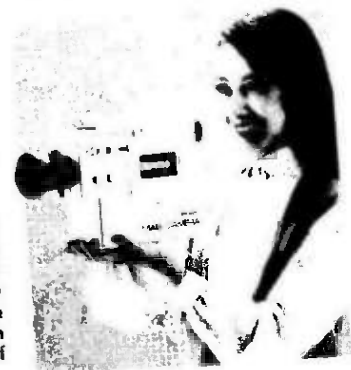
## Hitachi MAGic

Hitachi have developed an experimental colour video camera combined with a video tape recorder — provisionally christened the 'MAG Camera'. Using high density recording techniques, the combination is little bigger than an 8 mm cine camera. The cassette, using 1/4" tape, is almost as small as an audio cassette and allows two hours of recording/playback. The complete unit weighs only 2.6 kg, including a rechargeable battery pack. Watch this space for news on development of the MAG Camera.



ETI NEWS JAN 1981

From a firm called James Niell comes the Micro 2000 to rise into our News Digest with carefully measured precision. This instrument gets our vote for the best innovation of the year already! A digital *micrometer* no less.

As you can see from the picture, it actually reads out a measurement in seven-segment format. Goodbye verniers. It has so many features and advances, it is perhaps best simply to list them.

Accuracy to  $\pm 0.002$  mm., with a 'constant force' spindle and self-calibration facility. As soon as it is switched on, the 2000 self zeros.

The zero reset means that it can be used as a comparator against a known standard, and variations from that can

## BRITISH? PRECISELY!



be read directly. Also in awkward situations, the instrument can be

zeroed, utilised, and then removed to be read.

ETI NEWS JUNE 1977

## Sat 54

Well, it was Satcom 3 actually, but the plot is reminiscent of that old, old American telly series. The Car 54 in this case, however, was an RCA communications satellite, last heard of in December, 22,000 miles above mother Earth.

If anyone finds a communications satellite answering to the name of Satcom 3, send it to RCA, nto us. Mind you, if it has gone up in a puff of smoke, it has probably burned up on its way back to Earth. NASA quick to assure us that it won't cause another Skylab incident. So, you needn't dust off your anti-Skylab umbrella, yet.

ETI NEWS MARCH 1980

## Text To Talk

**K**urzweil Computer Products of Cambridge, Massachusetts has developed a machine to turn written text into speech.

The machine contains an optical scanner, a small computer, a small synthesiser and a loud-speaker unit.

The page to be read is placed over the scanning unit which then converts the written text to digital signals for the computer. The computer then converts them into sound

ETI NEWS APRIL 1980

## junk calls

From the land that brought us Muzak and MPUs comes the Junk call — the same as Junk mail but verbal! A machine is being used to dial up to 1,000 numbers a day and make a pre-recorded sales pitch, unlike junk mail there is no way of knowing when the call will be junk or not. By dialing up numbers from 0001 to 9999 the machine annoys everybody who answers on a particular exchange, even if you hang up

it holds the line open until the pitch is finished — this has caused emergency calls to be delayed in some cases.

Ten states are considering legislation to curtail the activities of the machines. However they intend to exempt charities, pollsters and politicians. Some people want an electronic 'no thanks' sign to be developed, although nobody is quite sure how it would work. What next?!

ETI NEWS SEPT 1978

## HP AT A (CALCULATED) LOSS;

Hewlett-Packard — renowned for their up-market calculators, are apparently running this section of the business at a loss. Equipment and other activities are keeping them in the black, and H.P. cite the delays occurring on the introduction of new models as the cause for this. Also named as a culprit is "severe price erosion in the pocket calculator marketplace". Pick the bones out of that ye rivals of the beast.

ETI NEWS NOV 1976

## CEEFAX AND ORACLE SYSTEMS COMBINED

The BBC and IBA, together with BREMA and the Broadcasting Department of the Home Office have agreed on a unified system of data broadcasting.

Until now the BBC have been working on CEEFAX, the IBA on ORACLE. Both systems allow a TV viewer to select at will from a number of different 'pages' of information and put these onto his screen.

ETI NEWS JULY 1974

★ A computer system capable of controlling the lighting and heating in up to one hundred buildings has been set up in London by Honeywell. The system, called BOSS, is the first of its kind in the UK . . .

ETI NEWS MAY 1978

## ELECTRONICS ENGINEERS' SALARIES FALL BEHIND

The 'Survey of Salaries', published by the Management Survey Centre this August, shows that the salaries of electronic engineers working for large companies have stagnated whilst other engineers' salaries have increased. Senior chemists have done best - their salaries have increased 3-4 times more quickly than the average.


For a senior professional in development (with major responsibilities) the median salary is £4,174; for electronic engineers in particular the median at this level is £3,720.

ETI NEWS OCT 1973
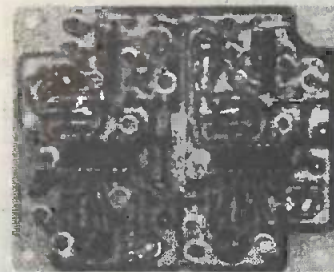
## ANRS INTEGRATED INTO A SINGLE IC CHIP

In 1972, JVC first introduced their Automatic Noise Reduction System (ANRS) into their top-range cassette decks. Since then, ANRS has been incorporated into a wide range of tape decks. Recent improvements however, in cassette deck quality and the possibility of "noise-reduced" FM broadcasts have meant improvements in the quality of noise reduction systems and the application of these systems to components other than cassette tape decks.

To meet these new requirements, JVC has recently completed the development of the ANRS IC.



ETI NEWS OCT 1975

A Preview from the Next Issue of

AMBIT  
INTERNATIONAL'S

# WORLD of RADIO & ELECTRONICS

CONCISE PARTS CATALOGUE

ISSUE NO.3 ON SALE  
AT YOUR NEWSAGENT  
FROM END OF MARCH  
- ORDER YOUR COPY NOW -

The **LOWEST PRICE**  
**Full-Spec. NICADS**  
**in the UK**



	<b>D</b>	<b>C</b>	<b>AA</b>	<b>PP3</b>
1-9	<b>£3.05</b>	<b>£2.35</b>	<b>£0.80</b>	<b>£3.70</b>
10-49	<b>£2.85</b>	<b>£1.99</b>	<b>£0.74</b>	<b>£3.50</b>

Prices for 50 or more on application.

Prices exclude VAT  
Postage & Packing 50p per order.


Send your orders to: Ambit International  
200, North Service Road,  
Brentwood,  
Essex CM14 4SG

Don't Forget to Use Your  
WR&E Discount  
Vouchers

HI-FI  
TV  
VIDEO

# HY-TEK ELECTRONICS

DISCO  
IN-CAR  
CB

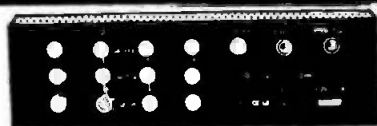


**HY-TEK PA150 A** multi purpose mixer-amp, delivers 150 watts into 4ohms, fully open and short circuit proof. There are 4 i/p channels with mic/line selection on each. The pre amp has facilities for connecting an echo unit, also featured are BASS and TREBLE controls, a slave socket and a master volume.  
**Hy-Tek Special Offer Price only £79.90 (p&p £2.50)**  
Slave version available £59.90 (p&p £2.00)



**DISCO MIXER**  
Hy-Tek knockdown price **£94.99** (p & p £2.00)  
5-channel stereo disco mixer with 7-band graphic equaliser built in, i.e.d. display, headphone monitor, cross fade and mic, over-ride controls. And many other features.




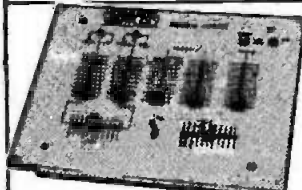**World's most versatile alarm chronograph watch Casio AX210**  
Alternative displays over 60 useful functions. Continuous display of hrs, mins, seconds, am/pm, date, day Auto calendar set at 28 days for February Accuracy. ± secs/month.  
**Price £27.90 (p&p £1.00)**




**HOWLAND WEST MX750**  
**4-channel STEREO DISCO MIXER**

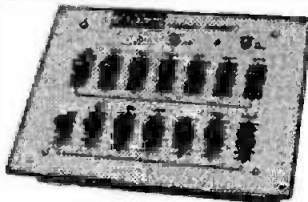Switchable phono/line i/ps. Cross fade on decks. P.F.L. on deck i/ps. Master volume control. Mains operated.  
**£59.90 (p & p £2.00)**



**HOWLAND WEST MX850**  
**STEREO GRAPHIC EQUALIZER**

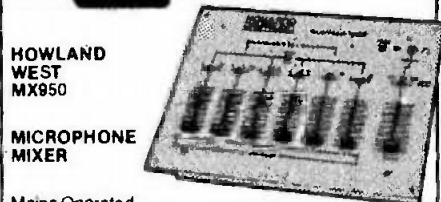7 band/channel. Tape monitor button. 12DB boost and cut (each band). Mains operated.  
**£59.90 (p & p £2.00)**



**HOWLAND WEST MX950**  
**MICROPHONE MIXER**


Mains Operated  
6 mic i/ps. 2 stereo line i/ps. Slide volume control for each. Stereo/mono control output. **£59.90 (p & p £2.00)**



**HYTEK DM404 HIGH QUALITY DISCO MIXER**  
2 x turntable i/ps. 1 x tape i/p. Mic i/p with separate Bass and Treble.  
Headphone monitor facility. **£34.90 (p&p £1.50)**  
Requires power supply (30V-50V DC). Suitable power supply available **£5.99 (p&p 75p)**



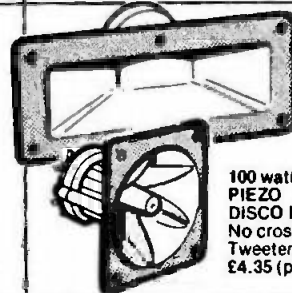**SHARP RT 10 STEREO CASSETTE DECK**  
L.E.D. V.U. meters, Dolby system, metal and chrome facilities, and a soft eject system plus sound quality you would expect from the Sharp company.  
**HY-TEK SPECIAL OFFER £49.95 (p&p £2.00)**




**100 watt PIEZO FLAIED HORN**  
No crossover. Low distortion. **£8.80 (p & p free)**

**100 watt PIEZO DISCO HORN**  
No crossover. Tweeter. **£4.35 (p & p free)**
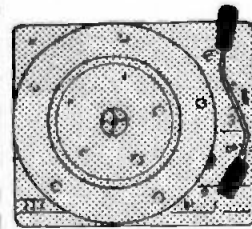
## DISCO & P.A. EQUIPMENT

140W Disco with Flexi Lights ..... **£249.99**  
120W Disco (without lights) ..... **£199.99**  
180W Double 12" Cabinet (pair) with Goodmans 12" & Piezo Tweeters ..... **£174.99**  
90W Single 12" Cabinet (pair) with Goodmans 12" & Piezo Tweeter ..... **£109.99**  
250W Slave Amplifier ..... **£94.99 (p&p £2.95)**  
500W Slave Amplifier ..... **£244.99 (p&p £4.50)**  
Digital Echo Unit ..... **£78.99 (p&p £1.95)**  
LC3003 CHNL Sound Chaser ..... **£34.99 (p&p £1.50)**  
Mono Headphones with mic. Boom ..... **£12.99 (p&p £1.25)**  
Condenser Microphone/Dual Impedance ..... **£12.99 (p&p £1.25)**  
Sound Effects Generator (57 different sounds) ..... **£39.99 (p&p £1.25)**  
3 Channel Rope light fitted with 8 pin Bulging Plug 21ft long ..... **£44.99 (p&p £2.00)**

**GOODMANS LOUDSPEAKER CHASSIS**  
8" 60W General Purpose ..... **£10.90 (p&p £1.50)**  
12" 90W General Purpose ..... **£24.99 (p&p £2.00)**  
12" 120W Disco Speaker ..... **£29.99 (p&p £2.00)**  
18" 230W Bass Speaker ..... **£65.99 (p&p £4.00)**  
High Quality Dome Tweeter 2kHz-22kHz ..... **£7.99 (p&p £1.00)**  
Crossover Network 2Way 100W ..... **£4.99 (p&p £1.00)**  
3 Way 100W ..... **£5.99 each**



**BSR Chassis**  
Fitted with stereo ceramic cartridge exceptional quality, great value, single play or automatic decks available.  
Single play **£14.99**  
auto play **£15.99 (p&p £1.50)**

## MISCELLANEOUS ITEMS

240V - 110V Converter Transformer 100W Type ..... **£8.99**  
240 - 110V Converter Switching 1000W Type ..... **£10.99 (p&p £1.00 each)**  
Atari 2600 Video Computer Game Including Combat Cartridge ..... **£89.99 (p&p £2.50)**  
\*Wide Range of Atari & Activision Cartridges Available. P.O.A.  
Pair of quality stereo mics suitable for most music centres & cassette decks supplied with 1/4 & 3.5mm jacks ..... **£14.99 (p&p £1.25)**

## CB EQUIPMENT RIGS

Fidelity 1000 40 ch. UK Legal ..... **£59.99**  
Fidelity 2000 40 ch. UK legal ..... **£79.99**  
Roteil RVC 230 40 ch. UK legal ..... **£79.99 (p&p £2.00 each)**

Tristar 777 CB27/B1 40 ch. UK legal rig capable of 120 ch. AM/FM USB LSB 5KC ..... **£199.99**  
Coit 510 CB27/B1 40 ch. UK legal rig capable of 120 ch. AM/FM ..... **£115.99**

Beta 1000 Slimline 40 ch. UK legal **£89.99**  
Beta 2000 Slimline 40 ch. UK legal **£79.99**  
Beta 3000 Slimline 40 ch. UK legal **£89.99**  
with Channel 9 Priority (p&p £1.50)

all rigs supplied with Mic & Fixing Kits

## CB ACCESSORIES

SWR Meter ..... **£7.99 (p&p 75p)**  
SWR Antenna Matcher/Power Meter ..... **£17.25 (p&p £1.00)**  
Patch Lead ..... **£1.99 (p&p 40p)**  
Mobile Aerials  
Magnetic Mount ..... **£11.99 (p&p £1.00)**  
Boot Lip Mount ..... **£10.99 (p&p £1.00)**  
Antenna Matcher ..... **£5.99**  
Slide Mount ..... **£5.99 (p&p £1.00)**  
Power Supplies (13.8V Stabilised)  
3A ..... **£12.99 (p&p £1.90)**  
5A ..... **£15.99 (p&p £1.90)**



**FOR MAIL ORDER**

For mail order just add postage and packing (all prices include VAT) and send PO/Cheque made payable to Hy-Tek Electronics, or phone stating Access/Barclaycard Number (Dalston address)



ALL OFFERS ARE SUBJECT TO AVAILABILITY

48 Dalston Lane,  
London, E8  
Tel 01-249 4814

Open 10am to 6pm Mon-Fri  
9.30am to 5.30pm Sat

# THE MUSIC MAKERS

TAKE ADVANTAGE  
OF THE HY-TEK  
PRICE POLICY

# AUDIOPHILE

Soon burglars won't be bothering to nick your whole hi-fi; they'll just take the cartridge. This month Ron Harris reviews two new pickups, one with a gemstone cantilever and the other a work of modern art.


**N**ews just in of a new piece of British circuitry genius. This is a new protection circuit, soon to be added to a famous manufacturer's product, which is claimed to make an amplifier totally invulnerable electrically.

Totally in this case means "even from 240 V mains at input or output". Ultra-fast relays are set at the output and on the supply lines to the PCB. These are driven from the new circuit, which has as its final stage a voltage amp with an incredibly high slew rate. This ensures a high speed of operation for the relays.
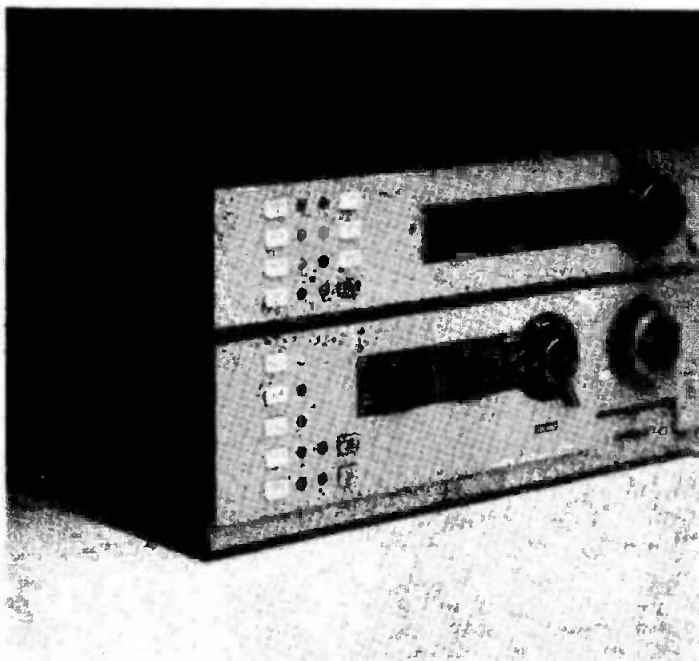
## Out Of Phase

The protection circuit operates like this: if an amplifier is suddenly faced with a massive input signal, the ratio of the feedback signal to input will drop dramatically. A comparator senses the change and a 'low-feedback' signal is generated. This by itself is sufficient to trip the supply relays, so that the overload cannot be passed on to the output stages, thus destroying them — and probably the speakers.

A second block within the circuitry watches the supply rails and any surges which are outside the requirements of normal drive will trip the protection circuit, since this is a "low-feedback likelihood situation" as the designer puts it. Great play is made of the fact that the music signal and the feedback voltage are in anti-phase at the point of comparison, so no interaction within the buffer is likely. 'Anti-phase reset', as it is called, thus introduces no colouration. Hence the protection reset of the relays can occur either in the case of low feedback-to-signal ratio, or in event of an "overload likelihood". I suppose this is where the somewhat pompous title of the circuit is derived — Anti-Phase Reset In Low Feedback (Or Overload) Likelihood.



## Shure MV30HE

A dedicated offshoot of the renowned V15 IV design, the MV30HE is for use in the SME Series III or IIIS only. The cartridge is built into a SME carryarm such that no headshell is used, or needed.

The moving components are those of the V15, save that no damper is provided. The cartridge body is all new, however, and quite a few problems it must have given them getting the coils and poles into a body as slim as this. The design is so arranged that the point of bearing intersection and the stylus line up parallel to the record. This will tend to aid stability in the replay of warped records.

As in the V15 a hyperelliptical stylus is used, which will give lower distortion results than either a spherical or elliptical tip. Tip mass is commendably low and output level is on a par with the V15 IV.

Once fitted into the SME the MV30HE looks very smart indeed and is visually extremely classy!

## Testing an Armful

In the lab the MV30HE had an easy time passing just about every test. It tracks as well as the V15 IV and measures slightly better. There is no higher technical accolade than that. The LF resonance came out — surprisingly — at around 16 Hz, a little higher than optimum in my opinion. Best values are somewhere around 10-12 Hz so as not to affect extreme LF reproduction. Best tracking was obtained at around 1.0 g, and no improvement was forthcoming for increased force.

Frequency response was boringly perfect at 20 Hz — 20 kHz  $\pm$  1.3 dB with a separation figure of 27 dB at 1 kHz. Compliance measured very high at 34 cu, so only the smallest damping paddle is required. It is required however — see later.

## Instructive Stuff

The instruction booklet is worth a special mention. It is a straight 'copy' of the SME style, right down to the little diagrams with ticks and crosses for right and wrong answers. Some sort of deal has been struck here, methinks!

One point that I just *have* to mention here; I could not,

At long last Quad have released their new tuner, the FM 4. It was shown for the first time at the Audio 82 exhibition in Swiss Cottage recently. Designed to match the Quad 44 control unit (preamp to the rest of us) the FM - only unit has digital tuning and seven pre-set stations. Programme locations are stored in memory.


A tuning knob has been retained in preference to a set of push-buttons, since Quad say it is easier to use.

### Brief Specification:

Full limiting	1 V	IF Rejection	100 dB
S/N (1 V input)	7 dB (stereo)	AM Suppression	60 dB
Distortion (1 KHz)	0.15%	Image Rejection	80 dB
Capture Ratio	2.5 dB	Crosstalk (1 KHz)	40 dB



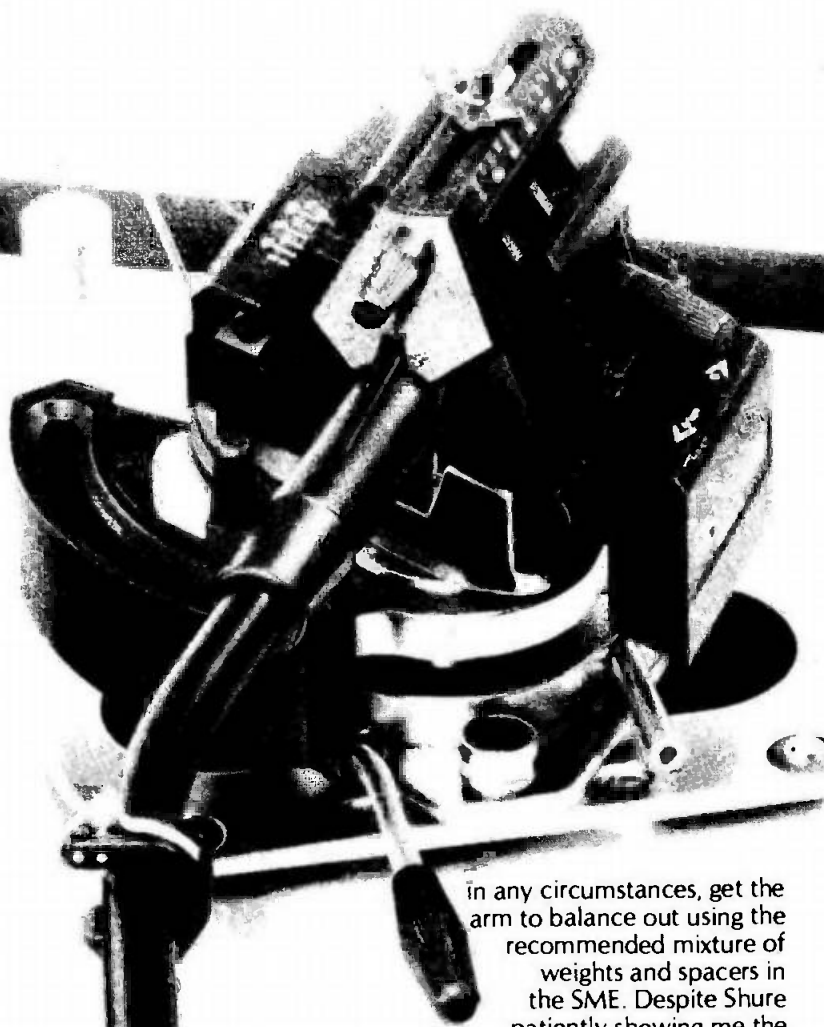The MV30HE set up in a Series III. About the best looking piece of hi-fi you'll ever see. As the compliance is very high only the smallest damper paddle is required, despite the lack of dynamic stabiliser (as fitted to V15 IV).



in any circumstances, get the arm to balance out using the recommended mixture of weights and spacers in the SME. Despite Shure patiently showing me the same arm set up perfectly in their Series III, would it balance once I left the factory? It would not!

I would be most interested to hear from any MV30HE purchaser as to balance requirements. I agree the total mass is 11.8 g but I'll be damned to an eternity of music centres playing Barry Manilow before I'll agree that an MV30HE balances in an SME Series III with four weights and six spacers.

## Down To Sound

I suppose the obvious comparison with the MV30HE must be the V15 IV. So, as I'm getting old and predictable (I *still* hunger after Felicity Kendal . . .) that was the first pickup against which I auditioned the unit. Frankly, I had expected to discern no difference, and initial tests confirmed this to some degree. However, having settled in at home with my own system around me and the reassuring brandy in hand, subtle differences began to manifest themselves. The MV30HE has a more coherent sound — the mid-range is more open under close examination and the bass is 'cleaned-up' and tighter, if a little more prominent. These are *exactly* the changes to be expected from a unit which simply matches

the arm better, but has a higher resonance. Which, of course, if I'd thought about, is *exactly* the MV30HE/V15 IV relationship. Serves me right for being so sure of myself!

In comparison to the market as a whole, the MV30HE/SME pickup stands well-up with the best. The damper is not significantly missed, provided the SME paddle is employed. Leave it off and boom is liable to result, as is a certain lack of stability on warped records.

A limited application, then, but a very creditable performance and one which will compete with Shure's own V15 IV. After all, if you've got an SME and were contemplating a V15 IV, the MV30HE is a better bet all around. It is no more expensive than the V15 IV with a CA1 arm to hold it and it provides a cleaner, more refined performance. All in all, a nice touch Shure. Whither goest thou now?

## Dynavector Karat Ruby

Both this month's cartridges are unusual in their own way; Dynavector's Karat is notable for its gemstone cantilever. This 2.5 mm long piece of single-crystal ruby is cut with a laser to accept the stylus (diamond) and then allowed to cool, thus fixing the stylus in place. The length is remarkably short, since Dynavector say that the less material the stylus information has to pass through, the higher will be the fidelity of the output.

Wave propagation through a medium is something not many of us take up as a hobby, but someone down at Dynavector must have it all well sussed! Apparently this equation:-

$$\frac{EI}{m} \frac{\partial^4 y}{\partial x^4} + \frac{\partial^2 y}{\partial t^2} - \frac{\rho EI}{m} \left( \frac{1}{E} + \frac{\gamma}{G} \right) \frac{\partial^4 y}{\partial x^2 \partial t^2} + \frac{\rho^2 \gamma}{mG} \frac{\partial^4 y}{\partial t^4} = 0$$

$$C_B = \alpha \sqrt{2\pi f} \left[ 1 - \frac{1}{4} \beta \frac{2\pi f}{\alpha^2} + \frac{1}{4} \delta (2\pi f)^2 + \dots \right]$$

where E = Young's modulus; I = secondary moment of section area; G = shear modulus; m = mass per unit length of a cantilever;  $\rho$  = density of the cantilever material; x = distance from the end of the cantilever; y = flexural displacement of the cantilever; r = constant; t = time.


sums up the vibrational behaviour of a cantilever under dynamic conditions. It can also be used to prove that rigid materials, such as ruby and diamond, make for better cantilevers than boron, beryllium and the rest.

(There is a 'big brother' to the Ruby, which has a diamond cantilever and costs around £450 as opposed to the Ruby's £100. If I can persuade the ever-helpful Dynavector into lending one I hope to report on the differences soon. Maybe if I say "please"....?)
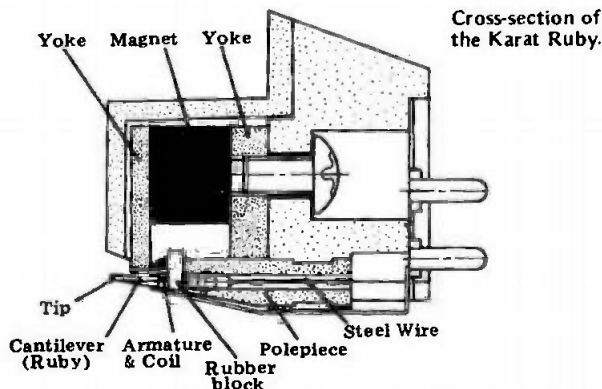
## Temperate Zones of Test

Another piece of original thinking has gone into solving the problem of temperature dependence and damping material. The only rubber used in the Karat is to prevent the cantilever taking its jewelled self up into the body whilst playing records. Normally the pivot damping in a cartridge is accomplished by a rubber block and this is prone to suffer from changes in temperature and slow deterioration as it ages — the Karat suffers neither of these weaknesses.

In fact, due to the short rigid construction of the cantilever, the Ruby requires no damping at all.



Under test the Karat showed a ruler flat response from 100 Hz to 30 kHz of under  $\pm 0.5$  dB! It was only 1 dB down at 30 Hz and separation measured an excellent 24 dB at 1 kHz and a more than adequate 18 dB at 20 kHz. Stylus resonance fell at 49 kHz and in the SME Series III (what else?). LF resonance was well placed at 12 Hz, below audibility and above warps.



Tracking was exemplary for a moving-coil unit — at 1.75 g it tracked all my test bands perfectly; the first moving coil to do so. Bias was set for 2.0 g, a high value, but one that worked well. In actual use the Karat was never caught out by any recorded information.

If at this point you're looking around the pages in search of the usual response graphs, don't bother — I haven't included any. If you really want to see a straight line, go buy a ruler. Dishearteningly disappointing for us cynics.

## Listening Out

As the Karat Ruby matches the SME Series III so well, it was left in that arm all through the listening test. One brief excursion into a Linn Itokk showed the two to be completely incompatible in my opinion, as the sound stage broke up and the bass became so loose as to be positively flapping! Strange that, as both are capable of much better and there is little on paper to point to such obvious mutual abhorrence.

The loudspeakers used were my trusty KEF 105 II's fed by a variety of amplification from Crimson, Monogram and Trio. Source equipment remained at Thorens 160S/SME III throughout.

On the very first LP side I played with the Ruby it was obvious that here was something special. The sound is so detailed and open, with such tight control of the bass that it makes you sit up and take notice of the music. This is a cartridge that will be much appreciated by reviewers, as it is so easy to listen *through* for long periods.


In fact there is little I can say against the Karat. It is a trifle recessed — I cannot account for this impression from the lab results, however, but it remains a definite impression — but is so relaxed and balanced a sound that none but the most obnoxious could find aught to quibble with. The sound quality reminded me greatly of the Ortofon MC30, but with greater resolution of complex passages and a more extended bass end.

At around £100 the Karat Ruby is an excellent bargain. Even accounting for the required step-up device, this pickup is required listening for anyone in the market. I have no hesitation in saying that it out-performs many units costing much, much more and will give more musical pleasure than just about any other cartridge I know.

Mind you, I haven't heard the Karat Diamond yet... but can it *really* be worth £350 more? On this evidence I would doubt it! (Pause while Dynavector work out whether this is a compliment or an insult...)

# ELECTRONIC IGNITION

Makes a good car better

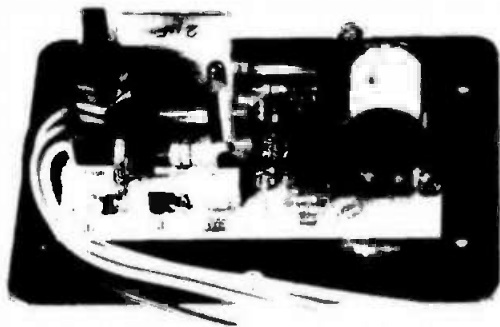

As a  
**KIT**  
or  
**READY  
BUILT**

**TOTAL ENERGY DISCHARGE** electronic ignition gives all the well known advantages of the best capacitive discharge systems.

**PEAK PERFORMANCE** — higher output voltage under all conditions.

**IMPROVED ECONOMY** — no loss of ignition performance between services.

**FIRES FOULED SPARK PLUGS** no other system can better the capacitive discharge system's ability to fire fouled plugs.

**ACCURATE TIMING** — prevents contact wear and arcing by reducing load to a few volts and a fraction of an amp.

**SMOOTH PERFORMANCE** — immune to contact bounce and similar effects which can cause loss of power and roughness.

## PLUS

**SUPER POWER SPARK** — 3½ times the energy of ordinary capacitive systems — 3½ times the power of inductive systems.

**OPTIMUM SPARK DURATION** 3 times the duration of ordinary capacitive systems — essential for use on modern cars with weak fuel mixtures.

**BETTER STARTING** — full spark power even with low battery.

**CORRECT SPARK POLARITY** unlike most ordinary C.D. systems the correct output polarity is maintained to avoid increased stress on the H.T. system and operate all voltage triggered tachometers.

**L.E.D. STATIC TIMING LIGHT** for accurate setting of the engine's most important adjustment.

**LOW RADIO INTERFERENCE** fully suppressed supply and absence of inverter 'spikes' on the output reduces interference to a minimal level.

**DESIGNED IN RELIABILITY** an inherently more reliable circuit combined with top quality components — plus the 'ultimate insurance' of a changeover switch to revert instantly back to standard ignition.

## IN KIT FORM

it provides a top performance electronic ignition system at less than half the price of competing ready-built systems. The kit includes everything needed, even a length of solder and a tiny tube of heatsink compound. Detailed easy-to-follow instructions, complete with circuit diagram, are provided — all you need is a small soldering iron and a few basic tools.

## AS REVIEWED IN

ELECTRONICS TODAY INTERNATIONAL June '81 Issue  
and EVERYDAY ELECTRONICS December '81 Issue

**FITS ALL NEGATIVE EARTH VEHICLES**,  
6 or 12 volt, with or without ballast

**OPERATES ALL VOLTAGE IMPULSE TACHOMETERS**  
Some older current impulse types (Smiths pre '74) require an adaptor —  
PRICE £2.95

**STANDARD CAR KIT** £14.85

**Assembled and Tested** £24.95

**TWIN OUTPUT KIT** £22.95

For MOTOR CYCLES and CARS with twin ignition systems  
**Assembled and Tested** £34.70

PLUS  
£1.00  
U.K.  
P. & P.  
Prices  
Include  
VAT.

**DIMENSIONS:**  
Length 12.5 cm  
Width 8.9 cm  
Height 4.3 cm  
Lead length 100.0 cm

## TECHNICAL DETAILS

The basic function of a spark ignition system is often lost among claims for longer 'burn times' and other marketing fantasies. It is only necessary to consider that, even in a small engine, the burning fuel releases over 5000 times the energy of the spark, to realise that the spark is only a trigger for the combustion. Once the fuel is ignited the spark is insignificant and has no effect on the rate of combustion. The essential function of the spark is to start that combustion as quickly as possible and that requires a high power spark.

The traditional capacitive discharge system has this high power spark but, due to its very short spark duration and consequential low spark energy, is incompatible with the weak air/fuel mixtures used in modern cars. Because of this most manufacturers have abandoned capacitive discharge in favour of the cheaper inductive system with its low power but very long duration spark which guarantees that sooner or later the fuel will ignite. However, a spark lasting 2000µS at 2000 rev/min. spans 24 degrees and 'later' could mean the actual fuel ignition point is retarded by this amount.

The solution is a very high power, medium duration, spark generated by the TOTAL ENERGY DISCHARGE system. This gives ignition of the weakest mixtures with the minimum of timing delay and variation for a smooth efficient engine.

**SUPER POWER DISCHARGE CIRCUIT** A brand new technique prevents energy being reflected back to the storage capacitor, giving 3½ times the spark energy and 3 times the spark duration of ordinary C.D. systems, generating a spark powerful enough to cause rapid ignition of even the weakest fuel mixtures without the ignition delay associated with lower power 'long burn' inductive systems.

**HIGH EFFICIENCY INVERTER** A high power, regulated inverter provides a 370 volt energy source — powerful enough to store twice the energy of other designs and regulated to provide sufficient output even with a battery down to 4 volts.

**PRECISION SPARK TIMING CIRCUIT** This circuit removes all unwanted signals caused by contact volt drop, contact shuffle, contact bounce, and external transients which, in many designs, can cause timing errors or damaging un-timed sparks. Only at the correct and precise contact opening is a spark produced. Contact wear is almost eliminated by reducing the contact breaker current to a low level — just sufficient to keep the contacts clean.

## TYPICAL SPECIFICATION

	TOTAL ENERGY DISCHARGE	ORDINARY CAPACITIVE DISCHARGE
SPARK POWER (PEAK)	140 W	90 W
SPARK ENERGY	36 mJ	10 mJ
(STORED ENERGY)	135 mJ	65 mJ
SPARK DURATION	500 µS	160 µS
OUTPUT VOLTAGE (LOAD 50pF EQUIVALENT TO CLEAN PLUGS)	38 KV	26 KV
OUTPUT VOLTAGE (LOAD 50pF + 500 KΩ EQUIVALENT TO DIRTY PLUGS)	26 KV	17 KV
VOLTAGE RISE TIME TO 20 KV (Load 50pF)	25 µS	30 µS

TOTAL ENERGY DISCHARGE should not be confused with low power inductive systems or hybrid so called reactive systems.

## ELECTRONIZE DESIGN

Dept. D, Magnus Road, Wilnecote  
Tamworth, B77 5BY  
Phone: (0827) 281000



# C.T. ELECTRONICS (ACTON) LTD.

Registered in England 1179820

267 & 270 ACTON LANE, LONDON W4 5DG. Telephone: 01-747 1555  
Telex 291429 01-994 6275

9.30 a.m. - 6 p.m.  
MON. - SAT.  
CONTINUOUS

## ALUMINIUM BOXES:

AB7 5.25x2.50x1.50in. (133x63.5x38.1mm)	£0.96
AB8 4x4x1.50in. (101.6x101.6x38.1mm)	£0.96
AB9 4x2.25x1.50in. (101.6x57.2x38.1mm)	£0.96
AB10 4x5.25x1.50in. (101.6x133.4x38.1mm)	£1.12
AB11 4x2.50x2in. (101.6x63.5x50.8mm)	£0.96
AB12 3x2x1in. (76.2x50.8x25.4mm)	£0.70
AB13 5x4x2in. (127.0x101.6x50.8mm)	£1.30
AB14 7x5x2in. (177.8x127.0x50.8mm)	£1.64
AB15 8x6x3in. (203.2x152.4x76.2mm)	£1.98
AB16 10x7x3in. (254.0x177.8x76.2mm)	£2.70
AB17 10x4.50x3in. (254.0x114.3x76.2mm)	£2.28
AB18 12x5x3in. (304.8x127.0x76.2mm)	£2.52
AB19 12x8x3in. (304.8x203.2x76.2mm)	£3.04

## BLACK PLASTIC BOXES

75x50x25mm	65p
80x60x40mm	52p
90x70x40mm	59p
115x75x30mm	50p
110x90x45mm	£1.18
170x100x50mm	£1.65
200x120x80mm	£3.55

## BLUE REXINE COVERED ALUMINIUM BOXES

RB1 6x4.50x2.50in. (152.4x114.3x50.8mm)	£1.98
RB2 8x5x3in. (203.2x127.0x76.2mm)	£2.52
RB3 9x5x3.50in. (228.6x127.0x89.1mm)	£2.72
RB4 11x8x4in. (279.4x152.4x101.6mm)	£3.14
RB5 11x7.50x4.50in. (279.4x190.5x114.3mm)	£3.98

## RELAYS

### CONTINENTAL

By Omron, Verley, Siemens etc. 2 PCO..... 85p ea.  
4PCO..... 100p. Bases 20p

**SUBMIN POWER**, 5A contacts, small physical size. 4PCO  
100p, bases 25p

**POWER RELAYS**. Plug in octal and 11-Pin 2 and 3 PCO types with 7½ Amp contact ratings. By Schrack, B&R Omron, etc.  
Only 2.00p ea.

### ZETTER LOW PROFILE (Type AZ5 and 6)

Just in, a large quantity of 'flat pack' relays in standard, heavy duty and latching types. We can offer these at a fraction of list price in many coil voltages and contact arrangements. Full data supplied on request. Send SAE or ring for list.

### DIL Relays

Form A..... Only 1.00p ea.

## SWITCHES

Special offers include:

### ILLUMINATED

Licon 01-800 push fit 2PCO switches. Separate bulb contacts (T¼ flange) 5A rated contacts, lenses included. Latching or momentary action..... Only 1.50p

**MATCHING INDICATORS**..... 60p ea.

Attention: Licon stocks rapidly diminishing - BUY NOW and SAVE.

### ROCKER

Illuminated mains rocker switches, 16A contacts  
DPST. Red, push fit, 26x30mm standard type..... 75p  
SPST. Amber, push fit, 14x30mm standard type..... 30p

### ROTARY

1P12W, 2P6W, 3P4W Lortin type..... 50p ea.  
2P11W Elma gold plated adjustable. High quality..... £1 ea.

### MICRO

V3 roller, arm or standard..... 40p ea.  
V4 roller, arm or standard..... 50p ea.

### DIL

4xDPDT; 5xDPDT, gold contacts, by ERG & CTS, only..... 80p

### Industrial type

2 Pole 12A/600VAC	£1.50
8 Pole 10A/380VAC	3.00
10 Pole 12A/600VAC	3.00

## CABLE

Our cable stock must be seen to be believed, so it is impossible to list it all. ELECTRICIANS... buy our 2.5mm<sup>2</sup> for only £6/100 and 1.5mm<sup>2</sup> only £5/100. VIDEO CABLE. UR75 75Ω Coax Mil spec. only £20/100. BELDEN CABLE. Hook up wire in 24, 20 and 18 AWG. Super prices. MAINS CABLE in 0.5mm<sup>2</sup>, 0.75mm<sup>2</sup>, 1mm<sup>2</sup>, 1.5mm<sup>2</sup>. T.V. DOWNLEAD, excellent rates for 100m. MULTICORES of all types. RIBBON CABLE. We've got it. Why not see for yourself.

## SEMICONDUCTORS

We of course carry a full range of transistors, diodes, CMOS, TTL, Linears, Triacs, Thyristors and other devices but lack space to print long boring lists. Suffice to say we will beat most of our competitors on price, availability and quality of product.

The following are available in enormous quantity, generous trade discounts are offered:

BC184L - BUY69C - BFR87 - ZTX342(npn) - ZTX542(pnp)  
BY208. Our price 2.00p - 2N3373. Our price 1.80p

### 74LS Series TTL

The following numbers are held in quantity. Maximum savings.

LS01... 02... 10... 11... 30... 73... 75... 76... 138... 175...  
192... 193... 221... 251... 273... 290... 293

### Standard TTL

7401... 02... 04... 05... 15... 20... 25... 75... 86... 123...  
452.

### Heatsinks

Redpoint TV4 (for TO-220 package)..... 15p ea. discount on qty.  
TO5 tpe (50°C/W)..... 8p ea. discount on qty.

## CONNECTORS

### RF CONNECTORS

BNC Plug (50R or 75R)	50p
BNC Line socket	50p
BNC Chassis socket	
Flange	45p
SHF	45p
PL259 Plug	40p
Reducer	14p
SO239 Flange Chassis socket	40p
PL258 Double socket	50p
PL259 to BNC (male) adaptor	1.20p

PET100 plugs	50p
PET100 Chassis socket	50p
N-Type Plugs (Amphenol)	75p
N-Type Chassis sockets (SHF Amphenol)	75p

### MULTIWAY CONNECTORS

We carry good stocks of new and bargain priced used D-Series rectangular connectors from 9 to 50 way.

Example:	
New D15 socket	60p
New D9 plug	60p

### AUDIO CONNECTORS

We stock all types of jack, phone and DIN plugs too numerous to list, phone for details. In professional types we have: CBC Type ring locking multiway connectors fashioned in heavy duty nickel plated steel with cable clamp. In 2, 3, 4, 5 and 6 way.  
Only £1.00 per pr.

Switchcraft XLR Series, the professionals choice:

A34M 3 pin free plug	1.20p
A3F 3 pin free skt	1.32p
D3M 3 pin chassis plug	1.10p
D3F 3 pin chassis skt	1.60p

**FUSES:** 20mm QB 7p. AS 10p. ¼ inch QB 7p. A/S 12p. ⅜ inch 6p each.

**HOLDERS:** 20mm P/M 35p. Chassis mounting 10p. ¼ inch Panel mounting 40p. C/M 10p. ⅜ inch P/M 25p.

**MAINS FILTERS:** Computer grade but ideal for HiFi, etc. 8 or 15 Amp..... £4 ea.

**SLOW MOTORS:** Mains or 115V operation, great for timing purposes or discos..... £1.50 ea.

**NEON BULBS:** We have very large quantities in stock.

**QI BULBS:** 50W 12V projector type, to clear..... 50p ea.

**LOCTITE:** Penetrating adhesive. It really sticks. 50ML for only..... £3

**DIGITAL MULTIMETERS:** Superb value, copy of professional model. Full ranges and specs..... OUR PRICE £40

**TMK500 METERS:** Tough dependable Multimeter 20K/V sens. Full ranges in V, A & R..... OUR PRICE £24

**CAR SPEAKERS:** 3 way 20 watt shelf mounting. 4" Bass driver, 2½" Midrange, 1" Tweeter. Internal passive crossover. Great sound £32/pr. PLUS 4" driver BALL SPEAKERS, real 20W output, crisp, clean sound, a genuine bargain at..... £12 pr.

**SOLDER:** 60/40 18SWG, 500gm £6.50. 250gm £3.50.

**IRONS:** Antex X25 £4.50. Antex C15 £4.50. 12V 25W Irons £6.

This advertisement is mainly of our excess stockholding. We also have excellent stocks of semiconductors, hardware, cables, etc. etc. For further details send for our lists and retail price catalogue, phone or visit our shop. All prices are exclusive of VAT (and P&P). Minimum Mail Order £5 + P&P + VAT. Government departments, schools, colleges, trade and export welcome.

# C.T. ELECTRONICS (ACTON) LTD.

Registered in England 1179820

267 & 270 ACTON LANE, LONDON W4 5DG. Telephone: 01-747 1555  
Telex 291429 01-994 6275

9.30 a.m. - 6 p.m.  
MON. SAT.  
CONTINUOUS

## STABILISED POWER SUPPLIES

**FARNELL A15:** 210/240V 1P. Dual Op. 12-17v per rail at 100mA. Remote sensing, current limit protection. (164x130x38mm), with manual. £12.

**FARNELL 7/3SC:** 120/240V 1P. Adjustable current limit. Remote sensing. (188x96x93mm.) Two versions available: 15V at 2A or 30V at 1A. £15 ea.

**COUTANT OA2:** Op. amp. psu, 120/240V IP. Dual Op. 12-15v at 100mA. (138x80x45mm.) £12 ea. or 2 for £22.

**BRANDENBURG** Photomultiplier PSU. 19in. rack mounting. Metered, current limit protection.

374 300V-1KV at 5mA                      376 660V-1K6V at 10mA  
375 500V-1K5V at 6mA.                      All models £40.

**PIONEER MAGNETICS POWER SUPPLIES** ... 5V 150 amp, output input 115 vac. (Switchmode) Price £120 each.

Various other makes of power supplies in stock. Please send for lists. S.A.E. please.

## D TO A CONVERTERS

15MHz, 8 BIT

By Micro Consultants Ltd. 50Ω cable drive op. Linearity 0.25%, max. 0.125% typ. Settling time: 2V step 70nS typ. 2MV step 50nS colour television transmission standard. Diff. gain 0.5% diff. phase shift 0.5° types rad 802 and MC2208/8. Unused. Ex-maker's pack.

SPECIAL OFFER PRICE: £20

### NEW IN STOCK

A range of high quality transformers SPECIALLY WOUND for us. By buying direct we can offer these superb SPLIT PRIMARY & SECONDARY transformers at highly competitive prices.

6VA	0-12, 0-12		0-12V, 0-12V	3.80
	0-15, 0-15	2.20	0-15V, 0-15V	
12VA	0-4V5, 0-4V5		0-20V, 0-20V	
	0-6V, 0-6V		50VA 0-6V, 0-6V	
	0-9V, 0-9V		0-9V, 0-9V	
	0-12V, 0-12V	2.99	0-12V, 0-12V	4.75
	0-15V, 0-15V		0-15V, 0-15V	
	0-20V, 0-20V		0-20V, 0-20V	
20VA	0-4V5, 0-4V5		120VA 0-30V, 0-30V	
	0-6V, 0-6V		0-40V, 0-40V	8.90
	0-9V, 0-9V			

### CASED AUTO TRANSFORMERS

240V Cable input. American outlet socket.

Rating	Price	750VA	£23.50
300VA	£13.00	1000VA	£27.00
500VA	£18.00	1500VA	£36.00
<b>Other Transformers</b>			
1.2VA. 6-0-6, 9-0-9, 12-0-12	all 1.14	12VA	
1.5VA		0-12, 0-12	2.96p
12V	80p	18VA	
15V	1.00p	9-0-9	2.64p
2.4VA		24VA	
12-0-12	1.48p	12-0-12	3.36p
24V(pcb)	1.00p	12V	4.84p
4VA		30VA	
5-0-5	1.25	15-0-15	3.62p
6VA		36VA	
24V	1.50	9-0-9	4.70p
		50VA	
		0-2-4-6-8-10	6.00p

## VERO PRODUCTS

Veroboard 0.1 Copper		Apple proto boards	4.00p
2 1/2 x 3 3/4	70p	Veroboxes - 2 tone grey/white plastic boxes	
2 1/2 x 5	80p	4x2x1	1.99p
3 3/4 x 3 3/4	80p	4x2x1 1/2	2.22p
3 3/4 x 5	90p	4 1/2 x 2 1/2 x 1 1/2	2.51p
2 1/2 x 17	2.40p	7 1/2 x 4 1/4 x 2 1/2	3.75p
3 3/4 x 17	3.15p	7x4 1/2 x 2 1/4 (aluminium front)	3.51p
4.7x17	4.20p	Veroboxes	
0.1 plain		Veroboxes	
2 1/2 x 3 3/4	50p	4 1/2 x 3 1/4 x 1 1/2	78p
3 3/4 x 5	75p	7x4 1/2 x 2 1/4	1.42p
V-Q Board	1.30p	Veropins	45p/100. Stand off 45p/100. Track cutters £1.18p.
DIP Board (113x156mm)	3.26p		
RS DIP Board (100x160mm)	3.00p		

## 4 MILLION I.T.T. ELECTROLYTICS NEW AND BOXED NOW IN STOCK

EN 1212 AXIAL EN 1235 RADIAL

The whole range available at unbeatable prices. Send for list.

5 million Disc Ceramics in stock. Ceramic plate. Multi-layer ceramic. Low voltage discs. Monolithics. Ceramics. High voltage discs. Subminiature plate, epoxy cased. Send for lists or please phone for details.

**MULLARD:** Series 106 Computer grade electrolytics 10,000µF at 16V. Brand new and boxed. 39p ea.  
**SPRAGUE:** Series 36D Computer grade electrolytics 3,300 at 40V. Brand new and boxed. 35p ea.  
**SIEMENS:** Procond Radial Polyester Film Capacitors. 10µF at 63V. Brand new. Only 40p  
Quantity available

### RESISTORS - PRESETS - POTS

**CARBON FILM:** 1/4W from 10 to 12M. Only £1/100 or £5/1000  
**METAL OXIDE:** TR4, TR5, TR6, TR8 in E24 range, by Electrotil or Philips in 5%, 2%, 1%. Save £££s on manufacturer's prices.  
**WIREWOUND:** We specialise in Welwyn Vitreous Enamelled W-series types in 2 1/2W to 12 Watt. Also a good selection of HSA type metal clad power resistors and TV dropper replacement sections.  
**HIGH STABILITY:** 0.1% Tolerance Resistors for instrumentation purposes. By Filmet or Welwyn. 3K, 10K, 30K, 1M. Only 30p ea.  
**PRESETS:** Skeleton and enclosed, horizontal or vertical Piher quality presets. Range from 100P to 5M. Popular PT10 size 10p each AND GREAT DISCOUNTS ON QUANTITY.  
**CERMET PRESETS:** Top quality presets, good range stocked. Only 15p ea.  
**MULTITURN PRESETS:** 3/4" and 1 1/4" Bourns type Only 50p each.  
**SPECIAL!** 100K 15 turn 3/4". Only 20p each.  
**SWITCHED POTS:** Push switch pots from AB. In 22K lin and 100K lin. Switch independent of pot action. 30p ea.  
**RESISTOR NETWORKS:** Large range in DIL & SIL packages by Beckman & AB. Send SAE or phone for list.  
**WELWYN STRAIN GAUGE:** (Precision Micro-Measurements). Romulus Michigan type MA-09-500B4-350. Our price £1.25 ea. List price £3.95. Large quantities available.

## WE PURCHASE

Surplus component stocks, redundant materials, obsolete computers, for cash.

We also collect - distance no object. Just call!

### C. T. Electronics (Acton) Ltd.

267 & 270 Acton Lane, London W4 5DG


Telephone 01-747 1555; 01-994 6275.

Telex 291429

This advertisement is mainly of our excess stockholding. We also have excellent stocks of semiconductor hardware cables, etc etc. For further details send for our lists and retail price catalogue phone or visit our shop. All prices are exclusive of VAT (and P&P). Minimum Mail Order 15 - P&P - VAT. Government departments, schools, colleges, trade and export welcome.
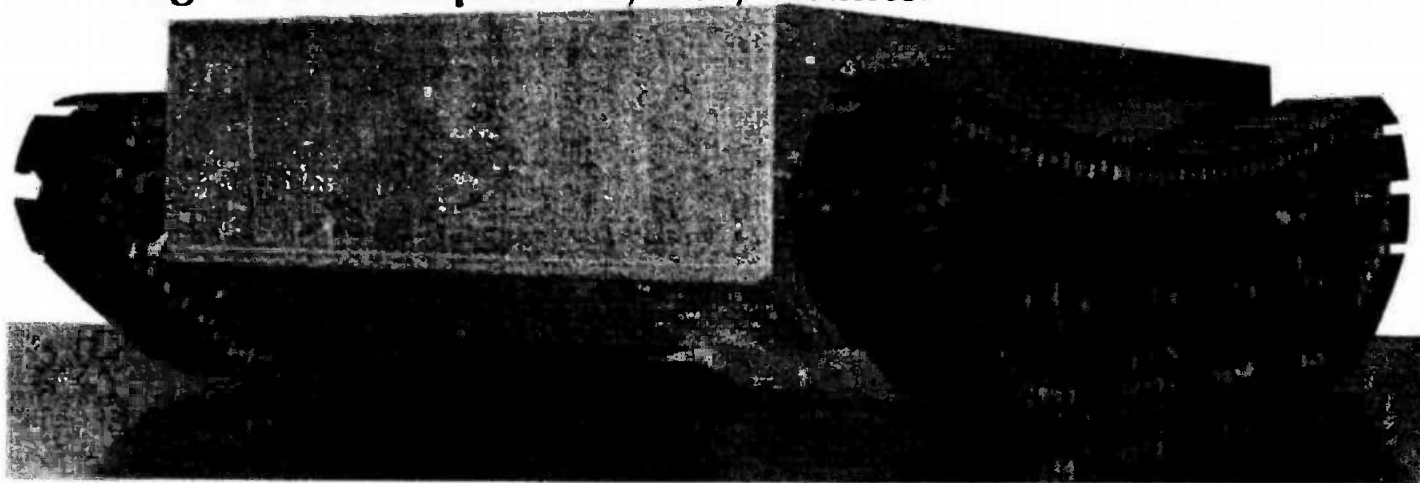
# ROBOT MOTOR CONTROL

This month we feature a control board for last month's motor driving board. This is part 2 in a series of DIY robot modules — collect them all! Design and development by Rory Holmes.



In this second part of the series on the ETI intelligent programmable mobile we shall describe the design of an analogue pulse width modulator for controlling the motor driver stage featured last month. We shall also take a brief look at some of the modules being offered later in the series which can be added in stages to enhance the motorised vehicle. The intention is to build up to a complete computerised mobile.

A lot of flexibility has been allowed for in the actual use and configuration of the modules, as we are well aware that constructors interested in this type of project have firm ideas of their own on the final form and capabilities of their mobile. Construction and interconnection details for all the modules we are presenting will be given along with guidelines to a range of applications.

The facilities we have planned for the mobile will continue with the digital motor control and an on-board programmable computer for overall control of other modules. A light-weight manipulator arm complete with teaching arm has also been designed, for mounting on the front of the mobile. It is powered by four radio control servo motors and the electronics interface between the servos and computer will be described

along with details of the arm mechanics. Optical proximity detectors for object sensing, and infra-red tachogenerators for speed sensing will also be featured on the ETI mobile.

It is hoped that the designs will also prove useful as stand-alone modules for individual use in other applications. Optical proximity detectors, for example, have numerous applications in batch counting, limit sensing, detection, alarms and so on.

The digital pulse width modulator in next month's issue will find many uses in the control of analogue functions; how about a computer interfaced to a pulse width modulated optical data link, for analogue information transmission? Our version will control two pulse width modulated channels, with a resolution of one part in 256, via an eight bit data port; modulation being achieved solely by logic to satisfy the all-digital purists.

## Optical Proximity Detectors

These have been designed as small independent units with as much in-built versatility as possible. The circuitry is housed in a short length of aluminium tube axially aligned in the detector direction, with three external

connecting points; ground, positive supply, and an open collector digital output. A number of detectors can thus be easily mounted in strategic locations. All circuit operating parameters are independent of the supply voltage, which can be anywhere between 5 and 35 V at a current of 20 mA.

The proximity switch works on the principle of transmitting and detecting a modulated infra-red beam. The infra-red transmitter receives 1 A peak current pulses, of 10  $\mu$ s duration, with a modulation frequency of 1 kHz. The 100:1 duty-factor thus achieved allows high currents to be used to increase the detection range, while reducing the average supply current to only 10 mA.

The sensor can be set by a preset pot, accessible through a small hole, to detect an object at any distance in the range 1 cm to 35 cm.

A small amount of hysteresis is introduced into this switching distance to ensure clean switching thresholds and stability of the output signal. The use of tuned detector amplifiers provides excellent infra-red interference rejection.

## Analogue Speed Control

The analogue speed control has

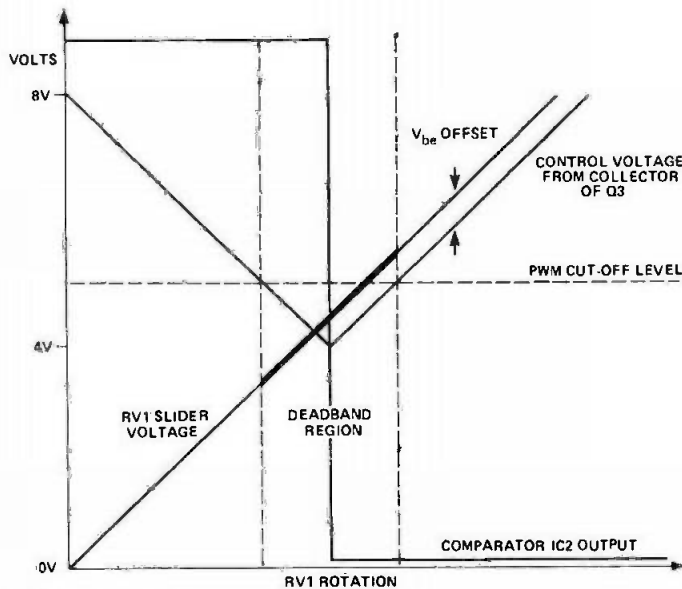


Fig. 1 Various voltages associated with the circuitry around Q3. The control voltage is measured at point A in Fig. 5.

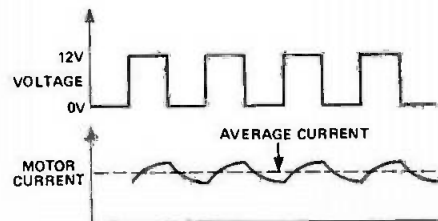


Fig. 2 PWM motor driving waveforms for last month's circuit.

been devised for manual control of the main traction motors; it provides two pulse width modulated signals suitable for the motor driver amplifier.

The circuit is designed to provide a linear control-voltage-to-pulse-width relationship for greater flexibility in application, and to simplify the addition of speed feedback velocity control.

The modulator can be built either single or dual, and the manual control section, if not required, is easily omitted. Speed control is achieved via two remote potentiometers, allowing speed to be set in either forward or reverse directions independently for each traction drive.

Since both motors are controlled via switching amplifiers from the same battery supply, it is important to reduce the peak currents that are drawn. This can be achieved by offsetting the phase of the switching waveforms relative to each other, such that at 50% duty cycle modulation, power

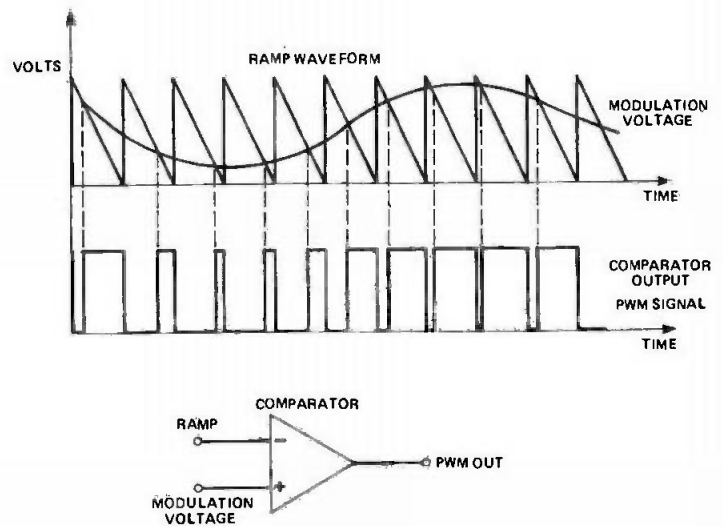


Fig. 3 How PWM waveforms may be generated using a comparator.

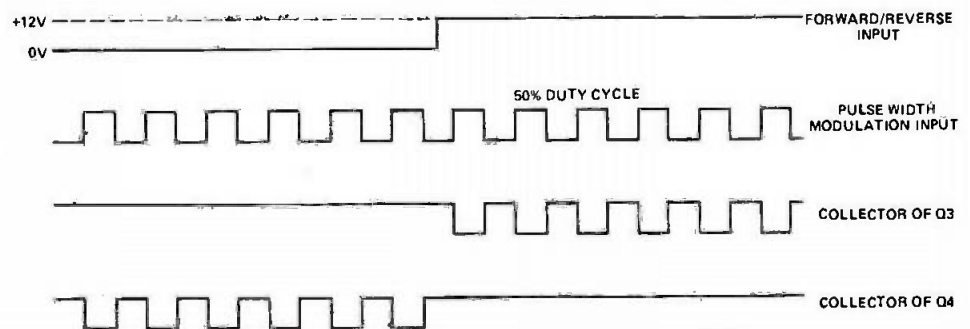


Fig. 4 The waveforms needed by our motor driver board, published last month. (Q3 and Q4 refer to last month's circuit.)



An internal view of the driver unit showing the interwiring to the bridge rectifier of one channel. Constructional details for the pulse width modulator will appear next month.

## BUYLINES

No problems here with any of the components specified — most mail order companies who advertise in the magazine will be able to supply everything. We can supply the PCB — see page 44 for details.

The circuit for the dual analogue pulse width modulator is shown in Fig. 5; it will be seen that each channel is identical with the exception of the circuitry around the CMOS gates IC1 and IC4. As described earlier the two switching waveforms must be the same frequency and synchronized 180° out of phase, to distribute the motor current peaks more evenly through the cycle. This is achieved by synchronizing both pulse generators to a master clock based around IC1a and b. A 20 kHz square wave is generated by this conventional astable arrangement and its frequency, set by R1 and C1, is fairly independent of supply variations.

The output of IC1d at pin 6 provides a buffered square wave in the same phase as the output on pin 10 of IC1b. C2 and R3 differentiate the positive-going edge of the square wave to produce a very short logic low pulse at the output of Schmitt inverter gate IC1c. In similar fashion C9 and R16 produce a logic high pulse coinciding with the negative-going square wave edge. IC4b further inverts this signal to a logic low pulse. Two separate trains of 500 nS negative-going pulses are thus provided in the correct phase relationship for resetting the charging cycle of two sawtooth oscillators as described below.

The pulse width modulators are identical from here on and we shall refer to the topmost circuit for description. Voltage controlled pulse width modulation is, in principle, very simple; a ramp waveform (sawtooth) is applied to one input of a comparator and the modulation voltage to be encoded is applied to the other, producing the required PWM squarewave at the comparator output. Figure 3 illustrates this operation.

Due to the design requirement of a linear relationship between control voltage and pulse width, a constant current source formed from Q2 is used to generate the linear ramp waveform. LED1 and the base-emitter junction of Q2 are forward biased by R6 and together define a temperature-compensated voltage across R7 which in turn defines a constant emitter and collector current of about 1 mA. C3 is charged up negatively from this current, until the negative-going reset pulse arrives from inverter IC1c. This pulse turns Q1 hard on for a very short period (500 nS), during which C3 is completely discharged, taking the ramp voltage back to +8 V. This process repeats at the clock frequency of 20 kHz, providing a negative-going sawtooth of about 3 V peak-to-peak referenced to the +8 V rail.

IC3b, the comparator used to perform the modulation, is an LF353 dual op-amp, chosen for its large bandwidth and high slew-rate. The inverting terminal on pin 2 is fed from the ramp waveform, while the non-inverting terminal is fed from op-amp IC3a, an inverting amplifier configured to sum control voltage inputs relative to a 4 V reference.

The potential divider R11 and R12 provides the 4 V reference to the non-inverting terminal of IC3a, and the control voltage applied to R13 at point A is summed relative to the 4 V. An offset voltage set by PR1 is also summed at the inverting terminal of IC3a, and is used to bring the control voltage into the correct operating range and for setting a deadband region on the manual control pot RV1.

The output of op-amp IC3b (and indeed most others) will not swing to the full supply rail voltages, so the inverter gate IC1e is used to buffer the square wave to full CMOS logic levels.

The manual control system included in this circuit enables a single potentiometer to control the speed in both forward and reverse directions. When the pot is at centre travel, and for a certain deadband around this point, the motor must be stopped and no switching pulses should occur (ie the PWM signal is continuously low).

As the pot is turned in either direction from its midpoint, the pulse width should in-

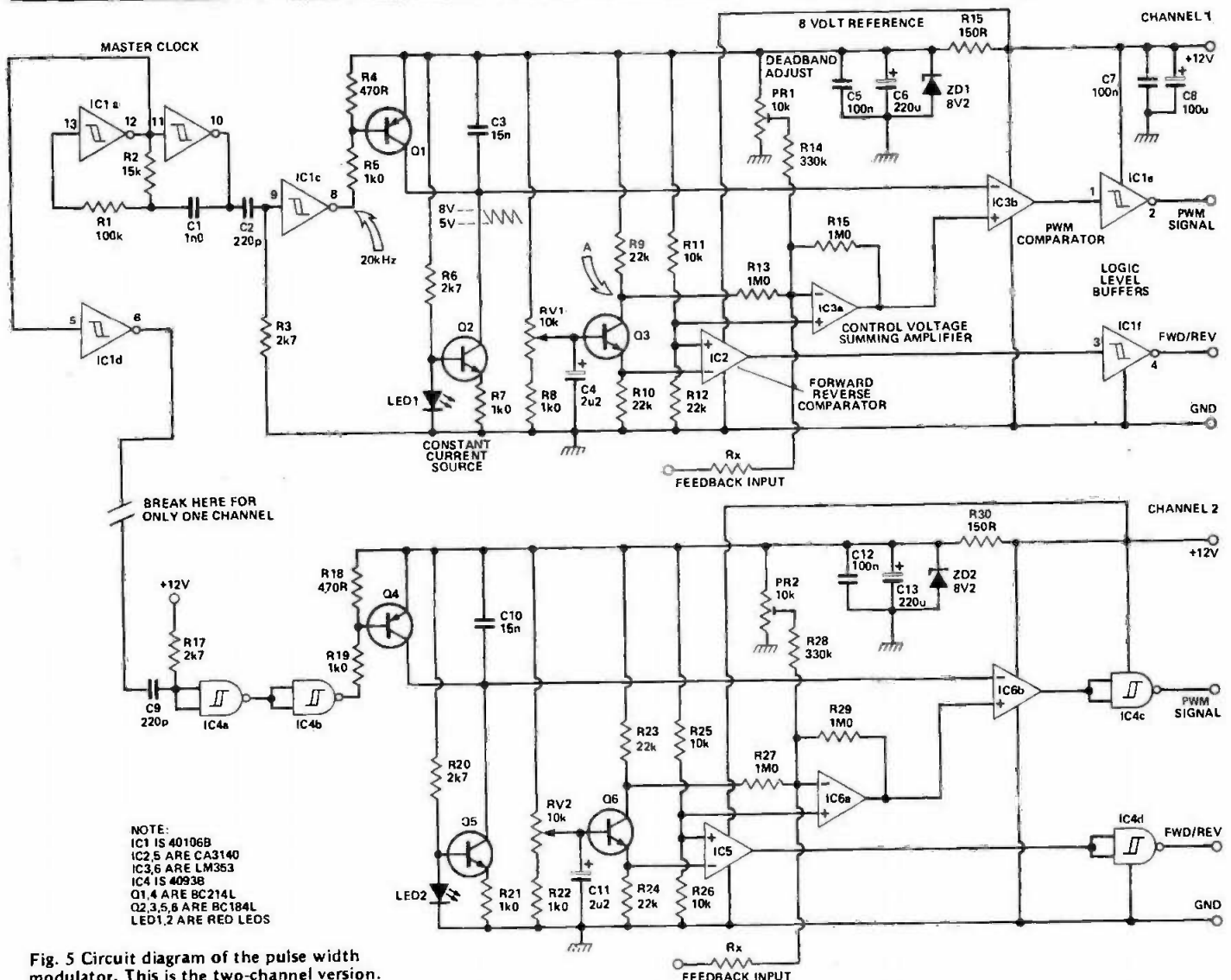


Fig. 5 Circuit diagram of the pulse width modulator. This is the two-channel version.



# PROJECT : Robot Motor Control Part 2

## PARTS LIST

crease and this requires a positive-going input voltage to the summing amplifier IC3a. The forward/reverse logic level should also change state as the pot moves through its midpoint. Q3 provides the necessary voltage transfer function from the pot RV1 to the control voltage summing amplifier, as explained graphically in Fig. 1.

The emitter and collector resistors of Q3 are both equal and the base voltage is taken directly from the slider of the manual control pot RV1. The output voltage is taken from the collector of Q3 to feed the summing amplifier, and will be held at +8 V via R9 when Q3 is switched off. As the slider of RV1 moves toward the centre of travel, the base voltage rises, slowly turning on Q3 and lowering the collector voltage.

When Q3 is turned hard on as RV1 reaches its mid-point, R9 and 10 will form a potential divider giving 4 V as the minimum control voltage. Further increase of base voltage can now only increase the emitter and collector voltages back up to the positive rail, reaching a maximum at one  $V_{be}$  drop from the +8 V rail.

During the above process the voltage on the emitter of Q3 rises from zero to the same maximum voltage, and is fed to the inverting terminal of IC2, a CA3140 used as a comparator. The other comparator input receives 4 V derived from the potential

divider R11 and R12. This provides the required forward/reverse signal that corresponds to each half of the control pot. Inverter gate IC1f buffers the output of IC2.

C7 and C8 provide supply decoupling for both channels, while C5 and C6 provide further smoothing for the 8 V zener regulator formed by R16 and ZD1. This 8 V reference rail is used for two reasons; firstly to allow for fluctuation in the 12 V battery power supply that would otherwise affect the output pulse width, and secondly to ensure that the op-amp supply voltage is well above the maximum input voltage.

The resistor marked as Rx in the circuit shows where a speed feedback voltage will be added to the controller to close the velocity control loop. An infra-red tachometer module to directly sense the traction speed will be described later in the series.

If the manual control input is not required, the components associated with this can be simply omitted (ie RV1, R8, R9, R10, C4, Q3, IC2 and their equivalents in the other channel). Control voltages may now be fed to the unconnected end of R13, where a variation of 3 V, set by PR1 to be anywhere in the range 0 V to 8 V, will provide 100% control of the output pulse width. Forward/reverse switching must also be applied to the input of IC1f on pin 3.

### Resistors (all 1/4 W, 5%)

R1	100k
R2	15k
R3,6,17,20	2k7
R4,18	470R
R5,7,8,19,	
21,22	1k0
R9,10,23,24	22k
R11,12,25,26	10k
R13,15,27,29	1M0
R14,28	330k
R16,29	150R

### Potentiometers

RV1,2	10k linear
PR1,2	10k linear miniature horizontal preset

### Capacitors

C1	1n0 ceramic
C2,9	220p ceramic
C3,10	15n polycarbonate
C4,11	2u2 35 V tantalum
C5,7,12	100n ceramic
C6,13	220u 16 V axial electrolytic
C8	100u 25 V axial electrolytic

### Semiconductors

IC1	40106B
IC2,5	CA3140
IC3,6	LF353
IC4	4093B
Q1,4	BC214L
Q2,3,5,6	BC184L
LED1,2	red LED
ZD1,2	8V2 400 mW zener diode

### Miscellaneous

PCB (see Buylines)

will be switched alternately to each motor. This spreads the current peaks more evenly over the switching cycle.

Construction and setting up with interconnection details for the motor driver will be described next month.

**RELAY-A-QUIP**

**TOGGLE**

3amp  
250VAC

ON/OFF/ON - 88p  
ON/NONE/ON - 85p

**30W SEIKO**

**SOLDERING IRON**

220vac £2-95 £3-75

**FREE! NEW CATALOGUE**

**WE SUPPLY try us**

**?% OFF INDUSTRY ALSO.**

high impact styrene

**Z-BOX**

natural aluminium lid

a - 150(d) x 90(h) x 50(w)mm	£1-55 £1-94
b - 196(d) x 113(h) x 60(w)mm	£2-05 £2-65
c - 130(d) x 68(h) x 41(w)mm	£1-10 £1-28
d - 83(d) x 54(h) x 28(w)mm	£0-80 £1-00

**THE ALL ROUND RIBBING ALLOWS PCB's TO BE MOUNTED EITHER WAY**

**DIODES**

1N4148 - 2p  
1N4001 - 3p  
1N4002 - 3½p  
1N4003 - 4½p  
1N4004 - 5p

**Bridge Rectifier** 1amp 50v  
W0.005 - 16-5p

**mini relay. 4p2t.** 185ohm . 12v coil  
BASE - 45p  
Gold pt terms x 14 **£2-95** £3-75

**metal cabinets**

These are beautifully manufactured cabinets with an aluminium base and 18 gauge steel covers. They come fitted with rubber feet (to please the wife!), louvers for ventilation and finished in an attractive two-tone finish. They make excellent cabinets for power supplies, remote control units and many more projects.

a - 102(d) x 56(h) x 83(w)mm	£1-70 £2-12
b - 160(d) x 61(h) x 103(w)mm	£2-55 £3-20
c - 150(d) x 76(h) x 134(w)mm	£3-04 £3-80
d - 184(d) x 70(h) x 160(w)mm	£4-08 £5-00

**R.A.Q. 19" RACK-MOUNTING CABINET.**

★ Top, bottom and rear cover removable for access ★ Plates have heavy duty grey paint finish ★ Front panel is heavy gauge - 3mm aluminium ★ Strong screwed construction throughout - screws included ★ Heavy gauge chassis mounting plate is pre-drilled and has four mounting positions to choose from ★ Front panels of brushed aluminium finish enhanced with heavily chromed handles.

Front Panel 480 x 150 mm  
Rear Case 425 x 250 x 140 mm

£23-95  
**£19-50**

**TOP QUALITY**

Or Free Standing

This is a professional rack mounting cabinet that will allow you to get all your equipment off the floor. Rack mounting provides security for your equipment and easy access for maintenance. This Professional rack mounting cabinet has all the features you would expect from a professional unit. cat 8102480

ADD VAT at std rate %  
Order value under £5-00  
Add 50p. P and Pkg

**POWERSINK**

£1-35  
£1-70

Available in quantities to accept two power transistors of most types, including TO 3 TO 126, TO 220 TO-66 Size 75(1) x 102(w) x 25(d)mm. Thermal resistance mounting surface to ambient - 1°C/Watt (2 Oh/sec air velocity). Mounting surface temperature use above ambient 60°C = 30W heat dissipation

**SLIDE SWITCHES**

1P2T	10p	6P3T pcb	42p
2P2T pcb	12p	4P4T	45p
2P2T	12p	6P3T+	45p
2P3T	20p	4P3T side	48p
1P4T pcb	26p	1P2T spg/r/n	20p
4P2T	28p	6P3T toggle	55p
4P3T	35p	+ ALL KNOWN	

**ILLUMINATED**

Push to Make £1.35

**RELAY-A-QUIP PRODUCTS.**  
Moat Lodge, Stock Chase,  
MALDON, Essex, U.K. CM9 7AA.  
0621-58686

**VISA USE IT**



# CRICKLEWOOD

CRICKLEWOOD is a new name in electronics, but CRICKLEWOOD has been the home of electronic components since the 1960s, originally under a different name which many of you will be familiar with, but as they are still trading it would be unethical to mention their name.

Tel: 01 452 0161

TRY OUR SERVICE & WE HOPE YOU WILL BE DELIGHTED!  
Our phones are always manned and your written queries always receive a reply.

11587	60p	1N1196A	2.41	PW01 (100)	50p	VA1077	40p	LM301AH	2.00	LM3403	3.30	74181	1.80	74LS365	30p	74C911	9.50	4528	78p	6845	10.00	GRAPHIC
11588A	62p	1N1198A	2.65	PW02 (100)	75p	VA1074	40p	LM301A	2.00	MC3405 =	3.30	74182	90p	74LS366	45p	74C912	1.10	4527	1.10	6846	10.00	PROCESSORS
11590	20p	1N1201A	97p	PW04 (400)	85p	VA1086	40p	LM305AH	2.90	LM3405	4.10	74184	90p	74LS367	30p	74C914	1.98	4528	72p	6850	62.00	EF536
11591	30p	1N1204A	1.00	PW06 (600)	90p	VA1091	40p	LM305H	2.90	NE531N	1.50	74185	1.20	74LS368	81p	74C918	2.98	4532	80p	6852	42.00	EF536
11592	30p	1N1208	1.20			VA1098	40p	LM307H	1.90	NE544N	1.80	74186	3.30	74LS373	75p	74C920	2.50	4536	3.10	8131	3.75	HEAT SINKS
11593	60p	1N1305	1.80	25 amp type		VA1103	40p	LM308AH	3.15	NE555	20p	74187	72p	74LS378	75p	74C922	4.50	4538	1.20	8134	3.75	CLIP-ON
11594	60p	1N1306A	1.80	Metal clad with		VA1108	40p	LM308AH	3.15	NE555	20p	74188	72p	74LS378	75p	74C922	4.50	4538	1.20	8135	3.75	TO1 (AC128)
11595	60p	1N1307	1.80	hole		VA1104	40p	LM308AH	3.15	NE555	20p	74189	72p	74LS378	75p	74C922	4.50	4538	1.20	8136	3.75	TO2 (BF151)
11596	60p	1N1308	1.80			VA1108	40p	LM308AH	3.15	NE555	20p	74190	72p	74LS378	75p	74C922	4.50	4538	1.20	8137	3.75	TO18 (BC109)
11597	60p	1N1309	1.80			VA1109	40p	LM308AH	3.15	NE555	20p	74191	72p	74LS378	75p	74C922	4.50	4538	1.20	8138	3.75	TO220 (TIP2)
11598	60p	1N1310	1.80	Proprietary		VA1110	40p	LM308AH	3.15	NE555	20p	74192	72p	74LS378	75p	74C922	4.50	4538	1.20	8139	3.75	Many other sinks
11599	60p	1N1311	1.80	400V 1500V		VA1111	40p	LM308AH	3.15	NE555	20p	74193	72p	74LS378	75p	74C922	4.50	4538	1.20	8140	3.75	in stock including
11600	60p	1N1312	1.80	400V 1500V		VA1112	40p	LM308AH	3.15	NE555	20p	74194	72p	74LS378	75p	74C922	4.50	4538	1.20	8141	3.75	power sinks
11601	60p	1N1313	1.80	400V 1500V		VA1113	40p	LM308AH	3.15	NE555	20p	74195	72p	74LS378	75p	74C922	4.50	4538	1.20	8142	3.75	Please phone
11602	60p	1N1314	1.80	400V 1500V		VA1114	40p	LM308AH	3.15	NE555	20p	74196	72p	74LS378	75p	74C922	4.50	4538	1.20	8143	3.75	
11603	60p	1N1315	1.80	400V 1500V		VA1115	40p	LM308AH	3.15	NE555	20p	74197	72p	74LS378	75p	74C922	4.50	4538	1.20	8144	3.75	
11604	60p	1N1316	1.80	400V 1500V		VA1116	40p	LM308AH	3.15	NE555	20p	74198	72p	74LS378	75p	74C922	4.50	4538	1.20	8145	3.75	
11605	60p	1N1317	1.80	400V 1500V		VA1117	40p	LM308AH	3.15	NE555	20p	74199	72p	74LS378	75p	74C922	4.50	4538	1.20	8146	3.75	
11606	60p	1N1318	1.80	400V 1500V		VA1118	40p	LM308AH	3.15	NE555	20p	74200	72p	74LS378	75p	74C922	4.50	4538	1.20	8147	3.75	
11607	60p	1N1319	1.80	400V 1500V		VA1119	40p	LM308AH	3.15	NE555	20p	74201	72p	74LS378	75p	74C922	4.50	4538	1.20	8148	3.75	
11608	60p	1N1320	1.80	400V 1500V		VA1120	40p	LM308AH	3.15	NE555	20p	74202	72p	74LS378	75p	74C922	4.50	4538	1.20	8149	3.75	
11609	60p	1N1321	1.80	400V 1500V		VA1121	40p	LM308AH	3.15	NE555	20p	74203	72p	74LS378	75p	74C922	4.50	4538	1.20	8150	3.75	
11610	60p	1N1322	1.80	400V 1500V		VA1122	40p	LM308AH	3.15	NE555	20p	74204	72p	74LS378	75p	74C922	4.50	4538	1.20	8151	3.75	
11611	60p	1N1323	1.80	400V 1500V		VA1123	40p	LM308AH	3.15	NE555	20p	74205	72p	74LS378	75p	74C922	4.50	4538	1.20	8152	3.75	
11612	60p	1N1324	1.80	400V 1500V		VA1124	40p	LM308AH	3.15	NE555	20p	74206	72p	74LS378	75p	74C922	4.50	4538	1.20	8153	3.75	
11613	60p	1N1325	1.80	400V 1500V		VA1125	40p	LM308AH	3.15	NE555	20p	74207	72p	74LS378	75p	74C922	4.50	4538	1.20	8154	3.75	
11614	60p	1N1326	1.80	400V 1500V		VA1126	40p	LM308AH	3.15	NE555	20p	74208	72p	74LS378	75p	74C922	4.50	4538	1.20	8155	3.75	
11615	60p	1N1327	1.80	400V 1500V		VA1127	40p	LM308AH	3.15	NE555	20p	74209	72p	74LS378	75p	74C922	4.50	4538	1.20	8156	3.75	
11616	60p	1N1328	1.80	400V 1500V		VA1128	40p	LM308AH	3.15	NE555	20p	74210	72p	74LS378	75p	74C922	4.50	4538	1.20	8157	3.75	
11617	60p	1N1329	1.80	400V 1500V		VA1129	40p	LM308AH	3.15	NE555	20p	74211	72p	74LS378	75p	74C922	4.50	4538	1.20	8158	3.75	
11618	60p	1N1330	1.80	400V 1500V		VA1130	40p	LM308AH	3.15	NE555	20p	74212	72p	74LS378	75p	74C922	4.50	4538	1.20	8159	3.75	
11619	60p	1N1331	1.80	400V 1500V		VA1131	40p	LM308AH	3.15	NE555	20p	74213	72p	74LS378	75p	74C922	4.50	4538	1.20	8160	3.75	
11620	60p	1N1332	1.80	400V 1500V		VA1132	40p	LM308AH	3.15	NE555	20p	74214	72p	74LS378	75p	74C922	4.50	4538	1.20	8161	3.75	
11621	60p	1N1333	1.80	400V 1500V		VA1133	40p	LM308AH	3.15	NE555	20p	74215	72p	74LS378	75p	74C922	4.50	4538	1.20	8162	3.75	
11622	60p	1N1334	1.80	400V 1500V		VA1134	40p	LM308AH	3.15	NE555	20p	74216	72p	74LS378	75p	74C922	4.50	4538	1.20	8163	3.75	
11623	60p	1N1335	1.80	400V 1500V		VA1135	40p	LM308AH	3.15	NE555	20p	74217	72p	74LS378	75p	74C922	4.50	4538	1.20	8164	3.75	
11624	60p	1N1336	1.80	400V 1500V		VA1136	40p	LM308AH	3.15	NE555	20p	74218	72p	74LS378	75p	74C922	4.50	4538	1.20	8165	3.75	
11625	60p	1N1337	1.80	400V 1500V		VA1137	40p	LM308AH	3.15	NE555	20p	74219	72p	74LS378	75p	74C922	4.50	4538	1.20	8166	3.75	
11626	60p	1N1338	1.80	400V 1500V		VA1138	40p	LM308AH	3.15	NE555	20p	74220	72p	74LS378	75p	74C922	4.50	4538	1.20	8167	3.75	
11627	60p	1N1339	1.80	400V 1500V		VA1139	40p	LM308AH	3.15	NE555	20p	74221	72p	74LS378	75p	74C922	4.50	4538	1.20	8168	3.75	
11628	60p	1N1340	1.80	400V 1500V		VA1140	40p	LM308AH	3.15	NE555	20p	74222	72p	74LS378	75p	74C922	4.50	4538	1.20	8169	3.75	
11629	60p	1N1341	1.80	400V 1500V		VA1141	40p	LM308AH	3.15	NE555	20p	74223	72p	74LS378	75p	74C922	4.50	4538	1.20	8170	3.75	
11630	60p	1N1342	1.80	400V 1500V		VA1142	40p	LM308AH	3.15	NE555	20p	74224	72p	74LS378	75p	74C922	4.50	4538	1.20	8171	3.75	
11631	60p	1N1343	1.80	400V 1500V		VA1143	40p	LM308AH	3.15	NE555	20p	74225	72p	74LS378	75p	74C922	4.50	4538	1.20	8172	3.75	
11632	60p	1N1344	1.80	400V 1500V		VA1144	40p	LM308AH	3.15	NE555	20p	74226	72p	74LS378	75p	74C922	4.50	4538	1.20	8173	3.75	
11633	60p	1N1345	1.80	400V 1500V		VA1145	40p	LM308AH	3.15	NE555	20p	74227	72p	74LS378	75p	74C922	4.50	4538	1.20	8174	3.75	
11634	60p	1N1346	1.80	400V 1500V		VA1146	40p	LM308AH	3.15	NE555	20p	74228	72p	74LS378	75p	74C922	4.50	4538	1.20	8175	3.75	
11635	60p	1N1347	1.80	400V 1500V		VA1147	40p	LM308AH	3.15	NE555	20p	74229	72p	74LS378	75p	74C922	4.50	4538	1.20	8176	3.75	
11636	60p	1N1348	1.80	400V 1500V		VA1148	40p	LM308AH	3.15	NE555	20p	74230	72p	74LS378	75p	74C922	4.50	4538	1.20	8177	3.75	
11637	60p	1N1349	1.80	400V 1500V		VA1149	40p	LM308AH	3.15	NE555	20p	74231	72p	74LS378	75p	74C922	4.50	4538	1.20	8178	3.75	
11638	60p	1N1350	1.80	400V 1500V		VA1150	40p	LM308AH	3.15	NE555	20p	74232	72p	74LS378								

# HOW TO SUCCEED IN THE ELECTRONICS BUSINESS:

Available at your  
newsagent or  
direct for  
**60p p&p  
inc**

# INVEST 60p AND MAKE £2.40 net profit

Buy Ambit's new concise component catalogue and get £1 vouchers. Use them for a £1 discount per £10 spent. But even without this, you will still find WR&E offers the low prices, fast service and technical support facility second to none. Here are some examples from the current issue:



### I.C. SOCKETS

A range of high quality, low cost, low profile DIL sockets ideally suited for both the OEM and hobbyist. All types feature double sided phosphor bronze contacts, tin-plated for low contact resistance.

8 x 0.3" 12p	22 x 0.3" 20p
14 x 0.3" 13p	22 x 0.4" 20p
16 x 0.3" 13p	24 x 0.6" 22p
18 x 0.3" 18p	28 x 0.8" 25p
20 x 0.3" 19p	40 x 0.8" 35p
20 x 0.4" 19p	42 x 0.8" 38p

### VOLTAGE REGULATORS

78XX1A TO-220 pos	0.58
79XX1A TO-220 neg	0.60
78G 1A TO-220 adj pos	1.10
78G 1A TO-3 adj pos	3.95
78H5A TO-3 5v pos	4.25
78H5A TO-3 12v pos	5.45
78HG5A TO-3 adj pos	7.45
79HG5A TO-3 adj neg	7.45
LM317.5A adj pos	1.30
LM337.5A adj neg	1.75
78S401.5A adj pos sw reg	1.20

### DISCRETES

BC237	8p	BC566	12p	2SK168	35p
BC238	8p	BC560	12p	J310	69p
ZTX238	9p	BC639	22p	J176	65p
BC239	8p	BC640	23p	40823	65p
BC307	8p	25C1775A	22p	3SK45	49p
BC308	8p	25A872A	18p	3SK51	54p
BC309	8p	25D666A	30p	3SK60	58p
BC413	10p	25B646A	30p	3SK88	99p
BC414	11p	25D668A	30p	MEM680	75p
BC415	10p	25B648A	40p	BF960	99p
BC416	11p	BF256	38p	BF961	70p
BC546	12p	25K55	28p	BF963	99p

### XTALS

1MHz	3.00
3.2768MHz	2.00
4MHz	1.70
4.194MHz	1.70
4.43MHz	1.25
5MHz	2.00
6.5536MHz	2.00
7MHz	2.00
8MHz	2.00
9MHz	2.00
10MHz	2.00
11MHz	2.00

Prices shown exclude VAT. Postage 50p per order (UK). ACCESS/BARCLAYCARD may be used with written or telephone orders - official MA details on application, and a special prize for those who read our ads carefully - a free 4 or 8MHz crystal with every CPU IC you buy - just clip out this paragraph and attach it to your order. E&OE.

<b>CMOS</b>	4077 0.18	4705 4.24	7447N 0.62	74153N 0.55	74366N 0.85	74LS109N 0.20	74LS248N 1.35	<b>74CXX</b>	<b>Processors</b>
4000 0.11	4078 0.18	4706 4.50	7448N 0.56	74154N 0.55	74367N 0.85	74LS112N 0.20	74LS249N 1.35	74C00 0.20	<b>8080 series</b>
4001 0.11	4081 0.12	4720 4.00	7450 0.14	74155N 0.55	74368N 0.85	74LS113N 0.20	74LS251N 0.35	74C02 0.20	<b>8080AFC/2</b> £7.30
4002 0.12	4082 0.18	4723 0.95	7451N 0.14	74156N 0.55	74390N 1.85	74LS114N 0.18	74LS253N 0.35	74C04 0.20	8212 2.30
4007 0.13	4093 0.30	4724 2.95	7453N 0.14	74157N 0.55	74393N 1.85	74LS122N 0.35	74LS257N 0.40	74C08 0.20	8214 3.50
4008 0.50	4099 0.80	4725 2.24	7454N 0.14	74159N 1.90	74490N 1.85	74LS123N 0.35	74LS258N 0.37	74C10 0.20	8216 1.85
4008AE 0.80	4175 0.80	40014 0.50	7460N 0.14	74160N 0.55		74LS124N 1.80	74LS259N 0.60	74C14 0.95	8221 3.50
4009 0.25	4502 0.80	40085 0.99	7470N 0.28	74161N 0.55	<b>74LSN</b>	74LS125N 0.24	74LS260N 0.50	74C20 0.20	8224 8.21
4010 0.30	4503 0.50	40098 0.54	7472N 0.27	74162N 0.55	74LS00N 0.10	74LS126N 0.24	74LS265N 0.22	74C30 0.20	8255 5.40
4011AE 0.24	4506 0.70	40106 0.69	7473N 0.28	74163N 0.55	74LS01N 0.10	74LS132N 0.42	74LS279N 3.20	74C32 0.20	
4011 0.11	4507 0.37	40160 1.05	7474N 0.28	74164N 0.55	74LS02N 0.11	74LS133N 0.24	74LS275N 3.20	74C42 0.80	
4013 0.25	4508 1.50	40161 1.05	7475N 0.35	74165N 0.55	74LS03N 0.11	74LS138N 0.20	74LS279N 3.20	74C48 1.03	
4015 0.50	4510 0.55	40162 1.05	7476N 0.30	74166N 0.70	74LS04N 0.14	74LS139N 0.30	74LS280N 2.50	74C73 0.50	
4016 0.22	4511 0.45	40163 1.05	7480N 0.26	74167N 1.25	74LS05N 0.13	74LS139N 0.30	74LS280N 2.50	74C74 0.50	
4017 0.40	4512 0.55	40174 1.05	7481N 0.20	74170N 1.25	74LS06N 0.12	74LS145N 1.20	74LS283N 0.50	74C76 0.48	
4019 0.38	4514 1.25	40175 1.05	7482N 0.75	74173N 1.10	74LS08N 0.12	74LS151N 0.30	74LS293N 0.40	74C83 0.98	
4020 0.55	4515 1.25	40192 1.08	7486N 0.75	74174N 0.75	74LS10N 0.12	74LS153N 0.27	74LS295N 1.50	74C85 0.98	
4021 0.55	4516 0.80	40193 1.08	7488N 0.75	74175N 0.75	74LS11N 0.12	74LS154N 0.88	74LS298N 0.76	74C86 0.26	
4022 0.55	4518 0.35	40194 1.08	7489N 1.04	74176N 0.75	74LS12N 0.12	74LS155N 0.35	74LS365N 0.32	74C89 2.68	
4023 0.15	4520 0.60	40195 1.08	7490N 0.25	74177N 0.75	74LS13N 0.20	74LS156N 0.37	74LS366N 0.34	74C90 0.80	
4024 0.33	4521 1.30	<b>TTL</b>	7491N 0.30	74178N 0.75	74LS14N 0.30	74LS157N 0.30	74LS367N 0.32	74C93 0.80	
4025 0.15	4522 0.89	7400N 0.10	7492N 0.35	74179N 0.90	74LS15N 0.12	74LS158N 0.30	74LS368N 0.35	74C99 0.80	
4026 1.05	4527 0.80	7401N 0.10	7493N 0.35	74179N 0.90	74LS16N 0.12	74LS159N 0.30	74LS369N 0.35	74C107 0.48	
4027 0.26	4528 0.85	7402N 0.10	7494N 0.70	74180N 0.75	74LS20N 0.12	74LS160N 0.37	74LS373N 0.70	74C151 1.52	
4028 0.50	4529 0.70	7402N 0.10	7494N 0.70	74181N 1.22	74LS22N 0.12	74LS161N 0.37	74LS374N 0.70	74C152 2.26	
4029 0.55	4531 0.85	7403N 0.20	7495N 0.60	74182N 0.70	74LS22N 0.12	74LS162N 0.37	74LS375N 0.40	74C154 2.26	
4030 0.35	4532 0.80	7404N 0.12	7495N 0.60	74182N 0.70	74LS25N 0.12	74LS163N 0.37	74LS377N 0.85	74C155 1.52	
4035 0.67	4534 4.00	7405N 0.12	7497N 1.40	74184N 1.20	74LS26N 0.14	74LS163N 0.37	74LS377N 0.85	74C160 0.80	
4040 0.50	4536 2.50	7406N 0.22	7497N 1.40	74185N 1.20	74LS27N 0.12	74LS164N 0.40	74LS378N 0.65	74C161 0.80	
4042 0.50	4538 0.85	7406N 0.22	74100 1.10	74188N 3.00	74LS28N 0.15	74LS165N 0.80	74LS379N 0.60	74C162 0.80	
4043 0.50	4539 0.80	7407N 0.22	74104 0.62	74188N 3.00	74LS30N 0.12	74LS166N 0.80	74LS384N 2.50	74C163 0.80	
4043AE 0.33	4543 0.80	7408N 0.15	74105 0.62	74188N 3.00	74LS32N 0.12	74LS166N 0.80	74LS385N 2.05	74C164 0.80	
4044 0.60	4549 3.50	7409N 0.15	74107 0.26	74188N 3.00	74LS33N 0.15	74LS169N 0.85	74LS386N 0.29	74C165 0.84	
4046 0.60	4553 2.70	74109N 0.15	74109N 0.35	74188N 3.00	74LS37N 0.15	74LS170N 0.80	74LS389N 0.68	74C173 0.72	
4047 0.68	4554 1.20	74110N 0.12	74110N 0.54	74188N 3.00	74LS38N 0.14	74LS173N 0.80	74LS393N 0.61	74C175 0.72	
4049 0.74	4555 0.35	74111N 0.18	74111N 0.68	74188N 3.00	74LS40N 0.13	74LS174N 0.40	74LS395N 2.10	74C192 0.80	
4050 0.74	4556 0.40	74112N 0.19	74112N 0.70	74188N 3.00	74LS42N 0.30	74LS175N 0.40	74LS396N 1.99	74C193 0.80	
4051 0.55	4557 2.30	74113N 0.27	74116N 1.98	74188N 3.00	74LS47N 0.35	74LS181N 1.05	74LS398N 2.75	74C195 0.80	
4052 0.55	4558 0.80	74114N 0.51	74118N 0.85	74188N 3.00	74LS48N 0.45	74LS183N 1.75	74LS399N 2.30	74C196 0.80	
4053 0.55	4559 3.50	74116N 0.27	74119N 1.20	74188N 3.00	74LS49N 0.55	74LS189N 1.28	74LS445N 1.40	74C200 4.52	
4054 1.30	4560 2.50	74117N 0.27	74120N 0.95	74188N 3.00	74LS51N 0.13	74LS189N 1.28	74LS447N 1.95	74C221 1.06	
4055 1.30	4561 1.00	74118N 0.51	74121N 0.34	74188N 3.00	74LS55N 0.14	74LS190N 0.45	74LS490N 1.10	74C221 1.06	
4056 1.30	4562 2.50	74119N 0.27	74122N 0.34	74188N 3.00	74LS57N 0.21	74LS192N 3.45	74LS668N 1.05	74C901 0.38	
4059 0.75	4566 1.20	74120N 0.22	74123N 0.40	74188N 3.00	74LS73N 0.21	74LS193N 0.42	74LS669N 1.05	74C902 0.38	
4060 0.75	4568 1.40	74121N 0.22	74125N 0.40	74188N 3.00	74LS74N 0.16	74LS194N 0.35	74LS670N 1.70	74C903 0.38	
4063 1.15	4569 1.70	74122N 0.22	74126N 0.22	74188N 3.00	74LS75N 0.22	74LS195N 0.35	<b>RAM</b>	74C904 0.38	
4066 0.30	4572 0.22	74123N 0.22	74128N 0.65	74188N 3.00	74LS76N 0.20	74LS196N 0.55	2102	74C905 5.64	
4067 4.30	4580 3.25	74124N 0.22	74132N 0.50	74188N 3.00	74LS78N 0.19	74LS197N 0.60	2112	74C906 0.38	
4068 0.16	4581 1.40	74125N 0.22	74136N 0.65	74188N 3.00	74LS83N 0.40	74LS200N 3.40	2114 2	74C907 0.38	
4069AE 0.14	4582 0.70	74126N 0.22	74141N 0.45	74188N 3.00	74LS85N 0.60	74LS202N 3.45	4027	74C908 0.84	
4070 0.16	4583 0.80	74127N 0.22	74142N 1.85	74188N 3.00	74LS86N 0.14	74LS221N 0.50	4116 2	74C909 1.52	
4071 0.16	4584 0.27	74128N 0.22	74143N 2.50	74188N 3.00	74LS90N 0.32	74LS240N 0.80	4116 3	74C910 1.52	
4072 0.16	4585 0.45	74129N 0.22	74144N 2.50	74188N 3.00	74LS91N 0.28	74LS242N 0.70	4116 4	74C911 0.86	
4073 0.16	4586 0.45	74130N 0.12	74145N 0.75	74188N 3.00	74LS92N 0.31	74LS243N 0.70	6116P-3	74C912 0.86	
4075 0.16	4587 0.48	74131N 0.22	74146N 0.62	74188N 3.00	74LS93N 0.31	74LS244N 0.60	6116P-4	74C925 4.32	
4076 0.16	4588 0.48	74132N 0.22	74147N 1.50	74188N 3.00	74LS95N 0.40	74LS245N 0.80	8264	74C926 4.32	
4076 0.55	4589 0.48	74133N 0.22	74148N 1.09	74188N 3.00	74LS96N 0.20	74LS245N 0.80		74C927 4.32	
4076 0.55	4590 4.24	74134N 0.22	74149N 0.79	74188N 3.00	74LS107N 1.35	74LS247N 1.35			

TELEPHONE (STD 0277) 230909 TELEX 995194 AMBIT G POSTCODE CM14 4SG

**AMBIT international** 200 North Service Road, Brentwood, Essex

# SOLID STATE REVERB UNIT

Where have all the spring lines gone? Gone to lesser projects in other magazines, that's where. Meanwhile we present this cheap, simple, but high-quality unit using solid state technology.  
Design by Charles Blakey.



**A**t last — a reverberation unit which is not a pseudo echo effect and does not suffer from the defects of spring line devices. The unit described below will interface with virtually any preamplified signal and is ideal for direct use with most musical instruments or for incorporating in the 'echo-send' line of mixers. The design has been made possible by a new 3328-stage bucket brigade device having six tapped delays and capable of producing a useful reverberation time of about three seconds.

Sound emitted in an enclosed space will be subjected to both simple and multiple reflections from internal surfaces. Since these surfaces are at varying distances, the time for these reflections to occur and then decay by absorption will vary. The effect is a build-up of sound known as reverberation. When playing a musical instrument in the home, small studio or some other venue, the decay time can be very small coupled with a high absorption loss; the result is a weak sound when compared to recorded music or to live music played in a large hall.

Until now the only low-cost method of simulating acoustic reverberation has been the use of spring lines. These units, however, are prone to vibration, require a high

power consumption for effective driving and are prone to producing distorted resonant peaks. Furthermore it is not possible to adjust the reverberation time and in many instances a short reverberation can be very effective. Another option has been available for some years, namely, the use of bucket brigade devices to electronically delay signals. While claims have been made for reverberation effects based on these products, a realistic unit would require at least three dual 512-stage BBDs, such as the Reticon SAD1024A. The cost and complexity of the latter approach puts it beyond the reach of the average constructor.

## Beyond The Pail

The reverberation unit utilizes the MN3011, which is the latest in a series of bucket brigade devices for audio applications to come from National Panasonic. They are all fabricated in PMOS and for a start you can forget most of what you may have read about the disadvantages of PMOS BBDs. It is a fact that they are somewhat limited in clocking speed (10 kHz to 100 kHz) and also have a limited bandwidth, typically 10 to 12 kHz. The latter, however, is not usually a limitation since the bandwidth is often restricted

by the desire for long delay times. What makes the series ideal for audio applications is their low insertion loss, low distortion and excellent signal-to-noise ratio and for the MN3011 the specified values are 0 dB, 0.4% and 76 dB respectively.

The IC is unusual in that it has 12 pins but is the length of a normal 18-pin package; the functional block diagram and pinout for the MN3011 is shown in Fig. 1. As is normal with such devices it requires two power supplies,  $V_{DD}$  and  $V_{GG}$ ; the former may be up to  $-18$  V with respect to ground while  $V_{GG}$  should be  $+1$  V higher than  $V_{DD}$ . Bucket brigade, or charge coupled, devices are analogue shift registers which operate by sampling the input signal at a rate determined by an external clock. The signal level at the time of sampling is stored on an internal capacitor; this charge is then clocked down a series of capacitors by means of internal switches. The transfer process is accomplished by a dual clock whose outputs are in antiphase and so are alternately opening and closing adjacent switches. It will be apparent that the slower the clock speed the longer the delay. Since the devices operate at high clocking speeds the input signals are faithfully reproduced at the output.

The most interesting feature of the

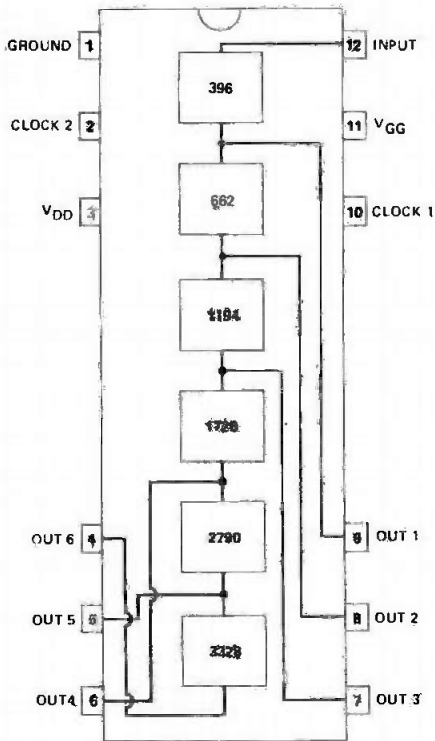



Fig. 1 Pinout and internal layout of the MN3011. The centre three pins on each side of this 18 pin package are absent.

MN3011 is that it has six tapped delays and Fig. 1 shows the number of stages for each tapping. The tapplings are not evenly spaced since otherwise the reverberant sound would have a distinct flutter. If the device was being clocked at 10 kHz then the delays from outputs one to six would be 19.8, 33.1, 59.7, 86.3, 139.5 and 166.4 milliseconds respectively. If these delay times are multiplied by 0.33 then one obtains the equivalent room path length for one trip, ie the longest delay is equal to a room length of 55 metres (181 feet). Reverberation time is usually measured as the time taken for the power to decay to one millionth of its initial level (60 dB down). For the present design the time was measured for the output level to fall to one hundredth of its initial level (-40 dB) and at the longest delay this was found to be about three seconds.

## Blocks 'n Clocks

The block diagram of the circuit for the reverberation unit is shown in Fig. 2. First there is the dual clock driver, which is another National Panasonic device, the MN3101. It has an oscillator, divider and wave form shaping and produces the dual clock pulses required by the MN3011. It reduces component count and is lower in cost than other alternatives, such as a 4007. A further advantage is that it also generates the required  $V_{GG}$  voltage.

The unit will operate satisfactorily

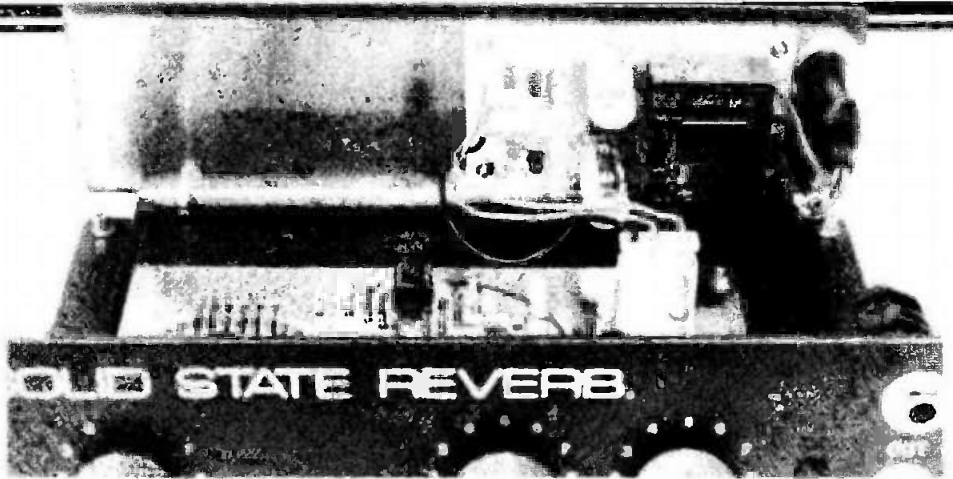

with any input signal greater than 280 mV RMS and higher input signals are attenuated by the input potentiometer. The signal is also reduced by half in amplifier A1 and inputs higher than 140 mV to the first filter are indicated by a LED peak detector circuit. Although the MN3011 will accept signal levels up to 780 mV before the distortion value stated earlier is exceeded, it will become apparent that the effect of reverberation can lead to reinforcement of signals and consequently this has to be allowed for. The only preset in the circuit is used to apply a bias voltage to the signal. The precise value of this voltage is not very critical in the current design and the object is to keep the signal at a level where it will not be distorted or clipped within the BBD.

The main problem with BBDs is the inability to completely cancel out the clock pulses and these can form audible cross products with the input signal. In order to prevent this foldover distortion, the bandwidth of the input signal should be limited to between a half and a third of the clock frequency. Filter F1 in Fig. 2 is a lowpass filter with a cut-off frequency of 3.6 kHz. This may seem rather low but in fact it is equivalent to the upper reverberation limit of most spring lines and the BBD scores in respect of low frequency responses since springs usually give rise

to 'booming' below 100 Hz. The limited bandwidth is compensated by mixing the original signal with the reverberated signal at the output stage. The filtered signal goes to the MN3011 and the six output stages are summed to give a composite signal with different delay times. This signal is again filtered with a lowpass filter with a cut-off frequency of 3.6 kHz, to remove residual clock glitches, prior to mixing with the original signal at the output amplifier, A2.

The most important feature, however, is that the signal from the longest delay is returned, slightly attenuated, to the input and subjected to further delays. This is the reverberation effect and with the times given earlier the sound will simulate the effect of the first reaching a surface 55 metres away (assuming slowest clocking rate) and then being reflected back as well as being reflected from other surfaces closer than the 55 metre surface. The whole process is repeated until the original delayed signal and its reflections die away. In the meantime new signals are being recycled and the overall effect is a build-up of sound — reverberation.

## Construction

The construction is very straightforward but the following precautions should be observed. First,

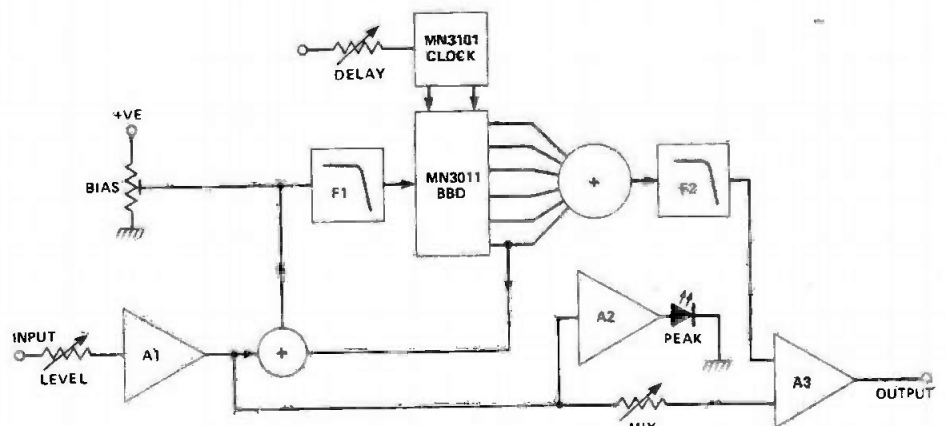


Fig. 2 Block diagram of the ET1 Solid State Reverberation unit.

# PROJECT : Solid State Reverb

## BUYLINES

The PCB and a kit of components for the reverberation unit is available for £32.00, inclusive of postage and VAT, from Digisound Limited, 13 The Brooklands, Wrea Green, Preston, Lancs PR4 2NQ. The power supply may also be obtained for an inclusive price of £7.00. As the PCBs are copyright they will not be available from our PCB Service; however, the foil patterns are reproduced at the back of the magazine. National Panasonic do not distribute active components in the UK and the ICs may *only* be obtained from Digisound.

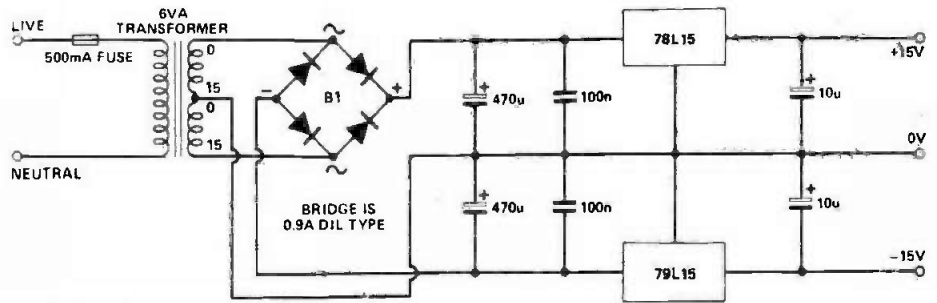


Fig. 4 Circuit diagram of a suitable PSU for this project.

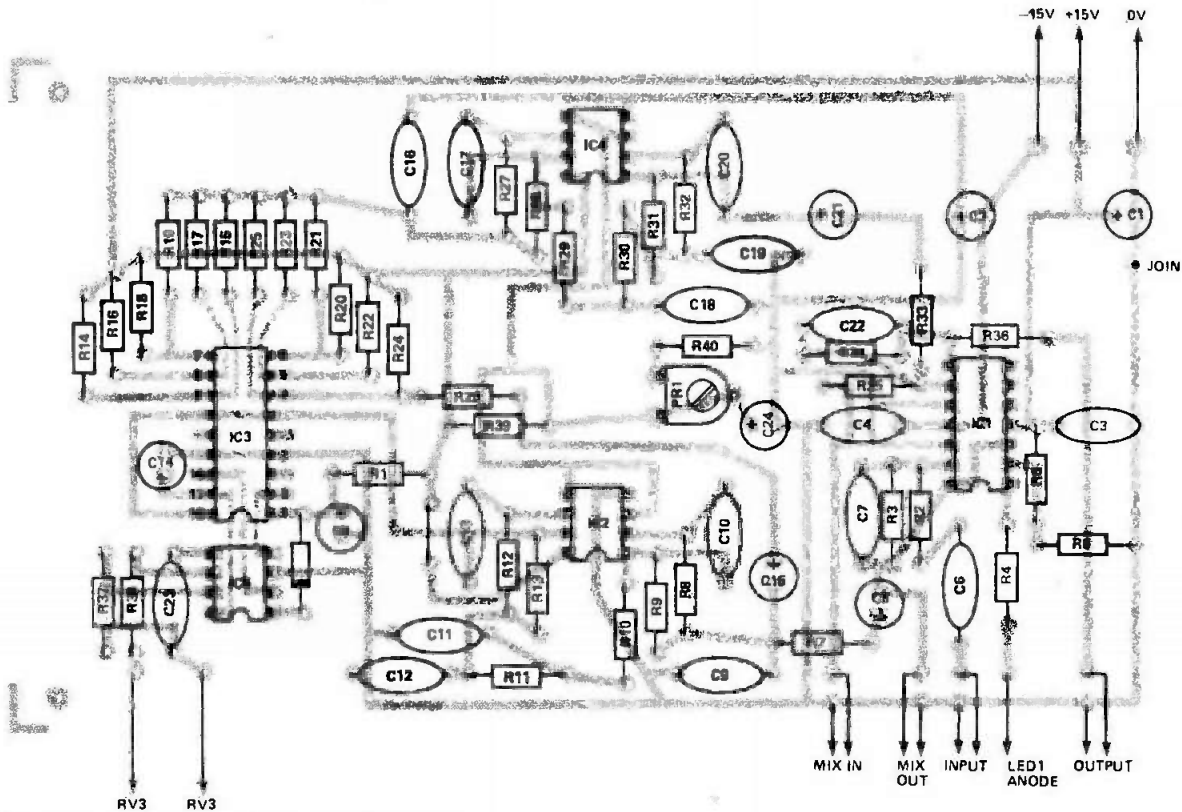


Fig. 3 Component overlay for the reverberation unit.

make sure you get the correct orientation of the ICs which are clearly shown on the component overlay. Second, the MN3011 is a CMOS device and with the advent of 'B' series devices we have all become rather careless as regards handling such ICs. For the MN3011, however, take the precaution of working on a grounded

## PSU PARTS LIST

**Capacitors**  
 C1,2 470u 35 V PCB electrolytic  
 C3,4 100n polyester  
 C5,6 10u 35 V PCB electrolytic

**Semiconductors**  
 IC1 78L15  
 IC2 79L15  
 BR1 0A9 DIL type

**Miscellaneous**  
 PCB (see Buylines); PCB-mounting transformer (15-0-15, 6 VA); 500 mA mains fuse and chassis-mounting holder.

## PARTS LIST

**Resistors (All 1/4 W 5% except where stated)**

R1 10R 1/2 W  
 R2,5,7,9, 13,32,33,39 100k  
 R3,34 51k  
 R4 330R  
 R6 1k3  
 R8,12,27,31 33k  
 R10,29,37 47k  
 R11,30 56k  
 R14,16,18,20, 22,24 56k 1%  
 R15 100k 1%  
 R17 110k 1%  
 R19 120k 1%  
 R21 130k 1%  
 R23 150k 1%  
 R25 160k 1%  
 R26 200k  
 R28 82k  
 R35 18k  
 R36 1k0  
 R38 36k  
 R40 68k

**Potentiometers**  
 RV1 100k logarithmic  
 RV2 10k logarithmic  
 RV3 470k linear

PR1 47k miniature horizontal preset

**Capacitors**

C1,2 10u 35 V PCB electrolytic  
 C3,4 100n polyester  
 C5 22u 35 V PCB electrolytic  
 C6 220n polyester  
 C7,10,13, 20,22 220p polystyrene  
 C8,14,15, 21,24 3u3 63 V PCB electrolytic  
 C9,11,12, 18,19 2n7 polystyrene  
 C16 2n2 polystyrene  
 C17 270p polystyrene  
 C23 33p polystyrene

**Semiconductors**

IC1 TL074  
 IC2, 4 LM358  
 IC3 MN3011  
 IC5 MN3101  
 D1 1N4148  
 LED1 5 mm red LED

**Miscellaneous**

SK1,2 mono jack sockets  
 PCB (see Buylines); IC sockets; case (Vero order no. 91-2673G).

metal surface, such as a piece of aluminium foil, do not insert the IC with the power on and do not use a soldering iron on the PCB with the IC installed.

The PCB supplied with the kit has a ground plane to reduce interference from and to other electronic equipment as well as to reduce noise. This feature allows greater freedom in locating the unit, eg it does not have to be housed in a separate metal case. A ground plane comprises a metallized surface on the component side except for small areas around the holes for the components. Ensure that the component leads do not touch the ground plane — which is not difficult — and preferably solder the resistors and axial capacitors in place with a thin piece of card between the component and the board so that the former are not in physical contact with the ground plane. After soldering the card is removed. The latter step is not essential. The one wire link must be made with insulated wire. The ground plane has to be connected to the 0 V line and some 15 mm from where the latter is connected to the PCB there is a hole marked 'join'. A piece of wire should be placed through this hole and soldered on both sides of the PCB.

The PCB has been laid out such that the BBD and clock are as far away as practical from the signal input and output. This separation should be maintained if the unit is housed in a

box and all wiring should be kept as short and as neat as practical, with the audio connections being made with miniature screened cable.

The unit requires a  $\pm 15$  V power supply and the current consumption is a miserly 13 mA at +15 V and 9 mA on the -15 V line. If a separate power

supply is required then a suitable PSU is shown in Fig 4. A PCB-mounted transformer is preferred, and it should be mounted as far away from the BBD as practical. The photographs show the unit inside a Vero 'G' range case with internal dimensions of approximately 218 x 138 x 50 mm.

## HOW IT WORKS

The input signal is attenuated by RV1 and also by the inverting amplifier built around IC1a which has a gain of about 0.5. From IC1a the signal goes three ways. A comparator built around IC1b forms a peak detector to indicate optimum signal level, while RV2 and R35 allow mixing of the original signal with the reverberated signal in the inverting amplifier configured around IC1c. The component values in this section are such that equal proportions of the two signals may be mixed. Finally the signal also passes to two active filters constructed around IC2 which have a 12 dB/octave roll-off for each stage and a cut-off frequency of 3.6 kHz.

From the above filter stages the signal passes into the MN3011 and the six delay outputs are summed by the resistor network formed by R14 to R25. Note that the shorter the delay, the less the attenuation. From the longest delay (pin 4) the signal goes via R25 back to the input of the filter and thus provides recycling of the delayed signal in order to generate a true reverberation effect. The reverberated signal is filtered by two active filters constructed around IC4 and these have the same characteristics as the input filters. Between the active filter stages some passive filters have also been

added to increase the roll-off; the loss in these filters is compensated by increasing the gain of the active filters.

The dual clock for the MN3011 is provided by IC5 and with the components shown, the clock frequency may be manually varied with RV3 over the range 10 kHz to 100 kHz, allowing maximum first pass delays from 16.64 to 166.4 milliseconds. Pin 8 of IC5 provides the  $V_{CC}$  voltage for the MN3011. Since both IC3 and IC5 are P-channel CMOS it would be normal to operate them from a -15 V supply. Voltages are, however, relative and by connecting +15 V to the ground pin and ground (0 V) to the  $V_{DD}$  pin they will operate happily with positive signal inputs. R1 and C5 prevent clocking signals getting back into the power lines. The filters are also operated from a single +15 V supply and this avoids any problems which may arise from excessive bipolar signals, ie they will be clipped at +15 V or ground and not damage the BBD. The bias voltage required by the BBD and the filters is primarily to allow them to accept bipolar signals; this voltage is provided by the resistive divider using components R39, PR1 and R40 and is applied to the non-inverting input of the filter op-amps.

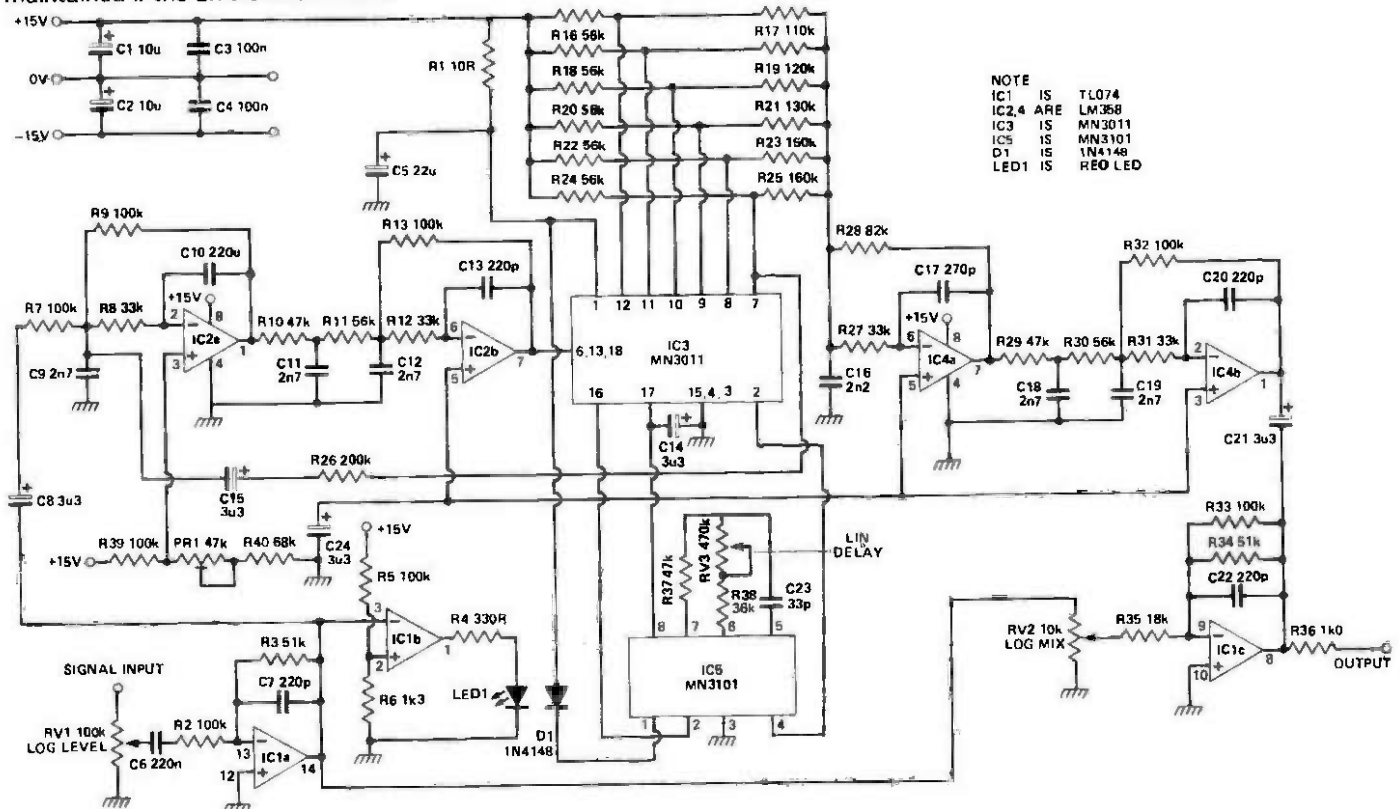



Fig. 5 Circuit diagram for the ETI Reverb.


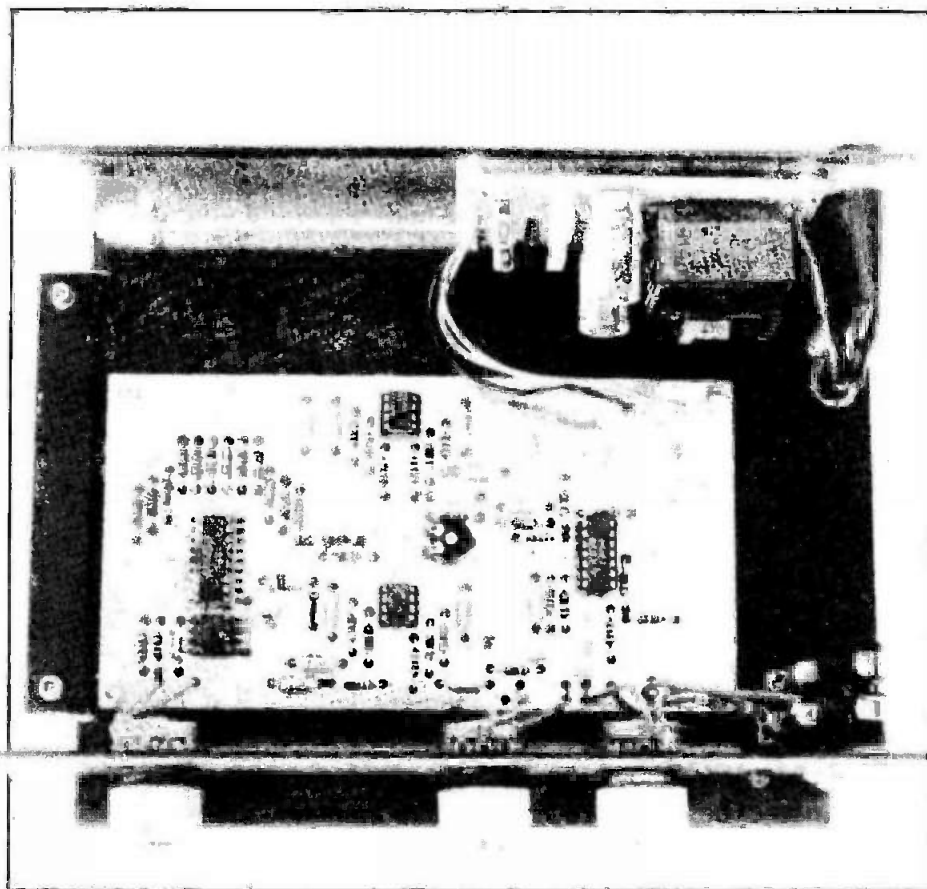
## Setting Up And Use

The only setting up required is adjustment of PR1. If a sine wave source is available then the latter may be used as the signal source and PR1 adjusted by ear, or with an oscilloscope, for minimum distortion. Alternatively measure the voltage at the junction of PR1 and R40 and adjust PR1 to give a reading of 6V2.

The unit has a signal-to-noise ratio of better than 60 dB but this requires that it is operated with the peak indicator LED just glowing or occasionally illuminating. The output level will vary from about 0V5 to 1 V RMS, depending on the amount of mixing of the original signal, and these levels should ensure adequate response from most amplifiers, mixers, and so on. In other words, by keeping input signals at maximum level the amplifier setting will be such that during periods of no signal the residual noise will not be obtrusive. This is common practice with recorders, many of which have much lower signal-to-noise ratios.



ETI



## For the man who has everything else . . .

... there is the ETI binder. Spend your nights enjoying the finer things in life, secure in the knowledge that the finer magazines of life are safe and sound. Order one now, and let the Joneses keep up with you.

ETI Binders cost **£3.95 each** for UK residents, including postage, packing and VAT. For overseas orders add 30p. Send the completed coupon together with your remittance to:

**ETI Binders, Argus Specialist Publications Ltd,  
145 Charing Cross Road, London WC2H 0EE.**

Please allow three-four weeks for fulfillment of order.

### ORDER FORM

Please send me  ETI Binders. I enclose cheque/postal order for £

I wish to pay by Access/Barclaycard. Please debit my account.

5	2	2	4																
4	9	2	9																

Signed \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

TTL CMOS 74LS LEDs

# LB ELECTRONICS

LINEAR RAMS EPROMS SURPLUS

TELEPHONE UXBRIDGE 55399

**SUPERSALE '81**  
All full spec. brand new devices.  
2114 (450ns) £1.00, 4116 (200ns) £1.15, 2708 £1.85, 2516 (single rail) £3.00, NEC 2732 £5.50, 2532 £6.00, 2114 (200ns) £1.40. P/P 35p on above devices.  
Brand new and boxed, Lie Detector. Made for the Open University. size: 150mm (length) x 100mm (width) x 90mm (height). Complete with 100 microamp motor movement 90mm x 76mm. Supplied complete with leads and pads, less batteries (2 x 4.5v) £7.50 + £2 p/p.

**SELF-CONTAINED** battery powered digital recorders. Complete with data entry keyboard with 10 digit LED display plus modern interface and charger. Some data £25 per system. Sorry, callers only.

**ZETTLER** low profile PCB relay 30mm x 36mm 4.8/6.9v d.c. 2/2.6 amps a.c. contacts. 85p p/p 35p.

**D TYPE CONNECTORS**  
9 Way Socket (solder) 75p  
15 Way wirewrap plug £1.00  
37 Way Plug (solder) £1.80  
37 Way Socket (solder) £1.80  
25 Way Plug (solder) £1.85  
25 Way Socket (solder) £1.85  
25 Way Plug (insulation piercing) £2.65  
25 Way Socket (insulation piercing) £2.65  
50 Way Plug (solder) £2.00  
P/P on above 35p

**COVERS**  
37 Way (Plastic) £1.00, 50 Way (Plastic) £1.20, 25 Way (Plastic) 95p, 25 Way (Metal) £1.25, 25 Way (Metal) ITT open £1.00, 15 Way (Plastic) 60p, 15 Way (Metal) 95p  
P/P on above 35p

**DISPLAYS**  
HP 5082/7414 4 digit DIL display full spec £1.50 each, p&p 35p. Large quantities POA

HP5082/7650 .4"cc, left and right decimal point, high brightness, only 85p, 12 for £6.50, p&p 35p.

**SUPERSAVER 1**  
DIL Header Plugs (No covers) 14 way 18p, 16 way 25p, 24 way 95p (all gold plated) p/p 35p. Ansley Header plugs, 14 Way 75p, 16 Way 95p, 24 Way £1.50. (insulation piercing type) p/p 35p. Ansley I/O Header plugs PCB Mounting .1in 26 Way straight 65p, 40 Way r/a £1 p/p 35p.

**SUPERSAVER 2**  
Tantalum Capacitors 25 volt. 4.7 uF, 14 for £1, p&p 35p.

**PRICE SMASH PND500** 5in. LED displays, full spec 65p each, p&p 35p, large quantities POA.

**SUPERSAVER 5**  
3M 34 way (17 x 17) .1" insulating piercing edge connectors for disc drives etc. £3.50 each, p/p 35p.

**SUPERSAVER 6**  
VIDEO LEAD  
1 1/2 metres with PL259 plug £1.00 p/p 35p

**SUPERSAVER 7**  
Thyristors Type 16 Ria 100 Vrrm 1000 Volts at 22 amps £1.85 each. Limited stock, p/p 35p  
Stud mounted rectifiers, type 40 HF 100 1250 volts, 40 amp, 4 for £2.50 p/p 35p

**SUPERSAVER 8**  
ONE ONLY - TEXAS SILENT 700 TERMINAL RS232 110 baud. As new - £235. Carriage at cost.

**SUPERSAVER 9**  
VELLEMAN EPROM Programmer kit £200. Built £300 + VAT. S.A.E. for full descriptive leaflet.

**SUPERSAVER 10**  
Tangerine Microtan 65 Blank PCB. Brand new plus circuit diagram £4.50, p/p 50p (6502 based, 1K on board).

**SUPERSAVER 11**  
PAPST MINI-FAN 3 1/4" x 3 1/4" x 1.5" deep. 220V 50Hz. Brand new and boxed. £9.50 p/p £1.00.

**SUPERSAVER 12**  
2.5mm power plug and 2 metres of cable. Suitable for Acorn Atom, ZX81 etc. Only £1.00 per 10 p/p 25p. Trade enquiries welcome.

**SUPERSAVER 14**  
BOX FANS 115V 50/60Hz. 120mm x 120mm. New. £4.50. P/P £1.00.

**SUPERSAVER 15**  
5K 3/4" multiterm trim pots, PCB mounting, per box of 14 £2.50. As above 1K and 50K, p&p 35p.

**SUPERSAVER 16**  
OPTRON OPTO SLOTTED SWITCH (Type OPB-814) £1, p&p 35p.

**SUPERSAVER 17**  
VU METER 48mm x 50mm approx. overall size. Face size 50mm x 28mm approx. Brand new. £1.15 p&p 35p. (Sent at purchaser's risk).

**SUPERSAVER 18 SALE**  
PCB AMP (LM380) Unused. 65mm x 95mm approx. 9-12V DC. 85p p&p 35p.

**SUPERSAVER 19**  
10 DIGIT (Red). LED display. (1.22in. digit size). With built-in driver chip and built-in lens magnifier. Data sheet supplied. Brand new. £1.50 p&p 35p.

**SUPERSAVER 20**  
4 1/2in. JUMPER LEAD, 16 DIL header to 16 DIL header. 95p p&p 30p.

**SUPERSAVER 21**  
2 1/2in. JUMPER LEAD, 14 DIL header to 14 DIL header. 55p p&p 30p.

**SUPERSAVER 22**  
1lb reel of solder 18 SWG 64/36 alloy £5.50 p&p 90p.

**A TERRIFIC GIVEAWAY. MC 1489 RS232 RECEIVER.** Brand new 46p each, 10 for £3.50. Large quantities p.o.a. p&p 30p.

**SUPERSAVER 23**  
16K EPROM PCB 275mm x 18mm takes 8 x 4K eeproms + address decoder logic ranged as 16K x 16. Sorry no data. £3.50 p/p 30p.  
**JUST ARRIVED** large quantity of assorted Microwave Wave Guides, various bands + noise sources from £5. Callers only.

**CMOS SCOOP**  
CD4012 10 for £1.50, CD4013 10 for £2.25, CD4018 60p each, CD4019 10 for £3.85, CD4022 10 for £4.00, CD4023 10 for £1.30, CD4027 10 for £3.00, CD4035 10 for £6.00, CD4049 10 for £2.25, CD4050 10 for £2.50, P/P 35p per lot.

**GIVEAWAY** 18 pin low profile dill socket 13p EACH or 8 for £1

**AUGAT IC SOCKETS**  
(The best available)  
16 Dill 20p 24 Dill 50p  
18 Dill 25p 40 Dill 55p

**WE STOCK** a vast range of TTL, CMOS, some 74LS, MINIATURE TOGGLE, etc.  
PSUs. We have a large stock of power supplies at very realistic prices (callers).

**NEW LINES**  
UECL Edge connector .1" 75 Way gold plated (wire wrap) £1.65 each p/p 35p.

**REG PCB** (less components), 5V 1 amp, 12V 1 amp and heatsink (60mm x 90mm). Brand new, £1.00. Heatsink only, 55p. P/P 35p.  
**NEC FIP4B13** 4 digit glass display (green with centre colons and plus and minus sign), only £1.35. P/P 30p.

**PL259 SOCKET CHASSIS MOUNT.** 50p p&p 30p.

**TRANSFORMERS** 012, 024 1 amp £2.50, P&P 50p.  
TTL SALE 7410 9p, 7413 18p, 7416 18p, 7490 28p, 74155 45p, 74174 60p, 74181 74285 £2.25. P&P 35p.

**WHY PAY POUNDS? -** Just arrived Amphenol 36-way plug and socket (used) to fit all your printer. Only £2.75 per pair. P/P 35p.  
Terms cash with order (official orders welcomed from colleges, etc). All enquiries s.a.e. please. All prices inclusive of VAT, unless otherwise stated. Postage as shown per item.

**STOP PRESS**  
2716 Single rail Eprom (fused). Fully erased, replacement guaranteed. £1.95, 10 for £17.  
**P/P FREE**

**PLEASE DO NOT ORDER GOODS FROM OLD ADVERTS. PHONE BEFORE ORDERING.**  
**SURPLUS STOCKS PURCHASED FOR CASH**

**LB ELECTRONICS**  
11 HERCIES ROAD  
HILLINGDON, MIDDLESEX  
UB10 9LS, ENGLAND  
All enquiries s.a.e. please  
Telephone answering machine service out of business hours.  
New retail premises, now open Mon, Tues, Thurs, Fri, and Sat, 9.30-6.00. Lunch 1-2.15 weekdays. Closed all day Wednesday. We are situated just off the A40 opposite Master Brewer.  
**ALL PRICES INCLUSIVE OF VAT**  
**UXBRIDGE 55399**  
All components full spec

## ONE STOP SHOPPING

No need to waste your time and money searching for components. No need for unfinished projects because you are unable to obtain that last component.  
We stock complete sets of parts for ETI projects - leaving you to concentrate on the electronics and construction.

### 3 WAYS TO BUY:

**FULL KITS** - include printed circuit board, all components, hardware, IC sockets, case etc. (Not batteries).  
**LESS CASE** - as above but less the case.  
**PCB + PCB MOUNTED COMPONENTS** - PCB plus all the parts which are mounted on the board - plus leds, potentiometers + off board semi-conductors.

	FULL KIT	LESS CASE	PCB PLUS
INFINITE IMP. DET. Mar 82	15.98	9.50	-
ROBOT MOTOR CONTROL (OUAL) Mar 82	38.67	33.72	-
1 CHING COMPUTER Feb 82, less book	£32.83	£24.20	-
HIGH QUALITY PHONO AMPLIFIERS Feb 82	-	-	-
MOVING COIL STAGE	17.98	-	-
MOVING MAGNET STAGE	17.68	-	-
PEST CONTROL Feb 82	6.77	-	-
INFANT GUARD Jan 82	6.39	-	-
PARKING METER TIMER Jan 82	8.99	-	-
GUITAR TUNER Jan 82	28.98	26.27	18.98
ALCOHOMETER Dec 81	£26.49	£22.99	-
COMPONENT TESTER Dec 81	£7.98	£6.17	-
BODYWORK CHECKER Dec 81	£8.88	£4.59	-
MUSIC PROCESSOR Nov 81	49.98	36.98	31.84
PHONE BELL SHIFTER Nov 81	19.35	13.61	8.32
VOICE OVER UNIT Nov 81	27.62	21.22	15.32
CAR ALARM Nov 81	17.98	14.45	12.80
ENLARGER TIMER Oct 81	26.59	21.85	9.98
SOUND BENDER Oct 81	20.76	15.76	11.77
MICROPOWER THERMAL ALARM Oct 81	-	9.88	-
MICROPOWER PENDULUM Oct 81	-	5.50	-
LAB PSU Sept 81	-	37.98	22.40
WATCHDOG SECURITY ALARM Aug 81	43.33	35.83	19.98
RECHARGEABLE BATTERY	19.98	-	-
HEARTBEAT MONITOR Aug 81	26.26	21.65	13.80
HANDCLAP SYNTHESIZER Aug 81	29.98	23.58	18.44
FLASH SEQUENCER Aug 81. Less flash sockets.	35.65	29.25	21.25
SMART BATTERY CHARGER July 81	31.98	25.98	9.84
WAH PHASE June 81. Less pedal	-	13.44	9.14
LED JEWELLERY June 81	Cross	2.47	-
Star	9.41	-	Spiral 7.20

ALIEN ATTACK Jan 81	19.76	16.47	12.83
MINI DRILL SPEED CONTROLLER June 81	25.13	21.13	12.60
GUITAR NOTE EXPANDER - ETI April 81	16.47	11.25	6.44
DRUM MACHINE April 81	59.98	46.94	35.38
MUSICAL BOX April 81	12.54	-	-
ENGINEERS STETHOSCOPE Mar 81	19.19	14.92	11.10
SOUND PRESSURE LEVEL METER Feb 81	39.98	32.98	-
INFRA RED ALARM Feb 81	54.98	46.12	35.38
MULTI-OPTION SIREN Jan 81	26.91	21.63	15.25
4 INPUT MIXER Dec 80	19.77	15.71	11.98
MUSICAL DOORBEL Dec 80	11.61	10.61	9.39
AUDIO TEST OSCILLATOR Nov 80	18.30	-	-
RIAA PRE-AMP (stereo) Nov 80	6.83	-	-
METRONOME Nov 80	5.98	-	-
SUSTAIN/FUZZ BOX Oct 80	24.99	21.49	18.72
CASSETTE INTERFACE Oct 80	-	11.57	-
ULTRASONIC BURGLAR ALARM Aug 80	26.82	22.98	17.62
CAPACITANCE METER Aug 80	20.26	16.46	8.21
CMOS LOGIC TESTER Aug 80	10.97	-	-
SIGNAL TRACER Mar 80	11.98	-	-
TUNING FORK Feb 80	13.48	-	-
CLICK ELIMINATOR April 79	61.55	46.57	-
GUITAR EFFECTS UNIT April 79	14.78	10.97	6.41
COMPLEX SOUND GENERATOR Oct 78	-	21.97	-

**THIS MONTHS PROJECTS WRITE (SAE) OR PHONE FOR PRICES**  
If you do not have the issue of E.T.I. which includes the project you will need to order the instruction reprint as an extra - 45p each  
Reprints available separately 45p each + p&p 40p

**GUITAR TUNER**  
Full kit as described in Jan 82. Includes case, pcb's and meter etc £28.98  
All parts available separately

**MAGENTA ELECTRONICS LTD.**  
EU11, 135 HUNTER STREET, BURTON-ON-TRENT, STAFFS, DE14 2ST  
0283-65435. 9-5 MON-FRI. MAIL ORDER ONLY

ALL PRICES INCLUDE VAT  
ADD 45p P&P TO ALL ORDERS  
S.A.E. WITH ALL ENQUIRIES PLEASE

Irish Republic & B.F.P.O. Europe deduct 10% from prices shown. Payment must be in sterling.  
Access and Barclaycard (Visa) orders accepted by phone or post.

# POWERTRAN

# IS BRINGING THE FUTURE A STEP NEARER


WITH THEIR

## NEW MICROPROCESSOR CONTROLLED
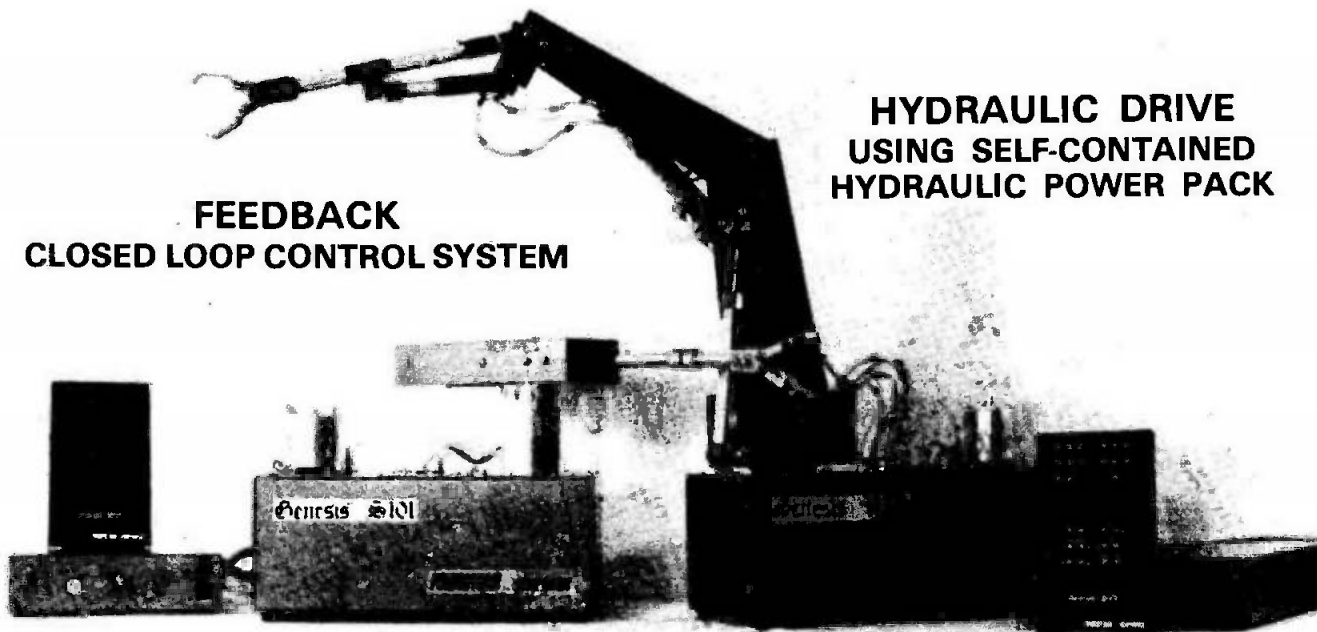
## PROGRAMMABLE *Genesis* ROBOTS

FEEDBACK  
CLOSED LOOP CONTROL SYSTEM

HYDRAULIC DRIVE  
USING SELF-CONTAINED  
HYDRAULIC POWER PACK



UNITS MAY BE OPERATED USING ROBOTS OWN DEDICATED  
MICROPROCESSOR SYSTEM OR BY AN EXTERNAL COMPUTER

### Features

- Low cost
- Up to 6 controllable movements
- Positional sensing
- Continuous path motion
- Microprocessor controller
- Learning ability
- RS232C computer interface


Kit prices below.  
Prices for ready  
built systems on  
request.

	4 axis	5 axis	6 axis	Interface Processor Electronics	Hand Held Controller Box
Genesis M101 <i>Including wheelbase</i>	£374	£424	—	£135	£47
Genesis S101	£355	£405	—	£175	£33
Genesis P101	£450	—	£545	£175	£33.50

ALL PRICES VAT EXCL.

AS BEING PUBLISHED IN

### PRACTICAL ELECTRONICS

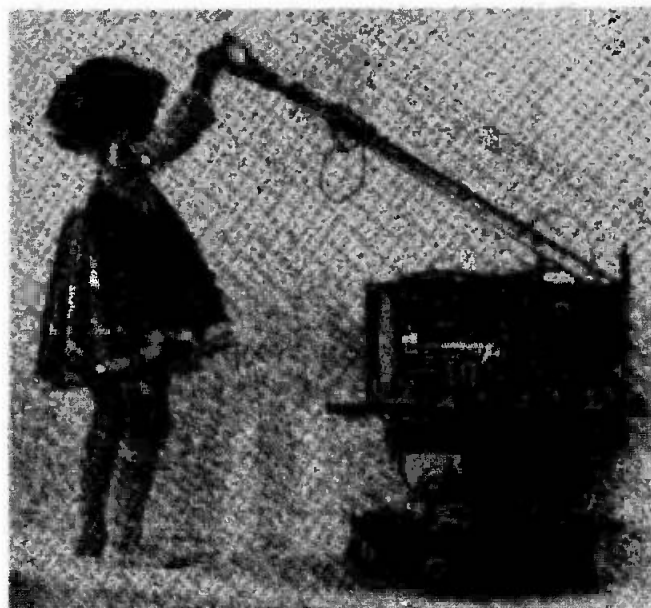

M101 MOBILE

For further details please contact:—

### POWERTRAN CYBERNETICS


PORTWAY INDUSTRIAL ESTATE, ANDOVER, HANTS SP10 3NM

Telephone: ANDOVER (0264) 64455

# AUTORANGING CAPACITANCE METER

Look — no hands! The only control on this piece of test-gear is the on/off switch; the only connection is to the test terminals. This month — construction.

Design and development by Phil Walker.

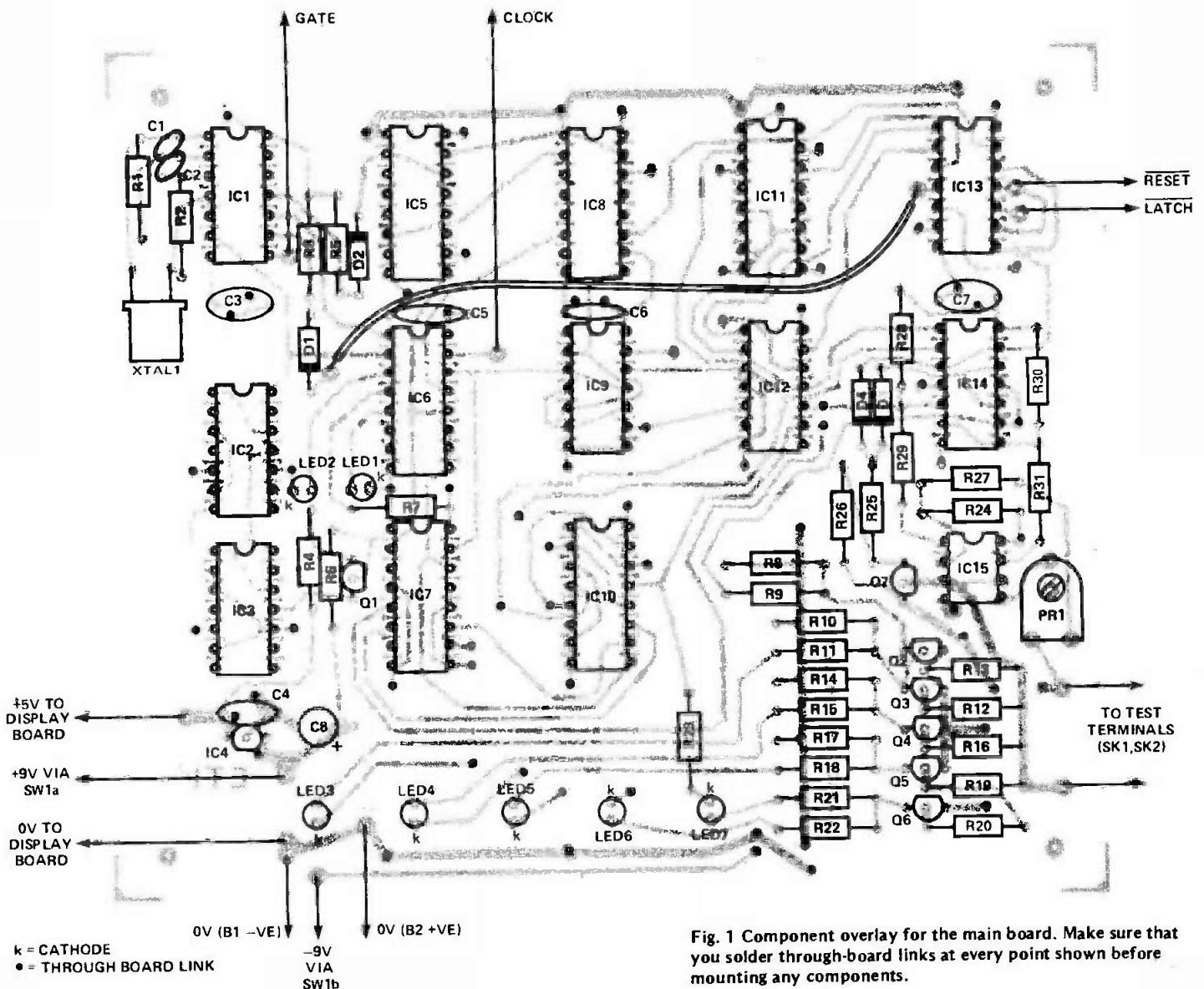

This is a fairly complex project and should only be attempted by those with a good deal of constructional experience. It is well worthwhile checking the PCB for shorts between tracks before doing anything else. Ensure that there is a hole through the board under the PR1 position to facilitate adjustment later.

Put links through the board at all positions marked with a dot on the overlay and solder on BOTH sides of the board. The other components may now be inserted into the board — preferably using sockets for all the ICs except IC4 and IC15. IC4 is a T092-type package 100 mA regulator and does not need a socket, while IC15 may foul PR1 if a socket is used.

The LEDs should not be fitted until the board is test-fitted in position as

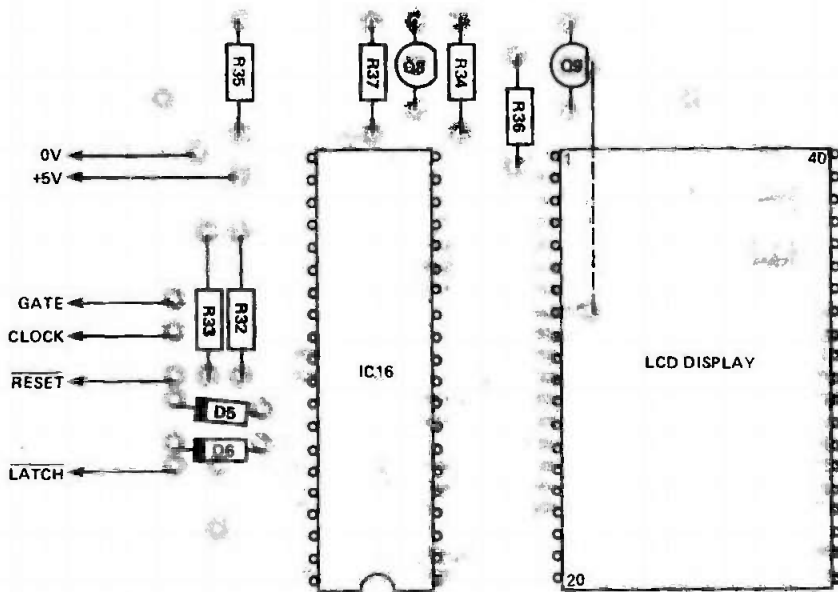
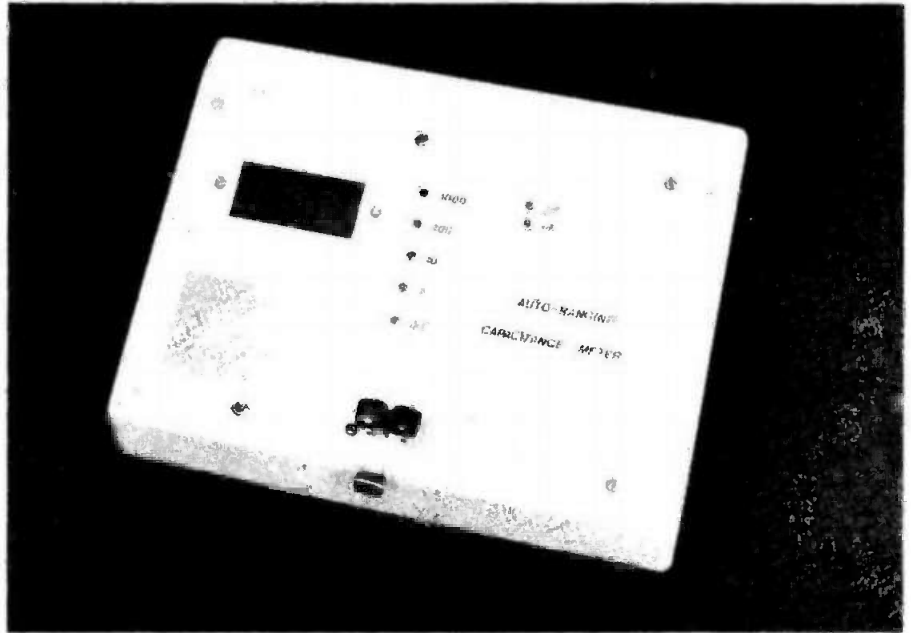


Fig. 2 Component overlay for the display board. Insert the link under the display first.

they are intended to protrude through the panel as indicators. Attach power supply wires and fit up to the panel, position the LEDs and solder in position.

Assemble the display board components and attach the logic and power supply wires from the main board. Wire the remaining power leads via the on/off switch to the battery connectors and attach the two boards to the front panel using pillars or long bolts and lock nuts. Our prototype just fitted into a slope fronted instrument case made by Vero Industries (see Parts List).

## BUYLINES

Very few unusual components in this project; all the logic is standard CMOS. The ICM7224 and the LCD display is stocked by Watford Electronics, while the LF353 is available from Rapid Electronics. The two PCBs can be obtained from our PCB Service, advertised on page 44.

## PARTS LIST

### Resistors (all 1/4 W, 5% except where stated)

R1,2	470R
R3,4,5	
28-37	15k
R6,25	4k7
R9	10k
R10,14,17, 21	100k
R11,15,18, 22,23	1k0
R12	100R 1%
R13	1M0 5% or better
R16	1k0 1%
R19	10k 1%
R20	100k 1%
R24,27	27k 2%
R26	1k8
R24,27	27k 2%

### Potentiometer

PR1	47k miniature horizontal preset
-----	---------------------------------

### Capacitors

C1	10p ceramic
C2	1n0 ceramic
C3-7	100n ceramic
C8	100u 10 V tantalum

### Semiconductors

IC1	74LS04
IC2,3	74LS90
IC4	78L05
IC5,8	4518B
IC6	4053B
IC7	4029B
IC9	4013B
IC10	4051B
IC11	4049B
IC12	4012B
IC13	4011B
IC14	4001B

IC15	LF353
IC16	ICM7224
Q1,7,8,9	BC182L
Q2-6	BC212L
Q3-7	BC212L
D1-6	1N4148
LED1-7	miniature green LEDs

### Miscellaneous

XTAL1	miniature 10 MHz crystal
SW1	DPDT toggle switch
SK1,2	press terminals (one red, one black)

PCBs (see Buylines); 3 1/2 digit LCD display; IC sockets; display socket (if required); PP9 battery and connectors; PP3 battery and connectors; mounting hardware; case (Vero 220 x 156 mm sloping front box, order no. 65-2523E).

# Greenbank

Greenbank Electronics  
(Dept T4E), 92 Chester Road, New Ferry  
Wirral, Merseyside L62 5AG  
(Tel. 051 645 3391)



TERMS, VAT, C.W.G. Cheques etc payable to Greenbank Electronics and crossed.  
Add VAT to all prices at 15% except where stated otherwise. Post etc: UK 40p  
(+6p VAT = 46p per order). Export: 80 VAT but add 40p (E.R.). E1 (Europe) and  
£3.50 elsewhere. Access. Barclaycard. Vis. telephoned orders for immediate  
dispatch on account.



## QUARTZ

32.768KHz Iwatch	£2.50
60 KHz	£1.35
100 KHz	£1.50
200 KHz	£1.70
204.8 KHz	£1.52
262.144 KHz	£1.52
307.2 KHz	£1.52
312.5 KHz	£1.52
455.0 KHz	£1.80
1.000 MHz	£2.50
1.008 MHz	£2.50
1.200 MHz	£1.52
1.5 MHz	£1.52
1.8432 MHz	£1.16
1.8 MHz	£1.52
2.000 MHz	£1.52
2.097152 MHz	£1.52
2.4576 MHz	£1.52
2.500 MHz	£1.52
2.56576 MHz	£1.52
3.000 MHz	£1.52
3.2768 MHz	£1.52
3.579545 MHz	£1.52
3.93716 MHz	£1.52
4.000 MHz	£1.52
4.032 MHz	£1.52
4.096 MHz	£1.52
4.194304 MHz	£1.52
4.433616 MHz	£1.52
4.500 MHz	£1.52
4.800 MHz	£1.52
4.9152 MHz	£1.52
5.000 MHz	£1.52
5.008 MHz	£1.52
5.625 MHz	£1.52
5.760 MHz	£1.52
6.000 MHz	£1.52
6.144 MHz	£1.52
6.250 MHz	£1.52
6.55360 MHz	£1.52
7.000 MHz	£1.52
7.168 MHz	£1.52
7.680 MHz	£1.52
7.86432 MHz	£1.52
8.000 MHz	£1.52
8.08333 MHz	£1.52
8.38968 MHz	£1.52
8.867237 MHz	£1.52
9.375 MHz	£1.52
10.000 MHz	£1.52
10.245 MHz	£1.52
10.700 MHz	£1.52
10.92 MHz	£1.52
11.000 MHz	£1.52
14.0 MHz	£1.52
14.31918 MHz	£1.52
16.000 MHz	£1.52
18.432 MHz	£1.52
19.968 MHz	£1.52
20.000 MHz	£1.52
20.134 MHz	£1.52
24.0 MHz	£1.52
26.690 MHz	£1.52
27.0 MHz	£1.52
27.145 MHz	£1.52
27.648 MHz	£1.52
38.566 MHz	£1.52
48.000 MHz	£1.52
100.000 MHz	£1.52
116.000 MHz	£1.52

## YEROCARD

0.1" Pitch with copper strips	£2.50
2 1/4" x 1 1/2" (up to 4) E1.01	75p
2 1/4" x 1 1/2" 80p	83p
2 1/4" x 1 1/2" £2.51	£2.51
3 1/4" x 1 1/2" £1.52	£1.52
3 1/4" x 1 1/2" 95p	95p
3 1/4" x 1 1/2" £3.26	£3.26
4 1/4" x 1 1/2" £4.28	£4.28
0.1" Flamboard (no strips)	£2.50
3 1/4" x 1 1/2" 52p	52p
3 1/4" x 1 1/2" 79p	79p
3 1/4" x 1 1/2" £2.11	£2.11
Termination post £1.50/500	£1.50
W.P. board £1.58	£1.58
W.P. board £1.58	£1.58
Spot laser cutter £1.82	£1.82
Pin insertion tool £1.82	£1.82

## EUROCARD Z80 COMPUTER BOARDS, CUSTOM 80 SYSTEM

The Custom 80 System has been designed as a fully expandable modular computer system. The circuits are supplied as a full kit of parts, all you need are tools and solder.

The colour VDU card gives a teletext format, 24 lines of 40 characters, upper case, lower case, pixel graphics, congruous, non congruous, single height, double height, memory mapped etc. The kit is supplied with all the components for colour and is used with your own colour or monochrome TV set.

The keyboard Port card is used to interface the ASCII keyboard to the computer. It is interrupt driven giving fast response to keystrokes. On this card is included 1K of user RAM (this is in addition to the 1K of VDU test RAM) and space for a 2K EPROM such as the CSYS operating system. The ROM and RAM can be switched by software, which is desirable if full use is to be made of the dynamic RAM expansion cards.

The CPU board uses the high speed version of the Z80 microprocessor and operates at full 4MHz. Full use can be made of the Z80's powerful interrupt structures, including mode 2 (vectored) interrupts. The CPU can insert wait states when requested and utilises pulsed reset for full dynamic RAM.

For a full 64K system two RAM expansion cards are required. These may be purchased singly if required. For example if 32K is sufficient for your initial needs.

The microcomputer cards plug into the Custom 80 Micro Bus circuit board which is mounted in the high quality Custom 80 rack, which is in turn fitted with a case conversion kit or a good looking instrument case.

For high speed machine code work the CSYS operating system has been designed to allow maximum use to be made by the user's own programs, of the various subroutines and utilities contained in the firmware.

Programs can be stored using framed files on cassette. The dual cassette interface includes facilities for an RS232 or 20 mA. current loop to drive a printer. The band rate is software selectable between 300 and 2400 baud. The card also has a Z80A counter timer circuit.

For users who would prefer to write programs in BASIC there is a 4K integer BASIC supplied on cassette tape. It includes commands for setting colour, black and white, graphics etc. PLDT (to point), draw (to line), erase (to line) etc. A 12K Custom 80 BASIC is in development and this will be produced in both interpreting and compiling versions.

Also in development is an interface to floppy disks (and disk operating systems). If you are working on a tight budget, the various kits of parts can be purchased one at a time. Prices range from £34.08 for the Micro Bus kit with 5 connectors or £43.22 for the CPU kit up to £74.56 for the colour VDU kit.

Send for more details (a large SAE is not essential but helps us) and a comprehensive Custom 80 price list.

**NEW RELEASE**

We are now able to sell the bare PCB's without the components but including full documentation. Custom 80 CPU £18.83, Custom 80 KBP £19.39, Custom 80 Micro Bus £13.87, Custom 80 32K RAM £21.25, Custom 80 VDU £23.70. Ask us for details of Bare Boards for Custom 80 System.

## CMOS

4000 14p	4042 60p	4083 43p	4409 £7.90	4531 £1.30
4001 14p	4043 70p	4094 £1.88	4410 £7.20	4532 £1.10
4002 66p	4044 86p	4095 90p	4411 £5.86	4534 £5.00
4006 66p	4045 £1.70	4098 90p	4412VP £8.00	4536 £2.96
4007 18p	4046 75p	4097 £3.20	4415V £4.80	4537L £28.10
4008 82p	4047 75p	4098 88p	4422 £6.56	4538 £1.16
4009 35p	4048 55p	4099 95p	4433 £7.70	4539 £1.15
4010 40p	4049 60p	4100 £1.32	4435V £5.40	4541 £1.19
4011 15p	4050 30p	4101 £1.30	4450 £3.50	4543 £1.36
4012 16p	4051 78p	4102 £1.80	4461 £3.93	4549 £3.96
4013 34p	4052 78p	4103 £1.76	4462 £4.81	4552 £1.86
4014 55p	4053 78p	4104 95p	4480P £3.50	4553 £2.99
4015 68p	4054 £1.28	4105 £1.16	4490P £3.14	4554 £3.38
4016 32p	4055 75p	4106 75p	4501 25p	4555 50p
4017 48p	4056 £1.20	4107 60p	4502 £1.20	4556 55p
4018 68p	4059 £4.80	4108 £4.50	4503 70p	4557 £3.20
4019 42p	4060 90p	4109 £1.00	4506 £5.71	4558 £1.32
4020 61p	4062 £3.95	4110 £3.00	4508 50p	4559 £3.96
4021 95p	4063 99p	4111 £1.77	4507 £1.98	4560 £1.80
4022 62p	4064 25p	4112 £1.41	4516 75p	4561 81p
4023 20p	4067 £1.25	4113 £1.54	4518 £4.16	4562 £4.95
4024 45p	4068 22p	4114 £1.54	4519 £4.16	4563 £4.95
4025 19p	4069 20p	4115 £1.54	4512 75p	4568 £2.38
4026 £1.30	4070 26p	4116 £1.54	4513 £1.99	4569 £6.39
4027 38p	4071 20p	4117 £1.03	4514 £1.99	4570 38p
4028 59p	4072 20p	4118 £1.03	4515 £1.99	4571 38p
4029 77p	4073 20p	4119 £1.03	4516 75p	4581 £2.50
4030 50p	4075 20p	4192 £2.41	4517 £4.16	4582 99p
4031 £1.70	4076 60p	4193 £2.41	4518 £4.16	4583 99p
4032 £1.26	4077 26p	4208 £7.54	4519 29p	4584 48p
4033 £1.66	4078 26p	4209 £7.54	4520 78p	4587 £2.44
4034 £1.96	4081 26p	4180 85p	4521 £2.00	4590 £1.96
4035 95p	4086 65p	4181 95p	4522 £1.11	4599 £5.96
4037 £1.16	4085 65p	4182 99p	4526 95p	4700 £1.75
4038 £1.10	4086 65p	4183 99p	4527 £1.16	ICM7038A
4039 £2.79	4087 60p	4174 99p	4528 80p	£4.25
4040 59p	4088 11p	4175 01p	4529 £1.30	
4041 78p		4194 £1.06	4530 70p	


## 74C

74C00 28p	74C02 28p	74C04 28p	74C08 28p	74C10 28p	74C12 30p	74C14 30p	74C16 30p	74C18 30p	74C20 28p	74C22 28p	74C24 28p	74C26 28p	74C28 28p	74C30 28p	74C32 28p	74C34 28p	74C36 28p	74C38 28p	74C40 28p	74C42 28p	74C44 28p	74C46 28p	74C48 28p	74C50 28p	74C52 28p	74C54 28p	74C56 28p	74C58 28p	74C60 28p	74C62 28p	74C64 28p	74C66 28p	74C68 28p	74C70 28p	74C72 28p	74C74 28p	74C76 57p	74C78 57p	74C80 57p	74C498 57p	74C500 57p
-----------	-----------	-----------	-----------	------------	------------	------------	------------	------------

## 74LS

74LS00 28p	74LS02 28p	74LS04 28p	74LS08 28p	74LS10 28p	74LS12 30p	74LS14 30p	74LS16 30p	74LS18 30p	74LS20 28p	74LS22 28p	74LS24 28p	74LS26 28p	74LS28 28p	74LS30 28p	74LS32 28p	74LS34 28p	74LS36 28p	74LS38 28p	74LS40 28p	74LS42 28p	74LS44 28p	74LS46 28p	74LS48 28p	74LS50 28p	74LS52 28p	74LS54 28p	74LS56 28p	74LS58 28p	74LS60 28p	74LS62 28p	74LS64 28p	74LS66 28p	74LS68 28p	74LS70 28p	74LS72 28p	74LS74 28p	74LS76 28p	74LS78 28p	74LS80 28p	74LS82 28p	74LS84 28p	74LS86 28p	74LS88 28p	74LS90 28p	74LS92 28p	74LS94 28p	74LS96 28p	74LS98 28p	74LS100 28p	74LS102 28p	74LS104 28p	74LS106 28p	74LS108 28p	74LS110 28p	74LS112 28p	74LS114 28p	74LS116 28p	74LS118 28p	74LS120 28p	74LS122 28p
------------	------------	------------	------------	-------------	-------------	-------------	-------------	-------------	-------------	-------------	-------------	-------------	-------------	-------------	-------------

# WIN £50's WORTH OF VEROBOXES!

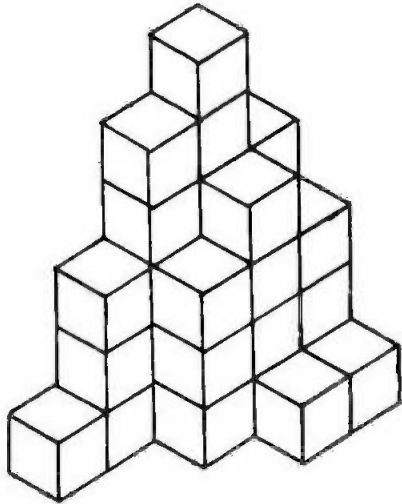

There's no doubt that no matter how clever the project you've built is, your friends and family are not going to be impressed with it if you display it in a cardboard box or the proverbial tobacco tins. What's more, the feeling of satisfaction you get from project-building can be that much greater if you end up with something that looks as good as commercial equipment.

One of the companies with the largest range of cases is Vero Industries. They've given us a collection of their cases worth £50, and we're going to give them to one of you — but the lucky recipient has to have

answered these three questions correctly.

(1) How many boxes in the pile on the left? (There are no concealed box tops).

(2) How many of this month's projects are housed in Veroboxes?

(3) Is the Vero 'G' range of cases made from plastic or metal?

Answers on the form on page 133 please, together with your name and address, to reach us before April 30th, 1982.

### RULES

1. Closing date is April 30th 1982, and all entries post-marked later than this date will be discounted.
2. The coupon provided in the magazine must be used. Photocopies are NOT acceptable.
3. Employees of ASP and their relatives are not eligible for entry.
4. The judges' decision is to be considered final and no correspondence will be entered into concerning the competition.

<p>TTL CMOS 74LS LEDES</p> <h2>LB ELECTRONICS</h2> <p>LINEAR RAMS EPROMS SURPLUS TELEPHONE UXBRIDGE 55399</p>																										
<p><b>D TYPE CONNECTORS</b></p> <p>9 way r/angle skt £1.25                  9 way (solder) skt £0.75                  9 way (crimp) plg £0.75                  15 way (w/wrap) plg £1.00                  15 way (solder) plg £0.95                  15 way (solder) skt £0.95                  25 way (solder) plg £1.85                  25 way (solder) skt £1.85                  25 way (ins/peirce) plg £2.65                  25 way (ins/peirce) skt £2.65                  25 way (w/wrap) skt £2.00                  37 way (solder/tail) plg £1.80                  37 way (solder/tail) £1.80                  50 way (solder/tail) plg £2.00                  50 way (solder/tail) skt £2.00</p> <p><b>'D' TYPE COVERS</b></p> <p>Plastic 9 way £0.60                  Plastic 15 way £0.50                  Plastic 25 way £0.95                  Plastic 37 way £1.00                  Plastic 50 way £1.20                  Metal 15 way £0.95                  Metal (ITT) 25 way £1.00                  Metal 25 way £1.25                  Metal (ITT) 50 way £1.25                  Metal 50 way £1.85</p> <p>P/P on all above items 45p</p> <p><b>SUPERSAVER 30</b>                  PAPTST Mofinan 3/4" sq. 1 1/2" deep 220V. 50 HZ. Brand new and boxed £9.50 P/P 50p</p> <p><b>SUPERSAVER 31</b>                  UECL Gold plated Edge connector. 1" 75 way £1.65 PP 45p (wire wrap)</p> <p><b>SUPERSAVER 32</b>                  12 Volt Relay. P.C.B. Mntg S/pole d/CHANGE over £0.65 P/P 25p</p>	<p><b>SUPERSAVER 33</b>                  JECKERSON NICAD £8.75                  Batt charger for 4 x AA, D, D. Same as above plus P.P.3. £10.00 P/P £1.00 each</p> <p><b>SUPERSAVER 34</b>                  ANTEX 15 watt solder iron £4.95 P/P 75p</p> <p><b>SUPERSAVER 35</b>                  A Treat '82. 16 meters of 16 core cable with non-standard 'D' type plg/skt £1.50 P/P £1.00</p> <p><b>SUPERSAVER 36</b>                  Mains lead 2 meters + with moulded I.E.C. mains plug 6A 250V £1.00 each P/P 50p</p> <p><b>SUPERSAVER 37</b>                  MEKTRON M-823793 16 way buss rail. 4 for £1.00 P/P 35p</p> <p><b>SUPERSAVER 38</b>                  T&amp;B Ansley I.D.C. Connectors                  26 way straight plug 65p                  40 way straight plug 90p                  40 way R/A plug £1.00                  16 way skt 55p P/P 25 each</p> <p><b>SUPERSAVER 39</b>                  MOLEX 6W skt. 1" will butt end to end still giving .1" PCB mounting. 4 for 12p; 12W plg 12p each.                  16W plg &amp; skt 45p for pair.                  2W plg &amp; skt 25p for pair.                  3V plg &amp; skt (mains) 45p for pair. P/P 25p.</p>	<p><b>SUPERSAVER 40</b>                  .1" 30 x 30 Gold plated P.C.B. plug. £1.00 each.                  .1" 20 way PCB skt 20p each.                  36W plg .1" R/A 50p each. P/P 25p each.</p> <p><b>SUPERSAVER 41</b>                  AUGAT IC skts (The best available) round turned pins. The I.C. pin cuts a groove in the skt for 100% connection reliability. 16 way 20p; 18 way 25p; 24 way 50p each. P/P 25p.</p> <p><b>SUPERSAVER 42</b>                  Header plgs (gold plated)                  14 way (no CVR) 18p each                  16 way (no CVR) 25p each                  24 way (no CVR) 95p each                  14 way HDR plgs with CVR 45p each                  16 way HDR plgs with CVR 60p each                  Ansley 14 way HDR plgs RBN I/P 75p                  Ansley 16 way HDR plgs RBN I/P 95p                  Ansley 24 way HDR plgs RBN I/P £1.50 P/P 15p each</p>	<p><b>SUPERSAVER 43</b>                  2516 used fully erased guaranteed replacement single rail EPROM 350ns £1.95 each; Ten for £17.00 P/P FREE</p> <p><b>SUPERSAVER 44</b>                  Tangerine Microtan 65 blank P.C.B. Brand new + circ. diagram £4.50 (6502 based, IK on board) P/P 50p each.</p> <p><b>MICRO REVOLUTION</b>                  The new Z8 Processor complete P.C.B. and parts to produce this new R.S. 232 CPU. Built in tiny BASIC and 4K RAM only 4.5" by 4.5". Price on application. Further details to follow.</p> <p><b>SUPERSAVER 45</b>                  M.C. 1489 RS 232 Receiver I.C. 46p each P/P 20p</p> <p><b>SUPERSAVER 46</b></p> <table border="0"> <tr><td>2708</td><td>£1.85 ea.</td></tr> <tr><td>1702</td><td>£5.00 ea.</td></tr> <tr><td>2732</td><td>£5.50 ea.</td></tr> <tr><td>2532</td><td>£6.50 ea.</td></tr> <tr><td>2114 (450ns)</td><td>£1.00 ea.</td></tr> <tr><td>2114L (450ns)</td><td>£1.35 ea.</td></tr> <tr><td>2114 (200ns)</td><td>£1.45 ea.</td></tr> <tr><td>4116 (200ns)</td><td>£1.00 ea.</td></tr> </table> <p>Quantity on above P.O.A. P/P FREE</p>	2708	£1.85 ea.	1702	£5.00 ea.	2732	£5.50 ea.	2532	£6.50 ea.	2114 (450ns)	£1.00 ea.	2114L (450ns)	£1.35 ea.	2114 (200ns)	£1.45 ea.	4116 (200ns)	£1.00 ea.	<p><b>SUPERSAVER 47</b>                  Approx. 2 meters + coax lead with plgs either end £1.00 each P/P 35p</p> <p><b>SUPERSAVER 48</b>                  FND 500 .5" LED displays. 7 seg. Red. 65p each. Large quantity P.O.A. P/P 35p</p> <p><b>SUPERSAVER 49</b>                  64 way DIN41612 edge connectors to fit Microtan etc. plg or skt £3.45 each P/P 35p each                  Amphenol 36 way plg &amp; skt (used) to fit all your printers £2.75 per pair P/P 35p</p> <p><b>SUPERSAVER 50</b>                  2.5mm Power plg + 2 metres of cable to fit Acom Atom ZX81 etc. etc. Only £1.00 for 10. P/P 25p.                  TRADE ENQUIRIES WELCOME</p> <p>POSTAGE STATED IS FOR ONE ITEM. IF YOU ORDER SEVERAL ITEMS, PLEASE USE YOUR OWN DISCRETION.</p> <p><b>SUPPORT DEVICES</b></p> <table border="0"> <tr><td>8251</td><td>£3.00 each</td></tr> <tr><td>8253</td><td>£6.00 each</td></tr> <tr><td>8224</td><td>£2.00 each</td></tr> </table> <p>P/P 35p</p>	8251	£3.00 each	8253	£6.00 each	8224	£2.00 each
2708	£1.85 ea.																									
1702	£5.00 ea.																									
2732	£5.50 ea.																									
2532	£6.50 ea.																									
2114 (450ns)	£1.00 ea.																									
2114L (450ns)	£1.35 ea.																									
2114 (200ns)	£1.45 ea.																									
4116 (200ns)	£1.00 ea.																									
8251	£3.00 each																									
8253	£6.00 each																									
8224	£2.00 each																									



**L.B. ELECTRONICS**  
 11 HERCIES ROAD, HILLINGDON, MIDDLESEX UB10 9LS  
 TEL: UXBRIDGE 55399



# CLEF ELECTRONIC MUSIC

## ELECTRONIC PIANOS

**SPECIALISTS SINCE 1972**

Clef Pianos adopt the most advanced form of Touch Sensitive action which simulates piano Key inertia using a patented electronic technique.

### 7 1/2 OCTAVE DOMESTIC MODEL COMPONENT KIT £244 COMPLETE KIT £395.70 MANUFACTURED £675

Two Domestic Models are available including the 88 note full-size version. Four interchangeable Voice Controls may be used to obtain a wide variation of Piano tone, including Harpsichord. Both Soft and Sustain Pedals are incorporated in the Design and internal Effects are provided in the form of Tremolo, Honky-Chorus, and Phase/Flanger. A power amplifier integrates into the Piano top which may be removed from the Back for easy transportation.

### SIX OCTAVE DOMESTIC MODEL COMPONENT KIT £217 MANUFACTURED £395

Component Kits include Keyboard, Key-switch hardware, and all electronic components and may be purchased in four stages at no extra cost. Complete Kits further contain Cabinets, wiring harness, Pedals and in the case of Domestic Models both Power Amplifier and Speaker. The Six Octave Stage Piano has the same range of Voices and Effects and is designed for use with an External Amplifier and Speaker.

### SIX OCTAVE STAGE MODEL COMPONENT KIT £217 MANUFACTURED £330

Since 1972 Clef Products have consistently produced leading designs in the field of Electronic Musical Instruments, many of which have been published in technical magazines. With musical quality of paramount importance, new techniques have been evolved and the latest musically valid technology has been incorporated into projects which have been successfully completed by constructors over a wide range of technical capability. Back up TELEPHONE advice to our customers is available from the Designer of all Kits advertised.

### STRING ENSEMBLE

(As Published in conjunction with "Practical Electronics")  
A very popular Keyboard Synthesizer Kit, for Group or Home use, with a four octave compass and spin Keyboard facility.

The instrument is fully polyphonic and has two rich Multi-String Voices plus woodwind and Brass Effects for individual or Mixed use. Variable Attack and Sustain Controls give a good Orchestral Mix with the added concert hall reverberation effect produced by sustain coupled with phase modulation in the Chorus Unit. The Component Kit includes Keyboard, Key switch hardware, and all electronic components plus tone generator linking wire and Volume Pedal. A copy of the P.E. project series can be supplied for £3.00 inc. post.

COMPONENT KIT £178.00

### ROTOR-CHORUS

Comprehensive two speed organ rotor simulator plus a three phase chorus generator on a single 8" x 5" pcb. The kit includes all components for mains operation and a stereo headphone driver pcb. Easily integrated with existing organ/amplifier system.

COMPONENT KIT £98.00

### KEYBOARDS

Our Square Front Keyboards are chosen for their superior feel to the discerning musician whilst giving adequate physical strength for the high impact playing present in the Piano application.

88 NOTE (A-C) £57.00  
73 NOTE (F-F) £47.00  
FIVE OCTAVE £38.00  
FOUR OCTAVE £28.75

### EXPERIMENTERS

A number of our Sub-Kits are of interest to Electronic Music and COMPUTER Experimenters. These include the 8502 based MICRO CONTROLLER and Music system kit used in the BAND-BOX; plus a 49 note four pitch diode Keyboard system. See our lists for Sub Kit prices.

PRICES INCLUDE VAT, UK CARRIAGE & INSURANCE (CARRIAGE EXTRA ON MFD PIANOS). Please send S.A.E. for our complete lists, or use our telephone VSA/ACCESS Service. Competitive quotations can be given for EXPORT orders - in Australia please contact JAYCAR in Sydney.

## CLEF PRODUCTS (ELECTRONICS) LIMITED

(Dept. ET1144A Bramhall Lane South, Bramhall Stockport, Cheshire SK7 1AH 061 438 3297)

## "THE COMPUTER BAND-BOX" CURRENTLY IN "PRACTICAL ELECTRONICS"

COMPLETE KIT £289

£399 MANFD.



PRICES INCLUDE MASTER RHYTHM

A revolution in the field of Computer Music Generation!

A MUSICIANS INSTRUMENT FOR SOLOISTS - SINGERS - RECORDING - PRACTICE LIVE PERFORMANCE - COMPOSITION

The BAND BOX provides an Electronic Backing Trio consisting of Drums, Bass, and a Chord Instrument (one of 16 Waveform/Envelope combinations), with the capacity to store over 1000 User Programmable Chord Changes on more than 120 different Chords. Using advanced Microprocessor technology, Playback of 50 100 Scores can be executed in any Key and at chosen Tempo. Complete Music Pad is electronically indexed and stored on secondary battery back up. Facility exists for composition of Intro, Repeat Chorus, and Coda sections including Multiple Score Sequences. Sockets are provided for Volume Pedal and Footswitch plus separate and mixed instrument Outputs. Total size 19" x 11" x 4 1/2" incorporating Master Rhythm.

## THE PROGRAMMABLE DRUM MACHINE

(As Published in conjunction with "Practical Electronics")

EIGHT TRACK PROGRAMMING/TWENTY-FOUR PATTERNS/TWELVE INSTRUMENTS SEQUENCE OPERATION COMPLETE KIT £78.00 MANFD £118.00



The Clef Master Rhythm is capable of storing 24 selectable rhythmic drum patterns, invented, modified, and entered by the Operator on to Eight Instrumentation tracks. A three position Instrumentation control expands the number of instruments available to twelve; grouped into sounds typical of playing with Drumsticks, Brushes, or Latin American Bongos and Claves.

Sequence operation allows two rhythm sections to be coupled with the second (B) section appearing at four, eight or sixteen Bar repetition. All drums can be adjusted for level and resonance on internal controls to suit individual taste, thus producing good musical sounds in a battery driven unit 8 1/2" x 5" x 2 1/2".



COMPLETE KIT £395.70



COMPLETE KIT £245

### POWER DIMMING MODULES

- Fully isolated
- Multi channel common wiring lines
- Master dimming over banks
- Remote override
- Dead "kill" and "all on"
- Low voltage feed lines
- Common neutral or live outputs

Power Dimming Modules  
A range of isolated digitally controlled dimming modules, complete with panels. Each type requires connection to the supply/reference board.

Slave power controllers (SPC)  
Controls up to 1000W via the slider.  
RFI suppressed/fused  
Slave power unit (BPU)  
Controls up to 1000W via a logic signal from a remote slave.  
Master controllers (MC)  
Will master dim from 1 to a bank of 20 SPC units.  
Remote slaves (RS) - (Praset)  
Will override an SPC at a remote location to the main system or control an SPU.  
Supply/reference board  
Provides the necessary supply voltages and signals to all units. Facilities for "Kill" and "all on" Supplies up to any combination of 50 modules.

PRICES (1 of):  
SPC ..... £13.90  
BPU ..... £9.90  
MC ..... £7.20  
RS ..... £8.50  
Supply ..... £18.20

SPECIAL DISCOUNTS  
Are available on power dimmers.  
Total your order up and deduct:  
£100 to £199 ..... 20%  
£200 to £299 ..... 25%  
£300 to £399 ..... 30%  
£400 + ..... 40%

### 3 CHANNEL SOUND/LIGHT CHASER

LB31000SLC £35.70

A high performance sound to light system which automatically switches to a chase when the music ceases. Super sensitive with an anti-interference circuit, the unit will operate from practically any amp and control up to 1,000W/channel, 5Hz to 70K. Controls: bass/mid/treble/master sensitivity/chase speed.

### STEREO DISCO MIXER/PREAMP

LBPA3 M Magnetic C - Ceramic £33.70

All the requirements of a stereo disco preamp on one board, left and right deck mixers/level controls/misc mixer/tonic/mic auto fade over decks/and P.F.L. The unit can be used with either LB100/150/250

### NEW NEW NEW 4 CHANNEL SOUND LIGHT AUTO-CHASER

- Bass/mid/presence/treb
- Automatic level filter control
- Automatic input gain control
- L.E.D. monitor drivers
- 10Hz to 30KHz response
- Super sensitive
- Zero reference triggering
- Fascia/LED, etc. available

£49.90 (panels, etc. £9.20)

Phone or write for immediate details of the LB41000SLC

### PROGRAMMABLE - 8

£114.90

P/P INS £1.50

Complete with blue panel/white letters

- 8 channel 400W each
- 16, 32, 64, 128 patterns
- Automatic program recycle
- Adjustable cycle on/off speed
- Optically isolated, suppressed
- Either common Neutral or live lamps

An advanced lighting module allowing any chase or sequence effects to be programmed, stored and recalled. Up to 128 patterns can then be replayed in the stored order, with control over the cycle on and off time. At the end of the program the system re-cycles to the start to maintain a continuous display. Full monitoring on the control panel over the outputs and control status is provided, and the program may be halted at any time. Although removing the mains supply to the module will delete the stored patterns the use of calculator type push buttons allows speedy programming ready for the following night's performance. The module obviously provides unlimited effects and is a must for all serious lighting shows.

### MULTI - 4

£48.90

Attractive blue panels with white letters, complete with LED monitors, knobs and means illuminated switch.

extra £9.70

### NEW NEW NEW 2/4/8 CHANNEL CHASER

LB81000LC

£28.00

An all logic chaser system for use with up to 8 channels at 1,000Watts each. Facilities include footswitch trigger and module cascading (16, 24, 32 channel, etc.), chase speed and re-cycle delay.

### 3 CHANNEL SOUND/LIGHT

LB31000SL £22.70

All the advantages of the SLC without chase. Controls: bass/mid/treble/master sensitivity.

### 3-WAY ACTIVE CROSSOVER

LBACO1 £17.90

Bass/mid/treble active crossover with stage booster! Available with crossover points of 200 or 300Hz, and 2K or 3KHz (please specify) LBPSU1 supply for LBACO1 (1 or 2).

### NEW NEW NEW 4 CHANNEL SEQUENCER

LB41000LS

£19.20

A 4 channel sequence generator for banks of lamps up to 1,000W per channel. Two speed controls, cross effect to provide settings between seconds and rapid burst.

## L & B ELECTRONIC MODULES

PROFESSIONAL ENGINEERING BY PROFESSIONALS

45 Wortley Road, West Croydon Surrey CR0 3EB. Tel. 01-689 4138



# TECH TIPS

## Frequency-To-Phase Controlled Power Supply

Dilbay Singh (B.Tech), Crawley

The circuit shown in the diagram was initially designed to obtain a phase-controlled power supply to use with a ¼ horsepower stepping motor. The phase angle can be varied over the complete


cycle period and is dependent on the frequency of the input. Clearly the circuit can be used to control resistive loads such as lamps or motors.

The first stage of the circuit consists of a frequency-to-voltage converter. C1, R1, and Q1 effectively differentiate and amplify the input signal waveform to provide triggering pulses for the 555 timer, which is used in the monostable mode. The output of the monostable is used to charge C3 by a constant amount of charge every time a pulse is received

at the base of Q2. The voltage across C3 acts as an input to the common collector stage formed by Q3. The voltage across C3 is DC-shifted by means of the zener diode ZD2 to a suitable value, providing the input to the trigger IC (the Mullard TCA280A). The TCA280A provides the phase control signal for the gate of the thyristor.

A triac may be used in place of the thyristor, if phase-controlled AC is required.

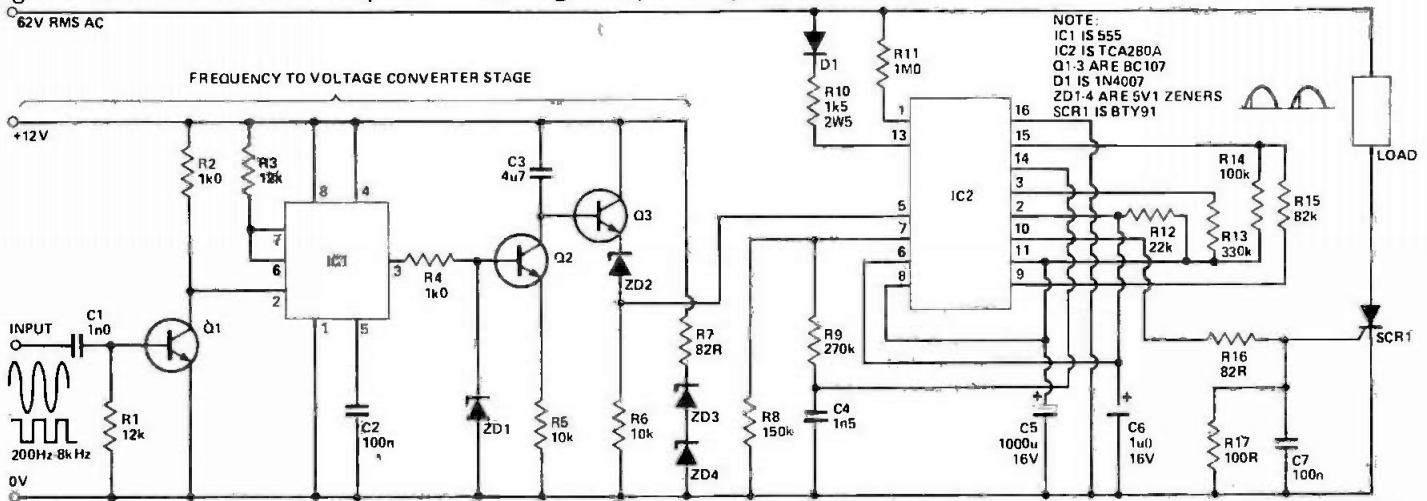
The component values shown are suitable for providing phase control using frequencies in the range 200 Hz-8 kHz on the control input. The firing angle can be varied from 0° at 8 kHz to 170° at 200 Hz.


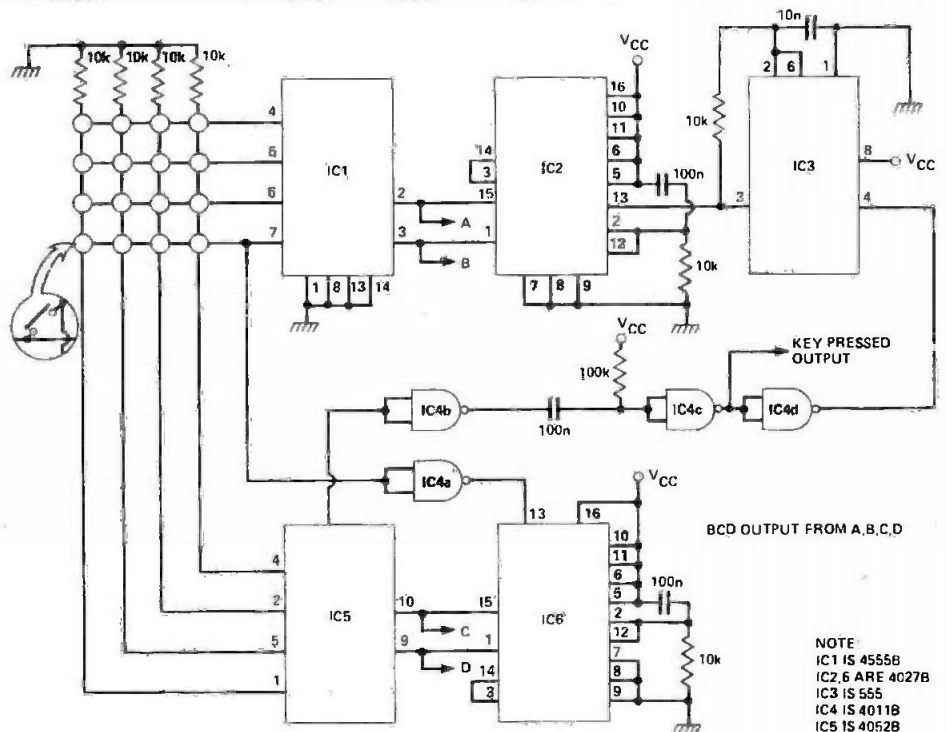
## Fully Debounced Keyboard

Graham Kyte, Bexleyheath

This circuit produces a debounced output whenever a key is pressed. Each matrix point is scanned in turn and the output of the 4052 data distributor goes high when a pressed key is detected. This stops the scanning oscillator (555) for about 10ms and a 'key pressed' output is produced, thus enabling the BCD output to be stored in a latch or otherwise made use of. The use of CMOS ICs enables current consumption to be minimised, making the circuit suitable for operation in a car. The circuit is easily modified for a larger number of keys by using an eight-way data distributor (with relevant counter made from three J-K flip-flops rather than the two as used here).



ETI is pleased to accept articles for consideration for this page. All items used will be paid for if a suitable article is published. The author's name and address should be typed. Text and drawings must be in black ink. The author's name and address should be typed. Text and drawings must be in black ink. The author's name and address should be typed. Text and drawings must be in black ink. 145 Charing Cross Road, London WC2H 9SL

# Remote Camera Release


Geoffrey Ammon, Welling

When taking photographs from a distance, a pneumatic remote release is normally used. These will only work over a limited distance and it is not always possible to tell if the camera has operated. This simple circuit uses a low current trigger circuit to operate the camera and provides a visible indication that the camera or flashgun has worked correctly.

The circuit operation is as follows. When the remote release push-button PB1 is operated, a current flows via the extension lead, which may be a 100 metres or more in length, to switch transistors Q3 and Q4. This combination provides the load current of up to 2 A for the camera release solenoid. When the flashgun fires, light falling on the CdS cell

causes a current pulse to appear at the base of Q1. When Q1 switches on it will discharge C2, extending the pulse duration to about one second. While C2 is charging Q2 will be turned on, causing a large enough current to flow in the extension lead to operate LED1. If a flashgun is

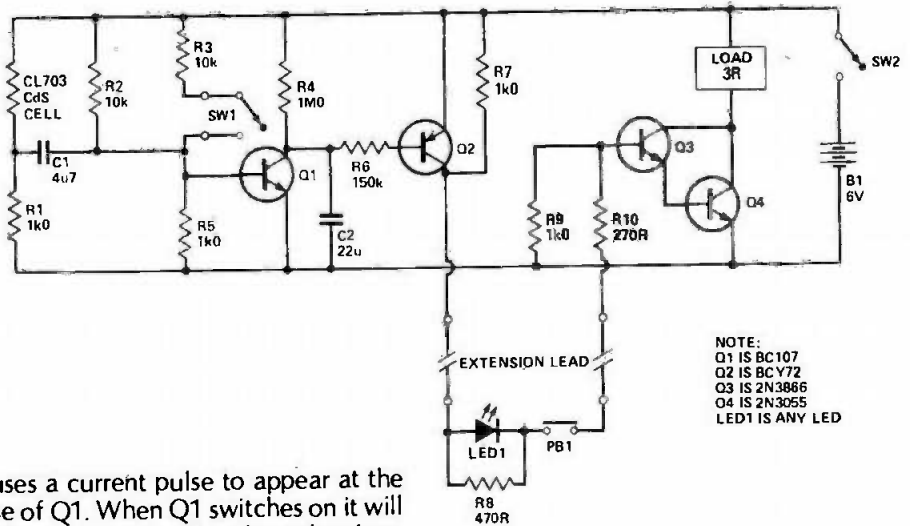not used, the camera flash contacts (SW1) may be connected to bypass the CdS cell and remotely operate the indicator LED1.



NOTE:  
Q1 IS BC107  
Q2 IS BCY72  
Q3 IS 2N3866  
Q4 IS 2N3055  
LED1 IS ANY LED


# Room Thermometer

J. P. Macaulay, Crawley

With the advent of the LM3911 temperature controller IC the task of measuring temperature has become simple in the extreme. The internal circuitry of this device comprises a temperature sensing element, an op-amp and a stable reference voltage. The device gives, in its simplest form, a stable 10 mV change in output for every 1° change in temperature over the range -25 to 85°C. For the application of room thermometer it is only necessary to utilise part of this range from, say, 0° - 50°C. The circuit to be described measures this range.

The figure shows the complete circuit of the thermometer. The meter, a 500 uA FSD type, is connected between the output and inverting input of the internal op-amp. Resistor R1 connects the inverting input to the output of the 741 op-amp. This is used with 100% AC and DC feedback to form a unity gain voltage follower with a current output capacity of several milliamps. The input of the 741 is connected to the slider of PR1 which in turn is connected across the stable supply voltage produced by the IC. D1 and D2 protect the meter from overrange temperatures and thus protect its delicate movement from harm.

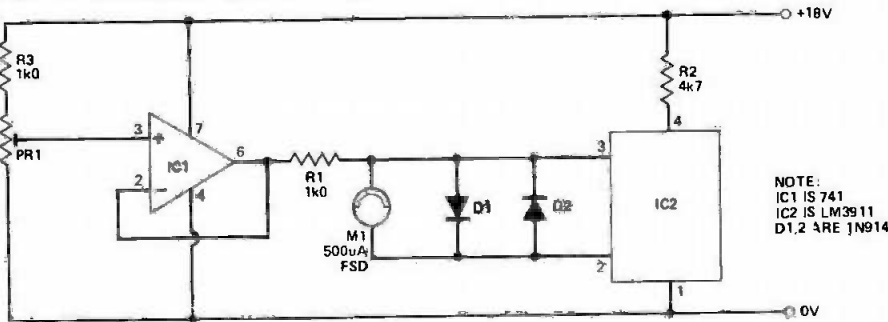Once completed, a calibration can be made with a room thermometer of known accuracy. Simply leave the equipment in the room for 10 minutes or so for its own temperature to stabilise and then adjust PR1 until both thermometers read the same; the calibration is now complete.




NOTE:  
IC1 IS 741  
IC2 IS LM3911  
D1,2 ARE 1N914

# Cheap PET Cassette

D.J. Cocker, Portsmouth

In view of the price of the Commodore cassette unit, the following adaptation may be of interest. I have been using this arrangement for some time and have experienced very few problems. In order to signal the PET when the PLAY key has been pressed, a switch must be incorporated into the cassette key assembly—a small microswitch is ideal. This is an improvement on the Commodore unit,

in which any key activates the switch, leading to confusion and ambiguity. The 'signal present' LED is very useful in locating the start and end of the data tape. The cassette recorder is supplied with power from the PET, batteries only being required for fast forward and rewind functions—a switch should be fitted to facilitate this. When the PLAY key is depressed, the PET has control of the tape motor. It may be found necessary to disable any tone control circuitry or AGC which may be fitted in the cassette recorder. Any suitable TTL Schmitt gate may be used as IC1.

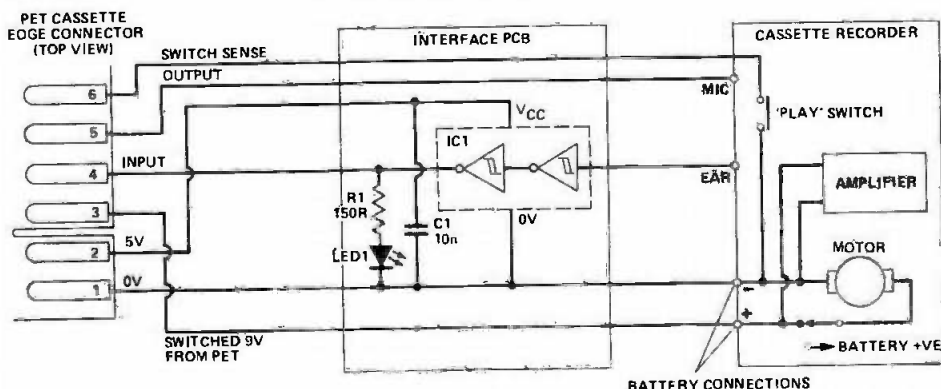


## Enlarger Timer

C. E. Basson, South Africa

The circuit of the enlarger timer can time periods from 0 to 99.9 seconds in 0.1 second steps. PR1, C1, R1, IC1a,b form an oscillator that feeds a 10 Hz signal to the first 4017 counter stage. Either the 'carry out' or '0' outputs of IC2 and IC3 can be used to feed the next stage, as the frequencies are the same and the positive-going edges of the pulses appear at the same time. Outputs '0' to '9' go high in sequence as the pulses are received at the 'clock in'. The desired time is selected by SW2, SW3 and SW4.

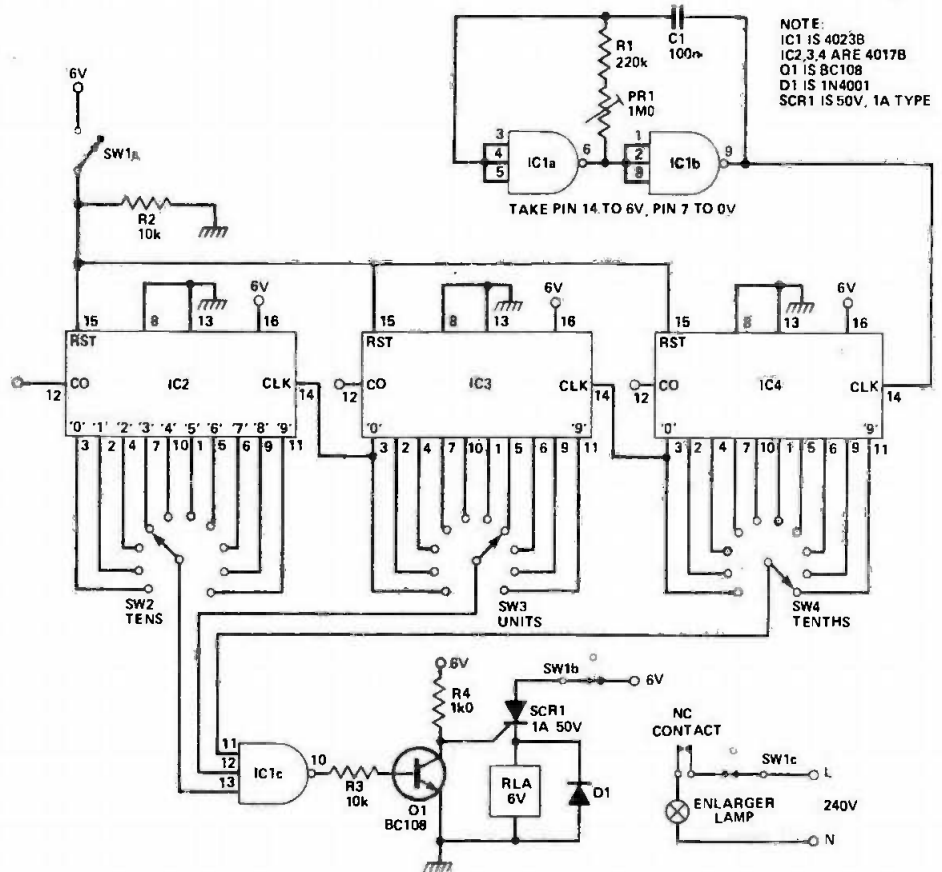Q1 is used as an inverter and with the NAND gate it performs the same function as an AND gate. As soon as the desired time is reached, all the inputs on the gate will be high and this will trigger SCR1. The relay will be turned on and switch off the enlarger lamp. The lamp will remain off until the circuit is reset.

The circuit can be reset by closing SW1a and opening SW1b and SW1c. SW1a will reset the 4017s and keep them in the reset condition. SW1b will remove the current from SCR1 to reset it. SW1c prevents the light from going on when in the reset condition. When SW1 is switched back to normal, the light will go on and remain on for the desired time.



## Comprehensive CMOS Logic Gate Test Rig

David Ian, Surrey


This simple test rig will check out all possible functions of any type of dual input CMOS logic gate allowing, for example, a faulty gate to be pinpointed so that the rest of the IC may still be used.

Each gate is provided with a green LED to indicate a high output and a red LED to show a low output.

Use a 14-pin holder for the IC and orientate the LEDs to relate to their appropriate gate.

SW1 connects power and a logic 1 to all inputs: press A to put a 0 onto one input of each gate; B puts 0 onto the other inputs; A and B together force all inputs low.

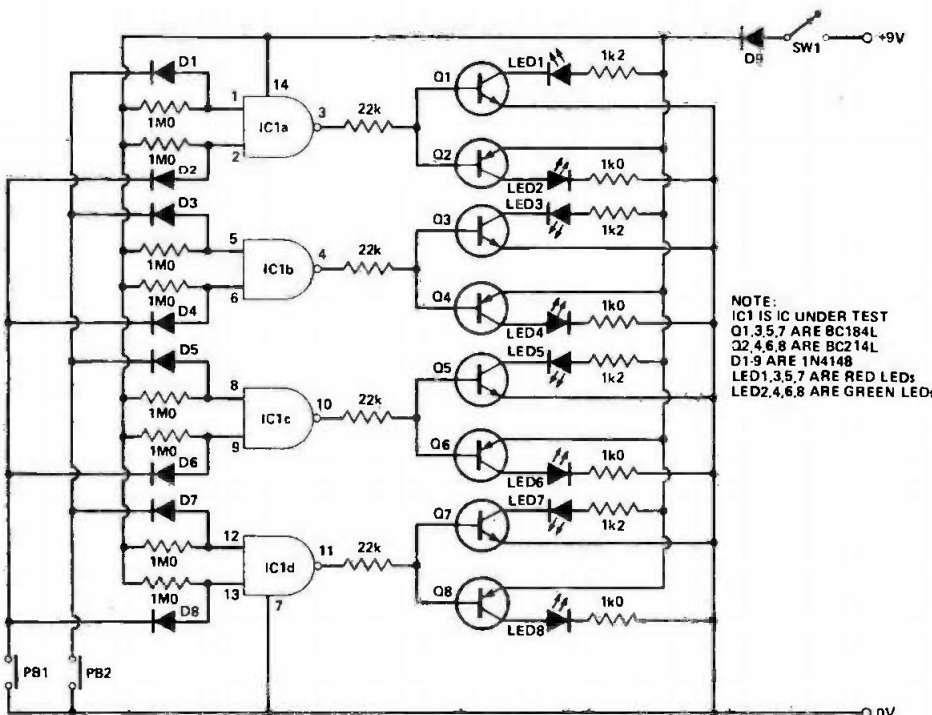A milliammeter in series with a 9 V supply should only indicate the current drawn by the LEDs, ie about 7 mA per LED. An appreciably higher reading indicates a completely faulty IC.



4011 (NAND)		
SW1	GREEN	RED
ON	OFF	ON
OFF	ON	OFF
PB1	ON	ON
PB2	OFF	OFF
BOTH	OFF	ON

4001 (NOR)		
SW1	GREEN	RED
ON	ON	OFF
PB1	ON	OFF
PB2	ON	OFF
BOTH	OFF	ON

4081 (AND)		
SW1	GREEN	RED
ON	ON	ON
PB1	ON	OFF
PB2	ON	OFF
BOTH	ON	OFF

4071 (OR)		
SW1	GREEN	RED
ON	OFF	ON
PB1	OFF	ON
PB2	OFF	ON
BOTH	ON	OFF

4070 (EXOR)		
SW1	GREEN	RED
ON	ON	OFF
PB1	OFF	ON
PB2	OFF	ON
BOTH	ON	OFF

4077 (EXNOR)		
SW1	GREEN	RED
ON	OFF	ON
PB1	ON	OFF
PB2	ON	OFF
BOTH	OFF	ON

SW1 ONLY - BOTH INPUTS HIGH  
 PB1 PRESSED - ONE INPUT LOW  
 PB2 PRESSED - OTHER INPUT LOW  
 BOTH PRESSED - BOTH INPUTS LOW

# NAMAL ASSOCIATES

No. 1 CLAYGATE ROAD, CAMBRIDGE CB1 4JZ  
Tel. 0223 248257 TLX 817445

## COMPUTERS

We stock computers and accept Sinclair ZX 81 in part exchange. Minimum of £20.00 is offered for your ZX81 in part exchange for a VIC 20 or Arcom colour Computers.

### NEW

#### Domestic cassette INTERFACE for VIC 20 ONLY £17.00

Simply connects your VIC 20 to any Cassette player. A bargain at half the usual price,

### NEW

#### VIC 20 Memory expansion Packs

3K RAM ..... £21.00  
8K RAM ..... £58.70

(Expandable to 16K)

16K RAM ..... £83.48

Simply plug into the existing expansion port of VIC 20.

Battery Ram backup available. Price on application.

#### WE GUARANTEE FACTORY PRIME PARTS

In depth stocks. Competitive prices. Government and colleges orders welcome. Please inquire for special prices for quantity orders. Please add P&P £1 & VAT. Minimum Order £10. Access orders welcome.

#### Computer I.C.s

2144-200	.99	27	.12	132	.44
2144-200LP	.99	28	.15	138	.33
2532	4.10	30	.12	145	.74
2716	1.95	32	.12	148	.95
2732	4.10	33	.16	151	.30
4116-150	.75	37	.15	153	.28
4116-200	.65	38	.15	154	.80
6116	4.75	40	.12	155	.38
5516	7.50	42	.33	156	.36
6800	2.75	47	.38	157	.30
6802	3.60	48	.59	161	.37
6809	8.75	49	.59	162	.40
6810	1.15	51	.14	163	.38
6821	1.15	54	.14	164	.46
6850	1.40	55	.12	165	.90
8085A	5.25	73	.21	173	.69
8224	1.85	74	.16	174	.46
8228	3.75	75	.24	175	.46
8255	3.30	76	.20	193	.45
Z80 CPU	3.25	78	.19	196	.57
Z & ACPU	3.60	83	.44	197	.60
Z80 P10	3.60	85	.60	240	.87
Z80 AP10	3.60	86	.15	241	.87
Z80 CTC	2.75	90	.30	242	.78
Z80 ACTC	3.25	91	.74	244	.60
		92	.33	245	.88
		93	.33	247	.60
		95	.42	248	.60
		109	.21	257	.43
		112	.21	259	.78
		113	.21	266	.22
		123	.43	273	.70
		124	.90	290	.55
		125	.24	373	.70
		126	.25	374	.72
				393	.60

#### Voltage Regu:

7805 5V +	.35
7812 12V +	.35
7815 15V +	.35
7905 5V +	.35
7912 12V	.35
7915 15V	.35
7924 24V	.35
LM323K	3.00

#### Crystals

100Hz	2.75
2.00MHz	2.65
3.276MHz	1.00
3.579MHz	1.00
3.932MHz	1.00
4.000MHz	1.58
4.194MHz	1.35
6.000MHz	1.00
6.144MHz	1.25
6.400MHz	1.50
10.000MHz	1.50

#### IC Sockets


8 PIN	.06
14 PIN	.09
16 PIN	.09
18 PIN	.13
20 PIN	.14
22 PIN	.17
24 PIN	.18
28 PIN	.25
40 PIN	.25

#### 74LS Series

00	.10	109	.21
0104	.12	112	.21
05	.14	113	.21
08-13	.12	123	.43
14	.38	124	.90
15-22	.12	125	.24
26	.16	126	.25
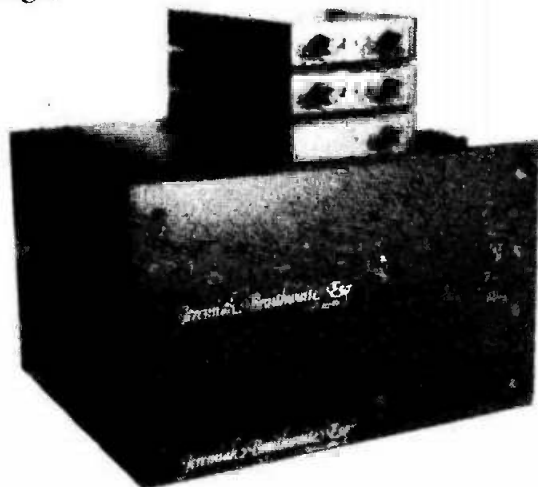
## The Finest Amplifiers deserve the Finest Kits

The Electronics Today System A, designed by Stan Curtis comprises two monophonic Class A Power Amplifiers and a modular pre-amplifier of such superlative performance that they stand comparison with commercial products in any price range.



## DRAMATIC PRICE REDUCTION!

Increased production has enabled us to slash the price of the complete system (two power amps; pre-amp & power-unit) by 30% to £386 incl VAT & carriage.

**YES a 30% Price Reduction!**  
But no reduction in performance.

Details and price list from:


**Braithwaite KITS**

215, High Street, Offord Cluny,  
Huntingdon, Cambs. (0480) 811659

# BIRTHDAY COMPETITION

PROGRAMMABLE CALCULATOR

CASIO

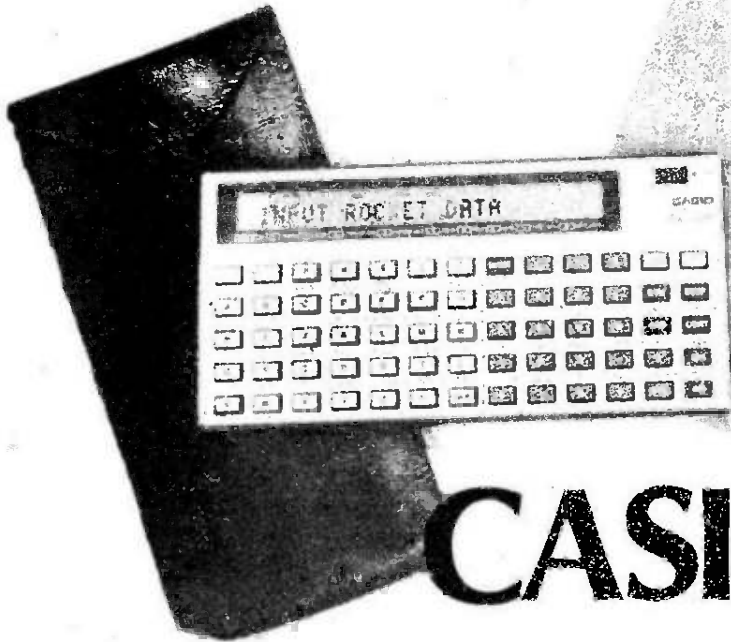

# WIN A CASIO FX-702P

That's right — in this competition we're offering you a chance to win the fabulous Casio FX-702P pocket BASIC computer, kindly donated for the occasion by Tempus. The features of this computer include:—

- A scrolling LCD alphanumeric dot matrix display
- A memory which can be varied between 1680 program steps and 26 memories to 86 program steps and 226 memories

- Auto power off

- All data and programs are retained in the memory when the computer is switched off

- Up to 10 different programs may be stored at once

- Subroutines may be nested to 10 levels

- FOR/NEXT loops may be nested to eight levels

- Full debugging and editing facilities

- 55 built-in functions (including regression and correlation), all of which may be used in programs

- Program or data storage on tape (using an FA-2 adaptor)

All this would normally cost you £134.95 (recommended retail price) but it can be yours — FREE — if you can answer one simple (!) question. Eyes right . . . . .

First, let  $A\$ = STR\$(\text{the product of } 7K \text{ (in decimal) and the standard audio bandwidth})$ . We'll use this later. Now, add the UK AC mains frequency to yellow/violet/red and divide by the number of our modular synth project. Divide the result into  $VAL(RIGHT\$(A\$,4)) - VAL(MID\$(A\$,5,3)) / LEN(A\$)$ . Add to this result the difference between our office street number and the TTL prefix. Multiply by the log (to base 10) of the sum of the digits of a CMOS quad EXNOR IC divided by the number of pins on a 555. Finally, add the decimal number represented in binary by 10111.

If you've managed all that (hint — people who know BASIC well have an advantage), write the answer on the entry form (page 133) with your name and address and send it to us by April 30th 1982. Answers to six decimal places, please.

## RULES

1. Closing date is April 30th 1982, and all entries post-marked later than this date will be discounted.
2. The coupon provided in the magazine must be used. Photocopies are NOT acceptable.
3. Employees of ASP and their relatives are not eligible for entry.
4. The judges' decision is to be considered final and no correspondence will be entered into concerning the competition.

# SOUND EFFECTS 2: STEAM TRAIN

Railway modellers looking for something special to improve their layout need look no further. Our second sound effect project simulates a steam train and whistle. Design by Phil Wait.

Ahhh, the nostalgia! If you're young at heart, old in years, or both, then this is for you — a steam train (chuff-chuff) and whistle. The *electronic* construction details are given on page 50 in the bomb drop project; but for that *authentic* touch, deft constructors can also fashion a cow-catcher out of tinned copper wire to attach to the unit!

The chuff-chuff runs continuously once power is applied and the whistle sounds when the push-button is pressed. The VCO is used to provide the whistle while the SLF modulates the noise generator/filter output to produce the steam train's chuff-chuff sound. The chuff-chuff rate may be varied by changing the values of R1 and C1, while the chuff-chuff sound may be varied by changing the values of R2 and C2. For a special effect, you can control the chuff-chuff rate manually by replacing R1 with a 1M $\Omega$  potentiometer.

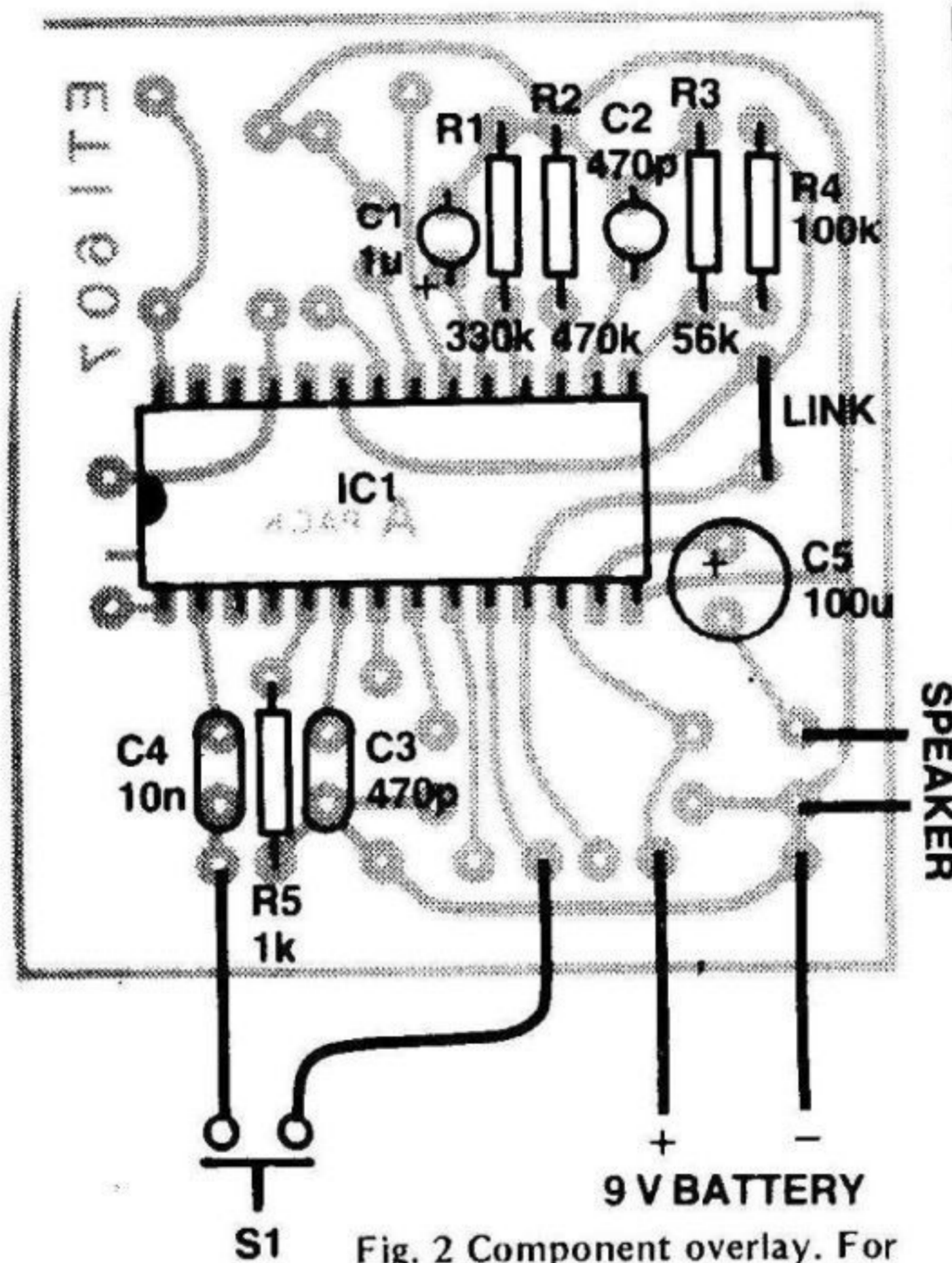


Fig. 2 Component overlay. For Buylines, see page 51.

## HOW IT WORKS

In this unit the Noise Generator/Filter is employed to produce the basic 'steam engine' sound, this being modulated by the SLF to produce the 'chuff-chuff' so characteristic of steam locomotives. The whistle is produced by the VCO, which is set to a particular non-varying pitch, and the output is switched into the audio input pin to produce the whistle.

The broadband noise from the Noise Generator is modified by the Noise Filter, the frequency characteristics being determined by R5 and C3 connected to the Noise Filter Control pins (5 and 6). The Noise Filter Output is fed via the Mixer and the Envelope Generator (which doesn't function here) to the audio output stages. The SLF square wave output effectively modulates the noise to produce a noise burst followed by a silent period, then another noise burst. Thus the chuff-chuff sound is produced. This sound is continuous whilst power is applied to the unit.

A resistive divider, R3/R4, provides about 1V8 at the VCO frequency to a convenient pitch within its range, providing a suitable pitch for the whistle. The VCO output is coupled to the audio input (pin 10) via C4 and the push-button, PB1. When PB1 is pressed, the whistle is heard over the chuff-chuff sound.

The SLF frequency is determined by C1 and R1, while the combination of R2/C2 and the voltage on pin 15 determines the VCO frequency. Output to the loudspeaker is coupled via C5, a 100 $\mu$ F electrolytic capacitor.

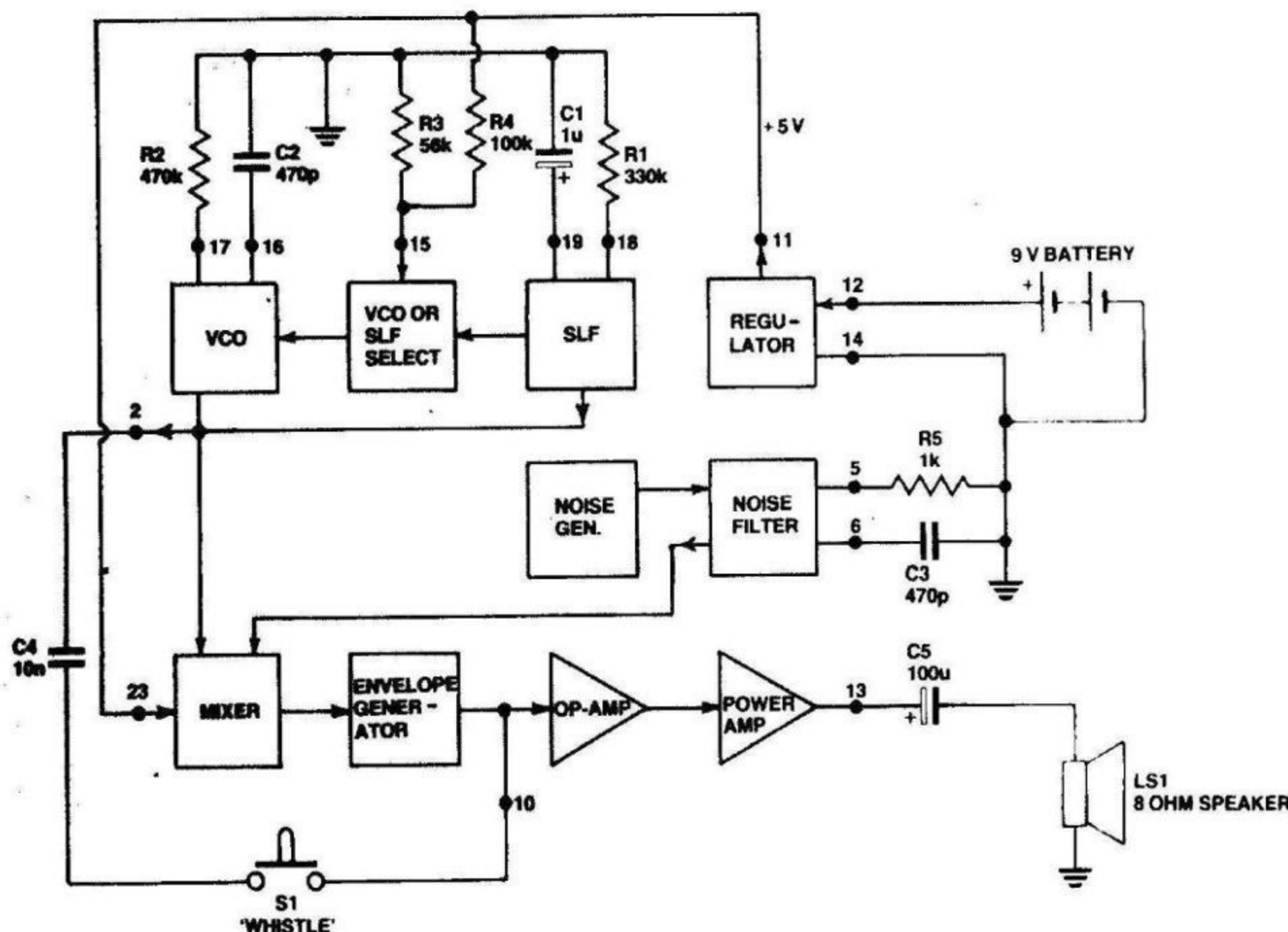


Fig. 1 Circuit diagram of the Steam Train and Whistle unit.

## PARTS LIST

### Resistors (all 1/4 W, 5%)

R1	330k
R2	470k
R3	56k
R4	100k
R5	1k $\Omega$

### Capacitors

C1	1 $\mu$ 0 16 V tantalum
C2, 3	470p ceramic
C4	10n ceramic
C5	100 $\mu$ 16 V PCB electrolytic

### Semiconductors

IC1	SN76488 (see Buylines)
-----	------------------------

### Miscellaneous

PB1	SPST push-button switch
PCB (see Buylines)	50 mm diameter 8 ohm speaker; PP3 battery and clip.

Having trouble containing yourself?

Then why not  
**BOX CLEVER**  
with one of our  
**STANDARD or CUSTOMISED**  
**BIMENCLOSURES**



Instrument Cases  
Small ABS Desk Consoles  
Low Profile Keyboard Consoles  
Easy Access Hinged Lid Consoles  
Diecast and ABS Multi-Purpose Boxes  
All Metal or Genuine Wood Panelled Consoles

**BIMCASES**  
**BIMBOXES**

**BIMCONSOLES**

**FOR PROFESSIONAL QUALITY**  
**AT REALISTIC PRICES**

**BOSS**  
**INDUSTRIAL MOULDINGS LTD**

James Carter Road, Mildenhall, Suffolk.  
Mildenhall (0638) 716101  
Telex: 818758

# Beginners' luck

**30% OFF**  
10 selected kits  
for first-time  
builders



Shortwave  
Listener's  
Receiver

With Heathkit, you're all set for a great deal. And not just big savings.

Whichever kit you choose, you'll find it easy to build. Simple, but detailed instructions take you through every stage. Everything is included. Even the solder you need

*Digital Clock*

is there.



Follow the steps and you'll end up with a hand-crafted, well-designed piece of equipment. One you'll be proud

of. Because you built it yourself.

There are 10 great kits to start you off. An interesting choice of a digital clock to a metal locator, including a short wave listener's receiver, windspeed and direction indicator, digital readout electronic scale and five more useful kits.

All at 30% off to first-timers. Send for your catalogue right now for a start.



Metal  
Locator



Windspeed and Direction  
Indicator

To Heath Electronics  
(UK) Limited, Dept (ET4),  
Bristol Road, Gloucester GL2 6EE

ET4

To start me off, please send me  
a copy of the Heathkit catalogue.  
I enclose 28p in stamps.



Name \_\_\_\_\_

Address \_\_\_\_\_


HEATH  You build on our experience

# HEATHKIT



# Road Runner<sup>®</sup>

## ELECTRONIC PRODUCTS

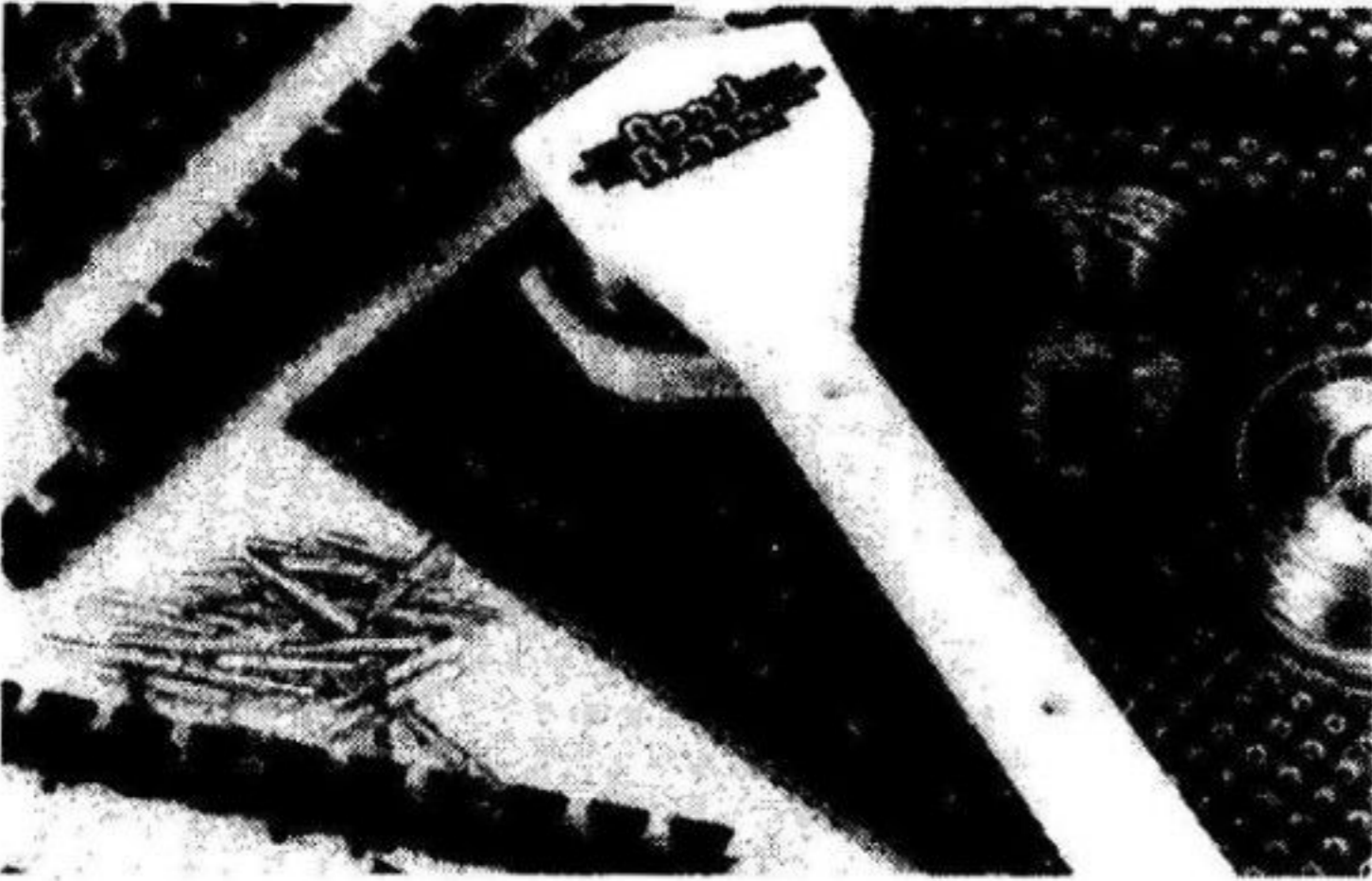

**E.T.I. 10TH ANNIVERSARY ISSUE  
SPECIAL OFFER  
10% OFF ANY ORDER OVER £10**

WIRING SYSTEM	£	LOW PROFILE IC SOCKETS	ONE-PIECE GUIDE BLOCKS
EURO INTROKIT	15.99	TINNED CONTACTS	0.8" CARD PITCH
HOBBY KIT	7.26	8 WAY 9p 14 WAY 12p 16 WAY 14p	3U & 6U/84HP - 2 per ack
MINI KIT A	6.68	18 WAY 16p 20 WAY 18p	3U/40HP " " 1.43
MINI KIT B	6.21	22 WAY 21p 24 WAY 22p	3U/20HP " " 0.78
PCB REPAIR KIT	5.41	28 WAY 25p 40 WAY 35p	INDIVIDUAL RAILS
TRAINING KIT	8.95	GOLD CONTACTS	0.16
GEN. GLUE STRIPS 20/PKT	3.10	8 WAY 17p 14 WAY 18p	DIN 41612 Conn. fixing screws
H/D GLUE STRIPS 20/PKT	3.39	16 WAY 20p 18 WAY 24p	0.36/20
PRESS STRIPS 20/PKT	2.71	20 WAY 27p 22 WAY 28p	*Other accessories available.
OSE PENCIL	2.99	24 WAY 31p 28 WAY 40p	
TCW PENCIL	2.94	40 WAY 50p	
BLUE BOBBINS 4/PKT	2.12	DIN 41612 CONNECTORS	ROADRUNNER IRONS
COPPER COLOUR	2.12	32 way B type Plug	High temp Iron
GREEN COLOUR	2.12	32 way Socket WW Pins	General Purp. Iron
PINK COLOUR	2.12	32 way Socket Solder tag	Iron stand
MIXED PACK OF 4	2.20	64 way C type Plug	Spare Iron bits, ea
TCW BOBBINS 2/PKT	0.98	64 way Socket WW Pins	Welder Iron bits, ea
HOBBY BOARD S/SIDED	1.75	64 way Socket Solder tag	Desolder braid, ea
PROJECT EUROCARD S/SIDED	3.80	96 way also available	Microshears
SINGLE EUROCARD D/SIDED	4.50	EUROCARD SUBRACKS	Knife
DOUBLE EUROCARD D/SIDED	8.60	Kits of 2 end plates, 2 front & rear rails, fixing screws and integral fixing for DIN 41612 Connectors	Tweezers
		3U/84HP 19" wide frame	Spotface cutter
		3U/40HP 10 1/4" wide frame	Pin inserter
		3U/20HP 6 1/4" wide frame	Solder Pins/100
		6U/84HP 19" wide frame	22 SWG Xersin
			Glue strip adhesive

**USE ROADRUNNER PRODUCTS FOR  
VERSATILITY, ECONOMY AND  
PROFESSIONAL RESULTS**

**TAKE ADVANTAGE OF THIS E.T.I. 10TH  
ANNIVERSARY OFFER AND ORDER NOW!**

**WHEN ORDERING ASK FOR THE NEW  
ROADRUNNER CATALOGUE FREE!**

**VISIT THE ROADRUNNER STAND 384  
HALL B UPPER AT THE ALL ELECTRONICS SHOW,  
THE BARBICAN, CITY OF LONDON, APRIL 20-22.  
FREE TICKET  
SUPPLIED WITH EACH ORDER**

ADD 5% TO NET ORDER VALUE TO COVER CARRIAGE AND PACKAGING. THEN ADD 15% VAT.

Please supply requested items.

I enclose cheque/P.O. for £ .....  
or debit my Barclay Card/Access No. ....

Signature .....

Name (Please print) .....

Address .....

Orders to: ROADRUNNER ELEC. PRODS, 116 BLACKDOWN RURAL INDUSTRIES,  
HASTE HILL, HASLEMERE, SURREY GU27 3AY (0428 53850)

# ELECTRO SUPPLIES

## FLOPPY DISC DRIVES

Drico 7200 Dble. Sided 8" Drives (New) P.&P. £4	£200
National Disc Drive Board BLC 8201 (New) P.&P. £1	£160
National CPU Board BCL 8010 (New) uses 8080A CPU P.&P. £1	£120
15" VDU High Resolution Green Phosphor (New) 30 VAC/TTL Sync. I/P P.&P. £5	£50

These Units are in Open Chassis Form

## FARNELL POWER SUPPLIES (ALL NEW)

G6-10S (5V 10A Switched Mode)	£60
FT15/1 (15-0-15V 1A)	£35
G24-1-4M (24V 1.4A Switched Mode)	£40

Each item P.&P. £2

ALL ITEMS INCLUSIVE OF VAT.

**MAIL ORDER DEPT.**  
(Callers please phone first)  
**BOWNESS MILL, SHAWCLOUGH RD,  
WATERFOOT, ROSSENDALE, LANCS.  
TEL: ROSENDALE 215556**

**RETAIL SHOP**  
(Open 6 days)  
**6A TODD ST  
MANCHESTER**  
(next to Victoria Stn)  
**TEL: 061-834 1185**

# TIMEDATA for ZX

## The Explorer's Guide to the ZX81

IF YOU'VE GOT A ZX81 THEN YOU NEED THIS BOOK!

Programs for 1K RAM, and programs for 16K RAM.  
Games, Business and Engineering Applications.  
RAM & IO Circuits. ROM Routines. Hints & Tips.

And Much Much More, for only ..... £ 4.95

## Mastering Machine Code on your ZX80/81

This 180 page book by Tony Baker is ideal for those who want to explore the full potential of their ZX. Whether you know nothing at all about machine code, or whether you are an experienced Z80 programmer, this is definitely the book for you. £ 5.95


## Getting Acquainted with your ZX81

This book by Tim Hartnell is designed to get your ZX81 up and running worthwhile, interesting, programs from the very first day. £ 4.95

## The ZX80 Magic Book \*WITH 8K ROM/ZX81 SUPPLEMENT\*

Games programs, computer music, converting programs written in other BASICS, improving the picture, RAM and I/O circuits, and much more. £4.75

23+23 WAY ZX80/81 EDGE CONNECTOR SOCKET	£3.50
23+23 WAY ZX80/81 GOLD PLATED PLUG EXTENSION	£3.50

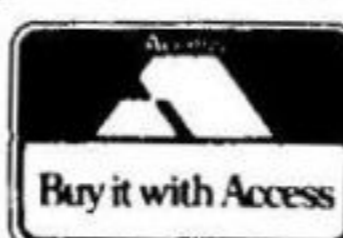

Tel; (0268) 411125 Mon-Fri

Payment with order



**TIMEDATA Ltd. 57 Swallowdale, Basildon, Essex**



# GUITAR PRACTICE AMPLIFIER

Simple construction, low cost, good performance and super neighbour relations are the features of this project! Design and development by David Tilbrook.



This project has been designed to enable guitarists to put in long hours of practice and still keep that high power amp in the cupboard, where it belongs! It is a compact amp capable of about 7 W into a 4 ohm load. This is enough power for practice purposes and just think of the greatly improved relations you will have with your neighbours.

We were in a considerable quandary as to how to present the project, whether it should be done as a complete practice unit with inbuilt speaker or simply as an amplifier to be connected to an external speaker. Finally we chose a compromise. The PCB has been designed in such a way that it can be used as a totally self-contained unit. The heatsinks for the output stage have been mounted on the PCB so that the only components separate to the board are the power transformer, 240 volt power switch controls, input and output jacks. We have shown the project mounted in its own box with power transformer but it should be a simple matter to construct the whole unit inside a small loudspeaker cabinet.

The unit has two inputs so that two guitars can be mixed together using the relative settings of the two input level controls. A preamp output enables your main high power amp to be driven from the guitar practice amp using the practice amp as foldback.

We provided the PCB with the necessary circuitry for a battery input but you might elect not to use this feature. If so diode D8 and the battery switch can be omitted with points 'A' and 'C' connected together by a wire link.

## Construction

Construction of the project is reasonably simple since it is almost entirely devoted to construction of the PCB. Start as always by mounting the resistors and non-polarised capacitors. Mount the tantalum and electrolytic capacitors next, being careful to orient them correctly. These components could be irreparably damaged if inserted the wrong way around. Mount the LM301 IC, transistors and diodes, again being careful to insert these the correct way round.

Finally the output devices can be mounted. Although the transistors are in TO220 packages, our PCB is laid out to accept heatsinks drilled for TO3 transistors. The overlay and photograph should make the construction method clear. Cut the centre (collector) lead off. This lead is connected to the case of the transistor internally, so in this case, electrical connection is made through the mounting screw that also serves to hold the heatsink in place. Place the heatsinks on the PCB and secure with the lower nut and bolt (nut used to mount the transistors). There is only one right way round. Bend the leads of the output transistors and, using a small amount of thermal compound, mount the transistors with the leads protruding through the PCB.

Secure each transistor with a nut and bolt through both the transistor 'flag' and heatsink. Use a star washer between the head of the bolt and the copper pad on the PCB to ensure good electrical contact. Now the base and emitter leads can be soldered to their pads.

The prototype unit was constructed in a steel box measuring

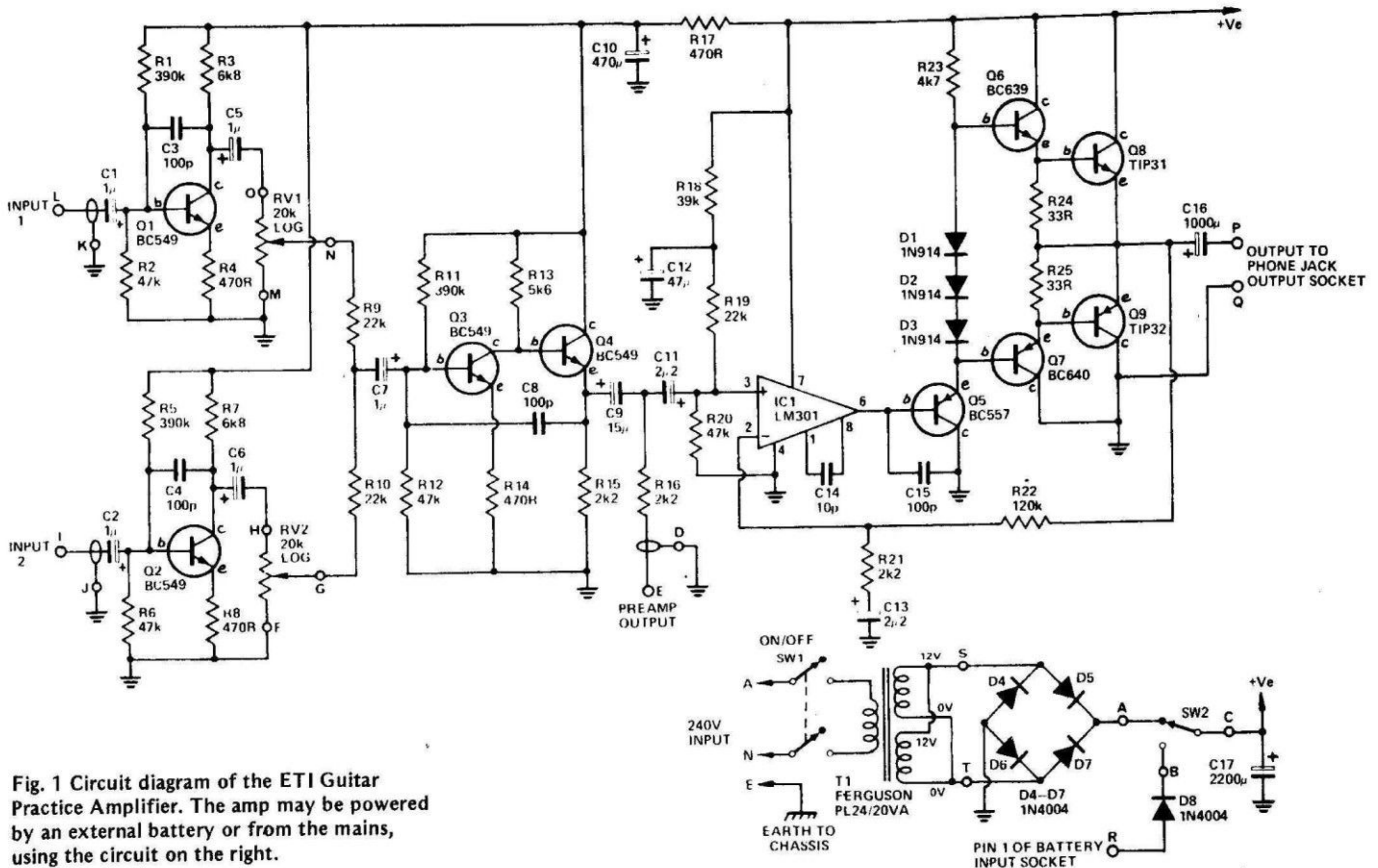


Fig. 1 Circuit diagram of the ETI Guitar Practice Amplifier. The amp may be powered by an external battery or from the mains, using the circuit on the right.

## HOW IT WORKS

The two input stages formed around Q1 and Q2 are identical. Resistors R1, R2 and R4 form a very stable biasing configuration around Q1. The gain of this type of circuit is determined by the values of R3 and R4 (specifically, the gain is  $R3/R4$ ). The load impedance on the output of the input stages is in parallel with R3, effectively decreasing the total value of impedance from collector to ground. Remember that, as far as signal is concerned, the positive supply rail is a short circuit to ground, since it is connected to ground through C17, a 2200 $\mu$ F capacitor. When all these factors are taken into account the gain of the first stage is about 10 since the impedance from collector to ground is about 4k7.

The signal, which should now be around 200 mV, is then applied to the input of the second stage through potentiometers RV1 and RV2. The 22k resistors R9 and R10 prevent the output of one of the stages being shorted to ground when the other is turned right down.

The second stage works in exactly the same manner as the input stages, resistors R11, R12 and R14 forming the bias network for Q3. The voltage present on the collector of Q3 is around 9 V which is approximately half the supply voltage. This is used to bias Q4 which is an emitter follower. This type of amplifier has no voltage gain but provides a low output impedance to drive the preamp output socket. Q3 has a gain of approximately 10. If the volume controls RV1 and RV2 are used in their middle positions, the voltage out will be around one tenth of the voltage at their inputs since these are logarithmic pots. So, the signal voltages into Q3 should be in the order of 20 mV. This will be amplified to a level of 200 mV and applied to the input of the power amp. The power amp has been designed to deliver full power with an input voltage of 300 mV, so the amp should be easily driven to

full output with usable settings.

Since this is a guitar amplifier, it will spend most of its life hard into clipping. The output stage had to be robust! The basis of the output stage is the LM301 op-amp. This device gives all of the voltage gain in the power amp. The output IC1 is fed through a voltage follower Q5. This has no voltage gain and, like Q4, serves to decrease the impedance feeding the output stage. The three diodes, D1, D2 and D3, maintain 1V8 between the bases of Q6 and Q7. Each of these transistors will drop approximately 0V6 across their base-emitter junctions. This leaves a total of 0V6 to be dropped by the two 33R resistors, R24 and R25. Since these are of equal value they will each drop 0V3 and hold this voltage across the base-emitter junctions of the two output transistors Q8 and Q9. As these transistors require 0V6 to turn on they will remain off until the applied signal voltage causes the voltages on their bases to rise above 0V6. The extra 0V3 needed to turn on the output devices will be supplied by a mere 10 mA of current through the 33R resistors. Resistor R22 forms a feedback loop around the entire output stage to decrease distortion, stabilise the DC output voltage and set the overall gain of the power stage (a process too difficult to go into here).

The op-amp will at all times attempt to make the DC voltage at the output equal to that voltage set up on its positive input. This voltage is determined by the potential divider formed by R18, R19 and R20. Since this is also the main input to the power amp any noise which might be on the positive supply rail (and supplies can get very noisy sometimes!) will be communicated directly to the input of the power amp, only to be amplified and applied to the loudspeaker. Capacitor C12 prevents this from happening by bypassing to ground any noise above a frequency of around 0.1 Hz.

approximately 250 x 210 x 80 mm. Mount the pots and switches on the front panel, using the pot and switch nuts to secure the front escutcheon if you have one. Mount the output and battery input sockets on the rear panel. If you are using a battery input socket use something different to the output socket (which is usually a two-pin DIN socket or a 6.5 mm jack socket) to avoid confusion.

Mount the power transformer and make the 240 V connections. The mains lead should be terminated immediately inside the case into a terminal block and the earth lead secured firmly to the chassis by a solder lug bolted to the case using a star washer. This lead must be the longest. A length of 240 V cable should be used between the terminal block and the power switch. Wire the transformer to the power switch as shown in the circuit diagram, then wrap the whole switch with insulation tape or enclose in large diameter heat-shrink tubing so that no 240 V connection is exposed.

Finally, the fully-loaded PCB can be secured into the case using short metal spacers. If Veropins are used, all the connections to the board can be made after the board has been mounted. Connect the front panel controls, rear panel sockets and input sockets, using short lengths of shielded cable to make the connections to the two inputs and preamp output.

# PROJECT : Guitar Practice Amp

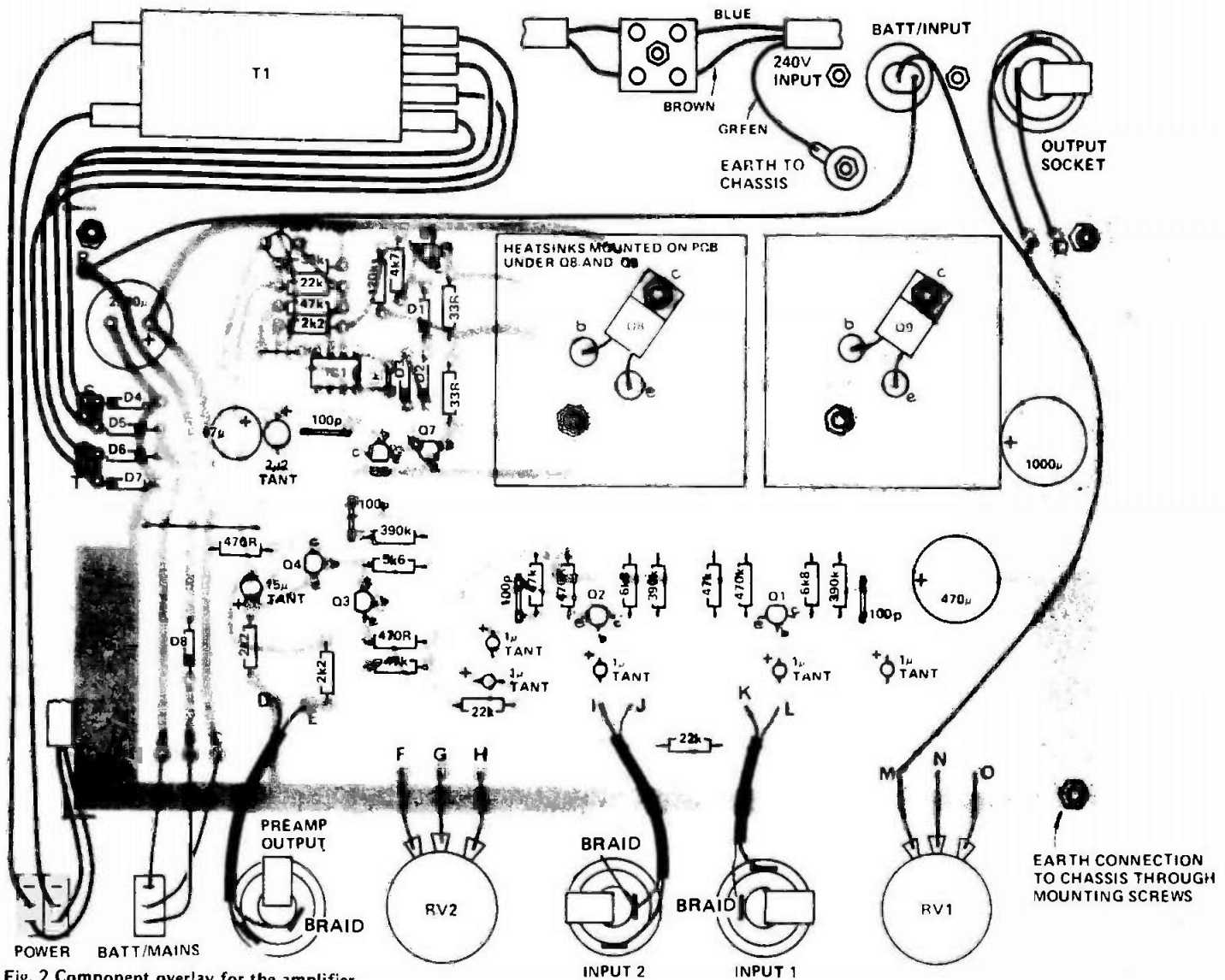


Fig. 2 Component overlay for the amplifier. The original design used a BC639/BC640 complementary pair for Q6 and Q7, and these are shown on the overlay, but they may prove hard to obtain. Consequently the PCB we will be supplying is laid out for a BC140/BC160 pair, which have different pad layouts — the b, c and e pads are etched onto the board for your guidance.

## Powering Up

Make a final check of the wiring and PCB. If all is well, apply power. A slight turn-on thump should be heard at the moment of turn-on. If the 'Input 1' volume control is now wound up, some hiss should be heard from the loudspeaker. Do the same check on the other input. There is no set-up procedure since the power amp stage is operating in class B and requires no bias adjustment.

## BUYLINES

Lots of nice, standard, easy-to-obtain components in this project, so you shouldn't encounter any problems with supply. The PCB will be available from our PCB Service at the price listed on page 44.

## PARTS LIST

### Resistors (all 1/2 W, 5%)

R1,5,11	390k
R2,6,12,20	47k
R3,7	6k8
R4,8,14,17	470R
R9,10,19	22k
R13	5k6
R15,16,21	2k2
R18	39k
R22	120k
R23	4k7
R24,25	33R

### Potentiometers

RV1,2	22k logarithmic
-------	-----------------

### Capacitors

C1,2,5,6,7	1u0 35 V tantalum
C3,4,8,15	100p disc ceramic
C9	15u 16 V tantalum
C10	470u 25 V PCB electrolytic
C11,13	2u2 35 V tantalum
C12	47u 25 V PCB electrolytic
C14	10p disc ceramic

C16	1000u 25 V PCB electrolytic
C17	2200u 25 V PCB electrolytic

### Semiconductors

IC1	LM301
Q1-4	BC549 or BC109
Q5	BC557 or BC179
Q6	BC140
Q7	BC160
Q8	TIP31
Q9	TIP32
D1-3	1N914
D4-8	1N4004

### Miscellaneous

SK1-4	mono jack sockets
SK5	DIN socket (or other type — see text)
SW1	DPDT toggle switch (mains rated)
SW2	DPST toggle switch
Transformer (12-0-12-0, 20 VA); TO3 type PCB-mounting heatsinks; PCB (see Buylines); case to suit; mounting hardware.	

# FOR A SOUND DIAGNOSIS...

New CLEAN N CHECK is a unique and complete cassette machine maintenance pack.

The patented \*Drive Analyser will check in seconds the drive mechanism of your cassette machine to locate faults which can lead to damage and breakdown.

If the Drive Analyser shows no fault, then you can confidently use the tape head and capstan cleaning solutions provided to ensure optimum performance.

Proper maintenance of any machine should consist not only of cleaning, but also of checking the mechanism.



The Clean-n-Check pack contains

- Head cleaning solution.
- Capstan cleaning solution.
- Cotton buds and holder.
- Drive analyser cassette with indicator registering as faulty/normal/service required soon, on play/rewind/FFwd functions of your cassette player.

The check drive analyser is presently being used by growing numbers of hi-fi service organisations.

## Clean·n·Check™

*"Because good sound...sounds good!"*

TO: TECHNOLOGY RESOURCES LTD,  
88-90, GRAYS INN ROAD, LONDON, WC1X 8AA

Please send me ..... CLEAN·N·CHECK packs at £4.50 each (incl. p&p). Total enclosed: £

NAME: .....

ADDRESS: .....

(Allow 14-21 days delivery. 28 day money back guarantee)  
Registered in England No. 1428994

This model is not suitable for use with car cassette players.

ETI.4.82

## CAMBRIDGE LEARNING SELF-INSTRUCTION COURSES

### A PRACTICAL DIGITAL ELECTRONIC KIT FOR ★ LESS THAN £20 ★



### SUITABLE FOR BEGINNERS

Learn the wonders of digital electronics and see how quickly you are designing your own circuits. The kit contains:

seven LS TTL integrated circuits, breadboard, LEDs, and all the

DIL switches, resistors, capacitors, and other components to build interesting digital circuits; plus a very clear and thoroughly tested instruction manual (also available separately). All this comes in a pocket size plastic wallet for only £19-90p inc VAT and p&p. This course is for true beginners:

- needs no soldering iron.
- asks plenty of questions, but never leaves you stuck and helpless.
- teaches you about fault-finding, improvisation, and subsystem checking.
- the only extra you need is a 4½V battery (Ever Ready 1289, or similar), or a stabilised 5V power supply.

Using the same breadboard you may construct literally millions of different circuits.

This course teaches boolean logic, gating, R-S and J-K flipflops, shift registers, ripple counters, and half-adders. Look out for our supplementary kits which will demonstrate advanced arithmetic circuits, opto-electronics, 7-segment displays etc.

Other self-instruction courses from Cambridge Learning Ltd include:

COMPUTER PROGRAMMING IN BASIC	£10.50
DIGITAL COMPUTER LOGIC AND ELECTRONICS	£ 8.50
DESIGN OF DIGITAL SYSTEMS	£14.00

Please send for full details (see coupon below).

**GUARANTEE** No risk to you. If you are not completely satisfied, your money will be refunded upon return of the item in good condition within 28 days of receipt.

CAMBRIDGE LEARNING LIMITED, Unit 14 RIVERMILL SITE, FREEPOST, ST IVES, CAMBS, PE17 4BR, ENGLAND.  
TELEPHONE: ST IVES (0480) 67446. VAT No 313026022

All prices include worldwide postage (airmail is extra - please ask for prepayment invoice). Giro A/c No 2789159.

Please allow 28 days for delivery in UK

Please send me:

.....SUPERKIT(S) @ £19.90

.....Free details of your other self-instruction courses.

I enclose a \*cheque/PO payable to Cambridge Learning Ltd for £..... (\*delete where applicable)

Please charge my:

\*Access / American Express / Barclaycard / Diners Club  
Eurocard / Visa / Mastercharge / Trustcard

Expiry Date..... Credit Card No .....

Signature.....

Telephone orders from card holders accepted on 0480 67446  
Overseas customers (including Eire) should send a bank draft in sterling drawn on a London bank, or quote credit card number.

Name.....

Address.....

Cambridge Learning Limited, Unit 14 Rivermill Site, FREEPOST, St Ives, Huntingdon, Cambs, PE17 4BR, England. (Registered in England No 1328762).



# The MICRO-PROFESSOR ...



MICRO-PROFESSOR is a low-cost Z80 based microcomputer which provides you with an interesting and inexpensive way to get into the microprocessor world. MICRO-PROFESSOR is a microprocessor learning tool for students, hobbyists and personnel. It is also an ideal microprocessor educational tool for teaching in schools and universities. Besides, MICRO-PROFESSOR is more than a learning tool. It provides a wide range of applications such that you will be surprised at its amazing power.

The main object of MICRO-PROFESSOR is for the user to understand the software and hardware of a microcomputer easily and conveniently. Besides

the complete hardware/software system, you have the User's experiment manual available to you. It includes self-learning text with 20 experiments which range from simple software programming to design a complex electronic game.

2K bytes of monitor source program with documentation is also provided in the manual. It shows how to write system programs including system initialization, keyboard scan, display scan, tape write and tape read.

#### APPLICATIONS:

Learning and teaching tool  
Low cost prototyping tool  
Low cost development tool  
Tester

MICRO-PROFESSOR is a trade mark of Multitech Industrial Corporation.

Process controller  
Electronic game  
Electronic music box  
Master mind  
Timer  
Noise generator  
Home appliance control  
Burglar alarm  
System control simulation  
... and many more.

**Low Price, High Capability  
experimental tool for only**

# £59.95

**POWER SUPPLY** + p & p  
A 9V, 0.5A Adaptor is provided.


Z80 is a trade mark of Zilog Inc.

# solves the 'mystery' of micro-processors.

## TECHNICAL SPECIFICATION

<b>CPU</b>	Z80 CPU high performance microprocessor with 158 instructions.
<b>SOFTWARE COMPATIBILITY</b>	Capable of executing Z80/8080/8085 machine language program.
<b>RAM</b>	2K bytes expandable to 4K bytes.
<b>ROM</b>	2K bytes of sophisticated monitor expandable to 8K bytes.
<b>INPUT/OUTPUT</b>	24 system I/O lines.
<b>MONITOR</b>	2K bytes of sophisticated monitor. It scans the keyboard and executes the command entered immediately after the power is turned on. The monitor includes: system initialization, keyboard scan, display scan tape write and tape read.
<b>DISPLAY</b>	6 digit 0.5" red LED display.
<b>AUDIO CASSETTE INTERFACE</b>	165 bit per second average rate for data transfer between memory and cassette tape.
<b>EXTENSION CONNECTORS</b>	Provides all buses of CPU, channel signals of CTC and I/O port bus of PIO for user's expansion.
<b>COUNTER TIMER CIRCUITS</b>	Socket is provided. Z80-CTC IC extra.
<b>PARALLEL I/O CIRCUITS</b>	Socket is provided. Z80-P10 IC extra.
<b>SPEAKER AND SPEAKER DRIVER CIRCUITS</b>	A 2.25" - diameter speaker is provided for user's applications.
<b>USER AREA</b>	Provides a 3.5" x 1.36" wire wrapping area for user's expansion.
<b>POWER REQUIREMENT</b>	Single +5V DC.
<b>USER'S AND EXPERIMENT MANUAL</b>	Complete self-learning text with experiments and applications.
<b>OPTIONS (Prices on application)</b>	Z80 - CTC EPROM programmer board Prototyping board Z80 - PIO Speech synthesiser board Audio Cassette 2K Ram
<b>KEYBOARD</b>	36 keys including 19 function keys, 16 hex-digit keys and 1 user defined key.

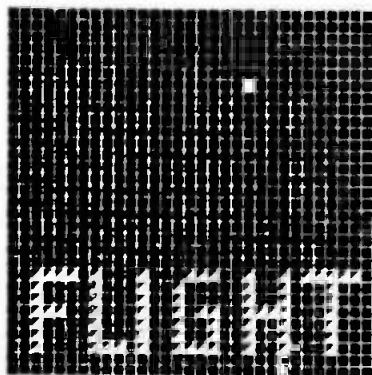Use the unique MICRO-PROFESSOR to truly understand the inside workings of microprocessors. Open up a whole new spectrum of projects in home electronics, or simply use the MICRO-PROFESSOR as a practical learning/teaching aid.



Flight Electronics Ltd.

To receive your MICRO-PROFESSOR Complete the coupon today!

Please send me ..... MICRO-PROFESSOR(S)


I enclose cheque/P.O. for £..... (+ £2.95 p & p)

Name: .....

Address: .....

Please allow 21 days for delivery

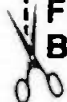**Flight Electronics Ltd. Flight House, Quayside Road,  
Bitterne Manor, Southampton, Hants SO2 4AD.**



Tel: (0703) 34003/31323

**INFRA RED IMAGE CONVERTOR** type 9606 (CV144) 1 1/2" dia. Requires single low current 3KV to 6KV supply. Individually boxed. With data. £12.50 ea. 10 off £10.

**INFRA RED QUARTZ LAMPS.** 230V 620 Watts Size 1 3/8" x 1/2" dia. £1.50 ea. 10 off £1.0. 240V 1650 Watts Size 2 1/2" x 1/2" dia. £3 ea. 10 off £2.5.

**FANS 115V 13 Watt** Size 3 1/4" x 3 1/4" x 1 1/4". Secondhand £2.50 ea. **CENTAUR FANS 115V** Size 4 1/4" x 4 1/4" x 1 1/4". New £4.50 ea. Secondhand £2.50 ea.

**DELAY LINES** 50 nanoseconds. Ground-in-out. Size 2 x 7/16 x 5/16". New 25p ea. 10 off £2.

**PULSE TRANSFORMERS.** Sub min Size 1/2" x 5/16" x 1/4". Secondhand metal taped. New. Suitable for Thyristor triggering. 20p ea. 10 off £1.80. 100 off £15.

**MOTORS 12V DC** with pulley & semiconductor speed control. New £1 ea. 10 off £8.

**DIAMOND H CONTROLS ROTARY SWITCH** Single pole 10 way. Printed circuit mount. New 10p ea. 100 off £7. 1000 off £50.

**STEPPING MOTORS** - 200 Steps 20 oz/in torque. 12/24V input. 5 wire. £12 ea.

**STEPPING MOTORS** - 200 Steps 20 oz/in torque 120V input 3 wire. £4 ea.

**STEPPING MOTORS** - 5 Volt 3.3 Amp operation 2 Wire. PPS 0.220. RMP 0.250. Usaf £18 ea.

**STEPPING MOTORS** - 6/12 position can be used as a tach. 12/24V will work on 5V £1.80 ea. 5 for £5.

**SINGLE PLY TELEPRINTER PAPER** Size 8 7/16" x 3 7/16". 1.25 each or 12 rolls for £12 P&P £3.50.

**BLACK RIBBONS FOR TELEPRINTERS** 75p each or 5 for £4.

**MIN KEYBOARD** Push contacts, marked 0-9 A-F & P for £0.01. £1.75 ea. 10 for £16.

**KEYBOARD PAD** Size 3 x 2 1/2 x 2" high with 12 Alma Reed Switches. Blue keys marked in green. 0-9 & star with one blank. £4 ea. 5 off £16. P&P £2.50.

**DON'T TAKE CHANCES** Use the proper EMT Cable 10p metre. £7.50 100 metres P&P £2.

**RAPID DISCHARGE CAPACITORS** 8 mfd 4KV ES each. P&P £2.

**HUNTS CAPACITOR** 0.1 mfd 3KV DC Wkg. Size 1 1/2" dia x 3". £1.25 ea. 10 for £10.

**E.M.T. CAPACITOR** 500 pF 8KV 20p each.

**DECOUPLING CAPS** 0.05mfd 10V, 0.01mfd, 0.047 250V, 330pF. 100 off one type £1.50.

**CAPACITORS** all at 5p each. 3300pF, 220V 250V, 0.01mfd 160V, 0.1 of 400V.

**REMO TV Type MULTIPLIER.** Two high voltage outputs & focus £1 each. 10 for £8.

**RANCO 250V 18A THERMOSTATS** with Control Knob calibrated 50-200°C. £2.50 each.

**MICROPHONE/EARPIECE INSERTS.** Ex Min. Brand New wrapped. 75p ea. 10 off £6.

**TRANSFORMERS** - All Brand New.

Auto 240V input 115V 1 Amp output £1.25 ea.

240V Input Sec 6V 1.80A. Size 2 1/2" x 2" x 2". Good quality £1.50 ea.

240V Input Sec 12V 100MA. Size 80 x 40 x 42mm 50p ea.

240V Input Sec 12-0 12V 50MA. Size 53 x 45 x 40mm £1 ea.

115V Input Sec 5V 250MA Size 1 1/16" x 1 1/8" x 1 1/8". 2 for 50p.

240V Input Sec 2 windings 12V and 24V 1 Amp. Size 2 1/2" x 2" x 2". £2 ea.

Sub Min 0-120 240V Input Sec 12-0 12V rated 4VA. 75p ea. 10 off £6. 100 off £45.

**TOROIDAL 0 116-230V** input. Output 13.5-0-13.5V rated 8VA. £1.70 ea. 10 off £15.

**TOROIDAL 0-120-240V** input. Output 0-12V. 10VA per winding. Encapsulated identical to R.S. Components at £9.40. OUR PRICE £5 ea.

**TELEPHONES** - P&P £1.50 ea. 5-10 units £6. Over by arrangements. 7000 Black, Gray, Blue, Green ES.50 ea. 10 off £45. Discoloured £4 ea. 10 off £27.50.

748 style Black or Gray £7.50 ea. Older Black style £2.50 ea.

**SOME EHT TRANSFORMERS & CAPACITORS** always available - please enquire.

**VARIACS** - 2 Amp. Ex-equipment. Good condition. £12 ea. P&P £3.

**TRANSISTOR INVERTOR.** 115V AC 1.7 Amp input. Switching at 20KHZ output windings from Pot Core. Can be re-wound or broken for components. Circuit Supplied. £1.25 ea. P&P £2. 10 off £10 Carriage £5.

Convert this unit to a **SUPER BATTERY CHARGER.** Attractive green military quality case - removable top/bottom plates - heavy duty power switches - high power resistors to control current - centre mounted amp meter - wing nut terminals on front panel for connecting leads. £3.50 ea. P&P £5 FOUR UNITS £12 Carriage £8.

Miniature **VARIAC** 0.6 amp in Blue Case size 10 1/2" x 6 1/2" x 6 1/2" with 20 coloured screw style 4mm sockets giving multiple voltage & current outputs. As new £12 P/P £4.

**AMPLIFIER BOARD** complete with Heat Sink & two output Transistors type 2N5293 Circuit supplied £1.50 ea.

**CABLE TIES** Black 13cm long 0.8 White 9cm. 50 for 50p.

**TOGGLE SWITCH** Centre off. 30p ea. 10 for £2.70.

**4 CORE CURLY WIRE** extending to 2 metres. 20p ea. 10 off £1.80. 100 off £15.

**Min Potentiometer** - Enc 1K Lin, 3.3K Lin, 4.7K Lin All 15p each. 100 off £12.

**WIRE WOUND RESISTORS 4 WATTS** - all at 10p ea. 10 off 85p. 100 off £7.

Values - 10, 20, 24, 28, 30, 33, 36, 40, 45, 50, 56, 60, 68, 75, 82, 91, 100, 110, 120, 150, 180, 200, 220, 240, 270, 300, 330, 360, 400, 450, 500, 560, 600, 680, 750, 820, 910, 1000, 1100, 1200, 1500, 1800, 2000, 2200, 2400, 2700, 3000, 3300, 3600, 4000, 4500, 5000, 5600, 6000, 6800, 7500, 8200, 9100, 10000.

**MULTICORE CABLE** 18-Way. Multi colour. 75p per metre. 100 metre drum £55. Carr £5.

**GEC 4 Button UHF TUNER** £1.50 ea. 10 off £12.

**GEC 6 Button UHF/VHF TUNER.** £2 ea. 10 off £16.

**SOLID STATE UHF TUNER** 30MHz to 100MHz. £2 ea. 10 off £18.

**PHOTOMULTIPLIERS** - All with info material - P&P all tubes £1.50 ea.

British 2" window £2 ea. American 2" £3 ea. RCA type 2020 £4 ea. Special American by RCA £6 ea. MULLARD 150AVP Useful dia 32mm £4 ea.

**HONEYWELL STRIP CHART PAPER** 12 1/2" rolls. Ref no 378528-0100. Even 12/68. 50p per roll. 10 rolls £4 P&P £3.50.

**BLUE THERMAL PAPER** 430M roll 9 1/2" wide. £2 per roll P&P £2. 6 rolls £10 Carr. £5.

FOR FULL COMPONENT & TEST EQUIPMENT LIST WRITE OR PHONE

**WAYNE KERR BRIDGE B221** £70 ea.

**WAYNE KERR UNIVERSAL BRIDGE BS21 (CT375)** £50 ea.

**MARCONI SIGNAL GENERATOR TF801D/15** £150 ea.

**10-485 MHz** £65 ea.

**AVO VALVE TESTER CT160** £20 ea.

**ADVANCE AUDIO SIGNAL GENERATOR J1A** £30 ea.

**TELETYPE PRINTERS**

ASR33 ASCII keyboard with 8 bit paper tape punch and reader £75

KSR33 Ino punch and reader £50

PDP8 in 6H RACK CABINET £100

**AVO SIGNAL GENERATOR**

No. 2 AM/FM

AM 0.45-225MHz FM 20-100MHz

£75 each

**TEKTRONIX PLUG-IN'S**

TYPE D Single Trace High Gain DC Differential £20

TYPE E Single Trace Low Level AC Differential £20

TYPE G Single Trace Wide Band DC Differential £28

TYPE L Single Trace 30MHz High Gain £26

TYPE M 4 Trace DC-20MHz £125

TYPE O Operational Amplifier £96

TYPE P Transducer & Strain Gauge £75

TYPE R Transistor Rise Time £75

TYPE T1 2 Testing £25

TYPE W Differential Comparator £128

TYPE Z Differential Comparator £75

TYPE 1A5 DC-50 MHz Differential £75

TYPE 1S1 Sampling £175

**MULTIMETER**

Russian type 4324 AC/DC volts; AC/DC current; ohms etc. £12.50 each P&P £2.50

**SINE & SQUARE WAVE AUDIO GENERATOR**

Type T22

20Hz-200KHz. Portable. As new ONLY £35 each P&P £4

**GENERAL PURPOSE OSCILLOSCOPE TECH TYPE 2**

Single beam. Size approx 6 x 7 x 9 in. Weight 7lbs. Ideal for the beginner or school user. ONLY £35 each P&P £4

**IKEGAMI 20" BLACK & WHITE MONITORS**

Solid State. Video in. Int & Ext Sync. £75 each.

**SCOPE STYLE CASE** with attractive blue covers and strap handle. Black chassis with prop up stand & rubber feet containing two 5" fluorescent strip lights. Illuminated mains on/off switch, 2 pots with knobs, side switch, 1 1/2 metres 2 core mains cable, small fuse holder mains transformer and PCB. (As is TACHISTOSCOPE) ideal for the home constructor. £4.50 each P&P £2

MINIMUM ORDER OF GOODS £3. MINIMUM PACKAGING & POSTAGE £1.50. VAT at 15% MUST be added to TOTAL of GOODS & PACKAGING, BUT PLEASE ensure sufficient monies is sent to cover PACKAGING and Postage to avoid delays in us dispatching your order. CALLERS VERY WELCOME STRICTLY BETWEEN 9am-1pm and 2-5pm Monday to Saturday inc. BARCLAYCARD (VISA) and ACCESS taken. Official orders welcome.

# CHILTEARD LTD

NORWOOD ROAD, READING

TELEPHONE NO. READING 669656


(2nd turning left past Reading Technical College in King's Road then first right - look on right for door with "Spoked Wheel")

MARCH SALE				Send SAE for bulk offers								
<b>PWR SUPPLY:</b> For micros and TTL Stabilised 1A5/15V. Built tested uncase - 580p	LF351N 45p	LF356N 90p	LM100C 460p	OPP12 80p	1N4005 5p	LS11/12 15p	7445 72p	74194/5 64p	BC212 9p	BFX86 18p	2N1308 23p	7447A 20p
<b>AS ABOVE</b> less transformer 240p	LM308AN 20p	LM308N 30p	LM311 80p	TIL38 16p	1N5401 12p	LS14 24p	7447A 35p	74197 44p	BC212L 9p	BFX87 23p	2N1308 30p	7448 20p
<b>PCB</b> for above or 12V or 15V 100p	LM311 80p	LM318H 90p	LM318N 100p	LEDs 12mm (IR) 16p	1N5402 13p	LS14 24p	7450 11p	74198 98p	BC213 9p	BFX88 22p	2N1613 21p	7448 20p
<b>CERAMIC CAPACITORS (50V)</b>	LM318H 90p	LM324N 40p	LM324N 40p	3mm clip 3p	1N5404 14p	LS21/27 15p	7451 8p	74199 80p	BC214 9p	BFY50 20p	2N2217 18p	7450 11p
33pF to 50,000pF 3p	LM339N 45p	LM339N 45p	LM339N 45p	5mm clip 3p	LS30 14p	LS30 14p	7452 25p	74200 22p	BC214L 9p	BFY52 18p	2N2222A 15p	7452 25p
<b>POLYSTYRENE CAPACITORS (50V)</b>	LM339N 45p	LM339N 45p	LM339N 45p	3mm & 5mm RED LED 10p	LS32 17p	LS32 17p	7453 25p	74201 22p	BC217 7p	BFY53 10p	2N2464 18p	7453 25p
10pF to 1000pF 3p	LM339N 45p	LM339N 45p	LM339N 45p	GREEN LED 11p	LS32 17p	LS32 17p	7454 19p	74202 22p	BC217 7p	BRV39 30p	2N2464 18p	7454 19p
<b>POLYESTER CAPACITORS (100V)</b>	LM339N 45p	LM339N 45p	LM339N 45p	YELLOW LED 11p	LS32 17p	LS32 17p	7455 19p	74203 22p	BC218 7p	BRV39 30p	2N2464 18p	7455 19p
1nF to 500nF 6p	LM339N 45p	LM339N 45p	LM339N 45p	RECT GREEN 13p	LS32 17p	LS32 17p	7456 19p	74204 22p	BC218 7p	BU205 105p	2N2904 17p	7456 19p
<b>ELECTROLYTIC CAPACITORS (uF)</b>	LM339N 45p	LM339N 45p	LM339N 45p	VOLTAGE REGULATORS 401B 14p	LS32 17p	LS32 17p	7457 19p	74205 22p	BC219 7p	BU205 105p	2N2904 17p	7457 19p
1/25 to 150/25 6p	LM339N 45p	LM339N 45p	LM339N 45p	401B 14p	LS32 17p	LS32 17p	7458 19p	74206 22p	BC219 7p	BU205 105p	2N2904 17p	7458 19p
220/25 470/25 10p	LM339N 45p	LM339N 45p	LM339N 45p	401B 14p	LS32 17p	LS32 17p	7459 19p	74207 22p	BC220 7p	BU205 105p	2N2904 17p	7459 19p
1000/10 2200/15 12p	LM339N 45p	LM339N 45p	LM339N 45p	401B 14p	LS32 17p	LS32 17p	7460 19p	74208 22p	BC221 7p	BU205 105p	2N2904 17p	7460 19p
2000/18 33p	LM339N 45p	LM339N 45p	LM339N 45p	401B 14p	LS32 17p	LS32 17p	7461 19p	74209 22p	BC222 7p	BU205 105p	2N2904 17p	7461 19p
<b>TRANSFORMER 0-5V 2 Amp</b> 360p	LM339N 45p	LM339N 45p	LM339N 45p	401B 14p	LS32 17p	LS32 17p	7462 19p	74210 22p	BC223 7p	BU205 105p	2N2904 17p	7462 19p
<b>HEAT SINK 10-220 18" CIVIL</b> 40p	LM339N 45p	LM339N 45p	LM339N 45p	401B 14p	LS32 17p	LS32 17p	7463 19p	74211 22p	BC224 7p	BU205 105p	2N2904 17p	7463 19p
<b>VERO BOARD (0.1" copper clad)</b>	LM339N 45p	LM339N 45p	LM339N 45p	401B 14p	LS32 17p	LS32 17p	7464 19p	74212 22p	BC225 7p	BU205 105p	2N2904 17p	7464 19p
<b>2.5 x 5" 60p</b> 3.75" x 5" 100p	LM339N 45p	LM339N 45p	LM339N 45p	401B 14p	LS32 17p	LS32 17p	7465 19p	74213 22p	BC226 7p	BU205 105p	2N2904 17p	7465 19p
<b>SWITCHES</b>	LM339N 45p	LM339N 45p	LM339N 45p	401B 14p	LS32 17p	LS32 17p	7466 19p	74214 22p	BC227 7p	BU205 105p	2N2904 17p	7466 19p
DIL 3 way SPST 20p	LM339N 45p	LM339N 45p	LM339N 45p	401B 14p	LS32 17p	LS32 17p	7467 19p	74215 22p	BC228 7p	BU205 105p	2N2904 17p	7467 19p
DIL 3 way SPDT 30p	LM339N 45p	LM339N 45p	LM339N 45p	401B 14p	LS32 17p	LS32 17p	7468 19p	74216 22p	BC229 7p	BU205 105p	2N2904 17p	7468 19p
DIL 7 way SPST 30p	LM339N 45p	LM339N 45p	LM339N 45p	401B 14p	LS32 17p	LS32 17p	7469 19p	74217 22p	BC230 7p	BU205 105p	2N2904 17p	7469 19p
<b>ROTARY 2A/250V DPST 9mm bush</b> 18p	LM339N 45p	LM339N 45p	LM339N 45p	401B 14p	LS32 17p	LS32 17p	7470 19p	74218 22p	BC231 7p	BU205 105p	2N2904 17p	7470 19p
<b>TANTALUM BEAD CAP</b> 11p	LM339N 45p	LM339N 45p	LM339N 45p	401B 14p	LS32 17p	LS32 17p	7471 19p	74219 22p	BC232 7p	BU205 105p	2N2904 17p	7471 19p
<b>SLIDE 1A/250V SPDT</b> 6p	LM339N 45p	LM339N 45p	LM339N 45p	401B 14p	LS32 17p	LS32 17p	7472 19p	74220 22p	BC233 7p	BU205 105p	2N2904 17p	7472 19p
<b>SLIDE 1A/250V DPDT</b> 7p	LM339N 45p	LM339N 45p	LM339N 45p	401B 14p	LS32 17p	LS32 17p	7473 19p	74221 22p	BC234 7p	BU205 105p	2N2904 17p	7473 19p
<b>SLIDE 3A/150V DP 3 way or 1A/250V with 1 throw panel cutout</b> 10p	LM339N 45p	LM339N 45p	LM339N 45p	401B 14p	LS32 17p	LS32 17p	7474 19p	74222 22p	BC235 7p	BU205 105p	2N2904 17p	7474 19p
<b>RESISTORS (1/4W 5% carbon film)</b> 10 ohms to 10Mohms E12 2p	LM339N 45p	LM339N 45p	LM339N 45p	401B 14p	LS32 17p	LS32 17p	7475 19p	74223 22p	BC236 7p	BU205 105p	2N2904 17p	7475 19p
<b>PRESETS (miniature horizontal)</b> 10 ohms to 10Mohms 6p	LM339N 45p	LM339N 45p	LM339N 45p	401B 14p	LS32 17p	LS32 17p	7476 19p	74224 22p	BC237 7p	BU205 105p	2N2904 17p	7476 19p
<b>CERMET: (1 Watt)</b>	LM339N 45p	LM339N 45p	LM339N 45p	401B 14p	LS32 17p	LS32 17p	7477 19p	74225 22p	BC238 7p	BU205 105p	2N2904 17p	7477 19p
100K linear precision 40 turn 30p	LM339N 45p	LM339N 45p	LM339N 45p	401B 14p	LS32 17p	LS32 17p	7478 19p	74226 22p	BC239 7p	BU205 105p	2N2904 17p	7478 19p
<b>POTENTIOMETERS (1 1/4W):</b> Linear and Log Scale 4K7 to 2M2 28p	LM339N 45p	LM339N 45p	LM339N 45p	401B 14p	LS32 17p	LS32 17p	7479 19p	74227 22p	BC240 7p	BU205 105p	2N2904 17p	7479 19p
<b>ZENER DIODES (400mW)</b>	LM339N 45p	LM339N 45p	LM339N 45p	401B 14p	LS32 17p	LS32 17p	7480 19p	74228 22p	BC241 7p	BU205 105p	2N2904 17p	7480 19p
2V7 to 33V 5p	LM339N 45p	LM339N 45p	LM339N 45p	401B 14p	LS32 17p	LS32 17p	7481 19p	74229 22p	BC242 7p	BU205 105p	2N2904 17p	7481 19p
<b>TRIACS: C206D 400V:3A</b> 55p	LM339N 45p	LM339N 45p	LM339N 45p	401B 14p	LS32 17p	LS32 17p	7482 19p	74230 22p	BC243 7p	BU205 105p	2N2904 17p	7482 19p
<b>600V: 10A 50p</b> 15A 50p 30A 85p	LM339N 45p	LM339N 45p	LM339N 45p	401B 14p	LS32 17p	LS32 17p	7483 19p					





**EX STOCK!**

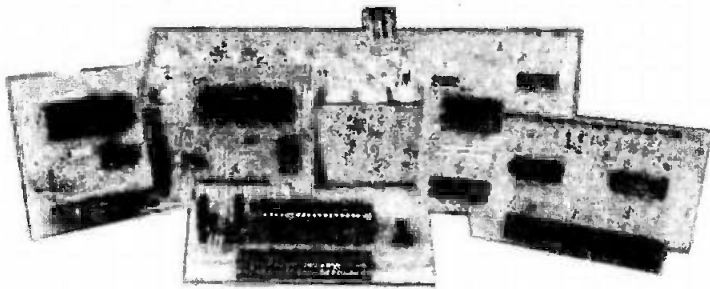

Kit keyboard . . . . .	£20.75
Built keyboard . . . . .	£25.75
Case for keyboard . . . . .	£10.30
Built keyboard in case . . . . .	£36.15
16 bit LED board (kit) . . . . .	£9.50
24 line in/out port . . . . .	£16.95
built . . . . .	£18.95
3 channel music bd . . . . .	£16.95
built . . . . .	£18.95
Motherboard with 2 connectors . . . . .	£15.75
built . . . . .	£18.50
23 way edge connector . . . . .	£2.95
23 way male connector . . . . .	£1.30

**BOOKS**

Getting acquainted with your ZX81 . . . . .	£4.95
Mastering machine code (ZX80 or 81) . . . . .	£5.95
Programming for real applications . . . . .	£6.95
Tape for above . . . . .	£11.44

**REDDITCH ELECTRONICS**




DEPT ET1,  
21 FERNEY HILL AVE.,  
REDDITCH,  
WORCESTERSHIRE,  
B97 4RU

Prices included Postage and VAT.  
(Overseas add £1.80)  
SAE for free illustrated catalogue

**QUALITY DOES NOT HAVE TO COST VERY MUCH!**


ALL PRICES INCLUDE VAT

**AUDAX HI-FI - SPECIAL PURCHASES**

	HQ20B25H4C 8" Bass mid range Bextrene cone 40/60 watt systems	£9.95
	HQ24S452C 10" high performance bass. Foam suspension 60/80 watt systems	£12.95
	HD13B25H4C 5 1/2" bass mid range Bextrene cone 40/60 watt systems: Heavy magnet.	£6.95
	HD13B25J Smaller magnet version	£5.95
	HIF20JSMC 8" bass mid range foam surround square silver front 30/50 watt system	£8.95
	HIF20ESM 8" bass mid range. For 30/50 watt systems roll surround treated cone. 4 ohm £6.95 8 ohm £7.95	
	HIFB7BSMO 4" closed back mid range for 30/50 watt systems	£5.50
	HD10025HR 1" dome tweeter. 4" frame for 60/80 watt systems.	£5.95

All models for 8 ohms unless stated. (UK Post etc. Speakers 70p tweeters and mid range 50p)

**TV SOUND FROM YOUR HI-FI (Mk III)**

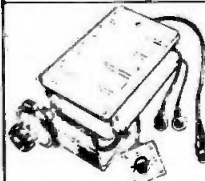

High quality TV sound converter, plugs into aerial socket of your FM tuner 9 volt battery operated (battery not supplied). Nothing to look at... but just listen! Covers all U.K. UHF Channels.

\*Fitted slow-motion drive (Mk III) **£11.50**  
Four button push-button version £14.50 c/p 65p. (UK Post etc. 65p)  
On Demonstration for callers to 301 Edgware Road.

**PIEZO TWEETERS**



Clean sound. Very low distortion tweeters. No crossover required.		
1	64d range horn for discolor/groups	£7.95
2	Tweeter horn for hi-fi/discolor/groups	£5.95
3	Popular hi-fi and disco	£4.95
4	Flat type hi-fi	£3.95
5	Round version of No 3	£4.95
6	Round free standing hi-fi piece	£8.95
UK Post Free		£17.50

On Demonstration to callers

**ORDER BY POST (OR PHONE) OR CALL IN**

ALL PRICES INCLUDE VAT



Cubegate Limited

**AUDIO ELECTRONICS**

301 Edgware Rd. London W2 1BN

Tel: 01-724 3564

Also at Henrys Radio 404 Edgware Rd. W2

**FREE**  
Catalogue  
send large  
20p SAE

BELLS & HOUSINGS-CAR ALARM-CARAVAN ALARM-CONTACTS

**BURGLAR ALARM**

**EQUIPMENT**

**FOR THE**

**D.I.Y. MAN**



4 HELSTON CLOSE, LINTON,  
BURTON ON TRENT, STAFFS. DE12 6PN  
PHONE: BURTON (0283) 761877  
24 Hour Phone Answering Service

CONTROL PANELS-PRESSURE MATS-SIRENS-WINDOW FOIL-ETC

# MICRO TIMES

19 Mill St., Bideford, North Devon  
EX39 2JR, England (ET1A)  
Telephone Bideford (023 72) 79798

**ORDERING INFORMATION**  
Please add 50p P&P plus 15%  
VAT to all orders.  
EXPORT ORDERS  
Add 15% P&P VAT not  
applicable



ACCESS/BARCLAYCARD  
WELCOME  
Schools, Univ., Official  
Orders welcome.  
All items brand new,  
full spec.

<b>EPROMS</b>		
2708 450s	£2.30	
2716 5v 450ns	£2.30	
2732 Intel type	£6.00	

**NEW ELECTRONIC DRUM KIT**  
6 Programmable rhythms. 5 Instruments: snare,  
hi-hat, tom tom, cymbal, bass drum. Optional  
stereo output £23.95

<b>MEMORIES</b>		
2112 450ns	£1.20	
2114 300ns	£1.20	
TC5514P 450ns	£3.50	
4K Cmos RAM		
11K x 4J		
4116 200ns	£1.20	
4116 150ns	£1.35	
5101	£3.00	
HM6116-3 (116K 150ns)	£8.00	

**RITS FOR BEGINNERS**  
Wheel of Fortune £5.00  
Ultronic Fly Repeller £4.50  
Light Activated Switch £3.75

**ANTEX SOLDERING IRONS**  
Model CX 17W £4.80  
Kit SK 1 15W £6.50  
Incl. Base, stand, solder  
Kit SK 3 17W £6.50  
Kit SK 4 25W £6.50  
MLX Repair Kit £5.30  
Spare Bits, each 60p

**CMOS AND 74LS SERIES**  
AVAILABLE AT COMPETITIVE  
PRICES ON REQUEST

**AY-38910**  
G.I. SOUND COMPUTER CHIP  
Special Price £6.95

**ELECTROWARE**  
DISTRIBUTORS  
Tools, kits, boards, etc.  
Catalogue available.  
Please send 30p P&P

**8809 SINGLE BOARD**  
COMPUTER KIT  
IEEE S-100 STANDARD  
Complete Kit  
Plus 15% VAT £1 P&P  
Bare Board £48  
Uses 8809, 6850, 6821,  
ADSMON (2716) £24  
DATA AVAILABLE ON 8809  
S.A.E. please

**S-100 KLUDGE CARD**  
SIMPLIFY YOUR PROJECT  
WITH A PROTOTYPE  
BREADBOARD WITH EXTRAS!  
Bare Board & Manual £33  
Deliver: 2 weeks

**S-100 PROM BLASTER - NEW**  
PROGRAMS MOST FAMILIES  
OF EPROMS!  
Bareboard £49  
Promwriter £40  
Kit £175  
Incl. all parts, sockets and Prom-  
writer.  
Deliver: 2 weeks

**VERO PRODUCTS**  
VEROBLOC £3.85  
S 100 Prototyping Board:  
Microboard pattern 06-2175L

Sq. ad. Universal Patt. £17.95  
Prototyping Board for Apple  
ITT2020 £9.15  
Other Vero Products available on  
request.

**VOLTAGE** 100mA  
**REGULATORS** 78L05 5v 29p  
78L12 12v 29p  
500mA  
1A  
7805 5v 45p  
7812 12v 50p  
7905 5v 55p  
7912 12v 55p

**TILs**  
Oil sockets 8p  
8 pin 11p  
16 pin 12p  
18 pin 15p  
22 pin 24p  
24 pin 24p  
28 pin 26p  
40 pin 29p

**THYRISTORS** 28p  
Intersil ICL 7560 £2.00  
Volt Converter

<b>LINEAR ICs</b>		
NE555	16p	
NE55	48p	
RC4136	85p	
LM301AN	26p	
LM311P	45p	
LM318	£1.45	
LM324N	42p	
LM339N	40p	
LM339N	40p	
LM348N	64p	
LM358P	38p	
LM390	65p	
LM3300N	£4.00	
LM3314	£2.00	
LM3915	£2.00	
LM13600	£1.20	
LM1871	£1.90	
LM1872	£1.90	
SN75477N	£1.75	
UA709	28p	
LM741	14p	
UA733	68p	
UA747	58p	
UA748	26p	
TL074CN	£1.00	
TL081CP	38p	
TL082CP	56p	
TL084	95p	
KM3025	£1.50	
TL490	85p	
1488	60p	
1489	60p	
8728	£1.35	
8728	£1.35	
8795	£1.35	

**SN78477N** £1.75  
Sound Effects  
Generator  
Data 75p Lge. 26p  
S.A.E.

# Happy Memories

Part type	1 off	25-99	100 up
4116 200ns	.95	.85	.65
4116 250ns	.90	.80	.60
2114 200ns Low power	1.20	1.10	.95
2114 450ns Low power	1.10	1.00	.85
4118 250ns	3.25	2.95	2.65
6116 150ns CMOS	4.95	4.45	3.65
2708 450ns	1.95	1.85	1.75
2716 450ns 5 volt	2.25	2.15	1.95
2716 450ns three rail	6.40	6.00	4.95
2732 450ns Intel type	4.25	3.95	3.35
2532 450ns Texas type	4.25	3.95	3.35

**Z80A-CPU £4.75 Z80A-P10 £4.25 Z80A-CTC £4.25**  
Low profile IC sockets: Pins 8 pp, 14 10p, 16 11p 18 14p,  
20 15p 22 18p, 24 19p, 28 25p, 40 33p  
Soft-secotred floppy discs per 10 in plastic library case:  
5 inch SSD £17.00 5 inch SSDD £19.25 5 inch DSDD £21.00  
8 inch SSD £19.25 8 inch SSDD £23.65 8 inch DSDD £25.50  
74LS series TTL, large stocks at low prices with DIY discounts  
starting at a mix of just 25 pieces. Write or phone for list.  
Please add 30p post & packing to orders under £15 and VAT to  
total.  
Access & Barclaycard welcome 24hr service on (054 422) 618  
Government & Educational orders welcome, £15 minimum  
Trade accounts operated, phone or write for details  
Prices are still tending to drop, phone for a quote before you  
buy

Happy Memories (ETI), Gladestry, Kington,  
Herefordshire HR5 3NY Tel: (054 422) 618 or 628

# ILP TOROIDALS UNBEATABLE VALUE FOR MONEY!

New production capacity at Canterbury has increased our range,  
decreased our prices, improved our special customer  
design service. Choose from toroidal transformers in  
a range of 98 types.



Order using  
the FREEPOST  
coupon below.  
Trade enquiries are welcome.

Supplied with rigid mounting kit with centre bolt  
steel and neoprene washers. GUARANTEED 5 YEARS

TYPE	SERIES	NO.	SECONDARY	RMS	PRICE	PRICE
			VOLTS	CURRENT	EXC. VAT	EX. VAT
110 VA 70 x 30mm 0.45 Kg Regulation 18%	X1000	6+6	2.50	1.78	£4.28	£4.48
		9+9	1.66	1.25	-D 0.87p	+0.87p
		12+12	1.25	0.90		
		15+15	1.00	0.72		
		18+18	0.83	0.60		
		21+21	0.68	0.50		
140 VA 80 x 30mm 0.9 Kg Regulation 13%	X2010	6+6	4.16	2.97	£9.83	£4.93
		9+9	2.77	1.98	£11.10	£11.10
		12+12	2.06	1.48		
		15+15	1.58	1.13		
		18+18	1.00	0.83		
		21+21	0.83	0.68		
180 VA 110 x 30mm 1.3 Kg Regulation 7%	X3010	6+6	6.44	4.51	£16.51	£15.47
		9+9	4.42	3.13	£11.43	£11.43
		12+12	3.33	2.26		
		15+15	2.22	1.61		
		18+18	1.61	1.13		
		21+21	1.30	0.90		
240 VA 140 x 30mm 1.7 Kg Regulation 5%	X4010	6+6	10.00	6.66	£31.55	£28.38
		9+9	6.66	4.42	£11.43	£11.43
		12+12	5.00	3.33		
		15+15	4.00	2.66		
		18+18	3.33	2.22		
		21+21	2.66	1.78		
300 VA 170 x 30mm 2.2 Kg Regulation 3%	X6010	6+6	16.00	10.66	£53.55	£48.38
		9+9	10.66	7.11	£11.43	£11.43
		12+12	8.00	5.33		
		15+15	6.40	4.26		
		18+18	5.33	3.55		
		21+21	4.26	2.84		
360 VA 190 x 30mm 2.7 Kg Regulation 2%	X8010	6+6	20.00	13.33	£66.55	£60.38
		9+9	13.33	8.89	£11.43	£11.43
		12+12	10.00	6.66		
		15+15	8.00	5.33		
		18+18	6.66	4.42		
		21+21	5.33	3.55		
420 VA 210 x 30mm 3.2 Kg Regulation 1%	X10010	6+6	24.00	16.00	£80.55	£73.38
		9+9	16.00	10.66	£11.43	£11.43
		12+12	12.00	8.00		
		15+15	9.60	6.40		
		18+18	8.00	5.33		
		21+21	6.40	4.26		
480 VA 230 x 30mm 3.7 Kg Regulation 0%	X12010	6+6	28.00	18.66	£96.55	£89.38
		9+9	18.66	12.44	£11.43	£11.43
		12+12	14.00	9.33		
		15+15	11.20	7.46		
		18+18	9.33	6.25		
		21+21	7.46	5.04		
540 VA 250 x 30mm 4.2 Kg Regulation 0%	X14010	6+6	32.00	21.33	£112.55	£105.38
		9+9	21.33	14.22	£11.43	£11.43
		12+12	16.00	10.66		
		15+15	12.80	8.53		
		18+18	10.66	7.11		
		21+21	8.53	5.68		
600 VA 270 x 30mm 4.7 Kg Regulation 0%	X16010	6+6	36.00	24.00	£128.55	£121.38
		9+9	24.00	16.00	£11.43	£11.43
		12+12	18.00	12.00		
		15+15	14.40	9.60		
		18+18	12.00	8.00		
		21+21	9.60	6.40		
660 VA 290 x 30mm 5.2 Kg Regulation 0%	X18010	6+6	40.00	26.66	£140.55	£133.38
		9+9	26.66	17.77	£11.43	£11.43
		12+12	20.00	13.33		
		15+15	16.00	10.66		
		18+18	13.33	8.89		
		21+21	10.66	7.11		
720 VA 310 x 30mm 5.7 Kg Regulation 0%	X20010	6+6	44.00	29.33	£152.55	£145.38
		9+9	29.33	19.55	£11.43	£11.43
		12+12	22.00	14.66		
		15+15	17.60	11.73		
		18+18	14.66	9.77		
		21+21	11.73	7.81		
780 VA 330 x 30mm 6.2 Kg Regulation 0%	X22010	6+6	48.00	32.00	£164.55	£157.38
		9+9	32.00	21.33	£11.43	£11.43
		12+12	24.00	16.00		
		15+15	19.20	12.80		
		18+18	16.00	10.66		
		21+21	12.80	8.53		
840 VA 350 x 30mm 6.7 Kg Regulation 0%	X24010	6+6	52.00	34.66	£176.55	£169.38
		9+9	34.66	23.11	£11.43	£11.43
		12+12	26.00	17.33		
		15+15	20.80	13.86		
		18+18	17.33	11.55		
		21+21	13.86	9.22		
900 VA 370 x 30mm 7.2 Kg Regulation 0%	X26010	6+6	56.00	37.33	£190.55	£183.38
		9+9	37.33	24.88	£11.43	£11.43
		12+12	28.00	18.66		
		15+15	22.40	14.93		
		18+18	18.66	12.44		
		21+21	14.93	9.95		
960 VA 390 x 30mm 7.7 Kg Regulation 0%	X28010	6+6	60.00	40.00	£204.55	£197.38
		9+9	40.00	26.66	£11.43	£11.43
		12+12	30.00	20.00		
		15+15	24.00	16.00		
		18+18	20.00	13.33		
		21+21	16.00	10.66		
1020 VA 410 x 30mm 8.2 Kg Regulation 0%	X30010	6+6	64.00	42.66	£218.55	£211.38
		9+9	42.66	28.44	£11.43	£11.43
		12+12	32.00	21.33		
		15+15	25.60	17.00		
		18+18	21.33	14.22		
		21+21	17.00	11.33		
1080 VA 430 x 30mm 8.7 Kg Regulation 0%	X32010	6+6	68.00	45.33	£232.55	£225.38
		9+9	45.33	30.22	£11.43	£11.43
		12+12	36.00	24.00		
		15+15	28.80	19.00		
		18+18	24.00	15.99		
		21+21	19.00	12.99		
1140 VA 450 x 30mm 9.2 Kg Regulation 0%	X34010	6+6	72.00	48.00	£246.55	£239.38
		9+9	48.00	32.00	£11.43	£11.43
		12+12	36.00	24.00		
		15+15	28.80	19.00		
		18+18	24.00	15.99		
		21+21	19.00	12.99		
1200 VA 470 x 30mm 9.7 Kg Regulation 0%	X36010	6+6	76.00	50.66	£260.55	£247.38
		9+9	50.66	33.77	£11.43	£11.43
		12+12	38.0			

# ELECTROMART

**MONTHLY IN ELECTRONICS TODAY — YOUR OWN 'WHERE TO BUY IT' GUIDE**

**LOOKING FOR COMPONENTS! HARDWARE! CASES! TRY YOUR LOCAL LISTED STOCKIST**

**FOR YOUR BUSINESS TO BE INCLUDED, CALL ELECTROMART ON 01-437-1002.**

## BEDFORDSHIRE

### BROADWAY ELECTRONICS

1 The Broadway, Bedford,  
Tel: 0234 213639

Open: 6 days 9-5.30. ½ day Thur.  
lunch 1.30-2.30.  
Specialists in electronic components and  
Acorn computers.

## HAMPSHIRE

### GAINS ELECTRONICS

3, West Street, Fareham.  
Tel: (0329) 234891

Open: 6 days 9am-5.30pm.  
RS component stockist. Wide range of components for  
the enthusiast.

## HERTFORDSHIRE

**GODDARDS COMPONENTS**  
110 London Road, St. Albans.  
Tel: St. Albans 64162

Open: Mon-Sat 9.30am-5.30pm  
(½ day Thur)

**FOR SERVICE AND CONVENIENCE — USE YOUR LOCAL DEALER!**

## S. IRELAND

### peats the world of electronics

25 Parnell St, Dublin 1,  
Tel: Dublin 740662

Open: 6 days 9am-5.30pm  
Components. Computers. Video games.

## LANCASHIRE

**ETESON ELECTRONICS**  
15B Lower Green,  
**E.E.** Poulton-le-Fylde, Blackpool  
Tel: (0253) 885107

Open: 9.30am-12.30. 1.30-5.30. Closed Wed & Sun.  
Electronic Component Specialists

## NOTTINGHAMSHIRE

**DAMON electronics**  
99 Carrington St. Nottingham.  
Tel: 53880 (mail order available)

Open: 6 days 9.30am-5.30pm.  
Specialists in T.V. F.M. aerials.

## TYNE AND WEAR

### AITKEN BROS & CO

35 High Bridge  
Newcastle Upon Tyne.  
Tel: 326729

Open: 9am-5.30pm (Sat 5pm) closed Wed.  
Retail and Wholesale supplied.

## S. WALES

### CARDIGAN ELECTRONICS

Chancery Lane, Cardigan,  
Tel: Cardigan (0239) 614483

Open: Mon-Sat 10am-5pm. Closed Wed.  
Electronic components &  
Acorn computer stockist

## WILTSHIRE

### camlab electronics

27 Faringdon Rd. Swindon  
Tel: (0793) 34917

Open: 6 days 9am-5.30pm  
Specialists in loud speakers. Wide selection: 1¼"-18"

## YORKSHIRE



**ACE MAILTRONIX LTD.**  
3A Commercial Street,  
Batley. Tel: (0924) 441129

Open: Mon-Fri 9am-5.30pm. (Sat 1pm)  
Retail and wholesale.

**PLEASE MENTION ELECTRONICS TODAY WHEN USING THESE SHOPS!**

If you would like your business details to be included in Electromart — please fill in the below coupon and post to: Electromart, Electronics Today International, 145, Charing Cross Road, London WC2H 0EE

Please include my business details in the next available issue of ELECTRONICS TODAY INTERNATIONAL:

BUSINESS NAME: .....

ADDRESS: .....

TEL. NO.: .....

OPENING HOURS: .....

RETAIL  WHOLESALE  MAIL ORDER  (Please tick)

CONTACT: (FOR OFFICE USE ONLY) .....







# COMPUTER WAREHOUSE

NOW OPEN  
MONDAY SATURDAY  
9 30 5 30

**BULK BUY SPECIALS**



### RAM SCOOP

4116 200 NS 8 for £12.95  
4184 200 NS 8 50 each  
2182-650 NS 8 for £5.50  
INC VAT

### 25 WAY "D" CONNECTORS

	50+	100+
25p	1.70	1.10
25s	1.80	1.20
	ALL + VAT	

### WIRE WRAP SKTS.


24 Pin Vero 28p  
14 Pin Gold 22p  
18 Pin Gold 24p  
100 PCS Min Ord.

**C10 DATA CASSETTES**  
10 for £5.75  
Inc. VAT

### RF CONNECTORS

50Ω BNC PLG 60p  
75Ω BNC PLG 60p  
P1250 PLG 40p  
S0230 SKT 35p  
100 PCS MIN ORD.

## TELETYPE ASR33 I/O TERMINALS

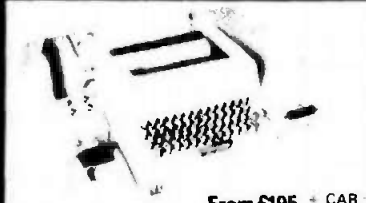


From £195 + CAR + VAT

Fully fledged industry standard ASR33 data terminal. Many features including: ASCII keyboard and printer for data I/O, auto data detect circuitry, RS232C serial interface, 110 baud, 8 bit paper tape punch and reader for off line data preparation and ridiculously cheap and reliable data storage. Supplied in good condition and in working order. Options: Floor stand £12.50 + VAT

KSR33 With 20ma loop interface £125.00 + VAT.  
Sound proof enclosure £25.00 + VAT

## "OLIVETTI TE300" PRINTER/TERMINALS

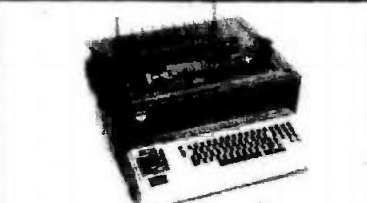

A complete I/O terminal with integral 8 hole paper tape punch and reader, full ASCII keyboard, 120 column printer, and control unit. The printer is capable of 150 baud with a serial TTL or balanced input-output sold in good overall condition but untested. Complete with circuit unguaranteed. Connect direct to your micro at ONLY £99.00 + £11.50 carr + vat

## MPU EXPERIMENTATORS + 5v, 12v, 12v+24v POWER SUPPLY

Once again we are very pleased to offer this superb Power Supply Unit, and hope to satisfy most of our previous customers who were disappointed when we sold out due to demand last time they were advertised!! These units may just have well been made for your lab... they consist of a semi-enclosed chassis measuring 180mm x 120mm x 350mm containing all silicon electronics to give the following fully regulated and short circuit proof outputs of:  
+ 5v @ 2 amps DC  
- 12v @ 800 ma DC  
+ 12v @ 800 ma DC  
+ 24v @ 350 ma DC  
and if that's not enough a fully floating 5v output @ 50 ma DC which may be sensed to give a host of other voltages. All outputs are brought out to the front panel via miniature jack sockets and are also duplicated at the rear on short flying leads. Units accept standard 240v mains input. They are ex GPU and may have minor scratches on the front panels, they are sold untested but in good internal condition. £16.50 each + £2.50 p+p complete with circuit and component list. Transformer guaranteed. HURRY WHILE STOCKS LAST!!

## HIGH SPEED DATA MODEMS

A superb piece of engineering made by SE Labs Ltd. is a "no cost spare" spec for the GPU, the Modem 12 is a synchronous Modem for use on GATEL 2412 services, or other data feeds. Many features include switchable V28 modulation, 2400 baud full duplex, 800/1200 standby, auto answer, 4 wire or 2 wire operation. Self test, LED status indication, CMOS technology, modular construction, original cost over £700 each. Believed brand new, supplied complete with PSU etc.  
£185.00 + £9.50 carriage + VAT.  
\* Permission may be required for connection to PD lines.

## DISTEL ©

"Dial our Database!"  
Get information on 1000's of stock items and order via your computer. 300 baud on 01-689 6800  
18.30 to 0900 6 days a week and all day Sundays. IT'S FREE!

## DIABLO S30 DISK DRIVES

Another shipment allows us to offer you even greater savings on this superb 2.5 MB (formatted) hard disk drive. Two types are available both fully refurbished and electronically identical, the only difference is the convenience of changing the disk packs.

S30 front loader, pack change via front door £550 + vat  
S30 fixed, pack change via removal of top cover £295 + vat  
+ & - 15v PSU for 2 drives £125 + vat  
Carriage & insurance on drives £15.00 + vat fully DEC RK05, NOVA, TEXAS compatible further info on controllers etc on request.

## MAINS FILTERS

Professional type mains filters as used by "Main Frame Manufacturers" ideal for curing those annoying hang ups and data glitches, fit one now and cure your problems! Suppression Devices SD5 A10 5 amp £6.95  
Concom Inc F1900 30 amp £13.95 + pp £1.00

## DC SYSTEM SUPPLY

Professional fully cased fan cooled system supply. Standard 240 V ac Input with the following DC outputs 5V @ 11 amps + 15-17v @ 5amps, 15-17v @ 8 amps and +24v @ 4 amps. All outputs are fully crowbar protected and the 5 volt output is fully regulated. Sold tested and in a new or little used condition complete with circuit £55.00 + carr £8.50 + vat DIM 15.5" x 9" x 6"

## NATIONAL MA1012 LED CLOCK MODULE

★ 12 HOUR  
★ ALARM  
★ 50/60 HZ  
The same module as used in most ALARM/CLOCK radios today, the only difference is our price! All electronics are mounted on a PCB measuring only 3" x 1 1/2" and by addition of a few switches and 5/16 volts AC you have a multi function alarm clock at a fraction of cost. Other features include snooze timer, am, pm, alarm set, power fail indicator, flashing seconds cursor, modulated alarm output etc. Supplied brand new with full data only. Suitable transformer £1.75. £5.25

ELECTRONIC COMPONENTS & EQUIPMENT  
**66% DISCOUNT**

Due to our massive bulk purchasing programme which enables us to bring you the best possible bargains, we have thousands of I.C.'s, Transistors, Relays, Cap's, P.C.B.'s, Sub-assemblies, Switches, etc. etc. surplus to our requirements. Because we don't have sufficient stocks of any one item to include in our ads., we are packing all these items into the "BARGAIN PARCEL OF A LIFETIME!" Thousands of components at giveaway prices! Guaranteed to be worth at least 3 times what you pay plus we always include something from our ads. for unbeatable value!! Sold by weight!

2.5kts £ 4.75 + pp £1.25  
10kts £11.75 + pp £2.25  
5kts £ 6.75 + pp £1.80  
20kts £19.98 + pp £4.75

## THE PRINTER SCOOP OF THE YEAR THE LOGABAX Z80 MICROPROCESSOR CONTROLLED LX180L MATRIX PRINTER

A massive bulk purchase enables us to offer you this superb professional printer at a fraction of its retail cost of over £2000. Utilising the very latest in microprocessor technology, it features a host of facilities with all electronics on one plug in P.C.B. Just study the specification and you will instantly realise it meets all the requirements of the most exacting professional or hobbyist user.

STANDARD FUNCTIONS ★ Full ASCII character set ★ Standard ink ribbon ★ RS232C/24 serial interface - 7 xtal controlled baud rates up to 9600 ★ 194 characters per line ★ Parallel interface ★ Handshakes on serial and parallel ports ★ 4 Type fonts, italic script, double width, italic large, standard ★ Internal buffer ★ Internal self test ★ 170 CPS ★ Variable paper tractor up to 17.5" wide ★ Solid steel construction ★ All software in 2708 eeproms easily reconfigured for custom fonts etc.

All this and more, net refurbished but BRAND NEW At Only **£525 +VAT**

OPTIONAL EXTRAS\* lower case option £25.00 \* 16k buffer £30.00 \* Second tractor for simultaneous dual forms £85.00 \* Floor stand £45.00 \* specialist carriage £19.00 All items plus VAT data sheet on request.

## 8" FLOPPY DISK DRIVES

Unbelievable value the DRE 7100 & 7200 8" disk drives utilise the finest technology to give you 100% bus compatibility with most drives available today, the only difference being our PRICE and the superb manufacturing quality. The 7100 single sided & 7200 double sided drive accept hard or soft sectoring IBM or ANSI standard giving a massive 0.8 MB (7100) & 1.6 MB (7200) of storage. Absolutely SHUGART, BASF, SIEMENS etc compatible. Supplied BRAND NEW with user manual and 90 day warranty.



7100 single sided £225.00 + 9.50 carr + vat  
7200 double sided £295.00 + 9.50 carr + vat  
full technical manual £20.00 alone £9.00 with drive, refund of difference on purchase of drive.  
Data sheet on request.  
SPECIAL new, KODE PSU, drives 2 DRE drives £39.99 + carr + vat  
B" single sided, single or double density diskettes £1.80 each £15.00 for 10 inc. lib case + vat.

## COOLING FAN SPECIAL

Keep your equipment cool and reliable with our range of professional fans.  
ETRI 99XU01 Miniature equipment fan 240 vac working DIM 92 x 92 x 25 mm BRAND NEW complete with finger guard. Makes price £16 our price £10.25  
BUHLER 69.11 22 micro miniature 8-16 vDC reversible fan. Measures only 62 x 62 x 22 mm. Uses a brushless DC servo motor, almost silent running ideal portable equipment. Life in excess of 10,000 hours. BRAND NEW manufacturers price £32.00 our price £13.95  
MUFFIN/CENTAUR cooling fans, tested ex equipment 240v £6.80, 115v £6.60 + p&pp £1.90  
KOOL TRONICS Powerful small type blower gives massive air movement with centrifugal rotor DIM as above 8" x 8" x 6" air apertures 2.5" x 2.6" with flange fixing. BRAND NEW 110v/50 Hz ac working DONLY £9.85 + £1.90 p&pp.

## SOFTY 1 & 2 EPROM BLOWER

Software development system invaluable tool for designers, hobbyists, etc. Enables open heart surgery on 2716, 2708 etc. Blows, copies, reads EPROMs or emulates EPROM/ROM/RAM in situ whilst displaying contents on domestic TV receiver. Many other features. £115 + carr. + VAT. Optional 2716, 2716 Function Card £40 + VAT. PSU £20 + £1.50 carr. + VAT.  
Softy 2 for 2716/2732 £169 + VAT  
Write of phone for more details.

## 9" VIDEO MONITORS

Ex-equipment 9" Motorola Video Monitors 75Ω composite input, tested but unguaranteed. £39.99 + £7.50 carriage + VAT. Complete with circuit.

## SEMICONDUCTOR GRAB BAGS

Mixed Semis amazing value contents include transistors, diodes, linear, i.c.'s, track, diodes, bridge rects, etc. etc. All devices guaranteed brand new full spec with manufacturer's markings, fully guaranteed. 50+ bag £2.95 100+ bag £5.15 TTL 74 Series.  
A massive purchase of an "across the board" range of 74 TTL series I.C.'s enables us to offer 100's mixed "mostly TTL" grab bags at a price which two or three chips in the bag would normally cost to buy.  
Fully guaranteed at I.C.'s full spec. 100+ £8.88 200+ £12.38 300+ £18.68

## RCA FULLY CASED ASCII CODED KEYBOARDS

IDEAL - TANGERINE, OHIO ETC.  
Straight from the U.S.A. made by the world famous R.C.A. Co., the VP600 Series of cased freestanding keyboards meet all requirements of the most exacting user, right down to the price! Utilising the latest in switch technology Guaranteed in excess of 5 million operations. The keyboard has a host of other features including full ASCII 128 character set, user definable keys, upper/lower case, rollover protection, single 5V rail, keyboard impervious to liquids and dust, TTL or CMOS outputs, even an on-board tone generator for keypress feedback, and a 1 year full R.C.A. backed guarantee.  
VP601 7 bit fully coded output with delayed strobe, etc. £43.95  
VP611 Same as VP601 with numeric pad. £54.95  
VP606 Serial, RS232, 20MA and TTL output, with 6 selectable Baud Rates. £64.28  
VP616 Same as VP606, with numeric pad. £84.34  
Plug and cable for VP601, VP611 £2.25  
Pkg for VP606, VP616 £2.10  
Post, Packing and Insurance. £1.95  
ORDER NOW OR SEND FOR DETAILS.

## 5v D.C. POWER SUPPLIES


Following the recent "SELL OUT" demand for our 5v 3 amp P.S.U. we have managed to secure a large quantity of ex-computer systems P.S.U.'s with the following spec.: 240 or 110v A.C. input. Outputs of 5v @ 3-4 amps, 7.2v @ 3 amps and 6.5v @ 1 amp. The 5v and 7.2v outputs are fully regulated and adjustable with variable current limiting on the 5v supply. Unit is self contained on a P.C.B. measuring only 12" x 6" x 3". The 7.2v output is ideal for feeding "on board" regulators or a further 3 amp LM323K regulator to give an effective 5v @ 7 amp supply.  
Supplied complete with circuit at only £10.95 + £1.76 pp. Believed working but untested, unguaranteed.

# ELECTRONICS

Dept. E.T.I., 64-66 Mefford Rd., Thornton Heath, Croydon, Surrey. Tel: 01-889 7702 or 01-889 6800  
MAIL ORDER INFORMATION  
Unless otherwise stated all prices inclusive of V.A.T. Cash with order. Minimum order value £2.00 Prices and Postage quoted for U.K. only. Where post and packing not indicated please add 80p per order. Bona Fide account orders minimum £20.00. Export and trade enquiries welcome. Orders despatched same day where possible. 3% surcharge on Access and Barclaycard orders.
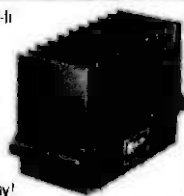
# YOU CAN'T BEAT ILP BIPOLAR POWER AMPS FOR POWER AND PRICE

Get maximum power at minimum price, yet still with hi-fi specifications and a wide choice of outputs. ILP Bipolar power amps, now with or without heatsinks are unbeatable value for domestic hi-fi — but for disco, guitar amplifiers and PA choose the new range of heavy duty power amps, again with or without heatsinks, with protection against permanent short circuit, added safety for the disco or group user. Connection in all cases is simple — via 5 pins.



Every item has a 5 year no quibble guarantee and includes full connection data. So send your order FREEPOST today!

Load impedance, all models: 4 ohm — infinity. Input Impedance, all models: 100k ohm. Input sensitivity, all models: 500 mV. Frequency response, all models: 15Hz-50kHz-3db.

**BIPOLAR Standard, with heatsinks**

Model No	Output Power Watts rms	DISTORTION T.H.D. Typ at 1kHz	I.M.D. 50Hz/7kHz 4:1	Supply voltage Typ/Max	Size mm	Wt gms	Price inc. VAT	Price ex VAT
HY 30	15w/4-8Ω	0.015%	<0.006%	+18+20	76 x 68 x 40	240	£8.28	£7.29
HY 60	30w/4-8Ω	0.015%	<0.006%	+25+30	76 x 68 x 40	240	£9.58	£8.33
HY 120	60w/4-8Ω	0.01%	<0.006%	+35+40	120 x 78 x 40	410	£20.10	£17.48
HY 200	120w/4-8Ω	0.01%	<0.006%	+45+50	120 x 78 x 50	515	£24.39	£21.21
HY 400	240w/4Ω	0.01%	<0.006%	+45+50	120 x 78 x 100	1025	£36.60	£31.83

**BIPOLAR Standard, without heatsinks**

Model No	Output Power Watts rms	DISTORTION T.H.D. Typ at 1kHz	I.M.D. 50Hz/7kHz 4:1	Supply voltage Typ/Max	Size mm	Wt gms	Price inc. VAT	Price ex VAT
HY 120P	60w/4-8Ω	0.01%	<0.006%	+35+40	120 x 26 x 40	215	£17.83	£15.50
HY 200P	120w/4-8Ω	0.01%	<0.006%	+45+50	120 x 26 x 40	215	£21.23	£18.46
HY 400P	240w/4Ω	0.01%	<0.006%	+45+50	120 x 26 x 70	375	£32.58	£28.33

Protection: Load line momentary short circuit (typically 10 sec). Slow rate 15V/μs. Rise time 1μs. S/N ratio 100db. Frequency response (-3dB) 15Hz-50kHz. Input sensitivity 500mV rms. Input impedance 100kΩ. Damping factor (8Ω/100Hz) >400.

**HEAVY DUTY with heatsinks**

Model No	Output Power Watts rms	DISTORTION T.H.D. Typ at 1kHz	I.M.D. 50Hz/7kHz 4:1	Supply voltage Typ/Max	Size mm	Wt gms	Price inc. VAT	Price ex VAT
HD 120	60w/4-8Ω	0.01%	<0.006%	+35+40	120 x 78 x 50	515	£25.85	£22.48
HD 200	120w/4-8Ω	0.01%	<0.006%	+45+50	120 x 78 x 60	620	£31.49	£27.38
HD 400	240w/4Ω	0.01%	<0.006%	+45+50	120 x 78 x 100	1025	£44.42	£38.63

**HEAVY DUTY without heatsinks**

Model No	Output Power Watts rms	DISTORTION T.H.D. Typ at 1kHz	I.M.D. 50Hz/7kHz 4:1	Supply voltage Typ/Max	Size mm	Wt gms	Price inc. VAT	Price ex VAT
HD 120P	60w/4-8Ω	0.01%	<0.006%	+35+40	120 x 26 x 50	265	£22.82	£19.84
HD 200P	120w/4-8Ω	0.01%	<0.006%	+45+50	120 x 26 x 50	265	£27.17	£23.63
HD 400P	240w/4Ω	0.01%	<0.006%	+45+50	120 x 26 x 70	375	£39.42	£34.28

Protection: Load line, PERMANENT SHORT CIRCUIT (ideal for disco/group use should evidence of short circuit not be immediately apparent). The Heavy Duty range can claim additional output power devices and complementary protection circuitry with performance specs as for standard types.

How to order Freepost: Use this coupon, or a separate sheet of paper, to order these products, or any products from other ILP Electronics advertisements. No stamp is needed if you address to Freepost. Cheques and postal orders must be crossed and payable to ILP Electronics Ltd. Cash must be registered. C.O.D. — add £1 to total order value. Access and Barclaycard welcome. All UK orders sent post free within 7 days of receipt of order.

Please send me the following ILP modules

Total purchase price  
 Enclose Cheque  Postal Orders  Int. Money Order

Please debit my Access/Barclaycard No

Name  
 Address

Signature  
 ET 2/4

Post to ILP Electronics Ltd, Freepost 2, Graham Bell House, Roper Close, Canterbury, CT2 7EP, Kent, England. Telephone (0227) 54778. Technical (0227) 64723. Telex 965780.

<b>B.I.L. MINIATURE ON-OFF SWITCHES</b> Gold-plated contacts. Solder-base. Ideal for programming. 6-position at less than half manufacturer's price. <b>ONLY 75p</b> Will fit into 14-pin di socket. Ten at 60p ea.; per 100 80p ea.	<b>HONEYWELL PROXIMITY DETECTOR</b> Integral amplifier. 2v. D.C. £2.99 on PHOTO CONDUCTOR CELL. £1.25. High-power Cds cell, 600mW, for control circuits. Resistance 800 ohm to 8k. Max volts 240. Size 1/2 x 1/2. <b>NARROW MICROPHONE</b> With pre-amp on chassis. £1.75.	<b>MULLARD MODULES</b> LP1171 IF Strip £1.99 LP1179 AM, FM Front end Pair £5.75 Complete with Data LP1186 Med & Long Tuner £3.50 LP1187 varicap & Long Tuner £3.50	<b>ULTRA SONIC TRANSDUCERS</b> 40KCS. Complete on 18-pin. Screened cable. £1.75 each; pairs £2.80. <b>ULTRA SONIC TRANSMITTER</b> Complete unit. Encased requires 15V; £3.25. <b>FOSTER DYNAMIC MICROPHONES</b> 200 ohm impedance. Moving coil. Complete on chassis. £1.75 pair.
<b>U.L.F. MODULATORS</b> Lower type, adjustable. Ideal for computers. With data circuit. Size 1.75 x 1 inch. <b>Only £2.00</b> to external base.	<b>LM309 Amplifier</b> ... 85p <b>LM318N Hi-Slew Op. Amp</b> £1.50 <b>LM323K</b> 5v. 3-amp. reg. £2.80 <b>LM310N Volt. Follower</b> Amp. £1.20 <b>LM311N High Part. Volt. Comparator</b> £1.00 <b>LM324N 5-watt Amp</b> £1.20 <b>LM303N Dual Com.</b> ... 80p <b>7505 Reg.</b> ... 75p	<b>CRYSTALS COLOUR TV</b> <b>QUALITY FANS</b> "Whisper Model" by Roton. Low power consumption. Less than 10 watts! Silent running. 115v. Two in series for 230v. 5060M2. Size 4" x 4" x 1 1/2". <b>Only £8.50 inc. VAT</b> <b>BRAND NEW</b> 5% less than manufacturer's price.	<b>CHIPS</b> 2102 450 n/s £1.00 2114 300 n/s £1.75 4116 200 n/s £1.50 2732 450 n/s £7.50
<b>MINIATURE EDGE MOUNTED</b> with Removable diode. Size 8 1/2. 1.50 with mounting. See 15 x 1 1/2 x 1/2. Only £1.80.	<b>STEREO CASSETTE TAPE HEADS</b> Quality replacement for most all recorders with mounting plate. Record/Replay £2.00 <b>MARRIOTT TAPE HEADS</b> Quarter track. Type XRP518 Record/Replay £2.00 XRP538 Record/Replay (each) £2.00 XES11 Erase (each) £1.00	<b>HEWLETT-PACKARD DISPLAYS</b> <b>5802-7850</b> HIGH EFFICIENCY AND VERY BRIGHT. Only £1.80 each. Set of 6 for £5. Half-inch rad common cathode will replace DL207. 14-pin Di.	<b>EX-MOTOROLA 5+5-WATT CAR STEREO AMPLIFIERS</b> Complete and tested units. Medium and Long Wave. Supplied as two built units (5 x 2 x 2in) with circuit and data. Only £5.00 each. Includes pre-amp.
<b>MOBIANO</b> Half-inch + 1 Display. High Intensity. £1 each. Set of 4 £3.50. Common anode. 14 Pin Di Package.	<b>RECHARGEABLE BATTERIES</b> VARTA 3.6 volts DEAC. £1.50 AAH 25. £1.50 DRYFIT 6-volt 4.5 amp. £7.50	<b>"CHERRY" ADD-ON KEYPAD</b> Compact 12-button keypad suitable for use with Cherry Keyboard to extend its functions plus four extra keys. Supplied brand new with data. A 3 x 4 non-enclosed single mode keyboard.	<b>BRIDGE RECTIFIER</b> 100 VV 25 amp. 1 1/2 x 1 1/2 x 1/2. £2.00
<b>RELAY</b> General purpose. 1/2-6v. single pole changeover. 200 ohms (open type). 1 x 1 x 1 inch. 80p.	<b>MINIATURE M.P.C. POTENTIOMETERS</b> Model M2. High quality. 5% tolerance. 2-watt with lin. spindle. All values. 47 ohms-47k. Only 80p each. per 10; 50p each per 100; 40p each.	<b>XTAL FILTER</b> 10.7mcs. 12.500 separation. 1/2 x 1/2 x 1/2 inch. £1.00 100KCS + 1 meg. 3-pin. £2.00	<b>EX-MOTOROLA 5+5-WATT CAR STEREO AMPLIFIERS</b> Complete and tested units. Medium and Long Wave. Supplied as two built units (5 x 2 x 2in) with circuit and data. Only £5.00 each. Includes pre-amp.

**QUANTITY DISCOUNTS** on ALL items (unless stated). 15% per 10, 20% per 50, 25% per 100. All items **BRAND NEW** (unless otherwise stated). **DELIVERY** from stock — Add Post 35p per order.

**EXPORT enquiries invited.** **TELEX 262284 Transonics Mono 1400**

**Henry's** 01-723 1008/9  
 404 EDGWARE ROAD, LONDON W2 1ED

**PARNDON ELECTRONICS LTD.**  
 Dept. No. 23, 44 Paddock Mead, Harlow, Essex CM18 7BB. Tel. 0279 32700

**RESISTORS:** 1/4 Watt Carbon Film E24 range ± 5% tolerance. High quality resistors made under strictly controlled conditions by automatic machines. Banded/coloured and colour coded.  
 £1.00 per hundred mixed. (Min 10 per value)  
 £8.50 per thousand mixed. (Min 50 per value)  
 Special stock pack 60 values 10 off each £5.50

**DIODES:** IN4148 3p each. Min order quantity — 15 items. £1.60 per hundred.

**DIL SWITCHES:** Gold plated contact in fully sealed case — solve those programming problems.  
 4 Way 86p each. 8 Way £1.00 each. 8 Way £1.20 each.



**DIL SOCKETS:** High quality low profile sockets.  
 8 pin — 10p. 14 pin — 11p. 16 pin — 12p. 18 pin — 13p. 20 pin — 21p. 22 pin — 23p. 24 pin — 25p. 28 pin — 27p. 40 pin — 42p.

**ALL PRICES INCLUDE V.A.T. & POST & PACKING — NO EXTRAS**  
 MIN ORDER — UK £1.00 OVERSEAS £5 CASH WITH ORDER PLEASE



**AUDIO VIDEO SERVICES**  
 19 Gaisworth Avenue, Romford RM6 4PX  
 01 593 6680  
 Mail Order: CWO Please add 40p P&P  
 VAT 15%. Send see for price list

TTL 7400 10p 7402 10p 7403 14p 7404 14p 7407 25p 7409 17p 7410 14p 7413 25p 7414 34p 7416 25p 7420 14p 7428 15p 7438 25p 7441 85p 7442 40p 7447 45p 7451 18p 7454 18p 7473 25p 7474 25p 7486 25p 7490 25p 7492 25p 7493 30p 74107 32p	74109 35p 74121 32p 74123 35p 74141 45p 74151 40p 74153 40p 74157 80p 74180 55p 74181 55p 74182 84p 74184 55p 74174 78p 74175 70p 4025 16p 4027 27p 4029 75p 4040 60p 4046 70p 4049 28p 4050 28p 4051 82p 4052 62p 4053 82p 4056 80p 4060 88p 4066 36p 4069 11p 4081 22p 4082 22p 4511 85p 4518 45p 4520 85p 4543 115p 4565 40p 74LS LS00 12p LS100 54p LS03 18p LS04 15p	LS174 58p LS175 56p LS221 70p LS242 95p LS244 85p LS245 110p LS12 17p LS13 32p LS14 48p LS20 18p LS26 19p LS30 18p LS42 36p LS51 17p LS54 18p LS73 30p LS74 25p LS80 33p LS92 42p LS93 38p LS107 36p LS109 30p LS123 60p LS126 54p LS128 43p LS133 32p LS138 68p LS139 40p LS147 87p LS180 54p LS181 54p LS164 49p	<b>MICROS</b> 2102 105p 2114 145p 4116.3 145p 2708 210p 2718 375p 8080A 400p <b>TRANSISTORS</b> BC107/8 11p BC108 12p BC147/8 5p BC157/8 10p BC182/4 9p BC212/4 9p BCY71/2 22p BD131/2 40p BF194/7 10p BF259 32p BFY51 30p BU206 150p 2N3055 44p <b>OPTO</b> DL704 95p DL707 95p <b>LEDs</b> Green, Red Small 12p Large 15p <b>REGS. TO-220</b> 7805 55p 7812/5 60p 7905/12/5 60p <b>VEROBORDS</b> Copperclad 0.1" 2.5" x 3.75" 73p 2.5" x 5" 83p 3.75" x 3.75" 85p 5" x 3.75" 93p 3.75" x 17" 326p 4.7" x 17" 426p
--	---	---	---


# PCB FOIL PATTERNS

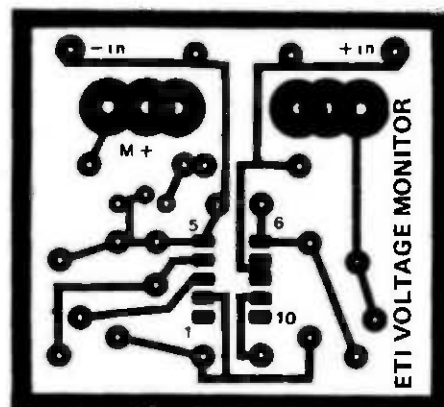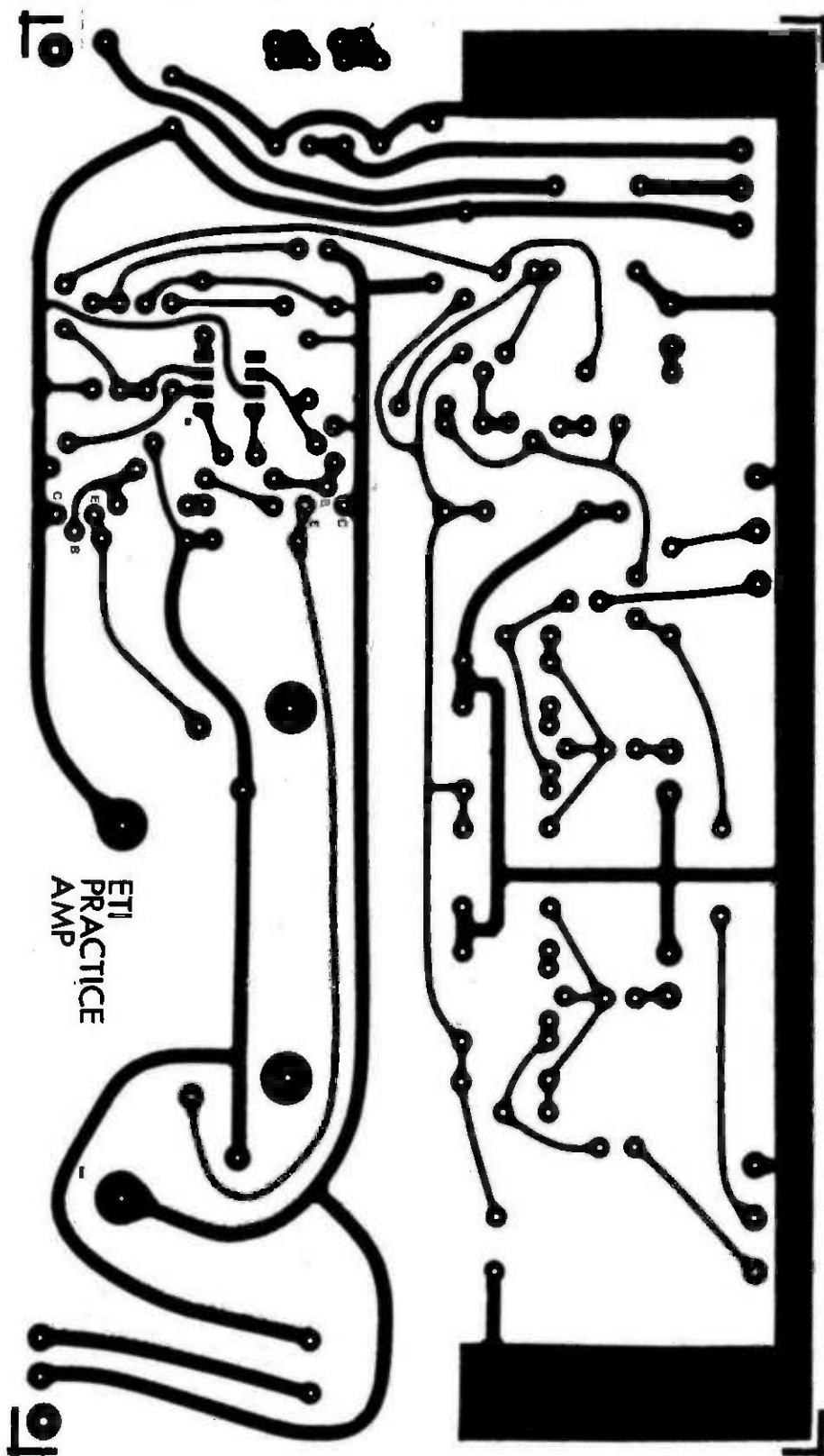

Above: the PCB for the Voltage Monitor.

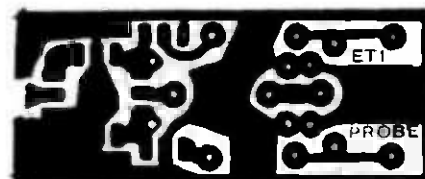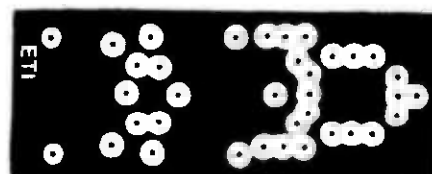

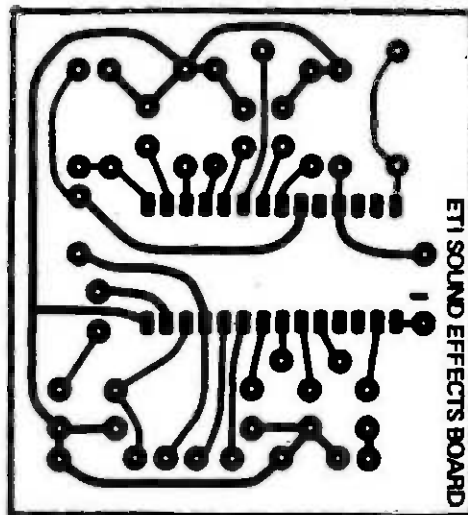Above: the two foils for the double-sided 100 MHz High Impedance Probe PCB.



Above: the board for the two sound effects projects.


Left: the board for the Guitar Practice Amplifier. Please note the alteration to the pad layout for Q6 and Q7.

The Computer Expansion PCBs are the copyright of Watford Electronics and are not reproduced here. Readers wishing to etch their own boards should contact Watford for the foil patterns.




# PCB Foil Patterns


ETI REVERB.

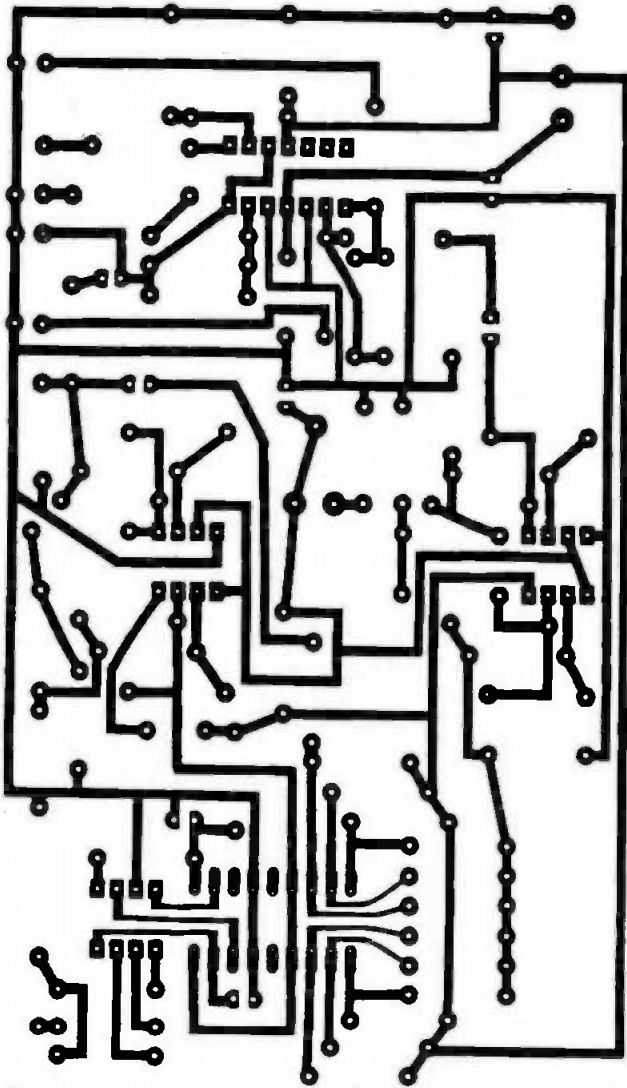

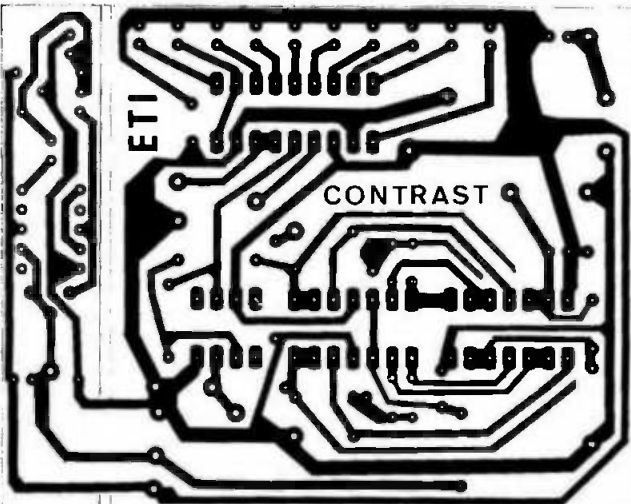Above: the foil pattern for the ETI Solid State Reverb unit. Commercial firms should note that this board is the copyright of Digisound, and may not be reproduced for sale.



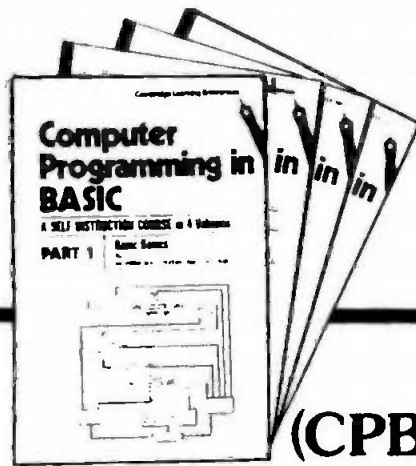Above: the board for the ETI Contrast Meter. You may use the board as it is or cut it in two where marked, as we did.



(CPB)

Microcomputers are here - teach yourself to program! Learn BASIC, the easiest and most widespread language for the small computer. 60 illustrated lessons teach the essentials of good programming: problem definition, coding, flow-charting, debugging and clear documentation. And you don't even need a computer!

**£10.50 inc p&p**

## ZX81 Supplement

When used in conjunction with the above course, it enables you to apply your knowledge to the Sinclair ZX81 microcomputer. It includes some amusing programs to help get you started on the new machine.

50 pence if purchased with CPB,  
75 pence (inc p&p) if purchased alone.

Credit card orders may be phoned through on 0480-67446 (24 hrs).

## Cambridge Learning

Unit 14A Rivermill Site, FREEPOST,  
St Ives, Cambs PE17 4BR England  
VAT No 313026022 Giro No 2789159

All credit cards accepted. Prices include worldwide post and packing (airmail extra - ask for proforma invoice). Overseas customers (inc Eire) should send a bank draft in sterling drawn on a London bank, or quote credit card number. Allow 28 days for delivery in the UK.  
**Guarantee** No risk to you. If you are not completely satisfied, full refund given on return of the item, in good condition, within 28 days.

Please send me:

- Computer Programming in BASIC (CPB) £10.50
- ZX81 Supplement 50p with CPB  
75p alone
- FREE BOOKLIST

I enclose a cheque/PO for £

Or charge my credit card

No. Expire date

Signature

Name

Address

Cambridge Learning Ltd, Unit 14A Rivermill Site,  
FREEPOST, St Ives, Cambs, PE17 4BR, England.  
(Registered in England No 1328762)

# CLASSIFIEDS

## ETI RATES

1-5 Insertions **£10.00** per scc  
 6-11 Insertions **£9.00** per scc  
 12+ Insertions **£8.00** per scc  
 35p per word (min 15 words)  
 Box No. **£2.50**  
 Closing date 1st Friday in month preceding publication

## HE RATES

1-3 Insertions **£8.00** per scc  
 4-11 Insertions **£5.50** per scc  
 12+ Insertions **£5.00** per scc  
 21p per word (min 15 words)  
 Box No. **£2.00**  
 Closing date 2nd Friday in month preceding publication

Classified Advertisements must be prepaid  
 Advertisements are accepted subject to the terms and conditions printed on the advertisement rate card (available on request).

SEND TO:- ETI/HE CLASSIFIED, 145, CHARING CROSS ROAD, LONDON WC2H 0EE. TEL: 01-437 1002 Ext. 50.

## 600 RESISTORS

High quality Carbon Film 1/4W 5% E12 series  
 60 values 10 per value

£5 INCLUDING VAT P&P

### COVE COMPONENTS

58 Southwood Rd., Cove,  
 Fernborough, Hants GU14 6JJ  
 Mail Order only

**CHEAP** hard copy. Teletype 32 ASR 75 Baud, as new, £55. Basidon 22254, around 6pm best.

**TRANSCENDANT 2000** Boxed. Working almost new. Extras, £189. Offers. Misisonic MK2, £129. Phone Bridge 01-735 1862.

## NEW 1982 ACE COMPONENT CATALOGUE

Let your problems be our business. Be certain; have your components delivered quickly and efficiently and get that project working. **Send 30p now** for the easy to use 1982 Catalogue to: Ace Mailtronix, Dept E.T.I. 3A, Commercial Street, Batley, W. Yorks WF17 5HJ.

### MAIL ORDER PROTECTION SCHEME

If you order goods from mail order advertisers in this magazine and pay by post in advance of delivery, this publication *Electronics Today International* will consider you for compensation if the advertiser should become insolvent or bankrupt, provided:

1. You have not received the goods or had your money returned; and

2. You write to the publisher of this publication *Electronics Today International* explaining the position not earlier than 28 days from the day you sent your order and not later than 2 months from that day.

Please do not wait until the last moment to inform us. When you write, we will tell you how to make your claim and what evidence of payment is required.

We guarantee to meet claims from readers made in accordance with the above procedure as soon as possible after the advertiser has been declared bankrupt or insolvent to a limit of £1,800 per annum for any one advertiser, so affected and up to £5,400 p.a. in respect of all insolvent advertisers. Claims may be paid for higher amounts, or when the above procedure has not been complied with, at the discretion of this publication *Electronics Today International* but we do not guarantee to do so in view of the need to set some limit to this commitment and to learn quickly of readers' difficulties.

This guarantee covers only advance payment sent in direct response to an advertisement in this magazine (not, for example, payments made in response to catalogues, etc, received as a result of answering such advertisements): Classified advertisements are excluded.

**PARAPHYSICS JOURNAL** (Russian translations); Psychotronic Generators, Kirlianography, gravity lasers, telekinesis. Details: SAE 4 x 9". Paralab, Downton, Wilts.

**AMAZING ELECTRONICS PLANS.** Lasers, Super-powered Cutting Rifle, Pistol, Light Show, Ultrasonic Force Fields, Pocket Defence Weaponry, Giant Tesla, Satellite TV Pyrotechnics, 150 more projects. Catalogue 95p — From Placentre, 16 Mill Grove, Bilbrook, Codsall, Wolverhampton.

**SECURITY ALARMS** Kits from £37. Full range of accessories. MFP Ltd, Harrison Road, Erdington, Birmingham B24 9AB. 021-373 0450.

**PROXIMITY SENSORS** infra-red range 3 inch single 5-7V supply ideal for mobile robots £21.95 leaflet. Cheshire Micro Design, 66 Close Lane, Alsager, Stoke-on-Trent, Staffs.

**COPPER CLAD BOARD** double sided fibre glass. **10 sheets** 12" x 8" £6.00. **5 sheets** 12" x 8" £4.00. Including P&P. Complete PCB service. Davron, 1 Bank-side, off New Street, Chelmsford.

**CENTURION BURGLAR ALARM EQUIPMENT** Send SAE for free list or a cheque/PO for **£5.95** for our special offer of a full sized decoy bell cover. To Centurion Dept ET1265, Wakefield Rd., Huddersfield W. Yorkshire. **Access & Barclaycard** Telephone orders on 0484-35527.

**CIRCUIT DESIGN**, Prototype construction, analogue or Digital, Single Circuits or Complete Instruments/Systems. Write A. J. ATTWOOD, C.Eng., MIERE, Heathercote, Heatherton Park, Taunton, Somerset, TA4 1ET, or Phone Bradford-on-Tone (082-346) 536.

## DO YOU TRANSMIT AUDIO SIGNALS OVER CABLE CIRCUITS?

We manufacture a full range of interface equipment for transmission of audio signals over private wire of telephone circuits, from Narrow Band STD systems (300Hz-3.4kHz) up to Wide Band Music Circuits.

## PARTRIDGE ELECTRONICS

(A. C. Partridge Ltd.)

56 Fleet Road, Benfleet, Essex  
 Tel: (STD 03745) 3256

We also manufacture audio mixers and sub-assemblies

## RADIATION DETECTORS

BE PREPARED

VIEW THRU LENS



■ THIS DOSIMETER WILL AUTOMATICALLY DETECT GAMMA AND X-RAYS

■ UNIT IS SIZE OF FOUNTAIN PEN & CLIPS ONTO TOP POCKET

■ PRECISION INSTRUMENT METAL CASE WEIGHT 20Z

■ MANUFACTURERS CURRENT PRICE OF A SIMILAR MODEL OVER £25 EACH

British design & manufacture  
 Tested & fully guaranteed  
 Ex-stock delivery

**£6.95** inc VAT  
 Post & Pack 60p

Ideal for the experimenter  
**COMPLETE WITH DATA**


**HENRY'S**

404 EDGWARE ROAD, LONDON W2 1ED


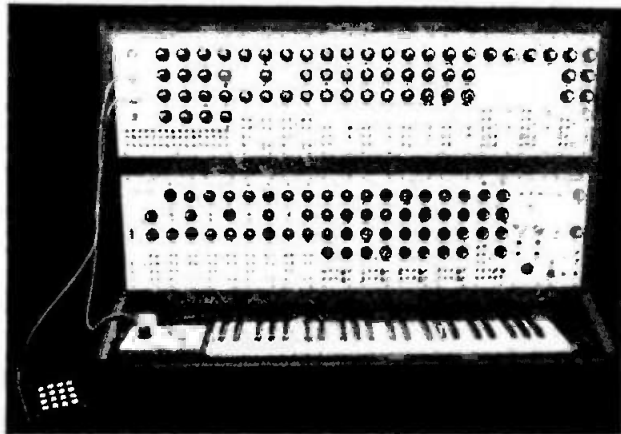
# DIGISOUND 80 MODULAR SYNTHESISER

A synthesiser for the professional and amateur keyboard player, for education and for the beginner. The DIGISOUND 80 suits all levels of keyboard skill. If you want to know how, then read on.



**BEGINNERS:** A small synthesiser may be assembled at a price comparable with pre-set types. The DIGISOUND 80 has unique facilities and you can learn about electronic music synthesis with the aid of our User's Manual. When you are ready to go beyond the 'mini-synth' stage then simply add more modules to suit your requirements and your purse.

**EDUCATION** The modular concept is ideal for teaching both music and the physics of sounds. The micro-processor add-on converts it to a project of even wider application.

**KEYBOARD PLAYERS:** The use of the ALPHADAC 16 microprocessor controller allows up to 16 voices in the polyphonic mode as well as providing many other real time keyboard control routines. NEW recording/composing/sequencing programs provide you with the opportunity to create exciting music — imagine playing back a composition with each voice set to a different instrument!

**KEYBOARD SKILL:** The ALPHADAC programs have facilities for composing and recording in both real time and not real time. The latter allows entry of notes at any speed and subsequent playback at the required tempo. The not real time mode is essential to synthesists of limited skill and a boon to the experienced player.

**THE DIGISOUND 80 — IN ANY CONFIGURATION — OFFERS YOU THE BEST PRICE/PERFORMANCE CHARACTERISTICS**

Kits supplied ex stock and ready built modules, or complete synthesisers, are available to order.

NEW IC's from Curtis electromusic Specialties; NEW modules; NEW users manual plus easy to follow construction notes.

Write or telephone for more information from the ELECTRONIC MUSIC SPECIALISTS:



**DIGISOUND LIMITED**  
13 THE BROOKLANDS, WREA GREEN,  
PRESTON, LANCS. PR4 2NQ  
TEL:0772 683138


# WHY AN ILP MOSFET POWER AMP?

Because ILP MOSFET power amps give you ultra-fi performance without costing big money. Performance you thought you couldn't afford at a price you know you can.

All ILP modules are compatible with each other — you'll find many more in other ILP ads in this magazine. Choose ILP MOSFET power amps when you need the fastest possible slew rate, low distortion at high frequencies, better thermal stability. MOSFET power amps work with complex loads without difficulty and without crossover distortion. Connection is simple — via 5 pins. With other ILP modules you can create almost any audio system, whatever your age or experience.

ILP MOSFET power amps are now available with integral heatsink (no extra heatsink required), or ready for mounting on to your own heatsink or chassis. Full dissipation detail on data sheet, available on request. Each carries a 5 year no quibble guarantee and comes with full connection data.

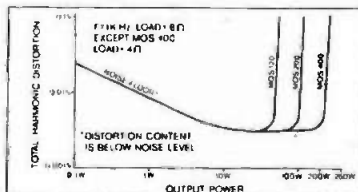Send your order FREEPOST today on the coupon at the foot of this ad



Load impedance, all models, 4 ohm — infinity  
Input impedance, all models 100K ohm  
Input sensitivity, all models, 500 mV  
Frequency response, all models 15Hz-50kHz-3db

## MOSFET Ultra-Fi, with heatsinks

Model No	Output power Watts rms	DISTORTION T.H.D. Typ		Supply voltage Typ/Max	Size mm	Wt gms	Price inc VAT	Price ex. VAT
		1kHz	50kHz/7kHz					
MOS 120	60w/4-8Ω	<0.005%	<0.006%	±45±50	120×78×40	420	£29.76	£25.88
MOS 200	120w/4-8Ω	<0.005%	<0.006%	±55±60	120×78×80	850	£38.48	£33.46
MOS 400	240w/4Ω	<0.005%	<0.006%	±55±60	120×78×100	1025	£52.20	£45.39

## MOSFET Ultra-Fi without heatsinks

Model No	Output power Watts rms	DISTORTION T.H.D. Typ		Supply voltage Typ/Max	Size mm	Wt gms	Price inc VAT	Price ex. VAT
		1kHz	50kHz/7kHz					
MOS 120P	60w/4-8Ω	<0.005%	<0.006%	±45±50	120×26×40	215	£26.82	£23.32
MOS 200P	120w/4-8Ω	<0.005%	<0.006%	±55±60	120×26×80	420	£32.81	£28.53
MOS 400P	240w/4Ω	<0.005%	<0.006%	±55±60	120×26×100	525	£44.75	£38.91

## Protection:

Able to cope with complex loads, without the need for very special protection circuitry (fuses will suffice).

## Ultra-fi specifications:

Slew rate 20V/μs. Rise time 3μs. S/N ratio 100db. Frequency response (-3dB) 15Hz-100kHz. Input sensitivity 500mVrms. Input impedance 100k. Damping factor (8Ω/100Hz) >400.

## How to order Freepost:

Use this coupon, or a separate sheet of paper, to order these products, or any products from other ILP Electronics advertisements. No stamp is needed if you address to Freepost. Cheques and postal orders must be crossed and payable to ILP Electronics Ltd; cash must be registered. C.O.D. — add £1 to total order value. Access and Barclaycard welcome. All UK orders sent post free within 7 days of receipt of order.

Please send me the following  
ILP modules \_\_\_\_\_

Total purchase price \_\_\_\_\_

Enclose Cheque

Postal Orders

Int. Money Order

Please debit my Access/Barclaycard No. \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

Signature \_\_\_\_\_

ET 3/4

Post to: ILP Electronics Ltd, Freepost 2, Graham Bell House, Roper Close, Canterbury CT2 7EP, Kent, England.  
Telephone: (0227) 54778. Technical: (0227) 64723. Telex: 96578Q.



**ILP  
ELECTRONICS LTD**

**STAY AHEAD. STAY WITH US**

## D2114L2

Intersil, ceramic  
200ns Static RAM

Limited	1	8	24
Stock	£1.20	£1.10	£1.05

P&P 40p for RAM under £20

Micro Computer CASSETTE in library box,  
GUARANTEED

<b>C-12</b>	10	25	100
	40p	35p	30p

P&P 40p per 5 cassettes

Please add VAT at 15% to TOTAL

### INTELLIGENT COMPUTING ELECTRONICS

5 Dryden Court, London SE11 4NH  
Tel: 01-735 6408

**DIGISOUND (80)** Modular Synth Cased & Calibrated. Contents: 6 UCO's, 1 LFO, 4 LP Filters, 2 State Variable Filters, 3 Dual UCA's, 2 Dual ADSR's, 2 UC Envelope Generators, 2 Processors, 1 Dual Ring Modulator, 1 Noise/S-hold, 1 UC Mixer, 1 External input, 1 Stereo amp, 1 A per rail PSU, £500.00 ono. Alphasynth Synth Controller 42 Quad DAC Boards, Keyboard & Keyboard Controller £200 ono. Solartron 10 meg Scope £50 ono. All items must go. Owner emigrating. Contact P. Lewis, 50 Acres Lane, Stalybridge, Cheshire.

## The Complete Infra Red Burglar Alarm System

for Domestic & Commercial use

Designed to specifically  
detect body heat and motion



Introductory Offer  
£32.50+VAT  
(including P and P)

Ideal for Caravans  
Yachts  
Shops

FD Kendall & Co  
256 A/B Lewisham High St  
London SE 13

- Piercing alarm
- Horizontal Arming Control
- 9V Battery Powered (Battery not included)
- Normal - Delay - Walk Test Function Switch
- Remote Alarm Terminal Control
- Low Battery Warning Signal
- 9V D.C. Adaptor Socket

### UNREPEATABLE OFFER

Digital Thermometer 5" LED Display, calibrated in degrees C range -50° to +99.9°C with Platinum Resistance Probe. 12v operation. B.C.D. Outputs available housed in A.B.S. DIN styled case, W96 x H48 x D150mm

Give away at £49.95 inc. VAT. (valued at £135.50)  
Mains Adaptor for above unit £5.75 inc. VAT  
P&P £2.50

Circuit Date supplied

Cheques or P.O. with Order to:-

**MICRO ELECTRONIC SYSTEMS**  
Martin Buildings, Stonehouse St.,  
Middlesbrough, Cleveland  
Telephone No. 0642 829238

### MOS-FET AUDIO MODULES

Hitachi devices, Hitachi spec., glass boards, extruded heatsinks, tested, guaranteed 24 months.

120 watts/8 ohms; 120v/2A supply; £13.95.  
240 watts/4 ohms; 120v/4A supply; £19.95.  
400 watts/2 ohms; 120v/7A supply; £29.95.

Power supplies/pre-amps available. Post/packing 80p. Stamp for details. Quantity discount.

**Audio-Tech., 8 Parsons Close, Church Crookham, Aldershot, Hants GU13 0HL.**  
Tel: 02514 22303.

**T. & J. ELECTRONICS COMPONENTS** - Quality components, competitive prices. Illustrated catalogue 45p. 98 Burrow Road, Chigwell, Essex.

**CLOSE ENCOUNTERS GROUP.** Personal introductions/dances, parties, talks, social events. Meet interesting, attractive people. All areas. - Tel. (Liverpool) 051-931 2844 (24 hours).

**SPARE PARTS** For all digital watches. Batteries, crystals, displays etc. Send SAE for full list. Profords, Copnersdrive, Holmergreen, Bucks HP15 6SG.

**ETI International 4600 Synthesiser:** fully working, maplin case and front panel. Immaculate, £450 ono. Colin Jenkins, 6 John Street, Pontrypridd, Treforest, Mid-Glam.

**KEYBOARD,** 74 key, ASCII output, cased, connection diagram, £55; HP keyboard, 107 key, uncoded, only £35; Tektronix 581A Scope, type 82D/B plug in module, probe, manuals £150+Carr. SAE for details, 14 Lechlade Gardens, Fareham, Hants.

**1000 ASSTD 5% resistors,** pre-formed for PCB mounting, £2.50. 50 asstd full-spec LED's, 3 & 5mm, all colours, £3.20. 50 asstd full-spec transistors, BC182/212/237/308 etc £3.00. 100 asstd PC mntg electrolytics, £3.00. One of each pack £11. All post free. SAE Wholesale list. PC Electronics 1, Thornhill, ETI, Romsey Road, Whiteparish, Salisbury, Wilts.

**ONE PCB** by Cemeche gives you ALL the following facilities for your ZX81: fully buffered 8K memory; 8 output - 13 input lines; 8-bit D/A + A/D conversion; wire-wrap area for your own circuits.

Quality fully documented pre-drilled silk-screened fibreglass board. PCB, circuit diagram and example software - £12.95 from **Cemeche Ltd., 136 Cromwell Rd., London SW7.** Access/Barclaycard accepted.

**BURGLAR** alarm equipment. Ring Bradford (0274) 308920 for our catalogue, or call at our large showrooms opposite Odsal Stadium. C.W.A.S. Ltd.

### COLOUR MODULATOR

- R G B inputs, PAL/UHF output
- Unlimited colour combinations
- TTL etc interface details supplied
- 1000's already in use!

KIT: only **£12** Built & Tested: only **£18**

- please add VAT at 15% to all prices  
- Barclay/Access orders accepted by telephone

**WILLIAM STUART SYSTEMS Ltd** Dower House, Billericay Road, Herongate, Brentwood, Essex CM13 3SD  
Telephone Brentwood (0277) 810244

# CCAT

CAMBRIDGESHIRE COLLEGE  
OF ARTS AND TECHNOLOGY

## Courses in Electronics


### BSc IN ELECTRONIC ENGINEERING

A four year part-time degree course for mature students. Of particular interest to those engaged in Digital, Telecommunications or Control Systems. Entry qualification required is an HNC or equivalent in Electrical and Electronic Engineering or Applied Physics. This CNAA degree is considered by the Council of Engineering Institutions as meeting their C.Eng. academic requirements.
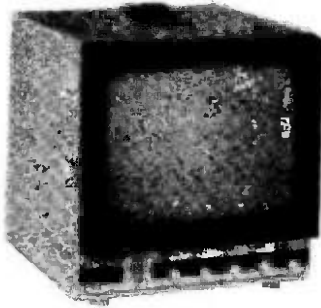
### CEI PART II

One year full-time or two years part-time course in preparation for the CEI Part II examination which is the present academic qualification for Chartered Engineers. Subjects offered include Electronics, Communication, Control and Computer Engineering. Entrants should have passed CEI Part I or have been exempted; holders of HNC and endorsements or HND are so qualified.


Further details and application forms are available from the Information Office, Room 1306, Cambridgeshire College of Arts and Technology, Cambridge, CB1 2AJ. Telephone (0223) 63271.



Metal cased 9" PM101  
**CROFTON  
MONITOR**

10 MHz Bandwidth  
P4 Standard  
Also available with  
P31. Price on  
application.

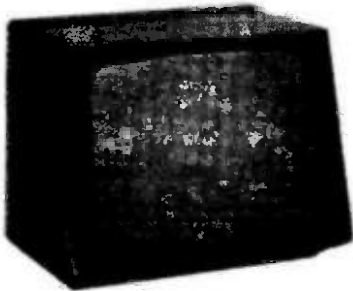Plastic cased 12"  
**NEW-PRINCE MONITOR**



High resolution  
24 MHz Bandwidth  
P31 (green) and P4  
high resolution  
standard. Price on  
application.

Dealer and OEM enquiries welcome

**CROFTON ELECTRONICS LTD**  
35 Grosvenor Road, Twickenham, Middx TW1 4AD  
01-891 1923/1513

## WRONG TIME?

**MSF CLOCK IS ALWAYS CORRECT** — never gains or loses, SELF SETTING at switch-on, 8 digits show Date, Hours, Minutes and Seconds, auto GMT/BST and leap year, can expand to Years, Months, Weekdays and Milliseconds, also parallel BCD output for computer or alarm etc. **STOPCLOCK** and audio to record and show time on playback, receives Rugby 60KHz atomic time signals, built-in antenna, 1000KHz range, **GET THE RIGHT TIME, only £62.80.**

**60KHZ RUGBY RECEIVER**, as in MSF Clock, serial data output for computer etc, decoding details, **£17.90.**

Each fun-to-build kit includes all parts, printed circuit, case, postage etc, instructions, money back assurance so **GET yours NOW**

**CAMBRIDGE KITS**  
45 (TD) Old School Lane, Milton, Cambridge

# ALARMS

## DIY KITS 'N' BITS

PROFESSIONAL EQUIPMENT AT DISCOUNT PRICES!

- KITS £32, £50, £75, £85 including full instructions
- CONTROL PANELS £18, £23, £29, £37
- BELL BOXES £6.25, £7.50
- PRESSURE PADS £1.06, £1.45, £1.95
- 4 CORE CABLE (100m) £8
- SIRENS £7.50
- CONTACTS 72p, 74p, 76p
- ULTRASONICIS £34.50
- DOOR PHONES £49.42

**BUY A KIT OR DESIGN YOUR OWN SYSTEM**

SEND SAE OR PHONE NOW FOR FREE FULLY ILLUSTRATED CATALOGUE.  
IT TELLS YOU ALL YOU NEED TO KNOW!

Carriage included. VAT Extra 15%

A.D. Electronics, 217 Warbeck Moor, Aintree, Liverpool L9 0HV 051 523 8448

Trade Enquiries Welcome


# LOTS OF NEW ILP ENCAPSULATED PRE-AMPS— COMPATIBLE WITH ALL ILP MODULES

Suddenly, instead of two ILP encapsulated pre-amps, there are eight — everything from the simple mono pre-amp (HY6), through mixing mono pre-amps (HY12 and HY69), to a dual stereo pre-amp (HY71). Plus a new guitar pre-amp (HY73).

Each gives the very best reproduction from your equipment that your money can buy, and all are protected against short circuit and wrong polarity.


All ILP modules are compatible with each other — combine them to create almost any audio system. Every item carries a 5 year no quibble guarantee and includes full connection data.

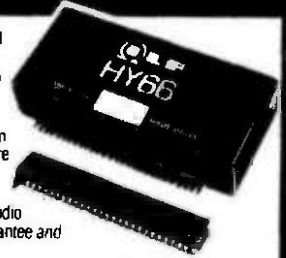So send your order today — the Freepost coupon needs no stamp.



### PRE-AMPS

Model No.	Module	What it does	Current required	Price inc. VAT	Price ex VAT
HY 6	Mono pre-amp	Provides inputs for mic/mag. cartridge/tuner/lape/auxiliary, with volume/bass/treble controls	10 mA	£7.41	£6.44
HY 9	Stereo pre-amp	Two channels: mag. cartridge, mic + volume control	10 mA	£7.71	£6.70
HY 12	Mono pre-amp	Mixes two signals into one, with bass/mid-range/treble controls	10 mA	£7.71	£6.70
HY 66	Stereo pre-amp	Two channels, with inputs for mic/mag. cartridge/lape/tuner/auxiliary, with volume/bass/treble/balance	20 mA	£14.02	£12.19
HY 69	Mono pre-amp	Two input channels: mag. cartridge mic, with mixing and volume/treble/bass controls	20 mA	£12.02	£10.45
HY 71	Dual stereo pre-amp	Provides four channels for mag. cartridge/mic with volume control	20 mA	£12.36	£10.75
HY 73	Guitar pre-amp	Provides for two guitars (bass + lead) and mic with separate volume/bass/treble and mixing	20 mA	£14.09	£12.25
HY 75	Stereo pre-amp	Two channels, each mixing two signals into one with bass/mid-range/treble controls	20 mA	£12.36	£10.75

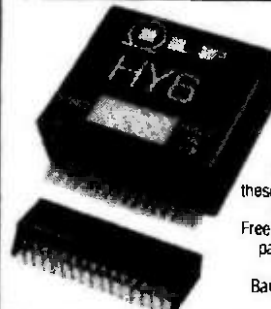

For easy mounting we recommend B 6 mounting board for modules HY6-HY13 £0.90 inc. VAT (0.78 ex VAT.) B 66 mounting board for modules HY66-HY77 £1.12 inc. VAT (0.99 ex VAT.) All modules are encapsulated and include clip on edge connectors. All operate from +15V minimum to +30V maximum, needing dropper resistors for higher voltages. Modules HY6 to HY13 measure 45 x 20 x 40mm. HY66 to HY77 measure 90 x 20 x 40mm.

**How to order Freepost:**  
Use this coupon, or a separate sheet of paper, to order these products, or any products from other ILP Electronics advertisements. No stamp is needed if you address to Freepost. Cheques and postal orders must be crossed and payable to ILP Electronics Ltd; cash must be registered. C. D. D. — add £1 to total order value. Access and Barclaycard welcome. All UK orders sent post free within 7 days of receipt of order.

Please send me the following ILP modules

Total purchase price

Enclose Cheque  Postal Orders  Int. Money Order

Please debit my Access/Barclaycard No.

Name

Address

Signature

ET 4/4

Post to: ILP Electronics Ltd, Freepost 2 Gillingham Bell House, Roper Close, Canterbury CT2 7EP, Kent, England  
Telephone (0227) 54778 Technical (0227) 64723 Telex 965780



**ILP  
ELECTRONICS LTD**

## STAY AHEAD. STAY WITH US

**\* BIG EARS \*** STOP! GO! LEFT! RIGHT!

**SPEECH INPUT FOR ANY COMPUTER**



Hugely successful Speech Recognition System, complete with microphone, software and full instructions.

**BUILT TESTED & GUARANTEED ONLY £49**

PLEASE STATE COMPUTER: UK101, NASCOM2, BBC MICRO, ZX80/81, PET, TRS80, M280K, APPLE II, VIC 20, MICRON

---

**ZX80 ZX81**

**MUSIC SYNTHESISER + 16 LINE CONTROL PORT**



Play 3-part music, sound effects, drums etc. Full control of attack, decay and frequency. Input/Output lines provide control and monitor facility for Home Security, Robot Control, Model Railway, etc etc. Works with or without 16K RAM.

Add keyboard to make a live performance polyphonic synthesiser! Full instructions/software included

**AMAZING VALUE AT ONLY £19.50 (KIT)**

Extra connectors £2.50 BUILT £25.50

---

**COLOUR MODULATOR** KIT £12 BUILT £18

RGB in, PAL/JHF out

---

**UK101/NASCOM COLOUR GRAPHICS** KIT £45 BUILT £60

Inc. Modulator. Still the best selling system!

Please add VAT at 15% to all prices. Barclay/Access orders accepted by telephone.

**WILLIAM STUART SYSTEMS Ltd** Dower House, Billericay Road, Herongate, Brentwood, Essex CM13 3SD. Telephone: Brentwood (0277) 810244

**AERIAL AMPLIFIERS** Improve weak television reception. Price £6.70, S.A.E. for leaflets. Electronic Mailorder, Ramsbottom, Lancashire BL0 9AGH.

**VHR/FM TRANSMITTER KIT.** New IC design means low price and better performance. Smaller than all imitations — ideal bug etc. Receive on domestic radio (VHF 88-106MHz). Instructions etc all included. **Only £1.95+30p P&P.** (Unlicensable). M. Henry, Dept ET1, 30 Westholme Gardens, Ruislip.

**CORDLESS TELEPHONES** Build your own simple and inexpensive units. Send £3.00 for plans to: j. F. Ashley, Birley Grange Cottage Farm, Baslow Road, Cutthorpe, Derbyshire.

'MAGIC' proximity (no metal touchplate), light dimmer kit, replaces domestic lightswitch. Illuminated frontplate. £9.48. Printers: Epson MX80T I £397, MX80F/T I £441. Prices inclusive. Tremorran Data Systems, Torrs Park, Ilfracombe, Devon.

**PRINTED CIRCUITS.** Make your own simply, cheaply and quickly! Golden Fotolac light-sensitive lacquer — now greatly improved and very much faster. Aerosol cans with full instructions, £2.25. Developer 35p. Ferric Chloride 55p. Clear acetate sheet for master 14p. Copper-clad fibreglass board, approx. 1mm thick £1.75 sq. ft. Post/packing 75p. White House Electronics, Castle Drive, Praa Sands, Penzance, Cornwall.

**WANTED** Circuite or service information on Nagard Oscilloscope type DT103 and power supply. Will buy or hire. Tel. evenings or weekends 44063 Cheltenham or write Watton, 245 Prestbury Road, Cheltenham.

**GET THE MESSAGE**

Now you can build your own telephone answering machine for less than £10!

Our advanced and well proven design uses readily available components and connects to any cassette recorder with little or no modification required.

Send only £2.95 for detailed circuit diagrams and construction details. Plans sent First Class return of post.

**UNITECH (MIDLANDS) FREEPOST**  
Sutton Coldfield West Midlands B74 2BR  
(No stamp required)

**IONISER KIT (Mains Operated)**

This negative ion generator gives you the power to saturate your home or office with millions of refreshine ions. Without fans or moving parts it puts out a pleasant breeze. A pure flow of ions pours out like water from a fountain, filling your room. The result? Your air feels fresh, pure, crips and wonderfully refreshing.

All parts, PCB and full instructions ..... **£12.50**  
A suitable case including front panel, neon switch, etc. .... **£10.50**

Price includes post & VAT. Barclaycard/Access welcome

**T. POWELL**  
Advance Works, 44 Wallace Road, London N1 Tel: 01-226 1489  
Hours: Mon-Fri 9-5 pm Sat 9-4.30 pm

**USE ELECTRONICS TODAY INTERNATIONAL'S CLASSIFIED**  
(30p per word, minimum 15 words. Box Nos. £2.00 extra or £9.00 per single column centimetre — all prepaid).

Just write your ad on the form below and send it with your cheque, made payable to A.S.P. Ltd, to Jenny Naraine, 145 Charing Cross Road, London WC2 0EE.

1	2	3	4	5
6	7	8	9	10
11	12	13	14	15

Please place my ad in the next available issue of E.T.I.:


Name .....

Address .....

Tel. No. ....

I enclose my cheque/P.O. for the value of £ .....

1  
9  
8  
2

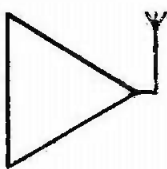

## FINAL RADIO AND ELECTRONICS EXHIBITION AT BELLEVUE

by the  
NORTHERN AMATEUR RADIO SOCIETIES ASSOCIATION  
in the

**LANCASTER HALL  
BELLEVUE, MANCHESTER  
on SUNDAY 4th APRIL 1982**

Doors open at 11 a.m.

### The North's Premier Amateur Radio and Electronics Event

#### Features:

Inter-Club Quiz Grand Raffle Construction Contest Amateur Computer Stands  
R.S.G.B. bookstall Radio Society's Stands and Trophy  
Home Office and Raynet Stands  
The following traders have booked space:

Eurova Ltd  
J. Birketh  
Radiotronics  
Lowe Electronics  
P.M. Electronic Services  
P.K.G. Electronics  
D.S. Electronics  
Thanet Electronics  
Electrovalve Ltd  
Elphan Electronics  
J. Peterson  
Elkan Electronics  
Sutton Electronics  
S.M.C. (Jack Tweedy) Ltd  
Wilson Valves

Amateur Radio Exchange  
The Amateur Radio Shop  
Microwave Modules  
John's Radio  
New Cross Radio  
W.H. Westlake  
Telecom  
Leed Amateur Radio  
Newton Engraving  
Packer Communications  
Micro Print Ltd  
Chris Moulding  
Gemini Communications  
R.S.G.B. Books  
Scorpio Amateur Aerials

Stephens James Ltd  
Isherwood Electronics  
Bredbury Electronics  
Display Electronics  
S.G.S. Electronics  
The Computer Junk Shop  
Arrow Electronics Ltd  
Royd Electronics  
Ace Mailtronix Ltd  
Gemini Electronic  
Components  
Tony's Radios  
J.M.G. Electronics  
Sota Comm. Syst. Ltd  
M.K. Electronics


*Belle Vue has ample car parks*

F.M. Talk in on GR3NRS & G8NRS/A on 145MHz CkS22 R2 R6  
and on 433MHz Chs SU8 RB4 RB14

**ADMISSION 60p BY RAFFLE TICKET AND EXHIBITION PLAN  
ENTER AT REAR OF BELLEVUE OPPOSITE MAIN CAR PARK  
OFF HYDE ROAD A57**
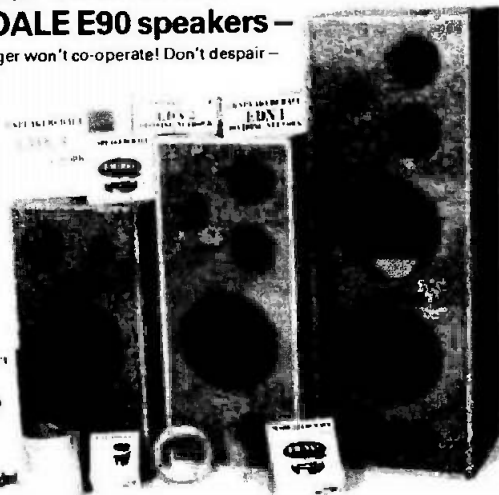
## So you've fancied some WHARFEDALE E90 speakers -

But the bank manager won't co-operate! Don't despair - now there are Wilmslow Audio flat-pack kits for the Wharfedale E50, E70 and E90. A few hours of easy and interesting work will complete your speakers at a very considerable saving on buying 'assembled' E systems.



The kits contain all cabinet components - accurately machined for easy assembly - all drive units, crossover networks, acoustic wadding, reflex port trim, nuts, bolts, terminals, grille fabric, etc. The cabinets can be painted or stained or finished with iron-on veneer. Easy, foolproof assembly instructions are supplied - no electronic or woodworking knowledge necessary.

Prices: E50 kit **£182** per pair including VAT, carriage and insurance £ 8  
E70 kit **£220** per pair including VAT, carriage and insurance £ 8  
E90 kit **£330** per pair including VAT, carriage and insurance £10  
Pro E90 kit **£369** per pair including VAT, carriage and insurance £10

Credit terms available: Deposit 20%, balance over 12 months (charges currently 31.2 APR)



☎  
0625 529599

35/39 Church Street, Wilmslow, Cheshire SK9 1AS



Lightning service on telephoned credit card orders!



# MIXERS, FADERS, VU METER DRIVERS AND MORE - ALL NEW FROM ILP!

Just some of the 28 new amazingly compact modules from ILP Electronics, Britain's leader in electronics modules - you'll find more new products in the amps and pre-amps advertisements.

All ILP modules are compatible with each other - you can combine them to create almost any audio system. Together they form the most exciting and versatile modular assembly system for constructors of all ages and experience.

Every item from ILP carries a 5 year no quibble guarantee and includes full connection data. So send your order on the Freepost coupon below today!

#### MIXERS

Model No.	Module	What it does	Current required	Price inc. VAT	Price ex. VAT
HY 7	Mono mixer	Mixes eight signals into one.	10 mA	£5.92	£5.15
HY 8	Stereo mixer	Two channels, each mixing five signals into one.	10 mA	£7.19	£6.25
HY 11	Mono mixer	Mixes five signals into one - with base/treble controls	10 mA	£8.11	£7.50
HY 68	Stereo mixer	Two channels, each mixing ten signals into one.	20 mA	£9.14	£7.95
HY 74	Stereo mixer	Two channels, each mixing five signals into one - with treble and bass controls	20 mA	£13.17	£11.45

#### AND OTHER EXCITING NEW MODULES

Model No.	Module	What it does	Current required	Price inc. VAT	Price ex. VAT
HY 13	Mono VU meter	Programmable gain/LED overload driver.	10 mA	£6.84	£5.95
HY 67*	Stereo headphone driver	Will drive stereo headphones in the 4 ohm-2K ohm range.	80 mA	£14.20	£12.35
HY 72	Voice operated stereo fader	Provides depth/delay effects.	20 mA	£15.07	£13.10
HY 73	Guitar pre-amp	Handles two guitars (bass and lead) and mic with separate volume/bass/treble and mix.	20 mA	£14.09	£12.25
HY 76	Stereo switch matrix	Provides two channels, each switching one of four signals into one.	20 mA	To be announced	
HY 77	Stereo VU meter driver	Programmable gain/LED overload driver.	20 mA	£10.64	£9.25

For easy mounting we recommend:

B 6 mounting board for modules HY13 - HY13 £0.90 inc. VAT. (0.78 ex. VAT.)  
B 66 mounting board for modules HY66-HY77 £1.12 inc. VAT. (0.99 ex. VAT.)

\*All modules are encapsulated and include clip-on edge connectors. All operate from ±15V minimum to ±30V maximum, needing dropper resistors for higher voltages. HY67 can be used only with the PSU 30 power supply unit. Modules HY6 to HY13 measure 45 x 20 x 40mm. HY66 to HY77 measure 90 x 20 x 40mm.

#### FP 480 BRIDGING UNIT FOR DOUBLING POWER

Designed specially by ILP for use with any two power amplifiers of the same type to double the power output obtained and will function with any ILP power supply. In totally sealed case, size 45 x 50 x 20mm with edge connector. It thus becomes possible to obtain 480 watts rms (single channel) into 8Ω. Contributory distortion less than 0.005%. Price: £5.51 inc. VAT. (Ex. VAT £4.79.)

#### How to order Freepost:

Use this coupon, or a separate sheet of paper, to order these products, or any products from other ILP Electronics advertisements. No stamp is needed if you address to Freepost. Cheques and postal orders must be crossed and payable to ILP Electronics Ltd: cash must be registered. C.O.D. - add £1 to total order value. Access and Barclaycard welcome. All UK orders sent post free within 7 days of receipt of order.

Please send me the following  
ILP modules

Total purchase price \_\_\_\_\_

I enclose Cheque  Postal Orders  Int. Money Order

Please debit my Access/Barclaycard No. \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

Signature \_\_\_\_\_

ET 5/4

Post to: ILP Electronics Ltd, Freepost 2, Graham Bell House, Ropey Close,  
Canterbury CT2 7EP, Kent, England.  
Telephone (0227) 54778 Technical (0227) 64723 Telex 965780



**ILP  
ELECTRONICS LTD**

HE 5/3

# STAY AHEAD. STAY WITH US

Don't miss  
the May issue  
of E.T.I.  
Phone Jennie  
on  
01-437 1002  
for all your  
classified advertising  
requirements  
Deadline Friday  
March 5th

From the Publishers of E.T.I.

**CIRCUITS**

**No. 1 and No. 2**

A series of idea books for experimenters which uses such sources as Tech-Tips, the popular E.T.I. column, to produce these invaluable experimental source books.

Contents include: (No. 1) alarms, amplifiers, converters, rectifiers, signal generators, filters, currents, low voltages, zeners, diodes, crystals, batteries, etc. (No. 2) automobiles, comparators, conversion tables, crossovers, detectors, indicators, logic data, mixers, special effects, switching, etc.

Send £1.90 per book (inclusive of p&pt) to ARGUS SPECIALIST PUBLICATIONS, 17A5 Charing Cross Road, London WC2H 0BE. Please indicate which circuit book(s) you want!

**It's easy  
to complain  
about  
advertisements.**

The Advertising Standards Authority. ✓  
If an advertisement is wrong, we're here to put it right.  
A.S.A. Ltd., Brook House, Torrington Place, London WC1E 7HN.

Please  
mention  
**E.T.I.**  
when replying  
to all  
adverts

**RADIATION DETECTORS**

**BE PREPARED** VIEW THRU LENS ▶

Ideal for the experimenter

- THIS DOSIMETER WILL AUTOMATICALLY DETECT GAMMA AND X-RAYS
- UNIT IS SIZE OF FOUNTAIN PEN & CLIPS ONTO TOP POCKET
- PRECISION INSTRUMENT
- MANUFACTURERS CURRENT PRICE OF A SIMILAR MODEL OVER £25 EACH

British design & manufacture  
Tested and fully guaranteed. Ex-stock delivery.

**HENRY'S** 01-723 1008/9  
404 EDGWARE ROAD, LONDON W2 1ED

FREE RECHARGE SERVICE AFTER PURCHASE  
**£6.95**  
inc. VAT Post & Pack 60p  
COMPLETE WITH DATA




# LECTRO-LINES

101 Hainault Road, Romford, Essex RM5 3HF.  
Tel. Romford 22018/9

**SPECIAL OFFER**

## AM/FM STEREO TUNER MODULE 3 BAND

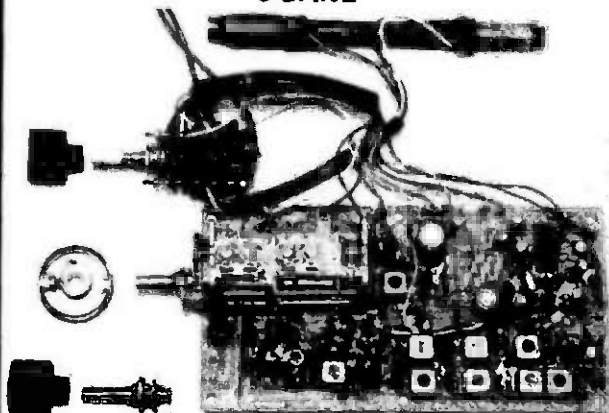

New boxed pre-aligned and tested. Complete with ferrite rod aerial, 6 way function switch, drive drum, cord drive, knobs, sample calibration scale and circuit diagram.


3 stage FM tuning, phase lock loop decoder, L.E.D. stereo indicator, FM sensitivity 4 uV.

**Wavebands** FM 88-108 MHz, LW 160-280 KHz,  
MW 525-1650 KHz.

Output approximately 200 mV. Input 12v DC.

**Price only £10.95 including VAT**  
plus £1.70 P & P

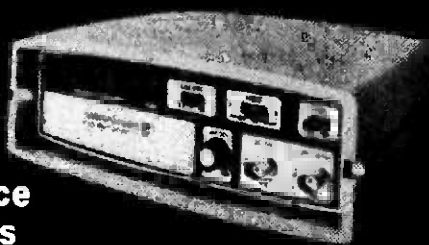**An entire  
range of  
low-cost  
high-  
performance  
instruments**



**sabtronics**

**'Making Performance Affordable'**

- |  |   |
|--|---|
| *2010A 3½-Digit L.E.D. Bench DMM                               | 5020A 1Hz-200KHz Function Generator             |
| *2015A 3½-Digit L.C.D. Bench DMM                               | *8110A 100MHz 8-Digit Frequency Meter           |
| 2020 3½-Digit L.E.D. Bench DMM<br>with Microcomputer Interface | *8810A 600MHz 8-Digit Frequency Meter           |
| 2033 3½-Digit L.C.D. Hand DMM                                  | *8810B 600MHz 9-Digit Frequency Meter           |
| *2035A 3½-Digit L.C.D. Hand DMM                                | 8000B 1GHz 9-Digit Frequency Meter              |
| *2037A 3½-Digit L.C.D. Hand DMM<br>with Temp.                  | 8700 10MHz Universal Frequency<br>Counter/Timer |
| LP-10 10MHz Logic Probe  | PSC-65 600MHz Prescaler                         |
|  | 9005 5MHz Single Trace Oscilloscope             |
- \* Also available in kit form.

Test our low priced test equipment. It measures up to the best. Compare our specs and our prices - no-one can beat our price/performance ratio.

Full colour illustrated  
brochure and price list from:  
**BLACK STAR LTD.**,  
9a Crown Street, St. Ives,  
Cambs. PE17 4EB  
Tel: (0480) 62440. Telex 32339



# ILP POWER SUPPLIES- MOST WITH ILP TOROIDAL TRANSFORMERS

Space-saving, efficient ILP power supplies are designed to give you flexibility in planning audio assemblies. Nine of the eleven models have toroidal transformers manufactured on new cost-efficient high technology machines in our own factory. So we keep the quality up, and the price down.

ILP power supplies are compatible with all other ILP modules — combine them to produce almost any audio system. All carry the ILP 5 year no quibble guarantee and include full connection data.

So send your order on the Freepost coupon below today!



### POWER SUPPLY UNITS

Model No	For use with	Price inc VAT	Price ex VAT
PSU 30	±15V combinations of HY6/66 series to a maximum of 100 mA or one HY67.	£5.18	£4.50
	The following will also drive the HY6/66 series except HY67 which requires the PSU 30.		
PSU 36	1 or 2 HY 30	£9.32	£8.10
PSU 50	1 or 2 HY 60	£12.58	£10.94
PSU 60	1 x HY 120/HY 120P/HD 120/HD 120P.	£15.00	£13.04
PSU 65	1 x MOS 120/1 x MOS 120P	£15.32	£13.32
PSU 70	1 or 2 HY 120/HY 120P/HD 120/HD 120P.	£18.31	£15.92
PSU 75	1 or 2 MOS 120/MOS 120P.	£18.63	£16.20
PSU 90	1 x HY 200/HY 200P/HD 200/HD 200P	£18.63	£16.20
PSU 95	1 x MOS 200/MOS 200P.	£18.77	£16.32
PSU 180	2 x HY 200/HY 200P/HD 200/HD 200P or 1 x HY 400/1 x HY 400P/HD 400/HD 400P.	£24.54	£21.34
PSU 185	1 or 2 MOS 200/MOS 200P/1 x MOS 400 1 x MOS 400P.	£24.68	£21.46

All models incorporate ILP toroidal transformers except PSU 30 and PSU 36 which include our own laminated transformers.

#### How to order Freepost:

Use this coupon, or a separate sheet of paper, to order these modules, or any products from other ILP Electronics advertisements. No stamp is needed if you address to Freepost. Cheques and postal orders must be crossed and payable to ILP Electronics Ltd; cash must be registered. C.O.D. — add £1 to total order value. Access and Barclaycard welcome. All UK orders sent post free within 7 days of receipt of order.

Please send me the following  
ILP modules

Total purchase price

Enclose Cheque  Postal Orders  Int. Money Order

Please debit my Access/Barclaycard No.

Name

Address

Signature

ET 6/4

Post to: ILP Electronics Ltd, Freepost 2, Graham Bell House, Roper Close,  
Canterbury CT2 7EP, Kent, England.  
Telephone (0227) 54778. Technical (0227) 64723. Telex 965780



**STAY AHEAD. STAY WITH US**

# TRAIN FOR SUCCESS

in Radio, Television & Electronics

ICS have helped thousands of ambitious people to move up into higher paid more secure jobs in the field of electronics - now it can be your turn. Whether you are a newcomer to the field or already working in the industry, ICS can provide you with the specialised training so essential to success.

## Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful, is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

## City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

Telecommunications Technicians  
Radio, T.V. Electronics Technicians  
Radio Amateurs  
Electrical Installation Work

## Diploma Courses

Colour T.V. Servicing  
CCTV Engineering  
Electronic Engineering & Maintenance  
Computer Engineering and Programming  
Radio, T.V. and Audio, Engineering & Servicing  
Electrical Engineering, Installations, & Contracting

## Other Career Courses

A wide range of other technical and professional courses are available including GCE.

To ICS, Dept. T265, Intertext House,  
London SW8 4UU

Name \_\_\_\_\_

Address \_\_\_\_\_

Age \_\_\_\_\_

**ICS**

To ICS, Dept. T265, Intertext House,  
London SW8 4UU  
or telephone 01-622 9911 (all hours)

## AD INDEX

A.d. Electronics	141
Ambit International	86 & 100
Amtron (UK) Ltd	47
Audio Electronics	38, 66 & 130
Audio Video Services	135
Aura Sounds	22
Bi-Pak Semiconductors	42 & 43
BK Electronics	16 & 61
Black Star Ltd	145
B.N.R.S.	62
Boss Industrial Mouldings	119
Braithwaite Kits	116
Calculator Sales & Service	32
Cambridge Kits	141
Cambridge Learning	91 & 124
Castle Electronics	8
Chiltmead Ltd	128
Clef Products	112
Cricklewood Electronics	98 & 99
Crimson Components	129
Crimson Elektrik	14
Crofton Electronics	141
C.T. Electronics Ltd	92 & 93
Delta Techn & Co.	128
Digisound Ltd	139
Display Electronics	134
E.D.A.	71
Electronize Design	105
Electro Supplies	120
Electrovalue	78
Flight Electronics	126 & 127
Greenbank	110
Greenweld	81
Happy Memories	131
Health Electronics	119
Henry's Radio	135
Hy-Tek	87
ILP	131, 135, 139, 141, 143 & 145
LB Electronics	106 & 111
L & B Electronics	112
Lectro Lines	145
LEM Services	54
Linton Electronics	130
Magenta Electronics	106
Mawson Associates	125
Memotech Ltd	10
Micro Times	131
Midwich Computer Co.	30
Namal Associates	116
N.A.R.S.A.	143
Parndon Electronics	135
Powertran Electronics	2, 107 & 148
Rapid Electronics	12
Radditch Electronics	77 & 130
Relay-A-Quip	97
J. W. Rimmer	34
Riscomp Ltd	55
Roadrunner Electronics	120
R.T.V.C.	60
Silica Shop	72
Silicon Speech Systems	54
Sinclair Research	6, 7 & 147
Solid State Security	125
Swanley Electronics	61
Swift of Wilmslow	47
Technology Resources	124
Technomatic Ltd	56 & 83
Tempus Ltd	52 & 53
Timedata Ltd	120
TK Electronics	48 & 49
Velleman (UK) Ltd	25
Videotone Ltd	129 & 133
Watford Electronics	4 & 5
West Hyde Developments	125
Wilmslow Audio	143

# Make the most of your Sinclair ZX Computer...

# Sinclair ZX software on cassette.

## £3.<sup>95</sup> per cassette.



The unprecedented popularity of the ZX Series of Sinclair Personal Computers has generated a large volume of programs written by users.

Sinclair has undertaken to publish the most elegant of these on pre-recorded cassettes. Each program is carefully vetted for interest and quality, and then grouped with other programs to form a single-subject cassette.

Each cassette costs £3.95 (including VAT and p&p) and comes complete with full instructions.

Although primarily designed for the Sinclair ZX81, many of the cassettes are suitable for running on a Sinclair ZX80 - if fitted with a replacement 8K BASIC ROM.

Some of the more elaborate programs can be run only on a Sinclair ZX Personal Computer augmented by a 16K-byte add-on RAM pack.

This RAM pack and the replacement ROM are described below. And the description of each cassette makes it clear what hardware is required.

### 8K BASIC ROM

The 8K BASIC ROM used in the ZX81 is available to ZX80 owners as a drop-in replacement chip. With the exception of animated graphics, all the advanced features of the ZX81 are now available on a ZX80 - including the ability to run much of the Sinclair ZX Software.

The ROM chip comes with a new keyboard template, which can be overlaid on the existing keyboard in minutes, and a new operating manual.

### 16K-BYTE RAM pack

The 16K-byte RAM pack provides 16-times more memory in one complete module. Compatible with the ZX81 and the ZX80, it can be used for program storage or as a database.

The RAM pack simply plugs into the existing expansion port on the rear of a Sinclair ZX Personal Computer.



### Cassette 1 - Games

For ZX81 (and ZX80 with 8K BASIC ROM)

**ORBIT** - your space craft's mission is to pick up a very valuable cargo that's in orbit around a star.

**SNIPER** - you're surrounded by 40 of the enemy. How quickly can you spot and shoot them when they appear?

**METEORS** - your starship is cruising through space when you meet a meteor storm. How long can you dodge the deadly danger?

**LIFE** - J. H. Conway's 'Game of Life' has achieved tremendous popularity in the computing world. Study the life, death and evolution patterns of cells.

**WOLFPACK** - your naval destroyer is on a submarine hunt. The depth charges are armed, but must be fired with precision.

**GOLF** - what's your handicap? It's a tricky course but you control the strength of your shots.

### Cassette 2 - Junior Education: 7-11-year-olds

For ZX81 with 16K RAM pack

**CRASH** - simple addition - with the added attraction of a car crash if you get it wrong.

**MULTIPLY** - long multiplication with five levels of difficulty. If the answer's wrong - the solution is explained.

**TRAIN** - multiplication tests against the computer. The winner's train reaches the station first.

**FRACTIONS** - fractions explained at three levels of difficulty. A ten-question test completes the program.

**ADDSUB** - addition and subtraction with three levels of difficulty. Again, wrong answers are followed by an explanation.

**DIVISION** - with five levels of difficulty. Mistakes are explained graphically, and a running score is displayed.

**SPELLING** - up to 500 words over five levels of difficulty. You can even change the words yourself.

### Cassette 3 - Business and Household

For ZX81 (and ZX80 with 8K BASIC ROM) with 16K RAM pack

**TELEPHONE** - set up your own computerised telephone directory and address book. Changes, additions and deletions of up to 50 entries are easy.

**NOTE PAD** - a powerful, easy-to-run system for storing and

retrieving everyday information. Use it as a diary, a catalogue, a reminder system, or a directory.

**BANK ACCOUNT** - a sophisticated financial recording system with comprehensive documentation. Use it at home to keep track of 'where the money goes,' and at work for expenses, departmental budgets, etc.

### Cassette 4 - Games

For ZX81 (and ZX80 with 8K BASIC ROM) and 16K RAM pack

**LUNAR LANDING** - bring the lunar module down from orbit to a soft landing. You control attitude and orbital direction - but watch the fuel gauge! The screen displays your flight status - digitally and graphically.

**TWENTYONE** - a dice version of Blackjack.

**COMBAT** - you're on a suicide space mission. You have only 12 missiles but the aliens have unlimited strength. Can you take 12 of them with you?

**SUBSTRIKE** - on patrol, your frigate detects a pack of 10 enemy subs. Can you depth-charge them before they torpedo you?

**CODEBREAKER** - the computer thinks of a 4-digit number which you have to guess in up to 10 tries. The logical approach is best!

**MAYDAY** - in answer to a distress call, you've narrowed down the search area to 343 cubic kilometers of deep space. Can you find the astronaut before his life-support system fails in 10 hours time?

### Cassette 5 - Junior Education: 9-11-year-olds

For ZX81 (and ZX80 with 8K BASIC ROM)

**MATHS** - tests arithmetic with three levels of difficulty, and gives your score out of 10.

**BALANCE** - tests understanding of levers/fulcrum theory with a series of graphic examples.

**VOLUMES** - 'yes' or 'no' answers from the computer to a series of cube volume calculations.

**AVERAGES** - what's the average height of your class? The average shoe size of your family? The average pocket money of your friends? The computer plots a bar chart, and distinguishes MEAN from MEDIAN.

**BASES** - convert from decimal (base 10) to other bases of your choice in the range 2 to 9.

**TEMP** - Volumes, temperatures - and their combinations.

### How to order

Simply use the order form below, and either enclose a cheque or give us the number of your Access, Barclaycard or Trustcard account. Please allow 28 days for delivery. 14-day money-back option.

## Sinclair ZX SOFTWARE

Sinclair Research Ltd,  
6 Kings Parade, Cambridge,  
Cambs., CB2 1SN. Tel: 0276 66104.

To: Sinclair Research, FREEPOST, Camberley, Surrey, GU15 3BR. Please print  
Please send me the items I have indicated below.

Qty	Code	Item	Item price	Total
	21	Cassette 1 - Games	£3.95	
	22	Cassette 2 - Junior Education	£3.95	
	23	Cassette 3 - Business and Household	£3.95	
	24	Cassette 4 - Games	£3.95	
	25	Cassette 5 - Junior Education	£3.95	
	17	*8K BASIC ROM for ZX80	£19.95	
	18	*16K RAM pack for ZX81 and ZX80	£49.95	
		*Post and packing (if applicable)	£2.95	
			Total £	

\*Please add £2.95 to total order value only if ordering ROM and/or RAM.

I enclose a cheque/PO to Sinclair Research Ltd for £

Please charge my Access\*/Barclaycard/Trustcard no.

\*Please delete as applicable.

Name: Mr/Mrs/Miss

Address:

# PRECISION - by POWERTRAN

THE FIRST WORDS AND THE LAST WORD IN ELECTRONIC KITS

For more than eleven years Powertran have been designing and manufacturing the finest quality electronic kits. All of our now considerable range have featured in the electronics press and literally thousands have been bought and built by contractors in the UK and World-wide.

Our philosophy is always the same — we offer ingenuity and originality in the construction phase by using only top class designers. We offer machines with power, versatility and performance — capability fully equal to their factory built rivals. We offer only the highest quality materials and components throughout to ensure years of useful and reliable service, we offer clear comprehensive and easy to follow construction manuals to place our kits within the scope of the careful first time builder as well as the dedicated enthusiast.

Our hallmark of success lies in the number of our clients who have built our whole range — many assembling several units for others to use often on the professional music scene.

We believe in taking every care throughout — months spent checking and testing the design and development. Vigorous checking of every component, constant pre-despatch quality control, careful packaging... even door to door delivery by Securicor!

We are naturally very proud of our Transcendent range of synthesizers designed by Tim Orr and regularly featured in ETI. They represent the best in constructional interest and in musical performance.

**TRANSCENDENT POLYSYNTH** — A four octave polyphonic synthesiser with outstanding design characteristics and versatility and performance to match.  
Complete kit £275.00 plus VAT (single voice).  
Extra voice (up to three more) 42.00 plus VAT.

**EXPANDER** — A new matching 4 voice expander to team up with your polysynth for even a greater range and capability.  
Complete kit £249.00 plus VAT.

**TRANSCENDENT DPX** — Offers a five octave keyboard with power to match. Two audio outputs (can be used simultaneously) to give harpsichord and piano/honkytonk or reed with strings/brass and both are fully polyphonic. Other features include switchable touch sensitivity and a chorus ensemble unit with strong/mild effect switching. An advanced design made simple with our clearly laid out instruction manual.  
Complete kit £295.00 plus VAT.

**TRANSCENDENT 2000** — Although only a 3 octave keyboard the '2000' features the same design ingenuity, careful engineering and quality components of its larger brethren. The kit is well within the scope of the first time builder — buy it, build it... play it! You will know you have made the right choice.  
Complete kit £165.00 plus VAT.

**1024 COMPOSER** — Come right up to the minute with this new design. It will control your synthesiser with a sequence of up to 1024 notes — or an equal selection of shorter sequences. The Composer is mains powered with automatically charged battery to preserve your programme after switch-off.  
Complete kit £85.00 plus VAT.

**DEMONSTRATION TAPE** — Demonstration tape now available of all three kits (30 minutes).  
£2.00



**T20 + 20** — Originally designed by Texas Engineers. This is a 20 watt amplifier with true Hi-Fi performance at a minimal cost. New features include true Toroidal transformer, new wiring, single circuit board and improved presentation. An ideal beginners project. Complete kit £29.50 plus VAT. Also T30 + 30 — 30 watt version complete kit £34.50 plus VAT.

**LINSLEY HOOD 75 DE LUXE** — A 75 watt amplifier originally published in Hi-Fi News. Superb performance characteristics with less than .01% distortion. Modular construction with 14 interconnecting boards — virtually no wiring so assembly is easy as is subsequent checking and maintenance. Complete kit £75.00 plus VAT.

... Quite simply the best way to make music



## WORLD LEADERS IN ELECTRONIC KITS.

**PRICE STABILITY:** Order with confidence irrespective of any price changes we will honour all prices in this advertisement until the end of the month following the month of publication of this issue. (Errors and VAT rate changes excluded).  
**EXPORT ORDERS:** No VAT. Postage charged at actual cost plus £1 handling and documentation.  
**U.K. ORDERS:** Subject to 15% surcharge for VAT. No charge is made for carriage, or at current rate if changed. Cheques, Access, Barclaycard accepted.  
**SECURICOR DELIVERY:** For this optional service (U.K. mainland only) add £2.50 (VAT inclusive) per kit. **FREE ON ORDERS OVER £100.**  
**SALES COUNTER:** If you prefer to collect kit from the factory, call at Sales Counter. Open 9a.m - 12 noon, 1-4.30p.m. Monday-Thursday.

PORTWAY INDUSTRIAL ESTATE, ANDOVER, HANTS SP10 3WW (0264) 64455.

Order by phone  
0264 64455  
or telephone us with your order and  
quote your Access or Barclaycard number  
40 page catalogue free — contains  
full details of all our kits.