


electronics today

INTERNATIONAL

DECEMBER 1984 99p

RESTRAIN YOUR DIGITS!

Digital delay line for musical effects

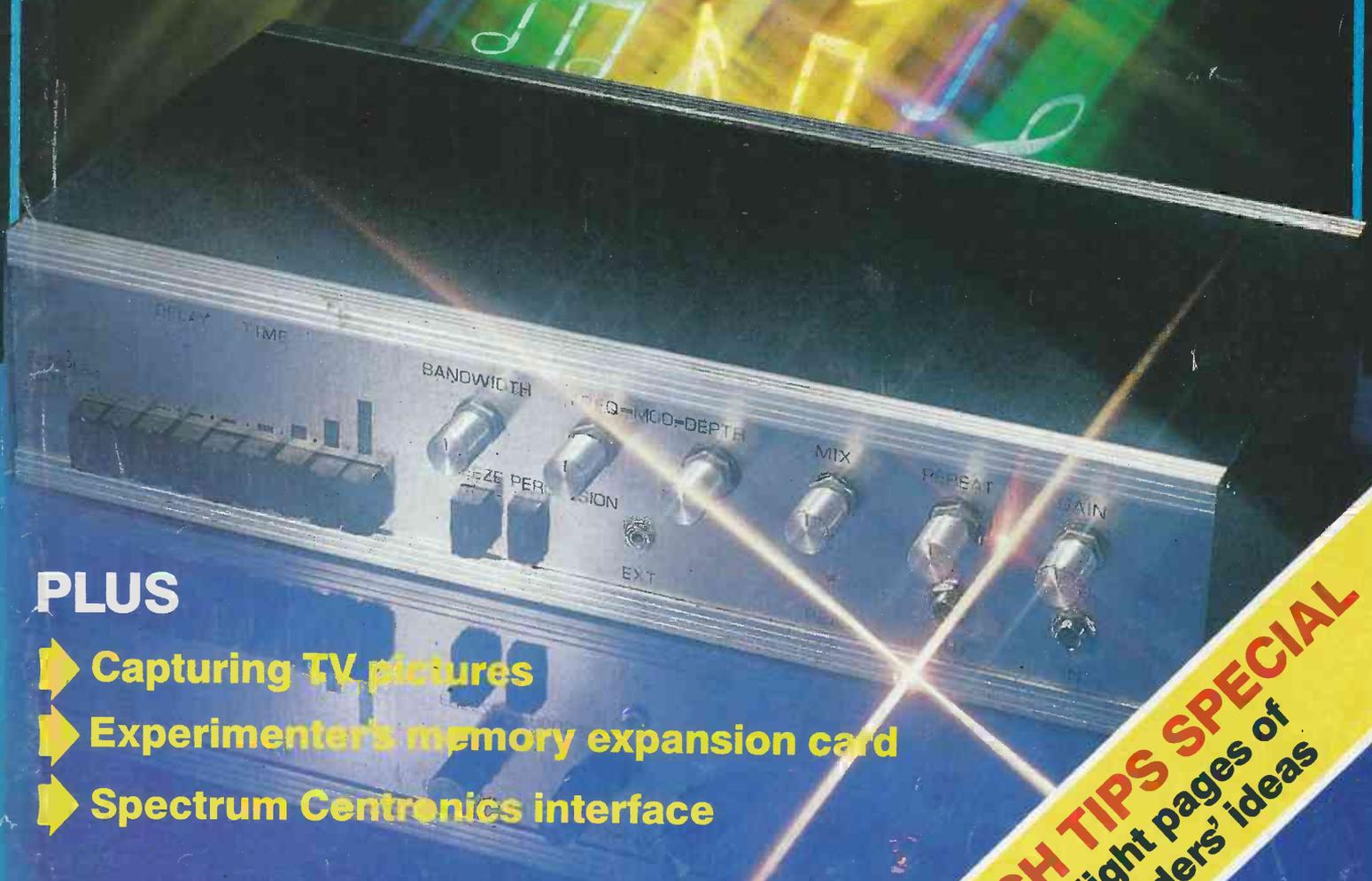


PLUS

- ▶ Capturing TV pictures
- ▶ Experimenter's memory expansion card
- ▶ Spectrum Centronics interface

TECH TIPS SPECIAL
Eight pages of readers' ideas

YOU'LL ENJOY THE EXPERIENCE

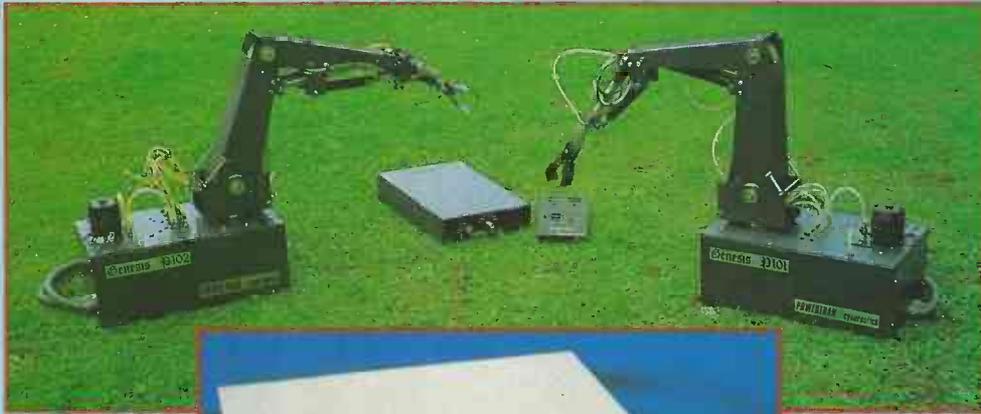GENESIS P102
Hydraulic Robot System
from £1476



GENESIS P101
Hydraulic Robot arm
from £750

CORTEX II
16 bit microcomputer
Ready-Built
from £399



CORTEX II
16 bit microcomputer
from £299 in kit form

HEBOT II
Robot Turtle
From £95.00



MICROGRASP
Electric Robot
from £215

Powertran's educational robots and the remarkable Cortex microcomputer have been tried and tested in universities, colleges, schools and homes throughout the world.

Our own experience in the field of electronics kits has been supplemented by the Feedback Group's 25 years of supplying technical equipment to the Educational sector. Our first year as a member of the Group has seen numerous improvements to our already popular products.

All the products illustrated can be supplied either in kit form for added economy or factory-built. Contact our Sales Office for details.

(Prices quoted are exclusive of VAT and apply to the UK only.)

POWERTRAN *cybernetics Ltd.*



PORTWAY INDUSTRIAL ESTATE, ANDOVER, HANTS SP10 3ET Tel: 0264 64455

electronics today

INTERNATIONAL DECEMBER 1984 VOL 13 NO 12



EDITORIAL AND ADVERTISEMENT OFFICE

1 Golden Square, London W1R 3AB. Telephone 01-437 0626.
Telex 8811896.


FEATURES

DIGEST..... 7
ETI dusts off a few more press releases.

READ/WRITE..... 67
ETI responds to the latest batch of data which has arrived in the input port.

TECH-TIPS SPECIAL..... 39
Eight pages of un-alloyed ingenuity from our ever-clever readership.

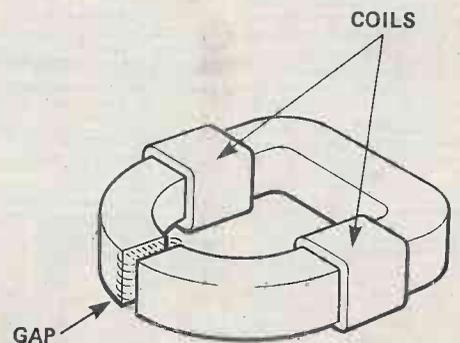MIND YOUR HEAD..... 49
Vivian Capel explains the ins and outs of tape transducers in terms which won't be above anybody's head.



PROJECTS

DIGITAL DELAY LINE..... 16
Just the thing for musicians with restless digits.

ACTIVE-8 LOUDSPEAKER 24
Barry Porter completes his description of the basic Active-8 system and goes on to offer some encouragement for those with sensitive ears and sympathetic bank managers.

EXPERIMENTER'S DRAM CARD 31
The 64 K DRAM board we described in September last year proved very popular but there were a number of problems with it. Phil Walker has designed an improved version and also come up with a modification which can be added to existing boards.

SPECTRUM CENTRONICS INTERFACE..... 57
We seem to have produced Cen-

tronics interfaces for micros right across the computer spectrum, so it would be a shame not to cater for this one.

TV FRAMESTORE 61
For a mere couple of hundred pounds or so (!) we can put you in the picture about video storage techniques.

VARIO UPDATE..... 71
Lindsay Ruddock takes his vertical speed indicator to even greater heights of sophistication.

Our apologies to readers who have been holding their breath since last month in anticipation of John Linsley Hood's promised distortion meter design. Due to lack of space we have decided to hold part one over until next month when we will present both parts together.

INFORMATION

NEXT MONTH'S ETI..... 69
ETI BOOK SERVICE 74
PCB FOIL PATTERNS 75

ETI PCB SERVICE..... 78
ADVERTISER'S INDEX..... 82

Dave Bradshaw: Editor
Phil Walker: Project Editor
Ian Pitt: Assistant Editor
Jerry Fowler: Technical Illustrator
Paul Stanyer: Ad. Manager
Kerry Fowler: Copy Control
Jim Connell: Chairman

PUBLISHED BY:
Argus Specialist Publications Ltd.,
1 Golden Square, London W1R 3AB.
DISTRIBUTED BY:
Argus Press Sales & Distribution Ltd.,
12-18 Paul Street, London EC2A 4JS
(British Isles)
PRINTED BY:
The Garden City Press Ltd.
COVERS PRINTED BY:
Alabaster Passmore.

OVERSEAS EDITIONS and their EDITORS

AUSTRALIA — Roger Harrison
CANADA — Halvor Moorshead
GERMANY — Udo Wittig
HOLLAND — Anton Kriegsman



Member of the
Audit Bureau
of Circulation

Electronics Today is normally published on the first Friday in the month preceding cover date. □ The contents of this publication including all articles, designs, plans, drawings and programs and all copyright and other intellectual property rights therein belong to Argus Specialist Publications Limited. All rights conferred by the Law of Copyright and other intellectual property rights and by virtue of international copyright conventions are specifically reserved to Argus Specialist Publications Limited and any reproduction requires the prior written consent of the Company. © 1984 Argus Specialist Publications Ltd □ All reasonable care is taken in the preparation of the magazine contents, but the publishers cannot be held legally responsible for errors. Where mistakes do occur, a correction will normally be published as soon as possible afterwards. All prices and data contained in advertisements are accepted by us in good faith as correct at time of going to press. Neither the advertisers nor the publishers can be held responsible, however, for any variations affecting price or availability which may occur after the publication has closed for press.

□ Subscription Rates. UK £15.00 including postage. For further details and Airmail rates etc, see the Readers' Services page.

WATFORD ELECTRONICS

33/34 CARDIFF ROAD, WATFORD, HERTS, ENGLAND

MAIL ORDER, CALLERS WELCOME
Tel: Watford (0923) 37774/4058, Telex. 8956095

ALL DEVICES FULLY GUARANTEED. SEND CHEQUE, P.O.s, CASH, BANK DRAFT WITH ORDERS. TELEPHONE ORDERS BY ACCESS/MASTER CHARGE ACCEPTED. GOVERNMENT & EDUCATIONAL ESTABLISHMENTS OFFICIAL ORDERS WELCOME. P&P ADD 75p TO ALL CASH ORDERS. OVERSEAS ORDERS POSTAGE AT COST. PRICES SUBJECT TO CHANGE WITHOUT NOTICE.

VAT Export orders not VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 15% to the total cost including P&P. We stock thousands more items. It pays to visit us. We are situated behind Watford Football Ground. Nearest Underground/BR Station: Watford High Street. Open Monday to Saturday: 9.00am to 6.00pm. Ample Free Car parking space available.

ELECTROLYTIC CAPACITORS: (Values in μF) 500v, 10 μF 52, 47 7 μF 63V 0.47, 1.0, 1.5, 2.2, 3.3, 4.7 8p 10 10p; 15, 22 1p 33 1.5p 47 1p 66 20 100 19p 220 26p; 1000 70p 2200 99p; 50V, 68 20p, 100 17p, 220 24p; 40V, 22 9p 33 12p 330, 47 30p 1000 45p 1500 45p 2200 99p 25V, 1.5, 4.7, 10, 22, 47 8p 10p 100 11p 150 12p 220 15p 330 22p 470 25p 880, 1000 34p 1500 42p 2200 50p 3300 76p 4700 92p 16V, 47, 68, 100 9p 125 12p 330 18p 470 20p 680 34p 1000 27p 1500 31p 2200 26p, 4700 72p

TAG-END CAPACITORS: 64V, 2200 139p, 3300 199p, 4700 245p; 50V: 2200 110p, 3300 184p; 40V: 4700 180p, 25V: 2200 90p, 3300 99p, 4000, 4700 99p; 10,000 320p; 15,000 345p; 16V: 22 100p 350p.

POLYESTER RADIAL LEAF CAPACITORS: 250V 10 μF 15n, 22n, 33n, 47n, 68n, 100n 8p; 100n 8p; 150n 10p; 220n 30p; 330n 42p; 470n 52p; 680n 1uF 68p; 1u 2u 82p. 1000V: 1nF 17p; 10nF 30p; 15n 40p; 22n 35p; 33n 42p; 47n, 100n 42p.

POLYESTER RADIAL LEAF CAPACITORS: 250V 10 μF 15n, 22n, 33n, 47n, 68n, 100n 8p; 100n 8p; 150n 10p; 220n 30p; 330n 42p; 470n 52p; 680n 1uF 68p; 1u 2u 82p. 1000V: 1nF 17p; 10nF 30p; 15n 40p; 22n 35p; 33n 42p; 47n, 100n 42p.

TANTALUM BEAD CAPACITORS 50V: 0.1 μF , 0.22, 0.33 15p 0.47, 0.68, 1.0, 1.5 18p; 2.2, 3.3 18p; 4.7, 6.8 22p 10 28p; 18V: 2.2, 3.3 16p; 4.7, 6.8, 10 18p; 15, 30p; 22, 45p; 33, 47 50p; 100 95p; 10V: 1.5, 2.2, 3.3, 4.7 50p; 10 80p; 6V: 100 55p.

MYLAR FILM CAPACITORS 100V: 1nF, 2, 4, 4nF, 10 8p; 15nF, 22n, 30n, 40n, 47n 7p; 56n, 100n, 200n 9p; 50V: 47nF 12p.

CERAMIC CAPACITORS 50V: Range: 0.5pF to 10nF 4p, 15nF, 22nF 33nF, 47nF, 50pF, 100nF/300V 7p, 200nF/6V 8p.

POLYSTYRENE CAPACITORS: 10pF to 1nF 8p; 1.5nF to 12nF 10p.

SILVER MICA (Values in pF) 2, 3.3, 4.7, 6.8, 8.2, 10, 12, 15, 18, 22, 33, 39, 47, 50, 56, 68, 75, 82, 85, 100, 120, 150, 180p 15p each; 200, 220, 250, 270, 300, 270, 360, 390, 450, 500, 600, 820 21p each; 1000, 1200, 1800, 2200 30p each; 3300, 4700p 80p.

MINIATURE TRIMMERS Capacitors 2-6pF 2-10pF 22p 2-25pF; 5-65pF 30p; 10-88pF 30p. £16

RESISTORS Carbon Film, miniature, Hi-Stab. 5% RANGE Val 1-99 100+ 0.25W 22 Ω - 10M E24 3p 1p 0.5W 22 Ω - 4M7 E12 3p 1p 1W 22 Ω - 10M E12 6p 4p 2% Metal Film 51 Ω - 1M E24 6p 4p 1% Metal Film 51 Ω - 1M E24 5p 4p 100+ price applies to Resistors of each type not mixed.

RESISTORS NETWORK S.I.L. 7 Commoned: (8 pins) 100n, 680n, 1K 2K, 4K7, 10K, 47K, 100K 25p 8 Commoned: (8 pins) 150n, 180n, 270n, 330n, 1K, 2K, 4K7, 6K8, 10K, 22K, 47K & 100K 20p.

DIODES BRIDGE RECTIFIERS 75 SERIES

AA119 15 1A/50V 18 75107/8 98
AA129 20 1A/50V 18 75110 90
AA30 15 1A/100V 20 75114/5 150
15A100 15 1A/100V 25 75121/2 130
BY100 24 2A/50V 30 75154 125
BY126 12 2A/200V 40 75158 150
BY127 14 2A/400V 46 75159 150
CRO33 250 2A/600V 66 75160 420
OAS 40 6A/100V 98 75162 650
OAS7 12 6A/400V 98 75182/4 99
OAS10 12 10A/200V 215 75188/9 100
OAS19 15 10A/600V 296 75322 140
OAS1 20 8A/600V 240 75324 380
OAS5 15 25A/600V 398 75325 00
OAS8 15 8V/16A 56 75361/3 150
OAS9 8 75451/2 52
OAS20 8 75453 70
1N914 4 1N914 4
1N916 5 1N916 5
1N4003 6 1N4003 6
1N4004/5 7 1N4004/5 7
1N4006/7 8 1N4006/7 8
1N4148 7 1N4148 7
1N5401 15 1N5401 15
1N5404 16 1N5404 16
1N5406 17 1N5406 17
1N5408 19 1N5408 19
1S44 10 1S44 10
1S92 9 1S92 9
6A/100V 40 6A/100V 40
6A/400V 50 6A/400V 50

ZENERS

Range 2V7 to 39V 400mW 8p each
Range 3V3 to 33V 3W 15p each

TRIACS

3A200V 54 3A200V 54
3A400V 56 3A400V 56
8A100V 69 8A100V 69
8A200V 115 8A200V 115
12A100V 78 12A100V 78
12A200V 82 12A200V 82
12A400V 88 12A400V 88
16A100V 103 16A100V 103
16A200V 106 16A200V 106
6A/800V 60 6A/800V 60

VARIACAPS

BA102 50 BA102 50
BB105B 40 BB105B 40
BB106 40 BB106 40
BB109 45 BB109 45
VM4M2 105 VM4M2 105

DIAC

ST2 25 ST2 25

TRANSISTORS

AC126/7 35	BC327 15	BF336/7 35	MP5U06 60	ZTX107/8 12	2N3820 60	2SC2335 200
AC141/2 35	BC337/8 15	BF394 40	MP5U02 65	ZTX109 12	2N3822/3 80	2SC2547 40
AC142 35	BC416 65	BF421 35	MP5U05 60	ZTX12 28	2N3866 90	2SC2612 200
AC187 35	BC477 40	BF494/5 40	MP5U06 60	ZTX14 28	2N3870 90	2SC2934 74
AC188 35	BC516/7 40	BF594/5 40	OC26 170	ZTX302 16	2N3895/6 15	2SK42 80
AC199/21 75	BC547/8 12	BF694/0 40	OC28 220	ZTX303 25	2N3906 17	2SK288 225
AD142 120	BC549C 15	BF741/79 25	OC35 50	ZTX304 17	2N4037 70	2SK283 225
AD149 79	BC568/81 25	BF781 25	OC38 75	ZTX326 30	2N4054 15	2SK285 225
AD161 42	BC590/40 85	BF829 35	OC42/75 50	ZTX45 14	2N4056 15	2SK286 225
AD162 42	BC614/2 30	BF841 45	OC47/72 50	ZTX500 14	2N4264 30	3N140 115
AF11 5/6	BC642 30	BF845 50	OC57/76 55	ZTX501/2 15	2N4286 25	30315 90
AF188 80	BC645 50	BF850 50	OC81/82 50	ZTX503 18	2N4289 25	30316 90
AF124/26 70	BC670/1 18	BF950/51 30	OC83/84 35	ZTX504 18	2N4400 78	30324 100
AF138 40	BC72 25	BF952 30	OC87/91 40	ZTX505 28	2N4401 70	40326/7 70
AF178 75	BC778 30	BF953 35	OC90 70	ZTX550 28	2N4427 80	40347 90
AF186 70	BC810 14	BF954/56 56	OC92/93 38	ZTX552 30	2N4471 80	40348 120
AF239 55	BD121 95	BF954 30	OC96 38	ZTX553 30	2N4513/6 30	40380 60
BC107 12	BD124 115	BF981 120	OC98 220	ZTX554 30	2N4513 25	40381 70
BC107/B 14	BD131/32 65	BF990 80	OC99 37	ZTX555 30	2N4514 25	40382 70
BC107/C 14	BD133 70	BRV39 50	OC99A 37	ZTX556 30	2N4515 25	40383 70
BC108 14	BD135 70	BRV40 50	OC99B 37	ZTX557 30	2N4516 25	40384 70
BC108C 14	BD136/37 40	BSX26/29 45	OC99C 37	ZTX558 30	2N4517 25	40385 70
BC109 12	BD138/39 40	BSY26 35	OC99D 37	ZTX559 30	2N4518 25	40386 70
BC109B 14	BD140 40	BSY95 35	OC99E 37	ZTX560 30	2N4519 25	40387 70
BC109C 14	BD141 40	BU144/45 180	OC99F 37	ZTX561 30	2N4520 25	40388 70
BC114/5 30	BD158 88	BU205 180	OC99G 37	ZTX562 30	2N4521 25	40389 70
BC117/8 25	BD205/5 110	BU202 180	OC99H 37	ZTX563 30	2N4522 25	40390 70
BC137/9 40	BD245 65	BU208 200	OC99I 37	ZTX564 30	2N4523 25	40391 70
BC140 38	BD378 70	BU209 200	OC99J 37	ZTX565 30	2N4524 25	40392 70
BC142 38	BD414 190	BU210 200	OC99K 37	ZTX566 30	2N4525 25	40393 70
BC147 12	BD517 75	MJ295 80	OC99L 37	ZTX567 30	2N4526 25	40394 70
BC148 12	BD645 80	MJE170 150	OC99M 37	ZTX568 30	2N4527 25	40395 70
BC148 12	BD695A 150	MJE180 150	OC99N 37	ZTX569 30	2N4528 25	40396 70
BC149 12	BD696A 150	MJE340 54	OC99O 37	ZTX570 30	2N4529 25	40397 70
BC149 12	BD697A 150	MJE340 54	OC99P 37	ZTX571 30	2N4530 25	40398 70
BC149C 15	BD698A 150	MJE371 100	OC99Q 37	ZTX572 30	2N4531 25	40399 70
BC182L 10	BF167 35	MJE520 85	OC99R 37	ZTX573 30	2N4532 25	40400 70
BC183L 10	BF173 35	MJE521 98	OC99S 37	ZTX574 30	2N4533 25	40401 70
BC183L 10	BF175 35	MJE521 98	OC99T 37	ZTX575 30	2N4534 25	40402 70
BC184 10	BF18 35	MJE295 98	OC99U 37	ZTX576 30	2N4535 25	40403 70
BC186/7 28	BF179 35	MJE295 98	OC99V 37	ZTX577 30	2N4536 25	40404 70
BC186/7 28	BF179 35	MJE295 98	OC99W 37	ZTX578 30	2N4537 25	40405 70
BC186/7 28	BF179 35	MJE295 98	OC99X 37	ZTX579 30	2N4538 25	40406 70
BC186/7 28	BF179 35	MJE295 98	OC99Y 37	ZTX580 30	2N4539 25	40407 70
BC186/7 28	BF179 35	MJE295 98	OC99Z 37	ZTX581 30	2N4540 25	40408 70
BC186/7 28	BF179 35	MJE295 98	OC99AA 37	ZTX582 30	2N4541 25	40409 70
BC186/7 28	BF179 35	MJE295 98	OC99AB 37	ZTX583 30	2N4542 25	40410 70
BC186/7 28	BF179 35	MJE295 98	OC99AC 37	ZTX584 30	2N4543 25	40411 70
BC186/7 28	BF179 35	MJE295 98	OC99AD 37	ZTX585 30	2N4544 25	40412 70
BC186/7 28	BF179 35	MJE295 98	OC99AE 37	ZTX586 30	2N4545 25	40413 70
BC186/7 28	BF179 35	MJE295 98	OC99AF 37	ZTX587 30	2N4546 25	40414 70
BC186/7 28	BF179 35	MJE295 98	OC99AG 37	ZTX588 30	2N4547 25	40415 70
BC186/7 28	BF179 35	MJE295 98	OC99AH 37	ZTX589 30	2N4548 25	40416 70
BC186/7 28	BF179 35	MJE295 98	OC99AI 37	ZTX590 30	2N4549 25	40417 70
BC186/7 28	BF179 35	MJE295 98	OC99AJ 37	ZTX591 30	2N4550 25	40418 70
BC186/7 28	BF179 35	MJE295 98	OC99AK 37	ZTX592 30	2N4551 25	40419 70
BC186/7 28	BF179 35	MJE295 98	OC99AL 37	ZTX593 30	2N4552 25	40420 70
BC186/7 28	BF179 35	MJE295 98	OC99AM 37	ZTX594 30	2N4553 25	40421 70
BC186/7 28	BF179 35	MJE295 98	OC99AN 37	ZTX595 30	2N4554 25	40422 70
BC186/7 28	BF179 35	MJE295 98	OC99AO 37	ZTX596 30	2N4555 25	40423 70
BC186/7 28	BF179 35	MJE295 98	OC99AP 37	ZTX597 30	2N4556 25	40424 70
BC186/7 28	BF179 35	MJE295 98	OC99AQ 37	ZTX598 30	2N4557 25	40425 70
BC186/7 28	BF179 35	MJE295 98	OC99AR 37	ZTX599 30	2N4558 25	40426 70
BC186/7 28	BF179 35	MJE295 98	OC99AS 37	ZTX600 30	2N4559 25	40427 70
BC186/7 28	BF179 35	MJE295 98	OC99AT 37	ZTX601 30	2N4560 25	40428 70
BC186/7 28	BF179 35	MJE295 98	OC99AU 37	ZTX602 30	2N4561 25	40429 70
BC186/7 28	BF179 35	MJE295 98	OC99AV 37	ZTX603 30	2N4562 25	40430 70
BC186/7 28	BF179 35	MJE295 98	OC99AW 37	ZTX604 30	2N4563 25	40431 70
BC186/7 28	BF179 35	MJE295 98	OC99AX 37	ZTX605 30	2N4564 25	40432 70
BC186/7 28	BF179 35	MJE295 98	OC99AY 37	ZTX606 30	2N4565 25	40433 70
BC186/7 28	BF179 35	MJE295 98	OC99AZ 37	ZTX607 30	2N4566 25	40434 70
BC186/7 28	BF179 35	MJE295 98	OC99BA 37	ZTX608 30	2N4567 25	40435 70
BC186/7 28	BF179 35	MJE295 98	OC99BB 37	ZTX609 30	2N4568 25	40436 70
BC186/7 28	BF179 35	MJE295 98	OC99BC 37	ZTX610 30	2N4569 25	40437 70
BC186/7 28	BF179 35	MJE295 98	OC99BD 37	ZTX611 3		

SWITCHES TOGGLE: 2A 250V SPST 35p DPDP 48p	DIP SWITCHES (SPST) 4 way 65p; 6 way 80p; 8 way 85p; 10 way 125p (SPDT) 4 way 190p	VEROBOARD 0.1in 2 1/2 x 3 1/4 95p 2 1/2 x 5 110p 3 1/4 x 3 1/4 110p 3 1/4 x 5 125p 3 1/4 x 17 420p 4 1/4 x 17 590p Pkt of 100 pins 55p Spot/face cutter 150p Pin insertion tool 185p	VA BOARD 195p DIP Board 395p Vero Strip 95p	IDC CONNECTORS PCB with Plugs Female Female Attach Pins Header Plug Edge Strt Angle Conct Conct	PANEL METERS FSD 46 x 35mm 0-50mA 0-100mA 0-500mA 0-1mA 0-50mA 0-100mA 0-500mA 0-2A 0.2V 0.50V AC 0.300V AC "VU" 490p each	RELAYS Miniature, enclosed, PCB mount SINGLE POLE Changeover RL-91 205R Coil, 12V DC, (10V5 to 19V5) 10A at 30V DC or 250V AC 195p DOUBLE POLE Changeover, 6A 30V DC or 250V AC RL-100 53R Coil, 6V DC (5V4 to 9V9) 190p RL-111 205R Coil, 12V DC (10V7 to 19V5) 195p RL-114 740R Coil, 24V DC (22V to 37V) 200p
SUB-MIN TOGGLE SPST on/off 58p SPDT cover 84p SPDT centre of 85p SPDT biased both ways 105p DPDT 6 tags 80p DPDT centre of 88p DPDT biased both ways 145p DPDT 3 positions on/off 185p 4-pole 2 way 220p	ROTARY SWITCHES (Adjustable Stop type) 1 pole/2 to 12 way; 2 pole/2 to 6 way; 3 pole/2 to 4 way; 4 pole/2 to 3 way 48p	VERO WIRING PEN + spool 380p Spare spool 75p Combs 8p	PROTO DECS Veroblock 480p Eurobreadboard 395p Eurobreadboard 590p Bimboard 1 575p Superstrip SS2 1350p	EURO CONNECTORS Gold Flashed Contacts DIN41617 170p - 175p DIN41612 2 x 32 A + B 275p - 220p 285p DIN41612 2 x 32 A 295p - 240p 300p A + B + C 360p 385p 280p 395p	CRYSTALS 32.768KHz 100 100KHz 545 200KHz 370 455KHz 370 1MHz 275 1.008M 275 1.2288M 450 1.6MHz 395 1.8MHz 345 1.8432M 250 2.0MHz 225 2.4576M 300 3.1278M 150 3.5794M 98 3.6864M 300 4.0MHz 150 4.032MHz 290 4.19430M 200 4.433619M 100 4.608MHz 200 4.608MHz 200 5.0MHz 180 5.185MHz 300 5.24288M 390 6.0MHz 140 6.144MHz 150 6.5536MHz 225 7.0MHz 150 7.168MHz 250 7.7328MHz 250 7.68MHz 150 8.0MHz 150 8.089333M 250 8.86723M 250 9.000MHz 175 10.0MHz 175 10.24MHz 200 10.5MHz 150 10.7MHz 150 12.0MHz 175 12.528M 300 14.31814M 170 15.0MHz 240 16.0MHz 220 18.0MHz 180 18.432M 150 19.988MHz 150 20.0MHz 200 24.0MHz 170 24.930MHz 325 25.68M 150 27.500MHz 180 38.6667M 240 48.0MHz 200 100.0MHz 295 116.0MHz 300	ASTEC UHF MODULATORS Standard 6MHz 375p Wideband 8MHz 550p
SLIDE 250V: DPDT 1A 14p DPDT 1A c/off 15p DPDT 1/2A 13p	ROTARY: Mains DP 250V 4 Amp on/off 68p ROTARY: (Make a switch) Make a multiway switch. Shafting assembly has adjustable stop. Accommodates up to 6 wafers (max 6 pole/12 way + DP switch). Mechanism only 90p	FERRIC CHLORIDE 1 lb bag Anhydrous 195p + 50p p&p	DALO ETCH RESIST PEN Plus spare tip 100p	RIBBON CABLE price per foot Grey Colour 3.278M 150 10 way 15p 28p 16 way 25p 40p 20 way 30p 50p 24 way 40p 65p 28 way 55p 80p 34 way 60p 85p 40 way 70p 90p 50 way 100p 135p 64 way 120p 160p	BUZZERS miniature, solid-state 6V, 9V & 12V 70p	ASTEC UHF MODULATORS Standard 6MHz 375p Wideband 8MHz 550p
PUSHBUTTON 6p with 10mm Button SPDT latching 150p DPDT latching 200p SPDT moment 150p DPDT moment 200p	WAFERS: (make before break) to fit the above switch mechanism. 1 pole/12 way 2 pole/6 way 3 pole/4 way 4 pole/3 way 6p x 6p x 5p Mains DP 4A Switch to fit Spacers 4p. Screen 8p.	COPPER CLAD BOARDS Fibre glass Single-sided Double-sided S.R.B.P. 6" x 6" 100p 125p 95" x 65" 110p 6" x 12" 175p 225p	EDGE CONNECTORS 24 way - 111p 24 x 2 way - 16p 24 x 5 way - 18p 24 x 8 way 210p 175p 24 x 22 way 215p 250p 24 x 23 way 175p 24 x 25 way 285p 275p 24 x 28 way 190p - 24 x 30 way 310p - 24 x 36 way 380p - 24 x 40 way 380p -	COVERS 80p 75p 75p 90p	LOUDSPEAKERS Miniature, 0.3W 2in, 3" x 1in, 2" x 1in, 3in 2 1/2in 40 64 or 80 80p	BUZZERS miniature, solid-state 6V, 9V & 12V 70p
ROCKER SWITCHES ROCKER 5A/250V SPST 28p ROCKER 10A/250V SPDT 38p ROCKER 10A/250V DPDT 1/2 c/off 95p ROCKER 10A/250V DPST with neon 85p	ROCKERS: Make a switch Make a multiway switch. Shafting assembly has adjustable stop. Accommodates up to 6 wafers (max 6 pole/12 way + DP switch). Mechanism only 90p	ULTRASONIC TRANSDUCER 40KHz 475p	DALO ETCH RESIST PEN Plus spare tip 100p	DIL PLUG (Header) Solder IDC 14 pin 40p 90p 16 pin 48p 105p 24 pin 88p 178p 28 pin 290p 295p 40 pin 250p 255p	CRYSTALS 32.768KHz 100 100KHz 545 200KHz 370 455KHz 370 1MHz 275 1.008M 275 1.2288M 450 1.6MHz 395 1.8MHz 345 1.8432M 250 2.0MHz 225 2.4576M 300 3.1278M 150 3.5794M 98 3.6864M 300 4.0MHz 150 4.032MHz 290 4.19430M 200 4.433619M 100 4.608MHz 200 4.608MHz 200 5.0MHz 180 5.185MHz 300 5.24288M 390 6.0MHz 140 6.144MHz 150 6.5536MHz 225 7.0MHz 150 7.168MHz 250 7.7328MHz 250 7.68MHz 150 8.0MHz 150 8.089333M 250 8.86723M 250 9.000MHz 175 10.0MHz 175 10.24MHz 200 10.5MHz 150 10.7MHz 150 12.0MHz 175 12.528M 300 14.31814M 170 15.0MHz 240 16.0MHz 220 18.0MHz 180 18.432M 150 19.988MHz 150 20.0MHz 200 24.0MHz 170 24.930MHz 325 25.68M 150 27.500MHz 180 38.6667M 240 48.0MHz 200 100.0MHz 295 116.0MHz 300	PIEZO TRANSDUCERS PB2720 70p
THUMBWHEEL Mini: front mounting switches Decade Switch Module 275p B.C.D. Switch Module 298p Mounting Cheeks (per pair) 75p	ROCKER: Make a switch Make a multiway switch. Shafting assembly has adjustable stop. Accommodates up to 6 wafers (max 6 pole/12 way + DP switch). Mechanism only 90p	EDGE CONNECTORS 24 way - 111p 24 x 2 way - 16p 24 x 5 way - 18p 24 x 8 way 210p 175p 24 x 22 way 215p 250p 24 x 23 way 175p 24 x 25 way 285p 275p 24 x 28 way 190p - 24 x 30 way 310p - 24 x 36 way 380p - 24 x 40 way 380p -	DIL SOCKET 0.1" Pitch 20 way 65p	RIBBON CABLE price per foot Grey Colour 3.278M 150 10 way 15p 28p 16 way 25p 40p 20 way 30p 50p 24 way 40p 65p 28 way 55p 80p 34 way 60p 85p 40 way 70p 90p 50 way 100p 135p 64 way 120p 160p	CRYSTALS 32.768KHz 100 100KHz 545 200KHz 370 455KHz 370 1MHz 275 1.008M 275 1.2288M 450 1.6MHz 395 1.8MHz 345 1.8432M 250 2.0MHz 225 2.4576M 300 3.1278M 150 3.5794M 98 3.6864M 300 4.0MHz 150 4.032MHz 290 4.19430M 200 4.433619M 100 4.608MHz 200 4.608MHz 200 5.0MHz 180 5.185MHz 300 5.24288M 390 6.0MHz 140 6.144MHz 150 6.5536MHz 225 7.0MHz 150 7.168MHz 250 7.7328MHz 250 7.68MHz 150 8.0MHz 150 8.089333M 250 8.86723M 250 9.000MHz 175 10.0MHz 175 10.24MHz 200 10.5MHz 150 10.7MHz 150 12.0MHz 175 12.528M 300 14.31814M 170 15.0MHz 240 16.0MHz 220 18.0MHz 180 18.432M 150 19.988MHz 150 20.0MHz 200 24.0MHz 170 24.930MHz 325 25.68M 150 27.500MHz 180 38.6667M 240 48.0MHz 200 100.0MHz 295 116.0MHz 300	PIEZO TRANSDUCERS PB2720 70p
JUMPER LEADS (Ribbon Cable Assembly) Length 14 pin 16 pin 24 pin 40 pin Single ended DIP (Header Plug) Jumper 24 inches 145p 185p 240p 380p Double ended DIP (Header Plug) Jumper 6 inches 185p 205p 300p 485p 12 inches 215p 245p 350p 535p 24 inches 210p 235p 345p 540p 36 inches 290p 370p 480p 525p	ROCKER: Make a switch Make a multiway switch. Shafting assembly has adjustable stop. Accommodates up to 6 wafers (max 6 pole/12 way + DP switch). Mechanism only 90p	ANTX SOLDERING IRONS C15W 525p C18W 550p C19W 550p Spare Bits 175p Iron Stand 175p	SIL SOCKET 0.1" Pitch 20 way 65p	RIBBON CABLE price per foot Grey Colour 3.278M 150 10 way 15p 28p 16 way 25p 40p 20 way 30p 50p 24 way 40p 65p 28 way 55p 80p 34 way 60p 85p 40 way 70p 90p 50 way 100p 135p 64 way 120p 160p	CRYSTALS 32.768KHz 100 100KHz 545 200KHz 370 455KHz 370 1MHz 275 1.008M 275 1.2288M 450 1.6MHz 395 1.8MHz 345 1.8432M 250 2.0MHz 225 2.4576M 300 3.1278M 150 3.5794M 98 3.6864M 300 4.0MHz 150 4.032MHz 290 4.19430M 200 4.433619M 100 4.608MHz 200 4.608MHz 200 5.0MHz 180 5.185MHz 300 5.24288M 390 6.0MHz 140 6.144MHz 150 6.5536MHz 225 7.0MHz 150 7.168MHz 250 7.7328MHz 250 7.68MHz 150 8.0MHz 150 8.089333M 250 8.86723M 250 9.000MHz 175 10.0MHz 175 10.24MHz 200 10.5MHz 150 10.7MHz 150 12.0MHz 175 12.528M 300 14.31814M 170 15.0MHz 240 16.0MHz 220 18.0MHz 180 18.432M 150 19.988MHz 150 20.0MHz 200 24.0MHz 170 24.930MHz 325 25.68M 150 27.500MHz 180 38.6667M 240 48.0MHz 200 100.0MHz 295 116.0MHz 300	PIEZO TRANSDUCERS PB2720 70p
ICD Female Header Socket Jumper Leads: 36" 20 pin 26 pin 34 pin 40 pin Single ended 180p 200p 280p 300p Double ended 290p 370p 480p 525p	ROCKER: Make a switch Make a multiway switch. Shafting assembly has adjustable stop. Accommodates up to 6 wafers (max 6 pole/12 way + DP switch). Mechanism only 90p	ANTX SOLDERING IRONS C15W 525p C18W 550p C19W 550p Spare Bits 175p Iron Stand 175p	SIL SOCKET 0.1" Pitch 20 way 65p	RIBBON CABLE price per foot Grey Colour 3.278M 150 10 way 15p 28p 16 way 25p 40p 20 way 30p 50p 24 way 40p 65p 28 way 55p 80p 34 way 60p 85p 40 way 70p 90p 50 way 100p 135p 64 way 120p 160p	CRYSTALS 32.768KHz 100 100KHz 545 200KHz 370 455KHz 370 1MHz 275 1.008M 275 1.2288M 450 1.6MHz 395 1.8MHz 345 1.8432M 250 2.0MHz 225 2.4576M 300 3.1278M 150 3.5794M 98 3.6864M 300 4.0MHz 150 4.032MHz 290 4.19430M 200 4.433619M 100 4.608MHz 200 4.608MHz 200 5.0MHz 180 5.185MHz 300 5.24288M 390 6.0MHz 140 6.144MHz 150 6.5536MHz 225 7.0MHz 150 7.168MHz 250 7.7328MHz 250 7.68MHz 150 8.0MHz 150 8.089333M 250 8.86723M 250 9.000MHz 175 10.0MHz 175 10.24MHz 200 10.5MHz 150 10.7MHz 150 12.0MHz 175 12.528M 300 14.31814M 170 15.0MHz 240 16.0MHz 220 18.0MHz 180 18.432M 150 19.988MHz 150 20.0MHz 200 24.0MHz 170 24.930MHz 325 25.68M 150 27.500MHz 180 38.6667M 240 48.0MHz 200 100.0MHz 295 116.0MHz 300	PIEZO TRANSDUCERS PB2720 70p

CMOS 4000 20 4075 25 4536 275 4001 25 4076 26 4538 80 4002 25 4078 25 4544 150 4006 75 4081 25 4548 40 4008 60 4082 25 4549 400 4009 45 4085 60 4553 245 4010 60 4088 125 4555 35 4011 25 4093 37 4556 55 4012 25 4099 70 4557 250 4013 60 4094 70 4558 120 4014 60 4095 85 4558 120 4015 60 4097 275 4560 180 4016 60 4098 80 4561 104 4017 60 4099 110 4562 350 4018 58 4100 95 4566 165 4019 58 4101 95 4568 165 4020 90 4162 96 4569 175 4021 58 4163 96 4572 45 4022 67 4174 98 4580 255 4023 30 4175 105 4581 125 4024 50 4181 90 4582 90 4025 22 4408 850 4583 100 4026 90 4409 850 4584 80 4027 43 4410 725 4585 70 4028 45 4411 725 4587 330 4029 45 4412 805 4589 155 4030 35 4415 590 40085 90 4031 130 4419 280 40097 45 4032 70 4422 770 40098 42 4033 130 4435 850 40100 215 4034 148 4440 900 40101 130 4035 70 4450 360 40102 140 4036 275 4451 350 40103 412 4037 115 4480 450 40104 120 4038 75 4501 385 40105 60 4039 280 4502 60 40107 55 4040 80 4503 40 40108 325 4041 57 4504 99 40109 100 4042 50 4505 385 40110 235 4043 42 4506 100 40114 240 4044 50 4507 45 40114 194 4045 110 4507 45 40114 194 4046 60 4508 130 40113 75 4047 60 4510 55 40124 75 4048 55 4511 55 40125 75 4049 38 4512 55 40181 80 4050 35 4513 150 40182 80 4051 70 4514 115 40192 75 4052 60 4515 115 40193 95 4053 60 4516 55 40194 70 4054 85 4517 275 40195 75 4055 85 4519 48 40214 198 4056 85 4519 32 40245 198 4057 1000 4520 53 40256 198 4058 435 4521 115 40271 220 4059 68 4522 125 40274 220 4060 500 4526 60 40308 586 4061 500 4527 65 4062 986 4528 68 4063 85 4528 68 4064 45 4529 150 4065 245 4530 90 4066 25 4531 130 4067 25 4532 60 4068 25 4534 400 4069 25 4534 400	OPTO ELECTRONICS LEDs with clips TL709 10 TL1211 GRN 14 TL1212 Yel 14 TL1220 2" Red 12 2" Green, Yellow or Amber 10p 0.2" Bi-colour 14p Red/Green 100p Red/Green/Yellow 85p Hi-Brightness Red 58 High-Bi Green or Yellow 68 Flashing red 12 Red 12 Square LEDs, Red 55 Green, Yellow 30 Rectangular Stackable LEDs 6 Red/Green/Yellow 18 Triangular LEDs 60 Green or yellow 22 LD271 Infra Red 48 SIRC205 Detector 118 TL132 Infra Red 52 TL176 Detector 55 TL138 50 TL130 75 BARGRAPH Red 10 segments: 275	ISOLATORS IL74 145 ILD74 145 ILD75 275 TL111 2 70 TL112 2 70 TL113 2 70 TL114 2 70 TL115 2 70 TL116 2 70 TL117 125 TL118 125 TL119 125 TL120 125 TL121 125 TL122 125 TL123 125 TL124 125 TL125 125 TL126 125 TL127 125 TL128 125 TL129 125 TL130 125 TL131 125 TL132 125 TL133 125 TL134 125 TL135 125 TL136 125 TL137 125 TL138 125 TL139 125 TL140 125 TL141 125 TL142 125 TL143 125 TL144 125 TL145 125 TL146 125 TL147 125 TL148 125 TL149 125 TL150 125
--	--	--

COMPUTER CORNER ● EPSON RX80 Printer.....£229 ● EPSON RX80 F/T Printer.....£245 ● EPSON FX80 Printer.....£316 ● EPSON FX100 Printer.....£435 ● KAGI/TAXAN KP810 Printer.....£235 ● KAGI/TAXAN KP910 Printer.....£339 ● SEIKOSHA GP100A Printer.....£339 ● BROTHER HR15 Daisywheel.....£339 Cable for above printers to interface with BBC Micro.....£7 ● TEX EPROM ERASER - Erases up to 25 EPROMs. Has a built-in safety switch.....£30 ● SPARE UV Lamp bulb.....£8 ● C12 Computer CASSETTES in Library cases.....£36p ● 8 1/2" & 9 1/4" Fan Fold paper (1000 sheets).....£7 (Carr. 150p) (Securicor Carriage charge on printers is £7)	CALL AT OUR SHOP FOR A DEMONSTRATION ON ANY OF THE ABOVE ITEMS. BE SATISFIED BEFORE YOU BUY OR WRITE IN FOR OUR DESCRIPTIVE MICRO PERIPHERALS LEAFLET.
---	---

DISC DRIVES (CUMANA) DRIVES CASED WITH PSU & CABLES ● CS100 - Single Cased with PSU, 40 Track, 5 1/4" S/S 100K.....£129 ● CD200 - Twin Cased with PSU, 40 Track, 5 1/4" S/S 200K.....£265 ● CS200 - Single Cased with PSU, 80 Track, 5 1/4" S/S 200K.....£175 ● CD400 - Twin Cased with PSU, 80 Track, 5 1/
--


OMP POWER AMPLIFIER MODULES

* PRICES INCLUDE V.A.T. * PROMPT DELIVERIES * FRIENDLY SERVICE * LARGE S.A.E. 28p STAMP FOR CURRENT LIST

OMP POWER AMPLIFIER MODULES

Now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models available to suit the needs of the professional and hobby market, i.e., Industry, Leisure, Instrumental and Hi-Fi, etc. When comparing prices, NOTE all models include Toroidal power supply, Integral heat sink, Glass fibre P.C.B., and Drive circuits to power compatible Vu meter. Open and short circuit proof.

Supplied ready built and tested.

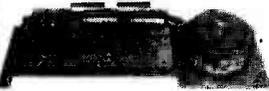

OMP100 Mos-Fet Output power 110 watts R.M.S. into 4 ohms, Frequency Response 15Hz - 30KHz -3dB, T.H.D. 0.01%, S.N.R. -118dB, Sens. for Max. output 500mV at 10K, Size 360 x 115 x 72mm. PRICE £32.99 + £2.50 P&P.



OMP/MF100 Mos-Fet Output power 110 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz -3dB, Damping Factor 80, Slew Rate 45V/uS, T.H.D. Typical 0.002%, Input Sensitivity 500mV, S.N.R. -125dB, Size 300 x 123 x 60mm. PRICE £39.99 + £2.50 P&P.



OMP/MF200 Mos-Fet Output power 200 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz -3dB, Damping Factor 250, Slew Rate 50V/uS, T.H.D. Typical 0.001%, Input Sensitivity 500mV, S.N.R. -130dB, Size 300 x 150 x 100mm. PRICE £62.99 + £3.50 P&P.



OMP/MF300 Mos-Fet Output power 300 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz -3dB, Damping Factor 350, Slew Rate 60V/uS, T.H.D. Typical 0.0008%, Input Sensitivity 500mV, S.N.R. -130dB, Size 330 x 147 x 102mm. PRICE £79.99 + £4.50 P&P.



Vu METER Compatible with our four amplifiers detailed above. A very accurate visual display employing 11 L.E.D. diodes (7 green, 4 red) plus an additional on/off indicator. Sophisticated logic control circuits for very fast rise and decay times. Tough moulded plastic case, with tinted acrylic front. Size 84 x 27 x 45mm. PRICE £8.50 + 50p P&P

NOTE: Mos-Fets are supplied as standard (100KHz bandwidth & Input Sensitivity 500mV). If required, P.A. version (50KHz bandwidth & Input Sensitivity 775mV). Order - Standard or P.A.



19" RACK CASED MOS-FET STEREO AMPLIFIERS with twin power supplies and L.E.D. Vu meters plus X.L.R. connectors. Three models (Ratings RMS into 4 ohms)
MF200 (100 + 100w) £182.85
MF400 (200 + 200w) £228.85
MF600 (300 + 300w) £274.85
 Securicor Delivery £10.00

LOUDSPEAKERS

5 to 15 INCH Up to 300 WATTS R.M.S. All speakers 8 ohm Impedance.



POWER RANGE
8" 50 WATT R.M.S. Hi-Fi/Disco.
 20 oz. magnet. 1 1/2" ally voice coil. Ground ally fixing escutcheon. Res. Freq. 40Hz. Freq. Resp. to 6KHz. Sens. 92dB. PRICE £9.90 Available with black grille £10.90. P&P £1.50 ea
12" 100 WATT R.M.S. Hi-Fi/Disco
 50 oz. magnet. 2" ally voice coil. Ground ally fixing escutcheon. Die-cast chassis. White cone. Res. Freq. 25Hz. Freq. Resp. to 4KHz. Sens. 95dB. PRICE £26.00 + £3.00 P&P ea.
15" 100 WATT R.M.S. Hi-Fi/Disco
 50 oz. magnet. 2" ally voice coil. Ground ally fixing escutcheon. Die-cast chassis. White cone. Res. Freq. 20Hz. Freq. Resp. to 2.5KHz. Sens. 97dB. PRICE £34.00 + £3.00 P&P ea.

McKENZIE
12" 85 WATT R.M.S. C1285GP Lead guitar/keyboard/Disco.
 2" ally voice coil. Ally centre dome. Res. Freq. 45Hz. Freq. Resp. to 6.5KHz. Sens. 98dB. PRICE £24.99 + £3.00 P&P ea
12" 85 WATT R.M.S. C1285TC P.A./Disco 2" ally voice coil. Twin cone.
 Res. Freq. 45Hz. Freq. Resp. to 14KHz. PRICE £24.99 + £3.00 P&P ea
15" 150 WATT R.M.S. C15 Bass Guitar/Disco.
 3" ally voice coil. Die-cast chassis. Res. Freq. 40Hz. Freq. Resp. to 4KHz. PRICE £49.99 + £4.00 P&P ea

WEM
5" 70 WATT R.M.S. Multiple Array Disco etc.
 1" voice coil. Res. Freq. 52Hz. Freq. Resp. to 5KHz. Sens. 89dB. PRICE £20.00 + £1.50 P&P ea.
8" 150 WATT R.M.S. Multiple Array Disco etc.
 1" voice coil. Res. Freq. 48Hz. Freq. Resp. to 5KHz. Sens. 92dB. PRICE £27.00 + £1.50 P&P ea.
10" 300 WATT R.M.S. Disco/Sound re-enforcement etc.
 1 1/2" voice coil. Res. Freq. 35Hz. Freq. Resp. to 4KHz. Sens. 92dB. PRICE £30.00 + £2.00 P&P ea.
12" 300 WATT R.M.S. Disco/Sound re-enforcement etc.
 1 1/2" voice coil. Res. Freq. 35Hz. Freq. Resp. to 4KHz. Sens. 94dB. PRICE £38.00 + £3.00 P&P ea.

SOUNDLAB (Full Range Twin Cone)
5" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco etc.
 1" voice coil. Res. Freq. 63Hz. Freq. Resp. to 20KHz. Sens. 86dB. PRICE £8.99 + £1.00 P&P ea.
6" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco etc.
 1" voice coil. Res. Freq. 56Hz. Freq. Resp. to 20KHz. Sens. 89dB. PRICE £9.99 + £1.50 P&P ea.
8" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco etc.
 1 1/2" voice coil. Res. Freq. 38Hz. Freq. Resp. to 20KHz. Sens. 89dB. PRICE £11.99 + £1.50 P&P ea.

PANTEC HOBBY KITS. Proven designs including glass fibre printed circuit board and high quality components complete with instructions.

FM MICROTRANSMITTER (BUG) 90/105MHz with very sensitive microphone. Range 100/300 metres. 57 x 46 x 14mm (9 volt) Price: £8.62 + 75p P&P.
3 WATT FM TRANSMITTER 3 WATT 85/115MHz varicap controlled professional performance. Range up to 3 miles 35 x 84 x 12mm (12 volt) Price: £13.74 + 75p P&P.
SINGLE CHANNEL RADIO CONTROLLED TRANSMITTER/RECEIVER 27MHz. Range up to 500 metres. Double coded modulation. Receiver output operates relay with 2amp/240 volt contacts. Ideal for many applications. Receiver 90 x 70 x 22mm (9/12 volt). Price: £17.82. Transmitter 80 x 50 x 15mm (9/12 volt). Price: £11.27 P&P + 75p each. S.A.E. for complete list.



BURGLAR ALARM

Better to be 'Alarmed' than terrified. Thandar's famous 'Minder' Burglar Alarm System. Superior microwave principle. Supplied as three units, complete with interconnection cable. FULLY GUARANTEED.
Control Unit - Houses microwave radar unit, range up to 15 metres adjustable by sensitivity control. Three position, key operated fascia switch - off - test - armed. 30 second exit and entry delay.
Indoor alarm - Electronic swept freq. siren. 104dB output.
Outdoor Alarm - Electronic swept freq. siren. 98dB output. Housed in a tamper-proof heavy duty metal case.
 Both the control unit and outdoor alarm contain rechargeable batteries which provide full protection during mains failure. Power requirement 200/260 Volt AC 50/60Hz. Expandable with door sensors, panic buttons etc. Complete with instructions.
SAVE £148.00 Usual Price £228.85
BKE's PRICE £79.99 + £4.00 P&P
 ? Why buy a collection of self-assembly boards!

IDEAL for Work-shops, Factories, Offices, Home, etc. Supplied ready built.



OMP LINNET LOUDSPEAKERS

The very best in quality and value. Made specially to suit today's need for compactness with high sound output levels. Finished in hard wearing black vinyl with protective corners, grille and carry handle. All models 8 ohms. Full Range 45Hz - 20KHz
OMP 12/100 watts 20" x 15" x 12" £125.00 per pair
OMP 10/200 watts 18" x 15" x 11" £145.00 per pair
OMP 12/300 watts 20" x 15" x 11" £169.00 per pair
 Delivery: Securicor £8.00 per pair



STEREO CASSETTE DECK

STEREO CASSETTE DECK
 Ideal for installing into Disco and Hi-Fi cabinet/Consoles. Surface mounting (Horizontal). Supplied as one unit with all electronics including mains power supply.
 * Metal top panel Black finish
 * Piano type keys including pause
 * Normal/Chrome tape switch
 * Twin Vu Meters
 * 3 Digit counter
 * Slider Record Level control
 Size 171 x 317 mm Depth 110 mm
PRICE £35.99 + £3.00 P&P



1 K-WATT SLIDE DIMMER

* Control loads up to 1Kw
 * Compact Size 4 3/4" x 1" x 2 1/2"
 * Easy snap in fitting through panel/cabinet cut out
 * Insulated plastic case
 * Full wave control using 8 amp triac
 * Conforms to BS800
 * Suitable for both resistance and inductive loads. Innumerable applications in industry, the home, and disco's, theatres etc.
PRICE £12.99 + 75p P&P (Any quantity).




BSR P256 TURNTABLE

P256 turntable chassis * S shaped tone arm
 * Belt driven * Aluminum platter * Precision calibrated counter balance * Anti-skate (bias) device * Damped cueing lever * 240 volt AC operation (Hz) * Cut-out template supplied * Completely manual arm. This deck has a completely manual arm and is designed primarily for disco and studio use where all the advantages of a manual arm are required.
Price £33.60 each. + £3.00 P&P ea
ADC Q4 mag. cartridge for above. Price £4.99 ea. P&P 50p.



PIEZO ELECTRIC TWEETERS - MOTOROLA

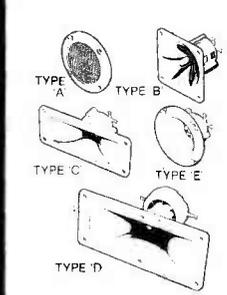
Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.



TYPE 'A' (KSN2036A) 3" round with protective wire mesh, ideal for bookshelf and medium sized Hi-Fi speakers. Price £4.90 each + 40p P&P.
TYPE 'B' (KSN1005A) 3 1/2" super horn. For general purpose speakers, disco and P.A. systems etc. Price £5.49 each + 40p P&P.
TYPE 'C' (KSN6016A) 2" x 5" wide dispersion horn. For quality Hi-fi systems and quality discos etc. Price £6.49 each + 40p P&P.
TYPE 'D' (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-fi systems and quality discos. Price £8.99 each + 40p P&P.
TYPE 'E' (KSN1038A) 3 3/4" horn tweeter with attractive silver finish trim. Suitable for Hi-fi monitor systems etc. Price £5.49 each + 40p P&P.
LEVEL CONTROL. Combines on a recessed mounting plate, level control and cabinet input jack socket. 85 x 85 mm. Price £3.99 + 40p P&P.

STEREO DISCO MIXER

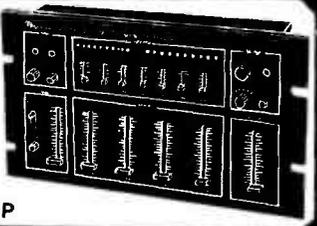
STEREO DISCO MIXER with 7 band graphic equaliser and 10 segment L.E.D. Vu Meters. Many outstanding features.
 5 Inputs with individual fader controls:-
 2 Mag. turntable, 2 Aux. plus Mic. with talk-over switch. Headphone monitor. Master output control with Hi-Low outputs. Compatible with our OMP Power Amplifiers.
 Size: 360 x 200 x 120 mm. Supply 240V/50Hz AC.
PRICE £119.99 + £3.00 P&P



B. K. ELECTRONICS
 UNIT 5, COMET WAY, SOUTHEND-ON-SEA, ESSEX, SS2 6TR TEL: 0702-527572

POSTAL CHARGES PER ORDER £1.00 minimum. OFFICIAL ORDERS WELCOME. SCHOOLS, COLLEGES, GOVERNMENT BODIES, ETC. PRICES INCLUSIVE OF V.A.T. SALES COUNTER VISA/ACCESS/C.O.D. ACCEPTED.

DIGEST

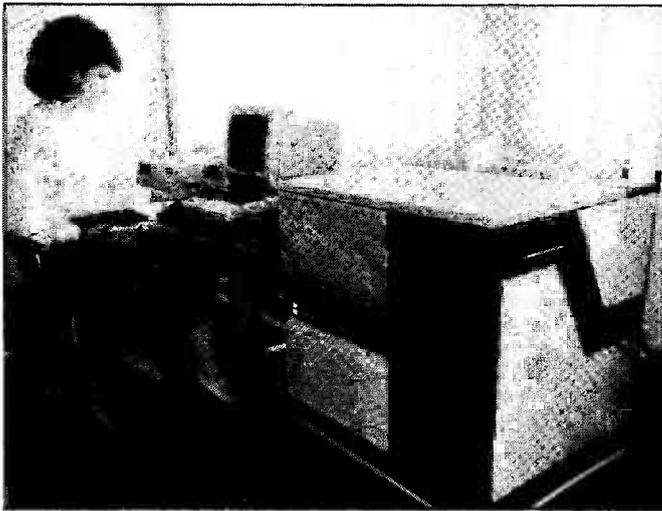

BT Voice Mail

Is your 'phone call a shot in the dark? You know the situation — you call them but they're not there so you leave a message. They call back but you've nipped

out for a few minutes and so it goes on.

For a mere £30,000 the basic VM600 Voice Mail system could revolutionise your communications. The system works like an electronic pigeon hole array in which voice messages can be dictated, edited to get the sense right

and deposited in the machines memory. At some later date the intended recipient can call up the memory and will receive whatever messages have been left.

The hardware consists of a free-standing equipment rack which contains the heart of the system and a number of pocket tone generators. The system can be connected directly between an existing push-button telephone system and the PABX without the need for any extra equipment. Users of the attached telephones can then access the VM600 using a personal password to place and retrieve messages. From other telephones or when calling in over the public network, the small tone generator is used.

When access to the system has been gained, spoken messages guide the user through the process of leaving or locating messages. This removes the need for typing or other skills, allowing the whole procedure to be carried out using only a button.

The VM600 is built around a dedicated microcomputer and the basic version has a 32M byte disc store which caters for up to 60 users and gives three hours worth of message storage. The system can be expanded to handle up to 600 users and give 30

hours of storage time. A separate console which can be sited up to 100m away from the main unit is used to set up the passwords and the facilities available to each user, and it can also be used to obtain statistics on usage and other operational information.

In addition to the facilities outlined above, the VM600 can send stored messages to up to sixty users or can be instructed to leave a message dormant until a certain date and time. For authorised users there are useful facilities like giving one message priority over others, checking that a message has been received, repeat calling for urgent messages and security coded messages for sensitive information.

The system is expected to be of interest to companies with sales or service staff who spend a lot of time away from the office but frequently need to send back information or receive instructions. It would also be useful for companies who deal regularly with people in other time zones as there are frequently only short periods during which business hours coincide.

For more information on the Voice Mail contact the local British Telecom sales office or ring 01-725 5577.

Personal Radiation Monitor

Impulse have recently introduced a simple to use, pocket-sized personal radiation monitor. Monitor 4 combines new electronic techniques with simplicity to provide an effective radiation alert which gives maximum user protection.

Monitor 4 has no external wires


or probes and is sensitive to a broad spectrum of ionizing radiation including alpha, beta, gamma and X-Rays. The level of radiation is indicated by an easy-to-read meter, a count light and a bleeper that can be switched off for silent monitoring.

The monitor reads in three ranges from 0-50mr/h and uses an industry standard halogen-quenched GM tube with a mica end window. It is easily calibrated and runs for up to 2,000hrs on one 9V alkaline battery at background

radiation levels.

The unit detects alpha down to 2.5 MeV and typical detection efficiency at 3.6 MeV is more than 80%. Beta is detected at 50 keV with 35% typical efficiency; typical efficiency of 150 keV is 75%. Gamma and X-rays are detected down to 10 keV typically through the end window and 40 keV minimum through the case.

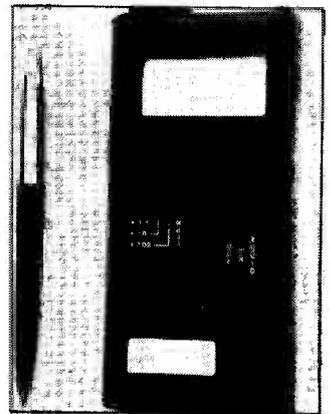For further information contact Impulse Sales & Marketing, 29a Egerton Street, Chester CH1 3ND.



Don't look now, but that handsome bloke standing between Cirkit Chief Executive Christopher Sawyer (right) and Richard Bulgin, Head of Consumer Services, is your very own editor, Dave Bradshaw. The occasion was the launch of Cirkit's first catalogue which contains all the products listed by their predecessors, Ambit, as well as a number of new lines. It costs 85p and includes three vouchers worth one pound each when presented with orders worth £15 or more. The catalogue is on sale at branches of W.H. Smith throughout the country or may be obtained direct from Cirkit, Park Lane, Broxbourne, Hertfordshire EN10 7NQ, tel 0992-444111.



AM/FM Radio

Upon reflection, we realise that we should have quoted the order numbers for the inductors and filters in this project as they're rather hard to find in Cirkit's catalogue! The order numbers are as follows:

YMRS 16726 (L4) 35-67260 (42p); CFU 050D (L5) 16-05006 (84p); YMCS 2A740 (L6) 35-07400 (42p); CLNS 30569 (L7) 35-05690 (66p); SFE10.7MA (F1, 2) 16-10755 (49p); CDA 10.7MA (F3) 16-10770 (84p). Prices quoted here are taken from Ambit's most recent catalogue, but need VAT and p&p.

Rotary Coded Dilswitches


A range of 10 position and 16 position ERG dual-in-line switches for PCB mounting is now available from Semiconductor Supplies International. The switches are expected to find employment in a wide range of control applications, and their memorability has been further enhanced by the adoption of a punning title almost worthy of ETI — they are to be called dial-in-line switches!

Three types are available, two with knob operation and one with a screwdriver slot. One type is suitable for vertical or horizontal mounting on the edge of a PCB and all are fully sealed and suit-

able for flow soldering and solvent cleaning.

Contact ratings are 125 mA, 30 VDC with an initial contact resistance of typically 50 mΩ maximum at 10 mVDC/10 mA. The insulation resistance is 100 MΩ minimum at 240 VDC for one minute, and the life within rated load is 20,000 rotary detent steps.

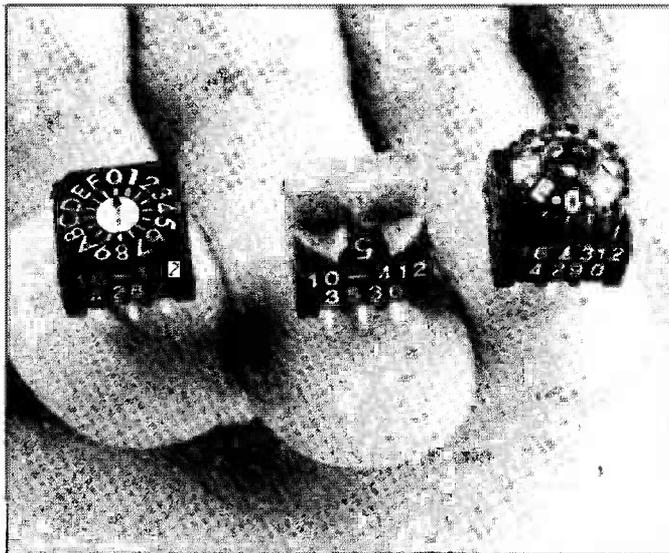The dimensions are 10 × 10 × 6 mm for screwdriver operation and 10 × 10 × 11 mm for the switch with the large knob. Maximum contact resistance found when testing to five million dry circuit switching operations monitored at 10 mVDC/10 mA was less than 20 mΩ. Semiconductor Supplies International Ltd, Dawson House, 128-130 Carshalton Road, Sutton, Surrey SM1 4RS, tel 01-643 1126.



Sound Moves

The re-organisation of A.F. Bulgin and Company PLC, one of the results of which is the recent re-appearance of Ambit under the new name of Cirkit, continues apace. Soundex Ltd, manufacturers of peak pro-

gramme meters, drive amplifiers and audio measuring sets, have been purchased from Bulgin by professional broadcast equipment suppliers Allotrope Ltd. Allotrope plan to extend the Soundex range with the addition of complementary products in the near future and have appointed Cirkit as distributors. The re-organisation allows Bulgin to

concentrate on its traditional manufacturing interests and the newly-formed Power Conversion Division while Cirkit Holdings PLC undertakes distribution.

Allotrope Ltd, 114 Wardour Street, London W1V 3LP, tel 01-434 3344. A.F. Bulgin and Company PLC, Bypass Road, Barking, Essex IG11 0A2, tel 01-594 5588.

● Marco Trading have issued a 124-page catalogue which lists their range of electrical fittings, connectors, test equipment, semiconductors and general components and even valves. The catalogue comes with an order form, reply-paid envelope and special offers list and is available from Marco Trading, The Maltings, High Street, Wem, Shropshire SY4 5EN, tel 0939-32763.

BBC Loudspeaker Agreement

The BBC has signed a licence agreement with the two British companies, Spondor Audio Systems Ltd and Swisstone Electronics Ltd, which allows them to manufacture the medium size, high quality, LS5/9 Studio Monitoring Loudspeaker. The agreement will enable these two

companies to market the loudspeaker worldwide.


The LS5/9 cabinet is only a quarter of the volume of the BBC's principal, much larger, high quality monitor the LS5/8, but the sound reproduction is a close approximation. The dimensions are 280 mm wide, 460 mm high, and 275 mm deep, and the weight is only 14 kg. As a result it is ideal for use where portability is required or where space is limited.

The loudspeaker uses two drive units with a passive crossover,

and an equaliser which provides a flat, free-field axial response over the range 50 Hz to 16 kHz. The tweeter is a proprietary soft dome type, and the low frequency unit is a BBC design which uses a polypropylene diaphragm. The levels of coloration and harmonic distortion are very low. A 50 W amplifier is required to obtain the maximum sound level output of 105 dB relative to 20 μPa at 1 m.

Engineering Information Department, BBC Broadcasting House, London W1A 1AA, tel 01-927 5432.

● Rockwell international have brought out the second edition of their 1984 data book. Its 1362 pages cover their entire line of solid-state devices and board-level micro-computer products and there are sections on 8 and 16 bit microprocessors, memory products, intelligent display controllers and integral and stand alone modems. Contact Rockwell International Ltd, Semiconductor Products Division, Heathrow House, Bath Road, Hounslow TW5 9QQ, tel 01-759 2366.

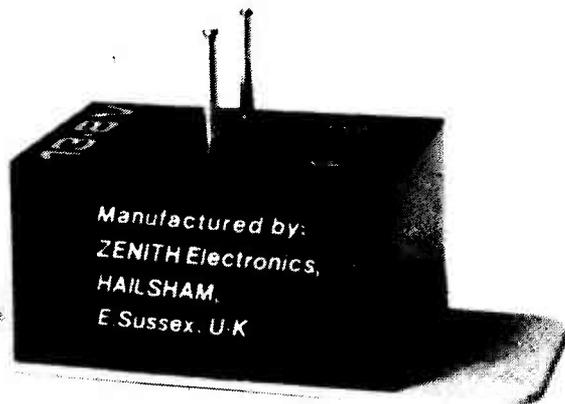

Hybrid Protector Modules

Zenith have introduced a range of overvoltage protection modules (OVPs) which are designed to protect sensitive electrical and electronic circuits from supply voltage transients. The modules come in nine standard voltage trip ratings and simply connect across the output terminals of any current-limited DC supply.

The modules employ circuitry that contains hybrid thick-film integration and are potted in epoxy compound for thermal stability. There are four basic models available rated at 3, 5, 15 and 25 amps, each of which can be supplied with any of the nine standard trip voltage ratings between 5 and 30 V DC. Special versions operating at other voltages are also available to order. The modules measure 30 × 20 × 15 mm and connection is via twin Molex connector pins or 6 mm spade terminals.

Zenith Electronics, 21 Station Road Industrial Estate, Hailsham, East Sussex BN27 2EW, tel 04353-2647.

QUALITY COMPONENTS FROM CRICKLEWOOD! This list contains only a FRACTION OF OUR STOCK, which is constantly being updated. Prices quoted are for "one-offs" - quantity discounts by negotiation. Official orders from Schools, Colleges, Goods Dept etc welcomed. WE SPECIALISE IN CREDIT CARD PHONE ORDERS. A quick call will check stock position and current prices. Add 60p p&p + 15% VAT to all orders. All in-stock items despatched same day unless notified.

CRICKLEWOOD

ELECTRONICS LTD

40 CRICKLEWOOD BROADWAY

LONDON NW2 3ET

01-452 0161/01-450 0955 Tlx: 914977

PRICES SUBJECT TO CHANGE




RESISTORS	10/16V 18p 10/35V 27p 10/15V 22p 15/16V 30p 15/25V 32p 22/26V 36p 22/16V 41p 33/10V 30p 10/10M 10p 47/6.3V 34p 47/16V 75p 1W E12 15p 2W E12 15p	7442 58p 7444 65p 7445 75p 7446 75p 7447 75p 7448 75p 7450 29p 7451 29p 7452 29p 7453 29p 7454 29p 7460 29p 7470 49p 7472 49p 7473 35p 7474 49p 7475 49p 7476 49p 7480 1.29p 7481 1.29p 7482 1.29p 7483 9p 7484 9p 7485 9p 7489 9p	74LS112 45p 74LS113 39p 74LS114 39p 74LS122 59p 74LS123 59p 74LS124 1.19p 74LS125 55p 74LS126 55p 74LS132 49p 74LS133 39p 74LS138 89p 74LS145 99p 74LS147 1.49p 74LS148 2.59p 74LS151 59p 74LS153 59p 74LS154 2.35p 74LS157 403p 74LS158 75p 74LS162 75p 74LS163 85p 74LS164 85p 74LS168 99p 74LS169 1.29p 74LS170 99p 74LS173 99p 74LS175 85p 74LS181 1.05p 74LS181 1.45p 74LS181 1.45p 74LS190 85p 74LS191 85p 74LS192 85p 74LS193 85p 74LS194 85p 74LS195 85p 74LS196 65p 74LS197 65p 74LS222 1.15p 74LS240 99p 74LS241 99p 74LS242 99p 74LS243 99p 74LS244 99p 74LS245 99p 74LS247 1.65p 74LS249 1.20p 74LS251 1.20p 74LS252 1.20p 74LS253 75p 74LS254 75p 74LS255 75p 74LS259 99p 74LS261 1.19p 74LS262 99p 74LS266 55p 74LS271 1.49p 74LS272 1.75p 74LS273 1.75p 74LS279 75p 74LS280 75p 74LS283 75p 74LS290 75p 74LS293 65p 74LS295 75p 74LS298 75p 74LS299 75p 74LS321 1.75p 74LS322 1.75p 74LS326 2.99p 74LS327 2.99p 74LS347 1.75p 74LS348 1.75p 74LS351 1.75p 74LS352 1.75p 74LS353 1.75p 74LS362 1.99p 74LS365 49p 74LS366 49p 74LS367 49p 74LS373 2.80p 74LS374 2.80p 74LS378 3.45p 74LS381 3.45p 74LS382 3.45p 74LS383 3.45p 74LS499 3.45p 74LS500 3.45p	4006 89p 4007 25p 4008 89p 4009 89p 4010 29p 4011 29p 4012 29p 4013 29p 4015 65p 4016 45p 4017 45p 4018 59p 4019 59p 4020 99p 4021 99p 4022 99p 4023 49p 4024 99p 4025 99p 4026 53p 4027 89p 4028 89p 4029 89p 4030 89p 4031 1.60p 4032 1.60p 4033 1.60p 4034 1.99p 4035 1.99p 4036 2.69p 4037 1.19p 4038 1.19p 4039 1.19p 4040 1.19p 4041 1.19p 4042 1.19p 4043 1.19p 4044 1.19p 4045 1.19p 4046 89p 4047 75p 4048 54p 4049 45p 4050 45p 4051 75p 4052 75p 4053 75p 4054 85p 4055 85p 4056 85p 4057 85p 4058 85p 4059 4.49p 4060 2.79p 4061 3.39p 4062 3.19p 4063 3.19p 4064 3.19p 4399 3.19p 4400 3.19p	AD0C817/ 100A ask INS1771 1.29p RO25131C 7.50p RO25130C 7.50p SAA5000 1.75p SAA5001 1.68p SAA5002 1.75p SAA5003 1.75p SAA5004 1.75p SAA5005 1.75p SAA5292 1.7
------------------	---	--	--	--	---

Mitsubishi MSX Micros

Mitsubishi Electric (UK) Limited, the UK manufacturing and marketing Division of the Mitsubishi Electric Corporation, has announced its version of the MSX range of home computers. Developed in conjunction with Microsoft in America, the MSX range was conceived to provide a common stan-

dard in home computing and Mitsubishi is the only company so far to offer a choice of MSX computers.

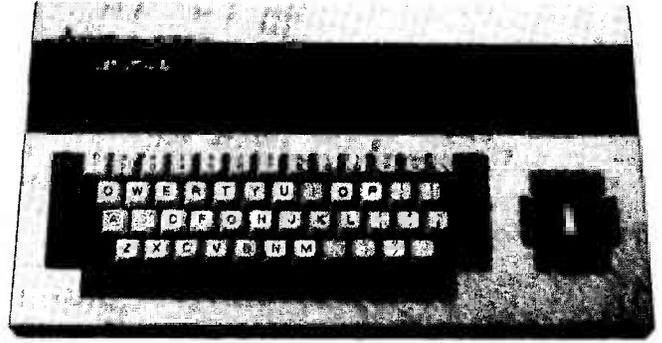The two systems—ML-F80 and ML-F48—are based on a Z80-equivalent chip. The ML-F80 has 64KB RAM, the ML-F48 32KB, and both systems have 32KB ROM, with the ML-F48 being expandable to its larger stablemate. The keyboards are ASCII layout and include full alphanumeric and special characters. There are also five special function keys, which, using the shift key, give the home programmer




ten possible programmable functions.

The screen display is 40 characters × 24 lines in text mode and 192 × 256 dots in graphics mode. Both systems also provide a range of sound effects. A number of socket outlets are incorporated on the computers, including a Centronics printer interface. Others are for joystick, ROM cartridges, audio, video and cassette units and of course TV.

A range of games software is already available for MSX computers, and the fact that Mitsubishi offers two systems

provides the user with a greater choice of programs. Software packages include home budget, word processing and database programs, language courses and games. The computers also run Microsoft extended Basic.

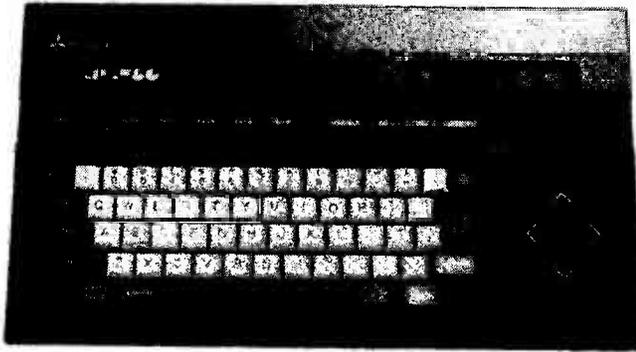Mitsubishi's two MSX systems will be available from its existing video and hi-fi outlets from November, at £299 for the ML-F80 and £249 for the ML-F48. Mitsubishi Electric (UK) Limited, Hertford Place, Denham Way, Maple Cross, Rickmansworth, Herts WD3 2BJ, tel 0923-770000.



Multipurpose Function Generator


New from Global Specialties Corporation is the Model 2005 multipurpose function generator which provides sine, triangle, square, ramp and TTL pulse waveforms with variable amplitude, symmetry and offset over a 50mHz to 5MHz frequency range. The output can be continuous, gated or triggered either by an external signal or by a front panel manual switch.

When the instrument is used as a sweep generator, an internal ramp with a variable duration provides a recurring linear sweep over a 1000:1 (linear) or 10,000:1

(logarithmic) frequency range. The maximum output amplitude is 20V into an open circuit or 10V into 50Ω and the signal can be attenuated at 20dB, 40dB or 60dB.

Other features include an adjustable DC offset voltage of ±10V into open circuit or ±5V into 50Ω, and the ability to be frequency modulated with an external signal using V_{CO} IN as the frequency modulation input. With a dial accuracy of ±5% of full scale and jitter of less than 0.1%, the instrument has a 1ms to 5s sweep rate and a sweep output of 0 to 5V ramp.

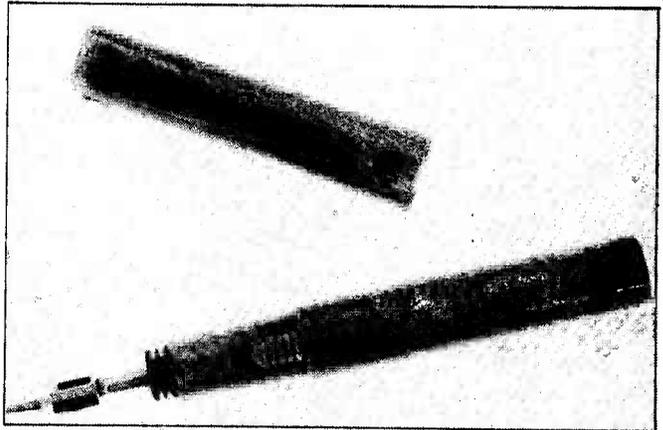The Model 2005 costs £632.50 inclusive of VAT and postage and is available from Global Specialties Corporation, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ, tel 0799-21682



Portable Butane Soldering Iron

Greenwood Electronics is launching a new butane powered portable soldering iron, the Oryx Portasol. Little bigger than a felt tip pen, the Portasol works on entirely different principles from conventional gas-powered irons. There is no flame during operation, the chemical energy of the butane gas being converted directly to heat by means of a patented catalytic converter in the solder tip. Conversion rate is adjustable to provide control over tip temperature and, at its maximum setting, the iron delivers power equivalent to a 60

watt electric soldering iron, the tip temperature being adjustable between 250 and 450°C.

The Oryx Portasol iron will run for up to 60 minutes on its internal gas supply and refuelling, which takes seconds, is identical to filling a gas cigarette lighter. The same principles that make gas cigarette lighters safe are applied to the Portasol.

The Portasol can be carried in the pocket. It is supplied with a protective cap and is immediately ready for use, the cap including an igniter to start the catalytic conversion.

The dimensions of the Portasol are 175mm long × 19mm diameter, and replacement tips—which include the converter—are readily available. Greenwood Electronics, Portman Road, Reading, Berkshire RG3 1NE, tel 0734-595844.



for low-cost training in real-life robotics

The advanced design of the Neptune 2 makes it the lowest cost real-life industrial robot.

It is electro-hydraulically powered, using a revolutionary water based system (no messy hydraulic oil!)

It performs 7 servo-controlled axis movements (6 on Neptune 1) – more than any other robot under £10,000.

Its program length is limited only by the memory of your computer.

Think what that can do for your BASIC programming skills!

And it's British designed, British made.

Other features include:

Leakproof, frictionless rolling diaphragm seals.

Buffered and latched versatile interface for BBC VIC 20 and Spectrum computers.

12 bit control system (8 on Neptune 1).

Special circuitry for initial compensation.


Rack and pinion cylinder couplings for wide angular movements.

Automatic triple speed control on Neptune 2 for accurate 'homing in'.

Easy access for servicing and viewing of working parts.

Powerful – lifts 2.5 kg. with ease.

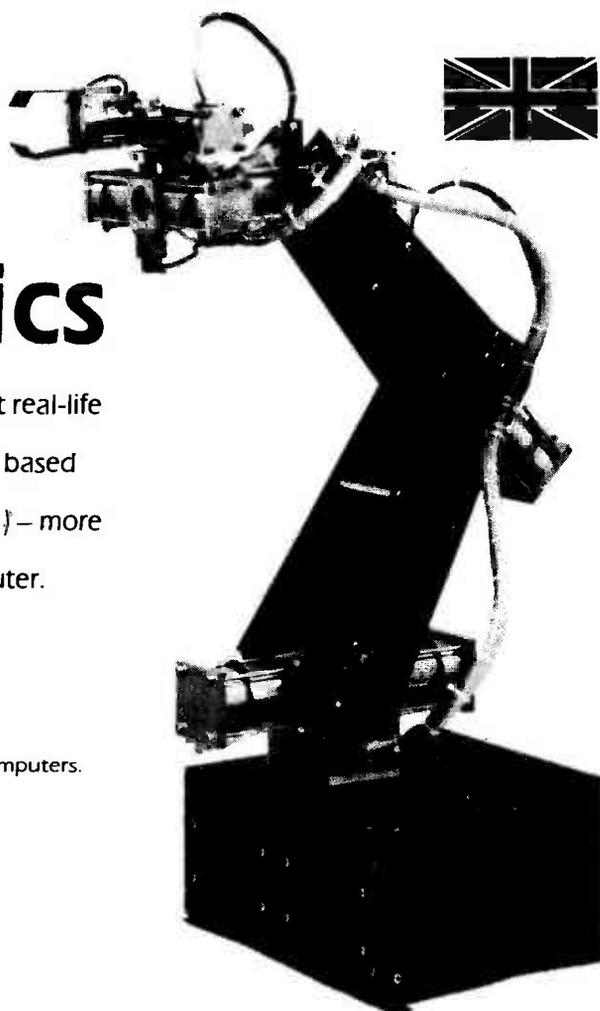Hand held simulator for processing (requires ADC option).



Neptune robots are sold in kit form as follows:

Neptune 1 robot kit (inc. power supply)	£1250.00	ADC option (components fit to main control board)	£95.00
Neptune 1 control electronics (ready built)	£295.00	Hydraulic power pack (ready assembled)	£435.00
Neptune 1 simulator	£45.00	Gripper sensor	£37.50
		Optional extra three fingered gripper	£75.00
Neptune 2 robot kit (inc. power supply)	£1725.00	BBC connector lead	£12.50
Neptune 2 control electronics (ready built)	£475.00	Commodore VIC 20 connector lead and plug-in board	£14.50
Neptune 2 simulator	£52.00	Sinclair ZX Spectrum connector lead	£15.00

All prices exclusive of VAT and valid until the end of **March 1985**


desk-top robot

This compact, electrically powered training robot has 6 axes of movement, simultaneously servo-controlled. It gives smooth operation, and its rugged construction makes it ideal for use in educational establishments. Other features include long-life bronze and nylon bearings, integral control electronics and power supply, special circuitry for inertial compensation, optional on-board ADC, and hand-held simulator as the teaching pendant. Like Neptune, Mentor's program length is limited only by your computer's memory. Programming is in BASIC.

Mentor is all-British in design and manufacture and comes in kit form at an astonishingly low price:

Mentor robot kit (inc. power supply)	£345.00
Mentor Control electronics (ready built)	£135.00
Mentor Simulator (requires ADC option)	£42.00
ADC option (Components fit to control electronics board)	£19.50
BBC connector lead	£12.50
Commodore VIC 20 connector lead and plug-in board	£14.50
Sinclair ZX Spectrum connector lead	£15.00

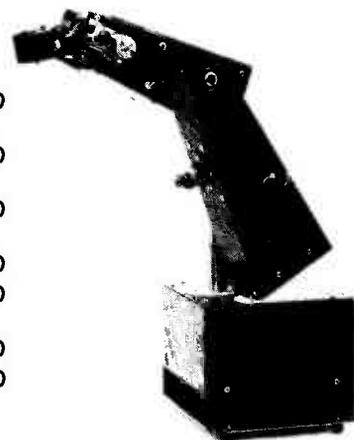All prices exclusive of VAT and valid until the end of **March 1985**



PORTWAY TRADING ESTATE, ANDOVER, HANTS SP10 3ET
TEL: (0264) 50093 Telex: 477019

2kV Isolation DIL Relays


C.P. Clare have introduced two new dual-in-line relays to complement their established DIL product families. Both versions have 2000 VAC isolation between coil and contact to cater for the growing number of applications where a high isolation is required.

The first type, designated DSS7, incorporates a standard 10VA rated dry reed switch as

used in the established PRMA/PRME series. Standard coil resistances are 500-2150 ohms.


The second, designated MSS7, incorporates a unique MMR mercury reed capsule which is completely non-position sensitive, thus allowing full PCB mounting flexibility for OEM equipment. MSS7 is rated at 30VA switching with a maximum contact resistance of 100 milliohms throughout its life of 200 million expected operations.

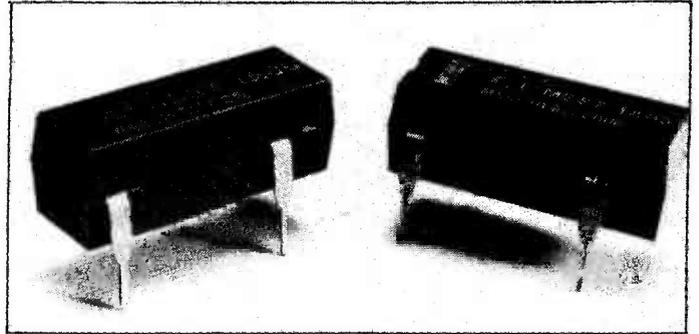Both relays have single, normally open contacts and are available with nominal operating voltages of 5, 12 and 24V DC. An



optional modification, the addition of a transient suppression diode to the coil, is available on both types.

For further information contact Ron Bannister, C.P. Clare Division, General Instrument (UK) Ltd, tel 08956-39901.

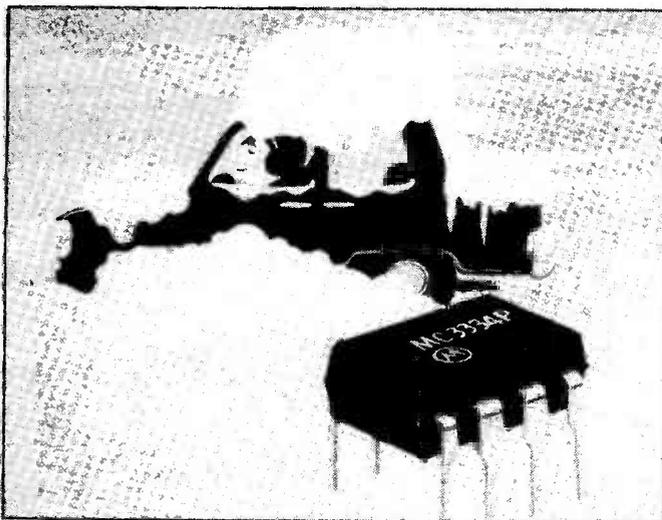

Auto IC

Motorola have added a high-energy ignition circuit to their range of automotive linear ICs. Originally designed to suit Delco five-terminal ignition applications, the MC3334 is said to meet the circuit timing and current control requirements of modern advanced ignition systems and offers optimised spark energy at minimum power dissipation.

The circuit is designed to process a control signal from a reductor (magnetic) type pick-up and generates a precisely-controlled ignition coil drive voltage via an external Darlington transistor. Features include adjustable dwell angle for optimum stored energy with minimum waste, adjustable peak output coil current and a rugged design which has input and output transient protection to reduce the risk of damage to the IC and Darlington. Very few external support components are required and none of the resistors are critical.

The MC3334 is available in an 8-pin plastic DIP package for PCB

mounting, a chip version and a 'flip' or 'bumped chip' version for inverted reflow assembly. Motorola claim that the pin-out adopted suits both thick-film and printed circuit module designs and allows layouts to be produced without crossovers.

Also new from Motorola is a series of DC-DC converter ICs which are said to offer twice the output current capability of existing 8-pin DIP DC-DC converters. The MC34063 series are intended for step-up or step-down voltage conversion over the range 2.5 to 40 volts and offer an output current of 1.5 amps. Quiescent current is a mere 2.4mA. All functional circuitry is contained within the ICs including temperature-compensated reference, oscillator, cycle-by-cycle current limiting and feedback sense for voltage regulation.

For information on these devices contact Motorola, quoting release number 30/84 for the ignition IC and 32/84 for the DC-DC converters. Motorola Ltd, European Literature Distribution Centre, 88 Tanners Drive Blakelands, Milton Keynes MK14 5BP, tel 01-902 8836.

Carrying Bags for Apples, Apricots and Acorns

For people who really can't put their micros down, Inmac now stock a series of specially designed carrying bags for the Apple II, Apple II Plus, Apple IIe, Apricot and BBC Micro Computers.

Made from strong, tear-proof Cordura nylon and thick, high density foam padding, these bags are tailored to provide a safe means of transportation. The wide-grip handles and the adjustable shoulder strap are made of seat-belt strength webbing for safety, and the zips are heavy duty industrial grade that will not rust

and open completely for easy loading.

A matching bag is available for the Apple II disk drive which can carry two drives and has a foam lined "wallet" that protects cables and provides padding between the drives. There is also a matching bag for an Apricot Monitor. All bags are lined with anti-static material and prices range from £17.00 to £27.50 each.

Delivery is ex-stock and can be same day for the London, Greater Manchester and Merseyside areas or next day for the rest of the country. The bags are available on a thirty day, risk-free trial period and are guaranteed for a year.

Further details can be found in Inmac's full-colour catalogue of over 1000 accessories for mini- and micro-computers which is available free from Inmac UK Limited, Davy Road, Astmoor, Runcorn, Cheshire WA7 1PZ, tel 09285-67551.



BBC Micro Computer System

ACORN COMPUTER SYSTEMS:
 BBC Model B Special offer... £320 (a)
 BBC Model B + Econet... £389 (a)
 BBC Model B + DFS... £409 (a)
 BBC Model B + DFS + Econet... £450 (a)

UPGRADE KITS
 A to B Upgrade Kit... £75 (c)
 DFS Kit... £95 (c)
 Econet Kit... £45 (c)
 Speech Upgrade Kit... £47 (c)

ACORN ADDON PRODUCTS:
 280 2nd Processor... £265 (a)
 6502 2nd Processor... £175 (b)
 Teletext Adaptor... £190 (b)
 IEEE Interface... £282 (b)
 Prestel Adaptor... £99 (b)
 RH Light Pen... £39.50 (c)

BBC FIRMWARE:
 1.2 Operating System ROM... £7.50 (d)
 BASIC II ROM... £22.50 (d)
 VIEW Word Processor Rom... £48.00 (c)
 WordWide Word Processor Rom... £34.00 (c)

BCPL ROM/Disc... £28.00 (d)
Utility ROMS:
 Disc Doctor/Gremlin Debug Rom... £28

EXMON/TOOL KIT ROM... £20 (a)
Printmaster (FX80)/Graphics ROM... £28 (a)
ULTRACALC spreadsheet ROM... £59 (a)

VIEWSHEET ROM... £52 (c)
COMMUNICATIONS ROMs
 Termi Emulator... £28 (d)
 Communicator... £59 (d)
 Commstar... £29 (d)

TORCH UNICOM products including the IBM Compatible GRADUATE in stock. For detailed specification on any of the BBC Firmware/Peripherals listed here or information on our complete range please write to us.

PRINTERS

EPSON
 RX80FT £225 (a) FX80 £315 (a) FX100 £450 (a)
KAGA TAXAN
 KP810 £249 (a) KP910 £369 (a)
JUKI 6100 £345 (a) **BROTHER HR15** £349 (a)

ACCESSORIES

EPSON
 Serial Interface: 8143 £28 (c) 8148 with 2K £58 (c)
 Paper Roll Holder £17 (c) FX80 Tractor Attachment £37 (b)
 Ribbons: FX/RX/MX 80 £5 (d) FX/RX/MX 100 £10 (c)
 RX/FX80 Dust Cover £4.50 (d)
KAGA TAXAN
 RS232 with 2K Buffer £85 (b) KP810/910 Ribbon £6.75 (a)
JUKI 6100
 RS232 with 2K Buffer £60 (b) Ribbon £2.50 (d)
 Tractor Attachment £99 (a) Sheet Feeder £199 (a)
 BBC Parallel Lead £7 (d) Serial Lead £7 (d)
 2000 Sheets Fanfold Paper with extra fine perforation
 9.5" x 11" £13 (b) 14.5" x 11" £18 (b)
 Self Adhesive Labels 2 3/4" x 1 7/16"
 Single Row £5.25/1000 (d) Triple Row £5/1000 (d)

MODEMS — All modems listed below are BT approved

MIRACLE WS2000:
 The ultimate world standard modem covering all common BELL and CCITT standards up to 1200 Baud. Allows communication with virtually any computer system in the world. The optional AUTO DIAL and AUTO ANSWER boards enhance the considerable facilities already provided on the modem. Mains powered £129 (b). Auto Dial Board/Auto Answer Board £30 (c) each. Software lead £4.50.

TELEMOD 2:
 Complies with CCITT V23 1200/75 Duplex and 1200/1200 Half Duplex standards that allow communications with VIEWDATA services like PRESTEL, MICRONET etc. as well as user to user communications. Mains powered. £64 (b).
BUZZ BOX:
 This pocket sized modem complies with V21 300/300 Baud and provides an ideal solution for communications between users, with main frame computers and bulletin boards at a very economic cost. Battery or mains operated. £52 (c). Mains adaptor £8 (d). BBC to Modem data lead £7.

DISC DRIVES

These are fully cased and wired drives with slim line mechanisms of high quality, Shuggart A400 standard Interface. Drives supplied with cables manuals and formatting disc for the BBC computer suitable. TEAC 80 track drives are supplied with 40/80 track switching as standard. All drives can operate in single or dual density format.

1x100K: TS55A TEAC 40 Track £100 (a) CS55A TEC with psu £135 (a)
 1x200K: TS55E TEAC 80/40 £155 (a) CS55E TEC with psu £155 (a)
 Sw
 1x400K: TS55F TEAC 80/40 £175 (a) CS400 Mit. with psu £185 (a)
 Sw
 2x100K TD55A 40T TAEC with psu £275 (a)
 2x200K TD55E 80/40 Sw TEAC with psu £380 (a)
 2x400K TD55F 80/40 Sw TEAC with psu £400 (a)
 2x400K TD55M 80T Mitsubishi with psu £375 (a)

3M 5 1/4" FLOPPY DISCS

High quality discs that offer a reliable error free performance for life. Each disc is individually tested and guaranteed for life. Ten discs are supplied in a sturdy cardboard box. Price per pack of ten:

40T SS DD £15 (c) 40T DS DD £21 (c)
 80T SS DD £24 (c) 80T DS DD £28 (c)

DRIVE ACCESSORIES

FLOPPICLENE Disc Head Cleaning Kit with 20 disposable cleaning discs ensures continued optimum performance of the drives... £14.50 (c)
 Single Disc Cable... £6 (d) Dual Disc Cable... £8.50 (d)
 10 Disc Library Case... £1.95 (c) 30 Disc Storage Box... £8 (c)
 30/40 Disc Lockable Box... £14 (c) 70/80 Disc Lockable Box... £19 (b)

MONITORS

MICROVITEC 14" RGB:

1431 Std Res... £195 (a)
 1451 Med Res... £260 (a)
 1441 Hi Res... £420 (a)
 1431 AP Std Res PAL/AUDIO... £215 (a)
 1451 AP Std Res PAL/AUDIO... £325 (a)
 1451 DQ3 Med Res... £239 (a)

Above monitors are now available in plastic or metal cases

KAGA Super Hi Res Vision III RGB Monitor £345 (a)

MONOCHROME MONITORS 12":

Kaga Green KX1201 G... £106 (a)
 Kaga Amber KX1201 A... £116 (a)
 Santo Green DM8112CX... £99 (a)
 Swivel Stand for Kaga Monochrome... £22.50 (b)

All monitors are supplied with leads suitable for the BBC Computer. Spare leads available.

ATTENTION

All prices in this double page advertisement are subject to tax changes without notice.
ALL PRICES EXCLUDE VAT
 Please add carriage 50p unless indicated as follows:
 (a) £8 (b) £2.50 (c) £1.50 (d) £1.00

SPECIAL OFFER

2764-25... £4.90
 27128-25... £18
 27128-30... £16
 6264-15... £28
 6262LP-15... £31
 6264-12... £35

GANG OF EIGHT INTELLIGENT FAST EPROM COPIER

Copies up to eight eproms at a time and accepts all single rail eproms up to 27256. Can reduce programming time by 80% by using manufacturer's suggested algorithms. Fixed Vpp of 21 & 25 volts and variable Vpp factory set at 12.5 volts. LCD display with alpha moving message. £395 (b).

SOFTY II

This low cost intelligent eprom programmer can program 2716, 2516, 2532, 2732, and with an adaptor, 2564 and 2764. Displays 512 byte page on TV — has a serial and parallel I/O routines. Can be used as an emulator, cassette interface. Softy II... £195 (b)
 Adaptor for 2764/2564. £25.00 (c)

UV ERASERS

All erasers with built in safety switch and mains indicator.
 UV1 B erases up to 6 eproms at a time... £47 (c)
 UV1 T as above but with a timer... £59 (c)
 UV140 erases up to 14 eproms at a time... £61 (b)
 UV141 as above but with a timer... £79 (b)

I.D. CONNECTORS

No of ways	(Speedblock Type)		Edge Conn.
	Header	Recep. table	
10	90p	85p	120p
20	145p	125p	195p
26	175p	150p	240p
34	200p	180p	320p
40	220p	190p	340p
50	235p	200p	390p

D CONNECTORS

No of Ways
 9 15 25 37

MALE:			
Ang.Pins	120	180	230 350
Solder	60	85	125 170
IDC	175	275	325 -
FEMALE:			
St Pin	100	140	210 380
Ang.pins	160	210	275 440
Solder	90	130	195 290
IDC	195	325	375 -
St Hood	90	95	100 120
Screen	130	150	175
Lock			

TEXTUOL ZIF

SOCKETS	
24-pin	£5.75
28-pin	£8.00
40-pin	£9.75

EDGE CONNECTORS

	0.1"	0.156"
2 x 6-way (dommodore)	—	300p
2 x 10-way	150p	—
2 x 12-way (vic 20)	—	350p
2 x 18-way	—	140p
2 x 23-way (ZX81)	175p	—
2 x 25-way	225p	—
2 x 28-way (Spectrum)	200p	220p
2 x 36-way	250p	—
1 x 43-way	260p	—
2 x 22-way	180p	—
2 x 43-way	385p	—
1 x 77-way	400p	500p
2 x 50-way (S100conn)	600p	—

EURO CONNECTORS

DIN 41612		
2 x 32 way St Pin	230p	275p
2 x 32 way Ang Pin	275p	320p
3 x 32 way St Pin	260p	300p
3 x 32 way Ang Pin	375p	400p
IDC Skt A + B	275p	
IDC Skt A + C	350p	

For 2 x 32 way please specify spacing (A + B, A + C).

AMPHENOL CONNECTORS

36 way plug Centronics (solder) 500p (IDC) 475p
 36 way skt Centronics (solder) 500p (IDC) 500p
 24 way plug IEEE (solder) 475p (IDC) 475p
 24 way skt IEEE (solder) 500p (IDC) 500p
 PCB Mtg Skt Ang Pin
 24 way 700p 36 way 750p

GENDER CHANGERS

25 way D type
 Male to Male... £10
 Male to Female... £10
 Female to Female... £10

RS 232 JUMPERS

(25 way D)	
24" Single end Male	£5.00
24" Single end Female	£5.25
24" Female Female	£10.00
24" Male Male	£9.50
24" Male Female	£9.50

DIL SWITCHES

4-way	90p	6-way	105p
8-way	120p	10-way	150p

TELEPHONE CONNECTORS

4 way plug	110p
6 way plug	180p
6 way rt ang.skt	180p
Flexible cable	
4 way	50p/m
6 way	72p/m

RIBBON CABLE

(grey/metre)			
10-way	40p	34-way	180p
16-way	80p	40-way	180p
20-way	85p	50-way	200p
26-way	120p	64-way	280p

DIL HEADERS

Solder		IDC	
14 pin	40p	100p	
16 pin	50p	110p	
18 pin	80p		
20 pin	75p		
24 pin	100p	150p	
28 pin	200p		
40 pin	200p	225p	

MISC CONNS

21 pin Scart Connector. 200p
 8 pin Video Connector. 200p

LINEAR ICs

COMPUTER COMPONENTS

Table listing various linear ICs including 74 Series, 74LS Series, and 74S Series. Columns include part numbers, pin counts, and prices.

Table listing various linear ICs including 4000 Series, 4010 Series, and 4020 Series. Columns include part numbers, pin counts, and prices.

Table listing various computer components including PROMs, EPROMs, MEMORYs, SUPPORT DEV CES, TRANSISTORS, OPTO-ELECTRONICS, OPTO-ISOLATORS, LEDS, COUNTERS, and CHARACTER GENERATORS. Columns include part numbers, pin counts, and prices.

TELEPHONOMATIC LTD. MAIL ORDERS TO: 17 BURNLEY ROAD, LONDON NW10 1ED. SHOPS AT: 17 BURNLEY ROAD, LONDON NW10. PLEASE ADD 50p p&p & 15% VAT. Orders from Government Depts. & Colleges etc. welcome. Detailed Price-List on request. Stock items are normally by return of post.

DIGITAL DELAY LINE

Delay things a little — or anything up to a few seconds — by building this versatile, quality delay unit. Design and development by Ray Lowe.

This delay line has been designed and developed with value for money as the pre-requisite, and the unit presented must be the best value around for the ambitious music maker or sound recordist. It is a high quality unit and contains some novel circuitry in the digital/analogue conversion stages which could be useful elsewhere.

The unit offers some features not found on many lower-end commercial products such as percussion, freeze and full control over bandwidth versus maximum delay time.

Words

The input signal is represented as nine bit data words. This has been found to give good dynamic performance without resorting to compansion and its undesirable 'pumping' or 'breathing' type side effects. The minimum memory requirement is 4 K, ie the number of memory chips that have to be present for the unit to operate is two, which helps keep minimum construction cost low.

This minimum configuration gives a maximum useful delay of a couple of hundred milliseconds, plus associated effects such as chorus, flanging, etc. However, the basic PCB can accept a further 13 K bytes, enough for 350 milliseconds at a full bandwidth of about 16.5 kHz through to (continuously variable) 1.3 seconds at 5 kHz bandwidth.

An optional memory expansion board may be easily added, giving a total of 36 K bytes capacity which will double the above delay figures.

Effects

Many interesting and useful effects can easily be obtained including chorus, flanging, vibrato, reverb (pseudo), slapback and long echoes, single or multiple echoes decaying over many seconds, scrambling, double tracking, etc. In addition, a sound from any source may be sampled and frozen in memory, much like a continuous tape loop, to be recalled or triggered either internally or externally (by a sequencer or drum contact for example) at any time; also there are various ways that the same can be modified. On a different tack, if you have a scope then, by using the freeze facility, you could give it audio frequency storage capability!

Inputs

Since it has a high input impedance, the unit will accept inputs from most sources, including electric guitar, synthesiser, microphone, hi-fi tape output, and many others. Input signals in the range 200 mV to 2.5 V P-P are suitable.

The frequency characteristics of the pre-emphasis used have been tailored for electric guitar as well as normal signals so as to keep quantisation distortion at bay on low strings (see later for more details) whilst a hi-fi tape signal will be virtually indistinguishable from the original when using the maximum bandwidth setting.

A switch is also available which doubles the nominal sampling rate; this can be used for special effects or for enhanced fidelity when using only short delay.

Emphasising Pre-emphasis

The average music signal, or voice, is bass-heavy as far as amplitude is concerned, although most information is carried by mid-range frequencies. This is in general terms, and a fair spread exists in the power spectrums of everyday audio signals.

In the case of electric guitar, the process of converting mechanical to electrical energy strongly favours the thicker, lower strings. A strong twang on a low string may well overload an input stage, whereas the same twang power on a top string will generate a much smaller voltage. However, the signal amplitude produced will decay very rapidly (exponentially) with time so that, unless a sustain/compression unit is used, the guitar signal has a large dynamic range.

This problem is especially relevant if the circuitry following the input has a limited dynamic range that it can handle, which is the case when using relatively short data words to represent musical signals in an analogue to digital conversion. Compact disc players use 16 bits per sample word to achieve their dynamic range but the design presented here uses nine. Why not use more? Because the cost of A/D converters escalates rapidly above eight bits.

In order to give both high and low frequencies a better chance of simultaneously being within dynamic range, high frequencies are boosted, with special consideration given to the mid-range; in other words, the signal is pre-emphasised before the analogue to digital conversion stage. The

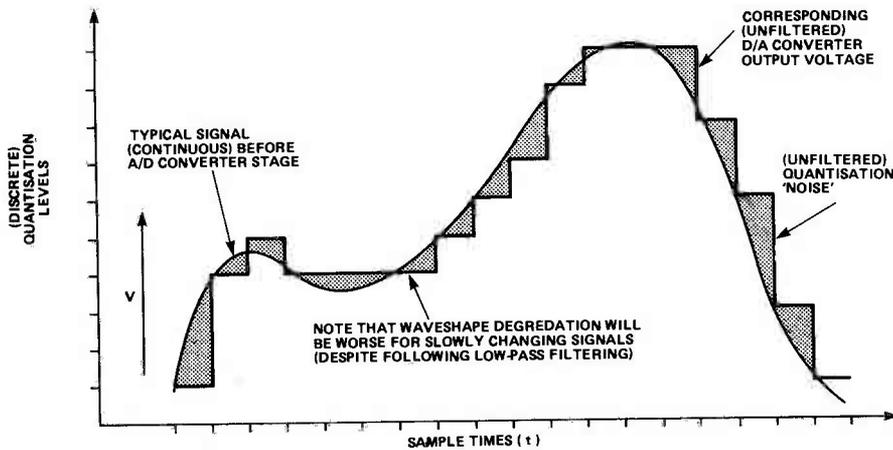


Fig. 1 The generation of quantisation noise during A-D conversion.

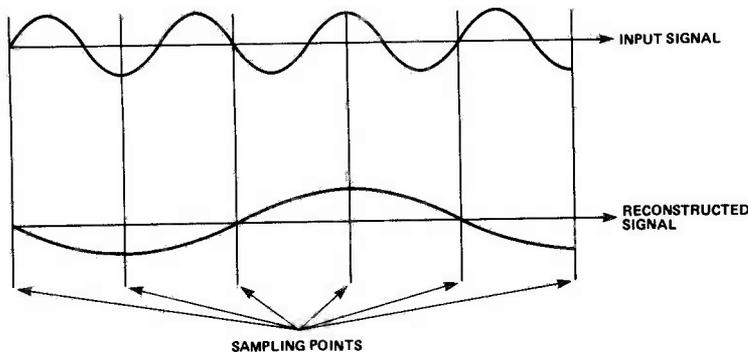


Fig. 2 How the use of too low a sampling rate leads to the reconstruction of a different 'alias' frequency.

pre-emphasis characteristic used has been determined by experiment over a wide range of signal sources.

Quantisation

Use of pre-emphasis has another benefit, namely that of killing off most of the quantisation noise.

Quantisation noise arises as a result of the finite number (2^n , where n is the word length) of analogue levels available with which to represent real (continuous) signals using pulse code modulation. Real signals are thus rounded up in the conversion process to the nearest discrete value mapped by a digital code. When the digital code is converted back to analogue, the resultant errors are ramp-like excursions away from the original waveform — see Fig. 1.

These error excursions sound like noise, called quantisation noise, accompanying the signal proper. Since these error excursions have fast leading edges, the resultant noise has a wide frequency spectrum (from elementary Fourier analysis) and it is

particularly objectionable when superimposed upon low frequency sinusoidal type waveforms, emerging as an annoying buzz in the background.

Buzz Off!

Use of pre-emphasis before A/D conversion obviously requires that de-emphasis be used after D/A conversion. Fortunately this 'treble cut' operates on the quantisation noise as well, thus reducing its high frequency content and therefore its overall unpleasantness.

Sampling Complications

There is a well-known theorem, called the Nyquist sampling theorem, which says that to get an accurate representation of a signal as a stream of sample values, the samples must be taken at a rate that is at least twice the maximum frequency present in the signal. Failure to meet the requirement of the theorem will result in a phenomenon known as *aliasing*, which is demonstrated in Fig. 2. Although this diagram misses out many of the technical niceties (for instance, the reconstructed signal

would not be a nice, clean sine wave), it does show what happens — that if a frequency higher than half the sampling frequency is input, it will actually appear at the output as a different, 'alias' frequency, which is lower than half the sample frequency. In audio terms, the sound becomes noticeably 'gurgled'; obviously, we must limit the bandwidth of the signal before it is sampled.

In this design, the sampling rate and the bandwidth limit are coupled by the choice of a switched-capacitor filter to do the low-pass filtering. The same master clock is used to drive both the filter and the sampling, so that as one changes, the other changes to keep pace; the particular filter used is configured as a sixth-order low-pass filter.

In the real world, infinite cut-off filters are not available, so some aliasing always exists; however, with the filter used here, the level of the aliasing is such that it is masked by other imperfections such as quantisation distortion.

The Unit Together

The block diagram of the whole unit is shown in Fig. 5. The pre-emphasis and anti-aliasing filters have already been explained. To make signal-handling easier, the signal is made uni-polar (ie, rectified) and a polarity bit, bit 9 (or D8), is generated by the polarity remover. It may seem rather a waste of effort to do this here, but the equivalent would be to use a nine-bit A-to-D rather than an eight-bit device (obviously the D-to-A would also have to be nine-bit too), and this would add quite a lot to the cost.

The final analogue stage before conversion is the sample and hold and the purpose of this unit is to ensure that the A-to-D sees a steady voltage while it is doing a conversion; this will help to prevent errors occurring.

The next stage in the signal path is the A-to-D itself; this is a continuous approximation device, which means that it works by testing to see which bits should be on or off, starting with the most significant bit (MSB) and working to the least significant (LSB). It takes about $10 \mu\text{s}$ to do a conversion. The converted signal is passed to the static memory.

The address counter points to the memory location in use at any one time, and while the unit is working normally it will con-

The voltage-controlled oscillator used, and from which all the system timing is derived, is contained within a 4046 phase-locked-loop chip, IC37; only the VCO is used from this device. With no external capacitor connected between pins 6 and 7, the VCO will run at about 1 MHz, its maximum frequency with a 5V supply. Normally pin 5 is held low by R59, enabling the oscillator (but see later).

The master clock, CLK, is fed directly to the switched capacitor filter stages on the analogue board to control their cut-off frequency, the mark/space ratio of CLK being adequate even for this pur-

pose. The CLK frequency is divided by either 1 or 2, selection being made by SW10, before it drives decade counter IC35. In this way the sample rate/filter frequency ratio can be selected as either 2.5:1 or 5:1 approx.

IC35 is a five-stage Johnson decade counter, and is used to produce most of the timing requirements of the memory read/write and the A-to-D and D-to-A converters — see the timing diagram Fig. 4. The complete control cycle occupies 10 CLK cycles. For the purpose of explanation, let us assume that a control cycle begins with Q_0 output high. The address of the memory location

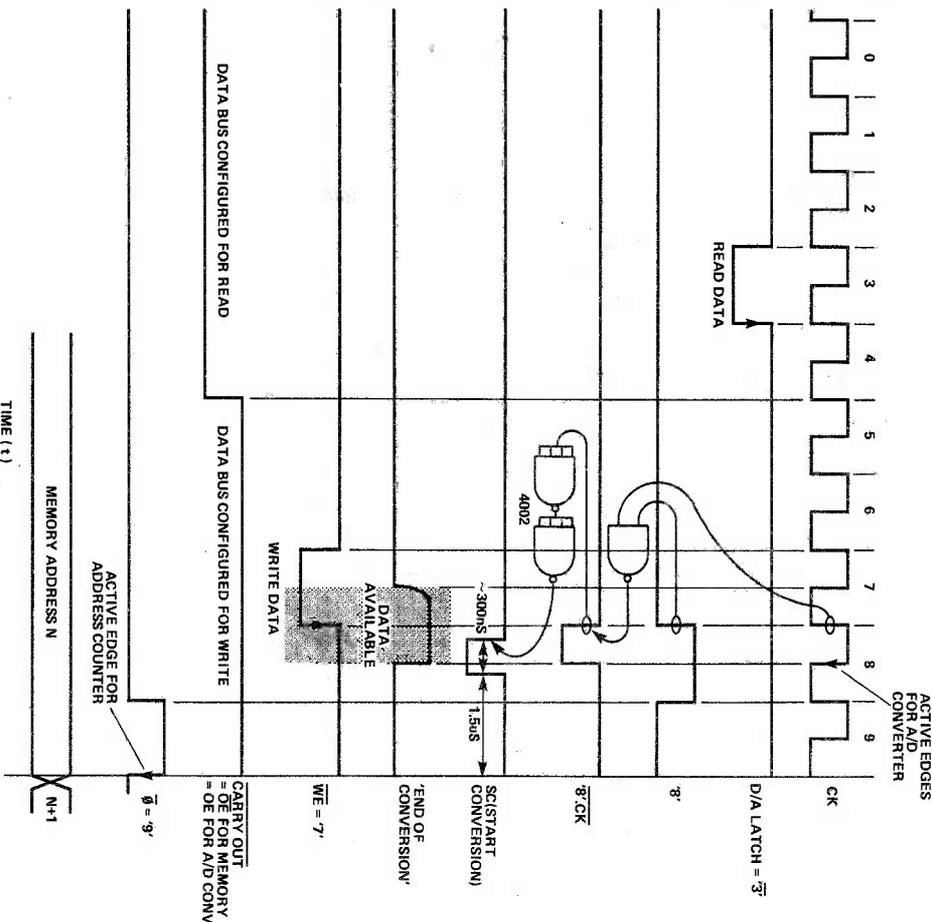


Fig. 4. Timing diagram for the logic.

currently being accessed is given by the contents of (non-synchronous) ripple counters IC32, IC33. Suppose that at the start of a cycle the address is n . Upon receipt of the next rising CK edge the decade counter, IC35, will advance to $n+1$. Provided that SW9 is open, IC29 pin 8 will be high and IC29 pin 10 will pulse WR low, writing the result of the last A-to-D conversion into memory location n . (Assume for the time being that data is available etc.) If SW9 is closed then IC29d is disabled and the contents of memory are not overwritten.

It is now time to start the next A-to-D conversion process. The ZN427 specification states that the active negative edge of SC must not occur within 200 ns of a CK clock edge. On receipt of the next CK edge, IC35 is clocked so that Q_0 is the high output, Q_1 is gated via IC29c with CK to produce a negative-going pulse for only the first half of a CK cycle. Passing this pulse through two inverting stages made from CMOS quad-input NOR gates delays it for the required minimum amount, due to the long propagation delays of the 4002. The SC pulse is applied to the start conversion input of the A-to-D converter. The next CK edge of the cycle puts Q_1 high and is also the point at which the A-to-D, a successive approximation type, decides on the MSB value for this conversion. When Q_0 goes high, on the next CK edge, Q_0 goes low, which clocks the memory address counter (-ve edge triggered) to $n+1$.

The next event in the cycle occurs when Q_3 goes high; this output is inverted by IC29b and then used to latch the current data bus words into the D-to-A converter's register.

The carry (CY) output of IC35, pin 12, is used to control the data bus direction, after inversion by IC29a (the carry output from IC35 is high when outputs Q_0 to Q_4 are high, and low when outputs Q_5 to Q_9 are high). When OE is tri-state, the data bus outputs from the A-to-D are driven into the high impedance state, while the RAM outputs are enabled.

To summarise, the control cycle runs as follows: start A-to-D conversion; advance address; transfer contents of addressed memory location to the D-to-A; wait for A-to-D conversion to complete; write new data into addressed location; start A-to-D conversion; advance address; and so on.

The ZN427 A-to-D has an accurate hand-gap voltage reference diode on chip and this is used to provide the A-to-D D-to-A and peak level indicator with a

full scale reference. The A-to-D requires that a small negative bias current be applied to pin 5 for internal transistors to operate properly.

The analogue board provides step-like positive samples to V_{in} and if these exceed V_{ref} in amplitude, comparator IC27's output will go -ve and LED1 will glow. Note that this peak indicator is fairly crude and is frequency sensitive to some extent, due to the limited full gain bandwidth of IC27, hence it should be used for guidance only. However, if desired, a higher quality op-amp can be used here.

SW11-SW8 select the maximum address count before IC32, IC33 are reset to zero via IC26, etc, and hence these control memory usage. By this means, only one of IC15-IC22 need be present for the unit to work, albeit with limited delay capability. The maximum selectable memory usage corresponds to twice the on-board memory capacity, and an optional memory expansion board will be described later.

The four most significant address lines are used to perform memory chip selection via IC24, which is a 1-of8 multiplexer with common input connected to ground. Whenever A14 goes high, on-board memory is deselected and its outputs tristated. In this condition IC30d pin 11 goes low to uninhibit or select the expansion memory, if present.

The address count is reset to zero whenever IC30 pin 10 goes low, which occurs if all IC26's inputs go high, as is the normal case or in an external trigger signal is applied to the trigger input; reset can, therefore, be externally overridden at any time.

In percussion mode, ie, with SW11 connected to IC37's EN then address counting will continue until the address selected by the delay switches is reached, at which time all action ceases since the oscillator is disabled. Action can be restarted by externally resetting via the trigger input or by moving SW11 to normal, thus a one-shot function is possible. Note that the contents of memory are retained during this time since static memory (based on flip flops) is used. D7, D8, R55 etc, are present to protect the NOR input.

Bit 9 is stored independently in a 6116 type memory, whose eight bit words are multiplexed into eight single-bit locations. The ceramic capacitors provide temporary charge storage during read then write cycles which of course are common to all 8 bits simultaneously, and thus avoids data corruption.

HOW IT WORKS

LOW FREQUENCY OSCILLATOR

IC14a is a slow running astable, the hysteresis in the switching point being determined by the ratio R44/R45. This ratio is kept small so that the waveform appearing at the inverting input is a relatively linear triangle wave since C19, C20 are allowed to charge or discharge only a small way along the exponential capacitor charging curve before IC14a's output changes state.

The rate of charging of the capacitors and hence the astable running frequency is determined by RV5 and R46 and is adjustable between about 0.15 and 8 Hz. C19, C20 are back-to-back to provide effectively a non-polarised capacitor and attenuates the triangular waveform before passing it to the high input impedance non-inverting input of IC14b. A potential divider is formed by R47, RV6 and R48, the potential of RV6's slider being variable over a limited range. This negative voltage is applied to IC14b and is unity gain inverted. IC14b's output is a steady positive voltage level which may be modulated by the signal on its non-inverting input i.e. the size of which is set by adjustment of RV4.

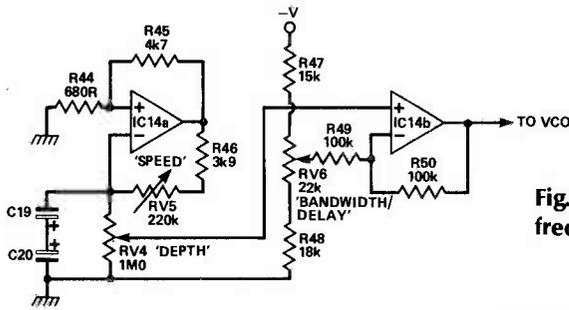


Fig. 6. Circuit diagram of the low frequency oscillator.

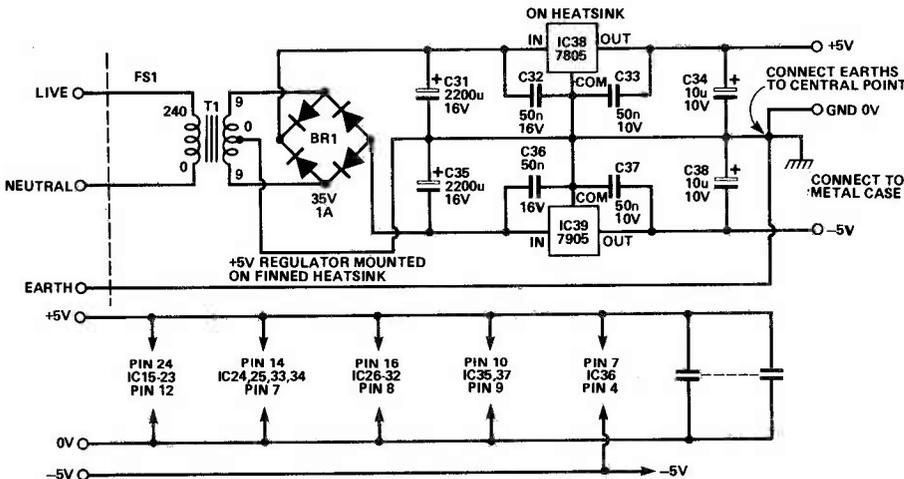


Fig. 7 Circuit diagram of the power supply.

ETI


SECURITY

Assemble and install your own system and save pounds

SECURITY

A COMPLETE SECURITY SYSTEM FOR ONLY £39.95 + V.A.T.

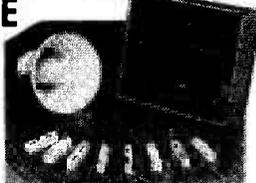contains
Control Unit
Enclosure & mechanical fixings
Key Switch & 2 keys
L.E.D.'s
5 1/2" Horn Speaker
4 high quality surface mounting Magnetic Switches



With only a few hours of your time it is possible to assemble and install an effective security system to protect your family and property, at the amazingly low cost of £39.95 + V.A.T. No compromises have been made and no corners have been cut. The outstanding value results from volume production and direct supply. Assembly is straight forward with the detailed instructions provided. When installed you can enjoy the peace of mind that results from a secure home. Should you wish to increase the level of security, the system may be extended at any time with additional magnetic switches, pressure pads or ultrasonic sensors. Don't wait until it's too late - order today. Order code: CS 1370.

EXTENDED SYSTEM CS 1480 Price £62.50 + V.A.T.

This system contains, in addition to the CS 1370, an ultrasonic detector type US 5063 + its enclosure, an additional horn speaker and a further 2 magnetic switches. This system represents outstanding value for money for the high level of security provided. Order Code - CS 1480.

SELF-CONTAINED ULTRASONIC ALARM UNIT CK 5063 only £37.00 + V.A.T.

Requires no installation. Easily assembled using our professionally built and tested modules.

- Adjustable range up to 25 ft.
- Built-in entrance and exit delay
- Built-in timed alarm
- Key operated switch - Off, Test and Operate
- Provision for an extension speaker
- Fully self-contained
- Uses US 5063, PSL 1865, Key Switch 3901, 3" Speaker 3515

Now you can assemble a really effective intruder alarm at this low price using tried and tested Riscomp modules. Supplied with full instructions, the kit contains everything necessary to provide an effective warning system for your house or flat. With a built-in LED indicator and test position the unit is easily set-up requiring no installation. It may simply be placed on a cupboard or desk. Movement within its range will then cause the built-in siren to produce a penetrating 900bs of sound, or even 1100bs with an additional speaker. All parts included and supplied with full instructions for ease of assembly. Size 200 x 180 x 70mm Order as CK 5063

ALARM CONTROL UNIT CA 1250



Price £19.95 + V.A.T.

The heart of any alarm system is the control unit. The CA 1250 offers every possible feature that is likely to be required when constructing a system whether a highly sophisticated installation or simply controlling a single magnetic switch on the front door.

- Built-in electronic siren drives 2 loud speakers
- Provides exit and entrance delays together with fixed alarm time
- Battery back-up with trickle charge facility
- Operates with magnetic switches, pressure pads, ultrasonic or I.R. units
- Anti-tamper and panic facility
- Stabilised output voltage
- 2 operating modes full alarm/anti tamper and panic facility
- Screw connections for ease of installation
- Separate relay contacts for external loads
- Test loop facility

HARDWARE KIT HW 1250



only £9.50 + V.A.T.

This attractive case is designed to house the control unit CA 1250, together with the appropriate LED indicators and key switch. Supplied with the necessary mounting pillars and punched front panel, the unit is given a professional appearance by an adhesive silk screened label. Size 200 by 180 by 70mm

Add 15% VAT to all prices
Add 70p post and packing to all orders
Units on demonstration
Shop hours 9.00 to 5.30 p.m.
Closed Wednesday
Saturday 9.00 to 1.00 p.m.
SAE with all enquiries
Order by telephone or post using your credit card

SIREN & POWER SUPPLY MODULE PSL 1865

only £9.95 + V.A.T.

A complete siren and power supply module which is capable of providing sound levels of 110dbs at 2 metres when used with a horn speaker. In addition, the unit provides a stabilised 12V output up to 100mA. A switching relay is also included so that the unit may be used in conjunction with the US 5063 to form a complete alarm.

POWER SUPPLY & RELAY UNIT PS 4012 Price £4.95 + V.A.T.

Provides stabilised 12V output at 85mA and contains a relay with 3 amp contacts. The unit is designed to operate with up to 2 ultrasonic units or 1 infra-red unit IR 1470.

SIREN MODULE SL 157

Produces a loud penetrating sliding tone which, when coupled to a suitable horn speaker, produces S.P.L.'s of 110dbs at 2 metres. Operating from 9-15V. Price £2.95 + V.A.T.

5 1/2" HORN SPEAKER HS 588

This weather-proof horn speaker provides extremely high sound pressure levels (110dbs at 2 metres) when used with the CA 1250. PS 1865 or SL 157. Price £4.95 + V.A.T.

3-POS. KEY SWITCH 3901

Single pole, 3-key switch intended for use with the CA 1250. Price £3.43 + V.A.T.

MAGNETIC SWITCH MS 1025

Surface mounting superior quality. Price £1.17 + V.A.T.

US 4012 ULTRASONIC MODULE

Basic low cost ultrasonic detector suitable for wide range of movement detection applications featuring 2 LED indicators and having adjustable range 5-25 ft. Price £10.95 + V.A.T.

DIGITAL ULTRASONIC DETECTOR US 5063



only £13.95 + V.A.T.

- 3 levels of discrimination against false alarms
 - Crystal control for greater stability
 - Adjustable range up to 25ft
 - Built-in delays
 - 12V operation
- This advanced module uses digital signal processing to provide the highest level of sensitivity whilst discriminating against potential false alarm conditions.

ULTRASONIC MODULE ENCLOSURE

only £2.95 + V.A.T.

Suitable metal enclosure for housing an individual ultrasonic module type US 5063 or US 4012. Supplied with the necessary mounting pillars and screws etc. For US 5063 order SC 5063; for US 4012 order SC 4012.

INFRA-RED SYSTEM IR 1470 only £25.61 + V.A.T.



Consisting of separate transmitter and receiver both of which are housed in attractive moulded cases, the system provides an invisible modulated beam over distances of up to 50ft. operating a relay when the beam is broken. Intended for use in security systems, but also ideal for photographic and measurement applications. Size 80 by 50 by 35mm.

RISCOMP LIMITED

Dept ETI/23
21 Duke Street,
Princes Risborough,
Bucks HP17 0AT
Princes Risborough (084 44) 6326

Cirkit. Making it

Cirkit stock all the components, accessories and tools and the kits you're looking for.

Designed and selected to offer the best possible standards at the best possible price.

Cirkit's always well stocked.

As soon as new products are available, Cirkit has them.

When it comes to kits, Cirkit's got the lot. At the price you want to pay.

Just send for our catalogue or visit one of our three outlets at:

200 North Service Road,
Brentwood, Essex. CM14 4SG;
53 Burrfields Road,
Portsmouth, Hampshire. PO3
5EB; Park Lane, Broxbourne,
Hertfordshire. EN10 7NQ.

Please add 15% VAT to all advertised prices and 60p post and packing. Minimum order value £5 please. We reserve the right to vary prices in accordance with market fluctuation.

Cirkit Kits

CIRKIT ELECTRONICS TOOL KIT

Contains: 15W Soldering Iron 2 spare bits, heat shunt, solder, pliers, cutters, and screwdriver 40-00007 15.56

AUDIO FUNCTION GENERATOR

Versatile waveform generator with sine, triangular and square wave outputs. On board mains PSU 41-01302 27.00

STEREO 40W AMPLIFIER

Single board 40W per channel stereo amplifier 41-01301 38.00

STEREO VU METER

5 LED per channel stereo VU meter for use with stereo amplifiers 41-01401 11.50

5W AUDIO AMP

A very compact audio output stage for use in a wide range of equipment 41-01406 4.60

UNIVERSAL AMP

A universal audio pre-amp with a gain of 10 41-01604 6.45

MONO REVERBERATION UNIT

Single channel, spring line reverb unit to add echo effects to tape recording etc. 41-01602 10.00

TONE GENERATOR AND DETECTOR

Very low distortion tone generator and signal detector for circuit fault finding 41-01603 10.45

10MHz DFM

8 Digit LED digital frequency meter and period measurement 41-01500 54.10

50MHz PRESCALER


Extend the range of the 10MHz DFM to 50MHz 41-01501 8.55

1.5MHz PRE AMP

Low frequency pre-amp and waveform shaper for the 10MHz DFM 41-01502 5.13

1-30V 1mA-2A PSU

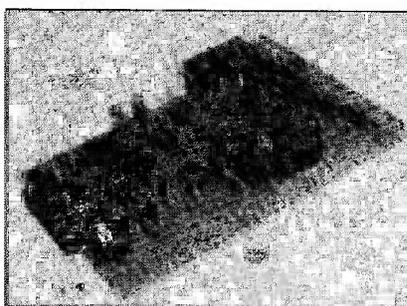Adjustable 1-30V Power supply with pre-settable current limit from 1mA-2A 41-01600 37.46



Centronics Interface

5-12V 1A PSU


Adjustable PSU from 5-12V with current protection, 1 amp max output 41-01504 6.45

1-30V 1.5A PSU

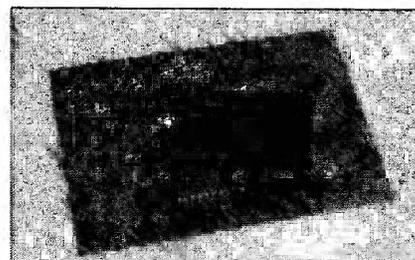1-30 volt adjustable PSU with protected output up to 1.5 Amps 41-01402 10.45

3 DIGIT LED DVM

DVM to read up to 99.9 volts or configured as an ammeter to read up to 9.99 amps 41-01403 17.00



10MHz DFM

INFRA RED LINK

Single channel IR Link with relay output 41-01300 9.60

TEMPERATURE SENSOR

Thermistor based temperature sensor with relay output 41-01303 6.20

LOCOMOTIVE SOUND GENERATOR

Realistic steam sound and whistle for model railways 41-01304 9.20

LAMP DIMMER

Control lamps and drill speed 41-01305 5.70

WATER LEVEL ALARM

Alarm to indicate high water level or flooding 41-01601 2.70

3 NOTE CHIME

Doorbell chime with adjustable tones 41-01503 7.00

2M PRE AMP

Miniature low-noise MOSFET pre-amp for the 2m amateur band 41-01307 3.91

2M CONVERTER

Low noise 144MHz-28MHz amateur band converter 41-01306 17.35

2M POWER AMP

20W - 10dB gain - power amplifier for the 2m band. Automatic TX switch over. RX pre-amp, robust construction 41-01404 32.87

70cm PRE AMP

Low noise, miniature pre-amp for the 70cm amateur band 41-01506 4.78

70cm CONVERTER

70cm to 144MHz low noise converter featuring pre-aligned helical filter, schottky diode mixer and low noise transistors 41-01405 21.50

70cm PA

10W Power amp to boost the output of handheld and portable 70cm transceivers 41-01505 33.82

CRYSTAL CALIBRATOR

Crystal reference calibrator for alignment of receivers, outputs at 4.2, 1MHz, 100, 50 AND 10KHz 41-00801 4.32

CB NOISE SQUELCH

Improves to mute performance of the majority of CB rigs 41-01605 5.40

CENTRONICS INTERFACE

Connect your personal computer to the outside world via the Centronics printer output 41-01406 22.50

To: Cirkit Holdings PLC, Park Lane, Broxbourne, Hertfordshire. EN10 7NQ.
I enclose 85p. Please send me your latest catalogue and 3 x £1 discount vouchers!
If you have any enquiries please telephone us on Hoddesdon (0992) 444111.

Name _____

Address _____

Telephone _____

Area of Special Interest _____

ETH12

Cirkit
Bigger Stock. Better Service.

New Winter
Catalogue
Out Now!

bigger and better.

Nicad Batteries & Chargers

High quality nickel cadmium rechargeable batteries. Equivalent in size with popular Dry Cell sizes e.g. HP7 (AA), HP11 (C), and HP2 (D). Minimum life 600 (300 PP3 size) full charge/discharge cycles. Batteries must be charged from a constant current source only. All batteries are supplied only with a residual charge and should be charged before used.

DATA & PRICES

Type	V(nom)	Capacity	Stock No.	1-9	10-49
AA	1.2V	500mAh	01-12004	0.80	0.74
C	1.2V	1.2AH	01-12024	2.35	1.99
D	1.2V	1.2AH	01-12044	2.00	2.00
PP3	8.4V	110mAh	01-84054	3.70	3.50

CH/4/50

To recharge up to 4 AA size NiCads.
Size: 112 x 71 x 37mm

01-00409 4.95

CH1/22

To charge PP3 type NiCads.
Size: 70 x 50 x 32mm

01-00159 4.30

CH8/RX

Will recharge AA, C, D and PP3 size cells with automatic voltage selection. Will recharge following combinations: 4xD, 4xAA, 4xC, 2xPP3, 2xD + 2xC, 2xD + 2xAA, 2xD + 1xPP3, 2xC + 2xAA, 2xC + 1xPP3, 2xAA + 1xPP3. Charge rate: 11mA for PP3, 45mA for AA size, 120mA for C and D size, for 16 hrs. Power: 240V 50Hz. Output Voltage: 2.9V for AA, C and D size, 11.0V for PP3 size. Weight: 0.475kg. Size: 199 x 109 x 55mm.

01-02204 9.45



HT320

High quality, high specification meter at a reasonable price. In addition to the usual ranges, facilities are provided for measuring transistor parameters such as I_{ceo} and H_{fe} .

Meter movement fully protected against overloads. 3-colour mirrored scale in robust case. Supplied complete with comprehensive instructions, test leads, transistor test leads and batteries (2 x HP-7, 1 x PP3).

DC Volts: 0.1V, 0.5V, 2.5V, 10V, 50V, 250V, 1kV (20k Ω/V). AC Volts: 10V, 50V, 250V, 1kV (18k Ω/V). DC current: 50 μ A, 2.5mA, 25mA, 250mA. Resistance: 2k, 20k, 2M, 20M Ω . AF Output: -10dB to +22dB for 10VAC (0dB/0.775V, 600 Ω). Leakage (I_{ceo}) 15 μ A, 15mA, 150mA. H_{fe} : 0-1000 (Lc/Tb). Weight: 410gms.

56-83201 14.00


RF Generator LSG17

A stable wide-range generator for the hobbyist, service technician, schools, colleges, etc.

Frequency range: A/100kHz-300kHz, B/300kHz to 1MHz (Harmonics 96-450MHz) C/1MHz-3.5MHz, D/3.0MHz-11MHz, E/10MHz-35MHz, F/32MHz-150MHz. Accuracy: $\pm 1.5\%$. Output greater than 100mV (no load). Ext. xtal osc for 1 to 15MHz crystal. Power required: AC100, 115 or 230V 3VA.

Size & Weight: 150(H) x 238(W) x 130(D)mm, 2.5Kg approx.

56-90017 115.00

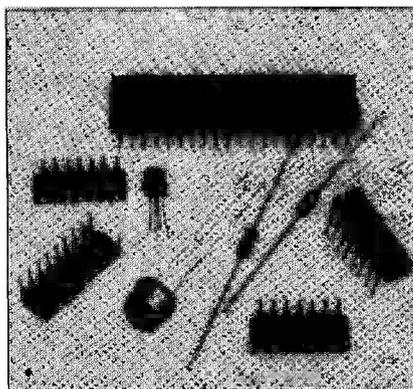

Linear ICs


		Stock No.	Price
LF351	Bi-FET op amp	61-03510	0.49
LF353	Dual version of LF351	61-03530	0.81
LM380N	1W AF power amp	61-00380	1.45
LM381	Stereo pre-amp IC	61-00381	3.27
NE554	14 pin DIL servo driver IC	61-00544	1.80
NE555N	Multi-purpose low cost timer	61-05550	0.21
uA741CN	DIL low cost op-amp	61-07411	0.42
TDA1062	RF oscillator and mixer system for 1-200MHz	61-01062	1.95
TDA1083	Portable radio AM/FM audio in one IC	61-01083	1.95
HA1388	18W PA from 14V	61-01388	2.75
MC1496P	Double balanced mixer/modulator	61-01496	1.25
TDA2002	8W into 2 ohms power amp	61-02002	1.25
ULN2283	1W max 3-12V power amp	61-02283	1.00
CA3089	FM IF amp, detector, mute, AFC, AGC system	61-03089	2.84
CA3130E	BIMOS op amp	61-31300	0.80
CA3140E	BIMOS version of 741	61-31400	0.46
MC3359	Low current dual conversion NBFM IF and det	61-03859	2.95
LM3900	Quad norton amp	61-39000	1.20
LM3909N	8-pin DIL LED flasher	61-39090	0.68
KB4412	Two balanced mixers IF amp with AGC for AM/SSB	61-04412	1.95
ICM7555	Low power CMOS version of 55 timer	61-75550	0.98
HA11225	Low noise FM IF	61-11225	1.45
HA12017	83dB S/N phono preamp 0.001% THD	61-12017	0.80
MC14412	300 baud MODEM controller (Euro/US specs)	61-14412	6.85

Selected Lines

PB2720	80dB Piezo Buzzer	43-27201	0.55
10M15A	10.7 Filter	20-10152	2.10
10M08AA	10.695 Filter	20-11152	3.49
FC177	LCD Freq. Meter	39-17700	20.00
CM161	Min LCD Clock	40-80161	8.25
BBC to Centronics Cable		03-10019	7.25
Dragon to Centronics Connect Cable		03-10017	7.25
C12 Computer Cassette Tape		21-00012	0.55
8 x 0.3"	IC socket	28-00800	0.12
14 x 0.3"	IC socket	28-14000	0.13
16 x 0.3"	IC socket	28-16000	0.13
6V	KUIT-A Relay	46-80000	0.48
9V	KUIT-A Relay	46-80001	0.48
12V	KUIT-A Relay	46-80002	0.48
CX120P	COAX Relay	46-90120	11.96
CX520D	COAX Relay	46-90520	26.98
CX540D	COAX Relay (BNC)	46-90540	26.98

Books

Beginners Guide to Amateur Radio	02-11262	4.50
Beginners Guide to Electronics	02-04134	4.50
Active Filter Cookbook	02-21168	12.70
CMOS Cookbook	02-21398	11.85
TTL Cookbook	02-10358	11.00
Design of Active Filters	02-21539	10.15
Design of Op-amp Circuits with experiments	02-21537	9.30
Effectively Using the Oscilloscope	02-21794	9.30
The ZX Spectrum	02-00100	5.95
Practical Design of Digital Circuits	02-11831	10.45
Electronic Projects for Home Security	02-05351	3.80
Electronic Telephone Projects	02-21618	7.60
55 Timer Applications Sourcebook	02-21538	6.40
Television Engineers Pocket Book 7th Ed	02-21313	8.50
Electronics Pocket Book	02-21309	7.50
99 Practical Electronic Projects	02-21635	5.90
More Electronic Projects in the Home	02-21307	3.80
The Radio Amateurs Question and Answer Reference Manual	02-02157	5.95
Basic Programming on the BBC Microcomputer	02-06640	5.95
Using Microprocessors and Microcomputers: The 6800 Family	02-98728	11.05
Z-80 Microcomputer Design Projects	02-21682	12.70
Z8000 Microprocessor: A Design Handbook	02-37345	16.10

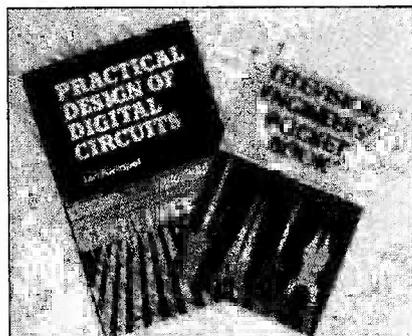

68000: Principles and Programming	02-21853	12.70
8085A Cookbook	02-21697	13.55
Handbook of Electronic Tables Formulas	02-21532	11.00
Popular Circuits: Ready Reference	02-04585	13.95
Semiconductor Data Book 11th Edition	02-04797	9.00

ACTIVE-8 LOUDSPEAKER

Warning! This introduction contains a pun which may be harmful to readers of a sensitive disposition! Barry Porter sets his active imagination to work once more and brings this series of articles to a tri-amp-hant close (Ouch! — Ed.)

Once completed, the units should be tested. Initially, remove the plug-in boards, switch on and ensure that the correct voltages appear where they should. Having established that the mother board is operating correctly, in particular that the 15-0-15V supply rails are present, the plug-in boards should be inserted one at a time. It should be possible to connect a signal generator to the input and verify that each board is working by checking its output. If any problems appear,

make sure that the IC voltages are correct — namely that +15V and -15V are on the supply pins and that both inputs and the output are within a few mV of 0V. Non-working stages should be carefully inspected for faulty soldering and component insertion, and if no obvious error can be seen, the IC should be changed.

Once everything is working, the response of the two outputs should be plotted and compared to similar measurements taken from the second unit. If these

agree to within about 0.25dBm, it is safe to assume that no major errors are present, and proceed with the final connection to the speakers.

The high and low frequency outputs of the filter unit are connected to the two channels of a stereo power amplifier. A number of factors will probably decide the choice of amplifiers, not the least being cost. It is important that the four power stages of a stereo pair of Active-8 units are as identical as

PARTS LIST —

DELAY UNIT

RESISTORS (all 1/4 W 1% metal film)

R32, 34, 35, 37, 38, 33k
40, 41, 43
R33, 36, 39, 42 10k
R44 430R
R45 1k
R46, 47 22R

CAPACITORS

C36-39 1n5 polystyrene
C40 100n polycarbonate
C41 22μ 16V non-polarised electrolytic
C42, 43 100μ 25V radial electrolytic
C44, 45 100n polyester

SEMICONDUCTORS

IC6, 7 NE5532

MISCELLANEOUS

PCB; 10-way PCB socket.

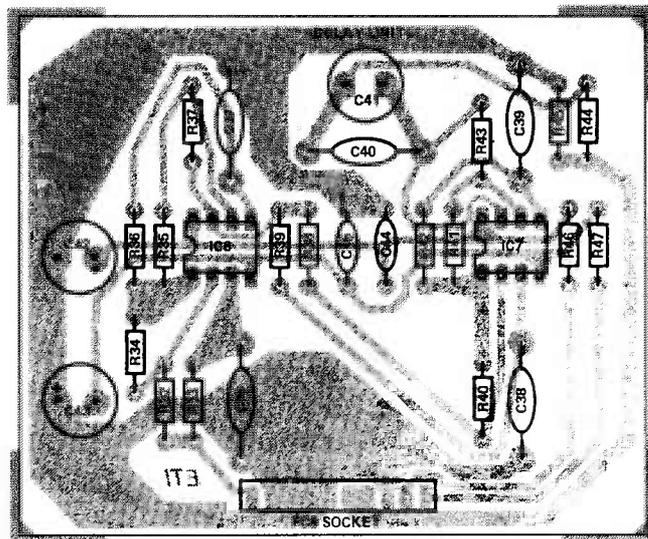


Fig. 1 The missing link — the PCB overlay we didn't have room for last month.

possible. Regarding amplifier power, the speakers will operate at their best when driven by good quality units in the 100-150 watts region; anything below 50 watts per channel should be avoided, as transient clipping is likely to happen too often for comfort. At the top end, providing they are used with caution, there is no reason why 200 or 250 watts should cause any problems.

Before making the final connections the protection relay RL1, should be fitted — preferably inside the cabinet where, if an octal based version is used, the base can be screwed to the cabinet with 20mm chipboard screws passing through 10mm tubular spacers.

Once everything is connected up, the complete unit should be tested, making sure that both relays operate correctly so that a delay of about 6 seconds occurs at switch-on, and RL1 is released before RL2 when the units are switched off.

If everything is working, connect the speakers to your pre-amplifier using good quality screened cable. When fed from a balanced output, the connecting cable should contain a twisted pair of conductors within an outer screen. The conductors carry the signal to the inverting and non-inverting inputs, the screen being connected to the 0V contact. For unbalanced operation, the signal should be applied to the non-inverting (+) input, and the inverting (-) contact of the connecting plug should be connected to the cable screen. If you are using a pre-amplifier with a high output capability it may be advantageous if there is less gain in the system, and this can be achieved by leaving the inverting input unconnected. Some amplifiers (such as the Quad 303 and 405) invert the signal phase, so if you are using such a power stage the overall phase integrity may be maintained by connecting the pre-amplifier output to the inverting input of the buffer amplifier, with the non-inverting and N contacts joined to the screen of the connecting cable. Of course, if your pre-amplifier is also of the inverting type, this will cancel the power amplifier inversion, in which case the non-inverting input of the buffer should be used.

All that now remains is to put stylus to groove, sit back, and discover the joys of being 'Active-8-ed'!

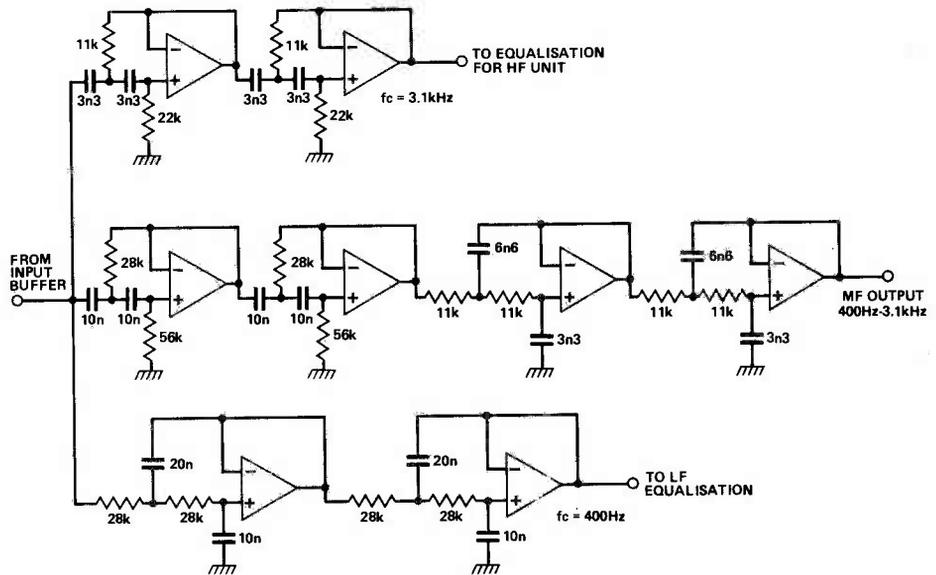


Fig. 2 Basic circuit diagram for a three-way cross-over. You'll have to work out the details (and the PCB) yourself.

Three Ways To Improve The System

The Active-8 was designed to be used with a stereo power amplifier providing power for each channel, which limited the number of drive units that could be used to two. Experimentation is the essence of speaker building (it is one form of building that doesn't require planning permission, except of the matrimonial kind) and most speaker builders go through a phase of Bigger is Better thinking. If, for reasons of sound output level or to impress the next door neighbours, you decide to use a larger than 200mm bass driver — say a 250 or 300mm unit — you will have to start thinking in terms of tri-amplification and mid range units. Although a few manufacturers claim to have produced 300mm units that will

operate up to 2 or 3 kHz, in practice they leave much to be desired, so the additional complexity of adding a mid range driver is certainly worthwhile.

There are several good units available, but the author has always favoured the KEF B110 in its high power handling form (KEF part no. SP1057).

Depending upon the parameters of the chosen bass unit, you are likely to be using a cabinet of 60 to 120 litres. The basic rules are to keep the cabinet as narrow as possible with drive units close together and vertically in line. If your cabinet building ability is above average, you may like to consider putting the mid and high frequency units in a small enclosure separated from the main cabinet, which allows the acoustic

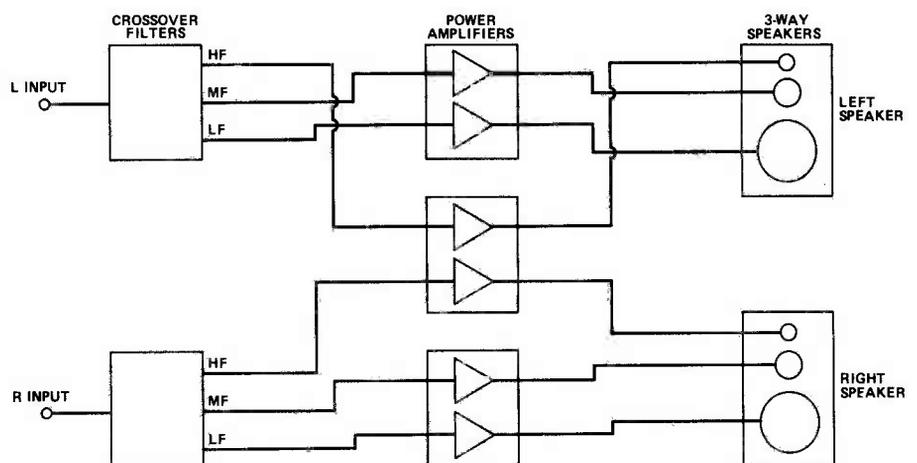


Fig. 3 Suggested set-up for a tri-amped system.

centres of all three units to be in-line and removes the need for signal delay. So what if it looks like a B&W 801 or KEF105 — you're not planning to go into competition with them, are you?

Using a 300mm bass driver such as the KEF B300.B or SEAS 33F-ZBX/DD (about the only unit to have the same transient attack as a JBL 15" monitor, but at about a quarter of the price), a B110 mid range and T33A high frequency unit, the network filters should be 24 db per octave using the series Butterworth arrangement previously explained. A basic circuit diagram of the filters is shown in Fig. 2. Equalisation should not be required for the B110, but the bass unit and T33A will require treatment similar to that provided in the Active-8.

As the name suggests, you will require three stereo amplifiers for a tri-amplified set-up. These should all be of the same type to avoid system gain differences, and should be connected as shown in Fig. 3. Note that we have given no constructional details or PCB layout for this modification — it is intended purely as a starting point for those wishing to experiment further.

Sixth Order Bass Alignment

One of the drawbacks of the equalised closed box form of the Active-8 is the rather excessive cone excursion caused by subsonic signals — and there are plenty of those to be found on the average analogue record. Most record playing systems have some degree of subsonic filtering, but often this is too gentle to be effective, or begins to roll-off at a frequency well into the audio band. If you want to obtain very low bass output without subsonic excursion problems, you may like to experiment with a sixth order alignment. The basic requirement for this is that the reflex cabinet resonance (f_B) is lowered by half an octave, and that an active two-pole filter is introduced into the signal path, this having a Q value of 2 and a cut off frequency the same as the revised cabinet frequency. The Active-8 therefore has its f_B reduced from 34.7 to a new value given by:

$$f_{B(\text{new})} = \sqrt{\frac{f_B^2}{2}} = 24.5 \text{ Hz}$$

This requires that the tuning vent length becomes almost 500mm which is likely to be a problem. A quick calculation shows that a vent with 50mm internal diameter should be 207 mm long, which is a bit more manageable. You will find that if you select the appropriate grade of plastic pipe, one with a 50mm internal diameter will slide comfortably into a 75 mm one. It also has sufficient wall thickness of glue the outer end to a new escutcheon, so it is quite possible to have interchangeable 4th and 6th order alignments.

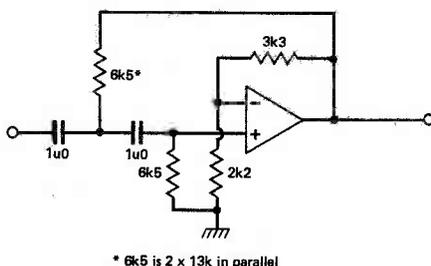


Fig. 4 Circuit for a second-order filter.

The 2nd order filter shown in Fig. 4 should be inserted in the low frequency path in place of the closed box equalisation circuit. It is tuned to 24.5 Hz ($f = 1/2 \pi RC$) with a Q of 2 being set by the gain of 2.5 from the relationship:

$$\text{Gain} = 3 - (1/Q)$$

The main problem with a 6th order system is the amount of phase shift that it introduces. Although this can cause some types of bass sound to become less solid, there is no sign of this with low organ notes, so perhaps this alignment is best recommended to those who are turned on by that sort of thing.


ETI

References

- Linkwitz S.H., *Loudspeaker System Design*. Wireless World May, June & December 1978.
- Linkwitz S.H., *Active Crossover Networks for Noncoincident Drivers*. JAES January 1976
- Margows G. & Small R.H., *Loudspeaker System Design*. JAES, June 1981
- Marshall-Leach Jr. W., *Active Equalisation of Closed Box Loudspeaker Systems*. JAES, June 1981
- Snyder P.F., *Design of Vented Loudspeaker Systems*. JAES reprint 1307
- Thiele A.N., *Loudspeakers in Vented Boxes*, JAES, May & June 1971

BUYLINES

1% metal film resistors are available from a number of suppliers in almost all of the values required, the only difficult item being the 15k4 specified for R51 and R52. We don't know of a supplier for this so we can only suggest you use two resistors in series and stand them on end on the PCB. A 13k and a 2k4, both available from Maplin, should do the trick; ordinary mortals may well find that a 15k 1% is perfectly adequate on its own. The NE5532 and NE5534 are available from Watford, Technomatic, Rapid, etc, and the PCB-mounting transformer and most of the capacitors are also widely available. Non-polarised electrolytics in radial form are not readily available to the amateur, but Maplin and Cirkit both stock 50V axial components which could be mounted end-on. These two companies are also among those which stock the PCB plugs and sockets used, but note that there are some interesting discrepancies in stocking habits here and that you may need to order from more than one supplier to get the matching plug and socket halves you need. RL2 is also a Maplin type, and any relay with the correct contact arrangement and coil voltage can be used for RL1. The XLR type audio connectors recommended in the text are available from numerous suppliers including Electrovalue, Cricklewood, Maplin and Cirkit, and the PCBs are all available from our PCB Service.

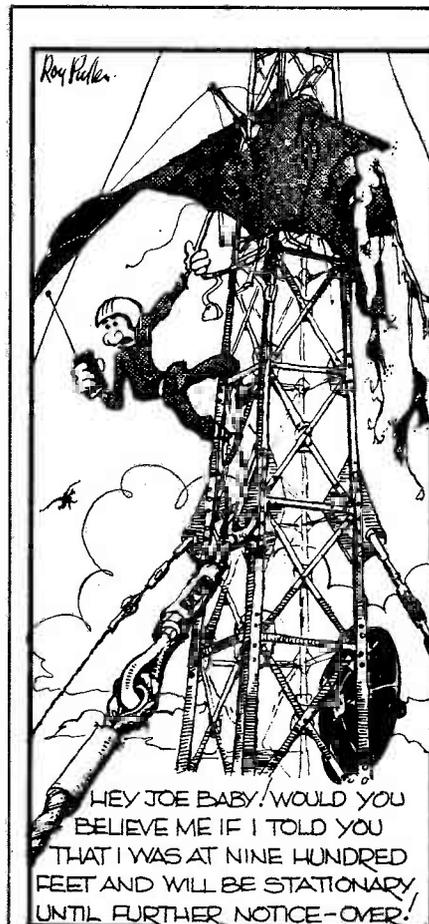

HEY JOE BABY, WOULD YOU BELIEVE ME IF I TOLD YOU THAT I WAS AT NINE HUNDRED FEET AND WILL BE STATIONARY UNTIL FURTHER NOTICE-OVER!

Turn to page 71 for details of how to update your Vario!

'THE USUAL PROBLEMS OF MAN MEETS WOMAN'

*** solved by Dateline!**

Michael Wheeler is an articulate, good-looking businessman in his mid-thirties. Born and bred in London, his work has taken him all over the world. Despite his busy life-style he found time to marry, but unfortunately his marriage failed and he found himself back in London, trying to rebuild his social life.

'My cousin, who lives in London, suggested that I should join Dateline. I must admit, I found the idea appealing because I was aware of Dateline. In fact, I had been a member way back in the sixties. I found no great romantic successes at that time but many, shall we say, nice encounters, so when my cousin suggested the idea again I thought 'Why not, I'm only going to live once, why not make the best of it?'

Michael didn't join Dateline to find 'the woman of my dreams'. 'I joined because after a long absence from a city like London you tend to find that your friends and acquaintances have married or moved away. Although I obviously missed female company, I also found that I had no circle of friends left at all.'

'When my first list of names from Dateline arrived and I began to receive calls from women with whom I had been matched on the computer, my social life improved out of all recognition almost overnight! My only problem was time, because all of the women I spoke to were so pleasant that I felt I had to meet them. In the event, I met four from my first list of names. Two I felt I could quite happily be friends with; the other two meant rather more.'

Michael doesn't mind people knowing he is a member of Dateline. 'There's not the adverse reaction from family and friends that I think some people may expect,' he said. 'I did perhaps feel, as many people probably do, that there's some sort of stigma about admitting to feeling lonely. But that's rubbish as loneliness affects every person at some stage of their life, no matter what their circumstances. It's something that has to be

overcome by any means available to us. Dateline may sound cold-blooded to some people, but I have found it certainly isn't. It may perhaps be more socially acceptable to meet people of the opposite sex in pubs or clubs, but really Dateline wins above those places. I don't like competing with smoke and noise, and it's far nicer to know that the woman you're telephoning has the interests and desires you're looking for. It provides a basic understanding before you even say hello. Obviously, all the usual problems of man meets woman are still there, but you have conquered quite a few of the barriers that so often make a relationship fail before its really started.'

He stopped to consider for a moment. 'I don't know what you need from life. All I really want is happiness, and a large part of the happiness I seek is the happiness that can be gained from the



relationship between a man and a woman. At least two of the women I have met directly through Dateline have become friends and it's good to know that if I am at a loose end there's someone I can 'phone for a chat or to arrange an evening out.'

Michael has recently suspended his membership of Dateline. He has met a young woman who is a friend of one of his Dateline introductions. Their relationship has blossomed into love and they are now engaged to be married.

If you would like to be one of the many thousands of people nationwide who have been enjoying a new social life, and finding love and happiness through Dateline, complete the simple questionnaire below. We will send you confidentially and completely free, full details about Dateline and how it works, and details of just one of the Dateline members who are compatible with you. Send to:

Dateline Computer Dating, 23 Abingdon Rd., London W8. Tel: 01-938 1011.

FREE: Computer Test to Find Your Ideal Partner.

CONFIDENTIAL

1 START HERE Do you consider yourself:

<input type="checkbox"/> Shy	<input type="checkbox"/> Generous
<input type="checkbox"/> Extrovert	<input type="checkbox"/> Outdoor type
<input type="checkbox"/> Adventurous	<input type="checkbox"/> Creative
<input type="checkbox"/> Family type	<input type="checkbox"/> Practical
<input type="checkbox"/> Clothes-conscious	<input type="checkbox"/> Intellectual

2 Indicate which activities and interests you enjoy by placing a '1' (one) in the appropriate box. If you dislike a particular activity, write a '0' (nought) in the box. If you have no preference, leave the column blank.

<input type="checkbox"/> Pop music	<input type="checkbox"/> Politics
<input type="checkbox"/> Fashion	<input type="checkbox"/> Classical music
<input type="checkbox"/> Pubs	<input type="checkbox"/> Art/Literature
<input type="checkbox"/> Sport	<input type="checkbox"/> 'Live' theatre
<input type="checkbox"/> Pets	<input type="checkbox"/> Science or technology
<input type="checkbox"/> Folk music	<input type="checkbox"/> Creative writing/painting
<input type="checkbox"/> Jazz	<input type="checkbox"/> Poetry
<input type="checkbox"/> Travelling	<input type="checkbox"/> Philosophy/Psychology/Sociology
<input type="checkbox"/> Cinema	<input type="checkbox"/> History/Archaeology
<input type="checkbox"/> Good food	<input type="checkbox"/> Conversation

3 I am over seventeen and would like you to send me completely free and without obligation, a description of my ideal partner. Plus a free full colour brochure and lots more information about Dateline. I enclose two first class stamps.

Your sex put M or F **Your Height** ft. ins

Your Age yrs. **Age you would like to meet** Min. Max.

Christian Name _____

Surname _____

Address _____

Nationality _____ **Religion** _____

Occupation _____

Send today to:
Dateline, Dept ETA
23/25 Abingdon Rd.
London W8.
01-938 1011

Dateline

TERMS OF BUSINESS

- * All prices exclude V.A.T. and carriage. Please add carriage to order total before adding V.A.T.
- * Carriage charges extra on all orders as follows:
Components £0.75
Books/Data/Software £2.00
Printers, Monitors, Disc drives, etc. £4.50
- * Strictly cash with order or credit card (Access or VISA) only.
- * Delivery is normally from stock but please allow up to 28 days.
- * Any query or complaint regarding an order should be made in writing within 7 days of receipt of the order. No telephone queries will be entertained.

- * Goods incorrectly ordered cannot be accepted for replacement without our prior agreement. Due to high processing costs, a minimum of 15% handling charge may be levied on any returns or cancelled orders.
- * We will issue a full immediate refund, if requested, for out of stock items.
- * All items carry full manufacturers warranty.
- * A V.A.T. receipt will be supplied with all orders.
- * Prices quoted are correct at the time of going to press but we reserve the right to effect changes without prior notice.

Hi-Tech

HI-TECH COMPONENTS,

<p>6502 FAMILY</p> <p>6502 3.50 6502A 4.95 6520 2.25 6520A 2.45 6522 3.40 6522A 4.45 6532 5.45 6532A 5.95 6551 5.95</p> <p>8086 FAMILY</p> <p>8086 29.50 8088-2 22.50 8216 0.75 8237A-5 23.50 8251A 7.50 8253A 7.50 8255A-5 7.00 8259A 6.60 8272 35.00 8284A 9.50 80C86 46.65 80C88 46.65 82C52 15.68 82C54 19.04 82C55A212.98 82C59A 15.22 82C82 6.26 82C84A 8.94 82C88 16.80</p> <p>6800 FAMILY</p> <p>6800 2.15 6802 2.70 6803C 8.40 6809E 6.25 6809P 6.25 6810 1.70 6821 1.70 6840 3.70 6845 6.45 6850 1.70 6862 3.75 6875 4.95 68800 4.30 68809 9.95 68B10 1.88 68B21 3.70 68B40 6.60 68B50 1.58 68B54 7.95</p> <p>6805 FAMILY</p> <p>MC1468052P 12.60 MC146818P 7.20 MC146823P 8.80 MC68705KT3 75.00 MC68705R3L 40.00 MC68705U3L 36.00</p> <p>68000 FAMILY</p> <p>MC6800G10 50.00 MC6800DL8 50.00 MC6800DL8 45.00 MC68230L8 19.50 MC68451L8 67.00 MC68901P 75.00</p> <p>TI 9900 FAMILY</p> <p>TMS9901-95 4.50 TMS9902 4.50 TMS9918 35.00 TMS9927 11.60 TMS9928 13.00 TMS9929 13.00 TMS9937 6.70 TMS9980 17.20 TMS9995 13.70</p> <p>MEMORIES — EPROM</p> <p>2532-300ns 4.95 2532-450ns 3.95 2564-300ns 6.95 2708-450ns 3.95 2716-450ns 3.50 2716-3 RAIL 7.95 2732-350ns 4.95 2732-450ns 4.45 2764-200ns 7.95 2764-250ns 5.15 2764-300ns 4.75 2764-300ns 10.95 27C64-250ns 10.45 27C64-300ns 10.45 27128-250ns 19.00 27128-300ns 16.00</p> <p>MEMORIES RAM</p> <p>4116-150ns 1.28 4116-200ns 1.20 4164-150ns 4.45 4416-200ns 4.70 4532-200ns 2.45 4564-150ns 4.45 B118-100ns 1.95 81256-150ns 25.00 8416-200ns 6.00 8416-LP-200ns 6.40 8417-200ns 6.00 8417-LP-200ns 6.00</p> <p>MEMORIES — RAM CMOS*</p> <p>MK48202B-150ns 32.00 MK48202B-200ns 24.00 MK48202B-250ns 23.00</p> <p>BIPOLAR PROMS</p> <p>TBP185030N 1.54 TBP185A030 1.38 TBP24510N 2.06 TBP24541N 6.68 TBP24581N 5.50 TBP245A10N 1.40 TBP245A41N 4.40 TBP28L22N 3.10 TBP28LA22N 4.14 TBP28S166N 19.00 TBP28S42N 4.50 TBP28S46N 4.50 TBP28S86N 5.00 TBP28SA42N 4.50 TBP28SA46N 4.50 TBP28SA86N 8.62 AM27513PVC 3.74 AM27519PC 1.92 AM275191DC 15.00 AM27525DC 15.00 AM27529DC 6.46 AM27535DC 22.00</p> <p>MEMORIES E2 PROM</p> <p>X2804AP-300ns 14.95 X2804AP-350ns 13.45 X2804AP-450ns 12.75 X2816AP-300ns 29.95 X2816AP-350ns 25.00 X2816AP-450ns 22.50</p> <p>LINEAR/INT. DEV.</p> <p>4702 8.90 HCI-55564-5 10.66 (Speech Synthesis) AM7910DC 34.88 AM7911DC 34.88 25L52518PC 3.60 25L52521PC 3.28 25L52538PC 2.72 25L52539PC 2.72 26L531PC 2.62 26L532PC 2.62 6402 6.40 75107BN 0.69 7510AN 0.86 75150P 0.86 75154N 1.05 75159 2.30 75160AN 2.60 75161AN 2.82 75162AN 4.08 75172NG 1.96</p>	<p>75173N 1.44 75174 2.82 75175 1.96 FD1771P 35.00 FD1791 15.50 FD1791-02 11.00 FD1793 18.40 FD1793-02 11.00 FD1795 25.00 FD1797 21.00 WD1691 14.00 WD2143 12.00</p> <p>F.D. CONTROLLERS</p> <p>8272 35.00 75451BP 0.22 75452BP 0.22 75453BP 0.22 75454BP 0.22 75468N 0.88 75491N 0.31 75492N 0.41 AY-3-1015 3.50 AY-3-1270 9.40 AY-3-8910 6.40 AY-5-3600 8.84 DPB304 4.50 L203 0.99 LF398 3.80 LM301AN 0.30 LM308AN 0.94 LM308N 0.56 LM311N 0.60 LM311T 0.84 LM317T 1.06 LM319N 3.30 LM324N 0.50 LM337T 1.20 LM339 0.48 LM339N 0.48 LM348N 0.64 LM350T 3.12 LM358N 0.60 LM3900 0.68 LM393N 0.48 LM725CN 3.00 741CP 0.16 LM747CN 0.60 LM748CN 0.30 MC14113P 0.80 MC14116 0.80 MC14411 10.10 MC14412 14.20 MC1458CP1 0.35 MC1495L 1.40 MC1496P 4.40 MC1723P 3.10 MC3242A 4.14 MC3302P 6.30 MC3340P 2.36 MC3357P 1.90 MC3423PL 0.81 MC3441AP 2.90 MC3446AP 2.90 MC3447P 4.30 MC3448A 3.99 MC3470P 6.44 MC3480 7.76 MC3487 1.80 NE555P 0.25 NE556CP 0.65 RO32513-L 9.40 RO32513-U 9.40 TL010-CP 0.44 TL061-CLP 0.28 TL062-CP 0.47 TL064-CN 0.95 TL066-CP 0.28 TL071-CP 0.56 TL072-CP 1.10 TL081-CP 0.29 TL082-CP 0.49 TL084-CN 1.02 TL091-CP 0.39 TL092-CP 0.72 TL094-CN 1.30 TL487-CP 0.59 TL489-CP 0.59 TL494-CN 1.99 TL496-CP 0.59 78540DM 1.22 78540PC 6.08 ZN450-E 7.40 ZN451-E 29.95 ZN451-KIT 29.95</p> <p>DATA CONVERTERS</p> <p>ZN425E-8 3.76 ZN425J-8 8.00 ZN426E-8 1.90 ZN427E-8 6.68 ZN427J-8 12.50 ZN428E-8 5.10 ZN428J-8 9.70 ZN429E-8 1.60 ZN432C-10 20.79 ZN432E-10 13.00 ZN433C-10 25.00 ZN434 0.98 ZN435 4.38 ZN436E 1.26 ZN440 55.00 ZN441 46.80 ZN447 7.80 ZN448E 6.66 ZN448J 12.48 ZN449 2.72 ZN451 22.50 ZNA234E 9.40</p> <p>VOLTAGE REF.</p> <p>ZN404 0.50 ZN423 0.98 ZN458 0.92 ZN458A 0.80 ZN458B 1.12 ZN458C 1.12 ZN458D 1.12 ZN458E 1.12 ZN458F 1.12 ZN458G 1.12 ZN458H 1.12 ZN458I 1.12 ZN458J 1.12 ZN458K 1.12 ZN458L 1.12 ZN458M 1.12 ZN458N 1.12 ZN458O 1.12 ZN458P 1.12 ZN458Q 1.12 ZN458R 1.12 ZN458S 1.12 ZN458T 1.12 ZN458U 1.12 ZN458V 1.12 ZN458W 1.12 ZN458X 1.12 ZN458Y 1.12 ZN458Z 1.12</p> <p>BUFFERS</p> <p>81LS96 1.10 81LS97 1.10 81LS98 1.10 8T26A 1.10 8T28 1.10 8T28A 1.10 8T95 1.10 8T97A 1.10 8T98 1.10</p> <p>OPTOISOLATORS</p> <p>AN25 0.75 AN26 0.75 AN33 0.90</p> <p>UHF MODULATORS</p> <p>UM1111 2.95 UM1233 3.45</p> <p>VOLTAGE REG.</p> <p>7805 0.75 7812 0.75 7815 0.75 78HO5SC 0.72 78H12ASC 1.30 78HGASC 0.59 78L05 0.30 78L12 0.30 78L15 0.30 78540DM 7.50 78540PC 3.00 7905 0.95 7912 0.95 7915 0.95 LM309K 0.95 LM317K 2.45 LN323K 4.95 LM338K 4.50</p> <p>FAIRCHILD FAST</p> <p>74F00PC 0.60 74F04PC 0.60 74F08PC 0.65 74F109PC 0.65 74F11PC 0.52 74F138PC 0.52 74F151 1.26 74F151 1.26 74F157 1.26 74F158 1.17 74F161 2.34 74F164 1.68 74F175 1.82 74F181 3.90 74F189 5.10 74F190 3.20 74F191 3.20 74F194 1.68 74F20PC 0.52 74F240 3.16 74F241 2.42 74F243 2.80 74F244 2.96 74F245 6.08 74F251 1.26 74F251 1.26 74F257 1.26 74F258 1.34 74F280 1.74 74F283 1.74 74F32PC 0.52 74F352 1.26 74F373 3.16 74F374 3.16 74F379 1.83 74F381 6.62 74F382 4.22 74F398 3.16 74F399 2.70 74F521 2.76 74F533 3.16 74F534 3.16 74F537 6.02 74F538 4.38 74F539 4.38 74F64PC 0.52 74F74PC 0.58 74F86PC 0.77</p> <p>HIGH SPEED CMOS</p> <p>74HC00N 0.42 74HC02N 0.42 74HC03N 0.64 74HC04N 0.44 74HC08N 0.42 74HC107N 0.78 74HC109N 0.50 74HC10N 0.64 74HC112N 0.86 74HC113N 0.86 74HC132N 1.28 74HC137N 1.81 74HC138N 1.20 74HC139N 0.78 74HC151N 1.16 74HC153N 0.90 74HC157N 1.02 74HC158N 1.02 74HC160N 0.90 74HC161N 0.90 74HC162N 1.51 74HC163N 1.51 74HC164N 0.95 74HC165N 2.34 74HC173N 1.35 74HC174N 0.80 74HC175N 0.78 74HC194N 1.28 74HC195N 1.28 74HC20N 0.40 74HC237N 1.80 74HC240N 1.38 74HC241N 1.34 74HC242N 2.24 74HC243N 2.24 74HC244N 1.32</p> <p>74LS22 0.25 74LS221 1.08 74LS240 1.40 74LS241 1.40 74LS242 1.36 74LS243 1.36 74LS244 1.40 74LS245 1.95 74LS248 1.16 74LS249 1.16 74LS251 0.78 74LS253 0.78 74LS257 0.78 74LS258 0.78 74LS259 1.77 74LS26 0.30 74LS261 2.60 74LS266 0.35 74LS27 0.25 74LS273 1.35 74LS279 0.77 74LS28 0.25 74LS283 1.00 74LS290 0.86 74LS293 0.86 74LS30 0.25 74LS32 0.25 74LS33 0.30 74LS365 0.55 74LS366 0.55 74LS367 0.55 74LS368 0.55 74LS37 0.25 74LS373 1.22 74LS378 1.22 74LS379 1.50 74LS38 0.25 74LS386 0.50 74LS390 1.10 74LS393 1.10 74LS40 0.25 74LS42 0.85 74LS48 1.00 74LS49 1.00 74LS51 0.25 74LS54 0.25 74LS55 0.25 74LS57 0.30 74LS573 2.30 74LS574 0.35 74LS575 0.35 74LS576 0.35 74LS578 0.35 74LS583 1.10 74LS585 1.16 74LS586 1.16 74LS590 0.60 74LS591 0.60 74LS592 0.66 74LS593 0.66 74LS595 0.77</p> <p>CRYSTALS</p> <p>A1118 1MHz 4.50 A112A 1.008MHz 4.00 A113A 1.8432MHz 3.50 A116A 2.4576MHz 2.00 A120B 4MHz 1.25 A132A 6MHz 1.25 A140A 8MHz 1.25 A169A 3.6864MHz 2.00 A173A 9.8304MHz 2.75 A182A 19.6608MHz 2.50</p> <p>DIL SKTS TIN</p> <p>07070802 8 PIN 0.07 07071402 14 PIN 0.09 07071602 16 PIN 0.09 07071802 18 PIN 0.15 07072002 20 PIN 0.19 07072202 22 PIN 0.21 07072402 24 PIN 0.24 07072602 26 PIN 0.26 07074002 40 PIN 0.29</p> <p>DIL SKTS GOLD</p> <p>06060802 8 PIN 0.16 06061402 14 PIN 0.20 06061602 16 PIN 0.21 06061802 18 PIN 0.22 06062002 20 PIN 0.28 06062202 22 PIN 0.32 06062402 24 PIN 0.42 06062802 28 PIN 0.46 06064002 40 PIN 0.66</p> <p>4000 Series</p> <p>4000 0.25 4001 0.52 4002 0.25 4003 0.90 4004 0.25 4005 0.92 4006 0.25 4007 0.25 4008 1.18 4009 1.28 4010 0.45 4011 0.50 4012 0.65 4013 0.46 4014 0.63 4015 0.46 4016 0.39 4017 0.46 4018 0.46 4019 0.82 4020 0.34 4021 0.66 4022 0.25 4023 0.74 4024 0.52 4025 0.34 4026 0.93</p> <p>DIL SKTS W/WRAP TURNED PIN</p> <p>9090802 8 PIN 0.36 9091402 14 PIN 0.75 9091602 16 PIN 0.86 9091802 18 PIN 1.06 9092002 20 PIN 1.09 9092202 22 PIN 1.18 9092402 24 PIN 1.28 9092802 28 PIN 1.50 9094002 40 PIN 1.70</p> <p>ZIF SOCKETS</p> <p>08082402 24 PIN 5.70 08082802 28 PIN 6.95 08084002 40 PIN 8.25</p>
---	--

Hi-Tech
components



0379 4131

components

GILRAY ROAD, DISS, NORFOLK. TEL: 0379 4131

INSULATION DISPLACEMENT CONNECTOR SYSTEM

LEADERS	SHROUDED 90°	OPEN 90°	OPEN — STRAIGHT PINS
10 way	0.86	0.65	0.47
12 way	1.22	0.83	0.59
14 way	1.34	0.92	0.65
16 way	1.36	1.13	0.77
18 way	1.70	1.40	0.95
20 way	2.04	1.78	1.19
22 way	2.28	2.07	1.37
24 way	2.70	2.54	1.67
26 way	3.20	3.02	1.96

CABLE ASSEMBLIES

IDC JUMPERS SINGLE ENDED

36" cable	IDC socket
10 way	1.72
14 way	2.07
16 way	2.22
20 way	3.14
26 way	3.75
34 way	3.98
40 way	4.23
50 way	5.36
60 way	6.36

DIP JUMPERS

Single Ended — 24" cable

14 pin	1.73
16 pin	1.90
24 pin	2.73
40 pin	3.96

Double Ended

6" cable	12" cable	18" cable
14	2.74	2.84
16	3.03	3.14
24	4.18	4.36
40	5.89	6.18

SOCKETS

10 way	0.88
12 way	1.06
14 way	1.16
16 way	1.38
18 way	1.66
20 way	1.94
22 way	2.08
24 way	2.78
26 way	3.34

DIP PLUGS

14 way	0.92
16 way	1.06
20 way	1.60
24 way	2.40

DISC DRIVE CONNECTING CABLES

34 way card edge to 34 way card edge 1M	11.30
34 way card edge to 2 x 34 way card edge 1.5M	18.00
34 way card edge to 34 way IDC SKT (BBC) 1M	8.50
34 way card edge to 2 x 34 way IDC KT (BBC) 1.5M	14.50
BBC Power Cable — Single Drive	3.50
BBC Power Cable — Dual Drive	4.75

RIBBON CABLE (PRICED PER FOOT)

GREY	RAINBOW
10 way	0.86
16 way	1.17
20 way	1.37
26 way	1.67
34 way	1.87
40 way	2.23
20	0.28
25	0.34
26	0.35
34	0.45
40	0.52
50	0.64
60	0.76

BBC MICRO CONNECTORS

DIN PLUG 7 PIN	0.40
DIN PLUG 6 PIN	0.40
DIN PLUG 5 PIN 180°	0.40
DIN PLUG 5 PIN DOMINOE	0.40
POWER PLUG (36" CABLE)	3.00
ANALOGUE INPUT PLUG	2.25
5 WAY DIN SKT 180°	0.90
5 WAY DIN SKT DOMINOE	0.90
6 WAY DIN SKT	0.90
7 WAY DIN SKT	0.90
15 WAY DIN SKT	2.15

Connecting cables for personal computers

A comprehensive range of high quality interconnecting cables for popular micro computers. All cables utilise high quality connectors and are individually tested to ensure trouble free use.

Part number	Description	Computer	Price
ON100	Phono plug to phono plug (2M)		1.20
ON101	Phono plug to BNC plug (2M)		2.95
ON102	BNC plug to BNC plug (2M)		3.95
ON107	6 pin DIN to open end (1M)	BBC	1.05
ON108	6 pin DIN to 6 pin DIN (1M)	BBC	1.50
ON119	Phono plug to coax plug		1.35
ON160	DIN plug to 2 phono plugs	Dragon	1.20

Cassette recorder cables

ON109	7 pin DIN to open end	BBC	1.25
ON110	7 pin DIN to 2 x 3.5mm + 1 x 2.5mm J/plug	BBC	2.50
ON111	7 pin DIN to 5 pin DIN + 2.5mm J/plug	BBC	2.50
ON118	5 pin DIN to 2 x 3.5mm J/plugs	Spectrum/ZX	2.50
ON117	5 pin DIN to 2 x 3.5mm + 1 x 2.5mm J/plug	Dragon	2.50

Parallel printer cables

ON130	36 way plug to 36 way plug (2M)	Sirius/Apricot	18.00
ON131	36 way plug to 36 way plug (5M)	Sirius/Apricot	26.50
ON132	36 way plug to 36 way socket (2M)		18.00
ON133	36 way plug to 36 way socket (5M)		26.50
ON144	36 way plug to 25 way male D type (2M)	IBM/TI PC	19.00
ON145	36 way plug to 25 way male D type (5M)	IBM/TI PC	27.50
ON134	36 way plug to 25 way male D type (2M)	RML/Apple	19.00
ON135	36 way plug to 25 way Male D type (5M)	RML/Apple	27.50
ON142	36 way plug to 20 way IDC socket (2M)	Dragon	13.95
ON139	36 way plug to 26 way IDC socket (2M)	BBC	9.95
ON140	36 way plug to 26 way IDC socket (5M)	BBC	22.95
ON141	36 way plug to 34 way card edge (2M)	TRS80 Lev. 1	18.50
ON143	36 way plug to 34 way IDC socket (2M)	TRS80 Lev. 2/ Memotech	10.95

RS232 Cables

ON106	25 way male D type to 5 pin DIN	BBC	5.85
ON128	'Universal' RS232 cable (pins 1-8, 20 connected and 20 jumpered as required) 2M		15.95
ON164	'Universal' RS232 cable as above but 5M		20.95
ON120	25 way male to male 1-25 connected (2M)		16.95
ON121	25 way male to male 1-25 connected (5M)		22.50
ON122	25 way male to male 1-25 connected (10M)		32.50
ON123	25 way male to male 1-25 connected (30M)		68.00
ON124	25 way male to female 1-25 connected (2M)		15.45
ON125	25 way male to female 1-25 connected (5M)		21.00
ON126	25 way male to female 1-25 connected (10M)		31.00
ON127	25 way male to female 1-25 connected (30M)		66.50
ON129	25 way male to 9 way male	Spectrum	15.95
ON162	25 way male to 9 way male	Macintosh	15.95
ON163	25 way male to 5 pin DIN	RML 480Z	14.95

PART NO.	DESCRIPTION	MAIL ORDER PRICE
BBC MICROS AND ACCESSORIES		
ANB01	BBC Model B Micro	£325.00
ANB02	BBC Model B Micro with Econet I/F	£385.00
ANB03	BBC Model B Micro with Disc I/F	£406.00
ANB04	BBC Model B Micro with Disc & Econet	£445.00
ALA01	Acorn Electron	£139.00
ANB21	DNFS ROM	£17.91
ANB23	Disc Interface Kit	£71.65
ANB14	Speech Interface	£40.00
ANK01	IEEE488 Interface Adaptor	£277.75
ANB22	Econet I/F Kits	£35.00
BBC 45	Joysticks	£8.00
STAND	Monitor Stand	£7.50
SRE1	Sideways ROM Expansion Board	£25.95

DISC DRIVES WITHOUT POWER SUPPLY

BBC30	Single 100k TEC 40 track single sided	£99.95
BBC31S	Single 100k TEC (expandable to dual) 40 track	£115.00
BBC31D	Dual (2 x 100k) TEC 40 track single sided	£225.00
BBC34	Single 400k TEC 80 track double sided	£174.00
BBC34S	Single 400k TEC (expandable to dual) 40/80 track switchable double sided	£194.00
BBC34SW	Single 400k TEC 40/80 track switchable double sided	£184.00
BBC34D	Dual (2 x 400k) TEC 40/80 track switchable double sided	£310.00
BBC34S/80	Single 400k TEC (expandable to dual) 80 track double sided	£184.00
BBC34D/80	Dual (2 x 400k) TEC 80 track double sided	£300.00

DISC DRIVES WITH POWER SUPPLY

BBC30P	Single 100k TEC 40 track single sided with P.S.U.	£130.00
BBC31SP	Single 100k TEC (expandable to dual) 40 track with P.S.U.	£150.00
BBC31DP	Dual (2 x 100k) TEC 40 track single sided with P.S.U.	£250.00
BBC34P	Single 400k TEC 80 track double sided with P.S.U.	£209.00
BBC34SP	Single 400k TEC (expandable to dual) 80 track with P.S.U.	£229.00
BBC34DP	Dual (2 x 400k) TEC 40/80 track switchable with P.S.U.	£345.00

MECHANISMS

FB501	TEC 100k single sided	£91.00
FB504	TEC 400k double sided	£150.00

FLOPPY DISCS

MD-1C/B	Nashua single sided, single density 40 track (10 discs)	£12.00
MD-1DC/B	Nashua single sided, double density 40 track (10 discs)	£13.00
MD-2DC/B	Nashua double sided, double density 40 track (10 discs)	£15.50
MD-2FC/B	Nashua double sided, quad density 80 track (10 discs)	£17.85

SPECIAL OFFER

BBC40TD	BASF double sided, double density 40 track (10 discs)	£14.00
---------	---	--------

DISC STORAGE BOXES

MDT25/3	3 1/2" Flip 'N' file Micro disc box (cap. 25)	£7.75
DT25/5	5 1/4" Flip 'N' file lockable disc box (cap. 25)	£18.77
DT60/5	5 1/4" Standard lockable disc box (cap. 60)	£10.65

MONITORS

9MON	9 inch green screen high resolution NEC high quality monitor	£125.00
12MON	12 inch green screen high resolution NEC high quality monitor	£135.00
1431	Microvitec 14" RGB colour monitor	£175.00
1441	Microvitec 14" RGB colour monitor high resolution	£410.00
1451	Microvitec 14" RGB colour monitor medium resolution	£295.00
1431/AP/MS	Microvitec 1431 PAL & RGB inputs and sound facility	£225.00

BBC COMPATIBLE SOFTWARE

5BB03	View Rom	£45.00
5BB04	View Printer Driver	£7.50
AES20	Fileserver Level 1-40 track	£80.50
AES21	Fileserver Level 2-80 track	£202.00
5NB08	Acornsoft Invoicing program	£16.00
5NB09	Acornsoft Mailing System program	£16.00
5NB10	Acornsoft Accounts Receivable program	£16.00
5NB11	Acornsoft Stock Control program	£16.00
5NB12	Acornsoft Order Processing program	£16.00
5NB13	Acornsoft Accounts Payable program	£16.00
5NB14	Acornsoft Purchasing program	£16.00
SNL01	Forth — 40 track	£15.00
SNL02	Lisp — 40 track	£15.00
SNL04	Microtext — 40 track	£47.50

MATRIX PRINTERS

RX80	Epson RX80 100cps matrix printer	£204.00
RX80F/T	Epson RX80F/T 100 cps matrix printer friction or tractor feed	£231.00
FX80	Epson FX80 150cps matrix printer	£328.50
MTB0SP	Mannesmann Tally MTB0 matrix printer friction or tractor feed with film ribbon and tear off facility	£209.00

LETTER QUALITY PRINTERS

HR5	Brother HR5 Thermal printer A/C mains or battery	£115.00
HR15	Brother HR15 Daisy wheel printer (13cps)	£326.00
HR25	Brother HR25 Daisy wheel printer (23cps)	£550.00
UCHIDA	Uchida DWX305 Daisy wheel printer (20cps)	£227.00

PRINTER SUPPLIES

11241P160	11 x 9 1/2 part plain listing paper (2,000)	£11.25
11241P2C1	11 x 9 1/2 part (otc) plain listing paper (1,000)	£14.00
11241P3C1	11 x 9 1/2 part (otc) plain listing paper (700)	£16.25
11370R1C1	11 x 14 1/2 part ruled listing paper (2,000)	£13.50
11370R2NC	11 x 14 1/2 part (nct) ruled listing paper (1,000)	£22.50
11370R2C1	11 x 14 1/2 part (otc) ruled listing paper (1,000)	£15.00
12235P160S	12 x 9 1/2 part plain listing paper with side perms (2,000)	£12.00
HR1R	Brother HR1 ribbon	£2.20
RIB119	Diablo Hytype II Multistrike film ribbon	£1.75
GP205	Diablo Hytype II fabric ribbon	£2.50
MX80	Epson MX80, RX80, FX80, fabric ribbon	£3.00
MT80	Mannesmann Tally MT80 film ribbon	£6.50
RIB117	Uchida DWX305 multistrike film ribbon	£2.75
HR5R	Brother HR5 ribbon	£2.20
HR15R	Brother HR15 multistrike ribbon	£4.00
HR25R	Brother HR25 multistrike ribbon	£4.00
	Brother daisy wheels	£14.00
	Uchida/Qume daisywheels	£4.00
LAB089361C	3 1/2 x 1.7/16 Labels — 1 wide (12,000)	£20.00
LAB089361S	3 1/2 x 1.7/16 Labels — 1 wide (2,000)	£13.00
LAB070363F	2 1/2 x 1.7/16 Labels — 3 wide (1/10") (2,000)	£8.00

COME AND JOIN US!

Due to Phil Walker's impending move to a senior position in industry, we are seeking a **Project Editor** to take over his role on ETI. The job involves designing, prototyping and writing-up projects for publication in ETI, checking submissions from other authors, answering queries, and generally being our resident know-it-all and technical genius. For a particularly experienced appointee, there could be scope for a role as technical referee on the group of ASP electronics magazines.

We have an open mind over the sort of person who might do this job. However, the person appointed will definitely have a good, practical knowledge of electronics, and would be competent to design in digital, including computer, electronics as well as analogue.

Please **write** to Dave Bradshaw, Editor, Electronics Today International, 1 Golden Square, London W1R 3AB, enclosing your CV and, where possible, brief details of one or two items that you have designed yourself. Closing date for applications will be 30th November 1984.

ATTENTION ALL WRITERS . . .

... or just those of you who sometimes think "I could do better than that!"

We want to hear from you!

The magazine you hold in your hand is part of ASP's electronics group of titles. These include *ETI*, *Ham Radio Today*, *Digital and Micro Electronics*, and our new magazine, *Electronics*. All these magazines are looking for new authors, so if you've designed something for yourself that you think may be of interest to others, or if you've a subject you'd like to write a feature article on, then drop us a line with an outline of what you have in mind.

We particularly need:

- Projects for the Commodore Vic 20 and 64, the Amstrad, the BBC A and B, and the Electron computers;
- Simple projects that do something useful, perhaps in a novel or instructive way;
- Radio projects (not necessarily for radio amateurs);
- Features on amateur satellite radio.

If you're interested in writing for us, send an outline of your proposed article to: Dave Bradshaw, Group Editor (Electronics), Argus Specialist Publications, 1 Golden Square, London W1R 3AB.

Please note that while we take ever care, we cannot be held responsible for the loss of unsolicited manuscripts. We advise all authors to keep a photocopy or carbon copy of any article they send us.

EXPERIMENTERS' 64K DRAM CARD

Gnosis: knowledge of spiritual mysteries (Concise Oxford Dictionary); Gnos-ex: expandable memory system (ETI Dictionary). Phil Walker tries again for the obscure pun of the year award.

The ETI GNOS-EX is the expandable, flexible dynamic memory system for the keen experimenter. Using the 4416 16K X 4 dynamic memory devices, the system can be populated and configured for from 16K to 64K blocks with the capability of deleting or including memory in 1K blocks.

Last time we published a DRAM card for the 6502, we used the 74LS608 memory controller. Since then, we've discovered there are problems with this device (don't worry if you're trying to get that board going — we're working on a fix!). So this system was designed to do without any very special control devices and rely, so far as possible, on absolutely standard ICs which will be (we hope!) readily available for some time to come and cheap. In the final design the most unusual devices are the 4416 memories and the PROM. This latter device is not actually absolutely essential for the operation of the project and could be replaced by suitable logic.

The layout of the PCB is intended to be such that it will plug into a Microtan system bus, although at the time of writing this it has not been tested. The original development work was carried out on the author's Ohio Superboard, somewhat modified with the processor running at 1.25MHz.

The Circuit

The basic ideas behind this project are much the same as any other which makes use of dynamic memories. There are two distinct phases of operation; the first, and most important as far as the user is concerned, is the reading or writing data, ie actually using the memory. The second is the periodical refreshing of the stored data to make sure that it is remem-

bered correctly. Ideally, the refresh operation should not be apparent to the user, and so it must take place when the processor is not using the memory.

In the case of the 6502 microprocessor, for which this project is designed, the processor is concerned with accessing the memory for only half the time. The remaining time can be used for refreshing the memory with no effect on the processor. With the 6502 running at 1MHz there is about 500ns in which the processor will read or write data as necessary, followed by 500ns or so in which the processor is doing internal operations and not interested in the outside world; this is the time we use to do a refresh operation.

The 4416 specification requires that the whole memory be refreshed at least every 4ms. To do this, 256 different addresses must be put on the address lines and the RAS input pulsed low for a cer-

tain time for each one. All this must be done within the 4ms allowed. In this design it will be done every 256 μ s with a 1MHz processor clock.

The circuit consists of several elements. First, there is an address multiplexer which takes the 16 address lines from the processor and switches them to the eight address lines of the memories during the processor access cycle. Only 14 of the address lines are used, eight are latched into the memory ICs by the RAS signal and six by the CAS signal.

Second, and allied to the above, there is the refresh address counter and buffer. The eight-bit counter is incremented at the end of each refresh cycle and provides the 256 addresses necessary for the complete operation. The tri-state bus buffer puts the output from the counter on the memory address pins starting mid-way through the previous processor

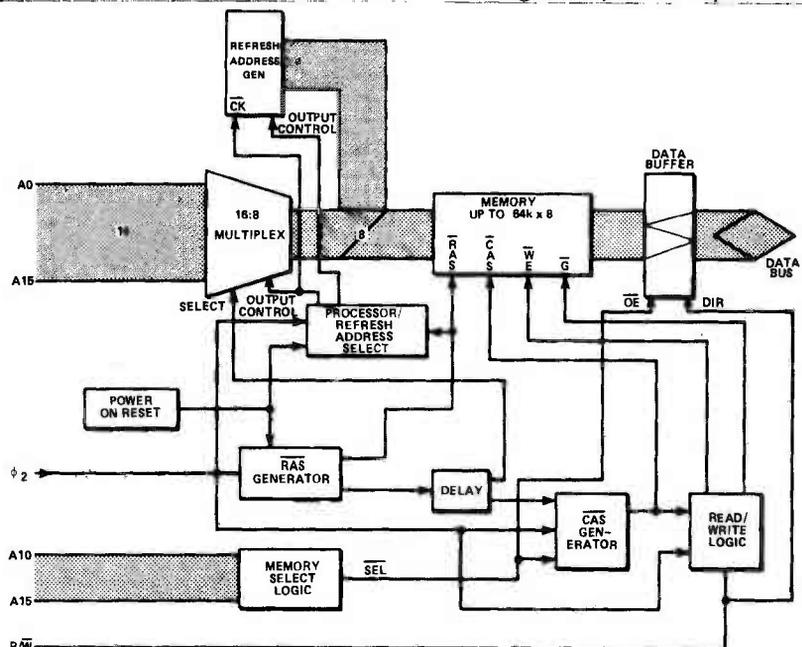


Fig. 1 Block diagram of the card

NOTE
 IC1 IS 74LS245
 IC2,3 ARE 74LS257
 IC4 IS 74LS10
 IC5 IS 74LS16
 IC13 IS 74LS244
 IC14 IS 74LS393
 IC16 IS 74LS122
 IC17 IS 74LS14
 IC18 IS 74LS14
 IC19 IS 74LS128

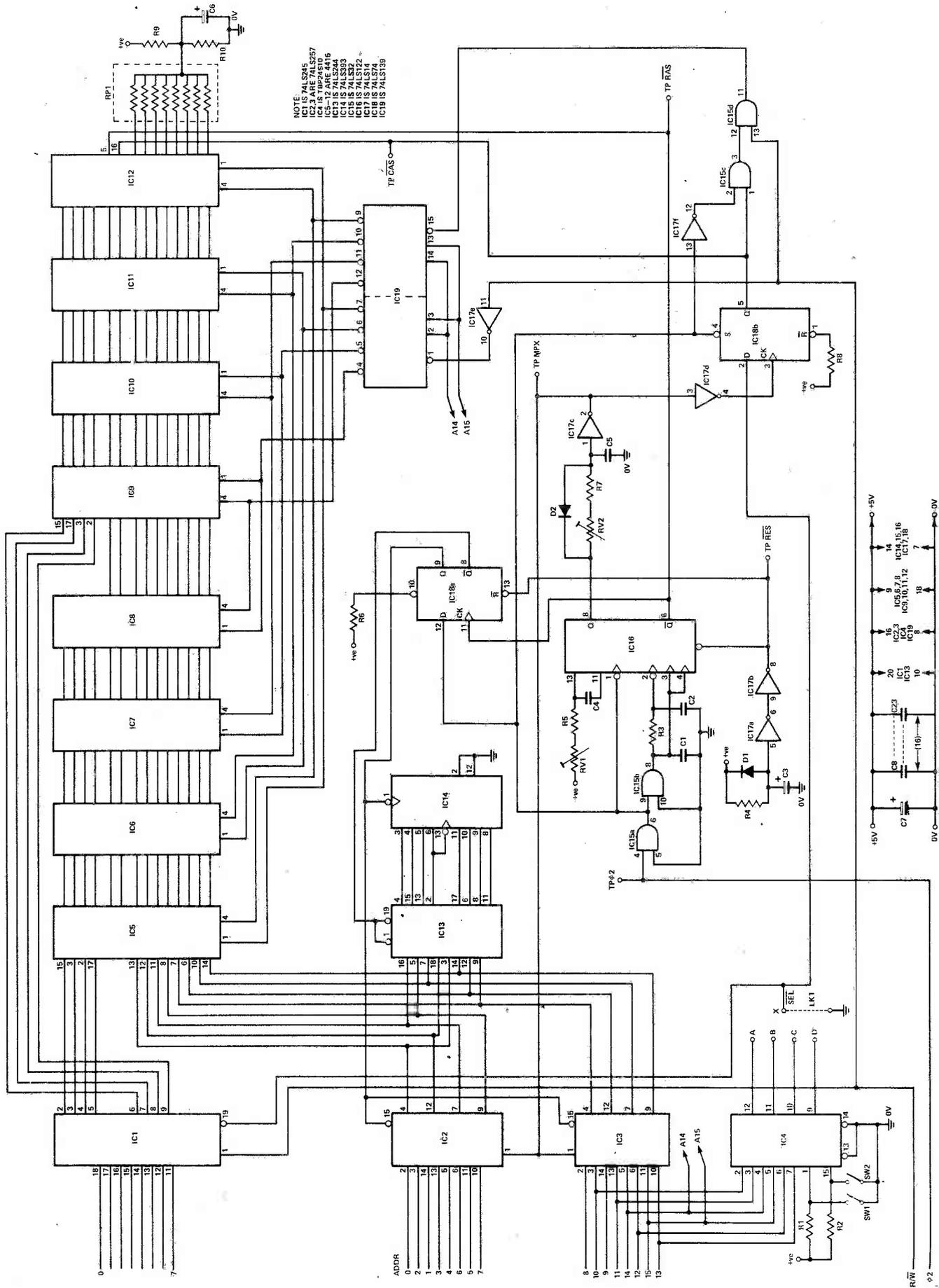


Fig. 2 Main circuit diagram

HOW IT WORKS

In this section we shall dispose of the simpler functions first. IC1 is an eight bit bi-directional data buffer. Its direction of transmission is determined by the state of the R/W line from the processor. It is enabled by the SEL signal from the address decoding PROM when the processor requires access.

The address decoder PROM is about the easiest way of providing full decoding of the address space into 1K byte blocks. As supplied by the manufacturer the TP24S10 has all its memory cells at a logic high level. In this project this corresponds to the board not being selected. In order that the memory will respond to any block of addresses, the corresponding locations in the PROM must be blown to the low state. Since the PROM has four bits per location, three more memory maps can be blown into the device to cater for future modifications to your system and link LK1 moved to use the appropriate bit. Also, since only six of the eight address lines are used for the decode, SW1 and 2 are provided so that you can have up to four address maps for each link position.

If the blowing of a PROM is difficult for you then a 74LS151 one of eight selector IC can be used to simulate some of its operation.

In order to ensure that the circuit starts up correctly when power is applied, R4 and C3 together with IC17a and b form a power-on-reset circuit which gives a logic low for 25ms or so after the power is first applied. D1 across R4 ensures that C3 is discharged rapidly when power is removed and also protects the input circuitry of IC17a.

IC2 and 3 are quadripole two-to-one multiplexers which are used to switch the 16 processor address lines onto the eight memory address lines at the right time. 'LS257s are used here instead of the more usual 'LS157s because they have outputs which can be made high impedance by the state of a single input pin. By using this facility the processor address bus is applied to the memory at the start of the processor access cycle. At the end of the processor cycle the outputs of IC2 and 3 are turned off and IC13 outputs are turned on, allowing the state of the refresh counter IC14 to be applied to the memory address inputs in readiness for a refresh cycle.

IC13 is an eight-bit bus buffer while IC14 is a dual four-bit binary counter connected to provide the eight bit refresh address. To ensure that the outputs

of IC14 are steady while the refresh cycle is in progress, IC14 is clocked as the outputs of IC13 are disabled thus the transitions of IC14 will be over long before the next refresh address is gated onto the memory inputs.

The next part of the circuit is where the main work is done. The main timing signal ϕ_2 from the processor goes to IC15a where it is buffered; from IC15a a output it passes through IC15b where it is delayed a little and through R3 and C2 where it is delayed a little more. When ϕ_2 goes low the falling edge at IC16 pin 1 causes IC16 to generate a pulse at its output. IC16 is a monostable whose period is set by RV1, R5 and C4. Note that due to the delays in IC15b and R3/C2, pins 2, 3 and 4 will still be at a high level when this occurs. This satisfies the trigger conditions for the device in this case.

When, on the other hand, ϕ_2 goes high, pin 1 will go high first followed by pins 3 and 4 and then pin 2. The combination of pin 2 low and pins 3 and 4 going high is another valid triggering combination for IC16 and it will trigger again. This arrangement gives a pulse at both the rising and falling edges of the ϕ_2 input signal.

The low-going output from the Q output of IC16 is used as the RAS or row address strobe signal for the memories. Its falling edge causes the first eight bits of the address to be latched internally.

The high-going signal from the Q output of IC16 is somewhat delayed by RV2, R7 and C5 and inverted by IC17c. This signal causes the address multiplexers IC2 and 3 to apply the other eight address bits to the memory inputs ready for the next operation. The output from IC17c is inverted and, incidentally, slightly delayed by IC17d before going to the clock input of IC18b.

Normally the Q output of IC18b is set to the high state every time ϕ_2 is low, but if ϕ_2 is high and the clock input goes high, the state of the SEL signal is transferred to the Q output. If the memory board is selected, SEL will be low and IC18b Q output will go low, otherwise it will remain high.

The output from IC18b is used as the CAS or column address strobe signal for the RAMs. Its falling edge causes six more addresses to be latched into the memories, making the total up to the 14 necessary to access one of the 16384 locations.

A little while later, the monostable

IC16 finishes its pulse. The delay network RV2, R7 and C5 is reset quickly via D2 ready for the next RAS cycle. As the Q output or RAS signal goes high it also clocks IC18a. This transfers the state of the ϕ_2 signal to its outputs which in turn control the outputs of the refresh buffer and processor multiplexers.

If ϕ_2 is high the next RAS cycle will be a refresh and IC13 will be enabled. If ϕ_2 is low the next RAS cycle will be a processor access if required and the outputs of IC2 and 3 will be enabled.

Note that the power-on-reset circuit ensures that the control logic starts up with the RAS generator disabled and the multiplexers enabled. It must be arranged that the software allows at least eight RAS only cycles of the memory before it is accessed. This would normally occur while the processor registers are being initialised.

The remaining logic is concerned with reading and writing the memories. The design of the project does not aim for minimum power consumption so all the memories are accessed during each cycle. However, to read data from one pair of them, its G input must be low. This signal is derived by simply inverting the R/W signal from the processor and passing it through IC19a. This is half of a one-of-four demultiplexer and its output driven is determined by the states of the

two most significant address lines. The selected output then enables one of the four pairs of memories and allows it to output its data.

To write data into the memories, the WE input must be taken low. To accomplish this, the R/W signal is gated with the inverted ϕ_2 signal from IC17f and the CAS signal. This is done to ensure that it cannot occur at the wrong time. The outputs from IC15c and d then enable IC19b which routes it to the WE inputs of the pair of memories determined by the states of A14 and A15 of the address bus. This arrangement also delays the write command a little and allows a little extra time for the data to arrive from the processor.

The last components on the PCB worth a mention are the resistor pack and R9, 10 and C6. These are provided to terminate the address lines and suppress reflections of the signals travelling back along them. On this size of board, they may well not be necessary.

The final point to note is that the top address lines A15 and A14 are multiplexed onto the memory address inputs during the CAS cycle, but the memory ICs ignore them. This may prove useful if 64K by 4 bit devices become available (with eight multiplexed address pins) in the near future.

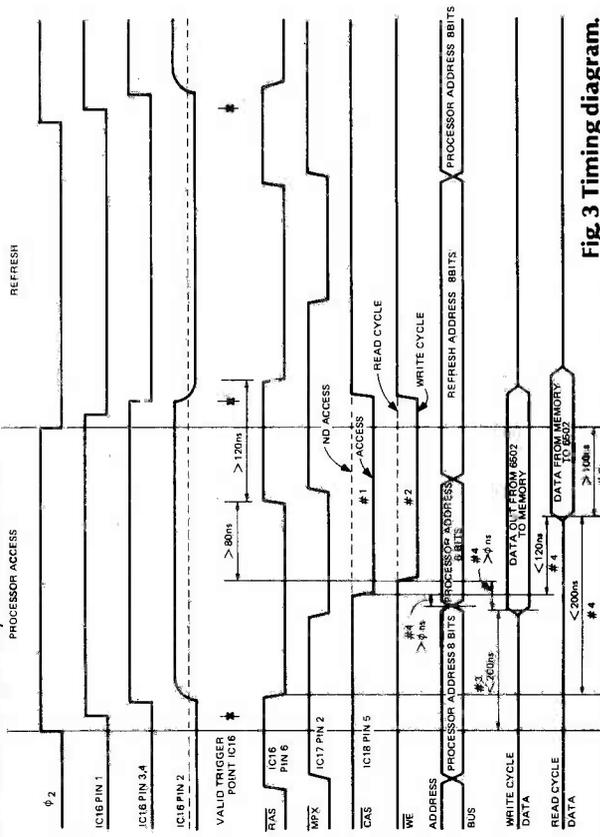


Fig. 3 Timing diagram.

cycle until mid-way through the refresh cycle. During this time, the outputs from the multiplexer ICs are made high impedance to avoid conflict.

The next section, and possibly the most important as far as this design is concerned, is the RAS generator. This is basically a monostable but with extra logic to make it trigger from both the rising and falling edges of the ϕ signal. The ϕ signal is the main timing output from the 6502 processor. The dual triggering capability enables the circuit to generate the row address strobe (RAS) signal for both refresh and processor access with one device and one adjustment.

Following on from the $\overline{\text{RAS}}$ generator, there are two functional

blocks, one of which determines the memory address source for the next cycle from the current state of the ϕ signal. The other provides a short delay in which the first eight bits of the processor address are held steady before switching over to the next six bits in readiness for the CAS signal.

The delay circuit also triggers the column address strobe (CAS) generator which, if all its input conditions are correct, will provide a low output signal to the end of the cycle. Note that this signal will only occur if ϕ is high and the select logic output is low. The state of the select logic is sampled after a delay from the RAS signal falling edge; if it is low then the CAS output may go low. If, however, ϕ is low then CAS will stay

high. This occurs during a refresh cycle. If, during a processor cycle, the CAS output does go low it will remain low until the end of the cycle when ϕ going low will force it high again. This allows data to remain available at the output of the memories until the end of the processor cycle without the use of a separate latch.

The last major section of the circuit consists of the read/write select logic. This also performs the function of selecting which pair of memory chips is accessed. Each memory device has a write enable (WE) input and an output control (G). The latter has the effect of allowing data to be output from the device only when this line is low. The former causes data to be written into the memory matrix

when it is taken low provided that the RAS and CAS signals have been properly set up. The WE signal is allowed to be generated only if a CAS signal is present, and so will occur only in a processor cycle when the select logic output is low and the R/W is also low.

In order to keep the loading on the processor data bus low and to avoid handling problems due to static on the memory data pin, a data buffer is provided. Its direction of transmission is determined by the state of the R/W line and it is enabled when required by the SEL signal from the select logic.

The select logic on the board is intended to be a TBP24S10 256 x 4 bit PROM. Only the six MSBs of the address bus are connected to the PROM and thus only 64 of

Programming The PROM

- require programming skip steps 5 through 11.
- Increase V_{CC} to $V_{CC(p)}$ with a minimum current capability of 250 milliamperes.
 - Apply $V_{S(p)}$ to all the S, E or G inputs. $I_{S(p)} \leq 25$ milliamperes. Active-high enables may be left high.
 - Connect all outputs, except the one to be programmed, to

- Only one bit is to be programmed at a time.
- Apply the output programming pulse for 20 microseconds. Minimum current capability of the programming supply should be 250 milliamperes.
- After terminating the output pulse, disconnect all outputs from V_{IL} conditions.
- Reduce the voltage at S, E, or

G inputs to V_{IL} .


- Decrease V_{CC} to 0 volts.
- Return to step 4 until all outputs in the word have been programmed.
- Repeat steps 2 through 11 for each word in memory.
- Verify programming of every word after all words have been programmed using V_{CC} values of 4.5 and 5.5 volts. Note that registered PROMs must be checked to verify the output condition.

As already stated, the PROM address lines are not used in order; the connections are as follows:

Address Line	PROM Pin	PROM Pin Designation
A15	5	A0
A14	4	A3
A13	7	A2
A12	6	A1
A11	3	A4
A10	2	A2

When you come to do the programming, program one location at a time. The manufacturers do not recommend manual programming of this device, but you may get away with it. The recommended programming procedure is as follows:

- Address the word to be programmed, apply 5 volts to V_{CC} .
- Verify the status of a bit location by checking the output level.
- Decrease V_{CC} to 0 volts.
- For bit locations that do not

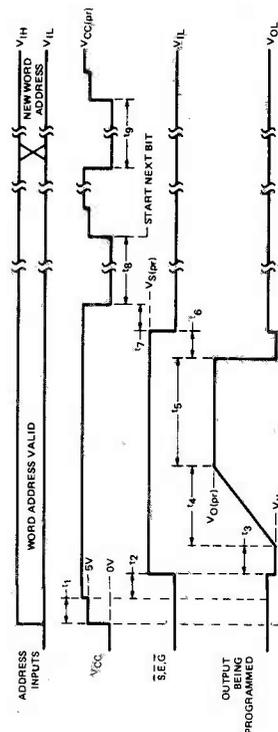

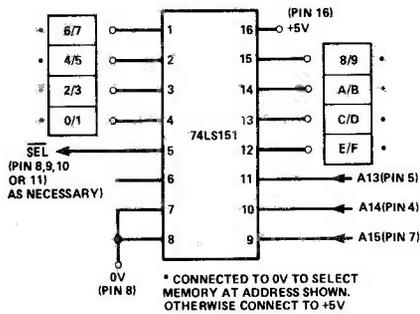


Fig. 7 Use of 74LS151

the locations are available. SW1 and SW2 can be used to gain access to three others sets of 64 locations. Also, only one of the four output bits of the PROM is used — selected by LK1 — so a total of 16 different memory maps can be held by each PROM. Note that unlike a previous design for a memory board using this device, the output of the PROM must be programmed LOW to enable the appropriate part of the memory map. Note also that the address lines are not used in order.

If desired it should be easy to wire one or two chips to a 16 pin DIL plug for use in place of the PROM.

Construction

This stage of the project is not difficult but just seems exceedingly tedious. Step one is to check that all the components will fit their holes. Note that the DIN 41612 connector usually needs 1mm holes for its leads as does C7. All the other components, except RV1 and 2 which need 1.2 to 1.5mm holes, will fit into 0.8mm holes.

Step two is to take all the components off the PCB (you didn't solder them on — did you?) and make all the through-board links. The easiest way we know of doing this cheaply is to take a length of 22swg tinned copper wire, stretch it a little to make it straight and stiff, squeeze the very end with pliers to flatten it out so that it will not fall through the holes in the PCB and then cut off about ¼ inch (6mm). Repeat this process until you have enough pieces to go through all the link holes.

Support the PCB clear of the table top with the component side uppermost. Working from one end of the board, put about a dozen of the links in the proper holes and solder them in place. Turn the board over and put it flat on the table with a piece of kitchen tissue for protection, and solder all the links on this side as well. Clip off

all excess wire and repeat until all the links are made.

Step three is to fit all the IC sockets. Note that IC5 to 12 are the opposite way round to the others. Then fit the DIN 41612 edge connector and the other passive components except R9. Make sure that the diodes and electrolytic capacitors are the right way round.

At this stage it is advisable to check that there is not short circuit on the power supply lines. If this test is OK then R9 can be fitted. Check also that 0V and +5V supplies are connected to each IC socket. Examine the PCB tracks carefully, especially around the edge-connector socket, for breaks or solder bridges, as these will be very difficult and possibly expensive to find later.

Step four is to insert IC15, 16, 17 and 18. Apply power to the board and check that it does not draw more than 100mA or so. Now connect a 1MHz TTL compatible square wave signal to the ϕ_2 test point. With an oscilloscope (or otherwise, as equipment allows) monitor the RAS test point and adjust RV1 such that the high time is about 150ns. If this cannot be done, check your PCB again and verify the component values of RV1, R5 and C4. Also check that there are two pulses per 1 μ s — check C1, 2 and R3 if not. CAS testpoint should be continuously high.

If you have got this far successfully, remove power from the PCB and link X to E. Reapply power and check RAS signal again. Now check that the CAS testpoint has a low pulse while the ϕ_2 signal is high. Adjust RV2 if necessary to see this. If this signal does not appear check RV2, R7, D2 and C5 and the signals at IC17c and d.

If all is correct, adjust RV2 such that the CAS signal goes low about 100ns after the RAS signal goes low. This should set the main timing to about the right area for normal operation.

Switch off the power again and insert IC2, 3, 13, 14 and 19. Switch on again and check that all eight outputs of IC14 are counting. Check that the outputs of IC18a are switching on the rising edge of the RAS signal. Check also that IC19 pin 4 is permanently low and all other outputs from IC19 are high. Now connect the R/W input to the board to 0V and check that all outputs from IC19 except pin 9 are permanently high. Pin 9 should

be pulsing low with approximately the same signal as that on the CAS testpoint. Pulling A14 or A15 inputs low should alter the pin numbers but not the signal.

If you have got this far successfully there is only one more thing to do before inserting the memory devices. This is to check the power-on-reset circuit. Incidentally if this does not work correctly it could have given you problems earlier. Temporarily short-circuit C3 and monitor the output of IC17b. This should be low. Remove the short from C3 and check that the output of IC17b stays low for at least 200ms (probably nearer 500ms). During this time the RAS and CAS signals will be high. Note that ϕ_2 signal should be present as early as possible to ensure that the CAS signal is forced high, although the ϕ_2 line being low will also accomplish this.

The last thing to do now is to insert the 4416 memory devices and IC1. The memory ICs are accessed in pairs, so if you are not using the full complement you must insert IC8/9, 7/10, 6/11 and 5/12 in pairs. This is also the order in which they appear in the memory space. Remove the X-E link and insert a TBP24S10 suitably programmed into the IC4 socket and link X to A, B, C or D as appropriate. Alternatively, plug a 16-pin header into IC4 socket with, for example, a 74LS151 connected up to select the memory in 8K blocks. However you do it, the SEL signal at X must be low to read or write to or from the board.

A feature of this design is that the SEL signal needs to be low only a short time before the CAS signal is generated in order to activate the memory control but must be held until the end of the ϕ_2 cycle for a read operation or the end of the RAS signal for a write cycle in order for valid data to be read or written by a 6502 processor. This should not be a problem for any normal address decoder logic.

ETI

BUYLINES


Everything you need is readily available. Technomatic, Watford, Cricklewood and others supply all of the semiconductors (but note that the TBP24S10 is usually listed simply as a 24S10) and the PCB is available from our PCB Service.

PRINTED CIRCUIT MATERIALS

A small selection from our catalogue -

TRACK TAPES

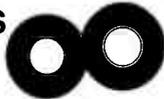Precision slit black crepe tapes (1 roll/pack).



HB209	TAPE .020"	£1.05
HB210	TAPE .025"	£1.05
HB211	TAPE .031"	£1.05
HB212	TAPE .040"	£1.05
HB213	TAPE .050"	£1.05
HB214	TAPE .062"	£1.05
HB215	TAPE .080"	£1.20
HB216	TAPE .100"	£1.20

PADS

Pre-printed dense black on .0012 acetate film (500/roll)



	O/D	I/D	
HB222	PAD .062/.025		£3.05
HB223	PAD .075/.025		£3.05
HB224	PAD .100/.031		£3.05
HB225	PAD .125/.031		£3.05
HB226	PAD .150/.031		£3.05
HB227	PAD .180/.040		£3.05
HB228	PAD .200/.040		£3.05
HB229	PAD .220/.040		£3.05
HB230	PAD .250/.040		£3.05

IC PACK (Dual-in-line)

Pre-printed dense black on .0012 acetate film (125 symbols/pack)

●●●●●●	HB280/B	16 Pin DIL 1:1	£3.20
●●●●●●	HB281/B	16 Pin DIL 2:1	£3.45
●●●●●●	HB284/C	16 Pin DIL 1:1	£3.45
●●●●●●	HB285/C	16 Pin DIL 2:1	£4.00
●●●●●●	HB286/D	16 Pin DIL 1:1	£3.20
●●●●●●	HB287/D	16 Pin DIL 2:1	£3.45

CONNECTORS

Polyester Film-Strips 420mm Long

●●●●●●	HB/324	Conn/D 1:1 (20)	£7.10
●●●●●●	HB/325	Conn/D 2:1 (10)	£7.10
●●●●●●	HB/326	Conn/L 1:1 (10)	£7.10
	HB/327	Conn/M 2:1 (10)	£7.10

ARTWORK ACCESSORIES

HB202	Artwork Film A4 (5)	£1.78
HB/CKGA3	Precision Grid A3 (1)	£7.00
HB/352	Artwork Knife (1)	£1.44
HB/353	Blade (5)	£0.40
HB/354	Blade (5)	£0.50

PLAIN COPPER CLAD PCB

Top Quality FR4 Fibreglass

HB019	S/Sided 3"x4" (3)	£1.26
HB020	S/Sided 6"x4" (2)	£1.68
HB021	S/Sided 6"x9" (1)	£1.89
HB026	D/Sided 6"x4" (2)	£1.92
HB027	D/Sided 6"x9" (1)	£2.16

VEROBOARD

Pre-Pierced Stripboard



HB137 V/	Board 63x 95mm (1)	£1.10
HB138 V/	Board 63x127mm (1)	£1.27
HB140 V/	Board 95x431mm (1)	£5.00

UV EXPOSURE UNIT

PHOTO-RESIST & FOTOTOOL materials require exposure to UV light - the type of light used determines the quality of reproduction - this simple-to-make D.I.Y. kit comes complete with UV lamp, holder, shade etc. and full working instructions to build your own glass contact frame - KIT HB/UV1 D.I.Y. EXP. UNIT £27.00

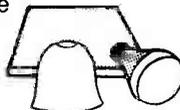


PHOTO-RESIST PCB MATERIALS

Top Quality, Positive Photo-Resist PCB

HB031	Pos S/Sided 3"x4" (3)	£2.29
HB032	Pos S/Sided 6"x4" (2)	£2.73
HB050	Pos S/Sided 6"x9" (1)	£2.79
HB039	Pos D/Sided 3"x4" (3)	£2.86
HB040	Pos D/Sided 6"x4" (2)	£3.43
HB058	Pos D/Sided 9"x6" (1)	£3.49
HB062	Positive Developer (1 lit)	£2.06
HB012	Ferric Etchant (1 lit)	£1.78
HB014	Process Tray (1)	£2.54
HB017	Copper Cleaner (1)	£1.49

FULL PHOTO RESIST KIT

HB/2 Complete Photo Resist Kit £29.00

PHOTO-TOOL MATERIALS

PCB photo masters made to highly professional standards. UV Exposure. High intensity Image. Pos or neg for simplicity of multi-imaging.

HB3	Fototool Kit Complete	£27.00
HB101	Foto pos film 15x20cm (6)	£5.07
HB102	Foto pos film 20x30cm (6)	£8.77
HB105	Foto neg film 15x20cm (6)	£4.10
HB106	Foto neg film 20x30cm (6)	£6.49
HB109	Fototool Developer (1 lit)	£2.90
HB111	Fototool Fixer (1 lit)	£1.89

LABEL & PANEL MATERIALS

Convert Fototool masters into highly professional labels and panels. Simple process - durable finish. Packs include lamination film and Double sided adhesive.


HB114/YELL.	Yellow Fotolam 20x30 (3)	£2.76
HB114/BLUE.	Blue Fotolam 20x30 (3)	£2.76
HB114/BAL.	Brushed Aluminium 20x30 (3)	£5.17

ELECTRONIC PROJECT KITS

A special selection of popular electronic projects from Argus Publications is now available. A wide choice of interest is covered including ★Computing★Music★Hi-fi★Security★Novelty. All kits include PCB, components, case & panels and instructions, and are offered at prices to suit all pockets. SEND TODAY FOR OUR "ELECTRONIC KITS" BROCHURE.

PRINTED CIRCUIT DRILL

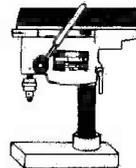COMPACT 2- SPEED PCB DRILLING M/C MAINS POWERED. PRECISION MACHINE FOR PRECISION DRILLING.



HB 187 PCB DRILL £152.00

PCB DRILLS (CARBIDE)

LONG LIFE SOLID CARBIDE FOR PRECISION

HB189	CARBIDE DRILL	0.9mm (1)	£2.02
HB190	CARBIDE DRILL	1.0mm (1)	£2.02
HB191	CARBIDE DRILL	1.1mm (1)	£2.02
HB192	CARBIDE DRILL	1.3mm (1)	£2.02
HB193	CARBIDE DRILL	1.6mm (1)	£3.05
HB194	CARBIDE DRILL	2.0mm (1)	£4.09
HB195	CARBIDE DRILL	3.0mm (1)	£5.22

COMPUTER ADD-ONS

A comprehensive range of add-on Kits ★ROBOTICS★MUSIC★SPEECH★ and many other interesting projects.

COMPUTER LEADS & CABLES

A comprehensive range of Ribbon connectors, cables and connectors is available for most popular computing applications.

Easy add-ons for ZX Spectrum

Explicitly detailed book to build address decoder and 17 electronic add-on projects.

HB/2000 BOOK + DECODER KIT £24.00

QTY	REF	DESCRIPTION	PRICE	TOTAL

Total Inclusive of VAT & Carrage £
Cheque/P.O. enclosed made payable to HOBBYBOARD. ETI/12/4

ACCESS

Name

Address

Please forward the following Catalogues.

- Hobbyboard Electronic Kits
 Computer Add-ons Computer Cables

KELAN ENGINEERING LTD.
Circuit Products & Components Division,
27-29 Leechill Lane - Harrogate,
North Yorkshire HG2 9NJ.
Tel: (0423) 870938.

Discomixer Phonic 6050

- ★ 2 mag deck i/p
- ★ 2 line i/p
- ★ 1 mic i/p
- ★ 7 band graphic
- ★ twin vu meter
- ★ headphone monitor
- ★ mic over ride
- ★ mains operated

£119.98
p&p 2.50



Discomixer Phonic MX7700

- ★ 2 mag deck i/p
- ★ 2 switchable mic/line inputs
- ★ 5 band graphic
- ★ led vu meters
- ★ cross-fade
- ★ separate record output
- ★ mains operated

£109.98
p&p 2.50



Discomixer Phonic SM 501

- ★ Full headphone monitor
- ★ 2 x line i/p
- ★ 2 x mag deck i/p
- ★ 1 x mic i/p
- ★ twin vu meters
- ★ mains operated


£44.98
p&p 2.00



Howland & West MX950 Microphone Mixer

- ★ six mic i/p's
- ★ stereo line i/p
- ★ headphone monitor
- ★ stereo/mono sw
- ★ master fader
- ★ mains operated


£65.98
p&p 2.00

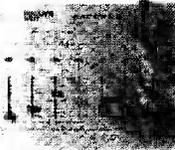

Howland & West MX850 Stereo Graphic Equaliser

- ★ 7 bands/channel
- ★ 12db boost or cut
- ★ tape monitor button
- ★ mains operated

£65.98
p&p 2.00

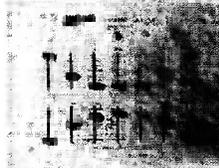

Phonic EQ1005 Stereo Graphic Equaliser

- ★ 5+5 equaliser bands
- ★ led vu meters
- ★ tape monitor
- ★ meter level controls
- ★ connections by phono plugs

£44.98
p&p 2.00



DEI Analog Echo Machine

- ★ BBD echo system
- ★ mic i/p
- ★ line i/p
- ★ foot switch skt
- ★ output attenuator
- ★ peak led
- ★ mains operated

£79.98
p&p 2.50



Stereo 2 & 3 way Electronic Crossovers

- 2 way**
- ★ cross over frequency 500 Hz
 - ★ level control for low and high
 - ★ 19" rack mount

£79.98
p&o £2.00



- 3 way**
- ★ cross over frequency 500Hz+3KHz
 - ★ level controls for BASS, mid & high
 - ★ 19" rack mount

£89.98
p&o £2.00

Echo Microphone

- ★ echo volume control
- ★ echo on/off
- ★ battery operated
- ★ 10ft cable
- ★ vinyl carrying case

£34.98
p&p 2.00



27 Band Mono Graphic Equaliser

- ★ 27 separate sliders
- ★ By-pass switch
- ★ L.E.D. overload indicator
- ★ 15dB Boost or cut
- ★ 19" rack mount
- ★ Low distortion 0.05% TYP

£199.98
p&p 4.00



Cassette Recorder for VIC20/64

- ★ pre set levels
- ★ save led
- ★ simple operation
- ★ plugs direct into VIC20/64
- ★ tape counter

£29.98
p&p 2.00



1,000 Watt Stereo Slave Amp

- ★ 500 watts per channel
- ★ Twin VU meters
- ★ Jack inputs
- ★ Cannon outputs
- ★ 19" rack mount
- ★ cooling fan
- ★ short circuit protection

£399.98
p&o £6.00



250W Power Amp

- ★ 125w per channel into 4ohms
- ★ 20-20khz frequency response
- ★ open & Short circuit proof
- ★ cannon i/p & o/p
- ★ level control for each channel x twin vu metres
- ★ 19" rack mount

£169.98
p&p 5.00



400W MOS-FET Power Amp

- ★ 2 x 200W
- ★ 5Hz to 30KHz + 1 db frequency response
- ★ latest mosfet technology
- ★ twin o/p meters
- ★ fully short circuit proof
- ★ x 19" rack mount.

£234.98
p&p 5.00



700W Power Amp

- 2 x 350W/channel into 4 ohms
- ★ 20Hz to 20KHz frequency response
- ★ cooling fan
- ★ cannon i/p + o/p connectors
- ★ twin vu meters.

£324.98
p&p 5.00



FOR MAIL ORDER

48 Dalston Lane,
London, E8
Tel 01-249 4814
Open 10am to 6pm Mon-Fri
9.30am to 5.30pm Sat


ALL OFFERS ARE SUBJECT TO AVAILABILITY

TRADE ENQUIRIES WELCOME

TAKE ADVANTAGE
OF THE HY-TEK
PRICE POLICY

THE MUSIC MAKERS

TECH TIPS

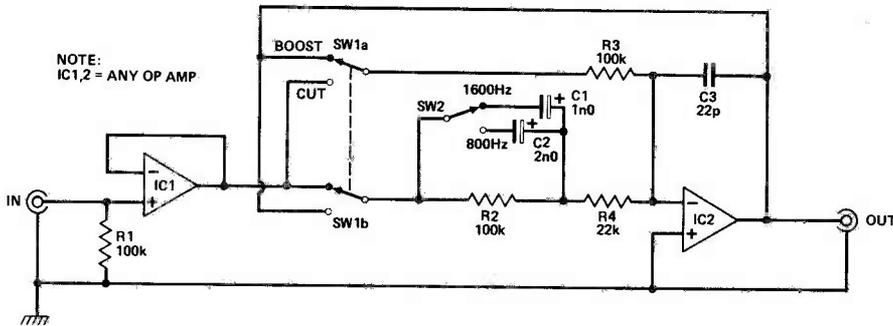

Tape Noise Reducer

W. Wirth
Sri Lanka

Amateur-made multi-track recordings often suffer from tape noise caused by the accumulated noise floors of individual tracks and multiple generations of tape to tape

transfers. Encode/decode units like Dolby and dbx are effective but are costly and critical in alignment and use. Playback only noise reducers are also sensitive to alignment errors and have side effects such as "breathing".

This simple circuit uses the principle of pre- and de-emphasis to obtain its noise reduction. The treble frequencies are boosted during recording and given a complementary cut on playback so that the

signal remains flat but high frequency noise is reduced by 8–10 dB.

IC1 is a high impedance buffer which prevents loading of the input and interaction with the reactive components R2, 3, 4 and C1, 2 which are configured around IC2. Switch SW1a, b selects either the boost or cut mode. SW2 chooses a turnover frequency of 800 or 1600 Hz.

Fixed frequency/amplitude units such as this work best on signals with restricted high frequency content like bass, acoustic guitar and vocal tracks. The greatest noise reduction (10 dB @ 10 kHz) can be obtained with these signals using a turnover of 800 Hz. Drum, synth, and similar high frequency content signals can be processed but it would be best to use the 1600 Hz turnover and set the recording level conservatively.

C3 reduces gain at very high frequencies to help avoid saturation. Its presence in both boost and cut modes causes a tracking error resulting in a 3 dB loss at 20 kHz. This was felt to be insignificant. Although any op-amp can be used, best results are obtained from low noise devices; an RC4136 is a good choice for a two channel unit.


Quiz Machine

G. J. Phillips
Durham

The circuit shown has been designed for use in a quiz where each contestant has a button and the first person to press causes his light to illuminate, thereby cueing the question master. The circuit can be used for any number of buttons from two to ten. The design features automatic reset after a preset time delay so that no intervention is required by the question master.

IC1 (pins 1 to 6) is connected as an astable multivibrator which feeds the clock input of a decade counter IC2. As the counter cycles, each of its outputs Q0, Q1, etc goes to logic 1 in turn.

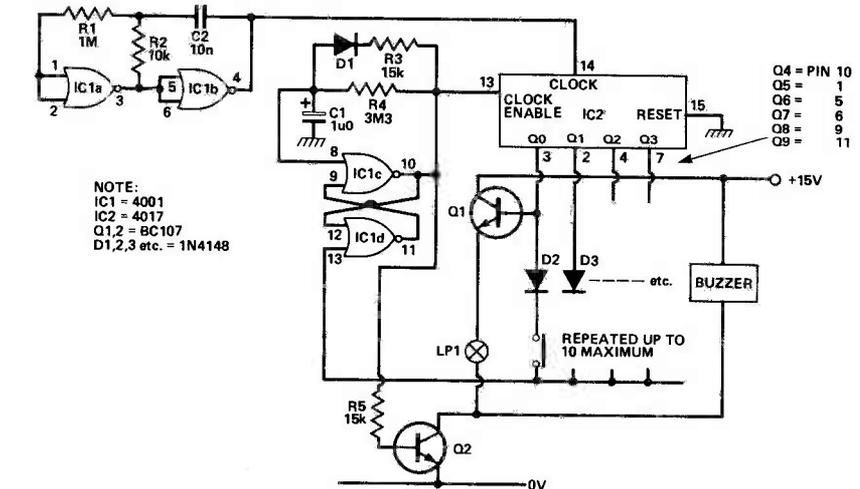When a contestant presses his button, the bistable formed by IC1 (pins 8–13) is reset thereby inhibiting the clock of IC2 and effectively freezing the counter at the Q output associated with the button pressed. For example if button PB1 is pressed, the counter freezes at Q0 causing Q2 to turn on. Q1 is turned on also irrespective of which button is pressed. Lamp LP1 is therefore lit



indicating that PB1 has been pressed. LP1 remains lit for a time period set by C1, R4 (approx. 3 seconds) after which the bistable is set via pin 8. Lamp LP1 is then extinguished and the circuit is ready for another round.

The cyclic nature of IC2 ensures that two or more lamps can never be lit simultaneously. It may be argued that the circuit is unfair in that if the counter has just cycled past Q0 and

PB1 is pressed before say PB3, then PB3 will win even though it was pressed later. In practice, however, the counter is cycling very fast and the "who pressed 1st" judgement is made in a fraction of a millisecond, many times faster than human judgement can be made.

A buzzer is connected between the collector of Q1 and the +15V rail to give audible indication that a button has been pressed.


Shunt Regulated Spectrum Power Supply

A. S. Hughes
Holywell

The Sinclair Spectrum power supply unit has an unregulated output which is capable of operating both the computer and the Sinclair printer. Consequently, when it is used to power the computer alone, the supply voltage can rise to well above 9 volts. A friend of mine has 12 volts supplied to his 16K model.

Since the computer takes about 0.8 A, the internal 5 V regulator has to dissipate $(12 - 5) \times 0.8 = 5.6$ watts. This, together with high ambient temperatures causes the computer to become very warm. This shunt regulator circuit, when interposed between supply and computer, will reduce the Spectrum working temperature.

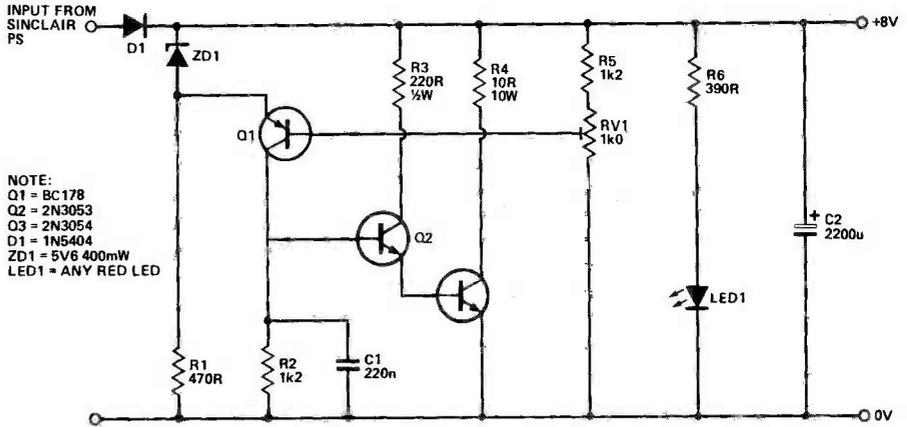As we all know, the 5 volt regulator is perfectly happy with an input voltage of 8 volts. I have also learnt that the printer does not object to 8 volts either. It therefore makes sense to supply the spectrum with 8 volts to achieve the lowest possible operating temperature.



NOTE:
Q1 = BC178
Q2 = 2N3053
Q3 = 2N3054
D1 = 1N5404
ZD1 = 5V6, 400mW
LED1 = ANY RED LED

The advantage of shunt regulation, as opposed to the more usual series regulation, is that there is no significant voltage drop across the supply circuit in series with the computer. Therefore, on full load, when there is no voltage to spare, this circuit can cope.


Q1 emitter is clamped at 5.6 volts below the positive supply rail. The base of Q1 goes to the potential divider formed by R5 and RV1. If the supply voltage should rise, the bias to Q1 increases, causing Q2 collector current to rise, which in turn increases Q3 collector current. The large current taken by Q3 tends to keep the supply voltage down. If the load current should increase, Q3

reduces its collector current to compensate.

D1 drops 0.8 volts thereby ensuring that the Sinclair supply unit is not overloaded. R4 reduces the dissipation in Q3 to less than 3 watts. If the unit is left switched on with no load connected the power dissipated in R4 will be about 8 watts.

I took the opportunity to include a few luxuries in this circuit, such as the power on indicator (LED1) and extra smoothing capacitor C2.

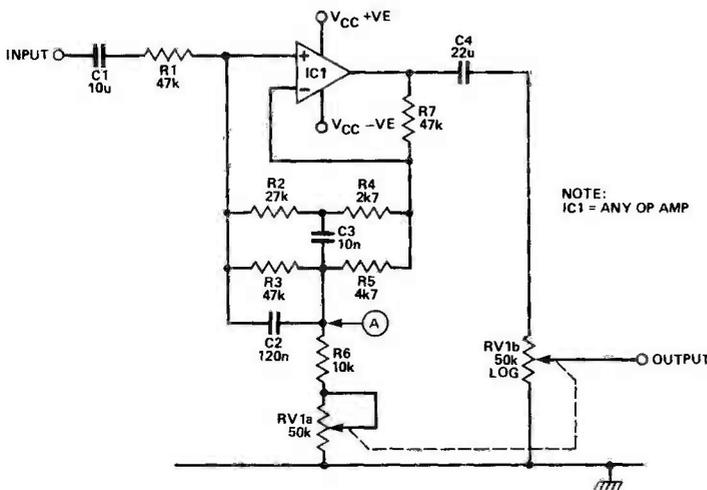To set up the circuit, connect the output to an 8 ohm 10 watt power resistor (4 R7 and 3 R3 in series) and adjust RV1 for an output of 8.2 volts.



NOTE:
IC1 = ANY OP AMP

Loudness Control

R. Leach
Reading

Most audio amplifiers equipped with a loudness control employ a tapped volume control to allow bass

and treble boost at low volume settings. This is intended to account for the non-linearity of the ear at these levels.

The circuit shown allows the same effect to be obtained using only an ordinary 50K dual-gang potentiometer. A four-gang potentiometer would be required for

stereo operation (Circuit supply one) or alternatively two dual-gang ones could be used, one for each channel.

The IC could be a 741 or any similar device but for best results a high quality op-amp such as the TL071 is preferable. The gain of the circuit is effectively unity at 1kHz but approximately 10 dB bass boost is provided at 100Hz and high frequency attenuation in the feedback loop gives approximately 5 dB gain at 10kHz. As the setting of volume control RV1b is increased, so also is that of RV1a which reduces the effects of the frequency selective networks around the op-amp. At maximum volume the amplifier frequency response is flat over the audio spectrum.

The unit could be arranged so that it might be switched in and out, either by re-routing the signal path or by inserting a switch at point A. This would isolate the frequency selective networks from ground and leave the IC functioning as a unity-gain amplifier with a flat frequency response.

Memory Map Simplification

P.M. Buckley
Leeds

Although very simple, this idea speeds up I/O processing and shortens machine code programs considerably.

In microsystems using the 6821, selection of the internal registers in the PIA is usually achieved by attaching A0 & A1 of the address bus to RS0 & RS1 on the 6821. This gives the memory map shown in Table 1.

A1	A0	REGISTER SELECTED
0	0	DDRA AND I/O REGISTER A
0	1	CONTROL REGISTER A
1	0	DDRB AND I/O REGISTER B
1	1	CONTROL REGISTER B


Table 1

This is awkward as the I/O registers are two bytes apart, which means 16 bit registers such as the index register in the 6800 cannot be used to read and write to the I/O ports. Instead two eight bit operations have to be used.

By simply swapping over the connections to RS0 and RS1 the memory map changes to that shown in Table 2.

A1	A0	REGISTER SELECTED
0	0	DDRA AND I/O REGISTER A
0	1	DDRB AND I/O REGISTER B
1	0	CONTROL REGISTER A
1	1	CONTROL REGISTER B

Table 2

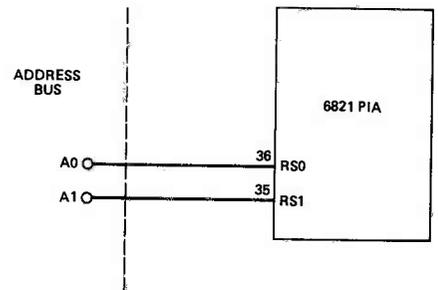

Square/Triangle Generator with Variable Mark/Space Ratio

P. J. Thompson
Lancashire

The problem with most methods of obtaining a variable mark/space ratio from normal astable circuits is the tendency of the ratio to alter with frequency and vice-versa. With this circuit both adjustments can be made independently of the other. It also produces constant amplitude outputs.

IC1a, IC1b and associated components form a fast (non-saturating) Schmitt trigger. Trigger voltage is set by the current, to virtual earth, through R2 multiplied by the input resistance RV2a and R8.

The potentiometer RV1, IC1c, C1 and associated components control the mark-space ration. The rate at which C1 charges is controlled by the resistance between the output of the Schmitt (IC1b) and the virtual earth of IC1c. Hence over one cycle the average value of resistance equals $(RV1/2) + R7$ eliminating the effect of this control on the frequency.

When the output of IC1c rises to the positive trigger voltage IC1b's output switches to a positive value determined by R3 and R4, thus the output of IC1c starts to fall as it discharges C1. Upon reaching the negative trigger voltage IC1b switches to its negative value (R5 and R6) so IC1c's output starts to rise, and the cycle is repeated.



The frequency is controlled by

RV2a, which determines the trigger voltages and hence the time taken to charge (discharge) C1. (Large RV1a = Large trigger voltages = Long times = Low frequency).

The triangle (ramp) waveform is derived from the output of IC1c. However, as the amplitude at this point is determined by the trigger voltages, use is made of a dual-ganged potentiometer. The first side (RV2a) controls the frequency, and the second (RV2b) corrects the triangle amplitude; the peak input

current to the Schmitt trigger equals the current through R2, (a constant) and as RV2a should equal RV2b the peak current into IC1d's virtual earth is constant, and therefore so is the output amplitude. As $R2 = R10$ the square and triangle amplitudes are the same.

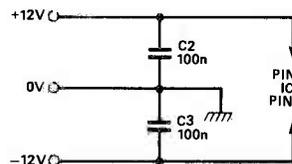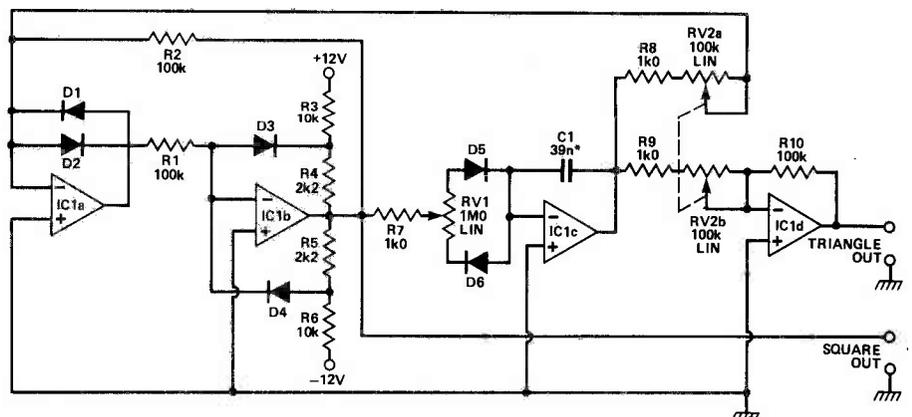It is recommended that FET input op-amps are used because of their superior slew-rate; a poor slew-rate would degrade the high frequency performance and cause the mark-space to alter the frequency.



NOTE:
IC1 = TL074
D1-6 = 1N4148
*C1 = 390n for 2Hz-200Hz
= 39n for 20Hz-2kHz
= 3n9 for 200Hz-20kHz

$$\begin{aligned}
 \text{Square wave amplitude} &= \pm \left(R4 \left[\frac{V+0.7}{R3} \right] + 0.7 \right) \text{ Volts} \\
 \text{Frequency} &= \frac{(V_{IC1b} - 0.7) R7}{2 \cdot V_{IC1b} (RV2a + R8) C1 \left(\frac{RV1 + R7}{2} \right)} \text{ Hz} \\
 &= \text{approx } \frac{0.08}{(RV2a + R8) C1} \text{ Hz}
 \end{aligned}$$


Simple ZX80/81 Tape Mod.

S. Beet
West Kirby


The recently published ZX80/81 tape mods are both simple and cheap, but I have used an even simpler, and completely free, modification for several months without any problems.

Most of the problems associated with saving programs on cassette, are due to mains-induced hum in the connecting leads. The ETI mods overcome this by increasing the signal level so that the mains hum becomes less significant. However, by transferring the 1 kΩ resistor from across the output of the ZX80/81 to the input of the tape recorder, the hum is still attenuated by a similar amount but, since the mains hum is

ORIGINAL SINCLAIR CONFIGURATION

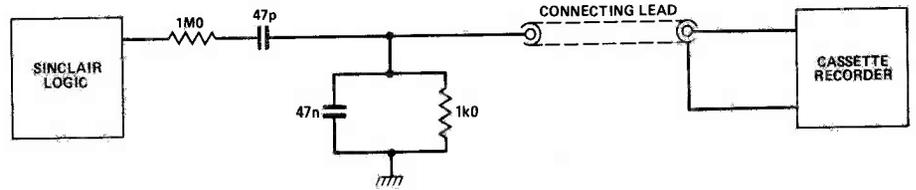

REVISED ARRANGEMENT TO AVOID HUM PICKUP

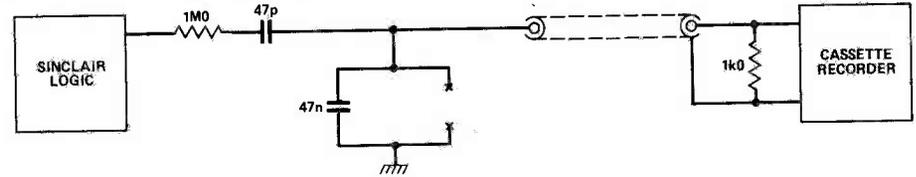

much smaller than the 5V logic level, the input signal-to-hum ratio becomes very large and reliable data transfer is much more likely.

Ideally the 47 nF capacitor should also be removed, but its impedance

at 50Hz is negligible so this is not usually necessary.


The resistor can either be placed inside the cassette recorder or in the plug at the cassette end of the lead.

Signal/Peak Indicator

R.M. Bland
Rugby

This circuit was designed as a cheaper version of the normal LED bargraph type VU meters and uses only two LEDs. The green one is a "signal present" indicator which starts to glow with an input signal of about -30dBm and glows progressively brighter with increasing input signal. At around 0dBm the red "peak" indicator switches on.

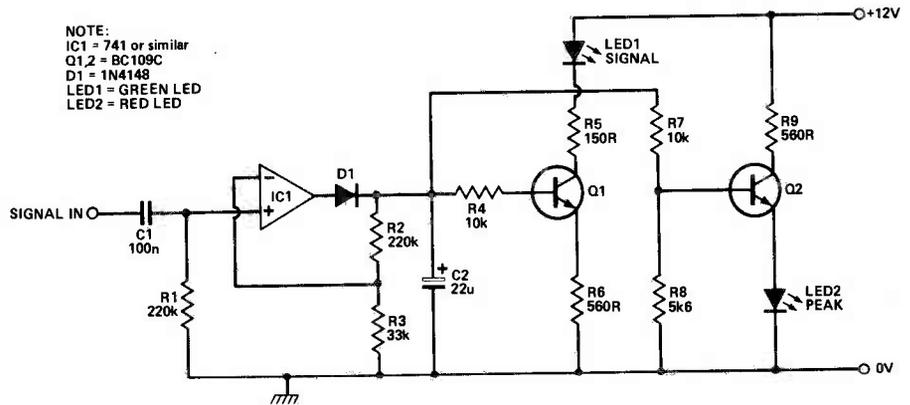The input is AC coupled into 220k ohms to avoid loading the signal source. The op-amp is any standard 741 type (non-latching),



NOTE:
IC1 = 741 or similar
Q1,2 = BC109C
D1 = 1N4148
LED1 = GREEN LED
LED2 = RED LED

and functions as a half-wave rectifier with a gain of about 7. The signal is then smoothed by C2. Q1 functions as a voltage controlled current sink


and controls the brightness of LED1. Q2 operates in the switching mode and switches on LED2 when its base reaches about 2V.

CMOS Monostables


P. Harding
Exeter

The circuits presented here are a further variation on the basic CMOS monostable design; the NOR type is reset by a positive pulse and, the NAND type by a negative pulse. Hence the reset pulse polarity matches that of the trigger pulse.

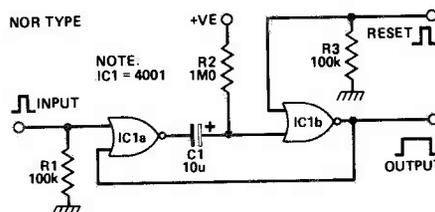Circuit operation is simple. Taking the reset input of the NOR version high forces IC1 b's output low, removing the feedback to IC1 a. The original trigger signal must have



NOTE:
IC1 = 4001

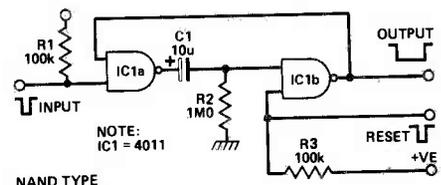

NOTE:
IC1 = 4011

been removed before the monostable can be reset. Operation of the NAND version is similar to that of the NOR type, but with reversed logic polarity.

With the values shown, the circuit has a period of about 6s, although component tolerances (in


C1) will have a large effect on the actual period. Care must be taken when using high values of R2 with an electrolytic for C1; leakage currents may prevent the capacitor charging to the CMOS high threshold so that the monostable never times out.

Micropower 5 Volt Regulator

B. Hunter
Dundee

The voltage regulator shown here was designed to supply a CMOS microprocessor data logger which had to run for several days from Ni-Cad cells without recharging. An ordinary low power voltage regulator such as a 78L05 consumes several milliamps and in a circuit with a very low quiescent current would contribute quite significantly to the battery drain. The regulator shown here requires a little over 100µA, giving a considerable saving in battery current. The common or garden low power regulator also requires an input voltage about 2 volts above the output voltage; the design given here will work with an input only 0.5 volts higher than the output voltage so fewer cells can be used to power the circuit.

The 9491 is a bandgap voltage

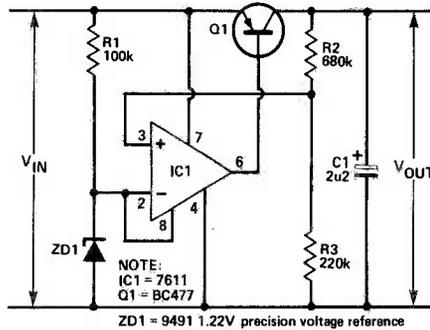

reference which gives a very stable 1.22V and can operate from a current as low as 50µA. This reference voltage is fed to the inverting input of a CMOS op-amp where it is compared with a fraction of the output voltage. The output of the op-amp drives the base of the BC477 and this transistor increases the output current of the amplifier.

If the output voltage starts to decrease due to increased load, then the fraction of V_{out} on the non-inverting input of the op-amp decreases. This causes the output voltage of the op-amp to fall and

thus turn the PNP transistor on more to compensate for the increased load.

Pin 8 of the op-amp sets the quiescent current of the device to one of three values. If it is connected to $v+$ then the quiescent current is 10µA, if connected to $v-$ the quiescent current is 1 mA, and if connected to a voltage between $v- + 0.8V$ and $v+ - 0.8V$, then the quiescent current is 100µA. Thus connecting pin 8 to the reference voltage gives a quiescent current of 100µA. The capacitor across the output prevents any oscillation of the circuit.

Using the component values given, the circuit performs as follows.

For $V_{out} = 5.06$ volts:-

V_{in} minimum = 5.27 volts with 10mA load

V_{in} minimum = 5.57 volts with 40mA load

No load current = 112µA

Desoldering Tool Improvement

S.S. Norman
Sunbury-on-Thames

The following idea is a method of making de-soldering tool nozzles last forever.


If a neoprene sleeve (RS Components Part No. 399-729) is fitted over the nozzle as shown, with the sleeve protruding about an eighth of an inch over the end, it can be seen that the nozzle will never get hot enough to melt and eventually wear out. The sleeve also improves the efficiency of the tool by forming a

seal over the iron and joint to be desoldered, which results in more solder being removed in one operation.

When the end of the sleeve gets worn it can either be turned around or cut back, so a single sleeve can be used at least two or three times.

The price for one sleeve is about one hundredth of the cost of a new PTFE nozzle, thus the use of the sleeves can produce quite a saving where these tools are used frequently and in large numbers.

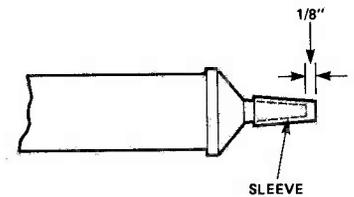If it proves difficult getting the sleeve on, a tiny amount of sleeving lubricant (RS Part No. 544-077) can be used to ease it on.




Note: RS Components will only supply trade and professional customers. If you are unable to use them because of this and can find no other source of neoprene sleeving, Crewe-Allan & Company of 51, Scrutton Street, London EC2 will order the RS parts you need for a small extra handling charge.

Reducing Relay Power Consumption

S.T. Jones
Solihull

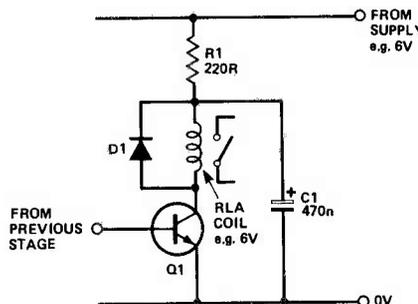Most relays need much more current to 'pull-in' than to stay closed. For example, a six-volt relay may need 80mA to pull-in but only 20mA to stay closed, so the extra



60mA is wasted current. In the circuit shown, current consumption is

reduced by limiting the current drawn to 20mA with a suitable resistor. Normally this would prevent the relay closing at switch-on, but capacitor C1 charges to the supply voltage when the relay is off and discharges to provide a high current at switch-on. When the switching transistor turns on, this current pulse is sufficient to close the relay. D1 provides the usual back-EMF protection and can be almost any general-purpose type. C1 is electrolytic and should be of 200u or more.

ADSR For Electronic Organ

C.A. Van Latum
Rotterdam


While constructing an organ based on the SGS-Ates M108 organ chip, I found the normally used ADSR circuits far too expensive to construct.

The ADSR-unit described below incorporates all the normal ADSR functions and is very cheap and simple. The whole circuit is based on one op-amp wired as a comparator.

The trigger outputs of the M108 are first inverted and buffered (not included in the circuit diagram as one inverter-buffer circuit can be used to trigger all ADSR-blocks). As a key is pressed TDS will become high for about 9ms. The output of the comparator IC1 will turn high and capacitor C1 will be charged at a rate determined by R4/RV2 (attack). When C1 has reached a voltage

$V = V_{\text{supply}} \cdot R1 / (R1 + R3)$
the comparator output will turn low. C1 will then be discharged via R5/RV4 (decay) to a level determined by RV3 (sustain level).

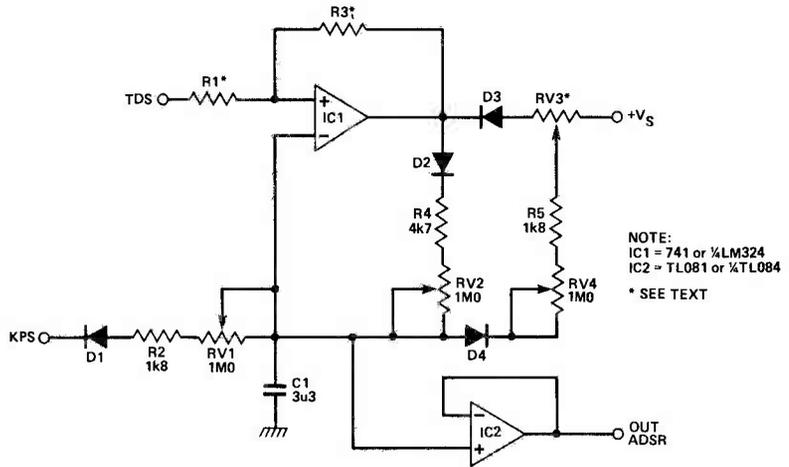All this assumes that the key is still pressed, so KPS is high. As the key is released KPS will turn low and C1 will discharge via R2/RV1 (release). As C1 must not be given the chance to discharge via the output op-amp a high input resistance device must be used, for example a TL081. Note that IC1 must not be an open-drain output op-amp.



NOTE:
IC1 = 741 or ¼LM324
IC2 = TL081 or ¼TL084
* SEE TEXT

As quad op-amp ICs can be used, four independent ADSR units can be constructed with just two ICs. The connections to the control panel can be made very easily as only four wires are required per unit!

The necessary equations to calculate the component values are:


$$V_{\text{max.out}} = V_{\text{supply}} \cdot R1 / (R1 + R3) \\ = x \cdot V_{\text{supply}}$$

$$\text{Attack time } t_a = R \cdot C \cdot \ln(x)$$

$$\text{Sustain level } V_s = P \cdot V_{\text{supply}} / 20 \\ \text{where } P = \text{fraction of RV3} \\ (0-10)$$

$$\text{Decay time } t_d = 2,3 \cdot R \cdot C \text{ where } R \\ \text{is } R5 + RV4 + R_p \text{ (voltage divider res.)}$$
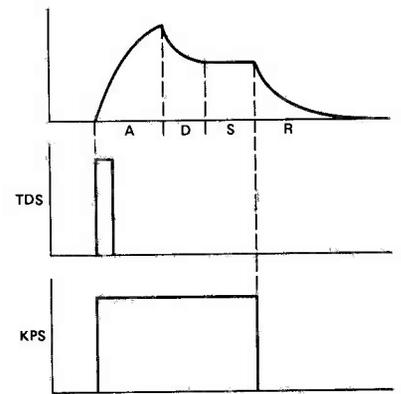
$$\text{Release time } t_r = 2,3 \cdot R \cdot C \\ \text{Voltage divider resistance } R_p \\ = 100 \cdot P \cdot (20 - P) / 20$$




The timing component values chosen give the following periods:-
 $t_a = 0,01$ to 2 Sec.
 $t_d = 0,01$ to 5 Sec.
 $t_r = 0,01$ to 7 Sec.
Note that the decay time varies with the sustain level but this was found to be quite acceptable.

Remote Noise Alarm

S. Huckstepp
Colchester

This alarm allows a microphone to be placed at a great distance from the alarm and power supply circuitry yet includes a preamp at the microphone end to reduce noise pickup along the line and uses only two wires.

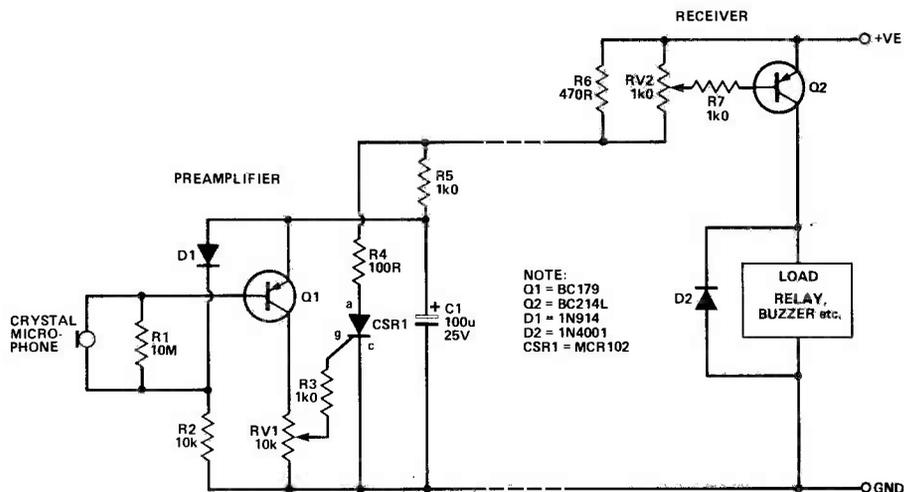Q1 amplifies the voltage induced in the microphone while D1 provides a reference voltage 0.6V less than the supply to overcome the transistor's base-emitter voltage drop. When the level of the amplified signal tapped off by RV1 exceeds the thyristor gate threshold, CSR1 conducts and increases the current consumed by this part of the circuit. C1 and R1 provide a



delay to prevent CSR1 triggering at switch-on.

The voltage at the bottom end of R6/RV2 is usually less than 0.6V


below the supply voltage, but when CSR1 conducts this is pulled down and Q2 conducts. RV2 is adjusted to ensure that Q2 saturates.

TTL Clock Delay


Phil Walker

Some circuits require non-overlapping clocks for their operation, notably the 6500 series microprocessors and certain audio delay lines. It is not always easy to obtain this type of waveform without special chips so this circuit was devised using TTL gates as delay devices. The original circuit was intended to reconstruct the ϕ_1 and ϕ_2 from a 6502 based micro when only the ϕ_2 signal was available at the connector interface.

As shown the circuit will give a period of about 50 to 80ns from the time one output goes to 0V until the other goes to the high level. Omitting IC1b and c will shorten the time while inserting the spare section of IC2 between IC1b and c will lengthen it. The operation of the circuit is not dependent on the input clock frequency but the rise and fall times should be better than 10ns if possible. If this is a problem, use the spare section of IC1 to sharpen the input signal (74LS14 preferred) and swap the designations of the outputs. This will add a gate delay to the reconstructed signals.

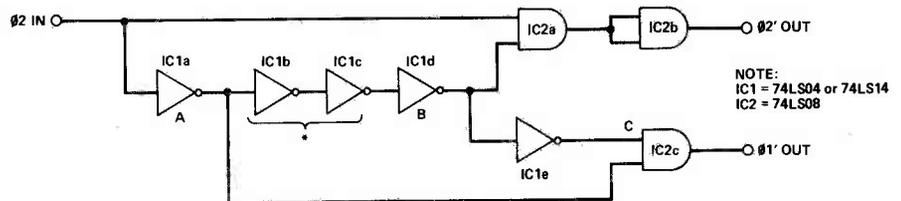

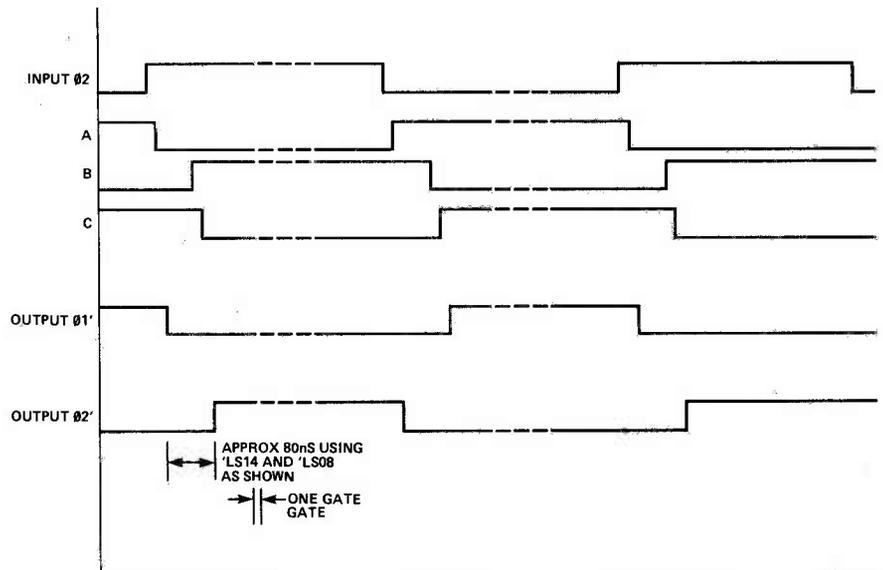*OMIT OR REPLACE WITH 1 SECTION OF 'LS08 FOR SHORTER ϕ_1 DELAY. INSERT SPARE SECTION OF 'LS08 BETWEEN INVERTERS FOR LONGER DELAY




Automatic Car Alarm

G. Landry
Natal, S.A.

The problem with most car-burglar alarms is that one tends to forget to activate them. This little circuit does so automatically.

Upon switching the ignition off, Q1 turns off and C1 starts discharging through R2. This maintains the output level of the OR gate (D2, D3, R4) high. During this discharge period (set at two minutes by the values of R2 and C1) the driver can leave his car without setting the alarm off. However, after this period, the voltage across C2 is lower than the Schmitt NAND gate IC1a threshold. If an intruder opens a door, the OR gate goes low and the monostable around IC1a, IC1b is turned on. This in turn switches on Q2 which operates the relay for a period depending on C2 and R6 (set for 1 minute).

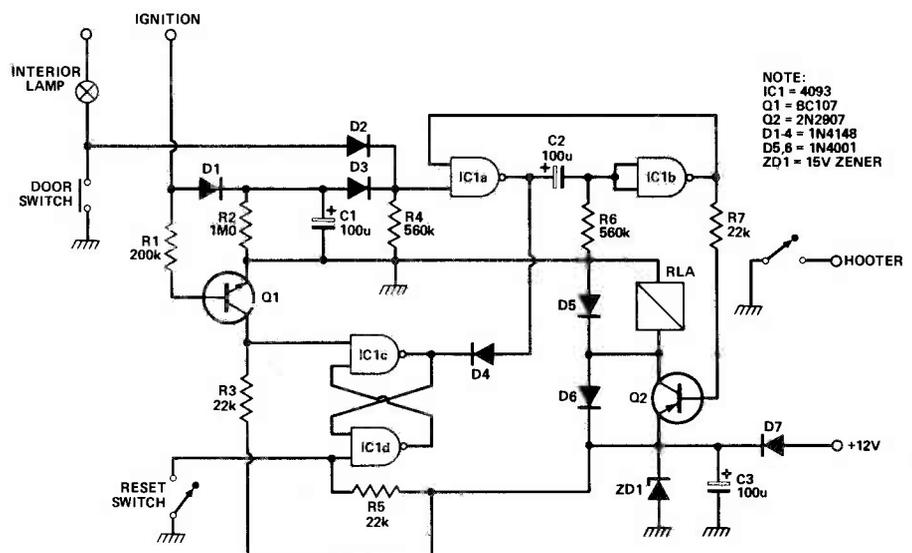The only way to disable the alarm is to operate the external switch (a



magnetic switch was used in the prototype). This causes the NAND latch around IC1c and IC1d to set, putting an earth on D4 which will reset the monostable. The car can now be entered without fear of sett-

ing the alarm off as the NAND latch will only reset when the ignition is turned on again. The circuit is protected against transients by D7, C3 and ZD1 and consumes about 20 μ A when on standby.


'A' Weighting Filter

**B. Porter
Kings Lynn**

The 'A' weighting is used to compensate for the unevenness in the average human hearing. Human beings are, for the most part, much more sensitive to middle range frequencies than to either extremely low or extremely high frequencies.

This circuit will match the official 'A'-weighting curve very closely indeed and can be used in conjunction with an audio millivoltmeter to give an indication of the apparent loudness of a signal.

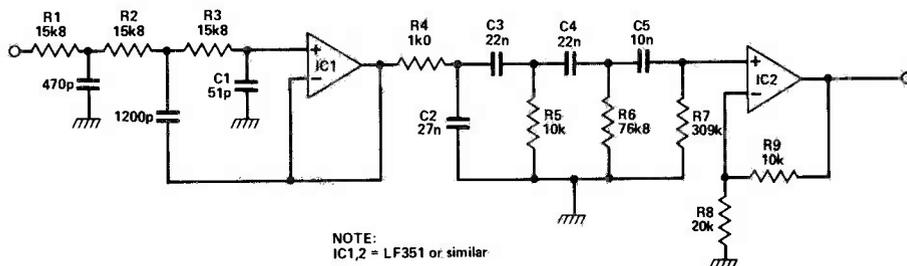The resistor values given are for 1% types but if accuracy is not too



NOTE:
IC1,2 = LF351 or similar

important you can use 5% types and select the nearest available value. If you do use 1% types you may find it necessary to do a little substitution. A 15k and an 820R in series will prove an acceptable substitute for the 15k, an 82k and a 1M2 in

parallel can be used instead of the 76k, and a 330k and a 4M7 in parallel can be substituted for the 309k. A 47p capacitor and a 4p7 in parallel will prove a sufficiently close approximation to the 51p specified.

Ultra Low Cost Light-Pen

**G. Parker
London**


This light-pen is intended for use with a ZX Spectrum and is the cheapest, simplest design you're ever likely to find: it does not even need an edge connector.

The unit (which can easily be housed inside an opaque biro case) is connected to the EAR socket and the +9V line. The latter can be obtained by either soldering a wire to the 9V socket inside the computer or adding an extra socket and plug to the power supply line.

The advantage of using the EAR socket is, aside from cutting out the expense of an edge-connector, that no address decoding or data isolating is needed. You can put pulses on the Ear socket and unless the computer is performing that particular IN command it will ignore them with no damage to the circuitry.

To see what state the pen is in, an IN84 command should be used.

Photo-transistor Q1 is a BC109, the top of which has been cut off with a pair of stout scissors. It has a high dark impedance and in the dark transistor switch Q2 will be off and when PB1 is pushed no current will flow. In the light, the transistor Q2 will switch on, allowing a positive voltage to flow through PB1. The

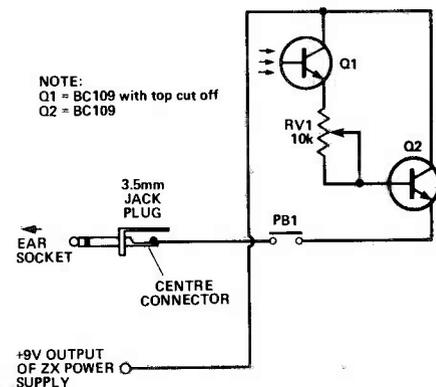

amount of light required for switch-on can be adjusted by RV1 to suit different colours on the screen.

Casio fx-180P Resistor Decoder

**R. Hutchison
West Kilbride**

This program is designed to convert resistor colour codes to their correct numerical value. It works with both four and five band resistors, and, although designed for use with the fx-180P, should be easily adaptable to suit most other programmable calculators.

The program listing is as shown in Table 1. In order to make the best use of this system, part of the keyboard has to be colour coded. The easiest way to do this is to make a colour template to fit around the 0-9, √, and +/− keys. This is really quite straightforward if drawn out on 1mm squared paper. Once you have got the template to fit correc-

tly, it is a good idea to sandwich it between two layers of clear Fablon. The colour coding for the template is given in table 2. A 2mm wide coloured band around each key is very effective.

Use of the system is as follows. Firstly load the program into the machine, then fit the template. Enter the colours of the first two (or three) bands; press RUN: enter the colours of the third (or fourth) band; press RUN. The calculator will now display the value of the resistor in engineering notation, i.e. 10^3 (kΩ); 10^6 (MΩ); etc.

Examples:
green-blue-red-yellow: display shows 5.62×10^6 , i.e. 5.62 MΩ.
yellow-violet-gold: display shows 4.7×10^0 , i.e. 4.7 Ω.

Note that it is necessary to press both gold or silver coloured keys when a gold or silver band is encountered.

ENG
ENT 47
x
1
EXP
ENT 3
=
INV RTN.

Table 1. Program Listing

Key	Colour
0	Black
1	Brown/Gold
2	Red/Silver
3	Orange
4	Yellow
5	Green
6	Blue
7	Violet
8	Grey
9	White
+/-	Gold/Silver

Note that the √ key is included in the template even though it is not used in this program.

Table 2. Template Colouring **ETI**

AMPLIFICATION

CHOOSE CRIMSON. THE NAME THAT MEANS QUALITY

Before buying elsewhere check out the features of CRIMSON quality:-

ALL OUR MODULES:-

- superior p.c.b., component identification, solder resist.
- non-potted so non-disposable if damaged.
- metal film resistors.
- negligible noise and distortions.

OUR BIPOLAR POWER AMP MODULES:-


- fuseless electronic shut-down with re-set facility.
- reverse polarity protection.
- high output current capability (>25 Amps on CE1704).
- 18 transistors, 7 diodes.

OUR MOSFET POWER MODULES:- (FE908, FE1704)

- reponse down to d.c.
- j-fet inputs.
- common source output for highest efficiency.

OUR CPR2 PREAMPLIFIER

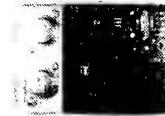- ultimate sound quality.
- 42 semiconductors and perfect symmetry topology.
- anti-thump circuitry.
- selected passive components.



NEW PRODUCT: FET3 POWER MODULE UP TO 450W. 900W BRIDGED MODE. 100V R.M.S. BRIDGE. £74.50

Examples from our range of built, tested and guaranteed modules.

Module	Power/Load	Price Inc. VAT & Delivery
CE608	60W/8R	£21.00
CE1004	100W/4R	£24.50
CE1008	100W/8R	£27.50
CE1704	170W/4R	£35.00
CE1708	170W/8R	£35.00
FE908	120W/8R	£29.50
FE1704	240W/4R	£52.00
CE3004	300W/4R	£49.00
BO1	BRIDGER	£8.20
CPR2	PREAMP	£47.95

Write or phone for details:-

CRIMSON ELEKTRIK STOKE,
Phoenix Works, 500 King St.,
Longton,
Stoke-on-Trent ST2 1EZ.
Tel: 0782 330520


or contact our agents:-

BRADLEY-MARSHALL,
325 Edgeware Road, London
and (especially for demonstrations):-
WILMSLOW AUDIO,
35-39 Church St, Wilmslow, Cheshire.

Interak 1

A METAL Z80A COMPUTER

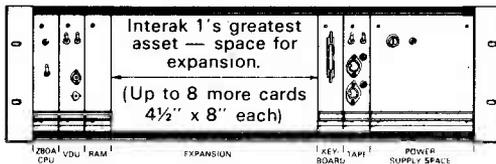Colleges, Universities, Individuals: Build your own modular Z80A-based metal 19" rack and card Interak computer. Uses commonly available chips — not a single ULA in sight (and proud of it). If you can get your own parts (but we can supply if you can't) all you need from us are the bare p.c.b.s and the manuals.



(P.c.b.s range in price from £10.95 to £17.75 + VAT; manuals £1 - £5.)

The Interaktion User Group has 14K BASIC, Assembler, Fig Forth, Disassembler, Debug, Chess and a Book Library, Newsletters etc. No fears about this one going obsolete — now in its fifth successful year! Send us your name and address with a 21 p stamp and we'll send you 40 pages of details (forget the stamp if you can't afford it!) You've already got a plastic computer for playing games, now build a metal one to do some real work: Interak, Interak, Interak!

Greenbank

Greenbank Electronics (Dept T12E), 92 Chester Road,
New Ferry, Wirral, Merseyside L62 5AG
Telephone: 051-645 3391

FREE CAREER BOOKLET

Train for success, for a better job, better pay

Enjoy all the advantages of an ICS Diploma Course, training you ready for a new, higher paid, more exciting career.

Learn in your own home, in your own time, at your own pace, through ICS home study, used by over 8 million already!

Look at the wide range of opportunities awaiting you. Whatever your interest or skill, there's an ICS Diploma Course there for you to use.

Send for your **FREE CAREER BOOKLET** today—at no cost or obligation at all.

TICK THE FREE BOOKLET YOU WANT AND POST TODAY

ELECTRONICS ENGINEERING

TV & AUDIO SERVICING

ELECTRICAL ENGINEERING

RUNNING YOUR OWN BUSINESS

Name

Address

ICS
Division of National Education Corporation

DEPT EBSC4
ICS School of Electronics
160 Stewarts Road
London SW8 4UJ



01 622 9911
(all hours)

ELECTRONIC SIREN KIT

Produces an extremely loud piercing sweet frequency tone from a 9-15V supply. Enable input for easy connection to alarm circuits. Includes 5in. Horn Speaker.

£7.90


Mini Siren

As above, but with a small speaker (instead of horn speaker) for internal use.

£4.30

SECURITY PRODUCTS

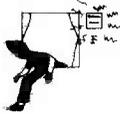Protect your home and property and save by building your own burglar alarm system.



- Stair Mat 23 x 7 in (950 120) £1.70
- Floor Mat 29 x 16 in (950 125) £2.60
- Tamper-proof connecting block (950 110) £0.30
- Door/Window Contacts. Flush mounting, 4 wire, Magnet/switch Per Pair. (950 140) £1.05
- Window Tape 0.5" wide, 50m (950 145) £2.50
- Window Tape Terminations Per pair. (950 150) £0.36
- Key-operated Switch. 1.5A/250V (350 128) £4.50
- SPST Heavy chrome metal. (950 160) £26.00
- Passive Infra-Red Detector Detects intruder's body heat. Range 10 metres. 12V DC, n/o & n/c contact. Size: 4 x 2 x 2 ins. (950 135) £45.00
- Alarm Control Unit. 4 input circuits, 2-instant and 2-delayed. Adjustable entry, exit and alarm times. Built and tested. Full instructions supplied. Size: 180 x 130 x 30mm. Supply: 12V DC. (950 160) £26.00
- Ultrasonic Burglar Alarm. Self-contained mains or battery powered unit complete with horn and AC adaptor. £45.00 + p&hp £2.20
- 8W Horn Speaker. 5.5 ins. 8 ohm. Ideal for sirens, etc. 2.5m lead and 3.5mm jack plug. (403 148) £6.15

IR GARAGE DOOR CONTROLLER KIT

For controlling motorised garage doors and switching garage and drive lights on/off up to a range of 40ft.



Lots of applications like controlling lights and TVs,

etc., in the home. Ideal for aged or disabled persons, this coded kit comprises of a mains-powered infra-red receiver with a normally open relay output plus two latched transistor outputs, battery-powered transmitter and opto-isolated solid state mains switch.

- XK103 £25.00
- XK105 Extra transmitters £10.50

PANTEC KITS

- PN2 FM Micro Transmitter £7.50
- PN3 Stabilised Power Supply £13.70
- PN5 2 x 10w Stereo Amplifier £14.50
- PN6 2 x 40w Stereo Amplifier £24.95
- PN7 Pushbutton Stereo Preamp £12.80
- PN8 Tone & Volume Control £13.60
- PN11 3w FM Transmitter £11.95
- PN13 Single Channel FM Transmitter £9.80
- PN14 Receiver for above £15.50

TOP QUALITY . . . TOP SERVICE BOTTOM PRICES!

For FREE CATALOGUE send 9" x 6" SAE — contains full list of stock range all at very competitive prices. Cash with order (except account customers). Access or Barclaycard telephone orders welcome. Add 65p p&p + 15% VAT to all UK orders. Overseas customers add £2.50 p&p Europe, £6.00 elsewhere. Giro No. 529314002. Goods by return subject to availability. Shop open 9am — 5pm (Mon-Fri). 10am — 4pm (Sat). ALL PRICES EXCLUDE VAT



CHRISTMAS PRESENTS GALORE

BEGINNERS' PROJECTS PACK
Contains solderless breadboard, components and booklet with instructions to build TEN fascinating electronic projects, e.g. thermostat, burglar alarm, light operated switch, electronic lock, touchswitch, siren. Requires 9V PP3 battery. £12.50

MW RADIO KIT
Based on ZN414 IC, kit includes PCB, wound aerial and crystal earpiece and all components to make a sensitive miniature radio. Size: 5.5 x 2.7 x 2 cms. Requires PP3 9v battery. IDEAL FOR BEGINNERS. £5.50

3-NOTE DOOR CHIME
Based on SAB0600 IC the kit includes all components, loudspeaker, PCB, pre-drilled box (95 x 71 x 35mm) and full instructions. Requires a 9V battery and pushswitch. IDEAL PROJECT FOR BEGINNERS. Order as XK102. £5.50

20kV MULTIMETER
19 ranges including 10A dc. Resistance to 10M, ac & dc volts to 1kV. Battery checker and continuity buzzer. Size: 135 x 89 x 40mm. (405 104) £11.75


DIGITAL MULTIMETER
19 ranges including dc current to 10A, resistance to 20M, ac & dc volts and npn/pnp transistor gain. Full overload protection. Comes with test leads, battery and case. Size: 175 x 93 x 42mm (405 204) £32.00

20kV MULTIMETER
23 range quality multimeter with 12A dc current, ac and dc volts to 1200V, resistance to 1M and dB scale. Transistor gain and leakage scales, battery tester. Size: 155 x 102 x 56mm. (405 106) £16.95

STOCKING FILLERS All full spec. branded devices.

- PACK (1) 650 Resistors 47 ohm to 10Mohm — 10 per value £4.00
- PACK (2) 40 x 16V Electrolytic Capacitors 10µF to 1000µF £3.25
- PACK (3) 60 Polyester Capacitors 0.01 to 1µF/250V — 5 per value £5.55
- PACK (4) 45 Sub-miniature Presets 100 ohm to 1 Mohm — 5 per value £2.90
- PACK (5) 30 Low Profile IC Sockets 8, 14, and 16 pin — 10 of each £2.40
- PACK (6) 25 Red LEDs (5mm dia.) £1.50

INFRA-RED REMOTE CONTROL KITS

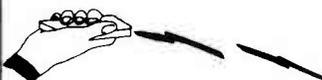

These kits are designed to enable infra-red remote control to be incorporated into virtually any application from switching car locks or alarms to controlling Hi-Fi or TV. The application will determine the interface circuitry between the receiver and the controlled device. General instructions and applications are supplied. The kits are coded and provide a high degree of security and noise immunity.

Keyboards for MK 18

- MK9 4-way for use with MK 12 £1.90
- MK10 16-way for use with MK 12 £5.40
- MK11 11-way for use with MK 11 £4.35


MK11 Receiver Kit — mains powered. Provides 10 latched plus 3 analogue outputs ideal for controlling audio amplifiers, TV or lighting where control of light brightness is required. £13.50

MK14 AC Power Controller Kit — for (phase) controlling AC loads from MK11 analogue outputs, eg lamp dimming. £5.20

MK19 Stereo Amplifier Controller Kit — for remote control of bass, treble and volume (or balance) by MK11. Includes a one of 10 decoder remote channel or input selection. May be connected between the pre-amp and power amp of almost any audio system. £10.70

MK12 Receiver Kit — mains powered with 16 latched or momentary outputs. Latched version is for applications requiring one output on at a time, eg TV channel selection. Momentary type gives an output only during transmission. Lines may be latched as required. Size: 9 x 4 x 2cms. £13.50

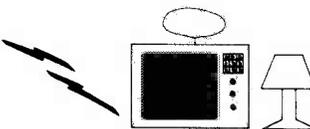MK15 Dual Latched Solid State Relay — for switching mains loads such as lamps, TVs, etc. from the outputs of the MK12 (momentary). 15 items may be switched independently using 8 MK15s. Triacs (not supplied) switch at mains zero to reduce interference. £4.50



MICROPROCESSOR TIMER KIT

Designed to control 4 outputs independently switching on and off at preset times over a 7-day cycle. LED display of time and day, easily programmed via 20-way keyboard. Ideal for central heating control (including different switching times for weekends) Battery back-up circuit. Includes box. 18 time settings.



- CT6000K £39.00
- XK114. Relay Kit for CT6000 includes PCB, connectors and one relay. Will accept up to 4 relays. 3A/240V c/o contacts £3.90
- 701115 Additional Relays £1.65

ELECTRONIC LOCK KIT

With hundreds of uses indoors, garages, car anti-theft devices, electronic equipment, etc. Only the correct easily changed four-digit code will open it! Requires a 5-15V DC supply. Output 750mA. Fits into standard electrical wall box. Complete kit (except front panel) £11.50

XK101 Electric Lock Mechanism for use with existing door locks and the above kit. (Requires relay.) 12V AC/DC coil (701 150) £14.95

HOME LIGHTING KITS

These kits are designed to replace a standard wall switch to control up to 300w of lighting



- TDR300K Remote Controlled Light Dimmer £14.95
- MK6 Transmitter for above £4.50
- TD300K Touch Dimmer £7.75
- TS300K Touch Switch £7.75
- TDE/K 2-way extension for above kits £2.50
- LD300K Rotary controlled Light Dimmer £3.95

DISCO LIGHTING KITS

DL1000K — This value-for-money 4-way chaser features bi-directional sequence and dimming. 1kW per channel. £15.95

DL21000K — A lower cost uni-directional version of the above. Zero switching to reduce interference. £8.95

Optional opto input allowing audio 'beat'/light response (DLA/1) 70p

DL3000K — 3-channel sound to light kit features zero voltage switching, automatic level control and built-in microphone. 1kW per channel. £12.95

OTHER KITS


- CT1000K Clock/Timer £14.90
 - CT1000KB Clock/Timer + Box £17.40
 - XK126 DVM/Thermometer £15.50
 - MK1 Thermostat £4.60
 - MK2 Solid State Relay £2.60
 - MK4 Temperature Control £6.50
 - MK5 Mains Timer £6.50
 - MK6 Infra Red Transmitter £4.50
 - MK7 Infra Red Receiver £10.50
- All kits include PCBs, components and assembly instructions. For further details send S.A.E.

ELECTRONICS

11-13 Boston Road
London W7 3SJ

ORDERS 01-567 8910 ENQUIRIES 01-579 9794

01-579 2842 TECHNICAL AFTER 3pm

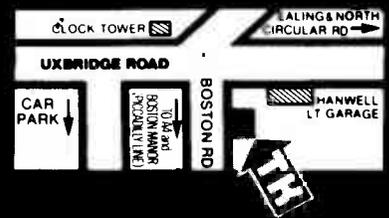

MIND YOUR HEAD!

How many heads do you have? Are they laminated or solid? And how wide are the slits in them? Vivian Capel reveals all that you need to know about your tape heads (what else?)

While it is easy to understand the mechanical aspects of tape recording, and the electronic ones are quite straightforward, the operation of the heads and the various factors affecting them are generally less readily understood. In this article, we do not intend to go deeply into magnetic theory, but rather to explore some of the practical whys and wherefores, so that the recorder user will have at least a nodding acquaintance with the head and what it does.

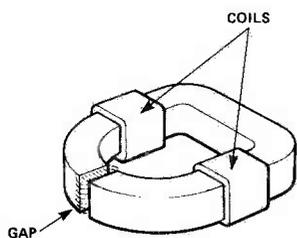


Fig. 1 Magnetic recording head showing core, gap and coils.

Construction

The construction of a tape head is really quite simple, see Fig. 1. In essence it consists of a squared-off ring of magnetic material on which is wound one or two coils. One end of the ring is rounded and in the centre of this is a fine vertical slit or gap which is filled with a shim of non-magnetic material.

In the case of a stereo head there are two ring-cores and sets of coils, one stacked above the other, separated by a magnetic shield to reduce cross-talk between them.

When a current is passed through the coils a magnetic field is set up through the core and across the gap; the two sides of the gap form the poles of an electromagnet, one north and the other south, depending on the direction of the current through the coils.

Most of the magnetic field passes through the gap via the shortest path, that is from one gap face to the other, but not all. There is also an external field which forms a roughly hemi-cylindrical pattern around the outside of the gap. It is through this external field that the tape passes.

As the tape travels across the gap it is magnetized in sympathy with the signal currents through the coils, and thus a series of magnetic zones are created along the tape track. The height of these (which is the width of the track) is the same as the height of the gap and so is fixed, but the width along the tape depends on the frequency

recorded: high frequencies produce narrow zones while low frequencies give rise to wide ones.

During playback, the magnetized zones passing back over the gap induce varying fluxes in the core which in turn generate corresponding EMFs in the coil windings; the recording process is the reverse, approximately.

Two Heads?

Obviously, the same head that made the recording can serve to play it back, and in the majority of recorders this is the practice. It would in fact seem that this was an ideal arrangement, as there thus can be no alignment or azimuth differences with the same head gap doing both jobs. Yet we find that in the more expensive machines two heads are provided (in addition to the erase head) one for record and the other for playback. Where space is limited as it is in the audio cassette recorder, the two heads may be mounted side-by-side in the same casing. If one head seems to do the job well enough in most machines, why go to the trouble of having two? Suspicious-minded individuals may wonder if this is just a ploy to hike the price and sell the goods, rather like those early "10-transistor" radios that had three of them soldered to the printboard doing nothing.

In this case, there are several advantages in having separate record and playback heads. Firstly it makes AB monitoring possible, whereby you can switch from the source to the playback head whilst actually recording, and compare; any deficiencies in the recording can be immediately detected. However, some machines have separate heads but do not give the AB monitoring facility, so there must be other reasons.

To appreciate the playback head, we need to take a closer look at it, and in particular, its gap. We have already mentioned that high recorded frequencies are represented by narrow magnetic zones. To read them accurately, we need a narrow gap that is less than half-a-wavelength of the highest recorded frequency wide.

To see why this is so, imagine a complete cycle of a high frequency recorded on the tape; it has two sections, the positive half cycle and the negative, which are represented by corresponding north and south pole regions along the tape. If the playback gap is a whole wavelength wide, as in Fig. 2a, both sections appear across the gap at the same time and the flux cancels, giving no output. The gap width then, is one of the main limiting factors to the highest frequencies that can be replayed.

When the gap width equals half a wavelength, output is at maximum, Fig. 2b. We can then calculate the theoretical upper limit for a particular gap width, or alternatively specify a maximum width to obtain a given

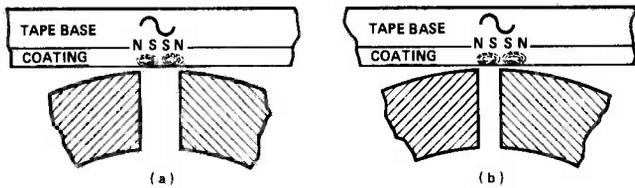


Fig. 2 When the playback gap is equal to a whole recorded wavelength, the fields of opposite half-cycles cancel and produce zero output (a). When the gap is equal to half a wavelength (b), output is at maximum.

upper limit. The standard compact cassette tape speed is 1 7/8 inches per second, or 47,500 microns per second. Dividing that by any particular frequency will give its recorded wavelength in microns. So for 20 kHz, the wavelength on tape is 2.4 microns. Half of this is 1.2 microns which is therefore the maximum width for a gap which would be required to record up to 20 kHz.

Actually there are various losses which take place that affect the high frequencies more than the low. These cause a fall-off from around 4 kHz, but electronic equalization can boost the signal above that point so that a reasonably level response is achieved toward the theoretical maximum. Boosting beyond the limit set by the gap width is useless because cancellation occurs and boosting nothing produces nothing — except noise.

A Wide Gap

One might, therefore, assume that a narrow gap in the region of 1.2 microns is necessary to obtain a good HF response from the record head too. Some surprise may be caused by the discovery that dedicated record-head gaps are much wider, up to 10 microns in many cases. According to our above calculations, for a 10 micron gap the half-wavelength frequency is a mere 2.4 kHz. How does it manage to record wavelengths many times shorter than its width, and why is the gap made so wide?

Fig. 3a shows the goings on at the head, but an analogy might help us to see how it is done. Supposing a long strip of material is required to be painted in alternate inch-wide black-and-white stripes. It is moved past a machine which has two spray guns filled respectively with quick-dry black and white paint, at a speed of one inch in two seconds. The machine fires the spray guns through a mask with an inch-wide slot alternatively every two seconds. Thus one stripe is just beyond the mask as the next one is sprayed.

Could half-inch stripes be obtained? Yes, by simply operating the guns every second. The first stripe is an inch wide, but it has only travelled halfway across the mask before the next one is sprayed. So it overlaps the first, and in the same way the third overlaps the second. The result is a series of half-inch stripes. Even narrower ones could be obtained by firing the guns more frequently, yet with the same 1-inch mask.

In the recording head, for frequencies having a shorter wavelength than the gap, the flux partially erases what has gone before, leaving only that which has passed beyond the range of the gap; the trailing edge of the gap effectively 'writes' the recording.

Actually, the audio signal is superimposed on a steady high-frequency bias signal which carries it over the non-linear low-level portions of the magnetizing curve. The bias signal magnetizes the tape but is almost completely self-erased by succeeding half-cycles, leaving the superimposed audio. The bias frequency ideally should be as high as possible to avoid intermodulation distortion

with the high audio frequencies, but this raises problems in the head as we shall see later.

Why A Larger Gap?

As we have seen earlier, the external field from the record head gap extends in an approximately hemicylindrical configuration around it. The presence of the tape, being a magnetic material, modifies this somewhat. However, the distance that the field extends from the gap is proportional to the width of the gap, being roughly half that of the gap width.

With a narrow gap, there is only a small external field, hence a shallow penetration of the magnetic coating on the tape, Fig. 3b. On the other hand, a wide gap, Fig. 3c, produces a more extensive field and deeper penetration. Deeper penetration in turn means more of the coating is utilized and gives a better signal-to-noise ratio and a higher magnetic saturation point. Hence, by employing two heads, the optimum gap can be used for each, a narrow one in the playback head to obtain maximum HF response, and a wider one for the record head to achieve deep penetration and utilization of the tape coating.

This, incidentally, explains a phenomenon which has puzzled some recorder users. Dirty heads prevent intimate contact between head-face and tape, and have a similar effect to widening the gap. Tapes replayed suffer from a loss of high frequencies, and with really dirty heads, sound badly muffled. If a recording has been inadvertently made with a dirty head and subsequently played back it might be thought to have been hopelessly ruined. Not necessarily so: after cleaning the head and re-playing it is often found to be not as bad as feared. While the signal level is lower and noise higher than normal, the HF response is reasonable, and the recording may be passable.

If then you have gone to a lot of trouble to record a computer programme and then find it turns out more SIC than BASIC because of a dirty head, try cleaning and reloading before giving up! Better still, make sure the head is clean beforehand!

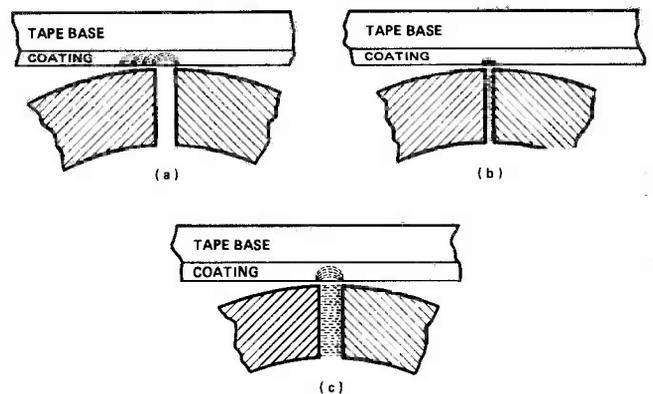


Fig. 3 A wide gap in a recording head can record short wavelength signals by overlapping and partially erasing the previous half-cycles. External gap from the field is roughly hemicylindrical (semi-circular when viewed from the top) and the depth of the field in the tape is roughly half the gap width (the gap is the diameter of the circle and the depth the radius). A narrower gap (b) leads to a smaller depth than a wider gap (c).

Perpendicular Or Horizontal?

When recording medium to low frequencies, the recorded wavelength is long in comparison with the field depth and the resulting internal field produced in the tape-coating is mainly longitudinal, that is, it lies along

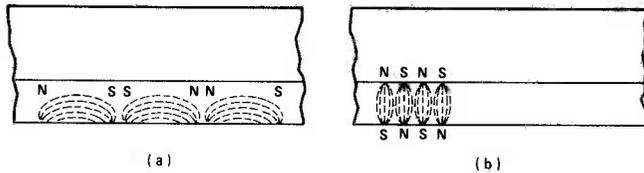


Fig. 4 Conventional recording heads produce longitudinal magnetic zones in the tape coating, with NS, SN, NS polarity, (a). Perpendicular recording in which the tape passes between the recording poles gives a greater packing density, and N, S, N, S adjacent pole polarity.

the tape in the direction of travel, Fig 4a. Only at the ends of each zone does the flux have a vertical component and become perpendicular to the tape surface.

To achieve a strong field in the longitudinal direction, the active magnetic particles in the coating are not of random shape like gravel chips, but acicular (needle-shaped). When the coating is applied during manufacture, it is passed through a powerful magnetic field before it dries to align all or most of the needles along the length of the tape.

At present, much research is being conducted in various fields to pack as much information as possible in the smallest space. Video and digital audio systems demand high information packing densities so stimulating the search. Attention has turned to making the recording field principally perpendicular, Fig 4b. Just as you can get more people in a high-rise block of flats than in bungalows of the same ground area, more information can be stored by perpendicular fields.

This would mean orientating the needle particles so that they would all be standing on end. Though not impossible it would pose problems for the tape makers. The recording field would be applied by passing it through rather than across the tape, which would mean the tape travelling through the gap. One way of doing this would be to construct a head having a very fine magnetic pole-piece surrounded by non-magnetic material, with a permalloy plate behind the tape to complete the magnetic circuit.

The magnetic zones thus created would alternate NSNS and resemble a collection of bar magnets arrayed side by side with opposite poles adjacent. This is much less prone to self de-magnetization than the present system whereby the zones NSSNS are equivalent to bar magnets assembled end-to-end with similar poles adjacent.

Information packing densities closer than the wavelength of visible light are possible, which makes feasible many applications that could not be seriously considered with the present technology. Linear video recordings may be possible, thus eliminating the mechanical complexity of rotating head-drums and helical scan.

Bias

So we may see radical changes in tape-head design in the future. But now back to the present, and in particular, tape bias. We have already alluded to HF bias, but why is it necessary and what exactly is its effect?

When any magnetizable material is magnetized, the process does not proceed at first in a linear manner; in fact the plot of magnetism against magnetizing force is quite curved. After this initial non-linearity though, the plot straightens and the characteristic becomes linear. The effect is similar to the operating curves of valves and transistors but with one exception, the magnetic curve has a negative component. The material can just as well

be magnetized in the opposite direction, whereas of course you cannot reverse the current through a transistor.

A typical curve is shown as part of Fig 5a; the negative section is identical but opposite to the positive section. One point to note is that this is the curve for an (initially) unmagnetized piece of tape; if the tape were magnetized, the magnetic field would, obviously, not be zero when the magnetizing force was zero, and we'd have a completely different curve; this sort of situation is dealt with in detail by text-books on electricity and magnetism.

If we applied a signal to the recording head in the form of sine wave, the resulting magnetization (and hence the resulting signal on replay) would be grossly distorted, due to the non-linear central portion of the characteristic, Fig 5a. The simplest solution is to apply a DC bias current to the record head in addition to the AC signal, so that the AC signal sits entirely with the relatively linear section of the curve, as shown in Fig 5b.

This works well enough in practice, but it is wasteful of the tape's recording potential. With the negative portion unused, the maximum recordable signal is less than

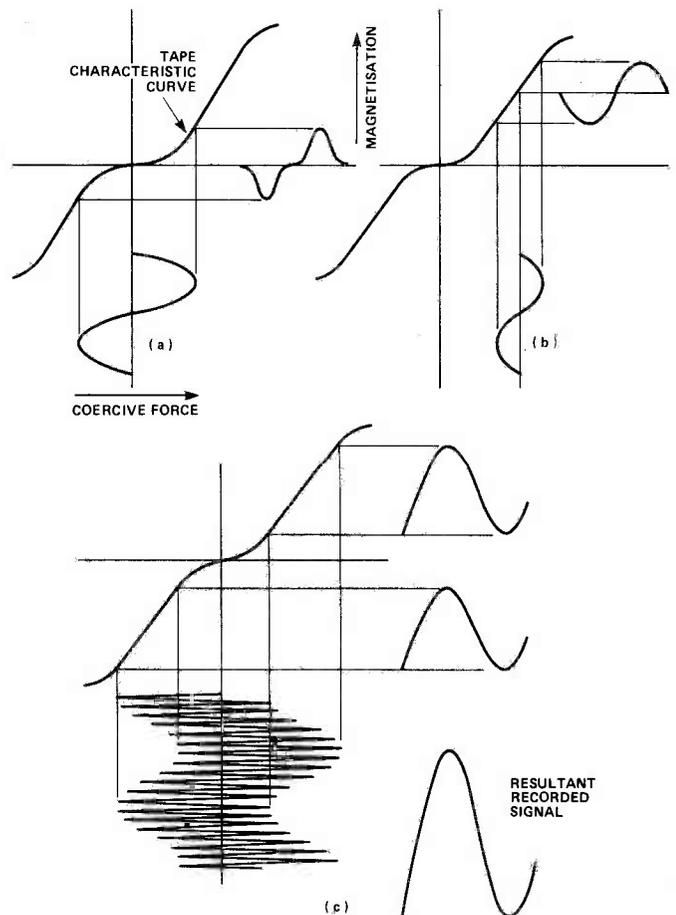


Fig. 5 Initial magnetizing characteristic of recording tape. (a) A sine wave signal recording over the curved lower portions of negative and positive characteristic, resulting in distortion and low volume. (b) DC bias lifts the operating point to the middle of upper straight portion giving linear output, but limited amplitude. (c) AC high-frequency bias bridges the curved non-linear portions so presenting the superimposed audio to both straight sections. The result is a linear, large amplitude recorded signal.

half what it could be if both portions were used and the signal-to-noise ratio is also less than half what it would be. For this reason, DC bias is used only on cheap cassette recorders.

AC bias is used in all the better and hi-fi recorders, and it does make use of the whole magnetisation curve. The audio signal is added to a high-frequency (several times the maximum audio frequency, and typically 30-100 kHz) sine wave, to give the effect shown in Fig. 5c (note that this is *not* amplitude modulation, and Fig. 6 shows the difference!)

When this composite signal is applied to the tape, distortion occurs where the composite signal traverses the non-linear parts of the curve. But the distortion is only of the lower portions of the HF bias; the audio which is riding on the crest of the bias waves is unaffected. The upper and lower portions of the composite wave affect the positive and negative parts of the characteristic, producing complementary audio signals. These add to produce the final recorded audio signal of large amplitude.

What happens to the bias signal? It has been said that it is not recorded because the frequency is too high. Well, it is recorded on the tape, otherwise it could have no effect on the tape's magnetization curve; the bias frequency is recorded by the 'paint stripe' effect already described for high-frequency audio.

However, it does not **remain** on the tape for more than a few microseconds. This is due to self-erasure. A magnetic field does not have hard and fast boundaries; it diminishes rapidly beyond the main field, but it does exist outside it. Hence the field from the gap extends along the tape for a very short distance; so even though the tape has passed it, it is still within a quickly diminishing field.

Now this has little or no effect on long wavelengths because most of the recorded half-cycle has passed well beyond the reach of the field before the next and opposite half cycle starts to build up. With very short wavelength is not so; the field from the gap at one half-cycles extends sufficiently to erase the preceding one, and as the tape proceeds away, the diminishing field zeros out, until there is nothing left.

We end up with nothing on the tape except the audio signal. This effect accounts for another phenomenon. Self erasure can also occur with high audio frequencies, although to a lesser extent than with the bias. At the high signal levels, the stray field is stronger and so erases further along the tape, affecting longer wavelengths than with low signals. Hence the high frequency response taken at 0 VU on the recording level meter is always poorer than when taken at a lower level.

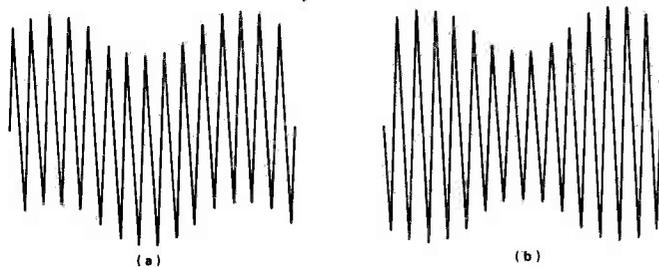


Fig. 6 The difference between a superimposed signal (a) and a modulated one (b). With the superimposed signal, the amplitude of the high-frequency component remains unaffected, hence it is not modulated.

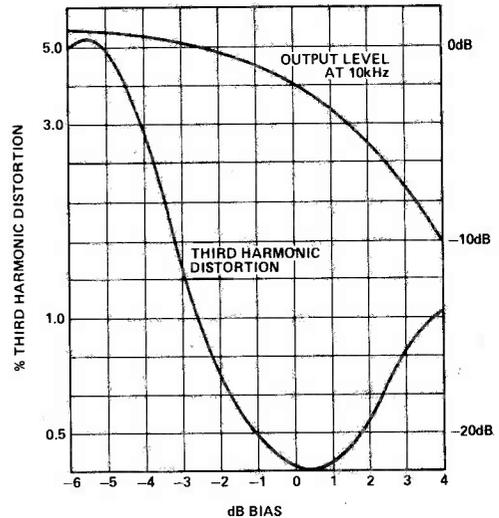


Fig. 7 Relationship between distortion and frequency response with a change of bias level. Optimum point for minimum distortion also produces a drop of 3 dB in the 10 kHz signal level (for one brand of C120; tapes vary in amount of distortion and HF loss).

Another associated effect is that too high a bias level curtails the audio high-frequency response. This is a rather unfortunate effect because there is an optimum bias level at which the distortion is at a minimum, and going either higher or lower will increase distortion. Unfortunately this optimum level for distortion is too high for maximum HF response, as self-erasure by the bias signal will have begun to make inroads into the higher audio frequencies.

So, bias can be set for either maximum HF response or minimum distortion, but the two settings do not coincide, see Fig. 7. Usually a compromise setting is chosen somewhere between the two. Each make of tape has its own bias requirements so a tape that performs well on one machine may not give of its best on another which has a different bias setting. Understandably, makers tend to set the bias for best results on their own make of tapes, if they also manufacture tape. If desired, bias can be re-set using suitable test equipment, to optimise for a particular brand of tape.

Head Materials

Various head materials are currently being used by the manufacturers and are often specified in their brochures. What are the characteristics of these materials and which, if any, is the best?

The standard material used in the majority of ordinary cassette recorders and many hi-fi decks is Permalloy which is an alloy of about 78% nickel and iron with a small proportion of molybdenum. It accepts a high flux density without saturating which means that it will take high recording levels without distortion. It also has a high permeability, which gives a good flux at the tape.

Unfortunately, the permeability drops as frequency increases so that at 10 kHz it is between a fifth and a tenth of its value at 1 kHz. Hence, the head response falls with increasing frequency, with poor results at the upper end of the range. As self-erasure and other losses affect the high frequencies too, this characteristic is particularly unwelcome.

Another problem is caused by eddy currents. When an electrical conductor is situated in a changing

magnetic field, currents are induced in it. So the flux produced by the signal currents in the coil when recording, or by the tape during playback, produce currents within the core itself, because Permalloy is a good conductor. These eddy currents give rise to heat and therefore losses; furthermore, they increase as the frequency rises. So here is another factor that impairs the high-frequency response. In particular, such losses set a limit on the highest frequency that can be used for the bias. A high bias frequency reduces the possibility of intermodulation distortion, but this advantage cannot be realised with Permalloy heads.

To reduce eddy currents, Permalloy cores are assembled as a stack of laminates, similar to an iron-cored transformer. Unfortunately this brings another snag: it is almost impossible to assemble a stack of laminates so that the sides are perfectly in line; they may appear so to the naked eye, but through a microscope, they can be seen to be staggered to varying degrees. This matters little around the periphery of the core, but it does at the gap, where, owing to the small size of the gap itself, any staggering can increase the effective gap width (Fig. 8) which is especially detrimental in the case of the playback head where a narrow gap is essential.

A further drawback with Permalloy is its softness. It rates 130-140 on the Vickers hardness scale and wears rapidly compared to other materials, in the order of 120 microns per thousand hours, and 1,000-2,000 hours is about the average life before performance deterioration dictates a replacement. The non-magnetic shim which fills the head gap and thus prevents it becoming clogged with magnetic material shed from the tape, is chosen to have similar rate of wear as the core material. For Permalloy it usually is beryllium copper foil.

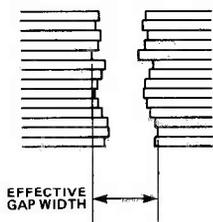


Fig. 8 Laminated stack with imperfect alignment. Effective gap width is increased. With widths of little more than one micron, small irregularities matter.

So as to avoid the various disadvantages of Permalloy, sintered-ferrite was developed as a head material. This is a combination of various oxides, mainly iron oxide, zinc oxide, manganese oxide, and nickel oxide, in fine grain form with a ceramic filler and binder.

At first glance the material seems inferior to Permalloy; it permits about half the maximum flux density, and has only around a tenth of its permeability. However, the permeability is less dependent on frequency, being three-quarters at 10 kHz of its 1 kHz value. It has a comparatively high electrical resistance which means minimal eddy currents, so the HF response is well maintained and the bias frequency can be high, reducing distortion levels. Absence of eddy currents means that the core can be solid instead of laminated, making it easier to make an accurate gap. Finally, a major advantage is the hardness, which at 400 on the Vickers scale, is three times harder than Permalloy.

There are, however, a number of disadvantages. As already noted, the permeability is much lower as is the

maximum flux density. Also, the material is brittle and liable to chip. Tiny air bubbles can sometimes be found in it, which could result in cavities in the face when it is machined into shape. Residual magnetism tends to be higher, requiring a larger coercive force to overcome it which can result in a higher noise level.

These and other disadvantages have led to the search for a method of improving the characteristics of ferrite, and the development of HPF (hot-pressed ferrite). As its name implies, this is produced by compressing ferrite at high temperature during manufacture, pressures of 7,000 lb per square inch at 1,400°C being typical.

The permeability of HPF is not only better than ferrite but greater even than Permalloy, while the permeability consistency with frequency is as good as sintered-ferrite. Residual magnetism too is far better, being less than ferrite and Permalloy. Maximum flux density though is the same as ordinary ferrite which is less than Permalloy.

As regards hardness, HPF scores again being even harder than ferrite at 650-700 on the Vickers scale, making it five times harder than Permalloy. To give comparable hardness, the gap filler is usually made of hard glass. One manufacturer claims a wear factor of 0.4 micron per 1,000 hours which is very good indeed. HPF heads are also used in video recorders, but they have a much shorter life there because of the high head-to-tape speed. A life of 1,000-2,000 hours is the normal expectation.

No bubbles can remain in HPF heads so the possibility of unexpected cavities is eliminated. Like ordinary ferrite it can take a high polish and so ensure intimate tape/head contact with minimum drag.

It might seem that HPF has nearly everything going for it but there is a major problem — metal tape. This needs a much higher flux density both to record and erase, and as we have seen ferrites are inferior to Permalloy in this one respect.

So the search continues for the ideal tape-head material and various substances have been tried. One of these is Sendust, which has the sensitivity of Permalloy and the hardness of ferrite. The snag is low electrical resistance though, leading to eddy currents. This has been overcome by making it in ribbon form by blasting it through rollers when hot, then rapidly cooling. Laminates are made from the ribbon, so we are back to laminated stacks and their problems of staggered gaps.

However, as the high permeability is most needed during recording on metal tape, and as recording-head gaps are wider than playback ones, gap accuracy is less of a problem. Laminated Sendust can be used for the record-head while a solid HPF head can be used for playback.

	Permalloy	Ferrite	HPF
Constituents	Ni Fe Mo	MnO Fe ₂ O ₃ ZrO ₃ NiO	MnO Fe ₂ O ₃ ZrO ₃ NiO
Permeability:			
1 kHz			
10 kHz	18000	1200	20000
Max Flux Density	1500	900	10000
(gauss)	7000	4000	4000
Coercive Force	0.02	0.5	0.015
(oersteds)			
Specific Resistance	5 × 10 ⁻⁵	>100	>100
(ohm.cm)			
Vickers Hardness	135	400	700

Table 1 Head materials and characteristics.

Azimuth

Correct positioning of the head or heads is essential. Firstly, the height must be such that the tape is in a perfectly straight line across the head assembly. If one head is out of line, the tape-guide on the side of the head will pull the tape up or down at that point, resulting in damage to the tape edge or a weaving motion producing regular variations of signal level and HF response.

Next, the head must be vertical from front-to-back. A backward lean, for example, results in imperfect contact between the top half of the tape and the head, increasing the likelihood of drop-outs.

Finally, the azimuth or side-to-side angle must also be vertical. Theoretically, the azimuth doesn't matter as long as the playback setting is the same as the recording. This is obviously the case with single-head machines when tapes recorded on the same machine are played back. However, problems occur when tapes recorded on other machines are played back on the faulty machine (or tapes recorded on the faulty machine are played on others) and also with pre-recorded tapes.

The reason is that a slanted record head produces corresponding slanted magnetic zones on the tape. A vertical playback azimuth will bridge across the narrow slanted zones, as a slanted head will bridge across vertical zones (see Fig. 9a). In both cases, the effect is that of increasing the head gap width. As it is only the narrow zones that are so affected, the result is a loss of short-wavelength high frequencies, the loss increasing with increasing angle difference.

This effect is quite well known, but there is another which is less commonly appreciated. When a stereo head is incorrectly set the two playback gaps are not exactly one above the other. The top one will be slightly in advance or behind the bottom as the tape runs past, hence one channel is delayed.

The delay is too small to be noticeable as such, but it will result in phase-differences in the high and higher mid frequencies, which will lead to poor stereo image. Also, switching to 'mono' and combining the two stereo channels into one can lead to a severely curtailed high-frequency response — this can happen even when the stereo doesn't sound too bad! So, if a recorder gives poor stereo image from pre-recorded tapes but a good image with tapes recorded on it, then the likely cause is the playback head azimuth setting.

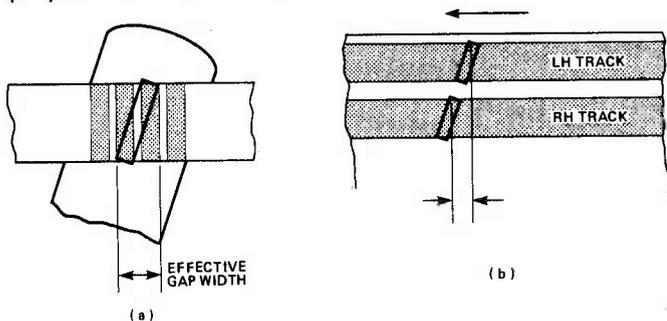


Fig. 9 When azimuth is not vertical, gap bridges across short wavelength zones, increasing its effective width and thus losing the high frequencies, (a). With a stereo head, (b), incorrect azimuth produces a delay between channels which can impair stereo image by upsetting the phase relationships. Azimuth errors shown here are exaggerated for the purpose of illustration.

To conclude, although the heads in your recorder are quite simple devices, there is rather more involved than you may think. We will undoubtedly see further developments as times goes on.

ETI

HENRY'S

AUDIO ELECTRONICS

UK'S NO.1 FOR ELECTRONICS

ALL PRICES INCLUDE VAT

STEREO RADIO TUNER


Ready built
Mw-Lw Stereo FM
By well known
Hi-Fi manufacturer
Approx. 6 1/2 x 3 1/2 x 1 1/2"

With Data **£4.95** post 65p



HEXADECIMAL KEYPAD

16 button
(requires IC's) **£7.50**

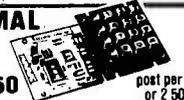


CHERRY ADD-ON KEYPAD

16 button pad non-encoded
£5.95 (UK post 50p per 1 to 2)



CASSETTE MECHANISMS

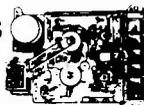Fitted counter. Motor. Stereo record and erase heads
Solenoid, etc. Brand new available 6V DC or 12V DC (state which) **£5.95** (UK C/P 65p)



THERMAL PRINTER

COMPLETE WITH FULL HANDBOOK
3 ROLLS PAPER

£49.95 (UK C/P £1.05)

SUITABLE FOR TANDY BBC ORIC NASCOM GEMINI ACORN DRAGON ETC. ETC. (interface unit with leads £15 - state model) (your enquiries invited)

NICADS/DEACS

Rechargeable packs
EVEREADY 8.4 Volt HEAVY DUTY
NICAD approx. 3 1/2" Diam x 3 1/2"
with magnetic switch **£5.95** post 55p



Two for **£11.00:** Four for **£20.00**
post 65p post 85p

DEACS (UK post 50p)

24 Volt 225 mA **£3.95**
6 Volt 90 mA **£1.25**
3.6 Volt 225 mA **£1.50**

COMPUTER POWER SUPPLIES

Large range in stock - many at very low prices

RECHARGEABLE BATTERIES & CHARGER

Charger takes any 4 'AA', 'C' or 'D' cells plus PP3 type.
With free mains plug **£5.50**
(UK C/P & ins 65p)



4 x 'AA' (HP7 size) rechargeable cells **£3.50**
(UK C/P 30p) Other sizes in stock

COMPUTER FANS

(UK C/P 60p each, £1.00 per pair)



4 1/2" 220/230V AC Brand new **£7.50** each
3 1/2" 115V/115V AC Brand new **£8.75** each
4 1/2" 220/240V AC Ex-units **£5.50** each
4 1/2" 110/115V AC Ex-units **£5.00** each

MARRIOTT TAPE HEADS

(UK post 50p per 1 to 4)
1/2" TRACK
XRP36 Low imp. **£3.50**
XRP38 Med imp. **£2.50**
XES11 Erase for above **£1.25**
1/2" TRACK
BX RP03 R/P **£2.25**
Erase for above **£1.25**



CASSETTE HEADS

Stereo **£2.95** Mono **£1.95**
Stereo erase **£1.00**

TOROIDAL TRANSFORMER

100 watts Isolation 230/240 V AC
plus 0-0-8V 4A 15-0-15V 9.845A
30V 0.18A size approx. 4 1/2" dia. x 1 1/2"
(UK C/P 75p) **£7.95**




UHF MODULATORS

(UK C/P 40p)
Video Input RF outputs casad for computers etc.

Astec UM 1233 **£3.50**
ITT version **£3.50**

ITT 2020 CABINET

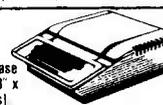Professional computer case with keyboard cutout. 18" x 15.5" x 4.5" (front slopes) Ideal for single board computers like the Nascom or Gemini Multiboard (3 cards, etc). Very heavy gauge (25") plastic with metal base. Attractive silver grey finish.
£22.95 (UK post £2.05)



ASC11 KEYBOARD

69S DS Compact. 64 key + 5 function keys. Hall effect keyboard with reprogrammable (2716) ASCII output decoder EPROM. Steel key frame for good rigidity. Negative going strobe. Requires +5 volt -12 volt supplies.
£24.95



COMPACT 58 KEY ASCII KEYBOARD

Contactless capacitive high reliability keys. Full 128 ASCII codes. Steel key frame for positive rigidity. 1ms strobe, single +5 volt supply. Repeat key, control and caps. lock. **£32.50** (UK C/P £1.00 either model)

TV AMPS/ DISTRIBUTION


UHF SET BACK
Ku700 7dB **£6.95**
KuHG 14 dB high gain **£10.95**
Ku650 7dB for 2 x TV's **£8.50**



UHF MAST TMB 30dB (MKD) **£18.95**
DISTRIBUTION - VHF/UHF 40 to 860MHz
4 way **£28.95** 6 way **£37.95** 8 way **£42.95**

POCKET RADIATION DETECTORS

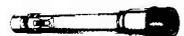Dosimeter for Gamma and X-Rays. 0-5r (UK Post 55p)
£6.95



STEREO TUNER/AMPLIFIER 1000's sold

4 wave-band stereo tuner amplifier by GEC MW/LW/SW stereo FM radio 10 + 10 watt stereo amplifier. Inputs for PU tape in/out. Supplied as two assembled units. - easy to connect.
as illustrated **£21.95**
(UK C/P £1.50)



MODEM CARDS/COUPLER

Brand new. Tested, answer and originate 300 BAUD uncessed acoustic modem card by famous manufacturer. RS232 Input/output, power supply +/- 12V at 180mA. Requires 2 magnetic earpieces. 2 switches. 2 LEDs and connectors to complete. Data supplied.
Card only **£28.95**
Card and remainder of small components **£33.45**
Telephone Direct Line coupler type LTU 11 MK11. Suitable for direct coupling PRESTEL adaptors and the above acoustic modems. Integral Line select and autodial relays requiring TTL inputs data supply.
£14.95
1200 BAUD receive 75 BAUD send direct coupled modem for PRESTEL. Requires +5V supply with TTL inputs for data. Line select and autodial. LTU 11 direct coupler required. See above. Data supplied.
£14.95

CB/HAM RADIO

Large range in stock - ask for leaflets



ALL PRICES INCLUDE VAT

ORDER BY POST OR TELEPHONE

CALL IN AND SEE FOR YOURSELF
OPEN 6 DAYS A WEEK

VISIT OR PHONE

**OPEN 6 DAYS
A WEEK
ALL STOCKS
ON DISPLAY**

HENRY'S

AUDIO ELECTRONICS



EQUIPMENT • COMMUNICATIONS • COMPUTERS • COMPONENTS


ALL PRICES INCLUDE VAT

SCOPES

(UK C/P £8.00 or £18.00 Securitor)

HITACHI

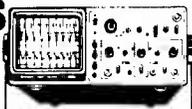
2 year warranty
ALL MODELS
WITH 2 PROBES
V212 Dual 20 MHz 6" CRT
line
V222 As 212 plus DC offset, etc
V203F Dual 20MHz Sweep delay 5" CRT
All other models available.



£343.85
£431.25
£431.25

HAMEG

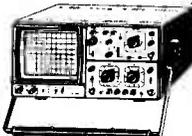
warranty Optional
probes see below
HM103 Single track
10MHz 8 x 7cm
display component
tester **£182.05**
HM203/5 Dual 20MHz 8 x 10cm
display component tester, etc. etc.
£303.60
HM204-2 Dual 20MHz, sweep
delay, 1mV, component tester, etc.
£419.75
Also HM605 Dual 60MHz



£303.60
£419.75
£592.25

CROTECH

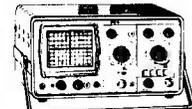
Optional probes
see below
3030 Single trace
15MHz component
tester 9cm display
3035 Single trace 15MHz 13cm
15" display component tester
3132 Dual 20MHz Trig to 40MHz 2mV/div 130mm (5")
display, algebraical add/sub Reg DC 0/P's - 5V AD ±
12V. Built-in component comparator



£205.85
£227.70
£341.50

LOW COST

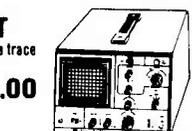10MHz 5mV single trace
75mm CRT general
purpose **£169.00**



THANDAR

2 year warranty
SC110A 10MHz battery
portable 32 x 28mm display
with batteries **£189.75**
(UK post, etc. £1.50)



OPTIONS Carry case **£6.84**
AC adaptor/charger **£7.99** Nicad pack **£12.65**

DIGITAL MULTIMETERS

Controls
s=Slide, R=Rotary
PB=Push button
All feature AC/DC volts,
DC amps (many with AC
amps) others, etc.
(UK C/P 85p) * WITH CARRY CASE



- * KD25C 12 range 0.2A DC 2 Meg ohm(s) **£27.95**
- * KD30S 14 range 10A DC/20 Meg ohm(s) **£29.80**
- * KD30C 26 range 1A AC/DC/20 Meg ohm (R) **£35.80**
- * METEX 3500 30 range 10A AC/DC 20 Meg ohm (R) **£39.68**
- * METEX 3510, 30 range 10A AC/DC, 20 meg ohm plus Hfe tester plus cont. tester (R) **£43.70**
- 6010 28 range 10A AC/DC 20 Meg ohm (PB) **£43.50**
- * KD55C 26 range 10A AC/DC/20 Meg ohm (R) **£44.50**
- * KD615 18 range 10A DC 2 Meg ohm plus Hfe tester (R) **£39.95**
- 7030 As 6010 but 0.1% basic (PB) **£53.95**
- HC 5010 31 range 10A AC/DC Cont. buzzer 20M ohm (R) **£49.95**
- * DM3350 Autorange plus cont. tester 18 range 10A AC/DC 2 Meg ohm (R) **£49.95**
- * DM2350 Mini autorange plus cont. tester 19 range 10A AC/DC (20A Max) 2 Meg ohm (PB) **£69.95**
- * 3100 Pen type auto ranging AC/DC V 20 Meg ohm + Buzzer **£44.85**
- SOAR MES40 Manual/Autoranging plus cont. buzzer, 19 range 10A AC/DC 20 Meg ohm (R) **£44.85**

ANALOGUE MULTIMETERS

(mirror scale) (UK C/P 65p)
HC1015 15 range pocket 10K/Volt
1 Meg ohm **£8.95**
M200 30 range 20K/Volt 20KHZ
SPECIAL PURCHASE **£7.95**
HM102B Z 22 range 20K/Volt 10A DC
plus cont. buzzer 10 Meg ohm **£14.50**
ETU3000 20 range 30K/V 12A DC
12 meg ohm **£21.00**



- NH58R 22 range 10K/Volt 6 Meg ohm **£12.95**
- 830A 26 range 30K/Volt 10AC/DC 10 Meg ohm **£24.95**
- 360TR 23 range bench, 100K/Volt large scale 10A AC/DC plus Hfe tester 10 Meg ohm **£45.00**
- AT2100 31 range de luxe 100K/Volt 10A AC/DC 100 Meg ohm **£34.95**
- AT1020 18 range de luxe 20K/Volt plus Hfe tester 5 Meg ohm **£22.50**
- YN 360TR 19 range 20K/Volt plus Hfe tester 1 Meg ohm **£15.95**
- KRT5001 Range doubler 35 range total 50K/Volt 10A DC 20 Meg ohm **£21.95**
- ST303TR 22 range 20K/Volt plus Hfe tester 12A DC 1 Meg ohm **£21.00**

LCD COUNTERS

(UK C/P & INS 65p)




THANDAR battery portable 8 digit LCD counters. Size 255 x 150 x 50mm. Complete with batteries. Optional: Carry case **£6.84** AC adaptor **£7.99**
TF040 10HZ to 40MHZ, 1HZ Res. 49mV sensitivity, **£138.00**
TF200 10HZ to 200MHZ, 1ppm res. 10mV sensitivity, many features. A&B inputs, etc. **£189.75**
TP600 600MHZ prescaler (Powered by computer) **£51.75**
TP1000 1000MHZ (10HZ) Prescaler with power supply **£74.75**
PFM200A Pocket 20HZ to 200MHZ LEO counter 0.1HZ res. 10mV sensitivity **£79.73**
NEW TF600 LED 600 MHZ counter **P.O.A.**



GENERATORS

Function and Pulse (UK C/P 65p)
THANDAR bench mains portable. Size 255 x 150 x 50mm **£6.84**
Options: Carry case **£6.84**
TG101 0.02HZ to 200KHZ function, sine, square, triangle. Variable DC offset, TTL D/P Ext sweep mode. Variable 600 ohm 10V PP **£120.75**
TG102 0.2HZ to 2MHZ function Sine, square, triangle. Variable DC offset, TTL D/P, Ext. sweep mode variable 600 ohm 0/P, 10V PP **£178.25**
TG105 5HZ to 5MHZ pulse, TTL and Sync D/P. Variable 50 ohm D/P. Free run, gated or trig. modes. **£120.75**

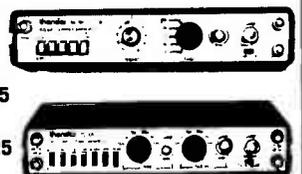

LCD & LED MULTIMETERS

(UK C/P 65p)



THANDAR BENCH PORTABLES Size 255 x 150 x 50mm Option: Carry case **£6.84**
TM355 3 1/2 digit LED, 29 ranges, 0.25% basic, 100mV res. 10A AC/DC, 20M ohm **£97.75**
(AC adaptor option **£8.95**)
TM356 3 1/2 digit LCD 29 ranges as TM355 3000 hour battery life (supplied) **£109.25**
TM351 3 1/2 digit LCD, 29 ranges, 0.1% basic. Ranges as above, 2000 hour battery life. **£132.25**



LED COUNTERS


(UK C/P 65p)
METEOR mains or battery portable 8 digit LED counters. Size 219 x 240 x 98mm, 5mV sensitivity 0.1HZ resolution
100 5HZ to 100MHZ **£109.25**
600 5HZ to 600MHZ A&B inputs **£138.15**
1000 5HZ to 1000MHZ (10HZ) A&B inputs **£189.75**



Options:
6 NICAOS **£12.19** RF pickup Aerial **£8.91** (AC adaptor included)

FUNCTION GENERATOR

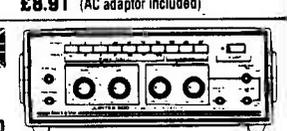(UK C/P 85p)
JUPITER 500 Function generator 0.1HZ to 500KHZ or better. Sine, square, triangle 0/P to ±30 volts. TTL 0/P, DC offset ±15V variable. Ext AM and sweep facilities 220/240V AC operated. **£126.50**



HIGH VOLTAGE METER

Direct meter reading
LHM80A 0/40KV **£32.20**
(UK C/P £1.00)



AC CLAMP METER

0/300A 0/800V AC 0/1K ohm
Total 9 ranges with carry case and lead
ST300 **£35.50** (UK C/P 65p)




COMPONENTS & TOOLS ACCESSORIES

LARGE RANGE IN STOCK
Tel: 01-723 1008 for small or large quantities.

TRANSISTOR TESTER

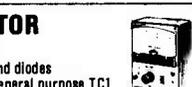Direct PNP/NPN and diodes
Hfe, leakage, etc. General purpose TC1
(UK C/P 65p) **£27.95**



ELECTRONIC INSULATION TESTER

500V/0-100 Meg ohm with carry case, leads, etc.
YF501 **£82.50**
(UK C/P 85p)



LOGIC PROBES

TTL DTL, etc.
LP2 1.5 MHz **£24.15**
DP70 30MHz **£28.75**
DP71 50MHz **£59.80**
(UK C/P 55p each)



VARIABLE POWER SUPPLIES

(UK C/P £1.00)
220/240V AC input
PP241 single meter A/V
0/30V 1 amp **£37.95**
PP243 3 amp version **£59.95**



DIGITAL CAPACITANCE METER

(UK C/P 85p)
0.1 pF to 2000 mfd LCD 8 ranges
DM6013 **£69.50**



PROBE KITS

In wallets with adaptors, etc. BNC fittings for scopes/counters/generators, etc.
X1 **£7.95** X10 **£9.50**
X100 **£18.40** X1/X10 Switchable **£11.50**
Demodulator **£18.50**
(UK C/P free with other items or 85p per 1 to 3 kits).

DIGITAL THERMOMETER

Pocket size LCD thermometers complete with battery. Accept any type K probe
(UK C/P 85p)
TH301 LCD -50° to +75°C 1°C resolution with thermocouple **£68.43**



LEAFLETS available for most items send SAE (Large 25p for latest catalogue)

GENERATORS

220/240V AC
(UK C/P, etc. £1.20)
AUDIO
LEADER LAG275 5 band sine/square 0/P 0/5V RMS 0.1 to 0.05% 10HZ to 1MHZ **£106.95**
TE220 4 range sine/square 0/P 5V RMS 0.5% Diat 20HZ to 200KHZ **£82.95**
TRIO A8202A 4 band 20HZ to 200KHZ, 10V RMS 0/P 0.5% diat CR OSC **£102.35**



RF
TRIO 3G402 8 range 100KHZ to 30MHZ RF 0.1V RMS Int/ex mod **£82.80**
LEADER L8617 8 band 100KHZ to 150MHZ Int/ex Mod. AF 1 KHZ volt 11 MHZ xtal optional **£3.50** **£132.25**
TE200 8 range low cost version of above up to 110MHZ (300MHZ Harmonics) **£74.95**

TR DIP METER
1.5 to 200MHZ 8 band
(UK C/P 65p) **£56.00**



SUPPLIERS OF ELECTRONICS FOR EVERY PURPOSE

Official orders welcome. (Subject to confirmation)

ALL PRICES INCLUDE VAT

ORDER BY POST OR PHONE



Up to £1000 instant credit
Available through Lombard Tricity Finance

301 Edgware Road, London, W2
Test Equipment, Audio, Communications 01-724 3564

404 Edgware Road, London, W2
Computers 01-402 6822 • Equipment 01-724 0323 • Components 01-723 1008



CALL IN AND SEE FOR YOURSELF All mail to Cubegate Ltd, 1st Floor, 406 Edgware Road, London W2 1ED

COMPUTER WAREHOUSE

1000's OF BARGAINS FOR CALLERS

THE 'ALADDIN'S' CAVE OF COMPUTER AND ELECTRONIC EQUIPMENT

HARD DISK DRIVES

Fully refurbished **DIABLO/DRE** Series 30 25 Mb disk drives. **DEC RKOS, NOVA, TEXAS** compatible. Front load. Free stand or rack mount. Exchangeable type (via lid removal) me3029 PSU unit for 2 drives. **£550.00** **£295.00** **£175.00**

DIABLO/DRE 44-4000A/B 5+5 ex stock from 1000's of spares for S30, 4000, 3200, HAWK ex stock. Plus in house repair, refurbishing service. Call for details or quotation. **£995.00**

EX STOCK INTEGRATED CIRCUITS OVER 100,000 ITEMS INCLUDING:

Intel **D8085AH-2** **£25.00** **D8271** **£65.00**
D8202 **D8257-5** **£25.50** **D3002**
2732 EPROM SPECIAL fully guaranteed
450ns **£3.75**, **350ns** **£4.00**, **300ns** **£4.50**

COOLING FANS

Keep your hot parts **COOL** and **RELIABLE** with our range of **BRAND NEW** professional cooling fans.

ETRI #XUOI Dim. 92 x 92 x 25 mm. Miniature 240 v equipment fan complete with finger guard. **£9.95**.

GOULD JB-3AR Dim. 3" x 3" x 2.5" compact very quiet running 240 v operation. **NEW £8.95**

BUHLER 69.11.22 8-16 v DC micro miniature reversible fan. Uses a brushless servo motor for extremely high air flow, almost silent running and guaranteed 10,000 hr life. Measures only 52 x 52 x 22 mm. Current cost **£32.00**. **OUR PRICE ONLY £12.95** complete with data.

MUFFIN-CENTAUR standard 4" x 4" x 1.25" fan supplied tested **EX EQUIPMENT** 240 v at **£6.25** or 110 v at **£4.95** or **BRAND NEW** 240 v at **£10.50**. 1000's of other fans **EX Stock**. Call for Details. Post & Packing on all fans **£1.60**

DUAL 8" DISK DRIVES

Current, quality, professional product of a major computer company, comprising 2 x 40 track **MPI** or **Shugart FULLY BBC COMPATIBLE** single sided drives in a compact, attractively styled, grey ABS structured case with internal switched mode PSU. The PSU was intended to drive both drives and an intelligent **Z80** controller with over 70 ic's. The controller has been removed leaving ample space and current on the +, -, +12 and -12 supply for all your future expansion requirements. Supplied tested with 90 day guarantee in **BRAND NEW** condition with cable for **BBC micro**. **EX Stock** at only **£259.00** + £10.00 **car. Limited Quantity Only**

GE TERMPRINTER

A massive purchase of these desk top printer-terminals enables us to offer you these quality 30 cps printers at a **SUPER LOW PRICE** against their original cost of over £1000. Unit comprises of full **QWERTY**, electronic keyboard and printer mech with print face similar to correspondence quality typewriter. Variable forms tractor unit enables full width - up to 13.5" 120 column paper, upper - lower case, standard **RS232** serial interface, internal vertical and horizontal tab settings, standard ribbon adjustable baud rates, quiet operation plus many other features. Supplied complete with manual. Guaranteed working **£130.00** or untested **£85.00**, optional floor stand **£12.50** **Car & Ins** **£10.00**.

DATA MODEMS

Join the communications revolution with our range of **EX TELECOM** data modems. Made to most stringent spec and designed to operate for 24 hrs per day. Units are made to the **CCITT** tone spec. With **RS232C** i/o levels via a 25 way 'D' skt. Units are sold in a tested and working condition with data. Permission may be required for connection to **PO** lines.

MODEM 20-1 Compact unit for use with **MICRONET**, **PRESTEL** or **TELECOM GOLD** etc. 2 wire direct connect 75 baud transmit 1200 baud receive. Data i/o via **RS232C** 'D' socket. Guaranteed working with data. **£99.95**

MODEM 20-2 same as 20-1 but 75 baud receive 1200 baud transmit. **£130.00**

TRANSDATA 307A 300 baud acoustic coupler **RS232C** i/o **£95.00** brand new. **CE4.50**

NEW DSL1213 Multi Standard modem selectable **V21** 300-300 bps, **V23** 75-1200, **V23** 1200-75 full duplex. Or 1200-1200 half duplex modes. Full auto answer via modem or CPU. LED status indicators. **CALL** or **ANS** mode Switchable **CCITT** or **BELL 103 & 202**. Housed in **ABS** case size only 2.5" x 8.5" x 9". **£286.00** + VAT.

For further data or details on other **EX STOCK** modems contact sales office.

Carriage on all modems **£10.00** + VAT.

HOT LINE DATA BASE

DISTEL ©

THE ORIGINAL **FREE OF CHARGE** dial up data base. 1000's of stock items and one off bargains. **ON LINE NOW** - 300 baud, full duplex **CCITT** tones, 8 bit word, no parity. **01-679 1888**

STILL IN STOCK

FP1500 Heavy Duty 25 cps daisy wheel **RS232** interface, bi directional printers, **Brand New** at **£499.00**
CALL FOR MORE DETAILS

SAVE **£250**

SUPER PRINTER SCOOP

BRAND NEW CENTRONICS 739-2



The "Do Everything Printer" at a price that will **NEVER** be repeated. Standard **CENTRONICS** parallel interface for direct connection to **BBC, ORIG, DRAGON** etc. Superb print quality with full pin addressable graphics and 4 type fonts plus **HIGH DEFINITION** internal **PROPORTIONAL SPACED** **MODE** for **WORD PROCESSOR** applications. 80-132 columns, single sheet, sprocket or roll paper handling plus much more. Available **ONLY** from **DISPLAY ELECTRONICS** at the ridiculous price of **ONLY £199.00** + VAT Complete with full manual etc. Limited quantity - Hurry while stocks last.

Options: interface cable (specify) for **BBC, ORIG, DRAGON** or **CENTRONICS** 36 way pig **£12.50**. Spare ribbon **£3.50** each **BBC** graphics screen dump utility program **£8.60**. Carriage and ins. **£10.00** + VAT.

SPECIAL 300 BAUD MODEM OFFER

Another **GIGANTIC** purchase of these **EX BRITISH TELECOM, BRAND NEW** or little used 28 data modems allows us to make the **FINAL REDUCTION**, and for **YOU** to join the exciting world of data communications at an **UNHEARD OF PRICE OF ONLY £29.95**. Made to the highest **POST OFFICE APPROVED** spec at a cost of hundreds of pounds each, the 2B has all the standard requirements for data base, business or hobby communications. All this and more!!

- 300 baud full duplex
- Full remote control
- CCITT tone standards
- Supplied with full data
- Modular construction
- Direct isolated connection
- CALL, ANSWER and AUTO modes
- Standard **RS232** serial interface
- Built in test switching
- 240v Mains operation
- 1 year full guarantee
- Just 2 wires to comms. line

NOW ONLY £29.95

Order now - while stocks last. Carriage and Ins. **£10.00**

8" 19MB WINCHESTER DISK DRIVE

Made in the UK by a subsidiary of the World's largest disk drive manufacturer. This **BRAND NEW** "end of line" unit offers an outstanding opportunity to add a **MASSIVE 19 mb** of storage to your computer system. Superbly constructed on a heavy die cast chassis the **DRE 3100** utilises 3 x 8" platters in a dust free cavity. All drive functions are controlled by microprocessor electronics using an **INTEL 8035** cpu and **TTL** support logic. Data to the outside world is via two comprehensive 8 bit **TTL** level bi directional data busses with full status reporting for ease of interfacing. Many features such as Av. seek time 35 ms, 512 bytes per sector, +24, -24 and +5 v DC supply, plug in card system, and compact size of approx. 19cm H x 21cm W and 42cm D etc, make this item a real snip.

Units are **BRAND NEW** and **BOXED** and sold at a **FRACTION** of original cost - hence unguaranteed. Complete with 150 page manual, circuits and applications guide.

ONLY £225.00 Carriage **£10.00**

Suitable power supply unit - sold **ONLY** with drive **£39.95**.

PROFESSIONAL KEYBOARD OFFER

An advantageous purchase of brand new surplus allows a great **QWERTY**, full travel, chassis keyboard offer at fractions of their original costs.

ALPHAMERIC 204/60 full **ASCII** 60 key, upper, lower + control key, parallel **TTL** output plus strobe. Dim 12" x 6" + 5 & -12 DC. **£39.50**

DEC LA34 Unencoded keyboard with 67 quality, **GOLD**, normally open switches on standard **X, Y** matrix. Complete with 3 **LED** indicators & i/o cable - ideal micro conversions etc. pcb DIM 15" x 4.5" **£24.95** Carriage on keyboards **£3.00**

66% DISCOUNT

Due to our massive bulk purchasing programme which enables us to bring you the best possible bargains, we have thousands of **IC's**, Transistors, Relays, Caps, PCB's, Sub-assemblies, Switches, etc. etc. surplus to our requirements. Because we don't have sufficient stocks of any one item to include in our ads, we are packing all these items into the **'BARGAIN PARCEL OF A LIFETIME'**. Thousands of components at giveaway prices! Guaranteed to be worth at least 3 times what you pay. Unbeatable value!! Sold by weight.

2.5kls **£4.25** + pp **£1.25** 5kls **£9.90** + **£1.80**
 10kls **£10.25** + pp **£2.25** 20 kls **£17.50** + **£4.75**

ALL PRICES PLUS VAT

All prices quoted are for U.K. Mainland, paid cash with order in Pounds Sterling **PLUS VAT**. Minimum order value **£2.00**. Minimum Credit Card order **£10.00**. Minimum **BONAFIDE** account orders from Government depts, Schools, Universities and established companies **£20.00** Where post and packing not indicated please **ADD £1.00**. + VAT Warehouse open Mon-Fri 9.30 - 5.30. Sat. 10.15 - 5.30. We reserve the right to change prices and specifications without notice. Trade, Bulk and Export enquiries welcome.

32 Biggin Way, Upper Norwood, London SE19 3XF
 Telephone 01-679 4414 Telex 27924

COMPUTER 'CAB'

All in one quality computer cabinet with integral switched mode PSU, Mains filtering, and twin fan cooling. Originally made for the famous **DEC PDP8** computer system costing thousands of pounds. Made to run 24 hours per day the PSU is fully screened and will deliver a massive +5v DC at 17 amps, +15v DC at 1 amp and -15v DC at 5 amps. The complete unit is fully enclosed with removable top lid, filtering, trip switch, 'Power' and 'Run' LEDs mounted on All front panel, rear cable entries, etc etc. Units are in good but used condition - supplied for 240v operation complete with full circuit and tech. man. Give your system that professional finish for only **£49.95** + Carr. Dim 19" wide 16" deep 10.5" high. Useable area 16" w, 10.5" h, 11.5" d. Also available **LESS PSU** with **FANS** etc. Internal dim. 19" w, 16" d, 10.5" h. **£19.95**. Carriage & insurance **£9.50**.

BUDGET RANGE VIDEO MONITORS

At a price **YOU** can afford, our range of **EX EQUIPMENT** video monitors defy competition! All are for 240v working with standard composite video input. Units are pre tested and set for up to 80 col use on **BBC micro**. Even where **MINOR** screen burns MAY exist - normal data displays are unaffected.

1000's SOLD TO DATE

- 9" **HITACHI** very compact fully cased, dim. 21cm H x 21cm W x 22cm D. Black and white screen. **£44.95**
- 12" **KGM 320-321**, high bandwidth input, will display up to 132 columns x 25 lines. Housed in attractive fully enclosed brushed alloy case. **B/W** only **£32.95** **GREEN** screen **£39.95**
- 24" **KGM** large screen black & white monitor fully enclosed in light alloy case. Ideal schools, shops, clubs etc. **ONLY £55.00**
- 14" **BRAND NEW** **Novex COLOUR** type **NC1414-CL**. Many exciting features such as **RGB TTL** and composite video input, **GREEN TEXT** key, internal speaker and audio amp. Even finished in **BBC micro** matching colours. Fully guaranteed. **ONLY £199.00**

Carriage and ins on ALL videos **£10.00**

SEMICONDUCTOR 'GRAB BAGS'

Mixed **Semis** amazing value contents include transistors, digital, linear, **IC's** triacs, diodes, bridge recs., etc. etc. All devices guaranteed brand new full spec. With manufacturer's markings, fully guaranteed. **50 + £2.95** 100 + **£5.15**

TTL 74 Series A gigantic purchase of an "across the board" range of 74 **TTL** series **IC's** enables us to offer 100+ mixed "mostly **TTL**" grab bags at a price which two or three chips in the bag would normally cost to buy. Fully guaranteed all **IC's** full spec 100 + **£6.90** 200 + **£12.30** 300 + **£19.50**

EX STOCK DEC CORNER

- BA11-MB 3.5"** Box, PSU, LTC **£385.00**
- DH11-AD 16 x RS232 DMA** interface **£2100.00**
- DLV11-J 4 x EIA** interface **£310.00**
- DUP11** Sych. Serial data i/o **£650.00**
- DZ11-B 8 line RS232** mux board **£650.00**
- LA36** Decwriter EIA or 20 ma loop **£270.00**
- LAXX-NW LA180 RS232** serial interface and buffer option **£130.00**
- LAX34-AL LA34** tractor feed **£85.00**
- MS11-JP** Unibus 32 kb Ram **£80.00**
- MS11-LB** Unibus 128 kb Ram **£450.00**
- MS11-LD** Unibus 256 kb Ram **£850.00**
- MSC4804** Qbus (Equiv MSV11-L) 256 kb **£499.00**
- PDP11/05** Cpu, Ram, i/o, etc. **£450.00**
- PDP11/40** Cpu, 124k MMU **£1850.00**
- RT11** ver. 3B documentation kit **£70.00**
- RK05-J 2.5 Mb** disk drives **£850.00**
- KLBJA PDP 8** async i/o **£175.00**
- M18E PDP 8** Bootstrap option **£75.00**
- VT50** VDU and Keyboard - current loop **£175.00**

1000's of **EX STOCK** spares for **DEC PDP8, PDP8A, PDP11** systems & peripherals. Call for details. All types of Computer equipment and spares wanted for **PROMPT CASH PAYMENT**.

DISPLAY ELECTRONICS

PROJECT: Spectrum Centronics

is stable, and the printer takes the BUSY line high when it has read the data.

Design Details

The final design is based on the Z80A parallel input/output chip. Only two other chips, IC1 and 2, are used in the interface, making it cheap and easy to construct.

The PIO has two data ports, A and B, and two control registers (one for each port). Each port can be set to either input or output (or a combination of I/O) by programming its control register (see Table 1). It was decided to make port A input, so that the BUSY signal from the printer could be monitored (bit PA0), and port B output so data could be sent to the printer. The PIO generates its own data valid, or STROBE, signal.

Address Decoding

Table 2 gives the port addresses used by Tasword Two, and if you are designing your own software, you will have to use these addresses in your software. It can be seen that there are three outputs and one input. Since we are using a Z80A PIO, the STROBE signal is automatically generated so the data output to port 59 can be ignored. Similarly, the control words for a Z80A PIO will be different from any other interface so the data output to port 127 should also be ignored.

The DATA should obviously be directed to port B on the PIO and the BUSY input from port A. The only bits of the address that vary between port addresses are A2 and A6; hence by directing all unwanted output data to port A (which is configured in input mode) the data will be ignored. This is achieved with IC2b and IC2c. We also wish to be able to program the PIO initially, so A7 is used as a control/data select. Note that A2 is used by Tasword Two so the ZX printer should be disconnected when using the interface.

Figure 1(a) gives the full circuit diagram of the interface. With Interface 1 connected, the clock output from the Spectrum is inadequate to drive the PIO directly and requires some reshaping. Figure 1(b) gives a simple waveform-shaping circuit that can be used with Interface 1.

Construction

A PCB has been designed to accommodate the interface, and this is shown in Fig. 2. This has been designed so as to be fairly small, so some care will be

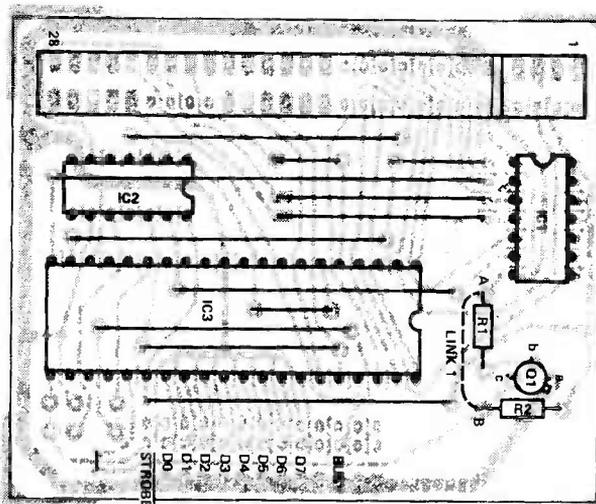



Fig. 2 PCB overlay and Spectrum edge connector details for masochists who want to design their own circuit. We haven't given full details of the printer connector, as these seem to vary; however, we hope that just about any socket will fit the board!

required when soldering! Another point to watch is that many of the links pass beneath IC1, and whether you use a socket or not, you will have to remember to insert these links before anything is soldered in the IC1 position. Components R1,2 and Q2 may be used, or the link used instead, as required.

Using the Interface

Before the interface can be used it is necessary to program the port control registers of the PIO. Port A's control register is selected when all eight address lines are high — this corresponds to port 255. From Table 1 the 'input' mode word is 4Fh or 79 decimal, hence OUT 255,79 will put port A into input mode. Similarly port B's control register is selected when all address lines except A2 are high, or port 251. From Table 1 the 'output' mode word is 0Fh or 15 decimal, hence OUT 251,15 will put port B into output mode.

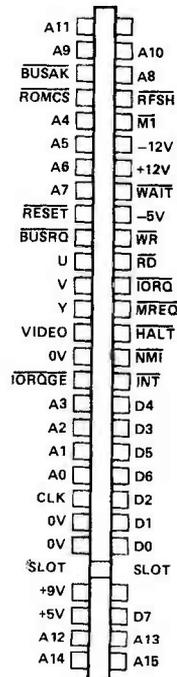The easiest way to make sure that the ports are initialised before attempting to dump a file is to incorporate the control register programming into the Tasword Two BASIC; that way it will auto-



PARTS LIST

SEMICONDUCTORS

IC1 74LS30
IC2 74LS02
IC3 Z80PIA

MISCELLANEOUS

PCB; Spectrum edge connector; connectors for Centronics printer.

ADDITIONAL PARTS FOR USE WITH INTERFACE 1

R1 2k2 ¼ W 5%
R2 470R ¼ W 5%
Q1 BC108C or BC182

run on loading and perform the necessary initialisation: first load Tasword Two and enter BASIC by pressing STOP, b and ENTER, EDIT line 10 and add OUT 255,79; OUT 251,15: to the beginning of the line, then RUN, STOP, t and ENTER to save the modified program. Any text file can now be printed out by loading the file into Tasword (if it is not already there) and using the 'print text file' option in the menu.

ETI

BUYLINES

There shouldn't be much to cause you any problems here; the PCB is available through our PCB service, and everything else is fairly easy to get hold of.

		A7	A6	A5	A4	A3	A2	A1	A0	PORT NO
STROBE	OUTPUT	0	0	1	1	1	0	1	1	59
DATA	OUTPUT	0	1	1	1	1	0	1	1	123
BUSY	INPUT	0	0	1	1	1	1	1	1	63
CONTROL	OUTPUT	0	1	1	1	1	1	1	1	127

Table 2 Ports used by Tasword Two software.

GREENWELD

— The Pack People!!

More packs — more in them — more value!
All our packs contain brand new, marked full spec components at a fraction of the normal price and offer constructors the widest range of parts at the lowest cost! How do we do it? By buying manufacturers end-of-run and surplus components. Because we have an extremely wide range of top quality parts — too costly to sort hence the packs are ideal for schools, groups or clubs.

NEW PACKS:

K524 OPTO PACK — a variety of single point and seven segment LEDs (incl. dual types) of various colours and sizes, opto isolators, numicators, multi digit gas discharge displays, photo transistors, infra red emitters and receivers. 25 assorted £3.95; 100 £14.95; 250 £35.

K525 PRESET PACK — Big, Big variety of types and sizes — submin, min and std, MP, slider, multiturn and cermet are all included. Wide range of values from 20R to 5M. 100 assorted £6.75; 1250 £12.95; 1000 £48.

K526 HEATSINK PACK — Lots of different sizes and shapes of heatsink for most diode and transistor case styles. A pack of 25 assorted including several large finned types — total weight over 1kg. £5.50 100 £19.50.

K527 HARDWARE PACK — This has a large variety of pk and self tapper screws from 2 x 1/4" up to 8 x 1 1/4" also washers, some BA, metric and Whit. screws plus other miscellaneous brackets, captive nuts and bits and pieces. 1kg (up to 1000 pieces) £4 3kg £9 10kg £25.

K528 ELECTROLYTIC PACK — All ready cropped for PCB mounting, this pack offers excellent value for money. Good range of values and voltages from 0.47uF to 1000uF, 6V to 100v. 100 £3.95; 250 £8.95; 1000 £32.

K531 PRECISION RESISTOR PACK — High quality, close tolerance R's with an extremely varied selection of values mostly 1/4 and 1/2w tolerances from 0.1% to 2% — ideal for meters, test gear etc. 250 £3 1000 £10.

K532 RELAYS — wide selection of styles voltages and contacts. 4V - 240V. 20 for £8; 100 £25.

ESTABLISHED FAVOURITES

517 TRANSISTOR PACK — 50 assorted full spec marked plastic devices PNP NPN RF AF. Type numbers include BC114 117 172 182 183 198 239 251 214 255 320 BF198 255 394 2N3904 etc etc. Retail cost £7+ Special low price £275p.

K523 RESISTOR PACK — 1000 — yes 1000 1/4 and 1/2 watt 5% hi-stab carbon film resistors with pre-formed leads for PCB mounting. Enormous range of preferred values from a few ohms to a several megaohms. Only 250p, 5000 £10 20,000 £35.

K520 SWITCH PACK — 20 different assorted switches — rocker, slide, push, rotary, toggle, micro etc. Amazing value at only 200p.

K522 COPPER CLAD BOARD — All pieces too small for our etching kits. Mostly double-sided fibreglass, 250g (approx. 110 sq. ins) for 100p.

K541 VERO OFFCUTS — It's back! Our most popular pack ever. This has been restricted for some time, but we have now built up a reasonable stock and can once again offer 100 sq. ins. of vero copper clad offcuts, average size 4 x 3". Offered at around 1/2 the price of new board 320p.

K530 100 ASSORTED POLYESTER CAPS — All new modern components, radial and axial leads. All values from 0.01 to 1uf at voltages from 63 to 1000V


K518 200 DISC CERAMIC CAPS — big variety of values and voltages from few pF to 2.2uF; 3V to 3kV £1.00.

K514 100 SILVER MICA CAPS — from 5pF to a few thousand pF. Tolerances from 1% to 10% £2.00.

K503 100 WIREWOUND RESISTORS — from 1W to 12W, with a good range of values £2.00

K505 20 ASSORTED POTENTIOMETERS — all types including single, ganged, rotary and slider £1.70.

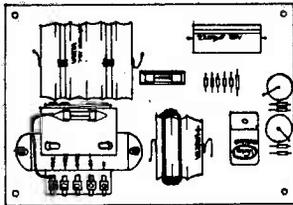W 4700 PUSH BUTTON BANKS — an assortment of latching and independent switches on banks from 2 to 7 way, DPCO to 6PCO. A total of at least 40 switches for £2.95, 100 £8.50, 250 £14.00.




NI-CAD PANEL

177 x 114mm PCB with one massive Vara Deac 57 x 50mm 0 rated 7.2V 1000mA and another smaller Deac 32 x 35mm 0 rated 3.6V 600mA. The price of these NI-cad stacks new is over £20. Also on the panel is a mains input charger transformer with two separate secondaries wired via bridge rectifiers, smoothing capacitors and a relay to the output tags. The panel weighs 1kgm. All this for just 56.00.

"TORUS"

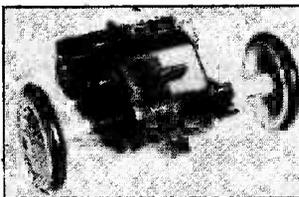An introduction to computer controlled Robots. This kit is easily assembled and utilizes the motorized gearbox described below. Further details on request.



MOTORIZED GEARBOX

These units are as used in a computerized tank, and offer the experimenter in robotics the opportunity to buy the electro-mechanical parts required in building remote controlled vehicles. The unit has 2 x 3V motors, linked to a magnetic clutch, thus enabling turning of the vehicle, and a gearbox contained within the black ABS housing, reducing the final drive speed to approx 50rpm. Data supplied with the unit showing various options of driving the motors etc. £5.95. Suitable wheels also available 79mm. Dia plastic with blue tyre, drilled to push-fit on spindle. 2 for £1.30 (limited qty). 3" dia aluminium disc 3mm thick, drilled to push-fit on spindle. 2 for 60p.

1984/5 CATALOGUE

84 page A4 size — Bigger, Brighter, Better, — more components than ever before! With each copy there's discount vouchers, Bargain List, Wholesale Discount List, Bulk Buyers List, Order Form and Reply Paid Envelope. All for just £1.00!!! (FREE to Schools etc). Winter Supplement due out November — Send large SAE for your free copy.

PANELS

Panels with assorted TTL Inc LS types. Big variety. 20 chips £1.00; 100 chips £4.00; 1000 chips £30.00.

Z904 Panel 240 x 165mm with 6 x 4099, 723 all in sockets, 14 x 8A 200V triacs, 45 small signal transistors, 14 R/C networks, 30 x IN4001, sub-min relay, R's, C's, etc. £4.95.

Z908 Panel 247 x 38mm with 2 x TDA 1004 6W audio amp IC's not soldered in! so they can easily be removed. Also 1000/16, 1000/10 x 2, 470/16 elec, ceramic discs, R's, also choke. (All easily removed) Stereo Amp? Only £3.00 (IC's cost £4 ea).

K529 RESISTORS — only for bulk buyers, these parcels have all new boxed and banded resistors. This means between 1 and 5000 of one value, so to get reasonable selection you'll need to buy 25000 or more. Most are 1/4 and 1/2w at various tolerances. Carbon, film and oxide types 25000 £28, 100,000 £90, 250,000 £200 + CARR 1 million £900 + CARR.

Ring for appointment to view, samples on request.

Newrad


NEWRAD INSTRUMENT CASES LTD

Manufacturers for the Electronics Industry

UNIT 19 · WICK INDUSTRIAL ESTATE · GORE ROAD

NEW MILTON · HANTS · BH25 6SJ

Telephone: NEW MILTON 615774/621195

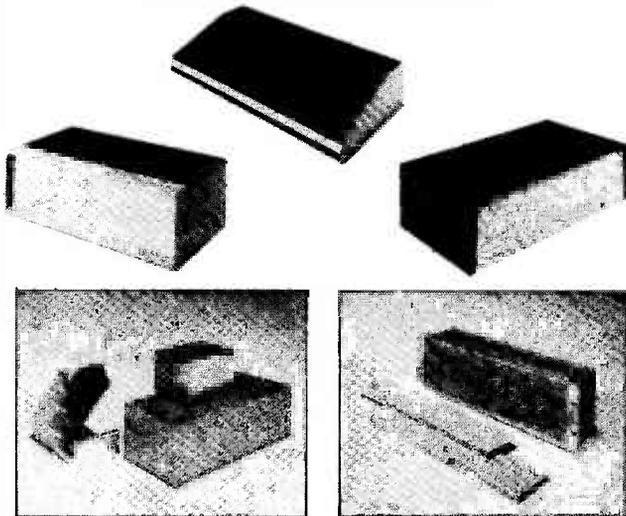

WE MANUFACTURE BEAUTIFUL ENCLOSURES

At prices you will find difficult to beat.

Alloy boxes from 80p to rack mounted units from £15 and a host of ranges and sizes in between. Well made - well finished - and all British.

Send large SAE for catalogue which includes £5 in vouchers.



"Run more than ten tasks on a ZX81-FORTH ROM?"

Sure! More than 10 tasks simultaneously and, in some cases, up to 300 times faster! That's what replacing the basic ROM with the new FORTH does for the ZX81 — and more!

The brains behind the breakthrough belong to David Husband, and he's building Skywave Software on the strength of it. Already orders are flooding in and it's easy to see why.

The ZX81-FORTH ROM gives you a totally new system. In addition to multi-tasking and split screen window capability, you can also edit a program while three or four others are executing, schedule tasks to run from 50 times a second to once a year, and with a further modification switch between FORTH and BASIC whenever you like.

The ZX81-FORTH ROM gives you a normal keyboard with a 64 character buffer and repeat, it supports the 16k, 32k, 64k RAM packs, it is fig-FORTH compatible and it supports the ZX printer.

The price, too, is almost unbelievable. As a "fit it yourself Eprom", complete with manual, it's just £25 + VAT. Add £3.45 p&p UK (£6.00 Europe, £12.00 outside Europe) and send your order to the address below.

Skywave

SOFTWARE

David Husband

73 Curzon Road, Bournemouth,

BH1 4PW, ENGLAND.

Tel: (0202) 302385.

International +44 202 302385.

ETI/22

GREENWELD

Our shop has enormous stocks of components and is open from 9-5.30 Mon-Sat. Come & see us!

Minimum Access order £5.00



443A Millbrook Road
Southampton SO1 0HX
Tel (0703) 772501/783740
ALL PRICES INCLUDE VAT
JUST ADD 60p P&P

Cortex

HARDWARE
SOFTWARE

MDEX disc O/S + BASIC £95
 MDEX Professional Dev. Sys. £275
 CORTEX POWER-BASIC disc extensions £43

MDEX Languages

ASM FORTH PASCAL SPL QBASIC META
 Software to make the CORTEX go!

Disc Drives

80 track double-sided double-density £190
 40 track single-sided double-density £120


E-BUS Floppy/Winchester Controller £135
 E-BUS 64/128 K/bytes DRAM card £145/£245
 E-BUS 9995 Processor card £145
 80*24 Character video card £48

CORTEX tapes

Space Bugs, Pontoon, Small, Breakout, Micropede,
 Pengo. each £6

Cassette Wordprocessor £13

Please add VAT to all prices.

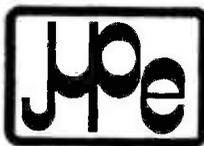

MICRO PROCESSOR ENG LTD
 21 HANLEY ROAD SHIRLEY
 SOUTHAMPTON
 SO1 5AP
 TEL: 0703 780084



ELECTROVALUE

Your SPECIALIST SUPPLIERS for
SOLDER TOOLS



From a simple 15 watt model to a precision temperature controlled iron, we stock solder irons to suit all manual requirements together with supporting stocks of bits, desolder tools, materials etc.

ANTEX

C.240 - 15W/240V;
 CS - 17W/240V
 XS - 25W/240V

Replacement bits from 3/32" to 1/4"

De-solder heads, stands, elements and handles.

ERSA

'Sprint' high speed iron: 80/150W, 240V. Heats in 10 seconds!

ORYX

Temperature controlled solder iron TC.82 45W/240 with scale.
 Oryx 50 - 50 watt temp. controlled

Standard types

Oryx 30 - 30W/240V

Viking - 27W/240V

Oryx M.3 - 17 watts, 12 volts.

A wide range of replacement tips available for all models, also tips from 0.8 to 6.4mm dia. and flat tips.

Oryx safety stand.

Oryx de-solder tool.

MINIATURE SOLDER STATION

SOLDER and DE-SOLDER BRAID

Solder in various grades.

Please mention this journal when sending for latest free illustrated A-Z list now 44 pages

BRITAIN'S LEADING QUALITY COMPONENT SUPPLIERS - SEND FOR FREE 44 PAGE A-Z LIST
 ATTRACTIVE DISCOUNTS - FREE POSTAGE - GOOD SERVICE & DELIVERY

ELECTROVALUE LTD

28 St. Judes Rd.,
 Englefield Green,
 Egham, Surrey
 TW20 0HB.

(0784) 33603; Telex 264475.
 North - 680 Burnage Lane, Manchester. 061-432 4945.
 EV Computing Shop -
 700 Burnage Lane, Manchester. 061-431 4866.

ACCESS AND
 BARCLAYCARD
 Phoned Orders
 Welcome

T.V. SOUND TUNER


SERIES II BUILT AND TESTED Complete with case. £26.50 + £2.00 p&p.

In the cut-throat world of consumer electronics, one of the questions designers apparently ponder over is "Will anyone notice if we save money by chopping this out?" In the domestic TV set, one of the first casualties seems to be the sound quality. Small speakers and no tone controls are common and all this is really quite sad, as the TV companies do their best to transmit the highest quality sound. Given this background a compact and independent TV tuner that connects direct to your Hi-Fi is a must for quality reproduction. The unit is mains-operated. This TV SOUND TUNER offers full UHF coverage with 5 pre-selected tuning controls. It can also be used in conjunction with your video recorder. Dimensions: 10 1/2" x 7 1/2" x 2 1/2". E.T.I. kit version of above without chassis, case and hardware. £16.20 plus £1.50 p&p.



Also available with built-in headphone amp. ONLY £32.50 + £2.00 p&p.

HI-FI SPEAKER BARGAINS

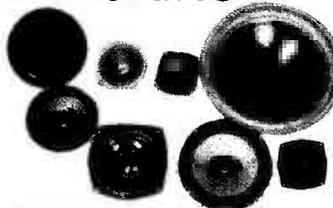

TOKUDEN - 8", 8 ohm full range 7 1/2W twin cone speaker. £3.50 + £1.10 p&p.

GOODMANS 12", 65W, impedance 4 ohms. Freq. res.: 35 - 6,500 Hz. Magnet: 1 1/2" x 4 1/2" dia. Foam surround vinyl laminated cone. For use in Hi-Fi systems up to 65 watts. Bass/Mid. £15.95 + £2.20 p&p. 7" 60W Bass/Mid. speaker. 8 ohm impedance. Freq. res.: 40 - 6,000 Hz. 4 1/2" x 1 1/2" magnet. £14.95 + £1.75 p&p.

4 1/2" 25W Bass/Mid. speaker. 4 ohm impedance. With rolled surround. £4.95 + £1.50 p&p.

Tweeters: 8 ohm soft dome radiator type. (3 1/2" sq.) For use in systems up to 40 watts. £3.95 ea. + £1 p&p. or £6.95 pr. + £1.50 p&p.

EAGLE Full range 8" 20W, 8 ohm. Twin cone with rolled surround. £6.95 + £2.20 p&p.

Full range 6 1/2" 15W, 8 ohm. Twin cone with rolled surround. £5.95 + £2.20 p&p.

Full range 4" 8W, 8 ohm. With rolled surround. £4.95 + £1.50 p&p.

125W HIGH POWER AMP MODULES

The power amp kit is a module for high power applications - disco units, guitar amplifiers, public address systems and even high power domestic systems. The unit is protected against short circuiting of the load and is safe in an open circuit condition. A large safety margin exists by use of generously rated components, result, a high powered rugged unit. The PC board is back printed, etched and ready to drill for ease of construction and the aluminium chassis is preformed and ready to use. Supplied with all parts, circuit diagrams and instructions.

Accessories: Stereo mains power supply kit with trans. £10.50 + £2 p&p. Mono: £7.50 + £2 p&p.



SPECIFICATIONS:
 Max output power (RMS): 125 W. Operating voltage (DC): 50 - 80 max. Loads: 4, 16 ohm. Frequency response measured @ 100 watts: 25Hz - 20KHz. Sensitivity for 100w, 400mV @ 47K. Typical T.H.D. @ 50 watts, 4 ohms: 0.1%. Dimensions: 205x90 and 190x36mm.

KIT £12.00 + £1.15 p&p. BUILT £17.50 + £1.15 p&p.

NICAD CHARGERS/BATTERIES



SAFT/MAZDA BATTERIES:
 RX6 (HP7/AA size) £1.10 ea. or 4 for £3.50.
 RX14 (HP11/C size) £2.45 ea. or £4.10 a pair.
 RX22 (PP3 size) 9 volt. £4.95 ea., £9.00 a pair.
 50p p&p per order on batteries.
 SAFT/MAZDA RX22 Charger (takes 2 PP3's) £2.75 + 80p p&p.
 UNIVERSAL CHARGER, takes 4 x AA's, or 4 C's or D's + 1 PP3. £5.50 + £1.40 p&p.

PAIR 10W SPEAKERS

Incorporates 4 1/2" 10 watt speaker. Finished in teak veneer simulate. Built, ready to use. Ideal extension spkrs. 1 1/2 x 7 1/2 x 4 1/4 ins. £14.95 + £1.75 p&p.

STEREO TUNER KIT

SPECIAL OFFER!
 £13.95 + £2.50 p&p.

This easy to build 3 band stereo AM/FM tuner kit is designed in conjunction with PE (July 81) For ease of construction and alignment it incorporates three Mullard modules and an I.C. IF System. Front scale size 10 1/2" x 2 1/2" approx. With diagram and instructions.

BSR RECORD DECKS

Auto-Changer model - takes up to 6 records with manual override. Supplied with stereo ceramic cartridge. £12.95 plus £1.75 p&p.
 3 speed, auto, set-down; with auto return. Fitted with viscous damped cue, tubular aluminium counter-weighted arm, fitted with ADC magnetic head. Ideally suited for home or disco use. £25.95

Manual single play record deck with auto return and cueing lever. Fitted with stereo ceramic cartridge 2 speeds with 45 rpm spindle adaptor ideally suited for home or disco. 13" x 11" approx. £14.95 plus £1.75 p&p.

MONO MIXER AMP

Ideal for halls and clubs. £45.00 + £2 p&p.
 50 Watt, six individually mixed inputs for 2 pickups (Cer. or mag), 2 moving coil microphones and 2 auxiliary for tape tuner, organs etc. Eight slider controls - 6 for level and 2 for master bass and treble, 4 extra treble controls for mic. and aux. inputs. Size: 13 1/2" x 6 1/2" x 3 3/4" app. Power output 50 W RMS (cont.) for use with 4 to 8 ohm speakers. Attractive black vinyl case with matching fascia and knobs. Ready to use.

All mail to: 21E HIGH ST, ACTON W3 6NG.
 Callers: Mon - Sat 9.30 - 5.30. Half day Wed.
 Access phone orders on 01-992 8430.
 Note: Goods despatched to U.K. postal addresses only. All items subject to availability. Prices correct at 31/9/84 and subject to change without notice. Please allow 14 working days from receipt of order for despatch. RTVC Limited reserve the right to update their products without notice. All enquiries send S.A.E. Telephone or mail orders by ACCESS welcome.

CALLERS TO: 323 EDGWARE ROAD, LONDON W2. Telephone: 01-723 8432. (5 minutes walk from Edgware Road Tube Station) Now open 6 days a week 9 - 5.30. Prices include VAT.



DIGITAL FRAMESTORE

This project definitely rates the tag 'experimental'; and with the necessary ADC at around £100, and 48 64K DRAMs included, it isn't going to be cheap either! However, we think that our readers will be interested in the techniques involved. Design by Daniel Ogilvie.

A framestore is a device that can capture an entire image from a TV screen and freeze it electronically. The captured image can then be manipulated or combined with or compared to others.

Using a framestore, one TV camera could be used to fade between two images; one would be captured on the framestore, then the TV camera pointed at the second. A video mixer would be used to fade from one image to the other. More complex effects could be achieved by using the same image for both, with minor changes or manipulations between the two images.

Storage of the image can be synchronised with one-off events;

for example, it could be synchronised with a flash gun going off; the flash is synchronised to occur during the field blanking (fly-back) time and the resultant image is read into the store on the next frame scan.

A technique known as target integration can be used; here the electron beam in the camera is shut off and a faint image is built up over a period of time on the target, then the beam is turned back on again to read it into the framestore. This is similar to long exposure photography — and uses of this include astronomy.

In the design described here, the image is stored in digital form, which makes it possible to analyse or manipulate the picture using a

home computer; this will be discussed at length in a future article.


Camera tubes are available which can see into the infra red or the ultra violet, which enables us to extend our view of the world beyond conventional visible optics. For example, finger prints can be viewed under UV light, stored in the framestore, enhanced by computer and then compared with a library of finger prints for a match. Also, inks can be made to be luminous in the infrared making it possible to check for cheque or passport forgeries.

Some Television Fundamentals


Most readers will be familiar with the conventional television system used in this country which is raster scanned. The information on the brightness of the camera lense's field of view is encoded in a serial form and superimposed on synchronizing pulses which enable it to be easily recovered. Looking at your television screen, the trace starts at the top left hand corner and moves across horizontally until it reaches top right where it resets back to the left, a little bit down, and scans across again.

The time taken for the horizontal line scan is $64\mu\text{s}$ and this is known as the line period. The line scan is performed $312\frac{1}{2}$ times, until the trace reaches the bottom of the screen when it returns to the middle top of the screen. The trace performs a further $312\frac{1}{2}$ line scans, filling in the gaps between the first $312\frac{1}{2}$ line scans, see Fig. 1.

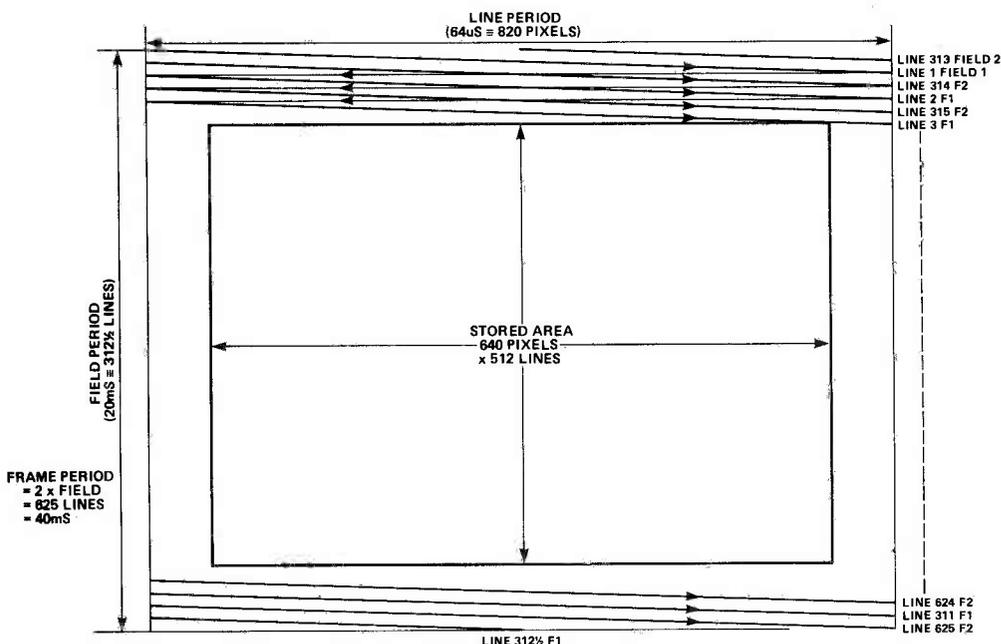Each set of $312\frac{1}{2}$ line scans is called a *field* and requires $312\frac{1}{2} \times$



CONTROL CARD

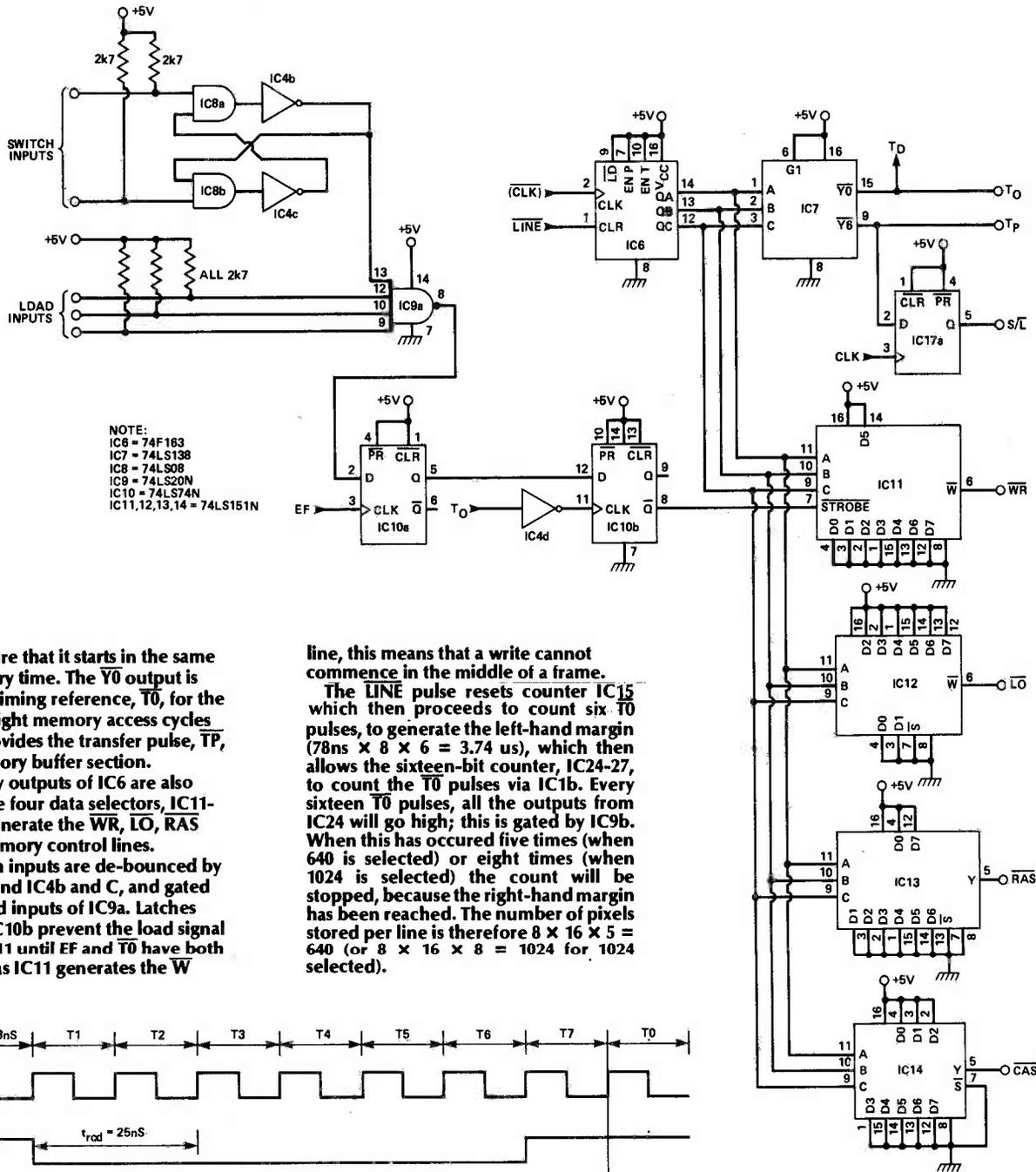


LINE to ensure that it starts in the same position every time. The **Y0** output is used as the timing reference, **T0**, for the first of the eight memory access cycles while **Y6** provides the transfer pulse, **TP**, for the memory buffer section.

The binary outputs of IC6 are also used to drive four data selectors, IC11-14, which generate the **WR**, **LO**, **RAS** and **CAS** memory control lines.

The switch inputs are de-bounced by IC8a and b and IC4b and C, and gated with the load inputs of IC9a. Latches IC10a and IC10b prevent the load signal reaching IC11 until EF and **T0** have both gone high; as IC11 generates the **W**

line, this means that a write cannot commence in the middle of a frame.

The **LINE** pulse resets counter IC15 which then proceeds to count six **T0** pulses, to generate the left-hand margin ($78\text{ns} \times 8 \times 6 = 3.74 \text{ us}$), which then allows the sixteen-bit counter, IC24-27, to count the **T0** pulses via IC1b. Every sixteen **T0** pulses, all the outputs from IC24 will go high; this is gated by IC9b. When this has occurred five times (when 640 is selected) or eight times (when 1024 is selected) the count will be stopped, because the right-hand margin has been reached. The number of pixels stored per line is therefore $8 \times 16 \times 5 = 640$ (or $8 \times 16 \times 8 = 1024$ for 1024 selected).

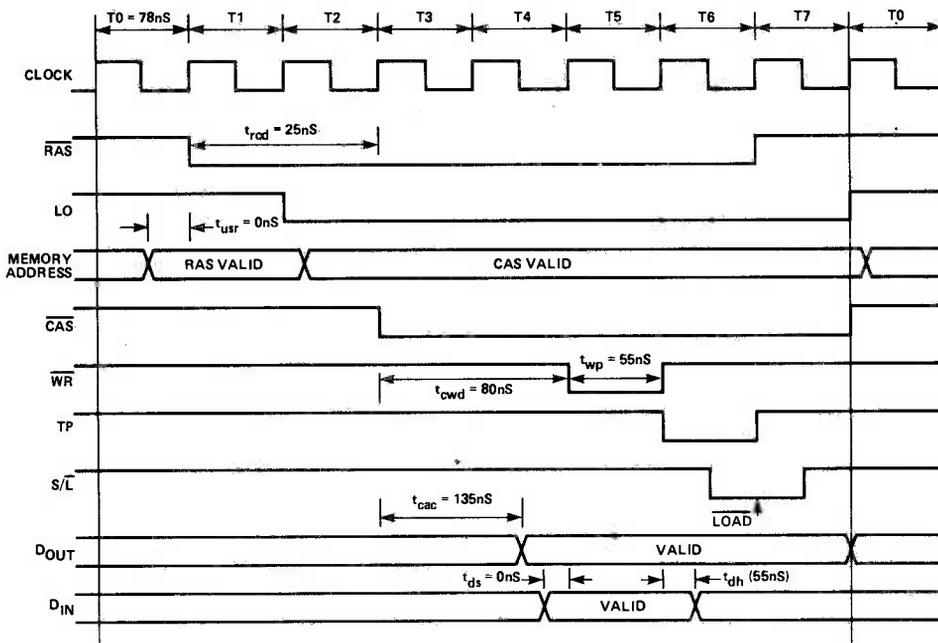

The top and bottom margins are generated by IC20 and 21, which count the **LINE** pulses; when 32 line pulses have occurred, the flip-flop IC17b is cleared via IC18c; this takes its Q output high, allowing IC18a output to go low, so that **T0** pulses can pass through IC16b and be counted; so the address counters can only increment while IC17b remains cleared. Decoders IC 26 and 27 monitor the top four address lines to provide a line counter. When the counters reach $4 \times 4906 \times 8 / 640$ counts = 256 lines the **Y4** output of IC26 clocks IC17b via IC8d which sets this latch and halts the count until the 32 lines of the second field have elapsed when IC27 performs similarly ($9 \times 4096 \times 8 / 640$ counts = 512 lines). The counters are reset by the EF (even field) pulse which indicates the start of the new frame.

64 μ s = 20ms to be completed. The two fields are related in that the information in the second field augments the information in the first. The two fields together are called a frame and this requires 2x20ms = 40ms to be completed.

The two fields are said to be *interlaced*. The reason for this interlace is to provide a fast enough screen refresh rate without just resorting to sending the information faster which would result in the need for a higher bandwidth.

The Video Waveforms

As I have already mentioned, the information broadcast is superimposed on synchronizing pulses, which indicate where the top and left of the screen are. A typical video waveform is shown in Fig. 2, which shows line synchronizing pulses. Each pulse initiates a flyback of the trace across the screen from right to left ready for the next line of information. The field pulses caused the trace to reset to the top left of the screen and initiated the slower vertical scan downwards which ensures each line appears below the previous one.


The video waveform superimposed on the sync pulse represents the brightness of the scene. The higher the voltage at any particular point in the waveform, the whiter the corresponding point on the screen. The set-up voltage is defined as black and is about 45mv above the 'back porch' of the line waveform (see Fig. 2.). The sync pulses are, therefore notionally, darker than black and this ensures that the flyback is not visible on the screen. We derive a pulse during the period of the back porch to clamp the incoming video to black to ensure we obtain a stable grey scale to our stored picture.

There are a number of other features regarding the video waveform that will concern us, but we will deal with these as we need to.

We are concerned with the storage of one frame of this information. The method we shall use is to convert the TV screen into little packets of information and store them into a digital memory as values representing the brightness of the scene.

Memory Needs

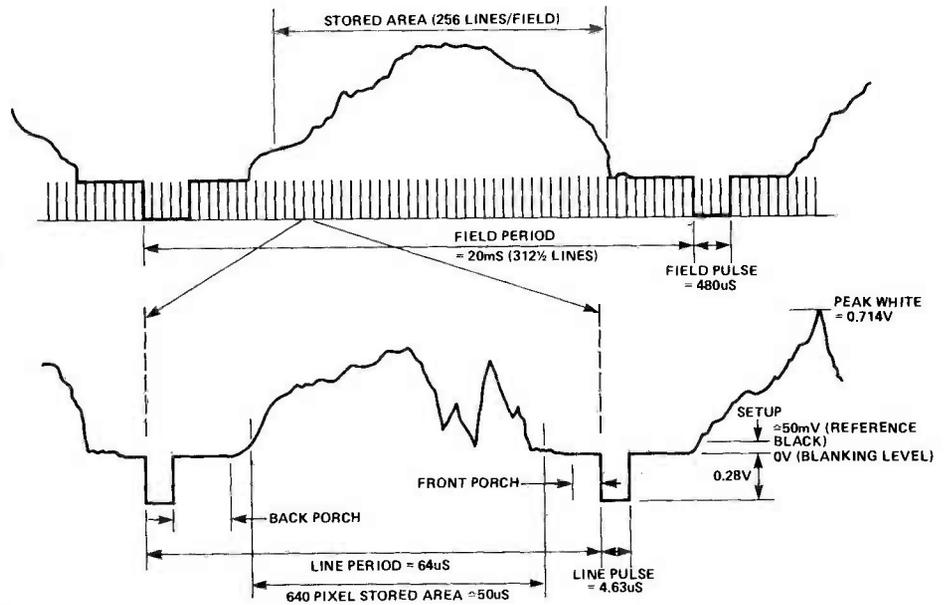With 625 lines to store, if we stored only one byte representing the average brightness across each line, we would require 625 bytes of



memory. Obviously this is not very representative of the scene we may be looking at.

Well, let's store 625 values across the line and see what that requires, assuming that each value stored will be in the form of an eight-bit byte. We now need enough memory to store 625 lines of 625 elements (the elements are called *pixels*); this requires 625² bytes, ie 390,625 bytes: rather a lot!

There is an additional consideration. The line duration is 64 μ s, and we want to break this up into 625 pixels which means we have only 64 μ s/625 = 120ns to convert the video into a digital word and store it.

Looking at the sync waveforms again we can see that there is a left and right, top and bottom margin to the screen. Storing the video waveform from these parts of the screen is a waste because there is very little useful information there. It is at the extremes of linearity of the camera scans, the lense and the television screen. We would lose little by storing only the 512 central lines.

Similarly the line scans contain little of use at the edges, so we need only store the central section of the lines. The screen is wider than it is deep (it has a 4:3 aspect ratio), so to maintain a similar horizontal resolution to the vertical resolution, we will need to store more than the 512, say around the 625 pixels first envisaged. Actually, the generation of the clock signals is eased considerably by prudent choice of numbers (you'll have probably already noticed the 512 lines!), and in practice it was found


that 640 pixels stored across a nominal total line length of 820 pixels (much of the residue being taken up with sync and fly-back) worked out reasonably neatly. Putting these numbers together, we arrive at a memory store requirement of 640 x 512 = 327,680 bytes.

The memory requirement has been reduced to some extent, but we have increased the speed requirement of the A-to-D converter and of the memory. This is unfortunate because speed is costly in both these areas. It also makes the design of the timing and control logic more critical. The conversion and storage of each pixel will have to take place in 64 μ s/820 = 78 ns.

It's Been Framed!

A block diagram of the whole system is shown in Fig. 3. The crystal clock generates the pixel clock rate — which is our highest frequency. We require 820 pixels across a line which gives us a crystal frequency of 1/64 μ s x 820 or 12.81225MHz. We generate twice this, (25.625MHz) to ensure an even square wave master clock waveform. This is sent through the lower address counters which divide the 12.8125MHz by 820 and generate a binary address for the memory. The output from this counter will be at line frequency; the left and right margins are also generated by these counters.

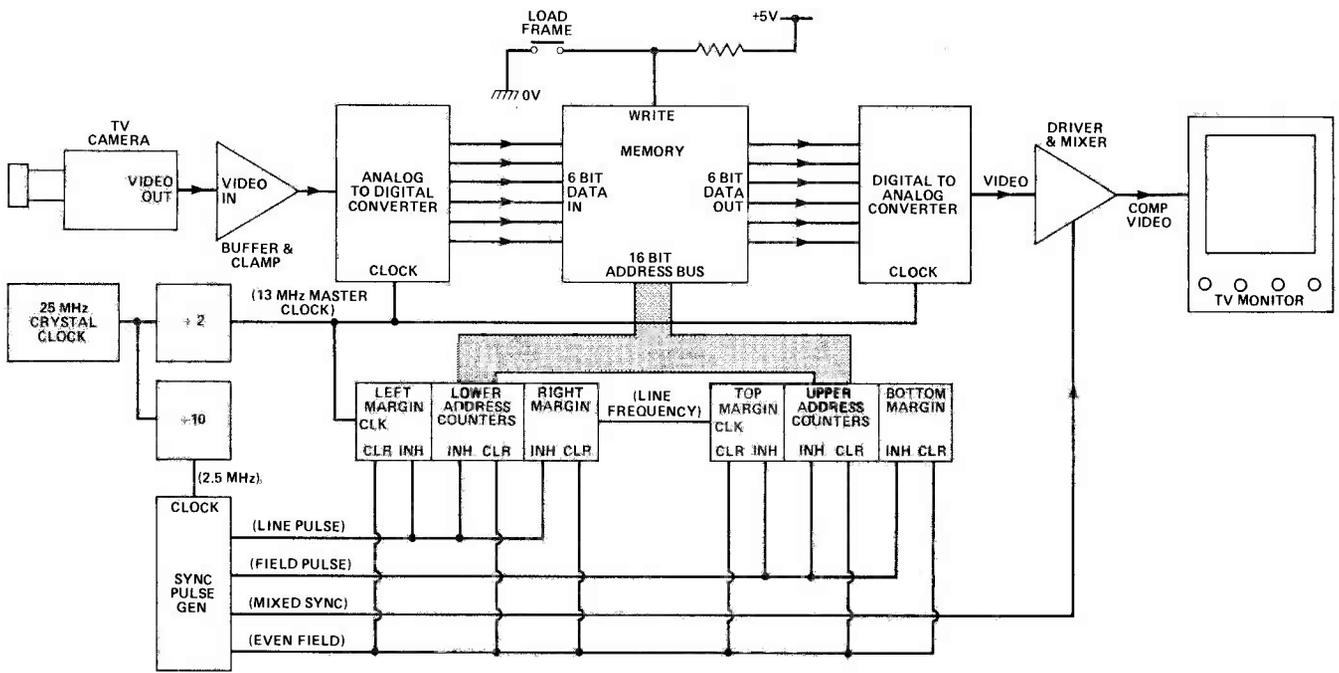The line frequency is fed to the upper address counters which divide the line frequency by 625 to provide the upper address lines to the memory, and also generate the top and bottom margins. At the



end of a frame the address counters are reset by the sync pulse generator and the process continues again.

Most of the time, we will be using the framestore to read out of memory; while this is happening, data is being sent from the memory to the DAC for conversion back to

analogue and, after mixing with synchronising pulses, display on the monitor.


To store video, from, for example, a video camera, the write line on the memory is held down for the duration of one frame, while the input signal is converted by the ADC. As already mentioned,

the ADC will be converting at a rate of 12.8125MHz.

To be completed next month.

ETI

AMPLIFIERS

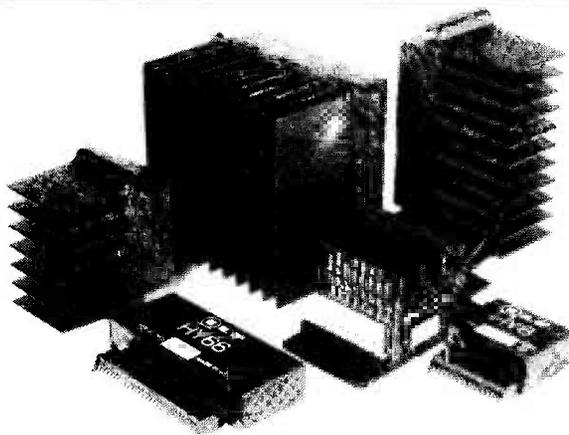

WHY ILP? Years of experience in audio, unique designs, world wide sales and outlets, reliable delivery and friendly service.....

BIPOLAR MODULES

Ideal for Hi Fi, Full load line protection integral Heatsink, slew rate 15v/μs

Distortion less than 0.01%

Type	Output Power Watts (rms)	Load Impedance Ω	Price	Type	Output Power Watts (rms)	Load Impedance Ω	Price
HY30	15	4-8	£8.45	HY244	120	4	£26.95
HY60	30	4-8	£9.95	HY248	120	8	£26.95
HY6060	30 + 30	4-8	£19.45	HY364	180	4	£39.95
HY124	60	4	£20.95	HY368	180	8	£39.95
HY128	60	8	£20.95				

MOSFET MODULES

Ideal for Disco's, public address and applications with complex loads (line transformers etc.). Integral Heatsink slew rate 20v/μs distortion less than 0.01%

Type	Output Power Watts (rms)	Load Impedance Ω	Price	Type	Output Power Watts (rms)	Load Impedance Ω	Price
MOS128	60	4-8	£30.45	MOS364	180	4	£45.95
MOS248	120	4-8	£39.95				

PREAMPLIFIER MODULES

All modules are supplied with in line connectors but require potentiometers, switches etc. If used with our power amps they are powered from the appropriate Power Supply.

Type	Application	Functions	Price
HY6	Mono Pre Amp	Full Hi Fi facilities	£7.95
HY66	Stereo Pre-Amp	Full Hi Fi facilities	£14.95
HY73	Guitar Pre-Amp	Two Guitars plus Microphone	£15.95
HY78	Stereo Pre-Amp	As HY66 less tone controls	£14.45

MOUNTING BOARDS: For ease of construction we recommend the B6 for HY6 £0.95 B66 for HY66-78 £1.45.

POWER SUPPLY UNITS


Type	For Use With	Price	Type	For Use With	Price
PSU212	1 or 2 HY30	£11.95	PSU542	1 HY248	£17.95
PSU412	1 or 2 HY60, 1 HY6060, 1 HY124	£13.95	PSU552	1 MOS248	£19.95
PSU422	1 HY128	£15.95	PSU712	2 HY244	£21.95
PSU432	1 MOS128	£16.95	PSU722	2 HY248	£22.95
PSU512	2 HY128, 1 HY244	£17.45	PSU732	1 HY364	£22.95
PSU522	2 HY124	£17.45	PSU742	1 HY368	£24.45
PSU532	2 MOS128	£17.95	PSU752	2 MOS248, 1 MOS368	£24.45

All the above are for 240v operation.

FOR FREE DATA PACK PLEASE WRITE TO OUR SALES DEPT.


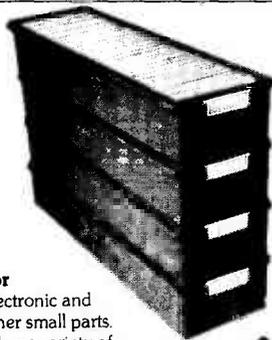
Post to: ILP Electronics Ltd., Dept. 6
Graham Bell House, Roper Close,
Canterbury, Kent. CT2 7EP
Tel: (0227) 54778 Telex: 965780





Component

MINIFILE

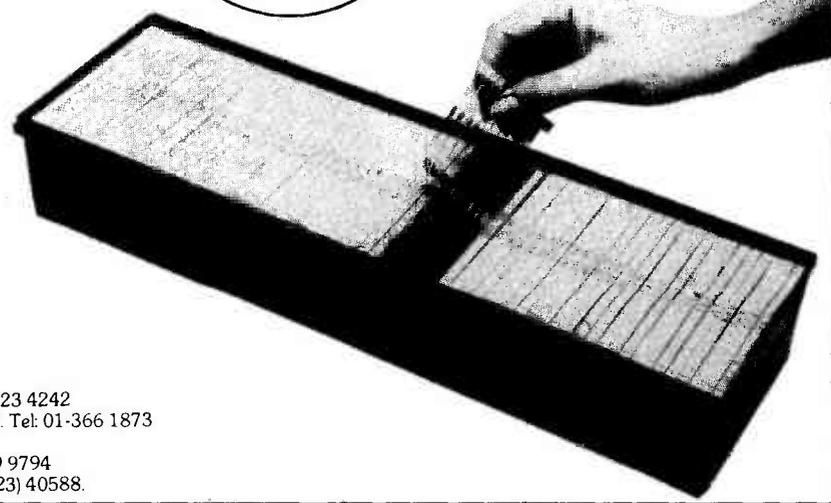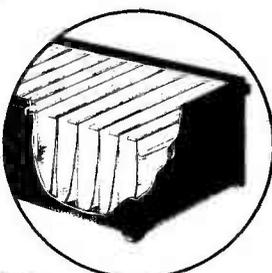

For
Electronic and other small parts. A large variety of components can easily be kept well organized. 60 storage pockets per unit.

Unit size:
L400 W125 H77mm.

Material: Injection-moulded in impact resistant polystyrene. 4 and 6 Drawer Steel cabinets available.

The 6 Drawer cabinet, practical for field service, has lock and carrying handle.

Recommended prices (excluding V.A.T.):

- 6 drawer cabinet with lock and handle £92.00
- 4 drawer cabinet with lock and handle £59.00
- Single drawer £11.00

Typical Minifile applications:

- R & D Departments Prototype Kits
- Production Test & Rework Service Departments
- Field Service Engineers The Electronic Hobbyist
- Repair kits for computers CNC-machines.

Stocked by:

- Bradley Marshall, 325 Edgware Road, London W2 1BN. Tel: 01-723 4242
- Enfield Electronics, 208 Baker Street, Enfield, Middlesex EN1 3JY. Tel: 01-366 1873
- Henry's, 404-406 Edgware Road, London W2. Tel: 01-724 0323
- TK Electronics, 11-13 Boston Road, London W7 3SJ. Tel: 01-579 9794
- Watford Electronics, 33/34 Cardiff Road, Watford, Herts. Tel: (0923) 40588.



Abbots Hill Chambers
1st Floor, Gower Street,
Derby DE1 1SD

Tel: Derby 0332/382433

Modules	Power RMS	Load	Volt Max	Size (mm)	Price
RVM150S	70-150W	4-8	±60	31x80x100	1+23.50 10+19.98 20+19.80
RVM300S	120-300W	4-8	±65	31x102x136	1+32.87 10+27.94 20+26.30
RVM400S	170-400W	4-8	±65	47x89x136	40.92
RVM700S	300-700W	2-8	±70	47x90x197	60.96
RVM700S Mounted on Heat Sink					70.40

KIT PRICE

RVM150S	1+19.50	10+15.98	20+15.80
RVM300S	1+28.87	10+23.94	10+22.30

MAIL ORDER ONLY

RVM RANGE OF POWER MOSFET AMPLIFIER MODULES. These Power Mosfet Modules are very reliable, driving difficult loads is no problem. Application from hi power systems to studio to domestic hi-fi.

All of our modules are built and tested and carry a 2 year guarantee.

We also supply a range of heat sinks, specially recommended for RVM modules.

*All prices include post & packing.
(Quantity discount available)*

To order send cash with order, or cheque/postal order.

Delivery on our Modules and Heat Sink or same day dispatch when order is received with cash, allow 7 days with cheque or postal order.

MICRORANGE ELECTRONICS

UNIT 258, STRATFORD WORKSHOPS, BURFORD ROAD (near Stratford Centre)
LONDON E15 2SP. TEL: 01-536 1415

Recently opened component shop in the heart of Stratford, we have lots of special offers. (You will find us on the 2nd Floor.)

We specialize in the manufacture of:

Printed Circuit Boards
No quantity is too small.
We also supply:
Photo Board and associated chemicals at very keen prices.
See below:

- 6x4" Single sided 1.80
- 8x5" Single sided 2.10
- 6x4" Double sided 2.00
- 8x5 Double sided 2.40
- Other sizes available

ALL PRICES INCLUDE VAT
Please add 50p for P&P

SOME SPECIAL OFFERS
(Many others in stock)

- NE5534 1 off 1.15 10 off 1.05
- NE5532 1 off 1.45 10 off 1.15
- TL071 1 off 45p 10 off 42p
- TL072 1 off 55p 10 off 50p
- TL074 1 off 85p 10 off 78p
- 78P05 5V 10A Reg 5.50 each
- 7812 12V 1A Reg 30p each
- VN67AF Power Fet 65p each
- 60W Spot Bulbs various colours 70p each
- 100W Spot Bulbs various colours 1.25 each
- 2 metre x 1 metre SPK Cloth 2.95
- 10x12" Fibreglass PC Board 2.25 each
- 150W Power amp module 12.50
- 3 Way 700W Sound to Lite unit 17.50
- Telephone recording unit 15.00

Please come and see our range

Please mention
E.T.I.
when replying
to all
adverts

READ/WRITE

Standing Physics On Its Head

Dear Sir,

It is a well-known mathematical paradox that a perfect low-pass filter must begin to react to a pulse on its input before that pulse is applied. However, this piece of mathematics has eluded physical realisation — until now. Look at the oscillogram you display in your review of the Bridage scopes in the September ETI. The bottom trace clearly shows the SB121 overshoot-ing before every edge of the square wave input.

There would be many applica-tions for a circuit which detects pulses before they happen. Clicks could be removed from audio recordings without using a delay-line buffer. Delicate equipment could be protected from mains surges. Digital circuit designers need no longer worry about clock skew — just insert a few endo-chronous filters into the longer signal paths. But the most obvious use is in oscilloscopes themselves: a predictive trigger to capture those intermittent events which conventional trigger circuits cannot handle. The absence of such a documented feature from the scopes under review suggests that it is an accidental phenomenon which has gone unnoticed by the manufacturers. Perhaps one of their component suppliers is making his capacitors out of resub-limited thiotimolines?

Yours faithfully,
Richard Kennaway
Norwich

Fascinating as the possibilities outlined by Mr. Kennaway are, we have succeeded in tracking down the source of this phenomenon and found the problem to be a surprisingly simple one — our photographer was holding his camera upside down!

The One That Got Away

Dear Sirs,

I refer to your article in ETI of June 1984 in the Digest section, concerning a new battery developed by Matsushita and marketed by Panasonic UK Limited. This is the BR 211 Lithium battery.

As an angler, not an electronics follower, this item interested me very much from the point of view of illuminating fish-rod tips, with

which I have been experimenting for several years now. Also, as press officer of the Bournemouth based BAC Angling Club, my experiments are of interest to a good number of local anglers.

With this in mind, I wrote to Panasonic UK Ltd enclosing details, drawings and observations, regarding my strugglings with batteries and LEDs etc, and enquiring where I may track down a supplier of their advertised battery. This letter was sent at the end of May this year.

Since we are now well into August, I feel it is fair to assume that I am not likely to receive a reply or even acknowledgement from Panasonic UK Ltd. I wonder if you could help. I am no longer concerned whether they are interested in my dabbings or not, but I would like to know where to buy 'The World's Smallest Battery' as it was described. Perhaps it is so small that nobody can find it?

Yours faithfully,
Martin Hursthouse
Bournemouth

We telephoned Panasonic UK but no-one there seemed to know much about the BR211. They passed us on to Panasonic Industrial, who told us that the information we published must have come directly from the Japanese arm of the company. There are plans to distribute the BR211 in this country but no agents have yet been appointed and it is unlikely to be available before the beginning of next year at the earliest. In addition, because they are concerned only with industrial electronics, Panasonic Industrial were unable to assure us that the agents appointed would include a company prepared to sell directly to the public in small quantities. We can only suggest that you drum up as much support in the angling world (and elsewhere) as you can and keep lobbying Panasonic — if it becomes clear to them that there really is a demand for the BR211 in the domestic market they may feel encouraged to appoint a suitable distributor as quickly as possible.

Beating The Common Code

Dear Sir,

I have recently purchased and installed a home security system

that you reviewed in the July 1984 issue of ETI. The article was entitled 'Housewatch 2000 Burglar Alarm' (page 50) and featured the Coloroll Ltd/Munford & White Control Panel.

I have therefore been in a position to practice button pushing on the control panel and have found a serious fault in the ULA that comprises the system security. It is possible, with the panel in the Day condition where it can be operated by any person or villain, to find out the 4 digit control code within 2 minutes and without tampering with the unit in any way. The average time to crack the code is only 1 minute.

I have written the method on a separate sheet which is in a form that I present to visitors to play at code-cracking when they visit the house.

Yours sincerely,
M. Brandligt
Oxford

Whilst we agree that it is quite easy to find the code of the alarm when it is in the 'day' state, this doesn't actually affect the security of the alarm. Let's look at the arithmetic.

With the alarm in the 'day' state, there are nine possible first digits in the code and eight possible second digits making a total of $9 \times 8 = 72$ combinations, only one of which will put the alarm into its test state.

To get the alarm out of the test state there are seven possible first digits (the third digit of the full code) and six possible second digits, making a total of $7 \times 6 = 42$ possible combinations.

It is relatively easy to find this code provided:

- 1) you know how the alarm operates in the first place — a clever, professional thief will have done his or her homework, but aren't the majority of domestic break-ins the work of opportunist amateurs?
- 2) you are allowed to play with the alarm in the 'day' state.

It is on this second point that your argument falls down. If the alarm is armed, the thief will have to find the full four-digit code in one go. There are $9 \times 8 \times 7 \times 6 = 3024$ possible combinations, far more than a thief could hope to try in the twenty-five seconds allowed after arriving through the entry-zone, and if a thief gets in by some other route the alarm will go off immediately anyway. We think your home is secure — unless any of your

invited visitors return later, uninvited!

Of course, if you do suffer a break-in at a time when the alarm is un-armed, it would be sensible to change the code as well as changing all the locks. However, changing the code is very straightforward.

Disc-usted

Dear Sir,

I have been reading Linsley Hood's articles on audio amplifiers for many years and good as his latest design is I don't think I will be making it. He seems not to have heard of the Compact Disc.

Yours Truly,
B.A. Thacker
Crewe

Although this was not brought out in the series of articles, the design was produced with Compact Disc very much in mind. This is one of the reasons why the volume and balance controls have been placed in the power amplifier rather than the pre-amplifier and why that unit has been provided with an unusually sensitive and high-impedance input. Signals from Compact Disc units can thus be fed directly into the power amplifier without having to pass through unnecessary connectors, switching, and signal handling stages in the pre-amplifier. This being so, the Audio Design amplifier is probably better suited for use with Compact Disc players than almost any other amplifier around.

Tip Of The Iceberg

Dear Sir,

I hope you have a few minutes to spare, because I am about to relate the Saga of the Missing Tech-Tip.

Once upon a time (14/1/84) an intrepid ETI reader (me) sent what he thought was a rather elegant piece of software to the Mighty ETI Tech-Tips Feature. His idea was a program to read resistor colour codes using the Casio fx-180P calculator. The reader waited, with bated breath (he had run out of Polo mints) for a reply from ETI. He waited for three months, and then wrote to ETI again, along the lines of "Oi, mush, wot's happened to me software?" or words to that effect.

Still no reply having plopped on his doormat (it wasn't house-trained) by the middle of June '84, he was prompted to write again. Which is why he is now writing to Heap Big Boss Man of ETI.

I think it's safe to assume that my design has gone astray, encountered a time warp or been half-inched by the Vogons (remember them?). If you could write and reassure me that two-way communication via letter is still possible, I would be much obliged. I would also be pleased to re-submit the design, assuming that it doesn't turn up in the ETI offices.

I look forward to hearing from you (please).

Yours Faithfully,
Ronald Hutchison
(State Registered ETI Reader)
West Kilbride

Sadly, Mr. Hutchison is not the only reader to have experienced this upsetting phenomenon of Tech Tips apparently vanishing into the fourth dimension (otherwise known as the ETI filing system). We hope that he and the others affected will accept our apologies and the following explanation.

The problems with the Tech Tips feature arose partly because of its success. We have had so many sent to us that we now have two bulging files full and contributions are still arriving at the rate of a dozen or so a month. This flood of items has coincided with a period during which we have frequently not had enough space to put all the things we wanted to

in the magazine, and Tech Tips has often been left out to make room for other articles. Not having the staff to cope with the filing necessary to keep such a large number of contributions in order, the whole system has become rather disorganised and letters querying the whereabouts of particular Tech Tips have all too often vanished themselves!

Rather belatedly we have got around to doing something about all this. The Tech Tips special in this issue marks our first assault on the ever-growing file and we intend to include the feature on a far more regular basis from now on. Mr. Hutchison may also like to note that his program is amongst the items featured.

We will also be looking closely at the conditions under which Tech Tips are accepted to see if they can be tightened-up slightly. It would obviously be better to reject a few more items in the first place than to have them on-file for months, being considered and then rejected.

In the meantime, why not consider if your Tech Tip could actually be a project. We do quite often ask readers to re-vamp their ideas because they are substantial enough to be full-blown projects, and we and our sister magazines, Electronics Monthly and Digital and Micro Electronics, are always looking for good projects.



YES MR QUIGLEY, YOUR 'TECH-TIP' FOR THE BUILDING OF A TWENTY MILE DIAMETER ANTI-MATTER PARTICLE ACCELERATOR WITH NUCLEAR FUSION CHAMBER AND GRAVITATION DEFLECTION STORAGE RING HAS INDEED BEEN RECEIVED!

ETI

electronics today

INTERNATIONAL

NEXT
MONTH

The MC6804 P2

Remember our article on Motorola's MC68020, the world's first true 32-bit micro (depending on what definition of a 'true' 32-bit micro you adopt)? Well, Motorola have been busy at the other end of the scale, with a four-bit micro too. A sequel to the story of its bigger brother, we'll be taking a little look at the world of the Micro-microprocessor — and its one device that could well find itself used quite heavily by hobbyists in the none-too-distant future.

Active Bass Speaker


Just in case you might have got the impression that all the next issue will be features, here's a project for you. Mind you, your neighbours may well sink to bribing your newspaper deliverer to hang onto your copy of ETI, because this sub-resonant speaker should certainly rattle a few walls and floor-boards!

Readers' Survey

The time to seek your opinions has rolled around once again, with the added bonus of the possibility of winning a year's subscription.

Distortion Meter

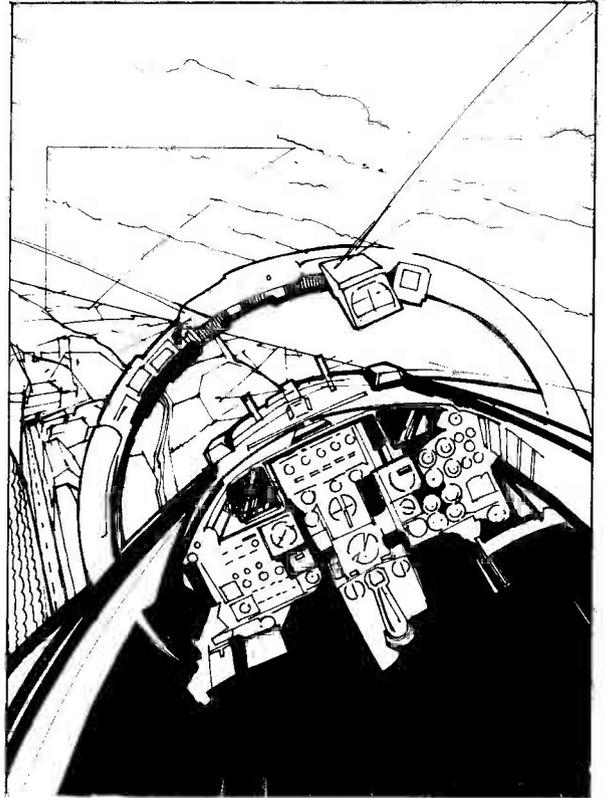Well, this item got squeezed out of this issue, for which we apologise, there just wasn't room to get in everything we wanted to get in. However, we promise, cross our pulse generators and hope to die, that it will be in the next issue.



IS ELECTRONICS RELIABLE?

There are a number of question marks over the performance and reliability of electronics, not a few of which have turned up in ETI projects! The space shuttle fails to get off the ground. An IC will not work within its specifications, and duplicates also fail to work. The Nimrod 'eye in the sky' radar system won't work as it was designed to do and is sent nearly all the way back to the drawing board. A leading semiconductor company admits that many of its ICs have not been properly tested, and initiates a hastily assembled crash testing programme. Anyone who reads the electronics trade press will have seen these stories; next month's ETI will attempt to get them in perspective.

ALL THIS AND MORE IN THE NEXT ISSUE OF ETI. RESERVE YOUR COPY OF THE JANUARY ISSUE NOW!

All the articles listed above are at a late stage of decay in the Editor's in tray. However, the availability of space and other factors beyond our control (like the Assistant Editor being strangled by an innocent passer-by after one of his appalling puns) may limit our ability to bring them to you.

Lot No.	Description	Qty.	Price Excluding VAT	Lot No.	Description	Qty.	Price Excluding VAT	Lot No.	Description	Qty.	Price Excluding VAT
1	H.P. SHF Signal Generators Type 420A/420B/420A	3	£340	51	Teletest Oscilloscope Type D43R	1	£150	101	Co-ax Cable Type Ultracord M412	300	£100
2	Schomandl Waveformers Type FDI with converters	2	£60	52	Radiometer Signal Generator Type M 27g	2	£330	102	Tektronix Oscilloscope Type 551 C/W Plug Ins & Trolley	1	£90
3	EH Research Labs Pulse Generator Type 139MB	1	£60	53	Coulter Power Unit 7A 12V 12V 12V 12V 4V 3A 24V 7A	1	£40	103	Rhode & Schwartz Microwave Power Meter Type BW242	1	£40
4	H.P. Rn Meter Type 220B	1	£150	54	Marconi 100 Watt 70db Attenuator Type 1P2580	1	£150	104	Marconi Microwave Sweep Oscillator Type 6000A	1	£120
5	Alrmec Millivoltmeter Type 301A	3	£150	55	H.P. DC Power Supply 0-40V 3 amp	1	£200	105	Marconi Signal Generator Type 1P955A	1	£60
6	Alrmec Millivoltmeter Type 301	3	£60	56	H.P. VVM Model 40D	2	£50	106	Schomandl Modulator Model 1962	1	£150
7	Data Dynamics Terminal	1	£20	57	Jenold Field Strength Meter Model T 7048	1	£60	107	Schomandl Decade Sig. Gen. 300-100KHz Type NDRDM	1	£250
8	Marconi Timebase Delay Generator Type TF1415	1	£20	58	Marconi Universal Bridge Type TF 868A	2	£120	108	Rhode & Schwartz Decade Signal Gen. Type BNH104	1	£250
9	Marconi FM/AM Modulation Meter Type 1P2300	1	£275	59	Marconi Standard Signal Generator Type TF 867	2	£60	109	Teletest Oscilloscope Type 552	4	£150
10	AIM Electronics Variable Function Generator	1	£45	60	Alrmec Sweep Signal Generator Type 352	1	£40	110	Marconi AM Signal Generator Type TF 801D/85	1	£75
11	Pye VHF Signal Generator Type 552V	1	£100	61	Solatron Digital Voltmeter Type LM 1420 2	1	£40	111	Marconi VHF Signal Generator Type TF 1004B/6M	1	£150
12	Pye HF Transceiver 6 channel Type 558130	1	£150	62	Marconi Program FM/AM Mod. Meter Type 1P2001A	1	£150	112	Marconi Universal Bridge Type TF 868B	2	£75
13	Pye Signal Generator Type 555U	1	£150	63	Marconi Programmable VCF Attenuator Type TF 2168	1	£50	113	Marconi Tr & Rx Output Test Set Type TF 1005	2	£95
14	Pye Battery Charger Type TCO 9 volt	95	£40	64	Dawie True RMS Volt Meter Type 612A	3	£45	114	H.P. SHF Signal Generator Model 616B	1	£120
15	Pye Modulation Meter Type MM1	3	£150	65	Racal VHF Calibrator Type 850	10	£100	115	Marconi Noise Generator Type TF 1100/2	2	£40
16	H.P. Wave Analyser Model 302A	1	£40	66	Edgetone Communications Receiver Type 680X	1	£80	116	Marconi Signal Generator Type TF 995A/5	2	£250
17	Tektronix Oscilloscope Type 545A Less Plug Ins	2	£60	67	Sanders Microwave Oscillator Type CLC2.4	1	£65	117	Marconi Signal Generator Type TF 995B/5	2	£400
18	ESM Electronics Pulse Generator Type 118/D	2	£80	68	General Radio Standard Signal Generator Type 1006	1	£180	118	Marconi VHF Alignment Oscilloscope Type TF 1104/1	1	£180
19	EMI Electronics Oscilloscope Plug-ins Type 17/6	2	£25	69	Teletest Oscilloscope Type D43	1	£180	119	Marconi Signal Generator Type TF 1005B/5	1	£45
20	EMI Electronics Oscilloscope Plug-ins Type 17/4	6	£50	70	Marconi Frequency Selector Unit Type 1K7047	1	£50	120	Teletest Oscilloscope Type RM 17	1	£45
21	Pye Microphone Portables Mid Band Dynamic Oscilloscope Type D 7100	1	£200	71	Marconi RF Power Meter Type TK 7056	1	£95	121	Teletest Oscilloscope Type 52	1	£20
22	Wayne Kerr Universal Bridge Type CT 375	2	£40	72	Marconi Programmable Voltmeter Type TK 2407	1	£85	122	Teletest Oscilloscope Type 543	2	£80
23	Dacwiler Terminal	1	£70	73	Marconi Programmable Voltmeter Type TK 2407	1	£85	123	Marconi FM Signal Generator Type F2006 10-220MHz	1	£300
24	Ferro - Mag 3ph 240v 5.4kva Transformer	1	£20	74	BRP Super Megohmmeter Type RM 170	1	£50	124	Philips Millivoltmeter Type GM4012	14	£200
25	Tektronix Oscilloscope Plug-ins Type G	4	£40	75	Honeywell Power Line Test Set Type P11-1	1	£35	125	Racal Communications Receiver Type RA 17	1	£185
26	Marconi RF Power Meter Type TF 1020A	2	£160	76	Teknec Digital Voltmeter Type 1E31333	1	£120	126	Advance Oscilloscope Type CS 25A	1	£80
27	Marconi 100 Watt 70db Attenuator Type 1P2580	1	£120	77	Charl Recorders Various	3	£60	127	Marconi UHF Signal Generator Type TF 1004/2	2	£150
28	Advance Oscilloscope Type OS 2000R	1	£190	78	Honeywell Power Line Test Set Type P11-1	1	£35	128	Lan. Elec. Ltd. Stabilised P.U. Type LP 4011	1	£30
29	Marconi VHF Signal Generator Type TF 1004B	1	£120	79	Marconi AF Power Meter Type TF2900	1	£120	129	SE Labs Oscilloscope Type SM 111	1	£185
30	Rhode & Schwartz Power Signal Generator Type BN41001	1	£120	80	Rhode & Schwartz Std Signal Gen. Type BNH409	1	£150	130	Advance Oscilloscope Type OS 2200	2	£400
31	Ferranti Computer Terminal Type WDM 2000	1	£120	81	Trendola Test Set No. 5	1	£50	131	Rhode & Schwartz UHF Test Receiver Type BNH523	1	£50
32	Pye IF Signal Generator	1	£40	82	General Radio VHF Oscillator Type 1363	3	£159	132	Tektronix Oscilloscope Type 647 Less Plug-ins	1	£150
33	Marconi Oscilloscope Type TF 1331A	1	£90	83	Tektronix Oscilloscope Type 545B Less Plug-ins	1	£50	133	Asiac 10" Video Monitor Type VM20475	4	£100
34	Brueel & Kjaer Microphone Amplifier Type T 2604	1	£50	84	Nargard Oscilloscope Type 311 C/W 3 Plug-ins	1	£50	134	Alrmec Modulation Meter Type 409	2	£180
35	Tektronix Oscilloscope Type 531A C/W Type H Plug-ins	4	£160	85	Marconi Deviation Test Set Type 6075B	4	£30	135	Marconi RC Oscillator Type TF 1101	2	£40
36	Teletest Oscilloscope Type 547 C/W Type 1A2 Plug-ins	4	£160	86	Sciamp Galvanometers	10	£100	136	Hewlett Packard Sweep Oscillator Type TFH 100	2	£60
37	Advance Signal Generator Type C2	1	£80	87	Electronic Capacitors 2000micra 25volt	1500	£75	137	Foster Oil Filled Varico D 2700V 40 amp	1	£300
38	Marconi 25 MHz Pulse Generator Type TF 2025	1	£100	88	Electrochome TV Video Monitors	4	£100	138	Hewlett Packard Sweep Oscillator Type 692D	1	£600
39	Rhode & Schwartz Power Test Adapter Type BN413116	1	£100	89	Equipment & Multi Core Cables	16	£40	139	Tektronix Time Mark Generator Type BM 181	1	£40
40	Marconi Frequency Converter Type TF2400/TM7104	1	£20	90	Sony Emly Video Tape Reels Type 518	33	£15	140	Tektronix Time Mark Generator Type 108A	1	£80
41	Solatron Recorder Drive Unit Type A205	1	£20	91	Sony Emly Video Tape Reels Type RH 7V	1	£10	141	Teletest Oscilloscope Type 544R	1	£75
42	Marconi UHF FM Signal Generator Type TF 2012	1	£350	92	Belco Power Supply Unit Type 1876	1	£40	142	Teletest Oscilloscope Type 531R	1	£30
43	Wander & Goldmann Filter Unit Type LDEF-2	1	£20	93	Advance Millivoltmeter Type 77A	5	£50	143	Sony Video Tape Type W-30H	106	£110
44	Rhode & Schwartz Waveformers Type BN 1522F1	3	£40	94	Reband Double P.S.U. Type I 104	1	£40	144	Teletest Oscilloscope Type 531R	1	£40
45	Pye UHF Signal Generator	1	£50	95	Marconi Output Power Meter Type TF 903	3	£20	145	Teletest Oscilloscope Type 531R	1	£40
46	H.P. Signal generator Model 606A	1	£80	96	H.P. Storage Oscilloscope Type 181 with Manuals	1	£300	146	Teletest Oscilloscope Calibrator Type C1	1	£40
47	Avo Signal Generator	1	£40	97	Marconi AF Power Meter Type TF 893A	3	£150	147	Marconi 20MHz Sweep Generator Type TF 1099	2	£60
48	Rhode & Schwartz Polykop Type SWOB 11	1	£200	98	Marconi Valve Volt Meter Type TF 041	2	£80	148	Transistors Type 2N3740	750	£200
49	Marconi White Noise Test Set Type OA 2090B	1	£200	100	Teletest Oscilloscope Type 544	2	£250	149	Vanner Digital Counter Type 15A-63AA/2	2	£60

B. BAMBER ELECTRONICS GOVERNMENT AND MANUFACTURERS SURPLUS

5 STATION ROAD,
LITTLEPORT,
CAMBS. CB6 1QE

Phone Ely (0353) 860185

ELECTRONIC COMPONENTS
TELECOMMUNICATION EQUIPMENT
TEST GEAR

LIGHTING

BAND — THEATRE — CLUB — DISCO




Great news has arrived for theatre, band, club and disco. The new high tec series 2 means it is now cheaper than ever to own your own lighting system. With complete packages from just £190 it makes a sound investment. Compared to the cost of hire, your money is recovered in a matter of months. At M.J.L. we have an extensive range of desks, power packs and control equipment, at the most competitive prices in the UK. And for those with really limited funds, a range of DIY modules. So if its just 5KW, or 500KW, give us a call.

M.J.L. SYSTEMS LTD
45 Wortley Road
W. Croydon
Surrey CR0 3EB
Tel: 01-689 4138

HOUSE OF MULTIMETERS

BEWA

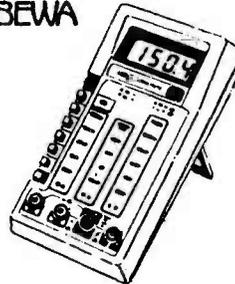


SOAR



METEX



AVO

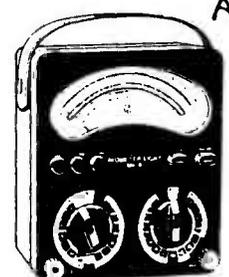

HOUSE OF INSTRUMENTS

Clifton Chambers, 62 High Street
Saffron Walden, Essex CB10 1EE
Telephone: (0799) 24922 (3 lines)

hi!

VARIO UPDATE

Lindsay Ruddock's vertical speed indicator project in our April and May issues aroused considerable interest. Here the author replies to some of the suggestions made by readers regarding the design.

One modification which has been suggested is the addition of 'total energy' compensation (see Read/Write, August '84 ETI, page 62). It is the author's intention to develop such a system at some stage, but it would require such extensive modifications that it might be better to think in terms of designing a new vario from scratch. There seems to be little demand for total energy compensation from hang glider pilots, probably because of the extra complication introduced by the need to plumb in a source of pitot pressure and because hang glider pilots are more aware of their airspeed than are sailplane pilots. There is, in any case, at least one variometer on the market with total energy compensation, and interested readers might like to contact the manufacturers at the address given at the end of this article.

That having been said, there may still be a few readers who really are interested in total energy compensation and who are prepared to do a little experimenting in order to achieve it. The following notes may be of some help to them.

The ETI design senses only static pressure, which it feeds directly to the differentiator. To provide total energy compensation, the input to the differentiator should be modified to:—

$$P - \frac{1}{2} \rho v^2 \dots \dots \dots (1)$$

where p = static pressure

ρ = air density

v = velocity of glider

The quantities " p " and " v " are not directly available so more manipulation is necessary:

$$p - \frac{1}{2} \rho v^2 = 2p - p - \frac{1}{2} \rho v^2 \dots \dots \dots (2)$$

$$= 2p - (p + \frac{1}{2} \rho v^2) \dots \dots \dots (3)$$

$$= 2 \times (\text{STATIC PRESSURE}) - \text{PITOT PRESSURE}$$

This expression is realizable, since the quantity $(p + \frac{1}{2} \rho v^2)$ is, in fact, the pitot pressure which can be sensed by a second pressure transducer plumbed into a pitot source.

Pitot pressure is the extra pressure that arises in a tube when the mouth of the tube faces into a stream of air. It appears in books on aerodynamics and fluid flow, and is well-known to amateur fliers and aerodynamicists — but not to ETI's assistant editor, who carefully amended 'pitot' to 'pilot', all the way through the original script, then wondered why the author had so consistently made the same rather curious typing error - t and l being well-removed from each other on a conventional QWERTY keyboard. We're ashamed to add that the editor, despite his back-

ground in physics, had little more idea as to what pitot pressure was!

What is required, therefore, is to modify the input to the differentiator by subtracting the right amount of pitot pressure in accordance with expression (3). One possibility is to place a summing amplifier between the static pressure transducer buffer and the differentiator, as shown in Fig. 1.

It should be emphasised that this is only a suggestion aimed at those willing and able to develop their own circuitry. The author has not tried the system and cannot offer any further practical information. Readers who are particularly interested in total energy compensation should obtain a copy of the September 1975 issue of "Soaring" magazine in which the subject is fairly well covered.

Temperature Compensation

In an effort to present as straightforward a circuit as possible in the ETI vario design, temperature compensation of the transducer was kept simple.

Better temperature compensation of the Sensym LX0503A can be easily achieved by 'tuning' the regulated voltage to the device. Since the vario circuit is not sensitive to supply voltage, it is convenient to make the regulated voltage to the complete circuit adjustable. This is implemented by replacing the 78L05A regulator chip with an adjustable op-amp regulator based on the LM10.

The original PCB was designed so as to leave space for a satellite board carrying the LM10 regulator circuit just above the transducer and to the left of the existing 78L05A regulator. There is also some space available on the underside of the transducer PCB and this can be used if there is insufficient space above, as might be the case if one of the larger transducer types has been used.

A suitable veroboard layout for the new regulator circuit is shown

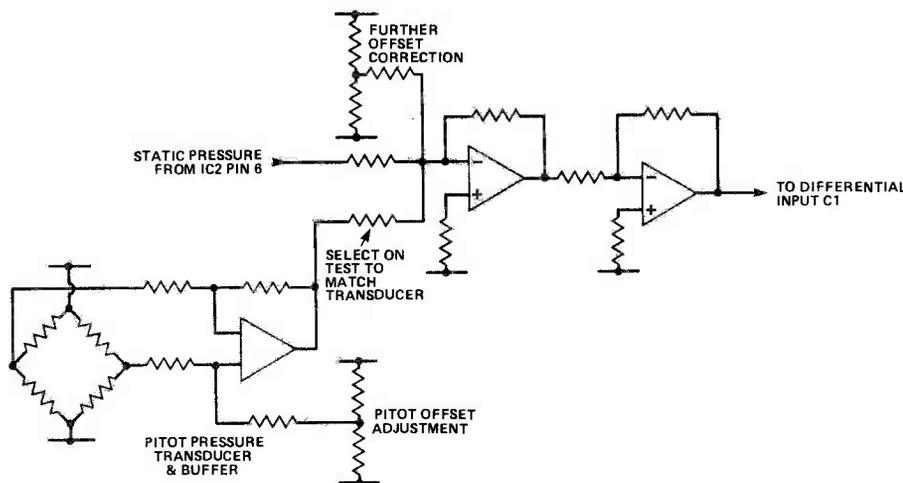


Fig. 1 Suggested modification to the original vario circuit to give total energy compensation.

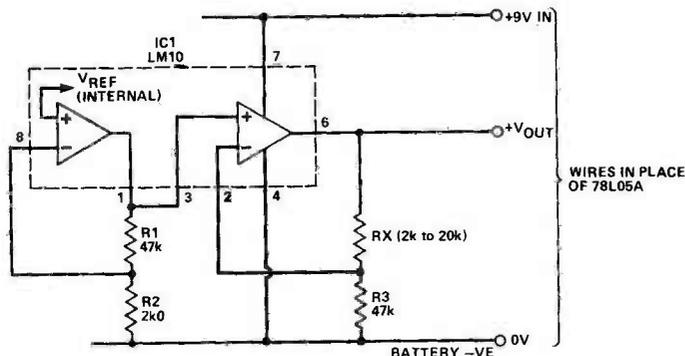


Fig. 2 Adjustable regulator arrangements to replace the 78L05A.

in Fig. 3. It was not considered worthwhile producing a PCB layout for such a small board and so simple a circuit. Note, when you come to assemble the board, that one of the links is underneath the IC and don't forget to break the tracks in the positions indicated. Do not use an IC socket as this would make the board too deep to fit easily in the available space. It is quite a good idea to solder short leads in place of R_x to begin with as this will save you having to remove the board to try different values of resistance and will also reduce the risk of damage to the tracks caused by repeated soldering and desoldering.

When complete, the new board is wired directly in place of the original 78L05A regulator. A little tape or a sticky pad should be sufficient to hold it in place and prevent it from touching any other part of

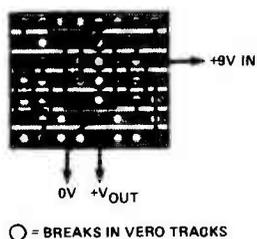


Fig. 3 Veroboard layout for the regulator circuit. The component values are given in Fig. 2.

the circuitry. Note that the previously optional 100uF decoupling capacitor, C4, should now be fitted.

The resistor R_x sets the regulated voltage. eg $R_x = 1k$, $V = 5V$, $R_x = 13k$, $V = 6.25V$

$$V = 4.9 \times \left(\frac{R_x + 47k}{47k} \right) V$$

A good starting voltage is 5.5V, $R_x = 5.6k$.

R_x is adjusted downwards if the vario reads sink as it cools (use the fridge to find out) and vice versa. A large percentage of LX0503A devices end up with satisfactory temperature compensation with supply voltages of between 5 and 5.5 volts, which explains why the LX0503A is shown wired across 5V in the original design.

Further benefits of using the LM10 are that battery life is tripled to a hundred hours from an alkaline battery and ordinary zinc carbon types may also now be used, giving about 50 hours. This is because not only is battery drain halved (the 78L05A draws 3mA standing current), but the battery endpoint voltage is lowered — the LM10 regulator requires only 0.2 volts input to output differential compared to 2.5V for the 78L05A. Other adjustable regulators can be used, but have not been checked out.

Note that while tuning the supply voltage is recommended as a method of temperature compensa-

tion for the LX0503A, the alternative transducer, the MPX100A, can only be compensated by the single series resistor/constant supply excitation voltage method as outlined in the original article.

Some people have acquired Foxboro transducers. For these, and Druck-Keller types, constant current excitation is best. The precise current affects sensitivity but for compensation purposes the absolute value does not matter. A suitable circuit is shown in Fig. 4.

All the compensation methods mentioned compensate explicitly only for span. Since the operating pressure range is not too great, it is not worth considering offset errors separately.

A word of explanation for all these compensation methods is probably in order. The major temperature dependent parameters of a piezoresistive pressure transducer are:

1. temperature coefficient of bridge resistance (approx. +2000ppm/C.).

2. temperature coefficient of gauge factor or pressure sensitivity (approx. -2000ppm/C.). Note the opposite signs of these coefficients.

In the best transducers, eg Foxboro, Druck-Keller, these coefficients are equal as well as opposite, which explains why constant current excitation provides automatic compensation.

In the case of the MPX100A, constant current excitation causes over compensation as the magnitude of the temperature coefficient of bridge resistance is greater than the temperature coefficient of gauge factor. Something in between has to be used, which is why a compensating resistor in series with a constant voltage is recommended. Adjustment is easy and the method gives very satisfactory compensation, even for use as an altimeter.

In the case of the LX0503A, the least consistent of all the low-cost transducers on the market, the gauge factor temperature coefficient is much greater than the bridge resistance temperature coefficient. Compensation must be by some other method such as using the internal V_{be} multiplier.

ETI

The total energy compensated variometer mentioned in this article is manufactured by Thunderbird Electronics Ltd, 20 Buttgarden Street, Bideford, Devon, tel 02372-5133.

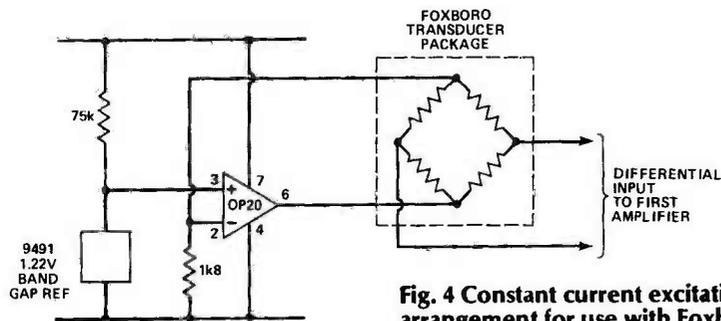


Fig. 4 Constant current excitation arrangement for use with Foxboro transducer.

If an advertisement is wrong we're here to put it right.

If you see an advertisement in the press, in print, on posters or in the cinema which you find unacceptable, write to us at the address below.

The Advertising Standards Authority.

ASA Ltd, Dept 3 Brook House,
Torrington Place, London WC1E 7HN

LOOK!
UNBEATABLE VALUE
TANDON 5 1/4" THINLINE FLOPPY DISK DRIVES
SINGLE SIDED DOUBLE DENSITY £100
DOUBLE SIDED DOUBLE DENSITY £130
BRAND NEW
DON'T DELAY—
ORDER TODAY!

H.P. SPECTRUM ANALYSER 8551A 10MHZ - 12.4GHZ with P.O.A. 851B display	
TEK455 Dual Trace 50MHZ Delay Sweep	£650
GOULD DS 3500 Dual Trace 60MHZ Delay Sweep	£600
OSCILLOSCOPES	
2 TEK 454 Dual Trace 150 MHZ Delay Sweep	£700
6 TELEQUIPMENT D83 Dual Trace 50MHZ Delay Sweep	£400
7 Tel 453 Dual Trace 50MHZ Delay Sweep	£375
9 COSSOR 4100 Dual Trace 75MHZ Delay Sweep	£375
10 SOLARTRON CD1740 Dual Trace 50MHZ Dual TB	£250
14 TEK 585A Dual Trace 85MHZ Dual TB Delay Sweep	£200
15 COSSOR CDU 150 Dual Trace 35NHZ Delay TB	£200
17 SELABS SM111 Dual Trace 20MHZ	£200
23 SOLARTRON CD1400 Dual Beam 15MHZ	£100
STORAGE OSCILLOSCOPES	
35 TELEQUIPMENT DM64 Dual Trace 10MHZ	£350
36 TEK 564 Dual Trace 10MHZ Delay Sweep	£275
37 TEK Spectrum Analyser 50HZ-1MHZ. 547 Mainframe with 11.5 Plug-in Unit.	£700
40 TELEQUIPMENT CT71 CURVE TRACER.	£400
42 H.P. SHF SIG GEN 620B 7-11GHZ	£350
46 H.P. UHF SIG GEN 612A 450-1230MHZ	£200
50 MARCONI AM/FM Sig Gen TF2008 10KH-510MHZ	£1,250
52 MARCONI AM/FM Sig Gen TF1066B/6 10-470 MHZ	£325
59 MARCONI AM/FM Sig Gen TF995A/21 5-220MHZ	£250
62 MARCONI VHF Sig Gen TF1064B/5M 66-108, 110-185-450-470MHZ	£110
63 MARCONI OUTPUT TEST SET TF 1065 for use with TF1064 & TF995 range Sig Gens	£75
66 ADVANCE AM Sig Gen E2 100KHZ-100MHZ	£40
72 TEK Constant Amplitude Sig Gen 99B 350KHZ/50MHZ	£160
74 MARCONI WIDE RANGE OSC TF1370A 5/MHZ (Square wave to 100KHZ)	£95
80 WAYNE KERR AF Sig Gen S121 10HZ-120KHZ	£40
87 H.P. Pulse Gen 214A 10HZ-1MHZ	£250
89 LH PULSE GEN 139L 1KHZ-20MHZ Single/Double Pulse	£200
98 TEK TIME MARK GEN 180	£40
102 BONTON Q METER 260A 50KHZ-50MHZ	£250
104 MARCONI Q METER TF329G 50KHZ-50MHZ	£150
106 MARCONI UNIVERSAL BRIDGE TF1313 0.25%	£200
108 MARCONI INSITU UNIVERSAL BRIDGE TF2701 Battery Operated	£300
109 Wayne Kerr Autobalance Component Bridge 8421	£250
114 Wayne Kerr Component Bridge B521 (CT375) L 100uH-500KH. C1P-F5. R1 milliohm-1000Mohm	£35
117 Wayne Kerr VHF Admittance Bridge B801 with Source S161 & Detector R161	£400
119 MARCONI AM/FM Mod Meter TF2300S 2-100MHZ	£375
123 AIRMEC MOD METER AM/FM type 210 3-300MHZ	£95
124 MARCONI RF MILLIVOLTMETER TF2603 50KHZ-1500MHZ 1mV-3V FSD	£375
125 MARCONI ELECTRONIC VOLTMEETER TF260420HZ-1500MHZ AC/DC/Ohms AC300mV-300V FSD. DC 200mV-1KV FSD.	£175
144 AVO MULTIMETER Model 7 P&P E7	£20
146 AVO MULTIMETER Model 8 P&P E7	£45
152 MULTIMETER U4324 33 switched ranges 20K Ohm per volt. Complete with leads & battery. Brand New. One year guarantee P&P E4	£10
160 FARNELL STAB PSU TSV30/5 0-30V 5A. Current limiting Metered	£65
161 FARNELL STAB PSU TSV30/2 0-30V 2A Current limiting metered	£50
163 ROBAND VARECO PSU type 33-2 0-33V 2A Current limiting metered (in current production)	£100
169 KINGSHILL STAB PSU Model 500 0-60V 0.5A. Current limiting Metered P&P E7	£40
180 BRANDENBURGH PHOTOMULTIPLIER PSU 47R 10-2100V 5mA Metered	£200
190 VOLTEX PSU Model 82-635 +/- 5V. -12V. -24V High current un-used	£15
191 AC/DC ELECTRONICS PSU MODULE 251 5V 2A +/-12V 0.4A Un-used P&P E3	£15
206 B&K LEVEL RECORDER 23D5	£400
209 B&K MEASURING AMPLIFIER 2605 2HZ-200KHZ	£600
210 B&K BAND PASS FILTER SET Octave & 3rd Octave Weighing Networks ABCD	£550
211 B&K DIGITAL EVENT RECORDER 7502	£1,500
225 DAWE OCTAVE BAND SOUND LEVEL METER type 6419c	£150
281 H.P. LOGICSTATIC ANALYSER 1602A	£450
286 AVO VALUE CHARACTERISTIC METER VCM 163	£275
293 MARCONI AF POWER METER TF893A	£75
297 MARCONI DIFFERENTIAL DC VOLTMEETER TF2606 0-1100V	£225
300 R&S POLYSKOP SWOB1 BN 4244/2/50	£350


Also in stock NEW OSCILLOSCOPES, MULTIMETERS etc.

THIS IS A VERY SMALL SAMPLE OF STOCK, SAE or Telephone for LISTS
Please check availability before ordering. Carriage all units £10 VAT to be added to Total of Goods & Carriage.

STEWART OF READING
110 WYKEHAM ROAD, READING, BERKS RG6 1PL
Telephone: 0734 68041
Callers welcome 9 a.m. to 5.30 p.m. Monday to Saturday inclusive

MASTER Electronics - Microprocessors - Now! The PRACTICAL Way!

- Electronics - Microprocessors - Computer Technology is the career and hobby of the future. We can train you at home in a simple, practical and interesting way.
- Recognise and handle all current electronic components and 'chips'.
- Carry out full programme of experimental work on electronic & computer circuits including modern digital technology.
- Build an oscilloscope and master circuit diagrams.
- Testing and servicing radio - T.V. - hi-fi and all types of electronic/computer/industrial equipment.

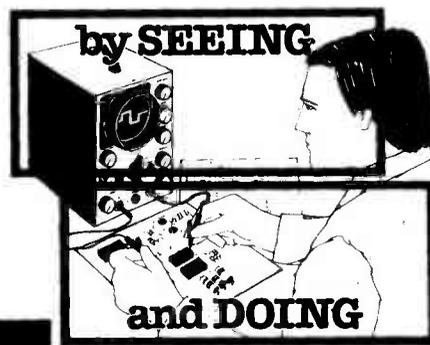

New Job? New Career? New Hobby?

SEND THIS COUPON NOW.

Please send your brochure without any obligation to: — I am interested in:

NAME _____

ADDRESS _____

ETI 12 _____ BLOCK CAPS PLEASE

- ELECTRONICS
 MICROPROCESSORS
 RADIO AMATEUR LICENCE
 CITY & GUILDS EXAMS

Other Subjects _____



British National Radio & Electronics School Reading, Berks. RG1 1BR



OR TELEPHONE US
0734 51515 OR
TELEX 22758
(24 HR SERVICE)

electronics today international BOOK SERVICE

How to order: indicate the books required by ticking the boxes and send this page, together with your payment, to: ETI Book Service, Argus Specialist Publications Ltd, 1, Golden Square, London W1R 3AB. Make cheques payable to ETI Book Service. Payment in sterling only please. All prices include P & P. Prices may be subject to change without notice.

BEGINNERS GUIDE

<input type="checkbox"/>	Beginner's Guide to Basic Programming Stephenson	£5.35
<input type="checkbox"/>	Beginner's Guide to Digital Electronics	£5.35
<input type="checkbox"/>	Beginner's Guide to Electronics	£5.35
<input type="checkbox"/>	Beginner's Guide to Integrated Circuits	£5.35
<input type="checkbox"/>	Beginner's Guide to Computers	£5.35
<input type="checkbox"/>	Beginner's Guide to Microprocessors	£5.35

COOKBOOKS

<input type="checkbox"/>	Master IC Cookbook Hallmark	£10.15
<input type="checkbox"/>	Microprocessor Cookbook M. Hordeski	£7.70
<input type="checkbox"/>	IC Op Amp Cookbook Jung	£14.25
<input type="checkbox"/>	PLL Synthesiser Cookbook H. Kinley	£7.70
<input type="checkbox"/>	Active Filter Cookbook Lancaster	£13.40
<input type="checkbox"/>	TV Typewriter Cookbook Lancaster	£11.15
<input type="checkbox"/>	CMOS Cookbook Lancaster	£11.85
<input type="checkbox"/>	TTL Cookbook Lancaster	£10.95
<input type="checkbox"/>	Micro Cookbook Vol. 1 Lancaster	£15.30
<input type="checkbox"/>	BASIC Cookbook K. Tracton	£6.00
<input type="checkbox"/>	MC6809 Cookbook C. Warren	£7.25

ELECTRONICS

<input type="checkbox"/>	Principles of Transistor Circuits Amos	£8.50
<input type="checkbox"/>	Design of Active Filters with experiments Berlin	£11.30
<input type="checkbox"/>	49 Easy to Build Electronic Projects Brown	£6.00
<input type="checkbox"/>	Electronic Devices & Circuit Theory Boylestad	£13.20
<input type="checkbox"/>	How to build Electronic Kits Capel	£3.55
<input type="checkbox"/>	How to Design and build electronic instrumentation Carr	£9.35
<input type="checkbox"/>	Introduction to Microcomputers Dagless	£7.20
<input type="checkbox"/>	Electronic Components and Systems Dennis	£15.00
<input type="checkbox"/>	Principles of Electronic Instrumentation De Sa	£11.40
<input type="checkbox"/>	Giant Handbook of Computer Software	£12.95
<input type="checkbox"/>	Giant Handbook of Electronic Circuits	£17.35
<input type="checkbox"/>	Giant Handbook of Electronic Projects	£11.75
<input type="checkbox"/>	Electronic Logic Circuits Gibson	£5.55
<input type="checkbox"/>	Analysis and Design of Analogue Integrated Circuits Gray	£30.25
<input type="checkbox"/>	Basic Electronics Grob	£11.30
<input type="checkbox"/>	Lasers - The Light Fantastic Hallmark	£7.70
<input type="checkbox"/>	Introduction to Digital Electronics & Logic Johnson	£5.25
<input type="checkbox"/>	Electronic Testing and Fault Diagnosis Loveday	£7.85
<input type="checkbox"/>	Electronic Fault Diagnosis Loveday	£6.25
<input type="checkbox"/>	Essential Electronics A-Z Guide Loveday	£7.50
<input type="checkbox"/>	Microelectronics Digital & Analogue circuits and systems Millman	£12.70
<input type="checkbox"/>	103 Projects for Electronics Experimenters Minis	£9.30
<input type="checkbox"/>	VLSI System Design Muroga	£34.10
<input type="checkbox"/>	Power FETs and their application Oxner	£9.40
<input type="checkbox"/>	Practical Solid State Circuit Design Dlesky	£25.00
<input type="checkbox"/>	Master Handbook of IC Circuits Powers	£12.85
<input type="checkbox"/>	Electronic Drafting and Design Raskhodoff	£22.15
<input type="checkbox"/>	VOM - VTVM Handbook Risse	£9.50
<input type="checkbox"/>	Video and Digital Electronic Displays Sherr	£29.85
<input type="checkbox"/>	Understanding Electronic Components Sinclair	£7.50
<input type="checkbox"/>	Electronic Fault Diagnosis Sinclair	£4.50
<input type="checkbox"/>	Physics of Semiconductor Devices Sze	£17.35
<input type="checkbox"/>	Digital Circuits and Microprocessors Taub	£32.00
<input type="checkbox"/>	Active Filter Handbook	£7.60
<input type="checkbox"/>	Designing with TTL Integrated Circuits Texas	£15.20
<input type="checkbox"/>	Transistor Circuit Design Texas	£15.20
<input type="checkbox"/>	Digital Systems: Principles and Applications Tocci	£12.95
<input type="checkbox"/>	Master Handbook of Telephones Traister	£10.00
<input type="checkbox"/>	How to build Metal/Treasure Locators Traister	£6.00
<input type="checkbox"/>	99 Fun to Make Electronic Projects Tymony	£8.50
<input type="checkbox"/>	33 Electronic Music Projects you can build Winston	£6.95

COMPUTERS & MICROCOMPUTERS

<input type="checkbox"/>	BASIC Computer Games Ahl	£6.35
<input type="checkbox"/>	From BASIC to PASCAL Anderson	£9.95
<input type="checkbox"/>	Mastering Machine Code on your ZX81 T. Baker	£7.25
<input type="checkbox"/>	UNIX - The Book Banaham	£8.75
<input type="checkbox"/>	Z80 Microcomputer Handbook Barden	£10.95
<input type="checkbox"/>	Microcomputer Maths Barden	£11.90
<input type="checkbox"/>	Digital Computer Fundamentals Barter	£9.90
<input type="checkbox"/>	Visicalc Book. APPLE Edition Bell	£15.55
<input type="checkbox"/>	Visicalc Book. ATARI Edition Bell	£15.55
<input type="checkbox"/>	Introduction to Microprocessors Brunner	£23.00
<input type="checkbox"/>	Programming your APPLE II Computer Bryan	£9.25
<input type="checkbox"/>	Microprocessor Interfacing Carr	£7.70
<input type="checkbox"/>	Microcomputer Interfacing Handbook A/D & D/A Carr	£9.50
<input type="checkbox"/>	Musical Applications of Microprocessors Chamberlain	£29.85
<input type="checkbox"/>	30 Computer Programs for the Home Owner in BASIC D. Chance	£9.25
<input type="checkbox"/>	Microcomputers Dirkson	£9.30
<input type="checkbox"/>	APPLE Personal Computer for Beginners Dunn	£9.50
<input type="checkbox"/>	Microcomputers/Microcomputers - An Intro Gioone	£11.80

<input type="checkbox"/>	Troubleshooting Microprocessors and Digital Logic Goodman	£9.25
<input type="checkbox"/>	Getting Acquainted with your VIC 20 Hartnell	£8.50
<input type="checkbox"/>	Getting Acquainted with your ZX81 Hartnell	£8.95
<input type="checkbox"/>	Let your BBC Micro Teach you to program Hartnell	£7.90
<input type="checkbox"/>	Programming your ZX Spectrum Hartnell	£8.50
<input type="checkbox"/>	The ZX Spectrum Explored Hartnell	£8.95
<input type="checkbox"/>	How to Design, Build and Program your own working Computer System Haviland	£9.30
<input type="checkbox"/>	BASIC Principles and Practice of Microprocessors Heffer	£7.15
<input type="checkbox"/>	Hints and Tips for the ZX81 Hewson	£5.25
<input type="checkbox"/>	What to do when you get your hand on a Microcomputer Holtzman	£9.95
<input type="checkbox"/>	34 More Tested Ready to Run Game Programs in BASIC Horn	£7.70
<input type="checkbox"/>	Microcomputer Builders' Bible Johnson	£12.40
<input type="checkbox"/>	Digital Circuits and Microcomputers Johnson	£14.55
<input type="checkbox"/>	PASCAL for Students Kemp	£7.20
<input type="checkbox"/>	The C - Programming Language Kernighan	£18.20
<input type="checkbox"/>	COBOL Jackson	£9.25
<input type="checkbox"/>	The ZX81 Companion Maunder	£9.50
<input type="checkbox"/>	Guide to Good Programming Practice Meek	£6.40
<input type="checkbox"/>	Principles of Interactive Computer Graphics Newman	£13.95
<input type="checkbox"/>	Theory and Practice of Microprocessors Nicholas	£11.35
<input type="checkbox"/>	Exploring the World of the Personal Computer Niles	£12.95
<input type="checkbox"/>	Microprocessor Circuits Vol. 1. Fundamentals and Microcontrollers Noll	£9.80

<input type="checkbox"/>	Beginner's Guide to Microprocessors Parr	£5.35
<input type="checkbox"/>	Microcomputer Based Design Peatman	£11.30
<input type="checkbox"/>	Digital Hardware Design Peatman	£9.80
<input type="checkbox"/>	BBC Micro Revealed Ruston	£8.45
<input type="checkbox"/>	Handbook of Advanced Robotics Safford	£14.45
<input type="checkbox"/>	1001 Things to do with your own personal computer Sawusch	£9.50
<input type="checkbox"/>	Easy Programming for the ZX Spectrum Stewart	£7.15
<input type="checkbox"/>	Microprocessor Applications Handbook Stout	£34.40
<input type="checkbox"/>	Handbook of Microprocessor Design and Applications Stout	£37.60
<input type="checkbox"/>	Programming the PET/CBM West	£17.80
<input type="checkbox"/>	An Introduction to Microcomputer Technology Williamson	£8.20
<input type="checkbox"/>	Computer Peripherals that you can build Wolfe	£12.40
<input type="checkbox"/>	Microprocessors and Microcomputers for Engineering Students and Technicians Wooland	£7.10

REFERENCE BOOKS

<input type="checkbox"/>	Electronic Engineers' Handbook Fink	£58.45
<input type="checkbox"/>	Electronic Designers' Handbook Gioacietto	£59.55
<input type="checkbox"/>	Illustrated Dictionary of Microcomputer Technology Hordeski	£9.45
<input type="checkbox"/>	Handbook for Electronic Engineering Technicians Kaufman	£27.50
<input type="checkbox"/>	Handbook of Electronic Calculators Kauffman	£35.00
<input type="checkbox"/>	Modern Electronic Circuit Reference Manual Marcus	£44.00
<input type="checkbox"/>	International Transistor Selector Towers	£10.70
<input type="checkbox"/>	International Microprocessor Selector Towers	£16.00
<input type="checkbox"/>	International Digital IC Selector Towers	£10.95
<input type="checkbox"/>	International Op Amp Linear IC Selector Towers	£8.50
<input type="checkbox"/>	Illustrated Dictionary of Electronics Turner	£12.95

VIDEO

<input type="checkbox"/>	Servicing Home Video Cassette Recorders Hobbs	£12.95
<input type="checkbox"/>	Complete Handbook of Videocassette Recorders Kybett	£9.25
<input type="checkbox"/>	Theory and Servicing of Videocassette Recorders McGinty	£12.95
<input type="checkbox"/>	Beginner's Guide to Video Matthewson	£5.35
<input type="checkbox"/>	Video Recording: Theory and Practice Robinson	£14.40
<input type="checkbox"/>	Video Handbook Van Wezel	£21.90
<input type="checkbox"/>	Video Techniques White	£12.95

Please send me the books indicated. I enclose cheque/postal order for £..... Prices include postage and packing. I wish to pay by Access/Barclaycard. Please debit my account.

5	2	2	4																
---	---	---	---	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--


4	9	2	9																
---	---	---	---	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Signed.....


Name.....

Address.....


FOIL PATTERNS

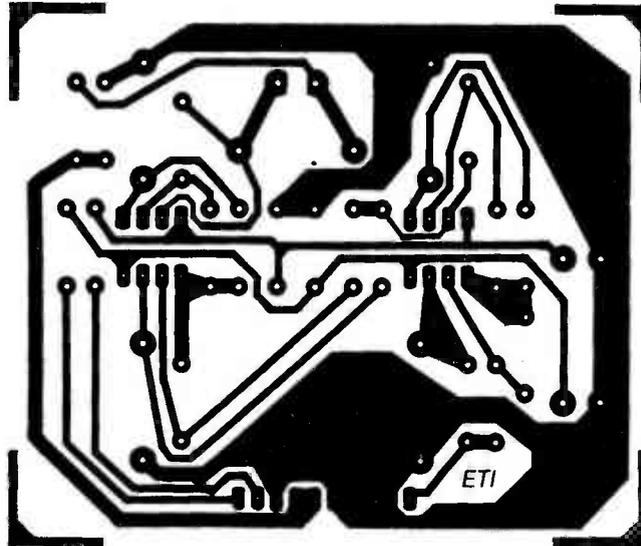


The Active-8 delay unit board.

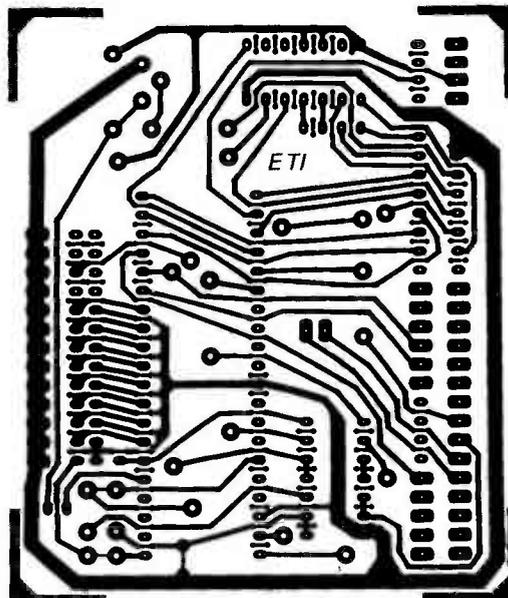

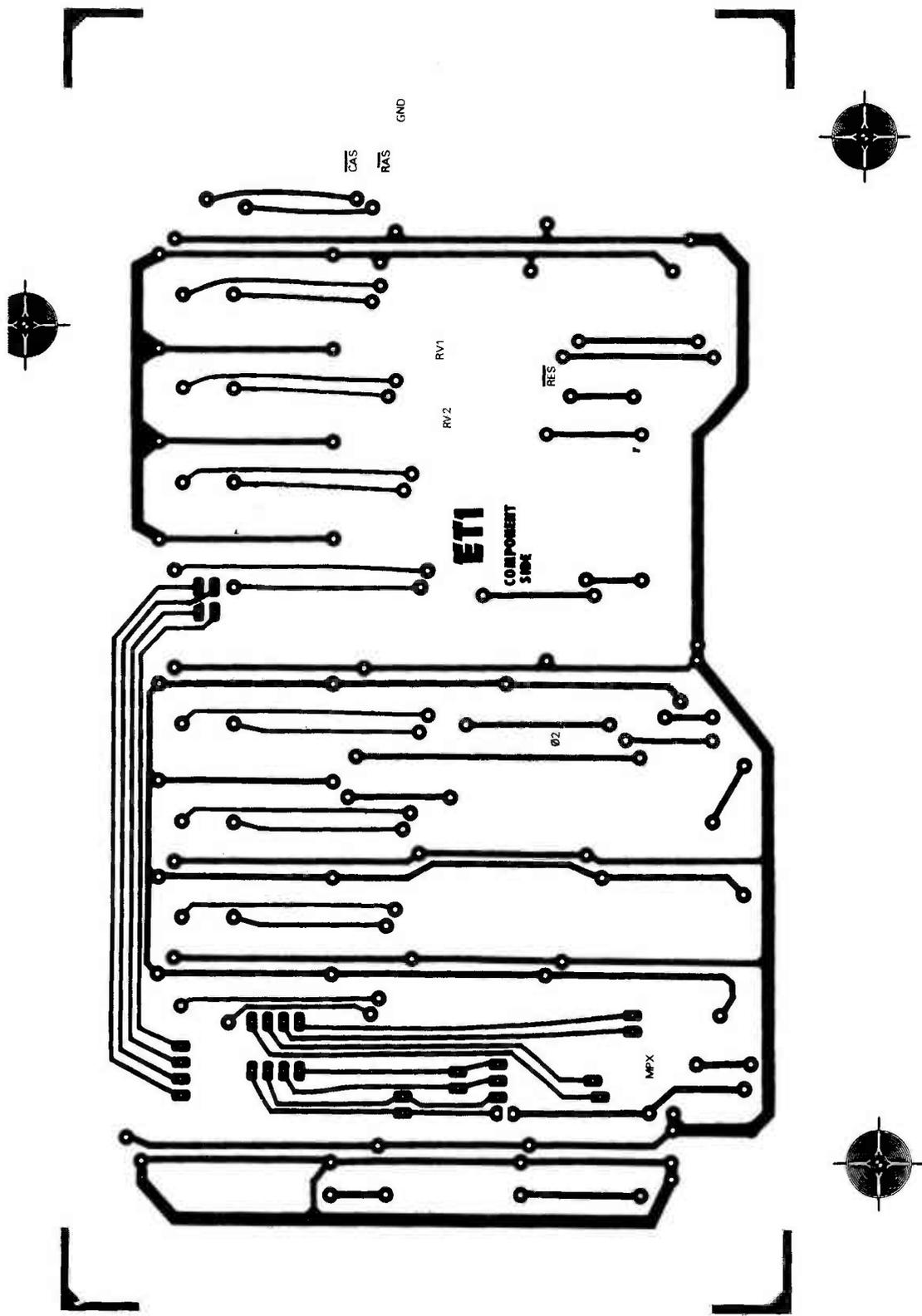The board for the Spectrum Centronics Interface.



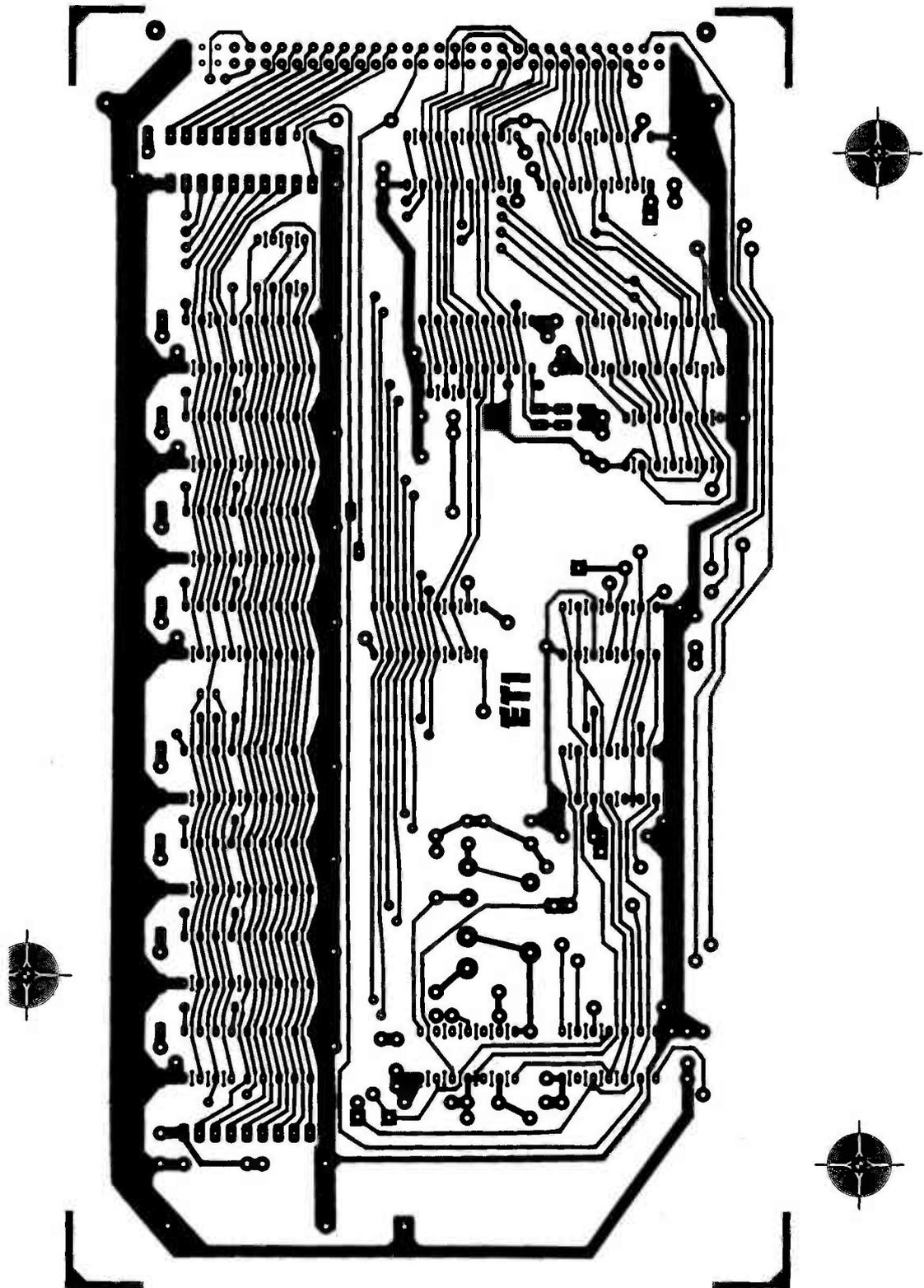The top and bottom foils for the experimenters' DRAM.



ETI PCB SERVICE

In order to ensure that you get the correct board, you must quote the reference code when ordering. The code can also be used to identify the year and month in which a particular project appeared: the first two numbers are the year, the third and fourth are the month and the number after the hyphen indicates the particular project.

Note that these are all the boards that are available — if it isn't listed, we don't have it.

Our terms are strictly cash with order — we do not accept official orders. However, we can provide a pro-forma invoice for you to raise a cheque against, but we must stress that the goods will not be dispatched until after we receive payment.

1981

- E/8106-8 Waa-Phase 1.76
- E/8106-9 Alien Attack 4.00
- E/8107-1 System A-Input
(MM or MO) 3.05
- E/8107-2 System A — Preamp 5.95
- E/8107-3 Smart Battery Charger 2.27
- E/8108-3 Hand Clap Synth 4.57
- E/8108-5 Watchdog Home
Security (2 boards) 6.11
- E/8109-1 Mains Audio Link
(3 boards) 8.45
- E/8109-4 Laboratory PSU 5.21
- E/8110-1 Enlarger Timer 3.91
- E/8110-2 Sound Bender 3.05
- E/8111-1 Voice Over Unit 4.57
- E/8111-2 Car Alarm 3.23
- E/8111-3 Phone Bell Shifter 3.40
- E/8112-4 Component Tester 1.71

1982

- E/8201-3 Guitar Tuner (2 boards) 6.38
- E/8202-1 Ripple Monitor 2.21
- E/8202-2 Allez Cat Pest Repeller 1.93
- E/8202-5 Moving Magnet Stage 4.01
- E/8202-6 Moving Coil Stage 4.01
- E/8203-4 Capacitance Meter
(2 boards) 11.66
- E/8205-1 DV Meg 3.13
- E/8206-1 Ion Generator
(3 boards) 9.20
- E/8206-4 MOSFET Amp Module 7.80
- E/8206-5 Logic Lock 3.52
- E/8206-6 Digital PWM 3.84
- E/8206-7 Optical Sensor 2.00
- E/8206-9 Oscilloscope
(4 boards) 13.34
- E/8207-7 TV Bargraph Main 5.24
- E/8207-3 TV Bargraph Channel 2.62
- E/8207-4 Hotwire 3.02
- E/8207-5 Bridging Adapter 2.74
- E/8208-1 Playmate (3 boards) 8.28
- E/8208-4 Kitchen Scales 2.12
- E/8209-2 Dual Logic Probe 2.22
- E/8211-4 Pulse Generator 6.08
- E/8212-1 ELCB 2.77
- E/8212-2 Servo Interface
(2 boards) 6.75
- E/8212-4 Spectracolumn 5.54

1983

- E/8301-1 Fuel Gauge 3.45
- E/8301-2 ZX ADC 2.59
- E/8301-3 Programmable PSU 3.45

- E/8303-1 SoundBoard 12.83
- E/8303-2 Alarm Module 3.62
- E/8303-3 ZX81 User Graphics 1.07
- E/8303-4 Logic Probe 2.50
- E/8304-1 Real Time Clock 8.74
- E/8304-2 Thermometer
(2 boards) 9.74
- E/8304-4 Stage Lighting— Main 13.73
- E/8304-5 Stage Lighting — Display 3.45
- E/8305-1 Compressor/Limiter 6.19
- E/8305-2 Single PSU 3.16
- E/8305-3 Dual PSU 4.01
- E/8305-4.2 NDFL Amp 7.88
- E/8305-5 Balance Input Preamp 3.23
- E/8305-6 Stage Lighting
Autofade 6.19
- E/8305-7 Stage Lighting —
Triac Board 4.74
- E/8306-1 to 3 PseudoROM
(3 boards) 3.62
- E/8306-4 Immersible Heater 2.30
- E/8306-5 Atom Keypad 5.18
- E/8307-1 Flash Sequencer 2.67
- E/8307-2 Trigger Unit Main Board 2.67
- E/8307-3 Trigger Unit Transmitter 1.66
- E/8307-4 Switched Mode PSU 16.10
- E/8308-1 Graphic Equaliser 9.10
- E/8308-2 Servo Fail-Safe
(four-off) 2.93
- E/8308-3 Universal EPROM prog 9.64
- E/8309-1 NiCad Charger/Regen 3.77
- E/8309-2 Digger 3.40
- E/8309-3 64K DRAM 14.08
- E/8310-1 Supply Protector 2.19
- E/8310-2 Car Alarm 3.98
- E/8310-3 Typewriter Interface 4.17
- E/8311-1 Mini Drum Synth 3.07
- E/8311-2 Alarm Extender 3.21
- E/8311-3 Multiswitch 3.59
- E/8311-4 Multiple Port 4.34
- E/8311-5 DAC/ADC Filter 3.22
- E/8311-6 Light Pen 4.60
- E/8311-7 Logic Clip 2.51
- E/8311-8 MC Head (JLLH) 3.17
- E/8312-1 Lightsaver 1.85
- E/8312-2 A-to-D Board 12.83
- E/8312-3 Light Chaser (2 bds) 7.54
- E/8312-4 ZX Alarm 6.04

1984

- E/8401-1 Vector Graphics 8.27
- E/8402-1 Speech Board
(Mini-Mynah) 10.97

MODULAR PREAMP:

- E/8402-2 Disc input (mono) 3.73
- E/8402-3 Output stage (stereo) 3.73
- E/8402-4 Relay/PSU 3.73
- E/8402-5 Tone, main (mono) 3.73
- E/8402-6 Tone, filter (stereo) 3.73
- E/8402-7 Balanced output (st) 3.73
- E/8402-8 Headphone amp (st) 3.73
- E/8402-9 Mother board 9.01
- E/8403-1 Power Meter 5.81
- E/8403-2 Z80 DRAM 9.79
- E/8403-3 Obedient Die 3.76
- E/8404-1 School Timer 4.07
- E/8405-1 Auto Light Switch 4.01
- E/8405-2 ZX81 EPROM Prog 10.53
- E/8405-3 Mains Borne RC 5.07
- E/8405-4 Centronics Interface 4.09
- E/8405-5 Vario 6.62
- E/8405-6 Midi Drum Synth 3.59
- E/8406-1 Oric EPROM Bd 19.58
- E/8406-2 Spectrum Joystick 3.30
- E/8407-1 Warlock Alarm 8.19
- E/8408-1 Joystick Interface 3.07
- E/8408-2 EPROM Emulator 9.11
- E/8408-3 Infrared Transmitter 3.70
- E/8408-4 Infrared Receiver 3.98
- E/8408-5 CMOS Tester 4.60
- E/8409-1 EX42 Kybd. Interface 3.82
- E/8409-2 Banshee Siren 3.19
- E/8409-3 Dry Cell Charger 2.80
- E/8410-1 Joystick Unit 3.92
- E/8410-2 Digital Cassette 9.80
- E/8410-3 Disco/Party Strobe 4.80
- E/8411-1 AM/FM Radio (4 bds) 13.02
- E/8411-2 Control Port-control bd 12.15
- E/8411-3 Control Port-I/O bd 6.33
- E/8411-4 Capacitance Meter 3.55
- E/8411-5 Video Vandal (3 bds) 12.10
- E/8411-6 Temperature Controller 2.88
- E/8411-7 Mains Failure Alarm 2.54
- E/8411-8 Knife Light 3.25
- E/8411-9 Stage Lighting Interface 3.73
- E/8411-10 Perpetual Pendulum 3.14
- E/8412-1 Spectrum Centronics 3.51
- E/8412-2 Experimenter's DRAM 14.08
- E/8412-3 Active-8: Motherboard 9.37
- E/8412-4 Active-8: Protection Unit 3.67
- E/8412-5 Active-8: Crossover 3.67
- E/8412-6 Active-8: LF EQ 3.67
- E/8412-7 Active-8: Equaliser 3.67
- E/8412-8 Active-8: Delay Unit 3.67

How to order: indicate the boards required by ticking the boxes and send this page, together with your payment, to: ETI PCB Service, Argus Specialist Publications Ltd, 1 Golden Square, London W1R 3AB. Make cheques payable to ETI PCB Service. Payment in sterling only please. Prices subject to change without notice.

Total for boards £
Add 45p p&p 0.45
Total enclosed £

**PLEASE ALLOW
28 DAYS FOR
DELIVERY**

Signed

Name

Address

.....

Lineage:

40p per word (minimum 15 words)

Semi Display: (minimum 2 cms)

£11.00 per single column centimetre

Ring for information on series bookings/discounts

All advertisements in this section must be prepaid.

Advertisements are accepted subject to the terms and conditions printed on the advertisement rate card (available on request)



01-437 0699

Send your requirements to:
Jason Inskip
ASP Ltd.,
1 Golden Square,
London W1.

ALARMS

ALARMS

A
D
E

FREE BOOKLET
on
BURGLAR ALARMS
with
LOWEST U.K. DIY PUBLISHED PRICES

PHONE OR WRITE FOR YOUR COPY
051-523 8440
AD ELECTRONICS
217 WARBRECK MOOR
AINTREE, LIVERPOOL L9 0HU

A1 INTRUDER ALARMS

Wholesale Alarm Suppliers

Latest D.I.Y. & Wholesale Published Catalogue.
Write off for your copy

86 Derby Lane, Old Swan, Liverpool 13
Tel: 051 228 3483 or 051-220 0590

IT'S ALARMING!

HOW MANY PEOPLE DON'T
PROTECT THEIR VALUABLE
EQUIPMENT.
TO ADVERTISE HERE
AND INFLUENCE THEIR DECISION
RING JASON INSKIP.
TEL: 437 0699 x331

FOR SALE

AUDIO SIGNAL GENERATORS
10Hz to 100KHz sine, square, toneburst. Sine distortion 0.01%. Accurate calibration. 3V variable plus switched attenuator. Mains powered, £47.50. 100W Mosfet audio amplifier boards with offset protection and thermal cutout. Now only £19.50 including postage. SAE for full details. Renardson Electronics, 119 Lomond Rd., Hull, HU5 5BS.

POWERTRAN CORTEX MICRO-COMPUTER; ready-built, 10 months old, hardly used: £350 o.n.o. (marriage forces sale!) C. Pye 051-521 5762.

VAT INCLUSIVE PRICES. 7805 1A 5v voltage regulator 33p. Resistors, 1/4W carbon film 5% tol. £12 10ohms — 1M (61 resistors) 40p/pack or 0.75p each. di1 sockets 8pin 6p up-to 40 pin 18p. Also capacitors transistors and more. 50p p+p. Phone (0283) 703071 for price list. Hunt Electronics, P.O. Box 57, Derby, DE6 6SN.

EPROMS. Brand new Z716 £3.00 each; 2732 A-4 £4.00 each; 2764-30 £5.00 each; 27128 £18.00 each; 2114 £1.00 each; 4116 £1.20 each; veroracks 19" wide 3v size £15.00 each. VAT. Postage extra. Camberley (0276) 28208.

SECURITY Alarm Systems

FREE COMPREHENSIVE CATALOGUE!

- LOWEST DISCOUNT PRICES
- HIGHEST QUALITY EQUIPMENT
- FREE DIY DESIGN GUIDE
- FULLY ILLUSTRATED
- MICROCHIP CIRCUITRY
- QUICK DESPATCH SERVICE
- FULL INSTRUCTIONS

SEND SAE OR PHONE

C. TEC SECURITY, Dept E |
60 Market St, Wigan WN1 1HX
Telephone (0942) 42444

Trade Enquiries Welcome

BURGLAR Alarm Equipment. Please visit our 2,000 sq. ft. showrooms or write or phone for your free catalogue. C.W.A.S. Ltd., 100 Rooley Avenue, Bradford BD6 1DB. Telephone 0274 731532.

HOME GUARD SYSTEMS

If you want professional alarm/C.C.TV/Door entry/security lighting equipment or DIY kits at genuine trade prices don't delay phone today for our free illustrated catalogue.

Tel: 01-651 2449
Freepost, South Croydon
Surrey CR2 9PU
(no stamp required)

FOR SALE

STEREOAMPS 120 Watt (60+60) ... Case — D.I.N. sockets and controls ... 9-40v/Smoothing ... protected outputs 3/15 -O.H.M. tested and diagrams £10/inc ... KIA-8 Cunliffe Rd., Ilkley.

BARGAIN PACKS our speciality. Send S.A.E. for details plus free samples. Projek Electronics, 44 Mathie Crescent, Gourrock PA19 1YX.

100 WATT FET POWERAMPS £10. Automatic relay protection — mirror input & delayed switch-on ... glass/pcb built ... KIA-8 Cunliffe Road, Ilkley ... Free slider/V.C.

POWERTRAN CORTEX Computer. Basic unit. Most IC bases fitted for optional extras (RS232, discs). £220 o.n.o. Bedford (0234) 766111 evenings) weekends except Friday.

100W AMPLIFIER — £9.95 built or use the same board for 50W, 150W, 200W into 4 or 8 ohms etc., by using alternative output transistors & P.S.U. S.A.E. for full details to ESS Amplification, Unit 11, Argyle St., Hull.

KITS

PRINTED CIRCUITS Make your own simply, cheaply and quickly! Golden Fotolac light-sensitive laquer - now greatly improved and very much faster. Aerosol cans with full instructions, £2.50. Developer 35p. Ferric Chloride 60p. Clear acetate sheet for master 15p. Copper-clad fibreglass board, approx. 1mm thick £2.00 sq. ft. Post/packing 75p. White House Electronics, Castle Drive, Praa Sands, Penzance, Cornwall.

WRONG TIME?

MSF CLOCK is ALWAYS CORRECT — never gains or loses, SELF SETTING at switch-on, 8 digits show Date, Hours, Minutes and Seconds, auto GMT/BST and leap year, also parallel BCD for computer, receives Rugby 60KHz atomic time signals, built-in antenna, 1000Km range, £79-70, get the right TIME. Fun-to-build kit (ready made to order) includes ALL parts, printed circuit, case etc, by-return postage, list of other kits.

CAMBRIDGE KITS
45 (TM) Old School Lane, Milton, Cambs.

VHF TRANSMITTERS

140mm x 370mm. Extremely sensitive, powerful. Operates from 1.5V battery ready built tested only **£9.95** (in kit form **£7.50**).

Also available Automatic Telephone Recorder built tested **£11.95** (in kit form **£8.50**).

All fully guaranteed. Send cash, cheque or P.O. to:

SHAH ELECTRONICS
11 Livingstone Road
Southall, Middlesex
UB1 1TH

ECOLIGHT (ETI July 84) full kit as per article. £21.05. P.C.B. only £4.50. GP Electronics, 87 Willow Tree Ave., Durham DH1 1DZ.

LINSLEY HOOD DESIGNS LOW DISTORTION AUDIO SIGNAL GENERATORS

A0 113 Kit	£28 (p.p. £1)
A0 149 Kit	£39 (p.p. £2)

Super Hi-Fi Amplifier (ETI)
P.C. Boards from £4

Send S.A.E. for further details:
TELERADIO ELECTRONICS
325 Fore Street, London N9 0PE
Tel: 01-807 3719

FOR SALE

ELECTRONIC ORGAN KEY-BOARDS and other parts being cleared out as special offer. Elvins Electronic Musical Instruments, 40A Dalston Lane, London E8. 01-986 8455.

KITS

MINIATURE FM TRANSMITTERS. Frequency 60-145 MHz, range 1/2 mile S.G.F. — P.C.B. All components. Full instructions 9-12v operation, broadcast reception. Super sensitive microphone. Pick-up on FM radio. £6.95 inc; or ready built £8.95: Same day despatch — Zenith Electronics, 21 Station Rd., Industrial Estate, Hallsham, E. Sussex BN27 2EW.

PLANS 'N DESIGN

AMAZING ELECTRONIC plans, lasers, gas, ruby, light shows, high voltage teslas, van de graph surveillance devices, ultrasonics, pyrotechnics, new solar generator, 150 more projects, catalogue. S.A.E. Plancentre, Bromyard Road Industrial Estate, Ledbury HR8.

REPAIRS

MICRO-COMPUTER repairs. ZX Spectrum, VIC 20, C64 Pets, Commodore computers, printers and floppy disk. Phone Slough (0753) 48785. Monday to Saturday.

MISCELLANEOUS

IMPROVE YOUR PROSPECTS

with skills that all employers want. Train the easy way with modern home study courses from Ideal Schools.

MODERN ELECTRONICS

Takes you from the beginning, right up to C & G 224 course, and BTEC national Level.

COMPUTER PROGRAMMING

Learn BASIC with a Spectrum included if you wish



For a free booklet, write today, to: **IDEAL SCHOOLS** (Ref: ETD 2) Freepost, Glasgow G1 4BR

WANTED

TURN YOUR SURPLUS transistors, IC's etc into cash. Contact Coles Harding & Co., 103 South Brink, Wisbech, Cambs. Tel: 0945 584188. Immediate settlement.

BOOKS

PARAPHYSICS JOURNAL (Russian translation); psychotronics, kirlianography, heliophonic music, telekinetics. Computer software. S.A.E. 4 x 9", Paralab, Downton, Wiltshire.

COMPONENTS

FREE! Parcel of components worth £10. Send only 80p postatge. D. Horsley, 113 Clare Rd., Braintree, Essex.

UNAVAILABLE COMPONENTS? If we can't get them nobody can. Quote without obligation or charge. Quote or order period approx 2 weeks. No order is too small. Rickman Components, South Ronaldsay, Orkney KW17 2TW. Phone 085683-430.

Betatran Electronics Supplies

Toroidal transformers primary 250V secondaries 0-40, 0-40V, 0-50, 0-50V, 0.55, 0-55V, 0-70, 0-70V at 300VA £17.55, 500VA £24.70, 625VA £30.50. Can Electrolytics 63V, 6800uF SA 2£4.35. 10,000uF 7A £5.45. 100V 6800uF 8A £6.23. 4700uF 8A £5.50. 3300uF 7A £4.20. 2200uF 7A £3.00. Computer Grade 10,000uF 15A £14.69. MOS-FETs 2SJ 50/2SK 135 £8.50. 2SJ83/2SK 227 £8.20 price per pair. 35A 200V bridge rectifiers £3.25. VAT inclusive £1.00 p&p under £7.00. Full spec. many more. Resistors, capacitors, transistors, heatsinks, amplifiers, speakers, transformers, etc. Send 4 x 9 self addressed envelope for large list.

Laver St., Cavendish, Suffolk CO10 8AP. Tel: 0787 280639.

DIODES IN4001 2 1/2p. UB4005 3p. IN5400 7p. IN5404 9p. IN5408 1 1/2p. BZY88C Zeners 4 1/2p. RESISTORS 1/4 watt 1/2p. Minimum 100 off each item add 15% VAT + 50p carriage.

Webb Electronics
41 Winwick Street, Warrington WAS 2AS
Tel: 54174

DON'T LEAVE IT TO CHANCE, BOOST YOUR BUSINESS NOW BY ADVERTISING IN THE CLASSIFIED PAGES OF ETI PHONE

01-437 0699

FOR DETAILS. BOOKS EXCHANGE SERVICE

BOOKS WANTED FOR CASH

Have you got technical books you no longer need? OR Do you need to read up on a new topic? Then EXCHANGE BOOK CLUB can help YOU! We buy and sell previously read books on electronics and computing. For list of currently available titles and details of our guaranteed buy back plan SAE please to: **JAMES ELECTRONICS, P.O. Box 2 Rothwell, Leeds LS28 0UY**

DO YOU WISH TO LEGALLY TRANSMIT AUDIO SIGNALS OVER BRITISH TELECOM CIRCUITS?

We manufacture approved Interface Equipment for NARROW or WIDE BAND PRIVATE WIRE and PUBLIC SWITCHED TELEPHONE NETWORK circuits. Also TELECOM LINE CIRCUIT SAFETY BARRIERS.

PARTRIDGE ELECTRONICS
The Mixer People

56 Fleet Road, Benfleet, Essex, SS7 5JN, England. (Telephone 03745 3256)

BUMPER BOX OF BITS

WOW! We've got so many components in stock, we can't possibly list them all — So buy a box. In it you'll find resistors, capacitors, displays, switches, panels with transistors, diodes, IC's etc., coils, pots... and so on. All modern parts — guaranteed at least 1000 items, minimum weight 10lbs. ONLY £8.50 inc. 48 page catalogue 50p.

ELECTRONICS WORLD
1e Dews Road, Salisbury, Wilts SP2 7SN

IRISH READERS

MAIL ORDER COMPONENTS

Top quality components
Great prices
Return-of-post service

Write or phone for free price list
WAVEFORM ELECTRONICS
12 Effra Road, Rathmines, Dublin 6.
Phone (01) 0001 if England 987507
Mail order only please

SERVICES

PRINTED CIRCUIT BOARDS manufactured to your specification. Quality, Quick service. Competitive Prices. COPPER-CLAD fibreglass boards cut to size. 1mm thick £1.80 sq. ft. 1.6mm £2.20 sq. ft. Postage 75p. Mondo Circuits Ltd, 35 Grosvenor Road, Twickenham, Middx. Tel: 01-891 5412.

SCOPES

Repaired & recalibrated, all makes, all models. Scopex Safgan, Older TEK, TQ
MENDASCOPE LTD
Otter House
Western Underwood, Olney Bucks MK46 5JS
Tel: Bedford (0234) 712445

JBA ELECTRONICS

Manufactures to design or specifications. One offs, small batch prototypes. Analogue digital electronic equipment. Complete electronic service — no job to small.

1st Floor, 4a Lion Yard
Brecon, Powys, South Wales
Tel: (0874) 611177

FREE PROTOTYPE of the finest quality with every P.C.B. artwork designed by us. Competitive hourly rates, and high standard of work. Halstead Designs Limited. Tel: halstead (0787) 477408.

USE ETI CLASSIFIED SECTION TO SELL YOUR PRODUCT/SERVICE

MISCELLANEOUS

AGENTS

Wanted to Sell Computer Software for most computers. We now have the Dialog Electronics Part I in stock, Pools Winner & Course Winner. We can supply business software, games and computer ad ons. Phone (0288) 4179 up to 9pm most nights for your free list and details about our agents.

SOFTWARE APPLICATIONS

CORTEX SOFTWARE

For the Powertran Cortex computer. **FORTH** — Supplied in two 2564 eproms. Totally standalone supports cassette, 5.25" & 8" discs. Price £35.00 inclusive.

DISCS — Forth utilities, use with above eproms, contains editor, assembler, and utilities. Price £30.00 inclusive.

AUTO-BOOT DISCS
FORTH — Use the Basic 'BOOT' command to download the Forth system, the Forth eproms are not required. Price £55.00 inclusive.

CDOS — Adds file support to Cortex Basic, named program and data files. Includes format and configure utilities. Price £50.00 inclusive. Disc orders, please state 5.25" or 8" s.a.e. with all enquiries to:-

LOMBARD SYSTEMS
18 Lombard Street, Liddington
Bedford MK43 0RP


Either fill in the coupon or phone

01-437 0699

ADVERTISERS INDEX

B. Bamber	70
B.K. Electronics	6
B.N.R. & E.S.	73
Cirkit	22/23
Cricklewood Electronics	10
Crimson Elektrik	47
Cybernetic Applications	12
Dateline	27
Display Electronics	56
Electrovalue	60
Greenbank	47
Greenweld	59
Henry's Audio Electronics	54/55
House of Instruments	70
Hy-Tek Electronics	38
ICS	47
ILP Electronics	65
Kelan Engineering	37
Kemplant	82

Maplin	OBC
Microprocessor Engineering	60
Microrange Electronics	66
Midwich	28/29
MJL Systems Ltd	70
Newrad	59
Powertran	IFC/IBC
Rapid Electronics	8
Riscomp	21
R.T.V.C.	60
R.V.M. Audiotronics	66
Ship Co. Ltd	66
Skywave Software	59
SME	82
Steward of Reading	73
Systems Electronique	82
Technomatic	14/15
TK Electronics	48
Watford Electronics	4/5

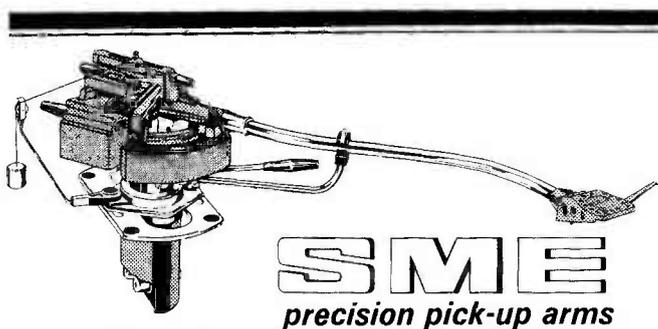

SME
precision pick-up arms

Please call or write:
SME Limited, Steyning, Sussex, BN4 3GY
Telephone: 0903 814321 Telex: 877808 G

'GRIPMATE'
ELECTRONIC ENGINEERS NEED
'Extra hands' for soldering and assembling

The basic 'GRIPMATE' kit consists of a base block secured with the simple but firm clamp. Two 'stayput' wires, with croc-clip ends are held into the block with thumb screws rapidly and positively adjusted to an infinite number of positions to hold and grip small parts and components

BASIC KIT (BLOCK - CLAMP - 2 FLEXI-ARMS) £3.85
2 EXTRA FLEXI-ARMS £1.00
MAGNET ARM £1.50
MAGNIFIER ARM £2.50
ALL INCL VAT POST & PKG
SEND NOW CHO/PO OR SAE DETAILS:

KEMPLANT LTD DURFOLD WOOD,
PLAISTOW, BILLINGSHURST,
WEST SUSSEX, RH14 0PN

TEL 048 649 344

LOOK - IT'S HIS FIRST XMAS SPECIAL!



BEARPARTS

We are the main stockists for **'BEARPARTS'**, the new name in electrical, electronic and audio components.

Interested? Send S.A.E. and receive your **FREE 'BEARPARTS' sample pack.**

CONTENTS OF PACK:
BC 612 Transistor, Red LED, 1N4004 Diode, 11 646 Diode, 560pf 200v Capacitor, 1mf Ceramic Disk Capacitor, 10k, 150k Resistors, 2k Multiturn Potentiometer, 4BA Crimp Eyelet, Rubber Grommet, Instrument Wire, Sleeving.

TREAT YOURSELF THIS XMAS!


COMPLETE SOLDERING KIT

(For the Hobbyist/Electronics Engineer)
FOR LESS THAN £10!!

- Comprises of:-
- Antex Miniature 15W 240v AC Soldering Iron
 - Antex Iron Stand c/w Sponge
 - Desolder Pump
 - 2 mtr Solder
 - Desolder Braid
 - 13A Plug

ONLY £9.85 EX. VAT

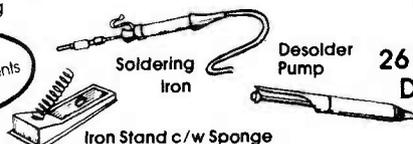10% OFF Bearparts Components & Kits until 1985



LIMITED OFFER WHILE STOCKS LAST!

Call in and see our new counter now open **9.00 - 5.00 Mon-Fri**
9.00 - 12.00 Sat

Too far to call? Don't worry, export/mail order is our speciality. Why not write and find out more.

SYSTEMS ELECTRONIQUE

(U.K.) LTD.

26 Engineer Park, Sandycroft, Deeside, Clwyd CH5 2QD.
Tel: (0244) 536700.

Featured in
Electronics &
Music Maker

TAKE COMPLETE CONTROL OF YOUR MUSIC with the MCS-1 MIDI CONTROLLED SAMPLER

Once again, Powertran and E&MM combine to bring you versatility and top quality from a product out of the realms of fantasy and within the reach of the active musician.

The MCS-1 will take any sound, store it and play it back from a keyboard (either MIDI or 1/8 octave). Pitch bend or vibrato can be added and infinite sustain is possible thanks to a sophisticated, looping system.

All the usual delay line features (Vibrato, Phasing, Flanging, ADT, Echo) are available with delays of up to 32 secs. A special interface enables sampled sounds to be stored digitally on a floppy disc via a BBC microcomputer.

The MCS-1 gives you many of the effects created by top professional units such as the Fairlight or Emulator. But the MCS-1 doesn't come with a 5-figure price tag. And, if you're prepared to invest your time, it's almost cheap!

Specification

- Memory Size: Variable from 8 bytes to 64K bytes.
- Storage time at 32 KHz sampling rate: 2 seconds.
- Storage time at 8 KHz sampling rate: 8 seconds.
- Longest replay time (for special effects): 32 seconds.
- Converters, ADC & DAC: 8 bit companding. Dynamic range: 72 dB.
- Audio Bandwidth: Variable from 12 KHz to 300 Hz.
- Internal 4 pole tracking filters for anti-aliasing and recovery.
- Programmable wide range sine wave sweep generator.
- MIDI control range: 5 octaves.
- +1 V octave control range: 2 octaves with optional transpose of a further 5 octaves.

Digital Delay Line



Introduced in 1982, Powertran's DDL has brought digital quality effects to thousands of musicians. Still available in kit form at only £179.00 + VAT.

£499+
VAT IN KIT
FORM
£699+VAT
READY
BUILT



professional quality MIDI-controlled sampling unit

Write or phone now to place an order.
Powertran Cybernetics Limited,
Portway Industrial Estate,
Andover, Hants, SP10 3EM.
Telephone: 0264 64455



POWERTRAN cybernetics Ltd

PORTWAY INDUSTRIAL ESTATE, ANDOVER, HANTS SP10 3ET

HUNDREDS OF NEW LINES

The amazing Maplin Catalogue is here again! The new edition is packed with hundreds and hundreds of new electronic components to bring you right up to date with all the latest developments. As all home constructors agree (and a good many professionals too) the Maplin Catalogue is the one essential piece of equipment they really need. And now with all our **prices on the page** the Maplin Catalogue is better value than ever.

On Sale From 10th November 1984.

Pick up a copy as soon as it's published at any branch of W.H. Smith or in one of our shops. The price is still just £1.35, or £1.75 by post from our Rayleigh address (quote CA02C).

Post this coupon now for your copy of the 1985 catalogue.
Price £1.35 + 40p post and packing. If you live outside the U.K.
send £2.40 or 11 International Reply Coupons.
I enclose £1.75.

Name

Address

ET112 84

MAPLIN
ELECTRONIC SUPPLIES LTD

Maplin Electronic Supplies Ltd. Mail Order: P.O. Box 3, Rayleigh, Essex SS6 8LR.
Tel: Southend (0702) 552911. • Shops at: 159-161 King Street, Hammersmith,
London W6. Tel: 01-748 0926. • 8 Oxford Road, Manchester. Tel: 061-236 0281.
• Lynton Square, Perry Barr, Birmingham. Tel: 021-356 7292.
• 282-284 London Road, Westcliff-on-Sea, Essex. Tel: 0702-554000.
• 46-48 Bevois Valley Road, Southampton. Tel: 0703-25831. All shops closed all day Monday.

