


PRACTICAL

ELECTRONICS

JANUARY 1976

35p



DIGITAL LOGIC CHECKER

ALSO IN THIS ISSUE...

ROAD-ICE WARNING INDICATOR · AUDIO COMPRESSOR

CMOS FIRST PART OF A NEW SERIES

ALL MAIL ORDER BY
RETURN. C.O.D. SERVICE
WELCOME

C. T. ELECTRONICS

V.A.T.
Unless otherwise stated all prices are
exclusive of VAT. Please check whether
the goods you are ordering are 25% or 8%
Carriage orders under £5 please add 33p
Order over £10 post free in U.K. only
This to be at our discretion

All mail order and enquiries to 270 Acton Lane, Chiswick W4 5DG. Tel. 01-994 6275

SEMICONDUCTORS

AAZ12 25p	BC238 15p	MJ2801 £1.25	TIP35B £2.71	2N2905 30p
AC107 35p	BC239 15p	MJ2901 £1.95	TIP36B £3.50	2N2906 25p
AC125 25p	BC300 30p	MJE340 50p	TIP41B 79p	2N2907 25p
AC126 25p	BC301 30p	MJE370 50p	TIP42B 85p	2N2925 13p
AC128 25p	BC302 30p	MJE371 90p	TIP29C 82p	2N3053 25p
AC175 25p	BC303 35p	MJE520 65p	TIP30C 73p	2N3055 50p
AC187 27p	BCY31 35p	MJE2955 £1.20	TIP31C 80p	2N3232 £1.00
AC188 27p	BCY32 85p	MJE3055 75p	TIP32C 81p	2N3255 £1.10
AC189 27p	BCY33 80p	MM1613 45p	TIP33C £1.20	2N3553 £1.40
AC198 25p	BCY34 85p	MM1712 95p	TIP34C £1.30	2N3643 30p
AC209 25p	BCY38 85p	MFP102 45p	TIP35C £3.00	2N3702 12p
AC219 25p	BCY39 85p	MFP103 45p	TIP36C £3.74	2N3703 12p
AC221 25p	BCY55 £1.50	(MNS457) 35p	TIP41C 90p	2N3704 12p
AD140 68p	BCY70 20p	MFP104 20p	TIP42C £1.00	2N3705 12p
AD142 80p	BCY71 20p	(MNS458) 35p	TIS50 41p	2N3706 12p
AD161 45p	BD121 75p	(MNS459) 40p	ZTX107 15p	2N3707 12p
AD162 45p	BD122 75p	(MNS460) 40p	ZTX300 15p	2N3708 14p
AF114 25p	BD124 70p	OA17 10p	ZTX301 15p	2N3709 14p
AF115 25p	BD131 40p	OA79 10p	ZTX501 25p	2N3771 £1.50
AF116 25p	BD132 50p	OA81 10p	ZTX502 25p	2N3772 £1.80
AF117 25p	BD135 50p	OA90 10p	ZTX550 25p	2N3792 £1.00
AF118 50p	BD136 50p	OA91 10p	IN659 8p	2N3794 30p
AF124 30p	BD139 75p	OA200 10p	IN914 8p	2N3819 35p
AF239 80p	BD140 80p	OA201 10p	IN918 8p	2N3820 55p
BA102 30p	BD153 80p	OA210 35p	IN918 8p	2N3822 70p
BA112 50p	BD156 80p	OA211 35p	IN4001 8p	2N3866 35p
BA114 15p	BDY17 £1.50	OC16 90p	IN4002 9p	2N3904 22p
BA155 15p	BDY18 £1.75	OC19 85p	IN4003 9p	2N3905 25p
BA156 15p	BDY19 £1.90	OC22 55p	IN4004 10p	2N3906 25p
BC107 13p	BF102 20p	OC26 85p	IN4005 12p	2N4014 30p
BC108 12p	BF152 20p	OC28 85p	IN4006 12p	2N4036 82p
BC109 14p	BF166 30p	OC35 80p	IN4006 14p	2N4037 44p
BC109C 14p	BF173 35p	OC36 85p	IN4007 15p	2N4058 14p
BC113 13p	BF180 35p	OC42 40p	IN4007 15p	2N4059 14p
BC114 13p	BF194 16p	OC44 20p	IN2696 25p	2N4061 12p
BC115 15p	BF196 16p	OC45 25p	IN2697 25p	2N4062 12p
BC116 15p	BF197 16p	OC71 15p	IN2706 12p	2N4126 18p
BC117 20p	BF200 35p	OC72 20p	IN2708 12p	2N4280 25p
BC118 15p	BF224 13p	OC75 25p	IN2929 24p	2N4287 25p
BC119 30p	BF24J 18p	OC76 25p	IN2930 25p	2N4289 30p
BC143 25p	BF245 45p	OC77 40p	IN1132 20p	2N4290 25p
BC147 12p	BF259 55p	OC81 25p	IN1302 30p	2N4291 32p
BC148 12p	BFK29 30p	OC82 25p	IN1303 30p	2N4302 45p
BC149 12p	BFK34 30p	OC84 25p	IN1304 30p	2N4444 £1.90
BC149C 14p	BFK39 30p	OC139 30p	IN1305 30p	2N4871 35p
BC157 14p	BFK85 30p	OC170 25p	IN1306 30p	2N4903 £1.30
BC158 14p	BFK86 30p	OC171 30p	IN1307 30p	2N4919 90p
BC159 15p	BFK88 30p	OC200 66p	IN1308 30p	2N5069 £1.30
BC167 14p	BFY10 35p	OC201 65p	IN1309 30p	2N5191 95p
BC168 14p	BFY44 50p	OC202 75p	IN1613 30p	2N5192 £1.20
BC169 14p	BFY50 25p	OC203 75p	IN1613 30p	2N5194 £1.10
BC169C 15p	BFY51 25p	TIP29A 50p	IN1680 80p	2N5195 £1.40
BC172 13p	BFY52 25p	TIP30A 55p	IN1690 85p	2N5245 45p
BC182 12p	BFY53 25p	TIP31A 57p	IN2145 15p	2N5246 35p
BC182L 12p	BFY90 85p	TIP32A 88p	IN2147 90p	2N5296 55p
BC183 12p	BSV68 70p	TIP33A £1.00	IN2160 80p	2N5298 50p
BC183L 12p	BSW63 65p	TIP34A £1.40	IN2217 25p	2N5457 35p
BC184 12p	BSW66 80p	TIP35A £3.29	IN2218 25p	2N5458 35p
BC184L 12p	BSX19 15p	TIP35A £3.58	IN2219 25p	2N5459 40p
BC185 35p	BSX20 15p	TIP41A 70p	IN2222 20p	2N5485 55p
BC186 27p	BSX21 25p	TIP42A 85p	IN2222A 25p	2N5490 55p
BC212 12p	BY127 20p	TIP29B 54p	IN2306 70p	2N5555 85p
BC212L 14p	BY164 85p	TIP30B 60p	IN2369A 50p	2N5777 40p
BC213 12p	IS100 15p	TIP31B 85p	IN2477 30p	
BC213L 12p	IS103 15p	TIP32B 77p	IN2646 50p	
BC214 14p	MJ340 50p	TIP33B £1.08	IN2846 £1.50	
BC214L 15p	MJ481 95p	TIP34B £1.62	IN2904 25p	

QTY DISCOUNTS 12 - 10%, 25 - 15%, 100 - 20%

TTL (full stocks available)

SN7400 18p	SN7412 22p	SN7433 70p	SN7453 20p	SN7451 20p
SN7401 18p	SN7413 40p	SN7437 50p	SN7454 20p	SN7483 £1.00
SN7402 20p	SN7416 30p	SN7440 20p	SN7460 20p	SN7484 90p
SN7403 20p	SN7417 30p	SN7441A 75p	SN7470 30p	SN7489 45p
SN7404 20p	SN7420 20p	SN7442 75p	SN7472 30p	SN7490 75p
SN7405 20p	SN7422 38p	SN7443 £1.00	SN7473 40p	SN7491A 10p
SN7406 30p	SN7423 33p	SN7445 £1.79	SN7474 48p	SN7492 75p
SN7407 30p	SN7425 38p	SN7446 £2.00	SN7475 55p	SN7493 75p
SN7408 20p	SN7427 42p	SN7447 £1.50	SN7476 45p	SN7494 80p
SN7409 40p	SN7428 50p	SN7448 £1.75	SN7480 80p	SN7495 80p
SN7410 13p	SN7430 20p	SN7450 20p	SN7481 £1.25	SN7496 £1.00
SN7411 23p	SN7432 42p	SN7451 20p	SN7483 £1.00	SN7497 £2.25

PERSONAL
CALLERS
ALWAYS
WELCOME

S.C.R.

CRS1 05 40p	CRS1 10 56p	CRS1 20 60p	CRS1 40 65p	CRS1 60 90p	CRS3 10 82p	CRS3 20 82p	CRS3 40 90p	CRS7 400 £1.00	CRS16.100 85p	CRS16.200 90p	CRS16.600 £1.60	C108B 45p	C108D 70p	40669 90p	TIC44 35p	2N4444 £1.90	BT10 500A 90p
-------------	-------------	-------------	-------------	-------------	-------------	-------------	-------------	----------------	---------------	---------------	-----------------	-----------	-----------	-----------	-----------	--------------	---------------

BRIDGE RECTIFIERS

W02 1A 200V 38p	BY164 1 4A 57p	200V 2 6A 80p	100V 2 6A 80p
-----------------	----------------	---------------	---------------

ZENER DIODES

BZV88 Series 400mW	3 3V-33V, 5% 11p	1 5W range 25p	1 10W range 45p
--------------------	------------------	----------------	-----------------

L.E.D.

TIL209 38p	HP5082 28p	MA2082R 20p
------------	------------	-------------

L.D.R.

ORP12 60p

TO3 VOLTAGE REGULATORS

L005 5V 650mA	L036 12V 500mA	L037 15V 450mA
---------------	----------------	----------------

£1.60 each

VEROBOARD

2 1/2 x 3 1/2 32p	0-15 23p
2 1/2 x 5 35p	30p
3 1/2 x 3 40p	35p
3 1/2 x 5 45p	41p
17 x 2 1/2 £1.05	
17 x 3 £1.43	
17 x 5 £1.84	
PIN INS. TOOL 72p	72p
S.P.F. CUTTER 52p	52p
100 PINS SS 30p	30p
100 PINS DS 30p	30p
500 PINS SS £1.55	£1.55
500 PINS DS £1.55	£1.55

ALSO STOCKED

BNC PLUGS at 35p each
UHF (N) PLUGS at 50p each
U.H.F. V.S.W.R. probes ex U.H.F. transmitter
tts 5 each + 8% VAT
All the above are new in original packets.
Please add 8% VAT P & P 30p.

Potentiometers

Linear or Log	Single	Double
Rotary Pots	17p	45p
Rotary Switched	25p	—

★★ SPECIAL OFFERS ★★

MINIATURE MAINS TRANSFORMER. PRI
240V SEC 12V 100mA Manuf Hinchley
Size 36 x 45 x 40mm F.C. 53mm.
Price 1—85p. 100—60p ea. 1,000—50p ea.
10,000—40p ea. 8% VAT.

MINIATURE MAINS TRANSFORMER.
Primary 115/240V Sec. 18W/250mA at 80p ea.
+ VAT and postage 33p. 8% VAT.

MULLARD POT CORE TYPE FX2241 at 60p
ea. + 33p p.p. 8% VAT

24V D.C. SOLENOID by MAGNETIC DEVICES
60p each. 2 1/2 in long x 1/2 in x 8% VAT

240V A.C. SOLENOID. Reversible operation.
twin coil Size approx. 2 1/2 x 1 1/2 x 1 1/2 in 90p

MFC4000 250mW Reg £1.90
Audio 75p
TBA800 5 Watt £1.90
Audio 93p
709C Op Amp D.I.L. 75p
TO99 45p
741C Op Amp 814 D.I.L./TO99 35p
748C Op Amp 75p
D.I.L. 75p
747C Dual Op £1.20

50 GE Diode OA47 equivalent £1.00
8uF 600V WKG PAPER CAPACITORS, ideal
for Strobe Constructors £1.50 each + 8%
VAT + 33p post.

Many other values of PAPER CAPACITORS
in stock. Phone for details.

JACKSON AIRSPACED CAPACITORS
to suit 1/2 in spindle:
100pF Two Gang at 55p + 25% VAT
500pF Two Gang at 75p + 25% VAT.

MULLARD TUBULAR CERAMIC UHF TRIM-
MERS (PROFESSIONAL)
Type 092 0.8-2.2pF }
801 0.8-2.2pF } Price 10p ea.
991 0.5-1.3pF }

QUANTITY DISCOUNTS PLEASE TELEPHONE
1,000pF Feedthrough capacitor 5p ea.
Miniature tubular P.C. trimmers
3-5-13pF 10p ea.
6-30pF 50p ea.
4p c/o Varley 700n relay 50p ea.
Gold Flashed professional TRANSISTOR
SOCKETS. To suit small signal TO18, etc.
30 for £1.00 + 8% VAT.

W. WOUND POTS 10-100kΩ at 30p each
Colvern or Reliance styles + 25% VAT.

VERO EDGE CONNECTOR 24 way 0-1in pitch
30p each + 8% VAT. All the other sizes in
stock.

SIEMENS VARLEY RELAY 4P C/O 700N 24V
50p each.

PLESSEY RELAY 2P C/O 6V operation 40p
each.

MODERN DISC CERAMICS £1.00 a hundred,
£8.00 a thousand + 25% VAT. Phone or write
for list.

ACCESSORIES
DIL SOCKETS, 8 pin 14p, 14 pin 14p, 16 pin
14p. Mica Washers + 2 Bushes (TO3 or
TO66) 4p.

METAL BOXES

ALUMINIUM BOXES IDEAL FOR VERO-
BOARD WITH BASE AND P.K. screws

Length	Width	Height	
AB7 2 1/2 in	5 1/2 in	1 1/2 in	55p
AB8 4 in	4 in	1 1/2 in	55p
AB9 4 in	2 1/2 in	1 1/2 in	55p
AB10 4 in	5 1/2 in	1 1/2 in	55p
AB11 4 in	2 1/2 in	2 in	65p
AB12 3 in	2 in	1 in	50p
AB13 6 in	4 in	2 in	77p
AB14 7 in	5 in	2 1/2 in	90p
AB15 8 in	6 in	3 in	£1.16
AB16 10 in	7 in	3 in	£1.32
AB17 10 in	4 1/2 in	3 in	£1.10
AB18 12 in	5 in	3 in	£1.32
AB19 12 in	8 in	3 in	£1.80

ALUMINIUM BOXES WITH SLOPING TOP
PANEL—IDEAL FOR PRE-AMPS, ETC.,
USING SLIDER CONTROLS

AB20 8 in Long 9 in Wide 3 1/2 in High at
back £2.20
2 in High at front 6 in Slope to front
With P.K. Screws

AB21 As above but 10 in long £2.20
AB22 As above but 12 in long £2.50

★ ★ SPECIAL OFFERS ★ ★

MULTICORE CABLE. 20 way 14/0076 plus Screen at 70p
per yard plus postage by weight.

MULTICORE CABLE. 25-way, individually screened, 14/0076,
£1.00 per yard plus V.A.T. Postage by weight.

3 CORE PVC INSULATED MAINS CABLE. GREY ML6550.
3 x 7/0-2mm Price 100m £4.50; 1,000m £35; 10,000m £330.

METAL OXIDE RESISTORS TR4/5/6 in stock. All values.
1-off price 3p each. Discount on quantity.

10 TURN TRIMPOTS by Bourns, Mec, Painton, etc. All
values in stock. 50p each. Discount on quantity.

KOKUSAI MECHANICAL FILTER. 455 kc/s, 5 kc/s overall
ideal for A.M. £5 each inc. VAT. Postage 33p each.

TRANSFORMER 240V a.c. Primary 1185-0-1185V at 360mA
Secondary. £12 plus 8% VAT plus £1.50 postage.

OMRON OCTAL RELAY 240V A.C. 3P c/o 75p each plus
8% VAT.

SLEEVING 2000 pieces approx. size 1/2 in x 2mm Price £1.60
plus 33p P. & P. plus VAT 8%.

We are open from 9.30 a.m.—6.00 p.m. Monday—Saturday

We have the largest retail selection of components available. Phone or write if you are in difficulties obtaining a particular component.

C.O.D. service welcome. All mail order by return. Official orders welcome by Government establishments, Education authorities, etc.

Tel. 01-994 6275

PRACTICAL ELECTRONICS

VOLUME 12 No. 1 JANUARY 1976

CONSTRUCTIONAL PROJECTS

- ROAD-ICE WARNING INDICATOR** *by A. M. Owen*
A simple early warning device for monitoring driving conditions 22
- IC50 GUITAR AMPLIFIER—2** *by B. W. Terrell & C. F. Terrell*
This concluding article deals with construction and testing 25
- DIGITAL LOGIC CHECKER** *by D. Coles*
A visual in-circuit pocket logic checker 52
- AUDIO COMPRESSOR** *by S. Whitt*
Obtain better recordings with this inexpensive unit 56
- RANDOM TONE GENERATOR** *by W. G. Ross*
An electronic doorbell which can provide a variety of "tunes" at the press of the door switch 58

GENERAL FEATURES

- INGENUITY UNLIMITED**
Headlight Dimmer—Skin Resistance Indicator—Random Generator—Sawtooth Generator—
Sequencing Oscillator—Output Meter—Simple Lights Flasher—Temperature Sensing Device—
Time Switch—Voltage Controlled Zener—Lights-on Reminder—Voice Operated Fader
Modifications—Dwell Meter Modifications 35
- USING CMOS DIGITAL I.C.s—1** *by D. B. Johnson-Davies & A. M. Marshall*
An introductory course to operating principles, practical guidance and experimental
circuits for this fast moving technology 44
- SEMICONDUCTOR UPDATE** *by D. W. Coles* 48
A review of interesting devices

NEWS AND COMMENT

- EDITORIAL**—Small Mercies 21
- SPACEWATCH** *by Frank W. Hyde*
Jodrell Bank—Black Holes and White Holes 31
- BOOK REVIEWS**
Selected new books we have received 32
- MARKET PLACE**
Interesting new products 42
- INDUSTRY NOTEBOOK** *by Nexus*
What's happening inside industry 55
- NEWS BRIEFS**
Viewdata Service—IERE Golden Jubilee 60, 62
- POINTS ARISING**
Light Modulation Unit 62
- PATENTS REVIEW**
Tape Noise Reduction—Electrostatic Loudspeaker—Patent News 65
- READOUT**
A selection of readers' letters 66

Our February issue will be published on Friday, January 9, 1976
(for details of contents see page 49)

© IPC Magazines Limited 1976. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.



CHINAGLIA



PROFESSIONAL QUALITY TEST EQUIPMENT FROM ONE OF ITALY'S LEADING MAKERS **CORTINA MINOR** 33 RANGE POCKET MULTIMETER

- SENSITIVITY 20k Ω /V d.c. and 4k Ω /V a.c.
- ACCURACY $\pm 2.5\%$ d.c. and Ω $\pm 3.5\%$ on a.c.
- 33 RANGES, d.c. V, 0-100mV, 1.5V, 5V, 15V, 50V, 150V, 500V, 1.5kV; d.c. 1, 0-50 μ A, 5mA, 50mA, 500mA, 2.5A; a.c. V, 0-7.5V, 25V, 75V, 250V, 750V, 1.5kV; a.c. 1, 0-25mA, 250mA, 2.5A; 12.5A; dB, -10 to +69 in 6 ranges; Ω 0-10k Ω , 10M Ω .
- ROBUST PROTECTED PRECISION MOVEMENT.
- CLEAR UNAMBIGUOUS DIAL CALIBRATION WITH ANTI-PARALLAX MIRROR.
- COMPACT, MEASURING 155 x 85 x 40mm. WEIGHT 350g WITH INTERNAL BATTERIES.
- PROFESSIONAL COMPONENTS AND CONSTRUCTION STANDARDS THROUGHOUT.
- FULL AFTER-SALES SERVICE AND SPARES FACILITIES.
- SUPPLIED COMPLETE WITH TOUGH CARRYING CASE, LEADS, HANDBOOK AND FULL 12-MONTH GUARANTEE.
- OPTIONAL 30kV d.c. PROBE AVAILABLE.

Meter £19 inc. VAT (80p p.p.). 30kV Probe £9.50 inc. VAT

For details of this and the many other exciting instruments in the Chinaglia range, including multimeters, component measuring, automotive and electronic instruments please write or telephone:

CHINAGLIA

(U.K.) LTD. 19 Mulberry Walk, London
SW3 6DZ Tel: 01-352 1897

TRADE ENQUIRIES WELCOMED

FREE

YOURSELF FOR A BETTER JOB WITH MORE PAY!



Do you want promotion, a better job, higher pay? "New Opportunities" shows you how to get them through a low-cost home study course. There are no books to buy and you can pay-as-you-learn.

This helpful guide to success should be read by every ambitious engineer. Send for this helpful 76 page FREE book now. No obligation and nobody will call on you. It could be the best thing you ever did.

POST NOW

CUT OUT THIS COUPON

CHOOSE A BRAND NEW FUTURE HERE!

Tick or state subject of interest. Post to the address below.

- | | | |
|---|---|--|
| <input type="checkbox"/> Practical Radio and Electronics (Technetron) | <input type="checkbox"/> C & G Radio, TV & Electronics, Mechanics | <input type="checkbox"/> C & G LI Installations and Wiring |
| <input type="checkbox"/> Electronic Engineering | <input type="checkbox"/> Radio Amateurs | <input type="checkbox"/> General Electrical |
| <input type="checkbox"/> Television Maintenance and Servicing | <input type="checkbox"/> Practical TV Colour Television | <input type="checkbox"/> Engineering Society of Engineers (Electrical Engineering) |
| <input type="checkbox"/> General Radio and TV Engineering | <input type="checkbox"/> Servicing Computer Electronics | <input type="checkbox"/> Electrical Installations and Wiring |
| <input type="checkbox"/> Radio Servicing, Maintenance and Repairs | <input type="checkbox"/> C & G LI Radio TV Servicing cert. | <input type="checkbox"/> C & G Electrical Technicians (Primary) |
| | <input type="checkbox"/> Post Master General 1st & 2nd class certs. | <input type="checkbox"/> C & G Telecommunications |
| | <input type="checkbox"/> C & G Electrical Engineering Practise | |

To **ALDERMASTON COLLEGE** Dept. EPE13
Reading RG7 4PF
Also at our London Advisory Office, 4 Fore St. Avenue, Moorgate, London EC2Y 5EJ. Tel: 01-828 2721.

NAME (Block Capitals Please) _____

ADDRESS _____

Other subjects _____ POSTCODE _____

Accredited by C.A.C.C. Member of A.B.C.C.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

See our advert in "Everyday Electronics" for a superb 4 digit clock. Send for details of exciting CMOS design for timing applications.

6 DIGIT CLOCK KITS—contain all components necessary, except for the case, to build an attractive 6 digit alarm clock with beep alarm, snooze function, intensity control.

With 0.5" LED's £23.76

With 0.3" LED's £19.86

Attractive slim case for above with red perspex front panel £2.94

CRYSTAL TIMEBASE KIT: Will provide stable 50 cps for clock IC's, including MK50253 used in our kits, giving time accurate to a few seconds a month; contents: small PCB, 32.768kHz crystal, 3 CMOS IC's, trimmer, zener, C's, R's, IC skts. £8.28

32.768kHz Miniature Watch Quartz Crystal—high accuracy/stability £3.60

MK50253 Versatile clock IC £5.60

AY51224 4 digit clock IC £3.66

MM5314 4/6 digit clock IC £4.44

DL704E 0.3" Red CC LED 85p

FN0500 0.5" Red CC LED £1.50

5LT01 4 digit display £5.80

DL747 0.6" CA LED £2.45

SOLDERCON IC PIN SOCKETS

The sensible method for low cost sockets for IC's, displays, CMOS, strip of 100 for 50p.

40 for £2, 1,000 for £4, 3,000 for £10.50.

CMOS-RCMOTOROLA

Widest stock range in UK—at the new manufacturers' one-off prices

E	E	E	E	E
CD4000 0-17	CD4021 0-83	CD4039 2-86	CD4057 20-35	CD4082 0-18
CD4001 0-17	CD4022 0-79	CD4040 0-89	CD4059 10-64	CD4085 0-59
CD4002 0-17	CD4023 0-17	CD4041 0-89	CD4060 0-92	CD4086 0-59
CD4006 0-97	CD4024 0-64	CD4042 0-89	CD4061 16-43	CD4093 0-86
CD4007 0-17	CD4025 0-17	CD4043 0-83	CD4062 7-33	CD4095 0-86
CD4008 0-79	CD4026 1-42	CD4044 0-77	CD4063 0-90	CD4096 0-86
CD4009 0-46	CD4027 0-46	CD4045 1-15	CD4066 0-58	CD4099 1-50
CD4010 0-46	CD4028 0-74	CD4046 1-10	CD4068 0-18	MC14501 0-32
CD4011 0-17	CD4029 0-94	CD4047 0-74	CD4069 0-18	MC14502 0-85
CD4012 0-17	CD4030 0-46	CD4048 0-46	CD4070 0-18	MC14508 4.20
CD4013 0-46	CD4031 1-81	CD4049 0-46	CD4071 0-18	MC14510 1-26
CD4014 0-83	CD4032 0-88	CD4050 0-46	CD4072 0-18	MC14511 1-95
CD4015 0-83	CD4033 1-14	CD4051 0-77	CD4073 0-18	MC14518 1-83
CD4016 0-46	CD4034 1-56	CD4052 0-77	CD4075 0-18	MC14520 1-83
CD4017 0-83	CD4035 0-97	CD4053 0-77	CD4076 1-27	MC14528 0-87
CD4018 0-83	CD4036 1-82	CD4054 0-95	CD4077 0-18	MC14553 4-07
CD4019 0-46	CD4037 0-78	CD4055 1-08	CD4078 0-18	MC14586 1-21
CD4020 0-92	CD4038 0-88	CD4056 1-08	CD4081 0-18	MC14585 1-45

RCA 1975 CMOS Databook: Pin-Outs, 400 pages of data, 200 pages of circuits, applications and use, £2.87 (no VAT or P. & P.).

ADD VAT at 8% (higher rate does not apply to any of above), 15p P. & P. on orders under £3 (despatch is 1st class post). Price List sent FREE with any order, or on request (a S.A.E. helps). Official orders welcomed (written or phoned)—Universities, Polytechnics, Government, Companies, etc. Export orders (no VAT): add 35p (Europe), £1 (overseas) for air mail P. & P.

SINTEL

53b Aston Street, Oxford Tel. 0865 43203

SAXON

ENTERTAINMENTS LTD.

SYSTEM 7000


professional standards · realistic prices

NEW POWER AMPLIFIERS FROM 30 TO 120 WATTS R.M.S.

From Saxon Entertainments come three brilliant new power modules each employing the same circuitry, using 10 transistors, three diodes and one zener diode with electronic over temperature cutout as well as normal thermal protection, load line short circuit and incorrect load protection, integrally mounted output capacitor. Fused supply and output terminals. May be solder or screw connected. The input impedance is high enough to accept all types of mixer having an output of 250mV. Since its recent introduction, the SA.1208 with its 120 watts R.M.S. into 8Ω and excellent reliability has proved exceptionally popular all round.

New features—new performance standards

- ★ New 90°C overtemperature cutout (electronic not mechanical).
- ★ New integral output capacitor, no external components required for normal operation.
- ★ Short circuit load line type protection with twin summing amplifiers.
- ★ Inherently open circuit proof.
- ★ Input sensitivity — 10dBm (240mV into 100k) ie suitable for most mixers. Response 20Hz-40kHz ± 1dB.
- ★ Typical distortion 0.4% (Noise — 80dB).
- ★ Compact: 15cm × 8cm × 3cm.
- ★ Suitable for all public address, discotheque, and group applications.
- ★ Fused supply terminal.
- ★ Single supply line (split supply not required).

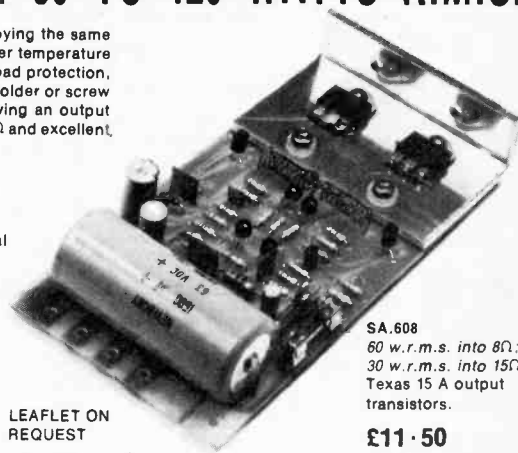


LEAFLET ON REQUEST

SA.1208
120 watts RMS
into 8Ω £16.00

SA.608
60 w.r.m.s. into 8Ω;
30 w.r.m.s. into 15Ω
Texas 15 A output
transistors.

£11.50
SA.308
30 watts RMS
into 8Ω £9.00

SYSTEM 7000 DISCOTHEQUE CONTROL UNIT

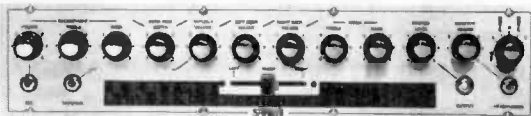

- ★ Mono or stereo.
- ★ 2 Deck and one tape inputs, individually controlled, plus L/R deck fader (ineffective at central).
- ★ Wide range bass and treble controls plus separate MIC volume bass and treble controls. Overall master control.
- ★ Continuously variable autofade depth and threshold.
- ★ Five position monitoring switch with two mute positions—ample headphone power.
- ★ Complete, cased with all terminations by plug/socket, etc.
- ★ Noise — 80dB. Response 20Hz-50kHz ± 1dB.
- ★ Stainless steel escutcheon, boldly designed.

Mono £28.50

Stereo £45.00

Send for full descriptive leaflet.

IN MODULAR FORM

Assembled on P.C.B. Similar characteristics to above. Ideal for constructors.

Mono £18.50 Stereo £27.50

SYSTEM 7000 MODULAR MIXING—UP TO 20 CHANNELS

- Complete versions of the IM7001 and IM7200 modules shown in our advertisement make a professional quality versatile mixer to your requirements using these modules mono and stereo inputs may be combined.
- ★ The mixing modules split mono signals.
 - ★ Each input module has own monitor switch.
 - ★ Stainless steel panel on 15cm × 5cm matrix (approx.).
 - ★ Input equalisation for all types of signal inc. magnetic cartridge.
 - ★ Complete system may comprise twenty channels, mono or stereo with ample monitoring power.
 - ★ May be patched in with disco mixers or Minotaur amplifier.



Mono Input Module £8.50

Stereo Input Module £12.00

Mono Mixer Module £8.50

Stereo Mixer Module £12.00

Power Supply Unit for up to 20 Modules £7.50

NEW POWER SUPPLY UNITS

- ★ One piece, ready to wire assembly with integral glassfibre pcb.
- ★ Grain oriented laminated transformers for compactness.
- ★ Facilities for preamp supply.
- ★ Fully fused.
- ★ Size of all models 10 × 8 × 13cm.

PM1201 95 volts for one SA1208 £11.00
 PM1202 95 volts for two SA1208 £14.00
 PM601 65 volts for one or two SA608 £9.00
 PM301 45 volts for one or two SA308 £7.50

MINOTAUR AMPLIFIER

- 100W r.m.s. into 8Ω.
- ★ Two mixed inputs, wide range bass and treble controls.



- ★ May be operated as a slave amplifier.
- ★ Extremely compact (27cm × 16cm × 10cm).
- ★ Fully protected against all incorrect loads and short circuits.

£47.50

SYSTEM 7000 LIGHTING CONTROL UNIT

- ★ 1000 watts per channel. Sound light and SEQUENTIAL and OVERRIDE.
- ★ Individual control of bass middle and treble.
- ★ Master control for easy adjustment.
- ★ Plug/socket terminations throughout.
- ★ Slider control for function, allows sound/light, sequencing or combination of both.
- ★ Stainless steel front panel to match disco control unit.
- ★ Electronic override eliminates clicks.



£35.00

SAXON SUPERFECT LIGHT UNIT

THE MODULAR VERSION OF SYSTEM 7000 LIGHT CONTROL UNIT
 Sequential display with variable speed. Continuously variable function display with no signal. Carries 1,000 watts per channel. Separate bass, middle, treble and master audio controls, etc.

£19.75

SAXON SOUNDLITE

Our outstandingly successful 3,000 watt unit in modular form. £13.50

GUARANTEE

All Saxon Entertainments' modules and units are guaranteed for twelve months from date of purchase.

Terms of business

Phone orders to 01-684 6385 for C.O.D. payment or by Access or Barclaycard.
 Ordering by post, make cheques, postal orders payable to Saxon Entertainments Ltd., crossed, or send Access or Barclaycard No.
 Shop hours—Monday to Saturday 9 a.m. to 5 p.m.
 Prices subject to alteration without notice.

TRADE ENQUIRIES TO:

NORMAN ROSE ELECTRICAL LTD.

Phone—London: 01-837 9111; Manchester: 061-273 1498; Birmingham: 021-236 4710; Bradford: 0274 24008.

PRICES INCLUDE CARR. & PACKING, BUT V.A.T. AT 8% MUST BE ADDED TO VALUE OF ALL ORDERS. S.A.E. WITH ALL ENQUIRIES
SAXON ENTERTAINMENTS LTD. 329 Whitehorse Road, W. Croydon, Surrey CR0 2HS
 Telephone: Sales 01-684 0098; Service 01-684 6385

CRESCENT RADIO LTD.

11-15 & 17 MAYES ROAD, LONDON N22 6TL
(also) 13 SOUTH MALL, EDMONTON, N.9

MAIL ORDER DEPT.
1 ST. MICHAELS TERRACE, WOOD GREEN
LONDON N22 4SJ Phone 888-4474

BARGAIN PROJECT BOX

A plastic box with moulded extrusion rails for PC or Chassis panels with metal front plate fitted with four screws (all supplied).
An ideal box to give a small project a professional finish.
SIZE (Internal) 81mm x 61mm x 28mm.
OUR PRICE 40p. + 8%.



10in 8ohm DUAL CONE L/S Manufactured by "ELAC" to a very high standard.

These loudspeakers are a real bargain. SPEC:—Size—10in. Dual Cone Power—10 Watts. Frequency—40-12000Hz. + 25%. Our price £3.75 ea.

I.C. SOCKETS + 8%

D.I.L.
8 pin—13p 24 pin—24p
14 pin—14p 28 pin—28p
16 pin—14p 36 pin—36p

MINIATURE RELAYS

Brand new range of British made relays, size: 1 1/4in x 1in x 1in. All two changeovers with 250V 1.5A contacts and suitable for fitting on 0.1m veroboard.
Type Volts Current Ohms
27/A 12V 17mA 700 All
21/A 12V 28mA 430 £1.30
12/A 6V 33mA 18p + 8%.

MINI LOUSPEAKERS

2 1/2" 80 ohm 60p
2 1/4" 40 ohm 60p
2 1/4" 8 ohm 60p
+ 25%.

LOW PRICE TRANSISTORS

BF308B 15p TIP42A 75p
AC142R 25p OGT75 26p
BC149B 15p AA129 8p

I.C.

EXTRACTION TOOL
Saves damage to valuable I.C.s
ONLY 40p + 8% VAT

CRESCENT BUBBLE LIGHT SHOW

This budget system compares very favourably with more sophisticated and higher priced models.
Specifications:
Projector—150W convection cooled. At 30ft the projected image is 16ft.
Motor—1 rev. per 2 min.
Liquid Wheel—6in diameter multi colour.
The motor is fitted to the projector and can only be purchased as a single unit.
The liquid wheel is our standard model and may be purchased separately.
A bargain at: Projector, £15; Wheel, £5. Total £20. Plus 75p carr. + 8%.

CABLE LESS SOLDERING IRON WAHL "ISO-TIP"

* Completely portable.
* Solders up to 150 joints per charge.
* Recharges in its own stand.
* Fine tip for all types of soldering.
* Only 8in long and weighs just 6 ozs.
OUR PRICE £9.75 + 8%.
(Spare bits are available)

"CRESCENT" 100 WATT R.M.S. ALL PURPOSE AMPLIFIER U. BUILD IT

We supply the three modules for you to build this Disco-Group-P.A. amplifier into the cabinet of your choice.

★ THE POWER AMP MODULE
170W r.m.s. sq. wave 300W instantaneous peak into 8 ohm (60W into 16 ohm).

★ THE PRE-AMP MODULE
Four control pre-amp, Vol. Bass, Treble, Middle controls. Designed to drive most amplifiers using F.E.T. first stage.

★ THE POWER SUPPLY
Is supplied complete with the mains transformer. Complete fixing instructions are supplied and no technical knowledge is required to connect the three ready wired modules. A fantastic bargain. £27.50, carr. £1.20. Send B.A.E. for further details on this or our ready built amplifiers. + 8%.

12-0-12V 500M/A

240V primary transformer bargain. Approx. size: 60mm x 40mm x 50mm; fixing centres: 75mm. Our price £1.20. + 8%.

FERRIC CHLORIDE

Anhydrous ferric chloride in double sealed one pound poly pack. Size: 100mm x 100mm x 100mm. Our Price 65p per lb. + F/P + VAT @ 8%.

LOW NOISE, LOW PRICE CASSETTES

Good quality tape in well made screw type cassettes. Presented in single plastic cases.
C60 81p C90 42p C120 63p
10% discount on ten or more cassettes of one type. + 8%.

ABS PLASTIC BOXES

Handy boxes for construction projects. Moulded extrusion rails for P.C. or chassis panels. Fitted with 1mm front panels. 1006, 105mm x 75mm x 45mm 55p; 1006, 150mm x 75mm x 47mm 72p; 1007, 184mm x 124mm x 60mm £1.28; 1021, 106mm x 74mm x 45mm (sloping front) 55p. + 8%.

P.C. ETCHING KIT

This kit contains all that the constructor will need to etch the circuits of his own design. Contents: Plastic etching dish. Sample copperclad board. Laminiate Cutter. 1 lb Ferric Chloride. Large Plastic Spoon. Etch Resist Pen. Full Etching Instructions. Complete and Big Kit Value at £3.75 + 8% VAT.

2in. PANEL METERS

Size 59mm x 46mm
0-50µA —ME6 0-100mA —ME13
0-100µA —ME7 0-500mA —ME14
0-500µA —ME8 0.1A —ME15
0-1mA —ME9 0-50V —ME16
0-5mA —ME10 0-300V a.c. —ME17
0-10mA —ME11 S meter —ME18
0-50mA —ME12 V.U. meter —ME19
£3 each. + 8%.

POWER PACKS


PP1 Switched 3-41-6.71-9 and 12V at 500M/A with on/off switch and pilot light. Size 130M/M x 55M/M x 75M/M. only £4.
PP2 Switched 6.71-9V Battery Eliminator. Approx. size 2 1/2in x 2 1/2in x 3 1/2in. Ideal for cassette recorders, £3.25.
PP3 Car converter. From 12V Pos. or Neg. to = 6.71-9V. Easy to fit and transistor regulated. £3.90. + 8%.

TELESCOPIC AERIAL

Nine section fully swivelling telescopic aerial with 1/4in single bolt fixing or two hole fixing bracket. Fully extended 43". Fully closed 7". Our Price 50p + F/P + VAT @ 25%.

3 KILOWATTS PSYCHEDELIC LIGHT CONTROL UNIT

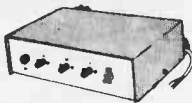Three Channel: Bass, Middle, Treble. Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier, and connect three 250V up to 1000W lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed.)
£18.50 plus 75p P. & + 8%.



12in LONG PERSISTENCE CRT. Full spec. Price £6.50 to include V.A.T. and Carriage.

MAKE YOUR SINGLE BEAM SCOPE INTO A DOUBLE WITH OUR NEW LOW PRICED SOLID STATE SWITCH. 2Hz to 8MHz. Hook up to a 9 volt battery and connect to your scope and have two traces for ONLY £6.75, P. & P. 25p. (Not cased, not calibrated.)

WIDE RANGE WOBBLATOR. 5MHz to 150MHz up to 15MHz sweep width. Only 3 controls, preset RF level, sweep width and frequency. Ideal for 10-7 or TV IF alignment filters. receivers. Can be used with any general purpose scope. Full instructions supplied. Connect 6-3V a.c. and use within minutes of receiving. All this for ONLY £6.75, P. & P. 35p. (Not cased, not calibrated.)

20Hz to 200kHz WB, SINE and SQUARE GENERATOR. Four ranges. Independent amplitude controls, thermistor stabilised. Ready to use. 9V supply required. £8.85 each. SINE WAVE only £6.85 each. P. & P. 35p. (Not cased, not calibrated.)

GRATICULES 12cm x 14cm high quality plastic 15p each. P. & P. 8p.

*Large quantity of good quality components—NO PASSING TRADE—so we offer 3lb of ELECTRONIC GOODIES for £1.70. Post paid.

*METER PACK—3 different meters for £2. P. & P. 55p.

MIN TRANSFORMER. 240V input. 3V 1A output. Brand new 65p each, P. & P. 20p. P.C.B. PACKS. S & D. Quantity 2 sq. ft—no tiny pieces. 50p, P. & P. 37p.

*CAPACITOR PACK—50 brand new components, only 50p, P. & P. 37p.

*TRIMMER PACK. 2 twin 50/200pF ceramic. 2 twin 10/60pF ceramic; 2 min strip with 4 preset 5/20pF on each; 3 air spaced preset 30/100pF on ceramic base. ALL BRAND NEW. 25p the lot, P. & P. 15p.
*PHOTOCELL equ. OCP71, 13p each.
*MULLARD OCP70, 10p each.

DELIVERED TO YOUR DOOR, 1cwt of Electronic Scrap chassis, boards, etc. No rubbish. FOR ONLY £4.

*MODERN TELEPHONES. Type 706: two tone grey or black. £3.75 each. Type 7006: two-tone grey or green. £3.75 each. Style similar to Type 746: grey, or black. £3 each. As above but discoloured, grey only. £2 each. P. & P. all types 45p each.

*HANDSETS. Complete with 2 inserts and lead. £1.25 each, P. & P. 37p.
*DIALS. ONLY 50p each, P. & P. 25p.

*HIGH VALUE—PRINTED BOARDPACK. Hundreds of components, transistors, etc.—No 2 boards the same. No short leaded transistor computer boards. £1.75, post paid.

*CRYSTALS & 43MHz. Brand new. £1.25 each, P. & P. 15p.

RESETTABLE COUNTERS—4 digit by Sedoc/Stonebridge. 1,000 ohm coil. £2 each, P. & P. 35p.

*BEEHIVE TRIMMER 3/30 pF. Brand new. Qty 1-9 13p each, P. & P. 15p; 10-99 10p each, P. & P. 25p; 100-999 7p each, P. & P. free.

HE CRYSTAL DRIVE UNIT. 19in rack mount. Standard 240V input with superb crystal oven by Labgear (no crystals) £5 each, Carr. £2.

*1,000pF FEED THRU CAPACITORS. Only sold in packs of 10. 30p, P. & P. 15p. SOME OSCILLOSCOPES ALWAYS AVAILABLE. S.A.E. stating specification and price range.

VAT NOT INCLUDED IN PRICE
Goods marked * 25% VAT, otherwise 8%
OPEN 9 a.m. to 6 p.m. ANY DAY



CHILTHEAD LTD

7/9 ARTHUR ROAD, READING, BERKS.
(rear Tech. College) Tel: Reading 582605.




ANOTHER PRICE BREAKTHROUGH!

6 DIGIT CLOCK KIT

£6.95

+ 75p Airmail postage

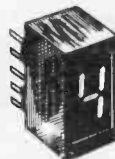

- ★ SLOW SET
- ★ FAST SET
- ★ TIME HOLD
- ★ 12/24 HOUR
- ★ 50/60HZ
- ★ BRIGHT LEDS

Readout shown actual size

From the people who brought you the world's first Digital Wristwatch Kit, comes another fine quality timepiece at a remarkably low price. You get only prime quality, tested components with all our kits.

KIT COMPRISES





- 1—NATIONAL MM5314 clock chip 12/24 hour, 50/60Hz option.
- 6—FAIRCHILD Readouts, bright red, 0.27in character height.
- 7—Npn + 6 pnp silicon transistors.
- 4—1N4001 rectifier + 1—1N914 switching diodes.
- 9—Carbon film resistors.
- 1—1000µF/25V filter cap + 2 disc caps.
- 2—Pushbutton switches for slow and fast settings.
- 1—Slide switch for time hold.
- 2—Etched and drilled printed circuit boards.
- 1—Illustrated assembly instructions manual.

NO KNOWLEDGE OF ELECTRONICS REQUIRED TO BUILD THIS KIT. All you need to provide is a 9-15V/200mA transformer and a case of your choice. SATISFACTION GUARANTEED.



The above price shown in British £'s is the approximate equivalent of U.S. \$16.50 for the kit including airmail postage. Send Bank Draft of International Money Order in U.S. funds. The prices quoted do not include any taxes leviable by a purchaser's country of residence.

SABTRONICS INTERNATIONAL

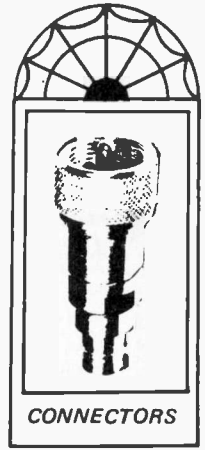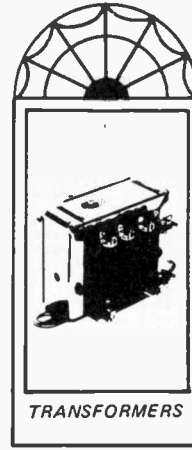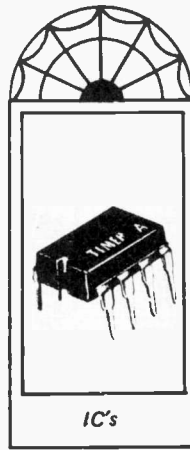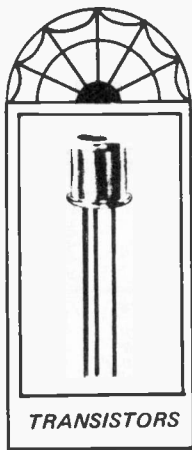P.O. Box 64683, Dallas, Tx. 75206, U.S.A.



Use DORAM components for your project

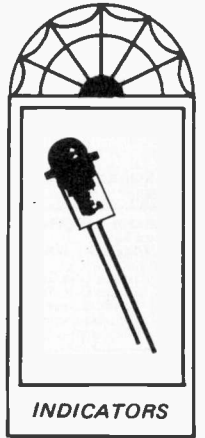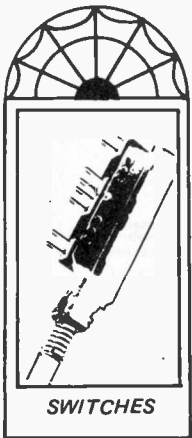

The doorway to Amateur Electronics



- ★ DORAM'S NEW CATALOGUE OFFERS THOUSANDS UPON THOUSANDS OF QUALITY ELECTRONIC COMPONENTS AND AUDIO ACCESSORIES FROM TRUSTED BIG NAME MANUFACTURERS.
- ★ ALL COMPONENTS ARE INDIVIDUALLY CODED AND PRICED - MANY NEW COMPONENTS ADDED FROM CUSTOMER REQUESTS.
- ★ 16 EXTRA PAGE DATA SECTION.
- ★ UNIQUE FREE UP-DATE PRODUCT INFORMATION SERVICE DURING LIFE SPAN OF CATALOGUE.
- ★ ALL COMPONENTS SENT BY RETURN OF POST.
- ★ POST AND PACKING FREE (only applies for Great Britain, N. Ireland and B.F.P.O. Nos. - overseas orders F.O.B.)
- ★ NO QUIBBLE REPLACEMENT PART SERVICE

The doorway to amateur electronics

DORAM

DORAM ELECTRONICS LIMITED
P. O. Box TR8
Leeds LS12 2UF

I enclose 60p. Please send me by return my new Doram Catalogue. (Overseas orders except for B.F.P.O., please add 30p for post and packing surface only).

An Electrocomponents Group Company

PLEASE PRINT BLOCK CAPITALS



NAME _____

ADDRESS _____

Post Code _____

COMPONENTS

CARBON RESISTOR PAKS

These Paks contain a range of Carbon Resistors, assorted into the following groups:

R1	50	Mixed	100 ohms-820 ohms	1/8th W	0-60
R2	50	Mixed	1K ohms-8.2K ohms	1/8th W	0-60
R3	50	Mixed	10K ohms-82K ohms	1/8th W	0-60
R4	50	Mixed	100K ohms-820K ohms	1/8th W	0-60
R5	30	Mixed	100 ohms-820 ohms	1/2 W	0-60
R6	30	Mixed	1K ohms-8.2K ohms	1/2 W	0-60
R7	30	Mixed	10K ohms-82K ohms	1/2 W	0-60
R8	30	Mixed	100K ohms-820K ohms	1/2 W	0-60

THESE ARE UNREPEATABLE PRICES

LOW COST CAPACITORS

500	µF	50V Elect	0-09 each
0-01	µF	400V	0-03 each

REPANCO CHOKES & COILS

RF Chokes	CHI	2.5mH	0-27
	CH3	7.5mH	0-29
	CH5	1.5mH	0-26
	CH2	5.0mH	0-28
	CH4	10mH	0-31

COILS DRX1	Crystal set	0-29 DRR2	Dual
range			0-42

CARBON POTENTIOMETERS

Log and Lin	4.7K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M,		
VC 1	Single Less Switch		0-14
VC 2	Single D.P. Switch		0-26
VC 3	Tandem Less Switch		0-43
VC 4	1K Less Switch		0-14
VC 5	100K anti-Log		0-43

HORIZONTAL CARBON PRESETS

0-1W			0-06 each
100, 220, 470, 1K, 2.2K, 4.7K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M, 4.7M,			

REPANCO TRANSFORMERS

240V, Primary, Secondary voltages available from selected tapings 4V, 7V, 8V, 10V, 40V, 50V and 25V 0-25V.			
Type	Amps	Price	P & P
MT50/4	1	£1.79	0-45p
MT50/1	1	£2.24	0-48p
MT50/2	2	£3.06	0-60p

COIL FORMERS & CORES

NORMAN 1/2"	Cores & Formers	0-07p
1/4"	Cores & Formers	0-09p.

SWITCHES

DP/DT Toggle	0-28p	SP/ST Toggle	0-22p
--------------	-------	--------------	-------

FUSES

1 1/2" and 20mm, 100mA, 200mA, 250mA, 500mA, 1A, 1.5A, 2A QUICK BLOW.			
Anti-serve 20mm only		0-30p each	0-08p each

VEROBOARDS

VBI containing approx. 50 sq. ins various sizes all 0-1 matrix		★0-60p
VB2 containing approx. 50 sq. ins various sizes all 0-15 matrix		★0-60p

DECON-DALO 33PC Marker

Ech resistant printed circuit marker pen. Full instructions supplied with each pen. ★0-92p

BATTERY HOLDERS

Takes 6 H.P. 7s complete with terminal clip and lead ★0-31p each

CABLES

CP 1	Single lapped screen	Per Metre	★0-08
CP 2	Twin Common Screen		★0-11
CP 3	Stereo Screened		★0-12
CP 4	Four Core Common Screen		★0-21
CP 5	Four Core individually screened		★0-28
CP 6	Microphone Fully Braided Cable		★0-11
CP 7	Three Core Mains Cable		★0-11
CP 8	Twin Oval Mains Cable		★0-08
CP 9	Speaker Cable		★0-06
CP 10	Low Loss Co-Axial		★0-14

INSTRUMENT CASES ★

(In 2 sections, Black Vinyl covered top and sides and bezel)

No.	Length	Width	Height	Price
BV1	8"	x 5 1/2"	x 2"	★£1.25
BV2	11"	x 6"	x 3"	★£1.62
BV3	6"	x 4 1/2"	x 1 1/2"	0-92
BV4	9"	x 5 1/2"	x 2 1/2"	£1-39

ALUMINIUM BOXES ★

No.	Length	Width	Height	Price
BA1	5 1/2"	x 2 1/2"	x 1 1/2"	★0-45
BA2	4"	x 4"	x 1 1/2"	★0-45
BA3	4"	x 2 1/2"	x 1 1/2"	★0-45
BA4	5 1/2"	x 4"	x 1 1/2"	★0-54
BA5	4"	x 2 1/2"	x 2"	★0-45
BA6	3"	x 2"	x 1"	★0-39
BA7	7"	x 5"	x 2 1/2"	★0-79
BA8	8"	x 6"	x 3"	★£1-02
BA9	6"	x 4"	x 2"	★0-63

(Each complete with 1/2" deep lid & screws) PLEASE ADD 20p POSTAGE AND PACKING FOR EACH BOX.

COMPONENT BOXES

Pak No.	Qty.	Description	Price
C1	200	Resistors mixed values approx. count by weight	0-60
C2	150	Capacitors mixed values approx. count by weight	0-60
C3	50	Precision Resistors mixed values	0-60
C4	75	1/8th value Resistors mixed preferred values	0-60
C5	5	Pieces assorted Ferrite Rods	0-60
C6	2	Tuning Gangs, MW/LW VHF	0-60
C7	1	Pak Wire 50 metres assorted colours	★0-60
C8	10	Reed Switches	0-60
C9	3	Micro Switches	0-60
C10	15	Assorted Pots & Pre-Sets	0-60
C11	5	Jack Sockets 3 x 3.5m, 2 x standard Switch Type	0-60
C12	30	Paper Condensers preferred types mixed values	0-60
C12 20		Electrolytics Trans. types	0-60
C14	1	Pack assorted Hardware - nuts/Bolts, Grommets, etc.	★0-60
C15	5	Mains Slide Switches, 2 Amp.	0-60
C16	20	Assorted Tag Strips & Panels	0-60
C17	10	Assorted Control Knobs	0-60
C18	4	Rossey Wave Change Switches	0-60
C19	2	Relays 6-24V Operating	0-60
C20		Sheets Copper Laminat	★0-60

Please add 20p post and packing on all component packs, plus a further 10p on pack nos. C1, C2, C19 & C20.

AVDEL BOND ★

SOLVE THOSE STICKY PROBLEMS!

with

CYANOCRYLATE C2 ADHESIVE

The wonder bond which works in seconds - bond plastic, rubber, transistors, components permanently, immediately!

OUR PRICE ONLY 60p for 2gm phial

ACCESSORIES ★

BIB HI-FI

Ref.	Description	Price
B	Stylus and turntable cleaning	★31p
J	Tape head cleaning kit	★60p
P	Hi-Fi cleaner	★30p
9	Wire stripper/Cutter	★94p
31	Cassette head cleaner	★50p
32	Tape editing kit	★£1-64
32A	Stylus balance	★£1-24
66A	Record stylus cleaning kit	★32p
42	De Luxe Groov-Kleen	★£1-84
43	Record care kit	★£2-68
45	Auto changer groove cleaner	★90p
46	Spirit level	★60p
58	Hi-Fi stereo hints & tips	★30p
60	Chrome finish as above	★£1-72

ANTEX EQUIPMENT ★

SOLDERING IRONS

X25.21W	★£2-45
Model G. 18W	★£2-70
CCN 240. 15W	★£2-90
SK2. Soldering Kit	★£3-90

BITS AND ELEMENTS

Bit No.			
102	for model CN240 3/32"	★42p	
104	for model CN240 3/16"	★42p	
1100	for model CCN240 3/32"	★42p	
1101	for model CCN240 3/8"	★42p	
1102	for model CCN240 1/2"	★42p	
1020	for model G240 3/32"	★42p	
1021	for model G240 1/8"	★42p	
1022	for model G240 3/16"	★42p	
50	for model X25 3/32"	★44p	
51	for model X25 1/8"	★44p	
52	for model X25 3/16"	★44p	

ELEMENTS

Model EX25	★£1-20
Model ECN240	★£1-10
Model EG240	★£1-35
Model ECCN240	★£1-35

SOLDERING IRON STAND

ST3 Suitable for all models	★£1-10
Antex heat shunt	★10p

PLUGS

PS	Description	Price
PS 1	DIN 2 pin (Speaker)	0-10
PS 2	DIN 3 pin	0-11
PS 3	DIN 4 pin	0-14
PS 4	DIN 5 Pin 180°	0-15
PS 5	DIN 5 Pin 240°	0-15
PS 6	DIN 6 Pin	0-16
PS 7	DIN 7 Pin	0-17
PS 8	Jack 2.5mm Screened	0-17
PS 9	Jack 3.5mm Plastic	0-11
PS 10	Jack 3.5mm Screened	0-17
PS 11	Jack 1/2" Plastic	0-14
PS 12	Jack 1/2" Screened	0-20
PS 13	Jack Stereo Screened	0-33
PS 14	Phono	0-09
PS 15	Car Aerial	0-14
PS 16	Co-Axial	0-14

INLINE SOCKETS

PS	Description	Price
PS 21	DIN 2 Pin (Speaker)	0-18
PS 22	DIN 3 Pin	0-19
PS 23	DIN 5 Pin 180°	0-19
PS 24	DIN 5 Pin 240°	0-19
PS 25	Jack 2.5mm Plastic	0-13
PS 26	Jack 3.5mm Plastic	0-13
PS 27	Jack 1/2" Plastic	0-28
PS 28	Jack 1/2" Screened	0-32
PS 29	Jack Stereo Plastic	0-28
PS 30	Jack Stereo Screened	0-35
PS 31	Phono Screened	0-17
PS 32	Car Aerial	0-20
PS 33	Co-Axial	0-20

SOCKETS

PS	Description	Price
PS 35	DIN 2 Pin (Speaker)	0-07
PS 36	DIN 3 Pin	0-09
PS 37	DIN 5 Pin 180°	0-09
PS 38	DIN 5 Pin 240°	0-10
PS 39	Jack 2.5mm Switched	0-11
PS 40	Jack 3.5mm Switched	0-11
PS 41	Jack 1/2" Switched	0-19
PS 42	Jack Stereo Switched	0-28
PS 43	Phono Single	0-07
PS 44	Phono Double	0-09
PS 46	Co-Axial Surface	0-09
PS 47	Co-Axial Flush	0-19

P.C.B. KITS & PENS ★

PROFESSIONAL D.I.Y. PRINTED CIRCUIT KIT £7-80

Containing 6 sheets of 6" x 4" single sided laminate, a generous supply of etchant powder, etching dish, etchant measure, tweezers, etch resistant marking pen, high quality pump drill with spare, cutting knife with spare blades, 6" metal ruler, plus full easy to follow instructions. Spare container of etchant for above ★60p

PCB Pens 2 x Quality marker pens specifically designed for drawing fine line etch resistant circuits on copper laminate. Complete with full instructions. ★£1-53 per pair.

LOW NOISE CASSETTES ★

C60	★33p
C90	★44p
C120	★56p

AUDIO LEADS

S221	5 pin DIN plug to 4 phono plugs length 1.5m	£1-08
S222	5 pin DIN plug to 5 pin DIN socket length 1.5m	68p
S237	5 pin DIN plug to 5 pin DIN plug mirror image length 1.5m	£1-20
S238	2 pin DIN plug to 2 pin DIN socket length 5m	68p
S268	5 pin DIN plug to 3 pin DIN plug 1 & 4 and 3 & 5 length 1.5m	£1-00
S270	2 pin DIN plug to 2 pin DIN socket length 10m	80p
S271	5 pin DIN plug to 2 phono plugs connected to pins 3 & 5 length 1.5m	70p
S275	5 pin DIN plug to 2 phono sockets connected to pins 3 & 5 length 1.5m	68p
S318	5 pin DIN socket to 2 phono plugs connected to pin 3 & 5 length 23cm	68p
S404	Coiled stereo headphones extension cord extends to 7m	£1-40
S217	3 pin DIN plug to 3 pin DIN plug length 1.5m	80p
S219	5 pin DIN plug to 5 pin DIN plug length 1.5m	80p
S474	3.5mm Jack to 3.5mm Jack length 1.5m	68p
S600	5 pin DIN plug to 3.5mm Jack connected to pins 3 & 5 length 1.5m	80p
S700	5 pin DIN plug to 3.5 jack connected to pins 1 & 4 length 1.5m	80p

CROSSOVER NETWORK

K4007 1/P Impedance 8 ohms. Insertion (2-way) Loss 3dB. Crossover Frequency 3 KHz. PRICE £1-12

H/PHONE JUNC. BOX

H1012 Enables change over from loud-(3-way)-speaker to headphone listening. Also has a centre position for both outputs. PRICE £1-73

ALL PRICES EX PLEASE ADD VAT ITEMS EXCEPT GIRO NUMBER 388-7006

Postage & Packing add extra for airmail.

HANDBOOKS

TRANSISTOR DATA BOOK DTE 1 227 Pages packed with information on European Transistors. Full specification including outlines. #Price £2-95 each

TRANSISTOR EQUIVALENT BOOK BPE 76 256 Pages of cross references and equivalents for European, American and Japanese Transistors. This is the most comprehensive equivalents book on the market today and has an introduction in 13 languages. #Price £2-68 each

DIODE EQUIVALENT BOOK DE 74 144 Pages of cross references and equivalents for European, American and Japanese Diodes, Zeners, Thyristors, Triacs, Diacs and LEDs. #Price £1-95 each


THE WORLDS BROADCASTING STATIONS WBS 75 An up to the minute guide for those interested in DX-ing. Contains all the world's broadcasters on SW, MW and LW, as well as European FM/TV stations. #Price £3-74 each

TTL DATA BOOK DIC 75 Now complete Data book of 74 series TTL (7400-74132). Covering 13 main manufacturers in the U.S.A. and Europe, this book gives full data as well as equivalents. #Price £3-74 each

A full range of technical books available on request.

PO BOX 6, WARE, HERTS.

VISIT OUR COMPONENT SHOP
18 BALDOCK ST., WARE, HERTS (A10)
 Open Mon.-Sat. 9-5.30 p.m. Tel. 61593

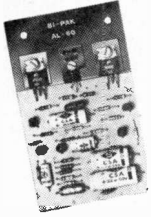


AL 60

50W. PEAK (25W. R.M.S.)

● Max Heat Sink temp 90°C. ● Frequency Response 20Hz to 100kHz. ● Distortion better than 0.1 at 1kHz. ● Supply voltage 15-50V. ● Thermal Feedback. ● Latest Design Improvements. ● Load—3, 4, 5 or 16 ohms. ● Signal to noise ratio 80dB. ● Overall size 63mm x 105mm x 13mm. Especially designed to a strict specification. Only the finest components have been used and the latest solid state circuitry incorporated in this powerful little amplifier which should satisfy the most critical A.F. enthusiast.

ONLY £3.95


STABILISED POWER MODULE SPM80

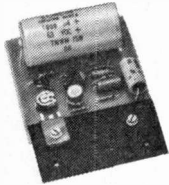

SPM80 is especially designed to power 2 of the AL60 Amplifiers, up to 15 watt (r.m.s.) per channel simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Mains Transformer BMT80, the unit will provide outputs of up to 1.5A at 35V. Size: 63mm x 105mm x 30mm. These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications including:—Disco Systems. Public Address Intercom Units, etc. Hand-book available 10p.

TRANSFORMER BMT80 £2.60

STEREO PRE-AMPLIFIER TYPE PA100

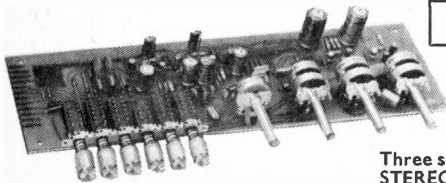

Built to a specification and NOT a price, and yet still the greatest value on the market, the PA100 stereo pre-amplifier has been conceived from the latest circuit techniques. Designed for use with the AL50 power amplifier system, this quality made unit incorporates no less than eight silicon planar transistors, two of these are specially selected low noise NPN devices for use in the input stages.

Three switched stereo inputs, and rumble and scratch filters are features of the PA100 which also has a STEREO/MONO switch, volume, balance and continuously variable bass and treble controls.

PRICE £13.20


GUARANTEE
 SATISFACTION OR
 YOUR MONEY RETURNED

MK 60 AUDIO KIT
 Comprising: 2 x AL60, 1 x SPM80, 1 x BTM80, 1 x PA100, 1 front panel, 1 kit of parts to include on-off switch, neon indicator, stereo headphone sockets plus instruction booklets.
COMPLETE PRICE: £27.55 plus 45p postage

TEAK 60 AUDIO KIT
 Comprising: Teak veneered cabinet size 16½" x 11½" x 3½", other parts include aluminium chassis, heatsink and front panel bracket, plus back panel and appropriate sockets, etc.
KIT PRICE: £9.20 plus 45p postage

CLUDE VAT
AT 25% TO ALL
★ADD 8%
≠ NO VAT
 add 25p* Overseas
 Minimum order 75p


STEREO 30 COMPLETE AUDIO CHASSIS

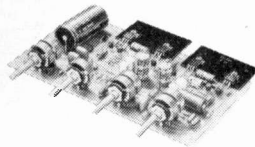

7 + 7 WATTS R.M.S.

The Stereo 30 comprises a complete stereo pre-amplifier, power amplifiers and power supply. This with only the addition of a transformer or overwind, will produce a high quality audio unit suitable for use with a wide range of inputs, i.e. high quality ceramic pickup, stereo tuner, stereo tape deck, etc. Simple to install, capable of producing really first class results, this unit is supplied with full instructions, back front panel, knobs, mains switch, fuse and fuse holder and universal mounting bracket, enabling it to be installed in a record plinth, cabinets of your own construction or the cabinet available. Ideal for the beginner or advanced constructor who requires Hi-Fi performance with a minimum of installation difficulty. (Can be installed in 30 mins.) **PRICE: £15.75 plus 45p postage and packing. TRANSFORMER: £2.45 plus 45p postage and packing. TEAK CASE: £3.65 plus 45p postage and packing.**

AL 10/AL 20/AL 30

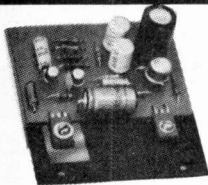

The AL10, AL20 and AL30 units are similar in their appearance and in their general specification. However, careful selection of the plastic power devices has resulted in a range of output powers from 3 to 10 watts R.M.S.

The versatility of their design makes them ideal for use in record players, tape recorders, stereo amplifiers and cassette and cartridge tape players in the car and at home. **AL10 £2.30, AL20 £2.65, AL30 £2.95.**

M.P.A. 38

Enjoy the quality of a magnetic cartridge with your existing ceramic equipment using the new BiPak M.P.A.30 which is a high quality pre-amplifier enabling magnetic cartridges to be used where facilities exist for the use of ceramic cartridges only. Used in the construction are 4 low noise, high gain, silicon-transistors. It is provided with a standard DIN input socket for ease of connection. Supplied with full, easy to follow instructions. **PRICE £2.65**

STORAGE / CARRYCASES ★

RECORD CASES
 7 in E.P. 18½th in x 7 in x 8 in (50 records) ★£2.48
 12 in L.P. 13½ in x 7½ in x 12½ in (50 records) ★£3.30

CASSETTE CASES
 Holds 15. 10 in x 3½ in x 5 in. Lock and handle. ★£1.50

8-TRACK CARTRIDGE CASES
 Holds 14. 13 in x 5 in x 6 in. Lock and handle. ★£2.20
 Holds 24. 13½ in x 8 in x 5½ in. Lock and handle. ★£3.20

CARTRIDGES

ACOS
 GP91-1SC 200 mV at 1.2cms/sec £1.11
 GP93-1 280mV at 1cm/sec £1.43
 GP96-1 100mv at 1cm/sec £2.31

TTC
 J-2005 Crystal/Hi Output 97p
 J-2010C Crystal/Hi Output Compatible £1.11
 J-2006S Stereo-Hi Output £1.52
 J-2105 Ceramic/Med. Output £1.81
 J-2203 Magnetic 5mV/5cm/sec. including stylus £4.78
 J-2203B Replacement stylus for above £2.88
 AT-55 Audio-technica magnetic cartridge 4mV/5cm/sec. £3.06

DYNAMIC MIC'PHONE

TYPE B1223. 200 ohms impedance. Complete with stand, on/off switch and 2.5mm and 3.5mm plugs. Suitable for cassette tape recorders. **PRICE £1.67**

JUST OUT!
STEREO FM TUNER
 WRITE NOW FOR FULL DETAILS



for fast easy reliable soldering

EASY TO USE DISPENSERS AND REELS

IDEAL FOR HOME CONSTRUCTORS

Ersin Multicore Solder contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux is required.

SAVBIT handy solder dispenser



A coil of Ersin Multicore Savbit Solder in a dispenser 7ft 6in of 18 s.w.g. (2.2 metres of 1.22mm). The Solder that reduces the wear of soldering iron bits.

Size 5
32p

SAVBIT solder for general purpose work

A handy plastic reel of SAVBIT alloy, 63ft of 18 s.w.g. (19.2 metres of 1.22mm)

Size 12 £1.80



ALU-SOL for soldering aluminium

New Multicore Alu-sol flux-cored solder in 16 s.w.g. No extra flux needed. Plastic reel holds 36ft. Supplied with full instructions. Also available in solder dispenser.

Size 4 £2.32



Fine gauge solder for soldering small components

Fine gauge solder for soldering small components 138ft of 22 s.w.g. (42.0 metres of 0.71mm) Ersin Multicore 5 core solder wound on a plastic reel. Suitable for intricate work and small components.

Size 10 £1.44



For soldering fine joints



Dispensers of Ersin Multicore Solder make those small jobs easier. 21ft of 22 s.w.g. (6.4 metres of 0.71mm) solder, specially suitable for soldering line wires, small components and for repairing printed circuits.

Size 15 40p

Or size 19A for kit wiring or Radio and T.V. repairs 7ft. (2.1 metres) of 18 s.w.g. (1.22mm) Ersin Multicore Solder.

Size 19A 34p

NEW BIB WIRE STRIPPER & CUTTER



Fitted with unique 8 gauge selector with handle locking device and easy grip handles. Spring incorporated for automatic opening. Strips insulation from flex and cables in seconds and can also be used as a cutter.

Model 8B.80p

NEW SOLDER WICK



Absorbs solder instantly, from tags and printed circuits. Only needs 40 to 50 Watt soldering iron. Quick and easy to use. Does not need flux and is non-corrosive.

Size 18 90p

Bib Hi-Fi Accessories Limited,

Sole U.K. Sales Concessionaires. P.O. Box 78 Hemel Hempstead, Herts. HP2 4RH

Prices shown are recommended retail excluding VAT. From Electrical and Hardware Shops. If unobtainable, send 20p P & P plus VAT at 8p in the £1. Prices and specifications subject to change without notice

PATENT PENDING



Sparkrite mk2

The tried, tested, proven, reliable, complete, professional, capacitive discharge,

Electronic Ignition Kit

"Sparkrite" was voted best of 8 systems tested by Popular Motoring Magazine

ORDER NOW

TO ELECTRONICS DESIGN ASSOCIATES DEPT. PE1,
82 Bath Street, Walsall, WS1 3DE. Phone 33652.

FROM Name _____

Address _____

City _____

SPARKRITE MK 2 DIY Assembly kits @ £10.93

SPARKRITE MK 2 Ready Built Negative earth @ £13.88

SPARKRITE MK 2 Ready Built Positive earth @ £13.88

Ignition changeover switches @ £2.79

R.P.M. Limit systems in the above units @ £2.42

I enclose cheque/P.O.s for £ _____

Cheque No. _____

(Send SAE if brochure only required)

Sparkrite MK2 is a high performance, high quality, capacitive discharge, electronic ignition system. Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire because contact breaker bounce is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and therefore eliminates the possibility of blowing the transistors or the SCR. (Many capacitive discharge ignitions are not completely foolproof in this respect.)

Sparkrite can therefore give you—

- up to 20% better fuel consumption, instant all weather starting, cleaner plugs — they last up to 5 times longer without attention, faster acceleration, higher top speeds, longer coil and battery life, efficient fuel burning and less air pollution, smoother running, continual peak performance.

THE KIT COMPRISES EVERYTHING NEEDED

Ready drilled pressed steel case coated in matt black epoxy resin, ready drilled base and heatsink, top quality 5 year

guaranteed transformer and components, cables, coil connectors, printed circuit board, nuts, bolts, silicon grease, full instructions to make the kit negative or positive earth and 10 page installation instructions.

OPTIONAL EXTRAS

Electronic R.P.M. limitation.
This can be included in the unit to prevent over revving, an advantage to most companies, hire firms, high performance drivers etc.

Electronic/conventional ignition switch.
Gives instant changeover from "Sparkrite" ignition to conventional ignition for performance comparisons, static timing etc., and will also switch the ignition off completely as a security device. Includes: switch, connectors, mounting bracket and instructions. Cables excluded.

PRICES

DIY assembly kit £10.93 incl. V.A.T. post and packing

Ready built unit £13.88 incl. V.A.T. post and packing (Both to fit all vehicles with coil/distributor ignition up to 3 cylinders.)

Switch for instant changeover from "Sparkrite" ignition to conventional ignition £2.79 incl. V.A.T. post and packing (Fitted in case on ready built unit, dashboard mounting on kit.)

CALLERS WELCOME

ORDER DIRECT FROM THE U.S. AND SAVE

SHIPMENT MADE WITHIN 3 DAYS FROM RECEIPT OF ORDER VIA AIR MAIL - POSTAGE PAID

10% Off on orders over £10
15% Off on orders over £50
20% Off on orders over £100

JANUARY SPECIALS

1/2 PRICE SALE

TTL		
7447	BCD to 7 seg decoder-driver	40p
7483	4 bit binary full adder	35p
7490	Decade counter	23p
74153	Dual 4-input multiplexer	32p
74180	Parity generator-checker	40p
74193	Binary up-down counter	43p
9602	Dual one-shot	25p
74C00	Quad 2-input NAND gate (CMOS)	11p

LINEAR

301	Hi performance OP AMP mDIP	22p
339	Quad comparator DIP	46p
340T	5V positive volt reg. TO-220	54p
340T	15V positive volt reg. TO-220	54p

CALCHIP

5005	12 dig. 4 funct. w/mem.	1-21p
------	-------------------------	-------

8038 FUNCTION GENERATOR

Voltage controlled oscillator sine, square, triangular output 16 pin DIP with data £2-50

MEMORY

7489 (82525)	64 bit RAM TTL	£1-25
82523	Programmable ROM	£2-00

MV5020 LED

Jumbo red dome 10p

7001 CLOCK CHIP

4-6 digit, 12-24 hr, alarm, timer & date circuits with data £4-00

TTL



7400	£0.11	7448	£0.80	74150	£0.75
7401	11	7450	12	74151	60
7402	11	7405	13	74153	71
7403	11	7453	13	74153	105
7404	13	7454	14	74155	95
7405	13	7460	11	74156	71
7406	22	7464	21	74157	71
7407	22	7465	21	74161	96
7408	14	7472	22	74163	105
7409	14	7473	26	74164	125
7410	11	7474	26	74165	125
7411	16	7475	41	74166	115
7413	35	7476	26	74173	95
7415	22	7483	70	74175	95
7416	22	7485	80	74176	95
7417	22	7486	24	74177	85
7420	11	7489	1-50	74180	80
7422	22	7490	45	74181	2-50
7423	22	7491	71	74182	80
7425	22	7492	44	74184	155
7426	23	7493	44	74185	145
7427	22	7494	49	74190	95
7430	12	7495	49	74191	95
7432	22	7496	55	74192	90
7437	25	74100	1-25	74193	85
7438	21	74105	60	74194	95
7440	11	74107	27	74195	80
7441	60	74121	32	74196	1-00
7422	55	74122	50	74197	75
7443	55	74123	55	74198	170
7444	60	74125	50	74199	170
7445	75	74126	50	74200	390
7446	85	74141	68		
7447	80	74145	75		

LOW POWER

74L00	£0.16	74L51	£0.16	74L90	£0.93
74L02	16	74L55	18	74L91	80
74L03	16	74L71	18	74L93	89
74L04	18	74L72	27	74L95	89
74L06	18	74L73	38	74L98	153
74L10	16	74L74	38	74L164	153
74L20	16	74L78	44	74L165	153
74L30	16	74L85	85		
74L42	89	74L86	38		

HIGH SPEED

74H00	£0.16	74H21	£0.16	74H55	£0.20
74H01	16	74H22	18	74H60	21
74H04	16	74H30	18	74H61	21
74H08	16	74H40	16	74H62	20
74H10	16	74H50	16	74H74	32
74H11	15	74H52	18		
74H20	16	74H53	20		

8000 SERIES

8091	£0.33	8214	£0.93	8811	£0.38
8092	33	8220	93	8812	60
8095	76	8230	142	8822	142
8121	48	8520	142	8830	142
8122	88	8551	91	8831	142
8130	120	8552	137	8836	27
8200	142	8554	137	8880	73
8210	192	8810	44		

9000 SERIES

9002	£0.21	9309	£0.49	9601	£0.54
9301	63	9312	49	9602	49

CMOS

74C00	£0-21	74C74	£0-63	74C162	£1-78	4000A	£ 18	4013A	£ 32	4025A	£ 18	4069A	£ 31
74C02	30	74C76	93	74C163	1-78	4001A	18	4014A	1-06	4027A	42	4071A	19
74C04	41	74C107	82	74C164	1-92	4002A	18	4015A	1-06	4028A	70	4072A	25
74C08	41	74C151	1-59	74C173	1-59	4006A	96	4016A	40	4030A	32	4073A	28
74C10	36	74C154	1-92	74C195	1-65	4007A	19	4017A	85	4035A	90	4075A	28
74C20	36	74C157	1-20	80C95	82	4008A	1-27	4020A	1-06	4042A	1-05	4078A	28
74C42	1-18	74C160	1-78	80C97	82	4009A	41	4021A	98	4049A	42	4081A	19
74C73	.85	74C161	1-78			4010A	38	4022A	78	4050A	42	4082A	25
						4011A	21	4023A	18	4066A	63	4528A	1-14
						4012A	18	4024A	63	4068A	31	4585A	1-49

MEMORIES w/data

1101	256 bit RAM MOS	£0.96
1103	1024 bit RAM MOS	2.72
5203	2048 bit erasable PROM	13.68
5260	1024 bit RAM Low Power	2.16
7489	64 bit RAM TTL	1.50
8223	Programmable ROM	2.72

CALCULATOR & CLOCK CHIPS w/data

5001	12 DIG 4 funct fix dec	£ 1.46
5002	Same as 5001 exc btry pwr	1.95
5005	12 DIG 4 funct w/mem	2.42
MM5725	8 DIG 4 funct chain & dec	1.10
MM5736	18 pin 6 DIG 4 funct	2.42
MM5738	8 DIG 5 funct K & Mem	2.42
MM5739	9 DIG 4 funct (btry sur)	2.92
MM5311	28 pin BCD 6 dig mux	2.42
MM5312	24 pin 1 pps BCD 4 dig mux	1.94
MM5313	28 pin 1 pps BCD 6 dig mux	2.42
MM5314	24 pin 6 dig mux	2.42
MM5316	40 pin alarm 4 dig	2.42

LED'S

MV10B	Red TO 18	£0.14
MV50	Axial leads	8
MV5020	Jumbo Vis Red (Red Dome)	18
	Jumbo Vis Red (Clear Dome)	18
ME4	Infra red diff. dome	18
MAN 1	Red 7 seg 270°	1.38
MAN 2	Red alpha num .32"	2.72
MAN 4	Red 7 seg 190°	1.18
MAN 5	Green 7 seg 270°	1.62
MAN 6	6" high solid seg	3.81
MAN 7	Red 7 seg 270°	74
MAN 8	Yellow 7 seg 270°	2.17
MAN 64	4" high solid seg	2.45
MAN 66	6" high spaced seg	2.55
MCT2	Opto iso transistor	38

MULTIPLE DISPLAYS

NSNJJ	3 digit .12" red led 12 pin	£-90
	vis ikt.	
HF5082	3 digit .11 led magn. lens	1-80
	com. cath	
HF5082	4 digit .11 LED magn.	1-70
	lens comm. cath.	
INA37	4 digit 7 seg led RH dec. cl.	2-75
	magn. lens	
SP-425-09	4 digit .15" neon direct inter-	98
	face with MOS/LSI, 180 VDC, 7 seg	

DTL

930	10	932	10	949	10
932	10	944	10	962	10
936	10	946	10	963	10

LINEAR CIRCUITS



300	Pos V Reg (super 723)	TO 5	£0.43
301	Hi Perf Op Amp	mDIP TO 5	18
302	Volt follower	TO 5	43
304	Neg V Reg	TO 5	49
305	Pos V Reg	TO 5	52
307	Op Amp (super 741)	mDIP TO 5	38
308	Micro Pwr Op Amp	mDIP TO 5	60
309K	5V 1A regulator	TO 3	91
310	V Follower Op Amp	TO 5 mDIP	65
311	Hi perf V Comp	mDIP TO 5	58
319	Hi Speed Dual Comp	DIP	71
320	Neg Reg 5.2, 12, 15	TO 3	74
322	Precision Timer	DIP	60
324	Quad Op Amp	DIP	107
339	Quad Comparator	DIP	92
340K	Pos. V. reg (5, 6, 8, 12, 15, 18, 24)	TO 3	120
340T	Pos Volt Reg (6V-8V, 12V, 15V, 18V, 24V)	TO 220	1-07
370	AGC/Squelch AMPL	TO 5 or DIP	65
372	AF-IF Strip detector	DIP	44
376	Pos. V. Reg	mDIP	33
377	2w Stereo amp	DIP	147
380	2w Audio Amp	DIP	81
380.8	6w Audio amp	mDIP	69
381	Lo Noise Dual preamp	DIP	98
382	Lo Noise Dual preamp	DIP	98
555	Pres V Reg	DIP	54
550	Timer	mDIP	44
556A	Dual 555 Timer	DIP	89
560	Phase Locked Loop	DIP	194
562	Phase Locked Loop	DIP	194
565	Phase Locked Loop	DIP	120
566	Function Gen	mDIP	120
567	Tone Decoder	mDIP	120
709	Operational AMPL	DIP	27
710	Hi Speed Volt Comp	DIP	21
711	Dual Difference Compar	DIP	44
723	V Reg	DIP	38
739	Dual Hi Perf Op Amp	DIP	65
741	Comp Op Amp	mDIP TO 5	27
747	Dual 741 Op Amp	DIP or TO 5	44
748	Freq Adj 741	mDIP	27
1304	FM MulpX Stereo Demod	DIP	65
1307	FM MulpX Stereo Demod	DIP	45
1458	Dual Comp Op Amp	mDIP	38
14L211	Dual LM 211 V. Comp	DIP	107
3900	Audio preamp	DIP	44
3900	Quad Amplifier	DIP	33
7524	Core Mem Sense AMPL	DIP	104
7534	Core Mem Sense Amp	DIP	142
8864	9 DIG Led Cath Drrv	DIP	137
75451	Dual Peripheral Driver	mDIP	21
75452	Dual Peripheral Driver	mDIP	21
75453	(351) Dual Periph. Driver	mDIP	21
75491	Quad Seq Driver for LED	DIP	50
75492	Hex Digit Driver	DIP	55

Data included with order on request. Add 20p ea. if item is priced below 50p ea. Add 40p ea. if item is not ordered.

Satisfaction guaranteed. Send bank cheque with order. If international money order is used, send receipt with order. The above prices do not include any taxes leviable by a purchaser's country of residence. Minimum order £2-50.

INTERNATIONAL ELECTRONICS UNLIMITED
 P.O. BOX 1708 MONTEREY, CA. 93940 USA
 PHONE (408) 659-3171

The above prices do not include any taxes leviable by a purchaser's country of residence



Join the Digital Revolution

Understand the latest developments in calculators, computers, watches, telephones, television, automotive instrumentation. . .

Each of the 6 volumes of this self-instruction course measures 11½" x 8½" and contains 60 pages packed with information, diagrams and questions designed to lead you step-by-step through number systems and Boolean algebra, to memories, counters and simple arithmetic circuits, and on to a complete understanding of the design and operation of calculators and computers. Design of Digital Systems.



£5.95

plus 50p packing and surface post anywhere in the world.

Payments may be made in foreign currencies.

Quantity discounts available on request.

VAT zero rated.

Also available—a more elementary course assuming no prior knowledge except simple arithmetic. Digital Computer Logic and Electronics

In 4 volumes:

1. Basic Computer Logic
2. Logical Circuit Elements
3. Designing Circuits to Carry Out Logical Functions
4. Flipflops and Registers

£3.95

plus 50p P. & P.

Offer Order both courses for the bargain price £9.25, plus 50p P. & P.

**Designer
Manager
Enthusiast
Scientist
Engineer
Student**

These courses were written so that you could teach yourself the theory and application of digital logic. Learning by self instruction has the advantages of being quicker and more thorough than classroom learning. You work at your own speed and must respond by answering questions on each new piece of information before proceeding to the next.

Guarantee—no risk to you

If you are not entirely satisfied with Design of Digital Systems or Digital Computer Logic and Electronics, you may return them to us and your money will be refunded in full, no questions asked.

To: Cambridge Learning Enterprises
FREEPOST, St. Ives, Huntingdon, Cambs. PE17 4BR

*Please send me... set(s) of Design of Digital Systems at £6.45 each, p & p included

*or... set(s) of Digital Computer Logic and Electronics at £4.45 each, p & p included

*or... combined set(s) at £9.75 each, p & p included


Name

Address

*delete as applicable

No need to use a stamp—just print FREEPOST on the envelope. PE1

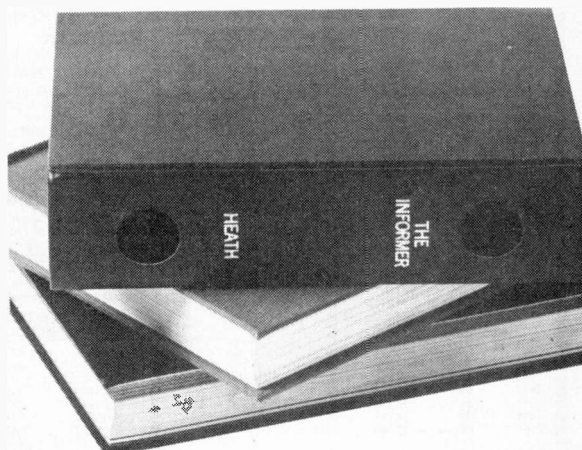Enough books are written about crime, this one stops it.



Outside it's a book. Inside it's an ingenious ultrasonic burglar alarm from Heathkit. The GD-39.

A complete kit that can be assembled in only a few enjoyable hours, with the help of a very easy to follow instruction manual.

The GD-39 works by transmitting a silent, ultrasonic signal throughout the room. And continuously monitoring it. Any movement made by an intruder in the room will then automatically produce a change in the signal. Which triggers off a lamp and, thirty seconds later, a remote buzzer, that just you hear, or a loud bell.


Enough to scare the living daylights out of a burglar.

For more details, and a bookful of other ideas, just post the coupon now for your Heathkit catalogue.

Or, if you're in London or Gloucester, call in and see us.

The London Heathkit Centre is at 233 Tottenham Court Road. The Gloucester showroom is next to our factory in Bristol Road.

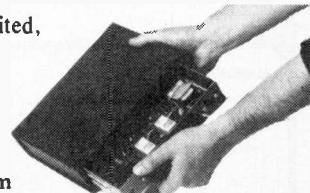Heath (Gloucester) Limited,
Dept. PE-16, Bristol Road,
Gloucester GL2 6EE.
Tel: (0452) 29451.



The GD-39 Ultrasonic Burglar Alarm

To: Heath (Gloucester) Limited, Dept. PE-16, Gloucester GL2 6EE. Please send me a Heathkit catalogue. I enclose a 10p stamp for postage.



Name

Address

Postcode

Monthly buy sheet plan available



OR CHOICE

SEW PANEL METERS

STOCKED AT
481 Oxford Street 311 Edgware Road
42 Tottenham Court Rd. 3 Lisle Street
branches or by mail order.


USED EXTENSIVELY BY
INDUSTRY, GOVERNMENT
DEPARTMENTS, EDUCATIONAL
AUTHORITIES ETC.

Over 200 ranges in stocked - other ranges to
order. Quantity discounts available. Send
for fully illustrated brochure.

CLEAR PLASTIC MODEL SD640

Size: 85 x 64mm

50uA	£4.20		
100uA	£4.15		
200uA	£4.10		
500uA	£4.05		
50.0-500uA	£4.15		
100.0-1000uA	£4.10		
1mA	£4.05		
5mA	£4.05		
10mA	£4.05	10V DC	£4.05
50mA	£4.05	20V DC	£4.05
100mA	£4.05	25V DC	£4.05
500mA	£4.05	50V DC	£4.05
1A DC	£4.05	300V DC	£4.05
5A DC	£4.05	15V AC	£4.15
10A DC	£4.05	300V AC	£4.15
5V DC	£4.05	VU Meter	£4.95

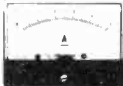

CLEAR PLASTIC MODEL SW100

Size: 100 x 80mm

50uA	£5.05		
100uA	£4.95		
500uA	£4.75		
50.0-500uA	£4.95		
100.0-1000uA	£4.90		
1mA	£4.75		
1A DC	£4.75		
5A DC	£4.75		
20V DC	£4.75	150V AC	£4.90
50V DC	£4.75	300V AC	£4.90
300V DC	£4.75	VU Meter	£6.25



MODEL ED107 EDUCATIONAL METER

Size: 100 x 90 x 150mm including terminals

A range of high quality moving coil instruments ideal for school experiments and other bench applications. 3" mirror scale. The meter movement is easily accessible to demonstrate internal working.



50uA	£9.35		
100uA	£8.70		
50.0-500uA	£8.70		
1mA	£8.40		
10.0-1mA	£8.40		
1A DC	£8.40	20V DC	£8.40
5A DC	£8.40	50V DC	£8.40
5V DC	£8.40	300V DC	£8.40
10V DC	£8.40	500mA 5A DC	£9.50
15V DC	£8.40	5V 50V DC	£9.50
		5V 15V DC	£9.50
		1A 15A DC	£9.50

CLEAR PLASTIC MODEL SD460

Size: 59 x 46mm

50uA	£3.85		
100uA	£3.80		
200uA	£3.75		
500uA	£3.70		
50.0-500uA	£3.80		
100.0-1000uA	£3.75		
1mA	£3.65		
5mA	£3.65	5V DC	£3.65
10mA	£3.65	10V DC	£3.65
50mA	£3.65	20V DC	£3.65
100mA	£3.65	50V DC	£3.65
500mA	£3.65	300V DC	£3.65
1A DC	£3.65	15V AC	£3.80
5A DC	£3.65	300V AC	£3.80
10A DC	£3.65	VU Meter	£4.65



*Items with asterisk are Moving Iron type, all others are Moving Coil

ALL PRICES INCLUDE VAT

BARCLAYCARD & ACCESS Phone
your order to
01-200 1321 or
call into any branch



CLEAR PLASTIC MODEL SD830

Size: 110 x 83mm

50uA	£4.75		
100uA	£4.65		
200uA	£4.60		
500uA	£4.55		
50.0-500uA	£4.65		
100.0-1000uA	£4.60		
1mA	£4.50		
5mA	£4.50		
10mA	£4.60		
50mA	£4.50	10V DC	£4.50
100mA	£4.50	20V DC	£4.50
500mA	£4.50	50V DC	£4.50
1A DC	£4.50	300V DC	£4.50
5A DC	£4.50	15V AC	£4.60
10A DC	£4.50	300V AC	£4.60
5V DC	£4.50	VU Meter	£6.60



CLEAR PLASTIC MODEL MR 45P

Size: 50 x 50mm


50uA	£3.55		
100uA	£3.50		
200uA	£3.45		
500uA	£3.30		
50.0-500uA	£3.50		
100.0-1000uA	£3.45		
100.0-500uA	£3.25		
1mA	£3.25		
5mA	£3.25		
10mA	£3.25		
50mA	£3.25	15V AC	£3.40
100mA	£3.25	300V AC	£3.40
500mA	£3.25	5 Meter 1mA	£3.75
1A DC	£3.25	1A AC	£3.30
5A DC	£3.25	5A AC	£3.25
10V DC	£3.25	10A AC	£3.25
20V DC	£3.25	20A AC	£3.25
50V DC	£3.25	50A AC	£3.25
300V DC	£3.25	30A AC	£3.25



CLEAR PLASTIC MODEL MR 38P

Size: 42 x 42mm

50uA	£3.45		
100uA	£3.40		
200uA	£3.30		
500uA	£3.10		
50.0-500uA	£3.40		
100.0-1000uA	£3.30		
500.0-5000uA	£3.05		
1mA	£3.05		
1.0-1mA	£3.05		
2mA	£3.05		
5mA	£3.05	10V DC	£3.05
10mA	£3.05	15V DC	£3.05
20mA	£3.05	20V DC	£3.05
50mA	£3.05	50V DC	£3.05
100mA	£3.05	100V DC	£3.05
200mA	£3.05	150V DC	£3.10
300mA	£3.05	300V DC	£3.10
500mA	£3.05	500V DC	£3.15
750mA	£3.05	750V DC	£3.15
1A DC	£3.05	15V AC	£3.15
5A DC	£3.05	50V AC	£3.15
10A DC	£3.05	150V AC	£3.15
5A DC	£3.05	300V AC	£3.15
10A DC	£3.05	500V AC	£3.30
3V DC	£3.05	5 Meter 1mA	£3.50
		VU Meter	£4.10

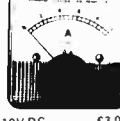

CLEAR PLASTIC MODEL MR 85P

Size: 120 x 110mm

50uA	£6.00		
100uA	£5.95		
200uA	£5.90		
500uA	£5.80		
50.0-500uA	£5.95		
100.0-1000uA	£5.90		
500.0-5000uA	£6.65		
1mA	£5.75		
1.0-1mA	£5.75		
5mA	£5.75		
10mA	£5.75	50V DC	£5.75
50mA	£5.75	150V DC	£5.75
100mA	£5.75	300V DC	£5.75
500mA	£5.75	15V AC	£5.85
1A DC	£5.75	50V AC	£5.85
5A DC	£5.75	100V AC	£5.85
10A DC	£5.75	150V AC	£5.85
15A DC	£5.75	300V AC	£5.75
30A DC	£5.75	10A AC	£5.75
10V DC	£5.75	20A AC	£5.75
20V DC	£5.75	30A AC	£5.75



EDGWISE MODEL PE70

Size: 90 x 34mm

50uA	£4.55		
100uA	£4.50		
200uA	£4.45		
500uA	£4.30		
50.0-500uA	£4.50		
100.0-1000uA	£4.45		
1mA	£4.25		
10V DC	£4.25		
300V DC	£4.35		
VU Meter	£5.50		



BAKELITE MODEL S80 Enlarged Window

Size: 80 x 80mm

50uA	£4.95		
100uA	£4.90		
500uA	£4.60		
50.0-500uA	£4.80		
100.0-1000uA	£4.85		
1mA	£4.60		
1A DC	£4.60		
5A DC	£4.60		
20V DC	£4.60		
50V DC	£4.60		
300V DC	£4.60		
300V AC	£4.75		
VU Meter	£5.95		



CLEAR PLASTIC MODEL MR 52P

Size: 60 x 60mm

50uA	£4.10		
100uA	£3.95		
500uA	£3.70		
50.0-500uA	£3.85		
100.0-1000uA	£3.70		
1mA	£3.65		
5mA	£3.65		
10mA	£3.65		
50mA	£3.65		
100mA	£3.65		
500mA	£3.65		
1A DC	£3.65		
5A DC	£3.65		
10V DC	£3.65		
20V DC	£3.65		
50V DC	£3.65		
300V DC	£3.65		
15V AC	£3.75		
30V AC	£3.75		
300V AC	£3.75		



BAKELITE MODEL MR 65

Size: 80 x 80mm

25uA	£4.40		
50uA	£4.40		
100uA	£4.35		
500uA	£4.05		
50.0-500uA	£4.35		
100.0-1000uA	£4.30		
500.0-5000uA	£3.95		
1mA	£3.95		
1.0-1mA	£3.95		
5mA	£3.95		
10mA	£3.95		
50mA	£3.95		
100mA	£3.95		
500mA	£3.95		
1A DC	£3.95		
2A DC	£3.95		
5A DC	£3.95		
10A DC	£3.95		
15A DC	£3.95		
30A DC	£3.95		
50A DC	£4.20		
5V DC	£3.95		
10V DC	£3.95		
15V DC	£3.95		
20V DC	£3.95		
50V DC	£3.95		
150V DC	£3.95		



CLEAR PLASTIC MODEL MR 65P

Size: 86 x 78mm

50uA	£4.35		
100uA	£4.25		
200uA	£4.20		
500uA	£4.15		
50.0-500uA	£4.25		
100.0-1000uA	£4.20		
500.0-5000uA	£4.10		
1mA	£4.10		
1.0-1mA	£4.10		
5mA	£4.10		
10mA	£4.10		
50mA	£4.10		
100mA	£4.10		
500mA	£4.10		
1A DC	£4.10		
5A DC	£4.10		
10A DC	£4.10		
15A DC	£4.10		
20A DC	£4.20		
30A DC	£4.25		
50A DC	£4.10		
5V DC	£4.10		
10V DC	£4.10		
15V DC	£4.10		
20V DC	£4.10		
50V DC	£4.10		
150V DC	£4.10		



240° Wide Angle

1mA METERS

MW1-8.80 x 80mm

£7.45P + P Ins 15p



REDUCED TO CLEAR

YAMABISHI VARIABLE VOLTAGE TRANSFORMERS

Excellent quality at low cost. Input: 230V 50/60Hz. Output 0-280V.

MODEL S260 BENCH MOUNTING

P/P + Ins

1A £7.30 - £1.50

8A £19.45 - £1.50

10A £23.75 - £1.50

12A £25.90 - £1.50

20A £60.45 - £1.50

25A £64.75 - £1.50



TMK 200 MULTIMETER KIT

Build yourself a quality 2000



U432 MULTIMETER

extremely sturdy instrument for general electrical use. 6670ppv. 0/0.3/1.5/7.5/30/60/150/300/600/900V DC & 75mV/0/0.3/1.5/7.5/30/60/150/300/600/900V AC, 0/300mA/1.5/6/15/150/60/600mA/11.5/6A DC, 0/1.5/16/160/150/600mA/1/10/100ohms/1/10/100ohms/1/10/100ohms. DC accuracy 1%. AC 1.5%. Knife edge pointer, mirror scale. Complete with sturdy metal-carrying case, leads and instructions.



TKM MODEL TW50K

46 ranges, mirror scale, 50kV DC, 50kV AC. DC Volts: 0.125/0.25/1.25/2.5/5/10/25/50/125/250/500/1000. AC Volts: 1.5/3/15/10/25/50/125/250/500/1000. DC current: 25/50mA/2.5/5/25/50/250/500mA/5/10A. Resistance: 10k/100k/1 Meg/10 Meg ohms. -20 to +81.5dB.



U4313 MULTIMETER

High sensitivity (20,000 opv on DC and 2,000 opv on AC) and accuracy of 1.5% on DC and 2.5% on AC. Ranges: DC and AC current: 0.6 mA/3.15/60/300/1.5A. DC and AC Voltage: 1.5V/3/7.5/15/30/60/150/300/600; DC resistance 1kohm/10/100/1,000, -10 to +12dB, etc. Complete with steel carrying case and leads, manual.



U4317 MULTIMETER

High sensitivity instrument for field and laboratory work. Knife edge pointer, 86mm mirror scale. Overload protection. Ranges: 100mV/0.2/2.5/10/25/50/100/250/500/1000V DC. 0.5/2.5/10/25/50/100/250/500/1000V AC. Current: 50uA/0.5/1.5/10/50/250mA/1.5A DC. 0.25/0.5/1.5/10/50/250mA/1.5A AC. Resistance: 0.5/10/100/200 ohms/1/3/30/300k ohms. Decibels: -5 to +10dB. Battery operated. Size: 210 x 115 x 30mm. Supplied in carrying case complete with leads.



U91 Clamp VOLT AMMETER

For measuring AC voltage and current without breaking circuit. Ranges: 300/600V AC. Current: 10/25/100/250/500A. Accuracy 4%. Size 283 x 94 x 36mm. Complete with carrying case, leads and fuses.



MODEL 500

30,000 opv with overload protection. Mirror scale. 0/0.5/2.5/10/25/100/250/500/1000V DC. 0/50uA/0.5/5/10/50/250mA/1.5A AC. Resistance: 0.5/10/100/200 ohms/1/3/30/300k ohms. Decibels: -5 to +10dB. Battery operated. Size: 210 x 115 x 30mm. Supplied in carrying case complete with leads.



SWR METER Model SWR3

Handy SWR meter for transmitter antenna alignment, with built-in field strength meter. Accuracy 5%. Impedance 52. Indicator 100uA DC. Full scale 5 section collapsible antenna. Size 145 x 50 x 60mm.




KAMOEN 360 MULTIMETER

High sensitivity (100kchm/V AC 10kchm/V 5" mirror scale, overload protected. High current: 0.5/2.5/10/50/250/1000V DC. 5/10/50/250/1000V AC. Current: 0.01mA/0.5/5/50/500mA/10A. Resistance: 0.1/1/10/100ohms/1/10/100ohms/10/100ohms. Decibels: -20 to +52dB. Battery operated. Size: 180 x 140 x 80mm. Supplied complete with test leads etc.



Model HT10084 MULTIMETER

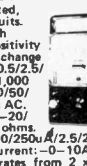Overload protected, shock proof circuit. 9.5uA Meter with mirror scale. Sensitivity 100kV. Polarity change switch. Ranges: 0.5/2.5/10/50/250/500/1,000 Volts DC. 2.5/10/50/250/1,000 Volts AC. DC resistance: 0-20/200k/2/20 Meg. ohms. DC current: -10/250uA/2.5/25/250 mA/10A. AC current: -0-10A. -20 to +82dB. Operates from 2 x 1.5V batteries. Size: 180 x 134 x 79mm.



KAMOEN HM720B FET VOM

Input impedance 10 Megohms. Ranges: 0/0.25/1.25/5/10/100V DC. 0/2.5/10/50/250/1000V AC. 0/25uA/2.5/25/250 mA DC. 0/5k/50k/500k/5M 500 Megohms.




MODEL AF.105 VOM

50,000 opv. Mirror scale. Meter protection. 0/3/12/60/120/300/600/1200V DC. 0/6/30/120/300/600/1200V DC. 0/30uA/60/300 mA/12 Amp. 0/10K/1m/10m/100 Meg Ohms. -20 to 17 dB.



MODEL AS.1000 VOM

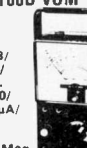100,000 opv. Mirror scale. Built-in m.m. protection. 0/3/12/60/120/300/600/1200V DC. 0/6/30/120/300/600V AC. 0/10uA/6/60/300mA. 12 Amp. 0/2k/200k/2M/200 Meg Ohm. -20 to -17 dB.




U4341 Multimeter & Transistor Tester

27 ranges, 16,700ppv. Overload protected. Ranges: 0.3/1.5/6/30/60/150/300/900V DC. 1.5/5/30/150/300/750V AC. Current: 0.06/0.6/6/60/600mA. DC. 0.3/3/30/300mA AC. Resistance: 0.06/0.6/20/200k ohms/2 Mohms. Battery operated. Supplied complete with probes, leads and steel carrying case. Size: 115 x 215 x 90mm.



KAMOEN TT35 TRANSISTOR TESTER

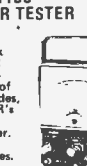Instrument to test reverse leak current and DC current. Amplification factor of NPN, PNP, diodes, transistors, SCR's etc. 4" square clear scale meter. Operates from internal batteries. Complete with instructions, leads carrying handle.



SDOUTR MULTIMETER TRANSISTOR TESTER

100,000ppv. Mirror scale. Overload protection. 0/0.12/0.6/3/12/30/120/600V DC. 0/6/30/120/600V AC. 0/12/60mA/12/300mA/6/12A DC. 0/10k/1 Meg/10 Meg. -20 to +50dB. 0.01-0.2 MFD. Transistor tester measures Alpha, Beta and ICO. Complete with instructions, batteries and leads.



C15 PULSE OSCILLOSCOPE

For display of pulsed and periodic waveforms in electronic circuits. VERT. AMP. Bandwidth: 100kHz. Sensitivity at 100kHz VRMS/mm: 0.1-25; HOR. AMP. Bandwidth: 500kHz. Sensitivity at 100kHz VRMS/mm: 0.3-25. Preset triggered sweep 1-3000cps. Free running 200-2000 kHz in nine ranges. Calibrator pipes. 220 x 360 x 430mm. 115-230V AC.



J70WTR MULTIMETER

Features AC current range up to 20,000ppv. 0/0.5/2.5/10/50/250/500/1000V DC. 0/2.5/10/50/250/500/1000V AC. 0/50uA/1/10/100 mA/1/10A DC. 0/10mA/100 mA/1A/10A AC. 0/5k/50k/500k/5 Meg/50 Meg. Decibels: -20 to +62dB.



KAMOEN 72.200 Multitester

High sensitivity tester. 200,000 opv. Overload protected. Mirror scale. Ranges: 0/0.6/3/3/30/120/600/1200V DC. 0/3/12/60/11200 V AC. 0/6uA/1.2mA/120mA/600mA/12A DC. 0/1/2A AC. -20 to +62dB. 0/2k/200k/2 Meg/200 Megohms.



TE-200 RF SIGNAL GENERATOR

Accurate wide range signal generator covering 120 kHz-500 MHz on 6 bands. Directly calibrated. Variable RF attenuator audio output. Xtal socket for calibration. 220/240V a.c. Brand new with instructions. Size 140mm x 215mm x 170mm.




ARF 300 AF/RF SIGNAL GENERATOR

Compact fully portable. AF sine-wave 18Hz to 220 kHz. AF square-wave 18Hz to 100k Hz. Output Square/Sine wave 10V. P.P. RF 100kHz to 200MHz. Output 1V maximum. 220/240V AC operation. Complete with instructions and leads.



TRANSORISED L.C.R. A.C. BR/8 MEASURING BRIDGE

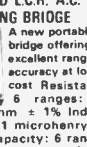A new portable bridge offering excellent range and accuracy at low cost. Resistance: 6 ranges: 0.1 ohm-11.1 megohm ± 1% Inductance: 6 ranges: 1 microhenry-111 henries ± 2% Capacity: 6 ranges: 10pF-1110 nF ± 2% Turns Ratio: 6 ranges: 1:1/1000-1:11100 ± 1%. Bridge Voltage at 1,000cps. Operated from 9-volt battery. 100 microamp meter indication. Size 71" x 5" x 2" P/P & Ins 60p.



TE22 SINE SQUARE WAVE AUDIO GENERATOR

Sine 20cps to 200kHz on 4 bands. Square 20 cps to 30 kHz. Output impedance 5000 Ohms. 200/250V AC operation. Supplied brand new guaranteed, with instruction manual and leads.



MODEL TE20 RF SIGNAL GENERATOR

Six bands. 120kHz-260MHz. Dual output RF terminals. Separate variable audio output. Accuracy ± 2%. Audio output to 8V. Power requirements. 105-125V, 220-240V AC. Size: 193 x 265 x 150mm. Complete with test leads etc.



NEW GOLDRING CK2 KIT

Best-drive 2-speed turntable in kit form complete with pick up arm and headshell. P/P & Ins 60p. OUR PRICE £21.15

INCREDIBLE FERGUSON CASSETTE DECK BARGAIN

THE FERGUSON 3429 Stereo Cassette Deck is being offered by LASKYS at an incredible price, and this is what you get: a beautiful teak/aluminium stereo cassette deck with 3-digit tape counter, manual or automatic level controls, DIN input/output, slider controls, level meter, a monitor earphone output, and a stereo microphone with deck stand. P/P & Ins. OUR PRICE £37.50



WALKIE TALKIES SKYFON MV7

Super low cost transmitter/receivers. 100MW with call buzzer and on/off volume control. 7 transistors. Telescopic rod antenna. P/P & Ins 50p. OUR PRICE £43.60



NATIONAL PORTABLE MULTI-BAND RADIOS

Two magnificent multi-band portable (DC) radios from National Panasonic - one of the world's largest manufacturers of fine radio equipment. The RF-905 (not illustrated) is an AM/FM 5-band (FM/LW/MW/SW1/2) 15-transistor 19-die unit with station presets, slider level controls, fine tuning, and a full, smooth sound! And the RF-1700 is an 8-band (FM/AIR/PSB high/PSB low/AM/Marine/SW1/SW2) radio with band indicator, dial light, loudness control, AFC, fine tuning, tone, and squelch - a real enthusiast's radio! P/P & Ins. OUR PRICE £34.95



LOUDSPEAKERS AT LASKYS

Hundreds of incredible loudspeaker bargains at LASKYS - Famous names like TANNOW, WHARFEDALE, and GOODMANS, and all offered at astoundingly low prices! Hurry while stocks last!

SINCLAIR SPECIALS AT LASKYS

These Sinclair Project 80 modules are famous world-wide for the ease with which they make up into high-quality, reliable Hi-Fi components. Thanks to special purchases, LASKYS have slashed prices to the bone! Compare these prices - you'll be amazed!

SINCLAIR Project 80 Modules

240 Power Amp. £3.75 P/P & Ins. 15p
280 Power Amp. £6.95 P/P & Ins. 15p
Stereo 80 Pre-Amp. £7.50 P/P & Ins. 15p
Active Filter Unit. £4.50 P/P & Ins. 15p
FM Tuner. £7.50 P/P & Ins. 15p
Stereo Decoder. £4.95 P/P & Ins. 15p
PZ5 Power Supply. £2.75 P/P & Ins. 30p
PZ6 Power Supply. £4.50 P/P & Ins. 30p
PZ8 Power Supply. £7.90 P/P & Ins. 30p
Transformer for PZ8. £5.05 P/P & Ins. 30p

SINCLAIR DM2 DIGITAL MULTIMETER

Will measure AC and DC volts, AC and DC current, and resistance in a total of 20 ranges. The large light emitting diode display will read up to 1999 and automatically indicate polarity. Indication of positive and negative overload is also provided. The instrument is fitted with a combined carrying handle and bench stand and sockets are provided for the connection of an external power supply. RANGES: DC VOLTS: 1v, 10, 100v, 1000v AC VOLTS: 1v, 10v, 100v, 1000v.. DC CURRENT: 1mA, 10mA, 100mA, 1000mA. AC CURRENT: 1mA, 10mA, 100mA, 1000mA. RESISTANCE: 1k, 10k, 100k, 1000k. OUR PRICE £63.70 P/P & Ins 50p



SINCLAIR PROJECT 805

Now available at special low prices LASKYS prices the famous project 805 no-solder amplifier kit. Included are all necessary wires, push-on connectors, P80 pre-amp, two Z40 power boards giving 12w rms/PZ5 power supply, and a comprehensive manual. List Price £49.93. OUR PRICE £17.50 p/p & Ins. £1.65




SINCLAIR PROJECT 80 RECEIVER

World-famous Sinclair modules in sophisticated black metal Scandinavian livery delivers 20 watts rms per channel into 8 ohms, with FM stereo tuner, all slider controls on the tuner section are neatly recessed into the top of the unit. Fine performance and truly remarkable value for money. OUR PRICE £56.25 P/P & Ins. £1.65



SINCLAIR PROJECT 80 AMPLIFIER

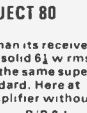Lower-powered than its receiver brother, but still a solid 61 w rms per channel, with the same superb performance standard. Here at last is a budget amplifier without the "budget look". P/P & Ins. OUR PRICE £28.10 £1.65



SPECIAL OFFER! SINCLAIR 4000 AMPLIFIER AND FM TUNER

Streamline elegance and great performance from SINCLAIR - the 4000 amplifier gives 17W RMS per channel (both driven) into 8 ohms, phones jack, active switchable scratch filter, low noise and distortion, and much more. List Price £74.95 p/p & Ins. OUR PRICE £33.95 £1.65



ALL PRICES INCLUDE VAT

CALCULATOR PRICE BREAKTHROUGH!



CASIO PERSONAL MINI ELECTRONIC CALCULATOR
Mini-sized pocketable calculator at an amazingly low price. Simple to operate; provides four basic functions with automatic constant. 6x6 Digit green display. Square/Power and reciprocal. Fully floating decimal. Size only 52" X 23" X 1".
ONLY £4.95 p/p & Ins. 50p
AC ADAPTOR £4.05 optional extra.

ELECTRONIC CALCULATORS



We carry a tremendous range of both pocket and desk calculators by Sinclair, Hamamex, Texan, Hewlett Packard, Novus, Casio, Unixtrix, Litronix, etc. etc. Owing to the demand it is not possible to include them in this advertisement, so send for our latest price list or call into any branch.

GARRARD AT LASKYS

LASKYS know how good Garrard is, so we stock an enormous selection of Record Deck Packages and Chassis Units.



RDP 14

One of the most popular record decks, the SP25 is now in its Mark IV guise, and performs better than ever. With fine Garrard styling and precise attention to production detail, the SP25 Mk IV features the famous Garrard synchronous motor, a low mass arm for minimal record wear, calibrated stylus force, bias compensator, and a host of other facilities. The fully damped cueing lets you lay the included Shure M756SM cartridge gently in the groove. The teak-veneered plinth and smoked dustcover protect both deck and records.
OUR PRICE £40.35
p/p & Ins. £1.65



SENN SOUND 4-CHANNEL ADAPTOR

Simple couple this unit to your existing stereo amplifier and add a pair of speakers, and enjoy the realism of the concert hall.
OUR PRICE £4.95 p/p & Ins. £1.35



ELIZABETHAN 8/LZ-1
8-Track Stereo Player. Home 8-Track player with automatic and manual programme change and illuminated channel indicators for use with your hi fi system. Size 7 1/2" w x 12" D x 2 1/2" h. List Price £28.90.
OUR PRICE £14.90 p/p & Ins. £1.35

MINIATURE ORGAN MUSIC MASTER AM100



Spanning nearly two octaves, including semi-tones. This instrument will give hours of enjoyment to all the family. Beautifully finished. The Keyboard range can be adjusted to be in tune with any instrument. Operates from internal 9V battery. Fitted with on/off switch, vibrato switch, earphone socket and external 9V D.C. socket.
Size 229mm x 127mm x 64mm
OUR PRICE £8.25 p/p & Ins 50p



FANTAVOX FMT1 STEREO FM TUNER

9v Battery operated FM Stereo Tuner with A. F. C. FM88-108 MHz. Seven 3/2" twin telescopic aerial. Edgewise Tuning and volume controls. Size only 151x66x108mm. Socket for external power supply. Simple connections.
OUR PRICE £12.40 p/p & Ins. £1.65



HI-FI CATALOGUE

OUT NOW Our Bumper 48-page LASKYS Christmas Catalogue, packed with the best in Hi-Fi, accessories, calculators, test gear, explanations of LASKYS great services - AND a lot of GREAT GIFT IDEAS!
Get one FREE from any LASKYS branch, or fill in the handy coupon below. A must for every electronics enthusiast!

AUDIOTRONIC EXCLUSIVE TO LASKYS

AUDIOTRONIC Model ATM1

Top value 1,000 opv pocket multi-meter. Ranges: 0/10/50/250/1,000 volt AC and DC. DC current 0.1mA/100mA. Resistance: 0/150k ohms. Decibels: -10 to +22dB. Size 90 x 60 x 28mm. Complete with test leads.
OUR PRICE £7.95 p/p & Ins 25p



AUDIOTRONIC MODEL ATM5

Jewel mesh attractively moulded case with edgewise ohms adjustment. Ranges: 0/15/150/300/1200V AC. (2500 opv), 0.6/30/300/600V DC. (5000 opv), 0.3/300 uA/0.300mA DC. Resistance: x 10 & x 100. -10 to +16dB. Supplied with battery test leads and data booklet. Size: 121 x 73 x 29mm.
OUR PRICE £5.40 p/p & Ins 25p



AUDIOTRONIC ACD 7700
Cassette Deck with Dolby. Twin VU meters, program counter, DIN and phono input outputs, level slider controls, in sleek black, brushed aluminium, and teak. Freq. response: 40-12 kHz on normal tape and 40-16 kHz on CrO2 tape. W/F 0.2% and with the Dolby Noise Reduction System in a signal to noise ratio of 57dB.
OUR PRICE £79.95 p/p & Ins. £1.65



ADC22
24-hour clock radio, covering MW, FM wavebands. 60-minute sleep timer, timer. Choice of Grey or White cabinet. P/P & Ins.
OUR PRICE £17.50

AUDIOTRONIC HEADPHONES

LSH20 Individual volume controls. Mono stereo switch. 40-19,000 Hz. 8 ohms.
OUR PRICE £6.50 p/p & Ins 50p

LSH30 Individual tone and volume controls. Mono stereo switch. 30-20,000 Hz. 8 ohms.
OUR PRICE £10.50 p/p & Ins 30p

LSH40 Two-way speaker system. Individual volume controls. 20-20,000 Hz. 8 ohms.
OUR PRICE £12.95 p/p & Ins 30p

LSH100
Our newest and lightest headphones, with the same high quality reproduction.
OUR PRICE £14.95 p/p & Ins. £1.10

LSH 80 Individual volume controls. 20-20,000 Hz. 8-100 ohms.
OUR PRICE £14.50 p/p & Ins. £1.10

AUDIOTRONIC AHA101

Stereo Headphone Amplifier. All silicon, transistor amplifier operates from magnetic, ceramic or tuner inputs with twin stereo headphone outputs and separate volume controls for each channel. Operates from 9V battery. INPUTS: 5mV and 100mV. OUTPUT: 50mV per channel.
OUR PRICE £10.65 p/p & Ins 30p

AUDIOTRONIC LOW NOISE CASSETTES

MODEL 5 10 15
C60 £2.05 £3.88 £5.50
C90 £2.81 £5.34 £7.57
C120 £3.59 £6.80 £9.64

AUDIOTRONIC HIGH ENERGY LOW NOISE CASSETTES

MODEL 5 10 15
C60LN £3.59 £6.80 £9.64
C90LN £6.13 £9.72 £13.77
C120LN £6.15 £11.66 £16.52
p/p & Ins. 15p per order

See the rest of the exclusive Audiotronic range - stereo receivers, speakers, amplifiers, tuners pickup cartridges (made for us by SHURE), digital clock radios, and cassette radios - all built to the same high standard, all at realistic prices!

ALL PRICES INCLUDE VAT



A SERVICE THAT MAKES SENSE!

CUSTOMER SERVICES Our Customer Services Division at Head Office will answer all your enquiries - just ring 01-200 1321.

EXPORT Personal exports arranged for overseas visitors. Goods specially packed, insured and despatched to all parts of the world at minimum cost exclusive of VAT. Payment by bank transfer, certified cheque, postal order or money order in any currency.

LASKYS GIVE YOU CREDIT!

Cheques to the value of £30 accepted from personal shoppers with bankers card. In other cases and for amounts in excess of £30. Please allow time for clearance. Bankers Drafts accepted. Cheques to any value accepted for mail orders.

BARCLAYCARD & ACCESS

Phone your order to 01-200 1321 or call into any branch.



YOUR NEAREST BRANCH:

NOTTINGHAM		49897
5-7 Lower Parliament Street		
OXFORD		722870
16 Westgate Centre		
READING		
6 Friars Walk, Friars St.	0734 595459	
33 Tottenham Court Rd. W1	636 2605	948 1441
42-45 Tottenham Court Rd. W1	636 0845	20218
257-8 Tottenham Court Rd. W1	580 0670	
SLOUGH		
3 Lisie Street, WC2	437 8204	24401
118 Edgware Road, W2	723 9789	
193 Edgware Road, W2	723 6211	205/206 Churchill West 612241
207 Edgware Road, W2	723 3271	WINOON 12 Brunel Pl. Now Open
311 Edgware Road, W2	262 0387	TUNBRIDGE WELLS
346 Edgware Road, W2	723 4453	53/57 Camden Road 23242
383 Edgware Road, W2	723 4194	WOLVERHAMPTON
109 Fleet Street, EC4	353 5812	30 Wulfrun Way 23394
15 23 Fleet Street, EC4	353 2833	
LEWISHAM 29 Riverdale, The Lewisham Centre	318 2297	
BIRMINGHAM		
116 Corporation Street	021-236 3503	
BRISTOL		
16-18 20 Penn Street	20421	
CHATHAM		
The Pentagon Centre	Now Open	
CROYDON		
1046 Whitgift Centre	681 3027	
DARTFORD		
The Arndale Centre	Now Open	
KINGSTON 38/40 Eden St.	546 1271	
LEICESTER 45 Market Pl.	537678	
NORTHAMPTON		
78 Abington Street	35753	

TO LASKYS CUSTOMER SERVICES DIVISION (Dept PE1)

Audiotronic House, The Hyde, London NW9 6JJ.
Tel: 01-200 1321

Please send me the following items

Name _____

Address _____

Signature _____

TOTAL PURCHASE PRICE _____ (inc. P/P & Ins.)


Please send me FREE 32-page Hi-Fi catalogue price list

I enclose cheque postal order money order

I wish to pay by Barclaycard/Access and my number is _____

Registered in England No. 347947 at Lower Grosvenor Place, London SW1 0EX

INVERTORS

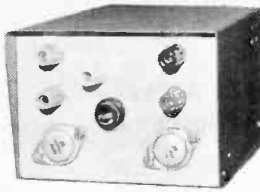

240v-50Hz from your 12v car battery.

25 watt—£4.20 150 watt—£19.10
40 watt—£7.35 300 watt (12v)—£29.85
75 watt—£10.71 300 watt (24v)—£23.75

All above invertors are in kit form but may be purchased built up in metal case & ready for use. Price list sent on receipt of s.a.e. Prices include post & packing.

P.W. AUTOMATIC EMERGENCY SUPPLY

240v-50Hz-150 watt inverter with built in battery charger. In event of power failure switches over automatically from battery charging to inverter operation. Cct. as appeared in Dec. 72 P.W. Complete kit of parts (excluding meter) £22.50 + £1.10 p. & p.

FLOUORESCENT LIGHT INVERTOR KIT
8 watt-12v-Fluorescent light, suitable for tents, caravans, houses, boats & secondary lighting for factories, hotels, etc.
12"-8 watt—£2.90 + 25p p. & p. Built up—£4 + 25p.
21"-13 watt—£3.30 + 30p p. & p. Built up—£4.50 + 30p.

TRANSFORMERS & COILS

Both high volume & small order capacity available.

Special offer. Miniature mains transformer 12-0-12v-6V A.—85p plus 10p p. & p.

TRADE & EXPORT ENQUIRIES WELCOMED

P.E. ORION STEREO AMPLIFIER




20 + 20 Watts r.m.s. into 8 ohm load. Distortion less than 0.01% 100Hz-10kHz. Frequency response \pm 1dB 20 Hz to 20 kHz. Hum level virtually nil with vol. full on.

This is a power amplifier of superb quality incorporating the very latest design features. Professional hi-fi enthusiasts have classed it as fantastic and real value for money. The CCT incorporates a low flux transformer and inputs for disc, tape, tuner, etc.

Complete kit of parts including slim line bookend case, silk screened front panel & knobs. £43 incl. VAT & p. & p.

The bookend case, I.C.s & semiconductors, P.C. board, Transformer, etc. may be purchased separately if desired. Send S.A.E. for further information

ASTRO IGNITION

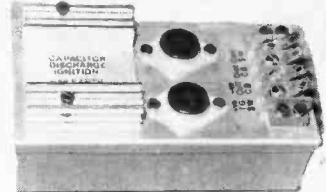

ASTRO IGNITION SYSTEM

Complete kit of parts for this proven and tested system £9.50 incl. VAT. Ready built with only two connections to alter £12.50 incl. VAT. Thousands have used this system both home and abroad. Consider these *advantages* more power, faster acceleration, fuel economy, excellent cold starting, smoother running, no contact breaker burning. Also because of the high energy spark, the fuel mixture can be made weaker giving further economy and fewer plug problems. Fitting time when built 5 minutes approx. Please state whether positive or negative earth. Trade and export enquiries welcomed.

ASTRO ELECTRONICS

Spring Bank Road, West Park
Chesterfield.

B. BAMBER ELECTRONICS

5 STATION ROAD, LITTLEPORT, CAMBS., CB6 1QE

Telephone: ELY (0353) 860185 (2 lines) Tuesday-Saturday

ALL BELOW—ADD 8% VAT

SPERRY 7-SEGMENT P.G.D. DISPLAYS, digit height 0.3in red, with decimal points, 150V to 200V (nominal 180V) operation. These are high-volt industrial type, and therefore brighter than normal displays. All brand new. AT THE BARGAIN PRICE OF 50p PER DIGIT. TYPE 332 (two digits in one mount) £1.90 each. TYPE 333 (three digits on one mount) £1.50. (Sorry, no single digit available.) Data supplied.

3 Switch Push Button Units (3 x 2 pole, 2 way), min. push-pull switches, $\frac{1}{2}$ in dia. buttons, mounted on one unit, 40p. Perspex coil formers, $\frac{1}{2}$ in x $\frac{1}{2}$ in dia., 5 for 25p.

PC board withdrawal handles, mixed coils, 8 for 50p.

Solder, 20SWG, 80/40 alloy, approx. 8yds, 25p.

25-way ISEP PLUGS AND SOCKETS, 40p set (1 plug + 1 skt.).

DIE CAST BOXES (approx. size in inches)

4.3 x 2.3 x 1.2 85p
4.8 x 2.8 x 1.5 75p
4.8 x 3.8 x 1 85p
4.8 x 3.8 x 2 £1.00
6.8 x 4.8 x 2 £1.45
6.8 x 3.8 x 3 £1.55
6.8 x 4.8 x 4 £2.25
6.8 x 5.8 x 2 £1.85
10.6 x 6.8 x 2 £2.25

MAINS TRANSFORMERS

All 240V input, voltages quoted approx. RMS. (Please quote type no. only when ordering.)

TYPE 10/2, 10-0-10V at 2A, £1.50 each.
TYPE 28/4, 28V at 4A + 125V at 500mA, £4.
TYPE 63/1, 6-3V at 1A, 85p each or 2 for £1.50.

TYPE 129, 400V at 20mA + 200V at 10mA + 6-3V at 500mA, £1.25.
TYPE 727/3, 400V at 10mA + 200V at 5mA + 6-3V at 400mA, £1.25.
TYPE 7046/2, 250-0-250V at 80mA + 6-3V at 3A, £1.75.

TERMS OF BUSINESS: CASH WITH ORDER (minimum order £1) POST FREE (UK ONLY). PLEASE ADD VAT AS SHOWN

Export enquiries welcome. Callers welcome. Tues. to Sat. Please enclose S.A.E. with ALL enquiries.

ALL BELOW—ADD 8% VAT

WELLER SOLDERING IRONS
SP15D, 15W £2.52
SP25D, 25W £2.52
Spare bits MT8 (15W) £0.42
MT4 (25W) £0.35
Weller Expert gun £6.80
Weller Expert kit £9.80
Weller Expert spare bits (7135) £0.26 per pair.

S.A.E. for list of soldering irons, electronics tools, etc.

Turret tags, $\frac{1}{4}$ in dia., 25p pack.
Rotary switches, min. 4 pole 2-way, 2 for 50p.

Telephone type earpiece insert, 50p.
 $\frac{1}{2}$ in polythene chassis mounting fuseholders, 8 for 30p.

LES lamps, 24V 1/2W, 10 for 40p.
Mullard tubular ceramic trimmers, 1-18pF, 6 for 50p (as featured in Rad. Comm. Jan. p. 25).

I.C.s, some coded, 14DIL type, untested, mixed, 20 for 25p.
Miniature slider switches, 2 pole, 2-way, 5 for 50p.

TRANSISTOR HEATSINKS, to take 2 x TO18 transistors, screw in clamps, block size 1 x $\frac{1}{2}$ x $\frac{1}{2}$ in, with holes for mounting, 3 for 50p.
TO3 transistor insulator sets, 10 for 50p.

ALL BELOW—ADD 25% VAT

TV-plugs, metal type, 8 for 50p.
TV sockets, metal type, 5 for 50p.

TV line connectors (back-to-back socket), 6 for 50p.

OC200 transistors, 6 for 50p.
BSY95A transistors, 6 for 50p.
BFV51 transistors, 4 for 50p.
BCY72 transistors, 4 for 50p.

PNP audio type TO5 transistors, 12 for 25p.
IF cans $\frac{1}{2}$ in square, suitable for rewind, 6 for 30p.

DIN SPEAKER SOCKETS (2-pin) 4 for 30p.
HIGH QUALITY SPEAKERS, 8 $\frac{1}{2}$ x 6in elliptical, only 2in deep, inverse magnet, 4 ohms, rated up to 10W, £1.50 each, or 2 for £2.75 (qty. discount available).




CJL LTD. P.O. BOX 34, CANTERBURY, CT1 1YT

ALL PRICES INCLUDE P & P AND V.A.T.

AERIALS Telescopic, 15-120 cm £1.50
KEYNECTORS Rapid connect to mains. Built-in piano switches, neon & 13A fuse £3.55
MULTIMETERS Vdc/ac-10, 50, 250, 1,000, ldc-0.1A, R-150k £4.95
PRINTED CIRCUIT KITS Contain all items necessary to produce printed circuits £3.99
SIGNAL INJECTORS Audio through video signals, ideal servicing amplifiers, radio and tv £4.25
TEST SWITCHES 5 miniature push to test switches £1.00
AUDIO LEADS
5p din plug to 5p din plug, 1.5m £1.20
2p din plug to 2p din skt. 10m £1.45
5 pin din plug to 2 phono plugs £1.20
BIB HI-FI ACCESSORIES
Groov-Kleens /42 £1.95
"Tape Editing Kits /23 £1.50
Cassette Editing Kits /24 £1.65
Cassette Head Cleaners /31 £0.65
Hi-Fi Stereo Test Cassette £2.15
Cassette Wallets (hold 6) £0.90
CASSETTE HEAD DEMAGNETISER
Shaped pole piece-saves time £3.65
EARPHONES Stethoscope style, 8 ohm dynamic £1.20
Crystal earphone-lead & plug £0.65
INTERCOMS 2-station, ideal for the home-baby alarm, office, with cable and staples £6.35
MICROPHONES Dynamic, remote start/stop, 200 ohms, 100-10kHz 6mV output £2.15


STEREO HEADPHONES Superb stereo listening in comfort and privacy, 30-15kHz, 8 ohms £4.85
STEREO HEADPHONE JUNCTION BOXES 3 way unit selects phones only, speakers only or both £2.30
STEREO PRE-AMPLIFIERS
3-30mV, RIAA, Out: 200-800mV flat, 20-20kHz, Supply: PP3 £7.30
SPEAKERS Miniature, 75mm dia., 8 ohms £0.95
SOLDERING IRONS (ANTEX)
15W, 'C' miniature irons, slide on & off 3/32" bit £2.30
3/32", 1/8", 3/16", bits—each £0.45
'C' Elements £1.10
25W, X25 irons, low leakage, slide on & off 1/8" bit £2.30
3/32", 1/8", 3/16", bits—each £0.47
X25 Elements £1.15
Soldering Kits, SK1, 'C' iron, 2 spare bits 3/32" & 5/32", heat sink, solder, base, booklet £3.85
Stands, ST3, High grade base, spring, sponges, accommodation—spare bits £1.10
SOLDER -in handy Bib dispenser £0.43
TRY SQUARES
10 tools in one—ideal—marking out Cabinets, Chassis, PCB's £2.50
WIRE STRIPPERS & CUTTERS
Bib 8B, 8 gauge selector, automatic opening, easy grip handles £0.85
FOOT SWITCHES
Push on/off, Anti skid £2.70

SUPERSOUND 13 HI-FI MONO AMPLIFIER

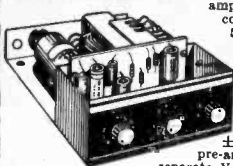

A superb solid state audio amplifier. Brand new components throughout. 5 Silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz. 30KHz \pm 3db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3" high x 6" wide x 7 1/4" deep. AC 200/250V. PRICE £15.00. P. & P. 85p.

DE LUXE STEREO AMPLIFIER

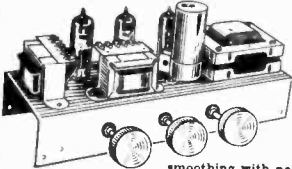

A.C. mains 200-240 v. U.S.A. heavy duty fully isolated mains transformer with full wave rectification giving adequate smoothing with negligible hum. Valve line-up: 2 x ECL86 Triode Pentodes x EZ80 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 8 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" w x 4" d. Overall height including valves 5". Ready built and tested to a high standard. £12.50. P. & P. 85p.

ALL PURPOSE POWER SUPPLY UNIT 200/240V. A.C. Input. Four switched fully smoothed D.C. outputs giving 6v. and 7 1/2v. and 9v. and 12v. at 1 amp on load. Fitted insulated output terminals and pilot lamp indicator. Hammer finish metal case overall size 6" x 3 1/4" x 2 1/4". Ready built and tested. Price £6.35. P. & P. 85p.

VYNAIR & REXINE SPEAKERS & CABINET FABRICS app. 64 in. wide. Our price £1.30 yd. length. P. & P. 35p per yd. (min. 1 yd.). S.A.E. for samples.

HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3-5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. A.C. mains 200/240V. Supplied absolutely Brand New completely wired and tested with good quality output transformer. P. & P. 85p. BARGAIN PRICE £5.00

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 15 alternatives. Primary: 0-210-240V. Secondary combination: 0-5-10-15-20-25-30-35-40-50-60v. half wave at 1 amp, or 10-10-10, 20-20-20, 30-30-30v. at 2 amps full wave. Size 3in. long x 3 1/4in. wide x 3in. deep. Price £2.75. P. & P. 75p.

MAINS TRANSFORMER. For power supplies. Pri. 200/240V. Sec. 9-0-9 at 500 mA. £1.35. P. & P. 35p. Pri. 200/240V. Sec. 12-0-12 at 1 amp. £1.50. P. & P. 55p. Pri. 200/240V. Sec. 10-0-10 at 2 amp. £2.20. P. & P. 70p.

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P.U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-18v. battery or from H.T. line 200/300V. Frequency response 15Hz-25KHz. Gain 26dB. Solid encapsulation size 1 1/4" x 1 1/4" x 1/4". Brand new complete with instructions. Price £1.50 P. & P. 15p.

STEREO-DECODER SIZE 2" x 3" x 1 1/2"

Ready built. Pre-aligned and tested. Sens. 20-60mV for 9-15V neg. earth operation. Can be fitted to almost any FM VHF radio or tuner. Stereo beacon light can be fitted if required. Full details and instructions (Inclusive of hints and tips) supplied. £6.25 plus 20p P. & P. Stereo beacon light if required 45p extra.



QUALITY RECORD PLAYER AMPLIFIER MK. II
A top quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in wide x 3in deep x 6in high. Ready built and tested. PRICE £8.50. P. & P. 90p.
ALSO AVAILABLE mounted on board with output transformer and speaker. PRICE £7.75. P. & P. £1.00.


Open 9.30-5.30 Monday to Friday. 9.30-5 Saturday
Closed Wednesday.
Prices and specifications correct at time of press. Subject to alteration without notice

HARVERSON SURPLUS CO. LTD.

(Dept. P.E.) 170 HIGH ST., MERTON, LONDON, S.W.19 Tel.: 01-540 3985

A few minutes from South Wimbledon Tube Station
SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

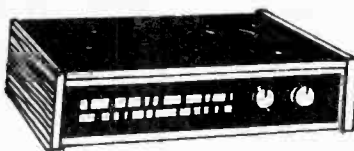HARVERSONIC MAINS OPERATED SOLID STATE STEREO FM TUNER



Enjoy Fabulous Stereo Radio at this Low Introductory Price!

Designed and styled to match our 10 + 10 amplifier but will suit any other standard stereo amplifier. The design incorporates the very latest circuitry techniques with high-grain, low noise IF stages. Automatic frequency control to 'lock on' station and prevent drift. IC stereo decoder for maximum stereo separation. L.E.D. for stereo beacon indicator. Nominal output of tuner 100mV. Approximate size 12 1/2in wide x 8in deep by 2 1/2in high. Supplied ready built, fully tested and fully guaranteed (not available in kit form). Price £27.50. Post and Packing £1.20.

LATEST ACOS GP91/18C mono compatible cartridge with T/O stylus for LP/EP/78. Universal mounting bracket. £1.75. P. & P. 18p.

CERAMIC STEREO CARTRIDGE. Universal mounting brackets and turnover stylus. 70mV per channel output. ONLY £2.06. P. & P. 18p.

SONOTONE 9TACH COMPATIBLE STEREO CARTRIDGE T/O stylus Diamond Stereo LP and Sapphire 78. ONLY £2.62. P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. £3.18. P. & P. 18p.


LATEST GENERAL T/O STEREO COMPATIBLE CARTRIDGE for EP/LP/78. £1.98. P. & P. 18p.

LATEST T/O MONO COMPATIBLE CARTRIDGE for playing EP/LP/78 mono or stereo records on mono equipment. Only £1.75. P. & P. 18p.

SPECIAL OFFERS

Mullard LP1159 RF-IF Double Tuned Amplifier Module for nominal 470KHz. Size approx. 2 1/2" x 1 1/4" x 1 1/4" 7-6V + earth. Brand new pre-aligned. Full specification and connection details supplied. £2.50 + P. & P. 12p.

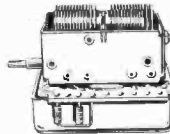Fye VHF/FM Tuner Head covering 88-108M/Hz. 10.7M/Hz IF output 7-8V + earth. Supplied pre-aligned, with (illus.) full circuit diagram and connection details supplied. Beautifully made with precision-gear FM and 323 Ft + 323 Ft AM Tuning Gauge only £3.50 + P. & P. 35p.



PRECISION MADE

Push Button Switch bank. 8 Buttons giving 16 S/P C/O interlocked switches plus 1 Cancel Button Plus 3 d/p c/o. Overall size 5" x 2 1/2" x 1". Supplied complete with chrome finished switch buttons £1.50 ea. + 10 P. & P.

HI-FI LOUSPEAKER SYSTEM Mk II

Beautifully made simulated teak finish enclosure now with most attractive slatted front. Size 16 1/2" high x 10 1/2" wide x 9" deep (approx.). Fitted with E.M.I. Ceramic Magnet 13" x 8" bass unit, H.F. tweeter unit and crossover. AVAILABLE IN NOMINAL 4 ohm, 8 ohm or 16 ohm impedance (state which).

OUR PRICE £12.50 each. Carr. £1.60

Cabinet Available Separately £7.50. Carr. £1.20.

Also available in 8 ohms with EMI 13" x 8" bass speaker with parasitic tweeter £11.00. Carr. £1.60

LOUDSPEAKER BARGAINS


5in. 3 ohm £1.45, P. & P. 35p. 7 x 4in. 3 ohm £1.60, P. & P. 48p. 10 x 6in. 3 or 15 ohm £2.50, P. & P. 75p. E.M.I. 8 x 5in. 3 ohm with high flux magnet £2.06, P. & P. 50p. E.M.I. 13 1/2" x 8in. with high flux ceramic magnet with parasitic tweeter 3, 8 or 15 ohm £4.12, P. & P. 85p. E.M.I. 13 x 6in. 3, 8 or 15 ohm with inbuilt tweeter and crossover network £5.50. P. & P. 95p. E.M.I. tweeter. Approx. 3". Available 3 or 8 or 15 ohms. £2.00 + 25p. P. & P.

"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 11 1/2" x 14 1/2" x 1 1/4" deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls. Send S.A.E. for details. Only £7.68 each. P. & P. 70p.

Now also available 8", 10 watts r.m.s. 20 watt peak 40 Hz-20,000 Hz. Overall depth 1". Ideal for Hi-Fi or for use in cars. £5.18 + 40p P. & P.

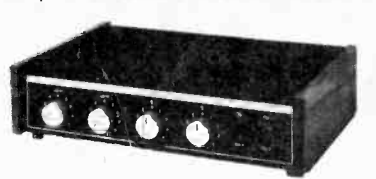
HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal Cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 8 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specifications: Power output: 14 watts r.m.s. per channel into 8 ohms. Frequency response \pm 3dB 12-30,000 Hz. Sensitivity: better than 80mV into 1M Ω . Full power bandwidth: \pm 3dB 12-15,000 Hz. Bass, boost approx. to \pm 12dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 35v. at 1-0 amp.

Overall Size 12" w. x 8" d. x 2 1/2" h.
Fully detailed 7 page construction manual and parts list free with kit or send 25p plus large S.A.E. AMPLIFIER KIT £15.00 P. & P. 66p (Magnetic input components 33p extra) POWER PACK KIT £5.35 P. & P. 85p CABINET £5.35 P. & P. 75p P. & P. only £1 if all units purchased at same time. Full after sales service.

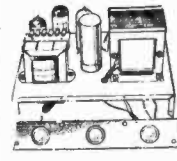Also available ready built and tested £32.50. P. & P. £1.00. Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi-Fi Discotheque use, etc.



3-VALVE AUDIO AMPLIFIER HA34 MK II.

Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis size 7 1/2" w. x 4" d. x 4 1/4" h. Incorporates ECC83, EL84, EZ80 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £7.75. P. & P. 85p.

HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. £6.50. P. & P. 80p.

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls. A separate bass and treble control are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EFS6 and EZ80 rectifier. Simple instruction booklet 25p x SAE (Prec with parts). All parts sold separately. ONLY £12.00. P. & P. £1.25. Also available ready built and tested £16.50. P. & P. £1.20.



SPECIAL OFFER

Limited number of the latest BSR CI 41R1 Auto/Manual changer de-luxe. Lightweight tubular arm cue-ing lever bias compensator £14.00 + £1.10 P. & P.

OUR PRICES INCLUDE VAT AT CURRENT RATES

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

ENGINEERS

FREE



YOURSELF FOR A BETTER JOB WITH MORE PAY!

Do you want promotion, a better job, higher pay? "New opportunities" shows you how to get them through a low-cost, Home Study Course. There are no books to buy and you can pay as you learn.

This easy to follow GUIDE TO SUCCESS should be read by every ambitious engineer. Send for this helpful 76-page free book NOW! No obligation, nobody will call on you. It could be the best thing you ever did.

CHOOSE A BRAND NEW FUTURE HERE

CUT OUT THIS COUPON

Tick or state subject of interest. Post to address below.

- | | | |
|---|--|--------------------------|
| ELECTRICAL & ELECTRONICS | Air Registration Board Certs. | <input type="checkbox"/> |
| Practical Radio & Electronics (with kit) | MAA/IMI Dip. | <input type="checkbox"/> |
| Electronic Engineering Certificate | CONSTRUCTIONAL | |
| General Elect. Eng. Certificate | Heating Ventilating & Air Conditioning | <input type="checkbox"/> |
| C. & G. Elect. Installations | Architectural Draughtsmanship & Design | <input type="checkbox"/> |
| Elect. Install. & Work | L.I.O.B. | <input type="checkbox"/> |
| C. & G. Elect. Technicians | Carpentry & Joinery | <input type="checkbox"/> |
| | Plumbing Technology | <input type="checkbox"/> |
| | General Building | <input type="checkbox"/> |
| | Painting & Decorating | <input type="checkbox"/> |
| RADIO & TELE-COMMUNICATIONS | MECHANICAL | |
| Colour TV Servicing | A.M.S.E. (Mech.) | <input type="checkbox"/> |
| C. & G. Telecoms. Technician's Cert. | General Mech. Eng. | <input type="checkbox"/> |
| C. & G. Radio, TV & Electronics Mech. Cert. | Inst. Engineers & Technicians | <input type="checkbox"/> |
| Radio & TV Engineering Course | Maintenance Engineering | <input type="checkbox"/> |
| Radio, Servicing & Repairs | Welding | <input type="checkbox"/> |
| Radio Amateur's Exam | MANAGEMENT & PRODUCTION | |
| | Computer Programming | <input type="checkbox"/> |
| | Inst. of Cost & Managements Accts. | <input type="checkbox"/> |
| AUTO & AERO | DRAUGHTSMANSHIP & DESIGN | |
| Motor Mechanics | General Draughtsmanship | <input type="checkbox"/> |
| C. & G. Motor V. Mechanics | A.M.I.E.D. | <input type="checkbox"/> |
| General Auto Engineering | Electrical Draughtsmanship | <input type="checkbox"/> |
| A.M.I.M.I. | | |

POST NOW

G.C.E.
—58 'O' & 'A' Level Subjects
—over 10,000 Group Passes!

Aldermaston College

Dept. TPE13, Reading RG7 4PF
also at our London Advisory Office, 4 Fore Street Avenue, Moorgate, London EC2Y 5EJ. Tel. 01-628 2721.

NAME (Block Capitals) _____
ADDRESS _____
Postcode _____
Other subjects of interest _____ Age _____
Accredited by C.A.C.C. Member of A.B.C.C.

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Unbeatable VALUE

Genuine GOLDRING Stylus P. & P. 25p

G800	£2.35	G850	£1.95
G800/H	£2.35	G800/E	£4.42

MICROPHONES P. & P. 25p

- UD130—Cardioid dynamic dual impedance 600 and 50kΩ **£6.58**
- ECM81—Cardioid condenser omni-directional 600 and 50kΩ impedance **£11.99**
- RX201—Cardioid dynamic 600Ω echo mike, 4 transistors, 1.5sec reverberation time, with volume control and on-off switch **£9.93**
- Philips type cassette mike **£1.65**
- Cassette stick mike with remote control **£1.30**
- Gem 2 station intercom (baby alarm) **£3.85**

CASSETTES (Low Noise) P. & P. 25p

	1-5	over 6
C60	35p	32p
C90	43p	40p
C120	55p	52p

SOLDERING IRONS P. & P. 25p

12V d.c. 15 watt **£1.24** 250V a.c. 40 watt **£1.40**

CABINET KITS P. & P. 85p per pair

12" x 8" x 4 1/2"	(8" x 5" or 7" x 4" cutout)	£2.90 each
12" x 12" x 7 1/2"	(10", 8" or 8" x 5" cutout)	£4.05 each
18" x 11" x 7 1/2"	(8" and 3", 8" x 5" or 8" cutout)	£5.10 each
22" x 14" x 7 1/2"	(13" x 8" or 12" and 3" cutout)	£6.15 each

ALL PRICES INCLUDE VAT
Items subject to availability and manufacturers' increase. U.K. only.

Riversdale Electronics
Mail Order Department **PE1**
P.O. Box 470, Manchester M60 4BU

P.E. ORION

Complete Kit of semiconductors £10.95
High quality printed circuit £3.40

THIS GLASS FIBRE P.C.B. IS ROLLER TINNED AND SCREEN PRINTED WITH COMPONENT LOCATIONS.

FERRANTI semiconductors

BFS59 17p	ZTX301 16p	ZTX502 20p	ZS174 29p
BFS60 18p	ZTX302 19p	ZTX503 21p	ZS176 38p
BFS61 19p	ZTX303 21p	ZTX504 25p	ZS178 65p
BFS96 18p	ZTX304 24p	ZTX530 22p	ZS270 16p
BFS97 19p	ZTX320 20p	ZTX531 23p	ZS271 25p
BFS98 20p	ZTX330 21p	ZTX550 20p	ZS272 28p
ZTX107 14p	ZTX331 23p	ZTX551 21p	ZS274 35p
ZTX108 12p	ZTX382 20p	2N3055 76p	ZS276 43p
ZTX109 14p	ZTX383 19p		ZS278 69p
ZTX212 19p	ZTX384 21p	* DIODES *	
ZTX213 18p	ZTX450 20p	ZS142 44p	
ZTX214 22p	ZTX451 20p	ZS170 14p	* ZENERS *
ZTX239 13p	ZTX500 16p	ZS171 19p	KS030A to
ZTX300 15p	ZTX501 17p	ZS172 25p	KS180A 41p
			BZV19 series 18p

- ZN414 radio microcircuit, with circuits and data **£1.25**
- ZN424E low noise audio i.c. with circuits and data **£1.50**
- ZN1034E precision timer i.c. with data **£3.23**
- ZN1040E universal count/display i.c. with data **£12.96**

PE TV SOUND SEPARATOR

Complete kit of semiconductors **£2.40**
High quality printed circuit board **£1.25**
Murata filters—SFE6-OMA 38p; CDA6 OMC 38p.
MOTOROLA BD699 £1.27; BD700 £1.41; MJE2955 £1.50; MJE3055 87p; MC1357PO £1.60; MJ4032 £4.88; MJ4035 £4.66.
PE JOANNA 77 ZTX108 £6.25, 183 ZS170 £18.30.
POSTAGE AND PACKING 15p per order. Orders over £5 post free.
All devices top grade, brand new, and to full manufacturers spec. We do not sell seconds or rejects. Send SAE for our data sheet and price list. We can supply any Ferranti device to order. SAE for quotation.
ALL PRICES INCLUDE VAT AT THE APPROPRIATE RATE

DAVIAN ELECTRONICS
PO BOX 38, OLDHAM, LANCS, DL2 6XJ

BI-PRE-PAK

The people for component bargains



Makers of Stirling Sound audio equipment

ORIGINATORS OF PRE-PACKED COMPONENTS IN BRITAIN—AND STILL LEADING!

XMAS OFFER TO SAVE £12

A Bi-Pre-Pak super special!

- ★ Prices include VAT and postage and packing in U.K.
- ★ Total Value £30—You pay £18
- ★ Satisfaction guaranteed
- ★ Order now—delivery by return

By buying 4 units together for £18 to make a Stereo FM Tuner/Amp. Separate, you still save 33 $\frac{1}{3}$ %

- F.M. TUNER FRONT END**
Ganged tuning; A.F.C. facility. Reduction-gear drive, 88–108 MHz. Usual price inc. VAT £8.01 **£5.34**
- I.F. BOARD**
Using I.C., designed for use with above front-end. Usual price inc. VAT £6.76 **£4.50**
- STEREO DECODER, USING I.C.**
Designed for use with the above modules, can also be used with other mono F.M. tuners. Ready aligned. (L.E.D. for stereo beacon available at 18p.) Usual price inc. VAT £7.22 **£4.82**
- 5 + 5 WATT MUSIC POWER I.C. AMP.**
Useful stereo power amplifier with good performance, at economy price. Usual price inc. VAT £8.01 **£5.34**

TOTAL VALUE AT REGULAR ADVERTISED PRICE £30. YOU PAY £18

SPECIAL OFFERS

LM 380 AUDIO I.C. (Marked SL 60745). Brand new and to spec. 3 watts R.M.S. out. With data. 75p*

Three 2XSN 7490. Brand new I.C.s to spec. decode counters. Only £1.20*

Five 3XSN 7400 Quad 2 input Nan gate I.C.s. Only 60p*

SUNDRY

RI PAK—Approx. 170 short-lead semi-conductors and components. PNP, NPN, diodes, rectifiers, etc. on PCBs. At least 30% factory marked. Some data supplied. 50p.

UHF 825 line tuner, rotary. £2.50.

Rev Counter (for cars) (8%), £1.00.*

Books by Bernard's Publications, Newnes-Butterworth's, etc.

THE FREE CATALOGUE

New edition better than ever. It's your's for free and well worth getting—only please send large S.A.E. with 10p stamp if we have to post it to you.

TERMS OF BUSINESS:

VAT at 25% must be added to total value of order, except for items marked * or (8%), when VAT is to be added at 8%. No VAT on overseas orders. POST & PACKING Add 22p for UK orders unless shown otherwise. Minimum mail order acceptable—£1. Overseas orders, add £1 for postage. Any difference will be credited or charged. PRICES Subject to alteration without notice. AVAILABILITY All items available at time of going to press when every effort is made to ensure correctness of information.

BI-PRE-PAK LTD

Co. Reg. No. R27019

222 224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SSO 9DF.

TELEPHONE: SOUTHEND (0702) 46344.

FOUNDED IN 1959

NEW RANGE TRANSISTOR AND COMPONENT PACKS

TP SELECTION

- TP5** 20 Transistors. PNP Germanium, Red Spot A.F.
- TP6** 20 Transistors. PNP Germanium, White spot RF.
- TP7** 1 2N174 150V 80Vce Power Transistor, with mounting assembly.
- TP19** 100 diodes, mixed Germanium, Gold-bonded, etc. Marked/Unmarked.
- TP23** Twenty NPN Silicon uncodded TO5. Similar to BFY50/2, 2N696, 2N1613, etc. Complementary to TP24.
- TP24** Twenty PNP Silicon, uncodded TO5. Similar to BFY64, 2N2904/5.
- TP29** 8 power diodes 400V, 1.25A Silicon FST 3/4.

UT SELECTION

- UT1** 50 PNP's Germanium, AF and RF.
- UT2** 150 Germanium diodes, min. glass.
- UT4** 100 Silicon diodes, min. glass, similar to IN914, IN916.
- UT5** 40 250mW Zener diodes OAZ24 range; average 50% good.
- UT7** 30 Silicon rectifiers 750mA, mixed voltages. Top Hats, etc.
- UT9** 40 NPN Silicon planers. Similar to 2N3707-11 range. Low noise amps.
- UT12** 25 2N3702/3 Transistors. PNP Silicon. Plastic to 92.

CP SELECTION

- CP1** Mixed bag of capacitors—Electrolytic, Paper, Silver Mica (Approx. 150—sold by weight).
- CP2** 200 (approx.) Resistors, various types, values, watts. (Sold by weight.)
- CP3** 40 Wire-wound resistors, mixed.
- CP4** 12 pots—pre-set, w/wound, carbon, dual, with/without switches—all mixed.
- CP7** Heat sinks, assorted. To fit SO-Z (OC72) TO-1 (AC128), etc.


ALL ABOVE PACKS—60p EACH. TP Tested and Guaranteed; UT Untested, unmarked; CP Components

CAPACITOR DISCHARGE IGNITION KIT

Simple to assemble and fit. Improves car performance. SAVES ON FUEL. P. & P. 50p.

£7.50*

BI-PRE-PAK X-HATCH GENERATOR MK. 2

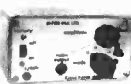

Four-pattern selector switch
3in x 5in x 3in
Ready-built and tested
In kit form

£9.93*

£7.93*

Case add 50p for postage and packing. Is valuable to industrial and home user alike. Improved circuitry assures reliability and still better accuracy. Very compact, self-contained. Robustly built. Widely used by TV rental and other engineers. With reinforced fibreglass case. Instructions, but less batteries. (Three U2 type required.)

TV SIGNAL STRENGTH METER*

Complete kit as described in 'Television' £19.50 plus 40p for P. & P. plus VAT at current rate.

SS300 POWER SUPPLY STABILISER

Add this to your ungalvanised supply to obtain a steady working voltage from 16 to 60V for your audio system, workbench, etc. Money saving and very reliable

£3.25*

PLASTIC POWER TRANSISTORS

40 WATT SILICON*

Type	Polarity	Gain	VCE	Price
40N1	NPN	15	15	20p
40N2	NPN	40	40	30p
40P1	PNP	15	15	20p
40P2	PNP	40	40	30p

90 WATT SILICON*

Type	Polarity	Gain	VCE	Price
90N1	NPN	15	15	25p
90N2	NPN	40	40	35p
90P1	PNP	15	15	25p
90P2	PNP	40	40	35p

If you prefer not to cut coupon out, please mention PE12 when writing.
* Phone, Write or Call. Give us your Access number and we will do the rest.

To BI-PRE-PAK, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX

Please send

for which I enclose inc VAT

NAME


ADDRESS

PE1

RETURN OF POST MAIL ORDER SERVICE

BSR HI-FI NEW CHANGER STEREO & MONO

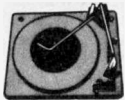Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability BCS 18 months' guarantee. AC 200/250V. Size 18 1/2 x 11 1/2 in.



Above motor board 3 1/2 in. Below motor board 2 1/2 in. with STEREO and MONO XTAL £10.95 Post 60p.

PORTABLE PLAYER CABINET


Modern design. Bezels covered. Large front grille. Lift-up lid. Chrome fittings. Approx. size 17 1/2 x 15 1/2 x 7 in. Few only in red and black reline. £5.25 Post 50p. Motor board cut for Garrard deck

B.S.R. SINGLE PLAYER

NEW MODEL. IDEAL DISCO PLAYER. 3 SPEEDS. BALANCED ARM. CURING DEVICE. STEREO CERAMIC CARTRIDGE. BARGAIN. SIMILAR TO MP60



£17.50 PLUS POST 75p

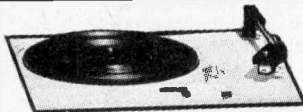

R.C.S. DISCO DECK SINGLE RECORD PLAYER

Fitted with auto stop. Compatible cartridge. Baseplate. Size 11 1/2 x 8 1/2 in. Turns table. Size 7 in diameter. A/C mains. 200/250V motor has a separate winding 14 volt to power a small amplifier. Three speeds. Plays all records.

£6.95 Post 45p

TWO FOR £12.95. Post 75p

HEAVY METAL PLINTH

Post 75p

With P.V.C. Cover. Cut out for most B.S.R. or Garrard decks. Size 18 1/2 x 14 1/2 x 7 1/2 in.

£5.95

R.C.S. STEREO BARGAIN

Two full size loudspeakers 18 1/2 x 8 1/2 in. Player unit clips to loudspeakers making it extremely compact. Overall size only 18 1/2 x 10 x 8 1/2 in. 3 watts per channel, plays all records 33 r.p.m., 45 r.p.m. Separate volume and tone controls. 250V AC Mains.

FEW ONLY



Attractive Teak finish Weight 18 lb.

Bargain Price £25 85p Carriage

SPECIAL OFFER! SMITH'S CLOCKWORK 15 AMP TIME SWITCH UP TO 60 MINUTES

OUR PRICE £2.50 Post 45p



ALUMINIUM BOXES. 3 x 3 x 3 1/2 in 75p; 4 x 4 x 4 in 90p; 6 x 4 x 4 in 110p; 9 x 4 x 4 in 130p; 12 x 4 x 4 in 150p.

BLANK ALUMINIUM CHASSIS. 18 s.w.g. 3 1/2 in sides 6 x 4 in 55p; 8 x 6 in 65p; 10 x 7 in 80p; 12 x 8 in 95p; 14 x 9 in 110p; 16 x 10 in 130p; 18 x 10 in 140p. ALUMINIUM PANELS 18 s.w.g. 6 x 4 in 15p; 8 x 6 in 25p; 10 x 8 in 35p; 12 x 10 in 45p; 14 x 12 in 55p; 16 x 14 in 65p; 18 x 16 in 75p. 1 1/2 inch DIAMETER WAVELENGTH SWITCHES, 45p ea. 2 p. 3-way, or 2 p. 6-way, or 3 p. 4-way. 1 p. 1. 2-way, or 4 p. 2-way, or 4 p. 3-way. TOGGLE SWITCHES. 3p. 20p; 4p. 25p; 4p. dt. 30p.


BRITISH FM/VHF TUNING HEART

88 to 108 Mc/s British made. 2 Transistors ready aligned —requires 10-7 Mc/s L.F. Complete with tuning gang. Connections supplied but some technical experience essential.

Our price £1.95 Post 20p

TESTED I.F. STRIP 44.95. TESTED DECODER 24.95

R.C.S. STEREO FM TUNER BRITISH MADE

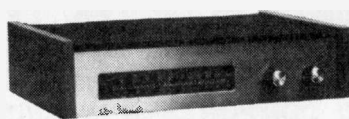

This completely cased mains powered HI-FI Tuner with brushed aluminium fascia is British made using the latest circuitry. Few Only. Post 75p. £30

R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Hubs, Tape, P.T., Guitar, etc. Can be used with Battery 9-12V or H.T. Lin. 200-300V d.c. operation. Size: 1 1/2 x 1 1/2 in. Response 25 cps to 25 kc/s. 26 dB gain. For use with valve or transistor equipment. £1.45 Full instructions supplied. Details S.A.E.

R.C.S. POWER PACK KIT

18 VOLT, 750mA. Complete with printed circuit board and assembly instructions. £3.25 Post 45p
12 VOLT 300mA KIT, 23 9 VOLT 1 AMP KIT, 23.25.

4MFD 800V DC PAPER CAPACITOR Block Capacitor. Ideal as Filter Unit in 100 watt Loudspeaker Systems. 95p each, post 30p.

NEW ELECTROLYTICS		CAN TYPES	
2/350V	20p	250/25V	18p
4/350V	30p	500/25V	20p
8/350V	22p	100 + 100/275V	85p
16/350V	30p	150 + 200/275V	70p
32/350V	50p	2 + 2/250V	50p
25/25V	10p	8 + 16/850V	50p
50/50V	10p	16 + 16/850V	50p
100/25V	10p	32 + 32/850V	50p
		4700/83V	95p

LOW VOLTAGE ELECTROLYTICS. 1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p. 500mF 12V 15p; 25V 20p; 50V 30p. 1000mF 12V 20p; 25V 35p; 50V 47p; 100V 70p. 2000mF 8V 25p; 15V 40p; 30V 57p. 2500mF 6V 25p; 3000mF 25V 47p; 50V 65p. 5000mF 6V 25p; 12V 42p; 25V 75p; 35V 85p; 50V 95p. CERAMIC 1pF to 0.01mF, 4p. Silver Mica 2 to 5000pF, 4p. PAPER 350V-0.1 7p; 0.5 18p; 1mF 15p; 2mF 160V 15p. 200V-0.001 to 0.06 4p; 0.1 10p; 0.25 23p; 0.47 25p. TWIN GANG. 40-0° 200pF + 175pF 21 20p. 200mF motor drive 365pF + 365pF with 250V + 25pF, 50p; Twin 600pF 75p. Twin 410pF 50p. Twin 120pF 50p. SHORT WAVE SINGLE. GANGABLE 60pF, 65p. NEON PANEL INDICATORS 250V AC/DC. Amber 30p. RESISTORS. 1/4 W, 1/2 W, 20% 2p; 2W, 10p. 100 to 10M. HIGH STABILITY. 1/2 W 2% 10 ohms to 6 meg., 10p. Ditto 5%. Preferred values 10 ohms to 10 meg., 4p. WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt, 10 ohms to 100K 12p each. TAPE OSCILLATOR COIL Valve type 35p. FERRITE ROD 8 x 1/2 in 20p; 6 x 1/2 in 20p; 3 x 1/2 in 10p

MAINS TRANSFORMERS

ALL POST Small 45p each Large 75p each

250-0-250 80mA. 6-3V 2 amp £2.90
250-0-250 80 mA. 6-3V 3-5A 6-3V 1A or 5V 2A £4.60
350-0-350 80 mA 6-3V 3-5A, 6-3V 1A or 5V 2A £5.80
300-0-300V 120mA. 6-3V 4A C.T.; 6-3V 2A £7.00
SMALL 250V 45mA. 6-3V 2A 2 1/2 x 2 1/2 in £1.25
HEATER TRANS. 6-3V 1 amp 86p; 3 amp £1.40
GENERAL PURPOSE LOW VOLTAGE. Tapped outputs at 2 amp, 3 A, 5, 6, 8, 9, 10, 12, 15, 18, 24, 30V £4-60
1 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £4-60
2 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £7-00
5 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £11-25
10, 30, 40V 2 amp. £2; 20V 3 amp. £2.80; 5, 8, 18V, 5 amp. £1-50; 6-0-5V 500mA 2 1/2; 9V 1 amp. £1; 12V 300mA. £1.75; 15V 500mA. £1.12V 750mA. £1; 40V 2 amp. £1.75; 23-0-23V 4 amp. D.C. £2.45; 16V 1 amp. 95p; 16V 2 A. £2; 5V, 8V, 10V, 16V 1 A. £1.90; 20V 1A. £2. AUTO TRANSFORMERS. 115V to 230V or 230V to 115V 160W 25; 250W 26; 400W 27; 500W 28. CHARGER TRANSFORMERS. 11A 23-75 4 amp £4-60. FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12V outputs. 1 1/2 amp 40p; 2 amp 55p; 4 amp 85p.

MAINS ISOLATING TRANSFORMER

Primary 0-110-240V. Secondary 0-240V 3 amps 720 watts. Insulated terminals. Varnish impregnated. Fully enclosed in steel case with fixing feet. £13.50 Carr. Famous make (Value £19) OUR PRICE 95p Can be used as 800 watt auto transformers 240-110V.

VOLUME CONTROLS 80 Ohm Coax 5p yd.

Long spindles. Midget Size 5 K. Ohms to 2 Meg. LOG AMP. L/S 25p. D.P. 40p. STEREO L/S 55p. D.P. 75p. FRINGE LOW LOSS 10p per yd. Ideal 625 and colour. 9 p yd

Wire Wound controls 1 1/2 in diam. 3 Watts. 10 ohms to 100K British Made with long spindles 1 in. 85p each. DUAL CONCENTRIC POT 500K LOG AMP AND 500K LIN D.P. switch. Inner spindle 3 1/2 in; outer spindle 2 1/2 in 75p.

E.M.I. 13 1/2 x 8 in. SPEAKER SALE!

With tweeter and crossover. 10 watt. State 8 or 8 ohm. As illustrated. Post 45p £5.25

With flared tweeter cone and ceramic magnet. 10 watt. Bass res. 45-60 c/s. Flux 10,000 gauss. State 3 or 8 or 15 ohm. Post 45p 13 x 8 in Bass unit 20 watt 8 or 15 ohm 26-80. £3.45



LOUDSPEAKER FRONT GRILLES

Teakwood strips mounted on cloth backing, easily glued on to baffles to modernise cabinets. Size 18 1/2 in x 10 1/2 in. 75p Or size 10 1/2 in x 7 1/2 in. 45p

GOODMANS 6 1/2 in. HI-FI SPEAKER

8 ohm. 10W. Large ceramic magnet. Special Rubber cone surround. Frequency response. Twin cone. 30-12,000 c/s. Ideal F.A. Columns. HI-FI Enclosure Systems, etc. £4.60



ELAC CONE TWEETER

The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 c/s to 18,000 c/s. Size 2 1/2 x 3 1/2 x 2 in deep. Rating 10W, 3 ohm. Crossover £1-85 £2.20 Post 30p.

GOODMANS 8 in. WOOFER

8 ohm 15 watt. Rubber surround. Heavy ceramic magnet. Bass resonance 35 cps. Frequency response 30-8,000 cps. Ideal bass unit for HI-FI system. Post 50p £6.75



SPECIAL OFFER LOUDSPEAKERS

3 ohm, 2 1/2 in; 3 1/2 in; 5 in; 7 x 4 in; 8 x 5 in. 8 ohm, 2 1/2 in; 3 1/2 in; 5 in; 8 in; 4 in; 5 in; 6 x 4 in. 15 ohm, 3 1/2 in; 6 x 4 in; 5 x 4 in; 7 x 4 in. 25 ohm, 2 1/2 in; 5 x 3 in; 6 x 3 in; 7 x 4 in. 35 ohm, 3 in; 6 in. 64 ohm 2 1/2 in. 80 ohm, 2 1/2 in; 2 1/2 in. 120 ohm 3 in. £1.25 EACH

RICHARD ALLAN TWIN CONE LOUDSPEAKERS. 3 in diameter 4W 22-60, 10 in diameter 5W 22-85; Post 25p 12 in diameter, 6W, 22-90; 3 or 8 or 15 ohm models. SPEAKER COVERING MATERIALS. Sample Large S.A.E. Horn Tweeters 2-18K/c/s. 8W 6 ohm or 15 ohm £2-50 De Luxe Horn Tweeters 2-18K/c/s. 15W. 15 ohm £4-60 TWO-WAY 3,000 c.p.s. CROSSOVERS 3, 8 or 15 ohm 21-85

CASSETTE MACHINE MOTOR. 6 Volt. Will replace many types 21-25.

R.C.S. 3 WAY CROSSOVER

Complete with 12 ft. twin lead fitted with din speaker plug. Ready assembled with leads for speakers, bass, mid and tweeter. Crossover frequencies—950 cps and 3,000 cps. For systems up to 25 watts. £2.25

VALVE OUTPUT TRANSFORMER 50p. MIKE TRANSFORMER MU metal 100-1 £1-25. PUSH-PULL VALVE OUTPUT TRANSFORMERS. 50 watt £14-00 100 watt £20-00

ELECTRO MAGNETIC PENDULUM MECHANISM

1.5V d.c. operation over 200 hours continuous on SP2 battery, fully adjustable swing and speed. Ideal displays, teaching electro magnetism or for metronomes. 95p Post 30p

R.C.S. "MINOR" 10 watt AMPLIFIER KIT

This kit is suitable for record players, guitars, tape playback, electronic instruments or small F.A. systems. Two versions available: Mono, £12-50; Stereo, £20. Post 45p. Specification 10W per channel; input 100mV; size 9 1/2 x 3 x 3 in. approx. S.A.E. details. Full instructions supplied.

COAXIAL PLUG 10p. PANEL SOCKETS 10p. LINE 18 OUTLET BOXES. SURFACE MOUNTING 50p. BALANCED TWIN RIBBON FEEDER 300 ohms, 7p yd. JACK SOCKET 3rd. open-circuit 20p. closed circuit 30p; Chrome Lead Socket 45p. Phone Plugs 7p. Phone Socket 7p. JACK PLUGS 3rd. Chrome 30p; 3-5mm Chrome 20p. DIN SOCKETS Chassis 3-pin 10p; 5-pin 10p. DIN SOCKETS Lead 3-pin 25p; 5-pin 25p. DIN PLUGS 3-pin 25p; 5-pin 25p. VALVE HOLDERS 5p; CERAMIC 10p; CANS 5p.

CASH PRICES INCLUDE VAT • 30p MINIMUM POST AND PACKING • CALLERS WELCOME •

RADIO COMPONENT

Illustrated Brochure, Radio Books & Component Lists 10p Written guarantee.

RETURN OF POST MAIL ORDER SERVICE

JUST RELEASED R.C.S. 100 watt VALVE AMPLIFIER



Four inputs. Four way mixing, master volume, treble and bass controls. Suits all speakers. This professional quality amplifier chassis is suitable for all groups, disco, P.A., where high quality power is required. 5 speaker outputs. A/C mains operated. Slave output. Produced by demand for a quality valve amplifier. Price **£85**, carr. **£2-50** suitable carrying cabinet **£14**.

ANOTHER R.C.S. BARGAIN!

ELAC 9 x 5in. HI-FI SPEAKER TYPE 59RM
This famous unit now available, 10 watts, 8 ohm.
Price **£3-45** Post 40p



8" or 10" x 6" ELAC HI-FI SPEAKER

Dual cone plasticised roll surround. Large ceramic magnet. 50-16,000 cps. Bass resonance 55 cps. 8 ohm impedance. 10 watts.

10in round **£5**.

£4-35


TEAK VENEER HI-FI SPEAKER CABINETS Fluted Wood Fronts

MODEL "A". 20 x 13 x 12in For 12 in. dia. or **£12-50** Post 95p

MODEL "B". 16 x 10 x 9in For 12 x 8in. or **£6-95** Post 8 in. speaker

MODEL "4C". 30 x 20 x 12in. Reflex cabinet will accept 1-12in. bass unit, 1-2in. mid range, 1-2in. tweeter. Teak finish. Grooved front. **£21-50** Carr. **£3**

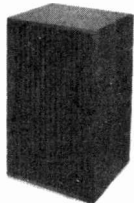
LOUDSPEAKER CABINET WADDING 18in wide, 20p ft.



GOODMANS CONE TWEETER

3in. diam. 18,000 C.P.S. 25 WATTS 8 Ω **£3-60**

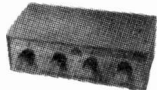BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt battery operated. **£5-20**



STEREO VERSION OF ABOVE £6-85.

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built with volume, treble and bass controls. 18 volt battery operated. Mains Supply **£3-45**.

THE "INSTANT" BULK TAPE BRAKE & HEAD DEMAGNETISER. Suitable for cassettes, and all sizes of tape reels. A.C. mains 200/250V. Leaflet S.A.E. **£4-35** Post 40p




WAFER HEATING ELEMENTS THIN

OFFERING 1001 USES for every type of heating and drying applications in the home, garage, greenhouse factory (available in manufacturing quantities). Approx size 10½ x 8½ x ¼ in. Operating voltage 200/250V. a.c. 250 watts approx. Printed circuit element enclosed in asbestos fitted with connecting wires. Completely flexible providing safe Black heat. British-made for use in photocopyers and print drying equipment.

Ideal for home handymen and experimenters. Suitable for Heating Pads, Food Warmers, Convector Heaters, etc. Invaluable aid for bird houses, incubators, etc., etc. Can be used in series for lower heat. Or in parallel for higher heat applications.

ONLY 40p EACH (FOUR FOR £1-50)
ALL POST PAID - Discounts for quantity.

BAKER MAJOR 12" £11-50

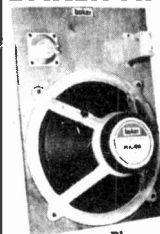

Post 60p
30-14,500 c/s. 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwell. Bass resonance 40 c/s Rated 25 watts. NOTE: 3 or 8 or 15 ohms must be stated.

Module kit. 30-17,000 c/s with tweeter, crossover, baffle and instructions. **£14-50**

Please state 3 or 8 or 15 ohms. Post 60p

BAKER SPEAKERS "BIG SOUND"

Robustly constructed to stand up to long periods of electronic power. As used by leading groups. Useful response 30-13,000 cps. Bass Resonance 55 cps.

GROUP "25"

12in 30 watt
3, 8 or 15 ohms.

£8-95

Post 50p

GROUP "35"

12in 40 watt
3, 8 or 15 ohms.

£10-50

Post 50p

GROUP "50"

15in. 60 watt
8 or 15 ohms.

£19-50

Post 90p

GROUP "50/12"

12in 75 watt professional model. 8 ohms or 15 ohms

£14-50

Post 80p

MAJOR 100 WATT ALL PURPOSE TRANSISTOR AMPLIFIER

All purpose transistorised. Ideal for Groups, Disco and P.A. 4 inputs speech and music. 4 way mixing. Output 8/15 ohm a.c. Mains. Separate treble and bass controls. Guaranteed. Details S.A.E. **DE-LUXE MODEL IN WOOD CABINET. BLACK. £75.**




£65 Carr. **£1-00**

NEW MODEL MAJOR 50 WATT

4 inputs, 2 way mixing, £49-95. Carr. £1. Ideal disco amp.

QUALITY LOUDSPEAKER ENCLOSURE

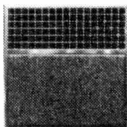Teak veneered ½ in thick wood cabinet. Size 18½ in x 18½ in x 8½ in. Weight 28lb. This cabinet features a wide mesh Silver Grill covering a separate compartment for mounting Tweeters or Mid-Range Horn. The fully sealed bass compartment is cut out for 6½ in Woofer. **£7-50**. Carr. **85p**. Rosewood Version **£8-50**. Carr. **85p**. Baffle could be cut for larger speaker.



P.W. SOUND TO LIGHT DISPLAY

Complete kit of parts with R.C.S. printed circuit. Three 1000 watt channels. As featured in December Practical Wireless. Price **£12-50**
Cabinet extra **£3**.

R.C.S. STEREO DECODER

British made. Stereo aligned and tested. Complete **£4-95** with instructions. Size 3in x 2in.

WEYRAD TYPE COILS

P50/20C	40p	RAFW	85p
P50/LAC	60p	OFTI	65p
P50/20C	40p	LFDT4	65p
PCAL	85p	Twin gang	£1-20

E.M.I. TAPE MOTOR

4 pole, 240 v. 135 mA. Size 3½ x 2½ x 2½ in. 1200 rpm. Spindle ¼ in. diameter. 80v version **£1**.

£1-85

Post 45p

E.M.I. GRAM MOTOR

120V or 240V a.c. 2,400 rpm. 2-pole 70mA. Size 2½ x 2½ x 2½ in.

£1-25

Post 35p

BAKER HI-FI SPEAKERS HIGH QUALITY — BRITISH MADE REGENT

12in. 20 watts

An inexpensive unit for the beginner in high fidelity and for general purposes. May be used to improve any Radio, Amplifier, Hi-Fi or Television receiver. Bass Resonance 45cps Flux Density 12,000 gauss Useful response 45-13,000cps 3 or 8 or 15 ohm models.

£10-50 Post 50p

DE-LUXE Mk II 12in. 15 watts

Especially designed to provide full range reproduction at an economical cost. Suitable for use with any high fidelity system. Built-in concentric tweeter cone. Bass Resonance 30cps Flux Density 14,000 gauss Useful response 25-16,000cps 8 or 15 ohms models.

£13-50 Post 50p

SUPERB

12in. 25 watts

A high quality loudspeaker, its remarkable low cone resonance ensures clear reproduction of the deepest bass. Fitted with a special copper drive and concentric tweeter cone resulting in full range reproduction with remarkable efficiency in the upper register. Bass Resonance 25cps Flux Density 16,500 gauss Useful response 20-17,000cps 8 or 15 ohms models.

£17 Post 80p

AUDITORIUM 12in. 35 watts

A full range reproducer for high power. Electric Guitars, public address, multi-speaker systems, electric organs. Ideal for Hi-Fi and Discotheques. Bass Resonance 35cps Flux Density 15,000 gauss Useful response 25-16,000cps 8 or 15 ohms models.

£15-50 Post 80p

AUDITORIUM 15in 45 watts

A high wattage loudspeaker of exceptional quality with a level response to above 8,000 cps. Ideal for Public Address, Discotheques, Electronic instruments and the home Hi-Fi. Bass Resonance 35cps Flux Density 15,000 gauss Useful response 20-14,000cps 8 or 15 ohms models.

£19-50 Post 90p

Hi-Fi Enclosure Manual containing plans, designs, crossover data and cubic tables. 68p.

CUSTOMERS FREE CAR PARK


OPEN 9-6 p.m. WEDNESDAYS 9-1 p.m., SATURDAYS 9-5 p.m. (Closed for Lunch 1.15-2.30)

SPECIALISTS 337, WHITEHORSE ROAD · CROYDON

(Export: Remit cash and extra postage.)

Buses 50, 68, 159. Rail Selhurst

Telephone 01-684-1665

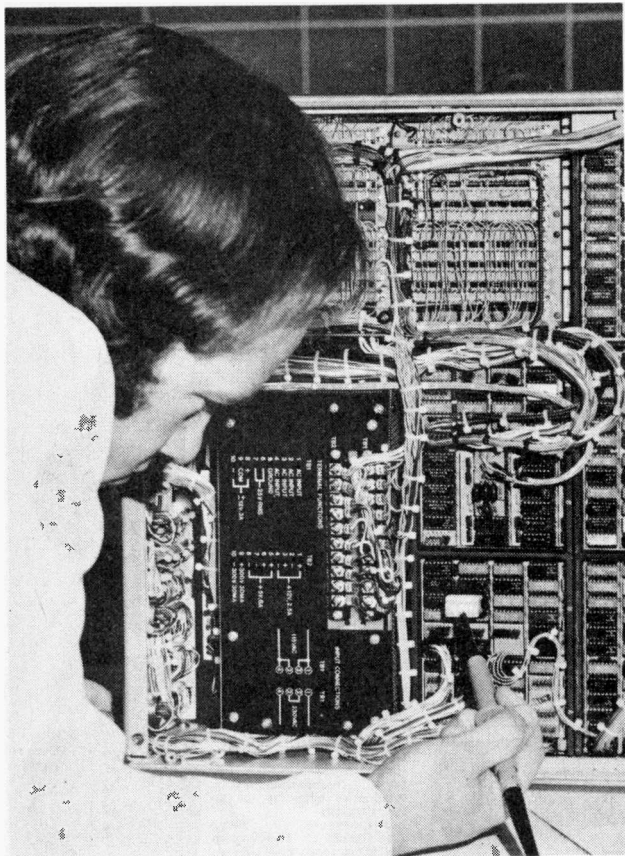

This hobby brings big rewards.

A soldering iron and a screwdriver. If you know how to use them, or at least know one end from the other, you know enough to enrol in our unique home electronics course.

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.


You build, see and learn as, step by step, we take you through all the fundamentals of electronics and show you how easily the subject can be mastered and add a new dimension not only to your hobby but also to your earning capacity.

All the training is planned to be carried out in the comfort of your own home and work in your own time. You send them in when you are ready and not before. These culminate in a final test and a certificate of success.


1

Build an oscilloscope.

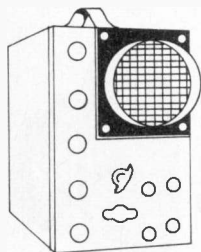As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.




2

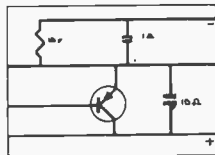

Read, draw and understand circuit diagrams.

In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.

3

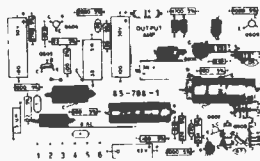


Carry out over 40 experiments on basic circuits.

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

To find out more about how to learn electronics in a new, exciting and absorbing way, just clip the coupon for a free colour brochure and full details of enrolment.

PLUS FREE GIFT!

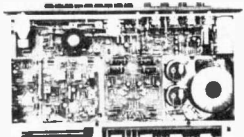

ALL STUDENTS ENROLLING IN OUR COURSES RECEIVE A FREE CIRCUIT BOARD ORIGINATING FROM A COMPUTER AND CONTAINING MANY DIFFERENT COMPONENTS THAT CAN BE USED IN EXPERIMENTS AND PROVIDE AN EXCELLENT EXAMPLE OF CURRENT ELECTRONIC PRACTICE

Brochure without obligation to:
**BRITISH NATIONAL RADIO
 & ELECTRONICS SCHOOL, Dept. EL16**
 P.O. Box 156, Jersey, Channel Islands

NAME _____

ADDRESS _____

(Block caps please)

SMALL MERCIES

ALL in all it has been a pretty grim year, with the pound in the pocket shrinking month by month. And the economists and financial experts predict there's worse to come before things bottom-out and the slow upward haul to more prosperous and cheerful times begins. So there is every reason to be thankful for any small mercies, like the downward trend in semiconductor prices that has taken place during the last twelve months.

Digital i.c.s have shown a spectacular fall, and CMOS devices the most notable of all. Keen rivalry between device manufacturers competing for a stake in the large and growing computer field has stimulated the development of new monolithic technologies, and CMOS is now established as a possible alternative to TTL. The battle is likely to continue with the bipolar protagonists fighting back with more recently developed techniques such as emitter coupled logic and integrated injection logic, to say nothing of charge coupled devices and CDI. All these different families of i.c.s have promising futures for each has some unique advantages to offer which will be important in specific applications.

The lively competition augers well for the future of the electronics industry because the constant aim is the worthy one of more circuit functions per chip for a lower cost with, wherever possible, enhanced operational performance. A commercial philosophy which could well be emulated by other industries, since all too often it seems some sacrifice of quality or quantity is the only way a price reduction can be realised.

It is fortunate that the chief building blocks of electronics are extremely viable in present day terms, with continuing downward tendencies in cost rather than the reverse. Fortunate for *everyone* in the long term—because electronics has a most vital part to play, directly or indirectly, in improving the economic wellbeing of the country and the standard of living of the individual.

The private designer and constructor already enjoys some of these benefits. Active devices are likely to account for the smaller portion of the total material cost in a modern design. Not unexpectedly there is sometimes a temptation to extravagance in the use of i.c. devices, simply because they are modestly priced. At least, this might be considered to be the case by those brought up with a more frugal outlook during the pre-semiconductor era. Yet however cheap and versatile the components, the project designer owes it to himself and to those who may imitate his work to observe sound design principles throughout and to strive for elegance in circuit arrangement and economy in component count, no less than in price. Small is beautiful, it is said. Good housekeeping is laudable in good and bad times alike. That goes without question.

F.E.B.

Editor
F. E. BENNETT

Editorial
D. BARRINGTON *Production Editor*
G. GODBOLD *Technical Editor*
R. W. LAWRENCE, B.Sc.

Art Dept.
J. D. POUNTNEY *Art Editor*
D. J. GOODING
R. J. GOODMAN
K. A. WOODRUFF

Advertisement Manager
D. W. B. TILLEARD
Phone: 01-634 4202

P. J. MEW
Phone: 01-634 4210

C. R. BROWN, *Classified*
Phone: 01-634 4301

Editorial & Advertising Offices:
Fleetway House, Farringdon St.
London EC4A 4AD
Phone: Editorial 01-634 4452
Advertisements 01-634 4202

ICE will begin to form on roads when air temperature is between 36°F and 32°F (2.2°C–0°C) in our damp winter conditions. This device monitors the air temperature by means of a thermistor and gives warning of impending icy road conditions by variable flash duration of a light-emitting diode. The completed unit is so small that the entire assembly may be housed in a small metal canister and fixed through the dash of a car by a single $\frac{1}{8}$ in bush.

CIRCUIT FUNCTION

This circuit depends upon the ratios of currents flowing and is therefore insensitive to fluctuations in the car's battery potential and most interference derived from the vehicle's electrics. Power-line regulation is therefore unnecessary, but a 0.1–1microfarad capacitor across the power input to the unit may be needed in extreme circumstances. (C2 in Fig. 1.)

Section IC1a of the quad op-amp package (MC 3401) forms a comparator looking at the current through the thermistor compared with that flowing in the "CAL" network, and R3 defines the output gradient of the amplifier according to the required response to temperature. For 36°F (2.2°C), the output is approximately 7.2V and at 32°F, 3.6V.

The multivibrator IC1b is similarly designed so that the upper and lower voltages across C1 are of the same order, determined by R4, 5, 6. The oscillator has a period of approximately 1 second.

The third section of the op-amp is used as a comparator looking at the charge on C1 and comparing this to the output of IC1a. When the charge on C1 is lower than the output of IC1a, the output of

IC1c goes positive and current flows through the l.e.d. whose maximum drain is limited by R7 to about 22–25mA.

As IC1b produces a rough sawtooth waveform across C1 the on-time of the l.e.d. varies, as only the peaks lower than IC1a's output will cause IC1c to turn on. Thus we obtain flashes from the l.e.d., starting as very short ones, at about 36°F, and gradually becoming longer as IC1c's trigger-level is shifted by the action of the thermistor through IC1a passing less current as it gets cooler. Finally the l.e.d. will be on continuously at about 32°F as IC1c will never be cut off.

SENSOR PROBE


The sensor probe consists simply of a thermistor of 15 kilohms resistance (at 25°C) mounted in an enclosure to baffle it from moving air as this could cause false indication. The whole assembly should be mounted as close to the ground as is practical, perhaps the best place being below the front apron or scuttle of the vehicle. It is important to keep the probe unit well away from any hot engine or radiator parts.


It is suggested that the thermistor element be mounted in an old cigar tube to act as a baffle, and suspended therein by small annular pieces of thick polyethylene sheet. No filler should be used, as this increases the conductivity to the thermistor and the baffle effect of the tube will be degraded.

No short-circuits should occur when the printed circuit assembly is inserted into the tube/baffle. The thermistor and the printed circuit board must be protected from the ingress of moisture and/or condensation.

ROAD - ICE WARNING INDICATOR

By A.M. OWEN

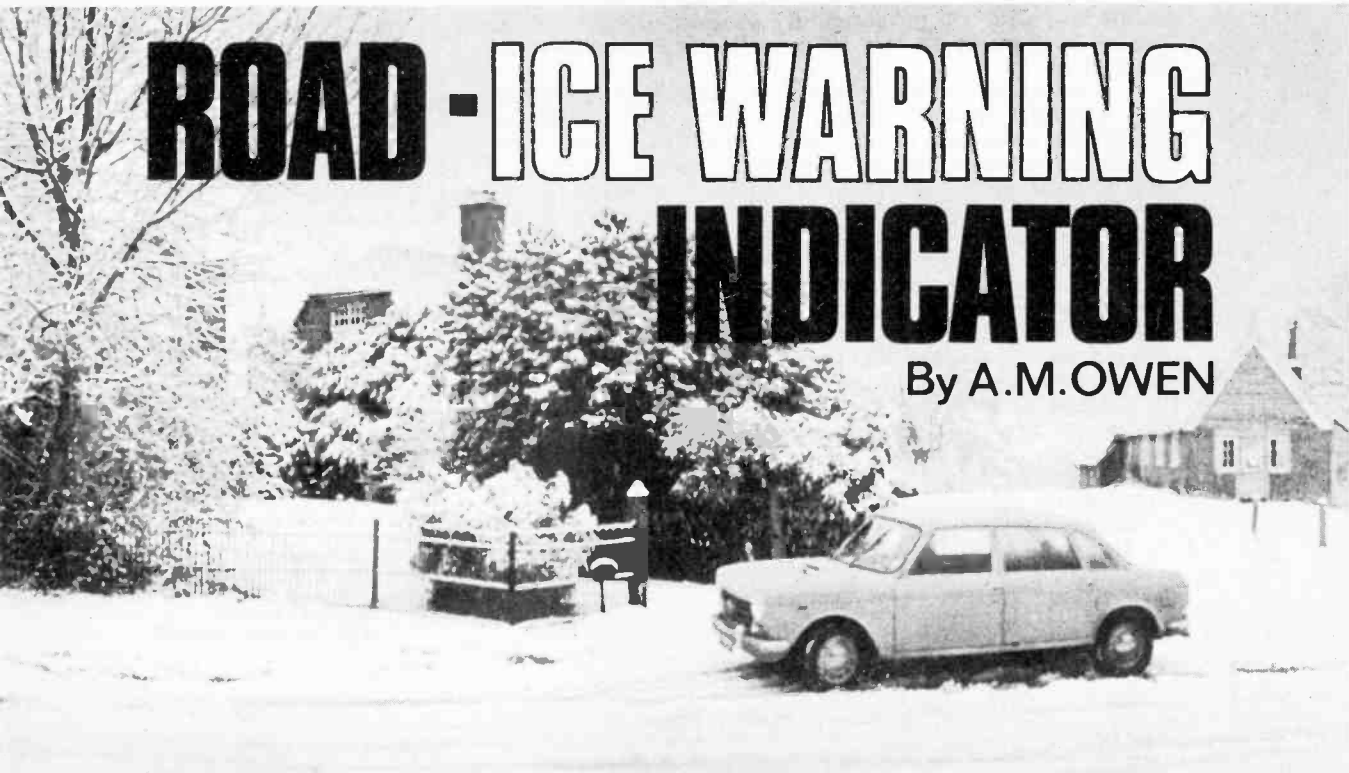

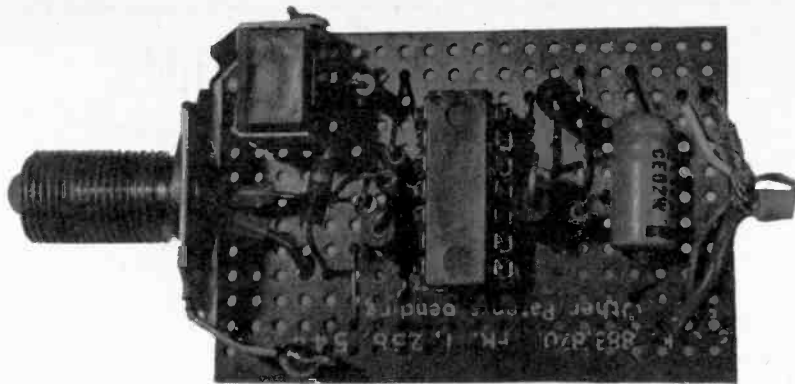

Completed prototype circuit board. Note that the l.e.d. is mounted inside the $\frac{1}{2}$ in dashboard mounting bush

Ensure good isolation between the terminations of the thermistor by removing the copper from the track as shown in Fig. 3.

Coat the whole of the p.c. board with a thin layer of 5-minute epoxy-resin to prevent moisture affecting the resistance of the assembly.

Faster response to temperature might be achieved by filling the bottom of the tube, prior to insertion of the thermistor assembly, with silicone grease, although this has not been tried in practice.

Size of printed circuit board used and shown in the diagram is only arbitrary and will of course vary depending on the size of mounting tube available.

CONSTRUCTION

The unit has been designed to be as small as possible and is non-critical in its layout. However, in order to ensure that the unit works properly after

Typical housings for the probe and circuit board



Thermistor mounted on the probe board and covered with an epoxy-resin

construction and remains a reliable device, it is well to be sure that no dry-joints or track-bridging or shorts between components have occurred during the course of construction. The upper leads of R1, 6, 9 should be sleeved.

CALIBRATION

This is very simply accomplished by wrapping the thermistor, before mounting in the baffle-tube, in a polyethylene bag, to keep away the ice and water mixture in which it is to be immersed. The assembly is then plunged into the well stirred saturated solution of ice and water.

After about a minute, and with the unit fully wired and connected to a 12V source, adjust VR1 to the point where the l.e.d. just comes on steady. A very slight "wink" may be noticed due to a slight imbalance between the outputs of IC1a, IC1b because of resistor tolerances.

If it is not possible to obtain a steady illumination of the l.e.d. when the thermistor is at 32°F, it may be necessary to add a 10M Ω (R10) at the -ve input (Pin 3) and connect the other end to chassis.

OTHER APPLICATIONS

If the unit is provided with a suitable 12V battery supply there is no reason why this instrument may not be used as a portable monitor to check for the possibility of ice forming on outdoor swimming pools or fish ponds so that precautionary measures may be taken.

The unit may also be made to operate on other temperature ranges by changing the values of R1, 2, 3.

In view of the low current drain it was not considered necessary to incorporate an on/off switch for the in-car device. ★

IC50

By B.W. TERRELL & C.F. TERRELL



GUITAR AMPLIFIER

LAST month we discussed the power supplies, pre-amplifier and power amplifier circuits of the guitar amplifier; this month we conclude with the wiring, construction and testing procedures.


PREAMPLIFIER BOARD


A full-size drawing of the preamplifier printed circuit board is shown in Fig. 8. The layout of the components on the topside is shown in Fig. 5.

Ensure that the fixing holes at each corner are drilled before commencing assembly, and begin by inserting and soldering in the p.c.b. pins.

Although the integrated circuits used in the pre-amplifier are tough devices, it is strongly recommended that integrated circuit sockets be used and that the latter be soldered in position with the i.c. removed, thus avoiding possible damage from the heat of the soldering iron. In the event of the i.c.s needing replacement, it will then be an easy matter not requiring the removal of the board and not involving desoldering, which can be tricky. The layout of the board has been designed so that all the i.c.s "face" the same way. Do likewise with the i.c. sockets to avoid confusion at a later stage.

Fig. 5. Component layout for the pre-amplifier board. A full size p.c.b. master is given in Fig. 8

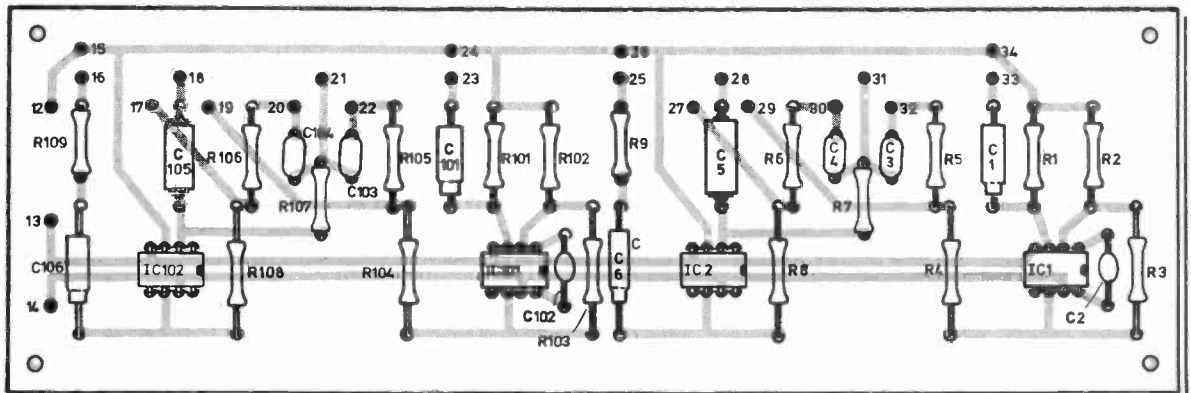

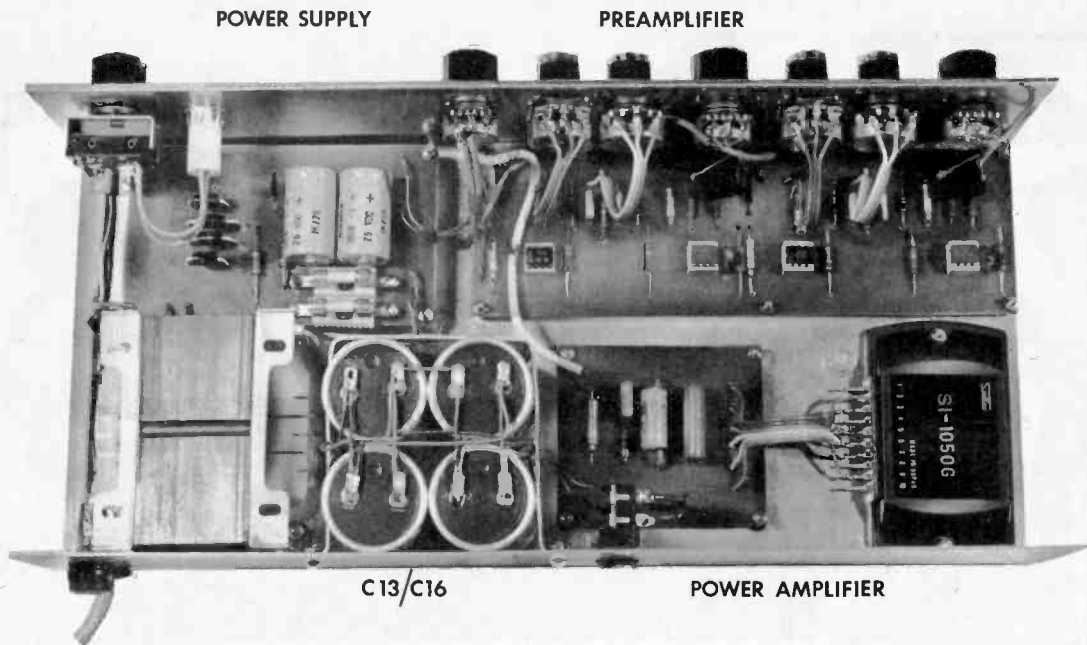

The finished guitar amplifier showing positioning of all the boards

Special note should be taken to observe correct polarity when soldering in the electrolytic capacitors. Do not attach any flying leads at this stage.

POWER AMPLIFIER BOARD

The printed circuit board to accommodate the components associated with IC3 is shown full-size in Fig. 8. The layout of the components on the top-side of the board is shown in Fig. 6. Before embarking on component assembly, ensure that the four fixing holes have been drilled and that all the printed circuit pins have been inserted and soldered in place. Construction is straightforward, but pay attention to capacitor polarities. Do not attach any flying leads yet.

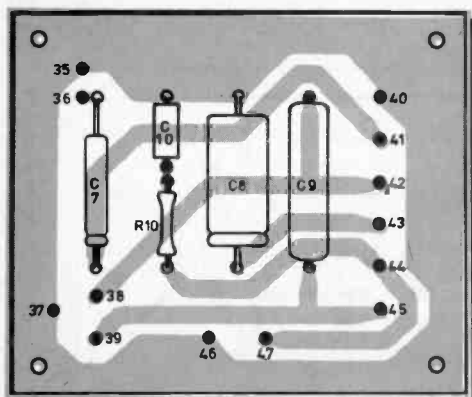


Fig. 6. Component layout for the power amplifier board

POWER SUPPLY BOARD

The smaller components of the power supply section are mounted on a printed circuit board; the layout of the components on this board can be seen in Fig. 7. The full-size drawing of the copper clad side are shown in Fig. 8.

When positioning and soldering these components in place, special attention should be paid to the diodes and capacitor polarities, as a mistake in this section could have disastrous (and expensive) effects. Do not solder in any lead-out wires at this stage.

CHASSIS DETAILS

The prototype chassis was made from two L-shaped pieces of 1.5mm thick aluminium sheet and

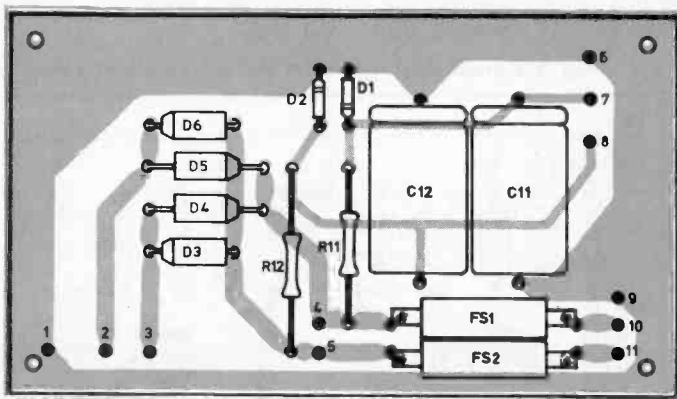


Fig. 7. Component layout for the power supply board. The p.c.b. master is shown opposite full size


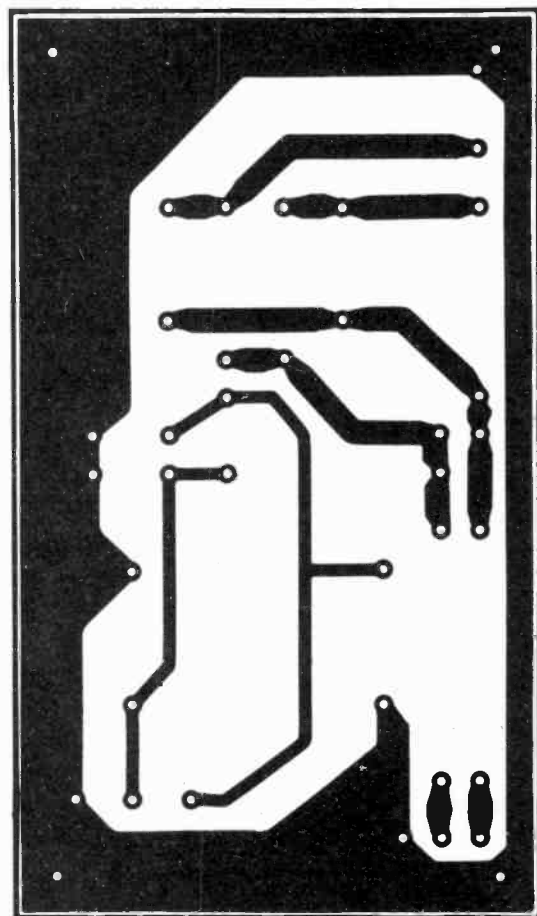
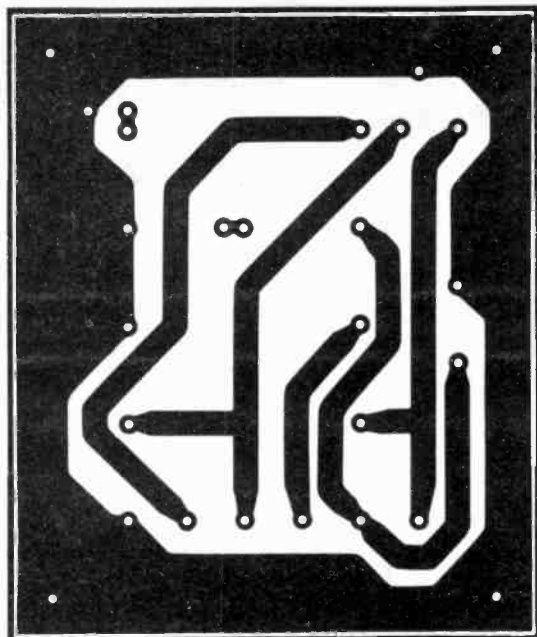


Fig. 8. Full size printed circuit masters for the IC50 Guitar Amplifier

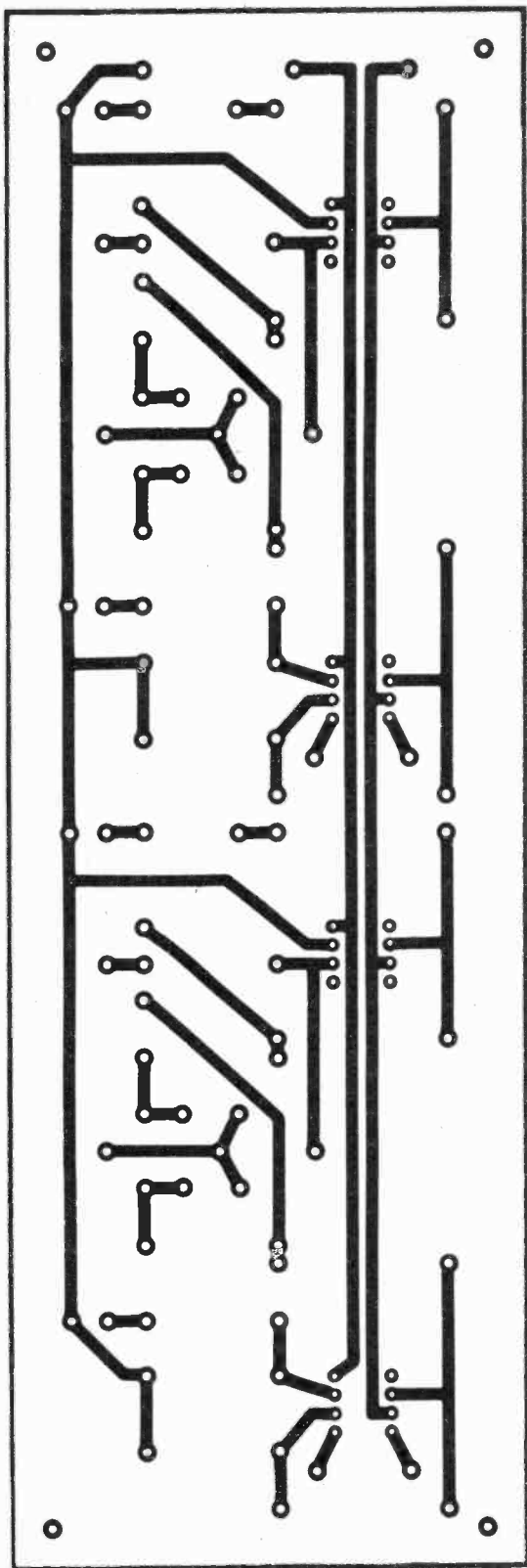

CHASSIS DRILLING

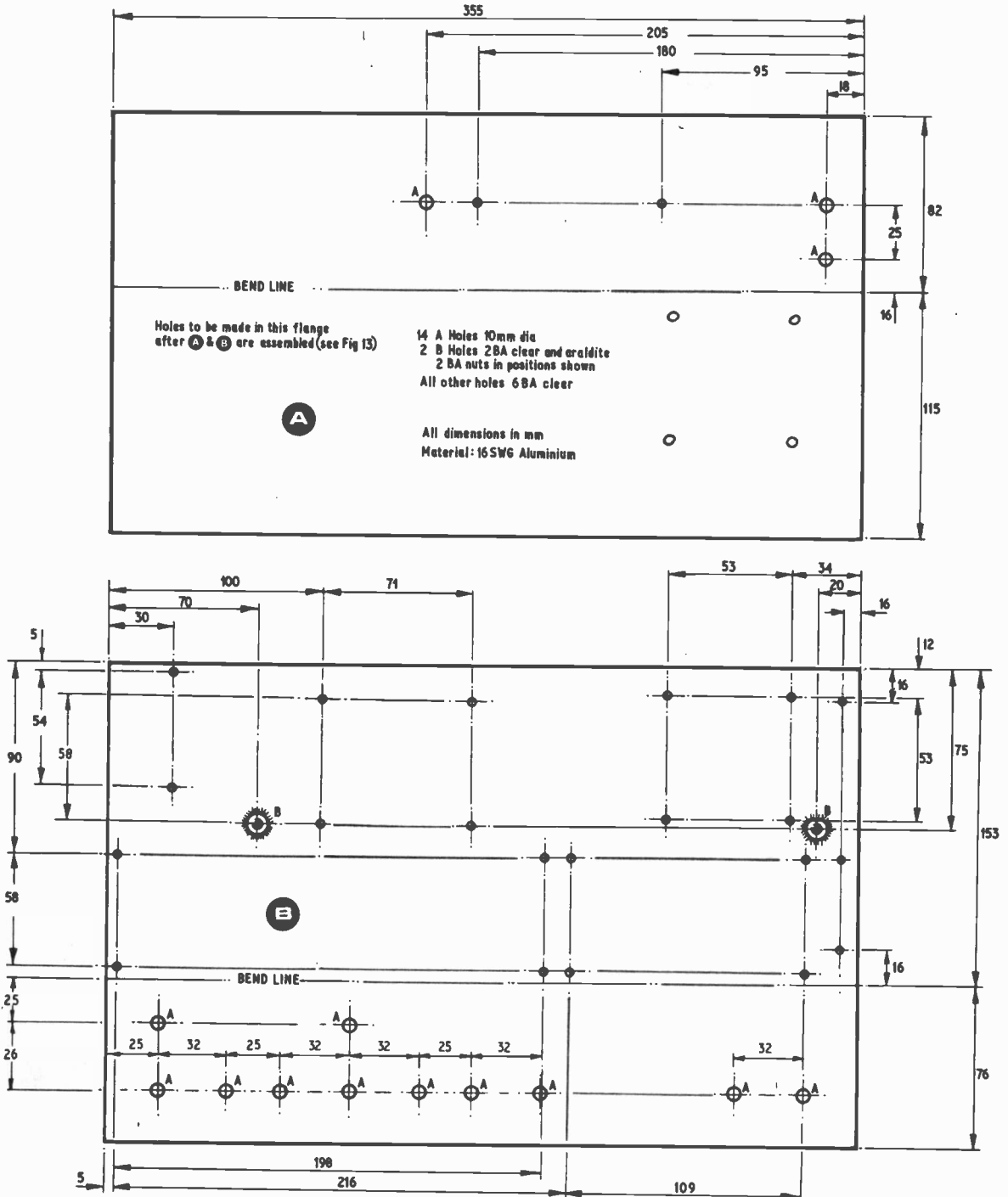


Fig. 9. Complete drilling details for the amplifier chassis. The front panel drilling can be marked from panel B

bolted together, using the component and component board fixing bolts to form a U-shaped chassis. Complete drilling and marking out details are given in Fig. 9. Both sheets should be marked out and drilled according to the details, and all the holes drilled before bending. Drilling details for the base of sheet A are incomplete (intentional), only the transformer fixing holes are shown. It is recommended that sheet A base section and sheet B base section be drilled (as shown) and then bolted together, and then sheet B used as a template. This method ensures that the holes in each sheet will be correctly aligned, whereas separate drilling may cause problems.

Once all the holes are drilled the right-angled bends should be made as indicated. A bracket is necessary for holding the power supply smoothing capacitors. Details are given in Fig. 11.

The front panel drilling details are taken from Fig. 9. It has the same dimensions as the chassis front and is commercially available guillotined to this size. The holes on the front panel were punched out using Q-max cutters which give a clean finish. The choice of decoration and finish on the front panel is left to the individual requirements of the constructor. In the prototype coloured adhesive film was used, the lettering and borders done with Letraset, and was then sprayed with Letragloss for protection.

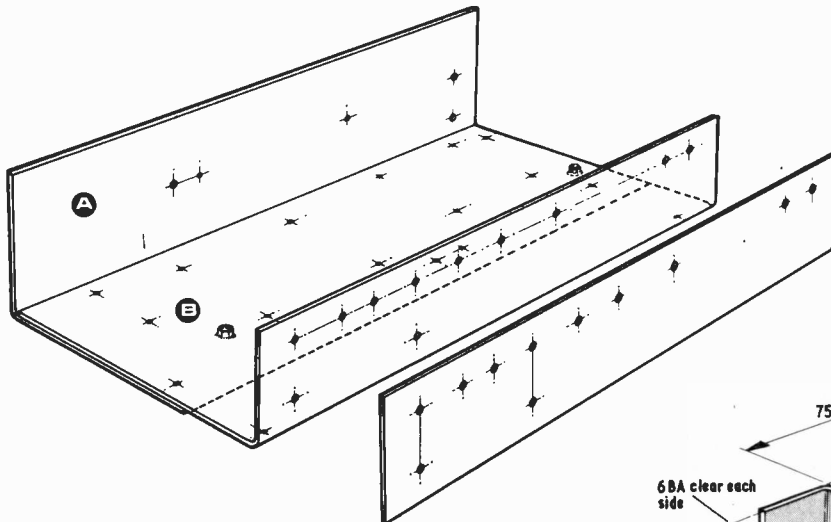


Fig. 10. Showing how the various chassis parts are positioned to form the final chassis

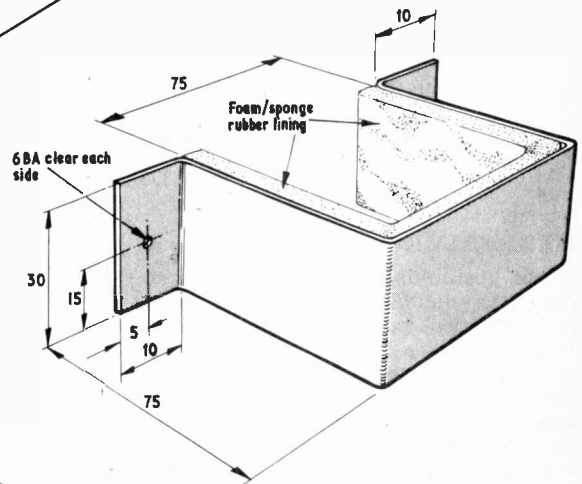


Fig. 11. Drilling and bending details for the capacitor clamp

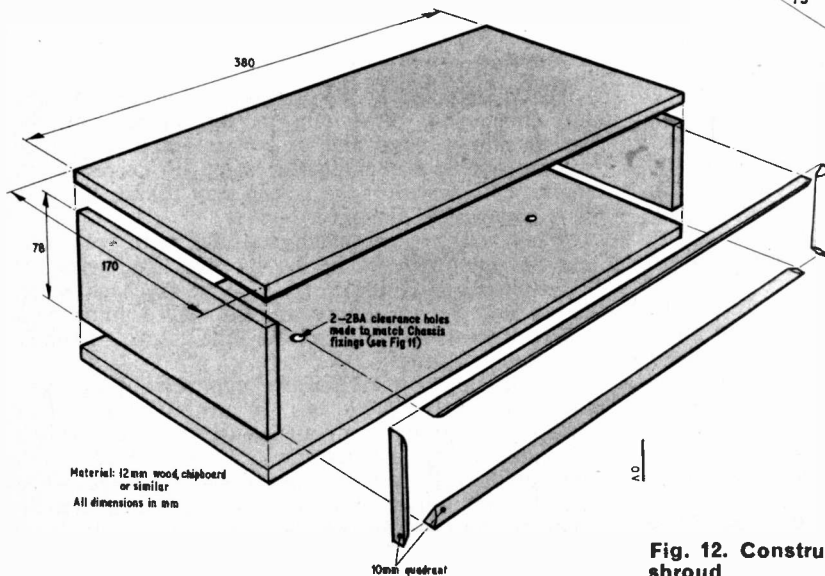


Fig. 12. Constructional details for the wooden case shroud

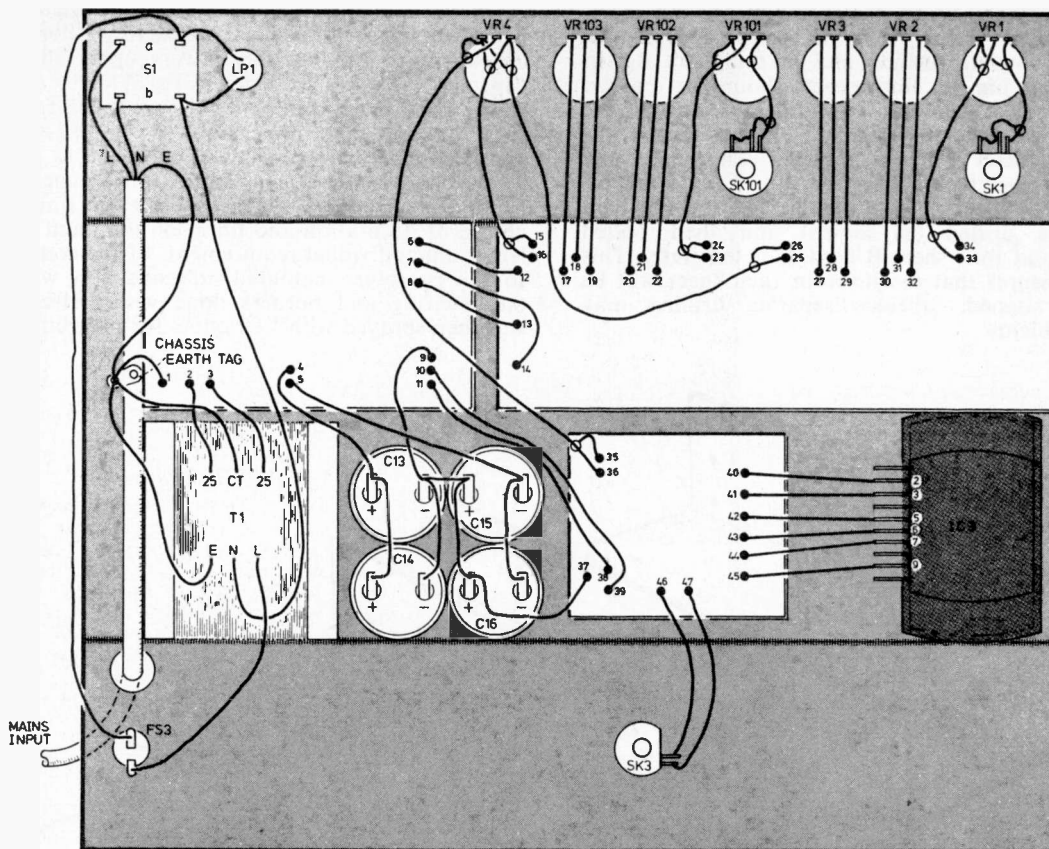


Fig. 13. Interwiring details for the guitar amplifier

ASSEMBLY

The positioning of components, circuit boards and complete interwiring details are shown in Fig. 13. Assembly will be found easiest if carried out in the following order.

Begin by securing the transformer in place on the two chassis sections using 4BA nuts, bolts and shake-proof washers, thereby forming a single U-shaped chassis. Next fix all the completed component boards to the chassis using 6BA nuts, bolts, shake-proof washers and 5mm long spacers such that the undersides of the boards stand clear of the chassis base. The use of a lock-nut is recommended.

The control potentiometers, jack sockets, neon and rotary on/off switch should next be secured to the front panel through the chassis front. All the potentiometers should have their connecting tags uppermost. Now fix IC3 in position using some silicon grease on the area of contact between IC3 and chassis to ensure good thermal contact. Screw the output jack socket SK3 in position and fix the panel mounting fuse to the rear panel. Insert a rubber grommet in the mains feedthrough hole immediately below the fuseholder. Bolt the chassis earth tag in place and then the cable clips to hold the mains lead.

It is now necessary to interconnect the four smoothing capacitors C13 to C16. To hold these together during wiring up, a wrapping of Sellotape will be found useful. Take special care that capacitor polarities are obeyed. When they are satisfac-

torily wired up, place them in position in the chassis and bolt on the capacitor bracket. Now wire up according to Fig. 13. It will be found useful to tick off the connections as you make them and also to use different colours of connecting wire. Try and use brown wire for positive supply rails, blue for the negative rails and green for all earth connections. This way wire tracing will be more simple.

TESTING

When completed, the wiring should be checked out thoroughly, especially in the vicinity of the power supply board and the power output board. In particular, check that SK3 is wired up correctly. If the latter is wired in the wrong way round, IC3 can be permanently damaged.

When you are completely satisfied with your wiring up, the fuses should be inserted, 2A types for the supply board and a 1A type in the back panel fuseholder. Fit the knobs and turn all volume controls anti-clockwise and set the tone controls to their midway positions.

First of all, with no speaker connected, plug in to the mains and switch on. If any fuses blow, or smoke or burning components are observed, switch off immediately and investigate. If all appears well the supply rail voltages should be measured. The preamplifier rails should be ± 15 volts and the main amplifier rails approximately ± 35 volts.

continued on page 47

JODRELL BANK

A grant of nearly £2 million has been made by the Science Research Council, for the purpose of setting up a multi-unit interferometer.

Three of the telescopes that will make up the new group are already in existence, the Mark 1 and the Mark 2 at Jodrell Bank together with the 80ft dish at Malvern. The addition of the fourth unit will considerably assist the work controlled from Jodrell Bank.

The extension of facilities will enable a much greater resolution to be obtained and Jodrell bank are hoping to achieve an accuracy of 0.03 seconds of arc. The manner of the disposition of the units will reduce the data to some extent, but it is considered that the increased resolution will more than compensate.

In order to make the best use of the grant it has been decided that the fourth unit shall be an "off the line" dish from America. A regular production line dish 25m in diameter and fitted on an altazimuth mounting is available from E Systems Inc of Dallas, Texas. It will be installed at Knockin, near Oswestry, and be linked by landline and a reserve back-up microwave system.

The work involved in the future observations will be a continuing story and will include the study of the detailed structure of novae, pulsars, quasars and the areas where star formation is active.

BLACK HOLES

Until recently the writer and a small number of people were of the opinion, "that the rotating black hole was possibly the gateway to an alternative space time". This seems not to be true after all and according to an advertisement the Bacon Foundation is offering a prize of £300 for the solution to the problem of a space ship to make the journey.

The problem as stated is, according to current theory, that rotating black holes are the actual gateways to an alternative spacetime. How, therefore, could a space vehicle pass through a rotating black hole into another region of spacetime, without being crushed by the gravitational field of a singularity?

This is so near to the ideas found in space fiction that perhaps here begins the new thinking, making further progress in the inevitable revolution in physics. The outcome of this challenge will be eagerly awaited.



WHITE HOLES

While white holes are not often in the news their claims are now being seriously advanced. There has been activity in this field for a number of years now and it is not surprising that the same sort of people as those concerned with black holes are involved.

However, in the past white holes have not been taken too seriously. This attitude is not really justified and some new light is thrown on this subject by Professors J. V. Narlikar and K. M. V. Apparao.

The name of Narlikar is closely associated with the continuous creation theory advocated by Fred Hoyle. Narlikar was in fact a protégé of Fred Hoyle and many papers were issued under their joint names.

At the Tata Institute and among cosmologists, Narlikar is known for his extreme views. The creation of matter in the universe is an idea not much removed from the possibility of singularities which are projecting their energy out into the universe and so interacting with the matter around.

To this end Narlikar and Apparao have been looking more closely at the kind of spectrum which should appear from a white hole. The term white hole is not really apt but since it implies the opposite of black it will no doubt continue to be used. They are suggesting that the Seyfert galaxies could be a white hole effect. They are able to offer an explanation for all the facts observed including the particle production.

There is another possibility and that is that if a black hole is the entrance to another region of space time, could not the white hole be the emergence of the other side of a black hole?

The idea of a white hole of necessity involves blue shift. The name of Kapp comes to mind in connection with blue shift. Several years ago when his book appeared it caused a stir, for the claim made was that matter was being concentrated in certain areas, and that it was moving towards the observer, thus the blue shift.

CO-OPERATION

For the first time a United States series of experiments will be flown in a Soviet Spacecraft. The scheme was discussed during the joint working group meetings on space biology and space medicine.

Four NASA developed life science experiments will be taken on board the spacecraft in special containers manufactured in the Soviet Union. The maximum weight of the containers including the experiments will be less than 2.5 kilogrammes each.

A unique feature of the spacecraft is the onboard centrifuge. The U.S. experiments will be divided with some on the centrifuge platform and some on the stationary platform.

The four experiments are concerned with the investigation of sensitive plant systems. The effect of weightlessness on embryonic plant systems. A heavy particle radiation experiment, small lexan plastic nuclear track detectors will be inside the containers on the centrifuge and in the stationary biological containers. And finally, an experiment with minnows to discover the effect of weightlessness on the vestibular system of developing embryos.

WIND ON THE MOON

When making an analysis of the lunar soil samples delivered to earth by *Luna 16* and *Luna 20*. Soviet scientists found that the *Luna 20* material contained four times as much mercury as *Luna 16*.

The unevenness is thought to come about by the emanation of mercury vapour during the Lunar day, at a temperature of 150°C, toward the colder areas by the lunar wind. As it cools it would be deposited on the rocks in the cold areas.



BOOK REVIEWS

AUDIO ON WHEELS

By Vivian Capel
Published by Newnes-Butterworths
199 pages, 142mm x 222mm. Price £6.00 (Hardback)

WITH the seemingly ever increasing interest in "in-car entertainment" it is surprising that, until now, very little information on installing audio equipment in the car has been published. Of course, this does not include manufacturers' literature, which invariably only give part of the story anyway.

This book is divided into two parts, Basic Principles and Practical Applications, and sets out, fairly successfully in my opinion, to cater for the radio engineer, motor mechanic and the amateur. It covers all aspects of in-car entertainment from basic principles of radio and tape recording to the installation of complete systems.

The different types of radio, cassette and cartridge equipment, including stereo and quad systems are discussed and assessed. The chapters on power supplies, aerials, loudspeakers and interference suppression on a.m. and f.m. is covered in some depth and are probably the most useful sections in the book.

The chapter on setting-up a workshop is interesting and the final chapter on "Repair and Maintenance" contains some very good pointers on fault diagnosis and basic test procedures, together with the necessary test equipment needed.

The only criticism I can find (apart from price) is that it's a pity that the interference suppression section could not have been expanded to cater for solid state or CDI (Capacitor Discharge Ignition) systems. This could easily have been accomplished by deleting the references to the ancient valve vibrator power supply circuits.

D.G.B.

BASIC DIGITAL ELECTRONICS

By Ray Ryan
Published by Tab Books (No. 728)
210 pages, 130mm x 210mm. Price \$7.97 Hardback, \$4.95 Paperback

ADVANCED APPLICATIONS FOR POCKET CALCULATORS

By Jack Gilbert
Published by Tab Books (No. 824)
304 pages, 130mm x 120mm. Price \$8.95 Hardback, \$5.95 Paperback

ALTHOUGH these two books are of American origin, they offer a good basic grounding in their relevant subjects. For the student or person who wants to realise the full potential of his calculator this book should prove a reasonable acquisition.

The main emphasis in the digital electronics book is on presenting the various types of digital circuits and describing the features pertinent to these circuits. Today, discrete circuits are seldom used and almost all logic is performed with integrated circuits. For this reason, there is a slight bias throughout towards the assumption that a given logic function is just that—a function.

The logic symbols used throughout are not to British Standards, but several chapters explain the basics of

logic and introduce the logic diagram and truth table. Because a system of *one's* and *zero's* probably seems strange to the uninitiated, the early chapters describe the binary number system and the different codes digital systems use in some depth. There is even a chapter on CMOS logic.

The pocket calculator book covers 4-function, scientific, programmable, electronic slide rules, metric converters and business units.

This book shows how the ability of the calculator to multiply and divide can be used to calculate square roots, cube roots, powers of numbers, logarithms and all the trigonometric functions to five or seven places. As an example the author shows how to perform the scientific computations above using an elementary 4-function unit.

The book also shows how to solve such problems as quadratic equations, right angles, compound interest mortgage problems and even determine satellite orbits.

D.G.B.

GUNN-EFFECT ELECTRONICS

By B. G. Bosch and R. W. H. Engelmann
Published by Pitman Publishing Ltd.
434 pages, 240mm x 160mm. Price £16.00

WITH microwave technology very much on the increase, this book looks at one of the effects often used in microwave devices, that of the "transferred electron" or better known "Gunn" effect. The book is clearly aimed at those directly concerned with microwave device development or post-graduate students, and gives an authoritative account of the whole device technology.

Also the book serves to collate the great deal of work which has been done on the subject over the last few years not only through its own text, but also through the vast number of references that appear after each chapter.

The book commences by looking into the Gunn Effect in the strict sense (space-charge dipole domains) and then moves on to dipole-domain free operation. Mode classification, frequency limitations, efficiency, power and noise performance are then covered, followed by a detailed look at the actual manufacturing processes involved in producing Gunn devices.

The final few chapters deal with some application considerations and the book finishes by detailing the use of Gunn technology in logic circuits.

R.W.L.

PE SUBSCRIPTION SERVICE

Copies of Practical Electronics can no longer be supplied on direct subscription. The publishers have found it necessary to close the subscription service chiefly on account of escalating costs on packing and postage.

No new subscriptions will be accepted. Existing annual subscriptions will continue to be serviced until expiry.

This action is very much regretted, but it should not mean any reader being deprived of his regular copy of the magazine.

Present subscribers should make arrangements with their local newsagent or bookseller for Practical Electronics to be delivered to their home address or to be reserved for collection each month, immediately their current subscription has expired.

Any readers outside the United Kingdom who have difficulty in locating a supplier should write direct to the editor who will be pleased to advise them of the local agent for IPC Magazines.

MAPLIN ELECTRONIC SUPPLIES

P.O. BOX 3, RAYLEIGH, ESSEX

Tel: Southend-on-Sea (0702) 44101

ALL PRICES INCLUDE VAT & POSTAGE & PACKING

(U.K. only)

(20p handling charge if order under £2)

PRICES: Some prices shown on this page may change after December 31, 1975. For details send a.s.e. for our latest newsletter (see back cover). Overseas customers deduct VAT; details in our newsletter.

Visit our shop 284 London Road Westcliff-on-Sea Essex

MAINS TRANSFORMERS

Conform to BS415. Split bobbin construction.

0-8V, 500mA + 0-8V, 500mA	MIN TR 8V	£1.35
0-8V, 500mA + 0-8V, 500mA	MIN TR 8V	£1.85
0-12V, 250mA + 0-12V, 250mA	MIN TR 12V	£1.55
0-20V, 150mA + 0-20V, 150mA	MIN TR 20V	£1.55
0-36V, 83mA + 0-36V, 83mA	MIN TR 36V	£1.87
0-12V, 1A + 0-12V, 1A	TR 12V 1A	£1.99
0-8-9V, 1A + 0-8-9V, 1A	TR 9V 1A	£2.00
0-28V, 1A + 0-28V, 1A	TR 28V 1A	£3.87
0-15-20V, 1A + 0-15-20V, 1A	Double sided, PIN 2144	
	TR 20V 1A	£3.80

For quantities over 25 special discounts are available



Uncoppered boards
147 x 114 58 x 42 (0.11") SRBP 0.1in. 48/sp
127 x 95 33 x 24 (0.15") SRBP 0.15in 34p

Terminal Pins (Verobooks of 36 pins)
For 0.11" Verobooks Single sided PIN 2145 13p
PIN 2144 13p
For 0.15" Verobooks and both uncoppered boards Single sided PIN 2140 20vsp
Double sided PIN 2140 20vsp

Verobooks of 36 pins
Terminal Pins (Verobooks of 36 pins)
For 0.11" Verobooks Single sided PIN 2145 13p
PIN 2144 13p
For 0.15" Verobooks and both uncoppered boards Single sided PIN 2140 20vsp
Double sided PIN 2140 20vsp

Verobooks of 36 pins
Terminal Pins (Verobooks of 36 pins)
For 0.11" Verobooks Single sided PIN 2145 13p
PIN 2144 13p
For 0.15" Verobooks and both uncoppered boards Single sided PIN 2140 20vsp
Double sided PIN 2140 20vsp

P.E. JOANNA

P.C.B.'s 14-board set £17.50
See our latest newsletter (send s.a.e.) for details of our special offer on the bulk components, and all the other parts you need

L.E.D.'s

High-brightness with panel clip
0.2in Red 16p
Green 43p
Yellow 43p

DIN	Plug	Chassis Socket
2-pin L/S	10p	9p
3-pin	11p	10p
4-pin	15p	10p
5-pin (180°)	15p	10p
5-pin B (240°)	15p	10p
6-pin	15p	11p
7-pin	15p	10p

MAINS
SA Chassis Mounting 3-pin Plug SA2190 37vsp
SA Line 3-pin Socket SA1862 (surfs SA2190) 44p
SA Chassis Socket and Line Plug (sold only together) P437
19A Chassis Plug and Line Socket (sold only together) P360
19A Chassis Socket and Line Plug (sold only together) P438
2-pin Flat Pin Line Plug (USA Mains Plug)
2-pin Flat Pin Chassis Socket (Flat Pin M.S.)
2-pin Flat Pin Line Socket (Flat Pin Conn)

ELECTROLYTIC CAPACITORS

Cap. Voltage Case	Cap. Voltage Case	Cap. Voltage Case
(µF) (V) Size	(µF) (V) Size	(µF) (V) Size
1.6 63 3	47 63 6	330 16 00
1.5 63 3	68 16 4	470 6.3 6
2.2 63 3	68 63 00	470 10 01
4.7 63 3	100 4 4	470 40 02
6.8 63 3	100 25 5	980 6.3 00
10 63 3	100 63 01	980 16 01
15 16 2	150 6.3 4	680 25 02
15 40 3	150 16 4	680 40 03
15 63 4	100 63 01	1000 4 00
22 10 2	150 16 00	1000 16 02
22 25 3	150 63 01	1000 25 01
22 63 3	220 4 4	1500 6.3 01
33 6.3 2	220 10 5	1500 10 02
33 16 3	220 16 5	1500 16 03
33 40 4	220 25 00	2200 6.3 02
47 4 2	220 40 01	2200 10 03
47 10 3	220 63 00	3300 6.3 03
47 25 4	330 4 4	4700 4 03
47 40 5	330 10 6	

Case Size	Length	Diameter	Price
2	12.5	4.8	71p
3	12.5	6.1	71p
4	20	6.7	71p
5	20	8.3	71p
6	10	8.3	10p
00	33	10.4	221p
01	33	12.9	25p
02	33	15.4	49p
03	33	18.4	44p

VEROBOARD

Size (mm)	No. of holes (matrix)	Order code
127 x 63	50 x 24 (0.11")	VERO 10345
95 x 63	37 x 24 (0.11")	VERO 10346
127 x 95	50 x 36 (0.11")	VERO 10347
95 x 95	37 x 36 (0.11")	VERO 10348
95 x 63	25 x 16 (0.15")	VERO 43P16
127 x 95	33 x 24 (0.15")	VERO 45P16

48/sp
34p
42p
31p
56p

JACKS
2.5mm Plastic Plug 11p
2.5mm Screened Plug 11p
2.5mm Screened Line Socket 11p
2.5mm Plastic Plug 11p
3.5mm Screened Plug 11p
3.5mm Open-type Chassis Socket 11p
3.5mm Plastic Line Socket 11p
3.5mm Screened Line Socket 11p

5td Vain. Plastic Mono Plug 14p
5td Vain. Screened Mono Plug 14p
5td Vain. Plastic Stereo Plug 14p
5td Vain. Screened Stereo Plug 14p
5td Vain. Open-type Mono Chassis Socket 19vsp
5td Vain. Moulded Mono Chassis Socket with 2 break contacts 15p
5td Vain. Moulded Stereo Chassis Socket with 3 break contacts 19vsp
5td Vain. Plastic Mono Line Socket 21vsp
5td Vain. Screened Mono Line Socket 21vsp
5td Vain. Plastic Stereo Line Socket 24p
5td Vain. Screened Stereo Line Socket 24p

Line Socket 12vsp
9p
14p
10p
17vsp
10p
17vsp
21p
17vsp

Line Socket 12vsp
9p
14p
10p
17vsp
10p
17vsp
21p
17vsp

Line Socket 12vsp
9p
14p
10p
17vsp
10p
17vsp
21p
17vsp

Line Socket 12vsp
9p
14p
10p
17vsp
10p
17vsp
21p
17vsp

Fane POP 50

8x50W 12 Inch
Bass Speaker
Frequency Response
50Hz-8kHz
Flux Density 13,000 Gauss
£12.45

Please note: no discount vouchers given on this item

8x50W 12 Inch
Bass Speaker
Frequency Response
50Hz-8kHz
Flux Density 13,000 Gauss
£12.45

Please note: no discount vouchers given on this item

8x50W 12 Inch
Bass Speaker
Frequency Response
50Hz-8kHz
Flux Density 13,000 Gauss
£12.45

Please note: no discount vouchers given on this item

8x50W 12 Inch
Bass Speaker
Frequency Response
50Hz-8kHz
Flux Density 13,000 Gauss
£12.45

Please note: no discount vouchers given on this item

8x50W 12 Inch
Bass Speaker
Frequency Response
50Hz-8kHz
Flux Density 13,000 Gauss
£12.45

QUALITY COMPONENTS - FAST!

PLUGS and SOCKETS

CO-AX Plug Aluminium Plastic barrel 14p
Co-ax Socket Panel fixing Flush fixing 11p
2.5mm Open-type Chassis Socket 11p
2.5mm Screened Line Socket 11p
2.5mm Plastic Plug 11p
3.5mm Screened Plug 11p
3.5mm Open-type Chassis Socket 11p
3.5mm Plastic Line Socket 11p
3.5mm Screened Line Socket 11p

Slide sub-min DPDT 13p
Slide std DPDT 14p
Push to make non-locking SPST 15p
Push to break non-locking SPST 15p
Microswitch SA 250V AC 250V (Type A) SPDT 14p
Push-on, Push-off Locking DPST 250V 4A 39p
Rocker DPST 250V 10A 45p
Toggle Sub-miniature 2A 250V (Type E) DPDT 50p
Toggle DPDT 250V 1.5A with ON/OFF Plate 21p

Toggle Sub-miniature 2A 250V (Type E) DPDT 50p
Toggle DPDT 250V 1.5A with ON/OFF Plate 21p

Toggle Sub-miniature 2A 250V (Type E) DPDT 50p
Toggle DPDT 250V 1.5A with ON/OFF Plate 21p

Toggle Sub-miniature 2A 250V (Type E) DPDT 50p
Toggle DPDT 250V 1.5A with ON/OFF Plate 21p

Toggle Sub-miniature 2A 250V (Type E) DPDT 50p
Toggle DPDT 250V 1.5A with ON/OFF Plate 21p

Toggle Sub-miniature 2A 250V (Type E) DPDT 50p
Toggle DPDT 250V 1.5A with ON/OFF Plate 21p

Toggle Sub-miniature 2A 250V (Type E) DPDT 50p
Toggle DPDT 250V 1.5A with ON/OFF Plate 21p

Toggle Sub-miniature 2A 250V (Type E) DPDT 50p
Toggle DPDT 250V 1.5A with ON/OFF Plate 21p

Toggle Sub-miniature 2A 250V (Type E) DPDT 50p
Toggle DPDT 250V 1.5A with ON/OFF Plate 21p

Toggle Sub-miniature 2A 250V (Type E) DPDT 50p
Toggle DPDT 250V 1.5A with ON/OFF Plate 21p

Toggle Sub-miniature 2A 250V (Type E) DPDT 50p
Toggle DPDT 250V 1.5A with ON/OFF Plate 21p

Toggle Sub-miniature 2A 250V (Type E) DPDT 50p
Toggle DPDT 250V 1.5A with ON/OFF Plate 21p

Toggle Sub-miniature 2A 250V (Type E) DPDT 50p
Toggle DPDT 250V 1.5A with ON/OFF Plate 21p

Toggle Sub-miniature 2A 250V (Type E) DPDT 50p
Toggle DPDT 250V 1.5A with ON/OFF Plate 21p

Toggle Sub-miniature 2A 250V (Type E) DPDT 50p
Toggle DPDT 250V 1.5A with ON/OFF Plate 21p

Toggle Sub-miniature 2A 250V (Type E) DPDT 50p
Toggle DPDT 250V 1.5A with ON/OFF Plate 21p

Toggle Sub-miniature 2A 250V (Type E) DPDT 50p
Toggle DPDT 250V 1.5A with ON/OFF Plate 21p

Toggle Sub-miniature 2A 250V (Type E) DPDT 50p
Toggle DPDT 250V 1.5A with ON/OFF Plate 21p

Toggle Sub-miniature 2A 250V (Type E) DPDT 50p
Toggle DPDT 250V 1.5A with ON/OFF Plate 21p

Toggle Sub-miniature 2A 250V (Type E) DPDT 50p
Toggle DPDT 250V 1.5A with ON/OFF Plate 21p

Toggle Sub-miniature 2A 250V (Type E) DPDT 50p
Toggle DPDT 250V 1.5A with ON/OFF Plate 21p

Toggle Sub-miniature 2A 250V (Type E) DPDT 50p
Toggle DPDT 250V 1.5A with ON/OFF Plate 21p

ORGAN COMPONENTS

Keyboards Morell — as used by the professionals.
4-note C to C £20.40
61-note C to C £28.00
Sweet pedal with 10k log pot £20.00
Pedalboard 13-note C to C £28.00
— with changeover contacts fitted £28.00
Spring Line Unit (Short) £4.10
Spring Line Unit (Long) £10.30
Reverberation Driver Module £6.87

S.A.E. please for full details: Leaflet M653A
Gold-clad phosphor bronze wire 18p
Palladium earth bar per octave length 18p
Contact Blocks changeover single pole (GJ) 25p
two pole make (GB) 25p
three pole make (GC) 35p
four pole make (GE) 45p
five pole make (GH) 87p
Stop Tabs unengraved (black, grey, red or white) with DPDT switch (rocker type) 74p

S.A.E. please for full details: Leaflet M653A
Gold-clad phosphor bronze wire 18p
Palladium earth bar per octave length 18p
Contact Blocks changeover single pole (GJ) 25p
two pole make (GB) 25p
three pole make (GC) 35p
four pole make (GE) 45p
five pole make (GH) 87p
Stop Tabs unengraved (black, grey, red or white) with DPDT switch (rocker type) 74p

S.A.E. please for full details: Leaflet M653A
Gold-clad phosphor bronze wire 18p
Palladium earth bar per octave length 18p
Contact Blocks changeover single pole (GJ) 25p
two pole make (GB) 25p
three pole make (GC) 35p
four pole make (GE) 45p
five pole make (GH) 87p
Stop Tabs unengraved (black, grey, red or white) with DPDT switch (rocker type) 74p

S.A.E. please for full details: Leaflet M653A
Gold-clad phosphor bronze wire 18p
Palladium earth bar per octave length 18p
Contact Blocks changeover single pole (GJ) 25p
two pole make (GB) 25p
three pole make (GC) 35p
four pole make (GE) 45p
five pole make (GH) 87p
Stop Tabs unengraved (black, grey, red or white) with DPDT switch (rocker type) 74p

THE AMAZING DMO2

A ready-built, tested and guaranteed digital master oscillator. Accurately generates the top 13 notes for your organ system and reduces the complete tuning of your organ to ONE SIMPLE adjustment. New design gives selectable C to C output ranges of (approx.) 4k to 8k (highest) or 2k to 4k or 1k to 2k, etc. right down to 16Hz to 32Hz! And this new compatible design is even smaller: only 3.5in. x 3.7in. including gold-plated edge connexion.

DMO2T includes built-in variable depth and rate frequency shift tremulant.
DMO2 £15.31. DMO2T £17.81.
SAJ 110: 7-stage frequency divider 1n 14-pin DIL package. Sine or square wave input. Square wave output may be converted to saw-tooth. £1.94 each or 6 for £10.74 or 12 for £19.61.

RESISTORS

CARBON FILM
25W (MIN RES) 1 ohm to 1M: 5%, 1M2 to 10M: 10%, E12 2p each
1/2W (STD RES) 1 ohm to 10 ohm: 5%, 1M2 to 10M: 10%, E12 — 11 ohm to 1M: 5% E12 and E24 2p each

METAL OXIDE
1/4W (OXIDE) 10 ohm to 1M: 2% E12 and E24 5p each
WIREWOUND
3W (W/W MIN) 0.22, 0.27, 0.33, 0.47 ohms, 1 ohm 5% 11p
1.2 ohm to 270 ohm: 5% E12 15p

Also 1/2W Oxide, 1/4W Carbon Film, 5W and 10W Wirewound types stocked.
E12: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and decades.
E24: 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and decades.

TRANSISTORS & DIODES

AC127 19vsp	BC213L 19p	BFY51 24p	2A 400PIV Bridge 55p
AC128 19vsp	BC214L 22vsp	BFY52 21vsp	2N2219 33vsp
AC176 18vsp	BC227 22vsp	BFY53 41p	2N2603 48vsp
AD161 2MP £1.07	BC228 26p	BZK61 series 44p	2N2905 35vsp
AF117 27p	BC337 27vsp	BZY88 series 13p	2N2926 Or. Ye 15p

INGENUITY UNLIMITED



A selection of readers suggested circuits. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought. Any idea published will be awarded payment according to its merits. Why not submit YOUR IDEA?

forms a potential divider, whose output voltage depends on skin resistance. Transistor TR1 compares the voltage with a reference and feeds a current proportional to the difference between the voltage and the reference to a multivibrator TR2 and TR3. The frequency of the multivibrator depends upon the current from TR1. A crystal microphone insert acts as a speaker. Simple electrodes may be made from a pair of thimbles to which wires have been soldered.

In operation the two thimbles would be put on two fingers of one hand, and VR1 rotated to give an intermediate tone pitch. Upon relaxing the tone pitch should fall slowly.

A. Russell,
Whinmoor.

SKIN RESISTANCE INDICATOR

THERE is a relationship between the electrical resistance of a person's skin and state of relaxation. A device to make people aware of changes in their skin resistance can tell them how relaxed they are (bio-feedback) and thus help them relax. The skin resistance indicator, Fig. 1, provides an audible tone which falls as the state of relaxation increases (skin resistance rises).

The circuit is shown in Fig. 1. Potentiometer VR1 and the skin resistance between the electrodes

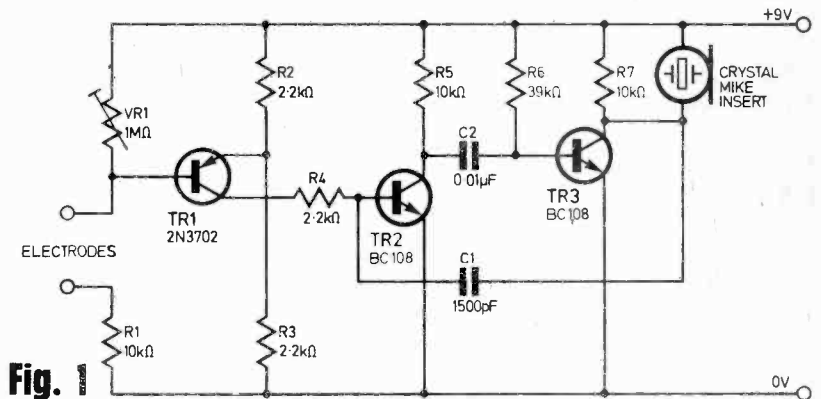


Fig. 1

SIMPLE SAWTOOTH GENERATOR

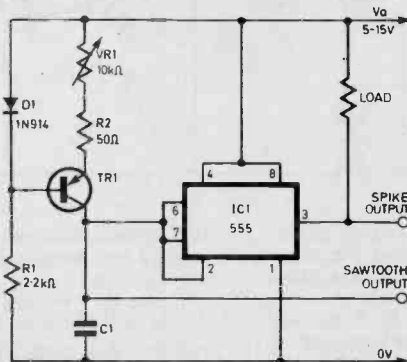


Fig. 1

A SIMPLE sawtooth generator may be constructed with the 555 timer and a germanium transistor. The circuit is shown in Fig. 1. TR1, D1 and R1 form a constant current source. C1 thus charges at a constant rate until the 555 internal comparator triggers. C1 is then discharged quickly, and the cycle repeats itself. Variation of VR1 alters the charging current of C1 and thus the output frequency. A sawtooth output may be taken from C1 through a high impedance buffer, and a spike output of the same frequency is available from pin 3. Output frequency may be varied by about 50:1, and the sawtooth linearity is about 5%.

A linear voltage versus period characteristic can be achieved by applying a modulating voltage to pin 5, which sets the comparator threshold.

J. N. Paine,
Oxford.

A GATED OUTPUT RANDOM GENERATOR

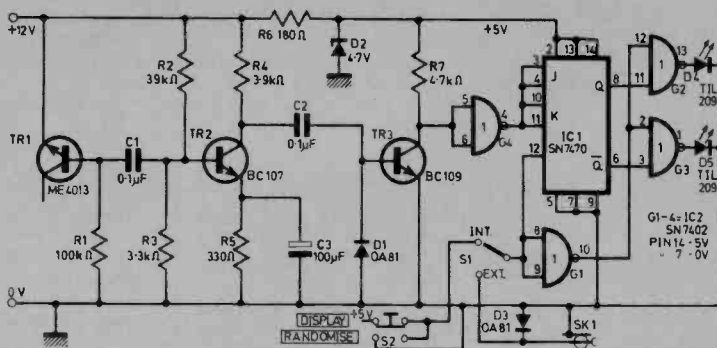


Fig. 1

THE following circuit (Fig. 1) was devised to act as a random generator of similar type to those used in parapsychology or ESP experiments. That is to say, it has an "off" period when neither of the light emitting diodes is illuminated followed by an "on" period when one or other, but not both of the l.e.d.'s is lit. Which l.e.d. is lit during this period is unpredictable, and this is the random aspect of the circuit.

The circuit consists of two sections: the random generator, and the gating circuitry. The random generator consists of a noise source (TR1) whose output is amplified

and shaped by the following stages and fed to NOR gate G4 which acts as a buffer.

The gating circuitry functions as follows. While the clock input (pin 12) of the 7470 J.K. flip-flop is at "0", its output is allowed to follow its input signal, i.e. it is changing state for every input pulse. This output is not seen on the l.e.d. display however, as the clock signal is inverted by gate G1 and used to disable l.e.d. driver NOR gates G2 and G3. When the clock signal goes to logic "1", the output circuits of the SN7470 are isolated from its input gates and are held, one at logic "1", the other at logic "0".

The clock signal is again inverted by gate G1, and enables the appropriate NOR gate G2 or G3, depending which is fed from the "0" output of the SN7470. Thus the appropriate l.e.d. is illuminated.

The clock input is shown as a simple push button switch in the diagram, but provision is made for an external clock. This should be a positive going square wave not exceeding five volts. The mark-space ratio of this square wave will give the "randomise" to "display" times of the unit.

C. Cartlidge,
Stafford.

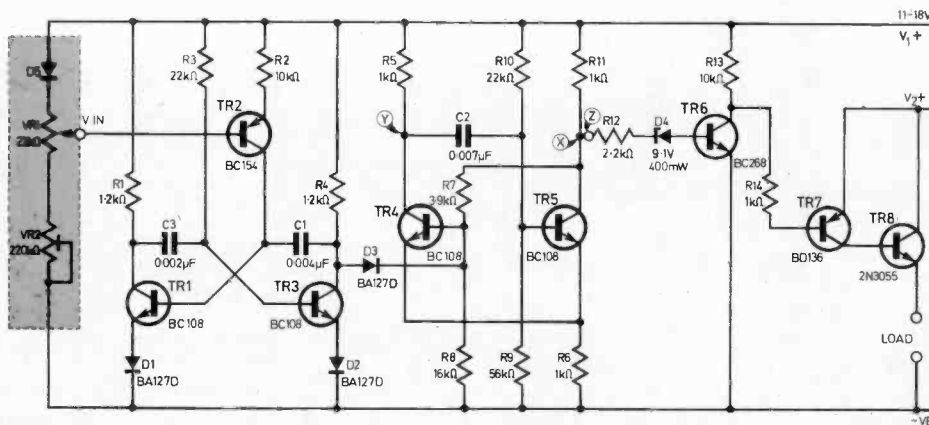


Fig. 1

HEADLIGHT DIMMER

THIS idea was suggested by an article in a motoring magazine concerning sidelight visibility. The circuit is capable of reducing the current to the headlamps (or to any other resistive load). Their output is thus reduced to sidelight level, whilst superior visibility is retained.

The limited space behind the dashboard made remote voltage control a necessity. The circuit generates a

square wave with a variable mark-space ratio, thus the lamps are either on or off and no power is dissipated by the circuit.

The circuit consists of a voltage controlled multivibrator driving a monostable which in turn drives the headlamps. This arrangement does not permit full control of the headlamps, but with a 12V supply and Z on the diagram connected to point X 0-10V was obtained, or 4-12V with Z connected to Y. A

little experimentation with C1 and C2 may be necessary for optimum performance.

A supply voltage between 11-18V is satisfactory, but V_2 (which provides the current) must not be higher than V_1 , or more than 5V lower. The maximum safe current is 10 amps. A suitable source of V_{in} is shown in the shaded portion.


J. A. Heathcote
Newport.

RADIO EXCHANGE LTD.

ALL PRICES INCLUDE VAT
We regret we cannot for the time being accept Overseas Orders. Open to U.K. and Ireland residents only.

NEW EDU-KIT MAJOR

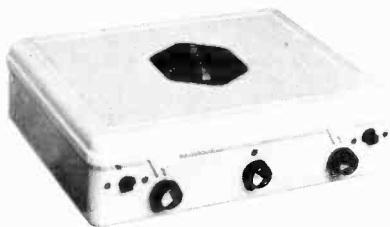COMPLETELY SOLDERLESS ELECTRONIC CONSTRUCTION KIT BUILD THESE PROJECTS WITHOUT SOLDERING IRON OR SOLDER



- 4 Transistor Earpiece Radio
- Signal Tracer
- Signal Injector
- Transistor Tester NPN - PNP
- 4 Transistor Push Pull Amplifier
- 5 Transistor Push Pull Amplifier
- 7 Transistor Loudspeaker Radio MW/LW
- 5 Transistor Short Wave Radio
- Electronic Metronome
- Electronic Noise Generator
- Batteryless Crystal Radio
- One Transistor Radio
- 2 Transistor Regenerative Radio
- 3 Transistor Regenerative Radio
- Audible Continuity Tester
- Sensitive Pre-Amplifier
- 24 Resistors
- 21 Capacitors
- 10 Transistors
- 3 1/2" Loudspeaker
- 2 Volume Controls
- 2 Slider Switches
- 1 Tuning Condenser
- 3 Knobs
- Ready Wound MW/LW/SW Coils
- Ferrite Rod
- 6 1/2 yards of wire
- 1 yard of sleeving, etc.

Complete kit of parts including construction plans

Total building costs £10.30
P.P. and Ins. 65p

ELECTRONIC CONSTRUCTION KITS

E.C.K. 1


3 Transistor Easy Stage Earpiece Receiver Kit, Full medium wave coverage. Complete with ready wound ferrite rod aerial, high efficiency Air spaced tuning capacitor. Sensitive crystal earpiece and gain control. Operates from a 9 volt P.P. 7 battery (not supplied with kit). This electronic construction kit is a good starter for those interested in kit building and soldering.



Complete kit of parts **£4.50** P.P. and Ins. 45p
INCLUDING CONSTRUCTION PLANS

E.C.K. 2


Self Contained Multi-Band V.H.F. Receiver Kit. 8 transistors and 3 diodes. Push pull output. 3in loudspeaker, gain control, superb 9 section swivel ratchet and retractable chrome plated telescopic aerial, V.H.F. tuning capacitor, resistors, capacitors, transistors, etc. Will receive T.V. sound, public service band, aircraft, V.H.F. local stations, etc. Operates from a 9 volt P.P. 7 battery (not supplied with kit).

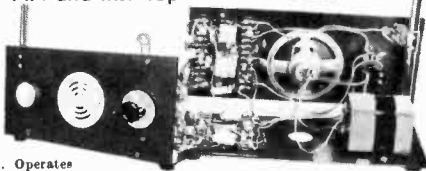

Complete kit of parts **£7.95** P.P. and Ins. 55p
INCLUDING CONSTRUCTION PLANS

E.C.K. 3

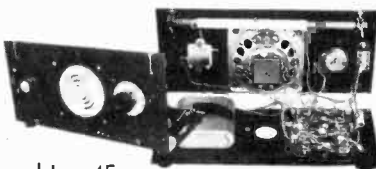
5 Transistor Medium Wave Receiver Kit. Class "A" output with 3in loudspeaker. Simple to operate with full medium wave coverage. Ready Wound 8in ferrite rod aerial. No external aerial required. 7 stages, 5 transistors and 2 diodes, Tuning capacitor, gain control, etc. Operates from a 4 1/2 volt Battery (not supplied).



Complete kit of parts **£5.40** P.P. and Ins. 45p
INCLUDING CONSTRUCTION PLANS

E.C.K. 4

7 Transistors, 6 tuneable wavebands, MW, LW, Trawler Band, 3 Short Wave Bands, Receiver Kit. With 5in x 3in loudspeaker. Push pull output stage, gain control, and rotary switch. 7 transistors and 4 diodes. 6 section chrome-plated telescopic aerial. 8in sensitive ready wound ferrite rod aerial, tuning capacitor, resistors, capacitors, etc. Operates from a 9 volt P.P. 7 battery (not supplied with kit).

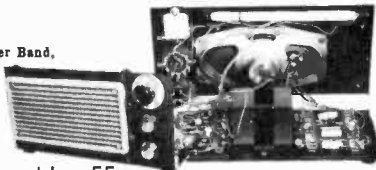

Complete kit of parts **£7.25** P.P. and Ins. 55p
INCLUDING CONSTRUCTION PLANS

V.H.F. AIR CONVERTER KIT

Build this converter kit and receive the aircraft band by placing it by the side of a radio tuned to medium wave or the long wave band and operating as shown in the instructions supplied free with all parts.

Uses a retractable chrome plated telescopic aerial, gain control, V.H.F. tuning capacitor, transistor, etc.

All parts including case and plans **£4.35** P.P. & Ins. 40p



ROAMER TEN MARK 2

WITH VHF INCLUDING AIRCRAFT Now with free earpiece and switched socket. 10 transistors. Latest 4in 2 watt ferrite magnet loudspeaker. 9 tuneable wavebands, MW1, MW2, LW, SW1, SW2, SW3, trawler band, VHF and local stations, also aircraft band.

Built in ferrite rod aerial for MW/LW. Chrome plated 6 section telescopic aerial, can be angled and rotated for peak short wave and VHF listening. Push pull output using 600mW transistors. Car aerial and tape record sockets. 10 transistors plus 3 diodes. Ganged tuning condenser with VHF section. Separate coil for aircraft band. Volume on/off. Wave Change and tone controls. Attractive Case in black with silver blocking Size 9in x 7in x 4in. Easy to follow instructions and diagrams. Parts price list and plans 50p free with parts.

Total building costs **£11.87** P.P. & Ins. 65p



RADIO EXCHANGE LTD.

To: RADIO EXCHANGE LTD.
61A High Street
Bedford MK40 1SA

Tel.: 0234 52367, REG NO. 788372

- Callers side entrance "Lavelle's" Shop.
- Open 10-1, 2.30-4.30 Mon Fri. 9-12 Sat

I enclose £..... for

Name

Address


PEI

EDU-KIT JUNIOR

Completely Solderless Electronic Construction Kit. Build these projects without Soldering Iron or Solder.


- Crystal radio medium wave coverage—No battery necessary.
 - One transistor radio.
 - 2 transistor regenerative radio.
 - 3 transistor earpiece radio medium wave coverage.
 - 4 transistor medium wave loudspeaker radio.
 - Electronic noise generator.
 - Electronic metronome.
 - 4 transistor push pull amplifier.
- All parts including loudspeaker, earpiece, MW ferrite rod aerial, capacitors, resistors, transistors, etc.

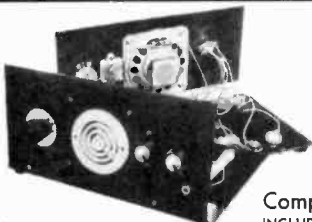Complete kit of parts **£7.50** P.P. and Ins. 45p
INCLUDING CONSTRUCTION PLANS





New from Connoisseur - BD3 Transcription Unit
 With a studio style rising turntable giving accurate cueing. Run up time is only a fraction of a second.
 Other important features include an external power source and consequently no hum field. A belt driven turntable with neon illuminated stroboscopic disc with 3 speeds, 33, 45 and 78 - all featuring variable control.
 The BD3 arm is lightweight and incorporates a unique method of magnetic stabilisation with an interchangeable head shell tracking cartridges down to 0.6 grams.
 The unit features brushed aluminium trim and is mounted on a matched wooden plinth complete with acrylic dust cover.

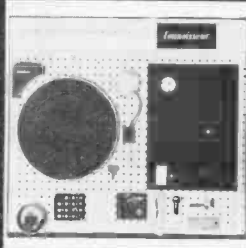

*Connoisseur
 Sound
 Design*



BD2 Turntable Assembly
 The famous BD2 belt drive turntable features push button speed change, an SAU2 pick up arm with damped lowering device, brushed aluminium trim, and specially designed turntable mat.
 It is available in chassis form, or as illustrated mounted on a slimline wooden plinth, with acrylic cover which features an easy hinged on hinged off movement.

BD1 Turntable Kit
 The BD1, well known for its excellent performance and superb quality is available in kit form, which

allows greater freedom of choice for the practical enthusiast with regard to mounting, selection of arm etc. Construction is simplicity itself with no soldering required. Now it's easy to own the best.

SAU2 Pick Up Arm
 Recognised as one of today's most advanced pick up arms. Among its star features is an Auto Bias compensator, hydraulic lowering device, precision balance and an adjustable head shell which can be matched to a wide variety of decks and pick up cartridges, ideal for the demanding practical audiophile.

For further details of all Connoisseur products, the BD3 or BD2, the BD1 kit or SAU2 arm, to the still popular SCU1 cartridge and our precision stylus balance, please contact your dealer or send a stamp for brochure.

Top left: The BD1 Turntable Kit.
 Top: The SAU2 pick up arm.
 Top right: The BD2 Turntable Assembly.
 Right: The BD3 Transcription Unit.



Connoisseur

Manufactured by:-

A. R. Sugden & CO. (Engineers) Ltd. Atlas Mill Rd, Brighouse, Yorks, HD61ES
 Tel: Brighouse (04847) 2142. Telegrams & Cables: Connoisseur, Brighouse.




TRAMPUS
 ELECTRONICS LTD. WINDSOR

58-60 GROVE RD.
 WINDSOR, BERKS. SL4 1HS.

ADD 8% VAT TO PRICES MARKED *
 ADD 2% VAT TO ALL OTHER PRICES
 SEND C.W.O. (EXCEPT GOVT DEPTS)
 POST & PACKING 20P FOR THE UK

NEW PART SERVICE. LOW PRICES.
 MONEY BACK IF NOT SATISFIED.
 ALL BRAND NEW TOP GRADE FULL
 SPEC DEVICES. CALLERS WELCOME!
 NEW CATALOGUE LIST FREE SAE.
 BARCLAYCARD & ACCESS BY POST.
 SORRY NO SALES TELEPHONE.

Digital Displays

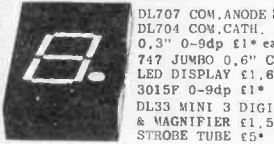

LEDS red 12p.

209 STYLE OR 0.2" NO CLIP 12p*
 TIL209 or 0.2" RED & CLIP 14p*
 GREEN LARGE/SMALL & CLIP 19p*
 ORANGE LARGE/SMALL & CLIP 19p*
 ORP12 57p* 2N5777 33p*
 TEC12 PHOTO IC SCWITT 14p*
 IC AY51224 4 DIGIT CLOCK 14p*
 MM5311 OR MM5314 6 DIGIT 15p*

CAPACITORS

CERAMIC 22pf-0.1uf 50v 5p.
 ELECTROLYTIC: 10/50/100 uf in
 25V 7P. 50V 9P. 2uf/10V 6p.
 1000uf 25V 18p. 200/500uf 9p.
 POTENTIOMETERS LIN/LOG 14p.
 PRESETS 6p. RESISTORS 14p ea

**HEATSINKS: T05 & T018 5p* TV4 15p*
 TV3/T03 16p* EXTRUDED 4" 4Y1 29p***

SWITCHES: SPST 19p. DPDT 25p.
 DIN PLUGS ALL 12p. SOCKETS ALL 9p

ALI CASES AB5/AB7 50p. AB13 65p*
 TRANSFORMERS 1/1A 6 or 12V 11.50*

TRAMPUS FULL SPEC PAKS ALL 11 ea
 PAK A 10 RED LEDS our choice 11p*
 PAK B 5 741C OP AMP 3 PIN 11p*
 PAK C 4 2N3055 11p. D 19 BC109 11p*
 PAK E 10 BC182 11p. F 11 2N3704 11p*
 PAK G 8 BFY51 11p. H 9 2N3819 11p*
 PAK J 9 2N3053 11p. K 40 1N914 11p

INTEGRATED CIRCUITS

703 RF/IF	26p	MC1303	11.50
709 T099	22p	MC1310	12.20
709 DIL 14	28p	MC1312 SQ	12.50
710 DIL 14	31p	MC1318	12.50
723 Regul'r	45p	MC1330	75p
741 DIL 8	21p	MC1339	11.40
741 DIL 14	31p	MC1350/1/2	75p
741 T099	31p	MC1466 /9	13
747 2x741	67p	MFC4000 1W	49p
748 DIL 8	27p	NE536 FETOPA	12
7805 5V	11.25p	NE540	11.10
7812 12V	11.25p	NE550 2Vr	11
7815 15V	11.25p	NE555 TIMER	42p
7900 Series	12p	NE556 2x	88p
76013 6W AF	75p	NE560 PLL	14.00
CA3046	54p	NE561 PLL	14.00
CA3048	12	NE562 PLL	14.00
CA3054	11.50	NE563	12.25
ICL8038 SGEN	13p	NE565	11.55
LM390	11.50p	NE567	12.20
LM301 OPA	41p	SN72741 741	21p
LM304 0-40V	13p	SN7660 IP	75p
LM308 HI BO	95p	SN7811 IF	11
LM309K 5V	11.75p	TAD100 81P	12
LM372 IF	12.00p	TBA800	89p
LM377 2x2W	13	TBA810 7WAF	99p
LM380 80745	88p	TBA820	75p
LM381	11.50	TBA820	99p
LM3900 40PA	63p	ZN414 RX	99p

749 TTL

7400	11p*	7474	29p*
7401	13p*	7476	29p*
7402	13p*	7490	39p*
7404	15p*	7491	43p*
7410	13p*	7492	43p*
7413	29p*	7493	39p*
7420	13p*	7494	46p*
7430	13p*	7496	74p*
7440	13p*	74100 1	27p*
7441	54p*	74121	27p*
7447	69p*	74123	65p*
7470	26p*	74141	64p*
7472	24p*	74173	12p*
7473	29p*	74174	11p*
		74175	85p*

TRANSISTORS

PRICE EACH:-	MATCHING	20p*	
AC127 & 128	11p*	INS. BUSH SET 6p*	
AC176	9p*	TIP29 & 30	43p*
AC187 & 188	11p*	TIP31 & 32	54p*
AD149	45p*	TIP41	68p*
AD161 & 162	33p*	TIP42	74p*
BC107	8p*	TIP2955	99p*
BC107B	12p*	TIP3055	67p*
BC108	8p*	T1S40 UJCT	32p
BC108B	12p*	T1X107/8/9	11p
BC109	9p*	ZTX300 1/3/4	20p
BC109C	12p*	ZTX500 1/5/4	42p
BC147/8/9	9p	2N706 & 708	11p
BC157/8/9	12p	2N2646 UJT	38p*
BC167/8/9	12p	2N2904 & 5	20p*
BC177/8/9	18p	2N2926B rony	9p
BC182/3/4/4A/4L10p		2N3053	16p*
BC212/3/4/4A/4L12p		2N3054	42p*
BCY70/1/2	16p*	2N3055 115W	37p*
BD131 & 132	39p*	2N3055 RCA	60p*
BF488 250V	35p	2N3702/3/4/5	9p
BFY50	14p*	2N3705/7/8/9	9p
BFY51	14p*	2N3710 & 11	10p
BFY52 & 53	14p*	2N3819E FET	14p
BSX19/20/21	16p*	2N3820 FET	40p
4J2955 T03	75p*	2N3820E FET	16p
MJE2955	99p*	2N3904/5/6	15p
MJE3055	67p*	2N4289 mint	31p
MPU131 PUT	49p	2N5457 FET	45p

CMOS LOGIC

CD4000 MC14 & 145K AVAILABLE.			
CD4000	15p*	CD4028	11.29p*
CD4001	16p*	CD4046	12p*
CD4002	16p*	CD4047	11.49p*
CD4009	65p*	CD4049	59p*
CD4011	20p*	CD4054	11.89p*
CD4013	53p*	CD4055	11.89p*
CD4016	49p*	CD4060	12.25p*
CD4017	11.15p*	CD4071	23p*
CD4018	11.69p*	CD4081	33p*
CD4022	11.55p*	CD4501	11.39p*
CD4023	18p*	CD4511	12.25p*
CD4024	11.15p*	CD4528	11.10p*
CD4027	89p*	CD4558	12.35p*

DIODES

OA91 & OA91 GERMANIUM	50p.
1N4001 1A50V 1N4002	5p*
1N4004 60* 1N4007	9p*
1N4148 & 1N914 SILICON	4p.
ZENERS 82V88 400mW	9p.
ZENERS 11V 17P. Z1Jnoise1	18p
BRIDGE RECTIFIER 1A50	18p
1A400V 25p. 4A100V	45p

SCR'S TRIACS

SCR'S TAG1/400 1A400V	50p*
1A50V 38p. 1A 400V 70p*	
C196D 4A400V SCR ONLY	47p*
TRIAC SC143D 10A400V	11p*
TRIAC DISCO 15A400V	12p*
DIACS: ST2 20p. BR100	25p

vero pen 69P

DALO ETCH RESIST PEN 69p*
 PEC ETCH PAK 500mg 89p*
 6x4" COPPER BOARD 50p*
 PCB KIT 3 ITEMS 12p*
 CASSETTE MECHANISM 10p & 13
 TGS GAS DETECTORS 30setcf2*

DIL sockets

TOP QUALITY NYLON
 SOCKETS 8PIN 12p*
 14PIN 13p. 16PIN 14p.
 SOLDERCON PINS:
 100 65p*. 1000 14p*



LIGHTS-ON REMINDER

THIS circuit (Fig. 1) can be used to remind one to switch on sidelights when darkness falls. During the day the l.d.r. is in a low resistance state, TR1 is turned on and the relay RLA energised. Contacts RLA1 are thus open (RLA is a normally closed type).

When the ambient light drops to a level preset by VR1, TR1 turns off, contacts RLA1 close and RLB (normally open) is energised via the side and tail filaments causing the buzzer to sound. When the sidelights are switched on RLB drops off and the buzzer is thus silenced.

D. Doughton,
Merseyside.

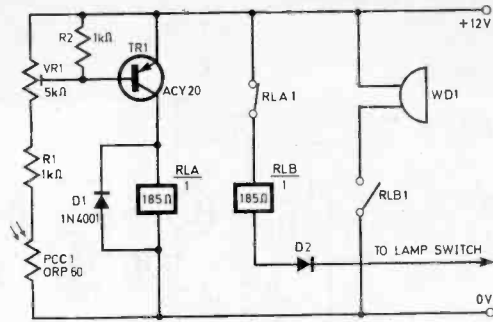


Fig. 1

SIMPLE TIME SWITCH

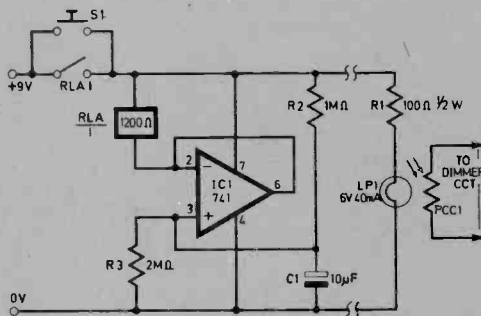


Fig. 1

A TIME switch to save wasteful use of lighting on a staircase is shown in Fig. 1. The circuit operates a lamp for several seconds and consumes no power when not in use.

When S1 is momentarily depressed it becomes bypassed by the relay switch. After several seconds the relay loses holding current, and the supply to both timer and lamp is broken. The timing network consists of R2, R3 and C1. Charge build-up on the capacitor is prevented by R3.

The addition of a light dependent resistor to a conventional lamp dimmer will allow control of mains lighting—the lamp being optically coupled to the l.d.r.

S. L. Thompson,
Stafford.

SEQUENCING OSCILLATOR

THIS circuit (Fig. 1) uses a 7413 and a 7490 to produce a repeating series of ten notes. R1, C1, G1 (IC1a) form a low frequency oscillator which drives the decade counter. G2 (IC1b), R2, C2, R3, R4, C4, R5, C5 form another oscillator. Sections of this oscillator can be disabled by holding the input terminals of the decade counter at V_{ce} .

The outputs of the decade counter (A, B, C and D) are connected to the input terminals of the oscillator (1, 2, 3 and 4). Any combination of inputs and outputs can be used (one input to one output). As

the decade counter counts, different parts of the oscillator are disabled, resulting in a series of ten notes.

The frequency can be changed by altering the value of the capacitors.

W. H. Montgomery, Lorne.


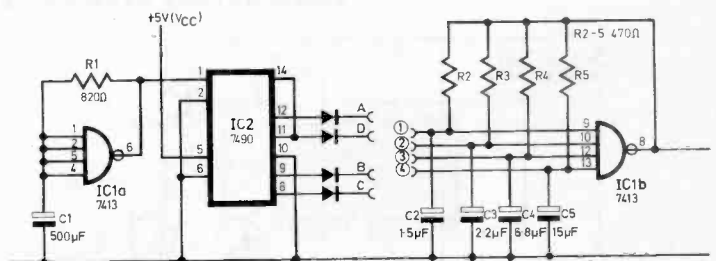


Fig. 1

Fig. 1a

**VOICE OPERATED
FADER
MODIFICATIONS**

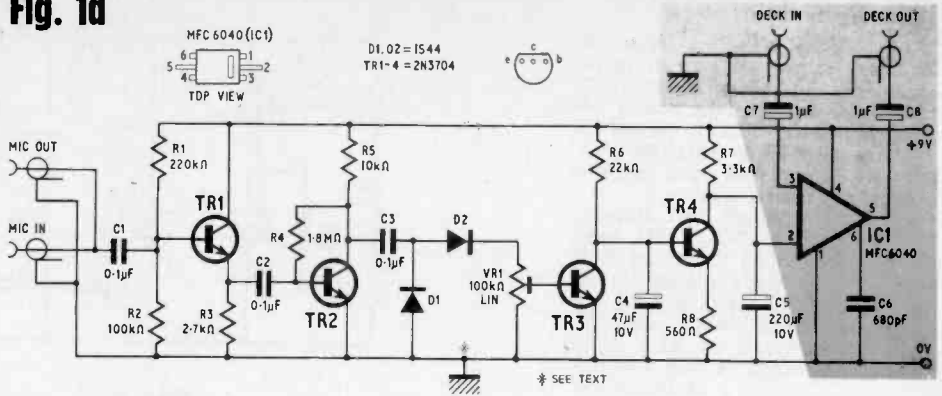

WITH a little modification the Voice Operated Fader (P.E. December 1973) can be made to drive f.e.t.'s instead of the more expensive (and harder to get) MFC 6040. The original circuit is shown in Fig. 1a. The shaded section should be deleted and the circuitry in Fig. 1b inserted.

The control voltage at the collec-

tor of TR4 is fed to the gates of the f.e.t.'s TR5 and TR6 via the presets VR2 and VR3. The presets are incorporated to prevent image shift problems arising due to the f.e.t.'s pinch-off voltages being different.

The circuit uses the f.e.t.'s property of being a voltage controlled resistor; in this case the f.e.t.'s are

off with no "voice" input (TR4 on) and are driven on when there is a "voice" input. This results in attenuation of the left and right channels when a "voice" signal is present.

Since this is a shunt attenuator it would not be suitable for direct connection to a ceramic cartridge as in the original arrangement. *Note*

OUTPUT METER

THE record level meter in less expensive tape-recorders is not used in the replay mode. Where the drive to the meter is a rectified, smoothed version of the record amplifier output, a simple switch and circuit can be used to display the audio output.

Fig. 1 shows the arrangement for the modified meter. S1 is operated where possible by the record button such that the meter is only driven by the existing circuitry when in the record mode. When in playback the speaker drive signal is rectified by D1 (any germanium signal diode) and the response of the meter is damped by capacitor C1.

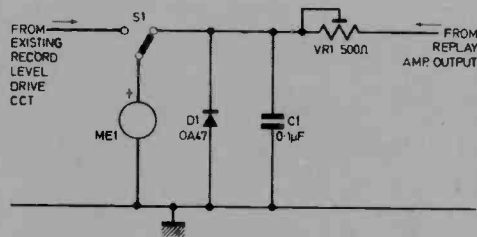


Fig. 1

Since the meter is less than 1mA f.s.d. the series potentiometer VR1 limits the current to a safe value. The indication on the meter is therefore the positive peaks of

the audio with the attack/decay time set by C1 and the deflection for a given signal by VR1.

J. C. Sadler,
Altrincham.

TEMPERATURE SENSING DEVICE

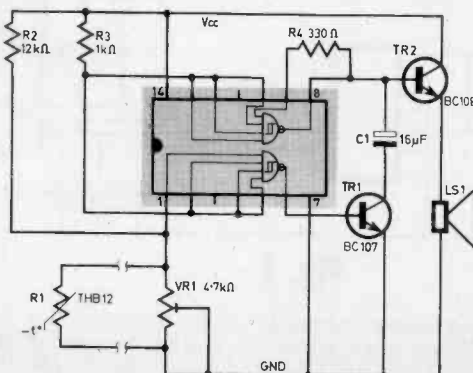



Fig. 1

THIS circuit (Fig. 1) uses the Schmitt properties of the dual 4 input NAND gate 7413. A potential divider is formed with the thermistor R1 in parallel with VR1, and R2. When the voltage from the potential divider exceeds the Schmitt threshold, an oscillator formed around the remaining components is activated. Potentiometer VR1 allows adjustment of the threshold temperature.

The whole circuit may be built on a piece of Veroboard 5cm by 5cm.

P. R. G. Reynolds,
Benfleet.

Fig. 1b

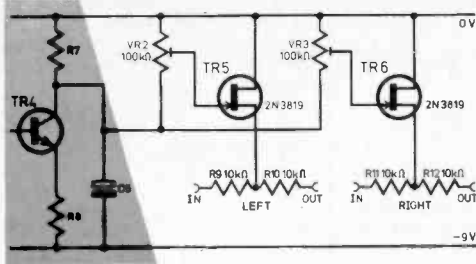

that the earth should be changed from the lower (negative) rail to the upper (positive), since the f.e.t.'s are working around the positive rail.

N. Valentine,
Angus.


VOLTAGE CONTROLLED ZENER

THE circuit shown in Fig. 1 can be used as a voltage controlled Zener diode. If the f.e.t. is replaced with a resistor R2 the standard "amplified diode" configuration is obtained.

The addition of a f.e.t. merely provides a voltage control of one of the resistors and thus a control over the voltage at which the transistor turns on.

I. D. Evans,
Cambridge.

Fig. 1

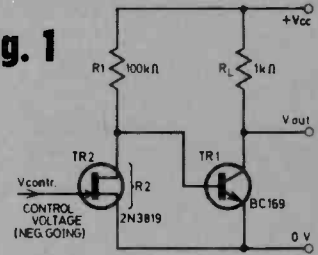

DWELL METER MODIFICATIONS

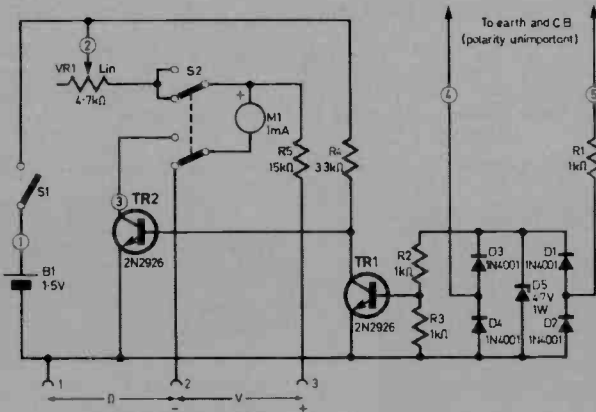


Fig. 1

WITH the simple addition of a few more components the Dwell Meter (P.E. Dec. 74) can be used as a voltmeter, ohmmeter and to check the opening of the points—as well as the original capability of being a dwell meter.

Fig. 1 shows the modified circuit. It operates in the following way.

To read dwell angle S1 made; S2 to left.

To read ohms; S1 made; S2 to right and adjust VR1 for full scale reading with terminals 1 and 2 shorted. (There is no need to cali-

brate the scale in ohms as one only requires an indication of good or bad continuity.)

To read volts; S1 is open and with the 15kΩ resistor in circuit a full scale reading of 15V is obtained. It is advisable to use this range and calibrate the dial from 0–15V accordingly, whereby a reasonable indication of 12V is obtained. It may be necessary to adjust this on test to obtain an accurate reading.

W. E. Priest,
Bradford-on-Avon

SIMPLE LIGHT FLASHER

THE circuit shown in Fig. 1 can be used to flash Christmas tree lights. An 80W fluorescent lamp starter is placed in series with the set of lamps and it is this that causes them to flash. No suppression is required since the starter has a capacitor included. No radio or TV interference was detected. The total power supplied should not exceed 80W.

S. Judson,
Halifax

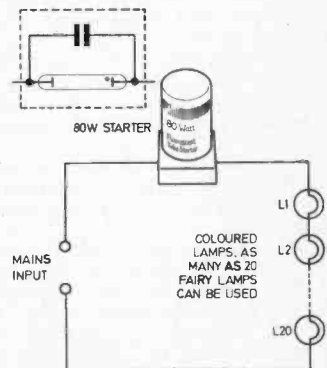


Fig. 1

MARKET PLACE

Items mentioned in this feature are usually available from electronic equipment and component retailers advertising in this magazine. However, where a full address is given, enquiries and orders should then be made direct to the firm concerned. All quoted prices are those at the time of going to press.

DIGITAL WATCH

The long awaited **Sinclair** digital watch has now been launched onto the market. Referred to as the "Black Watch", this instrument is a typical example of the individual styling expected from Sinclair. The watch is housed in a specially designed plastic case—almost unique in the field of digital watches in that the case is custom built and not just a normal type of watch housing.

Flexible diaphragms form an integral part of the plastics case and provide an economical and reliable solution to the switch problem. These "pressure pads" are easy and convenient to use. Another important feature for the user is the readily removable plug type of cover for the battery compartment.

The watch circuitry is contained within a single integrated circuit using injection logic technology (I²L). This bipolar process is claimed to have produced very high packing density and excellent speed-power product, with important production cost benefits. The chip was designed by Sinclair and has been produced by IIT in Britain. The other components are a crystal, a trimming capacitor, the l.e.d. display and two small mercury cells.

Hours and minutes or minutes and seconds are displayed depending which switch pad is depressed. The display is internally timed for one second or will stay on as long as the switch is closed. The third switch is on the rear of the case and is used for setting the watch and holding the time.

The display is fitted with a lens magnifier which allows brightness to be maintained at lower current consumption.

Sinclair guarantee an accuracy of better than one second per day. In principle, depending upon the precision to which the quartz crystal is trimmed, the watch is capable of maintaining time to within one or two minutes per year.

The watch comes complete with a black nylon reinforced polyurethane strap.

In kit form, price £17.95, the Sinclair digital watch appears likely to offer little problem to the average constructor. (We hope to include a review of assembling the watch in a future issue.)

POWER SLAVES

It is at this time of the year that one starts to worry about the problems of winter and tries to prepare for the likelihood of any possible industrial unrest and service breakdowns.

With this in mind Jermyn's seem to have timed the launching of their new range of excellent invertors at the most opportune moment. These new invertors now use silicon transistors throughout their range. They claim this increases their reliability and back their claim with a one year guarantee.

Two versions are available, type 150-3 with a load of 150W powered from a 12V car battery and a 300W version, type 300-3, powered from two 12V car batteries.

A feature of the invertors is that if you are not at home when the mains fails, the unit will automatically switch over to battery operation. The average running time for battery operation is 3 hours, depending on load. When the mains is restored the units automatically switch back to stand-by operation and recharge the battery.

Apart from lighting other typical applications are: running central heating (pumps and thermostats); tropical fish tank heaters; powering professional equipment, dentist

drills and telex machines, etc.; and office calculators and typewriters. Also the units are ideal for running any normal household mains equipment such as power drills, television and radio. For outdoor use when camping, caravanning or boating the invertors are invaluable.

Further details and prices can be obtained from **Jermyn Manufacturing, Sevenoaks, Kent**.


CAR RADIO

Claimed as the first all British designed and built car a.m./f.m. stereo radio, the Radiomobile 1190FMS features an interference rejection circuit module in the f.m. stereo tuner. Known as AIR, active interference rejection, this module is their latest development in combating the problem of interference.


The set has an output of 5W per channel with a bass/treble tone control. The six button tuner, combined with manual tuning, permits simple pre-setting of any three f.m., two medium and one long wave stations. The tuning ranges cover 87.5-104MHz f.m., 525-1620kHz m.w. and 150-275kHz l.w.

Provision is provided for a tape input with a sensitivity of 30mV for 5W output per channel. In this connection Radiomobile are planning to introduce a "tape mate" at a later date.

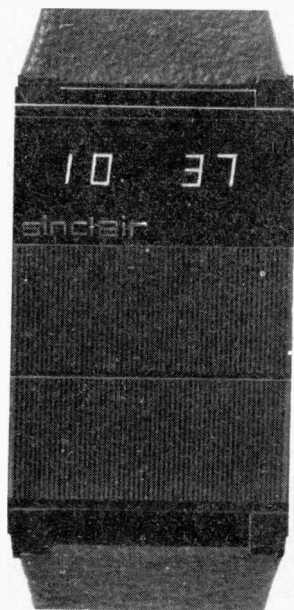No price has been announced for the 1190FMS but further details can be obtained from **Radiomobile Ltd, Goodwood Works, North Circular Rad, London, NW2 7JS**.



Sinclair "Black Watch"

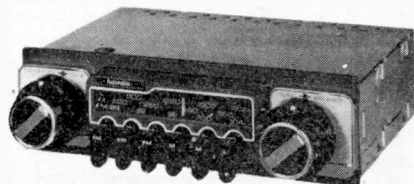

The 1190FMS a.m./f.m. stereo radio from Radiomobile



Jermyn 300W inverter

DIGITAL CAPACITOR METER

A new digital readout capacitance meter, type DCM 302, is announced by Aim Cambridge Ltd.

The meter automatically ranges over 6 decades of measurement, from 1999pF to 19.9 μ F full scale, and the $3\frac{1}{2}$ digit seven segment display gives a resolution of 0.05 per cent of reading.

Designed for ease and speed of operation, no complex nulling or other adjustments are required, the only control is a touch pad which is used to initiate a measurement. If powered by batteries the meter automatically switches off after 10 seconds. Two 9V (PP3) high power batteries give a typical operating life of at least 6,000 measurements. A mains power pack is available.

The DCM 302 is of British design and is available direct from Aim Cambridge Ltd., Nuffield Road, Industrial Estate, St. Ives, Huntingdon. The price of the meter is £89.

BATTERY

A dated battery with a stated shelf life is now being marketed by West Hyde Developments Ltd.

Known as the "Wonder Top" each battery is date stamped at manufacture with a guaranteed shelf-life of up to two years. The batteries have a plastics/cap which operates a break-off cover protecting them against unwanted discharge. The protective cap is unscrewed for testing but is overscrewed to break the seal to allow installation in equipment.

Ideal for all types of battery operated equipment the batteries are claimed to give excellent performance. For instance, the TOP 20 (HP20 etc.) has a short circuit current of 6A. A maximum electrical capacity of 7.8Ah with a power of 2.5W. Tested to the C.E.I. intermittent 5 ohm load (4 hours a day) the life is over 20hrs to a voltage of 1V, at 40 ohms this rises to 190hrs.

The smallest of the three batteries offered, a pen cell, provides a 1.5Ah maximum with a short circuit current of 3A.

Full technical details of the complete range and addresses of nearest stockists can be obtained from West Hyde Developments Ltd., Ryefield Crescent, Northwood Hills, Northwood, Middx, HAS INN.

SWITCHES

A range of fire resistant plastics encapsulated rotary switches is now available from Lorlin Electronic Ltd.

These switches, type CK, are available in 1, 2, 3 or 4-pole versions with 30 degree indexing up to 12 positions single pole. An adjustable stop allows the number of ways to be selected to individual requirements.

The silver plated brass contacts are rated at 150mA at 250V a.c./d.c. and 350mA at 110V a.c./d.c.

Further information on the complete range of Lorlin switches is available from Lorlin Electronic Co. Ltd., Daux Road, Billingshurst, Sussex.

IN BRIEF

To coincide with the opening of two new audio shops in Reading and Notting Hill Gate, London, Henry-Lindair announce an audio part exchange scheme.

Customers who take their old equipment to any Henry's-Lindair store will, in future, be able to obtain a trade-in allowance which can be set against the purchase of new equipment from that particular store. The trade-in item is passed to the Service Department where it is tested and overhauled.

All selected trade-in items are then sold through one of the groups newly established "Bargain Centres" in Edgware Road, and Tottenham Court Road, London, with a three month guarantee.

We understand that A. Marshall (London) Ltd. have signed an agreement to supply ITT Semiconductors components to both the trade and the amateur.

Initial stocks will mainly be confined to products such as transistors, diodes, and rectifiers, together with selected specialist integrated circuits for television and other applications.

ITT Semiconductors manufacture specialised i.c.s. with applications in areas such as remote control, hi fi, clocks, watches and automobiles and Marshall's hope to introduce selected items and kits from this range into the consumer and amateur markets in the near future.

A new 24-page MOS products catalogue entitled "It's Standard at AMI" has just been published by AMI Microsystems.

This short form catalogue is an up-to-date listing of all current, recently introduced and future AMI products. It includes sections dealing with micro-control systems, microprocessors, memories, interface circuits, communications modules, wristwatch, clock, calculator and electronic organ circuits and liquid crystal displays.

Copies of the catalogue can be obtained from AMI Microsystems Ltd., 108a, Commercial Road, Swindon, Wilts.


For readers interested in Disco equipment, Saxon Entertainments Ltd. have released brochures on their System 7000 sound and light modules.

Included amongst their amplifiers, mixers and lighting units is a Sound/Lite Sequencer capable of handling up to 1000W per channel.

Copies of the brochures are available from Saxon Entertainments Ltd., 327-333 Whitehorse Road, Croydon, Surrey.

NOTE

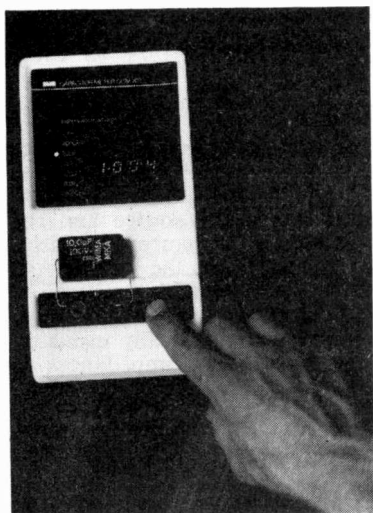
We regret that an incorrect address for Barclay Electronics was given last month. This should be: Barclay Electronics, 1115 Finchley Road, London, N.W.11.



Digital capacitor meter type DCM302 from Aim Cambridge



"Wonder Top" batteries from West Hyde

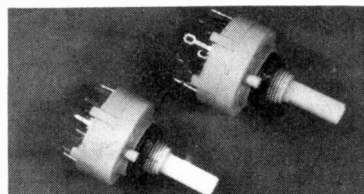


Lorlin CK Rotary switches

Using

CMOS

digital I.C.s

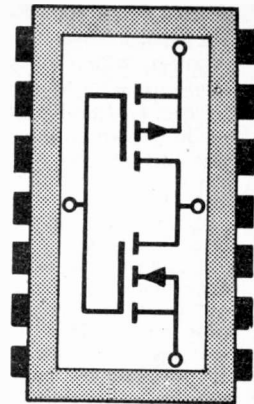

By D.B. JOHNSON-DAVIES & A.M. MARSHALL B.A.

PART 1

This series of articles will acquaint the reader not only with the basic characteristics but also the practical applications of CMOS as succeeding parts will give tested circuits with full description of operation.

Readers who have never used any logic family, either due to lack of funds or lack of confidence will find CMOS an excellent introduction as it is well suited to the experimenter. Its microwatt power consumption, single supply operation from non-regulated 3 to 15V supplies, high noise immunity, abilities to switch analogue signals and operate as high gain linear amplifiers are all qualities which make it ideal for this role.

THE first commercial complementary MOS device was shown by RCA in March 1967 at the New York IEEE show. The CD4000 range was launched the following year and by 1971 a wide range of plastic packaged devices with operation from 3 to 15V was available. This was the year that CMOS finally evolved into a fully-fledged rival to other logic families with Motorola announcing proprietary products of its own—the MC14500 series. The following years have seen a phenomenally rapid growth both in the range of devices and usage.

Prices have steadily fallen until, in the last year they have literally tumbled to, in many cases, below TTL prices. The one-off price of a 4-gate package is now 17p, while MSI packages which would require two TTL packages show a considerable price advantage. This year, despite the recession, RCA, which has a 40 per cent share of the CMOS market, intends to introduce a further 40 new CD4000 series devices. This will bring the total number in the series to 182.

DEVELOPMENT

For a long time bipolar TTL has been the standard medium-speed logic family. In the last few years MOS (metal oxide semiconductor) technology has made possible the fabrication of the high-density calculator, clock and, more recently, microprocessor integrated circuits.

It is the complementary form of MOS—CMOS—that has developed into a comprehensive logic family with a number of significant new features that offer a serious challenge to TTL.

MOS i.c.s are those fabricated entirely from MOS field-effect transistors or MOSFETs. Basically a MOSFET consists of a metal gate electrode insulated from a channel of silicon by a thin oxide layer. It is this metal oxide semiconductor sandwich that gives the technology its name.

The channel is doped with one polarity and two other electrodes are formed by troughs of opposite polarity on each side of the gate. These are called the drain and the source. Two types are possible: an *n*-type or a *p*-type, according to the doping of the channel.

MOSFET AS A SWITCH

The MOSFET behaves as an excellent switch, since when the gate voltage is raised to a critical level (known as the threshold voltage) the device switches on and current flows between the source and the drain. This gate voltage induces a change of polarity in the material under the gate, i.e. the channel, so that with an *n*-type a positive switching voltage is needed on the gate, and similarly a negative voltage with a *p*-type. Since the gate is electrically insulated from the silicon, MOSFETs have input impedances of the order of 10^{12} ohms (one million megohms). Therefore, to all intents and purposes, no current flows in the gate circuit, and switching is achieved by electrostatically induced charges.

MOSFETs AS LOGIC ELEMENTS

Now the question arises—how are these basic electronic switches used to build logic elements? A PMOS inverter is shown in Fig. 1.1(a); a low input

(below the threshold voltage) produces a high output and vice-versa.

Suppose we require the output to go high when any one of a number of inputs is low. The circuit of Fig. 1.1(b) satisfies this requirement, and its PMOS equivalent is a 3-input NOR gate. In other words the output is high if "NOT (A OR B OR C)".

PMOS AND NMOS

In practice the resistor is replaced by a second *p*-type MOSFET which is biased on by a second supply line of about twice V_{SS} . This is called V_{cc} since it is connected to the gates of the load devices. The resulting PMOS inverter is shown in Fig. 1.1(c). In the on state a single PMOS inverter has a significant power dissipation of about 10mW.

The great advantage of PMOS is that very high packing densities can be achieved on a single chip since each gate is extremely simple. The disadvantage is the power dissipation—a typical clock chip consumes about 10mA, as much as one of the displays it is driving. Furthermore, two power supply rails are generally needed and the speed of operation is fairly low.

Integrated circuits made entirely with *n*-channel MOSFETs give a greatly improved performance and density, but until recently, the inherent fabrication difficulties have prevented NMOS from being a viable production technology. Now that these difficulties have been resolved, NMOS is making possible a whole

new range of high speed, high density memories and microprocessors.

COMBINING BOTH TYPES

A third way of using MOS is to combine *p*-type and *n*-type MOSFETs on the same chip. The formidable fabrication problems involved, especially at high production levels, were overcome by RCA by the late 1960s. The inverter now becomes a *p*-type and an *n*-type connected in a complementary-symmetry (hence RCA's trade name COSMOS) push-pull configuration across the supply rails. The gates are connected together to form the input—Fig. 1.1(d). The d.c. power dissipation of the PMOS inverter is now reduced virtually to zero, being a product of the nanowatt leakage current of the MOSFETs.

A new general purpose logic family was born. Its great versatility and unique features account for the fact that it has reached its present maturity in such a remarkably short time.

MARKET GROWTH

RCA market the family as the CD4000 series with the trade name COSMOS, and there are at present more than 140 devices in the family. The first major manufacturer to second-source the 4000 series was Motorola in 1971, using the trade name MCMOS. At the same time Motorola introduced devices of their own design, designated the 14500 series. Today there are more than a dozen suppliers with the latest

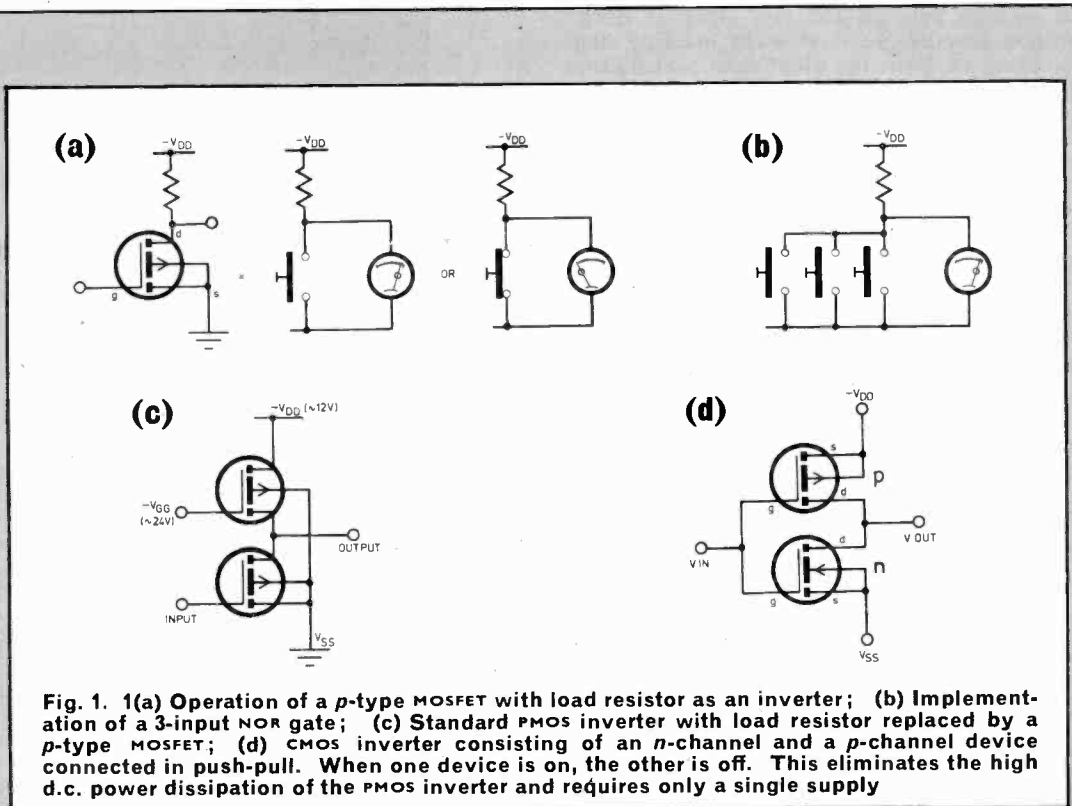


Fig. 1. 1(a) Operation of a *p*-type MOSFET with load resistor as an inverter; (b) Implementation of a 3-input NOR gate; (c) Standard PMOS inverter with load resistor replaced by a *p*-type MOSFET; (d) CMOS inverter consisting of an *n*-channel and a *p*-channel device connected in push-pull. When one device is on, the other is off. This eliminates the high d.c. power dissipation of the PMOS inverter and requires only a single supply

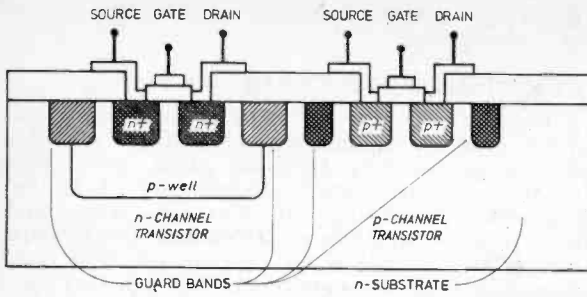


Fig. 1.2. Typical CMOS structure, showing a *p*-channel and an *n*-channel device diffused on the same substrate

entrant to the market being Philips with an initial introduction of 35 4000 and 4500 series CMOS parts.

CMOS FABRICATION

A cross section of the basic CMOS element, a *p*-channel and an *n*-channel device on the same substrate is shown in Fig. 1.2. The starting substrate is made of *n*-type silicon into which is diffused a well, forming a *p*-type substrate for the *n*-channel transistor. Each substrate then has *p* or *n*-type pockets diffused to form the sources and drains of the *p* or *n*-channel transistor.

Protective guard bands are also diffused around the *p* and *n*-type transistors, of opposite polarity to prevent leakage between the two types of device. The process generally requires seven masking steps, the last being to form the aluminium metallisation etched to form the appropriate circuit interconnections.

In spite of all this, CMOS circuits have a much higher packing density when compared with bipolar

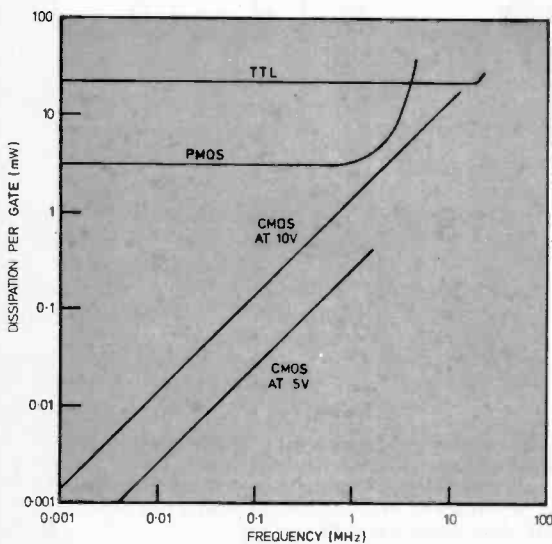


Fig. 1.3. Power versus speed comparison for CMOS, PMOS and TTL. Power consumption of CMOS approaches that of TTL at high speed, but at 1kHz is only $1\mu\text{W}$

technology. Less chip area is required per function through the elimination of resistors and capacitors and the extremely low power dissipation.

INVERTER STATIC OPERATION

As mentioned, one of the basic building elements of CMOS i.c.s is the complementary inverter. The *n*-channel device is connected to the negative supply and the *p*-channel device to the positive rail. When the input is at the negative supply potential, the *n*-channel device is off and appears as a resistance of several thousand megohms. The *p*-channel device is at the same time on and has a resistance of about 750 ohms. The output of the inverter is thus clamped to within a few millivolts of the positive supply rail.

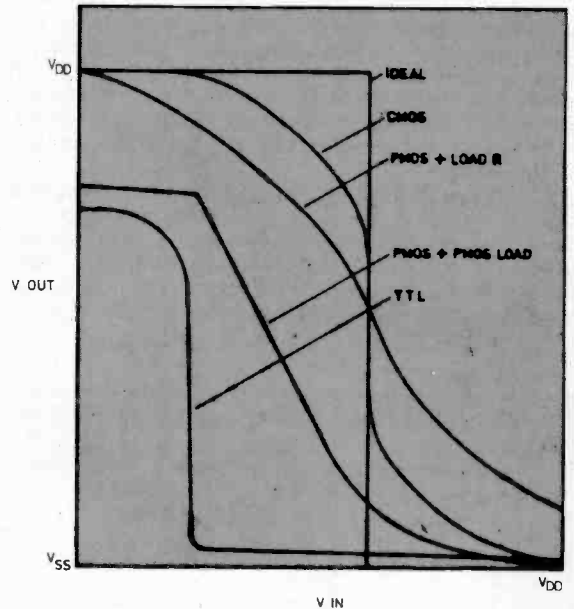


Fig. 1.4. Switching characteristics of CMOS, PMOS and TTL. CMOS approximates far more closely to the ideal switch

Equally when the input to the inverter is at the positive rail, the output is virtually at the negative rail. In either state the static power consumption is of the order of a few nanowatts only.

The MOSFETs of the inverter have threshold voltages of around 45 per cent of V_{DD} . This gives the inverter its highly symmetrical switching characteristic, coupled with high noise immunity. The transfer characteristic approaches that of an ideal switch more closely than that of any other inverter configuration—Fig. 1.4. Allowing for production spreads in threshold voltages, the guaranteed d.c. noise immunity is usually 30 per cent but will typically be 45 per cent of V_{DD} . Thus at a supply voltage of 5V, the noise immunity will be about 2V. This means that, as well as having a high immunity to input noise spikes, CMOS does not require well-regulated power supplies. Simple RC smoothing is often all that is required.

POWER DISSIPATION

Since the supply voltage is greater than the sum of the threshold voltages, both of the devices will be on simultaneously as the inverter switches during a transition of 10 per cent of V_{DD} . This causes a peak of current to be drawn from the supply. However, the majority of the dissipation does not come from the resistive flow through both the partly on transistors, but from the charging and discharging of stray and load capacitances.

The output is held at very nearly V_{SS} or V_{DD} during this simultaneous conduction period and the current is diverted to the capacitance itself. Thus the switching power dissipation of the CMOS inverter is almost entirely due to capacitive loading and the more frequently the inverter passes through this mid-point region the higher will be the power dissipation until, at 10MHz, it reaches that of TTL (Fig. 1.3).

So in order to realise the micropower operation of CMOS the operating frequency should be kept low. While the CMOS inverter shows an idling or quiescent power dissipation, P_0 of the order of nanowatts, when switching the power dissipation, P_D , is given by $P_D = P_0 + C_L \cdot V_{DD}^2 \cdot f$ (where f is the operating frequency).

OPERATING VOLTAGE RANGE

As we have seen the CMOS inverter operates from a single supply (Fig. 1.1). Thus V_{SS} is 0V when the input swing is positive. However, if it is also negative, then V_{SS} must be negative by at least the same amount. Standard CMOS devices operate from 3 to 15V, with an output logic swing within a few millivolts of the supply rails.

HANDLING AND USAGE

The extremely high input impedance of MOS allows electrostatic charges to build up which could easily puncture the very thin input gate oxide layer. Present day CMOS devices are pretty thoroughly protected against such charges by diode-resistor-capacitor input networks and, provided simple earthing precautions are taken, devices can be handled quite safely.

One precaution, however, must be emphasised. Devices can be destroyed when driven by low impedance sources, such as a signal generator or even the outputs of other CMOS devices, if the V_{DD} supply is disconnected. In this case one of the protective diodes may become forward biased causing possible damage to the diode or the input metallisation.


UNUSED INPUTS

All unused inputs should be connected to one or other of the supply rails, as appropriate. Floating inputs not only waste power but can cause erratic operation of the rest of the device. The outputs of most devices are virtually short-circuit proof. This is because of the inherent current-limiting characteristic of the complementary inverter, whereby the output current is limited to one or two milliamps. The only restriction is that the total package dissipation of 200mW should not be exceeded.

Next month: The other basic element from which CMOS i.c.s are built; the transmission gate. Also included are practical CMOS circuits.

GUITAR AMPLIFIER

continued from page 30

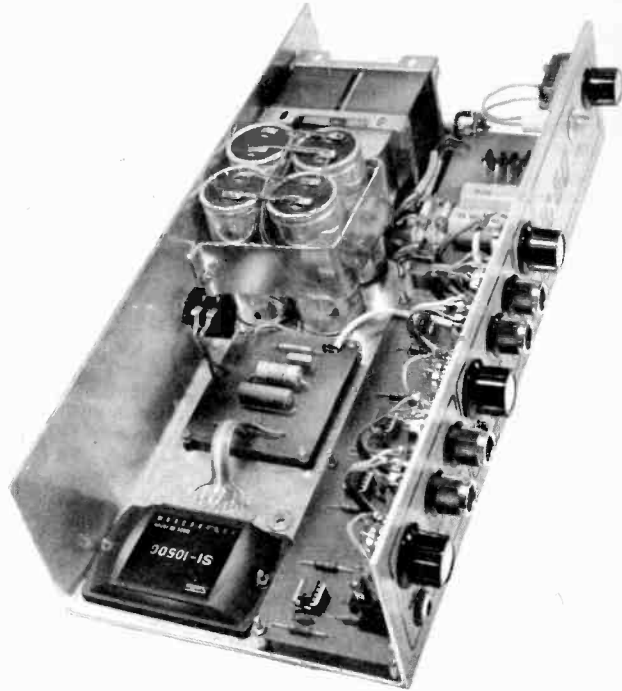

The voltage reading at the output socket (SK3) should be almost zero. On the prototype this reading was minus 200 millivolts.

Switch off and replace FS1 with an ammeter. Switch on and measure the quiescent current. It should be in the order of 20 milliamps.

If all the above tests have been successful, a suitably rated 8 ohm loudspeaker can be connected and the amplifier tested with an input signal such as from a signal generator (if available—in which case further tests can be carried out) or from a guitar pick-up, microphone or electronic organ.

Check the performance of the volume controls by slowly turning them clockwise to increase the volume. Clockwise rotation of the treble and bass controls should boost treble and bass frequencies.

CASE

Construction details of the amplifier case as used in the prototype are given in Fig. 12. The material used was 12mm thick blockboard, glue and nails being suitable for the butt joints. The inside front was faced with 10mm quadrant glued and nailed all round, with mitred joints.

Two holes need to be drilled on the underside to align with the chassis fixing nuts, through which two 25mm long 2BA bolts fitted with large washers will hold the chassis assembly firmly in position against the quadrant facing.

Thoroughly sand down and fill in any indents there may be in the finished case and paint or cover the case as required. Black Rexine was used on the prototype case and glued on using pearl/crystal glue. To finish off, fit four rubber feet and a snap-back flush carrying handle on the top, see photographs. ★

SEMICONDUCTOR UPDATE

By R.W. COLES

ULN2275 AY-3-9400/10
ULN2277 M142
ULX2276 ILQ74

STEREO TRIO

If you're like me, it's possible that you sometimes wonder whether the integrated circuit manufacturers do not so much *make* the little blighters, as *breed* them! I must confess to having taken these suspicions a little further than reasonably necessary, because I once imprisoned a couple of 741 op-amps in a matchbox, just to see what would happen.

Well, to cut a long story short, I never actually caught them at it, and not so much as a bonny bouncing quad two i/p nand gate ever resulted, but I still have nagging doubts, and these have been aroused once more by a trio of new devices from Sprague.

If I'm wrong and Sprague actually do *make* i.c.s, they're doing a grand job, because these three new chips form a closeknit little family which promises to make audio amplifier problems a thing of the past. The type numbers are **ULN 2275**, **ULN 2277** and **ULX 2276**, and each of these handy little 14-pin i.c.s contains not one, but two audio amplifiers, each with an impressive specification.

You may think that putting two audio amplifiers in one d.i.l. package will mean that their output power capability must be very restricted, but this certainly isn't so. The 2275 gives a creditable 1W per channel of continuous power over a supply voltage range of from 9 to 20V, for only 28mV of signal input. The 2277 is even more powerful at 2W per channel, and the 2276 (which is still undergoing evaluation tests) promises an incredible 4W each side, making it a definite candidate for the *Guinness Book of Records!*

These powerful devices don't necessarily need special heatsinks either, since they can dissipate the heat, via their tabs, to the copper areas of the p.c.b. A trio of real thoroughbreds in fact!

PHONE TONES

You may remember that I recently featured the Plessey MP 9100 dial code generator (October '75), which is intended for use with Strowger-type telephone systems. In the MP 9100, dialled digits are sent out as a series of slow on/off pulses to activate stepping uniselectors at the exchange. This is not the only

system in use for telephone dialling, and a new chip from General Instrument, the **AY-3-9400**, demonstrates the other point of view.

Like the MP 9100, the AY-3-9400 is intended for use with push-button telephones, but instead of sending out a string of pulses for each digit, the new chip sends out a pair of m.f. tones. The push buttons on the telephone instrument are arranged as a key-pad, or matrix, and when a single key is depressed, two signals, one for the row position and one for the column position, are generated. If the key-pad has 4-rows and 3-columns (i.e. 12 keys) it is possible to allocate a unique tone pair from seven basic tone generators.

The AY-3-9400 generates seven accurate tone frequencies between 695-28Hz and 1,631-78Hz, and is controlled by a 559-7KHz ceramic resonator (or crystal) external to the chip. The chip is made with an *n*-channel ion-implant m.o.s. technology which ensures operation from a single low voltage supply.

The operation of the circuitry is mainly digital, consisting of some keyboard logic, two programmable prescaler counters to generate the necessary frequencies from the main clock oscillator, and two digital to analogue converters to give a fair approximation of a sinewave for each m.f. tone.

Now, I don't suppose that anyone is thinking of going into competition with the Post Office by providing an alternative telephone system, but this new device could be used for many other things besides. An obvious use is as a remote control tone generator for an ultrasonic or radio link, perhaps to control a T.V. set or model.

The 9400 comes in a 14-pin package, but if seven tones and 12 key positions aren't sufficient for your needs, there is the **9410** version which handles 16 keys with eight tones and comes in a 16-pin pack.

BIG SHIFT

If you dabble in t.t.l. logic (and who doesn't) you may have occasionally cast envious glances at some of the logic power available in the more exotic m.o.s. technology. If you

have ever wanted a long shift register, for example, the prospects for building it with t.t.l. are a bit bleak, since an eight bit device is about the biggest available.

With *p*-m.o.s. on the other hand, registers very much longer are commonly available, but unfortunately they don't help much, because to put a *p*-m.o.s. register in a t.t.l. system often means extra power supplies and special interface circuits which makes the m.o.s. solution about as broad as it is long (no pun intended!).

Thanks to the relatively new *n*-m.o.s. technology, however, the mixing of m.o.s. power with t.t.l. versatility has now become a real possibility, even for small amateur projects. Take, for example, the SGS-ATES **M142** quad 80-bit static shift register (yes, that's right, *four* 80-bit shift registers in a 16-pin d.i.l.). This common or garden *n*-m.o.s. device is fully t.t.l. compatible on all inputs and outputs, and even works from the standard +5V t.t.l. supply rail. The data in the register can remain static if required, or can be shifted at a clock rate of up to 3MHz.

Four 80-bit registers in parallel could be used to store 80-b.c.d. digits (0-9) and so could provide a powerful but simple data storage system for many kinds of digital projects.

QUAD COUPLER

Opto-couplers consist of an i.e.d. in close proximity to a photo diode or transistor, the whole thing being sealed in a small plastic or hermetic package. Input signals to the i.e.d. cause a light output which is sensed by the photo diode or transistor to produce an output. The name of the game is isolation, and by using light as the coupling medium, isolation resistances of 100 megohms and breakdown voltages of over 1,000V can be achieved.

All this is history, but Litronix have recently introduced a new i.c., the **ILQ74**, which consists of no fewer than four opto-couplers in a single 16-pin d.i.l.! Applications include thyristor triggering, high voltage stabilised power supplies and signal isolation circuits, with inputs and outputs being t.t.l. compatible.

NEXT MONTH

CAR/CARAVAN CLOCK

A crystal controlled clock with combined independent journey timer. Jumbo size six digit display with automatic intensity control makes for easy readability. An alarm facility is included



SOIL SATURATION METER...

With food prices causing more and more people to embark on the "grow your own" course, this simple device is bound to find popularity with gardeners trying to get that little extra from their plot or greenhouse




LIGHT COUPLED REV COUNTER...

Measures the propeller speed of a model aircraft engine without connection. Ideal for getting peak performance from fuel mixtures



Programmable WASH/WIPE CONTROLLER

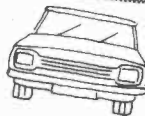A car windscreen wiper delay unit with a difference. As well as the standard "variwipe" control, a programmable wash-wipe facility is also incorporated



Plus... Using CMOS Digital I.Cs.

PART 2 Continues the description of the basic elements used in this important technology

PRACTICAL ELECTRONICS

FEBRUARY ISSUE ON SALE JANUARY 9, 1976

TO AVOID DISAPPOINTMENT PLACE A REGULAR ORDER WITH YOUR NEWSAGENT—NOW!

Now...the most exciting Sinclair kit ever


The Black Watch kit

At £17.95, it's

★ **practical** – easily built by anyone in an evening's straightforward assembly.

★ **complete** – right down to strap and batteries.

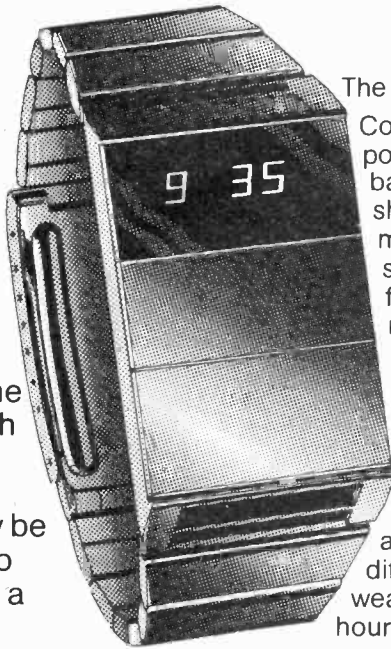★ **guaranteed.** A correctly-assembled watch is guaranteed for a year. It works as soon as you put the batteries in. On a built watch we guarantee an accuracy within a second a day – but building it yourself you may be able to adjust the trimmer to achieve an accuracy within a second a week.



The Black Watch by Sinclair is unique. Controlled by a quartz crystal... powered by two hearing aid batteries... using bright red LEDs to show hours and minutes and minutes and seconds... it's also styled in the cool prestige Sinclair fashion: no knobs, no buttons, no flash.

The Black Watch kit is unique, too. It's rational – Sinclair have reduced the separate components to just four.

It's simple – anybody who can use a soldering iron can assemble a Black Watch without difficulty. From opening the kit to wearing the watch is a couple of hours' work.




The special features of The Black Watch

Smooth, chunky, matt-black case, with black strap. (Black stainless-steel bracelet available as extra – see order form.)

Large, bright, red display – easily read at night.

Touch-and-see case – no unprofessional buttons.

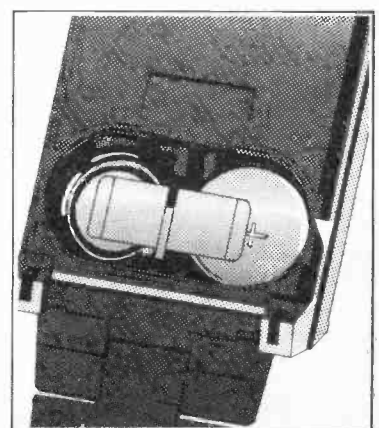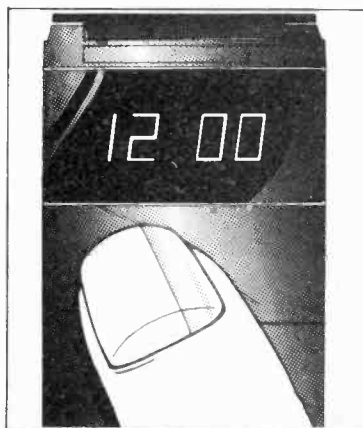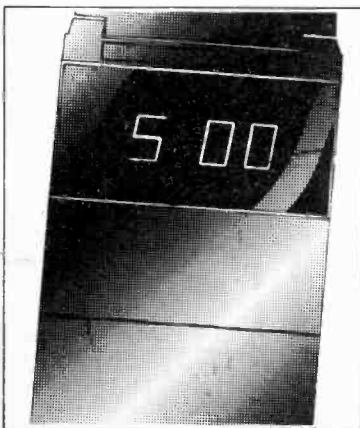Runs on two hearing-aid batteries (supplied). Change your batteries yourself – no expensive jeweller's service.



The Black Watch—using the unique Sinclair-designed state-of-the-art IC.

The chip...

The heart of the Black Watch is a unique IC designed by Sinclair and custom-built for them using state-of-the-art technology—integrated injection logic.

This chip of silicon measures only 3 mm x 3 mm and contains over 2000 transistors. The circuit includes

- a) reference oscillator
- b) divider chain
- c) decoder circuits
- d) display inhibit circuits
- e) display driving circuits.

The chip is totally designed and manufactured in the UK, and is the first design to incorporate all circuitry for a digital watch on a single chip.

...and how it works


A crystal-controlled reference is used to drive a chain of 15 binary dividers which reduce the frequency from 32,768 Hz to 1 Hz. This accurate signal is then counted into units of seconds, minutes, and hours, and on request the stored information is processed by the decoders and display drivers to feed the four 7-segment LED displays. When the display is not in operation, special power-saving circuits on the chip reduce current consumption to only a few microamps.

Complete kit £17.95!

The kit contains

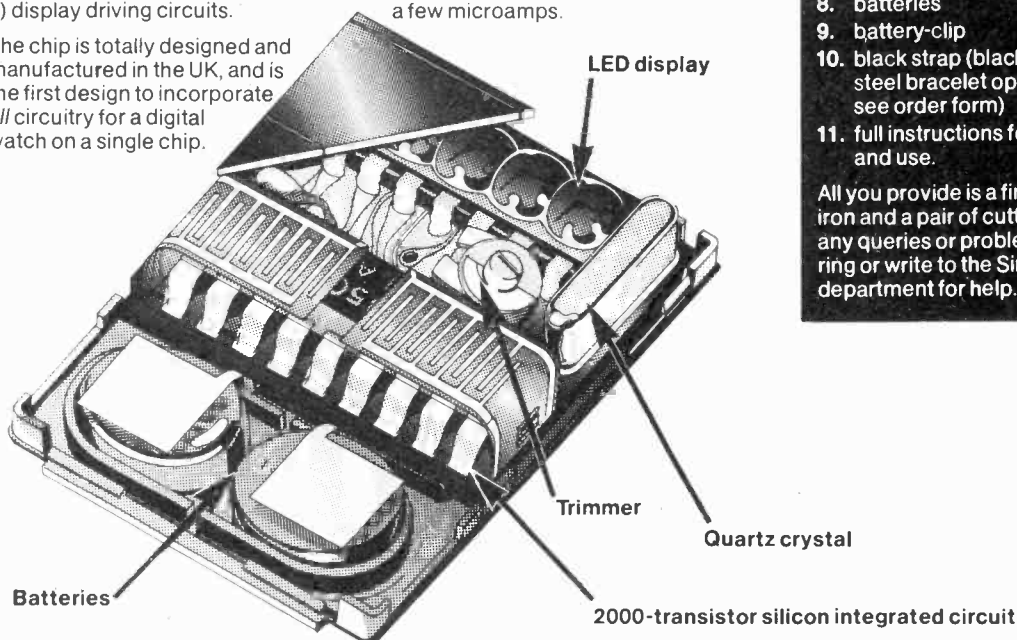1. printed circuit board
2. unique Sinclair-designed IC
3. encapsulated quartz crystal
4. trimmer
5. capacitor
6. LED display
7. 2-part case with window in position
8. batteries
9. battery-clip
10. black strap (black stainless-steel bracelet optional extra—see order form)
11. full instructions for building and use.

All you provide is a fine soldering iron and a pair of cutters. If you've any queries or problems in building, ring or write to the Sinclair service department for help.



Take advantage of this no-risks, money-back offer today!

The Sinclair Black Watch is fully guaranteed. Return your kit within 10 days and we'll refund your money without question. All parts are tested and checked before despatch—and correctly-assembled watches are guaranteed for one year. Simply fill in the FREEPOST order form and post it—today!

Price in kit form: £17.95 (inc. black strap, VAT, p&p).

sinclair

Sinclair Radionics Ltd,
London Road, St Ives,
Huntingdon, Cambs., PE17 4HJ.
Tel: St Ives (0480) 64646.

Reg. no: 699483 England. VAT Reg. no: 213817088.

To: Sinclair Radionics Ltd, FREEPOST, St Ives, Huntingdon, Cambs., PE17 4BR.

Please send me	Total £	
..... (qty) Sinclair Black Watch kit(s) at £17.95 (inc. black strap, VAT, p&p).	* I enclose cheque for £..... made out to Sinclair Radionics Ltd and crossed.
..... (qty) black stainless-steel bracelet(s) at £2.00 (inc. VAT, p&p).	* Please debit my *Barclaycard/Access/American Express account number
	

Name _____

Address _____


P. E. 1

Please print. FREEPOST—no stamp required.

*Delete as required

DIGITAL LOGIC CHECKER

By D. COLES

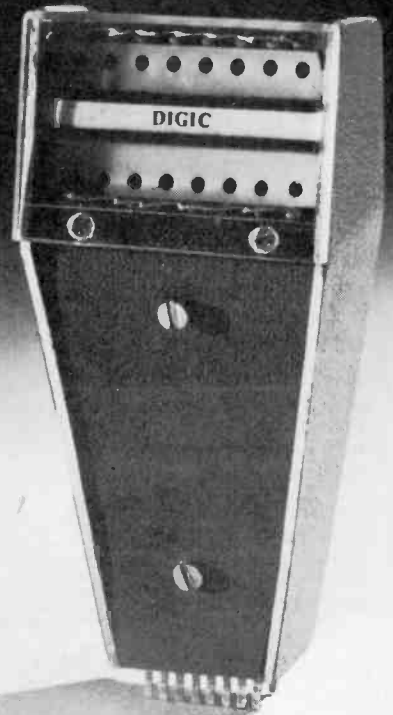

SEVERAL devices have recently appeared on the market which display the logic conditions of an i.c. upon a matrix of light emitting diodes. These devices cost about £30 and while they are of sophisticated design, they are out of the reach of many amateurs' pockets.

The device described below can be built for under £4 and, in the author's opinion, the lack of sophistication is more than balanced by the difference in cost.

Power for the logic checker is taken directly from the i.c. under test so that separate batteries are not required. High and low logic levels and the power supply are indicated by appropriate l.e.d.s being activated; the l.e.d. position indicating the i.c. pin in question. The checker can be used to display the logic states of any integrated circuit having up to 16 dual-in-line pins at a 0.1in pitch.

THE CIRCUIT

The circuit consists of a pair of electrical pathways between each pin connection and a common rail (see Fig. 1). Only one of each pair is open to current, the other being blocked by a diode or light emitting diode.

In order to demonstrate the circuit function in greater detail, the following assumptions are made for Fig. 1: pin 16 is at logic level 1, pin 15 is at logic level zero and pin 1 is ground or negative supply.

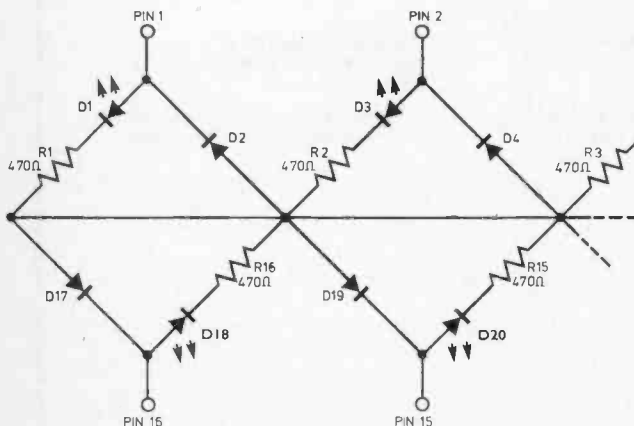


Fig. 1. Four of the 16 networks needed

COMPONENTS . . .

Resistors

R1-R16 470Ω (16 off)
All 5% 1/8 watt carbon

Diodes

D1-D3-D5-D7-D9-D11-D13-D15-D18-D20-D22-D24-D26-D28-D30-D32 All RL54 l.e.d.s (A. Marshall Ltd.)
D2-D4-D6-D8-D10-D12-D14-D16-D17-D19-D21-D23-D25-D27-D29-D31 All OA200

Miscellaneous


Veroboard, edge connector contacts, plastic case, scrap perspex sheet

Conventional current flow will proceed from pin 16 to pin 1 via D18, R16 and D2; its passage along the alternate route being blocked by D17 and D1. D18 will be activated by the passage of current and the positive voltage on pin 16 will be indicated. Resistor R16 limits the current flowing in D18. In practice, some current will also flow from pin 16 to pin 15 via D18, R16 and D19.

Pin 15 is assumed to be at logic zero and will thus have a voltage of between zero and 0.4 volts; this is too low a voltage to overcome the forward voltage threshold of the l.e.d. and diode which lie in its path to ground. (In exceptional cases, the two thresholds may be overcome and a small but insignificant current will flow.)

In considering all 16 circuits networks, some current will flow between pins at logic level 1 and those at logic level zero as well as the ground pin. However, these do not upset the functioning of the circuit.

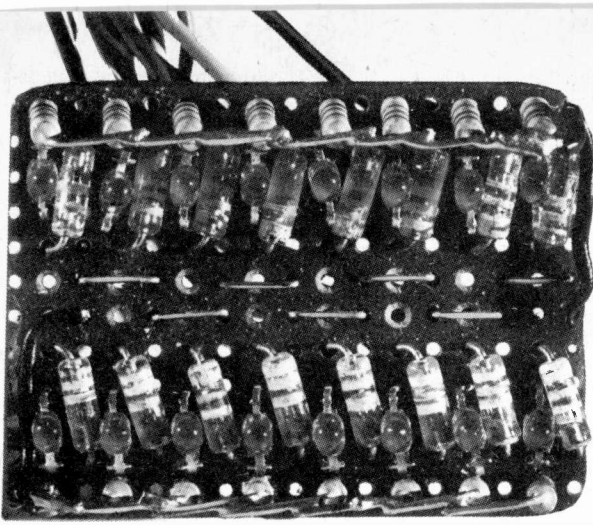The positive supply pin is treated as a pin at logic level 1 and is also displayed by an illuminated l.e.d. in the appropriate position.



CIRCUIT AND DISPLAY BOARD

A 16-by 12 hole piece of Veroboard of 0.1in pitch is used for the circuit. Layout and the positions of the cuts in the copper strips are shown in Fig. 2. The resistors are mounted first followed by the diodes and, finally, the light emitting diodes. Care should be taken to avoid overheating the diodes and, particularly the l.e.d.s which are very small and therefore particularly sensitive. The resistors are mounted vertically while the diodes are soldered in a horizontal position. The l.e.d.s are mounted so that the plastic lens part is above the diodes and about on a level with the top edge of the resistors.

THE SPRING CONTACT BOARD

A second piece of Veroboard is used for the base. The pitch is, again, 0.1in; with ten copper strips and six rows of holes. The outer two copper strips are scraped off with a sharp knife. The 16 spring contacts are fashioned from the individual contacts from an edge connector and soldered into the Veroboard, slight widening of the Veroboard holes with a knife will allow the contacts to be eased in without their bending. The sequence of operations for making the contacts is shown in Fig. 2; the gold plated contacts make excellent prongs for this project and, being individually sprung, they allow all 16 contacts to slide tightly over the i.c. pins.

It is important that the tips of all the contacts are arranged at the same height, alterations to the angle at which each contact is soldered can be made by bending each one slightly until they are all in line.

Flying leads of thin stranded wire are used to connect the two Veroboards together. In both cases the leads are attached on the copper side of the Veroboard.

Fourteen to 16 pin i.c. test clips are available from Guest Electronic Distribution Ltd. While this component would make a much more professional job of the i.c. contact assembly, the cost would increase by over 50 per cent and the case would require a different design.

TESTING

A four and a half volt battery, or other power source, can be used for testing. Briefly touch the battery contacts against any of the spring contacts and, wherever the positive supply touches a contact, the appropriate l.e.d. should light. Faults may be due to

crossed leads, damaged l.e.d.s or diodes and l.e.d.s being connected in reverse.

THE CASE

The shape of the case has been chosen to provide a convenient hand grip and a small sized base. The small base and tapering shape allow it to be inserted onto an in-circuit i.c. without interfering with neighbouring components.

Aluminium was chosen as the material but, because of the small size of the case, it is difficult to bend a single piece of aluminium at the necessary points. In order to avoid this difficulty, four separate pieces of aluminium were cut, bent and glued together with Araldite, the areas of metal covered by the glue being well roughened to give good adhesion. Fig. 2 shows the separate aluminium pieces and their assembly into a somewhat coffin-shaped box.

The display area where the l.e.d.s are viewed is covered by thin Perspex. Araldite is not recommended for securing Perspex and Evostik was used for this operation.

The small base end of the case is cut to provide a hole for the spring contacts to protrude through and this piece of Veroboard is secured into the base with generous amounts of Araldite. The copper strip side of the Veroboard is also smeared with Araldite to reinforce the soldered joints of the spring contacts.

The circuit and display board is fitted behind the Perspex window and wedged into position with small scraps of foam plastic. It is advisable to insulate the interior of the case with insulation tape to ensure that accidental shorting of the display board does not occur.

USING THE LOGIC CHECKER


In use, the spring contacts are pushed over the operating i.c. to be tested, care being taken to ensure that the spring contacts do not bridge the small gaps between the i.c. pins.

The l.e.d.s on the display board will now glow and indicate the positive supply pin and those pins which are at logic level 1.

The constructor should be warned that where i.c.s are being used with capacitors, for instance, where gates are cross coupled to form an astable multivibrator, the checker will disturb and may freeze the circuit action. This is because alternative charge/discharge paths are set up through the checker which will significantly alter the time constants in the circuit.

At a nominal supply voltage of 5 volts, each l.e.d. is limited to a current of about 10.5mA by the series resistor. The l.e.d.s are quoted as a 40mA device but the reduced current is still sufficient to provide a light output which can be easily seen in most conditions. Most d.i.l. i.c. devices can provide a logic 1 output of 160mA, quite sufficient to power the checker. If an operating i.c. is already approaching its maximum fan-out (usually 10) it is a wise precaution to disconnect some of the devices being fed from the well loaded gate outputs before using the checker.

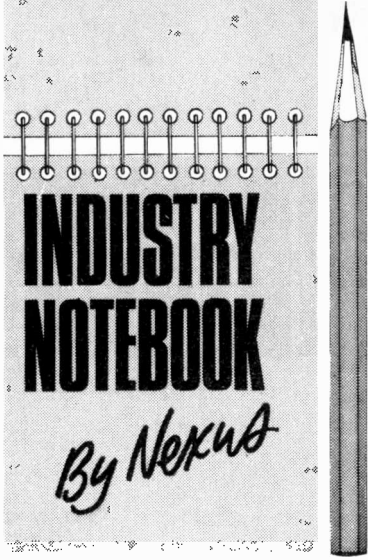If two sewing pins are cut to about 5mm length, heated and pushed into the Perspex window at either end, these can be used for attaching a piece of card or stiff paper. The block diagram of the i.c. can be sketched on the card with the input/output lines to each gate drawn to each l.e.d. The logic levels for each gate can then be seen with ease. ★



INDUSTRY NOTEBOOK

By Nexus

OUTLOOK '76

The Autumn season of electronic exhibitions and a few company reports and news items gave forecasters for '76 little on which to base firm conclusions because the general economic outlook was, and is, filled with uncertainties.

Consumer electronics is still in the doldrums. Colour TV deliveries last August, for example, were 36 per cent down on the previous August. And, because of this, component suppliers really suffered. AB Electronic Components reported a heavy drop in volume of components supplied although inflation kept turnover at £11.15 million compared with £12.05 million a year earlier.

Profits were down from a pre-tax figure of £908,063 to £379,205 reflecting lower margins. On the other hand AB went ahead with a heavy investment programme showing confidence in the future but at the same time stated that more emphasis is being placed on business outside the area of consumer products.

Erie Electronics also suffered from the consumer slump and the sale of the UK operation to ITT Components Group Europe should be established, according to industry sources, by early in the New Year if not before.

Decca's big interests in TV, radio, audio and records, showed a decline in pre-tax profits from £10.9 million to £6.8 million but the balance was redressed by the radar, navigation, and other professional capital goods output which showed an increase in profit from £6.7 million to £9.1 million.

Fortunate indeed are those companies strong in capital goods. EMI Electronics has to thank its world-beating EMI-Scanner X-ray

equipment for a doubling in profit from £7 million to £14.6 million. The total order book for these machines has now topped 300, worth some £60 million. And as there is no competition there is a handsome profit on every delivery. Strange to say, this project was nearly abandoned at one stage.

If we look across the Atlantic, the Wescon show in San Francisco last September was full of optimism with strong support for the view that business was on the upturn although some cautious opinions were expressed that it would be a long haul and positive results may not be apparent before mid-'76. European electronics would follow on, it was said, with a time lag of seven to eight months.

In Britain, the Internecon/UK '75 show held in October was the biggest ever and one of the busiest. The show concentrates on plant and equipment for electronics manufacture and there was plenty of evidence that manufacturers are investing now for future production. Perhaps not as heavily as they should in some cases, but there was movement and that's better than nothing.

The immediate outlook, then, is for consumer electronics to remain depressed but for capital goods to do well, especially in the export market where, with a devalued pound, British goods are very competitive.

MOBILES AND PAGING

Every cloud has a silver lining. Vandalism and terrorism in London's famous double-decker bus fleet has brought Redifon Telecommunications back into mobile radio. The company has an initial order for 200 radiotelephones to enable bus crews to call for help if need be.

Apart from ordinary two-way telephony there will be a number of strategically sited emergency buttons on the bus which actuate an auto-alarm. But later, the sets will also be used for data transmission as part of a new scheme being introduced for en-route control of the fleet.

Pocket radio paging is to go ahead in the London area under a Post Office scheme due to start next Spring. This follows on from field trials in the Reading area. The Post Office expects to get 20,000 subscribers initially and each one, of course, will need to be supplied with a pocket "bleeper" which will respond to a radio signal personally coded.

On the Reading trials the Post Office used pagers manufactured by Motorola. But for the London scheme they have ordered 10,000 units from the British company Multitone at a reported contract price of £1 million.

The Multitone equipment has already been proved in service in wide area paging systems in Toronto and Ottawa. One of its features is a muting switch which cuts out the "bleep" and stores the signal in a memory circuit. The user can access the memory to see if he has been paged when it is convenient for him to do so.

The use of the mobile radiotelephone continues its upward growth almost unnoticed. In 1971 there were 90,000 licences issued. Today there are some 200,000 mobiles operating in the UK including a staggering figure of 50,000 within a 50-mile radius of Central London.

REMCON

A little-publicised sector of industry emerged into prominence in November with an international gathering of industrial telemetry experts for a three-day conference in London. The event was REMCON with a strong panel of speakers led by conference chairman Professor H. C. A. Hankins of the University of Manchester Institute of Science and Technology.

The big users of remote control and supervisory equipment are water, gas and electricity authorities and petrochemical companies, with many of the larger systems now being controlled by computer. I hope to comment more fully on this event in a future issue.


DEFENCE SCENE

Minister of Defence, Mr Roy Mason, is hinting hard at new methods of military procurement. His defence budget is under attack from the left wing of his party and he is now telling industry that he must buy in the cheapest market, even if this means shopping overseas. At the same time, his political colleagues are urging the nation to buy British. The Minister's posture on this occasion was clearly defensive following the cancellation of two British missile projects in favour of U.S. missiles.

Apart from any change in outright purchasing policy there also seems to be a move away from Ministry-sponsored R and D. There is a new tendency to look at PV (private venture) projects for military use and so the old-style development contracts which have kept many a laboratory in funds may soon be a thing of the past. If this is the case and risk capital goes on speculative development, it is bound to be reflected in the final product price and this, in turn, could affect defence exports.

Of course, Ministers don't always say what they mean, or mean what they say, but it is clear that the defence scene will become more intensely competitive.

AUDIO

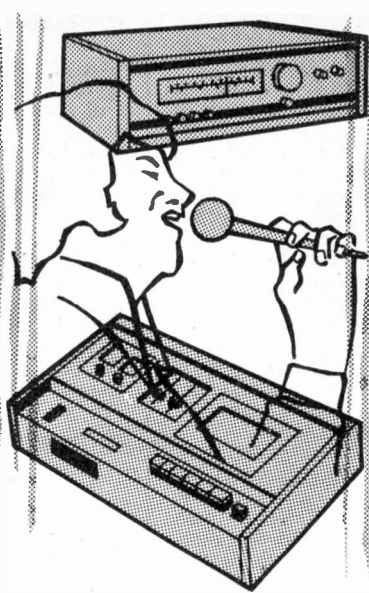

COMPRESSOR

By S. WHITT

An easy-to-build device for the home recording enthusiast

THIS simple audio compressor can be built simply and cheaply, and probably with components from one's spares box. It will compensate for fading signals in a radio, prevent overmodulation of a transmitter and will adjust to whispers or shouts into a microphone.

Its basic function is to maintain a relatively constant amplitude output over a varying range of input amplitudes. Although it will cope with several hundred millivolts input, smaller inputs cause less harmonic distortion (low enough for most applications).

CIRCUIT OPERATION

The circuit diagram of the compressor is shown in Fig. 1. The signal is first amplified by TR1 in the common emitter mode and then passed on to the next stage via C4. Large input signals cause a larger voltage to be induced in the secondary of T1. This voltage is rectified by D1 and reapplied as a negative-going d.c. voltage to the base of TR1, thus lowering the bias voltage and consequently lowering the gain.

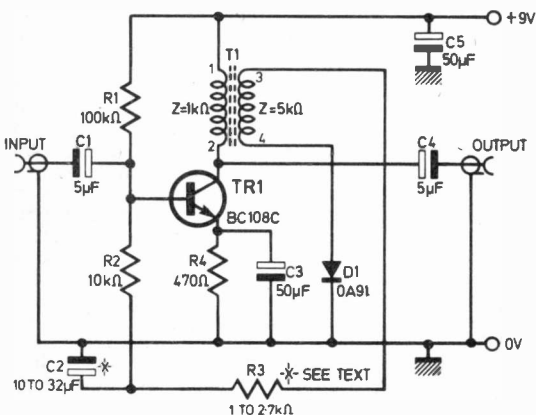


Fig. 1. Circuit diagram of the audio compressor

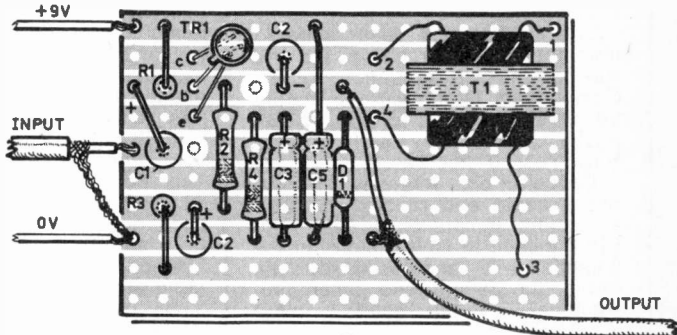


Fig. 2. Component layout and Veroboard cutting details

TIME CONSTANT

When a small signal is applied though, the gain of this stage rises after about 50ms (the time constant of C2R3). This time constant should maintain the gain between syllables of speech. It can, however, be easily altered to suit the application by varying either C2 or R3.

TRANSFORMER

There is much room for experimentation, especially with T1, which must be a step-up transformer and should have impedances approximately as shown. However, an unlabelled driver transformer from an old radio was found to work just as well.

CONSTRUCTION AND USE

The circuit was built on a small piece of Vero-board as shown in Fig. 2 and the layout is not at all critical.

The author found that when positioned directly after the volume control and before his headphones, the compressor all but eliminated fading in his receiver. It was also found to function well between a microphone and a tape recorder, compensating for varying voice levels and varying distances from the microphone.

ALTERATIONS

If too large an input signal is applied, the negative a.g.c. voltage can be high enough to cause TR1 to clip the signal. If R2 is increased to 120k Ω , apart from increasing the overall gain, it will allow higher input levels to be accommodated before clipping.

For small signals (such as microphone inputs) the original circuit could be used unaltered. A preset potentiometer (about 100k Ω) in series with R2 would make the compressor more versatile, however. ★

COMPONENTS . . .

Resistors

- R1 100k Ω
- R2 10k Ω
- R3 1k Ω -2.7k Ω (see text)
- R4 470 Ω
- All resistors 10% \pm W

Capacitors

- C1 5 μ F elect.
- C2 10 μ F-32 μ F elect. (see text)
- C3 50 μ F elect.
- C4 5 μ F elect.
- C5 50 μ F elect.
- All capacitors 12V

Diode

- D1 OA91

Transformer

- T1 See text

Transistors

- TR1 BC108, BC107 or other npn silicon (e.g. 2N2926, 2N2925, etc.)

Miscellaneous

- Vero-board (see Fig. 2). Phono socket, case



FREE Brochure on New KITS

Whether professional,
student, teacher or amateur,
the field of electronics can open
up a new world for you.

Send 15p to cover postage



CROFTON don't just sell kits, we offer you a technical back up service to ensure your success

The following is a selection of some of the more popular kits -


- ★ Mullard CCTV Camera
- ★ PE CCTV Camera
- ★ PE Rondo Quadraphonic Four Channel Sound (Designer Approved)
- ★ Electronic Ignition
- ★ Sound Operated Flash
- ★ PW Tele-Tennis Game
- ★ UHF Modulator
- ★ Bench Power Supply
- ★ Wobbulator
- ★ All ETI Top Projects
- ★ Many of the Elektor Projects

NOTE PCBs for most published projects available to order

CROFTON ELECTRONICS LTD

Dept E 124 Colne Road, Twickenham, Middx O1 898 1569

Test Equipment

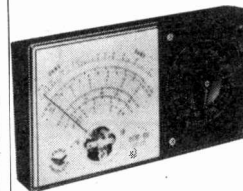

Multimeters


The Eagle range of multimeters covers every possible need of the electrical or electronic engineer. They cost from about £6 to £58 (inc V.A.T.). There's at least one which suits your job precisely.

We have a lot of other test equipment too. Send the coupon and we'll send you our complete catalogue.

Please send me details of all your test equipment

NAME

ADDRESS

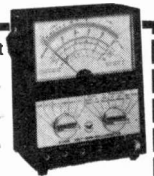

Eagle International Ltd., Precision Centre, Heather Park Drive, Wembley HA0 1SU
Tel(01)-902 8832

Eagle

PE

RANDOM TONE GENERATOR

By W. G. ROSS

THE Random Tone Generator was primarily designed as an electronic door bell which would produce an endless variety of "tunes" at the press of the door switch. Thus the boredom of continual repetition of a single tune along with the difficulty in selection of a suitable tune are removed. However, it is thought that the random tone generator may provide an aid to musical composition as well as providing amusement.

In operation it produces a train of notes which is seldom duplicated and musical interest is maintained by not only changes in pitch but in note duration.

U.J.T. CLOCKS

The circuit (Fig. 1) uses two unijunction transistors, TR1 and TR2, as relaxation oscillators producing frequencies of approximately 50kHz and 2Hz respectively. The 50kHz pulses at the base 1 of TR1 are used to clock a decade counter type SN7490. The four output lines (A, B, C and D) are fed to a quad latch where the binary information is periodically sampled and stored. The sampling rate is determined by the oscillation frequency of TR2 and may be varied by means of VR1.


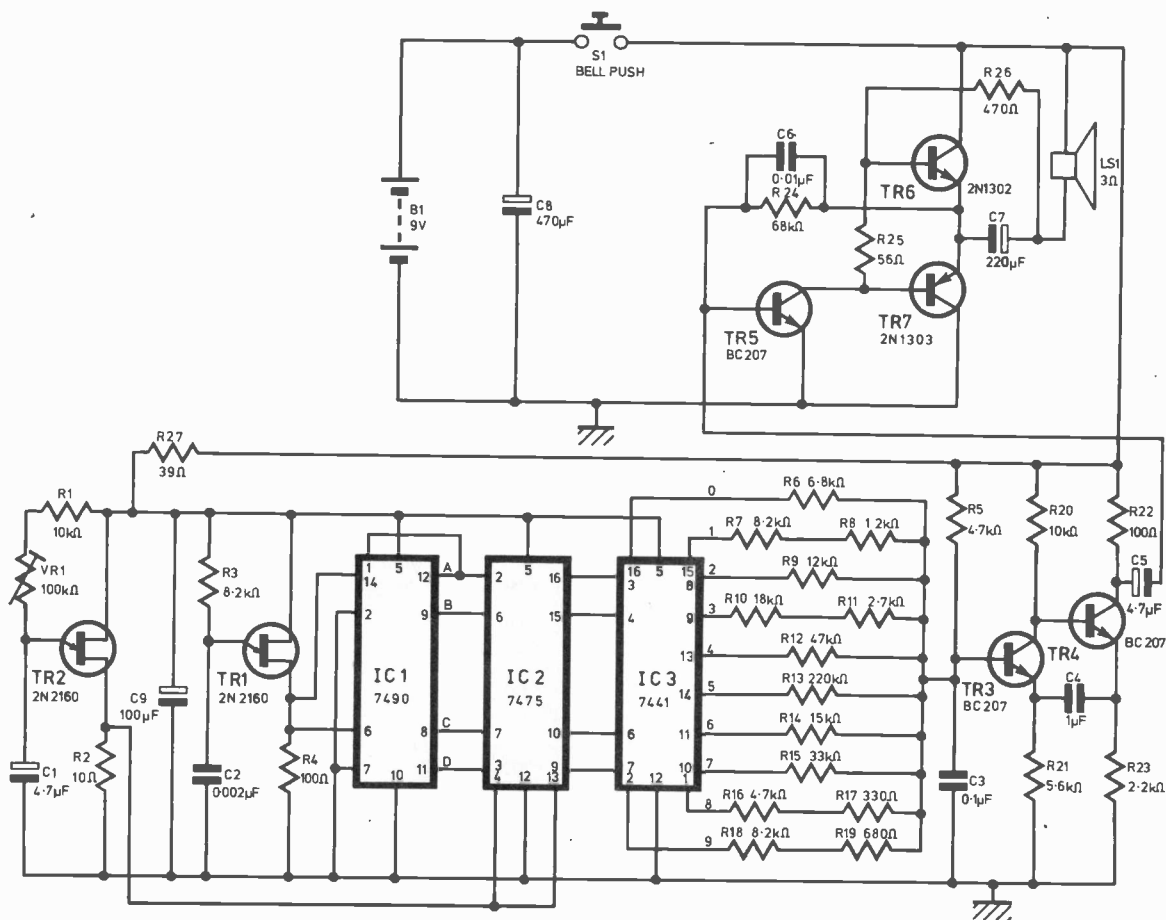


Fig. 1. Circuit diagram of Random Tone Generator

Decoding of the stored binary information is performed by a Nixie tube decoder/driver type SN7441 which provides 10 open-collector outputs. The output transistors of the decoder conduct randomly because of the wide frequency difference between the two unijunction oscillators and the temperature dependence of their frequency determining components.

An emitter coupled multivibrator provides a harmonically rich tone from TR4 collector, the frequency of which can be altered by variation of TR3 base voltage. This is achieved by using a potential divider comprising R5 and R6 to R19, the latter being selected randomly by the decoder. The values of R6 to R19 are chosen such that the notes generated correspond approximately to the musical scale over one octave.

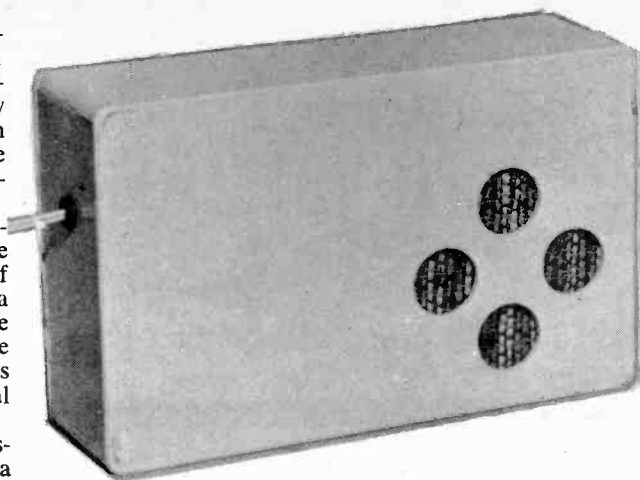Audio amplification is provided by a simple class-B push-pull amplifier, TR5, TR6, TR7, driving a 3 ohm speaker. The unit is powered by a 9 volt battery, the 5 volt supply for the integrated circuits being obtained via resistor R27.



Generator housing

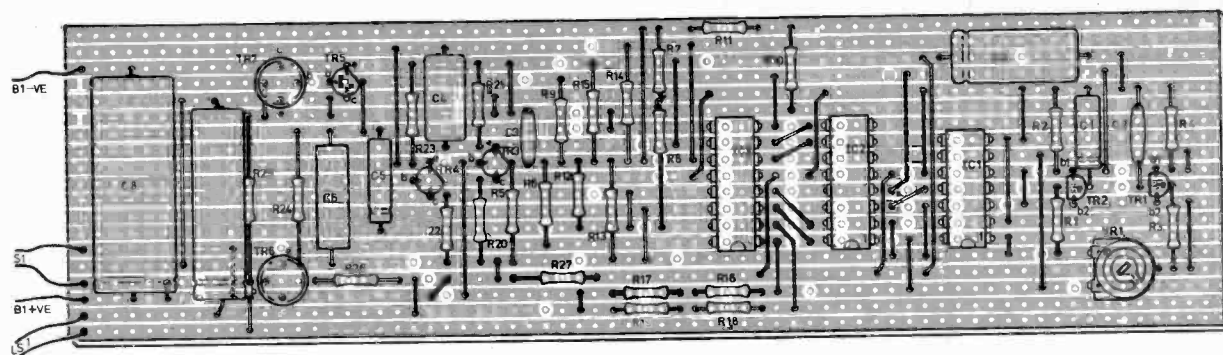


Fig. 2. Component layout and wiring details

COMPONENTS . . .

Resistors

R1	10k Ω	R14	15k Ω
R2	10 Ω	R15	33k Ω
R3	8.2k Ω	R16	4.7k Ω
R4	100 Ω	R17	330 Ω
R5	4.7k Ω	R18	8.2k Ω
R6	6.8k Ω	R19	680 Ω
R7	8.2k Ω	R20	10k Ω
R8	1.2k Ω	R21	5.6k Ω
R9	12k Ω	R22	100 Ω
R10	18k Ω	R23	2.2k Ω
R11	2.7k Ω	R24	68k Ω
R12	47k Ω	R25	56 Ω
R13	220k Ω	R26	470 Ω

All $\frac{1}{2}$ W, 10% carbon

Capacitors

C1	4.7 μ F elect. 63V
C2	0.002 μ F
C3	0.1 μ F
C4	1 μ F polyester
C5	4.7 μ F elect. 63V

C6	0.01 μ F
C7	220 μ F elect. 25V
C8	470 μ F elect. 25V
C9	100 μ F elect. 25V

Potentiometer

VR1 100k Ω skeleton preset

Transistors


TR1-TR2	2N2160 (2 off)
TR3-TR5	BC207 (3 off)
TR6	2N1302
TR7	2N1303

Integrated Circuits

IC1	SN7490
IC2	SN7475
IC3	SN7441

Miscellaneous

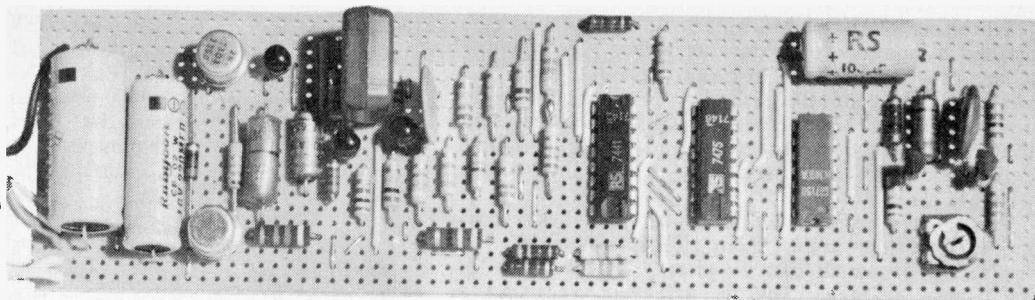S1—Push switch, LS1-3 Ω 3in speaker, Veroboard $7\frac{3}{8}$ in (188mm) \times $4\frac{1}{8}$ (119mm) \times $2\frac{5}{8}$ in (54 mm).




CONSTRUCTION

All the components, with the exception of the battery and speaker, are soldered on to a single piece of 0.1in Veroboard. The prototype was built in a die-cast box which also contains the loudspeaker and battery. The Veroboard was cut to slot lengthwise into the box, as can be seen from the photograph. Soldering should be thoroughly inspected before power is applied as short circuits on adjacent copper tracks can cause some curious effects such as tone "hang-up" or no sound at all.

TESTING

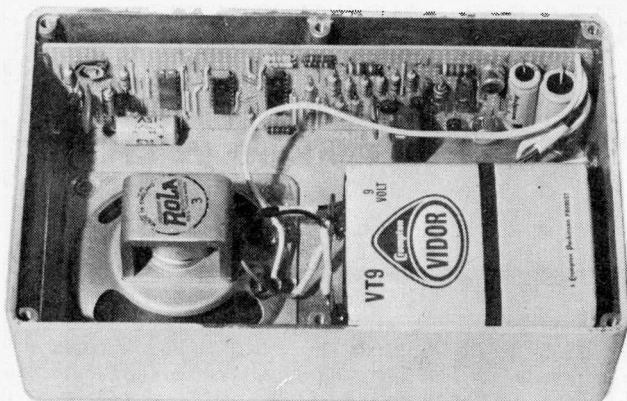With assembly and inspection completed VR1 wiper should be adjusted to mid-range and power applied to the circuit. The Random Tone Generator should immediately start "composing" an endless train of note patterns. According to taste the rate can be varied by VR1. The frequency range of the output can be changed by altering the value of C4. ★



Interior layout for Generator

NEWS BRIEFS

Post Office Unveils Viewdata

A RADICALLY new telephone service, in which a wide range of information can be called up over the telephone and displayed quickly on an ordinary television set, is being planned by the Post Office.

Known as Viewdata, the service would be completely automatic, providing information at the touch of a button. Trials for the new system are due to start in January and a full public service could start in 1978-79.

With Viewdata, information on a wide range of subjects such as news, entertainment, holidays, job advertisements and commercial intelligence would be stored in a computer databank connected to the public telephone network. By having their telephone linked to their t.v. sets users would have access to the wide range of information services which Viewdata can provide. The user would control the entire service with a simple hand-held control unit.

To receive Viewdata information, users would first switch on the t.v. set and then call up the service over the phone by pressing a button on the control unit. They would not even have to lift the telephone receiver. Then, at another touch of the button, the Viewdata opening display (an index listing the subjects on which information is available) would appear on the t.v. screen. Following simple instructions displayed on the screen, users would select the information they wanted by pressing further buttons.

As an alternative to the telephone link to a domestic television, business users could have a purpose-made Viewdata terminal, with built-in controls and telephone.

MAIL BAG

The on-going increase in postal and telephone charges does not seem to have made any difference to our post bag or our telephone bell. Enquiries continue to flood in.

We find that there are two points we are constantly mentioning. In the first place we just cannot afford to reply to any *readers' letters*, particularly those not associated with projects we have published, unless they are accompanied by a *stamped addressed envelope*. Were we to undertake to do so our post bill would become astronomical.

We cannot deal with *technical enquiries by telephone*. Readers should write in, giving details of symptoms and perhaps some test point readings, when requesting technical help so that we can at least give the relevant author some idea of the problems involved.

Finally, whilst we normally supply details as to source of components in each project we do assume that the constructor refers to advertisements and has an awareness of general sources. Thus, where goods are generally available we do not specify a source. You could save the cost of a letter by reading the advertisement pages first.

AUDIO FAIR 75

By R. LAWRENCE

THE Audio Fair this year was rather smaller than in previous years, with a lot of companies not exhibiting. The largest stands at the Fair were taken for the most part by Japanese or foreign based firms and there was a distinctive lack of British representation.

It is difficult to guess the reasons behind this, but some say that the basic character of the Fair has altered and perhaps moved from the connoisseur to the consumer market, where electronic gadgetry is playing a greater and greater part.

Prices of equipments continue to boggle the mind and soar ever higher and higher. Sony have actually introduced a "Higher-Fi" range of equipment and both the equipment and the corresponding prices have to be heard to be believed (just one speaker in the top range costs £700).

VFETs

One or two new terms are likely to be added to the hi-fi buff's repertoire after visiting the show. VFET is one of these terms and this at present is found in the specifications of a couple of popular Japanese manufacturers. It stands for Vertical Field Effect Transistor. The f.e.t.s are being used in the output stages of the amplifiers where they are replacing transistors with their attendant crossover and biasing problems. Yamaha and Sony are the two major pioneers in this field.

It will be interesting to see how Quad's recently released "current-dumping" amplifier compares with them. (They have got around output stage problems by using novel circuit techniques.) Quad incidentally, were one of the British manufacturers not present at the show.

LINEAR PHASE

Another relatively new term heard at the Fair is "linear phase". This is not a new guitar effect but describes the operation of a new development in loudspeakers. Bang and Olufsen have hit upon a method of overcoming phase distortion—a rather nebulous quantity, the existence of which is apparently debatable. One of the effects of having no phase distortion is to enable speakers to reproduce square waves with minimum waveform distortion.


The system uses an extra drive unit known as a "Filler Driver" which operates in the crossover region of the base and mid-range units. The result is certainly a clean sounding speaker, whether or not it is attributable to the lack of phase distortion.

TURNTABLES


The vogue in turntables has moved from idler drive to belt drive in its time. The latest trend is to electronic speed control with direct drive to the turntable. A relatively new firm, Strathearn Audio Limited, have produced several models with these features. Their SMA2 turntable also has touch start, stop, and speed controls and is attractively styled in a sleek case with a tinted dust cover.

Strathearn is also shortly to introduce a new speaker which uses ribbon techniques. The sound quality is equivalent to if not better

The Sony "High-Fi" speakers

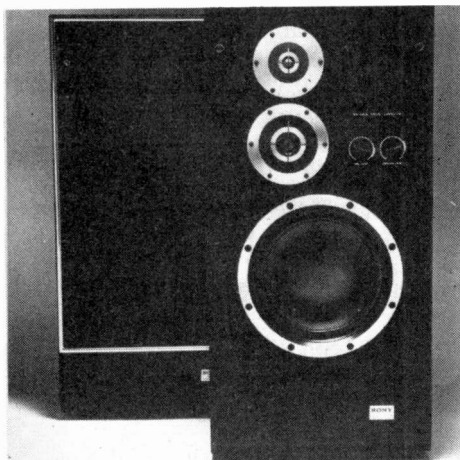

New "Linear Phase" range from B & O

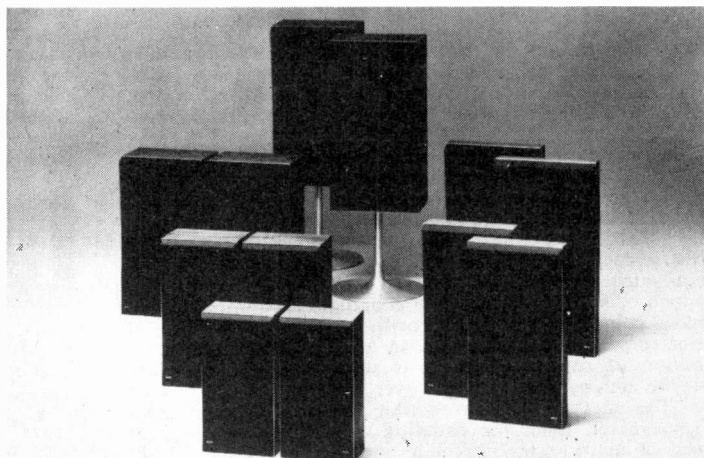

than that obtained with electrostatics and the speaker should have a very promising future.

Connoisseur, makers of the simple but very effective BD1 and BD2 turntables, have brought out a BD3 type which uses a servo-system for speed control. An external power source is also used to keep the possibilities of hum pick-up down.


SOUND THEATRE

One of the major centres of interest at the Fair was the Sound Theatre. A fully functioning modern recording studio was constructed using high quality equipment from a large number of top manufacturers. The BBC, LBC and Capital Radio broadcast from the theatre, and various impressive quad and stereo demonstrations also took place. Procuring and setting up the studio equipment was very competently co-ordinated by Ian Grant.


One of the lectures given in the Theatre was by Doug Shaw on synthesiser techniques. He demonstrated the Minisonic Mk 2, and the highlight of the lecture was a live performance with several musicians and minisonics, and despite a last minute time change his lecture was very well attended.



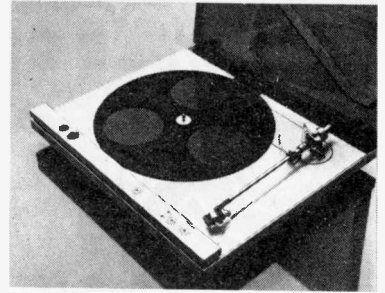Yamaha B1 amplifier with VFET output stage featured with their CT800 GL cassette deck



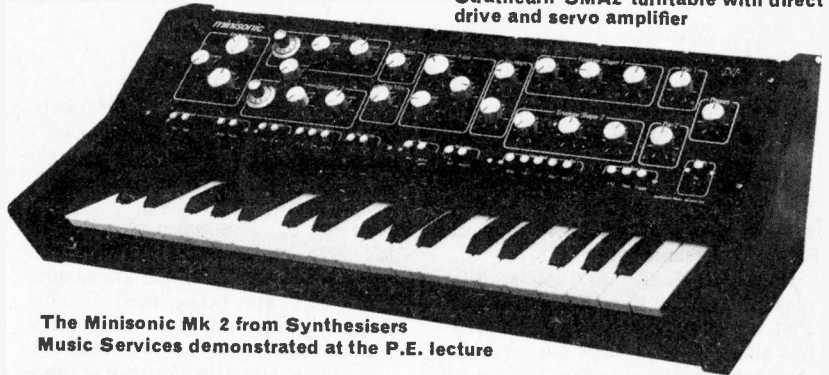Strathearn SMA2 turntable with direct drive and servo amplifier



The Minisonic Mk 2 from Synthesisers Music Services demonstrated at the P.E. lecture

CHANGE OF CHARACTER

It is interesting to note that where in the past there have been a multiplicity of technical lectures and demonstrations, this year's Fair saw very few. This tends to go along

with the observation that the Audio Fair is changing its character and pandering less and less to the connoisseur. Rather a pity, most will agree.

NEWS BRIEFS

HERE GOLDEN JUBILEE

THE Institution of Electronic and Radio Engineers celebrated its 50th anniversary during 1975. Last October, at the Annual General Meeting held in London, the Duke of Kent was installed as 25th President of the Institution.

In his inaugural address, the new President reviewed some of the developments in electronics.

"I don't think any of you need reminding of the great changes that have swept over the world during this last half century; changes which are without question the widest and deepest that have taken place in any equivalent period of history. That this extraordinary epoch of social, political and economic revolution should have coincided with the growth of the new science of electronics is not I am sure an accident—although attribution of cause and effect is something for historians of the 20th century to argue over, not me.

"The fact is that throughout this period, electronics has evolved from the fledgling of 'wireless' to a great and in many cases dominant industry spanning a huge field from communications to data management, transport to process control and medicine to entertainment. It was the belief in the great future that lay ahead that stirred our founding fathers—not that even they could

have foreseen what was to come—to establish our Institution, despite some cynicism from the older institutions of that day."


The President then went on to predict probable advances of the next 50 years in communications, domestic equipment, manufacture, aircraft safety and medicine. The last example holding promise of some very striking and praiseworthy achievements in alleviating the handicap of a few—"but if access and connection to the brain becomes a matter of standard practice, what dramatic developments might not ensue?" The possibility of contact with the brain via electromagnetic waves leads to the possibility of thought control, and this brings one on to some very tricky ground. The idea may be appalling—but it is essential that we recognize such possibilities even if for one reason or another they have eventually to be rejected.

POINTS ARISING


LIGHT MODULATION UNIT (October 1975)

The 40430 outline connections in Fig. 1 are incorrect. The MT1 and Gate terminals should be transposed.

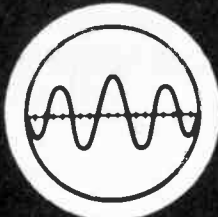In the circuit diagram MT1 and MT2 connections should also be transposed, i.e. MT2 terminals for CSR3 and 4 should be connected to L1 and L2 respectively.




TUAC

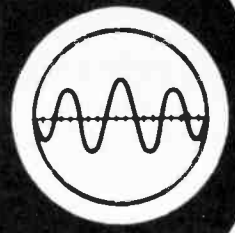

TRANSISTOR UNIVERSAL AMPLIFICATION CO. LTD
163 MITCHAM RD LONDON SW17 9PG 01-672 3137 9080

4 CHANNEL SOUND TO LIGHT SEQUENCER—4LSMI

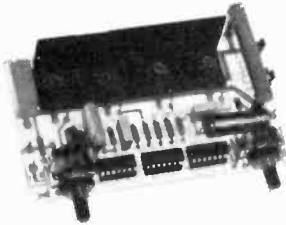


- RCA 8A Triacs
- 1000W per channel
- Fully suppressed and fused
- Switched master control for sound operation from μ W to 125W
- Speed control for fixed rate sequence from 8 per minute to 50 per second
- Full logic integrated circuitry with optical isolation for amplifier protection
- Full wave control
- 13 easy connections

Patents applied for

£22-00

3 CHANNEL LIGHT MODULATOR

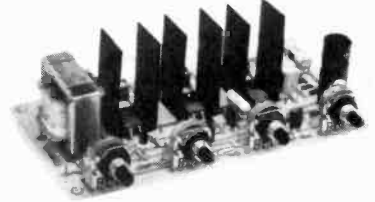- RCA 8A Triacs
- 1000W per channel
- Each channel fully suppressed and fused
- Master control to operate from 1W to 100W
- Full wave control
- 12 easy connections



£15-50

Single Channel Version 1500 Watts **£7-25**

ADD SEQUENCE AND DIMMING EFFECTS TO YOUR TUAC 3 CHANNEL LIGHT MODULATOR



- Speed Control
- 3 per min. to 10 per sec.
- Full logic integrated circuitry
- Dimmer control to each channel
- 9 easy connections

SEQUENCE DIMMER MODULE—3SDMI

£9-50




Dimmer control for each channel
7 easy connections

£4-25

DIMMER MODULE—LMDI

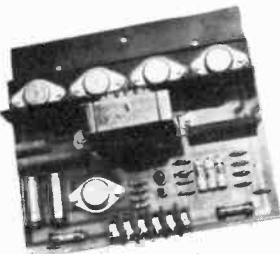TUAC POWER MODULES offering more power and quality than ever before




- 125 watts RMS continuous sine wave output
- 4 RCA 150 watt 15 amp output transistors

TP125
7 x 6 1/2 x 3in
£19-50


- Rugged layer wound driver transformer
- Short—Open—and Thermal overload protection
- Only 6 connections

Specifications on all power modules:
All output power ratings ± 0.5 dB; Output Impedance 8–15 ohms; THD at full power 2% typically 1%; Input sensitivity 60mV into 10k Ω ; Frequency response 20Hz–20kHz ± 2 dB; Hum and noise better than –70dB.

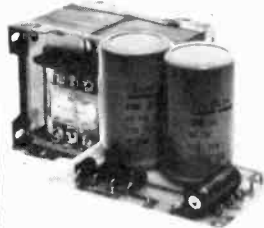Power supplies vacuum impregnated. Transformers with supply board incorporating pre-amp supply.



PS 125 ± 45 volts for TP125 **£12-25**
 PS 100 ± 43 volts for TL100 **£11-25**
 PS 60 ± 38 volts for TL60 **£10-00**
 PS 30 ± 25 volts for TL30 **£5-90**
 PSU 2 for supplying disco mixer **£4-75**

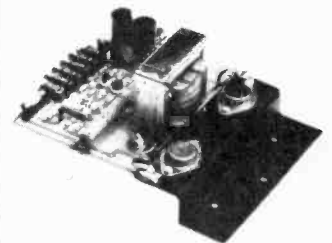

TL60

5 x 5 x 3in

- 60 watts RMS continuous sine wave output
- 2 RCA 110 watt 15 amp transistors

£12-50

TL100

5 x 5 x 3in

- 100 watts RMS continuous sine wave output
- 2 RCA 150 watt 15 amp transistors

£15-00

TUAC DISCOTHEQUE MIXER WITH AUTO FADE



Designed for the discerning D.J. of professional standard. Offering a vast variety of functions. Controls: Mic Vol; Tone, over-ride depth; auto/Manual Sw; Tape Vol; L & R Deck Faders; Deck Volume; Treble and Bass; H. Phon Vol Selector; Master Vol On/Off Sw. Max output 1 V RMS.
Specification: Deck Inputs—50mV into 1M Ω ; Deck Tone Controls—treble +20 –10dB at 12kHz; Bass +22 –15dB at 40Hz; Mic Input—200 ohms upwards, 2mV into 10k Ω ; Mic Tone Control—Total Variation Treble 15dB, Total Variation Bass 10dB; Tape Input—30mV into 47k Ω ; Power Requirements—30–50 volts at 50mA.

PANEL SIZE 18 x 4 1/2 in DEPTH 3in **£31-50**

HOW TO ORDER BY POST. Make cheques/P.O.s payable to TUAC LTD. (PE16), or quote Access/Barclay Card No. and post to TUAC LTD. (PE16), 163 Mitcham Road, London SW17 9PG.

In a hurry . . . Phone us for local stockist. **PERSONAL SHOPPERS:** Mon., Tues., Thurs., Fri., Sat. 9 a.m.–6 p.m. Wed. 9 a.m.–1 p.m.

ALL PRICES INCLUDE V.A.T. (8%) AND POSTAGE AND PACKING

ACCESS & BARCLAY CARDS ACCEPTED—JUST SEND OR PHONE US YOUR NUMBER

HP ENQUIRIES INVITED

**IDEAL
FOR DISCOS**

Sound to Light Master Unit



600 WATTS PER CHANNEL
Connects to your loudspeaker or
loudspeaker socket. The unit can
be connected to your existing
spotlight fittings or to our type A
or B fittings.


£30^{·95}



including channel output plugs
and mains input socket.

ALL PRICES INCLUDE V.A.T. and POST & PACKING
(These prices apply to the United Kingdom only)

Twin Bank 6 LIGHT UNIT

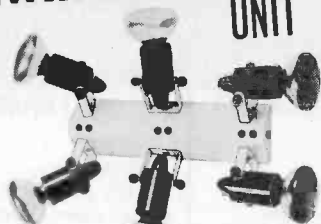

(less lamps)

B.C. FITTING
£9.55 (each)

Length 14½ inches

E.S. FITTING
£10.35 (each)

Type A

(less lamp)

B.C. FITTING
£1.95 (each)

E.S. FITTING
£2.12 (each)



100 WATT SPOT LAMPS


Red, pink, yellow, green,
blue, clear. **£1-18** each

Only **£1** B.C. or E.S. Fitting

Minimum
3 lamps
£3-54

Type B 3 BANK UNIT

(less lamps)

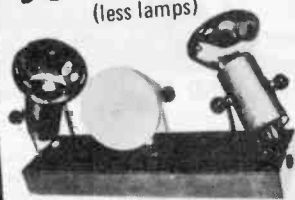


B.C.
FITTING
£6.90
(each)

E.S.
FITTING
£7.26
(each)

Twin Bank 12 LIGHT UNIT

Length 31¾ inches

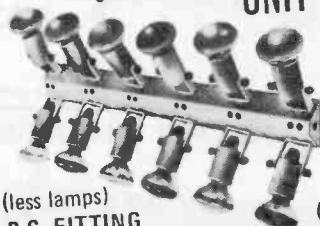

(less lamps)

B.C. FITTING


£15.60 (each)

(each)

E.S. FITTING £17.00

Send 20p for illustrated leaflet & price list.

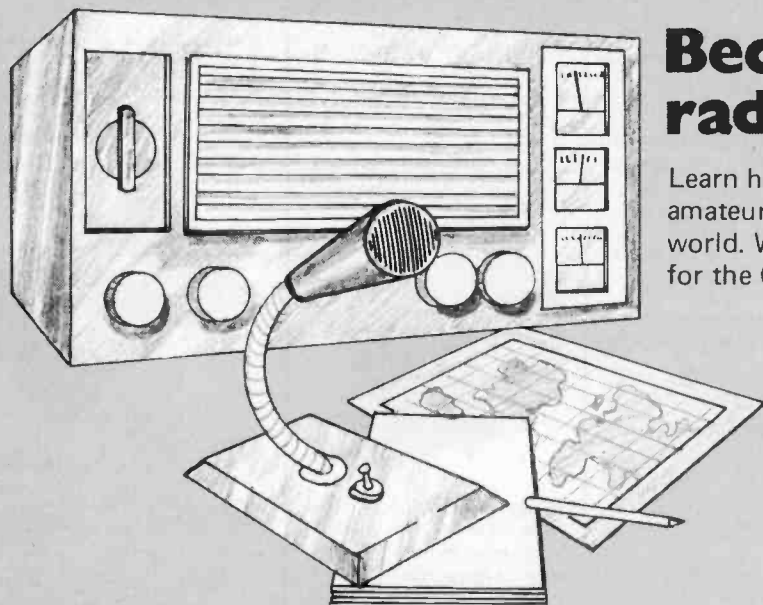TRAFALGAR SUPPLIES
Dept.H.T., STANDISH STREET,
BURNLEY, LANCs.



Become a radio amateur.

Learn how to become a radio-
amateur in contact with the whole
world. We give skilled preparation
for the G.P.O. licence.

Free!

Brochure, without obligation to:

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, Dept. EB16

P.O. Box 156, Jersey, Channel Islands.

NAME _____

ADDRESS _____

Block caps please

PATENTS REVIEW...

TAPE NOISE REDUCTION

In BP 1 382 096, Matsushita Electrical Industrial Co. Ltd. patents an automatic noise reduction system for use with tape recorders. Using compression and expansion techniques the block diagram of the system is shown in Fig. 1.

The compression characteristic (a) on record, the expansion characteristic (b) on playback and the resultant, theoretical, linear characteristic (c) which follows from the combination of (a) and (b) is shown in Fig. 2. Thus, the process is complimentary and therefore the output should be a replica of the input.

Noise is reduced because it is introduced between the two stages and is thus subjected only to the expansion curve. In other words, process noise is reduced relative to programme content.

Because the expansion-compression effect is active only below a threshold point (where the curves in Fig. 2 (a) and (b) become linear), noise is reduced only when the signal level is low. This avoids overloading the tape with excessive signal and is acceptable because the subjective level of noise present in a high level signal is less noticeable because it is masked by the signal.

In practice, the compression and expansion operation is effected only in the presence of high frequency signal components. The circuit shown in the patent is designed to provide processing of only the high frequency signal components, because the majority of tape noise is in the upper frequency range, i.e. tape hiss.

The system outlined in the patent more closely resembles that marketed by JVC than Dolby.

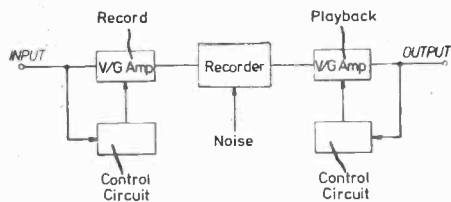


Fig. 1

ELECTROSTATIC LOUDSPEAKER

BP 1 387 453

In BP 1 387 453, Matsushita Electric Industrial Co. Ltd. describes an electrostatic loudspeaker which requires no d.c. polarising voltage.

A vibratile film electret, made of a polymer such as plastics resin and with a permanent surface charge, is coated on one side by a very thin layer of a conductive paint or metal. Fixed perforated electrodes permit acoustic radiation and are spaced one each side of the coated electret.

An a.c. audio frequency signal is applied between the fixed electrodes via a matching transformer, balance capacitors and a resistor which controls higher harmonic distortion. Alternatively, a push-pull transformer may be employed as the audio power source.

The conductive layer acts as an electrostatic earth, so the electric field due to the permanent charge on the film electret exists in one air gap between the electret and the fixed plates, but not in the other air gap. Thus no static electricity due to the charge is generated between the film and the non-charged electrode and the only force between the film and this electrode is generated by the audio signal.

However, the force between the film and the charged electrode is generated by the superposition of the electrostatic voltage due to the electret charge on to the audio signal. The resultant imbalance causes vibration of the electret and transduction of the audio signal into sound waves propagated through the perforations in the electrodes.

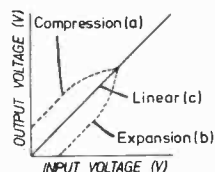


Fig. 2

PATENT NEWS

Of necessity, patents for inventions reported in this column are relatively simple. It is physically impossible to précis an invention covered by a hundred-page patent in a few lines of print. For this reason, the most complicated inventions and the most lengthy patents must usually pass unrecorded.

This is a pity, because a lengthy patent can be a valuable source of information. It can also be a very cheap one, because all British Patents cost only 33p each, regardless of length. They may also be studied free of charge by any member of the public at various libraries around the country, such as the Science Reference Library attached to the Patent Office at Southampton Buildings, Chancery Lane, London WC2.

With this in mind, we shall in future be referring simply by name, number and the briefest of explanatory comment to any lengthy new electronics patents that may be of value to readers with a specialist interest.

BP 1 402 320—Sansui Electric Co. Ltd. *Decoder for use in 4 : 2 : 4 matrix playback system.* One of many patents now appearing for the various four channel and quadraphonic systems, this one covers the Sansui Variomatrix principle. Separation between channels is enhanced by sensing the amplitude of signals in the various channels and varying the matrix parameters to accentuate them.

BP 1 404 460—Standard Telephones & Cables Ltd. *Device for transmitting cursive script or drawing over a telephone.* A matrix of metal conductive strips is mounted under a domestic telephone, to translate a sketched diagram into different resistance values which are transmitted via the telephone.

BP 1 402 571—Mitche and Jeffrey. *Method for identifying the components of a file.* A system for reading the contents of any data file, which may for instance be a punched card, to aid automatic data retrieval. (See also BP 1 402 572.)

BP 1 382 096

Copies of Patents can be obtained from the Patent Office Sales, St. Mary Cray, Orpington, Kent Price 33p each

Readout—

A SELECTION FROM OUR POSTBAG

Readers requiring a reply to any letter must include a stamped addressed envelope. We regret that we cannot answer any technical queries on the telephone.

Good-Bye ?

Sir,—This is a farewell letter. For nine years, to the exact month, I have enjoyed every issue of PRACTICAL ELECTRONICS. Its specially written articles have added to my knowledge of electronics. Its construction projects have brightened my spare moments, and even helped in my work. Indeed, my subscriptions to P.E. have been one of the wisest investments I ever made.

But now, your publishers inform me that they are discontinuing the subscription service. This means that those of us outside the U.K. who had relied on subscriptions for obtaining regular supplies of P.E. can no longer do so. I know there must have been genuine economic reasons for taking such decisions, but this seems to ignore the confidence we have had in you for a long time. It is, after all, very true, isn't it, that economic considerations are hardly the best recipe for maintaining a friendship. But then, even the publishers of P.E. are in business too!

So, it is good-bye to P.E. God bless.

A. J. Isong,
Nigeria.

We trust this is not "farewell" as you suggest, but only *au revoir*. Our agent in Nigeria should be able to supply you with PE regularly.

Other subscribers, home or overseas, please see notice on page 32.

A Bit Flat

Sir,—I was interested to read your article in the November P.E. on an "Electronic Tuning Fork". I should like to point out that this device would not be suitable for tuning a piano.

I have already developed a tuner using a cathode ray tube for visual aid, I have experimented with the master oscillator 12-note frequency derivative integrated circuit, but so far, I have not used it, as I am in favour of using a tapped oscillator coil for greater accuracy.

When tuning a piano, the treble end of the scale is slightly sharp, and the bass end slightly flat. "Zero" deviation occurs at the centre of the keyboard.

Pianos are tuned only by aural means, and when tuned, become mathematically incorrect.

Therefore, by introducing a plus and minus frequency deviation switch, a much more realistic tuned piano is possible. On this theory, I claim that no frequency divider organs are in tune but nobody seems to mind, but I have tuned several pianos flat, but they are noticeable.

I don't suppose you were really trying to encourage your readers to put piano tuners out of business, so perhaps you may consider your circuit good enough.

D. Marquis,
Essex.

Your observations on piano tuning are very interesting, I have, in fact, heard that some professional tuners do tune sharp at the top of the scale and flat at the bottom end. Unfortunately, nobody has told me why they do this, if in fact they do.

When researching this project, I took as my main source of reference a book entitled "The Physics of Music" by Alexander Wood (Pub Methuen), which goes into considerable detail on the subject of piano tuning. This book definitely states that pianos are tuned in perfect accordance with the tempered scale. Illustrated in the book (Page 200) are graphs of the state of tune three days after tuning has taken place. The trend is for the low notes to drop considerably whilst the upper notes show considerable variations but all on the high side. This deterioration is similar to their figures. I have taken these figures to be percentages of a semitone interval, as percentages of the actual frequency are clearly a nonsense for the values you give.

If indeed, pianos are tuned in this fashion, one wonders if the same applies for other orchestral instruments when played in the extreme registers.

Finally, I'm sure piano tuners aren't going to become redundant, perhaps this instrument will save some piano's from the scrap heap. Should any piano tuner feel threatened, he should retaliate. I'm sure you'll agree, there are tremendous prospects in the electronic musical instrument field!—P.W.B.

Happy Chance

Sir,—By a happy chance I have come across your article "Electronic Tuning Fork" in P.E. for Nov.

It would be much more convenient if each octave began on C according to usual musical usage, i.e. the C2 C1 c c' c'' etc., notation, and the 16' 8' 4' etc. of organ nomenclature. Would it be possible to incorporate a circuit to double the frequency of the A# and B outputs from IC1? Or failing that, alternatively to halve the frequency of the other ten outputs?

For my purposes, I think the most convenient form of display would be a centre-zero meter calibrated to indicate the pitch difference in vibrations/second + or —. Is this at all feasible?

For many purposes the tuning errors of your instrument (maximum on C# of -0.29 in an interval of 15.6) are not really acceptable and one would certainly have to make a correction according to the beat indication.

M. B. Card, Herts.

Your requirement for a range spanning C to C1 is simply facilitated by increasing the master oscillator frequency to 999.68 kHz. The tuning core of the coil L1 will probably accommodate this, but should this be not so, decrease C5 and C4.

Your further requirements are not so easily satisfied; although it is possible to determine and indicate whether the pitch is greater or less than standard, the extra complexity would not be worthwhile as when using the "fork" it is at once obvious when the instrument is detuned, and opposite action is applied without thought.

A meter indication of your description would indeed be a great improvement, however, the problems involved are considerable. The advantages of the beat method are simplicity, but the drawback is a variation in accuracy over the range of the scale.

A meter performing the beat counting task would have to sample for at least the period between two beats which becomes infinite when the tuning is spot on.

Your final comment on the accuracy rests with the i.c. manufacturer. The worst case I concede is C# which is less than 2% of the semitone interval or 2 cents in musical parlance. Ideally, errors should be less than one cent and it is unfortunate that General Instruments did not choose to divide by larger integers, especially as master clock frequencies of up to 2.5MHz can be accommodated, so the top end of the scale need not be sacrificed.

In conclusion, it is well documented that a good piano will give errors greater than 10 per cent only three days after "perfect" tuning so I feel that only the most discerning ears will be grieved by our small inaccuracies.—P.W.B.

RELAYS SIEMENS, PLESSEY, Etc. MINIATURE RELAYS

Col. (1) Coil ohms	1	2	3	4
Col. (2)	52	4-8	2 c/o	75p*
Working	58	5-9	6 c/o	85p*
d.c. volts	120	10-12	6M	65p*
Col. 3	230	9-18	2 c/o HD	85p*
Col. 3	430	15-24	4 c/o	85p*
Contacts	700	12-24	2 c/o	65p*
Col. (4)	700	16-24	4 c/o	85p*
Price	1,250	18-36	2 c/o	65p*
	2,500	31-43	2 c/o HD	65p*
HD =	2,500	36-45	6M	65p*
Heavy duty	9,000	70-70	2 c/o	65p*
	15k	85-110	6M	65p*

*Incl. Base. All prices incl. P. & P.

OPEN TYPE RELAYS

9 VOLT D.C. 1 make contacts 35p. Post 15p.
 9 VOLT D.C. RELAY
 3 c/o 5 amp contacts. 70 ohm coil. 75p. Post 15p.
 12 VOLT D.C. RELAY
 3 c/o 5 amp contacts. 120 ohm coil. 75p. Post 15p.
 24 VOLT D.C. 3 c/o 75p. Post 15p.

ENCLOSED TYPE RELAYS

24 VOLT D.C. 3 c/o 75p. Post 20p. Base 15p extra.
 24 VOLT A.C. Mfg. by I.T.T.'s h.d. c/o contacts.
 55p. Post 20p. Base 15p.

55 VOLT A.C. RELAY

3 h.d. c/o contacts. Price 55p. Post 20p. Base 15p.
 100 VOLT A.C. 3 c/o sealed type. 75p. Post 20p.
 Base 15p.

240 VOLT RELAY

3 h.d. c/o contacts. Price 75p. Post 20p. Octal
 plug in base 15p extra.

230/240 VOLT A.C. RELAY. Mfg. by Arrow 2 h.d.
 15 amp c/o contacts. Amp connectors. Price £1.
 Post 20p.

220/240 VOLT A.C. RELAY

3 c/o 5 amp contacts. Sealed. Mfg. ISKRA.
 £1.25. Post 20p. Base 15p extra.

CLARE-ELLIOTT TYPE RPT741 G8
 Miniature relay. 675 ohm coil. 24 VOLT D.C. 2 c/o.
 70p post paid.

110V. 2 c/o. 20 amp contacts. £1.25. Post 10p.
 Many others from stock—phone for details.

C/O MICRO SWITCH

VERY SPECIAL OFFER. Mfg. by
 C.E.M. 3 amp 250 volt. 10 amp 125
 volt. 50 for £3. Post 36p. 100 for £5.
 Post 50p. £1,000 for £45. Post paid.

Bulk purchase means LOW! LOW! prices.
 DOUBLE POLE C/O or 2 make/2 break micro
 switch. 10 amp 250v a.c. With detachable roller
 assembly. 10 for £2.50. Post 50p (min. order 10).

LATCHING RELAY

Twin latching relay, "flip-flop" 2 c/o
 each relay. Mfg. contacts. 115V
 A.C. or 50V D.C. operation. 240V
 A.C. with 2.5K resistor. 85p. Post 20p.

230/250 VOLT A.C. SOLENOID

Approximately 1 1/2 lb. pull. Size of feet 1 1/4" x 1 1/8".
 Price £1.00. Post 20p.

HEAVY DUTY TYPE. 10 lb. (approx.) pull. £2.50.
 Post 50p.

24 VOLT DC SOLENOIDS

UNIT containing 1 heavy duty solenoid approx. 25lb
 pull 1 inch travel. Two x approx. 1lb pull 1/2 inch
 travel. 6 x approx. 4oz. pull 1/4 inch travel. One
 24 volt d.c.. 1 heavy duty single make relay. Price
 £2.50. Post £1. ABSOLUTE BARGAIN.

600 WATT DIMMER SWITCH
 Easily fitted. Fully guaranteed by makers.
 Will control up to 600V of lighting
 except fluorescent at mains voltage.
 Complete with simple instructions.
 £2.75. Post 25p.

1,000 watt model, £4. Post 25p.
 2,000 watt model, £8. Post 40p.

CENTRIFUGAL BLOWER

Mfg by Smiths Industries. 230/240V
 a.c. Miniature Model. Series SE/200.
 Size 95mm x 82mm x 82mm.
 Aperture 38mm 31mm. 12
 c.f.m.. £2.75. Post 50p.

Mfg. by Airflow Developments Ltd.
 Precision made, continuously rated, smooth running.
 230/240V a.c. motor, 80 c.f.m. As illustrated but
 with round aperture, £6.50. Post 75p.

Mfg. by Woods.
 Extremely powerful. 220/250V a.c. 0-3A 2,700 r.p.m.
 continuously rated. Capacitor start. Cast construction.
 Aperture 66mm x 50mm. O/A 200mm. £12.
 Post £1.

INSULATION TESTERS NEW!

Test to I.E.E. Spec. Rugged metal
 construction, suitable for bench or
 field work, constant speed clutch.
 Size L.8in, W.4in, H.6in, weight 6lb.
 500V, 500 megohms, £30. Post 80p.
 1,000V, 1,000 MΩ, £36. Post 80p.

ALL MAIL ORDERS—CALLERS—AMPLE PARKING

Dept. PE12, 57 BRIDGMAN ROAD
 CHISWICK, LONDON W4 5BB
 Phone 01-995 1560
 Showroom open Mon.-Fri.

VARIABLE VOLTAGE TRANSFORMERS

INPUT 230/240V a.c. 50/60 OUTPUT

VARIABLE 0-260V All Types

SHROUDED TYPE

200 watt (1 amp) £10.00

0.5 KVA (2 1/2 amp) (MAX) £11.50

1 KVA (5 amp) (MAX) £15.00

2 KVA (10 amp) (MAX) £27.50

3 KVA (15 amp) (MAX) £30.00

4 KVA (20 amp) (MAX) £60.00

37.5 amp (MAX) £102.50

CARRIAGE AND PACKING EXTRA



L.T. TRANSFORMERS

0, 6, 12 Volt at 10 amp. £5.60. Post 70p.

0, 10, 17, 18 Volt at 10 amp. £7.90. Post £1 00

0, 4, 6, 24, 32 Volt at 12 amp. £9.90. Post £1 00

0, 6, 12 Volt at 20 amp. £9. Post £1 00

0, 12, 24 Volt at 10 amp. £9.20. Post £1 00

0, 6, 12, 17, 18, 20 Volt at 20 amp. £10.40. Post £1 00

Other types to order at short notice—Phone your
 enquiries.

STROBE! STROBE! STROBE!

Build a Strobe Unit, using the latest type Xenon
 white light flash tube. Solid state timing and
 triggering circuit. 230/250V a.c. operation.

HY-LIGHT STROBE MK III
 For use in large rooms, halls and utilises a silica
 tube, printed circuit. Speed adjustable 0-20 f.p.s.
 Light output greater than many (so called 4
 Joule) strobes £14. Post 75p.

RANGE OF THREE OTHER STROBE

KITS FROM STOCK. From £6.30 to £22.
 S.A.E. (Foolsap) for details.

BIG BLACK LIGHT

400 Watt. Mercury vapour ultra violet lamp.
 Powerful source of u.v. P.F. ballast is essential.
 Price of matched ballast and bulb £21.
 Post £1.50. Spare bulb £8. Post 65p.

BLACK LIGHT FLUORESCENT U.V. TUBES

4ft 40 watt, £5.50 (callers only).

2ft 20 watt, £4.25. Post 60p. (For use in
 standard bi-pin. MINI. 12in 8 watt, £1.60.
 Post 25p. 9in 6 watt, £1.30. Post 25p.

Complete ballast unit and holders for 9in and
 12in tube, £1.70. Post 30p. (9in and 12in
 measures approx.)

U.D.I. SINGLE CHANNEL
 750 WATT MANUAL/AUTO DIMMER
 750V Solid State Fader, with three functions.
 Manual fade; Auto fade-up; Auto fade-down.
 Automatic cycling up and down. Functions
 selected with 'three-position' rocker switch.
 Two ranges of cycling for 'Flashing' or 'Slow
 light' obsolete. Completely electrically and
 mechanically noise free. Can be used on same
 circuit as radio mixes or sensitive amplifiers.
 A whole new range of lighting effects possible
 with astounding results. Already in use in
 London's foremost theatres, night clubs and
 light shows. Conforms to all R.F.I. tests, including
 Common Market Regulations. Supplied in
 tough, well designed case with embossed
 front panel. Price only £60. Post 75p. S.A.E.
 (Foolsap) for further details.

U.D.I. SINGLE CHANNEL
 750 WATT MANUAL/AUTO DIMMER
 750V Solid State Fader, with three functions.
 Manual fade; Auto fade-up; Auto fade-down.
 Automatic cycling up and down. Functions
 selected with 'three-position' rocker switch.
 Two ranges of cycling for 'Flashing' or 'Slow
 light' obsolete. Completely electrically and
 mechanically noise free. Can be used on same
 circuit as radio mixes or sensitive amplifiers.
 A whole new range of lighting effects possible
 with astounding results. Already in use in
 London's foremost theatres, night clubs and
 light shows. Conforms to all R.F.I. tests, including
 Common Market Regulations. Supplied in
 tough, well designed case with embossed
 front panel. Price only £60. Post 75p. S.A.E.
 (Foolsap) for further details.

U.D.I. SINGLE CHANNEL
 750 WATT MANUAL/AUTO DIMMER
 750V Solid State Fader, with three functions.
 Manual fade; Auto fade-up; Auto fade-down.
 Automatic cycling up and down. Functions
 selected with 'three-position' rocker switch.
 Two ranges of cycling for 'Flashing' or 'Slow
 light' obsolete. Completely electrically and
 mechanically noise free. Can be used on same
 circuit as radio mixes or sensitive amplifiers.
 A whole new range of lighting effects possible
 with astounding results. Already in use in
 London's foremost theatres, night clubs and
 light shows. Conforms to all R.F.I. tests, including
 Common Market Regulations. Supplied in
 tough, well designed case with embossed
 front panel. Price only £60. Post 75p. S.A.E.
 (Foolsap) for further details.

U.D.I. SINGLE CHANNEL
 750 WATT MANUAL/AUTO DIMMER
 750V Solid State Fader, with three functions.
 Manual fade; Auto fade-up; Auto fade-down.
 Automatic cycling up and down. Functions
 selected with 'three-position' rocker switch.
 Two ranges of cycling for 'Flashing' or 'Slow
 light' obsolete. Completely electrically and
 mechanically noise free. Can be used on same
 circuit as radio mixes or sensitive amplifiers.
 A whole new range of lighting effects possible
 with astounding results. Already in use in
 London's foremost theatres, night clubs and
 light shows. Conforms to all R.F.I. tests, including
 Common Market Regulations. Supplied in
 tough, well designed case with embossed
 front panel. Price only £60. Post 75p. S.A.E.
 (Foolsap) for further details.

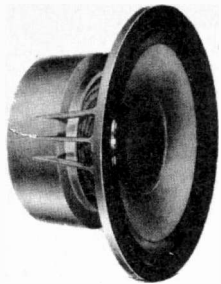

WILMSLOW AUDIO

THE Firm for speakers!

SPEAKERS

Baker Group 253, 8 or 15 ohm	£8-64
Baker Group 35 3, 8 or 15 ohm	£10-25
Baker Group 50/12 8 or 15 ohm	£14-00
Baker Deluxe 12in d/cone	£13-75
Baker Major 12in d/cone	£11-87
Baker Regent	£10-00
Baker Superb	£18-12
Baker Auditorium 12	£16-25
Castle Super 8 RS/DD	£10-31
Celestion MH1000, 8 or 15 ohm	£13-50
Celestion P58 for Unilex	£3-75
Celestion G12M 8 or 15 ohm	£12-95
Celestion G12H 8 or 15 ohm	£15-95
Celestion G15C 8 or 15 ohm	£26-95
Celestion G18C 8 or 15 ohm	£34-50
Decca London Ribbon Horn	£30-00
Decca London and crossover	£42-25
Decca DK30 and crossover	£24-06
EMI 13in x 8in 150 d/c 8 ohm	£2-84
EMI 13in x 8in type 350 8 or 15 ohm	£9-56
EMI 13in x 8in 25W bass	£9-00
EMI 6in 93850 4 or 8 ohm	£2-90
EMI Sin 14A/7030 mid range 8 ohm	£3-50
EMI 14in x 8in Bass 8 ohm	£13-25
Eagle DT33 30W tweeter	£8-31
Eagle HT15 horn tweeter	£4-40
Eagle CT5 cone tweeter	£2-06
Eagle CT10 tweeter 8 or 16 ohm	£3-00
Eagle MHT10 horn tweeter	£4-44
Eagle crossover CN23, CN28, CN216	£1-75
Eagle FR4	£8-12
Eagle FR65	£9-82
Eagle FR8	£12-31
Elac 9 x 5.59RM109 15 ohm, 59RM114 8 ohm	£3-44
Elac 6in 6RM171 d/c roll surr.	£4-06
Elac 6in 6RM220 d/cone	£3-12
Elac 4in tweeter TW4	£1-75
Elac 8in 8CS175 3 ohm	£2-87
Fane Pop 15W 12in	£5-25
Fane Pop 25T 30W 12in	£7-50
Fane Pop 50W 12in	£12-00
Fane Pop 55 80W 12in	£13-95
Fane Pop 80W 15in	£17-25
Fane Pop 100W 18in	£25-95
Fane Crescendo 12A 100W 12in	£34-50
Fane Crescendo 12B bass	£36-50
Fane Crescendo 15in 100W	£47-50
Fane Crescendo 18in 150W	£62-95
Fane 801T 8in d/c roll surr.	£9-95
Fane 807T 8in d/c roll surr.	£5-75
Fane 808T 8in d/c	£3-95
Fane 910 horn	£14-95
Fane 920 horn	£33-95
Goodmans 8P 8in 8 or 15 ohm	£5-50
Goodmans 10P 8 or 15 ohm	£5-80

Goodmans 12P 8 or 15 ohm	£13-95
Goodmans 12P-D 8 or 15 ohm	£16-95
Goodmans 12P-D 8 or 15 ohm	£15-95
Goodmans Audiomax 12AX 100W	£38-50
Goodmans Audiomax 15AX	£40-25
Goodmans 15P 8 or 15 ohm	£21-00
Goodmans 18P 8 or 15 ohm	£36-00
Goodmans Hifax 750	£16-00
Goodmans Axent 100 tweeter	£8-44
Goodmans Audiom 100 12in	£13-90
Goodmans Axiom 402 12in	£20-00
Goodmans Twinaxiom 8	£10-14
Goodmans Twinaxiom 10	£10-75
Jordan Watts Module	£17-06
Kef T27	£8-06
Kef T15	£8-94
Kef B110	£8-37
Kef B200	£9-50
Kef B139	£16-95
Kef DN8	£2-31
Kef DN12	£5-95
Kef DN13	£4-50
Peerless Dome Tweeter KO10DT	£9-06
STC 4001G Super Tweeter	£8-56
Radford BD25	£18-44
Radford FN11a	£13-95
Radford FN12a and 12b	£12-75
Radford MD9	£11-50
Radford TD3	£9-06
Richard Allen CG8T d/c r/surr.	£7-50
2in 84 ohm, 70mm 80 ohm, 70mm 8 ohm	£0-77
2in 75 ohm	£0-59
7in x 4in 3 or 8 ohm	£1-83
8in x 5in 3 or 8 ohm	£1-75
10in x 6in 3, 8 or 15 ohm	£2-66

SPEAKER KITS

Baker Major Module	each £13-44
Goodmans Mezzo twinkit	pair £47-19
Helme XLK30	pair £19-00
Helme XLK35	pair £24-00
Helme XLK40	pair £26-00
Helme XLK50	pair £56-00
Kefkit 1	pair £33-00
Kefkit 3	each £48-00
Richard Allan Twinkit	each £10-95
Richard Allan Triple 8	each £16-50
Richard Allan Triple 12	each £23-95
Richard Allan Super triple	each £28-75
Wharfedale Linton 2 kit	pair £23-12
Wharfedale Glendale 3 kit	pair £40-82
Wharfedale Dovedale 3 kit	pair £83-12

Baker, Linear and Eagle PA disco amplifiers in stock. Send stamp for list.

Prices correct at 12 November, 1975

FREE with Speaker Orders over £7

"Hi-Fi Loudspeaker Enclosures" book.

All units guaranteed new and perfect. Prompt despatch. Carriage and packing: speakers 50p each, 12in and up 75p each, speaker kits 80p each (£1-60 pair), tweeters and crossovers 30p. Send stamp for free booklet "Choosing a Speaker"

Including VAT 25% on HI-FI, 8% on PRO and PA
WILMSLOW AUDIO (Dept. PE)

Loudspeakers: Swan Works, Bank Square, Wilmslow, Cheshire SK9 1HF.
Discount Radio, PA, Hi-Fi: 10 Swan Street, Wilmslow.
Discount TV, Hi-Fi: Swift of Wilmslow, 5 Swan Street, Wilmslow.


The Ultimate Radio!

GRUNDIG SATELLIT 2000

You've got your yacht, private aircraft, Rolls Corniche?—then all you need for a full set of status symbols is this latest model Grundig Satellit, Germany's top radio! Radio performance, appearance and sound quality are all superb. VHF/FM, MW, LW 10 SW bands plus bandspeed, 27 transistors and 22 diodes, Battery/Mains (110/240V) 2 speakers, 57in telescopic aerial.

Our price £161.45 inc. carr., ins. and VAT. Big discounts on Grundig ITT, Koyo, etc. Send stamp for list.

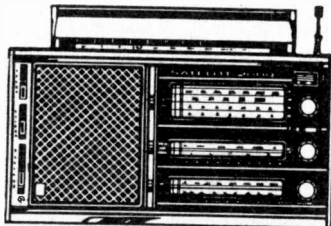WILMSLOW AUDIO
(Dept. PE)
10 SWAN STREET
WILMSLOW, CHESHIRE



THE RADIO SHOP

18 CHERRY LANE
BRISTOL BS1 3NG



TELEPHONE
0272-421198

TRIACS

1-8AMP PLASTIC*		8-AMP ISOLATED TAB	
NAS 0161W 100V	0-28	NAS 0651W 100V	0-65
NAS 0181X 100V	0-28	NAS 0651X 100V	0-65
NAS 0182W 200V	0-30	NAS 0652W 200V	0-61
NAS 0182X 200V	0-29	NAS 0652X 200V	0-61
NAS 0184W 400V	0-40	NAS 0654W 400V	0-70
NAS 0184X 400V	0-38	NAS 0654X 400V	0-70
NAS 0168W 600V	0-50	NAS 0656W 600V	0-88
NAS 0168X 600V	0-48	NAS 0656X 600V	0-76
10AMP ISOLATED TAB		3-5AMP CLIPPED TAB	
NAS 1001W 100V	0-72	NAS 0351W 100V	0-52
NAS 1001X 100V	0-72	NAS 0351X 100V	0-52
NAS 1002W 200V	0-78	NAS 0352W 200V	0-56
NAS 1002X 200V	0-76	NAS 0352X 200V	0-56
NAS 1004W 100V	1-09	NAS 0354W 400V	0-68
NAS 1004X 400V	1-04	NAS 0354X 400V	0-67
NAS 1008W 600V	1-36	NAS 0356W 600V	0-85
NAS 1008X 600V	1-36	NAS 0356X 600V	0-84
8-5AMP ISOLATED TAB		15AMP ISOLATED TAB	
NAS 0851W 100V	0-68	NAS 1501W 100V	1-05
NAS 0851X 100V	0-68	NAS 1501X 100V	0-95
NAS 0852W 200V	0-76	NAS 1502W 200V	1-02
NAS 0852X 200V	0-76	NAS 1502X 200V	1-02
NAS 0854W 400V	0-88	NAS 1504W 400V	1-51
NAS 0854X 400V	0-85	NAS 1504X 400V	1-48
NAS 0856W 600V	1-10	NAS 1506W 600V	1-89
NAS 0856X 600V	1-08	NAS 1506X 600V	1-84

Devices with internal trigger have "W" suffix; "X" denotes standard triac.

THYRISTORS

1-8AMP TO-5*		4AMP ISOLATED TAB	
NAS 006P 50PIV	0-28	NAS 106P 50PIV	0-28
NAS 006Q 100PIV	0-28	NAS 106Q 100PIV	0-30
NAS 008R 200PIV	0-31	NAS 108R 200PIV	0-30
NAS 008S 400PIV	0-40	NAS 108S 400PIV	0-37
NAS 008T 600PIV	0-52	NAS 108T 600PIV	0-50
8AMP ISOLATED TAB		8AMP ISOLATED TAB	
NAS 206P 50PIV	0-67	NAS 306P 50PIV	0-41
NAS 206Q 100PIV	0-62	NAS 306Q 100PIV	0-47
NAS 208R 200PIV	0-50	NAS 308R 200PIV	0-50
NAS 208S 400PIV	0-77	NAS 308S 400PIV	0-65

CLOCK CHIPS

CT 7001 28 pin	4-85	AY-5-1224 16 pin	3-75
28 pin ekt	0-55	16 pin ekt	0-18
Delta	0-15	Delta	0-15
704 LED 0-3" Common Anode Display	1-00		
704 LED 0-3" Common Cathode Display	1-00		
747 LED 0-6" Common Anode Display	1-85		

Thyristors C106 Series 4Amp

50V 0-32 100V 0-37 200V 0-48 400V 0-58 600V 0-70	
--	--

INTEGRATED CIRCUITS

TAA 565 TO18 0-34	*T8A 800	0-78	*708 14 pin	0-87
TAA 283 TO18 0-82	*T8A 210AS	1-08	*741 8 pin	0-35
555 8 pin	0-40	*2N 414 TO18 0-78	*748 14 pin	0-80
556 8 pin	1-05		*723 14 pin	0-87

* Please add 25% VAT. Remainder 8% Postage and packing 20p per order.
Phone in your Access and Barclaycard order.

NEW CHIPS AND PRICES

LITRONIX FULL SPEC LEDS

DL701, 704, 707	£1-48
DL721, 727, 728	£3-75
DL746, 747, 750	£2-45

LITRONIX CLASS 11 PRODUCTS

DL707E	£0-70
DL727E	£1-80
DL747E	£1-50

NEW MOSTEK COUNTER CHIPS

6 digit UP/DOWN with BCD preset, compare and clear. BCD and 7 segment multiplexed outputs with latch, LZB, etc.
MK50395 (6 decade)
MK50396 (HHMSS)
MK50397 (MMSS.99) Price £14-50

NEW NATIONAL CHIPS AND PRICES

MM5309	£5-69
MM5311	£5-69
MM5314*	£4-88
MM5316	£10-17
MM5318	£3-36
MM5371	£8-14
MM5378*	£6-73

* Also available in MHI kit form.

All other National clock chips available—S.A.E. for details.

Terms: CWO, Access, Barclaycard (simply quote your number and sign). Credit facilities to accredited account holders.

VAT—All prices exclude VAT (8%), P. & P. 1p

BYWOOD

68 Ebbens Road, Hemel Hempstead
Herts. HP3 9QRB

Tel. 0442 62757

BARCLAY ELECTRONICS

MONEY SAVERS

CBM SR7919D

- 8 digit or 5 digit + 2 exponent
- Sine, Tan, Cos and their inverse
- Natural Logs, Common Logs, Anti Logs
- Square Root
- Reciprocals



- Y^x
- x^2
- π
- Register Exchange
- Memory plus
- Store Recall
- Sign Change
- Algebraic Logic

ONLY £12.50 +8% VAT

1 year Manufacturer's Guarantee
CBM mains adaptor. Please add £2.50 to total

DECIMO 2001E



THE ONLY TRUE SCIENTIFIC CALCULATOR WE KNOW THAT ACTUALLY FITS IN YOUR POCKET (WITHOUT STRETCHING IT TO THE LIMIT) AND YET HAS A LARGE BRIGHT AND CLEAR 12 DIGIT L.E.D. DISPLAY AND SINGLE FUNCTION KEY-BOARD

We can continue this special offer only till Dec. 31st

- Only 6.75 x 1.75 x 14cm
- 10 figure mantissa
- 2 figure exponents
- 2 sign display
- Common logs, natural logs and antilogs

- Memory
- Memory + -
- Sign change
- Reciprocals
- Square roots
- π
- Automatic constant
- Exponent key
- y^x
- Clear last entry
- Register exchange
- Memory exchange (can be used as a parenthesis)
- Mean and standard deviation, also polar rectangular co-ordinates can be worked out using the appropriate formulae

FUNCTION FOR FUNCTION THIS IS UNBEATABLE

- Floating point
- Positive feel keyboard
- Radians, degrees, grads
- Hyperbolics
- 25 hour battery time
- Own carry case
- Algebraic logic
- Full 1 year manufacturer's guarantee
- Cos, Sine, Tan and their Inverse

ONLY

£24.90

+8% VAT

If mains adaptor required, please add £3 to total

NOVOUS 4515 100 STEP PROGRAMMABLE

The new 4515 (by National Semiconductors) 100 step programmable is the answer to those ridiculous prices one had to pay for a machine that could do what this beautifully made machine can do, and it costs a fraction of what it should cost. The programming is simple to operate, and many different programmes can be contained at the same time. Constant and variable factors can be inserted when or where you want. You can correct mistakes, and even skip out programmes out of a number of other programmes.

This is truly an unbeatable machine

- 8 digit
- Common and natural logs, and anti log
- Sine, Cos, Tan and their inverse
- Reciprocals
- Y^x
- x^2
- 3 level stack
- π
- Register exchange
- Sign change
- Memory
- Memory + x^2
- Degree radian conversion
- Rechargeable (Recharger included in price)
- Vinyl case (full instruction manual)



OUR PRICE £39.50

+8% VAT

including recharger

If you need scientific notation, then the Novous 4525 is your answer. 8 digit + 2 exponent 100 step programmable + 4 roll stack and everything else the 4515 has.

ONLY £59.90 +8% VAT

Full one year manufacturer's guarantee

SCIENTIFIC

ALGEBRAIC

	£
CBM 4148 12 digit + 2 exp.	39.95
TEXSAS SR16 8 digit + 2 exp.	31.50
TEXSAS 50A 10 digit + 2 exp.	43.50
TEXSAS 51A 10 digit + 2 exp.	63.50
ROCKWELL 51R 8 digit conversion	27.50
ROCKWELL 63R 8 digit + 2 exp.	29.99
ROCKWELL 61R 8 digit	27.50
SINCLAIR OXFORD 300 5 digit + 2 exp.	21.95
REALTONE SC60 (3) 10 digit + 2 exp. 3 memory scientific station	49.90
REALTONE SC60 (10) 10 digit + 2 exp. (similar functions to the HP45) 10 memory, scientific station	62.00

REVERSE POLISH LOGIC

	£
SINCLAIR Scientific 5 digit 2 exp.	11.50
NOVOUS 4510 8 digit mathematic	19.50
NOVOUS 4515 8 digit mathematic, 100 step programmable	39.50
NOVOUS 4520 8 digit 2 exp. 4 roll stack	34.50
NOVOUS 4525 8 digit 2 exp. 4 roll stack, 100 step programmable	59.90
NOVOUS 6010 8 digit conversion	21.50
NOVOUS 6020 8 digit financial	33.50
NOVOUS 6025 8 digit financial, 100 step programmable	59.90
NOVOUS 6030 8 digit statistical	38.00
NOVOUS 6035 8 digit statistical, 100 step programmable	59.90

ORDINARY

	£
DECIMO VATMAN green	9.75
SUPER VATMAN green, M. %	14.95
ROCKWELL 8R	7.50
ROCKWELL 20R, M. %	12.50
ROCKWELL 21R, M. %	14.80
ROCKWELL 31R, V	16.95
ROCKWELL 51R, Metric	27.50
NOVOUS 850	6.50
NOVOUS 826	7.90
NOVOUS QUIZ KID	8.95
TEXSAS + 1200	7.50
TEXSAS + 1250	9.95
TEXSAS SR10	19.95
CBM 774D	5.80
CBM 766D	6.40
CBM 976D	8.75
CBM 887D, M. %	9.50
CBM 976R, M. %	10.95
CBM 989R	12.90
SINCLAIR CAMBRIDGE	8.75
SINCLAIR CAMBRIDGE Memory	11.95
SINCLAIR OXFORD 100	8.95
SINCLAIR OXFORD 200	13.95

RANGE OF CALCULATORS

THE NEW DECIMO DIGITAL CLOCK RADIO AS ON TV



Recommended price £50
Our price £35.90 inc. VAT plus £1 packing

What is unique about this beautiful Clock Radio? Besides being a first class AM and FM radio, it is its unique 1 1/2 inch computer type display. You don't have to fret about the irritating blip or pulsating glare of other types of clock radios—this has a soft, restful and silent orange glow, with a dimmer to adjust its brightness to suit your taste.

Just look at these superb features!

- Unique light emitting 1 1/2 inch computer-type orange numerals are large, clear and easy to read from across the room and can be seen from any angle.
- Time setting can be done clockwise or anti-clockwise. Wake-to-music or Wake-to-alarm system.
- Touch 'N' drowses—to give you extra minutes to sleep without re-setting the buzzer alarm.
- Sleep switch shuts off radio automatically. Adjustable up to 80 minutes. Lets you go to sleep to music.
- Electronic 12-hour alarm that can be set at 10 minute intervals.
- Dimmer switch for time display brightness control.
- Radio features highest quality components. Solid state circuitry and advanced engineering for crisp, clean sound in full tonal range. Convenient top-mounted push-button controls.
- Side mounted tuning control knob. Front mounted tone and volume slide controls.
- Precision variable tuning slide rule dial with back-lit green-lighted log scale, also lighted pointer for easy and accurate tuning. Continuous slide type tone control for adjusting tone and bass response.
- Switchable automatic frequency control (A.F.C.) On FM. Switch in for drift-free listening. Switch-out for precision tuning. Automatic gain control (A.G.C.) on MW stabilises signal.
- Three-inch top-mounted speaker to float sound around the room.
- Dual built-in FM antennas. One on line cord, and an indoor line-wire tube for hard-to-get FM stations.
- Built-in ferrite rod antenna for MW.
- Output jack to accommodate optional earphone. Pillow or auxiliary speaker.
- Charcoal Grey high impact resistant-styrene cabinet, with Teak finish and silver front.
- Dimensions 4in H. 12 1/2in W. 6 1/2in D. Power: Source AC 240 Volts. 50 Hz.

Although correct at time of going to press prices may be subject to alteration without notice. Please add 8% VAT to total plus 55p postage.

PHONE CALLS AND PERSONAL CALLERS WELCOME
MONDAY-THURSDAY BETWEEN 2 and 5 p.m.

To: BARCLAY ELECTRONICS Dept. 2PE
STANLEY HOUSE, 1115 FINCHLEY ROAD, LONDON N.W.11

Please send me
with/without optional mains adaptor. I enclose cheque/money order
total value £ Including 55p to cover packing.
NAME
ADDRESS

FRONTIER

POSSIBLY THE MOST ACCURATE FULL 6 FUNCTION L.E.D. QUARTZ CRYSTAL WRISTWATCH ON THE MARKET TODAY
This offer can continue only to the 31st Dec.



ONLY £34.50 +8% VAT

- FULL 6 FUNCTIONS (do not confuse with cheaper 2, 3 or 4 function watches) ● Single button operation
- Displays hours, minutes, seconds, month, date of month
- ULTRA ACCURATE to less than 1 second a week
- Easily readable, bright L.E.D. display
- Automatic 3 second HOLD and FADEOUT display
- AUTOMATIC COMPUTERIZATION for 28, 30 and 31 day month. ● Top quality stainless steel. ● Manufacturer's full 1 year guarantee. ● Arrives in free presentation gift box. ● Includes BEAUTIFUL MATCHING STAINLESS STEEL BRACELET. ● Replace battery only once a year. ● Water and shock resistant. ● Anti-magnetic. ● Silent.

SCOOP! AUDIO MAGNETIC GOLD LABEL BLANK CASSETTES—Price per box of ten: C60 £3.00, C90 £4.20, C120 £5.40. Post 22p per order

ALL GOODS ARE FULLY GUARANTEED. IF NOT SATISFIED MONEY REFUNDED IF RETURNED UNDAMAGED WITHIN 7 DAYS

RTVC


FOR SPEAKERS AT FANTASTIC REDUCTIONS

ELIZABETHAN STEREO TUNER AMPLIFIER

This compact Tuner Amplifier gives you full medium wave and V.H.F. coverage and FM stereo. With inputs for your turntable and tape recorder. It has rotary tuning, Volume, Balance, Bass and Treble controls and push button selection switches for Phono/tape FM Stereo, FM mono, Medium wave and A.F.C. has built-in stereo beacon and switched headphone socket.

Technical Specifications
15 transistors, 11 diodes, integrated circuit.

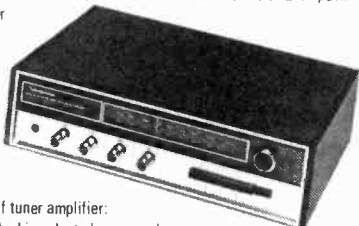Power output 8 watts. Size of tuner amplifier: 4" x 10" x 15½" approx. Finished in selected rosewood veneer with brushed aluminium front panel and matching controls.



£29.00
+p & p £1.50

THE 'COMPACT'

EASY BUILD SPEAKER KIT

A compact bookshelf speaker system giving a high electro acoustic efficiency for the low powered amplifier. The professional finish can be obtained with the minimum of tools, the infinite baffle type enclosures come ready mitred and professionally finished, simply apply glue, fold up around baffle board, and fix together with masking tape till glue dries. The cabinet measures 12"x9"x5" deep approx finished in simulated teak, incorporating a quality 7"x4" elliptical speaker, power handling 4 watts, flux density 30,000 maxwells, impedance 8-15 ohms nominal, voice coil dia ¾" magnet size 2½" approx.



£6.00
pair inclusive, P & P £1.70

EASY TO BUILD SPEAKER KITS

These superb simulated teak-finished speaker kits have been specially designed by RT-VC for the cost-conscious hi-fi enthusiast who wants top quality speakers but doesn't want to spend the earth. Built to EMI's exacting specification, these new RT-VC speaker kits (350 type kit) incorporate 13" x 8" woofer, 3¼" tweeter and matching crossover.

Easily put together with just a few basic tools. **Specification (each speaker):** Impedance 8 ohms. Power handling 15 watts RMS (30 watts peak). Response 20-20,000 Hz. Size 20" x 11" x 9½" approx. Comparable built units (EMI LE3) sold elsewhere for over £45 pair.




£22.00 pair complete +£5.20 p & p.

Complete with crossover Components and circuit diagram

STEREO CASSETTE TAPE DECK

This compact stereo cassette deck is designed to link up with your stereo system. It incorporates features normally found in machines costing far more, these include large illuminated recording level meters, slider level controls, Chromium Dioxide (CrO₂) selector switch, pause control, and autostop, tape/digit counter, Din or Phono connections, two mic. inputs and outputs for your stereo headphones.

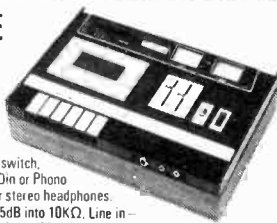

£35.00
+p & p £1.50

Technical Specifications - Input level Mic - 65dB into 10KΩ. Line in - 20dB into 1MΩ. DIN - 47dB into 100KΩ. Output levels Line out - 500mV 10KΩ. DIN - 500mV 10KΩ. Frequency response - Normal 50-10KHz. Chrome 50-14KHz. Signal noise ratio - better than 40dB.

RTVC*

VISCOUNT IV STEREO SYSTEM

System 1a. £69.00

The new 20+20 watt Stereo Amplifier incorporating the latest silicon transistor solid state circuitry, the RT-VC VISCOUNT IV gives you a powerful 20 watts RMS per channel into 8 ohms. Superb teak-finished cabinet, with anodised fascia to harmonise with any decor. Polished trim and knobs.

The VISCOUNT IV has a comprehensive range of controls - volume, bass, treble, balance, mono/stereo, mode selector, and scratch filter.

Front panel socket for stereo headphones. And a host of sockets at the rear - for left and right speakers, tape recorder, auxiliary, tuner, disc and microphone.

SPECIFICATION: 20 watts RMS per channel 40 watts peak. Suitable 8-15 ohms speakers. Total distortion @ 10 watts better than 0.2%. Six switched inputs: 1. Magnetic P.U. - 3 millivolts @ 47 K ohms (R.I.A.A.); 2. Crystal/ceramic P.U. - 50 millivolts @ 50 K ohms (R.I.A.A.); 3. 4. 6. Tape Tuner/Aux. - 140 millivolts @ 50 K ohms (flat frequency response); 5. Microphone - 3 millivolts @ 50 K ohms (flat frequency response).

CONTROLS: Push button ON/OFF, stereo/mono, scratch filter. 6 position rotary selector. Individual rotary controls for treble, bass, balance and volume. Headphone socket, tape out socket. Aux. mains output. Frequency response: 25 Hz to 25 KHz @ full rated output. Signal to noise ratio: better than -50 dB on all inputs. Tone control range: Bass ± 15 dB @ 50 Hz; Treble ± 12 dB @ 10 KHz. Power requirements: 200-250V A.C. mains @ 60 watts. Approx. size: 15¼" x 3" x 10".

MP60 type deck with magnetic cartridge, de luxe plinth and cover.

Two Duo Type IIa matched speakers - enclosure size approx. 19¼" x 10¾" x 7¼" in simulated teak. Drive unit 13" x 8" with 3" tweeter. 15 watts handling 30 watts peak.

Complete System with these speakers **£69.00** +£6.50 p & p.

System 2. £85.00

Viscount IV amplifier (As System 1a)
MP60 type deck (As System 1a)

Two Duo Type III matched speakers

- Enclosure size approx. 27" x 13" x 11½". Finished in teak simulate.

Drive units 13" x 8" bass driver, and two 3" (approx.) tweeters. 20 watts RMS. 8 ohms frequency range - 20 Hz to 18,000 Hz.

Complete System with these

speakers **£85.00** +£7.60 p & p.

PRICES: SYSTEM 1a
Viscount IV R103 amplifier £27.50 +£1.90 p & p.
2 Duo Type IIa speakers £30.00 -£6.50 p & p.
MP60 type deck with Mag. cartridge de luxe plinth and cover £22.00 +£3.30 p & p.
Total if purchased separately: £79.50
Available complete for only: **£69.00** +£6.50 p & p.

PRICES: SYSTEM 2
Viscount IV R103 amplifier £27.50 +£1.90 p & p.
2 Duo Type III speakers £46.00 +£7.50 p & p.
MP60 type deck with Mag. cartridge de luxe plinth and cover £22.00 +£3.30 p & p.
Total if purchased separately: £95.50
Available complete for only **£85.00** +£7.60 p & p.



20x20 SYSTEM

Scotland and the Orkneys P & P Surcharge
System 1a £1.75 System 2 £3.50

PUSH BUTTON CAR RADIO KIT— THE TOURIST TT*



NO SOLDERING REQUIRED

NOW BUILD YOUR OWN PUSH BUTTON CAR RADIO

Easy to assemble construction kit comprising fully completed and tested printed circuit board on which no soldering is required. All connections are simple push fit type making for easy assembly. Fine tuning push button mechanism is fully built and tested to mate with printed circuit board.

TECHNICAL SPECIFICATION: (1) Output 4 watts RMS output. For 12 volt operation on negative or positive earth. (2) Integrated circuit output stage, pre-built three stage IF Module.

Controls volume manual tuning and five push buttons for station selection, illuminated tuning scale covering full, medium and long wave bands. Size chassis 7" wide 2" high and 4 1/2" deep approx. **£9.50** + £1.05 p & p. Speaker including baffle and fixing strip **£2.00** + 45p p & p. Car Aerial Recommended — fully retractable **£1.60** + 40p p & p.

The Tourist 1 Kit For the experienced constructor. If you can solder on a printed circuit board you can build this model. Same technical specification as Tourist TT. **Price £8.20** + £1.05 p & p.

*STEREO 21 QUALITY SOUND FOR LESS THAN £24.00



Stereo 21, easy to assemble audio system kit. No soldering required.

The unit is finished in white P.V.C. and the acrylic top presents an unusually interesting variation on the modern deck plinth.

Includes — BSR 3 speed deck, automatic, manual facilities together with stereo cartridge.

Two speakers with cabinets.

Amplifier module. Ready built with control panel, speaker leads and full, easy to follow assembly instructions.


Specifications — For the technically minded:

Input sensitivity 600mV. Aux. input sensitivity 120mV. Power output 2.7 watts per channel. Output impedance 8–15 ohms. Stereo headphone socket with automatic speaker cutout. Provision for auxiliary inputs — radio, tape, etc., and outputs for taping discs. Overall Dimensions. Speakers approx 15 1/2" x 8" x 4". Complete deck and cover in closed position approx. 15 1/2" x 12" x 6".

Complete only £23.20 + £3.00 p & p.

Extras if required. Optional Diamond Stylus **£1.60**. Specially selected pair of stereo headphones with individual level controls and padded earpieces to give optimum performance **£5.80**.

*DISCO AMPLIFIER

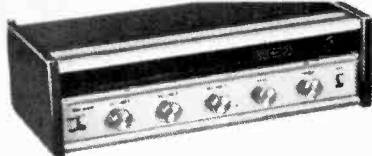

Reliant Mk IV Mono Amplifier, ideal for the small disco or house parties. Output 20 watts RMS into 8 ohms (suitable for 15 ohms).

Inputs * 4 electrically mixed inputs. * 3 individual mixing controls. * Separate bass and treble controls common to all 4 inputs. * Mixer employing F.E.T. (Field Effect Transistors). * Solid State circuitry. * Attractive styling.

INPUT SENSITIVITIES — Input — 1). Crystal mic. guitar or moving coil mic. 2 and 10mV. (Selector switch for desired sensitivity.) — Inputs — 2), 3), 4). Medium output equipment — ceramic cartridge, tuner, tape recorder, organs, etc. — all 250mV sensitivity. AC Mains, 240V operation. Size approx: 12 1/2" x 6" x 3 1/2".

£20.00 + £1.35 p & p.

8 TRACK HOME CARTRIDGE PLAYER



Elegant self selector push button player for use with your stereo system. Compatible with Viscount IV system, Unisound module and the Stereo 21. Technical specification Mains input, 240V. Output sensitivity 125mV.

Yours for only

£16.20 + £1.70 p & p.


BUILD YOUR OWN STEREO AMPLIFIER*



For the man who wants to design his own stereo — here's your chance to start, with Unisound — pre-amp, power amplifier and control panel. No soldering — just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum. 240V. AC only.

Also available with 2 speakers (7" x 4") **£10** + £1.75 p & p. **£8.95** + £1.05 p & p. Also available with the "Compact" (see opposite page) easy build speaker kit **£13.50** + £2 p & p.

PORTABLE DISCO CONSOLE*

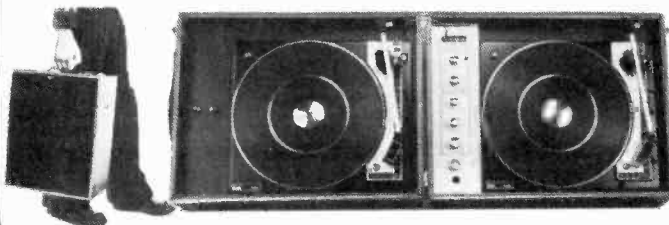

INCORPORATES: Pre-Amp with full mixing facilities, including switched input for mic with volume control, switched input for auxiliary with volume control, bass and treble controls, volume control and blend control for turntables. Two* B.S.R. MP60 type single play professional series decks, fitted with crystal cartridges.

TECHNICAL SPECIFICATION:

Pre amp — Output — 200mV. Auxiliary inputs — 200mV and 750mV into 1 meg. Mic input — 6mV into 100K. 240 volt operation. Turntables capacity — 7", 10" or 12" records. Rumble, wow and flutter Rumble Better than — 35dB. Wow Better than 0.2% Flutter Better than 0.06% (Gaugmont kalee meter). Finish — Satin black mainplate with black turntable mat inlaid with brushed aluminium trim. Tonearm and controls in black and brushed aluminium.

Console size —

Unit Closed — 17 1/2" x 13 1/2" x 8 1/2" (app.) Unit Open — 35 1/2" x 13 1/2" x 4 1/2" (app.) This disco console is ideally matched for the Reliant IV and Disco 50 or any other quality amplifier. The unit is finished in black PVC with contrasting simulated teak edging, diamond spun control knobs with matching control panel.

Yours for only

£49.00 + £6.50 p & p.

All prices include VAT at current rates



DO NOT SEND CARD

Just write your order giving your credit card number

Mail orders to Acton. Terms C.W.O. All enquiries stamped addressed envelope. Goods not despatched outside U.K.

Leaflets available for all items listed thus* Send stamped addressed envelope. All items subject to availability. Prices correct at 1st Dec. 1975 and subject to change without notice.

Minimum order on ACCESS/BARCLAYCARD — £11.




21D HIGH STREET, ACTON, LONDON W3 6NG
323 EDGWARE ROAD, LONDON W2

Personal Shoppers EDGWARE RD: 9 a.m.—5.30p.m. Half day Thurs
ACTON: 9.30a.m.—5p.m. Closed all day Wed.

100 WATTS!

HY200

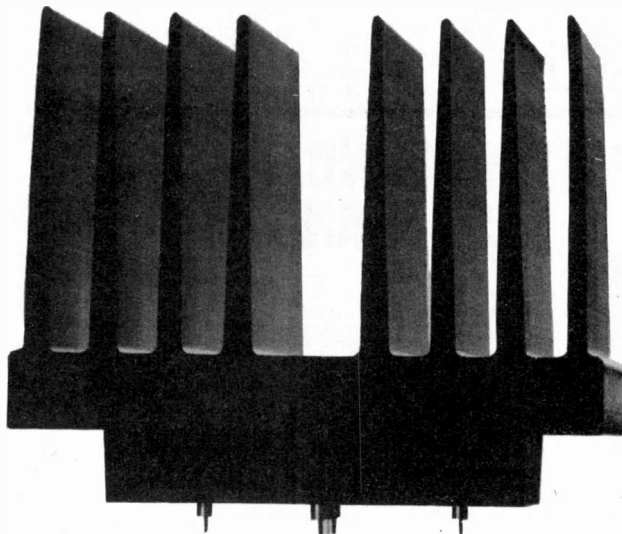

The HY200 is a 100 watt amplifier of hybrid construction with an integral heatsink. Internally the HY200 features open and short circuit protection with the added feature of thermal shutdown when the heatsink rises above a predetermined temperature, with these features the HY200 can be installed into any equipment with the confidence that it is virtually indestructible under any operating conditions. The low distortion and high signal to noise ratio together with wide band width makes the HY200 an amplifier of true Hi-Fi performance and these factors coupled with its robustness make it suitable for Hi-Fi, Group, Disco, PA, etc.

Specification

Output power 100 watts into 8 Ω . Input sensitivity 500mV R.M.S. Input impedance 100k Ω . Signal/noise ratio 96dB at 100 watts. Power bandwidth 10Hz-45kHz -3dB. Distortion 0.05% typical. Weight 1kg (2.2lb).

£21 - 20

plus £5.30 VAT. P. & P. free

Power supply PSU90 for one HY200 output 45-0-45V d.c. at 2 amps.

£10 - 56

plus £2.64 VAT. P. & P. free

TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS

I.L.P. Electronics Ltd.
Crossland House,
Nackington, Canterbury
Kent CT4 7AD
Tel (0227) 63218

Please supply

Total Purchase price

I Enclose: Cheque Postal Orders Money Order

Please debit my Access account Barclaycard account

Account number

Name and Address

.....

Signature

ENTER
* THE

BI-PAK

GREAT
CHRISTMAS
COMPETITION!

WIN A 22"
COLOUR T.V.
FREE!



2nd Prize: A complete Hi-Fi outfit comprising a Legationaire Amplifier, Record Deck and EMI Speaker Kits.

3rd Prize: Black and White Mains/Battery Television.

4th Prize: An Electronic Calculator.

Plus: 49 runner-up prizes of Electronic Slide Rules.

1. UNIJUNCTION TRANSISTOR
2. ELECTROLYTIC CAPACITOR
3. THERMISTOR
4. HEXODDE VALVE
5. DIAC
6. LIGHT DEPENDENT RESISTORS
7. GAS FILLED DISCHARGE TUBE
8. FIELD EFFECT TRANSISTORS
9. NPN TRANSISTOR
10. CAPACITOR
11. L.F. CHOKE
12. MICROPHONE
13. THERMO-COUPLE
14. AERIAL (GENERAL)
15. EARTH
16. NEON
17. ZENER DIODE
18. TETRODE VALVE
19. PNP TRANSISTOR
20. RESISTOR (VARIABLE)
21. SELENIUM CELL
22. AERIAL (TRANSMITTING)
23. PRESET RESISTOR
24. ELECTRO MAGNET
25. PLUG AND SOCKET
26. FUSE
27. SILICON CONTROLLED RECTIFIER
28. RECTIFIER
29. SPARK GAP
30. COAXIAL PLUG & SOCKET

HOW TO ENTER

You are allowed one line for every £1 spent with Bi-Pak. Opposite you will find illustrated, 20 electronic symbols. Just choose the correct descriptions for these from the 30 alternatives shown and enter the numbers of the descriptions in the entry coupon alongside the letter indicating the symbol—should you need more columns you will find a coupon in every electronic publication. Then write a slogan of not more than 10 words but including the name BI-PAK.

RULES

There is no entry fee but one line is allowed for every £1 spent with BI-PAK (SEE OUR ADVERTISEMENT ON PAGES 6-7). Every entry must be made on a proper entry coupon and must bear the entrant's full name and address.

All accepted entries will be examined and the Adjudicating Committee will award the FIRST PRIZE of a COLOUR TELEVISION to the competitor they consider to show the correct answers and who submits the best slogan. The remaining prizes will be awarded for the next best entries in order of merit.

Closing date February 29th. Entries arriving after the closing date will be disqualified, as will any received incomplete, illegible, mutilated or altered or not complying with the instructions and rules exactly. No responsibility can be taken for entries lost or delayed in the post or otherwise. Proof of posting will not be accepted as proof of receipt. All decisions of the Adjudicating Committee will be final and legally binding. No correspondence will be entered into. Winners will be notified and the result published in the earliest possible issues of this magazine.

The competition is open to all except employees (and their families) of Bi-Pak Semiconductors. We regret that this competition is restricted to U.K. residents only. Entrants must agree to abide by the rules of the competition.

All entries become the property of Bi-Pak Semiconductors and any slogan submitted may be used at the discretion of the company.

A	B	C	D	E	F	G	H	I	J										
K	L	M	N	O	P	Q	R	S	T										
A	B	C	D	E	F	G	H	I	J	K	L	M	N	O	P	Q	R	S	T


SLOGAN

Name

Address

P.E.

SEND TO BI-PAK, P.O. BOX 6, WARE, HERTS

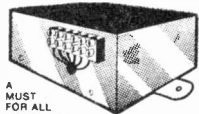

P.E. SCORPIO MK II ELECTRONIC IGNITION

DIRECT FROM MANUFACTURER
SAVE PETROL—SAVE MONEY

The improved Scorpio Mk II Dual Capacitive Discharge Electronic Ignition Unit.

This unit features one of the best tried systems on the market, giving: more miles per gallon; longer life for points, plugs, battery; easier starting; smoother running, etc.

Available in 12V or 6V version. Both models used on either positive (+) or negative (-) earth cars.

The Scorpio—tested and guaranteed with full installation instructions. (Including post, packing and VAT) State 12V or 6V when ordering.

E. & A. PRODUCTS
Barrow Hill, Chesterfield, Derbyshire
Tel. Staveley (024-687) 3758


N.S.E. KITS

- 3 CHANNELS—3,000 WATTS
- *High sensitivity
 - *Stabilised supply
 - *Easy to follow instructions
 - *Ready-drilled fibre-glass board
 - *Top quality components
 - *Scintillating performance
 - *Advanced silicon circuitry
 - *Isolated input—accepts all amplifiers
- £12.50 inc. VAT, post and packing

329 WHITEHORSE ROAD,
CROYDON, SURREY, CR0 2HS

- FOUR CHANNEL MIXER
- *Four high impedance inputs
 - *Wide range tone controls
 - *Fibre-glass drilled board
 - *Low-noise circuitry
 - *Suit discotheques, groups, etc.
 - *Easy to follow instructions
 - *Carbon film resistors
 - *Electronic mixing—no interaction
- £12.50 inc. VAT, post and packing

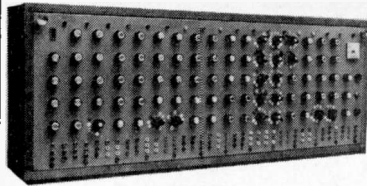C.O.D. or C.W.O. We accept Access and Barclaycard
Just telephone 01-684 0098 with your number



SYNTHESISERS AND KEYBOARDS


P.E. JOANNA

(P.E. May to Aug. 1975)

The new electronic piano that has switchable alternative voicing of Piano Honky-Tonk and Harpsichord. All PCB's are "as published".

- Power Supply** £8.85
- Tone Generator and Top C Envelope Shaper** £10.26
- PCB (for above)** £1.30
- Envelope Shapers** £32.16
- 12 sets (full requirement)** £15.00
- Set of 12 PCB's (full requirement)** £7.99
- Voicing and Pre-Amplifier Circuits** £1.80
- PCB for above circuits**

Remaining circuits: prices in lists.

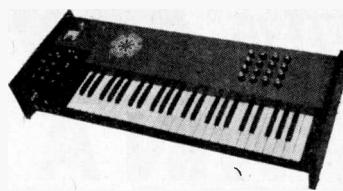

P.E. MINISONIC

(P.E. Nov. 1974 to March 1975)

A portable, battery or mains operated, miniature sound synthesiser, with keyboard circuits. Although having slightly fewer facilities than the large P.E. Synthesiser, the functions offered by this design give it great scope and versatility.

P.E. SYNTHESISER

(P.E. Feb. 1973 to Feb. 1974)

The well acclaimed and highly versatile large-scale mains-operated Sound Synthesiser complete with keyboard circuits. All function circuits may be used independently, or interconnected. The greater the number of circuits, the greater the versatility. Other circuits in our lists may be used with the Synthesiser to good advantage.

THE MAIN SYNTHESISER

- Stabilised Power Supply** £12.05
- Two Linear Voltage Controlled Oscillators and one Inverter—all 3 circuits:** £16.28
- PCB (2 are required)—each** £1.48
- Two Ramp Generators and Two Input Amplifiers—all 4 circuits** £5.62
- PCB (holds all 4 circuits)** £1.38
- Sample-and-Hold and Noise Generator—PCB (holds both circuits)** £6.52
- Tone Control, £2.43; PCB, 72p** £1.64
- Reverberation Amplifier** £6.26
- Sprinkle Line unit for Reverb Amp** £4.95
- Ring Modulator** £3.44
- Peak Level Meter Circuit** £1.50
- 100µA Panel Meter** £3.75
- PCB for Rev., R-Mod. & Meter Ccts., Envelope Shaper, £5.24; PCB, £1.42** £1.86
- Voltage Controlled Amp. and Diff. Amp. PCB (holds both circuits)** £6.70
- PCB (holds both circuits)** £1.26

- THE SYNTHESISER KEYBOARD CIRCUITS** can be used without the Main Synthesiser to make an independent musical instrument)
- 2 Log. Voltage Controlled Oscillators** £14.51
- PCB for both log VCO's** £2.32
- Divider, 2 Hold Circuits, 2 Modulation Amplifiers, Mixer and 2 Envelope Shapers** £19.46
- PCB (Holds the first 6 circuits)** £1.80
- PCB for both Envelope Shapers** £1.50
- Keyboard Stabilised Power Supply** £7.30
- Printed Circuit Board** 94p

Kimber-Allen Keyboards as required for many published circuits including the P.E. Joanna, P.E. Minisonic and P.E. Synthesiser. The manufacturers claim that these are the finest moulded plastic keyboards made.

- 3 Octave Keyboard (37 notes C to C)** £20.50
- 4 Octave Keyboard (49 notes C to C)** £23.50
- 5 Octave Keyboard (61 notes C to C)** £27.00
- Contact Assemblies for use with above keyboards:**
- Single-pole change-over (SP) as for P.E. Joanna and P.E. Minisonic. Two-pole normally-open make-break (2P) having 4 poles, 3 of which are normally-open make-break contacts and the fourth is a change-over contact—this special assembly enables the same keyboard to be used with the P.E. Synthesiser, P.E. Minisonic, and P.E. Synthesiser simultaneously thus avoiding the cost of more than one keyboard.**

Contact	Each	3 Octave Set	4 Octave Set	5 Octave Set
SP	20p	£7.40	£9.80	£12.20
2P	24p	£8.88	£11.76	£14.64
4PS	48p	£17.76	£23.52	£29.28

Printed Circuit Boards for use with the above contacts and thus eliminating most of the inter wiring required, are available—details in our lists.

KEYBOARDS

PHONOSONICS

FOR ADDRESS, INFORMATION REGARDING POST AND PACKING, VAT, LISTS, AND EXPORT TERMS SEE OUR OTHER ADVERTISEMENT ON OPPOSITE PAGE

Photos: 2 of our units containing some of the P.E. projects built from our kits and PCBs. (The cases were built by ourselves and are not for sale.)

ELECTROVALUE

The good components service

In relatively few years, Electrovalue has risen to a position of pre-eminence as mail-order (and industrial) suppliers of semi-conductors, components, accessories, etc. There are wide ranges and large stocks to choose from as well as many worthwhile advantages to enjoy when you order from Electrovalue.

CATALOGUE 8 NOW READY

Enlarged to 144 pages. New items. Opto-electronics, Diagram of components, applications, I.C. circuits, etc. Better than even No. 7. Post free 40p, including voucher for 40p for use on order over £5.00 list value.

DISCOUNTS

On all C.W.O. mail orders, except for some items marked NETT. on orders list value £5 or more **5%** on orders list value £15 or more **10%**

FREE POST AND PACKING

On all C.W.O. mail orders in U.K. over £2 list value. If under, add 10p handling charge.

PRICE STABILIZATION POLICY

Prices are held and then reviewed over minimum periods of 3 months.

QUALITY GUARANTEE

On everything in our Catalogue—No manufacturers rejects, seconds or sub-standards merchandise.

ELECTROVALUE LTD

All communications to Dept. 2/1, 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB. Telephone Egham 3603, Telex 284475. Shop hours 9.5-3.30 daily, 9-1 pm Sats.

NORTHERN BRANCH: 680 Burnage Lane, Burnage, Manchester M19 1NA. Telephone (061) 432 4945. Shop hours Daily 9-5.30 pm; 9-1 pm Sats.

P.C. ETCHING KIT Mk. II

Contains 1lb Ferric Chloride, 100 sq.in copper clad board, DALO quick-dry etch resist, pen, abrasive cleaner, etching dish, 2 miniature drills and instructions. £3.65.

7lb BARGAIN PARCELS

Hundreds of new components—pots, resistors, capacitors, switches, PC Boards with transistors and diodes, loads of odds and ends. Only £3.25.

COMPUTER PANELS

Large quantity always available. 3lb asstd. £1.75; 7lb £3. Pack with at least 50 transistors, about 500 components altogether £1. 12 high quality panels with power transistors, IC's, multivibrator trim-pots, etc. £2.80.

FERRIC CHLORIDE

Anhydrous technical quality in 1lb double sealed packs, 1lb 90p; 3lb £1.90; 10lb £4.80; 100lb £35.50

TRANSFORMERS

All have mains primaries. 6-0-6V 100mA 90p; 9-0-9V 100mA 95p; 12-0-12V 100mA £1; 12-0-12V 50mA 85p; 20V 55mA 85p; 24-0-24V 500mA £2.95; 30V 1A multi-tapped to give 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24 or 30V, or 12-0-12V, or 15-0-15V £3.20. 2A version £4.50; 30-0-30V 1A £3.30.

RESISTOR AND CAPACITOR PACKS

400 asstd. carbon resistors £1.50. 250 Hi-stab. 1%, 2, 5%, £1.40. 100 Wirewounds 2W-15W £2. 200 Miniature 1/2, 1 and 1/2W, mostly carbon film £1.10. 200 ceramic, mica, etc. caps £1.15. 100 Polyester, 0.01-1mfd £1.30. 200 Miniature electrolytics, mostly unmarked so only £1.35. 15 airspaced and compression trimmers £1.10.

JUMBO PACK—1 each of the above—

£10.90 value for only £8.50!!!

8 PIN DIL 741'S

10 + 28p; 25 + 23p; 100 + 21p each.

All prices quoted include VAT and UK/BFPO postage. SAE with enquiries or for list. Send 10p stamp for Multimeter Booklet (free on orders over £3). Surplus components and equipment wanted for cash.

GREENWELD (PE1)

51 Shirley Park Road, Southampton. SO1 4FX. Tel (0703) 772501. Also callers at 21 Deptford Broadway, SE8. Tel. 01-692 2009, and 38 Lower Addiscombe Road, Croydon. Tel. 01-688 2950.

BARGAIN PACKS

12 BC107	£1.20	22 1N4002	£1.20
12 BC108	£1.20	20 1N4003	£1.20
12 BC109	£1.20	18 1N4004	£1.20
15 BC148	£1.20	16 1N4005	£1.20
12 BC149	£1.20	14 1N4006	£1.20
12 BC157	£1.20	12 1N4007	£1.20
12 BC158	£1.20	40 1N4148	£1.20
12 BC159	£1.20	3 2N3055	£1.20
2 2N2646	£1.20	1 9N7660	£1.20
10 BC328	£1.20	1 9N76013	ND
12 BF194	£1.20		£1.20
7 BF173	£1.20	4 741C	£1.20
5 BF181	£1.20	2 555	£1.20
12 BF195	£1.20	6 BY103	£1.20
12 BC548	£1.20	16 BC348B	£1.20

555 TIMERS 3 + 55p; 10 + 45p; 25 + 43p each.

TRANSISTOR PACKS

200 asstd. out of spec., mostly unmarked transistors—NPN, PNP, plastic TO5, TO18, TO3 power, AF, RF, etc. About 70% OK. £1.80.

1,000 unmarked 1N4148, 95% OK £4.

100 unmarked untested BC108 £2.10.

10 out of spec. 2N3055 £1.

700N plug-in relay. 4c/o contacts 35p.

90V neons 5p, 10 for 40p, 100 for £3.50.

301A IC only 40p. 2N3442 £1.30.

"PE" Gas Igniter Kit still available at the same price. Only £3.

ODDS AND SODS

Screw mixture—Approx. 500 asstd. screws, 2BA to 5BA + some self-tappers, few nuts and washers, etc. Only £1.

VHF Power transistors. Texas type 2N3375. Only £1.

96kHz Xtal £1.—send for list of Xtals.

Grommet Mixture. Over 150 all shapes and sizes. Only 50p.

800V 1A Bridge Rect., silicon 40p. 400mW Zeners, full range 10p each. 16 pin DIL sockets, gold plated 6 for £1. 8 pin DIL sockets 15p, 8 for £1. BC119/139 Audio Pair 40p. BFY64 12 for £1.20.

4 x 80V 10A rectis. on heat sink, ideal for battery charger £1.25.

SAE for 1% and better resistor list and wholesale list of transistors, etc.

Light Sensor Type H61—Made by Texas, sold for over £4 each. Dark current 0.01µA

Light current 250µA. Only 2-1mm dia. x 15mm long with integral focus lens.

Only 75p, 10 for £5.

ALUMINIUM BOXES—Big range available.

AB13 6 x 4 x 2in 90p

AB11 4 x 2 x 2in 85p

AB7 5 1/2 x 2 1/2 x 1 1/2in 85p

PHONOSONICS

SUPPLIERS OF QUALITY PRINTED CIRCUIT BOARDS, KITS AND COMPONENTS TO A WORLD-WIDE MARKET

SOUND-TO-LIGHT (P.E. Apr./Aug. 71)

The ever-popular AURORA—4 or 8 channels each responding to a different sound frequency and controlling its own light. Can be used with most audio systems and lamp intensities. A MUST for any Disco, and a fascinating visual display for the home.

- 4 channel component set (excl. thyristors) £12-83
- 8 channel component set (excl. thyristors) £22-16
- Power supply component set £4-86
- PCB for 4 frequency channels £3-32
- PCB for power supply and 8 lamp drivers £1-56
- 1 Amp 400V thyristors (1 per chan. requ.) each 75p
- Panel meter (1µA) (optional) £3-75

VOICE OPERATED FADER (P.E. Dec. 73)

For automatically reducing music volume during "talk-over" particularly useful for Disco work or for home-movie shows.

- Component set incl. PCB £2-95

TAPE-NOISE LIMITER

Very effective circuit for reducing the hiss found in most tape recordings.

- Component set (incl. PCB) £2-50
- Regulated power supply (incl. PCB) £3-98

P.E. TUNING FORK

DETAILS IN LIST

GUITAR EFFECTS PEDAL (P.E. July 75)

Will modify an audio signal not only from a guitar but from any audio source, producing 8 different switchable effects that can be further modified by manual controls. Possibly the most interesting of all the low-priced sound effects units in our range.

- Component set with special foot operated switches £6-16
- Alternative component set with panel mounting switches £4-60
- Printed Circuit Board £1-10

HI-FI TAPE-LINK (P.E. Mar./Apr. 73)

Designed for use with reasonable quality tape-decks, this high performance pre-amp includes record, playback and metering circuits.

- Stereo component set (excl. panel meter) £23-48
- Mono component set (excl. panel meter) £14-19
- Power supply component set £5-93
- Stereo main PCB £2-74
- Stereo sub-assembly PCB 98p

VOLTA GE CONTROLLED FILTER (P.E. Oct. 74)

An independently designed VCF that can be used with the P.E. Synthesiser.

- Component set £3-41
- Printed circuit board £1-20

ENVELOPE SHAPER

The new ADSR Envelope Shaper published in P.E. October 1975 and having manual control of its Attack, Release and Sustain functions.

- Component set incl. PCB £3-87

Component sets include all necessary resistors, capacitors, semiconductors, potentiometers and transformers. Fuller details are in our lists.

Transistors	BFY51	22p	2N3055	48p	Integrated Circuits	Zeners	Electrolytic Capacitors (µF/V)	Polyester (µF)	Tantalum (µF/V)	
AC128	20p	BFY52	24p	2N3702	12p	3-3V 400mW	5p 0-47/63	8p 100/40	7p 220/40	71p
AC176	20p	BFY55	24p	2N3703	12p	3-9V 400mW	5p 1-0/63	6p 100/63	13p 2800/100390p	0-01 3p
BC107	13p	ME2955	110p	2N3704	12p	4-7 1W	5p 1-5/63	6p 150/16	6p 330/63	133p
BC108	13p	MJE3055	75p	2N3819	35p	5-1V 400mW	5p 2-2/63	6p 150/63	13p 3300/100390p	0-022 3p
BC109	13p	OC28	60p	2N3823E	39p	5-1V 1W	5p 4-7/63	6p 220/10	6p 4700/16	60p
BC147	12p	OC71	14p	2N4060	12p	5-6V 400mW	5p 6-8/40	6p 220/25	7p 4700/25	75p
BC148	12p	OC72	14p	2N4871	7p	5-6V 1W	5p 10/25	6p 220/25	11p 4700/40	93p
BC149	12p	ORP12	66p	2N5245	51p	6-2V 400mW	5p 10/63	6p 220/40	14p	
BC157	13p	ORP12	66p	2N5777	45p	6-8V 400mW	5p 15/40	6p 220/63	21p	
BC158	13p	ZTX107	72p			9-1V 400mW	5p 22/10	6p 330/10	6p	
BC159	13p	ZTX108	72p	Diodes		10V 400mW	5p 22/25	6p 470/6-3	6p	
BC182L	12p	ZTX501	13p	1N914	4p	11V 1W	5p 33/6-3	6p 470/10	12p	
BC184	12p	ZTX503	13p	1N4001	6p	12V 400mW	5p 33/40	6p 470/25	16p	
BC187	23p	ZTX531	23p	1N4002	7p	15V 1W	5p 33/40	6p 470/40	20p	
BC204	14p	2N706	13p	1N4004	8p	15V 400mW	5p 33/50	6p 500/6-4	48p	
BC209C	14p	2N914	22p	1N4006	9p	15V 1W	5p 47/10	6p 680/6-3	10p	
BC212L	14p	2N1304	22p	1N4007	10p	18V 400mW	5p 47/25	6p 680/25	20p	
BC213	15p	2N2905	27p	OA91	7p	18V 1W	5p 47/40	6p 1000/10	14p	
BC218	29p	2N2907	27p	OA200	8p	20V 400mW	5p 47/63	6p 1000/25	30p	
BC478	29p	2N3503	27p	OA202	8p	20V 1W	5p 100/10	6p 1000/40	54p	
BCY71	22p	2N3057	18p	Z5 (Z1L)	75p	27V 400mW	5p 100/25	6p 220/25	45p	
BFY50	22p	2N3054	66p	Z5171	16p					

LIST
Send S.A.E. with all U.K. requests for free list giving fuller details of PCBs, kits, and other components.
Overseas enquiries for list:
Europe—send 20p.
Other countries—send 30p.

POST AND HANDLING
U.K. orders: under £15 add 22p. over £15 add 40.
Optional: Fee for compensation against loss or damage in post (U.K., Eire & C.I. only): 35p.

VAT
Add 25% (or current rate if different) to full total of goods, post and handling. Overseas—VAT does not currently apply.

Overseas—will be charged extra. minimum charge 70p. Details of kit weights, and postage rates will be sent with list.
Eire and Channel Isles classify as overseas for posting purposes.

MAIL ORDER AND C.W.O. ONLY DON'T FORGET VAT!

RHYTHM GENERATOR

(P.E. Mar./Apr. 74)

Programmable for 64,000 rhythm patterns from 8 effects circuits (high and low bongos, bass and snare drums, long and short brushes, blocks and soft cymbal), and with variable time signatures and rhythm rates. Really fascinating and useful. Tempo, Timing and Logic circuits £12-57
Component set for all 8 effects circuits £1-84
PCB for above circuits (double-sided) £10-49
Set of 4 PCB's to hold all 8 effects £4-74
Simple mixer (no PCB available) £2-76
Alternative mixer with external volume controls and adjustable gain (independently designed), including PCB £9-22
Power Supply, including PCB £6-32

SOUND BENDER (P.E. May 74)

A multi-purpose sound controller, the functions of which include envelope shaper, tremolo, voice operated fader, automatic fader and frequency-doubler.

Component set for above functions (excl. SWs) £6-36
Printed circuit board £1-54
Optional extra—additional Audio Modulator, the use of which, in conjunction with the above component set, can produce "jungle-drum" rhythms.
Component set (incl. PCB) £2-47

PHASING UNIT (P.E. Sept. 73)

A simple but effective manually controlled unit for introducing the "phasing" sound into live or recorded music.

- Component set (incl. PCB) £2-40

PHASING CONTROL UNIT (P.E. Oct. 74)

For use with the above Phasing Unit to automatically control the rate of phasing.

- Component set (incl. PCB) £3-65

P.E. JOANNA

SEE OUR ADVERTISEMENT ON OPPOSITE PAGE

WIND AND RAIN UNIT

A manually controlled unit for producing the above-named sounds.

- Component set incl. PCB £2-63

POWER SUPPLIES

Sophisticated low-noise highly-stabilised power supply kits complete with PCB's and detailed information are now available. Details in list.

Other PCBs (all "as published") While stocks last
Bench Power Supply (P.E. Sept. 1974) 70p

CCTV:

Master Logic, Video Amp., Sync Mixer and Cathode Switch PCB (P.E. Oct. 1974) £2-20
PCB for remaining Circuits (P.E. Oct. 1974) £2-20
Digital Power Supply (P.E. Aug. 1972) 50p

Electronic Piano:

Pre-amp PCB (P.E. Oct. 1972) 85p
Power Supply PCB (P.E. Oct. 1972) 60p
Power Slaves: Power Supply PCB (P.E. Aug. 1974) 55p

Rondo:

CBS SQ Decoder PCB (P.E. Sept. 1973) 60p
Pre-Amp PCB (P.E. Oct. 1973) 60p
Tone, Balance and Volume Control PCB (P.E. Oct.) £1-40

BIOLOGICAL AMPLIFIER (P.E. Jan./Feb. 73)

Multi-function circuits that, with the use of other external equipment, can serve as lie detector, alphaphone, cardiophone, etc.

- Pre-Amplifier Module £3-60
- Component set and PCB

Basic Output Circuits

Combined component set with PCBs, for alphaphone cardiophone, frequency meter and visual feedback lamp driver circuits £5-31

Audio Amplifier Module

- Type PC7 £5-50

SINE AND SQUARE WAVE GENERATOR (P.E. July 75)

Suitable for audio, digital, or general purpose. Controllable through 4 decade ranges 10Hz to 100kHz. Switched attenuation through 10 ranges from 10V to 1mV peak-to-peak.

- Component set £7-16
- PCB for above components £1-55
- Power Supply £6-32
- PCB for Power Supply 72p

P.E. MINIMIX 6

DETAILS IN LIST

REVERBERATION UNIT (P.W. Nov./Dec. 72)

A high quality unit having microphone and line input pre-amps, and providing full control over reverberation level.

- Component set (excl. spring unit) £7-49
- Printed circuit board £1-66
- 9 inch spring unit £4-95
- Panel meter (50µA) (optional) £3-75

ULTRASONIC TRANSMITTER-RECEIVER

(P.E. May 1972). A highly sensitive, tight-beam, long-range, "invisible beam" detection circuit with numerous applications.

- Component set with PCBs but excluding transducers £4-60

SEMI-CONDUCTOR TESTER (P.E. Oct. 73)

Essential test equipment for the enterprising home constructor. While stocks last.

- Set of resistors, capacitors, semiconductors, potentiometers, makaswitches and PCB £7-96
- Panel meter (500µA) £3-75

PHOTOPRINT PROCESS CONTROL (P.E. Jan./Feb. 72)

For colour and B & W, an indispensable dark-room unit for finding exposure, controlling enlarger timing, and stabilising mains voltage.

- Component set (excl. meter) £10-18
- Printed Circuit Board £1-74
- Panel meter (1mA) £3-75

ENLARGER EXPOSURE METER AND THERMOMETER (P.E. Sept. 73)

Dual-purpose dark-room unit with good accuracy. Component set with PCB but excl. meter £4-78
Panel meter (100µA) £3-75

SEE OUR LIST FOR OTHER GOODS STOCKED


Prices are correct at time of press. E. & O.E. deliveries subject to availability.

PRECISION PETITE LTD.


119A HIGH STREET,
TEDDINGTON TW11 8HG

Tel. 01-977 0878

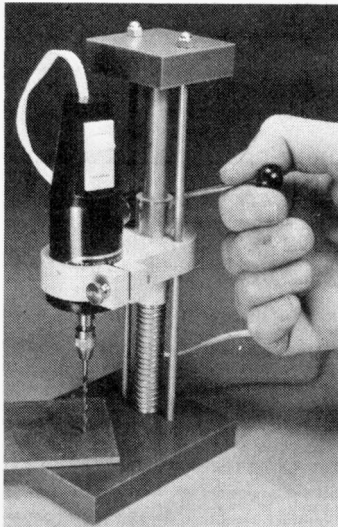INTRODUCING A
MINIATURE
PRECISION 12V. D.C.
DRILL DESIGNED FOR
THE ELECTRONIC
ENGINEER



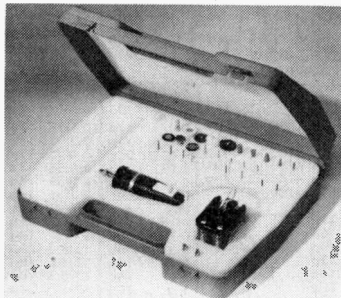Drill only £7.00 p.p. 35p
Stand £3.75 p.p. 58p



Complete kit as illustrated (less batts.) with a variety of 30 tools. Space for Stand and Transformer.

KIT 30 TOOLS £15.01 p.p. 75p
STAND £3.76 p.p. 58p
TRANSFORMER £5.50 p.p. 75p

S.A.E. FOR DETAILS

OSMABET LTD

We make transformers amongst other things

LOW VOLTAGE TRANSFORMERS

Prim. 200/240V a.c., 5V 1A 50p; 6.3V 1.5A £1.65; 3A £2.10; 6A CT £3.75; 12V 1.5A £2.10; 3A £3.75; 6A CT £3.25; 18V 1.5A CT £3.45; 24V 1.5A CT £3.75; 3A CT £3.25; 5A £3; 8A £11.25; 12A £18.50; 40V 3A CT £7.50; 50V 6A CT £18.75; 25V 2A + 25V 2A £7; 12V 4A + 12V 4A £7.

LT TRANSFORMERS TAPPED SEC. Prim 200/240V 0-10-12-14-16-18V 2A £4; 4A £5.25. 0-12-15-20-24-30V 2A £4.50; 4A £8.75. 0-5-20-30-40-60V 1A £4.85; 2A £8.75. 0-40-60-80-100-110V 1A £7.

MIDGET RECTIFIER TRANSFORMERS

For FW rect. 200/240V a.c., 6.0-0-6V 1.5A or 9.0-0-9V 1A £1.80 each; 12.0-12V 1A, or 20.0-20V 0.75A, or 9.0-0-9V 0.3A, or 12.0-12V 0.25A, or 20.0-20V 0.15A, or 6V 0.5A + 6V 0.5A, or 9V 0.35A + 9V 0.35A, or 12V 0.25A + 12V 0.25A, or 20V 0.15A + 20V 0.15A, all at £2 each.

LOUDSPEAKERS

2 1/2in 8 or 75Ω, 2 1/2in 8 or 25Ω, 3in 3, 8 or 35Ω, 3 1/2in 8, 15 or 80Ω, 95p each; 8 x 5in 3, 8, 15 or 25Ω, £1.75; Goodmans speakers, 5in full throw 8Ω 10W, £4.25; 6 1/2in double cone 4Ω, £3; 12in 25W 4 or 15Ω, £9.

"INSTANT" BULK TAPE/CASSETTE ERASER

Instant erasure any diameter tape spool or cassette, demagnetises tape heads, 200/240V a.c., £3.75.

TAPE RECORDER MOTORS

New, blowers, fans, etc., 110V a.c., 50p (75p pair).

SYNCHRONOUS GEARED MOTORS 200/240V a.c.

Brand new Smiths, built in gearbox, 2 r.p.h., 75p each.

PAPER TUBULAR CONDENSERS

4.7mF, 160V, 30 x 20mm, 20p (100 for £10).

SPEAKER MATCHING AUTO TRANSFORMER

12W, 3 to 8 or 15Ω, up or down, £1.65.

CABLES — CABLES — CABLES

MICROPHONE TWIN H/DUTY, BRAIDED SCREEN

For stage, studio, outdoor, PVC covered 15p per metre.

MULTI WAY SCREENED, PVC COVERED

36 way £1; 25 way 75p; 14 way 50p per metre.

CO-AXIAL CABLE

Cellular standard UHF, white, 75Ω, 10p per metre.

3 CORE CABLE

15A 20p; 6A 15p; 2A 8p per metre. Mini 1A 100 metre drums only £3.

ALL TYPES DOMESTIC AND COMMERCIAL CABLES,

ALL SIZES AND COLOURS CONNECTING WIRES, MULTI SCREENED AND UNSCREENED CABLE, SAE LIST. TRADE ENQUIRIES INVITED.


Carriage and VAT extra on all orders

S.A.E. ENQUIRIES. LISTS. MAIL ORDER ONLY

46 Kenilworth Road, Edgware, Middx. HA8 8YG

Tel. 01-958 9314

INTER LOCKING PLASTIC STORAGE DRAWERS

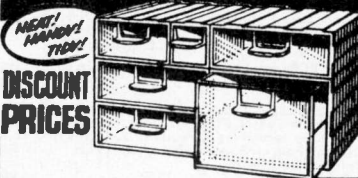

NEW! NORMAN! TRON!
DISCOUNT PRICES

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. 1D and 2D have space dividers. Build up any size cabinet for wall, bench or table top.

BUY AT DISCOUNT PRICES!

SINGLE UNITS (1D) (5ins x 2 1/2ins x 2 1/2ins). £2 DOZEN.

DOUBLE UNITS (2D) (5ins x 4 1/2ins x 2 1/2ins). £3.50 DOZEN.

TREBLE (3D) £3.50 for 8.

DOUBLE TREBLE 2 drawers, in one outer case (6D2), £4.90 for 8.

EXTRA LARGE SIZE (6D1) £4.50 for 8.

PLUS QUANTITY DISCOUNTS!

Orders over £20, less 5%.
Orders over £60, less 7 1/2%.

PACKING/POSTAGE/CARRIAGE: Add 50p to all orders under £10. Orders £10 and over, please add 10% carriage.

QUOTATIONS FOR LARGER QUANTITIES

Please add 8% V.A.T. to total remittance

FLAMLINE (Dept. PE1), 124 Cricklewood Broadway, London, N.W.2.
Tel. 01-450 4844

JC12 AMPLIFIER

6W IC audio amp with free data and printed circuit £2.80. Special offer: only £2.45 if bought with deluxe kit.



DELUXE KIT FOR THE JC12

Includes all parts for the printed circuit and volume, bass and treble controls needed to complete the mono version £2.29. Stereo model with balance control £4.95.

JC12 POWER KIT

Supplies 28V 0.5 amps £3.95.

PREAMP KITS FOR THE JC12

Type 1 for magnetic pickups, mics and tuners. Mono model £1.95. Stereo model £3.45. Type 2 for ceramic or crystal pickups. Mono 95p. Stereo £1.90.
SEND S.A.E. FOR FREE LEAFLET ON KITS

SINCLAIR IC20 AMPLIFIERS

IC20 10 + 10W stereo amp. kit with free booklet and printed circuit £8.58.

PZ20 power supply kit for above £3.91.

VP20 volume, tone control and preamp kit including printed circuits £7.95.

SEND S.A.E. FOR FREE DATA BOOKLET

BATTERY Eliminator Bargains

6-WAY SPECIAL

The most versatile battery eliminator ever offered. Switched output of 3, 4, 6, 7 1/2, 9 and 12V at 500mA £4.95.



3-WAY MODEL

Switched outputs of 6, 7 1/2 and 9V at 250mA with unique 4-way multi-jack plug and socket output connector £2.95.



RADIO MODELS

50mA output with poppet battery connectors for transistor radios, etc. 6V £2.95; 9V £4.05; Double 4 1/2 + 4 1/2V £3.95; 6 + 6V £3.95; 9 + 9V £4.43.



TAPE RECORDER MAINS UNITS. 7 1/2V output complete with 5 pin DIN plug to run cassette tape recorders from the a.c. mains £4.61.

SINCLAIR CALCULATORS

Cambridge	£8.95	MAINS UNITS
Cam. Memory	£13.95	For Oxford Series
Scientific	£13.95	£3.19
Oxford 100	£8.95	For Cambridge, Cam.
Oxford 200	£13.45	Mem. and Scientific
Oxford 300	£22.98	£3.15

CBM CALCULATORS

* 776MD 7 digits/memory/4 function £7.16.
385R 8 digits/constant/4 function/%/rechargeable batteries/complete with charger £10.99.
* 887D 8 digits%/memory/constant £9.95.
SR4148R £43.95. Mains unit for * machines £2.95.

FERRANTI ZN414


IC radio chip with data £1.71. Also available kit of extra parts including printed circuit to complete a radio £3.60. Case £1 extra. Send S.A.E. for free leaflet.

SINCLAIR PROJECT 80

AFU £7.55	FM Tuner £13.25
Z40 £5.75	Stereo decoder for above £8.55
Z60 £7.10	Transformer for PZ8 £5.40
Q16 £9.71	Stereo 80 £9.95
PZ5 £3.95	Project 80S £28.95
PZ6 £8.70	Project 80 Quadraphonic decoder
PZ8 £8.20	£14.95

S-DECS and T-DECS

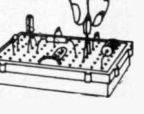S-DeC £2.34.
T-DeC £4.15.
µ-DeC A £4.55.
µ-DeC B £7.85.
IC carriers: 16 dil; plain £1.18; with socket £2.21.
10 T05: plain £1.09; with socket £2.08.



SWANLEY ELECTRONICS

P.O. Box 68, Swanley, Kent BR8 8TQ
Prices include post and VAT.
Official credit orders from schools, etc., welcome.
No VAT charged on overseas orders.

Don't miss your copy of HENRY'S NEW CATALOGUE

only 50p Plus 20p P&P



- ★ OVER 5,000 ITEMS – largest UK range of electronic components for home constructors.
- ★ 200 PAGES – every aspect of electronics and components for amateurs and hobbyists – kits, projects, test gear.
- ★ DOZENS of new lines and new ranges.
- ★ MANY price reductions throughout the new Catalogue.
- ★ A Discount Voucher with every copy, worth 50p.

FREE TO EDUCATIONAL ESTABLISHMENTS when ordered on official notepaper.

Write now for your copy, enclosing 70p remittance

ELECTRONIC FOOTBALL AND TENNIS WITH THE FABULOUS VIDEO SPORT ON YOUR OWN TV

Play three exciting electronic ball games. FOOTBALL, TENNIS. HOLE IN THE WALL on your own TV! Just plug Video Sport into the aerial socket of your TV and away you go. Completely safe for you, your children and your TV. Mains operated.



OUR INCREDIBLE PRICE £29.50 incl. VAT
NOW AVAILABLE AS A KIT £19.50
Demonstrations now in all CENTRES!

AM/FM MODULES

LP1179 LP1171

Combined AM/FM tuner modules, together with a small number of R's and C's and Ferrite Aerial, make up a sensitive FM/MW/LW tuner. 6 Volts supply, supplied with data and circuit sheets.

LP1171 combined IF strip £4.80.
LP1179, FM front end and AM gang £4.60.
£8.42 the pair.
Suitable Ferrite aerial 87p.



UHF TV TUNERS

625 line receiver UHF transistorised tuners U.K. operation Brand new. (Post/packing 25p each).
TYPE A variable tuning slow motion drive £3.50.
TYPE B 4-button push button (adjustable) £4.60.
TYPE C variable tuning £2.90.
TYPE D 6-button UHF/VHF tuner £5.20

BUILD THE TEXAN + FM TUNER TEXAN 20 + 20W STEREO AMP

Features glass fibre PC board, Gardners low field transformer, 8:1 C.s., 10-transistors plus diodes, etc. Designed by Texas Instruments engineers for Henry's and P.W. 1972. Overall size 151 x 24 x 69mm. Mains operated. Free test sleeve with every kit.



£29.95 (carriage 50p)
(also built and tested £39.95)

HENELEC STEREO FM TUNER

Features capacity diode tuning, lead and tuning meter indicators, mains operated. High performance and sensitivity. Overall size in test sleeve 8 x 24 x 69mm. Complete kit with test sleeve.

£26.25 (carriage 50p)
(also built and tested £31.20)

JOIN THE LARGE BAND OF CONSTRUCTORS!

GARRARD CT4

SPECIAL OFFER—STEREO CASSETTE TRANSPORT MECHANISM

Features: *Stereo heads. *Built in motor stabiliser. *Auto stop. *Fast control. *12V d.c. operation. Robust precision engineered mechanism based on the STARR patented design. Ideal for use in car stereo cassette players. Hi-Fi stereo cassette recorders. Industrial and many other applications. Suitable for the PW Ascot Stereo Cassette Deck.



£13.50 INCL. VAT P. & P. 35p

NOW OPEN
ELECTRONIC SUPERMARKET
309 EDGWARE ROAD W.2

ALL PRICES INCLUSIVE OF VAT

HENRY'S

Electronic Centre
304-306 Electronic Components & Equipment 01-402 8381
354 PA Disco Lighting High Power Sound 01 402 5854
303 Special offers and bargains store
231 Tottenham Court Road W1. 01-581 3459
94-96 Upper Parliament Street Nottingham Tel: 053 42668
All mail to 303 Edgware Road, London W2 1BW
Prices correct at time of preparation. Subject to change without notice. E.A.O.E.

Hi-Fi and Electronics Centres Open 9am - 6pm

Dimmit range of light dimmers and lighting control systems

Illustrated is the popular PMSD1000 module. A 1kW slider control dimmer, interference suppressed, 60mm slider range size 4 1/2 x 2 x 1 1/2 in. Ideal for low cost stage and disco lighting. Used by schools, theatres, studios, etc. Complete with scale plate, fixing screws and full instructions. £8.60 inc. VAT and postage and packing.

Complete compact light dimmer systems for stage, club and disco lighting, etc.

DD61M (illustrated). Six 1kW channels, six outlet sockets, master control, mains on/off switch, size 23 x 8 1/2 x 5 in. Price £108.00 inc. VAT.

DD61. As DD61M but without master control. Price £86.40 inc. VAT.

DD261. As DD61M but with two-preset arrangement, size 23 x 10 x 5 in. Price £117.72 inc. VAT.

DD62M. As DD61M but with six 2kW channels, size 25 x 10 1/2 x 6 in. Price £156.60 inc. VAT.

DD62. As DD62M but without master control. Price £129.60 inc. VAT.


Add £2.20 postage and packing for all systems.

The Dimmit range includes rotary and slider control dimmers and sound to light converters for home, entertainment and professional applications. Ratings 1kW, 2kW, 3kW.

All products are guaranteed and are supplied with full instructions and applications. Full after-sales service. Technical advice given.

For full information on all modules and lighting control systems send 15p for our illustrated catalogue and price list. Callers welcome, visit our showroom for a demonstration of any of the modules or systems. Mon.-Fri. 9.30 to 6.0 p.m. Sat. by arrangement.

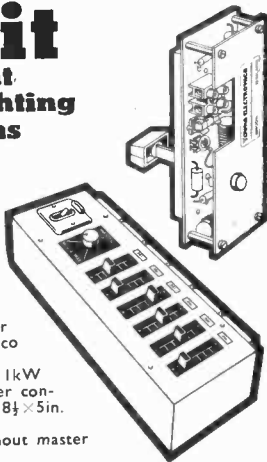YOUNG ELECTRONICS LTD.
184 Royal College Street, London NW1 9NN Tel. 01-267 0201



ELECTROLYTIC CAPACITOR OFFER

10000/63	£1.88	2200/40	30p	220/63	18p
10000/50	£1.50	1000/180	63p	160/25	9p
5000/70	76p	1000/40	25p	100/40	13p
5000/50	75p	1000/30	25p	100/12	7p
5000/35	50p	1000/25	25p	8/450	25p
5000/12	25p	470/63	23p	16/450	25p
3000/25	30p	470/35	20p	50/450	30p
2500/70	63p	330/100	30p	32 + 32/450	38p
2200/6.3	20p	250/64	20p	50/50	8p

Micro Switches (make or break) 33p
Cable Ties 3p
TOS Heat Sinks 13p
Pot cores (14mm or 18mm), complete 40p
180° Plastic Din Sockets 13p

DIGITAL I.C.s

Large range of 7400 series In stock. Prices from 18p.

INTEGRATED AUDIO POWER AMPS.

20W RMS. 1 off £6.38, Stereo pair £11.95.
30W RMS 1 off £7.95, Stereo pair £14.80.
50W RMS 1 off £12.38, Stereo pair £22.76.

50W RMS (4Ω) amp. kits complete with building and application details. Suitable for instruments, disco, hi-fi, etc. £8.95.

S.A.E. FOR DETAILS

SEMICONDUCTORS

AC141	57p	BC167	14p	BD124	97p	MJ3001	£2.80	2N3053	26p
AC142	42p	BC168	14p	BD131	52p	MJ4200	£5.88	2N3054	66p
AD161	62p	BC169	15p	BD132	64p	MJE2955	£1.48	2N3055	59p
AD162	62p	BC182	13p	BD135	58p	MJE3055	75p	2N3702	
BC107	13p	BC212	16p	BD136	63p			2N4371	14p
BC108	12p	BC301	32p	BFY50	23p	TIP29A	69p		
BC109	16p	BC302	56p	BFY51	22p	TIP30A	95p	40361	55p
BC147	14p	BC303	37p	BFY52	24p	TIP31A	87p	40362	60p
BC148	12p	BCY70	18p	MJ481	£1.36	TIP32A	99p	40406	55p
BC149	14p	BCY71	50p	MJ491	£1.52	TIP41A	72p	40407	40p
BC157	14p	BCY72	16p	MJ2500	£2.75	TIP42A	£1.27	40408	63p
BC158	12p	BD115	67p	MJ2501	£2.85	TIP2055	£1.38	40409	
BC159	12p	BD121	£1.48	MJ3000	£2.68	TIP3055	75p	40410	65p

ALL PRICES INCLUDE VAT
P. & P. 25p on all orders. Hundreds of other types of semiconductors held in stock. S.A.E. with all inquiries.

EBA
Elliott Blunt Audio Ltd

40 YORK STREET, TWICKENHAM, MIDD.
Tel. 01-891 1692

Opening hours 9.30 a.m. to 6 p.m. Monday to Saturday

LIGHTING EFFECTS UNIT

The Lightmaster 300 from Zero 88

THE PROFESSIONAL
LIGHTING CONTROLLER
THAT GIVES ALL
5 EFFECTS A WORKING
D.J. NEEDS



THE 5 EFFECTS Sound to light, Sound sequence, Auto sequence, All flash and manual strobe are selected by push buttons any of which may be selected at once for multiple effects.

The highly effective 'set and leave' circuitry specially developed for the LIGHTMASTER 300, requires only one control to set up the 3 channel, 12dB per octave, sound to light.

The fully floating audio input is via a ¼ inch jack (sensitivity from 100mV preamp level to 100V speaker lines) and completely automatic operation of effects is ensured by the use of CMOS logic control and IC filters.

Each output from a 13A socket, is conservatively rated at 1000W and has a LED indicator. Each triac, with a peak rating of 120A is protected by a 5A quick blow fuse.

The whole unit is controlled by a 15A mains fuse and switch, and is completely free from RF and mains borne interference.

The LIGHTMASTER 300 is constructed in a free standing steel case and is provided with panel mounting brackets, which may be reversed to form protective handles.

Available from your local dealer or direct from Zero 88 Lighting Ltd., 115 Hatfield Road, St. Albans, Herts., AL1 4JS. Tel: (0727) 63727.

Phone your Access/Barclaycard number for 'by return' delivery.

Price £63 (+ £6.25 P & P VAT)

BUILD YOURSELF A 25W AMP FOR ONLY

£29-95
+ 4-05 VAT

COMPLETE KIT SUPPLIED

DORAM, one of Britain's leading mail-order distributors of audio accessories & components brings you the 'INTERNATIONAL 25' - a 25W per channel Stereo Amp - that you can build yourself!

This 'real-value-for-money' kit is supplied with clear assembly instructions and reliable components to give you a big sound to be proud of.

- * Triple Op-amp pre-amplifier
- * Power 'Darlington's' in output stage
- * 25W per channel into 8 ohms
- * Modern, elegant styling

GENUINE
BIG-SOUND VALUE!



MANY MORE INTERESTING
AUDIO KITS AND COMPONENTS
LISTED IN DORAM'S CATALOGUE
PRICED AT ONLY 60p

DORAM

DORAM ELECTRONICS LTD
P.O. Box TR8, Leeds LS12 2UF
Tel. Leeds (0532) 34222

- ★ ELECTRONIC
PIANO KIT
- ★ SYNTHESISER
KIT
- ★ ELECTRONIC
ORGAN KITS



There are five superb Electronic Organ kits specially designed for the D-I-Y enthusiast. With the extreme flexibility allowed in design, you can build an organ to your requirements, which will compare with an organ commercially built costing double the price.

★ Portable organ with 4 octave keyboard, £145-29. ★ Console organ with 5 octave keyboard, £250-93. ★ Console organ with 2 x 4 octave keyboards and 13 note pedal board, £470-65. ★ Console organ with 2 x 5 octave keyboards and 32 note pedal board, £680. ★ Console organ with 3 x 5 octave keyboards and 32 note pedal board, £980. ★ W/W Sound Synthesiser Part Kit, £149. ★ W/W Touch Sensitive Electronic Piano Part Kit, £110. ★ 2 speed rotating speaker units, Bass unit £68, Mid-Range £75, Hi Fi Twin Horns £89.

All components can be purchased separately, i.e., semiconductor devices, M.O.S. master oscillators, coils, keyboards, pedal boards, stop tabs, draw bars, key-contacts, etc.

Send 60p for catalogue which includes 5 x 10p vouchers or send your own parts list, enclosing S.A.E. for quotation.

Elvins Electronic Musical Instruments

Showroom and Head Office, 12 Brett Road, Hackney, London E8 1JP (Tel. 01-986 8455); 8 Putney Bridge Road, London SW18 1HU (Tel. 01-870 4949); 40a/42a Dalston Lane, Dalston Junction, London E8 (Tel. 01-249 5624).

Business hours: Open 9 a.m. to 6 p.m. Monday to Saturday. Closed all day Thursday. Open 10 a.m. to 1 p.m. Sunday by appointment.
Vacancy for shop assistant with electronic knowledge

Marshall's

A. Marshall (London) Ltd. Dept. PE
 42 Cricklewood Broadway London NW2 3ET
 Tel: 01-452 0161/2 Telex: 21492
 & 85 West Regent St Glasgow G2 2OD
 Tel: 041-332 4133
 & 1 Straits Parade Fishponds Bristol BS16 2LX
 Tel: 0272 654201/2
 & 27 Rue Danton Issy Les Moulineaux Paris 92
 Tel: 644 2356

Call in and see us 9-5.30 Mon-Fri 9-5.00 Sat
 Trade and export enquiries welcome

Catalogue price 25p

Top 500 Semiconductors From the Largest Range in the U.K.

2N456	0-80	Orange	0-12	2N5192	1-24	AF106	0-40	BC186	0-25	BF159	0-27	LOOST1	1-50	OC35	0-60
2N456A	0-85	2N3053	0-25	2N5195	1-48	AF109R	0-40	BC187	0-27	BF180	0-23	LM380	1-10	OC42	0-50
2N457A	1-20	2N3054	0-20	2N5245	0-47	AF114	0-35	BC207	0-12	BF163	0-32	LM381	2-20	OC45	0-32
2N490	4-00	2N3055	0-75	2N5294	0-48	AF115	0-35	BC208	0-18	BF166	0-40	LM702C	0-75	OC72	0-75
2N491	4-38	2N3390	0-45	2N5295	0-48	AF116	0-35	BC212K	0-16	BF167	0-25	LM709	0-25	OC72	0-25
2N492	5-00	2N3391	0-28	2N5296	0-48	AF117	0-35	BC212L	0-16	BF173	0-27	T099	0-48	OC81	0-25
2N493	5-20	2N3391A	0-29	2N5298	0-50	AF118	0-35	BC214L	0-18	BF177	0-29	8D1L	0-38	OC83	0-24
2N696	0-22	2N3392	0-15	2N5457	0-49	AF124	0-30	BC237	0-16	BF178	0-25	14D1L	0-40	ORP12	0-55
2N697	0-16	2N3393	0-15	2N5458	0-46	AF125	0-30	BC238	0-15	BF179	0-25	LM710	0-47	RS3	1-80
2N698	0-82	2N3394	0-15	2N5459	0-49	AF126	0-28	BC239	0-15	BF180	0-35	LM723C	0-30	SL141A	1-80
2N699	0-59	2N3402	0-18	2N5492	0-58	AF127	0-28	BC251	0-12	BF181	0-38	LM741	0-30	SL610C	1-70
2N706	0-14	2N3403	0-19	2N5494	0-58	AF139	0-65	BC253	0-25	BF182	0-35	T099	0-40	SL612C	1-70
2N706A	0-16	2N3414	0-20	2N5496	0-61	AF186	0-46	BC257	0-16	BF183	0-55	8D1L	0-40	SL621C	2-60
2N708	0-17	2N3415	0-21	2N5577	0-45	AF200	0-65	BC258	0-16	BF184	0-30	14D1L	0-38	SL620C	2-60
2N709	0-42	2N3416	0-24	2N6027	0-45	AF239	0-65	BC259	0-17	BF185	0-30	LM747	1-00	SL621C	2-60
2N711	0-50	2N3417	0-29	2N3128	0-73	AF240	0-90	BC261	0-25	BF194	0-12	LM748	0-12	SL623	4-59
2N718	0-23	2N3440	0-59	2N3139	1-42	AF279	0-70	BC262	0-25	BF195	0-12	8D1L	0-60	SL640C	3-10
2N718A	0-28	2N3441	0-97	2N140	1-00	AF280	0-25	BC263	0-25	BF196	0-18	AD1L	0-73	SL641C	3-10
2N720	0-57	2N3442	1-40	2N141	0-81	AL102	1-00	BC300	0-38	BF197	0-15	LM390S	0-70	SL8000	2-92
2N914	0-39	2N3638	0-15	2N200	2-49	AL103	1-00	BC301	0-34	BF198	0-18	LM7805	2-00	SN76013N	1-95
2N916	0-28	2N3638A	0-15	40361	0-40	BC107	0-14	BC302	0-29	BF200	0-20	LM7812	2-50	SN76023N	1-60
2N918	0-32	2N3639	0-27	40362	0-45	BC108	0-14	BC303	0-54	BF225J	0-43	LM7815	2-50	SN76033N	2-92
2N929	0-37	2N3641	0-17	40363	0-88	BC109	0-14	BC307	0-17	BF244	0-25	LM7824	2-50	ST2	0-20
2N930	0-22	2N3702	0-12	40369	0-46	BC113	0-15	BC308A	0-15	BF245	0-41	MC1303	1-50	TAA263	1-10
2N1302	0-19	2N3703	0-15	40414	0-86	BC115	0-17	BC309C	0-20	BF246	0-20	MC1304	1-50	TAA300	1-80
2N1303	0-19	2N3704	0-15	40385	0-85	BC116	-18	BC317	0-27	BF247	0-65	MC1330P	0-90	TAA350	1-80
2N1304	0-28	2N3705	0-15	40406	0-44	BC116A	-17	BC318	0-12	BF254	0-19	MC1351P	0-20	TAA550	0-60
2N1305	0-24	2N3706	0-15	40407	0-35	BC117	-21	BC337	0-20	BF255	0-19	MC1352P	0-80	TAA611C	2-20
2N1306	0-31	2N3707	0-18	40408	0-35	BC118	-14	BC338	0-20	BF257	0-47	MC1466	3-50	TAA621	2-03
2N1307	0-30	2N3708	0-14	40409	0-52	BC119	0-29	BCY30	0-80	BF258	0-53	MC1469	2-75	TAA661B	1-32
2N1308	0-47	2N3709	0-15	40410	0-52	BC121	0-35	BCY31	0-85	BF259	0-55	ME0402	0-20	TBA641B	2-25
2N1309	0-47	2N3710	0-15	40411	2-00	BC125	0-16	BCY32	1-15	BF299	0-24	ME0404	0-13	TBA651	1-89
2N1310	0-54	2N3711	0-15	40594	0-74	BC126	0-23	BCY33	0-85	BF779	0-20	ME0412	0-11	TBA660	1-40
2N1671A	1-67	2N3712	1-20	40595	0-84	BC132	0-30	BCY34	0-79	BF521A	1-38	ME4102	0-11	TBA670	1-20
2N1671B	1-85	2N3713	1-20	40601	0-67	BC134	-13	BCY38	1-00	BF528	1-38	ME4104	0-11	TBA820	1-15
2N1711	0-45	2N3714	1-38	40602	0-61	BC135	-13	BCY39	1-50	BF561	0-27	MJ480	0-95	TBA920	2-30
2N1907	5-50	2N3715	1-50	40603	0-58	BC136	-17	BCY40	0-97	BF598	0-25	MJ481	1-20	TIL209	0-40
2N2102	0-80	2N3716	1-80	40604	0-58	BC137	-17	BCY42	0-28	BFX29	0-30	MJ490	1-05	TIP29A	0-39
2N2147	0-78	2N3717	1-20	40636	1-10	BC140	-88	BCY58	0-30	BFX30	0-27	MJ491	1-45	TIP29C	0-80
2N2148	0-84	2N3722	1-80	40663	0-41	BC141	-88	BCY59	0-30	BFX84	0-24	MJ505	1-00	TBA800	1-40
2N2160	0-80	2N3723	2-65	40673	0-73	BC142	-83	BCY70	0-17	BFX85	0-30	MJ5340	0-40	TIP30C	0-85
2N2218A	0-22	2N3789	2-06	AC126	0-20	BC143	-25	BCY71	0-22	BFX87	0-28	MJ5255	1-20	TIP31A	0-62
2N2219	0-24	2N3790	2-40	AC127	0-20	BC147	-14	BCY72	0-15	BFX88	0-25	MJ5305	0-75	TIP31C	1-20
2N2219A	0-26	2N3791	2-35	AC128	0-20	BC148	-14	BD115	0-75	BFX89	0-90	MJ5370	0-85	TIP32A	0-74
2N2220	0-25	2N3792	2-60	AC151V	0-27	BC149	-15	BD116	0-75	BFY50	0-23	MJ5371	0-75	TIP32C	1-25
2N2221	0-18	2N3793	0-24	AC152V	0-49	BC153	-18	BD121	1-00	BFY51	0-23	MJ5320	0-80	TIP33A	1-01
2N2221A	0-21	2N3819	0-37	AC153	0-49	BC154	-18	BD124	0-67	BFY52	0-21	MJ5321	0-70	TIP33C	1-01
2N2222	0-20	2N3820	0-64	AC153K	0-40	BC157	-16	BD124	0-67	BFY53	0-18	MP8111	0-32	TIP34A	1-51
2N2222A	0-25	2N3823	0-78	AC154	0-25	BC158	-16	BD131	0-40	BFY90	0-75	MP8112	0-40	TIP34C	2-60
2N2268	0-25	2N3904	0-27	AC176	0-30	BC160	-60	BD132	0-50	BRV39	0-38	MP8113	0-47	TIP35A	2-60
2N2369	0-20	2N3906	0-27	AC176K	0-40	BC167B	-15	BD135	0-43	BSX20	0-21	MPF102	0-39	TIP36A	3-70
2N2369A	0-22	2N4036	0-67	AC187K	0-35	BC168B	-15	BD136	0-47	BSX21	0-29	MPSA05	0-25	TIP41A	0-79
2N2646	0-55	2N4037	0-42	AC188K	0-40	BC168C	-15	BD137	0-55	BU104	0-25	MPSA06	0-31	TIP41C	1-40
2N2647	0-38	2N4058	0-18	ACY18	0-24	BC169B	-15	BD138	0-83	BU105	0-25	MPSA12	0-35	TIP42A	0-30
2N2904	0-22	2N4059	0-15	ACY19	0-27	BC169C	-15	BD139	0-71	CI06D	0-85	MPSA55	0-25	TIP42C	1-60
2N2904A	0-24	2N4060	0-15	ACY20	0-22	BC170A	-15	BD140	0-87	CA3018A	0-85	MPSA56	0-31	TIP49C	0-70
2N2905	0-25	2N4061	0-15	ACY21	0-26	BC171	-15	BD529	0-80	CA3020A	1-80	MPSU05	0-65	TIP53	1-70
2N2905A	0-26	2N4062	0-15	ACY28	0-20	BC172	-17	BD530	0-80	CA3028A	0-79	MPSU06	0-58	TIP2955	0-88
2N2906	0-19	2N4126	0-21	ACY30	0-58	BC177	-28	BDY20	1-05	CA3035	1-37	MPSU55	0-83	TIP3055	0-50
2N2906A	0-21	2N4289	0-38	AD142	0-57	BC178	-27	BF115	0-38	CA3046	1-50	MPSU56	0-50	TIV43	0-28
2N2907	0-22	2N4919	0-95	D143	0-68	BC179	-38	BF117	0-55	CA3049	2-11	NE555V	0-70	ZTX300	0-13
2N2907A	0-24	2N4920	1-10	AD149V	1-20	BC182	-12	BF121	0-35	CA3052	1-86	NE560	4-48	ZTX301	0-13
2N2924	0-20	2N4921	0-83	AD150	1-15	BY182L	-12	BF123	0-35	CA3089E	1-96	NE561	4-48	ZTX302	0-20
2N2925	0-20	2N4922	1-00	AD161	0-50	BC183	-12	BF125	0-35	CA3090Q	4-23	NE561	4-48	ZTX500	0-15
2N2926	0-20	2N4923	1-00	AD162	0-50	BC183L	-12	BF152	0-20	LM301A	0-48	NE565A	4-48	ZTX501	0-13
Green	0-12	2N5190	0-92	AD161	1-20	PR	0-13	BF153	0-25	LM308	2-50	OC23	1-35	ZTX502	0-18
Yellow	0-12	2N5191	0-96	AD162	1-20	BC184L	-13	BF154	0-20	LM309K	1-88	OC28	0-78	ZTX530	0-23

PW TELE TENNIS KIT

As featured on BBC Nationwide and in the Daily Mail 2 Oct. 74. Ideal game for whole family. No need to modify your TV set, just plug in to aerial socket.
 Parts list as follows: A Resistor Pack £1 P. & P. 20p; B Potentiometer Pack £1.25 P. & P. 20p; C Capacitor Pack £3.10 P. & P. 20p; D Semiconductor Pack £14.50 P. & P. 20p; E IC Sockets £4 P. & P. 20p; F Transformer £1.15 P. & P. 25p; G PCBs £7.50 P. & P. 20p; H Switches £1.90 P. & P. 20p; I 1UHF Modular Kit £7.50 P. & P. 20p.
 Special Prices—complete kit excluding case £38 P. & P. 50p; Sections A-F incl. £23.50 P. & P. 30p; Assembly instructions with complete kit or 75p on request.

P.C. Marker Pen Dalo 33PC 0-87p.

Zeners 400MW, 11p; 1W, 17p.
 IC Sockets 8 DIL 10p; 14 DIL 12p; 16 DIL 13p.
 Resistors $\frac{1}{2}$ W 2p; $\frac{1}{4}$ W 3p; 2 $\frac{1}{2}$ W 9p; 5W 10p; 10W 12p.

Scorpio Car Ignition Kit—£12.50 + VAT.

1 1MF440V £1.50.
 B5T8C245 £1.20, Transformer £3.
 OPTO and LEDs
 Red, green and yellow.
 0.2 diameter 33p; 0.20 diameter 33p.
 DL707 £2.25 or 4 for £8.
 Minitor £11.55.

Cmos Circuits (CD Range)

4000	0-36	4016	0-86	4030	0-87
4001	0-36	4017	1-72	4031	5-19
4002	0-36	4018	2-55	4037	1-93
4006	1-50	4019	0-86	4041	1-86
4007	0-36	4020	1-91	4042	1-38
4008	1-63	4021	1-72	4043	1-80
4009	1-18	4022	1-66	4044	1-80
4010	1-18	4023	0-36	4045	2-85
4011	0-36	4024	1-24	4	


At Home Soldering?

You should be — with the LITESOLD CONQUEROR

A superbly handling lightweight iron, fully insulated and earthed for safety. Bits are interchangeable, non-seize, and are available in 16 different shapes and sizes, from 1/16" up to 1/4", in copper and long-life types. (Standard fitting, 1/8" copper single chisel shape). Covers a range of work often needing several different irons.

A special spring stand gives safe, easy location of the iron and spare bits. The heavy heat-resistant base is complete with non-slip pads and bit cleaning sponge.

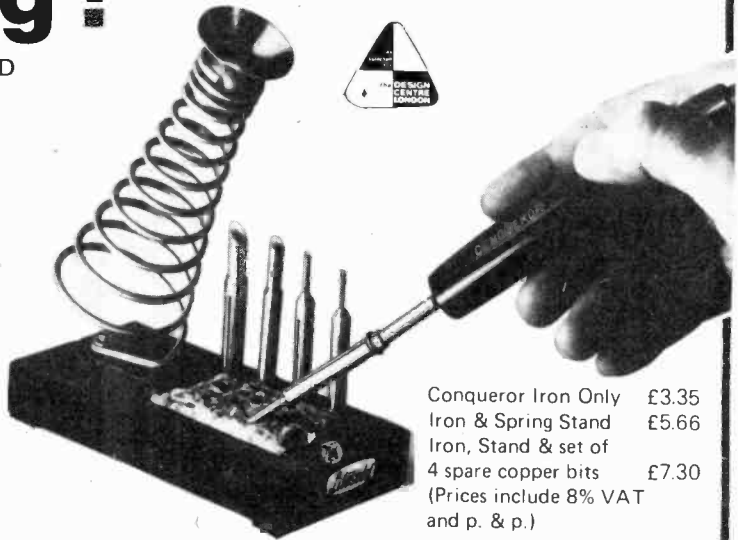Send cheque/PO direct, or ask for leaflet.



Conqueror Iron Only £3.35
 Iron & Spring Stand £5.66
 Iron, Stand & set of 4 spare copper bits £7.30
 (Prices include 8% VAT and p. & p.)

LIGHT SOLDERING DEVELOPMENTS LTD

97-99, Gloucester Road, Croydon, CRO 2DN. 01-689 0574

LS/M

TRANSISTORS

BC182	10p
BC184	12p
BC204	11p
BC209C	11p
BC212	14p
BC213	15p
BC214	16p
MPS-L01	39p
MPS-L51	41p
MPS-U07	69p
MPS-U57	85p
ZTX300	15p
ZTX500	17p
2N2219	22p
2N2484	51p
2N2904	30p
2N2905	27p
2N3054	100p

ARRAYS

CA3046	75p
CA3096AE	120p

DIODES

BA148	25p
1GP7	10p
1N914	5p
1N5401	21p
1SJ50	12p

RECTIFIERS

EA100/10	100p
MDA942A	210p
REC41A	120p
REC46	255p
REC70	40p

INTRODUCING THE



MINISONIC 2 Electronic Music Synthesiser

As Demonstrated "live" at the Audio Fair 1975
 Based on the original P.E. Minisonic, the Mk. 2 is a three octave keyboard instrument which sets new standards of performance and flexibility. Designed for construction by the amateur electronics enthusiast or do-it-yourself musician, the Minisonic 2 has a truly "professional" sound which has to be heard to be believed.

- ★ Finished case plus panels
- ★ Two VCOs (3Hz-50KHz)
- ★ VCO cross modulation
- ★ Variable Portamento
- ★ VCO sync. facility
- ★ Fixed/Variable Span
- ★ Envelope indicators
- ★ Pan pots at output
- ★ Push Button Patching
- ★ Headphone amplifiers
- ★ Low Current drain
- ★ Mains/Batt. Operation

A complete kit of parts is available to build this fabulous instrument or to convert your Mk. 1 Minisonic.

Ready made instruments are also available, complete with guarantee plus instruction booklet.

Want to know more? For full details send a 9 x 4in S.A.E.

MINIMIX 6 THE IDEAL MIXER FOR HOME STUDIO OR LOCATION RECORDING

Cases and ready made panels and PCBs available separately or as a complete kit—complete to the last nut and bolt!
 Kit now includes free PCB and details for equalised hi-sensitivity amplifier.
 Illustrated data sheet and comprehensive price list—send 9 x 4in S.A.E.

NOISE DIODES	
Z5J (Z1J)	75p
Z1M	120p

OP. AMPS	
709 (8-dil)	41p
710 (TOS)	39p
741 (8-dil)	24p
748 (8-dil)	51p

LINEARS	
MFC4000B	70p
MFC6040	100p
SG1495D	290p
SG3402T	174p
µA7815	220p
723	180p

RESISTORS	
Triple rated high stability carbon film, 1p each.	
E24 values from 4R7 to 3M9.	
Metal oxide half watt, 5 for 76p.	
E12 values 10R to 1M0.	

POTENTIOMETERS	
Carbon 24mm, lin and log, 5kΩ to 1MΩ, 25p.	
Wirewound 1W, lin only, 10Ω to 25kΩ semi-precision, 82p.	

SPECIAL OFFERS

741 only 24p
 8 pin DIL. First grade devices from well known manufacturer.

V.U. METERS only £1.40
 Moving coil meters, scale 36 x 21mm. Overall 40 x 40mm 400µA approx.
 ★ Ideal for the MINIMIX 6 ★

ZENERS only 8p
 Standard values 2.7V to 15V 400MW devices.

EATON AUDIO

DEPT. PE, P.O. BOX 3
 ST. NEOTS, CAMBS.
 PE19 3JB

TERMS: MAIL ORDER ONLY. C.W.O. MINIMUM ORDER £1. VAT: Please add 25% to value of order inc. P. & P. unless otherwise stated. Cheques or P.O.s payable to Eaton Audio. Orders over £5 free of P. & P., otherwise please add 10p in the £1.



4 1/4in x 3 1/2in **METER.** 30μA, 50μA or 100μA, £3.85. 16p P. & P.

TAPE RECORDER LEVEL METER



500μA, 70p. 10p P. & P.



CARDIODYNAMIC MICROPHONE

Model UD-130. Frequency response 50-15,000c/s. Impedance Dual 50K and 600 ohms, £7.40. 26p P. & P.

42 x 42mm meters 1mA, 10mA, 100mA, 500mA, £2.76. 16p P. & P.

60 x 45mm meters 50μA, 100μA, 500μA and 1mA VU meter, £2.92. 11p P. & P.

Edgewise meters 90mm x 34mm 1mA, £3.40. 16p P. & P.

MULTI-METER

Model ITI-2
20,000 ohm/volt, £6.90.
26p P. & P.



3 WATT STEREO (1 1/2 + 1 1/2) PER CHANNEL AMPLIFIER
£4.30. 16p P. & P.

All above prices include V.A.T. LARGE S.A.E. for List No. 11. Special prices for quantity quoted on request.

M. DZIUBAS

158 Bradshawgate • Bolton • Lancs. BL2 1BA

DIGITAL CLOCK KITS

NEW SENSATIONAL OFFER

ALARM VERSION



MAINS OPERATED
12-24 Hour
6 1/2 x 3 x 2 1/2"

£16

STANDARD CLOCK still only £14

(All prices include P. & P. and VAT)

- Fast building comprehensive kits
 - No electronics knowledge needed
- FULLY WORKING READY BUILT ELECTRONICS FOR STANDARD CLOCK

£11.88

MM5314N Clock Chip 12-24 hr 2.95
0.63" LED Displays NSN61L 1.65
Segment Driver Chip DM8865N 0.50
Mains Transformer 8.5/15V 1.50
Circuit Assembly Manual 0.50
Futuristically styled case 4.60

Black, White, Red, Blue, Green, Mauve
Wood case . . . extra 70p on kit price
Standard Clock Kit excluding case 11.60

Pulse Electronics Ltd

PE4, 202 Shefford Road, Clifton, Shefford, Beds.
Tel. Hitchin (0462) 814477

TRANSFORMERS

ALL EX-STOCK—SAME DAY DESPATCH

MAINS ISOLATING				VAT 8%		12 AND OR 24 VOLT PRIMARY 240-250 VOLTS			
Prim. 120/240V. Sec. 120/240V Centre tap with screen 115V or 240V sec. only						12V 24V			
Ref.	VA (Watts)	£	P & P	Ref.	£	Ref.	£	P & P	P & P
07*	20	3.77	58	111	0.5	0.25	1.54	58	58
149	60	4.69	72	213	1.0	0.5	1.88	58	58
150	100	5.33	85	71	2	1	2.41	58	72
151	200	8.54	1.12	18	4	2	2.87	72	72
152	250	10.32	1.41	70	6	3	4.43	72	72
153	350	12.47	1.41	108	8	4	5.09	85	85
154	500	14.33	1.61	72	10	5	5.50	85	85
155	750	21.84	BRS	116	12	6	5.90	97	97
156	1000	30.57	BRS	17	16	8	7.48	97	97
157	1500	34.89	BRS	115	20	10	10.81	1.61	1.61
158	2000	38.82	BRS	187	30	15	14.20	1.41	1.41
				226	60	30	17.87	BRS	BRS

30 VOLT RANGE				50 VOLT RANGE			
Prim. 200/240V. Sec. 0.12-15-20-24-30V				Prim. 200/240V. Sec. 0.18-25-33-40-50V			
Ref.	VA (Watts)	£	P & P	Ref.	VA (Watts)	£	P & P
No.				No.			
112	0.5	1.90	58	102	0.5	2.71	58
79	1.0	2.52	72	103	1.0	3.55	72
3	2.0	3.77	72	104	2.0	4.95	85
20	3.0	4.70	85	105	3.0	6.10	97
21	4.0	5.56	85	106	4.0	7.98	1.12
51	5.0	6.75	97	107	6.0	12.71	1.25
117	6.0	7.52	1.12	118	8.0	13.63	1.61
88	8.0	10.20	1.25	119	10.0	17.75	BRS
89	10.0	10.36	1.41				

60 VOLT RANGE				AUTO TRANSFORMERS				
Prim. 200/240V. Sec. 0.24-30-40-48-60V				Ref. VA Auto Taps				
Ref.	VA (Watts)	£	P & P	Ref.	VA (Watts)	£	P & P	
No.				113	20	0.15-210-240	1.75	51
124	0.5	2.40	72	64	75	0.15-210-240	3.05	72
126	1.0	3.68	72	4	150	0.15-200-220-240	4.33	72
127	2.0	5.33	85	66	300	0.15-200-220-240	6.11	85
125	3.0	7.90	97	67	500	0.15-200-220-240	9.38	1.25
123	4.0	9.19	1.41	64	1000	0.15-200-220-240	14.36	1.61
40	5.0	10.26	1.25	93	1500	0.15-200-220-240	18.02	BRS
120	6.0	12.07	1.41	95	2000	0.15-200-220-240	25.41	BRS
121	8.0	15.75	BRS	93	3000	0.15-200-220-240	36.84	BRS
122	10.0	19.40	BRS					
189	12.0	20.25	BRS					

CASED AUTO TRANSFORMERS			
240V mains lead input and U.S.A. 2-PIN outlets.			
Ref.	VA	£	P & P
20VA	£3-29	P. & P. 72p	113W
150VA	£8-37	P. & P. 85p	4W
500VA	£10-97	P. & P. £1-25	67W
1000VA	£18-39	P. & P. BRS	84W

HIGH VOLTAGE MAINS ISOLATING			
Prim. 200/220V or 400/440V			
VA.	Ref.	£	P & P
60	243	4.37	97
350	247	10.93	1.41
1000	250	28.31	BRS
2000	252	44.12	BRS

PLUS

BRIDGE RECTIFIERS		POWER UNIT	
50V	2A 35p	CC12-05 Output Switched	
100V	2A 49p	3-4-5-6-7 5-9-12V at 500mA. £4.08. P & P 48p. VAT 25%	
200V	1A 45p		
400V	4A 65p		
600V	2A 50p		
500V	10A(PM 7A6) £2-35		
	P & P 15p		
TEST METERS		HIGH QUALITY MODULES	
AVO 8 MK5	£55.88	3 W RMS Amplifier	£2.30
AVO 72	£21.72	5W RMS Amplifier	£2.65
U4313*	£13.85	10W RMS Amplifier	£2.95
U4315*	£11.80	25W RMS Amplifier	£3.95
* (USSR) inc. steel carrying case		Pre-Amp for 3-5-10W	£4.03
P. & P. £1.10. VAT 8%		Pre-Amp for 25W	£13.20
		Power Supplies 3-5-10W	88p
		Power Supplies 25W	£3.00
		Transformer 3W	£1.48
		Transformer 5-10W	£2.13
		Transformer 25W	£2.60
		P. & P. Amps/Pre-Amps/Power Supplies 18p	
		P. & P. Transformers 37p. VAT 25%	
ANTEX SOLDERING IRONS		BSR MINI-DECK	
15W	£2.68, 18W £2.45, 25W £2.26.	4 Speed Autochanger	£8.00
	Soldering Iron Kit £3.81.	P. & P. 72p. VAT 25%	
	Stand for above £1.13.		
	P. & P. 25p. VAT 25%		
MAGNETIC TO CERAMIC CARTRIDGE CONVERTOR		CAR STEREO SPEAKERS	
Operating voltage 20-45V only £2.65 P. & P. 18p. VAT 25%		8Ω angled £3.56 pr.	
		P. & P. 51p. VAT 25%	
INSTRUMENT CASES		CARBON POTENTIOMETERS	
In 2 sections, black vinyl covered top and sides and bezel.		Log and Lin. P. & P. 12p each. VAT 25%	
P. & P. 25p. VAT 8%		4K7, 10K, 22K, 47K, 100K, 220K, 470K.	
8 x 5 1/2 x 2 1/2in	£1.25	1M, 2M	
11 x 6 x 3 1/2in	£1.62	Single O.P. switch	
6 x 4 1/2 x 1 1/2in	£0.82	Tandem less switch	
9 x 5 1/2 x 2 1/2in	£1.39	1K Lin less switch	
		14p	
		28p	
		43p	
		14p	

PLEASE ADD VAT AFTER P & P
Audio Accessories and Bargain Component Paks.
Electrosil and Semi-Conductor stockists.
Callers welcome (Mon-Fri) or send stamp for lists

Barrie Electronics Ltd.

3, THE MINORIES, LONDON EC3N 1BJ

TELEPHONE: 01-488 3316/8

NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST

TELEVISIONS AND SPARES TO THE TRADE

MONOCHROME TELEVISIONS

BBC 2 Dual Standard TVs (19in, 23in) in batches of 10—£3 each (makes include Bush, Thorn, Philips, Pye/Ekco, Baird). Many with transistorised tuners. GEC 2000, Thorn 950 series, Bush 141, Philips Style 70, Baird 600 and 700 series all at £7 each.
Thorn 1400, Bush 160/170 series, Philips 210, Pye-Ekco Olympic, etc., Baird 673, Push Button—all at £12-50 each.
20in and 24in square screen Dual Standard sets—Thorn, GEC, etc., 20in—£15, 24in—£16-50.
20in and 24in Single Standard Thorn 1500, GEC, Bush Acoustic, 20in—£19-50, 24in—£22.

- (1) Discounts for quantities. (2) All monochrome spares supplied free of charge. (3) All tubes guaranteed. (4) All cabinets very good. (5) All sets "walk and talk". (6) All sets guaranteed complete inside and out. (7) Delivery and VAT extra.

COLOUR TELEVISIONS

Colour TVs 19in and 25in. Makes include Thorn 2000, Bush CTV25, Decca CTV 19/25in, Pye-Ekco, Baird 700 and 710 series, Philips G6, GEC 2028. All sets guaranteed complete inside and out—cabinets first class and tubes guaranteed. From £65 each.
20in and 22in Colour Televisions are always available in varying quantities—please telephone for availability and cost.

Please Note: (1) We deliver anywhere by our own transport. (2) All goods are blanket wrapped in our vans. (3) All orders with half deposit, balance on delivery after inspection. (4) Cheques most welcome. (5) Any quantity supplied. (6) We do not sell rubbish, and we stand by our guarantees. (7) We aim to please. (8) All spares supplied free of charge (mono only).

N.B. Special arrangements for delivery to North and South Ireland and world-wide exports orders welcomed.

TEST BENCH FACILITIES ALWAYS AVAILABLE

WORLD WIDE DELIVERIES OF TVs, SPARES

MISCELLANEOUS ITEMS

Large quantities of stereograms, fridges, deep freezers, Hoovermatics, radios, etc., always at hand—prices on request.

Colour All dual standard £5 plus £1 P. & P.
SCAN COILS All makes £2 inclusive. Mono

VALVES
All colour valves 40p each plus 5p P. & P. per valve.
All mono valves 10p each plus 2p each P. & P.

TUBES
19in—£15, 22in—£22, 25in—£20 (post. insurance, packing £5).
19in—£4, 20in—£5-50, 23in—£5, 24in—£7 (post. insurance, packing £3-50).

CABINETS
19in—£12, 22in—£16, 25in—£14 (post. insurance, packing £5).
All cabinets—£5 including post. insurance, packing.

LOPTs
All dual standard colour £5-50 plus £1 P. & P. All makes available.
All dual standard mono £2-50 plus £1 P. & P. All makes available.

SLOT METERS
10p meters—£1-50 each including postage and packing.

SPEAKERS
6in x 4in, 5in Round, 8in x 2in 30p each plus 10p P. & P.

PLEASE ALLOW 2 WEEKS DELIVERY. S.A.E. PLEASE FOR ENQUIRIES. ALL STOCK EX-EQUIPMENT BARCLAYCARD, ACCESS AND PROVIDENT WELCOME

TRADE DISTRIBUTORS

EMPIRE BUILDINGS, CHELTENHAM PARADE, HARROGATE, YORKSHIRE

Telephone: (STD 0423) 3498 and 62347

Colour IF, Decoder and Convergence—frame IF, Line timebase £3 plus £1 P. & P. All output for all dual standard models dual standard models in stock. from £7-50 plus £1-50 P. & P. All models available.

MAIL ORDER SERVICES

BLACK/WHITE TELEVISIONS

Working: 19in—£12-50, 23in—£15, 20in—£25, 24in—£29-50.
Untested (but guaranteed complete with good tubes): 19in—£4, 23in—£5, 20in—£15, 24in—£19.
(Postage, packing and insurance £4-50 each, prices include VAT.)
N.B. All tubes guaranteed

COLOUR TELEVISIONS

Working: 19in—£85, 22in—£125, 25in—£130.
Untested (but guaranteed complete with good tubes): 19in—£70, 22in—£90, 25in—£95.
(Postage, packing and insurance £9 each; prices include VAT.)
Thorn 2000, Bush CTV25, Philips G6, GEC2028, Baird 700, Decca CTV25

MAIL ORDER SPARES. Special Offer—Brand new spares:

BRC 2000 panels, video, convergence, and regulator—only £12-50 plus £1-50 P. & P.

Bush CTV 25 Line timebase-tower unit including LOPT and valves Mk. I and II only—£18 plus £3 P. & P.

BRC single standard colour 4 button tuners colour and mono—£7-50 plus £1 P. & P.

UHF Vari-cap tuner units—£6-50 plus £1 P. & P.

VHF Vari-cap tuner units—£7-50 plus £1 P. & P.

Pye-Ekco CTV Tripler units—£6-25 plus 75p P. & P.

Philips G8 Tripler units—£7-50 plus 75p P. & P.

KB VC Series LOPT £2-50 including P. & P.

Bush 125 and 135 IF PANELS—£3-50 plus 75p P. & P.

Thorn 850 IF Panels—£2-50 plus £1 P. & P.

GEC 2000 IF Panels—£3-50 plus £1 P. & P.

EX-EQUIPMENT TUNERS:

Colour:
All dual standard colour push button—rotary and integrated models in stock from £4-50 plus £1 P. & P.

Mono:
All VHF tuners available from £2 plus £1 P. & P.
All UHF tuners for dual standard models in stock. Push button—£4-50 plus £1-50 P. & P.
Rotary—£2-50 plus £1 P. & P.

Integrated (UHF and VHF) £4-50 plus £1-50 P. & P.

Comprehensive list of capacitors, resistors, etc., too numerous to mention. Prices on request.

SPECIAL MAIL ORDER OFFERS:

11in Portable Colour TVs, single standard converted made by German Kuba £95 each plus £5 post, packing and insurance.

19in Portable Thorn TVs—£29-50 each plus £4-50 post, packing and insurance. Hundreds of first class colour and monochrome sets available on display for personal callers who are most welcome.

We have an Urdu-speaking representative available at all times. (Please contact Mr. Boots.)

PRESENTING THE WAHL 'ISO-TIP' CORDLESS SOLDERING IRON

Completely portable.
Mains rechargeable automatically on its own stand.
Heats in 5 seconds.
Solders up to 150 joints or more per charge.

Only £10 + 75p Inc.

VAT & postage from

A.L. Spares Ltd. The Vale, London NW11.



TOWNSEND COATES LIMITED

LUNSFORD ROAD, LEICESTER, LE5 0HH

Telephone: (0533) 769191. Telex: 34321

PLESSEY POTENTIOMETERS

TYPE MP DEALER, PRINTED CIRCUIT, PRESET

Linear Law. 0-25W at 55°C. Wkg. V 500V d.c. Tol. ± 20%.
220Ω, 270Ω, 560Ω, 3K3, 5K6, 33K, 47K, 56K, 100K, 150K, 220K, 270K, 470K, 560K. Qty. 1-9: 25p each. Qty. 10+: 22p each. 2M2 28p each. (All plus 45p P. & P., plus VAT at 8%).

TYPE E ADJUSTABLE

Linear Law. 2W at 70°C. Wkg. V 500V d.c. Tol. ± 20%.
56K 1in spindle. 100K 1½in spindle. 24p each plus 45p P. & P., plus VAT at 8%.

SUBMINIATURE, ADJUSTABLE, PCB MOUNTING, 0-5W, LENGTH 1½in


Type 200P, 1K £1-25 each + 45p P. & P. + VAT at 8%
Type 200P, 25K £1-35 each + 45p P. & P. + VAT at 8%
Type 275, 5K £1-00 each + 45p P. & P. + VAT at 8%
Type 275, 50K £1-25 each + 45p P. & P. + VAT at 8%

EMIHUS ZENER DIODES

HS2068 Nom. V 6-8 250mW. HS2165 Nom. V 16-5 250mW. HS2200 Nom. V 20-0 250mW.
HS2270 Nom. V 27-0 250mW. HS7043 Nom. V 4-3 400mW. Qty. 1-9: 14p each. Qty. 10+: 12p each. (All plus 45p P. & P. plus VAT at 8%).

REMITTANCE WITH ORDER PLEASE

SYNTHESISER Modules by Dewtron®

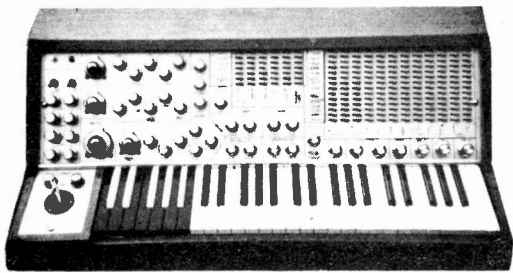

The synthesiser illustrated was built using Dewtron modules, as sold to constructors for some years now. With over 10 years' experience in mail-order, we have supplied many famous people and groups. Over 30 types of synthesis modules, some of extremely precision design, e.g. VCO-2 log-law oscillator; 3-wave o/p/s; sample/hold/envelope module; 3-octave keyboards, contacts, special tuning-ladder resistors, etc. Famous "Modumatrix" patching system makes other patching a thing of the past! Send just 20p for full catalogue to:

D.E.W. LTD.

254 Ringwood Road, Ferndown
Dorset BH22 9AR

RST VALVE MAIL ORDER CO.

16a WELLFIELD ROAD, LONDON SW16 2BS
SPECIAL EXPRESS MAIL ORDER SERVICE

sp	sp	sp	sp	sp					
1N21	0-17	AFZ11	1-15	BYZ13	0-25	OAZ205	0-45	Z8170	0-10
1N23	0-35	AFZ12	2-00	BYZ10	0-45	OAZ206	0-45	Z8271	0-18
1N85	0-88	ASV26	0-25	BYZ11	0-40	OAZ207	0-45	ZT21	0-25
1N253	0-50	ASV27	0-25	BYZ12	0-40	OAZ208	0-40	ZT43	0-25
1N256	0-50	ASV28	0-25	BYZ13	0-42	OAZ209	0-40	ZTX107	0-12
1N645	0-16	ASV29	0-30	BYZ15	1-25	OAZ210	0-40	ZTX108	0-10
1N725A	0-20	ASV30	0-20	BYZ16	0-60	OAZ211	0-40	ZTX300	0-13
1N914	0-06	ASV31	0-40	BZY88	0-10	OAZ222	0-45	ZTX304	0-24
1N4007	0-12	ASV33	0-20	C111	0-55	OAZ223	0-45	ZTX500	0-13
18113	0-25	ASV35	0-20	CR81/05	0-35	OAZ224	0-45	ZTX531	0-25
18202	0-23	ASV62	0-25	CR81/40	0-50	OAZ241	0-25		
2G371	0-75	ASV66	0-35	CSB3	1-90	OAZ242	0-15		
2G381	0-22	ASZ23	0-75	DD000	0-15	OAZ244	0-25		
2G414	0-30	AU104	1-00	DD003	0-15	OAZ246	0-15		
2G417	0-95	AUY10	1-50	DD006	0-25	OAZ290	0-38		
2N404	0-22	BC107	0-14	DD007	0-40	OC16T	1-00		
2N697	0-16	BC108	0-13	DD008	0-38	OC19	0-50		
2N698	0-30	BC109	0-14	GD3	0-33	OC22	1-00		
2N706	0-12	BC113	0-30	GD4	0-10	OC23	1-25		
2N706A	0-12	BC115	0-20	GD5	0-33	OC24	1-10		
2N708	0-15	BC116	0-20	GD8	0-25	OC25	0-40		
2N708	0-15	BC116A	0-22	GD12	0-10	OC26	0-40		
2N708	0-15	BC118	0-20	GET102	0-50	OC28	0-66		
2N1981	0-45	BC121	0-20	GET103	0-40	OC29	0-65		
2N1131	0-25	BC122	0-20	GET113	0-35	OC30	0-40		
2N1132	0-24	BC123	0-20	GET114	0-30	OC35	0-65		
2N1302	0-18	BC126	0-65	GET887	0-35	OC40M	0-60		
2N1303	0-18	BC140	0-55	GET116	0-85	OC41	0-35		
2N1304	0-22	BC147	0-10	GET120	0-60	OC42	0-40		
2N1305	0-22	BC148	0-08	GET872	0-30	OC43	0-70		
2N1306	0-22	BC149	0-10	GET875	0-40	OC44	0-40		
2N1307	0-22	BC157	0-14	GET880	0-80	OC44M	0-17		
2N1308	0-22	BC158	0-12	GET881	0-25	OC45	0-20		
2N2147	0-78	BC159	0-12	GET887	0-35	OC49M	0-15		
2N2148	0-80	BC169	0-14	GET885	0-40	OC58	0-27		
2N2160	0-78	BCY31	0-45	GEX44	0-08	OC57	0-60		
2N2218	0-23	BCY32	0-65	GEX45/1	0-45	OC58	0-60		
2N2219	0-25	BCY33	0-38	GEX941	0-45	OC59	0-60		
2N2389A	0-25	BCY34	0-45	GJ3M	0-50	OC66	0-50		
2N2444	1-99	BCY38	0-55	GJ4M	0-50	OC70	0-18		
2N2613	0-75	BCY39	1-50	GJ5M	0-25	OC71	2-25		
2N2646	0-50	BCY40	0-80	GT4M	0-50	OC72	0-25		
2N2904	0-20	BCY42	0-39	HG1005	0-60	OC73	0-50		
2N2904A	0-25	BCY70	0-18	HR100A	0-20	OC74	0-30		
2N2906	0-20	BCY71	0-22	MAT100	0-20	OC75	0-30		
2N2907	0-22	BCZ10	0-60	MAT101	0-25	OC76	0-30		
2N2924	0-13	BCZ11	0-65	MAT120	0-20	OC77	0-54		
2N2925	0-12	BD121	1-00	MAT121	0-25	OC78	0-25		
2N2926	0-15	BD123	1-00	MJE340	0-60	OC79	0-20		
2N3054	0-48	BD124	0-65	MJE520	0-63	OC81	0-29		
2N3055	0-45	BDY11	1-45	MJE2955	1-27	OC81D	0-28		
2N3702	0-11	BF115	0-20	MJE3055	0-77	OC81M	0-20		
2N3706	0-15	BF167	0-25	MFP102	0-40	OC81DM	0-18		
2N3706	0-11	BF173	0-22	MFP103	0-35	OC81Z	0-45		
2N3707	0-13	BF181	0-25	MFP104	0-35	OC82	0-28		
2N3709	0-10	BF184	0-25	MFP105	0-35	OC82D	0-25		
2N3710	0-11	BF185	0-22	NKT128	0-45	OC83	0-35		
2N3711	0-11	BF194	0-10	NKT129	0-30	OC84	0-80		
2N3819	0-38	BF195	0-13	NKT121	0-25	OC114	0-88		
2N4289	0-30	BF196	0-15	NKT213	0-25	OC122	1-00		
2N5027	0-58	BF197	0-18	NKT214	0-24	OC123	1-10		
2N5088	0-23	BF861	0-25	NKT216	0-40	OC139	0-40		
2S301	0-69	BF898	0-25	NKT217	0-20	OC140	1-14		
28304	1-15	BFX12	0-20	NKT128	0-45	OC141	0-80		
28501	0-75	BFX13	0-25	NKT219	0-33	OC189	0-20		
28703	1-00	BFX29	0-22	NKT222	0-30	OC170	0-30		
AA129	0-20	BFX30	0-28	NKT224	0-25	OC171	0-30		
AAZ12	0-75	BFX35	0-88	NKT251	0-24	OC200	0-75		
AAZ13	0-12	BFX63	0-50	NKT271	0-20	OC201	1-50		
AC107	0-51	BFX84	0-25	NKT272	0-20	OC202	1-50		
AC126	0-25	BFX85	0-25	OC293	0-20	OC204	1-50		
AC127	0-25	BFX86	0-25	NKT274	0-20	OC204	1-50		
AC128	0-15	BFX87	0-25	NKT275	0-25	OC205	1-75		
AC187	0-21	BFX88	0-24	NKT277	0-20	OC206	1-10		
AC198	0-20	BFY10	0-50	NKT278	0-25	OC207	1-00		
ACY17	0-75	BFY11	0-40	NKT301	1-00	OC460	0-20		
ACY18	0-27	BFY17	0-40	NKT304	1-00	OC470	0-30		
ACY19	0-27	BFY18	0-45	NKT403	1-00	OC271	0-20		
ACY20	0-35	BFY19	0-55	NKT404	1-00	ORP12	0-60		
ACY21	0-35	BFY24	0-45	NKT678	0-30	ORP60	0-55		
ACY22	0-35	BFY44	1-00	NKT713	0-30	ORP61	0-48		
ACY27	0-25	BFY50	0-21	NKT773	0-25	SX68	0-20		
ACY28	0-25	BFY51	0-20	NKT777	0-38	SX631	0-45		
ACY39	0-78	BFY52	0-20	OA5	0-72	SX635	0-55		
ACY40	0-22	BFY53	0-17	OA6	0-15	SX640	0-75		
ACY41	0-22	BFY64	0-88	OA7	0-08	SX641	0-75		
ACY44	0-22	BFY90	0-81	OA70	0-10	SX642	0-65		
AD140	0-50	BR100	0-40	OA71	0-20	SX644	0-85		
AD149	0-50	BX27	0-50	OA73	0-15	SX645	0-85		
AD161	0-44	BX60	0-93	OA74	0-15	SX645	0-85		
AD162	0-44	BX60	0-93	OA79	0-10	TIC44	0-29		
AF106	0-30	BX76	0-18	OA81	0-18	V15/30P	0-75		
AF114	0-25	BSY26	0-17	OA85	0-15	V30/201P	0-75		
AF115	0-25	BSY27	0-20	OA86	0-15	V60/201	0-50		
AF116	0-35	BSY51	0-50	OA90	0-07	V60/201P	0-75		
AF117	0-24	BSY95A	0-12	OA91	0-07	XA101	0-10		
AF118	0-57	BSY95	0-12	OA95	0-07	XA102	0-18		
AF119	0-20	BT102/500R	0-20	OA200	0-08	XA151	0-15		
AF124	0-30	BTY42	0-92	OA202	0-06	XA152	0-15		
AF125	0-30	BTY79/100R	0-75	OA210	0-20	XA161	0-25		
AF126	0-30	BTY79/400R	0-75	OA211	0-35	XA162	0-25		
AF130	0-41	BY100	0-27	OA220	0-50	XB101	0-43		
AF178	0-55	BY126	0-14	OA2201	0-45	XB102	0-30		
AF179	0-65	BY127	0-12	OA2203	0-45	XB103	0-35		
AF180	0-55	BY127	0-12	OA2204	0-45	XB113	0-30		
AF181	0-50	BY182	0-85	OA2204	0-45	XB121	0-43		
AF186	0-48								

INTEGRATED CIRCUITS

7400	0-16
7401	0-16
7402	0-16
7403	0-16
7404	0-28
7405	0-28
7406	0-42
7407	0-42
7408	0-28
7409	0-28
7410	0-16
7411	0-25
7412	0-25
7413	0-25
7416	0-28
7417	0-38
7420	0-18
7422	0-25
7423	0-37
7425	0-37
7427	0-37
7428	0-40
7430	0-16
7432	0-37
7433	0-37
7437	0-37
7438	0-37
7440	0-37
7441AN	0-22
7442	0-78
7450	0-16
7451	0-16
7453	0-16
7454	0-16
7460	0-38
7470	0-38
7472	0-38
7473	0-41
7474	0-42
7475	0-59
7476	0-65
7480	0-65
7482	0-65
7483	1-10
7484	1-00
7486	0-47
7490	0-55
7491AN	1-00
7492	0-70
7494	0-80
7495	0-80
7496	0-95
7497	3-87
74100	1-89
74107	0-45
74110	0-58
74111	0-88
74118	0-90
74119	1-88
74121	0-80
74122	0-70
74123	1-00
74141	0-90
74145	1-26
74150	1-75
74151	1-00
74154	2-00
74155	1-00
74156	1-00
74157	0-95
74170	2-52
74174	1-57
74175	1-10
74176	1-28
74180	2-00
74181	2-00
74182	2-00
74183	2-00
74184	1-80
74185	1-10
74187	1-20
74188	2-77
74189	2-52

Plug in sockets
—low profile
14 pin DIL
0-15
16 pin DIL
0-17

Open daily to callers: Mon.-Fri. 9 a.m.-5 p.m.
Valves, Tubes and Transistors • Closed Sat. 1 p.m.-3 p.m.
Terms C.W.O. only • Tel. 01-677 2424-7
Post and Packing 12p per order.
V.A.T. Transistors 25%. Integrated Circuits 8%.

Prices correct when going to press.

4-STATION INTERCOM



£15.95
+ VAT £1.28

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in robust plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospitals, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft and other accessories. P. & F. 7.6p.

Practical Electronics Classified Advertisements

RATES: 13p per word (minimum 12 words). Box No. 35p extra. Semi-Display £10.00 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisement Manager, "Practical Electronics" IPC MAGAZINES LTD., Fleetway House Farringdon Street, London EC4A 4AD. Tel. 01-634 4451.

RECEIVERS AND COMPONENTS

250 WATTS

Power amplifier. 1 volt input. Output into 4 or 8 ohms.

Silicon transistors, all standard types.

Guitar or microphone two input preamp with level, bass, treble and extra high switch.

Microphone preamp 200 ohms to 50k, for stage use. Will take overload up to 300 mV without distortion. Level and gain controls.

Ready drilled circuit boards and all construction information.

Prices include tax and postage.

250 Power amp £2-25
Guitar preamp £1-20
High level preamp 90p

ALFA ELECTRONICS

96a Glengall Road, London, N.W.6
S.A.E. for more information. Mail order only

VALVES, RADIO, TV, TRANSMITTING, INDUSTRIAL. 1930 to 1975. 2,200 types in stock, many obsolete. List 20p. Quotation S.A.E. Postal export service. We wish to purchase new and boxed valves. Dealers, wholesalers, etc., stocks purchased. COX RADIO (SUSSEX) LTD., The Parade, East Wittering, Sussex. Tel. West Wittering 2023.

TTL AT NEW REDUCED PRICES!
(Fast delivery. All prices include VAT)
SPECIAL OFFER OF 7400, 7410, 7420, 7430, 7440 at 11p each, ZTX108 at 8p each.
Above offer ends January 31, 1976, and is regardless of quantity ordered.

Type	1/24	25/99	Type	1/24	25/99
7400	0-14	0-12	7483	0-80	0-75
7401	0-14	0-12	7484	0-92	0-89
7402	0-14	0-12	7485	1-30	1-09
7403	0-14	0-12	7486	0-30	0-26
7404	0-16	0-13	7489	2-99	2-80
7405	0-16	0-15	7490	0-46	0-40
7406	0-36	0-31	7491	0-65	0-55
7408	0-16	0-15	7492	0-48	0-45
7410	0-14	0-13	7493	0-46	0-40
7411	0-23	0-20	7495	0-59	0-55
7412	0-16	0-15	7496	0-77	0-69
7413	0-32	0-31	74100	1-08	0-89
7414	0-69	0-60	74107	0-34	0-28
7417	0-30	0-29	74109	0-54	0-48
7420	0-14	0-13	74121	0-34	0-28
7422	0-24	0-22	74122	0-47	0-39
7425	0-27	0-25	74123	0-65	0-61
7427	0-14	0-13	74141	0-7	0-63
7430	0-14	0-13	74145	0-68	0-58
7432	0-27	0-25	74150	1-05	0-95
7437	0-27	0-25	74151	0-91	0-88
7440	0-14	0-13	74153	0-76	0-72
7441	0-75	0-62	74154	1-60	1-45
7442	0-65	0-55	74155	0-95	0-85
7445	0-85	0-71	74157	0-83	0-79
7447A	0-81	0-79	74160	1-05	0-95
7450	0-14	0-13	74164	1-25	1-05
7451	0-14	0-13	74174	0-99	0-83
7453	0-14	0-13	74175	0-99	0-83
7454	0-14	0-13	74181	2-09	1-95
7460	0-14	0-13	74190	1-25	1-15
7472	0-25	0-21	74191	1-25	1-15
7473	0-30	0-25	74192	1-35	1-14
7474	0-32	0-26	74193	1-35	1-14
7475	0-45	0-39	74195	0-88	0-79
7476	0-32	0-26	74196	1-64	1-34
7480	0-47	0-42			

TTL (except special offers) may be mixed for quantity prices.
All devices full spec. by famous manufacturers. S.A.E. for full lists. All goods sent by 1st class post. 12p. P. & P. on orders below £2 (12p P. & P. on all orders for special offers).
J. C. JONES
(Dept. PE13) 46 BURSTELLARS ST. IVES, HUNTINGDON PE17 4XX (Mail Order only)

TRANSISTOR BONANZA: Branded devices equivalent 50 popular semiconductor BC108, BC147, BC148, BC212LA, BC309, BF196, BC159, BF258, BF371. Any 10 or multiple of 10 £1. inc. V.A.T. P. & P. 15p. TELE-SERVICE, 13 Worcester Street, Wolverhampton. Tel. 772293.

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact COLES-HARDING & CO., P.O. Box 5, Frome, Somerset. Immediate cash settlement.

PRECISION POLYCARBONATE CAPACITORS

ALL HIGH STABILITY—EXTREMELY LOW LEAKAGE

0.1µF (27 x 12.7)	51p	Value	±1%	±2%	±3%
0.22µF (33 x 16)	64p	0.47µF	67p	50p	45p
0.33µF (33 x 16)	67p	2.2µF	98p	75p	61p
0.47µF (33 x 19)	80p	4.7µF	£1-62	£1-13	94p
0.5µF (33 x 19)	87p	6.8µF	£1-96	£1-38	£1-13
0.68µF (50.8 x 19)	98p	10µF	£2-40	£1-95	£1-64
1.0µF (50.8 x 19)	£1-08	15µF	£3-22	£2-79	£2-24
2.0µF (50.8 x 25.4)	1.5µF	22µF	£4-28	£3-68	£3-08

TANTALUM BEAD CAPACITORS—Values available: 0.1, 0.22, 0.47, 1.0, 2.2, 4.7, 6.8µF at 15V/25V or 35V; 10.0µF at 16V/20V or 25V; 22.0µF at 6V/10V or 16V; 33.0µF at 6V or 10V; 47.0µF at 3V or 6V; 100.0µF at 3V ALL at 10p each. 10 for 95p, 50 for 44.

TRANSISTORS: BC183/183L 11p BFY50 20p
BC107/8/9 9p BC184/184L 12p BFY51 20p
BC114* 12p BC212/212L* 14p BFY52 20p
BC147/8/9* 10p BC647/558A* 12p AF178 30p
BC159/7/8 12p BF184* 12p OC71 12p
BC182/182L* 11p BF197* 13p 2N3055 50p

POPULAR DIODES—IN914 6p, 8 for 45p, 18 for 90p; IN918 6p, 8 for 45p, 14 for 90p; 1S84 5p, 11 for 60p; 24 for £1; IN4148 5p, 9 for 27p, 12 for 45p; IN4001 5p; IN4002 6p; IN4003 6p; IN4004 7p; IN4005 7p; IN4006 8p; IN4007 8p.

LOW PRICE ZENER DIODES—400mW. Tol. ±5% at 5mA. Values available: 3V, 3.3V, 3.6V, 4.7V, 5.1V, 5.6V, 6.2V, 6.8V, 7.5V, 8.2V, 9.1V, 10V, 11V, 12V, 13V, 15.0V, 15V, 16V, 18V, 20V, 22V, 24V, 27V, 30V, 33V. ALL at 7p each, 5 for 33p, 10 for 65p. SPECIAL OFFER: 100 Zeners (may be mixed) for 28.0p.

RESISTORS—High stability, low noise carbon film 5% ¼W at 40°C, ¼W at 70°C. E12 series only—from 2.2Ω to 2.2MΩ. ALL at 1p each, 8p for 10 of any one value, 70p for 100 of any one value. SPECIAL PACK: 10 of each value 2.2Ω to 2.2MΩ (70 resistors) 45p.

SILICON PLASTIC RECTIFIERS—3.5 amp, brand new wire ended DO27: 100 P.I.V. 7p (4 for 28p); 400 P.I.V. 8p (4 for 30p).

BRIDGE RECTIFIERS—2½ amp: 200V 40p; 350V 45p; 600V 55p.

SUBMINIATURE VERTICAL PRESETS—0-1W only: ALL at 8p each: 50Ω, 100Ω, 220Ω, 470Ω, 680Ω, 1kΩ, 2.2kΩ, 4.7kΩ, 6.8kΩ, 10kΩ, 15kΩ, 22kΩ, 47kΩ, 100kΩ, 250Ω, 680kΩ, 1MΩ, 2.5M, 5M.

PLEASE ADD 15p POST AND PACKING ON ALL ORDERS BELOW £5. ALL EXPORT ORDERS ADD COST OF SEA/AIRMAIL.

Send S.A.E. for lists of additional ex-stock items. Wholesale price lists available to bona fide companies.
MARCO TRADING
Dept. E.1, The Old School, Edinstaton, Le. Wem, Shropshire
Tel.: WHIXAL 40415 (STD 0948 72)
(Proprs: Minicost Trading Ltd.)

BETA DEVICES

TRANSISTORS	ICs*	DIODES & RECT
AC187/188	709C D.I.L.	IN914 0-04
PR	709C D.I.L.	IN4148 0-04
BC107	741C D.I.L.	OA202 0-09
BC108	741C D.I.L.	IN4001/2 0-05
BC109C	728C D.I.L.	IN4003/4/5 0-08
BC147/8/9	747C D.I.L.	IN4006/7 0-08
BCY70/71/720-13	748C D.I.L.	BRIDGES
BFX56/87/88		50V 1A 0-18
	3016F	100V 1A 0-20
BFY50	TBA800	600V 1A 0-30
BFY51/52	SGS-ATES	200V 25A 2-00
OC28	2N3055	ZENERS
OC35		D.I.L. SOCKETS
2N2846		BZY88 3-3
2N3053	8-Pin	38V 5% 0-09
OC25	14-Pin	1 Watt 6-8
OC38	16-Pin	200V 5% 0-15
TIP41A		L.E.D.
TIP42A		209-Red 0-17
		17% V.A.T. L.E.D. Clip 0-02

C.W.O. PLUS P.P. 15p to BETA DEVICES
4 High Bridge Street, Waltham Abbey, Essex

PLEASE MENTION
PRACTICAL ELECTRONICS
WHEN REPLYING TO
ADVERTISEMENTS

BRAND NEW COMPONENTS BY RETURN. Electrolytics 16V, 25V, 50V, 0.47, 1.0, 2.2, 4.7, 10mfds, 5p; 22, 47, 82p (50V, 6p); 100, 7p (50V, 8p); 220, 8p (50V, 10p); 500, 11p (50V, 16p); 1000/25V, 18p. Subminiature bead-type tantalums. 0.1/35V, 0.22/35V, 0.47/35V, 1.0/35V, 2.2/35V, 4.7/35V, 10/20V, 22/16V, 47/6V, 100/3V, 11p. Mylar Film 100V, 0.001, 0.002, 0.005, 0.01, 0.02, 3p; 0.04, 0.05, 3½p. Mullard tubular polyester 400V E6 series, 0.001-0.022, 3½p; 0.033-0.1, 4½p. Mullard polyester 160V tubular or 250V miniature for vertical mounting E6 series, 0.01-0.047, 3½p; 0.068, 0.1, 4½p; 0.15, 0.22, 6p; 0.33, 7p; 0.47, 9p; 0.68, 11p; 1.0, 14p; 1.5/250V, 18p; 2.2/250V, 22p. Mullard miniature C333 ceramics 63V E12 series 2% 1.8pF-47pF, 3p; 56pF-330pF, 3½p. Plate ceramics 50V E6 series 470pF-47,000pF, 2p. Polystyrene 63V. E12 series 10pF-1,000pF, 3p; 1,200pF-10,000pF, 4p. Miniature highstabil carbon film resistors ¼W E12 series 6% (10% over 1MΩ) 1Ω-10MΩ, 1-2p; 1N4002, 6p; 1N4006, 8p; 1N4148, 4p. Postage 10p. Prices VAT inclusive. THE C.R. SUPPLY CO., 127 Chesterfield Road, Sheffield, S8 0RN.

**AXIAL PRODUCTS LTD**

DEPT 212
23 AVERY AVENUE
DOWNEY
HIGH WYCOMBE
BUCKS. (0484 33968)
Callers by appointment

AC127/8	15p	7400	15p	Zener Diodes	47V	11p
BC107/8	12p	7403	15p	10W 3-200V		19p
BC109	12p	7404	20p	IN4001	6p	
BC113	12p	7405	20p	IN4002	6p	
BC147/8	11p	7410	15p	IN4007	9p	
BC149	12p	7412	17p	IN4148	5p	
BC157/8	12p	7413	17p			
BC159	14p	7442	76p	Linear ICs		
BC173	30p	7475	45p	LM301	50p	
BC213	14p	7448	97p	LM741	35p	
BCY70	22p	7474	38p	LM555	60p	
BF173	30p	7475	45p	IC Sockets		
BF184	32p	7478	48p	8 pin	14p	
BF194/5	12p	7490	49p	14 pin	15p	
BFY50/1	19p	7495	60p	16 pin	16p	
TIP3055	45p	74121	37p			
2N3055	38p	74610	113p			
2N3819	35p	74192	140p			

4 Element VHF/FM £4.75 + 75p P. & P.
18 Element UHF/TV £2.50 + 50p P. & P.
10 Element UHF/TV £2.19 + 50p P. & P.

Lashing Kit. £1-24 + 50p P. & P. 75 Ohm Low Loss.
Wall Bracket for 1in mast. £1.50 per metre.
84p + 50p P. & P. 300 Ohm Twin Feeder.
6ft x 1in Mast. £1.50 per metre.
84p + 50p P. & P. Coax Plug. 12p each.

All prices include VAT. Semiconductor 10p P. & P. per £ any mix. Orders over £2 P. & P. free.

MINIATURE CARBON FILM RESISTORS, 5%, ¼W, ¼W, ½W, E12 Series, 22 ohm to 1 Mohm, 10 for 10p, 50 for 45p, 100 for 80p. P. & P. 10p. Mixed values and wattages to your choice. CANDAR, Freepost, Reading, RG1 1BR.

Bank of 20 Neons 74p (16p); 5 figure resettable Counter 18/22 v, works on 12, £2-50 (50p); Box with 20 x LA2 Pos Cores + 20 x 1% Caps £1-75 (75p); Copper clad Fax Panels 5½" x 5½" 6-75p; 12" x 12" 75p; 16" x 9½" 75p; 8" x 9½" 3-11.5p; Fibre Glass 12½" x 7" 90p, 18" x 4" 85p, 7" x 8" 60p. Double-sided plus 10%. All CP. 74 Series ICs on Panel (10) - 85p (10p); 100 Ass. Polystyrene Caps 80p (10p). Lists 15p. Refund on purchase. 7 lbs assorted components £2-50 c.p.

J. W. B. RADIO
2 Barnfield Crescent, Sale, Cheshire M33 1NL
Postage in brackets Mail order only

AERIAL BOOSTERS. Improve weak Radio and Television reception. Price £3.60. P. & P. 25p. S.A.E. for Leaflets. Bargain Pack Polyester (C280) Capacitors: 250 V/W and 400V/W. Very good mixed selection from 0.01µF to 2.2µF. Price 100 £1. P. & P. 15p (our choice). Bargain Pack Electrolytic Capacitors: good mixed selection unused and marked. Price 100 £1. P. & P. 15p (our choice). LAN-CASHIRE MAIL ORDER, 6 William Street, Stubbins, Ramsbottom, Bury, Lancs.

BULK OFFERS

1N4001	£2.50	BC147	£8.00	BF244B	£13.00
1N4002	£2.80	BC148	£5.00	BF194	£6.00
1N4003	£3.20	BC149	£6.00	BF195	£6.00
1N4004	£3.50	BC157	£8.00	BSY95A	£6.00
1N4005	£3.90	BC158	£8.00	2N2646	£34.00
1N4006	£4.30	BC159	£8.00	2N3055	£28.00
1N4007	£4.70	BC161	£10.00	2N3442	£75.00
1N4148	£2.20	BC267	£8.00	2N5224	£21.00
BC107	£7.00	BC328	£10.00	NE555V	£38.00
BC108	£7.00	BC548	£8.00	709C	£15.00
BC109	£7.00	BD131	£16.00	741C	£19.00
BC119	£12.00	BF173	£14.00	7440	£5.00
BC139	£14.00	BF181	£20.00	SN76660	£22.00

All prices per minimum quantity of 100

Ferric chloride £30 per 100lb bag.
Miniature mains transformers, 100mA sec: 6-0-6V £5-80 for 10; 9-0-9V £8-30 for 10; 12-0-12V £8-90 for 10.

Miniature ceramic plate capacitors, 33pF 2% £7 per 1,000; 100pF 2% £7-50 per 1,000.
Siemens polystyrene, 470pF 5% £8 per 1,000; 100pF 40V £4 per 100; 470uF 25V £8 per 100.
PP3 battery snap connectors £4 per 100.
Crystal microphone inserts, 1/16in dia. £20 per 100.
90V neon £3 per 100; £25 per 1,000.
Coaxial back to back connectors £4-20 per 100.
Coaxial plugs £4-70 per 100.
H61 Texas light sensors £32 per 100.

Minimum order £5 (excluding VAT); Carriage free. Add VAT at the appropriate rate. S.A.E. enquiries, list.

JUNIPER ELECTRONICS (PE1)
PO Box 61, Southampton SO9 7EE

SCOOP! CAPACITORS/RECTIFIERS.
10mfd/12V, 80mfd/150V, 10/20p, 100/£1.
10mfd/70V, 22mfd/50V, 10/25p, 100/£1-25.
100mfd/16V, 1000mfd/6V, 10/30p, 50/75p.
1N4002 10/30p. 1N4004 10/40p. 1N4007 10/50p. Bridges 1A/200V 2/50p. 2A/200V 2/65p. P. & P. 20p. AUDIO-OPTICS, 19 Middleway, Chinnor, Oxon.

LED panel clip 1p	S	0-125	0-2	INFRA RED 550uW Axial lead 49p				
	RED	15p	18p	1-5mW TO46 £1-10				
	G/Y	27p	33p					
	OR	27p	33p					
OPTO-ISOLATORS								
IL74	1-5kV. 150kHz	£1	T05 1A	25p	27p	46p		
4350	2-5kV. 5MHz	£2-25	T066 3A	27p	35p	50p		
Data free with all OPTO			TRIAc	T05	2A	400V 66p		
AC125/6/7/8 15p					2N2926(G) 12p		VOLTAGEREGS.	
AD161/162 40p					2N3053 15p		5V 7805 Plastic	
AF117 20p					*N3055 41p		12V 7812 1 Amp	
AF124/5/6/7 34p					2N3702/3/4 12p		15V 7815 all	
BC107/8/9 9p					2N3823/4/5/6 16p		18V 7818 £1-50	
BC109C 12p					2N2646 35p		723 T099 50p	
BC147/8/9 10p					MPF102 40p		BRIDGE RECTS.	
BC157/8/9 11p					2N3819 25p		2A 50V 30p	
BC167/8/9 11p					2N3823 30p		2A 100V 36p	
BC169C 12p					BR100 Diac 21p		2A 200V 41p	
BC177/8/9 17p					IN814 5p		2A 400V 46p	
BC182/3/4/11 11p					IN4001 5p		ZENERS BZY88	
BC186/7 30p					IN4002/3 6p		2-7-33V 8p	
BC212/3/4/L 12p					IN4004/5 7p		NE555V 60p	
BCY70/71/72 13p					IN4006/7 8p		NE556 £1-10	
BF194/5 12p					IN4148 14p		LN380 £1-00	
BF198/7 14p					OA7 6p		ZN414 £1-10	
BF195/51 15p					OA70 OA79 8p		7400 18p	
BFX29 30p					OA81 OA90 7p		D.I.L. SOCKETS	
BFX84 24p					OA81 OA95 6p		8-pin 12p	
BSX19/20 16p					OA200 8p		14-pin 13p	
OC71 10p					OA202 7p		16-pin 14p	
2N1708 10p					OP. AMPS		Mica + bushes	
2N1711 20p					709 all 25p		TO3 5p	
2N2119 20p					741 8-pin 25p		TO66 5p	
2N2904/5/6/7 16p					748 D.I.L. 36p		Diode Pen 70p	
2N2904/5/6A 18p								
2N2926(R) 7p								
PRICES INCLUSIVE + 15p P. & P. (1st class)								
ISLAND DEVICES, P.O. Box 11, Margate, Kent								

BOOKS AND PUBLICATIONS

UFO CHARTS: Wave Prediction 56p; Daily Flight Pattern 50p; TV Doppler Detection, 68p; Propulsion Theory 57p; "Anti-Gravity" 57p. Map 52p. Numerous Circuits: detection, radiometers, multidigit testers, clocks, S.A.E. Lists + 10p. R. & E., Highlands, Needham Market, Suffolk.

LADDERS

LADDERS, varnished 20' 9" extd. £19-82. Carr. £1-40. Leaflet. Also aluminium ext. and loft ladders. Tel. Telford 586644.

EDUCATIONAL

TELEVISION TRAINING

16 MONTHS' full-time practical and theoretical training course in Radio and TV Servicing (Mono and Colour) for beginners, with GCE (or equivalent) in Maths & English.

13 WEEKS' full-time Colour TV Servicing course. Includes 100 hours practical training. Mono revision if necessary. Good electronics background essential.

NEXT SESSION commences on January 5th.

Prospectus from London Electronics College, Dept. A1, 20 Penywern Road, London SW5 9SU. Tel. 01-373 8721.

TECHNICAL TRAINING.

Get the training you need to move up into a higher paid job. Take the first step now—write or phone ICS for details of ICS specialist homestudy courses on Radio, TV, Audio Eng. and Servicing, Electronics, Computers; also self-build radio kits. Full details from: ICS SCHOOL OF ELECTRONICS, Dept. 316, Intertext House, London, SW8 4UJ. Tel. 01-622 9911 (all hours).

SITUATIONS VACANT

MEN!
£90 p.w.
can be yours

Tens of thousands of new computer personnel needed over the next few years alone.

Now for the first time anybody (no special qualifications are needed) can train outside the computer industry for an exciting career as a computer operator in only 4 weeks. It can pay around £35 p.w. as a starter and can reach over £90 p.w. We subscribe to the code of practice for Computer schools of the National Computing Centre—a non-profit organisation which was set up and sponsored by the British Government. Write without obligation for FREE details TODAY.

London Computer Operators Training Centre C37

Oxford House, 9-15 Oxford Street, W.1

Tel. 01-734 2874

FOR SALE

PRACTICAL ELECTRONICS for sale, 90 copies, Nov. 64 to Dec. 74, as one lot. Offers to R. Williams, 3 Elm Close, Butlers Cross, Aylesbury, Bucks.

CITY & GUILDS EXAMS.

Study for success with ICS. An ICS homestudy course will ensure that you pass your C. & G. exams. Special courses for: Telecoms. Technicians. Electrical Installations, Radio, TV & Electronics Technicians, Radio Amateurs. Full details from: ICS SCHOOL OF ELECTRONICS, Dept. 315, Intertext House, London, SW8 4UJ. Tel. 01-622 9911 (all hours).

COLOUR TV SERVICING.

Learn the techniques of servicing Colour TV sets through new homestudy course approved by leading manufacturers. Covers principles, practice and alignment with numerous illustrations and diagrams. Other courses for radio and audio servicing. Full details from: ICS SCHOOL OF ELECTRONICS, Dept. 317, Intertext House, London, SW8 4UJ. Tel. 01-622 9911 (all hours).

SERVICE SHEETS

BELL'S TELEVISION SERVICES for service sheets, manuals and books on Radio/TV, etc. Service sheets 50p plus S.A.E. Service sheet catalogue 25p. Back issues of magazines from April, '74 onwards. Cover price plus 12p post. Free booklists on request. S.A.E. with enquiries please to: B.T.S. 190 Kings Road, Harrogate, Yorkshire. Tel. Harrogate (0423) 55885.

SERVICE SHEETS for radio, TV, tape recorders, stereo, etc., with free fault-finding guide, 50p and S.A.E. HAMILTON RADIO, 47 Bohemia Road, St. Leonards, Sussex.

SERVICE SHEETS, radio, TV, etc., 10,000 models. Catalogue 24p plus S.A.E. with orders-enquiries. TELRAY, 154 Brook Street, Preston, PR1 7HP.

WANTED

RADIO AND TELEVISION SERVICING books wanted from 1963-1964 edition onwards. £2 paid per copy by return of post. BELL'S TELEVISION SERVICES, 190 Kings Road, Harrogate, N. Yorks. Tel.: Harrogate 55885.

TOP PRICES PAID
NEW VALVES AND TRANSISTORS
Popular T.V. and Radio types
KENSINGTON SUPPLIES (B)
367 Kensington Street
Bradford 8, Yorks.

£40 CASH for 100W Monitor Power Slave built to P.E. specification in good condition. Tel. Rushlake Green 397 (evenings).

MISCELLANEOUS

LIGHTING CONTROL UNITS

3 x 1½kW per channel sound-to-light converter using isolated control circuitry for maximum safety. The unit comes in kit or ready built form and features individual sensitivity controls, sensitivity range switch and dimming switch. (Bypass controls as an optional extra.) Kit: £13-99. Ready built: £16-99. Details of dimmers, sequencers and other lighting control units available on request. Mail order or written enquiries only to:

SELEKTRON

21 Prior's Road, Windsor, Berks. SL4 4PD

PRINTED CIRCUIT BOARDS. All prices inclusive of P. & P., etc. No extras. We offer PCB's ready for assembly for: The "P.W." Disco Amplifier **£3-60** each. "P.W." Disco Light Modulator **£2-90**. "P.W." Tele-tennis (6 PCB's) **£3-70**; sound effects **£1-10**; Ball-speed **£1-10**. Ferret **85p**. Derby **£1**. Electronic Clock **£2-07**. Easy-Build Organ (2 PCB's) **£5-80**. Home Telephone Exchange **£1-64**. "P.E." Joanna (all issues) **£1-25** each, all 14 **£15**. Power Slaves (3 PCB's) **£1-62**. CCTV (2 PCB's) **£2-18**. Orion **£2-26**. Many others available. S.A.E. for lists of PCB's and direct PCB supplies. We also sell direct, Art/Graphic aids and supplies. Cat. 40p. **PRODUCTION SPACE AVAILABLE**, for PCB production, silk-screen printing, tinning, PCB design, electroplating, plus all art/graphic, photographic and design facilities. Production estimates by return upon submission of "Rough Copy", PCB Master or Circuit Diagram or phone: W.K.F. ELECTRONICS, Welbeck Street, Whitwell, Worksop, Notts., S80 4TW. Tel. Whitwell (Derbys.) 695 STD 090974. Callers seen by appointment only at 1-3 Station Road, Whitwell.

ELECTRO SPARES
ARE STILL SUPPLYING BOTH THE P.E. VARICAP STEREO PUSH BUTTON F.M. TUNER KIT Easy to construct, highest quality reproduction. **£33-50 inc. VAT & Postage.** S.A.E. for brochure.


AND P.E. 'GEMINI' STEREO AMP. All components available. Send 55p + 9p P. & P. for full constructional booklet containing performance details, specification assembly instruction and fault finding guide, etc., etc.

CAR OWNERS! DON'T FORGET THE 'MANTA' ELECTRONIC IGNITION SYSTEM, for reduced petrol consumption and smoother running. Kit **£15-50 inc. VAT** and P. & P. Assembled **£17-15**.

ELECTRO SPARES, DEPT. PE1
288 ECCLESHALL ROAD - SHEFFIELD S11 8PE

DO-IT-YOURSELF LOUDSPEAKERS for hi-fi are our speciality. Full range of components and accessories including chassis speakers, cross-overs, sound absorbent, grille fabrics, etc., always available. We stock the fabulous value Helme speaker kits (complete with full and easy instructions), also Peerless and Wharfedale kits. Just about the lowest prices anywhere! Send 8p stamp for bargain list to: AUDIOSCAN, Dept. PE1, 4 Princes Square, Harrogate, North Yorkshire.

MINI ACCUMULATORS

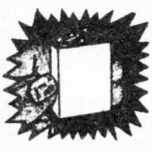

2 volt 'MULTI-USE' Sealed Lead Acid Rechargeable Cells.
Size L450—1.4" x 1.1" x 0.44". 3 for **£2-15** inc. P. & P.
Size GA2—1.7" x 1.3" x 0.3". 3 for **£2-65** inc. P. & P.
Suits Fi-Cord

GARFIELDS, 295 Rye Lane, London SE15

LOW COST I.C. MOUNTING for any size DIL package. 100 pin sockets **50p**. 7 and 8 hole plastic supports **5p** pair. Quantity rates. S.A.E. details and sample. Trial pack **50p**. (P. & P. 10p order). P.K.G. ELECTRONICS, Oak Lodge, Tansley, Derbyshire, DE4 5FE.

OVAL DIGITAL CLOCK CASES
Attractive stoneware pottery cases; 'oatmeal' glazed; suitable for most digital clock circuits that use 4 or 6 digit L.E.D. displays.
ONLY **£3-60** inclusive
Send S.A.E. for full details of above and many others, to:
J. BARRIE-SMITH
56 Conifer Road, Coxford, Southampton, Hants.

CLEARING LABORATORY, scopes, recorders, testmeters, bridges, audio, R.F. generators, turntables, tapeheads, stabilised P.S.U.s, sweep generators, test equipment, etc. Lower Beeding 236.

BUILD THE **TREASURE TRACER MK III** Metal Locator



- Varicap tuning
- Britain's best selling metal locator kit
- Fitted with Faraday shield
- Speaker and earphone operation
- Knocks down to only 17in.
- Prebuilt search coil assembly
- Five transistor circuit
- Thoroughly professional finish
- You only need soldering iron, screw-driver, pliers and snips
- As seen on BBC-1 and BBC-2 TV

Send stamped, addressed envelope for leaflet

Complete kit **£10-90** Post 60p - 92p VAT (8%)
Built and tested **£15-25** Post 60p - £1-27 VAT (8%)

MINIKITS ELECTRONICS, 6g CLEVELAND ROAD LONDON E18 2AN (Mail Order Only)

ENAMELLED COPPER WIRE

S.W.G.	1lb reel	1/2 lb reel
10 to 19	£2-40	£1-35
20 to 29	£2-45	£1-40
30 to 34	£2-60	£1-50
35 to 40	£2-85	£1-60

All the above prices are inclusive of postage and packing in the U.K.

COPPER SUPPLIES
102 Parrwood Road, Withington, Manchester 20
Telephone 061-445 8753

SUPERB INSTRUMENT CASES by Bazelli, manufactured from heavy duty PVC faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range, competitive prices start at a low 75p. Examples, Width, Depth, Height, 8" x 5" x 3" **£1-55**; 10" x 6" x 3" **£2-20**; 10" x 8" x 3" **£2-75**; 12" x 10" x 3" **£3-60**; 8" x 4" x 4" **£1-80**; 10" x 6" x 4" **£2-70**; 12" x 8" x 4" **£3-60**; 7" x 7" x 5" **£2-65**; 8" x 10" x 6" **£3-60**; 12" x 8" x 7" **£4-12**; 12" x 12" x 7" **£4-40**. Plus 8% VAT & 50p postage. Over 200 models to choose from. Prompt despatch. Free literature (stamp would be appreciated). BAZELLI, Dept. No. 23, St. Wilfrid's, Foundry Lane, Halton, Lancaster LA2 6LT.

KIMBER-ALLEN
The world's finest keyboard

Frictionless knife-edge pivots; laminated keys; perfect touch; strong alloy frame.
KA are the sole makers of the "G" series gold wire contact blocks. You get lower prices and delivery priority by ordering from the distributor:

ALAN DOUGLAS
Lees Barn Road
Radcliffe on Trent
Notts NG12 2DS

12 VOLT 21in 13 watt **FLOURESCENT LIGHTING** (by THORN/AEI) with diffuser and on/off switch. Ideal, caravan, boat, emergency lighting, etc. Guaranteed



£5-50 inc. VAT and post. List price £7-02 inc. VAT

SALOP ELECTRONICS Tel. 53208
23 Wyle Cop. Shrewsbury. Shropshire

ALUMINIUM PROJECT BOXES, lids and screws included

Box No.	Length"	Width"	Height"	Price
7	5 1/2	2 1/2	1 1/2	47p
8	4	4	1 1/2	48p
9	4	2 1/2	1 1/2	46p
10	5 1/2	4	1 1/2	49p
11	4	2 1/2	2	46p
12	3	2	1	38p
13	6	4	2	58p
14	7	5	2 1/2	75p
15	8	6	3	93p
16	10	7	3	£1-14

Prices include VAT (at 8%) but 18p should be added to the total order value for postage & packing.

8 WATT 12V FLOURESCENT LIGHT KIT Complete Kit including all components, heatsink, channel, tube, etc. Only **£3-49** inc. VAT p. & p. Ready built **£4-10** inc. VAT p. & p. Diffuser **95p** extra inc. VAT p. & p.
Send cheque or P.O.'s with your order direct to:
ELECTRONICS DESIGN ASSOCIATES
Dept. PE, 82 Bath Street, Walsall, WS1 3DE.
Phone, Walsall 33652

DIGITAL CLOCK COMPONENTS. AY-5-1224 clock chip, **£3-66**. 0-3in high economy type LED displays, DL-704E, **85p**; 0-6in high ditto, DL-747E **£1-70**. P.C.B. to suit chip and displays, etc. (two types), **95p** each. MK 50253 alarm clock chip, **£5-50**. Full details of both chips, circuit diagrams, data, etc., free on request. Add 10p per order and VAT at 8%. **GREENBANK ELECTRONICS** (Dept. ECP), 94 New Chester Road, New Ferry, Wirral, Merseyside, L62 5AG.

BUILD YOUR OWN
YOU ARE INVITED TO SEND S.A.E. FOR LISTS ON OUR VERY EXTENSIVE RANGE OF HIGH QUALITY AMPLIFIERS, PRE-AMPS, F.M. TUNERS, INSTRUMENTS, RADIO CONTROL, IGNITION UNITS AND MANY OTHER KITS. STATE REQUIREMENTS.

TELERADIO ELECTRONICS
325 Fore St., Edmonton, London N9

HOME SCIENTISTS
Get the key to a FANTASTIC WORLD of previously UNHEARD-OF PROJECTS. The NEW Boffin catalogue lists LOTS of HIGHLY UNUSUAL, LOW-COST BARGAINS, READY-BUILT MODELS.

Here are just a few examples, there are stocks more!

Dazzling MINI-STROBE (pocket size) **£3-50**
PEOPLE DETECTOR **£4-20**
Big-Ear SOUND-CATCHER **£4-20**
Mini DREAM LABORATORY **£4-20**

Don't take our word for it though! GET A COPY AND SEE! SEND ONLY 20p and we'll RUSH YOU A COPY (YOU'LL GET THE 'GOODIES' JUST AS QUICKLY TOO!)

BOFFIN PROJECTS
4 Cunliffe Road, Stoneleigh Ewell, Surrey
(Mail Order U.K. only)

BREAK INTO I.C.S. THIS WINTER
Using our I.C. Experimental/Educational Kits, you can learn all about the modern digital logic techniques. These step-by-step Kits contain specially selected I.C.s, Holders, Veroboard, L.E.D.s, instructions and data. Available at **£3-50** each (including P. & P.). Kit One: Gates. Kit Two: Flip-Flops. Kit Three: Shift Registers. Kit Four: Counters. S.A.E. for further details to:
AUTOMATED HOMES
69 High Street, Ryton, Coventry, CV8 3FJ.
(Mail order only.)

PRINTED CIRCUITS and HARDWARE

Readily available supplies of Constructors' hardware, Aluminium sheet and sections. Printed circuit boards, top quality for individual or published designs.

Prompt service.

Send 15p for catalogue.

RAMAR CONSTRUCTOR SERVICES
Masons Road, Stratford on Avon
Warwicks. Tel. 4879

THE SCIENTIFIC WIRE CO.

Copper—Nickel Chrome—Eureka—
Manganin Wires.
Enamelled—Silk—Cotton—Tinned
Coverings.
No minimum charges or quantities.
S.A.E. Brings Lists.
Trade and export enquiries welcome.
P.O. BOX 30, LONDON E4 9BW

ENTHUSIAST DISPOSING of surplus equipment. Quantity of fibre p.c. boards, s/s, d/s, Bakelite sheets, all cut to size **1p/sq. in.** Intercom units **£1** each; pocket TXs; crystal insert mics; Yaxley switches; TX crystals 8500kHz; micro-wave diode CS2/A. 20-way pvc cable **15p** metre. Also various components. Phone Ware (Herts) 4008.

SPECIAL CABLE OFFER
Coax UR95 3p per Metre. UR70 6p per M. UR43 6p per M. Twin mic cable 5p per M.
Mains Twin PVC Oval, 16/0.2mm 5p per M.
4-core Screened 8p; 8-core 10p; to Max 23m coils.
20-core Screened 15p per M; to Max 7m coils.
Equipment wire £1 per 100m; £4.25 per 500; £8 per KM.
Mains Isolation Transformer, 240V, 250 watt **£2.95** post 90p.
All items include VAT; Carriage Extra; S.A.E. samples and lists.
W. H. WESTLAKE, CLAWTON, HOLSORTHY, DEVON

GLASS FIBRE P.C.B.s. Send 1:1 master and **50p** per board plus **7p** per square inch tinned, or plus **9p** per square inch drilled and tinned. Discount for quantity. **PROTO DESIGN, 4 Higheliffe Way, Wickford, Essex, SS11 5LA.**

2½kg parcels surplus electronic components, resistors, capacitors, switches, pots etc. £1.20 p & p 75p.
Wirewound resistors 2W and upwards mixed values 120 for £1, p & p 42p.
Lights bulbs mixed voltage and wattage eg. 2.5v, 6v, 12v etc. from 0.5 watt upwards, including panel lights and vehicle bulbs 30 for £1, p & p 30.
R. A. Stobbs, 933 Manchester Road, Cowlesley, Huddersfield, Yorks HD45TA

INDEBIT WASHING MACHINE service Manuals. Diagrams, faults. Complete with spare parts order forms. Send **£2.50. MERCHANT.** Domestic Services, Shotton, Clwyd, N. Wales.

CABINET FITTINGS

FOR

Stage Loudspeakers and Amplifier Cabs
Fretcloths, Coverings, Recess Handles, Strap
Handles, Feet, Castors, Locks and Hinges,
Corners, Trim, Speaker Bolts, etc., etc.
Send 2 x 8p Stamps for samples and list.

ADAM HALL (P.E. SUPPLIES)

Unit A, Starline Works, Grainger Road
Southend-on-Sea, Essex.

FANTASTIC NEW MICROTEST 80

MEASURES ONLY


90 x 70 x 18mm
ELECTRONIC ZERO Ω



Amazing Value at **£11.95**
8 fields of measurement
and 40 ranges

PRINTED CIRCUIT BOARD IS REMOVABLE WITHOUT SOLDERING

Volts d.c. 8 ranges: 100mV, 2V, 10V, 50V, 200V, 1.000V (20kΩ/V), 2% precision on 2, 5 and 50.
Volts a.c. 5 ranges: 1.5V, 10V, 50V, 250V, 1.000V (4kΩ/V).
Amp. d.c. 6 ranges: 50μA, 500μA, 5mA, 50mA, 500mA, 5A.
Amp. a.c. 5 ranges: 250μA, 2.5mA, 25mA, 250mA, 2.5A.
Ohms 4 ranges: Low Ω, Ω x 1, Ω x 10, Ω x 100 (from 1/10 of Ω until 5MΩ).
V Output 5 ranges: 1.5V, 10V, 50V, 250V, 1.000V.
Decibels 5 ranges: +6dB, +22dB, +36dB, +50dB, +62dB.
Capacity 4 ranges: 25μF, 250μF, 2.500μF, 25.000μF.

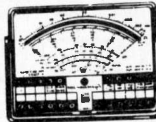

SUPERTESTER 680R ICE
20,000 Ohm per Volt sensitivity
● Fully screened against external magnetic fields ● Scale width and small case dimensions (128 x 95 x 32mm) ● Accuracy and stability (1% in D.C., 2% in A.C.) of indicated reading ● Simplicity and ease of use and readability ● Full ranges of accessories


● 1,000 times overload ● Printed circuit board is removable without desoldering ● More ranges than any other meter. Ask for free catalogue.
Accessories (extra) available to convert Microtest 80 and Super Tester 680R into following: LIGHTMETER, GAUSS METER, ELECTRONIC VOLTMEASURER, AMPER-CLAMP, TRANSISTOR TESTER, TEMPERATURE PROBE, PHASE SEQUENCE INDICATOR, Ω x 100kΩ Multiplier, SIGNAL INJECTOR—Send for details.

£18.50

Accessories Extra

MORE RANGES FOR LESS MONEY!


AC/DC Multimeter type U4324

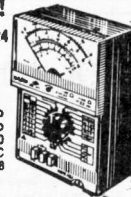

A-DC 0-06-3A-6 Ranges.
A-AC 0-3-3A-5 Ranges.
V-DC 0-6-120V V-9 Ranges.
V-AC 3-900 V-8 Ranges.
Frequency in the range of 45 to 20kHz. Resistance: 500 ohm to 5 Mohm—5 ranges. Decibel: -10 to +12dB. Accuracy: ±2.5% DC ±4% AC. Dimensions: 167 x 98 x 63mm.
Only £9.25

ALPHANUMERIC NIXIE TUBES B7971

The Alphanumeric NIXIE tube has the ability to display all the letters of the alphabet, numerals 0 thru 9 and special characters in a single tube. From the standpoint of both readability and electrical characteristics, the Alphanumeric NIXIE tube provides many unique benefits including: * 170V-21mA * All d.c. operation * Uniform, continuous line characters of equal height * Memory with simple solid state drive circuits * Readability in high ambient light * 200 footcandle brightness * Long life with no loss of brightness * Character height 2½in.

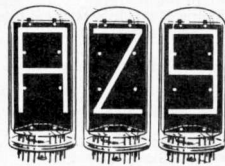

Bases for above 80p each.
Price only 99p each plus 18p P.P.

JUST ARRIVED! !

NUMERIC INDICATOR TUBES

Ultra-long life, high quality, 0-9 and 2 independent decimal points. Supply voltage 200V d.c. Current 14mA. Pulse duration 100μs. Character height 0.51, overall size 1.4.
Brand new, guaranteed. Surplus to manufacturer's requirements. Type B5853at

1-25 **£1.00**; 25+ **90p**; 100+ **80p**;
1,000+ price on application.

Add 8% VAT to all items + 35p P. & P.
ELECTRONIC BROKERS LTD.
49-53 Pancras Road, London NW1 2QB
Tel. 01-837 7781

PRINCIPLES OF TRANSISTOR CIRCUITS

by S. W. Amos Price **£3.45**

NEW EDITION

RADIO VALVE AND SEMICONDUCTOR DATA by A. M. Ball Price **£2.50**

110 OPERATIONAL AMPLIFIER PROJECTS FOR THE HOME CONSTRUCTOR by R. M. Marston Price **£2.00**

ELECTRONICS SELF-TAUGHT WITH EXPERIMENTS AND PROJECTS by J. Ashe Price **£2.10**

TRANSISTOR POCKET BOOK by R. G. Hibberd Price **£3.00**

PRINCIPLES OF TRANSISTOR CIRCUITS by S. W. Amos Price **£3.45**

ELECTRONICS AN ELEMENTARY INTRO. FOR BEGINNERS by L. W. Owers Price **£1.65**

ELEMENTARY TELECOMMUNICATION PRACTICE by J. R. G. Smith Price **£1.50**

SCR MANUAL INCLUDING TRIACS AND OTHER THYRISTORS 5th edition by G.E. Price **£1.90**

SOLID STATE HOBBY CIRCUITS by R.C.A. Price **£1.20**

TEST EQUIPMENT FOR THE RADIO AMATEUR by H. L. Gibson Price **£2.05**

FOUNDATIONS OF WIRELESS AND ELECTRONICS 9th edition by M. G. Scroggie Price **£2.25**

★ PRICES INCLUDE POSTAGE ★

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST of British and American Technical Books

19-21 PRAED STREET

LONDON W2 1NP

Phone 01-723 4185

Closed Saturday 1 p.m.

BRIDGE

ELECTRONICS COMPONENTS

AC126	£	BD138	£	2N2218A	£
AC127 <td>0-13</td> <td>BD139</td> <td>0-29</td> <td>2N2219</td> <td>0-17</td>	0-13	BD139	0-29	2N2219	0-17
AC128	0-11	BD140	0-32	2N2219A	0-18
AC151	0-18	BDY56	1-00	2N2221	0-17
AC152	0-25	BF115	0-20	2N2221A	0-18
AC153	0-27	BF199	0-12	2N2222	0-17
AC176	0-14	BF194	0-09	2N2646	0-30
AC187K	0-27	BF195	0-09	2N2904	0-18
AC188K	0-27	BF198	0-12	2N2905	0-18
AD161	0-35	BF199	0-12	2N2906	0-18
AD162	0-35	BF257	0-24	2N2907	0-18
BA102	0-10	BF258	0-24	2N2926G	0-09
BAK13	0-03	BF259	0-24	2N3053	0-20
BAK16	0-04	BFK29	0-22	2N3054	0-40
BC107	0-09	BFK30	0-22	2N3055	0-45
BC108	0-09	BFK84	0-20	2N3393	0-12
BC109	0-09	BFK85	0-27	2N3441	0-56
BC147	0-09	BFY50	0-18	2N3442	0-56
BC148	0-09	BFY51	0-18	2N3638	0-19
BC149	0-09	BFY52	0-19	2N3638A	0-19
BC167	0-10	BY126	0-11	2N3702	0-18
BC168	0-10	BY127	0-11	2N3704	0-18
BC180	0-10	CA47	0-36	2N3706	0-19
BC182	0-09	CA80	0-04	2N3708	0-10
BC183	0-09	CA91	0-04	2N3771	1-25
BC184	0-09	CA200	0-05	2N3772	1-35
BC212	0-09	CA202	0-36	2N3773	0-90
BC213	0-09	IN114	0-04	2N3904	1-11
BC214	0-09	IN4004	0-05	2N3906	0-12
BC237	0-01	IN4007	0-06	2N5294	0-35
BC238	0-08	IN4148	0-03	2N5296	0-35
BC239	0-08	IS20	0-25	2N5494	0-30
BC307	0-09	2N697	0-15	2N3819	0-30
BC308	0-09	2N698	0-14	2N4036	0-55
BC309	0-09	2N708	0-10	2N4037	0-40
BC327	0-12	2N709	0-10	2N4821	0-80
BC328	0-12	2N918	0-23	2N5080	0-25
BCY70	0-13	2N1305	0-25	2N4289	0-25
BCY71	0-13	2N1307	0-25	2N5447	0-12
BCY72	0-12	2N1308	0-25	2N5449	0-12
BD135	0-25	2N1613	0-15	2N5457	0-30
BD136	0-26	2N1711	0-15	2N5458	0-27
BD137	0-27	2N2218	0-17	2N8027	0-48

FULLY GUARANTEED

Mail order only VAT extra p&p 20p
Bridge Electronics
PO Box No. 10 Fishponds Bristol BS16 2LX

CHROMASONIC electronics

Dept 2, 56, Fortis Green Road,
Muswell Hill, London, N10 3HN.
telephone: 01-883 3705

C-MOS I.C. SOCKETS LINEAR I.C.'s

C-MOS	MIX PRICES		
	1-24	25-99	100 up
CD4000AE	19p	17p	14p
CD4001AE	19p	17p	14p
CD4002AE	19p	17p	14p
CD4006AE	£1.59	£1.33	£1.06
CD4007AE	23p	19p	15p
CD4008AE	£1.75	£1.46	£1.17
CD4009AE	Use	CD0409*	
CD4010AE	Use	CD0405*	
CD4011AE	19p	17p	14p
CD4012AE	19p	17p	14p
CD4013AE	59p	50p	46p
CD4014AE	£1.75	£1.46	£1.17
CD4015AE	£1.75	£1.46	£1.17
CD4016AE	55p	48p	44p
CD4017AE	£1.29	£1.07	93p
CD4018AE	£1.89	£1.56	£1.25
CD4019AE	80p	66p	53p
CD4020AE	£1.97	£1.64	£1.31
CD4021AE	£1.75	£1.46	£1.17p
CD4022AE	19p	17p	14p
CD4022AE	£1.83	£1.53	£1.22
CD4024AE	£1.26	£1.05	84p
CD4025AE	19p	17p	14p
CD4026AE	£2.79	£2.32	£1.86
CD4027AE	98p	82p	65p
CD4028AE	£1.53	£1.28	£1.02
CD4029AE	£1.89	£1.56	£1.15
CD4030AE	71p	59p	47p
CD4035AE	£1.75	£1.46	£1.17
CD4040AE	£2.01	£1.69	£1.34
CD4042AE	£1.49	£1.24	99p
CD4046AE	£2.15	£1.79	£1.44
CD4049AE	69p	58p	46p
CD4050AE	69p	58p	46p
CD4051AE	£2.78	£2.32	£1.85
CD4052AE	£2.78	£2.32	£1.85
CD4056AE	£2.12	£1.76	£1.41
CD4060AE	£2.39	£1.99	£1.55
CD4066AE	£1.13	94p	75p
CD4068AE	28p	24p	19p
CD4069AE	28p	24p	19p
CD4070AE	28p	24p	19p
CD4071AE	28p	24p	19p
CD4072AE	71p	59p	47p
CD4081AE	28p	24p	19p
CD4082AE	28p	24p	19p
CD4085AE	£1.38	£1.06	85p
CD4086AE	£1.28	£1.06	85p
CD4093AE	£1.56	£1.20	£1.04
CD4099AE	£2.95	£2.46	£1.96
CD4511AE	£2.36	£1.79	£1.44
CD4528AE	£1.30	£1.08	87p

I.C. SOCKETS



Pin Sockets, pins in strips of 100. Just snap off what you need. 65p per strip.

Dual in line *

8 pin 13p 24 pin 26p TOS 70S
14 pin 15p 28 pin 30p 8 pin 31p
16 pin 15p 36 pin 39p.

FREE CIRCUITS

Our 8 Page A4 Audio I.C. Booklet is supplied FREE with purchases of Linear I.C.'s worth £1. or more (35p. if sold alone) Contains circuits and pin connections

15 Amplifiers 250 mV to 20 watts
5 Audio Pre-Amplifiers
1 Tape Pre-Amplifier
1 Power Driver
1 Instrument Amplifier (Bifet)
1 General Purpose Mini Amplifier
1 D.C. Controlled Gain Amplifier
1 Micro-mini Radio (2 I.C.'s)

PHOTO-DARLINGTON



Vcc 25v 2N5777
Vcc 25v
Veb 8v
I_l 250 mA
Pd 200 mW
Hfe 2500

LINE-O-LIGHT



NEW LED Linear Cursors each device contains 10 light emitting diodes in a 20 pin dual in-line package. Ideal for solid state analogue meters or dials. Type 101 RED £2.26. * Complete with leaflet.

74 TTL

74 TTL	MIX PRICES		
	1-24	25-99	100+
7400	14p	12p	10p
7401	14p	12p	10p
7402	14p	12p	10p
7403	15p	12p	10p
7404	16p	13p	11p
7408	16p	13p	11p
7409	16p	13p	11p
7410	16p	13p	11p
7413	29p	24p	20p
7417	27p	22p	20p
7420	16p	13p	11p
7427	27p	22p	18p
7430	16p	13p	11p
7432	27p	22p	18p
7437	27p	22p	18p
7441	75p	62p	50p
7442	65p	55p	43p
7445	85p	71p	57p
7447	81p	75p	65p
7448	75p	62p	50p
7447A	95p	83p	67p
7470	29p	25p	20p
7472	25p	21p	17p
7473	30p	25p	20p
7474	30p	26p	21p
7475	47p	39p	31p
7476	37p	26p	21p
7482	75p	67p	50p
7485	£1.30	£1.09	87p
7486	32p	26p	21p
7489	£2.92	£2.80	£2.10
7490	49p	40p	32p
7491	60p	55p	45p
7492	57p	46p	36p
7493	45p	40p	32p
7495	67p	55p	45p
74100	£1.08	89p	72p
74107	35p	28p	22p
74121	34p	28p	23p
74122	47p	39p	31p
74141	78p	65p	53p
74145	68p	58p	48p
74154	£1.67	£1.48	86p
74174	£1.00	83p	67p
74180	£1.06	88p	71p
74181	£3.20	£2.50	£1.90
74192	£1.35	£1.14	90p
74193	£1.35	£1.14	90p
74196	£1.64	£1.34	99p

555 (8 pin dip)	55p
555 (TO-9)	81p
556 (14 pin dip)	£1.29
703 (RF/IF Amp)	68p
709 (8 pin dip)	38p
709 (TO-9)	45p
709 (14 pin dip)	39p
710 (8 pin dip)	39p
710 (TO-9)	45p
710 (14 pin dip)	44p
711 (TO-9)	51p
711 (14 pin dip)	44p
720 (A.M. Radio)	£1.76
723 (TO-9)	£1.09
723 (14 pin dip)	55p
741 (8 pin dip)	30p
741 (TO-9)	43p
741 (14 pin dip)	36p
747 (14 pin dip)	£1.04
748 (TO-9)	42p
748 (14 pin dip)	49p
753 (F.M. 1st. f.)	£1.08
75491	88p
75492	£1.10

Regulators 100mA	
78105WC (TO-9)	60p
78112WC (TO-9)	60p
78115WC (TO-9)	60p
Regulators 100mA	
78105AWC (TBA625A)	90p
78112AWC (TBA625B)	90p
78115AWC (TBA625C)	90p

Regulators 500mA	
78M05HC	£1.35
78M12HC	£1.35
78M15HC	£1.35
78M18HC	£1.35
78M24HC	£1.35


Regulators 1A	
7805KC (TO-3)	£2.09
7812KC (TO-3)	£2.09
7815KC (TO-3)	£2.09
7818KC (TO-3)	£2.09
7824KC (TO-3)	£2.09
Regulators 1A	
7805UC (TO-220)	£1.72
7812UC (TO-220)	£1.72
7815UC (TO-220)	£1.72
7818UC (TO-220)	£1.72
7824UC (TO-220)	£1.72

IC18030	£3.52
LM0011 (TO-3)	£1.46
LM0311 (TO-3)	£1.46
LM0371 (TO-3)	£1.46
LM129 (SOT-3)	85p
LM130 (SOT-3)	85p
LM131 (SOT-3)	85p
LM301T (TO-9)	65p
LM301S (8 pin dip)	59p
LM301A (8 pin dip)	59p
LM307 T (TO-9)	59p
LM307 S (8 pin dip)	59p
LM308 T (TO-9)	£1.76
LM308 S (8 pin dip)	99p
LM308A T (TO-9)	£2.92
LM308A S (8 pin dip)	£6.90
LM309K	£2.34
LM339	£2.25
LM370N	£2.85
LM371	£2.08
LM372N	£1.99
LM373N	£2.99
LM377N	£2.71
LM380	£1.25
LM381	£1.85
LM382	£1.64
LM402	£1.64
LM4820	£1.03

LM2111	£1.12
LM3900	69p
LM3909	66p
MC1303L	£1.94
MC1306L	85p
MC1310P	£2.10
MC1312P	£2.52
MC1314P	£4.34
MC1315P	£4.85
MC1327P	£1.48
MC1330P	89p
MC1339P	£1.80
MC1350	68p
MC1351	92p
MC1352	92p
MC1357	£1.60
MC1358 (CA3065)	£1.23
MC1375	£1.86
MC1455 (555T)	65p
MC1456CG	£1.77
MC1458CP1	89p
MC1468G	£2.30
MC1495L	£4.48
MC1496G	£1.01
MC3302P	£1.65
MC3401P	81p
MFC4000B	87p
MFC4060A	85p
MFC6030A	85p
MFC6040	£1.01
MM5314	£4.80
MM5316	£9.99

MVRSV (TO-3)	£1.45
MVR12V (TO-3)	£1.45
MVR15V (TO-3)	£1.45
NE540L	£1.25
NE545A	£1.16
NE555V	69p
NE556	£1.29
NE560B	£5.06
NE561B	£5.06
NE562B	£5.06
NE563	£2.96
NE565N	£2.63
NE566V	£1.87
NE567V	£2.63
SD6000	£1.22
SL414A	£2.09
SL415A	£2.75
SL437D	£7.05
SL440	£2.84
SN75491	88p
SN75492N	£1.10
ZN414	Leaflet free with devices (10p alone)
ZN414	£1.26

3 1/2 DECADE DVM I.C.

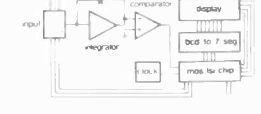


This state-of-the-art MOS LSI chip contains all the logic necessary for a 3 1/2 decade, dual slope integrating, automatic polarity detecting DVM. Supplied with free data and circuit booklet. AY-5-3507

OUR PRICE ONLY £6.59 * (Data and Circuit Booklets alone 20p.)

The AY-5-1224 tick-tock

Another marvel from G.I. A 16 pin 12-24 hr. Clock I.C. with 25 pin capability and low external parts count. Supplied with manufacturers detailed leaflet £3.95p (inc VAT) (Leaflet alone 20p.) Full Kit (excluding case) available towards end of 1975. Phone Clive for details.

MULLARD MODULES

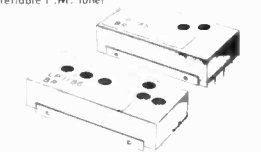

Still make the simplest, highly reliable F.M. tuner

LP1186 Varactor front end	£8.60
LP1185 1 F. Strip	£6.95
LP1400 Multiplex decoder	£9.02

7400	14p	12p	10p
7401	14p	12p	10p
7402	14p	12p	10p
7403	15p	12p	10p
7404	16p	13p	11p
7408	16p	13p	11p
7409	16p	13p	11p
7410	16p	13p	11p
7413	29p	24p	20p
7417	27p	22p	20p
7420	16p	13p	11p
7427	27p	22p	18p
7430	16p	13p	11p
7432	27p	22p	18p
7437	27p	22p	18p
7441	75p	62p	50p
7442	65p	55p	43p
7445	85p	71p	57p
7447	81p	75p	65p
7448	75p	62p	50p
7447A	95p	83p	67p
7470	29p	25p	20p
7472	25p	21p	17p
7473	30p	25p	20p
7474	30p	26p	21p
7475	47p	39p	31p
7476	37p	26p	21p
7482	75p	67p	50p
7485	£1.30	£1.09	87p
7486	32p	26p	21p
7489	£2.92	£2.80	£2.10
7490	49p	40p	32p
7491	60p	55p	45p
7492	57p	46p	36p
7493	45p	40p	32p
7495	67p	55p	45p
74100	£1.08	89p	72p
74107	35p	28p	22p
74121	34p	28p	23p
74122	47p	39p	31p
74141	78p	65p	53p
74145	68p	58p	48p
74154	£1.67	£1.48	86p
74174	£1.00	83p	67p
74180	£1.06	88p	71p
74181	£3.20	£2.50	£1.90
74192	£1.35	£1.14	90p
74193	£1.35	£1.14	90p
74196	£1.64	£1.34	99p

LED DISPLAYS




Litronic Double Digit Displays
0.5" Common Anode; 2 R/H
Decimal Points
DL21 ±
DL22 ±
Suitable for Clocks, Meters, Instruments, Channel Indicators
Our Price £4.75 each

Low cost Red GaAsP	0.33
Motorola MLED 500	0.33
in a 1092 package	0.33
	0.43
	0.63

15p.

DIGITAL SWITCH



BCD encoded digital switch Reading 0 to 9. Suitable for digital clock alarm setting DVM input scaling etc.

1 to 9. £1.49 each

LIGHT EMITTING DIODES

Free snap-on plastic retainer

0.125" dia lens	10			100		
	1p	15p	13p	27p	24p	23p
Red	1p	15p	13p	27p	24p	23p

FREE To PE READERS THE CURRENT MAPLIN SUPER CATALOGUE UNTIL JANUARY 31, 1976

Projects for you to build

4-digit clock, 6-digit clock, 10W high quality power amp., High quality stereo pre-amp., Stereo Tuner, F.M. Stereo decoder, etc., etc.

CIRCUITS . . . Frequency Doublers, Oscillators, Timers, Voltmeters, Power Supplies, Amplifiers, Capacitance Multiplier, etc., etc.

Full details and pictures of our wide range of components, e.g. capacitors, cases, knobs, veroboard, edge connectors, plugs and sockets, lamps and lampholders, audio leads, adaptor plugs, rotary and slide potentiometers, presets, relays, resistors (even 1% types!), switches, interlocking pushbutton switches, pot cores, transformers, cable and wire, panel meters, nuts and bolts, tools, organ components, keyboards, L.E.D.s, 7-segment displays, heatsinks, transistors, diodes, integrated circuits, etc., etc.



132 pages!

ALL IN OUR SUPER CATALOGUE
REALLY GOOD VALUE FOR MONEY AT JUST 40p.


56 Penn

**MAPLIN
ELECTRONIC
SUPPLIES**

**SUPERSONIC
SAME-DAY-SERVICE
QUALITY COMPONENTS
-FAST!**

NOW TURN TO PAGE 33
FOR A SELECTION OF
THE COMPONENTS
WE STOCK

ELECTRONIC ORGAN

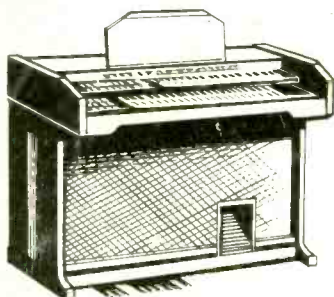

Build yourself an exciting Electronic Organ. Our leaflet MES51, price 15p, deals with the basic theory of electronic organs and describes the construction of a simple 49-note instrument with a single keyboard and a limited number of stops.

Leaflet MES52, price 15p, describes the extension of the organ to two keyboards each with five voices and the extension by an octave of the organ's range.

Solid-state switching and new footages along with a pedal board and a further extension of the organ's range are shown in leaflet MES53, priced at 35p. (Pre-publication price 15p.)

No more doubts about prices

Now our prices are GUARANTEED (changes in VAT excluded) for two month periods—and we'll tell you about price changes in advance for just 30p a year (refunded on purchases). If you already have our catalogue send us an S.A.E. and we'll send you our latest list of GUARANTEED prices. Send us 30p and we'll put you on our mailing list—you'll receive immediately our latest price list then every two months from the starting date shown on that list you'll receive details of our prices for the next GUARANTEED period before the prices are implemented!—plus details of any new lines, special offers, interesting projects—and clip-off coupons to spend on components to repay your 30p when used as directed.

NOTE: The price list is based on the Order Codes shown in our catalogue so an investment in our super catalogue is an essential first step.

Call in at our shop, 284 London Road, Westcliff-on-Sea, Essex. Please address all mail to P.O. Box 3, Rayleigh, Essex, SS6 8LR.

SYNTHESISER



A reprint of the complete article giving full construction details published by "Electronics Today International" between January-

September '74 of the International Voltage Controlled Synthesiser, developed as a "state of the art", now available, price £1.50. S.A.E. please for specification.

GRAPHIC EQUALISER



A really superior high quality stereo graphic equaliser as described in the January edition of "Electronics Today International". We stock all

the parts (except woodwork) including the metalwork drilled and printed. 15p brings you a reprint of the article.

**MAPLIN
ELECTRONIC
SUPPLIES**

P.O. Box 3 Rayleigh Essex SS6 8LR.
Telephone: Southend-on-Sea (0702) 44101