

# PRACTICAL WIRELESS

NOVEMBER  
1971

20p

BUILD THIS  
2-Octave  
Miniature Organ



What  
to look  
for at the  
**AUDIO  
FAIR**

Also:

Basic Signal Generator  
Comprehensive Multi-Band Receiver

# ADCOLA Soldering Instruments add to your efficiency

## THE NEW 'INVADER'

### ADCOLA L.646

for Factory Bench Line Assembly

A precision instrument—supplied with standard 3/16" (4.75 mm) diameter, detachable copper chisel-face bit\*.

Standard temp. 360 c at 23 watts.


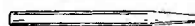
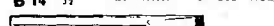

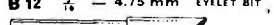
Special temps. from 250°c—410°c.

**PRICE**  
**£1.85**




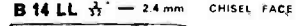


#### \*Additional Stock Bits (illustrated) available

##### COPPER

-  **B 38**  $\frac{1}{4}$ " — 3.2 mm CHISEL FACE
-  **B 14**  $\frac{3}{16}$ " — 2.4 mm CHISEL FACE
-  **B 24**  $\frac{1}{4}$ " — 4.75 mm SCREWDRIVER FACE
-  **B 12**  $\frac{3}{16}$ " — 4.75 mm EYELET BIT
-  **B 58**  $\frac{1}{2}$ " — 6.34 mm CHISEL FACE

##### LONG LIFE

-  **B 42 LL**  $\frac{1}{4}$ " — 4.75 mm CHISEL FACE
-  **B 38 LL**  $\frac{1}{4}$ " — 3.2 mm CHISEL FACE
-  **B 14 LL**  $\frac{3}{16}$ " — 2.4 mm CHISEL FACE
-  **B 44 LL**  $\frac{1}{4}$ " — 4.75 mm SCREWDRIVER FACE

Don't take chances. We don't. All our ADCOLA Soldering Instruments are of impeccable quality. You can depend on ADCOLA day after day. That's why they're so popular. You get consistent good service... reliability... from our famous thermally controlled ADCOLA Element and the tough steel construction of this ideal production tool.

\*  
Write for price list and catalogue

# ADCOLA

(Regd Trade Mark)

**ADCOLA PRODUCTS LTD.,**  
(Dept. M), ADCOLA HOUSE, GAUDEN RD., LONDON, S.W.4.  
Telephone: 01-622 0291/3 • Telegrams: Soljoint London Telex • Telex: Adcola London 21851



## for fast, easy, reliable soldering

Contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux required.

### SAVBIT ALLOY ALSO REDUCES COPPER BIT WEAR.

Economically packed for general electrical and electronic soldering. 75ft. 18 gauge on plastic reel. Recommended retail price **75p**



Size 12

### THIN GAUGE SOLDER, ESSENTIAL FOR

soldering small components and thin wires. High tin content, low melting point, 60/40 alloy, 170ft. 22 gauge on plastic reel. Recommended retail price **75p**



Size 10

### A RANGE OF SOLDERS IN HANDY DISPENSERS.

REF.	ALLOY	SWG		
19A	60/40	18	18p*	
Size 5 (ultra-Savbit)		18	18p*	
15	60/40	22	22p*	

\* Recommended Price



### INVALUABLE FOR STRIPPING FLEX, THE NEW AUTOMATIC OPENING BIG WIRE STRIPPER AND CUTTER,

easily adjustable for all standard diameters. Plastic covered handles can also be used as wire cutter. Recommended retail price **50p**



From Electrical and Hardware shops. If unobtainable, write to: **Multicore Solders Ltd., Hemel Hempstead, Herts.**

## AUDIO POWER AMPLIFIERS

TYPE S1-1010A  
MAX CONTINUOUS  
OUTPUT POWER  
10 W.  
SINGLE ENDED  
PUSH-PULL  
CIRCUIT

TYPE S1-1020B  
MAX CONTINUOUS  
OUTPUT POWER  
20 W.  
CAN WITHSTAND  
5 SEC. SHORT  
CIRCUIT

PRICES FROM  
£2.75 to £11 ea.  
ACCORDING TO  
TYPE & QUANTITY

TYPE S1-1020A  
MAX CONTINUOUS  
OUTPUT POWER  
25 W.  
HARMONIC DISTORTION  
LESS THAN  
0.5%

TYPE S1-1050A  
MAX CONTINUOUS  
OUTPUT POWER  
50 W.  
FREQUENCY RANGE  
20 HZ to 100 KHZ

FOR FULL  
INFORMATION  
WRITE TO

# PHOTAIN CONTROLS LTD.

RANDALLS ROAD, LEATHERHEAD. 72776-75517

**Build  
your  
own**



**Peerless**  
**stereo**  
**loudspeakers**

It's very easy. And you only pay for the materials. The result is a world-famous Peerless hi-fi loudspeaker system of superior quality. For particulars about the various loudspeaker kits, please apply to

**Peerless**

**P. F. & A. R. Helme Ltd.**

(Dept P.W.11-P)

Summerbridge

Harrogate HG3 4DR Yorkshire

Telephone: Darley 279 (STD 0423-72)



The great sound happening of the year

# THE 1971 INTERNATIONAL AUDIO FESTIVAL AND FAIR

October 26-30



You must see and hear the most comprehensive demonstration of Hi-Fi ever staged in Europe. Come to Olympia and see the big names of the Sound Industry displaying the latest reproduction equipment. Tape recorders, Cassette Players and Cassettes, Loudspeakers and Earphones, VHF radios, Stereo Multiplier Receivers, Tapes and Discs — you can hear them all in action in 100 specially constructed Audio Studios.

And you can relax in the comfortable Hi-Fi Theatre with daily presentations, lectures and discussions by the industry's top names. Everyone interested in Hi-Fi must come. This is the greatest event in the history of sound techniques.

## OLYMPIA

Tuesday to Saturday 10 - 9 daily LONDON

Admission 30p

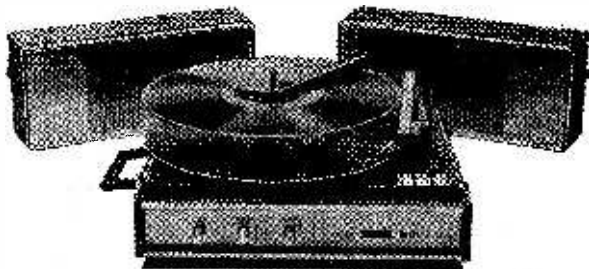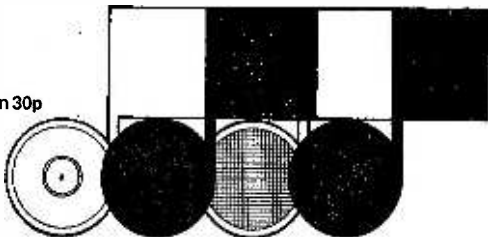

A super stereo for £40.50

## £5 Gift Voucher FREE when you buy the Boots Auto Stereo

This popular Boots Auto Stereo is great value at £40.50 (including transparent cover) but now we're giving away a £5 Gift Voucher with every auto player sold! This voucher can be exchanged at any branch of Boots or Timothy Whites — just think of all the many things you can get there with £5, especially in the gift buying season. And you can be sure that you're

getting a really superb stereo player. The Auto Stereo is specially made for Boots by Philips, and is acclaimed by the press; "What a player!" said the Daily Express; "Hi-Fi connoisseurs were full of admiration" said the Observer. The range of Boots audio equipment is expanding rapidly—stereo headphones, low noise cassettes—but why not come and see for yourself.

This Boots Voucher/Stereo offer is available at all **BOOTS** or **TIMOTHY WHITES** Record and Audio Departments — but hurry the offer ends on November 6th.



## VALVES SAME DAY SERVICE NEW! TESTED! GUARANTEED!

SETS 1R5, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DL92, DL94. Set of 4 for £1.02, DAF96, DF96, DK96, DL96, 4 for £1.48.

1R5	-28 30C1	-28 DY87	-25 EL500	-62 POL82	-32 UABC80	-82
1S5	-22 30C15	-58 DY802	-35 EM80	-41 PCL83	-57 UAF42	-51
1T4	-16 30C17	-79 EABC80	-32 EM81	-41 PCL84	-34 UBC41	-58
3S4	-26 30C18	-61 EAF42	-50 EM84	-32 PCL85	-38 UBF80	-34
3V4	-37 30F5	-69 EB41	-40 EM87	-36 PCL86	-40 UBF89	-82
5U4G	-26 30FL1	-61 EB91	-11 EY61	-38 PCL88	-68 UCC84	-38
5V4G	-35 30FL12	-70 EBC83	-40 EY86	-29 PCL800	-75 UCC85	-85
5Y3GT	-26 30FL14	-68 EBC41	-54 EZ40	-43 PEN44	-77 UCF80	-38
8Z4G	-25 30L1	-29 EBC90	-22 EZ41	-43 PEN36C	-70 UCH42	-58
9J30L2	-54 30L15	-57 EBF80	-32 EZ80	-22 PFL200	-53 UCH81	-38
6AL5	-11 80L17	-71 EBF89	-29 EZ81	-23 PL35	-49 UGL82	-82
6AM6	-13 30P4	-65 ECC81	-17 GZ30	-35 PL81	-44 UGL83	-55
6AQ5	-22 30P12	-72 ECC82	-20 GZ32	-40 PL8A	-49 UF41	-58
6AT6	-30 30P19	-57 ECC83	-35 GZ34	-48 PL82	-81 UFR89	-80
6AU6	-20 30P11	-68 ECC85	-26 KT41	-77 PL83	-33 UL41	-67
6BA	-20 30P113	-75 ECC804	-56 KT61	-55 PL84	-80 UL44	£1.06
6BE6	-21 30P114	-65 ECF80	-27 KT66	-78 PL500	-63 UL84	-80
6BJ6	-41 30P115	-90 ECF82	-26 LN319	-63 PL504	-63 UM84	-92
6BW7	-52 35L6GT	-45 ECH35	-30 LN329	-72 PM84	-35 UY41	-42
6CD6G	£1.07 35W4	-25 ECH42	-61 LN339	-63 PX25	£1.00 UY85	-85
6F14	-42 35Z4GT	-25 ECH81	-29 N78	-87 PY32	-56 VP4B	-77
6E23	-63 807	-45 ECH83	-40 P61	-45 PY33	-55 Z77	-28
6F25	-57 9063	-69 ECH84	-38 PABC80	-34 PY81	-25 Transistors	-17
6K7G	-12 AC/VP2	-77 ECL80	-30 PC86	-47 PY82	-25 AC107	-17
6K8G	-17 B349	-65 ECL82	-31 PC88	-47 PY83	-28 AC127	-18
6Q7G	-27 B729	-62 ECL86	-38 PC96	-47 PY88	-33 AD140	-87
6SNTGT	-80 CCB35	-67 EFP39	-38 PC97	-39 PY800	-34 ADF115	-80
6V6G	-23 CV31	-50 EF41	-60 PC900	-33 PY801	-84 ADF116	-80
6V6GT	-31 DAF91	-22 EFB80	-23 PC854	-29 R19	-36 ADF17	-23
6X4	-23 DAF96	-36 EFB85	-28 PC855	-27 R20	-53 ADF118	-48
6X5GT	-28 DF33	-38 EFB86	-31 PC888	-42 U25	-64 ADF125	-17
7B7	-33 DF91	-16 EFB89	-28 PCC89	-48 U26	-56 ADF127	-17
10113	-58 DF96	-38 EFB91	-18 PCC189	-48 U47	-65 OC26	-85
12A4T7	-17 DH77	-20 EFB98	-65 PCC805	-56 U49	-53 OC44	-12
12A U6	-20 DK32	-23 EFB83	-23 PCC806	-61 U50	-26 OC45	-12
12A U7	-20 DK91	-28 EFB84	-31 PCF82	-31 U52	-31 OCT71	-12
12A X7	-22 DK92	-38 EFB90	-37 PCF86	-45 U78	-24 OCT72	-12
19BG6G	-87 DK96	-38 EL33	-55 PCF800	-58 U191	-59 OCT75	-12
20F2	-67 DL35	-40 EL34	-46 PCF801	-20 U193	-42 OCT81	-12
20P3	-20 DL92	-23 EL41	-54 PCF802	-44 U251	-66 OCT8D	-12
20P4	-22 DL94	-37 EL34	-23 PCF805	-31 U301	-35 OCT89	-12
25L6GT	-20 DL96	-38 EL90	-28 PCF806	-56 U329	-66 OCT8D	-12
25U4GT	-57 DY86	-25 EL95	-38 PCF808	-65 U801	-98 OCT10	-28

## READERS RADIO

85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX. Tel. 01-550 7441.

Postage on 1 valve 5p, on 2 or more valves 3p per valve extra. Any parcel insured against damage in transit 3p extra.






# JUST BEGINNING?

Then try out **8-Watt, 10-Transistor Stereo Amplifier R.137**

**ROC price**  
**£10.50**

Separate tone and volume controls for each channel, inputs for turntable (ceramic cartridge), tuner and tape. Attractive black crackle finish with brushed aluminium front. Frequency response: 70-20,000 Hz  $\pm$  3dB. Output: 4 watts per channel @ 8 ohms. Inputs: Phono 80mV; tuner/aux 80mV.


Normal retail price: **£14.70**

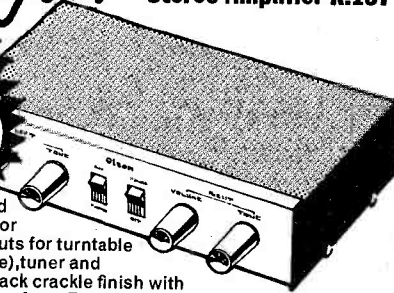

# FIRST STEP TO STEREO!

**5-Watt Transistor Stereo Amplifier Chassis R.123**  
Completely self-contained, fully transistorised, mains-powered (240v AC) amplifier, needing only cabinet and knobs. Ideal for adapting mono players to stereo. Frequency response: 40-17,000 Hz  $\pm$  3dB. Output: 2.5 watts per channel @ 8 ohms. Input: Phono 600mV.

Normal retail price: **£7.30**

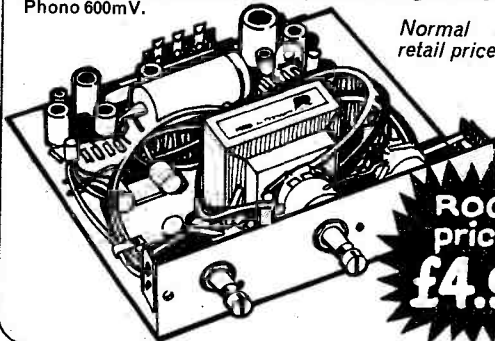


**ROC price**  
**£4.95**

# SOUNDS SENSATIONAL

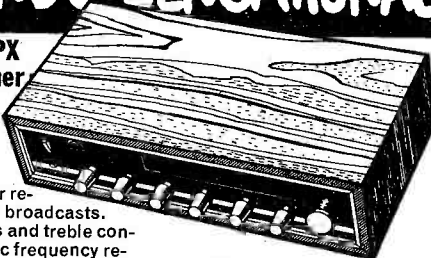**AM/FM/MPX Stereo Tuner Amplifier R.124**

A top quality amplifier with facility for receiving stereo broadcasts. Separate bass and treble controls, automatic frequency response, stereo headphone socket, output power: 8 watts. FM frequency range 88-108 MHz; AM frequency range 535-1605 KHz. Inputs for turntable (ceramic cartridge) and tape. Frequency response: 50-10,000 Hz  $\pm$  3dB. Output: 4 watts per channel @ 8 ohms. Inputs: Phono 200mV, tape 100mV. FM: Sensitivity 20 $\mu$ V, stereo separation 26dB, image rejection 55dB. AM: Sensitivity 300 $\mu$ V.

Normal retail price: **£42.00** **ROC price: £29.95**




# World wide reception

**Professional Solid-state, Four-band Communications Receiver R.135**

Fully transistorised with continuous coverage from 555K Hz to 30 MHz in four bands (with illuminated bandspread for 160-10 metres). Incorporates internal speaker, automatic noise limiter, SSB/AM/CW switch, AVC switch, S Meter, Receive and Standby switch, external socket for headphone or speaker, bandspread control, BFO control, on/off/AF gain, band selector, antenna trimmer and RF gain. Runs off 240 v AC, batteries or any 12 v DC negative ground source. Frequency ranges (in MHz): Band A, 535-1.6; B, 1.55-4.5; C, 4.5-13; D, 13-30. Sensitivity: 0.5 $\mu$ V @ 30MHz. Bandspread: 10-160 metres.

Normal retail price: **£65.00**

**ROC price:**  
**£45.00**

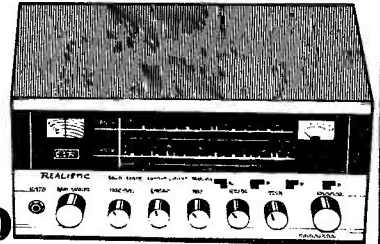


# AMAZING OFFER!

**Stereo Cassette Tape Unit R.142**

Complete stereo record and playback unit with line and microphone inputs. Fitted with tape counter, separate pause control, recording level metres for each channel, pop-up cassette ejection. Supplied complete with two pencil microphones. Wow & flutter better than 0.3%, frequency response 100-10,000 Hz. Tape speed: 1 1/2 IPS, 4.75 CMS. Rewind time: Better than 60 sec (C.60 cassette).  
Normal retail price: **£65.00**

**ROC price**  
**£49.50**

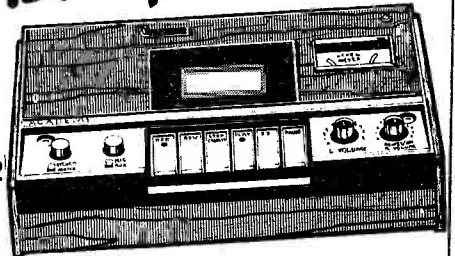


# We don't want you to

Every piece of electronic or audio-equipment we sell is built to our specifications. It comes complete with a Guarantee. And it's tested before it leaves us.

We bend over backwards in our advertising to make sure everything we say is factually accurate. But, buying mail-order, even though you're buying from us, we accept you could still end up with a piece of equipment that's not exactly what you wanted. And we think that's unfair.

# FANTASTIC BARGAIN

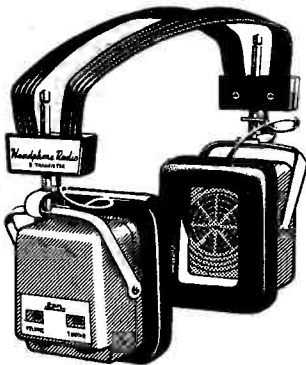

## Headphone Radio R.143


For completely private listening without the distortion of the ordinary earphone adaptor. Battery operated; PP3. Fully transistorised. Frequency range: 535-1600 K Hz, Medium Wave Band. Maximum output: 300mW.

**ROC price**  
**£6.90**

Normal retail price: £9.40

# 2 for the price of one!

## Matched Stereo Speakers R.446

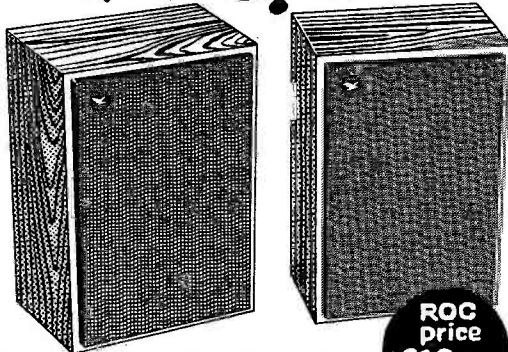

Heavily lagged teak finish cabinets each with large dual cone base unit and separate tweeter. Power handling: 10 watts peak; frequency range: 40-18,000 Hz, impedance: 8 ohms. Size: 14 x 8½ x 6½.

**ROC price**  
**£16.40**

Normal retail price: £19.60

## pay for your mistakes

So we've got a proposition for you. If you buy a piece of Roc equipment, and it's not quite what you expected, send it back within seven days, and as long as it's as good as new we'll give you your money back. O.K?

Return of post mail-order service; orders over £10 post free, (U.K. only) add 25p for p & p to orders under £10. HP terms available.

### ROC ELECTRONICS LIMITED

B. Jory Esq 193A Edgware Rd., London W2 1ET. 01-723 6211.  
Callers at Shop welcome 9-6 Mon to Sat (Thurs 1pm)

# STEREO headphones

only  
**£2.40**




## Stereo Headphones R.328

Light and comfortable, with a frequency response of 30-15,000 Hz for real listening pleasure. Complete with jack plug. Impedance 8-16 ohms.  
Normal retail price: £2.95

# Don't read this!
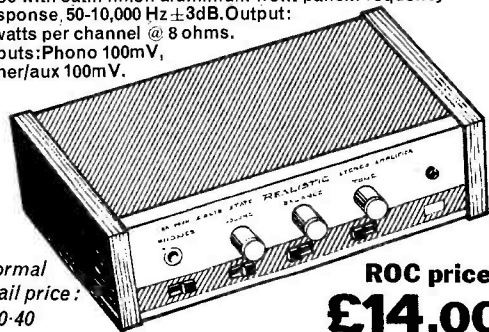
## 10-watt Transistor Stereo Amplifier R.136

Ganged volume, balance and tone controls. Inputs for turntable (ceramic cartridge), tuner (see R.134) or tape. Oiled walnut case with satin finish aluminium front panel. Frequency response, 50-10,000 Hz ±3dB. Output: 5 watts per channel @ 8 ohms. Inputs: Phono 100mV, tuner/aux 100mV.



Normal retail price: £20.40

**ROC price:**  
**£14.00**

# The Perfect match!

## AM/FM/MPX Stereo Tuner R.134



Matching unit to the R.136 amplifier. Covers AM and FM tuning bands with automatic stereo signal light. FM frequency range: 88-108MHz; AM frequency range: 535-1605kHz. FM: Sensitivity 5µV, stereo separation 25dB @ 1kHz, image rejection 50dB. AM: Sensitivity 250µV.

**ROC price**  
**£22**

Normal retail price: £28.60

# FAMOUS TELETON-AM/FM

## Stereo Tuner Amplifier R8000

Supplied complete with 2 speakers. Total 12 watts RMS. Specification MPX Beacon, AFC Connections for Tape Recorder, Stereo Headphone Socket, etc. Mfgs. Rec. Price £63.50  
P.S.P. FANTASTIC OFFER **only £39.95**



Plus GARRARD DECK 2025. Fitted in Famous 'Thorpe Grenville' Plinth & Cover with patented moulded motor board. Fitted with superb Sonotone 9TAHCO cartridge. P.S.P. offer

**ONLY IF YOU BUY THE ABOVE only £15.40**



SAVE ££s

ANOTHER PSP SUPER SCOOP

All orders C.W.O. Special Securicor fast delivery £3.

### SUPERB 'THORPE-GRENVILLE' PLINTHS

with Tinted Perspex Covers incorporating the Patented Moulded Motor Board. Our Price £4.50 p.p 35p.

### Suggested System.

SAQ 206 Amplifier, SP25 III Plinth and Cover, G800 cartridge, pair large 3-way speaker system. Also available with EM1 13 x 8 speaker system £63.95. Would normally cost £85 complete. Our price £59.95.

### TELETON SAQ 206 STEREO AMPLIFIER

Latest release, beautifully styled in walnut case, 6+6 watts r.m.s. Switched inputs for magnetic Xtal, aux. Tape. Incorporates volume, bass, treble and, slide balance control, scratch filter and loudness control. Rec. £32.50. Our price £19.95.

Also available standard perspex cover, £3.25 p.p 35p.

Also available complete ready wired using above Plinths GARRARD 2025 with Sonotone 9TAHC-Diamond, £15.40 p.p 35p.

GARRARD SP25111 with G800 fitted in above superb Plinths. £20.95 p.p 35p.

**Also a very special bargain only available to customers buying the R8000 and Garrard Deck. TELETON SUPER HI-FI STEREO HEADPHONES RETAILING AT £5.00 — ONLY £1.95**

### PERSONAL SHOPPERS PLAN LTD.

The Centre  
36-38 West Green Road, Tottenham, N.15  
Tel. No. 01-800 5533

## The BATTERIES That Won't Let You Down! RECHARGEABLE

Cells in U2, U11 and Penlite U7 sizes  
Kestral Battery Charging Unit



### Uses:

Tape recorders, Portable radio and TV, Radio controlled model aircraft and boats, Cine cameras, Flashguns, Cordless shavers and other battery appliances.

Whenever you *must* have utterly dependable battery power—then these new Alkaline-Manganese rechargeable cells will provide it. The cells can be recharged many times, a simple job with the Kestral Charging Unit which has been specially designed for these new type batteries.

### PRICES

Batteries U2 equiv. £1.25

Penlite U7 equiv. 50p

U11 equiv. £1.03

Charging unit £3.99 with one battery holder

**KESTREL**

Bush & Meissner

Send to:  
275 WEST END LANE  
LONDON, N.W.6  
01-794 9611

## 4-STATION INTERCOM



£7.25

4-Station Transistor Intercom system (1 master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. and other accessories. P. & P. £0.40.

### MAINS INTERCOM

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On off switch and volume control. Price £14.40 P. & P. £0.40

## INTERCOM/BABY ALARM



OUR PRICE ONLY £3.35

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 66ft. connecting wire. Battery 14p. P. & P. £0.25.

### Transistor TELEPHONE AMPLIFIER



£2.99

Why not boost business efficiency with this incredible De-luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume Control. Battery 14p. extra. P. & P. 22p. Full price refunded if not satisfied in 7 days.

WEST LONDON DIRECT SUPPLIES (P.W.8)  
169 KENSINGTON HIGH STREET, LONDON, W.8.

## U.H.F. T.V. AERIALS

SUITABLE FOR COLOUR AND MONOCHROME RECEPTION



All U.H.F. aerials now fitted with tilting bracket and 4 element reflector.  
LOFT MOUNTING ARRAYS  
7 element 2-25. 11 element 2-75. 14 element 3-25. 18 element 3-75.  
WALL MOUNTING c/w WALL ARM & BRACKET  
7 element 3-25. 11 element 3-75. 14 element 4-25. 18 element 4-75. CHIMNEY MOUNTING ARRAYS c/w MAST & LASHING KIT. 7 element 4-00. 11 element 4-50. 14 element 4-75. 18 element 5-25. MAST MOUNTING arrays only. 7 element 2-25. 11 element 2-75. 14 element 3-25. 18 element 3-75. Complete assembly instructions with every aerial. LOW LOSS coaxial cable 9np yd. KING TELEBOOSTERS from 3-75. LABGEAR all band V.H.F.—U.H.F.—F.M. radio mains operated pre-amps 7-50. State clearly channel number required on all orders. P.p. on all aerials 50np. Accs. 15np C.W.O. Min. C.O.D. charge 25np.

BBC—ITV—FM AERIALS  
BBC (band 1) wall S/D 2-00. LOFT inverted 'T' 1-25. EXTERNAL 'H' array only 3-00. ITV (band 3) 5 element loft array 2-50. 7 element 3-00. COMBINED BBC—ITV, loft 1+5 2-75. 1+7 3-50. WALL & CHIMNEY UNITS ALSO AVAILABLE. Pre-amps from 3-75. COMBINED U.H.F.—V.H.F. aerials 1+5+9 4-00. 1+5+14 4-50. 1+7+14 5-00. F.M. RADIO loft S/D 1-00 3 element 3-25. 4 element 3-50. Standard coaxial plugs 9np. Coaxial cable 5np yd. Outlet box 30np. P.p. all aerials 50np. Accs. 30np. C.W.O. Min. C.O.D. charge 25np. Send 5np for fully illustrated lists.

CALLERS WELCOMED  
OPEN ALL DAY SATURDAY

## K.V.A. ELECTRONICS

40-41 MONARCH PARADE, LONDON ROAD, MITCHAM, SURREY  
Telephone 01-648 4884



# BI-PRE-PAK LIMITED

## FULLY TESTED AND MARKED

AC107	4p	OC170	4p
AC126	0-15	OC171	0-23
AC127	0-13	OC200	0-25
AC128	0-17	OC201	0-25
AC176	0-25	2G301	0-13
ACV17	0-15	2G303	0-13
AF239	0-37	2N711	0-50
AF186	0-50	2N1302-3	0-20
AF139	0-37	2N1304-5	0-25
BC154	0-25	2N1306-7	0-30
BC171 = BC107	0-13	2N1308-9	0-35
BC172 = BC108	0-13	2N3819FET	0-45
BF194	0-15		
BF274	0-15	<b>Power Transistors</b>	
BFY50	0-20	OC20	0-50
BSY25	0-57	OC23	0-30
BSY26	0-13	OC25	0-25
BSY27	0-13	OC26	0-25
BSY28	0-13	OC28	0-30
BSY29	0-13	OC35	0-25
BSY95A	0-15	OC36	0-37
OC41	0-13	AD149	0-30
OC44	0-13	AUY10	1-25
OC45	0-13	2S034	0-25
OC71	0-13	2N3055	0-63
OC72	0-13		
OC73	0-17	<b>Diodes</b>	
OC81	0-13	AAV42	0-10
OC81D	0-13	OA95	0-19
OC83	0-20	OA79	0-09
OC139	0-13	OA81	0-09
OC140	0-17	IN9114	0-07

# FREE!

PACKS OF YOUR OWN CHOICE UP TO THE VALUE OF 50p WITH ORDERS OVER £4

## CLEARANCE LINES

### COLOUR T.V. LINE OUTPUT TRANSFORMERS

Designed to give 25kV when used with PL509 and PY500 valves. As removed from colour receivers at the factory.

**NOW ONLY 50p each**  
post and packing 23p.

1 Amp Plastic Rectifiers. These are voltage, reverse Polarity and other rejects from the BY127 range. Ideal for low voltage Power Units etc. Price £1 per 100.

	Quantity	1-10	10-50	50+
BB105 Varicap Diodes		10p	8p	6p
OC71 or 72 Fully Tested				
Unmarked		5p	5p	4p
Matched Sets 1-OC44 and 2-OC45's. Per Set.		25p	20p	15p
Matched Sets of OC45's 1st and 2nd IF		15p	12p	10p
OA47 Gold-Bonded Diodes, Marked and Tested		3p	3p	2p
1-watt Zener Diodes 7-5, 24, 27, 30, 36, 43 Volts		5p	4p	3p
10-watt Zener Diodes 5-1, 8-2, 11, 13, 16, 24, 30, 100 Volts		20p	17p	15p
Micro Switches, S/P; C/O		25p	20p	15p
1-amp Bridge Rec's, 25-volt		25p	22p	20p

### INTEGRATED CIRCUITS

SL403D Audio Amp, 3-Watts	2-00	1-95	1-80
709C Linear Op. Amp.	50p	40p	35p
Gates, Factory Marked and Tested by A.E.I.	25p	22p	20p
J. K. Flip-Flops Factory, Marked and Tested by A.E.I.	40p	35p	30p
PA234 1-watt Audio Amp.	1-00	90p	80p
UL914 Dual 2 I/P Gate	40p	35p	30p

### BUMPER BUNDLES

These parcels contain all types of surplus electronic components, printed panels, switches, potentiometers, transistors and diodes, etc.  
**2 LBS IN WEIGHT FOR £1**  
Post and packing 25p.

## NEW TESTED AND GUARANTEED PAKS

B2	4	Photo Cells, Sun Batteries. 0-3 to 0-5V, 0-5 to 2mA.	50p
B79	4	IN4007 Sil. Rec. diodes, 1,000 PIV lamp plastic	50p
B81	10	Reed Switches, mixed types large and small	50p
B99	200	Mixed Capacitors. Postage 13p Approx. quantity, counted by weight	50p
H4	250	Mixed Resistors. Postage 10p. Approx. quantity counted by weight	50p
H7	40	Wirewound Resistors. Mixed types and values. Postage 8p.	50p
H8	4	BY127 Sil. Recs. 1000 PIV. 1 amp. plastic	50p
H9	2	OC71 Light Sensitive Photo Transistor	50p
H12	50	NKT155/259 Germ. diodes, brand new stock clearance	50p
H18	10	OC71/75 uncoded black glass type PNP Germ.	50p
H19	10	OC81/81D uncoded white glass type PNP Germ.	50p
H28	20	OC200/1/2/3 PNP Silicon uncoded TO-5 can	50p
H29	20	OA47 gold bonded diodes coded MCS2	50p

## F.E.T. PRICE BREAKTHROUGH!!

This field effect transistor is the 2N3823 in a plastic encapsulation, coded as 3B23E. It is also an excellent replacement for the 2N3819.

Data sheet supplied with device.

1-10 30p each, 10-50 25p each, 50+ 20p each.

Make a Rev. Counter for your Car. The "TACHO BLOCK". This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car. **£1 each**

## OUR VERY POPULAR 3p TRANSISTORS

FULLY TESTED & GUARANTEED

TYPE "A" PNP Silicon alloy, metal TO-5 can. 2S300 type, direct replacement for the OC200/203 range.  
TYPE "B" PNP Silicon, plastic encapsulation, low voltage but good gain, these are of the 2N3702/3 and 2N4059/62 range.  
TYPE "E" PNP Germanium AF or RF—please state on order. Fully marked and tested.  
TYPE "F" NPN Silicon plastic encapsulation, low noise amplifier of the 2N3708, 9, 10, 11.

## BULK BUYING CORNER

NPN/PNP Silicon Planar Transistors TO-18 mixed untested similar to 2N706-6A-8, BSY26-7A9-95A and BCY70 etc. £4-25 per 500. £8 per 1000.

NPN Silicon Planar transistors plastic encapsulation untested similar to 2N3707 to 3711. £4-25 per 500. £8 per 1000.

Silicon planar diodes do-7 glass similar to OA200-202, BA731-36. £4-50 per 1000.

NPN/PNP Silicon planar transistors plastic TO-18 similar to BC113-4, BC153-4, BF153-160, etc. £4-25 per 500. £8 per 1000.

NPN Silicon planar transistors TO-5 can similar to BC142/3, BFY50-2-3. £5-25 per 500, £10 per 1000.

OC44, OC45 transistors fully marked and tested 500 to 999, 8p each, 1000+ 6p each.

OC71 transistors fully marked and tested, 500 to 999, 6 each, 1000+ 5p each.

A amp miniature plastic diodes IN4001 at 500 to 999, 4p each, 1000+ 3p each.  
IN4004 at 500 to 999, 5p each, 1000+ 4p each.  
IN4006 at 500 to 999, 6p each, 1000+ 5p each.  
IN4007 at 500 to 999, 8p each, 1000+ 7p each.

## NEW UNMARKED UNTESTED PAKS

B66	150	Germanium Diodes Min. glass type	50p
B83	200	Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ.	50p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	50p
B86	50	Sil. Diodes sub. min. IN914 and IN916 types	50p
B88	50	Sil. Trans. NPN, PNP equiv. to OC200/1, 2N706A, BSY95A, etc.	50p
B60	10	7 Watt Zener Diodes Mixed Voltages	50p
H6	40	250mW. Zener Diodes DO-7 Min. Glass Type	50p
H10	25	Mixed volts, 1 1/2 watt Zeners. Top hat type	50p
H11	30	MAT Series "alloy" pnp Transistors	50p
H15	30	Top Hat Silicon Rectifiers, 750mA. Mixed volts	50p
H16	8	Experimenters' Pak of Integrated Circuits. Data supplied	50p
H20	20	BY126/7 Type Silicon Rectifiers, 1 amp plastic. Mixed volts.	50p

## FREE CATALOGUE AND LISTS for:—

**TRANSISTORS, RECTIFIERS, DIODES, INTEGRATED CIRCUITS FULL PRE-PAK LISTS & SUBSTITUTION CHART**

MINIMUM ORDER 50p CASH WITH ORDER PLEASE. Add 10p post and packing per order. OVERSEAS ADD EXTRA FOR AIRMAIL.

## 8 RELAYS FOR £1

Various Contacts and Coil Resistances. No individual selection. Post & Packing 25p

**FREE! A WRITTEN GUARANTEE WITH ALL OUR SEMICONDUCTORS**

# BI-PRE-PAK LTD

DEPT. D, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX  
TELEPHONE: SOUTHEND (0702) 46344

**CASH & CARRY GOODS**




**SINCLAIR Project 60**  
 SAVE nearly £7 Normal price £23.90

Designed for building into  
 pinths etc., complete with **£17** plus  
 two Z30 Output stages **50p**  
 (20 watt) and power supply unit. **carr.**  
 Send S.A.E. for full technical brochure.

Sinclair 2000 £24  
 Sinclair 3000 £33  
 Metrosound ST20 £27  
 Teleton 203  
 (Demonstration) £17  
 Teleton F2000  
 Tuner/Amp. £31  
 Alpha F212 £26

Please add 50p carr. per  
 amplifier. Other Ampli-  
 fiers — Tuners — Tape  
 Recorders etc. Prices on  
 application.

**This MONTH'S Best Buy . . .**



**AKG K50 Dynamic Stereo headphones**  
 Complete with spare ear muffs.

Total (value £10.40) Our Price **£5.90** + 23p p. & p.

Available only from us at this price. Due to entire purchase of manufacturer's remaining stock this fantastic offer is open only while stocks last.

\* High-fidelity reproduction due to broad frequency response (20-20,000Hz)  
 \* Substantially increased stereo effect \* Headphones fit the head gently and do not shift \* Earpieces fit ears snugly (Cardanic suspension) \* Tone quality superior to conventional loudspeakers. \* Only expensive studio loudspeakers can match the reproduction quality of the K50. \* Music can be reproduced at concert hall volume (l), preserving the lower bass notes and brilliant treble tones without causing any strain to the listener.



**GARRARD SP25**  
 mk III **£12.50** Plus 50p carriage  
 Normal price £15.57

Wired with mains cable and 5ft. twin screened stereo cable, 5 pin din plug. 53p extra.  
 AP75 Complete with base and cover £25 plus 75p carriage.

PLINTH AND COVER SUITABLE FOR GARRARD RANGE £5.25 plus 50p p. & p.

**PLUGS**



Pack 107 5-Pin Din .. 20p  
 Pack 108 3-Pin Din .. 18p  
 Pack 135 1/2" Jack .. 25p  
 Pack 130 1/2" Jack Stereo .. 48p  
 Pack 103 Loudspeaker Plug .. 15p  
 Pack 100 Phono Plug .. 6p  
 Pack 230 3-Pin Socket .. 23p  
 Pack 236 5-Pin Socket .. 30p  
 Pack 234 Loudspeaker Socket.. 30p

**Ready-made Leads**  
 3-pin to 3-pin Din .. 63p  
 3-pin to open end .. 53p  
 5-pin to 5-pin Din .. 80p  
 5-pin to open end .. 65p  
 5-pin to 4 phono plugs .. 93p  
 Speaker lead Din to spade 12ft 38p  
 Extension lead Din plug to socket 12ft 65p

All leads approx. 6ft. in length. Post free, by return.

**Replacement Stereo DIAMOND STYL**

8TA 9TA 9TAHC  
 GP91 ST4 ST9 **75p** each  
 EV28 GC8 +13p p. & p.

**Countdown SPEAKER**  
 Teak Cabinet

**£12** plus 38p carr. & ins.

A speaker of outstanding specifications and technical merit. Solid teak cabinet size: 14" x 10" x 6". Originally designed for use with our Countdown stereo budget system but now available separately.



**EMI 20w matched loudspeaker set 350**

Frequency range: **£7.50**  
 20 to 20,000Hz.  
 Normal price £13 plus 40p p & p

**EMI 10w matched loudspeaker set 450**  
 Our price **£3.75** plus 25p. p. & p.

13 1/2" x 8 1/2" elliptical loudspeaker and independent high frequency units with associated crossover network. Frequency range 55 to 13000Hz. The cone of the bass unit has a surround designed for high travel giving freedom from distortion when operated at low frequencies.

EMI 14A/770C **£14.50** plus 50p p & p  
 Base Speaker



**Magnetic cartridges**

Diamond **£4.00**  
 styl plus 13p p. & p.

Today's value £6.  
 Stylus replacement can be carried out without removing cartridge. Styl £2.13 + 13p p. & p.

Ronette 105 Stereo cartridge (Sapphire 78 Diamond L.P) £1.25 + 13p. p. & p.



**SONOTONE Cartridge ..**  
 (Fitted Diamond Styl)  
 (Ceramic) list price £4.10

Sensitivity: **£2.50**  
 9TAHC 55mV/cm/sec plus  
 rms minimum at 45° at 1,000Hz measured on 13p p. & p.  
 Decca SXL2067



# AT HOME SOLDERING ?

Our miniature irons are used all over the world in that most exacting market—the modern electronics industry, the rapidly developing technology of which has made possible the enormous growth of activities available to the technical hobbyist.

He now also requires equipment to the highest commercial standards. Like our soldering irons, for example.

Look at the ADAMIN Model 15. If there is a smaller iron for mains use, we haven't seen it. It weighs a mere 1/2 oz (less flex) and is about 7 inches long.

But it has a big performance. Used with interchangeable bits from 3/32" to 1/16" it is suitable for all work, from Hearing Aids to Colour Television.

Use the mains version at home or clip the 12 volt model to the car battery or 12 volt power unit (consumption only 1.25A).

Send for HOBBY PACK 10 consisting of Model 15 iron with four bits, 3/32", 3/16", 1/8", 1/16" and tube of Bit Lubricant. State voltage required—12v or 220/240v.

**PRICE: HOBBY PACK £2.30**  
 p & p FREE

**LIGHT SOLDERING DEVELOPMENTS LTD.**

28 Sydenham Road, Croydon, CR9 2LL  
 Telephone 01-688 8589 and 4559



**J. J. FRANCIS**  
 (WOOD GREEN) LTD  
 123 ALEXANDRA ROAD, HORNSEY,  
 LONDON, N.8. Tel: 01-888 1662

# Build yourself a TRANSISTOR RADIO

## NEW! ROAMER 10 WITH VHF INCLUDING AIRCRAFT

**10 TRANSISTORS. 9 TUNABLE WAVEBANDS, MW1, MW2, LW, SW1, SW2, SW3, TRAWLER, BAND, VHF AND AIRCRAFT BAND**


Built in Ferrite Rod Aerial for MW/LW. Retractable, chrome plated 7 section Telescopic Aerial, can be angled and rotated for peak short wave and VHF listening. Push Pull output using 600mw Transistors. Car Aerial and Tape Record Sockets. Switched Earpiece Socket complete with Earpiece. 10 Transistors plus 3 Diodes. 7in x 4in Speaker. Air Spaced ganged Tuning Condenser with VHF section. Volume on/off, Wave Change and Tone Control. Attractive Case in black with silver blocking. Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and easy build plans 30p (FREE with parts).

Total building cost

**£8.50**

P. P. & Ins. 50p

(Overseas P. & P. £1)

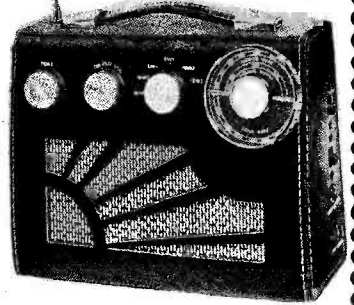

## ROAMER EIGHT Mk I

**NOW WITH SWITCHED TONE CONTROL**

7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Retractable chrome plated Telescopic aerial for Short Waves. Push pull output using 600mw Transistors. Car aerial and Tape record sockets. Selectivity switch. Switched earpiece socket complete with earpiece. 8 transistors plus 3 diodes. 7in. x 4in. Speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts Price List and Easy Build Plans 25p (FREE with parts).

Total building cost **£6.98** P. P. & (Overseas P. & P. £1) Ins. 41p.



## ROAMER SEVEN MK IV

7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Extra Medium waveband provides easier tuning of Radio Luxembourg, etc. Built in ferrite rod aerial for MW and LW. Retractable 4 section 24in. chrome plated telescopic aerial for SW. Socket for Car Aerial. Powerful push-pull output. 7 transistors and 2 diodes, including Micro-Alloy B.F. Transistors. 7 x 4in. P.M. speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning and wave change controls. Attractive case with carrying handle. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts price list and easy build plans 10p (FREE with parts). Earpiece with plug and switched socket for private listening, 30p extra.


Total building costs **£5.98** P. P. & (Overseas P. & P. £1) Ins. 41p.


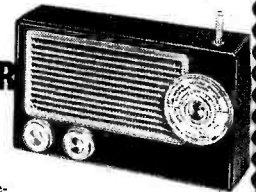
## ROAMER SIX

6 Tunable Wavebands: MW, LW, SW1, SW2, Trawler band plus an extra M.W. band for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. 5in. Speaker. 8 stages—6 transistors and 2 diodes including Micro-Alloy B.F. Transistors, etc. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2in. approx. Easy build plans and parts price list 15p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building costs **£3.98** P. P. & (Overseas P. & P. £1) Ins. 23p



## POCKET FIVE

3 Tunable Wavebands: MW, LW, Trawler Band with extended M.W. band for easier tuning of Luxembourg, etc. 7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker. Attractive black and gold case. Size 5 1/2 x 1 1/2 x 3 1/2in. Easy build plans and parts price list 10p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building costs **£2.23** P. P. & (Overseas P. & P. 63p) Ins. 21p



## TRANSONA FIVE

**NOW WITH 3in SPEAKER**

3 Tunable Wavebands: MW, LW and Trawler Band. 7 stage—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser volume control, fine tone 3in. moving coil speaker. Attractive case with red speaker grille. Size 6 1/2 x 4 1/2 x 1 1/2in. Easy build plans and parts price list 10p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.


Total building costs **£2.50** P. P. & (Overseas P. & P. 63p) Ins. 22p


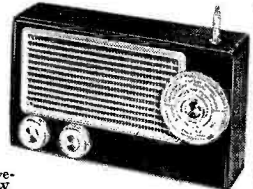
## TRANS EIGHT

6 Tunable Wavebands: MW, LW, SW1, SW2, SW3 and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 3in. Speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2in. approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 25p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building costs **£4.48** P. P. & (Overseas P. & P. £1) Ins. 31p




## NEW! "EDU-KIT"

**BUILD RADIOS, AMPLIFIERS, ETC. FROM EASY STAGE DIAGRAM. FIVE UNITS INCLUDING MASTER UNIT TO CONSTRUCT.**

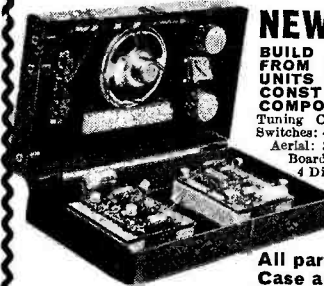**COMPONENTS INCLUDE:**

Tuning Condenser: 2 Volume Controls: 2 Slider Switches: 4x2 1/2" Speaker: Terminal Strip: Ferrite Rod Aerial: 3 Plugs and Sockets: Battery Clips: 4 Tag Boards: Balanced Armature Unit: 10 Transistors: 4 Diodes: Resistors: Capacitors: Three 1" Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction.

All parts including Case and Plans **£5.50** P. P. & (Overseas P. & P. £1) Ins. 31p



**FULL AFTER SALES SERVICE**

\* Callers side entrance Barratts Shoe Shop  
\* Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

## RADIO EXCHANGE CO

61 HIGH STREET, BEDFORD. Tel. 0234 52367

I enclose £..... please send items marked

ROAMER TEN <input type="checkbox"/>	ROAMER SEVEN <input type="checkbox"/>
ROAMER EIGHT <input type="checkbox"/>	TRANS EIGHT <input type="checkbox"/>
TRANSONA FIVE <input type="checkbox"/>	ROAMER SIX <input type="checkbox"/>
POCKET FIVE <input type="checkbox"/>	EDU-KIT <input type="checkbox"/>

Parts price list and plans for .....

Name .....

Address .....

PW.35

# Introducing R.S.C. MkIII SUPER 30 HI-FI STEREO AMPLIFIER

A COMPLETELY NEW DESIGN FURTHER IMPROVED IN BOTH APPEARANCE and PERFORMANCE. REPRESENTING VALUE FAR HIGHER THAN THE PRICES SUGGEST.

Only high grade components by leading manufacturers.

**£25** Carr. 65p



- ★ SATIN SILVER METAL FACIA with black lettering. Black edged knobs with bright silver centres.
- ★ PUSH-BUTTON SELECTOR SWITCHING
- ★ NEON INDICATOR
- ★ JACK SOCKET FOR HEADPHONES
- ★ CABINETED MODEL VENEERED IN SATIN TEAK. SUITABLE FOR ANY MODERN PICK-UP CARTRIDGE CERAMIC or MAGNETIC, REGARDLESS OF PRICE.
- ★ WE RECOMMEND USE WITH THE BEST ANCILLARY EQUIPMENT THAT CAN BE AFFORDED.

Or FACTORY BUILT with 12 months guarantee Dep. £3-75 and 9 monthly payments £3-50 (Total £37-25) **£33-75**  
Or FACTORY BUILT in cabinet as illustrated Dep. £6 and 9 monthly payments £3-86 (Total £40-74) **£36-75**

PRINTED CIRCUITRY. TWENTY SILICON TRANSISTORS. FOUR DIODES. FOUR RECTIFIERS.

TECHNICAL DETAILS (Applying to each channel where appropriate)  
CONTROLS: PUSH-BUTTON SELECTOR (1) Disc (2) Radio (3) Tape (4) Mono L (5) Mono R (6) SPEAKER DIS. (7) Mains on/off. Bass, Treble, and Balance. Plus Ceramic Mag P.U. Switch.

OUTPUT: 15 watts R.M.S. (Continuous) into 8 ohms. 10 watts R.M.S. (Continuous) into 15 ohms.  
HUM & NOISE - 75dB Min. Vol. - 65dB Full Vol. HARMONIC DISTORTION  
FREQUENCY RESPONSE: -3dB 7Hz to 70KHz 0-1% at 1000 Hz 10 Watts  
TREBLE CONTROL: +16dB to -12dB at 14KHz  
BASS CONTROL: +17dB to -16dB at 40Hz  
CROSS TALK - 58dB  
SENSITIVITIES: Disc Mag. 2-5mV. Ceramic 35mV. Radio 120mV. Tape 120mV.  
REAR PANEL SOCKETS ARE FOR 3 PAIRS OF INPUTS (1) P.U. (2) Radio. (3) Tape Amp. Plus pair for tape recorder signal take off and 2 pairs for speaker connections.

## R.S.C. HIGH FIDELITY STEREO 'PACKAGE' OFFERS

- ★ Four fully wired units ready to 'plug in.'
- ★ SUPER 30 AMPLIFIER (15 + 15 watt) in veneered housing
- ★ GARRARD SP25 MKIII Turntable on Plinth with cover
- ★ GOLDRING CS90 Ceramic Pick-up Cartridge with diamond stylus
- ★ PAIR OF STANWAY II Speaker Units

**£79-80**

Special Total Price Carr. £1-50

Terms: Deposit £12 and 9 monthly payments £8-55 (Total £88-95).

- ★ Super 30 Amplifier (15 + 15 watt) in veneered housing
- ★ Goldring GL69 II Transcription Turntable on Plinth as illustrated
- ★ Goldring Magnetic P.U. Cartridge.
- ★ Pair of Stanway II speaker units

Matching as recommended for optimum performance. Send S.A.E. for coloured brochure showing other money-saving offers.

Package prices apply providing all individual units are purchased from any branch within 3 months. See leaflet.



Stanway II

Special Total Price Carr. £1-50  
**£96-75**  
Terms: Deposit £14 and 9 monthly payments. £10-53 (Total £113-55)

ATTRACTIVE TEAK or AFORMOSIA VENEERED CABINETS and PLINTHS

- ★ TA12 AMPLIFIER 6-5+6-5 watt in veneered housing
- ★ GARRARD SP25 MK III Player unit on Plinth
- ★ GOLDRING CS90 Ceramic P.U. Cartridge with diamond stylus
- ★ PAIR OF DORCHESTER Loudspeaker Units

**£58**

Special Total Price Carr. £1-25  
Or Deposit £7-15 and 9 monthly payments £6-35 (Total £64-30). Trans. Plastic cover £3-15 extra.

Package as above but with Garrard 3000 Auto-changer and Sonotone 97A Ceramic Cartridge in lieu of SP25 £51-75 Carr. £1-25  
Or Deposit £6 and 9 monthly payments £5-70 (Total £57-30) Trans. Plastic cover £3-15 extra.

### 'YORK' HIGH-FIDELITY 3 SPEAKER SYSTEM

- ★ Moderate size only 25 x 14 x 10in. COMPLETE KIT **£22**
- ★ Response 30-20,000 c.p.s. Carr. 63p
- ★ Impedance 15 ohms
- ★ Performance comparable with units costing considerably more. Consists of (1) 12in. 15 watt Bass unit with cast chassis. Roll rubber cone surround for ultra low resonance, and ceramic magnet. (2) 3-way quarter section series cross-over system (3) 8 x 5in. high flux middle range speaker. (4) High efficiency tweeter. (5) Appropriate quantity acoustic damping material. (6) Handsome Teak veneered cabinet. (7) Circuit and full instructions. Terms: Dep. £4-50 and 9 monthly payments £2-25 (Total £24-75).

DEMONSTRATIONS AT ALL BRANCHES

### HIGH FIDELITY LOUDSPEAKER UNITS

Cabinets latest style Satin Teak veneer. Acoustically lined or filled acoustic damping. Ported where appropriate. Credit terms available.  
DORCHESTER (Illustrated) Size 16 x 11 x 9in. approx. Range 45-15,000 c.p.s. Rating 8-10 watts. Fitted High flux 13 x 8in. **£9-45** Carr. 40p.  
DUAL CONE speaker. Imp. 3 or 15 ohms.  
STANWAY II Size 20 x 10 1/2 x 9 1/4in. approx. Rating 10 watts. Inc. 13 x 8in. speaker with highly flexible cone surround, long throw voice coil and 10,000 line magnet. High flux tweeter. Handsome Scandinavian design cabinet. Range 35-20,000 c.p.s. Imp. 15 ohms. Gives **£17-85** smooth realistic sound output. See 'package offers' for illustration

### RSC G66 MkII 6+6 WATT high quality STEREO AMPLIFIER

Individual Ganged Controls: Bass, Treble, Volume and Balance. Printed circuit construction employing 10 Transistors plus Diodes. Output rating I.H.F.M. Frequency range 20-20,000 c.p.s. Bass Control ±12db. Treble Control ±13db. Selector switch for P.U. or Tape/Radio. For loudspeaker output impedances of 3 to 16 ohms. For standard 200-250v A.C. mains operation. Attractive Black and Silver finished metal facia plate and matching control knobs.



COMPLETE KIT OF PARTS INCLUDING FULLY WIRED PRINTED CIRCUIT and comprehensive wiring diagram and instructions **£10-50** Carr. 40p

Or FACTORY BUILT IN TEAK VENEERED CABINET as illustrated £13-99 or dep. £8 and 9 monthly payments £1-50 (Total £18-50).

### R.S.C. TA12 MKIII 6-5 + 6-5 WATT STEREO AMPLIFIER

FULLY TRANSISTORISED, SOLID STATE CONSTRUCTION HIGH FIDELITY OUTPUT OF 6.5 WATTS PER CHANNEL  
Designed for optimum performance with any crystal or ceramic Gram. P.U. cartridge, Radio tuner, Tape recorder etc. ★ 3 separate switched input sockets on each channel ★ Separate Bass and Treble controls ★ Slide Switch for mono use ★ Speaker Output 3-16 ohms ★ For 200-250v. A.C. mains ★ Frequency Response 20-20,000 c.p.s. -2dB ★ Harmonic Distortion 0.3% at 1,000 c.p.s. Hum and Noise - 70dB ★ Sensitivities (1) 50mV (2) 400mV (3) 100mV. Output rating I.H.F.M. ★ Handsome finish Facia plate & knobs. COMPLETE KIT OF PARTS WITH FULL WIRING DIAGRAMS & INSTRUCTIONS. **£15-50** Carr. 40p. guarantee **£19-50** or Deposit £2 and 9 mthly pymts £2-15 (Total £22-85) Or in Teak veneer housing **£23** Dep. £2 & 9 mthly payments £2-55 (Total £25-95). Send S.A.E. for leaflet



### R.S.C. PLINTHS

Superior Solid Natural Wood Construction for Record Playing units, cut for Garrard 1025, 2020, 3000, AT80, SP25 etc. **£3-15**  
WITH TRANSPARENT PLASTIC COVER **£6-30**



### SPECIAL HI-FI OFFERS

WHARFEDALE/F.A.L. 1 pr Wharfedale Super Linton Speakers, 1 F.A.L. Phase 32 15 + 15 watt Stereo Amplifier Total Rec. Retail Price £87-70 **£66-50**  
PACKAGE PRICE Above brand new goods. Following have been unpacked for display purposes only - LEAK MINI-SANDWICH **£18** (Teak finish)

ROGERS RAVENSBROOK STEREO AMPLIFIER **£39**  
TANDBERG 62X TAPE RECORDER **£88**  
(Stereo) GOODMAN'S AUDIOM 91 **£19-95**

WHARFEDALE SUPER LINTONS £36.75 PAIR Carr. Free

### LOW DEPOSIT CREDIT TERMS

AVAILABLE ON PURCHASES OVER £8 (KITS OF PARTS EXCEPTED) INTEREST CHARGES REFUNDED ON CREDIT SALES SETTLED IN 3 MONTHS

- BRADFORD 10 North Parade. (Half-day Wed.) Tel. 25349
- BLACKPOOL (Agent) O. & C. Electronics, 227 Church Street
- BIRMINGHAM 30/31 Gt. Western Arcade (Half-day Wed.) 021-236-1279
- DERBY 26 Osmaston Rd., The Spot (Half-day Wed.) Tel. 41361
- DARLINGTON 18 Priestgate (Half-day Wed.) Tel. 68043
- EDINBURGH 133 Leith St. (Half-day Wed.) Tel. 556 5766
- GLASGOW 326 Argyle St. (Half-day Tues.) Tel. CITY 4158
- HULL 91 Paragon Street (Half-day Thursday) Tel. 20505



MAIL ORDERS TO: Audio House, Henconner Lane, Leeds 13.  
TERMS C.W.O. or C.O.D. No C.O.D. under £1. Postage 25p extra under £2. 30p extra over £2 or as quoted. Trade supplied. S.A.E. please with enquiries  
Branches open all day Sats. MAIL ORDERS MUST NOT BE SENT TO SHOPS


- 32 High Street (Half-day Thurs.) Tel. 56420 LEICESTER
- 5-7 County (Mecca) Arcade, Briggate (Half-day Wed.) Tel. 28252 LEEDS
- 73 Dale St. (Half-day Wed.) Tel. CENTRAL 3573 LIVERPOOL
- 238 Edgware Road, W2 (Half-day Thurs.) Tel. PAD 1525 LONDON
- 60A Oldham Street (Half-day Wed.) Tel. CENTRAL 2778 MANCHESTER
- 106 Newport Rd. (Half-day Wed.) Tel. 47096 MIDDLESBROUGH
- 41 Blackett Street (Opp Fenwicks Store) (Half-day Wed.) Tel. 21465 NEWCASTLE UPON TYNE
- 13 Exchange Street (Castle Market Bldgs.) (Half-day Thursday) Tel. 20716 SHEFFIELD



# DISCOTHEQUE EQUIPMENT PACKAGE OFFERS

<b>F.A.L. PHASE 60 MK.II AMPLIFIER</b> PR. FANE POP 25/8 25W L/SPEAKERS Terms: Deposit £25.50 and 9 monthly payments of £4.72 (Total £47.98)	<b>£32.50</b> <b>£13.50</b> <b>£47.00</b>	<b>PACKAGE PRICE</b> <b>£44</b> carr. £1
<b>F.A.L. PHASE 60 MK.II AMPLIFIER</b> PR. FANE POP 50 L/SPEAKERS Terms: Deposit £10.50 and 9 monthly payments of £5 (Total £55.50)	<b>£32.50</b> <b>£21</b> <b>£53.50</b>	<b>PACKAGE PRICE</b> <b>£49.50</b> carr. £1
<b>F.A.L. PHASE 100 AMPLIFIER</b> PR. LISB 50W 1/8 in cabinets Terms: Deposit £22 and 9 monthly payments of £11.62 (Total £109.56)	<b>£61.95</b> <b>£59.90</b> <b>£121.75</b>	<b>PACKAGE PRICE</b> <b>£118</b> carr. £1.50
<b>F.A.L. PHASE 100 AMPLIFIER</b> 4 FANE POP 50 L/SPEAKERS Terms: Deposit £15 and 9 monthly payments of £10.52 (Total £109.50)	<b>£61.95</b> <b>£48</b> <b>£109.95</b>	<b>PACKAGE PRICE</b> <b>£99</b> carr. £1.50

## F.A.L. DISCOTHEQUE CONSOLE

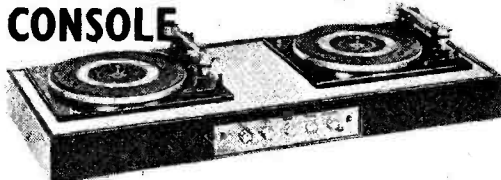

Incorporating twin Garrard SP25 Mk.III turntables and Goldring CS90 Ceramic Cartridges with diamond styli. Separate Vol. controls for each turntable. Also MONITORING FACILITIES, plus Treble and Bass Controls. Black Rexine covered Cabinet with lid.

**£65** Carr. £1.25  
Terms: Deposit £11 and 9 monthly payments of £8.70 (Total £71.30)

## AUDIOTRINE HI-FI SPEAKER SYSTEMS

Consisting of matched 12in. 11,000 line 15 Watt 15 ohm high quality speaker, cross-over unit and tweeter. Smooth response and extended frequency range ensure surprisingly realistic reproduction.

**£5.75** Carr. 30p  
OR SENIOR 15 WATT INC. **£6.75** Carr. 30p  
HF126 15,000 LINE SPEAKER carr. 30p

## AUDIOTRINE HIGH FIDELITY LOUSPEAKERS

Heavy construction. Latest high efficiency ceramic magnets. Treated Cone surround. "D" indicates Tweeter Cone providing extended frequency range up to 15,000 c.p.s. Impedance 3 or 8-15 ohms. PLEASE STATE CHOICE! Exceptional performance at low cost.

HF801D 8" 8W £2.71 HF120D 12" 15W £4.75  
HF102D 10" 10W £3.40 HF132 12" 15W £5.50  
HF120 12" 15W £4.25 HF126D 12" 15W £5.90

## FANE 807 HIGH FIDELITY LOUSPEAKERS

A full range 8in. 10 watt unit for excellent sound quality, in suitable enclosure. Cast chassis Roll P.V.C. cone surround and low throw voice coil to achieve very low fundamental resonance of 30 c.p.s. Tweeter cone is fitted to extend high note response. Frequency range 25 Hz to 15 KHz. Gussing 10,000. Impedance 3 or 8-15 Ω. STATE WHEN ORDERING

**£3.50**

## HI-FI SPEAKER ENCLOSURES

Modern design. Teak veneer finish. Acoustically lined. All sizes approx. Carr. 10p. per enclosure

JES Size 16 x 11 x 9in. Preset. £5.35  
SE8 For optimum performance with any 8in. Hi-Fi speaker. Size 22 x 15 x 9in. Ported. £6.47  
SE10 For outstanding results SE12 For exchit prince with 12in with 10in. Hi-Fi speaker. £6.74 Hi-Fi speaker and Tweeter. £7.87  
Size 24x15x10in. Pk'd. Size 25 x 16 x 10in.

## R.S.C. BATTERY/MAINS CONVERSION UNITS

TYPE BML. All all-dry battery eliminator. Size 5 1/2 x 4 1/2 x 2in. approx. Completely replaces batteries supplying 1.5v and 90v, where A.C. mains 200/250V. 50c/s is available. Complete kit with diagram £3 Assembled ready with diagram £3.50

## R.S.C. TA6 6 Watt HI-FI SOLID STATE AMPLIFIER

200-250v. AC mains operated. Frequency Response 30-20,000 c.p.s. —2dB. Harmonic Distortion 0.5% at 1,000 c.p.s. Separate Bass and Tape. Input selector switch. Output for 3-15 ohm spkrs. Max. sensitivity 5mV. Output rating I.H.F.M. Fully enclosed enameled case, 9 1/2 x 2 1/2 x 3 1/2 in. Attractive brushed silver finish fascia plate 10 1/2 x 3 1/2 in. and matching knobs. Complete kit of parts with full wiring diagrams and instructions.

**£7.50** Carr. 40p  
OR FACTORY BUILT WITH 12 MONTHS' GUARANTEE **£9.75**

## R.S.C. ALL HI-FI 12-14 WATT AMPLIFIER

PUSH-PULL OUTPUT. Two input sockets with sep. Vol. controls for mixing. High sensitivity, 5 valves. Bass and treble controls. Response ± 3dB 30-20,000 c/s. Hum level —60dB. Sensitivity 40 millivolts. For Crystal or Ceramic PUs. High Impedance "mikes". For Musical Instruments etc.

Std. AC mains. For 3 & 15 ohm spkrs. Complete kit. Full instructions and point-to-point wiring diagrams. Carr. 60p SAE for leaflet. Twin handled metal cover £1.75  
Factory built £14.75 or Dep. £3 and 9 mthly pymts of £1.60 (Total £17.40)

## R.S.C. COLUMN SPEAKERS

IDEAL FOR VOCALISTS AND PUBLIC ADDRESS

All types 15 Ohms covered in Rexine and Vynair

TYPE C4100 IS ALSO SUITABLE FOR BASS GUITAR OR ELECTRONIC ORGAN

**TYPE C485 25-30 WATTS**  
Fitted four 8" high flux 8 watt speakers. Overall size approx 48x10x6 in.  
Terms: Dep £2 and 9 monthly payments £2 (Total £21) Carr 50p **£17.75**

**TYPE C4125 50 WATTS**  
Fitted four 12" 11,000 line 15 watt speakers. Overall size approx 56 x 14 x 9 in.  
Terms: Dep. £4 and 9 monthly payments £3 (Total £31) Carr 75p **£27.50**

**TYPE C4100 100 WATTS** inc. four 12" 50 watt speakers for conservative rating. Extra heavy construction. Size approx 58 x 16 x 10" Acoustically filled and pressurised. Terms: Dep. £7.50 and 9 mthly. pym. £5.45 (Total £56.55). Carr. £1 **£50.50**

## 30 WATT HI-FI AMPLIFIER FOR GUITAR, VOCAL OR INSTRUMENTAL GROUP.

A 2 or 4 input, 2 vol. control Hi-Fi unit with Separate Bass and Treble controls. Current valves. Peak output rating. Strong Rexine covered cabinet with handles. Attractive black/gold P.V.C. fascia. Neon indicator. For 200-250V. A.C. mains. For 3 or 15 ohm speakers. ONLY **£19.95** Carr. 65p  
Send S.A.E. for leaflet. Terms: Deposit £3.70 and 9 monthly payments of £2.10 (Total £22.60)

## HIGH QUALITY LOUSPEAKER UNITS

IN TEAK VENEERED CABINETS

L18 13" x 8" 10 Watt 10,000 lines 3 or 15 ohms. State impedance required. **£5.25** carr. 40p

L12 12" 25 WATT 10,000 lines 15 ohms. Also supplied Rexine covered. **£10.50** carr. 45p

L125 50 WATT Two tone Rexine and Vynair finish. Fitted pair of 12" 50 watt high flux speakers for conservative rating. Impedance 8-15 ohms. Or deposit £4 and 9 monthly payments of £3.35. Total £34.15 Carr. 75p **£31**

## R.S.C. BASS REGENT 50 WATT AMPLIFIER

A powerful high quality all-purpose unit for lead, rhythm, bass guitar, vocalists, gram, radio, tape. Peak Output rating. Loudspeaker unit optional horizontal or vertical mounting. **£60** Carr. £1.50

\* Two extra heavy duty 12in. Loudspeakers  
\* Four Jack inputs and two Volume Controls for simultaneous use of up to four pick-ups or "mikes". Bass and Treble controls. Send S.A.E. for leaflet. Credit Terms Deposit £16 and 9 monthly payments of £5.75 (Total £67.75)

## FAL PHASE 50 MKII AMPLIFIER 50W FAL PHASE 100 AMPLIFIER 100W

Solid state 4 Separately controlled inputs. Plus master vol. control. Ind. Bass and Treble Controls. Protective circuit to guard against damage from accidental shorts. Output for Speaker/ 3-30 ohms. Size 17" x 7" x 7 1/2" 200-250V. A.C. mains. Output 60 watts music rating. Or deposit £6 & 9 monthly payments £3.50. Total £37.50. Carr. 65p

Solid state 4 Separately controlled inputs Plus master volume control. Ind. Bass and Treble Controls. Output for speaker/s 3-30 ohms. Protective circuit to guard against damage from accidental shorts. I.H.F.M. Output rating. **£61.95** Carr. 75p  
Or deposit £12 & 9 monthly payments £6.25. Send S.A.E. for leaflets. Total £88.25.

## FANE ULTRA HIGH POWER LOUSPEAKERS

All power ratings are R.M.S. continuous. 2 YEARS' GUARANTEE

High flux ceramic magnets. Heavy cast chassis. All carr. free.

**'POP' 100** 18" 100Watt 14,000 gauss 8/15Ω **£22.50**  
Dep. £6 and 9 monthly payments £2.15 (Total £25.50)  
FOR BASS GUITAR, ELECT. ORGAN, ETC.

**'POP' 60** 15" 60 Watt 14,000 gauss 8/15Ω **£12.90**  
Dep. £3.30 and 9 monthly payments. £1.30 (Total £15).

**'POP' 50** 12" 50 Watt 13,000 gauss 15Ω **£10.50**  
Dep. £2 and 9 monthly payments £1.15 (Total £12.55)  
Fits suitable all purposes

**F A N E LOUSPEAKERS 'POP' 25/2** 12in. 25 WATT Dual Cone 15Ω (for uses other than Bass Guitar or Electronic Organ). **£6.75** Carr. free or Dep. £1 and 9 mthly payments 75p (Total £7.75)

## R.S.C. A10 30 WATT ULTRA LINEAR HI-FI AMPLIFIER

Highly sensitive. Push-Pull high output. Hum level —70dB. Response ±3dB 30-20,000 c/s. All high grade components. Valves 6F86, 6F86, 6C0C83, 807, 6Z34. Separate Bass and Treble Controls. Sensitivity 36 millivolts. For High Impedance microphones. For Clubs, Schools, Theatres, Dance Halls, Outdoor Functions. For Electronic Organ, Guitar, String Bass, etc. Gram, Radio etc. For Electronic Organ, Guitar, String Bass, etc. Gram, Radio etc. For Electronic Organ, Guitar, String Bass, etc. Gram, Radio etc. For Electronic Organ, Guitar, String Bass, etc. Gram, Radio etc.

or Tape. Two separate inputs with vol. controls permit such as "mike" and Pick-up etc. to be used for mixing purposes. 200-250 v. 50 c/s A.C. mains. For 3 and 15 ohm speakers. Complete Kit of parts with wiring diagram and instructions. Twin-handled perforated cover. **£15.75** Carr. 65p  
TERMS: Deposit £4 and 9 monthly payments of £2.10 (Total £22.80). Send S.A.E. for leaflet.

## RSC TRANSFORMERS, L.F. CHOKES & RECTIFIERS

FULLY GUARANTEED. Impregnated and Interleaved where necessary

Primarys 200-250v. 50c/s. Screened	FILAMENT or TRANSISTOR POWER PACK
MIDGET CLAMPED TYPE 2 1/2 x 2 1/2 in.	Types 6.3v. 1.5a. 48p; 6.3v. 2a. 54p; 6.3v. 3a. 76p; 6.3v. 6a. £1.30; 12v. 1a. 56p; 12v. 3a. or 24v. 1.5a. £1.35; 0.9-18v. 12a. £1.10; 0.12-25-42v. 2a. £1.76
250-0-250v. 60mA. 6.3v. 2a. 0-5-6.3v. 2a. £1.05	CHARGER TRANSFORMERS 0.9-15v. 11a. 99p; 2.5a. £1.10; 3a. £1.25; 5a. £1.45; 6a. £1.65; 8a. £2.00
FULLY SHROUDED UPRIGHT MOUNTING	AUTO (Step Up/step DOWN) TRANSFORMERS
250-0-250v. 100mA. 6.3v. 4a. 0-5-6.3v. 3a. £1.40	0-110/120v. 200-230-250v.. 50-80 watts £1-10; 150 watts, £1.90 250 watts £2.75; 500 watts £5.75.
250-0-250v. 100mA. 6.3v. 4a. 0-5-6.3v. 3a. £2.20	OUTPUT TRANSFORMERS
300-0-300v. 100mA. 6.3v. 4a. c.t., 6.3v. 1a. £2.20	Standard Pentode 6,000 Ω to 7,000 Ω to 3 Ω 50p
For Mullard 510 Amplifier £2.45	Push-Pull 8 watts EL84 to 3 or 15 Ω 85p
350-0-350v. 100mA. 6.3v. 4a. 0-5-6.3v. 3a. £2.65	Push-Pull 10 watts 6E4, 6CL8 to 3, 5, 8 or 15 Ω £1.37
425-0-425v. 200mA. 6.3v. 4a., c.t., 5v. 3a. £4.95	Push-Pull EL84 to 3 or 15 Ω 10-12 watts £1.85
425-0-425v. 200mA. 6.3v. 4a., 6.3v. 3a., 6v. 3a. £5.10	Push-Pull Ultra Linear for Mullard 510, etc. £2.20
450-0-450v. 250mA. 6.3v. 4a., c.t., 5v. 3a. £5.50	Push-Pull 15-18 watt, sectionally wound 6L6, KT86, etc., for 3 or 15 Ω £1.90
TOP SHROUDED DROP-THERO' TYPE	Push-Pull 20 watt high quality sectionally wound EL34, 6L6, KT76 etc. to 3 or 15 Ω £3.80
250-0-250v. 70mA. 6.3v. 2a. 0-5-6.3v. 2a. £1.35	SMOOTHING CHOKES 150mA, 7-10H. 250 Ω 70p; 100mA, 10H, 200 Ω 60p; 80mA, 10H, 350 Ω 50p; 60mA, 10H, 400 Ω 25p.
250-0-250v. 100mA. 6.3v. 3.5a. £1.60	
250-0-250v. 100mA. 6.3v. 2a., 6.3v. 1a. £1.80	
350-0-350v. 100mA. 6.3v. 2a., 0-5-6.3v. 2a. £1.85	
250-0-250v. 100mA. 6.3v. 4a., 0-5-6.3v. 3a. £2.20	
300-0-300v. 100mA. 6.3v. 4a., 0-5-6.3v. 3a. £2.20	
300-0-300v. 130mA. 6.3v. 4a., 0-5-6.3v. 1a. Suitable for Mullard 510 Amplifier £3.60	
350-0-350v. 100mA. 6.3v. 4a., 0-5-6.3v. 3a. £2.20	
350-0-350v. 150mA. 6.3v. 4a., 0-5-6.3v. 3a. £2.60	

SELENIUM RECTIFIERS F. W. (Bridged) All 6/12v. D.C. output. Max. A.C. input 18v. 1a. 25p. 2a. 35p. 3a. 50p. 4a. 60p. 5a. 80p.

**Fully guaranteed  
Individually packed  
VALVES**

B12H	41p	ECH200	62p	OA2	35p
CY31	35p	ECL50	45p	OB2	35p
DAF96	38p	ECL82	32p	PABC80	37p
DF96	37p	ECL83	65p	PC97	40p
DK96	41p	ECL86	42p	PC900	47p
DL92	32p	EF36	45p	PC084	37p
DL94	40p	EF37A	45p	PC089	45p
DL96	41p	EF39	40p	PC089	55p
DM70	30p	EF40	40p	PC089	75p
DY86	45p	EF41	62p	PC089	45p
DY87	55p	EF42	25p	PC082	38p
DY802	48p	EF83	55p	PC084	48p
EB80C/01	£1.80p	EF85	32p	PC086	57p
		EF86	31p	PC089	77p
E180C	42p	EF89	28p	PC091	77p
E180C	90p	EF91	16p	PC091	48p
E182C	£1.05	EF92	37p	PC092	45p
		EF95	30p	PC095	72p
EABC80	82p	EF183	32p	PC096	65p
EAF42	50p	EF184	35p	PC098	72p
EB91	15p	EF1200	70p	PC1200	70p
EB33	50p	EL34	52p	PC181	47p
EB41	52p	EL41	57p	PC182	37p
EC81	30p	EL42	59p	PC185	85p
EBF80	42p	EL84	23p	PC184	42p
EBF83	42p	EL85	40p	PC185	42p
EBF89	30p	EL86	40p	PC186	42p
EC91	30p	EL90	30p	PC1200	57p
EC92	25p	EL85	35p	PL36	55p
EC93	30p	EL500	85p	PL41	60p
EC94	20p	EM31	25p	PL82	40p
EC95	40p	EM80	40p	PL88	42p
LC086	50p	EM84	35p	PL84	35p
EC088	37p	EM87	55p	PL80	78p
ECC189	52p	EY51	40p	PL804	75p
ECF80	35p	EY33	60p	PY33	60p
ECF82	35p	EY81	35p	PY80	37p
ECF83	75p	EY88	40p	PY81	25p
ECF801	62p	EZ41	42p	PY82	27p
ECF802	62p	EZ20	25p	PY83	35p
ECF85	60p	EZ81	27p	PY88	37p
ECF82	60p	EZ84	55p	PY80	52p
ECB81	25p	KT86	£1.80p	PY801	85p
ECB83	42p	KT88	£2.15p	QQV03-10	£1.25p
ECB84	45p	N78	£1.25p		

29/41t. AERIALS each consisting of ten 3ft. jin. dia. tubular screw-in sections. 11ft. (6-section) whip aerial with adaptor to fit the 7in. rod, insulated base, stay plate and stay assemblies, pegs, reamer, hammer, etc. Absolutely brand new and complete ready to erect. In canvas bag £4. P. & P. 50p.

**METERS**

Full list of our very large stock of meters on request.

**TRANSISTORS, ZENER DIODES etc.**

SPECIAL OFFER	OC25	37p	OC200	40p	2N3055	75p	AD149	50p	BYZ13	85p
094 tube	OC26	25p	OC201	60p	2N3730	50p	AD161	37p	BYZ16	85p
	OC28	62p	OC206	90p	2N3731	£2.75p	AD162	37p	CRS1/10	28p
	OA5	£1.75	OC29	62p	IN21	17p	2N8109	£2.05p	AF118	62p
	OA10	20p	OC35	50p	IN21B	25p	4082	60p	AF137	17p
	OA70	10p	OC44	17p	IN25	60p	82303	60p	AF139	30p
	OA71	10p	OC45	17p	IN27	10p	3F100	67p	AF178	48p
	OA73	10p	OC70	12p	IN702-72536p	3N128	87p	AF186	40p	
	OA74	10p	OC71	15p	IN823A	£1.30	IN139	£1.70p	AFY26	25p
	OA79	10p	OC72	15p	IZMT5	35p	IN140	25p	ASX28	25p
	OA81	10p	OC73	30p	IZMT10	35p	IN164	90p	ASX47	48p
	OA91	7p	OC75	25p	IZT5	67p	IN159	£1.45p	BAW19	25p
	OA200	7p	OC76	25p	IZT10	63p	6FR5	45p	BC107	12p
	OA202	10p	OC81	25p	2G385	51p	12FR60	73p	BC108	12p
	OA210	25p	OC81D	20p	2G400	15p	10D1	16p	BC113	25p
	OA211	37p	OC81DM	20p	IN4785	50p	40694	£1.37p	BC118	35p
	OA2201	50p	OC82	25p	2N2727	52p	40696	£1.37p	BUY72	15p
	OA2202	47p	OC83	25p	2N1918	37p	40688	£1.45p	BF115	25p
	OA2206	42p	OC83B	25p	2N1304	25p	40689	£1.35p	BF173	30p
	OA2207	47p	OC84	25p	2N1306	25p	AC126	25p	BFY51	20p
	OA2208	40p	OC122	50p	2N1307	25p	AC127	25p	BS05	38p
	OA2213	32p	OC139	25p	2N1307	25p	AC128	25p	BS	45p
	OA2223	20p	OC140	37p	2N2147	75p	AC176	25p	BS2	47p
	OA2225	50p	OC170	35p	2N2904A	32p	AC176	25p	BS2	47p
	OC16	50p	OC171	30p	2N3058	25p	ACX17	30p	BSY29	25p
	OC22	50p	OC172	37p	2N3054	37p	ACX28	17p	BU100	£1.80p

MANY OTHERS IN STOCK include Cathode Ray Tubes and Special Valves. U.K. P. & P. Up to £1 12p, £1-£2 17p, £2-£3 22p. Over £3 post free. C.O.D. 20p extra.



ALL valves guaranteed

**INTERGRATED CIRCUITS—  
MANY OTHERS IN STOCK**

QV06-40A	UBC41	47p	UY85	30p	3Q4	37p	6AK5	30p	6BA6	25p
	UBF80	35p	VR105/30	35	384	35p	6AK8	32p	6BB6	30p
R17	UBF89	35p	VR150/30	35p	3V4	45p	6AL5	15p	6BC6G	60p
R19	UC085	40p	Z759	£1.65p	5B254M	£2.20	6AL6W	40p	6BJ6	40p
STV280/40	UCF80	55p	Z801U	£18.00p	5B255M	6AM6	30p	6BQ7A	35p	
STV280/80	UCH81	35p	Z803A	£1.25p	5B255M	£1.75	6AN8	50p	6Y9G	60p
	UCL82	70p	Z900T	75p	5R4CY	60p	6AQ5	35p	6BZ17	30p
TT21	UCL83	65p	IL4	15p	5U4G	35p	6AQ5W	50p	6Z4	42p
U25	U25	75p	UL14	50p	5V4G	40p	6AS6	37p	6C4	30p
U26	U26	75p	UL41	60p	5Y4G	40p	6AS7G	80p	6C6	25p
U27	U27	50p	UL84	30p	5Y3GT	35p	6AT6	30p	6CH6	55p
U191	U191	70p	UL84	30p	6A4	75p	6A6	25p	6CL6	49p
U801	U801	£1.00p	UL84	30p	6ZAGT	40p	6AX4GT	40p	6D6	90p
UAB080	U801	£1.00p	UL84	30p	6AB7	30p	6AX5GT	65p	6EA8	55p
UAF42	U801	£1.00p	UL84	30p	6AC7	15p	6B7	40p	6F23	75p
	U801	£1.00p	UL84	30p	6AH6	50p	6BK7	40p	6F83	£1.60

Colomar (Electronics) Ltd.  
170 GOLDHAWK ROAD, LONDON W12.  
Tel: 01-743 0899  
Open 9-12.30, 1.30-5.30 p.m. Thursday 9-1 p.m.

**"Stella 99"**

**INSTRUMENT CASES**



Size  
6" W x 4" H  
x 4" D

Price  
£1.25p  
+ 25p p.p.

We believe the finest instrument case in the country. Beats all competitors for price and strength

Fibreglass Press Moulded in Grey, and Blue. Supplied with 4 Rubber Feet. 18 SWG Alloy Chassis. 16 SWG Alloy Front Panel. Front Panel has Protective Film for marking out and protection. Chromed die cast handle. The case has two sets of Runners Moulded in which will take Alloy or P.C. Board Chassis. Same day off-the-shelf delivery. This size of case can be turned on end to make 4" W x 6" H x 4" D. Please advise if handle and feet to be supplied loose. Panel Punching available on 100 up. Trade and quantity discounts on request.

Full list of Accessories Available, sent with each order, i.e. Switches, Panel Lamps, Amplifiers, Fuses, etc.

E. R. NICHOLLS

46 Lowfield Road, Stockport, Cheshire  
Tel: 061-480 2179

**BUILD YOUR CIRCUITS  
ON  
VEROBOARD**

—the Universal Wiring Board—  
obtainable from your local Retailer

Trade enquiries to:  
**NORMAN ROSE (ELECTRICAL) LTD.**  
8 St. Chad's Place, Gray's Inn Road, London, W.C.1

Technical enquiries to:  
**VERO ELECTRONICS LTD.**  
Industrial Estate, Chandler's Ford, Hants



**AMAZING MINI-DRILL**

FOR PRECISION  
**MODEL  
WORK**



+ 6 TOOLS

Indispensable for precision drilling, grinding, polishing, etching, gouging, shaping. Precision power for the enthusiast. Shockproof. Completely portable power from 4½ volt external battery. So much more scope with MINI-DRILL. Super Kit (extra power, interchangeable chuck) £4.50, p.p. 13p. De Luxe Professional Kit with 17 tools £7.00 p.p. 23p. Money ref. g' tee.

**MERLIN SUPPLY CO.**

Dept. PW11D Nailsea, Bristol BS19 2LP

# AUDIO SUPPLIES

## SLASH PRICES! UP TO 60%

### SPEAKERS (KITS AND CHASSIS) p.p. 50p. Prices Per Pair

Richard Allan Twin Assembly	£17-00
Richard Allan Triple Assembly	£28-00
Richard Allan Super Triple Assembly	£32-00
Wharfedale Unit 3	£20-00
Wharfedale Unit 4	£28-50
Wharfedale Unit 5	£38-50
Goodmans Axlette 8	£12-25
Twin-Axlette 8	£14-25
Axlon 10	£15-00
Axlon 201	£21-25
Axlon 301	£30-50
Axlon 401	£29-00
Axlon 8P	£8-50
Axlon 10P	£8-50
Axlon 81	£19-00
Axlon 61	£27-50
Axlon 12P	£19-50
Axlon 15P	£33-00
Axlon 18P	£52-95
Twin Axlon 10	£15-85
ARU 172	£7-00
Trebox 100	£11-75
Trebox 5K/20XL	£14-50
Midex	£17-95
Attenuator	£4-75
XO/850/5000	£14-00
XO/5000	£4-00
Wharfedale Rin. bronze/R5/DD	£7-50
Wharfedale Super 8/R5/DD	£14-00
Wharfedale Super 10/R5/DD	£22-50
Wharfedale WMT1 matching transformer	£1-50
Any other make	P.O.A.

### STEREO AMPLIFIERS p.p. 50p

ARMSTRONG 521	£44-00
AMSTRAD 8000	£15-00
H.L. SA707	£18-00
TELETON SA Q208B	£18-00
VICEROY VASTO	£42-00
VICEROY 55	£16-00
SANSUI full range in stock P.O.A.	
METRO SOUND ST20E	£28-00
SINCLAIR 2000 MkII	£22-00
SINCLAIR 3000	£32-00
SINCLAIR NEOTERIC	£46-00
SINCLAIR A.F.U.	£4-50
SINCLAIR S60 + 2 Z30/PZ5	£15-00
SINCLAIR S60 + 2 Z30/PZ6	£17-50
SINCLAIR S60 + 2 Z50 + PZ8 and Mains trans.	£22-00
Sonab special offer for personal callers only	

### TUNER AMPLIFIERS p.p. 50p

ARMSTRONG 526	£80-00
ARMSTRONG 525	£70-00
RODGERS RAVENSBROOK	P.O.A.
TELETON CR10T with speakers	£25-50
TELETON F2100	£30-00
WHARFEDALE 100-1	£100-00
PHILIPS RH781	£53-50
GOODMANS MODULE 80	£72-00
TELETON R8000 with speakers	£35-00
TOSHIBA range P.O.A.	
Sonab special offer for personal callers only	

### TUNERS p.p. 50p

ARMSTRONG M8	£7-75
ARMSTRONG 523	£40-00
ARMSTRONG 524	£31-00
SINCLAIR Pro. 60	£19-50
RODGERS RAVENSBORNE FET2 Chassis	£45-00

Easy to find—50 yards from (B.R.)  
Stoke Newington Stn.  
67, 149, 247, 73, 76, 243 Buses Pass our  
door.

### TAPE DECKS AND RECORDERS p.p. £1-50p

Ferrograph 722/724	£196-00
Ferrograph 702/704	£166-00
Philips 2202	£22-00
Philips 2205	£33-00
Philips 4404	£73-00
Philips 4407	£89-00
Philips 4307	£37-50
Philips 4500	£97-75
Philips 4408	£107-00
Philips N4308	£46-00
Teleton FXB 510D	£47-00
Teleton 999	£82-50

### PLINTHS AND COVERS p.p. 50p

For Garrard 1025, 2035, 3000, 3500, SP25, 40B, SL65B, base finished in teak cover perspex.

### STAR PRICE £3-25.

Star Super Plinths and Cover, base made of aluminium and cover is vacuum formed RRP £8.

### STAR PRICE £5-75.

Plinths and Covers for AP75, AP76, SL72B, SL75B, SL95B which allow cover to be left in position when playing £4-50. Also Plinths and Covers for BSR McDonald range £4-25.

### SPEAKERS (PRICES PER PAIR) p.p. £1-50.

Wharfedale Dentons	£26-50
Wharfedale Super Lintons	£39-00
Wharfedale Doveedale III	£63-00
Wharfedale Melton	£48-00
Wharfedale Rosedale	£100-00
Wharfedale Aston	£35-00
Wharfedale Triton	£39-00
Leak 600	£70-00
Leak 300	£44-00
Leak 200	£33-00
Cambridge R50	£150-00
Goodmans Ministor	£36-00
Goodmans Magister	£82-00
Goodmans Maxim	£30-00
Goodmans Mezzo 3	£47-00
Goodmans Magnum K2	£64-00
Celestion Ditton 15	£47-00
S & W DM1	£45-50
Richard Allan Pavane	£46-00
Sinclair Q16	£13-00
Kelatron 500	£15-50
Stema 400	£34-00
Stema 300	£48-00
Stema Hi-Fi 4	£77-00
Stema Hi-Fi 3	£83-00
Metro sound HFS10	£21-00

### SCOOP CARTRIDGES p.p. 10p.

M.C.15	£4-00
SMC 101	£2-95
Shure M31/M32	£8-00

### PICKUP ARMS p.p. 25p.

SME 3009/S2	£24-00
SME 3012/S2	£25-00
Goldring L75	£9-50
Goldring L69	£7-50
Neat G30	£9-00
Ortofon RS212	£23-00
Ortofon AS212	£25-00
RMG 309	£20-00
M Shell	£1-20
Any other make	P.O.A.

FOR ALL YOUR NEEDS IN HI-FI  
EQUIPMENT SEND A LARGE S.A.E.  
or PAY A VISIT

2 SHOWROOMS DEVOTED TO  
DEMONSTRATING SPECIALLY  
SELECTED SYSTEMS

## SPECIAL OFFERS

GARRARD SP25 Mk. III  
GOLDRING G800 Superb Plinth  
and Cover.

SINCLAIR Project 60—Stereo 60  
Pre-Amplifier and Control Unit.  
2 Z30's and PZ5. 2 WHARFEDALE  
Unit 3. List Price £84-00. OUR PRICE  
£55. P. & P. £1-75.

GARRARD SP25 Mk III  
GOLDRING G800  
Plinth and Cover complete  
OUR PRICE £19-50. P. & P. £1-75.

### HEADPHONES p.p. 25p.

Koss PRO4AA	£22-00
Koss 727B	£13-00
Koss K6	£9-75
Koss ESP-6	£34-00
Koss ESP9	£53-00
Koss KRDT11	P.O.A.

### CARTRIDGES p.p. 10p

GOLDRING G850	£4-00
GOLDRING G800	£7-00
GOLDRING G800/E	£10-75
GOLDRING G800/SE	£16-00
SHURE M3D	£4-75
SHURE M44/5/7/C	£7-00
SHURE M55E	£9-00
SHURE M75E type 2	£14-00
SHURE V15 type 2	£30-00
SHURE 44E	£8-00
SHURE 31E	£9-00
SHURE 32E	£8-00
SONATONE 9TAHCD	£1-50
AUDIO TECHNICA AT66	£4-00
ADC 10/E MkII	£21-00

### GARRARD ZERO/100 IN STOCK SPECIAL PRICE £35-00.

### TURNTABLES p.p. 50p

GARRARD SP25/Mk. III	£10-50
GARRARD 2025TC with Sonotone 9TAHC Diamond Cartridge	£3-50
GARRARD A70 Mk. II	£11-00
GARRARD SL65B	£13-00
GARRARD AP76	£18-00
GARRARD SL72B	£23-00
GARRARD SL75B	£24-00
GARRARD 401	£32-00
GARRARD SL95B	£32-00
GOLDRING GL75P	£36-00
GOLDRING GL75	£28-00
GOLDRING GL69	£20-00
THORENS TD125	£21-00
THORENS TD150AB/2	£41-00
PIONEER PL11AC complete	£39-00
DUAL 1209	£34-00
PHILIPS 202A	£52-00

### SONAB IN STOCK

Connoisseur BDI ch.	£13-00
Connoisseur DBI P and C	£21-00
Connoisseur BDI with SAU 2 P and C	£31-50
Connoisseur BD2 SAU 2 ch.	£24-00
Connoisseur BD2 SAU 2 P and C	£31-00
Any other make	P.O.A.

All prices subject to change without notice

SEND CHEQUES, P.O., MONEY ORDER, etc. to—

# AUDIO SUPPLIES

PERSONAL CALLERS PLEASE NOTE—Cheques are only accepted when accompanied by a Bank Cheque Card (not Barclay Card).

PW11. 50 STAMFORD HILL, LONDON, N.16.  
Telephone: 01-806 3811/7311

# Train for tomorrow's world in Radio and Television at The Pembroke College of Electronics Your first day on Television: 5th January, 1972

This is your opportunity to train as a television and radio engineer on our full-time 2 year College Diploma Course. That is the way to get into a rapidly growing industry with a tremendous demand for skilled technicians. You will be given theoretical and practical instruction on colour television receivers, following a syllabus specially designed to cover the new City and Guilds Radio, Television and Electronic Technicians' Course.

Minimum entrance requirements are Senior Cambridge or 'O' Level, or equivalent in Mathematics and English.

Complete the coupon below and we will send you the details about training for an exciting, new career.



To: The Pembroke College of Electronics, (Dept. PW7), 34a Hereford Road, London, W2 5AJ.

Please send, without obligation, details of the Full-time Course in Radio, Television and Electronics.

NAME .....


ADDRESS .....

OSCILLOSCOPES	
E.M.I. WM16. Complete with Dual Trace Plug-in Amp/Differential Plug-in Amp.	£175
SOLARTRON CD.1820. With Wide Band Unit	£190
SOLARTRON CD.1820. With Dual Trace Unit	£220
SOLARTRON CD.1820. With Differential Amp Unit	£240
SOLARTRON CD.7118.2. Double Beam	£60
CAWELL REMSCOPE 80.1. Storage Oscilloscope	£300
E.M.I. W.M.3. Complete with Amplifier Type 8	£55
TEST GEAR	
WAYNE KERR. Universal Bridge Type B.221	£65
MARCONI Q Meter Type TF 329G	£45
MARCONI Video Oscillator Type TF 885A 20Hz-5MHz	£45
MARCONI Vacuum Tube Voltmeter TF 104A	£60
MARCONI FM/AM Signal Generator TF995A/4	£175
POWER UNIT. 240V. a.c. 1P.DC Output 400V 170mA/6-3V 3A	£10
R.F. GENERATOR. 200 Mc/s. 275 Watts	£85
R.F. GENERATOR. 25 Watts	£15
SERYOMEX CONTROLS LTD. Motor Controller Type MC47 Complete with Motor	£65
T.V. CAMERA LENSES	
BANK TAYLOR HOBSON VIDITAL LENSES. Standard "C" Mounts. Focal lengths 2cm, 6cm, 8cm	£25 each
R.C.A. AR88. Receiver	£40
MINIATURE GEARED MOTORS	
1 R.P.M. HAYDEN. 240V a.c. Clockwise Rotation	} .. 80p each
1/5 R.P.M. CROUZET. 240V a.c. Anticlockwise Rotation	
2 R.P.M. CROUZET. 20V a.c./12V d.c. Anticlockwise Rotation	
RELAYS	
SIEEMENS/VARLEY PLUG-IN. Complete with Transparent Dust Cover 2 Pole C/O 35p each. 4 Pole C/O 50p each	
S.T.C. Miniature Sealed Relays. 6V, 12V, 24V, 48V. 2 Pole C/O	50p each
C.P.O. Relays. 3000Ω. 2p C/O 50p. 4p C/O 60p each	
HEAVY DUTY. Relays 5A and 10A Contacts 12V, 24V. d.c. 110V, 240V a.c. 2p. C/O	90p each
LATCHING RELAYS. B. & R. Type EO2/T498 2p. C/O	95p each
SOLENOIDS	
12V. d.c. 2 1/2" x 1 1/2" Dia.	50p each
WIRE WOUND POTENTIOMETERS	
COLVERN. RELIANCE. All Values from 1Ω-100KΩ. Brand New	19p each
360° WIRE WOUND POTS. COLVERN CLR/6605/418 30KΩ	£1.50 each
BOURNS. 10 Turn Pots. 10KΩ ± 6% LIN 0-25% ..	£1.98 each
ILLUMINATED PUSH BUTTON SWITCHES	
Non-Locking Only. 2p C/O	35p each
PUSH BUTTON SWITCHES	
Multibank Push Button Switch assemblies now in Stock. Any combination, latching, non-latching, push-push, push to change over, push to hold etc.	
2p. C/O	80p per button.
4p. C/O	80p per button.
8p. C/O	40p per button.
MULTIPIN PLUGS AND SOCKETS	
PAINTON/JONES 2/4/6/8/12/16/24/32 Way.	
P.R.T., B.N.C., AMPHENOL, CANNON, D.I.N.. Plus Complete Audio Range.	
TRANSFORMERS	
D. C. TIBBLES & CO. P.R.I. 0-100-110-220-240V. SEC. 12V. 20A	£6-50 each
MINIATURE TRANSFORMERS. P.R.I. 240V SEC 12V 100mA	
2" x 1 1/2" x 1 1/2"	P.R.I. 240V SEC 0, 20V, 30V 100mA
	P.R.I. 240V SEC 0, 18, 35, 0, 18, 36 100mA
	All Types 65p each
SHROUDED TRANSFORMERS. P.R.I. 0-120-240V SEC. 24V 1A	£1.25 each
C-CORE TRANSFORMERS. P.R.I. 240V SEC 26V 1A	£1.80 each
HEATER TRANSFORMERS. P.R.I. 240V SEC 0, 7 1/2, 15V 1A	£1.20 each
HEATER TRANSFORMERS. P.R.I. 0-110-200-220-240 SEC 6-3V 3A	£1.00 each
ALARM BELLS	
Suitable for Burglar Alarms. AGRO Type 4145 200/250V a.c.	£3-50 each
PANEL METERS	
SIFAM MOVING COIL 1mA Size 4 1/2" x 4"	£3-25 each
SIFAM MOVING COIL 100μA Size 3 1/2" x 3"	£3-00 each
TAYLOR MOVING COIL 50-0-50μA Edgewise 2 1/2" scale	£4-25 each
ERNEST TURNER 270° Movement/Centre zero Circular 0-0-0-0-5 mA	
2 1/2" Dia.	£3-00 each
ERNEST TURNER 270° Movement/Centre zero Circular 1-0-1mA	
3 1/2" Dia.	£4-25 each
SARGAMO-WESTON ILLUMINATED METER 500μA F.S.D. 4 1/2" x 3 1/2"	£2-90 each
SARGAMO WESTON. 50μA F.S.D. 4 1/2" x 3 1/2"	£4-75 each
We also have a large number of assorted meters of different shapes/sizes/movements in stock.	
SOUND-TO-LIGHT MODULES SUITABLE FOR DISCO THEQUES ETC.	
SINGLE CHANNEL 750 Watt Model	£8-00 each
THREE CHANNEL MODEL	£18-00 each
150W. LIQUID OIL WHEEL PROJECTORS COM.	
PLETE WITH WHEEL	£25-00 each
EXTRA WHEELS 6" Dia	£6-00 each
COMPONENTS	
METAL OXIDE RESISTORS. 2% T.R.5 Complete Range always in Stock. 1 off 50 each. 100 off 3p each.	
MULLARD ELECTROLYTIC CAPACITORS. Complete Range always in Stock.	
MULLARD POLYESTER CAPACITORS. Complete Range always in Stock.	
LEMCO SILVER MICA CAPACITORS. Complete Range always in Stock.	
POLYMER FILM CAPACITORS. Complete Range always in Stock.	
WIREWOUND RESISTORS. 1W, 3W, 6W, 12W, 15W, 30W. Complete Range always in Stock.	
SEMICONDUCTORS. Transistors, Diodes, Rectifier Blocks, Thyristors, U.J.T.'s Discs, Triacs, P.E.T.'s, Zeners, Photocells etc.	
10% DISCOUNT	10% DISCOUNT
On any Cash Sale for Customers Presenting this Advertisement.	
C. T. ELECTRONICS	
267, ACTON LANE, LONDON, W.4	01-994-6275
Nearest Underground—Chiswick Park (District Line), Acton Town (Piccadilly Line). Bus Routes E2, 88, 207, 15, 7, 260.	
(Please note: As yet we do not have a catalogue available. Any queries please phone or call at the above address).	
BUSINESS HOURS: MON.-SAT. 9.30 a.m.-6 p.m. WED. 9.30 a.m.-1 p.m.	
WANTED. SURPLUS OR REDUNDANT COMPONENTS AND TEST EQUIPMENT	



## SUPER SPEAKER BARGAINS WHARFEDALE DENTONS

A compact system sold in matched pairs for a perfectly balanced stereo system. Each Denton contains an 8in. bass unit with 3in. pressure unit, coupled by a Wharfedale crossover network. Rated input: 15 watts maximum. Frequency response: 65-17,000Hz. Impedance: 4/8 ohms. Cabinet 9 1/2in. x 14in. x 8 1/2in. These most attractive units are available in oiled teak, white or matt walnut and are small enough to blend in with most surroundings.

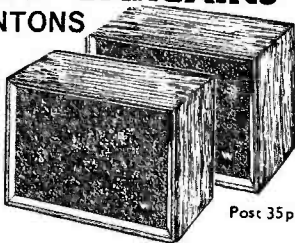


Post 35p

LIST PRICE £39.90 **£27.00** Teak

## WHARFEDALE TRITONS

A new and exciting addition to the Wharfedale range, this three speaker system will satisfy the most ardent Hi-Fi enthusiast. Shelf or floor standing—hand finished in oiled teak or polished walnut. Frequency response 55-22,000Hz. C.A.B. Dome pressure unit. Bass unit 8in. Mid-range unit 5in. Treble unit 2 1/2in. Impedance 8 ohms. Size 21 1/2in. x 9 1/2in. x 9in.

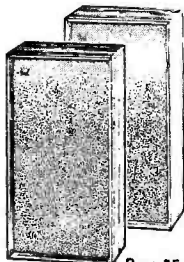

Post 35p.

LIST PRICE £59.90  
**LASKY'S £36.00** Teak  
**PRICE**

## BSR McDONALD MP60

High precision low-mass counterbalanced pick-up arm, heavy balanced turntable, simple to operate controls, viscous cueing device, slide in cartridge carrier, 4 pole motor.



**LASKY'S PRICE £12.50** Post 35p

### BSR McDONALD UNITS & PACKAGES

A. Chassis only. B. Complete with Lasky's plinth and cover. C. Complete with Lasky's plinth, cover and AD76K cartridge. D. Comp. wired on BSR plinth with cover. E. As D plus AD76K cartridge.

MODEL	A	B	C	D	E
MP.60	11.20	15.50	19.00	19.25	22.00
HT.70	15.90	20.00	23.50	24.50	27.00
610	14.50	18.57	22.00	23.00	25.50
510	12.10	16.50	19.85	20.00	22.85
310	9.75	14.00	17.25	17.90	20.25
210					9.95
MP.60 TPD2 Styrene base				18.00	21.00

## GARRARD UNITS AND PACKAGES

### GARRARD SL 55B

Four speed autochanger

**LASKY'S £10.50** Post 35p  
**PRICE**



Now available ZERO 1005

£49.95, post 35p.

Garrard SP25 Mk. III ... £11.50

Garrard SL40B ... £9.95  
Garrard AP76 without cart. £20.95  
Garrard 3000 with 9TA cart. £10.50  
Garrard 2025TC with 9TA cart. £9.85

### GARRARD PACKAGES

Garrard AP76 with AD76K cart. and Lasky's plinth and cover ... £35  
Garrard AP76 with Shure M44E cart. and Lasky's plinth and cover ... £40  
Garrard SP25 Mk. III, AD76K cart. and Lasky's plinth and cover ... £20  
Garrard SP25 Mk. III, Micro M2100/e cart. and Lasky's plinth and cover ... £25

## LASKY'S NEW LOW NOISE CASSETTES FROM THE USA

Type	Singles	5	10	20
C-60	32p	£1.52	£2.96	£5.60
C-90	50p	£2.37	£4.62	£8.75
C-120	69p	£3.28	£6.38	£10.85

Post Each 5p. 5-20p. 10-25. 20-50p.

# Lasky's Radio Limited

Branches

207 EDGWARE ROAD, LONDON. W.2 Tel: 01-723 3271  
33 TOTTENHAM Ct. RD., LONDON. W.1 Tel: 01-636 2605  
Open all day 9 a.m. - 6 p.m. Monday to Saturday

152/3 FLEET STREET, LONDON. E.C.4 Tel: 01-353 2833  
Open all day Thursday, early closing 1 p.m. Saturday

The Home of High Fidelity

42-45 TOTTENHAM CT. RD., LONDON. W.1 Tel: 01-580 2573  
Open all day 9 a.m. - 6 p.m. Monday to Saturday


### NEW CITY BRANCH NOW OPEN

109 FLEET STREET, LONDON. E.C.4 Tel: 01-353 5812  
Open all day Thursday, early closing 1 p.m. Saturday

ALL MAIL ORDERS AND CORRESPONDENCE TO: 3-15 CAVELL ST., TOWER HAMLETS, LONDON, E.1 Tel: 01-790 4821

## SONY 8FC 59WA SCOOP

### DIGITAL AM/FM CLOCK RADIO

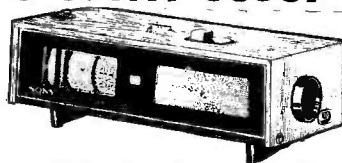

Digital Alarm Clock Radio. The digital clock shows you the time minute by minute with matchless accuracy and once set the Digimatic will wake you up at the same time every morning without having to be re-set. The radio section features Sony's unique sleep button, you fall gently to sleep lulled by the sweet tone of the radio, which switches itself off at a predetermined time. Available in either black or white. Frequency range 330-1,605KHz (AM); 87-108Hz (FM). Uses 8 transistors and 8 semi-conductors, built-in ferrite aerial and 3 1/2in loudspeaker. Power requirements: 230V AC 50Hz. Dimensions: 12 1/2in x 3 1/2in. x 5 1/2in.

LIST PRICE £30.00

**LASKY'S PRICE £16.75** Post 35p

## KATONE AM/AIRCRAFT PORTABLE RADIO


### BATTERY/MAINS

A combined battery and mains portable of exceptionally attractive design. Housed in a leatherette covered case, size 8 1/2in. x 5 1/2in. x 3 1/2in., fitted with an 8-section external telescopic aerial for FM and internal ferrite rod for MW wave bands, and clear easy-to-read dial with logging scale. Wave band coverage is FM 88-108MHz, AM 535-1,600KHz. A highly selective circuit using 9 transistors and 9 semi-conductors operating from either 4 x 1.5 volt torch batteries or direct from 230 volts 50Hz AC house mains, from a built-in mains unit. A socket is fitted for a personal earphone. Easy-to-use silver colour knobs, with "woodgrain" panel enhances the appearance of this fine radio.



**LASKY'S PRICE £9.95** Post 15p

## DIGITAL CLOCK SCOOP

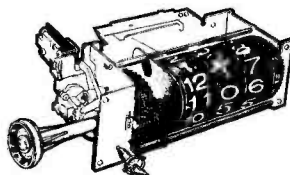

EXCLUSIVELY  
FROM LASKY'S

for you to mount into any housing. The clock measures 4 1/2 W x 1 1/2 H x 3 1/2 D (overall from front of drum to back of switch). SPEC.: 210/240V a.c., 50Hz operation; switch rating 250V, 3A. Complete with instructions. HUNDREDS OF APPLICATIONS. COMPLETE WITH KNOBS.

- MADE ESPECIALLY FOR LASKY'S BY FAMOUS MAKER
  - MAINS OPERATION
  - 12-HOUR ALARM
  - AUTO "SLEEP"
  - SWITCH
  - HOURS, MINUTES AND SECONDS READ-OFF
  - FORWARD AND BACKWARD TIME ADJUSTMENT
  - SILENT OPERATION SYNCHRONOUS MOTOR
  - SHOCK AND VIBRATION PROOF
  - BUILT IN ALARM BUZZER
- SPECIAL QUOTES FOR QUANTITIES

**LASKY'S PRICE £6.50** Post 20p

## TRIO HS.1 & HS.2 STEREO HEADPHONE BARGAINS

Models HS-1 and HS-2. Both these sets by TRIO offer really superb stereo reproduction in a lightweight, fully adjustable headset designed for optimum comfort. Listening fatigue is unknown with TRIO headphones. Brief spec. both models: Input imp. 8Ω nominal (matching 4 to 8Ω); max. input 0.5W; frequency response 20-19 kHz; output sensitivity at 1mW input: HS-1 118 dB, HS-2 111 dB; weight 0.66lbs. Identical in appearance—both models are finished in ivory with contrasting foam filled ear pads and head band.




LIST PRICE £8.40 LIST PRICE £6.75  
**HS.1 £5 HS.2 £4** Post 18p



# COMET

## HI-FI DISCOUNT WAREHOUSES

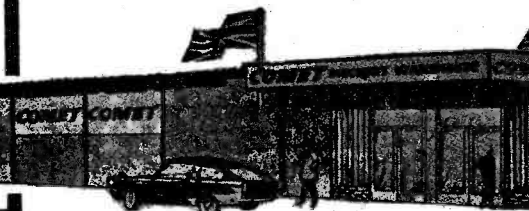

	Rec. Price	Retail Price	Comet Price
<b>STEREO AMPLIFIERS</b>			
ALBA UA 700	34-50	26-00	
AMSTRAD Stereo 8000	25-95	16-95	
ARMSTRONG 521	56-00	41-75	
DULCI 207M	32-00	19-95	
FERROGRAPH F307 Mk. II (Cased)	64-00	45-95	
FERROGRAPH F307 Mk. II	60-00	45-95	
GOODMANS Maxamp	54-00	37-95	
LEAK Stereo 30 Plus	56-50	40-95	
LEAK Stereo 30 Plus, in teak case	62-50	45-95	
LEAK Stereo 70 Chassis	69-00	49-50	
LEAK Stereo 70 cased	75-00	54-50	
METRO SOUND ST20E	59-50	27-95	
PHILIPS RH 591	79-00	54-95	
PHILIPS RH 580	52-00	36-95	
PHILIPS RH 580	29-00	18-50	
PIONEER SA500	62-10	39-25	
PIONEER SA700	98-00	67-95	
PIONEER SA900	134-10	94-45	
PIONEER Reverberation	45-50	31-95	
RANK Rotel 310	45-00	32-95	
RANK Rotel 610	69-00	49-95	
ROGERS Ravensbourne	59-50	42-95	
ROGERS Ravensbourne (cased)	64-00	47-95	
ROGERS Ravensbrook Mk. II	47-50	34-95	
ROGERS Ravensbrook (cased) Mk. II	52-50	38-95	
SINCLAIR 2000	35-00	23-75	
SINCLAIR Project 60/2 x Z30/P25	23-90	15-95	
SINCLAIR PROJECT 60/2 x Z50/P28/trans.	34-86	23-25	
SINCLAIR AFU	5-95	4-45	
SINCLAIR Neoteric	61-95	43-95	
SINCLAIR 3000	45-00	31-50	
TELETON SAQ 206	32-50	17-50	
TELETON GA101	37-50	28-50	
VOLTEX 100w. Stereo Discotheque, 8 electronically mixed inputs	185-00	139-00	
All the above take both ceramic and magnetic cartridges.			

	Rec. Price	Retail Price	Comet Price
<b>TUNER/AMPLIFIERS</b>			
AKAI AA 8500	221-85	175-00	
AKAI 6500	137-34	108-00	
AKAI 5300	123-85	99-95	
ARENA R500	82-00	67-00	
ARENA 2400	90-30	72-00	
ARENA 2600	111-30	89-95	
ARENA 2700	88-63	73-95	
ARENA T9000	303-45	265-00	
ARMSTRONG 92 Decoder	9-50	7-70	
ARMSTRONG 525	98-55	69-95	
ARMSTRONG 526	100-90	79-95	
GOODMANS Mod. 80, 35w. R.M.S.	91-59	68-95	
MIDLAND 19/542	49-95	37-50	
PHILIPS 882	96-50	76-95	
PHILIPS RH 790	134-00	98-95	
PIONEER SX770 AM/FM	159-79	125-95	
PIONEER SX990 AM/FM	192-61	148-95	
PIONEER 440	119-62	95-00	
TANDBERG 1171 comp. with decoder	110-00	94-00	
*TELETON F2000	51-50	28-95	
TELETON 7AT20	119-75	69-95	
TELETON 10AT1 150w. RMS	160-00	94-00	
TELETON TFS30	79-65	52-95	
TELETON TFS 50LA MWLW/VHF	86-64	69-95	
*TELETON R.8000 with Speakers	63-25	37-50	
TELETON CR55	125-26	74-95	
WHARFEDALE 100-1	139-00	89-95	
Starrd items above take ceramic cartridges only. All others take both ceramic and magnetic cartridges.			
All the above Tuners and Tuner/Amplifiers include MPX Stereo Decoder with the exception of Armstrong where decoder is extra as listed.			

	Rec. Price	Retail Price	Comet Price
<b>CARTRIDGES</b>			
GOLDRING 800	12-95	6-75	
GOLDRING 200E	18-16	10-50	
GOLDRING 800 Super E	25-10	15-95	
*GOLDRING CS90 Stereo	5-02	4-10	
*GOLDRING CS91E	7-53	6-00	
GOLDRING G850	6-27	3-95	
EMPIRE 1000ZE/X	69-34	51-25	
EMPIRE 999VE/X	43-00	34-95	
EMPIRE 999TE/X	25-09	21-00	
EMPIRE 999SE/X	20-31	16-95	
EMPIRE 999E/X	15-89	12-50	
EMPIRE 999V/X	12-95	10-25	
EMPIRE 909E/X	12-37	9-95	
EMPIRE 909V/X	9-26	7-75	
EMPIRE 902E/X	9-56	7-95	
ORBIT Magnetic NM 22	Special Price	2-95	
ORTOFON SL15E	28-62	22-95	
ORTOFON 2X15K Transformer	7-00	4-95	
SHURE M3DM	7-19	4-30	
SHURE M3E	11-63	8-75	
SHURE M32E	10-73	8-05	
SHURE M32-3	9-84	7-80	



### COMET for after-sales service

THROUGHOUT THE U.K.  
 Pictured, Service Dept. at Clough Rd., Hull also at Leeds, Stockton, Goole, Wakefield, Doncaster, Bridlington and Birmingham

	Rec. Price	Retail Price	Comet Price
SHURE M44-5	10-73	7-19	
SHURE M44-7	9-84	7-15	
SHURE M-44C	9-84	7-15	
SHURE M44E	11-63	7-50	
SHURE M55E	12-52	8-95	
SHURE M75G	15-93	13-75	
SHURE M75-6	16-10	12-45	
SHURE M75EJ	18-78	14-95	
SHURE M75E	20-57	12-95	
SHURE V15-11	39-35	27-95	
SHURE V15-11-7	37-95	27-95	
Starrd cartridges above are ceramic. All others are magnetic.			

	Rec. Price	Retail Price	Comet Price
<b>PICKUP ARMS</b>			
GOLDRING Lenco L75	13-98	0-50	
GOLDRING Lenco L69	10-04	6-50	
SME 3009 with S2 Shell	33-26	24-95	
SME 3012 with S2 Shell	35-42	26-45	

**TURNTABLES**

The following Turntables are complete with base, plinth, perspex cover and cartridge. Fully wired and ready for use. All at special prices.

GARRARD SP25 Mk 111 with Goldring G.800	Special Price	£21-95
GARRARD SP25 Mk 111 with Shure M.44/7	Special Price	£22-95
GARRARD SP25 Mk 111 with Shure M.55E	Special Price	£23-95
GARRARD AP76 with Goldring G800	Special Price	£30-95
GARRARD AP76 with Shure M55E	Special Price	£32-95
GARRARD AP76 with Shure M75E	Special Price	£36-95
GARRARD 2025 with Sonotone 9TACM	Special Price	£14-50
GOLDRING 705/P with G800	Special Price	£15-95
GOLDRING GL15 with G800	Special Price	£39-95
GOODMANS 3025 with G800	Special Price	£26-90

DUAL 1219 transcription	60-40	50-00
DUAL 1209 transcription	42-82	35-00
GARRARD SP25 Mk III	20-48	13-45
GARRARD SL75 B	39-20	26-50
GARRARD SL95 B	49-23	32-95
GARRARD 401	39-26	27-45
GARRARD SL72 B	31-93	23-95
GARRARD 3500, with GKS Cartridge and Cover to fit GARRARD SP25, SL65, SL65B and 3500	Special Price	£3-50
GARRARD 40B	13-34	10-49
GARRARD AP76	27-85	18-90
GOLDRING GL69 Mk. II	27-60	19-50
GOLDRING GL69P Mk. II	36-21	26-95
GOLDRING GL75P	40-15	28-95
GOLDRING GL75P	48-76	35-95
GOLDRING Covers for 69P and 75P	4-48	3-30
GOLDRING C99-plinth and cover for G99	11-05	9-75
GOLDRING G99	26-89	19-95
GOODMANS 3025	37-74	21-95
McDONALD MP 60	15-20	10-95
McDONALD 610	19-28	14-50
McDONALD HT 70	21-22	17-50
McDONALD HT 70 Inc. Plinth and Cover	30-68	24-95
Base and Cover for McDONALD MP 60 and 610	Special Price	£4-25
PHILIPS GA146	30-35	23-95
PHILIPS 202 Electronic	66-50	49-95

	Rec. Price	Retail Price	Comet Price
PHILIPS 308 transcription unit complete with base and cover	37-60	29-95	
PIONEER PL12A with base & cover	48-34	36-95	
THORENS T25 cover	8-52	6-95	
THORENS T0125	78-03	59-95	
THORENS T0125AB	115-57	94-50	
THORENS T0150A Mk. II	44-40	34-50	
THORENS T0150AB Mk. II	48-05	40-25	
THORENS TX11 Cover	4-26	3-50	

	Rec. Price	Retail Price	Comet Price
<b>SPEAKERS</b>			
B & W Model 70	159-50	114-95	
B & W DM3	83-00	48-40	
B & W DM1	38-47	31-95	
CELESTION Ditton 120	28-85	22-95	
CELESTION Ditton 15	38-47	31-95	
CELESTION Ditton 25	65-00	46-95	
GOODMANS J.1 Minister	24-10	17-45	
GOODMANS Magister	62-50	41-95	
GOODMANS Maxim	19-66	14-95	
GOODMANS Mezzo 3	34-00	22-95	
GOODMANS Magnum K2	44-00	29-95	
J & S Model SXMT (pair)	26-95	14-95	
KEF Cresta	22-17	19-00	
<b>KELETRON Speakers</b>			
KN500 4 speaker system (pair)	23-00	15-50	
KN700 4 speaker system (pair)	27-50	18-25	
KN1000 4 speaker system	19-25	13-95	
KN1500 4 speaker system	24-75	18-95	
KN2000 4 speaker system	38-75	19-95	
LEAK 300	30-19	18-45	
LEAK 300	39-33	21-95	
LEAK 600	49-50	34-95	
LOWTHER Acousta (with PM6)	52-50	45-50	
LOWTHER Acousta (with PM7)	65-00	54-00	
LOWTHER Ideal Baffle	37-50	32-00	
METRO SOUND HFS103 (pair)	30-05	19-95	
METRO SOUND 202	21-50	15-95	
METRO SOUND HFS20	23-59	17-95	
METRO SOUND HFS10 (pair)	26-65	21-95	
PHILIPS RH481	10-60	8-45	
PHILIPS RH482	17-35	14-45	
SINCLAIR Q16	8-95	6-20	
STE-MA 400	24-00	16-95	
TANDBERG TAN 7	28-00	23-95	
TANDBERG TAN 11	19-00	16-25	
TANDBERG TAN 15	45-00	35-95	
<b>WHARFEDALE Speakers</b>			
Denton	19-23	14-70	
Super Linton	24-05	18-45	
Melton	32-50	21-95	
Dovedale 3	43-00	28-95	
Rosedale	65-00	48-50	
Trikon (pair)	72-16	39-95	
Unit 3 Speaker Kit	12-15	9-70	
Unit 4 Speaker Kit	18-00	12-50	
Unit 5 Speaker Kit	26-00	18-90	

	Rec. Price	Retail Price	Comet Price
<b>CHASSIS SPEAKERS</b>			
GOODMANS Axiote 8	7-81	6-25	
GOODMANS Twin-axiote 8	8-84	6-95	
GOODMANS Axiom 10	9-26	7-50	
GOODMANS Axiom 80	27-29	22-75	
GOODMANS Axiom 201	14-45	10-45	
GOODMANS Axiom 401	17-36	13-95	
GOODMANS Twin Axiom 10	9-88	7-50	
GOODMANS Axiom 8P	5-35	4-05	
GOODMANS Axiom 10P	5-83	3-25	
GOODMANS Axiom 51	13-05	9-59	
GOODMANS Axiom 61	18-95	13-50	
GOODMANS Axiom 12P	12-37	9-59	
GOODMANS Axiom 15P	20-00	16-50	
GOODMANS Axiom 18P	34-00	25-95	
GOODMANS ARU172	4-50	3-25	
GOODMANS Trebas 100	8-60	5-58	
GOODMANS Trebas 5K/20XL	9-70	7-25	
GOODMANS Midax 650	12-95	8-50	

(OVER 1,520 sq. yds.)

# OVER 1000 ITEMS ALWAYS IN STOCK

## ALL FULLY GUARANTEED - WITH AFTER-SALES SERVICE

All items offered are brand new, latest models in manufacturers' sealed cartons

### COMPLETE HI-FI SYSTEMS

Completely wired, mounted and ready for use.

	Rec. Retail Price	Comet Price
GOODMANS Attenuator	3-55	2-25
GOODMANS Crossover Networks XO/950/5000	9-75	7-15
GOODMANS Crossover Networks XO/950	7-40	5-50
GOODMANS Crossover Networks XO/5000	2-65	1-60
WHARFEDALE 8in. Bronze/RS/DD	4-82	3-50
WHARFEDALE Super 8/RS/DD	8-19	6-75
WHARFEDALE Super 10/RS/DD	11-20	9-50
WHARFEDALE WMT1 Matching Transformer	0-84	0-70

#### HI-FI STEREO SYSTEMS COMPLETE

ALBA UA552	45-86	35-50
ALBA UA662	60-32	46-95
DECCA Sound 613	70-14	57-95
DECCA Sound 614	66-55	54-95
DECCA Sound 1204	89-44	72-95
DECCA Compact 3	119-56	103-95
ECKO SRG 609 with radio	35-44	29-95
ECKO ZUS with radio	159-29	99-00
FERGUSON 3422	84-80	65-95
FERGUSON 3423	114-15	89-95
FERGUSON 3425 with radio	140-10	108-00
FERGUSON 3450 with radio	72-40	59-95
FIDELITY UA2 Music Master	44-41	31-95
FIDELITY UA1 Music Master with radio	103-29	79-95

#### SPECIAL OFFER

GOODMANS Max-amp Stereo Amplifier, Goodmans Stereo-max AM/FM Tuner with Decoder, Pair of Goodmans Magnum K2 Spea- kers, Garrard A.P. 76 Turntable in base, complete with cover and Goldring G.800 Cartridge. Beauti- fully finished in Walnut	257-13	189-95
H.M.V. 204/5/6 with radio	198-30	155-95
HMV 242 with stereo radio	85-85	53-95
HMV 2450 with stereo radio	134-20	109-00
KB KA1250 complete with two 653 speakers	71-55	58-50
KB KA1250 complete with two 651 speakers	80-25	64-95
KB 2010 with radio and two 653 speakers	94-70	76-95
LEAK 30/Goldring/Wharfedale	182-65	142-95
LEAK 70/Thorens/Wharfedale	228-87	175-00
MARCONI Unit 3	64-80	64-95
MARCONI 4450 with radio	72-40	55-50
MARCONI 4452	76-00	55-95
METRO SOUND Stereo 1010 com- plete with speakers	79-34	55-95
PHILIPS 880/481/105	71-00	55-95
PHILIPS GF 823	47-80	38-95
PHILIPS GF 824	67-10	52-95
PHILIPS GF 833	67-10	52-95
PHILIPS GF 834	86-40	65-95
PHILIPS GF 417	96-06	69-95
TELETON 2580F with radio	72-40	53-95
TELETON STP 8-track Stereo System	54-75	48-00
TOSHIBA SP8507	245-00	175-00
ULTRA 6405	77-00	64-95

#### TAPE RECORDERS AND TAPE DECKS

AKAI 1710L 4-track Stereo	89-85	59-95
AKAI 1720L 4-track Stereo	83-73	65-95
AKAI 4000 D 4-track stereo deck	89-95	65-95
AKAI CR 80D 8-track stereo tape deck	91-55	76-95
AKAI CR80 8-track stereo recorder	110-83	96-95
AKAI X200D	145-95	115-00
AKAI 1800SD	153-00	119-00
AKAI 2000SD	289-00	234-95
BUSH Discacassette DC70	21-19	16-95
BUSH TP60 Cassette tape recorder	28-38	23-95

	Rec. Retail Price	Comet Price
BUSH TP70 Cassette, battery/mains tape recorder	28-91	23-50
FERGUSON 3245 Twin track	36-70	27-95
FERGUSON 3246 4-track	42-55	32-95
FERGUSON 3247 4-track	47-95	37-95
FERGUSON 3248 4-track	53-75	41-95
FERGUSON 3252 4-track	100-52	80-95
FERROGRAPH 702 2-track tape deck	220-22	185-00
FERROGRAPH 704/W 4-track tape deck	220-22	185-00
FERROGRAPH 722	256-52	209-00
FERROGRAPH 702 Dolby	272-25	229-00
FERROGRAPH 724	256-52	209-00
FERROGRAPH 722 Dolby	308-55	262-00
GRUNDIG C200 De Luxe Cassette	38-45	28-95
GRUNDIG TK 121 twin track	55-30	41-95
GRUNDIG TK 141 4-track	61-55	47-95
GRUNDIG TK 146 4-track Auto	67-25	51-95
GRUNDIG 222 stereo cassette	57-70	47-95
GRUNDIG TK 147 4-track Auto	93-35	74-95
MIDLAND TC 144 cassette	18-00	11-95
PHILIPS 2202 cassette	26-90	19-95
PHILIPS 2204 cassette, battery/mains	32-30	23-95
PHILIPS 2205 cassette tape recorder	41-60	33-50
PHILIPS 3302 cassette	23-05	17-50
PHILIPS 4303 new release	40-55	32-50
PHILIPS 4307 4-track	47-80	35-95
PHILIPS 4308 De Luxe 4-track	58-40	43-50
PHILIPS 4404 2-track stereo recorder	91-70	69-95
PHILIPS 4407 4-track stereo recorder	106-20	85-95
PHILIPS 4500 4-track stereo tape deck	121-65	94-95
PHILIPS 4408 4-track stereo	134-20	104-50
PHILIPS 2503 Cassette Stereo tape deck	52-05	41-95
PHILIPS 2400 stereo cassette less L/S	65-55	56-45
PYE Cassette Recorder/Radio 9000 battery/mains	43-86	35-95
TANDBERG 1841 4-track stereo tape deck	68-00	58-95
TANDBERG 3021X twin track stereo	107-00	91-00
TANDBERG 304X 4-track stereo	107-00	91-00
TANDBERG 4021X twin track stereo	174-00	145-00
TANDBERG 4041X 4-track stereo	174-00	145-00
TANDBERG 6041X 4-track stereo	188-00	158-00
TANDBERG 6021X twin track stereo	188-00	158-00
TELETON T110 cassette	26-75	14-95
TELETON TC110 cassette battery/ mains	26-79	18-95
TELETON TRC130 cassette with VHF/AM Radio, Batt./Mains, twin motors	40-31	27-95
TELETON 511 battery/mains		
TELETON FXB 510 D 4-track stereo	29-50	17-50
TOSHIBA GT 601V twin track	65-16	50-95
TOSHIBA 850 SA 4-track stereo tape deck	43-95	35-95
WHARFEDALE Dolby DC9 cas- sette stereo tape deck	91-50	47-95
	110-84	94-50

#### BASES AND COVERS

GARRARD WB1 Base	3-71	3-25
GARRARD WB4 Base	5-49	4-75
GARRARD SPC 1 Cover	3-60	2-95
GARRARD SPC 4 Cover	4-27	3-75
Special offer of Base and Cover to fit GARRARD SP25, SL55, SL65B and 3500	Special Price	4-00
GOLDRING Plinth 75	8-60	7-00
GOLDRING Plinth 69	4-50	7-00
GOLDRING Covers for 69P and 75P	4-48	3-75
THORENS TX25 (for TD125AB)	8-52	6-95
THORENS TX11 Cover	4-26	3-75
Base and Cover for TD 125	15-04	12-45
SME Plinth System 2000	41-36	30-50
MOTORBOARDS only	5-22	3-25

GOODMANS AUDIO SUITE, Goodmans Maxamp stereo ampli- fier, Goodmans stereomax AM/ FM Tuner with decoder, Pair of Goodmans Magnum K2 speakers, Garrard AP76 turntable in base, complete with cover and Gold- ring G800 Cartridge. Beautifully finished in walnut	257-13	169-95
--	--------	--------

GOLDRING 705P turntable complete with G850 Cartridge, Midland Tuner/Amp., Pair of Metro Sound 103 Speakers	99-56	69-95
---	-------	-------

GOODMANS Module 80 Tuner/ Amplifier, Garrard AP76 Turn- table with Goldring G800 Car- tridge and 2 Goodmans Minister Speakers	199-00	139-00
---	--------	--------

METRO SOUND 448 8-track stereo play-back unit complete with 2 HFS 10 Speakers	83-56	70-95
---	-------	-------

GOLDRING 705P turntable complete with G850 Cartridge, Teleton 206 Amplifier, pair of Keletron KN500 Speakers	77-00	49-95
---	-------	-------

TELETON STP 801 Stereo 8 track tape Audio system complete with speakers	54-75	48-00
---	-------	-------

GARRARD SP 25, Mk. III mounted in base, plinth and cover with GOLDRING G800 Cartridge, Teleton 206 Stereo Amplifier 12 watts RMS, and 2 KELETRON KN500 Speakers, each speaker is a 4 speaker system	88-33	58-95
---	-------	-------

PIONEER PL 12 turntable, Good- mans Maxamp, Shure M55E Car- tridge, 2 Keletron KN 700 speakers (each speaker cabinet contains 4 speakers)	144-38	105-00
---	--------	--------

GARRARD AP76 turntable com- plete with Goldring G800 Car- tridge, base and cover, Rogers Ravensbrook Amplifier in teak case and 2 Goodmans Minister Speakers	142-51	108-50
---	--------	--------

LEAK 30/THORENS/WHARFEDALE	182-65	142-95
----------------------------	--------	--------

GOLDRING GL 75P mounted in teak base with hinged perspex cover complete with GOLDRING G800E Cartridge, Leak Stereo 30 Plus Amplifier in Teak case, 2 GOODMANS Mezzo 3 Speakers	200-50	154-20
---	--------	--------

THORENS TD 150AB Mk. II with TX11 dust cover, SHURE M55E Cartridge, LEAK Stereo 70 Amplifier in Teak case, 2 Whar- fedale Dovedale 3 Speakers	226-87	175-00
---	--------	--------

THORENS TD 125AB Electronic Turntable complete with cover, SHURE V15-11 Cartridge, GOOD- MANS Maxamp, GOODMANS Stereomax AM/FM Tuner, 2 GOODMANS Magister Speakers	422-48	309-00
---	--------	--------

TELETON STP 801, Stereo 8 track Tape Audio Systems comp. with speakers	54-75	48-00
--	-------	-------

Complete Price List FREE on request!

## COMET HIGH FIDELITY DISCOUNT WAREHOUSES

(Dept. P.W.) Reservoir Rd., Clough Rd., Hull HU6 7QD Tel. 407066 and 407877

(Dept. P.W.) 68A Armley Rd. (Artist St.), Leeds LS12 2EE Tel. 32855

(Dept. P.W.) Teesway, Portrack Lane, North Teesside (5 lines) Tel. 66132/65218

(Dept. P.W.) Teesway, Portrack Lane, North Teesside Industrial Estate, Teesside, TS18 2RH

(Dept. P.W.) Heeley Road, Selly Oak, Birmingham Tel. 821-472 6181

Comet guarantees that all prices quoted are genuine. All items offered available at these prices at the time this issue closed for press.

Add 75p for postage, packing and insurance on all orders (Cartridges 20p) or, if Securicor delivery required, add £1.75 only.

Make cheques, Money Orders payable to "COMET".

Free  
Technical  
Advisory  
Service. If  
in doubt,  
ask us!



All in-stock items delivered by  
**SECURICOR**  
WITHIN 72 HOURS  
(Add £1.75 only for Securicor delivery)  
ALL GOODS FULLY INSURED AGAINST  
LOSS OR DAMAGE WHILST IN TRANSIT

Open daily to  
the public from  
9-0 A.M. until—  
  
5-30 P.M. MON.  
1-0 P.M. TUES.  
8-0 P.M. WED.  
8-0 P.M. THUR.  
8-0 P.M. FRI.  
5-30 P.M. SAT.  
  
Customers are  
welcome to call—  
Ample car parking  
facilities

# BENTLEY ACOUSTIC CORPORATION LTD.

38 CHALCOT ROAD, CHALK FARM, LONDON, N.W.1  
THE VALVE SPECIALISTS Telephone 01-721-9090

0A2	.30	6CB6A	.28	6B67GT	.33	128Q7GT	.50	5763	.50	EBF89	.27	EF98	.85	KT66	.90	PFL200	.53	UCH21	.60	AAZ13	.18	BCY38	.23	OA70	.15
0B2	.30	909	.78	68H7	.53	1487	1.15	AC2/PEN	.98	EC86	.63	EL32	.27	KT81	2.00	PL36	.47	UCH42	.60	AC107	.15	BCZ11	.33	OA73	.15
1A76GT	.33	6C18A	1.05	68J7	.85	19A95	.24	AC9/PEN/	.88	EC88	.96	EL84	.22	KTW61	.63	PL81	.44	UCH81	.30	AC113	.25	BF158	.39	OA79	.08
1B3GT	.37	6C88A	.50	68K7GT	.28	19G6	1.45	DD	.98	EC92	.85	EL85	.42	KTW62	.83	PL82	.50	UCH82	.33	AC127	.17	BF159	.25	OA81	.08
1HG3T	.33	6CH6	.38	68L7GT	.28	19P6	1.45	AC6/PEN/	.88	EC94	.85	EL86	.42	KTW63	.50	PL83	.33	UF41	.50	AC156	.20	BF173	.85	OA90	.13
1L4	.13	6CL6	.48	68M7GT	.88	20D4	1.05	AC6/PEN/	.88	EC98	1.50	EL86	.38	EL24	.46	MHLD6	.75	PL84	.30	UF42	.60	AC157	.25	OA91	.09
1N5GT	.37	6CM7	.50	6V6G	.17	20F2	6.05	AC/PEN(7)	.88	EC33	1.50	EL86	.38	EL25	1.00	N78	2.00	PL84	.30	UF42	.60	AC157	.25	OA91	.09
1R5	.27	6CU5	.50	6V6GT	.30	20L1	.98	AC/PEN(7)	.88	EC33	1.50	EL86	.38	EL26	.87	N309	.95	PL84	.30	UF42	.60	AC157	.25	OA91	.09
1B4	.22	6CW4	.88	6X4	.20	20P1	.88	AC/TH1	.50	EC33	1.50	EL86	.38	EL27	.87	N309	.95	PL84	.30	UF42	.60	AC157	.25	OA91	.09
1U4	.22	6DE7	.50	6X5GT	.25	20P3	.88	AC/TH1	.50	EC33	1.50	EL86	.38	EL28	.87	N309	.95	PL84	.30	UF42	.60	AC157	.25	OA91	.09
1U5	.48	6DT6	.50	7A7	.88	20P4	.89	AL60	.78	EC33	1.50	EL86	.38	EL29	.87	N309	.95	PL84	.30	UF42	.60	AC157	.25	OA91	.09
2D21	.35	6EW6	.55	7B6	.88	20P5	1.00	ATP4	.41	EC33	1.50	EL86	.38	EL30	.87	N309	.95	PL84	.30	UF42	.60	AC157	.25	OA91	.09
2GK5	.50	6F1	.59	7B7	.85	25A6G	.29	AZ1	.40	EC33	1.50	EL86	.38	EL31	.87	N309	.95	PL84	.30	UF42	.60	AC157	.25	OA91	.09
3D6	.19	6F6	.63	7C6	.80	25L6G	.22	AZ21	.40	EC33	1.50	EL86	.38	EL32	.87	N309	.95	PL84	.30	UF42	.60	AC157	.25	OA91	.09
3Q4	.38	6F6G	.25	7E7	.88	25Y5	.30	AZ41	.88	EC33	1.50	EL86	.38	EL33	.87	N309	.95	PL84	.30	UF42	.60	AC157	.25	OA91	.09
8Q5GT	.35	6F13	.33	7F7	.85	25Y6G	.43	CL33	.59	EC33	1.50	EL86	.38	EL34	.87	N309	.95	PL84	.30	UF42	.60	AC157	.25	OA91	.09
2B4	.27	6F14	.43	7Z4	.85	25Z4G	.30	CY1C	.53	EC33	1.50	EL86	.38	EL35	.87	N309	.95	PL84	.30	UF42	.60	AC157	.25	OA91	.09
3V4	.32	6F18	.45	9D7	.78	25Z5	.40	CY31	.31	EC33	1.50	EL86	.38	EL36	.87	N309	.95	PL84	.30	UF42	.60	AC157	.25	OA91	.09
4CB6	.50	6F23	.68	10C2	.50	25Z6G	.43	DAF91	.20	ECF80	.37	EF88	.48	EL37	.87	N309	.95	PL84	.30	UF42	.60	AC157	.25	OA91	.09
5C68	.50	6F24	.68	10D7	.50	30C1	.28	DAF96	.38	ECF82	.37	EF91	.53	EL38	.87	N309	.95	PL84	.30	UF42	.60	AC157	.25	OA91	.09
5V4G	.35	6F25	.68	10E9	.45	30C15	.60	D901	.14	ECF86	.85	EZ40	.40	EL39	.87	N309	.95	PL84	.30	UF42	.60	AC157	.25	OA91	.09
5Y8GT	.28	6F28	0.7	10F18	.35	30C17	.77	DF96	.38	ECF80A2	.18	EZ41	.42	EL40	.87	N309	.95	PL84	.30	UF42	.60	AC157	.25	OA91	.09
5Z4G	.35	6F32	.16	10LD11	.53	30C18	.60	DE76	.28	ECF81	.68	EZ80	.31	EL41	.87	N309	.95	PL84	.30	UF42	.60	AC157	.25	OA91	.09
6J30L2	.55	6GH8A	.50	10P13	.54	30F3	.70	DK40	.55	ECF82	.61	EZ81	.32	EL42	.87	N309	.95	PL84	.30	UF42	.60	AC157	.25	OA91	.09
6A8G	.33	6GK5	.50	10P14	1.10	30FL1	.60	DK92	.38	ECF81	.37	EZ90	.20	EL43	.87	N309	.95	PL84	.30	UF42	.60	AC157	.25	OA91	.09
6AC7	.15	6GK7	.50	12A6	.68	30FL2	.60	DE96	.38	ECF83	.39	FW4/800.75	.75	EL44	.87	N309	.95	PL84	.30	UF42	.60	AC157	.25	OA91	.09
6AG5	.25	6HG6T	.18	12A6G	.40	30FL12	.70	DI96	.38	ECF84	.34	FW4/800.75	.75	EL45	.87	N309	.95	PL84	.30	UF42	.60	AC157	.25	OA91	.09
6AJ9	.43	6JG5	.19	12AD6	.40	30FL14	.68	DM70	.30	ECL80	.30	GZ30	.35	EL46	.87	N309	.95	PL84	.30	UF42	.60	AC157	.25	OA91	.09
6AK5	.25	6JG6T	.25	12AE6	.48	30LI1	.29	DM71	.30	ECL82	.30	GZ32	.41	EL47	.87	N309	.95	PL84	.30	UF42	.60	AC157	.25	OA91	.09
6AM8A	.50	6J6	.18	12AT6	.23	30LI5	.59	DY87/6	.25	ECL83	.62	GZ33	.70	EL48	.87	N309	.95	PL84	.30	UF42	.60	AC157	.25	OA91	.09
6ANS	.49	6J7G	.24	12AT7	.16	30LI7	.69	DY802	.37	ECL84	.56	GZ34	.48	EL49	.87	N309	.95	PL84	.30	UF42	.60	AC157	.25	OA91	.09
6AQ5	.22	6J7GT	.38	12AU6	.21	30P4MR	.95	EB07	1.20	ECL85	.55	GZ37	.67	EL50	.87	N309	.95	PL84	.30	UF42	.60	AC157	.25	OA91	.09
6AR5	.30	6JU8A	.50	12AU7	.19	30P12	.69	EB3F	1.30	ECL86	.36	HAB80	.45	EL51	.87	N309	.95	PL84	.30	UF42	.60	AC157	.25	OA91	.09
6AU6	.18	6K7G	.18	12AV8	.23	30P19/	.69	EB8CC	.60	EF92	.63	HL42DD.40	.40	EL52	.87	N309	.95	PL84	.30	UF42	.60	AC157	.25	OA91	.09
6AV6	.30	6K8G	.18	12AX7	.22	30P4	.58	E92CC	.40	EF96	.38	HL41DD.98	.98	EL53	.87	N309	.95	PL84	.30	UF42	.60	AC157	.25	OA91	.09
6AW8A	.54	6L1	.96	12BA6	.30	30PL1	.59	E180F	.90	EF37A	.45	HL42DD.50	.50	EL54	.87	N309	.95	PL84	.30	UF42	.60	AC157	.25	OA91	.09
6AX4	.39	6L6GT	.39	12BB7	.27	30PL13	.75	E182CC1.18	.18	EF39	.40	HN309	1.40	EL55	.87	N309	.95	PL84	.30	UF42	.60	AC157	.25	OA91	.09
6B8G	.13	6L7GT	.63	12E1	.85	30PL14	.65	E1148	.58	EF40	.50	HVR2	.58	EL56	.87	N309	.95	PL84	.30	UF42	.60	AC157	.25	OA91	.09
6BA6	.20	6L15	.45	12F7GT	.33	35A3	.37	E1A50	.18	EF41	.86	HVR8A	.53	EL57	.87	N309	.95	PL84	.30	UF42	.60	AC157	.25	OA91	.09
6BC9	.50	6L19	1.38	12K5	.50	35L6GT	.42	EABC0	.30	EF44	.98	KT2	.25	EL58	.87	N309	.95	PL84	.30	UF42	.60	AC157	.25	OA91	.09
6BD6	.21	6LD90	.48	12K7GT	.34	35W4	.23	EAC91	.88	EF73	.75	KT44	1.00	EL59	.87	N309	.95	PL84	.30	UF42	.60	AC157	.25	OA91	.09
6BE6	.43	6N7GT	.48	12Q7GT	.28	3Z24GT	.24	EAF42	.48	EF80	.22	KT44	1.00	EL60	.87	N309	.95	PL84	.30	UF42	.60	AC157	.25	OA91	.09
6BF6	.39	6Q7	.48	12R7GT	.33	3Z26GT	.30	EB34	.20	EF83	.48	KT44	1.00	EL61	.87	N309	.95	PL84	.30	UF42	.60	AC157	.25	OA91	.09
6BQ7A	.38	6Q7G	.27	.40	6E8H5	.55	E291	.11	EF85	.28	KT44	1.00	EL62	.87	N309	.95	PL84	.30	UF42	.60	AC157	.25	OA91	.09	
6BR7	.79	6R7	.58	128C7	.35	50L6GT	.45	EB41	.48	EF86	.30	KT44	1.00	EL63	.87	N309	.95	PL84	.30	UF42	.60	AC157	.25	OA91	.09
6BZ8	.63	6R7G	.35	128G7	.23	85A2	.48	EB8C1	.33	EF89	.27	KT44	1.00	EL64	.87	N309	.95	PL84	.30	UF42	.60	AC157	.25	OA91	.09
6BW7	.55	6SA7GT	.35	128H7	.15	90C1	.59	EB91	.30	EF91	.17	KT44	1.00	EL65	.87	N309	.95	PL84	.30	UF42	.60	AC157	.25	OA91	.09
6BZ6	.31	6S7GT	.33	128K7	.24	5702	.80	EBF83	.38	EF97	.55	KT44	1.00	EL66	.87	N309	.95	PL84	.30	UF42	.60	AC157	.25	OA91	.09

# Give us six months, and we'll turn your hobby into a career.

You have a hobby for a very good reason. It gives you a lot of pleasure.

So if you can find a job that involves your hobby, chances are you'll enjoy your work more, and you'll do better work.


Now CDI can help you find such a job. A job where you'll be responsible for the maintenance of a computer installation. A job that pays well too. If you're interested in mechanics or electronics (without necessarily being a

mathematical genius), have a clear, logical mind and a will to work, then we can train you to be a Computer Engineer inside six months.

So give us a call. CDI. We're the Education Division of one of the world's largest computer manufacturers. And we have the experience to know if you can make it. A ten minute talk with us, and you could be on the way to spending the rest of your life with your hobby.

It's quicker and easier to phone, but if you prefer, send this coupon to: Control Data Institute, Wells House, 77 Wells Street, London, W.1.  
Please give me further information.

Name \_\_\_\_\_  
Address \_\_\_\_\_  
Age \_\_\_\_\_ Phone \_\_\_\_\_ SK1

**CONTROL DATA INSTITUTE**   
The Education Division of one of the world's largest Computer manufacturers.



# cut out this coupon and answer your soldering problems



### SK1 SOLDERING KIT

In rigid plastic "tool box" containing Model CN - 15 watts - 240 volts miniature iron fitted  $\frac{3}{16}$ " bit. Spare bits  $\frac{3}{32}$ " and  $\frac{3}{32}$ ". Reel of resin-cored solder, heat sink, cleaning pad, stand and booklet "How to Solder".

£2.75



### SK2 SOLDERING KIT

In polystyrene pack, containing 15 watt miniature soldering iron, 240 volts fitted with  $\frac{3}{16}$ " bit, 2 spare bits  $\frac{5}{32}$ " and  $\frac{3}{32}$ ". Coil of resin-cored solder, heat sink, 1A fuse and booklet "How to Solder".


£2.40



Model CN 240/2  
- 15 watts  
- 240 volts

Fitted with nickel plated  $\frac{3}{32}$ " bit and packed in handy transparent box.


£1.70

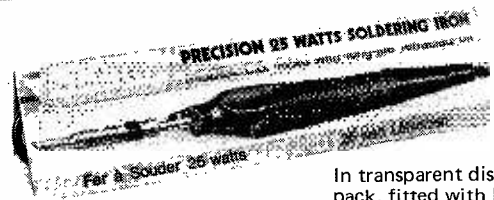

ES240 D 25 watt  
soldering iron

In transparent display pack, fitted with long life iron-coated bit  $\frac{1}{8}$ " diam. Interchangeable spare bits  $\frac{3}{32}$ ",  $\frac{1}{16}$ ",  $\frac{1}{4}$ " (extra) available. Improved design to ensure strong and reliable high speed iron. Heats up in 2 minutes.

£1.83

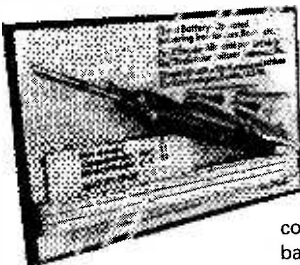

### M.E.S. Battery-operated 12 volt soldering iron

Complete with 15 ft (4.50m) lead, 2 heavy gauge clips for instant

connection to car battery and a guide 'How to Solder'.

Packed in strong plastic wallet.

Send me  
kit(s)

£1.95



from electrical and radio shops or by Free Post (No stamp required) from ANTEX Ltd. FREE POST. PLYMOUTH, PL1 1BR  
Tel: (0752) 67377/8

Please send the ANTEX colour catalogue.

Please send the following:

I enclose cheque / P.O. / Cash (Giro No. 2581000)

NAME

ADDRESS

PW11

# Music at midnight




Midnight is a time for listening. Let the music be as late and as loud as you like; with headphones, it disturbs no one. Let the headphones be A.K.G. and you will find the quality staggeringly good. Made by a company whose professional microphones are known throughout the world and much used in this country, A.K.G. stereo headphones reflect the same fine quality of design and meticulous manufacture. They are just about as good as anything you can buy at any price. Go to the dealer displaying the A.K.G. Superhead and hear for yourself, without obligation. Shown here, Model K.60 R.R.P. £15.00

# A K G

A.K.G. Equipment Ltd.

Eardley House

182-184 Campden Hill Rd. W8 7AS

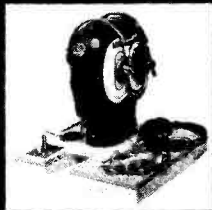

## JERMYN 50p BARGAIN PACKS

All fully coded, all from well-known manufacturers and now available, while stocks last, at better than bulk buyer's prices! Cash with order only.

### THIS MONTH:

<b>1N4148</b> Signal Diode (= 1N914)	18 for 50p
<b>1N5060</b> 1 Amp Rectifier 400V (= A14D) avalanche protected	7 for 50p
<b>2N2926</b> NPN Silicon Transistor (Red) hfe 55 - 110	8 for 50p
<b>2N2923</b> NPN Silicon Transistor hfe 90 - 180	7 for 50p
<b>2N3721</b> Gen. Purpose Transistor	8 for 50p

Post and packing 10p for 1 or 2 packs; 3 packs or more post free.

Order any quantity, till sold (but we regret packs cannot be subdivided).



P.O. or Cheque payable Jermyrn Industries,  
Vestry Estate, Sevenoaks, Kent.

## BAKER 12in. REGENT

An inexpensive unit for the beginner in high fidelity and for general purposes. May be used to advantage with any Radio, Amplifier or Television receiver.


Maximum Power 15 watts  
Bass Resonance 45 c.p.s.  
Flux Density 12,000 gauss  
Voice Coil impedance  
3 or 8 or 15 ohm models  
Useful response  
45-13,000 c.p.s.

Nett weight 5 lbs.

GUITAR MODEL "GROUP 25" £7

25 watt rating  
Latest catalogue 5p with enclosure plans.

# £7

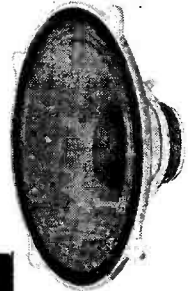

## Baker Reproducers Ltd

Bensham Manor Road Passage, Thornton Heath, Surrey. 01-684-1665

When in LUTON, BEDS, you must visit the . . .

### SELF-SERVICE RADIO COMPONENTS SHOP

Serve yourself from a selection of 1,200 boxes of Manufacturer's surplus stocks and save money.

9 a.m. to 5.30 p.m. every day.

Closed all day Wednesday.

### SURPLECTRONICS

216 LEAGRAVE ROAD, LUTON, BEDS

# everyday electronics

**No.1**

OUT FRIDAY  
OCTOBER 22


A NEW MAGAZINE  
BRINGING A FASCINATING  
HOBBY TO EVERYONE  
PROJECTS EASY TO CONSTRUCT  
THEORY SIMPLY EXPLAINED




This exciting new magazine will present easy-to-follow, step-by-step illustrated articles on useful and imaginative electronic gadgets for the home, car and other hobby applications. Theory will be simply explained. It will be edited by the expert team who have made "Practical Electronics" so successful.

- *Have fun building this super portable record player.*
- *HOME SENTINEL . . . excellent deterrent to burglars! Lights up your home as night falls!*
- *A must for motorists . . . make your own windscreen wiper control!*
- **FEATURES FROM NO. 1**  
*"TEACH-IN" . . . important series outlining the theory and practical techniques involved in electronics.*  
*"SHOP TALK" . . . advice on buying components and equipment.*  
*"ELECTRONICS PAST AND PRESENT" . . . illustrated account of the electronics story to date.*

## FREE

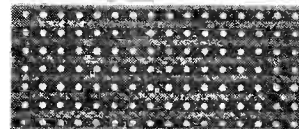

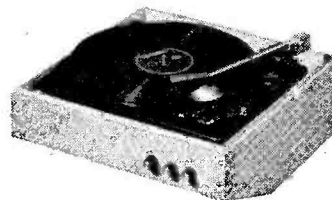A piece of Printed Circuit Board . . . a base on which two of the projects can be constructed.



**ORDER THIS GREAT NEW MAGAZINE \_ ONLY 15p**

# 28watts, r.m.s. 40Hz to 40kHz $\pm$ 3dB



## Viscount III Audio Suite complete £49

There are two stereo amplifiers—the R100 for ceramic cartridges, the R101 for magnetic and ceramic. Both incorporate FETs (FIELD EFFECT TRANSISTORS), just like top-priced units. FETs give you more of the signal you want, and almost none of the background hiss you don't. Both units have a jack socket to plug in headphones and there's a separate output for tape recorder. Filters (an unusual feature in this price range) and tone controls give a wide range of bass and treble adjustment which compensate for input deficiencies and domestic acoustic conditions.

### PRICES SYSTEM 1

Viscount III R101 amplifier	£22.00+90p p&p
2 x Duo Type II speakers,	£14.00+£2 p&p
Garrard SP25 Mk. III with MAG.	
cartridge, plinth and cover	£23.00+£1.50
	p&p
<b>Total</b>	<b>£59.00</b>

Available complete for only **£52.00+£3.50 p&p**

### SYSTEM 2

Viscount R101 amplifier	£22.00+90p p&p
2 x Duo Type III speakers	£32.00+ £3 p&p
Garrard SP25 Mk. III with MAG.	
cartridge, plinth and cover	£23.00+£1.50
	p&p
<b>Total</b>	<b>£77.00</b>

Available complete for **£69+£4 p&p**

### SYSTEM 3

Viscount III Amplifier R100	£17.00+90p p&p
2 x Duo Type II speakers, pair	£14.00+£2 p&p
Garrard SP25 Mk. III with CER. diamond	
cartridge, plinth and cover	£21.00+£1.50
	p&p
<b>Total</b>	<b>£52.00</b>

Available complete for only **£49.00+£3.50 p&p**

### SPEAKERS Duo Type II

Size approx 17" x 10 $\frac{1}{2}$ " x 6 $\frac{1}{2}$ ". Drive unit 13" x 8" with parasitic tweeter. Max. power 10 watts. 3 ohms. Simulated Teak cabinet. £14 pair+£2 p&p.

Duo Type III Size approx 23 $\frac{1}{2}$ " x 11 $\frac{1}{2}$ " x 9 $\frac{1}{2}$ ". Drive unit 13 $\frac{1}{2}$ " x 8 $\frac{1}{2}$ " with H.F. speaker. Max. power 20 watts at 3 ohms. Freq. range 20Hz to 20kHz. Teak veneer cabinet. £32 pair+£3 p&p.

### SPECIFICATION R101


14 watts per channel into 3 to 4 ohms. Total distortion @ 10W @ 1kHz 0.1%. P.U.1 (for ceramic cartridges) 150mV into 3 Meg. P.U.2 (for magnetic cartridges) 4mV @ 1kHz into 47K. equalised within  $\pm$  1dB R.I.A.A. Radio 150mV into 220K. (Sensitivities given at full power). Tape out facilities; headphone socket, power out 250mV per channel. *Tone controls and filter characteristics.* Bass: +12dB to -17dB @ 60Hz. Bass filter: 6dB per octave cut. Treble control: treble +12dB to -12dB @ 15kHz. Treble filter: 12dB per octave. *Signal to noise ratio:* (all controls at max) R101—P.U.1 and radio—65dB. P.U.2. —58dB. R100 same as R101 but P.U.2 (for crystal cartridges) 450mV into 3 Meg. *Cross talk* better than -35dB on all inputs. *Overload characteristics* better than 26dB on all inputs. Size approx 13 $\frac{1}{2}$ " x 9" x 3 $\frac{1}{2}$ ".

# R+TV

Radio and TV Components (Acton) Ltd. 21c High Street, Acton, London W3 6NG  
323 Edgware Road, London, W.2. Mail orders to Acton. Terms C.W.O. All enquiries S.A.E.  
Goods not despatched outside U.K.

# SOUND 50

50 WATT AMPLIFIER & SPEAKER SYSTEM

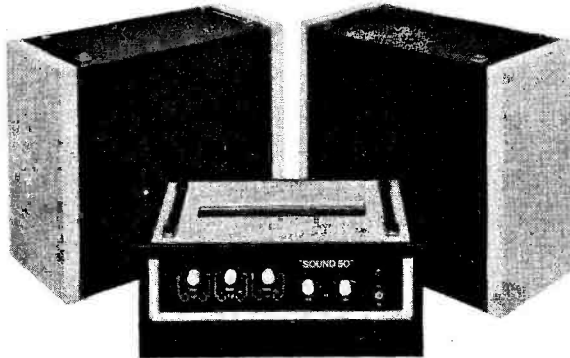

The Sound Fifty valve amplifier and speakers are sturdily constructed with smart housings and thoroughly tested electronics. They are designed to last—to withstand the knocks and bumps of life on the road. Built for the small and medium sized gig, they are easy to handle and quick to set up and can be relied upon to come over with all the quality and power you need.

**Output Power:** 45 watts R.M.S. (Sine wave drive). **Frequency response:** -3dB points 30Hz at 18KHz. **Total distortion:** less than 2% at rated output. **Signal to noise ratio:** better than 60dB.

**Speaker Impedance:** 3, 8 or 15 ohms. **Bass Control Range:** ± 13dB at 60Hz. **Treble Control Range:** ± 12dB at 10 KHz. **Inputs:** 4 inputs at 5mV into 470K. Each pair of inputs controlled by separate volume control. 2 inputs at 200mV into 470K.

To protect the output valves, the incorporated fail safe circuit will enable the amplifier to be used at half power.

**SPEAKERS!** Size 20" x 20" x 10" incorporating 12" heavy duty 25 watt high flux, quality loudspeaker with cast frame. Cabinets attractively finished in two tone colour scheme—Black and grey.

**COMPLETE SYSTEM £50** Plus £6 P. & P.  
Sound 50 amp and 2 speakers

or available separately.

Amplifier £28.50 plus £1.50 P. & P.  
Speakers £12.50 each plus £2.25 P. & P.

## THE ELEGANT SEVEN Mk. III

(350m W Output)




7 transistor fully-tunable M.W.—L.W. superhet portable. Set of parts. Complete with all components, including ready etched and drilled printed circuit board—back printed for foolproof construction.

**MAINS POWER PACK KIT:** 75p extra.

**Price £5.25 plus 50p. P. & P.**

**Circuit 13p FREE WITH PARTS.**

## THE DORSET (600m W Output)

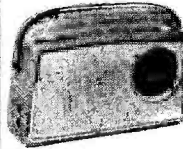

7-transistor fully tunable M.W.—L.W. superhet portable. Set of parts. The latest modulated and pre-alignment techniques make this simple to build. **Sizes:** 12 x 8 x 3in.

**Price £5.25 plus 50p P. & P.**

**Circuit 13p FREE WITH PARTS**

## CONTINENTAL 4 TRACK, 3 SPEED TAPE DECK



with high impedance heads

R.C. 74 tape deck. Three speeds—7½, 3½ and 1½ ips.


4-track record/playback head. Plus 4-track erase head. Positive pressure pad system. Takes any tape spool up to and including 7". The R.C. 74 is driven by a powerful 200/250V 50-cycle A.C. motor. A heavy, accurately balanced, flywheel brings wow and flutter levels down to approx. 0.3% total at 3½ and 7½ ips. Fast rewind in both directions.

Controls couldn't be simpler! Just five push buttons that interlock to cut out accidental tape damage. Efficient servo-action type braking. Easy drop-in tape loading.

The R.C. 74 comes with an attractive moulded deck cover, which has positions for tone and volume controls. The unit is built into a rigid die-cast frame, and overall size of the whole unit is 12½ x 11½ x 6 inches. Every single deck fully tested before dispatch. Spools not supplied.

**Price complete £15.00. Plus 75p P. & P.**

## RELIANT mk. IV

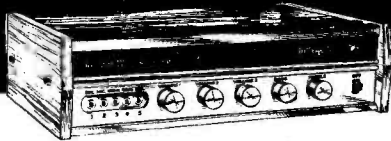

Provides a high standard of sound reproduction, with full mixing facilities. It's versatility makes it suitable for: Discotheque, P.A., Home Entertainment Applications, etc.

- ★ Five Electronically Mixed Inputs
- ★ Three Individual Mixing Controls
- ★ Separate base and treble controls common to all five inputs
- ★ Mixer employing F.E.T. (Field Effect Transistor)
- ★ Solid State Circuitry ★ Attractive Styling

**£9.50** plus P. & P. 60p.

**INPUTS:**—1. Crystal Mic or Guitar 8mV. 2. Moving coil Mic or Guitar 8mV. Inputs 3, 4 & 5 are suitable for a wide range of medium output equipment (Gram. Tuner, Monitor, Organ, etc.). All 250mV sensitivity.

**CONTROLS:**—3 Volume controls. Bass control range: 13db @ 60 Hz. Treble control range ±12db @ 15KHz. Separate ON/OFF Switch. Neon Indicator.

**POWER OUTPUT:**—12 Watts R.M.S. Into 3 to 4 ohms speaker

**SIGNAL/NOISE:**—Better than -60db on inputs 3, 4 and 5 & -50db on 1 & 2

**SUPPLY:**—220 - 250 AC Mains. **SIZE:**—12½" x 6" x 3½"

## TOURIST

MARK 3

## CAR RADIO



### ALL TRANSISTOR

Beautifully designed to blend with the interiors of all cars. Permeability tuning and long wave loading coils ensure excellent tracking, sensitivity and selectivity on both wave bands. R.F. sensitivity at 1MHz is better than 8 micro volts. Power output into 3 ohm speaker is 3 watts. Pre-aligned I.F. module and tuner together with comprehensive instructions guarantees success first time. 12 volts negative or positive earth. Size 7in x 2in x 4½in deep.

### SET OF PARTS

**£6.30**

plus P. & P. 50p.

Circuit diagram 13p. Free with parts  
Speaker, baffle and fixing kit £1.25  
extra plus 25p. p. & p. Postage free  
when ordered with parts.

See previous page  
for address

RADIO & TV COMPONENTS  
**R+TV**  
(ACTON) LIMITED





## High Salary A Dream House A New Car And A Secure Future

Get into the Computer Industry the fast and easy way.

Now for the first time, anybody (no special qualifications are needed) can train outside the computer industry for an exciting career as a **computer operator in only 4 weeks** — and can earn £2,000 ++ p.a.

How? We are the only commercial training organisation in the U.K. permitted to use the famous 'Eduputer'.

**JOBS GALORE!** 144,000 new operators will be needed over the next five years alone. And the moment you qualify our exclusive computer appointments bureau introduces you to computer users everywhere. This is your big opportunity to get out of a rut and into the world's fastest growing industry. Find out more **FREE** and without obligation by posting this coupon **TO-DAY**.



### London Computer Operators Training Centre

**C20**, Oxford House, 9/15, Oxford Street, London, W1.  
Telephone: 01-734 2874  
127/131 The Piazza, Dept. **C20**, Piccadilly Plaza,  
Manchester 1. Telephone: 061-236 2935.

Please send me your **FREE** illustrated brochure on exclusive Eduputer 'hands on' training for computer operating.

Name \_\_\_\_\_

Address \_\_\_\_\_

Tel \_\_\_\_\_

# WICKS FOR BARGAINS

## E.A. STEREO AMPLIFIER:

5 watts per channel; In attractive afromosia veneered sleeve. Controls: On-off volume: Bass: Treble: Balance: Selector: Headphone Jack. Ceramic or Magnetic PU. Radio and Tape Inputs: Tape output and speaker output. Fully guaranteed 12 months parts. 6 months free service. Size 14½"W x 9½"D x 45"H approx. **£16-50 inc. post.**

- **Guaranteed all brand new best quality goods. No rubbish.**
- **Mail order only.**
- **All enquiries SAE please.**

## 3 WAY SPEAKER SYSTEM:

8" twin cone Bass speaker and 3" tweeter, fitted in extremely elegant teak veneered cabinet. Size : 18½"W x 11½"D x 10"H. 8 ohms handle 10 watts. **£7-50 inc. Carr.**

## GARRARD OFFERS

**Garrard SP25 Mk III** (Rec. Price (£15-85) **Our Price £11-25.** Carr. & Ins. 50p.

**Garrard SP25 Mk III** ready wired in beautiful teak plinth with tinted perspex cover. (Fitted with 5-pin DIN plug or phono plugs—state choice) (Rec. Price £23-19) **Our Price £16.** Carr. & Ins. 75p.

Or with choice of fitted cartridges.

**SP25 Mk III/Sonotone 9TAHC** (Rec. Price £27-29) **Our Price £18.** Carr. & Ins. 75p.

**SP25 Mk III/Shure M3DM** (Rec. Price £31-02) **Our Price £20.** Carr. & Ins. 75p.

**SP25 Mk III/Goldring G800** (Rec. Price £36-19) **Our Price £21.** Carr. & Ins. 75p.

**SP25 Mk III/Shure M55E** (Rec. Price £36-16) **Our Price £21.** Carr. & Ins. 75p.

**Note!** Garrard **SL65B** (Automatic Changer version of **SP25 Mk III**) alternatively supplied—please add £3 to above prices.

**Garrard AP76** (Rec. Price £27-85) **Our Price £18-85.** Carr. & Ins. 50p.

**Garrard AP76** ready wired in beautiful teak plinth with perspex cover (fitted with 5 pin DIN or Phono plugs).

Please state choice. (Rec. Price £39-85). **Our Price £24-94** Carr. & Ins. 75p.

## OR WITH CHOICE OF FITTED CARTRIDGES.

**Garrard AP76/Shure M3D** (Rec. Price £47-26) **Our Price £28-94.** Carr. & Ins. 75p.

**Garrard AP76/Shure M55E** (Rec. Price £52-82). **Our Price £31-35.** Carr. & Ins. 75p.

**Garrard AP76/Goldring G800** (Rec. Price £52-82) **Our Price £31-35.** Carr. & Ins. 75p.

**Garrard 2025TC** fitted with stereo/mono cartridge. £8-99. Carr. Paid.

## TEAK PLINTH & PERSPEX COVER

Ready cut to take 2025TC, SP25 III, SL65B available at **£4-99.** Carr. & Ins. 35p.

## CARTRIDGES (All with diamond stylus)

**Sonotone 9TAHC** dia. Rec. Price £4-10. **Our Price £1-99**

**Shure M3DM** (Rec. Price £7-41) **Our Price £4-87.**

**Shure M55E** (Rec. Price £12-97)

**Our Price £9-00.**

**Goldring 800** (Rec. Price £13-00)

**Our Price £7-50.**

**Goldring 800 H** (Rec. Price £10-69)

**Our Price £6-99.**

P & P 18p any type

**Special Offer!**  
Grundig GDM312  
Dynamic Microphones. List £7.35  
**OUR PRICE £3.**  
P & P 30p

**Hi-Fi Stereo Headphones**  
(Value £5-00)  
Only £2-25 inc. post.

**Speaker Cloth**  
Best quality. Width 36". Under half price at 55p per yd. Black with gold fleck; will blend with any room setting. End of stock line, yds and yds must go.

## Plugs, Sockets and Leads.

Phono plugs; 3p each  
30p per dozen.  
2 pin Din sprk. plugs  
10p each.  
3 pin Din plugs.  
15p each  
5 pin Din plugs.  
15p each.  
5 pin Din sockets (chassis) 7p each.  
Stereo Jack Sockets c/cct. 13p each.  
Phono sockets (chassis) 2 way 3p; 3 way 4p; 4 way 5p.  
6ft. stereo lead 5 pin Din to open end. 45p  
6ft. stereo lead 2 phono to open end. 37p  
12ft. sprk. lead 2 pin Din to open end. 40p.  
Please add P & P5p.

## 100 Mixed Resistors

½ watt 10% all best quality (no ex government) 40p.

## Pots

100K x 100K lns & Logs. stereo. 35p inc. post.  
100K DP switch stereo, log. 45p inc. post.  
50K single Balance. 15p inc. post.

**4 B.A. brass nuts** 50 for 25p inc. post.

## Speaker cabinets

Attractively veneered in afromosia, black front. Size approx. 7½"W x 9½"D x 4½"H. Ready cut to take 8" x 5" speaker. **£1-99.** P. & P. 12p.

**D. T. WICKS & CO.** 49 North Station Rd, Colchester, Essex.

Tel: (0206) 78807



**C**  
**H**OME RADIO  
**H**OME RADIO  
**P**  
**H**OME RADIO  
**H**OME RADIO  
**N**  
**H**OME RADIO  
**E**  
**H**OME RADIO  
**T**  
**S**

**HOME RADIO (Components) LTD.**  
 Dept. PW, 234-240 London Rd.,  
 Mitcham, CR4 3HD. 01-648 8422

**When you think  
 of COMPONENTS  
 think of HOME RADIO**

Some things in life are just about inseparable—eggs and bacon, sausage and mash, Tweedle Dum and Tweedle Dee! Think of one and you think of the other. That's how thousands of radio and electronic enthusiasts think of Components and Home Radio Ltd. When they need the first they automatically contact the second. They simply flip through their Home Radio Catalogue, locate the items they need and telephone or post their order. If you have not yet experienced the simplicity and satisfaction of linking Components and Home Radio, why not make a start now? First of all you'll need the catalogue . . . in its 315 pages are listed more than 8,000 components, over 1,500 of them illustrated. Every copy contains 10 vouchers, each worth 5p when used as instructed. The catalogue costs 70p including postage and packing. Drop us a line or use the coupon below.

**POST THIS  
 COUPON  
 with your  
 cheque or  
 postal order  
 for 70p**



Please write your Name and Address in block capitals.

Name .....

Address .....

.....

**HOME RADIO (Components) LTD.**  
 Dept. PW, 234-240 London Rd., Mitcham, CR4 3HD



**24-hour  
 Phone  
 Service.  
 Ring  
 01-648 8422**

**Ask for  
 details of  
 our Credit  
 Account  
 Service.**

The price of 70p applies only to catalogues purchased by customers in the U.K. and to BFPO addresses.

# PRACTICAL WIRELESS

VOL 47 NO 7

Issue 777

NOVEMBER 1971

## Evolution of Audio

IT has been a long haul since the days when a pair of PX4's in push-pull represented the last word in "quality". Although the search for greater realism continues, and is reflected in the steady flow of improved products, the industry itself and its approach to marketing is undergoing fundamental changes.

For some years, hi-fi has revolved around a kind of cottage industry, the highest quality products coming from small, highly specialised companies. More recently, however, the big boys have been getting into the act. Generally speaking they had previously been unable to compete because mass production is incompatible with the "luxury trade" associated with products for the connoisseur.

Things, however, are changing. In the first place, the minnows are being swallowed by the whales so that high specification equipment can still be made but with the backing and resources of the bigger parent company. Secondly, hi-fi is now no longer the sole province of the more affluent and this has led to a huge market in so-called mid-fi—not the equipment for the more fastidious but representing a very fair sound at a reasonable price. And, thirdly, developing techniques and new devices such as ICs are making it more feasible to produce equipment of quality in greater quantity and within narrower tolerances.

But although there is now a vast selection of audio products to suit all pockets, there is a potential danger. The phenomenal boom in hi-fi is probably past its peak, although the industry as a whole continues to grow, and a slowing down seems to be inevitable. This will again put the pressure on reducing costs as the market cools down.

Largs of Holborn, a paradise for audio types, with a large auditorium and their famous £5,000 comparator, is already a casualty. David A. Larg says that a combination of over-heads and competition from undercutting competitors "who offer neither the listening and demonstration facilities nor the installation advice and after sales service of Largs" have forced the company to close down.

The specialist dealer offering the kind of service and facilities expected by the discerning enthusiast is, of course, at a disadvantage when facing dealers offering discounted goods albeit with little service. But this is the trend and if manufacturers are also forced to keep their eyes more on the ledgers than the quality then customers are in for a leaner time.

Let us hope, therefore, that in its evolution, audio will not retreat from its present pinnacle and degenerate into the cheap-and-nasty take-it-or-leave-it standards which have been the fate of other modern industries.

W. N. STEVENS—*Editor.*

## NEWS AND COMMENT

Leader	579
News . . . News . . . News . . .	580
Electronotes by <i>S. Ginsberg</i>	590
MW Column by <i>Charles Molloy</i>	601
Practically Wireless by <i>Henry</i>	617
On the Short Waves by <i>Malcolm Connah</i> and <i>David Gibson, G3JDG</i>	629

## CONSTRUCTIONAL

2-Octave Miniature Organ Part 1, by <i>F. C. Judd</i>	593
Comprehensive Multi-Band Receiver, Part 1 by <i>F. G. Rayer, G3OGR</i>	604
Digital Frequency Counter/Timer, Part 3, by <i>John Thornton Lawrence, GW3JGA</i>	613
Modular Audio Mixing System, Part 2 by <i>F. C. Judd</i>	619
Basic Signal Generator by <i>R. H. Longden</i>	622
Take 20, No. 31, General Purpose Audio Amplifier, by <i>Julian Anderson</i>	633

## OTHER FEATURES

Treasure Traced	602
Transistor Circuitry for Beginners, Part 2, by <i>H. W. Hellyer</i>	608
Going Back, by <i>Colin Riches</i> and <i>Arthur Dow</i>	618

## SPECIAL FEATURE

What to look for at the Audio Fair by <i>Donald Aldous</i>	582
---	-----

**DECEMBER ISSUE WILL BE  
PUBLISHED ON NOVEMBER 5th**

©IPC Magazines Limited 1971. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected, and reproduction or imitations in whole or in part are expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices are those current as we go to press. All correspondence intended for the Editor should be addressed to Fleetway House, Farringdon Street, London, EC4A 4AD. Queries must be accompanied by a stamped, addressed envelope. Address correspondence regarding advertisements to Advertisement Manager, Fleetway House, Farringdon Street, London, EC4A 4AD.

# NEWS... NEWS... NEWS...

## Project 605


Sinclair Radionics Limited, announce the introduction of Project 605, a stereo system designed for the do-it-yourself enthusiast who does not have any special audio or electrical knowledge.

Based on four of the Sinclair Project 60 modules, Project 605 has an additional unit—Masterlink—through which all internal connections are routed by means of push-on tags already fitted to wires of the correct length—soldering is completely eliminated.


In the very comprehensive and extensively illustrated twelve page instruction book which is included in every Project 605 pack there are full details of tested installations in plinths of some of the major manufacturers of record players.

The Project 605 pack contains:—two Z.30 power amplifiers; one Stereo 60 pre-amplifier and control unit; one PZ5 power supply; one Masterlink connector unit with all necessary inter-connecting wires tagged at each end; twelve page Instruction Book. The suggested retail price is £29.95.

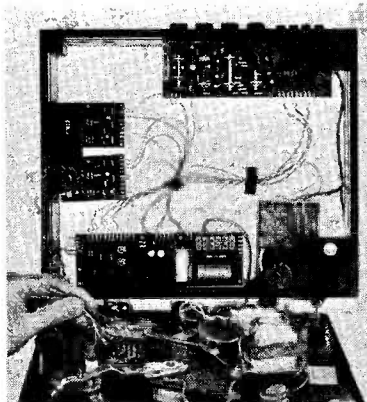Project 605 and all other Sinclair products are available from retailers in all parts of the Country or direct from the Company. The guarantee which extends over two years is direct with Sinclair who perform all service and repair work in their own large Service Department. *Sinclair Radionics Limited, London Road, St. Ives, Huntingdonshire, PE17 4HJ.*



## The PianoMate

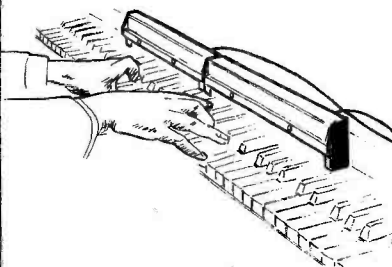

This device transforms any piano, whatever its age or condition into four octaves of blending electronic chords.

There are two double octave units that are simply placed onto the back of the piano keyboard *without any permanent fixing.*

These keyboard units (A) are then plugged into the 'Master control Unit' (B) which in turn is plugged into a power socket.

A Tone Selector Switch provides three different tone colours which include a 'Flute' sound which is ideal for standard tunes or ballads. A second tone is that of a Church Organ, the third has a 'Jazz Band' sound which is suitable for Latin American or Pop Music.

A two speed Vibrato Control provides a further variation of tone colours.

There is a Level Control giving predominance to either the Bass or Treble keyboard unit.

An Input Socket is also provided for those wishing to plug in a microphone or other instrument, or to amplify the piano itself.

A further socket is provided for a foot volume or Waa Waa pedal.

The PianoMate is completely tuneable via a single control for pianos which may be out of pitch by as much as a semi-tone.


It is possible to play the PianoMate without a piano at all. One would do this by using a dummy or practice keyboard. This would provide all the electronic variations, without of course the blending qualities of the piano.

The price of the PianoMate complete with Foot Volume Control will be £69.00, and it will be in production January 1972. *Dubreq Studios Limited, 249/289 Cricklewood Broadway, London NW2 6NX Tel : 01-450 5475.*


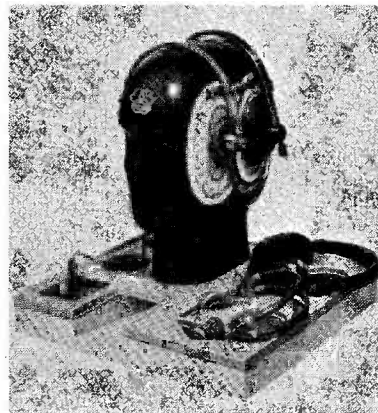
## A.K.G. Superhead

A.K.G. announce the introduction of their 'Superhead'. This is a novel demonstration unit which will be found at many A.K.G. retail stockists. It comprises a large life size black robot-like head with two faces, mounted on an orange coloured base. On this 'Superhead' unit are three or four different types of A.K.G. headphones which can be listened to instantly and judged for personal preference. This most unusual yet very helpful device will be found at dealers displaying an orange and black poster announcing that they have an A.K.G. 'Superhead' on demonstration inside.







# NEWS... NEWS... NEWS...

## SGS Module

SGS have entered the module market for the first time with their EA1000 unit. A compact solid-state audio amplifier assembled on a printed-circuit board, it is capable of delivering a minimum output power of 3W into a 16Ω load from a 24V supply.

The amplifier has been designed around the proven TAA621 monolithic silicon integrated circuit which contains all the active stages. The careful choice of associated components and of layout has given the unit considerable flexibility making it suitable for a wide range of applications at various supply voltages, load impedances and power outputs. Provision has also been made to alter the negative feedback and to vary the frequency response.

As a guide to obtaining the highest possible standards of performance from the EA1000 module, a 12 page handbook has been prepared which includes detailed information on its function, characteristics, and a number of applications. It includes a scheme for a stereophonic record player complete with volume, tone and balance controls. This publication is immediately available, price 10p. *SGS (United Kingdom) Ltd, Planar House, Walton Street, Aylesbury, Bucks.*

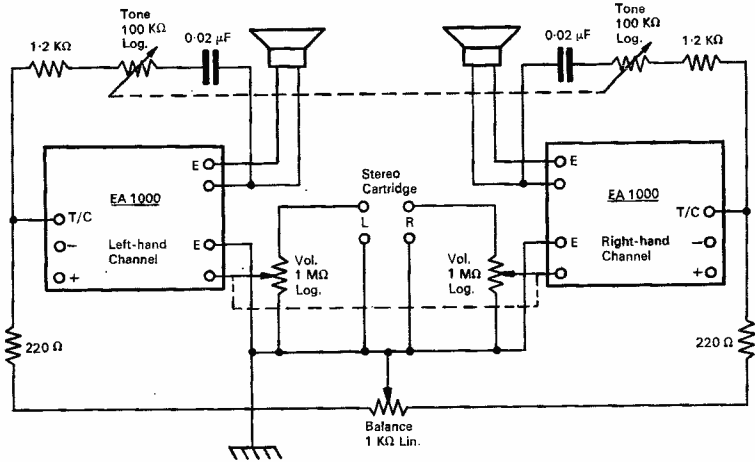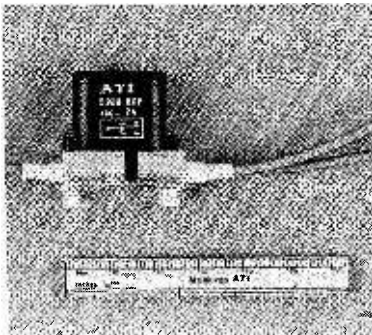

A typical application of the EA1000 in a stereophonic record player.

## Co-Axial Relays

McMurdo are extending their range of components, marketed under arrangement with Alliance Technique Industrielle of France, by the introduction of a miniature co-axial relay.

For frequencies up to 500MHz there are versions for PCB or chassis mounting. Three types are available—Type R has fixings, inputs and outputs on a 2.5 mm grid for PCB mounting. In Type RC the fixings and supply are PCB mounted whilst the h.f. circuits are fed via a co-axial cable.

For the chassis mounted version Type RCP (illustrated) the supply connections are by solder tags and those to the h.f. circuits by co-axial cable.


Supply voltage is either 12 or 24V d.c. at 1 Watt. The impedance is 50 ohms, VSWR is less than 1.15 and the cross talk at 300MHz is 45dB. Dimensions are length 26.8 mm (1.06in), height 24.8 mm (0.98in), width 10 mm (0.39 in). Further information from: *McMurdo, Rodney Road, Portsmouth, PO4 8SG.*

## Solder Feed

Leaving one hand free to hold the job, Anextra Solder Feed fits the majority of soldering irons and carries up to 4oz. reels of flux cored solder. Saves time on soldering in production, construction and repairs.

Injection moulded in tough, high impact polystyrene, with a life tested simple mechanism, easily reloaded, light weight, with comfort grip, suitable for right or left hand users, the Anextra provides an adjustable solder feed, for 22 to 18s.w.g. solder, which is fed onto the job.

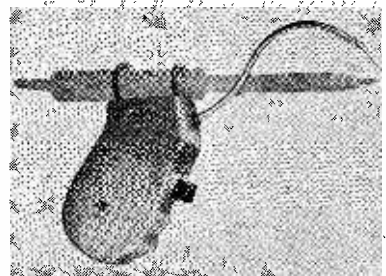Designed and made in England, the Anextra Solder Feed, with initial 1oz. reel of 60/40 core 22s.w.g. solder, and detailed instructions is obtainable direct from the makers at £4.25, spare 1oz. reels at £0.25, post free, c.w.o. S.a.e. for leaflet, *Anextra Ltd., Chiltern Works, Rear of 77/78 Chiltern View Road, Uxbridge, Middlesex, England.*



## International Audio Festival & Fair 1971

Come and visit us on stand 3 at Olympia, London,  
from October 26th to 30th.

What  
to look  
for at the  
**AUDIO  
FAIR**

**DONALD ALDOUS**

**M**ENTION of the title to this feature to a rather jaded audio trade friend evoked the reply "find the exit or the nearest bar!" Having been associated with audio fairs and like jamborees before there were any—if that isn't too paradoxical—I know what my friend meant. Tired feet allied to noise do not make for the best appreciation of high fidelity sound reproduction, which is presumably what such gatherings of the hi-fi clans should be all about.

Having made that point, I must go on to say that audiophiles with discerning eyes and ears can glean a lot of useful information about products to come, the latest technical developments in hi-fi, and by a discriminating choice of demonstrations to attend, gain a very helpful overall impression of what's happening in the home electronics entertainment world. Then after your visit to the 1971 International Audio Festival and Fair, Olympia, October 26 to 30th inclusive, 10 a.m. to 9.0 p.m. daily, admission 30p, go along to your local hi-fi dealer and have another session there or, if he will co-operate, have the equipment on test in your home. Reputable and well-organized hi-fi stores, many of which are members of the High Fidelity Dealers' Association—look for the HFDA sign—have demonstration showrooms or theatres, and facilities for A-B direct comparisons of systems or components.

At the last count, which may well have been increased by the time you visit Olympia, 66 exhibitors have stands at this year's exhibition, excluding the consumer and trade papers' stands. And, of course, these exhibits cover many brand names of products manufactured, imported and distributed, so a representative cross section of the world's hi-fi equipment and accessories is on display and demonstration.

This is not all you get for your admission fee, as four times a day for five days, an impressive lecture/recital programme is presented in the specially built theatre. Speakers taking part include H. W. Hellyer

(Tape Troubles), Professor Tristram Cary (Musical Value of Synthesizers), J. L. Linsley Hood (Amplifiers), Loudspeakers (Dr. A. Bailey), W. Woyda (Tape Cassettes/Cartridges), A. C. Griffith (Record Rejuvenation), R. Auger (Multi-Channel Sound), Howard Souther (Headphones), and two panel sessions, one on 'Women and Hi-Fi', and under the title 'Feed-Back-Chat' a number of well known audio personalities will tackle technical questions from the floor. This occasion will be recorded on the spot by BBC Radio London, and broadcast in November on their 'Sounds Good' programme.

Under the umbrella title 'home electronics entertainment media'—this is the new term at present in vogue—audiovisual recording systems are coming more and more into prominence, with applications extending into many areas from education to industry. At least five systems are now being promoted—VCR (video-cassette), EVR (electronic video recording), VTR (videotape recording), Super-8 film, and the Teldec *bildplatte* (picture-disc) from AEG-Telefunken-Decca. A colour version of this last disc technique was recently demonstrated in Berlin, at the big international radio and TV show.


Whilst a few of the firms participating in the audio exhibition at Olympia have one or other of these systems, they are not really eligible for presentation at a strictly audio assembly.

So let's turn our attention to techniques and products that immediately concern the audio enthusiast. Topics that are the talking points for engineers and the knowledgeable public are quadraphonic sound systems, noise reduction methods, cassette and cartridge tape recorders, headphones, and that hardy perennial—loudspeakers.


Starting with loudspeakers, the hundreds of models available in all shapes and sizes and prices do present a problem for the potential purchaser. The perfect loudspeaker does not exist and, although some families of transducers do have a 'household' sound—in most instances each system sounds a little different from the next and, so, ultimately, you must make your final choice by listening. The more experienced your ear is the better, naturally, and most audio purists would agree that regular ear purification by listening to 'live' music at concert halls is necessary to serve as a reference standard. A few audiophiles do exist still who tolerate the music to hear the equipment, but for the music lover-audiophile 'natural sound' is the goal for his domestic listening.

Home constructors will find several examples of D-I-Y loudspeaker enclosure kits at the show, ranging from Heathkit models to the latest Units 3, 4 and 5 from Wharfedale. Goodmans have now entered this field with their DIN 20 kit, as well as launching several new loudspeaker designs at Olympia.


The two new bookcase models from Goodmans are both three-way systems, but here the similarity ceases. The DoubleMaxim is intended for those with limited space. The bass and middle registers are shared between two small cone l.f. units and an h.f. dome unit handles the higher frequencies. The system will accept up to 30 watts (DIN). By employing three drive units—a bass model, a new mid-range and an h.f. dome radiator—Goodmans' engineers claim the division of the frequency range in the Havant model ensures a balanced natural sound. The DoubleMaxim is an IB design and the Havant is a reflex, and both models meet the DIN standards

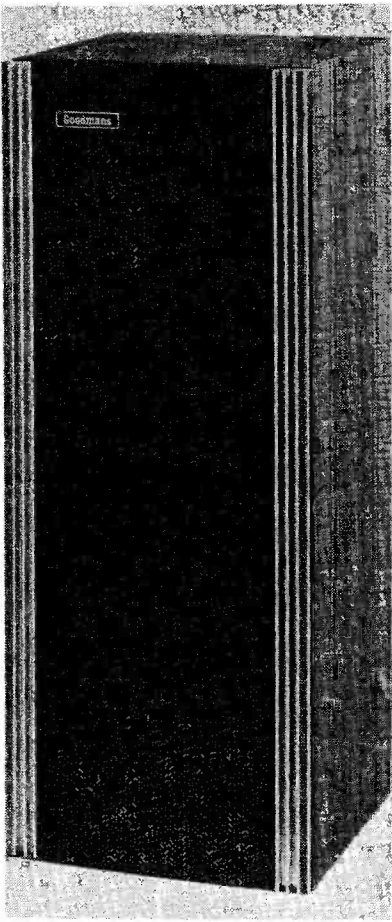

Goodmans Double Maxim speaker system.

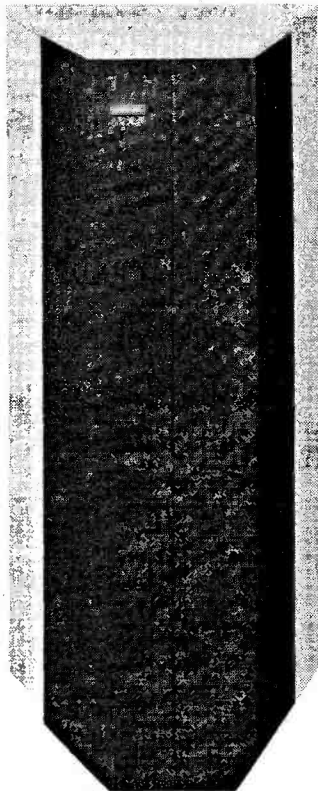


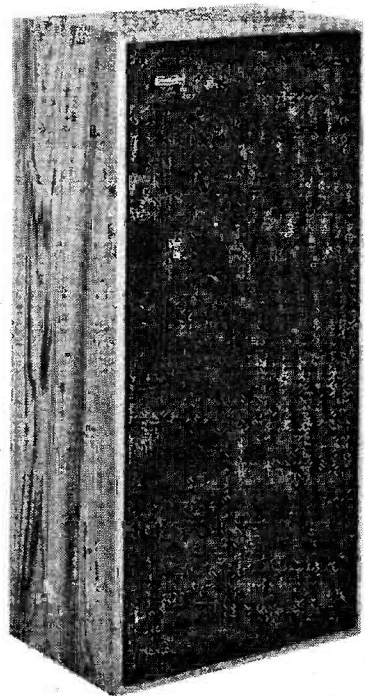Goodmans Dimension 8 bi-directional speakers.




Rola Celestion Ditton 44 Monitor

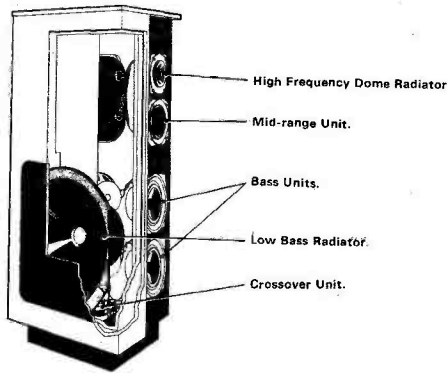(below) Wharfedale Unit 5 home-assembly Hi-Fi 3-unit Loudspeaker kit.




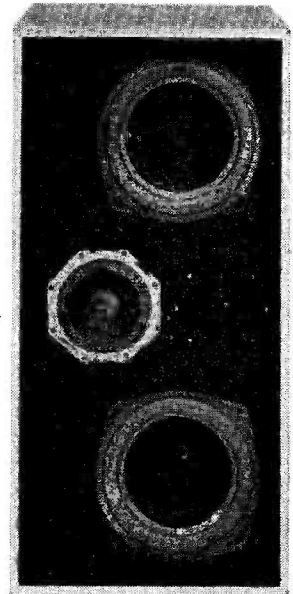(above) Units and functions in a Dimension 8 enclosure.



(right) B & O Beovox 4700 speaker enclosure.

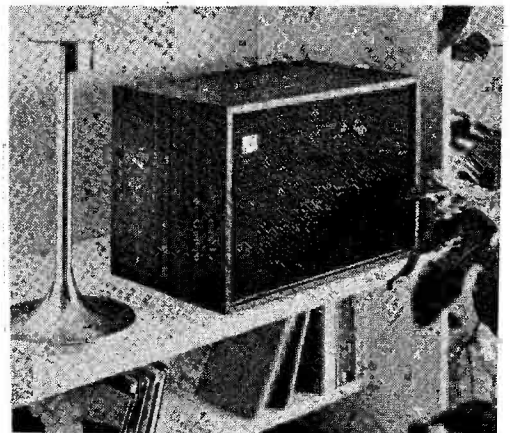(right) Wharfedale Denton 2 speaker for bookshelf mounting.



45:500 and 45:573.

The outstanding product in the new Goodmans' range is undoubtedly the Dimension-8 loudspeaker system. Described as bi-directional, to distinguish it from the traditional uni-directional and omni-directional systems, the designers believe it to be the first system planned to meet the twin requirements for ideal stereo—namely, radiating direct sound over a large listening area for accurate stereo placing and providing a controlled amount of indirect sound for natural stereo ambience (reflection and reverberation).

This effect is achieved by having one set of four drive units vertically arranged on each side of the cabinet so that the inward facing drive units (of a stereo pair) radiate direct sound over an appreciable listening area, whilst the outward facing units give indirect sound reflected off the side walls of the room.

The design philosophy of the Dimension-8 embraces the 'small cone concept' with a number of units which are carefully selected to match and so complement each other's output. The 'small cone' approach simply means using small diameter units working within their range, so avoiding cone break-up distortion. Four bass units handle the considerable rated input power of 60 watts nominal, or 35 watts r.m.s. Two new mid-range units, two dome h.f. radiators, and a 12in. 'sympathetic' low bass resonator complete the assembly. The output of these nine units is integrated by a crossover network using eight close tolerance components. The interior volume is 40 litres and its weight is 44lbs. The crossover frequencies are 80,800 and 4,000Hz. Its frequency response covers 30 to 22,000Hz within  $\pm 5$ dB. Physical dimensions:  $30\frac{3}{8} \times 14 \times 12\frac{1}{2}$  ins.

After a short period of listening to the Dimension-8s at the recent Berlin Radio and TV exhibition, I was impressed by their spacious and smooth sounding performance, so don't miss this demonstration at Olympia.

The radiation characteristics of loudspeakers are attracting interest lately, with the upsurge of enthusiasm by some designers—notably Stig Carlsson of Sweden—for an omni-directional pattern. The Sonab loudspeaker of this type disperses the sound in all directions so that all reflecting surfaces of a listening room are integrated, and the listening position for stereo sources is not critical, although room dependent to some extent. Yet another realisation of this concept are the omni-radial speakers from Sony. These have six acoustic-suspension drivers, and an individual dispersion dome over each cone distributes the highest frequencies evenly throughout a full 360° and from floor to ceiling. These speakers are housed in a barrel-shaped compound curved cabinet. Lastly, in this category of multi-directional loudspeakers, Arthur Radford, well known for his

amplifier and other loudspeaker designs, has created an unusual loudspeaker of special dispersion characteristics, which will be released shortly, I understand, by **Radford Audio Ltd.** of Bristol.

At this point, it must be mentioned that neither Sonab nor Radford is exhibiting at the Olympia audio exhibition, and Sony may not be showing their Omni-Radials, which have only lately come on to the market in Japan and in the USA. Sonab, however, did demonstrate their OA speaker range at the Northern Audio show in Harrogate in September. But enthusiasts will wish to know what developments are afoot in this controversial area of electro-acoustic transducer design.

Mention of kits, reminds me that **Sinclair Radionics** will show for the first time their new Project 605 at the Audio Fair, Olympia. Using modules, it is a novel extension of their popular Project 60 and sells for £29.95. The complete system can be assembled by any handyman without any soldering at all, as the printed circuit boards, etc. are all interconnected to inputs, outputs, through leads with push-fit tags. A fully illustrated instruction manual is supplied with the Project 605 system, which is certainly good value for outlay. The modules supplied include two Z.30 (15 watts r.m.s. per channel) power amplifiers, a pre-amp/control unit, and the PZ-5 power supply unit. (See "News . . .")

Audio fairs throughout the world seem to be using headsets as a practical means of reducing the bedlam of such conclaves and providing the audiophiles with a personal intimate sound demonstration. The latest designs of stereo headsets will be displayed and available for listening on the stands of such firms as **AKG** (75 on first floor), **Dynatron Radio** (47, first floor), **Grundig** (62, first floor), **Sony** (51 and 93), **T. M. Distributors (Koss)** on 68, first floor, and **Wilmex (Stax)**, 24 on ground floor, where six pairs of 'phones will be fed from disc/tape signals.

Many other manufacturers will have earphones on show, and my advice is not to miss the demonstrations of the latest Koss electrostatic ESP-9 studio monitor headset, and the Japanese Stax SR-3 so-called Ear Speakers. The ESP-9 model costs £69 and the Stax headset, with its SRD-5 adaptor, retails at £45.40. Once you have become used to listening via a headset, which fits comfortably and is non-fatiguing even after an hour or so's wearing, the experience can only be described as a sonic delight. Fed from a good source, the sound quality is clinically clean and undistorted. If you consider solo listening is anti-social in the home, Koss and other manufacturers produce connector boxes to permit attaching two or more pairs of headphones! Koss also offer among their collection of accessories, a stereo/mono adaptor cable, which simply switches from stereo to mono reproduction, as required, on the particular headphones. By the way, highly acceptable performance

## International Audio Festival & Fair 1971

All the big names of the Hi-Fi industry will be there in strength and there will be nearly 100 specially constructed audio studios where one can hear and compare sophisticated equipment spanning the whole price spectrum.


In the comfort of the Hi-Fi Theatre, one can enjoy special daily presentations, lectures and discussions by distinguished experts, technicians and personalities.

A series of lectures, demonstrations, etc. will be given daily in the Lecture Room. The full programme is in the catalogue, obtainable at the Exhibition.

Buses passing Olympia are 9, 27, 28, 49, 73. Green Line coaches are 701, 702, 704, 716. Underground train to Kensington, Olympia.

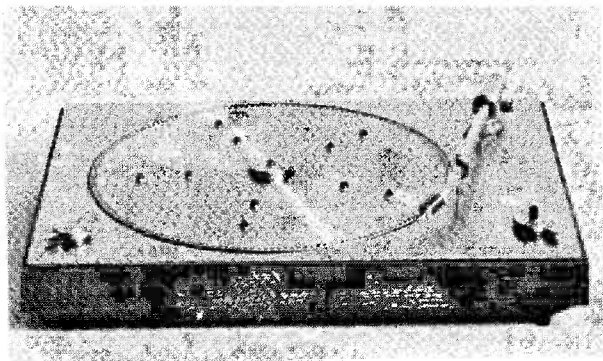**BEING HELD AT OLYMPIA, LONDON, OCTOBER 26—30 IS OPEN FROM 10 A.M. TO 9 P.M.**





B & O Beogram 1200 turntable on plinth.



Goodmans Model 80 fitted with Gold-ring Lenco G800E and Module 80 stereo f.m. tuner/amplifier.

Philips N4450 recorder/amplifier with auto reverse.




New Sony PSE 4000 turntable.

(below) Akai X2000 SD which accepts open reel, 8-track cartridge and Philips' type cassettes.



Beocord 1600 4-track recorder.

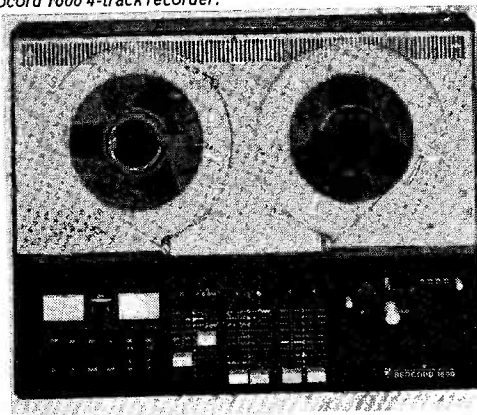



headphones are available for far less than the prices quoted of these 'state of the art' designs.

Peter Merrick, of Wilmex, tells me that there is a good chance that he will be able to show the latest Stax UA-7 pick-up arm, a sophisticated design, but it depends whether the samples from Japan reach our shores in time. Don't miss it, if it is on display. Before leaving headphones, we have just been told of the stereophonic 2-way, 4-speaker headphones, type DD1 from Wharfedale. These have dynamic elements, with separate bass and treble units, plus a crossover network, and a frequency response specified as from 16Hz to 22,000Hz but no tolerances given. Distortion less than 1 per cent and sensitivity (at 600Hz) is 100dB for 1mW input. Price: £11.

Wharfedale are showing, in addition to their well known Super 10/RS/DD, Super 8/RS/DD and 8in Bronze RS/DD units, their Dovedale 3 and Rosedale loudspeakers (both 3-unit systems) and the three Unit kits referred to earlier, will also introduce the Linton stereo amplifier (15+15 watts into 8 ohms) at 0.1 per cent distortion at all power levels up to 10 watts each channel driven at 1kHz into 8 ohm speakers, at £60. Another innovation from Wharfedale is the Linton 4-speed disc turntable, fitted with **Shure M44-7** cartridge, and selling for £35, including PT. Rumble is quoted as better than 35dB and wow better than 0.2 per cent, with flutter down to less than 0.06 per cent.

One wag has observed that the cassette revolution is not red but fully coloured these days. However, we are not dealing with video-cassette systems here, but the audio cassette revolution does concern us. In about six years, the fuss-free cassette has made tape recording more popular than ever, with modest recorders available at reasonable prices and **Philips** report that since the launch of the portable cassette recorder some five years ago, more than 6 million units have been sold in Western Europe.

Philips are marketing their new Cassetophone battery model, type N2000, styled in green polystyrene and weighing only 2lbs. It has one central control for playing, rewinding and fast forward, plus sockets for the addition of a mains supply unit and an earphone. Price is £13. A mains stereo cassette deck, N2503, is also now released from Philips. This design has one neat sliding control for setting the recording level and a 3-digit counter to give tape position. Another feature is that the motor stops automatically at the end of each cassette. This model sells for £52.05.

What might be called the 'home studio class' has been catered for in another new model from the Philips organization. Known as Model N4450, it is a 3-speed quarter-track recorder for vertical or horizontal operation with automatic and manual reverse. This facility means that the direction of the tape transport can be reversed at will or at the end of the tape, when it will automatically play in the other direction. The machine can accept up to 10½in reels and the built-in stereo amplifier develops 2×25 watts, and can be employed as a straight amplifier, with the motors and transport switched off.

Features in this advanced design include six heads, levers for cueing during fast forward and rewind, a tape tension comparator for constant winding torque, and a synchronous clock with built-in timing device for starting and stopping the recorder at any predetermined time. Following a trend, the volume, balance and treble/bass tone controls are

sliding potentiometers. Having played with an advance model of this N4450 I can vouch for its flexibility, and so don't miss examining this machine. It costs £280, including PT and will not be available till November.

We learn that Philips are engaged in producing hi-fi cassette machines, due for release in 1972, and this vast organization will take the initiative in proposing standards for this category of hi-fi cassette machine, but the standards will be reached—so they say—that the advantages of compact cassette systems, namely compatibility and ease of operation, will not be affected. Be it noted, however, that the prices of these models will be higher than existing equipment! These developments have been made possible by the release of tapes with high coercivity and improved magnetic heads on commercial recorders.

If you are a tape recordist, you will make special visits to the stands of **Agfa-Gevaert**, **BASF**, **3Ms (Scotch)** to find out about the latest chrome-dioxide tapes now manufactured by these companies. These are low noise tapes and the BASF cassettes have a new form of internal construction for even more reliable foolproof operation.

It will be evident now that this preview is highly selective, and, of course, cassette tape models (including new radio-recorders, with built-in radio tuners) incorporating various refinements can be seen on stands other than those mentioned. For example, Sony have several outstanding designs, as has Sanyo, Grundig, Akai, Sharp, National Panasonic, not forgetting the **Revox** open-reel tape machines.

**Uher** (Bosch) have a real innovation for them in their latest Compact Report Stereo 124 model, a mono-stereo cassette machine, which will accept Philips' type cassettes, work from all power sources, and has a built-in capacitor microphone, auto-reverse, remote controls and a power output of 1.3 watts r.m.s. per channel.

So we come to the noise bugaboo. Reams have been written about the brilliantly conceived Dolby noise reduction system, which in its professional A-type is widely used by all the major recording companies of the world, resulting in quieter surface commercial pressings. A simplified B-type Dolby system designed for home tape recorders is now available and used by more than 30 manufacturers of hi-fi equipment. Hundreds of cassettes processed for domestic playback with units having the Dolby system are already available from such firms as **Columbia (USA)**, **RCA (UK)**, **Decca/London**, **Ampex Stereo Tapes (USA)**, **Pye Precision Tapes**, and others.

The Dolby technique works in two stages. During recording, the Dolby circuit automatically analyses the sounds of the music and makes appropriate changes in the level of the programme. The same circuit, operating in reverse, removes these changes, during replay, and with them most of the intrusive noise produced by the tape. For the first time Ferrograph, that much respected name in the tape recorder world, has launched one of their machines incorporating Dolby B circuitry, which must not be overlooked at the show. Cassette machines fitted with Dolby noise-reduction circuit include **Harman-Kardon** (Highgate Acoustics), a **Rank-Wharfedale** model, and **Bell & Howell** also market such a unit.

Although it will not be seen in a production model, so far as I know, at Olympia, Philips have developed

—continued on page 589

**Radio Valve and Transistor Data, 9th Ed.**

Compiled by A. M. Ball  
0 592 05976 6 232pp 1970 75p

**Guide to Broadcasting Stations, 16th Ed.**

0 592 08131 1 160pp 1970 50p

**20 Solid State Projects for the Car and Garage**

R. M. Marston  
0 592 02866 6 cased } 115pp illustrated 1970 £1.80  
0 592 00048 6 limp } £1.20

**20 Solid State Projects for the Home**

R. M. Marston  
0 592 02867 4 cased } 105pp illustrated 1969 £1.40  
0 592 02872 0 limp } 90p

**110 Semiconductor Projects for the Home Constructor**

R. M. Marston  
0 592 02845 3 cased } 124pp illustrated 1969 £1.80  
0 592 02864 X limp } £1.20

**110 Integrated Circuit Projects for the Home Constructor**

R. M. Marston  
0 592 00063 X cased } 138pp illustrated 1971 £1.80  
0 592 00058 3 limp } £1.20

**Beginner's Guide to Radio, 7th Ed.**

Gordon J. King, MRTS, AIERE, AMIET, MITAI, MIPRE, MAES  
0 408 00016 3 194pp illustrated 1970 £1.00

**Colour Television Servicing**

Gordon J. King, MRTS, AIERE, AMIET, MITAI, MIPRE, MAES  
0 408 00044 9 328pp illustrated 1971 £4.40

**Practical Aerial Handbook, 2nd Ed.**

Gordon J. King, MRTS, AIERE, AMIET, MITAI, MIPRE, MAES  
0 408 00001 5 232pp illustrated 1970 £2.70

**Principles of Semiconductors**

M. G. Scroggie, BSc, CEng, FIEE  
0 592 02737 6 156pp illustrated 1961 £1.50

**Radio and Audio Servicing Handbook, 2nd Ed.**

Gordon J. King, MRTS, AIERE, AMIET, MITAI, MIPRE, MAES  
0 408 00018 X 283pp illustrated 1970 £3.00

**Television Servicing Handbook, 3rd Ed.**

Gordon J. King, MRTS, AIERE, AMIET, MITAI, MIPRE, MAES  
0 408 00033 3 358pp illustrated 1971 £3.80

**Servicing with the Oscilloscope**

Gordon J. King, MRTS, AIERE, AMIET, MITAI, MIPRE, MAES  
0 408 00032 5 176pp illustrated 1969 £1.40

**Hi-Fi and Tape Recorder Handbook**

Gordon J. King, MRTS, AIERE, AMIET, MITAI, MIPRE, MAES  
0 6004 0131 6 304pp illustrated 1969 £2.00

**Beginners Guide to Television, 4th Ed.**

Gordon J. King, MRTS, AIERE, AMIET, MITAI, MIPRE, MAES  
0 6004 1018 8 208pp illustrated 1968 £1.00

**Colour Receiver Techniques**

T. D. Towers, MBE, MA, BSc, AMIEE  
0 592 05943 X 88pp illustrated 1968 £1.75

**Rapid Servicing of Transistor Equipment**

Gordon J. King, MRTS, AIERE, AMIET, MITAI, MIPRE, MAES  
0 6004 1294 6 160pp illustrated 1966 £1.50

**Radio and Electronic Laboratory Handbook, 8th Ed.**

M. G. Scroggie, BSc, CEng, FIEE  
0 592 05950 2 610pp illustrated 1971 £4.75

**Foundations of Wireless and Electronics**

M. G. Scroggie, BSc, CEng, FIEE  
0 592 05961 8 cased } 521pp illustrated 1971 £3.00  
0 592 00041 9 limp } £1.80

Available from leading booksellers or



**The Butterworth Group** 88 Kingsway London WC2B 6AB

Showrooms and Trade Counter, 4-5 Bell Yard, London WC2.

# Now! A FAST EASY WAY TO LEARN BASIC RADIO & ELECTRONICS



Build as you learn with the exciting new **TECHNATRON** Outfit! No mathematics. No soldering—you learn the **practical way.**

Learn basic Radio and Electronics at home—the fast, modern way. Give yourself essential technical "know-how"—like reading circuits, assembling standard components, experimenting, building—quickly and without effort, and enjoy every moment. B.I.E.T.'s Simplified Study Method and the remarkable **TECHNATRON** Self-Build Outfit take the mystery out of the subject, making learning easy and interesting.

Even if you don't know the first thing about Radio now, you'll build your own Radio set within a month or so!

... and what's more, you will understand exactly what you are doing. The **TECHNATRON** Outfit contains everything you need, from tools to transistors—even a versatile Multimeter which we teach you to use. All you need give is a little of your spare time and the surprisingly low fee, payable monthly if you wish. And the equipment remains yours, so you can use it again and again.

A 14-year-old could understand and benefit from this Course—but it teaches the real thing. The easy to understand, practical projects—from a burglar-alarm to a sophisticated Radio set—help you master basic Radio and Electronics—even if you are a "non-technical" type. And, if you want to make it a career, B.I.E.T. has a fine range of Courses up to City and Guilds standards.

**You LEARN—but it's as fascinating as a hobby**

Among many other interesting experiments, the Radio set you build—and it's a good one—is really a bonus. This is first and last a teaching course, but the training is as fascinating as any hobby and it could be the spring-board for a career in Radio and Electronics.

### New Specialist Booklet

If you wish to make a career in Electronics, send for your FREE copy of "OPPORTUNITIES IN TELECOMMUNICATIONS / TV AND RADIO". This brand new booklet—just out—tells you all about **TECHNATRON** and B.I.E.T.'s full range of courses.



## FREE

### BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept. B8, ALDERMASTON COURT, READING RG7 4PF

### POST THIS COUPON FOR FREE BOOK

To B.I.E.T. Dept. B8 Aldermaston Court, Reading RG7 4PF

Please send books and full information — FREE and without obligation.



NAME..... AGE.....  
 ADDRESS.....  
 BLOCK CAPITALS PLEASE  
 OCCUPATION.....

**BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**  
 Accredited by the Council for the Accreditation of Correspondence Colleges.




# JACKSONS
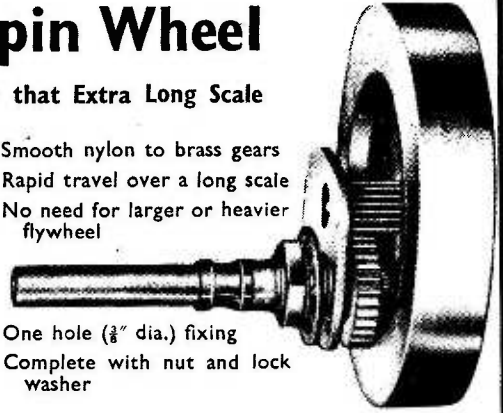
## Accelerator Spin Wheel

for that Extra Long Scale

- ★ Smooth nylon to brass gears
- ★ Rapid travel over a long scale
- ★ No need for larger or heavier flywheel



- ★ One hole ( $\frac{3}{8}$ " dia.) fixing
- ★ Complete with nut and lock washer

Write for literature:

**JACKSON BROTHERS (London) LIMITED**

Dept. P.W. Kingsway, Waddon, Croydon CR9 4DG.

Phone: 01-688 2754/5 Grams: Walfilco, Croydon.

U.S. Office: M. Swedgal,

258 Broadway, New York, N.Y. 10007

### Selections from FELSTEAD ELECTRONICS' List


(Send free for stamped addressed envelope to address below)

Transistors etc. AC126 124p. AF115 20p. AF116 15p. AF117 20p. OA5 71p. OA10 71p. OA81 71p. OA85 71p. OC28 324p. OC26 30p. OC26 371p. OC28 424p. OC35 424p. OC44 14p. OC45 124p. OC71 124p. OC79 124p. OC76 124p. OC81 124p. OC81D 124p. OC82D 124p. OC170 20p. OC171 124p. Many more in list. S.D.R. BY100 800piv 14p. 8 amp series: BYZ13 300piv 50p. BYZ12 600piv 25p. BYZ11 900piv 30p. BYZ10 1200piv 35p. (Charges 64p up to 11. paid for 12 and over). Sub-Min. Transformers: OUTPUT 3  $\Omega$  for OC72 etc.) 14p (up to 6. 64p). **SOLDERING IRON.** Slim, modern, British highspeed 84", all parts replaceable, highest quality, full guarantee: 21-074 (10p). **DIAMOND STYLII** Replacements for BSR TCS/LP, TCS/S, TCS/LP/STEREO; COLLARO 'O' - ROSETTE BF 40LP; Garrard GC2/LP and GC4LP; ACOS GPT8/9T, all at 40p (6p). ACOS GPT3, BF 40LP; Garrard GC2/LP and GC4LP; ACOS GPT8/9T, all at 40p (6p). ACOS GPT3, PHILLIPS AG3506, 3090 (3063, 3066, 3801, 3802, 3304); Garrard GKS25, GCM21, GC828 and many more 'Garrard' etc. types. All at 75p. (6p). All are of the very highest quality **DOUBLE DIAMOND:** ST4 (ST3, ST5); ST10 (ST9, ST8); 9TA, 9TAHC, 3306, GP91 (For GP92, GP98, GP94 cartridges); GP91-SC for all GP91-SC Cartridges. All at 21-50 each (6p). **SAPPHIRE STYLII.** All these types shown above under 'Diamond StylII at 40p' also GP37 at 174p each (6p) and GP91 and GP91SC at 40p (6p). No others. **FIGK-UP CARTRIDGES.** All Standard fittings and stylii. Mono GP67/2 80p. STEREO-COMPATIBLE (MONO) GP91/SC 21-10 STEREO GP98 21-30 STEREO CERAMIC GP94 21-85 SONOTONE STEREO 9TAHC (DIA.) 22-40. **RECORDING TAPE.** Sell the finest quality British Mylar available: Standard 5" 600ft. 36p. 5" 900ft. 50p. 7" 1200ft. 50p. LONG PLAY 6" 900ft. 50p. 5" 1200ft. 50p. 7" 1800ft. 50p. (74p on 5" and 54" 9p on 7"). Other sizes of Tapes, also dir., built-in vol. control, on/off switch, special lead, handle (as good as money can buy) 26-30. UD180 Uni-Dir. Ball, mesh, 50K/600 $\Omega$ . Adap. cable, jack plug 24-30. (20p). DM160 omni-dir., Ball, 50K Cable adaptor 23-87 (all at 274p). **MICROPHONE INSERTS.** Dia., 1.75" OR 0.9" either size 274p (6p). **BARTHOLOMEWS** lead and min. jack plug (2.5 or 3.5 mm., state which). Magnetic Sp Crystal (3.5 only) 24p (Up to 3 for 6p on any). **HEADPHONES** De-hux STEREO 8-16 Ohms 22-47. Same, fitted vol. control each earpiece 24-20. Both have lead and stereo jack plug (174p). High Res. 2000 ohm. Adjustable 924p (74p). **SPEAKERS** 12" ROUND fitted tweeter, 3 or 15  $\Omega$  (state which) 21-57 (274p) or for Stereo 24-25 pair, carr. paid. 24", 3 OR 8  $\Omega$  (state which) 874p (6p). EMI 13" x 8", 3, 8 or 15  $\Omega$  (state which) 22-124 (25p); with two tweeters and crossover network 16  $\Omega$  23-75 (25p). **VIBRATORS.** 12V 4-pin non-synch. 12LH14. 24" ex-pins. 274p. 12V 7-pin Synch. (12SER) 624p. (Both types 64p per vibrator). **CONNECTING WIRE.** Packs of 3 coils asstd. coils ea. coil 4yds. Solid core 14p (6p). Flexible 16p (74p). Super thin for transistor wiring 18p (6p). **FIGK-UP WIRE.** Super thin twin flex, screened and sheathed 6p yd. (6p up to 6yds.—over free). **RETRACTABLE Flex Leads.** (Curliies) Phonoplug each end 12ft. 30p. 6ft phono plug/phone socket other end 25p. 12ft 424p (6p per lead all types). **SEND S.A.E.** for full free list of mains eliminators, amplifiers, extension aerials (car and portable), electrolytics, vol. controls, more microphones, transistors, thyristors and S.D.R.s and other devices, switches of many types, rotary, toggle min. and sub-min. slide types, multitest meters, panel meters, all types of British and continental plugs and sockets, croc. clips, terminals, valve holders also Goldring G800 series cartridges etc. etc. 'Special Offer' lined at very low prices.

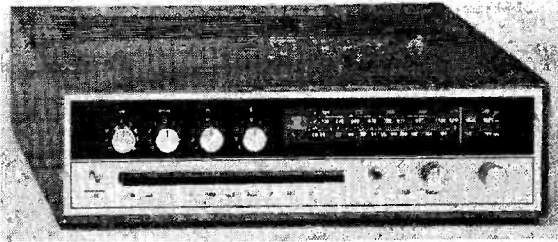
**FELSTEAD ELECTRONICS (PW 49)**

LONGLEY LANE, GATLEY, CHEADLE, CHES. SK8 4EE


Cash with order only. No COD or Caller Service. Charges (Min. 6p) in brackets after all items. Regret Orders under 25p excluding postage, unacceptable. SAE please for enquiries or cannot be replied to. Charges apply G.B. and Eire only. Overseas orders welcomed (lists free overseas).



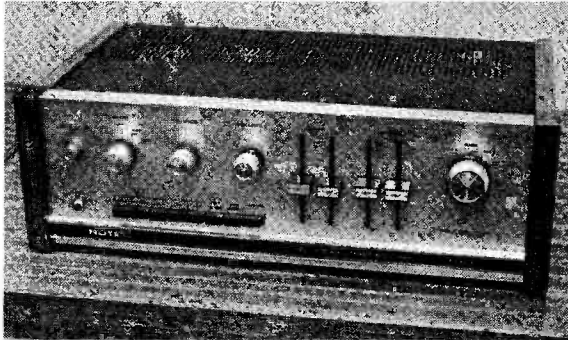
Armstrong 526 a.m./f.m. stereo tuner/amplifier.



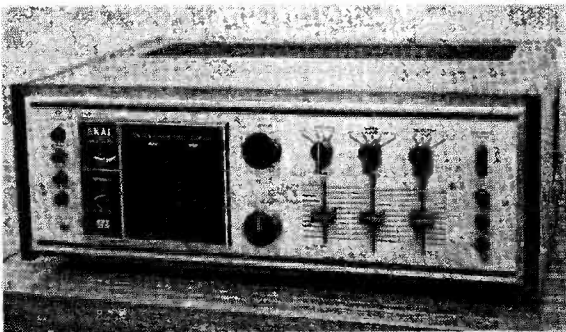Rotel RA 610 stereo amplifier with slider controls.





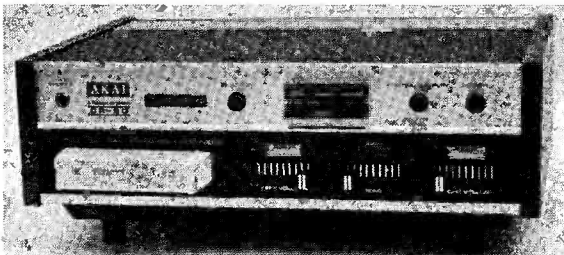Akai a.m./f.m. solid state stereo receiver AA 8500.



Akai CR 80 8-track cartridge record and player.

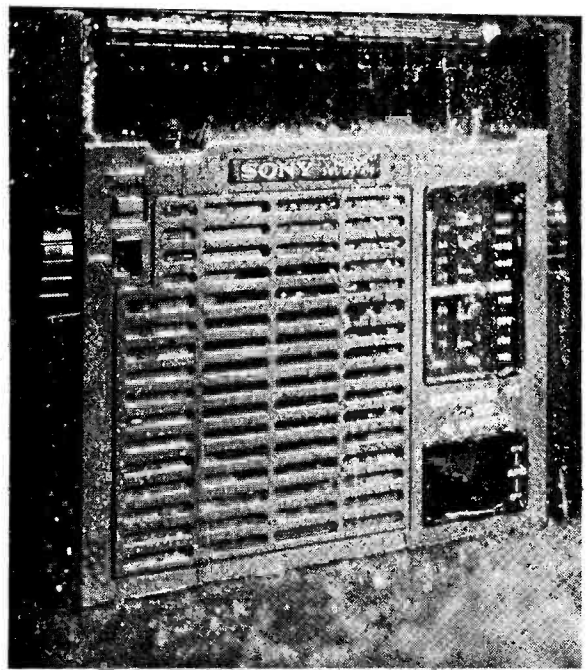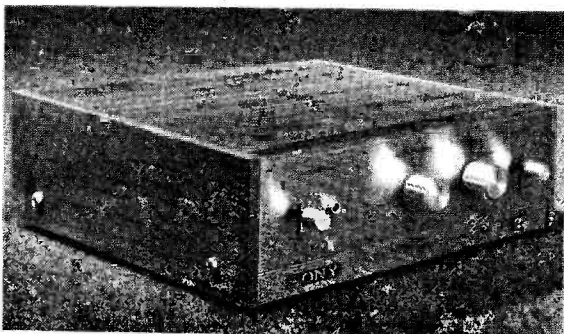
(below) Sony SQD—1000 Quadphonic Decoder.



Sony Sports 11 waterproof portable.



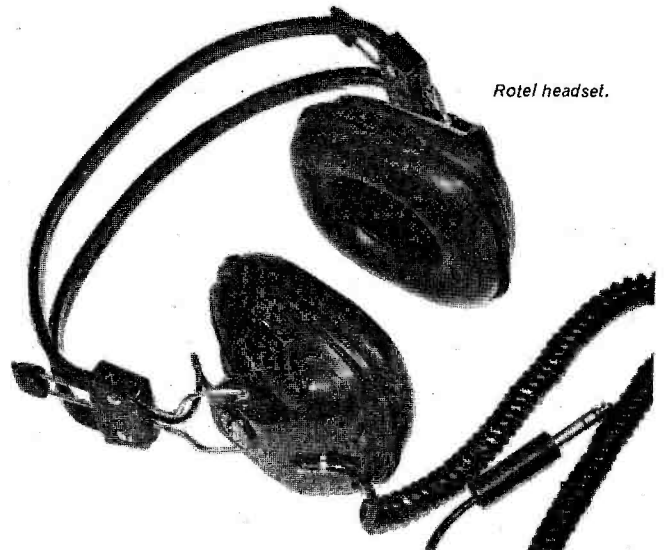Stax electrostatic headset SR3/SRD5 "ear speakers".



Rotel headset.


their DNL circuitry (which means Dynamic Noise Limiter) as an alternative system to the Dolby method. It operates as a steep low-pass filter in the absence of high signal frequencies, and it is tripped by high frequencies only, in such a way that the presence of high frequency signals above a certain level will by pass the filter action. It is claimed that unweighted measurements show an S/N ratio improvement of more than 10dB at 6kHz and 20dB at 10kHz. A prototype Philips cassette recorder with the DNL circuit incorporated was shown at Berlin, which has push buttons ready for all types of tape, from the newer chrome grades to standard hi-fi formulations. Perhaps next year production models will be available, but the news of this development indicates the importance attached to noise reduction systems for upgrading domestic sound recorders.

Denham & Morley's stand 65 (on first floor) will display and demonstrate JVC-Nivico equipment, and among this range is their ANRS circuit, meaning Automatic Noise Reduction System, another technique that seems to bear some resemblance to the Dolby method.

A lot of money and effort is being spent developing and promoting spatial sound systems, which are being given such names as quadraphonic, quadra-sonic, surround sound, tetrahedral sound, even multi-sound, and some of the competing 4-channel systems for the home environment include Sansui, E-V (Electro-voice), JVC-Nivico, Dyna (Hafler) and the CBS.SQ technique. In the last instance, Sony is manufacturing the hardware for reproducing these SQ (meaning stereo quadraphonic) discs. Benjamin Bauer (Vice President, CBS Laboratories), who led the team responsible for the system, has given some most impressive demonstrations of the method on the Continent and in London, at a recent Audio Engineering Society meeting. A specially prepared sampler LP, with David Frost as narrator, was used for this purpose, and it is promised that about 50 SQ processed discs will be produced in the coming months, so providing the needed software.

At the time of writing, no details are available of any company participating in the Audio Fair here that will be demonstrating a 4-channel disc system, although multi-channel tape systems will undoubtedly be heard. Propagandists for quadraphonic sound which recreates sound from four different source points, permitting a 360° sound perception, regard the technique as the most important advance in hi-fi sound recording since the advent of the stereo disc. This is not a universally held viewpoint, and some critics consider it rather gimmicky at this stage, offering all-round sound at the price of maximum fidelity for a given outlay. No standards exist yet, and only time will show which system will win, if at all in the UK, where the extra cost of decoder, amplifier and loudspeakers, linked to limited room size and problems of siting additional loudspeakers, may weigh more heavily than technical advances.

Lastly, BSR will show their attractive transcription hi-fi record playing deck, BSR McDonald 810 with many refinements, including push button control, and I hear that our old faithful Quad electrostatic loud-speaker will now be available in black finish, as an alternative to the long familiar bronze. Leak, too, have a new series of Delta equipment, including amplifiers, speakers, turntables, and a.m. f.m. tuner.

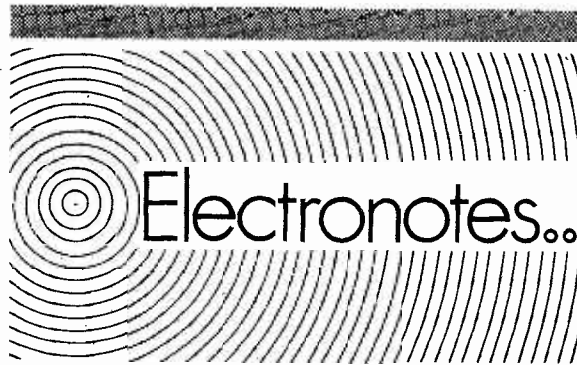

S. GINSBERG

**P**OWER supplies have long followed fairly standard rules. In the days of the valve, it resolved itself to a mains transformer, rectifier(s) and some form of smoothing, usually comparatively high value capacitors and a fairly hefty iron-cored choke.

With the advent of the transistor, much the same rules applied, except that whereas before it was a case of high voltage and low current the reverse was true. This was particularly so in the case of industrial applications such as computers. In many forms of instrumentation today, many logic chips are employed, all requiring some 5V and, since there can be many, needing quite a few amps of current.

An improvement came with active regulation, the use of large transistors as series regulators with some form of feedback sensing circuit to control variations in the final supply to within certain limits.

A snag is that the power supply has become, in many instances, the largest part of the equipment—and the heaviest. The two major offenders in space and weight considerations are the mains transformer and the series regulator heat sinks. In a series regulator, the total current passes through the device which also has a voltage dropped across it. This means heat, mainly because of inefficiency, and thus the heat sinks become vital to get rid of the heat and prevent the regulators from overheating and becoming ruined.

A new technique has now been launched which gets rid of both the big 50Hz mains transformer and the heat sinks all in one go. It uses switching techniques. The mains is taken and rectified. It is then applied to an inverter which is a form of oscillator using semiconductors. The oscillator has a working frequency of between 20 and 40kHz. The output is fed to a small ferrite torroid transformer and the output rectified by Schottky barrier diodes in a full wave rectifier circuit. The Schottky diodes have barely one third the voltage drop across them compared to conventional high-speed silicon rectifiers and they do not have the problems of reverse recovery. This means very much smaller heat sinks.

A 5V 20A unit, using these techniques, is so small it can be easily stood on the palm of one's hand. The power packing density, just for the mathematicians, works out at around 0.75in.<sup>3</sup>/W. Using conventional techniques to build a similarly rated unit would mean that the 50Hz mains transformer alone would be both bigger and heavier, than the whole power supply using switching techniques. Because the switching frequency is high (compared to 50Hz) and because it is effectively doubled by using full wave rectification, the smoothing components can be made extremely small.



## FIND BURIED TREASURE! TREASURE LOCATOR TRANSISTORISED


NOW IT'S HERE AT LAST, after experimenting for four and a half months with a multitude of different circuits and carrying out actual field tests with prototypes, our design team have come up with this real winner. This fully portable transistorized metal locator detects and tracks down buried metal objects—it signals exact location with loud audible sound (no phones used)—uses



ONLY  
**£2-37**  
(47/6)

any transistor radio which fits inside—no connections needed. FINDS GOLD, SILVER, LOST COINS, JEWELLERY, KEYS, WAR SOUVENIRS, ARCHAEOLOGICAL PIECES, METALLIC ORE, NUGGETS ETC. ETC. Outdoors or indoors. Extremely sensitive, will signal presence of certain objects buried several feet below ground! No knowledge of radio or electronics required. Can be built with ease in one short evening by anybody from nine years of age upwards, with the wonderfully clear, easy to follow, step-by-step, fully illustrated instructions—it really is as easy as A.B.C. transistorized—no valves. Uses standard PP3 battery. No soldering necessary. Size of detector head 13" x 10" x 2 1/2". Great demand expected at this remarkably low price—ORDER WHILE PRESENT STOCKS LAST. All parts including detector head case, nuts, screws, wire, simple instructions etc. etc. ONLY £2-37 (47/6) + 2p (5/6) p. & p. (Sectional handle as illustrated 75p (15/-) extra). Parts available separately. Made up looks worth £15!

## BUILD 5 RADIO AND ELECTRONIC PROJECTS

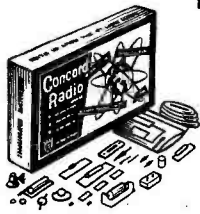


TOTAL BUILDING PRICE **£1-97**

(39/6)  
Amazing Radio Construction set! Become a radio expert for £1-97 (39/6). A complete Home Radio Course. No experience needed. Parts including simple instructions for each design. Illustrated Step-by-step plans, all Transistors, loudspeaker, personal phone, knobs, screws, etc., all you need. Presentation Box 37p (7/6) extra as illus. (if required) (extra parts available separately) no soldering necessary. Send only £1-97 (39/6) + 23p (4/6) p. & p.

phone, knobs, screws, etc., all you need. Presentation Box 37p (7/6) extra as illus. (if required) (extra parts available separately) no soldering necessary. Send only £1-97 (39/6) + 23p (4/6) p. & p.
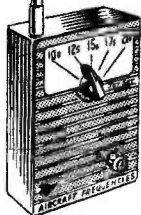
## EAVESDROP ON THE EXCITING WORLD OF AIRCRAFT COMMUNICATIONS—JUST OUT V.H.F. AIRCRAFT BAND CONVERTER

Many thousands of v.h.f. Aircraft Band Converters now selling in U.S.A. Listen in to AIRLINES, PRIVATE PLANES, JETPLANES. Eavesdrop on exciting crosstalk between pilots, ground approach control, airport tower. Hear for yourself the disciplined voices hiding tenseness on talk downs. Be with them when they have to take nerve rippling decisions in emergencies—Tune into the international distress frequency. Covers the aircraft frequency band including HEATHROW, GATWICK, LUTON, RINGWAY, PRESTWICK ETC., ETC. CLEAR AS A BELL! This fantastic fully transistorized instrument can be built by anyone nine to ninety in under two hours. (Our design team built four—everyone worked first time). No knowledge of radio or electronics required. No soldering necessary. Fully illustrated simple worked instructions take you step-by-step. Uses standard PP3 battery. Size only 4 1/2" x 3" x 1 1/2". All you do is extend rod aerial, place close to any ordinary medium-wave radio—(even tiny portables) NO CONNECTIONS WHATSOEVER NEEDED. Use indoors or outdoors. THERE WILL BE ENORMOUS DEMAND FOR THIS NEW DESIGN, SEND NOW, ONLY £2-37 (47/6) + 23p (4/6) p. & p. for all parts, including case nuts, screws, wire, etc. (Parts available separately).




ONLY  
**£2-37**  
(47/6)

## SOOTHE YOUR NERVES, RELAX WITH THIS AMAZING RELAXATRON


CUTS OUT NOISE POLLUTION—SOOTHE YOUR NERVES! Don't underestimate the uses of this fantastic new design—the RELAXATRON is basically a pink noise generator based on avalanche operated transistors. Besides being able to mask out extraneous unwanted sounds, it has other very interesting properties. For instance, many people find a rainstorm mysteriously relaxing, a large part of this feeling of well-being can be directly traced to the sound of falling raindrops—a well known type of pink noise. A group of Dentists have experimented on patients with this pink noise—NO ANESTHETICS WERE USED! The noise ostensibly created a most definite reaction on these patients' nervous systems with the results that their pain systems were blocked. IF YOU WORK IN VERY OR DISTRACTING SURROUNDINGS, IF YOU HAVE TROUBLE CONCENTRATING, IF YOU FEEL TENSED, UNABLE TO RELAX—then build this fantastic Relaxatron. Once used you will never want to be without it—use this amazing pink noise generator whenever you feel uneasy, can't relax or wish to concentrate. TAKE IT ANYWHERE, pocket sized. Uses standard PP3 batteries (current used so small that battery life is almost shelf-life) CAN BE EASILY BUILT BY ANYONE OVER 12 YEARS OF AGE using our unique, step-by-step, fully illustrated plans. No soldering necessary. All parts including case, a pair of crystal phones, Components, Nuts, Screws, Wire, etc. etc. no soldering. Send only £2-25 + 25p (45/- + 5/-) p. & p. parts available separately.

only  
**£2-25**  
(45/-)

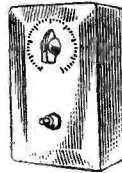


## GET A GOOD NIGHT'S SLEEP—EVERY NIGHT! INGENIOUS ELECTRONIC SLEEP INDUCER

only  
**£2-75**  
(55/-)

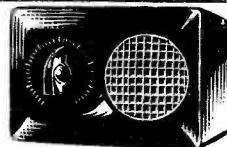

CAN'T SLEEP AT NIGHTS? DO YOU WAKE UP IN THE NIGHT AND CAN'T GET OFF TO SLEEP AGAIN? WOULD YOU LIKE TO BE GENTLY SOOTHE OFF TO SATISFYING SLEEP EVERY NIGHT? Then build this ingenious electronic sleep inducer. It even stops by itself so you don't have to worry about it being on all night! The loudspeaker produces soothing audio-frequency sounds, continuously repeated—but as time goes on the sounds gradually become less and less—until they eventually cease altogether, the effect it has on people is amazingly very similar to hypnosis. A control is provided for adjusting the length of times etc., all transistor, can be built by anyone over 12 years of age in about two hours. No knowledge of electronics or radio needed. Extremely simple, easy-to-follow, step-by-step, fully illustrated instructions included. No soldering necessary. Works off standard batteries—extremely economical. Size only 3" x 4" x 1 1/2"—take it anywhere. All parts including case, loudspeaker, components, nuts, wire, screws, etc. etc. THERE WILL BE A GREAT DEMAND FOR THIS UNIQUE NEW DESIGN—SEND NOW £2-75 + 25p (55/- + 5/-) p. & p. (parts available separately).

## REAL WORKING ELECTRONIC ORGAN

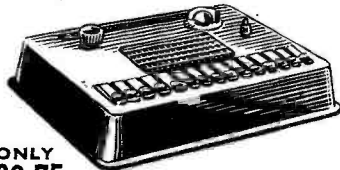

ONLY  
**£2-75**  
(55/-)

Anyone from nine years upwards can build it easily in one short evening following the fully illustrated step-by-step, simply worded instructions. BIG DEMAND ANTICIPATED FOR THIS UNIQUE INSTRUMENT at our low, low building price. ONLY £2-75 (55/-) + 25p (4/6) p. & p. for all parts, including case, loudspeaker, transistors, condensers, resistors, knobs, transformer, volume control, wire, nuts, screws, simple (but full) instructions, etc. etc. Use standard battery (parts available separately). Have all the pleasure of making it yourself, finish with an exciting gift for someone.


Don't confuse with ordinary electric organs that simply blow air over multi-organ type reeds etc. Eight months we spent in creating and testing this superb, revolutionary electronic organ. Fully transistorized—no valves. Proper self-contained loudspeaker. Fifteen separate keys span two full octaves—play the "Yellow Rose of Texas", play "Silent Night", play "Auld Lang Syne", play lots and lots of similar tunes on this real working electronic organ. Although it's no theatre organ it's certainly no tiny thing, it measures 13" x 10" x 2 1/2". You have the thrill and excitement of building it together with the pleasure of playing a real, live, throbbing electronic organ. Take it anywhere—play it anywhere, NO PREVIOUS KNOWLEDGE OF ELECTRONICS NEEDED—NONE WHATSOEVER. No soldering necessary, it really is as simple as a.b.c. to make.

## SHORTWAVE TRANSISTOR RADIO

ONLY  
**£2-25**  
(45/-)


Can be built in one evening

At last! After trying countless circuits searching for easy build, work first-time short wave. Giving advanced world-wide performance, we chose this "Sky Roma". Anyone from 9 years up can follow the step-by-step, easy-as-ABC, fully illustrated instructions. (We built ten prototypes and everyone worked first time) no soldering necessary. 76 stations logged on rod aerial in 30 mins.—Russia, Africa, USA, Switzerland, etc. Experience thrill of world wide news, sport, music, etc. Eavesdrop on unusual broadcasts. Uses PP3 battery. Transistorized (no valves!). Size only 3" x 4 1/2" x 1 1/2". As tremendous demand anticipated price held to only £2-25 (45/-) + 17p (3/6) p. & p. for all parts incl. Cabinet, screws, instructions, etc. (Parts available separately).

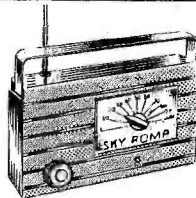
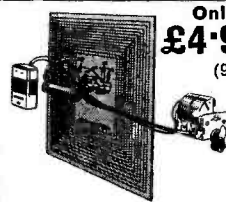
## ONLY £4-95 FIND BURIED TREASURE WITH THIS READY BUILT & TESTED Treasure Locator Module

BRAND NEW FULLY TRANSISTORISED PRINTED CIRCUIT METAL DETECTOR MODULE. Ready built and tested—just plug in a PP3 battery and 'phones and it's working. Put it in a case, screw a handle on and YOU HAVE A PORTABLE TREASURE LOCATOR EASILY WORTH ABOUT £20! Extremely sensitive—penetrates through earth, sand, rock, wood, dirt, water, etc.—EASILY LOCATES COINS, GOLD, SILVER, WATCHES, JEWELLERY, NUGGETS, METALLIC ORE, HISTORICAL RELICS, BURIED PIPES, KEYS, NAIL-IN-TREES, ETC., ETC. Signals exact location by "beep" pitch increasing as you near buried metallic objects. PRINTED CIRCUIT SEARCH COIL so stable and sensitive it will detect certain objects buried SEVERAL FEET BELOW GROUND! GIVES CLEAR SIGNAL ON ONE COIN! You could even pay for your holidays with two or three days electronic beachcombing—it's almost like having a license to print money! Unclaimed treasure now exceeds the combined wealth of all nations. ORDER NOW WHILE PRESENT STOCKS LAST—TREMENDOUS DEMAND EXPECTED AT THIS REMARKABLY LOW PRICE. DEMONSTRATIONS DAILY. ORDERS DESPATCHED IN STRICT ROTATION. SEND NOW £4-95 + 30p carr. (99/- + 6/-) etc. (High quality Danish Stethoscope headphones £2-75 (55/-) extra if required).



ONLY  
**£4-95**  
(99/-)

EXAMINE AT HOME FOR 7 DAYS. YOUR MONEY REFUNDED IN FULL IF NOT 100% DELIGHTED.

**CONCORD ELECTRONICS LTD (Dept. PW25)**  
(STAFF WANTED FOR ALL DEPARTMENTS)

8 Westbourne Grove, London W.2.  
(Nr Bayswater & Queensway Tubes, 1 minute ABC Cinema)  
Callers Welcome 9 a.m.-6 p.m. inc. Saturday

# WEYRAD

## COILS & TRANSFORMERS FOR CONSTRUCTORS

Special versions of our P50 Series are now available for AF117 or OC45 Transistors. They can be used in the standard superhet circuit with slight changes in component values.

Oscillator Coil .....	P50/1AC (For OC45)	P50/1AC (For AF117)	33p
1st I.F. Transformer .....	P50/2CC (For OC45)	P51/1 (For AF117)	36p
2nd I.F. Transformer .....	P50/2CC (For OC45)	P51/2 (For AF117)	36p
3rd I.F. Transformer .....	P50/3CC (For OC45)	P50/3V (For AF117)	36p
Rod Aerial .....	RA2W		72p
Driver Transformer .....	LFDT4/1		58p
Output Transformer .....	OPT1		58p
Printed Circuit .....	PCA1		58p

## I.F. TRANSFORMERS FOR "PRACTICAL WIRELESS" CIRCUITS

Components for several receivers are available, including the following for the "Clubman".

T41/1E	1st I.F. Transformer .....	39p
T41/2E	2nd I.F. Transformer .....	39p
T41/3T	3rd I.F. Transformer .....	57p
T41/3T	B.F.O. Coil .....	57p

Details of these and our other components are given in an illustrated folder which will be supplied on request with postage please.

**WEYRAD (ELECTRONICS) LIMITED**  
SCHOOL STREET, WEYMOUTH, DORSET

# NOW

FROM THE DESIGNER OF  
THE FIRST RECORD  
PLAYING PLINTH AND COVER

A design engineered Metal Plinth beautifully styled. Robustly constructed, brushed silver finish to match most equipment. All plinths are supplied with tinted transparent perspex covers.

THESE UNITS ARE AVAILABLE WITH ANY OF THE GARRARD RANGE OF TURNTABLES FITTED, WIRED AND COMBINE ATTRACTIVE APPEARANCE AND ECONOMY AT RECOMMENDED PRICES FROM UNDER £20.

**SM6 Plinth and Cover .. £7-50**    **SM5 Plinth and Cover .. £8-50** This is a larger plinth than SM6 and can be used with cover in position when playing record.  
**SM4 Plinth and Cover .. £9-50**    Suitable for AP75, AP76, SL75, SL95.

SM6 with Garrard Autochanger 2025 with Sonotone 9TA/HC stereo cartridge, 4 speeds, auto/manual facilities

SM6 with Garrard SP25 Mk. III. 3-speed single playing deck with cueing, bias and counterbalance facilities. Automatic stop at end of record. Plug-in cartridge shell. Less cartridge

SM6 as above but with Sonotone 9TA/HC stereo cartridge with diamond stylus

SM6 as above but with Goldring G800H magnetic stereo cartridge and diamond stylus

SM6 with Garrard SL65 3-speed Autochanger with manual facilities cueing, bias, stylus pressure counterbalance. 2-pole motor. Plug-in cartridge shell, but less cartridge

SM4 with Garrard AP76 3-speed single playing deck with dynamically balanced gimbal pick-up arm and with cueing and bias facilities, with Goldring G800 magnetic stereo cartridge



See these Plinths and Covers at your local Hi-Fi stockist or complete coupon for leaflet and details.

# ICP

**HAINAULT HOUSE**  
**HAINAULT ST. LONDON SE9**  
**TELEPHONE 01 850 0828**

To: ICP HAINAULT HOUSE, HAINAULT ST.  
LONDON, SE9

Dept. PW

Please send details of your Metal Plinths.

NAME .....

ADDRESS .....

PLEASE USE BLOCK LETTERS



# 2-Octave

## miniature Organ



F. C. JUDD

### PART 1

### ★ components list

As a "one off" project, the simple electronic organ described here is not a difficult one and actually involves more carpentry than electronics. Moreover, a half scale version of the real thing has tremendous appeal to young children and if you have junior members in the family, there could be a large demand for a project of this type. The prototype, shown on the front cover, was in fact patterned on a full size electronic organ and is approximately a half scale version.

The circuit employs only four transistors and it comprises a multi-vibrator tone generator, a vibrato oscillator and an amplifier stage providing quite a reasonable output. The organ has a two octave keyboard with a range from F at 174.6Hz to F at 698.4Hz. The vibrato can be switched on or off and there is a choice of two 'voices', one being slightly reedy and the other a softer flute-like sound. There is also an "expression" pedal which, although mechanical, provides the young player with some control over loudness. The organ uses a standard 9V battery from which the total current drain is about 20mA.

#### Resistors

R1	8.2kΩ	R9	3.9kΩ
R2	8.2kΩ	R10	4.7kΩ
R3	8.2kΩ	R11	18kΩ
R4	1.5kΩ	R12	56kΩ
R5	5.6kΩ	R13	56kΩ
R6	2.7kΩ		
R7	347kΩ		

All  $\frac{1}{2}$  or  $\frac{1}{4}$ W, 10% types

#### Capacitors

C1	250μF	C6	0.05μF
C2	1.5μF	C7	0.01μF
C3	1.5μF	C8	10μF
C4	1.5μF	C9	0.1μF
C5	100μF	C10	0.47μF

All electrolytics at least 10V working

#### Semiconductors

Tr1	OC71 or NKT213	Tr3	OC71 or NKT213
Tr2	OC71 or NKT213	Tr4	OC81

#### Miscellaneous

25-off  $\Omega$  01k preset skeleton pots, miniature type,  
1-off 50kΩ preset skeleton pot, miniature type, small  
loudspeaker, round or elliptical, 25-40Ω, 2-off  
switches, press on/off types, on-off toggle switch.

### THE ELECTRONICS

The circuit for the tone generator, vibrato oscillator and amplifier is shown in Fig. 1. Tr1 is a phase shift oscillator and runs at about 6 to 8Hz, the output from the junction of C2/R1 being taken to the base of Tr2 which is one half of the multi-vibrator tone generator. The output from Tr2/Tr3 is a typical multi-vibrator waveform and the frequency range is governed by the series connected 10kΩ preset potentiometers marked F1, F#2, G3 etc., between the base of Tr3 and the negative supply rail. The 50kΩ pre-set, PR1, is for adjustment of initial pitch. The output from Tr2/Tr3 is taken directly to the amplifier-cum-tone forming circuit, Tr4, and with a 25-40Ω small loudspeaker the nominal output is about 0.5W. The voicing is a very simple arrangement by means of

### ★ materials list

Plywood and hardboard to sizes in diagrams.  
1 x 1/2 in planed batten for keys, approx. 9ft.  
Felt or foam plastic 1/2 to 1/4 in wide approx. 20in.  
1 x 1/2 aluminium angle, 10in.  
16s. w.g. aluminium for brackets.  
Thin countersunk head woodscrews for key springs  
and contact guides, 75 off (these should not be  
more than 1/2 in long).  
Material for main front panel (speaker grill material).  
Sundry screws and glue.  
Tagstrip, 9in long.  
Gold clad wire (organ contact wire) 6ft (Henry's Radio  
Limited).  
Light tension springs approx. 1/2 in long, 25 off.

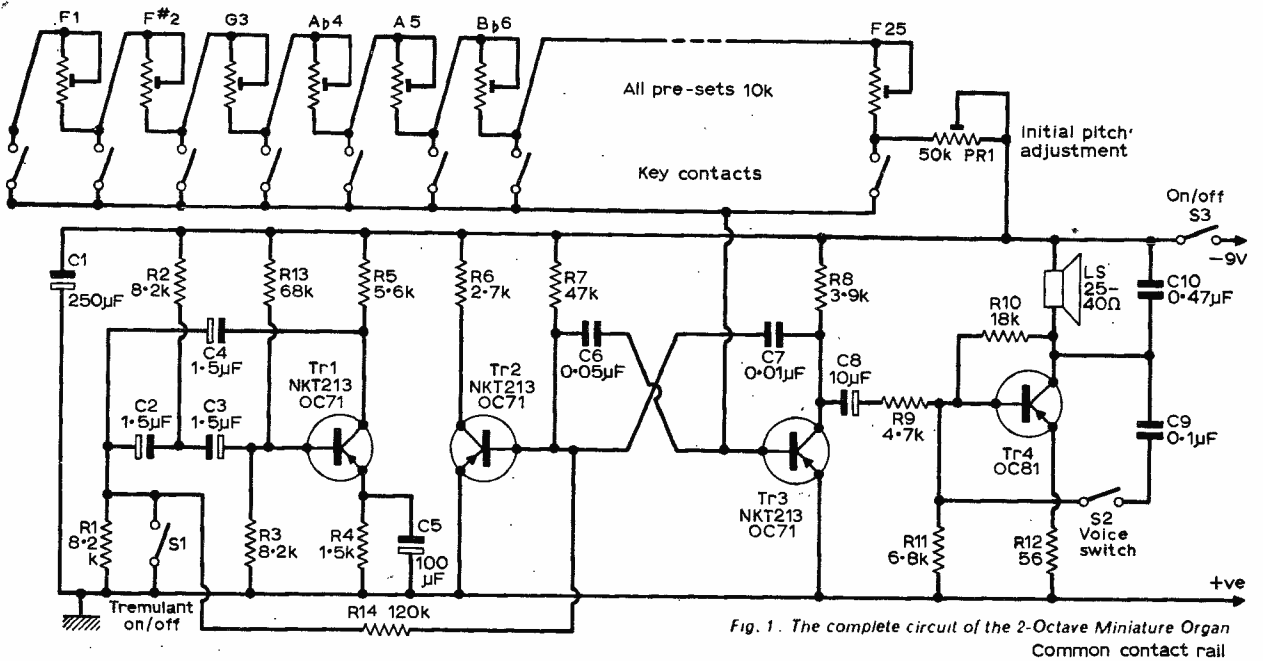


Fig. 1. The complete circuit of the 2-Octave Miniature Organ  
Common contact rail

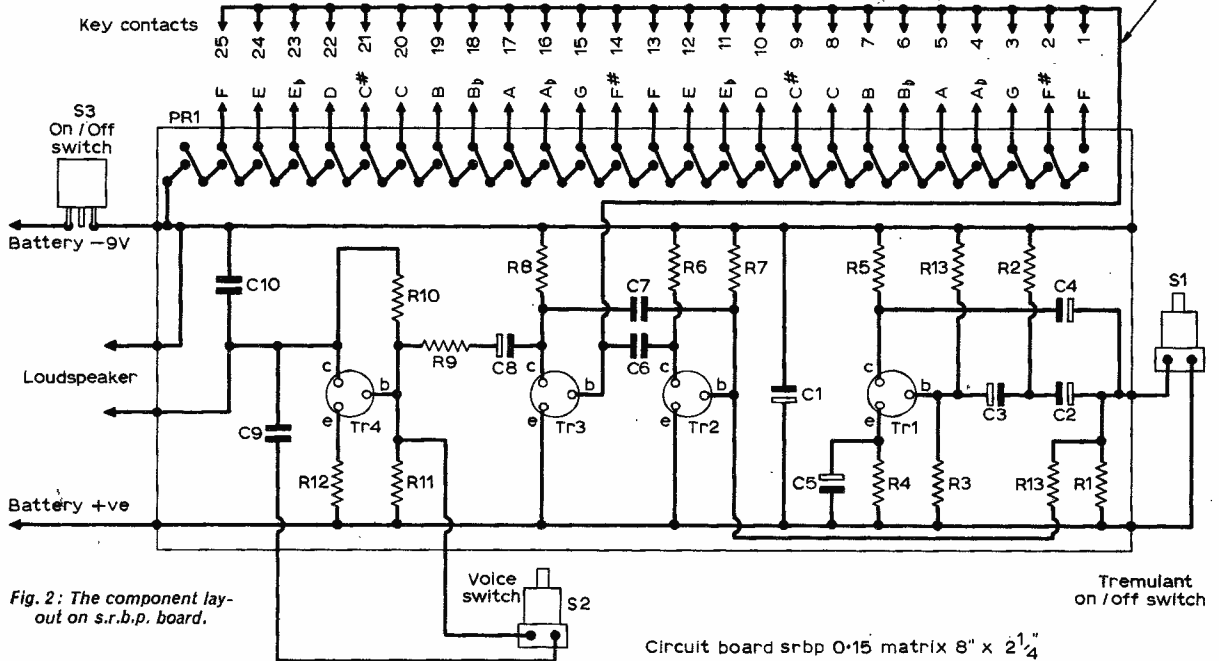


Fig. 2: The component layout on s.r.b.p. board.

Circuit board srbp 0.15 matrix 8" x 2 1/4"

negative feedback and gives two voices, one with a 'reed' sound and the other a 'flute' sound.

All the components, including the 25 miniature pre-sets, can be mounted on a piece of plain Veroboard 8 x 2 1/4 in. which is secured to the key base-board with a short strip of 3/8 x 3/8 in. aluminium angle or a small bracket either end. The component layout and wiring for the circuit board is shown in Fig. 2.

## CONSTRUCTION

The various diagrams show the dimensions used for the original, but these can be varied so long as similar space is provided for the keyboard and the electronics. A supply of assorted sizes of woodscrews and some glue are required for assembly and these,

together with the pieces of plywood, hardboard and planed batten etc., should be readily available from timber merchants or d.i.y. shops.

The main case should be built first, as shown in Fig. 3 and assembled complete with the inside shelf (for the keyboard etc.) and the rail at the rear on which the lid is hinged. The batten under the front edge of the inside shelf is used to support the upper front panel. An inside speaker baffle is necessary if the expression pedal feature is to be incorporated, otherwise the speaker can be mounted directly on the main front panel. In this case the speaker opening will be appropriate to the loudspeaker used and the cut out for the expression pedal will not be required.

The expression pedal is a simple mechanical

## SPECIAL PURCHASE!

### BRAND NEW FM MULTIPLEX STEREO DECODER UNITS.

Manufactured by PHILIPS. Size 9" x 3 1/2" x 1 1/2". All transistor 24v. at 6 mA. Supplied pre-aligned with full circuit diagram and connection details. £4 each Post Free.

### FEW ONLY—LEAK MK I TRANSCRIPTION PICK-UP ARMS

Using the world famous gimbal pivot system. Complete but less pick up head. £2.50 P. & P. 20p

### INPUT MATCHING TRANSFORMER

Beautifully made in heavy Mu-metal cylindrical case for minimum hum pick-up. Size 1 1/2" high x 1 1/2" dia. Ratio 150:1 approx. Especially suitable for matching dynamic or ribbon mikes or pick up from low to high impedance or vice versa. 75p each Post Free

### BLACK ANODISED 16g. ALUMINIUM HEAT SINKS

For TOS, complete with mica's & bushes. Size 2 1/2" x 3" approx. 25p pair P. & P. 5p.

## HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



### NEW IMPROVED MODEL WITH HIGHER OUTPUT AND IMPROVED SOUND. HIGH QUALITY READY DRILLED PRINTED CIRCUIT BOARD FOR EASY CONSTRUCTION

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Output stage for any speakers from 5 to 16 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled printed circuit board, attractive front panel, knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output: 14 watts r.m.s. per channel into 5 ohms. Frequency response ±3dB 12-30,000 Hz Sensitivity: better than 80mV into 1MΩ. Full power bandwidth: ±3dB 12-15,000 Hz. Bass boost approx. to ±12dB. Treble cut approx. to -16dB. Negative feedback approx. 15dB over main amp. Power requirements 25v. at 1.0 amp. Overall Size 12" w. x 8" d. x 2 1/2" h. Fully detailed 7 page construction manual and parts list free with kit or send 18p plus large S.A.E.


**PRICES**  
AMPLIFIER KIT . . . £10.50 P. & P. 15p  
POWER PACK KIT . . . £3.00 P. & P. 20p  
CABINET . . . £8.00 P. & P. 30p  
(Post Free if all units purchased at same time)  
Full after sales service

Also available ready built and tested £20.50. Post free.  
*Note: The above amplifier is suitable for feeding two mono source into separate (e.g. mikes, radio, twin record decks, etc.) and will provide mixing and fading facilities for medium powered Hi Fi Discotheque use, etc.*
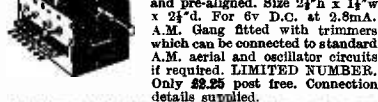
### SPECIAL PURCHASE OF MANUFACTURERS SURPLUS!

All Transistor P.M. tuner head with twin A.M. Gang incorporated. Beautifully engineered with precision geared reduction drive. FM RF Transistor, oscillator/Mixer and first I.F. stage (10.7 Mc/s) output with optional AFC connection.

Built on printed circuit panel and fully screened. Extremely stable over range 88-108Mc/s. Brand new and pre-aligned. Size 2 1/2" x 1 1/2" x 2 1/2". For 6v D.C. at 2.8mA. A.M. Gang fitted with trimmers which can be connected to standard A.M. aerial and oscillator circuits if required. LIMITED NUMBER. Only £2.25 post free. Connection details supplied.



**HIGH GRADE COPPER LAMINATE BOARDS.** 8 x 6 x 1/16 in. FIVE for 50p. P. & P. 13p.

**TELEPHONE AERIALS WITH SWIVEL JOINT.** They are angled and rotated in any direction. Section lacquered Brass. Extends from 6 to 29 1/2 in. approx. Maximum diameter 1/8 in. 25p each. P. & P. 5p.

**BRAND NEW MULTI-RADIO MAINS TRANSFORMERS.** Giving 13 alternatives. Primary: 0-210-240v. Secondary combinations 0-5-10-15-20-25-30-35-40-60v. half wave at 1 amp. or 10-0-10, 20-0-20, 30-0-30v. at 2 amps full wave. Size 3 1/2 in. long x 3 1/4 in. wide x 3 in. deep. Price £1.75 P. & P. 30p.

**MAINS TRANSFORMER.** For transistor power supplies. Pri. 200/240v. Sec. 0-0-9 at 500mA. 70p. P. & P. 13p. Pri. 200/240v. Sec. 12-0-12 at 1 amp. 85p. P. & P. 15p. Pri. 200/240v. Sec. 10-0-10 at 2 amp. £1.38. P. & P. 30p. Tapped Primary 200-220-240v. Sec. 21.5v. at 500mA. 68p. P. & P. 13p.

Open 9-5.30 Monday to Saturday

Early closing Wed. 1 p.m.

A few minutes from South Wimbledon Tube Station.

## SPECIAL OFFER! HI-FI LOUDSPEAKER SYSTEMS

Beautifully made teak finish enclosure with most attractive Tygan-Uynar front. Size 18 1/2" high x 10 1/2" wide x 5 1/2" deep. Fitter with E.M.I. Ceramic Magnet 18" x 8" bass unit, two H.F. tweeter units and crossover. Power handling 10 watts. Available 3 or 8 or 15 ohms impedance.

### OUR PRICE £8.40 Carr. 60p

Cabinet Available Separately £4.50 Carr. 60p  
Also available in 8 ohms with EMI 13" x 8" bass speaker with parasitic tweeter £6.50 Carr. 60p

### LOUDSPEAKER BARGAINS

3" x 4 ohm 60p, P. & P. 8p. 5in. 2 ohm 80p, P. & P. 15p. 7" x 4in. 3 ohm £1.05, P. & P. 30p. 10" x 6in. 3 or 16 ohm £1.90, P. & P. 30p. E.M.I. 8" x 6in. 8 ohm with high flux magnet £1.82. P. & P. 20p. E.M.I. 12 1/4" x 5in. 3 ohm with high flux ceramic magnet £2.10 (15 ohm £2.25), P. & P. 30p. E.M.I. 13" x 8in. 3 or 16 ohm with two inbuilt tweeters and crossover network £4.20, P. & P. 30p. E.M.I. 18" x 8" twin cone (parasitic tweeter) 8 ohm £2.25 P. & P. 30p.

**BRAND NEW.** 12in. 15w. H/D Speakers, 3 or 15 ohms. Current production by well-known British maker. Now with Hifur ceramic ferrobar magnet assembly £5.50. Guitar models: 25w. £6.50, 35w. £8.50. P. & P. 35p. E.M.I. 3 1/2in. HEAVY DUTY TWEETERS. Powerful ceramic magnet. Available in 3 or 8 or 15 ohms 95p each. P. & P. 18p.

12in. "BA" TWIN CONE LOUDSPEAKER. 10 watts peak handling, 3 or 15 ohm £2.20, P. & P. 30p. 35 ohm SPEAKERS 3in. only 68p. P. & P. 18p.

**VYNAL & REKINE SPEAKERS & CABINET FABRIC** app. 54 in. wide. Usually £1.75 yd., our price 75p yd. length. P. & P. 15p (min 1 yd.) S.A.E. for samples.

### HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexifoam ear-muffs. Wired and fitted with standard stereo 1/8 jack plug. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. PRICE £2.95. P. & P. 15p.

**SINGLE HEADPHONE.** With aluminium headband. Approx. 200 ohm. 25p. P. & P. 8p

**CRYSTAL MIKES.** High imp. for desk or hand use. High sensitivity. 85p. P. & P. 8p

**HIGH IMPEDANCE CRYSTAL STICK MIKES.** OUR PRICE £1.05. P. & P. 8p

### GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P.U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 3-15v. battery or from H.T. line 200/300v. Frequency response 15Hz-25KHz. Gain 26dB. Solid encapsulation size 1 1/2" x 1 1/2" x 1". Brand new complete with instructions. Price 85p. P. & P. 13p.

### BRAND NEW E.M.I. LIGHTWEIGHT PICK-UP ARM WITH ARM REST, STYLUS AND STYLUS AND CARTRIDGE FOR LP/78. ONLY £1. P. & P. 13p.

**QUALITY RECORD PLAYER AMPLIFIER MK II** A top quality record player amplifier employing heavy duty double wound mains transformer, EOC88, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. wide x 8in. deep x 6in. high. Ready built and tested. PRICE £8.75. P. & P. 40p

ALSO AVAILABLE mounted on board with output transformer and speaker ready to fit into cabinet below. PRICE £4.85 P. & P. 50p.

**DELUXE QUALITY PORTABLE R/P CABINET MK II.** UNLTD motor board size 14 1/2 x 12in. clearance 9in. below, 5 1/2in. above. Will take above amplifier and any B.S.R. or GARRARD changer or Single Player (except AT60 and SP25). Size 18 x 15 x 8in. PRICE £3.98. P. & P. 50p.

### 10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, EOC88, EF86 and E280 rectifier. Simple instruction booklet 13p (Free with parts). All parts sold separately. ONLY £7.97 P. & P. 55p. Also available ready built and tested complete with std. input sockets, £9.87. P. & P. 55p.


**BRAND NEW TRANSISTOR BARGAINS. GET 15 (Matched pair) 75p; V15/10p 50p; OC71 25p; OC76 30p; AF17 15p; 26889 (NPN) 15p.** Set of Mullard 6 transistors OC44, 2—OC45, AC128D matched pair AC128 £1.25; ORP12 Cadmium Sulphide Cells 55p. All post free.

**BRAND NEW TRANSISTOR BARGAINS. GET 15 (Matched pair) 75p; V15/10p 50p; OC71 25p; OC76 30p; AF17 15p; 26889 (NPN) 15p.** Set of Mullard 6 transistors OC44, 2—OC45, AC128D matched pair AC128 £1.25; ORP12 Cadmium Sulphide Cells 55p. All post free.

## SPECIAL PURCHASE! SPEAKER CABINET FROM FAMOUS MAKER!

Beautifully made all wooden construction cabinet with medium waldat finish front, gold anodised expanded aluminium grille and dark sides. Approx. size overall 11 1/2" high x 5" deep x 13 1/2" wide at base. Easily removable baffle cut out for 8" speaker. Fibre board back. Could accommodate smaller or radio together with speaker. An expensively made cabinet at a give away price. LIMITED NUMBER ONLY £1.98 Post Free.

### DE LUXE STEREO AMPLIFIER

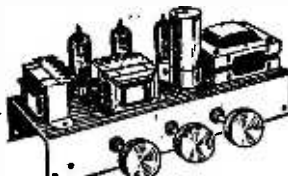

Valve line up:—2 x ECL86 Triode Pentodes. 1 x E280 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" w x 4" d. Overall height including valves 5". Ready built & tested to a high standard. PRICE £3.92 P. & P. 45p

### 4-SPEED RECORD PLAYER BARGAINS

Main models. All brand new in maker's packing. LATEST B.S.R. C100/AS1 4-SPEED AUTOMATIC. With latest mono compatible cartridge £6-97 Carr. 50p. With stereo cartridge £7-97 Carr. 50p. SUITABLE PLINTH UNIT FOR ABOVE with rigid plastic cover. £5-75 complete P. & P. 50p.

**LATEST GARRARD MODELS.** All types available 1025; 2025, SP25, 3000, AT80 etc. S.A.E. for latest Prices! PLINTH UNITS cut out for Garrard Models, 1025, 2025-2000, 3000, 3500 etc. With rigid transparent plastic cover. Special design enables above models to be used with cover in position. Also suitable for housing AT60 and SP25. OUR PRICE £5.75 complete. P. & P. 50p.

**LATEST ACOG GP81/18C** mono compatible cartridge with h/c stylus for LP/EP/78. Universal mounting bracket. £1.50 P. & P. 8p.

**SONOPHON STARG COMPATIBLE STEREO CARTRIDGE T/O STYLUS** Diamond Stereo LP and Sapphire 78. ONLY £2.50 P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. £3. P. & P. 10p.

**LATEST RONETTE T/O STEREO/COMPATIBLE CARTRIDGE** for EP/LP/Stereo/78. £1.63 P. & P. 10p. **LATEST RONETTE T/O MONO COMPATIBLE CARTRIDGE** for playing EP/LP/78 mono or stereo records on mono equipment. Only £1.50 P. & P. 10p.



**3-VALVE AUDIO AMPLIFIER HA34 MK II.** Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" w. x 4 1/2" d. x 4 1/2" h. Incorporates EOC88, EL84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £4.75. P. & P. 35p.

**HSL "FOUR" AMPLIFIER KIT.** Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. £3.98. P. & P. 40p.

**HARVERSON'S SUPER MONO AMPLIFIER** A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. AC mains 200/240v. Supplied absolutely Brand New completely wired and tested with good quality output transformer. FEW ONLY. BARGAIN PRICE £2.75 P. & P. 55p

### HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES

A must for servicemen and home constructors. 1971 edition including many 1000's of British, U.S.A., European and Japanese transistors. ONLY 40p Post 5p.

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

## HARVERSON SURPLUS CO. LTD.

170 HIGH ST., MERTON, LONDON, S.W.19

Tel.: 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES



# STROBE! STROBE!

Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/240V a.c. operation. **EXPERIMENTERS' ECONOMY KIT** Speed adjustable 1 to 36 Flash per sec. All electronic components including Veroboard S.C.R., Unijunction Xenon Tube and instructions £6.30 plus 25p P. & P.

**NEW INDUSTRIAL KIT** Ideally suitable for schools, laboratories, etc. Roller thin printed circuit. New trigger coil, plastic thyristor. Speed adjustable 1-80 f.p.s. Price £10.50. P. & P. 50p.

**HY-LIGHT STROBE MK III** This strobe has been designed and produced for use in large rooms, halls and the photographic field, and utilizes a silica plug-in tube for longer life expectancy, printed circuit for easy assembly, also a special trigger coil and output capacitor. Speed adjustable 0-30 f.p.s. Light output approx. 4 joules. Price £12.00 P. & P. 50p.

**SPECIALLY DESIGNED FULLY VENTILATED METAL CASE** including reflector. £4.00. P. & P. 45p Post Paid with kits.

## AND NOW! THE 'SUPER' HY-LIGHT KIT

Approx. four times the light output of our well proven Hy-Light strobe.

- Heavy duty power supply.
- Variable speed from 1-23 flash per sec.
- Fantastic Octal based tube with massive electrodes.
- Reactor control circuit producing an intense white light.

The brilliant light output of the SUPER HY-LIGHT gives fabulous effects with colour filters. Never before a Strobe Kit with so HIGH an output at so LOW a price. ONLY £20 plus 75p P. & P.

**ATTRACTIVE, ROBUST, FULLY VENTILATED METAL CASE** specially designed for the Hy-Light Kit. Including reflector £7.00. P. & P. 45p. 7-inch **POLISHED REFLECTOR** Ideally suited for above Strobe kits. Price £5p. P. & P. 13p or post paid with kits.

**VENNER ELECTRIC TIME SWITCH**

200/250V Ex. GPO. Tested. Manually set 2 on, 2 off every 24h. Override switch: 10A £2.75, 15A £3.25, 20A £3.75. P. & P. 20p. Also available with solar dial ON dusk, OFF dawn. Price as above.

## BODINE TYPE N.C.I. GEARED MOTOR

(Type 1) 71 r.p.m., Torque 10lb. inch. Reversible. 1/70th h.p., 50 cycle, 0.38 amp. (Type 2) 28 r.p.m., Torque 20lb. inch. Reversible. 1/80th h.p., 50 cycle, 0.28 amp. "As new" condition. Input voltage of motor 115V a.c. Supplied complete with transformer for 230/240V a.c. input. Price, either type £3.15 plus 35p P. & P. or less transformer £2.13 plus 27p P. & P.

## ELECTRONIC ORGAN KIT

Easy to build, Solid State. Two full octave (less sharps and flats). Fitted hardwood case. Powered by two penlite 1.5V batteries. Complete set of parts including speaker etc., together with full instructions and 10 tunes. Price £3.00. P. & P. 22p.

**50 in 1 ELECTRONIC PROJECT KIT** 50 easy to build Projects. No soldering, no special tools required. The kit includes Speaker, Meter, Relay, Transformer, plus a host of other components and a 56-page instruction leaflet. Some examples of the 50 possible Projects are: Sound Level Meter, 2 Transistor Radio, Amplifier, etc. Price £7.75. P. & P. 30p.

**CRYSTAL RADIO KIT** Complete set of parts, including Crystal Diode, Ferrite Aerial, Drilled Chassis and Personal Ear Piece. No soldering, easy to build, full step by step instructions. £1.75 inc. post.

**RECHARGEABLE BATTERY CELLS** 2 x 1.2V, 250 MA HR Nickel Cad. Cells, connected to give 2.4V @ 25 milliamp 10 hour rate. complete with 200/250V a.c. charger. Fully tested and unused Price 48p each plus 8p P. & P. or 2 units for £1.00 post paid.

# SERVICE TRADING CO

All Mail Orders. Also Callers, Parking Space. Dept. PW11, 57 BRIDGMAN ROAD, LONDON W4 5BB. Phone 01-995 1560. Showrooms now open, Mon.-Fri.

Personal Callers only. Open SAT. 9 LITTLE NEWPORT ST. LONDON. WC2H 7JJ 01-437 0576.

- PIEZO DYNAMIC MICROPHONE** 50k £1.00 pp 6p
- MULLARD BOREW TERMINAL CAP** 4,500uf 04v 50p pp 15p.
- BELLING LEE 1-5 amp in-line rubber covered interference suppressor** 25p pp 8p.
- SOLENOIDS 18 VOLT PULL ACTION** 2" x 1" x 1" 40p pp 8p.
- STC SEALED RELAYS DOUBLE POLE CHANGEOVER** 48v 2500 Ex-equip. 15p pp 5p. Miniature 12v 280 New 2 changeover 40p pp 5p new.
- SIEMENS MINIATURE RELAY.** Double pole changeover dust cover/base 48v 2500 50p pp 5p new.
- TELESCOPIC AERIALS** Chromed. 7" closed 28" extended 6 section ball jointed base 25p pp 8p new.
- MULLARD 4 DM 160 INDICATORS** in plastic holder/cover ex-equip. size approx. 1 1/2" x 1 1/2" x 1 1/2" 38p pp 8p.
- PRINTED CIRCUIT BOARD/19 ACY 19's 10 OA200** Diodes: 1 rect relay: 10 A 229 zener ass. capacitor/resistors. Power supply 23v 250 mA DC. Output 240v. AC £1 pp 20p ex-equip.
- TOGGLE SWITCHES.** Single pole Double Throw ex-equip. new condition. 50p doz. pp 13p.
- FIBRE GLASS TAPE.** 100 yd. roll: 3" 3 1/2" wide £1 per roll pp 20p.
- PAINTON PLUG SOCKETS** Type 159 series working voltage 350v AC/DC current max. 3 amp AC/DC 7 pin plug & socket 50p pp 10p. 15 pin plug & socket £1 pp 10p.

CASH WITH ORDER PLEASE

# FIELD ELECTRIC LIMITED

3 SHENLEY ROAD, BOREHAMWOOD, HERTS. Adjacent Elstree Mainline Station Tel: 01-953 6009.

## Vary the strength of your lighting with a DIMMASWITCH



The DIMMASWITCH is an attractive and efficient dimmer unit which fits in place of the normal light switch and is connected up in exactly the same way. The ivory mounting plate of the DIMMASWITCH matches modern electric fittings. Two models are available, with the bright chrome knob controlling up to 300w or 600w of all lights except fluorescents at mains voltages from 200-250V, 50Hz. The DIMMASWITCH has built-in radio interference suppression:

- 600W—£3.20, Kit form £2.70
- 300W—£2.70, Kit form £2.20


All plus 10p. post and packing.

Please send C.W.O. to:—

## DEXTER & COMPANY

2 ULVER HOUSE, 19, KING STREET, CHESTER CH1 2AH Tel: 0244-25883, As supplied to H.M. Government Departments.

# BETTER GET 'SET'

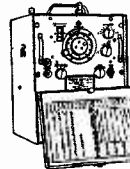

**BEST OFFER YET! FAMOUS BC.221 FREQUENCY METER** 125 KHz—20 MHz. Complete with valves, crystal and charts. ONLY £18.50. Carr. £1.50. Less charts £8, carriage £1.50. Less charts & crystal £5, carriage £1.50

## CRYSTAL CALIBRATOR

**No. 10** Crystal controlled heterodyne wave-meter covering 500 KHz—10 MHz (Harmonics up to 30 MHz). Power required 300V. D.C. 16mA. 12v. 0-3A. D.C. Test equipment for 62TM/RC.



ONLY £4.25 P. & P. 50p. FEW ONLY—No. 62 TM/RC 1.5—10 MHz £17.50. Carr. £2.

**MARCONI 801A SIGNAL GENERATOR** 10—310 MHz. In original transit case. £45. Carr. £2.50.

## AERIAL MAST EQUIPMENT

**20' TELESCOPIC MASTS** £37.75. Carr. £1. 5' 2" Extension Sections to fit bottom of above mast to increase height. £1.25 each (any number supplied). **25' MAST** (7—5" interlocking sections) with base plate and 12 nylon guys with semi-auto tensioner. £22.50. Carr. £2.50. **70' MAST** Ditto. 16 guys, block and tackle. £45. Carr. £2.75.



## AERIAL RODS 3ft.

Screw-in 1" dia. sections. Brand New, green finish. Suitable for many other uses. 10 for £2. Carr. 50p. 25 for £5. Carr. Paid.

## R.F. ANTENNA TUNER (A.T.U.)

Cylinder design 10" x 4 1/2". Precision calibrated scale. Suitable for tuning most aeriels for increased signal strength. A must for serious operators for RC or TM. Full instructions. ONLY £1.75. P. & P. 25p.

## R.F. ANTENNA TUNER (A.T.U.) OPEN TYPE

Mounted on ceramic former and feet. "Roller Coaster" design 16 G silver or silver plated wheel traversing on wire on ceramic former. Will handle considerable R.F. In original packing. As used with No. 63 Transmitter. ONLY £2.50. P. & P. 50p.



## No. 19 SET TRANSMITTER RECEIVER

Rebuilt. Complete station with PSU, Cables, Mic, Aerial, etc. £22.50. Carr. £3.

## No. 19 SET 500uA METERS

Scaled 0-600 and 0-15V. Brand new, boxed £1.25 Post Paid. (Quantity prices on request.)

## ALL No. 17 SPARES IN STOCK

Complete instruction book with circuits for No. 19 Equipment. 87p Post Paid.

## HEAVY DUTY BATTERIES

New in metal cases with carrying handles. 6v. 85 AH 13" x 9 1/2" x 7" £3.25. Carr. £1.25



## LIQUID PRISMATIC COMPASSES

2" diameter £7.50, p. & p. 25p

## FAMOUS TELE 'F' FIELD TELEPHONES

Suitable for Farms, Building Sites etc. Communication up to 5 miles or more. Rugged construction, will last a lifetime. ONLY £5.75 PAIR. Carr. £1. (Twin telephone wire for above available—ask for price.) Many other Ex-Govt. Surplus Equipment items in stock. Receivers etc. in small quantities too numerous to mention. Enquiries invited. L/S £25 Post Paid. (Refundable against purchases over £3.) C.W.O. Carriage charges apply to Mainland only. Minimum Export Order £50.



## Surplus Electronic Trading

DRIVERS END LANE, CODICOTE, HITCHIN, HERTS, SG4 8TP  
Hours of business: 8-5 Mon.-Fri., 8-12 Sat. Telephone: Codicote 242 for appointment

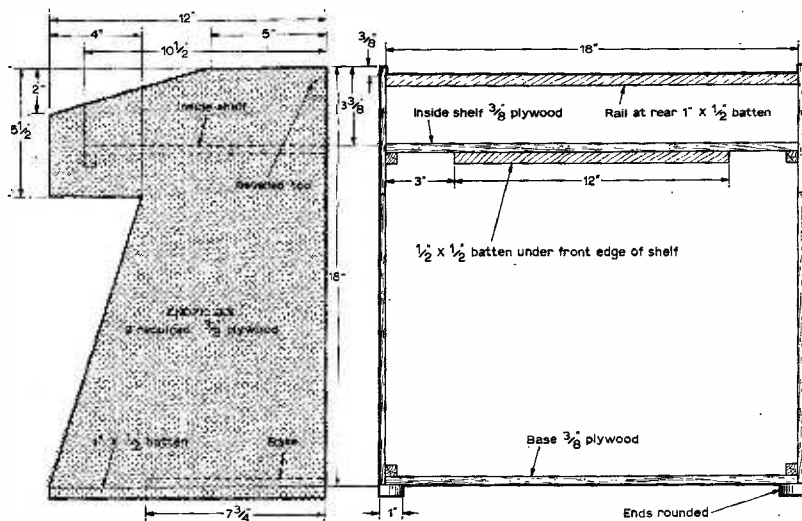


Fig. 3: Cutting dimensions for the main cabinet.

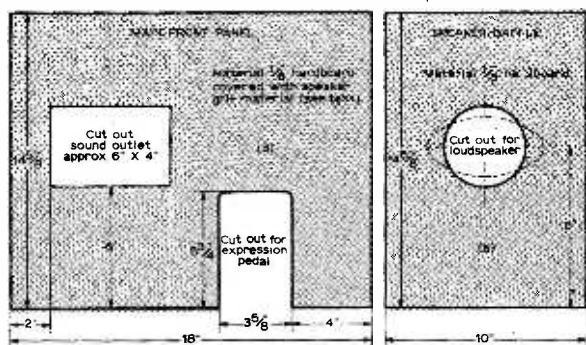


Fig. 4: Cutting details of the main front panel and speaker baffle.


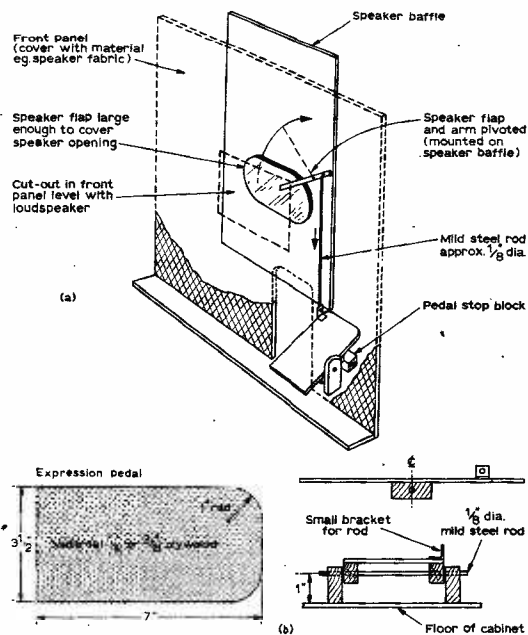


Fig. 5: Arrangement of the expression pedal.

arrangement that lifts a flap over the loudspeaker when the pedal is pressed downward. Although this only provides a small degree of change in loudness it is worthwhile including as it does at least simulate the use of an expression pedal. The general mechanical arrangement used for the prototype is shown in Fig. 5a. As the size of the speaker flap and the length of the arm attached to it may depend somewhat on the shape and size of the loudspeaker, no detailed dimensions have been given. All that is necessary however, is to ensure that the flap over the loudspeaker moves upward and clear of the speaker opening in the direction shown when the pedal is pressed downward. The arm on the flap, the position of the pivot and the length of the operating rod should be adjusted so that the flap just covers the speaker opening when the pedal is lifted. The position of the pedal stop block will help facilitate the correct amount of pedal movement.
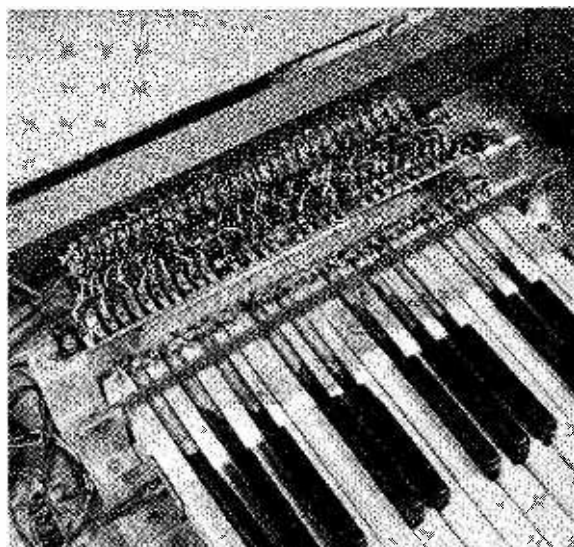
### THE KEYBOARD

This is the most difficult part because normally piano keyboards are cut from one piece so that they fit together precisely when reassembled on the frame. The keys for the children's electronic organ are slightly larger than half scale and are made separately. The general layout of the keyboard and the size of the white and black keys is shown in Fig. 6. The base is made from 3/8 in. thick plywood and the 'frame' consists of two end brackets and a length of 3/16 in. dia. mild steel rod. The best procedure is first to make the baseboard and the two end brackets (see Fig. 7b) and secure the left hand bracket in position as in Fig. 6. The spacers between each key are single turns of 22 s.w.g. wire, or if you



The completed keyboard of the prototype. The contact wires and the presets can be seen.

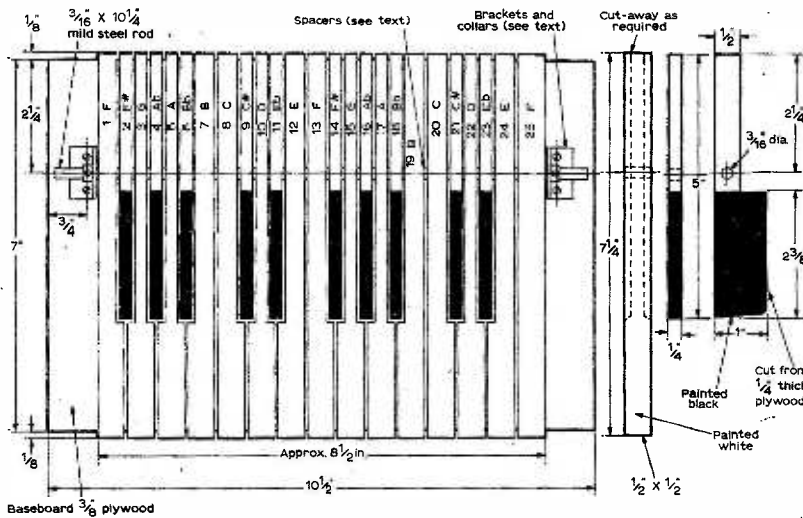


Fig. 6: Plan view of the keyboard with key dimensions given on the right.

to No. 1 with the right hand side only cut-away whilst keys No. 7, 12, 19 and 24 have only the left-hand side cut-away. The remaining key No. 25 has no cut-away.

First the 10 1/4 in. long mild steel rod should be ready to take the keys. Then make up the first half dozen keys, black and white, from No. 1 to No. 6. Cut and file the white keys until each fits snugly with its associated black key. Then proceed on the same lines until all the keys are made and fitted and, most important, numbered and marked as in Fig. 6.

Temporarily fit the remaining end bracket and ensure that the keys move up and down freely on the rod. They can now be removed and painted. Before re-fitting the keys secure the strip of hardboard along the rear of the key baseboard and the strips of felt under the keys as shown in Fig. 7a. When the keys have been re-assembled the rod can be secured with small brass collars each end as in Fig. 6 and 7a. Meccano collars were used originally but could be made quite easily from 3/8 in. dia. brass rod. Before fitting the tension springs as in Fig. 7a, make sure that each key moves freely up and down. The springs, which must not be too highly tensioned, are secured by small woodscrews as shown in Fig. 7c. When the springs have been fitted, make sure that each key moves freely downward with a light touch and returns to its upward position.

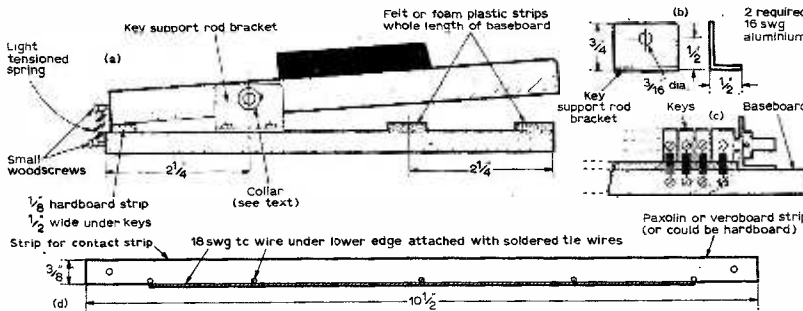


Fig. 7: Details of the keyboard construction.

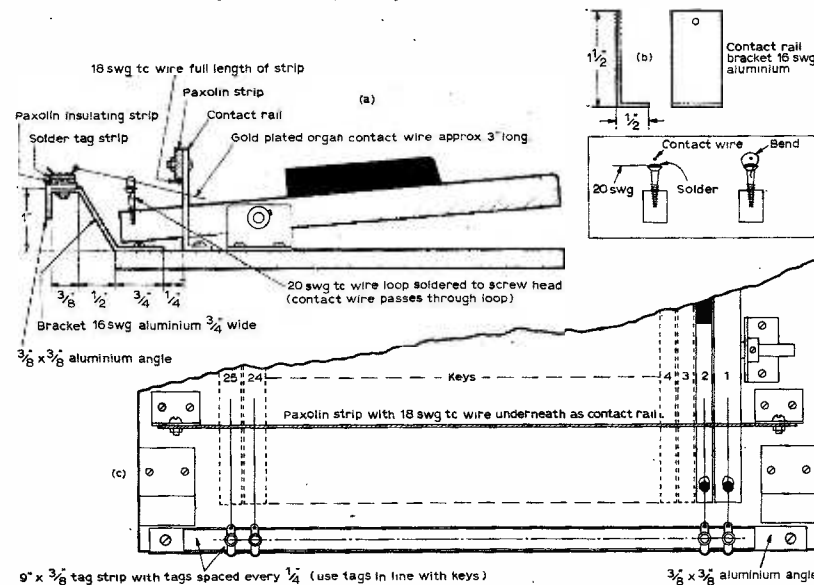


Fig. 8: Arrangement of the keying contacts—see text for explanation.

## KEYING CONTACTS

The keying contact system is a simple but effective one and the general assembly details for this are given in Fig. 8. The main contact rail as shown in Fig. 7d consists of a strip of insulating material such as paxolin (or hardboard would do) to which is secured a length of 18 s.w.g. tinned copper wire. This strip is fitted over the keys as in Fig. 8a by means of two brackets

can get them, 3/16 in. washers of similar thickness e.g. 1/32 in. It will be seen from Fig. 6 that the cut-away portions on each of the white keys varies according to its position. For instance, key No. 1 is cut-away only on one side to fit with the black key No. 2. Key No. 3 and also keys 5, 10, 15, 17 and 22 have cut-aways on both sides. Keys No. 8, 13 and 20 are similar

(Fig. 8b). The gold wire contacts, one for each key, are fitted as shown in Fig. 8 to a solder tag strip mounted on a length of 3/8 in. aluminium angle which is secured on two brackets projecting over the end of the baseboard as in Fig. 8a. Before fitting this assembly to the baseboard, small countersunk woodscrews are fitted one to each key and about

# ATTRACTIVE DISCOUNTS

# ELECTROVALUE Electronic Component Specialists

EVERYTHING BRAND NEW & TO SPEC • LARGE STOCKS • NO SURPLUS

## BARGAINS IN NEW SEMI-CONDUCTORS

MANY AT NEW REDUCED PRICES • ALL POWER TYPES WITH FREE INSULATING SETS

40361	55p	2N2905	44p	2N4291	15p	BC148	9p	BFX87	29p
40362	68p	2N2905A	47p	2N4292	15p	BC149	10p	BFX88	26p
2N696	17p	2N2924	20p	AC107	46p	BC153	18p	BFY50	23p
2N697	18p	2N2925	22p	AC126	30p	BC154	20p	BFY51	20p
2N706	12p	2N2926	11p	AC127	20p	BC157	18p	BFY52	23p
2N930	28p	2N3053	27p	AC128	20p	BC158	11p	BHX20	18p
2N1131	29p	2N3055	60p	AC153K	22p	BC169	12p	C407	17p
2N132	28p	2N3702	13p	AC176	16p	BC167	11p	MC140	25p
2N1302	18p	2N3703	13p	ACY20	20p	BC168	10p	MP8531	35p
2N1309	19p	2N3704	13p	ACY22	16p	BC169	11p	MP8534	30p
2N1304	26p	2N3705	13p	AD140	63p	BC177	14p	NKT211	25p
2N1305	28p	2N3706	13p	AD142	50p	BC178	13p	NKT212	25p
2N1306	33p	2N3707	13p	AD149	58p	BC179	14p	NKT214	23p
2N1307	32p	2N3708	10p	AD161	33p	BC182L	11p	NKT274	18p
2N1308	36p	2N3709	11p	AD162	36p	BC183L	10p	NKT403	65p
2N1309	36p	2N3710	13p	AF114	24p	BC194L	11p	NKT405	79p
2N1613	25p	2N3711	13p	AF115	24p	BC212L	18p	OC71	38p
2N1711	28p	2N3819	23p	AF117	23p	BC213L	18p	OC81	25p
2N1898	54p	2N3904	35p	AF124	24p	BC214L	16p	OC8D	25p
2N2147	95p	2N3906	35p	AF127	22p	BCY70	18p	ZTX300	14p
2N2218	34p	2N4058	18p	AF139	33p	BCY71	33p	ZTX301	16p
2N2218A	44p	2N4059	10p	AF239	36p	BFY72	15p	ZTX302	22p
2N2219	38p	2N4060	11p	ASV26	27p	BF115	23p	ZTX303	22p
2N2219A	53p	2N4061	11p	ASV28	27p	BF157	15p	ZTX304	27p
2N2370	68p	2N4062	12p	BC107	12p	BF173	18p	ZTX500	18p
2N2369A	19p	2N4124	18p	BC108	11p	BF194	14p	ZTX501	21p
2N2483	35p	2N4126	27p	BC109	12p	BF195	15p	ZTX502	25p
2N2484	42p	2N4284	15p	BC125	15p	BFX29	31p	ZTX503	22p
2N2646	47p	2N4285	16p	BC126	22p	BFX84	25p	ZTX504	52p
2N2904A	42p	2N4289	15p	BC147	10p	BFX55	32p		

Appointed distributors for  
**SIEMENS (U.K.) LTD.**

Appointed stockists for  
**NEWMARKET TRANSISTORS  
RADIOHM POTENTIOMETERS**

## SAVE £6.25 ON THE NEW ENGLEFIELD 840 AMPLIFIER

This latest Peak Sound high fidelity amplifier incorporates many strikingly original features including facility for adding in stereo FM tuner. Superb performance characteristics and luxurious styling. Electrovalue choice of simulated soft leather covering in black, blue, red or dark green. As now advertised at £49.50. Our price **£38.75** nett.

## MAINLINE AMPLIFIER KITS

70W. £12.60 nett. (main amplifier module).

## 30 WATT BAILEY AMPLIFIER PARTS

Transistors and PCB for one channel £8.48  
Capacitors, resistors (metal oxide), and transistors, one channel, £5.41.

Complete unregulated power supply pack, £4.75.  
Suitable heatsink 10DN 400C. 56p.

## SIEMENS TTL INTEGRATED CIRCUITS

We stock a very large range for a wide range of applications. For full details, see our latest catalogue.

## S-DeCS

Manufacturers' prices increase roughly by 20% on these on pages 51, 52 and 53 since printing our catalogue. S-DeC £1.44, Four pack £5.10, DeCSTOR pack £2.88, T-Dec, may be temperature-cycled (205 points), £2.88. µDeca, £3.18, µDecB, £5.94. Also I.C. carriers.

## INDICATOR LAMPS

NEON chrome bezel, round red NR/R, 24p; chrome bezel, round amber NR/A, 24p; chrome bezel, round clear NR/C, 24p. Neon, square red type LSC/P, 18p; amber type L55/A, 18p; clear type L55/C, 18p. All above are for 240V mains operation. Filament types: 6V, 0.04A square red type L55C/R-6V, 30p. 6V 0.04A amber type L55C/A-6V, 30p; 6V 0.04A clear type L55C/C-6V, 30p; 6V 0.04A green type L55C/G-6V, 30p; 12V 0.04A L55C/R-12V, 34p; 34V 0.04A L55C/R-28V, 45p.

## SIEMENS' 5% TOLERANCE POLYCARBONATE CAPACITORS

250V up to 0.1mF, 100V 0.1mF and above.  
0.27, 7p; 0.33, 0.39, 9p; 0.47, 10p; 0.56, 13p; 0.68, 15p.

## DIN CONNECTORS

Loudspeaker	2-pole	plug	socket
Audio	3-pole	12p	10p
Audio	4-pole	14p	12p
Audio	5-pole 180 deg.	15p	12p
Audio	5-pole 240 deg.	15p	12p
Audio	6-pole	15p	13p

Handbook of transistor equivalent and substitutes, 40p. (Postage 3p if ordered alone).

ELECTROVALUE 1971 CATALOGUE. 64 pages and covers. Packed with items and information. Post free 19p.

## RESISTORS 10% - 5% - 2%

Code	Power	Tolerance	Range	Values available	1 to 9	10 to 99 (see note below)	100 up
C	1/20W	5%	82 Ω-220K Ω	E12	9	9	7
C	1/8W	5%	4.7 Ω-470K Ω	E24	1	0-8	0-7
C	1/4W	10%	4.7 Ω-10M Ω	E12	1	0-8	0-7
C	1/2W	5%	4.7 Ω-10M Ω	E24	1-2	1	0-9
MO	1W	10%	4.7 Ω-10M Ω	E12	2-5	2	1-9
WW	1/2W	2%	10 Ω-1M Ω	E24	4	3-5	3
WW	3W	10% ± 1/20 Ω	0.22 Ω-3.9 Ω	E12	7	7	6
WW	3W	5%	12 Ω-10K Ω	E12	7	7	6
WW	7W	5%	12 Ω-10K Ω	E12	9	9	8

Codes: C = carbon film high stability low noise  
MO = metal oxide ElectroSil TR5 ultra low noise  
WW = wire wound Plessey.

Values:  
E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades.  
E24 denotes series: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

Prices are in pence each for same ohmic value and power rating, NOT mixed values. (Ignore fractions of 1p. on total value of resistor order)

## MULLARD polyester C280 series

250V 20% 0.01; 0.022; 0.033; 0.047 3p ea. 0.068; 0.1, 0.15 4p, 0.22 5p, 0.33 7p, 0.47 8p, 0.68 11p, 1µF 14p, 1.5µF 21p, 2µF 24p.

## MULLARD SUB-MIN ELECTROLYTIC

C426 range axial lead 6p each  
Values (µF/V): 0.64/64; 1/40; 1.6/25; 2.5/16; 2.5/64; 4/10; 4/40; 5/64; 6.4/64; 6.4/25; 8/4; 8/40; 10/2.5; 10/16; 10/64; 12.5/25; 16/40; 20/16; 20/64; 25/64; 25/25; 32/4; 32/10; 32/40; 32/64; 40/16; 40/25; 50/64; 50/25; 60/40; 64/4; 64/10; 80/2.5; 80/16; 80/25; 100/64; 125/4; 125/10; 125/16; 160/2.5; 200/64; 200/10; 250/4; 320/2.5; 320/64; 400/4; 500/2.5.

## LARGE CAPACITORS

High ripple current types: 1000/25 28p; 1000/50 43p; 1000/100 82p; 2000/25 37p; 2000/50 57p; 2000/100 2144; 2500/64 77p; 2500/70 88p; 5000/25 62p; 5000/50 2110; 5000/100 £2.81; 10000/50 £2.40.

## ★ COMPONENT DISCOUNTS

10% on orders for components for £5 or more. 15% on orders for components for £15 or more (No discount on nett items).

## POSTAGE AND PACKING

Free on orders over £2. Please add 10p if orders under £2. Overseas orders welcome: carriage and insurance charged at cost.

U.S.A. CUSTOMERS: U.S.A. orders charged at prices as advertised by ELECTROVALUE AMERICA, P.O. Box 27, Swarthmore, PA 1908.

## ZENER DIODES

5% full range E24 values; 400mW: 2.7V to 30V 15p each  
1W: 6.8V to 82V 27p each 1.5W: 4.7V to 75V 60p each  
Clip to increase 1.5W rating to 3 watts (type 266F) 4p.

## CARBON TRACK POTENTIOMETERS, long spindles

Double wiper ensures minimum noise level.  
Single gang linear 220 Ω, to 2.2M Ω 12p  
Single gang log 4.7K Ω to 2.2M Ω 12p  
Dual gang linear 4.7K Ω to 2.2M Ω 42p  
Dual gang log 4.7K Ω to 2.2M Ω 42p  
Log/antilog 10K, 47K, 1M Ω only 42p  
Any type with A.D.P. mains switch, extra 12p

Please note: only decades of 10, 22 and 47 are available within ranges quoted.

## CARBON SKELETON PRE-SETS

Small high quality, type PR, linear only 100 Ω, 220 Ω, 470 Ω, 1K, 2K2, 4K7, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M2, 5M, 10M Ω Vertical or horizontal mounting 5p each.

ENAMELLED COPPER WIRE even No S.W.G. only.  
2oz recs 16-22 S.W.G. 25p; 24-30 S.W.G. 30p; 32-34 S.W.G. 33p; 36-40 S.W.G. 35p; 42-44 S.W.G. 38p; 46-48 S.W.G. 41p.

# ELECTROVALUE

(Dept. PW.1171) 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY

Hours: 9—5.30: Sat. 1 p.m. Tel.: Egham 5533 & 4757 (STD 0784-3) Telex 264475

# LOW PRICE, HIGH QUALITY SPEAKER SYSTEMS

All cabinets are new and carefully designed acoustically with speakers mounted on 3/4 in. chipboard baffles. All speakers are ex-TV high quality with hi-flux magnets carefully matched and tested.

We still do the well known Shelley and Coxton column speaker systems.




## STEREO HEADPHONE JUNCTION BOX

Simple unit connects direct to amplifier and speakers to give attenuated headphone output, has 2 position switch to give headphones only—speakers only.  
Only £1-37 each P & P 12½.
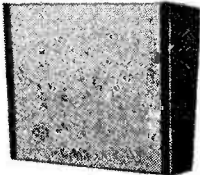
## CARTRIDGES-Stereo

Sonotone 9TA H/C Diamond £2.40. Ronette S105 Medium Output, £1.40. S106 High Output £1.40. Acos GP93/1 Sapphire, £1.90. GP94 1 Sapphire, £2. TA700 equivalent to B.S.R. SX1M, £1.75. Japanese equivalent to B.S.R. TC8s, £1.75. P. & P. 7np on each.



## DUDLEY

11" x 9½" x 5" deep, tapering to 3½" deep covered in Black resins and Mottled fawn Vynair £2-10 P & P 25p.

## SPEAKERS

E.M.I. 13½ x 8in, 3 ohm £2.50, 15 ohm. P. & P. 30np. E.M.I. 13½ x 8in, fitted two 2½in. tweeters, 15 ohm £4.50. P. & P. 30np. E.M.I. 13½ x 8in. (15 ohm) Hi-Fi quality £6.25. P. & P. 30np. Bakers 12in. 25 watt 8 and 15 ohms £7. P. & P. 30np. Eagle Crossover 86np. P. & P. 5np.

## VYNAIR

Widths from 50 to 54 in., 75np yd. off roll. P. & P. 10np, ½ yard 40np. P. & P. 10np. Send 5np stamps for samples.



## IMP

Wedge shaped extension speaker 7½ x 6½ x 4in. (max.). Covered in walnut wood grain cloth with mottled Vynair front. Keyhole slot at back. Fitted with 3 ohm speaker unit. Only £1.25. P. & P. 36np each

## CARTRIDGES-Mono


GP.91 Stereo Compatible £1.25. Acos GP67/2 will replace Collaro and Garrard Mono cartridges, 95np. T.T.C. Crystal High Gain, 75np. B.S.R. TC8H Jap. equivalent £1.25. P. & P. 7np.

## SPEAKER MATCHING


TRANSFORMERS 3, 7, 15 ohms, 8 watt, 70np. P. & P. 17np.
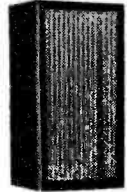
## FARRADAY

5½" x 11" x 4½" covered in White, Green or Black rexine or Teak cloth with Silver coloured metal front  
£2-90 P & P 25p.




## CLARENCE

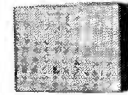

11" wide x 8½" x 4½" deep with volume control covered in Black rexine and Mottled Vynair.  
£2-25 P & P 25p.

## NOCTURNE 73 STEREO SYSTEM

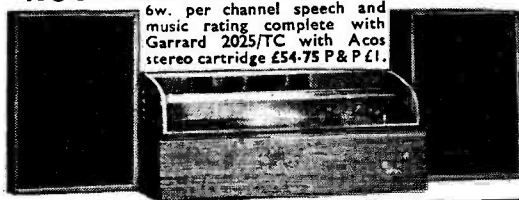

6w. per channel speech and music rating complete with Garrard 2025/TC with Acos stereo cartridge £54-75 P & P £1.

# BROADWAY ELECTRONICS

92 MITCHAM ROAD, TOOTING BROADWAY, LONDON S.W.17 01-672 3984  
(Nr. Tooting Broadway Underground Station)

(Closed all Wednesday)

# TV's


19" NOW £11.95

TWO YEARS GUARANTEE ALL MODELS

405/625: 19" £29.95; 23" £39.95

FREE CATALOGUE

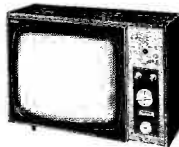DAILY DEMONSTRATIONS FOR PERSONAL SHOPPERS



## COMPONENTS MUST BE CLEARED

Transistor Radio Cases: 25p each. Size 9½" x 6½" x 3½". Post 15p.  
Speakers: 35p. 2½" 8Ω. Brand new. Post 15p.

VHF/FM Tuners: 95p. 88-108 mcs, takes EEC85 valve (extra). Post 15p.

BSR R/P Motors: 95p. Brand new. 200/250V. Post 20p.

Precision Tape Motors: £1-95. 200/250V. Famous German manufacturer. Post 20p.

Transistor Gang Condensers: 20p. Miniature AM. Post free.

Modern Gang Condensers: 30p. AM/FM or AM only 20p. Post 10p.


Transistors 15p each. Post free. AC126, AC128, AF114, AF117, OC45, OC71, OC81, OC81D.

Valve ELL80 50p. Only stock in the country.

Pots: 25p each. Post 5p. D/SW 500/500 KΩ. D/SW 500/100 KΩ. D/SW 1 meg/100 KΩ. S/SW 500/500 KΩ. S/SW 500/1 meg. 625 UHF/Aerial: £1-95. 10 Element fitting. Post 20p.

Knobs: 100,000 to clear. Brand New. 100 assorted radio and tv knobs. 50p. Post 25p.  
Radios £3-95 8 Transistor LW/MV. Free Case, Battery. Post 15p.  
Personal 6 Transistor MV. £2-95. Post 15p.

## TV TUBES REBUILT GUARANTEED 2 YEARS

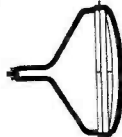

14" £3-95; 17" & 19" £5-95;

21" & 23" £6-45

Exchange Bowls carr. 55p.

## TEAK HI-FI STEREO CABINETS £14.95

Brand new 44" wide x 16" deep x 18" high with legs. A superb piece of furniture. Carriage £1. WHILE STOCKS LAST.

## DUKE & CO. (LONDON) LTD.

621/3 ROMFORD ROAD, MANOR PARK, E12  
Phone 01-478 6001-2-3 Stamp for Free List

# ELECTRONIC IGNITION june pw

Type P1/6 transformer, £1-50 including p&p. Complete kit including ready drilled case, screws, terminals, wire, etc. 12v only, state whether positive or negative earth system. £8-75 including p&p.

**MAGTOR LTD., 68, DALE STREET, MANCHESTER 1**

## P.W. COMMUNICATIONS RECEIVER

(P.W. DEC. '70—FEB. '71)

Was built entirely from parts supplied by us.

2nd Converter/I.F. kit..... £7-90  
Product Det. (with vol. control)..... £2-90  
Audio Amp ..... £1-80  
Pre-Sel./1st Con. .... £5-50  
Power Supply ..... £2-50

COMPLETE KIT all of above plus sub chassis material (formed tinplate) and F/T caps ..... £20-00

**P.W. F.M. TUNER** (Feb.-Mar. '69)

COMPLETE KIT inc. drilled chassis, scale etc. £8-20

**P.W. STEREO DECODER** (June '70)

COMPLETE KIT inc. chassis ..... £4-80

Post and Packing per order, 15p


**C & D ELECTRONICS**

1, Neville Road, St. Lukes Cross, Sunderland



$\frac{3}{8}$ in. back from the rear end of the key. Solder about  $\frac{1}{2}$ in. to  $\frac{3}{4}$ in. of 20 to 22 s.w.g. tinned copper wire to each screw head as in the inset in Fig. 8. These wires are wrapped loosely around the gold contact wires when the contact frame is finally placed in position.

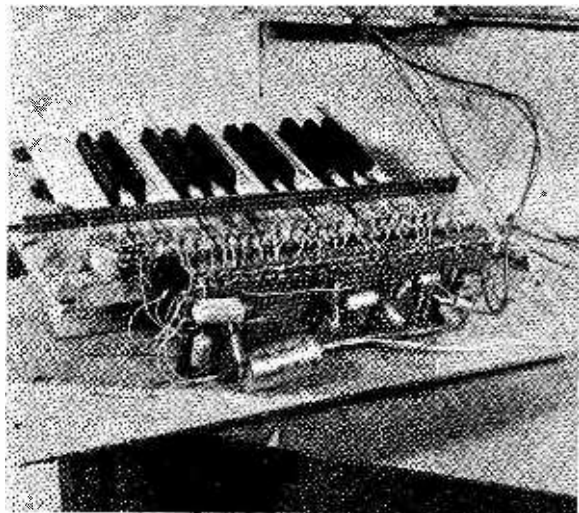The final stage of the keying assembly is to ensure that when the keys are at rest, the gold contact



A rear view of the keyboard showing the component board fixed in place.

wires are each about  $\frac{1}{8}$ in. clear of the main contact rail but do not touch the keys themselves. Check each contact with a continuity meter. The finished keyboard is shown in the photograph.

**TO BE CONTINUED**

## P.W. at the Fair

The **2-Octave Miniature Organ**, described above, will be just one of the constructional projects which can be seen at the **International Audio and Music Fair** which is to be held at Olympia, London, from October 26th to 30th.

This year Practical Wireless and Television will be showing more projects than ever before and there will often be someone from the technical staff to explain and answer questions.

Among the items that we are planning to show are the **Digital Frequency Counter/Timer**, **The Modular Audio Mixer**, **The P.W. Treasure Tracer**, **The P.W. Workshop Oscilloscope** as well as many other constructional projects.

P.W. is your magazine and we shall be at your service at Olympia on the dates mentioned. Be sure to visit us on Stand 3—right by the main entrance.

### **PRACTICAL WIRELESS AND TELEVISION STAND 3**

**INTERNATIONAL AUDIO  
AND MUSIC FAIR  
OLYMPIA, LONDON**

**OCTOBER 26th—30th**

10 a.m. to 9 p.m.

(Press preview and Trade day Oct. 25th)

**CHARLES MOLLOY**

# THE Medium Wave Column

**R**AMADAM starts on the 21st October this year and lasts until the 19th November. During this period Arabic speaking stations will be on extended schedule, many remaining on the air all night. From 2200hrs GMT onwards, listen for Algiers on 980kHz and 890kHz; Tunis on 962kHz and 629kHz; Libya with El Beida on 1123kHz and Tripoli on 1250kHz; Tangiers on 1232kHz; Batra Egypt on 620kHz. Among the less conspicuous are Riyadh, Saudi Arabia, 588kHz; Aleppo, Syria, 647; Bagdad, 760 (also on 908 after BBC4 closes down); Beirut, Lebanon, 876; Omdurman, Sudan, 960; Diyakir, Turkey, 1061; Tel Aviv, Israel, (in Arabic) 1286; Teheran, Iran, 1325; Kuwait, 1345; Ahwaz, Iran, 1390.

**M. Noctor** of South Norwood has had difficulty using his MW loop aerial with a transistor portable. A loop should not be connected to a receiver that has an interial aerial as the latter will mask the 'null' of the loop. **Dr. H. S. Brodribb** of St Leonards-on-Sea has solved this problem by mounting the receiver *inside* the loop so that the two rotate together. Coupling is between the turns of the loop and the windings on the ferrite rod inside the receiver and care should be taken that the nulls of both the loop and receiver are pointing in the same direction.

Medium Wave DXers will welcome the return of GMT this winter. Many European stations will close down at 2300hrs, clearing the band for North American DX before midnight. Paris 1070kHz signs off at 2300hrs GMT and, if the North American path is open, the 50kW Canadian at Moncton, New Brunswick, also on 1070kHz, should be audible after the Paris carrier is switched off. This station is a main outlet of the Canadian Broadcasting Corporation; it belongs to the "CBC Radio Network" and identifies on the hour and the half hour with the call letters CBA. Other Canadians that can be heard before midnight are CHER in Sydney, Nova Scotia, on 950kHz and CJON, St. John's, Newfoundland, on 930kHz. As midnight approaches look for WINS, 1010kHz, the all-news station in New York City; WNEW, 1130kHz, also in NYC; WBZ 1030kHz in Boston and WHN 1050kHz, NYC (After BBC4 signs off).

Newcomers to the medium waves are sometimes disappointed if North America is not heard at the first attempt. Propagation on this path is variable, with occasional fadeouts that last several days, so if you are unsuccessful the first time, try again a few days later. On a good night, many trans-atlantic stations peak-up by 0100hrs GMT. They can be logged on any communications receiver that covers the medium waves (the writer uses a CR100).

All reports and information concerning Medium Wave DXing should be sent to me at 132 Segars Lane, Southport PR8 3JG.

# TREASURE TRACED

At the end of the article describing the P.W. Treasure Tracer, we offered a small prize for the reader who sent in the most interesting letter mentioning items that had been found using the project.

Well, this article seems to have hit the jackpot. We know that several thousands have been built, so many in fact that for several weeks some components which were specified were in very short supply; we hope this did not put off some potential constructors.

The prize for the most interesting letter goes to 13-year-old Mark Read of Benfleet, Essex, who, on his first trip, found a .38 Smith and Wesson revolver in some nearby woods. Young Mark made the front page of his local evening newspaper with his find after he had done the sensible thing and handed it over to the police.

Mark admits to having had a little help with the building but he is a keen constructor and is tackling further P.W. projects by himself. His skill in using the Treasure Tracer must be very high as other finds include a .303 bullet and an iron axe head.

Competition for the most interesting finds was fierce. Mr. Peter Hope of West London found a total of £3 4s 3<sup>1</sup>/<sub>2</sub>d in his first week after building the project, enough he says to cover the cost of the Treasure Tracer—with a bit over.

Another reader found several transistors on the beach; how they got there we will probably never know but one has to admit that it is unusual.

Several letters mentioned sums of money that have been found and the total of all of them is nearly £20.

One point must be emphasised again and again. A lot of people complained that their results were poor compared to ours; when asked if they had spent much time trying, in nearly all cases they had done very little practice and were expecting good results immediately. **You will not become good with the Treasure Tracer without considerable practice.** One or two of those politely asked to put in more practice actually contacted us again saying that all was now fine and finds had been made.

Correspondence on the Treasure Tracer has been considerable but the points raised have all been very similar and answers are given below to the most common queries.

There are no mistakes in the article which will affect the operation, suspect your construction as a likely cause. Any type of 2N2926 transistor will do though the G (or green) may be better in the audio stages. Many readers felt that the volume was a little low and want to fit a louder amplifier. Any transistor amplifier capable of being run from a PP3



Mark Read with his Treasure Tracer and the revolver he found.

battery can be used instead of the amplifier of the prototype. Connections for this should be taken from the junction of D1 and C6, C5 may not be necessary. Experimenting with the value of R6 may help in some cases.

A lot of readers mentioned a Faraday shield, since these are fitted to most commercial types. The amount of information on metal locators is not very extensive. Experiments have shown that a Faraday shield is only useful or necessary if the frequency is a lot higher. The ground capacity effect on the Treasure Tracer is very small indeed and fitting a Faraday shield made no difference. However, another design was tried working on 700kHz; on this frequency the ground capacity effect was marked even with a Faraday shield.

There is room for experimenting with different coils. A larger diameter with fewer turns to obtain the same inductance will find large objects much deeper in the ground but it will not pick up small items, even on the surface; the size of the prototype seems to be the best operational size for general use.

Recent experiments have been carried out on encapsulating the coil in epoxy resin to hold the windings rigid. This works well and is an improvement but it does increase the weight of the head to an uncomfortable degree. Lacquering the search coil with a coil cement definitely helps.

And please, many letters were from readers who had not read the article through, they could have saved themselves a lot of trouble and time by reading the text as we had already anticipated their queries.

We hope that the above will help some readers and answer their queries. We regret that no back numbers are available at all. ■



**IN NEXT MONTH'S**

# 9-Band Short Wave Radio


"The world at your finger-tips" has become almost a cliché when advertising short wave receivers—but it's certainly true with this project. The nine bands means no dial cramping, enabling you to tune into stations with ease in the range 3.5 to 15 MHz. Worried by visions of lots of coils?—don't worry, there are only two, band selection is made by switching in pairs of fixed capacitors, greatly simplifying the construction.

# PRACTICAL WIRELESS

**EXTRA**
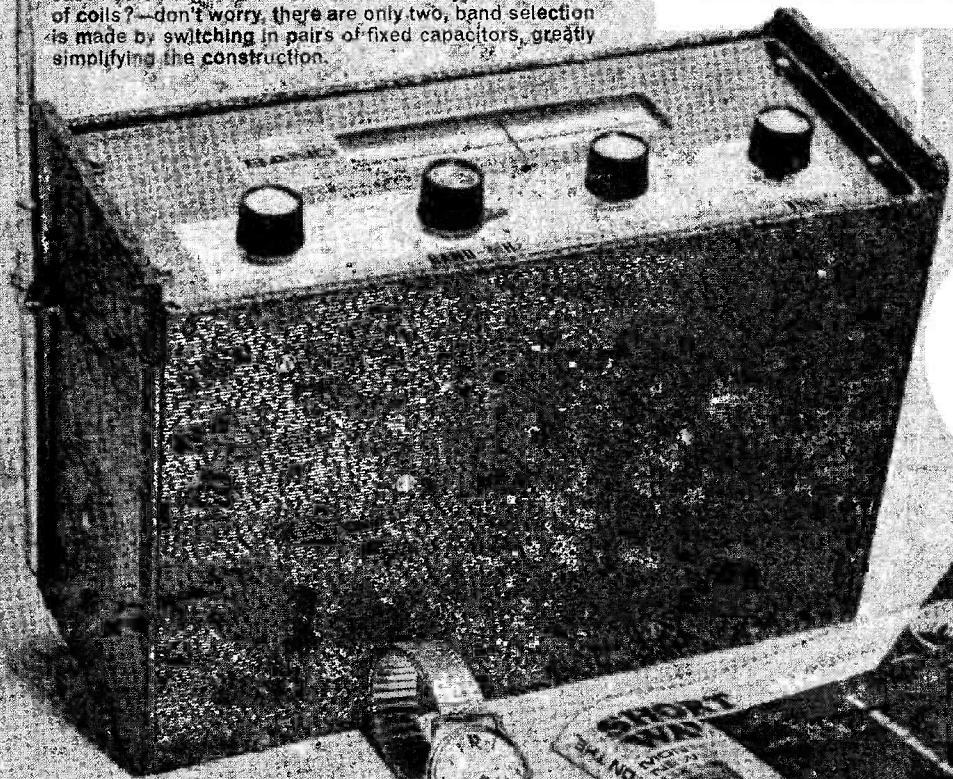
## COMPONENTS DICTIONARY SUPPLEMENT

Aerials to Zeners—that's the field covered in this extra supplement featured in the December issue. A detailed explanation is given of most of the important components used in today's electronics.



**ALL IN THE DECEMBER ISSUE ON SALE NOV. 5th**

**ALSO**

## 4-20V REGULATED POWER UNIT • TRANSISTOR TAPE RECORDER

Fed up with using a whole variety of batteries for your experiments? You'll be able to throw them away if you build our stabilised power supply covering 4V to 20V. The whole unit builds up into a smart, compact unit.

Earlier this year we promised you a mono tape recorder project. Well, it's in the December issue. Six transistors are used in this 4W circuit which combines both record and playback facilities. Constructional details and layout are given in full.



# COMPREHENSIVE MULTI-BAND RECEIVER

## PART 1

**T**HIS receiver, intended for use in the 550kHz to 30MHz range, has electrical bandwidth for all frequencies and is capable of very good general short wave reception. For the builder who is particularly interested in the amateur bands a crystal filter is incorporated and a product detector for the reception of single-sideband. For calibration purposes a harmonic crystal marker is included.

The circuit has the advantage that the receiver can be started in much simplified form, the crystal filter, carrier oscillator and other features being added later, as required. In any case, it will be found convenient to proceed in this way rather than to build the complete circuit before anything can be used or tested.

Miniature plug-in coils are used which enormously simplifies wiring and construction. These coils have to be changed by hand, but in practice this is often not so much of a disadvantage as may be supposed. For example, if most interest is in the h.f. amateur bands, 14, 21 and 28MHz, all these fall in the range of one set of coils. Again, both the l.f. amateur bands (1.8 and 3.5MHz) are tuned with another set of coils while for general s.w. listening, the range which falls between these will cover many of the useful broadcast frequencies.

Approximate coverage of the four ranges is as follows:

- Range 2. 550-1550kHz.
- Range 3. 1.5-4.8MHz.
- Range 4. 4.8-12.0MHz.
- Range 5. 12.0-30MHz.

These ranges are the maker's coil numbers. Range 1 is for long waves and may be employed if a high-performance receiver is wanted for these low frequencies.

### DESIGN

Fig. 1 shows the receiver stages in block diagram form. (1) is the r.f. amplifier, with r.f. gain control and panel aerial trimmer, allowing best results with any aerial. (2) is the frequency changer stage. (3) is the crystal filter and (4) the 1st i.f. amplifier. As selectivity with the filter adjusted for maximum

sharpness is much too narrow for a.m. reception a selectivity switch is incorporated, together with a phasing control which allows a rejection notch to be moved across the i.f. passband.

(5) is the 2nd i.f. amplifier and (6) a diode, for a.m. detection and a.g.c. (7) is the carrier oscillator, used for s.s.b. and as a beat frequency oscillator for c.w. reception, in conjunction with the double-triode product detector (8). (9) is a triode-pentode, for a.f. amplification and output, feeding the speaker. (10) is the crystal marker, a 1MHz crystal giving calibration points up to 30MHz.

For the beginner in particular, it is recommended that the receiver is built in the following order:

Stages (2), (5), (6) and (9). This is a straightforward superhet with three valves and one diode, capable of good results on any band.

The r.f. stage (1) is then added, improving sensitivity, and giving much more freedom from second channel interference on the h.f. ranges.

Stages (7) and (8) may then be added, allowing reception of s.s.b. and c.w. signals. The crystal filter (3) and its extra i.f. amplifier (4) can then be incorporated which are primarily intended to bring about the increased selectivity which proves so useful with crowded amateur and other bands.

The marker (10) plays no part in actual reception, but is a convenience for accurate calibration and accurate setting of the bandset ganged capacitor, when it is necessary to read frequencies from the bandwidth dial.

It is, of course, not necessary that the extra or optional stages are added in the order given, as this depends to some extent on the requirements of the user.

It is recommended that the "basic circuit" is built first, for the following reasons:



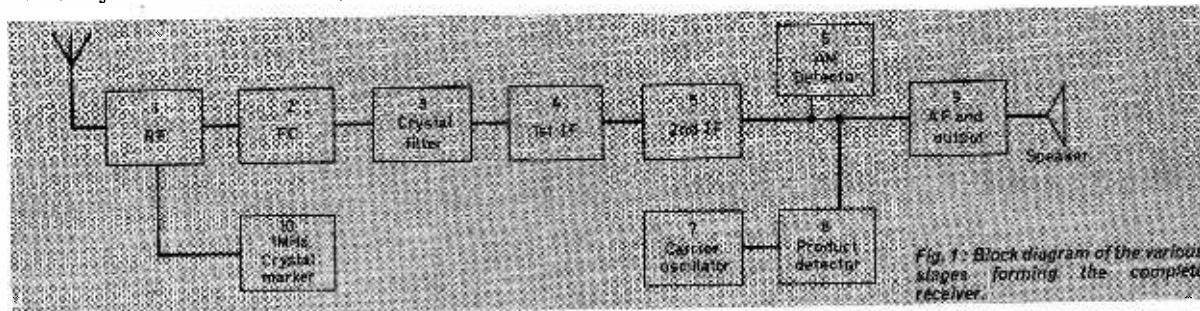


Fig. 1: Block diagram of the various stages forming the complete receiver.

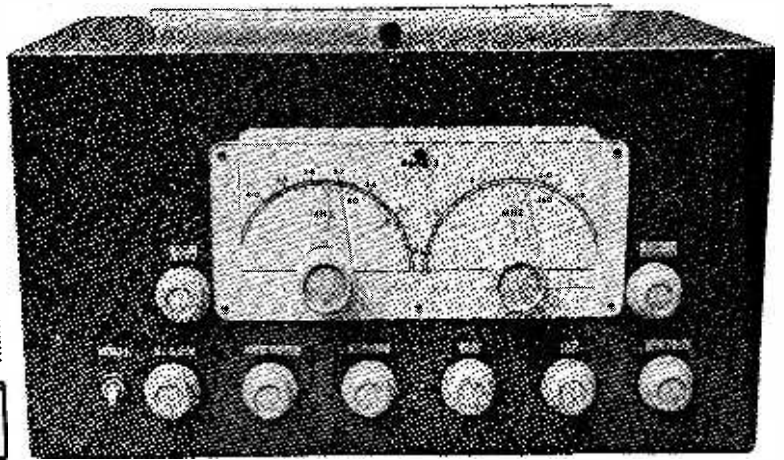

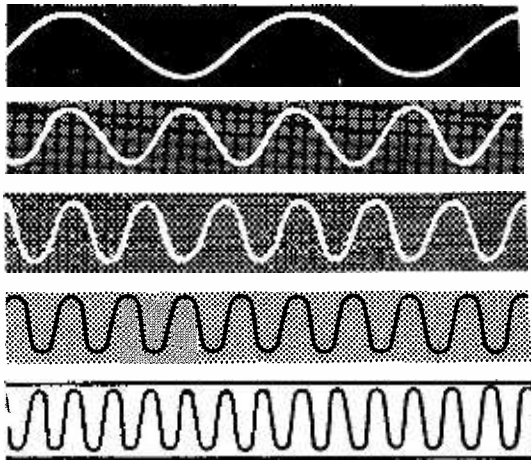

- (1) This consists only of stages 2, 5, 6 and 9, Fig. 1, so there is less chance of wiring or other errors.
- (2) The "building time" until a useful receiver is produced is much smaller.
- (3) If a fault should be present at this stage it will be much easier to locate.
- (4) The whole construction can be spread over a period, without the feeling that it will never be finished.
- (5) In some cases a simpler receiver will be adequate, so that some stages need not be built.

### METHOD OF CONSTRUCTION

The carrier oscillator, crystal frequency marker, and crystal filter (with i.f. stage and phasing capacitor) are built as three separate units on boxes readily made from "universal chassis" flanged members. When wired, they are bolted on to the main chassis, and connected to the receiver circuit.

The main chassis is 13×8in. To allow experimentation, and the easy changing of some parts of the circuit, the chassis was made from five "universal chassis" members, bolted together by the flanges to

form one assembly 13×8in. To the left, the power supply and a.f. amplifier occupy a 8×4in member, with space near the front for the carrier oscillator box, when required.

To the right, a 8×3in member takes the mixer section, with space for the crystal filter, when added. Between these, two 5×3in members accommodate the bandspread and bandset capacitors, and aerial coil.

At the back, a 6×3in member forms the i.f. and product detector strip. All make a chassis by bolting on a 13×2in member at the back and 8×2in sides.

If this method of construction is employed, place the five flanged members together with their flanges upwards, and mark and drill the flanges for two 6BA bolts between each member and those adjacent. Also drill and fit the back and sides. It is then possible to remove the bolts and take out any section, without much disturbance to other members.

If this method of construction is not favoured, it is in order to use a conventional chassis 13×8in. This would simplify preparation and metalwork to some extent.

The completed receiver is enclosed in a ready-made metal cabinet, the speaker being an external

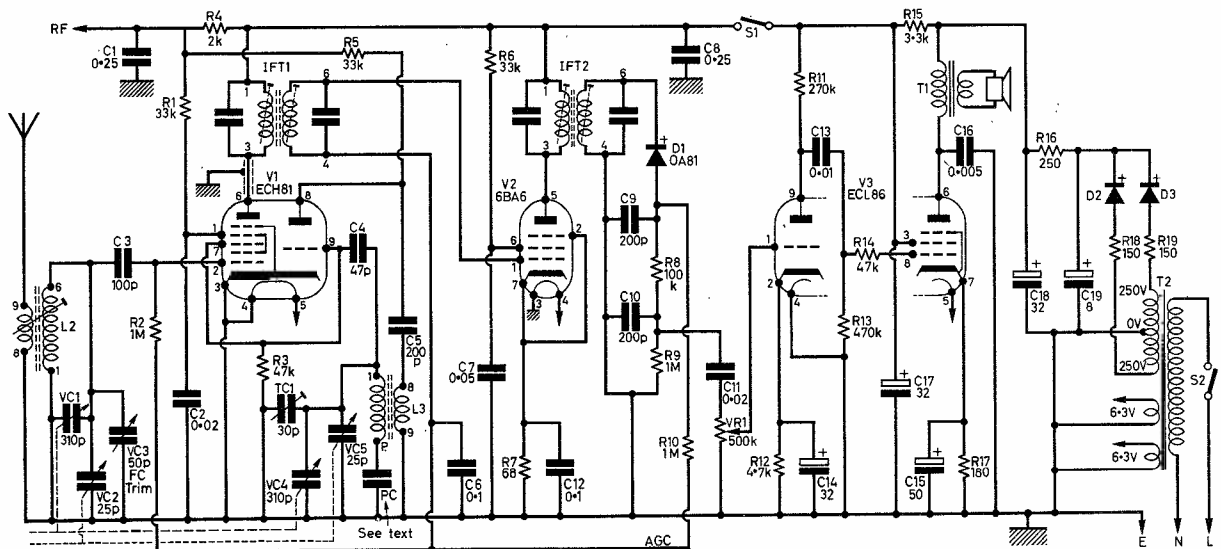


Fig. 2: Circuit diagram of the 3-valve basic receiver. The unused sections of the two 3-gang capacitors will be used for the r.f. stage added later.




unit. No reasonably-priced cabinet with a lifting lid could be obtained, so the top was sawn and hinged to allow access to the interior and changing of plug-in coils. If the receiver is later modified to include band-switching, this is still a useful feature.

## BASIC RECEIVER

Fig. 2 is the circuit of the basic receiver. The miniature plug-in coils are "Blue" for the aerial circuit, "Yellow" for the mixer grid (L2 in Fig. 2) and "Red" for the oscillator circuit (L3 in Fig. 2). With Fig. 2, it is necessary to have a pair of coils, one Blue and one Red, for each waveband. When the r.f. stage is included, a set of three coils is necessary for each waveband—Blue for aerial, Yellow for mixer, and Red for oscillator. Yellow coils will thus be placed in the L2 holder, Fig. 2, when this stage is reached.

Padder capacitors PC are of separate value for each Red coil, using a different pin for this purpose on each range. So all the padders are permanently wired to the holder and the correct value is automatically in circuit for any coil which is inserted. PC is 350pF to tag 2 for Range 2, 1000pF to tag 3 for Range 3, and 3000pF to tag 4 for Range 4. Range 5 has no padder and tag 6 must be connected to the chassis.

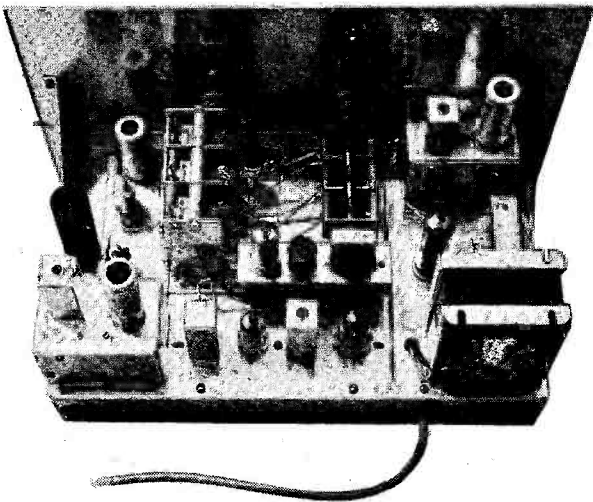

VC1/VC4 is the ganged tuning or bandsetting capacitor, and a 3-gang unit is fitted to allow tuning the r.f. stage when fitted. VC2/VC5 is of low value, so that its full movement covers only a narrow range of frequencies, for bandspreading (easy and more accurate short wave tuning). This unit is also 3-gang. Both variable ganged capacitors have ball drives.

The oscillator trimmer TC1 is left at the same setting for all coils, and VC3 is a panel aerial trimmer for peaking up signals.

V2 is the i.f. amplifier, and the two transformers IFT1 and IFT2 give a good degree of selectivity. When the crystal i.f. filter and extra i.f. stage are added, these come between V1 and IFT1. D1 is the a.m. detector which also gives automatic gain control voltage. When the product detector is provided, D1 is retained for a.g.c. and a function switch selects the appropriate mode of operation for a.m. or c.w./s.s.b. reception.

V3 is a 2-stage a.f. amplifier giving adequate output into a loudspeaker. Additional h.t. smoothing is

## ★ components list

BASIC RECEIVER		
<b>Resistors:</b>		
R1 33kΩ 1W	R8 10kΩ 1W	R13 3.3kΩ 3W
R2 1MΩ 1W	R9 1MΩ 1W	R15 250Ω 3W
R3 47kΩ 1W	R10 1MΩ 1W	R17 180Ω 1W
R4 2kΩ 1W	R11 270kΩ 1W	R18 750Ω 1W
R5 33kΩ 1W	R12 47kΩ 1W	R19 150Ω 1W
R6 33kΩ 1W	R13 470kΩ 1W	
R7 68Ω 1W	R14 47kΩ 1W	All 10% tolerance
VR1 500kΩ potentiometer 10g. with switch (50)		
<b>Capacitors:</b>		
C1 0.25μF 350V	C11 0.01μF 150V	
C2 0.02μF 350V	C12 0.1μF 150V	
C3 100pF 5M	C13 0.01μF 150V	
C4 47pF 5M	C14 22pF 5V	
C5 200pF 5M	C15 50pF 25V	
C6 0.1μF 150V	C16 6.005μF 500V	
C7 0.05μF 250V	C17 32μF 450V	
C8 0.25μF 350V	C18 32μF 450V	
C9 200pF	C19 8μF 450V	
C10 200pF		
VC1-VC4 VC6-3 × 310pF (Jackson Type E3-3 gang)		
VC2-VC5-VC7 3 × 25pF		
(VC6-VC7 are used in RF stage added later)		
TC1 50pF Variable (Jackson Type)		
TC2 50pF Trimmer (beehive style)		
PC Silver mica padding capacitors—		
Range 2: 350pF to pin 2		
Range 3: 1000pF to pin 4		
Range 4: 3000pF to pin 4		
On Range 5 pin 6 is connected to chassis		
<b>Valves and Slides:</b>		
V1 ECH81	D1 0A11	
V2 6BA6 (EFA)	D2 6Y110	
V3 ECL81	D3 6Y110	
<b>Inductors:</b>		
IFT1/IFT2 IFT1144 (Denco)		
L2 Miniature plug-in coils (Denco 'Blue' Ranges 2, 3, 4 and 5)		
L3 Miniature plug-in coils (Denco 'Red' Ranges 2, 3, 4 and 5)		
<b>Miscellaneous:</b>		
T1 Output transformer (Home Radio TO48)		
T2 Mains transformer (Home Radio TM1)		
Valveholders, 6Y6 with screen (1), 6Y6 (4) with one screen, S1 on/off blade switch, Ball drives (2) (Home Radio DL50A) and pointers (2) (Home Radio DL59), Brackets 4 × 4in (2), Knobs, feet (4), twin socket strips (Aerial/Earth, Speaker) tag strips		
Cabinet, 15 × 9 × 8in with panel (H.L. Smith Type W), Chassis, 13 × 8in aluminium plate with 13 × 1in (2) and 6 × 2in (2) flanged members (Home Radio)		

provided for early stages by R15 and C17. S1 is a "Standby" switch, leaving heaters on but h.t. on V3 only. This allows immediate on/off switching, as may be required when using the receiver with a transmitter.

## CONSTRUCTION

Fig. 3 shows the layout of the completed receiver, but the i.f. filter, carrier oscillator, marker, product detector and r.f. stage are added later in the way described. Punch chassis holes for the r.f. stage, aerial coil holder L1, and product detector holder, as this is awkward later if sections are not removable

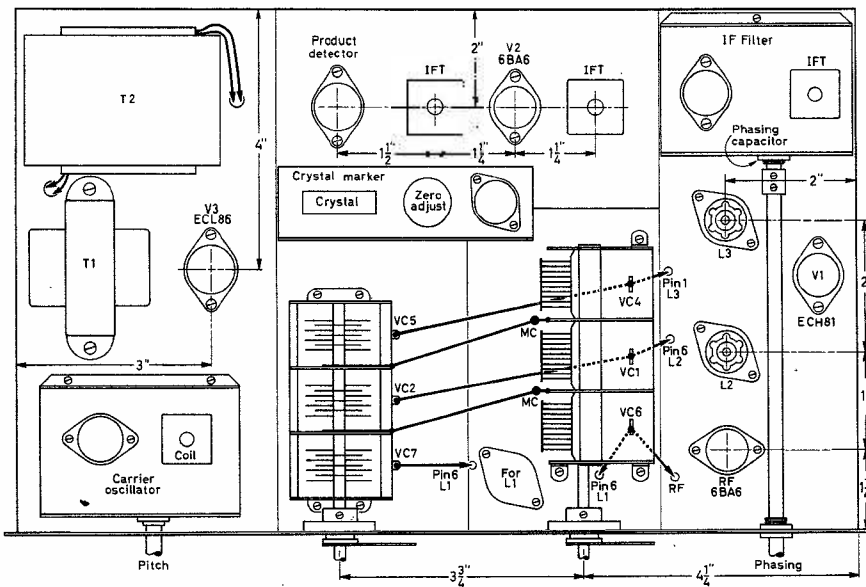


Fig. 3: (left) shows the disposition of the major components and units on top of the chassis while Fig. 4: (below) illustrates the wiring beneath.

the transformers T1 and T2 pass down through rubber grommets. Smoothing capacitors and other items are anchored by tagstrips. Later, h.t. for the r.f. stage is taken from the tag holding C1, while the "a.g.c." tag supporting R2 is the a.g.c. connection for the r.f. stage.

Leads carrying r.f. are stout and run clear of the chassis. AF circuits, such as to C11, are run against the chassis, as are heater and h.t. connections.

VC3 is mounted on a bracket near the holder for L2, as in Fig. 4, and its spindle is extended through the panel. This allows short leads and separation of r.f. and mixer circuits.


### ALIGNMENT

With the circuit of the basic receiver completed, insert a correct pair of coils, such as those for Range 2. Clip a test-meter, set for 10mA, across R7 with negative to chassis. Tune in any local BBC or other stable transmission.

The four cores of the two i.f.t.'s are then adjusted, with the correct type of core tool, for minimum meter reading. Each core should have quite a definite peak.

TC1 is set at about half capacitance and rotating VC3 with any pair of coils in use, and the bandset capacitor nearly fully open, should peak up signals. The receiver is then tuned towards the low-frequency end of the band, and if coverage is unsuitable, the core of L3 is adjusted to correct this. The core of L2 is then adjusted for best results (minimum meter reading). Set the core of L2 so that when tuning from the h.f. end of the band, to the l.f. end, the minimum re-adjustment of VC3 is required. Deal with each pair of coils separately, and lock the cores with 6BA nuts.

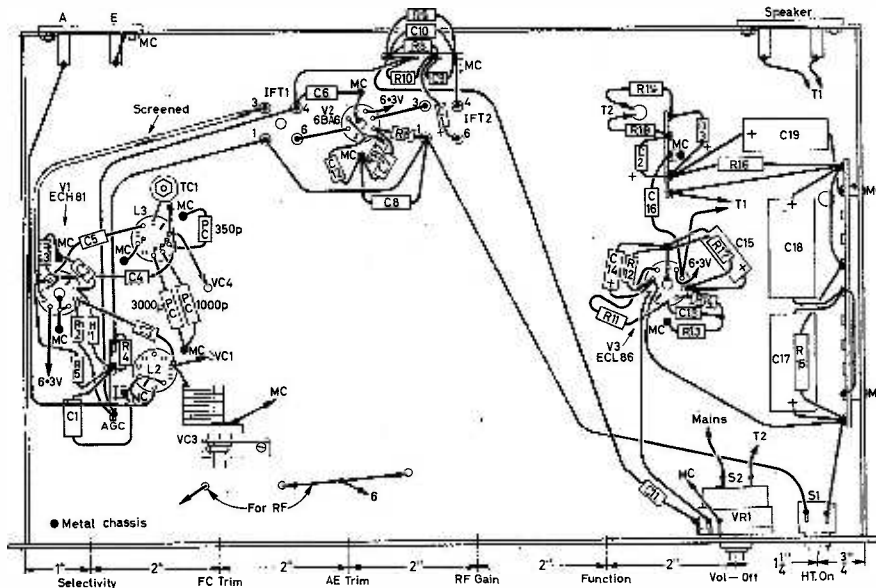**PART 2 NEXT MONTH WILL  
CONTAIN FULL DETAILS OF THE  
ADD-ON UNITS TO COMPLETE  
THE RECEIVER**




in the way explained.

Punch holes in the front 13x2in runner as in Fig. 4. Place this on the panel with 1/2in of the panel projecting below, and punch matching holes in the panel. The panel is held to the chassis by component bushes and a vertical bracket each side.

Mount the variable capacitors with their spindles at the same height, so that the ball drives fit in clearance holes, with the drive lugs bolted to the panel. Take insulated leads from the lower tags of the bandsetting capacitor, down through holes as in Fig. 3. Connect the bandspread capacitor with stout leads clear of the chassis. The rotor tags are wired to tags bolted to the chassis.

Fig. 4 shows connections and components under the chassis to assemble the circuit in Fig. 2. The absence of bandswitching simplifies this part of the work.

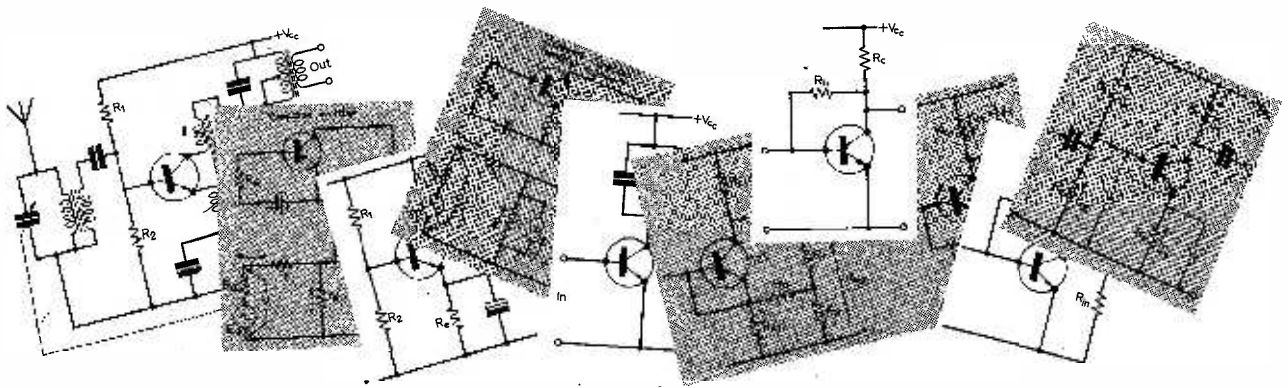Anchor the mains cord at a tag strip. Leads from



# TRANSISTOR CIRCUITRY for beginners

## PART 2

H.W. HELLYER

### Properties of Germanium and Silicon

The silicon diode has a more sharply defined 'knee' in the reverse characteristic than the germanium type. At a certain point, as the reverse voltage is increased, the current suddenly increases very rapidly. At the breakdown point the current can suddenly increase from a few microamps to many milliamps, and even amperes in some specially constructed devices. Advantage is taken of this characteristic which all semiconductors exhibit to some extent, in the development and application of a Zener diode.

### History of the Transistor

Although it was as recently as 1947 that Bardeen and Brattain of the Bell Telephone Laboratories earned themselves a Nobel prize with the development of the transistor from the types of semiconductor devices we have been discussing, it should not be imagined that the whole family of semiconductors has so short a history. The main research impetus, it is true, came during World War II, but as long ago as 1835 the rectifying properties of certain substances had been noted by Rosenshold. F. Braun revived interest in 1874 and Willoughby Smith Co. testing underwater telegraph lines, had already noted a variation of resistance according to the amount of light shining on the material some un-named technical assistant was using—which happened to be selenium. In Victorian times, the selenium cell, in rather primitive form, was a scientific curiosity, and its rectifying property was observed in 1876.

Even as Fleming was experimenting with his thermionic diode in 1904, J. C. Bose patented a semiconductor crystal diode, and in the early years of broadcasting, the crystal detector was much used. A silicon detector was invented in 1906 by Pickard—familiar to early experimenters under the name of the 'Perikon detector'. A patent for the improved version of this device was taken out in 1909.

Earlier devices—until 1941, anyway—were point-contact. Then a junction diode was brought out. Six years later came the first transistor. Bardeen

and Brattain developed a 'crystal diode' and the name 'Transistor' came from 'Transfer-resistor'.

There is nothing new under the sun. Many years before, the diode had been used as an oscillator, and in 1924, *Wireless World* carried an article by Victor Gabel, which dealt with the Russian Lossev's experiments with crystals as generators and amplifiers. To undermine our easy belief in progress yet further, we note that Eccles used a crystal diode as an oscillator way back in 1909!

The original work on point contact devices at Bell Telephone Laboratories brought the first transistors. Shockley was a leader among those, who, realising the limitations—high noise factor, relatively high production costs, lack of durability and the difficulty of manufacture—researched the junction device and eventually came up with a 'junction transistor'. This is the basis of most modern semiconductor devices.

A variety of techniques has developed: grown junction, alloying, surface barrier, alloy-diffused, diffused mesa, epitaxial diffused mesa, planar, epitaxial planer, diffused field effect, etc. Let's take a look at the more important among them.

### Development

It was during an investigation into the rectifying properties of surface potentials around a point contact that the scientists at Bell Telephone Laboratories used a second contact to prove the field. At spacings between the two probes of less than a couple of thousandths of an inch they noted a change in current in the main contact influenced the current flow in the other. From this, the germanium point contact transistor was developed.

Two springy wires with pointed ends about a thousandth of an inch apart, pressed on a flat piece of germanium, each having rectifying characteristics. The emitter has a forward bias and thus a low resistance while the collector is reverse biased, giving it a high resistance. A change in forward current through the emitter contact produces a change in the collector contact, and because of the difference in the resistances, power amplification takes place.

This is the important, noteworthy, fact about


### Flex Connector

A quick way to connect equipment to the mains safely and firmly—L, N, and E, coded to new colour scheme; disconnection by plugs prevents accidental switching on; has sockets which allow insertion of meter without disconnection cable inlet firmly held on hair wire on up to four 7.029 cables. 85p each.


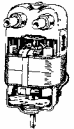
### MULTI-SPEED MOTOR

Six speeds are available 500, 550 and 1,100 r.p.m. and 8,000, 12,000 & 15,500 r.p.m. Shaft is 1 in. diameter and approximately 1 in. long. 230/240v. Its speed may be further controlled with the use of our Thyristor controller. Very powerful and useful motor size approx. 2 in. dia. x 5 in. long. Price 85p plus 23p postage and insurance.




### 2 OCTAVE MINI ORGAN

As described in this issue. Send today for list of parts
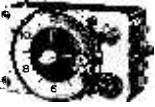
### 20 AMP ELECTRICAL PROGRAMMER

Learn in your sleep: Have Radio playing and kettle boiling as you awake—switch-on lights to ward off intruders—have warm house to come home to. All these and many other things you can do if you invest in an Electrical Programmer. Made by the famous Smiths Instrument Company. This is essentially a 230/240 volt mains operated Clock and a 20 amp Switch, the switch-off time of which can be delayed up to 12 hours (continuously variable not stepped). Similarly the switch-on time can be delayed. This is a beautiful unit, size 5 1/2 x 3 1/2 x 2 1/2 in. deep. Metal encased, glass fronted with chrome surround. Offered at £2.40 plus 23p postage and insurance.



### RESETTABLE FUSE

How long does it take you to renew a fuse? Time yourself when next one blows. Then reckoning your time at £1 per hour see how quickly our resettable fuse (auto circuit breaker) will pay for itself. Price only £1 each or £11 per dozen, specify 5, 10 or 15 amp—simply fit in place of switch.



### BLANKET SWITCH

Double pole with neon light, ideal for dark room light or for use with waterproof element, new plastic case 30p each. 3 heat model 40p.



### 2 1/2 kW FAN HEATER

Three position switching to suit conditions in the weather. Switch up for full heater (2 1/2 kW), switch down for half heat (1 1/2 kW), switch central blows cold for summer cooling effect—adjustable thermostat acts as auto control and safety cut-out. Complete kit £3.75. Post and ins. 38p.



### COMPUTER TAPES

2400' of the Best Magnetic Tape money can buy—users claim good result with Video and sound. 1" wide £1.45 plus 38p post and insurance, with cassette. 1/2" wide £1.25 plus 30p post and insurance with cassette. 3/4" wide £1 plus 25p post and insurance with cassette. Spare spools and cassettes—1" £1, 1/2" 85p, 3/4" 75p each plus 20p post and insurance.



### SPARTAN Portable RADIO

Long and medium wave, 7 transistor, size 6in. x 4in. x 1 1/2in. with larger than usual speaker giving very good tone. Built-in ferrite aerial and telescopic aerial for distant stations. A real bargain complete with leather case, carry sling, earplug and case £3.75 plus 23p post and ins.



### PROTECT VALUABLE DEVICES FROM THERMAL RUNAWAY OR OVER-HEATING

Thyristors, rectifiers, transistors, etc., which use heat-sinks can easily be protected. Simply make the contact thermostat part of the heat sink. Motors and equipment generally, can also be adequately protected by having thermostats in strategic spots on the casing. Our contact thermostat has a calibrated dial for setting between 50deg. to 190 deg. F. or with the dial removed range setting is between 80 to 800deg. F. Price 50p.




### CAPACITOR DISCHARGE CAR IGNITION

This system which has proved to be amazingly efficient and reliable was first described in the Wireless World about a year ago. We can supply kit of parts for improved and even more efficient version, (P.W. June), price £4.95. When ordering please state whether for positive or negative systems. Plus 30p post.

### ELECTRONIC IGNITION

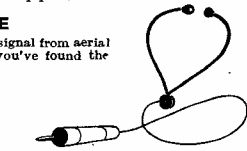
### RADIO STETHOSCOPE

Easiest way to fault find—traces signal from aerial to speaker—when signal stops you've found the fault. Use it on Radio, TV amplifier, anything—complete kit comprises two special transistors and all parts including probe tube and crystal earpiece. £2—twin stethoscope instead of earpiece 75p extra—post and ins. 20p.


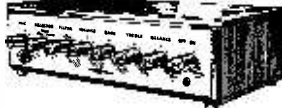
### P. E. GEMINI

Dual purpose twin 30 watt stereo amplifier for exceptional performance. Complete kit of parts less case £45 or reprint of data & parts list 55p.



### STANDARD WAFER SWITCHES

Standard size 1 1/2 wafer—silver-plated 5-amp contact, standard 2" spindle 2" long—with locking washer and nut.

No. of Poles	2 way	3 way	4 way	5 way	6 way	8 way	9 way	10 way	12 way
1 pole	40p	40p	40p	40p	40p	40p	40p	40p	40p
2 poles	40p	40p	40p	40p	40p	40p	40p	40p	40p
3 poles	40p	40p	40p	40p	40p	40p	40p	40p	40p
4 poles	40p	40p	40p	40p	40p	40p	40p	40p	40p
5 poles	40p	40p	40p	40p	40p	40p	40p	40p	40p
6 poles	40p	40p	40p	40p	40p	40p	40p	40p	40p
7 poles	70p	70p	70p	70p	70p	70p	70p	70p	70p
8 poles	70p	70p	70p	70p	70p	70p	70p	70p	70p
9 poles	70p	70p	70p	70p	70p	70p	70p	70p	70p
10 poles	70p	70p	70p	70p	70p	70p	70p	70p	70p
11 poles	70p	70p	70p	70p	70p	70p	70p	70p	70p
12 poles	70p	70p	70p	70p	70p	70p	70p	70p	70p


### THIS MONTH'S SNIP

**15 WATT 12in HI-FI SPEAKER.** Is undoubtedly one of the finest loudspeakers that we have ever offered, produced by one of the country's most famous makers. It has a die-cast metal frame and is strongly recommended for Hi-Fi and public address. Handling 15W R.M.S.—Cone moulded fibre—Freq. response 30 10,000 c.p.s.—specify 3 or 15 ohms. Chassis diam. 12in—12 1/2in over mounting flugs. Overall height 5 1/2in. A 10 speaker offered this month for £3.75 plus 30p. post and ins.


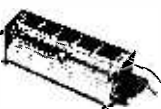
### TANGENTIAL HEATER UNITS

This heater unit is the very latest type, most efficient, and quiet running. Is as fitted in Hoover and blower heaters costing £15 and more. We have a few only. Comprises motor, impeller, 2kW. element and 1kW. element allowing switching 1, 2 and 3kW. and with thermal safety cut-out. Can be fitted into any metal line case or cabinet. Only need control switch. £3.50. 2kW. Model as above except 2 kilowatts £2.50. Don't miss this. Control Switch 35p. P. & P. 40p.



### HONEYWELL PROGRAMMER

This is a drum type timing device, the drum being calibrated in equal divisions for switch setting purposes with trips which are infinitely adjustable for position. They are also arranged to allow 2 operations per switch per rotation. There are 15 changeover micro switches each of 10 amp type operated by the trips thus 15 circuits may be changed per revolution. Drive motor is mains operated 5 revs per min. Some of the many uses of this timer are Machinery control, Boiler firing, Dispensing and Vending machines, Display lighting animated and signs, Signalling, etc. Price from makers probably over £10 each. Special snip price £3.75 plus 25p post and insurance. Don't miss this terrific bargain.



### INTEGRATED CIRCUIT BARGAIN

A parcel of integrated circuits made by the famous Plessey Company. A once-in-a-lifetime offer of Micro-electronic devices well below cost of manufacture. The parcel contains 5 ICs all new and perfect, first-grade device, featuring not sub-standard or seconds. 4 of the ICs are single silicon chip GP amplifiers. The 5th is a monolithic NPN matched pair. Regular price of parcel well over £5. Full circuit details of the ICs are included and in addition you will receive a list of many different ICs available at bargain prices 5/- upwards with circuits and technical data of each. Complete parcel only £1 post paid. **DON'T MISS THIS TERRIFIC BARGAIN.**



### DIGITAL COUNTER TIMER

Very stable & reliable crystal controlled circuit. Capable of work in excess of 15 MHz. Construction simplified by use of 15 integrated circuits. Complete kit with case £37.50 or construction data & price list 50p.



### TREASURE TRACER

Complete Kit (except wooden batens) to make the metal detector as the circuit in Practical Wireless August issue. £2.50 plus 20p post and insurance.

### DRILL CONTROLLER NEW I KW MODEL

Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. £1.50 plus 13p post and insurance. Made up model also available. £2.25 plus 13p post & p.



### CONSTRUCTOR PROJECTS

as described in this issue and in past issues. We can probably supply components. Send S.A.E. for list naming the project.

### HIGH ACCURACY THERMOSTAT

Uses differential comparator I.C. with thermostat as probe. Designer claims temperature control to within 1/10th of a degree. Complete kit with power pack 55.50.

### AUTO-ELECTRIC CAR AERIAL

with dashboard control switch—fully extendable to 40in or fully retractable. Suitable for 12v positive or negative earth. Supplied complete with fitting instructions and ready wired dashboard switch. £8 plus 25p post and ins.



### AUTO-LITE

as circuit in this month's issue. Kit of parts £1.20 post paid.

### TOGGLE SWITCH

3 amp. 250v. with fixing ring 7 1/2 inch, 75p doz.



### CAR ELECTRIC PLUG

Fits in place of cigarette lighter. Useful method for making a quick connection into the car electrical system. 88p each or 10 for £3.42.

### ROCKER SWITCH

15 amp self-fixing into an oblong hole, size approximately 1" x 1/2" 6p each, 10 for 54p.



### MAINS RELAY BARGAIN

Special this month are some single, double and treble pole changeover relays. Contacts rated at 15 amps. Operating coil wound for 240V A.C. Good British Make. Unused. Size approx. 1 1/2" x 1". Open construction. Single pole 25p each 10 for £2.25. Treble pole 40p each 10 for £3.50.



### BALANCED ARMATURE UNIT

500 ohm, operates speaker or microphone, so useful in intercom or similar circuits. 88p ea., £3.50 doz.



### THERMOSTAT

Continuously variable 30°-80°C. Has sensor bulb connected by 33in. of flexible tubing. On operation a 15 amp 250 volt switch is opened and in addition a plunger moves through approx. 1/2 in. This could be used to open valve on ventilator etc. £1.50 plus 23p. p. & ins.



### 5A 3-PIN SWITCHED SOCKETS

An excellent opportunity to make that bench dis board you have needed or to stock up for future jobs. This month we offer 6 British made (Hicraft) bakelite flush mounting shuttered switch sockets for only 50p plus 16p post and insurance. (20 boxes post free.)



### MAINS MOTOR

Precision made — as used in record decks and tape recorders—ideal also for extractor fan, blower, heaters, etc. New and perfect. Snip at 50p. Postage 15p for first one then 5p for each one ordered.



Where postage is not stated then orders over £5 are post free. Below £5 add 20p. Semi-conductors add 5p post. Over £1 post free. S.A.E. with enquiries please.

**J. BULL (ELECTRICAL) LTD.**  
Dept. P.W. 7, Park Street, Croydon CRO 1YD

# THE WORLD'S GREATEST NEWS STORIES OF OUR TIME!

THE HEADLINES THAT WERE  
FRONT PAGE SENSATIONS!

*Headlines* is the new and exciting publication for every man and woman who wants to read again the thrilling and true front-page stories of just how and when it happened.

**NO 2**  
**HEADLINES**  
12 STORIES THAT WERE FRONT PAGE NEWS

**NO 2 OUT  
OCTOBER 1  
ONLY 15p**

**EXTRA  
HESS  
FLIES TO  
SCOTLAND**

**SUB SUNK - 99 LIVES**  
HM & There is  
not dying

**Frenchman flies in  
English Channel**  
LOUIS BLERIOT  
FIRST FLIGHT

**SCOTT'S PARTY  
FEARED DEAD!**

**ROCKY'S  
CHAMP!**

**JESSE MAKES IT  
FOUR GOLD!**

**Acid Bath  
Murders**

New . . . thrilling . . . exciting . . .  
**HEADLINES** features more than 40,000  
words of absorbing reading with vivid  
and dramatic pictures.

**ALL THESE AMAZING STORIES INSIDE**

**THE FANTASTIC FLIGHT OF RUDOLPH HESS**—he dramatically parachuted into Scotland 'on a mission of humanity' to make peace between Britain and Germany . . . and wage a united war on Russia!

**LOUIS BLERIOT**—the unassuming Frenchman who accomplished the amazing first flight of the English Channel.

**GREAT GOD THIS IS AN AWFUL PLACE**—the harrowing account of Scott's nightmare return from the Antarctic which ended in he and his comrades dying in a grave of snow.

**THE KILLER DOCTOR**—hung for the gruesome and depraved crime of slaughtering and dismembering his wife and maid.

**EDWARD VIII**—torn between his duty to the nation and personal happiness—he relinquished his Crown for the woman he loved.

**THE BOLSHEVIK BUTCHER**—that was Beria—Head of Russia's Secret Police and responsible for the callous murder of thousands of 'anti-communists'.

**ROCKY MARCIANO**—the heavyweight champion with the iron punch that no man on earth could withstand.

**THE MURDER FACTORY**—that was the name given to the factory in Crawley where John Haigh destroyed the 6 bodies of his victims in a tank of acid!

**THESE AND OTHER GREAT FRONT-PAGE STORIES OF THE TWENTIETH CENTURY ARE ALL IN NO. 2 ISSUE**



the transistor, that it is essentially a current-operated device. However, it is the difference in input and output resistance that is the vital means of securing amplification. Hence the name—the process being basically one of transferring a current from a low to a high resistance, using a solid-state device. The advantage is reduced size and weight and no need for a heater supply as with a thermionic valve.

As development goes on, some of the disadvantages, power handling limitation, frequency characteristics, etc., will be overcome. Solid-state devices have almost completely ousted valves from portable equipment, have invaded the domestic entertainment field for table radios and record players, and most tape recorders, are already into high fidelity amplifiers and are now used for nearly all stereo radiograms, while television circuitry has been the subject of much experiment with transistors taking the place of valves in almost every stage. Transistor television receivers have been marketed and are gaining in popularity as prices level off.

In the commercial and industrial field, solid-state devices are imperative for many applications, where the number of switch-gates and amplifiers in a unit would militate against valves on the grounds of space alone, even if power consumption and heat dissipation were not important considerations. Transistors, allied to micro-electronics, modules, integrated circuits and other developments, have led to the production of computers with a wide range of facilities, yet no larger than an old-style adding machine.

## Operation

In considering the operation of the junction transistor, we must revert to the properties of the p-n junction. If two of these junctions are formed, back to back, in a single piece of semiconductor, and lead wires taken from the p and n sections, a transistor is formed. This formation can be either p.n.p. or n.p.n., with roughly opposite characteristics, as we shall observe. The first p region, called the emitter, emits holes into the base, the centre n region. The second p region, the collector, collects holes from the base and is negatively biased. This is the p.n.p. transistor, which we shall now consider.

Fig. 7 shows the p.n.p. transistor connected as an

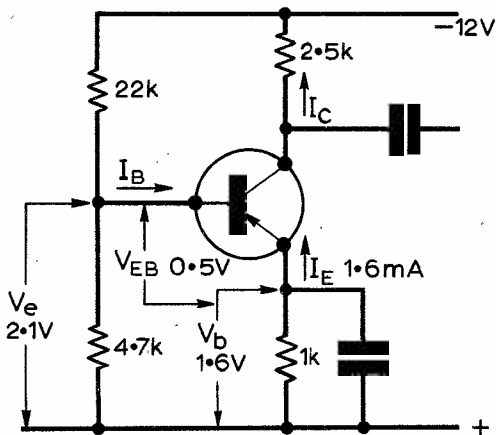


Fig. 7: A silicon p.n.p. transistor connected as a common-emitter amplifier.

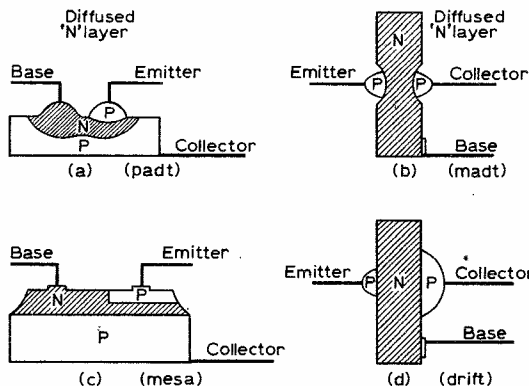


Fig. 8: Typical construction of some transistors.

amplifier, with appropriate supply voltages. In passing through the base region, the emitter current  $I_E$  decreases slightly by some holes recombining with electrons. To take the place of these 'lost' electrons, more flow in from the base contact, the current thus produced being equal to the difference between the emitter current and the collector current, or  $I_B = I_E - I_C$ .

Some actual constructions of p.n.p. transistors are shown in diagrammatic form in Fig. 8. These are (a) post alloy diffused, (b) microalloy diffused, (c) mesa type, and (d) 'drift' type. In the construction of transistors, a number of very delicate refining processes take place, and the following notes are only a brief look at production techniques.

## Production Techniques

Germanium occurs in certain coal formations and as an impurity in zinc and copper ores. It can be extracted from the flue dust of coal-burning power stations. It is chemically extracted from its source, converted to germanium dioxide and heated in hydrogen to reduce to the metal. Impurities at this stage are as low as one part in a million. To purify further, zone refining is carried out by concentrating power in one part of the ingot, producing a narrow molten zone and moving this to the end of the ingot, which tends to move the impurities toward the end, which may be cut off and rejected. Refinement to reduce impurities to as little as one part in  $10^{10}$  can be carried out in this way.

The selected donor or acceptor impurity is added in similarly small controlled amounts. This is done during the same process as seeding, when a small 'seed' of the metal is lowered into contact with molten germanium in a crucible heated a little above the melting point and raised very slowly so that a crystal solidifies on the seed.

This process of 'pulling from the melt' is also used in manufacture of silicon transistors. Silicon is a common substance (sand is mainly silicon dioxide) and chemical extraction is employed to refine it. A floating zone process is often used both to complete refining and to produce the correct crystal, whereby a rod of polycrystalline silicon is held vertically and a molten zone, narrow enough to be held in position by surface tension is passed up, from a single crystal seed at the bottom, to the top. As the zone passes up, silicon melts into it at

the top and boron and other impurities are taken to the top while the silicon solidifies out into single crystal form at the bottom.

After refinement and preparation, the single crystal material is sawn into slices about fifteen-thousandths of an inch thick, using diamond impregnated wheels. The slices are lapped to a thickness of about eight to ten thou' by carborundum and finally surface irregularity is removed by etching in an acid mixture. For some diffused types the whole subsequent process is carried out on the whole slice, which is then scribed and cut to size, but for many other applications the processing is done separately.

The junctions between the p and n type materials may be 'grown' during the process of pulling from the melt, or formed by other methods. These include alloying, diffusion and epitaxy. Epitaxial junctions are formed on a substrate wafer by growing a thin film of the same semiconductor on to it, hence the term 'epitaxial', meaning, on the same axis. Again, heating is the key to the process, and very precise methods of temperature control have been developed by transistor manufacturers.

Alloy diffused transistors are made by a combination of diffusion and alloying techniques. This gives a narrower base width and a better high frequency performance. They have a high current gain and an upper cut-off around 100 MHz.

Diffusion transistors of both germanium and silicon types have much better characteristics because of the more rigid control of dimensions of the elements during construction. In general, germanium offers higher frequency possibilities than silicon and germanium diffused transistors operating up to several thousand MHz are available. The method of construction gives rise to the term 'mesa', whereby an area of the diffused collector junction is defined by masking over the emitter and base stripes (evaporated gold contacts being used) and the wafer etched to leave a raised 'mesa' containing the active part of the transistor—a process that greatly aids mass production.

Silicon diffused transistors can be sub-divided into several types but most variations are the result of research into closer production control. Some forms similar to mesa etching are employed, and diffused mesa transistors are generally of the silicon type.

## Planar Transistors

A development of manufacturing processes to overcome instability caused by contamination at the surface of the mesa led to the planar type of silicon transistor. The process is quite involved, including the use of photo-etching techniques, deposition and diffusion, but the great advantage is the protection of the collector-base junction, resulting in very low collector leakage current. Very thin base layers are possible giving good high frequency performance, up to several thousands of MHz. Manufacturing techniques can be modified to easily make different size transistors and a whole range of types, from small signal high frequency, to high power medium frequency (typically 50 watts at 10 MHz) can be produced.

One disadvantage of the diffused transistor is the series resistance between the collector junction and the contact at the bottom of the wafer. This sets up an internal voltage drop when collector current

flows. To improve upon this, the epitaxial planar transistor has been developed. This is perhaps the most versatile transistor to date, with good, all-round characteristics. Manufacture includes the previous processes, but a composite slice of very low resistance substrate on which a thin epitaxial layer has been formed is now employed and the epitaxial structure can be developed by depositing alternate p and n layers on a suitable substrate.

## Field-effect Transistors


One very important development of this process is the construction of the field-effect transistor. Its special properties are likely to lead to a rapid increase in applications. In particular, its high input impedance makes it suitable for a number of circuit configurations where other types of transistor are not appropriate. Another important feature is that only one type of carrier is involved—the majority carrier in the basic bar of semiconductor. This is in contrast to the normal type of junction transistor, which depends for its action on the flow of minority carriers through the base region and majority carriers in the emitter and collector regions. A high impedance linked with a low noise factor makes this device eminently suitable for small-signal input stages. The most significant difference for the designer, is that the f.e.t. is a voltage-controlled device but more about f.e.t.'s later.

The zener diode is essentially a specially constructed diode designed to work in reverse, employing what would be regarded as the 'failure' part of the characteristic of an ordinary silicon diode. The silicon controlled diode or thyristor is a further device which finds special uses. Normally, this rectifier blocks current both ways, but when triggered by a pulse fed to a gate electrode, current is allowed to flow in the forward direction only. As this is basically a three-junction device, more detailed explanation will be left until later.



TO BE CONTINUED

# MAXWELL

by G8DSH

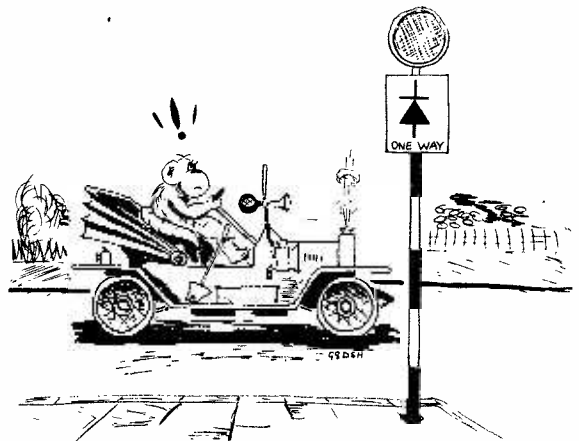

# DIGITAL FREQUENCY COUNTER/TIMER

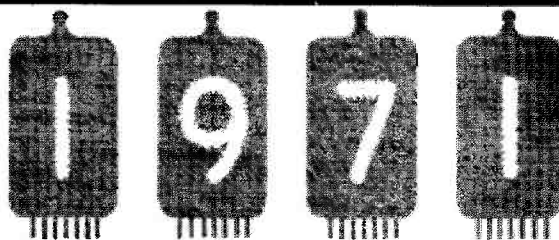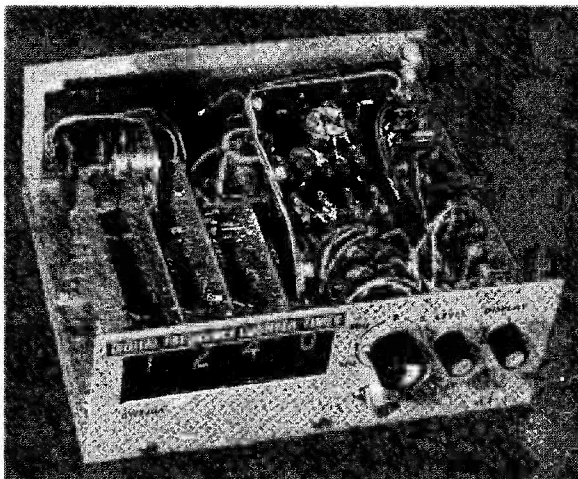

**J. THORNTON-LAWRENCE GW3JGA**

## PART 3 (continued from the October issue)

The cutting and drilling of the panels is shown in Fig. 15 and the drilling and position of the components on the chassis is shown in Fig. 16.

The top cover consists of a simple drop-over inverted 'U' shape. It is  $\frac{1}{2}$ in longer front to back than the chassis and overhangs the front panel by about  $\frac{3}{8}$ in to produce a 'visor' effect. The top cover is fastened by two 6BA screws on each side.

To conceal the screws which protrude through the chassis underneath, a snugly fitting base cover is fitted inside the underside of the chassis and the top cover screws pass through the sides of the chassis into the base cover. The base cover is drilled and tapped 6BA for this purpose, but 6BA self-tapping screws would be equally suitable. The base cover is fitted with four stick-on plastic feet.

To avoid any bending of metalwork, it would be possible to use a piece of  $\frac{3}{8}$ in plywood for the chassis and plastic covered hardboard for the cover. It would still be desirable to make the front and rear panels of aluminium.

The window cut-out for the indicator tubes can be made either by drilling a line of holes and then join-

ing these by filing through, or more simply by using an Abrafile in a hacksaw frame and finally finishing off with a flat file.

The front and rear panels are sprayed with car touch-up enamel and lettered with Letraset. The cover may also be sprayed or alternatively it may be covered with Contact or Fablon self-adhesive plastic material.

## Assembly and Wiring

The various sections of the Digital Frequency Counter/Timer are built separately and then assembled and wired to each other and to the supplies and controls on the main chassis and panels.

The operation of the complete working instrument

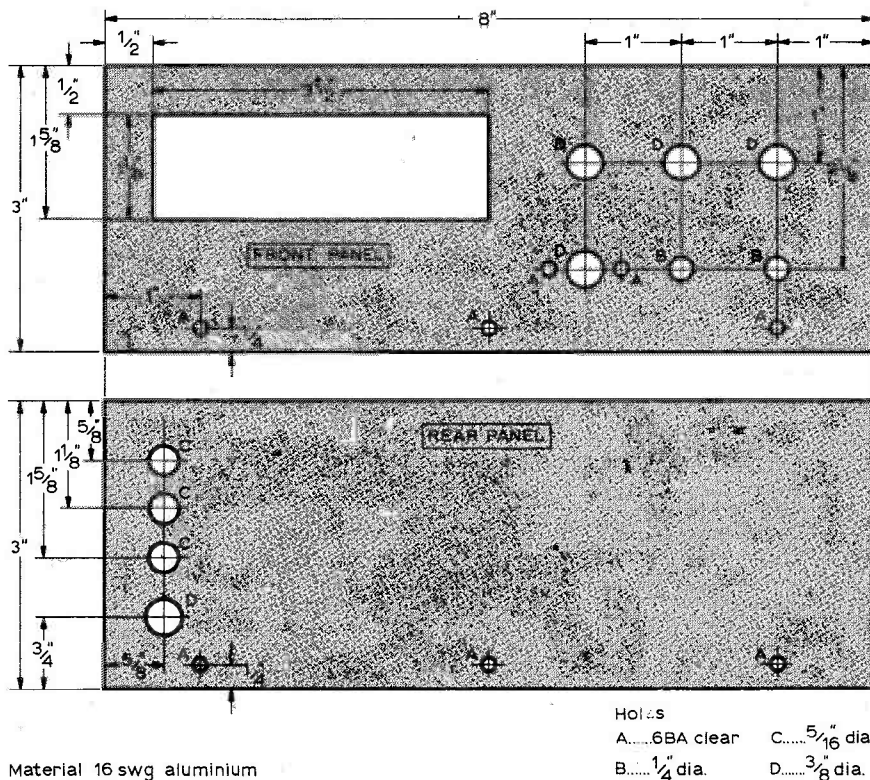


Fig. 15: Front and rear panel metalwork.

is not in itself very complicated, but should any part malfunction due to a wiring error or faulty component, the locating of the fault could prove to be very time consuming. This is mainly due to the fact that the cycle of operation depends on several stages operating in sequence. If the sequence is broken due to a fault condition, all stages become suspect and it may be quite difficult to locate the section containing the fault.

The operation of most of the panels can be checked before being assembled on the chassis and by doing this the possibility of building-in a fault is greatly reduced.

In any case it is always important to try to prevent wiring errors right from the outset and although, to some constructors, the following suggestions on wiring the Veroboard panels may be rather trivial, it is hoped that they will help to produce an instrument which will work first time.

## Main Chassis and Power Supply

It is suggested that this is constructed first as it will provide the various voltages required to test the other parts of the instrument.

The component positions and wiring are shown in Fig. 17.

### Testing

When operated without a load, the h.t. section of the power supply will develop an h.t. voltage of about +350 volts. The -5 volt section will not operate correctly until the h.t. section is loaded, but some negative voltage should be detected across D9, depending on the current drawn by the meter (approximately -5 volts on a 20,000 ohm/volt meter). All voltages are with respect to chassis.

The +5 volt section is regulated and here the no-load voltage will be about +5.2 volts. The voltage across C14 is about +8 volts.

## Crystal Clock and Divider (Panel B)

This panel is built and tested next, as it is needed to provide a test signal for testing the other panels. The components, links and pins are fitted in the manner suggested previously.

Connect the crystal and trimmer to the appropriate pins and, with temporary wires, connect the panel to the chassis earth and the +5 volt supply.


### Testing

The oscillator transistors Tr8 and Tr9 operate in class A and the voltage of +2.3 volts on each collector remains about the same whether the crystal circuit is oscillating or not.

However, the clipper stage Tr10 has a normal operating collector voltage of about +2 volts but if the oscillator is not functioning this voltage will rise to nearly +5 volts. The oscillator circuit has adequate gain for most crystals but for very stubborn surplus types which may refuse to oscillate, C8 may be reduced in value to 220pF. Any further reduction of C8 may cause the circuit to oscillate at some spurious frequency not controlled by the crystal.

With the oscillator and each stage of the divider chain functioning, the voltage at each output point will be approximately +1.6 volts d.c. with the oscillator not functioning the voltage at each point could be +3.5 volts or +0.1 volts depending on the state of the output of the decade counter.

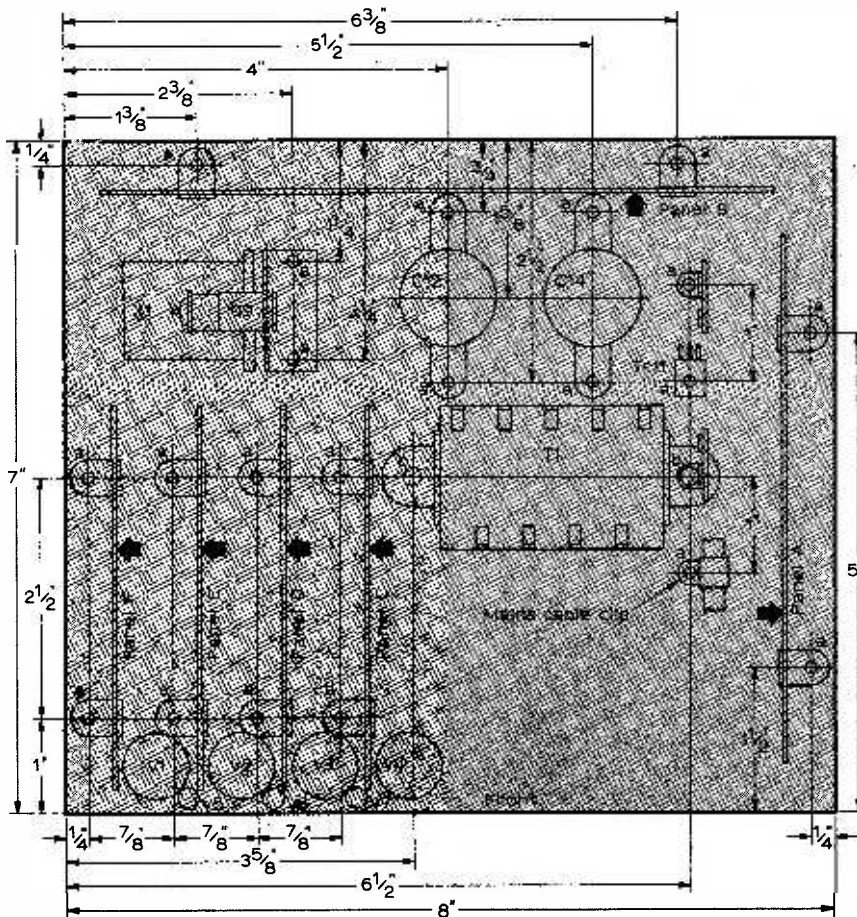The waveform at any of the divider outlets should be a square-wave of 1:1 mark-space ratio and 3.4 volts peak to peak amplitude and of the appro-



Note:—on veroboard panels

◄ Indicates component side of panel

Drilling a.....6BA clear  
b.....4BA clear

Fig. 16: Chassis metalwork and main component layout.

appropriate frequency. The 100kHz output at Tr10 collector should be about 4-7 volts peak to peak. The frequency of the 100kHz oscillator can be checked and set exactly by beating its second harmonic with the 200kHz signal from Droitwich (BBC Radio 2).

A simple way of doing this is by tuning a broadcast receiver to Radio 2 on 200kHz and by connecting

a length of insulated wire to the 100kHz output, B(3), to provide coupling. The wire is placed close to or around the receiver to cause a beat note or whistle to be heard. The trimmer capacitor C9 is then carefully adjusted so that the beat reduces to zero. If the 200kHz signal is very strong it will be necessary to reduce the pick-up of this signal by removing the external aerial or by rotating the set if it has an inbuilt ferrite rod aerial, to obtain a weak reception of the 200kHz transmission.

Near zero beat the difference frequency will be heard as a cyclic variation of the background noise rather than a 'note'. The final setting of the oscillator frequency should be made when the instrument is complete.

## Counter and Display Panels, C, D, E and F

The components, links and pins are fitted to the panel in the usual way.

The numeral indicator tube is fitted to the panel and held in place by the glass pip which fits snugly into a  $\frac{1}{8}$ in  $\times$   $\frac{1}{4}$ in grommet. The grommet is supported by a crossed loop of 20 s.w.g. wire fitted in holes A1 and A4.

The numbers must face the correct direction, the top of the glass pip should be in line with the top of the panel and the straight surface of the glass envelope should extend about  $\frac{1}{8}$ in beyond the end of the panel.

Wiring should commence with the low numbers and the lead-out wires sleeved using small diameter sleeving. The last few wires to be connected should pass over the previous wires. The wires, when soldered, effectively support the base end of the tube.

### Testing

Each panel should be tested separately by connecting it with temporary wiring to the +300 volt, +5 volt and earth, 0 volt, connections.

Connect the crystal clock and divider panel to the same +5 volt supply and using a croc-clip 'jumper' lead join the input of the counter panel (7) to the 1Hz output of the divider B(10).

As the reset input (4) is not connected to 0 volt the counter is continually in the reset condition and the numeral tube should indicate '0'. With another jumper lead join the reset input (4) to 0 volt (6). The numeral tube should now display continuous counting 0-9 at one digit per second.

Disconnecting the jumper lead between (4) and (6) at any time


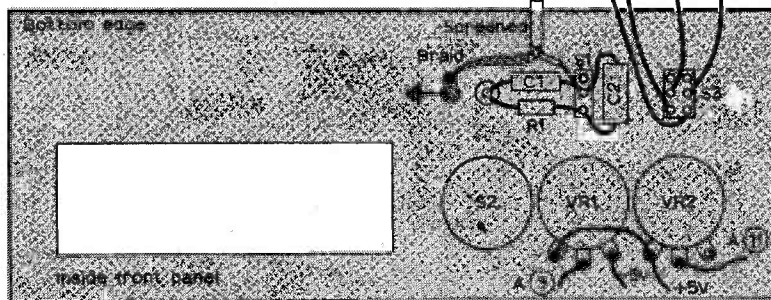
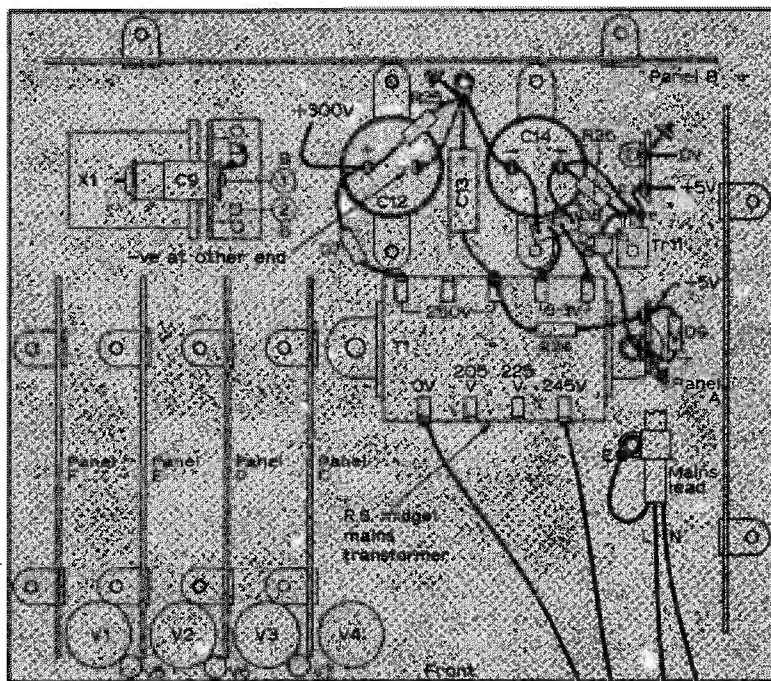


Fig. 17: Chassis and panel wiring.

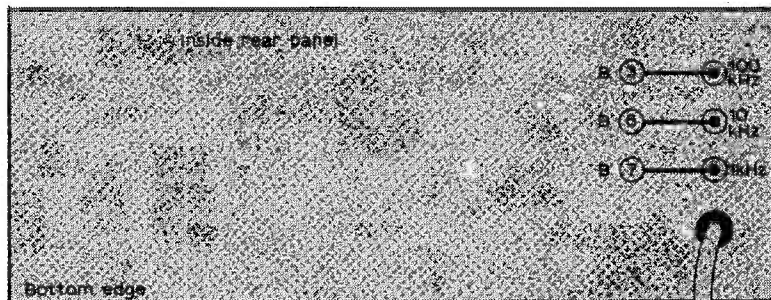

should reset the count to zero, '0'. Counting should recommence when the connection is remade.

The neon 'decimal point' may be checked by connecting a 220kΩ resistor between the decimal point connection (1) and 0 volt (6). A wrong sequence of numbers probably indicates a fault in the wiring of the numeral tube. Two numbers being on together is probably caused by a solder blob short circuiting two strips on the Veroboard, but also could be due to a faulty decoder-driver integrated circuit.

I.C.'s. can be checked by substitution and as four panels are required for the complete instrument a faulty panel can be easily checked against the other three.

When testing counter and display panels it is advisable to insulate the +300 volt connection to the panel in case a jumper lead going to an i.c. accidentally strays on to the +300 volt connection.

Each panel should be checked individually for correct operation and then mounted on the chassis and linked together as shown in Fig. 6. (Part 1, September issue.)

The counting and 'carry' operation of the complete counter and display section may be checked by applying the 1Hz output B(10) from the divider to the signal input C(7) and checking that the carry to the next higher decade is made on the transition from 9 to 0.

The previous remarks about the reset line now apply to all the panels simultaneously.

## Input Stage, Control Oscillator and Gate (Panel A)

To test this panel, it is necessary to have all the other panels installed on the chassis and connected to the appropriate supplies. This applies particularly to the +300 volt supply to the numeral tubes as without the normal loading on this supply the -5 volt supply will not regulate correctly under load. It is not necessary to have S2 connected in circuit when testing the operation of Panel A, and it is advisable to check the operation of all the sections before connecting S2 into circuit.

### Input Stage

With all the supplies connected to panel A, and to VR1 and VR2, connect A(3) to the slider of VR1 and monitor the output of Tr5 A(6) with a voltmeter. Slowly rotate VR1 until a point is found where the voltage at A(6) flips between +4.0 volts and +0.1 volt. Dual voltages are given at various points in the circuit diagram of the input stage and these may be checked if faulty operation is suspected. The actual position of VR1 at which the circuit operates depends on the individual gate characteristic of Tr1.

An oscilloscope check may be made by connecting the input components and S1 to A(1) and A(5) as shown in the circuit diagram and feeding in a 100mV r.m.s. audio frequency signal to the input socket. Switch S1 should be in the a.c. position and the output should be monitored at the output A(6).

The square-wave output should vary in mark-space ratio as VR1 is adjusted and the operating point is moved over the amplitude range of the input signal voltage.

### Control Oscillator

For the control oscillator to function, A(11) must be connected to VR2 as shown in the diagram. Depending on circuit conditions the oscillator circuit may be held in the clamped condition by D4 and D4

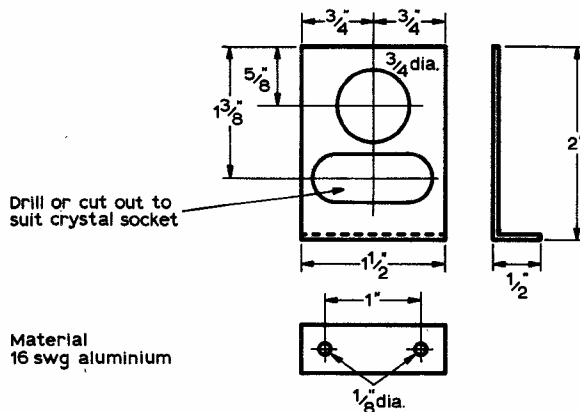


Fig. 18: Crystal mounting bracket.

should be temporarily disconnected by unsoldering one end to stop any clamping action.

The control oscillator should now free-run at a speed determined by the setting of VR2. The slowest speed is one cycle in about 4 seconds.

The square-wave output at Tr6 and Tr7 collectors should have a voltage swing from 0.1 volt to nearly +5 volts. An oscilloscope test may be made at A(8) to check the presence of the positive-going 200μS pulse which performs the resetting of the counter and the setting of IC1a. However, due to the short duration of the pulse and the low repetition rate it may be difficult to observe this pulse on a simple oscilloscope.

The diode D4 should be reconnected after this test.

If the oscillator refuses to run, check the collector voltages of Tr6 and Tr7, if either of these are low, about +0.1 volt, check the coupling capacitors for open circuit. If either is +0.6 volt, check the coupling capacitor for short circuit. If either collector voltage is about +5 volts check the appropriate base feed resistor circuit.

### Gate

The testing of the gate is most easily carried out with all the remaining sections of the instrument operational. The function switch S2 should be left disconnected and temporary wire links used to connect between the various sections.

All supplies should be connected to all panels. Temporary wire connections should be made as follows: Clock divider 1Hz output B(10) to clock period input A(7). Clock divider 1kHz output B(7) to signal input A(9). Gate output A(10) to signal input C(7). Reset output A(8) to reset input C(4).

With these connections made, the instrument should count the 1kHz output for a period of one second and display a reading of 1000. The counter should then reset to 0000 and then commence counting again. This is equivalent to the 'TEST' position on the function switch, position 6.

The time that the reading is displayed before resetting is determined by VR2.

With the exception of wiring errors, it is unlikely that a fault will exist in the gate circuit but in any event the sequence of operations can be followed through from the circuit description given previously and the fault diagnosed from the point in the sequence at which the operation ceased.

With all sections operating correctly the function

—continued on page 634

# practically wireless commentary by HENRY

No. 85

Made  
in  
Where?

**K**ILLED soldiers march across the sea to be sold in Aberdeen. It's enough to make a haggis weep. But until now, November 1971, there had to be, somewhere, a label denoting the country of origin. Or, at least, a tiny ticket under the sporrán that said, unequivocally, 'Foreign'.

Parliament, proud of British prowess, demanded that goods should be so marked way back in 1926. It has taken forty-two years for us to bring in the Trades Descriptions Act, and one of the things written-in when this became law, in 1968, was that by November 1971 the need for declaring a country of origin would end.

Philips introduction of the *Pop-master* radio woke up some of us stick-in-the-muds. Now, we have come to accept the flair of the Italians, the inventiveness of the Scandinavians, the engineering efficiency of the Germans. It is the idea of Oriental precocity that still fails to sink in.

Yet, as I write, the hold on the television market is being tightened by Far East competition. BREMA figures tell us that in the first quarter of this year British-made TV sets dropped from 484,000 to 401,000, i.e., a 16 per cent loss. The increase, taken up by importers, was

practically a total invasion from Japan. In the radio receiver market, we came down from 342,000 to 323,000. I dread to think what a survey of the audio market would reveal.

Henry gets rather hot under the collar when he hears of the 'rationalisation' that the big boys impose on a taken-over small concern. In no time, the special position that made the back-alley company worth taking-over has been flattened and stultified, making its products part of the bland image that the parent company projects.

In the name of 'efficiency' the economies imposed rob the product of all its individuality. It becomes just another wireless set, tape recorder, gramophone . . .

There is an ironically apt story in an American publication just out: 'Welcome to our conglomerate—you're fired!' Large concern takes over small, specialist company and sacks the boss. A little later, sales begin to slump and the whizz-kids search around for a reason. Can't be the absent boss—after all, he spent most of his time playing poker with the salesmen.

Then it comes out: the poker games were the breeding ground for ideas, and the way the boss instilled his very individual flair in his team.

We have seen the loss of the personal touch more than once in the audio world. A notable case has recently been exemplified by some facelifted models. A small firm with an international reputation is merged into a large group. Almost overnight its keen service fades; models are restyled and, basically similar, with no progressive modification, have a posher faceplate. The companion tuner-amplifier, however, is an imported model.

What's wrong with that? Oh, nothing, except that the *implied* 'Made in England' is held in the brand name. The imported gear does not even have its gramo-



"Welcome to our conglomerate—you're fired!"

phone pickup input equalised to the standards of the records we, in this country, are going to be able to buy. But to the unsuspecting public, this is a new (and by implication, better) product from the famous stable.

Many electronic goodies masquerade under strange flags. Home-grown labels mean little when the bits have been imported, needing only assembly, boxing and test.

Perhaps that is why the Government have said 'Drop it.'

Do you remember how Max Grundig started? Back in the days when the Germans were not allowed to purchase a complete radio, he brought out a radio, constructed except for the plugging in of a valve, sold the valve separately, circumvented the regulations and laid the basis of a fortune.


Using the Henry method—what the artistic circle call 'the aleatory technique of random connections and accidental parallels'—I present to you the following information. G.E.C. propose closing the Marconi-Elliott Micro-electronics factories at Witham, Essex and at Glenrothes. The first was especially built as recently as 1968. The second has a prospective new neighbour—a micro-circuit factory to be built at East Kilbride, Lanarkshire, for the great American concern, Motorola.

Will *their* chips be marked 'Made in Britain'?



Killed soldiers march across the seas.

# GOING BACK...

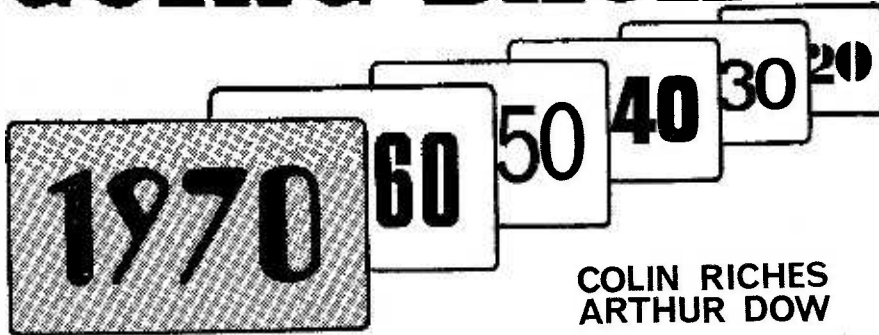

COLIN RICHES  
ARTHUR DOW




**O**UR request for information on the little buzzer unit shown in our September issue met with little response. However, Mr. F. Kirkby of Ruislip, Middlesex, came to the rescue in no uncertain way by producing what appears to be a more sophisticated version of the unit.

Recently Mr. Kirkby had the task of clearing out the house of an elderly relative and amongst the 'junk', some of which is thought to be over 100 years old, was found the wavemeter shown in the accompanying photograph. The circuit, mounted inside the lid of the teak case, is still perfectly clear and shows a parallel tuned circuit which, in the "receive" position of the changeover switch, is connected to an adjustable carborundum detector and to the telephone terminals at the front. In the "send" position the tuned circuit is connected to the buzzer and cell. The cell in the equipment appears to be the original Siemen's 'S' type cell.

The circuit notes that "the inductance is a 5-turn rectangular coil  $3\frac{1}{2}$ in.  $\times$  2in. lying close against the front face of the case" presumably to allow the wavemeter to be closely coupled to the external equipment under test.

The dial is finely engraved in steps from '45' to '95' and this is presumed to be the range covered, in metres. Anyway, a new cell was fitted to the wavemeter and the buzzer adjusted on "send" and the unit placed a few feet from a communications receiver tuned to 5MHz (60 metres) and sure enough the signal, if it can be called that, did peak when the dial of the wavemeter was tuned through the 60m. point on the dial.

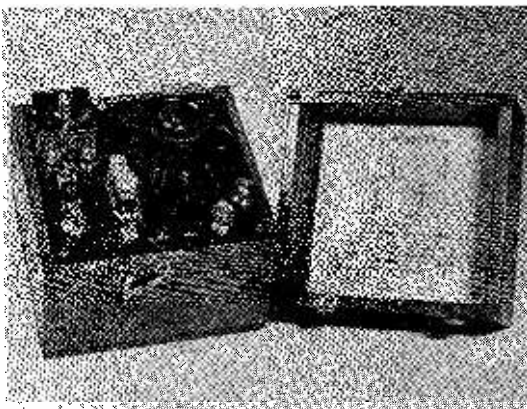


Since no aerial terminal is provided it is presumed that the "receiver" was used as a monitor for a local transmitter and used to set the transmitter to a particular wavelength.


Unfortunately there is no indication of the maker's name or the year of manufacture so once again we must ask our readers to help in identifying this bit of vintage equipment.

Mr. Kirkby is to be congratulated on his vigilance and for rescuing this piece of ancient equipment. We make no excuse for again reminding readers of the thousands of pieces of similar equipment that must be hidden away in sheds, attics and storerooms and which must not be allowed to finish up in some dustcart. There are collectors in the UK who will see that such equipment gets the attention it deserves.

Since writing the above we have heard further from Mr. Kirkby. He has now discovered some old documents including the photograph we show of an amateur radio station operating in 1922. The actual wavemeter under discussion can be seen at the left hand end of the operating desk. Mr. Kirkby now believes that the wavemeter dates from 1916 and that it was obtained as "Ordnance Disposal" or "Government Surplus" as we would call it today.

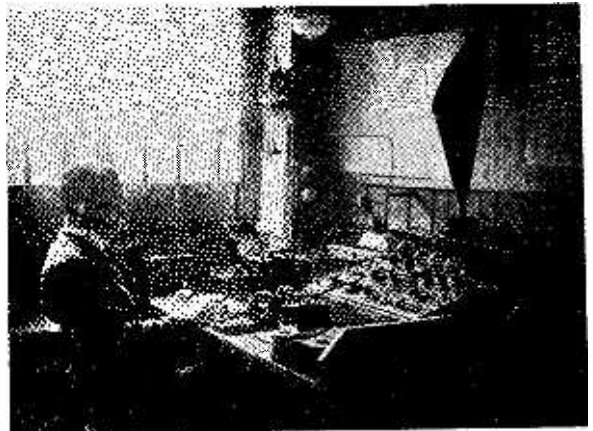

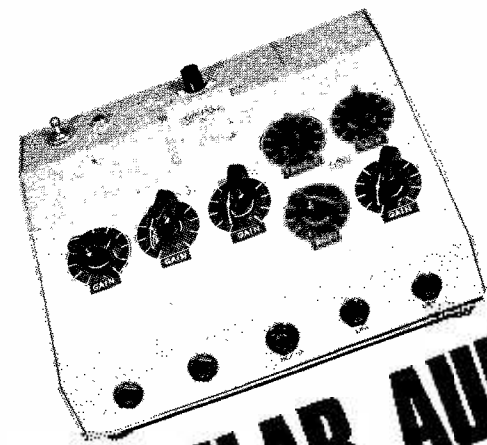Incidentally, the two wall charts to the right of the speaker were issued by the Marconi Company and represent the movement of ships equipped with wireless. Presumably listeners could estimate the "range" of their receivers by listening for these ships over varying distances.



# MODULAR AUDIO MIXING SYSTEM



F.C. JUDD

**D**ETAILS concerning the possible audio signal mixing combinations, and circuits for the line amplifier, a microphone pre-amp for low impedance microphones and a suitable power supply etc., were given in Part 1.

We continue now with more circuits for pre-amplifier stages beginning with one for crystal microphones (Code: Mic Hi-ZX). This is given in Fig. 11 and the circuit board layout is shown in Fig. 12. Crystal microphones have a high output impedance, hence the need for the high series input resistance, R1, to the base of Tr1. The circuit is conventional with d.c. stabilization and negative feedback which also sets the amplifier gain by the feedback network C5 and R3. The 100pF capacitor across R3 produces a roll-off in frequency response above about 30kHz to prevent pick up of r.f. signals as is often the case with preamplifiers having a high frequency response. As with all the preamplifier stages, the output is taken to the gain control VR1 and thence to the line amplifier (or tone control unit) via the passive mixing component R9. Details of the circuit board and screen construction for all the preamps and the tone control were given in Part 1.

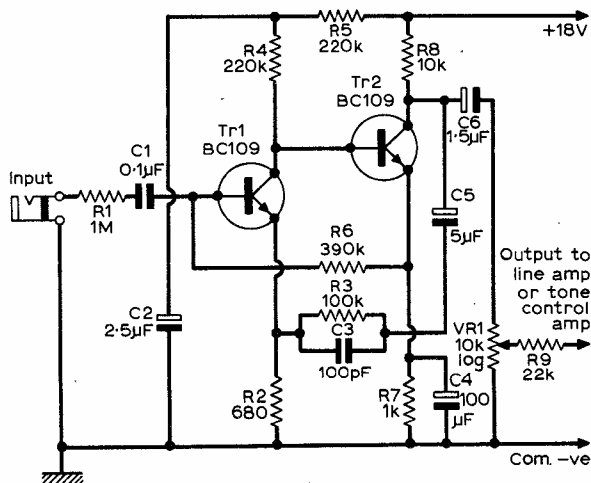


Fig. 11: The crystal microphone preamp circuit.

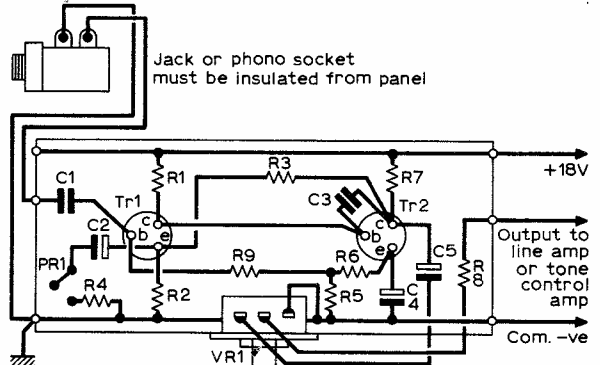


Fig. 12: The component layout for the crystal mic. preamp.

## PREAMPLIFIER FOR MAGNETIC PICK-UPS

The circuit is given in Fig. 13 and its code is **PU Mag.** Again a conventional BC109 pair is used with d.c. stabilization and a negative feedback equalization network between Tr2 collector and Tr1 emitter to obtain the correct R.I.A. response for magnetic cartridges. The actual response curve was

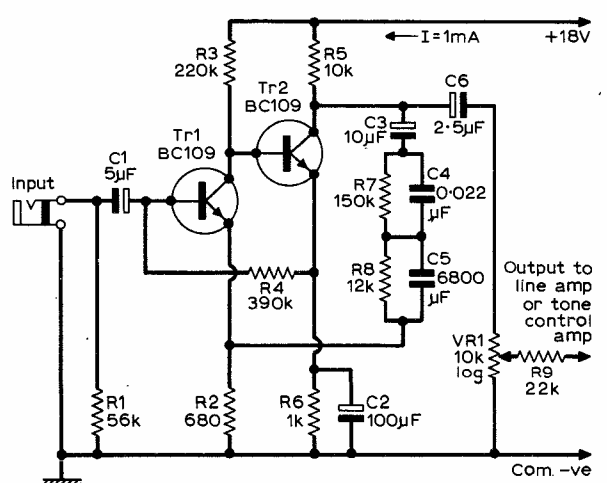


Fig. 13: The circuit of the magnetic pickup preamp.


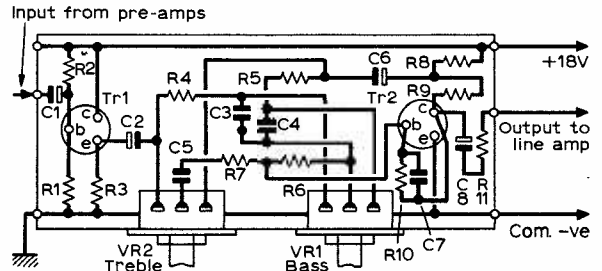
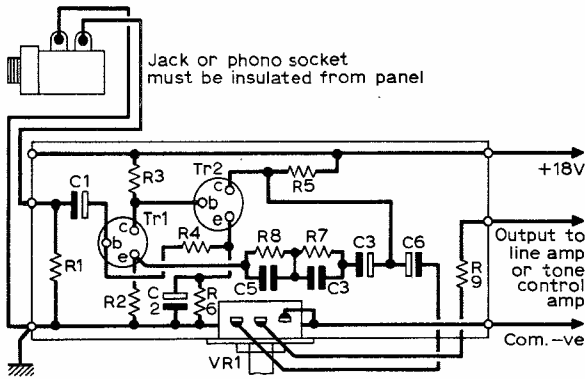


Fig. 14: (left) Component layout for mag. pickup preamp.  
 Fig. 15: (below) The tone control module circuit.  
 Fig. 16: (above) Layout of the tone control module.

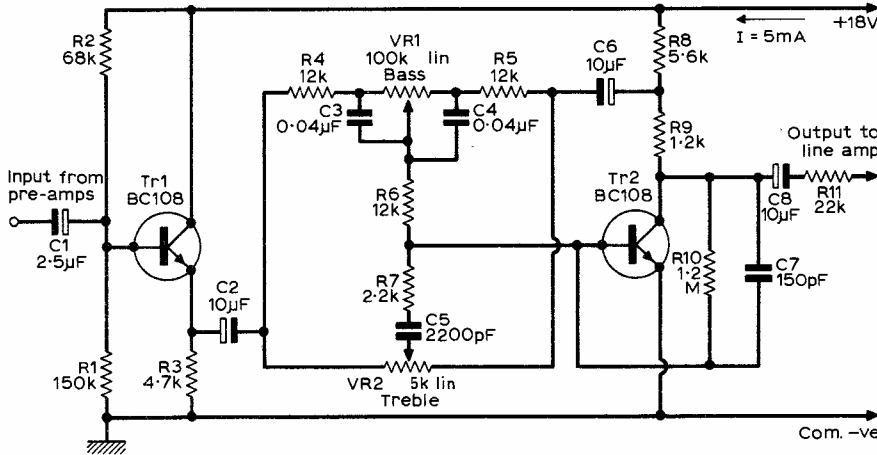

given in Part 1. The output, via VR1 and R9, is again as common to all the preamps. The input sensitivity is approximately 5mV and the overload margin at least 10 times this. The circuit board layout and wiring is given in Fig. 14.

## THE TONE CONTROL UNIT

This has unity gain and an input sensitivity of 100mV so the output is therefore 100mV. The tone control unit will accept the outputs from any of the preamps and one or more may be connected to its

## ★ components list

### Mic Pre-amp (Mic Hi ZX)

Tr1, Tr2 BC109  
 VR1 10kΩ Carbon log. pot.

#### Resistors

R1 1MΩ R6 390kΩ  
 R2 680Ω R7 1kΩ  
 R3 100kΩ R8 10kΩ  
 R4 220kΩ R9 22kΩ  
 R5 220kΩ  
 All ½W, 10% types

#### Capacitors

C1 0.1μF C4 100μF 25V  
 C2 2.5μF 25V C5 5μF 25V  
 C3 100pF C6 1.5μF 25V

### Magnetic p.u. pre-amp (PU Mag)

Tr1, Tr2 BC109  
 VR1 10kΩ Carbon log. pot.

#### Resistors

R1 56kΩ R6 1kΩ  
 R2 680Ω R7 150kΩ  
 R3 220kΩ R8 12kΩ  
 R4 390kΩ R9 22kΩ  
 R5 10kΩ  
 All ½W, 10% types

#### Capacitors

C1 5μF 25V C4 0.022μF  
 C2 100μF 25V C5 6800pF  
 C3 10μF 25V C6 2.5μF 25V

### Tone Control Unit (TC)

Tr1, Tr2 BC108  
 VR1 (bass) 100kΩ Carbon lin. pot.  
 VR2 (treble) 5kΩ Carbon lin. pot.

#### Resistors

R1 150kΩ R5 12kΩ R9 1.2kΩ  
 R2 68kΩ R6 12kΩ R10 1.2MΩ  
 R3 4.7kΩ R7 2.2kΩ R11 22kΩ  
 R4 12kΩ R8 5.6kΩ  
 All ½W, 10% types

#### Capacitors

C1 2.5μF 25V C4 0.04μF C7 150pF  
 C2 10μF 25V C5 2200pF C8 10μF 25V  
 C3 0.04μF C6 10μF 25V

### Ceramic p.u. amp (P.U. Cer)

Tr1, Tr2 BC109  
 VR1 10kΩ Carbon log. pot.

#### Resistors

R1 470kΩ R5 1.5MΩ R9 820Ω  
 R2 120kΩ R6 12kΩ R10 22kΩ  
 R3 150kΩ R7 120kΩ  
 R4 1.5kΩ R8 10kΩ  
 All ½W, 10% types

#### Capacitors

C1 0.1μF C4 100μF 25V  
 C2 0.1μF C5 2.5μF 25V  
 C3 2.5μF 25V



input. The output from the tone control unit is taken via the passive mixing component R11 so it may, in turn, be connected to the line amplifier together with any one or more preamps. Equally two or more tone control units each accepting a number of preamps may be simultaneously connected to the line amplifier. The circuit for the tone control unit is shown in Fig. 15. (Note that BC108 transistors are used) and the board layout in Fig. 16. The input is taken to the active (negative feedback) network via the emitter follower Tr1. The insertion loss of the tone control network is recovered by the amplifier stage Tr2 but amplification is controlled to obtain unity gain. The frequency response curves for the unit were given in Part 1 but it provides approximately 15dB cut and lift at 40 and 20,000Hz respectively.

## PREAMPLIFIER FOR CERAMIC PICK-UP CARTRIDGES

The requirements for the preamplifier input are generally similar to those for a crystal pick-up cartridge except that the input sensitivity is higher. The circuit in Fig. 17 provides a high input impedance and a sensitivity of about 60mV. Tr1 is an emitter follower and Tr2 the amplifier with negative

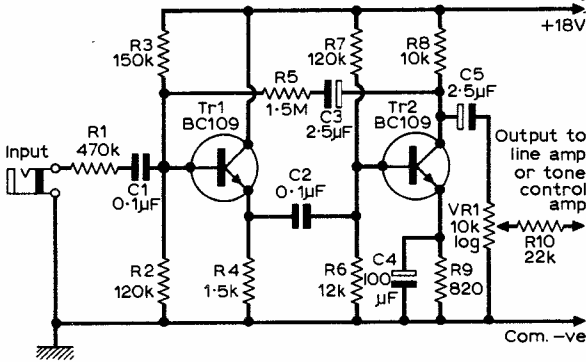


Fig. 17: The ceramic pickup cartridge circuit.

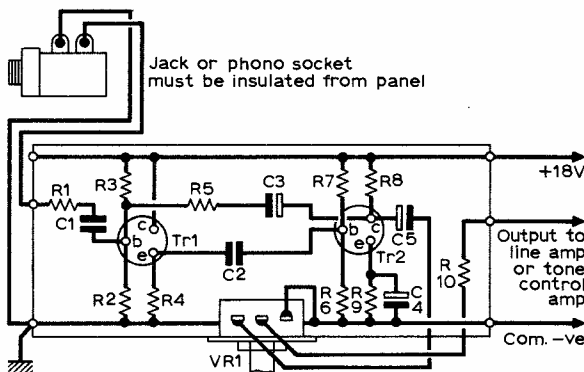


Fig. 18: The layout of the ceramic pickup preamp.

feedback between output and input to obtain the correct gain and wide frequency response. The output is taken via the gain control VR1 and the passive mixing component R10. The circuit board layout is shown in Fig. 18.

TO BE CONTINUED

## SPECIAL INTRODUCTORY OFFER FREE P & P this month only! COMPLETE STEREO SYSTEM



AMC can now offer this superb quality system at an unheard of price.

The backbone of the system is the HL SA 707 Stereo Amplifier. The unit is housed in a sturdy Teak Cabinet with a black & silver fascia. Power output 20 watts (speech and music). Frequency Response 15-20,000 Hz. Special features include, Scratch Filter, Headphone Sockets and facilities for all types of cartridges. Together with the matching high quality AMC 3-way speaker system, world renowned Garrard 2025TC deck including plinth, cover and Sonotone 9TAHC cartridge, make an unbeatable system.

Or as above, but with Garrard SP 25 Mk III deck with Goldring G.800 Magnetic Cartridge, £35.00 inc. leads & plugs, P & P £2.00.

**Yours for only  
£49**  
inc. leads & plugs  
P & P £2.00




### TELETON CRI0T Stereo System

AM/FM Stereo Tuner Amplifier in superb walnut cabinet 4 watts per channel, AFC, built-in MPX and Cer/XTAL input, complete with pair of matching Teleton speakers £29.95 inc. leads & plugs, P & P £2.00.

With matching Garrard 2025TC deck including plinth, cover and a Sonotone 9TAHC cartridge £42.00 inc. leads & plugs P & P £1.00.
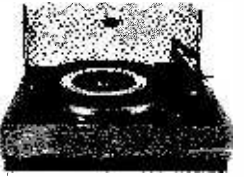
### TELETON SAQ 206 Stereo Amplifier

It's here, the latest model in a beautiful walnut case. Special sliding balance control, scratch filter, and loudness control. 6 x 6 watts RMS. Switched inputs for Xtal, aux. tape and Mag. £19.95 inc. leads & plugs, P & P 37p.



### GARRARD SP25 MkIII

Turntable complete with Goldring G.800 Magnetic Cartridge, plinth & cover.

### OUR FANTASTIC PRICE £19.95

inc. leads & plugs, P & P 50p.

### FANTASTIC KELETRON SPEAKER BARGAINS

Rec/Price	Our Price	P & P	Rec/Price	Our Price	P & P	
KN 400	£8.05 each	£5.80	75p	KN 1100	£20.40 each	£14.00
KN 600	£13.43 each	£9.99	85p	KN 1600	£25.20 each	£16.00
KN 800	£15.90 each	£10.50	£1.00	KN 2100	£30.60 each	£20.00

£1.50

#### DECKS

Goldring GL75 mounted in Teak Plinth, with Tinted Perspex Lid complete with G.800 magnetic cartridge. £45.00. P & P 50p.

Goldring GL69 mounted in Teak Plinth, with Tinted Perspex Lid complete with G.800 magnetic cartridge. £37.00. P & P 50p.

Garrard AP76 mounted in Teak Plinth, with Tinted Perspex Lid complete with Goldring G.800 magnetic cartridge. £30.50. P & P 50p.

#### CARTRIDGES

Goldring G850 £4.50  
Goldring G800 £7.50  
Goldring G800H £7.05  
Goldring G800E £11.15

ALL ITEMS ARE FULLY GUARANTEED AND COME BRAND NEW IN MANUFACTURERS SEALED CARTONS

#### DEMONSTRATIONS BY APPOINTMENT

#### MAIL ORDERS TO:

**AMC Co**

Dept. P.W., 149 Etchingam Park Road, London, N.3.  
Tel: 01-346 3313  
Make Cheques and Money Orders payable to AMC Co. E.O.E. Subject to availability.

# BASIC signal generator


R. H. LONGDEN

**A**LTHOUGH a signal generator is extremely useful for the testing, aligning and calibrating of receivers and for quick tests of audio circuits, the construction of such a project may be considered to be complicated and possibly expensive. In this case, however, the signal generator here should prove ideal. It has a basic circuit, requires only a few components, yet will easily fill most of the needs which arise when dealing with receivers.

The following outputs are available from the generator:

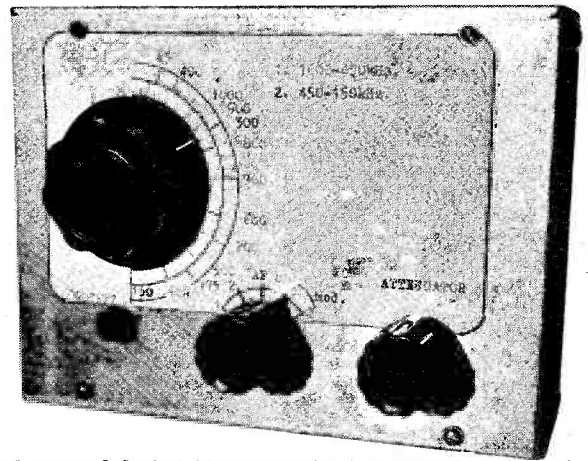1. Tone-modulated r.f. signal in the range 150-450kHz.
2. Tone-modulated r.f. signal in the range 450-1600kHz.
3. Audio tone.
4. Unmodulated signal in the range 150-450kHz.
5. Unmodulated signal in the range 450-1600kHz.

1 and 2 are used for the general alignment and testing of receivers, and includes the 455-470kHz i.f. frequencies. 4 and 5 are used for similar purposes



when modulation is not required. 3 allows testing of a.f. stages and amplifiers.

## THE CIRCUIT

Figure 1 shows the circuit and uses a single double-triode valve, one section performing as a tunable r.f. oscillator and the other section as an a.f. oscillator. Power is derived from a small 12·6V heater transformer and this also gives a little over 20V d.c. across C7 for the anode supply voltage.

V1a is the r.f. oscillator, tuned by VC1. With S1a in position 1, L1 and L2 are in series, for Range 1 (450-150kHz). With position 2, L2 is shorted, L1 covering about 450-1600kHz, for Range 2. V1b is the a.f. oscillator. Both valve anodes draw h.t. through the primary of T2, thus modulating the r.f. output.

R.F. is taken VR1 through C4 to the attenuator or output control VR1. With S1 in position 3, S1a shorts VC1 so that no r.f. is produced, and S1b brings in the larger capacitor C5, the a.f. output of V1b passing to VR1.


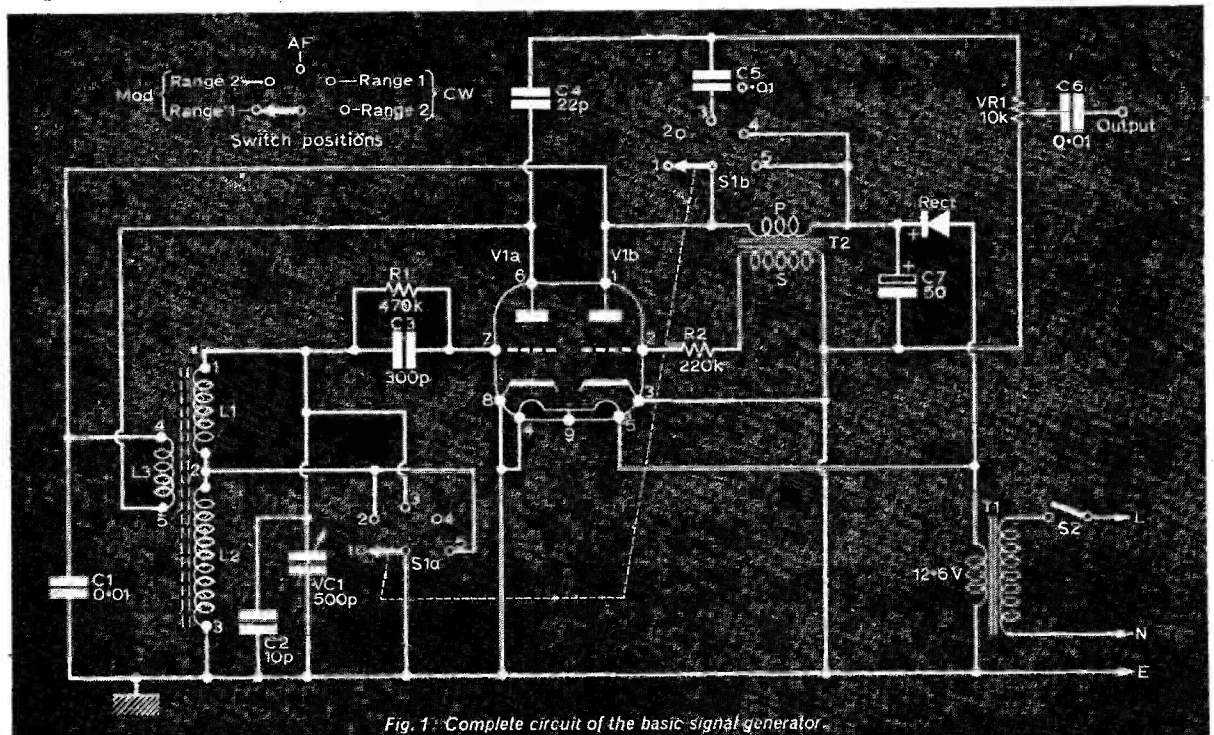


Fig. 1: Complete circuit of the basic signal generator.

**PHILIPS PORTABLE PLAYER CABINET**

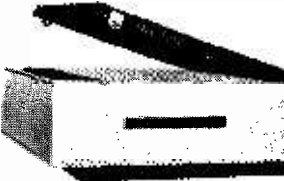

Size 18 x 15 1/2 x 7 1/2 in. Cut for B.S.E. UA12/14/15/16/25 deck. Amplifier space 14 x 6 x 3 1/2 in. Satin aluminium front grille. Ready smart appearance. £4 Post 25p Black/White. Chrome fittings.

**BSR C.109 SUPERSLIM STEREO AND MONO CHANGER**

Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months guarantee. AC 200/250v. Size 13 1/2 x 11 1/2 in. Above motor board 3 1/2 in. below motor board 2 1/2 in. with STEREO and MONO XTAL




£7.75 Post 25p

GARRARD SINGLE PLAY TA Mk II Stereo/Mono £10 GARRARD FLAVERS with Bonitone 9TA Cartridges. Stereo Diamond and Mono Sapphire. SP25 Mk II £15 Model 8500 Stereo and Mono Autochanger £14. Post 25p. RECORD PLAYER PORTABLE CABINET £7.75 Space for amplifier and autochanger. Post 25p. RCS DE-LUXE 3 WATT AMPLIFIER. Ready made with 2-stage triode pentode valve, 3 watts output. Tone and volume controls. Isolated mains transformer, knobs, loudspeaker valves ECL25, E2280. Response 50-12,000 cps. Sensitivity 200mV. Post 25p. £4

R.C.S. TEAKWOOD BASE. Ready cut out for mounting (State player make and model). £2.75 R.C.S. PLASTIC COVERS FOR ABOVE BASE. Durable tinted plastic, attractive appearance. £2.75 EMI PICK-UP ARM with mono xtal and stylus £1.25. HI-FI PICK-UP CARTRIDGES. Diamond Stereo/Mono-9TA £2-50; GP24 £2-50; GP28 £2-00; Mono GP21 £1-50; GCS £1-25; ACOS LP. Only 50p.

**AM-FM/VHF TUNING GANG**

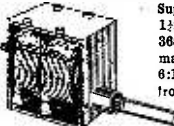

Super quality small size 1 1/2 x 1 1/2 in., plus spindle 1 1/2 x in. 365 + 365 pF with 25 + 25 pF. British made. Gears slow motion drive 6:1. Plastic dust cover. 6BA tapped front fixing. Cast aluminium frame 50p Post Free

WEYRARD P50-TRANSISTOR COILS  
RA2W Ferrite Aerial. 65p Spare Cores 3p  
Osc. P50/1AC. 30p Driver Trans. LFDT4 50p  
I.F. P50/2CC 470 kc/s. 38p Printed Circuit. PCAL 50p  
3rd I.F. P50/3CC. 38p W.B. Tuning Gang. 65p  
P51/1 or P51/2. 38p Jeyrad Booklet. 10p  
P50/3V. 38p OPTI. 55p  
Mullard Ferrite Rod 8 x in. 25p. 6 x in. 25p.

**VOLUME CONTROLS**  
Long spindles. Midget Size 5 K. Ohms to 2 Meg. LOG or LIN. L/S 15p. D.P. 25p. STEREO L/S 55p. D.P. 75p. Edge 5K. 3 P. Transistor 25p

**WIRE-WOUND 3-WATT POTS.** Small type with small knob. Values 10 Ω to 30 K. 25p

**VEROBOARD 0.16 MATRIX**  
2 1/2 x 5 in. 19p. 2 1/2 x 8 1/2 in. 16p. 3 1/2 x 8 1/2 in. 19p. 3 1/2 x 5 in. 26p. EDGE CONNECTORS 16 way 25p; 24 way 38p. PINS 36 per packet 17p. FACE CUTTERS 38p. S.R.E.P. Board 0.15 MATRIX 2 1/2 in. wide 8p per in., 3 1/2 in. wide 4p per 1 in.; 5 in. side 5p per in. (up to 17 in.). S.R.E.P. undrilled 4 in. Board 10 x 5 in. 15p.

**BLANK ALUMINIUM CHASSIS.** 18 s.w.g. 2 1/2 in. side. 8 x 4 in. 45p; 8 x 6 in. 49p; 10 x 7 in. 70p; 14 x 9 in. 90p; 16 x 6 in. 90p; 12 x 8 in. 50p.

**ALUMINIUM PANELS** 18 s.w.g. 6 x 4 in. 3p; 8 x 6 in. 15p; 10 x 7 in. 17p; 12 x 8 in. 23p; 14 x 9 in. 27p; 12 x 12 in. 32p.

1 1/2 inch DIAMETER WAVE-CHANGE SWITCHES 25p. 2 p. 2-way, or 2 p. 6-way or 3 p. 4-way 25p each. 1 p. 12-way, or 4 p. 2-way, or 4 p. 3-way 25p.

1 inch DIAMETER WAVECHANGE "MAKITS" 1 p. 12-way, 2 p. 6-way, 3 p. 4-way, 4 p. 2-way, 6 p. 2-way, 1 water 60p, 2 water 90p. Extra washers up to six 80p each.

**"THE INSTANT" BULK TAPE ERASER AND RECORDING HEAD DEMAGNETISER** 200/250 v. A.C. Leaflet S.A.E. £2.35 Post 15p



Minimum Post and Packing 15p RETURN OF POST DESPATCH. HI-FI STOCKISTS. CUSTOMERS FREE CAR PARK. CALLERS WELCOME

**RADIO COMPONENT SPECIALISTS** 337 WHITEHORSE ROAD, CROYDON Open 9-6 p.m. (Wednesdays 9-1 p.m., Saturdays 9-5 p.m.) List 5p. Written guarantee with every purchase. (Export: Remit cash and extra postage.) Buses 133, 68 pass door. S.R. Stn. Selhurst. Tel. 01-684-1665

R.C.S. STABILISED POWER PACK KIT  
All parts and instructions with Zener Diode, Printed Circuit, Bridge Rectifier and Double Wound Mains Transformer input 200/240v. AC. Output voltages available 6 or 9 or 12 or 15 or 18 or 20v. DC. at 100mA or less. PLEASE STATE VOLTAGE REQUIRED. £2 POST Details S.A.E.

**GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE**  
for Mike, Tape, P.U., Guitar, etc.  
Battery 9-12v or H.T. line 200-300v D.C. operation. Size 1 1/2 x 1 1/2 x 1". Response 25 cps. to 25 Kc/s. 26db gain. For use with valve or transistor equipment. Full instructions supplied. 90p Post Brand new. Guaranteed. Details S.A.E.

**NEW TUBULAR ELECTROLYTICS**  
2/850V .14p 250/25V .14p 16+16/500V .55p  
4/850V .14p 500/25V .27p 50+50/350V .35p  
8/850V .14p 1000/25V .42p 50+100/350V .55p  
16/450V 15p 1000/50V .47p 32+32/250V .15p  
32/450V 20p 8+8/450V 15p 32+32/450V .38p  
25/25V 10p 8+16/450V 20p 350+50/325V 50p  
50/50V .10p 16+16/450V 25p 32+32+32/350V 43p  
100/25V .10p 32+32/350V 25p 100+50+50/350V 48p

**SUB-MIN. ELECTROLYTICS** 1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p; 500, 1000mF 2V 15p; 2000mF 25V 35p.  
**CERAMIC** 1pF to 0.01 mF, 4p. Silver Mica 2 to 5000mF. 4p.  
**PAPER** 500V-0.1 4p, 0.5 15p; 1mF 15p; 2mF 150V 15p.  
**500V-0.001 to 0.05 4p; 0.1 5p; 0.25 8p; 0.47 25p.**  
**SILVER MICA.** Close tolerance 1% 2.2-500pF 8p; 500-2-200 pF 10p; 2.700-5,600pF 20p; 6,800pF-9.01, mid 30p; each.  
**TWIN GANG "0-0"** 205pF -176pF, 65p; Slow motion drive 365+365 with 25+25 50p. 4p. Silver Mica 2 to 5000mF. 4p.  
45p; small 3-gang 500pF 1.10. SHORT Wave. Single 25pF 55p  
**CHROME TELESCOPIC AERIAL,** swivel base. 23in. 20p.  
**TUNING.** Dielectric. 100pF. 500pF. 35p each.  
**TRIMMERS.** Compression 30, 50, 70pF, 5p; 100pF, 150pF, 5p; 250pF, 10p; 600pF, 10p; 600pF 10p; 125pF 10p.  
**RECTIFIERS** CRYSTALLITE COOLANT 100V 1A 38p; 85mA 48p. SILICON BYZIS 30p; BY100 80p; BY127 30p.  
**EX-GOVERNMENT RECEIVERS** 250V, 200mA, 30p.  
**NEON PANEL INDICATORS** 250V AC/DC Red or Amber 20p.  
**RESISTORS.** 1/2 w., 2 w., 20% 1p; 2 w. 5p.  
**HIGH STABILITY.** 1 w., 2%, 10 ohms to 1 meg., 10p.  
Ditto 5%. Preferred values 10 ohm to 10 meg., 4p.  
**WIRE-WOUND RESISTORS** 5 watt, 10 watt 15 watt, 10 ohms to 100K. 10p each; 21 watt, 1 ohm to 8.2 ohms 10p

**PHILIPS TRANSISTOR FM STEREO MULTIPLEX DECODER.** As used in LEAK Troughline Tuner. Brand New. Pre-aligned with 9 semi-conductors. 24v. DC at 6mA. Complete with circuit and connection details. £4. POST Size 3 1/2 x 2 1/2 in. FREE


**MAINS TRANSFORMERS ALL POST 25p each**  
250-0-250 80 mA. 6.3 v. 4 v. 11.0 v. £1.40  
250-0-250 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a. £2.00  
350-0-350 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a. £2.00  
300-0-300 v. 120 mA. 6.3 v. 4 a. C.T.; 8.3 v. 2 a. £2.80  
MINIATURE 200 v. 20 mA., 6.3 v. 1 a. 2 1/2 x 2 1/2 x 2 in. 75p  
MIDGET 220 v. 45 mA. 6.3 v. 2 a. 2 1/2 x 2 1/2 x 2 in. 80p  
P.E. AURORA TRANS. 12 + 12v. 500mA. £1.50  
MINI-MAINS 20v. 100mA. 1 1/2 x 1 1/2 x 1 1/2 in. 50p  
HEATER TRANS. 6.3v. 3 a. 60p  
Ditto tapped sec. 1.4 v., 2.3, 4, 5, 6, 8 v. 1 1/2 amp. 30p  
**GENERAL PURPOSE WOUND** Paper Output  
at 2 amp. 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24, 30 v. £2.00  
1 amp., 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60, £2.00  
2 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60, £3.00  
**AUTO TRANSFORMERS** 115v. to 230v. or 230v. to 115v.  
Isolated Output. 150-250, 220-500v. 25v. 1000v. £12.  
**CHARGER TRANSFORMERS.** Input 200-250v.  
for 6 or 12v., 1 1/2 amp. £1.20; 2 amp. £1.60; 4 amp. £2.00.  
**FULL WAVE BRIDGE CHARGER RECTIFIERS:**  
6 or 12 v. outputs, 1 1/2 amp. 40p; 2 amp. 55p; 4 amp. 85p.  
All transformers Postage 25p extra.

**E.M.I. 13 1/2" x 8in. LOUSPEAKERS**  
With twin tweeters and crossover, 10 watt. State 3 or 8 or 15 ohm. (As illustrated) Post 15p £4  
With flared tweeter cone and ceramic magnet, 10 watts. Bass resp. 15-50 cps. Flux 10,000 gauss, or 15 cps. State 3 or 8 or 15 ohm. Post 15p £2.25  
Recommended Teak Cabinet Size 16 x 10 x 9 in. Post 25p £5

**10W MINI-MODULE £3.25 LOUSPEAKER KIT** Post 25p  
Triple speaker system combining on ready cut baffle. 1/2 in. chipboard 15 in. x 8 1/2 in. Separate Bass, Middle and Treble loudspeakers and crossover condenser. The heavy duty 6 in. Bass Woofer unit has a low response cone. The mid-Range unit is specially designed to add drive to the middle register and the tweeter recreates the top end of the musical spectrum. Total response 20-15,000 cps. Full instructions for 3 or 15 ohm.  
**TEAK VENEERED BOOKSHELF ENCLOSURE.** 16 1/2 x 10 1/2 x 6 in. Modern Design, dark grey Tygan covered baffle. Post 25p £5

**ALL MODELS "BAKER SPEAKERS" IN STOCK**

**BAKER 12in. MAJOR £9**

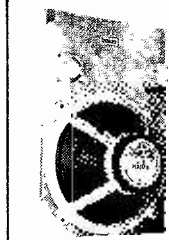

30-14,500 c.p.s., 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c.p.s. Rated 20 watts. Voice coils 3 or 8 or 15 ohms. Post Free  
Module kit, 30-17,000 c.p.s. with tweeter, crossover, baffle and instructions. £11.50

**BAKER "BIG-SOUND" SPEAKERS**  
'Group 25' 12 inch 25 watt 3 or 8 or 15 ohm £7  
'Group 35' 12 inch 35 watt 8 or 8 or 15 ohm £9  
'Group 50' 15 inch 50 watt 8 or 8 or 15 ohm £19

**TEAK HI-FI SPEAKER CABINETS.** Fluted wood front for 12in. round Loudspeaker £20. Post 25p For 18 x 6in. Loudspeaker £25. Post 25p For 10 x 6in. round Loudspeaker £24. Post 25p LOUSPEAKER CABINET WADDING 18in. wide. 15p ft.

**GOODMANS HI-FI 6in. WOOFER** 8 ohm, 10 watt. Large ceramic magnet. 30-12,000 cps. Ideal P.A. Columns. HI-FI Enclosures Systems, etc. £4

**ELAC CONE TWEETER-LATEST DESIGN**  
The moving coil diaphragm gives good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 cps to 18,000 cps. Size 3 1/2 x 3 1/2 in. deep. Rating 10 watts, 3 ohm or 15 ohm models. £1.90 Post 10p

Horn Tweeters 2-16kc/s, 10W 8 ohm or 15 ohm £1-60 De Luxe Horn Tweeters 2-8 kc/s, 15W, 8 ohm £2-00 TWO-WAY 3000cps CROSSOVERS 3 or 8 or 15 ohm 95p SPECIAL OFFER! 80 ohm, 2 1/2 in. dia.; 35 ohm, 3 in.; 3 in 25 ohm, 2 1/2 in. dia.; 3 in. dia.; 8 x 5 in.; 8 x 5 in. £1 EACH 15 ohm, 3 1/2 in. dia.; 7 x 4 in.; 8 x 5 in. £1 TYPE 8 ohm, 8 x 4 in.; 3 ohm, 2 1/2 in. dia. 3 in. 5 x 3 in. 7 x 4 in. LOUSPEAKERS P.M. 3 OHMS. 6 1/2 in. £1.10; 8 x 5 in. £1.25; 8 x 5 in. 20p; 8 in. £1.75; 10 x 6 in. £1.80  
5in. WOOFER 8 watts max. 30-10,000 cps. 8 or 15 ohm. £1-90. ELAC 8 in. De Luxe Ceramic 3 ohm or 15 ohm £2-50. RICHARD ALLAN TWIN CONE LOUSPEAKERS. 8in. dia. 4 watt; 10in. dia. 5 watt; 12in. dia. 6 watt 3 or 8 or 15 ohm models £1.95 each. Post 15p.  
OUTPUT TRANS. EL34 etc. 25p. MIKE TRANS. 50-1 25p. SPEAKER COVERING MATERIALS. Samples Large S.A.E. GOODMAN'S OUTPUT TRANSFORMER 5 watt push-pull for valves EL84 etc., 3, 8 and 15 ohms 85p. Post 20p

**BAKER 10W TATT ALL PURPOSE POWER AMPLIFIER** 4 inputs speech and music. 4 mixing facilities. Response 10-30,000 cps. Matches all loudspeakers. A.C. 200/250v. Treble and Bass controls. Guaranteed. Details S.A.E. £39 POST FREE

**ALL EAGLE PRODUCTS**  
SUPPLIED AT LOWEST PRICES ILLUSTRATED EAGLE CATALOGUE 20p. Post Free.  
**BARGAIN AM TUNER.** Medium Wave. Transistor Superhet. Ferrite aerial. 9 volt. £4  
**BARGAIN 4 CHANNEL TRANSISTOR MIXER** Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and turner with separate controls into single output. 9 volt. £3  
**BARGAIN FM TUNER 88-108 Mc/s** Six Transistor. 9 volt Printed Circuit. Calibrated slide dial tuning. Walnut Cabinet. Size 7 x 5 x 4 inch £10  
**BARGAIN FM TUNER** as above less cabinet £7.50  
**BARGAIN 3 WATT AMPLIFIER.** 4 Transistor Push-Pull Ready built, with volume control. 9v. £3.50

**COAXIAL PLUG 6p. PANEL SOCKETS 6p. LINE 18p. OUTLET BOXES, SURFACE OR FLUSH 25p. BALANCED TWIN FEEDERS** 5p. 80 ohms or 300 ohms. JACK SOCKETS Std. open-circuit 14p. closed circuit 23p; Chrome Lead Socket 45p. Phone Plugs 5p. Phone Socket 5p. JACK PLUGS Std. Chrome 15p; 3-5mm Chrome 14p. DIN SOCKETS Chassis 3-pin 10p; 5-pin 10p. DIN SOCKETS Lead 3-pin 18p; 5-pin 25p. DIN PLUGS 3-pin 18p; 5-pin 25p. VALVE HOLDERS, 5p; CERAMIC 5p; CANS 5p.

**E.M.I. TAPE MOTORS** 120v. or 240v. AC. 1,200 r.p.m. 4 pole 135mA. Spindle 0.187 x 0.75in. £1.25 Size 3 1/2 x 2 1/2 in. (illustrated). Post 15p  
**BALFOUR GRAM MOTORS** 120v. or 240v. A.C. 1,200 r.p.m. 4 pole 50mA. Spindle 1 x 3/20. Size 2 1/2 x 2 1/2 x 1 1/2 in. Post 15p 85p

www.americanradiohistory.com





Positions 4 and 5 of S1 give r.f. coverage as for positions 1 and 2, but S1b shorts the primary of T2, so that an audio tone is no longer present to modulate the output. C6 is an isolating capacitor for external circuits.


## THE R.F. COIL

This is wound on a ferrite rod about 5in. long and  $\frac{3}{8}$ in. in diameter, which gives a higher Q and requires fewer turns than an air-cored inductor. All windings are of 32 or 34s.w.g. enamelled wire and are wound on thin tubes made by winding paper round the rod. L1 and L2 can then be slid along to adjust band coverage if necessary.

## ★ components list

R1	470k $\Omega$ 1W, 10%
R2	200k $\Omega$ 1W, 10%
VR1	10k $\Omega$ pot. with switch
C1	0.01 $\mu$ F 250V disc ceramic
C2	10pF silver mica
C3	300pF silver mica
C4	22pF silver mica
C5	0.01 $\mu$ F 250V disc ceramic
C6	0.01 $\mu$ F 350V disc ceramic
C7	50 $\mu$ F 50V electrolytic
VC1	500pF Jackson variable
S1	2-pole, 8-way rotary switch
T1	240V, 12.6V, 0.5A or similar heater transformer
V1	ECC82

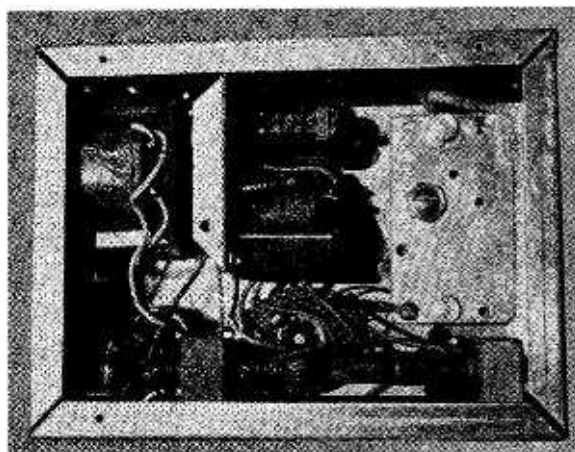B9A valve holder; Rectifier, GJM or similar (BY105 will do); T2, Radiospares intervalve, 3mA, 1:3 ratio; Ferrite rod, enamelled wire, tag strips, knobs, etc.; Case, Two 5 x 2in. and two 7 x 2in. universal chassis flanged members, two 5 x 7in. flat plates (Home Radio).



An internal view of the completed prototype; compare this with Fig. 2.

The ends of the windings can be secured with cotton or adhesive tape. After construction is finished, and coverage has been checked, windings and ends are secured using clear *Bostik*, as any movement here will upset dial calibration.

A space of about  $\frac{3}{4}$ in. is left to the end of the rod, and L1 is commenced at point 1. Seventy turns are wound on, side by side, and the wire is fixed at point 2. The beginning of L2 is about  $1\frac{3}{4}$ in. from the other end of the rod. L2 is wound in a compact pile about  $\frac{5}{8}$ in. long, and has 140 turns. End 3 of L2 will thus come about  $1\frac{1}{8}$ in. from this end of the rod. L3 has 25 turns side by side and is about  $\frac{1}{4}$ in. from L2.

The end of L1 and beginning of L2 are soldered together to form point 2. Windings must be in the same direction, as shown. Leads to L3 must not be reversed or feedback will be in the wrong phase.

## A.F. INDUCTOR

The transformer listed can easily carry the required primary current but other transformers could probably be used, though not transistor types. When the generator is first tested, set S1 at position 3, and listen for an audio output, either with phones or by taking a lead to an amplifier. If no tone is heard, reverse secondary connections to T2.

R2 raises the pitch of the tone produced and may be changed in value if necessary. Should an available transformer produce a tone of too high a pitch, this can be altered by connecting a capacitor of about 0.01 $\mu$ F (or as found necessary) across the primary or secondary.

## CONSTRUCTION POINTS

The complete generator occupies a case 7 x 5 x 2in. deep, made by assembling 7 x 2in. and 5 x 2in. "universal chassis" flanged members. The panel is a 7 x 5in. plate, and most of the construction is upon this, and on a 2 $\frac{1}{2}$  x 2in. chassis bolted to the panel. The chassis is most easily made by cutting a 2 $\frac{1}{2}$ in. length from a 2in. wide flanged universal chassis member.

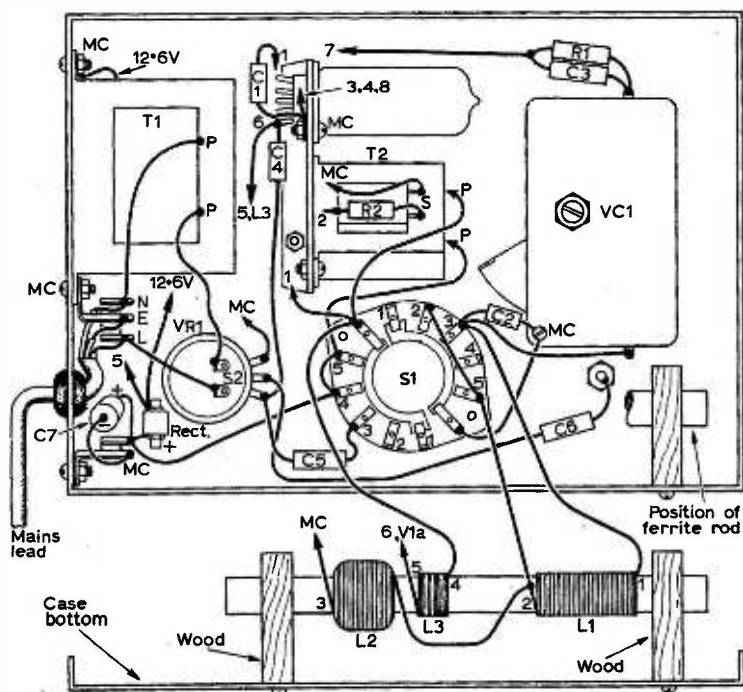


Fig. 2: Wiring details and the construction of the r.f. inductor.



Mount components on the panel in the positions shown in Fig. 2. Countersunk screws hold VC1 to the panel. Fit the valvholder and T2 to the small chassis, and bolt this to the panel, also with countersunk screws.

All wiring except for the r.f. inductor, mains transformer T1, rectifier, and C7 can now be done.

One 5×2in. flanged member is then drilled to take T1, and a grommet for the 3-core mains lead. The lead is anchored at a 3-tag strip. Equip the lead with a 13A type 3-pin plug having a 2A or 3A fuse. Use brown (or red) for L, which runs to S2, and blue (or black) for N, which is connected to the primary of T1. Yellow-green (or green) is for the earth or metal box connection.

The rectifier is supported on an insulated tag. When this part of the wiring is finished, assemble the top, bottom and sides of the case, securing them with bolts through the perforated flanges provided. The panel is then fitted in place and fixed with four bolts.

The leads from the tag-strip to S2, T1 to S2, and other circuit points can now be soldered on. All wiring is finished except for the r.f. inductor.

The ferrite rod is mounted by drilling two pieces of wood to take it and when in position it should be about  $\frac{5}{8}$ in. clear of the bottom of the case. Screws pass up through the bottom member into the wooden mounts. Insulated sleeving is fitted onto the wire ends of the windings, which are scraped and soldered to the various connecting points.

Coverage can be checked by taking a lead from the output socket and placing this near a receiver, or near a short wire connected to the receiver aerial terminal. Note that the two bands obtained should overlap, giving continuous coverage from about 1600kHz to 150kHz. This means that with S1 in position 2, and VC1 fully closed, the signal should be heard at the high frequency end of the long wave band of the receiver, or that with the generator switch in position 1, and VC1 fully open, the signal should be tuned in at the low frequency end of the receiver medium wave band. If necessary, slide L1 or L2 along the rod to achieve this, then cement the windings in place.

C2 in parallel with VC1 enables dial readings at the extreme minimum position of VC1 to be rather less crowded, so that frequencies around 1600-1400kHz can be more easily read.

All connections should be quite short and rigid. The flanged top and sides of the case allow a 5×7in. plate to be fixed on using self-tapping screws.

## SCALES

VC1 can have a fairly large knob with a pointer, or with a hair-line or cursor. Frequencies are read on two semi-circular scales drawn on thin card which can be cemented to the front of the case. The scales may be covered with transparent material for protection after calibration, or a piece of thin perspex, 7×5in., can be bolted on to cover the whole front.

## CALIBRATION

The simplest method of calibration is to plug a lead into the generator output socket and place this near a receiver, or its aerial or aerial lead. The receiver is then tuned to known frequencies, the generator is tuned to the same frequency and its scales are suitably marked. Alternatively, if a calibrated generator is available, tune both generators to the same frequency, by means of the receiver, and calibrate the scales.

A very good guide to markings can also be made by temporarily fitting a 0-100 scale, and preparing a graph with the aid of stations of known frequency. Round figures for the generator can then be read from the graph, and marked on the scales.

## HARMONICS

It is also possible to secure good calibration of the generator with an ordinary long and medium wave band receiver, using harmonics. This depends on the fact that if the generator is set to some particular frequency F, harmonics of this frequency will be heard on the receiver, at Fx2, Fx3, and other multiples. These grow weaker as the multiplier increases, the upper limit depending on receiver sensitivity. For this method, the following steps should be followed:—

1. Tune receiver (R) to 200kHz (BBC Radio 2).
2. Tune signal generator (SG) to this and mark scale 200kHz.
3. Leave SG untouched. Tune R to find Fx3, or 600kHz.
4. Leave R untouched. Tune SG to 600kHz and mark scale.
5. Tune SG to 300kHz and mark scale. (R is at Fx2.)
6. Leave SG tuning untouched. Tune R to 300kHz.
7. Tune SG to 150kHz and mark scale. (R is at Fx2.)
8. Tune R to 200kHz and SG to 200kHz.
9. Tune R to Fx3, or 600kHz.
10. Tune SG to 600kHz.
11. Leave SG untouched and tune R to Fx2, or 1200kHz.
12. Leave R untouched and tune SG to 1200kHz. Mark scale.
13. Leave R untouched and tune SG to 400kHz. Mark scale. (R is at Fx3.)
14. Tune SG to 200kHz and receiver to Fx5, or 1000kHz.
15. Leave R untouched. Tune SG to 500kHz. Mark scale. (R is at Fx2.)

By proceeding in this way, calibration points can be found through both bands, including frequencies outside the normal coverage of the usual 2-band receiver. For accuracy, obtain all reference points by tuning originally to zero beat with BBC Radio 2 on 200kHz, as at (8) not relying on *visual* readings of the 200kHz mark or other signal generator or receiver calibration markings. ■


### Back Numbers Important Announcement

We regret to inform readers that owing to the closure by the Company of the department concerned it will no longer be possible to supply back numbers of **Practical Wireless** and **Television**.

To ensure obtaining regular copies of these magazines readers are strongly urged to place a regular order with their local newsagent, or to take out an annual postal subscription.

Reference to past issues of the magazines may sometimes be obtained at certain public libraries who may hold bound volumes. A few libraries are said to offer a photostat service. Alternatively, we are always willing to insert a free request for specific back numbers in our "CQ" column which appears in most issues.

# electronics mastered!\*

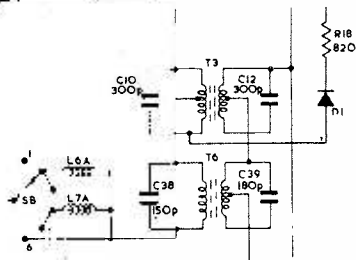

by our highly practical  
**BUILD, SEE & LEARN system**

Step by step we take you through the apparent intricacies of electronics and show you how easily you can master the subject. Write for the brochure which shows, in full detail, how you can do it.

**1**



We provide a full range of components and sub-assemblies, with details of what they do, so that you learn to recognise all the 'bits and pieces'. Using some of these you are instructed in how to build this oscilloscope, simply and quickly.

**2**

You are shown how to read and understand circuit diagrams so that you can later build more advanced equipment or draw your own diagrams.

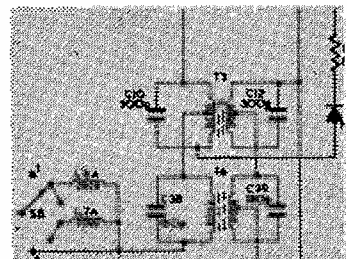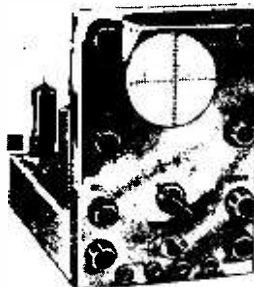**3**

- You can construct over 40 kits, including:—
- Valve experiments
  - Transistor experiments
  - Amplifiers
  - Oscillators
  - Signal tracer
  - Photo electric circuit
  - Computer circuit
  - Basic radio receiver
  - Electronic switch
  - Simple transmitter
  - a.c. experiments
  - d.c. experiments
  - Simple counter
  - Time delay circuit
  - Servicing procedures



This course has been designed to help even those who are complete newcomers to electronics. **No Maths needed!**

**POST NOW**  
**FOR**  
**FREE BROCHURE**  
BLOCK CAPITALS PLEASE

To: **British National Radio School, Reading, Berks.**  
Please send your free Brochure, without obligation, to:


NAME .....

ADDRESS .....

P11/71

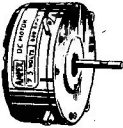**FREE**

**SPECIAL ELECTRONIC GIFT**  
to all our Students **POST COUPON NOW!**



**AMPEX 7.5v. D.C. MOTOR.** This is an ultra-precision tape motor designed for use in the AMPEX model AG20 portable recorder. Torque 450GM/CM. Stall load at 500ma. Draws 60 ma on run. 600rpm 5% speed adjustment. Internal AF/RF suppression 1/2 dia. 1" spindle, motor 3" dia. 1 1/2". Original cost £16.50. Our price £4.25. P. & P. 25p. Mu-metal enclosure available 75p each.

**SYNCHRONOUS MOTORS.** 220/380 v. 50/60 Hz. 250-300 rpm. 75p each.  
**MYCALEX MAINS.** Shaded pole, 1425 rpm, 3/4" spindle. 2 for £1.25. Carriage Paid.  
**MAINS INDUCTION MOTOR.** Open frame, 3/4" spindle, weight 1/2 lb. Powerful. 88p each. P. & P. 12p.

**GEARED MOTORS**  
 "Parvalux" Reversible 100 RPM Gearing Motor. Type S.D.14, 230/250v. A.C. 22lb./in. 3/4" spindle. 1st class condition. £7.50 each. P. & P. 50p. Also limited number only as above.  
**Brand New. £12.50 each. P. & P. 50p.**

**ELECTRO CONTROL (CHICAGO).** Shaded pole 240v. 50 Hz. 200 rpm. 10lb. in. £2.50. P. & P. 25p.  
**MYCALEX.** Open frame, shaded pole motors. 240v. 50 Hz. 7 rpm. 28 lb. in. 80 rpm. 12 lb. in. £2.25 each. P. & P. 25p.


**"CROUZET" TYPE 965.** 115/240v. 50 Hz. 47/68 watts. 50 rpm. Stoutly constructed. Size: 2 1/2" dia. x 3 1/2" long plus spindle 1" x 1/2" dia. Anti-clock. £2.75. P. & P. 25p.

**TYPE 955.** Same as above, but 3 rpm. £3.00. P. & P. 25p  
**UNISELECTORS.** 8 Bank 25-way. 24 volt Double sweep. Brand new in maker's boxes £5.25 P. & P. 25p.  
**PAINTON BOURNS TRIMPOTS.** 1k, 2k, 2.5k, 5k, 10k, 20k, 50k, 500k. Other Trimmer pots in stock. RIL 10k. MORGANITE 1k. MEC 200 Ω (tubular) 50Ω. Any 3 for £1.10 carr. paid.

**CURRENT FLOW INDICATOR.** Ideal for all types of battery operated equipment (portable machines, tape recorders etc.). Four white segments appear when current flows. Coil is 600Ω 6/12v. Drawing only 8 ma on function. Neat in appearance. Size: dia. 7/8" x 7/8" deep. Fixing centres 1 1/2". £1.25 each Carr. Paid



**PRECISION FAN CO. (SMITHS INDUSTRIES) DOUBLE ENTRY CENTRIFUGAL FAN/BLOWER.** This is a beautifully balanced particularly quiet running unit giving approx. 90 cubic ft./min. The motor is a 2 pole shaded pole Mycalex, drawing only 240ma on run. Weight 2 1/2 lbs. Sizes: case dia. 3-1 ins. width (case only) 3-125 ins. Width overall (inc. 5-25 ins. Aperture 3-125 ins. x 1-85 ins. Offered well below makers price at £2.95. P. & P. 25p.

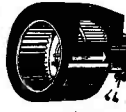

**Brand New "DISCUS" Centrifugal Blower by Watkins & Watson.** 240v. 50 Hz. Powered by A.E.I. continuous rating 2850 rpm motor. Cowl diameter 10". Outlet flange 2" I.D. Coupling flange supplied. These superb precision units are ideally suited for Organ construction. Offered at approx. half makers price £12.50. Carriage £1.50.


**L.T. TRANSFORMERS.** Prim. 0-110-240v. Sec. 4-5-0-4-5v. at 1 amp. Size 1 1/2 x 1 1/2 x 1 1/2". 60p. P. & P. 15p  
 Prim. 220/240 v. Sec. 0-5-10-15-20 v. at 2 amps. £1.25. P. & P. 15p.  
 Prim 200/240v Sec 0-1-5-5-8-60 at 3-5 amps plus 0-90 at 100 ma. wax impregnated with screw term blocks. Weight 10 lbs £3.60 plus 40p P. & P.

**"WODEN".** Prim. 10-0-200-220-240v. Sec. two separate windings 6v. @ 4a each. £2.50 plus 30p. P. & P.


**"WODEN" Prim.** 0-110-220-240v. Sec. 34-36-38v. @ 600va. £7.50 plus 50p. P. & P.

**VINKOR POT CORE ASS. TYPE LA. 2103 (Core L.A. 2100).** Normal price £1.48. Our price 75p each. Special quote for quantity.

**PROGRAMME TIMER BY HONEYWELL.** A bank of 15 micro-switches are each individually operated by 15 pairs of cams which in turn are individually adjustable to give switching periods of zero to 12 seconds with infinitely variable combinations. A mains synchronous motor drives the cam shaft at 1 rev. per 12 seconds (5 R.P.M.). Originally cost £15.00 plus. Many applications such as lighting effects etc. New in original makers cartons. First class value at £5.75 plus 25p. P. & P.

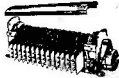

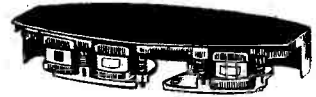Special offer of AMPEX professional tape heads. mu-metal shrouded. (Designed for model AG20). Full track record, or playback, £3.00. Erase head £2.00. Set of 3 with mounting bracket and cover £7.50. Half track record only. £3.00 each. Carriage paid.



**"BENSON BROS." 12v. D.C. HEAVY DUTY SOLENOID.** Size: 3" overall x 1 1/2" x 1". Very powerful, with secondary low current hold coil, Cont. rated £1.00 each. P. & P. 15p.

**"DECCO" MAINS SOLENOID.** Compact and very powerful. 16 lb. pull. 1/2" travel which can be increased to 1" by removing captive-end-plate. Overall size 2" x 2 1/2" x 2 1/2" high. £1.50. P. & P. 25p.

**"MAGNETIC DEVICES" Mains Solenoid—2" x 1 1/2" x 1 1/2" approx. 2lb. pull. Plunger Travel 1 1/2".** New in makers boxes; offered at half original cost. 75p. P. & P. 25p.

**"FIBRE GLASS" COPPER CLAD.** Top grade. One size only. 7 1/2" x 4 1/2" x 1/16". 3 panels £1.00. 12 panels £3.50. P. & P. 15p.

**"SRB" COPPER CLAD.** Sizes: 7 1/2" x 4 1/2" x 1/16", 16 for £1.00. 14 1/2" x 5 1/2" x 1/16", 8 for £1.00. 19 1/2" x 7 1/2" x 1/16", 4 for £1.00.

**"MALLORY" LONG LIFE BATTERIES.** Type A. RM12 cell 1-35v. 3,600 ma/H. CAP. 250/300 ma cont. current. Size: 2" x 2 1/2" x 5/8" or £2.00 per doz. Carr. Paid. Type B. Comprises 8 x RM 825 cells. Nom. volts. 1-35 each 10-5v. Overall, 350ma/H CAP. 20/25 ma cont. current. Size: 2 1/2" x 1 1/2" x 5/8", 3 for £1.00 or £3.00 per doz. Carr. Paid.

**A.C./D.C. MIRON AMMETERS.** 0-5 amps or 0-8 amps (suitable battery chargers etc.). Perspex front. Size: 1 1/2" x 1 1/2". Any 2 for £1.10. Carr. Paid.


**ERNEST TURNER 800µA METER.** 160Ω movement, 2" case elliptic, plastic front. Green-Red-Green uncalibrated scale £1.50 each. Carriage paid.



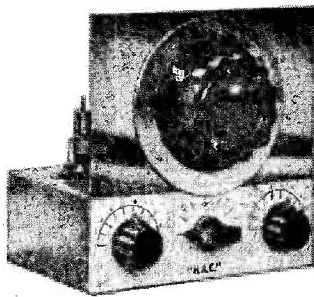**ELECTRO-TECH SALES**

**BUSINESS HOURS: 264 PENTONVILLE ROAD, LONDON, N.1** Tel. 01-837 7401/2  
 9.30-6 (1 p.m. Sat.) P.W.10 From early November our new address will be:—301 Edgware Road W.2

**H.A.C. SHORT-WAVE KITS**  
**WORLD-WIDE RECEPTION**




Famous for over 35 years for Short-Wave Equipment of quality, "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hains, etc.

**NEW "DX" RECEIVER**  
 Improved one-valve model "DX" mark 2. Complete kit—price £3.30 (post & packing 20p.). Customer writes: "Australia, India and America at loud volume. ... I am 14 years of age and have logged over 130 stations, plus countless Amateurs from all over the world."  
 Send S.A.E. for test report.

This kit contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other S.W. kits, including the famous model "X" and "K" plus (illustrated above). All orders despatched by return. (Mail order only.) Send now for free descriptive catalogue & order form.

**"H.A.C." SHORT-WAVE PRODUCTS**  
 29 Old Bond Street, London W.1

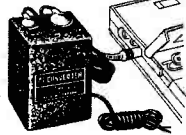**MAINS UNITS for all types of TRANSISTOR EQUIPMENT**



**RUN YOUR TAPE RECORDER OFF A.C. MAINS**  
 Mains unit supplied complete and ready to plug into your cassette recorder. (State voltage, model and plug required.)  
**£2.50 P. & P. 15p**

**12 VOLT CAR BATTERY UNIT**  
 Enables you to run your cassette recorder off 12V. car battery. (State 6v or 7 1/2v output, model and plug required.)  
**£2.00 P. & P. 15p**

**PLUS-3 MAINS UNIT**  
 Provides three separate switched output voltages 6v, 7 1/2v and 9v. D. attractive case with indicator light, mains lead output socket, plug and lead. Size 4 1/2 x 3 1/2 x 2 1/2 in.  
**£3.00 P. & P. 15p.**



Extra lead with plug to fit your cassette recorder 50p. (State model and plug required.)

**MAINS UNIT FOR ALL TRANSISTOR RADIOS, ETC., USING PP3 TYPE BATTERY. (ALSO AVAILABLE FOR 6V.)**  
**£1.15 P. & P. 10p.**



**MAIN UNITS**  
 For single outputs, 6v, 9v, 12v, 18v, £2.00. For two separate outputs, 4 1/2v + 4 1/2v, 6v + 6v, 9v + 9v, £2.50. P. & P. 15p. per unit. (Please state outputs reqd.)

All units are completely isolated from mains by double wound transformer ensuring 100% safety.

**R.C.S. PRODUCTS (RADIO) LTD.**  
 (Dept. P.W.), 31 Oliver Road, London, E.17

**LOOK AT THESE PRICES**

**CARTRIDGES**  
 Acos GP67-2, GP91-35C £1.12 1/2; Acos GP93-1 £1.83 1/2; Acos GP94-1 £1.62 1/2; Sonotone STAHC £1.97 1/2. All above in makers' cartons. BSR X4H £1.50.

**THIS MONTH'S SPECIAL OFFER**  
 Garrard SP25 Mk. III with KS40A cartridge. In good quality teak plinth with perspex dust cover. Complete with all leads ready to use £20. SP25 Mk. III deck only less cartridge £12.87.

**PLUGS & SOCKETS**  
 Phone plugs, assorted colours 4p; 45p per doz.; Coaxial plugs, aluminium 7p; Coaxial couplers 7p; 2 pin DIN plugs 15p; 3 pin DIN plugs 15p; 5 pin DIN plugs 17p; 2 pin, 3 pin & 5 pin DIN sockets 7p; Wander plugs 2p; sockets 3p; Banana plugs 5p; Sockets 5p; 3-5mm J/Plugs 7p and 12p; Standard J/Plugs with solder terminals 10p; Chrome 15p; Side Entry J/Plugs black and chrome 24p; Insulated J/sockets—o/cet 20p, c/cet 17p.

**ELECTROLYTIC CAPACITORS**  
 4uF 150v 4p; 8uF 500v 15p; 10uF 150v 4p; 12uF 25v 4p; 16uF 450v 14p; 16uF + 16uF 450v £24p; 30uF 10v 4p; 50uF 10v 4p; 100uF 9v 4p; 100uF 12v 4p; 150uF 15v 4p; 1500uF 30v 15p; 10uF 16v 7p; 5000uF 25v 50p; 10,000uF 25v 75p; 20,000uF 30v £1.05.

**MICROPHONES**  
 Acos Mic 45 £1.12 1/2; Acos Mic 60 99p; Planet CM70 £1.50; Hand Mike 75p.

**VALVES**  
 PY81 36p; PCL82 89p; EF.183 45p; EF184 45p  
 Postage extra.

**GEORGE FRANCIS (Dept PW),**  
 12-14, MIDDLE GATE, NEWARK, NOTTS  
 Telephone: Newark 4783.

# SHORT WAVES

## MONTHLY NEWS FOR DX LISTENERS

**T**HE first reporter this month is **Terry Gibbs** of Swindon who uses a Murphy 'Overlander' receiver and a long-wire which he has recently extended to 500 feet. This equipment enabled him to hear:—

- 3905 *New Hebrides B.C.* in broken English at 0700.
- 4895 *Mauritius B.C.* in English at 1800.
- 4895 *R. Malaysia* in vernacular at 1240.
- 4926 *R. Bata, Guinea* (Equat.) at 2300.
- 4975 *R. Timbira, Brazil* in English at 2330.
- 6055 *R. Continental, Peru* at 0600.
- 9610 *VLX9, R. Perth, Australia* at 1200.
- 11835 *4VEH, R. Haiti* in English at 2345.

**Philip Nichols** of Longlevens, Gloucester has an Eddystone 830 receiver and a 50 foot long-wire at 19 feet helping him to hear:—

- 6010 *RT Belge*, in French at 1506.
- 9630 *R. Sweden* with sign-on at 1100.
- 9555 *CBC, Canada* in French at 1830.
- 9582 *R. Australia* in English at 1832.
- 10530 *Alma Ata* in German at 1740.
- 11620 *AIR, Delhi* in English at 1820.
- 15200 *Nigeria* noted at 1835.
- 15265 *R. Afghanistan* in English at 1815.
- 15345 *R. Kuwait* in English at 1730.
- 21460 *HCJB, Quito, Ecuador* in English at 1900.
- 21495 *R. Portugal* in English at 0840.
- 21690 *WIBS, Windward Is.* at 2124.

A new reporter this time is **Ian Alexander Kelly** of Bulawayo, Rhodesia. Ian's equipment is best described in his own words: "My equipment comprises of two radio receivers, a 5-band a.m./f.m. supersonic PR127 (11 transistor) and a 6-transistor, 3-band home-made regeneration receiver. There are four different types of antenna systems which I use, there is a 100 foot inverted 'L' aerial; a 200 foot centre-top aerial; a 9 foot telescopic aerial and the internal telescopic aerial on the 5-band set." That impressive line-up enabled him to hear:—

- 2306 *RSA, South Africa* at 2045.
- 3250 *Lourenco Marques, Mozambique* at 2100.
- 3295 *R. Lusaka, Zambia* with news at 2105.
- 9410 *BBC World Service* to Europe at 2056.
- 9505 *R. Belgrade, Yugoslavia* at 2010.
- 11815 *NHK, Japan* in English at 1600.
- 11935 *R. Portugal* in Portuguese at 1830.
- 11980 *R. Prague, Czechoslovakia* at 1815.
- 15350 *ORTF relay from Brazzaville (Congo)*, 2028.
- 15400 *Ulan Bator, Mongolia* at 2345.
- 15600 *Manila, Philippines* at 1335.
- 21501 *R. Accra, Ghana* at 1500.
- 21520 *SBC, Berne, Switzerland* at 1900.

Another new reporter is **Ronald L. J. Winson** of Reading whose equipment consists of a Codar CR70A and an 80 foot long-wire antenna.

- 6020 *R. Nederland* in Spanish at 2130.
- 11970 *R. Bucharest, News* in Spanish at 2130.

## THE BROADCAST BANDS

Malcolm Connah

Frequencies in kHz ● Times in GMT

- 15295 *Sweden Calling DXers* at 0000.
- 15325 *CBC, Canada* in English at 2115.
- 21700 *Vatican Radio with News* at 1245.

**Ross Pullen** of Crawley has added an 18 foot vertical aerial and had his Murphy A72 re-aligned giving the following results:—

- 9510 *RTA, Algeria* in French at 1215.
- 9575 *Gronlands Radio (Greenland)* in Danish at 2207.
- 11735 *R.T.V. Morocco* in English at 1720.
- 15018 *Hanoi Radio* in English at 2000.
- 15115 *KBS, Seoul* in English at 0630.
- 15115 *R. diff. de Sao Paulo, Brazil* at 2335.
- 15170 *ELWA, Liberia* in French at 2040.
- 15200 *Nigeria* in English at 0735.

**Neil Smith** of Sutton Coldfield used his Unica UNR-30 receiver and a 170 foot long-wire to hear the following stations:—

- 7100 *RSA, South Africa* in English at 1900.
- 7108 *R. Budapest* in English at 1900.
- 9620 *R. Belgrade, Yugoslavia* in English at 2312.
- 9615 *Vatican Radio* in English at 2154.
- 9770 *Austrian Radio* in English at 1130.

**Tony Alcock** of Bath has a Codar CR70A receiver and a Joystick antenna which helped him to hear:—

- 9620 *Radio Belgrade, Yugoslavia* at 2200.
- 9805 *R. Cairo, U.A.R.* noted at 2235.
- 9833 *R. Budapest, Hungary*.
- 11060 *Radio Vilnius, Lithuanian SSR.* at 2240.
- 11740 *Vatican Radio* noted at 2045.
- 11765 *Radio Australia* noted at 0845.
- 15345 *Kuwait B.S.* at 1723.
- 17810 *R. Nederland, Bonaire* relay at 2230.
- 17825 *Radio Sofia, Bulgaria* at 1920.

## News

**Peter Reed** of Brighton has a R1155N receiver and a Joystick antenna. Peter used his equipment to send in several items of news including:—

**Finland:** Radio Finland can be heard from 2000 to 2100 on the following frequencies: 9530, 11755 and 15185.

**Ceylon:** The Ceylon Broadcasting Corporation transmits to Asia at 0212 on 15120 but the broadcast can be heard in this country.

**Tahiti:** Faint signals have been picked up from Radio Tahiti on 11825 at 1630.

**Turkey:** Radio Ankara has been heard broadcasting at 2300 on a frequency of 15160.

---

Reports should arrive by the 15th of the month and be addressed to the author at 5 Ranelagh Gardens, Cranbrook, Ilford, Essex.

---

## THE AMATEUR BANDS

David Gibson, G3JDG

Frequencies in kHz • Times in GMT

**I**T'S happened! A log has been received for 70cm. Honours for being first go to **Nick Richardson** (Wendover, Bucks) who has a 46-element multi-beam at 33ft. Receiving line-up is a BF180 preamp, AF239 converter, i.f. amp. and a Trio 9R59DE tuning 28-30MHz. The log shows the great majority of stations using a.m. on 70cm. Callsigns logged include: G2RD, G2FNW, G3BNL/P, G3COJ, G3DAH, G3EHM, G3HAZ, G3HXS, G3KEQ, G3KMS, G3LQR, G3LTN, G3ZYC, G5QA, G5UM, G6GN, G8ACN, G8AMG, G8ANZ, G8ARC, G8ATS, G8AZU/P, G8BBB, G8BGC, G8BII, G8BQH, G8BSH, G8CIT, G8DDC/P, G8DXJ/P, G8EFX/P, G8ERW, G8APZ/P (Merionethshire), GW8AWS/P (Flintshire).

Down on 144MHz, Nick uses an 8-element Yagi at 28ft. feeding an f.e.t. preamp, Garex converter, i.f. amp into the 9R59DE. Goodies on 2 metres were: DL1XJ, ON5NY, GW3GIZ, PA0BDH, PA0CBN, PA0DTC, PA0RLS, PA0TLX, PA0UVP all s.s.b. On a.m., 144MHz sigs. were received from: DL0DD, DK1OV, F1AOY, F1BCI, F3LP, ON5UI, PA0DMS.

"I am 12 years old," claims **Paul Dumbleton** of Dunstable. Paul uses a Corsor domestic receiver and a television aerial "mounted on the chimney." The log shows plenty of EU activity on 14MHz such as DJ, DK, DL, DM, EI, F, HA, HB9, II, LA, OH, OK, ON, OZ, SM, UA and YU. From further afield: DU4CC, ET9SPI, KANKI, K6YRD, VU1HH, VK3AP, WA6EGL, 4U1ITU, 9HIBG, 9K2AM, which is pretty good going no matter how old you are.

**Stephen Hopkins** (Gloucester), admits that "... this is the first report I have sent." Receiver is a H.A.C. DX Mk2 with a "slight modification." Antenna is 40ft. end-fed and raised EI9Q on 3.5MHz, F6ARC on 7MHz and HB9XUM/M, K1NJE, ON8WF/A, and W2BLQ on 14MHz s.s.b.

**Stephen Terry** writes from Banbury to take me to task for my remarks about the i.f. bands and DX. He includes the following callsigns as evidence of 80 metre activity: FP8CT, JY1/B, LU7AAC, OY7JD, PJ2CW, PY3APH, PY7AF, VE1AM, VE1ZZ, VE2XD, VE3FXT, VO1FG, ZS1MH.

Even dreaded 7MHz was persuaded to reveal signals from: CX7AP, HK3LT, PZ1AX, TF5TP, UW9AF, VP2AA, YV1BI, YV5CYA. All are s.s.b. and received on a Lasky's Skyrover MkII with a 120ft. end-fed.

**Alan Newman**, G8CXC (Portsmouth) used an HW17 transceiver on 144MHz to work PA0—RKS, PVC, CSL, ON5RE. Antenna is a 14-element Parabeam at 21ft. although Alan says he is at zero feet a.s.l. On 80 metres s.s.b. using 9R59DS, Alan logged CT2AK, FP8CT, FP0CA, KP4AN, KV4FZ, LU7AAC, PJ2CW, PZ1AX, PY1HA, PY3CIQ, PY7AF, PY0PK, TF3EB, WA6EGL/P/TF, VE1AAN, VO1AR, WA1KK, WA3WFJ, ZB2CC, ZP3AQ. Having received these (plus a long list of others) in some 3 hours of listening time, Alan is sold on 80 as a DX band and

is now polishing up his c.w.

Another first-timer with a log for this column is **David Bettington** (Upton) who has a CR150 which, he claims, "... is older than I am." A 20 metre dipole just fits into the loft-shack and gave s.s.b. messages from: JH1OMS, KP4DEY, OX3OJ, VP2MF, WA2OYP/MM, 4X4OH.

**Richard Mortimore** (Cardiff) can now receive c.w. at 20w.p.m. His log for 21MHz (c.w., of course) reads: CO2FC, EL2CB, JA4ONC, JA5FU/MM, JH1WKS, JH1YCW, K9YXA, LU9FAN, PY1KEK, WB6VVZ/MM, YV4AQ, 3A0ML, 4Z4KKI. Receiver is a 9R59DS and antenna is a 60ft. long wire.

**Tom Brosnan** (tnx QSL OM) uses a Windom antenna on 20 metres to feed his JR3LO receiver. Signals received (s.s.b.) include: AP5HP, EQ2BQ, ET3USA, JA1HBC, JA1JTH, JA6YG, KR6JX, TI2JU, VU2NH, ZE1DP, 9M8DEA. Fifteen metres s.s.b. revealed: CR6IY, JA6BSM, VQ9R, WB4BFZ, ZS5OV, 5Z4MW, 3V8ZK. QTH is Tadworth in Surrey.

The Modular Three featured in P.W. is the receiver used by **M. Evans** (Good Evans!) The antenna system consists of unspecified lengths of wire "tangled round the garden and fed to an a.t.u. with a coil former made from a drain pipe." Eighty metre sigs received from: CR7IC, CT1IPS, CT2HK, EA4LH, EL9LS, F0HH/M, JY1, OY2R, OY7JD, PY7AF, VE1IE, VP5KG, VP9GQ, WA6EGL/TF, ZB2CC, ZL3LE, ZL4JFA, ZS1MH, ZS5LB, 3V8ZK, 5Z4KL, 9K2AL.

Good samaritan of the month is G3ZRD who resurrected an ailing B40 belonging to a sad **Crispin Henderson**. Just to show how well things are going now, Crispin sends in a multiband, multimode log. On 160 c.w.: EI8H, EI9J. Signals on 80 s.s.b.: CT1MK, K4QM, VE1IE, W3EFX, W5SZ, W8KEX. Best on 40 c.w. were VK3CC and YV5DRN. Twenty c.w. raised: EA8FE, GM3UYF, HC8GG, HP7KAL, OX3HU, PY7GV, SM0FY, W7HBQ, ZC4CB, ZL2IR, 7Q7AA, 9H1BB. While s.s.b. on the same band was received from: CE3OE, HK1BQR/P7, KZ5OD, OY9LV, VK7MB, 4X4KM, 9K2AM, 9Y4VV. Fifteen c.w.: CR7FM, PY2YCC, Y06KBM, and s.s.b.—KP4AOW, LU5MAO, LU8LH, PY5DI, YV6JB, 4X4GB, 5Z4GK.

Many happenings in October for the keen contest enthusiast. October 9-10, 21-28MHz telephony contest; 9-10, VK/ZL Oceana c.w. contest; 13 (and 27), 70MHz contest; 23-24, 7MHz c.w. contest—well worth a listen; 30-31, 432MHz contest; 30-31, CQ WW phone contest; November 6-7, 144/432MHz c.w. contest; 6-7, 7MHz phone contest; 6-8, CHC/FHC—both phone and c.w.; 7, OK contest.

*Logs, in alphabetical order please, to arrive by the 15th of the month to:*

**12, Cross Way, Harpenden, Herts.**



# BUDGET HIGH-FIDELITY STEREO SYSTEMS



**ONLY £57.75**  
carr. £1.75

**ONLY £40.95**  
carr. £1.75

**PREMIER STEREO SYSTEM "ONE"** Consists of an all transistor stereo amplifier, Garrard 2025 T/C auto manual record player unit fitted stereo mono ceramic cartridge with diamond stylus and mounted in teak finish plinth with perspex cover and two matching teak finish loudspeaker systems. Absolutely complete and supplied ready to plug in and play. 2500 amplifier has an output of 5 watts per channel with inputs for pick-up, tape and tuner also tape output socket. Controls: Bass, Treble, Volume, Balance, Selector, Power on/off. Solid teak cabinet with aluminium front panel. Size 12 1/2" x 4 1/2" x 3 1/4" high (Amplifier available separately if required £14.95 Carr. 40p).

**PREMIER STEREO SYSTEM "THREE"** This consists of KLINGER KC903 stereo amplifier giving 6 watts rms per channel with Bass, Treble, Volume and Balance Controls. Inputs for Magnetic and ceramic pickup, tuner, tape in and out. Stereo cartridge, Garrard SP25 Mk III in teak finish plinth with cover and fitted Sonotone 9TAHCD diamond stereo cartridge. A pair of HMF Speakers size 16 1/2" x 10 1/2" x 9" fitted EMI units complete the matching system. **ONLY £57.75 Carr. £1.75**

ALL SYSTEMS SUPPLIED WITH FREE LEADS AND PLUGS

## PREMIER HI-FI OFFERS

- Amstrad 8000 Stereo Amplifier (List £25.95) **£16.75**
- Philips 580 Stereo Amplifier (List £29.00) **£21.00**
- Rogers Ravensbrook II Stereo Amplifier in teak case (List £52.50) **£39.50**
- Rogers Ravensbourne Stereo Amplifier in teak case (List £64) **£49.00**

**NOW AVAILABLE AGAIN !!**  
MODEL SAQ203 Stereo Amplifier  
—Return of this popular model  
1000's have been sold.  
**NOW AT NEW LOW PRICE** **£19.50**

- Metrosound ST20 Stereo Amplifier in teak case (List £16) **£24.50**
- Goldring GL75 less cartridge (List £41.61) **£29.00**
- Garrard SP25 III less cartridge **£11.90**
- Garrard SP25 III with Goldring G800 cartridge (List £28.35) **£18.40**
- Garrard AP76 less cartridge **£19.50**

Garrard 3500 with Sonotone 9TAHCD stereo cartridge (List £15.50) **£9.97**

- Garrard 2025 T/C with Sonotone 9TAHC Diamond Cartridge **£8.97**
- Garrard 2025 T/C with Sonotone 9TAHC Diamond Cartridge ready wired in teak plinth with cover **£14.00**

Carriage and Insurance 50p extra any item.

## SP25 MKIII SPECIAL!



GARRARD SP25 MK III SINGLE RECORD PLAYER. FITTED GOLDRING 850 or AT66 MAGNETIC STEREO CARTRIDGE as available. COMPLETE IN TEAK PLINTH WITH RIGID PERSPEX COVER.  
Total list price over £29.  
**PREMIER PRICE £19.90**  
P. & P. 50p.



**HI-FI STEREO HEADPHONES**  
Designed to the highest possible standard. Fitted 2 1/2" speaker units with soft padded ear muffs. Adjustable headband. 8 ohms impedance. Complete with 6ft lead and stereo jack plug.  
**£2.47 P. & P. 25p.**

STEREO STETHOSCOPE SET Low imp. **£1.25**  
MONO STETHOSCOPE SET Low imp. **52p.** P. & P. 10p.



**E.M.I. 13x8in. HI-FI SPEAKERS**  
Fitted two 2 1/2" tweeters and crossover network. Impedance 8 or 15 ohm. Handling capacity 10W. Brand new.  
**£3.47 P. & P. 40p**



**WELLER "EXPERT" SOLDER GUN.** Saves time and simplifies soldering in the home and service dept. Two position trigger gives instant dual heat. 100/140 watt. 240 volt A.C. **£3.97** P & P 30p

Marksmen Soldering Iron. Lightweight 1/4" pencil bit. Ideal for regular bench use and around the home. 25 watts. 240 volt A.C. **£1.50 P & P 15p**

**VERITAS V-149 MIXER**  
Battery operated 4-channel audio mixer providing four separate inputs. Size 6 x 3 x 2 1/2 in. suitable for crystal microphone low impedance microphone, with transformer, radio, tape, etc. Max. input 1.5v. Max. output 2.5v. Gain 6 dB. Standard jack plug socket inputs, phono plugs output. Attractive teak wood grain finish case.  
**MONO MODEL £3** **STEREO MODEL £3.47** P. & P. 12p

**TAPE CASSETTES**  
C60 (60 min.) 37p 3 for £1.05  
C90 (90 min.) 62p 3 for £1.80  
C120 (120 min.) 87p 3 for £2.55  
P. & P. 5p.

**FREE CASSETTE HEAD CLEANER** with every 10 cassettes purchased.  
All cassettes can be supplied with library cases at 3p. extra each

## "VERITONE" RECORDING TAPE

SPECIALLY MANUFACTURED IN U.S.A. FROM EXTRA STRONG PRE-STRETCHED MATERIAL. THE QUALITY IS UNEQUALLED. TENSILISED to ensure the most permanent base. Highly resistant to breakage, moisture, heat, cold or humidity. High polished splice free finish. Smooth output throughout the entire audio range. Double wrapped—actively boxed.

LP3	3"	250'	P.V.C.	25p	DT6	5 1/2"	1800'	POLYESTER	21.25
TT3	3"	450'	POLYESTER	37p	TT6	5 1/2"	2400'	POLYESTER	21.97
DT3	3 1/2"	600'	POLYESTER	57p	SP7	7"	1200'	P.V.C.	62p
SP5	5"	600'	P.V.C.	42p	LP7	7"	1800'	ACETATE	75p
LP5	5"	900'	P.V.C.	50p	DT7	7"	2400'	POLYESTER	21.25
DT5	5"	1800'	POLYESTER	75p	TT7	7"	3600'	POLYESTER	22.50

TAPE SPOOLS 3" 5p, 5", 5 1/2", 5 1/4", 7" 9p,  
Post and Packing 3" 5p, 5", 5 1/2", 5 1/4", 7" 10p. (3 reels and over Post Free).



# PREMIER RADIO

10 & 23, TOTTENHAM COURT ROAD, LONDON, W.1 TEL: 01-636 3451/2639  
HEAD OFFICE & MAIL ORDER DEPT. 23, TOTTENHAM CT. RD. TEL: 01-636 3451



# DISCOUNTS UP TO

# 60% ON BRANDED GOODS

ALL BRAND NEW in manufacturer's sealed cartons GUARANTEED 12 MONTHS.

SONY · LEAK · SINCLAIR · TELETON · ARMSTRONG · THORENS · PHILIPS · K.E.F. · TEAC · ROGERS · PIONEER

## SPECIAL OFFER £19.50

Garrard SP25 Mk III Goldring G800H Teak plinth and tinted cover Ready wired for immediate use. Please add £1.15 for post & packing

### TURNTABLES

Please add 75p for P. & P.

*Garrard SP25 Mk III	£10.45
*Garrard 2025TC with stereo cart	£8.00
*Garrard 2025TC with Sonotone 9TAHC	£8.95
*Garrard 3000 with Sonotone 9TAHC	£10.25
*Garrard SL65B	£13.25
*Garrard AP76	£19.95
*Garrard SL72	£24.00
*Garrard SL75B	£26.00
*Garrard SL95B	£35.50
Garrard 401	£27.00
*B.S.R. MP60	£10.75
Pioneer PL2AC	£36.00
Thorens TD 125	£52.50
Thorens TD 125AB	£89.50
Thorens 150 AB11	£42.50
Goldring GL69/2	£21.00
Goldring GL69 P2	£29.50
Goldring GL75	£29.00
Goldring GL75P	£36.50
Goldring AP76	£24.95

\*Items marked can be mounted in plinth and cover, ready wired for £4.50 extra plus 25p for post and packing.

### AMPLIFIERS

Please add 50p for P. & P.

Armstrong 521 (cased)	£41.95
Amstrad 8000	£17.70
Dulci 207	£15.95
Dulci 207m	£21.00
Europhon 10 + 10	£14.50
H. L. Audio 707	£17.75
Metrosound ST20	£26.95
Metrosound ST20E	£26.95
Philips R580	£20.50
Pioneer SA500	£41.50
Pioneer SA700	£67.00
Pioneer SA900	£94.50
Rogers Ravensbrook Chassis	£35.00
Rogers Ravensbrook Cased	£40.25
Rogers Ravensbourne Chassis	£31.50
Rogers Ravensbourne Cased	£48.00
Sansui AU101	£34.00
Sansui RA500	£38.00
Sansui AU222	£45.50
Sansui AU666	£75.00
Sinclair 2000 Mk. I	£21.00

Sinclair 2000 Mk. II	£22.50
Sinclair 3000	£32.50
Sinclair PRO 60/2 + Z30/PZ5	£15.75
Sinclair PRO 60/2 + Z30/PZ6	£17.75
Sinclair PRO 60/2 + Z50/PZ9 Trans.	£22.95
Sinclair AFU	£4.70
Teleton SAQ206B (New product)	£19.95
Wharfedale	£49.75

### CARTRIDGES

Please add 10p for P. & P.

Goldring G850	£3.75
Goldring G800H	£4.95
Goldring G800	£6.75
Goldring G800E	£10.50
Goldring G800SE	£15.25
Sonotone 9TAHC Diamond	£1.75
Shure M3DM	£4.75
Shure M44/5/7/C	£7.00
Shure M55E	£8.75
Shure M75E	£13.50
Shure V15 Type 2	£28.00
Shure M44E	£8.00
Shure M31E	£8.50
Shure M32E	£8.00
Audio-Technica AT66	£4.95
Audio-Technica AT35	£14.25
SMC 101	£2.79
MC 15	£4.50

### KIT RADIOS

Smallest Radio in the world. 5 years guarantee.

Sinclair Micromatic Radio	£2.75
Ready assembled	£3.25
Batteries 24p extra	

### PLINTHS & COVERS



£3.20 (as illustrated) plus 35p post & packing. Finished in real teak veneer with tinted dustcover. Ready to use (fully assembled). Suitable for Garrard SP25; 2025TC; 3000; AT60; 2000; 2500; 3500; 5100; 1025; SL65B. Also for B.S.R. McDONALD MP60 and others. Plinths and covers for AP76; AP75; SL72B; SL75; SL95B. £4.20 plus 35p post and packing. Also finished in walnut to match Japanese equipment—no extra charge.

# GLOBAL AUDIO DISCOUNT WAREHOUSES

Dept. P.W.3174 Pentonville Road, London, N1. Telephone 01-278 1769

Or: 4 High View Parade, Redbridge Lane East, Woodford Avenue, Ilford, Essex. Tel: 01-550 1086.

Open Monday to Saturday 9.30 a.m. to 6 p.m. LATE NIGHT FRIDAY 7 p.m.

MAIL ORDERS: Order with confidence. Send Postal Order, Cheque, Money Order, Bank Draft, Giro or Cash by Registered Mail. CALLERS: Please note that cheques can only be accepted together with cheque cards (not Barclay Card).

2 minutes from KING'S CROSS EUSTON & ST. PANCRAS on main road leading to the East and West Country

## M. & B. COMPONENTS (LEEDS) LTD.

(INCORPORATING M. & B. RADIO)

PO Box 125, 38 BRIDGE END, LEEDS 1 Telephone 0532-35649

EX-ARMY 88 WALKIE TALKIES. 3 channel. Less handset. Untested but complete and in clean condition. With circuit. £4.75, two for £8.00

9 TRANSISTOR 455Kc/s IF STRIPS. Ideal basis for receiver. £1.20  
6 to 12 VOLTS DC TRANSISTOR CONVERTER. 6v DC input 12v DC output at 4 amps conservatively rated. Ideal for VV owners. Brand New. £5.40

AD 108D MARCONI COMMUNICATION RECEIVER. 9 miniature valves plus Xtal filter and tunable BFO covering 260 to 510 Kc/s and 2 to 18.5 Mc/s in 4 switched bands. Slow motion deal with logging scale. Originally intended for 24v DC operation but supplied with details for conversion to mains. In very clean tested condition. £15.50

12v INVERTER TRANSFORMERS. Complete with circuit to build inverter to give 350v output at 300 m/a. £2.20

GEIGER COUNTERS. Well-known contamination meter comprising main unit fitted with meter marked in Milli Rontgens hour, probe lead and carrying case. Audio output available from socket on front panel. Supplied new or as-new condition. Model I fitted with vibrator PSU using 5 pen cell batteries. £4.85

MB2/20A TWO METRE TRANSCIEVER. Rx tunable over 2 metre band. 20 watts RF output AM modulated. Ideal for mobile or fixed station. Only requires connection to speaker, aerial and 12v DC supply to become fully operational. Full details on our lists. £50.00

All prices include carriage, packing, etc. U.K.

Send SAE for full lists with many bargains of general interest.

## YOUR CAREER in RADIO & ELECTRONICS ?

Big opportunities and big money await the qualified man in every field of Electronics today—both in the U.K. and throughout the world. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY & GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam.; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam. successes. We are the only privately run British home study College specialising in electronics subjects only. Fulllest details will be gladly sent without any obligation.

To: British National Radio School, Reading, Berks.

Please send FREE BROCHURE to

NAME ..... Block

ADDRESS ..... Caps.

..... Please

11.71

## BRITISH NATIONAL RADIO SCHOOL

# TAKE 20

JULIAN ANDERSON

A series of simple transistor projects, each using less than twenty components and costing less than one pound to build.

THE term "general purpose" amplifier is rather a sweeping one; a design suitable for one function may be poor for another. However, the characteristics of the one described here will allow it to fulfil a variety of needs.

The output is in the order of 750mW, peanuts perhaps when compared with the modern day "block-busters" but still quite sufficient for most purposes. For those who find it hard to relate output in watts to actual loudness, 750mW is the sort of level produced by a large portable transistor radio at full volume, which, of course, is adequate for most purposes. The input impedance of the amplifier is high which gives it far more versatility than low impedance types. It is perfectly O.K. to feed a low impedance source into a high impedance amplifier, though not the other way around. The cheaper sorts of transducers are usually high impedance, such as crystal pickups and microphones.

I hope that no one thinks that I am cheating, for our £1 limit does not include the battery, loudspeaker or the on-off switch; the latter should preferably be incorporated with the volume control.

## THE CIRCUIT

The first stage of the amplifier, represented by Tr1, is an emitter follower. This configuration has a very high input impedance, here it is likely to be at least 1MΩ though the actual figure depends on the gain of the transistor used. The volume control, a 5kΩ potentiometer, is directly in the emitter of the first transistor. If you do not require the high impedance input, this complete stage, together with C1 and R2, can be omitted, coupling the input directly across the volume control, however, although no gain will be sacrificed, it means that the input impedance will only be 5kΩ and this makes it rather less versatile.

The output from the volume control feeds into a fairly conventional driver/complimentary pair audio output stage. Tr2 operates as a conventional amplifier with a collector potential equal to half the supply potential. When the signal swings negative with respect to this potential, Tr3 conducts and Tr4 is held off; when the signal swings positive, Tr3 conducts and Tr4 is held off.

The output appears at the emitters of the two transistors and is coupled via C3 to the loudspeaker.

—continued overleaf

## No. 31

### GENERAL PURPOSE AUDIO AMPLIFIER

#### ★ components list

Tr1 2N2926 (any colour)	11p
Tr2 2N2926 (any colour)	11p
Tr3 AC176	16p
Tr4 AC128	20p
R1 1MΩ ±W, 5% type	1p
R2 22kΩ	1p
R3 220kΩ	1p
R4 47kΩ	1p
R5 47Ω	1p
R6 470Ω	1p
C1 5μF 12V	4p
C2 5μF 12V	4p
C3 100μF 12V	4p
C4 100μF 12V	4p
C5 0.1μF	4p
VR1 5kΩ log. pot.	12p
	96p

Prices are those recently advertised in Practical Wireless and may have changed. No allowance is made for minimum order costs or for post and packing; these should be checked before ordering.

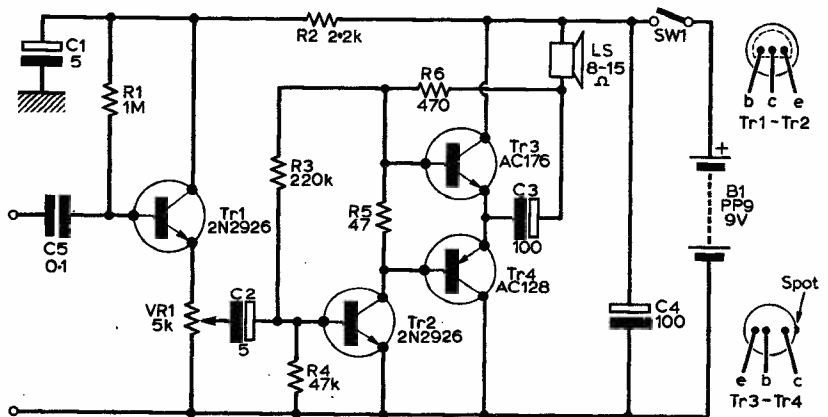


Fig. 1: The circuit of the amplifier.

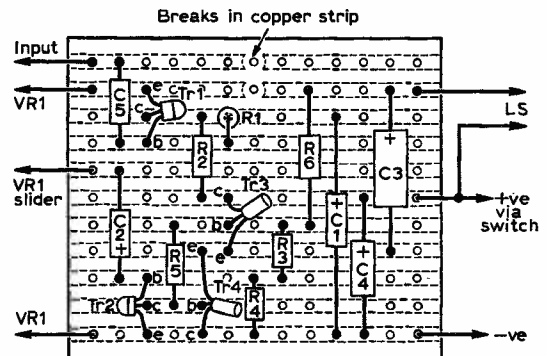


Fig. 2: A suggested layout on Veroboard.

Negative feedback is applied via R6 which is coupled to the "live" side of the speaker. Circuits of this type usually include resistors of 1Ω or 2Ω in the emitters of the output transistors but if the battery supply does not exceed 9V these are not really necessary. If the supply voltage is increased greater output is achieved but the output pair will overheat and eventually blow.


**CONSTRUCTION**

A suggested layout for the amplifier is shown in Fig. 2, but this is not critical. One point must be carefully checked. If R5 is not connected properly the output transistors will blow instantly, so be especially careful here with regard to dry joints etc. The speaker impedance can vary over a wide range and even 3Ω types work perfectly well though it is better not to go this low and 8Ω is the lowest that should be used for any length of time. ■



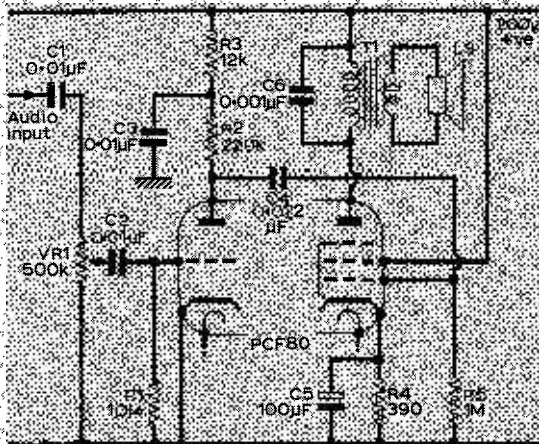**SERVICING—Part 6, October Issue**

We apologise for the wrong circuit being given in Fig. 1. The correct circuit is shown below.



**TESTING SURPLUS TRANSISTORS, October Issue.**  
The battery polarity is shown reversed in Fig. 4b.

**BINDERS**

If you are one of the tens of thousands of readers who keeps his old issues why not keep them neatly in our specially designed binder?

The cost is 85p, post paid, and when ordering please state the volume number (if any).

Orders should be sent to: The Binding Department, Practical Wireless, Carlton House, 66-69 Great Queen Street, London WC2B 5DD

switch S2 can now be connected. The temporary wires should be removed.

**Overall Check**

The crystal oscillator should be allowed to run for about 20 minutes and then the frequency should be checked and set against Droitwich as previously described.

Using an audio oscillator and then an r.f. signal generator check the operation of the counter on signals of various frequencies and amplitudes. The 'LEVEL' control should be adjusted carefully so that the input signal operates the input clipping stage correctly and ensures reliable operation of the counter and display.

The top operating frequency should be in excess of 15MHz and may be as high as 25MHz depending on the integrated circuits used. The time measurement may be checked by measuring the duration of one cycle of the 50Hz mains. A few volts from a mains stepdown transformer is suitable for this. With the function switch in the 'mS' positions, the time of one cycle will be very close to 20mS, depending on the true frequency.

In common with all digital frequency timer/counters of this type there is always the possibility of an error of one least significant digit. This is due to the input signal not being synchronised with the crystal oscillator from which the counting period is derived. For example, during one counting period *n* cycles of the input signal may be counted. The next counting period may be very slightly shifted in time with respect to the input signal so that this time *n*+1 cycles are counted. This error is not present in the internal check, position 6, as here the signal being counted is synchronised with the gate period, one having been divided from the other.

TO BE CONTINUED

**TELEVISION**

**SIMPLE UHF AERIAL PREAMP**

A recent transistor, the BF272, is used in a simple circuit housed in a 35mm. film can. The emphasis has been placed on simple construction and minimum expense. The earlier AF139 can be used as an alternative, reducing the cost still further.

**SERVICING TV RECEIVERS**

Continuing our coverage of chassis widely used in the rental trade, next month we deal with the Plessey/Defiant 9A50-9A52 series.

**PANORAMIC MONITOR**


... Or things you can do with varicap tuners! These are now readily available and are very versatile. One application highlighted is as a Band monitor—the tuner is swept across the Band and the output monitored on an oscilloscope.

**NOVEMBER ISSUE on sale OCTOBER 22nd**

**We regret that, due to shortage of space, I.C. of the Month and Servicing, Part 7 have had to be held over until next month.**

# new

## Super IC-12

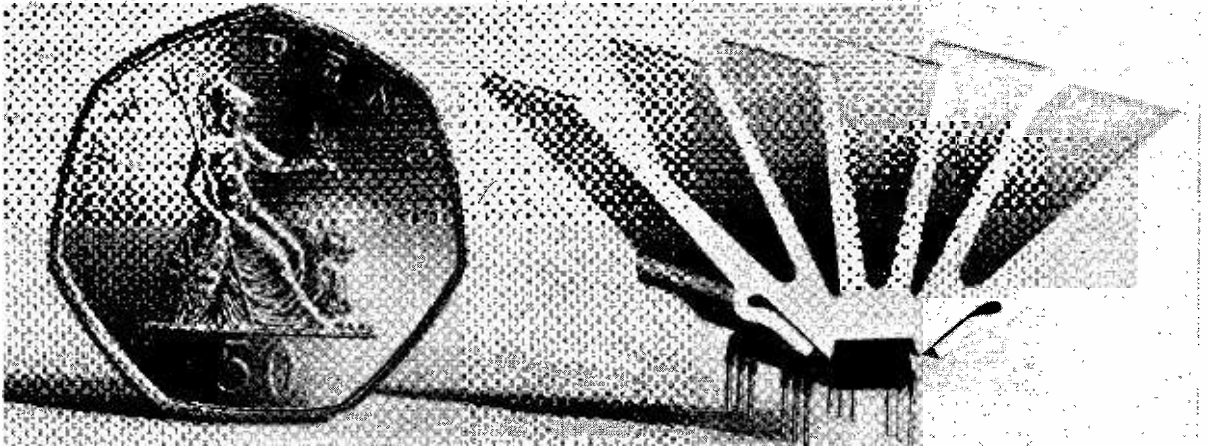

### High fidelity Monolithic Integrated Circuit Amplifier

Two years ago Sinclair Radionics announced the World's first monolithic integrated circuit Hi-Fi amplifier, the IC.10. Now we are delighted to be able to introduce its successor, the Super IC.12. This 22 transistor unit has all the virtues of the original IC.10 plus the following advantages:

1. Higher power.
2. Fewer external components.
3. Lower quiescent consumption.
4. Compatible with Project 60 modules.
5. Specially designed built-in heat sink. No other heat sink needed.
6. Full output into 3, 4, 5 or 8 ohms.
7. Works on any voltage from 6 to 28 volts without adjustment.
8. NEW 22 transistor circuit.

**Output power** 6 watts RMS continuous (12 watts peak).

**Frequency Response** 5 Hz to 100KHz  $\pm$  1 dB.

**Total Harmonic Distortion** Less than 1%. (Typical 0.1%) at all output powers and all frequencies in the audio band.

**Load Impedance** 3 to 15 ohms.

**Power Gain** 90dB (1,000,000,000 times) after feedback.

**Supply Voltage** 6 to 28 volts (Sinclair PZ-5 or PZ-6 power supplies ideal).

**Size** 22 x 45 x 28 mm including pins and heat sink.

**Input Impedance** 250 Kohms nominal.

**Quiescent current** 8mA at 28 volts.

With the addition of only a very few external resistors and capacitors the Super IC.12 makes a complete high fidelity audio amplifier suitable for use with pick-up, F.M. tuner etc. Alternatively, for more elaborate systems, modules in the Project-60 range such as the Stereo 60 and A.F.U. may be added. The comprehensive manual supplied with each unit gives full circuit and wiring diagrams for a large number of applications in addition to high fidelity. These include car radios, oscillators etc. The very low quiescent consumption makes the Super IC.12 ideal for battery operation.



Price, inc. FREE printed circuit board for mounting.

**£2.98** Post free

#### SINCLAIR GENERAL GUARANTEE

Should you not be completely satisfied with your purchase when you receive it from us, return the goods without delay and your money will be refunded in full, including cost of return postage, at once and without question. Full service facilities are available to all Sinclair customers.



Sinclair Radionics Ltd, London Rd, St. Ives Huntingdonshire PE17 4HJ  
Telephone St Ives (048 06) 4311

# sinclair


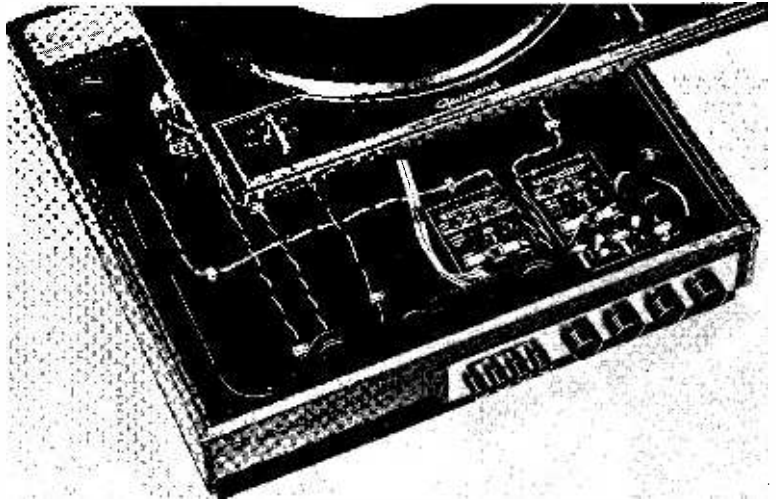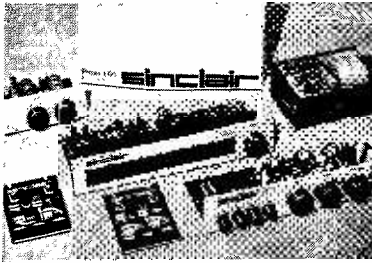
# Sinclair Project 60

The World's leading range of high fidelity modules



## New!

### Project 605

The easy way to buy and build Project 60



Project 605 is one pack containing: one PZ5, two Z30's, one Stereo 60 and one Masterlink. This new module contains all the input sockets and output components needed together with all necessary leads cut to length and fitted with neat little clips to plug straight on to the modules. Thus all soldering and hunting for the odd part is eliminated. You will be able to add further Project 60 modules as they become available adapted to the Project 605 method of connecting.

Complete Project 605 pack with comprehensive manual, post free **£29.95**

All you need for a superb 30 watt high fidelity stereo amplifier.

Sinclair Radionics Limited, London Road,  
St. Ives, Huntingdonshire PE17 4HJ.  
Tel: St. Ives (048 06) 4311

# sinclair

Project 60 offers more advantage to the constructor and user of high fidelity equipment than any other system in the world.

Performance characteristics are so good they hold their own with any other available system irrespective of price or size.

Project 60 modules are more versatile – using them you can have anything from a simple record player or car radio amplifier to a sophisticated and powerful stereo tuner-amplifier. Either power amplifier can be used in a wide variety of applications as well as high fidelity. The Stereo 60 pre-amplifier control unit may also be used with any other power amplifier system, as can the AFU filter unit. The stereo FM tuner operates on the unique phase lock loop principle to provide the best ever standards of sensitivity and audio quality. Project 60 modules are very easily connected together by following the 48 page manual supplied free with all Project 60 equipment. The modules are great space savers too and are sold individually boxed in distinctive white and black cartons. With all these wonderful advantages, there remains the most attractive of all – price. When you choose Project 60 you know you are going to get the best high fidelity in the world, yet thanks to Sinclair's vast manufacturing resources (the largest in Europe) prices are fantastically low and everything you buy is covered by the famous Sinclair guarantee of reliability and satisfaction.

#### Typical Project 60 applications

System	The Units to use	together with	Cost of Units
Simple battery record player	<b>Z.30</b>	Crystal P.U., 12V battery volume control	<b>£4.48</b>
Mains powered record player	<b>Z.30, PZ.5</b>	Crystal or ceramic P.U., volume control etc.	<b>£9.45</b>
20+20 W. stereo amplifier for most needs	<b>2 x Z.30s, Stereo 60, PZ.5</b>	Crystal, ceramic or mag. P.U., F.M. Tuner, etc.	<b>£23.90</b>
20+20 W. stereo amplifier with high performance spkrs.	<b>2 x Z.30s, Stereo 60, PZ.6</b>	High quality ceramic or magnetic P.U., F.M. Tuner, Tape Deck, etc.	<b>£26.90</b>
40+40 W. R.M.S. de-luxe stereo amplifier	<b>2 x Z.50s, Stereo 60 PZ.8, mains trsfrmr</b>	As above	<b>£34.88</b>
Indoor P.A.	<b>Z.50, PZ.8, mains transformer</b>	Mic., guitar, speakers, etc., controls	<b>£19.43</b>

F.M. Stereo Tuner (**£25**) & A.F.U. Filter Unit (**£5.98**) may be added as required.

# from a simple amplifier to a complete stereo tuner amplifier with Project 60 modules

## Z.30 & Z.50 power amplifiers



The Z.30 and Z.50 are of advanced design using silicon epitaxial planar transistors to achieve unsurpassed standards of performance. Total harmonic distortion is an incredibly low 0.02% at full output and all lower outputs. Whether you use Z.30 or Z.50 amplifiers in your Project 60 system will depend on personal preference, but they are the same size and may be used with other units in the Project 60 range equally well.

**SPECIFICATIONS (Z.50 units are interchangeable with Z.30s in all applications).**  
**Power Outputs**

**Z.30** 15 watts R.M.S. into 8 ohms using 35 volts; 20 watts R.M.S. into 3 ohms using 30 volts.  
**Z.50** 40 watts R.M.S. into 3 ohms using 40 volts; 30 watts R.M.S. into 8 ohms using 50 volts.  
**Frequency response:** 30 to 300,000Hz  $\pm 1$ dB.  
**Distortion:** 0.02% into 8 ohms.  
**Signal to noise ratio:** better than 70dB unweighted.  
**Input sensitivity:** 250mV into 100 Kohms.  
 For speakers from 3 to 15 ohms impedance.  
**Size:** 14 x 80 x 57 mm.


**Z.30**  
 Built, tested and guaranteed with circuits and instructions manual. **£4.48**

**Z.50**  
 Built, tested and guaranteed with circuits and instructions manual. **£5.48**
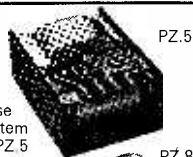
## Power Supply Units

Designed special for use with the Project 60 system of your choice. Use PZ.5 for normal Z.30 assemblies and PZ.3 where a stabilised supply is essential.

**PZ.5** 30 volts un stabilised **£4.98**  
**PZ.6** 35 volts stabilised **£7.98**  
**PZ.8** 45 volts stabilised (less mains transformer) **£7.98**  
**PZ.8** mains transformer **£5.98**



## Project 60 Stereo F.M. Tuner



**First in the world to use the phase lock loop principle**

The phase lock loop principle was used for receiving signals from space craft because of its vastly improved signal to noise ratio. Now, Sinclair have applied the principle to an F.M. tuner with fantastically good results. Other original features include varicap diode tuning, printed circuit coils, an I.C. in the specially designed stereo decoder and squelch circuit for silent tuning between stations. Good reception is possible in difficult areas, and often a few inches of wire are enough for an aerial. In terms of a high fidelity this tuner has a lower level of distortion than any other tuner we know. Stereo broadcasts are received automatically as the tuning control is rotated, a panel indicator lighting up as the stereo signal is tuned in. This tuner can also be used to advantage with any other high fidelity system.

**SPECIFICATIONS—Number of transistors:** 16 plus 20 in I.C. **Tuning range:** 87.5 to 108 MHz.  
**Capture ratio:** 1.5dB. **Sensitivity:** 2 $\mu$ V for 30dB quieting; 7 $\mu$ V for lock-in over full deviation.  
**Squelch level:** 20 $\mu$ V. **A.F.C. range:**  $\pm 200$  KHz. **Signal to noise ratio:** > 65dB. **Audio frequency response:** 10 Hz – 15 KHz ( $\pm 1$ dB). **Total harmonic distortion:** 0.15% for 30% modulation. **Stereo decoder operating level:** 2 $\mu$ V. **Cross talk:** 40dB. **Output voltage:** 2 x 150mV R.M.S. **Operating voltage:** 25-30 VDC. **Indicators:** Power on/tuning/stereo.  
**Size:** 83 x 40 x 207 mm.

Built and tested. Post free.

**£25**


## Stereo 60 Pre-amp/control unit



Designed for Project 60 range but suitable for use with any high quality power amplifier. Again silicon epitaxial planar transistors are used throughout, achieving a really high signal-to-noise ratio and excellent tracking between channels. Input selection is by means of push buttons and accurate equalisation is provided for all the usual inputs.

**SPECIFICATIONS—Input sensitivities:** Radio – up to 3mV, Mag. p.u. 3mV; correct to R.I.A.A. curve  $\pm 1$ dB; 20 to 25,000 Hz. Ceramic p.u. – up to 3mV; Aux – up to 3mV. **Output:** 250mV. **Signal to noise ratio:** better than 70dB. **Channel matching:** within 1dB. **Tone controls:** TREBLE  $\pm 15$  to  $-15$ dB at 10 KHz; BASS  $\pm 15$  to  $-15$ dB at 100Hz. **Front panel:** brushed aluminium with black knobs and controls. **Size:** 66 x 40 x 207 mm. **£9.98**  
 Built, tested and guaranteed.

## A.F.U. High & Low Pass Filter Unit

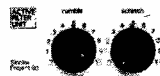

For use between Stereo 60 unit and two Z.30s or Z.50s, and is easily mounted. It is unique in that the cut-off frequencies are continuously variable, and as attenuation in the rejected band is rapid (12dB/octave), there is less loss of the wanted signal than has previously been possible. Amplitude and phase distortion are negligible. The A.F.U. is suitable for use with any other amplifier system. Two filter stages – rumble (high pass) and scratch (low pass). Supply voltage – 15 to 35V. Current – 3mA. H.F. cut-off ( $-3$ dB) variable from 28KHz to 5KHz. L.F. cut-off ( $-3$ dB) variable from 25Hz to 100Hz. Distortion at 1KHz (35V. supply) (0.02% at rated output. **Size:** 66 x 40 x 90 mm. **£5.98**  
 Built tested and guaranteed.

## The Sinclair Guarantee

If within 3 months of purchasing Project 60 modules directly from us, you are dissatisfied with them, we will refund your money at once. Each module is guaranteed to work perfectly and should any defect arise in normal use we will service it at once and without any cost to you whatsoever provided that it is returned to us within 2 years of the purchase date. There will be a small charge for service thereafter. No charge for postage by surface mail. Air-mail charged at cost.

To: SINCLAIR RADIONICS LTD LONDON ROAD ST. IVES HUNTINGDONSHIRE PE17 4HJ

Please send	Name
	Address
I enclose cash/cheque/money order.	

PW 10

# Sinclair Q16/Micromatic

## Q16 High fidelity loudspeaker

The Q16 employs the well proven acoustic principles specially developed by Sinclair in which a special driver assembly is meticulously matched to the characteristics of the uniquely designed cabinet. In reviewing this exclusive Sinclair design, technical journals have justly compared the Q16 with much more expensive loudspeakers. Its shape enables the Q16 to be positioned and matched to its environment to much better effect than is the case with conventionally styled enclosures. A solid teak surround with a special all-over cellular foam front is used as much for appearance as its ability to pass all audio frequencies without loss.

This elegantly designed shelf mounting speaker brings genuine high fidelity within reach of every music lover.

## Specifications:

**Construction:** Special sealed seamless sound or pressure chamber with internal baffle.

**Loading:** up to 14 watts RMS.


**Input Impedance:** 8 ohms.

**Frequency response:** From 60 to 16,000 Hz. confirmed by independently plotted B and K curve.

**Driver unit:** Special high compliance unit having massive ceramic magnet of 11,000 gauss, aluminium speech coil and special cone suspension for excellent transient response.

**Size and styling:** 9 $\frac{3}{4}$  in. square on face x 4 $\frac{3}{4}$  in. deep with neat pedestal base. Black all over cellular foam front with natural solid teak surround.

**Price £8.98.**

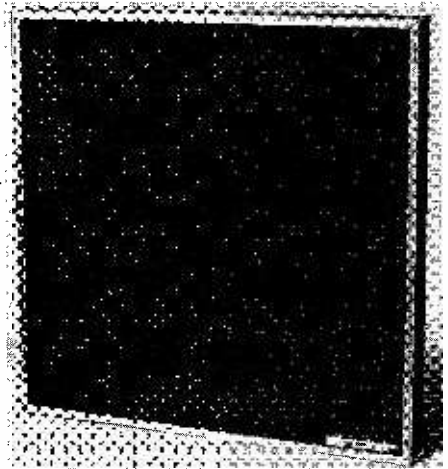

## Britain's smallest radio

Considerably smaller than an ordinary box of matches, this is a multi-stage AM receiver brilliantly designed to provide remarkable standards of selectivity, power and quality for its size. Powerful AGC counteracts fading from distant stations; bandspread at higher frequencies makes reception of Radio 1 easy. The plug-in magnetic earpiece provided, matches the Micromatic's output to give wonderful standards of reproduction. Everything including the special ferrite rod aerial and batteries is contained within the minute attractively designed case. Whether you build a Micromatic kit or buy this amazing receiver ready built and tested, you will find it as easy to take with you as your wrist watch, and dependable under the severest listening conditions.

## Specifications:

**Size:** 36 x 33 x 13 mm (1.8 x 1.3 x 0.5 in.)

**Weight:** including batteries, 28.4 gm (1 oz.)

**Case:** Black plastic with anodised aluminium front panel and spun aluminium dial.

**Tuning:** medium wave band with bandspread at higher frequencies (550 to 1,600 KHz).

**Earpiece:** Magnetic type.

**On/off switching:** By inserting and withdrawing earpiece plug.

Kit in pack with earpiece, case, instructions and solder **£2.48.**

Ready built, tested and guaranteed, with earpiece **£2.98.**

*Two Mallory Mercury batteries type RM675 required from radio shops, chemists, etc.*



To: SINCLAIR RADIONICS LTD LONDON ROAD ST. IVES HUNTINGDONSHIRE PE17 4HJ

Please send \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

\_\_\_\_\_ for which I enclose cash/cheque/money order

PW1171

Sinclair Radionics Ltd., London Rd, St. Ives  
Huntingdonshire PE17 4HJ.  
Telephone St. Ives (048 06) 4311

**sinclair**

TOP QUALITY — LOW COST



AMATEUR RADIO EQUIPMENT



**NEW!**




### MULTIBAND-6TRF SHORT WAVE RECEIVER KIT

In response to your many requests, we announce the all transistor version of the famous CR 45. This new T.R.F. Short Wave Receiver employs 6 Transistors, FET Regen Det./A.F. Hi-Gain Pre-Amp./Packaged A.F. Module giving loudspeaker output for an external 2/3 ohm loudspeaker. Its exceptional gain will provide world-wide reception even on a simple indoor aerial. It tunes 550 KHz to 30 MHz (540-10 metres) no gaps using miniature pre-aligned plug-in coils. Dials are calibrated in MHz and Degrees with separate Electrical Bandspread.

Handsome styling with Black Perspex Panel, Steel Cabinet with Black finish.

This is a quality CODAR-KIT with full 12 months guarantee. No technical knowledge required, printed circuit construction, Instruction Manual with pictorial drawings backed by friendly Help-U After Sales Service if you have any queries.

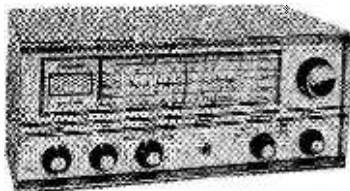Complete Kit (even to the resin-cored solder) with 3 Coils. £11.50 Carriage 50p.



### CR 70A COMMUNICATION RECEIVER

The CODAR CR 70A is an outstanding general coverage communication receiver, ideal for the keen S.W.L.

It tunes from 540 metres medium through to 10 metres with no gaps. Covers shipping, coastguard and distress frequencies, all five amateur bands 160-10 metres, international broadcast, Met. stations etc. etc. giving world-wide reception. Exclusive features include Air-spaced CODAR-COIL Hi-"Q" Aerial input, Illuminated "S" Meter and Slide Rule Scale, Two Speed vernier tuning, Separate B.F.O. for CW/SSB signals, 5 valves inc. two twin triodes giving 7 valve line-up, separate output for Tape recorder.

Ready to plug in to 200/240 volts A.C. it only needs your aerial and a 2/3 ohm loudspeaker to bring the world to your finger tips. 12 months full guarantee.

Complete ready built £24.50, Carriage 50p.

Ask the chap who's got one, there's lots of them!

# CODAR RADIO COMPANY

Unit 1, Meadow Road Industrial Estate, East Worthing, Sussex.

## PROGRESSIVE POWER SUPPLY MODULES

Ideal for many types of electronic instruments, these power supply modules are built to professional standards. Very modestly priced they are sold with a "Money Back" Guarantee of satisfaction.

**71Z RANGE.** Basic zener stabilised P.U. with floating output. For general use including switching & op. amp. circuits. Size 4" x 4".

71Z9 ± 9v at 30mA } Price £3.95  
71Z12 ± 12v at 15mA } each + £0.25  
71Z15 ± 15v at 10mA } P & P

**71ZR RANGE.** A more complex circuit than the 71Z Range giving greater stability with changing loads and with reduced ripple content. Output current limiting is included for general protection. An ideal P.U. for electronic instruments and control circuits. Size 4" x 3".


71ZR9 + 9v at 40mA nom. } Price £4.50  
71ZR12 + 12v at 40mA nom. } each  
71ZR15 + 15v at 40mA nom. } +£0.25  
P & P.

**71ZA.** An extension of the 71ZR embodying an error amplifier with current limiting and adjustable output voltage regulated to better than 1.5% for load and mains variations. Ripple better than 3mV. Size 4" x 4".

71ZA. 15v ± 3v at 100mA. Price £5.50  
each + £0.25  
P & P.

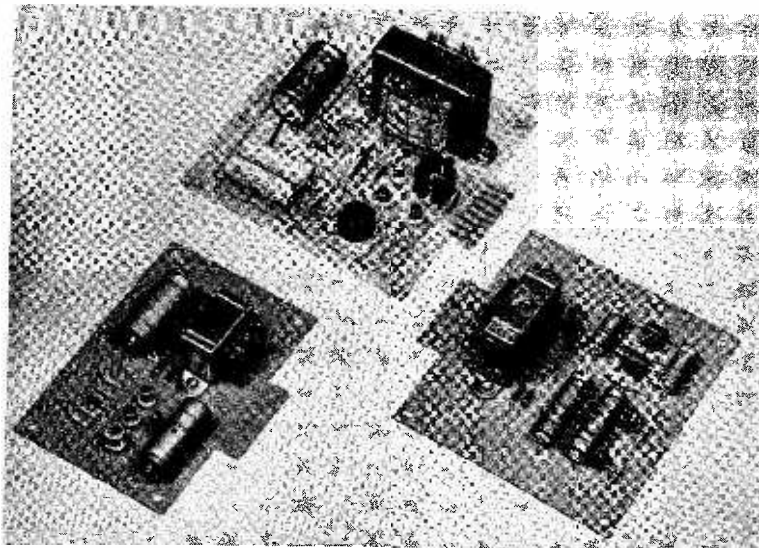**714.** Special power unit suitable for the Audio Signal Generator described in the May issue. Price £4.20 each + £0.25 P & P. Trade enquiries invited.

All units are completely assembled and tested and may be used by plugging in using the edge contact provided. Alternatively they may be wired in circuit.



OTHER TYPES OF POWER SUPPLY UNITS ARE ALSO AVAILABLE  
PLEASE SEND ENQUIRIES STATING YOUR REQUIREMENTS.

We are also distributors of the full range of Newmarket Transistors Limited's P.C. Modules

**HARVEY HALL (Dept. P.W.), BRECKLAND WORKS, EARLS ST., THETFORD, NORFOLK.**





# -the lowest prices!

## 74 series T.T.L. I.C.'s DOWN AGAIN IN PRICE



Check our 74 Series List before you buy any I.C.'s. Our prices are the lowest possible. All devices ex-stock. Full spec. guaranteed.

BI-PAK Order No.	Similar Types to:—Description	Price and qty. prices		
		1-24 \$p	25-99 \$p	100 up \$p
BF00 = 7400	Quad 2-input NAND gate	0-15	0-14	0-12
BF01 = 7401	Quad 2-input pos. NAND gate (with open collector output)	0-15	0-14	0-12
BF02 = 7402	Quad 2-input pos. NOR gates	0-15	0-14	0-12
BF03 = 7403	Quad 2-input pos. NAND gates (with open collector output)	0-15	0-14	0-12
BF04 = 7404	Hex Inverters	0-15	0-14	0-12
BF05 = 7405	Hex Inverter (with open-collector output)	0-15	0-14	0-12
BF10 = 7410	Triple 3-input pos. NAND gates	0-15	0-14	0-12
BF13 = 7413	Dual 4-input Schmitt trigger	0-29	0-28	0-24
BF20 = 7420	Dual 4-input pos. NAND gates	0-15	0-14	0-12
BF30 = 7430	8-input pos. NAND gates	0-15	0-14	0-12
BF40 = 7440	Dual 4-input pos. NAND buffers	0-15	0-14	0-12
BF41 = 7441	BCD to decimal nixie driver	0-67	0-64	0-58
BF42 = 7442	BCD to decimal decoder (4-10 lines, 1 of 10)	0-67	0-64	0-58
BF46 = 7446	BCD-to-seven-segment decoder/driver	2-00	1-75	1-50
BF47 = 7447	BCD-to-seven-segment decoder/drivers (15V outputs)	0-97	0-94	0-85
BF48 = 7448	BCD-to-seven-segment decoder/driver	0-97	0-94	0-85
BF50 = 7450	Expandable dual 2-input and-or-invert	0-15	0-14	0-12
BF51 = 7451	Dual 2-wide 2-input and-or-invert gates	0-15	0-14	0-12
BF53 = 7453	Quad 2-input expandable and-or-invert	0-15	0-14	0-12
BF54 = 7454	4-wide 2-input and-or-invert gates	0-15	0-14	0-12
BF60 = 7460	Dual 4-input expander	0-15	0-14	0-12
BF70 = 7470	Single-phase J-K flip-flop	0-29	0-28	0-24
BF72 = 7472	Master slave J-K flip-flop	0-29	0-28	0-24
BF73 = 7473	Dual Master slave J-K flip-flop	0-27	0-25	0-22
BF74 = 7474	Dual D type flip-flop	0-27	0-25	0-22
BF76 = 7476	Quad latch	0-47	0-45	0-42
BF76 = 7476	Dual J-K with pre-set and clear	0-43	0-40	0-38
BF80 = 7480	Gated full adders	0-67	0-64	0-58
BF81 = 7481	16-bit read/write memory	0-97	0-94	0-85
BF82 = 7482	2-bit binary full adders	0-97	0-94	0-85
BF83 = 7483	Quad full adder	1-10	1-05	0-95
BF86 = 7486	Quad 2-input exclusive NOR gates	0-32	0-30	0-28
BF90 = 7490	BCD decade counter	0-67	0-64	0-58
BF91 = 7491	8-bit shift registers	0-67	0-64	0-58
BF92 = 7492	Divide-by-twelve counters	0-67	0-64	0-58
BF93 = 7493	4-bit binary counters	0-67	0-64	0-58
BF94 = 7494	Dual entry 4-bit shift register	0-77	0-74	0-68
BF95 = 7495	4-bit up-down shift register	0-77	0-74	0-68
BF96 = 7496	5-bit parallel in parallel out shift register	0-77	0-74	0-68
BF100 = 74100	8-bit D bistable latches	1-75	1-65	1-55
BF104 = 74104	Single J-K flip-flop equivalent 9000 series	0-97	0-94	0-88
BF105 = 74105	Single J-K flip-flop equivalent 9001 series	0-97	0-94	0-88
BF107 = 74107	Dual Master slave flip-flops	0-40	0-38	0-36
BF110 = 74110	Gates master-slave flip-flops	0-55	0-53	0-50
BF111 = 74111	Dual Master slave flip-flop	1-25	1-15	1-00
BF118 = 74118	Hex set-reset latches	1-00	0-95	0-90
BF119 = 74119	Hex set-reset latches, 24-pin	1-85	1-25	1-10
BF121 = 74121	Monostable multivibrators	0-67	0-64	0-58
BF141 = 74141	BCD-to-decimal decoder/driver	0-67	0-64	0-58
BF145 = 74145	BCD-to-decimal decoder/driver O/C	1-14	1-40	1-20
BF150 = 74150	16-bit data selector	1-80	1-70	1-60
BF151 = 74151	8-bit data selectors (with strobe)	1-00	0-95	0-90
BF153 = 74153	Dual 4-line-to-1-line data	1-20	1-10	0-95
BF154 = 74154	4- to 16-line decoder	1-80	1-70	1-60
BF155 = 74155	Dual 2- to 4-line decoder	1-40	1-30	1-20
BF156 = 74156	Dual 2- to 4-line decoder O/C	1-40	1-30	1-20
BF160 = 74160	Sync. decade counter	1-80	1-70	1-60
BF161 = 74161	Sync. 4-bit binary counter	1-80	1-70	1-60
BF190 = 74190	Sync. up-down BCD counter	3-50	3-25	3-00
BF191 = 74191	Sync. binary up-down counter (single clock line)	3-50	3-25	3-00
BF192 = 74192	Sync. up-down decade counter	2-10	1-95	1-75
BF193 = 74193	Sync. binary up-down counter (two clock lines)	2-10	1-95	1-75
BF196 = 74196	Pre-settable 50MHz decade counter	1-80	1-70	1-60
BF197 = 74197	Pre-settable 50MHz binary counter	1-80	1-70	1-60
BF198 = 74198	8-bit parallel L-R shift register	5-50	5-00	4-00
BF199 = 74199	8-bit parallel access shift register	5-50	5-00	4-00

Devices may be mixed to qualify for quantity price. Larger quantities—prices on application (TTL 74 Series only). Data is available for the above series of I.C.'s in booklet form. Price 13p.


### TTL INTEGRATED CIRCUITS

Manufacturers "Fall outs"—out of spec. devices including functional units and part function but classed as out of spec. from the manufacturers' very rigid specifications. Ideal for learning about I.C.'s and experimental work.

PAK No.	PAK No.	PAK No.
UIC00 = 12 x 7400N 50p	UIC42 = 5 x 7430N 50p	UIC80 = 5 x 7480N 50p
UIC01 = 12 x 7401N 50p	UIC50 = 12 x 7450N 50p	UIC82 = 5 x 7482N 50p
UIC02 = 12 x 7402N 50p	UIC51 = 12 x 7451N 50p	UIC83 = 5 x 7483N 50p
UIC03 = 12 x 7403N 50p	UIC60 = 12 x 7460N 50p	UIC86 = 5 x 7486N 50p
UIC04 = 12 x 7404N 50p	UIC70 = 8 x 7470N 50p	UIC90 = 5 x 7490N 50p
UIC05 = 12 x 7405N 50p	UIC72 = 8 x 7472N 50p	UIC92 = 5 x 7492N 50p
UIC10 = 12 x 7410N 50p	UIC73 = 8 x 7473N 50p	UIC93 = 5 x 7493N 50p
UIC20 = 12 x 7420N 50p	UIC74 = 8 x 7474N 50p	UIC94 = 5 x 7494N 50p
UIC40 = 12 x 7440N 50p	UIC75 = 8 x 7475N 50p	UIC95 = 5 x 7495N 50p
UIC41 = 5 x 7441AN 50p	UIC76 = 8 x 7476N 50p	UIC96 = 5 x 7496N 50p

UICX1 = 25 x Ass'd 74 51-50  
Pake cannot be split but 20 assorted pieces (our mix) is available as PAK UICX1. Every PAK carries out BI-PAK Satisfaction or money back GUARANTEE.

## ANOTHER BI-PAK FIRST!

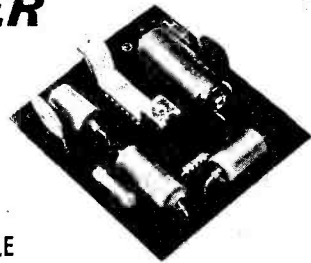

THE NEW S.G.S.  
EA 1000 AUDIO  
AMPLIFIER MODULE

\*GUARANTEED NOT LESS THAN 3 WATTS RMS

Especially designed by S.G.S. incorporating their proven Linear I.C. Audio Amp. TA/621 providing unlimited applications for the enthusiast in the construction of radios, record players, Audio and Stereo units. Also ideal for intercom systems, monitoring applications and phone answering machines. OTHER USES: portable applications where supply rails as low as 9V are of prime importance.

- Sensitivity 40 mV for 1 watt VOLTAGE GAIN 40dB but can be varied up to 73dB for some applications.
- Signal to Noise Ratio 86dB.
- Frequency response better than 50 Hz to 25 KHz for -3dB.
- Normal supply Voltage 9-24V.
- Suitable for 8-16 OHM Loads.
- Overall Size 2" x 3" x 1/2".
- Typical Total Harmonic distortion at 1 watt less than 1%.

\*Supply voltage (Vs) = 24V 15ohm load.

Module Tested and Guaranteed

Quantity 1-9 10-25  
Price each £2-63 £2-28  
Larger quantities quoted on request

Full hook-up diagrams and complete technical data supplied free with each module or available separately at 10p each.

### ROCK BOTTOM PRICES—CAN'T BE BEATEN!

LOGIC Type No.	Function	Price 1-24 25-99 100 up
BP930	Expandable dual 4-input NAND	12p 11p 10p
BP932	Expandable dual 4-input NAND buffer	13p 12p 11p
BP933	Dual 4-input expander	13p 12p 11p
BP935	Expandable Hex Inverter	13p 12p 11p
BP936	Hex Inverter	13p 12p 11p
BP944	Dual 4-input NAND expandable buffer without pull-up	18p 18p 11p
BP945	Master-slave JK or RS	25p 24p 22p
BP946	Quad, 2-input NAND	12p 11p 10p
BP948	Master-slave JK or RS	25p 24p 22p
BP951	Monostable	85p 60p 55p
BP962	Triple 3-input NAND	12p 11p 10p
BP9093	Dual Master-slave JK with separate clock	40p 38p 35p
BP9094	Dual Master-slave JK with separate clock	40p 38p 35p
BP9097	Dual Master-slave JK with Common Clock	40p 38p 35p
BP9099	Dual Master-slave JK Common Clock	40p 38p 35p

Devices may be mixed to qualify for quantity price. Larger quantity prices on application. (DTL 930 Series only).

### BRAND NEW LINEAR I.C.'s—FULL SPEC.

Type No.	Case	Leads	Description	Price 1-24 25-99 100 up
BP 201C—8L201C	TO-5	8	G.P. Amp	68p 58p 45p
BP 701C—8L701C	TO-5	8	OP Amp	68p 58p 45p
BP 702C—8L702C	TO-5	8	OP Amp Direct OP	68p 58p 45p
BP 702—72702	D.I.L.	14	G.P. OP Amp (Wide Band)	58p 45p 40p
BP 709—72709	D.I.L.	14	High OP Amp	58p 45p 40p
BP 709P—7A709C	TO-5	8	High Gain OP Amp	58p 45p 40p
BP 711—7A711	TO-5	10	Dual comparator	38p 50p 45p
BP 741—72741	D.I.L.	14	High Gain OP Amp (Protected)	75p 60p 50p
7A 703C—7A703C	TO-5	6	R.F.—I.F. Amp	48p 35p 27p
TAA 263—	TO-72	4	A.E.—A.F. Amp	70p 60p 55p
TAA 293—	TO-74	10	G.P. Amp	90p 75p 70p

All prices quoted in new pence Giro No. 388-7006  
Please send all orders direct to warehouse and despatch department

# BI-PAK

P.O. BOX 6, WARE, HERTS

Postage and packing add 7p. Overseas add extra for air mail.  
Minimum order 50p. Cash with order please.

Guaranteed Satisfaction or Money Back

# TECHNICAL TRAINING

## *in radio television and electronics*

Whether you are a newcomer to radio and electronics, or are engaged in the industry and wish to prepare for a recognized examination, ICS can further your technical knowledge and provide the specialized training so essential to success. ICS have helped thousands of ambitious men to move up into higher paid jobs—they can help you too! Why not fill in the coupon below and find out how?

*Many diploma and examination courses available, including expert coaching for:*

- C. & G. Telecommunication Techns'. Certs.
  - Radio Amateurs' Examination
  - Radio Operator Certificates
  - General Certificate of Education, etc.
- Now available Colour T.V. Servicing


**Examination Students coached until successful**

## NEW SELF-BUILD RADIO COURSES

Learn as you build. You can learn both the theory and practice of valve and transistor circuits, and servicing work while building your own 5-valve receiver, transistor portable, and high-grade test instruments—all under expert tuition. Transistor Portable available as separate course.

### POST THIS COUPON TODAY

for full details of ICS courses in Radio, T.V. and Electronics.



**INTERNATIONAL CORRESPONDENCE SCHOOLS**  
EST. 1891

Dept. 171, Intertext House, Stewarts Road, London, S.W.8 4UJ  
Please send me the ICS prospectus—free and without obligation.  
(state Subject or Exam).....

NAME .....  
(BLOCK CAPITALS PLEASE)

ADDRESS .....

AGE..... OCCUPATION..... 11/71

**INTERNATIONAL CORRESPONDENCE SCHOOLS**

## PADGETTS RADIO STORE

### OLD TOWN HALL, LIVERSEDEGE. YORKS

TEL. HECKMONDWIKE 4285

Latest Air Ministry Release. Radio Receiver Type R4187. 2-8 To 18 M.H.Z. in Three Bands. Complete with 17 Miniature Valves, 26 Volt Motor Power Supply Motor and Manually Tuned. Very Clean Condition but not tested. £5. Carriage and Insurance 75p.

Control Unit Type 4190. Complete with Three Miniature Valves 1½ 600 U.A. Meter, Six Relays, Model Makers Motor with Gears. 24 Press Buttons, lots of Spares. Very Clean condition. £1-50. Carriage and Insurance 75p.

Autostabilisor Amplifier Unit. Complete with Carpenter Relay and Base. Many Spares. 50p. P/P 33p.

Brand New Manufacturers Surplus Mains Transformers 250-0 250 80M.A. 6-3 4 Amps. £1-05. P/P 25p.

Reclaimed T.V. Tubes. All with 12 Months Guarantee. AW43/88 £2. AW43/80 £1-50. MW43/69 £1.

Special Offer Brand New Brimar Tubes. C17P-M. £1. Many older Types In Stock. Carriage and Insurance on any Tube £1-10.

Speakers Ex T.V. Tested and in perfect condition all 25p each Post Paid. 5" Round. 6" Round. 7x4. 6x4. 8x2. in Dozen lots mixed if required £2-75.

Toggle Switches. Ex Units. D.P.D.T. 10p. D.P.S.T. 5p. S.P.S.T. Spring loaded 10p. D.P.S.T. Press Button Spring Loaded 10p. P/P on any Switch 4p Doz Lots Post Paid.

G.P.O. Relays Ex Units. 400 Ohms and 600 Ohms. 50p doz. P/P 25p. Sample Relay 6p P/P 5p.

Miniature Lamp Holder, Brass. 10p P/P 5p. Doz. Lots 90p Post Paid. Base Board Type.

Best Quality Tapes. 7 L.P. 70p. 7" St. 59p. 5" L.P. 50p. 5" St. 39p P/P on any Tape 12p.

Jap Personal Ear Pieces. Large Plug 10p Post Paid.


Valve List Ex Equipment. All Valves Tested on a Mullard Valve tester before Despatched. 3 Months Guarantee on all Valves. Single Valves P/P 3p. Over three Valves P/P Paid.

ARP12	5p	PCC84	5p	U191	20p
EB91	4p	PCF80	5p	U251	12½p
EF85	12½p	PCL82	12½p	6BW7	10p
EF80	12½p	PCL83	12½p	6U4	10p
EF89	12½p	PCF82	12½p	6F23	20p
ECC81	10p	PL36	20p	20P1	20p
ECC82	12½p	PL81	17½p	20P3	10p
ECC83	12½p	PY81	7½p	20D1	10p
ECL80	7½p	PY33	17½p	30P4	20p
EF80	7½p	PY82	7½p	30P12	20p
EF91	4p	PL82	7½p	30FL1	20p
EY86	20p	PL83	7½p	6/30L2	20p
		PCL84	12½p		

## FANTASTIC BARGAIN OFFER!

# TRANSEUROPEAN

Transistorised Stereophonic High Fidelity  
AM FM Tuner Amplifier System.



This system includes this elegantly styled solid state Teak finished cabinet tuner/amplifier. Covering VHF/FM, Medium and long wavebands. The latest 4 Speed B.S.R. Mono/Stereo record changer with 2-10in. x 6in matching elliptical speakers. A complete Hi-Fi Stereo Radiogram at less than half normal price. **SPECIAL OFFER £44**  
P. & P. 88

Credit Terms available. First monthly payment of £5-83 followed by 9 monthly payments of £4-95. Total Credit Sale Price £49-50. Send £5-83 today.

### FABULOUS VALUE

Hi-Fi stereo at a new low. System Ten-Ten; 4 speed BSR autochanger with cue and pause control plus solid state amplifier, 20 watt total output. Frequency response 20-20,000 Hz. Two elliptical speakers in book shelf enclosures—100% complete.

**ONLY £4-93 DOWN** EASY TO INSTALL NO TECHNICAL KNOWLEDGE REQUIRED.

**CALLERS WELCOME** PLEASE SEND ME FREE DETAILS OF YOUR RANGE

Name .....  
Address ..... P11/71



**LEWIS radio** 100, Chase Side London N.14  
Tel: 01-886 3733/9666

# SEW PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES, ETC.  
 • LOW COST • QUICK DELIVERY • OVER 200 RANGES IN STOCK • OTHER RANGES TO ORDER

## NEW "SEW" DESIGNS!

### CLEAR PLASTIC METERS

**TYPE SW-100**  
100 x 80 mm.

50μA	...	\$3-47
50-500μA	...	\$3-74
100μA	...	\$3-37
100-100μA	...	\$3-25
500μA	...	\$3-12
1mA	...	\$3-97

20V. D.C. ... \$2-97  
 50V. D.C. ... \$2-97  
 300V. D.C. ... \$2-97  
 1 amp. D.C. ... \$2-97  
 5 amp. D.C. ... \$2-97  
 300V. A.C. ... \$2-97  
 VU Meter ... \$3-75

### BAKELITE PANEL METERS

**TYPE S-80**  
80 mm. square fronts

50μA	...	\$3-12
50-500μA	...	\$3-74
100μA	...	\$3-37
100-100μA	...	\$3-25
500μA	...	\$3-12
1mA	...	\$3-47
20V. D.C.	...	\$2-47

300V. D.C. ... \$2-47  
 50V. D.C. ... \$2-47  
 1 amp. D.C. ... \$2-47  
 5 amp. D.C. ... \$2-47  
 300V. A.C. ... \$2-47  
 VU Meter ... \$3-37

## "SEW" CLEAR PLASTIC METERS

**Type MR.52P. 4 1/4 in. fronts.**

50μA	...	\$2-60
100μA	...	\$2-60
500μA	...	\$2-60
1 amp.	...	\$2-60
5 amp.	...	\$2-60
15 amp.	...	\$2-60
30 amp.	...	\$2-60
20V. D.C.	...	\$2-60
50V. D.C.	...	\$2-60
150V. D.C.	...	\$2-60
300V. D.C.	...	\$2-60
10 amp. A.C.	...	\$2-60
300V. A.C.	...	\$2-60
S Meter 1mA	...	\$2-97
VU Meter	...	\$3-80
1 amp. A.C.*	...	\$2-60
5 amp. A.C.*	...	\$2-60
10 amp. A.C.*	...	\$2-60
20 amp. A.C.*	...	\$2-60
30 amp. A.C.*	...	\$2-60

**Type MR.52P. 1 1/2 3/8 in. square fronts.**

50μA	...	\$2-60
50-500μA	...	\$1-87
100μA	...	\$1-87
100-100μA	...	\$1-75
200μA	...	\$1-75
500μA	...	\$1-60
500-500μA	...	\$1-87
1mA	...	\$1-87
1-0-1mA	...	\$1-37
2mA	...	\$1-37
5mA	...	\$1-37
10mA	...	\$1-37
20mA	...	\$1-37
50μA	...	\$1-37
100μA	...	\$1-37
150μA	...	\$1-37
300V. A.C.	...	\$1-87
S Meter 1mA	...	\$1-87
VU Meter	...	\$2-10

**Type MR.52P. 2 1/4 in. square fronts.**

50μA	...	\$2-60
50-500μA	...	\$2-60
100μA	...	\$2-60
100-100μA	...	\$2-37
500μA	...	\$2-25
1mA	...	\$2-60
5mA	...	\$2-60
10mA	...	\$2-60
50μA	...	\$2-60
100μA	...	\$2-60
500μA	...	\$2-60
1 amp.	...	\$2-60

**Type MR.45P. 2 in. square fronts.**

50μA	...	\$1-50
50-500μA	...	\$1-50
100μA	...	\$1-50
100-100μA	...	\$1-50
200μA	...	\$1-50
500μA	...	\$1-50
500-500μA	...	\$1-50
1mA	...	\$1-50
5mA	...	\$1-50
10mA	...	\$1-50
50μA	...	\$1-50
100μA	...	\$1-50
500μA	...	\$1-50
1 amp.	...	\$1-50

## "SEW" BAKELITE PANEL METERS

**Type MR.55. 3 1/4 in. square fronts.**

50μA	...	\$1-75
1 amp.	...	\$1-75
5 amp.	...	\$1-75
15 amp.	...	\$1-75
30 amp.	...	\$1-75
50μA	...	\$1-75
100μA	...	\$1-75
5V. D.C.	...	\$1-75
10V. D.C.	...	\$1-75
20V. D.C.	...	\$1-75
50V. D.C.	...	\$1-75
300V. D.C.	...	\$1-75
15V. A.C.	...	\$1-75
30V. A.C.	...	\$1-75
150V. A.C.	...	\$1-75
300V. A.C.	...	\$1-75
S Meter 1mA	...	\$2-97
VU Meter	...	\$3-80
1 amp. A.C.*	...	\$2-60
5 amp. A.C.*	...	\$2-60
10 amp. A.C.*	...	\$2-60
20 amp. A.C.*	...	\$2-60
30 amp. A.C.*	...	\$2-60

## \*MOVING IRON—ALLOTTHERS MOVING COIL

Please add postage

### SEW EDUCATIONAL METERS

**Type ED.107.** Size overall 90mm x 103mm. A new range of high quality moving coil instruments ideal for school experiments and other bench applications. 3" mirror scale. The easily accessible to demonstrate internal working. Available in the following ranges:

50μA	...	\$4-50
100μA	...	\$4-50
1mA	...	\$4-25
50-500μA	...	\$4-55
1-0-1mA	...	\$3-97
1A d.c.	...	\$3-97
5A d.c.	...	\$3-97
10V d.c.	...	\$3-97

20V d.c. ... \$3-97  
 50V d.c. ... \$3-97  
 300V d.c. ... \$3-97

Dual range  
 500mA/5A d.c. \$4-25  
 5V/50V d.c. ... \$4-25

### EDGWISE METERS

**Type PE.70.** 3 17/32 in. x 1 15/32 in. x 2 1/2 in. deep.

50μA	...	\$3-00
50-500μA	...	\$3-00
100μA	...	\$2-97
100-100μA	...	\$2-75
200μA	...	\$2-75
500μA	...	\$2-60
1mA	...	\$2-37
10μA	...	\$2-37
100μA	...	\$2-37
300V. A.C.	...	\$2-37
VU Meter	...	\$2-25

### TE-40 HIGH SENSITIVITY A.C. VOLTMETER

10 meg. input 10 ranges: 01/-003/1/-3/1/3/10/30/100/300V. R.M.S. 4cps.-1-2 Mc/s. Decibels -40 to +60dB. Supplied brand new complete with 500mA leads and instructions. Operation 230V. A.C. \$17-50. Carr. 25p.

### TE-45 VALVE VOLTMETER

High quality instrument with 28 ranges. D.C. volts 1-5-1,000. A.C. volts 1-5-1,000V. Resistance up to 1,000 megohms. 200/240V. A.C. operation. Complete with probe and instructions. \$17-50. P. & P. 30p. Additional probes available. R.P. \$2-12; H.V. \$2-50.

# MULTIMETERS For EVERY purpose!

**TECH PT-3A.** 1,000 O.P.V. 0/10/50/250/500/1,000V. A.C. and 1V. C. 0/1/10/50/100. D.C. 0/100K. \$1-97. P. & P. 12tp.

**MODEL TE-200.** 20,000 O.P.V. Mirror scale, overload protection. 0/5/25/125/1,000 V.D.C. 0/10/50/250/1,000 V.A.C. 0/50 uA/250 mA. 0/60K/75 meg. Ω. -20 to +62 db. \$3-75. P. & P. 15p.

**MODEL TE-70.** 30,000 O.P.V. 0/3/15/30/60/120/200V. D.C. 0/6/30/120/600/1,200V. A.C. 0/300mA/3/30/300mA. 0/16K/160K/1.6M/16 Meg Ω. \$5-50. P. & P. 15p.

**MODEL TE-12.** 20,000 O.P.V. 0/0.6/3/6/30/120/600/1,200/3,000/6,000V. D.C. 0/6/30/120/600/1,200V. A.C. 0/60μA/0/600/600K/6 Meg Ω. 0.2mFd. \$5-97. P. & P. 17tp.

**MODEL PL436.** 20kΩ/Volt D.C. 8kΩ/Volt AC. Mirror scale. 0/3/12/30/60/120/200V. D.C. 3/30/120/600V. A.C. 50/600uA/60/600 mA. 10/100K/1 Meg/10 Meg Ω. -20 to +46db. \$5-97. P & P 12tp

**MODEL 500.** 30,000 O.P.V. with overload protection. Mirror scale. 0/5/25/50/100/250/500/1,000V. D.C. 1/2-5/10/25/100/250/500/1,000V. A.C. 0/50μA/5/50/500mA. 12 amp. D.C. 0/60K/75 Meg./80 Meg Ω. \$3-87. Post paid.

**TKM MODEL TW-300B FEATHERS RESISTANCE OVERLOAD PROTECTION.** 20K Ω/Volt D.C. 5K Ω/Volt A.C. D.C. Volts: 0-0.5, 2.5, 10, 50, 250, 1,000V. A.C. Volts: 0-2.5, 10, 50, 250, 1,000V. D.C. Currents: 0-0.05, 0.5, 5, 50, 500mA. Resistance: 0-5K, 50K, 0-500K. 5 MEG Ω. Decibels: -20 to +52 db. \$11-50. P. & P. 17tp.

**TKM LAB TESTER.** 100,000 O.P.V. 6 1/2 in. Scale Buzzer 50cps. Circuit Check. Sensitivity: 100,000 O.P.V. D.C. 5K Ω/Volt A.C. D.C. Volts: 5, 2.5, 10, 50, 250, 1,000 V. 50, 250, 500, 1,000V. D.C. Current: 10, 100uA, 10, 100, 500mA, 2.5, 10 amp. Resistance: 1K, 10K, 100K, 10MEG, 100 MEG Ω. Decibels: -10 to 49 db. Plastic Case with Carrying Handle. Size 7 1/4 in. x 6 1/4 in. \$18-90. P. & P. 25p.

**27° WIDE ANGLE 1mA METERS**  
 MW1-6 60mm square \$3-97  
 MW1-8 80mm square \$4-97  
 P. & P. extra

**TE-40 HIGH SENSITIVITY A.C. VOLTMETER**  
 10 meg. input 10 ranges: 01/-003/1/-3/1/3/10/30/100/300V. R.M.S. 4cps.-1-2 Mc/s. Decibels -40 to +60dB. Supplied brand new complete with 500mA leads and instructions. Operation 230V. A.C. \$17-50. Carr. 25p.

**TE-45 VALVE VOLTMETER**  
 High quality instrument with 28 ranges. D.C. volts 1-5-1,000. A.C. volts 1-5-1,000V. Resistance up to 1,000 megohms. 200/240V. A.C. operation. Complete with probe and instructions. \$17-50. P. & P. 30p. Additional probes available. R.P. \$2-12; H.V. \$2-50.

**HONOR TE.10A.** 20k Ω/Volt 5/25/50/250/500/2,500 V. D.C. 10/50/100/500/1,000 V. A.C. 0/50μA/2.5mA/250mA. D.C. 0/6K/75 meg. ohm. -20 to +62 db. 1-0-100 mfd. 0.100-0.1 mfd. \$3-47. P. & P. 15p.

**TKR MODEL WD.120**  
 Mirror scale, 20kΩ/Volt D.C. 10kΩ/Volt A.C. 30/60/300/600/3,000 V. D.C. 6/120/1,200 V. A.C. Current 0-600uA/0-12/100mA. 0-60K/0-6 Mohms -20 to +63 db. \$4-82. P & P 15p

**MODEL TE-90.** 50,000 O.P.V. Mirror scale, overload protection. 0/3/12/30/60/120/200 V. D.C. 0/6/30/120/600/1,200 V. A.C. 0.5/6/60/600mA. D.C. 16K/160K/1.6/16 MEG Ω. -20 to +63 db. \$7-50. P. & P. 15p.

**SKYWOOD SW-500**  
 50K Ω/Volt. Mirror scale. DC Volts 0/5/12/30/60/120/200/300/600V. DC Current 200mA/8/600mA. Resistance 10K/100K/1 Meg/10 Meg. Decibels -20 to +67 db. \$7-50. P. & P. 15p.

**MODEL AS-100D.** 100K Ω/Volt. 5in. mirror scale. Built-in meter protection 0/3/12/60/120/300/600/1,200 V. D.C. 0/6/30/120/600/600V. DC Current 200mA/12 Amp. 0/2K/200K/2M/200M Ω. -20 to +17 db. \$12-50. P. & P. 17tp.

**TE-90 20,000 Ω/VOLT GIANT MULTIMETER.** Mirror scale and overload protection. 5in. full view meter. 2 colour scale. 0/2/5/10/250/1,000/5,000 V. A.C. 0/25/125/10/50/250/1,000/5,000 V. D.C. 0/50mA/10/100/500mA/5 amp. D.C. 0/2K/200K/20 MEG. OHM. \$15. P. & P. 25p.

**FTC-401 TRANSISTOR TESTER**  
 Full capabilities for measuring A, B and I.C.O. NPN or PNP. Equally adaptable for checking diodes. Supplied complete with instructions, battery and leads. \$8-97. P. & P. 15p.

**HONEYWELL DIGITAL VOLTMETER VT.100**  
 Can be panel or bench mounted. Basic meter measures 1 volt D.C. but can be used to measure a wide range of AC and DC volt, current and ohms with optional plug in cards. Specification: Accuracy: ± 0.2, ± 1 digit. Resolution: 1mV. Number of digits: 8 plus fourth overrange digit. Overrange: 100% (up to 1,000) input impedance: 1000 Meg ohm. Measuring cycle: 1 per second. Adjustment: Automatic zeroing, full scale adjustment against an internal reference voltage. Overload: to 100V. D.C. Input: Fully floating (3 poles). Input power: 110-230V. A.C. 50/60-cycles. Overall size: 8 1/4 in. x 2 13/16 in. x 8 1/16 in. AVAILABLE BRAND NEW AND FULLY GUARANTEED AT APPROX. HALF PRICE \$49-97 1/2 Carr. 50p.

**G. W. SMITH & CO (RADIO) LTD.**  
 Also see next two pages

# SEMI-CONDUCTORS VALVES

ALL DEVICES COME BRAND NEW AND FULLY GUARANTEED

Transistors		2N3415	2N3416	2N3417	2N3549	2N3550
2G801	20p	2N3416	2N3417	2N3418	2N3550	

Integrated Circuits		FJH101	FJH111	FJH121	FJH991	FJH1001
CA3000	180p	FJH101	FJH111	FJH121	FJH991	FJH1001

VALVES		6AQ5	6BE6	6BE7	6BE8	6BE9	6BE10	6BE11	6BE12	6BE13	6BE14	6BE15	6BE16	6BE17	6BE18	6BE19	6BE20	6BE21	6BE22	6BE23	6BE24	6BE25	6BE26	6BE27	6BE28	6BE29	6BE30	6BE31	6BE32	6BE33	6BE34	6BE35	6BE36	6BE37	6BE38	6BE39	6BE40	6BE41	6BE42	6BE43	6BE44	6BE45	6BE46	6BE47	6BE48	6BE49	6BE50	6BE51	6BE52	6BE53	6BE54	6BE55	6BE56	6BE57	6BE58	6BE59	6BE60	6BE61	6BE62	6BE63	6BE64	6BE65	6BE66	6BE67	6BE68	6BE69	6BE70	6BE71	6BE72	6BE73	6BE74	6BE75	6BE76	6BE77	6BE78	6BE79	6BE80	6BE81	6BE82	6BE83	6BE84	6BE85	6BE86	6BE87	6BE88	6BE89	6BE90	6BE91	6BE92	6BE93	6BE94	6BE95	6BE96	6BE97	6BE98	6BE99	6BE100
6AK5	25p	6AQ5	6BE6	6BE7	6BE8	6BE9	6BE10	6BE11	6BE12	6BE13	6BE14	6BE15	6BE16	6BE17	6BE18	6BE19	6BE20	6BE21	6BE22	6BE23	6BE24	6BE25	6BE26	6BE27	6BE28	6BE29	6BE30	6BE31	6BE32	6BE33	6BE34	6BE35	6BE36	6BE37	6BE38	6BE39	6BE40	6BE41	6BE42	6BE43	6BE44	6BE45	6BE46	6BE47	6BE48	6BE49	6BE50	6BE51	6BE52	6BE53	6BE54	6BE55	6BE56	6BE57	6BE58	6BE59	6BE60	6BE61	6BE62	6BE63	6BE64	6BE65	6BE66	6BE67	6BE68	6BE69	6BE70	6BE71	6BE72	6BE73	6BE74	6BE75	6BE76	6BE77	6BE78	6BE79	6BE80	6BE81	6BE82	6BE83	6BE84	6BE85	6BE86	6BE87	6BE88	6BE89	6BE90	6BE91	6BE92	6BE93	6BE94	6BE95	6BE96	6BE97	6BE98	6BE99	6BE100

← See previous page • G. W. SMITH & Co. (RADIO) LTD. • See opposite page →



# HI-FI EQUIPMENT

SAVE UP TO  
**33 1/3% OR MORE**  
SEND S.A.E. FOR  
DISCOUNT PRICE LISTS  
AND PACKAGE OFFERS!



## RECORD DECKS

B.S.E. Mini Mono†	\$4-97
CI28†	\$8-70
MP60	\$11-80
510	\$15-15
310	\$10-55
MP60 T.P.D.I.	\$18-75
MP60 T.P.D.2	\$17-55
610 T.P.D.I.	\$22-12
510 T.P.D.I.	\$20-19
210 Package*	
H.T.70	\$11-80
H.T.70 Package	\$24-00
THORENS TD125	\$59-65
TD125AB	\$94-25
TX25	\$6-70
TD150AYI	\$34-80
TD150ABII	\$41-35
TX11	\$5-77



GARRARD 40 II*	\$8-40
2025 T/C*	\$8-50
3500*	\$9-75
SP25 III	\$10-95
A70 II	\$11-97
SL65B	\$14-40
AP76	\$18-95
SL72B	\$25-00
SL75B	\$27-50
SL95B	\$37-00
401	\$38-40
GOLDBRING GL69/2	\$21-25
GL75/2	\$23-50
GL75	\$29-97
GL75P	\$38-50
LD169/75	\$3-40
G99	\$8-97
PIONEER PL12AC	\$38-50

† Mono \* Stereo Cartridge  
All other models less Carriage  
Carriage 50p extra any model.


## RECORD DECK PACKAGES

Decks supplied ready wired in plinth and cover fitted with cartridge. Garrard 2025 T/C with Sonotone 9TAHCID- \$13-95  
Garrard SP25III with 9TAHCID- \$18-95  
Garrard AP76 Goldring G800.... \$29-85  
B.S.E. MP60 Audio Technica AT 55... \$21-00  
Goldring GL69/2 Goldring G500... \$37-50  
Goldring GL75 Goldring G800.... \$42-50  
Goldring GL75 Goldring G800E.... \$46-85  
Carriage 50p extra any model.



## SINCLAIR EQUIPMENT

Project 60. Package offers.

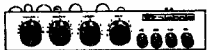

2 x Z30 amplifier, stereo 60 pre-amp, P25 power supply. \$18-75 Carr. 37p. Or with P26 power supply \$18-85 Carr. 37p. 2 x Z30 amplifier, stereo 60 pre-amp, P28 power supply. \$20-25 Carr. 37p.  
Transformer for P28. \$2-97 extra.  
Add to any of the above \$4-87 for active filter unit and \$13-90 for pair of Q16 speakers.  
Project 60 FM Tuner \$20-25. Carr. 37p.  
NEW PROJECT 605 \$20-97 Carr. 37p.  
All other Sinclair products in stock.  
2000 Amp \$24-50 Carr. 37p.; 3000 Amp \$24-50 Carr. 37p.; Neoteric Amp \$45-97 Carr. 37p.  
IC10/IC12 \$2-50  
NEW PROJECT 605 — \$20-97. Carr. 37p.


## LATEST CATALOGUE



SEND NOW!  
•  
STILL ONLY  
**37 1/2 p**  
P & P  
10p

Our new 6th edition gives full details of a comprehensive range of HI-FI EQUIPMENT, COMPONENTS, TEST EQUIPMENT and COMMUNICATIONS EQUIPMENT. FREE DISCOUNT COUPONS VALUE 50p 272 pages, fully illustrated and detailing thousands of bargains.

## TELETON SAQ-206 STEREO AMPLIFIER

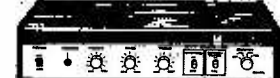

Latest exciting release. Brand new model. 6 + 6 watts rms. Inputs for mag, xtal, aux tape. Volume, bass, treble, sliding balance, scratch filter and loudness controls. List \$22.50 OUR PRICE \$18-50 Carr. 37p.

## TELETON SPECIAL OFFER I



CRIOI AM/FM STEREO TUNER AMPLIFIER WITH MATCHING PAIR OF SPEAKER SYSTEMS. Output 4 watts per channel. Excellent reception, AFC, built-in MPX. Car/XTAL Input. Total List \$50-25. OUR PRICE \$29-75. Carr. 62p.  
Also available with Garrard 2025T/C Record Changer, Plinth, cover and stereo cartridge. Ready wired \$36-50. Carr. \$1-00.

## ★ TRANSIORISED FM TUNER

6 TRANSIORISED HIGH QUALITY TUNER. SIZE ONLY 6x4x2 1/4in. 3 I.F. stages. Double tuned discriminator. Ample output to feed most 88-108Mc/s. Ready built ready for use. Fantastic value for money. \$8-87. P. & P. 12p.  
Stereo multiplex adaptors \$4-97.



## TE-108B STEREO HEADPHONES

Low cost high performance stereo headphones. Foam rubber ear cups. Adjustable head-band. 8 ohm impedance. 25-18,000 Hz. With lead and stereo jack plug. ONLY \$1-97. P. & P. 12p



## BELCO DA-20 SOLID STATE DECADE AUDIO OSCILLATOR

New high quality portable instrument. Sine 1 Hz to 100 KHz. Square 20 Hz to 20 KHz. Output max +10 dB (10 K ohms). Operation 220/240V. A.C. Size 216mm x 150mm x 120mm. Price \$27-50. Carr. 25p.

## TE-20 RF SIGNAL GENERATOR

Accurate wide range signal generator covering 120 kc/s-200 Mc/s on 6 bands. Directly calibrated variable R.F. attenuator. Operation 200/240V a.c. Brand new with instructions. \$15. P. & P. 37p. S.A.E. for details.




## B.C. 221 FREQUENCY METERS

latest release 125 KHz-20 MHz. Excellent condition. Fully tested and checked and complete with calibrator charts. \$27-50 each. Carr. 50p.


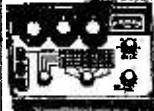
## TRANSIORISED L.C.R. A.C. MEASURING BRIDGE



A new portable bridge offering excellent range and accuracy at low cost. Ranges: R. 1Ω-11.1 meg Ω. C. Ranges ± 1% L. 1 μF to 11 μF. HENRY'S 6 Ranges ± % C. 10 pF to 1110 nF. D. 6 Ranges ± 2%. TURN'S RATIO 1:1/1000-1:11100. 6 Ranges ± 1%. Bridge voltage at 1,000 cps. Operated from 9 volts. 100 μA. Meter indication. Attractive 2 tone metal case. Size 7 1/2 x 5 x 2in. \$20. P. & P. 25p




TE-16A Transistorised Signal Generator. 5 ranges 400KHz-30MHz. An inexpensive instrument for the handyman. Operates on 9V battery. Wide easy to read scale. 800KHz modulation. 5 1/2 x 5 1/2 x 3 1/2in. Complete with instructions and leads. \$7-97. P. & P. 20p.

LAFAYETTE TE-46 RESISTANCE CAPACITY ANALYSER  
2 pF-2000 mF D 2 ohms 200 megohms. Also checks impedance, turns ratio, insulation, 200/250V. A.C.  
Brand New  
Carr. 37p



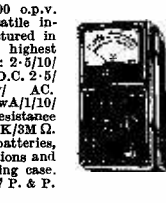
## RUSSIAN 22 RANGE MULTIMETER

Model U437 20,000 o.p.v. A first class versatile instrument manufactured in U.S.S.R. to the highest standards. Ranges: 2.5/10/50/250/500/1000V D.C. 2.5/10/50/250/500/100V AC. DC Current 100 μA/1/10/100mA/1A. Resistance 300 ohms/300/300K/2M Ω. Complete with batteries, test leads, instructions and sturdy steel carrying case. OUR PRICE \$5-97 P. & P. 25p.


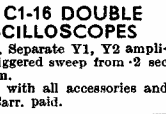
## RUSSIAN C1-16 DOUBLE BEAM OSCILLOSCOPES

5 MHz Pass Band. Separate Y1, Y2 amplifiers. Calibrated triggered sweep from -2 sec to 100 mill sec/cm. Supplied complete with all accessories and instructions \$37. Carr. paid.




## TEII. DECADE RESISTANCE ATTENUATOR

Variable range 0-111dB. Connections, Unbalanced T and Bridge T. Impedance 600 Ω range (0.1B x 10) + (1dB x 10) + 10 + 20 + 30 + 40dB. Frequency: d.c. to 200KHz (-3dB). Accuracy: ±0.05dB. +Indicator. ±B x 0.01. Maximum input less than 4W (50V). Built in 600 Ω load resistance with internal/external switch. Brand new. \$27-50. P. & P. 25p.


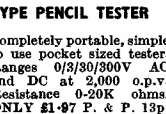
## ROUND SCALE TYPE PENCIL TESTER

MODEL TS-68 Completely portable, simple to use pocket sized tester. Ranges 0/30/300/300V AC and DC at 2,000 o.p.v. Resistance 0-20K ohms. ONLY \$1-97 P. & P. 13p.





## POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range extract. Single hole fixing. 1/2in. dia. shafts. Bulk quantities available. 25 WATT. 1/5/10/25/50/100/250/500/1000/1500/3500 or 5000 ohms. 72p. P. & P. 7p.  
50 WATT. 1/5/10/25/50/100/250/500/1000/2500 or 5000 ohms. \$1-05 P. & P. 7p.  
100 WATT. 1/5/10/25/50/100/250/500/1000 or 2500 ohms. \$1-37 P. & P. 7p.
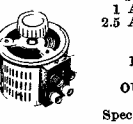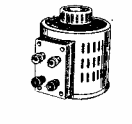
## "YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS

Excellent quality. Low price. Immediate delivery  
B-260 General Purpose Bench Mounting \$5-50  
1 Amp \$8-75  
2.5 Amp \$8-82  
Please add postage  
ALL MODELS INPUT 230 VOLTS, 50/60 CYCLES, OUTPUT VARIABLE 0-280 V. I.T.S.  
Special discounts for quantity



# G.W. SMITH & CO. (RADIO) LTD

27 TOTTENHAM CT. RD. LONDON, W.1 Tel: 01-636 3715  
3 Lisle Street, London, W.C.2 Tel: 01-437 8204  
34 Lisle Street, London, W.C.2 Tel: 01-437 9155  
311 EDGWARE ROAD, LONDON, W.2 Tel: 01-262 0387  
OPEN 3-6 MONDAY TO SATURDAY

All Mail Orders to:  
11-12, Redington Green,  
London, W.2  
Tel: 01-742 5582  
(Trade supplied)




# CASCADENT

**MAIL ORDER DEPARTMENT**  
No. 11 Mayes Rd., London, N22 6TL

## RADIO LTD

### BARGAIN COMPUTER BUMPER BOARDS

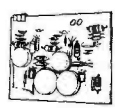

Many Resistors, Condensers, Diodes and Transistors (minimum of 4 transistors on each board).  
**5 BOARDS FOR 120p.**  
Post Free.

### BLACK TERMINALS



Length as indicated 1 inch  
10p per pair P. & P. 3p.

### BATTERY ELIMINATOR

Plug your Transistor Radio, Amplifier, Cassette, etc., into the a.c. mains through this compact eliminator. 2 1/2in x 2in x 3in approx. 41V £1.50, 6V £1.50, 9V £1.50, 7 1/2V complete with cable and plug for Philips Cassette. **£2** plus 8p P. & P. each.




**SEND S.A.E. FOR GREAT BARGAINS IN MICROPHONES, AMPS, DECKS, COMPLETE DISCOTHEQUE CONSOLS, SPEAKERS AND MANY OTHER ITEMS**

## BRANCHES

11e 40 MAYES RD LONDON N22 888 3206  
13 SOUTH MALL EDMONTON GREEN LONDON N9 803 1685

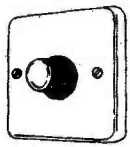
### LIGHT DIMMER

The unit comes complete with MK Ivory Front Plate and Control Knob, when used in place of Light Switch it will control your room lighting from off to full brightness. Power—up to 300 watts interference suppressed.  
**£2.75** P. & P. 8p


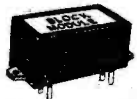
### SOLID STATE BLOCK MODULES

Phono pre-amp E1311 input 100k: gain 28dB max out 3 volt: max input 50mV. Tape pre-amp as above E1313. Power amp E1314 input 1,000 ohms gain 20dB 300mW. Organ tone osc E1315 tone freq. 200-1k. Hz output 80mV. All above modules 9 volt. Dual flasher E1318 flash time 1-4 secs power 6 volt. Lamp 6v 150mA. All at **£1.25** P. & P. 10p



### D.P.D.T. SLIDE SWITCH



SIZE  
1 1/2 ins long & wide  
**13p**  
3p Postage

### Transformer Scoop



Primary 220, 250 v. fused. Secondary 220 v. at 60mA, 6.3v. at 1 amp. Overall size 2 1/2" x 2" x 2 1/2" high. **63p** each. P. & P. 15p.

### COMPONENT CENTRE

8 x 6 Printed circuit board	10p each
By 100 Type rectifier 800 Flv 750 mA	18p
4 Pin transistor holders	8p
2 1/2 8 ohm speaker	33p
U2 Battery holders	5p
100HM W/W Pots	18p
OC81 Heat clips (double)	8p
Tape rev counters	35p
1,500mF 150V DC 4" x 2" dia approx	40p
Flex connector 2amp approx non-reversible	35p
Ideal for loudspeaker connections	8p
2 1/2 80 ohm Speaker	38p

Please include Post & Packing  
Send S.A.E. for return of post quote of your electronic project.


### CHROMOSONIC SOUND OPERATED LIGHT DISPLAY

This compact unit (size 8 1/2" x 5 1/2" x 3" high) is connected directly across the speaker output of an amplifier, it will then convert audio signals into a spectacular three colour light display (500 watts light output each colour). Send S.A.E. for further details or call in at any branch for demonstration.  
**£18.50** P. & P. 33p



## 100 WATT

### HIGH POWER AMPLIFIER

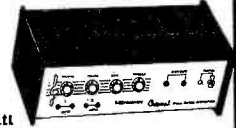

- In excess of 100 watt peak output
- Open and short circuit proof
- Sensitivity 10mV for full output
- Frequency Response 10-25,000Hz
- Safe with all loudspeaker systems 4 to 16 ohms
- Silicon transistors used throughout
- F.E.T. Front end

Send S.A.E. for further details.  
**£42.00** if purchased with light unit above **£40.00**  
Post and Insurance **£1.00**.  
**GUARANTEED 12 MONTHS**

### DWELL TIME UNIT


These small units contain the following components: 700 ohm DPDT relay with base, 1µF 250v. paper, 0.01µF 400v. paper, 50µF 35v. electrolytic, 3 diodes OC200 transistor, a 2N929 type transistor unmarked, a skeleton pre-set pot, 4 pin dim plug & skt., 4 foot of 4 core screen. All housed in a small neat metal box. Can be made into many timing devices. **43p** P. & P. 8p



## PRINTED CIRCUIT KIT

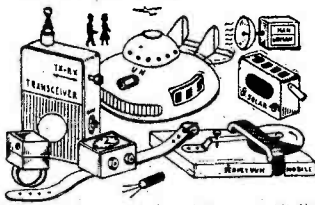**BUILD 50 INTERESTING PROJECTS ON A PRINTED CIRCUIT CHASSIS WITH PARTS AND TRANSISTORS FROM YOUR SPARES BOX**

CONTENTS: (1) 2 Copper Laminate Boards 4 1/2" x 2 1/2". (2) 1 Board for Match-box Radio. (3) 1 Board for Wristwatch Radio, etc. (4) Resist. (5) Resist. Solvent. (6) Etchant. (7) Cleaner/Degreaser. (8) 16-page Booklet *Printed Circuits for Amateurs* (9) 2 Miniature Radio Dials SW/MW/LW. Also free with each kit. (10) Essential Design Data, Circuits, Chassis Plans, etc. for 50 TRANSISTORISED PROJECTS. A very comprehensive selection of circuits to suit everyone's requirements and constructional ability. Many recently developed very efficient designs published for the first time, including 10 new circuits.



### EXPERIMENTERS PRINTED CIRCUIT KIT 60p


Postage & Pack. 10p. (U.K.)  
Commonwealth:  
SURFACE MAIL 20p  
AIR MAIL 60p  
Australia, New Zealand,  
South Africa, Canada

- Crystal Set with biased Detector.
- Crystal Set with voltage-quadrupler detector.
- Crystal Set with Dynamic Loudspeaker.
- Crystal Tuner with Audio Amplifier.
- arter Power Conversion Receiver.
- Split-Load Neutralised Double Reflex.
- Matchbox or Photocell Radio.
- "TRI-FLEXION" Triple Reflex with Self-adjusting regeneration (Patent Pending).
- Solar Battery Loud-speaker Radio.
- The smallest 3 designs yet offered to the Home Constructor anywhere in the World.
- 3 Miniature Radio Receivers based on the "Triflexion" circuit. Let us know if you know of a smaller design published anywhere.
- Postage Stamp Radio. Size only 1-62" x .95" x .25".
- Wristwatch Radio 1-15" x .80" x .55".
- Ring Radio 70" x 70" x .55".
- Bacteria-powered Radio. Runs on sugar or bread.
- Radio Control Tone Receiver.
- Solar Battery Loud-speaker Radio.
- Intercom.
- 17-valve Amplifier.
- Reliable Burglar Alarm.
- Light-Seeking Animal, Guided Missile.
- Perpetual Motion Machine.
- Metal Detector.
- Transistor Tester.
- Human Body Radiation Detector.
- Man/Woman Discriminator.
- Signal Injector.
- Pocket Transceiver (Licence required).
- Constant Volume Intercom.
- Remote Control of Models by Induction.
- Inductive-Loop Transmitter.
- Pocket Triple Reflex Radio.
- Wristwatch Transmitter/Wireless Microphone.
- Rain Alarm.
- Ultrasonic Switch/Alarm.
- Stereo Preamplifier.
- Quality Stereo Push-Pull Amplifier.
- Light-Beam Telephone "Photophone".
- Light-Beam Transmitter.
- Silent TV Sound Adaptor.
- Ultrasonic Transmitter.
- Thyratron Drill Speed Controller. . plus 10 Photo-electric Circuits, Alarms, Modulators, Stabilisers. . .

**YORK ELECTRICS, Mail Order Dept.**  
335 Battersea Park Road, London, S.W.11

Send a S.A.E. for full details, and a brief description of all Kits and Projects.

### MW/LW TRANSISTOR RADIO

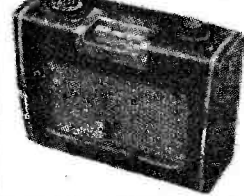

Complete set of parts for this MW/LW Transistor Radio. Originally sold by world-famous company as set for more than £17. Coverage 102-555m-1070-1570m 9 volt 6 transistor superhet using 3 AF117 in RF and IF stages powered by a two stage AF amplifier using 3 x AC128. Output approx. 500mW. Also works off car-serial. Full instruction book 19p free with parts. Red only, ply case, rexine covered. Requires PP7 battery, price 22p extra. 3 1/2in high-quality speaker. Price 26 plus 40p P. & P.

### STEREO AMPLIFIER Type SHV—2 x 3 watts

Fully built. Separate vol., base and treble controls each channel; 12 x 4 1/2 x 6in high. EZ60 and 2 x ECL86 valves. O.P. trans. for 8-ohm speakers. Double wound mains trans. Suitable for crystal, magn. cartridge, tuner, etc. with mono-stereo switch. 200-250V a.c. mains. £7.25, 50p P. & P.



A.M./F.M. (V.H.F.) tuning gang / 3 x 2 x 1 1/2in plus spindle 1/8in (1/8in dia.) 400 + 180 + 20 + 20pt; geared slow motion drive 6:1; no back lash; cast frame; Brand new; German 3 x 4b.a. fixings. 35p post pd. less 10% for 6.

### MAINS TRANSFORMERS (240-250V input)

Postage in brackets  
6.3V at 2 1/2A, 40p (15p).  
250V at 50mA and 6.3V at 1 1/2A, 50p (20p).  
23V at 1A, 6.3V at 2A and 250V at 50mA, 75p (25p).  
90V at 20mA and 1.4V at 250mA, 50p (15p).  
Deduct 10 per cent from total bill for more than one transformer.



Miniature A.M. transistor tuning gang. 250 + 250pt; 2 x 6b.a. fixings, size 1 1/2 x 1 1/2 x 1in; gearing 3:1 to 1/8in dia. moulded bush. Plastic dust cover; Plessey. 25p post pd., less 10% for 6.

## GLADSTONE RADIO

66 ELMS ROAD, ALDERSHOT, Hants  
(2 mins. from Station and Buses). FULL GUARANTEE. Aldershot 29240  
CLOSED WEDNESDAY. S.A.E. for enquiries please.

BRAND NEW GUARANTEED

SEMICONDUCTORS & COMPONENTS

RETURN OF POST SERVICE

SOLE AGENTS FOR SOLID STATE DEVICES INC., (USA), IN U.K.

TRANSISTORS

Table of transistor part numbers and prices. Columns include part numbers (e.g., 2N3404), quantities, and prices.

TTL. LOGIC I.C. NEW PRICES

Table of TTL logic IC part numbers and prices. Columns include part numbers (e.g., SN7400), quantities, and prices.

MULLARD SUB-MIN ELECTROLYTIC

CA25 range axial lead. Values: (μF/V): 0.64/64; 1/40; 1.6/25; 2.5/16; 2.5/64; 4/10; 4/40; 5/64; 6.4/6.4; 6.4/25; 8/40; 10/16; 10/64; 12.5/25; 16/40; 20/16; 20/64; 25/6.4; 25/25; 32/10; 32/40; 40/16; 50/6.4; 50/25; 50/40; 64/10; 80/2.5; 80/16; 80/25; 100/6.4; 125/10; 125/16; 200/6.4; 200/10; 320/6.4.

SILICON RECTIFIERS

Table of silicon rectifier part numbers and prices. Columns include part numbers (e.g., PIV 50), quantities, and prices.

DIODES & RECTIFIERS

Table of diode and rectifier part numbers and prices. Columns include part numbers (e.g., IN34A), quantities, and prices.

TRIACS

Table of triac part numbers and prices. Columns include part numbers (e.g., SC33D), quantities, and prices.

BRIDGE RECTIFIERS

Table of bridge rectifier part numbers and prices. Columns include part numbers (e.g., A. PIV), quantities, and prices.

THYRISTORS

Table of thyristor part numbers and prices. Columns include part numbers (e.g., PIV 50), quantities, and prices.

MULLARD C280 M/FOIL CAPACITORS

Table of capacitor values and prices. Columns include values (e.g., 0.01, 0.022), quantities, and prices.

HEAT SINKS

Table of heat sink part numbers and prices. Columns include part numbers (e.g., 4.8 x 4 x 1/2), quantities, and prices.

WIRE-WOUND RESISTORS

Table of wire-wound resistor values and prices. Columns include values (e.g., 2.5 watt, 5%), quantities, and prices.

POTENTIOMETERS

Table of potentiometer part numbers and prices. Columns include part numbers (e.g., Carbon), quantities, and prices.

PRESETS (CARBON)

Table of preset part numbers and prices. Columns include part numbers (e.g., 0.1 Watt), quantities, and prices.

THERMISTORS

Table of thermistor part numbers and prices. Columns include part numbers (e.g., R53), quantities, and prices.

RESISTORS

Table of resistor part numbers and prices. Columns include part numbers (e.g., Carbon Film), quantities, and prices.

Post & Packing 12p per order. Europe 25p. Commonwealth (Air) 65p (MIN.). Matching charge (audio transformers only) 12p extra per pair. Prices subject to alteration without prior notice.

Send 5p for new Comprehensive Semiconductor and I.C. list (24 pages).

CALLERS WELCOME. HBS. 9-5.30 MON-FRI. 9-5.0 SAT. 9-1.0 THURS.

Tel. 01-452 0161/2/3 Telex 21492

A. MARSHALL & SON 28 CRICKLEWOOD BROADWAY, LONDON, N.W.2

## TELETON CRIOT AM/FM STEREO TUNER AMPLIFIER

Output 4w per channel, with pair of Matching speakers .....

**£26**

A complete stereo system comprising the above CRIOT tuner amplifier and pair of matching speakers, with Garrard 2020TC record player complete with plinth and cover, and ready wired.

L & M BARGAIN PRICE **£38-50**

## A COMPLETE STEREO SYSTEM SAVE OVER £30

L & M STEREO SYSTEM comprises: Garrard SP25 Mk. 3 Record Player with Goldring G800 Magnetic Cartridge. Complete with plinth and cover and ready wired TELETON SA0206 Amplifier and two full size 30in x 10in x 7 1/2in. internationally acclaimed Musette Speakers.

L & M BARGAIN PRICE **£65**

## STEREO HEADPHONES ONLY £2-25

Wonderful value and excellent performance combined. Adjustable headband. 8 ohm impedance. 20-12,000 eps. Complete with lead and stereo jack plug.

## GARRARD TURNTABLES

BRAND NEW & FULLY GUARANTEED

2025TC ..... £8-50 SL65B ..... £14-95  
SP25 Mk. 3 ..... £11 AP76 ..... £19  
Plinth and covers for the above fully assembled. **£2-75**

Also available: LM5 plinth which enables cover to be left in position when playing record, £4-95. Send S.A.E. for full price list.

## L & M SENSATIONAL BARGAIN

GARRARD SP25 Mk. 3 RECORD PLAYER with Goldring G800 magnetic cartridge complete with plinth and cover, ready wired



**£19-00**

Also Garrard AP76/G800 complete with plinth and cover, ready wired, £30-00

TELETON GA101 30 watt stereo amplifier, normally £37-50. Our Price **£25**.  
TELETON SAQ206 stereo amp. 12 watt, normally £32-50. Our Price **£18-50**.

NEW a design engineered METAL PLINTH beautifully styled brushed silver finish to match most equipment, supplied with tinted transparent perspex cover.

MLM6 Plinth and cover ..... £7-50  
MLM5 Plinth and cover ..... £9-50  
this is a larger plinth than MLM6 and can be used with record in position when playing record.  
MLM4 Plinth and cover ..... £9-50  
suitable for AP75, AP76, SL95, etc.



## TELETON F2000 AM/FM STEREO TUNER AMPLIFIER

OUR PRICE **£30-50**

## TAPE CASSETTES

No. C60, each 37 1/2p, 2 for 72 1/2p, 3 for £1-05.  
No. C90, each 60p, 2 for £1-15, 3 for £1-65.  
No. C120, each 87 1/2p, 2 for £1-27 1/2p, 3 for £1-80;

CASSETTE HEAD CLEANER, removes deposit<sup>s</sup> from tape heads. Non-abrasive. Fits all compact cassette recorders 60p.

ALL PRICES ARE CARRIAGE PAID, CREDIT FACILITY AVAILABLE

## L. & M. SUPPLIES

HAINAULT HOUSE, HAINAULT STREET, NEW ELTHAM, S.E.9.  
Telephone 01-850 0829.

CALLERS WELCOME. OWN CAR PARK. Dept. FW

## poly-planar

20-Watt Full Range Speaker

Completely replaces the conventional cone speaker



Super-thin construction permits new installation ideas.

Power capability: 20 watts peak  
Frequency range: 40 Hz-20 KHz  
Sensitivity: 85 dB/M for 1 watt electrical input  
Input impedance: 8 ohms  
Operating temperature range: -20°F to +175°F  
Size (WxDxL): 1-7/16" x 11-3/4" x 14-11/16"  
Weight: 19 ounces

£5.75 (p&p20p) each

Stereo pair £11, 40 post free

## web europa

P.O. Box 162 Bushey  
Watford WD2 1LF

## INCOMPARABLE V.H.F. KIT

Johnsons CV2—unique triple-purpose (Converter, Receiver, Tuner-Feeder) kit for the Amateur enthusiast. Fantastic transistorized performance, World Wide Sales. Complete kit of top grade parts with coils covering 80-180 mHz, plus easy/build diagrams and instructions. £4 direct from makers or S.A.E. for free literature.

**JOHNSONS (RADIO)**  
ST. MARTINS GATE WORCESTER  
Est. 1943 Tel. 24864

(A division of the G-BAN Organization)

## NEW VALVES!

Guaranteed and Tested  
24-HOUR SERVICE

1R5	28	DF91	14	EF86	29	PCL85	37
1R6	21	DF96	35	EF89	24	PCL86	38
1T4	14	DK91	26	EF91	12	PL200	52
384	28	DK92	27	EF183	28	PL36	47
3V4	27	DK96	26	EF184	28	PL81	48
5Y3GT	25	DL92	37	EL33	54	PL82	29
6J80L2	53	DL94	37	EL37	75	PL83	29
6AQ5	21	DL96	38	EL84	22	PL84	28
6BW7	50	DY86	24	EY86	28	PL500	29
6F1	20	DY87	24	EZ80	20	PL504	22
6F23	27	DY802	30	EZ81	22	PY81	24
6F25	25	EACB80	30	KT61	54	PY82	24
6SN7GT	28	EB91	10	KT66	75	PY800	32
26L6GT	20	EB93	38	N78	26	PY801	32
30C15	26	EBF89	27	PO86	45	R19	29
30C18	28	ECC81	15	PC88	45	U25	32
30F5	27	ECC82	18	PC97	38	U26	56
30FL1	29	ECC83	21	PC900	30	U191	59
30FL14	27	ECC85	24	PC84	28	U251	25
30L15	26	ECC90	28	PC89	48	U325	25
30L17	28	ECC92	26	PC189	47	U3F89	29
30P4	20	ECH35	27	PCF80	27	UC85	34
30P10	26	ECH31	26	PCF86	43	UCH81	30
30P11	20	ECL50	29	PCF801	29	UCL82	31
30PL13	27	ECL82	29	PCF802	40	UCL83	49
30PL14	28	ECL86	32	PCF805	29	U89	28
DAF91	21	EF30	36	PC182	30	UL84	29
DAF96	25	EF80	22	PCL83	55	UY85	24
DCC90	20	EF85	26	PCL84	33	Z77	18

Postage on 1 valve 5p, on 2 or more valves 3p per valve extra. Any parcel insured against damage in transit 3p extra. Office address, no callers.

**GERALD BERNARD**  
83 OSBLEDSTONE ROAD,  
STOKE NEWINGTON, LONDON, N.16

NEW 3in. SPEAKERS 15 ohms 75p, p. & p. 10p.

BARGAIN PARCELS 14lb at £1-45 plus 32 1/2p p.p.: 28lb at £2-75 plus 52 1/2p p.p.: 56lb at £4-50 plus £1-25 p.p. Contain pots, Res. Valves, Diodes, Tagboards, Chassis, Valveholders, etc. Good value save £££. Lucky Dip Service.

FANTASTIC BARGAIN. New 6 inch tubes. VCR 97. 4VH, medium Persistence, green 1KV BHT. Ideal scope tube. List price £5. Our price £1-40 carriage paid.

500 μ AMP METERS. Approx. 1 1/2" on panel with plug and switch ex new equip. 75p p. & p. paid.

NEW HEAVY COAX CABLE dia. 3/4" 70 ohms approx. 50ft. lengths £1-40, p. & p. 30p. 100 ft. lengths £2-70, p. & p. 50p.

VHF AERIAL TUNING UNITS consisting of the following: 1-1 1/2" 500 micro/ampmeter. 1 small 2-gang 75 PF capacitor. 1 various large wattage resistors for dummy load. Pair gears B.N.C. type sockets. Will tune 10 mtrs with 25/30 watts R.F. input. Size only 6 1/2" x 4 1/2" x 3" Sealed. Price £1-37 1/2 p.p. 25p

CRYSTALS AS NEW: Hc 6u, 5,345; 5,030; 5,005; 4,945; 4,875; 4,840; 4,795; 4,580; 4,660; 4,520; 4,510; 2,300; 2,295 Kc/s. 50p each plus 8p. p.p.

SCOOP PURCHASE OF BRAND NEW CARBON RESISTORS. 10% tolerance 1/2 & 1/4 watt. Preferred values in packets of 10. Our price 50p per 100, 50p per 200, £1-35 per 300, 50p at £2-12 1/2. Our selection. p.p. 8p per 100 and 2 1/2p per extra 100.

TRIMMER BARGAINS. These are 10PF sub-min. air-spaced trimmers on board with min. wire ended Xtal. Brand new. No details: Contents 12 trimmers, some ceramic caps. Xtal frequency 3RD overtone 249 mc/s-260 Mc/s, 255 Mc/s. No choice. Trimmers without Xtal—60p per doz. plus 17 1/2p p.p. Trimmers with Xtal—75p per doz. plus 17 1/2p p.p. Also 20 PF min. brand new air spaced. 50p per doz. plus 17 1/2p p.p.

ANY HEIGHT AERIAL TUBULAR SECTIONS 1/2" dia x 3 ft. long. Brass screw in type, copper coated and painted. Good condition. 20p, p. & p. 5p each. Minimum order 10.

BRAND NEW HARTLEY OSCILLOSCOPES CT816 in original packing. Band width up to 5 Mc/s. Mains supply. Price £40, p. & p. £1-50p.

AERIALS NEW CONDITION. Whip type 4ft. 25p, 11ft. 70p, 14ft. 77p. Used condition 4ft 20p, 14ft. 62 1/2p. All collapsible type. P. & p. 4ft. 10p, rest at 17 1/2p. Bases for above 25p, p. 12 1/2p. New matching unit coax connection for above 80p, p.p. 5p.

Huge release of valves for the 62 set TX/RX. In original rubber packing consisting of QV04/7 x 61M, ARP12 etc. 10 valves in all at the bargain price as seen 87 1/2p plus 17 1/2p p.p.

R209. Set of valves 62 1/2p, p.p. 25p.

New Headphone and Mike rubber muff type. Low impedance. 97 1/2p, p. & p. 17 1/2p.

NEW AERIAL WIRE ON BOARDS 7/2 UNCOVERED. 75ft. 40p, 90ft. 47 1/2p, 100ft 55p, 150ft. 75p, 180ft. 95p, 250ft. £1-30p, p. & p. 20p.

Headphones, ex Gov. DLR No. 5 low impedance. New 87 1/2p 17 1/2p p.p. Used condition 62 1/2p 17 1/2p p.p.

## MUIRHEAD DECADE A.F. SIGNAL GENERATOR

This precision instrument can be used:

1. To Measure Gain up to 50 db.
2. To Measure Loss up to 45 db.
3. To compare Power levels (A.F.).
4. As an Audio Frequency Generator covering 100 Hz to 41 kHz. With a dial setting accuracy of ±0.5 Hz. Output 1-1 M/W into 600 SL complete with mains power unit. Tested. Good Condition. £12, p. & p. 75p.

ENCLOSED AERIAL RELAY COIL. Res. 700 ohms approx. 25 watts RF BNC outlet, working voltage 12v. 75p, p. & p. 10p. £1 with BNC plugs.

Also 1 1/2" 75 ohm Coax in 50ft coils with BNC plugs good condition. Price £1 + 30p, p.p.

2 BNC plugs on short length coax cable large size low loss plugs 30p + 5p, p.p.

NEW BOXED AMP METERS 1 1/2" 20-0-20 dc. 65p. p. & p. 5p.

C.W.O. CARRIAGE CHARGES MAINLAND ONLY

## A. H. THACKER,

Radio Dept.,  
HIGH STREET, CHESLYN HAY,  
Nr. Walsall. Staffs.

# INCREASE YOUR KNOWLEDGE



Established 1891



**MANY COURSES TO CHOOSE FROM incl.**  
 RADIO & TV ENGINEERING & SERVICING,  
 TRANSISTOR & PRINTED CIRCUIT SERVICING,  
 COLOUR TV SERVICING, ELECTRONICS,  
 NUMERICAL CONTROL ELECTRONICS,  
 TELEMETRY TECHNIQUES, CONTROL SYSTEMS,  
 ELECTRONICS FOR AUTOMATION,  
 COMPUTERS, ETC.

**ALSO EXAMINATION COURSES FOR**

C. & G. Telecommunication Technicians' Certificates  
 Radio Operator Certificates  
 Radio Amateurs' Examination  
 General Certificate of Education, etc.

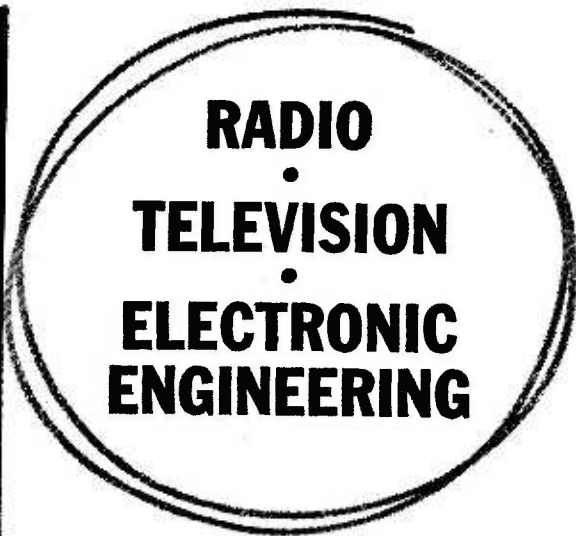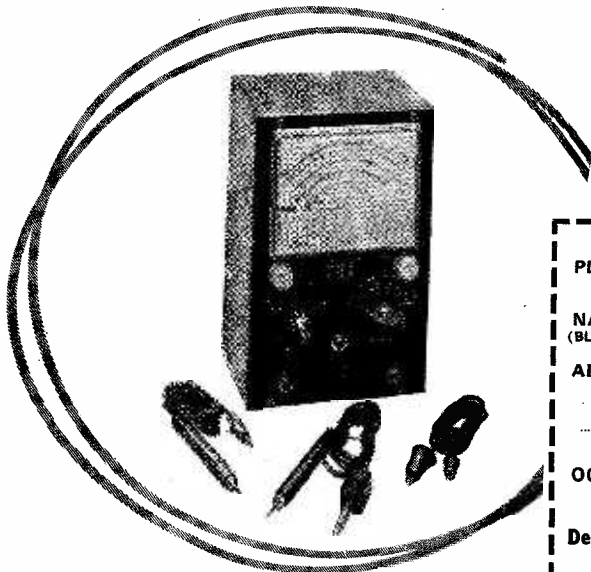**BUILD YOUR OWN RADIO AND INSTRUMENTS**

With an ICS Practical Radio & Electronics Course you gain a sound knowledge of circuits and applications as you build your own 5-valve Superhet Receiver, Transistor Portable, and high-grade test instruments (shown below). Everything simply explained. All components and tools supplied. For illustrated brochure, post coupon below.



**RADIO  
TELEVISION  
ELECTRONIC  
ENGINEERING**

MEMBER OF THE ASSOCIATION  
OF BRITISH CORRESPONDENCE COLLEGES

## THERE IS AN ICS COURSE FOR YOU

Whether you need a basic grounding, tuition to complete your technical qualifications, or further specialized knowledge, ICS can help you with a course individually adapted to your requirements.

There is a place for you among the fully-trained men. They are the highly paid men—the men of the future. If you want to get to the top, or to succeed in your own business, put your technical training in our experienced hands.

ICS Courses are written in clear, simple and direct language, fully illustrated and specially edited to facilitate individual home study. You will learn in the comfort of your own home—at your own speed. The unique ICS teaching method embodies the teacher in the text; it combines expert practical experience with clearly explained theoretical training. Let ICS help you to develop your ambitions and ensure a successful future. Invest in your own capabilities.

**FILL IN AND POST THIS COUPON TODAY**

You will receive the FREE ICS Prospectus listing the examination and ICS technical courses in radio, television and electronics PLUS details of over 150 specialized subjects.

PLEASE SEND FREE BOOK ON.....

NAME.....  
(BLOCK CAPITALS PLEASE)

ADDRESS.....

.....

OCCUPATION..... AGE.....

INTERNATIONAL CORRESPONDENCE SCHOOLS  
 Dept. 170, INTERTEXT HOUSE, STEWARTS ROAD, London, SW8 4UJ.

11/71

# Practical Wireless Classified Advertisements

The pre-paid rate for classified advertisements is 8½p per word (minimum 12 words), box number 7½p extra. Semi-displayed setting £6 per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent *registered post*. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd., Fleetway House, Farringdon Street, London, EC4A 4AD for insertion in the next available issue.

## Miscellaneous

### LIGHTWEIGHT TREASURE-PROBE

Look for BURIED COINS, silver, gold and metal relics PROFESSIONALLY with the BOFFIN solid-state TREASURE-PROBE. An extremely EASY-TO-BUILD kit that REALLY DOES WORK! SIMPLE-TO-FOLLOW INSTRUCTIONS. It comes to your doorstep with maximum-copper PRINTED-CIRCUIT BOARD plus ALL ELECTRONIC COMPONENTS including search-coil and earphone. Think of the fun you'll have BEACHCOMBING with the sensitive TREASURE-PROBE, and the expectancy of hearing its LOUD "BEEP" to tell you "YOU'RE ON TO SOMETHING" GET YOUR TREASURE-PROBE SEND £8-95 NOW!

### BOFFIN PROJECTS

4, CUNLIFF RD.  
STONELEIGH EWELL  
SURREY

Designed by GERRY BROWN & JOHN SALMON and presented on TV

### 12 VOLT FLUORESCENT LIGHTS



Beat Power Cuts, 12 ins 8 watt Tube, Ideal for Caravan, Tent, Emergency Lighting etc, Fully Transistorised, Low Battery Drain, With ON/OFF Switch and 12v Socket to Run other Lights or 12V Equipment.

Unbeatable at **£3.30** post paid  
or in kit form **£2.90**

SALOP ELECTRONICS Callers welcome  
23 Wyke Cop Shrewsbury, Shropshire S.A.E. for lists

### JOHN SAYS...

**RING MODULATOR** by Dewtron is professional, transformerless, 5-transistor, has adjustable F1/F2 rejection. Module £7. Unit £8-90. WAA-WAA Pedal kit of all parts, incl. all mechanics & instr. Only £2-45. **AUTO RHYTHM** from Dewtron modules. Simple unit for waltz, foxtrots etc. costs £16-95 in modules. **SYNTHESISER MODULES** and other miracles. Send 15p for illust. list. D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset.

**DAILY UFO** Flight Patterns, 37½p.. UFO Map, S. England, 37½p. TV Notes on UFO Detection, two Optical Circuits, 50p. UFO Wave Pattern and Prediction, 45p. R & P Publications, "Highlands," Needham Market, Suffolk.

**HEADPHONES** (Stereo) Diplomat Model by S. G. Brown, 10 pairs. Bargain £4-95 each. R.J.W. 27 Huxley Road, London, E.10. Tel. 01-556 8362.

**IRISH READERS.** Eagle products available, send 10p in stamps for latest illustrated catalogue to Toner Electronics, Lismore Park, Waterford.

**DO-IT-YOURSELF**... we stock a large range of audio and electronic components at very competitive prices, e.g.: chassis speakers, cross-over networks, hi-fi speaker kits (Wharfedale & Peerless), BAF sound absorbent, speaker grille fabrics, inductors, resistors, electrolytics (reversible and polarised), transistors, etc. Send for FREE list (2 x 3p stamps for fabric samples). Mail order ONLY. No callers please.

**AUDIOSCAN** Dept. PW11  
4, PRINCES SQUARE,  
HARROGATE, YORKS.

**BUILD IT** in a DEWBOX quality cabinet. 2in x 2½ in x any length. D.E.W. Ltd., Ringwood Road, FERN-DOWN, Dorset. S.A.E. for leaflet. Write now—Right now.

**RECORD TV SOUND** using our loud-speaker isolating transformer. Provides safe connection to recorder. Instructions included. 70p +10p P&P. CROWBOROUGH ELECTRONICS (P.W.), Eridge Road, Crowborough, Sussex.

### TAPE HEADS PICK-UP CARTRIDGES

**SERVICE MANUALS** for Pre 1958 H.M.V. and E.M.I. MODELS. Radio and Record Player Manuals 25p each. Television Manuals 37½p each. Send C.W.O. stating model required.

Send stamp for comprehensive lists of transformers, condensers, resistors, cartridges and tape heads.

R. D. I. LTD.,  
Chilton Works, Garden Road,  
Richmond, Surrey.

### SURPLUS

**NIXIE ZMI172** Mullard 95p, 4—£3-60.  
**TF144G** Sig. Gen. 85kHz-25MHz AM Mod 0-75% 1µV-1V £19-75 fully tested £2. p.&p.  
**TF428** Valve Voltmeter c/w spares £7-95  
£1 p.&p. 710076 Equip. Wire 500yd. £1-95, 100yd. 45p on reels BICC. **MANPACK BATTERIES**, separate 90v, 60v, 4/5v. high cap. 11" x 8" x 4" 75p, 20p p.&p. Mail order only. 123 Woodfield Green Dunstable 68515

### THE NEW

### ELECTRONIC MUSIC FOR YOU

Then how about making yourself an electric organ? Constructional data available—full circuits, drawings and notes! It has 5 octaves, 2 manuals and pedals with 24 stops—uses 41 valves. With its variable attack you can play Classics and Swing. Write NOW for free leaflet and further details to C. & S., 20 Maude Street, Darlington, Durham. Send 2½p stamp.

### SYNTHESISER MODULES

Send SAE for details of voltage-controlled modules for synthesiser construction to D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset.

### TOP TRANSISTORS

Brand New and Individually Tested Transistors supplied unmarked, but packed separately for identification and guaranteed to be within their correct specification or money refunded. All at 9p. each or

Any 25 transistors for only £1-90

ACY22	BFY51	OC72	2N3702
BC108	BFY52	OC202	2N3703
BC109	BSY27	ZTX300	2N3705
BC168	OC45	2N706	2N3706
BC169	OC71	2N2926	2N3708

Money back guarantee, P. & P. 10p.

J. M. KING (O)

17 Buckridge, Portpool Lane, London, E.C.1

### NO NEED TO WORRY ABOUT A TRANSMITTING LICENCE

because this GPO approved transmitter/receiver kit does not use R.F. and you can get one easily. Your transmissions will be virtually SECRET since they won't be heard by conventional means. Actually it's TWO KITS IN ONE because you get all the printed-circuit boards and components for both the transmitter AND receiver. You're going to find this project REALLY FUN-TO-BUILD with the EASY-TO-FOLLOW instructions. An extremely flexible design with quite an AMAZING RANGE—has obvious applications for HOUSE-TO-HOUSE USE, SCHOOL PROJECTS, LANGUAGE LABORATORIES, SCOUT CAMPS, etc.

GET YOURS! SEND £5-20 NOW

TO: 'BOFFIN PROJECTS'  
DEPT. KW2010  
4 CUNLIFFE ROAD  
STONELEIGH, EWELL, SURREY



Today's skies are full of exciting cross-talk as aircraft from giant jets to small private planes jostle to take off and land. Now you can eavesdrop on their tense conversations with this remarkable ready-to-use, fully-translat. batt. converter. Place it 1/2 way from any std. medium-wave radio (even tiny portable!) for crystal-clear reception on aircraft communications. Money back guarantee.

ONLY  
**£3-60**  
+15p PGP

**MARKTYME**  
(MAIL ORDER) LTD

DEPT. P.W.3  
72 WILLESDEN LANE  
LONDON, N.W.8  
01-624 4633



## Wanted

**WE BUY** New Valves and Transistors. State price: A.D.A. MANUFACTURING CO., 116 Alfreton Road, Nottingham.

**TOP PRICES PAID** for NEW VALVES. popular T.V. and Radio types.

**KENSINGTON SUPPLIES (C).**

367 Kensington Street, Bradford 8, Yorkshire.

**WE BUY** New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. **WALTON'S WIRELESS STORES**, 55 Worcester Street, Wolverhampton.

**CASH PAID** for New Valves. Payment by return. **WILLOW VALE, ELECTRONICS**, 4 The Broadway, Hanwell, London, W.7. 01-567/5400-2971.

**HIGHEST POSSIBLE** cash prices for Akai, B. & O., Brenell, Ferrograph, Revox, Sanyo, Sony, Tandberg, Uher, Vortexion, etc. 9.30-5.00. 01-242 7401.

**WANTED** to fulfil an export order: Surplus Broadcast Transmitter. Power range 100-150 kilowatts; should cover full high frequency range. Intermediate and penultimate stage tuning units must be intact, otherwise condition immaterial. Power supplies any condition preferable but not essential. Units of lower power ratings will be considered. Apply with inspection permits to: Box No. 99.

## Aerials

Direct from the Manufacturers

# U.H.F. AERIALS

EASY ASSEMBLY KITS

10 Element **SAVE 40%**

**£125** on normal retail price.

14 Element 18 Element  
**£150 £175**

Book, illustrated and 20p. 2000-2075. 2000-2075. 2000-2075. 2000-2075.

**APEX AERIALS (P.W.)**

10 DAY COURSE, 100% SAT., LONDON ONE, REINFORCEMENT



## Educational

### TRAIN FOR SUCCESS WITH ICS

Study at home for a progressive post in Radio, TV & Electronics. Expert tuition for C & G (Telecoms Techn's Cert and Radio Amateurs') RTEB, etc. Many non-exam courses including Colour TV Servicing, Numerical Control and Computers. Also self-build kit courses—valve and transistor. Write for FREE prospectus and find out how ICS can help you in your career. **ICS, DEPT. 541 INTERTEXT HOUSE, LONDON, SW8 4UJ**

**RTEB CERTS.**, City & Guilds, Colour TV, Radio, Computers, Radio Amateurs Cert., Practical Electronics (with kit). Thousands of successes. Send for full details of Home Study Courses and illustrated book—FREE: BIET, (Dept. H.7), Aldermaston Court, Reading, RG7 4PF.

**GO TO SEA** as a Radio Officer. Write: Principal, Nautical College, Broadwater, Fleetwood FY7 8JZ.

**CIE, AMSE**, City & Guilds, etc., on 'Satisfaction or Refund' terms. Thousands of exam. successes. Postal Courses for all branches of Engineering. Illustrated prospectus FREE. Please state subject of interest: BIET, (Dept. H.8), Aldermaston Court, Reading, RG7 4PF.

## Ladders

**VARNISHED TIMBER LADDERS** from manufacturer. Lowest prices anywhere. 15½ ft. extd. £6.20, 17ft. ext. £6.50, 20ft. ext. £7, 21½ ft. ext. £7.75, 24½ ft. ext. £8.90, 29ft. ext. £10.25, 31½ ft. triple ext. £12.25, 36ft. triple ext. £16. Carr. 30p. Free lists. Also Aluminium Ext. & Loft Ladders. Callers welcome.—(Dept. W.L.S.) Home Sales, Baldwin Road, Stourport, Worcs. Phone 02-993 2574/5222. Placing order on C.O.D.

## Metal Work

**METAL WORK:** All types cabinets, chassis, racks, etc., to your specifications. **PHILPOTTS METAL WORKS LTD.**, Chapman Street, Loughborough.

## Situations Vacant

**EAGLE INTERNATIONAL** require Audio Engineers; excellent prospects. Must be fully conversant with Stereo Amplifiers, Tuners, Multiplex, etc. Contact Mr. Morrow 01-903 0144.

# RADIO OPERATORS

**DO YOU HOLD PMG II OR PMG I OR NEW GENERAL CERTIFICATE OR HAD TWO YEARS' RADIO OPERATING EXPERIENCE?**

Looking for a secure job with good pay and conditions?

Then apply for a post with the Composite Signals Organisation. These are Civil Service posts, with opportunities for service abroad, and of becoming established, i.e., non-contributory pension scheme. Specialist Training Courses (free accommodation) starting January, April and September, 1972.

If you are British born and resident in the United Kingdom, under 35 years of age (40 for exceptionally well qualified candidates), write NOW for full details and an application form from:—

**GOVERNMENT COMMUNICATIONS HEADQUARTERS,**

Recruitment Officer, Oakley, Priors Road, Cheltenham, Glos. GL52 5AJ. (Telephone: Cheltenham 21491, Ext. 2270.)

## For Sale

# MORSE MADE !! EASY

**FACT NOT FICTION** If you start RIGHT you will be reading amateur and commercial Morse within a month (normal progress to be expected).

Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it, it's as easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed.

For details and course C.O.D. ring S.T.D. 01-660 2896 or send 4p stamp for explanatory booklet to: **G3HSC (Box 19), 45 GREEN LANE, PURLEY, SURREY**

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units, interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots / removable space dividers. Build up any size cabinet for wall, bench or table top

## INTER-LOCKING PLASTIC STORAGE DRAWERS

**NEAT! HANDY! TIDY!**

**DISCOUNT PRICES**

**SINGLE UNITS (5" x 2 1/2" x 2 1/2")** £1.35 Dozen

**DOUBLE UNITS** £2.25 Dozen

**TREBLE (3D)** £2.35 for 8

**DOUBLE TREBLE** 2 draws in one outer case (6D2) £3.65 for 8 extra large size (6D1) £3.30 for 8.

**5 SIZES ALL INTERLOCK**

**PLUS QUANTITY DISCOUNTS!** Order £5 and over Deduct 5% in the £. Order £10 and over Deduct 7 1/2% in the £. Order £20 and over Deduct 10% in the £. Pack./Post./Carr.: Add 35p to all orders under £5. Orders over £5 P/P/C free. (Dept. PW11) 124 CRICKLEWOOD BROADWAY, LONDON N.W.2

**IVORYET LIMITED**



If you have difficulty in obtaining

# PRACTICAL WIRELESS

Please place a regular order with your newsagent or send 1 year's subscription (£2 65) to Subscription Department, Practical Wireless, Tower House, Southampton St., London, W.C.2.

## For Sale

SEEN MY CAT? 5,000 items. Mechanical & Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PW, NEW MILLS, Stockport.

**YUKAN SELF-SPRAY** NO PROFESSIONAL TRAY  
**Get these NOW!** air drying **GREY HAMMER**  
**OR** **BLACK WRINKLE** (CRACKLE) finishes

Yukan Aerosol sprays contain 4500 fine quality durable easy instant spray. No stove baking required. Hammers available in grey, blue, Modern Eggshell Black, Winkles (Crackle) all at 85p at our counter or 90p carriage paid, per push-button self-spray can. Also Durable, heat and water resistant Black Matt finish (100% self-spray cans only) 75p carriage paid.  
**SPECIAL OFFERS:** 1 can plus optional transferable snap-on trigger handle (value 25p/for 90p), carriage paid. Choice of 13 self-spray plate colours and primer (Motor-car quality) also available. Please enclose cheque or crossed P.O. for total amount direct to:  
**YUKAN, 307a, EDGWARE ROAD, LONDON, W2 1BW**  
 We supply many Government Departments, Municipal Authorities, Institutes and Leading Industrial Organizations. We can supply you too.  
 Open all day Saturday. Closed Thursday afternoons.

Closed ALL DECEMBER for annual holiday

## Service Sheets

# LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS, CAR RADIOS)

Only 25p each, Manuals from 50p.  
**"PLEASE ENCLOSE LARGE S.A.E. WITH ALL ENQUIRIES & ORDERS"**  
 Otherwise cannot be attended to (Uncrossed P.O.'s please, original returned if service sheets not available.)

**C. CARANNA**  
 71 BEAUFORT PARK  
 LONDON, N.W.11

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number alternative.

Free TV fault tracing chart or TV list on request with order.  
 Mail order only.

## QUICK, EFFICIENT, UNIQUE SERVICE SHEET SERVICE

Very Large Stock  
 TVs, Radio, Amps, Test Gear.  
 Special Telephone Service available to Trade Customers.  
 Colour TV and Test Gear Circuits.  
 Exchange Service.

Full details with First Order.  
 List price 10p post free.

State Make and Model Number  
 Large S.A.E. and 25p unfiled P.O.

Mail Order Only.

**A.S.L., 21c Drydon Chambers,**  
**119 Oxford Street,**  
**London, W1R 1PB**

## Service Sheets

# ★ Service Sheets and Manuals ★

COVERING RADIOS, TELEVISIONS, TAPE RECORDERS, RECORD PLAYERS, ETC. FROM 1933 UP-TO-DATE FROM 40p. EACH - 1971 SERVICE SHEET INDEX LIST 20p. - S.A.E. WITH ENQUIRIES PLEASE

	Price + Post
<b>NEW BOOKS &amp; PUBLICATIONS</b> PRACTICAL OSCILLOSCOPE HANDBOOK by R.P. Turner. 236 pages . . . . . SERVICING TRANSISTOR RADIOS AND PRINTED CIRCUITS 263 pages . . . . . WIRELESS SERVICING MANUAL by W.T. Gasking. 286 pages . . . . . INTERMEDIATE ELECTRONICS by R.J. Maddock. Book One. 327 pages . . . . . INTERMEDIATE ELECTRONICS by R.J. Maddock. Book Two. 314 pages . . . . . GUIDE TO BROADCASTING STATIONS 16th Edition. 219 pages . . . . . TELEVISION ENGINEERING Vol.2. Principles and Practice. 296 pages . . . . . MEASURING OSCILLOSCOPES by J.F. Goiding. 272 pages . . . . . INTEGRATED CIRCUIT SYSTEMS by D.J. Walter. 234 pages . . . . . FIELD EFFECT ELECTRONICS by 3 eminent Authors. 372 pages . . . . . FM RADIO SERVICING HANDBOOK by G.J. King. 206 pages . . . . . SEMICONDUCTORS: BASIC THEORY AND DEVICES by I.Kampel. 272 pages . . . . .	£1.80 15p £1.50 15p £2.75 15p £2.75 15p £0.50 7p £3.50 25p £4.20 25p £3.50 25p £3.00 15p £3.00 15p

Send S.A.E. for 'FREE' List of Practical and Technical Books on Radio & Television now available to -

**BELL'S TELEVISION SERVICES**  
 Albert Place, Harrogate, Yorkshire. Telephone 0423-86844

**SERVICE SHEETS.** Radio, TV etc. 8,000 models. List 10p. S.A.E. enquiries. TELRAY, 11 Maudland Bank, Preston.

**SERVICE SHEETS (1925-1971)** for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., by return post, with free Fault-Finding Guide. Prices from 5p. Over 8,000 models available. Catalogue 13p. Please send S.A.E. with all orders/enquiries. Hamilton Radio, 54 London Road, Bexhill, Sussex. Telephone Bexhill 7097.

**SERVICE SHEETS.** TV, Radio, etc., 40p. Large stocks. S.A.E. with enquiries please, callers welcome. K. L. Bower, 35 Briarwood Drive, Wibsey, Bradford.

**RADIO, TELEVISION** and Tape Recorders, 50 mixed odd sheets 50p. Also large stock of Obsolete/Current Valves. John Gilbert TV, 1B Shepherds Bush Road, London W6. 01-743 8441. SAE enquiries.

## TRADER SERVICE SHEETS

40p. each plus postage

We can supply Trader Service Sheets for most makes and types of Radios, Tape Recorders and Televisions—Manuals for some.

Cheques and open P.O.s returned if sheets not available.

## OAKFIELD ENTERPRISES LIMITED

29 CHURCH ROAD, TUNBRIDGE WELLS, Kent

Make	Model	Radio/TV

1971 List now available at 10p plus postage

If list is required indicate with X

From .....

Address .....

enclose remittance of .....

(and a stamped addressed envelope) s.a.e. with enquiries please

**MAIL ORDER ONLY**

## Receivers and Components

**CIRCUITS CIRCUITS CIRCUITS**  
 Ten exciting circuits per month with instructions to build. Every month a completely new set. This month's circuits cover  
**MISCELLANEOUS PROJECTS**  
 Only 50p per set of ten p & p free  
 Free Data and Technical A-Z cards (build up the complete set month by month).  
 Cheques and PO to Dept PWC, Photronics, 3 Whitehall Gardens, London, E4.

**COMPLETE RANGE** of receivers by Trio, Lafayette, Hallicrafters, etc. Chassis, panels, cabinets. S.A.E. for lists. Stephens-James Ltd., 70 Priory Road, Liverpool 4. Tel. 051-263 7829.

**VALVES:** Vintage, mains, battery pre-war, new and used. Transmitting. S.a.e. lists. Taylor, 14 Willow Walk, Canewdon, Rochford, Essex SS4 3QH.

## EX-RENTAL TV's (Untested)

Complete with 18 channel tuners. Good cabinets. Carriage £1-50 extra.  
 17" Semi Slim (90° Tube) .. £2-50  
 17"/21" Slim (110° Tube) .. £4-50  
 19" Slimline .. .. £5-50  
 23" Slimline .. .. £8-50  
 19" BBC2 Sets .. .. £14-50

## TUBES EX EQUIPMENT (Tested)

Single Panel  
 17" Any Type .. .. £2-00  
 19"/21" Any Type .. .. £3-00  
 23" Any Type .. .. £4-00  
 Twin Panel (Bonded)  
 19" Bonded .. .. £5-00  
 23" Bonded .. .. £6-00  
 Panorama Tubes (Metal Rim)  
 19" Panorama .. .. £5-00  
 23" Panorama .. .. £6-00  
 Add £1-00 Carriage

## PERFECT SPEAKERS EX T.V.

Pin 8 ohm (minimum order two) 5 in. round, 8 in by 2 in rectangular—12p each. Add 7p per speaker p. & p.

## VALVES EX EQUIPMENT

EB91 6p	30L15 12½p	PL96	22½p
EBF89 12½p	30P4 12½p	PL81	17½p
ECC82 12½p	PC97 17½p	PY81	15p
EC180 7½p	PCF86 17½p	PY800	15p
EF80 12½p	PC84 7½p	PY82	7½p
EF85 12½p	PCF80 7½p	PY83	22½p
EF183 12½p	PCF89 12½p	U191	17½p
EF184 12½p	PCL86 22½p	6P23	17½p
ET86 17½p	PCL82 17½p	30PL1	22½p
30PL13 20p	PCL86 17½p	30PL2	20p
630LZ 12½p	PCL83 12½p	30F5	10p

Add 2½p per valve p. & p., orders over £1 p. & p. free

## UHF TUNERS

For Ferguson 850 900 chassis adaptable for KB, Ekco T416, 1084 Chassis £2-50, p. & p. 50p.

## SLOT METERS—SPECIAL OFFER

Smiths Mk. II 6d. Convertible to 5p. (Smiths Kit costs 35p each) £1 each inc. p. & pkg. or 10 for £5 inc. p. & pkg.  
 Please write with SAE for quotations on any spares.

## TRADE DISPOSALS (Dept. TS/PW)

Thornbury Roundabout, Leeds Road, Bradford. (Telephone 685670)

**LOOK AT THESE PRICES!**

ALL DEVICES BRAND NEW FULLY TESTED AND GUARANTEED

**Integrated Circuits TTL LOGIC Dual in line**

7400, 01, 02, 04, 05, 10, 20, 30, 40, 50, 51, 53, 54, 60 ALL 15p ea.  
7441, 42, 80, 83, 90, 92, 93, 94, 95, ALL 67p ea.  
7481, 82, 91, 118, 145, 151, ALL 95p ea. 7470, 72, 30p ea. 75, 76, 45p ea.  
7473, 74, 40p ea. 86, 121, 50p ea. 7447, 90p ea.

**Silicon Rectifiers**

P.I.V.	50v	100v	200v	400v	600v	800v	1000v
1A	4p	4.5p	5p	5p	8p	10p	13p
1A	4.5p	4.5p	5p	6p	9p	12p	14p
3A	13p	15p	19p	21p	23p	25p	28p

**Integrated Circuits Linear, D.I.L. or TO-5**

709, 40p 741, 60p

Discounts 10% Orders over £2 15% over £5. Post & Pack. 5p

Mail Order Only

**D J COMPONENTS**

14B, SUSSEX ROAD, HARROW, MIDDLESEX

**EX COMPUTER PRINTED CIRCUIT PANELS**  
2in x 4in packed with semi-conductors and top quality resistors, capacitors, diodes, etc. Our price 10 boards 50p, P. & P. 7p. With a guaranteed minimum of 35 transistors. Data on transistors included.

**SPECIAL BARGAIN PACK.** 25 boards for £1, P. & P. 18p. With a guaranteed minimum of 35 transistors. Data on transistors included.

**PANELS** with 2 power transistors similar to OC28 on each board—components 2 boards (4 x OC28) 50p, P. & P. 6p.

9 OA5, 3 OA10, 3 Pot Cores, 26 Resistors, 14 Capacitors, 3 GET 872, 3 GET 872B, 1 GET 875, All long leaded on panels 12in x 4in. 4 for £1, P. & P. 25p.

**700C OPERATIONAL AMPLIFIER**  
705 8 lead I.C. 1 off 50p; 50 off 35p; 100 off 20p.

**250 MIXED RESISTORS 62p**  
1/2 & 1 watt.

**150 MIXED HI STABS 62p**  
1/2, 1 & 1 watt 5% & better

**QUARTZ HALOGEN BULBS**  
With long leads. 12V 55W for car spot lights, Projectors, etc. 50p each. P. & P. 5p.

**GPO EXTENSION TELEPHONES**  
with dial but without bell.  
95p each, P. & P. 30p.  
£1.75 for 2, P. & P. 50p.

**BARGAIN RELAY OFFER**  
Single pole change over silver contacts 25V to 50V. 2-5kΩ coil. 8 for 50p. P. & P. 5p.

**KEYTRONICS mail order only**  
44 EARLS COURT ROAD,  
LONDON W.8 01-478 8499

**MICROCIRCUITS:**

SN76013 (like IC12) £1.50; 709 36p; 741 36p; PA230 90p; PA234 87p; PA237 £2.15; SL402A £1.75; SL702C 40p; TTL gates 19p; 7474 42p; 7490 80p; 7491 £1.20; MEL11 35p; D40C1 55p.

**TRANSISTORS:**

2N3055 54p; BC107B 9p; BC108C 9p; BC109C 9p; BCY70 16p; BFX86 15p; ME0402 21p; ME0411 20p; ME0412 20p; ME0413 15p; ME1002 11p; ME4101 11p; ME4102 12p; ME8101 15p; ME8102 19p; ME8001 17p; MP8111 35p; MP8112 45p.

**1 AMP RECTIFIERS**

50V 3p; 100V 4p; 200V 5p; 400V 6p. Bridges: 50V 30p; 100V 31p; 400V 32p.  
**PRINTED CIRCUIT RESIST PEN 80p.**  
1/16 W Miniature Resistors 44p.

**JEF ELECTRONICS (P.W.11)**

York House, 12 York Drive, Grappenhall, Warrington, Lancs. Mail Order Only. C.W.O.  
P.&P. 7p per order. Overseas 50p.  
Money back if not satisfied.  
List free on application.

**NEW MODEL V.H.F. KIT MK2**

Our latest Kit, improved design and performance plus extra Amplifier Stage, receives Aircraft, Amateurs, Mobile, Radio 2, 3, 4, etc. This novel little set will give you endless hours of pleasure and can be built in one evening. Powered by 9 Volt Battery, complete with easy to follow instructions and built in Jack Socket for use with Earphones or Amplifier.

Only £3.40. P. & P. Free U.K. only

Illustrated Catalogue of Selected Kits and Components 12p. P. & P. Free.

Cheques, Postal Orders to:

Dept. P.W.,  
Galleon Trading Co., 25 Avelon Road,  
Romford, Essex

**SINCLAIR BARGAINS**

Power units: PZ5 £3.80, PZ6 £6.40, PZ8 £6.40

Transformers for PZ8 £2.20  
Amplifiers: Z30 £3.60, Z50 £4.35. Stereo 60 £8.35.

Receivers: Micromatic Kits £2.25. Assembled £2.75. Batteries 27p extra.

**S-DECS**

S-DeCs £0.95. T-DeCs £2.25. µ-De C £3.10. Carriers with sockets to mount 14 and 16 pin in line ICs on T-DeCs and µ-De C £1.25.

**MULLARD UNILEX**

EP9000 Amp £2.40. EP9001 Pre-amp £2.60. EP9002 Power unit £3.90. Control unit £2.80. Unilex booklet £0.22.

**PROJECT 60 OFFERS**

Stereo 60/2 Z30/PZ5 .. .. . £16.40  
Stereo 60/2 Z30/PZ6 .. .. . £18.85  
Stereo 60/2 Z50/PZ8 .. .. . £28.25  
Transformer for PZ8 .. .. . £2.20  
Project 60 FM tuner .. .. . £20.50  
Active Filter Unit .. .. . £4.75  
Q16 Loudspeaker .. .. . £7.40  
Kit of extra capacitors, plugs, cables, fuse to complete Project 60 .. .. . £2.40  
Antex 15W soldering Iron CN240/2 .. .. . £1.70  
All items available separately.

**IC10 AND SUPER IC12**

Integrated circuit amplifiers and preamps, complete with instructions. IC10 £2.00. Super IC12 with free PC board £2.45.

**PNP SILICON TRANSISTORS**

From 2S300 series: Typical Vcb=25V, hfe=35, ft=1Mc, Pmax=30mW. Untested and unmarked, but at least 80% are perfect to maker's spec. 50 for 40p, 100 for 70p.

SINCLAIR 3000 £31.50 Post 30p

**SWANLEY ELECTRONICS**

32 GOLDSSEL RD., SWANLEY, KENT

Mail order only. Postage 37p on Project 60 orders, 10p on others. All goods are brand new. Money back if not satisfied.

**RESISTORS BRAND NEW, 1p each**  
1/2 W, 100 1K 10K. Discount 100+10%; 500+15%; 1000+20%. Minimum order 10 mixed or single value. Post 4p, over 100 post free. C.U. Resistors, 10 Auckland Avenue, South Shields, Co. Durham.

**Stella Nine Range Cases**

**LIST OF PRICES AND SIZES**

Width	Depth	4" Height	6" Height	7 1/2" Height
6 1/2"	3 3/4"	90p	£1.05	£1.23
6 1/2"	4 3/4"	96p	£1.23	£1.40
8 1/2"	3 3/4"	£1.05	£1.40	£1.40
8 1/2"	6 1/4"	£1.40	£1.74	£2.00
10 1/2"	7 1/4"	£1.88	£2.28	£2.45
12 1/2"	3 3/4"	£1.40	£1.74	£2.03
12 1/2"	5 3/4"	£1.85	£2.25	£2.43
12 1/2"	8 1/4"	£2.30	£2.74	£2.93
14 1/2"	3 3/4"	£1.65	£2.03	£2.25
14 1/2"	9 3/4"	£2.73	£3.50	£3.65
16 1/2"	6 1/4"	£2.45	£2.93	£3.24
16 1/2"	10 1/4"	£3.15	£4.05	£4.45

Cases—Post 25p. per order.

Discounts available on quantities.

**CHASSIS in Aluminium, Standard Sizes, with Gusset Plates**

Sizes to fit Cases. All 2 1/2" Walls

6" x 3"	33p	10" x 7"	51p	14" x 3"	44p
6" x 4"	34p	12" x 3"	40p	14" x 9"	84p
8" x 3"	39p	12" x 5"	45p	16" x 6"	64p
8" x 6"	46p	12" x 8"	64p	16" x 10"	95p

Chassis—Post 15p. per order.

Discounts available on quantities.

Electro magnetic counters. New Boxed. 500 ohm 4 digit 30p post free.

Copper Laminate Board 1/8" single sided. 12" x 12" 30p. post free.

P.O. relays (600 Type) 500 ohm + 500 ohm. 1 make 1 break 2 change over

New boxed 30p post free.

Heavy duty sliding reostat. 1 ohm 12 amp

New boxed £1.25p. post free.

**E. R. NICHOLLS**

Manufacturer of Electronic Instrument Cases

46 LOWFIELD ROAD  
STOCKPORT - CHESHIRE

Tel: 061-480 2179

**AERIAL BOOSTERS (£2-95)**

We make four types of R.F. high gain transistorized pre-amplifiers L45 U.H.F. TV, L12 V.H.F. TV, L11 V.H.F. radio, L10 medium and short wave. For full details send S.A.E.

**PRINTED CIRCUIT BOARDS**

2-9in by 4in boards with etching powder and instructions. 50p

**MAINS DROPPER**

Three section 33 ohms by 33 ohms by 33 ohms. 9p each

**TV VALVES (EX EQ)**

Any 5-45p, 10-70p. ECC82, ECL80, EF80, EF85, EF183, EB91, EY86, PCC84, PCC89, PCF80, PCF86, PCL82, PCL83, PCL84, PL36, PY33, PY81, PY82, Y800, 30L15

P&P ALL ORDERS 10p, SAE for details

VELCO ELECTRONICS, 62a Bridge St,

Ramsbottom, Bury, Lancs.

**CONSTRUCTORS. Stop Marking Out**

Heat Sinks. Use my non-wear drill Jig for all (TO3) Transistor Bases, e.g. OC25, OC28, OC20, etc. Price 40p plus 5p p&p. Enquiries: R. Camps, 115 St. Anthony's Drive, Chelmsford, Essex.

**VHF AIRCRAFT, Public Service band**

radios. FLIGHT 4: Medium Wave, FM 88-108, Aircraft 108-140, Public Service 140-175. AFC. 9in. x 7in. x 4in., £16. WALTHAM. MW/LW/SW/FM/VHF 108-175. Battery/mains. AFC 11in x 9in x 4in., £33. Full lists s.a.e. Money-back guarantee. Langtons Radio, High Street, ROCESTER, Staffordshire. Tel. 388.

## Receivers and Components

### AUDIO MIXER UNITS

MODULES AND BOARDS High quality units for constructing complete mixers in mono and stereo or for amplifier front ends etc.

S.A.E. for details

## PARTRIDGE ELECTRONICS

Dept. P.W.11. 21/25 Hart Road, Thundersley Benfleet, Essex.  
Tel. South Benfleet 3256

### SEMICONDUCTORS

25+ price for ANY MIXTURE

1-24	25+	1-24	25+		
AC126	17p	15p	OA90	5p	4p
AC128	17p	15p	OA91	17p	4p
AC176	20p	17p	OC170	17p	15p
AF239	32p	28p	RAS310AF	16p	14p
BC107	11p	10p	T848	12p	11p
BC108	10p	9p	1N4001	7p	6p
BC109	11p	10p	1N4002	8p	7p
BCY70	14p	11p	1N4006	14p	12p
BF167	21p	18p	1N4007	16p	13p
BF173	20p	17p	2N3819	25p	25p
BF180	35p	30p	2N3645	45p	40p
BFY50	20p	17p	7400	20p	18p
BSX19	11p	9p	7441	87p	85p
BYZ13	16p	14p	7473	42p	39p
BZY88			7475	46p	43p
(3-3-33v)	15p	13p	7490	80p	65p

Matched pairs at no extra charge. Post free over £1.50, under add 6p. Price list of all components, resistors, caps, pots, switches, etc., free on request.

### J. R. HARTLEY (P.W.)

78b High Street, Bridgnorth, Shropshire

**RADIO SPARES COMPONENTS** as specified for P.W. Digital Counter. Midget Mains Transformer, £1.75, p. & p. 25p. Min. wire neons, 12p each, p. & p. 5p. Min. Make-Switch shafting assembly, 40p. Spacers, 7p pkt. M-B wafers, 28p each, p. & p. on complete switch, 12p. We supply all 'Radiospares' components. S.a.e. with enquiries: The Hobbies Shop, 32 The Parade, Cwmbran Town Centre, Cwmbran, Mon.

**TRANSFORMERS** for all transistor projects. Prices reasonable. Rewind service available. S.a.e. details: Ratcliffe, 18 Beech Avenue, Thongsbridge, Huddersfield.

## CHROMASONIC electronics

supply only brand new guaranteed goods

LOW NOISE EI-STABS

1 watt 5% all E24 values 3 for 2p plus p. & p. 6p. For up to 50 resistors + 1p for each additional 50.

### INTEGRATED CIRCUITS

PA234	87p	MFC4000P	70p	µA709C	50p
PA237	£1.57	MFC4010P	75p	µA710	50p
PA246	£1.60	TAA700	£2	µA741C	75p

### TRANSISTORS & DIODES

AC187/88	30p	BC147	16p	2N3708/9	
				10/11	12p
AD161	63p	BC148	12p	2N3055	70p
AD182	pair	BC149	15p	2N2926	O/Y 15p
BC107	12p	2N3702/3	12p	2N1711	25p
BC108	11p	2N3704	17p	OA81/90/91	7p
BC109	12p	2N3705/6/7	15p	BZY88	15p

F.M. STEREO I.F. STRIP £3.50 + p. & p. 25p  
F.M. FRONT END £5.00 + p. & p. 25p  
F.M. STEREO DECODER £5.25 + p. & p. 25p

100µF 16v. 4p each.

Mullard C461 series capacitors:  
500µF 40v 28p 2000µF 25v 42p 4000µF 25v 62p  
1250µF 25v 42p 2500µF 40v 62p 4000µF 40v 77p  
1250µF 40v 42p 2500µF 64v 77p also  
C426 (6p), C437, C280, C333, S.MICA & polystyrene.

CARBON TRACK POTS, Single bang Log or Lin 12p  
Dual gang Log or Lin 40p, Mains Sw. 12p extra.  
SKELETON PRESETS, Vert. or Horiz. 0.1w 5p,  
0.25w 7p.

MAINS TRANSFORMER, Sec. 250v 25mA + 6.3v  
1.2A £1.90.

66, FORTIS GREEN ROAD, LONDON, N10 3HN  
FREE CATALOGUE p. & p. 3p  
p. & p. on all orders other than resistors 6p.

### NEW THIS MONTH MULTI-PURPOSE PRINTED WIRING BOARD

#### NIPPIBOARD

Type 'A' for making amplifiers, car gadgets, electronic music circuits, alarms, oscillators, in fact almost any electronic circuit using up to four transistors. NIPPIBOARD is a new design with grid references for quick component location and costs only 15p (plus 4p postage and packing). CASH WITH ORDER ONLY.

IDEAL FOR SCHOOL PROJECTS.  
SPECIAL OFFER (closes November 30, 1971)  
TWO NIPPIBOARDS for 25p; FOUR for 40p; (Add 5p post and packing). Trade enquiries welcome.

NEW SL403D short circuit proof 3V amplifier £1.99 plus 9p postage and packing. C.W.O.  
Dept. NB/W11, NIP Electronics, P.O. Box 11, St. Albans, Herts.

**BRAND NEW COMPONENTS** by return. Electrolytics 15 or 25V 1, 2, 5, 10 mfd.-3.5p; 25, 50-4p; 100-5p. Mylar Film 100V .001, .002, .005 .01, .02-2p; .04, .05-2.5p; .068, .1-3p. Mullard miniature Carbon Film resistors E.12 series 1/3W 1Ω-10MΩ 8 for 5p. Insured postage 8p. The C.R. Supply Co., 127, Chesterfield Rd., Sheffield S8.

**EX-GOVT. COMMUNICATIONS RECEIVERS**, calibrators, signal generators, components, etc., with money back guarantee. S.A.E. list. Callers welcome, please phone first. P. R. Gollidge, G3EDW, Glen Tor Torrington, Devon. (STD 08-052) 2411.

Please  
mention  
**PRACTICAL**  
**WIRELESS**  
when  
replying to  
advertisements

PROFESSIONAL RECEIVERS  
SUPPLIED TO GOVT. DEPTS.,  
INDUSTRY, LABORATORIES,  
RADIO & T.V. AUTHORITIES, ETC.

BUY DIRECT AT PRICES 15%  
BELOW RETAIL VALUES

### THE NEW JULIETTE MPR 3065

is a high quality  
COMMUNICATIONS  
RECEIVER

(replaces NA 5018A)  
Recommended Price  
£42.00

Our Price **£37.80**




(Cash only) plus 62p p. & p. Complete with standard batteries and earpiece. BFO (optional extra) add £1.75.

IT NOT ONLY RECEIVES Aircraft, Shipping (VHF & SW), Taxis, Ambulances, Fire Service, T.V. Sound, Hams, Gas and Electric Boards, Public Services and many other radio telephone mobiles—BUT ALSO Classical Music, Pop and all that Jazz.

The MPR 3065 is a communications receiver and entertainment source in one neat, transistorised, portable package. Features a colour coded illuminated tuning dial and band selector, AFC, squelch, BFO (optional extra), large speaker. Ext. Aerial Socket. Works off mains or batteries. Size: 10 1/2 x 7 1/2 x 4 inches. 22 Transistors/Diodes.

FREQUENCIES: Medium Wave, 540-1600 Kcs.; Marine, 1.6-4.6 Mcs.; FM/VHF, 88-108 Mcs.; Aircraft, 108-136 Mcs. (Military, Civil and Ground control); High VHF/PB, 146-176 Mcs. (Commercial and Industrial RT mobiles).

### MODEL MPR 3016 6 BAND

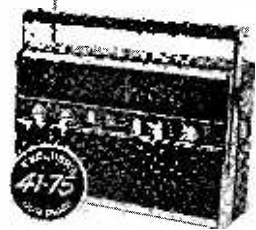

SAME BANDS & FREQUENCIES AS MODEL MPR 3065 PLUS ADDED FEATURE OF SW 5.0-12.0Mcs (with Fine Tuner). Plus 62p P/P.

BATTS & EARPIECE INCL.

Styled in elegant black case with luxury Chrome trim, soft padded speaker grille, die-cast sides and walnut insert. Size 8 1/2" x 11" x 3 1/2". Wt. 5lbs. approx.

Enclose 5d. stamp for reply. Trade supplied.

NEW! From "Lafayette" 4 band T.V. sound Battery portable with PB mobile band (146-176MHz).

TV SOUND CHANNELS 2-13, VHF/FM Local & National Radios, PSB RT Mobiles.

OUR PRICE £27.95 plus 50p P/P.  
Complete with Batteries, Earpiece, Circ. Diagram, AC Adaptor Socket; External Aerial Socket.

### STOCKTON PARTNERS (Dept. P.W.)

Importers and Distributors  
Brightongate, Grimsby, Lincs.  
Tel. 0472 64196/58815

Table of electronic components and their prices in pounds and new pence. Includes sections for VALVES, Transistors, and a large price list for various electronic parts.

Transistors section listing various transistor models such as 2N9218, 2N9219, 2N9269A, etc., with their respective prices.

TRANSISTOR POSTAGE 1p EACH, OVER 10 POST FREE

Express Postage & Insurance 5p one valve plus 1p each additional valve. ORDERS over £5 Post free. 6,000 types in stock send for lists, 5p.

R.S.T. logo

"Renowned for Service"

BLACKWOOD HALL, WELLFIELD RD., STREATHAM, SW16 2BF. Tel. 01-769-0199/1649. Open to callers Mon-Sat 9 a.m.—5 p.m. Closed Saturday 1.00—2.30 p.m.

INDEX TO ADVERTISERS

Large multi-column index listing various electronic companies and their page numbers in the advertisement, including AMC Co., Adcola Products Ltd., Baker Reproducers Ltd., and many others.



Head Office and Warehouse  
 44 WESTBOURNE GROVE  
 LONDON W2  
 Tel: 727 5641/2/3

**Z & I AERO SERVICES LTD.**

85 TOTTENHAM COURT ROAD

Please send all correspondence and Mail-Orders to Head Office

When sending cash with order, please include 12p in £ for postage and handling

LONDON W1  
 Tel: 580 8403

MINIMUM CHARGE 15np. No C.O.D. orders accepted

Please note that the valves offered below are not necessarily of U.K. origin

Open all day Saturday

0A2	0.38	6AR11	1.25	6F11	0.40	10D2	0.50
0A3	0.45	6A85	0.45	6F13	0.45	10F1	0.75
0E7	0.35	6A9G	0.70	6F14	0.70	10G6	0.60
0B3	0.70	6A76	0.35	6F15	0.65	10F18	0.60
0C3	0.38	6A6U	0.25	6F18	0.50	10L1	0.60
0D3	0.35	6AV6	0.30	6F23	0.85	10D11	0.55
1B3GT	0.40	6AW8A	0.80	6F24	0.75	10P3	0.60
1CP31	7.00	6BA6	0.25	6F25	1.00	10P14	1.10
1L4	0.20	6BE6	0.30	6F28	0.35	12AB5	0.70
1R4	0.45	6B76	1.00	6F28	0.35	12AC6	0.50
1R5	0.40	6BP6	0.55	6J4	0.50	12AD6	0.55
184	0.30	6BH6	0.75	6J6GT	0.30	12AE6	0.55
185	0.30	6BJ6	0.50	6J6	0.20	12AL5	0.50
1T4	0.30	6BK7A	0.80	6J7	0.45	12AQ5	0.50
1U4	0.30	6BN6	0.48	6K6GT	0.60	12AT6	0.30
1U7	0.80	6BN6	0.45	6K7	0.35	12AT7	0.35
1W9	0.50	6BQ5	0.25	6K8	0.40	12AT7	0.35
1X2B	0.50	6BR8	0.70	6K25	0.75	12A17	0.80
2D21	0.38	6B87	1.30	6L6GT	0.40	12AV6	0.40
3A4	0.40	6BW6	0.85	6L7	0.40	12A17	0.65
3BP1	3.00	6BW7	0.80	6L18	0.45	12A17	0.30
384	0.35	6BX6	0.25	6L20	0.60	12A17	0.30
3V4	0.45	6BZ6	0.40	6R9GT	0.45	12BA7	0.60
5B4GY	0.75	6C4	0.33	6P1	1.00	12BA6	0.40
5U4G	0.85	6C5GT	0.40	6P28	0.65	12BA7	0.40
5V4G	0.45	6CB6	0.35	6Q7	0.40	12BE6	0.40
5Y3GT	0.40	6CD6G	1.25	68A7	0.40	12BH7	0.45
5Z3	0.60	6CG7	0.55	68K7	0.40	12BT7	0.50
5Z4G	0.40	6CB7	0.40	68K7	0.40	12K1	0.70
6/80L2	0.80	6CL6	0.55	68L7GT	0.35	12KG7	0.40
6AB4	0.35	6CW4	0.65	68N7GT	0.35	12QG7	0.40
6AFA	0.55	6CY5	0.65	68Q7	0.40	19R7	0.40
6A7	0.40	6CY7	0.70	68R7	0.40	20D1	0.50
6AH6	0.50	6D3	0.50	6T3	0.35	20L1	1.10
6AL3	0.30	6DC6	0.80	6T3AGT	0.30	35LGT	0.50
6AK5	0.35	6DK6	0.50	6UA	0.40	20P4	1.10
6AK6	0.60	6DQ6B	0.70	6V6GT	0.40	20P5	1.20
6AL3	0.43	6D84	0.75	6X4	0.35	25C5	0.50
6AL5	0.20	6EA8	0.60	6X6GT	0.40	35LGT	0.50
6AM5	0.35	6E17	0.30	6X8	0.90	35Z4G	0.30
6AM6	0.35	6E3	0.85	6Y7	0.70	6Z5	0.55
6AQ5	0.35	6EW6	0.70	7Y4	0.65	30A5	0.50
6AQ6	0.65	6F1	0.75	9BWB	0.60	30A23	0.40
6AR5	0.45	6F5	0.75	10C2	0.50	30C1	0.30
6AR6	0.55	6F6G	0.35	10D1	0.55	30C15	0.80

First Quality Fully Guaranteed




APOLIX BRAND  
 ELECTRONIC VALVES

30C17	0.90	90AG	2.40	DY87	0.33	ECC189	0.65
30C18	0.80	90AV	2.50	DY80	0.35	ECP80	0.35
30F5	0.85	90C1	0.65	E88CC	0.65	ECP82	0.35
30FL1	0.75	90CV	2.40	E180F	1.00	ECP85	0.85
30FL12	0.20	807	0.60	E810F	2.00	ECP84L	0.55
30FL14	0.85	813	3.75	EAP300	3.5	ECH42	0.75
30FL13	0.85	866A	0.75	EAP72	0.55	ECH81	0.50
30L1	0.40	30L15	0.85	EBC33	0.50	ECH83	0.45
30L17	0.80	30L17	0.80	EBC41	0.55	ECH84	0.45
30P12	0.80	6146	1.60	EB8C1	0.30	ECL80	0.45
30P19	0.85	5360	1.25	EB8F0	0.40	ECL81	0.50
30P1L	0.75	6959	2.25	EBF83	0.40	ECL82	0.35
30P1L3	0.55	7199	0.80	EBF89	0.30	ECL83	0.70
30P1L4	0.90	7380	2.00	EC83	0.50	ECL84	0.55
35A3	0.55	7586	1.25	EC85	0.60	ECL85	0.55
35A5	0.75	7895	1.25	EC88	0.60	ECL86	0.40
35B5	0.65	9002	0.40	EC90	0.33	ECL800	0.50
35C5	0.50	9003	0.60	EC91	0.80	EF40	1.65
35D5	0.75	AZ1	0.55	EC92	0.85	EF40	0.50
35LGT	0.50	AZ31	0.55	EC93	0.65	EF41	0.65
35W4	0.35	CBL1	0.90	EC810	2.25	EF42	0.70
35Z3	0.70	CCL31	1.00	ECC40	0.65	EF90	0.25
35Z4G	0.35	CY31	0.35	ECC81	0.35	EF83	0.55
35Z6GT	0.80	DAF96	0.45	ECC82	0.30	EF85	0.35
35A5	0.75	DP96	0.45	ECC83	0.50	EF86	0.50
35L1	0.50	DK40	0.60	ECC84	0.80	EP89	0.35
50C5	0.50	DK92	0.55	ECC85	0.40	EP91	0.33
50DLG1	0.20	DL96	0.45	ECC88	0.40	EP92	0.35
50LGT	0.55	DM160	0.65	ECC89	0.60	EP95	0.35
55A2	0.50	DY86	0.33	ECC91	0.30	EP97	0.65

**TRANSISTORS**

2N096	0.17	AC127	0.20	BD121	0.55
2N097	0.17	AC128	0.15	BD123	0.80
2N098	0.30	AC132	0.35	BD131	0.85
2N098	0.30	AC133	0.35	BD132	0.85
2N098	0.30	AC134	0.15	BD135	0.90
2N098	0.15	AC137	0.20	BF115	0.20
2N753	0.25	AC169	0.10	BF167	0.18
2N929	0.22	AC176	0.25	BF173	0.20
2N930	0.25	AC187	0.30	BF178	0.25
2N987	0.30	AC198	0.30	BF179	0.25
2N1181	0.25	AC197	0.375	BF180	0.25
2N1132	0.25	AC198	0.20	BF181	0.25
2N1184	1.25	AC199	0.25	BF184	0.25
2N1301	0.40	AC20	0.20	BF185	0.20
2N1302	0.75	AC21	0.20	BF194	0.15
2N1304	0.25	AC22	0.15	BF195	0.15
2N1305	0.55	AD140	0.50	BF196	0.20
2N1306	0.25	AD149	0.50	BF197	0.20
2N1307	0.30	AD161	0.35	BF200	0.35
2N1308	0.25	AD169	0.35	BFW87	0.25
2N1309	0.90	AD171	1.25	BFW88	0.25
2N1613	0.25	AD212	1.25	BFW89	0.20
2N1711	0.55	AF114	0.20	BFW91	0.20
2N1756	0.75	AF115	0.20	BFX88	0.25
2N2147	0.75	AF116	0.20	BFY17	0.40
2N2160	0.65	AF117	0.20	BFY19	0.20
2N2217	0.30	AF118	0.45	BFY90	0.65
2N2316	0.85	AF125	0.50	BFY91	0.30
2N2319	0.25	AF127	0.20	BFY92	0.25
2N2369A	0.20	AF180	0.35	BSY26	0.20
2N2477	0.65	AF181	0.35	BSY27	0.20
2N2646	0.80	AF186	0.40	BSY28	0.20
2N2905	0.35	AF239	0.40	BSY65	0.20
2N2923	0.15	AF211	0.45	BSY96A	0.15
2N2924	0.15	ASY26	0.25	OC16	0.50
2N2926	0.125	ASY27	0.20	OC22	0.50
2N3053	0.25	ASY28	0.25	OC23	0.60
2N3054	0.70	ASY29	0.30	OC24	0.60
2N3065	0.85	ASY54	0.25	OC25	0.35
2N3193	0.25	ASZ15	0.70	OC26	0.25
2N3134	0.30	ASZ16	0.70	OC28	0.60
2N3391	0.20	ASZ17	0.75	OC29	0.60
2N3392	0.15	ASZ18	0.75	OC30	0.75
2N3393	0.15	ASZ20	0.25	OC35	0.50
2N3394	0.15	ASZ21	0.40	OC36	0.60
2N3395	0.20	BC107	0.125	OC37	0.30
2N3402	0.15	BC108	0.125	OC44	0.20
2N3403	0.15	BC109	0.125	OC45	0.15
2N3404	0.35	BC113	0.25	OC70	0.10
2N3414	0.20	BC118	0.30	OC71	0.12
2N3415	0.15	BC124	0.30	OC72	0.20
2N3416	0.25	BC147	0.175	OC73	0.30
2N3417	0.25	BC148	0.15	OC75	0.20
2N3702	0.12	BC149	0.15	OC76	0.20
2N3703	0.12	BC152	0.15	OC78	0.25
2N3704	0.12	BC158	0.15	OC78D	0.20
2N3707	0.15	BC175	0.20	OC81	0.25
2N3709	0.12	BC198	0.25	OC81D	0.25
2N3710	0.12	BCY30	0.35	OC83	0.20
2N3810	0.25	BCY31	0.40	OC139	0.30
2N3906	0.35	BCY33	0.35	OC140	0.35
28702	0.60	BCY34	0.30	OC141	0.60
28746	0.25	BCY72	0.20	OC170	0.25
AC113	0.15	BCZ10	0.30	OC171	0.25
AC125	0.30	BD111	0.25	OC202	0.30
AC128	0.20	BD115	0.80	OC292	0.85

**SYNCHROSCOPE TYPE C1-5**

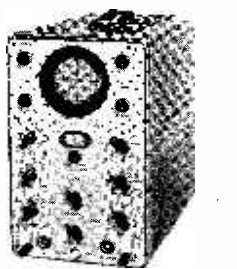

3-in tube fitted with telescopic viewing hood, giving bright display in full daylight.  
 Bandwidth 10 c/s—10 mc/s. Triggered sweep pre-set at 1-2-5-10-30-100-300-1000-3000  $\mu$ sec per stroke. Free-running time base 20 c/s to 2000kc/s with built-in crystal calibrator providing timing marks at .05-2-1-5-20-100  $\mu$ sec  $\pm$  5%.  
 Amplitude calibrator directly calibrated in volts.  
 Input attenuator 1-10-100.  
 Power supplies 127/230V AC.  
 PRICE £29.00. Packing and carriage 1.50

**TWO NEW MULTIMETERS FROM RUSSIA**



Type U4312  
**U4313**  
 with AC current ranges

Type U4312—Low sensitivity instrument (6697 o.p.v.) 1% accuracy on DC and 1-5% on AC. 9 current ranges on DC (300 $\mu$ A to 6A) and 8 current ranges on AC (1-5mA to 6A). 9 voltage ranges 0-3 to 900V AC/DC. Resistance 0-2 to 30k  $\Omega$ . Mirror scale.

PRICE, complete with leads and steel carrying case £9.75

Type U4313—20,000 o.p.v. DC and 2,000 o.p.v. on AC. 8 DC current ranges 60 $\mu$ A to 1.5A. 6 AC current ranges 0-6 to 1.5A. 9 DC and AC voltage ranges 1.5-500V. Resistance ranges 0-5-500k  $\Omega$ . Accuracy 1-5% DC and 2-5% AC. Mirror scale.  
 PRICE, complete with test leads and steel carrying case £10.50

**INTEGRATED CIRCUITS**

TAA263	Direct coupled 3-stage amplifier up to 702 $\mu$ sec. Supply voltage 6-8V output 10mW	0-75
TAA293	Medium frequency amplifier up to 600kc. Supply voltage 6V. output 10mW TO74 outline	0-85
TAA320	MOST stage followed by a bi-polar stage Gate-to-source voltage 9-14V. Power dissipation 200mW. TO18 outline	0-65
TAA570	Four-stage limiter-amplifier with F.M. quadrator detector and remote D.C. volume control facility. Nominal supply voltage 12V. TO74 outline	0-95
TAD100	AM receiver circuit containing all active components (except output stage) required to build a complete receiver	£1-95

**PHOTO-EMISSIVE DEVICES**

GAS Light emitting diode type M710B	£1-05
Photo-transistor OCT1	0-90
Photo-conductive cell ORP12	0-50
Photo-conductive cell ORP60	0-50
Photo-conductive cell ORP61	0-82
Photo-conductive cell ORP90	1-10
Photo-conductive cell ORP91	1-10
GAS Photocells 90AG	2-40
Vacuum Photocells 90AV	2-50
90CV	2-40

**AC/DC MULTIMETER AND TRANSISTOR TESTER**



8-DC voltage ranges 0-3-900V  
 6-AC voltage ranges 1.5-750V  
 5-DC current ranges 0-6-600mA  
 4-AC current ranges 0-3-300mA  
 4-Resistance ranges 0-5-500 Kohms  
 Transistor cut-off current 60 $\mu$ A max  
 Transistor DC current gain 10-350  
 Sensitivity: 16700  $\Omega$ /V DC;  
 3300  $\Omega$ /V AC  
 PRICE £10-50

OUR NEW 1971/1972 CATALOGUE IS NOW READY AND AVAILABLE FREE OF CHARGE. PLEASE SEND QUARTO STAMPED AND ADDRESSED ENVELOPE FOR THIS VALUABLE SOURCE OF REFERENCE LISTING MANY THOUSAND TYPES OF VALVES, SEMICONDUCTORS, TUBES, ETC.

# In just 2 minutes, find out how you can qualify for promotion or a better job in Engineering . . .

That's how long it will take you to fill in the coupon below. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. Home Study Course gets results fast - makes learning easier and something you look forward to. There are no books to buy and you can pay-as-you-learn on 'SATISFACTION - OR REFUND OF FEE' agreement. If you'd like to know how just a few hours a week of your spare time, doing something constructive and enjoyable, could put you out in front, post the coupon today. No obligation.

## WHICH SUBJECT WOULD INTEREST YOU?

**Mechanical**  
A.M.S.E. (Mech.)  
Inst. of Engineers  
Mechanical Eng.  
Maintenance Eng.  
Welding  
General Diesel Eng.  
Sheet Metal Work  
Eng. Inspection  
Eng. Metallurgy  
C. & G. Eng. Crafts  
C. & G. Fabrication

### Draughtsmanship

A.M.I.E.D.  
Gen. Draughtsmanship  
Die & Press Tools  
Elec. Draughtsmanship  
Jig & Tool Design  
Design of Elec. Machines  
Technical Drawing  
Building

### Electrical & Electronic

A.M.S.E. (Elec.)  
C. & G. Elec. Eng.  
General Elec. Eng.  
Installations & Wiring  
Electrical Maths.  
Electrical Science  
Computer Electronics  
Electronic Eng.

### Radio & Telecomms.

C. & G. Telecomms.  
C. & G. Radio Servicing  
Radio Amateurs' Exam.  
Radio Operators' Cert.  
Radio & TV Engineering  
Radio Servicing  
Practical Television  
TV Servicing  
Colour TV  
Practical Radio & Electronics (with kit)

### Auto & Aero

A.M.I.M.I.  
MAA/IMI Diploma  
C. & G. Auto Eng.  
General Auto Eng.  
Motor Mechanics  
A.R.B. Certs.  
Gen. Aero Eng.

### Management & Production

Computer Programming  
Inst. of Marketing  
A.C.W.A.  
Works Management  
Work Study  
Production Eng.  
Storekeeping  
Estimating  
Personnel Management  
Quality Control  
Electronic Data Processing  
Numerical Control  
Planning Engineering  
Materials Handling  
Operational Research  
Metrication

### Constructional

A.M.S.E. (Civ.)  
C. & G. Structural  
Road Engineering  
Civil Engineering  
Building  
Air Conditioning  
Heating & Ventilating  
Carpentry & Joinery  
Clerk of Works  
Building Drawing  
Surveying  
Painting and Decorating.  
Architecture  
Builders' Quantities

### General

C.E.I.  
Petroleum Tech.  
Practical Maths.  
Refrigerator Servicing.  
Rubber Technology  
Sales Engineer  
Timber Trade  
Farm Science  
Agricultural Eng.  
General Plastics

### General Certificate of Education

Choose from 42 'O' and 'A' Level subjects including:  
*English*  
*Chemistry*  
*General Science*  
*Geology*  
*Physics*  
*Mathematics*  
*Technical Drawing*  
*French*  
*German*  
*Russian*  
*Spanish*  
*Biology*

*B.I.E.T. and its associated schools have recorded well over 10,000 G.C.E. successes at 'O' and 'A' level.*

**WE COVER A WIDE RANGE OF TECHNICAL AND PROFESSIONAL EXAMINATIONS.**

*Over 3,000 of our Students have obtained City & Guilds Certificates. Thousands of other exam successes.*

## THEY DID IT— SO COULD YOU

"My income has almost trebled . . . my life is fuller and happier." - Case History G/321.

"In addition to having my salary doubled, my future is assured." - Case History H/493.

"Completing your Course meant going from a job I detested to a job I love." - Case History B/461.

## FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you.

# Free!

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). We'll send you full details and a FREE illustrated book. No obligation and nobody will call on you . . . but it could be the best thing you ever did.

## BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept B2, Aldermaston Court, Reading RG7 4PF.

## POST THIS COUPON TODAY

To: B.I.E.T., Dept B2, Aldermaston Court, Reading RG7 4PF.  
Please send me book and details of your Courses in

Name..... Age.....

BLOCK CAPITALS PLEASE

Address.....

Occupation.....

Accredited by the Council for the Accreditation of Correspondence Colleges.

453 A



**B.I.E.T.—IN ASSOCIATION WITH THE SCHOOL OF CAREERS—ALDERMASTON COURT, BERKSHIRE**

Published approximately on the 7th of each month by IPC Magazines Limited, Fleetway House, Farringdon Street, London, E.C.4 Tel: 01-634 4444. Printed in England by Index Printers, Dunstable, Beds. Sole Agents for Australia and New Zealand—Gordon and Gotch (A/asia) Ltd.; South Africa—Central News Agency Ltd.; Rhodesia and Zambia—Kingston Ltd.; East Africa—Stationery and Office Supplies Ltd. Subscription rate (including postage); For one year to any part of the world £2-6s.

PRACTICAL WIRELESS is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or any unauthorised cover by way of Trade, or affixed to as part of any publication or advertising, literary or pictorial matter whatsoever.


# HENRY'S RADIO LIMITED

## ENGLAND'S LEADING ELECTRONIC CENTRES

HENRY'S RADIO

HI-FI · COMPONENTS · TEST · PA · DISCOTHEQUE · ELECTRONIC ORGANS · MAIL ORDER

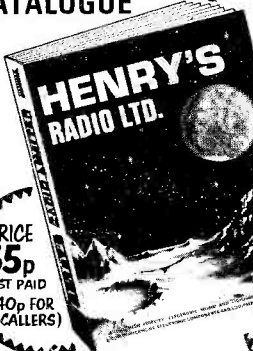**COMPLETELY NEW  
10th EDITION  
CATALOGUE**



**350**

pages fully detailed and illustrated covering every aspect of Electronics — plus data and information

**PRICE**

**55p**  
POST PAID  
(40p FOR CALLERS)

**10,000**

Stock lines at Special Low Prices and Fully Guaranteed

**PLUS! FIVE 10p VOUCHERS  
FOR USE WITH PURCHASES**

Send to this address—Henry's Radio Ltd., (Dept. PW), 3 Albemarle Way, London, E.C.1.—for catalogue only.


All other mail to "303" below

**A NEW HENRY'S CATALOGUE IS  
A MUST FOR ELECTRONICS TODAY!**
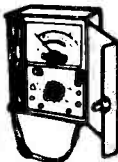
### TEST EQUIPMENT FOR EVERY PURPOSE



AF105 50kV/V multimeter (illus.). Price £8-50, p.p. 20p. Leather case £1-42. 200H 20kV/V. Price £3-87, p.p. 20p. Case 62p. 500 30kV/V multimeter. Price £8-87, p.p. 20p. Leather case £1-50. THL33 2kV/V. Price £4-12, p.p. 15p. Leather case £1-15. TE65 Valve voltmeter (illus.). Price £17-50, p.p. 40p. SE250B Pocket pencil signal injector. Price £1-75, p.p. 15p.



SE500 Pocket pencil signal tracer. Price £1-50, p.p. 15p. TE20D RF generator. Price £15, p.p. 40p. TE22D Matching audio generator. Price £17, p.p. 40p. TE15 Grid dip meter. Price £12-50, p.p. 40p. TO3 Scope 3 in. tube. Price £37-50, p.p. 50p. TE22 Audio Generator. Price £17, p.p. 40p. C1-5 Pulse Scope. £39 00, p.p. 50p.

### PANEL METERS

Complete range in stock. 38, 65 and 85 types plus large range Edge types also 240°-250° types. (Get a copy of our latest catalogue for full specifications and further ranges.)


**MORE OF EVERYTHING AT LOW  
PRICES ALWAYS FROM HENRY'S**

\* COMPONENTS IN STOCK FOR ALMOST ALL PUBLISHED DESIGNS. YOUR ENQUIRIES INVITED. SEND LARGE S.A.E. (WITH LIST) FOR PARTS QUOTE FOR ALL CIRCUITS.

SEE OUR ADVERTISEMENT INSIDE THIS MAGAZINE FOR THE LARGEST RANGE OF TRANSISTORS AND I.C.'S, ETC. AVAILABLE IN U.K.—FREE LIST No. 36 ON REQUEST.

**HENRY'S SUPPLY ALL YOUR  
AUDIO-ELECTRONIC NEEDS!**

### TRANSISTOR AMPLIFIERS

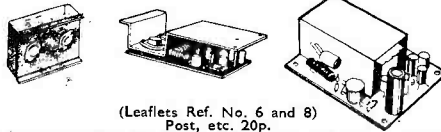

(Leaflets Ref. No. 6 and 8)

Post, etc. 20p.  
4-300 4TR 9V 300mV/V. £1-75 PA7 6TR 16V 7W £3-62  
104 4TR 9V 1W £2-12 608 6TR 24V 10W £4-12  
304 4TR 9V 3W £2-47 410 4TR 28V 10W £4-97  
555 6TR 12V 3W £2-75 MPA12/3 6TR 18V 12W £4-50


OPTIONAL POWER SUPPLIES Post, etc. 20p  
P500 (1 or 2) for 104, 304 £2-62  
PS20 (1 or 2) for PA7 £3-47  
MU24/40 (1 or 2) for MPA12/3 or MPA12/15 £4-50  
P11 for 608 £2-87 P15 for 410 £2-62

### SINCLAIR PROJECT 60 PACKAGE DEALS—SAVE POUNDS!



2xZ30 amplifier, stereo 60 pre-amp, PZ5 power supply, £16-75, Carr. 40p. Or with PZ6 power supply £18-25. Carr. 40p. 2xZ50 amplifier, stereo 60 pre-amp, PZ8 power supply £20-25 Carr. 40p. Transformer for PZ8 £2-45 extra. Any of the above with Active Filter unit add £4-75 or with pair Q16 speakers add £16. Also new FM Tuner £21. 2000 Amplifier £24-50, p.p. 50p. 3000 Amplifier £31-50, p.p. 50p. Also IC12 £2-50.

### LOW COST HI-FI SPEAKERS

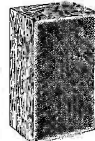

E.M.I. Size 13 1/2" x 8 1/2"  
TYPE 150 6 watt, 3, 8 or 15 ohms £2-12. Post 22p.  
TYPE 150TC Twin cone version £2-75. Post 22p.  
TYPE 450 10 watt with twin tweeters and crossover. 3, 8 or 15 ohms. £3-50. Post 25p.  
TYPE 350 20 watt with tweeter and crossover. 8 and 15 ohms. £7-50. Post 28p.



Polished CABINETS For 150, 150TC and 450 £4-50. Post 30p. TERRIFIC RANGE OF SPEAKERS, KITS AND CABINETS IN STOCK—SEE CATALOGUE OR YOUR ENQUIRIES INVITED.

### MONO, STEREO AND MIXING EQUIP- MENT. HIGH QUAL- ITY WITH LOW PRICES.



### SELF POWERED SILICON- FET CONTROL UNITS / PRE- AMPLIFIERS

FET 9/4 Mono or single channel. Adjustable levels. All facilities plus microphone. Mixing. Price £12-50  
FET 154 Stereo with all facilities, magnetic cart. input etc. Price £16-50

### SILICON POWER AMPLIFIERS FOR USE WITH ABOVE

PA 25 25 watts into 8 ohms £7-50  
PA 50 50 watts into 4 ohms £9-50  
ML442 Power Supply for 1 or 2 PA25's or 1 only PA50. £6-00. Post 20p.

FREE BROCHURE NO. 25 ON REQUEST.

NO SOLDERING—ALL UNITS INTERCONNECTED ON DEMONSTRATION AT "356"

### BUILD THIS VHF FM TUNER

5 MULLARD TRANSISTORS  
300 kc/s BAND-WIDTH  
PRINTED CIRCUIT, HIGH FIDELITY REPRODUCTION. MONO AND STEREO.  
A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately.

Free Leaflet No. 3 & 7.  
TOTAL £6-97 p.p. 20p. Cabinet 100p. Decoder Kit £5-97  
Tuning meter £1-75  
Mains unit (optional) Model PS900 £2-47  
Mains unit for Tuner and Decoder PS1200 £2-62



### NEW "BANDSPREAD" PORTABLE TO BUILD

Printed circuit all transistor design using Mullard RF/IF Module, Medium and Long Wave bands plus Medium Wave Bandspread for extra selectivity. Also slow motion geared tuning. 600 mW push-pull output, fibre glass PVC covered cabinet, car aerial. Attractive appearance and performance.  
TOTAL COST TO BUILD £7-98, p.p. 32p (Battery 22p). All parts sold separately—Leaflet No. 2.  
"IT" PORTABLE (as previously advertised) £6-98, p.p. 35p from stock—Leaflet No. 1.



### NIXIE TUBES

YN3 or XN13 0-9 side view with date sheet 85p each.

GN4 End view 0-9 with socket and data £1 75.

All I.C.'s for Digital Clocks in stock. HENRY'S CLOCK CIRCUIT No. 29, 10p.

### 20 WATT I.C. AMPLIFIER

Toshiba 20 watt Power Amplifier £4-87.

Toshiba Pre-Amplifier I.C. £1-50.

SL403D-3 watt I.C. Amp £1-50.  
Data and suggested circuits No. 42, 10p.

### FREE BROCHURES

\* P.A., DISCO, LIGHTING No. 18  
\* ELECTRONIC ORGANS IN KIT FORM No. 9  
\* HIGH FIDELITY No. 16/17  
\* TRANSISTORS, I.C.'s No. 36  
All details also in latest catalogue—see above.

Electronic Components,  
Audio and Test Gear Centre  
356 EDGWARE ROAD,  
LONDON, W.2.  
Tel: 01-402 4736

High Fidelity Sales &  
Demonstrations Centre  
354 EDGWARE ROAD,  
LONDON, W.2.  
Tel: 01-402 5854

Electronic Organs,  
P.A. & Discotheque Centre  
309 EDGWARE ROAD,  
LONDON, W.2.  
Tel: 01-723 6963

Mail Orders, Special Bargain  
Shop, Industrial Sales  
303 EDGWARE ROAD,  
LONDON, W.2.  
Tel: 01-723 1008/9

"354" & "356" OPEN SIX FULL DAYS A WEEK 9 am to 6 pm MONDAY TO SATURDAY