

Wireless

AUGUST 1992 \$9.95

wireless world

**Receiving
Meteosat II**

**Computing
insertion loss**

**Circuit
modelling by
home computer**

Australia A\$ 24.00
 Canada C\$ 9.95
 Denmark DKR 140.00
 Germany DM 6.50
 Greece DRD 160.00
 Holland Hfl. 9.00
 Italy L 31.00
 Norway Nkr 24.00
 Singapore S\$ 5.50
 Spain Ptas 240.00
 Switzerland Sfr 6.50
 U.S. \$ 9.95



THE GENIUS YOU CAN TAKE TO BREAKFAST.

Now, at last, real portable computer power. The new Sharp PC 1500 pocket computer. A pocket-sized genius that will travel with you to conferences, seminars and business breakfasts.

The PC 1500 has the capacity and BASIC language usage that is very nearly that of the desk-size Personal Computer. When fitted with the optional 4-colour graphic printer, it is one of the most powerful pocket computers on earth.

Chores can be handled swiftly and accurately any time of day, wherever you happen to be. Estimates, records and charts of sales, billings and other important data can be re-programmed, calculated and summoned

at the touch of a button. It can even play blackjack, analyse your biorhythms or give you a beeped reminder of a scheduled meeting.

Large memory capacity, up to 11.5K bytes. 4-colour print-out. Six user-programmable keys. The incredible new PC 1500. A revolution in pocket computers.

From Sharp. Where great ideas come to life.

SPECIFICATIONS PC 1500 Pocket Computer

CPU	C-MOS 8-bit CPU
Capacity	ROM: 16K bytes RAM: 3.5K bytes to 11.5K bytes

CE 150 Colour Graphic Printer/Cassette Interface (Optional)

Printing Digits	Standard 18 digits (36,18,12,9,7, 6,5,4 digits selectable)
Printing System	X-Y axis plotter system
Printing colours	Red, blue, green, black
Printing directions	Right, left, up, down
Cassette Interface	Up to two cassette tape recorders can be connected.

Please send details of the Sharp PC 1500

Type of application: _____

Name: _____

Address: _____

The world of
SHARP
where great ideas come to life.

Sharp Electronics (UK) Ltd, Computer Division, Sharp House, Thorp Road, Newton Heath, Manchester M10 9BE. Telephone: 061-205 2333



Design and specifications subject to change without notice.

WW-003 FOR FURTHER DETAILS

wireless world

WIRELESS WORLD AUGUST 1982 VOL 88 NO 1559

Receiving Meteosat II

Computing insertion loss

Circuit modelling by home computer

Australia \$4.45
Canada \$4.45
Denmark DKK 28.25
Germany DM 6.50
Greece GR 160.00
Hong Kong HK\$ 8.00
Italy L 31.00
Norway NOK 24.00
Singapore S\$ 5.50
Spain Ptas 60.00
Switzerland SFR 6.50
USA \$4.45



Autostore.

Low-cost voice-logging for people with more important things to do.

The problem: logging telephone and radio messages without spending a fortune on equipment or hiring an expensive technician to operate it.

The solution: the new Racal Recorders Autostore.

SIMPLICITY
With its automatic cassette-loading and fully automatic changeover from one deck to another, Autostore can—quite literally—be operated by whoever happens to be around.

And it provides over 24 hours of unattended continuous recording on eight channels.

VERSATILITY
Able to log radio and telephone messages simultaneously, Autostore can form part of a new system—or fit just as easily into an existing one. And its uses vary from ambulance, fire, police and security applications to the recording of financial transactions, conferences, oil installation communications and taxi services.

Racal Recorders

Racal Recorders Limited, Hardley Industrial Estate, Hythe, Southampton, Hampshire SO4 6ZH, England.
Tel: (0703) 843265 Telex: 47600



RELIABILITY
Available in 4 or 8 channel versions, and with integral micro-processor controlled automatic Timesearch capability to enable rapid message retrieval, Autostore is engineered to the very highest standards by the company which pioneered air traffic control recording techniques.

FULL DETAILS
For full details of Autostore send off the coupon today.

I am interested in recording my communications accurately and reliably. Please:

- send me full details of Autostore
- arrange for a demonstration at my own premises

Name _____

Position _____

Company _____


Address _____

Tel: _____

Racal Recorders Limited, Hardley Industrial Estate, Hythe, Southampton, Hampshire SO4 6ZH, England.

ww

WW-001 FOR FURTHER DETAILS

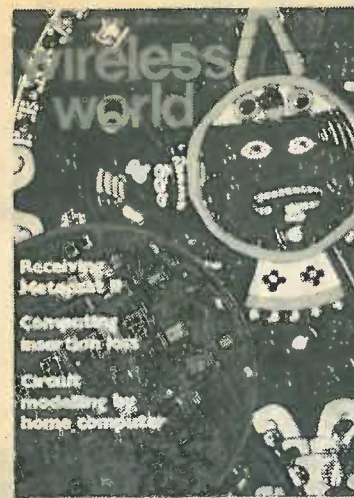

Front cover is a montage of an electronic watch circuit superimposed on an Aztec calendar wheel. Picture by Paul Brierley.

NEXT MONTH

Eprom emulator/programmer — enables program evaluation without constant alteration of eprom. When testing is finished, emulator transfers its contents to eprom.

Selective call for c.b. radio — allows keypad-generated data frame to modulate c.b. carrier and call designated receiver.

Simple low-frequency oscilloscope — suitable for audio work. Vertical bandwidth is 1MHz at 50mV/cm — triggered or free-running sweep. Costs around £40.

Current issue price 70p, back issues (if available) £1, at Retail and Trade Counter, Units 1 & 2, Bankside Industrial Centre, Hopton Street, London SE1. Available on microfilm; please contact editor.

By post, current issue £1.6p, back issues (if available) £1.50, order and payments to EEP General Sales Dept., Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.

Editorial & Advertising offices: Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.

Telephones: Editorial 01-661 3500. Advertising 01-661 3130.

Telegrams/Telex: 892084 BISPRS G. **Subscription rates:** 1 year £12 UK and £15 outside UK.

Student rates: 1 year £8 UK and £10 outside UK.

Distribution: Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. Telephone 01-661 3500.

Subscriptions: Oakfield House, Perry-mount Road, Haywards Heath, Sussex RH16 3DH. Telephone 0444 59188. Please notify a change of address.

USA: \$39 surface mail, \$98.30 airmail. US subscriptions from IPC B.P. Subscriptions Office, 205 E 42nd Street, NY 10017.

USA mailing agents: Expeditors of the Printed Word Ltd, 527 Madison Avenue, Suite 1217, New York, NY 10022. 2nd-class postage paid at New York.

© IPC Business Press Ltd, 1982 ISSN 0043 6062

ELECTRONICS
BROADCASTING
AUDIO

wireless world

COMMUNICATIONS
COMPUTING
VIDEO


AUGUST 1982 Vol 88 No 1559

- 27 **BY ANY OTHER NAME**
- 28 **80-100w MOSFET AUDIO AMPLIFIER**
by J. L. Linsley Hood
- 33 **DISC DRIVES**
by J. R. Watkinson
- 37 **ELECTROMAGNETIC ANALOGY**
by W. A. Scott Murray
- 40 **CIRCUIT MODELLING BY MICROCOMPUTER**
by R. I. Harcourt
- 43 **DIGITAL DIVIDERS WITH SYMMETRICAL OUTPUT**
by Cornelius van Kollen
- 47 **DIGITAL FILTER DESIGN**
by B. M. C. Cheetham and P. M. Hughes
- 53 **MICROCOMPUTER LINE PRINTER**
by P. L. Woods
- 57 **LETTERS**
- 61 **METEOSAT HIGH-RESOLUTION IMAGES**
by M. L. Christleson
- 65 **NEWS OF THE MONTH**
- 68 **CIRCUIT IDEAS**
- 70 **COMMUNICATIONS**
- 72 **NETWORK ANALYSIS WITH A ZX81**
by L. E. Weaver
- 75 **COST-EFFECTIVE ELECTRONIC IGNITION**
- 76 **DESIGNING WITH MICROPROCESSORS**
by D. Zissos and Jane Pleus
- 79 **ELECTRIC FIELDS IN SOLENOIDAL COILS**
by F. S. Chute and F. E. Vermeulen
- 81 **NEW PRODUCTS**



AMCRON INDUSTRIAL MUSCLE

- ★ POWER RESPONSE DC - 45KHz ± 1dB.
- ★ OUTPUT POWER IN EXCESS OF 1.5KW INTO 2.75 Ohm LOAD (CONTINUOUS R.M.S.)
- ★ D.C. OUTPUT 20 AMPS AT 100 VOLTS OR 2KVA.
- ★ HARMONIC DISTORTION LESS THAN 0.05% DC-20KHz AT 1kW INTO 6 OHMS.
- ★ PLUG-IN MODULES: CONSTANT VOLTAGE/CURRENT, PRECISION OSCILLATORS.
- ★ UNIPOLAR AND BIPOLAR DIGITAL INTERFACES, FUNCTION GENERATORS, AND MANY OTHERS.
- ★ OUTPUT MATCHING TRANSFORMERS AVAILABLE TO MATCH VIRTUALLY ANY LOAD.
- ★ FULL OPEN AND SHORT CIRCUIT PROTECTION GUARANTEED STABLE INTO ANY LOAD.
- ★ TWO UNITS MAY BE CONNECTED TO PROVIDE UP TO 4kW.
- ★ INTERLOCK CAPABILITY FOR UP TO EIGHT UNITS.
- ★ 3-YEAR PARTS AND LABOUR WARRANTY.
- ★ UNITS AVAILABLE FROM 100VA-12KVA.

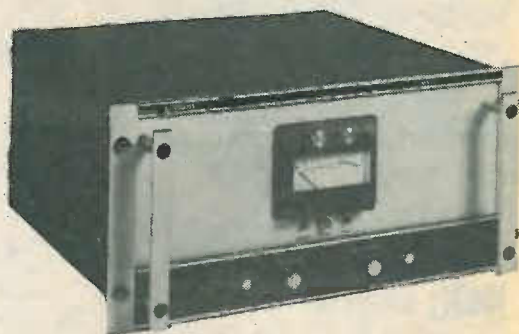

Model - M600

For full details on all Amcron Products write or phone Chris Flack

P.O. BOX 3
ATTLEBOROUGH
NORFOLK NR17 2PF
Tel: 0953-452477

Analogue Associates

PROFESSIONAL INDUSTRIAL ELECTRONICS

WW - 026 FOR FURTHER DETAILS

INSTANT PRINTED CIRCUITS!!

Make your own - to professional standards - within minutes using either "Fotolak" Light-sensitive Aerosol Lacquer or Pre-coated board. No Darkroom or Ultra-violet source needed!

Fotolak aerosol £2.50 (30p) Developer £0.30 (15p)
Ferric Chloride £0.60 (45p) Acetate Sheet £0.15 (15p)

Copper-clad Fibre-glass Boards: Single-sided £2 ft. sq. (45p)
Double-sided £2.25 ft. sq. (60p)

Pre-coated Fibre-glass Board:
8"x4 1/2" £1.75 (25p) 16"x9" £7 (60p) 24"x18" £18 (£1.70)
8"x9" £3.50 (45p) 24"x12" £13 (£1.20) Eurocard £1.25 (25p)

Double-sided Board (all sizes) add 20%
Postage individual items in brackets. Maximum charge £2 per order.

WHITE HOUSE ELECTRONICS

P.O. Box 19, Praa Sands, Penzance TR20 9TF
Telephone: Germoe (073-676) 2329

TV TUBE REBUILDING

Faircrest Engineering Ltd. manufacture a comprehensive range of equipment for processing all types of picture tubes, colour and mono. Standard or custom built units for established or new businesses. We export world-wide and have an excellent spares service backed by a strong technical team.

Full training courses are individually tailored to customers' requirements.

For full details of our service contact Neil Jupp

FAIRCREST ENGINEERING LTD.

4 Union Road, Croydon, CR0 2XX
01-684 1422/01-684 0246

WW - 059 FOR FURTHER DETAILS



L&J COMPUTERS

192 HONEYPOT LANE, QUEENSBURY, STANMORE, MIDDX HA7 1EE. 01-204 7525


THE "PET" SPECIALISTS

4016 16K Computer	£460
4032 32K Computer	£575
2031 171K Single Drive Floppy Disk	£350
4040 343K Dual Floppy Disk	£575
4022 Tractor Feed Printer	£350
8032 32K Computer	£750
8096 96K Computer	£995
8050 950K Dual Drive Floppy Disk	£750
8023 Tractor Feed Printer	£750
8422 22 Megabyte Winchester Disk	£3250
9000 SuperPet 134K Multilanguage Computer	£1295

WE HAVE A DAZZLING ARRAY OF CONNECTIONS WITH THE OUTSIDE WORLD! D TO A CONVERTERS (8, 12 & 16 BIT) A TO D CONVERTERS RESOLUTIONS X/Y PLOTTERS (A3 SIZE UPWARDS) DIGITAL INPUTS/OUTPUTS RS 232: IEEE: CENTRONIC INTERFACES

AS WELL AS BUSINESS SOFTWARE, WE ALSO CAN SUPPLY ENGINEERING REQUIREMENTS, LIKE: DATA ANALYSIS/STATISTICAL PACKAGES TAPEPREP FOR ONC MACHINE TOOLS SECTION CALCULATIONS FOR DRAWING OFFICES ANALYSIS FOR CONTROL SYSTEMS

COME AND SEE THE NEW VIC-20 £165

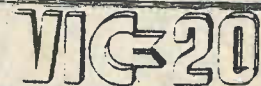

FULLY WORKING AND OPERATIONAL ASK US ABOUT ALL THE ADD-ON-GOODIES THAT GO WITH THE VIC

MASSSES OF BOOKS ON THE PET & VIC + INTERFACING & CONTROL

SEND US A LARGE STAMPED ADDRESSED ENVELOPE (12x9) AND WE WILL BE DELIGHTED TO SEND YOU ALL OUR CURRENT INFORMATION!

* PRICES DO NOT INCLUDE VAT

ALL GOODS SENT SAME DAY WHEREVER POSSIBLE
LARGE S.A.E. FOR LISTS ETC.



WW - 035 FOR FURTHER DETAILS

THE SOURCE OF ALL HIGH QUALITY USED TEST EQUIPMENT



Electronic Broker's new catalogue of current Used Test Equipment is hot off the press. Send for your FREE copy now!

Name

Company

Address


Position

Department Tel No

Post To: Electronic Brokers Ltd., 61/65 Kings Cross Road, London WC1X 9LN. Tel: 01-278 3461. Telex 298694


WW-200
FOR FURTHER DETAILS

Hilomast Ltd

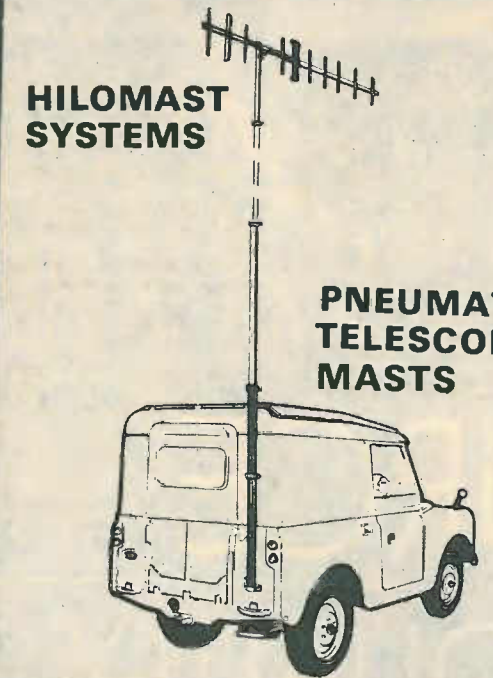

HILOMAST SYSTEMS

PNEUMATIC TELESCOPIC MASTS

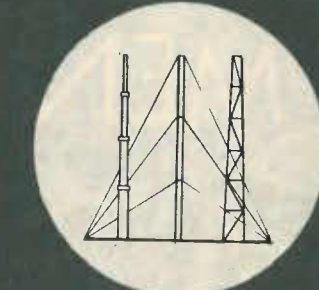

HILOMAST LIMITED
THE STREET HEYBRIDGE — MALDON
ESSEX CM9 7NB ENGLAND
Tel. MALDON (0621) 56480
TELEX NO. 995855

WW - 015 FOR FURTHER DETAILS

Toroidal Transformers

THE COTSWOLD "BUDGET RANGE" OFFERS BUILT-IN QUALITY COUPLED TO A RELIABLE DELIVERY SERVICE MOST TYPES FROM STOCK

IEC 65
VDE 0550
BS 415
TO ORDER

PHONE
TELEX, WRITE
FOR DATA SHEET
AND PRICE LIST

Budget Range Stockist
BARRIE ELECTRONICS LTD.
3 The Minories, London EC3N 1BJ. 01-488 3316

Cotswold Electronics LTD.

Unit T1, Kingsville Road, Kingsditch Trading Estate, Cheltenham GL51 9NX
Tel: 0242-41313 Telex: 897106

WW - 040 FOR FURTHER DETAILS

RADIATION DETECTORS

BE PREPARED VIEW THRU LENS

Ideal for the experimenter

- THIS DOSIMETER WILL AUTOMATICALLY DETECT GAMMA AND X-RAYS
- UNIT IS SIZE OF FOUNTAIN PEN & CLIPS ONTO TOP POCKET
- PRECISION INSTRUMENT
- MANUFACTURERS CURRENT PRICE OF A SIMILAR MODEL OVER £25 EACH
- 0-5 R

British design & manufacture.
Tested and fully guaranteed. Ex-stock delivery.
As supplied to Fire Services/Civil Defence

HENRY'S Office Orders welcome
01 723 1008/9

CALLERS: 404 EDGWARE ROAD, LONDON W2 1ED
Mail Orders/Export Enquiries to: 11-12 Paddington Green, London W2

FREE RECHARGE SERVICE AFTER PURCHASE
£6.95
Add. VAT, Post & Packing
COMPLETE WITH DATA

CLEF ELECTRONIC MUSIC

PIANOS SPECIALISTS SINCE 1972 DOMESTIC OR STAGE SIX OR 7 1/4 OCTAVES KITS OR MANUFACTURED

The most advanced form of touch-sensitive action simulating piano key inertia by patented technique.

Four mixable voices for serious tone variation plus electronic chorus and flanger effects.

Component Kits include Keyboard.

Full Kits further contain: Cabinets, Harness, Power Amp and Speaker.

Domestic Prices

£	SIX	7 1/4
Comp	234	266
Full	398	442
MFD	620	695

Kit £314
Mid £439
Regulation

VOCAL & INSTRUMENTAL SOLOISTS!

MASTER RHYTHM User Programmable DRUM MACHINE. Twenty-four patterns. Eight parallel tracks. Twelve instruments sequence operation.

BAND-BOX An Electronic Backing TRIO. Drums, Bass & Chord Instrument. User Programmable for 50-100 scores, using microprocessor.

£79 KIT £119 BUILT

Write or Phone for full details of our range of high quality Kit and manufactured Electronic Musical Instruments. Prices include V.A.T., Carr. & Ins. and we operate Telephone BARCLAY-CARD/ACCESS.
Competitive EXPORT Quotations given.

CLEF PRODUCTS (ELECTRONICS) LIMITED
Dept. W. 44a Bramhall Lane South
Bramhall, Stockport, Cheshire SK7 1AH
061-439 3297

WW - 044 FOR FURTHER DETAILS

TOROIDALS

The toroidal transformer is now accepted as the standard in industry, overtaking the obsolete laminated type. Industry has been quick to recognise the advantages toroidals offer in size, weight, lower radiated field and, thanks to I.L.P., PRICE.

Our large standard range is complemented by our SPECIAL DESIGN section which can offer a prototype service within 7 DAYS together with a short lead time on quantity orders which can be programmed to your requirements with no price penalty.

★ 294 TYPES TO CHOOSE FROM!
★ ORDERS DESPATCHED WITHIN 7 DAYS OF RECEIPT FOR SINGLE OR SMALL QUANTITY ORDERS
★ 5 YEAR NO QUIBBLE GUARANTEE

TYPE	SERIES No.	SECONDARY Volts	RMS Current	PRICE
30 VA 70x30mm 0.45Kg Regulation 10%	1x010	6+6	2.50	£5.12 +p/p £1.04 +VAT £0.92 TOTAL £7.08
	1x011	9+9	1.66	
	1x012	12+12	1.25	
	1x013	15+15	1.00	
	1x014	18+18	0.83	
	1x015	22+22	0.68	
	1x017	30+30	0.50	
50 VA 80x35mm 0.9 Kg Regulation 13%	2x010	6+6	4.16	£5.70 +p/p £1.30 +VAT £1.05 TOTAL £8.05
	2x011	9+9	2.77	
	2x012	12+12	2.08	
	2x013	15+15	1.66	
	2x014	18+18	1.38	
	2x015	22+22	1.13	
	2x017	30+30	0.83	
80 VA 90x30mm 1 Kg Regulation 12%	3x010	6+6	6.54	£6.08 +p/p £1.67 +VAT £1.16 TOTAL £8.91
	3x011	9+9	4.44	
	3x012	12+12	3.33	
	3x013	15+15	2.66	
	3x014	18+18	2.22	
	3x015	22+22	1.85	
	3x017	30+30	1.33	
120 VA 90x40mm 1.2 Kg Regulation 11%	4x010	6+6	10.00	£6.90 +p/p £1.67 +VAT £1.29 TOTAL £9.86
	4x011	9+9	6.66	
	4x012	12+12	5.00	
	4x013	15+15	4.00	
	4x014	18+18	3.33	
	4x015	22+22	2.72	
	4x017	30+30	2.00	
160 VA 110x40mm 1.6 Kg Regulation 8%	5x011	9+9	8.89	£7.91 +p/p £1.67 +VAT £1.44 TOTAL £11.02
	5x012	12+12	6.56	
	5x013	15+15	5.33	
	5x014	18+18	4.44	
	5x015	22+22	3.63	
	5x016	25+25	3.20	
	5x017	30+30	2.66	
225 VA 110x45mm 2.2 Kg Regulation 7%	6x012	12+12	9.38	£9.20 +p/p £2.00 +VAT £1.88 TOTAL £12.88
	6x013	15+15	7.50	
	6x014	18+18	6.25	
	6x015	22+22	5.11	
	6x016	25+25	4.50	
	6x017	30+30	3.75	
	6x018	35+35	3.21	
300 VA 110x50mm 2.6 Kg Regulation 5%	7x013	15+15	10.00	£10.17 +p/p £2.00 +VAT £1.83 TOTAL £14.00
	7x014	18+18	8.33	
	7x015	22+22	6.82	
	7x016	25+25	6.00	
	7x017	30+30	5.00	
	7x018	35+35	4.28	
	7x026	40+40	3.75	
500 VA 140x60mm 4 Kg Regulation 4%	8x025	25+25	10.00	£13.53 +p/p £3.35 +VAT £2.38 TOTAL £16.76
	8x017	30+30	8.33	
	8x018	35+35	7.14	
	8x026	40+40	6.25	
	8x025	45+45	5.55	
	8x033	50+50	5.00	
	8x042	55+55	4.54	
625 VA 140x75mm 5 Kg Regulation 4%	9x017	30+30	10.41	£16.13 +p/p £3.30 +VAT £2.79 TOTAL £21.42
	9x018	35+35	8.92	
	9x026	40+40	7.81	
	9x025	45+45	6.94	
	9x033	50+50	6.25	
	9x042	55+55	5.68	
	9x028	110	5.88	

IMPORTANT: Regulation - All voltages quoted are FULL LOAD. Please add regulation figure to secondary voltage to obtain full load voltage.

The benefits of ILP toroidal transformers are only half the weight and height of their laminated equivalents, and are available with 110V, 220V or 240V primaries coded as follows:
For 110V primary insert "0" in place of "X" in type number.
For 220V primary (Europe) insert "1" in place of "X" in type number.
For 240V primary (UK) insert "2" in place of "X" in type number.

How to order Freepost:
Use this coupon, or a separate sheet of paper, to order these products, or any products from other ILP Electronics advertisements. No stamp is needed if you address to Freepost. Cheques and postal orders must be crossed and payable to ILP Electronics Ltd. Access and Barclaycard welcome. All UK orders sent within 7 days of receipt of order for single and small quantity orders.
Also available at Electrovalue, Maplin and Technomatic.

Please send _____
Total purchase price _____
I enclose Cheque Postal Orders Int. Money Order
Debit my Access/Barclaycard No. _____
Name _____
Address _____
Signature _____
Post to: ILP Electronics Ltd., Freepost 5, Graham Bell House, Roper Close
Canterbury CT2 7EP, Kent, England.
Telephone Sales (0227) 54778; Technical (0227) 64723; Telex 965780.




WW - 027 FOR FURTHER DETAILS

WIRELESS WORLD AUGUST 1982

New Fluke 4 1/2 Digit Hand-held D.M.M.s

Now in Stock

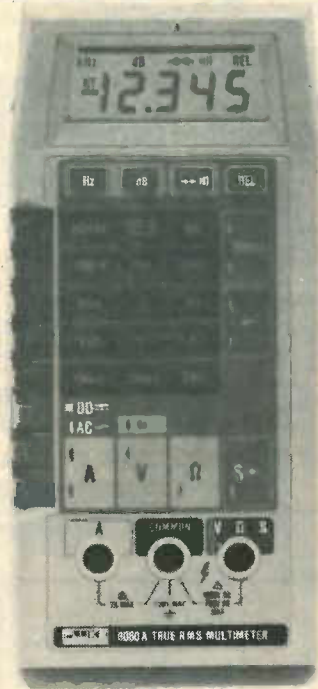

Basic dc accuracy 0.04%; 10µV, 10 nA and 10 mΩ sensitivity.
Display annunciators for low battery (BT) and special functions: frequency (kHz), dB, continuity (***, ||) and relative reference (REL).
Autorangeing MΩ measurements from 2 MΩ to 300 MΩ.
Conductance functions for resistance measurements to 10,000 MΩ.
Separate constant-current source diode-test function for checking semiconductor junctions.
Full range capability for voltage, current, resistance (200µA, 200mV and 200Ω ranges).
Wideband True RMS AC measurements to 100 kHz.
Overload protection to 750 VAC or 1000 VDC on voltage inputs and 500 V on resistance. Protection on current inputs provided by a 2A/250V fuse in line with a heavy-duty 3A/600V fuse.
Sophisticated self-diagnostics provided for all range and function selections plus LCD display, battery and CMOS circuitry.
Fluke's 8062A makes many of the same measurements as the 8060A, at a lower price.
Continuity and relative reference functions identical to 8060A.
True RMS measurements to 30 kHz.
Basic dc accuracy 0.05%; 10µV, 10 nA and 10 mΩ sensitivity.

Fluke 8060A **£275.00**
Fluke 8062A **£210.00**

Fluke 8022B With 2 year warranty **£85.00**
Fluke 8021B With 2 year warranty **£95.00**
Fluke 8020B With 2 year warranty **£125.00**
Fluke 8024B With 2 year warranty **£155.00**
Fluke 8050A Mains Model **£255.00** Mains Battery **£285.00**
Fluke 8012A Mains Model **£229.00** Mains Battery **£257.00**
Fluke 8010A Mains Model **£175.00** Mains Battery **£203.00**

ACCESSORIES

A81-230 Battery eliminator **£14.00**
C90 Carry case for hand held **£10.00**
801-600 Amp clamp **£68.00**
80J-10 Current shunt 10A **£22.00**
80K-40 H.V. probe 40kV **£56.00**
80K-6 H.V. probe 6kV **£40.00**
80T-150 Temperature probe **£72.00**
80T-H Touch hold probe **£36.00**
83RF R.F. probe 100MHz **£40.00**
85RF R.F. probe 500MHz **£69.00**
Y8102 Thermocouple probe **£41.00**
Y8103 Bead thermocouple **£18.00**
Y8104 K type thermocouple termination **£8.00**
Y8133 Deluxe test leads **£14.00**




Full Specs. on Request.
The above prices do not include carriage or VAT (15%).

Simply Phone or Telex your order for immediate dispatch.

Electronic Brokers Ltd
61/65 Kings Cross Road
London WC1X 9LN
Telephone: 01-278 3461
Telex: 298694 Elebro G

WW - 201 FOR FURTHER DETAILS

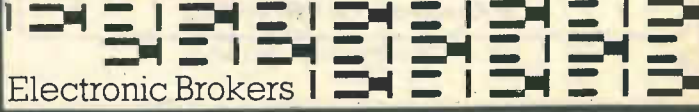

Electronic Brokers

MODEL 6010
DC ACCURACY 0.5%
£29.95
plus VAT

MODEL 7030
DC ACCURACY 0.1%
£35.95
plus VAT

Introducing two new hand-held digital multimeters
28 Ranges, each with full overload protection

10 amp AC/DC

SPECIFICATION 6010 & 7030
BATTERY: Single 9v dry cell. BATTERY LIFE: 200 hours. DIMENSIONS: 170 x 89 x 38mm. WEIGHT: 400g inc. battery. MODE SELECT: Push button. AC DC CURRENT: 200µA to 10A. AC VOLTAGE: 200mV to 750V. DC VOLTAGE: 200mV to 1000V. RESISTANCE: 200Ω to 20MΩ. INPUT IMPEDANCE: 10MΩ. DISPLAY: 3½ Digit 13mm LCD. O/LOAD PROTECTION: All ranges.

OTHER FEATURES:

Auto polarity, auto zero, battery-low indicator, ABS plastic case with tilt stand, battery and test leads included, optional carrying case.

Please add 15% to your order for VAT. Postage and packing is free of charge. Trade prices available on application.

ARMON ELECTRONICS LTD.

Cottrell House, 53-63 Wembley Hill Road
Wembley, Middlesex HA9 8BH, England
Tel. 01-902 4321 (3 lines). Tlx: No. 923985



WW - 051 FOR FURTHER DETAILS

Happy Memories

Part type	1 off	25-99	100 up
4116 200ns	.83	.72	.66
4116 250ns	.75	.65	.60
4816 100ns for BBC comp	2.95	2.70	2.50
4164 200ns	6.15	5.25	4.65
2114 200ns Low Power	1.15	1.00	.90
2114 450ns Low Power	.95	.85	.80
4118 250ns	3.25	2.85	2.65
6116 150ns CMOS	4.25	3.65	3.35
2708 450ns	2.60	2.25	2.10
2716 450ns 5 volt	2.60	2.25	2.10
2716 450ns three rail	5.75	5.00	4.65
2732 450ns Intel type	3.95	3.45	3.25
2532 450ns Texas type	3.95	3.45	3.25
Z80A-CPU £4.35	Z80A-PIO £3.25	Z80A-CTC £3.25	
6522 PIA £3.98	7805 reg. 50	7812 reg. 50	

Low profile IC sockets: Pins.....8 14 16 18 20 22 24 28 40
Pence.....9 10 11 14 15 18 19 25 33

Soft-sectored floppy discs per 10 in plastic library case:
5-inch SSSD £17.00 5-inch SSDD £19.25 5-inch DSDD £21.00
8-inch SSSD £19.25 8-inch SSDD £23.65 8-inch DSDD £25.50

74LS series TTL: Large stocks at low prices with D.I.Y. discounts starting at a mix of just 25 pieces. Write or phone for list.

Please add 30p post and packing to orders under £15 and V.A.T. to total. Access and Barclaycard welcome. 24-hour service on (054-422) 618. Government and Educational orders welcome; £15 minimum. Trade accounts operated—phone or write for details.

HAPPY MEMORIES (WW)
Gladestry, Kington
Herefordshire HR5 3NY
Tel: (054-422) 618 or 628

PRODUCTION TESTING
DEVELOPMENT
SERVICING

POWER UNITS
Now available with
3 OUTPUTS

Type 250VRU/30/25

OUTPUT 1: 0-30v, 25A DC
OUTPUT 2: 0-70v, 10A AC
OUTPUT 3: 0-250v, 4A AC

ALL Continuously Variable

Valradio

VALRADIO LIMITED, BROWELLS LANE, FELTHAM
MIDDLESEX TW13 7EN
Telephone: 01-890 4242/4837

WW - 036 FOR FURTHER DETAILS

FIRST IN THE WORLD
The ICM-12, synthesized, marine hand-portable radio

FEATURES:

- 12 channels – 6 and 16 fitted as standard.
- No waiting for crystals, can be diode programmed between 156-164MHz.
- Automatic semi-duplex for private and link calls.
- Slide-on nicad pack recharges from mains or 12V.
- Lots of options, speaker mics, alternative battery packs, 12V leads, and desk chargers.
- Complete with nicad battery pack, mains charger, belt clip, earphone, rubber antenna.
- Home Office type approved. RTD HP 105.
- **PRICE £199.13 + VAT. Free carriage.**

Also ICM-25D 25W, synthesized 25 channel VHF marine transceiver **£207.83 + VAT.**

Trade enquiries very welcome – Ask for Phil Hadler

We can also supply the ICOM IC100E Highband PMR Base and Mobile transceivers. Fully approved, very compact, built-in CTCSS and at very competitive prices. Dealer outlets required, ask for Dave Stockley.

Thonet Electronics **ICOM**
143 Reculver Road, Herne Bay, Kent
Tel: 02273 63859. Telex 965179

WW - 038 FOR FURTHER DETAILS

Quartz Crystals

Stocks of standard items exceed a quarter of a million. Individual units to the tightest specification made to order.

This technology is available now from

Interface Quartz Devices Limited
29 Market Street
Crewkerne
Somerset TA18 7JU
Crewkerne (0460) 74433
Telex 46283 inface g

WW - 012 FOR FURTHER DETAILS

Electronic Brokers
DEC SALE
a selection from our huge stocks
All items reconditioned unless otherwise stated

DISK DRIVES		PROCESSORS		PRINTERS/TERMINALS		INTERFACES		PDP8A	
RK05J2.5 meg	£975	PDP8A-205 32KW MOS (NEW)	£1,750	LA36 20mA	£450	DL11 W Asynchronous I/F	£395	PDP8A-205 Processor 10 1/2"	£1,750
RK05F5 meg fixed	£1,250	PDP8A-400 8KW Core	£1,500	LA36 R5232	£425	DUP11 DA Synchronous I/F	£525	32KW MOS (NEW)	£1,750
RK11D RK05 and Ctl	£1,870	PDP11/04 10 1/2" 32KB MOS	£3,825	LA34 R5232	£425	DUP11 DA Synchronous I/F	£750	PDP8A-400 Processor 8KW	£1,500
RK0614 meg (NEW)	£2,200	PDP11/34A 128KB MOS	£5,000	LA38 R5232	£495	KLBE Asynchronous (8E)	£175	Core: KMBAA, DKCBAA	£1,500
RK611 RK06 and Ctl (NEW)	£3,950	PDP11/34A 256KB MOS	£6,250	LA120 DA (NEW)	£1,225	KLBJA Asynchronous (8E, BA)	£275	KCBAA Programmers Console	£275
RK0728 meg	£4,500	PDP11/40 96KW Core, KT11D	£11,500	LA180 ED R5232 (NEW)	£870	M725B Printer I/F (PDP11)	£325	NMBAAB KW Core Memory	£500
RK711 RK07 and Ctl	£6,250	PDP11/44 256KB MOS	£11,500	LP04 Drum Printer (NEW)	£5,500	M8207 Printer I/F (LSI 11)	£175	NMBAAB 16KW Core Memory	£995
RL01 5 meg	£1,745	PDP11/44 CB 256KB TUS8	£12,750	VT50 20mA	£199	M8342 Printer I/F (8E, BA)	£225	MS8C8 32KW MOS Memory	£750
RL11 RL01 and Ctl	£1,450	PDP11/7051 2KB MOS (NEW)	£43,000	VT50 R5232	£225	M8256 RX02 Controller (PDP11)	£175	RX8E Dual Floppy & Ctl (NEW)	£995
RL02 10 meg	£2,200							RX2B Dual Floppy & Ctl	£1,250
RL211 10 meg and Ctl	£2,500								
RM02 67 meg	£8,500								
RJM02 RM02 and Ctl	£11,500								
RM03 67 meg	£8,250								
RWM03 67 meg and Ctl	£11,250								
RWM05 256 meg and Ctl	£24,500								
RPD4 80 meg	£4,950								
RJP04 RPD4 and Ctl	£7,950								
RP06-AB 167 meg	£12,500								
*RX1 1BD Dual Floppy and Ctl	£995								
*RX2 11BD Dual Floppy and Ctl	£1,450								
*Available in either rack mounting or desk top version.									

SYSTEMS		UPGRADES	
PDP11/44 SYSTEM	£24,750	PDP11/44 UPGRADES	P.O.A.
11/44 CPU 256KB MOS		Complete service offered including supply and installation of 11/44 CPU and trade-in of redundant processor	
Dual TUS8, H9642 Cab			
RK711 28MB Disk & Ctl			
RK07 Add-on Disk			
LA120 Console			
RSX11M Licence			
PDP11/44 SYSTEM (NEW)	£37,500		
11/24 CPU, 256KB, H9645			
Dual TUS8, H9642 Cab			
RJM02 67MB Disk & Ctl			
RM02 Add-on Disk			
LA120 Console			
RSX11M Licence			
PDP11/70 SYSTEM (NEW)	£78,000		
11/70 CPU, 512KB MOS,			
Data System Cab,			
RWM05 Disk Drive & Ctl,			
TWU77 Mag Tape & Ctl,			
LA120 Console			

HAZELTINE VDUs
SAVE UP TO 51%

HAZELTINE 1510 (MLP £880) Only **£550**

HAZELTINE 1520 (MLP £1050) Only **£625**

HAZELTINE 1552 (MLP £800) Only **£395**

HAZELTINE 1410 (MLP £475) Only **£295**

ADD 15% VAT TO ALL PRICES Carriage and Packing extra

Electronic Brokers Ltd., 61/65 Kings Cross Road, London WC1X 9LN. Tel: 01-278 3461. Telex 298694

Electronic Brokers

The lightweight mast with 101 applications

25 years in this specialist field



The smoothly operated QTM Mast comes fitted with handpump or can be vehicle mounted with 'Power Pack' for extension and retraction. Available in a range of heights up to 15 metres, the QTM mast can provide the ideal answer for:

- Mobile Radio Telephone
- Environmental - gas sampling collector
- Police Mobile HQ (UHF)
- Field Telecommunications
- Floodlighting
- Meteorology
- Anemometer and Wind Measurement
- And a host of other uses

CLARK MASTS

Find out more about the QTM series by writing or phoning:-

U.K.
CLARK MASTS LTD. (W.W.)
Evergreen House, Ringwood Road,
Binstead, Isle of Wight,
England PO33 3PA
Tel: Isle of Wight (0983) 63691
Telex: 86686

EUROPE
GENK TECHNICAL PRODUCTS N.V. (W.W.)
Woudstraat 21, 3600 Genk,
Belgium.
Telefoon 011-380831
Telex 39354 Genant B.

WW-041 FOR FURTHER DETAILS

TEST COMPONENTS ON THIS NEW OSCILLOSCOPE



...from **Farnell**

USE READER CARD FOR DETAILS

WW - 039 FOR FURTHER DETAILS

D.I.L. MINIATURE ON-OFF SWITCHES Gold-plated contacts. Sealed base. Ideal for programming. 6-position at less than half manufacturer's price. ONLY 75p Will fit into 14-pin DIL socket. Ten at 65p ea.; per 100 55p ea.	HONEYWELL PROXIMITY DETECTOR Integral amplifier, 8v. D.C. £3.50 ea. PHOTO CONDUCTIVE CELL £1.25. High-power Cds cell, 600mW, for control circuits. Resistance 800 ohm to 4K. Max. volts 240. Size 1/2 x 1/2in. RIBBON MICROPHONE with pre-amp. on chassis. £1.75.	MULLARD MODULES LP1171 AM, FM IF Strip Front end Pair £3.75 Complete with Data LP1180 varicap Med. & Long Tuner £2.50 LP1157 CRYSTALS COLOUR TV 4.433619 mc/s £1.25 Miniature type sealed	ULTRA SONIC TRANSDUCERS 40KC/S. Complete on 18in. Screened cable, £1.75 each; pairs £2.95. ULTRA SONIC TRANSMITTER Complete unit (encased requires 15V). £3.25. FOSTER DYNAMIC MICROPHONES 200 ohm impedance. Moving coil. Complete on chassis. £1.75 pair.
U.H.F. MODULATOR Latest type, adjustable, ideal for computers, with data circuit. Size 3x2 1/2 x 1 inch. Only £3.50 In screened case	LM380 Amplifier 85p LM318N Hi-Slew Op. Amp. £1.50 LM323K 5v. 3-amp. reg. £3.50 LM310N Volt. Follower Amp. £1.20 LM311H High Perf. Volt. Comparator £1.00 LM384N 5-watt Amp £1.20 LM393N Dual Com. 60p 7905 Reg. -5v. 75p	MINIATURE HIGH-QUALITY FANS "Whisper Model" by Roton. Low-power consumption (less than 10 watts). Silent running. 115v. (two in series for 230v.). 50/60Hz. Size 4 1/2 x 4 1/2 x 1 1/2in. ONLY £5.50 EACH incl. V.A.T. BRAND NEW 50% less than manufacturer's price	STEREO CASSETTE MECHANISMS 6 or 12 volt. Complete with Heads + Erase and Solenoid. Brand new. £5.50 ea. TV CENDERENCE POTS (LIM) 50 ohm ALL 50p 100 200 5K
MINIATURE EDGE INDICATOR METER With illuminated dial scale 0-10. F.S.D. 100 microamp. Size 1 1/2 x 1 1/2 x 1/2 deep. Only £1.65.	MONSANTO Half-inch + 1 Display High Intensity £1 each set of 4 £3.50 Common anode 14 Pin DIL Package	HEWLETT-PACKARD DISPLAYS 5082-7650 HIGH EFFICIENCY AND VERY BRIGHT. Only £1.00 each Set of 6 for £5 Half-inch red common anode will replace DLY14-pin DIL.	EX-MOTOROLA 5 + 5-WATT CAR STEREO AMPLIFIERS Complete and tested units. Medium and Long Wave. Supplied as two built units (5 x 2 x 2in.) with circuit and data. Only £5 pair. Includes pre-amp.
BRIDGE RECTIFIER 800 PIV 35 amps 1 1/2 x 1 1/2 x 1/2in. £3.50	STEREO CASSETTE TAPE HEADS. Quality replacement for most recorders with mounting plate. Record/Replay £2.00 MARRIOTT TAPE HEADS Quarter track. Type XRP518 Record/Replay (each) £2.00 XRP536 Record/Replay (each) £3.00 XES11 Erase (each) £1.00	"CHERRY" ADD-ON KEYPAD A compact 12-button keypad suitable for use with keyboard extend its functions plus four extra keys. Supplied brand new JUST PRICE £22.00 NOW PRICE ONLY £7.50 Incl. V.A.T.	
NATIONAL P.8080A Chips £2.95 6216 £1.75 IN448 DIODES Full spec. but no polarity band. Per 1,000. £10 MINIATURE M.P.C. POTENTIOMETERS Model M2. High-quality, 5% tolerance, 2-watt, with lin. spindles. All values, 47 ohms-47k only 60p each per 100; 50p each per 100; 40p each.	RECHARGEABLE BATTERIES VARTA 3.6 volts DEAC M/AH 225. £1.50 DRYFIT 6-volt, 4.5 amp. £7.50 XTAL FILTER 10.7 mc/s; 12.50B separation, 1 1/2 x 1 1/4 x 1 inch £7.00 100KCS + 1 meg. 3-pin £2.00		

QUANTITY DISCOUNTS on ALL items (unless stated), 15% per 10, 20% per 50, 25% per 100. All items **BRAND NEW** (unless otherwise stated).
DELIVERY from stock - Add post 35p per order.

HENRY'S EXPORT enquiries invited
01-723 1008/9

TELEX 262284
Transonics
Mono 1400

Callers to: 404 EDGWARE ROAD, LONDON W2 1ED
ALL MAIL ORDERS/EXPORT ENQUIRIES 11/12 PADDINGTON GREEN, LONDON, W2

WIRELESS WORLD AUGUST 1982

THE CASE FOR I.L.P.



Did you know

It's the chance every constructor wants



POWER AMPS



P.S.U.'s



PRE-AMP MODULES

It's something you have always wanted....something to build your equipment into that's smart, modern, strong, adaptable to requirement and not expensive. The 'UniCase' is yet another triumph of I.L.P. design policy. It presents totally professional appearance and finish, ensuring easier and better assembly to make it equal to the most expensive cased equipment. The all-metal 'UniCase' is enhanced by precision aluminium extruded panels engineered for speedy and perfect aligned assembly within a mere five minutes. Designed in the first case to accommodate I.L.P. power amps with P.S.U.'s, the range will shortly be extended to house any other modular projects.

WHAT WE DO FOR CONSTRUCTORS

Our product range is now so vast we cannot possibly hope to show it all in our advertisements without overcrowding or abridging information to the point of uselessness. So we have devised a solution which we invite you to take advantage of without delay. **ALL YOU NEED DO IS FILL IN AND FORWARD THE COUPON BELOW TO RECEIVE OUR NEWEST COMPREHENSIVE I.L.P. CATALOGUE POST FREE BY RETURN.** It gives full details of all current I.L.P. products for the constructor together with prices, full technical and assembly details, wiring and circuit diagrams etc. and it's yours, FREE. You don't even have to stamp the envelope if you address it the way we tell you.



FREEPOST 5
GRAHAM BELL HOUSE, ROPER CLOSE, CANTERBURY CT2 7EP
Telephone Sales (0227) 54778 Technical Only (0227) 64723 Telex 965780
FREEPOST
Mark your envelope clearly **FREEPOST 5** and post it **WITHOUT** a stamp to I.L.P. at address above. We pay postage when your letter reaches us.

I.L.P. are the world's largest designers and manufacturers of hi-fi audio modules?

I.L.P. pioneered encapsulated power amps and pre-amps for enhanced thermal stability, mechanical protection and durability?

There are TWENTY power amplifiers from 15 to 240 watts RMS including the very latest super-quality Mosfets to choose from?

TWENTY pre-amp modules allow you to incorporate exciting professional applications to your equipment never before available to constructors and experimenters?

I.L.P. are suppliers to the B.B.C., I.B.A., N.A.S.A., British Aerospace, Marconi, Racal, Ferranti, G.E.C., Rolls Royce etc?

Goods are despatched within 7 days of your order reaching us and covered by our 5 year no-quibble guarantee?

SEND COUPON (NO STAMP NECESSARY) FOR YOUR FREE I.L.P. CATALOGUE AND OPEN UP TO A NEW WORLD OF QUALITY & VALUE

To: I.L.P. ELECTRONICS LTD.
PLEASE SEND ME I.L.P. CATALOGUE, POST PAID BY RETURN

Name: _____
Address: _____

I HAVE/HAVE NOT PREVIOUSLY BUILT WITH I.L.P. MODULES


I.L.P. products are available also from Henry's, Marshall's, Technomatic & Watford.

WW - 024 FOR FURTHER DETAILS

WIRELESS WORLD AUGUST 1982


HART

LINSLEY HOOD CASSETTE RECORDER 2

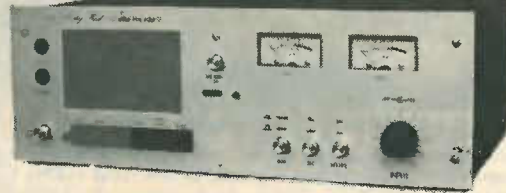

Our new improved performance model of the Linsley Hood Cassette Recorder incorporates our VFL 910 vertical front mechanism and circuit modifications to increase dynamic range. Board layouts have been altered and improved but retain the outstandingly successful mother-and-daughter arrangement used on our Linsley-Hood Cassette Recorder 1. This latest version has the following extra features: Ultra low wow-and-flutter of .09% - easily meets DIN Hi-Fi spec. Deck controls latch in rewind modes and do not have to be held. Full Auto-stop on all modes. Tape counter with memory rewind. Oil damped cassette door. Latching record button for level setting. Dual concentric input level controls. Phone output. Microphone input facility if required. Record interlock prevents rerecording on valued cassettes. Frequency generating feedback servo drive motor with built-in speed control for thermal stability. All these desirable and useful features added to the excellent design of the Linsley-Hood circuits and the quality of the components used makes this new kit comparable with built-up units of much higher cost than the modest, £94.90 + V.A.T. we ask for the complete kit.

LINSLEY HOOD CASSETTE RECORDER 1

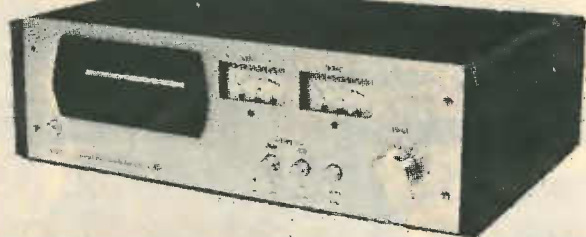

We are the Designer Approved suppliers of kits for this excellent design. The Author's reputation, tells all you need to know about the circuitry and Hart expertise and experience guarantees the engineering design of the kit. Advanced features include: High-quality separate VU meters with excellent ballistics. Controls, switches and sockets mounted on PCB to eliminate difficult wiring. Proper moulded escutcheon for cassette aperture improves appearance and removes the need for the cassette transport to be set back behind a narrow finger trapping slot. Easy to use, robust 'Lenco' mechanism. Switched bias and equalisation for different tape formulations. All wiring is terminated with plugs and sockets for easy assembly and test. Sophisticated modular PCB system gives a spacious, easily-built and tested layout. All these features added to the high-quality metalwork make this a most satisfying kit to build. Also included at no extra cost is our latest HS 16 Sendus Alloy super head, available separately at £8.20 but included free with the complete kit at £75 plus VAT. Reprints of the 3 original articles describing this design 45p. No VAT. Reprint of the subsequent postscript article 30p. No VAT.

PRACTICAL WIRELESS 'WINTON' TUNER

Brilliant new Ted Rule designed Tuner with everything! Gives you fantastic stereo f/m reception with pilot cancelling decoder i.c., fluorescent display, digital frequency readout along with clip and timer functions. In addition to f.m. covers l.w., m.w., s.w. and even TV sound. Further details are in our lists; send for your copy.

Part Cost of Post, Packing and Insurance
Order up to £10 - 50p
Orders £10 to £49 - £1 P&P
Over £50 - £1.50 Export Orders - Postage or shipping at cost plus £2 Documentation and Handling

Please send 9 x 4 S.A.E. or telephone for lists giving fuller details and price breakdowns.

Instant easy ordering, telephone your requirements and credit card number to us on Oswestry (0691) 2894.

ERASERS FOR THE DEVELOPMENT LAB



UVIT
Powerful, compact unit to erase up to six EPROMs quickly and safely. 10-60-minute electronic timer. £59.13 + V.A.T.

UVIB
As above but without timer. £46.95 + V.A.T.

Carriage paid (U.K.)
Send cheque or official order for prompt delivery.


Also available in London from:
Technomatic Ltd
Henrys Radio
Ambit International

IN USE IN DESIGN LABS & EDUCATIONAL ESTABLISHMENTS AROUND THE WORLD

NORTHERN ELECTRONICS
51 Arundel Street, Mossley, Lancashire Tel: Mossley (04575) 4119

WW - 047 FOR FURTHER DETAILS

LINSLEY-HOOD 300 SERIES AMPLIFIERS

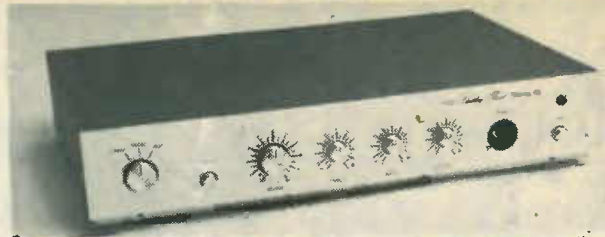

These latest designs from the drawing board of John Linsley-Hood, engineered to the very highest standard, represent the very best that is available on the kit market today. The delicacy and transparency of the tone quality enable these amplifiers to outperform, on a side-by-side comparison, the bulk of amplifiers in the commercial market-place and even exceed the high standard set by his earlier 75-watt design. Three versions are offered, a 30-watt with Darlington output transistors, and a 35- and 45-watt, both with Mosfet output devices. All are of identical outside appearance which is designed to match and stack with our Linsley-Hood cassette recorder 2. As with all Hart kits the constructors interests have been looked after in a unique way by reducing the conventional (and boring) wiring almost to the point of extinction. Any of these kits represents a most cost-effective route to the very highest sound quality with the extra bonus of the enjoyment of building a sophisticated piece of equipment. 30-watt Darlington amplifier, fully integrated with tone controls and magnetic pick-up facility. Total cost of all parts is £81.12. Special offer price for complete kits £72. 35-watt Mosfet amplifier. Total cost of parts £98.41. Special offer for complete kits, £87.40. 45-watt Mosfet amplifier. Total cost of parts £104.95. Special offer price for complete kits £94.80. Reprints of original Articles from Hi-Fi News 50p. Post free. No VAT. Reprints of MOSFET article 25p. No V.A.T. Post free.

FEED YOUR MICRO BYTES WITH OUR SOLENOID CONTROLLED CASSETTE DECK



Front loading deck with full solenoid control of all functions including optional read in fast wind modes. 12 volt operation. Fitted 3-digit memory counter and Hall IC Motion Sensor. Standard erase and stereo R/P Heads. Cheapest price ever for all these features. Only £38.90 plus VAT. Full technical specification included.

HART TRIPLE-PURPOSE TEST CASSETTE TC1

One inexpensive test cassette enables you to set up VU level, head azimuth and tape speed. Invaluable when fitting new heads. Only £2.70 plus V.A.T. and 50p postage.

CASSETTE HEADS

HS16 SENDUST ALLOY SUPER HEAD. Stereo R/P. Longer life than Permalloy. Higher output than Ferrite. Fantastic frequency response. Complete with data.....	£8.20
HC20 Stereo Permalloy R/P head for replacement uses in car players, etc.....	£4.25
HM90 Stereo R/P head for METAL tape. Complete with data.....	£7.20
H51 Special Erase Head for METAL tape.....	£4.50
H524 Standard Ferrite Erase Head.....	£1.50
4-Track R/P Head. Standard Mounting.....	£7.40
R484 2/2 (Double Mono) R/P Head. Std. Mtg.....	£4.90
ME151 2/2 Ferrite Erase. Large Mtg.....	£4.25
CCE/8M 2/2 Erase. Std. Mtg.....	£7.90

All prices plus VAT

HART

HART ELECTRONIC KITS LTD
OSWESTRY
SHROPSHIRE
phone (0691) 2894
Telex 35861
Hartel G

IN VIEW OF THE EXTREMELY RAPID CHANGE TAKING PLACE IN THE ELECTRONICS INDUSTRY, LARGE QUANTITIES OF COMPONENTS BECOME REDUNDANT. WE ARE CASH PURCHASERS OF SUCH MATERIALS AND WOULD APPRECIATE A TELEPHONE CALL OR A LIST IF AVAILABLE. WE PAY TOP PRICES AND COLLECT.

BROADFIELDS & MAYCO DISPOSALS

21 Lodge Lane, N. Finchley, London, N.12. 5 mins. from Tally Ho corner
Telephone 445 2713/0749 (9461)

WW - 043 FOR FURTHER DETAILS



Bigger and Better for 1982
the colourful Wilmslow Audio brochure
- the definitive loudspeaker catalogue!

Everything for the speaker constructor - kits, drive units, components for HiFi and PA.

50 DIY HiFi speaker designs including the exciting new dB Total Concept speaker kits, the Kef Constructor range, Wharfedale Speakercraft, etc.

Flatpack cabinet kits for Kef, Wharfedale and many others.

- ★ Lowest prices — Largest stocks ★
- ★ Expert staff — Sound advice ★
- ★ Choose your DIY HiFi Speakers in the comfort of our ★ two listening lounges (Customer operated demonstration facilities)
- ★ Ample parking ★

Send £1.50 for catalogue (cheque, M.O. or stamps - or phone with your credit card number)

★ Access - Visa - American Express accepted ★ also HiFi Markets Budget Card.



0625 529599

35/39 Church Street, Wilmslow, Cheshire SK9 1AS

Lightning service on telephoned credit card orders!

WW - 007 FOR FURTHER DETAILS

RADIOCODE CLOCKS

are powerful and comprehensive instruments which receive, decode and analyse time-coded standard frequency transmissions to provide accurate, secure and completely automatic time/calendar or synchronisation systems.



- Applications**
- Automatic master clock and slave controller.
 - Synchronisation of separate equipment and events.
 - Programmable energy management system.
 - Computer clock/calendar with battery backup.
 - Data logging and time recording.
 - Process and equipment control.
 - Broadcasting, Astronomy, Navigation.
 - Satellite tracking.

If you have a time or synchronisation problem, write or phone for further details of our portable and new microcomputer-controlled Radiocode Clocks.

Circuit Services, 6 Elmbridge Drive
Ruislip, Middlesex. Ruislip 76962

WW - 034 FOR FURTHER DETAILS

The Keithley 179A



A MEASURE OF ACHIEVEMENT.

Specification... Versatility... Accuracy... Price. In almost every major area the new 179A - a 4 1/2 digit bench/portable DMM - from Keithley Instruments sets some pretty impressive standards:

- 20 amp capability
- Full function: 27 ranges including true RMS AC Measurement
- Year's guarantee on spec
- 0.04% DC accuracy
- IEEE option
- Large display and 10µV dc resolution.

For those requiring 10 times more sensitivity and an analogue output there's the 177, a unit with similar specification to the 179A. Both models are part of a vast range of test equipment from one of the world's leading manufacturers.

For more information fill in the coupon at the bottom of the page.

Alternatively, phone our Instant Information Service on 0734 864784 now.

KEITHLEY

Keithley Instruments Ltd
1 Boulton Road Reading Berkshire RG2 0NL
Telephone (0734) 861287
Telex 847047

I'd like to know more...

Name _____

Position _____

Company _____

Address _____

Telephone _____

(WW/8)

WW - 028 FOR FURTHER DETAILS



The over and outperformer

SHURE

You simply can't make it
any clearer.

For the address of your nearest dealer together with full details of the Shure Microphone range, write to:
Shure Electronics Ltd., Eccleston Road, Maidstone ME15 6AU or telephone: 0622 59881.

WW - 050 FOR FURTHER DETAILS

wireless world

... By any other name ...

In a recent Letter to the Editor, a reader described his feelings at seeing a copy of *Wireless World* for the first time after a long interval. On seeing the content, he felt impelled to write and suggest that the journal might benefit from a change of title, to take account of the fact that the World is now rather more computer-shaped than it was when wireless was the current miracle.

The letter constitutes cast-iron evidence to support the assertion, made by *WW* staff for seventy years, that one simply cannot produce a journal like this — the whole thing is logically impossible. Philosophy and printed boards, audio amplifiers and microcomputers, exposure meters and clocks do not, it must be admitted, appear to share much common ground. Neither, indeed, do the types of reader to whom our articles are addressed: the enthusiast making an amplifier on the corner of the kitchen table experiences but modified rapture at the prospect of an article on Rademacher-Walsh functions, though he may read it and be interested. The professional engineer does not require instruction in the design of an a-to-d converter, but he might want to build the digital voltmeter to which the article is an introduction. And one of the continuing arguments on basic physics possibly leaves both of them glassy-eyed, but nonetheless entertained.

The fact is, of course, that *Wireless World* is a hybrid in so many senses that it almost defies description. Both professionals and amateurs read it; the articles it contains are theoretical, or practical, or both; its topics cover the field from logic design to a discussion of the best material with which to stuff loudspeaker enclosures and from

descriptions of optical-fibre communications systems to a design for an electronic cat-door.

In all this, the one common factor is electronics, in its wider sense. It leads us into any subject in which it is used — optics, chemistry, motoring, aviation — in addition to the more familiar area of telecommunications. Computers happen to be an important manifestation of electronic engineering and are therefore completely within our field of interest.

"Wireless" as a word disappeared in the forties or thereabouts, at around the time when "electronics" was born. But even then, *Wireless World* had been in existence for thirty-five years and its title was far too well known for Iliffe to risk causing an outcry by changing it.

Forty years on, computers, microprocessors and a mass of other digital circuitry have edged out the more traditional forms of electronic design — even sound reproducing is becoming digital in form. As this happens, it is clear that the content of the journal must change to meet new requirements, which is why a newcomer glancing at our contents page immediately after a look at the *Wireless World* logo might justifiably feel puzzled. If, however, a change of name after thirty-five years was felt to be too much of a shock for readers to bear, how much more of a jolt would it be after seventy-one?

The name is unimportant, except inasmuch as it sometimes misleads the casual bookstall browser and, perhaps, the not very well informed advertising agent. What is important is that the content should treat all aspects of electronics, which it will continue to do, no matter in what unexpected directions the subject leads us.

Editor:
PHILIP DARRINGTON

Deputy Editor:
GEOFF SHORTER, B.Sc.
01-661 8639

Technical Editor:
MARTIN ECCLES
01-661 8638

News Editor:
DAVID SCOBIE
01-661 8632

Drawing Office Manager:
ROGER GOODMAN

Technical Illustrator:
BETTY PALMER

Advertisement Manager:
BOB NIBBS, A.C.I.I.
01-661 3130

DAVID DISLEY
01-661 8641

BARBARA MILLER
01-661 8640

Northern Sales:
HARRY AIKEN
061-872 8861

Midland Sales:
BASIL MCGOWAN
021-356 4838

Group Classified Manager:
BRIAN DURRANT
01-661 3106

IAN FAUX
01-661 3033

Production:
BRIAN BANNISTER
(Make-up and copy)
01-661 8648

80-100W MOSFET AUDIO AMPLIFIER

The final section of this three-part article describes the complete amplifier circuit in detail, with the addition of a loudspeaker protection circuit.

by J. L. Linsley Hood

In the earlier parts of this article I discussed some of the design requirements of power mosfet audio amplifiers and described the evolution of a high-gain, symmetrical, class 'A' driver stage suitable for use with a power mosfet output. Inevitably, the final design of the gain stage, as shown in the completed power amplifier circuit of Fig. 14, shows some minor differences in comparison with the basic voltage-amplifier circuit, which underlines the point that any final design represents only the small tip of a large submerged iceberg of design effort. Unless one is lucky, or one's target performance is relatively modest, or one has considerable experience with closely similar designs, there is always a large amount of work necessary to convert a reasonably satisfactory basic design into a final version having, as nearly as possible, a blameless performance under all conceivable test conditions.

Design considerations

The choice of output power rating for any power amplifier is, inevitably, somewhat arbitrary and depends on the voltage ratings of the available components, and on the cost of the power transformer, smoothing capacitors and heat sinks which one is

prepared to afford. However, in practical terms, the major considerations which limit the possible output power are the voltage ratings of the output devices, and of the available electrolytic reservoir capacitors.

The output power mosfets I decided to use are the complementary n-channel and p-channel devices from Hitachi, since they are readily available, are reasonably inexpensive, appear to be adequately rugged, and have useful power ratings. These particular mosfets are available in peak working voltages up to 160V. However, there are other similar devices, either available now or promised in the near future, from Fairchild, Motorola, Ferranti, Supertex, International Rectifier and Intersil, so it seems likely that a design based on complementary power mosfets will not restrict the user to a single source of components.

Some earlier experiments with mosfet-output audio amplifiers had shown that the

r.m.s power output could be related to the available supply voltage in the manner shown in Fig. 15, over the range 25-100 watts. Since it had been decided, for various reasons, to use a symmetrical positive and negative supply, 63V electrolytic capacitors on each half would allow a safe working voltage, overall, of 120 volts, equivalent to a $\pm 60V$ supply. In practice, the limited regulation of a simple rectifier-capacitor power supply is likely to reduce this, on load, to some $\pm 55V$, giving an overall power output of 80 watts.

This output power requires a voltage swing of 25.3V r.m.s. across an eight ohm load, and if it is desired to drive this from an input voltage of '0VU' - which in audio-engineering terms implies 0.775V r.m.s. at a 600 ohm source impedance - the gain will require to be 32.6, which gives a suitable feedback resistor combination of 33k and 1041 ohms - though, in the event, for other considerations, it was decided to make this 1012, made up from a 1k and an 12 ohm series chain.

In the interests of d.c. symmetry, the input-circuit resistance should be also of the order of 33k. The values suggested are adequately close to this.

The performance of any feedback ampli-

fier under transient (step-function or square wave) input conditions is helped if the input rise time can be limited. This can be done most easily by an input RC integrating network, R_2C_2 , which gives a -3dB point at about 30kHz, allowing an adequate bandwidth for audio use.


A 470 ohm trimmer potentiometer in the emitter circuit of the input long-tailed pair allows accurate d.c. balance to be obtained with transistors having normal commercial spreads in V_{be} values and current gain. This is bypassed by a 100 μ F tantalum bead capacitor to avoid loss of open-loop a.c. gain. The output d.c. potential may be adjusted by means of this potentiometer to 0V, $\pm 20mV$.

Circuit performance depends strongly on the characteristics of the 'tail' of the 'long-tailed pair'. For correct operation of any such circuit, the dynamic impedance of the tail should be very large in comparison with the impedance as seen at the emitters of Tr_1 and Tr_2 . Also, ideally, to minimize common-mode problems, the current from this source should be largely independent of the dynamic emitter potentials. Finally, the tail circuit should provide an adequate isolation from unwanted signal components on the supply line. A junction fet satisfies all these requirements very fully, and also allows, as explained above, control of the operating current in the second-stage class A amplifier. To allow a wider range of negative supply-line voltages, the negative-line supply to this fet is derived from a Zener-diode-stabilized -12 volt source. The use of a separate power supply for the driver stages is of considerable assistance in avoiding the performance degradation which can occur due to the intrusion of distorted signal potentials from the high-current output stage.

The second stage, class 'A', voltage amplifier is similar to that shown earlier in Fig. 13, except that conventional, two-transistor, constant-current sources are used as the loads for each half, and that a small amount of a.c. positive feedback is derived from the output of Tr_5 , through R_8 and R_7 , in addition to the current stabilizing d.c. negative feedback path through R_9 to Tr_3 . The positive feedback restores the open loop a.c. gain to the 500,000 figure, over the frequency range 100Hz-3kHz, obtainable from the less d.c. stable configuration of Fig. 12.

The output power mosfets require a quiescent current value of 100mA for optimum performance - although it is difficult, because of the efficient operation of the n.f.b. loop, to see any significant change in the distortion residues, as this is adjusted, at any frequency below 10kHz - and this quiescent current is largely independent of the output device temperature. The 'amplified diode' circuit of Tr_{10} is not, therefore, used to sense the output transistor temperature, but used simply to generate a reasonably constant voltage drop.

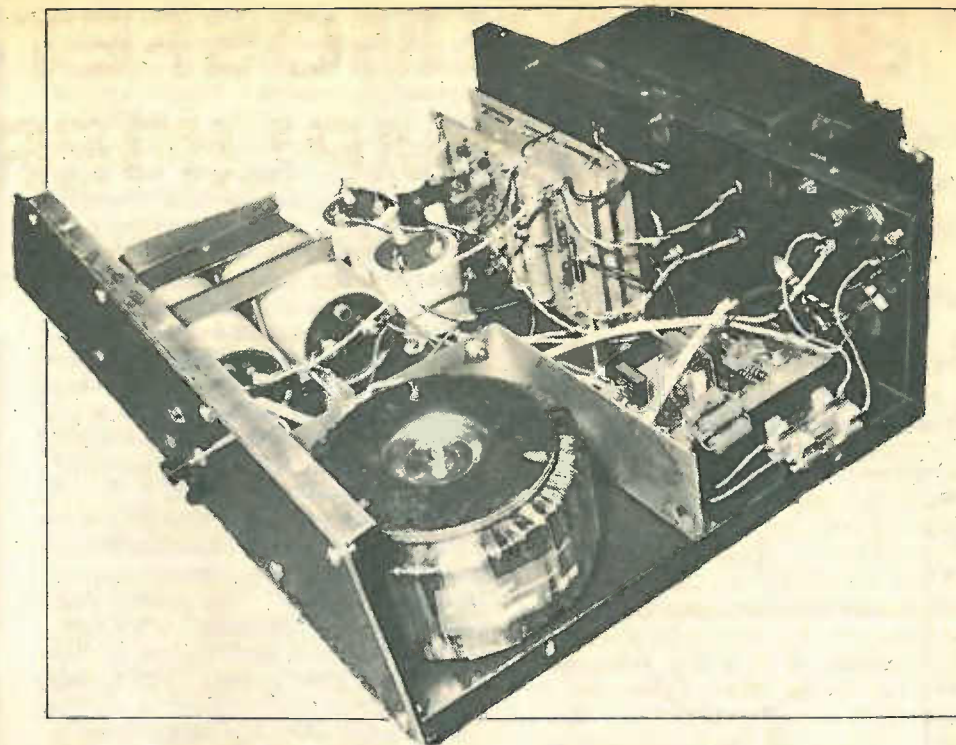Although the output devices present a very high l.f. input impedance, the effect of the 120pF total gate-source capacitance cannot be ignored, and the current



Prototype amplifier. Loudspeaker protection circuit is at rear right.

through Tr_6 - Tr_7 must be enough to avoid any slew-rate limiting within the rise-time levels allowed by the input CR network, (R_2C_2). A current of 7mA is adequate for this, and permits worst-case dissipations of 900mW for $Tr_{4,7}$ and 450mW for $Tr_{5,6}$, which are within their limits.

Since the Hitachi output devices are not protected by internal Zener diodes, it is unnecessary to exclude the possibility of reverse gate biasing, provided that this is within the $\pm 14V$ gate-source breakdown voltage limits. This gate breakdown protection can therefore be provided by a pair of back-to-back 8V zeners, while the gate-source capacitance and the 680 ohm gate 'stopper' resistor will exclude the possibility of very rapid extraneous noise pulses which could escape Zener limiting due to lead inductance or turn-on time delays. Ideally, $R_{17,19}$ and the Zeners should be mounted close to the power mosfet pins.

Feedback loop, and loop stability

Although the use of a two-stage voltage amplifier will not automatically guarantee, under all load conditions, that the internal phase shift will not approach 180° until the open-loop gain is negligible, the necessary conditions for an adequate phase margin, at unity gain, are very much easier to contrive in circuits in which only two successive gain stages are employed - provided that the additional phase shift of any other element in the feedback path is small enough to be neglected.

Unfortunately, in the case of the conventional junction-transistor Darlington or compound (p-n-p/n-p-n) emitter follower this additional phase shift is significant, even at a few hundred kilohertz where the loop gain is still high, so this loop gain must be artificially reduced at higher frequencies to preserve closed-loop stability. Two basic methods exist for this, of which the first, and simpler, is simply to connect an external capacitor across the whole of the gain stage so that this acts as an inte-

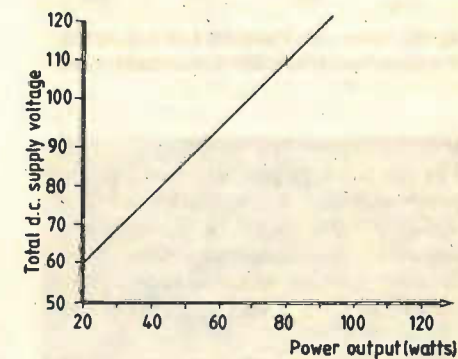


Fig. 15. Amplifier output power as function of supply voltage.

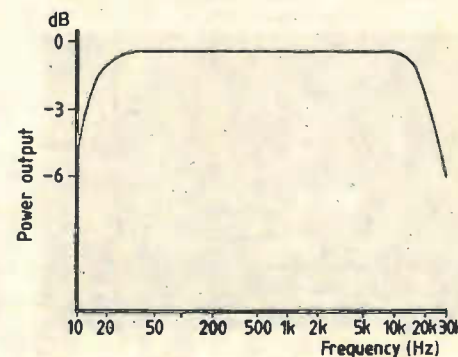


Fig. 16. Power bandwidth of amplifier.

gration network with a gain decreasing linearly by 20dB/decade from some l.f. break point. This has the advantage of allowing a wide phase margin of stability, and predictable performance characteristics. The second method is to tailor the h.f. performance so that it is maintained at as high a level as possible up to the point at which the loop phase shift approaches 180°, and then to reduce the gain rapidly, in a manner chosen not to exceed the 180° stability threshold, until it is less than unity.

This method is commonly employed in

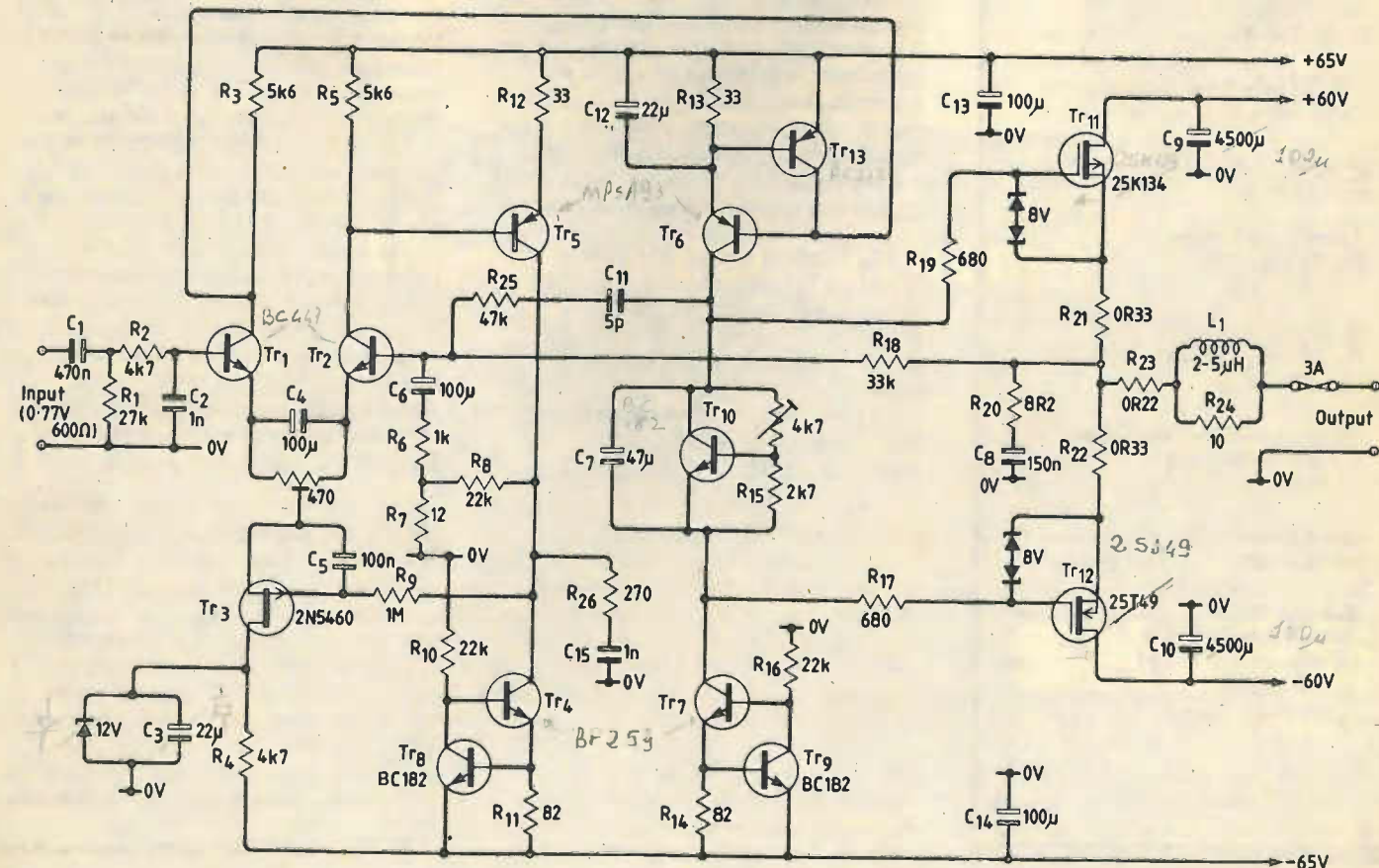


Fig. 14. Complete circuit diagram of the 100W amplifier.

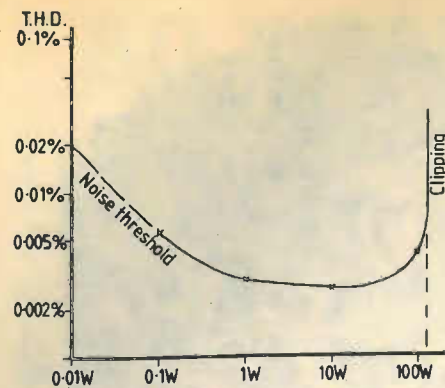


Fig. 17. Harmonic distortion as a function of output power (1kHz, 8Ω load).

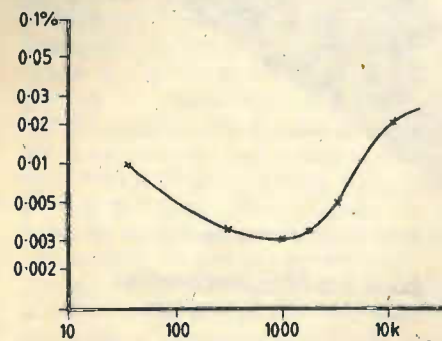


Fig. 18. Harmonic distortion as a function of output frequency (80W, 8Ω load).

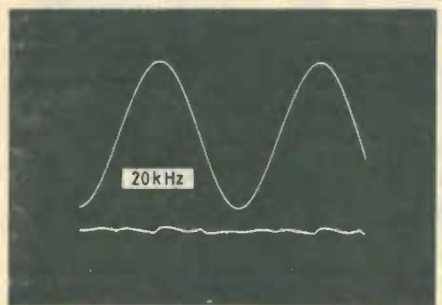
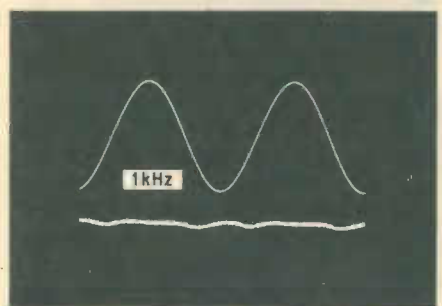
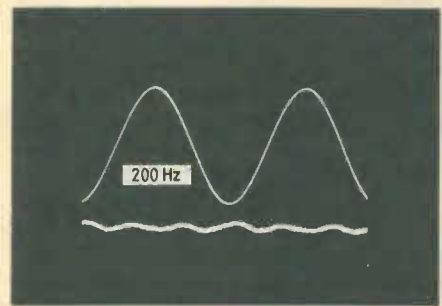


Fig. 19. Harmonic distortion residues at 80W/8Ω for 200Hz, (0.004% mainly second harmonic), 1kHz (0.0025%) and 20kHz (0.025%).

commercial transistor amplifier designs, often by the simple artifice of a capacitor between collector and base of the second stage amplifier transistor, because it allows better h.f. t.h.d. figures — and consequently better reviews in the 'Hi-Fi' journals. It does, however, carry with it the penalty that the phase margin of the amplifier is less good, with a consequently inferior transient response — manifest in respect of a less good 'settling time' — and a less predictable performance with differing loudspeaker load characteristics. In addition, the internal slew-rate limiting imposed by the second-stage collector-base capacitance (which is the mechanism by which the h.f. gain is reduced) leads to the predictable problem that signals accompanying large transient inputs will be blotted out during the period in which the amplifier is slew-rate limited. This is the phenomenon called 'Transient Intermodulation Distortion' by Otala⁷. This problem does not exist with the first method of h.f. compensation. A very good analysis of this problem was given by Jung⁸ (with a small addendum by myself⁹).

The biggest advantage, in this respect, conferred by power mosfet output devices, is that the inherent phase-shift of the output emitter-follower impedance conversion stage is sufficiently small that it may be neglected up the megahertz region. This means that, with care, feedback audio amplifiers having high orders of negative feedback (open-loop gain) can be designed without the need for any external control of h.f. gain, and which will exhibit the desirable characteristics given by systems in which the gain decreases with frequency at 20dB/decade, and the loop phase shift does not significantly exceed 90°.

Influence of negative feedback

The use of negative feedback is, unfortunately, not as well understood, even among electronics engineers, as one might sometimes wish, and this misunderstanding has spilled over into the more emotive, and less logical, realm of the 'Hi-Fi' fraternity, where the ill effects attendant upon the improper use of this technique have encouraged the attempt to design amplifiers believed by their authors to employ no negative feedback whatever — a case of discarding the baby along with the bath water, if there ever was one.

The necessary conditions which must be satisfied if the potential benefits are to be gained have been examined both by Baxandall^{10,11,12}, in his series on audio amplifier design in this journal, and also, from a different angle, by *Wireless World's* own Cathode Ray¹³. The message from all these contributions, if I may presume to precis, is that the amplifier in question must be made as linear as possible before negative feedback is applied; that the gain — at the frequency under consideration — must be enough, or the customary simplification of the mathematics will be inappropriate; and that a small amount of n.f.b., by injecting into the input an additional distorted signal, will worsen the harmonic distortion which would have been present without it.

Translated into design requirements,

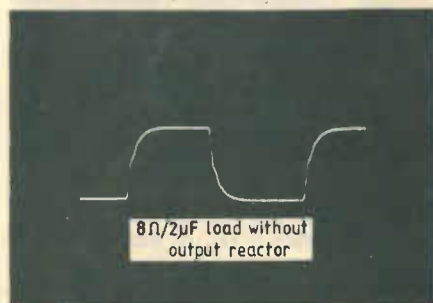
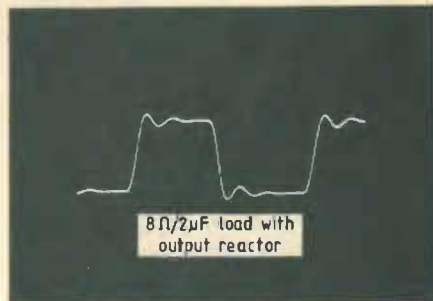
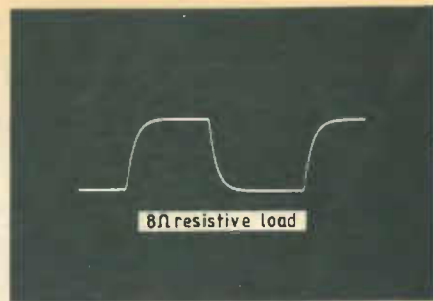


Fig. 20. Response of amplifier to 10Vp-p 100kHz square wave on resistive and reactive loads, with and without output inductor.

this implies that a high stage gain, coupled with good linearity and the lowest practicable phase shift, is the necessary design objective — most easily attained if not more than two gain stages are employed. The inclusion of a positive feedback path within the overall n.f.b. loop as a means of increasing the loop gain brings with it some supplementary requirements. These are that the phase shift within the positive feedback loop must be very small over the range of interest, since the p.f.b. will worsen it, and that the linearity of this part of the circuit must be much better than that of the remaining circuit outside the p.f.b. loop, or the benefits will be negated. Looked at in this light, the use of a bootstrapped driver load in an audio amplifier is not well advised, since the loop containing the 'bootstrap' will include the output devices whose linearity it is desired to improve.

In the particular case of the feedback loop built around Tr₂, Tr₅, R₈ and R₇, the linearity of this is very good because it is only driving a high-value resistive load, and the dominant phase shifts are those due to C₆ at the l.f. end, and the circuit stray capacitances in Tr₅ collector circuit at the h.f. end of the pass band. This gives a phase-linear bandwidth which is greater than that of the overall n.f.b. gain loop, and therefore satisfies the conditions for

improving the overall amplifier performance.

Because of the capacitive nature of the load presented to Tr₆ by the gate-source capacitance of the power mosfets, the h.f. loop gain of the amplifier falls below unity at about 30MHz, which is sufficient to give an adequate margin of stability, while still allowing some 60dB of negative feedback at 30kHz, the chosen upper operating frequency limit. No additional h.f. roll-off components are required.

Stability with capacitive loads

A minor problem associated with power mosfets, discussed by Hitachi in their design note¹⁴ is that the very high-frequency — 3dB point of the mosfet used as a source follower (typically 30-40MHz for the Hitachi devices) allows the inductance of the internal gate-contact lead — some 70nH — to produce a negative resistance condition, with consequent parasitic oscillation, under conditions of small capacitive load (0.01μF-0.22μF). Oscillation, under these conditions, but due to other causes, is not uncommon in audio amplifiers, and can be the cause of amplifier failure when used with the so-called low-impedance loudspeaker cables, even when the amplifier is completely stable under the 8ohm/2μF load combination frequently chosen by reviewers. Needless to say, this possibility of parasitic oscillation should be avoided and this is most easily done in this type of design by the inclusion of a small inductor of some 5μH inductance, (20 turns of 24s.w.g. enamelled wire, wound round the case of a 10ohm, 1watt carbon-rod resistor) in the output lead to the loudspeaker load.

This output inductance has two practical effects, apart from the avoidance of parasitic oscillation. The first of these is to reduce the total harmonic distortion of the circuit, as measured at the output at high audio frequencies, simply because it acts as an output low-pass filter. The second effect, due to the same cause is a 'ripple' on the square-wave/reactive-load test waveform, which is an inevitable effect of any steep-cut, low-pass filter. Without this output inductor, the 8ohm/2μF test waveform is smoothly rounded and free of any overshoots.

Output stage protection

Because of the freedom of power mosfets from secondary breakdown, and because they have an inherent positive temperature coefficient of resistance, output stage protection can be much simpler than is the case with normal junction transistors, and a simple fuse in the output circuit is quite adequate. This has a practical advantage over many of the electronic protection methods normally employed, in that it avoids hard clipping under dynamic conditions when the amplifier is required to drive fast h.f. transients into loudspeakers having a low h.f. impedance.

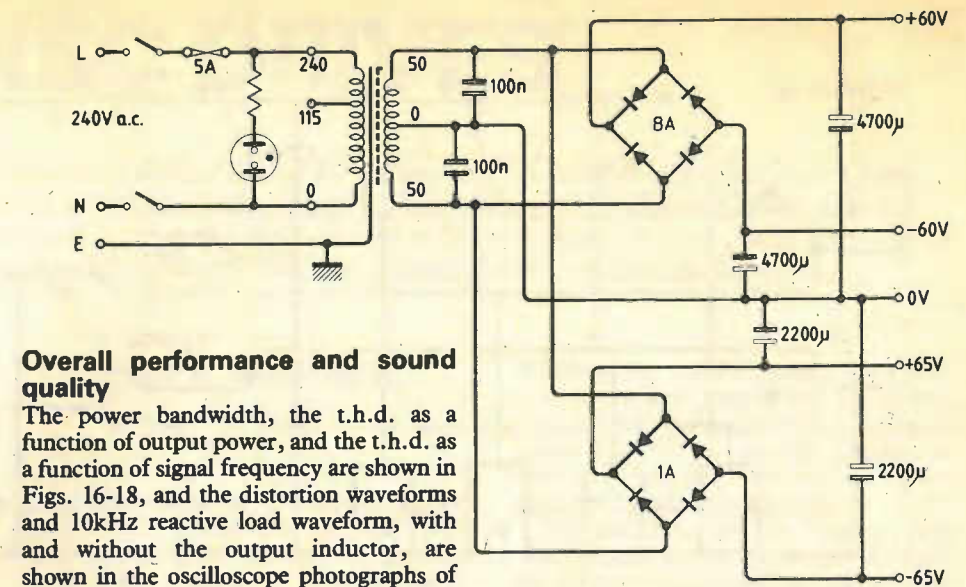


Fig. 22. Power supply used in prototype.

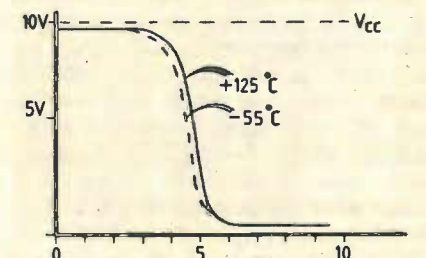


Fig. 23. Typical transfer characteristic of c.m.o.s. gate.


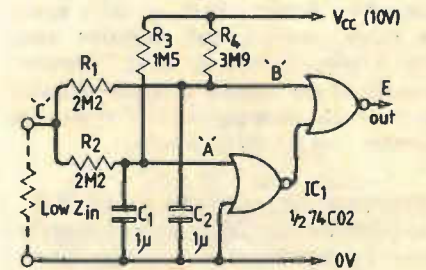


Fig. 24. Input d.c. level monitor using c.m.o.s. Nor.

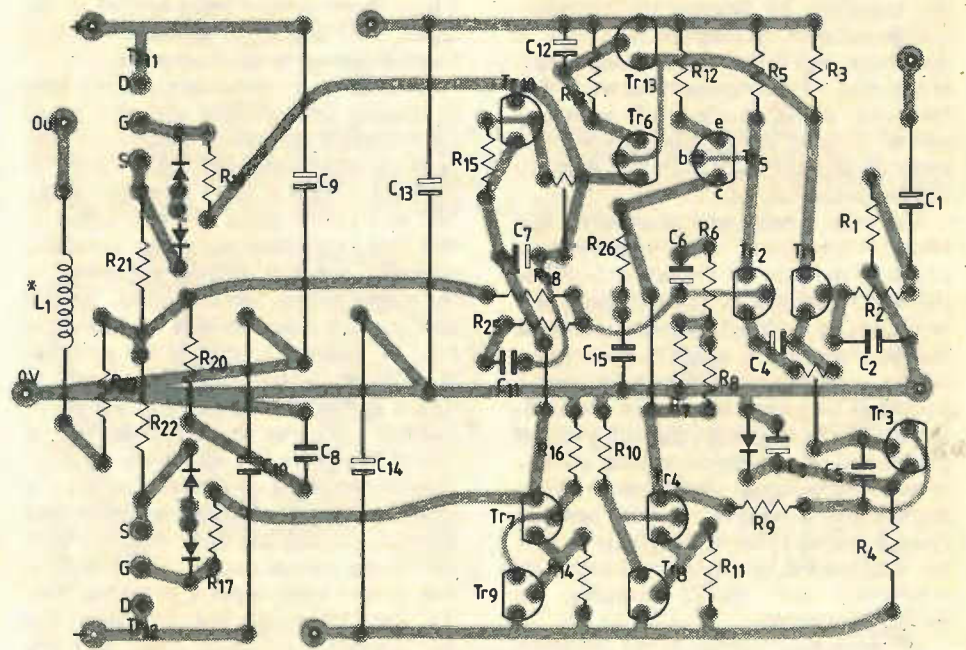

* L₁ is wound on R₂₄

Fig. 21. Printed-board for power amplifier.

DISC DRIVES

When a read/write head's position is determined by information on the disc surface, data-storage capacity can be greatly increased. As shown here, there are different methods of applying this technique which, in the case of a drive with ten discs in one pack, can increase the storage capacity four times despite a loss of 5% in data storage area.

by J. R. Watkinson
B.Sc., M.Sc.,

During track following, the correct position for the servo head is with half of each type of track beneath it. The read/write heads will then be correctly centred on their respective data tracks. This relationship is illustrated in Fig. 4.

The amplitude of dibits from A tracks with respect to the amplitude of dibits from B tracks depends on the relative areas of the servo head which are exposed to the

pulse will be negative. In addition, the A-track dibits are shifted by one half cycle with respect to the B-track dibits. The width of the magnetic circuit in the servo head is equal to the width of a servo track.

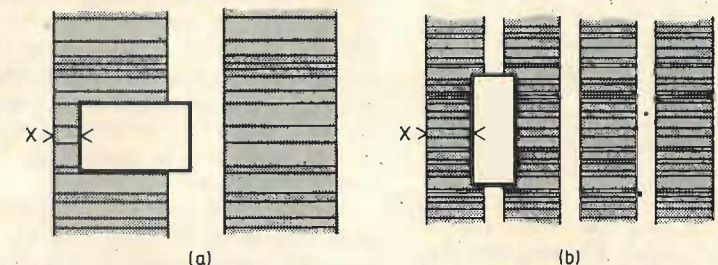


Fig. 1. At (a), misalignment x has little effect on the output signal, but at (b), the same misalignment in a system using four times greater track density causes unacceptable errors in the read signal. Distance x is not to scale.

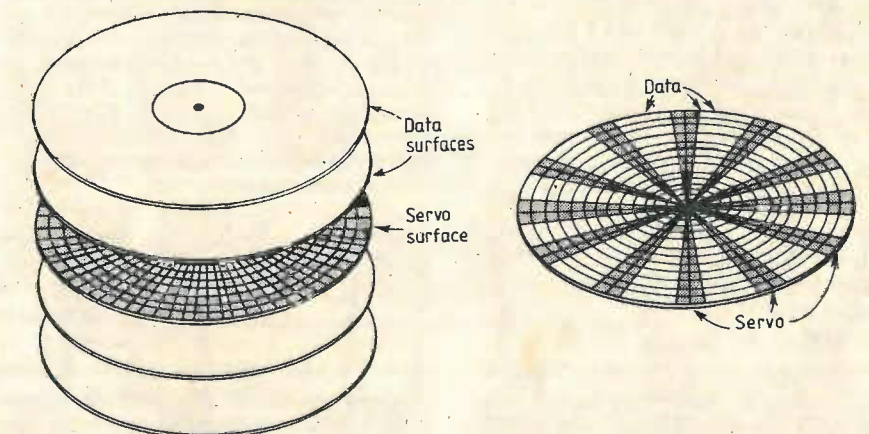


Fig. 2. In a multi-platter disc pack, one surface is dedicated to servo information, left, but as the number of platters in a pack falls, the percentage of data storage area lost to servo information rises. For this reason, some discs have servo information embedded in the data on the same side, as in the case of the single platter, right.

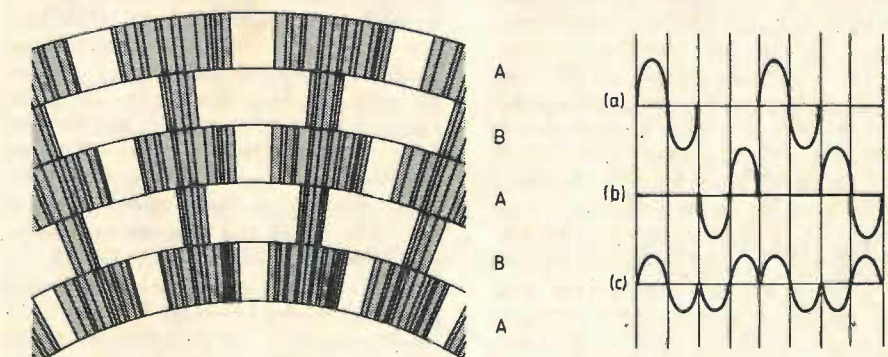


Fig. 3. The servo surface, left, has two types of track, A and B, which are 180° out of phase with each other and have opposite polarities. Waveform (a) results when the servo head is directly above track A, and waveform (b) appears when the head is above track B. When the head is correctly positioned, waveform (c) results.

Possibly the most significant event in the history of disc storage was the introduction of the servo-surface drive. Through the virtual elimination of thermal effects on head positioning, servo-surface drives, in which the head's position relative to the disc is determined by information on the disc surface, allow great increases in data storage density.

Changes of temperature in relatively simple disc-drive positioners, such as those discussed in the June issue of *Wireless World*, do not only affect accuracy through expansion and contraction in mechanical components such as head cantilevers. Thermal drift in the cylinder transducer and associated circuits also causes problems. How temperature changes limit the number of tracks on a given disc is illustrated in Fig. 1.

Because the position-error signal in a servo-surface disc drive is derived from a head reading the disc, these problems are drastically reduced. In a multi-platter drive, one surface of the pack holds servo information, which is read by the servo head. All of the read/write heads move with the servo head. In a ten-platter pack, this means that 5% of the usable data storage area is lost, but this is unimportant since the track density in a drive with a servo surface can be typically four times greater than in a drive without one.

Using one side of a single-platter cartridge for servo information would be unacceptable as it represents 50% of the usable data storage area so, in this case, servo information is interleaved with sectors on the read/write surfaces. Disc drives using this technique are usually referred to as 'embedded servo' drives.

Figure 2 shows the essential features of these two main categories of servo-surface drive, which will be described in turn.

Servo surface

As stated, one surface of the disc pack contains information to control the positioner. This surface is written when the disc is manufactured and, should it become corrupted, must be rewritten on special machine known as a servo writer.

The key to the operation of the servo surface is the way in which it is recorded by the servo writer. Recorded transitions are in adjacent pairs known as dibits, separated by a space, and Fig. 3 shows that there are two distinct types of servo track. On an A-type track, the first transition of the pair will cause a positive pulse on reading, whereas on a B-type track, the first

Digital Equipment Co.

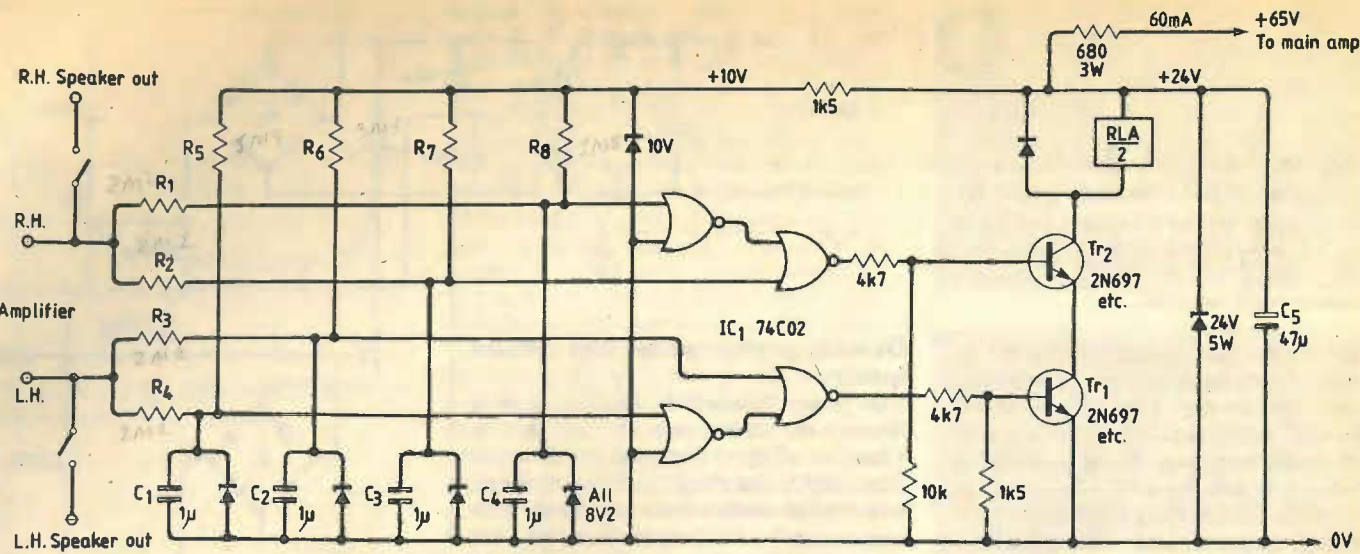


Fig. 25. Complete two-channel loudspeaker protection circuit with switch-on delay.

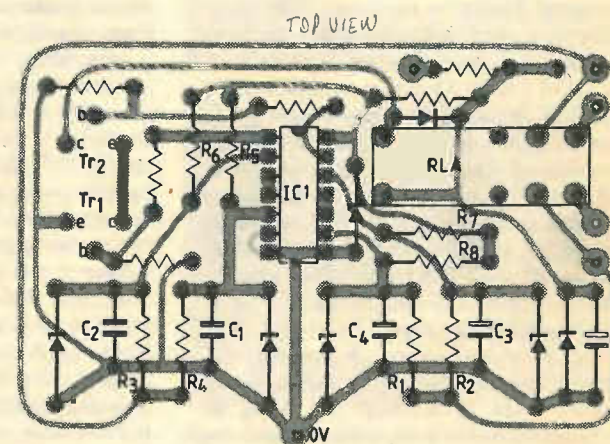


Fig. 26: Layout of printed board for circuit of Fig. 25.

Power supply

A suitable power supply circuit is shown in Fig. 22. As mentioned above, the output power of the amplifier depends almost entirely on the supply line voltages, and the original design was based on a conventional 'E' and 'I' cored transformer with a nominal 50-0-50 secondary winding, which gave a quiescent output d.c. voltage, after rectification, of $\pm 62V$. This was subsequently replaced by a 250VA 50-0-50V toroidal cored unit, in the interests of a lower residual 50Hz field, and this gave a d.c. output of ± 65 volts, and increased the power output, at 1kHz across an 8ohm, water-cooled, resistive load, from 83watts/channel to some 105watts/channel. It was thought prudent to uprate the reservoir capacitors to 80V types, but no other changes are necessary.

Loudspeaker protection circuit

Although the use of direct coupling between loudspeaker and amplifier output, together with the use of split positive and negative h.t. rails, undoubtedly helps in the economical design of high-powered audio amplifiers by limiting the necessary voltage rating of the reservoir capacitors, it does carry with it the implicit hazard that, in the event of a component failure within the power amplifier, the whole output of one or other of the supply lines may be switched into the output circuit, with expensive consequences.

The most elegant way of avoiding this hazard is to employ a small supplementary circuit to monitor the average d.c. potential of the amplifier output terminals, and to disconnect the loudspeakers in the event that an averaged d.c. offset of more than a volt or so is detected. Experiments over a period of time have shown that the loudspeaker can be connected through a pair of gold-plated relay contacts without audible or measurable signal degradation. Silver-plated contacts are excellent when new and clean, but tend to become partially rectifying if sulphided by exposure to urban atmospheres, and should therefore be avoided if possible.

An inevitable problem in the use of an 'average d.c. potential' monitoring circuit is the necessity for some compromise be-

tween speed of response, in disconnection following a fault condition, and the need not to diagnose a large but legitimate v.l.f. signal - especially if asymmetrical - as such a fault. My own choice is an integrating time-constant of about 2 seconds. This ignores all the normal l.f. signal components, at least at the largest signal levels I have so far used, but allows a switch-off in better than 80 milliseconds in the event of a large direct voltage being applied to the input. This should be adequate to avoid thermal damage to the loudspeaker.

In order to accommodate a fairly long integrating time-constant with the use of non-polarized capacitors, a high-input-impedance offset-detection logic circuit is essential. C.m.o.s. logic elements of the 74C or CD4*** series are well suited to this task, especially since the switching potentials are well defined in relation to the supply voltage line employed. Typical gate transfer characteristics are shown in Fig. 23. Because of this, if the gates are biased by an input resistor chain, as shown in Fig. 24, so that one sits below and one sits above this threshold level, a pair of Nor gates will effectively act as an input-threshold d.c. monitor circuit, in which the output will only be high so long as input A is high and input B is low. With the resistor values quoted, this condition will be met while input C is within $\pm 2V$ d.c., for a 10V supply line. The circuit also will provide a switch-on delay of a few seconds while C_1 charges up through R_3 to a potential above the $\frac{1}{2}V_{cc}$ level.

The complete, two-channel, loudspeaker protection circuit based on this arrangement needs only one Quad 2-input Nor gate, and a pair of switching transistors. The final circuit is shown in Fig. 25. It is 'fail-safe' in the sense that the relay contacts are normally open, and can only operate if the h.t. supply is present and both transistors are energized. The relay used is an RS Components p.c.b.-mounting, 24V unit, with 5A, 250V a.c.-rated gold-plated contacts, of d.p.d.t. operation. H.t. supply for this is best obtained from the output stage +65 volt line.

References

- Linsley Hood, J. L., *Wireless World*. Letters. Jan. 1975 p18.
 - Otala, M., *Trans. I.E.E.E.* AU-18, pp 234-239.
 - Jung, W. G., *Hi-Fi News and Record Review*. Nov. 1977, pp 115-123.
 - Linsley Hood, J. L., *Hi-Fi News and Record Review*. Jan. 1978, pp 81-83.
 - Baxandall, P. J., *Wireless World*. July 1978, pp 76-79.
 - Baxandall, P. J., *Wireless World*. Dec. 1978, pp 53-56.
 - Baxandall, P. J., *Wireless World*. Feb. 1979, pp 69-73.
 - 'Cathode Ray', *Wireless World*. Oct. 1978, pp 47-50.
 - Hitachi Ltd., Design Note DE 1A. Feb. 1979. (Central Res. Lab.)
- Editor's note: We understand that a kit of components for the amplifier is to be made available by Hert Electronic Kits, Ltd, Oswestry, Shropshire. A preamplifier design to match the mosfet power amplifier will be described later in the year. □

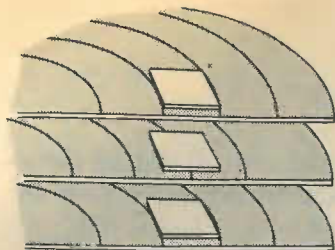


Fig. 4. When the servo head is straddling two servo tracks, the data heads are correctly aligned with their respective tracks.

respective tracks. As the servo head has only one magnetic circuit, it will generate a composite signal whose components will change with respect to one another as the position of the servo head changes. Figure 5 shows several composite waveforms obtained at different positions of the servo head. The composite waveform is processed by using the first positive and negative pulses to generate a clock. From this clock are derived clamping signals which permit only the second positive and second negative pulses to pass through. This resultant waveform has a d.c. component which, when filtered, gives a voltage proportional to the distance from the track centre. The position error reaches a maximum when the servo head is entirely above one type of servo track and further movement will cause it to fall. The next time the position error falls to zero will be at the centre line of the adjacent cylinder.


Cylinders with even addresses (l.s.b. = 0) will be those where the servo head is detented between an A track and a B track. Cylinders with odd addresses will be those where the head is between a B track and an A track. It can be seen from Fig. 5 that the sense of the position error becomes reversed on every other cylinder. Accordingly, an inverter has to be switched into

the track-following feedback loop in order to detent on odd cylinders. This inversion is controlled by the l.s.b. of the cylinder difference at the beginning of a seek, such that when the heads arrive at the target cylinder, the sense of the feedback will be correct.

Seeking across the servo surface results in the position error signal rising and falling in a sawtooth. This waveform can be used to count down the cylinder difference which controls the seek. As with any cyclic transducer there is a problem in finding an absolute position. This difficulty is overcome by making all servo tracks outside cylinder zero type A, and all servo tracks inside the innermost cylinder type B. These areas of identical servo tracks are called guard bands, and Fig. 6 shows the relationship between the position error and the guard bands. During a head load, the servo head generates a constant-maximum positive position error in the outer guard band. This drives the carriage forward until the position error first falls to zero. This, by definition, is cylinder zero. Some drives, however, load heads by driving the carriage at low speed across the disc until the inner guard band is detected, and then find cylinder zero by performing a full-length reverse seek.

Another, less common form of servo surface is shown in Fig. 7. In this type, there is a common sync. bit in both tracks,

Fig. 5. Waveforms resulting from several positions of the servo head in relation to the disc. Amplitudes of waveforms (a) and (b), components of the actual waveform (c), are proportional to the area of the servo head over the track concerned. A position-error signal, (d), is obtained by comparing the second positive and negative peaks in the composite waveform, (c).

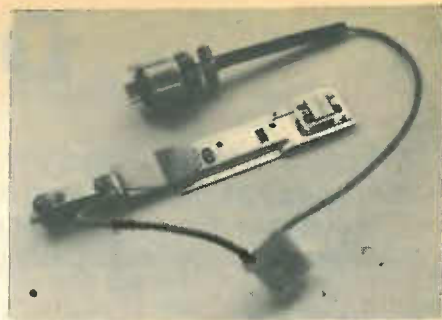

Servo head from a multi-platter disc drive. The rectangular plug is for mechanical support only.

and subsequent servo bits at different times afterwards. The position error is derived by opening sample and hold gates at different delay times after the sync. bit. As three distinct transitions can be seen in one cycle, the resultant waveform is known as a tritbit signal.

We have seen that a position error and a cylinder count can be derived from the servo surface, eliminating the conventional cylinder transducer. The carriage velocity could also be derived from the slope of the position error, but unfortunately such a signal is only available while the servo head is above the disc, and velocity feedback is needed when the heads are retracted. Some form of velocity transducer is still therefore necessary.

As there are exactly the same number of dibits on every track, it is possible to describe the rotational position of the disc simply by counting them. All that is required is a unique pattern of missing dibits, once per revolution to act as an index point, and the sector transducer can also be eliminated.

Unlike the read/write circuits, the servo circuits are active during a seek as well as

when track following, and so must be constructed in such a way that they do not suffer interference from pulse-width modulated e.m.a. drivers. The main problem comes when the index is due, where the presence of a noise pulse during a "missing" dibit could inhibit recognition of the index. There are two solutions to this problem. In the first, a preamplifier i.c. is incorporated in the servo-head cantilever, so that the servo signal leaves at high level and low impedance, making it noise immune. In the second approach, the sector counter predicts when an index pattern is due, by counting slightly less than the number of dibits in one revolution, and inhibits switching in the e.m.a. driver until index has been detected.

An advantage of deriving the sector count from the servo surface is that the number of sectors on the disc can be varied. Any number of sectors can be accommodated for by feeding the dibit-rate signal through a programmable divider, so the same drive may be used for storing, say, 22 sectors of 16-bit data for a minicomputer or 20 sectors of 18-bit words when connected to a main-frame (2 disc words are the same as 1 memory word).

In a non-servo disc drive, the write clock is usually derived from a crystal oscillator. As the disc speed can vary with supply voltage fluctuations, a tolerance gap has to be left at the end of each disc block to cater for the highest anticipated speed, to prevent overrun into the next block on a write. In a servo-surface disc drive, the write clock is obtained by multiplying the dibit-rate signal with a phase-locked loop. The write clock thus obtained is locked to the disc speed, and the recording density will be independent of supply fluctuations.

Most servo surface disc drives offer an offset facility, where a register written into by the system controls a d-to-a converter, which injects a small voltage into the track-following loop. The action of the servo is such that the heads move away from the theoretical track centre line until the position error is equal and opposite to the offset voltage. The position of the heads about the track centre line is thus program controlled, Fig. 8. Offset is only employed for the purpose of reading, if a write is attempted, the drive will return to the track centre line.

Head alignment. The servo-surface technique is also used for head alignment. On the data surfaces of the alignment disc, dibit patterns are written at the reference cylinder. A special test box is required for head alignment, and this usually contains an exact copy of the circuit board used by the drive to obtain a position error signal from a dibit signal. The module in the test box is fed not by the servo head, but by the data head to be adjusted. The position-error output drives a centre-zero meter which gives a direct reading of the head misalignment in micro inches. The selected head is adjusted radially in the carriage until the meter reading is within the specification. Precautions are taken to ensure that the alignment disc is not written over.

Program-controlled head-alignment measurement. In some test boxes, the posi-

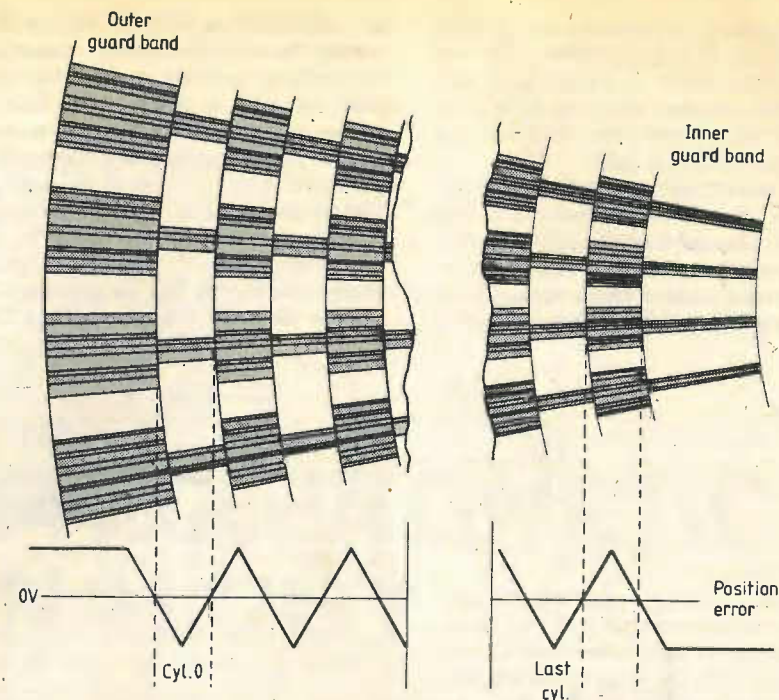


Fig. 6. The servo surface's working area is defined by the inner and outer guard bands, at which the position error signal is maximum.

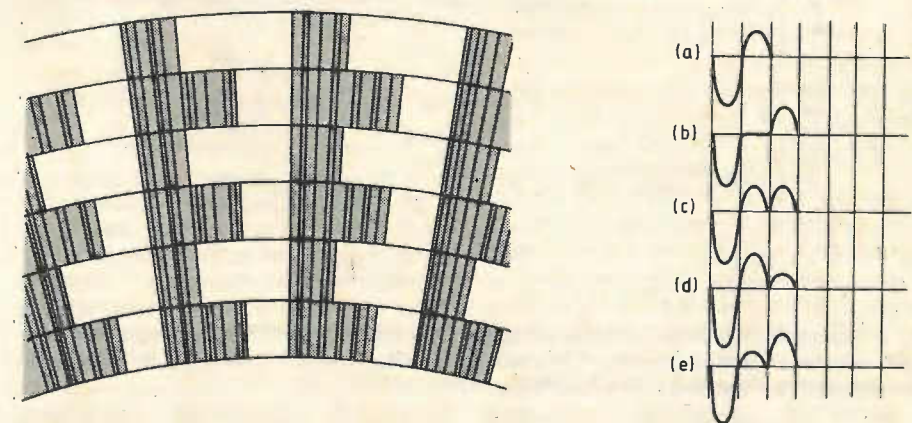


Fig. 7. The 'tritbit'-type servo surface in which the position-error signal is derived from pulses from two types of track following a common negative synchronization pulse. (a) and (b) are obtained when the servo head is directly above one or other of the tracks, (c) is the correct waveform, and (d) and (e) show typical off-track waveforms.


tion-error signal from the selected data head is compared with zero volts, to create a binary signal depending on the head position relative to the track centre line. This signal is fed back into the disc-control logic and becomes a bit in a register accessible to the system, known as 'sign change'. Under program control, the positioner is set to maximum offset, and then brought back until the sign-change bit changes state. The amount of offset needed to cancel the alignment error is equal to the error itself, Fig. 9. After sequentially testing all of the heads, the program can print out a table of the alignments. By comparison with the specification, an engineer can decide which, if any, heads need adjustment. The head alignment can also be checked at further reference tracks on both the innermost and outermost cylinders, as a check on carriage alignment accuracy.

Embedded-servo drives

In drives with few platters, the use of an entire surface for servo information gives a

high percentage loss of data recording area. In the embedded-servo drive, servo information is interleaved with data on the same surface, causing a smaller loss of data storage area.

The embedded-servo drive heads will be reading data at some times and alignment information at others as the disc rotates. A sector transducer is required to generate a pulse which is true when the head is reading servo information and false when reading or writing data. Figure 10 shows the principle. On all disc drives, the width of the read/write head is less than the track spacing to prevent crosstalk. As the servo head is also the read/write head here, it is slightly narrower than the spacing of the servo information. This has the harmless effect of rounding off the peaks of the triangular position-error waveform. During the pulse from the sector transducer, the head sees alignment information, and the servo circuit develops a position-error signal in much the same way as any servo drive. Within the servo area there are two sets of alignment patterns, the second be-

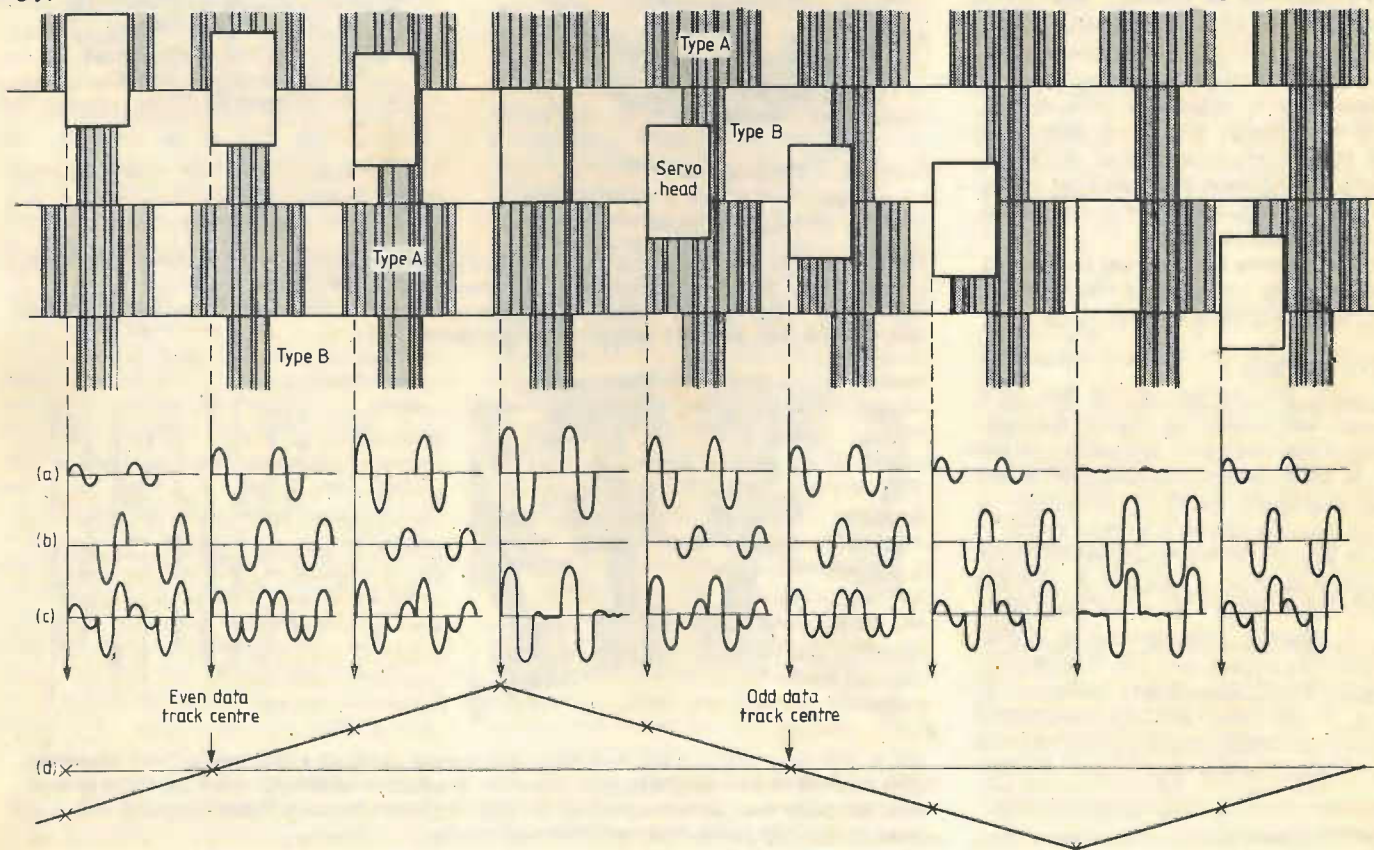

ing positioned to a position error of zero when the first is at a maximum. The two bursts of information are known as S1 and S2. Sample-and-hold circuitry is used to carry over the position error when the head is traversing read/write data.

The discontinuous nature of servo information means that cylinder crossing cannot be counted directly during a seek, as the positioner is fast enough to cross several tracks between servo bursts. With reference to Fig. 11, the cylinder crossings

are established as follows. During the S1 period, the position error is compared with zero volts to generate one data bit, whose state depends on whether the head was inside or outside the S1 null point. A similar process takes place during the S2 period, and the position of the head relative to the servo pattern is described as being in one of four places by the two bits. These bits are stored, and at the next servo bursts, two further bits are generated, describing the new position of the head.

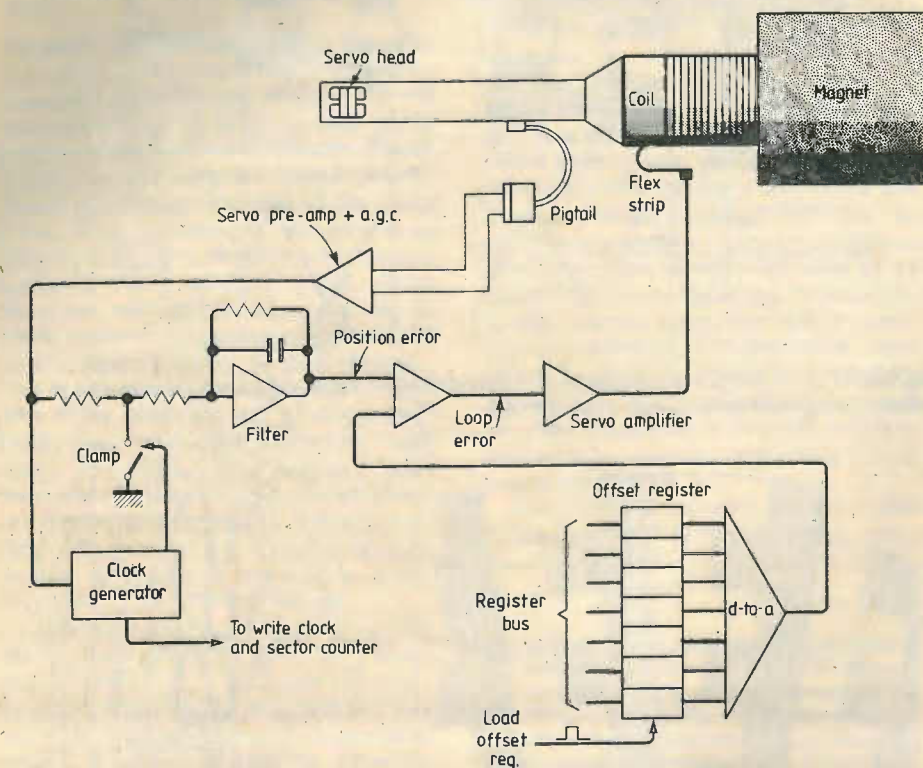


Fig. 8. Representation of servo-surface disc drive's feedback loop. The offset register drives a d-to-a converter which can modify the feedback loop, allowing the heads to be offset from the track centre line under control of the operating system.

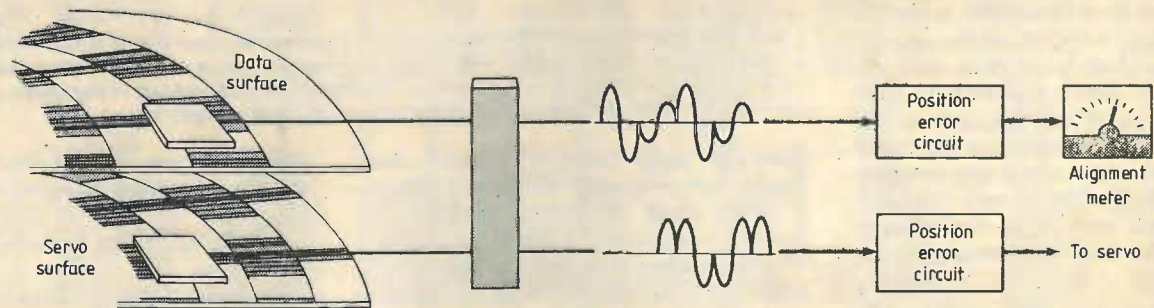


Fig. 9. Head alignment. An alignment disc with 'dibits' on its data surfaces is used in conjunction with a duplicate of the position-error circuit driving a head-alignment meter. Using offset, the program can move the servo head off track until the read/write head is in the correct position. The amount of offset necessary to achieve this is equal to the alignment error.

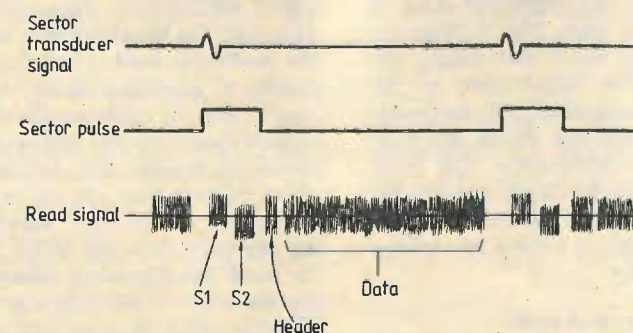


Fig. 10. In an embedded-servo drive, the same head is used for both servo information and data. During a sector pulse, the read signal is treated as servo information.

Figure 12 shows that there are a number of cases which can satisfy the same initial and final conditions. The only difference between the cases is the carriage velocity, so the output of the carriage-velocity transducer is digitized and used to resolve the ambiguity.

At every sector pulse, the two bits from the previous bursts, the two bits from the current bursts and the digitized velocity are fed into a rom which is pre-programmed to return the theoretically cor-

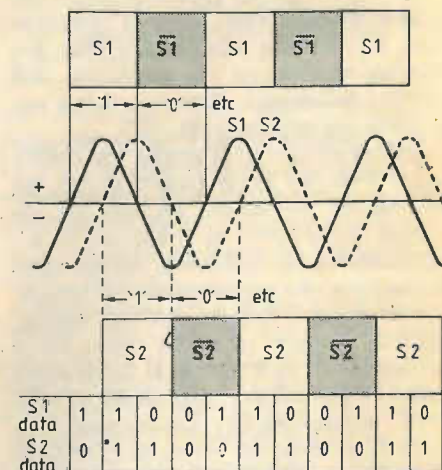


Fig. 11. There are two basic types of servo track, S1 and S2, recorded in two different positions and staggered. During S1, a position error signal is generated from the relative areas of the two types of track (S1 and $\bar{S1}$) under the head as in the conventional servo-surface drive. This position-error value is stored in a sample and hold circuit. For track counting, the position error value is compared with 0V to obtain a data bit. During S2, another position error signal and data bit are generated. The four possible combinations of the two bits are shown here in relation to the two position errors.

rect number of cylinders which must have been crossed for all combinations of inputs. This number is then subtracted from the cylinder difference counter which controls the seek. The calculation will only be valid for one disc rotational speed, so the disc motor requires a speed control. This is achieved by counting controller-clock pulses during the time between sector pulses, and developing a loop error by comparison with the desired number of pulses.

As the cylinder crossing count is deductive, there will be the odd occasion when the count is in error and the positioner comes to the wrong cylinder. In a conventional disc drive, this would be a mispositioning error which would warrant an en-

continued on page 46

A Heretic's Guide to Modern Physics

- 1 Theories and Miracles
- ▶ 2 Electromagnetic Analogy
- 3 Impact of the Photon
- 4 A more realistic Duality?
- 5 Quantization and Quantization
- 6 Waves of Improbability
- 7 Limitation of Indeterminacy
- 8 Haziness and its applications
- 9 The State of Physics Today

THE ELECTROMAGNETIC ANALOGY

In his second article Dr Murray takes a dispassionate look at Victorian electromagnetic theory and finds that, contrary to popular belief and textbook wisdom, it had begun to go decidedly green around the edges before it was thirty years old — a fact that many otherwise worthy men have preferred to ignore.

by W. A. Scott Murray
B.Sc., Ph.D.

The earliest organized investigation of the physical properties of light was undertaken in the seventeenth century by Sir Isaac Newton. Despite the evidence of some of his own experiments, Newton himself remained convinced throughout his life that light consisted of showers of particles, or "corpuscles". His authority among scientists was such that much philosophical argument arose before Thomas Young's famous experiment — on the mutual interference of light rays after passing through a double slit — was accepted as conclusive evidence for the wave nature of light, largely through the mathematical ingenuity of Fresnel. Incidentally, the most convincing demonstration that I know of in favour of "light waves" is due directly to Fresnel, and lies in the fact that the shadow of a one-penny piece has a bright spot at its centre.

That light behaves as a wave system is one of the most thoroughly researched and supported conclusions in all science. By assuming waves of a definite wavelength one can calculate numerically how light will behave in optical apparatus of any complexity one chooses and, lo and behold, that is precisely the way light does behave in practice. The accuracy of the prediction seems to be unlimited, and to depend only on the accuracy with which we can measure the result. I want to place special emphasis on the precision with which the wave theory describes the behaviour of light as observed in Nature, because it is primarily that precision which makes the wave theory of light so convincing. As long as we stick to light which is bright enough to be seen, and of ordinary visible wavelengths, the theory works perfectly every time.

The next major step in the wave theory

was taken in 1862 by James Clerk Maxwell, on the basis of his formulation of Michael Faraday's ideas of electricity and magnetism. Faraday had come to interpret his observations in terms of electric and magnetic fields of force, which Maxwell found could be expressed by exact analogy with the mathematical formulations of hydrodynamics — that is, the behaviour of incompressible fluids. Faraday's field concept conveniently bypassed the fundamental problem of action-at-a-distance. (namely, how can one electric charge repel another when there is no connecting rod between them?). It suggested that the electric field permeated everything and everywhere, like a fluid throughout all space, so that such actions really took place locally, within the field, rather than "at a distance".

By this means action-at-a-distance came to be regarded as a non-problem, the first of many difficulties so handled in physical science. Note that the non-problem technique does not solve the philosophical problem to which it is addressed, but evades it. It is clearly legitimate as a technique, to permit us to maintain our momentum and get on with the next phase of the job, provided we put up a marker flag to remind ourselves that we have left behind us a fundamental problem unsolved. It is philosophically dangerous to omit this precaution. For example, there are those who have specialized in field theory so strongly that they believe in an electric field, as if it were a physical entity having an independent physical existence in its own right — like an electron perhaps, or a

filing cabinet. Such folk do not envisage an electric field merely as a convenient mathematical trick for integrating a set of inverse-square-law forces.

I am discussing this concept of a "force field" at some length because it is the first instance we have encountered where an attractive product of romantic imagination has come to be treated, with no basis of experimental evidence whatsoever, as though it corresponded to an established or even a self-evident truth. It is in this romantic, unscientific way that doctrines arise in physics. (When a doctrine is subjected to criticism that it cannot withstand it usually turns into a dogma; it is then to be believed by faith rather than by evidence). In the present case the truth is that we know nothing of how or why one electric charge should be influenced by the distant presence of another, but only that it is so influenced and by precisely how much. It is another miracle.

These ideas may seem far removed from waves and light, but the connection between them was Maxwell's very great invention: he showed that a particular combination of his changing electric and magnetic fields, which can be written, down mathematically in the form of a "wave equation", would propagate through space at the velocity of light. Thence it needed but one further, obvious step to the postulate

"Light consists of electromagnetic waves".

That step was taken. Combining as it did the three topics of electricity, magnetism, and light under the single concept of wave motion, it was extraordinarily satisfying aesthetically and it seemed to remain true when tested to any depth. It came to be

believed by all scientists at the turn of the century and it is still believed by nearly all scientists today. Heinrich Hertz went on to cap it by generating radio waves electrically and showing that they belonged to the same family of phenomena.

Thus at the end of the "classical" period in physics all appeared superficially tidy. It was generally accepted that the entire spectrum of light from long-wave radio through and beyond the ultraviolet was a manifestation of electromagnetic waves of defined, invariant velocity c , whose "colours" were determined by their frequencies and corresponding wavelengths in accord with the general axiom of wave motion, frequency \times wavelength = c . Those must have been happy days of self-satisfied Victorian complacency before the storms broke...

A couple of minor points arose. First, the physical energy transported by the light waves, which propagated at the speed of light, was taken to be the energy contained in the electromagnetic field as described by a simple formula of the theory. Once launched into space, this energy had an independent existence even though its source, a star for instance, should later explode as a supernova. So here one had an electric field and a magnetic field, neither of which (according to the theory itself) could exist without continuous connection to a source and a sink of fluence, while their combination, the *electromagnetic* field, did have an independent existence. These static and dynamic fields were therefore quite different in their intrinsic natures, yet there was nothing in Maxwell's equations to suggest that one type of field was more physically "real" (that is, had any more independent, objective and existence) than the other.

Second, and on a slightly larger scale of discrepancy, Maxwell's formulation of electric and magnetic fields was mathematically equivalent to the behaviour of incompressible fluids, as has been mentioned already; yet the waves in his *electromagnetic* field were *transverse* waves, of a type which in the mechanical case require a solid substance to transmit them and will not propagate in a fluid medium. Thus the medium involved, which became known as the ether, was required to exhibit physical properties which differed from moment to moment, according to whether the field it was supporting was static or in motion. This gave rise to much trouble.

In view of the intellectual triumph of Maxwell's work it would indeed have been churlish to have raised such apparently insignificant points as these at the time. Yet in retrospect one can see that they were real discrepancies whose incidence formed part of a pattern of discrepancy in electromagnetic theory. (Remember, please, that we are not attacking the theory, but examining a miracle: a physical occurrence for which we can offer no physical explanation). For physical waves as normally understood are mechanical waves; they are waves in *something* — in air, or water, or at the air-water interface, or in solid rock, or what-have-you. Their

velocity is determined in relation to the medium in which they travel. Hence a careful measurement of the velocity of light in the laboratory, coupled with the assumption of the constancy of light velocity in its ether medium should, it was believed, reveal the velocity of the laboratory through the ether.

That experiment was duly performed, most famously by Michelson and Morley in a basement in the University of Chicago in 1887. The date is most interesting, being 25 years after the first publication of Maxwell's postulate of the electromagnetic nature of light, and 18 years before the publication by Einstein of the special relativity theory with which it is usually connected. That connection is something of a myth. Einstein did not refer to the Michelson-Morley experiment at all but assumed the velocity of light to be universally constant as a fact of nature (*it was not tested* in Michelson-Morley!). His other starting-point, the principle of relativity in the form of the denial of absolute motion, was in no sense new but had appeared in Newton's *Principia* just 200 years before.

Thus for contemporary thinkers the really shocking implication of Michelson and Morley's result was not that it might lead towards a new relativity theory some two decades later, but that it asserted, unmistakably and immediately, that *there was no ether* for the electromagnetic light waves to undulate in. It was of secondary importance that the medium in which electromagnetic waves travelled did not reveal any frame of reference of zero motion, or absolute rest. It was an equally red herring to say that it was merely the postulated electromagnetic waves that had no ether, because the experiment as performed was a straightforward experiment in light, having no reference to electricity or magnetism. The really crucial experimental result was that light waves, whatever their form, could not be waves in a physical medium. And if they were not waves in a physical medium, how could they be said to be waves at all? The answer to that question is *not* straightforward.

There was an immediate and almost instinctive reaction against the Michelson-Morley result. Some physicists (like Sir Oliver Lodge) simply refused to accept it, while others up to the present day have repeated the experiment with progressively more refined apparatus in the hope of proving it wrong. All such attempts so far have failed. Most of those experimenters believed themselves to be taking issue with Einstein and special relativity; only a discerning few have understood that they were really trying to save the electromagnetic theory, and with it the whole of the concept of fields of force of nineteenth-century physics. The Michelson-Morley experiment denies the existence of an ether, and there is no doubt about its finding: space is empty. There is nothing there.

In view of the admittedly overwhelming evidence that light consisted of waves (and very probably electromagnetic waves), physics at the turn of the century refused to face the consequences of the Michelson-

Morley result. Two lines of experimental evidence that seemed to be equally valid seemed also to be in absolute mutual conflict. The philosophical crisis was acute, and it has never been resolved. One approach has been to ignore the problem in the hope that in due course and in the light of later knowledge it will go away — this is the "don't care" or "too busy" reaction, which really means "too difficult" — but unfortunately this is a problem that *doesn't* go away. Another approach is to ask why a physical ether should be necessary for the waves to propagate in: why do they demand a *physical* medium? The answer would seem to be that according to the theory these "waves" carry physical energy in readily measurable amounts, so that they must be physical waves; and physical waves cannot be waves in nothing, unless we are to believe in miracles...

Then there are the semantic approaches, which seek to show that the problem is one of wording only and has no philosophical depth. "Very well", it has been said, "we have been denied a luminiferous ether; let us call the medium in which the waves travel 'space', or 'an inertial frame of reference'". The trouble with such proposals is that space, insofar as we can *measure* its properties, is empty, a vacuum, having no physical content. (Do not let us get bogged down with arguments about the "permittivity" or "im-

Summary

History of the scientific concepts of light: Newton (corpuscles), Young and Fresnel (waves), Faraday (fields of force), Maxwell (electromagnetic theory). The philosophical problem of "action-at-a-distance" was not solved but bypassed, setting a precedent; this raised the question of the nature of a field theory and led to the emergence of related doctrine and dogma. Some minor discrepancies were inherent in electromagnetic theory as propounded: depending on scenario its fields possessed differing degrees of physical reality, and differing properties were required of the medium, or ether, in which the electromagnetic phenomena occurred. A major problem arose in consequence; when the issue was put to the test, the famous Michelson-Morley experiment unequivocally denied the existence of a physical ether for electromagnetic waves to undulate in. Attempts were made to evade this philosophical crisis by ignoring it, by semantic arguments, and by attributing physical properties to non-physical, mathematical equations. The last of these ideas, which began to take root in the 1890s, re-introduced mysticism into natural philosophy after a banishment of only 350 years. An alternative approach (which was not acceptable in the climate of those times) might be to regard electromagnetic theory as an analogy of Nature which although often extremely useful may not always be a perfect analogy.

pedance" of empty space, which are artifacts of electromagnetic theory). We cannot manufacture a physical medium having physical properties out of nothing merely by coining phrases or by re-defining space.

Yet another approach — and this one had far-reaching philosophical consequences — arose from the remark that the *mathematics* of wave propagation predicted results in accord with observation even though the physical requirements for wave propagation were not satisfied. The temptation became very strong to say that these light waves were not physical waves at all, but *mathematical* waves. Here at a stroke one seemed to have a potential solution satisfying both aspects of the experimental evidence: (a) light consists of waves (*c.f.* Young and Fresnel, and perhaps also Maxwell and Hertz), while at the same time (b) the waves are not physical waves in a physical ether (*c.f.* Michelson and Morley), but of a purely mathematical nature.

This was the first move in the takeover, by default, of theoretical physics by the Mathematicians' Union. It wasn't a complete takeover until the 1930s when the mathematics of the new quantum mechanics became so obscure and esoteric that the ordinary physicist gave up trying to follow the wilder ramifications of the theory. The nature of the physicists' default was their failure to insist sufficiently strongly on the physical reality of the physical world. In the case of light, energy is

transmitted at a definite speed through a vacuum, and this energy is a physical entity which gives rise to measurable physical effects at its destination. Mathematical waves, being abstract and non-physical, cannot give rise to physical effects. If we accept mathematical waves as the basis for light, we are accepting miracles; for by our definition a miracle is a physical occurrence for which we can offer no *physical* explanation.

Mathematical explanations of physical events *will not do*. For those who believe that mathematics can take the place of physics, or who have merely failed to think about the suggestion deeply enough, I offer the following little mnemonic: Nobody ever became sunburnt as a result of exposure to a differential equation!

Thus in addition to being the first move in the general mathematical takeover, this was the beginning of the return of mysticism into Natural Philosophy after a banishment which had lasted no longer than 350 years. The evidence we shall put together will show that the process has continued steadily, until today the whole fundamentals area has become so permeated by mysticism that one can scarcely distinguish where the physics ends and the metaphysics begins. There is a way of making the distinction, but it calls for a certain old-fashioned ruthlessness in complying with physical discipline and rejecting unsupported mathematical speculation, however superficially attractive the latter

may appear. The process will become easier and more sure as our long-neglected critical faculty is gradually re-developed and applied to these problems.

What other alternatives do we have for dealing with the quandary in which the Michelson-Morley result has placed us? There is one approach which always carried a budding promise, although in the face of the mystical takeover it has received little more than lip-service. It is that light does not in fact consist of electromagnetic waves but *behaves like* a system of electromagnetic waves. The distinction here between "is" and "behaves like" is not merely tautological or semantic, but fundamental. It tells us to treat the great electromagnetic theory as an analogy or mathematical model of nature, which probably reflects some features of physical reality but not necessarily all features, and which may prove to be a more accurate model of nature in some circumstances than in others. Therefore we do not say that electromagnetic theory is wrong; indeed, we make use of it successfully every day of our lives. We simply say that the area of its applicability may be limited.

Armed with that kind of philosophical background, which is much more restrained and cautious than that of our predecessors at the turn of the century, we are far better placed than they were to withstand the next shock to physical thinking, which was about to be delivered (in 1899) by Max Planck. □

Next month

2Kbyte eprom emulator/programmer

A design for an emulator for 2516/2716 eproms, in which a ram, loaded with software by keypad, carries out the function of a rom and allows a program to be run and tested without the need for eprom reprogramming. Ram contents are easily modified, and the emulator plugs into the system eprom socket. When the program is satisfactory, the emulator transfers to eprom the tested ram contents.

Selective call for c.b. radio

To call any one of 64K similarly equipped c.b. receivers, enter a number on a keypad to generate a 16 data-bit frame to modulate the carrier. Only the selectively called receiver will respond. The device is easily modified for high-security applications, such as remote access and data interrogation.

Simple, low-frequency oscilloscope

A very simple design, using a surplus radar tube. It uses easily obtained components, is straightforward and costs only around £40.

Vertical bandwidth is up to 1MHz at 50mV/cm and the timebase is either astable or triggered.

Op-amp development

As a preliminary to a full description of his new, modular preamplifier, John Linsley Hood traces the development of the operational amplifier, from the early 741 types to the mosfet-input CA 3140 and the bipolar/fet TL071/2/4/ series, designed for use in audio work.

On sale August 18.

CIRCUIT MODELLING BY MICRO-COMPUTER

The small-signal a.c. properties of a circuit may be modelled on a computer. Here the implementation of a program uses techniques to reduce the computing time by 77%, or more, and to plot graphs of the frequency and phase responses.

A previous article on this subject¹ led me to implement circuit modelling on my home computer. I prefer to reserve the word 'analysis' for analytical, normally algebraic, methods such as complex variable theory. As home computers cannot do algebra, I have called the process 'circuit modelling'.

For the design of a 16-node active filter, I used a program to plot frequency responses on a printer, giving simultaneously phase and gain curves. The reduction of the infinite admittance determinant to a two-by-two was done for 50 frequencies in order to obtain enough points for a good curve. At first this took nearly two hours to run on my 4MHz Z80A microcomputer. The table shows a breakdown of the number of operations in Basic.

Operation Type	Number of Operations Originally	No. after Optimising Code
FOR X = ..	700	700
FOR P = ..	6650	6650
FOR Q = ..	74550	21150
ADDS	223650	43400
SUBTRACTS	298200	29800
DIVIDES	149100	14900
MULTIPLIES	745500	61000
ARRAY REFS.	1341900	86800
IF... THEN	0	28500
TOTAL	2840250	292900

Clearly any operation contained in the FOR...NEXT Q loop is carried out a far greater number of times than in any other position. The first step in reducing the running time is to move as many operations as possible outside this loop. The second step is to reduce the number of array references, as these take the longest time. Thirdly to eliminate any unnecessary computations: the determinant being evaluated is normally sparse because few nodes are interconnected. This causes many zero entries to appear and the computer dutifully subtracts zero for each unused node. This can be avoided by including a test for zero. For a typical 16-node circuit, these changes have reduced the number of computations ten-fold. The Basic interpreter code used is shown under. It uses the notation of A. S. Beasley's article¹ and cuts the time for a 50 frequency graph to 27 minutes, a saving of 77%. Note that the use of the exponentiation operator (**) has been avoided. I have used $A=Y1*Y1+Y2*Y2$ in place of $A=Y1**2+Y2**2$. Exponentiation is slower than multiplication and less accurate.

Further optimisation will be machine dependent, and the use of a Basic compiler

By R. I. Harcourt

```

FOR X=N TO 3 STEP -1
Y1=YR(X,X)
Y2=YI(X,X)
A=Y1*Y1+Y2*Y2
IF A=0 THEN 1600
FOR P=0 TO X-1
Y3=YR(P,X)
Y4=YI(P,X)
IF (Y3 = 0 AND Y4=0) THEN 1300
FOR Q=0 TO X-1
Y5=YR(X,Q)
Y6=YI(X,Q)
IF (Y5 = 0 AND Y6=0) THEN 1200
B=Y3*Y5-Y4*Y6
C=Y5*Y4+Y6*Y3
YR(P,Q)=YR(P,Q)-(B*Y1+C*Y2)/A
YI(P,Q)=YI(P,Q)-(C*Y1-B*Y2)/A
1200 NEXT Q
1300 NEXT P
1400 NEXT X
RETURN
1600 PRINT "NODE 'X:' UNUSED"
GOTO 1400
    
```

such as that produced by Microsoft is the simplest method. I did not use Fortran because it is rather hard to plot graphs using the Fortran Format statements. It is also much harder to write a proper command decoder using Fortran rather than Basic. However, rather than spending money on a Basic compiler, I decided to re-code the FOR...NEXT Q loop, using assembler, and call the machine code subroutine from the Basic. I will not describe the assembler code in detail as it depends on the computer in use; but I will describe the macro-codes I used. Provided a Macro-assembler is available, the macro-code will be the same for any computer.

Macro-codes

A macro is a block of code which is invoked whenever the macro call is used. The macro-assembler sees the name of the macro called, and automatically inserts in its place the block of code defined. This would be useful even if it just saved typing, but the technique really comes into its own when the macro can have arguments.

If I define a macro for multiplication, called, say, MPY, then I shall need to specify a multiplier, a multiplicand and a place for the answer. The macro MPY is used as follows:

MPY X,Y,Z is equivalent to $Z=X*Y$

It is defined by saying:

MPY MACRO A,B,C

*

*(code is entered here)

*

ENDM

The code for the multiplication is not shown but whenever MPY is used that

code replaces the macro-call. The real arguments X, Y and Z are substituted in place of the dummy arguments A, B and C. It is now possible to use expressions like:

MPY X,Y,Z

MPY Z,W,Z

which is the equivalent of $Z=W*X*Y$, and $MPY X,X,X$

this is the same as (LET) $X=X**2$

The macro-codes for use in the FOR...NEXT Q loop are shown in the appendix.

Graph plotting


Here is a Basic program for plotting gain and phase shift simultaneously on a line-printer or v.d.u. Examples are shown. It should be noted that both frequency and gain are plotted using logarithmic scales. Gain and phase axes are drawn so as to completely fill a page, with automatic scaling of axes. A gain point is plotted as a letter G, a phase point as a P, but if both coincide the letter B is used at that point. The code is as follows:

```


REM PLOT A GRAPH
INPUT "HEADING":C#
INPUT "FROM WHAT FREQUENCY":F1
INPUT "TO WHAT FREQUENCY":F2
INPUT "IN HOW MANY STEPS":NF
RA=EXP(LOG(F2/F1)/(NF-1))
LPRINT CHR$(12)
LPRINT TAB(30);"FREQUENCY RESPONSE CURVE - :C#"
LPRINT
MN=1E3B : MX=-1E3B : F=F1/RA
A1=-90 : A2=90
FOR I=1 TO NF
F=F*RA
FR(I)=F
GOSUB 20000
GOSUB 21000
GOSUB 22000
GOSUB 23000
IF MX<G THEN MX=G
IF MN>G THEN MN=G
IF A1<A THEN A1=A
IF A2>A THEN A2=A
GG(I)=A
AA(I)=A
NEXT I
RN=MX-MN
RA=A1-A2
ST=RN/20
SA=RA/20
LPRINT
LPRINT "GAIN dB (G) : "
FOR I=0 TO 20
LPRINT TAB(16+I*3) :
LPRINT USING "###.#":(MN+ST*I) :
NEXT I
LPRINT
FOR I=1 TO NF
LPRINT USING "#####.#" : FR(I) :
LPRINT " Hz" : TAB(20) :
GS=INT(100*(GG(I)-MN)/RN)
AS=INT(100*(AA(I)-A2)/RA)
IF GS=AS THEN S1=AS : C1$="P" : C2$="G" : S2=GS-AS-1
IF GS<AS THEN S1=GS : C1$="G" : C2$="P" : S2=AS-GS-1
IF GS=AS THEN C1$="B" : S1=GS : S2=1 : C2$=""
LPRINT SPC(5) :
LPRINT C1$ :
LPRINT SPC(2) :
LPRINT C2$ :
NEXT I
LPRINT
LPRINT "PHASE DEGREES : "
FOR I=0 TO 20
LPRINT TAB(16+I*3) :
LPRINT USING "###.#":(A2+SA*I) :
NEXT I
RETURN
    
```

All the print statements can be seen to be LPRINT statements and a 132 column printer was used. If v.d.u. output is required, then PRINT statements should be substituted and the graph should be scaled according to the width available.

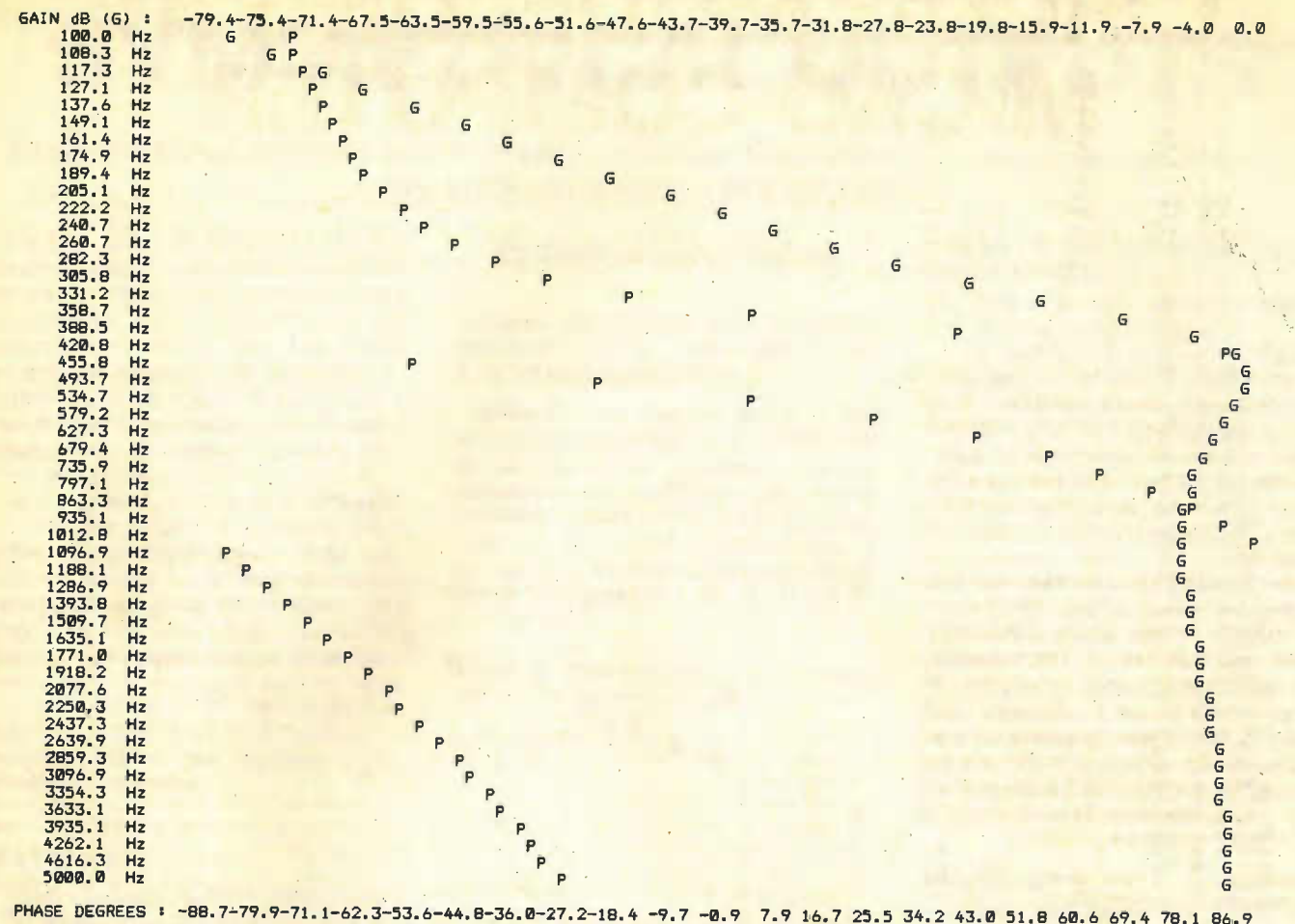
FREQUENCY RESPONSE CURVE - FIFTH ORDER LOW-PASS FILTER



FREQUENCY RESPONSE CURVE - LCR NETWORK

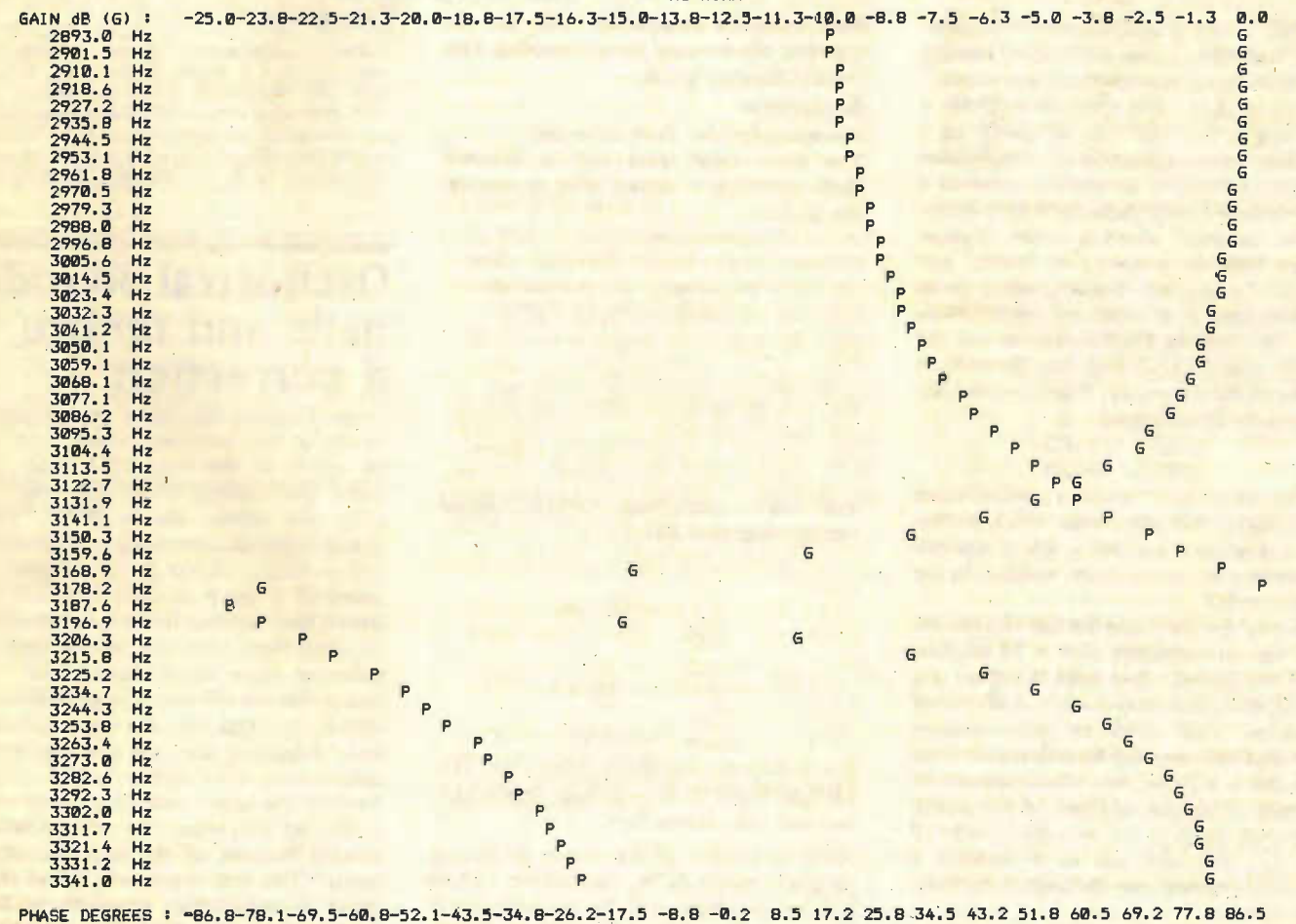

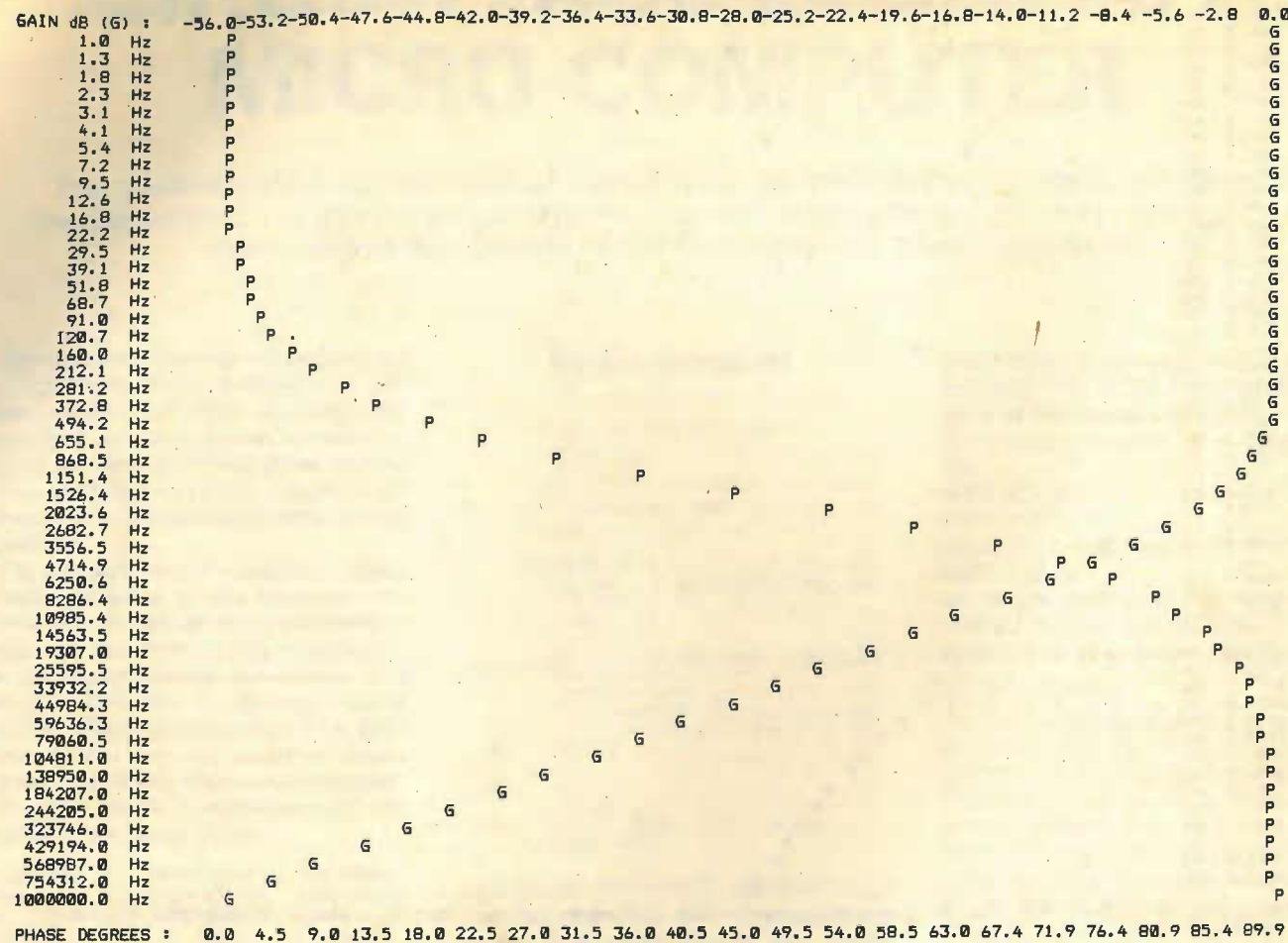Graphs produced by the program. The frequency axis is vertical, so the curves may make more sense if viewed from the side.



While working on loudspeaker crossovers, I wanted to model a crossover feeding two drive units, one of which was connected out of phase. For speakers in phase it was easy to find the sum by specifying a summing network, but for an out-of-phase speaker, I found it necessary to invent a non-existent circuit element. I have called this an 'inverter' which is a two terminal device with the property of 'losing' any current flowing into it while taking in an equal current at its other end which is also lost. This violates Kirchhoff's law and the charge conservation laws, but the method works on the computer. The 'inverter' has admittance determinant:

$$\begin{vmatrix} +1E5 & +1E5 \\ +1E5 & +1E5 \end{vmatrix}$$

and the value used (always a positive value added to the YR array) was +1E5, so that the net effect was of a small resistor connecting an out-of-phase speaker to the output node.

Having cut the time for our typical 16-node circuit frequency plot to 16 minutes from two hours, I then tried the effect of a BASIC compiler and used the Microsoft compiler. This produces true machine code and the time for 50 reductions from 16 nodes to a 2-by-2 was now 2 minutes 48 seconds. With the addition of the macro assembler codes to the two inner loops (P and Q), this was cut to 2 minutes 6 seconds, a saving over the original running time of 98%.

So it can be seen that with a little effort, much time can be saved. The purchase of a

Basic compiler compatible with the interpreter can turn the home computer into a useful designer's tool.

Appendix

Macro-codes for fast reduction
The macro-code used was as follows:
Each operation is shown with its equivalent in Basic:

```

MSB  Y3,Y5,Y4,Y6;B  :B=Y3*Y5+Y4*Y6
MAD  Y5,Y4,Y6,Y3;C  :C=Y4*Y5+Y6*Y3
MAD  B,Y1,C,Y2;D    :D=B*Y1+C*Y2
MSB  C,Y1,B,Y2;E    :E=C*Y1+B*Y2
DIV  D;A;D          :D=D/A
DIV  E;A;E          :E=E/A
SUB  YRPQ;D;YRPQ   :YR(P,Q)=YR(P,Q)-D
SUB  YIPQ;E;YIPQ   :YI(P,Q)=YI(P,Q)-E
RET
END
    
```

The macro definitions, which should precede their use, are:

```

MAD  MACRO  M1,M2,M3,M4;ANS
      MPY    M1,M2;T1
      MPY    M3,M4;T2
      ADD    T1,T2;ANS
      ENDM

MSB  MACRO  M1,M2,M3,M4;ANS
      MPY    M1,M2;T1
      MPY    M3,M4;T2
      SUB    T1,T2;ANS
      ENDM
    
```

All other macro definitions (ADD, SUB,MPY, DIV) are machine dependant, and are not shown here.

Note: A version of the circuit modelling program, called ACM, suitable for TRS80 micro-computers, will be available from Molimerx Ltd, 1 Buckhurst Road, Town Hall Square, Bexhill-on-Sea, E. Sussex.

References

This article is an extension of "Circuit analysis by small computer," by A. S. Beasley, *Wireless World*, Feb. and April 1980. Photocopies of this are available from WW, Editorial, at a price of 90p inclusive. An interesting discussion of the theory may be found in "Two-port representation of multi-mode networks by matrix partitioning," by R. T. Kennedy, *J.I.E.R.E.* Feb. 1969.

Orchestral sounds, halls and timbre - a correction

Denis Vaughan has kindly pointed out to us one or two misprints which crept into his article in the May 1982 issue: Just under the heading 'First reflections' on p.32, the phrase should read: "Their timing is exactly controlled by the width (1 foot ≈ 1ms)." In the middle of page 33, reference is made to Guildford and this should read Gilford. In the third column of the same page, there are two references to reflection times which should read: "this means that the effectively larger reflections start about 81ms after the original sound". and; "Kingsway has quite a lot of powerful reflections to offer within the first 105ms. Because the larger reflections continue to return up to 147ms, the substantial and lengthy support of the musicians is assured". The figures printed (18 and 14ms) could be misleading, especially to those interested in modelling electronically the initial reflection pattern of the hall.

DIGITAL DIVIDERS WITH SYMMETRICAL OUTPUTS

The author uses Johnson counters with controlled feedback to give symmetrical even and odd-numbered divisions of a clock pulse.

By Cornelius van Holten

Time and again, in literature on digital circuitry, ideas are published on the problem how to obtain a 50% duty cycle when a regular pulse train is divided by an odd number. Some clever (and less clever) methods are proposed, e.g. the use of exclusive-or gates in the clock pulse lines, a separate flip-flop with a delay of half a pulse period, the output of which is combined with the normal flip-flops, etc.

In my opinion, the use of EXOR-gates in clock lines should be avoided, since spikes on the output-signals of the flip-flops may occur; a better way is to combine the outputs signals of the flip-flops. The ideas, found in Refs. 3 and 4 are broadened in this paper, and a generalized scheme is proposed which may be easily expanded. Moreover, the control input is pure binary and there is no attempt to change the (odd or even) sequence length. Standard i.cs are used.

The Theory

When a Johnson or Möbius ring counter is fed back, a sequence length of n or 2n is derived, depending on whether a straight or twisted loop is used. The maximum sequence-length is 2n for n bits, and sequences of 2(n-1) etc, are derived when outputs, other than the last, are chosen. When two adjacent outputs are fed back via an AND-gate and negated, (Fig. 1.) any length between 2n and 2 may be obtained.

If an auxiliary flip-flop is connected to the chain and is switched on the opposite pulse edge, the output is shifted over 1/2T, where T is the clock pulse period. It is necessary for the incoming pulse train to have a duty cycle of 50%; if not, a divider is needed which will halve the frequency. In Fig. 2. the outputs of 2 flip-flops, FF₁, the last in the chain, and FF₂, the extra flip-flop, are combined in an OR-gate to

Table 1. Feedback signals and sequence length.

Feedback	Sequence/length
A	2
AB	3
B	4
BC	5
C	6
CD	7
D	8
DE	9
E	10
EF	11
F	12
FG	13
G	14
GH	15
H	16

obtain an odd sequence length (9) with a symmetrical output. In this case, D and E are fed back (see Table 1).

When an even sequence length is chosen, a symmetrical output is derived from the last flip-flop in the chain, only one (negated) output is fed back and no OR process is needed. In the Table 2, a list is given of all possible combinations; I through VIII are the controls signals which switch the (negated) I for A, II for B, ... VIII for H.

Table 2. Control inputs and corresponding sequence lengths.

Control inputs	Output (*T)
I	1 + 1 = 2
I I	1 1/2 + 1 1/2 = 3
I	2 + 2 = 4
I I	2 1/2 + 2 1/2 = 5
I	3 + 3 = 6
I I	3 1/2 + 3 1/2 = 7
I	4 + 4 = 8
I I	4 1/2 + 4 1/2 = 9
I	5 + 5 = 10
I I	5 1/2 + 5 1/2 = 11
I	6 + 6 = 12
I I	6 1/2 + 6 1/2 = 13
I	7 + 7 = 14
I I	7 1/2 + 7 1/2 = 15
I	8 + 8 = 16

Complete circuit

In Fig. 3, the complete diagram is given, consisting of 8 flip-flops (a shift register), a pulse circuit, an output, feedback gates controlled by the inputs I to VIII, and a decision making circuit with 4 full adders for odd and even lengths.

The latter operates as an EXOR-gate with 8 inputs: Y = I ⊕ III ⊕ IV. ... ⊕ VIII and therefore Y = '1' for odd and '0' for even lengths; the unused input of the full adder at the bottom is permanently held at a logical '1' level.

In the output circuit, the function H + YZ is realized. For Y = 0, the output

becomes H (for even length sequences) and for Y = 1, the output is H + Z (for an odd length) as shown in the time charts in Fig. 4a and 4b respectively.

The flip-flops A to H are D flip-flops, operating in the leading clock pulse edge and Z (auxiliary flip-flop) reacting on the trailing edge of it. The P flip-flop is needed when the input pulses are not symmetrical, and a buffer gate is used for amplification. The correction and enabling circuit is described in the Appendix. In normal circumstances, this circuit is inoperative and the shift register is loaded with all zeros by the enabling input, and cycles via 10000000, 11000000, 11100000, ... through 11111111, 01111111, etc. back to the all zero condition. This is the "normal" sequence, 1 out of the 16 possible cycles. Of course, other values of n than 8 are possible, this number has been chosen for comparison with the circuit described by Girolami and Bamberger².

Modification

In Fig. 3(a), there are 8 control inputs which are used separately (for even lengths) or in groups of adjacent pairs (for odd lengths). If one wishes to control the sequence length via a binary weighted control input, a decoder is needed as described in Table 3.

In Fig. 3(b), a read only memory is programmed as a decoder, and the input 1 may be used to control the output circuit: even or odd; the output function is H +

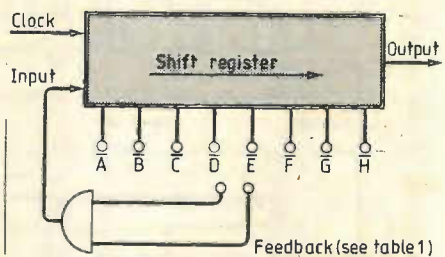


Fig 1. Basic principle of a variable length counter.

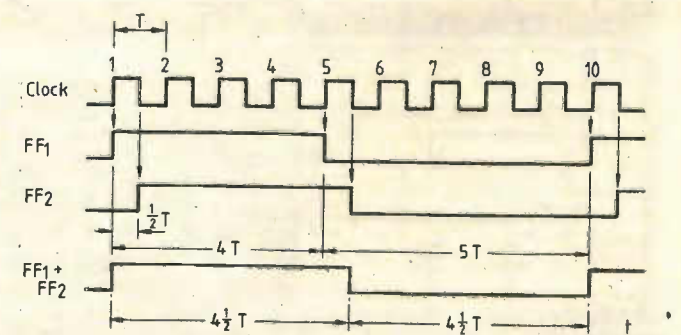


Fig 2. The addition of two asymmetrical flip-flop outputs leads to a symmetrical output.

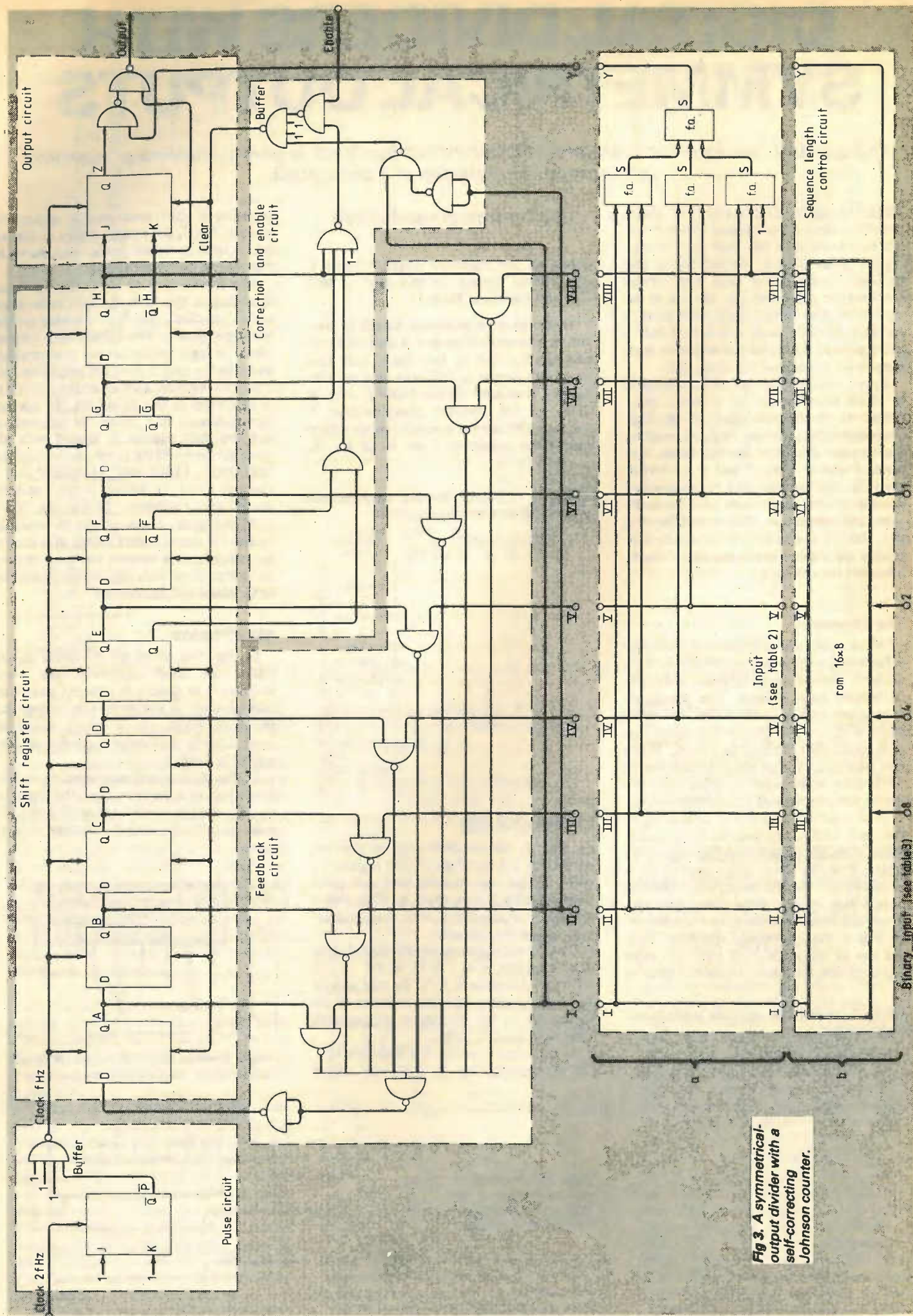


Fig 3. A symmetrical output divider with a self-correcting Johnson counter.

Table 3. Binary weighted control inputs and corresponding signals and sequence lengths.

Input	I	II	III	IV	V	VI	VII	VIII	Sequence length
8 4 2 1									
0 0 0 1				no sense					—
0 0 1 0	1	0	0	0	0	0	0	0	2
0 0 1 1	1	1	0	0	0	0	0	0	3
0 1 0 0	0	1	0	0	0	0	0	0	4
0 1 0 1	0	1	1	0	0	0	0	0	5
0 1 1 0	0	0	1	0	0	0	0	0	6
0 1 1 1	0	0	1	1	0	0	0	0	7
1 0 0 0	0	0	0	1	0	0	0	0	8
1 0 0 1	0	0	0	1	1	0	0	0	9
1 0 1 0	0	0	0	0	1	0	0	0	10
1 0 1 1	0	0	0	0	1	1	0	0	11
1 1 0 0	0	0	0	0	0	1	0	0	12
1 1 0 1	0	0	0	0	0	1	1	0	13
1 1 1 0	0	0	0	0	0	0	1	0	14
1 1 1 1	0	0	0	0	0	0	1	1	15
0 0 0 0	0	0	0	0	0	0	0	1	16

YZ, realized by NAND gates via the formula $\bar{H} \cdot YZ$

Conclusion

A method is proposed by which in a straightforward manner any sequence length may be chosen via a binary weighted input. The circuits are normal s.s.i. or m.s.i. i.cs; for an 8 bit integrated shift register, the clock input is buffered as is the clear input. The buffers may be left out. The output is symmetrical and no spikes occur, since the Johnson principle is in fact a Gray code of sorts, changing only 1 output per clock pulse.

The number of flip-flops is $\frac{1}{2}n$, when n is the sequence length, whereas for a normal counter $\log_2 n$ flip-flops are needed. There is little disadvantage, however, with low prices. In both cases the sequence is nonbinary.

Appendix

With $n = 8$, there are 256 possible zero-one bit patterns, of which only $16(8 \times 1 \text{ and } 8 \times 0 \text{ in groups of } 8)$ are valid. All



Cornelius van Holten holds an honours degree in electrical engineering from the Technical College at Rotterdam and a degree from the Delft University of Technology. He is in charge of a digital engineering laboratory for undergraduates in the Applied Physics Department of the Delft University, and lectures in measurement methodology. He has written a self instruction course in digital circuitry and some 20 papers in periodicals.

other sequences have to be detected and corrected; since 00000000 is a valid combination, resetting of all flip-flops is an easy way to correct.

If one wishes to correct any invalid combination immediately, a rather complex circuit is needed; it turns out, however, that with certain combinations, the register may be reset; within 16 clock pulses any error will be removed.

In the normal sequence, no '0' is present between '1's'; so 101 looks a good bit pattern to detect. However, not all sequences contain this combination; 1001 also occurs.

To check these sequences we write down any non-normal sequence, economizing space by writing the notation in a row, as follows:

e.g. 1110110100010010

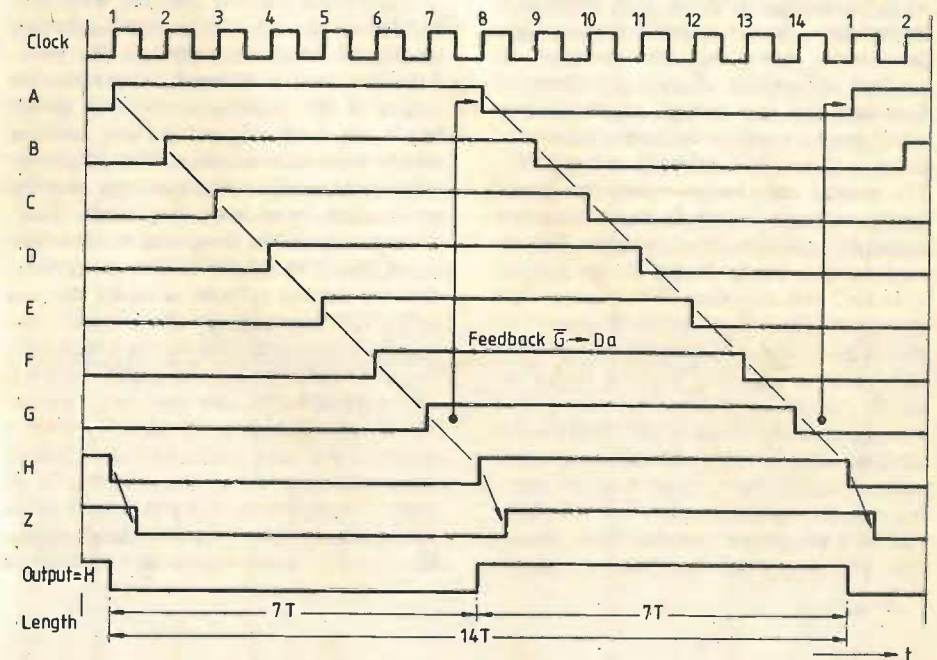


Fig 4a. Time chart for an even-numbered division (e.g. 14).

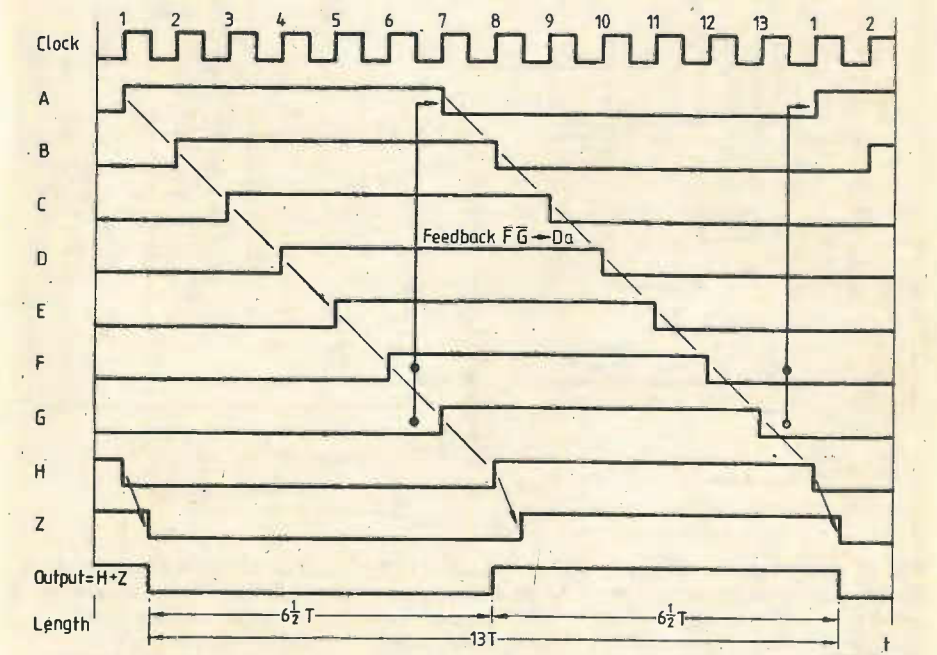


Fig 4b. Time chart for an odd-numbered division (e.g. 13).

The ends are in fact connected, so by checking 101 and 1001 "over the edge" if needed, the result is:

101: (3x) and 1001: (1x)
This means that FGH and EFGH have to be used; simplification gives:
(EF + F) GH = (E + F) GH or rewritten in NAND-form:

$\overline{E.F.GH}$
Since reset is a '0' signal, we invert this to: $\overline{E.F.GH}$; a buffer and an external enable (normally '1') signal results in the circuit as show in Figs. 3 and 4.

For a sequence of 2, however, this correction has to be corrected itself by an

I,II signal (I is 1, II = 0) since this short sequence the detection patten occurs.

A	B	C	D	E	F	G	H
0	1	1	0	0	0	0	0
0	0	1	1	0	0	0	0
1	0	0	1	1	0	0	0
1	1	0	0	1	1	0	0
0	1	1	0	0	1	1	0
0	0	1	1	0	0	1	1
1	0	0	1	1	0	0	1

Detection and correction follows: there is no reason, to choose EFGH; any group of 4 consecutive outputs is valid. The reset is asynchronous, i.e. not controlled by the

clock pulse, but within one period T the counter is ready and starts again, whatever the sequence length may be. □

References

1. L. E. Getgen. Divide symmetrical clock pulses by odd numbers, get a symmetrical output. *Electronic Design*, 5, March 1, 1980, p.110.
2. G. Girolami, P. Bamberger, Symmetrical-output dividers, *Wireless World*, February 1982, p.53, 54.
3. R. M. M. Oberman. *Electronic Counters*. Macmillan, London, 1973, p.151ff.
4. M. Morley. Two IC's restore symmetrical output to a ring counter. *Electronic Design*, February 18, 1982, p.206. □

continued from page 36

try in the system error log, as it indicates a malfunction. In the embedded-servo surface drive, however, the condition is handled differently. Figure 13 shows a flowchart for the control of the drive, which has no absolute cylinder-address register, and in which all seeks are relative. The system only knows where the heads are by reading a header. In order to reach a particular cylinder, the program has to read the first header it sees on the current cylinder, and calculate the cylinder difference required to get to the desired cylinder. This cylinder difference, which may be positive or negative, is sent to the drive, which performs a deductive seek. When this is complete, the program again reads a header. Most of the time the header will contain the desired cylinder address, proving that the seek was successful, but in the odd case where the cylinder count deduction was in error, the program simply

loops and calculates a new difference value until the correct cylinder is reached.

Since each surface has its own embedded-servo information, the heads may be aligned using a normal data disc pack. As a new head is selected, it becomes the source of the position error, and as the heads are only aligned to one another within a certain tolerance, the positioner will adjust itself to eliminate any position error when head switching takes place. This process takes time, and further time is necessary to read a header to confirm that the desired cylinder is under the new head. The time taken by this process is the same as that needed to perform a one cylinder seek, such as might be necessary when all tracks of a cylinder have been written but there is still data to transfer. With a conventional disc drive format, both of these processes would cause the loss of an entire revolution of the disc, waiting for sector zero to come under the heads again. Having abandoned the concept of absolute

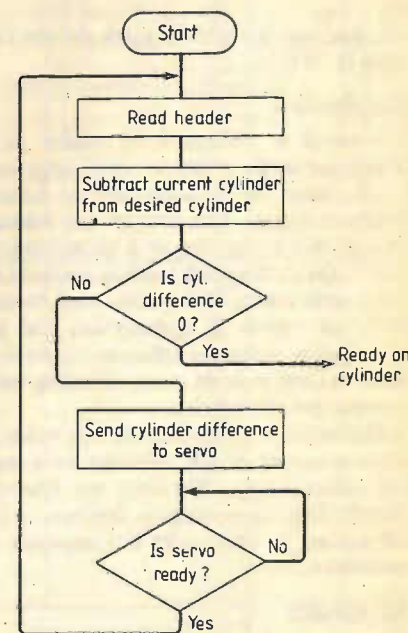


Fig. 13. Flow chart for an embedded-servo positioner system. An absolute cylinder-address register is not used, so all seeks are relative. Seek errors simply cause an extra execution of the loop.

cylinder addressing, which made it necessary to read headers to discover the head position, it is also possible to abandon the fixed index concept, as the sector number is contained in every header read. There is no index point on the disc, and all of the sector pulses are identical. The format of adjacent tracks is displaced to allow enough time for a seek or head change, and for a header to be read to confirm the position, before sector zero of the new track comes around. In the case of a long data transfer of many blocks, a significant transfer-time reduction is achieved, since rotational latency is eliminated.

It is possible to build two versions of the drive. In the first, only the position error developed during S1 is used for track following. In the second, the position error from S1 is used for track following on even cylinders, and that from S2 used on odd cylinders. The second version obviously has twice as many cylinders as the first, but in other respects is basically the same.

Winchester technology and floppy discs and their drives are discussed in the next part of this series. □

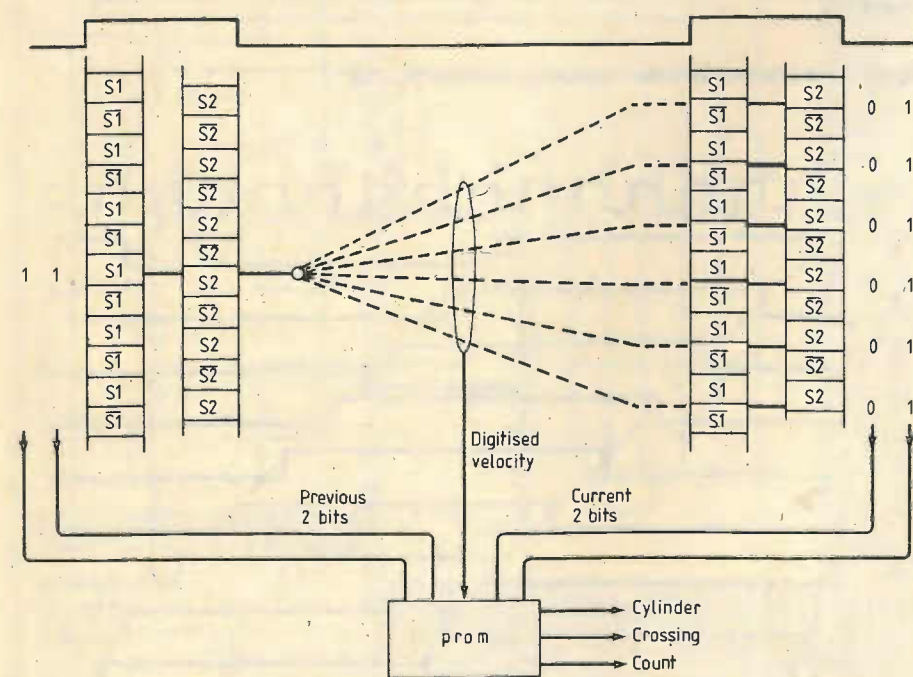


Fig. 12. Here, a seek is being carried out and value 11 from a servo sector has been stored for comparison with two bits from the next servo sector. As can be seen, there are many positions on the subsequent sector where the positioner appears to be on the correct cylinder. To avoid this ambiguity, digitized information from the carriage velocity transducer together with the two stored bits and two bits currently being read address a prom which returns the cylinder crossing count.

DIGITAL FILTER DESIGN

Fast numerical operations using limited precision fixed-point arithmetic are now being provided by new types of microprocessors and l.s.i. circuits. This third article in a series of four outlines some of the problems of using fixed-point arithmetic and gives a brief survey of the new devices, concentrating on the Intel 2920.

by B. M. G. Cheetham and P. M. Hughes

Three types of operation are required for digital filters: multiplication of samples by constant coefficients, addition, and temporary storage for delaying samples. The digital filter shown in Fig. 1, a bi-quadratic section, represents the sequence of mathematical operations that must be carried out for each input sample x_n referred to as X to produce an output sample y_n referred to as Y. The sequence of operations may be summarized as

1. Calculate W by adding W' multiplied by $-b_1$ and W'' multiplied by $-b_2$ to X. (W' and W'' are values of W stored during previous executions of this algorithm - see steps 3 & 4).
2. Calculate the output Y by adding W' times a_1 and W'' times a_2 to W.
3. Set W' to the number currently stored in W for next time.
4. Set W'' equal to the number currently stored in W.

Recursive digital filters are generally implemented as cascades of biquadratic sections i.e. the required transfer function H(z) is expressed as the product of second-order transfer functions $H_1(z), H_2(z) \dots$ each being realised by a distinct digital filter section of the type illustrated. A practical digital filter, therefore, would be a device or devices capable of performing the calculation sequence listed above for all biquadratic sections, for each input signal sample x_n . These calculations must be carried out accurately and within the time-span available between samples in real-time applications. Before looking at real-time digital filters, however, consider briefly their implementation on general-purpose digital computers.

Real-time processing

Although digital filters have been studied for many years, their use has until recently been mainly confined to research applications and computer simulations. This is likely to change rapidly with the development of special-purpose microprocessors and v.l.s.i. devices for signal processing. Such devices essentially execute the type of program discussed in the panel, but if the programmed filter is to be used for continuous signals sampled in the Nyquist rate, all numerical calculations must be completed for each input sample before the next one becomes available; otherwise an increasing backlog of samples would be built up. This imposes a speed requirement which is not present when processing blocks of stored data on a general purpose computer. Such processing would normally use the highly accurate floating-point arithmetic operations provided by high level languages but at great cost in processing time, typically 100µs per

multiply or add. The necessary increase in processing speed required for real-time filtering is currently possible only at the expense of accuracy through the use of fixed-point arithmetic. It is thus necessary to represent all samples, coefficients and results of additions and multiplications by binary numbers of limited wordlength with the equivalent of the decimal point, i.e. the binary point, assumed fixed at some position within the word.

For example, the 16-bit number 0.11000000001101 with fixed binary point represents the decimal number 0.75040 correct to about five significant figures, whereas 0.0075040 must be written as 0.00000011110110 which gives


only about three significant figures of precision. In contrast to floating-point numbers, the accuracy to which a fixed-point number represents a given number depends on its magnitude. Care must be exercised in positioning the binary point lest the addition of two numbers be allowed to overflow, producing a result too large for the chosen format. Negative numbers may be represented in two's complement form with a value obtained by subtracting 1.XXX... from the fractional part of the binary number. In this representation, the fixed-point numbers outside the range ± 1 are not allowed and all numbers likely to appear within a digital filter would have to be scaled accordingly.

The use of fixed-point number representations clearly introduces complications in the design of digital filters and introduces

Programming on general purpose computers

Digital filters are often programmed in high-level languages such as Fortran or Basic and run on general-purpose computers or microcomputers to process blocks of signal samples stored as data arrays. This approach may be used to analyse experimental data where unwanted effects must be filtered out or where particular features must be extracted; you may have used the "trapezoidal rule" for numerical integration $y_n = y_{n-1} + (x_n + x_{n-1})/2$, without realizing that the formula represents a type of digital filter.

Programming a digital filter on a desk-top computer is a very useful way of testing its design before building it. In this application the programmed filter is a simulation of the system to be built, which may be tested by feeding in special test signals generated or captured as blocks of data by the computer. Programming digital filters in high-level languages is straightforward and a good way of learning about their capabilities.

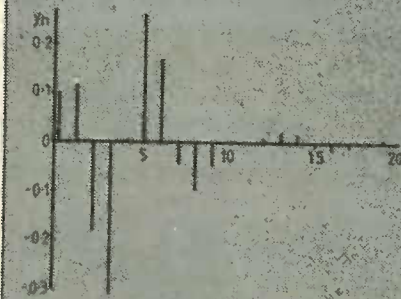

As an example, a Basic program for a fourth-order digital filter is given in the first listing. The filter consists of two biquadratic sections with transfer functions

$$\frac{1 - 2z^{-1} + z^{-2}}{1 + 1.0524z^{-1} + 0.6232z^{-2}}$$

and

$$\frac{1 + 2z^{-1} + z^{-2}}{1 - 0.1665z^{-1} + 0.5348z^{-2}}$$

This filter has a Butterworth type band-pass response (passband 0.125 f_s to 0.25 f_s , where f_s is the sampling frequency), as designed in the previous article. Each biquadratic section is implemented by calling a subroutine (GOSUB 800) with coefficients a_1, a_2, b_1, b_2 stored in the Jth elements of arrays A1, A2, B1, B2; J is 1 for the first biquadratic section and 2 for the second. The subroutine simply follows steps 1 to 4 derived from Fig. 1 with the Jth elements of arrays W1 and W2 holding W' and W'' as required for subsequent calls to the subroutine. Arrays W1 and W2 are zeroed before the first call to the subroutine. Variables X and Y are the input to and output from the programmed biquadratic section. For this example, an array X loaded with 21 samples of the discrete time impulse δ_n is used as an input signal. Output samples are stored in a second array Y and are also printed out. Graph shows the output obtained from this program. This method may be generalised to digital filters of any order with input and output data arrays of much larger dimension.

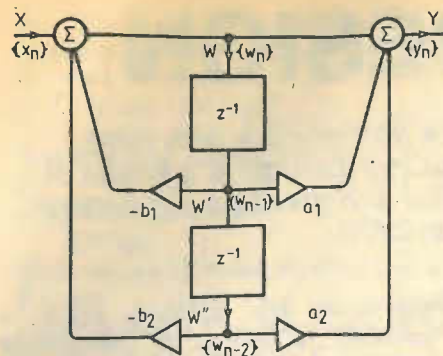


Fig. 1. Recursive digital filters are generally implemented as cascades of biquadratic sections, above. Diagram shows sequence of mathematical operations that must be carried out for each input sample $\{x_n\}$ to give output sample $\{y_n\}$.

innaccuracy which will tend to degrade performance as compared with the theoretical ideal. Some of the most important effects are next considered.

Quantization noise. The conversion of an analogue signal into digital form introduces a degree of distortion as a result of representing the sampled voltages as fixed-point binary numbers. This distortion effectively adds on error signal known as quantization noise to the original signal, as illustrated in Fig. 2. The level of this unwanted noise signal is determined by the wordlength available and the dynamic range allowed for the analogue signal i.e. its expected maximum and minimum voltages. It may be shown that an n-bit analogue-to-digital conversion (with $n > 4$) results in a quantization noise signal of r.m.s. value $\Delta/2\sqrt{3}$, $\Delta = (V_{max} - V_{min})/2^n$, is known as the quantization step. In theory, the noise is spread evenly over the frequency spectrum 0 to $f_s/2$. For a zero-mean input of r.m.s. value σ , the signal to quantization noise ratio is

$$20 \log_{10}(2\sqrt{3}\sigma/\Delta) \\ = 20 \log_{10}(2\sqrt{3}\sigma \cdot 2^n / 2V_{max}) \\ \approx 6n + 10.8 + 20 \log_{10}(\sigma/V_{max}) \text{ dB.}$$

For this formula to be valid, input signal must not exceed the prescribed dynamic range. Ensuring that $\sigma \leq V_{max}/4$ achieves this to reasonable accuracy for noise-like signals, giving a maximum s-n ratio of

$$6n + 10.8 + 20 \log_{10}(0.25) = 6n - 1.2 \text{ dB}$$

This formula may be used as a rule-of-thumb for a wide range of different types of input signal although higher ratios may be obtained by reducing σ/V_{max} for specific signals such as sinusoids. Clearly the maximum value depends on the number of bits in the digital representation, and increasing this number improves the figure by 6dB per bit.

Data wordlength. With fixed point number systems both the range and precision of the numbers which can be represented is limited. For convenience it is usual to think of all the signals within a digital filter as being in the range -1 to 1. Such signals require only one bit in front of the binary point, this being used as the sign bit to differentiate between positive

and negative numbers. The precision of the number representation is determined by the number of bits available for storing data. A sixteen-bit data word, for example, with one bit used for the sign, gives a quantization step size of 2^{-15} . All data must therefore be rounded to the nearest integer multiple of 2^{-15} . In practice it is difficult to determine exactly how many bits are needed to satisfy particular performance requirements. The present generation of special-purpose signal processing devices employ basic wordlengths of between 16 and 25 bits.

Coefficient quantization. When a digital filter is implemented in real time its coefficient values as well as its samples must be quantized and stored to limited precision. The effect is to degrade the frequency response as illustrated in Figure 3. A wordlength of about 12 bits is typically used for coefficients. The second program listed calculates the amplitude-frequency response of a digital filter with original unquantized coefficients and with quantized values as they would be represented in the filter. The maximum difference over the relative frequency range 0 to 0.5 is printed out as a measure of the degree of degradation suffered.

Dynamic range limitations. Signal overflow, which occurs when the result of an addition or multiplication within a filter is out of range, will cause incorrect operation. The errors generated can cause self-sustaining oscillation of large amplitude which are highly undesirable. The simplest way of avoiding overflow is to multiply the input to each biquadratic section by a suitable scaling factor S. The aim is to reduce the input signal level sufficiently to ensure that the largest internal number likely to be generated is within range. For a sinusoidal input, S may be set equal to $1/G_{max}$ where G_{max} is the maximum gain between the unscaled input and any point in the second-order section. This ensures that no internal signal exceeds the input in amplitude. In practice, it is sufficient to examine only the overall gain of the section $G(\omega)$, and the gain $G_1(\omega)$ between the input and the internal signal W . It can be shown that

$$G_{max} \leq 2 \max\{G(\omega), G_1(\omega)\} = 2M \\ 0 \leq \omega \leq \pi$$

$$\text{with } G(\omega) = |H_1(e^{j\omega})| =$$

$$\left| \frac{1 + a_1 e^{-j\omega} + a_2 e^{-2j\omega}}{1 + b_1 e^{-j\omega} + b_2 e^{-2j\omega}} \right|$$

$$\text{and } G_1(\omega) = \left| \frac{1}{1 + b_1 e^{-j\omega} + b_2 e^{-2j\omega}} \right|$$

M may be calculated by evaluating $G(\omega)$ and $G_1(\omega)$ over the range $0 \leq \omega \leq \pi$ and searching for the maximum modulus.

A Basic program for doing this is provided, see third listing. Choosing $S = 1/2M$ will eliminate the possibility of overflow for sinusoidal signals, and in practice will normally prove satisfactory for other types of signal. In many cases this result may be unduly pessimistic and larger scaling factors S may be used depending on the particular filter being implemented and the

type of arithmetic used. If G_{max} is significantly greater than the maximum value of $G(\omega)$ (overall gain) it may be necessary to scale up the output of a section to bring the overall passband gain to unity. Scaling factors are often approximated to the nearest power of two so that the required multiplication may be carried out by simply shifting the signal representation an appropriate number of bits to the left or right.

Example. Consider the scaling required for the first section of the bandpass filter whose impulse response is shown in the panel opposite. The coefficients a_1, a_2, b_1, b_2 for this section are $-2, 1, -1.0524, 0.6232$ respectively. By means of the program the maximum values of $G(\omega)$ and $G_1(\omega)$ are found to be 2.57 and 3.56 and hence $G_{max} \leq 2M = 7.12$. A suitable scaling factor is therefore $1/7.12 \approx 0.1404$. This would often be approximated to 2^{-3} , the nearest power of two, requiring the input to be shifted three bit positions to the right. As $G_1(\omega)$ is greater than $G(\omega)$ in this example, it would be necessary to scale up the output signal if a maximum gain of unity were required for the whole section.

Microprocessor implementation

In addition to its filtering task, a microprocessor may be required to control a-d and d-a converters, or alternatively interface with other digital devices as a means of signal input and output. When controlling converters it is necessary to provide some means of accurately maintaining a fixed sampling frequency.

The choice of microprocessor type depends mainly on the required sampling rate. The present generation of general purpose eight-bit microprocessors can provide digital filters with sampling frequencies of at most a few hundred hertz; the more powerful 16-bit microprocessors enables this to be increased to about 5 kHz.

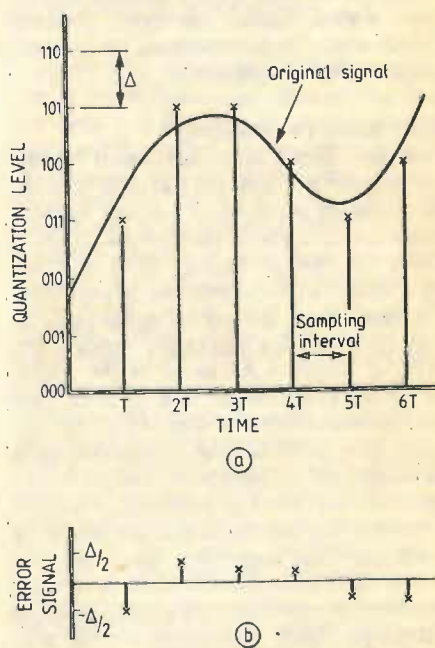


Fig. 2. Conversion of an analogue signal into digital form produces an error signal (quantization noise) which, in effect, is added to the original.

For the real-time filtering of audio band-width signals at sampling rates of about 8kHz and above, it has until recently been necessary to employ bit-slice microprocessors² or custom-designed hardware circuits which incur a high component count and circuit board complexity. The introduction in August 1980 of a microprocessor specifically designed for digital signal processing, the Intel 2920, significantly changed this position and marked the start of a new trend in digital signal processing. This is now being continued and emphasized by the introduction of a digital signal processor by NEC³ and the fad⁴, an l.s.i. digital filter designed by British Telecom. Details of other microprocessors intended for digital signal processing have been published⁵ by Texas Instruments and Bell Laboratories.

The Intel 2920 incorporates both a-d and d-a converters on-chip and when programmed as a typical eighth-order digital filter has a sampling rate of approximately 30kHz. As such, the device can be used simply as a one-chip replacement for audio-bandwidth analogue filters. More recent devices differ from the Intel 2920 in that they do not incorporate the converters, but provide the means for interfacing with external converters. These provide more powerful arithmetic facilities than the 2920, including fast high precision multiplication. Large program and data memories are provided by the NEC, Texas and Bell devices which should allow them to implement not only fixed filters, but also adaptive digital filters which automatically modify their frequency response as the characteristics of the input signal change.

The Plessey/British Telecom fad (filter and detect) is not strictly a microprocessor, but sacrifices flexibility for simplicity of operation. It contains on one chip all the circuitry necessary to implement the biquadratic filter section shown in Fig. 1. Used as a single second-order section, the device can operate at a sampling rate of 64000 samples per second, with each input and output sample being up to 16 bits in length. The fully programmable filter coefficients are supplied in serial form by external memory. As an alternative to act-

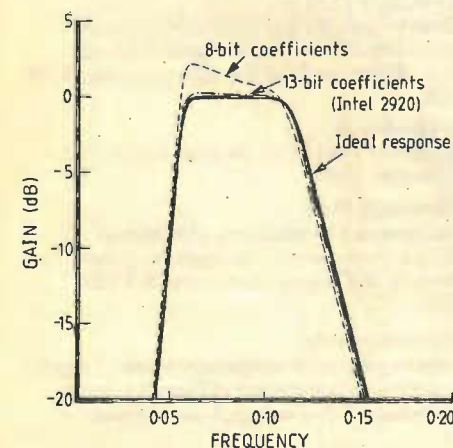


Fig. 3. Amplitude response of an eighth-order Butterworth bandpass filter shows effect of coefficient quantization.

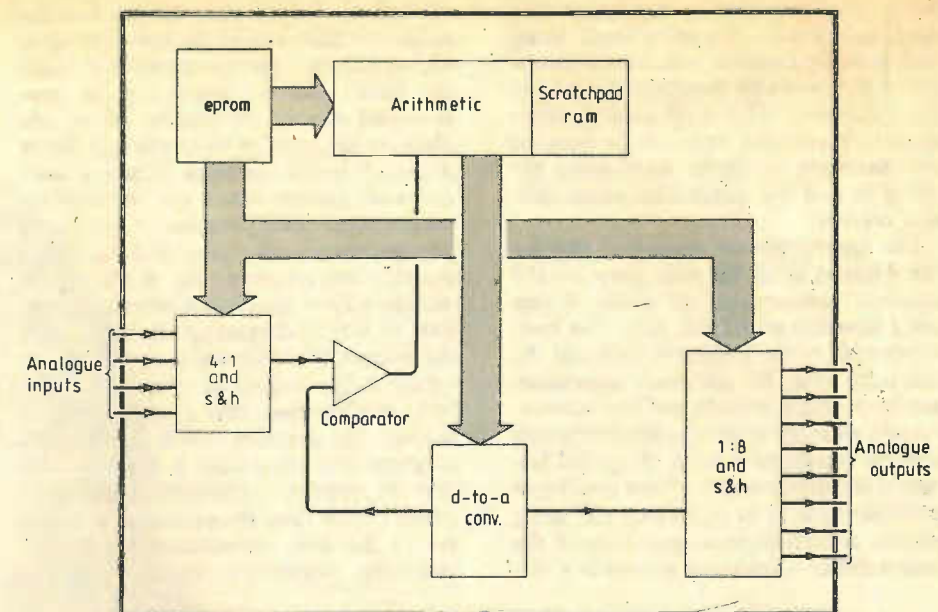


Fig. 4. Intel 2920 is basically a high-speed microprocessor connected to a nine-bit d-to-a converter, with eight multiplexed output channels under software control.

ing as a single second-order section, by using on-chip memory, the fad can be used in a multiplexed fashion to implement a cascade of eight second-order sections, providing a sixteenth-order filter with a sampling rate of 8000 samples per second. Cascades of between two and seven second-order sections can be implemented by modifying external connections.

To illustrate the full capabilities of microprocessor-implemented digital filters and to demonstrate how the techniques described may be applied to their design, consider in more detail the use of the Intel

2920. This device is now generally available, at gradually decreasing cost, and may be programmed by Intel users with a knowledge of digital filters without recourse to expensive design packages.

Intel 2920

Shown schematically in Fig. 4, the Intel 2920 consists basically of a high-speed microprocessor connected to a 9-bit d-to-a converter. The output is connected to a one-to-eight line multiplexer which is under software control. Eight signal output channels are therefore available. The out-

Program to implement fourth-order digital filter on general-purpose computer used in example on page 47

```

10 DIM P(100),Q(100)
20 PRINT "NO. OF SECTNS:"
30 INPUT N
40 PRINT "IDEAL COEFFS:"
50 GOSUB 170
60 FOR I=0 TO 100
70 P(I)=Q(I) @ NEXT I
80 PRINT "QUANTISED COEFFS:"
90 GOSUB 170
100 PRINT "FREQUENCY IDEAL AC
    TUAL(DB) @ N=0
110 FOR I=0 TO 100 @ F=1/200
120 PRINT USING "D.000,7D.2D,6D.
    2D": F,P(I),Q(I)
130 M1=ABS(P(I)-Q(I))
140 IF M1>M THEN M=M1
150 NEXT I @ PRINT "MAX DIFF=";M
160 STOP
170 FOR J=1 TO N @ K=J+J
180 PRINT J:" A1,A2,B1,B2="
190 INPUT C1(K-1),C2(K-1),C1(K),
    C2(K) @ NEXT J
200 FOR I=0 TO 100
210 W=PI*I/100 @ Q(I)=0
220 FOR J=1 TO 2*N
230 X=(1+C1(J)*COS(W)+C2(J)*COS(
    2*W))^2+(C1(J)*SIN(W)+C2(J)*
    SIN(2*W))^2
240 IF X<1.E-20 THEN X=1.E-20
250 Q(I)=Q(I)+(-1)^J*10*LG(X)
260 NEXT J @ NEXT I @ RETURN

```

```

5 DISP "A1,A2,B1,B2 ?"
10 INPUT A1,A2,B1,B2 @ A=1
15 GOSUB 35
20 DISP "MAX GAIN G(W) =" ;G
25 DISP "MAX GAIN G1(W) =" ;G1
30 END
35 G=-1 @ C1=-1
40 FOR F=0 TO .5 STEP .01
45 W=2*PI*F @ W2=2*W
50 R2=COS(W2) @ I1=-1*SIN(W)
55 I2=-1*SIN(W2) @ R1=COS(W)
60 N0=A+R1*I1+R2*A2 @ N=A1*I1
65 N1=N+A2*I2 @ D=1+B1*I1+B2*I2
70 D0=D @ D1=B1*I1+B2*I2
75 I=NUM(N0+J*N1)
80 I=DEN(D0+J*D1)-CVT TO EUL
85 N=N0*N0+N1*N1 @ N=SQR(N)
90 D=D0*D0+D1*D1 @ D=SQR(D)
95 H0=N/D @ H1=1/D
100 IF H0>G THEN G=H0
105 IF H1>G1 THEN G1=H1
110 NEXT F
115 RETURN

```

Program left compares responses of recursive filter with ideal and with limited wordlength coefficients. That above calculates maximum values of $G(\omega)$ and $G_1(\omega)$ for a biquadratic section.

put is also connected to one input of a signal comparator, the other input being derived from a sample and hold network driven by one of four multiplexed analogue input channels. This arrangement allows up to four analogue inputs to be sampled and converted to digital form using the converter and the comparator under software control.

The microprocessor section of the device contains an eeprom with space for 192 processor instructions, 40 words of ram and a specialist arithmetic unit. The basic wordlength of the arithmetic unit and the ram is 25 bits. All arithmetic operations provided, which include add and subtract but not multiply or divide, are performed in two's complement form. A special feature of the device which allows coefficient multiplications to be performed efficiently without a multiplication instruction is the binary shifter (sometimes known as a bar-

rel shifter). Before being loaded into the arithmetic unit, one of the operands in an add or subtract operation passes through the binary shifter, which can be programmed to shift the number up to two places to the right or up to thirteen places to the left in one operation. Hence, a 'shift and add' process which can be used for programmed multiplication is combined into one instruction. Other features which simplify the programming of the device include a fixed instruction execution time (600 or 800 ns depending on device) and the absence of conditional jumps which are replaced by conditional operations. The latter ensures that there is only one path through the program and hence that the program execution time is constant. An 'end of program' instruction is included, which causes program execution to transfer to the first instruction in memory, providing continuous repetition of the

program. As the input signal is normally sampled on each pass through the program, the sampling interval is equal to the product of the number of instructions and the instruction execution time. For example, a program containing 40 instructions run on a 600 ns device produces a sampling interval of 24µs i.e. a sampling rate of approximately 41666 samples per second giving a signal bandwidth of almost 21 kHz. This represents the theoretical upper limit and it is prudent in a practical system to allow some measure of oversampling and limit the signal bandwidth to say one third of the sampling frequency.

A technique based on the canonical signal digit code used for coefficient multiplications on the 2920 together with details of digital filters implemented using this device will be given in a subsequent article. □

References

1. Digital filter implementation on 16-bit microcomputers by H. T. Nagle & V. P. Nelson, *IEEE Micro*, February 1981, pp. 23-41.
2. Microprogrammable digital filter implementation using bipolar microprocessors, by M. E. Woodward *Microelectronics (GB)* vol. 10, September-October 1979, pp.23-31.
3. NEC µPD7720 data sheet, NEC Microcomputers, Inc., 1981.
4. Digital filtering using a custom designed device, by R. H. Macmillan & P. Millar, IEE Colloquium on Implementation of Digital Signal Processing Algorithms using Microprocessors, London November 1981.
5. Microcomputer with 32-bit arithmetic does

- high-precision number crunching, by K. McDonough *et al*, *Electronics*, 24 February 1982, pp. 105-10.
Bell System Technical Journal, September 1981, vol. 60, part 2 (various papers).
6. 2920 Design Handbook, Intel Corporation 1980.

References in June article

1. Oppenheim A. V. and Schaffer, R. W. *Digital Signal Processing*, Prentice Hall, 1975.
- Terrell, T. J. *Introduction to Digital Filters*, Macmillan 1980.
- Peled, A. and Liu, B. *Digital Signal Processing Theory, Design and Implementation*, Wiley, 1976.

2. Rader C. M. and Gold, B. Digital filter design techniques in the frequency domain, *Proc. IEEE*, vol. 55 1967, pp. 149-71.
3. Ackroyd, M. H. *Digital Filters*, Butterworth, 1973.
4. Constantinides, A. G. Spectral transformations for digital filters, *Proc. IEE*, vol. 117, 1970, pp. 1585-90.

Appendix to June article

To calculate \sqrt{x} where $x=a+jb$.
Convert x to Euler form $x=re^{j\theta}$, where
 $r=\sqrt{a^2+b^2}$, $\theta=\arctan b/a$.
Take square root $\sqrt{x}=\sqrt{r}e^{j\theta/2}$.
Convert \sqrt{x} to Cartesian form
 $\sqrt{x}=\sqrt{r}(\cos \theta/2+j \sin \theta/2)$.

EVENTS

August 5-6
Computational physics on the distributed array processor. Institute of Physics Conference at the University of Glasgow. Details from the Institute of Physics, 47 Belgrave Square, London SW1X 8QX.

August 14-17
Harrogate International Festival of Sound and Video at the Harrogate Exhibition Centre and at various hotels close by.

August 21-27
15th International Congress on high speed photography and photonics. San Diego, California, USA. Organised by the International Society for Optical Engineering, Washington 98227, USA.

August 26-September 5
Firato 82. Biennial exhibition and trade show for consumer electronics. At the RAI Exhibition Centre, Amsterdam.

September 2-6
SIM HI FIVES: International exposition of music and high fidelity has been extended this year to include a video and consumer electronics section. Milan Fair Centre, Italy.

September 6-7
Seventh annual microprocessor workshop at the University of Liverpool Computer Laboratory.

September 6-10
Annual Meeting of the British Association for the Advancement of Science. To be held at the University of Liverpool. BAAS, 23 Savile Row, London W1X 1AB.

September 6-9
Enrolment for course for the Radio Amateurs examination. Brixton College for Further Education, Brixton Hill, London SW2.

September 6-10
Microcoll 82: Seventh Colloquium on microwave communication. Budapest. Sponsored by the International Union of Radio Sciences and the Hungarian Academy of Sciences. Details from Microcoll, 1252 Budapest, 114, PO Box 15, Hungary.

September 7-10
6th International conference on computer communication. London. Details from ICC 82, PO Box 23, Northwood Hills, Middlesex HA6 1TT.

September 7-8
Semiconductor 82: Exhibition at the Bingley Hall, Birmingham.

September 7-9
Compec Scotland: Exhibition of computers, systems, peripherals and software. Sponsored by *Computer Weekly*. City Hall, Glasgow.

September 9-10
Microprocessors and their applications. Symposium at Bristol Polytechnic, Ashley Down Road, Bristol BS7 9BU.

September 9-12
The 5th Personal Computer World Show. Barbican Centre, London.

September 8-10
Eurographics '82: International congress for computer graphics. UMIST. Conference details from Andrew Yates, University of Manchester

Institute of Science and Technology, PO Box 88 Manchester M60 1RD.

September 13-16
12th European solid state device research conference, Munich. Details from Dr Zerbst, Siemens AG, Otto Hahn Ring 6, D-8000 Munchen 83, FRG.

September 13-17
12th European microwave conference, Finlandia Hall, Helsinki. Details from Microwave Exhibitions, 43 Dudley Road, Tunbridge Wells, Kent TN1 1LE.

September 14-16
ElectroWest; West of England electronics exhibition, Bristol. Exhibitions for Industry Ltd, 157 Station Road East, Oxted, Surrey RH8 0QF.

September 18
Computer Fair; Prestatyn High School PTA, Prestatyn, Clwyd.

September 18-21
International broadcasting convention: IBC82, Metropole Hotel, Brighton. Details from the IEE, Savoy Place, London WC2R 0BL.

September 19-24
Human aspects of computer systems: A short course at the Department of Human Sciences, University of Technology, Loughborough.

September 19-24
Industrial digital and microprocessor-based control systems. IEE vacation school at Baliol College, Oxford.



No hangover!

Hangover, a rather loose term to describe the stored energy resonance in a loudspeaker, the principal cause of colouration that immediately tells you you're listening to a loudspeaker.


Take it away and there's a new world – the loudspeakers have nothing more to say – instead there's just the orchestra and the magic of the music.



If music is an important part of your life, then a pair of ESL-63 loudspeakers could be the best investment you've ever made.

Perhaps even something to celebrate about.

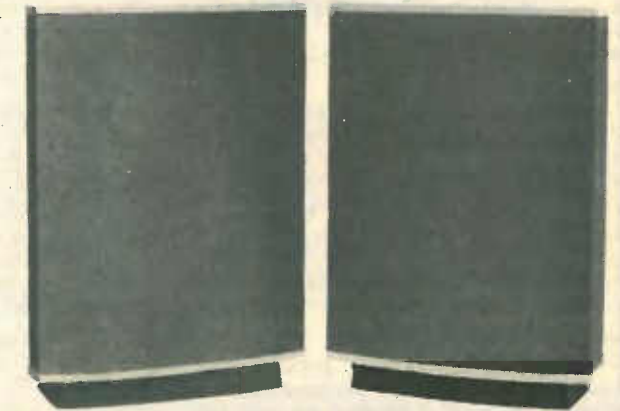For further details and the name and address of your nearest Quad ESL-63 retailer write or telephone The Acoustical Manufacturing Co. Ltd., Huntingdon, Cambs., PE18 7DB. Telephone: (0480) 52561.



QUAD 
for the closest approach
to the original sound

EP4000 EPROM EMULATOR PROGRAMMER



The microprocessor controlled EP4000 will emulate and program all the popular EPROMs including the 2704, 2708, 2716(3), 2508, 2758, 2516, 2716, 2532 and 2732 devices. Personality cards and hardware changes are not required as the machine configures itself for the different devices. Other devices such as bipolar PROMs and 2764 and 2564 EPROMs are programmed with external modules.

The editing and emulation facilities, video output and serial/parallel input/output provided as standard make the EP4000 very flexible to allow its use in three main modes:

- As a stand alone unit for editing and duplicating EPROMs.

Items pictured are: ● EP4000 Emulator Programmer - £545 + £12 delivery; ● BSC buffered simulator cable - £39; ● MESA 4 multi EPROM simulator cable - £98; ● 2732A Programming adaptor - £39; ● 2764 Programming adaptor - £64; ● 2564 Programming adaptor - £64; ●

- As a slave programmer used in conjunction with a software development system or microcomputer.
- As a real time EPROM emulator for program debugging and development (standard access time of the emulator is 300ns).

Data can be loaded into the 4k x 8 static RAM from a pre-programmed EPROM, the keypad, the serial or parallel ports and an audio cassette. Keypad editing allows for data entry, shift, move, delete, store, match and scroll, and a 1k x 8 RAM allows temporary block storage. A video output for memory map display, as well as the built-in 8 digit hex display allows full use of the editing facilities to be made.

BP4 (TEXAS) Bipolar PROM Programming module - £190
 Also available (not shown): ● VM10 Video monitor - £99; ● UV141 EPROM Eraser with timer - £78; ● GP100A 80 column Printer - £225; ● PI100 interface for EP4000 to GP100A - £65.
 VAT should be added to all prices

DISTRIBUTORS REQUIRED ● EXPORT ENQUIRIES WELCOME

GP Industrial Electronics Ltd.

Tel: Plymouth (0752) 332961
 Telex: 42513

Unit E, Huxley Close, Newnham Industrial Estate, Plymouth PL7 4JN

WW - 023 FOR FURTHER DETAILS

MICROCOMPUTER LINE PRINTER

This is the second of two articles describing an interface for driving a 40-column dot-matrix printer mechanism from Z80 signals. With the mechanism, addressing and interrupt sections covered, the author explains the controller i.c., power circuits, running the printer and modifications required to drive a 12V mechanism.

by P. L. Woods

Turning now to Fig. 3, the rest of the controller circuit can be considered. IC₂ is a bidirectional buffer designed to isolate the controller-board internal data bus from any noise on the system data bus, and vice versa. It is enabled only when the controller board is addressed, and the direction in which it passes data is determined by the \overline{WR} line buffered by IC_{1a} and IC_{3a}. To reduce noise problems, IC_{1a} is a Schmitt trigger, and similar buffers are used on the other control bus lines.

The control bus is connected to the printer controller chip, IC₁₄, and through three-state buffers, IC₁₃, to the status outputs of the controller i.c. It is also connected to IC₉, the interrupt reply byte circuit. Note that D0 from IC₉, pin 18, should go to D0 on IC₂, pin 2, and so on up to D7, pin 9 on IC₂ to pin 9 on IC₂.

A 6.0MHz clock for the controller i.c. is provided by an HC18/U or HC25/U crystal, XL₁. IC₁₄ contains the character generator for the printer, and the output

for the currently selected character appears on PS1 to PS7 (pins 27 to 33 respectively). High-voltage open-collector line drivers, IC₁₆ and IC₁₇, are used to send the signal to the solenoid drivers.

Two additional signals have to be sent to the printer; one is a paper advance signal, FS (at pin 21 of IC₁₄), the other is to turn the drive motor on and off, MT (pin 34).

Three status signals are needed back from the printer for correct operation. The first of these comes from a timing coil which allows the controller to correctly space the dots for each character. If no


timing pulses are found within 0.2s after the motor is turned on, the circuit assumes that the motor has stalled, so an error status is set (Error at pin 22), and the motor stopped to prevent it from burning out.

The second signal is from a reed relay which indicates when the printer carriage has reached the 'home' position, and that the motor may be stopped as it has finished printing a line.

The third status line is from a normally-closed pushbutton, connected to ground, which serves two functions. If the switch is depressed (open) when the Reset line goes high then the controller enters a test mode and prints lines of characters until the switch is closed. Otherwise, pressing the switch when the printer is idle advances the paper through the mechanism.

Solenoid and motor drivers
 Figure 4 shows a solenoid drive circuit. Seven of these circuits are required for the

Fig. 3. Controller i.c. and buffers. Mr Woods informs us that the controller, IC₁₄, is not the DPC-2 as given here and in last month's parts list, but is the DPC-4.

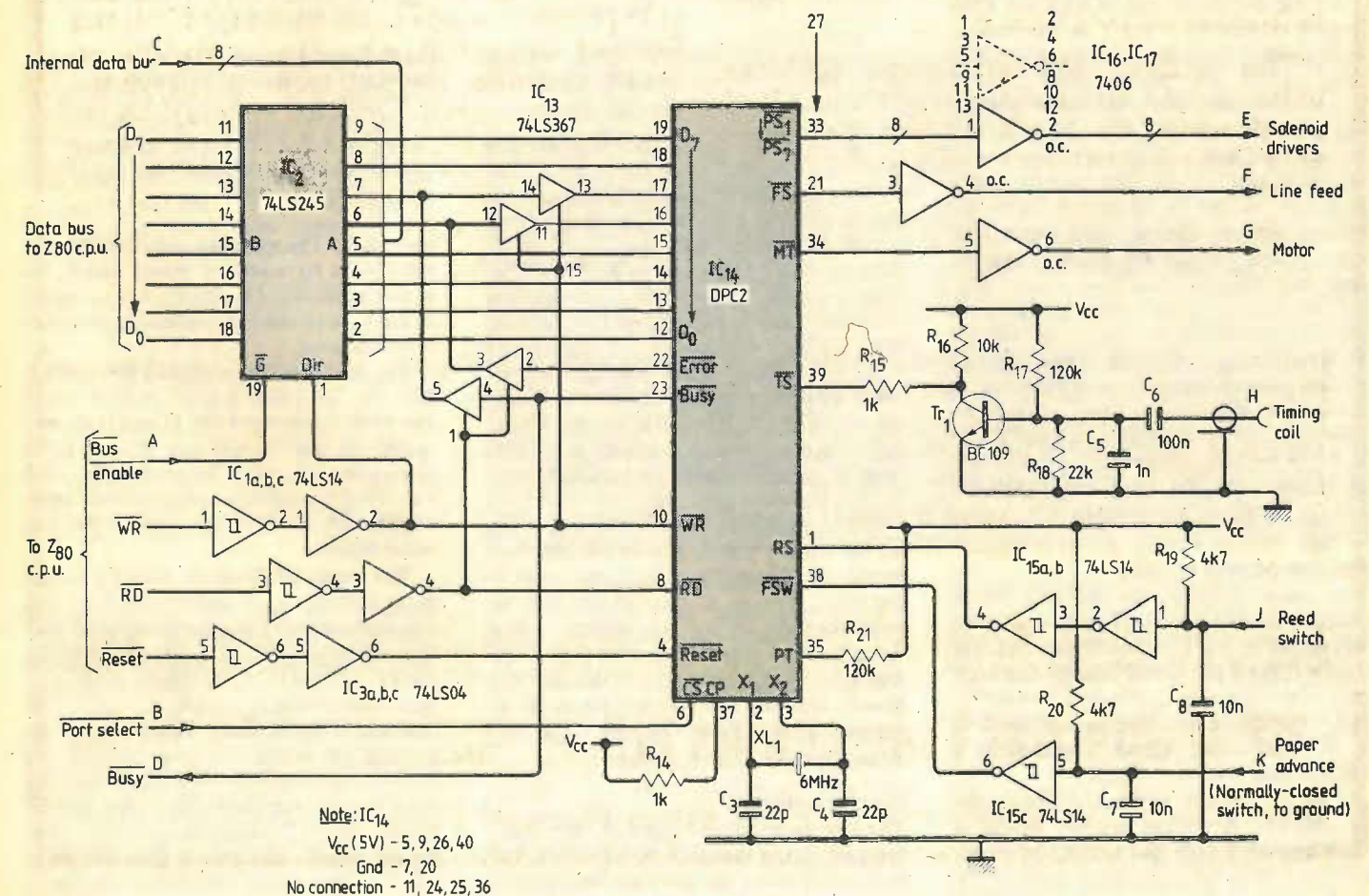

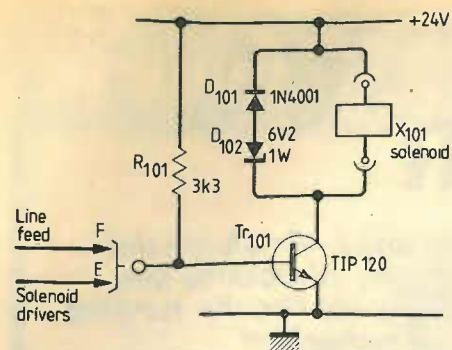


Fig. 4. Eight of these solenoid driver circuits are required, one for each of the seven needle drives and one for the line-feed solenoid. Tr101 is a power Darlington transistor.

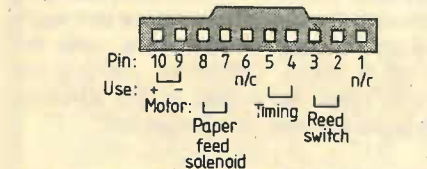
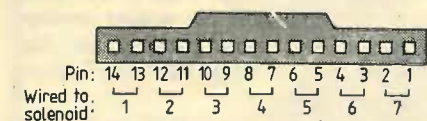


Fig. 7. Edge connector diagrams for the printer mechanism.

head solenoids and one for the line-feed solenoid.

As the circuit consists of only one Darlington transistor, it needs no discussion. One point worth mentioning though is that, should the circuit's input become open, as happens when the cable between the interface and printer board is disconnected, the solenoid is turned on. The effects of this will be explained later. No heat sink should be needed because, although the peak current is high (3.2A), the duty cycle is low. Diodes D101 and D102 are used to protect the transistor.

The driver for the motor is shown in Fig. 5, and is a little more complex because dynamic braking (through TR204) is used to stop the motor at the end of each line. A Darlington transistor, Tr203, is used to power the motor and will need a small heat sink. As with the solenoids, the motor will be turned on when the circuit's input is open.

Printer power supply

The circuit diagram for the two power supplies needed is shown in Fig. 6. Careful separation of the interface logic from the needle drivers has the advantage that each part of the circuit requires only one power rail. That for the interface logic (Figs 2 and 3) is 5V at about 300mA, supplied by a 7805 voltage regulator, IC301.

The 24V supply requires a little more explanation. A voltage doubler circuit is used because I only had a 12V, 2A transformer; a 24V, 1A transformer used with a

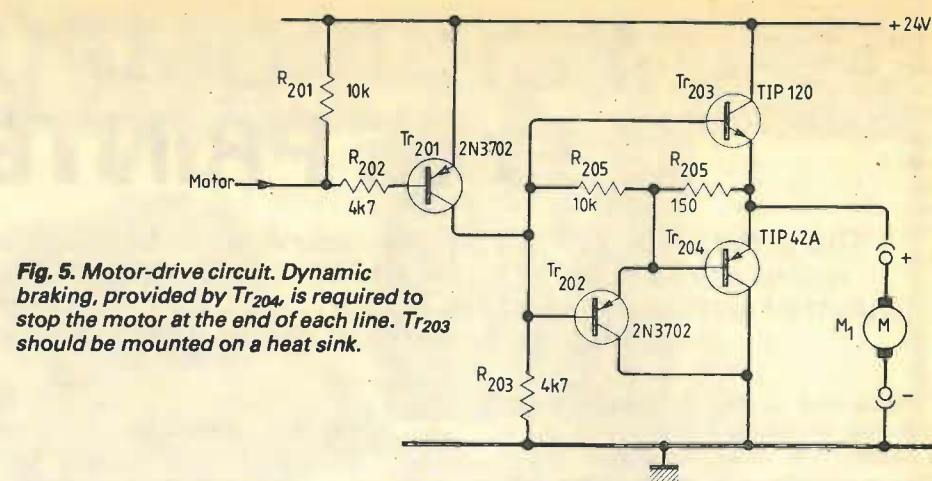


Fig. 5. Motor-drive circuit. Dynamic braking, provided by Tr204, is required to stop the motor at the end of each line. Tr203 should be mounted on a heat sink.

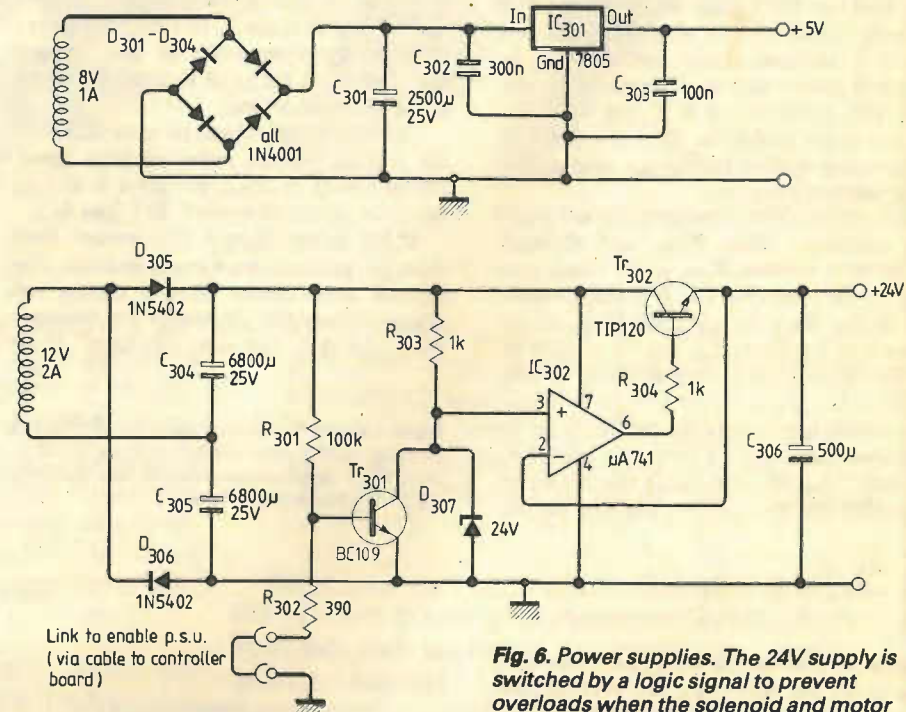


Fig. 6. Power supplies. The 24V supply is switched by a logic signal to prevent overloads when the solenoid and motor driving circuit inputs are open. The author had a 12V transformer in his 'junk box', hence the voltage doubler. Heat sinks are required for IC301 and Tr302.

bridge rectifier would perform equally well.

If the action of Tr301 is ignored, then the circuit is an op-amp, IC302, connected as a voltage regulator, with Tr302 as the series pass element. The purpose of Tr301 is to shut down the 24V rail should the control cable from the interface board to the solenoid drivers become disconnected. As mentioned above, in this event all the solenoid drivers, together with the motor driver, turn on. The resulting prolonged 30A current demand is sufficient to destroy the rectifier diodes, as happened during testing of the prototype.

So the link to enable the 24V rail is not on the supply board, but on the interface board, and two of the wires in the connecting cable are used to connect the link between the base of Tr301 and ground. Using a multipole connector ensures that if the flying lead is not plugged into the interface board, then the link will not be made, so turning off the 24V supply. Both IC301 and Tr302 will require heat sinks.

Construction

The circuit was constructed in two parts: the first is the interface board which was built to fit into a slot in one of the compu-

ter's cards. The solenoid and motor drivers were built on a second board which, together with the 24V supply, was mounted in the base of the box containing the printer mechanism.

The interface board should be carefully laid out, i.e., with a good ground mesh, and with the ground pin of each i.c. connected to that of the i.c.s around it. A decoupling capacitor is needed for each i.c., 10µF tantalum-bead capacitors alternating with 10nF ceramic disc capacitors being suitable.

The layout of the driver board is a little more difficult as it carries both t.t.l. signals and the heavy currents associated with the solenoids. Because of the solenoid surge currents mentioned earlier, a substantial cable is needed to connect the emitter of each driver transistor to the ground side of the 24V power supply. To avoid noise caused by the solenoids getting back into the interface, the digital ground return should be separate from the 24V-supply return, although it need not be as heavy. Once again, everything should be

Table 1: Program to display printer character set. This program was written to demonstrate the operation of the printer, and act as a confidence test for it. It is loaded at location 4000 (hex.) in memory, and should be entered, after the stack pointer has been set up, using a CALL instruction. This listing was produced on the printer described in this article, as was its result, shown in Table 2.

```

1 ; LISTING ONE.
2 ;
3 ; DISPLAY PRINTER
4 ; CHARACTER SET.
5 ;
6 ; COPYRIGHT.
7 ; PL WOODS. 1982.
8 ;
9 MAIN: EQU 4000H
10 ORG MAIN
11 LOAD MAIN
12 ;
13 ; PRINTER PORT ADDR.
14 PRT: EQU 11H
15 ;
16 ; RESET PRINTER
17 4000 CD5E40 CALL RESET
18 ; VALUE OF FIRST
19 4003 3E20 LD A,32
20 ;
21 ;
22 ; PRINT 14 LINES, EAC
23 ; BEGINNING WITH THE
24 ; VALUE OF THE CHAR
25 ; IN HEX. EACH LINE
26 ; CONSISTS OF FOUR
27 ; GROUPS EACH OF FOUR
28 ; CHARACTERS.
29 4005 060E LD B,14
30 4007 CD3140 LINE: CALL PRTHX
31 400A CD6540 CALL SPACE
32 ; SET UP FOR GROUPS.
33 400D C5 PUSH BC
34 400E 0604 LD B,4
35 4010 CD6540 GROUP: CALL SPACE
36 ; SET UP FOR EACH

```

Table 2: The printer's character set. This listing shows the result of running the program in Table 1. The first four lines (values 20 to 5F inclusive) are an upper case ASCII character set, while the last six lines (from A0 to FF) are a Kata Kana (Japanese) character set. The middle four lines are not specified for the controller chip used and so represent 'noise'.

```

20 ! " # $ % & ' ( ) * + , - . /
30 0 1 2 3 4 5 6 7 8 9 : ; < = > ?
40 @ A B C D E F G H I J K L M N O
50 P Q R S T U V W X Y Z [ \ ] ^ _
60 ` a b c d e f g h i j k l m n o
70 p q r s t u v w x y z { | } ~
80
90
A0
B0
C0
D0
E0
F0

```

```

37 ; CHARACTER.
38 4013 C5 ; PUSH BC
39 4014 0604 LD B,4
40 4016 CD6540 CHAR: CALL SPACE
41 ; PRINT CHARACTER.
42 4019 CD4C40 CALL PUTPRT
43 ; NEXT CHARACTER.
44 401C 3C INC A
45 ; END OF GROUP?
46 401D 10F7 DJNZ CHAR
47 ; END OF LINE?
48 401F C1 POP BC
49 4020 10EE DJNZ GROUP
50 ; TERMINATE LINE.
51 4022 CD2940 CALL NEWLIN
52 ; ALL LINES DONE?
53 4025 C1 POP BC
54 4026 10DF DJNZ LINE
55 ;
56 ; ALL DONE.
57 4028 C9 RET
58 ;
59 ; START A NEW LINE.
60 4029 F5 NEWLIN: PUSH AF
61 402A 3E0A LD A,0AH
62 402C CD4C40 CALL PUTPRT
63 402F F1 POP AF
64 4030 C9 RET
65 ;
66 ; PRINT 'A' AS TWO
67 ; HEX DIGITS.
68 4031 F5 PRTHX: PUSH AF
69 ; HIGH DIGIT.
70 4032 0F RRCA
71 4033 0F RRCA
72 4034 0F RRCA
73 4035 0F RRCA
74 4036 CD3E40 CALL PRTHX
75 ; LOW DIGIT.
76 4039 F1 POP AF
77 403A CD3E40 CALL PRTHX
78 403D C9 RET
79 ;
80 ; PRINT LOW 4 BITS OF
81 ; 'A' AS A HEX DIGIT.
82 403E F5 PRTHX: PUSH AF
83 ; MASK BITS
84 403F E60F AND 0FH
85 4041 B7 OR A
86 ; CONVERT TO ASCII
87 4042 27 DAA
88 4043 C6F0 ADD A,0FH
89 4045 CE40 ADC A,04H
90 4047 CD4C40 CALL PUTPRT
91 404A F1 POP AF
92 404B C9 RET
93 ;
94 ; PRINT THE CONTENTS-
95 ; OF THE 'A' REG.
96 404C F5 PUTPRT: PUSH AF
97 ; LOOP UNTIL PRINTER
98 ; READY.
99 404D DB11 PRLP: IN A,(PRT)
100 ; CHECK ERROR STATUS.
101 404F CB67 BIT 4,A
102 4051 2B08 JR Z,PRERR
103 ; BUSY BIT.
104 4053 CB57 BIT 2,A
105 4055 2BF6 JR NZ,PRLP
106 ; SEND CHARACTER.
107 4057 F1 POP AF
108 4058 D311 OUT (PRT),A
109 405A C9 RET
110 ;
111 ; HERE IF THERE IS
112 ; A PRINTER ERROR.
113 405B 76 PRERR: HALT
114 405C 18FD JR PRERR
115 ;
116 ; RESET PRINTER
117 ; CONTROLLER.
118 405E F5 RESET: PUSH AF
119 405F 3E11 LD A,11H
120 4061 D311 OUT (PRT),A
121 4063 F1 POP AF
122 4064 C9 RET
123 ;
124 ; PRINT A SPACE.
125 4065 F5 SPACE: PUSH AF
126 4066 3E20 LD A,' '
127 4068 CD4C40 CALL PUTPRT
128 406B F1 POP AF
129 406C C9 RET
130 END

```

Conversions for a 12V printer mechanism

After this article had been completed, a version of the printer mechanism for use with a 12V supply, the DP-824F-12, and associated controller, the DPC-4A, were introduced; this section describes modifications required to accommodate these.

Pin connections on the 12V mechanism are exactly the same as those on the 24V model. The DPC-4A i.c. can be used to control either version of mechanism by altering the signals on certain pins.

On the 12V mechanism, the solenoids require a 730µs pulse, as opposed to 400µs for those of the 24V version. This pulse length is determined by the controller and depends on the logic state at pin 35, the 'printer type' terminal (PT). When this pin

is tied to the +5V rail, as shown in Fig. 3, the pulse length is 400µs. For the 12V mechanism, R21 must be changed to 1kΩ and wired to ground instead of +5V.

Current requirements for the 12V mechanism's solenoids and motor are higher because of the lower supply voltage. Hence, R101 of Fig. 4 should be reduced to 2.2kΩ in all eight solenoid-driver circuits, and R202 of Fig. 5 reduced to 3.3kΩ.

Finally, the voltage doubler used in the 24V supply, Fig. 6, can be replaced by a bridge-type rectifier and single smoothing capacitor (say, 10 000µF, 25V). The zener diode, D307, should be replaced by a 12V type.


Both the 24V and 12V mechanisms mentioned are friction-feed types but sprocket-feed versions, available from the same manufacturer, may be used.

Demonstration program

Table 1 is a program, written in Z80 assembly language, which is designed to test the printer by causing it to display its complete character set. The results of this program are shown in Table 2. The program is loaded into memory at 4000 (hex.), a convenient location in my system, and is entered from a system monitor which first sets up the stack pointer (SP register), and then pushes a return address onto the stack (e.g. by the use of a CALL 4000 instruction). The test program exe-

The two boards (interface board and driver board) were interconnected by multi-core cable and sub-miniature 25-way 'D' connectors. The precise allocation of the pins to the various signals does not matter too much provided that there are ample ground-return lines. Cable length should not matter too much either, as the signals are all relatively low in frequency, but anything over 1m in length could cause noise problems. The screen of the connecting cable should be earthed to improve reliability.

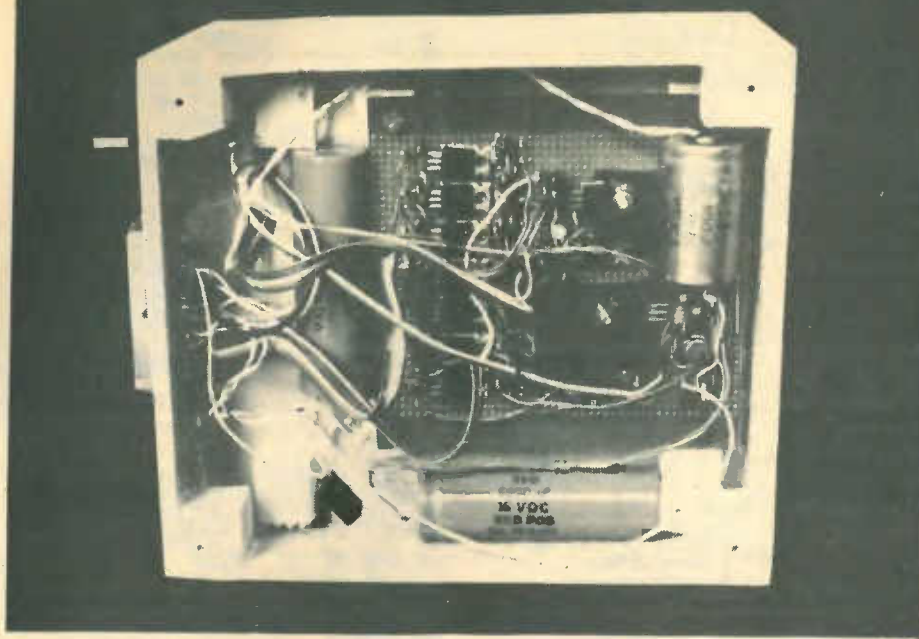Solenoid driver board. Mounted in the base of the printer box is a driver for each of the matrix needles, the paper advance relay and motor. There is also a 24V power supply.



cuts a RET instruction when finished.

This article is not the place to introduce assembly language programming, and so instead of a detailed description of the program, notes are given to assist those wishing to use all, or part, of the program for their own purposes.

The port address of the printer is declared in an EQU pseudo instruction at line 14. This address must correspond with the address used by the hardware.

There are three interface driver routines of interest, namely RESET, PUTPRT and NEWLIN. Starting at line 118 is a subroutine called RESET. The purpose of this is to 'set' the printer controller should a previous program error have left it in an unacceptable state. The same effect may be achieved by using the RESET bus signal. As good practice, a CALL to RESET should be made at the start of each program which accesses the printer. No

registers are modified by this subroutine.

The second subroutine of note, PUTPRT at line 96, may be regarded as causing the character sent to it from the 'A' register to be printed. PUTPRT waits until the printer is ready, then transfers a character from the 'A' register to a print buffer in the printer controller i.c. If the printer error bit is set, the subroutine will halt at address 405B. Normally this point would contain a code to alert the operator to a printer problem. If there is no error the subroutine returns, leaving all registers unmodified.

The third and final subroutine to inspect is NEWLIN, at line 60. The purpose of this is to cause printing of the line in the controller print buffer, which it does by sending an OA character (line feed) to the printer. Once again, this routine does not change any registers. It should be noted that this subroutine must be called at least once every 40 characters to avoid the print buffer becoming full, in which case, overflow characters will be lost.

Conclusion

In this article it has been shown that it is possible to build a low-cost printer for a home-computer system. Although this design was originally intended as a means of printing programs from a Z80-based system, it may easily be adapted to make it compatible with any popular microprocessor and for use in any application where a permanent printed record is required, such as data logging. That the controller only allows upper-case graphics characters to be printed is not a problem for the majority of applications. □

BOOKS

Computing

From Hardware to Software

by Graham Lee
454 pages, paperback/hardback
MacMillan, £8.95/£16.00

This is an introductory text, albeit an extremely thorough one, and covers both equipment and programming at a level suitable for A level or first-year university courses. The author has used a computer model - the Simple Digital Computer - throughout, with which to illustrate his points more generally than would have been possible with a commercial design.

Advanced 6502 Interfacing

by J. M. Holland
190 pages, paperback
Prentice-Hall, £9.05

This book is practical in its approach to the subject of persuading 6502 microprocessors to perform useful functions in timing, control, data acquisition and high-current load driving. It is written for those who are already familiar with microprocessors.

Introduction to 6800/6802 Microprocessor Systems

by R. J. Simpson and T. J. Terrell
238 pages, paperback
Newnes £6.95

For readers who may not be versed in the language of logic and binary arithmetic, the authors have included a useful first chapter on basics before embarking on a description of the 6800/6802 devices and their use. This is followed by chapters on programming and on input/output signals, the practical approach being the province of the final two chapters on the MEK6802D5 evaluation system, with some investigations to carry out with its help.

Microcomputer Data Communications Systems

by F. J. Derfler, Jr.
129 pages, paperback
Prentice-Hall, £9.70

Microcomputers can serve as terminals in a data communication network to provide information at home, as an alternative to what the author calls the 'time tyranny' of radio, television and newspapers. The book describes such systems, including sections on modems and terminals, and going on to show how Apples, TRS-80s and others can be employed in this way. There is also a piece on using the CP/M disc operating system with S-100 bus computers and others.

Video

Video-Tape Recording

by J. F. Robinson, revised by S. Howe
362 pages, hardback
Butterworth, £12.00

The third edition of a well known text, this covers the whole field of professional and domestic video tape recorders from the engineering point of view. New information is presented on the helical B and C formats, and the domestic type of machine, with additional coverage of timebase correction. Those familiar with television engineering are led easily into the subject by the way of a first chapter on tape recording in general terms.

Video Techniques

by G. White
299 pages, hardback
Butterworth, £10.95

Although the blurb says that this is for the engineer or technician in television or ancillary industries, it hardly seems detailed enough for that purpose. It is a descriptive book, which is well suited to readers in other fields who want to obtain a working knowledge of television, both broadcast and recorded, studio equipment, transmission, reception (including teletext and viewdata) and digital techniques.

LETTERS

BRITISH HI-FI

I'm informed by John Crabbe of *Hi-Fi News/Record Review* that the Acoustical manufacturing company's claim that the QUAD FM4 brings 'Home the world's best broadcasting system at the touch of a button' is ethically justified, as Acoustical, in contributing to the support of the Philharmonica, helps to pay the piper.

Most other British high fidelity manufacturers do not, and subsist upon music making of all kinds parasitically, and thus have no prestige or reputation internationally amongst serious consumers of reproduced music.

By and large, British high-fidelity products are not materially competitive or competitive in terms of dazzling or convenient features. But they are perhaps more competitive qualitatively. Unhappily, however, recognition of their qualities is pretty well reserved to engineers, technicians, and 'hi-fi fans'. Most serious consumers of reproduced music, here and abroad, don't know about them, and have precious little opportunity to learn.

Thus, while the programming and technical quality of the world's best broadcasting system is revered - and envied - internationally, British high-fidelity products are known about and coveted only by the membership of tiny audiophilic cults, here and abroad.

I have at hand No 1 of the 1982 Edinburgh Festival newsletter. It's publication was apparently entirely supported by the advertisements of hoteliers, restaurant-keepers, one or two insurance companies, and a bank or two. Many people who will attend Festival events, or wish to, and many who - due to privation or remoteness - are dependent upon broadcast reception and recordings for musical enjoyment during most of the year, will remain in ignorance of the products of Linn, Syrinx, Strathclyde Transcription Devices, the makers of the Systemdek, and even Tannoy - not to mention KEF, B&W, Sugden, Castle, Celef, Mitchell, Acoustical, Naim, Riga, C&J Walker, MB Creek, Boothroyd, Stuart-Meridian, and even Wharfedale, south of the border.

It would be too charitable to say that the British high-fidelity industry has its head in the sand. A harsher but more appropriate judgement would suggest that it is contemplating its own navel from the inside, is unwholesomely involved and beguiled subjectively by its own entrails.

John F. Withey
Pollockshields
Glasgow

SCIENTIFIC COMPUTER

Please could you note in your records that I am the new Editor of *The Sci. Comp.* 80 monthly newsletter for users of the scientific computer designed by John Adams, M.Sc., details of which were published in your magazine.

Any of your readers who built the SC80, who are not members of the group, would find it well worth joining. Back issues, still available, contain a plethora of hardware, software and firmware. Mr Adams contributes articles monthly, and has developed no less than five versions of the BURP high level language, an excellent 64K d.o.s. (CP/M compatible), a standard Basic interpreter and some excellent hardware improvements. These include a 32K

dynamic memory expansion, 64K mapping circuits, interrupt vector circuits, ASCII character generator modification and a floppy disc controller p.c.b. Details of all these are in the newsletter. One year's subscription is £6.50 for U.K. members, £8 for the continent, and £8.50 for elsewhere. Cheques sent to the address below.

I would like to take this opportunity to thank Mr Philip Probetts for the past two years of excellent newsletters under his editorship. I hope I can do as well.

John Hodson
189 Trent Valley Road
Oakhill
Stoke-on-Trent, ST4 5LE

AMATEURS AND CB

C. G. Howard's comments in the June issue of *WW* under 'Amateurs and c.b.' highlighted the indifference of the Home Office towards illegal c.b. amateur operations. But what about the specific identifiable violations where the Home Office attitude is downright irresponsible?

I am referring to the illegal pirate radio stations that flagrantly operate in the v.h.f./f.m. broadcast band. There are a number of them, but two examples serve to illustrate the general case - 'Thameside Radio' and 'Liberation Radio'.

I asked British Telecom why these stations were not closed down and imagine my surprise, as a legal broadcasting operator, when I was told that the Home Office would not give the necessary authorization for British Telecom to do so. Must a campaign be mounted privately to ensure that the law of the land is upheld when a government department refuses to do so? Continual violation of the law in this way is a form of anarchy, in principal every bit as bad as other, more subversive, movements.

The Home Office, in supporting the violation of statutory laws by its non-action is encouraging further escalation. This is yet another of a growing number of examples of where government legislation controls the actions of responsible citizens but not those who chose to flout the law of the land.

H. Clayton
Northwood
Middlesex

CARTRIDGE ALIGNMENT

Referring to P. E. Cryer's letter in the June 82 issue, I found some difficulty in understanding the layout instructions in his second paragraph together with the associated diagram on the next page. However, it is of course quite true, as he says, that it makes no difference to the geometry whether you think of the stylus traversing over the record, or the record traversing under the stylus; all that matters is the relative moment of the two.

Two or three points seems to warrant comment: firstly, there is nothing particularly new or useful in finding out that the *proportion* of tracking angle errors depends on the choice of setting radii - of course it does. It is necessary, in the interests of minimizing tracking error *distortion*, for the angular error to vary inversely with radius, and as Cryer's figures indicate, this is exactly what does happen. The relationship of tracking angle errors at both outer and inner radii to the error at the radius for minimum

angle (my R_{min}) depends on the amount of dip in the curve of angle across the record, as is obvious from my Fig. 1.

Secondly, I cannot understand Cryer's statement that my own factors "would place B on the other side of the datum line". If the datum line is defined as a line through the two points where the stylus cuts the circles having radii p and q as in his diagram, then obviously the intersections at both inner and outer record grooves (his B and A) must necessarily lie on one side of the said datum line, and none of my 'factors' can alter this condition.

Thirdly, Cryer's roundabout method of calculating p and q as described in his last paragraph, cannot work. The expression $p/q/p=(p+q)-p$, is meaningless, a mere identity which reduces to $q=q$. Obviously it cannot be used to separate q from p when $(q+p)$ is known. The whole point of my final paragraph in the Oct '81 issue, was to show that one did not need to go through the whole procedure based on formula 4(b) every time, in the light of the linear $y=a+bx$ relationship ascertained at middle of paragraph. The final outcome, which cannot be simplified or improved, was to evaluate p and q (my r_0 and R_0), from the empirical expression $R_0=79+hC/84$ and $r_0=12+hC/71$ or ideally L^2-C^2/R_0 . For the recommended overhang value of $h=2600/C$, this reduced further to $R_0=110$ and $r_0=49$ (ideally 48.81, but the 0.19 discrepancy is insignificant in practice).

If one uses a protractor, or my setting gauge, as in the November 1981 article, there is no need to evaluate the offset angle O (my B), but if desired it can be very easily obtained, within about 0.1° accuracy, from my empirical expression 4380/C.

R. J. Gilson
Winchester
Hampshire

HERETIC'S GUIDE TO MODERN PHYSICS

I was delighted to see you are still providing a forum for open and constructive criticism of modern theory.

That Dr Murray should need to assure his colleagues that he has "no wish to cause you offence" is a sad comment on the state of physics. Doubtless his article is the result of a long and critical investigation of modern theory, and he would welcome any constructive criticism of his article. Equally doubtless, a few of his colleagues know his investigation is a deliberate attempt to revive the flat earth theory and Maxwell's wave theory of light - an insult to Newton's corpuscular theory of light.

I predict Dr Murray will soon learn to appreciate the truth of the supreme investigator, Michael Faraday's bitter response to the hostility to his theories of the self-satisfied mathematicians of his day - "A man who makes assertions, or draws conclusions, regarding any given case, ought to be competent to investigate it."

Many Nobel prizes were awarded for contributions to the basic premise of relativity - that nothing in the universe can travel faster than the speed of light. Cerenkov received the 1958 prize for his experimental proof that "when charged atomic particles pass through water or other media at a speed in excess of that of light itself, a bluish light is emitted."

Aspden, Dingle, Essen, MacCausland and other critics of relativity are dismissed as cranks and crackpots by the Establishment. Is there any member of the Establishment competent to investigate the strange case of why the crank Cerenkov received a Nobel prize?
M. G. Wellard
Kenley
Surrey

WALSH FUNCTIONS

I write with respect to the recent articles on Walsh Functions by Mr T. Roddam (WW Dec. 1981, pp 31 et seq. and WW Jan. 1982, pp 47 et seq.) to raise the following points.

The Rademacher functions, shown in Fig. 4 of this series correspond to Wal (1,0), Wal (3,0), Wal (7,0), Wal (15,0) . . . The associated intermediate Walsh functions may be derived by "exclusive Or" processing all combinations of the Walsh functions. Thus, for example referring to Fig. 3, the Wal (2,0) function is derived from Wal(3,0)⊕Wal(1,0) and should be inverted in the Figure. Several other derived Walsh functions have been inverted in Fig. 3. A correctly-signed set is enclosed for reference.

There is also an error in Fig. 5.

$$\text{Wal}(5,0) = \text{Wal}(2,0) \oplus \text{Wal}(7,0)$$

which does not hold for this diagram. I enclose a modified diagram which will satisfy this requirement. Incidentally, the paper by Barratt, Gordon and Brammer also contains these errors.

I mention these slips since many people seem to be becoming interested in these functions that valuable introductory articles, such as Mr Roddam's are worth these small corrections in the interests of accuracy.

R. T. Irish
Swindon,
Wilts.

Mr Irish enclosed an amended set of functions, which we have regretfully been obliged to omit for reasons of space. They can be obtained from this office - Ed.

FUNCTION OF FUNCTIONS

With reference to Mr Sutherland's letter (June), I think that the view of sidebands as mathematical fiction is not entirely unfounded. I believe that a periodic complex waveform and its Fourier series expansion are not one and the same thing in the sense of somehow being freely interchangeable without the active involvement of suitable physical devices to perform the complex series and conversion and vice versa. On this view a modulated radio transmission propagates in its complex form and there is no need to postulate any sidefrequencies at the transmitter end. The sidefrequencies are generated at the receiving end by tuned circuits. These have the capability to store energy and thus perform integration, thereby generating the continuous waves known as Fourier series components or sidefrequencies. The physical process by which a sidefrequency is generated can be understood by considering the following experiment:

Suppose that a high "Q" tuned circuit is adjusted for resonance at 110kHz and placed near a 100kHz oscillator. Clearly, the tuned circuit will not begin to oscillate since any such oscillations would move in and out of phase with the oscillator, thus receiving just as much help as hindrance. However, should the amplitude of the oscillator be decreased whenever out of phase with the tuned circuit and increased when in phase, then the tuned circuit would receive more help than hindrance and would build up oscillations. It would oscillate at 110kHz whilst receiving its energy in burst of 100kHz. Assuming a very high "Q", the inertia of the tuned circuit would be large enough to smooth out any amplitude variations and it would appear to receive a continuous wave input (i.e. one of the sidefrequencies). In fact it would be generating the continuous wave.

For the above process to take place the amplitude of the oscillator would have to be altered (i.e. modulated) at 10kHz which is, of course, the appropriate modulating frequency for the

110kHz sidefrequency.

It is interesting to note that it would not be essential to alter the amplitude of the oscillator in order to generate the 110kHz response. The same effect could be achieved by alternating the phase of the oscillator at 10kHz, which suggests how sidefrequencies are generated in the case of suppressed carrier, frequency and phase modulation systems.

So, although the sideband concept is a very useful, even essential part of radio theory, it is not necessary to assume that sidefrequencies have physical existence prior to the complex waveforms arriving at the receiving equipment. As explained by the *Wireless World* contributor Cathode Ray (September 1955, under the heading "Fourier - Fact or Fiction") continuous sinewaves are not the only possible form into which complex waveforms may be "decomposed", and hence it makes sense to assume that the sine form occurs simply because of the sine-wave nature of oscillations in tuned circuits at the receiving end of transmitter - receiver link.
G. Berzins
Frimley
Surrey

REMOTE CONTROL FOR HI-FI

I read Mr Kirby's article on a remote control hi-fi system (WW, March 1982) with some interest, as I was at that time busy designing a similar system. I too used the Mullard voltage-controlled potentiometers for control of the audio signal path, but found a much simpler and cheaper remote control system.

The major drawback of Mr Kirby's system seem to be the fact that the Plessey receiver (ML 922) only has three analogue control outputs; hence the need to use a 'stepped' volume control. The Motorola remote control system (MC 14497 - transmitter and MC 6203 - receiver) has four analogue channels and a host of other useful features. For example, toggle action volume mute and a single button operation which sets three of the analogue channels to 50% and the fourth to 30%.

This system is the same as that used on Grundig remote control television and so the modifications for hi-fi applications are quite simple. I wondered whether Mr Kirby was aware of this possibility and if not, and he was interested, I could send him some details.

D. F. Lovely,
Bioengineering Unit,
University of Strathclyde.

The author replies:

It seems from Dr Lovely's comments that we are heading in opposite directions. I regard the use of the two analogue outputs on the Plessey ML 922 as a necessary evil! I would much rather have used all digital tone level setting controls. The reason I did not was my inability to design a stereo bass and treble control circuit using less than four of the Analog Devices AD7110 chips. These cost around £8 each and the extra expense compared to the use of the Mullard analogue tone control i.c. seemed unwarranted.

I chose the Plessey remote control chip set (after looking at several alternatives) because of the analogue and digital outputs available on the ML922, and their use of an infrared photodiode to logic level integrated preamp, which saves much trouble with discrete high gain amplifiers.

Also a whole family of receiver chips are available, including one with a 5 bit latched output for a microcomputer interface, all operated by the same transmitter.

There is a toggle output on the ML922; this is used to switch the loudspeaker headphones relay, a quite effective mute control. In practice the 3/8 full scale normalised level of the analogue outputs is not a disadvantage; I rarely alter the tone by more than 1/8 of the scale.

My choice of the AD7110 was for the relative simplicity of driving it from a single chip microcomputer (the Zilog Z80), which can be programmed in Basic, as well as machine code. Then the interface between the controlling computer, and the controlled preamp/tuner/record deck can be some simple buffers. All the decoding from the received codes to the sequences necessary to drive, say, a synthesising tuner could be handled in software. This would make it easily adaptable to the various units commercially available. The prom decoding and sequencing logic used in the published design are an interim solution.

D.C. INPUT OR R.F. OUTPUT?

In "Amateur radio" for June, 1982, Pat Hawker laments the replacement of "d.c. input power" regulations by new limitations on "dBW carrier power" in the revised Amateur Licence Schedule. While I tend to agree that the dBW is not particularly welcome, the change to an "r.f. output" criterion is long overdue.

"D.c. input" was firmly rooted in the days of valve transmitters and constant-carrier modes, when both h.t. voltage and anode current were metered, and the meter needles would stay still to be read! For most radio amateurs - like it or not - those days are gone. Either our transmitters tend to be solid-state and have only r.f.-output metering, or they are primarily designed for s.s.b. In both cases it makes more sense to measure r.f. output, and this can be done with acceptable accuracy for the Amateur Service. At low powers, the accuracy requirement is minimal (at least for regulatory purposes), and at higher powers either commercial power meters can be used, or extremely simple homemade equipment, such as an existing s.w.r. meter can be calibrated accurately by transfer.

Although a d.c.-input limit does encourage high-efficiency amplifiers, is that what we really need? In today's crowded bands, the most important characteristic of a signal is its quality, and an r.f.-output limit allows amateurs to operate their transmitters in a more linear, though less efficient, manner.

The demise of d.c.-input limits is a welcome advance, but other relics of the past remain in the new Schedule: for example, the 6dB difference between the power limits for c.w. (A1A/B) and for s.s.b. (J3E). Can anyone explain how a c.w. signal with a well-shaped keying waveform differs significantly in interference potential from an s.s.b. (J3E) signal of the same peak envelope power, and why the power limits for the two modes should not be the same? The 6dB penalty against c.w. is a legacy of the transition to s.s.b. from plate-and-screen modulation, and has no current relevance. In any further revisions of the Schedule it deserves a decent burial, alongside d.c. input limits.

Ian F. White, G3SEK
Abingdon
Oxfordshire

THE NEW ELECTRONICS

It is at least eight years since I shared the responsibility for selecting graduates for employment in an electronics development laboratory, and I read with interest and dismay Mr Jaques' article in the January issue.

I was interested in that some of Mr Jaques' questions were similar to the ones I put to interviewees, and dismayed because the responses he obtained mirrored so closely those that I obtained all too often. True, my own efforts were rewarded by the occasional interviewee who did *understand* some of the principles with which he had been presented and could perhaps even describe his final-year project clearly and accurately! Indeed a few such went on to become much respected colleagues.

However, it is not Mr Jaques' article which prompts the writing of this letter, but rather the contradictions and inconsistencies in the letters about this article which appeared in the March and April issues. In a letter of reasonable length I can only draw attention to a few of these.

There is much to agree with in Mr Graham's letter - I too would reach for my text books to deal with Tensor analysis etc., etc., etc., and must agree entirely with his reference to "learning by rote" - but what is the relevance to Mr Jaques' article?

Mr Jaques' questions are all of an elementary nature - for example, surely a qualified electronics engineer might reasonably be expected to derive the expression for the gain of the amplifier configuration in thirty seconds flat, even if didn't remember " $-R_2/R_1$ ". Does it really require a text book on op-amps to deal with this? (Why does it have to be an op-amp anyway?)

Perhaps Mr Graham would tell us - I really would love to know - which text book does he reach for when he wishes to remind himself about Ohm's Law?

Surely the point is that an elementary *understanding* of circuit theory and device fundamentals is all that is required to answer most of Mr Jaques' questions? That is, are they not nearly all designed to avoid testing the mere ability to recall tabulated data from the candidate's memory?

Even if a graduate cannot recall a precise expression governing the current/voltage relationship for a semiconductor device, is it not reasonable to expect him to understand that it is a function of temperature, for example?

On the subject of final year projects, my experience was that students got involved in much too complex systems without any hope of fully understanding them in the limited time available! Whilst I am sure that Exeter students have written many good final year reports, does Mr Graham really believe that the result of a few weeks project work is to produce an "expert specialist"?

Turning to Mr Wehner's letter, I will ignore the first part as being totally irrelevant, and in any case, highly suspect. However, he goes on to make my point for me very well. He takes Mr Jaques to task for not drawing his (Mr Wehner's), "standard" amplifier circuit. One might quibble with the precision of Mr Jaques' "the gain between X and Z" but there is no ambiguity. Mr Wehner wants to define the gain referred to some point not even present in the circuit - why? Even if "input impedance" is not given its normal meaning, the circuit shown does have an infinite "source" impedance - so

why the complication?

Whilst I do not see any ambiguity in Mr Jaques' Figure 2, surely a graduate might be reasonably expected to spot and question any such ambiguity?

It is my own belief that extraordinary progress in electronics has led to the very thing that Mr Graham objects to: learning and examination by rote. Inadequate emphasis is given to understanding and applying fundamentals. This may not matter for certain systems "designers". However, one would hope that some of the electronics engineers we are educating might actually be capable of designing the "guts" of those fascinating multilegged black boxes we all love so dearly. New processes, new devices, new circuits, all require an understanding of, and an ability to use, the fundamentals of which Mr Graham is so scornful - or have we already left it to the Americans and the Japanese?

Whilst writing this letter, I asked my son (who graduated with first class honours in Electronics Engineering and Physics about five years ago), to read and comment on your contributor's article and letters as I thought it appropriate to obtain a perhaps more modern view than my own. (Although I do not actually qualify for Mr Graham's unnecessary reference to "Grandpa".) My son's reaction was not inconsistent with my own, but I feel inclined to give him the "last word". He recalled a comment he made to his examiners - "I could have done better if I had spent more time simply memorizing information rather than trying to understand it all . . . the examination questions all too often merely required the regurgitation of chunks of lecture notes . . . a computer programmed to do the same in response to a few key words, could have got a degree."

C. W. Ward,
Yelverton,
Devon


THE DEATH OF ELECTRIC CURRENT

After Dermond O'Reilly's second blistering attack, May 1982, perhaps Ivor Catt should slink away with his tail between his legs.

When discussing a TEM wave, it is common practice to use the formula O'Reilly objects to, $E/H = \sqrt{\mu/\epsilon}$. See for instance Bell, *Wireless World*, August 1979, page 44, and also A. F. Kip, "Electricity and Magnetism", page 332, equation 12.34. Kip uses the popular convention, where vectors are written in bold type and the amplitudes of vectors are written in faint type. In *Wireless World*, July 1979, page 73, the diagram immediately above my equation (a) that O'Reilly objects to makes it clear that amplitudes are being discussed.

Para. 3. Where is it said by anyone but O'Reilly that a wave is called transverse EM because displacement current flows across it? On the contrary, a wave is described as TEM because E (not dD/dt) and M are transverse. dD/dt has nothing to do with it, and will not even exist in the case of a steady TEM signal. O'Reilly makes this very point earlier in the same paragraph, that the bulk of a steady TEM wave contains no displacement current.

Following your publication in the December 1980 issue of my article 'Death of electric current', you published a letter by R. T. Lamb and my reply to his letter, both in the March 1981 issue. The following quotations from my reply show that I found Lamb's letter muddled;

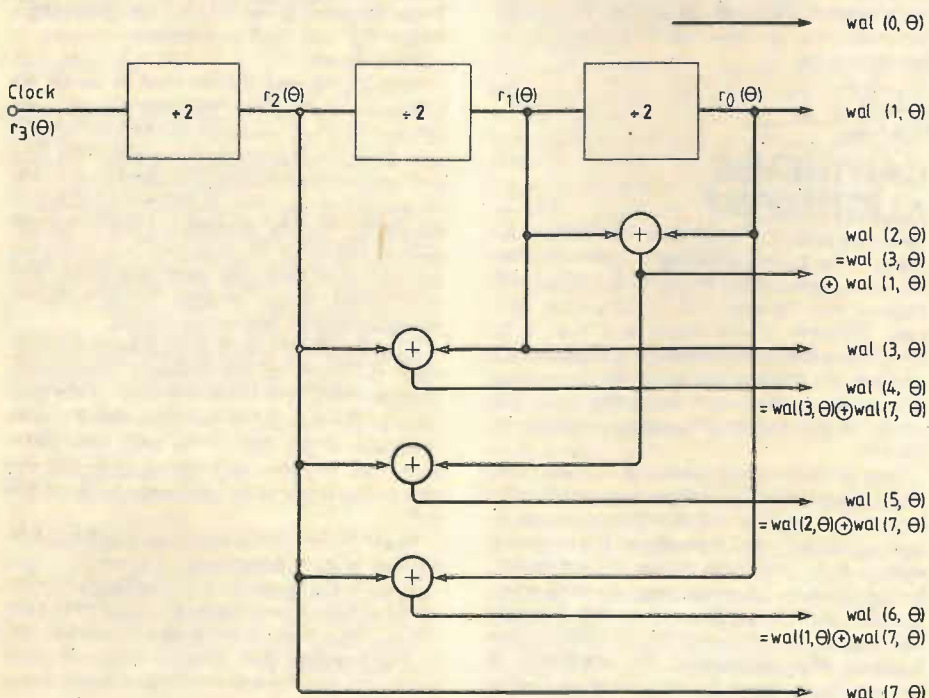

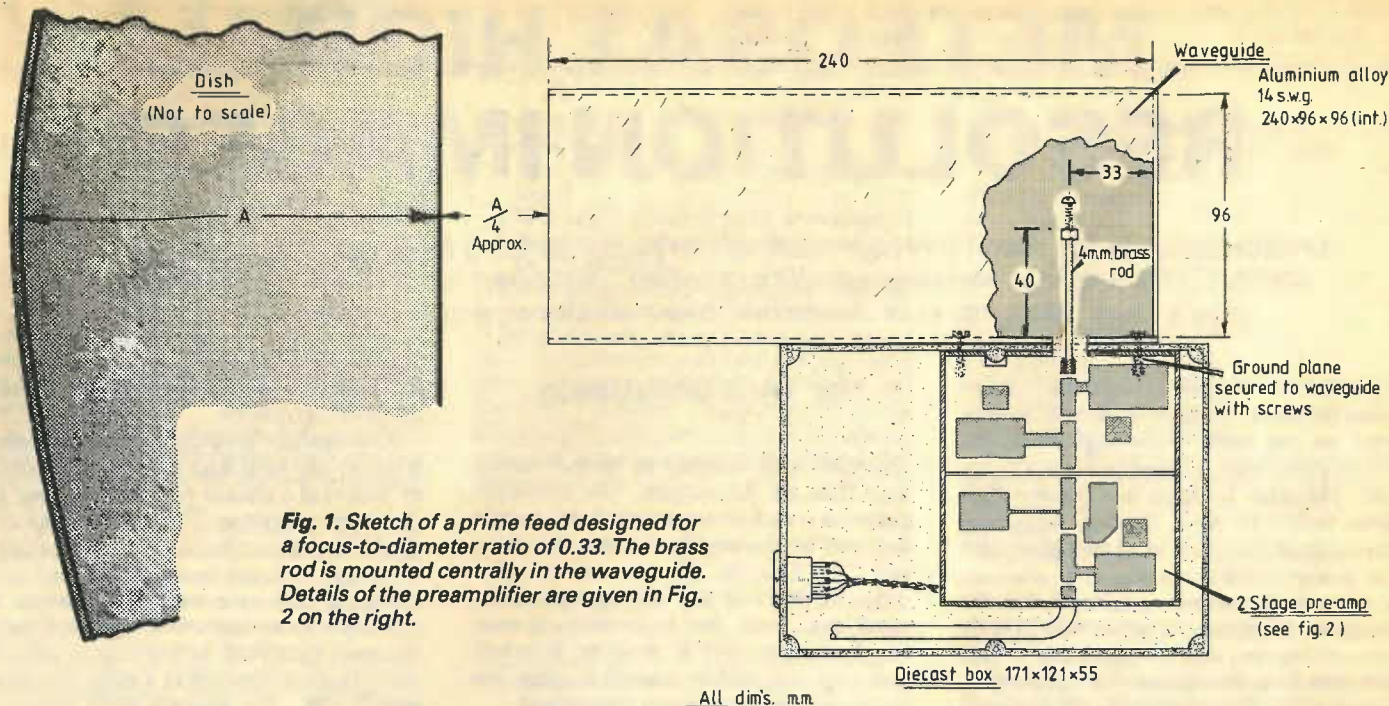


Fig. 1. Sketch of a prime feed designed for a focus-to-diameter ratio of 0.33. The brass rod is mounted centrally in the waveguide. Details of the preamplifier are given in Fig. 2 on the right.

All dims. mm.

the dish will depend on the focus-to-diameter ratio which determines the beam width that will fully illuminate the dish, but without spill-over. Figures 1 and 2 show a design which was optimized for a f/d ratio of 0.33. A smaller ratio presents an almost impossible design problem. A square section wave guide was used rather than a circular one because a slightly wider beam width can be obtained before the wave guide becomes too small to support wave transmission. If a dish with a larger f/d ratio were used a suitable circular section, sometimes known as a 'beer can feed' could be used. Construction of the pre-amplifier is identical to that used on the Tiros h.r.p.t. station except that the small receiving element is connected immediately before the first chip capacitor. The length of the element is adjusted, by means of the brass screw in the top, for optimum noise performance by pointing the waveguide, without the dish, in the general direction of Meteosat and adjusting it

using the s.d.u.s. transmissions. A usable but rather noisy facsimile picture could be obtained on the prototype.

The dish mounting may be rigid because the beam-width is not narrow enough for the satellite to move off beam during its daily movement of about two degrees. A reasonably unobstructed view of the sky must be available and the direction may be estimated from a nomograph or calculated.⁴ Once the signal has been acquired, final adjustment of direction, focus and polarization may be achieved.

Conversion to 10.7MHz is by the same converter system used for h.r.p.t. which was in turn based on one for Meteosat s.d.u.s. Careful adjustment of the interdigital filter is needed if it is required to pass h.r.p.t., as well as the Meteosat transmissions, without significant differences in performance on the four frequencies.

If the maximum benefit is to be gained from the lower bandwidth of the Meteosat transmission, the i.f. bandwidth should be

reduced to about 1MHz. The simplest way to do this is to remove the 2.2kΩ damping resistor across the tuned circuit in the mixer mosfet drain. The remainder of the wideband i.f. amplifier may be used without modification.

Phase demodulator

The method of modulation and the modulation index are identical to those used on the h.r.p.t. transmission and so the phase-locked loop demodulator may be used without change. The base bandwidth of the p.d.u.s. signal is considerably lower than the h.r.p.t., for which the post-detection filter was designed, and therefore a further filter must be added before the signal is applied to the p.d.u.s. decoder. This filter is placed after the existing filter output, in parallel with the existing connection to the h.r.p.t. decoder, and has a 3dB cut-off point of 280kHz, Fig. 3.

Data decoding

At this point in the system it is convenient to separate the p.d.u.s. chain from the h.r.p.t. system because the differences between the two become progressively more extensive. As before, the next step is to convert the s.p.l. data to n.r.z. and clock, in a manner that avoids most of the noise. The principle of s.p.l. decoding was covered before and the same definitions apply here. The h.r.p.t. system uses a digital integrator as a bit conditioner, and although this method could have been used again, because of the lower data rate a more conventional analogue implementation was used. Far simpler methods could be used to decode s.p.l., but it is well worth making the extra effort at this point because the decoder and front-end performance determines the overall error rate.

A complete circuit diagram of the decoder is shown in Fig. 4, and it operates as follows. Raw s.p.l. data is divided into two chains, one of which is clipped, and both positive and negative transitions used to regenerate the clock by pulsing a tuned

Table 3. The 24-word frame label broken down.

Word number	Meaning
1&2	Number of frames per subframes
3&4	Number of subframes in transmission
5&6	Current subframe number
7&8	Image line number (headers are zero)
9-12	Image number from mission start
13	Format indicator, A=00 B=FF (hex)
14	Vis 1 indicator } 00 = Data not present F0 = 1st half line present
15	Vis 2 indicator } 0F = 2nd half line present
16	IR indicator } 00 = Data not present
17	WV indicator } FF = Data present
18	Grid, 00 = No grid present
19	Reserved (00 on current operations)
20	Scan direction (normally 00 = S-N/E-W)
21-24	Spare (all zeros)

circuit at twice the data rate. Two c.m.o.s. phase-locked loop i.cs provide logic level clocks both in phase, and at 90° to the s.p.l. 'bits'. Two D-type flip flops generate clocks at data rate both in phase and at 90° to the incoming data. The two clock dividers can be initialized externally by the clock-error signal which goes high if a phase error is detected by the frame synchronizer. The clock signals are gated to produce the enable and reset pulses that operate the integrators and sampling circuits. At the end of each data bit the integrated values of both associated s.p.l. bits are held at the inputs of a comparator, the output of which is clocked into a further D-type flip flop. This forms the n.r.z. output. Both 180° and 90° clocks are used by the sync. detector. The waveforms marked on the circuit diagram are timed over a single data bit.

P.d.u.s.-frame format

Like the h.r.p.t. from Tiros the data stream is divided into blocks of words called frames. Each frame consists of 364, eight-bit words and the first three words of each frame are always the same; they form the synchronizing sequence. The transmission is structured as a number of sets of the frames, each set containing four frames in a B format and eight in an A format. These



One of eight registered primary data users, Mike Christieson, at his station. From left to right are colour-display electronics, computer-terminal and v.d.u. with colour monitor above it showing p.d.u.s. full-disc image, and the PDP9 mini-computer with four tape drives. The white panel below the tape drives is the satellite interface.

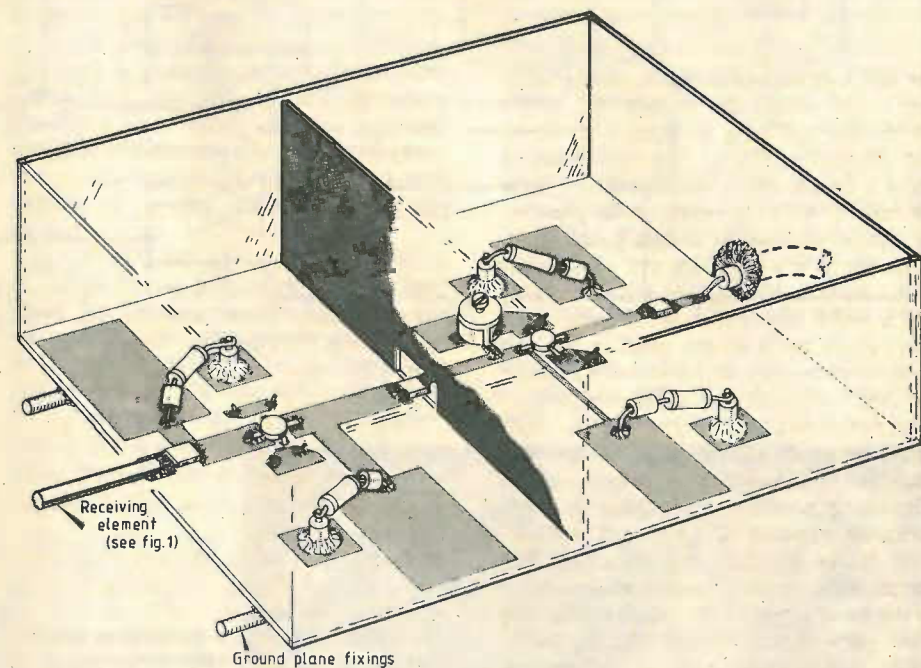


Fig. 2. Details of the two-stage preamplifier shown in Fig. 1. This is a slightly modified version of the one designed for receiving h.r.p.t. using the signal from NOAA-6, as described in the November 1981 issue of Wireless World.

Table 2. P.d.u.s. frame format. The first three words of each 364-word frame are always the same.

3 words	1 word	24 words	Spare		Data	
Sync.	Format ident	Frame number 0000	40 words in 'A'	8 words in 'B'		
Sync.	Format ident	0001	Data, radiance values sent m.s.b. first			
etc.	etc.	0010	Data			
1 Sub-frame All syncs. are 3 words 00000101 00001100 11011111	Most significant 4 bits 0111 = A format 0011 = B format	0011	Data 202 words	Further data in 'A' formats 158 words grid in 'B'		
		0100	Data (only exists in 'A' formats)			
		0101	Data Note: IR & WV have 8 bit resolution v.i.s. is 6 bit (to l.s.b.s filled by zeros)			
		0110	Data			
		0111	Data 44 words	Grid, 316 words (2500 grid bits plus 28 spare)		
4 words		360 words				

Background

The launch of Meteosat-2 on 19 June, 1981, began a new era of European space exploitation. It was the major part of the first active payload for Ariane, the European Space Agency's launch vehicle. After launch, the satellite was placed in a transfer orbit and then lifted into a near geosynchronous orbit by the apogee boost motor. On 20 June it was 86° W and drifting slowly eastwards at a rate of 2.8° per day. During the drift-phase, test transmissions were carried out and by the time it arrived on station on the morning of 21 July, most of the telecommunications system had been checked out. The first image scan in visible light was performed at 1030 GMT on 28 July, and in infrared on 30 July. The scheduled We-fax analogue service commenced on 17 August and the primary-data user station (p.d.u.s.) service on 15 September.

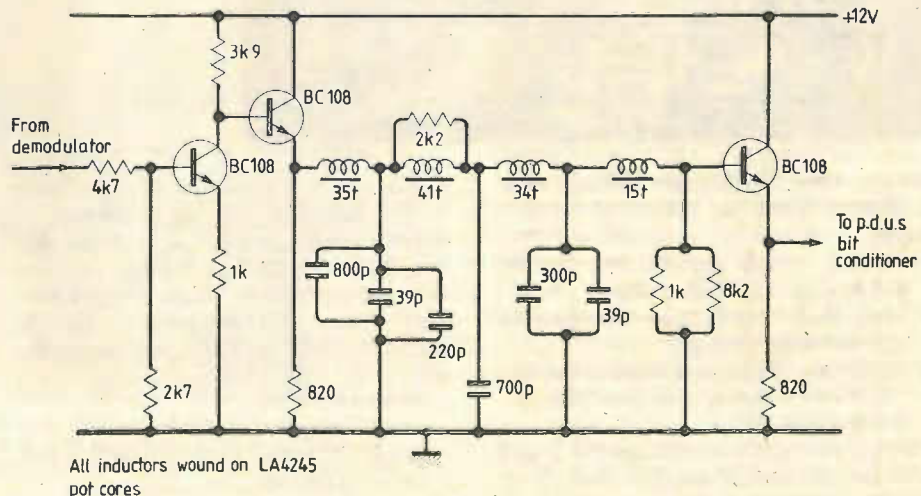


Fig. 3. Post-detection filter for p.d.u.s. with 3dB cut-off point of 280kHz.

Communications crisis

A pressure group, consisting members of companies and associations connected with the communications industry, has been set up to try and persuade the Government to speed up their liberalization of telecommunications. Many of the companies have invested money in anticipation of the liberalization and are now suffering financial hardship. The group calls itself the Communications Crisis Committee and its members include; Professor Lou Schnurr of the Chelmer Institute of Higher Education; The Mobile Radio Trade Association (MRTA); The Independent Telephone Supplies Association (ITSA); The Federation of Communications Services (FCS); The Mobile Radio Users' Association and the National Committee for the Legalization of Citizen's Band Radio (NATCOL-CIBAR).

They have put their opinions together into a document called the Report of the Communications Crisis Committee which consists of contributions from each of the corporate members of the Committee.

Professor Schnurr sets the scene by decrying the self-perpetuating monopoly of the present system. Even where free enterprise agreements exist, they are bound by licensing and technical approval procedures. A particular area for discontent is the allocations of the radio-frequency bands, especially the constraints on commercial development of the spec-

trum "controlled by an organization insensitive to market demand and without the philosophy of optimizing available spectral bandwidth for the purpose of services development. So long as such practices are contained within the moated walls of establishment privilege and internal decision making, the marriage of telephony and wireless cannot exist". This, he implies, impedes the whole of the diffusion of information technology throughout commerce.

Contributions from the other committee members also press for the liberalization of the use of British Telecom's network; to give access to mobile radio users, so that advanced data services for communication to mobile traffic. MRUA suggests that mobile services should have access to frequencies below 1,000MHz, frequencies above that being reserved for radio location and navigation. They also press for private network communications which would also have access to the public switched networks.

In a specific case study, Godfrey Wilson of Digital Paging Ltd bitterly complained about the inability to gain from BT the exchange facilities required for direct dial-in capability, available on his companies paging service. The unrealistic pricing of BT's radiopaging service; the "extortionate delays in obtaining services, and servicing from BT; excessive delays from the

Home Office in obtaining frequencies." Wilson feels it is unacceptable to be forced to compete with the body that issues the licences.

In conclusion, the committee puts forward several points for "direct, immediate action": Government departments should be asked to take steps to break the cycle of "time wasting tactics by BT and the Home Office Radio Regulatory Department; licensing powers should be transferred from BT to the Department of Industry; BT management to give fair and equitable access to BT competitors of the same facilities enjoyed by BT's own services and at the same price; require BT to set up self-accounting in all areas where there may be competition, ensuring public accountability. Pending the division of such areas, BT should suspend further commercial development; The Cabinet Office should take action to allocate some 60MHz of the radio frequency spectrum below 960MHz for private sector mobile radio services in conformity with the allocations of the 1979 WARC. There should be support and funding available to a private sector coordinating group. This would assist the administration and allocation of radio communications services, enabling medium-term commercial development of information technology and telecommunications services.

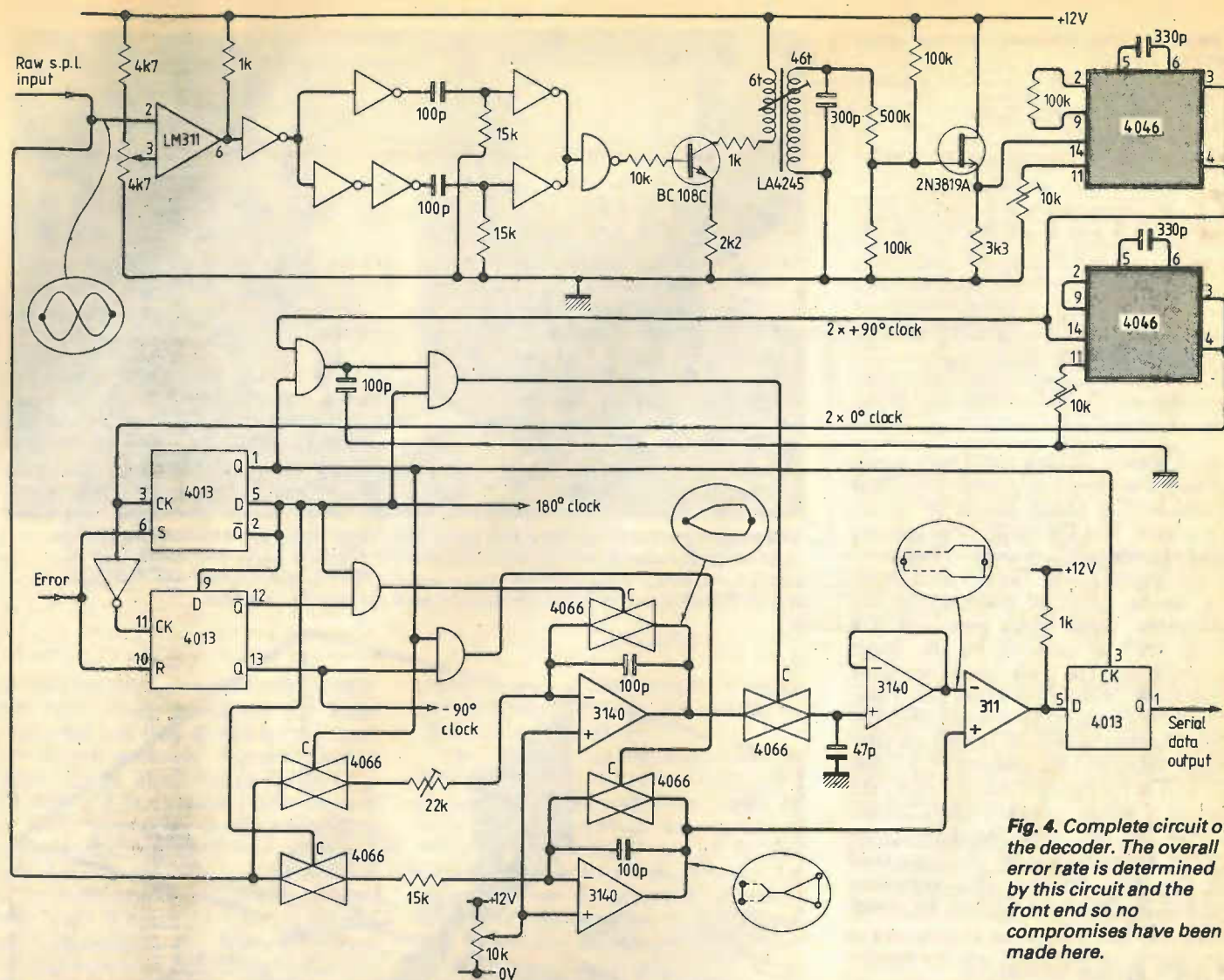


Fig. 4. Complete circuit of the decoder. The overall error rate is determined by this circuit and the front end so no compromises have been made here.

Note that when both visible channels are scheduled and only one channel is available, lines are duplicated.

All digital transmissions are preceded by a series of frames containing random data (with the label zero) to synchronise the receiver. The heading is then repeated 42 times in an A format and 84 times in a B format. Data then follows and the sequence is ended by one or two conclusion sub-frames. There is insufficient space here to describe fully the contents of the identification and the reader is referred to the ESA publications for this essential information.^{5, 6, 7, 8.}

References

- 1 High-resolution weather satellite pictures, M. L. Christieson, *Wireless World*, Nov., Dec. 1981, Jan. 1982
- 2 Meteosat earth station, M. L. Christieson, *Wireless World*, June, July 1979
- 3 Meteosat dissemination schedule, (published regularly) ESA.
- 4 *Meteosat dissemination news letter*, No 81/2, July 1981, ESA
- 5 Meteosat high-resolution image dissemination, ESA
- 6 Definition of h.r. format interpretation data, M. Jones, 79 06 11, ESA
- 7 Meteosat calibration reports, (published occasionally) ESA
- 8 Special response data for Meteosat-2, Meteosat systems guide annex B1, ESA

To be continued



A depression in the eastern Atlantic scanned by one of the satellite's two visible-light sensors

sets are rather confusingly referred to as subframes. There are three types of subframes

- heading, which contain identification and interpretation information
- data, which contain the image, and the grid-coastline bit map
- conclusion, which are similar to heading subframes but may contain updated information.

Table 2 shows the construction of a data subframe for both A and B formats. Each subframe has a 'label', consisting of 24

words, and its contents are shown in Table 3. The data from one line of infra-red or water vapour is sent in one subframe, but one line of visible data requires two consecutive subframes. When formats containing more than one image are sent the lines are interleaved in the following priority

- infra-red line one
- visible line one
- visible line two or water-vapour line one
- infra-red line two
- visible line three, etc.



Arthur C. Clarke, on the right, is receiving the Marconi Fellowship Award for 1982 from HRH Prince Claus of the Netherlands. Arthur Clarke was awarded the prize particularly for his pioneering ideas in the field of satellite communication. He originated proposals for the use of 'Extra-terrestrial relays', first published in an article in *Wireless World* in October 1945. Since then he has worked in similar proportions in both science fact and science fiction.

Old brain, new hat?

First announced as long as two years ago, the "hand-held" Newbrain personal computer emerged recently under the new parentage of Grundy Business Systems. Following Newbury Laboratories dropping of the project in 1980 - itself then only three years old - Bob Smith and colleagues left to seek new backing, ending up with a Grundy:BTG share arrangement of 70:30%. At the same time, the specification of the machine was improved so that Grundy now claim it is designed for "business, scientific and educational use as well as home computing". Now with its resident random-access memory increased to 32K (plug-in modules of 64, 128, 256 or 512 can take it to 2M) and 28K of read-only memory, it is designed to operate with a range of interchangeable and expandable program modules, or firmware. The hand-held claim is based on the built-in 16-character 14-segment vacuum fluorescent display together with optional one-hour battery module of the AD version, designed chiefly to occupy minimum desk space. But an MDB model with on-



board nickel-cadmium cells will allow display in its editing mode for four hours and preserve memory for 20 hours and should be available in six months time. The cheapest version, model A at £199 + vat, comes without this display but with tv and monitor ports instead, as well as dual cassette port, RS232/V24 printer and bidirectional ports. The screen display can provide, unusually, 40 or 80 characters per line and a resolution of 250 dots vertically by up to 640 dots, and may be mixed with a separately scrollable character-mode

display. The 512 character font includes viewdata mosaics, upper and lower case Greek letters, arc, and line drawing graphics, as well as the 96 ISO printing characters.

Firmware consists of interchangeable modules, communicating via hardware-independent interfaces, and may be expanded without interference with the hardware. The enhanced-ANSI Basic allows for user proofing of programs, direct interrupt handling, device-independent i/o, chaining and external calls. The

screen editor claims novelties for a microcomputer: backwards scrolling, multi-screen ability and direct cursor addressing. The operating system provides for peripheral device drivers to the processors — the cassette device involves a second processor which uses a learning algorithm to accommodate tape speed fluctuations. Additional rom slots are available in a buffer expansion module that accepts Z80 assembler, Comal structured Basic, statistics and text processing packages. The buffer module also has memory paging circuitry, parallel i/o ports, analogue ports, two multi-speed V24 ports, as well as rom space, which will be included on-board in the M models available later. Proprietary software packages may be used from cassette or *via* disc under control of the CP/M module, available September. A communications module, also available September, contains 32 V24 ports to give flexibility in sharing peripheral devices and connecting computers together. Unfortunately, a videotext module takes only low priority, and is planned for "some time next year".

Meeting Grundy's price targets meant adopting n.m.o.s. circuits instead of the more expensive c.m.o.s. types. Switch-off circuitry was incorporated to keep the circuits cool and power consumption within reasonable limits. "Other machines do have problems in this respect," says Grundy's Mike Wakefield, who is pleased to be able to claim a 0 to 45° C temperature range.

Welsh Dragon

The Dragon 32 computer is the first product of a new company, Dragon Data Ltd, a subsidiary of the toy manufacturers, Mettoy. Aimed at the first user, Dragon Data have concentrated their publicity in marketing a 'family home computer' where the children might use it for learning and games playing while the parents can compute family budgets, or index a collection.

The Dragon 32 is based on a Motorola 6809E which has an internal architecture so designed that it needs far fewer instructions to operate it than many other microprocessors and is very fast. It has a 16K rom with extended Microsoft colour Basic, which gives high-resolution graphics of up to 256 x 192 pixels: there is a modulated output to a domestic tv and there is also a monitor output. The basic computer includes a Centronics-type interface, so a 'professional' printer may be plugged in directly. The keyboard is similar to that used on DEC equipment and offers typewriter-style keys, guaranteed for 20 million key depressions. There is a 32K ram with the ability to expand to 64K. In addition there is a games cartridge slot with sockets for two joystick controls for the playing of games;



cartridges for the more popular amusement arcade games, space invaders, a 'Pacman'-type game and others, are available. Programmes may be stored on cassette tape. Dragon Data say that they have paid particular attention to the cassette interface so that the computer will work with a wide range of cassette recorders.

Some software on cassette is already available, particularly the Dragon Special Selection tapes which are games programs which explain how they work and so give some insight into their programming.

Especially useful for educational programs is the ability to switch sound from a cassette player through to the tv sound. Program and a sound commentary can be included on the same cassette. A language lesson could show the words on the screen while they are spoken through the speaker. The Dragon can also generate sound with five octaves of musical notes with selectable duration and volume. This too comes out through the tv speaker.

Future expansions and developments include a disc operating system, an RS232 port, a second microprocessor and an operating system together with Prestel and

Banking on video

Barclays Bank has found that the best way to keep their staff informed is through video programmes, shown on tv sets at the place of work. They have invested in a £1M recording studio and insist that their programmes should be of the highest quality both in content and presentation. So they have hired tv producers and popular tv performers to make the programmes look as much like the programmes the staff might watch at home, as possible. Such subjects as 'How to spot fraudulent use of Barclaycard' or the implications to the staff on the opening of the banks to the public on Saturday mornings, have been produced and are examples of the training and information functions. In order to generate enough copies of the video films for distribution, Barclays have a computer-controlled copying suite with quality monitoring also controlled by computer.

The next phase of the video network is to extend it to 2,300 outlets. Barclays have awarded a £3.5M contract to Soundcraft Network Video to install 700 additional Type 5 Sony U-Matic video cassette recorders and 1,900 Trinitron monitors, and to maintain the whole system.

Mike Pogson, the managing director of Soundcraft, told us that his company had made considerable investment in providing servicing back-up for such a system. He described the lack of fully-trained broadcast engineers who were necessary to diagnose as well as rectify any faults in the field. He saw the role of his company as removing all the technical problems from

teletext facilities. Other operating languages can be added, including Pascal, 'C' and Basic compilers.

Program cassettes and cartridges are planned for a wide range of applications. The Dragon is all British, designed by Dragon Data with the co-operation of the PATs Centre, and Motorola, whose chips, manufactured in Scotland are used in the computer.

Comparisons are always difficult but the nearest competitor to the Dragon is the Sinclair ZX Spectrum. The Dragon 32 has more memory and a particular advantage in having a 'professional' keyboard. The Centronics interface is also a big advantage. The Sinclair has more colours available at high resolution and the big (so far theoretical) advantage of the Microdrive; the miniature, low cost disc memory. However, there is a big difference in 'feel' with the ZX Spectrum feeling like a toy computer and the Dragon and its keyboard with the touch of a 'real' computer.

The Dragon 32 is in production at the Mettoy factory in Swansea, it will be on sale in the High Street early in August for just under £200.

the client's shoulders so that they can 'get on with producing and distributing the programmes'.

The Soundcraft deal is claimed to be the biggest contract by a corporate organization in Europe.

New technology and the graduate

The Department of Education and Science has approved the co-operation between the Science and Engineering Research Council and the Open University for a series of programmes of 'technological topping-up' courses. It is intended to provide a re-education for those graduates who have been working in industry for periods of 5 to 15 years. The SERC became aware of a need for such courses and have commissioned the OU to produce them.

The courses will use the OU's techniques for home study with tutorial support and study centre facilities for practical work. Two areas in particular have been identified for priority treatment, which are computer applications (including real-time monitoring and control systems), and manufacturing.

The computer applications course is expected to consist of a 'foundation' module on software engineering, computer systems architecture, and operating systems. This would be followed by a number of 'core' modules on monitoring systems, systems modelling, control systems and project management. There would also be optional modules on robotics, man/machine interactions, and computer-aided design. The full course will be

the equivalent of one year's full time study. Certificates would be awarded for each module of the course and a diploma for the successful completion of the whole course. Students may then be able to undertake a further project in a related area which would lead to an M.Sc.-level qualification.

Telecom showcase

British Telecom's new exhibition centre is not a museum, stressed Peter Benton, the Deputy Chairman of BT, although it does trace the history of telecommunications from the early days of telegraphy. The centre's full title is Telecom Technology Showcase and in addition to the historical aspect which is well covered with many working examples of, for example, a Strowger telephone exchange of 1940s vintage, there is an exhibition of BT's latest equipment and techniques. Currently these include many digital techniques, displays about optical fibres and satellite telecommunications with examples of some of the latest equipment. It is planned to change the displays regularly to keep them up-to-date.

The Showcase is situated in Queen Victoria Street, London, in part of BT's Baynard House and is next door to the Mermaid Theatre. Lord Miles, formerly Sir Bernard Miles, officially opened the showcase and pointed out the role that the Mermaid's Molecule Club had played in educating young people in science and technology. He hoped that the Showcase would also contribute towards the edification of the young. He also looked forward to the micro revolution which he felt would release us from the 'work ethic' and allow us to get on with living, without the encumbrance of work.

Projects Editor

Wireless World needs a Projects Editor, who will be responsible for running the laboratory.

The work consists of design and development of equipment subsequently to be described in *Wireless World*, commissioning articles on construction and testing pieces of commercial equipment.

The successful applicant will be experienced in both analogue and digital techniques and will be able to express himself clearly in writing.

If the post appeals to you, please write to the Editor, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS or telephone 01-661 3128.

CIRCUIT IDEAS


Extended addressing for the Z80

Current 40-pin memory-mapping i.cs are expensive and difficult to obtain. As this circuit shows, it is possible to extend the addressing capability of a Z80 to more than 16 bits using readily available 74S189, 64-bit t.t.l. rams.

The microprocessor's four most significant address lines are not used for memory access, but instead address one of 16 stores of eight or 12 bits which are used as most significant address lines; in essence the same function as carried out by dedicated memory-mapping i.cs.

Each store is loaded using an OUT(C),r instruction which, with the Z80, results in the contents of the B register being placed on the upper half of the address bus. To load a particular store, the program has to put the eight address bits into the A (or D, E, H or L) register, the store addressing the top four bits of B, then load C with the i/o address of the mapping circuit and issue an OUT(C),A (or D, E, H or L) instruction. If 12 address bits are to be generated, the top four bits must also be placed in the bottom four positions of B.

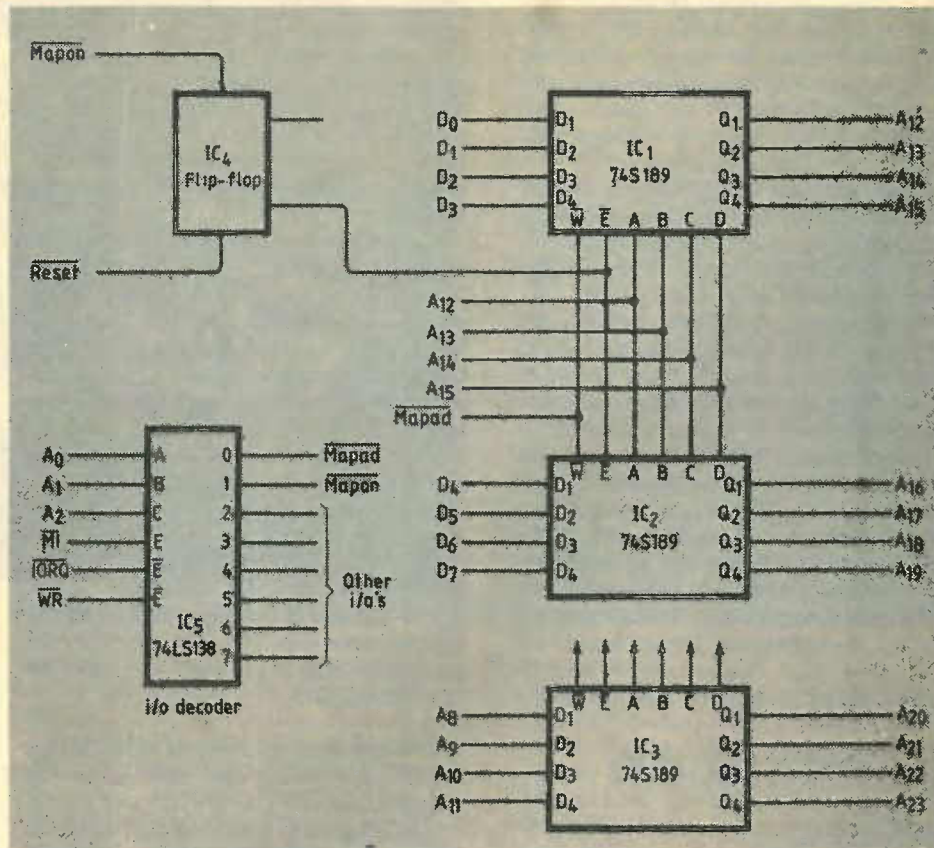Sixteen different stores are used so that various parts of the program can be allocated one or several locations, allowing each store to work on its own ram. For example, interrupt routines may be run without upsetting background pointers.



Initially, bistable IC₄ disables the stores, whose outputs are held high by resistors until a switch-on signal is generated using a spare i/o line. This gives a fixed value on

start up while the initializing program loads the 16 stores.
Brian Dillon
Dublin

Low-current voltage regulator

Standby consumption and output rating of this low-power regulator are 50µA and greater than 10mA respectively. Current limiting is included, brought about by gate-to-source voltage starvation in the 4007, and the output is short-circuit proof. Components used are cheap and readily available.

With the components shown, the output voltage is 12.78V, given by

$$V_{out} \approx V_{BR}(Tr1) + V_R$$


where $V_R = V_S - V_T$ and $V_T \approx 1.5V$. And

$$V_{RA} = V_F(D1) + V_{BR}(Tr1) - V_T$$

such that $V_{out} = V_{RA} + V_{RB}$. In this case, assuming a typical BC109 breakdown voltage of 8.2V for $Tr1$, a forward voltage for $D1$ of 0.4V and a threshold voltage of 1.5V, $V_{RA} = 7.1$ and $V_{RB} = 5.68$. Therefore $V_{out} = V_{RA} + V_{RB}$.

With a maximum input voltage of 20V, with V_R at around 4V, the c.m.o.s. device will be operating at around 16V which is inside its rating.


D. Roffey
Bromley

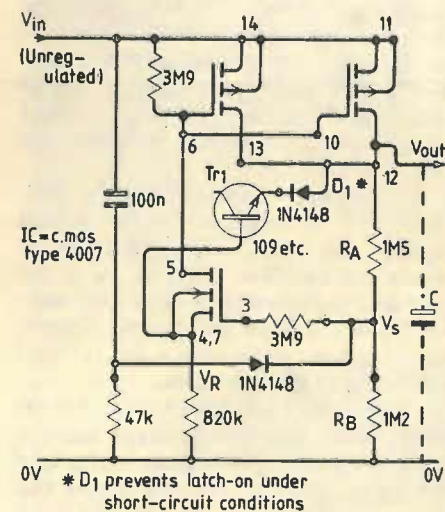


Programmable frequency divider

The 74163 4-bit binary counter may be used to divide the clock frequency by N, where $2 \leq N \leq 16$, by applying binary (16-N) to the data inputs and connecting the load input to the inverted carry output.

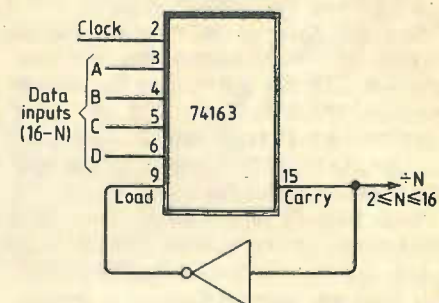N. H. Sabah
American University of Beirut



WIRELESS WORLD AUGUST 1982

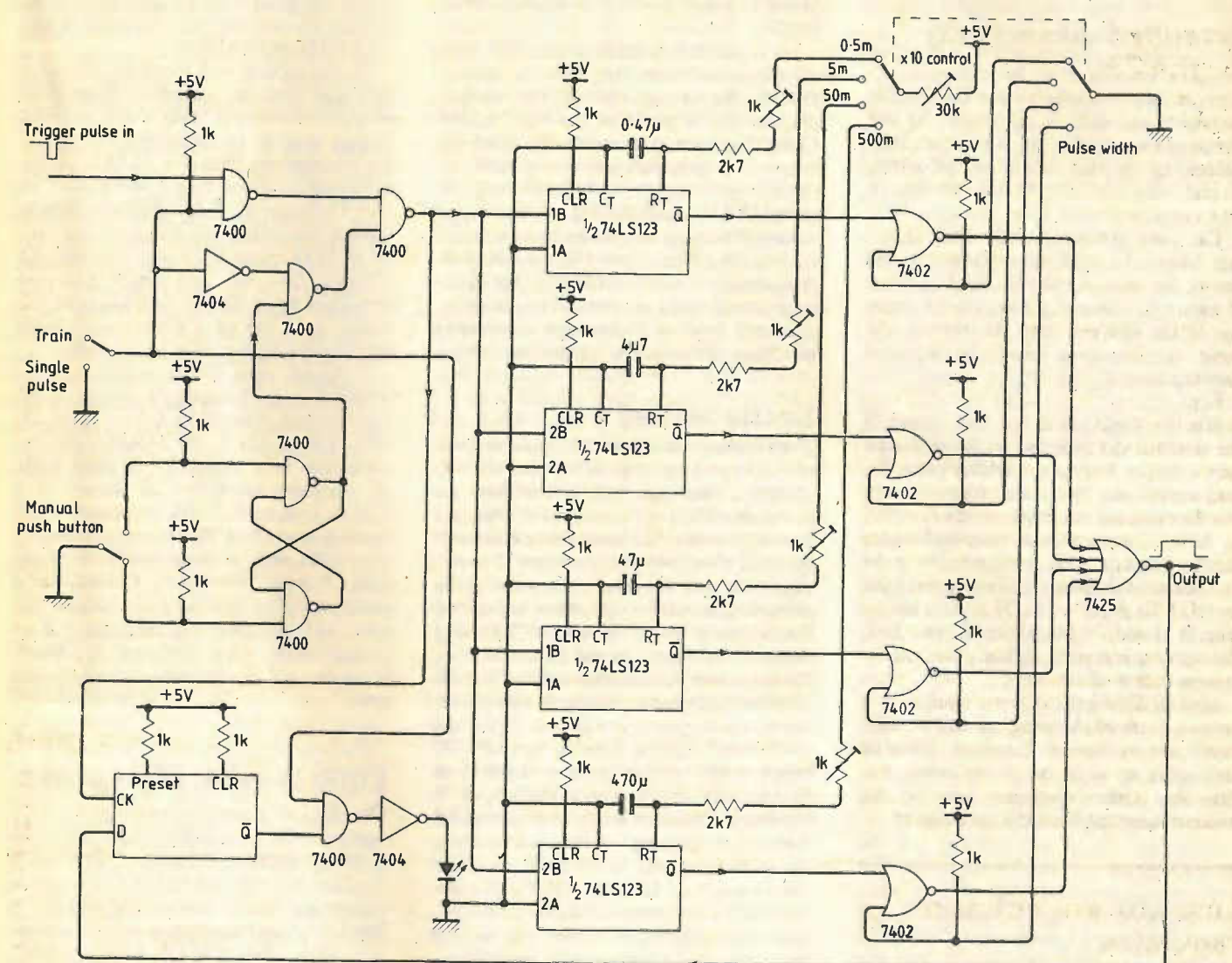

Pulse-generation using t.t.l.

Variable-pulse control using t.t.l. i.cs is not unusual, but most circuits use non-retriggerable monostables since they are less prone to false triggering from noisy supply lines and stray signals. However, when a 100% duty cycle is reached, output jitter occurs and above 100%, the pulse repetition frequency is reduced.

This circuit uses separate retriggerable monostables and is not prone to false triggering. Jittering near the 100% duty cycle does not occur and at and above 100%, an l.e.d. lights and the output becomes static. Further stages may be added.

A. R. Millichope
Birmingham


WIRELESS WORLD AUGUST 1982

Window discriminator

Two op-amps and numerous close-tolerance resistors used in conventional window discriminators are replaced by this circuit at the expense of convenient adjustment.

Designed to lift the pen of an X-Y recorder when the Y input exceeded the range 0.5 to 4.5V, the circuit uses the 555's control-voltage input to trim the trigger level. A potential divider was used at the input to change the voltage range to between 0.4 and 3.6V. Predictable operation is ensured by tying the threshold input to the positive rail and if a t.t.l. output is required, the open-collector output, pin 7, can be used in the conventional manner.

R. M. Jones
County Durham

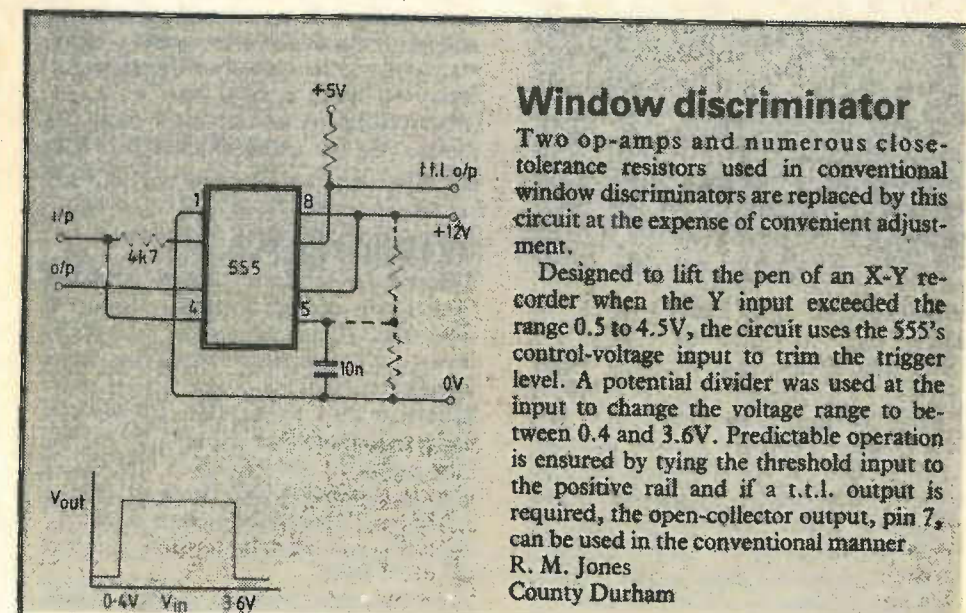

NETWORK ANALYSIS WITH A ZX81

Extensive insertion loss and group delay computations of ladder filters are faster with an inexpensive microcomputer than with a programmable calculator

The specification of the ZX81 reveals that it is also potentially a 'super-calculator' capable of handling much more extensive programs at a far higher computing speed than, for example, the Texas TI59. The 9½-digit accuracy is admittedly less but nevertheless perfectly adequate for a wide range of practical problems. The program described was written not only to fulfil a professional requirement, but also to test the capabilities of the ZX81 fitted with the 16K ram.

The menu it provides is as follows.

- Compute and display the insertion loss and group delay of a passive ladder network with up to 10 branches, excluding the terminations. For a frequency base in MHz the group delay is computed over an increment of 1kHz.
- Each branch can consist of a single inductor or capacitor, or a series or parallel tuned circuit. More complex structures can be handled by means of a simple device.
- A chosen value of dissipation can be assigned to the components.
- Component values entered can be listed and corrections made before computation starts.
- At the end of a calculation, individual frequencies and element values can be modified without re-starting the program from the beginning. This is invaluable for estimating the effect of component tolerances or for 'zooming in' on any particular area of the network response.
- Up to five group-delay equalizer sections can be added and the total resultant delay displayed. The display is in the form of the zero-frequency delay, followed by the differences from that value at the other points.
- Because the group delay values of the network are held in an auxiliary array, re-computation of the group-delay response after changes to the equalizer parameters is fast.
- Added loss due to dissipation in the equalizer can be displayed.

To give an idea of the running time, the ZX81 in the fast mode displays the insertion loss and group delay of a seventh-order elliptic-function filter at 15 points in around 75 seconds. Each successive attempt at group-delay equalization takes around 12 seconds, not including the time taken to enter values.

Because many users will not need the

by L. E. Weaver

group-delay equalization routine, the procedure for use is conveniently divided into two portions.

Computation of network response

First some general remarks. As I am principally concerned with video filters, the units chosen are Ω , μF , μH , MHz and μs . These can be replaced by any other self-consistent set, but obviously minor changes to the print statements will be needed.

It is assumed that the network is unbalanced and contains no bridged-T sections. The group-delay equalizers are dealt with quite differently. The branches are numbered from the input to the output, and the component values are entered in the same order so that for example, the fourth branch will contain L(4) and C(4), or perhaps L(4) or C(4) alone. As shunt and series branches alternate in a ladder network it is only necessary to specify the nature of one of these. This is chosen to be the branch facing the input termination.

The dissipation is expressed by D, which is the reciprocal of the Q factor, and must be specified at some frequency. This will often be the cut-off frequency or possibly one of the points of nominally infinite rejection. Because of the simplification in the expressions for the impedances, the standard device is employed of assuming that both the inductors and capacitors have the same dissipation, and that in a resonant circuit D is the sum of these. However, experience shows that provided D is less than about 0.02 ($Q > 50$) the individual dissipations do not need to be equal. It follows that if the capacitors can be considered as dissipationless, D can be taken as one half of the value which would otherwise apply. This may not sound very satisfactory but in practice it works surprisingly well.

With such a long program and only 16K of storage the display prompts necessarily have to be kept very short, so it seems desirable to set out the procedure in detail. Each input will, of course, be followed by NEW LINE.

Prompts	Inputs
FO?	Starting frequency
FM?	Maximum frequency
DF?	Frequency step
D?	Dissipation constant
FD?	Dissipation frequency (if

D=0 then a nominal positive value must be entered)

RI?	Input termination
RO?	Output termination
NO. OF BRANCHES?	Total excluding terminations
L+C? N=1	YES for a resonant circuit, NO for a single resistor or capacitor
SER OR PAR?	When previous input was YES, input SER for a series and PAR for a parallel resonant circuit
L? N=1	Enter L(1)
C?	Enter C(1). If only one L or C the other must be entered as zero



L. E. Weaver, B.Sc., M.I.E.E. is the author of three well-known works on television measurements, and of a number of monographs and papers both on that subject and on aspects of network design. Now a television engineering consultant, he was previously head of the measurements laboratory in the BBC designs department. While in that position he also used the experience previously gained in network design at STCs transmission laboratory to produce high-quality video filters, some of which have been commercially manufactured on a considerable scale.

This process will continue until the last branch has been entered. Then

SHUNT IN? YES for a shunt input, NO for a series
9/695 GOTO CHECK. This will then list the entered values. Modify by, for example, LET L (4) = 5.25. Do not enter RUN or CONT. When satisfied enter GOTO LOSS, which starts computation. After completion values can be modified and the network re-calculated by again using GOTO LOSS.

Group delay equalization

The insertion loss of a filter is usually required over a frequency range wide enough to cover both the pass and stop bands, but with delay equalization the situation is totally different. As a rough guide the important area in that instance lies between zero frequency and the 6dB point for a lowpass network, and between the 6dB points for a bandpass. It follows that a new set of frequencies must be selected up to the allowable total of 15, achieved by entries such as LET FM = 6 and LET FD = 0.5. The initial computation is then repeated by means of GOTO LOSS, which takes very little time as the component values do not have to be re-entered. The read-out must be completed, indicated by a 9 code.

The program allows for one first-order equalizer section followed by up to four second-order. Alternatively, up to five second-order sections may be used. Each is defined by a resonant frequency and a shape factor K, which must be made zero for the first-order section. The first-order section, if present, must be entered before the others.


The procedure is then as follows.

Prompts	Inputs
9/1590	CONT
V?	Total number of sections
FR? M=1	Resonant frequency of first section
K?	K-parameter of first section
FR? M=2	Resonant frequency of second section
K?	K for second section

As soon as the parameters for M=V have been entered the computation starts.

The initial attempt is not likely to be successful, so it will then be necessary to modify the equalizer parameters by inputs of the form LET F(2) = 2.2 and LET K(3) = 1.2. This must be followed by GOTO EQU, which repeats the calculation with the new values.

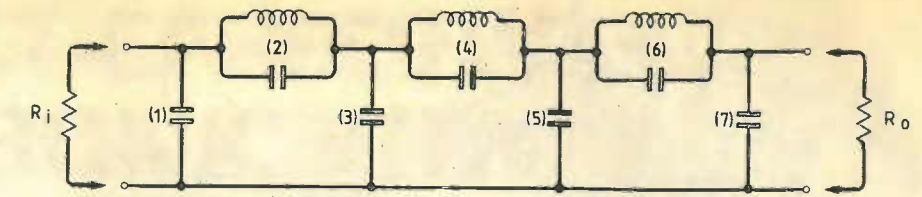At the end of the equalization process, GOTO DISS will provide a read-out of the equalizer dissipation corresponding to the value of D. This does not need to be the same as the D used for the insertion loss but may be re-entered before calling up the DISS routine.



Loss section								UNITS: Ω , μH , μF , MHz
$R_i=R_o=75$								
N	1	2	3	4	5	6	7	
L	0	1.58	0	3.09	0	1.67	0	
C	315.5 E-6	53.8 E-6	655 E-6	150 E-6	564 E-6	379 E-6	126 E-6	
Group delay equalizer								
M	1	2	3					
FR	2.0	3.0	4.5					
K	0	1.3	0.7					

Fig. 1. Component values of a 5MHz elliptic function lowpass filter in the form recommended for program entry. Suggested initial parameter values are included for a three-section group delay equalizer.

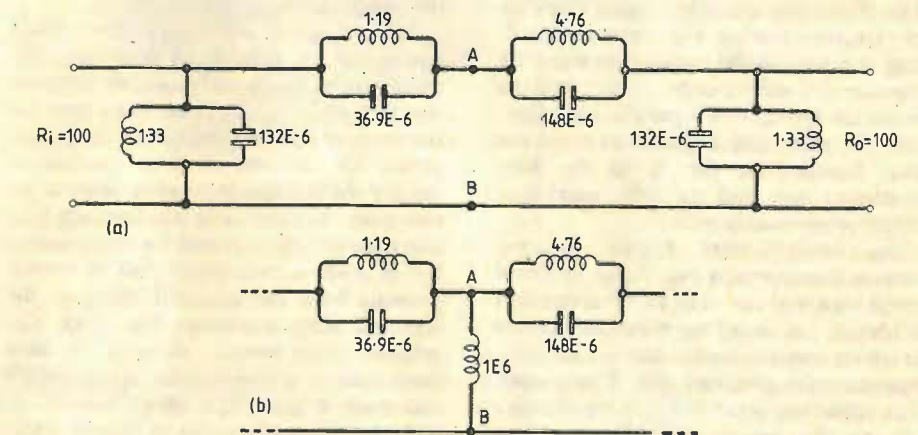


Fig. 2. Use of a dummy shunt branch where a series arm contains more than two components. Values shown are for a 10MHz bandpass filter with midband frequency 12MHz and rejection points at 6 and 24MHz. Original configuration at (a), dummy shunt branch inserted at (b).

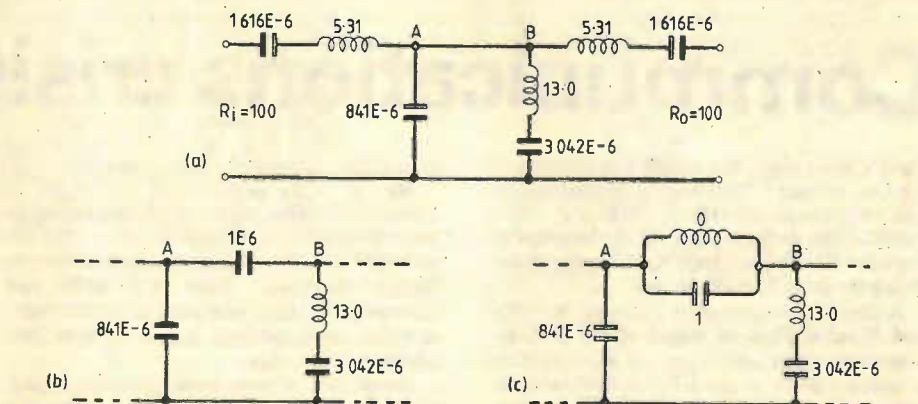


Fig. 3. Use of a dummy series branch where a shunt arm contains more than two components. Values shown correspond to a 3MHz bandpass filter with midband frequency 2MHz and a single rejection point at 0.8MHz. Original configuration at (a), dummy series branch suitable for bandpass structures only (b) and universally applicable dummy series branch (c).

In the absence of enough ram to run an optimization program, a graphical method has been found effective. This consists in plotting the combined group delay responses for successive parameter changes from some initial set of values, taking care not to try to deal with too many simultaneous changes. Some of these will inevitably be in the wrong direction, but one

quickly gets a feel for the way in which moves have to be made. Remember that the aim must be to minimize the absolute error, that is the positive and negative deviations must tend to equality, subject to the condition with video filters that the error may be allowed to increase with frequency. The display provides the deviations directly, which saves a great deal of

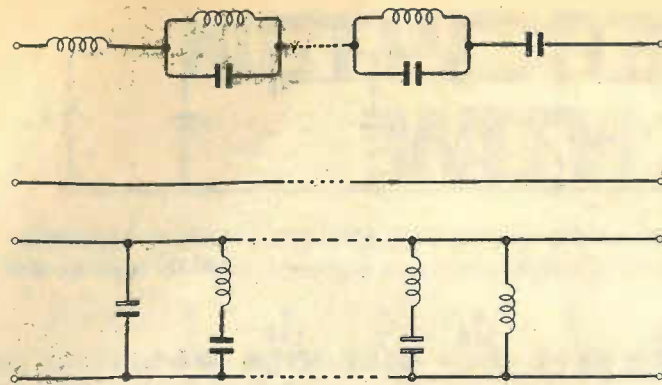


Fig. 4. Pair of canonical two-terminal reactance arms.

tedious plotting especially in the earlier stages of the process, since it is simple to note the maxima and minima at each stage without drawing the complete curve.

A brief guide to the shape of the delay equalizer responses may be found useful. The first-order network provides a group delay which falls steadily starting from the zero-frequency value. On the other hand, there is a very useful analogy between the response of a second-order section and the amplitude response of a parallel tuned circuit. The parameter K performs much the same function as the Q in the last-mentioned case, and the delay maximum roughly corresponds with FR .

The seventh-order elliptic function lowpass filter given in Fig. 1 may be found useful for a trial run. The loss is about 4dB at 5MHz. The delay equalizer parameters do not represent an optimum, but merely a suggestion for an initial trial. The component values are listed in the order of insertion into the program, with the capacitors provided in exponential notation, thus avoiding strings of zeros.

Before leaving the subject of insertion loss calculation, one still has to deal with the problem of network branches containing more than two reactances such as may be encountered in bandpass filters. In fact it can be very easily solved by the use of dummy branches as the following examples will make clear.

Fig. 2(a) shows a bandpass filter with a bandwidth of 10MHz, a mid-band frequency of 12MHz, and rejection frequencies at 8 and 24MHz. The series arm has the form of two parallel tuned circuits in series, i.e. a total of four reactances, usually the maximum number likely to be met with. The device in this instance is to add between points A and B a shunt inductor of such a magnitude that it cannot possibly have any practical effect on the loss and delay responses, Fig. 2(b). The original three-branch network is now converted to a five-branch ladder which can easily be handled by the program.

A shunt branch yields to similar treatment, as is illustrated by the bandpass filter of Fig. 3(a). This has a bandwidth of

3MHz with a mid-band frequency of 2MHz and a rejection frequency at 0.8MHz. Because it has a bandpass characteristic it is possible to employ the analogue of Fig. 2(b), that is the series insertion of a very large capacitor, Fig. 3(b). The resulting five-branch ladder can now be treated normally. In this instance, there is an alternative which applies equally to lowpass structures, that is the insertion of a parallel tuned circuit with a zero-valued inductor and a capacitor of any nominal size, Fig. 3(c).

It is worth stressing that the dummy branch technique can always be applied, subject to the limitation of a total of ten branches imposed by the present program. The justification for this is the theorem that a two-terminal reactance arm can always be transformed into one of the two configurations of Fig. 4 (ref. 1), for which reason they are sometimes called canonical networks. Of course, not all of the inductors and capacitors have to be present, so the two examples given above are obviously included. It will sometimes involve the transformation of one configuration into another, but this is comparatively simple provided a reference table of equivalent circuits is available².

References

1. R. M. Foster, Reactance theorem. *Bell System Technical Journal*, vol. 3, April 1924, pp. 259-67.
2. A. Zverev and H. Blinichikoff, Network transformations for wave filter design. *Electronics*, June 26 1959, pp. 52-4.

To be continued.

Communications crisis—a reply

On our news pages this month is a criticism of the Government's liberalisation programme for the telecommunications industry. John Butcher, the Parliamentary Under Secretary of State for Industry has made the following reply, listing the progress made to date.

A licence was granted in February to Cable and Wireless PLC on behalf of the Mercury Communications Limited to run a telecommunications system in the UK the first independent system of its kind outside North America. By the middle of next year the first subscribers should be connected to Mercury, surely an astonishing achievement in the time.

On the liberalisation of attachments progress has been remarkable. Already some 50 attachments, including about 25 telephones, 20 modems and five telex teleprinters can be supplied competitively which under the old regime would either have been completely unavailable or supplied only through BT.

November 1981 - Interim approved scheme for extension telephones from BT's special range. The latter have been added to since then and all of BT's special range telephones can now be supplied in competition with BT. The first approvals under this interim scheme have now

been made and more will follow shortly.

May 27 - An extension of this scheme to include callmakers, repertory diallers and apparatus incorporating integral modems. The Department is now considering applications for further evaluation. Now that BSI's new laboratory can undertake some of the test work, it should be possible to deal with more telephones more quickly.

March 31 - Orders made requiring apparatus to be marked to tell customers whether or not it is approved for connection to BT's networks. This is vital information for users if they are to choose apparatus that will not cause damage and produce inferior service.

Six draft standards have been written and made available for public comment in record time and further drafts will follow shortly. So far all standards are meeting their target dates.

May - The British Approvals Board for Telecommunications (BABT) was incorporated and will begin to accept applications for approval when the first standards are published.

The Department and BT have agreed on arrangements allowing BT's present suppliers of telex teleprinters to supply the models they now sell to BT direct to customers. This makes five

models available competitively if the manufacturers wish to take advantage of this arrangement.

"The Government has a duty" he continued "to make sure that apparatus connected to BT's network does not endanger consumers who use this equipment or BT's engineers and does not impair the quality of service that the network is able to provide to all. Much of the preparations that have been made over the past 12 to 18 months have been aimed at avoiding such dangers.

"In many cases little of this progress is visible to the outside observer but all of it is necessary if liberalisation is to be fair and to work. Critics do not do justice to the immense amount that has already been achieved."

"Since April private operators have been able to apply to the Department of Industry for a licence to provide services over the network. The provision of these value added network services (VANS) will help to satisfy the demand more quickly than at present and encourage the growth of a wider range of services, providing jobs and helping business in Britain to become more competitive.

COST-EFFECTIVE ELECTRONIC IGNITION

The popularity of Rod Cooper's ignition circuit design, published in the March issue, led to many requests for a component location diagram. In response, here is a component layout - regrettably held out of the last issue - designed to complement the board pattern originally given. A resistor and decoupling capacitors were omitted from the published circuit, so a corrected version is reproduced herewith, which now corresponds with the board design.

Printed boards to an alternative layout, with components horizontally arranged, is available from M. R. Sagin (see advertisement), who may also be able to supply wound transformers and discharge capacitors. Ferrite and bobbins are also available from Mullard stockists.

The graphs showing the relation between combustion efficiency and spark were originally published in an article entitled Ignition Design Trends by K. Garrett, in *Automotive Engineering*, April-May 1977. Oscilloscope traces were produced from equipment kindly loaned by Hewlett Packard.



Components for ignition circuit

Resistors

1	180
2	10k
3	180
4	33M
5	270
6	180
7	4.7k
8	2.2k
9	27k
10	2.2k
11	22k
12	1.2k
13	1.2k
14	330

Transistors


1	TIP3055,MJE3055
2	BFY52
3	2N3903
4	2N3903
5	TIP2955,MJE2955
6	BFY52

Capacitors

1	470n 1kV polypropylene (RS)
2	10n
3	1n 1kV polypropylene
4	470p
5	5n polyester
6	5n polyester
7,8	100 to 500µ10V electrolytic

Diodes

1	1N4001
2	1N4007
3	1N4007
4	1N4001
5	1N4148
6	1N4001
7	1N5402 or similar 3A rec.
Zeners 4.7 and 10V 400mW	

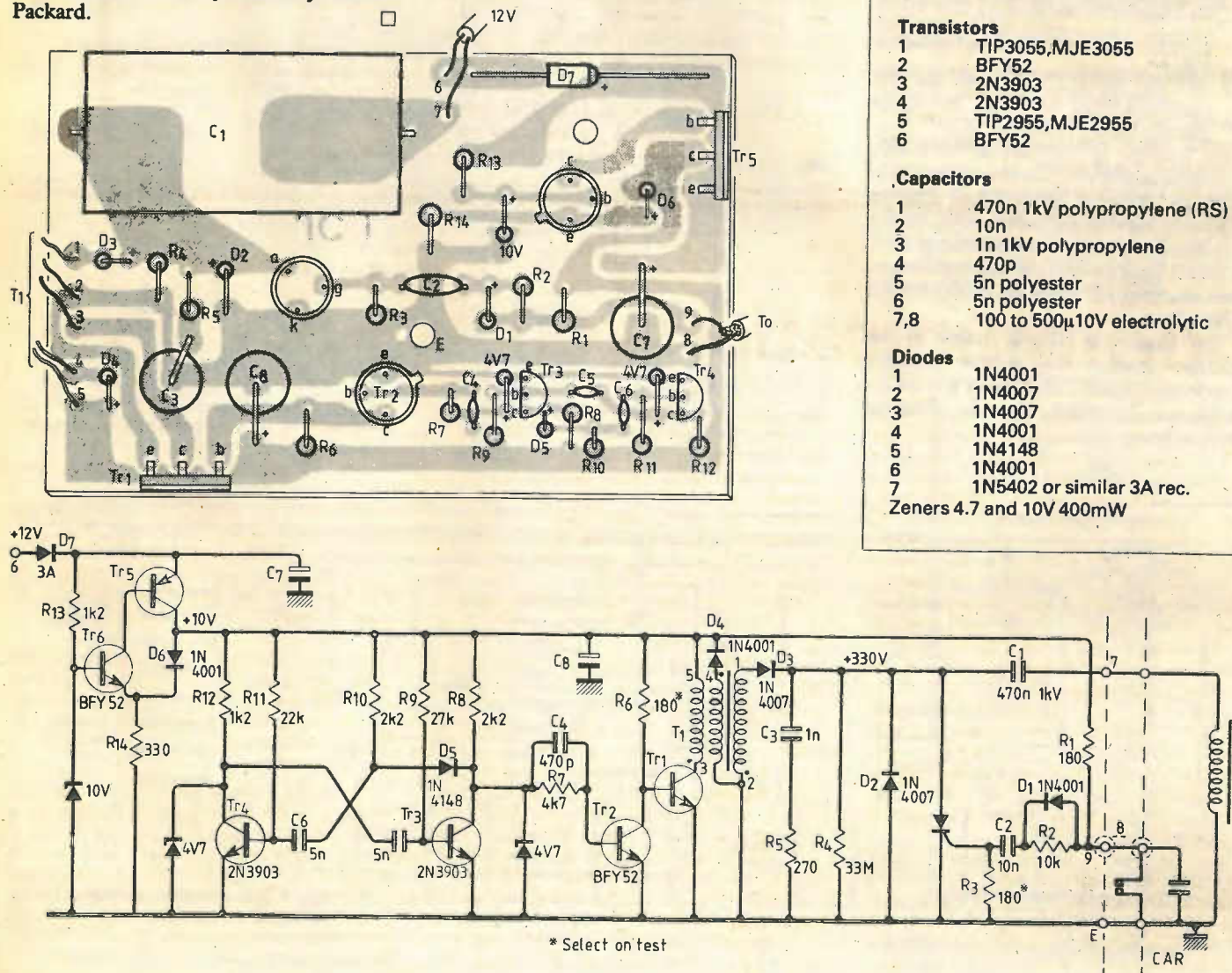

DESIGNING WITH MICROPROCESSORS

Step-by-step procedures for implementing microprocessor systems with commercially-available i/o chips – illustrated by a design problem – conclude this series of articles.

The most effective design strategy is to choose those i/o chips whose terminal characteristics can be programmed to match those of the peripheral in question. But such an objective however would be unrealistic because in practice the microprocessor system will have its own programmable i/o chips already interfaced to the microprocessor chip, as illustrated in Fig. 1. In situations like this a good starting point is to derive a simplified programming model of the i/o chip, omitting those features that are not likely to be used. Initially, a programming model should contain the ports, typically two per chip, the control and status registers. Programming models of the Intel 8155, p.i.a. and v.i.a. are shown in Fig. 2, 3 & 4.

The next items to be specified are

- 1 – how the interface initiates an m.p.u. read operation for moving data into a microprocessor (from peripheral 1 in Fig. 1)
- 2 – how the p.i.o. chip signals that the requested read operation has taken place to the interface.

For example in the case of the p.i.a., when programmed with control word 26 to move an item of information from a peripheral into the microprocessor, all the interface has to do is to pull terminal CA1 in Fig. 3 high. When the microprocessor reads the item the signal on terminal CA2 is pulled low.

The third and fourth items to be specified involve the reverse process, namely moving data from the m.p.u. into a peripheral, in which case the designer needs to know

by D. Zissos and Jane Pleus

- 3 – how the interface initiates an m.p.u. write operation for moving data from the microprocessor to a peripheral m.p.u. (peripheral 2 in Fig. 1)
- 4 – how the p.i.o. chip signals that the requested write operation has taken place.

In the case of the Intel 8155 chip, when programmed with control word 99 data is

requested from the m.p.u. by pulling the STROB terminal in Fig. 2 low when the m.p.u. responds when the requested item of information has been loaded into the 8155, the signal on terminal BBF changes to 1.

5 – the final item to be specified is the status flip-flop for each of the ports, as this is the signal looked at by the programmer in the test-and-skip mode.

For example in the case of the 8155, SFFA

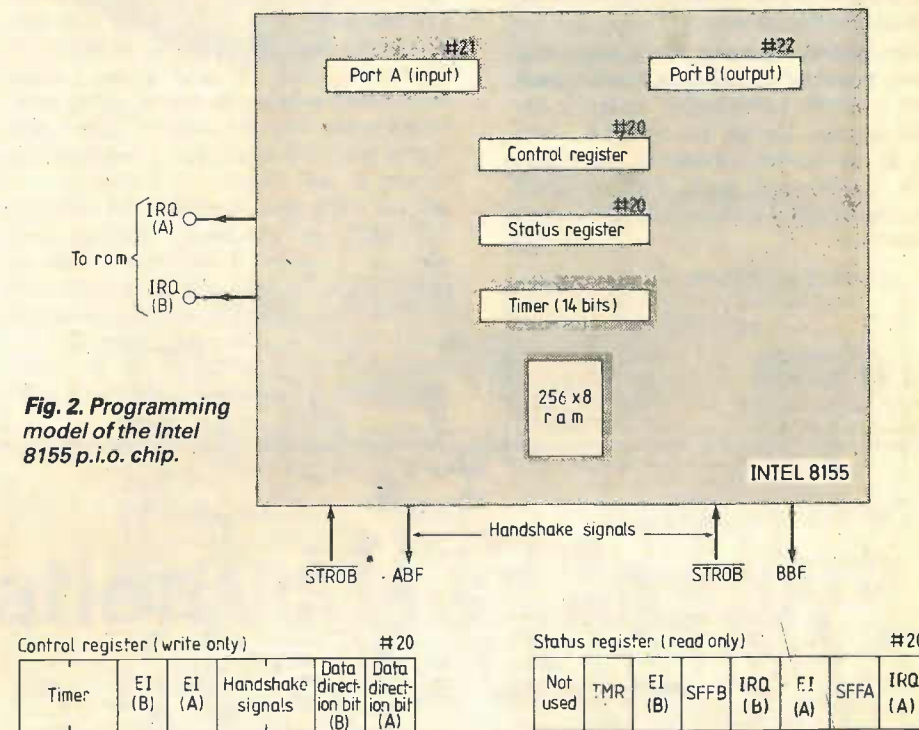


Fig. 2. Programming model of the Intel 8155 p.i.o. chip.

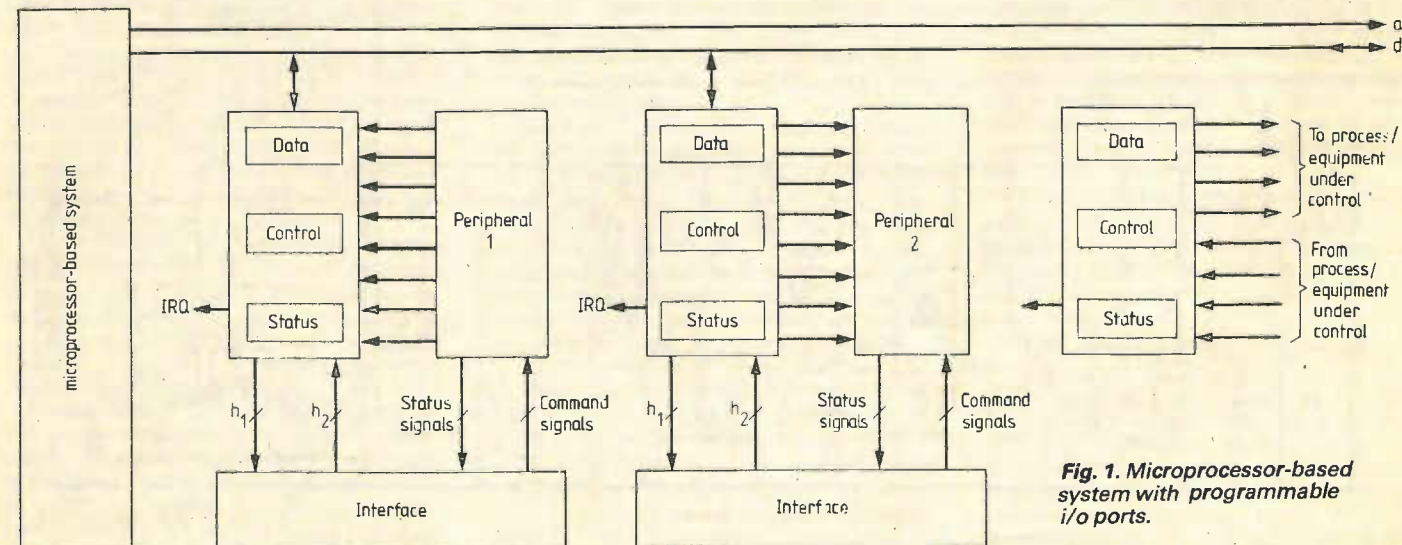


Fig. 1. Microprocessor-based system with programmable i/o ports.

Mnemonic and hex listings of the PRINT problems using programmable i/o chips and test-and-skip.

8085 & 8155				6800 & PIA				6502 & VIA				Comments
Mnemonics	Address	Opcode	Operand	Mnemonics	Address	Opcode	Operand	Mnemonics	Address	Opcode	Operand	
LXI SP, 20C8	2020	31	C8 20	JSR IOPRT	0200	BD 01 00	JSR IOPRT	0300	20 00 02	Initialize		
CALL IOPRT	23	CD 00	20	LDX #0300	03	CE 03 00	LDX #00	03	A2 00			
LXT H, 2080	26	21 80	20	LDAB #n	06	C6 n	LDY #n	05	A0 n			
MVI B, n	29	06 n		X0: DCR B	2B	05	X0: DECB	08	5A	X0: DEY	07 88	Decrement character count
JM X2	2C	FA 3D	20	X0: BMI X2	09	2B 13	X0: BMI X2	08	30 11			If no more characters, go to X2
INI 20	2F	DB 20		X1: LDAA F003	0B	B6 F0 03	X1: LDA A00D	0A	AD 0D A0			Read status register port
ANI 10	31	E6 10		ANDA #80	0E	84 80	AND #10	0D	29 10			Erase all but status flip-flops
JZ X1	33	CA 2F	20	LDAA 00, X	12	A6 00	LDA 0400, X	11	BD 00 04			If data not printed, go to X1
MOV A, M	36	7E		STAA F002	14	B7 F0 02	STA A000	14	8D 00 A0			Otherwise, get next character
OUT 22	37	D3 22		LDAA F002	17	B6 F0 02						Print
				INX H	39	23	INX	1A	08	INX	17 E8	Dummy clear to clear SFF of PIA
JMP X0	3A	C3 2B	20	X2: RST 1	3D	CF	X2: SWI	1E	3F	X2: BRK	1B 00	Point to next character
												Go to X0
												Return to monitor

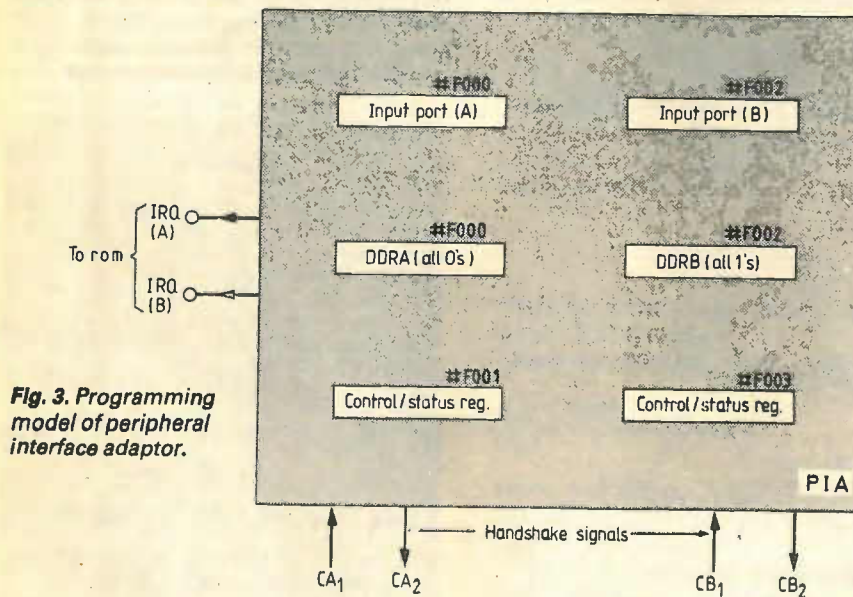


Fig. 3. Programming model of peripheral interface adaptor.

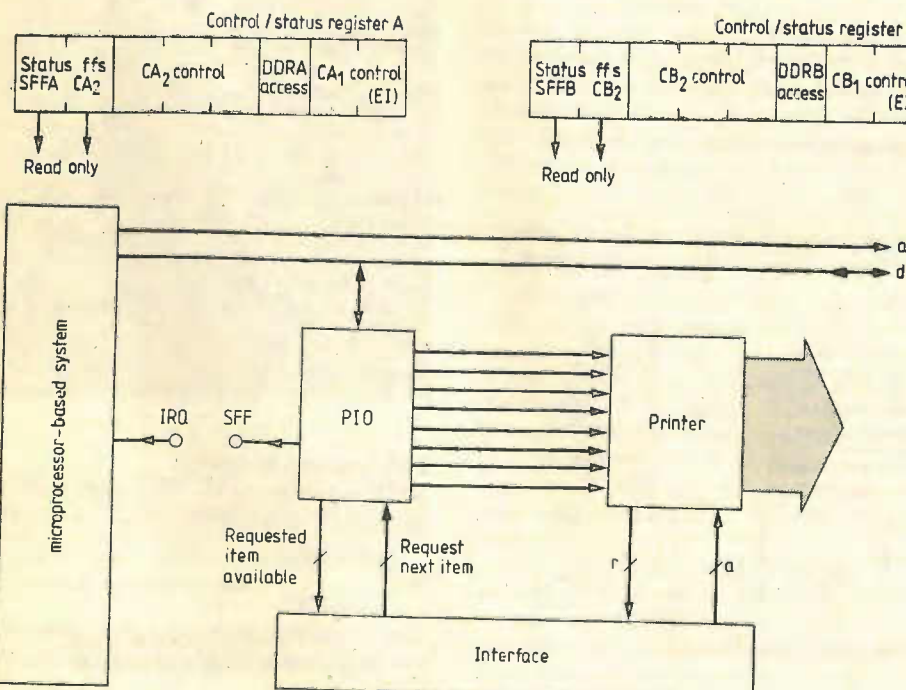


Fig. 4. Block diagram of the PRINT problem.

and SFFB are bits 1 and 4 of the status register – see Fig. 2. Status flip-flop signals are normally made available on terminals for use as interrupt flags if desired. Such flags can be disabled by program; bit 2 in Fig. 2, when 0 disables interrupt flag IRQ(A).

Programming models of the 8155, the p.i.a. and v.i.a. are shown in Figs 2 & 3.

Design problem

Objective: to consolidate the design steps described in the previous article.

Using programmable i/o chips, design a test-and-skip system that would allow the programmer to print a block of characters stored in consecutive memory locations. Implement the design using an action/status character printer and (a) the 8155 interfaced to the 8085 and (b) the p.i.a. interfaced to the Motorola 6800.

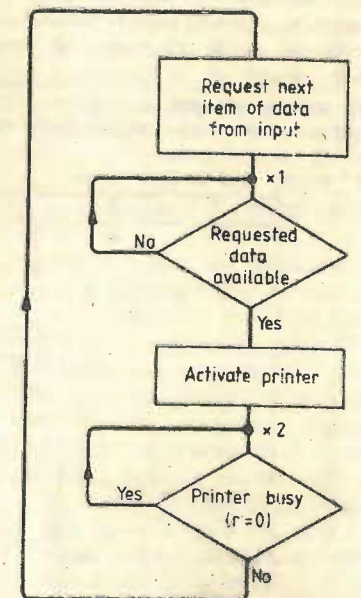


Fig. 5. Flow-chart of our solution to the PRINT problem.

Solution

Handshake signals Fig. 1

h1 - 1 indicates that the port is full (has new data) and 0 that the port is empty (data has been read).

h2 - 0-to-1 change requests an m.p.u. read cycle.

h3 - 0-to-1 change requests new data from the m.p.u.

A test-and-skip system that transfers blocks of data of specified length, byte-by-byte, from memory to a peripheral device through an i/o port using a microprocessor-based system with at least one programmable i/o port is shown in the

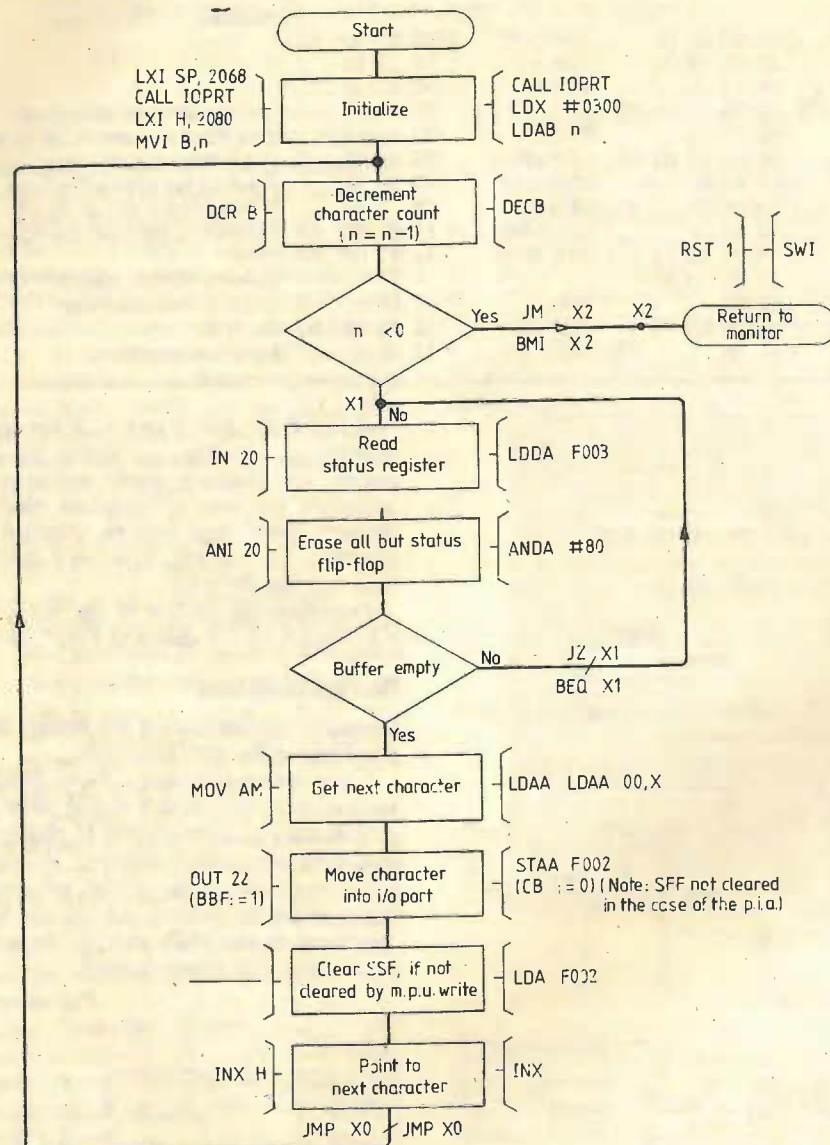


Fig. 6. Programming flowchart of the PRINT problem using programmable i/o chips and test-and-skip

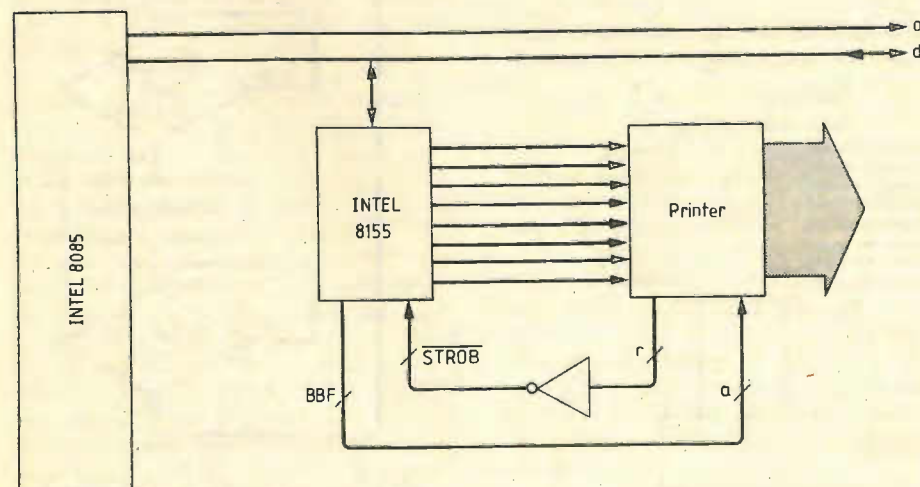


Fig. 7. 8155 implementation of the PRINT problem.

block diagram of Fig. 4, derived directly from Fig. 5 of the previous article. Its step-by-step operation is shown in the flow chart of Fig. 5. The hardware design consists of implementing the interface equations derived for each of the p.i.o. chips. The software design is the self-explanatory programming flow chart of Fig. 6. Ignore at this stage the statements to the sides of the boxes.


8155 implementation

By direct reference to the data sheet of the Intel8155 and to the definitions of handshake signals h1 and h2, we obtain

h1 = BBF
and
h3 = STROB.

The implementation of these equations constitutes the hardware component of our solution, Fig. 7.

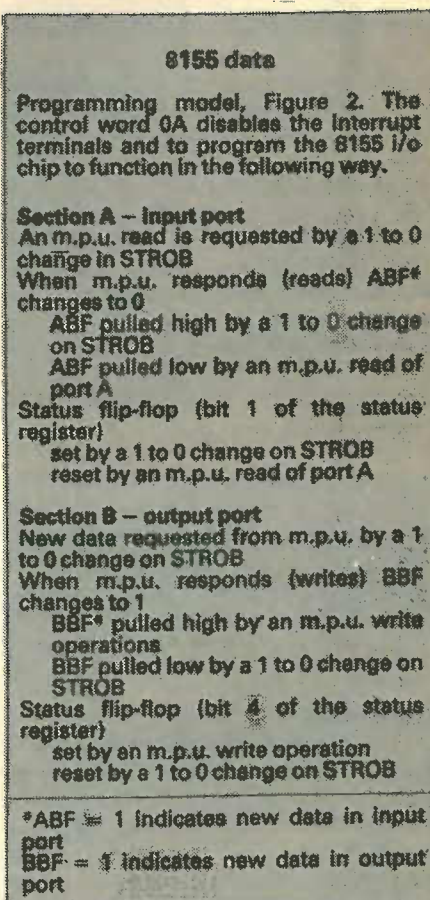Next refer to the 8085 instruction set to derive the mnemonic statements that implement the flowchart in Fig. 6. For ease of reference we list them to the left of each box. Finally, we tabulate these statements with the corresponding machine codes and comments on page 77.



PIA implementation

Referring to the p.i.a. data sheet and the definitions of handshake signals, we obtain

h1 = CB2
and
h2 = CB1.

Implementing these equations gives the pia implementation of our solution, Fig. 8.

continued on page 80

ELECTRIC FIELDS IN A SOLENOIDAL COIL

- often forgotten, more often misunderstood

The time-varying magnetic field in a coil gives rise to electric fields that in turn determine the terminal or circuit properties of the coil

*by F. S. Chute
and F. E. Vermeulen

Since the time of Michael Faraday's experiments, researchers have sought to understand the electromagnetic behaviour of the solenoidal coil, but a complete field solution has proved a difficult and elusive goal. While it is well known that the magnetic field within a long, multi-coil is predominantly axial and azimuthally symmetric, the associated electric fields are less clearly defined. However, a few fundamental points can be made regarding these electric fields without having to resort to a complete boundary-value solution.

When excited by an alternating current, the time variations of the axial magnetic field within the coil must, in accordance with Faraday's law of induction, produce an electromotive force around any closed loop linking the magnetic field. The result is an induced electric field in the circumferential direction, and it is just this field that gives rise to the eddy current that circulates whenever the coil is wound around a core of lossy material. However, the existence of this circumferential electric field at the surface of the coil causes a redistribution of charge along the helical conductor forming the coil, such that the negative charge is concentrated towards the opposite end of the coil. This separation of charge creates a secondary electric field that in the interior region of a long solenoid is predominantly axial. The redistribution of charge is precisely such that the sum of the magnetically induced circumferential electric field and the secondary axial electrical field arising from the charge separation is just equal to zero along the surface of the coil winding.

The relative magnitudes of these circumferential and axial components of the electrical field are easily estimated for a long solenoid of length l and radius a , comprised of N turns. If the magnetic flux linking a cross section of the coil of area πa^2 is defined as Φ , the electromotive force around a closed loop of radius a must in phasor form be given by

$$e.m.f. = j\omega\Phi$$

where ω is the angular frequency. An average value for the circumferential electric field at radius a can now be obtained by dividing this e.m.f. by the circumference of the coil. In other words,

$$E_{\phi a} = \frac{j\omega\Phi}{2\pi a}$$

where $E_{\phi a}$ is the average induced circum-

ferential electric field at the surface of the coil. Alternatively, since the terminal voltage, V , of the coil is just N times this e.m.f.

$$E_{\phi a} = \frac{V}{2\pi a N}$$

Neglecting end effects, an average value for the axial electric field, at radius a , can be obtained by dividing the terminal voltage by the length of the coil. Thus,

$$E_{za} = \frac{V}{l}$$

where E_{za} is the average value of the axial electric field at radius a .

Taking the ratio of E_{za} and $E_{\phi a}$ yields

$$\frac{E_{za}}{E_{\phi a}} = \frac{2\pi a N}{l} = \frac{2\pi a}{d} = \cot\psi \quad (1)$$

where d is the separation between turns and ψ is commonly referred to as the pitch angle of the winding.

For coil configurations commonly used this pitch angle is only a few degrees and the secondary axial electric field is typically more than an order of magnitude greater than the circumferential electric field! Moreover, the axial field E_z is nearly independent of distance from the axis of the coil, whereas the circumferential electric field E_{ϕ} decreases to zero at the coil centre. At interior points then, the dominating influence of the axial electric field will be even more pronounced than near the surface of the coil winding.

All too often this surprising result is not fully appreciated although it was pointed out as early as 1928 by Townsend¹ in conjunction with an investigation of gaseous discharges, and again in 1969 by Contaxes². It is of interest to note that both of these authors comment, more than 40 years apart, that the existence of such a large axial electric field is remarkably unknown.

It is only by virtue of the fact that the secondary electric field of the coil (whose source is the charge distributed along the winding) is much larger than the circumfe-

rential electric field (produced directly by the time-varying magnetic field), that a unique value of potential difference between the terminals of the coil can be defined. For a loosely wound coil with a large pitch angle ψ , the magnitudes of the two fields are more nearly equal and no unique value will exist for the terminal voltage. In this case the measured value of potential difference will depend upon the placement of the leads of the voltmeter that is used to measure the voltage across the coil.

In some earlier work^{3,4}, the authors have described a technique for visually displaying electrostatic fields and electromotive force by utilizing the heat-sensitive colour changes of cholesteric liquid crystals. In this technique, Mylar sheets coated with encapsulated liquid crystals are bonded to a sheet of Teledeltos resistive paper. Currents induced in the resistive paper in the presence of an electric field will cause heating, and produce a temperature variation that is characteristic of the distribution and intensity of the electric field vectors lying in the plane of the resistive paper. The apparent colour of the liquid crystal sheets used by the authors³ is black below about 25°C. Between 25°C and 30°C, the colour of the sheet changes with temperature from red, through yellow and green, to blue at about 30°C. Above 30°C, the apparent colour is again black. Regions of a uniform coloration represent regions of constant temperature or field intensity. While the limited thermal sensitivity of the liquid crystals and their nonlinear temperature response make serious quantitative measurement impractical, the liquid-crystal display does serve to provide the viewer with an immediate appreciation of the overall electric field distribution.

To display the axial and radial electric fields of a coil carrying a time-varying current, a sheet of resistive Teledeltos paper was bonded to a 3.2 mm thick, 60 x 60cm sheet of Perspex with spray adhesive. Four 30 x 30 cm sheets of liquid crystal were then similarly bonded to the resistive paper. This three-layer sandwich combination was then carefully drilled with 40 holes of 2.5 mm diameter to serve as a support plate for a 20 turn coil of No 14 A.W.G. copper wire. A continuous length of wire was then threaded through the holes in the support plate to create a coil of length 40 cm, diameter 10 cm, and turn spacing 2 cm, having a pitch angle so that $\cot\psi = 15.7$. The coil, which has an induc-

*Department of Electrical Engineering
University of Alberta

NEW PRODUCTS

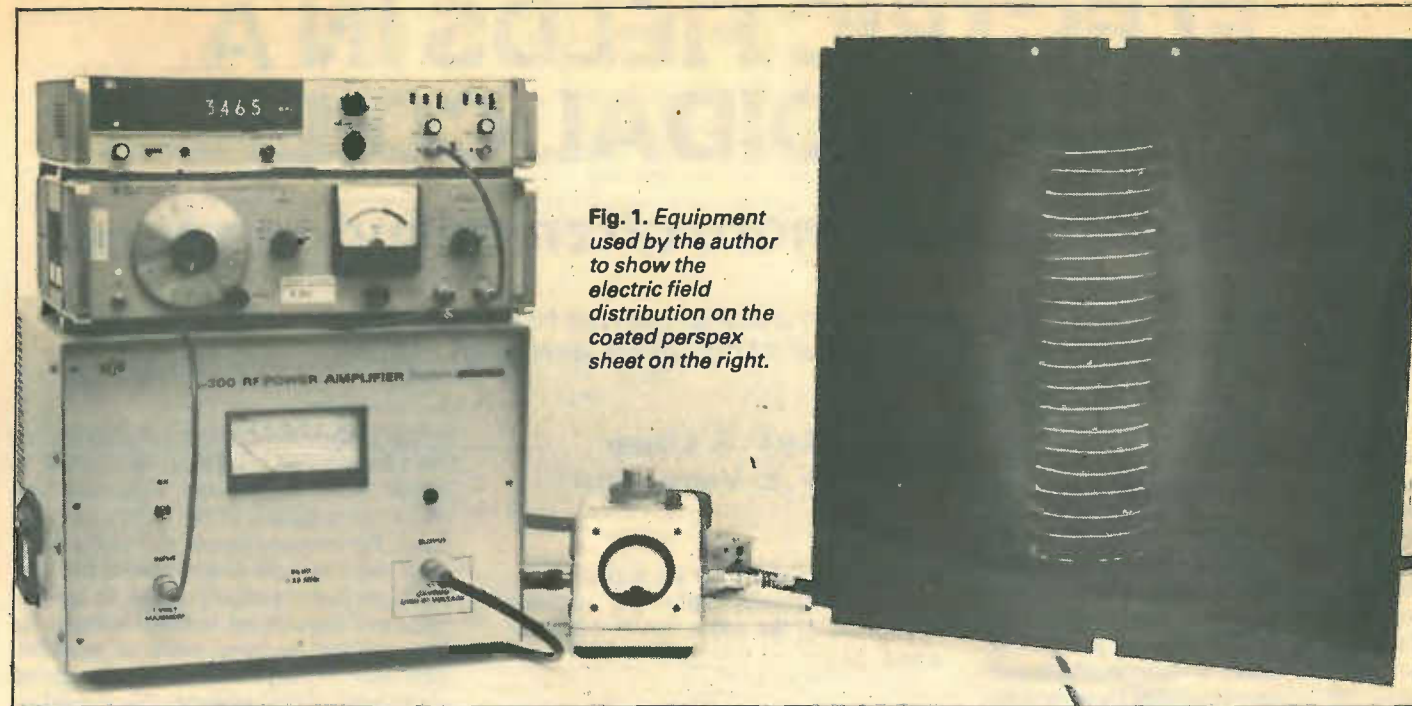


Fig. 1. Equipment used by the author to show the electric field distribution on the coated perspex sheet on the right.

tance of about $12 \mu H$, was series-connected to high-voltage capacitors to resonate at 3 MHz. The coil circuit was fed at 3 MHz from an Electronic Navigation Industries A-300 RF Power Amplifier driven by a Hewlett-Packard 651A Test Oscillator. Figure 1 is a photograph of the apparatus showing the distribution of the dominant secondary electric field surrounding the coil.

When the coil is energized, the liquid crystal sheets change colour almost instantly, in response to the current induced by the radial and axial electric fields around the coil, to produce the display.

The interior region is a uniform shade of blue except near the coil extremities, clearly indicating the uniform nature of the field within the coil. Indeed, the temperature differs by less than $2-3^\circ C$ over the entire central region of the photograph, which ranges through various shades of blue to shades of green in the original display. Near the ends of the coil, where all the field solutions quoted in this paper are modified by end effects, and hence, are only approximate, the axial electric-field intensity has decreased just enough so that not enough heating is produced to cause a perceivable liquid crystal response.

References

1. J. S. Townsend and R. H. Donaldson, "Electrodeless discharges," *Phil. Mag. J. Sci.*, vol. 5, pp. 178-191, 1928.
2. N. Contax and A. J. Hatch, "High frequency fields in solenoidal coils," *J. Appl. Phys.*, vol. 40, No. 9, pp. 3548-3550, 1969.
3. F. S. Chute and F. E. Vermeulen, "A visual demonstration of two-dimensional electrostatic fields," *Amer. J. Phys.*, vol. 24, pp. 1075-1077, Dec. 1974.
4. F. E. Vermeulen and F. S. Chute, "Visual demonstration of electromotive force and induced current," *Amer. J. Phys.*, vol. 45, pp. 309-310, Mar. 1977.

continued from page 78

The Motorola 6800 statements that implement the flow chart are obtained by referring to the 6800 instruction set (see Sept. 1980 issue). As in the case of the 8085, we list them in mnemonic form to the right of each box, and then tabulate them with their machine code, page 77.

Note that a write operation does not reset the status flip-flop, so in the case of the p.i.a. we need to execute a dummy read to clear SFF.

Invitation. Additional problems and solutions in this area are available from Professor D. Zissos, Department of Computer Science, University of Calgary, Calgary, Canada T2N 1N4.

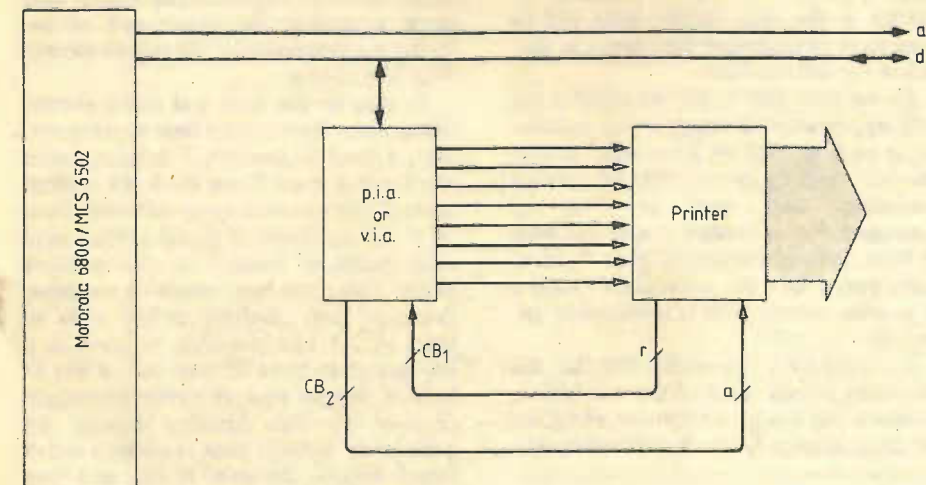


Fig. 8. PIA implementation of the PRINT problem.

PIA data

Programming model, in Fig. 3. Control word 26 for both sections disables the interrupt terminals and programs the PIA chip to function in the following way.

Section A - input port

An m.p.u. read is requested by a 0 to 1 change on CA1
When m.p.u. responds (reads) CA2 changes to 0
CA2 pulled high by a 0 to 1 change on CA1
CA2 pulled low by an m.p.u. read of port A
Status flip-flop (bit 7 of control/status register)
set by a 0 to 1 change in CA1
reset by an m.p.u. read of port A

Section B - output port

New data requested from m.p.u. by a 0 to 1 change of CB1
When m.p.u. responds (writes) CB2 changes to 1
CB2 pulled high by a 0 to 1 change on CB1
CB2 pulled low by an m.p.u. write into port B
Status flip-flop (bit 7 of control/status register)
set by a 0 to 1 change in CB1
reset by an m.p.u. read of port B

LOW-COST PRINTER FOR HOME COMPUTERS

Graphics and lower-case letters are possible on the Amber 2400 printer costing £69.95 excluding v.a.t. The unit prints 24 characters per line on a 58mm-wide plain-paper roll some 90 feet long. Data rates are selectable between 75 and 9600 bits/s. Four horizontally-aligned print solenoids oscillate from side to side, each covering $\frac{1}{4}$ of the paper width, under control of the unit's microcomputer, which also handles software routines and allows data input options. The 2400 is primarily intended for use with home computers. Amber Controls Ltd, Central Way, Walworth Industrial Estate, Andover.

WW301



WW301

FREQUENCY MEASURING D.M.M.

The main difference between this and Fluke's previous hand-held digital multimeters is the inclusion of a frequency measurement function - one of a number of additional facilities made possible by the inclusion of a Sharp 4-bit microprocessor and a CMOS measurement-processing circuit designed and manufactured 'in house'. Frequencies from 12Hz to 200kHz are measured on the 8060A in four automatically-selected

ranges, with 0.01Hz resolution on the lowest range (200Hz), and indicated on a $4\frac{1}{2}$ -digit l.c.d. Alternating voltages may be displayed directly in V r.m.s., in dBm (referred to 600 ohms), or in volts or decibels relative to a previously stored reference. This offset facility may be used with other measurement functions. Direct and alternating voltage, a.c. and d.c. functions are in five ranges, resistance in seven, and decibels in four. Basic d.c. accuracy is 0.04% and sensitivities are $10\mu V$, 10nA and 10m Ω . A 200nS range may be used to measure resistances up to 10G Ω . Further functions include diode test, audible/visual continuity test and self test. Normally, input impedance on the direct-voltage ranges is 10M Ω , but on the 200mV and 2V ranges, an input impedance of greater than 1G Ω may be selected. Fluke (GB) Ltd, Colonial Way, Watford, Herts WD2 4TT.

WW302

ANALOGUE/SWITCHING INTERFACE

This IEEE-bus-controlled interface, manufactured by CIL Microsystems, provides eight analogue inputs, four analogue outputs and four relay-activated change-over switches, for general-purpose control and monitoring applications in research and industry. A concise set of ASCII commands are handled by a 6502 microprocessor, which can also run specific operating programs loaded from the main computer into an optional 4K of ram. Two versions of the PCI 6000 are available, one with eight-bit resolution and one with 12-bit resolution. Facilities include differential inputs and programmable gain, and

the relay-contact ratings are 240V and 1A. CIL Microsystems Ltd, Decoy Road, Worthing, Sussex BN14 8ND.

WW303

64K EPROM PROGRAMMING ADAPTER


Any eprom programmer suitable for Texas 2532-type devices may be used to program 64K eproms by adding an adapter made by Elan

Digital Systems. The E6 adapter has a z.i.f. socket for 2564 or 2764 devices and a ribbon cable terminated by a plug which fits into the existing programmer. Each half of the 64K, selected by a switch, is programmed separately by the existing programmer in the usual manner. All automatic test or editing functions of the existing programmer are retained and an additional feature allows Intel 2732 or 2732A i.c.s to be read through the adapter. Elan Digital Systems Ltd, 16-20 Kelvin Way, Crawley, West Sussex RH10 2TS.

WW304

CMOS R.F. SWITCH

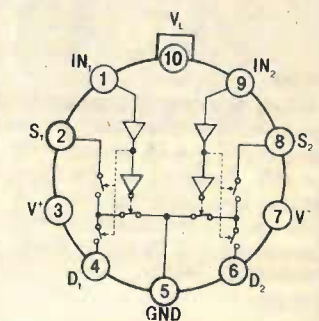The IH5341 is a dual-channel r.f. and video switch with t.t.l. and c.m.o.s.-compatible control inputs, manufactured by Intersil. Each channel has three switch elements, connected in a series/shunt formation, giving an $R_{DS(on)}$ of less than



75 Ω , flat response from 0 to 100MHz and 70dB isolation at 10MHz in the off state. Isolation between the two channels is greater than 60dB at 10MHz. Supply current is less than $1\mu A$ and switching speeds are 150ns, on and 80ns, off, giving break-before-make operation. A TO-100 package is used. Intersil Datel Ltd, 9th Floor, Snamprogetti House, Basingstoke, Hants.

WW305



WW303

NEW PRODUCTS

EPROM ERASER

Both models in Northern's eeprom eraser range cost under £60 excluding vat and can be used to erase up to six devices at once. The latest of these, the UV1T, is basically the same as the earlier UV1B, but with a 10 to 60-minute time switch fitted. Lamp life is quoted as being in excess of 3000h and all models, i.e., those mentioned for 220 to 240V operation and two others for 110 or 240V mains, comply with appropriate British Standards. Northern Electronics Ltd, 51 Arundel Street, Mossley, Lancs OL5 0LS. WW306

CODED ROTARY SWITCHES

Miniature rotary switches with ten or 16 positions, giving b.c.d. or hexadecimal outputs, have been added to the Elma range of ceramic wafer switches marketed by Radiatron. Measuring 10 by 10 by 11mm, these switches can be obtained for mounting either horizontally or vertically on a p.c.b. and with either a screwdriver slot or spindle. Gold-plated contacts are used, giving a contact resistance of less than 50mΩ and the contact rating is 50V at 0.2A between -40 and 85°C. Radiatron say that these switches have a life expectancy of more than 10⁴ rotations. Radiatron Components Ltd, 76 Crown Road, Twickenham, Middx. WW307

32 × 8 BIPOLAR PROM



A 'washed emitter' process has been used to produce two 256-bit Schottky bipolar proms with typical access times of 9ns. One, the 63S080 has open-collector outputs and the other, the 63S081 has three-state outputs. Applications of these 32 × 8-bit proms include address decoders, priority encoders and random-logic elements in high-speed systems. Monolithic Memories Ltd, Lynwood House, 1 Camp Road, Farnborough, Hants GU14 6EN. WW308

DISPOSABLE TEMPERATURE INDICATORS

Adhesive dots and strips for recording maximum temperatures are available from Cobonic Ltd. Within a second of reaching the temperature marked on it in both °C and °F, one of five different areas on the labels, or one area on



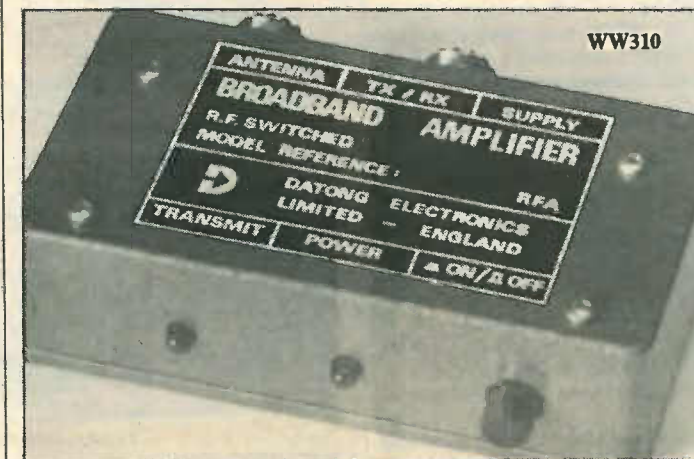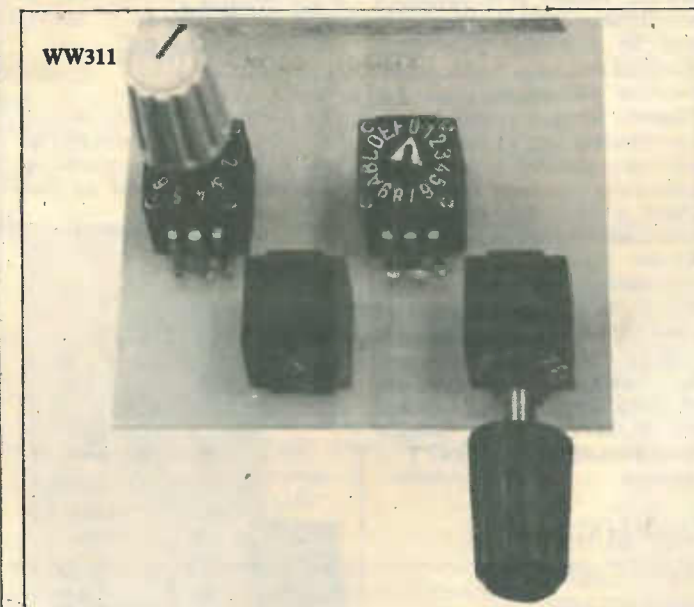the dots, changes irreversibly from white to black. There are 40 different temperature levels in the range, from 40 to 260°C, and each sensitive area changes colour at within 1% of the specified temperature. These products are useful for monitoring and recording maximum temperatures in hazardous and inaccessible areas. Cobonic Ltd, Lantern Yard, Ludlow Road, Guildford, Surrey GU2 5NW. WW309



BROADBAND R.F. PREAMPLIFIER

An r.f. preamplifier providing 9dB gain and suitable for use with low-power transceivers in the range 5 to 200MHz can be obtained from Datong. Send/receive switching is automatic, using r.f. sensing and an internal bypass relay, and the unit is claimed to handle large signals well (intercept point + 20dBm). Applications of the model RFA include private mobile v.h.f. transceivers, marine and aeronautical band reception, scanning receivers and antenna-loss compensation. Datong Electronics Ltd, Spence Mills, Mill Lane, Bramley, Leeds LS13 3HE. WW310

NON-INVASIVE X-RAY METER

An electronic system for non-invasive measurement of radiation intensity and exposure time in diagnostic X-ray equipment has been developed in Sweden by three researchers at the Chalmers Institute of Technology. The equipment,


produced by HB Innova Electronic and called Digi-X, consists of a measurement unit, with parameter, threshold and mode controls, and a detector which is attached to the patient. Peak kilovolt readings are indicated digitally and actual exposure time is calculated from previously stored threshold values selected by the operator. The system may also be used to check beam quality and, with an option, be used to calculate current and mAs values. HB Innova Electronic, Box 25062, S40031 Gothenburg, Sweden. WW311

METALLIZED-FILM CAPACITORS

Extensions in Rifa's range of metallized polypropylene capacitors have been made to include the PHE425 series. These components, with values ranging from 1.5 to 135nF, are relatively small since they incorporate a 4μm-thick metallized film. Capacitance tolerances are 1%, 2%, or 5% and insulation resistance is claimed to be better than 200GΩ at 20°C, 10V. Working voltages, dependent on value, may be 200, 100 or 63V, direct. Rifa AB, Market Chambers, Shelton Square, Coventry. WW312

T.T.L.-OUTPUT PATTERN GENERATOR

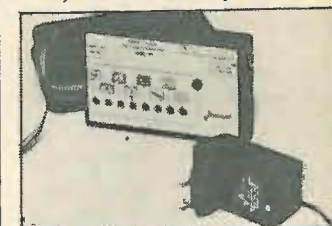
A hand-held pattern generator providing t.t.l.-compatible red, green and blue signals for servicing monitors and video displays is manufactured by Sadelta. Eight patterns are produced, colour bars, red, green, blue and white rasters, grey scale, cross-hatch and vertical lines, and the unit may be used for



up to four hours from one battery charge. The RGB11 is intended for servicing of commercial and hobby v.d.us, including video games, and c.c.t.v. monitors. House of Instruments, Clifton Chambers, 62 High Street, Saffron Walden, Essex CB10 1EE. WW313

Professional readers are invited to request further details on items featured here by entering the appropriate WW reference number(s) on the mauve reply-paid card.

The Professional Choice

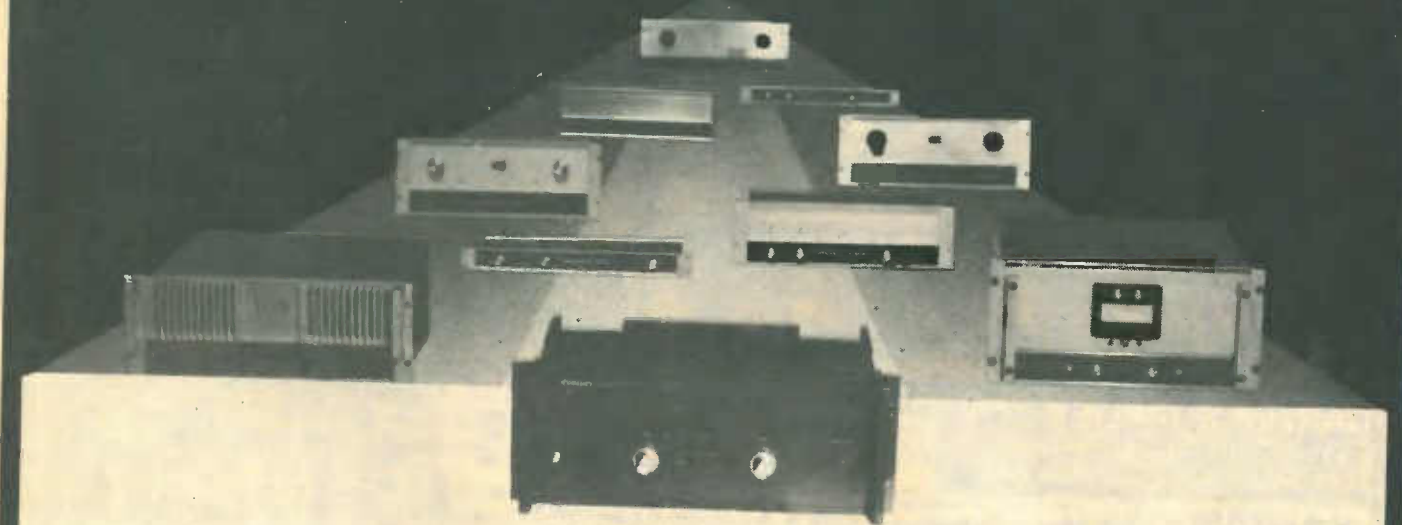

AMCRON 

Since the introduction of the DC300 in 1967, AMCRON amplifiers have been used worldwide - wherever there has been a need for a rugged and reliable amplifier. Their reputation amongst professional users, throughout industry, has made the name of AMCRON synonymous with power amplification. For power you can depend on - choose AMCRON, the professional choice.

For further details contact the UK Industrial distributor:

G.A.S.

G.A.S. ELECTRONICS

16, ST. ALFEGE PASSAGE, LONDON SE10

TELEPHONE: 01-853 5295

TELEX: 923393 LASFR G

DAROM SUPPLIES Dept. AW - Tel: (0925) 64764

4 Sandy Lane, Stockton Heath Warrington, Cheshire, WA4 2AY


sabtronics

FREQUENCY METERS

8 digit:

- ★ Convenient single input for entire range
★ Big easy to read LED display
★ Excellent sensitivity
★ 10MHz crystal controlled timebase
★ Battery or mains operated
★ 3 switch selectable gate times
★ Leading zero suppression

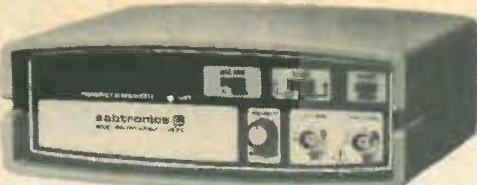8110A..... 20Hz-100MHz£67
8610A..... 20Hz-600MHz£82



9 digit:

- ★ 9 digit resolution for more precise readings
★ Excellent 30mV sensitivity up to 1GHz
★ 3 switch selectable gate times
★ 10 MHz crystal controlled timebase
★ 2 separate inputs for added versatility
★ Front panel sensitivity control
★ Battery or mains operated

8610B..... 10Hz-600MHz£99
8000B..... 10Hz.....1000MHz.....£155

WW - 72 FOR FURTHER DETAILS

HANDELD MULTIMETERS

High quality, precision 3 1/2 digit LCD DMMs with excellent price performance value



2033.....£36.75
AC/DC 100µV-1000V
AC/DC 10µA-2A
Ohms 1Ω-20MΩ
2035.....£62
AC/DC 100µV-1000V
AC/DC 0.1µA-2A
Ohms 0.1Ω-20MΩ

Add 15% V.A.T. on all prices - prices correct at 1-5-82 - E&OE cash with order or credit card - Carriage £5 for Express Delivery

VHF FM MOBILE RADIO

! And it's British !

MODEL CT210

- ★ APPROVED TO MPT 1301
★ MODULAR CONSTRUCTION
★ RANGE OF ACCESSORIES



MODEL CT210

- ★ MADE IN U.K.
★ COMPETITIVE PRICE
★ MULTI-CHANNEL CAPABILITY

Export and Dealer Enquiries Welcome

COM-TEK (MIDS) LTD. 506 Alum Rock Road - Birmingham B8 3HX

Telephone: 021-326 6343

Telex: 337000

WW - 061 FOR FURTHER DETAILS

UNITS

Table listing various electronic units with model numbers, descriptions, and prices. Includes VMOS wideband linear power amplifiers, frequency dividers, and RF preamplifiers.

COMPONENTS

Table listing various electronic components including transistors, diodes, capacitors, and resistors with their respective prices.

POST AND PACKING 50p - PLEASE ADD V.A.T. 15% ON TOTAL

ALL COMPONENTS AND UNITS ABOVE IN STOCK FOR IMMEDIATE DESPATCH

RESEARCH COMMUNICATIONS LIMITED

43A COURT STREET, FAVERSHAM, KENT ME13 7AL

WW - 020 FOR FURTHER DETAILS

reprints

If you are interested in a particular article / special feature or advertisement published in this issue of WIRELESS WORLD

why not take advantage of our reprint service.

Reprints can be secured at reasonable cost to your own specifications providing an attractive and valuable addition to your promotional material. (Minimum order 250.)

For further details contact Michael Rogers, IPC Electrical-Electronic Press Ltd. Phone 01-661 3036 or simply complete and return the form below.

To Michael Rogers, Reprints Department, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS

I am interested in... copies of the article / advertisement headed... featured in

... on page(s)... in the issue dated

Please send me full details of your reprint service by return of post.

Name

Company

Address

Tel. No.

LAINGREX SUPPLIES LTD RST
Climax House, Fallsbrook Rd., Streatham, London SW16 6ED
Tel: 01-677 2424 Telex: 946708 RST

Large multi-column table listing various electronic components including Semiconductors, Valves, Integrated Circuits, Bases, and CRTs, with their respective part numbers and prices.

Terms of business: C.W.O. Postage and packing valves and semiconductors 58p per order. CRTs £1.73. All prices include V.A.T. Price ruling at time of despatch. In some cases prices of Mullard and USA valves will higher than those advertised. Prices correct when going to press. Account facilities available to approved companies with minimum order charge £10. Carriage and packing £1 on credit orders. Over 10,000 types of valves, tubes and semiconductors in stock. Quotations for any types not listed: S.A.E.

Telephone 01-677 2424/7 Telex 946708 E & O.E.

Open to callers Monday-Friday 9 a.m.-5 p.m.

WW ... WW ... WW ...
 WW ... WW ... WW ...
 WW ... WW ... WW ...
 WW ... WW ... WW ...
 WW ... WW ... WW ...
 WW ... WW ... WW ...
 WW ... WW ... WW ...
 WW ... WW ... WW ...
 WW ... WW ... WW ...
 WW ... WW ... WW ...
 WW ... WW ... WW ...
 WW ... WW ... WW ...
 WW ... WW ... WW ...
 WW ... WW ... WW ...
 WW ... WW ... WW ...
 WW ... WW ... WW ...

Please arrange for me to receive further details of the products listed, the appropriate reference numbers of which have been entered in the space provided.

Name

Position in Company

Name of Company

Address

Telephone Number

Nature of Company/Business

No. of employees at this establishment

VALID FOR SIX MONTHS ONLY

CUT HERE

Postage will be paid by Licensee

Do not affix Postage Stamps if posted in Gt Britain, Channel Islands, N Ireland or the Isle of Man

BUSINESS REPLY SERVICE
Licence No 12045

WIRELESS WORLD
Reader Enquiry Service
429 Brighton Road
South Croydon
Surrey CR2 9PS

2

CUT HERE

Wireless World Subscription Order Form Wireless World, August 1982 WW 268

UK subscription rates
 1 year: £12.00
 Overseas 1 year: £15.00

USA & Canada subscription rates
 1 year: \$39.00

Please enter my subscription to Wireless World for 1 year

I enclose remittance value.....made payable to
IPC BUSINESS PRESS Ltd.

Name.....

Address.....



BEFORE



AFTER!

PUT A SMILE BACK ON YOUR OLD AVOMETER!

Send it now for estimate, repair or recalibration

Quick turn round on estimates/repairs

Large stocks of new AVOMETERS

Avo Sales and Service



Farnell International Instruments Ltd.,
 Sandbeck Way, Wetherby
 West Yorkshire LS22 4DH

Tel 0937 61961 Telex 55478 Farint G

WW-004 FOR FURTHER DETAILS

ELECTRIC SHOCK

2 WAYS TO RECOVERY

ACT AT ONCE - DELAY IS FATAL

ELECTRIC SHOCK ACT AT ONCE - DELAY IS FATAL

make sure it is safe to approach

If the casualty is not breathing

If the casualty is breathing

If the casualty is NOT breathing

start artificial respiration - speed is essential

If AFTER FOUR INFLATIONS casualty does not respond to artificial respiration

external heart compression

Get someone to call ambulance and while you

Check for a pulse

Check for a pulse

Check for a pulse

Check for a pulse

Display the ELECTRICAL REVIEW shock first aid chart (356x508mm) supplied in thousands to destinations world-wide. Recent deliveries include consignments to companies in Papua New Guinea, Dubai, United Arab Emirates, The Philippines, apart from UK commercial and industrial, educational, Central Government, Local Authorities' orders.

Carry the ELECTRICAL REVIEW pocket-size shock card (92x126mm) designed to help safety and training officers, medical and welfare personnel; all who might find themselves called to save a life. Always pocket your card; there's a useful two-year calendar on the back.

GET IT - READ IT - PRACTISE 1-4
 BE READY TO SAVE A LIFE.
 SOMEONE MIGHT SAVE YOURS.

ACT AT ONCE - DELAY IS FATAL!

To IPC Electrical-Electronic Press Ltd.,
 General Sales Department,
 Room 205,
 Quadrant House,
 Sutton, SM2 5AS,
 Surrey,
 England.

Company registered in England
 No 677128. Registered Office
 Quadrant House, The Quadrant,
 Sutton, Surrey SM2 5AS

Please send.....copy/copies as indicated

Pocket Card @ 70p each inc VAT
 Paper Chart @ 70p each post free
 Card Chart @ £1.40 each post free
 Plastic Chart @ £2.10 each post free

Discounts: 100 + copies 10%
 500 + copies 15%

(Overseas surface and air mail rates supplied on application.)

Appointments

Advertisements accepted up to 12 noon Wednesday, July 28th, for September issue, subject to space being available.

DISPLAYED APPOINTMENTS VACANT: £13.50 per single col. centimetre (min. 3cm).
 LINE advertisements (run on): £2.50 per line, minimum 5 lines. (Prepayable.)
 BOX NUMBERS: £1.50 extra. (Replies should be addressed to the Box Number in the advertisement, c/o Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.)
 PHONE: IAN FAUX, 01-661 3033 (DIRECT LINE)

Cheques and Postal Orders payable to IPC Business Press Ltd.

AMPEX SYSTEM MAINTENANCE ENGINEER

to join a resident team at a site of EXCEPTIONAL INTEREST situated in the St. James's Park area of London. The team is responsible for round-the-clock maintenance of a large INFORMATION STORAGE AND RETRIEVAL SYSTEM WHICH COMBINES both VIDEO AND COMPUTER TECHNOLOGY.

Ampex requires an Engineer with:

- Sound knowledge of Electronics/HNC or equivalent
- At least three years' experience of maintaining ANALOGUE and/or DIGITAL electronic equipment
- Preferably, specific experience with: VIDEO equipment, such as cameras, VTRs, etc, and/or DIGITAL equipment such as disk/tape drives, mini computers.

Good salary plus generous shift allowance.

Company car plus travel allowance.

Pension and Life Assurance and Permanent Health Schemes.

Please write or phone for an application form from Maureen Brake, Reading (0734) 875200, Ampex Great Britain Limited, Acre Road, Reading, Berkshire.

(1729)

ST BARTHOLOMEW'S HOSPITAL, LONDON EC1A 7BE

Electronic Engineer

in Radiation Physics Department required

to assist in the servicing of a modern 20 MeV Linear Accelerator and a 6 MeV Linear Accelerator which is about to be installed and in the manufacture of dosimetry equipment and devices required for development and research. Experience in Radar or Radiation Physics would be advantageous but not essential as appropriate training will be provided. Support given to obtain relevant higher qualifications. Applicants should possess ONC/HNC (Electronics) or other appropriate qualifications and at least three years' relevant experience. Salary on Medical Physics Technician Grade III scale: £6,468 to £8,087 per annum inclusive. For application form and job description please write to the Personnel Department or telephone 01-600 9000 Ext. 2271. Ref. no. TG/10. Closing date, 4 August, 1982.

(1733)

National Broadcasting School

The National Broadcasting School, an independent organisation under the auspices of the IBA, provides training for Independent Radio. As well as running full-time engineering courses, the Engineering Department also teaches the non-technical courses and maintains 6 broadcast-capable studios and ancillary areas.

PART-TIME LECTURERS IN ENGINEERING

Two part-time lecturers are required to contribute to 3-month Engineering Course starting 21 September. They must have considerable experience in radio broadcasting and the ability to pass on that experience. Salary negotiable.


BROADCAST ENGINEER

A Broadcast Engineer with several years' experience in maintaining modern sound broadcasting equipment and a recognised technical qualification is required. In addition to the maintenance of the school's studios, the job includes teaching Broadcast Engineers. A desire to teach is therefore essential and previous experience in this and local radio would be an advantage. Salary negotiable.

Applications, which will be treated in confidence, should be made to the Chief Engineer, NBS, 14 Greek Street, London W1.

(1717)

14 Greek Street
 London W1
 01-434-2411

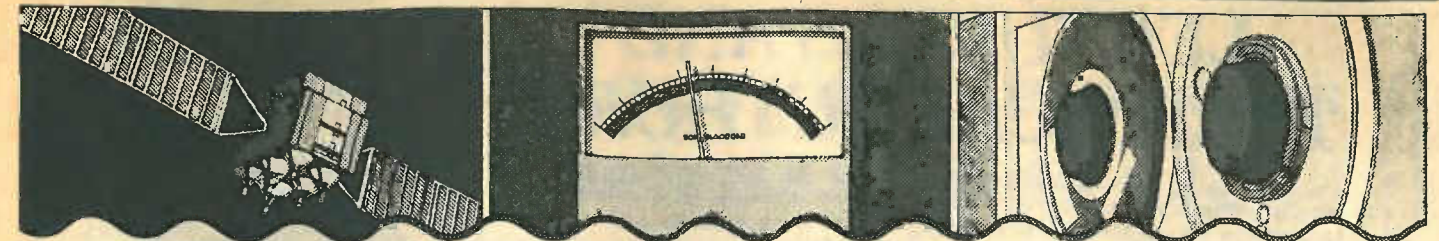

ELECTRONICS TECHNICIANS Total involvement across the spectrum of advanced communications

The Government Communications Headquarters at Cheltenham is one of the world's foremost centres for research, development and production in the fields of voice and data communications and communications security. Its comprehensive facilities, some of them unique, are geared towards producing creative solutions to complex communications problems using state-of-the-art techniques including computer/microprocessor applications.

There are currently opportunities for those with proven practical experience in electronics to become totally involved in complex systems spanning the whole spectrum of electronics technology. As a Telecommunications Technical Officer you will supervise a team of technicians involved in the management, construction, installation, testing, commissioning and maintenance of traditional and advanced technology communications and computer systems. Alternatively you will provide support for project engineers and scientists involved in the planning, research and engineering development of state-of-the-art systems.

You will work in one or other of the following fields:-

Telecommunications at HF, VHF and microwave frequencies, including satellite communications, computers and digital processing.

Data Transmission

Communications Security

Where necessary, in depth training will be provided and there are opportunities to attend familiarisation and management courses.

Posts are at two levels:-

At the lower level, the successful candidates will provide first line technical and supervisory control of a number of technicians involving work of a practical nature requiring 'hands on' participation. They may also undertake individual work of a highly technical nature with or without supervisory responsibilities.

The higher level posts involve the management of 2 or more teams as mentioned above. In many areas there is a close technical involvement requiring a high level of technical competence. Working as members of a multi-disciplinary team, the successful candidates will be expected to apply

their knowledge and experience to the broader fields of work planning and management, including the implementation of medium to large scale projects.

Cheltenham

A significant advantage for people working at GCHQ in Cheltenham is its location in this elegant Regency town set in the heart of the Cotswolds. You can choose to live in the town itself, or in one of the delightful villages that surround it. Either way, you will have easy access to good shops, schools, sports facilities and cultural amenities in Cheltenham and nearby Gloucester, and also enjoy fast road/rail links to London, the Midlands and the West Country. RELOCATION ASSISTANCE MAY BE AVAILABLE.

Qualifications


Candidates must possess a TEC/SCOTEC Certificate in Electronics, Telecommunications or similar discipline; or a City and Guilds Part II Telecommunications Technicians Certificate, or Part I plus Mathematics B, Telecommunication Principles B, and either Radio Line Transmission B or Computers B; or equivalent. Preference may be given to candidates with higher qualifications. Senior ex-service personnel with formal approved Service technical training may also be considered.

In addition, all candidates must have had appropriate training and will normally be expected to have about 4 years (lower level) or 7 years (higher level) experience in either radio communications transmitters or receivers, radar, data transmission, computers or similar electronic systems. High technical competence and/or proven managerial experience is also required.

Salaries up to £9085

Higher level posts: £8065 — £9085; lower level posts: £5980 — £8180. Level of appointment and starting salary according to qualifications and experience. There are good prospects of promotion to posts with salaries of up to £12,650.

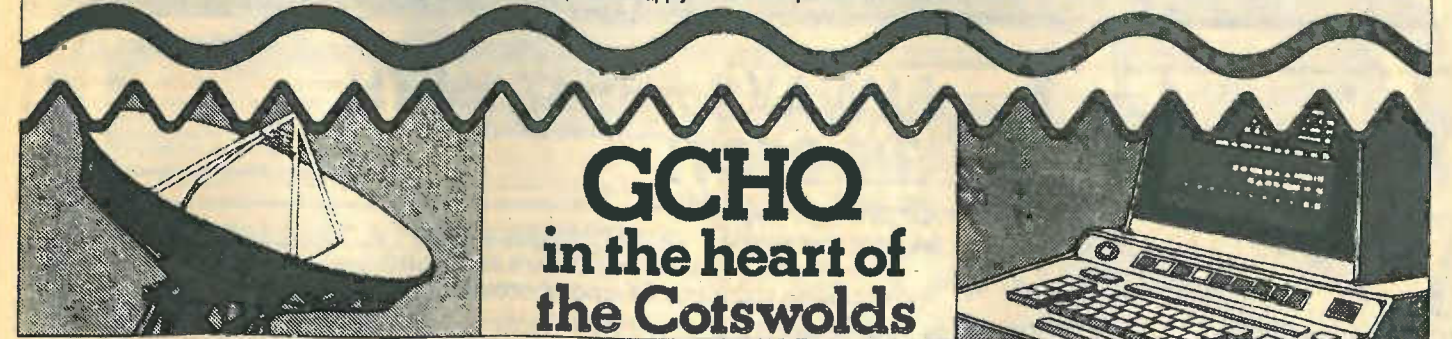For further information and an application form (to be returned by 12 August 1982) write to Civil Service Commission, Alencon Link, Basingstoke, Hants RG21 1JB, or telephone Basingstoke (0256) 68551 (answering service operates outside office hours). Please quote ref: T/5792/2.



GCHQ in the heart of the Cotswolds

CCTV SERVICE ENGINEER

required to carry out repair and maintenance on all types of surveillance equipment. Salary commensurate with age and experience. Please write, with full C.V., to: BOX No. 1711

(1711)

2-WAY RADIO SERVICE TECHNICIAN

Experienced in servicing V.H.F. and U.H.F. Land Mobile Equipment, required for expanding COMMUNICATIONS COMPANY in STAINES. SALARY: Commensurate with experience.

CONTACT: Chris Turner,
FRANK CODY ELECTRONICS LTD
STAR HOUSE, GRESHAM ROAD,
STAINES, MIDDLESEX
 Or telephone Staines 62682 for an appointment.

(1701)

LECTURERS AND TECHNICAL AUTHORS

The Engineering Training Centre situated near Evesham in Hereford and Worcestershire, trains the Corporation's technical staff, both on first appointment and thereafter in the technology of broadcasting. The site is residential for students and some 400 BBC staff normally work or are in training there.

LECTURERS

Duties will involve contributing towards the operational training of Technical Staff in Television and/or Radio Broadcasting. This includes instructing Technical Operators who are responsible for sound coverage, audio mixing, camera work and lighting in Television or operating Network Continuity Suites in Radio. The Training Centre has Radio and Colour Television Studios using the latest broadcasting equipment.

Candidates, male or female, should have recent experience in some aspect of Technical Operations or Engineering in the Broadcast or Closed Circuit field and a good technical knowledge of audio or video equipment. They should preferably have a qualification of HNC, C & G Full Technological Certificate in Telecommunications, a pass in the examination of the Council of Engineering Institutions or equivalent. Consideration will be given to providing appropriate training to otherwise suitable applicants who do not hold these qualifications.

TECHNICAL AUTHORS

Engineering Training Department includes a Unit, consisting of one Senior Author and four Authors, which provides overall systems descriptions for major installations throughout the Corporation and publishes technical standards and procedures. The unit is supported in-house by a drawing office and printing facilities, together with computer based phototypesetting, word processing and graphics.

The technologies covered by Technical Publications Unit are Radio, Television, Transmission and, increasingly within these fields, computers. Authors have substantial personal responsibility to assemble and present their material accurately and in a form acceptable to users.

The successful applicant will hold a degree in electronics or a reasonable equivalent such as a Higher National Certificate, have good experience of technical documentation and a good grasp of a significant area of broadcasting technology or of a closely related field of electronics. Increasing versatility across the whole field will be expected as experience grows. Appropriate training, including areas of broadcasting technology, will be provided if necessary.

Salary on appointment, for both positions will be between £9,435 and £10,293 rising to £12,254.

Excellent welfare and club facilities. Pensionable posts. Relocation expenses considered. For an application form and further information about the Technical Author vacancy please contact **Head of Training Section (Engineering), Mr J H Brooks**; those interested in the Lecturer vacancy, please contact **Head of Training Section (Operations), Mr D G Enoch**. BBC Engineering Training Centre, Wood Norton, Evesham, Worcs WR11 4TF. Telephone Evesham 45123.

Closing date for return of application forms is 14 days after publication.

BBC

(1723)

£25,000?

- DESIGN ENGINEER**
RF test equipment including VSWR test sets, frequency standards and RF measuring instruments for a small successful company. £ Negotiable - West Country.
- TEST ENGINEERS**
To test and service VHF and UHF transmitters and receivers - several clients. To £8,000 - Hants/Berks.
- RF DESIGN ENGINEERS**
To join a small team designing microprocessor-based signal sources. To £11,000 - Herts.
- PROJECT LEADER**
To head team engaged on microwave development, UHF/VHF techniques, microstrips and mixers. To £14,000 - Herts.
- ELECTRONIC ENGINEERS**
Development of digital-based intruder detection equipment. To £8,000 - Surrey.
- DESIGN ENGINEER**
To design all stages of microwave and satellite communication systems from base band to 6GHz. To £10,000 - Essex.

CLIVEDEN CONSULTANTS
87 St. Leonard's Road
Windsor, Berks.
Windsor (07535) 57818/58022
24-hour service (1640)

CLIVEDEN

UNIVERSITY OF EAST ANGLIA
Norwich

ELECTRONICS TECHNICIAN

Required to be responsible for the Electronics Workshop in the School of Mathematics and Physics. The workshop offers technical support to research and teaching in physics and electronics systems engineering. The successful applicant's responsibilities will include:

- the organisation and general supervision of the workshop;
- the design and construction of digital and analogue circuits;
- the repair and modification of electronic equipment including microcomputer systems.

Applicants must hold a suitable qualification in electronics, be able to work with minimum supervision and have substantial experience of modern electronic engineering techniques.

Salary on the Grade 7 scale £7,605-£8,542 per annum.

Application forms and further particulars can be obtained from the Senior Administrative Assistant, School of Mathematics and Physics, University of East Anglia, Norwich NR4 7TJ, to whom applications should be returned by 5 July, 1982.

1692

APPOINTMENTS IN ELECTRONICS to £15,000

MICROPROCESSORS
COMPUTERS - MEDICAL
DATA COMMS - RADIO

Design, test, field and support engineers - for immediate action on salary and career advancement, please contact

Technomark
Engineering and Technical Recruitment

11, Westbourne Grove
London W2. 01-229 9239 (9257)

UNIVERSITY COLLEGE, CARDIFF DEPARTMENT OF PHYSIOLOGY ASSISTANT EXPERIMENTAL OFFICER

(ELECTRONIC INSTRUMENTATION)

CORRECTED ADVERTISEMENT
Applications are invited for the above post - design experience essential, degree in electronics an advantage. Salary range: OR Gr. IB £5,286-£8,925 p.a. - duties to commence as soon as possible. Applications (two copies), together with the names and addresses of two referees, should be forwarded to the Vice-Principal (Administration) and Registrar, University College, P.O. Box 78, Cardiff CF1 1XL, from whom further particulars may be obtained. Closing date 11th August. Ref. 2428. (1728)

DIGITAL EXPERIENCE?
FIELD SUPPORT
R & D AND SALES
VACANCIES IN COMPUTERS
NC, COMMS., MEDICAL
VIDEO, ETC.

For free registration ring
0453 883264
01-290 0267

LOGEX

ELECTRONICS RECRUITMENT SERVICE
LOGEX HOUSE, BURLEIGH, STROUD
GLOUCESTERSHIRE GL5 2PW
TEL 0453 883264, 01-290 0267 (321)

TELECOMMUNICATION ENGINEERS SAUDI ARABIA C.£22,500 P.A. TAX FREE

SWITCHING SYSTEM ENGINEER
Exp. SPC switching system, analyse and evaluate tenders relating to electronic switching.
MOBILE TELEPHONE SYSTEM ENGINEER
Study requirements for new automatic mobile telephone system.
MARITIME TELECOMMUNICATIONS ENGINEER
Draw up tender specifications, coastal MF, HF, VHF stations.
COAXIAL CABLE SYSTEMS ENGINEER
Draw up tender specifications.
FREQUENCY MONITORING SPECIALIST
Study requirements for frequency spectrum management.
OUTSIDE PLANT NETWORK ENGINEER
Analyse and evaluate tenders and inspect contractors' work.
MICROWAVE SYSTEM ENGINEER
Study VHF, UHF and microwave link requirements and recommend appropriate system required.

Positions are offered on bachelor status. Candidates must be qualified to BSc. Age 35+. Leave is approx. 2 months per annum plus 3 economy excursion flights to UK. Telephone Montin (UK) Ltd on 0532-567141 for application form only or mail detailed résumé to Montin (UK) Ltd, Protection House, 83 Bradford Road, Pudsey, West Yorkshire LS28 6AT.

1700

Electronic Engineers salaries up to £13k

VIDEO is one of the World's fastest growing industries, and McMichael Ltd. is in the forefront of advanced video technology. We need young dynamic electronic engineers at all levels to join prestige high technology project teams.


As an analogue or digital video engineer, you would be involved in such projects as, video conferencing, broadcast effects, laser video transmission, precision displays, and other projects.

Our project teams are based at our new research and development Laboratories in Stoke Poges, Bucks., set in 37 acres of ground, with extensive sports and social facilities.

If you are experienced in high speed digital processing or analogue video, write or phone for an application form today.

McMICHAEL LIMITED

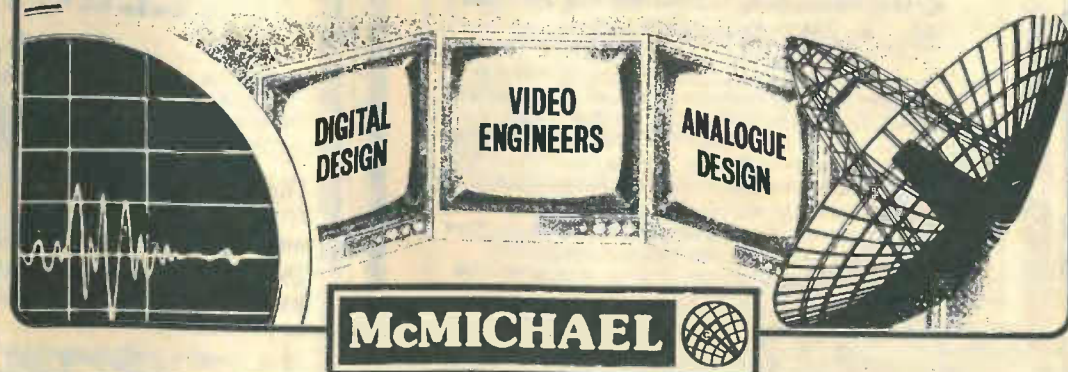Sefton Park, Bells Hill, Stoke Poges, Slough SL2 4DY
Telephone Fulmer (02816) 2777 Telex 849212



ecm

ALWAYS AHEAD WITH THE BEST!

£5,000-£15,000

★ Experienced in:

Mini/Microprocessor Hardware and Software Digital and Analogue circuitry; RF and Microwave techniques?

- ★ **Where does your interest lie:** Image processing; Automation; Datacomms; Radar Nav aids; Mobile Radio; Medical; Telemetry; Simulation; Satcom; Lans?
- ★ **There are opportunities in:** Design; Test; Service; Sales; Systems; Production; Quality and Research.
- ★ **Make your first call count - Contact MIKE GERNAT on 076 384 676/7 (usually until 8 p.m.)**

ELECTRONIC COMPUTER AND MANAGEMENT APPOINTMENTS LIMITED
148-150 High St., Barkway, Royston, Herts SG8 8EG.

(1734)

COMPUTER APPRECIATION

86 High Street, Bletchingley, Redhill, Surrey RH1 4PA. Tel: Godstone (0883) 843221

APPLE II, Europlus microcomputer with 48K memory, integer card, twin disc drives and 12" monitor. software includes VISI CALC, APPLE PILOT and DOS 3.3. Purchased earlier this year and as new..... £385
 APPLE II, Europlus microcomputer with 48K memory, colour card and modulator and disc controller card. With DOS 3.3. As new..... £535
 NCR Model 81-30 commercial microcomputer system. With 64K memory, twin floppy disc drives, VDU and 180 cps matrix printer. System is under 2 years old and cost over £15,000. Full support available from NCR..... £2,500
 RAYTHEON Model PTS 1200. Computer system comprising 64K byte MOS memory, 3 VDU terminals, DIABLO Series 30 2.5 megabyte disc drives, cassette drive and numerous multiplexor and option cards. Processor test set with integral cassette drive is included. The whole system is contained in 2 rack cabinets and was manufactured 1977/78..... £1,900
 RAYTHEON Model 704 16 bit processor. With front panel and 12 KW memory..... £150
 DTC MICROFILE MICROCOMPUTER. Compact 8080 based system with 56K bytes, dual serial interfaces and programmable front panel display. Machines are available with one PERSCI dual drive (Currently \$1,700 each). software includes operating system, powerful BASIC, assembler and letter writer..... £500
 MEMOREX Model 277B VDU. These VDUs are equipped with a network interface operating via a simple coaxial connector. Microprocessor controlled with firmware in 2708 EPROM. Details available shortly..... £35
 LICON VDU Keyboards. High quality attractive cased keyboards with cursor control and programmable functions keypads (total 29 extra keys). Manufactured 1979/80 and either new or nearly new..... £18.50
 IBM Model 1053 Golfball Printer. Compact 15 cps high-reliability mechanical printer in fully refurbished condition. Exactly equivalent to 735 less keyboard. Can be driven from PIA (or similar) with addition of PSU and solenoid driver ICs (details available). Accepts standard office golfballs..... £35
 TEXAS INSTRUMENTS Model 810. High speed (180 cps) matrix printer. With serial interface..... £495

DIABLO Series 30 removable DISC DRIVE. 2.5 megabyte with industry standard interface. These drives are hardware, software and media compatible with RK05, and PDP 11 interfaces are available from XYLOCICS at low cost..... £375
 POWER SUPPLY. For above..... £50
 DOCUMENTATION Model M600L compact card reader. CR11 compatible..... £250
 SYSTEME RK05 compatible controller for PDP 11 UNIBUS. Solid complete with twin RK05 - compatible DIABLO series 30 front loading disc drives and all cables and power supplies..... £385
 PERTEC. Miniature 9-track 800 c.p.i. tape drive..... £190
 LASER ASSOCIATES Nd GLASS LASER. 1.06 micron wavelength. 1-2 J per pulse. A single pulse from this laser burns a hole through a steel rule. Complete with cooling system and output monitor. FULLY OPERATIONAL..... £500
 FACIT Model 4091. 1000 cps capacitive paper tape reader..... £100
 TREND Model HSR 500 optical paper tape reader..... £100
 EMS SYNTHESIZER Model SYNTHI. A complete AKS keyboard and DK2 keyboard. Current (Jan. '81) new price £1,921..... £275
 GESTETNER Model FB12 plain paper photocopier with some supplies..... £150
 NASHUA Model 1215 plain paper photocopier..... £190

Please note:
 * VAT and carriage extra all items
 * Visitors welcome but by appointment please
 * We are keen to bid competitively for all good used equipment

INDEX TO ADVERTISERS AUGUST

Appointments Vacant Advertisements appear on pages 100-111

PAGE	PAGE	PAGE
Acoustical Mfg. Co. Ltd. 51	Faircrest Engineering..... 2	Northern Electronics 24
Active Components 21	Farnell Instruments Ltd. 16, Reader Card	
Albetros (Products) Ltd. 18		
Analogue Associates 2		
Anglia Components 87		
Antex (Electronics) Ltd. Cover iii		
Armon Electronics Ltd. 8		
Audio Electronics 19		
Avel Lindberg (Cotswold Electronics) 4		
Bamber, B. Electronics 18		
Barrie Electronics Ltd. 87		
Black Star Ltd. 12		
Broadfield & Mayco Disposals 24		
Bull, J. (Electrical) Ltd. 90, 91		
Cambridge Kits 84		
Carston Electronics Ltd. 14, 15		
Chiltham Electronics 96		
Chiltham Ltd. 88		
Circuit Services 25		
Clark Masts Ltd. 16		
Clef Products (Electronics) Ltd. 4		
Colomor Electronics Ltd. 22		
Computer Appreciation 112		
Com-Tek (Mid) Ltd. 94		
Darom Supplies 84, 94		
Dataman Designs 23		
Display Electronics 99		
DSN Marketing 93		
Electrical Review Shock Cards 97		
Electronic Brokers Ltd. 3, 5, 7, 9		
Electrovalve Ltd. 20		
Essex Electronics 6		
Japan: Mr. Inatsuki, Trade Meria - IBPA (Japan), B.212, Azabu Heights, 1-5-10 Roppongi, Minato-ku, Tokyo 106. Telephone: (03) 585 0581.		
United States of America: Ray Barnes, IPC Business Press, 205 East 42nd Street, New York, NY 10017 - Telephone: (212) 867-2080. Telex: 238327. Mr Jack Farley Jnr., The Farley Co., Suite 1584, 35 East Walker Drive, Chicago, Illinois 60601 - Telephone: (312) 63074. Mr Victor A. Jauch, Elmatex International, P.O. Box 34607, Los Angeles, Calif. 90034, USA - Telephone (213) 821-8581 - Telex: 18-1059.		
Mr Jack Mentel, The Farley Co., Suite 650, Ranna Building, Cleveland, Ohio 44115 - Telephone: (216) 621 1319. Mr Ray Rickles, Ray Rickles & Co., P.O. Box 2028, Miami Beach, Florida 33140 - Telephone (305) 532 7301. Mr Tim Parks, Ray Rickles & Co., 3116 Maple Drive N.E., Atlanta, Georgia 30305. Telephone: (404) 237 7432. Mike Loughlin, IPC Business Press, 15055, Memorial Ste 119, Houston, Texas 77079 - Telephone (713) 783 8673.		
Canada: Mr Colin H. MacCulloch, International Advertising Consultants Ltd., 915 Carlton Tower, 2 Carlton Street, Toronto 2 - Telephone (416) 364 2269. * Also subscription agents.		

OVERSEAS ADVERTISEMENT

AGENTS:
 France & Belgium: Norbert Hellin, 50 Rue de Chemin Veat, F-9100, Boulogne, Paris.
 Hungary: Mrs Edit, Bajusz, Hungexpo Advertising Agency, Budapest XIV, Varosliget.
 Telephone: 225 008 - Telex: Budapest 22-4525 INTFOIRE
 Italy: Sig C. Epis, Etas-Kompass, S.p.a. - Servizio Estero, Via Mantegna 6, 20154 Milan.
 Telephone: 347051 - Telex: 37342 Kompass.

Japan: Mr. Inatsuki, Trade Meria - IBPA (Japan), B.212, Azabu Heights, 1-5-10 Roppongi, Minato-ku, Tokyo 106. Telephone: (03) 585 0581.
 United States of America: Ray Barnes, IPC Business Press, 205 East 42nd Street, New York, NY 10017 - Telephone: (212) 867-2080. Telex: 238327.
 Mr Jack Farley Jnr., The Farley Co., Suite 1584, 35 East Walker Drive, Chicago, Illinois 60601 - Telephone: (312) 63074.
 Mr Victor A. Jauch, Elmatex International, P.O. Box 34607, Los Angeles, Calif. 90034, USA - Telephone (213) 821-8581 - Telex: 18-1059.

Mr Jack Mentel, The Farley Co., Suite 650, Ranna Building, Cleveland, Ohio 44115 - Telephone: (216) 621 1319.
 Mr Ray Rickles, Ray Rickles & Co., P.O. Box 2028, Miami Beach, Florida 33140 - Telephone (305) 532 7301.
 Mr Tim Parks, Ray Rickles & Co., 3116 Maple Drive N.E., Atlanta, Georgia 30305. Telephone: (404) 237 7432.
 Mike Loughlin, IPC Business Press, 15055, Memorial Ste 119, Houston, Texas 77079 - Telephone (713) 783 8673.
 Canada: Mr Colin H. MacCulloch, International Advertising Consultants Ltd., 915 Carlton Tower, 2 Carlton Street, Toronto 2 - Telephone (416) 364 2269.
 * Also subscription agents.

Printed in Great Britain by QB Ltd., Sheepen Place, Colchester, and Published by the Proprietors IPC ELECTRICAL-ELECTRONIC PRESS LTD., Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS, telephone 01-661 3500. Wireless World can be obtained abroad from the following: AUSTRALIA and NEW ZEALAND: Gordon & Gotch Ltd. INDIA: A. H. Wheeler & Co. CANADA: The Wm. Dawson Subscription Service Ltd, Gordon & Gotch Ltd. SOUTH AFRICA: Central News Agency Ltd. UNITED STATES: Eastern News Distribution Inc., 14th floor, 111 Eighth Avenue, New York, N.Y. 10011.

WE'RE MAKING A STAND FOR BETTER SOLDIERING!

And including it in the **NEW Antex all-in-one pack!**

The new ST4 stand with the big sponge on it's own or in the SK5 and SK6 kits with the new CS and XS low-leakage soldering irons. These new models have tougher, cooler handles, detachable hooks, the well known Antex doubleshaft insulation, the big range of push-on bits and fitted with or without moulded-on safety plugs.



SK5 Soldering Kit
 Contains Model CS230 iron and the ST4 stand. R.R.P. £6.25

SK6 Soldering Kit
 Contains Model XS230 and the ST4 stand. R.R.P. £6.35

SK5-BP and SK6-BP
 Soldering kits fitted with safety plugs.
 SK5-BP kit R.R.P. £7.10
 SK6-BP kit R.R.P. £7.20



Model ST4 Stand.
 R.R.P. £1.60

Model CS-BP - 17 Watts
 Fitted with safety plug 240 volts
 R.R.P. £5.45

Model XS-BP - 25 Watts
 Fitted with safety plug.
 240 volts

Model XS - 25 Watts
 Available for 240 and 115 volts
 R.R.P. £4.70
 50, 24 and 12 volts
 R.R.P. £4.80

Model CS - 17 Watts
 Available for 240 and 115 volts
 R.R.P. £4.60
 50, 24 and 12 volts
 R.R.P. £4.80

Model CCN - 15 Watts
 Ceramic shaft only 240 volts
 R.R.P. £5.00

Model C - 15 Watts
 Stainless steel shaft only.
 240 and 115 volts
 R.R.P. £4.60
 50 and 24 volts
 R.R.P. £4.80

TCSU1 Soldering Station
 for safe 24 volt temperature-controlled miniature soldering iron, variable tip temperature 65 - 430°C, antistatic earth connection, with XSTC or CSTC iron.
 R.R.P. £40.50

Excluding V.A.T. (15%) and Postage & Packing



Made in England


ANTEX (Electronics) Ltd.,
 Mayflower House, Plymouth, Devon.
 Tel: 0752 667377 Telex: 45296

Please send literature and price list to:

Name _____ Address _____

Tel. _____

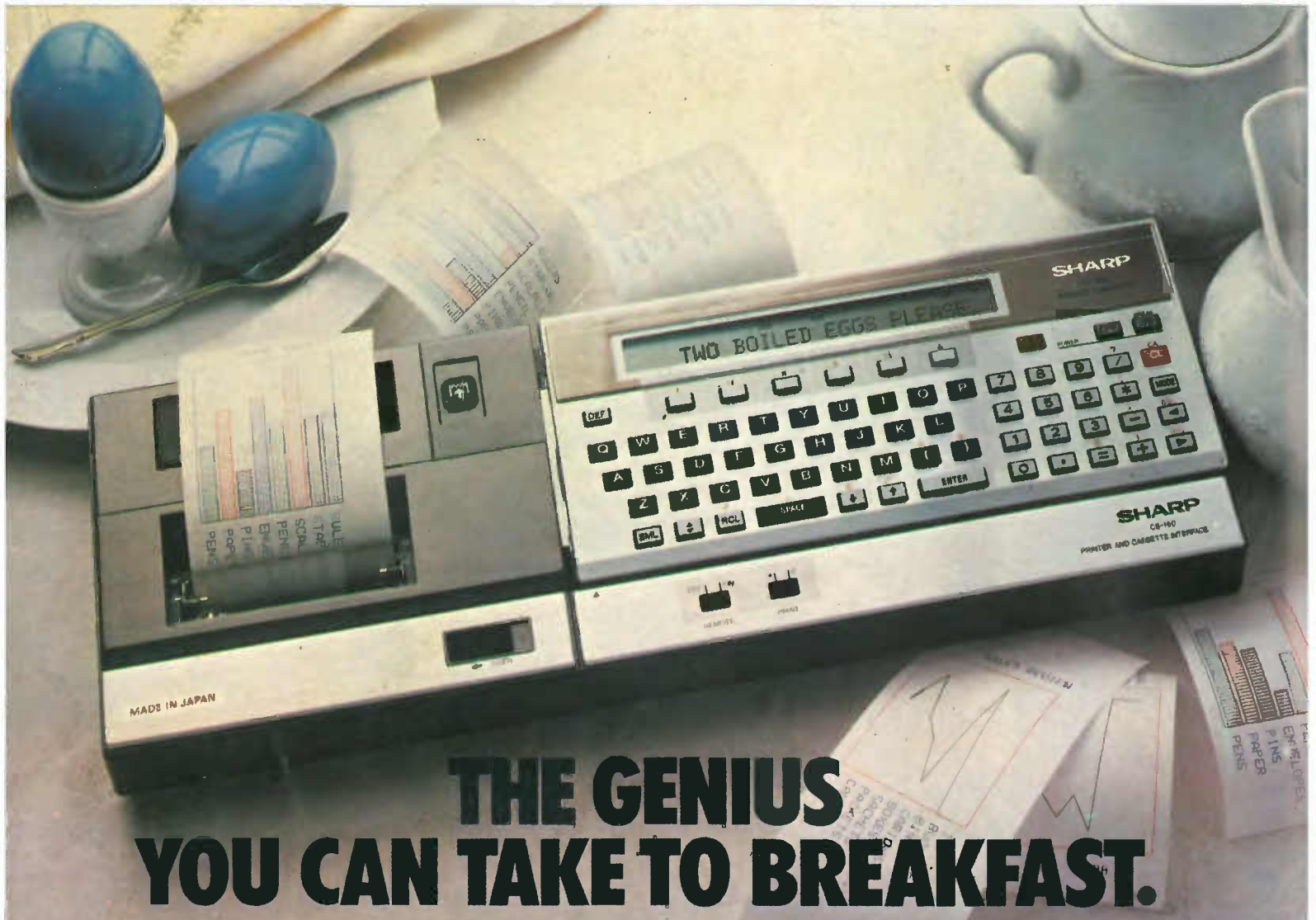Our products are widely distributed by wholesalers and retailers throughout the U.K. Please try your local dealer. w/w/B



THE GENIUS YOU CAN TAKE TO BREAKFAST.

Now, at last, real portable computer power. The new Sharp PC 1500 pocket computer. A pocket-sized genius that will travel with you to conferences, seminars and business breakfasts.

The PC 1500 has the capacity and BASIC language usage that is very nearly that of the desk-size Personal Computer. When fitted with the optional 4-colour graphic printer, it is one of the most powerful pocket computers on earth.

Chores can be handled swiftly and accurately any time of day, wherever you happen to be. Estimates, records and charts of sales, billings and other important data can be re-programmed, calculated and summoned

at the touch of a button. It can even play blackjack, analyse your biorhythms or give you a beeped reminder of a scheduled meeting.

Large memory capacity, up to 11.5K bytes. 4-colour print-out. Six user-programmable keys. The incredible new PC 1500. A revolution in pocket computers.

From Sharp. Where great ideas come to life.

SPECIFICATIONS PC 1500 Pocket Computer

CPU	C-MOS 8-bit CPU
Capacity	ROM: 16K bytes RAM: 3.5K bytes to 11.5K bytes

CE 150 Colour Graphic Printer/Cassette Interface (Optional)

Printing Digits	Standard 18 digits (36, 18, 12, 9, 7, 6, 5, 4 digits selectable)
Printing System	X-Y axis plotter system
Printing colours	Red, blue, green, black
Printing directions	Right, left, up, down
Cassette Interface	Up to two cassette tape recorders can be connected.

Please send details of the Sharp PC 1500

Type of application: _____

Name: _____

Address: _____

The world of
SHARP
where great ideas come to life.

Sharp Electronics (UK) Ltd, Computer Division, Sharp House, Thorp Road, Newton Heath, Manchester M10 9BE. Telephone: 061-205 2333



Design and specifications subject to change without notice.

WW-003 FOR FURTHER DETAILS

www.americanradiohistory.com