

electronics today

INTERNATIONAL

AUGUST 1980 60p



ETI
SPECIAL REPORT:
EMP....THE END OF CIVILISATION?
Nuclear Facts The Government Hasn't Told Us

100W MOSFET Amplifer Project

20 Car Circuits To Build

Video Buyer's Guide

Ultrasonic Alarm

...NEWS...PROJECTS...MICROPROCESSORS...AUDIO...

TRANSCENDENT 2000 SINGLE BOARD SYNTHESIZER

All kits also available as separate packs (e.g. P.C.B., component sets, hardware sets, etc.). Prices in FREE CATALOGUE.

LIVE PERFORMANCE SYNTHESIZER DESIGNED BY CONSULTANT TIM ORR (FORMERLY SYNTHESIZER DESIGNER FOR EMS LIMITED) AND FEATURED AS A CONSTRUCTIONAL ARTICLE IN ELECTRONICS TODAY INTERNATIONAL.

The TRANSCENDENT 2000 is a 3 octave instrument transposable 2 octaves up or down giving an affective 7 octave range. There is portamento, pitch bending, a VCO with shape and pitch modulation, a VCF with both low and high pass outputs and a separate dynamic sweep control, a noise generator and an ADSR envelope shaper. There is also a slow oscillator, a new pitch detector, ADSR repeat, sample and hold, and special circuitry with precision components to ensure tuning stability amongst its many features.

The kit includes fully finished metalwork, fully assembled solid teak cabinet, filter sweep pedal, professional quality components (all resistors either 2% metal oxide or 1/2% metal trim!) and it really is complete — right down to the last nut and bolt and last piece of wire! There is even a 13A plug in the kit — you need buy absolutely no more parts before plugging in and making great music! Virtually all the components are on the one professional quality fibreglass PCB printed with component locations. All the controls mount directly on the main board; all connections to the board are made with connector plugs and construction is so simple it can be built easily in a few evenings by almost anyone capable of neat soldering! When finished you will possess a synthesizer comparable in performance and quality with ready-built units selling for many times the price!

**COMPLETE KIT
ONLY
£168.50 + VAT!**

Comprehensive handbook supplied with all complete kits! This fully describes construction and tells you how to set up your synthesizer with nothing more elaborate than a multi-meter and a pair of ears!



Cabinet size 24.6" x 15.7" x 4.8" (rear) 3.4" (front)


**INCREASED CAPACITY AT OUR BIG NEW FACTORY
MEANS MANY PRICES DOWN! ALL OTHERS FROZEN!**

**WE'VE MOVED!
NEW FACTORY UP!
PRICES DOWN!**

TRANSCENDENT DPX

**DIGITALLY CONTROLLED, TOUCH SENSITIVE, POLYPHONIC, MULTI-VOICE SYNTHESIZER
ANOTHER SUPERB DESIGN BY SYNTHESIZER EXPERT TIM ORR — PUBLISHED IN ETI**

The Transcendent DPX is a really versatile new 5 octave keyboard instrument. There are two audio outputs which can be used simultaneously. On the first there is a beautiful harpsichord or reed sound — fully polyphonic, i.e. you can play chords with as many notes as you like. On the second output there is a wide range of different voices, still fully polyphonic. It can be a straightforward piano or a honky tonk piano or even a mixture of the two! Alternatively you can play strings over the whole range of the keyboard or brass over the whole range of the keyboard or should you prefer — strings on the top of the keyboard and brass at the lower end (the keyboard is electronically split after the first two octaves) or vice versa or even a combination of strings and brass sounds simultaneously. And on all voices you can switch in circuitry to make the keyboard touch sensitive! The harder you press down a key the louder it sounds — just like an acoustic piano. The digitally controlled multiplexed system makes practical touch sensitivity with the complex dynamics law necessary for a high degree of realism. There is a master volume and tone control, a separate control for the brass sounds and also a vibrato circuit with variable depth control together with a variable delay control so that the vibrato comes in only after waiting a short time after the note is struck for even more realistic string sounds.

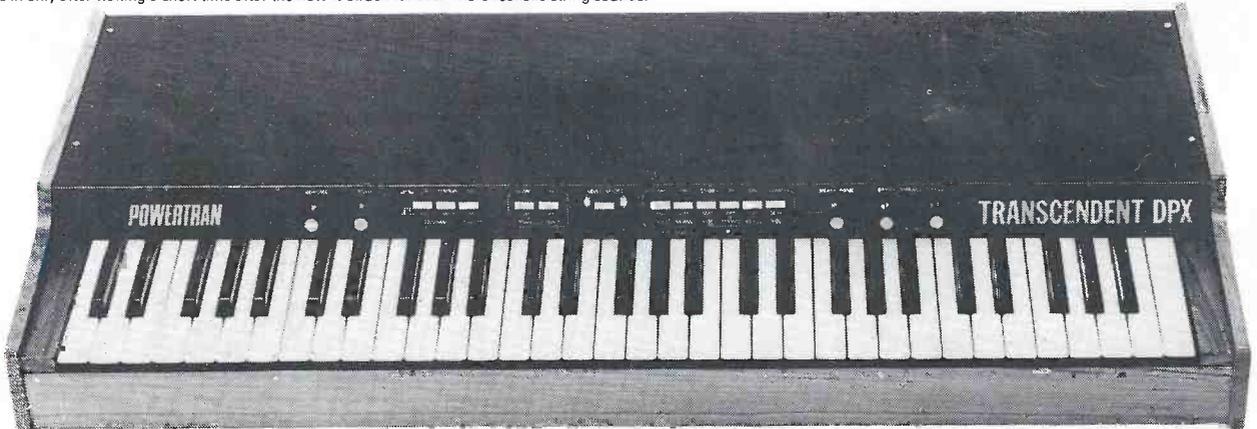

Cabinet size 36.3" x 15.0" x 5.0" (rear) 3.3" (front)

COMPLETE KIT ONLY £299.00 + VAT!

To add interest to the sounds and make them more natural there is a chorus/ensemble unit which is a complex phasing system using CCD (charge coupled device) analogue delay lines. The overall effect of this is similar to that of several acoustic instruments playing the same piece of music. The ensemble circuitry can be switched in with either strong or mild effects.


As the system is based on digital circuitry digital data can be easily taken to and from a computer (for storing and playing back accompaniments with or without pitch or key change, computer composing etc., etc.)

Although the DPX is an advanced design using a very large amount of circuitry, much of it very sophisticated, the kit is mechanically extremely simple with excellent access to all the circuit boards which interconnect with multiway connectors, just four of which are removed to separate the keyboard circuitry and the panel circuitry from the main circuitry in the cabinet.

The kit includes fully finished metalwork, solid teak cabinet, professional quality components (all resistors 2% metal oxide), nuts, bolts, etc., even a 13A plug — you need buy absolutely no more parts before plugging in and making great music! When finished you will possess an instrument comparable in performance and quality with ready-built units selling for over £1,200!

POWERTRAN

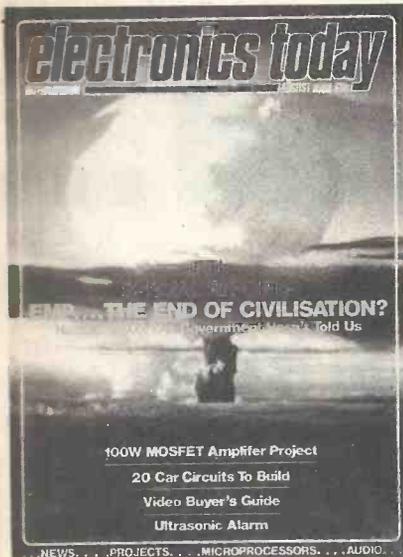**ORDERING INFORMATION AND MORE KITS
INCLUDING THE BLACK HOLE ON PAGE 8**



electronics today

AUGUST 1980 VOL 9 NO 8 INTERNATIONAL

FEATURES


- | | | |
|--------------------|----|---|
| NEWS | 9 | If its worth reading its here. |
| FIVE FIVE FIVE! | 16 | The ultimate way to review a book.... |
| EMP—SPECIAL REPORT | 24 | You should know about this. |
| AUDIOPHILE | 31 | Heavy amps and tiny cassettes. |
| MICROFILE | 36 | The final program? |
| TECH—TIPS | 39 | Talking to yourselves again! |
| EDDY CURRENTS | 45 | A distinctly backward effect. |
| VIDEO TODAY | 51 | Full market details and forecasts. |
| SPOT DESIGNS | 60 | New series of tried and tested circuits |

PROJECTS

- | | | |
|-------------------|-----|------------------------------------|
| 100W AMPLIFIER | 64 | Its MOS and its the best. |
| LOGIC TESTER | 73 | Simple and versatile testing aid. |
| VCA MODULE | 78 | Superb sound shaper. |
| ULTRASONIC ALARM | 86 | Doppler out the burglars. |
| CAPACITANCE METER | 93 | Measuring up to your capabilities? |
| FOIL PATTERNS | 100 | Building begins here. |

INFORMATION

- | | | |
|-----------------|----|----------------------------|
| NEXT MONTHS ETI | 15 | The lowdown on September. |
| BOOK SERVICE | 49 | Finest print in town. |
| SUBSCRIPTIONS | 84 | Get the future free. |
| ETIPRINTS | 98 | The only way to get board. |

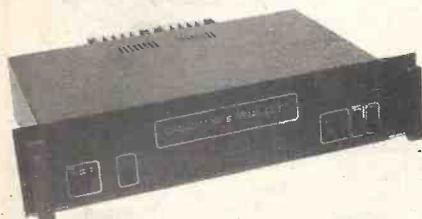

100MOSW? p.64



Sound protection p.86

OVERSEAS EDITIONS

- AUSTRALIA : Roger Harrison
Editor
- CANADA : Halvor Moorshead
Editor
- GERMANY : Udo Wittig
Editor
- HOLLAND : Anton Kriegsman
Editor



Member of the
Audit Bureau
of Circulation

EDITORIAL AND ADVERTISEMENT OFFICE

145 Charing Cross Road, London WC2H 0EE. Telephone 01-437 1002/3/4/5

- | | |
|----------------------|-----------------------------|
| Ron Harris B.Sc. | Editor |
| Ian Graham B.Sc. | Assistant Editor |
| Tina Boylan | Editorial Assistant |
| Diego M. Rincon | Art Director |
| Paul Edwards | Drawing Office Manager |
| Ray Marston | Project Editor |
| Christopher Surgenor | Group Advertisement Manager |
| Steven Rowe | Advertisement Manager |
| T.J. Connell | Managing Director |

PUBLISHED BY
DISTRIBUTED BY

Modmags Ltd., 145 Charing Cross Road, WC2
Argus Distribution Ltd. (British Isles)
12-18 Paul Street, London
Gordon & Gotch Ltd. (Overseas)
QB Limited, Colchester



PRINTED BY

Electronics Today is normally published on the first Friday in the month preceding cover date.
Distributed by: Argus Distribution Ltd, 12-18 Paul Street, London. 01-247 8233.
Printed by: QB Printers Ltd, Colchester.

©MODMAGS LTD 1980. All material is subject to worldwide copyright protection. All reasonable care is taken in the preparation of the magazine, contents, but the publishers cannot be held responsible for errors legally. Where mistakes do occur, a correction will normally be published as soon as possible afterwards. All prices and data contained in advertisements are accepted by us in good faith as correct at time of going to press. Neither the advertisers nor the publishers can be held responsible, however, for any variations affecting price or availability which may occur after the publication has closed for press.

Subscription Rates : UK £10 including postage. Airmail and other rates upon application to ETI Subscriptions Service, PO Box 35, Bridge Street, Hemel Hempstead, Herts.


Simply ahead...

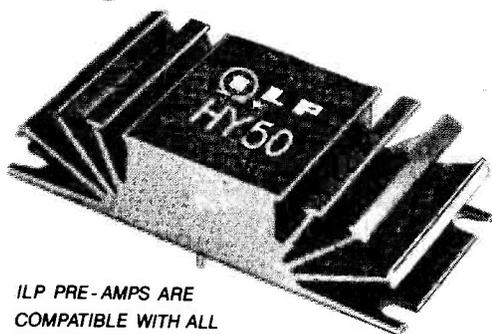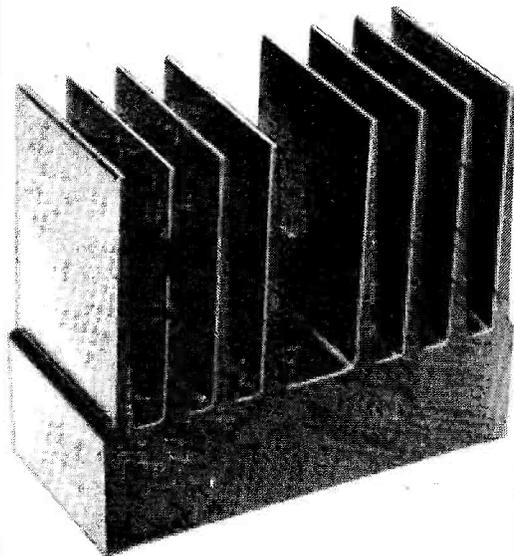

ILP PRE-AMPS ARE
COMPATIBLE WITH ALL
ILP POWER AMPS AND PSUs

POWER AMPLIFIERS

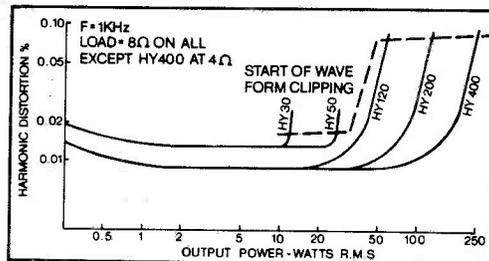ILP Power Amplifiers are encapsulated within heatsinks designed to meet total heat dissipation needs. They are rugged and made to last a lifetime. Advanced circuitry ensures their suitability for use with the finest loudspeakers, pickups, tuners, etc. using digital or analogue sound sources.



Model	Output Power R.M.S.	Distortion Typical at 1KHz	Minimum Signal/Noise Ratio	Power Supply Voltage	Size in mm	Weight in gms	Price + V.A.T.
HY30	15 W into 8 Ω	0.02%	100 dB	-20 -0+ +20	105x50x25	155	£6.34 + 95p
HY50	30 W into 8 Ω	0.02%	100 dB	-25 -0+ +25	105x50x25	155	£7.24 + £1.09
HY120	60 W into 8 Ω	0.01%	100 dB	-35 -0+ +35	114x50x85	575	£15.20 + £2.28
HY200	120 W into 8 Ω	0.01%	100 dB	-45 -0+ +45	114x50x85	575	£18.44 + £2.77
HY400	240 W into 4 Ω	0.01%	100 dB	-45 -0+ +45	114x100x85	1.15Kg	£27.68 + £4.15

Load impedance - all models 4 Ω - ∞
Input sensitivity - all models 500 mV
Input impedance - all models 100K Ω
Frequency response - all models 10Hz - 45 KHz - 3dB

POWER SUPPLY UNITS



AVAILABLE ALSO FROM WATFORD ELECTRONICS, MARSHALLS AND CERTAIN OTHER SELECTED STOCKISTS.

ILP Power Supply Units with transformers made in our own factory are designed specifically for use with ILP power amplifiers and are in two basic forms - one with circuit panel mounted on conventionally styled laminated transformer, for smaller PSU's - in the other, for larger PSU's, ILP toroidal transformers are used which are half the size and weight of laminated equivalents, are more efficient and have greatly reduced radiation.

PSU 30 $\pm 15V$ at 100mA to drive up to 12 x HY6 or 6 x HY66 £4.50 + £0.68 VAT

THE FOLLOWING WILL ALSO DRIVE ILP PRE-AMPS

PSU 36 for 1 or 2 HY30's £8.10 + £1.22 VAT

PSU 50 for 1 or 2 HY50's £8.10 + £1.22 VAT

PSU 60 with toroidal transformer for

1 HY 120 £9.75 + £1.46 VAT

PSU 70 with toroidal transformer for 1 or

2 HY120's £13.61 + £2.04 VAT




PSU 90 with toroidal transformer for

1 HY 200 £13.61 + £2.04 VAT

PSU 180 with toroidal transformer for

1 HY400 or 2 x HY200 £23.02 + £3.45 VAT

this time with two new pre-amps

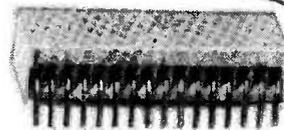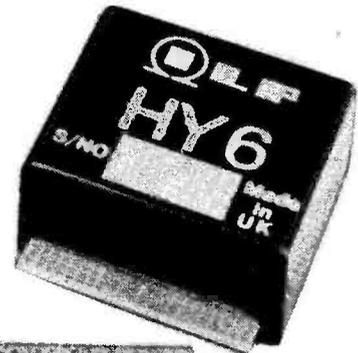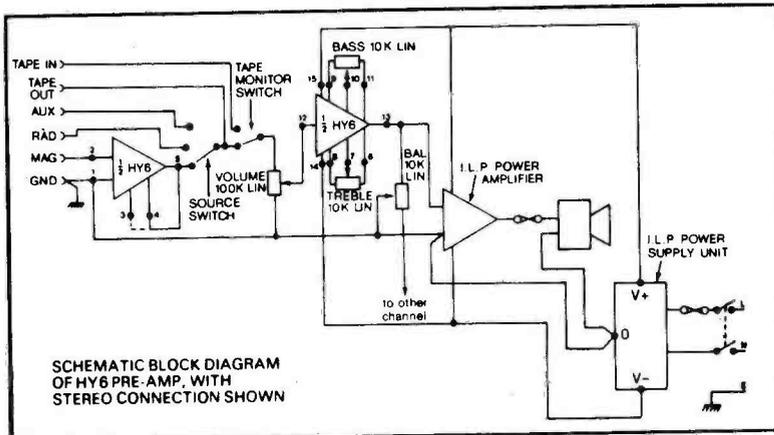

HY6 mono HY66 stereo

When ILP add a new design to their audio-module range, there have to be very special reasons for doing so. You expect even better results. We have achieved this with two new pre-amplifiers - HY6 for mono operation, HY66 for stereo. We have simplified connections, and improved performance figures all round. Our new pre-amps are short-circuit and polarity protected; mounting boards are available to simplify construction.

Sizes - HY6 - 45 x 20 x 40 mm. HY66 90 x 20 x 40 mm. Active Tone Control circuits provide ± 12 dB cut and boost. Inputs Sensitivity - Mag. PU - 3mV. Mic - selectable 1-12mV. All others 100mV. Tape O/P - 100mV. Main O/P - 500mV. Frequency response - D.C. to 100kHz - 3dB



HY6 mono

£5.60

+ VAT 84p

HY66 stereo

£10.60

+ VAT £1.59

Connectors included

B6 Mounting Board

78p + 12p VAT

B66 Mounting Board

99p + 15p VAT

- LOW DISTORTION - Typically 0.005%
- S/N RATIO - Typically 90 dB (Mag. P.U. - 68 dB).
- HIGH OVERLOAD FACTOR - 38 dB on Mag. P.U.
- LATEST DESIGN HIGH QUALITY CONNECTORS.
- REQUIRE ONLY POTS, SWITCHES, PLUGS AND SOCKETS.
- COMPATIBLE WITH ALL ILP POWER AMPS AND PSUs.
- NEEDS ONLY UNREGULATED POWER SUPPLY $\pm 15V$ to $\pm 50V$.

NO QUIBBLE
5 YEAR GUARANTEE
7-DAY DESPATCH ON ALL ORDERS
BRITISH DESIGN AND MANUFACTURE
FREEPOST SERVICE
see below

* ALL U.K. ORDERS DESPATCHED POST PAID HOW TO ORDER, USING FREEPOST SYSTEM

Simply fill in order coupon with payment or credit card instructions. Post to address as below but do not stamp envelope - we pay postage on all letters sent to us by readers of this journal.



FREEPOST 4 Graham Bell House, Roper Close,
Canterbury, Kent CT2 7EP.
Telephone (0227) 54778 Telex 965780

Please supply

..... Total purchase price £.....

Enclose Cheque Postal Orders International Money Order

Please debit my Access/Barclaycard Account No.

NAME

ADDRESS

Signature

CHROMATHEQUE 5000

POWERTRAN

5 CHANNEL LIGHTING EFFECTS SYSTEM

COMPLETE KIT

ONLY


£49.50 + VAT!



Panel size 19.0" x 3.5". Depth 7.3"

This versatile system featured as a constructional article in ELECTRONICS TODAY INTERNATIONAL has 5 frequency channels with individual level controls on each channel. Control of the lights is comprehensive to say the least. You can run the unit as a straightforward sound-to-light or have it strobe all the lights at a speed dependent upon music level or front panel control or use the internal digital circuitry which produces some superb random and sequencing effects. Each channel handles up to 500W and as the kit is a single board design wiring is minimal and construction very straightforward.

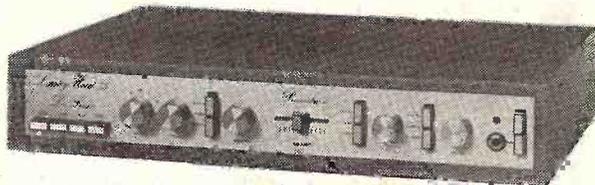Kit includes fully finished metalwork, fibreglass PCB controls, wire, etc. — Complete right down to the last nut and bolt!




DE LUXE EASY TO BUILD LINSLEY HOOD 75W STEREO AMPLIFIER £99.30 + VAT

This easy to build version of our world-wide acclaimed 75W amplifier kit based upon circuit boards interconnected with gold plated contacts resulting in minimal wiring and construction delightfully straightforward. The design was published in Hi-Fi News and Record Review and features include rumble filter, variable scratch filter, versatile tone controls and tape monitoring whilst distortion is less than 0.01%.

Above 2 kits are supplied with fully finished metalwork, ready assembled high quality teak veneer cabinet, cable, nuts, bolts, etc and full instructions—in fact everything!

All kits also available as separate packs (eg PCB, component sets, hardware sets etc). Prices in our FREE CATALOGUE.

Matching Tuners. See our FREE CATALOGUE

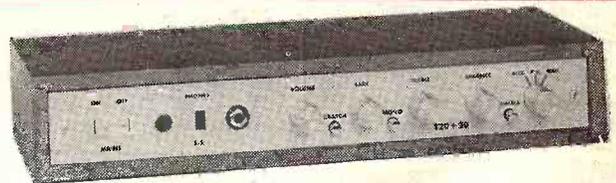

T20+20 20W STEREO AMPLIFIER £33.10 + VAT

This kit, based upon a design published in Practical Wireless, uses a single printed circuit board and offers at very low cost, ease of construction and all the normal facilities found on quality amplifiers. A 30-watt version of this kit (T30+30) is also available for £38.40 + VAT.


BLACK HOLE

MUSIC EFFECTS DEVICE AS FEATURED IN ELECTRONICS TODAY INTERNATIONAL.

The BLACK HOLE designed by Tim Orr, is a powerful new musical effects device for processing both natural and electronic instruments, offering genuine VIBRATO (pitch modulation) and a CHORUS mode which gives a 'spacey' feel to the sound achieved by delaying the input signal and mixing it back with the original. Notches (HOLES), introduced in the frequency response, move up and down as the time delay is modulated by the chorus sweep generator. An optional double chorus mode allows exciting antiphase effects to be added. The device is floor standing with foot switch controls, LED effect selection indicators, has variable sensitivity input, has high signal/noise ratio obtained by an audio compander and is mains powered — no batteries to change! Like all our kits everything is provided including a highly superior, rugged steel, beautifully finished enclosure.

COMPLETE KIT ONLY £49.80 + VAT (SINGLE DELAY LINE SYSTEM)

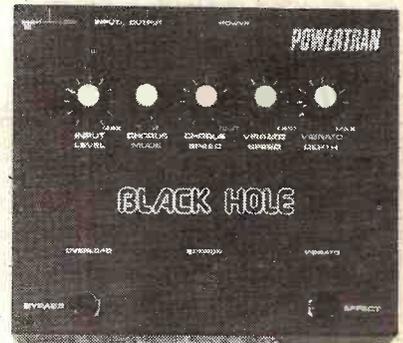
De Luxe version (dual delay line system) also available for £59.80 + VAT



MPA 200 100 WATT (rms into 8Ω) MIXER / AMPLIFIER

Featured as a constructional article in ETI, the MPA 200 is an exceptionally low priced — but professionally finished — general purpose high power amplifier. It features adaptable input mixer which accepts a wider range of sources such as microphone, guitar, etc. There are wide range tone controls and a master volume control. Mechanically the MPA 200 is simplicity itself with minimal wiring needed making construction very straightforward.

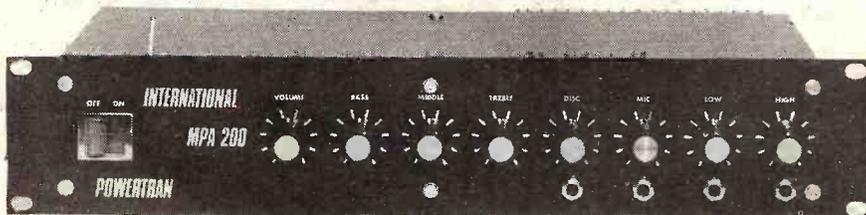The kit includes fully finished metalwork, fibreglass PCBs, controls, wire, etc. — complete down to the last nut and bolt.



Panel size 19.0" x 3.5". Depth 7.3"

COMPLETE KIT ONLY

£49.90 + VAT!

MATCHES THE CHROMATHEQUE 5000. PERFECTLY!

PRICE STABILITY: Order with confidence. Irrespective of any price changes we will honour all prices in this advertisement until September 30, 1980, if this month's advertisement is mentioned with your order. Errors and VAT rate changes excluded.

EXPORT ORDERS: No VAT. Postage charged at actual cost plus £1 handling and documentation.

U.K. ORDERS: Subject to 15% surcharge for VAT. No charge is made for carriage, or at current rate if changed.

SECURICOR DELIVERY: For this optional service (U.K. mainland only) add £2.50 (VAT inclusive) per kit.

SALES COUNTER: If you prefer to collect kit from the factory, call at Sales Counter, Open 9 a.m. - 12 noon, 1-4 30 p.m. Monday-Thursday.

NEW FACTORY ON SAME INDUSTRIAL ESTATE ADDRESS AND PHONE NUMBER UNCHANGED

OUR CATALOGUE IS FREE! WRITE OR PHONE NOW!

POWERTRAN ELECTRONICS

PORTWAY INDUSTRIAL ESTATE
ANDOVER, HANTS SP10 3NM

ANDOVER
(STD 0264) 64455

DIGEST

Design Cadet

Racal-Redac has introduced an interactive PCB design aid which, they claim, should pay its way even if only five boards are designed every year.


The user selects the required component symbols, which are displayed on a VDU. The machine, called Cadet, then shows the shortest straight-line routes between the components. The operator can then move the components round to find the best position with Cadet checking for track crossover and automatically minimising inter-connection length.

Cadet can store designs on cartridges, from which Redac can produce artwork and a prototype PCB. The system (screen, keyboard, electronic tablet and stylus) enables a designer to produce three times the number of PCB designs possible manually.

Cadet costs £20,000 from Racal-Redac, Tewkesbury, Gloucestershire GL20 8HE.

Fan-Tastic

Inspectron Limited of Foundry Lane, Horsham, West Sussex have announced their high performance, sub-miniature fan using a coreless motor, designed mainly for cooling electronic equipment. The fans are available to operate on 12 or 5 V DC with which fan motor speed is approximately 14,500 RPM, with an air flow of about 450 litres/minute. Current consumption is 150 mA and operation is virtually noiseless. The total weight of the fan is 56 g and two types of mounting are available; plain cylindrical for small ducts and rubber fixing brackets, and a flange fitting type for fitting direct to bulkheads or other flat surfaces.

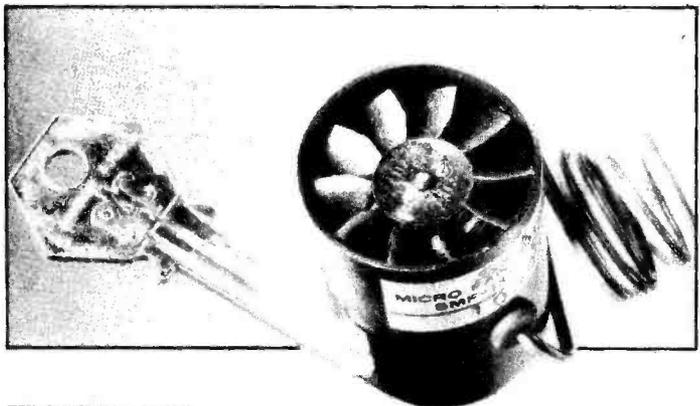

Rank Xerox, the first 21 years

Rank Xerox, the name synonymous with photocopiers, have just launched six new products to mark their 21st anniversary in the business. Twenty-one years ago, the 914, the world's first office copier, made its entrance. It still looks remarkably up-to-date. Indeed, a few are still in service.

The new models amply demonstrate that Rank Xerox make more than photocopiers. The 485 is a facsimile transceiver capable of transmitting documents all over the country (the world!) along the telephone lines, overcoming the expense and time involved in sending documents by post. Moreover, it's fully compatible with its forerunner, the 400.

The 850 word processing system is a step up from its predecessor, the 800. The 800 is capable of typing out 350 words a minute as a straightforward playback typewriter and can store its input on magnetic card or tape. The 850 will also display the text line by line (on a display on the typewriter itself) or page by page on a VDU.

Even their new photocopiers are not just copiers. During a demonstration one model took a few dozen pages of text, turned each one over, copied it and returned it, in order, to a collection tray. The number of copies selected were then fed to a sorter and even stapled, if necessary.

Xerox are now working with the Digital Equipment Corpora-

tion and Intel to develop the Ethernet network. This will link most of the electronic information equipment of tomorrow's office together, from a mainframe computer or a micro to a word processor to an intelligent copier to a data terminal, etc. Ethernet will allow information exchange at ten million bits per second. Global information exchange should be complete with Xerox's work, with its subsidiary Western Union International, on satellite communication via the Xten network.

Happy birthday Rank Xerox.

High Jump

The new model WK-1 wire jumper kit from CSC gives an easy means of linking up electronic components and circuits on test sockets, bus strips or solderless breadboard systems. The kit contains pre-cut, pre-stripped and pre-formed lengths of solid insulated wire (AWG 22) in 14 colour-coded lengths from 0.1 inch to 4 inches. Each length of wire has additional 0.25 inch ends bent at 90°. Twenty-five pieces of each length are supplied with a plastic compartmented case and the price is £5 excluding VAT plus postage and packing from Continental Specialties Corporation, Shire Hill Industrial Estate, Saffron Waldon, Essex CB11 3AQ.

Thin Time for Watches

A new addition to the Concord Delirium range of wrist-watches caused quite a stir at the Basle Fair. The Concord Delirium IV is the first watch to break the 1 mm barrier. It's 0.98 mm thick.

The Swiss design team have achieved the super thin profile by using a new battery (the world's smallest), a new motor and quartz tuning fork and microprocessor controlled time-setting. Accuracy

is quoted at ten seconds per month. The new battery, only 0.8 mm thick, should power the watch for more than a year.

If, as the Director of Concord Watch Company believes, 'thinness always serves as an indicator of technical superiority in the watch industry' the Delirium IV should be hard to beat. However, we don't as yet have any news of the price. With a solid gold backplate and face (not to mention the world's smallest battery) this is one watch you won't throw away when the battery lies down and dies.

It's faster and more thorough than classroom learning; you pace yourself and answer questions on each new aspect as you go. This gives rare satisfaction - you know that you are really learning and without mindless drudgery. With a good self-instruction course you become your own best teacher.

Understand Digital Electronics


In the years ahead digital electronics will play an increasing part in your life. Calculators and digital watches mushroomed in the 1970's - soon we will have digital car instrumentation, cash cards, TV messages from friends and electronic mail. After completing these books you will have broadened your career prospects and increased your knowledge of the fast-changing world around you.

DIGITAL COMPUTER LOGIC AND ELECTRONICS £7.00

This course is designed as an introduction to digital electronics and is written at a pace that suits the raw beginner. No mathematical knowledge is assumed other than the use of simple arithmetic and decimals and no electronic knowledge is expected at all. The course moves painstakingly through all the basic concepts of digital electronics in a simple and concise fashion: questions and answers on every page make sure that the points are understood.

Everyone can learn from it - students, engineers, hobbyists, housewives, scientists. Its four A4 volumes consist of:

- Book 1** Binary, octal and decimal number systems; conversion between number systems; conversion of fractions; octal-decimal conversion tables.
- Book 2** AND, OR gates; inverters; NOR and NAND gates; truth tables; introduction to Boolean algebra.
- Book 3** Positive ECL; De Morgans Laws; designing logic circuits using NOR gates, dual-input gates.
- Book 4** Introduction to pulse driven circuits; R-S and J-K flip flops; binary counters; shift registers; half-adders.

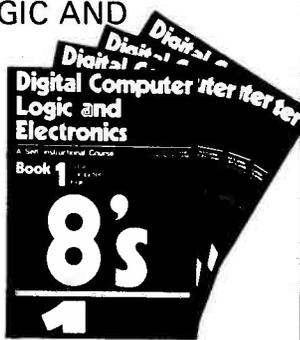

DESIGN OF DIGITAL SYSTEMS £12.50

This course takes the reader to real proficiency. Written in a similar question and answer style to Digital Computer Logic and Electronics, this course moves at a much faster pace and goes into the subject in greater depth. Ideally suited for scientists or engineers wanting to know more about digital electronics, its six A4 volumes lead step by step through number systems and Boolean algebra to memories, counters and arithmetic circuits and finally to an understanding of calculator and computer design.

- Book 1** Octal, hexadecimal and binary number systems; conversion between number systems; representation of negative numbers; complementary systems; binary multiplication and division.
- Book 2** OR and AND functions; logic gates; NOT, exclusive-OR, NAND, NOR and exclusive-NOR functions; multiple input gates; truth tables; De Morgans Laws; canonical forms; logic conventions; karnaugh mapping; three state and wired logic.
- Book 3** Half adders and full adders; subtractors; serial and parallel adders; processors and arithmetic logic units (ALUs); multiplication and division systems.
- Book 4** Flip flops; shift registers; asynchronous and synchronous counters; ring, Johnson and exclusive-OR feedback counters; random access memories (RAMs) and read only memories (ROMs).
- Book 5** Structure of calculators; keyboard encoding; decoding display data; register systems; control unit; program ROM; address decoding; instruction sets; instruction decoding; control programme structure.
- Book 6** Central processing unit (CPU); memory organization; character representation; program storage; address modes; input/output systems; program interrupts; interrupt priorities; programming, assemblers; computers; executive programs; operating systems and time sharing.



Flow Charts and Algorithms


are the essential logical procedures used in all computer programming and mastering them is the key to success here as well as being a priceless tool in all administrative areas - presenting safety regulations, government legislation, office procedures etc.

THE ALGORITHM WRITER'S GUIDE £4.00

explains how to define questions, put them in the best order and draw the flow chart, with numerous examples.

Microcomputers are coming - ride the wave! Learn to program.

Millions of jobs are threatened but millions more will be created. Learn BASIC - the language of the small computer and the most easy-to-learn computer language in widespread use. Teach yourself with a course which takes you from complete ignorance step-by-step to real proficiency with a unique style of graded hints. In 60 straightforward lessons you will learn the five essentials of programming: problem definition, flowcharting, coding the program, debugging, clear documentation. Harder problems are provided with a series of hints so you never sit glassy-eyed with your mind a blank. You soon learn to tackle really tough tasks such as programs for graphs, cost estimates, compound interest and computer games.

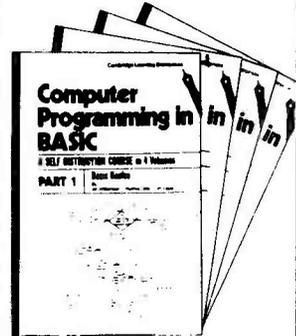

COMPUTER PROGRAMMING IN BASIC £9.00

- Book 1** Computers and what they do well; READ, DATA, PRINT, powers, brackets, variable names; LET; errors; coding simple programs.
- Book 2** High and low level languages; flowcharting; functions; REM and documentation; INPUT, IF...THEN, GO TO; limitations of computers, problem definition.
- Book 3** Compilers and interpreters; loops, FOR...NEXT, RESTORE; debugging; arrays; bubble sorting; TAB.
- Book 4** Advanced BASIC; subroutines; string variables; files; complex programming; examples; glossary.

THE BASIC HANDBOOK £11.50

This best-selling American title usefully supplements our BASIC course with an alphabetical guide to the many variations that occur in BASIC terminology. The dozens of BASIC 'dialects' in use today mean programmers often need to translate instructions so that they can be RUN on their system. The BASIC Handbook is clear, easy to use and should save hours of your time and computer time. A must for all users of BASIC throughout the world.

FORTRAN COLORING BOOK £5.40

"If you have to learn Fortran (and no one actually wants to assimilate it for the good of the soul) buy this book. Forget the others - this one is so good it will even help you understand the standard, dense, boring, unintelligible texts." *New Scientist*.

A.N.S. COBOL £4.40

The indispensable guide to the world's No. 1 business language. After 25 hours with this course, one beginner took a consulting job, documenting oil company programs and did invaluable work from the first day. Need we say more?

GUARANTEE - No risk to you

If you are not completely satisfied your money will be refunded on return of the books in good condition.

Please send me:-

-Digital Computer Logic & Electronics @ £7.00
-Design of Digital Systems @ £12.50
-Algorithm Writer's Guide @ £4.00
-Computer Programming in BASIC @ £9.00
-BASIC Handbook @ £11.50
-Fortran Coloring Book @ £5.40
-A.N.S. Cobol @ £4.40

FOUR WAYS TO PAY

- 1) A U.K. cheque or a U.K. postal order (Not Eire or overseas)
- 2) A bank draft, in sterling on a London bank (available at any major bank)
- 3) Please charge my Access/M.Ch Barclay/TrustC/Visa Am. Exp Diners
- 4) Or phone us with these credit card details - 0480 67446 (ansaphone) 24 hour service


Card No. Signed.....
THESE PRICES COVER THE COST OF SURFACE MAIL WORLDWIDE. AIRMAIL:
 Eur. N.A.F. Mid.E. add 1/2 to price of books: Jpn. Aus. N.Z. Pctc add 1/2; elsewhere add 1/2

Name

Address


U.K. Delivery: up to 21 days (or send 50p for 1st cl.p.)
 Cambridge Learning Enterprises, Unit 13, Rivermill Site, FREEPOST, St. Ives, Huntingdon, Cambs. PE17 4BR England.
 Proprietors: Drayridge Ltd., address as above. Reg. in Eng. No. 1328762

PCB FOIL PATTERNS

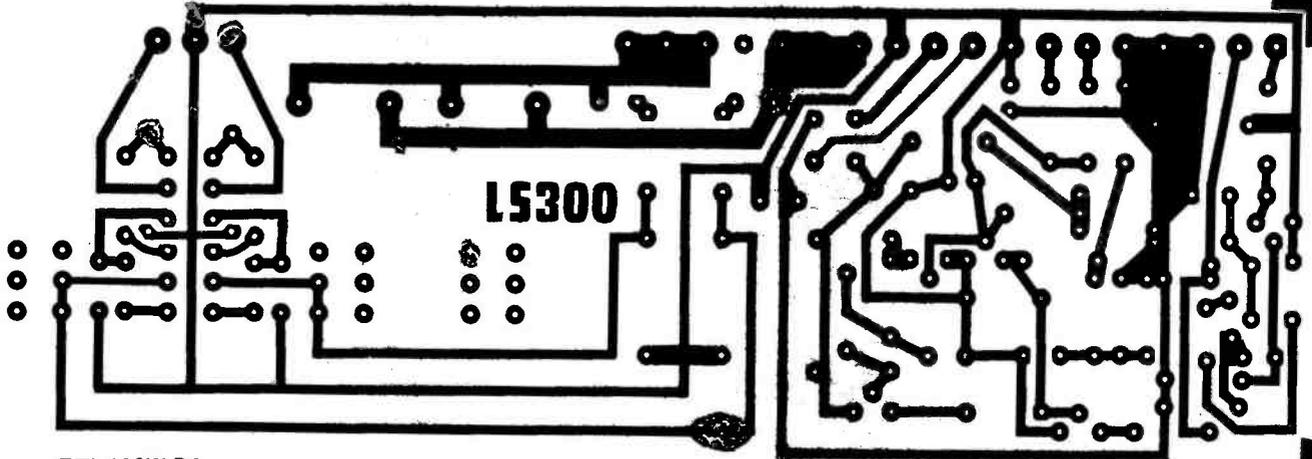

ETI 100W PA



© AMBIT

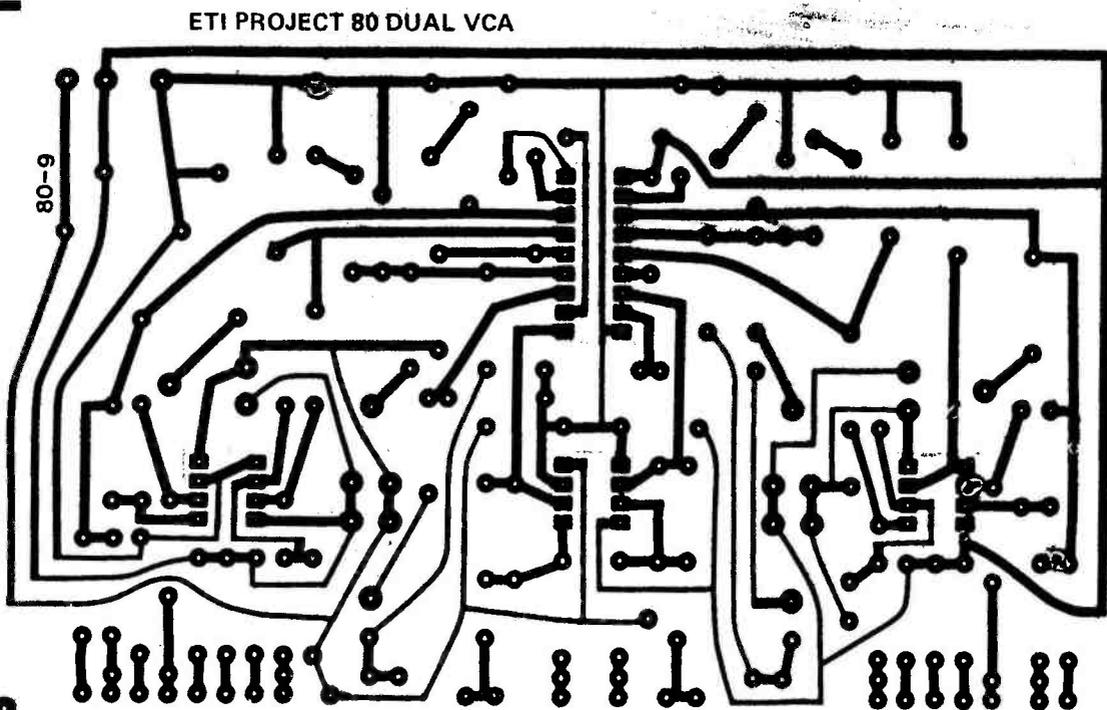

ETI PROJECT 80 DUAL VCA


© DIGISOUND

ETI alarm

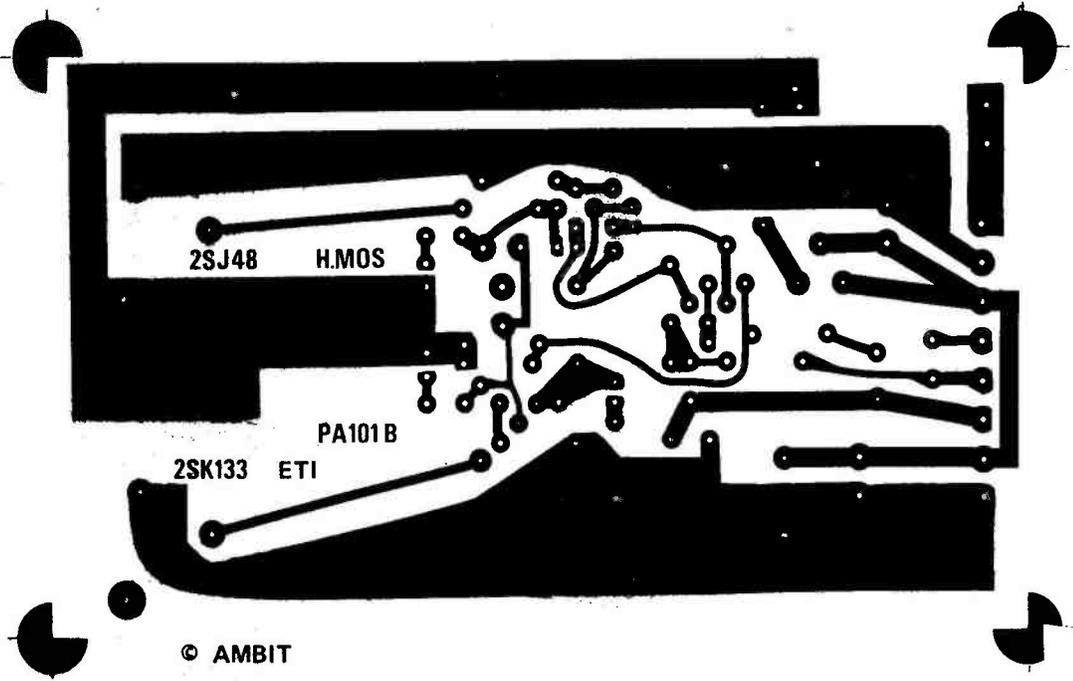
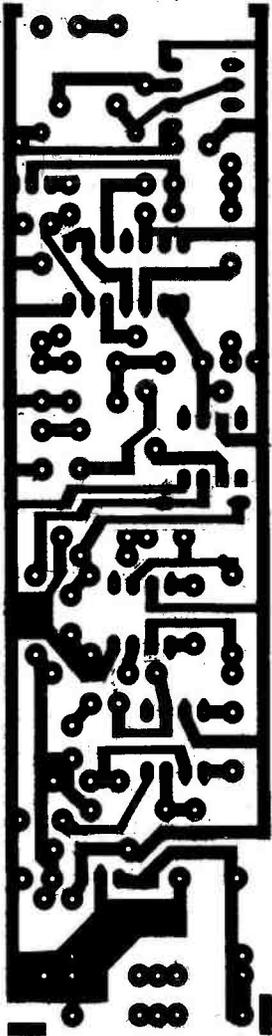


The Ambit Power Amplifier board (above) and Bar Graph Monitor board (below).

ETI BGM

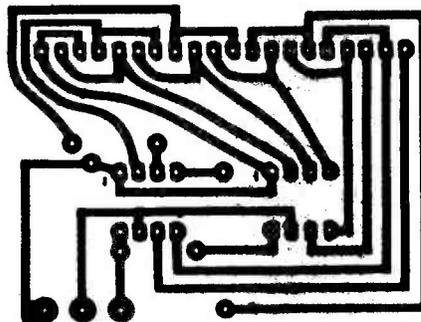

© AMBIT

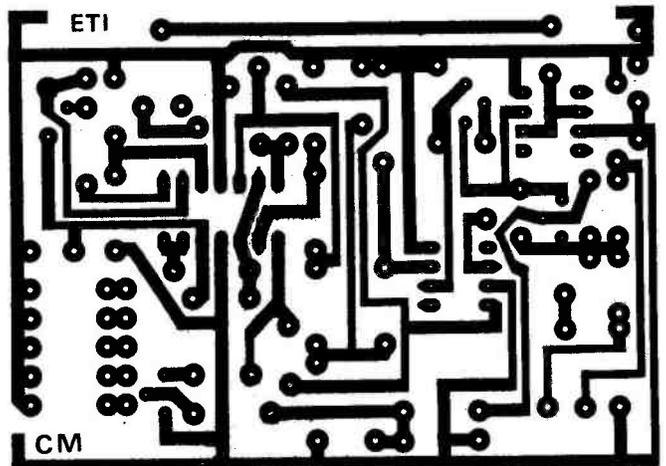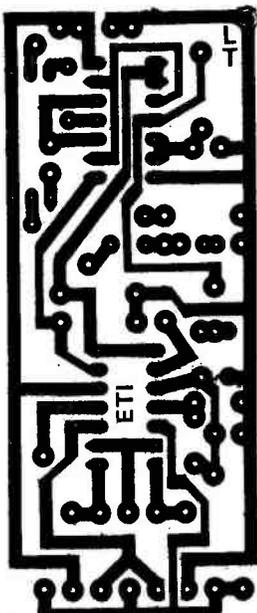

Foil Patterns for the Capacitance Meter (right) and the CMOS Logic Tester (left).

DIGISOUND

KITS AND SPECIAL PRODUCTS FOR ELECTRONIC MUSIC

I.C.s FROM SOLID STATE MICROTECHNOLOGY

SSM 2020 Dual Voltage Controlled Amplifier	365p
SSM 2030 Voltage Controlled Oscillator	485p
SSM 2040 Voltage Controlled Four Stage Filter	485p
SSM 2050 Voltage Controlled Transient Generator	365p

Complete set of Application Notes and Specifications for the above at 50p post paid, or 30p if added to an order for components. No VAT on data and stamps will be accepted in payment.

I.C.s FROM CURTIS ELECTROMUSIC SPECIALTIES

CEM 3310 Voltage Controlled Transient Generator	400p
CEM 3320 Voltage Controlled Four Stage Filter	390p
CEM 3330 Dual Voltage Controlled Amplifier	400p
CEM 3335 Dual Voltage Controlled Amplifier (Exp. only)	380p
CEM 3340 Voltage Controlled Oscillator	600p


Complete sets of Application Notes and Specification for the above at 50p post paid, or 30p if added to an order for components.

TEL LABS Q81. 1k, 1% 3500ppm temperature compensating resistor **185p**

OTHER COMPONENTS (Prices in pence)

741-8	23	LF 351	38
723-14	40	TL 081	38
1458-8	44	MC 34002/TL 082	65
LF 347/TL 084	130	CA 3080E	63
LM 348	90	LM 13800	125

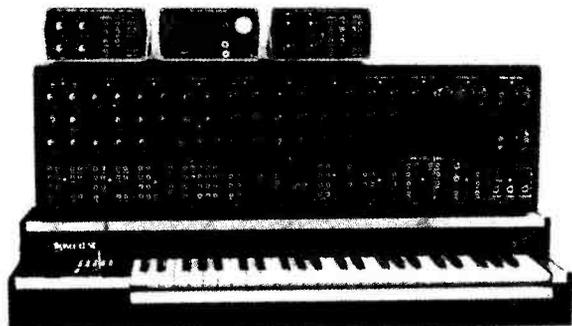All other components used in our kits are available separately and these are listed in the current price list — sent with orders or on receipt of 15p in stamps.



KITS FOR ETI 80 MODULAR SYNTHESISER. Components as specified in the issue of ETI listed which also contains the constructional details for the kits. Glass fibre and roller tinned PCB I.C. sockets.

KIT 80-1 ± 15V Power Supply (Feb 1980)	£16.70
KIT 80-2 Voltage Controlled Oscillator (Feb. 1980)	£16.10
KIT 80-3 Voltage Controlled Low Frequency Oscillator (Feb. 1980)	£16.10
KIT 80-4 Voltage Controlled Mixer (March 1980)	£21.10
KIT 80-5 Processor (with full instructions)	£5.20
KIT 80-6 Voltage Controlled Filters (May 1980)	£11.18
KIT 80-7 V.C. State Variable Filter (July 1980)	£17.18
KIT 80-8 Single ADSR Envelope Shaper (July 1980)	£8.25
KIT 80-8 Dual ADSR Envelope Shaper (July 1980)	£14.50
KIT 80-9 Dual Voltage Controlled Amplifier (August 1980)	£12.16

PCBs SEPARATELY

KIT 80-1	£1.60	KIT 80-6 (all types)	£1.60
KIT 80-2/80-3	£2.10	KIT 80-7	£2.35
KIT 80-4	£2.60	KIT 80-8	£1.75
KIT 80-5	£1.20	KIT 80-9	£2.30

9 x 3 inch panels for modules 80-2 up to 80-8 (Dual) inclusive to the design shown in ETI and made from white plastic coated steel with black lettering are available at £2.50 each.

PLEASE ADD 30p P&P TO TOTAL ORDER AND THEN ADD VAT AT CURRENT RATE.



DIGISOUND LIMITED,
13 THE BROOKLANDS, WREA GREEN,
PRESTON, LANCs. PR4 2NQ
Tel.: 0772 683138 (MAIL ORDER ONLY)

HAND HELD GAMES

Supersonic Mastermind	£21.00
Galaxy Invaders	£22.95
Mattel Soccer	£21.50
ENTERPRISE 4 in 1	£24.95
3 Games and calculator in one	
*Electronic Mastermind	£12.90
U.F.O. Master Blaster	£24.95
Amaze-A-Tron maze game	£18.95
Touch Me by ATARI (like Simon)	£26.95
Football (two players)	£24.95
ZAP missile game	£11.95
*DIGITS (like Mastermind)	£14.95

ALL GAMES HAVE SOUND EFFECTS EXCEPT*

ATARI video

computer **£138**

SPACE INVADERS CART	£29.95
STAR CHESS T.V. Game	£63.35
DATABASE Prog. T.V. Game	
NEW CHESSMATE 8 Level	£89.95
NEW CHESS CHALLENGER 7	£59.95
CHESS CHALLENGER 10	£99.00
VOICE CHALLENGER	£180.00
CHESS CHALLENGER 2	£219.00
CHESS CHALLENGER 4	£54.00
ZODIAC Astrology Computer	£90.00
NEW Snooze Alarm	£29.95
EL-MAC 5MHz Scope	£14.90
RADAT 10MHz Scope	£139.90
	£169.00

The latest from the U.S.A. PINBALL WIZARD

★ Still available ★
Featured in Nov. issue of E.T.I.
Home TV Game — B/W Kit
Basic Kit **£28.90**
Contains everything except box and controls
Box & Controls — **£6.50**, Mains Adaptor — **£3.90**
Play 7 games with 4 options on each game
4-Pinball games 2-Basket, 1-Breakout
Versatile car alarm kit **£18.90**
See review in Hobby Electronics November
CHROMA CHIME 24 tune door chimes kit **£10.75** Built **£15.95**
C.B. Aerials and Accessories

COMPUTERS — Home, Business etc.

PET 8K	£550.00
PET 16K	£670.00
SORCERER 8K	£747.50
SORCERER 16K	£874.00
SORCERER 32K	£887.75
SUPERBOARD II 4K	£180.00
UK 101 Kit 4K	£226.85
Built 4K	£286.35
TRS80 Level 2 16K	£409.40
5 1/4" Floppy Drive	£288.65
Dual Drive	£506.00
NASCOM 2 Kit	£339.25
2 Built	£396.75
HEATH WH89	£1,805.00
HEATH WH14 Printer	£586.50
Softy Kit	£115.00
Softy Built	£138.00
Intelligent EPROM Programmer	

PRINTERS: FLOPPY DISC: BOOKS

S.a.e. Enquiries. Please allow up to 21 days for delivery. All prices inc. of VAT.



N.I.C.
61 BROAD LANE, LONDON N.15 4DJ
Day 01-808 0377; Eve 01-889 9736



POWERFETS

Some day all power transistors will be made this way!

	CHAN	VDS max V	ID max A	PDISS max W	RDSON Type Ω	Case	Price
BD512	P	60	1.5	10	†(3.5)	T0202	85p
BD522	N	60	1.5	10	2.5	T0202	80p
VMP4	N	60	2.0	25	2.0	380-50E	1250p
VN10KM	N	60	0.5	1.0	4.0	T092†	55p
VN64GA	N	60	12.5	80	0.3	T03	750p
VN67AF	N	60	2.0	15	2.0	T0202	75p
2SJ49	P	140	7.0	100	1.0	T03	395p
2SK134	N	140	7.0	100	1.0	T03	395p

†/p protected †our selection. VN/VM, 96-page Design Cat. 20p. Heat clips T0202 12p, T092 8p.

MANUFACTURERS/DESIGNERS. We will be stocking Powerfets by IR, TI and Interil as well as by Hitachi, ITT and Siliconix. We can advise you on applications and type selection, supply samples and quantities.


REMEMBER Powerfets need virtually no drive current, switch in nanoseconds, and are 2nd breakdown free, etc. etc.

CA3026 70p	HI-FI ON TWO CHIPS	SCOPE TRACE DOUBLER P.C.B.
CA3080E 70p	HA12017 (Preamp 0.001% distortion)	Built C/W shift, chan select, choprate controls and instructions. Useful display from DC to 10MHz. Runs from 9v battery £9.95
CA3140E 38p	83dB S/N in phono application) 99p	
DA008 250p	HA1397 (Poweramp 20 watts in 8Ω)	VCA High quality design offers attenuation from 0dB to -90dB S/N 90dB. THD 0.01%. B.W. DC to 100KHz. Complete component set and circuit £2.50 .
DM2502 555p	0.02% distortion (typ) 195p	
LM308 50p	Both with data and circuits	
LM3900 43p	POWERFET AMPLIFIER semiconductor sets. High power designs offering very low distortions.	
MC3401 30p	80 watt (THD 0.008%) £8.75	
NE529 145p	120 watt (THD 0.004%) £16.65	
NE555 25p	(with circuits)	
SAD1024 1050p	†into 8Ω †at all powers and all audio frequencies	
SD532 30p		
TD1022 600p		
TLO81 29p	LED VU/PPM METER	
TLO82 55p	Complete component set. Displays positive and negative peak levels, and average levels simultaneously on 10 number LEDs, with 3dB resolution. With 10 reds £6 , with 7 green, 1 yellow and 2 red £6.40 .	
2102 80p		
4011B 17p		
709 15p		
710 25p		
733 50p		
741 18p		
78L05/12 29p		

30p post and packing. Mail order only to

J. W. RIMMER
148 Quarry Street
Liverpool L25 6HQ
Tel. 051-428 2651

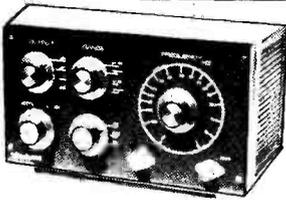Technical enquiries to: 367 Green Lanes, London N4 1DY.
Telephone 01-800 6667



**ECONOMICAL
VERY LOW DISTORTION
AUDIO SIGNAL
GENERATORS**

SINE/SQUARE 1v rms OUTPUT
Freq. 10hz-100 KHz

A0146-9 (dist. .0015% at 1Khz) A0113 below (dist. .0.2% at 1Khz.)

PRICES

A0113 batty. kit	£23	{ + UK Tax	£3.45)
A0113 batty. (assembled)	£28	{	£4.20)
A0113 Mains (assembled)	£36	{	£5.40)
A0146 Batty. Kit	£31	{	£4.65)
A0146 Assembled	£36	{	£5.40)
A0146/9 Mains, Made	£46	{	£6.90)
P.P. £2 (U.K.)			

TELERADIO ELECTRONICS

325 Fore Street, Edmonton, London N9 0PE

ALSO R.F. and Function Generators, THD Analyser, AC Millivoltmeter
Details on request Closed Thursdays 807 3719

**PLEASE MENTION
ETI WHEN REPLYING:
TO ADVERTS**

**CB
CITY**

PROUDLY PRESENT



**ACCESSORIES
CATALOGUE
SHOWROOM**

Telephone:
**ALDERSHOT
0252 318141**

Monday-Saturday
9 a.m.-6 p.m.

(NO RIGS)



WEST HYDE CASES FOR E.T.I. PROJECTS

- Bench Amplifier (August 1979) Order Code WEC 801
- Audiophile Pre-Amp (October 1979) Order Code CL2 CDL
- Audiophile Power Amp (October 1979) Order Code CL2 CGL
- Audiophile PSU (October 1979) Order Code CL2 AEL
- Pinball Wizard (November 1979) Order Code TEK 364
- Points Controller (December 1979) Order Code BOC 680
- Moving Coil Pre-Amp (January 1980) Order Code CL2 ADJ
- Synthesiser Project Order Code TEK A23G
- Stereo Image Co-ordinator (July, 1980). Order Code CL2 CDJ.



**PLEASE ASK FOR OUR FREE
80-PAGE CATALOGUE AND PRICE LIST**

THE BIGGEST SELECTION OF CASES IN EUROPE



WEST HYDE

WEST HYDE DEVELOPMENTS LIMITED, UNIT 9, PARK STREET INDUSTRIAL ESTATE, AYLESBURY, BUCKS TEL 0296 20441

Codespeed Electronics

P.O. BOX 23, 34 SEAFIELD ROAD, COPNOR, PORTSMOUTH,
HANTS. PO3 5BJ

GIANT 0.8" LED clock display, common cathode, non-multiplexed. With data £3.95 each. **ALARM** clock module with 0.7" LED display. With data £5.99 each. **LIQUID** crystal clock display, 0.5" digits. With data and FREE socket, £6.25 each. **FLUORESCENT** reject calculators. Modern, 10 function with full memory. Most repairable but no g'tees £2.99 each. **TEN** transistor I.F. transformers. All brand new. May include several types. 85p for 10. **CLOCK CHIP** MM5316 I.C. (has alarm output). Brand new, with data £2.35 each. **POLARIZING** filter, plastic, 0.008" thick. Any size cut from 1 sq. in. to max. size 12" x 250 feet. 3p per sq. inch. **MOMENTARY** (push to 'make') switch. Red cap. 15p each. **SLIDE** switch, 2 pole c.o. 18p each. **TWO** calculator keyboards (not compatible with 4204 calc chip). 99p the pair. **MULTIMETER CHIP**. MM5330 I.C. to build 4 1/2 digit d.m.m. (needs additional circuitry). With data £3.85 each. **KNOBS**, slider control knobs, fits 5 or 8mm shafts. State colour. 14p each. Rotary control knobs, black (18mm diam) with coloured cap, state colour required. 20p each. Skirted rotary knob, same as rotary control knob above but has 'flared' skin around base. State cap colour required. 27p each. Colours available, black, red, green, blue, yellow, grey, white. **8 DIGIT** common cathode calculator display, 0.1", multiplexed, with data, 99p each. **LED WRIST-WATCH CHIP** with data, 95p each. **LED WRIST-WATCH DISPLAY** matches above watch chip. With data, 95p each. **NOTE**, the wristwatch chip and display are housed in 'legless flatpack' style package and require some fairly fine soldering. **QUALITY** jack sockets, mono 25p each, stereo 30p each. **LMS5** timer I.C. with applications booklet, 25p each. **MEMORIES** 2102 static RAM with data, 99p each. **NORTEC** 4204, 4 function calc. chip. With data, 80p each. **UNTESTED** 0.1" LED displays, 10 single digit displays for 95p. 'U' to test.

Post and packing please add 40p (overseas orders add £1).

For your FREE copy of our latest catalogue please send MEDIUM sized SAE, VAT ADD 15% TO TOTAL COST (INCLUDING POST AND PACKING).

'Cash back' satisfaction guarantee on all items.

ETCH RESIST TRANSFER KIT SIZE 1:1

Complete kit 13 sheets 6in x 4 1/2in £3.00 with all symbols for direct application to P.C. board. Individual sheets 30p each. (1) Mixed Symbols (2) Lines 0.05 (3) Pads (4) Fish Plates and Connectors (5) 4 Lead and 3 Lead and Pads (6) DILS (7) BENDS 90° and 130° (8) 8—10—12 T.O.5. Cans (9) Edge Connectors 0.15 (10) Edge Connectors 0.1 (11) Lines 0.02 (12) Bends 0.02 (13) Quad in Line.

FRONT AND REAR PANEL, TRANSFER SIGNS

All standard symbols and wording. Over 250 symbols, signs and words. Also available in reverse for perspex, etc. Choice of colours, red, blue, black, or white. Size of sheet 12in x 9in. Price £1.20.

GRAPHIC TRANSFERS WITH SPACER ACCESSORIES

Available also in reverse lettering, colours red, blue, black or white. Each sheet 12in. x 9in contains capitals, lower case and numerals 1/4in kit or 1/4in kit. £1.20 complete. State size.

All orders dispatched promptly.

All post paid


Shop and Trade enquiries welcome
Special Transfers made to order

**E. R. NICHOLS
P.C.B. TRANSFERS**

DEPT. ET18

46 LOWFIELD ROAD
STOCKPORT, CHES. 061-480 2179

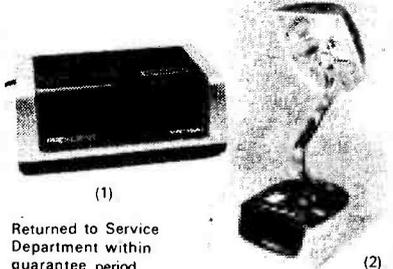BARGAINS FOR THE ELEC- TRONIC HANDYMAN BRANDED L.E.D. DIGITAL ALARM CLOCKS



Returned to Service
Department within
guarantee period.

1. With alarm repeat. S.R.S.P. of £17.00. Offered at £3.95, inc. VAT, or 3 for £9.95, inc. VAT.
2. With luxury lamp and repeat alarm. S.P.S.P. £31.00 Offered at £7.95 inc. VAT each, or 3 for £19.95 inc. VAT.

These will be sold as received from our customers with the existing fault(s) and without guarantee.

U.K. only

Discounts available on large bulk purchase.

**PRESCOTT CLOCK & WATCH CO.
LTD.**

PRESCOTT HOUSE, HUMBER ROAD, LONDON
NW2 6ER

CIRCUIT DESIGN, Prototype construction, Analogue or Digital, Single Circuits or Complete Instruments/Systems. Write A. J. ATTWOOD, C.Eng., MIERE, Heathercote, Heatherton Park, Taunton, Somerset, TA4 1ET or Phone Bradford-on-Tone (082-346) 536.

200 COMPONENTS £4. 100 diodes 85p. 150 caps £1.50. 100 resistors 85p. All mixed. Lists 15p. Sole Electronics (ETI), 37 Stanley Street, Ormskirk, Lancs. L39 2DH.

CLASSIFIED

TRANSFORMERS MANUFACTURED to specification, many popular types ex-stock. Fast turn around on volume production. Send enquiries to Louth Transformers, Queen Street, Louth, Lincs. Tel: (0507) 606436.

BURGLAR ALARMS AND EQUIPMENT. Contacts, Bells, Sirens, Wire etc. Plus special offer to ETI readers. S.A.E. for list. A. Barton, (ETI), Highbanks, Newport Road, Sandown, IOW.

INTENSIVE COURSES IN

BASIC AND PASCAL

including hands on mini-computer operation

These intensive courses are intended to instruct from minimal knowledge to an operational capability of computer programming.

Courses are fully residential, allowing maximum time for instruction and programming.

BASIC — Weekends from Friday Evening to Sunday Afternoon.

PASCAL — Weekdays Monday Morning to Friday Afternoon inclusive.

For further details, dates available, fees
Phone (0401) 43139, or write
CLEVELAND BUSINESS SERVICES
(Dept. ETI-2), Cleveland House
Routh, North Humberside HU17 9SR

PHILIPSG7000 TV GAMES. Computer and cartridges, brand new. Only used once. £139. Call at or write to Romeo Cervi, 20 Annandale Street, Edinburgh EH7 4AN.

NASCOM 1 OR 2

Pair of Joysticks + software £19.90
Light Pen + software £29.00
Load Nas1 tapes into Nas2 using this cassette
interface built + tested £15.00
No board cutting — easy to fit. SAE for details.

MK14 — built

Z80 conversion board £34.85
Keyboard £11.50
Display (1/2 inch) £16.00
Redecoding board £4.62
4Kstatic RAM board £49.00

Plus many others, spares, etc. Large SAE for list.

PRINTER

21 Column fast printer using standard paper.
Link to P10 port £112.00

BOUGHT AND SOLD

Any computer, printer, disc, etc., bought + sold. Write, stating offer/requirements.

REPAIRS


Nas1 £7.50, Nas2 £12.50, MK14 £4.50,
UK101 £12, Acorn and ZX80 £4.50. And
others plus parts + post.

REDDITCH ELECTRONICS

21 FERNEY HILL AVENUE
REDDITCH, WORCS. B97 4RU

If it's a case of making your project look good, then use one of ours.

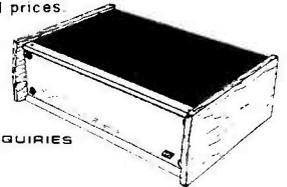Simply send a S.A.E. for
Details and prices.



TRADE ENQUIRIES
INVITED.

H. M. ELECTRONICS

271a/275a Fulwood Road,
Broomhill
Sheffield S10 3BD



C A M E R A

£110.00 + P/P £3.45 (inc. VAT)
+ VAT (£16.50) Optional extra manual
£6. Total £129.95

BEST OFFER EVER
**Camera Kit, Lens,
Vidicon & Modulator**

CROFTON

Tel: 01-891 1923 For full details

COMPUKIT UK101 EUROPE'S FASTEST SELLING ONE BOARD COMPUTER

SPACE INVADERS PROG.
£5 + VAT



NEW MONITOR FOR COMPUKIT UK101 • In 2K Eprom 2716
• Allows screen editing • Saves data on tape
• Flashing cursor • Text scrolls down **£22.00 + VAT**

- ★ 6502 based system — best value for money on the market.
- ★ Powerful 8K Basic — Fastest around
- ★ Full Qwerty Keyboard
- ★ 4K RAM Expandable to 8K on board.
- ★ Power supply and RF Modulator on board.
- ★ No Extras needed — Plug-in and go.
- ★ Kansas City Tape Interface on board.
- ★ Free Sampler Tape including powerful Dissassembler and Monitor with each Kit.
- ★ If you want to learn about Micros, but didn't know which machine to buy then **this is the machine for you.**

Build, Understand and Program your own Computer for only a small outlay.	KIT ONLY £199 + VAT NO EXTRAS NEEDED	AVAILABLE READY ASSEMBLED & TESTED READY TO GO FOR £249 + VAT
Specialty designed case for CompuKit in orange/black. With room for accessories. £29.50 + VAT	6502 Assembler/Editor for CompuKit £14.90 + VAT	

The **CompuKit UK101** comes in kit form with all the parts necessary to be up and working, supplied. No extras are needed. After plugging in just press the reset keys and the whole world of computing is at your fingertips. Should you wish to work in the machine code of the 6502 then just press the M key and the machine will be ready to execute your commands and programs. By pressing the C key the world of Basic is open to you.

This machine is ideal to the computing student or Maths student, ideal to teach your children arithmetic, and is also great fun to use.

Because of the enormous volume of users of this kit we are able to offer a **new reduced price of £199 + VAT**

- 8MHz Super Quality Modulators **£4.90**
- 6MHz Standard Modulators **£2.90**
- C12 Computer Grade Cassettes 10 for **£4.00**
- Super Multi-rail P.S.U. +5 -5 +12v **£29.50**
- Anadex Printer Paper—2000 sheets **£25.00**

NASCOM-2 MICRO-COMPUTER

only **£305 + VAT**

With **FREE 16K RAM Board Type B**

Your choice of freebies with every Nascom 2 purchased from us

either FREE POWER SUPPLY OR FREE GRAPHICS ROM OR FREE VERO CASE TO TAKE NASCOM 2

Microprocessors Z80A, 8 bit CPU. This will run at 4MHz but is selectable between 1/2/4 MHz. This CPU has now been generally accepted as the most powerful, 8 bit processor on the market.

INTERFACE
Keyboard New expanded 57 key Licon solid state keyboard especially built for Nascom. Uses standard Nascom, monitor controlled, decoding.
T.V. The tv peak to peak video signal can drive a monitor directly and is also fed to the on-board modulator to drive the domestic T.V.
I.O. On-board UART (int.6402) which provides serial handling for the on-board cassette interface or the RS232/20mA teletype interface.
The cassette interface is Kansas City standard at either 300 or 1200 baud. This is a link option on the NASCOM-2. The RS232 and 20mA loop connector will interface directly into any standard teletype.
The input and output sides of the UART are independently switchable between any of the options — i.e. it is possible to house input on the cassette and output on the printer.
PIO There is also a totally uncommitted Parallel I/O (MK3881) giving 16, programmable, I/O lines. These are addressable as 2 x 8 bit ports with complete handshake controls.
Documentation Full construction article is provided for those who buy a kit and an extensive software manual is provided for the monitor and Basic.
Basic The Nascom 2 contains a full 8K Microsoft Basic in one ROM chip with additional features like DEEK, DOKE, SET, RESET for simple programming.

only **£356 + VAT**

TRS80 LEVEL 2 16K

Fully converted to UK T.V. Standard. Comes complete with easy to follow manuals, UK Power Supply — Cassette Leads — Sample tapes. Special box to enable you to plug into your own TV. Recommended for first time-buyers. Just plug in and go. Full Range of Software Available

THE ATARI VIDEO COMPUTER SYSTEM

Atari's Video Computer System now offers more than 1300 different game variations and options in twenty great Game Program™ cartridges!

Have fun while you sharpen your mental and physical coordination. You can play rousing, challenging, sophisticated video games, the games that made Atari famous. You'll have thrill after thrill, whether you're in the thick of a dogfight, screaming around a racetrack, or dodging asteroids in an alien galaxy. With crisp bright colour (on colour TV) and incredible, true-to-life sound effects. With special circuits to protect your TV.

Cartridges now available All at **£13.90** each + VAT
Basic maths, Airsea Battle, Black Jack, Breakout, Surround, Spacewar, Video Olympics, Outlaw, Basketball, Hunt & Score*, Space War, Sky Diver, Air Sea Battle Codebreaker*, Miniature Golf.

Special Scoop
SPACE INVADERS CARTRIDGE £25. + VAT Ex-Stock

Extra Paddle Controllers — **£14.90 + VAT** *Keyboard Controllers — **£16.90 + VAT**

NEW REDUCED PRICES

8K **£399** } + VAT
16K **£499** }
32K **£599** }

RRP £795 for 32K **The PEDIGREE PETS**

Very popular for home & business use. 8K Microsoft Basic in ROM. 8K Pet 32K & 16K with new improved keyboard. All with green screen. Cassette deck **£55** extra. Full range of software available.

NEW TV GAME BREAK OUT

Has got to be one of the world's greatest TV games. You really get hooked. As featured in ETI. Has also 4 other pinball games and lots of options. Good kit for up-grading old amusement games.

MINI KIT — PCB, sound & vision modulator, memory chip and de-code chip. Very simple to construct. **£14.90 + VAT**
OR PCB **£2.90** MAIN LSI **£8.50** Both plus VAT

video 100

12" BLACK & WHITE LOW COST VIDEO MONITOR

only **£79 + VAT**

- Ideal for home, personal and business computer systems
- 12" diagonal video monitor
- Composite video input
- Composite video input
- Compatible with many computer systems
- Solid-state circuitry for a stable & sharp picture
- Video bandwidth - 12MHz + 3DB
- Input impedance - 75 Ohms
- Resolution - 650 lines Minimum In Central 80% of CRT; 550 Lines Minimum beyond central 80%.

COMP SHOP
"Europe's Largest Discount Personal Computer Store"

Please add VAT to all prices — Delivery at cost, will be advised at time of purchase. Please make cheques and postal orders payable to **COMP SHOP LTD.**, or phone your order quoting **BARCLAYCARD, ACCESS, DINERS CLUB or AMERICAN EXPRESS** number.
CREDIT FACILITIES ARRANGED — send S.A.E. for application form.

14 Station Road, New Barnet, Hertfordshire, EN5 1QW **Télex: 298755 TELCOM G**
Telephone: 01-441 2922 (Sales) 01-449 6596

OPEN - 10 am - 7 pm — Monday to Saturday
Close to New Barnet BR Station — Moorgate Line.

★ **NOW in IRELAND at: 80 Marlborough St., Dublin 1. Tel: Dublin 749933**

COMP COMPUTER COMPONENTS
(Part of the Compshop Ltd. Group)

Logos for American Express, Barclaycard, VISA, and other payment methods.

STEP INTO A NEW WORLD WHEN YOU DISCOVER **MAPLIN**

For beginners or professionals, the Maplin catalogue will help you find just about everything you need for your project.

Over 5,000 of the most useful components — from resistors to microprocessors — clearly described and illustrated.

Send the coupon for your copy
and **STEP UP TO
MAPLIN SERVICE
NOW**




Post this coupon now for your copy of our 1979-80 catalogue price 70p.

Please send me a copy of your 280 page catalogue. I enclose 70p (plus 46p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the U.K. send £1.35 or ten International Reply Coupons. I enclose £1.16.

NAME _____

ADDRESS _____

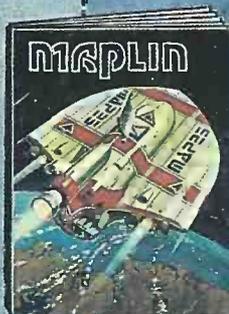

MAPLIN

ELECTRONIC SUPPLIES LTD

All mail to:-

P.O. Box 3, Rayleigh, Essex SS6 8LR.


Telephone: Southend (0702) 554155.

Shop: 284 London Road, Westcliff-on-Sea, Essex. (Closed on Monday).

Telephone: Southend (0702) 554000.

ET780

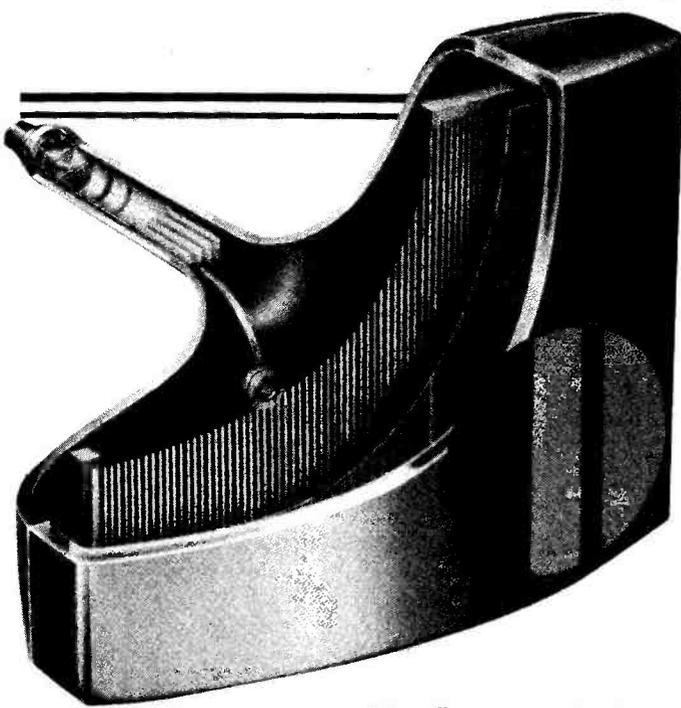Catalogue now available in all branches of **WHSMITH**  Price **£1.00**



In the Tube

Sony (UK) Ltd. has just received the Queen's Award for export for export for its Bridgend manufacturing plant which produces 125,000 Trinitron television sets per year, 50% of which are exported. Bridgend employs over 720 people and this factory already represents a £10 million investment for Sony. They have now decided to invest a further

£10 million to considerably increase their production facilities at Bridgend which will include a 27" picture tube manufacturing plant, the first in Europe (the other one outside Japan is in San Diego). The workforce will be increased to around 1,000 and production is expected to be 150,000 a year once the new annexe is completed in 1982. This means that a possible 90% of components for Trinitron sets manufactured in Bridgend will be supplied from Great Britain.

Army Exhibition

Four Plessey businesses will be exhibiting a wide range of equipment at the British Army Equipment Exhibition in Aldershot on June 23-27. Plessey Avionics and Communications will display their complete range of multi-combat radios and a selection of other defence communications products. There will be over 50 Plessey tactical radios in use or on display at the exhibition, either on Plessey stands or incorporated in other manufacturers' vehicle displays as working vehicle systems. Plessey Aerospace will show a wide range of military engine-driven generator sets ranging from 0.3 kW DC for battery charging applications up to 20 kW for communications equipment. Plessey Radar will exhibit products primarily concerned with upper air observations and windfinding radar. Plessey Defence Systems, formed in 1979, has current projects including the 'Ptarmigan' Tactical Trunk Communications System and 'Wavell', a military ADP system for battlefield command and control, a staff cell mock-up of which will be featured at the indoor site together with a cine-film. Both these systems have been developed for the British Army.

Flying High

Part of the Civil Aviation Authority's £100m re-equipment programme has now been finalised. It is for the replacement of the radar systems for the National Air Traffic Services, the total cost of which is estimated to be £24.5m, 30% of which will be met by the Ministry of Defence and at the conclusion of the programme more than half the total value will have been contracted or sub-contracted to British firms.

Delivery of the new radars are required progressively from 1981 to 1983. The timing of the setting up is critical if the National Air Traffic Services are to provide an effective and safe air traffic service. The radars currently in use need to be replaced as they are not compatible with the radar data processing systems in use and being developed by the London Air Traffic Control Centre. If these radars are not replaced by 1983, there could be a situation where civil flights would have to be delayed, re-routed or cancelled and military flights adversely affected. £14.5m worth of contracts have already been placed and a further £10m are still to be let principally in the UK for buildings, radar towers and associated works.

Pye on CB

Following the recent Government statement on CB Pye Telecommunications has just re-issued this statement, explaining the company's position.

"At a time when more and more interest is being shown in Citizens Band Radio (CB) and when more and more discussions and articles are appearing in the media, Pye Telecommunications Limited, Europe's largest supplier of Mobile Radio, feels that now is the appropriate time to make known its views on one aspect of CB.

In the event of H M Government deciding in favour of CB, Pye Telecommunications feels very strongly that the UHF frequency band would be the most appropriate.

The reasons for this recommendation are:

- (1) UHF is more suitable for the high population density of the UK.
- (2) Use of narrow deviation FM modulation at UHF allows more users in less spectrum, due to increased re-use of

channels by the suppression of weaker signals — 'Capture Effect'.

- (3) The use of UHF prevents interference with Hi Fi, television, radio and other electronic devices.
- (4) It would avoid the poor grade of service which results from congestion experienced on 27 MHz CB (USA) resulting from long range propagation ('Skip Effect').
- (5) UHF will avoid harmonic interference into other users of the spectrum, Police, fire, ambulance services, etc.
- (6) Selection of the UHF Band would avoid the problem of the re-allocation of existing users, which would make 27 MHz CB slow and costly to implement.
- (7) UHF has predictable range and channel re-usability.
- (8) UHF has high quality transmission and reception.

If any confirmation of the points listed above is needed, one has only to look at Australia, where the introduction of UHF CB has established the above principles."


Touch Dimmer (April 1980)

For size and availability we made R1 a 1W carbon type. If you find that this gets warm in use, replace it with a 2.5 W wire-

wound (or vitreous wirewound) type, but make sure the type you choose will fit before you part with any pennies.


Safety First

The Cyclic Guardscan from L.C. Automation of Preston, is a photo-electric safety shut-off system for use with mechanical/hydraulic press brakes, guillotines and other types of potentially dangerous cyclic machines. It ensures complete operator safety by creating a photo-electric curtain across the front and (if necessary) the rear of the machinery. If the operator breaks the 'curtain' during the dangerous parts of the machine cycle, it automatically cuts off. During 'safe' parts of the cycle the operator has full access to the equipment. The curtain consists of 20 infra red beams, 18 in the vertical column and two in the horizontal. The cam box and the linear cam use four proximity switches to detect the position of

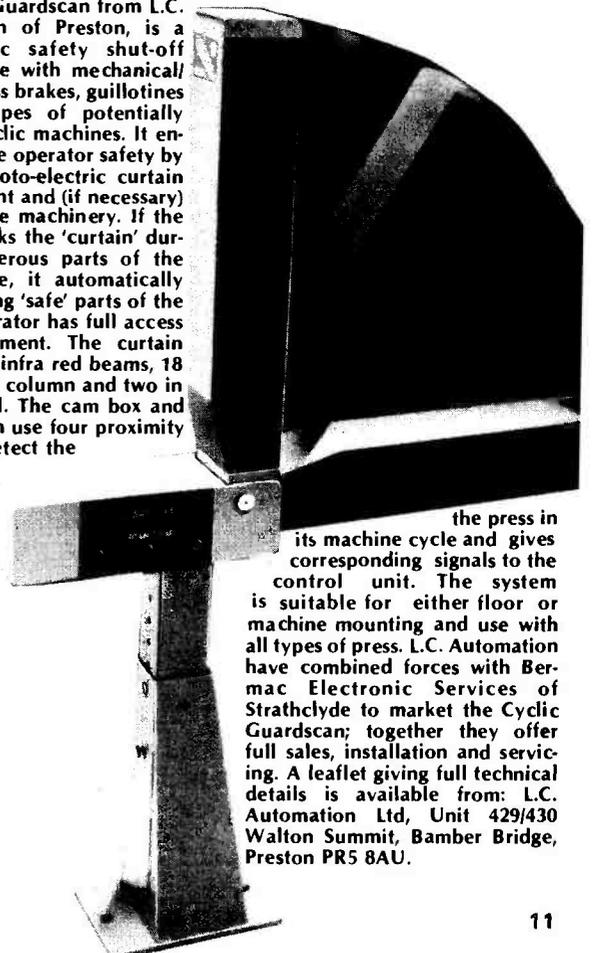

the press in its machine cycle and gives corresponding signals to the control unit. The system is suitable for either floor or machine mounting and use with all types of press. L.C. Automation have combined forces with Bermac Electronic Services of Strathclyde to market the Cyclic Guardscan; together they offer full sales, installation and servicing. A leaflet giving full technical details is available from: L.C. Automation Ltd, Unit 429/430 Walton Summit, Bamber Bridge, Preston PR5 8AU.

TTLs by TEXAS				931 SERIES				74S SERIES				TRANSISTORS				BFR39				TIP30A				2N3055				40364				10A 400V																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
7400	11p	74290	380p	4019	45p	9301	180p	74S00	60p	74S114	120p	AC126	25p	BFR40	25p	TIP30C	48p	2N3055	48p	40364	120p	10A 400V	200p	7401	12p	74298	200p	4022	110p	9302	175p	74S04	60p	74S124	120p	AC127	25p	BFR41	25p	TIP31A	58p	2N3553	240p	40408	80p	25A 400V	400p	7402	12p	74365	100p	4023	27p	9308	315p	74S05	75p	74S132	180p	AC187	8p	BFR79	25p	TIP31C	62p	2N3565	30p	40410	75p			7403	14p	74366	100p	4024	27p	9310	275p	74S08	75p	74S133	75p	AC187/8	25p	BFR80	25p	TIP32A	68p	2N3584	280p	40411	300p	ZENERS		7404	14p	74367	100p	4025	20p	9311	180p	74S10	60p	74S138	225p	AF116	500p	BFR81	25p	TIP32C	82p	2N3643/4	45p	40594	120p	2.7V-33V		7404A	14p	74368	100p	4026	130p	9314	165p	74S30	60p	74S157	250p	AD149	70p	BFR30	34p	TIP33A	84p	2N3673	132p	40595	120p	400W	1p	7405	14p	74369	100p	4027	50p	9316	225p	74S32	90p	74S174	250p	AD161/2	45p	BFX30	34p	TIP34A	115p	2N3706/7	14p	40673	75p	1W	8p	7406	40p	74393	200p	4028	84p	9321	225p	74S37	90p	74S175	320p	AU107/2	200p	BFX86/7	40p	TIP34E	160p	2N3708/9	12p	40871/2	80p			7407	40p	74490	225p	4029	100p	9322	150p	74S64	60p	74S194	350p	BC106	11p	BFX88	30p	TIP35A	225p	2N3773	300p			TRIACS		7408	17p	74LS SERIES		4030	100p	9334	380p	74S74	90p	74S241	450p	BC109	11p	BFW10	30p	TIP35C	290p	2N3819	25p			PLASTIC		7409	19p	74LS00	14p	4031	200p	9368	200p	74S85	300p	74S260	70p	BC117	10p	BFW10	30p	TIP36A	270p	2N3820	50p	BY127	12p	3A 400V	60p	7410	19p	74LS02	18p	4034	200p	9372	200p	74S86	180p	74S273	70p	BC147/8	9p	BFW10	30p	TIP36B	270p	2N4058	12p	BY36-300	20p	3A 500V	95p	7412	20p	74LS04	18p	4035	110p	9374	200p	74S112	120p	74S374	500p	BC149	10p	BFV56	33p	TIP41A	68p	2N3866	90p	OA47	9p	6A 500V	70p	7413	30p	74LS05	25p	4036	285p			BC157/8	10p	TIP41C	75p	2N3902	700p	OA81	15p	8A 500V	75p	7414	40p	74LS08	22p	4037	115p			BC158	11p	TIP42A	70p	2N3905/6	18p	OA85	15p	8A 400V	85p	7414A	40p	74LS10	20p	4038	285p			BC172	12p	TIP42C	82p	2N3905/6	20p	OA91	9p	12A 400V	85p	7417	27p	74LS13	40p	4041	80p			BC177/8	17p	TIP5A	160p	2N4037	95p	OA95	9p	12A 500V	100p	7420	40p	74LS14	72p	4042	80p			BC179	18p	TIP54	160p	2N4080	12p	OA95	9p	16A 400V	110p	7422	22p	74LS20	20p	4043	80p			BC182/3	10p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	7423	30p	74LS21	40p	4044	80p			BC184	11p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	7425	30p	74LS27	38p	4047	100p			BC187	10p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	7426	40p	74LS30	20p	4048	65p			BC212	11p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	7427	30p	74LS32	27p	4049	50p			BC237	15p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	7428	30p	74LS33	27p	4050	48p			BC337	16p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	7430	17p	74LS38	35p	4050	48p			BC341	16p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	7432	30p	74LS42	70p	4051	80p			BC346	16p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	7433	30p	74LS47	90p	4052	90p			BC347/8	16p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	7437	35p	74LS51	24p	4054	150p			BC348	16p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	7438	35p	74LS55	20p	4055	125p			BC349	16p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	7440	17p	74LS73	50p	4056	135p			BC357/8	16p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	7441	17p	74LS74	50p	4057	800p			BC358	16p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	7442A	60p	74LS75	45p	4059	800p			BC359	16p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	7443	30p	74LS76	45p	4060	140p			BC359B	16p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	7444	112p	74LS83	110p	4066	120p			BC370	17p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	7445	100p	74LS85	100p	4067	450p			BC371/2	22p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	7446A	63p	74LS86	40p	4068	27p			BC372	22p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	7447A	74p	74LS87	40p	4069	20p			BC373	22p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	7448	80p	74LS92	70p	4069	20p			BC374	22p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	7450	17p	74LS93	60p	4070	30p			BC375	22p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	7451	17p	74LS96	110p	4072	25p			BC376	22p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	7453	17p	74LS107	45p	4073	25p			BC377	22p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	7454	17p	74LS109	60p	4075	25p			BC378	22p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	7480	17p	74LS113	90p	4076	107p			BC379	22p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	7472	30p	74LS114	45p	4081	27p			BC380	22p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	7473	30p	74LS122	80p	4086	27p			BC381	22p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	7474	30p	74LS123	70p	4089	138p			BC382	22p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	7475	35p	74LS124	180p	4093	80p			BC383	22p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	7476	35p	74LS125	180p	4094	250p			BC384	22p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	7480	80p	74LS126	60p	4094	250p			BC385	22p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	7481	100p	74LS132	95p	4095	95p			BC386	22p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	7482	84p	74LS133	95p	4097	340p			BC387	22p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	7483A	84p	74LS136	55p	4098	120p			BC388	22p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	7484	100p	74LS138	75p	4099	200p			BC389	22p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	7485	110p	74LS139	75p	4100	220p			BC390	22p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	7486	36p	74LS145	134p	4103	132p			BC391	22p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	7489	175p	74LS147	220p	4101	132p			BC392	22p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	7490A	36p	74LS148	175p	4102	180p			BC393	22p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	7491	80p	74LS151	100p	4104	95p			BC394	22p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	7492A	48p	74LS153	60p	4105	90p			BC395	22p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	7493A	36p	74LS154	200p	4106	90p			BC396	22p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	7494	80p	74LS155	60p	4107	60p			BC397	22p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	7495A	70p	74LS156	90p	4107	60p			BC398	22p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	7496	65p	74LS157	60p	4108	470p			BC399	22p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	7497	180p	74LS158	90p	4110	300p			BC400	22p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	74100	130p	74LS160	130p	4114	250p			BC401	22p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	74107	35p	74LS161	100p	4102	120p			BC402	22p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	74109	65p	74LS162	60p	4105	120p			BC403	22p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	74116	200p	74LS163	100p	4103	70p			BC404	22p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	74118	130p	74LS164	120p	4107	95p			BC405	22p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	74119	210p	74LS165	180p	4110	95p			BC406	22p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	74120	110p	74LS166	180p	4110	150p			BC407	22p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	74121	34p	74LS167	100p	4111	150p			BC408	22p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	74122	48p	74LS174	110p	4112	80p			BC409	22p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	74123	48p	74LS175	110p	4114	285p			BC410	22p	TIP54	160p	2N4080	12p	OA95	9p	16A 500V	130p	

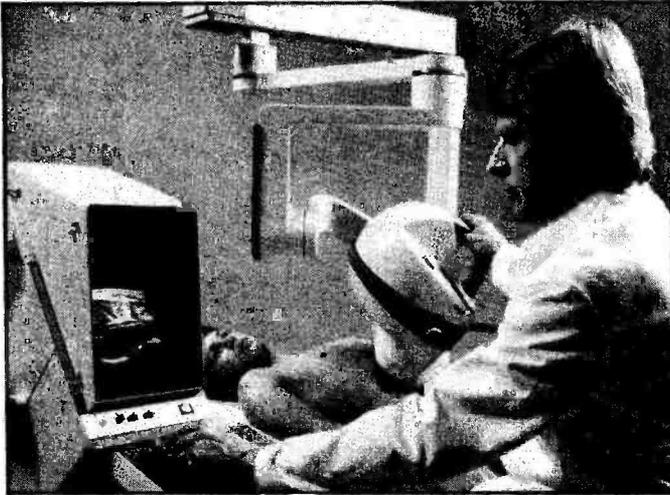

Invasion Of The Body Scanners

Siemens have introduced an improved version of their Vidoson 735 ultrasonic body scanner. The Vidoson 735 SM has a resolution of 4mm over the whole image. It uses an ultrasonic frequency of 3MHz and a parallel beam which penetrates to a maximum depth of 18cm.

Small structural features (inside organs, for example) can be displayed on the screen by a finely graded grey scale. This new system allows the wide dynamic range of echo signals to be adapted automatically to the pic-

ture tube characteristics, giving the optimum grey scale display. The picture is clearer and contours are sharper because small echoes can be suppressed by an adjustable signal threshold.

The system incorporates an electronic measuring device. Two marks can be positioned anywhere on the screen. The distance between them is then displayed digitally on the ultrasonic image. Thus, any long term change in the size of organs, for example, can be monitored over several scans, months apart perhaps.

Budding Dr. Kildares can get more information on the Vidoson 735 SM from Siemens Ltd, Siemens House, Windmill Road, Sunbury-on-Thames, Middlesex TW16 7HS.

Sun Spots

The concept of harnessing solar energy to power the national grid is now showing signs of becoming a reality. The Department of Industry has funded a six month study into the implications of British Industry of such a project. ERA and Marconi Space are assisting British Aerospace in this, and RAE, Farnborough are representing the Department of Industry.

This concept is already receiving attention in the USA by NASA, the Department of Energy and the aerospace industry in general, through a 20 million dollar programme. Although this is an entirely American effort, international co-operation would be expected. The proposed satellite for harnessing the sun's energy would measure something like 5 km by 10 km, with a 1 km diameter phased array microwave antenna pivoted at one end of the surface to convert the electricity into microwave energy for transmission back to earth. The ground receiving antenna (rectenna) would convert the microwave energy back into electricity. The microwave beam would need to be designed to produce no harm-

ful effects outside the rectenna. This, including its surrounding safety zone could occupy an elliptical site of 150-230 square kilometers. The energy delivered would be in the region of 5000 MW. The implications of this idea extend beyond the aerospace industry, into the possibility that Britain, at least, could obtain part of its electrical supply from this system during the 21st century.




Smart Heaters

A new type of heating element from Salford Electrical that can decide when it's too hot and regulate its temperature - and all without a single moving part. It isn't even microprocessor-controlled. It must be about the only thing that isn't these days, apart from Digest writers.

Designed for blown-air applications, PTC Honeycombe Heaters depend for their operation on the thermal properties of doped barium titanate, whose resistance increases sharply above a certain temperature - the switching temperature.

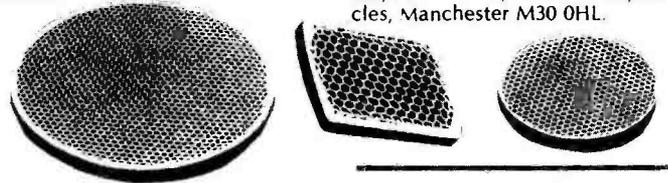The elements are available in round or rectangular shapes, with a honeycombe structure to facilitate air flow over a large surface area. Electrical connection is made to electrodes coated onto the two flat surfaces.



Drum Synth (June)

Three wire links are shown on the component overlay of the function board (p.89 Fig.9). The bottom link is an error and should not be fitted. Also the pad at the right hand end of the link (as seen on the component overlay) should be removed to stop it shorting the tracks on either side. The pad is also shown on the foil pattern and ET1 PRINT, which will have to be corrected too.

The resistor numbering in Fig.7, p.88 is incorrect. R34-41 should be labelled R30-37. Resistor numbering on the circuit diagram and parts list is correct.

Low initial resistance means rapid warm-up at switch-on. Air blown through the element reduces its temperature and, therefore, its resistance, which increases the input power. Thus the temperature of the block is maintained at the switching temperature. Heating power can be varied by controlling the air flow.

The two overwhelming advantages are safety (if the air flow stops, the heater limits itself to the switching temperature) and the elimination of radio frequency interference which occurs in conventional thermostatically controlled elements.

The new elements are available in a wide range of sizes, power ratings and switching temperatures. Further details of PTC Honeycombe Heaters from Salford Electrical Instruments Ltd, Peel Works, Barton Lane, Eccles, Manchester M30 0HL.

Image Co-ordinator

There is an error on the component overlay shown in Fig.4 on page 72. On the top right edge of the board the power connections should read (from the top) 0V, -Ve, +Ve, to match the connections to the board shown in Fig.5 on page 73. The interboard connections are shown in the photograph on page 72.

OK Cases

OK Machine & Tool's latest directory of packaging technology (catalogue of cases) recently reached us. The cases, by PacTec, come in over fifty models with all manner of variations available. They're made from impact-resistant ABS to stand up to rough treatment in service. Each case has a system of internal mounting bosses, vertical card guides and mounting rails with optional accessories available, producing a very flexible packaging system for your projects.

The range includes instrument cases with or without tilt stands, suitable for counters, timers, generators, etc. and a useful series of miniature cases, ideal for hand-held projects. Optional extras include ABS or metal front panels, special bezels and RFI shielding for the instrument cases and a belt clip, wrist strap and RFI shielding for the miniature cases.

For your free copy of OK's PanTec Catalogue, write to OK Machine & Tool UK Ltd, Dutton Lane, Eastleigh, Hants S05 4AA.



**Freeport
Birmingham
B19 1BR
021-233-2400**

- FREEPOST ON ORDERS
- VAT INCLUSIVE PRICES
- ADD 30p P&P
- 24 HR PHONE ANSWERING SERVICE
- ACCESS
- VISA
- CASH
- CHEQUE


ALL PRICES IN PENCE EACH UNLESS OTHERWISE STATED

CAPACITORS				Miniature Low Value				Polyester Radial Leads				RESISTORS					
Electrolytic Axial Leads				Polystyrene, Axial, ±1% Tol., >63V DC Wkg.				Dipped Type, C280/352 Style				Carbon Film, Fixed					
-10% to +50% Tol.				Ceramic Print, Radial, Low K, 100V DC Wkg.				Moulded Type, 10.2mm Pitch				0.25W, E24 Values (R0-10M, 5% Tol.)					
µF	V.d.c.	Order Code	Cap 018 + µF + V.d.c.	µF	424 (832)	µF	424 (832) 830	µF	352	360	µF	352	360	2 each	100/100 (Mult 10/Value)	Res R0/X	Order Code
1.0	5		40	1	100	18	7	0.1	352	360	0.1	352	360	3 each	150/100 (Mult 10/Value) <td>Res R0/X <td></td> </td>	Res R0/X <td></td>	
2.2	5		40	1.2	120	18	9	0.01	0.1	0.15	0.1	0.15	8	10			
3.3	5		40	1.5	150	18	9	0.022	6	7	0.22	9	11				
4.7	5		40	1.8	180	18	9	0.033	6	7	0.33	11	11				
6.8	5		40	2.2	220	18	9	0.047	6	7	0.47	14	14				
10	5		40	2.7	270	18	9	0.068	6	7	0.68	17	17				
15	5		40	3.3	330	20	9	0.1	6	8	1.0	21	21				
22	5		40	3.9	390	20	9	0.15	6	8	1.5	25	25				
33	5		40	4.7	470	20	9	0.22	6	8	2.2	30	30				
47	5		40	5.6	560	20	9	0.33	6	8	3.3	35	35				
68	5		40	6.8	680	20	9	0.47	6	8	4.7	38	38				
100	5		40	8.2	820	20	9	0.68	7	8	6.8	42	42				
150	5		40	10	1000	20	9	1.0	10	12	10	47	47				
220	5		40	15	1500	20	9	1.8	15	18	15	50	50				
330	5		40	22	2200	20	9	2.7	22	27	22	50	50				
470	5		40	33	3300	20	9	3.9	33	39	33	50	50				
680	5		40	47	4700	20	9	5.6	47	56	47	50	50				
1000	5		40	68	6800	20	9	8.2	68	82	68	50	50				
1500	5		40	82	8200	20	9	10	82	90	82	50	50				
2200	5		40	100	10000	20	9	15	100	120	100	50	50				

C.M.O.S.				74LS				LINEAR				SEMICONDUCTORS											
(BUFFERED)				Ceramic Print, Radial, Med K, 100V DC Wkg.				LM300N, LM300A, LM300B				OPTO ELECTRONICS											
HEF4001	22	HEF4044	105	HEF4517	136	74LS00	19	74LS03A	106	74LS174	141	74LS373	173	CA3046	84	LM914	5	2N3705	10	8C182L	12	BFX85	29
HEF4002	22	HEF4047	109	HEF4518	137	74LS01	19	74LS04	104	74LS175	141	74LS374	173	CA3080E	77	LM4001	5	2N3819	20	8C194L	11	BFY50	17
HEF4003	22	HEF4050	119	HEF4519	138	74LS02	19	74LS06	39	74LS181	206	74LS375	173	CA3140E	99	LM4002	5	2N3820	22	8C194L	12	BFV52	20
HEF4004	22	HEF4053	123	HEF4520	142	74LS03	19	74LS09	39	74LS190	117	74LS376	173	CA3140E	99	LM4007	7	2N3904	9	8C212L	11	BLX85	262
HEF4005	100	HEF4056	139	HEF4521	143	74LS04	19	74LS12	76	74LS191	117	74LS377	173	CA3140E	99	LM4007	7	2N3904	9	8C214	11	BRV39	50
HEF4006	100	HEF4059	143	HEF4522	144	74LS05	27	74LS13	76	74LS192	119	74LS378	173	CA3140E	99	LM4007	7	2N3904	9	8C214L	12	BSX20	21
HEF4007	22	HEF4062	147	HEF4523	145	74LS06	27	74LS14	43	74LS193	119	74LS379	173	CA3140E	99	LM4007	7	2N3904	9	8C214L	12	BSX20	21
HEF4008	22	HEF4065	151	HEF4524	146	74LS07	27	74LS15	43	74LS194	119	74LS380	173	CA3140E	99	LM4007	7	2N3904	9	8C214L	12	BSX20	21
HEF4009	22	HEF4068	155	HEF4525	147	74LS08	27	74LS16	43	74LS195	119	74LS381	173	CA3140E	99	LM4007	7	2N3904	9	8C214L	12	BSX20	21
HEF4010	22	HEF4071	159	HEF4526	148	74LS09	27	74LS17	43	74LS196	119	74LS382	173	CA3140E	99	LM4007	7	2N3904	9	8C214L	12	BSX20	21
HEF4011	22	HEF4074	163	HEF4527	149	74LS10	27	74LS18	43	74LS197	119	74LS383	173	CA3140E	99	LM4007	7	2N3904	9	8C214L	12	BSX20	21
HEF4012	22	HEF4077	167	HEF4528	150	74LS11	27	74LS19	43	74LS198	119	74LS384	173	CA3140E	99	LM4007	7	2N3904	9	8C214L	12	BSX20	21
HEF4013	22	HEF4080	171	HEF4529	151	74LS12	27	74LS20	43	74LS199	119	74LS385	173	CA3140E	99	LM4007	7	2N3904	9	8C214L	12	BSX20	21
HEF4014	22	HEF4083	175	HEF4530	152	74LS13	27	74LS21	43	74LS200	119	74LS386	173	CA3140E	99	LM4007	7	2N3904	9	8C214L	12	BSX20	21
HEF4015	22	HEF4086	179	HEF4531	153	74LS14	27	74LS22	43	74LS201	119	74LS387	173	CA3140E	99	LM4007	7	2N3904	9	8C214L	12	BSX20	21
HEF4016	22	HEF4089	183	HEF4532	154	74LS15	27	74LS23	43	74LS202	119	74LS388	173	CA3140E	99	LM4007	7	2N3904	9	8C214L	12	BSX20	21
HEF4017	22	HEF4092	187	HEF4533	155	74LS16	27	74LS24	43	74LS203	119	74LS389	173	CA3140E	99	LM4007	7	2N3904	9	8C214L	12	BSX20	21
HEF4018	22	HEF4095	191	HEF4534	156	74LS17	27	74LS25	43	74LS204	119	74LS390	173	CA3140E	99	LM4007	7	2N3904	9	8C214L	12	BSX20	21
HEF4019	22	HEF4098	195	HEF4535	157	74LS18	27	74LS26	43	74LS205	119	74LS391	173	CA3140E	99	LM4007	7	2N3904	9	8C214L	12	BSX20	21
HEF4020	22	HEF4101	199	HEF4536	158	74LS19	27	74LS27	43	74LS206	119	74LS392	173	CA3140E	99	LM4007	7	2N3904	9	8C214L	12	BSX20	21
HEF4021	22	HEF4104	203	HEF4537	159	74LS20	27	74LS28	43	74LS207	119	74LS393	173	CA3140E	99	LM4007	7	2N3904	9	8C214L	12	BSX20	21
HEF4022	22	HEF4107	207	HEF4538	160	74LS21	27	74LS29	43	74LS208	119	74LS394	173	CA3140E	99	LM4007	7	2N3904	9	8C214L	12	BSX20	21
HEF4023	22	HEF4110	211	HEF4539	161	74LS22	27	74LS30	43	74LS209	119	74LS395	173	CA3140E	99	LM4007	7	2N3904	9	8C214L	12	BSX20	21
HEF4024	22	HEF4113	215	HEF4540	162	74LS23	27	74LS31	43	74LS210	119	74LS396	173	CA3140E	99	LM4007	7	2N3904	9	8C214L	12	BSX20	21
HEF4025	22	HEF4116	219	HEF4541	163	74LS24	27	74LS32	43	74LS211	119	74LS397	173	CA3140E	99	LM4007	7	2N3904	9	8C214L	12	BSX20	21
HEF4026	22	HEF4119	223	HEF4542	164	74LS25	27	74LS33	43	74LS212	119	74LS398	173	CA3140E	99	LM4007	7	2N3904	9	8C214L	12	BSX20	21
HEF4027	22	HEF4122	227	HEF4543	165	74LS26	27	74LS34	43	74LS213	119	74LS399	173	CA3140E	99	LM4007	7	2N3904	9	8C214L	12	BSX20	21
HEF4028	22	HEF4125	231	HEF4544	166	74LS27	27	74LS35	43	74LS214	119	74LS400	173	CA3140E	99	LM4007	7	2N3904	9	8C214L	12	BSX20	21
HEF4029	22	HEF4128	235	HEF4545	167	74LS28	27	74LS36	43	74LS215	119	74LS401	173	CA3140E	99	LM4007	7	2N3904	9	8C214L	12	BSX20	21
HEF4030	22	HEF4131	239	HEF4546	168	74LS29	27	74LS37	43	74LS216	119	74LS402	173	CA3140E	99	LM4007	7	2N3904	9	8C214L	12	BSX20	21
HEF4031	22	HEF4134	243	HEF4547	169	74LS30	27	74LS38	43	74LS217	119	74LS403	173	CA3140E	99	LM4007	7	2N3904	9	8C214L	12	BSX20	21
HEF4032	22	HEF4137	247	HEF4548	170	74LS31	27	74LS39	43	74LS218	119	74LS404	173	CA3140E	99	LM4007	7	2N3904	9	8C214L	12	BSX20	21
HEF4033	22	HEF4140	251	HEF4549	171	74LS32	27	74LS40	43	74LS219	119	74LS405	173	CA3140E	99	LM4007	7	2N3904	9	8C214L	12	BSX20	21
HEF4034	22	HEF4143	255	HEF4550	172	74LS33	27	74LS41	43	74LS220	119	74LS406	173	CA3140E	99	LM4007	7	2N3904	9	8C214L	12	BSX20	21
HEF4035	22	HEF4146	259	HEF4551	173	74LS34	27	74LS42	43	74LS221	119	74LS407	173	CA3140E	99	LM4007	7	2N3904	9	8C214L	12	BSX20	21
HEF4036	22	HEF4149	263	HEF4552																			

ETI NEXT MONTH

Vocoder

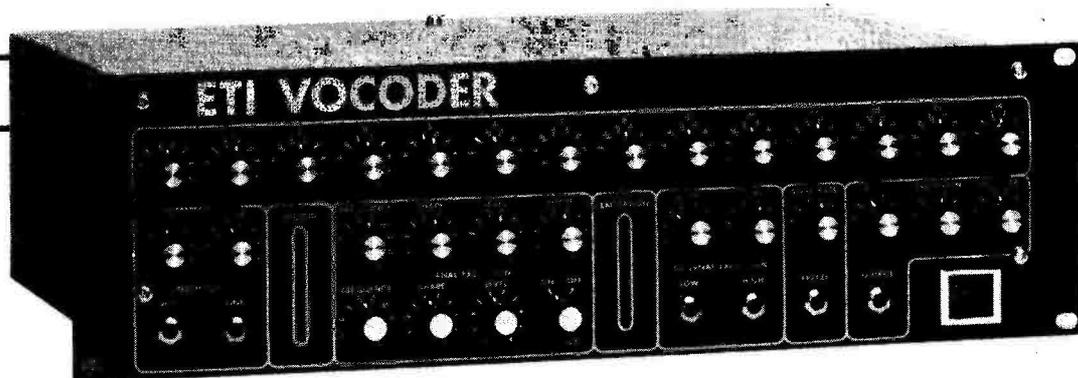

Now you can make your own synthesiser or guitar or even your cat speak or sing to you. This design uses 14 channels and has all the goodies like LED PPM meters, slew rate control, voiced/unvoiced detector and very versatile internal excitation! What more could you ask for? The ETI Vocoder's got the lot.

TV Sound Amplifier

You've read the book and seen the film. Now hear the TV version AS IT REALLY IS! Yes folks true glorious hi-fi sound from your telly! Broadcast sound is of an incredibly high standard and TV sound circuits are of an incredibly LOW standard. What a waste.

Improve your viewing and give your ears a treat by playing Crossroads in high fidelity. No messy wiring into the set either, its all self contained — complete with monitor amp — and is easily constructed.

Survival

The time interval is getting shorter and the ladder higher. Your opponent has turned up the skill level to maximum — one tiny slip and you're gonna hit the bottom and hard. Can you make it to the top? Can you survive? Good game, Good game!

Very Low Level Circuit Design

An absorbing article on the obstacles to be overcome at signal levels of a few microvolts and less. How do you minimise noise problems, when the amplitude of the noise is comparable to the amplitude of the signal? How about obtaining a decent gain without increasing hum pickup? An unusual and intriguing subject well explained.

Digital Test Meter

If we told you that next month we are running what is probably the ultimate digital meter project would you believe us? Probably not — but try anyway, because its true! You name it, this box will measure it — accurately. Frequency, voltage, resistance, current etc etc. It has an LCD display and costs a lot less to build than you think.

Articles mentioned herein are in an advanced state of preparation. However, circumstances may dictate changes to the final contents.

555 APPLICATIONS

In this chapter from his new book, Jules H. Gilder provides twenty circuits for the motorist employing the ubiquitous 555 timer

Our thanks to Newnes Butterworth for their kind permission to reproduce this extract from their book. The chapter is shown exactly as it appears in the original and gives a good indication of the high standards throughout the book.

6.1 electronic ignition system*

A capacitive-discharge automobile ignition system can be built with commonly available components. The system (Fig. 6-1) employs a 555 timer, which operates in an asynchronous square-wave mode, to drive the system's converter section. Thus, a common 6.3-V center-tap filament transformer of good quality can be used as the converter transformer. The rectified output of the converter transformer charges C2 to approximately 500 V dc.

When the points open, a positive-voltage pulse is coupled through R10, CR6, and C4 to the gate of the 2N4444 SCR. When the SCR fires, C2 discharges through the spark coil and starts to recharge with the opposite polarity. This polarity reversal provides a negative charge through R8 and CR8 to the SCR gate to prevent its retriggering after the SCR turns off.

When the points close, they discharge C4 through R9 and R10 so the SCR can be retriggered. The time required for this discharge provides delay to prevent erratic SCR firing caused by point bounce at high engine rpm.

This circuit is in actual use and has been bench-tested to an equivalent of 15,000 rpm on an eight-cylinder engine. With careful shopping, the entire system can be built for less than \$15.

6.2 voltage regulator†

A 555-type IC timer, in combination with a power Darlington transistor pair, can provide low-cost automotive voltage regulation. Such a regulator can even make it easier to start a car in cold weather.

* Morgan, L. G., "Electronic Ignition System Uses Standard Components," *Electronic Design*, Nov. 22, 1974, p. 198.

† Fusar, T. J., "IC Timer Makes Economical Automobile Voltage Regulator," reprinted from *Electronics*, Feb. 21, 1974, copyright © McGraw-Hill Inc., 1974. All rights reserved.


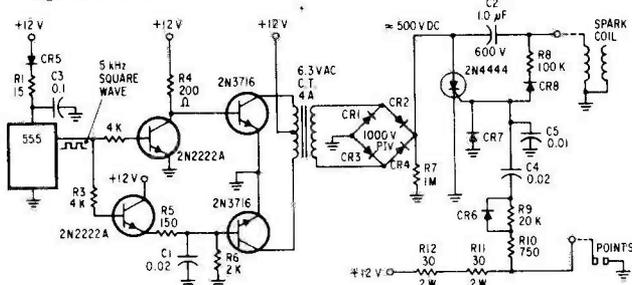


Fig. 6-1. Electronic ignition system.

As Fig. 6-2 shows, the circuit requires very few parts. The value of resistor R1 is chosen to prevent the timer's quiescent current, when the timer is off (output, pin 3, low), from turning on the Darlington pair.

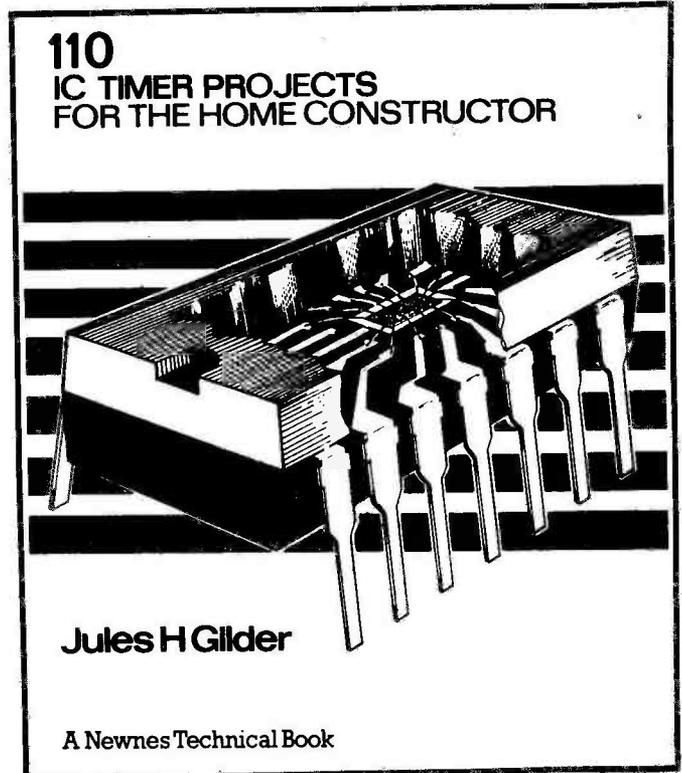If battery voltage becomes too low, the timer turns on, driving its output high and drawing a current of about 60 mA through resistor R2. This causes a sufficient biasing voltage to be developed across



resistor R1 and the Darlington turns on supplying the energizing current to the field coil of the car's alternator. Diode D1 suppresses the reverse voltage of the field coil when the Darlington pair is turned off.

The regulator's low-voltage turnon point is fixed by setting the voltage at the timer's trigger input (pin 2) to approximately half the reference voltage existing at its control-voltage input (pin 5). The high-voltage turnoff point is set by making the voltage at the timer's threshold input (pin 6) equal to the reference voltage at pin 6. At 77°F, the turnon voltage is typically 14.4 V, and the turnoff voltage is typically 14.9 V. These voltage levels, of course, should be set to match the charging requirement of a given car's specific battery-alternator combination.

The value of the reference voltage is established by the diode string D2 through D5; here, it is approximately 5.9 V. The output voltage has a negative temperature coefficient of $-11 \text{ mV}/^\circ\text{F}$.

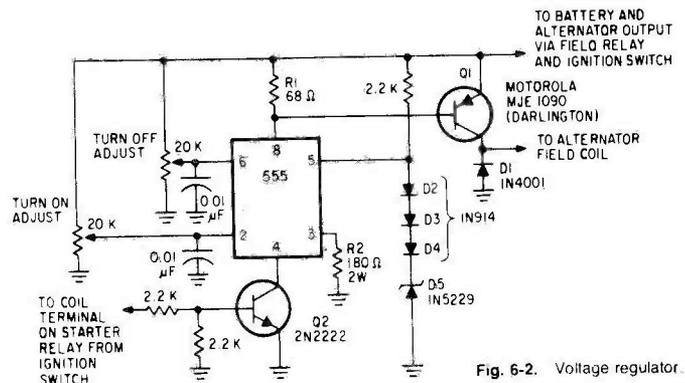


Fig. 6-2. Voltage regulator.

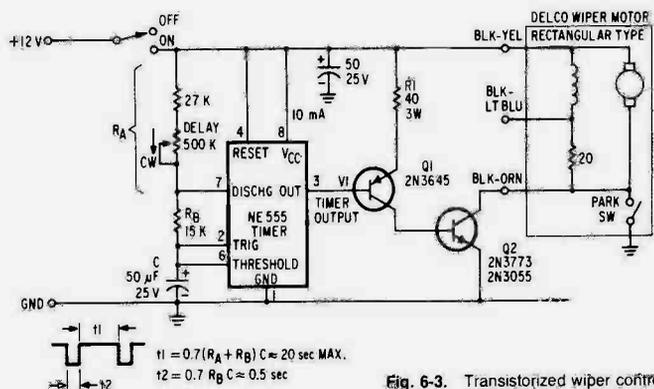


Fig. 6-3. Transistorized wiper control.

A transistor and a couple of resistors can be added to the circuit for better cold-weather starting. During starting, the transistor holds the timer in its off state lightening the load on the car's cranking motor. (And to prevent radio interference, a 10- μ F capacitor can be connected from the Darlington emitter to ground.)

6.3 transistorized wiper control*

An all-solid-state automobile wiper-control circuit allows the windshield wiper to sweep at selected frequencies from once a second to once every 20 sec. The circuit (Fig. 6-3) uses one IC, two silicon transistors, and seven discrete components.

Circuit timing is determined by a 555-timer IC and its external parts, R_A , R_B , and C . Transistor Q1 is switched on when V1 goes low, and npn transistor Q2 also turns on. The mechanical park switch takes over and conducts the motor current until one cycle of wiper motion is complete. At wiper park, the park switch opens and stops the wiper.

* Galluzzi, P., "Circuit Provides Slow Auto-Wiper Cycling with One to 20 Seconds Between Sweeps," *Electronic Design*, Dec. 26, 1974, p. 108.

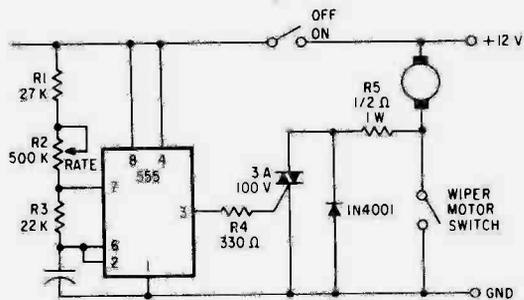


Fig. 6-4. Thyristor-switched wiper control.

Transistors Q1 and Q2 conduct for only about 0.5 sec. They do not conduct again until the next timer pulse. The delay between pulses is adjusted with the 500-k Ω delay resistor.

Resistor R1 limits the current into Q1 and the base of Q2. The peak collector current into Q2 is about 3 A. Since the duty cycle is normally very low, little heating occurs.

This circuit is in use on a GM-Delco rectangular-motor wiper system.

6.4 thyristor-switched wiper control

As in the previous circuit, the delay in this unit is adjustable from about 1-20 sec. The major difference between this wiper control (Fig. 6-4) and the earlier one is that this one uses a thyristor to do the switching. Like circuit 6.3, it is meant for cars in which the switch for the wiper motor breaks a connection to ground.

Diode D1 (1N4001) is included to prevent the back emf that is produced when the wiper opens at the end of a cycle from retriggering the thyristor and switching it on again without waiting for the delay. The diode can do this because it has a zener breakdown that is lower than that of the thyristor.

The addition of resistor R5 is to ensure that the current through the thyristor falls enough for it to switch off when the wiper contact closes. It may be necessary to increase the value of it a bit if this does not happen.

6.5 relay-switched wiper control

This wiper control (Fig. 6-5) is a more deluxe version of the two preceding ones. It uses a relay to perform the switching for the wiper and is meant for wiper motors whose switch breaks a connection to the

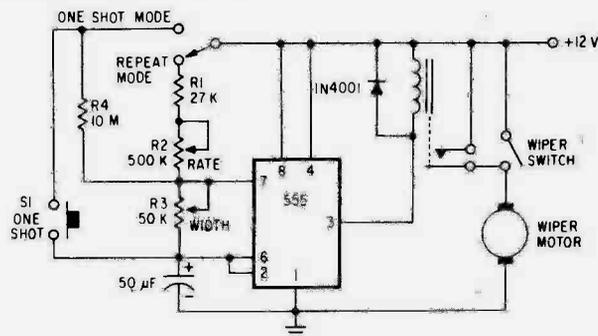


Fig. 6-5. Relay-switched wiper control.

positive supply rail (that could be changed by simply connecting the relay contacts to another spot).

The 555 astable drives a relay with a frequency that is adjustable by R2. A feature of this unit, which was not on the others, is that it has a variable-width control, so that the amount of time that the relay is on can be adjusted.

Another feature of this wiper control is that it offers two modes of operation: the normal cyclical mode and a one-shot mode. In the one-shot mode, the wipers can be activated for one cycle by pressing button S1 momentarily. If the button is not pressed again, in about 5.5 min the unit will itself activate the wipers for one cycle. This can serve as a reminder that it is still on.

6.6 seat-belt alarm

For those of you who like to wear seat belts in the car and have trouble convincing others that they should too, this circuit is ideal. It is an astable multivibrator whose output is connected to a power amplifier and a speaker (Fig. 6-6).

The loud wail that this circuit produces (about 5 W) should convince anyone to put on his seat belt, because that's the only way to stop it. It works like this: a magnetic reed switch that is normally open when there is no magnet near it is connected to the base of transistor Q1. So is R3. As long as the reed switch is open, R3 supplies current to the base of Q1 and turns it on. Q1 in turn permits current to flow to the astable circuit and the unit screams.

As soon as a magnet is brought near the reed switch, its contacts close, R3 is shorted to ground, Q1 turns off, and the oscillator turns off. All this takes place only if S2 is on, which occurs when someone sits in the seat. The reed switch and the magnet should be glued or

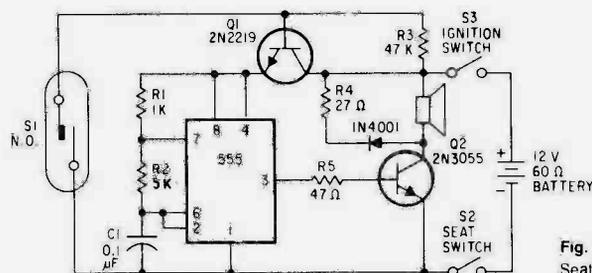


Fig. 6-6. Seat-belt alarm.

taped to the seat-belt buckle in such a way that when the seat belt is properly secured, they are in close proximity to one another.

6.7 seat-belt reminder

This circuit, unlike the previous one, does not force you to wear the seat belt when you are in the car. Rather, it reminds you that you should put it on, but obediently shuts up if you tell it to.

Once again, we see that the astable connection of the 555 is the one that comes in handy. Like the former circuit, this one (Fig. 6-7) uses a power amplifier on the output, to make sure you don't overlook the signal.

The hot lead for the circuit is connected to a point in the electrical system of the car that receives electricity only when the ignition switch is on. In most cars, a connection can be made to the supply lead for the radio. The ground lead for the timer circuit is connected to the anode

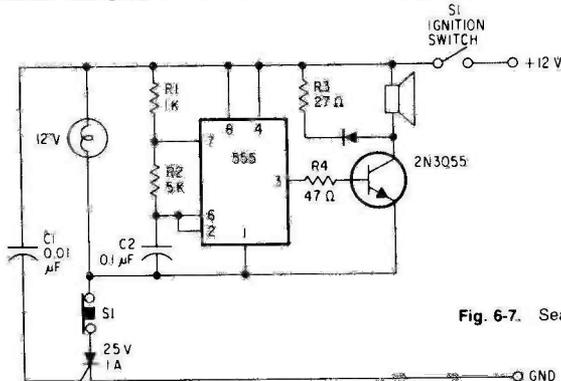


Fig. 6-7. Seat-belt reminder.

of an SCR via pushbutton S1. As long as the SCR is not triggered, the oscillator will not operate.

However, when the ignition is turned on, a pulse passes through capacitor C1 to the gate of the SCR, because for an instant, the capacitor behaves as a short circuit. The capacitor, however, quickly charges up and will prevent further triggering of the SCR. In the meantime, the SCR has been turned on by the trigger pulse and it acts as a short circuit so that now the astable starts to oscillate. The astable will remain on until the SCR is turned off. This is done by simply pressing on the pushbutton switch for a moment, to break the circuit.

The lamp in the circuit can serve a dual purpose. First, it is there to insure that enough current flows through the SCR so that it will remain in conduction. If the current is too low, as it might be with the astable circuit alone, the SCR would be starved and would not latch. Second, if the lamp is part of the switch assembly for S1, then it will be very easy to locate the shutoff switch at night, when the interior of the car is dark.

6.8 low-battery alarm

What's the condition of your car battery? Is it low? Have you ever checked it? Chances are you cannot answer any of these questions satisfactorily. And if not, then you need this circuit. It is a low-battery indicator that will sound a tone when the voltage on your battery drops below 10 V.

As seen in Fig. 6-8, a zener diode is chosen whose zener voltage is equal to the low-limit voltage of the battery under test.

In this case, it was decided that if the car battery voltage dropped to below 10 V, the alarm should go off. So a 10-V zener was selected. With the zener connected as it is, 10 V is dropped across the zener and 2 V is placed on the junction of R1 and R2. This causes transistor Q1 to conduct, which in turn prevents Q2 from conducting, hence no alarm.

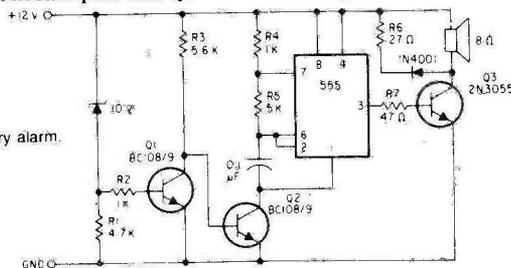


Fig. 6-8. Low-battery alarm.

However, if the voltage at the input to the circuit drops below 10 V, the zener diode will stop conducting and Q1 will turn off. This will cause Q2 to turn on, and will supply a ground return for the 555 oscillator, resulting in a tone being generated.

6.9 back-up alarm

Backing out of a long driveway can be dangerous, especially if there are small children around who cannot easily be seen. With this little circuit (Fig. 6-9), an audible warning tone will be sounded as soon as you put the car in reverse. The sound will stay on until you take the car out of reverse gear.

Basically, the device is an amplified oscillator whose output is used as the warning signal. For cars that have a separate set of back-up lights that turn on when the car is in reverse, connecting the unit to the car is extremely simple. In that case, the components inside the box are not needed and point A gets connected to the hot lead of the back-up lamp, while points B and C get connected together and are both connected to the chassis of the car (ground). Now whenever the car is put in reverse gear, the alarm, whose speaker should be mounted in the rear of the car so it can be heard, goes off.

But not all cars have separate back-up lights. Some of them turn on the blinker lights when the car is in reverse. In this case, the components in the box are needed and the circuit is constructed exactly as it appears in Fig. 6-9. In this case, points A and D are connected to the right and left rear blinker lights. Point A supplies power to the


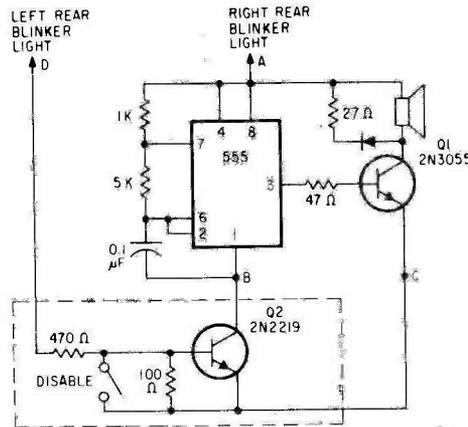


Fig. 6-9. Back-up alarm.

Fig. 6-10. Turn indicator.

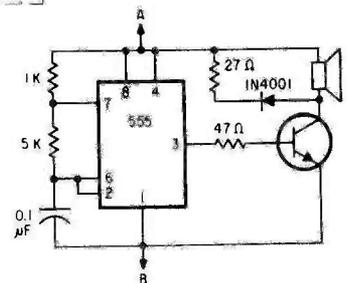

oscillator as normal and point D supplies power to the base of transistor Q2. This turns the transistor on and effectively shorts it to ground, causing the oscillator to work.

Remember, this happens only when both of the rear blinker lights are on at the same time. Thus, if your car has a hazard flasher that flashes the front and rear lights together, the back-up alarm will also turn on intermittently with the lights. To prevent this from happening, a disable switch has been included. This switch grounds the base of Q2 and prevents it from turning on.

6.10 turn indicator

Have you ever driven behind a person who had his turn indicator on but goes on for blocks on end without making a turn? It has probably happened to most of us at one time or another. The reason for this is that when the signal is turned on to indicate a lane change, or when one pulls away from the curb, the rotation of the steering wheel is not always enough to cause the mechanical return of the indicator switch. In addition, the clicking sound produced by the flasher inside the car is not always heard.

By using this circuit, which is very similar to the previous one, a loud flashing tone will be produced when the turn signal indicator is turned on, and turned off when the turn indicator goes off.

In the circuit shown in Fig. 6-10, point B is normally connected to the chassis of the car (for negative-ground cars). Point A has to get connected to a point that goes positive for each flash of the turn lights.

In some cars, where there is only one indicator light on the dashboard, it is only necessary to connect point A to the hot side of the light bulb. In most cars, however, there are two turn signal indicators on the dashboard. In that case, point A should be connected to one of the terminals on the flasher module that goes on with each flash.

6.11 headlight extinguisher

An automatic headlight extinguisher (Fig. 6-11) will allow you to turn off the car's ignition and still have a light to open the door by at night. After a predetermined period of time, which can vary from 10 sec to 1 min, the headlights will automatically shut off. Not only does this give you enough light to find your key in the dark, it also prevents you from accidentally leaving the lights on and finding a dead battery in the morning.

It operates like this. When the car ignition is turned on, current flows through resistor R3 and diode D1 to the relay. The relay then pulls in and makes it possible to turn on the headlights. When the ignition switch is turned off, a negative-going pulse is generated and applied to the trigger input of the timer (pin 2). Since the timer is configured to operate in the monostable mode, the pulse causes the output of the timer to go high for a period of time determined by $t = 1.1(R1 + R2)C1$. In this case, the pulse width is adjustable from about 10 sec to 1 min. The output of the timer is connected to the relay so the relay stays high for the additional period of time after the ignition is turned off.

It should be noted that the headlights will stay on only if the headlight switch is not shut off. In addition, you must remember to turn off the headlight switch the next morning, or you'll be driving around all day with your lights on.

6.12 light alarm

This alarm unit is a handy accessory to use with the headlight extinguisher in the previous section. As in most of the alarm-type

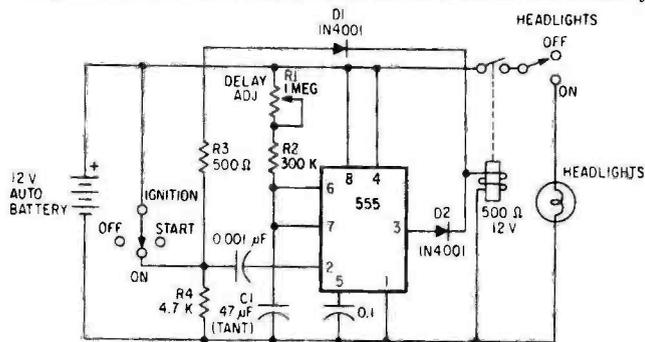


Fig. 6-11. Headlight extinguisher.

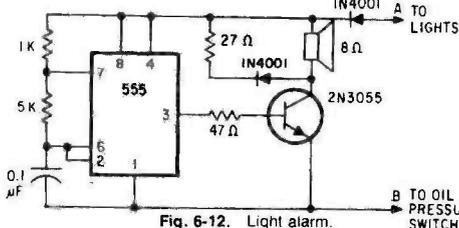


Fig. 6-12. Light alarm.

circuits, this one (Fig. 6-12) is composed chiefly of an amplified astable multivibrator. In addition, there is a diode in the positive power lead to protect the circuit from reverse voltages. Operation is very simple. When the ignition is on and the headlights are on, both point A and point B have +12 V applied to them, and the circuit has zero voltage drop across it so it does not operate.

When the ignition is turned off, however, the oil-pressure switch shorts to ground, and if the headlights are on, they supply power to the oscillator and a warning sound is generated.

6.13 automobile burglar alarm

With car theft on the rise, a good burglar alarm can be a useful thing to have. In Fig. 6-13 is a circuit for a simple alarm that uses a single 555 in the astable mode.

The alarm is connected to the already existing door switches that turn the dome light on when the door is opened. When the key switch, which is located on the fender of the car, is on, and one of the car doors is opened, a triggering voltage is applied to the gate of the SCR. This turns the SCR on and causes it to latch. The SCR thus applies power to the astable circuit, which oscillates at a frequency of about 1.5 Hz.

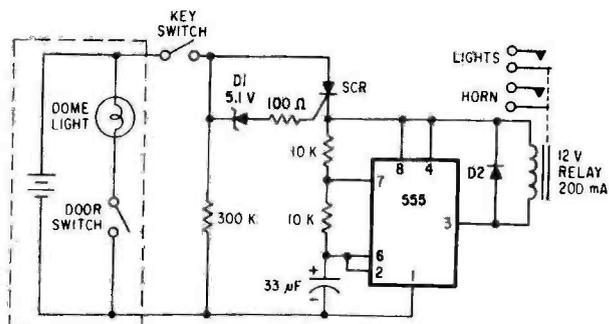


Fig. 6-13. Automobile burglar alarm.

The output of the oscillator drives a relay. Diode D2 is used to prevent the timer from latching on due to the back emf generated by the relay coil. If a double-pole relay is used, the circuit can turn both the horn and the headlights on and off. The horn blowing will surely scare away any potential thief, and the flashing headlights will indicate to passersby which car is being tampered with.

The SCR is used to latch the circuit on so that, even if the thief closes the car door right away, the alarm will stay on until it is shut off with the key switch.

6.14 keyless burglar alarm

A big disadvantage of the alarm in the previous section is that it requires that a key switch be mounted outside of the protected area, generally on the fender of the car. But by adding another timer, or using a dual timer such as the 556, an alarm circuit can be built that can be armed with a hidden switch that is located somewhere inside the car.

What makes this possible is the second timer, which introduces a time delay before it arms the alarm. As long as you leave the car and close the door before this delay period expires, you'll have no problems.

This circuit (Fig. 6-14) requires that special switches be installed at each door, because it cannot use the existing one. All of the switches must be connected in series and are all normally closed when the doors are shut. The door switches short out the timing capacitor of T2. When one of the doors is opened, the short across C4 is removed and the

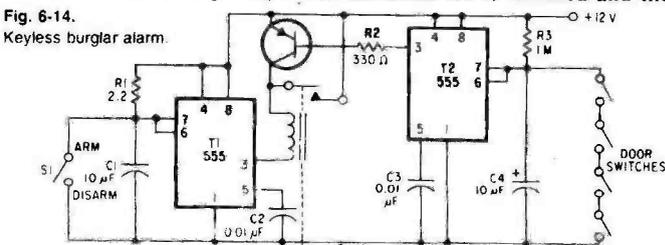


Fig. 6-14. Keyless burglar alarm.

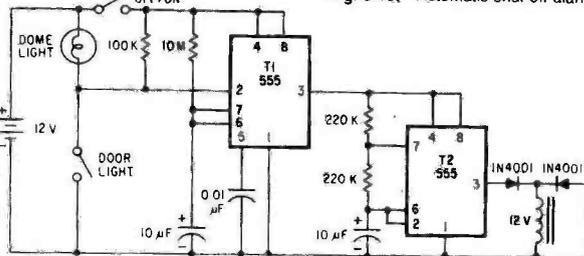


Fig. 6-15. Automatic shut-off alarm.

capacitor starts to charge up. This will take about 11 sec with the components shown. After 11 sec, the output voltage on pin 3 of T2 drops, and causes the transistor to turn on.

If the voltage at the output pin of T1 is low, the relay, driven by the transistor, will close. This does two things. It closes the contacts that are used to operate the car's horn and it also latches the relay on via a second set of contacts. Thus, the relay will remain on, and the horn will sound, as long as the output of T1 is low.

S1, the hidden switch, is used to arm and disarm the alarm and can be hidden somewhere inside the car. When S1 is closed, timing capacitor C2 is shorted and the voltage at the output of T1 is almost

at 12 V. Thus, the relay will not close when S1 is in this position. And if the alarm has been triggered, it may be silenced by closing S1.

To set the alarm, S1 is opened. You then have 25 (t = R1C1) sec to close all of the doors before the horn will sound. On returning to the car, you will have 11 sec (t = R3C4) to disarm the unit before the alarm sounds.

6.15 automatic shut-off alarm

A nice feature that neither the two previous alarm circuits has is automatic shutoff. This alarm (Fig. 6-15) uses two timers. T1 is set up as a monostable, which once triggered provides power to T2 for almost 2 min. T2 is set up as an astable that turns the relay on for 3 sec and off for 1, as long as it gets power from the monostable. After the monostable pulse ends, the alarm shuts off and is ready to be triggered again.

A big advantage of this circuit is that it uses existing door switches. And a key switch isn't absolutely necessary, although it does improve security. Here's how it works. S1 is the arming switch; it can be a key switch or simply hidden somewhere externally on the car. Once the alarm is triggered, it can only be shut off by opening S1. To turn the alarm circuit on, you get out of the car and lock all of the doors. Then turn on S1. Anyone who now opens a door will trigger the alarm, which will stay on for only 2 min unless the door remains open. In that case, the alarm continues to blow the car horn until 2 min after the door is shut or until S1 is opened.

6.16 engine immobilizer

An alarm alone is not sufficient protection from auto theft, especially if an experienced thief is involved. Generally, it's a good idea to have other obstacles in the way of the potential thief. One that is quite effective is an engine immobilizer.

Some immobilizers simply consist of a single-pole, single-throw (SPST) switch that is connected in parallel across the points in the distributor. When the switch is hidden, it does a fair job of making things difficult for a thief. But even they have discovered how to quickly recognize a switch of this type and can disconnect it in a matter of seconds.

But if the idea of an immobilizing switch is combined with a 555 timer, a good antitheft device can result. In Fig. 6-16 is the circuit of just such a device. The 555 is operated in its monostable mode, as a power-up monostable. That means it prevents power from being applied to the load until a certain time period (t = 1.1R1C1) has elapsed.

For our immobilizer, the monostable is connected to the 12-V supply via an arming switch, and the ignition switch. If the arming switch is closed and the ignition is turned on, current will flow to the monostable. The instant the timing capacitor starts to charge up, the output of the 555 goes high. Since the relay, which is connected to the timer's high output, is also connected to the positive 12-V supply, there is no voltage drop across the relay and it remains inactivated. Thus, the relay contacts remain open and the engine can be started.

The output of the timer remains high for 30 sec and therefore the car can be started and will run fine, but for only 30 sec. At that point,

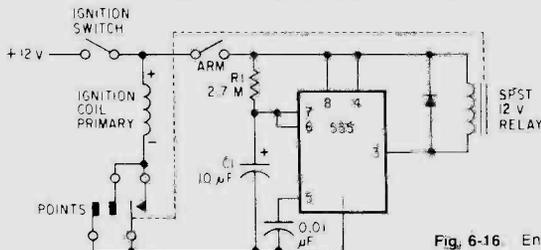


Fig. 6-16. Engine immobilizer.


the output of the timer will go low again and the relay will turn on, shorting out the points and cutting off the ignition circuit.

If the car is restarted, it will again run for 30 sec and stop. After two or three tries, any thief will abandon this troublesome car for one that is easier to move.

6.17 electronic turn flasher

An all-electronic alternative to the conventional turn-signal flasher is shown in Fig. 6-17. It offers the advantage of having an adjustable flash rate via R2 and overall higher efficiency. The flashing

Fig. 6-17. Electronic turn flasher.

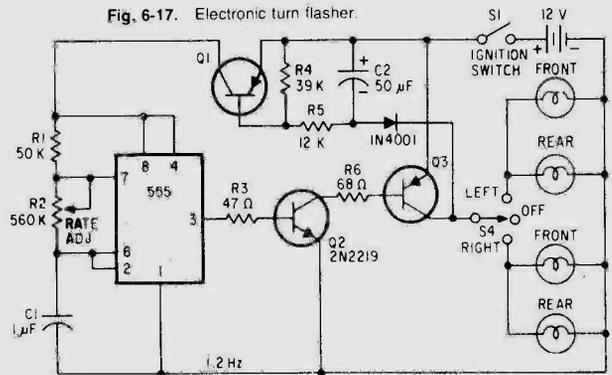

is produced by a 555 astable, but the most important part of the circuit is the circuitry that adapts the one-pole, three-position switch normally found in cars for operation with this circuit, which would ordinarily need a two-pole, three-position switch.

When the turn signal switch S2 is moved from the off position, it permits capacitor C2 to charge via the diode, and the base of transistor Q1 is held on via R5. This turns on Q1 and provides power to the astable. Q3 is prevented from discharging C2 by the diode.

As soon as the direction signal switch is returned to the normally off position, the bulbs stop flashing and shortly thereafter C3 becomes discharged and power is removed from the astable circuit.

6.18 light-up reminder

How often do you ride around in early evening and forget to turn your headlights on? If that happens to you, then this light-up reminder circuit is just what you need. By way of a flashing light in the car, it will tell you when the available light is low enough so that you should

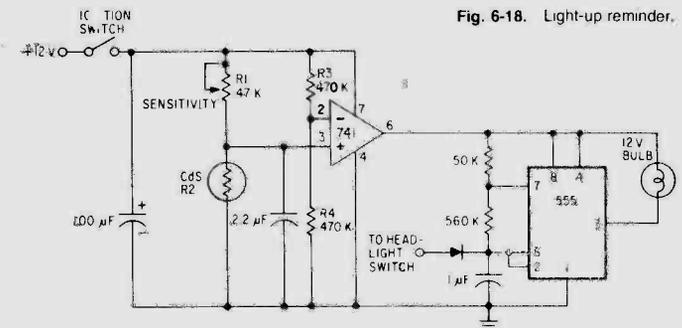


Fig. 6-18. Light-up reminder.

switch on your headlights. And, if you replace the astable circuit with a monostable and a relay, you can even have it turn the lights on for you automatically.

The circuit in Fig. 6-18 uses an operational amplifier as a comparator in a bridge circuit. R1 and R2 comprise one side of the bridge, while R3 and R4 make up the other. The inverting input of the op-amp is held at half the supply voltage by the R3R4 voltage divider. The voltage at pin 3, the noninverting input, is determined by the R1R2 divider. When the cadmium sulfide (CdS) photocell is brightly lit, its resistance is low and the voltage on pin 3 of the op-amp remains below that of pin 2. Under these conditions, the output of the op-amp will be a voltage that is very close to zero.

When darkness falls, the resistance of the CdS cell increases, thus raising the voltage at the noninverting input. When the voltage reaches the point where it is greater than the voltage on pin 2, the op-amp rapidly amplifies that small positive difference and produces a signal at its output that is close to 12 V. This is the signal that turns the warning circuit on.

The 555 timer is connected to the output pin of the 741 op-amp so that when its output goes high it receives power to cause it to oscillate. The oscillator can be used to drive a warning bulb, flashing it on and off.

Once you turn the lights on, you don't want the flashing light to bother you any more. This problem can be solved in one of two ways. Either you can place the photocell in such a way that it will be able to detect the light produced by the headlights as well as the ambient, or you can sense the voltage that is applied to the headlights.

FEATURE: 555 Applications

Sensing the voltage is really quite simple. All that is necessary is to connect a diode to the junction of pins 2 and 6 and the timing capacitor. The anode of the diode gets connected to the light switch, so that when voltage is applied to the headlights it is applied to the anode as well. What this does is to keep the timing capacitor constantly charged, and prevents the 555 from oscillating.

6.19 bad-light indicator

Many times you can drive your car without ever knowing that one or more of your lights isn't working. After all, who checks lights unless it's time to have the car inspected? Not many people, because it means you have to go in the car and turn the lights on then run around the car to make sure they're all working. And if you want to check your brake lights, you have to get another person to help you. One of you has to step on the brakes, while the other checks to see if the lights are on.

Well, checking your car lights can now be as simple as turning a knob. With the circuit in Fig. 6-19, all you have to do to check out all the lights on the car is to sit in the driver's seat and select the proper photocell to connect into the circuit.

In this case, the 555 is being used as a comparator. The photocell array and R1 and R2 compose a voltage divider. If a light is good, it illuminates one of the photocells and the resistance of that cell will drop. This will cause the voltage applied to pins 2 and 6 to rise. R2 is adjusted so that the voltage rise is above $\frac{2}{3}V_{cc}$. When that condition is met, the output of the 555 goes low and the voltage drop across the LED is close to zero. The LED doesn't light.

When a lamp is bad, the resistance of the photocell will be high. This causes the voltage at pins 2 and 6 to drop below $\frac{2}{3}V_{cc}$ and the output of the timer goes high, turning on the LED.

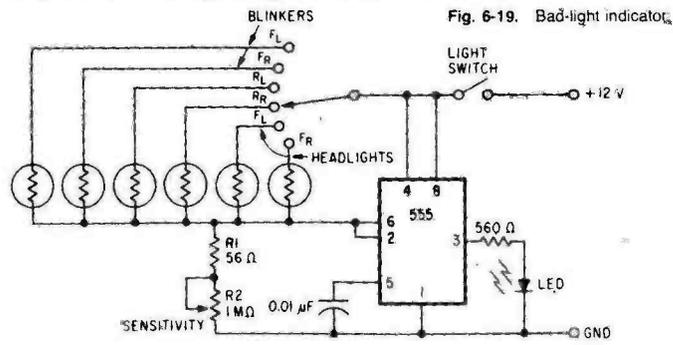


Fig. 6-20. Dome-light delay

6.20 dome-light delay

By configuring a monostable multivibrator so that it drives the line it senses, you can make a little device that will come in very handy: a delayed-extinguish dome light. This will be useful when you enter your car at night and have to fumble around until you find the ignition keyhole.

The circuit in Fig. 6-20 will keep the dome light on for an additional 15 sec before it turns it off. The time delay is figured out just like it is for a conventional monostable. The output drives a transistor that is connected across the door switch of the car and also to the trigger input.

When the door is opened, the switch shorts to ground and turns the light on. At the same time, it applies a negative spike to the trigger input and starts the monostable cycle. The output of the monostable goes high and stays high for the period $t = R1C1$. The high output turns on the transistor, which keeps a short across the door switch and keeps the dome light on.

Reprinted from '110 IC Timer Projects For The Home Constructor' by Jules H. Gilder, published by Newnes Technical Books, Borough Green, Sevenoaks, Kent TN15 8PH at £3.95.

ETI

CALCULATORS

SCIENTIFIC

***SPECIAL OFFER**
TEXAS T159 together with PC100C
(Complete as manufacturer's specifications)
£305.00

TEXAS/HP Accessories available	
*TEXAS T159 (Card prog 960 prog steps of 100 mem)	£158.50
*TEXAS T158 (Key prog 480 steps of 60 mem)	£60.00
*TEXAS PC100C (Printing Unit for T158/159)	£165.00
*TEXAS T157 (Key Prog 8 mem. 150 Keystrokes/50 Prog Steps)	£26.00

For your Texas T158/59 Calculator
ELECTRICAL ENG. MODULE
LEISURE (GAMES) MODULE
STRUCTURAL ENG. MODULE
NOW AVAILABLE

*TEXAS TI PROGRAMMER (Hexadecimal Oct)	£46.50
*TEXAS T151/iii (10 mem 32 Prog Steps Stat/Sci)	£28.50
TEXAS T150 LCD (Sci/Stat. 2 Con Mem)	£23.00
TEXAS T125 LCD (Sci/Stats)	£17.00
TEXAS T53 (Sci. 32 Prog Steps-Coa Mem +80 Prog List Applications book)	£25.00

Make more of your
Texas T158/59 Calculator
MATH/UTILITIES MODULE

If you write your own programs this library is for you! Most programs in this library are designed to be used either on their own or as subroutines of your programs. Applications range from utility programs such as printer formatting and large-scale plotting to advanced mathematical routines.

Module includes:

Prompter. Alpha Messages. Printer Formatting. Superplotter. Sorting. Data Arrays. Data Packing. Prime Factors. Hyperbolic Functions. Gamma/Factorial. Random Numbers. Normal Distribution. Interpolation. Roots of a Function. Minimax. Romberg Integration. Differential Equations. Discrete Fourier Series. Calculator Status. Variable Arithmetic. Module Check.	
*TEXAS T158 with Maths/Utilities	£90.00
*TEXAS T159 with Maths/Utilities	£186.50
*TEXAS T158 with Applied Statistics	£80.00
*TEXAS T159 with PC100C & Applied Statistics	£325.00

SUMMER SALE

*TEXAS T159 Calculator (complete as manufacturer's spec. master module, charger, etc.) PLUS statistics module and extra set of 40 Blank Prog. Cards with wallet, etc.
ONLY £180

NEW TEXAS T158C*

*Continuous program facility on all 480 Program steps/60 mem even when calculator switched off	£79.50
*TEXAS T158C (complete plus Applied Stats. Module)	£89.00
*TEXAS T158C + PC100C	£228.00

FREE while stocks last with every purchase of HP 32E or HP 33E
BATTERY HOLDER WITH RECHARGEABLE BATTERY* Normally costs £10.38
*HP 33E (8 mem Prog Sci/Stand £50.75)
*HP 32E (advanced SC1 with stand £40.50)

*HP67A (K Prog 224 Steps 26 Mem)	£188.70
*HP97A (Fully prog with Printer)	£384.35
HP41C (the newest calculator from HP)	£173.48
HP41C Card Reader/Printer etc. Modules	Now in stock
CASIO FXB100 (10 dig Sci/Stat. Stop Watch/Alarm)	£27.73
CASIO FX501P (Sci. LCD Prog. 128 Steps 11 Mem)	£47.50
CASIO FX502P (Sci. LCD Prog 256 Steps. 22 Mem)	£65.00
CASIO Prog Adaptor — permits Progs to be recorded on to standard cassette recorders for replay on Casio FX501P/FX502P at later stage	POA

LEXICON LANGUAGE TRANSLATOR

(With 6 Lang. Module — French / Italian / German / Spanish etc)

£128.70

NOW IT'S YOU AGAINST 'COMPUTERS'

CHESS CHALLENGER "7" (7 Levels of game)	£76.50
CHESS CHALLENGER "VOICE" (10 Levels — beginner to Master Plus) The strongest Prog yet in this series — twice as fast as the other challengers. A microprocessor with 128,000 to 160,000 bits of read only Mem. Over 8000 bits of Random Access Mem. Teaches opening & end game solutions. Plays against itself. Solves book problems etc — and in addition IT SPEAKS. Complete with Deluxe plywood board, hand carved men with magnetised base plus Deluxe carry case	£170.00
SARGON . The most advanced chess game yet with ad on module availability for other games (Our price inc. FREE rechargeable battery pack)	£279.00

FREE — mains / Charger included

LEARNING AIDS

TEXAS DATAMAN (Number Games-Table learning etc. 5/10 yrs)	£18.00
TEXAS SPELLING B (Spelling Games ideal 5/10 years)	£22.50
TEXAS SPEAK AND SPELL (for older children 8/13 years)	£39.95

IDEAL FOR STUDENTS

ALL WITH LCD DISPLAY	
TEXAS T120 (Un Sci + Con Mem)	£13.00
TEXAS T135 (Sci/Stat C Mem)	£17.00
TEXAS T138 (Sci/Con Mem Pola Rec Cony Dec Deg conv/ Deg Min Sec)	£19.95

GOODS FULLY GUARANTEED PRICES EXCLUDE VAT (ADD 15%)

Company / Hospital and Government orders accepted by phone

Barclaycard / Visa / Access accepted by phone

TEL. 01-455 9823

EXPORT ORDERS WELCOMED

Air Freight / Air Post Delivery
Quotations on request

MOUNTAINDENE

22 Cowper St., London, EC2

PRIME COMPONENTS LOW PRICES

Also our micro chips are at micro prices. Don't be fooled by low prices. We do not offer for sale, surplus, sub-spec or rebranded devices. All our parts are guaranteed new, first quality, factory prime, full spec devices. It is also our policy to offer you the best of new devices that become available and these are featured regularly. Prices are exclusive of p&p and VAT - please refer to "Ordering Information" before ordering. Official orders from Schools, Colleges, Universities and Gov. Authorities accepted.

DTL	
930	55p
935	65p
937	55p
944	65p
946	55p
957	55p
962	55p
9089	90p

7400	
7400	11p
7401	12p
7402	12p
7404	13p
7405	17p
7409	18p
7410	16p
7412	18p
7413	28p
7420	18p
7430	18p
7432	25p
7440	16p
7442	68p
7448	75p
7473	32p
7474	32p
7475	40p
7476	40p
7490	35p
7492	50p
7493	50p
7496	45p
74121	35p
74123	45p
74154	90p
74157	55p
74122	45p
74125	50p
74195	100p
74196	100p
74283	140p
74290	120p
74365	90p
74366	90p

74LS	
74LS00	18p
74LS01	12p
74LS04	15p
74LS08	20p
74LS10	19p
74LS11	30p
74LS12	30p
74LS14	80p
74LS15	38p
74LS20	19p
74LS30	19p
74LS32	25p
74LS40	26p
74LS42	58p
74LS47	78p
74LS48	85p
74LS49	95p
74LS73	30p
74LS75	35p
74LS86	39p
74LS90	40p
74LS107	40p
74LS123	69p
74LS125	50p
74LS138	79p
74LS151	75p
74LS153	75p
74LS155	65p
74LS161	78p
74LS163	90p
74LS164	90p
74LS168	190p
74LS174	99p
74LS175	99p
74LS195	87p
74LS221	110p
74LS244	375p
74LS245	325p
74LS252	110p
74LS290	95p
74LS329	120p
74LS366	57p
74LS372	170p
74LS374	170p
74LS376	140p
74LS377	180p
74LS393	135p
74LS490	140p
74LS670	260p

MEMORIES	
2114 450NS	250p
2114 300NS	275p
4116 200NS	300p
4116 150NS	395p
4315 (4Kx1) CMOS	495p
450NS	995p
6514 4K (1Kx4) CMOS	795p

MEMORIES	
2114 450NS	250p
2114 300NS	275p
4116 200NS	300p
4116 150NS	395p
4315 (4Kx1) CMOS	495p
450NS	995p
6514 4K (1Kx4) CMOS	795p

EPROMS	
1702A	450p
2708 450 NS	425p
2716 5V 450 NS	109p
2532 32K 450 NS	£39.95

UARTS	
AY-5-1013A	298p
AY-3-1015D	350p
IM6402	350p

CHARACTER GENERATOR	
RO-3 2513 UC	450p

KEYBOARD ENCODER	
AY-5 2376	795p

FLOPPY DISK CONTROLLERS	
F01771 B-01 Single density IBM Compatible	£29.95
F01791 B-01 Dual density IBM Compatible	£59.95

CPU'S	
6502	795p
6504	795p
6505	795p
6800	695p
6807	595p
8080A	995p
8085A	1095p
Z80	795p
Z80A	995p
Z8001	12500p
Z8002	9500p
WD9000B	19000p
Z8000D4	£10.99

SUPPORT DEVICES	
6520	45p
6522	795p
6532	895p
6851	1095p
6810	375p
6810	425p
6821	425p
6850	425p
6852	425p
8212	395p
8214	450p
8216	395p
8224	395p
8228	395p
8251	495p
8253	1125p
8255	485p
8257	1050p
8259	125p
MC14412VL	797p
Z80 PIO	595p
Z80A CTR	595p
Z80A CTR	595p
Z80A CTR	595p
Z80A DMA	2495p
Z80 SIO/0	2995p
Z80 SIO/1	3495p
Z80 SIO/2	3495p
Z80 SIO/2	3495p

INTERFACE LINEAR	
DM8123	125p
75150	125p
75154	125p
75182	195p
75322	250p
75324	325p
75325	325p
75361	350p
75365	295p
75451	50p
75491/2	75p
8726	175p
8728	175p
8795	175p
8797	175p

LEDS	
TIL209	9p
TIL211	13p
TIL212	15p
TIL220	12p
TIL222	15p
TIL224	18p

DISPLAYS	
FNDS00	80p
FNDS10	80p
FNDS56	125p
DL704	85p
DL707	85p
MV57164	225p

ISOLATORS	
IL074	120p
IL074	325p
MCT6	90p
TIL11	75p


SHIFT REGISTERS	
3341 PCFIFO 700KHZ	495p
3341 APC FIFO 1MHz	550p
3342 PC 64 bit shift register	495p
3347 PC 80 bit shift register	495p

DIL SWITCHES	
4 pole	99p
6 pole	115p
8 pole	140p

VOLTAGE REGULATORS	
7805/7812	55p
7905/7912	65p
78H05SC	575p
78HGKC	625p

SE 01 Sound Effects Kit

The SE-01 is a complete kit that contains all the parts to build a programmable sound effects generator. Designed under the new Texas Instruments SN 78477, Sound Chip, this board provides banks of MINI DIP switches and pots to program the various combinations of the SLF Oscillator, VCO, Noise, One Shot, and Envelope Controls. A Quad Op Amp IC is used to implement an Adjustable Pulse Generator, Level Comparator and Multiplex Oscillator for even more versatility. The 3 1/4" x 3" PC Board features a prototype area to allow for user added circuitry. Easily programmed to duplicate **Explosion, Phaser Guns, Steam Trains, or almost an infinite number of other sounds.** The low price includes all parts, assembly manual, programming charts, and detailed 76477 chip specifications. It runs on a 9V battery (not included). On board 100W amp will drive a small speaker directly, or the unit can be connected to your stereo with incredible results! (Speaker not included.)

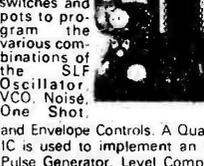

COMPLETE KIT ONLY £14.99
P&P 67p + VAT

UNIVERSAL SCR

C106D 400V/5A Sale 30p



This incredible music machine is based on the new GI Tunes Synthesizer chip AY-3-1350 which has a set of 25 different popular and classical tunes. In addition there are three different chimes. Use it for a musical door bell, up to 4 different mobile home toy or music box. Super easy to build. Tunes include STAR WARS, BEETHOVEN'S 5th and 9th JINGLE BELLS, YANKEE DOODLE, CLEMENINE, GOD SAVE THE QUEEN, WESTMINSTER CHIME and DESCENDING OCTAVE CHIMES plus many more. Envelope control gives piano or organ quality and there is facility for playing all the tunes in a Sequence! Works from 12V AC or DC or from mains via 240V transformer (not supplied).

LED BAR GRAPH AND ANALOG METER DRIVER

New from National LM3914. Drives 10 LED directly for making bar graphs, audio power meters, analog meters, LED Oscillators etc. Units can be stacked for more LEDs. A super versatile and truly remarkable IC. Special price. Only £2.25. 12 page data 75p. Matching red bar display MV57164 £2.25 Data 25p.

LIQUID CRYSTAL DISPLAY

● High Contrast Ratio
● 0.5 in. Digit Height
● ULTRA Low Power Consumption
LCD 106 £6.45

4K CMOS (1K x 4) 450NS ONLY £7.95

★ Low Power Dissipation
● 10pW/BIT (TYP) @ 3.0V (STANDBY)
● 100V/BIT (TYP) @ 5.0V (OPERATING)
★ Data Retention Voltage 2V to 5V
★ Single 5V Power Supply

From Toshiba. The TC5514P (industry type 6514) is a full static read/write memory organised as 1024 words by 4 bits using CMOS technology. Because of ultra low power dissipation, the TC5514P can be used as battery operated portable memory system and as a nonvolatile memory with battery back-up. The TC5514P operates from a single 5V power supply with a static operation, so that the no refresh periods are required. This simplifies the power supply circuit design.

The three state outputs simplify the memory expansion making the TC5514P suitable for use in a microprocessor peripheral memory. Since the minimum data retention voltage is 2V, the battery back-up system needs only simple circuitry. By using Toshiba's original CMOS technology, the device circuitry is not only simplified but wide operating margin and noise margin are also realised.

The TC5514P is mounted in a dual in line 18-pin plastic package. 0.3 inch in width.

X-RATED CLOCK!

ONLY £19.99
Custom built impact moulded case with ruby lens. £4.99 P&P 82p + VAT

ZULU II CLOCK KIT

WITH CALENDAR AND NOXIM CIRCUIT

X-TRA VALUE. All the components and high quality plated G-10 PC Boards are provided.
X-TRA CARE IN DESIGN. No wires between readout board and clock board. Large open layout.
X-CELLENCE IN IDEAS. 5 years of designed products for the amateur radio market.
X-CELLENCE IN INSTRUCTIONS. Clear step-by-step instructions with quality illustrations. The assembly manual is not a read-between-the-lines afterthought!

X-TRA FEATURES. There has never been a clock kit with so many features - at any price!
● Unit operates on either 12 VAC or 120 VDC.
● On board QUARTZ XTAL TIMEBASE.
● Automatic BATTERY BACKUP. Never worry about power failures again!
● Reads true 24 HOUR TIME and 31 DAY CALENDAR.
● Unique NOXIM CIRCUIT activates readouts with a handclap or they can be turned on constantly.
● When used mobile readouts blank ignition is off.
● Special NOISE SUPPRESSION and battery reversal circuits.
● Bright 1/2" LED's show hours, minute and seconds.

Just clap your hands and the time appears for 5 seconds followed by the date for 4 seconds. A low cost 9V transistor battery provides stand by power in the event of power failures up to 4 hours. With the addition of a low cost 12V 300 MA transformer, the unit will work on AC.

ULTRASONIC SENDER RECEIVER KIT

ONLY £19.93 P&P 67p + VAT

TOTAL SECURITY! Completely invisible ultrasonic (23KHz) Sound beam works like a photoelectric beam but is unaffected by light, heat or noise. Separate Transmitter and Receiver can be used from 6 inches to 25 feet! A solid object breaking the beam causes an output to go low that will sink up to 150 MA to Drive a Relay, TRIAC, etc. Complete electronics are provided. Works on 12VDC (unregulated) and draws less than 100 MA. Use it for burglar alarms, object counters, automatic door openers, automatic door bells, electronic rat trap(?) and more.

ONLY £19.93 P&P 67p + VAT

WARBLE ALARM Kit

A fun EASY kit to assemble that emits an ear piercing 10 watt dual tone scream. Resembles European siren sound. Great for alarms or toys. Operates from 5-12VDC at up to 1 amp (using 12VDC @ 8 ohm speaker). Over five thousand have been sold. All parts including PC board, less speaker. ONLY £4.99 P&P 67p + VAT

LM1871 RC ENCODER/TRANSMITTER

LM1872 RC RECEIVER/DECODER

New from National. The LM1871 is a complete six channel digital proportional encoder and RF transmitter intended for use as a low power, non-voice unlicensed communication device at carrier frequencies of 27 MHz or 49 MHz with a field strength of 10,000 uV/meter at 3 meters. In addition to radio controlled hobby toy and industrial applications, the encoder section can provide a serial input of six words for hard wired, infra-red or fibre optic communication links. Channel add logic is provided to control the number of encoded channels from three to six, allowing increased design flexibility. When used with the LM1872 RC receiver/decoder, a low cost RF linked encoder and decoder system provides two analog and two ON/OFF decoded channels. Super versatile carrier frequency operation - on-chip RF oscillator/transmitter - one timing capacitor for six proportional channels - programmable number of channels - regulated RF output power - external modulator bandwidth control - on-chip 4.6V regulator - up to 80 MHz carrier frequency operation. LM1871 £5.50 LM1872 £5.50 Pair £10.50. Data sheets 25p each.

INTERMIL 8 Digit - 10 MegaHertz

Digital - Universal Counter Kit
Includes:
● ICM7226AIDC IC
● 10 MHz Quartz Crystal
● (8) 7 Segment 3 1/2" LED Displays
● PC Board
Order Part Number ICM7226AEV/Kit ONLY £49.95

THE ULTIMATE RECEIVER

Multiband Dynamic Sound Portable Radio. It's a monitor too - monitors all 40 CB channels, TV (VHF), PB, and WB.
MODEL 724C. ONLY £39.95 p.p. £4.95 8-Vand Receiver

STAR FEATURES: AM - CB1 - CB2 - TV1 - FM - PB - WB - TV5. Swivel Telescopic Antenna, Tuning & Battery Indicator, AC/DC Switch Control DC: 6V UM-1 (Size D) x 4 AC: 220V. AFC Switch Control Tone Control Nylon Shoulder Strap or Plastic Handle 4" PM Dynamic Speaker. Dimensions: W 230 x H 22 x D 90mm

JAPANESE TRANSISTOR SUBSTITUTION MANUAL

An invaluable Japanese to Japanese substitution guide for approximately 3,000 transistors.
● Covers the 2SA, 2SB, 2SC and 2SD series
● Introduction includes a guide to understanding Japanese transistors.
Only £3.95

JAPANESE TRANSISTOR SPECIFICATION MANUAL

This fantastic new specification manual covers:
● Specs on VC80, V80 IC, TJ, IC80, HFE and more!
● Includes mechanical drawings that illustrate case styles and sizing of each transistor.
Only £4.90

AY-3-8910 Bang

AY-3-8910 PROGRAMMABLE SOUND GENERATOR
The AY-3-8910 is a 40 pin LSI chip with three oscillators, three amplitude controls, programmable noise generator, three mixers, an envelope generator, and three D/A converters that are controlled by 8 BIT WORDS. No external pots or caps required. This chip hooked to an 8 bit microprocessor chip or Bus (8080, 280, 8800 etc.) can be software controlled to produce almost any sound. It will play three notes chords, make bangs, whistles, sirens, gunshots, explosions, bleats, whines, or grunts. In addition, it has provisions to control its own memory chips with two I/O ports. The chip requires +5V @ 75ma and a standard TTL clock oscillator. A truly incredible circuit. ONLY £8.25. 80 page manual with S-100 interface instructions for control. Custom programming examples £2.25 extra (No VAT).

PROGRAMMABLE DUAL OP TRANSCONDUCTANCE AMPLIFIER

New from National Semiconductor, the LM13600 is a programmable dual operation transconductance amplifier designed to be used as a fundamental building block in current controlled amplifiers, filters and oscillators. It can also be used in multi-pliers, timers and even sample and hold circuits. It is well suited for use in electronic organs and music synthesizers, because it can modulate waveforms with ease. The 16 pin LM13600 is programmable over six decades, allowing it to function as a basic building block in a broad range of electronically programmable resistors and filters. A truly remarkable circuit. ONLY £1.25 + VAT Data 25p.

LM13600 BAR/DOT DRIVER IC

Drives 10 LEDs with adjustable analog steps. Units are cascadeable up to 10 (100 steps). Drives LEDs directly. Great for voltage, current or audio displays. Similar in operation to LM3914 with specs and circuit notes.
ONLY £1.75

Matching red bar display MV57164 £2.25 Data 25p

Ordering information. Unless otherwise stated, lot orders under £50 add 50p p&p. Add 15% VAT to total. All items are subject to price sale and therefore subject to availability. Prices are subject to change without notice.

Micro Circuits

4 Meeting Street, Appledore, Nr. Bideford, North Devon EX39 1RY. Tel: Bideford (02372) 79507. Telex: 8953084

EMP (ELECTROMAGNETIC PULSE)

Nuclear war has never been a more real threat to humanity. Should the inconceivable occur — and an exchange take place — how well prepared are we in Britain to survive? This disturbing article from Graham Packer points out what appears to be a major weakness in Britain's defensive thinking.

Relations between the super-powers are deteriorating rapidly and with the ever growing 'nuclear club' of nations the possibility of such weapons being used in anger in the not too distant future is very real indeed.

It would appear that one major effect of such use is largely unknown by the general public and is, to say the least, being dealt with too lightly by the authorities. It is an effect that has catastrophic consequences for solid state communications and computing equipment and which could reveal any well laid plans to cope with "the Bomb" to be futile and mis-guided.

I, the author, am a freelance writer, principally upon the topics of communications and amateur radio. All the information has been gleaned from normal technical publications and text books and can be freely obtained by any member of the public who cares to look.

Besides the well publicised phenomena associated with the detonation of a nuclear device (i.e. blast, heat and light) there is the ELECTROMAGNETIC PULSE (EMP) to contend with. Since the first weapon trials in 1945 the 'radio flash', as it was then known, has been observed and documented. Only in recent years, however, have the full implications of the EMP become apparent. Damage to most radio, landline and computer equipment, up to a maximum range of 2500 k, from ground zero (the point of detonation), is not just possible, but *probable*.

Mechanisms That Produce EMP

There are three situations where an EMP can occur at high enough strengths (See Fig. 1.) to be deadly to electronic communications.

1. A WEAPON BURST AT GROUND LEVEL OR BELOW 100 m ABOVE GROUND LEVEL.
2. A VERY HIGH AIR-BURST AT THE TOP OF THE ATMOSPHERE.
3. AN EXO-ATMOSPHERIC BURST

In cases 1 & 2 the EMP appears to be caused by Compton electrons, produced by the initial, high energy, gamma flux radiating from the point of detonation. These cause a vast outward current flow — the pulse of energy known as EMP.

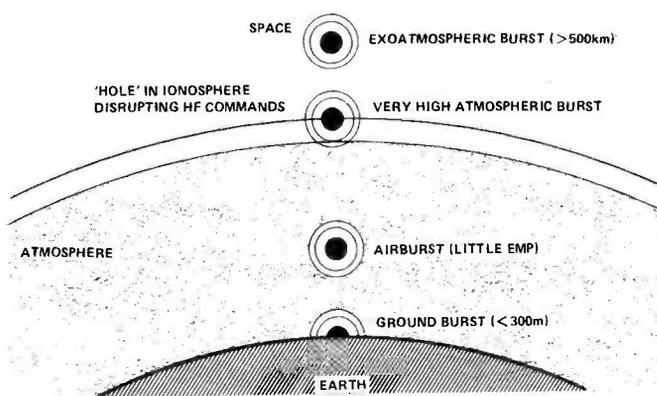


Fig. 1. The different methods of detonation of a nuclear device. Note that an airburst will maximise damage to surrounding environments physically but minimize EMP.

In the case of a ground burst an asymmetric condition exists and the energy is radiated upwards in electromagnetic form, away from the ground.

If a very high airburst occurs the reverse happens (as there are electrons to be excited only in the atmosphere and not in space). In this case the electromagnetic energy is radiated downwards in a particularly crippling manner.

If the weapon is 'air-burst' however, (between 10 m & 10 km say) the outward current flow is symmetrical and almost self cancelling. Fortunately, from an EMP point of view anyway, air bursts are the most efficient militarily, maximising heat and blast, and would probably constitute the majority of strikes in a major nuclear exchange.

An exo-atmospheric blast at, say, 1000 km altitude is the 'worst case'. With no absorptive medium surrounding the device, the energy from the weapon, mainly in the form of gamma and X-rays, reaches the upper atmosphere over a wide area simultaneously. Interaction with the electrons there causes a vast pulse of energy to be radiated downward over a huge area. EMP with a vengeance.

Effects Of The EMP

Neither the 1950 or 1957 issues of 'Effects of Nuclear Weapons' contain any reference to EMP. It is first mentioned in 1962 where a fairly brief description mentions that EMP is "of considerable interest". The 'interest' shown was in the results of the Johnstone Island exo-atmospheric test in 1958. This test produced failures to street lighting systems (presumably fed via overhead wiring) in Hawaii 1000 km away.

Unfortunately as the intensity of the effect was unexpected, no meaningful measurements of field strength were made.

Further tests were carried out and Fig.2 shows the field strengths to be expected from a one Megaton ground burst weapon, at various distances from ground zero.

Detonating that same weapon as an exo-atmospheric burst produces several thousand volts per metre over an area limited only by the curvature of the Earth! Figure 3 shows the areas in Europe that such a blast over the North Sea would encompass - producing widespread disruption to Europe's communications.

Whilst not violating any particular country's territorial integrity, (there being no blast or fall out associated with an exo-atmospheric blast) such a strike could well be a final 'sabre-rattling' exercise prior to commencement of more direct hostilities.

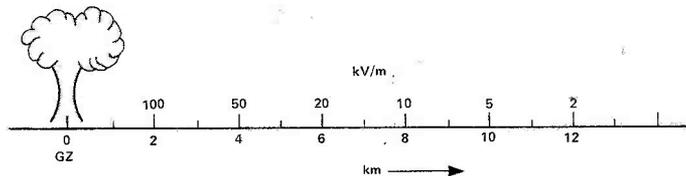


Fig. 2. The field strengths produced by detonating a one Megaton bomb. Remember too that a 20 Megaton warhead is very commonplace today - and to be expected in combat.

Of course Europe is not the only place that such a burst could be used and perusal of an atlas shows that there are other 'theatres' where an EMP could be generated such that 'innocent' countries (including perhaps the UK) would be subjected to its effect.

Rise Time

Figure 4 compares EMP to lightning. By comparison lightning can be seen as a very sluggish phenomena indeed! Rise times of 20 ns (20×10^{-9} seconds) have been reported, resulting in considerable energy up to several hundred of MHz. Radio amateurs and home computing enthusiasts need no reminding of the effects of large field strengths on their beloved electronics.

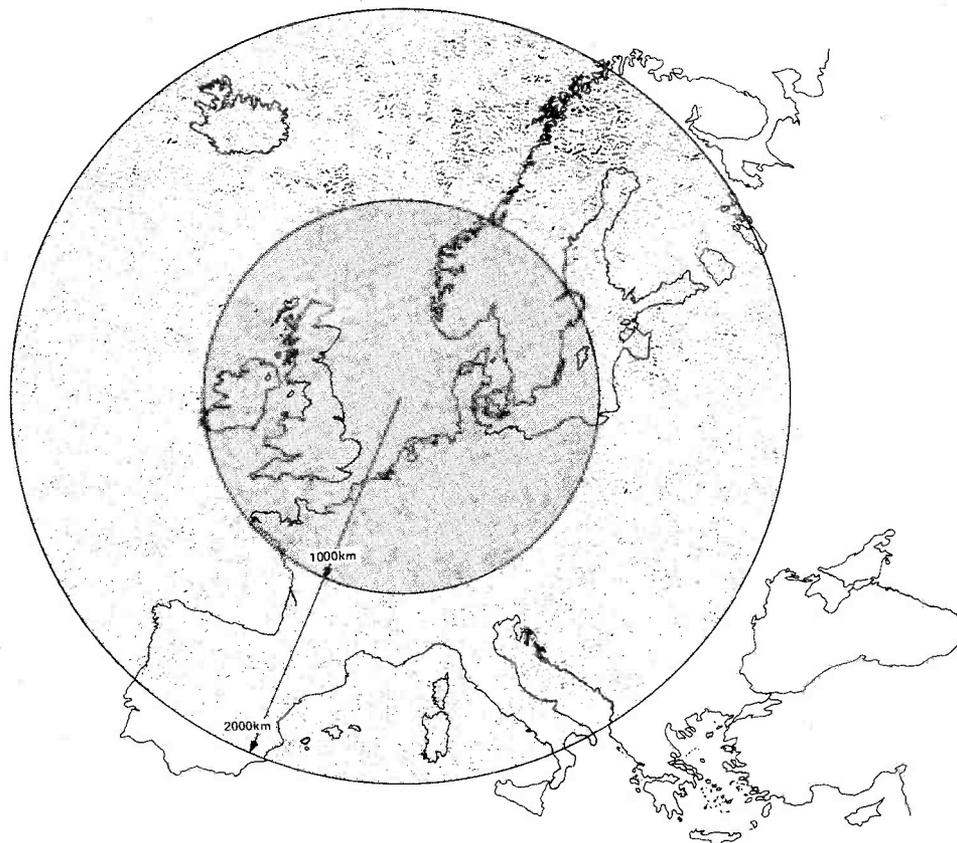


Fig. 3. A sketch of the European theatre, showing the level of effect from a one Megaton detonation over the North Sea. Such a blast does not actually infringe any single country's border integrity but affects all those shown.

The inner circle represents the radius of expected severe damage to equipment and the second circle is that within which some detrimental effect is to be expected.

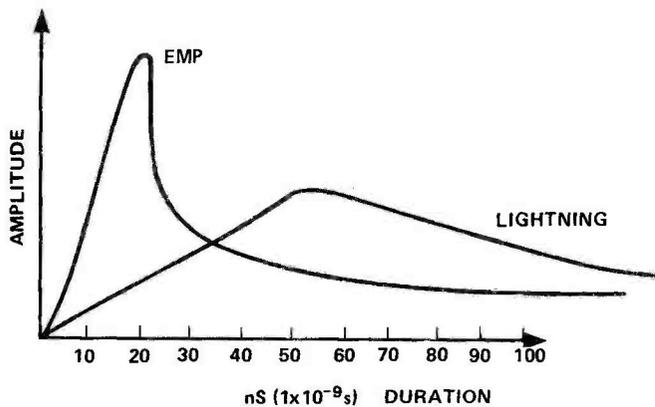


Fig. 4. Comparative rise-times of an EMP from a 1 Mt. bomb and an average lightning flash. Note that the EMP is many times faster.

Not for nothing do modern military receivers have POWER transistors and 2 W of local oscillator power present in the front ends! Don't entirely believe the sales talk about "large signal handling characteristics" that's just a spin off!

The interest shown in professional computer circles in 'line conditioners', 'transorbs' and RFI shielding has its roots in the military's requirements for protecting their data processing hardware.

EMP Collectors

HF aerials are of course text-book EMP 'collectors' and the increased use of broadband mixers and power output stages place this equipment especially at the risk from EMP.

However VALVE equipment is substantially immune to EMP — or can at least withstand levels of field strength orders of magnitude greater than solid state — rumour has it there could still be a place for '19' sets in World War III! (Russian and Warsaw Pact forces still employ valve equipment in quantity.)

Telephone lines, extending overhead for several kilometers at a time, are extremely vulnerable. They are being increasingly terminated in electronic exchanges, or transistor amplifiers WHICH ARE NOT EXPECTED to survive an EMP. Exit telephone communication.

Overhead power-lines are likewise excellent aerials and although the transient nature of EMP is unlikely to damage motors, tungsten lamps etc. etc, many pieces of electronic equipment, domestic, amateur and professional will be destroyed.

Table 1 gives items that are expected to survive or succumb to an EMP attack and should be carefully studied for the implicit effect upon Civil Defence communication after nuclear attack.

Radio Propagation

Little information seems to be available in the 'open' literature on radio propagation after a nuclear exchange. It is virtually certain that the ionosphere as we know it will be destroyed temporarily. The maximum usable frequency will probably be lowered dramatically (hence the vast low frequency, very low frequency and extremely low frequency military installations throughout the

TABLE 1

EQUIPMENT NOT EXPECTED TO SURVIVE EMP ATTACK

1. Fluorescent lights.
2. HF transistor transmitters and receivers, especially broadband.
3. VHF mobile equipment with long whip aerials.
4. VHF broadcast-band receivers with aerials extended.
5. All landline communications, especially electronic telephone exchanges.
6. Land "repeaters", which account for 90% of radio communication.

RELATIVELY IMMUNE EQUIPMENT

1. Tungsten lamps (or other filament).
2. Valve transmitters and receivers.
3. Electronic motors (NOT solid-state speed control)
4. Medium Wave portable with ferrite rod aerials.
5. SHF link equipment, AS LONG AS the feeder or waveguide does not conduct EMP to other parts of the equipment.

Study the table above carefully. It has far reaching implications. Ask yourself if a stable society could be set up, given the destruction of all viable long distance communications as a starting point.

world) and it is assumed that most satellite communications will cease. This will come about either as a direct result of the nuclear exchange, the 'satellite - killing' capability of the super-powers, or the 'neutralisation' of the satellite ground stations.

Conversely highly ionised patches could well result in sporadic 'E' beyond the wildest dreams of 2 m DX enthusiasts.

Conclusions

From the preceding it may be seen that deliberate detonation of a nuclear weapon to maximise the EMP effect could and probably would occur in a future conflict. This could effect this country even if the U.K. was not directly involved in the conflict itself.

Some possible measures to counteract the effects of EMP are given in Table 2, although without concerted action at a high level, Britain will remain very vulnerable to this type of attack.

TABLE 2

- | | |
|----|---|
| 1. | Disconnect all electronic equipment from aerials and power sources during that period. |
| 2. | Use Radio equipment 'on sked' for the minimum possible time. |
| 3. | Use high 'Q' ATU on HF or 'cavity' on VHF to reduce acceptance bandwidth to a minimum. |
| 4. | Earth all screens, coax outers etc. Treat as for massive TVI case. |
| 5. | Solder reverse parallel diodes across receiver front ends as for normal burnout protection. |
| 6. | Keep a supply of spare vital components such as front end transistors, diodes etc. in a screened container. |
| 7. | Consider the use of VALVE radios! |

DEATH BY NEGLIGENCE? It seems strange that such a potentially crippling product of nuclear warfare has received such little exposure to the public eye. Much has been made of late, by both press and TV, of the Soviet superiority in conventional, and indeed nuclear, materials and the effect upon this country of employing such forces against the West. It is to be hoped that such debate will bring with it much needed increases in the defence spending of this country.

Our Civil Defense programme could be well described as minimal, with little or no interest until recently in improving it. Compared to countries such as Sweden, Switzerland and - more significantly - the USSR, our efforts are nothing short of laughable.

Picture now some highly probable effects of an EMP upon our already pitiful survival resources. Telephone communications will be knocked out in most, if not all, parts of the country. Landline and repeater equipment used for the majority of communications in Britain, will be destroyed or rendered inoperative. All double frequency radio communication (i.e. anything using repeaters) will be impossible. All VHF broadcast receivers, with aerials extended, and mobile VHF equipment will have their front-ends severely damaged. HF transistor and receiver units will no longer operate, especially the widely used broadband radio and radar equipment.

In essence then, electronic communication in this country will cease to exist in its present form once a blast which produces a significant EMP has taken place. This is not a temporary blackout - as popular opinion supposes - *but a widespread and immediate destruction of equipment*, which will take extensive repairs to correct. Difficulties such as this would normally cause will be compounded many times in a shattered and disjointed community desperately struggling to regain some cohesion in the face of hideous adversity.

Result? Small isolated groups will be unable to communicate effectively with each other. People alone in their houses, following government instructions - such as contained in the "Protect and Survive" leaflet, will be completely cut-off unless they have a *medium wave portable*, which was not in use at the time of the attack. VHF receivers will be dead and in need of extensive repair.

We have been through the government literature covering nuclear warfare and its effects. There is no reference anywhere to EMP. It seems from this angle as though this is yet another case of "head-in-the-sand" defense. If so, then it is simply not good enough and it will cost lives we can ill afford.

We have sent copies of this article to the Home Office, Ministry of Defense and even the Prime Minister's Office and await an answer to the vital questions posed herein. ETI will carry the full text of such a reply as soon as we receive it and a page is reserved in our next issue especially for this purpose. I have a cold certain feeling it will be blank.

Ron Harris
Editor

ETI

NEW ★★★★★ Star Buys ★★★★★ FROM CASIO

We predict that this stylish watch will be a best seller!

CASIO F300
SPORTS CHRONO
ONLY £12.95



Hours, minutes, seconds, am/pm, day and date. Automatic four year calendar. 1/100 second chronograph to 12 hours, measuring net, lap and first and second place times. Backlight. 2 year lithium battery. Water resistant resin case with stainless steel trim. Mineral glass. A rugged, lightweight watch and chronograph for the sportsman.


F200 SPORTS CHRONO NOW £10.95

Something to sing about with twelve programmed melodies!

CASIO ML90
MELODY MAKER

RRP £21.95

ONLY £19.95

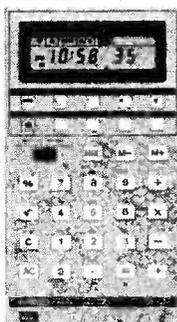

Clock, hourly chimes, calendar to 1999. Alarm 1: 7 different melodies, changing daily, a fixed melody or buzzer. Alarm 2: a fixed melody or buzzer. Date memory 1: "Happy Birthday". Date memory 2: "Wedding March" or "Drinking Song". On December 24/25 plays "Jingle Bells". Calculator with 11-note keyboard, full access memory, square roots, %, 7/32 x 2 1/2 x 4 1/2 inches. Wallet. 1 year batteries.

You asked for a metal version of the best selling C-80. Here

CASIO C-801

Watch
Calculator
Stopwatch
Dual time
RRP £34.95

ONLY £29.95



Finger touch keyboard. Hours, minutes, seconds, am/pm and day. Day, date, month calendar pre-programmed to 2009. Professional 24 hour stopwatch measuring net, lap and first and second place times to 1/100 second. Dual time (24 hour). 8 digit calculator. Backlight. Water resistant chrome plated case with stainless steel bracelet.

C-80 Black resin cased version £24.95



CASIO 110QS-37B

As F-300 above but with chrome-plated case and stainless steel bracelet.

RRP £19.95

ONLY £17.95

111QS-34B. Similar to above but without stopwatch function **£14.95.**
F-8C. Resin cased version **£8.95**

PLEASE NOTE

Casio's guarantee is **ONLY** valid if goods are purchased from an authorised dealer. Authorised dealers are easily recognised because they do not advertise goods below a minimum price (our price). Casio will **ONLY** supply authorised dealers.

Nevertheless we promise to **BEAT** (sensible) lower prices on the spot if the advertisers have stocks.

EXECUTIVE ALARM CHRONOGRAPHS

Full month calendar, tone control, hourly chimes



79CS-51B
Stainless steel
(£44.95) **£39.95**



79QS-39B
Chrome plated
(£34.95) **£29.95**

Hours, minutes, seconds, am/pm and date. Calendar display. Day, date, month and year. Monthly calendar from the year 1901 to 2099. 1/10sec stopwatch to 12hrs. Net, lap 1st & 2nd. 24-hour alarm with 10 step tone control. Hourly chimes, backlight, lithium battery.

8.6mm thick. Mineral glass, water resistant.

NEW SEIKOS

SOLAR ALARM CHRONO DER 028

Provisional specification. "Silver Wave" 100m water resistant. OK for swimming, skiing, etc. Comprehensive display, programmable weekly alarm, interval countdown alarm, hourly chimes. 1/100 sec. stopwatch. 10 year rechargeable battery.

ONLY £69.95



DFT 032. "Silver Wave" alarm chrono **£49.95**

OTHER NEW SEIKOS — SAE for details.

OVER 35 WATCHES TO CHOOSE FROM!

ILLUSTRATED CATALOGUE

Casio and Seiko products. Send 25p to: TEMPUS (Information and Service Centre), 19-21 Fitzroy Street, Cambridge CB1 1EH.

OUR BEST SELLING CALCULATOR



FX-8100

1 YEAR BATTERIES

Hours, minutes, seconds, am/pm, day. Calendar pre-programmed to year 1999. 24-hour alarm. Alarm timer, interval timer, or 1/100 second stopwatch; net, lap 1st and 2nd place. Fractions, %, cube roots; 5 levels parentheses, hyperbolics, standard deviations, coordinates, conversions. X to Y, X to M. 1/4 x 2 3/4 x 5 1/2" (RRP £27.95)

ONLY £24.95

OTHER CALCULATORS

LC.781 **£8.95**, MC.34 **£11.95**, HR.10 **£29.95**. With clock, etc. CQ.82 **£13.95**, PW.81 **£14.95**, AQ.1500 **£14.95**, AQ.2200 **£19.95**, MQ.12 **£19.95**, ML.71 **£22.95**, ML.81 **£22.95**, ML.82 **£19.95**. Scientifics, with clock FX.7100 **£24.95**. Others: FX.81 **£12.95**, FX.100 **£15.95**, FX.330 **£15.95**, FX.510 **£19.95**, FX.3200 **£21.95**, FX.501P **£54.95**, FX.502P **£74.95**, FA.1 **£19.95**.

SPECIAL OFFER. We are now sole suppliers of the Casio Master Pack (RRP £17.95) and are giving one **FREE OF CHARGE** with each FX.501P or FX.502P purchased.

81QS-35B ALARM CHRONOGRAPH

Now available from stock again



Stainless steel, mineral glass. Water resistant. 5 YEAR BATTERY. Hours, minutes, seconds, day and date, date, month and year. 12 or 24 hour display. 24 hour alarm, hourly chimes. Stopwatch from 1/100 second to 7 hours, net, lap and 1st and 2nd place times.

(£34.95) **£29.95**

Now available gold plated 81QGS-35B **£34.95**

MANY OTHER CASIO WATCHES AVAILABLE FROM STOCK. LADIES MODELS FROM £12.95

RETURN OF POST SERVICE

Postal and telephone orders received before 4.00 p.m. will normally be despatched the same day by FIRST CLASS POST.

Send your order by **FREEPOST** (2nd class post — no stamp required). Please phone urgent orders or use first class mail.

PRICE includes VAT, P&P. Send your Company Order, Cheque or P.O. or phone your ACCESS or B' CARD number to:

TEMPUS

Tempus (Dept. ETI)
FREEPOST, 164-167 East Road
Cambridge CB1 1BR. Tel. 0223 312866

BUILD YOUR OWN METAL DETECTOR VLF/TR VCO/TR IB/TR BFO...

Pre-aligned search heads — test equipment not required. Literature available in return for SAE. Manuals and parts sold separately: write or phone for price. Export welcome: write for quote.



Shadow VLF/TR. Full specification discriminator, not just ferrous/nonferrous indication. It works by measuring the conductivity of the target; now you can reject nails bottle caps even aluminium foil and ring pull tabs! Full ground effect exclusion over normal or high permeability soils.

The head is thermally and capacitively shielded. 4 modes: deepseeking VLF plus 3 TR discriminating ranges. Push button "memory" tuning. Performance equals commercial detectors costing £200! As described in ETI. Complete kit now only **£87.87 inc. VAT & post!**

Individual parts: Search head £21.33 PCB £6.80 Case £5.33 Adjustable shaft assy. £5.10. LM393 £1.12. Manual (gives more info. than ETI article — and extra function) £1.12. All inc. VAT & post! (Other parts also available separately)

Shadow TR/1B (illustrated). A true transmit receive/induction balance detector at a budget price for anyone who doesn't need discrimination. Waterproof and thermally insulated search head. Good sensitivity. Built-in speaker and headset jack. Complete kit **£25 + VAT** (post & Pkg. **£1.80**).

Shadow TV/VCO. An advanced version of the TR/1B. Use as a sensitive 1B machine or switch to VCO mode when the sound changes to a varying pitch, allowing easier use over mineralised ground and enabling detection of negative, high permeability anomalies. Kit price **£29 + VAT** (post **£1.80**).

Matching stereo headphones for all Shadow models **£4.90 + VAT** (post paid).

Beginners BFO model. A very detailed assembly manual and pre-wound coils make this an ideal first project. Simple high efficiency circuit. Full size (not a toy) but weighs only 300gms (10.5oz) with battery! FREE STETHOSCOPE HEADSET with every order. AL73 kit: **£12 + VAT** (post **£1.80**). Padded high Z headphones **£4.50 + VAT** (post paid).

Shel Kit. Consists of the (hard to find) hardware items, for detectors of your own design. Fully adjustable shaft with handle, search head mouldings (int. diam. 185mm) with hinge assembly, special clips to mount your own control housing (any box is suitable). Completely non-metallic and undrilled. With assembly instructions **£8.25 + VAT** (post **£1.50**).

ALTEK (ETI), 1 Green Lane
Watton-on-Thames Surrey

Order by post or phone (24 hours). Access & Visa Cards quote number. Callers by appointment only please. Phone (093 22) 44110 anytime!

AUDIO AND TEST EQUIPMENT CENTRE

Telephone your order with Access and Barclaycards or send cheque with order.



LONDON'S TEST GEAR CENTRE
OPEN 6 DAYS A WEEK 9 am-6 pm

HAMEG • TRIO • LEADER • SINCLAIR • LASCAR • LEVELL • CSC
Test Equipment now in stock—send large s.a.e.

SCOPES—(UK P/P £2.50 ea)

HM 307-3 10MHz single beam with Component Tester	170.00
HM 312-8 20MHz dual trace	287.50
HM 412-4 20MHz sweep delay dual trace	402.50
SINCLAIR 10MHz Miniscope P/S 4.00, Nicads 7.95, Case 8.80	152.50

PROBES x1/x10 12.95, x10 10.50, x1 8.50, x100 16.95

FREQUENCY COUNTERS

OPTO 7010 9 digit, 600MHz	
Portable 0.1Hz Resolution with N/CADS	139.95
MAX 50 50MHz 6 digit pocket counter	61.00
MAX 100 100MHz 8 digit portable counter	68.75
MAX 550 550MHz 6 digit pocket counter	106.00
500 MHz Prescaler for max 50 or max 100	40.00
PFM 200 Sinclair 200MHz Pocket Counter 8 digit	54.50
OPTIONAL P/S 4.00, Connector Pack PFM200	£9.95
c7216R, 10MHz 8 Digit Panel Mounting	55.80
c7216RP, 150MHz version	68.25

DIGITAL MULTIMETERS

DM235 Sinclair portable 3½ digit LED	56.50
PDM35 Sinclair Pocket 3½ digit LED	36.50
DM350 Sinclair 3½ digit with 10 amp range	78.50
DM450 Sinclair 4½ digit with 10 amp range	107.95
(30kV Probes 16.95, P/S 4.00, DM Nicads 7.95, Cases 8.80)	
M1200 Bench Portable 3½ digit LED, Resolution 1µA/0.1mV/0.01ohm	SPECIAL PRICE NOW £59.50
LMM100 Lascar 3½ digit 2A LCD Bench 0.1%	66.75
LM2001 Lascar 3½ digit 2A LCD Hand 0.1%	51.70
LM200 Lascar 3½ digit 2A LCD Economy 0.5%	43.40
ME502 3½ digit 10A LED plus transistor tester	£43.95

MULTI-METERS — GENERAL PURPOSE & ELECTRONIC

Multi-Range Instruments featuring AC/DC volts, AC current, Resistance Ranges (TM3 AC volts only), some with AC current, etc. *

TM11 incredible 120 Range Electronic Multi-meter	172.50
TM3B AC Micro voltmeter 3MHz > 4 Megohm (large scale)	166.75
TM3A AC Micro voltmeter 3MHz > 4 Megohm	149.50
360TR 100k/volt + 23 Range (plus transistor checker) Large scale	34.95
7080 20k/volt 26 Range, Large scale	26.85
7081 50k/volt 36 Range Multi-meter, range doubler	19.95
NH55 2kV 10 Range Multi-meter	6.95
NH56 20k/volt 22 Range Multi-meter	10.95
LT101 1k/volt 17 Range Pocket M multi-meter	5.95
YN50TR 20k/volt 19 Range Multi-meter plus transistor check	13.95
AT205 50k/volt 21 Range Multi-meter	24.95
ATI 2k/volt 12 Range Multi-meter Deluxe	7.95
TM5000 30/volt 23 Range Multi-meter, with case	22.95
ATI200 20/volt 19 Range Multi-meter with transistor tester Deluxe	16.95
AT2050 50k/volt 18 Range Deluxe Plus transistor checker	26.50
AT210 100k/volt 21 Range Multi-meter Deluxe	29.95

AVO 8s and a large range of replacement tests leads in stock

GENERAL EQUIPMENT

SE250 Signal Injector	4.95
TE7 Signal Tracer AF/RF	9.95
SWR50 SWR/Power Meter	13.95
DRS10 36 Value Resis. Box	3.95
RP124 0/24V 0/1 amp P/S Stabilised	42.00
RP324 3 amp version	54.00
RP230N 0/30V 0/1 amp P/S Twin Meters	85.00
TR1000 Transistor checker in/out circuit	11.95
MOD63 Signal injector	8.85
C3022 Transistor/Diode Checker	19.95
3101 Clamp Meter 0/1 K ohm, 0/150/300/500 AC volts 0/300 amp	32.95
SWR40/9 SWR & FS Meter	10.50
SWR10 SWR Meter	10.95
MS319 2x100 Watt Audio Watt Meter	13.95
*500V Megohmmeter 500 Megohms	51.00
*2½ Amp Variable transformer	21.95

DRILLS AND DRILL KITS

9 to 12 volt Operated, ¼" max SMALL DRILL with collets	6.85
MEDIUM DRILL with 3 collets	9.95
SMALL DRILL with 20 drills/tools	13.95
MEDIUM DRILL with 20 drills/tools	16.95
MAINS Eliminators	9.95
VARIABLE Speed	13.95
12 volt ¼" Heavy Duty Drill	12.50
MAINS DRILL with tool set	19.95

TV SOUND

High quality TV sound from your Hi-Fi. Simply plug into aerial socket of your FM tuner. **£8.50** (UK P&P 50p). PRICE INCREASE AS FROM 1/6/80

GENERATORS

TG152 Series 3Hz 300kHz 5 Ranges	92.00
TG152Dm (with meter)	113.85
TG200 Series RC Oscillators Sine/Square output, 1Hz-1MHz 12 Ranges	124.20
TG200Dm (with meter)	145.50
TG200Dmp (meter & fine control)	155.25
4001 Digital Pulse Generator 0.5Hz-5MHz	105.00
2001 Function Generator-Sine/Square/Triangle/TTL	86.00
SG2030 (RF) 6 bands 250kHz-300MHz	49.95
6052 PAL VHF/UHF Colour Bar Generator	250.00
AG761 (Audio) sine 19Hz-220Hz square 19Hz-220Hz	61.00
ARF300 (RF Audio) 18Hz-200MHz	78.50

PROTO BOARD IN STOCK
KITS PR 6.20, PR 100 11.80.
SEPARATES EXP300 5.95, EXP600 6.50, EXP350 3.45, EXP650 3.95

LOGIC PROBES AND MONITORS


LT2000 Economy Probe 10MHz	8.95
LM1 Monitor circuit powered	33.00
LP1 Probe 10MHz	35.50
LP2 1.5MHz	20.50
16 Pin IC test clip	1.95

PIEZO HORN TWEETERS

Up to 100 watts each. No x-over req'd only **4.95** each. Flared Horns **6.50**. Midrange Flared Horns **9.50** (UK Post Free)

ELECTROVALUE

FOR COMPONENTS THAT COUNT

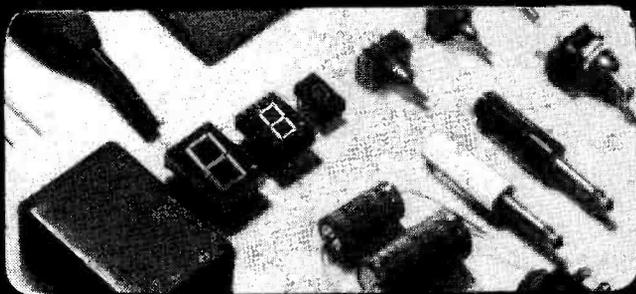


SIEMENS SEMI-CONDUCTOR CAPACITORS FERRITES	NASCOM MICRO COMPUTERS AND ANCILLARIES	VERO BOARDS CASES & KITS
ISKRA RESISTORS	RADIOHM POTENTIOMETERS	BREADBOARDS SOLDER TOOLS
	OPTO-ELECTRONICS	SWITCHES CATALOGUE 10

ALL GOOD PROJECTS START WITH CATALOGUE 10
IT'S FREE FOR THE ASKING

128 pages packed with almost everything everyone wants. There are attractive discounts and free postage in UK on orders £5.75 and upwards.

ELECTROVALUE LTD. HEAD OFFICE (Mail Orders)
28(H) St. Judes Road, Englefield Green, Egham, Surrey TW20 0HB. Phone Egham 33603. Telex 264475

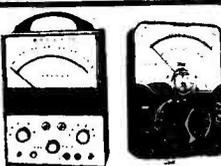NORTHERN BRANCH (Personal Shoppers Only)
680 Burnage Lane, Burnage, Manchester M19 1NA. Phone (061) 432 4945



TM11 TMK500
CALL IN AND SEE FOR YOURSELF

PRICES CORRECT AT 1/6/80


AUDIO ELECTRONICS

301 EDGWARE RD., LONDON W2 1BN
01-724 3564. OPEN 9-6, MON-SAT.

ALSO AT 248 TOTTENHAM COURT ROAD, W 1

SPECIAL BULK PURCHASE
GEC 10+10 watt
Tuner/Amplifier.
MW/LW/SW/Stereo FM. Supplied
as two easy to connect units.
£21.95 P&P £1.50

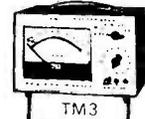IN STOCK NOW
Large range of
speakers and kits
public address
equipment,
microphones, mixers,
security systems,
intercomms, ham
equipment. See
catalogue



FREE CATALOGUE

SEND STAMPED
(17½p UK)
ADDRESSED ENVELOPE
(MIN. 9½ x 6½")
FOR YOUR COPY NOW

NASCOM-2 MICRO-COMPUTER

FREE 16k RAM Board
New improved RAM B

only £335
+ VAT
IMMEDIATE DELIVERY

Power supply £29.50

Z80A 8 bit. This will run at 4 Mhz but is selected between 2/4/Mhz.
On-board, addressable memory. 2K 2K Monitor — Nas-sys 1. 1K Video RAM (MK 4118). 1K work space/User RAM (MK 4118) (8K Microsoft Basic) (MK 3600 ROM) (8K Static RAM/2708E).

Microprocessors Z80A, 8 bit CPU. This will run at 4Mhz but is selectable between 2/4 MHz. This CPU has now been generally accepted as the most powerful 8 bit processor on the market.

INTERFACE

Keyboard New expanded 57 key Licon solid state keyboard especially built for Nascom. Uses standard Nascom, monitor controlled, decoding.

T.V. The tv peak to peak signal can drive a monitor directly and is also fed to the on-board modulator to drive the domestic T.V.

I.O. On-board UART (int. 6402) which provides serial handling for the on-board cassette interface of the RS232/20mA teletype interface.

The cassette interface is Kansas City standard at either 300 or 1200 baud. There is a link option on the NASCOM-2 for 2400 Baud.

The RS232 and 20mA loop connector will interface directly into any standard teletype.

The input and output sides of the UART are independently switchable between any of the options — i.e. it is possible to have input on the cassette and output on the printer.


PIO There is also a totally uncommitted Parallel I/O (MK 3881) giving 16, programmable, I/O lines. These are addressable as 2 x 8 bit ports with complete handshake controls.

Documentation Full construction article is provided for those who buy a kit and an extensive software manual is provided for the monitor and Basic.

Basic The Nascom 2 contains a full 8K Microsoft Basic in one Rom chip with additional features like DEEK, DOKE, SET-RESET for simple programming.

SYSTEM KITS from £225

80

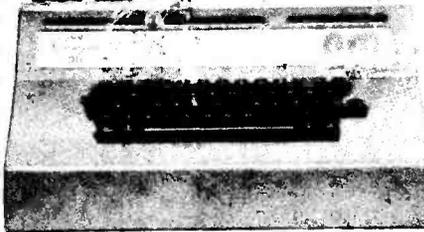

Microprocessor board* (Nascom 2)

4MHz Z80 CPU; TV or Video + 1200 baud Kansas City + Serial RS 232 printer Interfaces: Keyboard: 128 character ASCII plus 128 Graphics in 2 x 2K ROM; free 16-way parallel port; 8k BASIC; NAS SYS operating monitor. £280 built and tested.

Firmware & MOS ICs

Zeap Assembler (4, 1K x 8 EPROMS) £50
Nas Pen text editor (2, 1K x 8 EPROMS) £30

Floppy disc system

Double sided, double density 5¼in disc giving 280K bytes formatted, including controller board/PSU/Housing and interconnects. £480. Controller board £127.50. Second Disc £240. CP/M £80

System 80 housing

High strength GRP moulding Accepts 12 x 8 Nascom 2 CPU board, four 8 x 8 expansion boards. £85 incl. frame racking, interconnects and motherboard.

Expansion Boards* (in kit form)

16K RAM £127.50 • 32K RAM £175
48K RAM £220

High Resolution Programmable Graphics £90

Colour Board Kit £140

High Resolution Colour add on £37.50

All prices subject to VAT (add 15%)

No more slaving over a hot soldering iron. The Nascom 1 is now supplied BUILT!
Britain's biggest small system is available fully constructed for you to slot into your own housing for the ridiculously low price of £140 plus VAT (kit price still only £125 plus VAT).

nascom-1

12" x 8" PCB carrying 5LSI MOS packages, 16 1K MOS memory packages and 33 TTL packages. There is on-board interface for UHF or unmodulated video and cassette or teletype.

The 4K memory block is assigned to the operating system, video display and Eprom option socket, leaving a 1K user RAM.

The MPU is the standard Z80 which is capable of executing 158 instructions including all 8080 code.

NASCOM-1
P&P
£125
VAT
£1.50

NASCOM PRODUCT LIST + VAT

I/O board kit less I/O chips	45.00
UART + BAUD rate generator + crystal for I/O board	16.00
CTC — MK3882 multiple interrupt driven clock generator for I/O board	8.25
P/IO — MK3881 + interconnect for I/O board	8.50
P/IO interconnect only (for I/O board)	3.80
Econographics kit for additional 128 characters (N1 only)	30.00
270B/2716 Programmer suitable for N1 and N2 under NAS-SYS	20.95 + VAT
Nascom 19" rack mounting card frame for N1 and N2	32.50
Nas-DA disassembler 3 EPROM for Nas-sys	37.50
MK36271 BK BASIC in BK x 8 ROM	40.00
Naspen VS in 2 EPROM	30.00
Nas-sys monitor in 2 EPROM	25.00
NASBUG T2 1 x EPROM	12.50
Nasbug T4 2 x EPROM	25.00
Tiny Basic 2 x EPROM	25.00
Super Tiny Basic 3 x EPROM	37.50
Super Tiny Basic upgrade 1 x EPROM	12.50
Tape Software	
ZEAP 1, 2 tape and documentation for N1	30.00
ZEAP 2 tape and documentation for Nas-sys	30.00
8K BASIC tape and documentation for N1	15.00
MEMORIES Discounts 10% for 4, 15% for 8, 20% for 16	
MK3880 (Z80) for N1	7.50
MK3880-N4 (Z80A) for N2	7.95
MK4116 16K x 1 dynamic RAM	7.50
MK4027 4K x 1 dynamic RAM	2.25
2102 1K x 1 static RAM	1.00
411B 1K x 8 static RAM	12.75
Unprogrammed 2708	7.50
Unprogrammed 2716	19.95
IM6402 UART	4.50
2114 1K x 4 Static RAM	3.95
8080A	5.25

Ideal for NASCOM-PET-TRS80-TRITON



PLAIN PAPER PRINTER

Fully built and housed in a stylish enclosure for just £325 plus VAT

Interfaces with all micro computers

The Nascom IMP (Impact Matrix Printer) features are

- 60 lines per minute.
- 80 characters per line.
- Bi-directional printing.
- 10 line print buffer.
- Automatic CR/LF.
- 96 character ASCII set (including upper/lower case, \$, £).
- Accepts 8½" paper (pressure feed).
- Accepts 9½" paper (tractor feed).
- Tractor/pressure feed.
- Baud rate from 110 to 9600.
- External signal for optional synchronisation of baud rate.

IDEAL FOR WORD PROCESSING

COMPUTER KEYBOARDS



TASA 56 key touch sensitive keyboard. All ASCII characters including control keys. Parallel output with strobe. Shift lock. Keys coded in 3 colours to indicate function. 18 V DC at 35 mA. 15" x 6.25" x 0.385" thick. Black resin encapsulated.

£49.50 + VAT

Star Devices Mk III 71 key touch sensitive keyboard. With numeric pad. All ASCII characters including control keys. Auto key repeat. Parallel output with strobe. Shift lock with indicator LED. Built in 'beeper' with level control. 5 V DC at 300 mA 15" x 7" x 1.25". Grey case with white keys on blue.

£48.50 + VAT


Carter 57 key ASCII keyboard. Conventional keyboard. 128 ASCII characters including control keys. Parallel output with strobe. Shift lock. + 5V and -12 V DC. 12" x 5.5" x 1.5". Black keys with white legends.

£39.34 + VAT.

FERRANTI — "SIZE 14 x 6 x 3" SLOPING FRONT

55 Key ASCII Coded in steel case. Complete with Plug and Cable with circuit to convert to T.T.L. levels. In good condition at only £25 + VAT, P/P £2.50

CENTRONICS QUICK PRINTER

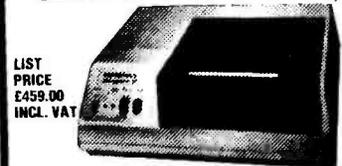

LIST PRICE
£459.00
INCL. VAT

OUR PRICE
£195.00
+ VAT

EXCLUSIVE TO HENRY'S 50% OFF MAKER'S PRICE

for: ● Software selectable 20, 40 and 80 TANDY, column using 120mm aluminium-ised paper, 1 roll supplied.

PET, ● 150 lines per minute. NASCOM/Centronics parallel data interface for Nascom, Tandy, etc.

● 240 volt mains input, ASCII character set

● Paper feed, and on/off select switches

BELL signal Weight 10lbs

Size: 13" x 10½" x 4½"

● New, boxed and fully guaranteed

POST PAID Price £195.00 + VAT

See COMPUTING TODAY Recommendations March/May issues

TANGERINE

COMPUTER SYSTEMS LONDON STOCKISTS

Microtan 65 Kit, Inc VAT	£79.35
Microtan 65 Assembled, incl. VAT	£90.85
Tanex (min. con) Kit, incl. VAT	£49.45
Tanex Assembled, incl. VAT	£60.95

Lower case pack, incl. VAT	£10.90
Chunky Graphics Pack, incl. VAT	£7.50
20 Way Keypad, incl. VAT	£11.50
Mini-mother board, incl. VAT	£9.95
Complete Tangerine range available	

SEND FOR COMPLETE COMPUTER BROCHURE FREEPOST TO ADDRESS BELOW

Your London & National Nascom Distributor.
Export Orders deduct VAT, but add 5% carriage
Official Export & Educational Orders welcome
Our Telex 262284 Mono Ref. 1400 Transonics

ADD VAT
15%
TO YOUR
ORDER
EXCEPT
WHERE
STATED



Henry's

Computer Kit Division
404 Edgware Road, London W2 1ED, England I.E.D.
01-402 6822



AUDIOPHILE

Opposite ends of the scale this month with a super-fi, super-heavy amp from JVC and a tiny portable player with hi-fi aspirations. Ron Harris reports.

I could tell it was going to be a *different* month right from the start. Two days gone since our last issue went to the printers at six-thirty on a Monday morning, and here I am, opening my flat door to the sight and sound of a little red-faced delivery man, sitting on a box barely smaller than him, perspiring freely and moaning in a high voice of the effect this job has had upon his hopes of an active married life.


After placating said tradesman — palms crossed with silver make up for more than I thought — and dragging this huge piece of hernia hi-fi into my living room (I understood his problems more fully now), only to find the box sealed with a tape possessed of a higher tensile strength than steel, it began to look like this month and me were not destined to get on very well. A view reinforced very rapidly by the complete absence of tea from my kitchen. Six-thirty on a Monday is NO time to discover such things.

Hospitals should have special emergency units set up to deliver intravenous shots of Tetleys for moments like that. National Health, (what's left of it) take note.

Super A or Eh!

It was two days and many cups of tea later that I finally obtained sound from the beast — a JVC A-X9 amplifier — having been held up slightly by the structural alterations required to sustain such mass. (Don't forget that what follows has all been made possible by that little man who sacrificed future generations in order that you may read this test report!)

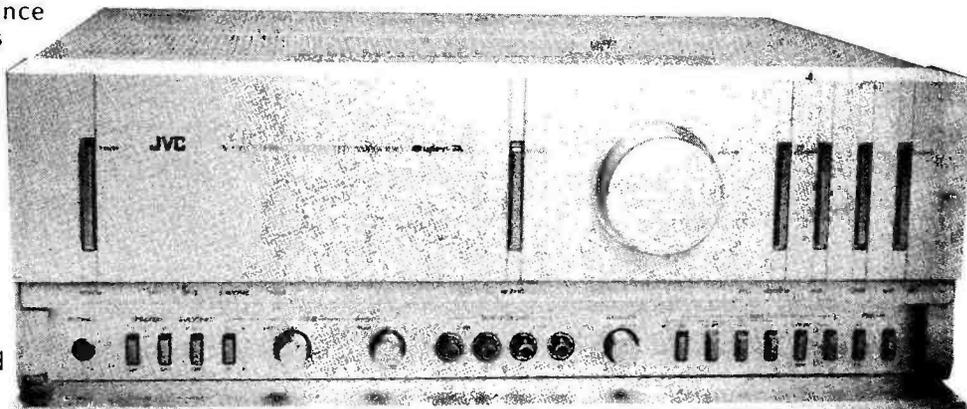The A-X9 takes its place at the head of JVC's new



amplifier range and employs their new variable bias circuit, which is claimed to allow class A operation at much higher powers than has hitherto been possible by increasing the efficiency of power transfer.

Normal class A amps — in which the output transistors are continually passing current — manage only about 25% efficiency. This would mean that a 100 W audio output requires some 300 W of heat to be dissipated. Great for musical evenings around the family heatsink in winter, but not a great deal of use otherwise.

Class B, on the other hand, runs around 75% efficient and the difference has meant that over 90% of output stages resting in hi-fi equipment cases today are either Class B or AB, the closely related derivative designed to defeat cross-over distortion.


The major drawback of the currents is their liking for odd-harmonic distortion components, mainly generated by the switching on and off (or nearly!) of the output transistors. Class A has long been held as a potentially better method of amplification. But how to employ it, at a realistic power level, without inventing the portable infinte heatsink? Ah, there lies the rub!

JVC's solution is to make the bias circuit signal dependent. The output stage is run in Class A normally, but the bias current is reduced down to an absolute minimum when there is no signal present to be amplified. Resulting efficiency is claimed to be around 70%, making the use of Class-A viable for high powers.

PSU 2, TIM O

Other refinements in the circuits include the use of a separate supply for the output stages and a tone control configuration which is in the feedback network of the POWER amp — as opposed to being a separate gain stage in the pre-amp.

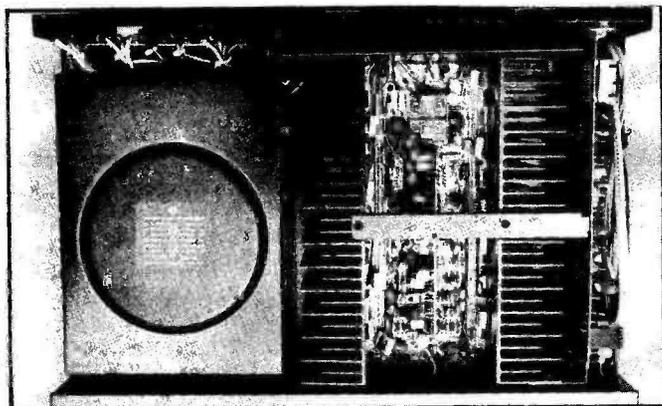In common with most Oriental designers, JVC have gone for an incredible power bandwidth — in this case



Note the massive PSU on the left and those huge heatsinks down the centre. This is one HEAVY amp.

somewhere close to 200 kHz (maybe they can hear things we cannot?) and this coupled with ultra-fast slew-rate leads a claim of ZERO TID (transient intermodulation distortion). Either variety of cartridge type can be accommodated and a switch is present on the front panel to switch from the MM to MC (from moving-magnet to moving coil). This is a mechanical operation at the panel, with a flexible drive transferring the command to PCB mounted switches close to the input sockets.

Taping facilities are comprehensive with three sets of input sockets, one hidden on the front panel, with which you can record onto either deck from source, or other tape machine.

All That Glitters . . . ?

So much for the principles, what of the appearance? By far the most striking feature of the A-X9 is its sheer size. It measures almost 9" (h) x 18" (w) x 17" (D) and weighs 37 lbs. Impossible to ignore, but beautifully made and with a confidently solid feel to it. All the "never used" controls, like tone and speaker switching, are hidden under that flap on the front, but so as you cannot forget that which you have operated, small legends light up on a chrome strip when the buttons are used. Very smart indeed. The volume control is nicely massive and smooth in operation and the tone and balance are "click-stopped" for convenience.

Overall the A-X9 is brilliantly made and a dream to use. No possible complaints there.




. . . Is Not Gold?

Trying to measure performance on a machine like this is silly, it betters specification and/or measuring equipment on all parameters, so I give only a selection from the results below — chosen for reasons which I hope will become apparent.

Marvellous engineering this and I moved on to have a good long listen with interest. My usual limit first, measure later policy having been defeated by the logistics of moving a 37 lbs cube of metal around . . .

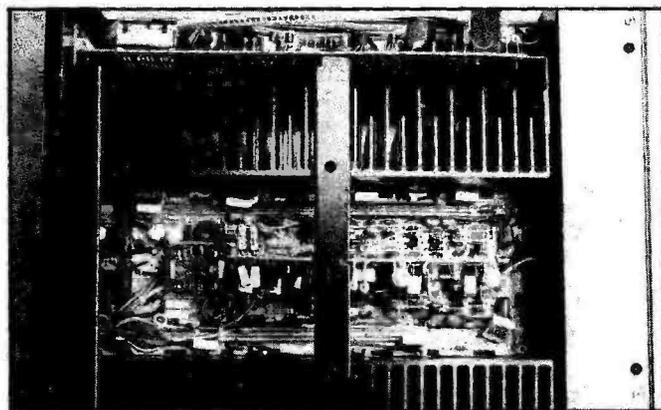Frankly I was very, very disappointed. I had expected great things from the A-X9— judging by book covers I suppose, well built or not, and was let down. This machine retails at around £530, putting it in direct competition with a whole host of excellent British units — Lecson, Meridian, Quantum and Crimson, to mention but a few.



Close up of the highly complex variable bias circuit.

I auditioned the JVC directly against a Lecson AC1/AP3 II and the Quantum 102/204 combination reviewed last month. Both delivered a superior performance in my opinion. The JVC seemed to lack punch and masked mid-range detail sufficiently to be immediately identifiable in A-B comparisons.

The signal-to-noise was better with A-X9, on all inputs, and it performed much better with tape or tuner as a source. This tends to point the finger at the disc input rather than the clever power amplifier and a second test confirmed this.

Slipped Disc?

I used the Quantum pre-amp as a "head amplifier" and fed the signal from this into the JVC's tape input, comparable with the Lecson set-up as reference. A different picture entirely now. Most of the missing detail is back and, allowing for the lower power output, a much more credible performance resulted.

Much as I would like to exonerate the main amplifier completely, I'm afraid I cannot do so. Overall the A-X9 is very 'edgy' on difficult signals, such as strings, and lacked the peak power 'headroom' to portray dynamics properly. At this price level, therefore, I must regretfully mark the A-X9 down.

It is so beautifully finished and presented, however, that provided you are not searching for absolute performance, it may well still appeal on ergonomic and engineering grounds.

Pickup amplifier board. The tubes carry a sliding metal strip which operates the moving coil/magnet selector, at the top centre of the PCB.



Sound quality is undeniably good, in fact its in a different class entirely to any portable recorder you've ever heard up to now. Biasing for prerecorded tapes is the only thing they could have done and it works well. I tried making up some tapes, both on Sony AHF and TDK formulations and was returned good results from both.

Winding Up

Frankly I can't see how this little thing can fail. Good quality sound anywhere you want it for around £90. Not a lot these days, if you say it quickly. Battery life is around three hours with standard cells and rechargeable packs are available, as are connectors to the mains and car batteries. Well thought out, you see.

The one I had on loan sat on my desk top playing away for hours, making me blissfully unaware of the clamorous call of telephone and outside world.

I think you're going to see a lot more of the Stowaway in the future — so next time someone bumps into you in the street have a look see if he's wearing MDR 3's before swearing at him — you could be wasting your breath.

ETI

Left: is this not the *worst* publicity photo you have ever seen? I'm convinced Sony did it on purpose it's so bad. In fact I think this deserves a good caption so I hereby declare the Second Audiophile Caption Contest open. The funniest caption to this photographic fiasco wins a year subscription to ETI. Please mark your envelope "Audiophile Contest" and send to our 145 Charing Cross Road address. Closing date is 31st August, 1980. Sharpen your wit (and pencils) and let's hear from you.

Stowaway Where?

Something pretty neat — but weird. Did I not tell you it was gonna be one of those months? First the world's heaviest amp — now the world's *smallest* stereo cassette. Called the Stowaway, or TPS-L2, it comes from Sony (again) who claim to be selling them abroad with an ease which makes me think they're giving free photos of Felicity Kendal away with every machine. Put me down for a dozen.

I reproduce Sony's handout shot here for two reasons. Firstly because it is so awful as to be a model of how *not* to do these things. Secondly because I didn't get to attend the press launch with Hot Gossip and this is as good a way as any of exacting revenge upon Sony's PR.

The machine really is small ($3\frac{1}{2} \times 5\frac{5}{16} \times 1\frac{7}{16}$ inches) and weighs well under a pound. The idea is to fit one to your belt, or use the carrying strap, thus obtaining a truly portable source good quality sound. Output is via those MDR-3 headphones of which I spoke a while back, resulting in a surprising sound quality. Intended source material is pre-recorded cassettes (no record facility) but the Stowaway is happy to play home recordings, as long as you use plain, ordinary non-chrome, non-metal tapes to do it.

Head For Success

Sockets exist for two pairs of MDR-3's to be used simultaneously and there is even a method of communication between sets. A built-in microphone will pick up sound upon depression of the "Hot Line" button and quiet the music to relay what it hears to the users.

With the MDR-3's though, there is little need to use the microphone — once the music is muted you can hear perfectly well anyway.

Fast wind in either direction leaves the heads in place, so that you can skip back and forwards to find the bits you want. A definite pop facility. Tone control is a switch, you have it or you don't. (It's only a treble cut circuit).



This is what the Stowaway really looks like, minus 1950's teen-age kitsch. Only complaint is a lack of Dolby B. Does not detract from a good compromise between performance size and price.

BI-PAK

GERM. DIODES
200 Mixed Diodes mainly Germ. OA81-91 1N34 60 GC61 62 etc Case DO-7. Coded and uncoded. Value all the way!
O No. SJ127 **£1 per Pak.**

SIL. DIODES
200 Mixed Diodes mainly SILICON case DO-7, OA200 202. General purpose 200mA marked and uncoded you to sort and test. Outstanding Value!
O No. SJ128 **£1 per pak**

AUDIO AMPLIFIER
5 watt Audio Amplifier Module. Special Clearance Offer
O No. AL20 **£2.50**

HEADPHONES
NEW Improved Lightweight Stereo Headphones including flexible headband and padded earcups. Impedance 80ohms Frequency 30 1800Hz. ALL Black.
O No. 885 **£4**
As above but with coiled lead and rotary volume controls
O No. 884 **£7**

HEADPHONE ACCESSORIES
7 metre Headphone Extension Lead
O No. 136 **£1.50.**

HEADPHONE JUNCTION BOX
Gives facility for using Stereo Headphones with amplifiers and radiograms which do not have a headphone outlet. TO CLEAR!
O No. 881. **£1.20 each.**

ANTEX
Antex X25 Iron 25 watt soldering iron. OUR SUPER SALE PRICE, £4.00.
O No. 1931 **£4.00.**
ST3 Iron Stand Suitable for above. OUR Sale Price
O No. 1939 **£1.25 each.**

METERS
23mm Level Meter Special Sale Price.
O No. 1320 **£1.00.**
40mm V U Meter. OUR SPECIAL PRICE
O No. 1321. **£1.50.**

PLUGS & SOCKETS
Set of 4 1 metre Colour coded leads with phono plug ends. ideal for audio and test use. Outstanding Value
O No. SJ122 **£1.00 per Pak**
1mm Plugs & Sockets in Red & black
O No. SJ123 **5 prs. £1.00**

CAPACITORS
SJ11 150 Capacitors mixed types and values **£0.50**
SJ12 60 Electrolytics all sorts mixed **£0.50**
SJ13 40 Polyester polystyrene capacitors mixed **£0.50**
SJ14 50 C289 type capacitors mixed **£1.00**
SJ15 40 High quality electrolytics 16u 470nfd **£1.0**
SJ16 40 Low volts electrolytics mixed values up to 10v **£0.50**

TRANSFORMERS
MINIATURE MAINS Primary 240v.
No. Secondary **£0.75**
2021 6v 0.9v 100mA **£0.75**
2022 9v 0.9v 100mA **£0.75**
2023 12v 0.12v 100mA **£0.95**
2025 240v Primary 0.55v 2A Secondary **£5.50**

BC108 FALLOUTS
Manufacturers out of spec. on volts or gain or neither. Metal TO18 case. You test!
O No. SJ124 **50 for £1**

DIODES
300 1N4148 Type uncoded Silicon Diodes. Case DO 35. you to test.
O No. SJ129 **£1 per Pak**
Silicon Fast Switch NPN like 2N706 2N2369. You select by test!
O No. SJ125 **50 for £1**

GERM. TRANSISTORS
The last of the Germanium PNP OC71 71.75 etc Mullard Black Glass Type. You test (5 could cost you that!)
O No. SJ126 **50 pcs £1**

GERM. POWER TRANS.
AD149.OC26-AD140 **£0.50 each**
AD142.OC28-2N3614 **£0.65 each**

VERO PLASTIC CASE
Complete with lid and fixing screws. Finished white. Size: 72mm x 50mm x 25mm.
O No. 173 **35p each**

NPN
BD131, TO-126-NPN. Untested.
O No. SJ84 **25 for £1**

SCRs
TO66 SCRs 5 Amp ALL good. Untested for volt. good yield 400+.
O No. SJ130 **10 for £1**

AERIALS
FM Indoor Tape/Ribbon Aerial
O No. 107 **40p each**
HI-FI CAR AERIAL
4-section fully retractable and locking.
SPECIAL PRICE
O No. 109 **£1.40 each**

STEREO 30
Complete 7 watt per channel Stereo Amplifier. Front panel, knobs, etc. PLUS transformer and real Teak Cabinet for that professional finish!
SPECIAL SALE PRICE
SAVING £5!
OUR PRICE £25

IC SOCKET PAKS
SJ36 14 8 pin SJ41 6 22 pin
SJ37 12 14 pin SJ42 5 24 pin
SJ38 11 16 pin SJ43 4 28 pin
SJ39 8 18 pin SJ44 3 40 pin
SJ40 7 20 pin
ALL AT ONLY £1 EACH

VOLTAGE REGULATORS
Cast TO220
Positive Negative
uA7805 **£0.65** uA7905 **£0.70**
uA7812 **£0.65** uA7912 **£0.70**
uA7815 **£0.65** uA7915 **£0.70**
uA7818 **£0.65** uA7918 **£0.70**
uA7824 **£0.65** uA7924 **£0.70**

TEXAS NPN
Texas NPN silicon transistors; metal can perfect and coded.
2S503 BC108, TO-18.
O No. SJ29 **50 off £2.50**
100 off £4. 1,000 off £35

AUDIO ACCESSORIES
SJ75 FM coax cable plain copper conduction cellular polythene insulated and plain copper braided PVC sheath impedance 75ohms. **£0.10 per metre**
SJ76. 1 Board containing 2 x 5pin DIN sockets 180 02 2pin DIN loudspeaker sockets **£0.30.**
SJ77. A 5pin DIN 180 chassis normal socket incl. DPDT Switch **£0.20.**

DISC CERAMIC CAP
100 Disc Ceramic CAP. Mixed values covering complete range 3PF 4.700PF. SUPER VALUE
O No. SJ121. **£1.00.**

SWITCHES
Push-to-make. 6mm panel mounting.
O No. SJ131 **5 for £0.50**
Push-to-break as above
O No. SJ132 **4 for £0.50**

LED
2nd Quality Paks
1507 10 Assorted colours and sizes **£0.65**
S122 10 125 RED **£0.80**
S123 10 2 RED **£0.50**
LED CLIPS
1508 125 125 **5 for £0.10**
1508 2 2 **5 for £0.12**

MISCELLANEOUS
SJ20 2 Large croc clips 25A rated ideal for battery chargers etc. **£0.30**
SJ21. Large 7 1/2" Mains Neon Tester screw-driver chrome finish **£0.85**
SJ22 Small pocket size Mains Neon Tester screwdriver **£0.55**
SJ23 Siemens 220v AC relay DPDT contacts 10amp rating, housed in plastic case. **£1.00**
SJ24 Black PVC tape (98) 15mm x 25mm strong tape for electrical and household use. **£0.35 per roll**

ODDMENTS
16170. 50 metres asst. colours single strand wire **£0.50**
16187 30 metres stranded wire mixed colours **£0.50**
16178 5 Mains slider switches assorted **£0.50**
SJ76. 1 Board containing 2 x 5 pin, DIN sockets 180 & 2 x 2-pin, DIN loudspeaker sockets. **£0.30**

KNOBBS
SJ62 5 15mm chrome knobs standard push fit **£0.50**
SJ63 Instrument knob black window 129 x 26mm with pointer 1/4" standard screw fit **£0.15**
SJ64 Instrument knob black silver aluminium top 17 x 15mm 1/4" standard screw fit **£0.12**

BI-PAK'S OPTO BARGAIN OF THE YEAR

Valued at over £10 - Normal Retail - We offer you a pack of 25 Opto devices to include LED's Large and Small in Red, Green, Yellow and Clear. 7 Segment Displays both Common Cathode and Common Anode PLUS bubble type displays - like DL-33. Photo Transistors - similar to OCP71 and Photo Detectors - like MEL11-12. This whole pack of 25 devices will cost you just **£4.00!**

And we guarantee your money back if you are not completely satisfied.

FULL data etc. included
O No. SJ120.



SILICON TRANS.
SJ25 100 Silicon NPN transistors all perfect and coded mixed types with data and equivalent sheet no rejects **£2.50**
SJ26. 100 Silicon PNP transistors all perfect and coded mixed types and cases, data and equivalent sheet. **£2.50**
SJ27 50 Assorted pieces of SCR's, diodes and rectifiers incl stud types, all perfect no rejects, fully coded data incl **£2.50**

TTL's
SJ28 20 TTL74 series gates assorted 7401-7460 **£1.00**
SJ53 Mammoth IC Pak Approx. 200 pcs assorted full out integrated circuits including logic 74 series Linear audio and DTL many coded devices but some unmarked you to identify **£1.00**

RESISTORS
SJ1 200 Resistors mixed values **£0.50**
SJ2 200 Carbon resistors 1/4 1/2 watt preformed **£0.50**
SJ3 100 1/8 watt miniature resistors mixed values **£0.50**
SJ4 60 1/2 watt resistors mixed values **£0.50**
SJ5 50 1/2 watt resistors mixed pot values **£0.50**
SJ7 30 2 1/2 watt wirewound resistors mixed **£0.50**

CASSETTES SUPER VALUE
And A GREAT SAVING!!!
C120 Cindy Cassettes Low noise outstanding value and sound O No. SJ32 **10 for £3.50**



PRECISION VOM MULTITESTER
20,000ohms volts DC Complete with test leads and instructions.
OUR SPECIAL OFFER PRICE £11.00 each
Use your Barclay or Access Card!
O No. 1323



NPN TRANSISTORS
SJ68 30 ZTX300 type transistors NPN preformed for PC Board colour coded Blue all perfect **£1.00**
SJ70 25 BC107 NPN TO106 case perfect transistors Green Spot **£1.00**
SJ71 25 BC177 PNP TO106 case perfect transistors code C1395 **£1.00**
SJ72 4 2N3055 silicon power NPN transistors TO3 **£1.00**

POTENTIOMETERS
16173 15 Assorted Pots **£0.50**
SJ54 20 Assorted Slider Pots **£1.00**
SJ56 10 100K Lin Slider Pots 40mm **£0.50**
16186 25 Pre sets Assorted **£0.50**
SJ49 8 Dual gang carbon pots log and lin mixed values **£1.00**
SJ50 20 Assorted slider knobs chrome/black **£1.00**

METAL SLIDERS
Metal Case Dual Slider Pots 45mm travel
SJ65 10K loq **£0.25 each**
SJ66 100K lin **£0.25 each**
SJ67 Chrome slider knobs to fit **£0.10 each**

BI-PAK

Send your orders to **DEPT ET18, BI-PAK PO BOX 6 WARE HERTS. SHOP AT: 3 BALDOCK ST. WARE HERTS. TERMS: CASH WITH ORDER, SAME DAY DESPATCH, ACCESS. BARCLAYCARD ALSO ACCEPTED. TEL: (0920) 3182. GIRO 388 7006**
ADD 15% VAT AND 50p PER ORDER POSTAGE AND PACKING

GREENWELD

443A Millbrook Road Southampton SO1 0HX

All prices include VAT @ 15% — just add 40p post

HAVE YOU GOT YOUR COPY OF THE AMAZING GREENWELD CATALOGUE YET????

WHY NOT?? — LOOK AT ALL THESE FEATURES:

- * 60p Discount Vouchers
 - * Quantity Prices for bulk BUYERS
 - * Bargain List Supplement
 - * Ready paid envelope
 - * Priority Order Form
 - * VAT inclusive prices
- Also included is the NEW VERO catalogue, normally 40p on its own!!
ALL THIS FOR JUST 40p + 35p post!!!
 Can you resist such an offer????

SLIDER POT SCOOP!!!

Made by Pihar, types PL40CP & PL60C. Sitty prices for superb goods!!
 PL40CP — 69x16x9mm, 40mm slide length, 220R, 2k2 or 10k (in only). Prices (any mix): 1-24 20p; 25-99 17p; 100+ 14p.
 PL60C — 84x10x7mm, 60mm slide length, 5k, 10k, 22k and 100k log. only. Prices (any mix) 1-24 20p; 25-99 22p; 100+ 17p.

BUZZERS, MOTORS & RELAYS

Z401 Powerful 6V DC buzzer, all metal construction, 50mm dia x 20mm 70p.
 Z402 Miniature type buzzer, 6, 9 or 12V, only 22x15x16mm Very neat 53p.
 Z450 Miniature 6V DC motor, high quality type 32mm dia x 25mm high, with 12mm spindle. Only 1.1.
 A372 Audible Warning device — solid state circuit drives high efficiency transducer to give high output. Voltage reqd 4-18V. Can also be driven direct from TTL or CMOS. Module size 45x21x12mm. Comprehensive data supplied 1.80.
 W892 Heavy Duty 12V relay, ideal for car use — single 15A make contact. Coil 25R in sealed metal can with mounting bracket 86p.
 W890 DIL Relay SPCO 2.4-10V, 200R coil. Only 1.20.

FSRA60 relay, 2 x 10A contacts, 1M, 18. Coil is 250R, and rated 60V ac, but works on 12-24 DC. Solid Encapsulation with screw terminals makes it ideal for car use. 1.20.

REGULATED PSU PANEL

Exclusive Greenweld design — better spec. than anything on the market being offered at the price. Panel 110x82x33mm high contains all components including bridge rectifier and smoothing capacitor. Ready built and tested — just add a 30V 2A transformer and two pots for a fully variable voltage and current supply.

SPEC: Output voltage 0-28V
 Output current 20mA-2A
 Source Impedance 0R1
 Open circuit ripple 10mV

* Send SAE for full details of the many ways this useful module can be used, together with price list of parts for various options. Only 1.75

TRANSISTOR PACK K516

Take advantage of this unbelievable offer!! Small signal NPN/PNP transistors in plastic package at an incredibly low, low price!! Almost all are marked with type number — almost all are full spec. devices. Some have bent leads. Over 30 different types have been found by us including BC184 / 212 / 238 / 307 / 328, BF 196 / 7, ZTX107 / B / 9 / 342 / 450 / 550, etc. Only available as a mixed pack at 1.25 per 100. 1.25 per 1000.

BUY A COMPLETE RANGE OF COMPONENTS AND THESE PACKS WILL HELP YOU

ALL PACKS CONTAIN FULL SPEC. BRAND NEW MARKED DEVICES. SENT BY RETURN OF POST. VAT INCLUSIVE PRICES.

- K001** 50V ceramic plate capacitors, 5%, 10 of each value 22pF to 1,000pF, total 210. 1.39.
K002 Extended range 22pF to 0.1µF, 330 values 1.59.
K003 Polyester capacitors, 10 each of these values: 0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1, 0.15, 0.22, 0.33, 0.47µ, 110 altogether for 1.59.
K004 Mylar capacitors, min 100V type 10 each all values from 1,000pF to 10,000pF. Total 130 for 1.59.
K007 Electrolytic capacitors 25V working small physical size, 10 each of these popular values 1, 2.2, 4.7, 10, 22, 47, 100µF. Total 70 for 1.59.
K008 Extended range, as above, also including 220, 470 and 1000µF. Total of 100 for 1.59.
K021 Miniature carbon film 5% resistors CR25 or similar, 10 of each value from 10R to 1M, E12 series. Total 610 resistors 1.15.
K022 Extended range, Total 850 resistors from 1R to 10M 1.59.
K041 Zener diodes 400mW 5% BZ88, etc. 10 of each value from 2.7V to 36V, E24 series. Total 280 for 1.37.

TM4030 RAM

4096 bit dynamic RAM with 300ns access time, 470ns cycle time, single low capacitance high level clock i/p, fully TTL compatible, low power dissipation. Supplied with data 1.25.

COMPONENT PANELS

Z525 Contains 11 800mA 60V 2N5061 SCRs, 11 6V8 zeners, 11 1N4004 diodes plus Rs, Cs, etc. Only 1.1.
 74 Series ICs — Gates and complex logic, 20 asst ICs on panels 1.1; 100 ICs 1.4.
 Z527 2x6V read relays 6x2S030 or 2S230, 6x400V rectx, plus Rs. Only 50p.
 Z531 Trippot Pack — Ex-computer panels with 20 mixed value multi-turn types 1.00.

VEROCASE SALE!!!

Only one size left now — these have sold very fast — if you want a 1/2 price case like 75-3008, only in GREEN, order one now!! 21051 180x120x85mm 1.20.

P.C. ETCHING KIT Mk IV

The best value in etching kits on the market — contains 100 sq ins copper clad board, 1lb Ferric Chloride, Etch resist pen, abrasive cleaner, two miniature drill bits, etching dish and instructions. **AM for 1.45.**


BULK SUPPLIES

All new full spec. devices. Prices are for a minimum of 100 of any one device and exclude VAT, which must be added at 15%. Minimum order value from this section is 10 + VAT + post. VAT receipt on request.

AC187K	.20	8F757	.27
AD181/2	.45	BFR40	.17
BC107	.07	BFV43	.32
BC108	.08	BFY17	.18
BC109	.07	BFY50	.13
BC114	.06	BFY51	.13
BC117	.07	BFY52	.13
BC118	.05	BFY58A	.16
BC119	.14	BFY58A	.16
BC125	.06	BFY54	.15
BC139	.14	BR101	.28
BC147	.06	BRX48	.095
BC148	.06	BRX46	.17
BC148B	.06	BSX20	.075
BC149	.06	BSY38	.12
BC159	.06	BSY56	.10
BC168C	.065	BSY82	.19
BC169C	.065	BSY85	.23
BC172C	.06	BSY95A	.065
BC177	.07	BT121	.90
BC182B	.045	BU205	.60
BC183B	.045	BU206	.60
BC184L(T05)	.045	BU407	.60
BC212	.045	CV7001	.23
BC212B	.045	CV7493	.19
BC213L	.045	CV7588	.18
BC234L(T05)	.045	ME0475	.065
BC237	.05	MJE340	.22
BC237B	.05	MPS2369	.08
BC237C	.065	MPS2369A	.06
BC238B	.06	MPS2381	.06
BC239B	.065	MPSA66	.24
BC252	.07	OC44	.19
BC256A	.05	OC45	.17
BC308	.05	OC139	.26
BC308B	.065	OC271	.63
BC320	.07	PBC108	.065
BC328	.07	TIP32	.22
BC337	.07	TIP41A	.28
BC348	.07	TIP42A	.29
BC361	.14	TIP2955	.46
BC413	.06	TIP3055	.45
BC485B	.06	TIS91	.12
BC486A	.06	ZTX107	.06
BC546B	.06	ZTX121	.06
BC547C	.065	ZTX121A	.06
BC548B	.06	ZTX303	.07
BC555A	.06	ZTX311	.07
BC556B	.06	ZTX313	.06
BC557A	.06	ZTX341	.07
BC737	.07	ZTX450	.06
BCX32	.06	ZTX501	.96
BCX33	.06	ZTX503	.07
BCY32	.12	ZTX550	.06
BCY71	.11	2N1021	.94
BCY72	.10	2N1132	.16
BD112	.64	2N1377	.62
BD131	.18	2N1711	.18
BD132	.18	2N1893	.16
BD133	.18	2N2389	.12
BD137	.20	2N2846	.34
BD138	.20	2N2894	.12
BD181	.40	2N2927	.045
BD184	.45	2N2928	.045
BD246	.30	2N3053	.13
BD278A	.32	2N3064	.34
BD433	.32	2N3055	.30
BD525	.24	2N3442	.78
BD526	.24	2N3583	.42
BD543A	.40	2N3618	.80
BD66A	.45	2N3702.10	.045
BD696A	.45	2N4124	.08
BF173	.13	2N4400	.08
BF181	.15	2N4401	.06
BF195	.065	2N4403	.06
BF196	.065	2N4410	.06
BF197	.065	2N5193	.20
BF198	.065	2N5195	.22
BF241	.065	2N5401	.17
BF255	.075	2N5447	.06
BF257	.19	2N5831	.08
BF258	.20	2N6121	.16
BF324	.13	2SC536	.06
BF337	.19	2SC1817	.62
BF355	.18	2SC2068	.43
BF394	.065	2SC2073	.45
BF414	.065		
BF450	.065		
BF451	.09		

Send SAE for latest bulk buyers list.

MONITORS MONITORS MONITORS

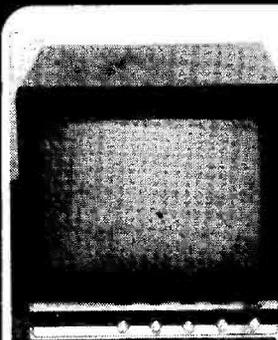

Uncased from 3" to 12"
 Cased from 5" to 20"

Semi professional or professional available from stock.

Monitor PCB's including Transformers and Tubes also in stock.

Phone or write for details.

CROFTON ELECTRONICS



Crofton Electronics Limited
 35 Grosvenor Road, Twickenham, Middx.
 Tel: 01 891 1513

Conquer the chip.

Be it career, hobby or interest, like it or not the Silicon Chip will revolutionise every human activity over the next ten years.

Knowledge of its operation and its use is vital. Knowledge you can attain, through us, in simple, easy to understand stages.

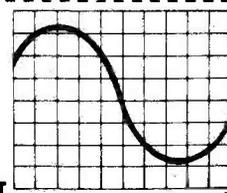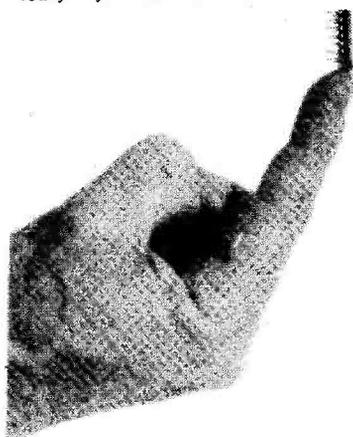Learn the technology of the future today in your own home.



TUTORCOURSE ELECTRONICS

Please rush me details of your ELECTRONICS COURSE

Name _____

Address _____

Block Caps. Please

Post now, without obligation to
 ETI 8
British National Radio & Electronics School.

4 Cleveland Road, St. Helier, Jersey, G.I.

FREE BROCHURES

No previous knowledge is necessary.
 — Just clip the coupon for a brochure

MICROFILE

... And as Henry Budgett sinks slowly in the West, we wish a fond farewell to Microfile. It's the last one folks.

After a year or so of producing this monthly column Microfile is taking off for pastures new. This is the last time these articles will appear in this format. More later, but first the news. Seldom does a week or even a day pass without a new computer or allied peripheral appearing on the market. Some are destined to survive, others disappear without trace. We first heard news of the new Sharp hand-held system some months ago in the form of a typical murmur from the depths of a Press lunch. Reality has arrived rather sooner than we expected in the top pocket of a South African visitor to our offices. Here is a brief taster of what the machine has to offer plus a couple of photographs to tantalise.

Sharp Pointed?

At first glance the PC 1211 looks not unlike a conventional pocket calculator, until you let your eyes roam the keys and find a full alpha set and several other definitely non-standard items like a 20 characters wide display. Inside are two very well packed PCBs, the three silver oxide cells and a piezo sounder that bleeps mad-deningly when you make stupid mistakes! Marks out of ten for packaging and useability are about 9½. Perhaps they could have made the key idents on the 'shifted' functions a little bolder.

The user has at his disposal a conventional four function calculator with the added bonus of a full Microsoft type BASIC and the capability to store the programs on cassette. The cassette cradle plugs into the left hand side of the machine and increases the length by about one third. This then connects directly to a conventional audio cassette. Program storage is slightly slow but adequate. One interesting point is that the system produces the sound of the data tones through the bleeper whilst loading or dumping — a good reassurance that at least something is happening.

The memory capacity is sufficient for about 1 to 2Ks worth of normal program, which is quite sufficient when looked at in terms of pure calculations, but the use of text in copious quantities is obviously going to reduce this.

Pocketability

The unit comes complete with expansive notes, manuals and programming examples, apparently of better quality English than previously encountered from Sharp.


Some of the BASIC command set is totally unexpected on a machine of this size. You can write to and read from files on tape, you have all the usual scientific functions such as sines and logs, you have PRINT USING for neatly formatted displays and you even have a debug mode. By this time many of you will be thinking that this souped-up, hand-held version of your programmable calculator will cost you a fortune and why replace your calculator anyway?

The expected UK cost of the system, complete with



Sharp's PC 1211 — the shape of things to come?

the cassette cradle, is between £125 and £130 and they are to be launched onto the market in late July. This is far more than a grown-up programmable calculator, for one thing it can work interactively. This means that when you run your programs after a few months writing them you can quickly remember what it did. You can, after all, name your programs when you store them — just try doing that with a conventional programmable! It has been reported that the system took on, and beat, an HP 41C to the considerable chagrin of that August company — we didn't have time to test this claim but would love to try and run a "Benchmark" type trial between this, the TI 58/59, the HP 41C and the Casio 501/2.

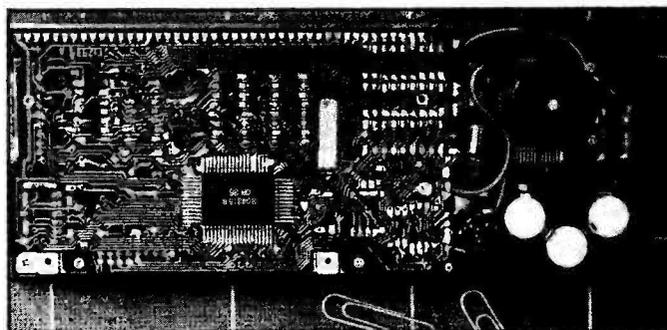

The PC 1211's PCB. Sometimes it sits and thinks, sometimes it just sits.

Overall, then, it is a very impressive piece of kit, certainly another strong indication of the way that things are moving, with new customised chips taking over from boards full of TTL and CMOS, rather like a miniature version of the HP 85. The owner of the machine that we borrowed was a mining engineer who was mainly involved in electronic control design, etc and after three months of use he had yet to find a job that was too big to fit into its memory.

The question left in my mind is "If the calculator killed the slide rule stone dead will this do the same to the programmable market?". If that sounds a little strong just try it against one and see!

Club Call

Some final entries into the list of computer clubs this month. Anyone into the TRS-80 and living in the North East of England might be interested in a new User Group. Acting as a sub-group of the Newcastle upon Tyne Personal Computer Society they hold meetings every third Wednesday in Room A 102 of the Polytechnic and cater for both the hardware and software enthusiast. Anyone interested in joining or receiving further details should contact Dr Stan Tetlow on Washington 462552 or Mr Barry Dunn on Stanley 30184.

Owners of the ZX80 may like to know of a National Users Club that has been formed. The main output will be a bi-monthly newsletter and a software bank as well as the provision of technical support. Membership fees have been set at £6 for the UK and £10 for overseas. Further information can be obtained from ZX80 Users Club, PO Box 159, Kingston upon Thames, Surrey KT2 5UQ, but please enclose an SAE.

Video What?

Microfile is currently trying to achieve the impossible dream and get connected to Prestel. Why the impossible dream? Well, we've tried two sets and had the PO connection re-wired three times so far without a great deal of success! The story of our mis-fortunes carries on and on, but — eventually — we got connected. This tale of woe is by no means unique and is a very sad state of affairs. We do have a considerable lead in the Viewdata field in this country, two years of operational experience, but we appear to be in considerable danger

of throwing it all away because people won't buy something they can't rely on. It is not the fact that the database computers fail sometimes (you do generally have a spare anyway) but that the people who install the PO lines and the people who make the sets and, worst of all, the people who sometimes install the sets all talk different languages. The sooner the PO put together a crack team of engineers who understand the equipment and use them and only them to install the necessary equipment the better off we'll all be.

This country is, for once, leading the world in one area of computer-based technology. It would be a great shame to see that lead lost because no-one could rely on the competence of the people who come to fit it. You wouldn't, after all, ask a TV repairman to fix your washing machine or an electrician to install your central heating. No-one is knocking the concept of Viewdata, but it is in severe danger of strangling itself with its own telephone wires!


69999 PRINT"END":END

The death of this column has been stimulated by the production of a new series for ETI on the fundamentals of computers. It is intended to start next month with an article on how technology has developed to give rise to the micro and the whole series will be orientated towards the hardware. It is also hoped that the material will be followed by some constructional features based on the developing microprocessor technology. So, until next month under a new heading it's farewell from Microfile

ETI

THE GOULD OS253

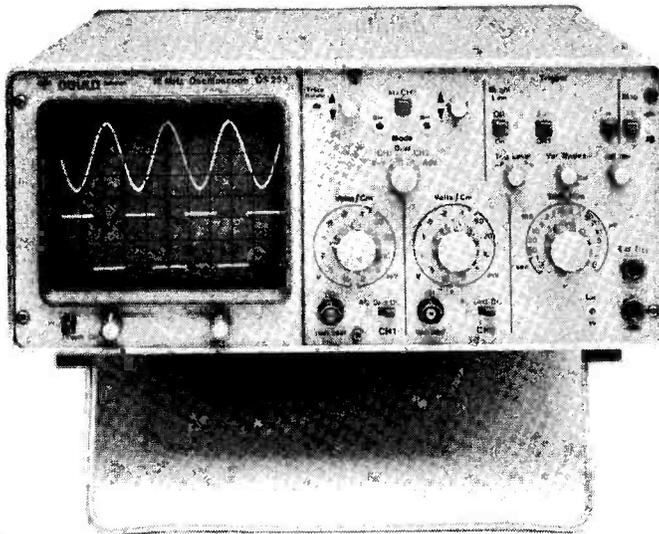A professional-quality, dual trace oscilloscope for just £299 including VAT & P&P



Faultfinding, circuit testing or servicing!
An oscilloscope is indispensable. Saves time and costly mistakes and enables you to tackle more ambitious electronic projects. Gould offer you this professional-quality, dual-trace instrument at a price which brings it within reach of every enthusiast. Just look at these great features — then compare the OS253 for value, and send for yours today!

- ★ DC-12MHz Bandwidth ★ 2mV/cm sensitivity
- ★ Dual-trace ★ Time-base speed to 100nS/cm
- ★ Clear controls, simple operation
- ★ Full 8 x 10 cm display
- ★ 2-year guarantee with every instrument


GOULD

Gould Advance Limited, Roebuck Road, Hainault, Essex IG6 3UE. Telephone: 01-500 1000

Please send me an OS253 Oscilloscope
I enclose herewith a cheque for £299 inc. VAT & Postage and Packing
Please make cheques payable to Gould Advance Ltd.

NAME _____
ADDRESS _____
Block Capitals Please
ETI 1

IT'S AS EASY AS A,B,C...

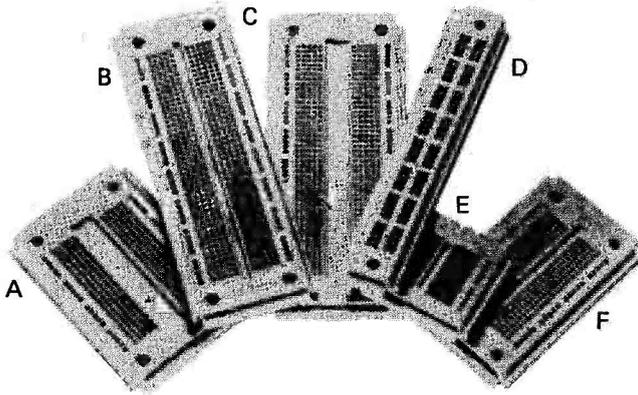

- A **EXP 650** For microprocessor chips. **£3.60**
- B **EXP 300** The most widely sold breadboard in the UK; for the serious hobbyist. **£5.75**
- C **EXP 600.6"** centre channel makes this the Microprocessor Breadboard. **£6.30**
- D **EXP 4B** An extra 4 bus-bars in one unit. **£2.30**
- E **EXP 325** Built in bus-bars accepts 8, 14, 16 and up to 22 pin ICS. **£1.60**
- F **EXP 350 270** contact points, ideal for working with up to 3 x 14 pin DIPS. **£3.15**
- G **PB6** Professional breadboard in easily assembled kit form. **£9.20** (Not illustrated.)
- H **PB 100** Kit form breadboard recommended for students and educational uses. **£11.80** (Not illustrated.)

& IT'S AS EASY AS 1,2,3 with THE EXPERIMENTOR SYSTEM


SCRATCHBOARD
-BREADBOARD
-MATCHBOARD

1. EXP 300PC which includes one item. A matchboard pre-drilled PCB - £1.32
2. EXP 302 which includes three items. Three 50-sheet scratchboard workpads - £1.68
3. EXP 303 which includes three items. Two matchboards and an EXP 300 solderless breadboard - £8.60
4. EXP 304 which includes four items. Two matchboards and EXP 300 breadboard and a scratchboard workpad - £9.30

The above prices do not include P&P and 15% VAT

TOMORROWS TOOLS TODAY

CONTINENTAL SPECIALTIES CORPORATION

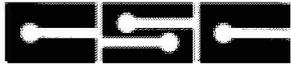

C.S.C. (UK) Limited, Dept. 900,
Unit 1, Shire Hill Industrial Estate,
Saffron Walden, Essex CB11 3AQ.
Tel: Saffron Walden (0799) 21682
Telex: 817477

NAME _____

ADDRESS _____

I enclose cheque/PO for £ _____

or debit my Barclaycard, Access, American Express card

No. _____ Exp. date _____

or Tel: (0799) 21682 with your card number and your order will be in the post immediately.

A EXP 650 £5.00	Qty. Reqd.	B EXP 300 £7.76	Qty. Reqd.
C EXP 600 £8.39	Qty. Reqd.	D EXP 4B £3.50	Qty. Reqd.
E EXP 325 £2.70	Qty. Reqd.	F EXP 350 £4.48	Qty. Reqd.
G PB6 £11.73	Qty. Reqd.	H PB 100 £14.72	Qty. Reqd.

Experimenter System

1 EXP 300 PC £2.38	Qty. Reqd.	2 EXP 302 £2.79	Qty. Reqd.
3 EXP 303 £11.04	Qty. Reqd.	4 EXP 304 £11.86	Qty. Reqd.

Boxed prices include P & P and 15% VAT
If no dealer in your area contact CSC direct. FREE catalogue tick box

Continental Specialties Corporation, (U.K.) Limited, Dept. 900,
Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex. Tel: (0799) 21682

...ASK OUR DEALERS.

AITKEN BROTHERS,
35 High Bridge, Newcastle Upon Tyne, NE1 1EW.
Tel: 0632 26729.

ARROW ELECTRONICS LTD.,
Leader House, Coptfold Road, Brentwood, Essex.
Tel: 0277 226470.

BASIC ELECTRONICS LTD.,
18 Epsom Road, Guildford, Surrey, GU1 3JN.
Tel: 0483 39984.

BI-PAK SEMICONDUCTORS,
P.O. Box 6, Ware, Herts.
Tel: 0920 3442.

F. BROWN & CO.,
45 George IV Bridge, Edinburgh, EH1 1EJ, Scotland.
Tel: 031 225 3461. Telex: 922131.

THE CHILDRENS SHOP & TACKLE BOX.,
73-75 High Street, Ryde, Isle of Wight.
Tel: 0983 63437.

CUBEGATE LTD.,
301 Edgware Road, London, W2 1BN.
Tel: 01 724 3565.

ETESON ELECTRONICS,
15b Lower Green, Poulton-Le-Fylde, Blackpool, FY6 7JL.
Tel: 0253 885107.

H. GEE ELECTRONIC SUPPLIES,
94a Mill Road, Cambridge, CB1 2BD.
Tel: 0223 358019.

LEEDS AMATEUR RADIO,
27 Cookridge Street, Leeds, LS2 3AG.
Tel: 0532 452657.

MARSHALLS,
108A Stokes Croft, Bristol.
Tel: 0272 426801.

85 West Regent Street, Glasgow, G2, Scotland.
Tel: 041 332 4133.

325 Edgware Road, London, W2.
Tel: 01 723 4242.

40 Cricklewood Broadway, London, NW2 3ET.
Tel: 01 452 0161.

RASTRA ELECTRONICS LTD.,
275-281 King Street, Hammersmith, London, W6.
Tel: 01 748 3143. Telex: 24443 RASTRA G.

SHUDEHILL SUPPLY COMPANY,
53 Shudehill, Manchester, M4 4AW.
Tel: 061 834 1449.

SPECTRON ELECTRONICS (M/C) LTD.,
7 Oldfield Road, Salford, M5 4NE.
Tel: 061 834 4583.

SWANLEY ELECTRONICS,
32 Goldsel Road, Swanley, Kent, BR8 8EZ.
Tel: 0322 64851.

TECHNOMATIC LTD.,
17 Burnley Road, London, NW10 1ED.
Tel: 01 452 1500. Telex: 922800.

TOMORROW'S TOOLS TODAY

Also ask your local stockist.

If no dealer in your area, contact CSC direct.

CONTINENTAL SPECIALTIES CORPORATION



C.S.C. (UK) Limited, Dept. 900,
Unit 1, Shire Hill Industrial Estate,
Saffron Walden, Essex CB11 3AQ.
Tel: Saffron Walden (0799) 21682
Telex: 817477

TECH TIPS


Linear Temperature To Frequency Transducer

J.P. Macaulay, Crawley

This circuit provides a linear increase of frequency of 10 Hz/°C over 0-100°C and can thus be used with logic systems, including micro-processors.

The heart of the system is the temperature probe Q1 whose V_{be} changes at 2.2 mV/°C. Since this transistor is incorporated in a "constant" current source circuit it follows that a current proportional to temperature will be available to charge C1.

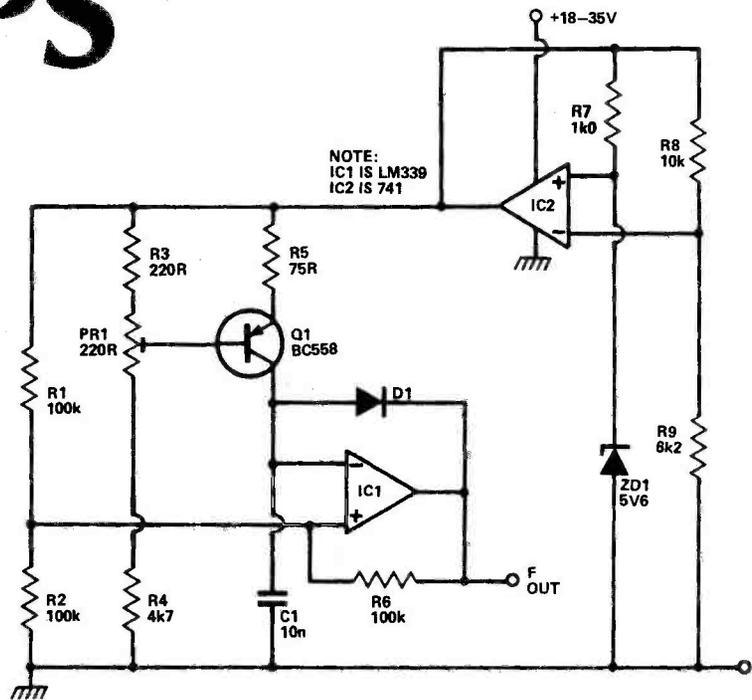The circuit is powered via the temperature stable reference



voltage supplied by the 741. Comparator IC1 is used as a Schmitt trigger, the output of which is used to discharge C1 via D1. To calibrate the circuit Q1 is immersed in boiling

distilled water and PR1 adjusted to give 1 kHz output.

The prototype was found to be accurate to within 0.2°C against a Comark thermocouple meter.


Ropelights Sequencer

G.J. Phillips, Durham

This circuit produces signals for the "travelling lights" disco ropelights effect. IC1a and b are connected as a standard CMOS astable. The frequency and hence speed of the travelling lights can be selected by SW1.

The output of the astable is fed to the clock input of the CMOS decade counter IC2. This counter has the advantage of having a built-in decoder giving a logic 1 at each output in turn. Reliable reset is provided at the count of four by the bistable formed by IC1c and d.

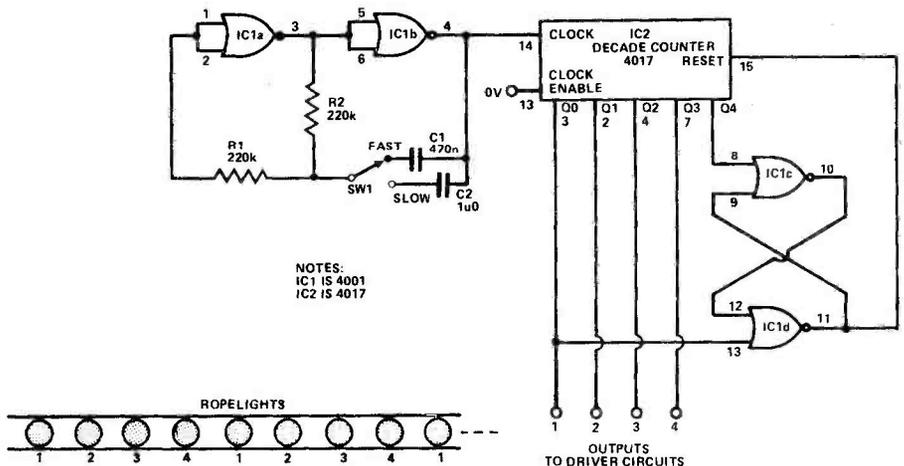Outputs 1,2,3,4 must be connected via drive circuits which can



be simply power transistors for low voltage lamps or triacs for series-connected mains operated lamps.

The outputs of the driver circuits are connected to the lamps in groups as shown.


Tech-Tips is an ideas forum and is not aimed at the beginner. We regret we cannot answer queries on these items. ETI is prepared to consider circuits or ideas submitted by readers for this page. All items used will be paid for. Drawings should be as clear as possible and the text should preferably be typed. Circuits must not be subject to copyright. Items for consideration should be sent to ETI TECH-TIPS, Electronics Today International, 145 Charing Cross Road, London WC2H 0EE.

Dimmer With RFI Suppression

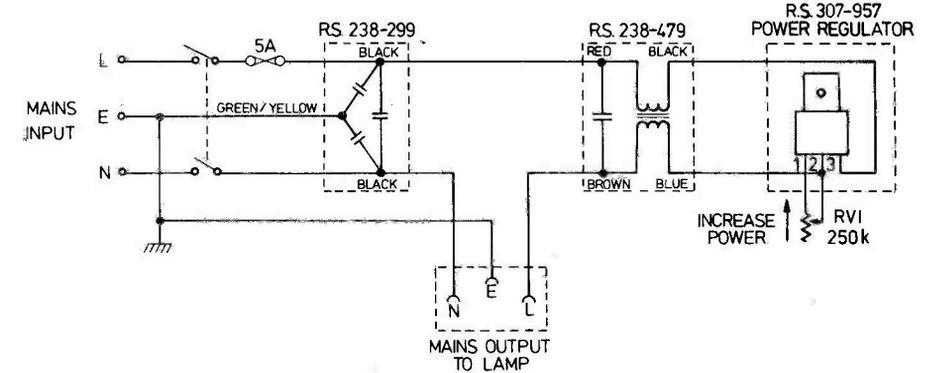D. Wedlake, Cardiff

The circuit shows how a mains power regulator can be used to control a 1 kW tungsten lamp with good radio interference suppression. It was built primarily for photographic applications but can be used with many other types of loads such as heaters or AC motors, providing the maximum rating is not exceeded. However, if used to control motors or any inductive loads, it will be necessary to connect a snubber network between terminals 2 and 3. A 100 R resistor in series with a 100 nF 250 V AC capacitor (eg RS 238-463) would be suitable.

The IC regulator used is a solid-state AC mains power three-terminal device which, when used with the external 250 k potentiometer, RV1, controls the power to the load by varying the phase angle of the applied AC potential. The typical control conduction angle is 0-155°



which corresponds to a maximum power transfer of approximately 98% for a resistive load. The graph shows how the output voltage varies with various values of RV1. When used at full load current, the device should be mounted on a heat sink having a thermal rating of 4°C/watt (eg RS 401-497). Alternatively, as the tab is electrically isolated, it may be fixed directly to the chassis for heat dissipation.

Note that as the slider of RV1 is at Mains Potential the potentiometer should have an insulated shaft.


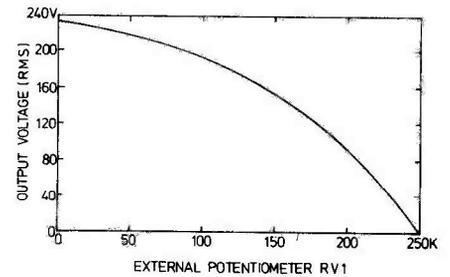


Fig. 2 Variation of output voltage with RV1 (input voltage = 240RMS)

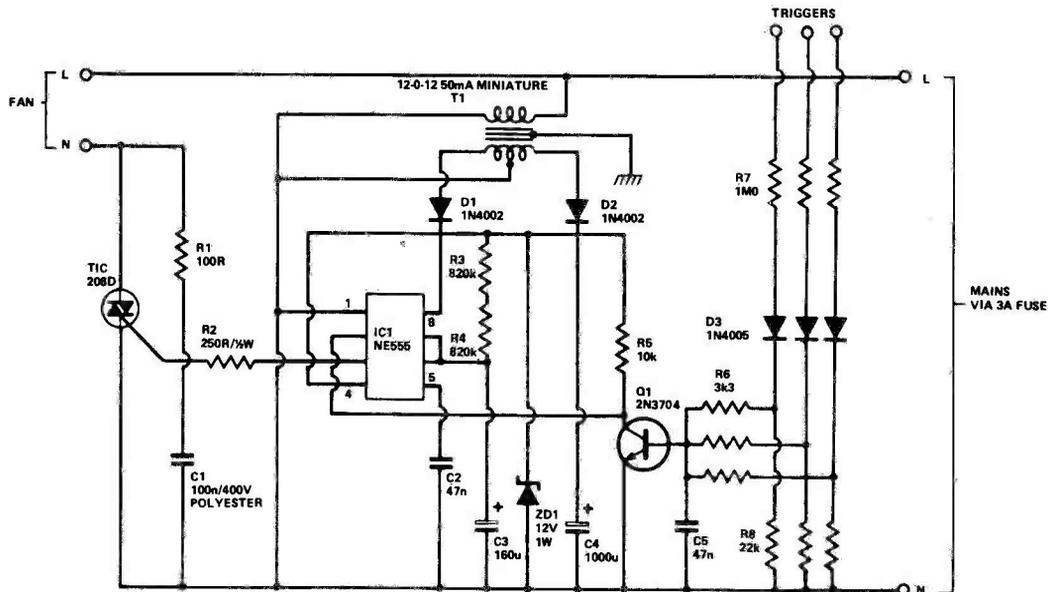

Extractor Fan Controller

B. Carrol, Aldershot

This timer is useful for controlling a bathroom extractor fan, if your family forgets to use it or leaves it

running indefinitely. The trigger or triggers are connected to the live side of one or more lights, which, when switched on, cause Q1 to conduct and trigger IC1. This is a monostable which gives a pulse period of about four minutes and its output gates the triac so that the fan runs. R1, C1 protect the triac against reswitching; C2, C5 protect against mains transients.

If the light is still on at the end of the timing period, the IC is retriggered, but, because C3 has not been fully discharged, the next pulse is less than four minutes. Thus, the fan runs for four minutes or the period the bathroom light is on plus two minutes, whichever is greater.

Note: Careful insulation of the PCB from the case is necessary.

Super Bass Excavator

J.P. Macaulay, Crawley

The main problem with small infinite baffle speaker systems is that the bass response rolls off rather sooner than their larger brothers. This circuit overcomes this problem by boosting the deep bass response of the power amp driving the speakers. Certainly this is not an altogether new idea as regular readers of this magazine well know but this particular circuit does the job rather better than most and the audible improvement is well worth the time and money spent.

The circuit is based around the well known quad op amp LM324. This device contains four independent op amps of the 741 type. Before any purists hold up their hands in horror it should be noted that these are capable of delivering 2 V RMS of 20 kHz sine wave without slew rate problems and that is more than enough to drive

99.99% of all known power amps into clipping.

In order to overcome the crossover distortion problems of these op amps the output stage of each is biased into class A by R7 and R10. C1, C2, R3 and R6 form a Butterworth second order filter which removes any signals below 20 Hz thus preventing amplifier overload from record warp signals. R5 and C2 in conjunction with R8 and C4 produce a shelf in the circuit's response below the frequency determined by the reactance of the capacitors.


Now it so happens that the rate

of roll-off of infinite baffle enclosure is 12 dB per octave and the slope of the filters is the same. Thus, by the simple expedient of choosing the capacitor values to be equal in value and by matching the quoted -3 dB point of the speakers with the +3 dB values in the table one extends the lower -3 dB limit of the speakers by half an octave.


The device must be inserted between the pre and power amplifiers and has a unity gain except in the bass. The maximum gain has been set at 6 dB to prevent amplifier overload.

(+3 dB)

NEW CUTOFF -3 dB POINT	OLD CUTOFF -3 dB POINT	C3,C4
38 Hz	50 Hz	47 nF
45 Hz	60 Hz	39 nF
52 Hz	70 Hz	33 nF
60 Hz	80 Hz	27 nF
68 Hz	90 Hz	22 nF
75 Hz	100 Hz	18 nF

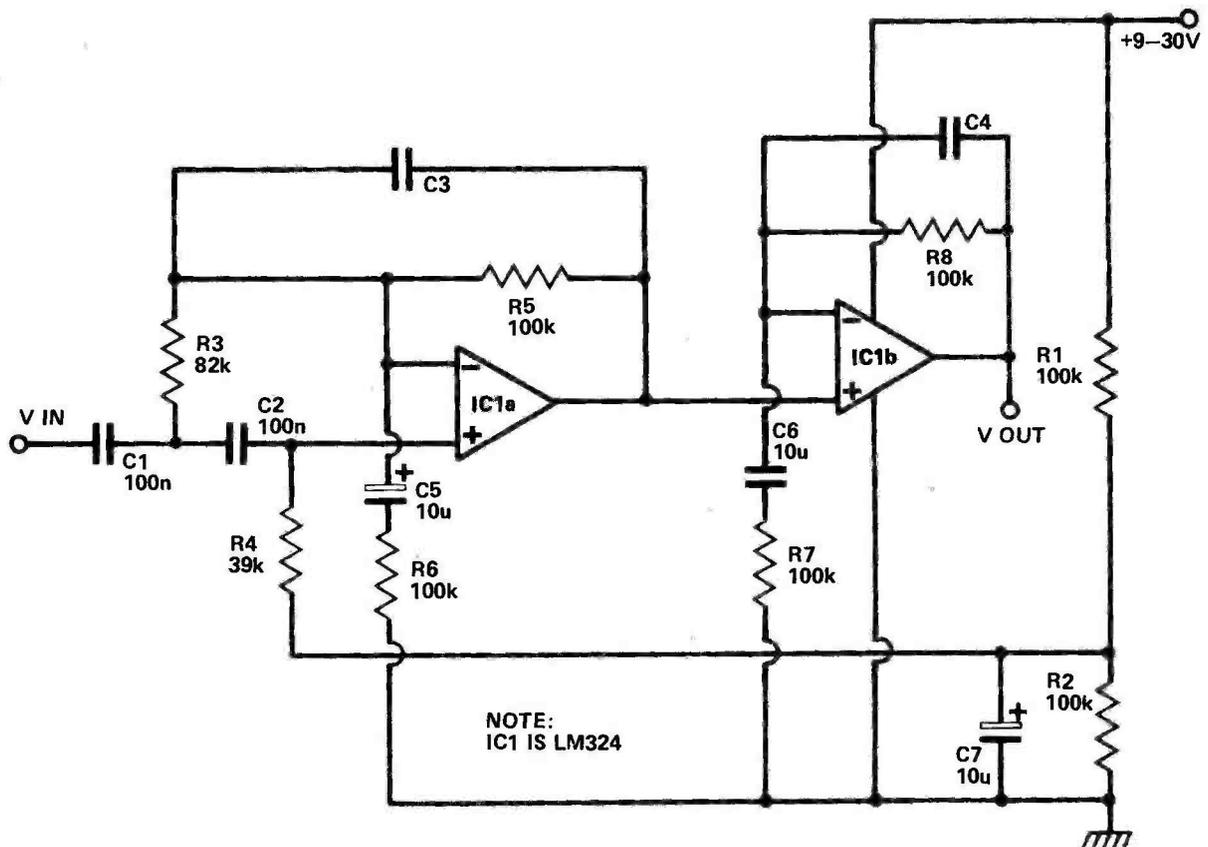

Complete Audio/Tuner Kits

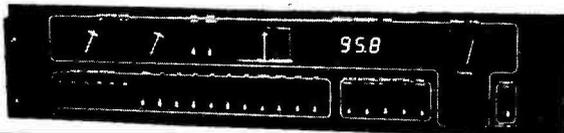

Mk III FM Tuner series

Carriage for Mk III tuner E3 inc

The Mark III series FM tuner has been updated, and now includes a centre zero tuning meter as standard. The instruction manual has been meticulously revised, enabling easy assembly by constructors of various levels of experience - a preview copy may be purchased for £1.00.

Mark III A series 'Reference series' tuner modules£171.35 inc.
 Mark III B series 'Hyperfi' modules, with switched IF BW, pilot cancel decoder£198.95 inc.

A matching synthesiser unit will be made available later this year, and can be retrofitted to either version. All versions include digital frequency readout/clock, VU deviation meters, 6 preset stations, 10 turn pot manual tuning, toroidal PSU, output level adjustment, 110/240v AC input. Full alignment service available.

Power Amplifier

Style and performance - with a real belt and braces PSU design.

After a couple of preview comments, it seems that many of you are waiting to hear about the matching H MOSFET power amplifier for the Mk III tuner. Well, it's out at last - complete with twin toroidal PSUs for comfortable 80W RMS per channel, over 100W peak, but limited by thermal shutdown of the H MOS. 10W-100W log LED output peak indicator, DC offset protection and switch-on pause relay. AC or DC input coupling, direct or relay protected output terminals. The works. Only one version of this item: Complete kit£178.25 inc. Carr. £5.

Preamplifier

More features and facilities, thanks to DC switching and control design


Previewing the most comprehensive audio preamplifier yet..... DC switching of 7 inputs, plus two tape in/outs. 2 low pass, 2 high pass active filters, genuine volume related loudness, 1dB channel matching, with DC volume, balance, bass and treble controls. Suitable for bus/remote control, tape dubbing, switched monitor etc. 80dB S/N+, THD 0.75dB or better. Pluggable PU equalization boards, tone control override. Price for complete unit about £149 ex VAT.

Semiconductors

Radio/Communications ICs

FOR COMPLETE LISTINGS - SEE OUR NEW PRICELIST


CA3089E	2.11	HA1197	1.61	SD6000	4.31
CA3189E	2.53	CA3123E	1.61	TDA4420	2.59
HA1137W	1.95	TDA1072	3.09	MC1330P	1.38
HA11225	2.47	TBA651	2.53	MC1350P	1.38
HA12412	2.81	TDA1090	3.51	KB4412	2.24
KB4420	1.95	TDA1220	1.61	KB4413	2.24
TBA120S	1.15	TDA1083	2.24	KB4417	2.53
KB4406	0.80	TDA1062	2.24	MC3357P	3.16

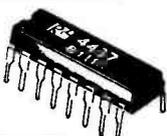

VARICAP DIODES.....

A section from our PL:

BA102	0.35	16:1 ratio AM tuning	2.93
BB204	0.41	KV1215 9v triple	2.01
BB105	0.41	KV1211 9v dual	2.01
BB109	0.31	KV1225 25v triple	3.16
MVAM2	1.93	BB212 9v dual	2.25

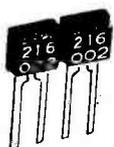

POWER MOSFETS

100W PA's made simple

Since pioneering the 100W complementary MOSFET technique - Hitachi have developed a range of output devices and drivers that ought to revolutionise opinions and attitudes towards the design of all LF amplification systems. We have a new 48 page application note (£1.50 inc) and complete sets of parts, modules and now the new complete PA system (see above).
 2SK133 120V N-ch 100W MOSFET £6.33 2SJ48 Pch complement £6.33
 2SK135 160V N-ch 100W MOSFET £7.29 2SJ50 Pch complement £7.39
 PA101B Kit for 100W MOSFET PA less Heatsink £16.10. (£23 inc heatsink/bkt)

ULTRA LOW NOISE PU PREAMPLIFIER

The HA12017 is the last word in PU preamps, and general low noise audio design. It is an SIL IC, with 86dB S/N in RIAA configuration, 10v RMS output capability, 0.002% typ THD at 10v RMS output (imagine the overload margin !!). It comfortably supercedes discrete circuit designs in terms of price/performance, and takes the art beyond the TDA1042's capabilities. (Replaces HA1457) £1.80 each - or an RIAA applications PCB with two ICs for £5.75. Complete with Rs&Cs £9.95.

Radio Control ICs

We have various RC ICs, including NE544 NE5044, and two new ones from OKI

KB4445 - 4 channel dig.prop. FM TX IC. 30mW out (amplifiable) -£2.30 inc
 KB4446 - 4/5 ch. dig. prop FM RX IC. Suits KB4445 or RCME syst. £2.65.
 KB4445/6 pair: £4.75. New 8 page data sheet 35p + SAE. More RC ICs in list

CMOS, LPSNTTL, TTL, MPU:

Most CMOS is available in low volume - also LPSN. Standard linears and TTL OK.

Listings in the new pricelist.

Things like ICM7216B, ICL8038, 8080A, 6800P, 2708, NE555, NE556, etc

Coming Soon..... Contain yourselves, RF fans! Not yet ready for a full launch until autumn, but previewed here:-

SSB transceiver system : 10kHz to 1000MHz !!

A modular VLF to UHF SSB TX/RX system at last. With the correct first mixer, the basic PCB covers 10kHz to 1000MHz - using LO fed from ext. source (Our 2 IC Mullard synth for instance) and RF PA for TX. OP. 0.2uV basic sensitivity in HF. Typ cost for HF synth SSB RX will be less than £200. Add an RF PA for full TRX for another £50. See one in our foyer, and marvel.

CATALOGUES 60p ea. all three for £1.60
 PRICES SHOWN HERE INCLUDE VAT
 POST/PACKAGE CHARGE NOW 35p

Please send an SAE with all enquiries. Phone orders by ACCESS - but minimum £5. Callers welcome.




200 North Service Road, Brentwood, Essex

TELEPHONE (STD 0277) 230909 TELEX 995194 AMBIT G POSTCODE CM14 4SG

Radio/Audio/Communications Modules

LW-MW-SW-SW DC tuned and switched

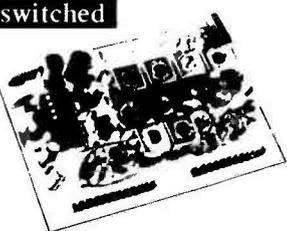91072- All switching of bands by a single pin to gnd. Varicap tuned, with LO output for synth. MW/LW version or MW/LW plus 1 or 2 SW bands MW/LW: £15.58 +1SW £16.73



VHF Tunerheads

Europe's largest stock range for broadcast and communications. Probably also the world's - details in the catalogues and PL. Specials are also supplied in the region 30-220MHz.

Pilot Cancel PLL Stereo decoders

Again, Europe's widest range of stereo decoders including pilot cancel PLL types. The pic shown the 944378 - pilot cancel including post decoder 26/38kHz filtering and muting preamp output



944378-2 £26.45

Switched bandwidth FM IF strips

Broadcast FM IF strips for all occasions, including the new 911225 - with diode switched narrow filter option, ultra linear phase ceramic filters, 84dB S/N, and 0.04% THD (40kHz deviation). Plus usual things like AGC, AFC, dev. mute, level meter drive. £23.95 (supplied in screen can with 0.1 edge connection system) Also the 7230 hyperfi series - as the 911225, but with slope controlled AFC that operates in conjunction with signal level - and an extra IF amp stage for DXing.

Various digital frequency displays

The World's largest range of receiver DFMs is now joined by the DFM7 (shown) - and L shaped version of the DFM3 with remote display mount connector possibility. 1kHz SW resolution with 455kHz or 10.7MHz offsets, 100Hz res up to 3.9999MHz, and VHF to 299.99 MHz in 10kHz steps : £41.75



Components

Crystal Filters

Most popular types are available - ex-stock, and in quantity.

10.7MHz	25kHz Channel spacing	8pole	£16.67
	12 1/2kHz	"	£17.82
	2.4kHz SSB	"	£19.78
	Monolithic dual roofing filter	"	£2.30
34.5MHz	1.3dB loss, 80dB stopband HF	first filter in synth. RX	£36.80
RC XTALS	FM pairs (no splits)	AM pairs	£3.74
	AM pairs	"	£3.57
USB/LSB	Xtals for 10.7SW filter	"	£2.88 ea



Piezo Sounders


The most efficient warning sounders yet

The latest thing in electro-acoustic efficiency. 1mA of drive from CMOS will give an SPL of 83dB - 10v RMS drive from CMOS uses 3mA for 100dB SPL at 4.8kHz (88dB at 1.65kHz). The data sheets shows various drive circuits, and give full specifications with regard to broadband responses and power consumption etc. 1 off 44p inc. 100 off 28.75p (25p ex vat)



Keyboard switches and caps

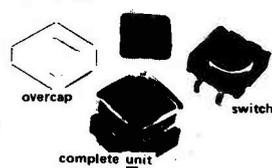From the world's most widely used switch manufacturers - ALPS - come the biggest and best range of keyswitches, and data entry keyboard switches. The SCMB1101 is shown here, with the KT5 2-part cap (with clear top, to enable easy fitting of your chosen legend. Other types are available with built in LED, 90° mounting etc. SCMB1101: 17p, KT5: 16p - or 29p/pair



LCD CLOCKS

Clocks use 1.5v at 15uA only. DVM 9v/1mA

CM161:	7mm LCD 12/24hr, alarms etc	£11.44 each
CM172:	13mm, 12hr, alarms, timer etc	£14.32 each
CM174:	13mm, 12hr, min/sec stopwatch	£14.32 ea
DVM 176:	ICM7106 based LCD 3 1/2 digit	£22.36 each



WHAT'S NEW at AMBIT

NEW PRICELIST/SHORTFORM: 28 pages, FOC with A5 SAE pse

Bigger print than our recent one page list - and vastly extended

If you still need convincing to invest £1.60 in the cats, be mean and get this first.


POWER MOSFET APPLICATIONS HANDBOOK by HITACHI :

£1.50 each - or free with pairs of H MOS and the PA101B.

Everything you should know about H MOSFET devices theory and applications.

Parts 1-3 AMBIT catalogues 60p ea, or £1.60 the lot.

'TUSCAN' FROM TRANSAM

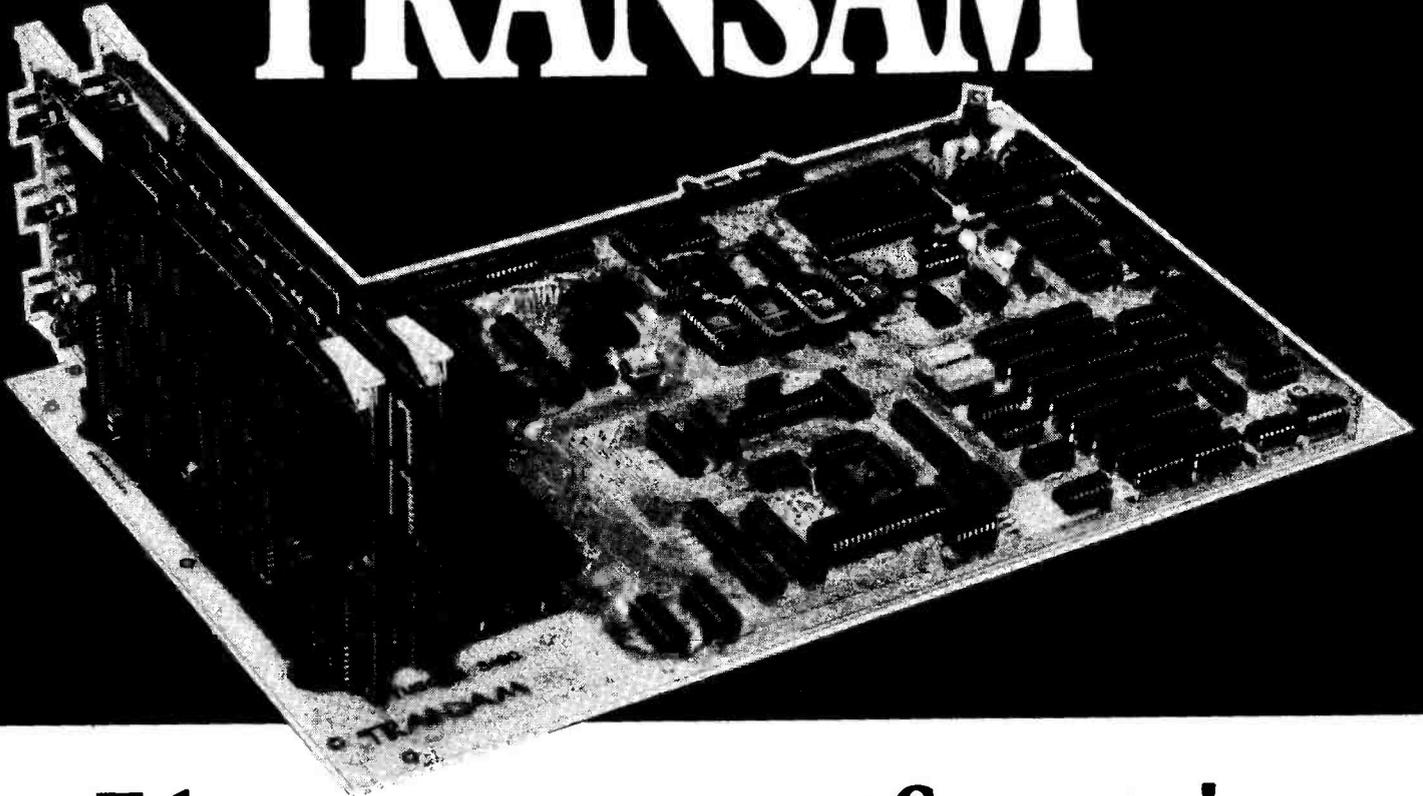

Take a step up to your next Computer!

THE CONCEPT

How many ways are there to build an S100 system? Not many, and all expensive. TUSCAN changes all that.

Five S100 boards on one single board—just for starters. Plus five extra slots for future expansion.

What a combination! Z80 and S100 with the TRANSAM total package of system and applications software.

How do we do it? Our prices start at £195 and you can build up in easy stages to a fully CP/M compatible disc based system. Something to think about!

THE HARDWARE

The first Z80 single board computer with integral S100 expansion. British designed to the new IEEE (8 BIT) S100 specification, the TUSCAN offers total system flexibility. A flexibility available now.

The board holds the equivalent of a Z80 cpu card, 8k ram, 8k rom video and I/O cards with 5 spare S100 expansion slots and offers a price/performance ratio which is hard to beat.

Just compare our price with a commercial S100 ten slot motherboard with this specification.

THE SOFTWARE

TUSCAN offers the user the choice of system monitor, editor, resident 8k basic, resident Pascal compiler or full CP/M disk operating system. All options are upwards

compatible and fully supported with applications software. Both 5¼" and 8" drives are supported in double density.

THE PACKAGE

TUSCAN is available in kit form or assembled. With several hardware and software options to suit your requirements and budget. Attractive desk top case also available holds 2 x 5¼" Drives.

TRANSAM

NOBODY DOES IT BETTER!


Send to Transam Components Ltd., 12 Chapel Street, London NW1

I am interested in the TUSCAN Z80 based single board computer with S100 expansion and enclose a S.A.E. for further details.

Name _____

Address _____


Telephone _____

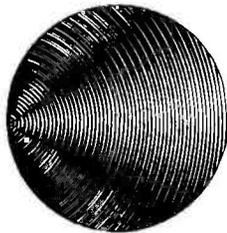


B.K. ELECTRONICS

A SOUND CHOICE

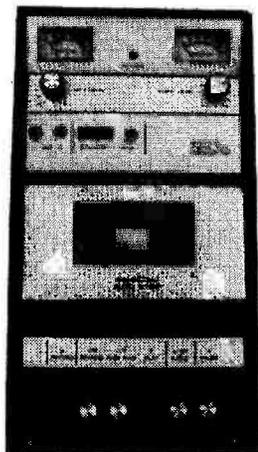★ PROMPT DELIVERY ★ PRICES INCLUDE V.A.T. ★ AMPLE STOCKS
A PERSONAL SERVICE FROM A SMALL EXPANDING COMPANY




STEREO CASSETTE TAPE DECK ASSEMBLY. Comprising of a top panel assembly and tape mechanism coupled to a record/play back printed board assembly. For horizontal installation into cabinet or console of own choice. Brand new, ready built and tested. **Features:** Pause control, auto stop, 3 digit tape counter, illuminated twin VU meters with individual level controls, twin mic, input sockets, AC erase system, LED record indicator. (Separate power amplifier required.) **Input Sensitivity:** 6 MV (with level control set at max). **Input Impedance:** 47 kOhms. **Output Level:** To both left and right hand channels 150 MV. **Output Impedance:** < 10k. **Signal to noise ratio:** 45 dB nominal. **Power Supply Requirements:** 12V AC at 300M/A. **Connections:** All connections to the unit are via a wander lead terminated with a nine pin plug (socket provided). **Dimensions:** Top panel — 11½in x 6½in. Mechanism fits through a cut out 5½in x 10½in. Clearance required under top panel 2¼in. Supplied complete with circuit diagram etc. **Price £30.50** plus £2.50 postage and packing.

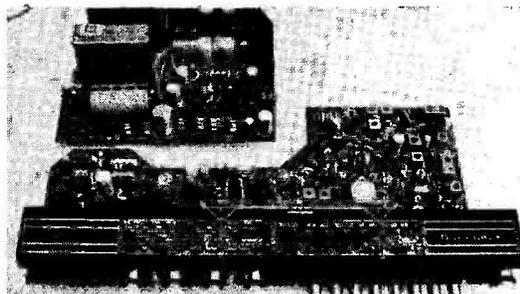

GEC AM/FM STEREO TUNER AMPLIFIER CHASSIS. Originally designed for installation into a music centre. Supplied as two separate built and tested units which are easily wired together. **Note:** Circuit diagram and interconnecting wiring diagrams supplied. **Rotary Controls:** Tuning, on/off volume, balance, treble, bass. **Push-button controls:** Mono, Tape, Disc., AFC, FM (VHF), LW, MW, SW. **Power Output:** 7 watts RMS per channel, at better than 2% THD into 8 ohms. 10 watts speech and music. **Frequency Response:** 60Hz-20kHz within ±3dB.


Tape Sensitivity: Output — typically 150 mV. Input — 300 mV for rated output. **Disc Sensitivity:** 100mV (ceramic cartridge). **Radio:** FM (VHF), 87.5MHz — 108MHz. Long wave 145kHz — 108kHz. Medium wave 520kHz — 1620kHz. Short wave 5.8MHz — 16MHz. **Size:** Tuner — 2¼in x 15in x 7½ in approx. Power amplifier — 2in x 7½in x 4½in approx. 240V AC operation. Supplied complete with fuses, knobs and pushbuttons, and LED stereo beacon indicator. **Price £21.50** plus £2.50 postage and packing.

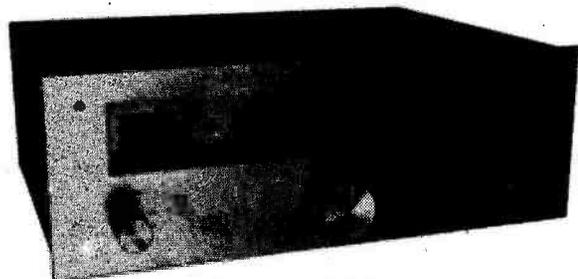

SCOTT AM/FM STEREO TUNER MODEL 516. This Scott tuner is one of the top American makes and is offered at a very realistic price. **Features:** ★ FM tuning range 87.5 to 108 MZ ★ AM tuning range 535 to 1605 kHz ★ Usable FM sensitivity 6.2dBf 2.2µV ★ 300 ohm & 75 ohm Aerial inputs for FM ★ Signal strength tuning meter ★ Stereo beacon indicator ★ Ferrite aerial for AM ★ Mute switch. **Size:** Height 5in, Width 14½in, Depth 12in. Silver front panel. Black body. Modern stacking format. **Price £40.50** plus £2.50 postage and packing.

PIEZO ELECTRIC TWEETERS — MOTOROLA

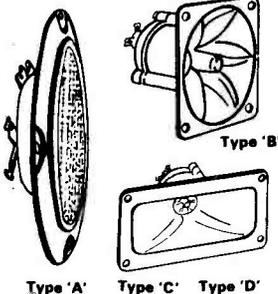Join the Piezo revolution: The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series).




Type 'A' 3in round with removable wire mesh. Ideal for bookshelf hi-fi speakers. **Price £3.80 each.**

Type 'B' 3½in super horn. For general purpose speakers disco and PA systems, etc. **Price £4.75.**

Type 'C' 2in x 5in wide dispersion horn. For hi-fi systems and quality disco etc. **Price £6.20 each.**


Type 'D' 2in x 6in wide dispersion horn. Frequency response extending down to mid-range (2000 c/s) suitable for hi-fi systems and quality disco. **Price £9 each.**

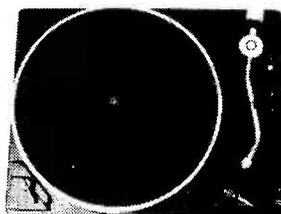Post and Packing, all types, 15p each (or SAE for Piezo leaflets).



JVC TURNTABLE. JVC Turntable supplied complete with an Audio Technica AT10 stereo magnetic cartridge. ★ 'S' shaped tone arm. ★ Belt driven. ★ Full size 12in platter. ★ Precision calibrated counterbalance weight (0.3 grms.) ★ Anti-skate (bias) device. Nylon thread weight. ★ Damped cueing lever. ★ 240V AC operation, (50Hz). ★ Cut-out template supplied. **Size** — 12¼in x 15¼in (approx). **Price £29** plus £2.50 postage and packing.

DE-SOLDERING PUMP

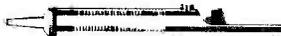

This de-soldering pump made to a very exacting specification is ideal for the removal of small components from printed circuit boards, etc. Comes complete with spare PTFE tip. **£5.30** post free.

B.S.R. P163 BELT-DRIVEN TURNTABLE

This famous B.S.R. turntable is ideal for both disco and hi-fi use where a more rugged unit is required.

- ★ 'S' shaped tone arm
- ★ Belt driven
- ★ Slide-in cartridge carrier
- ★ Calibrated styli pressure gauge
- ★ Calibrated anti-skate device
- ★ Damped cueing lever
- ★ 240v. 50Hz AC operation

Size approx. 11¼" x 13¼" **£22.00** + £2.50 P/P. Suitable magnetic cartridge type TTC/J2203.

Price £4 post free. (Also available separately)

LOUDSPEAKER

High quality full range 8" loudspeaker. 10 watts RMS. 80HM. Rolled surround with aluminium centre dome.

Price £3.75 each + 75p Postage and Packing.



B.K. ELECTRONICS

37 Whitehouse Meadows, Eastwood, Leigh-on-Sea, Essex SS9 5TY

★ SAE for current lists. ★ Official orders welcome. ★ All prices include VAT. ★ Mail order only. ★ All items packed (where applicable) in special energy absorbing PU foam. Callers welcome by prior appointment, please phone 0702-527572.

EDDY CURRENTS

A.S.Lipson brings you the life story of Eddy Current, last known to be circulating in the region of discs and transformers.

The branch of physics now known as electromagnetism can be said to have been born in 1819. It was in that year that Professor Oersted of the University of Copenhagen discovered that electricity and magnetism are related — that a current flowing in a conductor produces a magnetic field in the close neighbourhood of the conductor. Later, around the 1830s, the reverse effect — that an electrical current can be produced in a conductor by a changing magnetic field — was discovered simultaneously, and quite independently, by Faraday in England and Henry in America.

Both of these effects are used, for example, in the transformer; an alternating current in a coil creates a changing magnetic field, which, in turn, is used to produce an EMF (and hence a current, should a circuit be connected) in another coil. However, rather less people are aware of another, very closely related, and extremely interesting, effect — the phenomenon of eddy currents . . .

What's In A Name

Magnetic fields are not usually quite as selective as we would like them to be. A changing magnetic field will not only produce an EMF in any coils in its vicinity, but it will also produce EMFs, and hence currents, in any conductor around — even any old lumps of metal that may be just hanging about. These currents don't actually go anywhere — they just circulate round and round within the conductors, like eddy currents in a liquid. Hence the name — eddy currents.

Since eddy currents are the result of induced EMFs in conductors and because resistances within conductors can be very small, the currents can on occasion be quite sizeable, and so the effects produced by them can be very significant. In fact, eddy currents are far more than just a scientific curiosity. Depending on exactly where they are, and what they are doing, they can be either a curse or a blessing. However you view them, though, they are an interesting phenomenon, and can produce some fascinating effects, not all of which are totally useless!

Counting Your Blessings . . .

One of the more striking experiments on eddy currents is shown in Fig. 1a. A horseshoe magnet is suspended on a thread, above an aluminium disc which is itself free to turn about its centre. If the magnet is now spun round, the aluminium disc starts to rotate with it (although it never quite catches up with the magnet). Similarly, if you spin the aluminium disc, the magnet above it also starts to turn. This obviously cannot be due to ordinary magnetic effects — aluminium is non-magnetic, and if you try to pick up the disc with the magnet, you will find that you are unable to. It is apparent that something funny is going on. (No, air currents aren't dragging the disc round when the magnet rotates — you can put a sheet of paper between the two, and the effect still works!)

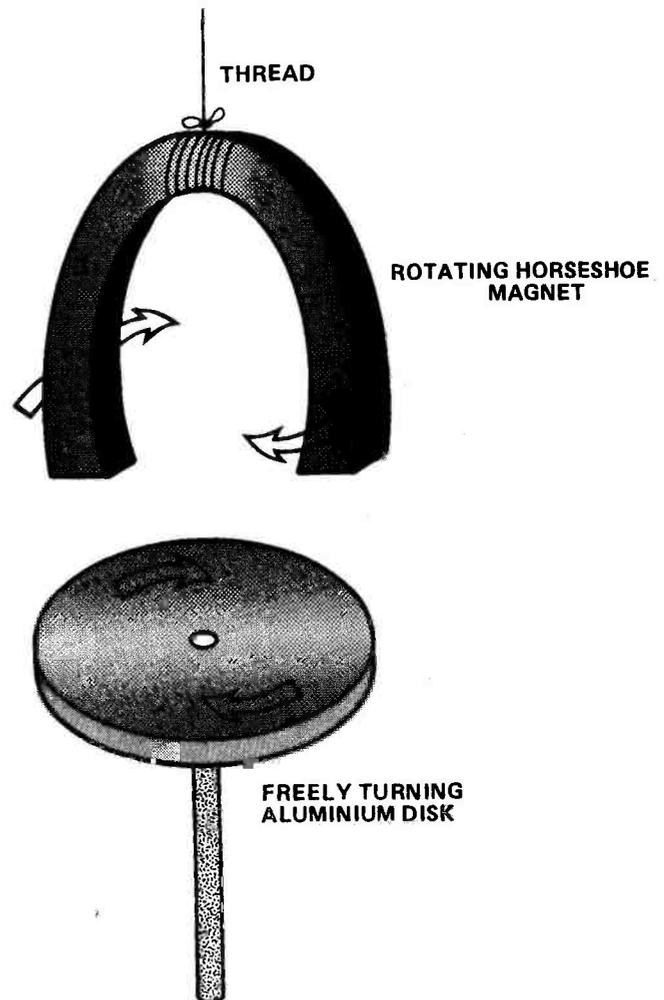


Fig.1a. The rotating magnet induces eddy currents in the aluminium disc .

Field Study

The relative movement between the magnet and disc is inducing eddy currents in the aluminium. These, in turn, create other magnetic fields, and it is these that cause the magnet and disc to move together — the magnetic field of the magnet interacting with the fields caused by the eddy currents (sounds a bit like pulling yourself up by your bootstraps, but it's correct) An interesting follow-up to this experiment is to replace the disc with one cut as shown in Fig. 1b. The slots tend to get in the way of the eddy currents and prevent them from flowing, so such a disc is not dragged round so easily by a magnet (which is another way of showing that air currents don't do the work — the slots shouldn't make any difference to them). ➔

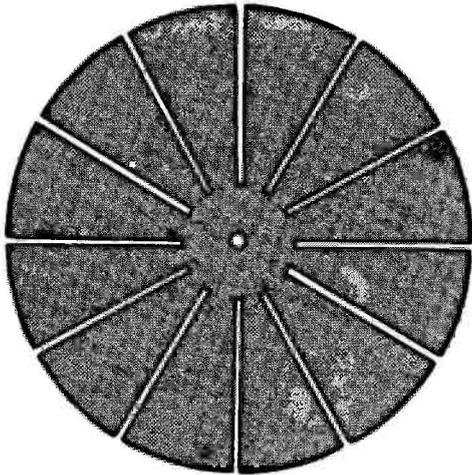


Fig.1b. If the disc in Fig.1a is replaced with one cut like this, the drag effect is greatly reduced, or even stopped.

Interestingly enough, this apparently insignificant effect actually has some practical application. It is used, for instance, in the normal car speedometer! The rotation of the wheels is transmitted, by various means, to a magnet, which itself rotates, with a speed proportional to that of the wheels. This rotating magnet induces eddy currents in an aluminium disc, (or its equivalent) and tries to drag it round. However, a spring is used to hold the disc, so it is unable to turn very far. The faster the car goes, though, the faster the magnet rotates, the greater the eddy currents, and the further round the aluminium disc is pulled. By attaching a little red or orange needle to this disc and seeing how far this needle rotates, we can work out how far the disc has turned, and hence the speed of rotation of the magnet. Thus, we find out the speed of the car. Yes, I wish I'd thought of it first, too.

Cutting Your Losses

Besides being useful, though, eddy currents can also be very annoying. They could justly be called the transformer designer's nightmare. The transformer is, basically, two coils, close together. However, in the middle there's a dirty great lump of metal (the core) and it doesn't sit there doing nothing, with all those magnetic fields about.

No prizes for guessing what happens. It might not seem that eddy currents in the transformer core would be much of a problem, but they are, for two main reasons. Firstly, the eddy currents mean a loss of power in the transformer and hence reduced efficiency. It stands to reason that if power is being used to drive currents around in the core, then that much less power is going to be available for use from the secondary coil. The second problem is no less serious, especially in large-scale transformers. The power being wasted in the core, driving eddy currents round, quite naturally ends up as heat, and consequently transformers are liable to get very hot. Indeed, large transformers, such as those on the national grid, may be oil-cooled, to prevent overheating.

It is obvious that, in transformers at least, eddy currents are not wanted. So what can be done about them? Well, if you've ever taken an old transformer apart for the wire, or even just out of curiosity (naughty, naughty), you will probably have noticed that the core is not just one solid lump; it is built up of flat metal laminations. This is not because they make the cores out of flattened baked bean tins. The laminations are separated by varnish or paper or some other insulator and this greatly increases the internal resistance of the cores, reducing eddy currents. Hence, both the loss of power and the unwanted heating are reduced.

Even the heating effect of eddy currents can be put to use, though. It is used in the production of pure crystalline samples of conductors like metals or semiconductors — germanium, for example. The impure sample of the material is passed, in a crucible, through a coil, which has passing through it a high frequency alternating current. The magnetic field produced by this current induces eddy currents in the specimen and the heating effect is great enough to melt it! As the sample passes through the coil, the molten zone within it is carried to one end (Fig. 2). Impurities within the sample are accumulated in the molten zone and hence get taken to one end of the specimen. This end is later removed. What is left is a very pure, crystalline sample of the substance. So eddy currents can be surprisingly useful!

Footnote

There is one final point which must be at least mentioned in connection with eddy currents. This is the induction motor, an indispensable servant of industry. It depends for its operation on eddy currents... full explanation of that, though, is another story altogether.

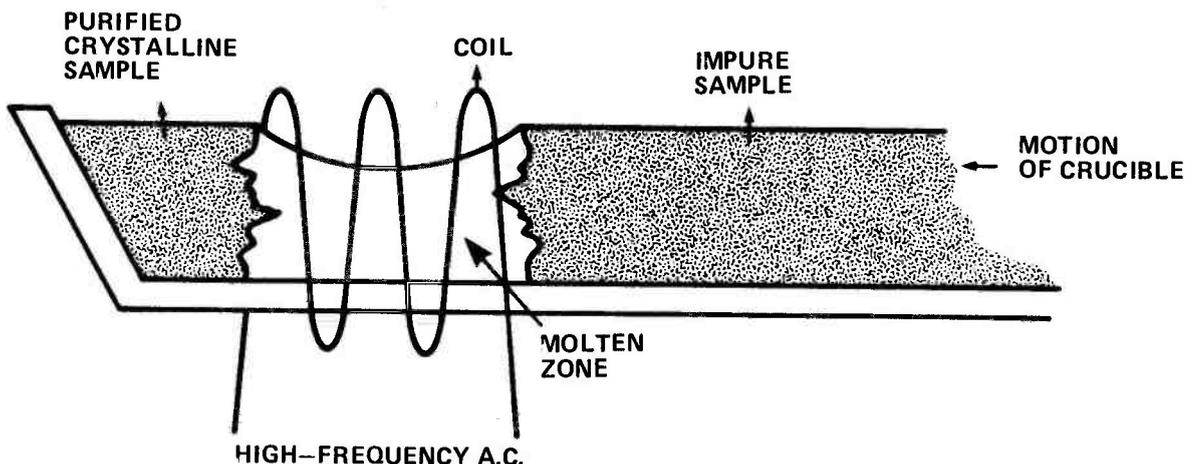


Fig.2. The heating effect of high frequency AC can be put to good use in semiconductor material manufacture.

Bind it

It's so easy and tidy with the Easibind binder to file your copies away. Each binder is designed to hold approximately twelve issues and is attractively bound and blocked with the ELECTRONICS TODAY INTERNATIONAL logo.

Price U.K. £3.95 including postage, packing and V.A.T., overseas orders add 30p. Why not place your order now and send the completed coupon with remittance to:-

EASIBIND LTD., 4 UXBRIDGE STREET, LONDON W8 7SZ. Tel: 01-727 0686

Please allow 3/4 weeks for fulfillment of order.

it's easy with EASIBIND

Easibind Ltd, 4 Uxbridge St., London, W8 7SZ.

Nat. Giro No. 5157552.

Order Form

ELECTRONICS TODAY INTERNATIONAL

I enclose p.o./cheque value

for binders

Years required

BLOCK LETTERS PLEASE

Name

Address

Date

Registration No. 307469



Mail Order Protection Scheme

If you order goods from mail order advertisers in this magazine and pay by post in advance of delivery, this publication *Electronics Today International* will consider you for compensation if the advertiser should become insolvent or bankrupt, provided

1. You have not received the goods or had your money returned; and
2. You write to the publisher of this publication *Electronics Today International* explaining the position not earlier than 28 days from the day you sent your order and not later than 2 months from that day.

Please do not wait until the last moment to inform us. When you write, we will tell you how to make your claim and what evidence of payment is required.

We guarantee to meet claims from readers made in accordance with the above procedure as soon as possible after the advertiser has been declared bankrupt or insolvent to a limit of £1800 per annum for any one advertiser so affected and up to £5400 p.a. in respect of all insolvent advertisers. Claims may be paid for higher amounts, or when the above procedure has not been complied with, at the discretion of this publication *Electronics Today International*; but we do not guarantee to do so in view of the need to set some limit to this commitment and to learn quickly of readers' difficulties.

This guarantee covers only advance payment sent in *direct* response to an advertisement in this magazine (not, for example, payments made in response to catalogues, etc., received as a result of answering such advertisements). Classified advertisements are excluded.

Make sure of your Heathkit catalogue... write now.



Keep up to date with the world's finest electronic kits—with the Heathkit catalogue.

48 product packed pages contain photographs and specifications of the widest possible range of kits. Everything from doorbells to digital clocks, multimeters to microcomputers.

Heathkit make it easy to build, easy on your pocket, and, as with 13 million Heathkit builders over 34 years, your success is guaranteed.

Make sure of your copy of the Heathkit catalogue. Send the coupon today, plus 25p in stamps and beat the demand.

To: Heath Electronics (U.K.) Limited, Dept (ET 8), Bristol Road, Gloucester, GL2 6EE.

Please send me a copy of the Heathkit catalogue.

I enclose 25p in stamps.

Name _____

Address _____

Soldering Iron offer FREE N.B. If you are already on the Heathkit mailing list you will automatically receive a copy of the Heathkit catalogue without having to use this coupon. When you receive your catalogue you will get details of this free offer.

HEATHKIT

Casio's new SUPERCALC! TRIO HAMEG



CASIO FX-8100

46 scientific functions, clock calendar, alarm, countdown alarm, interval alarm timer, hourly chimes, 1/100 sec stopwatch

ONE YEAR BATTERY LIFE (approx. used continuously). LC Display, 8 digit mantissa plus 2 digit exponent. 5 level parenthesis, full access memory. Trigs, logs, hyperbolics, standard deviations, co-ordinate conversions, sexagesimal to decimal conversions, fractions, percentage, cube roots, sign change, register exchange, Pi entry etc. **CLOCK** displays hours, minutes, seconds, am/pm and day. **CALENDAR** pre-programmed to 1999; day, date, month and year, 24 hour **ALARM**, hourly chimes. Countdown **ALARM TIMER**, interval (repeater), **ALARM TIMER** or 1/100 second **STOPWATCH** measuring net, lap and first and second place times to 10 hours. 6.6x70x129mm (¼x2¾x5½ inches). Leatherette wallet. RRP £27.95

Only £24.45

Mini SUPERCALC! FX-7100

1 YEAR BATTERIES 30 scientific functions. As FX-8100 but 8 digits, without hyperbolics, fractions and calendar. Only 1 countdown alarm timer (repeat) or stopwatch function. Alarm and hourly chimes. 3/16x2¼x3½". Leatherette wallet (£27.95) R.R.P.

£24.45



NEW SCIENTIFICS

Casio FX-100
LCD, 10 digits, 44 scientific functions as FX-8100 above but with 6 levels (1), FIX, SCI, NORM, ENG, RND and RAN in lieu of hyperbolics, % 7,500 hours battery ¼x3x5½ inches
£15.45
(£17.95 R.R.P.)

FXB1 £12.45 FX-330 £16.45 FX510 £19.45 FX-2600 £19.45
FX-3200 £21.45 FX501P £62.45 FX502P £72.45 FA-1 £19.45

TERMS OF BUSINESS: Please note all Casio items PRICE INCLUDES VAT P&P and insurance. Please send cheques or P.O.s or quote Barclaycard or Access No. to: **B. BAMBER ELECTRONICS, 24 HOUR PHONE SERVICE. (0353) 860185** Callers welcome Tues., Sat. 9.00 am-5.30 pm.



C-80 Calculator Watch

(Finger-touch keyboard) Hours, minutes, seconds, am/pm, day, date, month, auto calendar pre-programmed to 2009. Professional 24 hour stopwatch, net, lap, 1st & 2nd place to 1/100 sec. Dual time: 8 digit calculator. Nightlight. Water resistant. Glass. Black resin case/strap. R.R.P. (£29.95)

Only £24.45

LADIES CASIO WATCHES from £12.45

Send 20p for full details of all Casio watches and calculators

830S-41B Alarm Chronograph

S/S enclosed. Mineral glass. Water resistant. 3 YEAR BATTERY. Hours, minutes, seconds, date, am/pm, or hours, minutes, alpha day, date am/pm. 24 hour alarm, hourly chimes. Stopwatch from 1.10 second to 12 1/2 hours, net lap and 1st and 2nd place. Nightlight.

Only £24.45

R.R.P. (£27.95)



TRIO CS1566 20MHz triggered sweep oscilloscope £339.00
TRIO CS1562A 10MHz triggered sweep oscilloscope £299.00
HAMEG oscilloscope HM307 LP3 triggering bandwidth d.c. to 10MHz component tester. Timebase 0.2US - 0.2 S/CM £149.00
HAMEG H236 switchable probe for HM307 £11.00

DACTRON FX402 13.8 d.c. 3 amp continuous 4 amp max. fully stabilised power supply with overload protection £19.95

DACTRON PMS800 13.8 d.c. 5 amp continuous £39.50

DIN PANEL METERS DM7510 0-5 amps DM 715 0-150 volts DIN 730 0-300 volts DM 750 0-500 volts 72 x 72mm range £8.00

EAGLE D07 paging microphone. Impedance 600 ohm or 50 Kohms. sensitivity 2.25mV at 50 Kohms. Frequency response 300-9000Hz. Desk or wall mounted. £14.95 + VAT

EAGLE MULTIMETER EMS50 50,000 OPV DC volts: 0-1200 volts, AC volts: 0-1200 volts. DC current 0-6A, resistance 0-10 meg ohms £19.95 + vat

DRAPER SUPER CHROME ¼ in sq drive socket sets. 38 piece 9AF, hexagon, 3 AF, bi-sq sockets. 11mm hexagon sockets. 9 B.A. hexagon sockets and 6 accessories. £12.75 + VAT

SPIRALUX metric nut spinner sets. Contains 8 nut spinners. 4, 4.5, 5, 5.5, 6, 7, 8, 9, 10mm. Packaged in plastic wallet £7.35 + VAT

WELLER TCP3 Irms. 24 volt series, 3 wire power units. For application requiring earthed tip. Also PUS3 power units TCP3 £13.84 + VAT PUS3 £24.12 + VAT

WELLER INSTANT HEAT GUNS model no 81000 £13.21 + VAT

WELLER CORDLESS model no WC100 £25.47 + VAT

SUPA servical switch cleaner £0.72 + VAT

MARYPLASS storage boxes. SP2 combination draw pack (contains 1x600, 2x201, 5x10) interlocking storage boxes. Per Pack £4.40 + VAT

DRYX DE-SOLDER TOOLS model 583A, desoldering pump with built-in safety guard. Price £8.90 + VAT

IC TEST CLIPS, clip over IC while still soldered to pcb or in socket. Gold plated pins. Ideal for experiments or service engineers. 28 pin DIL £1.75, 40 pin DIL £2. Or save by buying one of each for £3.50

IC AUDIO AMP PCB output 2 watts into 3 ohm speaker. 12 volt DC supply. Size approx 5¼"x1¼"x1" high, with integral heatsink, complete with circuits £2 each + VAT

IC TEST CLIPS, clip over IC while still soldered to pcb or in socket. Gold plated pins. Ideal for experiments or service engineers. 28 pin DIL £1.75, 40 pin DIL £2. Or save by buying one of each for £3.50

IC AUDIO AMP PCB output 2 watts into 3 ohm speaker. 12 volt DC supply. Size approx 5¼"x1¼"x1" high, with integral heatsink, complete with circuits £2 each + VAT

IC TEST CLIPS, clip over IC while still soldered to pcb or in socket. Gold plated pins. Ideal for experiments or service engineers. 28 pin DIL £1.75, 40 pin DIL £2. Or save by buying one of each for £3.50

IC AUDIO AMP PCB output 2 watts into 3 ohm speaker. 12 volt DC supply. Size approx 5¼"x1¼"x1" high, with integral heatsink, complete with circuits £2 each + VAT

IC TEST CLIPS, clip over IC while still soldered to pcb or in socket. Gold plated pins. Ideal for experiments or service engineers. 28 pin DIL £1.75, 40 pin DIL £2. Or save by buying one of each for £3.50

IC AUDIO AMP PCB output 2 watts into 3 ohm speaker. 12 volt DC supply. Size approx 5¼"x1¼"x1" high, with integral heatsink, complete with circuits £2 each + VAT



B. BAMBER ELECTRONICS

DEPT: ETI, 5 STATION ROAD LITTLEPORT CAMBS CB6 10E



The finest amplification kits from Crimson Elektrik

CPR 1 - THE ADVANCED PRE-AMPLIFIER. The best pre-amplifier in the U.K. The superiority of the CPR 1 is probably in the disc stage. The overload margin is a superb 40dB, this together with the high slew rate ensures clean top, even with high output cartridges tracking heavily modulated records. Common-mode distortion is eliminated by an unusual design. R.I.A.A. is accurate to 1dB; signal to noise ratio is 70dB relative to 3.5mV; distortion <0.05% at 30dB overload 20kHz.

Following the stage us the flat gain/balance stage to bring tape, tuner, etc. up to power amp. Signal to noise ratio 86dB; slew-rate 3V/US; T.H.D. 20Hz - 20kHz <0.08% at any level. F.E.T. muting. No controls are fitted. There is no provision for tone controls. CPR 1 size is 138 x 80 x 20mm. Supply to be ± 15 volts.

MC 1 - PRE-AMPLIFIER. Suitable for nearly all moving-coil cartridges. Send for details.

X02: X03 - ACTIVE CROSSOVERS. X02 - two way, X03 - three way. Slope 24dB/octave. Crossover points set to order within 10%.

REG 1 - POWER SUPPLY. The regulator module, REG 1 provides 15.0-15v to power the CPR 1 and MC 1. It can be used with any of our power amp supplies or our small transformer TR 6. The power amp kit will accommodate it.

** NEW ISSUE 5 **


POWER AMPLIFIERS. Our new issue 5 power amplifier modules have automatic shut down that will not allow serious overloads for more than 0.1 sec - thus vastly increasing reliability at elevated temperatures. Other improvements to the circuitry have improved the subjective qualities which keeps CRIMSON even further ahead of the field.

POWER SUPPLIES. We produce suitable power supplies which use our superb TOROIDAL transformers only 50mm high with a 120-240 primary and single bolt fixing (includes capacitors/bridge rectifier).

PRE-AMP KIT

This includes all metalwork, pots, knobs, etc. to make a complete pre-amp with the CPR 1 (S) module if required.

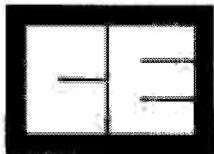All prices shown are U.K. only and include V.A.T. and post. C.O.D. 90p extra £100 limit. Export is no problem, please write for specific quote. Send large S.A.E. or 3 International Reply Coupons for detailed information.



Crimson Elektrik

1a STAMFORD STREET, LEICESTER LE1 6NL.
Tel. (0533) 553508

POWER AMPLIFIER KIT. The kit includes all metalwork, heatsinks and hardware to house any two of our amp modules plus a power supply. It is contemporarily styled and its quality is consistent with that of our other products. Comprehensive instructions and full back-up services enable a novice to build it with confidence in a few hours.



POWER AMPLIFIER MODULES
CE 608 £21.00
CE 1004 £24.50
CE 1008 £27.50
CE 1704 £35.00
CE 1708 £35.00

HEATSINKS

Light duty, 50mm, 2 C/W £1.70

Medium power, 100mm, 1.4 C/W £2.70

Disco/group, 150mm, 1.1 C/W £3.50

Fan mounted on two drilled 100mm heatsinks 2x4 C/W 65 max. when used with two 170W modules £38.00


THERMAL CUT-OFF, 70C £1.90

TOROIDAL POWER SUPPLIES

CP51 for 2x CE 608 or CE 1004 £18.50

CP53 for 2x CE 1004 or 1/2 x CE 1008 £23.50

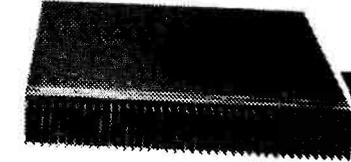CP56 for 1/2 CE 1704 or 1/2 CE 1708 £30.00



POWER AMP KIT £38.80

PRE-AMP KIT £39.80

PRE-AMPS

These are available in two versions - one uses standard components, and the other (the S) uses MO resistors where necessary and tantalum capacitors

CPR 1 £34.00

MC 1 £28.00

CPR 1S £44.50

MC 1S £37.80

ACTIVE CROSSOVER

X02 £19.00

X03 £28.35

POWER SUPPLY

REG1 £9.30 TR6 £2.50

BRIDGE DRIVER, BD1

Obtain up to 340W using, 2x 170W amps and this module BD1 £7.25

U.K. - Please allow up to 21 days for delivery

*Write for free literature or send 50p for application/users' manual.

ETI BOOK SERVICE

How to order: Make cheques payable to ETI Book Service. Payment in sterling only please. Orders should be sent to: ETI Book Service, Modmags Sales Office, 145 Charing Cross Road, London WC2. All prices include P&P. Prices may be subject to change without notice.

BEGINNERS

Beginners Guide to Electronics Squires £3.45
Beginners Guide to Transistors Reddihough £3.45
Electronics Self Taught Ashe £4.60
Beginners Guide to Integrated Circuits Sinclair £3.45
Understanding Electronic Circuits Sinclair £4.20
Understanding Electronic Components Sinclair £4.20
Beginners Guide to Radio King £3.45
Beginners Guide to Audio Sinclair £3.45

COOKBOOKS

TV Typewriters Cookbook £7.75
CMOS Cookbook £8.20
Active Filters £11.30
IC Timer Cookbook £7.50
IC Op-Amp Cookbook £10.00
Video Cookbook £7.00
TTL Cookbook £7.55
The Basic Cook £4.00 inc. p/p
IC Converter Cookbook £9.50

APPLICATIONS

Fire and Theft Security Systems B. Weis £2.15
How To Build Electronic Kits Capel £2.35
110 Electronic Alarm Projects R. M. Marston £3.95
110 Semiconductor Projects for the Home Constructor R. M. Marston £3.95
110 Integrated Circuit Projects for the Home Constructor R. M. Marston £3.95
110 Thyristor Projects Using SCRs R. M. Marston £3.95
110 Wave Form Generator Projects R. M. Marston £3.95

COMPUTING & MICROPROCESSORS

What is a Microprocessor? 2 cassette tapes plus a 72-page book £12.00
Beginners Guide to Computers and Microprocessors with Projects C. Adams £8.05
Basic Computer Games Ahl £6.05
Basic for Home Computers A self-teaching guide. B. Albrecht £6.15
Illustrating Basic D. Alcock £3.00
Intro to Microprocessors Aspinall £6.55
Z-80 Microcomputer Handbook W. Barden £7.75
How to Program Microcomputers W. Barden £7.25
Introduction to Microcomputers and Microprocessors A. Barna £8.60
Microprocessors in Instruments and Control R. J. Bibbero £13.00
Basic Basic J. S. Coan £7.80
Advanced Basic J. S. Coan £7.30
Getting Acquainted with Microprocessors L. Frenzel £7.25
Beginners Guide to Microprocessors C. M. Gilmore £4.90
Beginners Guide to Home Computers Grossworth £4.50
Beginning Basic R. E. Gosling £4.75
Microprocessor Programming for Computer Hobbyists N. Graham £7.15
Miniprocessors from Calculators to Computers Heiserman £5.00
Microcomputers, Microprocessors, Hardware, Software and Applications J. L. Hilburn £17.40
Basic Programming J. G. Kemeny £7.25
Microprocessor Systems Design E. Klingman £17.00
Intro to Microprocessors Leventhal £17.00
Microprocessors — Technology, Architecture & Applications D. R. McGlynn £10.55
Interactive Computing with Basic Mono £3.65
Basic with Style P. Nagin £4.25
Software Design for Microcomputers Ogdin £7.20
Microcomputer Design Ogdin £7.25
Microcomputer Base Design Peatman £5.70
Hands on Basic with a PET Peckham £9.55
Basic — A hands on method Peckham £6.95
6800 Software Gourmet Guide and Cookbook Scelbi £8.90
8080 Software Gourmet Guide and Cookbook £8.90
The 8080A Bugbook: Microcomputer Interfacing & Programming P. H. Rony £8.35
8080/8085 Software Design Titus £7.60
57 Practical Programs & Games in Basic Tracton £6.65
Microcomputer Primer M. Waite £6.50
Your Own Compaq Waite £1.60
Microprocessor/Microprogramming Handbook Ward £6.20

LOGIC

Logic Design Projects Using Standard ICs J. Wakerly £7.15
Practical Digital Design Using ICs J. Greenfield £16.00
Designing With TTL Integrated Circuits Texas Instruments £9.35
How To Use IC Circuit Logic Elements J. Streater £3.80
110 COSMOS Digital IC Projects for the Home Constructor R. M. Marston £3.95
Understanding CMOS Integrated Circuits R. Melen £4.15
Digital Electronic Circuits and Systems R. M. Morris £3.65
MOS Digital ICs G. Flynn £5.25

TEST INSTRUMENTS

The Oscilloscope In Use Sinclair £3.10
Working with the Oscilloscope A. Saunders £4.25
Servicing with the Oscilloscope A. King £6.65
Radio Television and Audio Test Instruments King £7.00

OP-AMPS

Applications of Operational Amplifiers Graeme (Burr Brown) £8.45
110 Operational Amplifier Projects for the Home Constructor R. M. Marston £3.95
Designing With Operational Amplifiers Burr Brown £18.35
Operational Amplifiers Design and Applications G. Tobery (Burr Brown) £7.55
Op-Amp Circuit Design & Applications J. Carr £4.15

COMMUNICATIONS

Communication Systems Intro To Signals & Noise B. Carlson £7.65
Digital Signal Processing Theory & Applications L. R. Rabiner £24.40
Electronic Communication Systems G. Kennedy £8.75
Frequency Synthesis. Theory & Design Mannasewitsch £25.00
Principles of Communication Systems H. Taub £8.40

THEORY

Introduction to Digital Filtering Bogner £10.60
Transistor Circuit Design Texas Instruments £9.75
Modern Electronic Maths Clifford £6.95
Foundations of Wireless Electronics M. G. Scroggie £5.25

REFERENCE

Electronic Engineers Reference Book (Ed. 4) L. W. Turner £34.50
Electronic Components M. A. Colwell £2.70
Electronic Diagrams M. A. Colwell £2.70
International Transistor Selector T. D. Towers New update £10.20
International FET Selector T. D. Towers £4.35
International Op-Amp Linear IC Selector Towers £7.65
Radio Valve and Semiconductor Data A. M. Bell £3.60
Radio, TV and Audio Technical Reference Amos £30.40

MISCELLANEOUS

Electronic Fault Diagnosis Sinclair £3.55
Integrated Electronics J. Milman £8.20
Practical Solid State DC Supplies T. D. Towers £6.40
Practical Triac/SCR Projects for the Experimenter R. Fox £2.35
Printed Circuit Assembly Hughes & Colwell £2.70

Fallen behind recent advances?

Just starting out?

Need a decent reference book?

ETI Book Service provides an easy way of getting your hands on the right title.

CHROMASONIC electronics

56 FORTIS GREEN ROAD, MUSWELL HILL, LONDON N10 3HN
 TELEPHONE 01-883 3705, 01-883 2289

YOUR SOUNDEST CONNECTION IN THE WORLD OF COMPONENTS

PETS

2001-8N (8K RAM)

£399

2001-16N (16K RAM) **£499**

2001-32N (32K RAM) **£599**

ALL WITH NEW KEYBOARD
 AND GREEN SCREEN

PERIPHERALS

Service & Assistance available.

Interfaces available are:

X-Y Plotters, Analogues to Digital Converter external cassette deck suitable 16 channel interfaces. Bi-directional interfaces etc.



FOR ALL PETS **£55**

MEMORY

D. RAMS	£	p
4027	2.75	
4050 (350NS)	2.35	
4060 (300NS)	2.39	
4116	4.35	

S. RAMS	£	p
2102A	1.09	
2102A2	1.09	
2112A	2.25	
21L02	.98	
2114-4045	2.95	
4035	1.07	
4044-5257	6.93	

BULK PURCHASE	£	p
8.2114	22.50	
8.4116	29.95	
8.21L02	7.00	

BULK PURCHASE	£	p
16.2114	39.95	
16.21L02	13.00	
32.21L02	25.00	
64.21L02	45.00	

UK101

£199 IN KIT FORM


£249 READY BUILT & TESTED

£275 COMPLETE IN CASE

- No extras required
- ★ Free sampler tape
- ★ Full Querty keyboard
- ★ 8K basic
- ★ Ram expandable to 8K on board (4K inc)
- ★ Kansas City tape interface
- ★ NEW MONITOR ALLOWS FULL EDITING & CURSOR CONTROL

8x2114 **£22.50**

ASSEMBLER
 EDITOR
 TAPE
£14.95

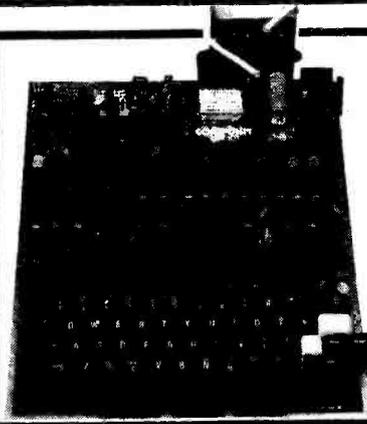

EPROMS

2708	4.95
2716 (5v)	13.95
2532	39.95

ROMS

2513 (UC)	5.95
2513 (LC)	5.95

CPUS

6502	9.50
8080	4.75
9900	25.95
6800	5.90
Z80	8.95

LATEST STOP PRESS AND PRICE LIST

Send sae or phone for up-to-date **PRICES** of all our range of items stocked

CASES

Available for
 U.K. 101, Superboard
 Nascom,
 Appx. DIM. 17" x 15"
 435 x 384 mm

PRICE £24.50

P. packing £1.50.

TAPES

Unique stackable tape
 storage unit. Interlocking
 drawers.
 45 drawers each containing 2
 C12 tapes

10 drawers **£9.50**
 5 drawers **£5.25**
 Single drawer **£1.10**

MEMORY EXPANSION KIT

Suitable for UK101. Superboard
 expansion using 2114's each board
 has 16K ram capacity kit contains:

- ★ On board power supply
- ★ 4K Eprom expansion
- ★ Fully buffered for easy expansion via 40 pin socket
- ★ 8K kit **£99.95**
- ★ 16K kit **£139.90**

BUFFERS

81LS95	1.25
81LS96	1.25
81LS97	1.25
81LS98	1.25
SN74365	.52
SN74366	.52
SN74367	.52
SN74368	.52
8T26	1.75
8T28	1.75
8T95	1.57
8T96	1.57
8T97	1.50
8T98	1.57

PRINTERS

TX-80 £395

EPSON TX-80 £395

Dot-matrix printer with Pet
 graphics Interface: Cen-
 tronics parallel, options: PET,
 Apple and serial.



BAUD RATE GENS


MC14411	8.75
MM5307	8.75

WARTS

AY-5-1013	3.45
AY-3-1015	3.98
MM5503	4.75
6011	3.55



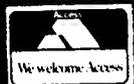Please add VAT 15% to all prices. Postage on computers, printers and cassette decks charged at cost, all other items P&P 30p. Place your order using your Access or Barclaycard (Mm) tel order (5). Trade and export enquiries welcome.



VIDEO TODAY



Richard Dean, editor of Television and Home Video, takes a look at the history and future of Home Video.

In the beginning there was television — Baird and all that. After many years of either broadcasting live or filming off a 405-line monochrome TV monitor, television output was mostly a 'here now, gone later' medium, until Ampex came up with the Quadruplex format in 1956—still the prime system in broadcasting today. It used 2 in tape travelling at 15 IPS, 'chopped' by four rotating video heads, producing segmented picture tracks vertical to the tape motion.

From these humble beginnings we can wind swiftly on to the start of 'Home Video', scanning only briefly the rise and fall of the BBC's VERA (Vision Electronic Recording Apparatus) and the Nottingham Electronic Company's Telcan. Both of these British developments used fixed-head scanning as opposed to today's helical scan. Ironically Japan's Toshiba corporation and the German tape giant BASF have resurrected this technique in prototype — nowadays called LVR or Longitudinal Video Recording, (scheduled for production next year as a home video recorder).

The early seventies saw Sony's U-Matic format using $\frac{3}{4}$ in tape encased in a plastic cassette. Although this was originally intended for the home market, various factors — the main one being cost — came into play, aiming the format toward the industrial sector, in which it holds an ubiquitous position today.

The first real domestic recorder came in 1972 with Dutch electrical giant Phillips' (helical scan) N1500 video cassette recorder. The machine contained the domestically essential timer — albeit a crude one — and an off-air tuner. For the first time viewers could programme a machine to record in their absence. The format was called VCR — logical at the time but destined to cause confusion as the term gained popularity as a general description for home video recorders.

And Then There Were Six

VCR uses co-axially mounted spools containing $\frac{1}{2}$ in tape and, as with all video recorders at the time, guard bands separated video tracks to prevent crosstalk. In 1977 Phillips'



pulled off another first — at least in Phase Alternation Line (PAL) territory — by introducing a longer playing version of VCR called VCR-LP (N1700 series machines). This increased the capacity of its coaxial cassettes from one hour on a VCR format machine to two and a half hours using a technique called "tilted azimuth recording".

Phillips technique, patented by a Japanese professor in 1959, has the two heads in the recorder's head drum tilted 14° relative to each other, or $\pm 7^\circ$ from true azimuth.

This eliminated the need for guard bands with an attendant increase in tape capacity. All subsequent helical scan formats were to adopt this technique.

In 1978, PAL versions of Sony's Betamax appeared, followed swiftly by JVC's VHS (Video Home System) — attempts at a common Japanese format had by this time been abandoned. The final format was Grundig's own variation of the Phillips' VCR (which it had been manufacturing under licence), the SVR (Super Video Recorder). Betamax and VHS impressed the trade with their compact, co-planar cassettes and longer playing time (three and a half hours Betamax, three hours VHS).

Grundig's SVR used the original Phillips VCR/VCR-LP cassette, but used a more critical tape formation to cope with a 4 hour capacity. The format didn't catch on in the face of a ruthless marketing onslaught by VHS, and to a lesser extent Betamax and Phillips.


Grundig was already suffering from the saturation of its home market by TVs, and decided to combine with Phillips to combat the Japanese threat. Recently the fruits of their association, the Video 2000 (eight hours a side) co-planar cassette format has been launched onto the PAL market. During this combat Phillips' original VCR format has ironically remained fairly intact — for the moment — because of its high initial penetration of education and institutional markets.

And It Came To Pass . . .

But where does this leave us today? Certainly VHS has scored a major success in the world market, nowhere more so than in Britain where there are as many as 75% of users with VHS machines. Worldwide JVC seems to have persuaded a greatest number of manufacturers toward VHS.

But Sony remain hopeful. The recently launched, feature-packed, C7 is evidence of the company's determination to win support from upgrading, as well as from first time buyers.

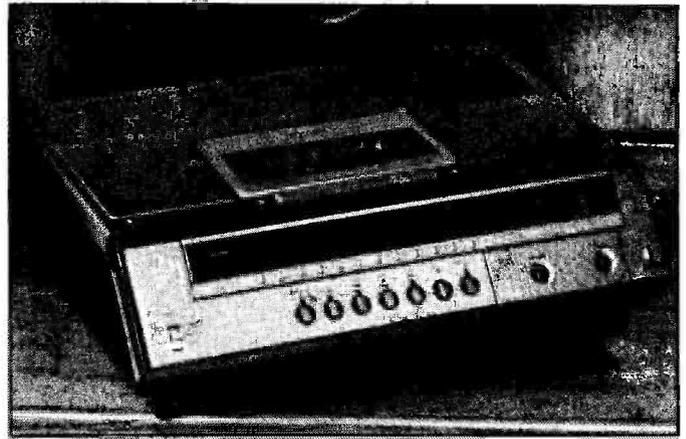If you've been watching the video scene so far you may conclude that the last thing a manufacturer should contemplate is halving the scanned tape width. Well Phillips has managed to get away with it — borrowing a technique called Dynamic Track following (DTF) from the industrial sector.



The Sanyo VTC 5500P

DTF involves mounting the video heads on a piezo-electric crystal base and recording four guide tones — which are combined with the video information — over four video tracks in turn.

On replay, beat frequencies generated by either head mistracking, causes a microprocessor to output 'up' or 'down' pulses to the respective head bases. If both heads are hopelessly out, the transport servo is adjusted. In this way tracking accuracy — essential to such a compact system of storage — is guaranteed. Phillips' claim that contemporary replay quality will be maintained. So far, nobody is prepared to refute this claim.

Instant Replay

However, the future format war will be — as it is at this moment — fought on features.

Here Phillips Video

2000 is in a good position, as fast wind with vision, slow motion and still frame are theoretically easy to perform with DTF.

Initial models from Phillips (VR-2020) and Grundig (V2 x 4) are not equipped with any of these features. Many





The JVC HR 7700E with full remote control.

observers see these first Video 2000 products as "too little, too late".

The Sony C7 was launched to the sound of £1 million worth of promotional trumpets; as the 'King Of The Format Jungle'. Its main claim to fame is the machine's feature repertoire, in particular the "cue and review" facility. This allows you to flip through a tape in forward (review) or rewind (cue), still in vision. The speed at which you can do this is inevitably reduced by the required intimacy of heads to tape — although Betamax format remains laced during winding modes — and on the C7 this varies from about x4 to x15 play speed, according to the diameter of the spool driving the tape.

Panasonic have used a new compact design to achieve lacing during winding modes, with the added elegance of a servo control on cue or review maintaining a constant x9 play speed.

The Cold War

There's more to come from the VHS faction, however. Not only is Dolby B noises reduction being introduced to the format's soundtrack, but Panasonic's NV-7000 incorporates back space, or pre-roll, editing. This directly counters Sony's improvements in editing performance and indeed substantially surpasses it. While Sony has tightened up the gap tolerance in pause mode, Panasonic borrows a technique used on professional gear. When 'record' mode is selected, the tape is wound back 1½ seconds in real time. When pause is cancelled, the transport moves the tape forward at play speed in the usual way, but the servo 'listens' to the sync. track on the edge of the tape and gets it in step with the incoming pulse chain. So when the original cue point is reached and recording begins, the picture instability is not just reduced, it is eliminated. This has far-reaching

implications for home movie makers and straightforward perfectionists alike.

In addition, VHS has a 4 hour tape waiting in the wings to combat Phillip's 4 hour capacity. The Betamax format uses thinner tape anyway, and so does not have the capability to pack more tape in without reducing tape thickness to a precariously low dimension.

Strictly Off The Record


The first video disc to arrive on the scene is almost certain to be Phillips VLP. But following in its tracks will be JVC's VHD/AHD (Video High Density/Audio High Density) and RCA's Selectavision.

Phillips' system uses a miniature laser inside the player to scan video sync. and reference signals encoded on a 10 in transport disc. Light bouncing off the disc's protectively coated surface reaches a photo-cell moving with the laser transmitter under servo control from the centre of the disc. Thirty minutes of information can be stored on each side using a constant rotational speed. But with development Phillips claims it could increase this to one hour per side. The main obstacle to the system is the critical conditions under which the disc must be pressed. However, its advantages are considerable. A frame or chapter indexing facility makes it the trick-play fanatic's dream, and, more importantly renders it ideal for educational and data retrieval applications. Another advantage is the discs ability to withstand misuse. You can put thumbmarks on it, pour beer on it, or even scratch it — up to a point — because the information lies beneath a transparent coating, such misuse never reaches the information. Minor scratches are, quite simply, so massive compared to the data that the photo cell ignores them.

JVC's VHD/AHD system poses a formidable threat to VLP. Thorn-EMI has just announced its backing for this format, which uses a grooveless capacitive disc in a protective sleeve. Thorn has a massive chunk of the rental and retail market in consumer electronics, and its EMI arm will become a ready-made software provider. Thorn-EMI chose VHD/AHD — which offers one hour per side with indexing and trick-play — on the basis of the player's ease of servicing and the disc's ease of pressing. Discs can be manufactured on conventional presses, after mastering on a lathe which, 'cuts' a photo sensitised glass plate. Phillips has meanwhile begun to equip a special VLP pressing plant in Blackburn, Lancashire.

So summarising on what is increasingly appearing to be a massive video game, there are some exciting moves to be made in the future. The stakes are indisputably high; and the outcome will reverberate through most of the electronics industry for many years to come.

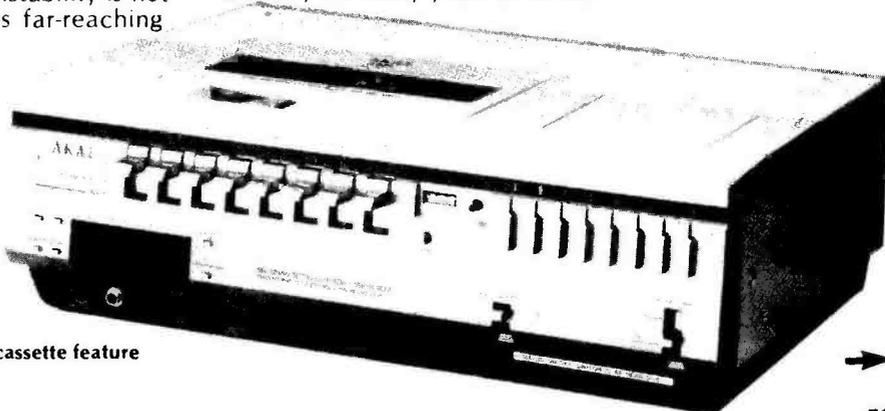Right: The Akai VS9800 VHS deluxe home video system



Left: The Grundig 2x4 Video 2000 with front loading cassette feature

	GRUNDIG VIDEO 2 X 4 V2000	PANASONIC NV 7000 VHS	PHILLIPS VR 2020 V2000	FERGUSON VIDEOSTAR 3V23 and JVC HR7700 FERGUSON and VIDEOSTAR 3V23	AKAI VS 9800 VHS	HITA VT 50 V
Typical Price:	£690 guide price	£650 approx.		Under £700 (available in Autumn 1980)		£539
Maximum Recording Time:	2 x 4 hours	3 hour	2 x 4 (flip Over)	3 hours	3 hours	3 Hours
Timer:	10 day/ 4 programme	14 day/ 8 programme	16 day/ 5 programme	14 day/ 8 programme	8 day	10 day
Remote Control:	Optional extra	12 mode supplied	Full function Optional Extra	Full function supplied	6 function included	Pause control only. Optional
Still Frame:		Yes		Yes and Frame Advance	Yes	Yes
Variable Speed Playback:		Double and half speed		Normal and double speed with sound	Double or slow motion	Single frame advance
Review Feature:				Yes		
Audio Dub:		Yes		Yes	Yes	Yes
Automatic Tuner:	Yes		Automatic Search Tuner	Yes		
Portable Recorder Available:				3V24	VP7100	
Camera:	FAC 1800	Socket included	V100 or V200	3V20	VC 30	VKC 500
Extra Features:	Dynamic Track Following Automatic Programme finding Dynamic Noise Suppression	Dolby Noise Reduction	'Go To' function Automatic Rewind Dynamic Noise Suppression	Dolby Noise Reduction 1 Hour Battery Back-Up in Power Failure Edit Start Control		Free Cassette

CHI NO ER S	JVC HR 3660EK VHS	SONY C7 BETA	SANYO VTC 5500P BETA	SHARP VC 6300H VHS	HITACHI 5500E VHS	MITSUBISHI HS 300G VHS
	£582	£649	£500	£650	£599	£650
	3 Hours	3½ hours	3¼ hours	3 hours	3 hours	4 hours
	8 Day	14 day/ 4 programme	7 day/ 5 programme	7 day/ 7 programme	7 day/ 5 programme	7 day/ 6 programme
	Playback only. Supplied	12 mode supplied	9 Function Optional Extra	Wired supplied		Wireless or wired (optional)
	Yes	Yes		Yes and Frame Advance	Yes and Frame advance	Yes and single frame advance
	Double and Slow motion	5 alternative speeds		6 speed		half and sevenfold
		Cue and Review				
	Yes	Yes	Yes	Yes	Yes	Yes
		Yes			Automatic Channel Lock (during recording)	
	HR4100	SL 3000P				
	GL4100	HVC 2000P	VCC 545P	XC-35H	VK C500E or VK C750E	
		Picture Search		Automatic programme Locater	Automatic Programme Search Battery back-up for short power failures	Low power consumption

VIDEO VIEWPOINT:

Tina Boylan examines the Video Recorder Marketplace.

The long awaited video disc, although perched firmly on the horizon of home video, will take a considerable time to descend to the plane of the general consumer as a viable mass market product. Even then the existing tape system will hold an unchallengable position in home entertainment, taking over where the cine-camera leaves off. At present manufacturers are improving facilities for home-movie making with high quality cameras, improved edit facilities, portable recorders and better sound reproduction — already available as peripherals to the higher quality machines. Even the newest and most advanced of the recorders, with 'the sky's the limit' facilities, are becoming something of an enigma. It seems that almost every month a new system is launched, which claims new and better features: An eternal game of manufacturers' leapfrog.



To Buy or Not to Buy...

However, the resultant cost of research and development, coupled with high manufacturing costs, (precision playing an important part in production) are inevitably relayed to the customer, despite the considerable drop in price of video equipment generally. This can, to a certain degree, leave manufacturers with marketing difficulties. In the final analysis, selling high price luxury items during an economic recession is tough going. Many machines are tentatively priced at 'around £700', which to Joe Public represents a considerable investment with so many other, and more economically justifiable, items monopolising his income. He needs considerable persuasion to embark upon this type of financial undertaking, and even having decided that he wants or needs a video recorder, finding a way around that price tag is going to hinder him further.

With a mere 1% penetration of the TV market in Britain, (225,000 recorders in 20 million TV-owning homes) today's video company can see all too clearly a large market waiting to be tapped, if it can discover how. Recently a number of them have done just that, focusing their attention on an already well established method — TV rentals.

Easy Access

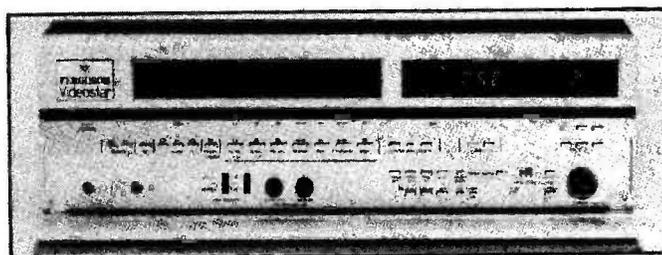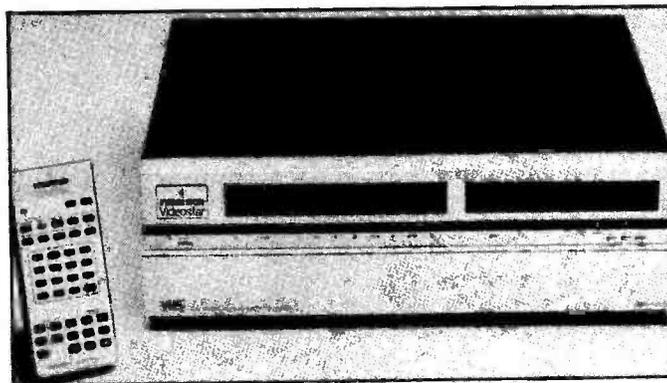The TV rental shop came into its own during the 1960's, as the price of traditional black and white television was coming down, and the more advanced colour models were arriving on the market. Its presence heralded the age of



The new Ferguson Videostar 3V23 due for launch in the Autumn

widespread TV ownership, as it enabled the average household to afford the most advanced and reliable sets available, without the subsequent financial responsibility for repairs and servicing.

Since then, chains of rental shops have appeared and prospered considerably, with most high streets in England boasting at least one well known name in television rentals — and it is here that the video industry has found an outlet.


Many of the large manufacturers are either directly affiliated to chain rental stores, (Ferguson to Thorn-EMI, through DER, Radio Rentals, Multi-Broadcast, Rumbelows and Rediffusion) or have made agreements with them — for example JVC has found outlets through Thorn-EMI. Sony too will now have rental access through its agreement with Telefusion, (a wise move) in order to market its innovative new creation, the C7.

Video For Everyone

These new developments through the rental industry, will not only allow the already interested consumer to obtain a video recorder at a reasonable price, but will also draw the attention of the remainder of the public to their existence. A prominent shop window display of video recorders is now on view to anyone walking down the high street who cares to glance toward the brightly lit interior of the, already familiar, rental shop.

Here, it seems, is the basis for a growth in home video, comparable perhaps to hi-fi during the past decade. Indeed it could well become an integral part of home entertainment, with a range of equipment as varied as can be found in stereo systems today, its impact will certainly effect the leisure industry far into the future.

The Mitsubishi MS 300.

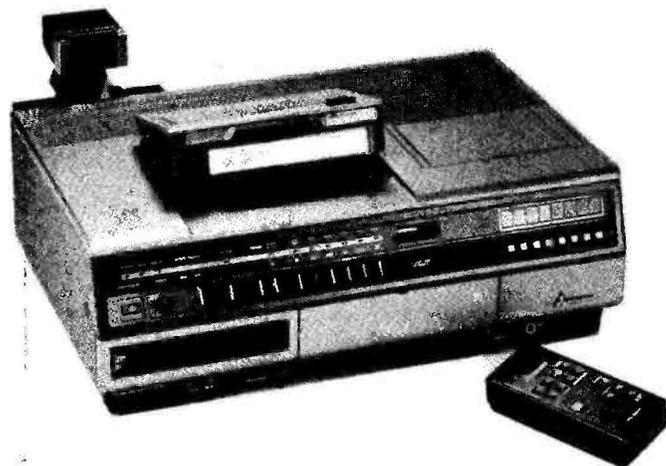

ETI

1

GENTS QUARTZ LCD. 5-function. Hours, minutes, secs, month, date, backlight.
ONLY £4.95

2

GENTS -QUARTZ LCD. SAME AS 1 - Alternative style.
ONLY £4.95

3

QUARTZ LCD Slim Chronograph. 11-function. Hours, mins, secs, 6 digit-month, date, day of week, 1/100 sec stopwatch, split and lap modes, backlight.
ONLY £7.95



4

QUARTZ LCD ALARM. 6 digit, hours, mins, secs, day, date. 24-hour alarm with on/off indicator.
ONLY £8.95



5

QUARTZ LCD Alarm/Chronograph. 22 functions. Hours, mins, secs, day, date, month, 1/10 sec stopwatch, split and lap modes, 12 and 24 hour modes, 24 hour alarm.
ONLY £12.95

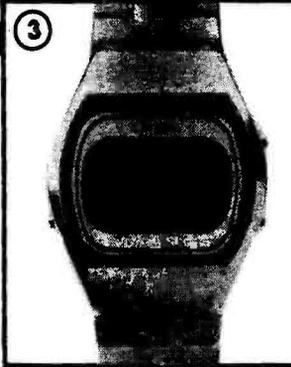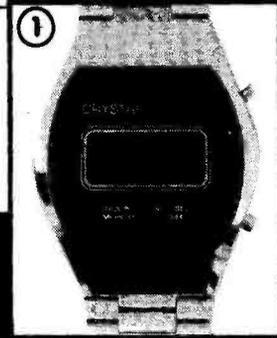We don't believe you can find better value combined with quality, than these - our special introductory prices. Compare the savings we offer and order now.




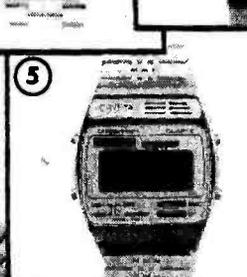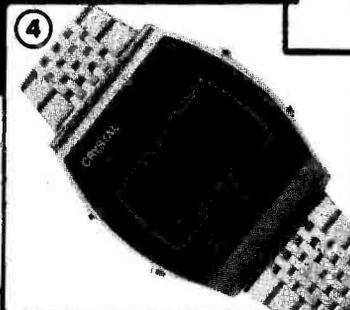14 CREDIT CARD CALCULATOR. Very slim with standard 4 functions plus memory, percentage and square root. Complete with a mock leather wallet with credit card pocket.
ONLY £6.95






13 BELTIME 29F. Alarm/Chrono. Advanced and accurate, this watch has 8 time functions, 4 alarm functions and 17 chronograph functions. Complete with backlight and stainless steel bracelet.
ONLY £19.95

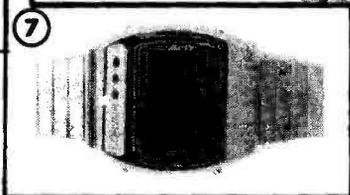
12 GENTS ANALOGUE QUARTZ. Conventional display, accuracy normally associated with digital watches. Automatic calendar, elegant and robust.
ONLY £19.95



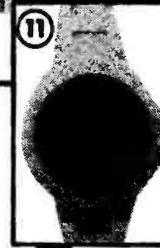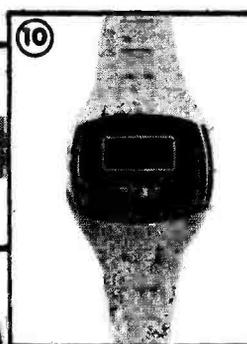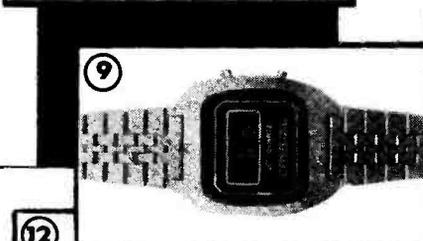11 LADIES QUARTZ LCD SAME AS 10. Alternative "Round" shape. Available in gold or silver colour.
ONLY £8.95



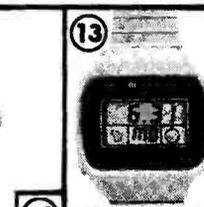LADIES QUARTZ LCD. SAME FUNCTIONS AS 8. - Alternative style. Available with black or white face.
ONLY £5.95



LADIES QUARTZ LCD. 5 functions. Dress Style. Functions same as 1. Available in gold or silver colour.
ONLY £8.95



Send stamped addressed envelope for Colour Brochure of 120 other bargains.

KEELMOOR LTD

78 CASTLE STREET, MELBOURNE, DERBY, DE7 1DY

Please send me items (list numbers)

I enclose cheques/POs for £

NAME

ADDRESS

Please add 35p P/P per item ET13

OLIVETTI PRINTER & KEYBOARD type Te 300
with PUNCH & READER. Upper case ASCII with V24 Interface. 240
volt operation.
£125 each

**709 DIL 14 PIN
OPERATIONAL AMPLIFIERS**
at **8p each**
100 off 25% discount

**CONVERT THIS UNIT TO A
SUPER BATTERY
CHARGER**

Attractive green ministry quality case with removable top & bottom plates — heavy duty power switches—high powered resistors to control current — good quality centre mounted Amp Meter — strip of wing nut terminals on front panel which can be used for connecting leads.
ALL THIS FOR £3.50. P&P £2.
FOUR UNITS FOR £12. Carriage £5.

**INFRA RED IMAGE
CONVERTER type 9606 (CV 144)**

1 3/4" diameter. Requires single low current 3KV to 6KV supply.
Individually boxed. With data

£12.50 each P&P 75p Infra Red Lamps also advertised

MINIATURE KEYBOARD
Push contacts, marked 0-9 and A-F and 3 optional function keys. **£1.75 ea. P&P 65p**

BLUE THERMAL PAPER
430ft. roll, 8 1/2" wide
£2 per roll. P&P £1.75

STEPPING MOTORS
200 steps — 20 oz./in. torque.
12/24 volt input, 4 wire.
£12 each P&P £1.50

STEPPING MOTORS
200 steps. 20 oz./in. torque.
120 volt operation, 3 wire.
£4 each P&P £1.50

STEPPING MOTORS
North American Philips. 5 volt
3 3 amp operation, 2 wire. PPS
0-200 revs per min. 0-250 used.
Tested.
£16 each P&P £1.50

STEPPING MOTORS
6/12 position with additional where the rotor is coils. Device can be used as a tacho. Diagram supplied. Will actually work on 5 volts. 12/24 recommended.
£1.50 each P&P 75p or 5 for £5 p&p £1.50

RXs 770R used **£120**
730/10 used **£85**
Limited quantity only

**MUST CLEAR
POLARAD SPECTRUM
ANALYSER**
5" Display. These are supplied with STU 2 plug-in. 1 to 45 GHZ.
£85 each

LARGE QUANTITY OF PHOTOMULTIPLIERS
all with information. British approx. 2" window **£2 ea.** British approx. 5" window **£3.50 ea.** American approx. 2" window **£4 ea.** Special American version by RCA **£6 ea.**
P&P all photomultipliers **£1.50 ea.**

BC172	5p	MC4001	15p	TIS92	10p	BC337	5p
BZ7884V7	10p	MC4012	15p	TIS93	10p	BC327	5p
BZ78813V	10p	MC4020	25p	2N3704	8p	BC251	5p
2N3006	5p	74C20	25p	2N5447	5p	BC171A	5p
1N4305	5p	74C08	25p	2N5449	5p	BF160	5p
BZ79C12	10p	74C10	20p	2N3053	15p	4013	30p
BC212E	5p	MC4049	35p				
SN76550	5p						
IC 7451	10p						

TRANSISTOR INVERTER
115V AC, 1.7Amp Input. Switching is at 20KHZ. Output windings from Pot Core. Can be rewound to suit own purpose or unit can be broken for host of components. Circuit supplied.
£1.25 each P&P £2

KEYBOARD PAD
Size 3 x 2 1/2 x 2" high with 12 Alma Reed Switches. Blue keys marked in green 0-9 and a star with one blank.
£4 each P&P £1
or **5 for £15 P&P £2**

REGULATORS — at **45p each.** MC7805, 7812, 7815, 7912, 7915
MC1498L 70p
15 pin DIL Socket **10p.** 14 pin DIL Socket **8p**
LED type TIL 209 Red with holder **10p each**
SLOTTED OPTO SWITCH supplied with data — normally over **£2** OUR PRICE **75p each**
ROCKER SWITCHES 2 pole c/o — **15p each**
Spring Action TERMINALS — normally over **30p ea.** OUR PRICE **15p each**
TOROIDAL TRANSFORMER 0.12V-240V Input 1.3V-0-13.5V rated 8VA Output **£1.70 each.** P&P 75p
Sub-min TRANSFORMER 0.12V-240V Input 1.2V-0-12V rated 4VA Output **75p each P&P 50p.**
L.E.D.s
Standard White 12p. Standard Yellow 15p. Small White 8p.

RXs 770R Mk. II
940
24V INVERTOR VERSION
SPECIAL GOVT. QUALITY

**VERY FEW
OF THESE
PRICE ON
APPLICATION**

We still have a large quantity of
**TEST GEAR, OSCILLOSCOPES,
SIGNAL GENERATORS ETC.,
and they are priced to move.**
Callers welcome or write or Better Still PHONE for details

**MAGNETOS
NEW BOXED**
Originally for 14 cyl-gipsy
Very adaptable
£4.75 each

**TANTALUM BEAD
CAPACITORS.** 4.7uf
25V. 10 off **£1;** 100 off
£7.50.
TEXAS Low Profile 40 pin
IC Sockets **45p each.**
SMALL TRANSFORMER. 240V Input.
Output 2 windings 12V &
24V 1 amp. **£2 each.**

SO SIMPLE — SO SAFE
Fit a push button CIRCUIT
BREAKER. Small compact.
3 ratings 0.8, 1.8 &
10AMP. State which one
when ordering. **75p each.**

AMP METER 2 1/2" dia
Scaled 0-60. Basic 75mV
FSD. Complete with external
60Amp Shunt. **£2.50**
each; P&P £1.50.

DIODES
All new full spec. devices IN3063; BAX 13,
IN4148; IS44. 100 off **£1.50** — 1,000 off
£10.

Miniature **MOTORS** 12V with geared wheel (8 teeth 3 1/8" dia)
Size 1 1/2 x 1/2" dia New **30p ea.**
MOTOR 12V DC with pulley and integral semiconductor. Speed
Control. New **£1 ea.**
LEDEX ROTARY SOLENOIDS. 115V DC. No switch assembly
15p ea.
DIAMOND H CONTROLS ROTARY SWITCH. Single pole
10-way Printed Circuit Mount. New **10p ea.**
DELAY LINE. 50 nanoseconds. 3 connections ground-in-out. Size 2
x 7.16 x 1/8". New **25p ea.**
PULSE TRANSFORMER. Sub min. Size 1/2 x 5/16 x 1/4"
Secondary centre tapped. New **20p ea.**
MOTOR by Inland Motor Corp. DC High Torque. Reversible
Usable torque at 5V. Max voltage 24V **£2.50 ea.** P&P £2
REMO TV TYPE MULTIPLIER. Two high voltage outputs and
focus. **£1 each.**
DON'T TAKE CHANCES. Use the proper EHT CABLE **10p per
metre** or **£7.50 per 100 metres/drum.** P&P 1/2"
MOTOR by Eastern Air Devices Inc. 125V reversible with toothed
shaft (10 teeth 1/2" dia). Size 2 1/4 x 2 1/4" dia **75p ea.** P&P £1
PHOTOGRAPHIC LAMPS. Pearl 230V 500 watt. Screw cap
75p ea. Box of 12 **£5.50.** P&P £1.50
MYSTERY IC PACK. Some 40 pin — good mixture — all new
devices. **25 ICs for £1.** P&P 50p. You find out what they are and
we'll bill you the information from you
VACUUM PUMPS — TRAPS, ETC. Send for list
DECOUPLING CAPACITORS. 0.05mfd 10V. 0.01mfd. 0.1mfd
50V. 0.047mfd 250V. All values 100 for **£1.**
E.H.T. CAPACITORS 500pF BKV 20p each.
10-WAY MULTI COLOUR RIBBON CABLE. New. **40p per
metre.** 10 metres for **£2.**
GEC UHF 4-button tuner **£1.50 each.**
CENTAUR 115V FANS 4" x 4 x 1 1/2" **£4.50 ea.**
EX-USED equipment tested. **60p each.**
POTTER & BRUMFIELD TIMER RELAY. 115V AC. Heavy
duty. 7 pole c. s. with 2 second delay. Charge R & C for different
timing. **50p each.**
SPEAKERS 2". 50 ohm 0.2W. New **40p each.**
RAPID DISCHARGE capacitors 8mfd 4kV **£5 each.** P&P £2
BIG INCH Motor. 110V AC 3 rpm 50 cycle. Very small. **50p
each.**
CONTACTORS. Heavy Duty 24V DC 5 make **£1 each.**
GEC UHF VHF 6 button tuner **£2 each.**
DIGITAL 24-HOUR CLOCK with built in alarm as used in Braun
Digital clocks. Silent running. Large illuminated numerals. AC
mains. Size 6" x 2 1/4 x 2 1/4". **ONLY £3.75 each.**
931A PHOTO MULTIPLIER in stainless steel container with
window and built-in resistor network. **£2 each.** P&P £1
SLIVER CONTROL 500W. Log. Single track. Complete with
switch. Length 3". **25p each.**
RAICO 250V 18A THERMOSTATS with Control knobs
calibrated 50-200 degrees C **£2.50 each.**
SOLID STATE UHF TUNERS. 30 pcs **£1 each.**
BRAND REX blue wire wraps. 30 metres for **£1.**
5in **SOLID RUBBER RINGS** 1 1/2" dia. rubber. Keep the kids safe

(dog) happy 4 for **£1.** P&P £1.50
TRANSFORMERS
AUTO 240V input 115V 1Amp output **£1.25 each.** P&P £1.25
240V input. Soc. 6V 1.86A 8kw. Size 2 1/2 x 2 x 2" Good
quality. **£1.50 ea.** P&P £1
240V input Rac. 12V 0.92A. Size 2 1/2 x 2 x 2 1/2". Good quality.
£1.50 ea. P&P £1
240V input 12V 100MA. Size 60 x 40 x 42mm. **50p each.**
240V input. Soc. 12-0-12V 50MA. Size 53 x 45 x 40mm. **£1
ea.**
115V input. Soc. 5V 250MA. Size 1 1/2 x 1 1/2 x 1 1/4" 2 for
50p.
SEMICONDUCTORS 1N4005 — 5p; 1N4003 — 3p.
3BC147, BC148B, BC151, BC158, BC237, BF197, OA90,
OA81 BA154 BA243
At 25p each: TIP31, TIP41A, 2N5966 AF139, 2TX341
BY127 10p; BF181 20p; BD239 49p; BD241 40p; MA343AT
40p; BD228 50p; BD233 & BD234 Comp Par 25W — 80p per
pr. at 50p each.
REGULATOR TBA625 B to 20V in — 5V out 100MA TO5 Con
50p each BF256C 20p. TV AMPLIFIER TBA 120 20p each.
Integrated Circuits

VARIACS EX Equipment Good condition 8 Amps **£25 ea.**
20 AMPS **£35 ea.**
Some 3 phase available. Please enquire

CRYSTALS
19 KHZ FLAT METAL CASE — **50p each.**
10 MHZ B7G **50p each.**

LOUD HAILERS
Transistorised hand held. No leads — standard internal
batteries supplied. Howl switch.
£20 each. P&P £2

TRANSFORMERS Standard Mains input
Secondary outputs
6KV 0.125A **£15 ea.**
3440V 0.68A with matching 40H Choke **£30 the pair**
3KV 50MA **£8 ea.** 4 Volts 750 Amps **£10 ea.**
18KV 30MA **£80.**
22 5KV 110MA **£50 ea.** 5KV 300MA **£15**
60KV 0.127A **£150.** 12KV 30MA **£20.**
MULTI PURPOSE MAINS TRANSFORMER 4 windings each
winding 0.10-110 125 at 48A **£15 ea.**
425V 50HZ 2 Wire input Output 8 5KV 2 55KVA. Could be
run on 240V at 1/2 rating **£15 ea.**
STEP DOWN ISOLATING TRANSFORMER Input 220-250V
50HZ Output 115V 1.8kVA BRAND NEW. These are very
conservatively rated! **£20 ea.**
CAPACITORS
2mfd 5KV **£4 ea.** 0.5 mfd 10KV **£4 ea.**
0.5 mfd 5KV **£4 ea.** 8 mfd 5 KV **£4 ea.**
CARRIAGE on these units will be charged at cost

INFRA RED QUARTZ LAMPS. 2 x 200 Watts. Size 1.3 1/2" x
1 1/2" dia. **£1.50**
BRIDGE RECTIFIER. 2 Amp **50p ea.**
PHOTODIODE DETECTOR 1" dia leads. **25p ea.**
AMPHENOL. 17 way brass contact edge connectors. 0.1
spacing. **15p ea.**
17 C standard **MAINS LEAD.** Multi-bend vertical flat pins centre
offset! **50p ea.**
FANS. 115V 1.3 Watts. Size 1 1/2 x 1 1/2 x 1 1/2". BRAND NEW
£4.50 ea. Second hand **£2.50 ea.**

7453	5p	74H74	12p	75325	£1
7451	5p	74H51	7p	SN15862	4p
7402	12p	74538	10p	MC4028	69p
7476	20p	74502	12p	7417	14p
7495	35p	74154	70p	7441	40p
74127	12p	74C02	15p	74C98	50p
74C00	17p	74C04	15p	74C161	24p
		74C74	18p		

MOTOROLA DUAL in Line 6 pin Opto Coupler **30p each.** Gold
plate tester version **50p each**
EPROMS 2708 **£5.50 each.**
TELEPHONES 706 style black or grey **£5.50 each.** 746 style
black or grey **£7.50 each.** Older style black **£2.50 each.** P&P
£1.50 per telephone
Honeywell humidity controllers **50p each.**
THYRISTOR TIMER. Solid State. 15 secs adjustable (reset) in
plastic relay case. Standard 7-pin base. Series delay **50p each.**
MINIATURE PC MOUNT SLIDE SWITCH. Single pole 3-way
10p each.
VARIACS. 2 amp Standard 240 Volts **£10 each.** P&P £2
ELECTROSTATIC VOLTMETERS. 7.5KV **£8 each.** P&P £1.50
Other ranges available. Please enquire
TRIMMERS. Sub min 0.25 to 1.25pf to 4.5pf 7 to 45pf All
at **6p each.**
CROWN replacement MOTOR for IBM GOLFBALL TYPEWRITER
115V 50HZ 1350 rpm **£4.50 ea.** P&P £2
SMITHS encapsulated transistorised AUDIBLE WARNING
DEVICES 4V-12V. Can be driven from TTL **65p each.**

MINIMUM ORDER £3 VALUE OF GOODS. MINIMUM P&P £1 — where P&P not stated please use own discretion — excess refunded. CARRIAGE ALL UNITS
£5 P&P or CARRIAGE and VAT at 15% on total MUST BE ADDED TO ALL ORDERS.
CALLERS VERY WELCOME STRICTLY BETWEEN 9am-1pm and 2-5pm Monday to Saturday inc.
BARCLAYCARD (VISA) and ACCESS taken. Official orders welcome.

CHILTMELD LTD
NORWOOD ROAD, READING TELEPHONE NO. READING 669656
(2nd turning left past Reading Technical College in King's Road then first right — look on right for door with Spoked Wheel)

Superboard II 8k MICROSOFT BASIC 4k RAM

At these prices why waste time and money on unauthorised kit copies? Just a little more in price than Sinclair for a whole lot more and fully expandable!



READY BUILT £159.95

NOW ON SHOW IN THE SCIENCE MUSEUM

610 Expansion Board 8k RAM ONLY £159.95 + VAT

IP CD3P Minifloppy Disc, Cased, PSU, 2 copies Dos ONLY £289+VAT

Set of 4k RAM (Superboard users only) ONLY £28 + VAT

Plastic Case, Beige ONLY £26+VAT

Challenger IP-Metal Cased, Superboard, PSU modulator ONLY £208 +VAT


NEW 50Hz version - NO FLICKER

Super Print 800

80 COLUMN HIGH PERFORMANCE IMPACT PRINTER

The ideal companion for PET, APPLE, TSR80, Exidy, Superboard, Compukit, Ohio Challengers and most micro's

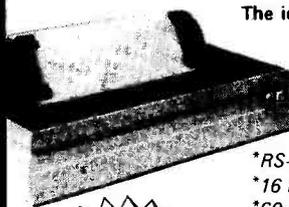Rugged metal enclosure makes it ideal for home computing, small business systems, data logging etc.



NEW

*RS-232, 20mA, IEEE 488 and Centronics I/O

*16 Baud Rates to 19,200

*60 Lines per minute - Bidirectional

*5 print densities 72,80,96,120 or 132 Chr/Line

*Self Test Switch *2k Buffer

*Tractor and Fast Paper Feed/Graphics

Model 800 MST ONLY £399 + VAT

Radofin Teletext Decoder

Get more out of your TV

ONLY £149.95 + VAT



Works on any TV (RF in/RF out), remote control unit, Teletext colours, CEEFAX and ORACLE via 6 preset tuner, enlarge facility, Time on, Time off facility, reveal button - for quiz games hold button.

ZT Driving Computer

ADD A NEW DIMENSION TO YOUR CAR WITH COST EFFECTIVE FUEL MANAGEMENT



*Miles per gallon - Instant *Miles per gallon - Average *Miles per hour - Instant *Miles per hour - Average *Gallons used since fillup *Miles to empty *Elapsed Time *Time to empty *Time on trip *Miles on trip

Accuracy: Time: ± 30 secs/month

Speed: ± 0.5 mph - Instant

± 0.005 mph - Average

Fuel Used: + 3%

Takes only about 2 hours to fit

ONLY £77.50 + VAT

Mighty Micro

BUY IN CONFIDENCE In the event that we are unable to deliver your goods within 7 days, we do not bank your remittance until such time we have the goods to despatch. If on receipt of your order the goods do not meet with your satisfaction, return within 7 days for full refund. All goods covered by manufacturers guarantee.

Please add VAT at 15%. Carriage extra, will advise at time of order. Official orders welcome. Product details on request. Trade and export enquiries welcome.

CALLERS - 33 CARDIFF ROAD, WATFORD, HERTS. Tel: (0923) 38923

MAIL ORDER - P.O. BOX 17, BASINGSTOKE, HANTS. Tel: (0256) 56417

Close to Watford Football Ground, Nearest Station B.R. Watford



TTL CMOS 74LS LEDS

LB ELECTRONICS

LINEAR RAMS EPROMS SURPLUS

TELEPHONE: UXBRIDGE 55399

PCB OFFERS

(1A) 100 bit shift register PCB, 115mm x 94mm containing 9x7491, 6x7496 and 1x7441. Terrific bargain 85p, p&p 30p.
(1B) Audio amp PCB (LM380) 9-18V d.c. output 2½ watts into 8 ohm with heatsink. 1.25 watt 40hm without heatsink. £1.50 p&p 25p.
(1C) PCB 215mm x 290mm 12xTMS 3122J (or sim.) Hex 32-bit Shift Reg. + 39 ICs. £2. + 50p p&p (limited stocks).

MPU CORNER

2122 (200ns), £3. 2114 (450ns) £4.50.
1702 £2.50. 2708 (400ns) £4.50.
2716 (Single Rail) £9.95
74125 for £1 + p&p 25p.
MK 1002P (dual 128 bit Shift Reg) 35p.
LM711CH (Voltage Comparator) 30p.
MM5240 Character Generator + Data 2560 Bit (64 x 8 x 5) £3.50, p&p 25p.
(All Full Spec)

2526 Character Generator (64 x 9 x 9) £2.95 + data & p&p 25p.

D TYPE CONNECTORS

15 Way: wirewrap plugs only 75p.
25 Way: ribbon plugs £1.20.
25 Way: sockets (solder) £1.00.
50 Way: skt (wirewrap) £1.85.
50 Way: skt £1.45, p&p 25p.

COVERS

37 Way: 80p. (plastic) p/p 25p.
25 Way: 65p. (plastic) p/p 25p.

DISPLAYS

HP 5082 4 digit DIL display full spec £1.80 each p&p 25p. Large quantities POA
MAN 72 7 seg CC £1.25 p&p 25p.
Burroughs Panaplex 9 Dig. + skt and bezel £1.00, p&p 25p.
LED 3 Digit DIL 65p, p&p 25p.
Bowmar 9 digit 1in LED with red bezel. (As used in calculators) £1.00 + 25p p&p

SUPERSAVER

Ribbon Cable Headers 16 DIL Jermyn, gold plated, with cover 45p, p&p 25p.

SUPERSAVER 2

Tantalum Capacitors 25 volt. 4.7 uF, 14 for £1.00, p&p 25p.

SUPERSAVER 3

PRICE SMASH FND 500 5in. LED displays, full spec 50p each, p&p 25p, large quantities POA

SUPERSAVER 4

HYBRID SYSTEMS DAC 371-8 8 Bit, DIL packaged, ideal MPU users with data, £2.95, p&p 25p.

SUPERSAVER 5

LM 323K Voltage Regulator, 5 volt 3A, £4.50, p&p 25p.

SUPERSAVER 6

RS 338-383 Miniature Decade Thumbwheel Switch. £1.65, p&p 25p.

SUPERSAVER 7

SN74116 Dual 4 Bit latch 75p, p&p 25p.
SN7418 Arithmetic Logic Unit, 80p, p&p 25p.
SN74194 4 Bit Register, 50p p&p 25p.
SN74198 8 Bit Shift Register, 75p p&p 25p.

SUPERSAVER 8

BC 108b 8p each or 100 for £7, P&P 25p.

SUPERSAVER 9

4 Digit 7 segment LED Bubble Display, NSA 1540A Ex equipment, 5 for £1, p&p 25p.

SUPERSAVER 10

9 way male/female connector, ELCO 8129, 0.1 inch pitch, gold-plated PCB mounting, ideal, for bussing two PCBs together. Superb value, 35p, p&p 25p.

SUPERSAVER 11

STAR OFFER. Dynamic hand microphone 200 ohm with lead and 5 pin plug, £1.25 (unrepeatable) p&p 30p.

SUPERSAVER 12

TMS 3128NC Static shift register, £1.50, p&p 25p.

SUPERSAVER 13

PL259 (UHF) Elbow Connectors, £50p each, p&p 25p.

SUPERSAVER 14

1S423 Stud mounting rectifiers, 440v, 10A, giveaway price, 10 for £2, p&p 25p.

SUPERSAVER

20K Painton multitrans trim pots, PCB mounting, per box of 14 £2.50, p&p 25p.

SUPERSAVER 16

Yet another star bargain. Astec UM111E36 modulator 65p each, p/p 25p.

LEDs (Full spec).

TIL209, red 10p, 0.2in, red 12p, 0.2in, green 28p, 0.2in, yellow 28p.

RL54 red Axial lead. 15p. P&p on all above 25p.

VERNITRON Ceramic filters type FM4 10 7MHz 45p, p&p 25p.

TRANSISTORS, BD236 40p, BC183L 10p, BF195 10p, SGS 2N3055 30p, p&p on all 25p.

TBA 810S, with data, 85p, 4-way DIL switches, 75p. MC1303 Dual Stereo preamp with data, £1.25.

7in. Nylon cable ties 100 for £1.50, All p&p 25p.

NEW SN76477 (Yes, back in stock). Sound Generator IC (Train, plane, explosion, laser gun etc.), with data £3.25, p&p 25p.

PCB KEYBOARD, 65mm x 82mm, 18 key Clickers less key tops, ideal Hexadecimal use 35p, p&p 25p.

CAPACITOR SCOOP, 1.600uF at 10v, 160uF at 25v. Axial lead. 2 dozen for £1 + 25p p&p.

PAPST min-fans 80mm x 80mm (approx) 220V 50Hz Brand new £8, p&p £1 (limited stocks).

Pewec Boxer. As above but 115v at £4.50 + p&p.

IEC mains chassis plug 75p suitable socket 35p, p&p 25p.

GIVEAWAY

22 pin low profile dil socket, gold plated

12p EACH

p&p 25p

WE STOCK PETS

8K version £599, SAE for the PET SORCERER software lists at discount prices.

We can also offer a 48-hour repair service for out of warranty PETS. Telephone for details, PET edge connector 40x04 £1.40 each p&p 25p.

IC HOLDERS (Low-profile)

8 DIL 12p 14 DIL 15p

16 DIL 17p 18 DIL 20p

22 DIL 28p 24 DIL 35p

28 DIL 45p All p&p 35p

WE STOCK a vast range of TTL, CMOS some 74LS, MINIATURE

TOGGLES, etc.

PSUs. We have a large stock of power supplies at very realistic prices (callers).

RELAYS

ITT 700 ohm Single pole changeover. 45p. BANOR resettable double pole changeover 12V £1. Both p&p 25p.

CIRCUIT BREAKERS

4450V AC 65v DC 0.5A 50p; ditto 7A 80p, p&p 25p.

ALLEN KEYS, 7/16in 5p; 12 for 50p; p&p 25p.

ASR33 (with tape punch reader), generally overhauled £225 inc. of VAT.

Centronics secondhand printers, various types (o/h), phone for your requirements.

MEMOREX 651 dual disk drives complete with power supplies and format electronics (sorry, no data as yet), £350 each inc. of VAT.

Recordcall telephone answering machines (GPO) line matching

transformer removed) sold as is from £2 to £10 depending on condition. Fitted with very nice standard cassette deck. With circuit diagrams. SORRY BUT FOR CALLERS ONLY.

Terms cash with order (official orders welcomed from colleges, etc.) All enquiries s.a.e. please. All prices inclusive of VAT, unless otherwise stated. Postage as shown per item.

FOR THE PROFESSIONAL USER. CP Clare Keyboard switches with buttons (blank) 65p each p&p 25p.

Gould PMA 47/10 015V 3A Brand new 45p p&p £3.50. Many more in stock but in small numbers. Please phone for requirements.

PLEASE DO NOT ORDER GOODS FROM OLD ADVERTS. PHONE BEFORE ORDERING.

SURPLUS STOCKS PURCHASED FOR CASH

LB ELECTRONICS 11 HERCIES ROAD HILLINGDON, MIDDLESEX UB10 9LS, ENGLAND

All enquiries s.a.e. please

New retail premises, now open Mon, Thurs Fri, and Sat, 9.30-6.00. Lunch 1-2.15 weekdays. Closed all day Wednesday. We are situated just off the A40 Opposite Master Brewer



UXBRIDGE 55399

All components full spec.


SPOT DESIGNS

A new series featuring some tried and tested circuits for you to build as you please!

Nicad Current Generator


This simple add-on circuit enables a DC bench power supply to be used as a Ni-Cad charger. These cells have a low internal resistance and can be damaged if a charge current significantly higher than the figure recommended by the manufacturer is used. Furthermore, the cell voltage increases as charging progresses, making it necessary to steadily increase the charge voltage as charging progresses, if the charge current is to be maintained.

This unit is a constant current generator circuit which limits the current fed to the Ni-Cad cell(s) to an acceptable level. In effect, the unit automatically adjusts the charge voltage to just the right level to give the desired charge current. The circuit is a standard constant current generator configuration with R1 and D1-4 being used as a sort of low voltage zener stabiliser. About 0V7 is developed across each of the four forward biased silicon diodes, giving a total zener voltage of about 2V8. Q1,2 are used as a Darlington pair and, therefore, have a very high combined gain, so that quite high output currents can be produced by the fairly low drive current available. About 0V65 is dropped across the base-emitter terminals of both Q1 and Q2, giving about 1V5 across emitter resistor RC. The emitter current can be controlled by RC. The collector current of Q1,2 is virtually identical to the emitter current and is actually just fractionally lower as the emitter current is equal to the sum of the base and collector currents. Thus, provided a low impedance load (such as Ni-Cad cells) is present at the output, the current fed to the load can be set by giving RC the appropriate value.

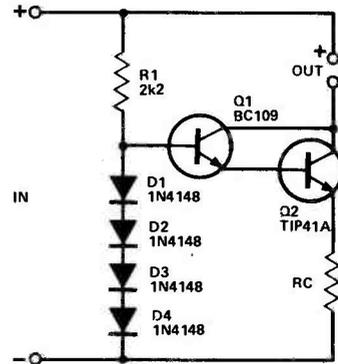

The value of RC is equal to 1,500 divided by the required output current in milliamps and would, for example, be 10 R for rapid charge Ni-Cads requiring a charge current of 150 mA ($1,500 \text{ divided by } 150 = 10 \text{ R}$).

The input voltage should be 3-6 V more than the total voltage of the cells being charged. The cells should be connected in series across the output. Of course, the power supply must be capable of supplying the charge current drawn by the cells plus the additional few milliamps drawn by the current generator circuit itself. For charge currents of more than about 100 mA it will probably be necessary to fit Q2 with a small finned heatsink to prevent it from overheating.

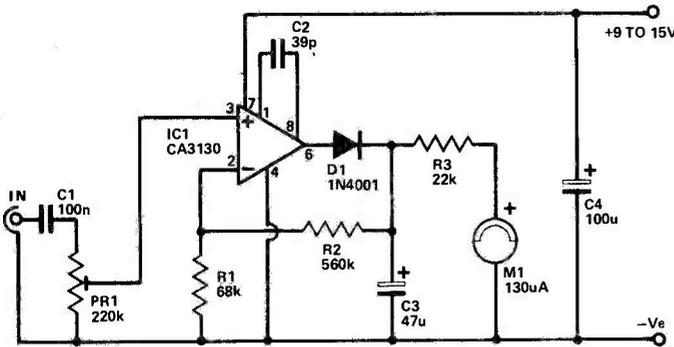

Peak Reading VU Meter

The type of VU meter normally employed in tape decks and other items of audio equipment is the average reading type. These can give misleading results on signals that have a pulse-like waveform of relatively low average amplitude for the peak

amplitudes involved. This can lead to overloading and consequent distortion on signals of this type eg piano and percussions. One way around this problem is to use a peak reading VU meter. This type of circuit has a fast attack and slow decay time so that it responds properly to brief and intermittent signals. The normal response times for a unit of this type are 2.5 mS attack and 1 S decay. This unit roughly adheres to these figures.

IC1 is an operational amplifier which is used in the non-inverting mode. R1,2 form a negative feedback network which sets the closed loop voltage gain of the circuit at a little under ten. D1 is included at the output so that IC1 can supply an output current, but a current cannot flow into the output of IC1. The feedback is taken from the junction of D1, R2 etc., so that the input voltage appears here amplified by about ten times and the feedback overcomes the non-linearity of D1. C3 is rapidly charged to the peak output voltage as it is fed from the fairly low impedance of IC1 and D1. Its only discharge paths are through the much higher impedances of R3-R2 and R4-M1. This gives the circuit the required fast attack and slow decay times. M1 responds to the voltage across C3, which is, of course, proportional to the peak positive input level (the circuit is a halfwave type and does not respond to negative going inputs). The VU meter movement used in the prototype had a FSD value of 130 uA, but the circuit should work with any type having a sensitivity of between about 50 and 200 uA.

R1 biases the non-inverting input of IC1 to the negative rail and also enables the sensitivity of the circuit to be adjusted to the correct level. At maximum sensitivity, less than 1 V peak to peak is needed for FSD of M1. Current consumption is only about 400 uA.

CALCULATORS

CENTRAL PROGRAMMABLES



FX 501P 10 + 2 digit, 128 step, 11 memories	£43.43
FX 502P 10 + 2 digit, 256 step, 22 memories	£60.83
FA1 Adaptor cassette interface	£17.35
FX501P+FA1	£57.35
FX 502P+FA1	£74.74
*TEXAS T151-111 32 step 10 memory	£25.17
TEXAS T153 Lcd 32 step constant memory	£22.57
TEXAS T157 50 step 8 memory	£23.44
TEXAS T158 480 step 80 memory	£58.22
*TEXAS T158C as above with prog retention	£73.87
TEXAS T159 960 step 100 memory mag card	£150.39
TEXAS PC100C Printer for 58/58C/59	£136.48
TEXAS PC100C IF ORDERED WITH 58/58C/59	£130.38
*INCLUDES — rechargeable battery pack/adaptor/charger	

PROGRAMME LIBRARIES FOR T158/58C/59

APPLIED STATISTICS	£22.57
BUSINESS DECISIONS	£22.57
ELECTRICAL ENGINEERING	£22.57
MATHS/UTILITIES	£33.00
LEISURE	£54.74
STRUCTURAL ENGINEERING	£54.74
SURVEYING 11	£19.09
PC100C PAPER ROLLS TEXAS TP30250 10 OFF	£6.04
BATTERY PACKS state model or BP number	

SCIENTIFICS 8 DIGIT Lcd

CASIO FX68	£16.48	CASIO FX100	£13.00
CASIO FX80	£12.13	CASIO FX510	£16.48
CASIO FX81	£13.87	CASIO FX3200	£18.22
CASIO FX330	£13.87	CASIO FX5000 10 MEM	£24.30
CASIO FX2600	£18.48	CASIO FX8100	£20.83
CASIO FX7100	£20.83	SHARP EL5806 (8+2)	£15.81
SHARP EL503	£11.26	SHARP EL5808 (8+2)	£13.87
TEXAS T125 or T135	£16.48	SHARP EL5812	£18.48
TEXAS T150	£19.98	NATIONAL NS108	£15.81

SCIENTIFICS 10 DIGIT Lcd

CASIO FX100	£13.00
CASIO FX510	£16.48
CASIO FX3200	£18.22
CASIO FX5000 10 MEM	£24.30
CASIO FX8100	£20.83
SHARP EL5806 (8+2)	£15.81
SHARP EL5808 (8+2)	£13.87
SHARP EL5812	£18.48
NATIONAL NS108	£15.81

TEXAS T142 M.B.A. 32 step 12 memory finance/stats	£35.61
TEXAS T1 PROGRAMMER	£43.43
TEXAS T144 Lcd constant memory statistical	£26.17
TEXAS TITTLE PROFESSOR	£11.26
TEXAS DATAMAN	£17.35
TEXAS SPEAK AND SPELL	£38.22
CASIO FX5000EP mains printer. List £196.48	£136.48

CLOCK CALCULATORS

CASIO MQ6 micro card watch in leather case	£17.35
CASIO PWB1 hourly chime/alarm	£13.00
CASIO ML81 hourly chime/2 alarm/timer/date/musical	£19.09
CASIO ML71 card version of ML81 with 1 alarm	£19.09
CASIO AQ1500 day/date/stopwatch	£13.87
CASIO AQ2200 hourly chime/alarm/calendar/stopwatch	£17.35
CASIO MQ12 card version of above	£17.35

TELEPHONE ANSWERING MACHINES twin cassette
PRICES EXCLUDE V.A.T. PLEASE ADD 15% PACKING & DELIVERY FREE £147.78

CALCULATOR SALES & SERVICE

Arrow Works, Arrow Road, Redditch B98 8NN
Tel. Redditch (0527) 43169



CLEF KITS



NEW — ELECTRONIC ROTOR

Two-speed organ rotor simulator plus a three-phase chorus generator on a single PCB (8" x 5"). Kit includes all components — IC sockets throughout — mains operation and stereo headphone driver PCB. Easily integrated with existing organ. Component kit **£89.00**.

KEYBOARDS

We believe that we have located the best manufacturer of square front Keyboards, as used in our Kits, and can also supply Keyswitch hardware including the industry standard soft plated contact springs.

73 NOTE C-C **£23.80**

73 NOTE F-F **£37.00**

88 NOTE A-C **£45.00**

All Keyboards are easily cut to provide your required length and compass. Quantity enquiries welcome.

BUILDING SERVICE

We are specialists in Electronic Piano Manufacture and can build your Piano for you — see lists.

INFORMATION

Please send S.A.E. quoting items of interest. Telephone BARCLAYCARD orders can be accepted, all prices include V.A.T., carriage & Insurance.

VISITS

Are welcome by appointment, otherwise Mail Order Only.

EXPORT

Enquiries welcome — in Australia please contact JAYCAR (Sydney).

High Quality Electronic Musical Instruments under the personal supervision of Specialist Designer A. J. BOOTHMAN.

JOANNA 72 & 88 PIANOS

Six and 7/4 Octave Electronic Pianos with unique Touch Sensitive Action as used in the P. E. JOANNA, which electronically simulates piano key inertia — a feature not available in any other design. Build this widely acclaimed professional instrument, for either Domestic or Stage use, from our top quality Component kits.

SIX OCTAVES — **£207**

7 1/4 OCTAVES — **£232**

P.E. STRING ENSEMBLE

The versatile String Synthesizer with a fantastic sound at an economic price. Split Keyboard facility with a range of impressive voices.

COMPONENT KIT — **£169**

Back up TELEPHONE advice is available from the designer to supplement the clear instructions included with the above Kits.

P.A.'s — SPEAKERS — CABINETS

Units can be supplied to add to the Component Kits, including Domestic or Stage Cabinets and portable tubular legs.

CLEF PRODUCTS (ELECTRONICS) LIMITED

(Dept. E.T.I.)

16 Mayfield Road, Bramhall, Cheshire SK7 1JU. 061 439 3297



A. Marshall (London) Ltd., Kingsgate House,
Kingsgate Place, London NW6 4TA
Industrial Sales: 01-328 1009
Mail Order: 01-624 8582
Also retail shops: 325 Edgware Road, London W2.
40 Cricklewood Broadway, London NW2. 85 West Regent St., Glasgow.
108A Stokes Croft, Bristol.

CAPACITORS:

Mullard Ceramic 63v range
1pF to 10,000pF E 24 range
all at £0.06 each

Siemens Ceramic 63v B37448/9
01: .022: .033: .047mF @ £0.06
.068: .1mF @ £0.08: .22mF @
£0.11

CSF High Voltage Ceramic Discs
Prices £0.07 to £0.18 Range
100pF to 10,000pF

Voltage range up to 6Kv.

See catalogue for details.
Comprehensive range Siemens
Layer Polyester Caps: .001 to
3.3mF

Prices £0.07 to £0.63.

See catalogue for details.
Large range of Mullard/Siemens
Electrolytic Axial/Radial
Capacitance values 1.0mF to
10,000mF

Voltage ranges 25v: 40v: 63v:
100v:

Prices and types as catalogue
Also Mullard C280; Siemens
B32231/4 and B32110. All prices
net + VAT and postage/packaging.

TOOLS BAHCO

Side Cutter with Bezel.
Side Cutter without Bezel.
End Cutter without Bezel.

Vero Metal Shears.
Other items as catalogue.



BOXES & CASES

See catalogue for full range.

Aluminium boxes 13 sizes.

Rexine Covered boxes 7 sizes.

NEW RANGE TMEC CASES

Send S.A.E. for details & types

Price range. £14.04 to £17.00

ABS PLASTIC BOXES

3" x 2 1/4" x 1 3/8"

3 3/4" x 2 3/4" x 1 3/8"

4 1/2" x 3 3/4" x 1 1/2"

8" x 4 3/4" x 3"

BAZELLI INSTRUMENT CASES

5 sizes.

Miscellaneous hardware

including

Vero Board: Superstrips:

Vero Breadboard.

Vero boxes (see catalogue for
full range).

Card Frames: Fliptop boxes:
etc etc.

Prices as
catalogue

TTL see catalogue for full range

SN7400N	£0.14	SN7491AN	£0.54
SN7401N	£0.14	SN7492N	£0.31
SN7402N	£0.14	SN7493N	£0.31
SN7403N	£0.14	SN7494N	£0.80
SN7404N	£0.14	SN7495N	£0.55
SN7405N	£0.15	SN7496N	£0.34
SN7406N	£0.34	SN7497N	£1.80
SN7407N	£0.28	SN74100N	£1.10
SN7408N	£0.15	SN74107N	£0.21
SN7409N	£0.18	SN74118N	£0.76
SN7410	£0.15	SN74119N	£1.20
SN7411N	£0.15	SN74121N	£0.25
SN7412N	£0.15	SN74122N	£0.48
SN7413N	£0.28	SN74123N	£0.42
SN7414N	£0.47	SN74124N	£0.53
SN7416N	£0.22	SN74125N	£0.40
SN7417N	£0.22	SN74161N	£0.50
SN7420N	£0.15	SN74145N	£0.64
SN7423N	£0.18	SN74148N	£1.05
SN7425N	£0.19	SN74150N	£0.39
SN7425N	£0.19	SN74151N	£0.55
SN7427N	£0.19	SN74153N	£0.55
SN7430N	£0.15	SN74154N	£0.90
SN7432N	£0.17	SN74155N	£0.60
SN7437N	£0.21	SN74157N	£0.59
SN7438N	£0.21	SN74160AN	£0.70
SN7440N	£0.15	SN74161AN	£0.70
SN7441AN	£0.52	SN74162AN	£0.70
SN7442N	£0.40	SN74163AN	£0.70
SN7445N	£0.66	SN74164AN	£0.80
SN7446AN	£0.46	SN74165AN	£0.80
SN7447AN	£0.48	SN74167N	£1.20
SN7448N	£0.45	SN74174N	£0.80
SN7450N	£0.15	SN74175N	£0.63
SN7451N	£0.15	SN74176N	£0.74
SN7453N	£0.15	SN74177N	£0.73
SN7454N	£0.15	SN74180N	£0.70
SN7450N	£0.15	SN74181N	£1.65
SN7470N	£0.26	SN74182N	£0.83
SN7472N	£0.24	SN74184N	£1.29
SN7473N	£0.25	SN74185AN	£1.10
SN7474N	£0.25	SN74186N	£1.35
SN7475N	£0.31	SN74188AN	£1.84
SN7476N	£0.26	SN74189N	£2.25
SN7480N	£0.39	SN74190N	£0.74
SN7481N	£0.11	SN74191N	£0.79
SN7482N	£0.65	SN74192N	£0.79
SN7483N	£0.60	SN74193N	£0.79
SN7484N	£0.95	SN74196N	£0.74
SN7485N	£0.70	SN74197N	£0.74
SN7486N	£0.25	SN74198N	£1.09
SN7489N	£1.66	SN74199N	£1.09
SN7490AN	£0.33		

KNOBES & SWITCHES

Big selection as catalogue
Also Resistors; Presets; Pots;
Opto; Semiconductors etc.

SOLDERING EQUIPMENT

IRONS-ANTEX

15 watt C15 £3.95

15 watt CCN £4.20

17 watt CX17 £4.20

25 watt X25 £4.20

Stand £1.50



DESOLDERING TOOL
Solder £6.50

MITRAD

MITRAD

QUARTZ L.C.D.s AT THEIR BEST!

MITRAD

GENT'S CHRONO ALARM FRONT BUTTON

Brand new 1980 style. Basic working modes of chronograph, 24-hour alarm and dual time zone. Constant display of hours, mins, secs and weekday indication with am/pm, T2 and A1 flags. Date indication. The chrono runs to 1/10th sec, with the 1/10th's running along the bottom of the watch. It has a twelve hour capacity. The 24-hour alarm system is actuated for a full 60 seconds. Dual timing facilities give the watch the added touch of compactness. Back-light, closely woven adjustable stainless steel strap.



ONLY £15.50

GENTS MELODY ALARM CHRONO DUAL TIME

Brand new Melody Alarm, Chrono. Constant display of hours, mins, secs, weekday, am/pm and mode square flag indication.

The chrono runs to a 1/10th sec (running horse style) split and lap mode facilities are standard. Dual timing facilities. The alarm system is unique in the fact that it plays the tune "Yellow Rose Of Texas" for 20 seconds.

The tune can be actuated at any instance by the press of a button. Backlight, infinitely adjustable stainless steel strap.

VERY LOWLY PRICED

£17.75



GENT'S QUARTZ ANALOGUE

A truly superb timepiece with extreme accuracy. A choice of two colours on this outstanding watch are available, blue or white.

The calendar in the watch can be set to give a readout in either French or English with date indication being automatic.

An infinitely adjustable stainless-steel strap is built in as part of the watch.

The watch is fitted with a long-life battery and comes with luminous markings to aid night-time vision.



YES ONLY £19.95

GENT'S ALARM CHRONO 12/24 CYCLE

A really superb watch and module. It can be set as a 12- or 24-hour watch with hours, mins, secs, am/pm and weekday indication always on display. A unique calendar is built into the watch. You can have month followed by date or date followed by month, it's entirely up to you. A 24-hour alarm can be set to any time within a 24-hour period.

The chronograph has a 12-hour capacity and runs at 1/10's. Split and lap mode facilities are available.

Battery hatch, mineral glass, long-life battery and a closely woven adjustable stain-



less steel strap finish the watch off with impeccable looks.

ONLY £16.50

THINKING OF BUYING A NEW DIGITAL WATCH—

THEN CONSULT OUR FREE FULL-COLOUR CATALOGUE FIRST

TEL. OR WRITE FOR YOUR COPY (0536) 522024

GENT'S FOUR-BUTTON ALARM LM40

A very compact and sleek-looking GENT'S Alarm Watch.

Constant display of Hours, Mins, and Secs., with an optional display of Month, Date and Weekday.

A very effective alarm is built in which can be set within a 24-hour period, and is activated for 60 seconds.

Back Light and a closely woven adjustable stainless-steel strap finish the watch off.

ONLY £10.25



GENT'S CHRONOGRAPH

Probably the best looking chrono on the market. Constant display of hours, mins, secs with am/pm indication. Also month, date and weekday indication. 1/100th and 1/10th sec with split and lap mode facilities. Back-light, closely woven adjustable stainless steel strap.



SPECIAL £8.95

LADIES' DRESS WATCH

An extremely popular ladies 5-function watch. Finished in gold.

Constant display of Hours and Mins, with Month and Date being available.

Auto-Calendar

Back Light and a closely woven adjustable strap.

£10.50



LADIES' SUGARCOATED

Another superb ladies watch with that extremely popular sugar frosted finish. Links can easily be removed from the strap and the clasp has a spring mechanism built in to give a comfortable fitting. Constant display of hours and mins, with month, date, secs, auto calendar and back-light.



£10.50

MITRAD WHERE RELIABILITY, STYLE AND ELEGANCE REALLY COUNT MITRAD

MITRAD

MITRAD

QUARTZ L.C.D.s AT THEIR BEST

MITRAD

GENTS MEMORY CALENDAR ALARM CHRONO



A really successful watch incorporating all the latest technology.

Hours, mins, secs, weekday and snooze alarm indication on constant display.

A further two optional display modes are available, one being the calendar and month, which can be increased or decreased to give the appropriate month of the year.

A 1/106th second chronograph with split and lap mode facilities are built into the watch with a 12-hour capacity.


A 21-hour alarm with a 10-minute snooze function is also standard to this watch. A further feature is the backlight and fully adjustable stainless steel bracelet.



**STAR VALUE
£19.95**

GENT'S MULTI-MELODY CHIME ALARM CHRONOGRAPH

"Latest technology" constant display of hours, minutes and seconds; weekday date and month, with mode and chime indication display. A musical alarm is built in and can be set to any time within 24 hours; once activated playing the tune "Oh Suzanna". Two further alarm systems are incorporated in this outstanding watch: (i) 24-hour alarm; (ii) count down alarm. The watch can be set to chime on every full hour. A 1/100th second chronograph with split and lap mode facilities is standard, the watch function may also be switched off. An excellent feature is the mineral glass face. This watch also has a battery hatch, backlight and infinitely adjustable stainless steel strap.

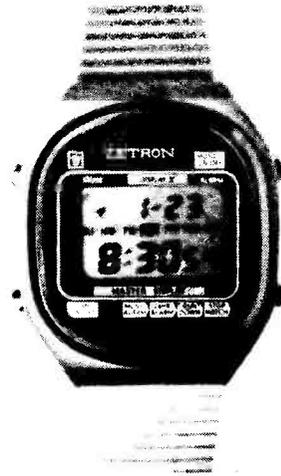

Value at **£19.95**

This month's special offer on the above two watches — a **FREE credit card calculator** currently being retailed at **£7.95**. 8 digits, square root, full memory, per cent keys, plus auto.

shut-off, coming in attractive **FREE wallet**. **REMEMBER — ABSOLUTELY FREE** with every one of the above watches ordered this particular month.

GENT'S CHRONOGRAPH SOLAR ALARM

The slimmest Chrono Solar Alarm in the World. Only 7mm thick.

This watch has a genuine solar panel. You can take the battery out and the watch will still function as normal. Battery hatch. Mineral glass.

Constant display of Hours, Mins. and Secs. with Date Flag. Optional display of Hours, Mins. and Date.

The alarm can be set to any time within a 24-hour period and is actuated for a full 60 seconds.

The chrono runs to a 1/10th Sec. with a maximum capacity of 24 hours. Lap Time and Freeze Facilities are available.

Dual timing facilities are readily available.

Back Light. Fully adjustable stainless-steel strap.

This watch is available in gold or silver.



OFFERED AT £19.95

LADIES' COCKTAIL

Elegance and style for the lady with the discerning taste. In gold or silver finish with matching bracelet. Constant display of hours and mins. with month, date, secs., auto. calendar and back-light.



**VERY SPECIAL
£10.50**

CREDIT CARD HOLDERS

Place your order over the phone and get your new time-piece despatched same day. 24-hour ansaphone service.

MITRAD

THE UNRIVALLED RANGE

MITRAD

We are able yet again to offer you the above watches plus a complete quartz watch range. All at unrivalled prices. Just look at the following points:

- (i) 48-hour despatch guaranteed on both retail and trade orders.
- (ii) Full instructions and 12 month manufacturers guarantee.
- (iii) Our own free back-up service.
- (iv) 10-day full money refund if not completely satisfied.
- (v) Free felt presentation case with each watch.

**M
I
T
R
A
D**


★ FULL COLOUR CATALOGUE NOW AVAILABLE ★

Write or phone for your free copy. Trade lists on application.

Earn £££s selling watches to all your friends. P/P per item 85p which includes insurance. Cheques or P.O.s made payable to Mitrad and sent to (Dept. ETI), 68-70 High Street, Kettering, Northants NN16 8SY.

Telephone: (0536) 522024

100W POWER AMPLIFIER

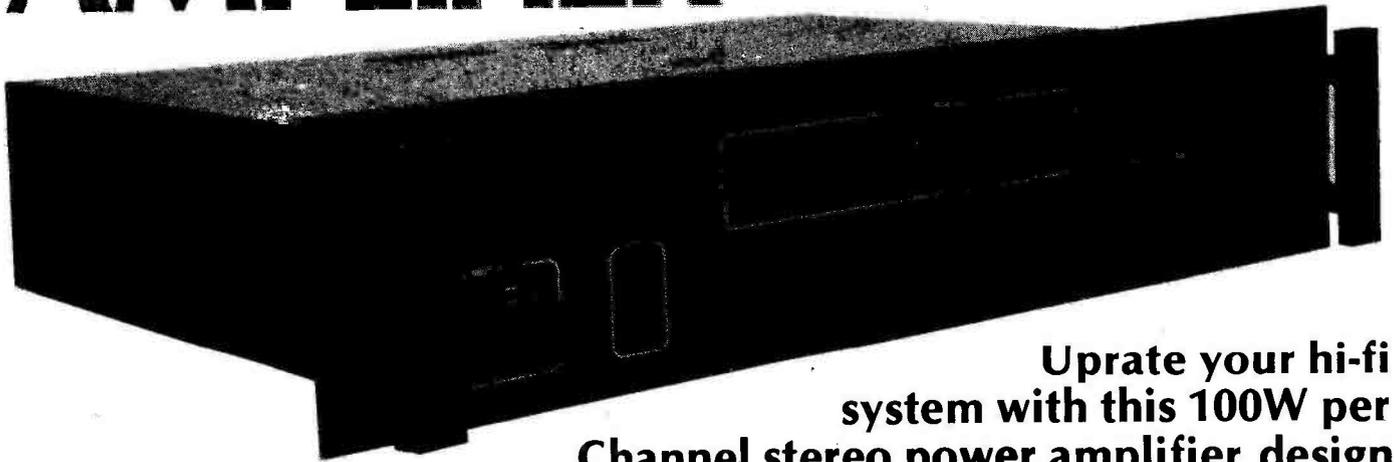

Uprate your hi-fi system with this 100W per Channel stereo power amplifier design from Ambit International, featuring ultra-fast MOSFET output stage.

There is no shortage of audio amplifier designs appearing in the enthusiast press, so to be worthy of close attention, anything new has to justify its existence with a number of innovative features. The amplifier described here is a (nearly) indestructible 100 W RMS per channel unit, employing ultra fast Hitachi MOSFET output transistors, providing excellent amplifier performance. The drive circuitry is considerably less complex than similarly powerful bipolar designs and makes construction far more straightforward.

Like all MOSFETs, the nature of the device construction is such that it is not susceptible to the thermal runaway and secondary breakdown, which is probably the single most pernicious aspect of high powered amplifier designs using conventional bipolar techniques. This means that much of the protection circuitry associated with bipolar amplifiers is unnecessary — and since the current limiting technique in bipolar circuitry involves inserting resistance between the output transistors and the load — the damping factor of the output stage is not compromised.

Fail-Safe

The major problem area with any DC coupled amplifier is the potential for damage to the loudspeaker by large DC offsets at the speaker terminals. In this design, a separate control circuit has been used to monitor the output DC levels and switch off a fail-safe relay in the event of a potential hazard. The same relay is also driven from a 'thump' prevention circuit that only connects the loudspeakers to the output stage when a suitably stable DC condition has been maintained for a brief time.

Whilst the power supply is active, but the relay is being held open by the protection circuitry, a LED in the front panel will flash intermittently. Yet more LEDs are employed in a switchable 10 W/100 W logarithmic output level bar graph indicator that provides functional (peak) indications.

The MOSFET output stage is a source follower system, requiring only sufficient drive to overcome the gate capacitance effects and thus very little drive power is consumed. So little, in fact, that plastic encapsulated extended TO92 devices are quite sufficient to drive a single output pair.

Silence Is Golden

The amplifier input stages are designed using low noise high voltage devices from Hitachi. So low noise that this is one of the few amplifiers where it is completely impossible to tell if the mains is switched on. Both AC and DC input coupling are selectable from the front panel.

Power Supply

A well regulated power supply is an important feature of a high powered PA. The power output of an amplifier is usually limited by the capacity of the power supply (and the load impedance), so the output can be doubled by halving the load resistance, provided the PSU can supply the necessary current.

The PSU of this amplifier uses two entirely independent transformers, rectifiers and reservoir capacitors which all serve to reduce interchannel crosstalk,

especially at low frequencies. It is desirable to achieve as little difference between the output voltage across the reservoir capacitors when the amplifier is operating at 10 W output, as it is when it is putting out full power. The design is specifically for transformers of 5-8% regulation, so that the DC supply voltage only moves between 47-55 V as the power varies. The use of a fully regulated PSU is not required, since factors such as the amplifier voltage gain are independent (or should be) of supply voltage. Separate windings and rectifier/reservoir systems are used to power the DC offset and relay protection circuitry on one unit and the LED bar graph output indicator from the other channel transformer.

Earth Talk

Perhaps the single most vital aspect of high current amplifier design is the correct layout of the earthing paths of those sections carrying high current. The fact that an earth is not necessarily an earth unless it is 0R impedance has led to the downfall of many PA designs.

Real earth leads contain a finite resistance, so in the example shown the load current (I_L) will be far greater than the input bias current — so V_1 will follow the output voltage directly. Since the input current is basically feeding the (+) side of the amplifier — this is positive audio feedback and can very easily lead to complete instability, or at the very least, increased distortion. Thus the policy is to use single point earthing of all such systems wherever possible. The temptation to lump earths together for the sake of convenience must be avoided.

These considerations also apply around the PSU, where ripple current can cause some similarly inconvenient effects.

Taking Precautions


The DC condition of each channel output is monitored via a 100k resistor feeding the bases of a differential amplifier (Q101, Q201). A 22uF capacitor at this point determines the maximum frequency that will trigger the relay circuit, according to the time constant. Assuming all is well on switch-on, the DC offset circuit does not trigger, but the 100uF capacitor sandwiched between the collector of Q2 and the base of Q103 takes approx. five seconds to charge up, holding the relay open with Q104 still off. As long as the relay is off, the multivibrator formed by Q105 and Q106 can function and so the LED in the collector load of Q105 will flash.

As soon as Q104 turns the relay on and the speakers are connected, the base of Q106 is clamped and the multivibrator stops oscillating with Q105 held permanently on.

Red Alert

If a DC offset should occur, or (depending on the time constant of the input network) a large low frequency 'thump' be transmitted through the system by a noisy switch connection in the preamp or tuner, either Q101 or Q102 will turn on, instantly charging a 100uF and switching off Q104 again. The LED starts flashing and you know something is wrong somewhere. As soon as the DC offset has been removed, the 100uF discharges and normal service will be resumed with the LED permanently on.

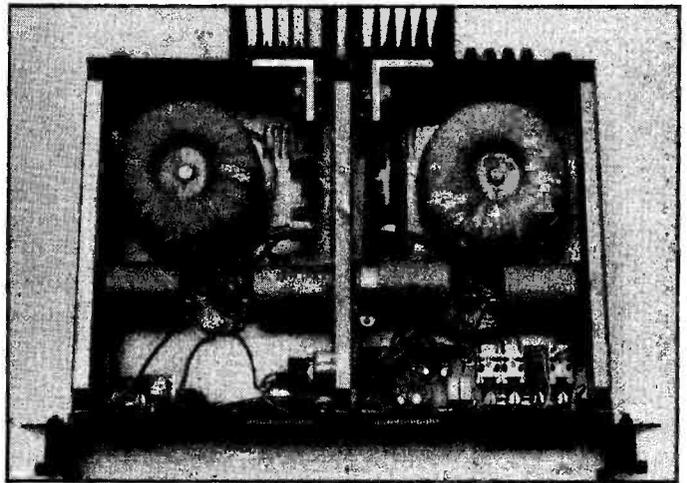For sheer simplicity, the AEG U257/U267 bargraph drivers are best. They are logarithmic units, which are used in cascaded form to provide a ten LED output (per channel) driven from the loudspeaker terminals. As well,



Take the lid off the 100W PA at your peril - those power supplies mean business.

as providing instantaneous output power indication, the fact that the detector is right at the front of the circuit means that the output bargraph can also indicate the presence of an ultrasonic instability. (ie bargraph reads, with no audible output — assuming you have connected the speakers to the output terminals.) Do not use DIN two pin speaker sockets, as they are not substantial enough for the currents carried in 100 W systems.

A switched resistor network provides attenuation to set the peak reading the bargraph to the desired level (nominally chosen at 10 W and 100 W).

Construction And Testing

Take careful note of the earth layout in particular. The amplifier modules are mounted via right angle brackets to the output heatsink and care should be taken to use enough heatsink for the sort of use you envisage.

The heatsinks shown are proprietary Redpoint units, just about sufficient for 200 W RMS operation. Since the PSU is capable of driving the amplifier to 250 W in total, you should increase the radiating area of the heatsinks to cope with a heavy duty application such as disco usage, etc. Many commercial amplifier designs of the 'domestic' variety use outrageously inadequate heatsinks, on the basis that even the most dedicated audiophile only ever listens to an average level of 20 W. 100 W crescendos and peaks are then either dealt with by the reserve margin of the heatsink or the fuses blow.

The MOSFET amplifier will get progressively quieter as the drain resistance increases under overheating conditions, so even if you skimp on the heatsinks, the chances are that the worst that can happen will be enforced pianissimo.

If you want to demonstrate the 'screwdriver across the output' trick to your friends unlucky enough to suffer from bipolar amplifier problems, then bypass the relay, since in the authors' experience the first things to get fouled are the relay contacts, which inconveniently weld themselves together at the same time as a large molten pit mark appears on your screwdriver. The switch-on thump is not at all serious even without the relay protection circuit, but there is a very real danger of evaporating the costly voice coil in your loudspeakers if a fault should occur causing the output to slam hard over to one of the rails.

Use large gauge wire (15A will do) for anything like a power amp earth or supply connection and all output leads, etc, and do not forget to fuse the transformer

On Top Of Old Smokey

As a final precaution, ensure that you have the MOSFETs in the right places. Turn on to check the current consumption. Set for approx 35 mA using the cermet preset. If the current cannot be set sufficiently low, or smoke and other unpleasantness ensues, turn off and check all the connections.

If all is well, fit the loudspeaker, but keep the 8R series resistor and fuse in place as a further precaution. Turn on and listen to the output to make sure that obvious problems like excessive noise and hum are not present. If the input is unterminated, there will be extraneous hum pickup, but shorting the input socket should remove this completely. The only earth connection of the system should be via the PA and the input lead earths.

If all is quiet, but the LED bargraph is lit, then it is possible that there is an HF instability occurring in the PA. Check with an oscilloscope. The points to observe are usually around the output (Zobel) network, where any sustained HF instability will cause the series resistor in the Zobel network to warm up. Persistent HF instability may easily be due to incorrect earthing and a host of interactive problems, but the modular construction of the PCB and connection systems should avoid insurmountable problems.

Unduly distorted sound whilst the DC conditions appear to check out can be due to many problems, but here is a list of the ones the authors have encountered:

Connecting the loudspeakers between the two outputs, not output and ground.

Components around Q1 and Q2 being wrong values.

Forward biasing electrolytic capacitors in the signal path (ie insertion the wrong way round) can lead to both distortion and noise.

On the assumption that your ears are likely to be as good a judge as anything, you can go ahead and connect the loudspeakers directly. Keep the volume setting low if your speakers are not 100 W RMS rated. There is always the chance of high voltage spikes getting through and causing damage. You can artificially suppress the gain by altering the gain setting resistors in the feedback loop, but the only certain way to limit the output power capability is to reduce the power supply voltage.

HOW IT WORKS

The whole circuit may be likened to a large 'op amp', with the (+) input being the main input, and the (-) input being used for the negative feedback connection — so the input will respond to DC equally as well as to AC and may thus be used for a very large form of servo control if so desired.

The gain of the amplifier is set at 22 according to the ratio of R8/R7 — so that an input of 1V RMS from the preamp will drive the output to 22V RMS, which by Ohm's law gives: $V^2/R = 22^2/8 = 60.5 \text{ W}$ (assuming 8R load).

To achieve 100 W output, you need:
 $28/22 = 1V_{28v}$ RMS input.

The two stages of differential voltage amplification use 120V transistors for maximum safety, with the collector of the driver stage being fed from a constant current source (Q5). This makes for exceptionally high open loop voltage gain in the overall system, so that very large amounts of negative feedback are applied. Some schools of thought feel that a lot of feedback in PA design is not a "Good Thing", but maybe they had not benefited from the speed of the HMOSFET. The problem in bipolar designs has usually involved the delay when getting the feedback information round the works, leading to transient intermodulation distortion (TIM). The HMOSFET is sufficiently fast to cope with all this and not produce any TIM.

The 22k (R8) in the negative feedback loop from the output is not compensated in any way due to the ultra-high speed of the MOSFETs and comparison with a bipolar design will usually reveal a substantial phase correction here in the guise of a parallel capacitor.

A high quality cermet preset is used between the gates of the output devices to set the quiescent current at approx. 30 mA by developing a voltage between the two MOSFET gates. Since Q5 is a constant current source, the voltage across the gates is then simply $I_c \times R_{Vr}$.

The gates are also provided with zener diode clamp protection to clip the drive voltage to below 14V (the maximum permissible). In normal use, the gate voltage never gets near 14V, so this is primarily a fault protection precaution and not any sort of general overload protection.

A Zobel network at the output is necessary to prevent HF instability, since, although MOSFET PA design is inherently more stable than bipolar design, it is still necessary to cope with problems associated with the high impedance inputs of the FETs and the uncertainties of finite earth path resistances. A choke coil in series with the output provides additional stability with particularly reactive loads — although it is debatable whether or not it is necessary in this design. Output protection is inherent in the HMOSFET, since as the temperature of the transistor rises, so the channel resistance increases, causing the maximum available output current to diminish. Rating this amplifier at 100 W is reasonably conservative, since with a correctly regulated power supply design (5%) as much as 160W RMS can be achieved — and still it is possible to short circuit the output without destroying the MOSFETs!

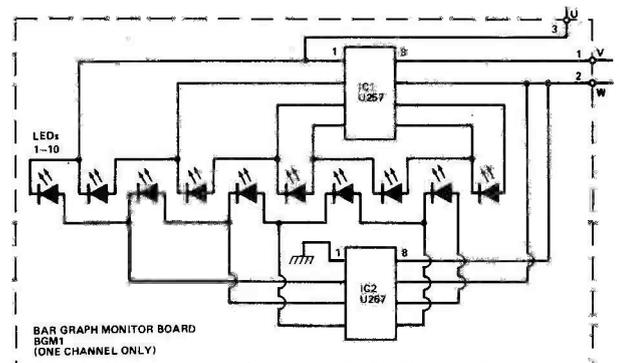
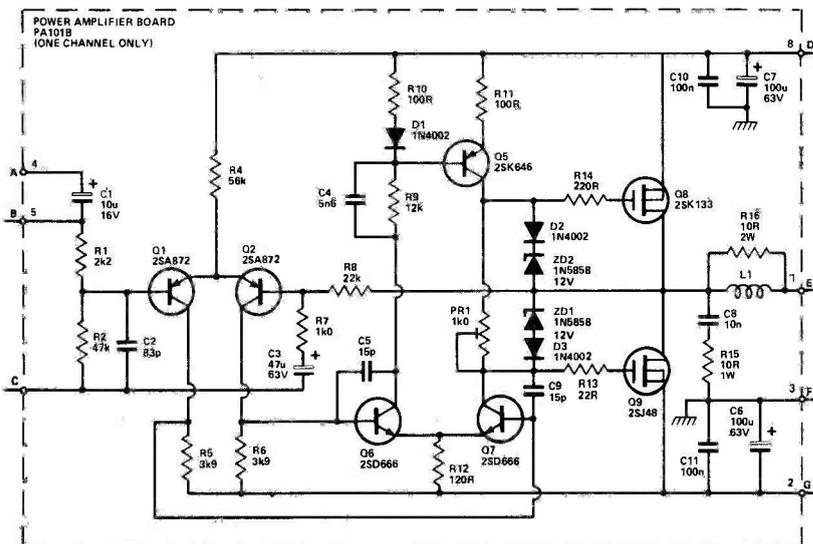


Fig.4. (left) Circuit diagram of the Power Amplifier.

Fig.5. (above) Circuit diagram of the Bargraph Monitor.


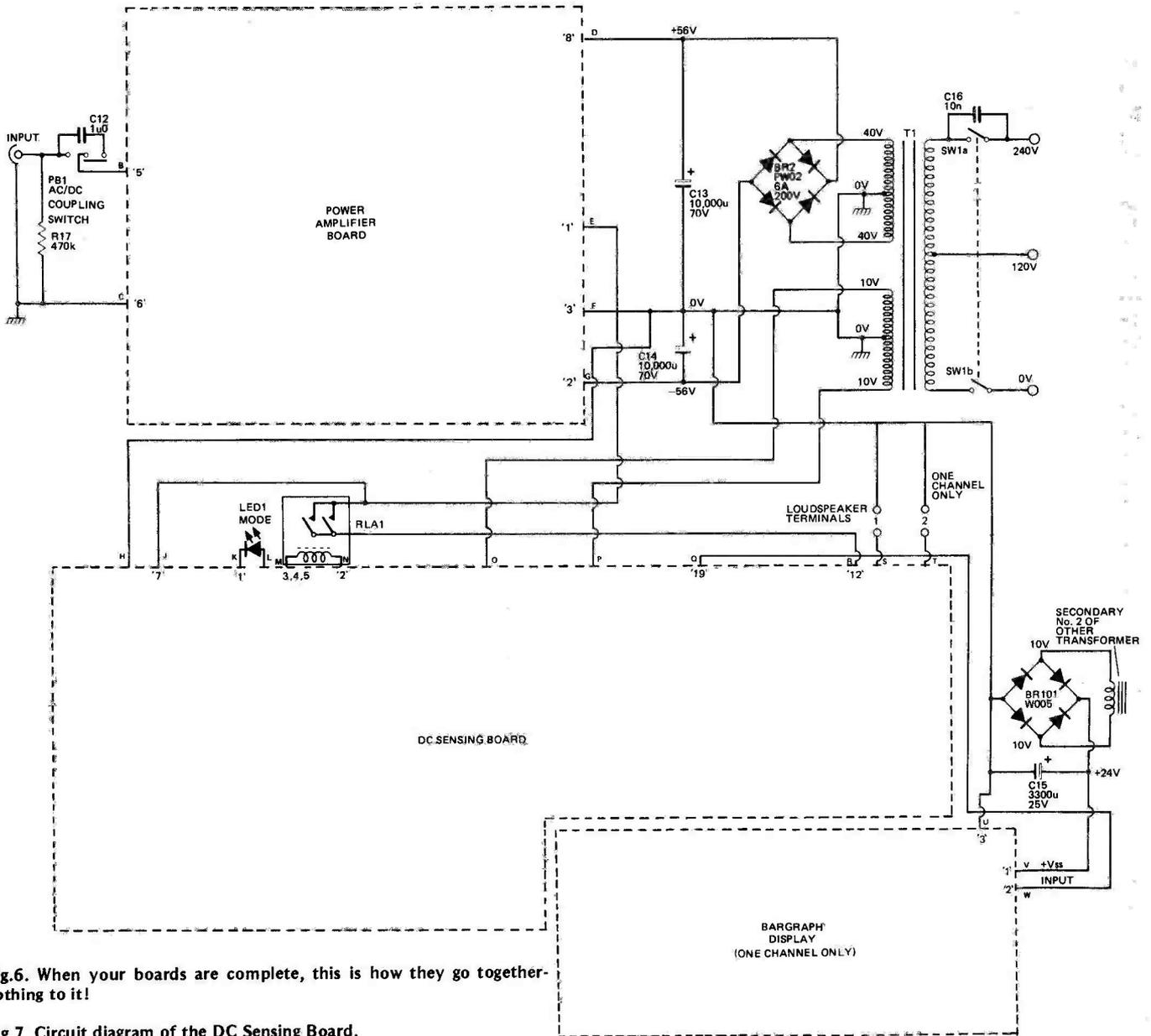


Fig. 7. Circuit diagram of the DC Sensing Board.

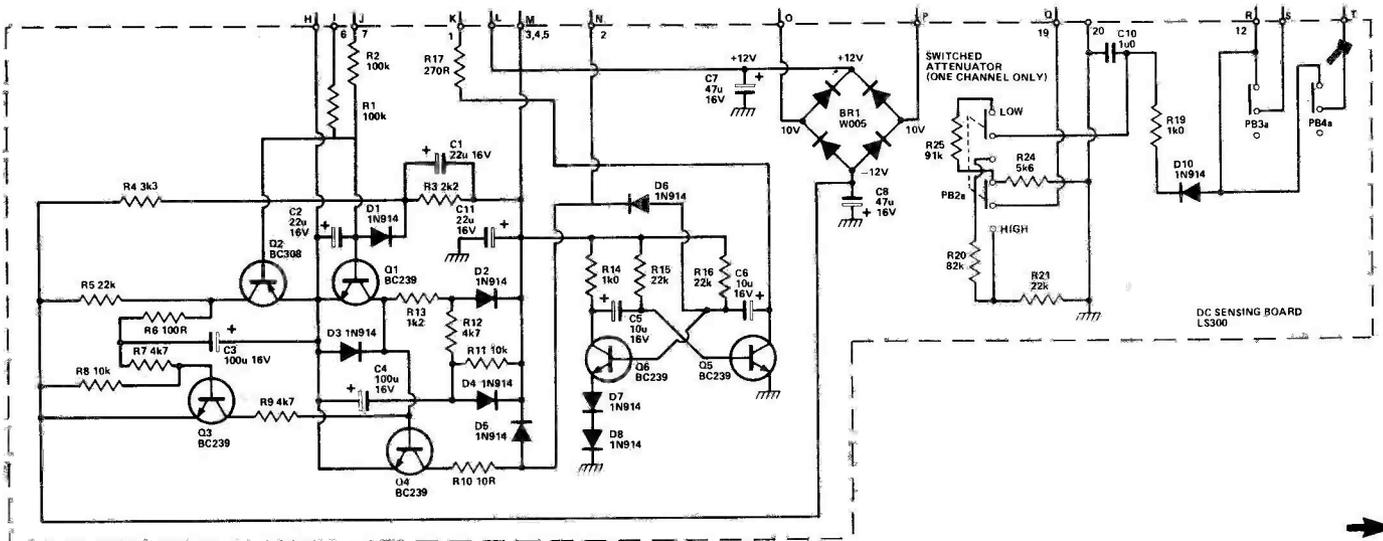

PARTS LIST

POWER AMPLIFIER BOARD (one channel)

Resistors 1/4W 5% unless specified

R1	2k2
R2	47k
R4	56k
R5,6	3k9
R7	1k0
R8	22k
R9	12k
R10,11	100R
R12	120R
R13,14	220R
R15	10R 2W
R16	10R 1W

(R3 has been deleted from this design)

POTENTIOMETER

PR1	1k0 linear preset
-----	-------------------

CAPACITORS

C1	10u 16V tantalum
C2	33p 160V polystyrene
C3	47u 63V electrolytic
C4	5n6 160V polystyrene
C5,9	15p 160V polystyrene
C6,7	100u 63V electrolytic
C8	10n 100V mylar
C10,11	100n 250V polyester

SEMICONDUCTORS

Q1,2	2SA872
Q5	2SB646
Q6,7	2SB666
Q8	2SK133
Q9	2SJ48
D1-3	1N4002
ZD1,2	1N5858

(Q3,4 have been deleted from this design)

MISCELLANEOUS

L1 12 turns 16 swg enamelled copper wire (around R17), PCB, 8 way 0.2" plug connector, 4 x 1 3/4" capacitor clips, 2 x 8 way flying lead sockets and 16 connector pins.

OFF-BOARD COMPONENTS

RESISTORS 1/4W 5%

R17	470k
-----	------

CAPACITORS

C12	1u0 250V polycarbonate
C13,14	10,000u 70V electrolytic
C15	3300u 25V electrolytic

SEMICONDUCTORS

BR2	PW02 (6A 200V)
LED 1	5 mm. red

DC SENSING BOARD

RESISTORS All 1/4W 5%

R1,2	100k
R3	2k2
R4	3k3
R5,15,16	
21,22	22k
R6	100R
R7,20,23	47k
R8,11,27	10k
R9,12	4k7
R10	10R
R13	1k2
R14,19	1k0
R17	270R
R24	5k6
R25	91k

(R18,26,27 are on other channel)

CAPACITORS

C1,11	33u 16V electrolytic
C2	4u7 16V electrolytic
C3,4	100u 16V electrolytic
C5,6	10u 16V electrolytic
C7,8	47u 16V electrolytic
C9,10	1u0 100V electrolytic

SEMICONDUCTORS

Q1,3,4,5,6	BC239
Q2	BC308
D1-10	1N914
BR1	W005 1A 50V

MISCELLANEOUS

PCB, 21 way 0.2" plug strip (multiples of 14 and 7 way).

BAR GRAPH DISPLAY (one channel only)

SEMICONDUCTORS

IC1	U257
IC2	U267
LED 1-6	Flat LED, green
LED 7	Flat LED, yellow
LED 8-10	Flat LED, red

MISCELLANEOUS

T1	40-0-40, 10-0-10, 250 VA mains transformer
RLA1	12V 4 pole Continental relay, 700R coil

1/4" stereo jacket socket, spring-loaded terminals (4 red, 4 black), 2 x 3A fuses and chassis mounting holders, filtered (or unfiltered) 3A mains socket, stereo phono socket, 2 way 20mm SUF switch (input), mains on/off switch, 4 pole C/O push button switch, 3 x 2 pole C/O push button switches.

primaries. Under no circumstances should you ever rely solely on the fuse in the mains plug.

Check that the mains fuse is in place. Do not connect the circuit boards to their respective PSUs yet. Switch on, and check all the various DC voltages with a meter. And make sure that you have clearly marked the positive and negative connections, as reversing the low impedance power connection to the output modules is one of the most certain ways of destroying the whole lot. The main PSU capacitors should be carefully checked for correct polarity, as 10,000uF on the ceiling makes a very unpleasant mess. Remember to ground the centre point of the PSU's.

DC Offset Protection

The first part of the circuit to verify is the output pro-

tection unit and switch-on delay PCB. Connect this to the PSU and switch on.

The result should be a flashing LED, which extinguishes after 5 S to the accompaniment of the speaker relay clicking 'in'. You can verify this by placing an ohmmeter across the relay terminals if you like. If not, ground the input to the offset detector (the connection from the amplifier output), since stray pickup could conceivably cause the failsafe to trip.

Failing this, an analysis of the circuit board construction and test voltages is the only solution. Make certain the diodes are in the correct way round, since this is one of the more frequent causes of trouble.

Assuming that a combination of sound construction/thorough debugging/luck leads to a correctly functioning circuit, check that the application of a DC offset to

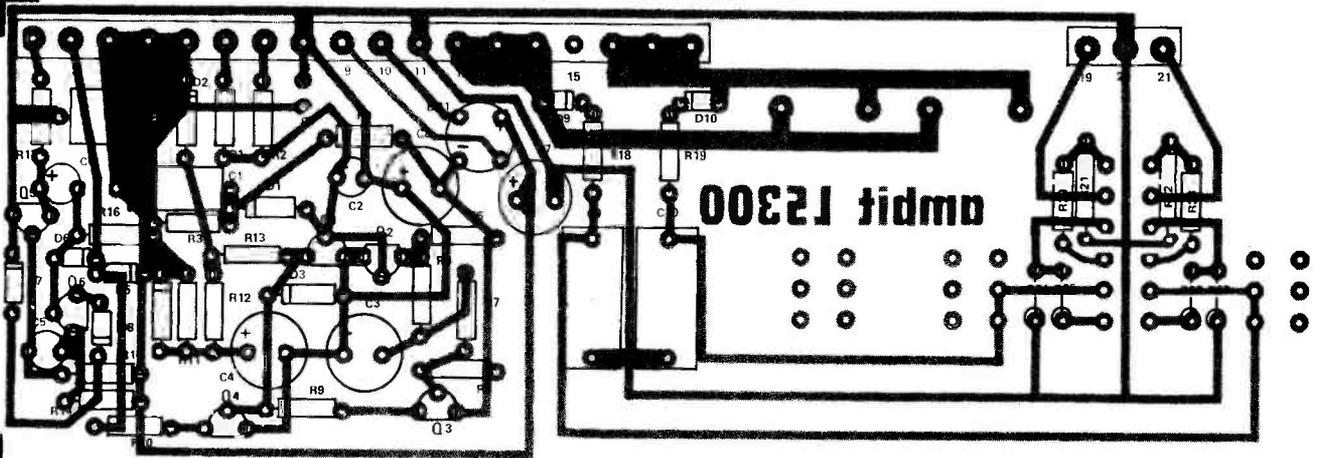


Fig.1. Component overlay of the DC Sensing Board. Note capacitor polarities.

the input (via the limiting resistor) (from a 1V5 battery for example) causes the relay to drop out and the LED to start flashing again.

Make certain that the loudspeaker connections are wired via the normally open contacts, since the circuit is fail-safe ie if the power to the relay is cut, the speaker path is discontinued.

Output Bargraph

Connect the power to the output bargraph driver PCB. With no output from the power amplifiers, inject a signal from your finger onto the input of the bargraph board. Depending on your conductivity and the amount of hum about, some or all of the LEDs should light. The input attenuator switch selects a potential divider from the rectified output of each channel, nominally set for FSDs of 10 W and 100 W, but if you are proposing to use the amplifier with speakers rated at less than 100 W (and most of them are) then set the attenuator to read the appropriate FSD. Simply adjust the potentiometer ratios pro-rata. The U257/U267 use logarithmic steps, covering a 26 dB range.

Home Welding

Now comes the hairy bit. +60 V on the ends of 10,000uF reservoirs is not to be trifled with, so make certain the first connection you make to the amplifier modules is the correct one. Before attempting this, switch off and discharge the main PSUs via a suitable resistor, such as 2k/2 W.

A quick dab with the screwdriver across the terminals of 10,000uFs will lead to a damaged screwdriver and a fresh set of underwear.

Fit a milliammeter in series with one of the supply leads (use one in each arm of the supply if you have two meters) and test one module at a time. Set the output quiescent preset to minimum resistance (minimum bias current) and connect the output to the DC offset sensing circuit. A load of 8R/10 W should be connected across the appropriate output terminals. Select the correct output via the panel switch. Do not connect direct to your favourite speakers at this stage. A 3 A fuse in series with the load is not a bad idea during testing. This should be removed once you are satisfied that all is well since the resistance of such fuses is a serious contribution to some of the distortions otherwise avoidable in high power audio amplifiers.

ETI

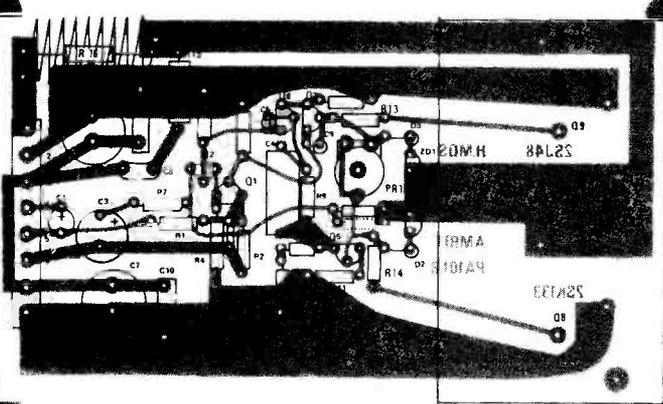


Fig.2. Component overlay of the Power Amplifier Board. Coil L1 is wound round R16.

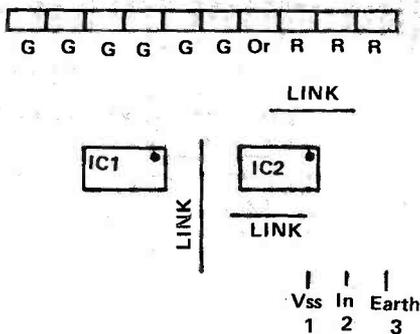


Fig.3. Component overlay of the Bargraph Monitor Board, using only two ICs.


BUYLINES

A complete kit for the HMOS Power Amplifier is available for £155 + VAT from Ambit International, 200 North Service Road, Brentwood, Essex. The PCBs, metalwork, etc can be bought separately. Contact Ambit for latest prices.

MICROTAN 65


£69
plus VAT

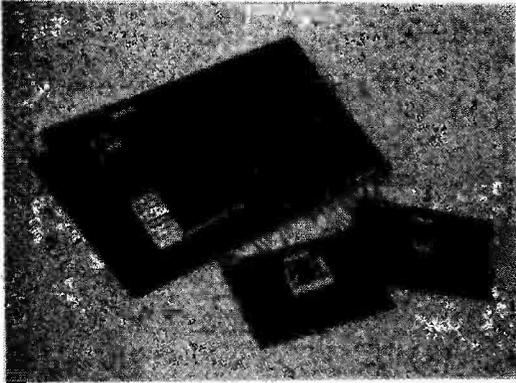The Microcomputer that thinks it's a Mini



The MICROTAN kit has won widespread acclaim for it's super presentation.

High quality, plated thru' hole printed circuit board, solder resist and component legends. Full set of I.C. sockets. 64 way D.I.N. edge connector. 6502 microprocessor. 1K monitor TANBUG. 1K RAM for user programme, stack and display memory. VDU alphanumeric display. Intelligent keyboard socket. A4 MICROTAN 65 system file binder. 136 page, bound, A4 size users hardware/software manual with constructional details and sample programmes. Logic and discrete components to fully expand MICROTAN 65.

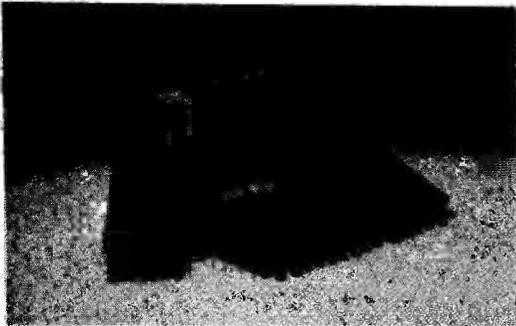


TANEX

from £43.00 plus VAT

Fully expanded TANEX offers; 7K RAM, 6K ROM, 8K MICROSOFT BASIC, 32 parallel I/O lines, two TTL serial I/O ports, a third serial I/O port with RS232 20mA, full modem control and 16 programmable baud rates, four 16 bit counter timers, cassette interface, data bus buffering and memory mapping.

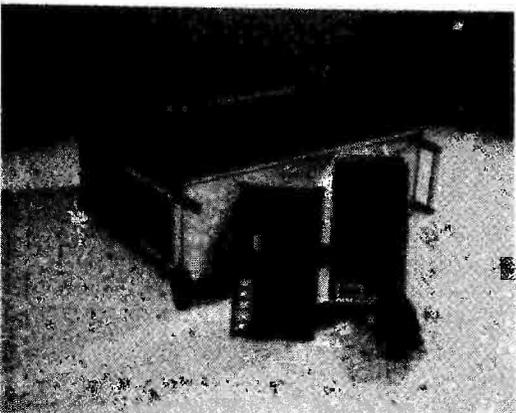Ready built the mini-mother board has two 64 way female connectors, a 4 way power supply connector and a reset switch on board. It is used to connect MICROTAN to TANEX, and will fit inside the mini system rack. **£10.00 plus VAT.**



Full System Rack

from £49.00 plus VAT

For the man that has everything! 19 inch wide system rack which accepts MICROTAN 65, TANEX, TANRAM, **NINE FURTHER EXPANSION BOARDS**, TANDOS AND THE SYSTEM POWER SUPPLY.

Available in many formats e.g. Individual module front panels, full width hinged front panel, back panel with or without connectors, etc.

We have produced a mini-rack which accepts MICROTAN 65 and TANEX, it has an integral power supply, just plug it into the mains and away you go! Finished in Black/Tangerine/Brushed aluminium, it gives your mini-system the professional finish. **£43.00 plus VAT**



Full ASCII keyboard

£49.00 plus VAT

The ASCII keyboard includes a numeric keypad and ribbon cable connector. Available only as fully built and tested.

Cabinet available at **£20.00 plus VAT.**


TANGERINE

COMPUTER SYSTEMS LIMITED

ETI AUGUST 1980

- An excellent kit
- The concept of TANBUG is excellent
- Rock steady VDU
- The extremely reasonable cost has not been achieved by skimping on design
- A gem of a product
- An excellent introduction to 6502 based systems

- A 6502 based microcomputer.
- Superb 1K monitor TANBUG.
- Expansion boards to make a full system.
- Fully socketed
- 1K RAM for user programme, stack and display memory
- 136 page software/hardware users manual, with example programmes and A4 size!
- Intelligent keyboard socket, accepts 20 key keypad or full ASCII keyboard
- Full alphanumeric video display on an un-modified domestic TV - makes programming much easier
- Optional lower case pack £9.48 + vat
- Optional chunky graphics pack £6.52 + vat

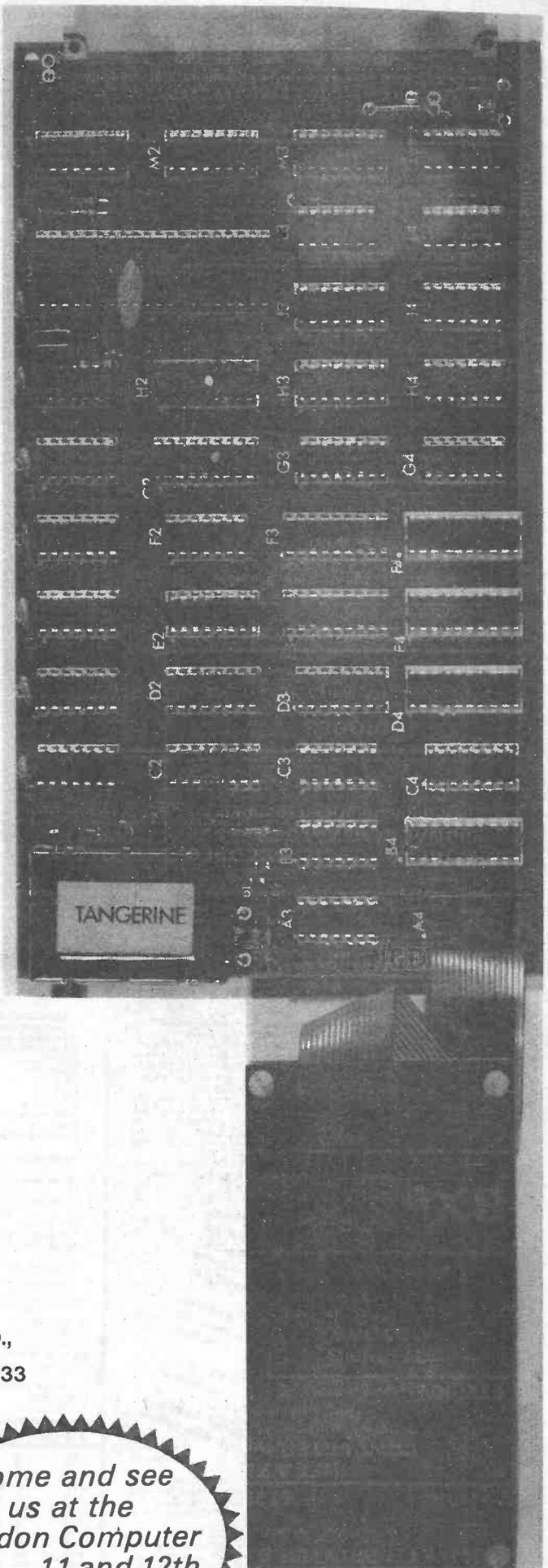

**BROCHURE AVAILABLE
ON REQUEST, 12p stamp**



**TANGERINE COMPUTER SYSTEMS LTD.,
FOREHILL, ELY, CAMBS. Tel: (0353) 3633**

NAME
ADDRESS

*Come and see
us at the
London Computer
Fair — 11 and 12th
July*

Greenbank

Greenbank Electronics
(Dept T8E) 92 New Chester Road, New Ferry
Wirral, Merseyside L62 5AG
(Tel 051 645 3391)

TERMS, VAT, C.W.O. Cheques etc payable to Greenbank Electronics and crossed. Add VAT to all prices at 15% except where stated otherwise. Post etc. UK 35p (+5p VAT = 35p) per order. Export: NO VAT but add 35p (Eire), 75p (Europe) and £2.50 elsewhere. Access: Barclaycard, Visa, telephoned orders accepted. (P.O.s, universities, gov. dept, etc can telephone their orders for immediate despatch on account.)



UV EPROM ERASERS



Two easy to use units designed for both the professional and amateur UV-prom user.

Features:

- Can erase up to 14 proms.
- Special short wave ultraviolet tube.
- Erase time variable between 5 and 50 minutes steps (preventing over exposure which may shorten prom life).
- Sliding tray carries proms on conductive foam.
- Safety interlock switch prevents the timing circuit from operating and switching on the tube with the tray open.
- "Mains on" and "Tube On" indicators.
- Smart textured case.
- Complete instructions supplied.

Supplied complete with mains plug and flex.

Model UV141: Price £77.70

Also available without timer as

Model UV140: Price £61.20

PROM WASHING SERVICE: 50p each prom

COMPUTER BOARDS

The following is an extract from our leaflet 'MPA', which is available free on request (a 9" x 6" SAE helps, but is not essential). See Microprocessor section to the right for board prices.

For many people the wide choice of micro-processors now available presents a difficult choice. To understand any particular microprocessor in depth a development system is almost essential, however in the past to understand more than one several separate development systems have had to be purchased.

The reason that separate systems, one for each processor, have been necessary is due to the fact that individual microprocessors have their own individual features: in one case to access memory a separate read strobe and write strobe is required, in another a 'read/write' line is used in combination with a combined strobe called 'valid memory address and phi-2'. With some processors, the same address bus can be used for both memory and input/output ports, under the control of a 'memory request' or an 'input/output request' control line.

Naturally, if a development system takes advantage of any of the particular unique features of any particular microprocessor, this makes it more difficult to graft some other unrelated microprocessor onto the same bus at a later date. A Universal Micro System provides a basic bus structure on which any one microprocessor can be connected. The system uses a CPU (Central Processor Unit) card which is separate from the rest of the system, and this allows the same memory and interfaces to be retained when a different MPU is used.

The basic system bus consists of data and address buses together with read and write strobes. By locating the data input (Keyboard) and output (VDU) in the memory space then such chips as the 8080/280 family, which normally use input/output ports, can now be used without any fundamental change to the bus (and as a bonus, users of these MPU's have all the ports entirely free for their own purposes).

The range of p.c.b.'s includes boards to implement a memory-mapped VDU, cassette interface, keyboard interface, PROM programmer, and a number of RAM and ROM cards. All the cards are of International Size 114 x 203mm (4 1/2" x 8") except for the larger power PSU. A power supply card. This latter card is sized so that it can be bolted to the side of a standard 4" chassis module which is then compatible with the other cards. The cards have a standard 43-way edge connector, with one position used for polarisation. We do not propose to defend the (relatively) small number of bus connections (42), against such standards as the 'S100' or 'Corona'. The S-100 bus, as it originated in America, is bigger and more expensive. In the same way, a Ford 'Granada' is bigger and more expensive than a 'Corona', but it doesn't mean a 'Corona' is a better car than a 'Granada' - it may even be better value.

The International Microprocessor Architecture (IMA) is a 13U 19" rack and a variety of other cards. The IMA is a firm 'R.S.' product. It is designed to complete the system. It is a complete assembly computer system. It is a complete computer system. It is a complete computer system.

NEW! 'IBUS-1.1'
Low-cost commercial quality computer back board, 13" x 4 1/2" x 1 1/2" approx., for the International Standard (114x203mm) cards. Although intended for the 86-way double sided connector, it can be used with the 43-way connector specified for the computer boards we advertise. (Pin 37 is used for polarization.) Takes up to 13 cards on 1" lines and provides for 4 power rails, 58 parallel address/data etc. bus lines and 3 'daisy chains'.

Epoxy glass, tinned, price £11.50. More details in our free leaflet 'IBUS-1.1'. Existing enquiries: Note Leaflets have been delayed, but will follow soon.

Often these cards are used in a system which has a microprocessor, a keyboard, a VDU, a power supply, and a cassette interface. The cards are designed to be used in a standard 4" chassis module. The cards are designed to be used in a standard 4" chassis module. The cards are designed to be used in a standard 4" chassis module.

Further details on request. Further details on request.

Further details on request. Further details on request. Further details on request. Further details on request. Further details on request. Further details on request. Further details on request. Further details on request. Further details on request. Further details on request.

Further details on request. Further details on request. Further details on request. Further details on request. Further details on request. Further details on request. Further details on request. Further details on request. Further details on request. Further details on request.

Further details on request. Further details on request. Further details on request. Further details on request. Further details on request. Further details on request. Further details on request. Further details on request. Further details on request. Further details on request.

CMOS

These cut prices for Amateur Users and Export. Note: industrial users - quantity prices available. Mostly Motorola, RCA

4001 18p	4042 80p	4096 95p	4451 £3.81	4549 £4.38
4002 18p	4043 90p	4097 £3.40	4461 £3.33	4552 £14.85
4003 25p	4044 90p	4098 £1.20	4462 £4.41	4553 £4.50
4006 95p	4045 £1.65	4099 £2.00	4490P £4.20	4554 £1.38
4007 18p	4046 £1.10	4100 £2.20	4490VP £3.14	4555 79p
4008 80p	4047 £1.00	4101 £1.32	4500 £6.95	4556 72p
4009 40p	4048 55p	4102 £1.80	4501 29p	4557 £3.26
4010 50p	4049 45p	4103 £1.00	4502 £1.20	4558 £1.25
4011 25p	4050 49p	4104 £1.90	4503 70p	4559 £4.38
4012 18p	4051 80p	4105 99p	4505 £5.71	4560 £2.50
4013 50p	4052 80p	4106 90p	4506 50p	4561 81p
4014 84p	4053 80p	4107 60p	4507 55p	4562 £9.60
4015 84p	4054 £1.50	4108 £4.70	4508 £2.90	4566 £1.59
4016 45p	4055 £1.25	4109 £1.00	4510 99p	4568 £2.38
4017 80p	4056 £1.30	4110 £3.00	4511 £1.50	4569 £2.50
4018 40p	4059 £6.00	4114 £2.50	4512 80p	4572 40p
4019 45p	4060 £1.15	40181 £3.39	4514 £2.65	4580 £4.77
4020 99p	4062T £10.00	40182 £1.40	4515 £3.00	4581 £2.62
4021 £1.10	4063 £1.20	40183 £1.40	4516 £1.10	4582 £1.14
4022 £1.00	4066 95p	40183 £1.40	4517 £4.48	4583 90p
4023 27p	4067 £4.50	40184 £1.18	4518 £1.00	4584 90p
4024 50p	4068 27p	40257 £1.48	4519 80p	4585 £1.27
4025 27p	4069 27p	4160 98p	4520 £1.00	4597 £2.44
4026 £1.30	4070 30p	4161 90p	4521 £2.50	4598 £2.98
4027 50p	4071 25p	4162 98p	4522 £1.11	4599 £6.95
4028 84p	4072 25p	4163 90p	4523 £1.30	4600 £1.75
4029 99p	4073 25p	4174 90p	4527 £1.50	
4030 55p	4075 25p	4175 1.15	4528 £1.30	
4031 £2.00	4076 £1.07	4194 £1.16	4529 £1.20	
4032 £1.31	4077 29p	4408 £3.37	4530 70p	
4033 £1.80	4078 29p	4409 £3.37	4531 £1.45	
4034 £2.00	4081 27p	4410 £3.30	4532 £1.30	
4035 £1.10	4082 27p	4411 £10.72	4534 £5.60	
4036 £2.95	4085 74p	4412P £1.93	4536 £3.69	
4037 £1.15	4086 72p	4415V £5.24	4537 £26.10	
4038 £1.20	4089 £1.38	4422 £5.66	4538 97p	
4039 £2.95	4093 80p	4453 £12.30	4539 97p	
4040 £1.00	4094 £2.50	4454 £4.54	4541 £1.19	
841 80p	4095 95p	4455 £3.81	4543 £1.80	

74C

74C00 28p	74C14 19p	74C15 19p	74C16 19p	74C17 19p	74C18 19p	74C19 19p	74C20 28p	74C21 28p	74C22 28p	74C23 28p	74C100 28p
-----------	-----------	-----------	-----------	------------

MODULATORS

UM1111 E36 VHF Ch.36 Vision Modulator £2.50	AC 5221S 5V/10A £99.90
UM1231 VHF Ch.35 Vision Modulator wide bandwidth (for computers etc) £4.70	AC 5221S 5V/5A, 12V/1A, -12V/1A, 5V/0.1A
UM1263 FM Sound Sub-carrier Modulator £2.50	AC 5215 5V/20A £99.20
	AC 9421S 5V/10A, 12V/2A, -12V/2A, 5V/0.1A £126.50

SWITCH MODE PSUs


6800 MPU £6.55	6802 MPU £9.95	6810 (128 x 8 RAM) £2.97	6810 (128 x 8 RAM) £3.75	6820 6821 PIA £3.96	6850 AIC £3.68	6860 AIC £3.04
6800 MPU £6.55	6802 MPU £9.95	6810 (128 x 8 RAM) £2.97	6810 (128 x 8 RAM) £3.75	6820 6821 PIA £3.96	6850 AIC £3.68	6860 AIC £3.04
6800 MPU £6.55	6802 MPU £9.95	6810 (128 x 8 RAM) £2.97	6810 (128 x 8 RAM) £3.75	6820 6821 PIA £3.96	6850 AIC £3.68	6860 AIC £3.04

MICROPROCESSORS

81LS95/5/7/8 £1.40	75491 LED driver 90p	75492 52p	75493 52p	75494 52p	75771 52p	75
--------------------	----------------------	-----------	-----------	-----------	-----------	----

CMOS LOGIC TESTER

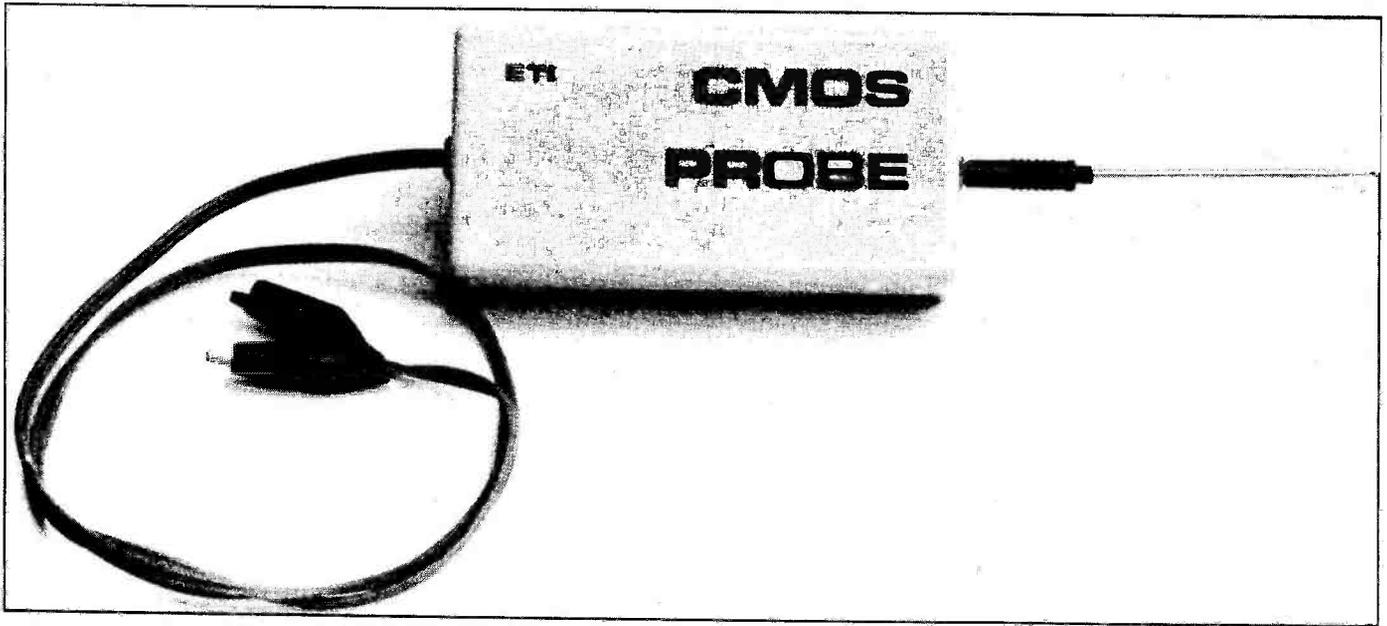Check you CMOS voltage levels with this economical piece of test gear.




This unit, powered from the equipment under test, enables the voltage levels of CMOS circuitry to be checked to determine if they are within the valid logic range. Two LEDs are used to indicate high and low logic levels, invalid levels and open circuit conditions.

1, 0, Or Just Out To Lunch

With no input, the internal current source is held off and neither LED is illuminated. One of the two LEDs will light to indicate a valid input signal. When the input is between thirty and seventy percent (CMOS logic thresholds) of the supply voltage, both LEDs will illuminate. Both LEDs are also on for an oscillating input. Although no provision has been made to detect single pulses, a simple 555 monostable circuit would accomplish this. If triggered from pin 10, IC2, the unit would detect both positive and negative going transitions.

2 Chips, 2 LEDs

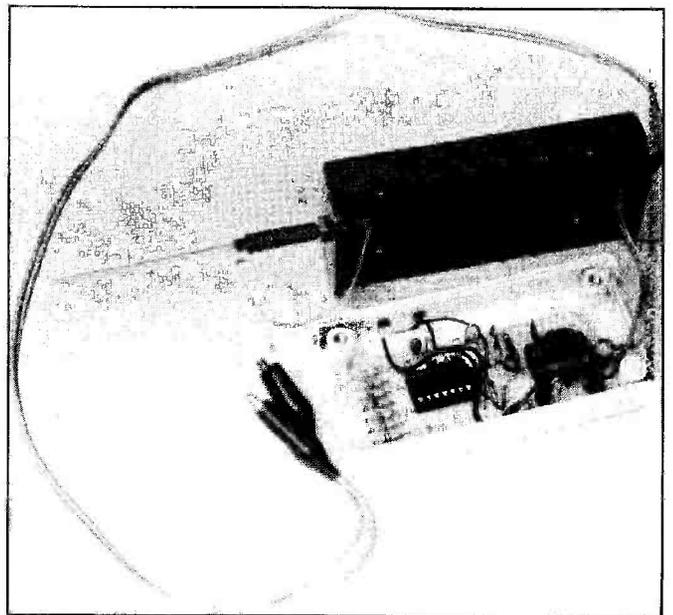Use of a quad comparator and a Schmitt input quad NAND package enable sophisticated performance to be obtained from a handful of chips and transistors. Use the transistors specified, as they are chosen for their high minimum current gain. Any type or colour LEDs can be



The inside story - the tester's board exposed.

used. Note that the LED current is set by R14 which can be reduced if you require a brighter display. With the value specified, a current of between 10 mA and 15 mA flows depending on the supply voltage. The use of a 'constant current' driver stage avoids the problem of excessive drive current at high supply voltages.

Although CMOS is characterised to operate at 3 V, it was felt that the extra circuitry required to ensure reliable operation of the unit at this level would have been uneconomical. The prototype gave good results at a supply level of between 4V5 and 18 V.

If you use our PCB design, you can't go wrong. Of course, any method of construction may be employed. Keep connecting leads short, especially around the comparator inputs. We used tantalum capacitors for the higher values. They are small, efficient and worth the extra cost. Use 35 V working types.

We were able to fit our unit in a small verobox by removing one of the internal pillars. They come out quite cleanly if you snip around them with a stout pair of wire cutters. However you build it, the CMOS logic probe will soon become a valuable addition to your range of test gear and help you get your projects up and running in double quick time.

PARTS LIST

Resistors	
R1,4,6,11	120k
R2,3,5,7,8	100k
R9	470k
R10	1M0
R12	22k
R13,15,16	47k
R14	82R
Capacitors	
C1	10u 35V tantalum
C2	4u7 35V tantalum
C3	10n ceramic
C4	22u 35V tantalum
Semiconductors	
IC1	LM339
IC2	4093B
Q1	BC477
Q2,3	BC184L
D1-D4	1N4148
LED 1,2	any LED
Miscellaneous	
Verocase 202-21027E, PCB.	

HOW IT WORKS

Valid voltage levels for CMOS operation are below 30% and above 70% of the supply voltage. This circuit uses four comparators to determine whether or not an input voltage is within the valid ranges and its polarity. There is also circuitry to detect an open circuit condition.

Gate IC2d is connected as an oscillator running at between 1 kHz and 5 kHz, depending on component tolerances and supply voltage. Its output is capacitively coupled to diode pump D1,2. A voltage is developed across C1 about 3-15 V more positive than the positive supply voltage and this provides the positive supply for the LM339 quad comparator. IC1d is used to compare the voltage at the probe with a bias voltage slightly greater than the positive supply. When the probe is unconnected, IC1d's output is off. When the probe is connected to a voltage within the supply range, IC1d's output (an uncommitted collector) goes low, sink-

ing current through R12 and turning on constant current source Q1. In summary, when the probe is unconnected Q1 is off and neither LED can light.

Comparators IC1a,c are connected as a conventional window comparator whose output is high when the probe input voltage is invalid. This signal, inverted by IC2a, causes IC2b,c to go high turning on Q2,3 and illuminating both LEDs. An oscillating unit will also cause both LEDs to illuminate.

With a valid input voltage, IC2a output will be high and LED 1 or 2 will light to indicate the polarity of the input signal. Comparator IC1b is used to determine input polarity, comparing it with a mid-supply voltage at the junction of R2,3. Note that when the probe is connected to a logic '0', the gate under test sinks about 50 uA max from the auxiliary positive supply and associated bias resistor, R9.

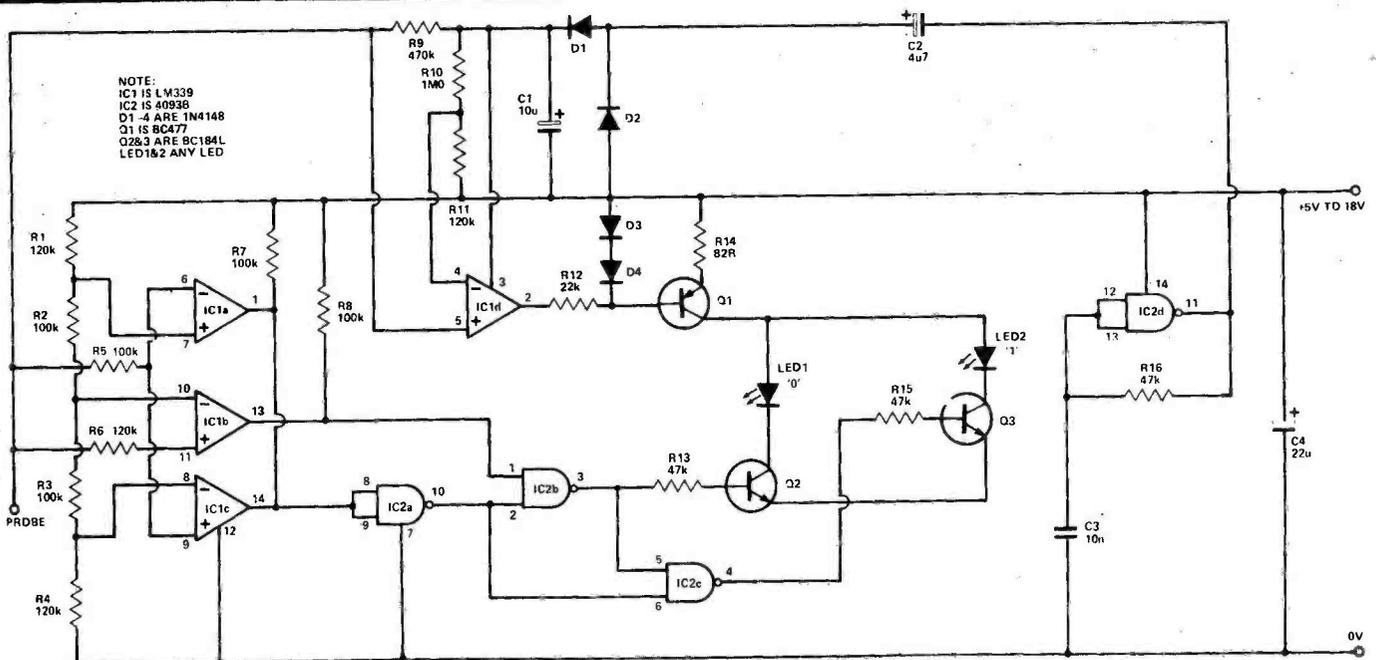


Fig.1. Circuit diagram.


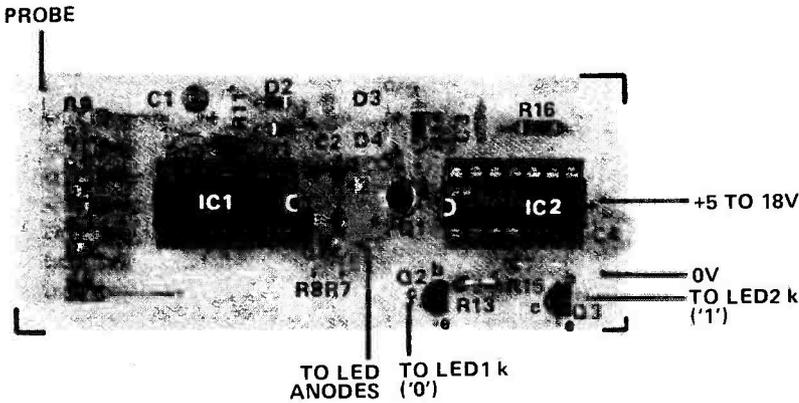


Fig.2. (above) Component overlay. Note the orientation of IC1 and IC2. Board construction is straightforward.

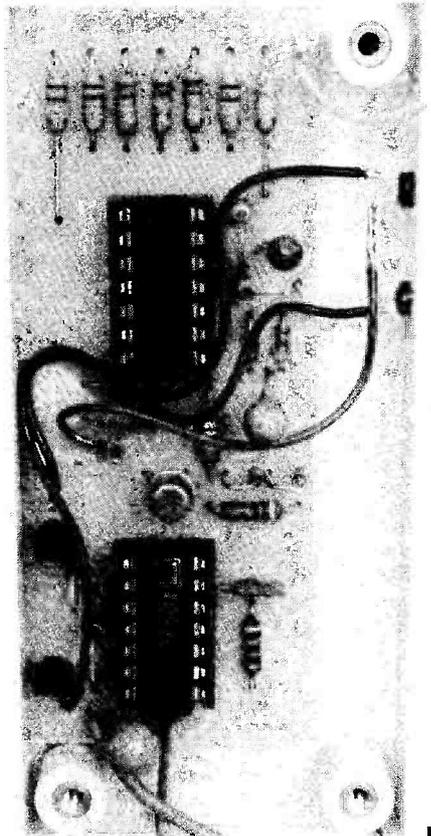The completed board (right) installed in the case. The two LEDs push-fit into the side of the case.



BUYLINES

All the components should be readily obtainable. In case of difficulty, try Watford, Marshall's or Technomatic or check with other suppliers advertising in ETI.

ETI

STEVENSON

Electronic Components



AT LAST! OUR NEW 1980/81 CATALOGUE IS NOW AVAILABLE.

Our new catalogue is just packed with components. It contains 100 illustrated pages detailing over 3000 line items. These include:

- | | | |
|-------------------|--------------------|--------------|
| Amplifier modules | Connectors | Meters |
| Books | Desoldering tools | Ni-cad cells |
| Breadboards | Drills | Op-amps |
| Cabinets | Etching equipment | Rams |
| Cables | Heatsinks | Resistors |
| Capacitors | IC sockets | Switches |
| CMOS | Knobs | Tools |
| Crossovers | Mains Transformers | Triacs |

Included with our catalogue you will receive:

- a reply paid envelope for your first order.
- a mail order form to facilitate rapid despatch
- a 50p discount voucher to be used against mail order purchases over £10.00.

Available now by post from the address below at a cost of **50p**

Due to stock and administrative problems over the last few months, the quality of our service had suffered considerably. These problems have now been resolved and we are confident that we can now offer the quality of service we had been accustomed to. We wish to convey our apologies to any customers who have been inconvenienced.

All prices include VAT. Please add 50p carriage on orders below £15. Contact our sales office with your requirements on: **01-464 5770**



OPTO

Red	0.125in	0.2in	
	TIL209	TIL220	10p
Green	TIL211	TIL221	16p
Yellow	TIL213	TIL223	16p
Chips	3p	3p	

DISPLAYS

DL704	0.3in	CC	130p
DL707	0.3in	CA	130p
FND500	0.5in	CA	100p

TRANSISTORS

AC127	25p	BC547	8p	TIP30C	70p
AC128	25p	BCY71	18p	TIP2955	65p
AD161	40p	BD131	35p	TIP3055	60p
AD182	40p	BD132	35p	ZTX107	12p
BC107	10p	BD139	35p	ZTX108	12p
BC108	10p	BD140	35p	ZTX109	12p
BC109	10p	BFX29	25p	ZTX300	14p
BC147	9p	BFX84	26p	ZTX500	15p
BC178	16p	BFY50	23p	2N3053	25p
BC182	10p	BFY51	23p	2N3055	55p
BC182L	10p	MJ2955	98p	2N3702	9p
BC184	10p	TIP29C	60p	2N3703	9p
BC184L	10p			2N3704	9p
BC212	10p	1N914	4p	2N3709	9p
BC212L	10p	1N4001	4p	2N3819	22p
BC214	10p	1N4006	7p	2N3905	10p
BC214L	10p	1N4006	7p	2N5777	50p

LINEAR

741	18p	LM324	52p	MM57160	650p
747	70p	LM339	55p	NE531	140p
748	40p	LM348	100p	NE555	23p
7106	850p	LM377	170p	NE556	60p
CA3046	70p	LM378	230p	NE567	120p
CA3080	75p	LM380	80p	RC4136	100p
CA3130	100p	LM381	140p	SN76477	230p
CA3140	60p	LM382	120p	TBA800	80p
LF347	170p	LM386	90p	TBA810	110p
LF351	45p	LM387	120p	TDA1022	630p
LF353	90p	LM1458	40p	TL081	45p
LF356	90p	LM1830	180p	TL082	85p
LM301A	35p	LM3900	60p	TL084	125p
LM318	85p	LM3909	72p	XR2206	390p
		LM3911	120p	ZN414	80p
		LM3914	320p	ZN425E	475p
		LM3915	320p		

PACKS

Specialty designed packs intended for development work at a considerable saving.

• 10 resistors. 10 of each value 4.7ohm to 1 Mohm a total of 650 resistors. 530p each

• 10 resistors. 10 of each value 4.7ohm to 1 Mohm a total of 650 resistors. 875p each

• Presets. Pack of 5 of each value from 100ohms to 1 Megohm. a total of 65 presets. 390p each.

• LED's. Pack containing 10 of each colour LED 0.2 size. Total of 30 LED's chips. 450p each

• Zeners. Pack of 5 of each value from 2U7 to 33V A total of 130 zeners 880p each.

CMOS

4001	25p	4025	25p	4072	25p
4002	25p	4026	150p	4081	30p
4006	95p	4027	50p	4082	30p
4007	25p	4028	90p	4085	85p
4011	30p	4029	110p	4093	80p
4013	45p	4040	110p	4095	110p
4015	85p	4042	85p	4510	90p
4016	48p	4046	110p	4511	100p
4017	80p	4048	60p	4518	90p
4018	90p	4049	50p	4520	110p
4020	110p	4050	50p	4527	165p
4022	100p	4052	80p	4528	100p
4023	25p	4060	120p	4532	125p
4024	60p	4066	63p	4543	170p
		4068	25p	4583	80p
		4069	25p	4585	115p
		4070	25p		
		4071	25p		

SKTS

8 pin	9p	22pin	20p
14pin	11p	24pin	22p
16pin	12p	28pin	26p
18pin	16p	40pin	38p
20pin	18p		

SWITCHES


TOGGLE			
Standard	SPST	40p	DPDT 55p
Miniature	SPDT	80p	DPDT 90p
Subminiature	SPST	65p	DPDT 85p
SLIDE	Standard	DPDT 17p	Miniature 16p each.
PUSH	Push to make	16p	Push to break 22p.

TTL

7400	15p	7447	65p	74123	50p
7401	15p	7448	65p	74125	60p
7402	15p	7472	35p	74126	60p
7404	16p	7473	38p	74132	70p
7406	38p	7474	36p	74141	95p
7408	22p	7475	40p	74145	90p
7410	18p	7483	80p	74150	110p
7413	35p	7485	80p	74157	80p
7414	35p	7486	35p	74164	120p
7415	35p	7490	45p	74165	120p
7416	35p	7492	55p	74174	100p
7417	35p	7493	45p	74175	95p
7420	16p	7494	70p	74190	100p
7427	30p	7495	70p	74191	100p
7430	30p	7496	70p	74192	100p
7432	35p	74121	45p	74196	100p

76 College Road, Bromley, Kent BR1 1DE.

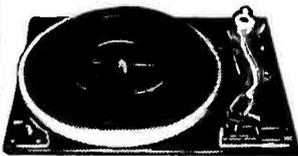EX-STOCK FROM US
J.V.C. BELT DRIVEN TURNTABLE
 WITH STEREO MAGNETIC AUDIO TECHNICA CARTRIDGE



LIST PRICE OVER £50

J.V.C. Turntable supplied complete with Audio Technica AT10 stereo magnetic cartridge. Belt driven

- 'S' shaped tone arm.
- Modern design
- Full size 12" platter.
- Calibrated counter balance weight (0-3 grms).
- Anti-skate (bias) device.
- Size — 12 1/2" x 15 1/4" (approx)

AT ONLY

LIMITED STOCKS £25.99

PLUS VAT £3.89 Post £2.50

GEC HIGH QUALITY STEREO
10 + 10 watt AMPLIFIER
 WITH AM/FM STEREO TUNER
 IDEAL FOR THE HOME

A cancelled export order brings you this offer from the world-famous firm of G.E.C.

AM/FM stereo Tuner Amplifier
 Ready built. Comprising of a tuner/pre-amp. board and separate power supply/power amp. board with wiring diagram.

Rotary Controls: Tuning, on/off volume, balance, treble, bass. Stereo Beacon indicator.
Push-button Controls: Mono, Tape, Disc, A.F.C., F.M. (VHF), L.W., M.W., S.W.

Power Output: 7 watts RMS per channel, at better than 2% THD into 8 ohms. 10 watts speech and music.

Frequency Response: 60Hz-20KHz within ± 3dB.
Tape Sensitivity: Output — typically 150 mv. input — 300 mv for rated output.

Disc Sensitivity: 100 mv (ceramic cartridge)

Radio: FM (VHF) 87.5MHz-108MHz.

Long Wave 145KHz-265KHz.

Medium Wave 520KHz-1620KHz.

Short Wave 5.8KHz-16MHz.

Size: Tuner — 2 1/2" x 15in. x 7 1/2". Power Amp — 2in. x 7 1/2in. x 4 1/2in.

LOW PRICE OFFER



ON/OFF BALANCE, TREBLE, BASS, MONO TAPE Phono AFC FM LW MW SW Tuning. Volume

Fully Guaranteed Ex-Stock

SUITABLE SPEAKERS IN CABINETS PAIR 10 WATTS

£19.95 INC. VAT
 POST £2.50 Pair

ONLY £19.95 + VAT £2.99 CARRIAGE £2.50

CAR STEREO CASSETTE MECHANISM

- ★ Front loading 12 volt transistorised
- ★ Speed & Voltage control
- ★ Ex-equipment — Tested O.K.
- ★ Takes standard C60 cassette

ONLY £7.50

INC VAT POST 80p

5 + 5 Watt Car Stereo Amplifier made for Motorola

- ★ WITH pre-amplifier and M. & Long wave assembly.
- ★ Supplied as two built and tested units.
- ★ R.F. and I.F. stereo preamplifier and radio 4 x 2 x 1".
- ★ 5+5 watt stereo amplifier 12/14 volt 4 x 2 x 1"
- ★ Complete with circuit, data and connection diagrams.
- ★ Limited quantity available, ex-stock.

BRAND NEW ONLY £5 + VAT + VAT Post 50p

BRAND NEW ONLY £5 + VAT BRAND NEW



Henry's

Phone (01) 723 1008/9
 404 Edgware Road, London W2, England I.E.D.



PRO M25 Professional capacitor boom-arm microphone by Eagle.
 A graceful 60 cm boom-arm capacitor studio microphone using a cardioid capsule. A high standard of finish for in-vision use and yet robust enough to withstand long periods between maintenance. Supplied complete with 1 red and 1 black windshield and 6 metres of twin screened cable terminating at the microphone end in an XLR connector.
Impedance: 600 ohms (floating). **Response:** 20-18,000 Hz. **Sensitivity:** — 70 dBV. **Cable:** 6 metres two conductor shielded. **Connector:** XLR 3 I.C. **Battery type:** HP7.

LIST PRICE £37.40
OUR PRICE £19.95 inc VAT POST £1.50

ATARI CARTRIDGES

COMPUTER GAMES


LOW COST SCOPES



Atari Basic Programming. You'll get the basics of computer language and programming. What to say. And how to say it.
£34.50



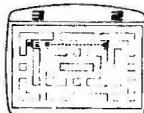
SPACE INVADERS Game Program
 The ultimate Game Programme with 112 game variations including Moving Shields, Zigzagging Laser Bombs, Fast Laser Bombs, Invisible Invaders and 1 & 2 Player Games! This superb cartridge uses the joystick controllers and costs only **£27.50** incl. VAT plus 50p Post and Packing. Order Now!
 Atari with space invaders. **£147.**



It's you and your favourite adversary, pursuing one another through bleak city streets. And blowing each other away with the bazookas on your hoods.
 The first to blast his opponent twenty-five times is the winner.
 So get set for the wildest action since cops discovered robbers. **£15.20.** Orders now taken.



GOLF — Now you can play golf at home, even in stormy weather. There are nine tournament-quality holes on Atari's course, each with a designated par. Total par for this course is 38 points. When playing a one-player game, try to match or beat par. In a two player game, the winner is the player with the least amount of strokes. But swing carefully. There are the usual sandtraps, lakes and trees to avoid. The wrong play may cost penalty strokes.

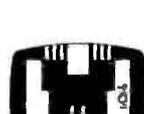


ADVENTURE — Adventure plays like the addictive Dungeons and Dragons fantasy role playing board game and includes the added dimension of video. A wicked magician has stolen an Enchanted Goblet and hidden it somewhere in the Kingdom. The object of the game is to rescue the Goblet and replace it inside the Golden Castle where it belongs — no easy task. Three deadly dragons and a black bat hinder your quest, but scattered throughout the Kingdom are objects to help you slay the dragons and outwit the evil magician. **£22.50** plus 50p P&P.

Also available: Air Sea Battle, Space War, Outlaw, Video Olympics, Breakout, Basketball, Surround, Blackjack, Chess, Backgammon, Bowling, Street Racer, Codebreaker, Hunt & Score, Braingames, Sky Diver.

Free 10:1 Probe
Eleex 5810 5" CRT (12.5MHz)
£181.71 + VAT. Vertical axis, 1 deflection sensitivity, 10mV/div Bandwidth — DC 12.5MHz (between 3dB points), AC 2Hz-12.5MHz (between 3dB points). Rise time 20n sec. Input Attenuator — 12 step — 10mV/div to 50V/div in 1-2-5 sequence calibrated. Time Base — Sweep range 0.5u sec/div to 0.1 sec/div in 12 steps, calibrated with <5 expansion. Fine control. Variable between steps includes TB calibration position.



6MHz OSCILLOSCOPE 3106B
 10mV to 50V/cm in 12 calibrated steps. 0.5 x 8 in 0.1Sec/cm sweep range in 6 calibrated steps plus 12.1 Variable. Magallifier x5. Fully automatic trigger. 90 to 1.5MHz horizontal bandwidth. Our 3106B with 1,600u acceleration voltage, 10 mv/cm sensitivity, auto trigger for the full bandwidth and x5 magnifier giving 1000u/cm. Fastest move time (horizontal) in 15 MHz ac/100uSec; SAE for brochures. Rival 3106C 10MHz 5" crt @ £148 + VAT. S.A.E. for details.

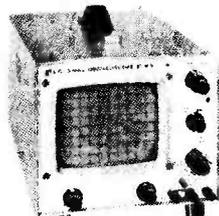

SAE for further details.

5" CRT £132 + VAT



The **OSC3C** is a compact 3" oscilloscope suitable for general laboratory and educational use.

SINCLAIR SC110 (mini scope) £148.20.
PEM 200 £52.20. DM450 £102.46.
DM350 £76.99. PDM35 £34.50.
DM235 £55.80.

Kramer & Co., Dept. ETI 29, October Place, London NW4. Tel: 01-203 2473. Telex 889941. Attn: K7.

Visa, Access, Barclaycard & Company orders accepted. Orders by telephone/telex. Open Mon-Fri (Sunday by appointment only).



AS RECOMMENDED BY ETI. £270.

SARGON 2.5 MODULAR CHESS SYSTEM. Contact for price. ● Unparalleled strengths through entire game. ● Opening Book Library. ● Mate-in-two problems solved in two minutes. ● Seven computer strength levels. ● Instructional mode features. ● Plays by USCF & BCF Rules. ● Audio Alert System. ● Exclusive rank display and position verification. ● Position programming. ● Backspace control. ● Tournament timer. ● Move monitor. ● Battery extra. ● Position storage memory. ● Halt/hint control. ● Changing sides. ● Alphabetic display.



SUPER SYSTEM III — LCD display of International symbols for all moves. ● Plays black/white or itself. ● Timed playing strength 0 secs to 100 hours. ● All International Chess Rules inc. Draw by 3 & 50 move rule. ● Move Counter. ● Set up your own position. ● Position verification. ● Illegal moves rejected. ● Automatic Casting & En-Passant. Computer does much more. **£154.95.** This is the start of a system. To fit your needs optional extras include: Rechargeable Power Pack, LCD Chess Board **£106.95.** Memory Unit to store games for up to 1 year. Plus the world's first Electronic Printer to record moves. SAE for details and prices of accessories.



SENSORY CHESS CHALLENGER. No keys to press. New sensory playing surface automatically tells the computer your every move.

'7 LEVEL' Chess Computer at a realistic price. Plays black, white or itself. Seven levels of play from beginner to expert. Does not permit illegal moves. Castles, Kingside, Queenside. En Passant. Plays opening defenses such as Sicilian, French, Ruy Lopez, Queens Gambit become declined. Analyses as many as 3,024,000 board positions. Establish your own position and watch the computer react. Pawn promotion sides changeable in Mid-Game. Size 12 1/2 x 8 x 1 inch. Mains powered. **VOICE CHESS CHALLENGER** available P.O.A. **£83.95**

We will match any lower price if competitor has stock. SAE for comprehensive chess reports on all the above.

Swiss watches are the finest in the world. Now you can see why.

Swiss watch manufacturers have always been famous for their quality, their design and their style.

And their watches are made to last a life-time.

No one would deny the Japanese their rightful place as the leaders of micro-miniaturisation. The quality of their products is beyond reproach and few can equal their speed and innovation.

But even the Japanese acknowledge the Swiss, the true masters of the art of recording the passage of time.

What better than a famous Swiss watch company combining its skills and know-how with the electronics wizardry of the best Japanese silicon chip house, to produce, we believe, the best digital quartz electronic watch in the world.

BULER MULTI-FUNCTION DUAL TIME ALARM CHRONO WITH COUNT-DOWN

A sensational watch from the famous Swiss company, Montres Buler SA of Bienne, a subsidiary of the giant 'Société pour L'Industrie Horlogerie' group which includes other famous names such as Omega, Tissot and Lanco.

This impressive watch is made from 100% stainless steel with a hard, mineral crystal lens and is water-resistant to 33ft of water. Yet, it is only 7mm thick.

There are 34 different functions in 5 separate modes of operation (Time 1; Time 2; Stop-watch; Alarm; Count-down) and amazingly all 5 modes can be operated independently and at the same time.

The alarm sound is an insistant and effective musical tone to get you up in the mornings, or to warn you your time has expired (count-down operation).

The stop-watch counts to 12 hours in second stops and has 1st and 2nd past the post split and lap timing modes.

The second time zone can be set to any part of the world.

There are 7 display indications and 6 digits.

The day of the week can even be in English, French, or German, whichever you prefer, and the strap is fully adjustable for all wrists. There is of course a back-light and the battery lasts for approximately 1½ years.

GUARANTEE

Like all products sold by Metac this fine Buler watch is guaranteed for one year. And, we even offer a 10-day money back offer.

24-HOUR DESPATCH

This is another unique Metac service.

Unlike other companies we don't believe you really want to wait 28 days for your watch, so we have opened a special 24-hour despatch centre.



Simply complete and return the coupon and this sensational new watch will be safely and securely on its way to you within 24-hours of your order being received.

Callers may buy from our shops in:
LONDON: 327 Edgware Road, W.2.
DAVENTRY: 67 High Street.
NORTHAMPTON: 11 St. Giles Square.
Credit Card Holders may telephone 03272-5883/4/5 or 01-723 4753.

Metac

ELECTRONICS & TIME CENTRES
47 High Street, Daventry, Northants.

ETI AUGUST 1980

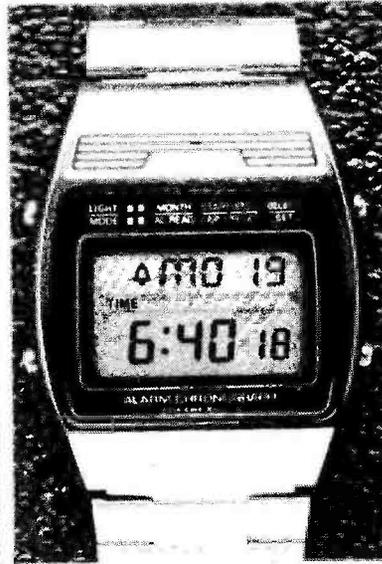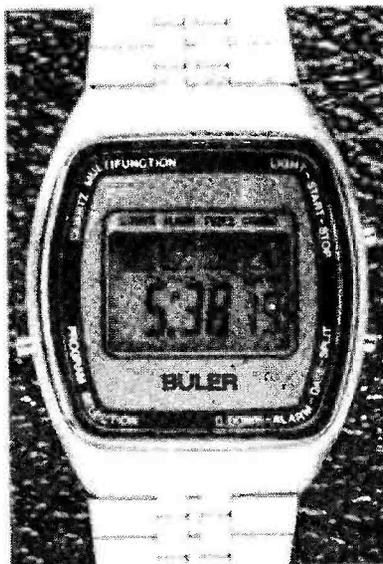

Buler dual time multi-function alarm chrono with count-down.
Special Metac price. **£24.95**

Time 1 Hours, mins, secs, day and date	✓/✓/✓/✓
Time 1 Automatic viewing of time, day and date	✓
Time 1 12/24 hour AM/PM display	✓
Time 1 24 hour alarm	✓
Time 1 Day of week in English	✓
Time 1 Day of week in French and German as well	✓/✓
Hourly chimes	
Time 2 Hours, mins, secs, day and date	✓/✓/✓/✓
Time 2 Automatic viewing of time, day and date	✓
Time 2 12/24 hour AM/PM display	✓
Time 2 24 hour alarm	✓
Time 2 Day of week in English, French and German	✓/✓/✓
Chronograph Measuring up to 12 hours	✓
Chronograph Measuring up to 24 hours	✓
Chronograph Split lap timing modes	✓
Count down timer up to 100 minutes	✓
Count down timer up to 23 hours 59 mins	✓
Number of digits	6
Number of symbols	8
Thickness	7mm
Battery life	1½ years
Battery availability	most battery retailers
Stainless steel construction	✓
Quartz mineral crystal lens	✓
Water resistant to a depth of	99ft

Seiko alarm chrono. **£42.95**
Lowest retail shop price.

Time 1 Hours, mins, secs, day and date	✓/✓/✓/✓
Time 1 Automatic viewing of time, day and date	✓
Time 1 12/24 hour AM/PM display	
Time 1 24 hour alarm	✓
Time 1 Day of week in English	
Time 1 Day of week in French and German as well	
Hourly chimes	
Time 2 Hours, mins, secs, day and date	✓/✓/✓/✓
Time 2 Automatic viewing of time, day and date	
Time 2 12/24 hour AM/PM display	
Time 2 24 hour alarm	
Time 2 Day of week in English, French and German	
Chronograph Measuring up to 12 hours	✓
Chronograph Measuring up to 24 hours	
Chronograph Split lap timing modes	✓
Count down timer up to 100 minutes	✓
Count down timer up to 23 hours 59 mins	
Number of digits	10
Number of symbols	7
Slinness	8mm
Battery life	2 years
Battery availability	Seiko dealer only
Stainless steel construction	✓
Quartz mineral crystal lens	✓
Water resistant to a depth of	Yes, but not specified

To: Metac 24-hour Despatch Centre,
47 High Street, Daventry, Northants.
Please send me Buler watches at £24.95 plus
75p&p. I enclose cheque/PO for £

Barclaycard Access No. _____
Name _____
Address _____

Please Complete


Name _____

Address _____

ET18

DUAL VCA

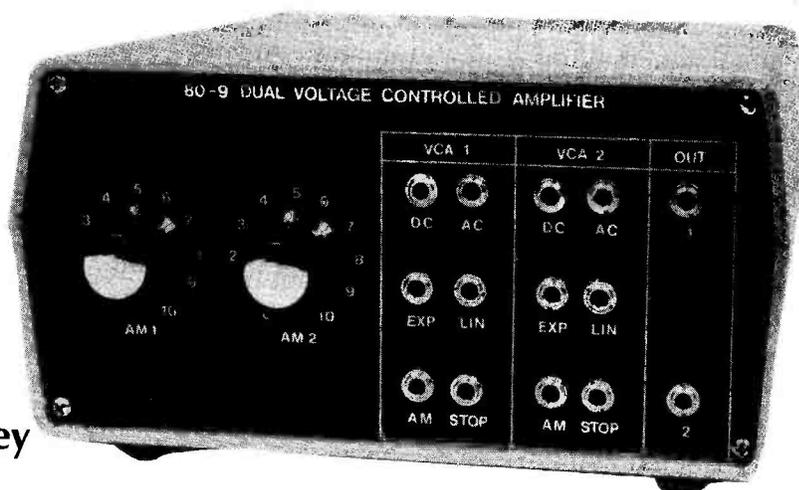The Project 80 family grows.
The latest addition~this
Dual VCA design by R.C. Blakey



A voltage controlled amplifier (VCA) when used in conjunction with an envelope shaper provides dynamic control over the amplitude of signals. Although the advantage of customised ICs for electronic music has been demonstrated in previous modules this dual VCA effectively illustrates their cost-performance benefits. It is a true dual VCA with each half having facilities for exponential or linear control; 0 to 100% linear amplitude modulation (tremelo); an external control of amplitude (expression). Furthermore, one can almost forget about overloading the VCAs and causing distortion, since they will accept ± 10 V signals and yet their low inherent noise is such that much smaller signal levels are acceptable. Each VCA also has a dynamic control range of some 80 dB using our standard 0 to +10 V control voltages.

Design Features

The design is based on the CEM 3330 Dual VCA IC produced by Curtis Electromusic Specialties, as used in Module 80-4 VCM.

A VCA is normally employed in conjunction with an ADSR envelope generator to provide the contour of sound dictated by this controller. Ideally the response to the envelope shaper voltage should be exponential since the human ear responds to loudness in a logarithmic manner. This facility is provided with a response of approximately 8 dB/volt. The overall response is such as to avoid problems arising from small levels of control voltage feedthrough from the envelope shaper. A linear control input is also included for other purposes but may be used with an envelope shaper to obtain a different type of response. In this instance, however, small amounts of control voltage feedthrough from the ADSR may be audible, although this can be cancelled out by applying an external positive voltage into the AM input. Increasing this voltage will bury the envelope voltage, that is, the attack and decay voltages will begin and end, respectively, at a voltage equal to the voltage applied to the AM input. The aural effect is more realistic since it effectively shortens the exponential decay time of the envelope — a technique adopted in some commercial synthesisers.

Another use of a VCA is for amplitude modulation (tremelo) and the design allows 0 to 100% amplitude modulation using any of the 0 to +10 V signals from the VCLFO (or VCO). The linear input or the linear AM input may also be used for loudness control, or expression, by using a

foot pedal outputting a control voltage or by taking a control voltage from, say, the keyboard. Another feature incorporated into the linear control input is a 'STOP' facility. In live performance it can be disconcerting when the rest of the group stops sharply at the end of a piece and the synthesiser is still playing as the envelope shaper continues its decay time.

Normally the signal into the VCA will be AC coupled, but if the VCA is being used for electronic control over the amplitude of signals which are to be processed further then a DC input is useful. Signals up to ± 10 V may be used and either AC or DC coupled. Mixing of signals at the VCA is not included since other ETI 80 modules have ample facilities for mixing prior to the VCA. Likewise the gain is fixed at about 0.6 so as to retain a very high signal to noise ratio for signals which will undergo further treatment and in other circumstances the output can be attenuated at the input of the power amplifier. If necessary the gain may be adjusted by using external control voltages, as described above.

The CEM 3330, from Curtis Electromusic Specialties, contains two voltage controlled amplifiers each of which consists of a variable gain cell and a log converter. The gain cell is the current-in, current-out type with an exponential control scale. The log converter generates the logarithm of the linear control input current while transmitting the exponential control input unchanged to its output, thus providing simultaneous linear and exponential controls.

Only one VCA using pins 1 to 9 of the CEM 3330 will be described since the other VCA using pins 10 to 18 is identical. The exponential control input (pin 6 of IC1) has a scale sensitivity of 18 mV/−6 dB and an increasing positive control voltage decreases gain. To reverse the polarity, so as to accept the 0 to +10 V control voltages used in the ETI 80 modules, IC2b with R12 and R14 provide a unity gain inverting stage and the voltage is attenuated by R15 and R16 to acceptable levels. R13 connected to −15 V produces a nominal 253 mV at pin 6, which sets the minimum level, and a +10 V control voltage applied to R12 will result in about −16.5 mV for maximum gain. Thus the nominal control range at this input is about 90 dB.

The overall gain of the VCA is given by

$$A_v = \frac{R_F}{R_i} \times \frac{I_{CL}}{I_{REF}} e^{-V_{CE}/V_T}$$

where R_F is the value of the output resistor (R24); R_i the signal input resistor (R17); I_{CL} the linear control current developed across

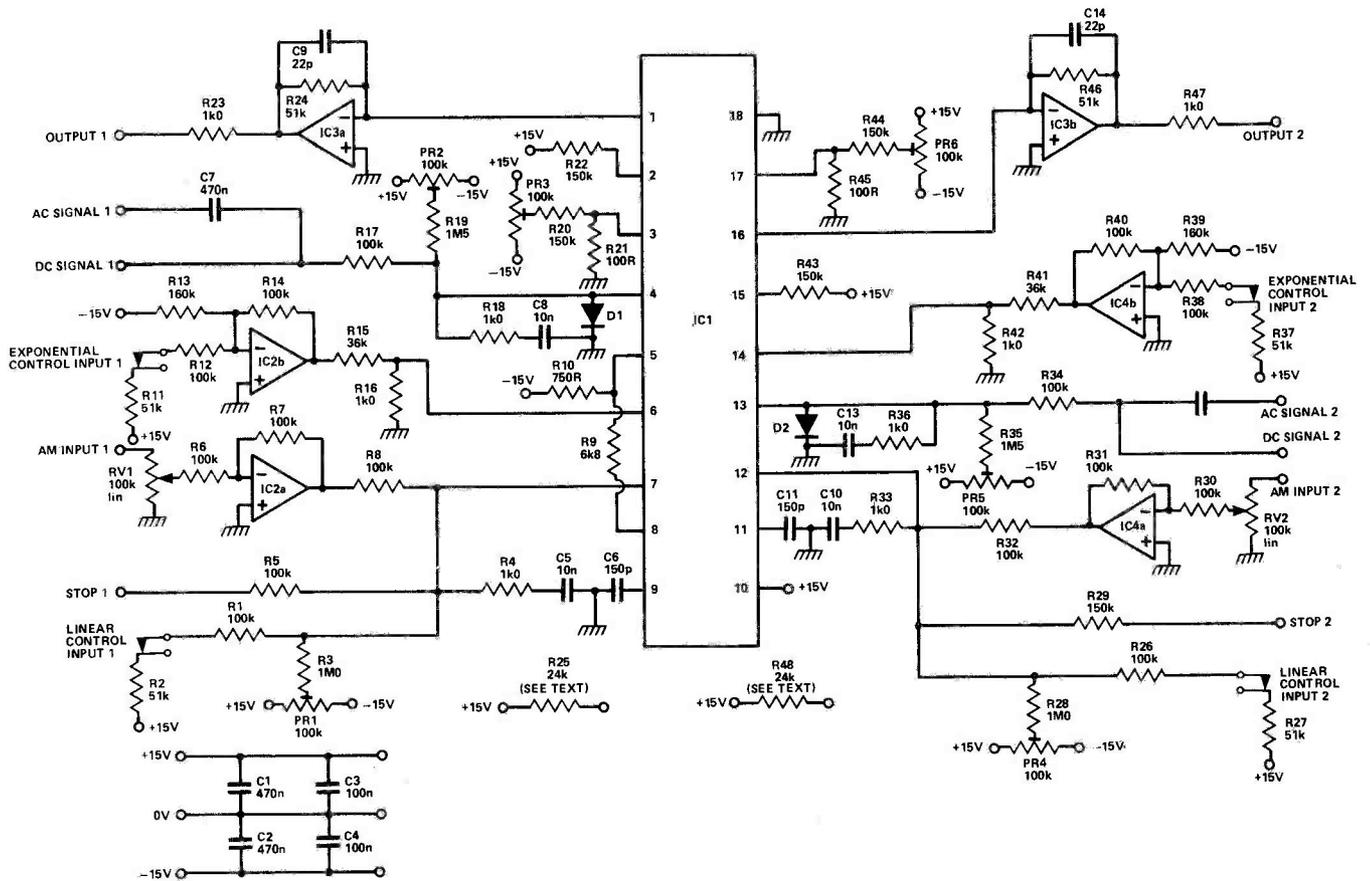


Fig.1. Circuit diagram of the Project 80 Dual VCA.

HOW IT WORKS

R1; I_{REF} the current input to pin 2 via R22 which has been set to 100 μ A for best overall performance; and V_{CE} the exponential control voltage discussed above. Thus +10 V into pin 7 via R1 (100k) produces maximum gain. By using jack socket inputs to both linear and exponential controls and connecting these to +15 V via R2 and R11 respectively, the VCA is operating at maximum gain. With a signal applied via R17 and no jack plugs inserted into either control socket the signal will pass through at maximum gain (about 0.75), which is a useful facility when setting up or tuning the synthesiser. A 0 to +10 V control voltage applied to either control socket will attenuate the signal over the full control range and with the appropriate control characteristics. These same facilities can be obtained by switches and R25 is included on the PCB for this purpose; it is connected via a switch to both control inputs (R1, R12) so as to allow signals to pass through the VCA at maximum gain. Normally the exponential input is used in conjunction with an ADSR envelope shaper and the linear control input used for amplitude modulation (tremelo). 0 to 100% amplitude modulation is obtained from the linear input using any 0 to +10 V waveform applied via RV1 and the inverting stage built round IC2a. Thus +10 V with RV1 at zero resistance will result in 100% modulation of the control voltage applied to the exponential input. PR1 and R3 are provided to balance the control voltage applied to the linear input, via R1 and R2, with the voltage applied to the AM input. Also connected to the linear input is a 'STOP' facility via R5 which may be activated externally by push button or foot switch connected to -15 V. Since a negative current at this input cuts the VCA completely off the 'STOP' action is functional at all times and allows the synthesiser output to be stopped on demand. Alternatively, a

foot pedal switch containing a 9 V battery (positive to jack socket ground) can be used if R5 and R29 are changed to 91k. Components R4 and C5 are for compensation purposes.

The signal input may be AC coupled via C7 and R17 or DC coupled direct to R17. R18, C8 and C6 are compensation components and D1 prevents latch up. PR2 and R9 allow trimming of control voltage feedthrough. The current output from pin 1 is converted to a voltage using IC3a and R24.

To operate the CEM 3330 from the standard ± 15 V supply a current limiting resistor must be added between pin 5 and the negative supply, which in the present application may be calculated from the formula $R_{EE} = (V_{EE} - 7.2)/0.010$; which for -15 V supply requires a 750R resistor (R10).

One of the unique features of the CEM 3330 is that the operating point of the amplifiers may be set anywhere from Class A to Class B according to which parameters are most important in a particular application. The quiescent standby current of the signal carrying transistors is varied by placing a resistor between the I_{EE} pin (pin 5) and the idle current adjust pin (pin 8). For this VCA application the amplifiers are run Class AB with the 6k8 resistor (R9) providing a standby current of about 7 μ A.

When operating the VCAs less than Class A, internal transistor mismatches will cause the gain during the positive portion of the input signal to differ from that during the negative portion, thus introducing even harmonic distortion — predominantly second. In this design the untrimmed distortion is typically less than 1%, at 1 kHz and 10 dB below clipping, but this can be improved by about a factor of ten if a small voltage is injected into the distortion trim pin (pin 3). R3, R20 and R21 provide an adjustment of ± 10 mV for this purpose, if required.

By employing jack sockets for the inputs the VCAs are normally open, that is, a signal applied to the input of either will be present at the appropriate output at a level governed by the maximum gain of the VCA. As soon as a jack plug is inserted into either the linear or exponential control input then the VCA is under the control of the external voltage and with 0 V at either input the signal is completely cut off. The normally open VCA is useful while tuning the VCOs and setting up patches. This same facility may also be obtained using switches. The necessary resistors are incorporated into the PCB layout to cope with the different methods of construction.

Other advantages of having a true dual VCA incorporating the controls described above are:

(1) The ability to use the VCAs for auto panning by applying the signals to both (the same or different signals) and controlling pan by, say, a sawtooth wave into the linear control input of one and into the AM control of the other. Many panning variations are possible by using the exponential control, the inverted voltages from the 80-5 processor module, and so on;

(2) Taking the output from one VCA whose signal has been amplitude modulated and applying further modulation in the second VCA.

A truly versatile module.

Construction


The module is designed for control voltages of 0 to +10 V and so if it is to be used in conjunction with ETI 80-8, whose peak voltage may reach +11 V, then resistors R11 and R37 should be replaced by 39k and R12 and R38 by 110k. This alteration is to prevent excessive output voltages and the substitute resistors are included in the kit of parts. R5 and R29 should also be changed to 91k if a footswitch with a 9 V battery is used to operate the 'STOP' control, as described in the previous section.

R25 and R48 need not be installed if jack sockets are used for the control inputs. With the latter method of construction R1, R12, R26 and R38 are wired to the jack socket connection which makes contact with a jack plug while R2, R11, R27 and R37 go to the respective socket connections which are disabled when a jack plug is inserted. If jack sockets are not used then a three position double pole slide switch may be employed for each VCA. For example, with VCA 1 the switch should be wired to connect R2 to R1 (position '1' to enable the exponential control); connect R11 to R12 (position '2' to enable the linear control); connect R25 to both R1 and R12 (position '3' to by-pass the VCA during tuning, etc.)

Calibration

Although there are three trimmers on each side the calibration can be carried out quickly with a minimum of equipment. During calibration the VCA must be in the open position, ie no jack plugs inserted into the control inputs (or R24/R48 switched to both control inputs). Set all trimmers to their mid position.

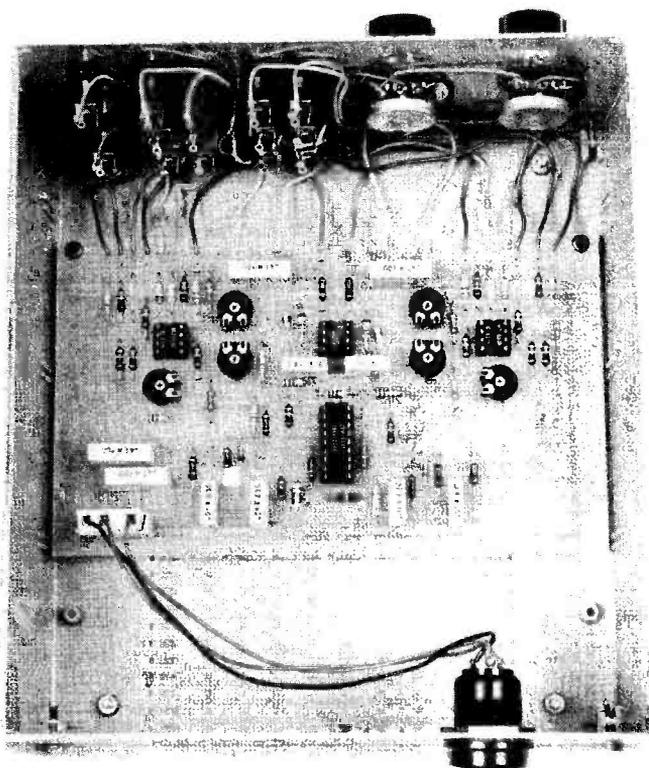1. To balance the AM input control voltage against the voltage applied to the linear control input via R2 and R27. Turn the AM control, RV1 or RV2, fully clockwise (minimum resistance) and apply a 10 V VCO signal to the DC input. Apply exactly +10V0 to the AM input, using a potentiometer as a voltage divider and either examine the output of the VCA being calibrated with an oscilloscope set to its maximum sensitivity or listen to the output by connecting it to an amplifier. Turn PR1 (PR4) so that the



The Dual VCA board fitted into the Teko Alba A23G case (available from West Hyde Developments).

PARTS LIST

RESISTORS 1/4W 5% carbon film unless stated

R1,6,7,8,12*,14,17, 26,30,31,32,34,38*, 40	100k
R2,11*,27,37*	51k
R3,28	1M0
R4,16,18,23,33,36, 42,47	1k0
R5,20,29,44	150k
R9	6k8
R10	750R
R13,39	160k
R15,41	36k
R19,35	1M5
R21,45	100R
R22,43	150k (1% metal film)
R24,46	51k (1% metal film)
R25,48	24k
*see text	

CAPACITORS

C1,2,7,12	470n polyester
C3,4	100n polyester
C5,8,10,13	10n polyester
C6,11	150p polystyrene
C9,14	22p polystyrene

TRIMMERS

PR1,2,3,4,5,6	100k carbon
---------------	-------------

POTENTIOMETERS

RV1,2	100k linear
-------	-------------

SEMICONDUCTORS

IC1	CEM3330
IC2,4	LM1458
IC3	TL072CP
D1,2	1N4148

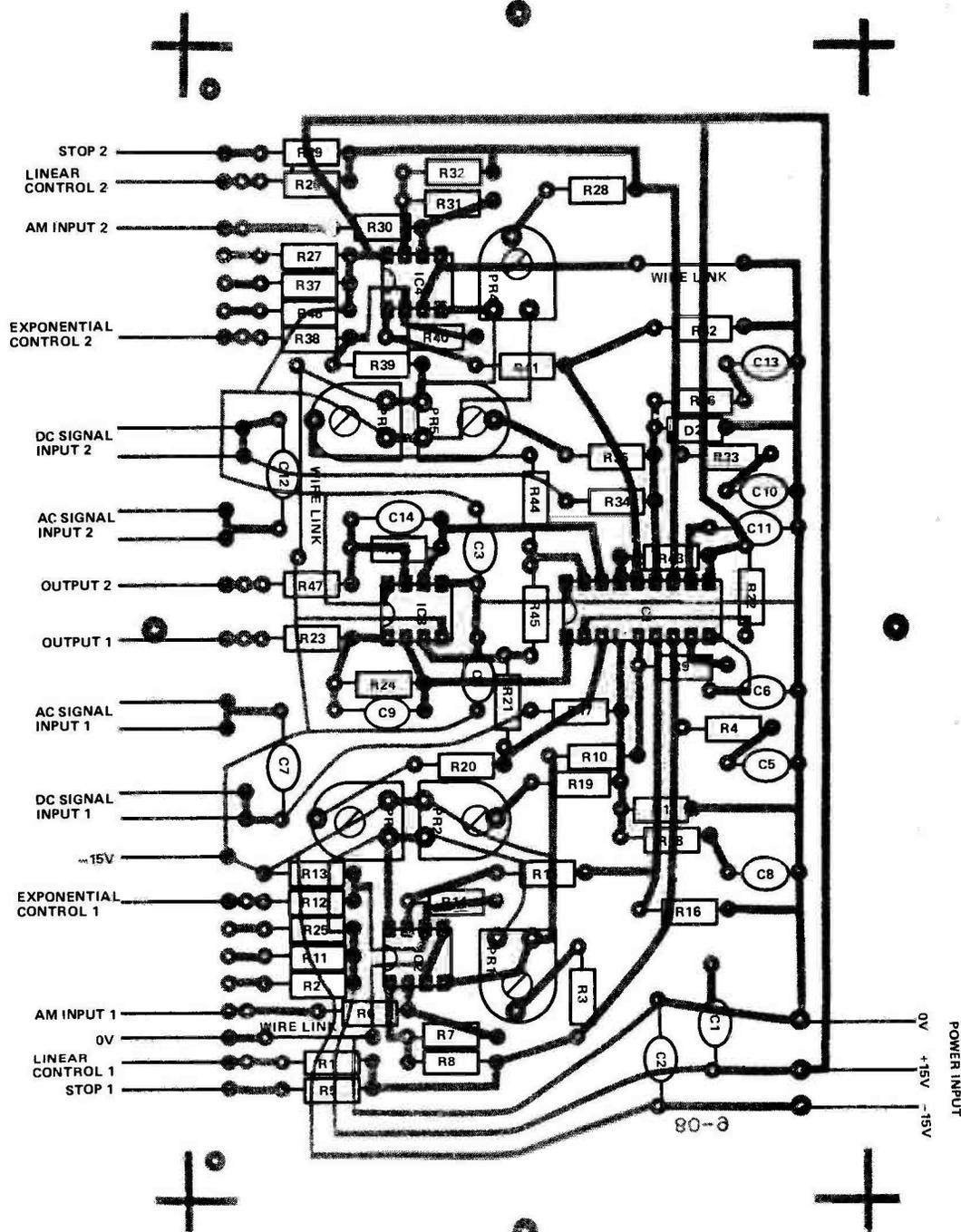


Fig.2. Component Overlay.

signal is seen (or heard) then reverse direction until the signal is just cut off.

2. Trimming distortion. Connect the output to a voltmeter and adjust PR3 (PR6) for zero output. Next connect a fresh 9 V battery to the DC signal input with the positive terminal to R17(R34) and the negative terminal to a ground point on the module. Measure the voltage at the output as accurately as possible. Reverse the battery leads and measure voltage again. Adjust PR3 (PR6) until the voltage obtained between +V applied and no voltage applied is exactly the same as that obtained with -V and no voltage. This difference must take into account any drift from zero output, with no voltage applied, as PR3 (PR6) is adjusted. The polarity reversal may have to be carried out several times to achieve the calibration step. NOTE: For those that find this step difficult or who are content with up

to about 1% distortion then components PR3, R20 and R21 (PR6, R44 and R45) may be omitted and the PCB connections for R21 and R45 replaced by wire links. In this event only calibration steps 1 and 3 are required.

3. Trimming control voltage feedthrough. With no connections to any VCA inputs adjust PR2 (PR5) to give exactly 0V output.

ETI

BUYLINES

The Dual VCA kit with PCB and all components shown in the circuit diagram, except jack sockets, is available for £14.33, inclusive of postage and VAT, from Digisound Limited, 13 The Brooklands, Wrea Green, Preston, Lancs PR4 2NQ.

Britain's first com puter kit.

The Sinclair ZX80.

£79.95

Price breakdown
ZX80 and manual: £69.52
VAT: £10.43
Post and packing FREE

Please note: many kit makers quote VAT-exclusive prices.

You've seen the reviews... you've heard the excitement... now make the kit!

This is the ZX80. 'Personal Computer World' gave it 5 stars for 'excellent value.' Benchmark tests say it's faster than all previous personal computers. And the response from kit enthusiasts has been tremendous.

To help you appreciate its value, the price is shown above with and without VAT. This is so you can compare the ZX80 with competitive kits that don't appear with inclusive prices.

'Excellent value' indeed!

For just £79.95 (including VAT and p&p) you get everything you need to build a personal computer at home... PCB, with IC sockets for all ICs; case; leads for direct connection to a cassette recorder and television (black and white or colour); everything!

Yet the ZX80 really is a complete, powerful, full-facility computer, matching or surpassing other personal computers at several times the price.

The ZX80 is programmed in BASIC, and you can use it to do quite literally anything from playing chess to managing a business.

The ZX80 is pleasantly straightforward to assemble, using a fine-tipped soldering iron. It immediately proves what a good job you've done: connect it to your TV... link it to an appropriate power source*... and you're ready to go.

Your ZX80 kit contains...

- Printed circuit board, with IC sockets for all ICs.
- Complete components set, including all ICs - all manufactured by selected world-leading suppliers.
- New rugged Sinclair keyboard, touch-sensitive, wipe-clean.
- Ready-moulded case.
- Leads and plugs for connection to domestic TV and cassette recorder. (Programs can be **SAVED** and **LOADED** on to a portable cassette recorder.)
- FREE course in BASIC programming and user manual.

Optional extras

- Mains adaptor of 600 mA at 9 V DC nominal unregulated (available separately - see coupon).
- Additional memory expansion boards allowing up to 16K bytes RAM. (Extra RAM chips also available - see coupon).

*Use a 600 mA at 9 V DC nominal unregulated mains adaptor. Available from Sinclair if desired (see coupon).

The unique and valuable components of the Sinclair ZX80.

The Sinclair ZX80 is not just another personal computer. Quite apart from its exceptionally low price, the ZX80 has two uniquely advanced components: the Sinclair BASIC interpreter; and the Sinclair teach-yourself BASIC manual.

The unique Sinclair BASIC interpreter offers remarkable programming advantages:


- Unique 'one-touch' key word entry: the ZX80 eliminates a great deal of tiresome typing. Key words (RUN, PRINT, LIST, etc.) have their own single-key entry.
- Unique syntax check. Only lines with correct syntax are accepted into programs. A cursor identifies errors immediately. This prevents entry of long and complicated programs with faults only discovered when you try to run them.
- Excellent string-handling capability - takes up to 26 string variables of any length. All strings can undergo all relational tests (e.g. comparison). The ZX80 also has string input to request a line of text when necessary. Strings do *not* need to be dimensioned.
- Up to 26 single dimension arrays.
- FOR/NEXT loops nested up 26.
- Variable names of any length.
- BASIC language also handles full Boolean arithmetic, conditional expressions, etc.
- Exceptionally powerful edit facilities, allows modification of existing program lines.
- Randomise function, useful for games and secret codes, as well as more serious applications.
- Timer under program control.
- PEEK and POKE enable entry of machine code instructions,USR causes jump to a user's machine language sub-routine.
- High-resolution graphics with 22 standard graphic symbols.
- All characters printable in reverse under program control.
- Lines of unlimited length.

Fewer chips, compact design, volume production - more power per pound!





The ZX80 owes its remarkable low price to its remarkable design: the whole system is packed on to fewer, newer, more powerful and advanced LSI chips. A single SUPER ROM, for instance, contains the BASIC interpreter, the character set, operating system, and monitor. And the ZX80's 1K byte RAM is roughly equivalent to 4K bytes in a conventional computer - typically storing 100 lines of BASIC. (Key words occupy only a single byte.)

The display shows 32 characters by 24 lines. And Benchmark tests show that the ZX80 is faster than all other personal computers.

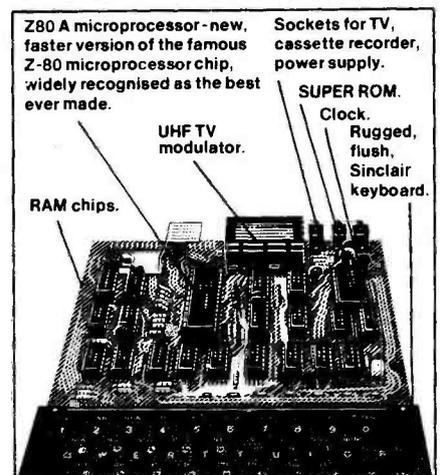No other personal computer offers this unique combination of high capability and low price.



plete

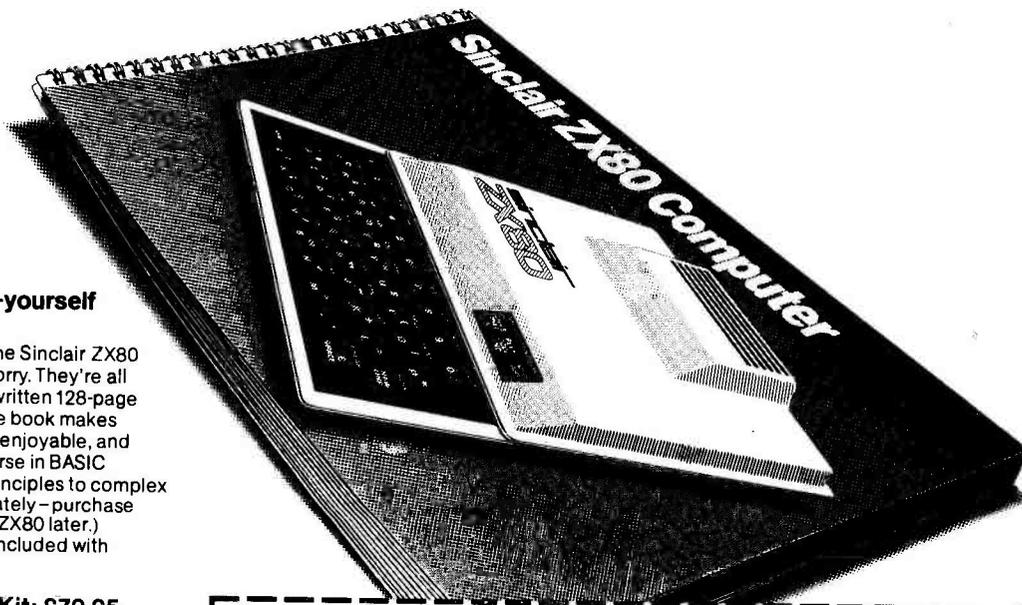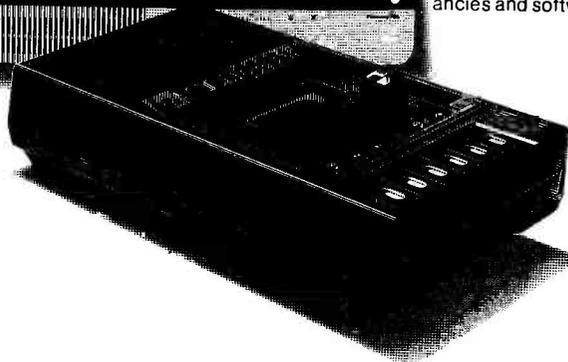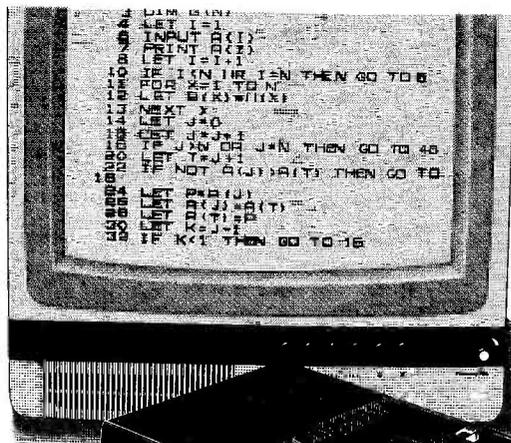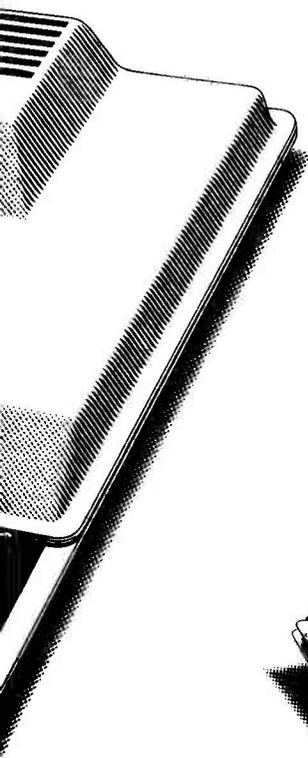

ZX80 software – now available!

See the advertisements in Personal Computer World (June) and Electronics Today International (July).

New dedicated software – developed independently of Science of Cambridge – reflects the enormous interest in the ZX80. More software available soon – from leading consultancies and software houses.

The Sinclair teach-yourself BASIC manual.

If the specifications of the Sinclair ZX80 mean little to you – don't worry. They're all explained in the specially-written 128-page book free with every kit! The book makes learning easy, exciting and enjoyable, and represents a complete course in BASIC programming – from first principles to complex programs. (Available separately – purchase price refunded if you buy a ZX80 later.) A hardware manual is also included with every kit.

The Sinclair ZX80. Kit: £79.95. Assembled: £99.95. Complete!

The ZX80 kit costs a mere £79.95. Can't wait to have a ZX80 up and running? No problem! It's also available, ready assembled, for only £99.95.

Demand for the ZX80 is very high: use the coupon to order today for the earliest possible delivery. All orders will be despatched in strict rotation. We'll acknowledge each order by return, and tell you exactly when your ZX80 will be delivered. If you choose not to wait, you can cancel your order immediately, and your money will be refunded at once. Again, of course, you may return your ZX80 as received within 14 days for a full refund. We want you to be satisfied beyond all doubt – and we have no doubt that you will be.

sinclair ZX80

Science of Cambridge Ltd

6 Kings Parade, Cambridge, Cambs., CB2 1SN.
Tel: 0223 311488.

ETI AUGUST 1980

ORDER FORM

To: Science of Cambridge Ltd, 6 Kings Parade, Cambridge, Cambs., CB2 1SN.
Remember: all prices shown include VAT, postage and packing. No hidden extras.
Please send me:

Quantity	Item	Item price £	Total £
	Sinclair ZX80 Personal Computer kit(s). Price includes ZX80 BASIC manual, excludes mains adaptor.	£79.95	
	Ready-assembled Sinclair ZX80 Personal Computer(s). Price includes ZX80 BASIC manual, excludes mains adaptor.	£99.95	
	Mains Adaptor(s) (600 mA at 9 V DC nominal unregulated).	8.95	
	Memory Expansion Board(s) (each one takes up to 3K bytes).	12.00	
	RAM Memory chips – standard 1K bytes capacity.	16.00	
	Sinclair ZX80 Manual(s) (manual free with every ZX80 kit or ready-made computer).	5.00	

NB. Your Sinclair ZX80 may qualify as a business expense.

TOTAL £

I enclose a cheque/postal order payable to Science of Cambridge Ltd for £

Please print

Name: Mr/Mrs/Miss

Address

ETI

SUBSCRIPTIONS

This year we present a new twelve-part, fiction series — ETI 1980. available from your newsagent every month.

Forget to buy it this month, or is your newsagent sold out?


Why worry when ETI gets to the shop? Sit back and wait for it to come to you. Take out an ETI Subscription. For only £10.00 we'll send you twelve issues of ETI PLUS A free copy of ETI 1999, a chronicle of future times including the first report of World War III. You've never seen anything like it before.

To claim your FREE ETI 1999 (and a years' supply of ETI, of course) send your PO or cheque direct to




ETI Subscriptions
MAP Publications
PO Box 35
Bridge Street
Hemel Hempstead
Herts.

MAIL ORDER ONLY		DELTA TECH & CO.		RESISTORS (5% E12)		DIL SOCKETS		TTL		AC128		BO121/3		TIP3055	
62 NAYLOR ROAD, LONDON, N20 0HN		Please add 35p for P&P		7812/15	65p	8 pin	*7p	7400/1	43p	74105	20p	75p	75p	75p	*30p
10 Ohms to 10Mohms		7818/24	65p	14 pin	*9p	16 pin	*10p	74107	22p	74107	20p	80124	81p	ZTX107/8	12p
PRESETS (.15W HORIZONTAL)		7905	75p	18 pin	16p	22 pin	21p	74109	40p	74110	25p	BD131/2	35p	ZTX109	12p
100 Ohms to 2 Mohms		7912/15	75p	24 pin	21p	28 pin	25p	74111	40p	74118	22p	BD135 to	35p	ZTX300/1	14p
POTENTIOMETERS (1/4 W)		7918/24	75p	40 pin	35p			74121	22p	74121	30p	BO140	35p	ZTX302/3	18p
Linear & Log Scales								74122	30p	74123	35p	BF178	30p	ZTX304	23p
4.7kOhms to 2.2Mohms								74123	45p	74125/6	35p	BF180	34p	ZTX311	18p
VEROBOARDS (.1" COPPER)								74124	45p	74127	35p	BF181	8p	ZTX341	22p
2.5" x 5"								74125	45p	74127	35p	BF183	34p	ZTX500/1	15p
3.75" x 5"								74126	45p	74128	35p	BF184/5	25p	ZTX502	20p
ZENER DIODES (400mW)								74127	45p	74129	35p	BF194	12p	ZTX503	17p
5V6 5p*								74128	45p	74130	40p	BF195/6	12p	ZTX504	24p
2V7 to 33V 8p								74129	45p	74131	40p	BF197	12p	2N696/7	20p
POLYSTYRENE CAP (50V)								74130	45p	74132	45p	BF224B	14p	2N698	20p
10 pF to 1000 pF								74131	45p	74133	45p	BF244B	35p	2N706	14p
CERAMIC CAP (50V)								74132	45p	74134	45p	BC117	23p	2N914	20p
33 pF to 4700 pF								74133	45p	74135	45p	BC142/3	30p	2N918	35p
POLYESTER CAP (100V)								74134	45p	74136	45p	BC147/8	10p	2N939	20p
1 nF to 68 nF								74135	45p	74137	45p	BC149	10p	2N979	32p
100 nF 150 nF								74136	45p	74138	45p	BC157/8	12p	2N1302/3	35p
220 nF 330 nF								74137	45p	74139	45p	BC159	12p	2N1304	35p
470 nF: 11p								74138	45p	74140	45p	BC167	14p	2N1306	30p
680 nF: 13p								74139	45p	74141	45p	BC169C	13p	2N1613	25p
1 uF: 18p								74140	45p	74142	45p	BC171	10p	2N1711	13p
2.2uF 22p 3.3uF: 15p* 4.7uF: 15p*								74141	45p	74143	45p	BC173	8p	2N1893	25p
ELECTROLYTIC CAP (uF/V)								74142	45p	74144	45p	BC177/8	16p	2N2217	18p
1/25 to 47/25: 6p 68/25: 100/35 8p								74143	45p	74145	45p	BC179	16p	2N2219	23p
150/25: 160/25								74144	45p	74146	45p	BC182B	10p	2N2224	23p
470/25: 10p								74145	45p	74147	45p	BC182L	7p	2N2369	17p
640/16: 5p*								74146	45p	74148	45p	BC183L	10p	2N2484	25p
1000/25: 22p								74147	45p	74149	45p	BC184	10p	2N2646	46p
1500/25: 12p*								74148	45p	74150	45p	BC186	25p	2N2904/5	21p
								74149	45p	74151	47p	BC187/8	25p	2N2906/7	21p
								74150	45p	74152	45p	BC190	10p	2N2926	10p
								74151	45p	74153	43p	BC192	10p	2N3053	20p
								74152	45p	74154	45p	BC193	10p	2N3054	40p
								74153	45p	74155	45p	BC194	10p	2N3055	45p
								74154	45p	74156	45p	BC195	10p	2N3055B	50p
								74155	45p	74157	45p	BC196	10p	2N3442	140p
								74156	45p	74158	45p	BC197	10p	2N3702 to	
								74157	45p	74159	45p	BC198	10p	2N3711	11p
								74158	45p	74160	45p	BC199	10p	2N3772	+80p
								74159	45p	74161	45p	BC200	10p	2N3773	250p
								74160	45p	74162	45p	BC201	10p	2N3819	21p
								74161	45p	74163	45p	BC202	10p	2N3820	40p
								74162	45p	74164	45p	BC203	10p	2N3823	70p
								74163	45p	74165	45p	BC204	10p	2N3866	+55p
								74164	45p	74166	45p	BC205	10p	2N3903/4	15p
								74165	45p	74167	45p	BC206	10p	2N3906	15p
								74166	45p	74168	45p	BC207/9	13p	2N3907	15p
								74167	45p	74169	45p	BC208	10p	2N4057/9	10p
								74168	45p	74170	45p	BC209	10p	2N4060/1	10p
								74169	45p	74171	45p	BC210	10p	2N4547/8	40p
								74170	45p	74172	45p	BC211	10p	2N4549	40p
								74171	45p	74173	45p	BC212	10p	2N4550	40p
								74172	45p	74174	45p	BC213	10p	2N4551	40p
								74173	45p	74175	45p	BC214	10p	2N4552	40p
								74174	45p	74176	45p	BC215	10p	2N4553	40p
								74175	45p	74177	45p	BC216	10p	2N4554	40p
								74176	45p	74178	45p	BC217	10p	2N4555	40p
								74177	45p	74179	45p	BC218	10p	2N4556	40p
								74178	45p	74180	45p	BC219	10p	2N4557	40p
								74179	45p	74181	45p	BC220	10p	2N4558	40p
								74180	45p	74182	45p	BC221	10p	2N4559	40p
								74181	45p	74183	45p	BC222	10p	2N4560	40p
								74182	45p	74184	45p	BC223	10p	2N4561	40p
								74183	45p	74185	45p	BC224	10p	2N4562	40p
								74184	45p	74186	45p	BC225	10p	2N4563	40p
								74185	45p	74187	45p	BC226	10p	2N4564	40p
								74186	45p	74188	45p	BC227	10p	2N4565	40p
								74187	45p	74189	45p	BC228	10p	2N4566	40p
								74188	45p	74190	45p	BC229	10p	2N4567	40p
								74189	45p	74191	45p	BC230	10p	2N4568	40p
								74190	45p	74192	45p	BC231	10p	2N4569	40p
								74191	45p	74193	45p	BC232	10p	2N4570	40p
								74192	45p	74194	45p	BC233	10p	2N4571	40p
								74193	45p	74195	45p	BC234	10p	2N4572	40p
								74194	45p	74196	45p	BC235	10p	2N4573	40p
								74195	45p	74197	45p	BC236	10p	2N4574	40p
								74196	45p	74198	45p	BC237	10p	2N4575	40p
								74197	45p	74199	45p	BC238	10p	2N4576	40p
								74198	45p	74200	45p	BC239	10p	2N4577	40p
								74199	45p	74201	45p	BC240	10p	2N4578	40p
								74200	45p	74202	45p	BC241	10p	2N4579	40p
								74201	45p	74203	45p	BC242	10p	2N4580	40p
								74202	45p	74204	45p	BC243	10p	2N4581	40p
								74203	45p	74205	45p	BC244	10p	2N4582	40p
								74204	45p	74206	45p	BC245	10p	2N4583	40p
								74205	45p	74207	45p	BC246	10p	2N4584	40p
								74206	45p	74208	45p	BC247	10p	2N4585	40p
								74207	45p	74209	45p	BC248	10p	2N4586	40p
								74208	45p	74210	45p	BC249	10p	2N4587	40p
								74209	45p	74211	45p	BC250	10p	2N4588	40p
								74210	45p	74212	45p	BC251	10p	2N4589	4

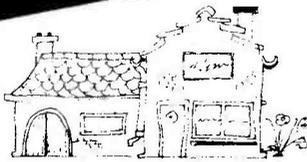

HOME

- Steam train and whistle (80019). Simulates the sound on steam and whistle **£6.50**
 Clap switch (79026). You clap your hands and the light comes on **£6.60**
 Elekdoorbell (79095). Program your own signature. **£22.00**
 Touch dimmer (78065). Room lighting controlled by single touch **£6.80**
 TV sound modulator (9925) **£3.75**
 Simple sound effects (79077) **£5.70**
 Electronic nuisance (80016) **£3.85**
 Ultrasonic transmitter (audio) (79510) **£7.65**
 Ultrasonic receiver (audio) (79511) **£9.95**
 DJ killer (79505) **£8.80**
 Quiz master (79033) **£6.50**
 Variable fuzz-box (9984) **£6.55**
 Ioniser (9823). Produces a high concentration of negative ions **£9.55**
 Oscillographics (9979). Random displays patterns on your oscilloscope **£11.25**
 Cackling egg timer (9985). Times your egg, then clucks like a hen! **£7.20**
 Pools forecaster (79053). Weighs up the odds and could win you a fortune **£8.15**
 Loudspeaking telephone amplifier (9987). Amplifies signal without direct connection **£11.50**
 Sensitive lightmeter (9886). Light measurement using silicon photodiode **£12.55**
 Nicad charger (79024). Automatically prevents over charge of cells **£15.20**
 Proximity detector (9974). Detects movement in a room (electric field change) **£9.80**
 Central alarm (9950). Master station slave station **£10.85**
 Alarm unit **£3.10**
 Touch tuning FM preselect unit (79519). With digital display **£17.50**
 Talk funny (80052). Deliberate electronic distortion of speech and music signals using a single IC, the 2206 **£9.80**
 Colour generator (80027). Using coloured light for an effective display **£19.70**
 Pools predictor (79053) **£8.15**

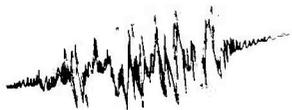

HIGH FREQUENCIES

- Aerial amplifier (80022). Improves the sensitivity of an existing receiver specify VHF/UHF **£5.45**
 UHF/VHF modulator (9976). Generates a carrier for TV signals **£6.25**
 Mini shortwave receiver (9920). Interesting introduction to SW radio **£6.95**
 FM IF strip (78087). Using the CA 3189 limiter demodulator IC **£13.05**
 Stereo decoder (79082). Compatible with the FM IF strip **£15.10**
 Digital tuning scale (80021). A sophisticated digital frequency indication **£46.30**
 Ohm aerial (80076 1 + 2). A practical shortwave aerial for 1.8-30MHz **£10.30**

Buying one of our PROJECT PACKS will save you the frustration of tracking down those evasive components that hold up the completion of your project. Our packs include Printed Circuit Board, all the components listed in the article together with sockets and solder. Cases, knobs, etc., can be supplied as extra items if required. Ask for more information ...!

MUSIC


- Chorosynth (80060). A cheap mini-synthesizer **£57.90**
 Elektor vocoder (80060). The first vocoder designed to be built from a kit with excellent features. It has 10 channels **£162.50**
 Front panels for vocoder per channel **£1.25**
 Analog reverberation unit (9973). Kit with 1 SAD 1024 **£27.70**
 Piano. Excellent kit of an electronic piano with three voices. **£37.00**
 Master tone oscillator/generator **£18.75**
 Octave PCB (9914) **£16.50**
 Filter PCB (9981) **£19.05**
 Power supply (9979) **£67.20**
 Digital reverberation unit main board **£46.30**
 Extension boards

NEW - NEW

- * **Battery protection (80109)**. Forgetting to turn off the headlights need no longer be a motorist's nightmare. This project is designed to monitor the battery voltage and switch off the lights automatically in all kinds of motor vehicles **£5.15**
- * **Transistor ignition (80084)**. A system which combines the most significant advantages of other systems including the conventional system! **£20.45**
- * **Intelligent wiper delay (80086)**. This wiper delay only needs to be told once what is required of it. It will then carry out your orders until you change them, which you can at any time, instantly **£15.85**
- * **Active car aerial (80018-1 + 2)**. If there is one place to use a good aerial it is in a car **£13.85**
- * **Stop thief! (80097)**. There are all sorts of systems for protecting cars, but this one is unusual: it is deception, rather than protection **£4.20**
- * **Battery voltage indicator (80101)**. Only a few components are needed to obtain an optional indication of the battery condition: a single lamp that changes colour as the battery goes into the danger area **£6.85**
- * **Pest Pester (80130)**. An electronic insect repellent. Confuses mosquitos with high pitch tone **£2.35**
- * **Morse Trainer (80072)**. Can be preset to generate the morse alphabet for tuition purposes. Morse key required **£11.00**
- * **Luxury Transistor Tester (80077)**. Not only checks that the device is functional but displays HFE group **£15.54**

NEW CATALOGUE

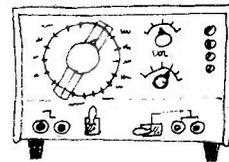Send 40p for our new catalogue giving details of our project packs and component range.



MEASURING

- Digital thermometer (80045)
 LCD display (supplied without relay) **£28.95**
 LED display (supplied without relay) **£23.20**
 Relay (two pole changeover) **£2.45**
 AC millivoltmeter (79035). FET input meter circuit and audio generator **£6.30**
 Universal digital meter (79005). Digital replacement for pointer instruments **£14.65**
 Precision timebase (9448). Generates a precision 1 Hertz pulse **£13.10**
 Power supply for timebase **£5.40**
 Universal timebase (78100). Crystal controlled timebase **£18.70**
 1/4 GHz counter (9887 1 + 2 + 3 + 4). Excellent kit count up to 250 MHz **£98.15**
 Minicounter (9927). 1KHz 4 digit display **£27.70**
 Audio analyser (9932). An analyser which can point the deficiencies in a particular audio chain or environment **£14.80**
 Spot sinewave generator (9948). Programmable sinewaves with less than 0.0025% THD **£12.95**
 Simple function generator (9453). Sine, square and sawtooth outputs **£27.70**
 Sinewave generator (79019). Always sinewaves when you need them **£8.80**
 TV scope basic version (9968 1/5). Produces display up to 1 KHz on TV **£34.50**
 TV scope advanced version (9969 1/3). Converts basic scope to 100KHz bandwidth **£48.25**
 Digscope (9926) **£32.35**
 Digitarad (79088). A digital capacitance meter with a wide range **£25.10**
 Gate dipper (79514). Checks the resonant frequency of a circuit **£16.00**

AUDIO


- Equaliser (9832). Single channel audio equaliser with slidepots **£17.70**
 with turnpots **£15.60**
 with preset pots **£13.95**
 UAA180 LED meter (9817). A two-channel display meter with LEDs **£13.00**
 Peak programme meter (9860). For use with UAA180 LED meter to give stereo audio display **£13.00**
 Luminant (9949 1 + 2 + 3). A novel LED audio level indicator **£20.70**
 Parametric equaliser (9897) filter section (9897-1) **£6.45**
 Tone control section (9897-2) **£5.20**
 Audio analyser (9932). An analyser which can pinpoint the deficiencies in a particular audio chain or environment **£14.80**
 Preconsonant (9954). A high-performance amplifier. **£5.75**
 Consonant (9945). A complete audio control preamplifier **£34.65**
 Topamp (80031). Mini preamplifier for Topamp or any other Hi-Fi poweramp **£34.30**
 Topamp (80023). Hybrid audio power amplifier with OM 931 (output 30 watt) **£18.50**
 with OM 961 (output 60 watt) **£33.40**
 Stentor (79070). A portable amplifier ideally suited for PA **£30.00**
 Assistentor (79071). A preamp for use with Stentor **£7.00**
 Elektornado (9874). A 2 x 50 watt or single 100-watt power amplifier **£19.50**
 Electret microphone preamp (9866). Compact design that fits into the mike **£4.85**

HOW TO ORDER:



Send a cheque or postal order to **DORAM ELECTRONICS LTD., Fitzroy House, Market Place, Swaffham, Norfolk, PE37 7QH**. All our prices include V.A.T. Please add 40p for postage and packing.

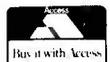Office hours: Monday-Friday, 9 a.m. to 5 p.m.
 Telephone Swaffham (0760) 21627. Telex 817912.




ULTRASONIC BURGLAR ALARM

Use our Doppler circuit movement detector to catch anything on the move. New design offers high sensitivity.

If you have even a passing interest in electronics, you'll know that there have been more than a few burglar alarm designs published — alarms set off when a switch opens or closes or when an invisible beam is broken or activated by a pressure mat. The permutations are endless. This project offers a novel movement detector based on the Doppler shift principle.

Super Shift

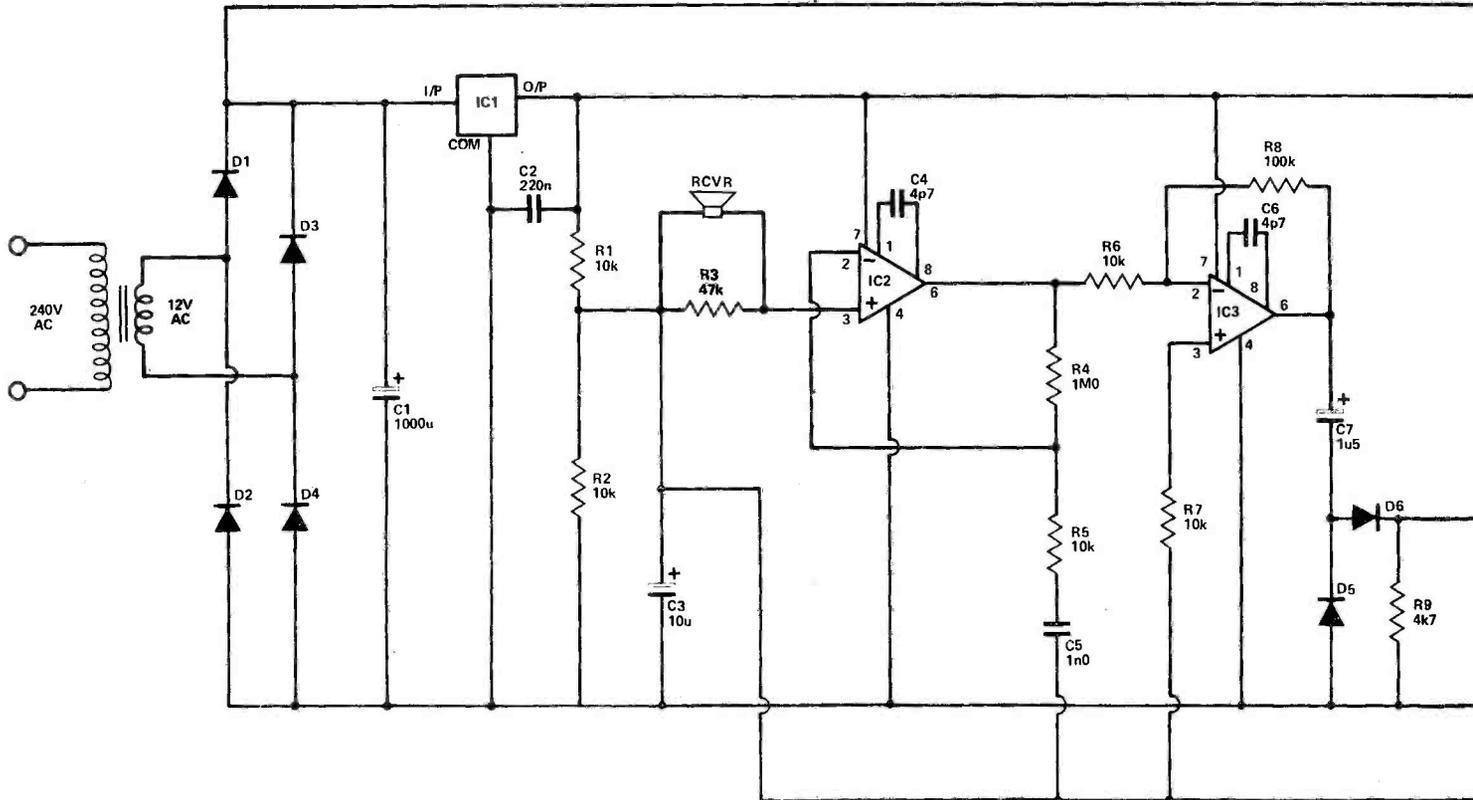The unit consists of an ultrasonic transmitter radiating at about 40 kHz. Energy reflected from a moving target is shifted in frequency slightly. When mixed with the original signal, a heterodyne or 'beat' note is generated. This is detected by



HOW IT WORKS

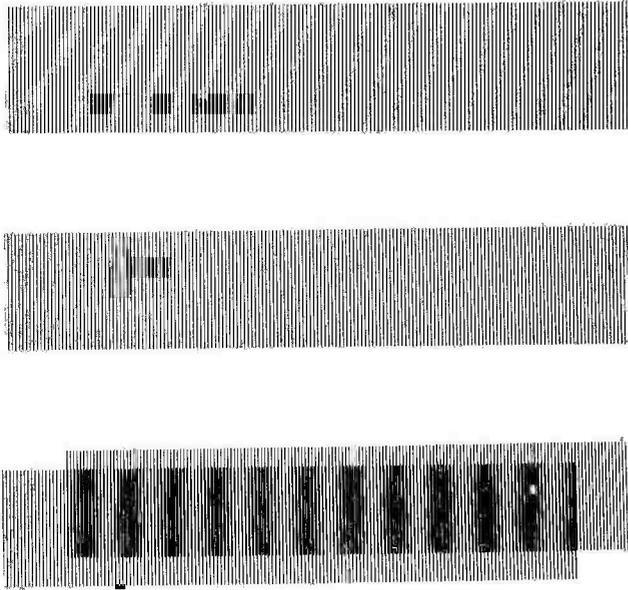


Fig.1. (above) When the received signal is mixed with the original signal, the slight difference in frequency produces a heterodyne or beat note.

Fig.2. (below) Circuit diagram.


An ultrasonic drive signal is generated by IC6, a 555 configured as an astable oscillator. The circuit differs from the conventional design, as it has the timing resistor returned to the output and the internal discharge transistor (pin 7) is unused. This arrangement was chosen as it enables a 50% duty cycle to be obtained providing a better drive signal to the transmitter transducer. If close tolerance components are used then RV2 should tune the circuit between approximately 30 and 50 kHz, enabling the transmitter to be set up for most efficient operation. The power supply to IC6 is decoupled by C15 directly at the chip.

The reflected ultrasonic waves are picked up by the receiver transducer. Signals from this are coupled directly to the non-inverting input of op-amp IC2. The 'Q' of the transducer is lowered by the shunt resistance of R3, facilitating 'setting-up' the unit. IC2 is a non-inverting amplifier with a gain of 100 at 40 kHz. Gain versus frequency is tailored for best response by C4 and C5. IC3, directly coupled via R6, operates as an inverting amplifier with a gain of 10. Compensation is provided by C6. The low frequency signals resulting from Doppler shifts are demodulated from the 40 kHz signal by the network around C9. They are then amplified by IC4. The gain of this stage is made variable by adjustment of RV1, enabling overall sensitivity of the unit to be controlled.


The AC output from IC4 is integrated by C12 and the associated network. When the voltage across C12 exceeds the upper threshold of the IC5 input, transistor Q1 will be driven on and the load energised. One section of IC5 is connected directly to IC4's output and drives the LED which indicates the major excursions of IC4's output. This is of considerable use when 'setting-up' the unit. Components R15 and C13 provide a delay following switch-on before the alarm becomes active.

The values of C12, R13 and C13, R15 may be changed to suit your particular requirements. For some applications, IC5 and its associated components may not be required. In such a case, they may be omitted and an output taken directly from IC4.

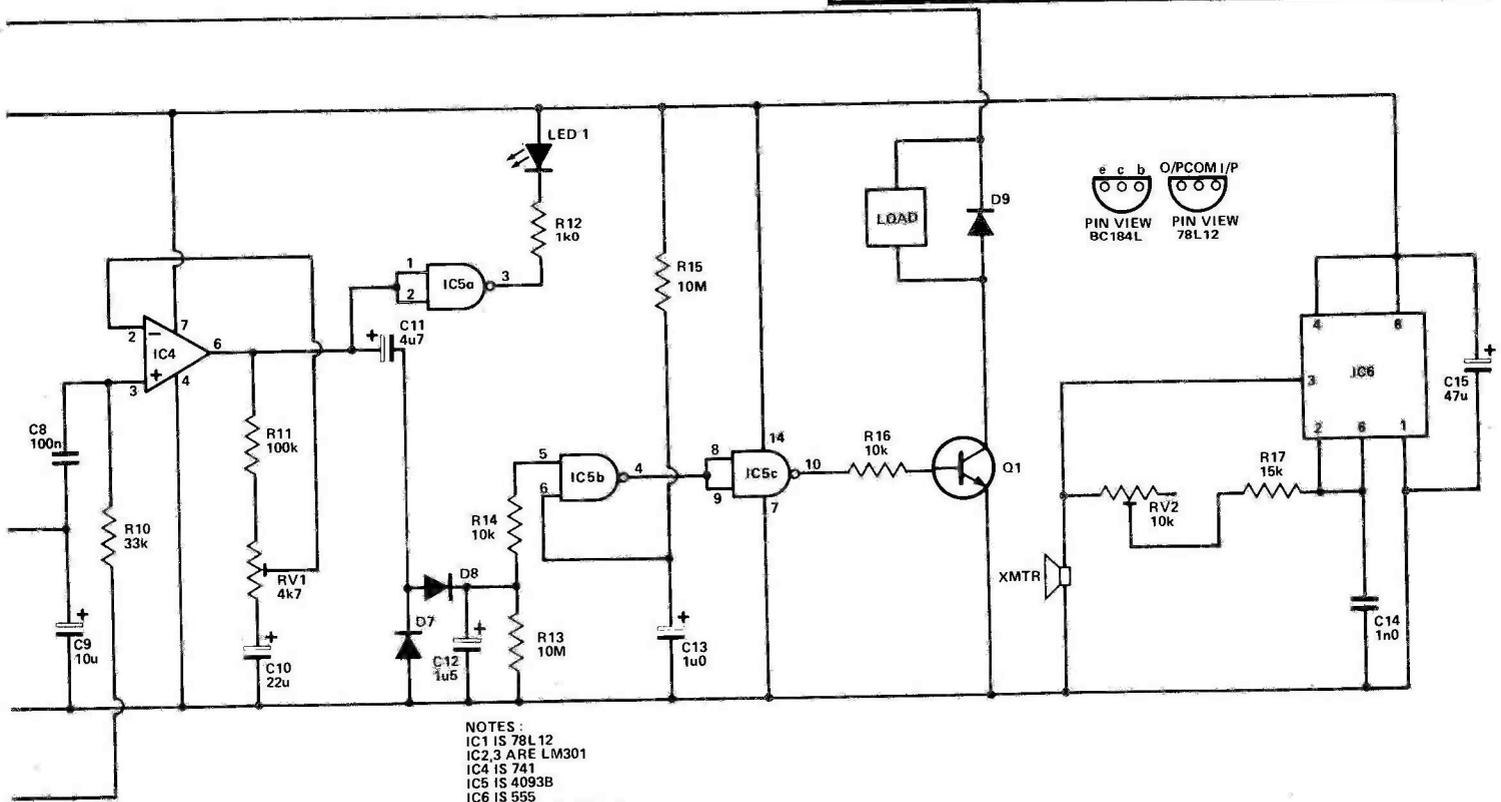The power supply for the unit is utterly conventional and needs no description here. Current consumption will depend on the load employed. The circuit draws only about 10 mA when unloaded.



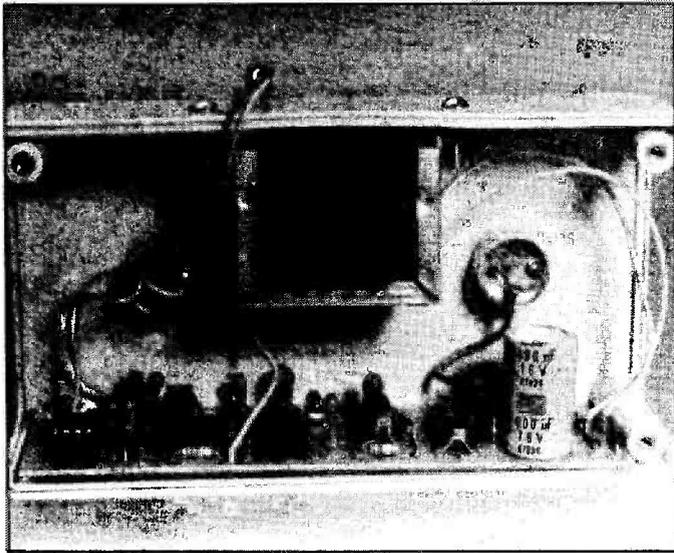- NOTES:
 IC1 IS 78L12
 IC2,3 ARE LM301
 IC4 IS 741
 IC5 IS 4093B
 IC6 IS 555
 D1,2,3,4,9 ARE 1N4001
 D5,6,7,8, ARE 1N4148
 Q1 IS BC184L
 LED 1 IS ANY LED
 XMTR RCVR ARE 40kHz TRANSDUCER PAIR



A behind-the-scenes view of the ET1 Ultrasonic Burglar Alarm. The two transducers can be held in place by a couple of spots of that well known contact adhesive. Note the use of the screened cable to connect the receiver transducer to the PCB. The single board contains power supply components together with transmitter and detector circuits, making the unit self-contained no-add-on-supplies or peripheral 'black boxes'. Note the use of IC sockets on the PCB. It's worth the expense. The board, transformer and transducers all fit neatly into a standard verocase (see Buylines).

demodulating the ultrasonic carrier. The frequency of the heterodyne depends on the speed of the moving target and its direction. Consequently the unit is most sensitive to objects moving directly towards or away from the sensors. A person walking directly towards the unit will normally produce heterodynes in the 0 to 30 Hz range. Higher frequencies are generated by the faster moving limbs, swinging arms and legs, for example.

A drawback with systems of this type is that they are sensitive to any movement, including swinging doors, fluttering curtains and even convection air currents from heating or air conditioning systems. However, by careful positioning of the unit, these problems can be largely overcome.

Construction

Although any method of construction can be used, our PCB provides a convenient and practical solution. Use of a PCB helps to prevent possible problems with instability as the ultrasonic amplifier has considerable gain. Only one wire link is needed and this should be soldered into place first, followed by the IC sockets (use them! It doesn't cost much and it can save lots of time afterwards), resistors, capacitors and semiconductors. Watch out for the polarity of the capacitors and semiconductors.

Current consumption of the unit is low; most of the current used will be that required by the load and a suitable transformer rating can be calculated from this. Flying leads connect the transducers to the board. Use shielded cable for the receiver connection; it doesn't matter for the transmitter. Note that a wire lead is required to return the load to the unregulated supply. The specified driver transistor will sink in excess of 100 mA.

When connecting the transducers, take care not to overheat them. A quick soldered joint should not cause any problems. Although the transducers are sensitive to mechanical

PARTS LIST

RESISTORS

R1,2,5,6,7,14,16	10k
R3	47k
R4	1M0
R8,11	100k
R9	4k7
R10	33k
R12	1k0
R13,15	10M
R17	15k

POTENTIOMETERS

RV1	4k7 miniature horizontal preset
RV2	10k miniature horizontal preset

CAPACITORS

C1	1000u electrolytic
C2	220n polycarbonate
C3,9	10u tantalum
C4,6	4p7 ceramic
C5	1n0 ceramic
C7,12	1u5 tantalum
C8	100n polyester
C10	22u tantalum
C11	4u7 tantalum
C13	1u0 tantalum
C14	1n0 polystyrene
C15	47u tantalum

SEMICONDUCTORS

IC1	78L12
IC2,3	LM301
IC4	741
IC5	4093B
IC6	555
D1,2,3,4,9	1N4001
D5,6,7,8	1N4148
Q1	BC184L
LED 1	any LED

MISCELLANEOUS

Ultrasonic transmitter-receiver pair, 12 V transformer, case.

vibration, no special mounting precautions will normally be needed. We fixed ours to the case with a few dabs of contact adhesive and that worked fine.

Setting Up

If you have an oscilloscope, then setting up will be very easy. Even without one, it will not be too difficult; in fact a small screwdriver is all you need. With power applied, adjust RV2 for maximum indication of signal from pin 6, IC3. If you don't have a 'scope then connect a voltmeter across C9 and adjust for a maximum here. You will probably find two positions for RV2 which produce a high reading. Use either. This operation tunes the transmitter to about 40 kHz; the operating frequency of the transducers. The required sensitivity may now be set by adjustment of RV1. Too much sensitivity will lead to the unit being triggered by fluctuating air currents, low flying bats, etc and LED 1 has been included to indicate large signals at IC4's output. You will soon find the best operating position for your unit. Avoid placing the unit near fires, radiators, etc and keep the area near the sensors clear as this could otherwise severely restrict sensitivity. Overall range will depend on the target and the working environment. Hard, reflective surfaces are best.

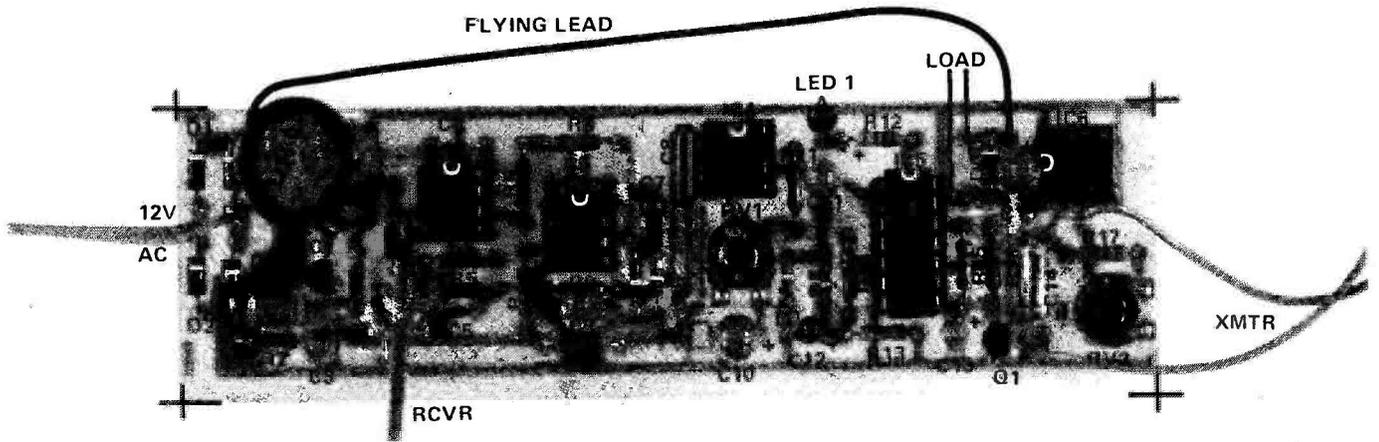


Fig.3. Component overlay.

Soft furnishings absorb the energising beam and fluttering curtains or swaying houseplants can generate considerable 'noise'. When first operating the unit, you may find it useful to connect an audio amplifier to the output of IC4 to monitor the 'noise'. A person's approach will be signalled by a rhythmic whooshing sound. We have not researched whether the unit is less sensitive to the gentler (and softer) sex. Why not build one and find out.

BUYLINES

We built our ultra-alarm in a verocase no. 202-21030K. Suitable ultrasonic transducers can be obtained from Dataplus Developments, 81 Cholmeley Road, Reading, Berks.

ETI

3½ DIGIT LCD MULTI-METER KIT

NEW


Build the Practical Electronics handheld DMM. This superb product offers professional precision with extended battery life. Five function operation (AC and DC VOLTS, AC and DC CURRENT, RESISTANCE) with ability to check diodes. 0.5" LCD display with 'Battery Low' warning. Auto-polarity, Auto-zero. Full protection against transients and overloads with ability to withstand mains on any range. 0.5% basic DC accuracy and 15 different ranges. It measures AC/DC voltages from 0.1mV to 500V. AC/DC current from 0.1µA to 2A. Resistance from 0.1Ω to 2MΩ. 200 hour battery life.

The Kit contains all parts needed to construct the multimeter plus assembly instructions, battery and test leads.

We also offer a calibration service (£5.00 + VAT) and a trouble-shooting and calibration service (£7.50 + VAT). Various other component parts are also available as listed.

The multimeter is also available fully assembled and calibrated at a cost of £39.70 + P&P + VAT.

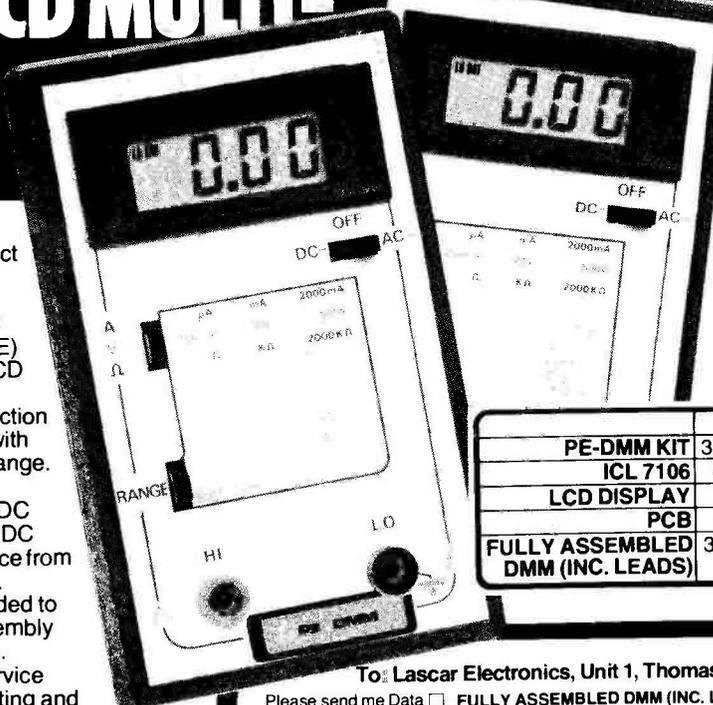Lascar Electronics Ltd., Unit 1, Thomasin Road, Basildon, Essex. Telephone No: Basildon (0268) 727383.



**FEATURED
AS A
PROJECT IN
PRACTICAL
ELECTRONICS**

	£	P & P	VAT	TOTAL
PE-DMM KIT	32.95	1.00	5.09	39.04
ICL 7106	8.95	0.50	1.42	10.87
LCD DISPLAY	7.95	0.50	1.27	9.72
PCB	4.95	0.50	0.82	6.27
FULLY ASSEMBLED DMM (INC. LEADS)	39.70	1.25	6.14	47.09

To: Lascar Electronics, Unit 1, Thomasin Road, Basildon, Essex.

Please send me Data FULLY ASSEMBLED DMM (INC. LEADS) £47.09
 PE-DMM KIT £39.04 ICL 7106 £10.87 LCD DISPLAY £9.72 PCB £6.27

Name _____


Address _____

Tel. No. _____

I enclose cheque/P.O. value _____

AT BLINKIN' LAST! COLOURBOARD II

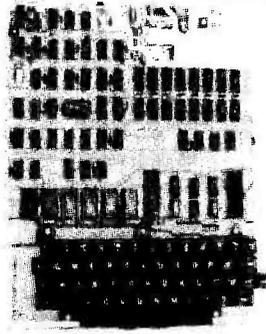THE NEW 50HZ COLOUR VERSION OF OHIO SCIENTIFIC'S SUPERBOARD II IS HERE AND LIKE A TON OF BRICKS DOWN CRASHES THE PRICE OF STANDARD SUPERBOARD II.



50HZ UK BLACK AND WHITE SUPERBOARD II

£159.95 + VAT POST FREE
COLOURBOARD II £205 + 15% VAT




THE UNIQUE SPECIAL OFFER YOU CAN'T RESIST

- ★ ★ ★ ★ ★ ★ ★ ★ ★ ★
- ★ If bought with superbord or colour board these items are at the reduced prices shown first. Also sold separately at the bracketed prices. Add 15% VAT.
- ★ Modulator and power supply kit £7.95 (£11). 4K extra ram £20 (£24). Case £23 (£26). Cassette recorder £13 (£15).
- ★ ★ ★ ★ ★ ★ ★ ★ ★ ★


WE CAN CONVERT YOUR SUPERBOARD TO COLOURBOARD. SEND A SAE FOR DETAILS

SINCLAIR PRODUCTS

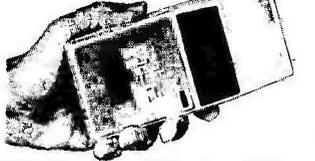

PPM200 £51.95, case £2.07, adaptor £4.20, connector kit £13.95. Microvision TV £89, mains adaptor £6.88. POM35 £34.73, mains adaptor £4.20, case £2.07. DM350 £76.70, DM450 £102.17, DM235 £65.58. Accessories for all 3 models — rechargeable batteries £7.99, mains adaptor/charger £4.20, case £8.90. Enterprise prog calculator £19.95. New SC110 10MHz oscilloscope £144.95.


COMPUTER GAMES

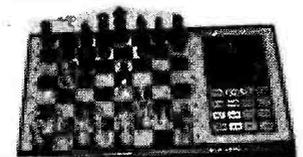

New Sensory Chess Challenger 8 £109. Chess challenger 7 (illustrated) £75. Chess champion 6 £49.95. Checker challenger 2 £39. Star Chess £82. Grandstand video entertainment computer £79.95. Videocarts £12.80. Phillips G7000 Atari Videocomputer £129. £138. Video paks £12.95. Atari Videocomputer £129. Cartridges £14.85 (except chess £43.95 and backgammon £33.95).

TV GAMES

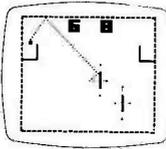AY-3-8500 chip £5.95. Kit £4.26. Stunt cycle AY-3-8780 chip £9.14, kit £4.95. 10 game paddle 2 AY-3-8600 chip £7.95, kit £7.03. Modified shoot kit £5.28. Colour generator kit £9.05.



MAINS TRANSFORMERS

6.0-6V 100ma 80p, 1 1/2 £2.80. 9.0-9V 75ma 80p, 1 £2.40. 2a £3.94. 12.0-12V 100ma 99p, 1 £2.90. 15.0-15V 1a £3.15.

JC12 and JC20 AMPLIFIERS

Integrated circuit audio amplifiers with data and printed circuits. JC12 6 watts £2.08. JC20 10 watts £3.54.

CONTINENTAL SPECIALITIES

PRODUCTS
EXP300 £6.61. EXP350 £3.62. EXP325 £1.84. EXP650 £4.14. EXP4B £2.64.

STABILIZED POWER KITS

The first price is for kit without transformer, the bracketed price includes transformer. TTL computer supplies 5V 2A £3.13 (£7.44). 5V 4A £5.12 (£12.00). 8-way types 3/4V/6/7V/9/12/15/18V 100ma £1.84 (£2.60). 1A £3.30 (£9.60). 2A £5.60 (£9.84). Variable voltage models 2-18V 100ma £1.84 (£2.60). 1-30V 1A £3.30 (£9.75). 1-30V 2A £5.60 (£12.10).

PRINTED CIRCUIT MATERIALS

PC etching kits — economy £2.42, standard £4.78. 40 sq inos pcb 45p. 1 lb FeCl £1.50. Etch resist pens — economy 50p, dalo 84p. Drill bits 1/32" or 1mm 34p. Etching dish 82p. Laminate cutter £1.20.

BI-PAK AUDIO MODULES

AL30A £4.53. PA12 £9.31. PS12 £1.75. TS38 £2.70. S420 £27.90. AL60 £5.62. PA100 £19.24. SPM80 £5.26. BM180 £6.08. Stereo 30 £23.94. AL80 £8.56.

2114

Full spec, memory chips
Low current, 250NS
Only £3.45

COMPONENTS

IN4148 0.09p. 1N4002 3.1p. 723 14 di 33p. NE555 8 dir 24p. 741 8 dir 18p. bc547, bc549, bc182, bc184, bc212, bc214, bc548 5.5p. tip31c, tip32c 36p. tip41c 40p. bc132 2.7p. plastic equiv bc12 4.5p. fuses 20mm x 5mm cartridge 15, 25, 5, 1, 2, 3, 5amp quickblow 2p. resistors 5% 1/4W E12 10R to 10M 1p, 0.8p for 50+ of one value. polyester capacitors 160V 0.15, 0.68mf 2.3p, 1mf 4.0p, 0.1mf 3.0p, 0.22, 0.33mf 3.3p, 0.47mf 4.0p, 15, 33mf 4.9p, 47mf 6.0p. polystyrene capacitors E12 63V 10 to 1000pf 3p, 1mf to 10m 4p. ceramic capacitors 50V E6 22pf to 47n 2p. electrolytic capacitors 50V 5, 1, 2mf 6p, 25V 5, 10mf 6p, 16V 2V, 33mf 6p, 47, 68mf 3.5p, 1000mf 3p, 330, 470mf 9p, 1000mf 11p, zeners 400mw E24 2V7 to 33V 7p. preset pots sub-miniature 0.1W horiz or vert 100 to 4M7 7p. potentiometers 4W 4K7 to 2M2 kg or Tin single 28p, dual 71p, 1/2" red LEDs 9.7p, ic sockets 8 di 8.7p, 14 di 10.1p, 16 di 12p.

BATTERY ELIMINATORS

3-way types with switched output and 4 way multi jack — 3/4V/5V 100ma £2.67, 6/7 1/2V/9V 300ma £3.14. 100ma radio type with press-stud connectors 9V £3.77, 6V £3.77, 4V 9V £3.77, 9+9V £4.99, 6+6V £4.99, 4 1/2+4 1/2V £4.99. cassette recorder mains unit 7 1/2V 100ma with 5 pin din plug £3.87. fully stabilised type 3/6/7 1/2V/9V 400ma £6.5V £1.92, 9+9V £1.92, cassette type 7 1/2V 100ma with din plug £1.49. heavy duty 13-way types 4 1/2/7 1/2/8 1/2/11/13/14/17/21/25/28/34/42V 1A £5.52, 2A £8.80. car converter input 12V dc, output 6/7 1/2V/9V 1A stabilized £1.35.



BATTERY ELIMINATOR KITS

100ma radio types with press-stud connectors 4 1/2V £1.49, 6V £1.49, 9V £1.49, 4 1/2+4 1/2V £1.92, 6+6V £1.92, 9+9V £1.92, cassette type 7 1/2V 100ma with din plug £1.49. heavy duty 13-way types 4 1/2/7 1/2/8 1/2/11/13/14/17/21/25/28/34/42V 1A £5.52, 2A £8.80. car converter input 12V dc, output 6/7 1/2V/9V 1A stabilized £1.35.

S-DECS AND T-DECS

S-Dec £3.79. T-Dec £4.99. u-Dec £4.69. U-Dec £7.16. 16 di adaptor £2.31.

SWANLEY ELECTRONICS

Dept. ET1, 32 Golsold Road, Swanley, Kent BR8 8EJ.

Mail order only. Please add 35p postage. Prices include VAT unless stated. List 27p post free. Overseas customers deduct 13%. Official credit orders welcome.

<p>MOTORS. 1.5V Medial motor 22P. 5oh. min. Big jack 115V DC 3 rpm motor 32p. Replacer 8 track 12V DC motor 55p. General motor 2 1/2 rpm. 75p. 115V AC 4 rpm motor 55p. Cassette motor 5-9V DC 4z, 400p. 70p. 9V DC Cassette motor 95p. 9V Cassette motor. new standard 1p. 15p. £1.25.</p>	<p>RECORDING TAPE. Low noise mylar. supplied unboxed: 7" 1200' £1.00. 7" 1800' £1.45. 10" 3600' £5.00. BLANK CASSETTES. 650 10 for £2.75. 650 10 for £3.85. LOW COST 1/4" TAPE-SPLICER £1.85.</p>	<p>SPECIAL OFFER DEC TYPE BREADBOARDS. Micro DEC "A" with 2 1/2 pin DIL carriers £3.95. Micro DEC "B" with 2 integral 16 pin DIL carriers £3.95. Both breadboards approximately half original selling price.</p>	<p>MOTOROLA PIEZO ELECTRIC TWEETERS  3" direct radiating type £3.65 3 1/2" flush mounting spec horn £4.50</p>	<p>TRANSFORMERS. All 240V DC primary (postage per transformer is shown in brackets after price). MINATURE RANGE 6.0-9V 100ma. 9.0-9V 75ma. 12.0-12V 50ma at 75p each (15p). 12V 200ma 75p (15p). 0.6-0.5 200ma £1.20 (20p). 6V 500ma £1.10 (22p). 12V 2A £2.35 (45p). 12V 4A £2.85 (45p). 15.0-15V 1A £2.25 (45p). 30.0-30V 1A £2.85 (45p). 20.0-20V 2A £3.65 (54p). 0.12-15-20-30V 2A 1A 75p (54p) 20V 2.5A £2.35 (54p).</p>	<p>KRT101 M/METER. 1,000 opp. 1KV AC/DC Volts. 150ma DC current. Resistance 0-2.5k. 0-100k. £4.35.</p>
<p>BUZZERS. Miniature solid state type. 33x17x15mm. 7ohm at 3 volt. 15ma drain. operates at 1.5V DC. 75p each. (DUN) 12 volt buzzer 50x20mm 83p. Carina 12V DC Miniature alarm siren £7.65. 6-volt version 55p. 12V DC SIREN. all metal rotary type. high pitched wail. £3.50. Battery alarm siren. 12V DC. 7mm plastic unit with mounting bracket. 06 x 70mm £4.50.</p>	<p>TOOLS. SOLDER Sucker. good suction. white nozzle. £4.99. Side cutters 5" £1.45. 6" £1.45. NEMO DRIVER or LONG 50p. NIYAMA 16 pin IC test clip £1.85. 5 PIECE precision screwdriver sets. individual handles. £1.05. JUMPER TEST LEAD SETS 10 pairs of leads with insulated crocodile ends and 50p. CRYMPING TOOL. a combination tool for crimping red, blue and yellow terminations also incorporates a wire stripper (3 gauges) and wire cutter. insulated handles. only £2.30.</p>	<p>COPPER LAMINATED PRINTED CIRCUIT BOARD. Fibreglass Single Sided type (approx. 2mm thick) 150x150mm 40p. 200x100mm 55p. 250x145mm 65p. Double-sided Fibreglass 1mm thick. 180x135mm 45p. PAXOLIN BASED TYPE: (2mm thick). 180x135mm 40p. 280x200mm 50p.</p>	<p>PIEZO TWEETERS. require no crossover and can be used with systems up to 100 watts. Frequency response 3.8 to 20KHz.</p>	<p>TRIAN XENON PULSE TRANSFORMERS. 11 (EPH) type/32p. 11plus 1 sub. min. pcb mounting 65p.</p>	<p>NH55 M/METER. 2,000 opp. 1KV AC/DC Volts. 100ma DC. Resistance 0-10k. 0-1 MEG. £5.50.</p>
<p>RELAYS. 2 types both operate on 12V DC. sealed plastic case type. 1-350 ohm with 2 make 5 amp contacts 75p. 2-1,000 ohm with 2 changeover 1 amp contacts 75p.</p>	<p>MICROPHONES. Min. Tin. pin. Oni. uses dead aid battery (supplied) £4.95. Low cost condenser ECM105 0ma. 600ohms. on/off switch standard jack plug. £2.95. EWS607 Condenser. on. 600ohms. 30 (8kt). High polished metal body. £7.95. DYNAMIC stick microphone dual imp. 600ohms or 20k. 70-15KHz. attractive black metal body. £7.75. EWS6 Condenser. cardiac. on. 600ohms or 50k. heavy chromed copper case. £12.95. DYNAMIC P.A. Mike. mobile radio etc. 1000 ohm 50k imp. £10.50. CASSETTE replacement microphone with 2.5/3.5 plugs £1.35. INSERT crystal replacement 35x10mm 40p. GRUWING Electronic inserts. with built in FET preamp 3.6V DC. £1.00.</p>	<p>TAPE HEADS. Mono cassette. £1.75. Stereo cassette £3.90. Standard 8 track stereo £1.95. 8SH MM 1330 1/2 track 50p. BSR 3AP90 1/4 track £2.10. TO10 dual head assembly 2 heads both 1/4 track R/P with built in erase £1.25.</p>	<p>RANK ARENA slotted cartridge pre-amplifier modules. suitable for magnetic cartridges. new, supplied with connection details. £1.95.</p>	<p>PROJECT BOXES. Sturdy ABS black plastic boxes with brass inserts and lid. 75x56x35mm 65p. 95x7x35mm 75p. 115x9x37mm 87p.</p>	<p>YER0 HAND HELD BOX. White ABS. 24in x 3.7in tapered, with screws 60p each.</p>
<p>SPECIAL OFFER SEMICONDUCTORS. 2N582 300p. 18p. B3304 opto isolator 25p. CA1310 95p. TDA005 50p. TDA1151 25p. 741 22p. 723 35p. NE555 24p. AD161/2 70p. 28p. 2N3055 36p. TDA005 10 for 35p. BD238 28p. BD438 28p. 7418 35p. 2N414 75p. TIL305 alpha numeric display £2.50. MANSA 3mm LED displays 45p. Min. Logic 30p. LEDs 0.2" CLEAR 15p. GREEN 12p. RED 10p. infra red clear LED 50p. MPU311 PUTs. ADV. 200ms. 375mA 15p. 2N3773 £1.70. Texas RI038 (T03) Power trans. 50p. TAG4443 32x 45p.</p>	<p>NEW STOCK ITEM — We are now stocking Expo mini hand-held drills. these are a precision British-made tool. Ideal for P.C. board drilling, model makers etc. They operate on 12V DC. Drill bit supplied in plastic hinged case, with drill and 21 accessories. drills, adapters, reamers, buffers, etc. complete kit only £14.25. Drill only £7.25. Drill stand to suit vertical drill press £12.95 (postage 6p).</p>	<p>SWITCHES. Sub. min. Toggle. SPST 8x5x7mm. 42p. DPDT (8x7x7) 55p. DPDT Centre off (12x11x7mm) 77p.</p>	<p>FINNED HEATSINKS. Supplied undrilled 4er thick. 27mm high. 75x124mm 60p. 150x124mm 95p. Smaller version 2.7mm thick. 75x108mm 48p. TRANSISTOR SOCKETS T05 or T018 9p each. T03 type 15p each.</p>	<p>YER0 POTTING PLASTIC boxes with lid and screws 70x50x20mm. black. 43p each.</p>	<p>YFN360 M/METER. 20,000 opp. 1KV AC/DC Volts. 250ma DC. 4 resist. each ranges 1c 20 Mag. also has built-in transistor tester with leakage and gain ranges £12.50.</p>
<p>LED VU METERS. Utilize sophisticated logic control circuit with adjustable rise and decay times via external capacitor. Spec: Response — 20Hz to 100KHz. Tolerance within ± 0.1k. operates on 12-15V DC. 82mm long 54mm high. MONO VERSION £6.95. STEREO VERSION £10.95</p>	<p>ROTARY SWITCHES (w/rot) 3P4W. 4P3W. 2P6W and 1P12W all 35p each.</p>	<p>PUSH SWITCHES (16x6mm). red top. push in make 15p each. push on break version black vinyl 17p each.</p>	<p>ALUMINIUM PROJECT BOXES. 18 S.W.G. with lid and lid screws. AB1 3x2x1 52p. AB2 4x3x1.5in 62p. AB3 4x3x2in 66p. AB4 6x4x2in 74p. AB5 6x4x3in 82p. AB6 6x6x2in £1.05. AB7 8x6x3in £1.65.</p>	<p>CLIFF CLICKTEST. 13 amp mains connector. Ideal for workshop, etc. provides rapid and safe mains connection. tough moulded case and lid with neon indicator and fuse. £5.15.</p>	<p>SPECIAL OFFER DEMAGNETIZER. Curved probe type. suitable for rail to rail or cassette machines. operates on 240V AC only £1.95.</p>
<p>ANTEX SOLDERING IRONS. All 240V AC. Model C 15 watts £3.95. Model ICL 17 watts £3.95. Model 225 25 watts £3.95. S73 SOLDERING IRON STAND. suits all Antex irons £1.65.</p>	<p>16 pin D.I.L. SWITCHES only 42p each.</p>	<p>SLIDE SWITCHES all DPDT 15x8x12mm 13p. 16x11x8mm 13p. 22x13x8mm 13p. 22x13x8 centre off 14p. Multiple alder double action (12 lags) 29x9x11mm 25p.</p>	<p>MURATA TRANSDUCERS. REC/SENDER. MA-01L 40KHz £3.50 pair.</p>	<p>POWER SUPPLIES. Switched type plugs into a 13 amp socket has 3-4, 5-6, 7.5 and 9 volts 0.5 amp at either 100 or 400ma. detachable £3.45. MC2448 stabilised power supply 3-6/7.5V DC at 400ma. has polarity reversing and on off switch and is fully regulated to give exact voltage from no load to maximum current £5.50.</p>	<p>TMK500 M/METER. 30,000 opp. 1KV AC/DC Volts. DC current to 10 amp. Resistance to 60 meg in 4 ranges. also has built-in buzzer for continuity testing. £20.95</p>

Terms. Cash with order (official orders welcomed from colleges etc) 30p postage please unless otherwise shown. VAT inclusive prices. S.A.E. for illustrated lists.

PROGRESSIVE RADIO

31 CHEAPSIDE, LIVERPOOL L2 2JD
ALL ORDERS DESPATCHED BY RETURN POST



COMPUTER WAREHOUSE

NOW OPEN
MONDAY-SATURDAY
9.30-5.30

THE CHIPS ARE DOWN MOSTEK, INTEL, NEC, MOTOROLA I.C. PRICES SLASHED!

A massive purchase of brand new "state of the art" data processing equipment enables us to offer the following chips at never, and we mean never to be repeated prices.


8085A-2	Central Processor	£11.99
8155C	256x8 Static Ram	£8.95
8253C	Programmable Interval Timer	£8.95
8255A	Programmable Peripheral Interface	£9.95
8259A-8	Programmable Interrupt Control	£4.75
8755A	2Kx8 Eprom 16 I/O Lines	£34.50
2716	5volt Single Rail 2Kx8 Eprom	£10.25
2708	1Kx8 Eprom	£4.95
4116	16K Dynamic 250ns Rams 8 for	£28.50
2102	1K Static 450ns Rams 8 for	£6.75
1702	256x8 Eprom	£3.75

And Remember All Chip Prices Include V.A.T.

All above I.C.s are brand new or removed from new unused socketed P.C.B.'s. Eproms supplied washed.

All full spec. and guaranteed

HIGH DEFINITION 9" VIDEO MONITOR

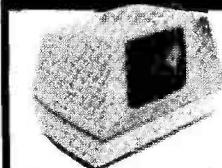

This superb ex computer video monitor was originally used as an information display on large computer systems. It features all silicon electronics, attractive style, housed in shatterproof two colour A.B.S. case with controls under flap. 240v operation, 625 lines, 75 or 50 ohm composite video input 50hz - 20 mhz frequency response. Supplied complete in good condition but untested and unguaranteed.

Connect direct to your M.P.U. at only
Require for carriage charge **£47.50**

HY GRADE SMOOTHING CAPS

MULLARD	1500mf	100v 60p	3300mf	40v 50p
PLESSEY	3300mf	63v 70p	1mf	600v MYLAR 28p
MALLORY	10,000mf	15v 11t	22,000mf	16v £1.10
SPRAGUE	100mf	250v 45p	2100mf	200v £2.50

*Ex equipment tested †P.P. 40p

SEMICONDUCTOR 'GRAB BAGS'

Amazing value mixed semiconductor components. Include transistors, digital, linear I.C.'s, triacs, diodes, bridge recs. etc. All devices guaranteed brand new, full spec. with manufacturers markings, fully guaranteed. 50 + BAG £2.95 100 + BAGS £5.15

MUFFIN FANS

Keep your equipment Cool and Reliable with our tested ex equipment "Muffin Fans" almost silent running and easily mounted. Available in two voltages 110 V.A.C. £5.05 + pp 65p OR 240v A.C. £6.15 + pp 65p DIMENSIONS 4 1/2" x 4 1/2" x 1 1/2"

ELECTRONIC
COMPONENTS
& EQUIPMENT

66%

DISCOUNT

Due to our massive bulk purchasing programme which enables us to bring you the best possible bargains, we have thousands of I.C.'s, Transistors, Relays, Cap's, P.C.B.'s, Sub-assemblies, Switches, etc. etc. surplus to our requirements. Because we don't have sufficient stocks of any one item to include in our ads., we are packing all these items into the "BARGAIN PARCEL OF A LIFETIME" Thousands of components at giveaway prices! Guaranteed to be worth at least 3 times what you pay plus we always include something from our ads. for unbeatable value!! Sold by weight

2.5kls £ 4.75 + pp £1.25 5kls £ 6.75 + pp £1.80
10kls £11.75 + pp £2.25 20 kls £19.99 + pp £4.75

DYNAMIC RAM SCOOP!

INTEL 1103A 18 pin DIL 150 ns IK Rams guaranteed full spec. complete with data.

8 for £2.99 16 for £4.99
32 for £8.50 64 for £13.99
18 pin DIL sockets 8 for £1.60

SHUGART SA800

8" Floppy Disk Drives
from **£150.00** + VAT
as new **£225.00** + VAT

SUPERVALUE P.C.B. SPECIAL

Another great buy. Board contents include 62 Digital I.C.'s all located in 14 pin D.I.L. sockets. Original cost over £90, our price only **£4.95 + PP 65p.**

OPTO SMASH!

TIL 302/MAN 7 7 segment LED readout common anode direct drive (via resistors) from 7447 £1.10 each
TIL 119/OC72 Darlington opto isolator 3 for £1.00.
TIL305 0.3" 7 x 5 matrix LED alphanumeric readouts £3.75 each.
PHOTO TRANSISTOR
Fairchild FPT-100 NPN silicon 30v 25ma. 4 for £1.00.

DISPLAY I.C. AND TRANSISTOR BARGAINS NEVER CHEAPER

All I.C.'s and Transistors by well known manufacturers and fully guaranteed. No fall outs. Comprehensive data on I.C.'s 15p per type
2N4351 N channel MOS FET.
2N4352 P channel MOS FET
60p each £1.00 per pair.
HIGH VOLTAGE NPN POWER SWITCHING transistors BVcbo 600v BVceo 500v BVebo 15v 1c 5 amps Pc 125 watts HFE 60 typ ft 2.5 mhz ideal invertors. etc. TO3 £1.60 each 4 for £5.40.
BF258 NPN 250v @ 200ma 45p each 3 for £1.08.
I.R. BSB01 2.5 amp 100v bridge rec. P.C. mount long leads 35p each 4 for £1.08.
IN4998 4 amp 100v P.C. mount diodes long leads 14p each 10 for £1.10.
LM309K + 5v 1.2 amp regulator £1.10 each 6 for £5.35.
AGFA C10 computer grade cassettes complete with library cases 68p each, 10 for £5.50
IN4004 SD4 1 amp 400v diodes 7p each 18 for £1.00.
I.R. 12 amp BRIDGE RECS. 400 Volt £1.25 each.

POWER OARLINGTON SCOOP!

MJ1000 NPN 60v 90w 8 amps TO3 35p each
2N6385 NPN 80v 100w 10 amps TO3 £1.25 each
MJ4030 NPN 60v 150w 16 amps TO3 £2.25 each

DECADE 0-9 THUMBWHEEL SWITCHES.

Stackable, gold plated contacts, dim. 33 x 43 x 8 mm. 90p each, 10 for £5.50.
Miniature Continental Series 12VDC 4c/o plug in relays £1.30 each.
Greenpar 50Ω BNC Chass. socket single hole fixing 65p
C90 Audio Cassettes screw type construction 45p each 3 for £1.00.
Bulbs 24v 14 watt white frosted S.B.C. 8 for £1.00
Bulbs 12v 100 watt clear, base similar S.B.C. 45p each.
S.B.C. Bulb Holders All steel cad. plated panel mount easily fixed via nut and round hole, ideal disco displays, scoreboards, etc. 4 for £1.10.
VMOS VMP1 Siliconix TO3 power FET 0-60v, DC-200 mhz will drive direct from CMOS etc. £1.50 each, full date 30p.
Heavy Duty Flat Insulated Earth Braid 100-200 amp braided tinned copper in heavy clear PVC sheath 50p per metre. £6 for 15 metres + PP £1 per 15 metres.
BULGIN miniature 6 way male chassis mount socket and matching free plug 60p each, 2 for £1.10.
Red L.E.D.'s full spec. 0.2" 14p each, 10 for £1.25.
Red L.E.D.'s (0.125" 10p each 10 for 80p)
Dynamic Stick Mics 600Ω with built in on/off switch complete with lead and min. jack plug £1.15 each, 10 for £11.00.
TOS HEATSINKS "Thermaloy" black anodised press on aluminium finned type 18p each, 8 for £1.00.

I.B.M. I/O GOLFBALL TYPEWRITERS

Still the cheapest way to superb quality print, when interfaced they will print at 15 C.P.S. and give indistinguishable copy as if typed by a highly paid secretary! A large range of type fonts make them ideal for all word processor applications, and even without the computer they still function as a quality electric typewriter. Supplied in 2 grades.

1) Good general condition with I/O mechanics! **£295.00 + VAT** electrics may require modification for full correspondence use. Complete with interface data-
2) Serviced, modified, and ready to go via aculab interface complete **£355.00 + CARR** + vat
ACULAB parallel to IBM inter- **£165.00 + CARR** face for Apple, Sorcerer, TRS80, etc. + VAT

BARGAINS GALORE!

In our walk round Warehouse
NOW open Monday to Saturday 9.30-5.30



Dept. E.T.I. 64-66 Melfort Rd., Thornton Heath, Surrey. **MAIL ORDER INFORMATION**
Telephone 01-689 7702 or 01-689 6800
Unless otherwise stated all prices inclusive of VAT. Cash with order. Minimum order value £2.00. Prices and Postage quoted for UK only. Where post and packing not indicated please add 40p per order. Bona Fide account orders minimum £10.00. Export and trade enquiries welcome. Orders despatched same day where possible. Access and Barclaycard Visa welcome.

In stock now test equipment, microprocessors, teletypes, transformers, power supplies, components, sig. gen's, motors, peripheral equipment, I.C.'s, tools, compasses, variacs, keyboards, transistors, microswitches, V.D.U.'s sub-assemblies + thousands of other stock lines. Just a mere fraction of our vast range, is displayed below: 100's of bargains for callers.

SUPER 77 KEY KEYBOARD KIT

We've done it again! We've purchased a large quantity of CPCLARE top quality keyboard reed switches plus full QWERTY keypad sets and thrown in a PCB to enable you to customise the keys just as YOU want them, just add and wire an encoder chip and you can arrange ASCII, BAUDOT, anything! Adding up to a quality keyboard which would normally cost around £100.00. Supplied with layout and assembly info at only **£26.99 + £1.50pp.**

HOW TO GET HERE

Victoria, London
Bridge or Holborn
Viaduct to
Thornton Heath.
1 minute from
Thornton Heath
Station.

POWER SUPPLY UNITS

5 VOLT 2.5/8 AMP TTL Made for TTL this compact ex computer systems unit features a 10 amp transformer. DC outputs of 5 volts @ 2.5 amps and 7.5 volts @ 5 amps are available. The 5v output is fully regulated and smoothed with electronic current limiting. May be easily modded for 5 volts @ 7-8 amps. Sold complete with circuit, believed working but untested. **£8.25 + £1.60pp.**

5 VOLT 3 AMP Ex computer systems, complete on one small chassis, features full regulation and crowbar over voltage protection. **£8.50 + pp 80p**

PRINTERS

CENTRONICS 101A 132 column Matrix printer, serial/parallel input **£525 + VAT**
DATA PRODUCTS 300 110 L.P.M. 80 column Barral printer, standard T.T.L. parallel interface **£650 + VAT**
Many other printers available from **£45.00**

KEYBOARDS

★ **76 KEY ASCII CASED** ★

At last a coded 76 key cased ASCII keyboard at the right price. Housed in an attractive light grey case, this unit was originally made for ICL for use in airport reservation systems so only the BEST parts were used. It has everything, we think, to meet your most exacting requirements, numeric keypad, upper and lower case, cursor controls, single 5 volt rail, serial and parallel data outputs, plus eight LEDs mounted on the case. Supplied with circuits, believed brand new, but may have minor scratches on cases.

Only **£43.50** + £1.60pp

★ LOW PRICE CHASSIS ★



A special bulk purchase enables us to offer the above keyboard at a lowest ever price. 49 coded keys enclosed into a direct TTL compatible 7 bit output. Features such as delayed strobe, 5 volt DC. single rail operation and rollover protection make this an absolute must for the MPU constructor! Supplied complete with connection diagram and edge connector, at a secondhand

"no time to test" price of only **£20.00** + P.P. **£1.60**

SUPER CASED VERSION Same as above spec. but housed in attractive two tone moulded, free standing case. Unit also includes an all TTL parallel to serial converter (no details) etc.

£27.50 + P.P. **£1.85**

TOROIDAL TRANSFORMERS

MP 240v pri. sec. 2 x 30v @ 4 amps 2 x 18v @ 1 amp £11.00 + p.p. £1.95
dimensions 4 1/2" x 7 1/2"
PM 240v pri. sec. 15.0 15 @ 2 amps dimensions 3" x 7 1/2" £4.95 + p.p. 99p
TM 240v/110v pri. sec. 15.0 15 8VA dimensions 2 1/2" x 1" £1.95 + p.p. 30p
All voltages measured off load

Plugs, Sockets & Connectors Cannon 'D' Range

Ways	Plug	Socket
9	£1.03	£1.26
15	£1.17	£2.01
25	£1.72	£2.58
37	£2.35	£4.14
50	£2.90	£5.46

25 way ex-equip. plug on socket £1.25
Amphenol 57 series 36 way plug £3.25

Edge connectors, gold plated

0.1" DS	85 way	£3.99
0.1" DS	45 way	£2.45
0.15" DS	56 way	£3.25
0.156DS	36 way	£2.00

All connectors easily cut to size
1000's of other connectors ex stock



Wilmslow Audio

THE firm for speakers!

SEND 50P FOR THE WORLD'S BEST CATALOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS ETC, AND DISCOUNT PRICE LIST.

AUDAX - AUDIOMASTER - BAKER - BOWERS & WILKINS - CASTLE - CELESTION - CHARTWELL - COLES - DALESFORD - DECCA - EAGLE - ELAC - EMI - FANE - GAUSS - GOODMAN'S - HARBETH - ISOPHON - I.M.F. - JORDON - JORDAN WATTS - KEF - LOWTHER - MCKENZIE - MISSION - MONITOR AUDIO - MOTOROLA - PEERLESS - RADFORD - RAM - ROGERS - RICHARD ALLAN - SEAS - SHACKMAN - STAG - TANNON - VIDEOTONE - WHARFEDALE.


WILMSLOW AUDIO

SWAN WORKS, BANK SQUARE
WILMSLOW, CHESHIRE SK9 1HF

Tel. 0625-529599 FOR MAIL ORDER AND EXPORT OF DRIVE UNITS, KITS, ETC.

Tel. 0625-526213 (SWIFT OF WILMSLOW) FOR HI-FI AND COMPLETE SPEAKERS.

HARD LABOUR?

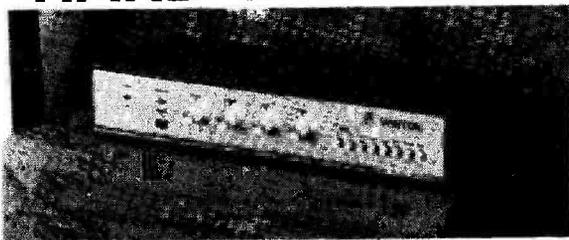

Not exactly, about 20 hours spent building the amplifier that was the success story of 1979, and has no peers in 1980.

The WINTON, 50+50 watts of real Hi-Fi using power Mosfet's and a specification and performance that is totally unprecedented in this price range.

You will find it an interesting and absorbing project, serve time and get your just deserts.

Act Now, send us a 12p stamp and we will send you a spec' sheet that will make you sit quietly for a while reflecting just how ordinary some amps really are, or get involved at once, send us your cheque for the best value in Hi-Fi kits around.

Power MOSFET's rule, ok?

COMPLETE KIT, of all parts necessary to build the P.W. WINTON **£133.50**

Order with complete confidence (C.W.O. only please) from:

T.&T. ELECTRONICS
Green Hayes, Surlingham Lane, Rockland St. Mary, Norwich,
NR14 7HH. Telephone 05088 632

PRICE INCLUSIVE OF V.A.T. & CARRIAGE.
Callers by appointment only

NEW CT4000 CLOCK/APPLIANCE TIMER KIT

The CT4000 has been designed to preset the state (on or off) of four outputs at four times per day for up to 7 days in advance, enabling the unit to control tape recorders, appliances, central heating, lights, etc. The times are set on a 0.1" high red LED display by means of a keyboard and the output states are displayed on four LEDs. Each output can switch up to 20mA at 9V. For mains loads use our Solid State Relay Kit (MK2). The kit includes a PCB, keyswitches, IC, 4 digit LED display, transformer, plus all other components and a screen printed and drilled box which can also accommodate up to 4 Solid State Relay Kits.

Size 10x12x4.5cms
Colour: Black

ONLY **£25.25**



D.V.M. THERMOMETER KIT

Based on the ICL 7106. This kit contains a PCB, resistors, presets, capacitors, diodes, IC and 0.5" liquid crystal display. Components are also included to enable the basic DVM kit to be modified to a Digital Thermometer using a single diode as the sensor. Requires a 3mA 9V supply (PP3 battery). **£20.75**

TOUCH CONTROL LIGHTING KITS

These KITS replace light switches and control up to 300 Watts of lighting. No rewiring. Inlaster depth boxes, insulated touchplates. Easy to follow instructions.

TD300K TOUCHDIMMER. Single touchplate with alternate action. Brief touch switches lamp on and off, longer touch dims or brightens lamps. Neon lamp helps find the switch in the dark. **£6.50**

TDE/K Extension Kit for TD300K for 2-way switching, etc. **£1.50**

TD300K TOUCHSWITCH & DIMMER. Single touchplate, small knob controls brightness. **£5.50**

TS300K TIME DELAY TOUCHSWITCH. Turns off after preset delay (2 secs. to 3 1/2 mins.) **£4.30**

LD300K Conventional Lightdimmer. **£2.90**

MINI KITS

These kits form useful subsystems which may be incorporated into larger designs or used alone. Kits include PCB, short instructions and all components.

MK1 TEMPERATURE CONTROLLER / THERMOSTAT. Uses LM3911 IC to sense temperature (80°C max) and triac to switch heater. **500W £3.20** **1KW £3.50**

MK2 SOLID STATE RELAY. Ideal for switching motors, lights, heaters, etc. from logic. Opto-isolated with zero voltage switching. Supplied without triac. Select the required triac from our range. **£2.80**

MK3 BAR/DOT DISPLAY. Displays an analogue voltage on a linear 10-element LED display as a bar or single dot. Ideal for thermometers, level indicators, etc. May be stacked to obtain 20 to 100 element displays. Requires 5 20V supply. **£4.75**

MK4 PROPORTIONAL TEMPERATURE CONTROLLER. Based on the TDA1024 Zero voltage switch. This kit may be wired to form a "burst fire" power controller or a "proportional temperature controller" enabling the temperature of an enclosure to be maintained to within 0.5°C. **1.5KW £5.25** **3KW £5.55**

MKS MAINS TIMER. Based on the ZN1034E Timer IC this kit will switch a mains load on (or off) for a preset time from 20 minutes to 35 hours. Longer or shorter periods may be realised by minor component changes. Maximum load 1KW. **£4.50**

INTEGRATED CIRCUITS

555 Timer	21p
741 Op. Amp	19p
AY-51224 Clock	£2.60
AY-51230/2 Clock/Timer	£4.50
AY-31270 Thermometer	£8.20
ICL 7106 DVM (LCD drive)	£7.00
LM377 Dual 2W Amp	£1.45
LM3795 Dual 6W Amp	£3.50
LM380 2W Audio Amp	80p
LM382 Dual/low noise Preamp	£1.00
LM386 250mW low voltage Amp	75p
LM1830 Fluid Level Detector	£1.50
LM2907 1/4 Converter (8 pin)	£1.40
LM2917 1/4 Converter (14 pin)	£1.80
LM3909 LED Flasher/Oscillator	55p
LM3911 Thermometer	£1.20
LM3914 Opt/Bar Driver	£2.10
MM74C91 1 1/4 digit display controller	£6.50
MM74C915 7 segment BCD converter	95p
MM74C926 4 digit counter with 7 seg o/p	£4.50
S5668 Touchdimmer	£2.50
S9263 Touchswitch 16-way	£4.85

DO MAGAZINE REMOTE CONTROL PROJECTS MAKE YOU SEE INFRA RED?



How many times have you considered building a remote control project but were put off by the dozens of ICs, special coils, lenses and other hard to get components, not to mention the need for a well equipped lab to set the unit up? T.K. ELECTRONICS have changed all that. Three ICs can build a sophisticated system that requires only a capacitor and resistor to set the clock frequency (which can drift up to 20% without affecting performance). Control radios, Hi-Fi (including bass, treble and volume), lighting, toys, garage doors, etc. Still not convinced? Then look at the prices!

LD271 IR Emitting Diode	38p	ML922 10-channel Receiver and 3 Analogue Outputs	£4.20
SF4205 Photo diode Detector	85p	ML926 16-channel Receiver (4 Momentary binary outputs)	£1.40
SL480 IC Pulse Amplifier	£1.40	ML928 16-channel Receiver (4 Latched binary outputs)	£1.40
SL490 Keyboard Controlled Encoder/Transmitter	£2.40	Data sheets (per device)	5p

If you do not require a sophisticated multi-channel remote control, we have developed a simple single channel ON/OFF infra red transmitter and receiver. The transmitter unit comes complete with a hand held box and requires a PP3 (9V) battery. The receiver unit comes complete with a triac capable of switching up to 500W at 240V a.c. and comprises a preamplifier, bistable latch and a mains power supply, making the unit completely self-contained. The small size of the receiver enables the unit to be "built into" all kinds of equipment from lamps to tape recorders. The minimum range is 20 feet.

ONLY **£12.00** (Order as RC500K)

INTEGRATED CIRCUITS

SN76477 Complex Sound Generator	£2.52
TBA800 5W Audio Amp	85p
TBA810AS 7W Audio Amp	85p
TDA1024 Zero Voltage Switch	£1.20
TDA2020 20W Audio Amp	£2.85
ZN1G34E Timer	£1.80

All ICs supplied with data sheets
Data Sheets only 5p each device

TRIACS

400V Plastic Case (Texas)			
3A	49p	16A	90p
8A	58p	20A	165p
12A	85p	25A	190p
6A with trigger			80p
BA isolated tab			65p
Diac			18p

SPECIAL OFFERS
orders must be received by 30.6.80

10x8pin sockets	65p	10x555	£1.80
10x14pin sockets	£1.00	10x741	£1.80
10x18pin sockets	£1.15	25x20 2" Red LEDs	£1.50
10x18pin sockets	£1.40	ORP12	50p
100x Soldercon pins	40p	2N3055	40p

ALL COMPONENTS ARE BRAND NEW AND TO SPECIFICATION. ADD VAT AT CURRENT RATE TO ABOVE PRICES. 40p P&P MAIL ORDER - CALLERS WELCOME BY APPOINTMENT



TK Electronics
(ETI), 106 STUDLEY GRANGE ROAD
LONDON W7 2LX. TEL. 01-579 9794



CAPACITANCE METER

Take the huff out of measuring μF s with this cheap and handy piece of test gear.

If you are the kind of constructor who keeps a 'junk box' . . . and in this impoverished age who can afford not to . . . you are bound to have come across the problem of unmarked components. Resistors can be checked quite easily on most multimeters but capacitors pose more of a problem. The 'ballistic' method usually results in the mysterious components becoming ballistic missiles — straight in the bin!


This useful piece of test gear will enable you to measure values of capacitance from 10pF to $10\mu\text{F}$ in five decade ranges. A simple modification would enable an ordinary voltmeter to be used as indicator, though our prototype used a $100\mu\text{A}$ movement mounted in the case. Power for the unit is provide by two nine volt batteries which results in a voltage of up to 18V across the capacitor under test. This should be borne in mind when testing low voltage electrolytics or tantalum capacitors which may be damaged by this voltage.

Simple PCB

Use of a quad op-amp package keeps the component count to a minimum and simplifies the PCB design. IC2 is a BIFET device and contains MOSFET transistors, though these are adequately protected and no special handling precautions are required.

Cap Testing

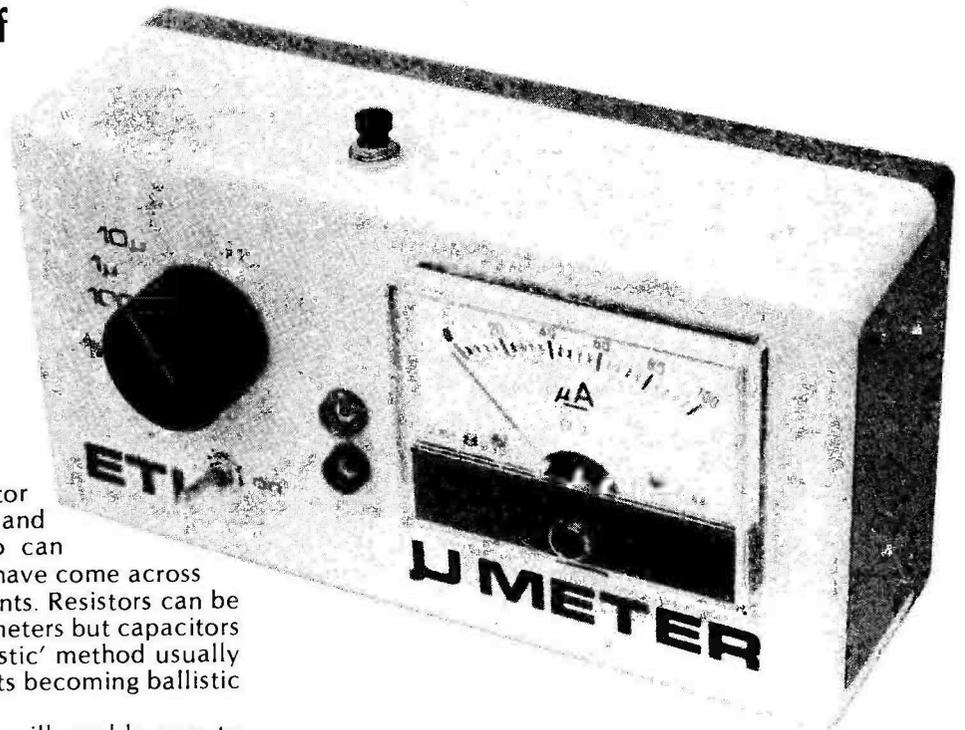In use the unknown capacitor is connected and PB1 is depressed. If you use 1% resistors for R5-9 then quite accurate readings can be obtained. Even with low tolerance resistors, the unit will find application in matching components for filter design, etc. Note that the meter



will hold a steady reading for quite a few seconds before a slow drift may become evident. Current consumption of the unit is quite high (about 10mA) owing to the currents required for the zener diode voltage references.

Construction

Any method of construction may be employed but we think PCBs are best. A fair number of interconnections will be required whatever method is chosen and the circuit will tolerate quite sloppy wiring layout. If you use 1% resistors, you may want to use a large meter scale to take advantage of the extra accuracy obtained. Using the prototype, which features a miniature meter movement, we were able to correctly identify values of capacitance as low as 12pF . If desired, the power switching may be incorporated in the range switch though this necessitates a 3 pole 6 position switch.

As mentioned above, an ordinary voltmeter may be used with the unit. One with a 3V FSD scaled 0-10 is required. As R23 and RV1 are not required, the full scale must be adjusted by trimming the current determining resistor R22. A value of about $5\text{k}\Omega$ should be right. Once you have built this unit, you'll wonder how you ever managed without it!




HOW IT WORKS

A glance at the block diagram will help you to understand operation of this unit. When the 'test' button is depressed (PB1 on the circuit diagram), the capacitor under test is charged to the positive supply and C2 is discharged. Upon releasing the pushbutton, Cx will discharge at a preselected rate (SW1 range switch determines this). Rate of change of voltage across Cx for a given constant discharge current is directly proportional to its capacitance. A measurement of this is obtained by timing the period during which the Cx voltage is between two reference voltage levels. For this period, a fixed current source is switched on by the output of the window comparator. Capacitor C2 thus develops a charge whose voltage is proportional to the value of the capacitor under test. As the unit produces a linear output, values may be read directly from a conventional meter scale.

The circuit blocks can be readily identified in the circuit diagram. IC1a, ZD1 and Q2 form the current sink. Values from 1 uA to 10 mA are obtained in decade steps by adjustment of SW1 range switch. The capacitor voltage is buffered by IC1b whose output drives the window comparator. Reference voltages are provided by the potential divider connected across ZD2. IC1c and IC1d together form the window comparator and their outputs are 'OR'ed and used to drive the switched fixed current source built around IC2. This section of the circuit is quite novel. The output of the 3140 op-amp used for IC2 can be strobed low by driving pin 8 close to the negative rail. This enables a very simple switched constant current source to be built using diode gating. A 741 op-amp is used to buffer C2. Potentiometer RV2 sets zero and RV1 sets full scale deflection.

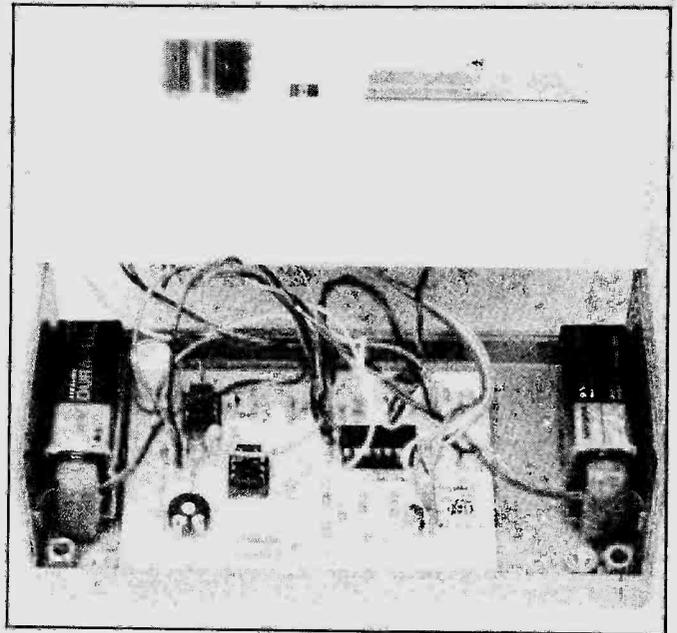Transistors Q1 and Q3 are switched on when PB1 is depressed to reset the circuit and initiate a new measurement. Reverse bias on Q3 is limited by D3. Overall decoupling is provided by C1.



Taking the lid off the Micrometer. We used two of those batteries that last longer than all the others.

BUYLINES

Nothing out of the ordinary here. All the components should be readily available from the larger mail order companies.


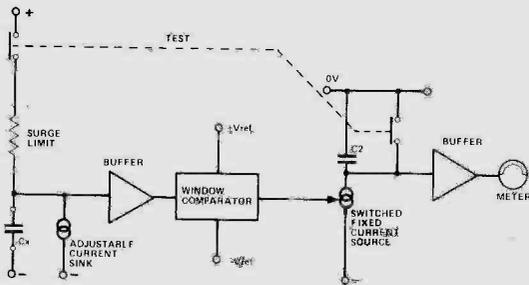


Fig.1. (left) Block diagram of the capacitance meter.

Fig.2. (below) Circuit diagram.

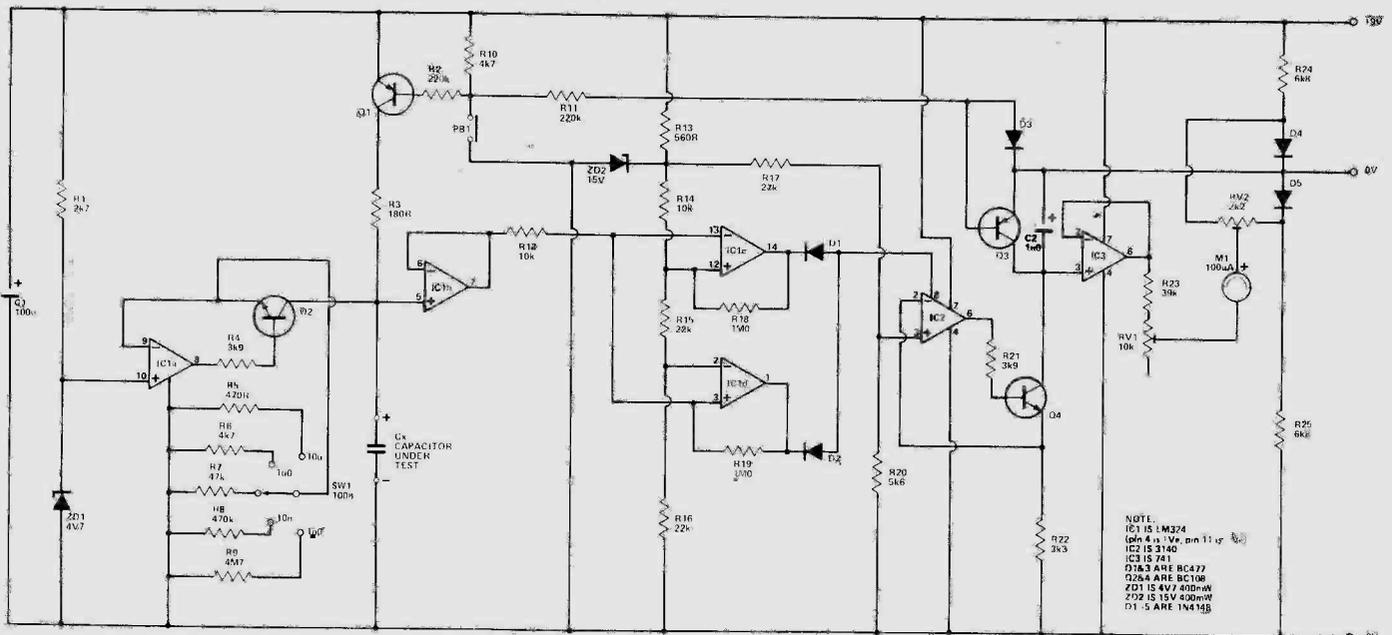

PARTS LIST

Resistors All 1/4W 5% unless specified

R1	2k7
R2,11	220k
R3	180R
R4,21	3k9
R5,10	470R
R6	4k7
R7	47k
R8	470k
R9	4M7
R12,14	10k
R13	560R
R15,16	22k
R17	27k
R18,19	1M0
R20	5k6
R22	3k3
R23	39k
R24,25	6k8
R5-9 should be 1% types for best accuracy.	
Potentiometers	
RV1	10k preset
RV2	2k2 preset
Capacitors	
C1	100u electrolytic
C2	1u0 tantalum
Semiconductors	
IC1	LM324
IC2	3140
IC3	741
Q1,3	BC477
Q2,4	BC108
ZD1	4V7 400mW zener diode
ZD2	15V 400mW zener diode
D1-5	1N4148
Miscellaneous	
Single pole 5-way switch, push button switch, 100 uA meter, PCB, Case, etc.	

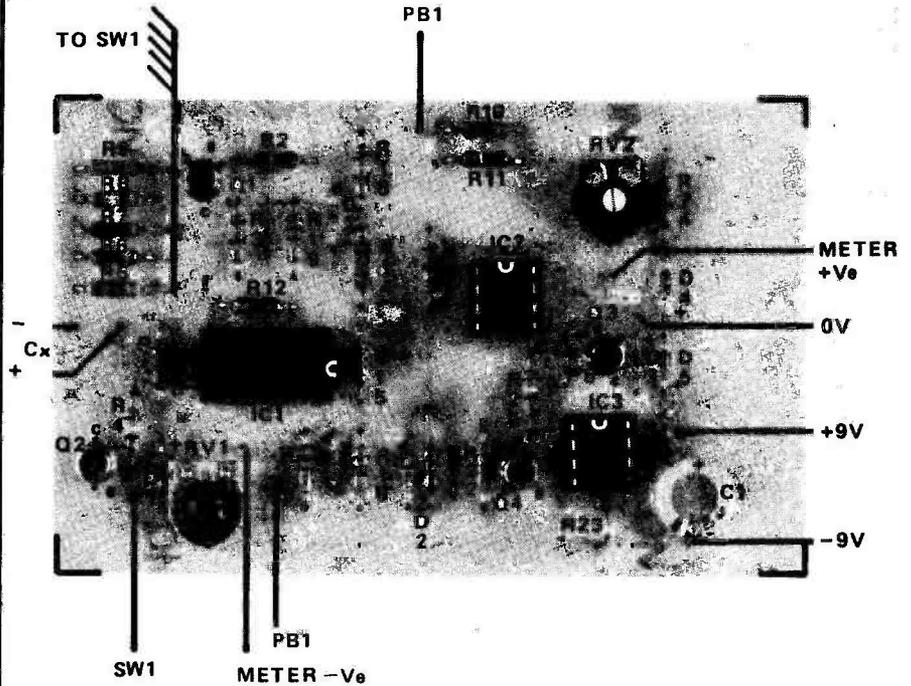


Fig.3. Component overlay. Note the orientation of the ICs. Insert them the wrong way at your peril.

ETI

TRANSFORMERS

Panel Meters, Bridge Rectifiers, Power Supply Units
Multimeters - Semi Conductors - Timers - Safabloc

Minimum & Sub Miniature

Volts	Milli-amps	Ref. No.	Price £	P&P
3-0-3	200	238	2.95	.65
0.6, 0.6	1A 1A	212	2.95	.70
9-0-9	100	13	2.25	.65
0.9, 0.9	330 330	235	2.10	.65
0.8-9, 0.8-9	500 500	207	2.70	.70
0.8-9, 0.8-9	1A 1A	208	3.80	.70
0-15, 0-15	200 200	236	2.10	.65
0-20, 0-20	300 300	214	2.70	.85
20-12-0-12-20	700(DC)	221	3.45	.85
0-15-20, 0-15-20	1A 1A	206	4.55	1.00
0-15-27, 0-15-27	500 500	203	4.00	.85
0-15-27, 0-15-27	1A 1A	204	6.05	1.00

12 AND/OR 24 VOLT

Volts	Amps	Ref. No.	Price £	P&P
12v	24V			
0.5	0.25	111	2.25	.70
1.0	0.5	213	2.70	.85
2	1	71	3.20	.85
4	2	18	4.00	.85
6	3	70	5.55	.90
8	4	108	7.40	1.15
10	5	72	8.20	1.15
12	6	116	8.80	1.15
16	8	17	10.80	1.25
20	10	115	13.80	1.45
30	15	187	16.80	1.45
60	30	226	33.30	1.75

30 VOLT (Pri: 220-240V) Sec: 0-12-15-20-24-30V

Amps	Ref. No.	Price £	P&P
0.5	112	2.80	.85
1.0	79	3.55	.85
2.0	3	5.55	1.00
3.0	20	6.25	1.15
4.0	21	6.55	1.15
5.0	51	9.55	1.15
6.0	117	11.05	1.15
8.0	88	14.30	1.45
10.0	89	16.55	1.45

50 VOLT (Pri: 220-240V) Sec: 0-19-25-33-40-50V

Amps	Ref. No.	Price £	P&P
0.5	102	3.55	.85
1.0	103	4.55	1.00
2.0	104	7.25	1.15
3.0	105	8.55	1.15
4.0	106	10.80	1.25
6.0	107	15.05	1.45
8.0	118	20.15	1.65
10.0	119	24.05	2.15

60 VOLT (Pri: 220-240V) Sec: 0-24-30-40-48-60

Amps	Ref. No.	Price £	P&P
0.5	124	3.80	.85
1.0	126	5.55	1.00
2.0	127	7.50	1.15
3.0	125	11.05	1.25
4.0	123	12.30	1.45
5.0	40	14.10	1.55
6.0	120	17.55	1.55

AUTO TRANSFORMERS Input/Output Tapped 0-115-210-240V


VA (Watts)	Ref. No.	Price £	P&P
20	113	2.60	.85
75	64	4.05	.85
150	4	5.55	1.00

Input/Output Tapped 0-115-210-220-240V

300	53	10.05	1.15
500	67	10.80	1.45
1000	84	18.55	1.55

Also 1500/2000/3000VA MAINS ISOLATING (Centre Tapped & Screened)

VA (Watts)	Ref. No.	Price £	P&P
60	149	6.55	1.00
100	150	7.55	1.25
200	151	11.05	1.25
250	152	13.25	1.45
350	153	16.25	1.55
1000	156	37.05	3.15

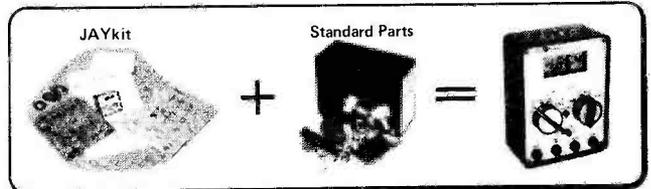

DM-2



DIGITAL MULTIMETER

- ★ DC Volts 1mV to 1000V
- ★ AC Volts 1V to 500V
- ★ DC Current 0.1mA to 0.2A
- ★ Resistance 1Ω to 20MΩ
- ★ 3 1/2 digit LCD
- ★ Auto Low Battery indication
- ★ Auto Polarity & Zero
- ★ 1% accuracy (DC volts)
- ★ Designed around Intersil 7106 IC
- ★ Total cost around £30 (incl. case)

FG-1a



FUNCTION GENERATOR

- ★ 30mV to 10V pk-pk
- ★ 1Hz to 100kHz
- ★ DC coupled
- ★ Sine, Square & Triangle
- ★ Separate TTL output
- ★ Designed around Intersil 8038 IC
- ★ Total cost around £30 (incl. case)

Provided in a JAYkit is a Printed Circuit Board, a punched and lettered Front Panel overlay, a Circuit Diagram and Instruction Sheet and a comprehensive and up to date Component List showing suppliers and current prices. Difficult to obtain pieces of hardware are supplied with the kit.

Jayven Developments, 21 Gladeside, Bar Hill, Cambridge CB3 8DY

To: JAYEN Developments
21 Gladeside, Bar Hill,
Cambridge CB3 8DY

Name: _____

Please send:

Address: _____

- DM-2 @ £5.45
 FG-1a @ £4.95
(Incl. VAT and P&P)

Money to be refunded if the kit is returned within 10 days.

JAYkits

NEW

CONSTRUCTORS PACK 7

ALL THE PARTS TO BUILD THE PRACTICAL ELECTRONICS TRAVELLER CAR RADIO

- * EASY TO BUILD * 5 PUSH BUTTON TUNING * MODERN STYLING DESIGN * ALL NEW UNUSED COMPONENTS
- * 6 WATT OUTPUT * READY ETCHED & PUNCHED P.C.B.
- * INCORPORATES SUPPRESSION CIRCUITS



£10.50 p&p £1.75

The pack contains all the electronic components to build the radio, you supply only the wire and solder as featured in the Practical Electronics March issue.

The P.E. Traveller features pre-set tuning with five push button options, black illuminated tuning scale, with matching rotary control knobs, one, combining on/off volume and tone-control, the other for manual tuning, each set on wood simulated fascia.

The P.E. Traveller has a 6 watts output, negative ground and incorporates an integrated circuit output stage, a Mullard IF module LP1181 ceramic filter type, pre-aligned and assembled and a Bird pre-aligned push button tuning unit.

The P.E. Traveller fits easily in or under dashboards. Complete with instructions.

CONSTRUCTORS PACK 7A
Suitable stainless steel fully retractable locking aerial and speaker (approx 6" x 4") is available as a kit complete.

£1.95 Per Pack, p & p £1.00.
Pack 7A may only be purchased at the same time as Pack 7.

NOTE: Constructor's pack 7A sold complete with radio kit **£15.20** including p&p.

A FEATURED PROJECT IN PRACTICAL ELECTRONICS



323 EDGWARE ROAD, LONDON W2. For Personal Shoppers Only.
21 E HIGH STREET, ACTON W3 6NG. Mail Order Only. No Callers.

Mon-Sat 9.30am-5.30pm
Closed Thursday

NEW 12+12

AMPLIFIER KIT

An opportunity to build your own 12 watts per channel stereo amplifier with up-to-the-minute features. To complete you just supply screws, connecting wire and solder. Features include din input sockets for ceramic cartridge, microphones, tape or tuner. Outputs—tape, speakers and headphones. By the press of a button it transforms into a 24 v. 1.1 mor-disco amplifier with twin deck mixing. The kit incorporates a Mullard LP1183 pre-amp module, plus 2 power amplifier assembly kits, also featured 4 slider level controls, rotary bass and treble controls and 6 push button switches. Silver finish fascia panel with matching knobs. Easy to assemble teak simulate cabinet and ready made metal work. For further information instructions are available price 50p. Free

Size 9 1/4" x 8 3/4" x 4" approx. with kit **£13.95**
NOTE: for use with 4 to 8 ohms speakers. p&p £2.55

TWO WAY SPEAKER KIT To suit above amp. Comprising 2, 8" approx Philips base unit, and 2, 3 1/2" approx tweeters with 2 crossover capacitors **£4.95** p&p £1.65



Available only to first time purchasers of the 12 + 12 kit.

50 WATT MONO

DISCO AMP

£30.60
p&p £3.20

Size approx 13 3/4" x 5 1/4" x 6 3/4"
50 watts rms, 100 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with infrequent push-pull switches. Independent bass and treble controls and master volume.



30 + 30 WATT STEREO AMPLIFIER
Viscount IV unit in teak simulate cabinet. Silver finish rotary controls and pushbuttons with matching fascia, red mains indicator and stereo jack socket. Functions switch for mic magnetic and crystal pickups, tape tuner and auxiliary. Rear panel features fuse holder, DIN speaker and input socket. 30 + 30 watts RMS 60 + 60 watts peak for use with 4 to 8 ohm speakers.
Size 14 1/4" x 3" x 10" approx. **£32.90**
BUILT AND READY TO PLAY p&p £3.30

Mullard

AUDIO MODULES IN BARGAIN PACKS

CURRENT CATALOGUE PRICE AT OVER

£25 PER PACK SEE OUR PRICES

1 PACK 1 2 x LP1173 10w RMS output power audio amp modules, + 1 LP1182/2 Stereo pre amp for ceramic and auxiliary input. OUR PRICE **£5.00** p&p £1.10

2 PACK 2 2 x LP1173 10w RMS output power audio amp modules + 1 LP1184/2 Stereo pre amp for magnetic, ceramic and auxiliary inputs. **illus. OUR PRICE £7.65** p&p £1.15

ACCESSORIES Suitable mains power supply parts, consisting of mains transformer, bridge rectifier, smoothing capacitor and set of rotary stereo controls for treble, bass, volume and balance, **£3.00** plus p&p £1.60

Two Way Speaker Kit Comprising of two 8" x 5" approx. 4 ohm bass and two 3 1/2" 15 ohm mid-range tweeter with two cross-over capacitors. Per stereo pair plus p&p **£4.05**

ACCESSORIES ARE ONLY AVAILABLE TO THOSE CUSTOMERS WHEN BUYING OUR BARGAIN PACKS



£76.00 p&p £4.00

100 WATT MONO

DISCO AMP

Brushed aluminium fascia and rotary controls. Size approx. 14" x 4" x 10". Five vertical slide controls, master volume, tape level, mic level, deck level, PLUS INTER DECK FADE FOR perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre fade level control (PFL) lets YOU hear next disc before fading it in. VU meter monitors output level. Output 100 watts RMS 200 watts peak.

EMI SPEAKER BARGAIN

Stereo pair 350 kit. System consists of 13" x 8" approx. woofers with rolled surround, 3 1/2" Goodman tweeter crossover components and circuit diagram. Frequency response 20 Hz to 20 KHz. Power handling 15 watts RMS 20 watts max 8 ohm impedance.

£18.25 Per stereo pair p&p £4.20



BSR P200

Belt drive chassis turntable unit semi-automatic, cueing device. p&p £3.00
Shure M75 B Magnetic Cartridge to suit. **£7.95**



Manual single play record deck with auto return and cueing lever. Fitted with stereo ceramic cartridge 2 speeds with 45 r.p.m. spindle adaptor ideally suited for home or disco use. **£12.25** p&p £2.75
OUR PRICE



PHILLIPS RECORD PLAYER DECK GC037

HiFi record player deck, belt drive complete with GP401 magnetic cartridge—LIMITED STOCK. **£27.50** complete. UNBEATABLE OFFER AT BUYER COLLECT ONLY.



BARGAIN OFFER
Ariston pick-up arm manufactured in Japan. Complete with headshell. Listed price over £30.00.

OUR £11.95 PRICE p&p £2.50



323 EDGWARE ROAD, LONDON W2
21 E HIGH STREET, ACTON W3 6NG

ACTON: Mail Order only, No callers
ALL PRICES INCLUDE VAT AT 15%
All items subject to availability. Price correct at 6.8.80 and subject to change without notice
All enquiries Stamped Addressed Envelope.

NOTE: Persons under 16 years not served without parent's authorisation.

Happy Memories

4116 200ns	£3.95	4116 150ns	£5.50
2114 200ns	£3.95	2114 450ns	£3.45
2708 450ns	£4.95	2716 5 volt	£13.50

MEMOREX mini discs soft sectored
£19.95 per ten

SALE

We're moving shortly to new premises and don't want to carry much
Bargains for all

All prices include VAT, 30p postage on orders below £10

Access and Barclaycard

All orders to:

Dept. ETI
19 Bevois Valley Road
Southampton, Hants. SO2 0JP
Telephone (0703) 39267

LINSAC

SINCLAIR ZX80 SOFTWARE (Sinclair Tested)

For free catalogue of games and educational programs designed for the ZX80, send SAE to:

LINSAC
68 Barker Road
Middlesbrough TS5 5EE

Also available:
THE ZX80 COMPANION
by Bob Maunder and
Terry Trotter
at £7.50




Target Electronics

16 Cherry Lane, Bristol BS1 3NG
Telephone: 0272 421196

Official orders welcomed, Gvt./Educational Dept., etc.

nm
Nascom Microcomputers

Panel Meters

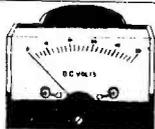

Dims:- 50 x 45 x 33mm. Require 38mm dia. cut out
cat. F.S.D.

MU50	0 - 50 UA	£3.20 + 15% VAT P&P 35p, 10 plus 10% Discount
MU100	0 - 100 UA	
MUJ	0 - 1 MA	
MUVU	"VU"	

Dims:- 60 x 47 x 33mm. Require 38mm dia. cut out

FINE QUALITY - JAPANESE MANUFACTURER


T21	0 - 50 UA	£3.75 + 15% VAT P&P 35p, 10 plus 10% Discount
T22	0 - 100 UA	
T23	0 - 500 UA	
T24	0 - 1 MA	
T25	0 - 5 MA	
T26	0 - 10 MA	
T27	0 - 50 MA	
T28	0 - 100 MA	
T29	0 - 100 MA	
T30	0 - 1 AMP	
T31	0 - 2 AMP	
T32	0 - 25 Volts	
T33	0 - 50V AC	
T34	0 - 300V AC	
T35	"5"	
T36	"VU"	
T40	50 - 0 - 50 UA	
T41	100 - 0 - 100 UA	
T42	500 - 0 - 500 UA	
T43	0 - 30V DC	

Dims:- 110 x 82 x 35mm. Require 58mm dia. cut out
FINE QUALITY - JAPANESE MANUFACTURER

043	0 - 30 UA	£4.75 + 15% VAT P&P 35p, 10 plus 10% Discount.
045	0 - 50 UA	
0410	0 - 100 UA	
0420	0 - 200 UA	
0430	0 - 500 UA	

Illuminating kit for meters. T21-T43/043-0450.

1K2	60p + 15% VAT.
-----	----------------

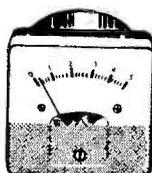

Dims:- 52 x 52 x 33mm. Require 45mm dia. cut out

cat. F.S.D.

MS50	0 - 50 UA	£2.88 + 15% P&P 35 10 plus 10% Discount
MS100	0 - 100 UA	
MSJ	0 - 1 MA	
MSVU	"VU"	




£1.70 + 15% VAT
P&P 35p
Ltd. quantity

This board is designed solely for the use of discrete components and is particularly useful for basic educational purposes.

(No. of contacts: 208)

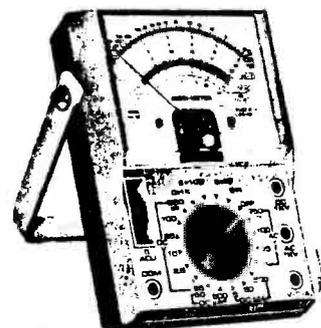VOM-MULTITESTER 20,000 ohms/volts dc model NH-56



ALTAI
AC volts:- 0 - 10 - 25 - 100 - 250 - 1000
DC volts:- 0 - 0.25 - 1 - 2.5 - 10 - 25 - 100 - 250 - 1000
DC current:- 0 - 50 ua - 500 ua
Resistance:- 0 - 5 ma - 50 ma - 500 ma - 600 K ohms - 60 K ohms - 600 K ohms - 6 meg ohms
Decibels:- -20 to +22db
Dims:- 130 x 88 x 37mm

£9.25 + 15% VAT
P&P 75p

Phone in your Access or Barclaycard
Order. Cat. 30p. Post paid



ETIPRINTS

ETIPRINTS are a fast new aid for producing high quality printed circuit boards. Each ETIPRINTS sheet contains a set of etch resistant rub down transfers of the printed circuit board designs for several of our projects.

ETIPRINTS are made from our original artwork ensuring a neat and accurate board. We thought ETIPRINTS were such a good idea that we have patented the system (patent numbers 1445171 and 1445172).


PARTS LIST

Shown below is the listing for the last year's ETIPRINTS.

Earlier sheets are available, ring Tim Salmon for details.

038	Buffer Moving Coil Preamp Process Controller	Jan 80	040B	ETI 80 - PSU Tuning Fork Filter Coin Toss	Feb 80	042B	Touch Dimmer, Battery Charger RC Guardian (Top,Bottom)1&2	Apr 80
039A	Hum Filter Logic Probe	Dec 79	041A	ETI Audiophile ETI VCA Signal Trace ETI HC Electromyogram	Mar 80	043	IR60 preamp, Receiver, PSU, Servo Tester, VU-PPM	May 80
039B	Long Period Timer Rain Alarm Touch Switch Flash Trigger Pseudo Random Noise Gen	Dec 79	041B	VCM Heater Controller	Mar 80	044A	IR60 Function Board (Top & underside) Control Circuit, Line Transmitter, Tape Response Meter Ohmmeter	June 80
039C	Function Generator	Dec 79	042A	300W Amp Module	Apr 80	044B	FM receiver PSU & Monitor Amp Drum Synth (function board)	June 80
040A	ETI 80 - VCO and VCLFO	Feb 80	033	Fuel Level Monitor, Alarm, Screen Controller Dynamic Noise Reducer	Sep 79			

HOW IT WORKS

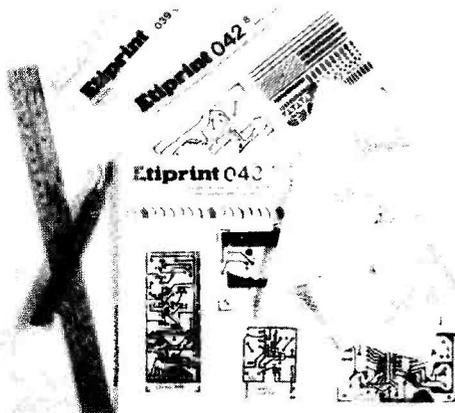

Lay down the ETIPRINT and rub over with a soft pencil until the pattern is transferred to the board. Peel off the backing sheet carefully making sure that the resist has transferred. If you've been a bit careless there's even a 'repair kit' on the sheet to correct any breaks!

ETIPRINTS

BUY LINES

ORDER TODAY

Send a cheque or PO (payable to ETI Magazine) to

ETI PRINT, ETI MAGAZINE 145 Charing Cross Road,
London WC2H 0EE.

Price £1.20p.

8K ON BOARD MEMORY!

5K RAM, 3K ROM or 4K RAM, 4K ROM (link selectable). Kit supplied with 3K RAM, 3K ROM. System expandable for up to 32K memory.

2 KEYBOARDS!

56 Key alphanumeric keyboard for entering high level language plus 16 key Hex pad for easy entry of machine code.

GRAPHICS!

64 character graphics option — includes transistor symbols! Only £18.20 extra!

MEMORY MAPPED

high resolution VDU circuitry using discrete TTL for extra flexibility. Has its own 2K memory to give 32 lines for 64 characters.

KANSAS CITY

low error rate tape interface.

**NEW FACTORY
UP!
PRICES DOWN!**

Increased capacity at our big new factory means many prices down! All others frozen!



Cabinet size 19.0" x 15.7" x 3.3". Television not included in price

2 MICROPROCESSORS

Z80 the powerful CPU with 158 instruction, including all 78 of the 8080, controls the MM57109 number cruncher. Functions include +, -, *, /, squares, roots, logs, exponentials, trig functions, inverses etc. Range 10⁻⁹⁹ to 9 x 19⁹⁹ to 8 figures plus 2 exponent digits.

EFFICIENT OPERATION

Why waste valuable memory on sub routines for numeric processing? The number cruncher handles everything internally!

RESIDENT BASIC

with extended mathematical capability. Only 2K memory used but more powerful than most 8K Basics!

1K MONITOR

resident in EPROM.

SINGLE BOARD DESIGN

Even keyboards and power supply circuitry on the superb quality double sided plated through-hole PCB.

**COMPLETE KIT
NOW ONLY**

£225 + VAT

POWERTRAN

PSI Comp 80. Z80 Based powerful scientific computer Design as published in Wireless World

The kit for this outstandingly practical design by John Adams published in a series of articles in Wireless World really is complete!

Included in the PSI COMP 80 scientific computer kit is a professionally finished cabinet, fibre-glass double sided, plated-through-hole printed circuit board. 2 keyboards PCB mounted for ease of construction, IC sockets, high reliability metal oxide resistors, power supply using custom designed toroidal transformer. 2K Basic and 1K monitor in EPROMS and, of course, wire, nuts, bolts, etc.



Value Added Tax not included in prices

PRICE STABILITY: Order with confidence. Irrespective of any price changes we will honour all prices in this advertisement until September 30, 1980, if this month's advertisement is mentioned with your order. Errors and VAT rate changes excluded.

EXPORT ORDERS: No VAT. Postage charged at actual cost plus £1.00 handling and documentation.

U.K. ORDERS: Subsequent to 15% surcharge for VAT. No charge is made for carriage. Or current rate if changed.

SECURICOR DELIVERY: for this optional service (U.K. mainland only) add £2.50 (VAT inclusive) per kit.

SALES COUNTER: If you prefer to collect your computer from the factory, call at Sales Counter. Open 9 a.m.-12 noon, 1-4.30 p.m. Monday-Thursdays.

KIT ALSO AVAILABLE AS SEPARATE PACKS

For those customers who wish to spread their purchase or build a personalised system the kit is available as separate packs eg. PCB (16" x 12.5") £43.20. Pair of keyboards £34.80. Firmware in EPROMS £30.00. Toroidal transformer and power supply components £17.60. Cabinet (very rugged, made from steel, really beautifully finished) £26.50. P.S. Will greatly enhance any other single board computer including OHIO SUPERBOARD for which it can be readily modified. Other packs listed in our FREE CATALOGUE.

PSI COMP 80 Memory Expansion System

Expansion up to 32K all inside the computer's own cabinet!

By carefully thought out engineering a mother board with buffers and its own power supply (powered by the computer's transformer) enables up to 3 8K RAM or 8K ROM boards to be fitted neatly inside the computer cabinet. Connections to the mother board from the main board expansion socket is made via a ribbon cable.

Mother board:

Fibre glass double sided plated through hole P.C.B. 8.7" x 3.0" set of all components including all brackets, fixing parts and ribbon cable with socket to connect to expansion plug £39.90

8K Static RAM board

Fibre glass double sided plated through hole P.C.B. 5.6" x 4.8" £12.50
Set of components including IC sockets, plug and socket but excluding RAMs £11.20
2114L RAM (16 required) £5.00
Complete set of board, components, 16 RAMS £89.50

8K ROM board

Fibre glass double sided plated through hole P.C.B. 5.6" x 4.8" £12.40
Set of components including IC sockets, plug and socket but excluding ROMs £10.70
2708 ROM (8 required) £8.00
Complete set of board, components, 8 ROMs £78.50

New Factory on same Industrial Estate
Address and Telephone Number unchanged

UK Carriage FREE

POWERTRAN ELECTRONICS

PORTWAY INDUSTRIAL ESTATE ANDOVER
ANDOVER HANTS SP10 3NM (0264) 64455