

AN ARGUS SPECIALIST PUBLICATION

# electronics today

INTERNATIONAL

May 1983 85p

## SPECIAL AUDIO ISSUE

Four Audio Projects:

**Power  
Amplifier  
Using NDFL**

**Power Supply  
Upgrade from  
Linsley Hood**

**Balanced Line  
Amplifier**

**Compressor  
Limiter  
System**



**AUDIO PULL-OUT  
WE TELL YOU  
WHICH SYSTEM**

...AUDIO....COMPUTING....MUSIC...

ROBOTICS...



# Star sounds \*\*


# Star quality \*\*

# Star features \*\*

**BIG NEWS  
ABOUT OUR  
LATEST  
ADVANCES IN  
ROBOTICS  
SEE INSIDE  
BACK COVER**

**Free  
SECURICOR  
DELIVERY**

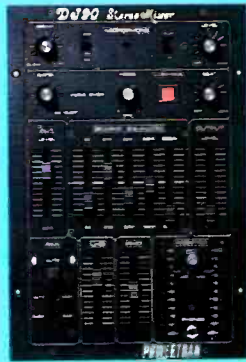on all orders over  
£100 (UK main and  
only) Add just £2.50  
on lower price  
orders



**DJ90 Stereo Mixer** — this is a really versatile new mixer that enables the constructor DJ to produce a professional performance every time. There are two stereo inputs for magnetic cartridges, a stereo auxiliary input and mike input. Other 'plus' features are auto-panning for fast or slow slider controls, multi-mixing, ducking, interrupt, input modulation, in short everything... the whole works — AND — under £100 complete! Complete kit **£97.50 + VAT**



**TRANSCENDENT 2000** — Although only a 3 octave keyboard the '2000' features the same design ingenuity, careful engineering and quality components of its larger brethren. The kit is well within the scope of the first time builder — buy it, build it — play it! You will know you have made the right choice.

Complete kit **£165.00 + VAT**

**SALES  
COUNTER**

Collect your order  
from the factory.  
Open 9-12/1-4.30  
Mon-Thurs Easy  
parking no  
waiting

**Digital Delay Line** — With its ability to give delay times from 1.6 mSecs to up to 1.6 secs. Many powerful effects including phasing, flanging, A.D.T., chorus, echo &



vibrato are obtained. The basic kit is extended in 400 mS steps up to 1.6 secs. Simply by adding more parts to the PCB.

Compare with units costing over £1,000!

Complete kit (400 mS delay)

**£130 + VAT**

Parts for extra 400 mS delay

**£9.50 + VAT**

## KIT PRICES

Input channel	<b>£19.90</b>	Base unit and wooden front	<b>£27.50</b>
Output channel	<b>£18.50</b>	Pair of mahogany end cheeks	<b>£12.50</b>
Auxiliary channel	<b>£22.50</b>	Power Supply and cabinet	<b>£19.50</b>
Blank Panel	<b>£3.00</b>		

**All prices are VAT exclusive**

**Free Soldering  
Practise Kit on  
request with your  
first kit — useful  
tips, well  
illustrated.**

**TRANSCENDENT POLYSYNTH** — A four octave polyphonic synthesiser with outstanding design characteristics and versatility and performance to match.

Complete kit **£275.00** plus VAT (single voice)

Extra voice (up to three more) **£42.00** plus VAT



**MPA 200** — is a low price, high power 100W amplifier, its smart styling, professional appearance and performance, make it one of our most popular designs. With adaptable inputs the mixer accepts a variety of sources yet straightforward construction makes it ideal for the first time builder. Complete kit **£49.90 + VAT**

**Chromathèque 5000** — a 5 channel lighting system powerful enough for professional discos yet controllable for home-effects. Sound to light, strobe to music level, random or sequential effects — each channel can handle up to 500W yet minimal wiring is needed with our unique single board design. Complete kit **£49.50 + VAT**

**ET1 VOCODER** — 14 channels, each with independent level control for maximum versatility and intelligibility. Two input amplifiers — for speech/excitation — each with level control and tone control. The Vocoder is a powerful yet flexible machine that is interesting to build and thanks to our easy to follow construction manual, is within the capability of most enthusiasts. Complete kit **£175.00 + VAT**

**SP2 200** twice the power with two of the reliable, durable and economic amps from the MPA 200, fed by separate power supplies from a common toroidal transformer. Superb finish and quality components throughout — up to (even over) the standard of high price factory-built units! Complete kit **£64.90 + VAT**



**Component  
packs for most  
kits are available  
See our great free  
catalogue, full  
details of all  
our range**

**WORLD  
LEADERS  
IN  
ELECTRONIC  
KIT DESIGN  
AND SUPPLY**

**PORTWAY INDUSTRIAL ESTATE**

**ANDOVER, HANTS SA10 3NM.**

**ORDER BY PHONE (0264) 64455**




VISA

Simply request your chosen kit and quote your Access or Barclaycard Number.

# electronics today

INTERNATIONAL

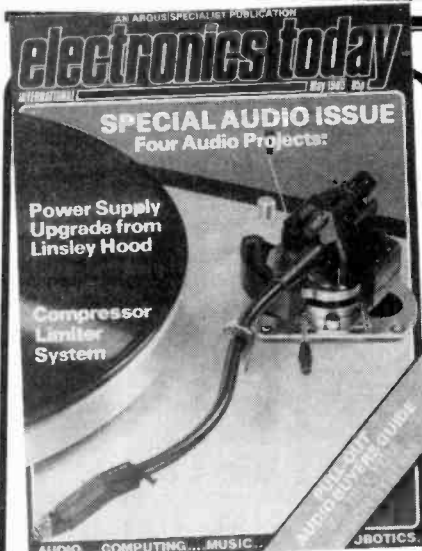

Our thanks to Howland-West International Ltd. for the cover photo.

**Dave Bradshaw:** Editor  
**Peter Green:** Deputy Editor  
**Phil Walker:** Project Editor  
**Jerry Fowler:** Technical Illustrator  
**Gary Price:** Divisional Advertisement Manager  
**Ron Harris B.Sc:** Managing Editor  
**T.J. Connell:** Managing Director

**PUBLISHED BY:**  
 Argus Specialist Publications Ltd.,  
 145 Charing Cross Road, London WC2H 0EE.

**DISTRIBUTED BY:**  
 Argus Press Sales & Distribution Ltd.,  
 12-18 Paul Street, London EC2A 4JS  
 (British Isles)

**PRINTED BY:**  
 QB Limited, Colchester.

**COVERS PRINTED BY:**  
 Alabaster Passmore.

**OVERSEAS EDITIONS and their EDITORS**  
 AUSTRALIA — Roger Harrison  
 CANADA — Halvor Moorshead  
 GERMANY — Udo Wittig  
 HOLLAND — Anton Kriegsman



Member of the  
 Audit Bureau  
 of Circulation

Electronics Today is normally published on the first Friday in the month preceding cover date. □ The contents of this publication including all articles, designs, plans, drawings and programs and all copyright and other intellectual property rights therein belong to Argus Specialist Publications Limited. All rights conferred by the Law of Copyright and other intellectual property rights and by virtue of international copyright conventions are specifically reserved to Argus Specialist Publications Limited and any reproduction requires the prior written consent of the Company. © 1983 Argus Specialist Publications Ltd. □ All reasonable care is taken in the preparation of the magazine contents, but the publishers cannot be held legally responsible for errors. Where mistakes do occur, a correction will normally be published as soon as possible afterwards. All prices and data contained in advertisements are accepted by us in good faith as correct at time of going to press. Neither the advertisers nor the publishers can be held responsible, however, for any variations affecting price or availability which may occur after the publication has closed for press.

□ Subscription Rates: UK £13.15 including postage. Airmail and other rates upon application to ETI Subscriptions Department, 513 London Road, Thornton Heath, Surrey CR4 6AR.

## EDITORIAL AND ADVERTISEMENT OFFICE

145 Charing Cross Road, London WC2H 0EE. Telephone 01-437 1002/3/4/5.  
 Telex 8811896.


## FEATURES

**DIGEST** ..... 11  
 All the latest news on the electronics scene: computing, audio, engineering, hi-fi, energy, lectures, a collection of shorts and two or three *extremely* silly items.

**BUYER'S GUIDE TO HI-FI** ..... 43  
 An eight-page special feature for anyone dipping a toe into the hi-fi market — or, indeed, anyone contemplating total immersion. A series of complete disc-playing systems is listed, each having the ETI stamp of approval and ranging from the affordable to the ridiculous. There's also advice on compact discs, cassette decks, tuners, and everything you wanted to know about shopping for hi-fi.

**CONFIGURATIONS** ..... 63  
 When is a diode not a diode? When it's got a couple of extra semiconducting layers and becomes a thyristor, that's when. Ian Sinclair takes a look at four-layer devices and their uses.

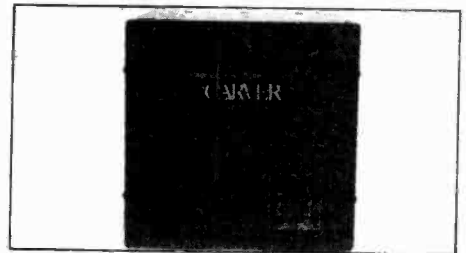**TECH TIPS** ..... 74  
 More circuit design ideas from our ever-inventive readership: this month we feature a simple stylophone and active circuitry for a bass guitar.



## PROJECTS

**STABILISED PSU** ..... 18  
 We welcome J. Linsley Hood to the pages of ETI with this article on the merits of stabilised power supplies, concluding with two designs that will give you the best from your hi-fi.

**60 W NDFL POWER AMP** ..... 24  
 After last month's feature on nested differentiating feedback loops, we present a 60 W, two-NDFL design with very low distortion. Use it as a module to upgrade your hi-fi or as the basis for a whole new power amp.

**COMPRESSOR/LIMITER** ..... 32  
 Banish the overload blues with our broadcast-quality compressor/ limiter. This unit uses common components but has a spec straight out of a professional studio.

**BALANCED LINE PREAMP** ..... 38  
 This balanced input differential preamp will allow the use of transducers having long leads, with low noise and low distortion.

**ZX81 MUSIC BOARD PART 2** ..... 54  
 To conclude this project we provide full listings and explanations of the software that enables you to use the music board to the full.

**ORGAN PART 4** ..... 67  
 Our final article in this very popular series describes the construction of the Victory organ and details all the parts and prices. A must for the serious musician.

**STAGE LIGHTING PART 4** ..... 70  
 The last part of this project gives you the remaining overlays for the autofade units and the triac power boards.

**FOIL PATTERNS** ..... 84

## INFORMATION

**NEXT MONTH'S ETI** ..... 7  
**BOOK SERVICE** ..... 81

**PCB SERVICE** ..... 87







SWITCHES

TOGGLE: 2A, 250V SPST 33p DPDT 44p
SUB-MIN TOGGLE SPST on/off 54p SPST c/cover 60p SPDT centre off 85p SPDT biased both 105p SPDT moment 99p DPDT moment 145p
THUMBUTTON 6A with 10mm Button SPDT latching 99p DPDT latching 145p SPDT moment 99p DPDT moment 145p
Mini Non Locking Push to Make 15p Push to Break 25p

DIL SWITCHES

(SPST) 4 way 70p; 6 way 85p; 8 way 90p; 10 way 145p. (SPDT) 4 way 190p.
ROTARY SWITCHES: (Adjustable Stop type) 1 pole/2 to 12 way; 2p/2 to 6 way; 3 pole/2 to 12 way; 4p/2 to 3 way 45p
ROTARY: Mains DP 250V 4 Amp on/off 68p
ROTARY: (Makfa-switch) Make a multiway switch. Shafting assembly has adjustable stop. Accommodates up to 6 wafers (max. 6 pole/12 way + DP switch). Mechanism only 90p
WAFERS: (make before break) to fit the above switch mechanism. 1 pole/12 way; 2 pole/6 way; 3 pole/4 way; 4 pole/3 way; 6/2 way; Mains DP 4A Switch to fit 45p Spacers 4P. Screen 6p
ROCKER: 5A/250V SPST 28p ROCKER: 10A/250V SPDT 38p ROCKER: 10A/250V DPDT c/off 95p ROCKER: 10A/250V DPST with neon 85p
THUMBWHEEL Mini front mount. Decade Switch Module B.C.D. Switch Module Mounting Cheeks (per pair) 75p

VEROBOARD

0.1in clad plain 2 1/2 x 3 1/4 85p 2 1/2 x 5 100p 3 1/4 x 3 1/4 100p 3 1/4 x 5 115p 3 1/4 x 7 390p 4 3/4 x 17 455p Pkt. of 100 pins 55p Spot face cutter 150p Pin insertion tool 185p
VQ Board 195p DIP Board 395p Vero Strip 85p
PROTO DECS Veroblock 405p S-Dec 380p Eurobreadboard 520p Superstrip 575p Superstrip SS2 1350p
DALO ETCH RESIST PEN Plus spare tip 90p
ULTRASONIC TRANSDUCER 40KHz 325 p

VEN WIRING

PEN + spool 340p Spare spool 75p Combs 6p
FERRIC CHLORIDE 1 lb bag Anhydrous 195p + 50p P&P

COPPER CLAD BOARDS

Single sided 6 x 6 90p 6 x 12 150p Double sided 9.5 x 8.5 110p 9.5p S.R.B 195p

DIL SOCKETS

Low Wire Prof Wrap 8pin 14p 10pin 16p 16pin 10p 42p 18pin 16p 62p 20pin 22p 80p 22pin 22p 85p 24pin 25p 70p 28pin 28p 80p 40pin 30p 80p

EDGE CONNECTORS

2 x 15 way 140p 2 x 18 way 180p 2 x 22 way 200p 2 x 23 way 175p 2 x 25 way 225p 2 x 28 way 190p 2 x 30 way 245p 2 x 36 way 295p 2 x 40 way 315p 2 x 43 way 395p 2 x 75 way 650p

ANTEX SOLDERING IRON

C-15W 465p CX17W 475p CCN-15W 495p CX25W 510p Spare tips, assorted sizes 210p Spare elements 50p Iron Stand with sponge 185p

SIL SOCKETS

0.1" pitch 20 way 65p

ETI PROJECTS

We stock most of the parts
6 inches 165p 200p 300p 450p 12 inches 195p 215p 315p 465p 24 inches 210p 235p 340p 540p 36 inches 230p 250p 375p 595p

JUMPER LEADS

(Ribbon Cable Assembly) Length 14 pin 16 pin 24 pin 40 pin Single ended DIP (Header Plug) Jumper 145p 165p 240p 380p Double ended DIP (Header Plug) Jumper 165p 205p 300p 465p 20 pin 26 pin 34 pin 40 pin 200p 280p 300p 540p

ETI

198p

ICD

Female Header Socket Jumper Leads 24" 150p 300p 480p 525p Single ended 160p 370p Double ended 290p 370p 480p 525p

TRANSFORMERS

3-0-3V; 0-0-6V; 0-0-9V; 12-0-12V; 15-0-15V @100mA 85p
pcb mounting. Miniature, Split Bobbin
3VA: 2x1V-0.25A; 2x9V-0.15A; 2x12V-0.12A; 2x15V-0.1A 200p
6VA: 2x6V-0.5A; 2x9V-0.3A; 2x12V-0.25A; 2x15V-0.2A 270p
Standard Split Bobbin type:
6VA: 2x6V-0.5A; 2x9V-0.4A; 2x12V-0.3A 220p
2x15V-0.25A
12VA: 2x4.5V-1.3A; 2x5V-1A; 2x9V-0.6A; 2x12V-0.5A; 2x15V-0.4A; 2x20V-0.3A 290p (35p p&p)
24VA: 2x6V-1A; 2x9V-1.2A; 2x12V-1A; 2x15V-0.8A; 2x20V-0.6A 330p (60p p&p)
50VA: 2x6V-4A; 2x9V-2.5A; 2x12V-2A; 2x15V-1.5A; 2x20V-1.2A; 2x25V-1A; 2x30V-0.8A 460p (60p p&p)
Specially wound for Multirail Computer PSUs 50VA: Outputs -5V/5A +12V, +25V, +50V -12V at 1A
100VA: 2x12V-4A; 2x15V-3A; 2x20V-2.5A; 2x25V-2A; 2x30V-1.5A; 2x50V-1A 920p (75p p&p charge to be added over and above our normal postal charge).

VOLTAGE REGULATORS

1A TO220 Plastic Caseing
5V 7805 40p 7905 46p 12V 7812 40p 7908 46p 15V 7815 40p 7912 46p 18V 7818 40p 7915 46p 24V 7824 40p 7924 46p
100mA TO92 Plastic package
5V 78L05 30p 79L05 60p 6V 78L06 30p 7V 78L08 30p 12V 78L12 30p 79L12 80p 15V 78L15 30p 79L15 80p

SOLDERCON PINS

ideal for making SIL or DIL sockets
100 pins 75p 500 pins 350p

ALUM BOXES

3 x 2 x 1" 85p 4 x 2 x 2" 85p 4 x 2 x 2 1/2" 103p 4 x 4 x 2" 105p 4 x 4 x 2 1/2" 120p 5 x 4 x 2 1/2" 120p 5 x 4 x 2" 120p 5 x 2 1/2 x 2 1/2" 120p 6 x 4 x 2" 120p 6 x 4 x 3" 180p 6 x 4 x 3 1/2" 180p 8 x 6 x 3" 210p 10 x 4 x 3" 240p 10 x 7 x 3" 270p 12 x 5 x 3" 280p 12 x 8 x 3" 290p

'D' CONNECTORS

miniature 9 way 15 way 25 way 37 way
Male Solder lugs 80p 105p 180p 250p Angle pins 150p 210p 250p 385p PCB pins 120p 130p 185p 285p
Female Solder lugs 105p 180p 280p 335p Angle pins 165p 215p 290p 440p PCB pins 150p 180p 240p 320p
IDC 25 way 'D' Plug 385p; Socket 450p

25 way 'D' CONNECTOR (RS232)

Jumpe Lead Cable Assembly 18" long, Single end, Male 495p 18" long, Single end, Female 525p 36" long, Double Ended, M/M 1025p 36" long, Double Ended, F/F 1050p 36" long, Double Ended, M/F 995p

SPECIAL OFFER

2764 1+ 50+ 450p 395p

OPTO ELECTRONICS

Table with columns for part numbers and prices. Includes items like TL209 Red, TL211 Grn, TL212 Yel, TL220 2" Red, etc.

ISOLATORS

Table with columns for part numbers and prices. Includes items like IL74, IL704, IL707, etc.

REFLECTIVE

Table with columns for part numbers and prices. Includes items like SW139 170p, SW139 170p, etc.

OPTO

Table with columns for part numbers and prices. Includes items like LS400C 255, OCP71 120, etc.

COMPUTER CORNER

● MX80FT/3 EPSON PRINTER 10" & Friction feed, 9x9 matrix 80 column, Speed 80CPS, Bidirectional, Centronics Interface standard, Baud-rate 110-9600 (B3S22, Hi-Res, Bit Image graphics, Subscript & Superscript, Underlining facility plus 500 sheets of paper FREE £324 + £7 carr
● MX100 EPSON Printer, 136 Column, 15" carriage, plus all the features of MX80FT/3. Plus FREE 500 sheets of Paper. Only £425 + carr.
● SEIKOSHA GP100A, 10" Tractor Feed, 80 Colmn, 30CPS, Normal and Double Width Char. Dot Res Graphics. £175 (£7 car)
● SEIKOSHA GP250X, 10", 50 CPS, Normal and Double width and height Char. RS232 and Centronix Infr. standard £240 (£7 car)
● Printer Cable for our printers and BBC £12
● SOFTY II. An intelligent Eprom Programmer and Emulator. Accepts a 24 pin 5V Eprom. Has Memory Map TV Display, RS232 and Centronics I/P & O/P. Copies, Emulates and programs. RS 232 and centronics routines standard. PSU included. £169
● TEXT EPROM ERASER Erases up to 32 ICs in 15-30 minutes...£33
● TEXT EPROM ERASER with a safety switch...£35
● TEXT EPROM ERASER plus our Solid State ELECTRONIC TIMER...£44
● ELECTRONIC TIMER, Solid state, 15-30 min. Connects directly to above Erasers. Protects your expensive Chips from overcooking. Our timer pays for itself in no time...£15
● SPARE 'UV' Lamp bulb...£8
● POWER SUPPLY, Regulated with Overload protection. Variable Output, 5V to 15V at 4A. Professionally finished...£38
● MULTIRAIL POWER SUPPLY KIT. Especially designed for Micros. Tested output: +5V/5A; +12V; +25V; -12V of 1A £37
● C12 COMPUTER GRADE CASSETTES in library cases...40p
● 8 1/2" & 9 1/2" Fan Fold paper (1000 sheets)...£7 + 150p carr

NEC PC8023BE-C PRINTER

£320 £7 car)
MICROLINE-82A PRINTER
80 column, 120 CPS bidirectional, Logic seeking Tractor & Friction feed 9x9 matrix, true decoders, 40,66,80 or 136 colms per line £325
ORIC MICROCOMPUTERS
16K and 48K versions available.
MONITORS
● MICROVITEC 1431. 14" Colour Monitor. RGB input (as used in BBC prog.) £250
● BMC BM1401 14" Colour Monitor, RGB input £235
● ZENITH 12" Green Monitor, Hi-Res Carriage on all Monitors is £7 (Securitor) £80
CASSETTE RECORDERS for MICROS
Slimline Portable Cassette players specially made for Microcomputers AC/DC operational £26
WEROM for ACORN ATOM
A highly sophisticated Acorn Utility ROM. Plugs straight into floating point Atom's Utility Socket. Gives many unique BASIC Extensions: Hi-speed Interf. 2 Key rollover Keyboard, Full disassembler, Memory dump modify, Machine code breakpoints: Basic error trapping; READ, DATA & RESTORE: Full BASIC Keyboard scanner (BBC like); Find line & delete; Auto line numbering; Plus: Chain, Cursor movement. Loopaborting; Easily extendible further. Manual supplied. £14
ULTIMUM
WATFORD'S own most versatile MICRO EXPANSION SYSTEM. Ideal for interfacing with APPLE, ATOM, DRAGON, PET, RESEARCH MACHINE, SPECTRUM, SUPERBOARD, VIDEO GENIE, ZX81, etc. Low Cost, High Spec. As published in Practical Electronics starting from November 1982.
Send SAE for details.

RELAYS

Miniature, enclosed, PCB mount. SINGLE POLE Changeover. RL-91 205V Coil, 12V DC, 10V5 to 19.5V, 10A at 30V DC or 250V AC 186p DOUBLE POLE Changeover. 6A 30V DC or 250V AC RL6-100 53V Coil, 6V DC (5V4 to 9V9 19V5) 195p RL6-114 740Q Coil, 24V DC (22V to 37V) 200p
AMPHENOL PLUGS
IEEE 24 Way 550 Centronics Parallel 36 Way solder 430 Centronics Parallel 36 Way IDC 596 Centronics 36 Way IDC Female 520p
BUZZERS, miniature, solid-state 6V, 9V & 12V 70p
PIEZO TRANSDUCERS PB2720 65p
LOUDSPEAKERS
Miniature, 0.3W; 8Ω 80p 2in, 3in, 2in, 3in 2in 40Ω, 64Ω or 80Ω 80p
ASTEC UHF MODULATORS
Standard 6MHz 325p Wideband 8MHz 480p
'WEMON' New Version WATFORD'S Ultimate Monitor IC
A 4K Monitor chip specially designed to produce the best from your: Superboard Series I & II, Enhanced Superboard & UK101. As reviewed by Dr. A. Bark in Practical Electronics, June 1981. Only £10
BBC MICRO AND UPGRADE KITS
(Our BBC Micro Upgrade Kits will save you £55s...)
BBC Micro Model A £299 (incl VAT) Model B £399 (incl VAT)
(Our BBC Micro Upgrade Kits will save you £55s...)
16K Memory (8 x 4816P) £18 Printer User I/O Port Kit £6.98 Complete Printer Cable 36" £12 Disc Interface Kit £65 Analogue I/O Kit £6.45 Serial I/O Kit £6.70 Expansion Bus Kit £6.10 Complete Upgrade Kit from Model A to Mod. B £43
We supply complete range of BBC Plugs, Sockets, Leads, Peripherals, Software etc. Send SAE for list

PANEL METERS

FSD 60 x 46 x 35mm 0-50µA 0-100µA 0-500µA 0-1mA 0-5mA 0-10mA 0-50mA 0-100mA 0-500mA 0-1A 0-2V 0-25V 0-50V AC 0-300V AC "S" "VU" 425p each
CRYSTALS
32.768KHz 100 100KHz 236 200KHz 288 455KHz 370 1MHz 275 1.008M 382 1.28MHz 392 1.6MHz 395 1.8MHz 395 1.8432M 200 2.0MHz 225 2.4576M 200 3.278M 150 3.5794M 98 3.6864M 300 4.0MHz 180 4.032MHz 200 4.800MHz 200 4.194304M 200 4.433619M 100 6.0MHz 180 5.185MHz 300 5.24288M 390 7.68MHz 140 8.144MHz 150 6.5536MHz 225 7.0MHz 150 7.168MHz 250 7.68MHz 200 7.68MHz 250 8.0MHz 160 8.08333M 365 8.86723M 175 9.00MHz 150 10.0MHz 175 10.24MHz 200 10.74MHz 150 12.0MHz 175 12.528M 300 14.31814M 170 16.0MHz 200 16.0MHz 180 18.432M 160 20.0MHz 200 21.0MHz 150 19.968MHz 160 24.0MHz 170 24.930MHz 325 26.89M 150 27.84M 170 27.145M 180 38.66667M 175 38.666M 170 100.0MHz 285 116.0MHz 250

RELAYS

10 way 80p 16 way 130p 20 way 145p 26 way 175p 34 way 205p 40 way 220p 60 way 235p
PCB Plugs with latch Female Header Pin Str. Angle 80p 95p 105p 110p 115p 120p Female Card Edge Connect 120p
EURO CONNECTORS
Female Socket Str. Angle Str. Angle Plug Angle Plug Angle
DIN41617 170p - - 175p
DIN41612 235p 320p 220p 285p
2 x 32 A+B 275p 340p 240p 300p
DIN41612 3 x 32 A+B+C 380p 385p 280p 335p
DIL PLUG (Header) Solder IDC 14pin 40p 95p 16pin 45p 105p 24pin 85p 170p 40pin 250p 255p
RIBBON CABLE price per foot Grey Color 10 way 15p 28p 16 way 25p 40p 20 way 30p 60p 24 way 40p 65p 34 way 80p 65p 40 way 70p 90p 50 way 100p 135p 64 way 120p 180p
ZIF DIL SOCKETS 24 pin 575p 28 pin 820p 40 pin 975p
'U' CONNECTORS
miniature 9 way 15 way 25 way 37 way
Male Solder lugs 80p 105p 180p 250p Angle pins 150p 210p 250p 385p PCB pins 120p 130p 185p 285p
Female Solder lugs 105p 180p 280p 335p Angle pins 165p 215p 290p 440p PCB pins 150p 180p 240p 320p
IDC 25 way 'D' Plug 385p; Socket 450p

RELAYS

VEROBOARD 0.1in clad plain 2 1/2 x 3 1/4 85p 2 1/2 x 5 100p 3 1/4 x 3 1/4 100p 3 1/4 x 5 115p 3 1/4 x 7 390p 4 3/4 x 17 455p Pkt. of 100 pins 55p Spot face cutter 150p Pin insertion tool 185p
VQ Board 195p DIP Board 395p Vero Strip 85p
PROTO DECS Veroblock 405p S-Dec 380p Eurobreadboard 520p Superstrip 575p Superstrip SS2 1350p
DALO ETCH RESIST PEN Plus spare tip 90p
ULTRASONIC TRANSDUCER 40KHz 325 p
VEN WIRING PEN + spool 340p Spare spool 75p Combs 6p
FERRIC CHLORIDE 1 lb bag Anhydrous 195p + 50p P&P
COPPER CLAD BOARDS Single sided 6 x 6 90p 6 x 12 150p Double sided 9.5 x 8.5 110p 9.5p S.R.B 195p
DIL SOCKETS Low Wire Prof Wrap 8pin 14p 10pin 16p 16pin 10p 42p 18pin 16p 62p 20pin 22p 80p 22pin 22p 85p 24pin 25p 70p 28pin 28p 80p 40pin 30p 80p
EDGE CONNECTORS 2 x 15 way 140p 2 x 18 way 180p 2 x 22 way 200p 2 x 23 way 175p 2 x 25 way 225p 2 x 28 way 190p 2 x 30 way 245p 2 x 36 way 295p 2 x 40 way 315p 2 x 43 way 395p 2 x 75 way 650p
ANTEX SOLDERING IRON C-15W 465p CX17W 475p CCN-15W 495p CX25W 510p Spare tips, assorted sizes 210p Spare elements 50p Iron Stand with sponge 185p
SIL SOCKETS 0.1" pitch 20 way 65p
'D' CONNECTORS miniature 9 way 15 way 25 way 37 way Male Solder lugs 80p 105p 180p 250p Angle pins 150p 210p 250p 385p PCB pins 120p 130p 185p 285p Female Solder lugs 105p 180p 280p 335p Angle pins 165p 215p 290p 440p PCB pins 150p 180p 240p 320p IDC 25 way 'D' Plug 385p; Socket 450p
25 way 'D' CONNECTOR (RS232) Jumpe Lead Cable Assembly 18" long, Single end, Male 495p 18" long, Single end, Female 525p 36" long, Double Ended, M/M 1025p 36" long, Double Ended, F/F 1050p 36" long, Double Ended, M/F 995p
SPECIAL OFFER 2764 1+ 50+ 450p 395p

RELAYS

SWITCHES TOGGLE: 2A, 250V SPST 33p DPDT 44p
SUB-MIN TOGGLE SPST on/off 54p SPST c/cover 60p SPDT centre off 85p SPDT biased both 105p SPDT moment 99p DPDT moment 145p
THUMBUTTON 6A with 10mm Button SPDT latching 99p DPDT latching 145p SPDT moment 99p DPDT moment 145p
Mini Non Locking Push to Make 15p Push to Break 25p
DIL SWITCHES (SPST) 4 way 70p; 6 way 85p; 8 way 90p; 10 way 145p. (SPDT) 4 way 190p.
ROTARY SWITCHES: (Adjustable Stop type) 1 pole/2 to 12 way; 2p/2 to 6 way; 3 pole/2 to 12 way; 4p/2 to 3 way 45p
ROTARY: Mains DP 250V 4 Amp on/off 68p
ROTARY: (Makfa-switch) Make a multiway switch. Shafting assembly has adjustable stop. Accommodates up to 6 wafers (max. 6 pole/12 way + DP switch). Mechanism only 90p
WAFERS: (make before break) to fit the above switch mechanism. 1 pole/12 way; 2 pole/6 way; 3 pole/4 way; 4 pole/3 way; 6/2 way; Mains DP 4A Switch to fit 45p Spacers 4P. Screen 6p
ROCKER: 5A/250V SPST 28p ROCKER: 10A/250V SPDT 38p ROCKER: 10A/250V DPDT c/off 95p ROCKER: 10A/250V DPST with neon 85p
THUMBWHEEL Mini front mount. Decade Switch Module B.C.D. Switch Module Mounting Cheeks (per pair) 75p
JUMPER LEADS (Ribbon Cable Assembly) Length 14 pin 16 pin 24 pin 40 pin Single ended DIP (Header Plug) Jumper 145p 165p 240p 380p Double ended DIP (Header Plug) Jumper 165p 205p 300p 465p 20 pin 26 pin 34 pin 40 pin 200p 280p 300p 540p
ETI PROJECTS We stock most of the parts
6 inches 165p 200p 300p 450p 12 inches 195p 215p 315p 465p 24 inches 210p 235p 340p 540p 36 inches 230p 250p 375p 595p
ICD Female Header Socket Jumper Leads 24" 150p 300p 480p 525p Single ended 160p 370p Double ended 290p 370p 480p 525p
TRANSFORMERS 3-0-3V; 0-0-6V; 0-0-9V; 12-0-12V; 15-0-15V @100mA 85p
pcb mounting. Miniature, Split Bobbin
3VA: 2x1V-0.25A; 2x9V-0.15A; 2x12V-0.12A; 2x15V-0.1A 200p
6VA: 2x6V-0.5A; 2x9V-0.3A; 2x12V-0.25A; 2x15V-0.2A 270p
Standard Split Bobbin type:
6VA: 2x6V-0.5A; 2x9V-0.4A; 2x12V-0.3A 220p
2x15V-0.25A
12VA: 2x4.5V-1.3A; 2x5V-1A; 2x9V-0.6A; 2x12V-0.5A; 2x15V-0.4A; 2x20V-0.3A 290p (35p p&p)
24VA: 2x6V-1A; 2x9V-1.2A; 2x12V-1A; 2x15V-0.8A; 2x20V-0.6A 330p (60p p&p)
50VA: 2x6V-4A; 2x9V-2.5A; 2x12V-2A; 2x15V-1.5A; 2x20V-1.2A; 2x25V-1A; 2x30V-0.8A 460p (60p p&p)
Specially wound for Multirail Computer PSUs 50VA: Outputs -5V/5A +12V, +25V, +50V -12V at 1A
100VA: 2x12V-4A; 2x15V-3A; 2x20V-2.5A; 2x25V-2A; 2x30V-1.5A; 2x50V-1A 920p (75p p&p charge to be added over and above our normal postal charge).

RELAYS

VEROBOARD 0.1in clad plain 2 1/2 x 3 1/4 85p 2 1/2 x 5 100p 3 1/4 x 3 1/4 100p 3 1/4 x 5 115p 3 1/4 x 7 390p 4 3/4 x 17 455p Pkt. of 100 pins 55p Spot face cutter 150p Pin insertion tool 185p
VQ Board 195p DIP Board 395p Vero Strip 85p
PROTO DECS Veroblock 405p S-Dec 380p Eurobreadboard 520p Superstrip 575p Superstrip SS2 1350p
DALO ETCH RESIST PEN Plus spare tip 90p
ULTRASONIC TRANSDUCER 40KHz 325 p
VEN WIRING PEN + spool 340p Spare spool 75p Combs 6p
FERRIC CHLORIDE 1 lb bag Anhydrous 195p + 50p P&P
COPPER CLAD BOARDS Single sided 6 x 6 90p 6 x 12 150p Double sided 9.5 x 8.5 110p 9.5p S.R.B 195p
DIL SOCKETS Low Wire Prof Wrap 8pin 14p 10pin 16p 16pin 10p 42p 18pin 16p 62p 20pin 22p 80p 22pin 22p 85p 24pin 25p 70p 28pin 28p 80p 40pin 30p 80p
EDGE CONNECTORS 2 x 15 way 140p 2 x 18 way 180p 2 x 22 way 200p 2 x 23 way 175p 2 x 25 way 225p 2 x 28 way 190p 2 x 30 way 245p 2 x 36 way 295p 2 x 40 way 315p 2 x 43 way 395p 2 x 75 way 650p
ANTEX SOLDERING IRON C-15W 465p CX17W 475p CCN-15W 495p CX25W 510p Spare tips, assorted sizes 210p Spare elements 50p Iron Stand with sponge 185p
SIL SOCKETS 0.1" pitch 20 way 65p
'D' CONNECTORS miniature 9 way 15 way 25 way 37 way Male Solder lugs 80p 105p 180p 250p Angle pins 150p 210p 250p 385p PCB pins 120p 130p 185p 285p Female Solder lugs 105p 180p 280p 335p Angle pins 165p 215p 290p 440p PCB pins 150p 180p 240p 320p IDC 25 way 'D' Plug 385p; Socket 450p
25 way 'D' CONNECTOR (RS232) Jumpe Lead Cable Assembly 18" long, Single end, Male 495p 18" long, Single end, Female 525p 36" long, Double Ended, M/M 1025p 36" long, Double Ended, F/F 1050p 36" long, Double Ended, M/F 995p
SPECIAL OFFER 2764 1+ 50+ 450p 395p

RELAYS

SWITCHES TOGGLE: 2A, 250V SPST 33p DPDT 44p
SUB-MIN TOGGLE SPST on/off 54p SPST c/cover 60p SPDT centre off 85p SPDT biased both 105p SPDT moment 99p DPDT moment 145p
THUMBUTTON 6A with 10mm Button SPDT latching 99p DPDT latching 145p SPDT moment 99p DPDT moment 145p
Mini Non Locking Push to Make 15p Push to Break 25p
DIL SWITCHES (SPST) 4 way 70p; 6 way 85p; 8 way 90p; 10 way 145p. (SPDT) 4 way 190p.
ROTARY SWITCHES: (Adjustable Stop type) 1 pole/2 to 12 way; 2p/2 to 6 way; 3 pole/2 to 12 way; 4p/2 to 3 way 45p
ROTARY: Mains DP 250V 4 Amp on/off 68p
ROTARY: (Makfa-switch) Make a multiway switch. Shafting assembly has adjustable stop. Accommodates up to 6 wafers (max. 6 pole/12 way + DP switch). Mechanism only 90p
WAFERS: (make before break) to fit the above switch mechanism. 1 pole/12 way; 2 pole/6 way; 3 pole/4 way; 4 pole/3 way; 6/2 way; Mains DP 4A Switch to fit 45p Spacers 4P. Screen 6p
ROCKER: 5A/250V SPST 28p ROCKER: 10A/250V SPDT 38p ROCKER: 10A/250V DPDT c/off 95p ROCKER: 10A/250V DPST with neon 85p
THUMBWHEEL Mini front mount. Decade Switch Module B.C.D. Switch Module Mounting Cheeks (per pair) 75p
JUMPER LEADS (Ribbon Cable Assembly) Length 14 pin 16 pin 24 pin 40 pin Single ended DIP (Header Plug) Jumper 145p 165p 240p 380p Double ended DIP (Header Plug) Jumper 165p 205p 300p 465p 20 pin 26 pin 34 pin 40 pin 200p 280p 300p 540p
ETI PROJECTS

# Rapid Electronics

**MAIL ORDERS:**  
Unit 1, Hill Farm Industrial Estate,  
Boxted, Colchester, Essex CO4 5RD.  
**TELEPHONE ORDERS:**  
Colchester (0206) 36412.

**ACCESS AND  
BARCLAYCARD  
WELCOME**

## LINEAR

555CMOS	80	ICL7106	790
556CMOS	150	ICL7611	95
709	25	ICL7621	180
741	14	ICL7622	180
748	35	ICL8038	295
9400C	350	ICM722A	200
AY-3-1270	720	ICM722A	200
AY-3-8910	370	CM7555	80
AY-3-8912	540	LF351	45
CA3040	60	LF353	85
CA3080	65	LF356	90
CA3089	190	LM10	360
CA3190AQ	375	LM301A	25
CA3130E	85	LM311	70
CA3140E	36	LM318	120
CA3161E	100	LM324	100
CA3189	290	LM334Z	100
CA3240E	110	LM335Z	125

LM339	45	LM3911	120
LM348	60	LM3914	175
LM358	60	LM3915	195
LM377	170	LM3960	105
LM380	65	MC1496	68
LM381	120	MC3340	135
LM382	120	MF10CN	350
LM384	130	ML922	400
LM386	65	ML924	195
LM387	120	ML925	210
LM393	100	ML926	140
LM709	25	ML927	140
LM711	60	ML928	140
LM725	350	ML929	140
LM733	75	MM5387A	465
LM741	14	NE529	225
LM747	60	NE531	150
LM1458	40	NE544	205
LM2917	200	NE555	16
LM3900	45	NE556	45
LM3909	70	NE565	110

NE566	140	TL064	96
NE567	100	TL071	30
NE570	370	TL072	50
NE571	370	TL074	95
RC4136	55	TL081	25
RC4158	60	TL082	45
SL480	170	TL084	95
SL490	250	TL170	50
SN7601B	150	UA2240	120
SN76477	380	ULN2003	85
SP829	250	ULN2004	90
TBA1205	70	XR2206	290
TBA800	75	ZN414	100
TBA810	96	ZN423	135
TBA820	70	ZN424	135
TBA950	220	ZN425E	350
TDA1008	320	ZN427E	330
TDA1022	490	ZN426E	650
TDA1024	125	ZN428E	480
TL061	40	ZN459	285
TL062	60	ZN1034E	200

## TRANSISTORS

AC125	35	BC149	9
AC126	25	BC157	8
AC127	25	BC158	10
AC128	20	BC159	8
AC129	25	BC160	45
AC187	22	BC168C	10
AC188	22	BC169C	10
AD142	120	BC170	8
AD149	80	BC171	10
AD161	40	BC172	8
AD162	40	BC177	18
AF124	60	BC178	18
AF126	50	BC179	18
AF139	40	BC182	10
AF186	70	BC182L	8
AF239	75	BC183	10
BC107	10	BC183L	10
BC107B	12	BC184	10
BC108	10	BC184L	7
BC108B	12	BC121	7
BC108C	12	BC122	7
BC109	10	BC123	10
BC109C	12	BC213L	10
BC114	18	BC214	10
BC115	22	BC214L	8
BC117	18	BC237	8
BC119	35	BC238	14
BC137	40	BC308	12
BC139	40	BC327	14
BC140	28	BC328	14
BC141	30	BC337	14
BC142	25	BC338	14
BC143	25	BC477	39
BC147	8	BC478	30
BC148	8	BC479	30

BC517	40	BF337	40
BC547	7	BF402	23
BC548	10	BF403	23
BC549	10	BF404	23
BC558	10	BF405	23
BC570	18	BF406	23
BC571	18	BF407	23
BC572	18	BF408	23
BD1131	10	BF409	23
BD133	35	BF410	23
BD135	35	BF411	23
BD136	35	BF412	23
BD137	35	BF413	23
BD138	35	BF414	23
BD139	35	BF415	23
BD140	35	BF416	23
BD141	35	BF417	23
BD142	35	BF418	23
BD143	35	BF419	23
BD144	35	BF420	23
BD145	35	BF421	23
BD146	35	BF422	23
BD147	35	BF423	23
BD148	35	BF424	23
BD149	35	BF425	23
BD150	35	BF426	23
BD151	35	BF427	23
BD152	35	BF428	23
BD153	35	BF429	23
BD154	35	BF430	23
BD155	35	BF431	23
BD156	35	BF432	23
BD157	35	BF433	23
BD158	35	BF434	23
BD159	35	BF435	23
BD160	35	BF436	23
BD161	35	BF437	23
BD162	35	BF438	23
BD163	35	BF439	23
BD164	35	BF440	23
BD165	35	BF441	23
BD166	35	BF442	23
BD167	35	BF443	23
BD168	35	BF444	23
BD169	35	BF445	23
BD170	35	BF446	23
BD171	35	BF447	23
BD172	35	BF448	23
BD173	35	BF449	23
BD174	35	BF450	23
BD175	35	BF451	23
BD176	35	BF452	23
BD177	35	BF453	23
BD178	35	BF454	23
BD179	35	BF455	23
BD180	35	BF456	23
BD181	35	BF457	23
BD182	35	BF458	23
BD183	35	BF459	23
BD184	35	BF460	23
BD185	35	BF461	23
BD186	35	BF462	23
BD187	35	BF463	23
BD188	35	BF464	23
BD189	35	BF465	23
BD190	35	BF466	23
BD191	35	BF467	23
BD192	35	BF468	23
BD193	35	BF469	23
BD194	35	BF470	23
BD195	35	BF471	23
BD196	35	BF472	23
BD197	35	BF473	23
BD198	35	BF474	23
BD199	35	BF475	23
BD200	35	BF476	23

BF337	40	MPS56	60
BF402	23	TIP29A	60
BF403	23	TIP29B	55
BF404	23	TIP29C	37
BF405	23	TIP30A	35
BF406	23	TIP30B	15
BF407	23	TIP30C	37
BF408	23	TIP31A	35
BF409	23	TIP31C	35
BF410	23	TIP32A	35
BF411	23	TIP32C	37
BF412	23	TIP33A	50
BF413	23	TIP33C	75
BF414	23	TIP34A	60
BF415	23	TIP34B	60
BF416	23	TIP35A	105
BF417	23	TIP35C	125
BF418	23	TIP36A	125
BF419	23	TIP36C	135
BF420	23	TIP41A	45
BF421	23	TIP42A	45
BF422	23	TIP42B	45
BF423	23	TIP42C	90
BF424	23	TIP42D	90
BF425	23	TIP42E	90
BF426	23	TIP42F	90
BF427	23	TIP42G	90
BF428	23	TIP42H	90
BF429	23	TIP42I	90
BF430	23	TIP42J	90
BF431	23	TIP42K	90
BF432	23	TIP42L	90
BF433	23	TIP42M	90
BF434	23	TIP42N	90
BF435	23	TIP42O	90
BF436	23	TIP42P	90
BF437	23	TIP42Q	90
BF438	23	TIP42R	90
BF439	23	TIP42S	90
BF440	23	TIP42T	90
BF441	23	TIP42U	90
BF442	23	TIP42V	90
BF443	23	TIP42W	90
BF444	23	TIP42X	90
BF445	23	TIP42Y	90
BF446	23	TIP42Z	90
BF447	23	TIP43A	90
BF448	23	TIP43B	90
BF449	23	TIP43C	90
BF450	23	TIP43D	90
BF451	23	TIP43E	90
BF452	23	TIP43F	90
BF453	23	TIP43G	90
BF454	23	TIP43H	90
BF455	23	TIP43I	90
BF456	23	TIP43J	90
BF457	23	TIP43K	90
BF458	23	TIP43L	90
BF459	23	TIP43M	90
BF460	23	TIP43N	90
BF461	23	TIP43O	90
BF462	23	TIP43P	90
BF463	23	TIP43Q	90
BF464	23	TIP43R	90
BF465	23	TIP43S	90
BF466	23	TIP43T	90
BF467	23	TIP43U	90
BF468	23	TIP43V	90
BF469	23	TIP43W	90
BF470	23	TIP43X	90
BF471	23	TIP43Y	90
BF472	23	TIP43Z	90
BF473	23	TIP44A	90
BF474	23	TIP44B	90
BF475	23	TIP44C	90
BF476	23	TIP44D	90
BF477	23	TIP44E	90
BF478	23	TIP44F	90
BF479	23	TIP44G	90
BF480	23	TIP44H	90
BF481	23	TIP44I	90
BF482	23	TIP44J	90
BF483	23	TIP44K	90
BF484	23	TIP44L	90
BF485	23	TIP44M	90
BF486	23	TIP44N	90
BF487	23	TIP44O	90
BF488	23	TIP44P	90
BF489	23	TIP44Q	90
BF490	23	TIP44R	90
BF491	23	TIP44S	90
BF492	23	TIP44T	90
BF493	23	TIP44U	90
BF494	23	TIP44V	90
BF495	23	TIP44W	90
BF496	23	TIP44X	90
BF497	23	TIP44Y	90
BF498	23	TIP44Z	90
BF499	23	TIP45A	90
BF500	23	TIP45B	90

## CABLES

20 metre pack single core connect-	
ing cable ten different colours, 65p	
Speaker cable	10p/m
Standard screened	16p/m
Twin screened	24p/m
2.5A 3 core mains	23p/m
10 way rainbow ribbon	65p/m
10 way rainbow ribbon	120p/m
10 way grey ribbon	38p/m
20 way grey ribbon	80p/m

## HARDWARE

PP3 battery clips	8
Red or black crocodile clips	6
Black pointer control knob	15
Pr Ultrasonic transducers	350
Pr 6V Electronic buzzer	60
Pr 12V Electronic buzzer	75
Pr 220V Piezo transducer	75
Pr 64mm 64 ohm speaker	70
Pr 64mm 8 ohm speaker	70
20mm panel fuseholder	25

## CAPACITORS

Polyester, radial, leads, 250v, C280	
type: 0.01, 0.015, 0.022, 0.033 -	
6p; 0.047, 0.068, 0.1 - 7p; 0.15, 0.22 -	
9p; 0.33, 0.47, 1.3p; 0.68 -	
20p; 1u - 23p	
Electrolytic, radial or axial leads:	
0.47/63V, 1/63V, 2.2/63V, 4.7/63V	
10/25V, 7p; 22/25V, 47/25V - 8p;	
100/25V - 9p; 220/25V - 30p;	
470/25V - 22p; 1000/25V - 30p;	
2200/25V - 50p	
Tan end power supply electrolytics:	
2200/40V - 110p; 4700/40V - 160p	
2200/63V - 140p; 4700/63V - 230p	
Polyester, miniature Siemens PCB:	
1n, 2n, 3n, 4n, 7n, 10n, 15n, 22n,	
27n, 33n, 47n, 68n, 80n, 100n, 9p;	
150n, 11p, 220n, 13p, 330n, 20p;	
470n 26p; 680n, 29p; 1u 33p; 2u, 2,	
50n	
Tantalum bead:	
0.1, 0.22, 0.33, 0.47, 1.0 @ 35V -	
12p; 2.2, 4.7, 10 @ 25V - 20p;	
15/16V - 30p; 22/16V - 27p; 33/	
16V - 45p; 47/6V - 27p; 47/16V -	
70p; 68/6V - 100p; 100/10V	



# electronics today

INTERNATIONAL

NEXT  
MONTH

## PSEUDOROM

We know, we know — we promised it *last* month. Well, it's taken us about that long to figure out how to fit it all into that sleek, compact shape you'll notice if you move your eyes a couple of inches to the right. Assuming you did, and have returned, then you have just been looking at 8K of low-power, CMOS RAM plus a bit of address decoding and battery backup which can be write-protected and made to appear as four 2K by 8 blocks, two 4K by 8 blocks, or one 8K by 8. Now you can develop software on a device which is faster than a speeding ROM and a lot easier to reprogram.

## SWITCHED MODE POWER SUPPLY


This professionally-designed unit is neat and compact, but it can deliver 12 V at 5 A without straining. Following on from our discussion of switched mode PSUs in the April issue, this project will shed more light on this seldom-discussed subject.

## DATA SHEET

With the runaway success of the Victory organ project that has been featured in the last four issues of ETI, have come requests for more information on the special chips used. Ever eager to oblige, next month's ETI contains a Data Sheet on both the M108 and the M208.
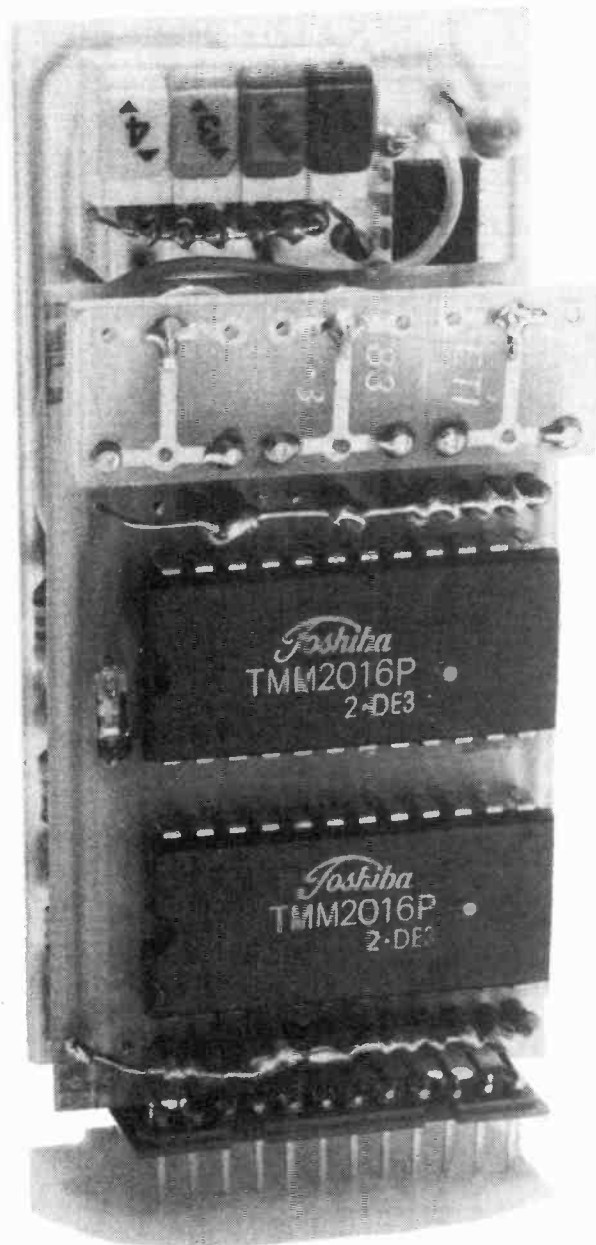
## COMPASS

This one's really something special. Not only does it display 16 points of the compass using an alphanumeric dot matrix read-out, but it uses a new kind of sensor that relies on an apparently new branch of number theory called cyclic binaries. It's pretty stylish and cheap, too. Get the next issue of ETI and you'll never lose your bearings in your boat or car.



DON'T MISS THE JUNE ETI

ON SALE 6th MAY

Articles described here are in an advanced state of preparation. However, circumstances may dictate changes to the final contents.





# CRICKLEWOOD — STOCKING PARTS OTHER STORES CANNOT REACH!

Items not fully covered on this list include: OPTO 7 seg LEDs, LCDs bezelled LEDs, Lamps, Lampholders, FUSES: 20mm 1/2 inch, slow or quick blow, Fuseholders, CONNECTORS: DIL, DIN, Phono, 1mm, 2mm, 4mm, Bulgun JSA, I.E.C. KNOBS: Plastic, Aluminium, Anodised, Collet, Pointer. SWITCHES: Toggle, Biased, Rocker, Rotary, Slide, Dip, Push. METERS: LCD, Analogue, Test and Panel. TOOLS: Pliers, Cutters, Strippers, Trimmers, Cable Cutters. And much, much more. All in stock items (that's 95%) posted same day, OFFICIAL ORDERS FROM SCHOOLS, GOVT DEPTS ETC WELCOME. OVERSEAS ORDERS WELCOME (CWO + ADEQUATE POSTAGE). QUANTITY DISCOUNTS BY NEGOTIATION. CRICKLEWOOD ELECTRONICS LTD., 40 CRICKLEWOOD BROADWAY, LONDON NW2 3ET. TEL: 01-452 0161. Telex 914977

★ THE LAZY WAY Phone your order through an Access, Barclaycard, Visa or American Express for immediate service; no extra charge, no minimum order.  
★ THE TRADITIONAL WAY Send cheque, PO or credit card number. Cash not encouraged but accepted (no coins please). All in stock items shipped same day.  
★ THE IDEAL WAY Call in and collect. We are on the main Edgware Rd (A5) just 1 1/2 miles from Staples Corner and approx 3 miles from Marble Arch.  
VAT Please add VAT at the current rate to all orders except books. VAT not chargeable abroad.  
POST, PACKING & INSURANCE Standard small order charge is 70p (more for heavier goods). Export orders minimum £1.50.

<p><b>TIS52</b> 46p <b>TIS64</b> 67p <b>TIS87</b> 60p <b>TIS88A</b> 62p <b>TIS90</b> 82p <b>TIS91</b> 30p <b>TIS92</b> 30p <b>TIS93</b> 54p <b>YN10KM</b> 80p <b>YN6AF</b> 80p <b>YN6AF</b> 80p <b>ZTX107</b> 10p <b>ZTX108</b> 10p <b>ZTX109</b> 12p <b>ZTX300</b> 13p <b>ZTX301</b> 15p <b>ZTX302</b> 23p <b>ZTX304</b> 15p <b>ZTX310</b> 35p <b>ZTX311</b> 32p <b>ZTX312</b> 35p <b>ZTX313</b> 34p <b>ZTX314</b> 24p <b>ZTX320</b> 35p <b>ZTX323</b> 35p <b>ZTX341</b> 35p <b>ZTX500</b> 14p <b>ZTX501</b> 14p <b>ZTX502</b> 17p <b>ZTX503</b> 17p <b>ZTX504</b> 24p <b>ZTX510</b> 34p <b>ZTX511</b> 24p <b>ZTX512</b> 24p <b>ZTX650</b> 46p</p> <p><b>DIACS</b> <b>BR100</b> 20p <b>ST2</b> 40p</p> <p><b>THYRISTORS</b> Sensitive Gate Small Signal <b>2N444</b> 1.80 <b>BT101</b> 500R 1.40 <b>BT106</b> 2.18 <b>BT107</b> 3.7p <b>BT108</b> 3.7p <b>BT109</b> 3.7p <b>BT802</b> 3.7p <b>BT803</b></p>
--

# BRADLEY MARSHALL LTD.

**SPECIALIST ELECTRONIC COMPONENT DISTRIBUTORS**  
**325 EDGWARE ROAD, LONDON W2 1BN Tel: 723-4242**

## CRIMSON ELEKTRIK

No	Modules	Price
2580	CE 608 40 Mono	18.26
2581	CE1004 100W 4 Mono	21.30
2582	CE1008 100W 8 Mono	23.90
2583	CE1704 170W 4 Mono	30.43
2584	CE1708 170 W 8 Mono	30.43
2585	CE3004 300W 4 Mono	42.60
	2585a	
FE 908	90W FET Mono	25.65
2585b	FE1704 170W FET Mono	33.48
2585c	BD1 Bridge Unit for Modules	7.13
2608	CPR 1X Pre-Amp Module	41.70

**WE ALSO STOCK ALL THE POWER SUPPLIES TO DRIVE THESE MODULES**  
**PS. THESE KITS AND MODULES ARE EXCLUSIVE OF VAT**

No	Complete Pre-Amp Kit	CK1010	Price
2615	Complete 40W Stereo Amp Kit	CK1040	£105.00
2616	Complete 80W Stereo Amp Kit	CK1080	£116.00
2616a	Complete 100W Stereo Amp Kit	CK1100	£131.00
2617	Add on Moving Coil Kit	MC12K	£21.74
2618	Pre-Amp Power Supply Kit	PSK	£17.39

## VELLEMAN KITS

No	Description	Price
K610	Mono UU using LEDs	8.18
K1798	Stereo UU using LEDs	15.53
K1874	Running Light Kit	12.56
K2571	Light Computer with EPROM	36.23
K2569	Three Tone Chime	6.56
K2575	Microprocessor Doorbell 25 tunes	15.53
K2544	Complex Sound Generator	8.28
K2032	Digital Panel Meter	15.53
K2557	Digital Thermometer	26.57
K2545	50Hz Crystal Time Base	11.39
K615	High Precision Stopwatch	43.13
	Description	Price

**WE STOCK A WIDE RANGE OF BOXES TO HOUSE THESE KITS IN. FROM VERY SMALL TO VERY LARGE 19" MAXIMUM**  
**PS. ALL KITS INCLUDE VAT**

Some are easy some are hard

No	Description	Price
K2543	Transistor Ignition	9.97
K2555	Digital Freq Counter for Receivers	37.74
K2566	3 Channel Coloured Light Organ	15.53
K2572	Universal Stereo Pre-Amplifier	6.56
K2574	Universal 4 Digit U/D counter with memory	34.16
K2577	Electric Motor Speed Control	7.59
K2579	Universal Start/Stop Timer	6.21
K2583	Heating Controller	75.00
K1682	Microprocessor Universal Timer (no case)	48.37
K2580	Electronic Power Switch Dimmer	10.00
K2551	Central Alarm Unit	18.70

## TELETEXT KIT

This unit will make your TV remote control (infra-red) and bring you closer to the amazing world of teletext. The kit can also be updated to incorporate full Prestel, and with a keyboard this can give you full message facilities for ordering foods or sending and receiving messages (E.G.) Booking your Holidays!

With a microcomputer as an alternative keyboard the world is even greater adding bulk updating to viewdata computers an receiving telesoftware for implementation to any personal computer.

Even without the Prestel option, Telesoftware from the Teletext pages free!

The full features of Teletext, including subtitles are all included in the basic kit.

An attractive stylish case is available to complement the finished kit.

Basic Teletext Kit (no box) £130 + VAT P/P £2.50  
 with box £144.95 + VAT P/P £3.00  
 box by itself £14.95 + VAT P/P 75p

## PRESTEL ADAPTOR

A Prestel micro computer adaptor to give full autodialing to your micro computer. All the usual Prestel facilities are added via this unit, plus many more, and, can operate to any viewdata computer.

You can shop from home, bank transmitt messages and receive software, which means that the uses your micro can be put to are limitless.

The unit is not restricted to just the UK, for at least 28 countries use the Prestel viewdata format, so you can also mail-order from anywhere. The Prestel unit is suitable for most micro computers even the ZX-81, so at the push of a button, the technology of tomorrow is in your home today.

## ANTEX

### Soldering Irons

X25	25W	5.30+
CX	17W	5.30+
C "iron"	15W	4.80+
CCN "ceramic"	15W	5.30+
Wide range of bits and elements in stock now.		
Soldering iron stand 2.40		
We stock multicore solder for normal use or fine.		

Iso-tip Cordless Iron 31-90+  
 Miniature low voltage soldering station 13.95+  
 Oryx50 50W temp controlled 15.50  
 Oryx super 30 5.90+  
 All irons are 240V mains. Earth Leakage current is less than 3 ua.  
 The temperature controlled iron can be controlled within  $\pm 2\%$  temperature range from 200°C to 400°C.

## ORYX

## COMPONENTS

Device	Price
Z80A	3.20
Z80A PIO	3.20
Z80A CTC	3.20
6800	6.50
6810	3.00
6821	4.25
65022CPU	7.50
2114(200ns)	1.80
2708	3.00
2716	3.20
2732	7.50
2532	3.50
2764 (200ns)	11.00
ADC0816 (8 bit)	14.90

We stock a very wide range of opto-devices, from Infra-Red to LED's to Opto-Couplers.

Check us out for competitive prices and helpful service.

We also stock 74 series 74LS, C mos, transistors, capacitors, resistors, LED's, zeners, diodes, jack plugs, mains plugs XLR plugs, cannon plugs, arrow switches BNC connectors, reducers, photolok, developer, PC board, sensitive & normal, boxes, wire cutters, strip-pers, Edge connectors, pots, batteries, digital pulsers, logic probes, proto-boards, vero board.

This is just a small sample of what we stock, if you like to see more send £1.00 to us for our NEW 1983 CATALOGUE.

PLEASE REMEMBER TO ADD VAT + 60P P/P

## BOOKS

### \*New Books

Please Note. Books are VAT exempt but add £1.00 to cover P/P

The 9900 Family Data Book	10.00
The Opto-Electronics Data Book	4.00
The Bipolar Microcomputer Databook	4.50
The Interface Circuits Data Book	7.00
The TTL Data Book	8.50
MDS Memory Data Book	3.95
The Linear Control Circuits Data Book	4.00
The Voltage Regulator Data Book	4.50
The Power-semiconductor Data Book	9.00
*TTI Data Book Volume I	9.00
*TTI Data Book Volume II	8.00

**Why not try our mail order service, it's fast and efficient. We take Barclay, Access, Am Exp, Diners or Cheque. Cheques made payable to Bradley Marshall Ltd.**



# DIGEST



## Disc Jokey?

Despite the fact that LP records are a bit bulky when strapped to your waist, Audio Technica will be introducing (in April, or so we're led to believe) their AT 727 Sound Burger. Assuming this is not an April Fool's joke played on gullible journalists, details are as follows: the Sound Burger will play LPs or singles through its own headphones or an external amp and speakers, on any 'reasonably flat' surface, driven by its own batteries or an optional mains adaptor. The turntable is belt driven, the arm is dynamically balanced (we think that means springs), the cartridge is magnetic and the price is £89.95 (recommended, including VAT). As we said, it'll be appearing in April...

## No More Surveys!

We've been overwhelmed at the response to the survey in the February issue — the box containing the replies is too heavy to lift — but if you haven't sent yours back yet, please don't bother, as processing will have taken place by the time you read this and it will be too late to count. A special thank you to all the overseas readers who replied, many of whom went to the trouble of posting their forms by airmail.

## Satellite Colloquium

UNISAT-1, Britain's first TV broadcasting and business satellite, is to be the subject of a full day colloquium, organised by the Institution of Electrical Engineers, to be held at the IEE, Savoy Place, London WC2, on Tuesday, 17th May, 1983 (9.15am to 4.45pm). Non-IEE members are very welcome.

Speakers have been invited from BTI, BAe, Marconi, INTLSAT and the BBC. This meeting is designed to have wide appeal and is expected to be very popular. Admission is £17.25 to IEE members, £28.75 to non-members. For further information and booking contact: Karen Kimpton, IEE, Savoy Place, London WC2R 0BL (telephone 01-240 1871 ext. 308).

of an old favourite, the LE40 24 V temperature-controlled iron. LSDI say that they have now incorporated proportional control and that this much improves temperature control without temperature swing or overshoot.

Recently introduced is the SK18 kit which includes an LC18 iron with three bits of different sizes, tweezers, three double-ended soldering tools, desoldering braid and three metres of cored solder. Ordered direct from Light Soldering Developments Limited, 97/99 Gloucester Road, Croydon CR0 2DN, Surrey, the kit will cost you £14.55.

## Drawing The Line Somewhere


AutoCAD is a two-dimensional computer-aided drafting and design package which runs on 8-bit and 16-bit microcomputers under CP/M-80, CP/M-86 or MSDOS/PCDOS. It is a general-purpose package, suitable for a wide variety of applications, including architectural and landscape drawings, mechanical, electrical, chemical, structural, and civil engineering, and printed-circuit design. The AutoCAD package, complete with drivers for all currently-supported devices, is available in the UK from PO Box 100A, Surbiton, Surrey KT5 8HY (01-399

8530) for approximately £630. Special dealer and distributor/OEM prices are also available.

AutoCAD acts like a word-processor for drawings. It lets the user make drawings from simple components such as lines (of any width), circles, arcs, and solid-filled areas. Drawings may be annotated with text of any size, inserted at any point and at any orientation. The drawings can be stored on disc and in turn used as components in other drawings. The ability to define parts libraries simply by drawing them, and to write custom menus (via ordinary text files), allows specialised application systems to be easily developed under AutoCAD. Drawings may be created through keyboard commands, with a light-pen and on-screen menu, or from existing paper drawings via a digitizing

tablet. The large set of editing commands allows drawn objects to be moved, copied, modified, erased, rotated, and scaled vertically and horizontally. Repetitive patterns such as brick walls or memory arrays can be generated automatically. A full bi-directional zoom facility allows working on the drawing at any level of detail.

Drawings can be plotted to any desired scale at any point during the drawing process. Each drawing color may be assigned to a plotter pen and line type. Utilities supplied with the package can convert drawings to or from an ASCII text file. This allows user programs to process information entered in graphic form through AutoCAD, or, conversely, the viewing or editing with AutoCAD of drawings produced by data from user programs. If the quality of these samples is anything to go by (originals were A4-sized), then AutoCAD would be useful in our workshop, let alone a design studio.

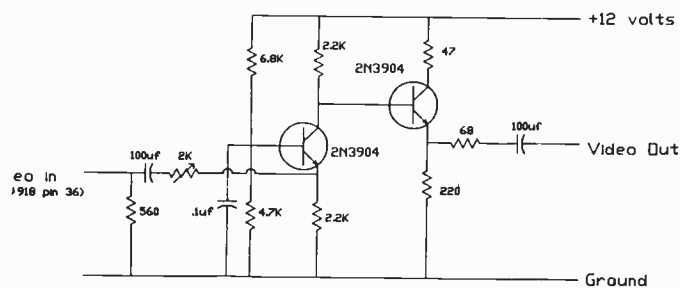

All resistor values in ohms unless marked



(c) 1978 Frank Lloyd Wright Foundation used by permission

## Make Light Of Soldering

Two new products from Light Soldering Developments Limited are aimed at making soldering easier. First is not entirely new, but a modified version



# ELECTRONIC KITS

**ALL NEW**  
to the  
**VELLEMAN**  
**RANGE**


Velleman electronic kits have gained respect for their high quality and the varied range which covers many applications in the vast field of electronics. All kits are designed and developed using the latest technology, giving them appeal, not only to the hobbyist and enthusiast but also to the experienced engineer.

The fully illustrated Velleman Kit Journal is available free of charge upon request and has full technical specification on each kit in the range. All kits are graded by difficulty from 1 to 3 and can be purchased direct or from the stockists listed below.

... and remember, we have a 'rescue service' for instances where enthusiasm exceeds ability!




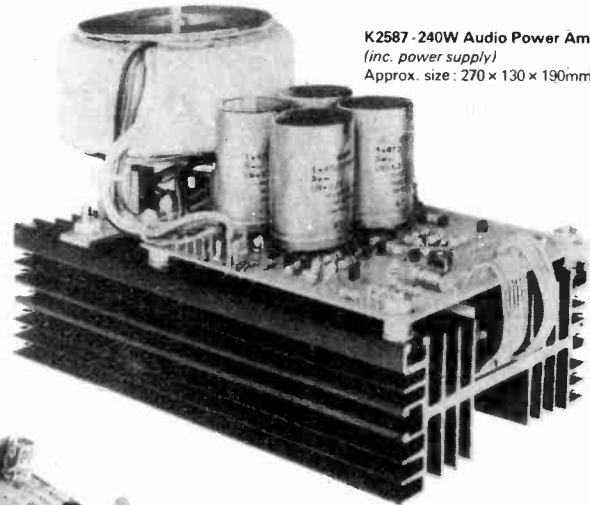**K2584 - Precision timer**  
(timing from 1 sec  
to 99 mins 99 secs.)  
Actual size: 235 x 110mm




**K2587 - 240W Audio Power Amplifier**  
(inc. power supply)  
Approx. size: 270 x 130 x 190mm high

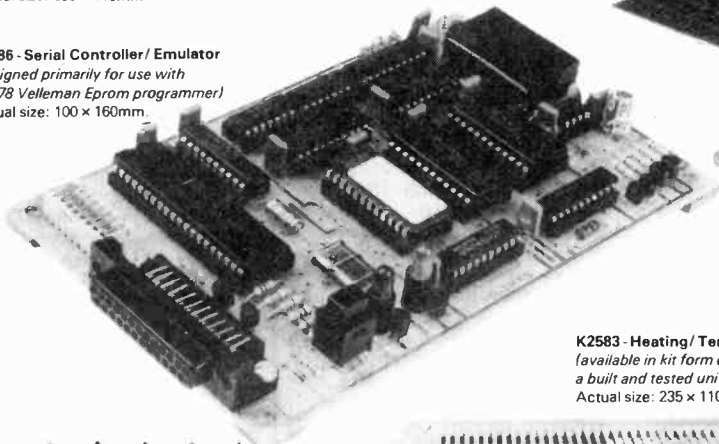**K2586 - Serial Controller/ Emulator**  
(designed primarily for use with  
K2578 Velleman Eprom programmer)  
Actual size: 100 x 160mm.



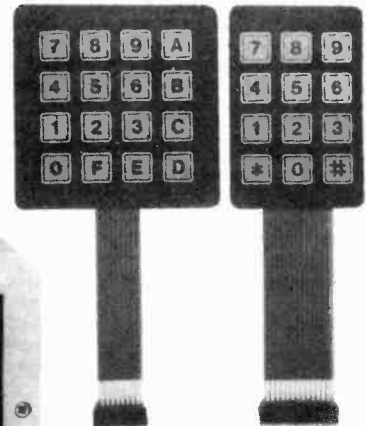
**K2583 - Heating/ Temperature Controller**  
(available in kit form or as  
a built and tested unit)  
Actual size: 235 x 110mm



**KBS16 and KBS12 - Membrane Keypads**  
(available with  
or without legend)  
Actual size:  
65 x 100mm  
100 x 100mm


**OTHER NEW KITS  
recently introduced**

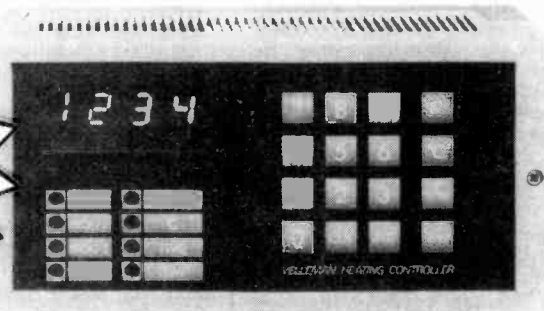- K2580 Electronic powerswitch dimmer
- K2581 Stereo volume and tone control
- K2582 Stereo audio input selector
- K2585 Codeclock
- K2588 3 Channel sound to light unit


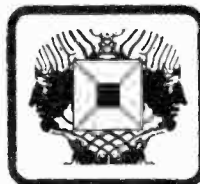
## VELLEMAN UK. Ltd


P.O. Box 30, St. Leonards-on-Sea,  
East Sussex TN37 7NL, England.  
Telephone: (0424) 753246


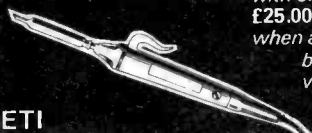
### VELLEMAN STOCKISTS

**Baxol Tele Exports Ltd.**, Ballinacash, Post Rathdrum,  
Co. Wicklow, Rep. of Ireland.  
**Bradley Marshall Ltd.**, 325 Edgware Road, London W2 1BN.  
**S & R Brewster Ltd.**, 86-88 Union Street, Plymouth, Devon.  
**Marshalls Electronics**, 85 West Regent Street, Glasgow, Scotland.  
*Retail outlets are required in most major towns and cities.  
Write for full details, including retail discounts.*

**FREE** SOLDERING IRON  
with orders of  
£25.00 and over  
when accompanied  
by this  
voucher.



ETI

Please send me your free catalogue of Velleman electronic kits:

Name: .....

Address: .....

.....

.....

ETI



## Shorts

● For those of you who know what DIN 41612 is, Enclosure Technology Ltd (Unit G, Southampton Airport, Southampton SO2 2HG) have added a wide selection of these standard edge connectors to their range. (Those who don't know what DIN 41612 is might care to take a look at either the Analogue Board or Real Time Clock projects published in the last couple of ETIs).

● Oops! We gave you the wrong address for BICC-Vero's new catalogue. The address we should have given you is: BICC-Vero Electronics Ltd, Industrial Estate, Chandlers Ford, Hampshire SO5 3ZR. Direct your mail thence, please.

● 3D Digital Design and Development, 18/19 Warren Street, London W1P 5DB inform us that they have introduced an interface card for the BBC micro that makes it possible to connect said machine to their low-cost IN-LAB modular interface system. Cards already existed for using Commodore, Apple, Sharp, Sirius and other micros with the system.

● Use your Apple as a storage 'scope. Details of the Applescope made by RC Electronics Inc., are available from Pete & Pam Computers, New Hall Hey Road, Rossendale, Lancs BB4 6JG.

● A new portable computer is on the way from Texas Instruments. Called the CC-40, it features enhanced BASIC, 6K (expandable to 16K) user RAM, ex-

pansion port, and TI's Hex-bus expansion peripheral port, all for a suggested price of £169.95.

● Digithurst have added a graphics package to their Microsight computer vision systems. They can be found at Leaden Hill, Orwell, Royston, Herts, SG8 5QH, telephone 0223 208926.

● More news from Texas, this time to say that they have been busy with their M<sup>2</sup>C<sup>2</sup>MOS process for gate arrays. The first of a new series of products is the SCX6224 (for which a performance evaluation device is available with data sheet) which is a 2400 gate array with internal gate delay times of 1 nanosecond and input frequency capability of 125 MHz.

● Looking for a modem? Thorn EMI have published a shortform catalogue (that means it ain't got many pages) of their range, claimed to be the largest manufactured in the UK. Thorn EMI Datech Ltd, Spur Road, Feltham, Middlesex TW14 0TD.

● Those people at TI have been busy — there's another new computer, aimed at beginners and called the TI-99/2. Costing around £75, it will feature an elastomeric keyboard (ugh!), 16-bit processor, 4.2K (expandable to 36.2K) user memory and software on solid state cartridges as well as cassettes. TI Ltd, Manton Lane, Bedford MK41 7PA.

● Norbain Electro-Optics are getting into micros — waves, that is, not computers. They will be marketing the Microwave Associates Communications Inc. range of GaAs Gunn oscillators,

transceivers, detectors, and antennae. Norbain Electro-Optics, Norbain House, Boulton Road, Reading, Berkshire RG2 0LT.

● Turn your ZX Spectrum into a word processor using the new Sinclair to Centronics interface that allows you to use high-quality printers. Some software is provided with the device, that comes from Euroelectronics, Zin House, Oakfield Street, Cheltenham, Glos GL50 2UJ.

● Order one for your living room: Control Data's CYBER 205 Series 600 computer is capable of 792 million calculations per second, has eight million 64-bit words of real memory (two trillion words of virtual storage), and models start at the bargain price of a mere £3 million.

● RAM Electro Acoustics Ltd, The Granary, Bracondale, Norwich NR1 2EG have been appointed sole UK agents for the Harksound range of audio turntables.


● 'Good morning campers' will probably not be the way you'll be woken up on one of Southampton University's Computer Holiday Camps. Details from Dr Lionel Wardle, Computer Holidays, 37 University Road, Southampton, SO2 1TL (send a large SAE).

● Salford University is also getting in on the act by organising machine-specific short courses. Details and dates from the Microprocessor Short Courses Unit, Dept. of Electronics and Electrical Engineering, University of Salford, Salford M5 4WT.
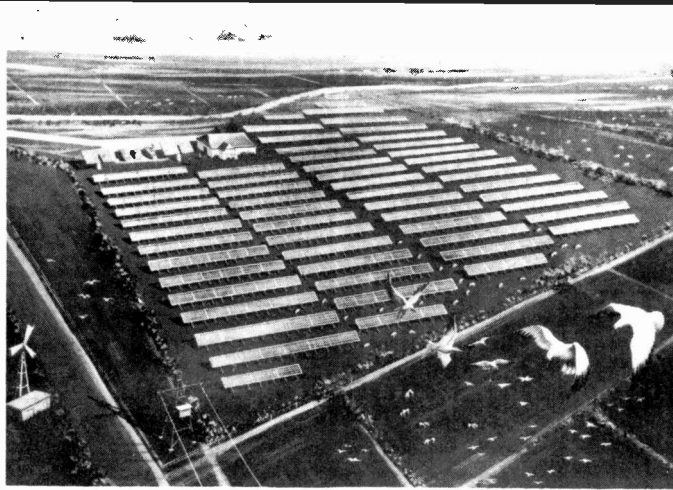
## North Sea Sun


On the West German North Sea island of Pellworm the construction of the largest solar power plant of Europe has started: from July 1983 the sun will provide the recreation centre and surrounding houses with electricity. On an area of 16,000 square metres, (the area needed for two football fields), AEG-Telefunken (West Germany) will build up the 300 kW solar generator which will directly convert the sunlight into electricity. In order to be able to continue to farm the island's valuable grassland the solar generators will be installed on structures with a minimum height of one metre above the ground. This DM 11 million (£3 million) project is financed mainly by the German ministry for research and development and the EEC. During the test phase the plant will provide technical data necessary for planning of future solar power plants up to the MW range. To this end, the economy and low maintenance requirements are very important criteria. Until now the solar experts of AEG-Telefunken have derived their experience mainly from solar plants in countries of the Third World.

As the recreation centre needs most energy in the summertime, it is very well suited for the utilization of solar energy. Battery storage provides the power during the night and during bad weather periods. As there will be more energy available than required by the recreation centre the surplus energy will be fed into the utility grid of the Schleswig. Nowadays the price for one kilowatt-hour "solar energy" is still about DM 2 (55p). The scientists of AEG-Telefunken researching on solar energy at Wedel near Hamburg are confident to cut the cost by building up a mass production between 1986 and 1988. Altogether the EEC is supporting 16 projects on the development of photovoltaic sources of energy. Apart from the complete solar power plant on Pellworm, AEG-Telefunken is building solar generators for a dairy farm in Ireland (50 kW) and for a navigational school on the Netherland island Terschelling (50 kW). It all sounds good, but who gets the job of cleaning off the bird droppings?


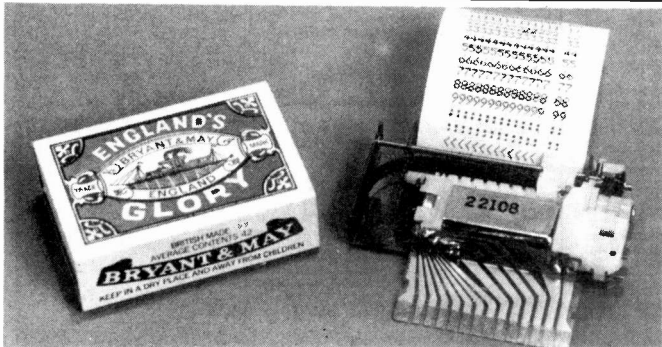
## Pico Print?

Data Limited of Altrincham have recently renewed their agreement to distribute the Epson range of mini-printers which includes the world's smallest thermal printer, the M-30 series. Measuring 60.2 mm wide x 32.9 mm deep x 10.8 mm high and weighing just 30 g, the 16 column M-30 makes it possible to manufacture ultra thin, pocket-size calculators and other hand held devices with a printing function. Also available from Datac is the Epson M-25 13 column model which has a similar specification. For further information on either the M-30 or the M-25 contact Datac Limited, Tudor Road, Altrincham, Cheshire, WA14 5TN. Telephone: 061-941 2361.



## Free File

Forget about catalogues — Elkan Electronics have produced the Elkan File, which contains details of all the items they sell. Sounds rather like a catalogue, doesn't it? The difference is that there are no staples! This is a very cunning move because it means that the contents spread themselves all over your desk making it impossible to ignore them.

Featured in the catalogue, I mean file, are the Nanos quick

reference cards for the ZX80 and the ZX81. It is claimed that the format of a card, as opposed to a book, makes it easier to locate information when you're actually sitting in front of the computer. This does depend on how many cups of coffee you've spilt over them. Cards for other computers are available or in the pipeline from Elkan Electronics, 11 Bury New Road, Prestwich, Manchester M25 6LZ, telephone 061-798 7613 (24 hours). The cards cost £3.50 each, but the file is free.





If undelivered please return to  
Subscription Services  
87 Mortimer Street  
London W1

2 POSTAGE PAID PHQ SERIAL NO 245

A BUSINESS SEMINAR  
YOU CANNOT MISS —

**USING  
TOMORROW'S  
TECHNOLOGY TO  
SOLVE TODAY'S  
BUSINESS PROBLEMS**

PAZOV  
DIRECTOR  
MUDMAGS LTD  
145 CHARITY CROSS ROAD  
LONDON WC2

B

The above envelope was received by us at our offices a few days ago. We don't think further comment is necessary.



## Inductive Loop Amp Tech-Deck

**R**eder Sound Ltd have just introduced their model DL1 Inductive Loop Amplifier. The DL1 is the smallest in their range and is primarily intended for use in the home. It features a current output stage, which ensures a constant current into differing load impedances, internal AGC and inputs for tape recorder/TV or high impedance microphone. The only front panel control is the on/off switch with an indicator LED. The unit is designed to operate in rooms up to 4 metres wide.

The range is completed by the LA2 and LA3 amplifiers. Both feature current output stages, inputs for microphone (low impedance), auxiliary and loudspeaker line (all balanced and floating), internal limiter and full thermal protection. The LA2 is a 30 W 2 A maximum output unit

**T**echnics is expanding its range of cassette decks with the RS-M235X, which has three noise reduction systems. The new cassette deck features Dolby B and C and dbx noise reduction systems, making it compatible with any type of recording and offering excellent sound reproduction. In addition, the RS-M235X offers a built-in dbx disc decoder, increasing its versatility.

and the LA3 is a 60 W 3 A maximum output unit.

Reder Sound also manufacture PA equipment and accessories as well as inductive loop equipment. All inductive loop equipment is designed to be used in accordance with BS 6083 pt4. Reder Sound Ltd are at Premier Works, High Street, Sutton, Ely, Cambridge CB6 2RB (telephone Ely (0353) 777252).

## A Thorn In The Swede

**A** Swedish nuclear power station is to be equipped with the latest British radiation monitoring systems for routine personnel contamination checks under an order worth several million Swedish crowns (sounds much more impressive than £s) placed with Nuclear Enterprises Limited, of Beenham, near Reading.

As the world's most sensitive contamination monitoring system of its type, the Nuclear Enter-

prises IPM7 establishes Britain's leadership in this exacting technology. The system permits highly accurate checks to be carried out extremely rapidly to ensure personnel are free from contamination when leaving control areas. In a matter of seconds, workers' hands, feet and clothing are scanned by banks of electronic detectors inside the IPM7's specially designed 'walk-through' cubicle.

Nuclear Enterprises is a subsidiary of Thorn EMI Technology, one of the major divisions of Thorn EMI's Engineering Group.

## A Code To Bank On

**A**n unbreakable code, which should prove of great interest to banks, businesses and other institutions requiring the confidential transmission of information, has been developed by Professor Adi Shamir of the Weizmann Institute's Department of Applied Mathematics and Dr Ronald L. Rivest and Leonard Adelman of MIT in the States, reports Bank Hapoalim, the leading Israeli bank. The cryptographic system is based on an idea originally suggested by computer scientists Whit Diffie and Martin Hellman of Stanford University in the United States.

The idea was to develop a coding system where different keys would be required for encryption and decryption. In this way, a subscriber could reveal his encryption (encoding) key, so that all users could send him messages, while the decryption (decoding) key would be known only to the receiver, ensuring complete secrecy. The new system uses very large prime numbers. It takes only a fraction of a second for a microcomputer to multiply two 100-digit prime numbers to obtain their 200-digit

product. On the other hand, it would require four billion years to solve the reverse problem: that is, to determine which two 100-digit prime numbers were used to yield a given product.


According to the system, a directory of registered subscribers will supply the public numbers of users. At the other end, the receiver will take the concealed communication and use his secret decryption key to obtain a comprehensible message. Because no prior exchange of secret information is necessary, the system is very convenient for widespread public usage. It also enables the transmission of legally binding 'signatures' to a message, so that contracts, purchase orders and cheques can be exchanged via telex.

With all conventional coding systems, both receiver and sender must possess the same confidential key. The new system, according to Professor Shamir, "is an entirely novel concept of public communication, one which we hope soon to see widely used." A prototype computer chip is now undergoing extensive testing in Boston. For further information contact: Department of Applied Mathematics, Weizmann Institute of Science, Rehovot, Israel.

dbx, the most powerful noise reduction system on the market, yields a signal to noise ratio of 92 dB with 100 dB dynamic range — more than enough to record any live performance, even a jet engine at take off! For simple operation, an auto-tape selector chooses the correct bias and equalisation for the type of tape being used. In addition, a new system of level and balance control features in the RS-M235X. A single master level slider adjusts both channels, while a separate

control balances left and right channels when necessary, permitting smooth fade-in/fade-out effects. Colour-coded, soft touch controls aid easy operation and wide range FL meters indicate signal response.

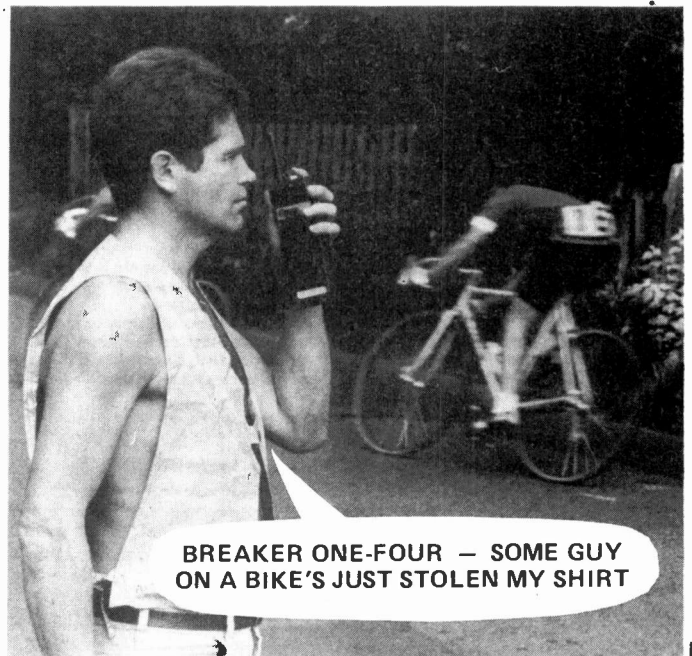Slim in style, the RS-M235X is available in silver or black finish and is designed to co-ordinate with the new range of Technics hi-fi separates. Retailing at £176.95 the RS-M235X can be obtained from the Technics network of authorised dealers.



# BI-PAK BARGAINS

## TRIACS — PLASTIC

4 AMP — 400v — T0202 — TAG 13SD

1 OFF	10 OFF	50 OFF	100 OFF
40p	£3.75	£17.50	£30.00
8 AMP 400v — T0220 — TAG 425			
60p	£5.75	£27.50	£50.00

## SLIDER POTENTIOMETERS

Plastic 40mm Travel Mono

SX63	5 x 470 ohm Lin	SX675	x 47k Log
SX64	5 x 1k Lin	SX685	x 47k Log
SX65	5 x 22k Lin	SX695	100k Log
SX66	5 x 22k Log	SX705	1 meg Lin

**ALL AT 50p PER PAK**

SX40	250 Silicon Diodes—Switching like IN4148 DO-35. All good—uncoded. Worth double our price 45v 75mA	£1.25
SX41	250 Silicon Diodes—General Purpose like OA200/202, BA13/16. Uncoded 30-100v 200mA DO-7	£1.25

## OPTO 7-Segment Displays Brand New 1st Quality LITRONIX DL 707R 14-pin

Red 0.3" Common Anode Display 0-9 with right hand decimal point TTL compatible 5v DC Supply. Data supplied.

5 pieces £3 (60p each)  
10 pieces £5 (50p each)  
IN PACKS 50 pieces £20 (40p each)  
OF 100 pieces £36 (36p each)  
1,000 pieces £300 (30p each)

**THE MORE YOU BUY — THE LESS YOU PAY!**

## BI-PAK'S OPTO 83 SPECIAL

A selection of Large & Small size LED's in Red, Green, Yellow and Clear, plus shaped devices of different types. 7 Segment displays, photo transistors, emitters and detectors. Types like MEL11, FPT100 etc. Plus Cadmium Cell DRP12 and germ. photo transistor OCP71. TOTAL OF 25 PIECES

O/NO. SX57A  
Valued — Normal Retail £12.00  
Our Price **£5.00**

## "IRRESISTABLE RESISTOR BARGAINS"

Pak No.	Qty*	Description	Price
SX10	400	Mixed "All Type" Resistors	£1
SX11	400	Pre-formed 1/4-watt Carbon Resistors	£1
SX12	200	1/4 watt Carbon Resistors	£1
SX13	200	1/4 watt Carbon Resistors	£1
SX14	150	1/4 watt Resistors 22 ohm-2m2 Mixed	£1
SX15	100	1 and 2 watt Resistors 22 ohm-2m2 Mixed	£1

Paks SX12-15 contain a range of Carbon Film Resistors of assorted values from 22 ohms to 2.2 meg. Save pounds on these resistor paks and have a full range to cover your projects.  
\*Quantities approximate, count by weight.

## GUARANTEED TO SAVE YOU MONEY

SX27A	60 Assorted Polystyrene Bead Capacitors Type 9500 Series PPD	£1.00
SX28A	50 Assorted Silver Mica Caps 5.6pF-150pF	£1.00
SX29A	50 Assorted Silver Mica Caps 180pF-4700pF	£1.00
SX30A	50 High Voltage Disc Capacitors 750V min up to 8KV Assorted useful values	£1.00
SX31A	50 Wirewound 9 watt (Arg) Resistors. Assorted values 1 ohm-12K	£1.00

**AUTO SCREWDRIVER/DRILL**  
Automatic spiral ratchet. Complete with 2 screwdriver blades, 5 & 6.5mm, 1 screwdriver cross point No. 1 & three drills — 2, 2.8 and 3.65mm — A MUST FOR ALL HOBBY-BUILDERS & CONSTRUCTORS. Order No. ASD/1 £3.50 each.

## "CAPABLE CAPACITOR PAKS"

Pak No.	Qty*	Description	Price
SX16	250	Capacitors Mixed Types	£1
SX17	200	Ceramic Capacitors Miniature Mixed	£1
SX18	100	Mixed Ceramics 1pF-56pF	£1
SX19	100	Mixed Ceramics 60pF-0.5mF	£1
SX20	100	Assorted Polyester/Polystyrene Capacitors	£1
SX21	60	Mixed C280 type capacitors metal foil	£1
SX22	100	Electrolytics, all sorts	£1
SX23	50	Quality Electrolytics 50-10000µF	£1
SX24	20	Tantalum Beads, mixed	£1

\*Quantities approximate, count by weight.

## IC SOCKETS The lowest price ever.

The more you buy the cheaper they come!

Pin	10 off	50 off	100 off
8 pin	85p	£3.50	£8.00
14pin	95p	£3.75	£8.50
16 pin	95p	£4.00	£7.00
28 pin	£2.50	£11.00	£20.00



## VOLTAGE REGULATORS T0220

Positive +	Negative +
7805 — 50p	7905 — 55p
7812 — 50p	7912 — 55p
7815 — 50p	7915 — 55p
7824 — 50p	7924 — 55p

## BARGAINS


SX91	20 x Large 2" RED LED	£1
SX42	20 small 125 Red LED's	£1
SX43	10 Rectangular Green LED's 2	£1
SX46	30 Assorted Zener Diodes 250mV-2 watt mixed voltages, all coded. New	£1
SX47	4 Black Instrument Knobs—winged with pointer 1/4" Standard screw Fit size 29 x 20mm.	50p
SX49	20 Assorted Slider Knobs. Black/Chrome, etc.	£1
SX80	12 Neons and Filament Lamps. Low voltage and mains — various types and colours — some panel mounting	£1

## SILICON BRIDGE RECTIFIERS

Comprising 4 x 1 1/2 amp rectifiers mounted on PCB.

VRM — 150 volts  
IFM — 1.5 Amps

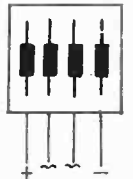Size: 1 inch square  
10 off £1.00  
50 off £4.50  
100 off £7.50



Order No. AS: 4RI  
BRect.

## 1 Amp SILICON RECTIFIERS

Glass Type similar IN4000 SERIES IN4001-IN4004 50 — 500v — uncod. J — you select for VLTS ALL perfect devices — NO dud's Min 50v. 50 for £1.00 — worth double ORDER NO SX76

Silicon General Purpose NPN Transistors TO-18 Case Lock lit leads — coded CV7644 Similar to BC147 — BC107 — ZT89 ALL NEW! VCE 70v IC500mA Hfe 75-250 50 off 100 off 500 off 1000 off	PRICE £2.00 £3.80 £17.50 £30.00
--	---------------------------------

Silicon General Purpose PNP Transistors TO-18 Case Lock lit leads coded CV9507 similar ZN2905A to BFX30 VC 60 IC 600mA Min Hfe 50 ALL NEW! 50 off 100 off 500 off 1000 off	PRICE £2.50 £4.00 £19.00 £35.00
--	---------------------------------

Order as CV7644

Order as CV9507



SX52 6 Black Heatsink will fit TO-3 and TO-220 Ready drilled. Half price value. £1

SX53 1 Power Finned Heatsink. This heatsink gives the greatest possible heat dissipation in the smallest space owing to its unique staggered fin design. pre drilled. TO-3 Size 45mm square x 20mm high 40p

SX54 TO-66 size 35mm x 30mm x 12mm 35p  
SX55 1 Heat Efficient Power Finned Heatsink 90mm x 80mm x 35mm High. Drilled to take up to 4 x TO-3 devices £1.50 each



## SINGLE SIDED FIBREGLASS BOARD

Order No.	Pieces	Size	Sq. Ins.	Price
FBI1	4	9 x 2 1/2"	100	£1.50
FBI2	3	11 x 3"	100	£1.50
FBI3	4	13 x 3"	156	£2.00

## DOUBLE SIDED FIBREGLASS BOARD

FBI4	2	14 x 4"	110	£2.00
------	---	---------	-----	-------

## SILICON POWER TRANSISTORS — T03

NPN like 2N3055 — but not full spec 100 watts 50V min. 10 for £1.50 — Very Good Value 100s of uses — no dud's Order No. SX90

## SEMICONDUCTORS FROM AROUND THE WORLD

100 A Collection of Transistors, Diodes, Rectifiers, Bridges, SCR's, Triacs, IC's both Logic and Linear plus Opto's all of which are current everyday usable devices

Guaranteed Value over £10 at Normal Retail Price


**£4.00** Data etc. in every pak. Order No. SX56


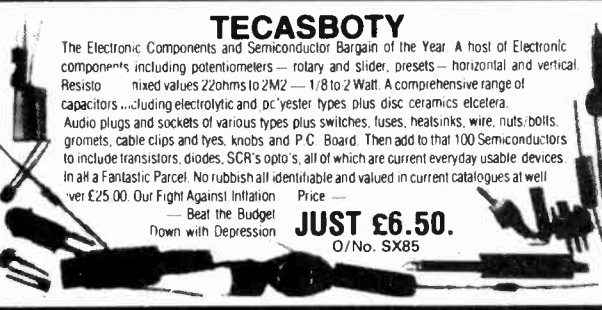
## TECASBOTY

The Electronic Components and Semiconductor Bargain of the Year. A host of Electronic components including potentiometers — rotary and slider, presets — horizontal and vertical. Resisto mixed values 22ohms to 2M2 — 1/8 to 2 Watt. A comprehensive range of capacitors including electrolytic and polyester types plus disc ceramics etcetera. Audio plugs and sockets of various types plus switches, fuses, heatsinks, wire, nuts, bolts, gromets, cable clips and ties, knobs and P.C. Board. Then add to that 100 Semiconductors to include transistors, diodes, SCR's opto's, all of which are current everyday usable devices in all a Fantastic Parcel. No rubbish all identifiable and valued in current catalogues as well

ver £25.00. Our Fight Against Inflation — Beat the Budget Down with Depression **JUST £6.50.** O/No. SX85



## PROGRAMMABLE UNIUNCTION TRANSISTOR

"PUT" case TO106 plastic MEU22 Similar to 2N6027/6028 PNP Silicon Price: 1-9 10-49 50-99 100+ Normal Retail Price £0.35 each

SX33A	6 small (min) SDST/SPDT Toggle Switches 240v 5amp	£1.00
SX35A	8 Rocker Switches 250v 2A	£1.00
SX32A	12 Assorted Jack & Phono plugs, sockets and adaptors, 2.5m, 3.5mm and standard sizes	£1.00
SX71	50 BC108 "Fallouts" Manufacturers out of spec on volts or gain You test.	£1.00
SX72	A mixed bundle of Copper clad Board Fibre glass and paper. Single and double sided. A fantastic bargain	£1.00

SX38	100 Silicon NPN Transistors—all perfect Coded mixed types with data and eqvt sheet. No rejects. Real value.	£3.00
SX39	100 Silicon PNP Transistors—all perfect. Coded mixed types with data and eqvt. sheet. No rejects. Fantastic value.	£3.00

2N3055 The best known Power Transistors in the World — 2N3055 NPN 115w. Our BI-PAK Special Offer Price: 10 off 50 off 100 off £3.50 £16.00 £30.00

BD312 COMPLIMENTARY PNP POWER TRANSISTORS: TO 2N3055. Equivalent MJ2955 — BD312 — T03 SPECIAL PRICE £0.70 each 10 off £6.50



## REGULATED VARIABLE Stabilised POWER SUPPLY

Variable from 2.30 volts and 0.2 Amps. Kit includes — 1 — VPS30 Module, 1 — 25 volt 2 amp transformer, 1 — 0.50v 2" Panel Meter, 1 — 0.2 amp 2" Panel Meter, 1 — 470 ohm wirewound potentiometer, 1 — 4K7 ohm wirewound potentiometer. Wiring Diagram included Order No. VPS30 KIT £20

**MINIATURE FM TRANSMITTER**  
Freq. 95-106MHz. Range: 1/4 mile  
Size: 45 x 20mm. Acc: 5v batt.  
Not licenced in U.K. ONLY £5.50  
Ideal for: 007-M15-FBI-CIA-KGB etc.



## MORE BARGAINS!

SX151	60 metres PVC covered Hook-up wire single and stranded. Mixed colours	£1
'SX58	25 Assorted TTL Gates 7400 Series. 7401-7460	£1
SX59	10 Assorted flip Flops and MSI TTL	£1
SX60	20 Assorted Slider Potentiometers	£1
SX62	40 Assorted Pre-Sets Hor/Vert etc.	£1
SX79	10 Reed Switches — glass type 3 Micro Switches — with lever	£1

# BI-PAK

Send your orders to Dept. HE4, BI-PAK PO BOX 6 WARE HERTS  
SHOP AT 3 BALDOCK ST., WARE, HERTS.  
TERMS: CASH WITH ORDER. SAME DAY DESPATCH. ACCESS.  
BARCLAYCARD ALSO ACCEPTED. TEL (0920) 3182. GIRO 388 7006  
Add 15% VAT AND 50p PER ORDER POSTAGE AND PACKING



Use your credit card. Ring us on Ware 3182 NOW and get your order even faster. Goods normally sent 2nd Class Mail.  
Remember you must add VAT at 15% to your order Total. Postage add 75p per total order.



# COMTECH ELECTRONICS

TRANSISTORS		BCY70		2N2222A		20p		LINEAR ICs		LEDs		IC SOCKETS		THIS MONTH'S SPECIAL OFFER WITH ALL ORDERS OVER £6 - A FREE, YES FREE!																					
BC107B	12p	BCY71	18p	2N2368	23p	555	15p	3mm RED	6p	8 pin	7p	YOU MAY DEDUCT 10% FOR ORDERS OVER £25																							
BC108C	12p	BD115	50p	2N2484	24p	556	43p	5mm RED	7p	14 pin	8p					HOW DO WE DO IT? WE SEARCH FOR THE LOWEST BULK PRICE AND THEN WE SELL THEM TO YOU AT GENUINE LOW PRICES (PROBABLY SOME OF THE LOWEST EVER)																			
BC109C	13p	BD131	47p	2N2904	20p	741	50p	3mm GREEN	9p	16 pin	9p	SPECIAL OFFERS																							
BC113.4	17p	BD132	47p	2N2904A	22p	747CN *	58p	5mm GREEN	10p	18 pin	11p					BC237	8p	78H05	530p																
BC115.6	18p	BD135	32p	2N2905	23p	748C	35p	3mm Y/LOW	10p	20 pin	14p	BC477	20p	C106D	24p																				
BC119 *	32p	BD136	32p	2N2905A	25p	CA3089	180p	5mm GREEN	11p	22 pin	14p	BC559C	5p	C206D	50p																				
BC139 *	30p	BD137	30p	2N2906	22p	CA3189	280p	Clips	2p	24 pin	16p	BD204	50p	C226D	60p																				
BC140	26p	BD138	35p	2N2906A	22p	ICM7556	150p	Rectangular	2p	28 pin	18p	BD206	50p	LF387N	95p																				
BC141	28p	BD139	35p	2N2907	23p	LF351 *	45p	Red	10p	40 pin	20p	TIP29C	30p	358N	45p																				
BC142/3	27p	BD140 *	35p	2N3053 *	23p	LF353 *	80p	Green	14p	***COMPONENT PACKS*** SUPER LOW PRICES***																									
BC161	42p	BD204	40p	2N3054	56p	LF355 *	85p	Yellow	15p							CP1 30 IC sockets, 8, 14, 16 pin (10 of each)	£2.20	CP2 20 BC182/BC122 Transistors (10 of each)	£1.25	CP3 20 BC549/BC559 Transistors (10 of each)	£1.25	CP4 6 2N2222 NPN Transistors	£1.00	CP5 6 2N2906 PNP Transistors	£1.10	CP6 6 2N2905A Transistors	£1.00								
BC169C *	9p	BD206 *	75p	2N3055	54p	LM301A	24p	AA119	9p	CP7 100 N814 Diodes	£2.40	CP8 100 N815 Diodes	£3.00	CP9 100 N8148	£1.50	CP10 100 N8148	£1.00	CP11 10 MC1458 (Dual Op. Amp.)	£3.00	CP12 20 BAX13 Diodes	£3.00	CP13 50 400mV Zeners, 2 each of 2V7-33V	£2.00	CP14 50 1.3W Zeners, 2 each of 4V7-51V	£4.00	CP15 50 Mixed Electrolytic capacitors (10, 16, 25 and 50V Radial, 1uF to 1000uF)	£3.80	CP16 4 LF351 JFET Op. Amps	£1.70	CP17 4 LF353 JFET Op. Amps	£3.00	CP18 50 Mixed LEDs	£4.00	CP19 50 Mixed resistors	£2.50
BC171B	9p	BD222	60p	2N3441	120p	LM301A	24p	AA119	9p	CP20 100 1W, 1% Metal Film resistors	£2.50	ORDERING: All components top quality and full spec. Please add 30p P&P to orders under £5. VAT to be added to total please. Send cheque or postal order: made payable to Comtech Electronics.																							
BC172C	9p	BFX29	28p	2N3442	125p	LM301A	24p	AA119	9p	RESISTORS																									
BC173C	9p	BFX84	27p	2N3702	9p	LM311	60p	AA119	9p					1W 5% Carbon film E24 series	10 ohm-1M ohm 2p each.	METAL FILM	1W 1% E24 series	10 ohm-1M ohm 4p each.	SEND S.A.E. FOR FREE PRICE LIST																
BC177B	16p	BFX87	27p	2N3703	9p	LM324	40p	AA119	9p	10 ohm-1M ohm 1p each.																									
BC178C	16p	BFX88 *	23p	2N3704	9p	LM339	47p	AA119	9p	10 ohm-1M ohm 1p each.																									
BC179C *	17p	3FY50	24p	2N3706	9p	LM348	60p	AA119	9p	10 ohm-1M ohm 2p each.																									
BC182B	9p	3FY51	24p	2N3707	9p	LM358	50p	AA119	9p																										
BC183B/C	9p	3FY52	23p	2N3708	9p	LM380	68p	AA119	9p																										
BC184B/C	9p	3FY53	30p	2N3711 *	170p	LM382	115p	AA119	9p																										
BC212B	9p	3SV95A	22p	2N3712 *	175p	LM384	125p	AA119	9p																										
BC213B/C	9p	SU205	150p	2N3713 *	195p	LM386	65p	AA119	9p																										
BC214B/C	9p	BZ026 *	170p	2N3819	20p	LM393	72p	AA119	9p																										
BC237B	10p	SU208	155p	2N3903	10p	LM393	72p	AA119	9p																										
BC238B/C	10p	MJE340	48p	2N3904	10p	LM711 *	14p	AA119	9p																										
BC239B/C	10p	MJE520	65p	2N3906	10p	LM741	14p	AA119	9p																										
BC251	10p	MJE521	70p	2N4037	40p	LM748	58p	AA119	9p																										
BC257/8	14p	MJE2355	80p	2N4058 *	9p	LM1458	38p	AA119	9p																										
BC259	16p	MJE3055	65p	2N4061/2	10p	LM3900	47p	AA119	9p																										
BC301/2	40p	MPSA05	20p	2N4547	28p	MC1455	16p	AA119	9p																										
BC303/4	40p	MPSA06	20p	2N4548	27p	MC1458	33p	AA119	9p																										
BC307A/B	10p	MPSA12	24p	2N4549	24p	MC1748	35p	AA119	9p																										
BC308B/C	10p	MPSA13	24p	2N4550	23p	MC3302 *	72p	AA119	9p																										
BC309B/C	10p	MPSA55	22p	2N6027	20p	RC4558	44p	AA119	9p																										
BC327 *	12p	MPSA56	22p	2N6028	23p	SN76115	125p	AA119	9p																										
BC328	12p	TIP29A/B	30p	BRIDGE RECTIFIERS		SN76660	110p	AA119	9p																										
BC337 *	12p	TIP29C	34p	1.5 Amp		TDA1024	130p	AA119	9p																										
BC338	12p	TIP30A/B	30p	W005 *	18p	TDAX2002 *	38p	AA119	9p																										
BC384	15p	TIP30C	36p	W01	20p	TDAX2030	200p	AA119	9p																										
BC413C	10p	TIP31A/B	33p	W02	22p	400mW	6p	AA119	9p																										
BC414C	10p	TIP32A/B	33p	W03	20p	2V7-36V	5p	AA119	9p																										
BC415C	10p	TIP41A	42p	W04	24p	1.3V	5p	AA119	9p																										
BC416C	10p	TIP42A	45p	W05	22p	3V3-47V	12p	AA119	9p																										
BC477	25p	TIP3055	59p	W06	28p	SEMs		AA119	9p																										
BC478 *	25p	TIS43	30p	W07	30p	C106D	35p	AA119	9p																										
BC479	25p	TIS44	30p	W08	32p	C116D	70p	AA119	9p																										
BC484	10p	TIS45	30p	W09	30p	C126D	95p	AA119	9p																										
BC485	10p	TIS91	24p	W10	30p			AA119	9p																										
BC486	9p	TIS92 *	24p	W11	30p			AA119	9p																										
BC487	9p	2N1613	30p	W12	30p			AA119	9p																										
BC496	10p	2N2218A	25p	W13	30p			AA119	9p																										
BC557B	9p	2N2219A	25p	W14	30p			AA119	9p																										
BC558B	9p	2N2221A	24p	W15	30p			AA119	9p																										
BC559C *	9p	2N2222 *	18p	W16	30p			AA119	9p																										

**Comtech Electronics**

**MAIL ORDERS**

205 STURDEE ROAD,  
LEICESTER LE2 9FY  
Telephone (0533) 779578

**SUPER LOW PRICES!**

## GIANT OPENING SALE

All items full spec guaranteed and made by well-known manufacturers

TRANSISTORS		BC213L		BF197		2N698		4001B		7407		LS75		LM308N-8		ML922	
AC127	10p	BC213L	6p	BF197	8p	2N706	7p	4006B	30p	7408	10p	74123	30p	LM376	15p	ML928	100p
AC128	12p	BC214	6p	BF198	8p	2N914	10p	4007	8p	7409	7p	74125	25p	LM378	13p	ML928	300p
AC141	15p	BC214L	6p	BF200	15p	2N918	11p	4008	25p	7410	8p	74126	25p	LM386	15p	ML928	100p
AC142	7p	BC237	6p	BF244C	13p	2N1131	6p	4009	15p	7412	8p	74132	28p	LM390	18p	ML928	130p
AC153	18p	BC238	4p	BF257	11p	2N1132	6p	4010B	20p	7413	13p	74141	35p	LM380	55p	ML928	100p
AC176	15p	BC261B	5p	BF258	17p	2N1304	12p	4011B	9p	7416	10p	74145	30p	LM381N	80p	ML928	50p
AC187	10p	BC478	5p	BF259	10p	2N1306	16p	4012	8p	7417	10p	74147	85p	LM382N	70p	TBA641BX1	150p
AC188	12p	BC301	20p	BF339	10p	2N1308	20p	4013B	15p	7420	8p	74150	45p	LM1458N	30p	TBA651	100p
AD149	40p	BC328	5p	BF341	15p	2N2217	15p	4014	35p	7421	15p	74151	30p	LM1458N	35p	TBA800	60p
AF118	23p	BC477	15p	BFX29	25p	2N2222A	10p	4016	14p	7423	15p	74153	30p	LM13915	200p	TD1004	250p
AF124	30p	BC547	5p	BFX86	15p	2N2369	10p	4020B	35p	7425	15p	74156	20p	LM13600	95p		
AF125	30p	BC549	7p	BFX87	15p	2N2484	10p	4021	30p	7427	12p	74157	25p	MC1310N	65p		
AF139	20p	BC557	5p	BFX88	22p	2N2904	10p	4022	25p	7428	12p	74161	24p	MC1495L	350p	TDA1008	250p
AF186	40p	BC558	5p	BFY50	13p	2N2906	10p	4023	8p	7432	12p	74162	26p	MC1495L	350p	UAA170	80p
AS54	10p	BC559	10p	BFY52	15p	2N2907	10p	4025	8p	7433	10p	74163	35p	MC1496P	60p	ZN424E	120p
AS555	10p	BCY30	40p	BFY53	8p	2N2926G	8p	4027	15p	7437	10p	74164	35p	MK50398	400p		
BC107	6p	BCY34	40p	BU205	180p	2N3053	15p	4028	30p	7438	8p	74165	35p				
BC108	6p	BCY59	12p	BU208	115p	2N3055	32p	4030	9p	7440	8p	74167	45p				
BC109C	6p	BCY70	10p	MJ2955	65p	2N3702	5p	4035	40p	7441	45p	74173	35p				
BC117	8p	BCY71	18p	MPF104	20p	2N3703	5p	4041	35p	7442	20p	74174	40p				
BC119	10p	BCY72	10p	MPF105	20p	2N3705	5p	4043	30p	7443	30p	74175	20p				
BC142	20p	BD115	15p	MPF106	20p	2N3708	5p	4044	28p	7444	35p	74177	30p				
BC143	20p	BD121	30p	OC28	40p	2N3707	5p	4044	28p	7445	30p	74180	23p				
BC147	5p	BD123	30p	TIP29B	20p	2N3708	5p	4048	30p	7446	5p	74181	80p				

The power supply can make the difference between an adequate amplifier and a great one. In this article, J. Linsley Hood explains the advantages of a stabilised PSU, and concludes with a simple and novel circuit to upgrade your hi-fi.

# STABILISED HI~FI PSU

If you look inside the boxes of some of the top name hi-fi power amplifiers — the ones that get the rave reviews from the 'golden-eared' fraternity — you will find, more often than not, that the power supply units are stabilised, rather than being of the simple transformer, rectifier, reservoir capacitor variety. The reason for this is twofold. First, the presence of a stabilised PSU is an indication of the rather greater care that has gone into the building of these amplifiers, and if you aim at the top, as a hi-fi manufacturer, this is a necessary part of your philosophy; and second, because the stabilised PSU really does confer some valuable advantages in the operation of the equipment. Let us look at some of these.

The amount of power one can get from a power amplifier, for any given load impedance, increases rapidly as the DC power line voltage is increased. However, so does the cost of the output power transistors (in fact, all the transistors), as well as the capacitors used in the design. As an aside, the fact that 50 V capacitors cost a lot less than half that of the equivalent 100 V ones is the main reason for the popularity among the high power amplifier manufacturers of direct coupled (two power supply lines of half the voltage) output stages. If Joe Public thinks that they also sound better, so be it!

Unfortunately, the realities of

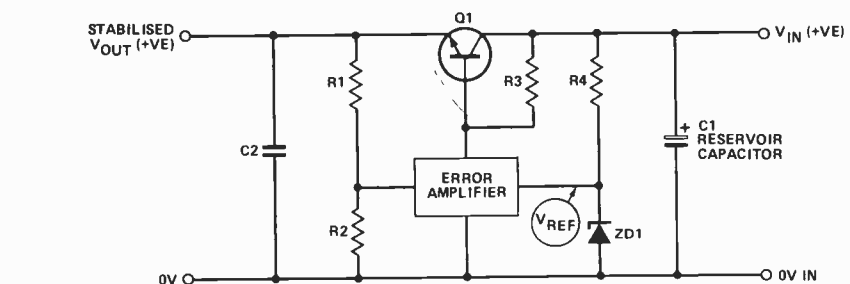


Fig. 1 Simple stabilised power supply.

life are not on our side. From the point of view of the power output, what is important is the actual supply line voltage at maximum load, but what the transistors have to support is the worst case condition of line voltage off-load, and the on-load voltage will always be a good bit less than this. If, on the other hand, one has a constant DC supply, one only needs to make sure that the transistors and capacitors will stand this, and this will also be the voltage available when one is driving to full power.

Just doing a cost assessment of stabilised versus cheap-and-cheerful gives a small overall cost advantage in favour of the simple system, which is why it is more commonly used. However, the stabilised PSU has other, more subtle, advantages which are of value to the discriminating user. These are those which follow from the low ripple level on the supply line of any properly designed stabiliser circuit, and its low supply line impedance. The first of these ensures that hum breakthrough is eliminated, not just at low power levels, which is easy, but also at high powers, when the voltage ripple on the reservoir capacitor is becoming significant. The second feature, that of the low line impedance, not only gives a

lower degree of LF breakthrough from one channel to another (at frequencies where the impedance of the reservoir capacitors is significant) but also gives a more firm and solid bass response. In fact, in my view, this is a more important contribution to the firmness of bass response than the absence of an output coupling capacitor in a 'direct coupled' system.

So, having reviewed the propaganda in favour of the use of constant, stabilised power supply lines two questions remain: can one upgrade an existing amplifier this way, and how simply could one be built? The answer to the first question is almost certainly 'yes' provided that one uses some care. The second I propose to explore. Since this will be done by starting with a basic circuit and adding components, the usual practice of numbering components from left to right and top to bottom will not be followed, so as to achieve continuity from figure to figure.

## The Stabilised PSU

These are normally designed along the lines shown in Fig. 1. In this a 'pass' transistor (Q1) is connected as an emitter follower



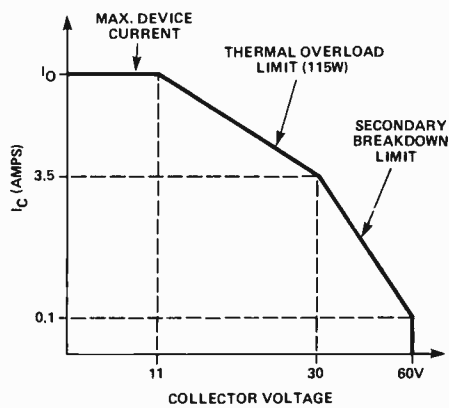


Fig. 2 Power transistor limiting values.

between the unstabilised DC input and the required stabilised DC output. The base drive current to this pass transistor is controlled by some form of error amplifier which compares some proportion of the output DC voltage with a reference voltage derived, perhaps, from a zener diode (ZD1) supplied through R4. Depending on the zener voltage, the controlled DC output can be adjusted, within the limits set by the DC input and the reference voltage, by a suitable choice of R1 and R2. A small capacitor is usually connected across the output to make sure that the output impedance remains low at HF.

This is a very good circuit arrangement, and is used in a very wide range of designs. Indeed, with a little more internal craftiness, very similar systems are employed in the 'three terminal' IC voltage regulators one can now buy for around fifty pence. However, there are snags.

In the case of the IC voltage regulators the main snags are that they are usually limited to input voltages less than 50 V, that the maximum output voltages are usually less than 35 V and that at these voltages the available output

currents will probably be less than 0.5 amps, which is rather too low to be of much use for audio power amplifiers. Nevertheless, where these can be used, they are the best possible solution in terms of performance in relation to cost.

In the case of DIY units of this kind built up from discrete components, though higher voltage and current operation can be organised, the most immediate problem is that of the 'safe operating area rating' or SOAR as shown in Fig. 2. This graph, which is that for a typical power transistor of the 2N3055 type, shows that there are limits on the permissible conditions of operation, and that, as a general rule, you cannot allow the transistor to pass much current at voltages above some 30 V without it blowing up, due to what is known as 'secondary breakdown'. (This arises because silicon diodes have a forward voltage which decreases as they get hotter. So, if enough current, at enough voltage, flows through the transistor the resultant heating will inevitably cause some localised area of the base-emitter 'diode' to get hotter than the remainder, and then all the transistor current will plough through this small area, with expensive and inconvenient results!)

Two ways of safeguarding against this snag are possible. The first (and simpler, if the amount of current needed is less than that permissible at the given input voltage  $V_{in}$ ), is simply to include a current limit circuit as shown in Fig. 3.

In this, Q2 is added, with R5. If the output current taken exceeds the amount needed for the voltage drop across R5 to turn on Q2, then this will 'steal' the base current from Q1 and hold the output current to the chosen limiting value.

However, circumstances often arise where this simple answer just isn't good enough, and then it is necessary to organise a rather more cunning scheme, known as 're-entrant' short-circuit protection. In this, the protection circuit is arranged so that the full, but limited, output current is allowable up to some prearranged voltage drop across the pass transistor Q1, which is known to be within safe operating limits. If the voltage across the pass transistor exceeds this value, some supplementary circuit comes into operation to instantaneously limit the current through the transistor to some lesser value appropriate to its new collector-emitter voltage drop.

This type of arrangement is a much better scheme, and allows stabilised PSUs to be built which will give quite large current outputs at the sort of voltages which would be of use in audio amplifier systems. Moreover, the fact that the output voltage and current will both collapse rapidly in the event of an overload can allow a good measure of protection, if the limit levels are set correctly, for both the amplifier itself and also things like loudspeakers used with it.

Of course, the usefulness of a stabilised power supply is not limited to improving audio amps. This was just one of the possible uses which might appeal to the hi-fi enthusiast in pursuit of an economical and sensible route to a rather higher-fi. Also, as it happens, it is an ingredient I have in mind for a future audio amplifier design for ETI, since I don't think that perfection in this field has yet been reached, or that the last word in cost effectiveness has yet been spoken.

## An Improved PSU

So — we want a simple PSU

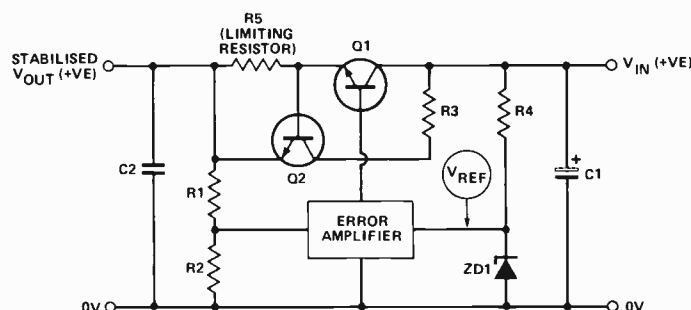


Fig. 3 A stabilised power supply with current limiter.

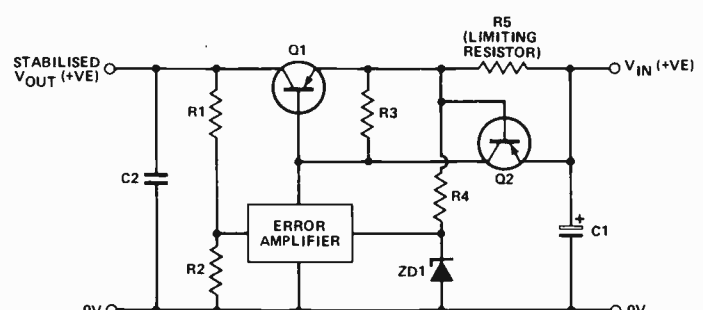


Fig. 4 An alternative arrangement to Fig. 3.

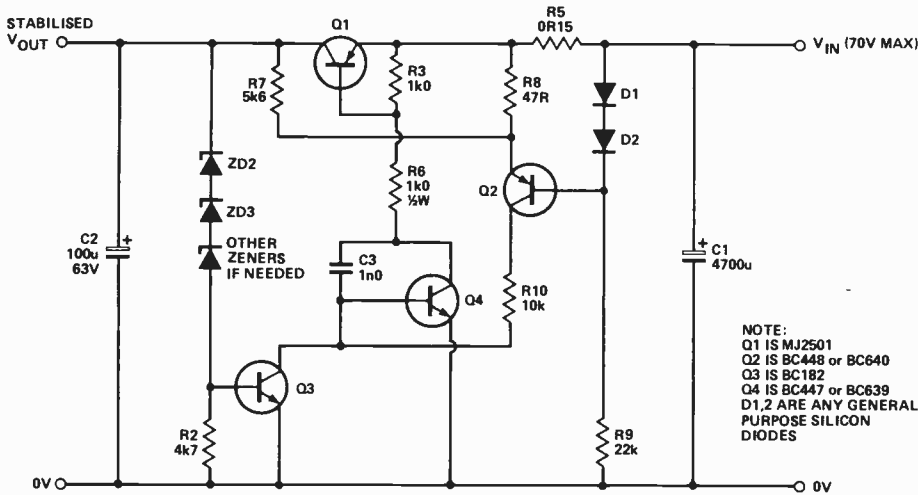


Fig. 5 A stabilised power supply unit with re-entrant short-circuit protection.

system, with an adequate degree of voltage stabilisation, and a re-entrant overload limit characteristic. How best can this be done?

The general scheme shown in Figs. 1 and 3 has several inherent snags, in spite of its popularity in the PSU circuit league. Of these snags, the first is that there must be a sufficient difference in voltage between  $V_{IN}$  and  $V_{OUT}$  for Q1 to be functional, and for an adequate current to flow through R3 to give the necessary output maximum current, with the lowest likely current gain in Q1. This would lead, say, in a 3 amp PSU to a value of R3 being chosen which would pass 100 mA at a 10 V input/output voltage drop. If we now have an input voltage of, say, 60 V, then when Q1 isn't asking for the full base bias current — as, for example, when the PSU was off load — the error amplifier will have to dissipate  $60 - 10 \text{ V} \times 100 \text{ mA} = 5 \text{ W}$ , with a further 1 W being dissipated in R3.

If, however, we turn Q1 the other way round, as in Fig. 4, then the base bias current can be supplied from the '0 V' line, which will mean that the minimum necessary voltage drop between  $V_{IN}$  and  $V_{OUT}$  can be reduced to, say, 3 V, which will reduce Q1's dissipation. Also, only as much current is fed into Q1's base as the output current calls for. This greatly reduces the quiescent dissipation in the error amp circuitry as well. Of course, we would then have to put the current limit transistor on the input side, if we were going to use the same kind of limiting system. We can, however, do a bit better than this — using the final circuitry

in Fig. 5.

In this circuit, I have shown a two-transistor error amplifier (Q3 and Q4) which uses the 0 V line as its voltage reference, allowing us to delete the reference voltage circuit R4 and ZD1. In this circuit, Q4 is turned on by current flowing into its base through R8, Q2 and R10. This causes an amplified current to flow in Q4's collector circuit and turn on Q1. However, when the output voltage rises to a high enough level, the zener diodes ZD2 and ZD3 conduct and start feeding base current into Q3. This promptly gobbles up the current that was previously flowing into the base of Q4 and prevents the voltage from rising further.

The use of one or more zener diodes in a chain to provide the necessary output voltage — the actual output controlled voltage will be about 0V5 greater than the sum of the zener voltages — gives a simple system if one specific output voltage is required. However, zener

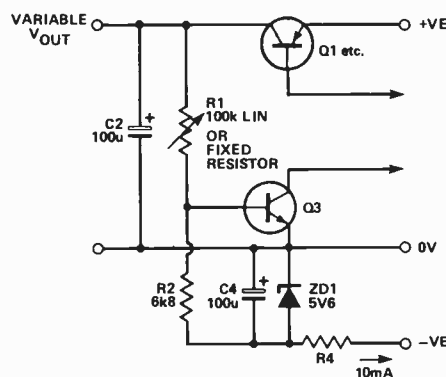


Fig. 6 This modification to the circuit of Fig. 5 allows a variable output voltage.

diodes are a bit noisy (especially if their individual breakdown voltages are high, which makes it preferable to use several lower voltage units in a string), so it may be advantageous to use the modified system shown in Fig. 6, if a convenient negative line is available, which would then allow the output voltage to be adjusted between 0V5 and some 3 V less than the available voltage.

Since the total amount of gain in the feedback circuit consisting of Q1, Q3 and Q4 is quite high, it is necessary to incorporate some HF stabilising element. In this case this function is performed by C3. The other part of the circuit, that of the 're-entrant' short circuit protection and current limiting action, is performed by Q2 with its associated resistors. The way this works is quite simple.

Assuming that there is no significant voltage drop across R8 and R5, Q2 will be turned on by current fed into its base by R9 (or R4 in Fig. 7), and an amplified current will be fed from the positive line into the base of Q4 via R5, R8, Q2 and R10. (R10 serves to limit the maximum current which can flow, and to reduce the amount of dissipation in Q2). The maximum forward bias potential which can be applied to Q2 is held to about 1V1 by the two forward biased diodes D1 and D2. So — if we try to take more current from the circuit than would produce a 0V6 drop across R5 then Q2 will lose its operating forward bias and no more current will be fed into Q4 or Q1, which will limit the possible output current to a level just a little less than this value.

However, this has ignored the contribution made by R7 and R8. If there is too much voltage across Q1, which, as we have seen above, would reduce its ability to handle large currents safely, part of this voltage will also appear across R8, and this will also tend to turn off Q2, or at least make it current-limit at lower levels of voltage drop across R5. This has the required effect of tying the output current limiting value to the voltage drop across Q1, and means that, under something approaching short-circuit conditions, only a much reduced output current will flow.

### Using The Circuit

So, here we have a fairly

# PROJECT: Stabilised PSU

simple, low quiescent dissipation stabiliser circuit which uses standard discrete components and transistors, and which can be used to stabilise a single positive DC supply line (or if its 'mirror image' circuit is built, as in Fig. 7, a negative supply line too!) up to the maximum input voltages and currents which the components can stand. How, then, can we use this to improve an existing audio amplifier, which just uses a simple transformer-rectifier-reservoir capacitor system, as envisaged at the start of this article?

A single line stabilised supply is shown in Fig. 5 and a twin positive and negative supply is shown in Fig. 7: the DC output voltages and currents can be determined from the values shown in the tables. Now let us envisage a possible application. Measurement shows that on a hypothetical amplifier 'A', all of the internal DC supplies are drawn from a single power supply source which has a quiescent output voltage level of 66 V, dropping to 55 V on full load. If, at half load, which is the worst case condition, the heatsinks don't get alarmingly hot (as we must hope), and the HT line voltage is, shall we say, 60 V, then we could assume that a fixed voltage input supply somewhere between 60 and 65 V would not over-stress the amplifier

components, and we could build this output voltage into the circuit of Fig. 5 by the use of an appropriate string of zener diodes.

Such a separate DC supply could then be housed in its own small box, with the DC feed being taken to the amplifier with which it is used. (This is assuming that there isn't room within the existing box for the larger, higher voltage transformer which will be needed, or for the other components.) What sort of benefits will this bring?

First, one would expect a significant reduction in the existing amplifier 'hum' level, if it is less than perfect in this respect. Second, one could expect an improvement both in the 'solidity' of the bass response, due to the lower LF dynamic impedance of the HT line in comparison with even a large value of supply line reservoir capacitor, and this should also give a lower level of LF channel crosstalk. This latter feature is also important because most of the crosstalk signal components are heavily distorted in typical transistor output stages. Third, one would obtain a greater immunity from consequential damage, such as loudspeaker units burning out if failure in the amplifier caused it to switch over to some unwanted high current mode; and finally, one

would get more power output from it.

This last consequence arises from the fact that output power is determined by the equation  $P = V^2/R$ , where  $V^2$  is the square of the RMS output signal voltage, and R is the loudspeaker load impedance. For a 30 W amplifier with an 8 ohm load and the HT supply voltage characteristic shown above, a change in full load HT voltage from 55 V to 65 V would give an increase in power from 30 to 45 W without the need for the replacement of any other components.

## PCB Layouts

It makes a tidier and more professional looking unit if the necessary small components are mounted on a printed circuit board, so I have shown two such suitable layouts, complete with component overlay, in Figs. 8 and 9. The circumstances in which a PSU of this type might be used to upgrade an existing audio amplifier are rather too varied for anything other than general guidance to be given. However, these circuit layouts also allow the experimentally inclined user to build himself a useful short-circuit protected bench supply, which is literally a unit with dozens of uses.

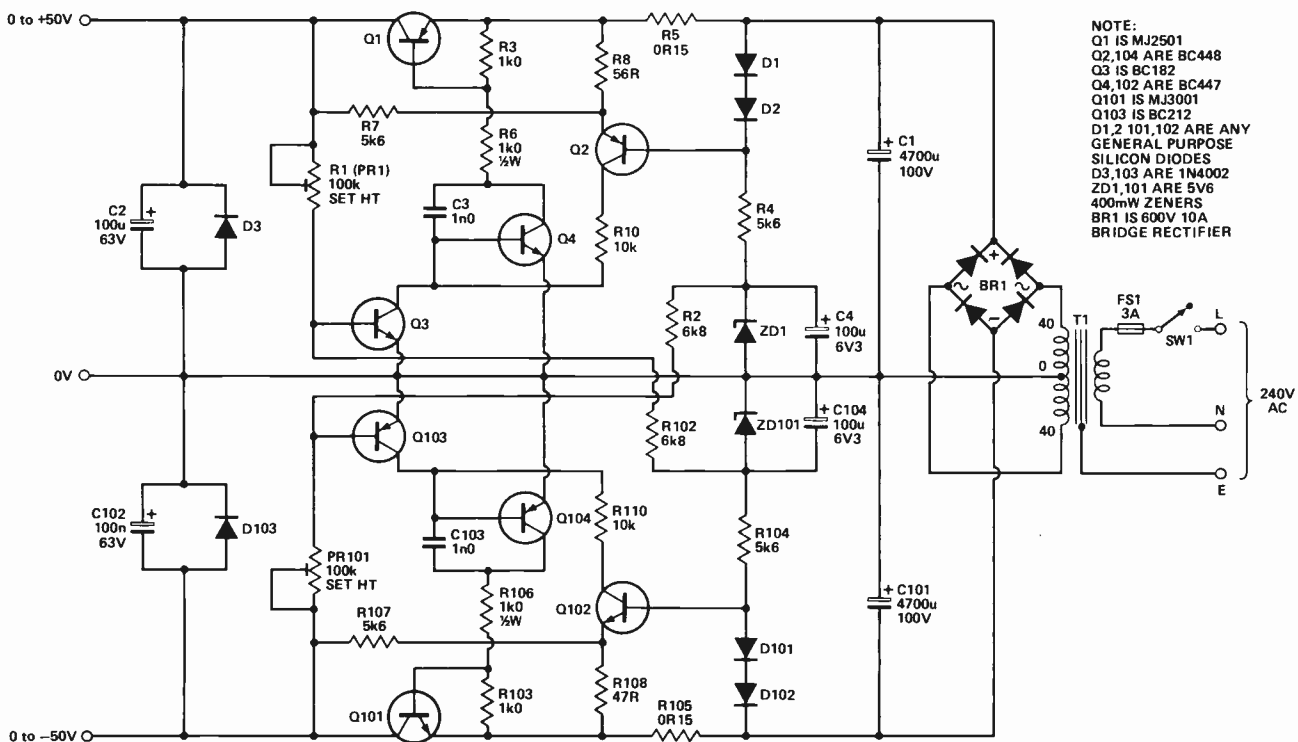


Fig. 7 Complete circuit for a twin stabilised power supply unit (current output 3 amps at 45 V).



# PROJECT: Stabilised PSU

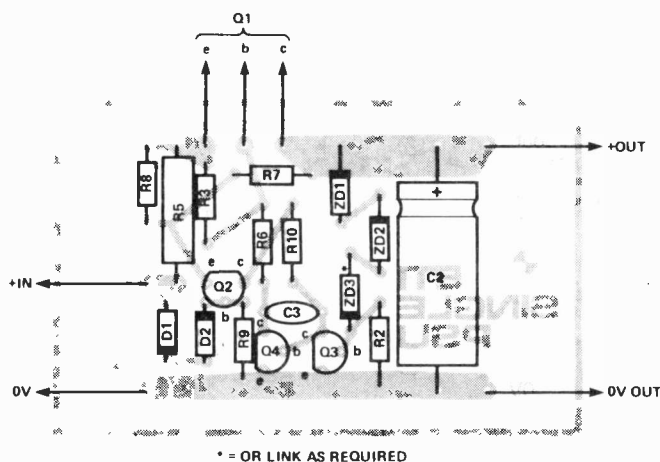


Fig. 8 Overlay for the circuit of Fig. 5.

**TABLE 1**

Maximum output voltage	Transformer voltage (per winding)	C1 minimum working voltage	R8
30	25	40	56R
40	33	50	56R
50	40	63	47R
60	48	80	43R

**TABLE 2**

Output current (amps)	Transformer secondary current rating (amps per winding)	R5
0.5	0.7	1R0
1	1.5	0R5
2	3	0R25
3	4.5	0R15
4*	6	0R12

\* (not recommended above 40 V)

## PARTS LIST

Resistors (all $\frac{1}{4}$ W, 5% except where stated)	C3	1n0 ceramic
R2	4k7	
R3	1k0	
R5	see Table 2	
R6	1k0 $\frac{1}{4}$ W	
R7	5k6	
R8	see Table 1	
R9	22k	
R10	10k	
Capacitors		
C1	4700uF electrolytic (see Table 1 for working voltage)	
C2	100uF 63 V axial electrolytic	
	Semiconductors	
	Q1	MJ2501
	Q2	BC448 or BC640
	Q3	BC182
	Q4	BC447 or BC639
	D1,2	general-purpose silicon diodes, eg 1N4148
	ZD2,3,etc	zeners to suit (see text)
	Miscellaneous	
	PCB (see Buylines); heatsink to suit.	
	See text for an explanation of the unusual component numbering.	

## BUYLINES

Two companies that can supply the transistors used in this project are Bradley Marshall, who advertise in this magazine, and Hart Electronics Ltd. of Oswestry, Shropshire. As a guide to price, Hart charge £1.50 plus VAT each for the MJ2501 and MJ3001, while the BC447 costs 20p plus VAT and the BC448 22p plus VAT. The PCBs can be obtained using the form on page 87.

## PARTS LIST

Resistors (all $\frac{1}{4}$ W, 5% except where stated)	
R1,101	suitable fixed resistor or (PR1,101) 100k miniature horizontal preset or off-board pot
R2,102	6k8
R3,103	1k0
R4,104,7,107	5k6
R5,105	see Table 2
R6,106	1k0 $\frac{1}{4}$ W
R8,108	see Table 1
R10,110	10k
Capacitors	
C1,101	4700uF electrolytic (see Table 1 for working voltage)
C2,102	100uF 63 V axial electrolytic
C3,103	1n0 ceramic
C4,104	100uF 6V3 axial electrolytic
Semiconductors	
Q1	MJ2501
Q2,104	BC448
Q3	BC182
Q4,102	BC447
Q101	MJ3001
Q103	BC212
D1,2,101,102	general purpose silicon diodes eg 1N4148
D3,103	1N4002
ZD1,101	5V6 400 mW zener
BR1	600 V, 10 A bridge rectifier
Miscellaneous	
PCB (see Buylines); heatsink to suit; centre-tapped transformer (see Tables 1 and 2); mains switch; 3 amp fuse and fuseholder.	

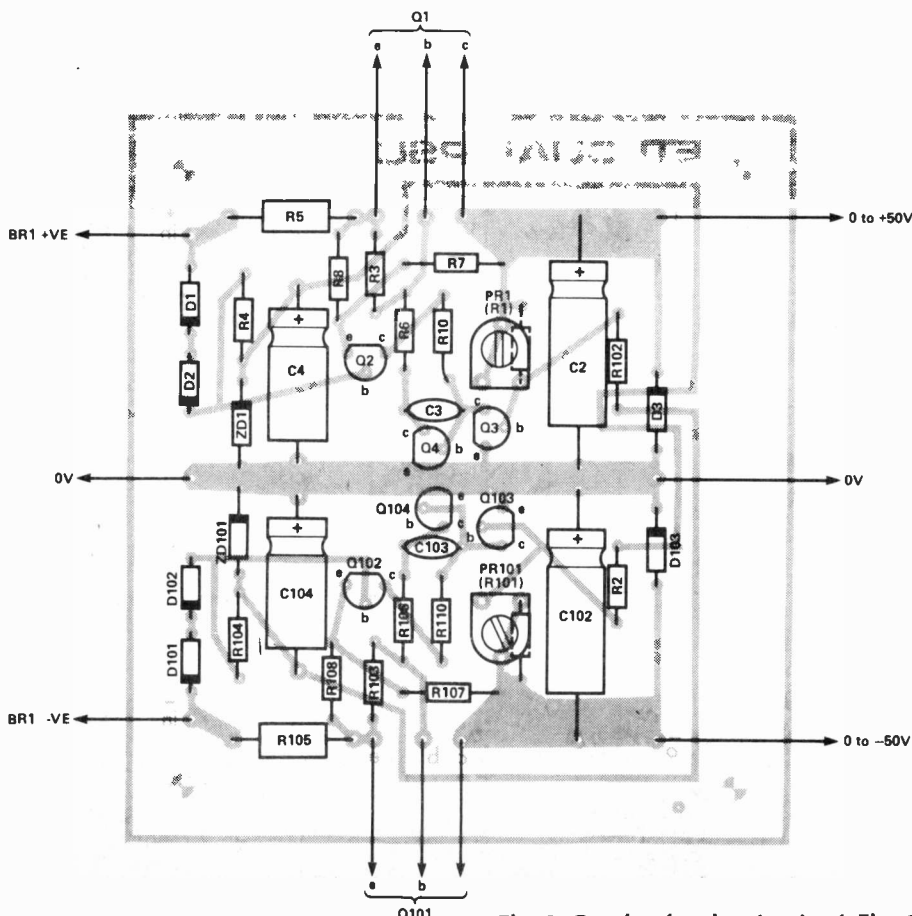


Fig. 9 Overlay for the circuit of Fig. 6.

# WORLD'S SMALLEST COMPUTER SYSTEM?

Breast Pocket Computer – A5 Book Size System.  
More powerful than pocket computers costing up to twice as much

Sharp PC-1251 Computer  
Plus FREE £5 software voucher **£74.95**

CE-125 Printer/Micro Cassette  
Plus FREE £5 software voucher **£94.95**

Custom made for Sales Executives. Ideal for Engineers and Hobbyists, or as a starter computer that grows into a powerful, reliable system.

**PC-1251.** Massive memory:- 4.2K RAM (3.7K user) and 24K ROM for extended BASIC, including DIM, STRING and INKEY\$. Up to 18 programs stored in memory at once, each with its own execute key, plus reserve mode for frequently used commands. One-touch mode selector for Reserve/Program/Run. Full range of math and science functions. QWERTY keyboard. 24 digit dot matrix display. Auto power-off, with memory protection.

**CE-125.** Half the size of this page and less than 1 inch thick! 24 character thermal-printing of data, computation results, programs, etc. Integral micro cassette recorder for error-free saving/loading, plus built-in interface for standard cassette recorder. Will run existing PC-1211 software but many times faster! Powered by rechargeable NiCad batteries, or mains adaptor (supplied).

SOFTWARE DETAILS ON REQUEST



**System Price £179.90**

Including VAT and Free £10 software voucher

### Dimensions

PC-1251. 135 x 70 x 9.5mm (5 1/16 x 2 3/4 x 3/8"). Weight: 115g

CE-125. 205 x 149 x 23mm (8 1/16 x 5 7/8 x 2 9/32"). Weight: 550g

## SHARP PC-1500 COLOUR COMPUTER

The world's most powerful pocket computer?

PRICES, including VAT and FREE software vouchers

PC-1500 Pocket Computer plus £10 software v ... **£159.95**

CE150 Colour Printer/Cass interface plus £10 v ... **£139.95**

CE-155 8K RAM Expansion Module plus £10 voucher ... **£79.95**

CE-159 8K RAM/ROM with battery back up + £10 v ... **£89.95**

CE-152 Custom Cassette Recorder plus £5 voucher ... **£39.95**

CE-153 140 key Software Board plus £10 voucher ... **£79.95**

CE-158 RS-232C Interface plus £20 voucher ... **£149.95**

SOFTWARE AND ACCESSORY LIST ON REQUEST

PRICES include VAT, P&P Offers are subject to availability Send cheques, P.O., or phone your credit card no. to


# MICROMAIL

Dept ETI, 31 Burleigh Street  
Cambridge CB1 1DG  
Telephone: 0223 12453

# MODULES FOR SECURITY & DETECTION

AS FEATURED IN PRACTICAL ELECTRONICS

## INTRUDER ALARM CONTROL UNIT CA1250

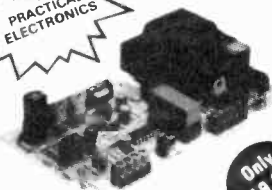

Only **£19.95** + VAT


This exciting new module offers all the possible features likely to be required when building an intruder alarm system. Whether used with only 1 or 2 magnetic switches or in conjunction with several ultrasonic alarm modules or infra-red units, a really effective system can be constructed at a fraction of the cost of comparable ready-made units. Supplied with a fully explanatory Data Sheet that makes installation straight forward, the module is fully tested and guaranteed.

\*available in kit form £16.95 plus VAT.

- Built-in electronic siren drives 2 loud speakers
- Provides exit and entrance delays together with fixed alarm time
- Battery back-up with trickle charging facility
- Operates with magnetic switches, u/sonic or I.R. units
- Anti-tamper and panic facility
- Stabilised output voltage
- 2 operating modes - full alarm/anti-tamper and panic facility
- Screw connections for ease of installation
- Separate relay contacts for switching external loads
- Test loop facility

## ULTRASONIC ALARM MODULE US 4012

Fully built & tested

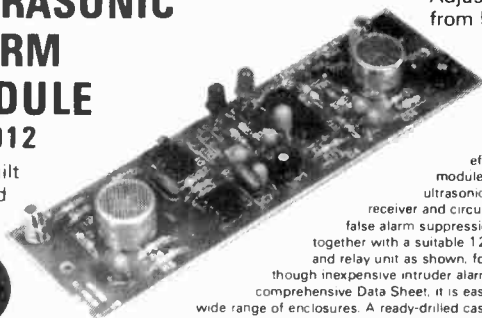

only **£10.95** + VAT

Adjustable range from 5ft. to 25ft.

A really effective fully built module containing both ultrasonic transmitter and receiver and circuitry for providing false alarm suppression. This module, together with a suitable 12V power supply and relay unit as shown, forms an effective though inexpensive intruder alarm. Supplied with comprehensive Data Sheet, it is easily mounted in a wide range of enclosures. A ready-drilled case and necessary hardware is available (see right).

## DIGITAL VOLTMETER MODULE DVM 314

Fully built & tested


only **£11.95** + VAT

## INFRA-RED SYSTEM IR 1470

only **£25.61** + VAT

Fully built & tested

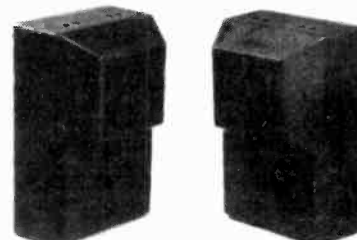- Range up to 50'
- 12V operation
- Supplied with full instruction
- Easily installed



Now available, a really effective infra-red system built to the high standards demanded by the security industry, and yet offered at this low price. The system consists of a transmitter and receiver which provide an invisible beam over distances from 1-50ft. or more. When the beam is interrupted, a relay is energised in the receiver unit. The use of a modulated beam combined with the infra-red filters, prevent interference from artificial or sunlight, whilst LED indicators ensure easy alignment of the beam. Both units are housed in attractive black moulded enclosures which are easily mounted. Supplied with full instructions, the unit is ideal for use in conjunction with the Control Unit CA 1250 or as an independent unit.

## Power Supply & Relay Units PS 4012

£4.25 + VAT

Provides a stabilised 12V output and relay with 3A contacts. The unit is designed to operate one or two of the ultrasonic units. Fully built and tested.

## Siren Module SL 157

£2.95 + VAT

Produces a loud and penetrating sliding tone operating from 9-15V. Capable of driving 2 off 8 ohm speakers to SPL of 110db at 2M. Contains an inhibit facility for use with shop lifting loops or other break to activate circuits.

## Hardware Kit HW 4012

£4.25 + VAT

A suitable ready-drilled case with the various mounting pillars, mains switch socket and nuts and bolts. Designed to house the ultrasonic alarm module together with its power supply. Size: 153mm x 120mm x 45mm.

## ★ ACCESSORIES ★

- 3-position Key Switch for use with CA 1250, supplied with 2 keys **£3.43**
- Magnetic switch (with magnet) **£1.17**
- 5" Horn speaker for use with CA1250 and SL157 **£4.95**

Add VAT & 50p post and packing to all orders.

Shop hours 9.00 - 5.30 p.m.

(Wed. 9.00 - 1.00 p.m.)

Units on demonstration - callers welcome. S.A.E. with all enquiries.



Telephone orders welcome

## RISCOMP LIMITED

Dept. PE4  
21 Duke Street,  
Princes Risborough, Bucks.

Princes Risborough (084 44) 632R

Please allow 7 days for delivery

# 60W NDFL AMPLIFIER

Following last month's article on nested differentiating feedback loops, here is a practical amplifier design, presented as a module, with very low distortion. Design by Edward M. Cherry, Associate Professor, Dept of Electrical Engineering, Monash University.

This amplifier will perhaps be of most interest to home constructors who want to rebuild an existing system and upgrade its performance without the expense of new major components. The power output transistors employed are the well-known types MJ802 and MJ4502 which have been around for several years and have proved their reliability. Indeed, the whole design is mature and home constructors should have no difficulty in making it work.

The theoretical basis for this amplifier was discussed in last month's ETI.

## Grounding

In any amplifier where the basic distortion has been reduced to a few parts per million, several distortion mechanisms not ordinarily considered may become significant. One such mechanism is associated with currents circulating in the ground leads and power-supply wiring.

Figure 1 explains the origin of this distortion. The current in each power transistor of a class B stage is a half-wave rectified version of the output. The two currents, drawn

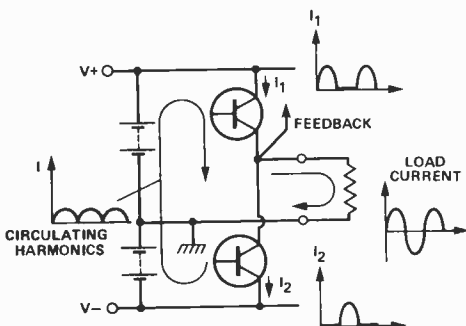


Fig. 1 Circulating even-harmonic current in a Class-B output stage.

## HOW IT WORKS

Figure 2 is the complete circuit of one channel of the amplifier; equations referred to in the explanation refer to last month's feature. The circuit is clearly based on Fig. 10 (last month's ETI), with major parameters

$$1/\beta = 32.9$$

$$\tau_x = 800 \text{ nS}$$

The value of  $\beta$  is set by the overall feedback resistors R11 and R12 (470R and 15k — see Equation 1).  $\tau_x$  is set by:

- R4 and R5 (330R) plus C6 and C8 (68p) in conjunction with the chosen value of  $\beta$  (see Equation 13);
- R15 and C7 (1k8 and 470p — see Equation 14);
- R32 and C14 (8R2 and 100n) plus the 8 ohm nominal load and L3 (6u8 H);
- R12 and C4 (15k and 33p) via the other constants in Equation 15.

The first stage requires little comment. Q1 and Q2 operate at 1.5 mA each, Q3 is a current source, Q4 is a common-base stage to equalize the quiescent voltages on Q1 and Q2; Q5 and Q6 constitute a current mirror. R1 and C2 form a 200 kHz low-pass filter against RF interference.

The Rush current amplifier operates at 3 mA, set by R18, and it incorporates a catching diode (D1) to accelerate recovery from overdrive. The pre-driver, Q10, operates at 8 mA; Q9 protects the stage against damagingly large currents under fault conditions. Driver quiescent current is 25 mA, set by R28.

Transistors Q12 and Q13 provide short-term protection for the power transistors. Short-circuit current is limited to about 4 A, and peak signal current is limited to 7 A. Long-term protection is provided by 2 A fuses in each supply rail; these should be 'ordinary' types, rather than delay or quick-blow. In the unlikely event of transistor failure, these fuses limit the loudspeaker current to 2 A, corresponding to 32 W into 8 ohms.

The common alternative of a single fuse in the loudspeaker lead is less satisfactory: it provides less protection for the amplifier; it provides less protection for the loudspeaker as the fuse must be rated to carry the full signal current, and it introduces distortion on large-

amplitude, low-frequency signals.

**LOW FREQUENCY COMPENSATION**  
A feature of Fig. 2 not discussed so far is a low-frequency compensating circuit, R13 and C5.

Amplifiers of the basic circuit topology of Fig. 2 (last month) have a group delay which is different for different signal frequencies. Some frequencies take longer or shorter times than others to pass through the amplifier. High-frequency group delay in NDFL amplifiers can be corrected, as described last month, by a small capacitor in the feedback network (see Equation 15). Errors in low-frequency group delay, in both Figures 2 and 10 (last month) are associated with the input coupling capacitor and the capacitor in series with R<sub>F1</sub>. Low-frequency square-wave inputs are reproduced with a 'tilt' as in Fig. 3a.

One approach to this problem is to use a truly direct-coupled amplifier, with no capacitors in series with the signal path; commercial audio power amplifiers of this type appeared in the 1970s. Unfortunately, such amplifiers are prone to drift. A significant DC voltage may appear at the output even when there is no input. Although it is possible to reduce drift in a power amplifier to an acceptable level, it is not possible with today's technology to build a system that is truly direct-coupled from pick-up input, through the RIAA network and the power amplifier.

In the last few years a generation of amplifiers has appeared which include some form of servo amplifier to correct the drift. All circuits known to the author re-introduce the problem of group delay, albeit in a lesser form.

The approach adopted in the design is to retain the coupling capacitors and thereby eliminate drift, but include a group-delay correcting circuit. Figure 4 shows the outline. Group delay is optically compensated if:

$$R_{F3} = 2 R_{F2}, \quad (16)$$

$$R_{F2} C_{F2} = R_{F1} C_{F1} \quad (17)$$

Figure 3b shows the improvement in square-wave response.

Low-frequency group-delay compensation could well be included in audio power amplifiers and preamplifiers other than NDFL types.



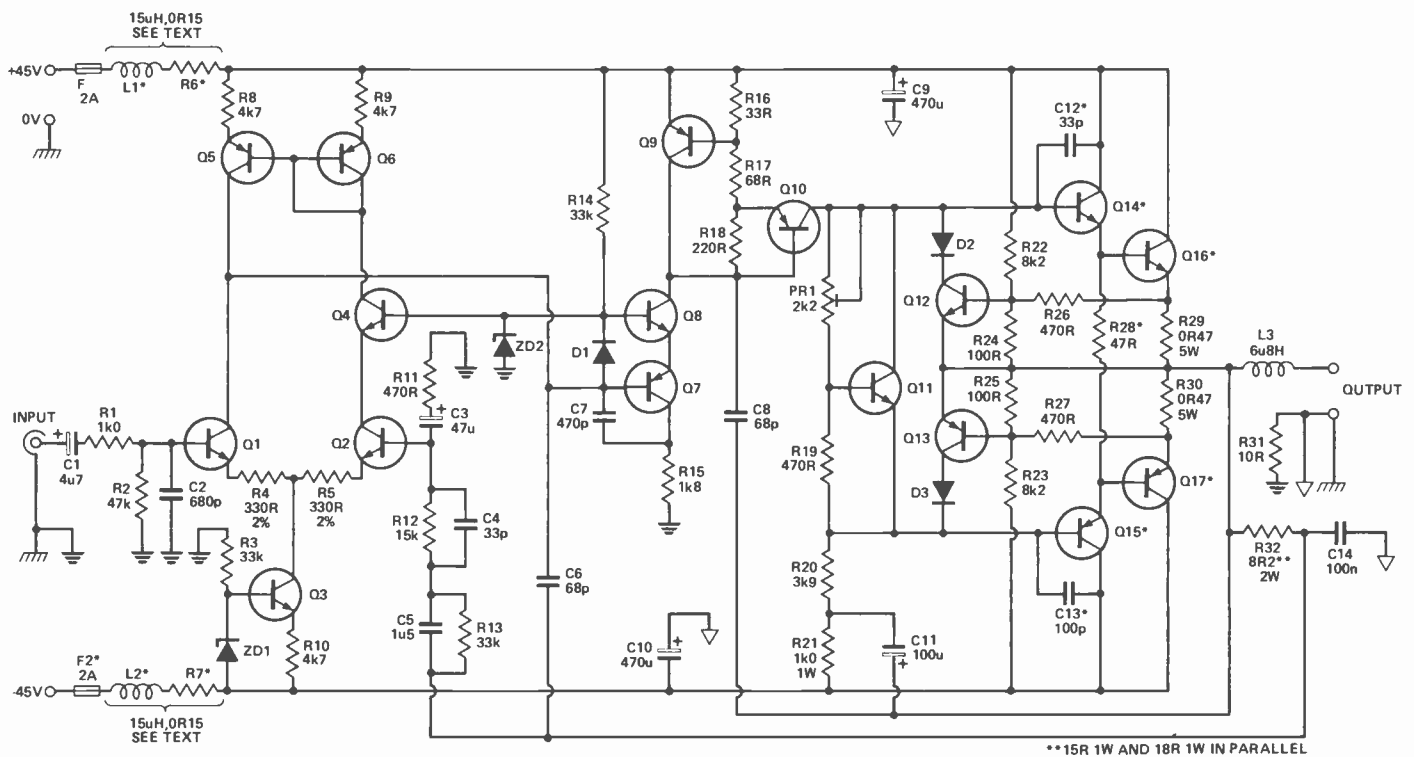


Fig. 2 Circuit diagram of the 60 W power amp. Components marked with a single asterisk are not mounted on the PCB.

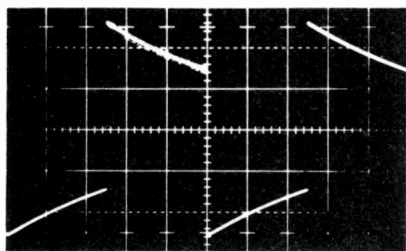


Fig. 3a Square wave response of the amp without group-delay compensation.

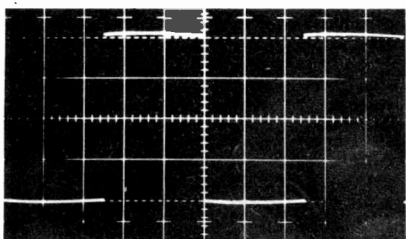


Fig. 3b Square wave response of the amp with group-delay compensation — note the improvement over Fig. 3a.

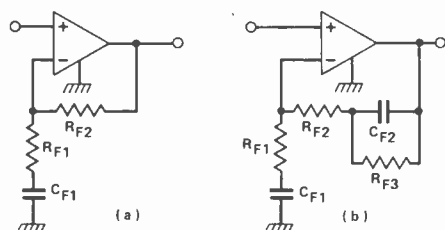


Fig. 4 Circuit for compensating low frequency group delay: (a) basic uncompensated circuit; (b) compensated circuit.

alternatively from the positive and negative supplies, are equivalent to a circulating full-wave rectified current and this is basically an even-harmonic distortion of the signal output. If there is any mutual inductance between the power-supply wiring (including the grounds) and the signal wiring (also including the grounds), then an even-harmonic distortion is induced in the amplifier and feedback is powerless to correct it.

The circuit board has been laid out so as to minimise this effect. The areas enclosed by some tracks are critical, and home constructors making their own PCBs are cautioned to follow the layout exactly; use the foil pattern on page 84, or, better still, purchase a ready made board.

Note that the circuit uses three distinct ground symbols.

- a) is the *quiet ground* track on the circuit board (one per channel).
- b) is the *noisy ground* track on the circuit board (one per channel).
- c) is the metal chassis ground (there are six connections to the chassis in total).

Each channel is connected to chassis ground at two points. The

input socket is connected to the chassis (rather than insulated from it), the input lead from socket to circuit board is screened, and the quiet ground track is connected to chassis ground at the input socket via the screen. Similarly, the ground output terminal is screwed into the chassis, the leads from the circuit board to the output terminals are a twisted pair and the noisy ground track is connected to chassis ground at the output terminals via the ground output lead. The remaining two connections to chassis are in the power supply (Fig. 5).

Note that a 10 ohm resistor, R31, links the quiet and noisy ground tracks. This resistor is short circuited at low frequencies by the input screen and neutral output wiring to chassis ground. However, the resistor takes over at high frequencies where wiring inductance become significant.

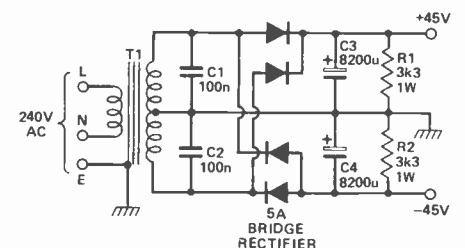


Fig. 5 Suggested PSU for the amplifier. Alternatively, see next month's ETI for a better choice.

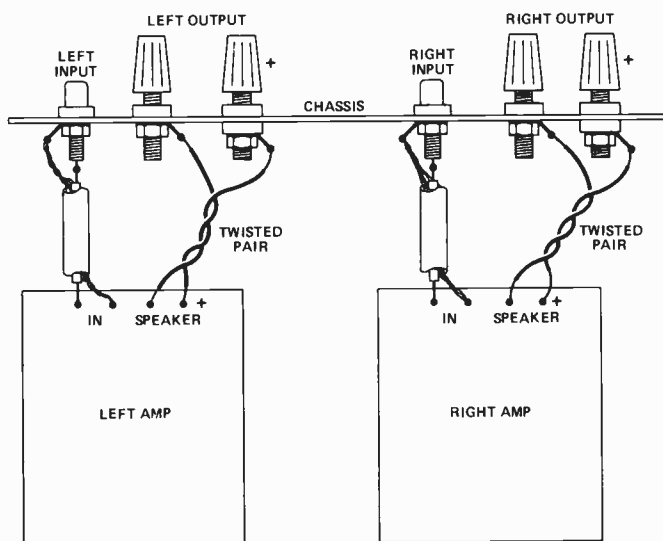


Fig. 6 Showing the general technique for connecting inputs, outputs and grounds to a stereo pair of modules.

The  $15\mu\text{H}$  filter inductors in the supply rails are also for suppressing circulating currents (R6 and R7 represent the winding resistances of L1 and L2).

This amplifier employs only two nested differentiating feedback loops and its distortion is not down to the ultimate limit. The benefit of including the filter inductors is therefore marginal. The author is not blessed with 'golden ears' and cannot hear the effect of removing the filters, although the difference is clearly measurable. The filters should certainly be included in amplifiers that use three or more NDFLs. As the inductors must be home-made, and therefore cost nothing but time, and as they do make a measurable (if small) improvement, most home constructors will probably wish to include them. Winding data is given in Table 1.

The precise values of inductance and resistance are not important —  $\pm 50\%$  is good enough — but do not use the 1.25 mm wire from L3 as something like 0.1 ohm series resistance is essential. For a similar reason, do not parallel the  $470\mu\text{F}$  bypass capacitors C9 and C10 with high-frequency types. Brass or steel mounting screws are perfectly satisfactory for the filter inductors, as linearity is not important.

### Critical Components

The majority of the components in this amplifier are not critical. Almost any small-signal diodes will do, such as the 1S44, 1N914, and 1N4148. Q1 and Q2 should be high-gain, low-noise types — BC109 and BC549 are among the cheapest available. The others could be

almost any small signal types: BC107 and BC547 are readily available NPN types, the BC177 and BC557 are suitable PNPs. The driver and output transistors should be the types shown: BD139 and BD140 for the drivers, MJ802 and MJ4502 for the power transistors. The biasing transistor, Q11, could be any NPN in a TO-126 pack that can be mounted on the heatsink: the BD135 and BD139 are readily available types that would suit.

Unless the contrary is indicated on the Parts List, resistors can be standard  $\frac{1}{2}\text{W}$  types and the capacitors can be the lowest available working voltage. A few components, however, do require special mention. A feedback amplifier cannot be more linear than its feedback network, so the various components that constitute the feedback network should have small voltage coefficients. Specifically:

- The overall feedback resistors R11 and R12 should be high-stability types, such as metal oxide or metal film;
- C4, C6 and C8 should be NPO ceramics, not high-K types (NPO means negative-positive zero, a low-K capacitor with a very low temperature coefficient; metallised plate ceramics, for example. Silvered mica capacitors are also suitable);
- C5 and C14 should be polycarbonate, polystyrene or polypropylene types, but not polyester (eg mylar types);
- C3 should be an ordinary cheap aluminium electrolytic, definitely not one of the relatively expensive resin-dipped tantalum types (this is not a misprint!).

TABLE 1

#### Formers

If a suitable type is not to hand, these may be turned from 25 mm diameter polystyrene rod to give 12 mm internal bobbin diameter with 7.5 mm winding space between cheeks.

#### Wire & Winding L1, 2

Take two 1680 mm lengths of 0.75 mm diameter enamelled copper wire and wind onto each former leaving 20 mm or so lead length at start and finish.

#### Wire & winding L3

Take a 1190 mm length of 1.25mm diameter enamelled copper wire and wind it onto the former. Leave 20 mm or so lead length at start and finish.

### HARMONIC ANALYSIS AT 1 kHz

Harmonic	Rated output	
	21V9 60 W	2V19 600 mW
2nd	19 ppm	5 ppm
3rd	14	3.5
4th	2.5	2.5
5th	3.0	1.5
6th	<1	<1
7th	1.8	1.8
8th	<1	<1
9th	1.0	<1
10th	1.8	<1

Notice how the harmonics drop away at small signal amplitude. In this regard a class-B NDFL amplifier is more like a conventional class-A amplifier than a class-B amplifier.

1 ppm = 0.0001%

### HARMONIC ANALYSIS AT 6 kHz

Harmonic	Rated output	
	21V9 60 W	2V19 600 mW
2nd	115 ppm	40 ppm
3rd	100	25
4th	32	15
5th	40	9

Harmonics higher than the 3rd are ultrasonic and hence inaudible.

### BUYLINES



Amongst the semiconductors, only Q16 (MJ802) and Q17 (MJ4502) could possibly present problems: these are both available from Bradley Marshall, Cricklewood and Technomatic.

Some care will be needed in ordering the capacitors mentioned as critical, though the types should not be that hard to find. The PCB is available through the ETI PCB service on page 87.

### PATENT PROTECTION

The principle of nested differentiating feedback loops, on which this amplifier depends, is patented in Britain and principal overseas countries. Commercial enquiries should, in the first instance, be directed to the Legal Office, Monash University, Clayton, Victoria 3168, Australia.

# PROJECT: 60 W NDFL Amp

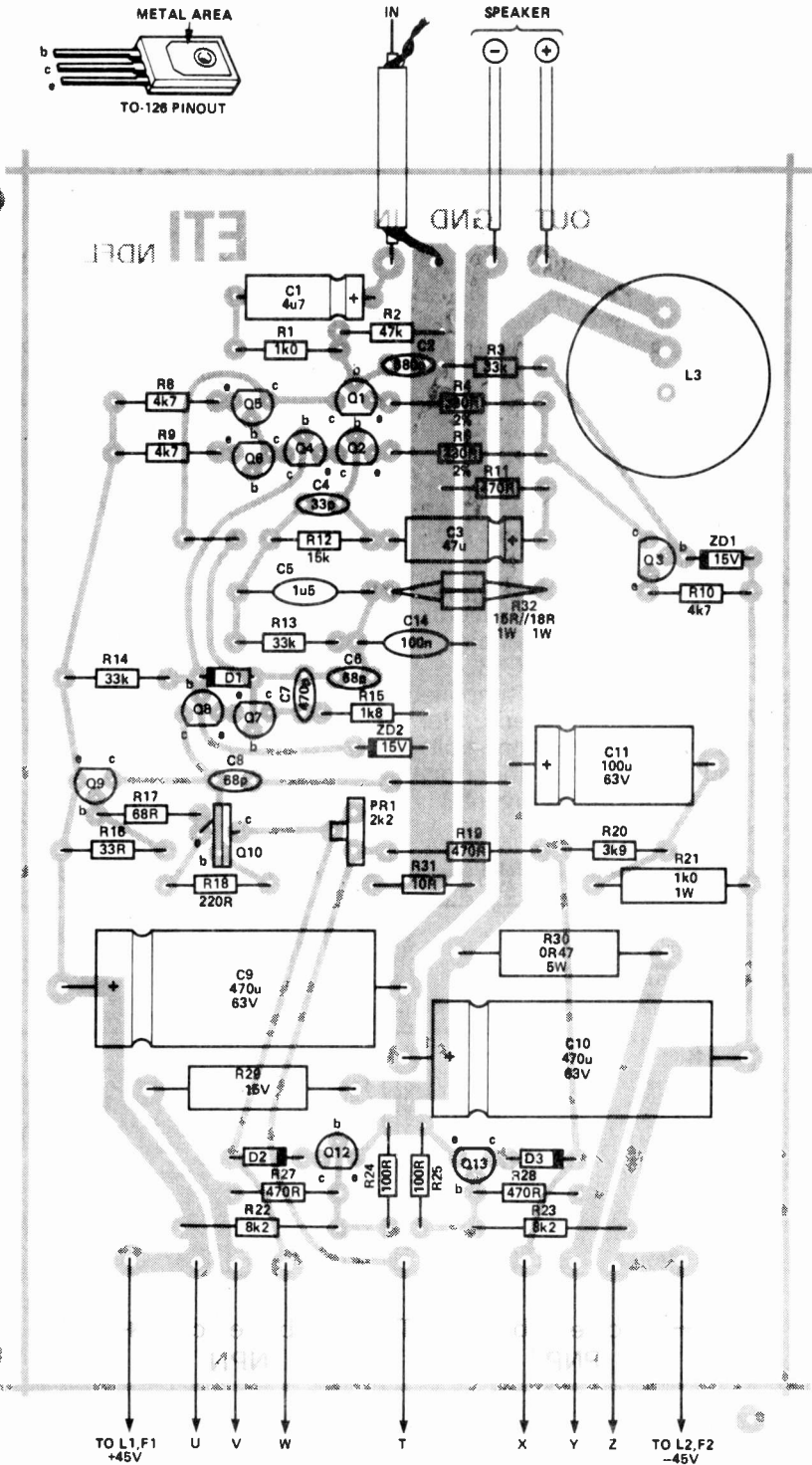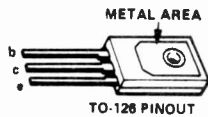

## PARTS LIST

Resistors (all 1/2W, 5% except where stated)	
R1	1k0
R2	47k
R3,13,14	33k
R4,5	330R 2%
R6,7	see text
R8-10	4k7
R11	470R metal oxide or metal film
R12	15k metal oxide or metal film
R15	1k8
R16	33R
R17	68R
R18	220R
R19,26,27	470R
R20	3k9
R21	1k0, 1 W
R22,23	8k2
R24,25	100R
R28	47R
R29,30	0R47, 5 W
R31	10R
R32	8R2, 2 W or 15R//18R, each 1 W
Potentiometer	
PR1	2k2 miniature vertical preset
Capacitors	
C1	4u7 axial electrolytic
C2	680pF ceramic
C3	47uF axial electrolytic
C4	33pF 100 V NPO ceramic
C5	1u5 polycarbonate
C6,8	68pF 100 V NPO ceramic
C7	470pF ceramic
C9,10	470uF 63 V axial electrolytic
C11	100uF 63 V axial electrolytic
C12,13	33pF 100 V ceramic
C14	100nF 100 V polycarbonate
Inductors	
L1, 2	15uH (see text and Table 1)
L3	6u8 H (see Table 1)
Semiconductors	
Q1,2	BC109, BC549 etc
Q3,4,8,12	BC107, BC547 etc
Q5-7,9,13	BC177, BC557 etc
Q11,14	BD139
Q10,15	BD140
Q16	MJ802
Q17	MJ4502
D1-3	1N4148, 1N914, 1544 etc
ZD1,2	15 V 400 mW zener
Miscellaneous	
F1,2	2 A standard fuse
PCB (see Buylines); one 4-way and one 5-way tagstrip; heatsink to suit (see text); PCB stakes; bobbins for inductors; wire, etc.	

Fig. 7 Component overlay for the power amplifier.

The 6u8 H inductor (L3) needs to be home-made. Winding data is given in Table 1. The bobbin should be mounted on the circuit board with a nylon screw; brass or steel must not be used, because of non-linear eddy current losses.

### Construction

Assembly of the PCB is quite straightforward. It is probably best to commence by soldering all the resistors in place. Note that R32


could be either a 2 W type (not common) or two 1 W resistors (15R and 18R) in parallel. Note that the emitter ballast resistors of Q16 and Q17 (R29 and R30) should have very low inductance and if you have trouble with high frequency instability, these resistors are likely to be the culprit. The best solution may be several carbon resistors in parallel. Mount R29 and R30 a few millimetres above the board.

Assemble the diodes next,

making sure you get them all the right way round. Install the links next. Follow with the capacitors. Note that C5 and C14 must be polycarbonate types and C4, 6 and 8 must be NPO ceramics. None of the other ceramic capacitors should be hi-K types, as mentioned earlier. When mounting C9 and C11, see that there is three or four millimetres between the capacitor body and the adjacent 5 W resistors (R29 and R30) to allow for



# PROJECT: 60 W NDFL Amp

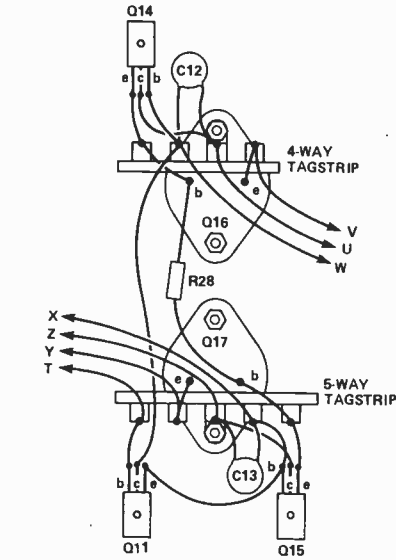

**Fig. 8 Wiring diagram for the components mounted on the heatsink.**

convection around the latter.

The transistors may be mounted now. See that each is oriented correctly. Wind L3 next and mount it on the board. Details are given in Table 1. It is not necessary to strictly follow the former dimensions

given, but the inductance needs to be close to 6u8 H and wound from 1.25 mm wire at least, for low resistance.

Assembly of the components mounted to the heatsink comes next. The heatsinks in the original were a standard type sold by many companies and masquerading under such names as type 6W-1 (Maplin) or RS 401-807. Each heatsink has a thermal resistance to ambient of about 1°C/W, and other types could, of course, be substituted. The specified thermal resistance permits continuous operation at full power: smaller heatsinks (up to 2°C/W) could be substituted if the amplifier is to be used only for domestic sound reproduction. Use one heatsink per channel.

Three small components are mounted on the heatsink adjacent to the transistors to keep certain leads short: R28, C12 and C13. Construction is very much simplified if a 4-way tagstrip is installed under one of the collector mounting bolts of Q16 and a 5-way strip under one of Q17's mounting bolts. Figure 8 shows details.

The collector and emitter leads from each power transistor to the circuit board should be twisted. The base leads to Q14 and Q15 could be twisted in with the corresponding collector and emitter leads (although this is not necessary) and the base lead of Q11 can be kept separate. Note that all transistors must be insulated from the heatsink. Note also that the BD140 specified for Q10 needs its leads dressed to fit the board.

Quiescent current in the power transistors should be set to 40-60 mA by PR1. *Be warned* that this quiescent current is almost zero until PR1 is about three-quarters of its maximum resistance, after which the current increases very rapidly; be sure that PR1 is set to *minimum resistance* when the amplifier is turned on for the first time.

A convenient way to check the quiescent current is by means of the voltage drop across R29 and R30; this should be 40-60 mV (total) for zero signal input to the amplifier.

**See the June ETI for details of a complete NDFL amplifier system. ETI**

All devices guaranteed Brand New and to full spec. Items ex stock despatched same day. Prices are EXCLUSIVE of VAT. Please add 60p to order to cover P&P BEFORE calculating VAT. Payment by cheque, Postal Order, Bankers Draft or Cash (PLEASE register) with order. Official orders from Govt. Dept.s and Educational Institutes Welcome. Trade Accounts opened subject to satisfactory status — send for details. We are pleased to receive overseas orders (please allow adequate postage — surplus to Bankers Commission and slight delay in despatch. Overseas trade enquiries welcome — send for full details. VAT not applicable to export orders. Price List detailing full range of components available — 30p refundable with first order. Please send SAE.

## COMPARE OUR PRICES

LINEAR				CMOS				74LS				TANTALUM				ZENER DIODES			
555CMOS	80	LM3909	70	ZN459	285	4000	11	4518	39	LS00	11	LS153	38	BEADS	2V7-33V 500MW	7			
556CMOS	140	LM3911	175	ZN1034E	200	4001	11	4520	48	LS01	11	LS155	29		5V1-75V 1.3W	14			
709	25	LM3914	120			4002	11	4521	90	LS02	11	LS156	33						
741	14	LM3915	195			4007	14	4522	105	LS03	11	LS157	25						
748	35	LM13600	105			4008	34	4526	55	LS04	12	LS158	27						
6400CJ	345	MC1496	68	AY-2376	590	4009	24	4527	55	LS05	12	LS160	30						
AT-3-1270	710	MC3340	120	MC1488	55	4011	11	4528	45	LS08	12	LS161	30						
AT-3-8910	370	MF10CN	350	MC1489	55	4011	11	4531	65	LS09	12	LS162	35						
AY-3-8912	540	ML924	195	MMS303	625	4012	14	4532	60	LS10	12	LS163	35						
CA3046	60	NE529	225	MMS307	1250	4013	20	4538	60	LS11	12	LS164	40						
CA3080	65	NE531	135	MMS58174	700	4015	39	4539	80	LS12	12	LS165	50						
CA3089	190	NE544	180	TMS6011	365	4016	20	4543	60	LS14	22	LS168	80						
CA3090AQ	370	NE555	16	ULN2003	75	4017	32	4555	35	LS15	12	LS170	70						
CA3130E	85	NE556	45	8T26	99	4020	42	4556	35	LS20	12	LS173	47						
CA3140E	38	NE565	110	8T28	120	4021	39	4561	100	LS21	12	LS174	36						
CA3161E	100	NE566	140	8T95	90	4022	39	4563	80	LS22	12	LS175	35						
CA3189	200	NE567	100	8T97	90	4023	39	4584	40	LS27	12	LS181	87						
CA3240E	170	NE570	370	81LS95	80	4024	32	4585	50	LS28	14	LS183	07						
ICL7106	680	NE571	370	81LS96	80	4025	12			LS30	12	LS190	05						
ICL7611	95	RC4136	55	81LS97	80	4027	20	COMPUTER ICs		LS32	13	LS191	35						
ICL7621	180	RC4558	45	81LS98	85	4028	37	1802	650	LS33	14	LS192	35						
ICL7622	180	SL490	250	6522	310	4029	43	2650A	1175	LS37	14	LS193	36						
ICL8038	290	SL76477	380	6532	675	4035	45	6502	320	LS40	12	LS194	32						
ICL8211A	150	SP8629	250	6821	110	4040	40	6800	220	LS42	28	LS195	32						
ICM72224	775	TBA120S	70	6845	650	4042	38	6802	250	LS47	35	LS196	43						
ICM7555	80	TBA800	75	6847	650	4043	40	6809	615	LS48	40	LS197	45						
LF353	85	TBA810	95	6850	110	4044	40	8035	345	LS49	50	LS221	50						
LF356	90	TBA820	70	6852	250	4049	22	8060	1090	LS51	14	LS240	55						
LM10	325	TBA950	220	6875	485	4050	22	8080A	250	LS54	14	LS241	55						
LM301A	24	TA100B	310	8155	350	4051	42	8085A	345	LS55	14	LS242	55						
LM311	70	TDA1022	480	8212	110	4052	48	Z80A	315	LS56	16	LS243	55						
LM318	120	TDA1024	115	8216	100	4053	48			LS74	14	LS244	55						
LM324	30	TL061	40	8224	110	4066	22	MEMORIES		LS75	16	LS245	70						
LM334Z	90	TL062	60	8226	250	4068	14	2101	395	LS76	16	LS251	28						
LM335Z	120	TL064	95	8228	220	4069	13	2114(220ns)	85	LS78	17	LS253	30						
LM339	45	TL071	25	8243	270	4071	13	2532	295	LS83	33	LS257	29						
LM348	60	TL072	45	8250	865	4072	13	2708	225	LS85	39	LS258	32						
LM358	55	TL074	95	8251	250	4073	13	2716(5V)	210	LS86	15	LS259	53						
LM377	165	TL081	24	8253	400	4075	13	2764	750	LS90	22	LS266	18						
LM380	65	TL082	45	8255	225	4076	44	2764	1000	LS92	25	LS273	53						
LM381	110	TL084	90	8257	400	4078	13	2708	225	LS93	21	LS279	30						
LM382	110	TL170	48	8259	395	4081	12	2764	750	LS95	36	LS283	38						
LM384	130	UA2240	115	8279	385	4082	12	4116(200ns)	80	LS109	20	LS290	40						
LM386	65	ULN2003	75	8832	250	4093	23	4118-3	325	LS112	20	LS293	40						
LM387	120	ULN2004	75	9602	220	4099	70	5101(450ns)	150	LS113	20	LS365	27						
LM389	95	XR2208	285	Z80ACTC	260	4502	50	5204	725	LS114	21	LS366	27						
LM711	60	ZN414	79	Z80ADART	775	4508	110	6116(150ns)	375	LS125	25	LS367	27						
LM725	325	ZN423	130	Z80ADMA	975	4510	45	6514	330	LS126	24	LS368	27						
LM733	69	ZN424	130	Z80AP10	270	4511	45	6810	115	LS127	25								
LM747	60	ZN425E	340	ZN425E8	320	4512	42			LS128	29	MICRO-MINI							
LM1458	40	ZN426E	290	ZN426E8	320	4514	110			LS136	23	100V CERAM							
LM2917	185	ZN427E	575	ZN427E8	575	4515	110			LS138	24	PLATE CAPS							
LM3900	45	ZN428E	395	ZN428E8	395	4516	50			LS139	27								
										LS151	30								

# MIDWICH COMPUTER COMPANY LIMITED

FAST EX-STOCK DELIVERY OF MICROCOMPUTER COMPONENTS AT UNBEATABLE PRICES

## Official BBC Dealer

**BBC COMPUTERS**  
Model B 348.95  
Model B + Disc Interface 441.95  
(carriage 6.50 by Securitor)

**BBC MICRO DISC DRIVES**  
BBC 31 Single 100K Drive Expandable to 2x100K 229.00  
BBC 32 Dual 100K Drives 340.00  
BBC 33 100K Upgrade for BBC 31 122.00  
BBC 34 Dual 400K Drives 649.00

All Disk Drives (except BBC 33) are complete with Manual, Utilities Disc, and Connecting Cables.

**BBC MICRO UPGRADE KITS**  
BBCA2B Complete A to B Upgrade 44.75  
BBC 1 16K Memory 18.00  
BBC 2 Printer/User I/O Kit 7.50  
BBC 3 Disc Interface Kit 95.00  
BBC 4 Analogue Input Kit 6.70  
BBC 5 Serial I/O & RGB Kit 7.30  
BBC 6 BUS Expansion Kit 6.45

All Kits are supplied with full fitting instructions.

**BBC CONNECTORS**  
BBC 21 Printer Cable and Amphenol Plug (not assembled) 13.00  
BBC 22 User Port Connector and Cable 36" 2.46  
BBC 23 Cassette Lead 3.50  
BBC 24 7 Pin DIN Plug 0.60  
BBC 25 6 Pin DIN Plug 0.60  
BBC 26 5 Pin DIN Plug 0.60  
BBC 35 Disc I/O Cable 34W IDC to 2x34 way card edge 12.00  
BBC 36 Disc Power Cable 6.00  
BBC 44 Analogue Input Plug and Cover 2.25  
BBC 66 IM Bus Connector + 36" Cable 3.50

**BBC ACCESSORIES**  
BBC 45 Joysticks (per pair) 11.30  
BBC 67 Eprom Programmer (assembled) 57.95  
BBC 71 Teletext Receiver 225.00  
BBC 72 Second Processor (6502) 170.00  
BBC 73 Second Processor (Z80) 170.00

**ACORN SOFTWARE FOR THE BBC**  
SBE03 Business Games 8.65  
SBE04 Tree of Knowledge 8.65  
SBE02 Peeko Computer Inc Manual 8.65  
SBE01 Algebraic Manipulation Pk 8.65  
SBX01 Creative Graphics Cassette 8.65  
SBX02 Graphics and Charts Cassette 8.65  
SBB01 Desk Diary inc Manual 8.65  
SBL02 LSP Cassette 14.65  
SBL01 FORTH Cassette 14.65  
SBG01 Philosophers Quest 8.65  
SBG07 Sphinx Adventure 8.65  
SBG03 Monsters 8.65  
SBG04 Snapper 8.65  
SBG15 Planetoid 8.65  
SBG06 Arcade Action 10.35  
SBG05 Rocket Raid 8.65  
SGB13 Meteors 8.65  
SGB14 Arcadians 8.65  
SGB10 Chess 8.65

**ACORN SOFTWARE BOOKS FOR THE BBC MICRO**  
SBD01 Creative Graphics 7.50  
SBD02 Graphs and Charts 7.50  
SBD04 LSP 7.50  
SBD03 FORTH 7.50

Please ring for current delivery on Acornsoft Products before ordering.

**BBC MICRO COMPONENTS**  
4516 100ns 2.25  
6522 3.19  
74LS244 0.50  
74LS245 0.69  
74LS163 0.34  
DS3691N 4.50  
DS88LS120N 4.50  
UPD7002 4.50

**BBC SOFTWARE IN EPROM**  
Wordprocessor "View" 52.00  
1.2 MOS 10.00

## SPECIAL OFFER

Spectrum 32K Upgrade Kit  
**24.95**

**DATA SHEETS** are available on items marked D. Prices are as follows:

D1 0.75  
D2 1.00  
D3 1.25  
D4 2.00  
D5 2.50  
D6 3.00  
D7 4.00

### MEMORIES

2114L 200ns D1 0.80  
2708 450ns D2 2.95  
2716 450ns D1 2.45  
2716 350ns D1 4.95  
2716 3 rai D1 7.25  
2532 450ns D2 3.45  
2732 450ns D1 3.45  
2732 350ns D1 5.45  
2764 300ns D1 5.99  
4116 150ns D2 0.85  
4116 200ns D2 0.80  
4118 150ns D1 3.25  
5516 200ns D2 9.45  
6116 150ns D1 3.30  
6116 Low Power 150ns D2 4.95  
4164 150ns TI D3 4.45  
4164 200ns TI D3 3.95  
4164 150ns Mostek D3 4.45  
4516/4816 100ns D2 2.25  
4532 200ns D2 2.95

### 8800 FAMILY

6800 D7 2.25  
6802 D5 2.50  
6809 D6 6.30  
6810 D1 1.15  
6821 D3 1.00  
6840 D4 3.75  
6845 D5 6.50  
6850 D2 1.10  
68488 D2 7.30  
68800 D7 5.25  
68809 D6 12.00  
68810 D1 2.26  
68821 D3 2.20  
68840 D4 6.00  
68850 D2 2.20

### Z80 FAMILY

Z80ACPU D2 2.99  
Z80BCPU D2 9.00  
Z80ACTC D1 2.60  
Z80BCTC D1 9.00  
Z80ADART D1 5.50  
Z80ADMA D2 6.95  
Z80AP10 D1 2.75  
Z80BP10 D1 9.00  
Z80AS10 D4 9.00

### 8080 FAMILY

8085A D4 3.50  
8212 1.10  
8216 1.00  
8224 2.10  
8228 3.27  
8251A D5 2.50  
8253 4.00  
8255A D5 2.25

### 6500 FAMILY

6502 D3 3.25  
6502A D3 5.00  
6520 D1 2.50  
6520A D1 3.16  
6522 D5 3.19  
6522A D5 5.50  
6532 D2 5.50

### FLOPPY DISC CONTROLLERS

8271 38.00  
FD1771 D5 15.00  
FD1791 D6 22.00  
FD1793 D6 23.00  
FD1795 D6 28.00  
FD1797 D6 28.00  
WD1691 D2 12.00  
WD2143-01 D2 6.99

### INTERFACE DEVICES

6402 3.80  
75107 0.47  
75110 0.56  
75150 0.84  
75154 0.77  
75160 2.56  
75161 2.80  
75162 3.95  
75172 1.95  
75173 1.44  
75174 1.95  
75175 1.44  
75182 0.50  
75183 0.50  
75188 0.37  
75189 0.37

### 75451 0.22

75452 0.22  
75453 0.22  
75454 0.22  
75468 0.88  
75491 0.31  
75492 0.42  
AY31015 D2 3.00  
AY31270 6.47  
AY38910 D6 4.40  
AY53600 D2 6.70  
DPB304 D1 2.50  
MC1488 D1 0.37  
MC1489 D1 0.37  
MC3242A 6.30  
MC3446 D1 2.50  
MC3448A D1 3.75  
MC3480 D5 7.30  
MC3487 D1 2.00  
MC14411 D1 7.65  
MC14412 9.45  
RG32513L D1 6.50  
RG32513U D1 6.50

### UMF MODULATORS

UM1111 6MHz D1 2.60  
UM1233 8MHz D1 3.90

### BUFFERS

81LS95 0.80  
81LS96 0.80  
81LS97 0.80  
81LS98 0.80  
81T26A 0.90  
81T28A 0.90  
81T95 0.90  
81T97A 0.90  
81T98 0.90

### LINEARS

L203 0.65  
LF98BN 4.75  
LM301AN 0.24  
LM308N 0.48  
LM311P 0.50  
LM319N 1.99  
LM324N 0.30  
LM348N 0.60  
NE555P 0.16  
NE555CP 0.45  
TL010 0.39  
TL011 0.32  
TL012 0.34  
TL014 0.36  
TL021 0.34  
TL061 0.29  
TL062 0.48  
TL064 0.98  
TL066 0.29  
TL068 0.32  
TL071 0.29  
TL072 0.47  
TL074 1.00  
TL081 0.26  
TL082 0.46  
TL084 1.58  
TL091 0.40  
TL092 0.58  
TL094 1.34  
TL487 0.82  
TL489 0.82  
TL494 1.65  
TL496 0.60  
TL507 1.33  
725 1.60  
741 0.14  
747 0.48  
748 0.27

### REGULATORS

78L05 0.30  
78L12 0.30  
78L15 0.30  
7805 0.40  
7812 0.40  
7815 0.40  
7905 0.45  
7912 0.45  
7915 0.45  
7916 1.20  
LM309K 2.40  
LM317K 4.50  
LM338K 6.25

### DATA CONVERTERS

UPD7002 D1 4.28  
ZN425 D1 3.45  
ZN426 D1 3.00  
ZN427 D1 5.99  
ZN428 D1 4.75

### ZM429 D1 2.10

ZM432 D1 13.00  
ZN449 D1 2.55  
**CRYSTALS**  
1M 2.75  
1008M 2.75  
18432M 1.92  
24576M 2.00  
36864M 1.86  
4M 0.84  
6M 0.88  
8M 0.88  
98304 1.68  
196608 2.48

### OIL SOCKETS (TEXAS)

PINS TIN GOLD WW  
8 7 16 25  
14 10 28 35  
16 10 29 40  
18 13 33 50  
20 15 37 60  
22 17 38 65  
24 21 46 70  
28 24 55 80  
40 30 76 99

### ZIF SOCKETS (TEXTOL)

24 pin 5.75  
28 pin 8.20  
40 pin 9.75

### CMOS 4000

4000 0.10  
4001 0.10  
4002 0.12  
4006 0.42  
4007 0.14  
4008 0.32  
4009 0.24  
4010 0.24  
4011 0.10  
4012 0.16  
4013 0.20  
4014 0.40  
4015 0.36  
4016 0.20  
4017 0.32  
4018 0.36  
4019 0.36  
4020 0.36  
4021 0.40  
4022 0.40  
4023 0.13  
4024 0.32  
4025 0.13  
4026 0.74  
4027 0.20  
4028 0.32  
4031 0.94  
4033 0.86  
4034 0.94  
4035 0.38  
4040 0.38  
4041 0.36  
4042 0.34  
4043 0.36  
4044 0.36  
4045 1.35  
4046 0.42  
4047 0.70  
4048 0.36  
4049 0.23  
4050 0.23  
4051 0.38  
4052 0.44  
4053 0.44  
4054 0.85  
4055 0.85  
4060 0.39  
4063 0.85  
4066 0.24  
4068 0.14  
4069 0.14  
4070 0.13  
4071 0.13  
4072 0.13  
4073 0.14  
4075 0.13  
4076 0.43  
4077 0.13  
4078 0.15  
4081 0.13  
4082 0.13  
4085 0.50  
4086 0.44  
4093 0.20  
4502 0.46  
4507 0.32  
4508 0.96

### 4510 0.40

4511 0.41  
4512 0.40  
4514 0.98  
4515 0.96  
4516 0.40  
4518 0.40  
4519 0.27  
4520 0.40  
4521 0.90  
4522 0.52  
4526 0.52  
4527 0.52  
4528 0.41  
4532 0.72  
4541 0.50  
4543 0.50  
4553 1.57  
4555 0.35  
4556 0.35  
4585 0.75

### 74LS SERIES

00 0.11  
01 0.11  
02 0.11  
03 0.12  
04 0.12  
05 0.12  
08 0.12  
09 0.12  
10 0.12  
11 0.12  
12 0.12  
13 0.12  
14 0.25  
15 0.12  
20 0.12  
21 0.12  
22 0.12  
26 0.12  
27 0.12  
28 0.12  
30 0.12  
32 0.12  
33 0.12  
37 0.12  
40 0.12  
42 0.28  
47 0.35  
48 0.45  
49 0.12  
51 0.12  
54 0.12  
55 0.12  
73 0.18  
74 0.16  
75 0.18  
76A 0.17  
78A 0.18  
83A 0.38  
85 0.42  
86 0.12  
90 0.28  
91 0.60  
92 0.32  
93 0.22  
95B 0.40  
109A 0.27  
112A 0.20  
113A 0.20  
114A 0.22  
122 0.28  
123 0.36  
125A 0.24  
126A 0.25  
132 0.34  
136 0.25  
138 0.25  
139 0.27  
145 0.57  
148 0.70  
151 0.40  
153 0.40  
155 0.30  
156 0.35  
157 0.25  
158 0.30  
160A 0.32  
161A 0.35  
162A 0.35  
163A 0.35  
164 0.40  
165A 0.50  
166A 0.60  
173A 0.55  
174 0.40  
175 0.36  
181 0.90  
190 0.35  
191 0.35  
192 0.35

### 193 0.35

194A 0.35  
195A 0.35  
196 0.45  
197 0.45  
221 0.46  
240 0.55  
241 0.55  
242 0.55  
243 0.55  
244 0.55  
245 0.70  
248 0.55  
249 0.55  
251 0.30  
253 0.35  
257A 0.30  
258A 0.35  
259 0.55  
261 1.00  
266 0.20  
274 0.54  
279 0.30  
283 0.40  
290 0.39  
293 0.39  
365 0.27  
366 0.27  
367 0.27  
368 0.27  
373 0.62  
374 0.62  
375 0.35  
377 0.60  
378 0.80  
379 0.90  
386 0.35  
390 0.45  
393 0.45

### OIL JUMPERS

Single Ended 24"  
14 PIN 1.45  
16 PIN 1.65  
24 PIN 2.40  
40 PIN 3.80

### Double Ended

6" 12" 18"  
14 PIN 1.85 1.98 2.42  
16 PIN 2.05 2.15 2.68  
24 PIN 3.00 3.15 3.96  
40 PIN 4.65 4.90 6.18

### 25 WAY D-TYPE CONNECTORS

Male-Male 36" cable 12.00  
Male-Female 36" cable 12.00  
Male single ended 18" cable 4.95  
Female single ended 18" cable 3.95

### IOC CONNECTORS

Shrouded Headers (with ejectors) (Right Angle)  
PCB Mtg) 0.86  
14 PIN 1.22  
16 PIN 1.34  
20 PIN 1.46  
26 PIN 1.76  
34 PIN 2.06  
40 PIN 2.32  
50 PIN 2.35  
60 PIN 3.20

### IDC SOCKETS

Fitted with 36" cable  
10 PIN 1.40  
14 PIN 1.82  
16 PIN 2.10  
20 PIN 2.48  
26 PIN 3.24  
34 PIN 3.80  
40 PIN 4.90  
50 PIN 5.48  
60 PIN 6.38

### DATA BOOKS by Texas Instruments

Linear Control Circuits 4.00  
Voltage Regulators 4.50  
MOS Memory 3.95  
Interface Circuits 7.00  
TTL 5th Edition 8.50  
Bipolar Micro 4.50  
TTL Pocket Guide 3.50  
Linear Pocket Guide 2.50

**CARRIAGE** Orders up to £199 sent by 1st class post and £200+ by Securitor.  
**CHARGES** 0-£100 = £0.50, £100-199 = £1.25, £200+ = £5.00.  
**PRICES** All prices and carriage charges quoted are exclusive of VAT and are subject to change without notice.  
**QUANTITY DISCOUNTS** Available on most products. Please telephone for details.  
**OFFICIAL ORDERS** are welcome from Educational Establishments, Government Bodies and Public Companies.



**CREDIT ACCOUNTS** Are available subject to status. Payment strictly nett 30 days.

**CREDIT CARDS** Payment by credit cards is accepted on most products with no surcharge.

**OUT OF STOCK** Items out of stock will follow with £0.45 Carriage charge at our discretion, or a refund will be issued if requested.

**DELIVERY** All stock orders received up to 3.30pm are despatched the same day.

# MIDWICH COMPUTER COMPANY LIMITED

DEPT ET1, RICKINGHALL HOUSE, RICKINGHALL, SUFFOLK IP22 1HH  
TELEPHONE (0379) DISS 898751

01-452 1500

TECHNOMATIC LTD

01-450 6597

**BBC Micro Computer**  
Please phone for availability



BBC Model B £399 including VAT plus £8 carr.  
Model A to Model B Fitting charge £15  
Individual upgrades also available

**WORD PROCESSOR 'VIEW'**  
16K ROM £52  
**TELETEXT ADAPTOR**  
£195.00

**PRESTEL ADAPTOR**  
£90.00  
**2nd PROCESSOR 6502** £170  
**2nd PROCESSOR Z80** £290

**FLOPPY DISC INTERFACE**  
Incl. 1.2 operating system  
£95 + £20 installation

Phone or send for our BBC leaflet

**BBC FLOPPY DISC DRIVES**  
Single drive 5 1/4" 100K £235 + £6 carr.  
Dual drive 5 1/4" 800K £799 + £8 carr.

**BBC COMPATIBLE DRIVES**  
These are drives with TEAC FD50 mechanism and are complete with power supply  
**SINGLE:** 100K £190; 200K £260; 400K £340  
**DUAL:** 200K £360; 400K £490; 800K £610  
Drive Cables: Single £8 Dual £12

ACORN SOFT/BBC SOFT/GAMES PADDLES IN STOCK

OFFICIAL **BBC** DEALER

**CASSETTE RECORDER**

BBC Compatible Cassette Recorder with Counter and Remote Control  
£26.50 + £1.50 carr.  
Cassette Leads £3.50  
Computer Grade Cassette  
£0.50p each £4.50 for 10 + £1 carr.

**MONITORS**

MICROVITEC 1431 14" Colour Monitor.....£249 + £8 carr.  
MICROVITEC 2031 20" Colour Monitor.....£319 + £8 carr.  
KAGA 12" RGB Monitor.....£255 + £8 carr.  
Lead for KAGA RGB.....£10  
SANYO 12" Hi Res Green Monitor.....£99 + £6 carr.

**ACORN ATOM**

Basic Built £135 Expanded £175 (carr £3 per unit)  
Atom Disc Pack £299 + £6 carr  
3A 5V Regulated PSU £26 + £2 carr.  
Phone or send for our BBC Atom list.

**NEC PC 8023 BE-C**

Features include:  
80 cols 100CPS,  
Bi-Directional, Logic seeking,  
Proportional Spacing,  
Forward & Reverse Line  
Feed, Hi-Res and Block  
Graphics, International  
and Greek characters,  
Auto-Underline, Super & Sub  
Scripts, Friction & Tractor,  
2K Buffer, Cartridge Ribbon.



£345 + £8 carr.

**PRINTERS**

**SEIKOSHA GP 100A**

80 Cols 30 CPS  
Full ASCII e GRAPHICS  
10" Wide paper

Now only £180+ £6 carr.  
Ask for details on GP 250A

Parallel Printer lead for BBC/Atom to most printers £13.50  
Variety of interfaces, ribbons in stock  
2,000 fan fold sheets 9 1/2" x 11" £13.50 + £3 p & p

**EPSON RX80 and FX80**

RX80 100CPS 80 Col  
Tractor Feed FX80  
160CPS 80 Col  
F & T Feed  
Logic seeking, Bi-directional, Bit image printing, 9 x 9 Matrix, Auto Underline, Centronix 8, Bit Parallel interface as standard  
RX80 £298  
FX80 £438  
(£8 carr/printer)



**RUGBY ATOMIC CLOCK**

This Z80 micro controlled clock/calender receives coded time data from NPL Rugby. The clock never needs to be reset. The facilities include 8 independent alarms and for each alarm there is a choice of melody or alternatively these can be used for electrical switching. A separate timer allows recording of up to 240 lap times without interrupting the count. Expansion facilities provided. See July/August ETI for details. Complete Kit  
£145 + £2.00 p&p

**MICROTIMER**

6502 Based Programmeable clock timer with  
★ 224 switching times/week cycle  
★ 24 hour 7 day timer  
★ 4 independent switch outputs directly interfacing to thyristor/triacs  
★ 6 digit 7 seg. displays to indicate real time, ON/OFF and Reset times  
★ Output to drive day of week switch and status LEDS.  
Full details on request. Price for kit £57.00

**I.D. CONNECTORS**

(Speedblock Type)  
No of Header Recep- Edge  
ways Plug tacle Conn  
10 90p 90p 200p  
20 145p 125p 240p  
26 175p 150p 300p  
34 200p 160p 380p  
48 220p 190p 550p  
50 235p 200p 600p

**CONNECTOR SYSTEMS**

**JUMP LEADS**

4in Ribbon Cable with headers  
14 pin 16 pin 24 pin 40 pin  
1 end 145p 165p 240p 380p  
2 ends 210p 230p 345p 540p  
24in Ribbon Cable with sockets  
20 pin 26 pin 34 pin 40 pin  
1 end 160p 210p 270p 300p  
2 ends 290p 380p 490p 540p  
24in Ribbon Cable with D. Conn  
25 way Male 500p Female 550p

**AMPHENOL CONNECTORS**

36 way Solder Type Plug (centronix type) 550p  
36 way Solder Socket (centronix type) 550p  
36 way IDC Plug (centronix type) 500p  
24 way Solder Plug (IEEE type) 500p  
24 way Solder Socket 500p  
24 way IDC Plug 485p

**RIBBON CABLE (Grey)**

10 way 60p  
14 way 80p  
16 way 90p  
20 way 105p  
26 way 140p  
34 way 220p  
40 way 265p  
50 way 330p  
64 way 370p

**D-CONNECTORS**

9 way 15 way 25 way 37 way  
MALE  
Solder 90p 130p 160p 250p  
Angled 160p 230p 265p 425p  
FEMALE  
Solder 110p 160p 210p 350p  
Angled 175p 240p 310p 500p  
Hood 95p 95p 95p 125p

**RS232 CONNS (25 way D)**

24" Single end Male £5.50  
24" Single end Female £6.00  
24" Female-Female £11.00  
24" Male-Male £10.00  
24" Male-Female £11.50

**EURO CONNECTORS**

(Indirect Edge Conn)  
DIN STD Plug Skt 2x18 way  
41617 21 way 170p 170p 2x22 way  
41617 31 way 180p 180p 2x23 way  
41612 2 x32 way 250p 320p 2x25 way  
Angled 2x32 way 325p 375p 1x43 way  
41612 3x32 way 275p 380p 2x43 way  
Angled 3x32 way - 400p 2x50 way  
2x32 way zidc a + c - 525p 1x77 way  
(for 2x32 way specify a + b or a + c) \$100 Conn

**EDGE CONNECTORS**


0.1in 0.156in  
- 140p  
- 140p  
200p 170p  
210p -  
225p 220p  
280p -  
395p -  
-  
700p -  
- 600p

**DIL HEADERS**

older IDC type type  
14 pin 40p 100p  
16 pin 50p 110p  
24 pin 100p 150p  
40 pin 200p 225p

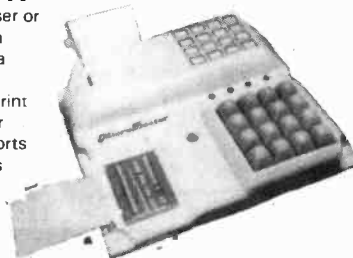**MICRODOCTOR**

This is not a logic analyser or an oscilloscope. It tests a microsystem and gives a printed reprint on RAM, ROM and I/O - it will print memory map, search for code, check dataline shorts and operates peripherals  
Microdoctor complete with PSU, Printer, probe cable and two configuration boards. £295.



**SOFTY II INTELLIGENT PROGRAMMER**

The complete micro processor development system for Engineers and Hobbyists. You can develop programs, debug, verify and commit to EPROMS or use in host computer by using softy as a romulator. Powerful editing facilities permit bytes, blocks of bytes changed, deleted or inserted and memory contents can be observed on ordinary TV. Accepts most +5v Eproms.  
Softy II complete with PSU, TV Lead and Romulator lead £169

**SPECIAL OFFER**

2114L 80p  
2716 L + 5v 250p  
2532 350p  
4116-2 80p  
4164-2 450p  
6116P-3 350p

**UV ERASERS**

UVIB up to 6 Eproms £47.50  
UVIT with Timer £60.00  
UV140 up to 14 Eproms £61.50  
UV141 with Timer £78.00  
(Carr £2/eraser)

All erasers are fitted with mains switches and safety interlocks

**'WIRELESS WORLD' PROJECTS**

Semiconductors inc. I.C., Transistors, Displays, Connectors and Sockets for most projects are stocked by us.

**BOOKS (No VAT p&p £1)**

CMOS Cook Book £7.75  
CRT Controller H/Book £7.95  
Programming the Z80 £11.50  
Z80 Microcomp. handbook £6.95  
Programming the 6502 £10.25  
6502 Assy. Lang. £12.10  
6502 Applications £10.20  
6502 Software Design £9.05  
6502 Games £10.52

Large selection of databooks, interfacing books, books on BBC, etc in stock. As for our list.

PLEASE SEND SAE FOR PRICE LIST



74S SERIES				74LS SERIES				74ALS SERIES				74ALS SERIES			
7400	11p	74221	55p	74LS251	35p	40244	180p	74LS500	11p	74LS563	140p	74LS500	11p	74LS563	140p
7401	11p	74251	55p	74LS252	35p	40245	180p	74LS501	11p	74LS564	140p	74LS501	11p	74LS564	140p
7402	11p	74259	100p	74LS256	150p	4018	45p	74LS502	11p	74LS565	140p	74LS502	11p	74LS565	140p
7403	12p	74285	45p	74LS257	35p	4019	25p	74LS503	12p	74LS566	140p	74LS503	12p	74LS566	140p
7404	12p	74273	120p	74LS258	55p	4020	48p	74LS504	12p	74LS567	140p	74LS504	12p	74LS567	140p
7405	15p	74278	100p	74LS259	55p	4021	40p	74LS505	12p	74LS568	140p	74LS505	12p	74LS568	140p
7406	18p	74278	100p	74LS280	20p	4022	45p	74LS506	12p	74LS569	140p	74LS506	12p	74LS569	140p
7407	18p	74279	40p	74LS281	130p	4023	13p	74LS507	12p	74LS570	140p	74LS507	12p	74LS570	140p
7408	14p	74283	50p	74LS282	130p	4024	32p	74LS508	12p	74LS571	140p	74LS508	12p	74LS571	140p
7409	14p	74284	160p	74LS283	40p	4025	13p	74LS509	12p	74LS572	140p	74LS509	12p	74LS572	140p
7410	14p	74285	160p	74LS284	30p	4026	80p	74LS510	12p	74LS573	140p	74LS510	12p	74LS573	140p
7411	14p	74286	160p	74LS285	30p	4027	20p	74LS511	12p	74LS574	140p	74LS511	12p	74LS574	140p
7412	14p	74287	160p	74LS286	30p	4028	20p	74LS512	12p	74LS575	140p	74LS512	12p	74LS575	140p
7413	14p	74288	160p	74LS287	30p	4029	45p	74LS513	12p	74LS576	140p	74LS513	12p	74LS576	140p
7414	14p	74289	160p	74LS288	30p	4030	125p	74LS514	12p	74LS577	140p	74LS514	12p	74LS577	140p
7415	14p	74290	160p	74LS289	30p	4031	80p	74LS515	12p	74LS578	140p	74LS515	12p	74LS578	140p
7416	14p	74291	160p	74LS290	30p	4032	80p	74LS516	12p	74LS579	140p	74LS516	12p	74LS579	140p
7417	14p	74292	160p	74LS291	30p	4033	125p	74LS517	12p	74LS580	140p	74LS517	12p	74LS580	140p
7418	14p	74293	160p	74LS292	30p	4034	45p	74LS518	12p	74LS581	140p	74LS518	12p	74LS581	140p
7419	14p	74294	160p	74LS293	30p	4035	45p	74LS519	12p	74LS582	140p	74LS519	12p	74LS582	140p
7420	14p	74295	160p	74LS294	30p	4036	275p	74LS520	12p	74LS583	140p	74LS520	12p	74LS583	140p
7421	14p	74296	160p	74LS295	30p	4037	110p	74LS521	12p	74LS584	140p	74LS521	12p	74LS584	140p
7422	20p	74370	100p	74LS296	30p	4038	110p	74LS522	12p	74LS585	140p	74LS522	12p	74LS585	140p
7423	20p	74390	75p	74LS297	30p	4039	290p	74LS523	12p	74LS586	140p	74LS523	12p	74LS586	140p
7424	20p	74393	90p	74LS298	30p	4040	40p	74LS524	12p	74LS587	140p	74LS524	12p	74LS587	140p
7425	18p	74393	90p	74LS299	30p	4041	40p	74LS525	12p	74LS588	140p	74LS525	12p	74LS588	140p
7426	18p	74393	90p	74LS300	30p	4042	40p	74LS526	12p	74LS589	140p	74LS526	12p	74LS589	140p
7427	18p	74393	90p	74LS301	30p	4043	40p	74LS527	12p	74LS590	140p	74LS527	12p	74LS590	140p
7428	18p	74393	90p	74LS302	30p	4044	40p	74LS528	12p	74LS591	140p	74LS528	12p	74LS591	140p
7429	18p	74393	90p	74LS303	30p	4045	40p	74LS529	12p	74LS592	140p	74LS529	12p	74LS592	140p
7430	14p	74393	90p	74LS304	30p	4046	40p	74LS530	12p	74LS593	140p	74LS530	12p	74LS593	140p
7431	14p	74393	90p	74LS305	30p	4047	45p	74LS531	12p	74LS594	140p	74LS531	12p	74LS594	140p
7432	14p	74393	90p	74LS306	30p	4048	45p	74LS532	12p	74LS595	140p	74LS532	12p	74LS595	140p
7433	22p	74502	11p	74LS307	30p	4049	45p	74LS533	12p	74LS596	140p	74LS533	12p	74LS596	140p
7434	22p	74502	11p	74LS308	30p	4050	45p	74LS534	12p	74LS597	140p	74LS534	12p	74LS597	140p
7435	22p	74502	11p	74LS309	30p	4051	45p	74LS535	12p	74LS598	140p	74LS535	12p	74LS598	140p
7436	22p	74502	11p	74LS310	30p	4052	45p	74LS536	12p	74LS599	140p	74LS536	12p	74LS599	140p
7437	22p	74502	11p	74LS311	30p	4053	45p	74LS537	12p	74LS600	140p	74LS537	12p	74LS600	140p
7438	22p	74502	11p	74LS312	30p	4054	45p	74LS538	12p	74LS601	140p	74LS538	12p	74LS601	140p
7439	25p	74502	11p	74LS313	30p	4055	45p	74LS539	12p	74LS602	140p	74LS539	12p	74LS602	140p
7440	25p	74502	11p	74LS314	30p	4056	45p	74LS540	12p	74LS603	140p	74LS540	12p	74LS603	140p
7441	55p	74502	11p	74LS315	30p	4057	45p	74LS541	12p	74LS604	140p	74LS541	12p	74LS604	140p
7442A	30p	74502	11p	74LS316	30p	4058	45p	74LS542	12p	74LS605	140p	74LS542	12p	74LS605	140p
7443	30p	74502	11p	74LS317	30p	4059	45p	74LS543	12p	74LS606	140p	74LS543	12p	74LS606	140p
7444	30p	74502	11p	74LS318	30p	4060	45p	74LS544	12p	74LS607	140p	74LS544	12p	74LS607	140p
7445	30p	74502	11p	74LS319	30p	4061	45p	74LS545	12p	74LS608	140p	74LS545	12p	74LS608	140p
7446A	50p	74502	11p	74LS320	30p	4062	45p	74LS546	12p	74LS609	140p	74LS546	12p	74LS609	140p
7447A	36p	74502	11p	74LS321	30p	4063	45p	74LS547	12p	74LS610	140p	74LS547	12p	74LS610	140p
7448	45p	74502	11p	74LS322	30p	4064	45p	74LS548	12p	74LS611	140p	74LS548	12p	74LS611	140p
7449	45p	74502	11p	74LS323	30p	4065	45p	74LS549	12p	74LS612	140p	74LS549	12p	74LS612	140p
7450	45p	74502	11p	74LS324	30p	4066	45p	74LS550	12p	74LS613	140p	74LS550	12p	74LS613	140p
7451	15p	74515	12p	74LS325	30p	4067	225p	74LS551	14p	74LS614	140p	74LS551	14p	74LS614	140p
7452	15p	74515	12p	74LS326	30p	4068	14p	74LS552	14p	74LS615	140p	74LS552	14p	74LS615	140p
7453	15p	74515	12p	74LS327	30p	4069	14p	74LS553	14p	74LS616	140p	74LS553	14p	74LS616	140p
7454	15p	74515	12p	74LS328	30p	4070	14p	74LS554	14p	74LS617	140p	74LS554	14p	74LS617	140p
7455	15p	74515	12p	74LS329	30p	4071	14p	74LS555	14p	74LS618	140p	74LS555	14p	74LS618	140p
7456	15p	74515	12p	74LS330	30p	4072	14p	74LS556	14p	74LS619	140p	74LS556	14p	74LS619	140p
7457	25p	74515	12p	74LS331	30p	4073	14p	74LS557	14p	74LS620	140p	74LS557	14p	74LS620	140p
7458	25p	74515	12p	74LS332	30p	4074	14p	74LS558	14p	74LS621	140p	74LS558	14p	74LS621	140p
7459	25p	74515	12p	74LS333	30p	4075	14p	74LS559	14p	74LS622	140p	74LS559	14p	74LS622	140p
7460	25p	74515	12p	74LS334	30p	4076	14p	74LS560	14p	74LS623	140p	74LS560	14p	74LS623	140p
7461	25p	74515	12p	74LS335	30p	4077	14p	74LS561	14p	74LS624	140p	74LS561	14p	74LS624	140p
7462	25p	74515	12p	74LS336	30p	4078	14p	74LS562	14p	74LS625	140p	74LS562	14p	74LS625	140p
7463	25p	74515	12p	74LS337	30p	4079	14p	74LS563	14p	74LS626	140p	74LS563	14p	74LS626	140p
7464	25p	74515	12p	74LS338	30p	4080	14p	74LS564	14p	74LS627	140p	74LS564	14p	74LS627	140p
7465	25p	74515	12p	74LS339	30p	4081	14p	74LS565	14p	74LS628	140p	74LS565	14p	74LS628	140p
7466	25p	74515	12p	74LS340	30p	4082	14p	74LS566	14p	74LS629	140p	74LS566	14p	74LS629	140p
7467	25p	74515	12p	74LS341	30p	4083	14p	74LS567	14p	74LS630	140p	74LS567	14p	74LS630	140p
7468	25p	74515	12p	74LS342	30p	4084	14p	74LS568	14p	74LS631	140p	74LS568	14p	74LS631	140p
7469	25p	74515	12p	74LS343	30p	4085	14p	74LS569	14p	74LS632	140p	74LS569	14p	74LS632	140p
7470	25p	74515	12p	74LS344	30p	4086	14p	74LS570	14p	74LS633	140p	74LS570	14p	74LS633	140p
7471	25p	74515	12p	74LS345	30p	4087	14p	74LS571	14p	74LS634	140p	74LS571	14p	74LS634	140p
7472	25p	74515	12p	74LS346	30p	4088	14p	74LS572	14p	74LS635	140p	74LS572	14p	74LS635	140p
7473	25p	74515	12p	74LS347	30p	4089	14p	74LS573	14p	74LS636	140p	74LS573	14p	74LS636	140p
7474	25p	74515	12p	74LS348	30p	4090	14p	74LS574	14p	74LS637	140p	74LS574	14p	74LS637	140p
7475	22p	74515	12p	74LS349	30p	4091	14p	74LS575	14p	74LS638	140p	74LS575	14p	74LS638	140p
7476	25p	74515	12p	74LS350	30p	4092	14p	74LS576</							

# COMPRESSOR/ LIMITER

When it comes to compressing those troublesome signals that are prone to overload, this ETI project really is the limit! Design by Ian Martin B.Sc.

Compressors and limiters have many uses in professional recording and broadcasting, and they can also be pretty useful to the amateur. Perhaps the single most important use is for overload protection: the limiter is set up so as to remain inactive until a signal occurs which would overload following circuits (perhaps a radio transmitter or power amplifier), at which point gain reduction cuts in and, without being very noticeable about it, the unit prevents blown fuses, gross distortion or worse.

The circuit described here has been designed to be capable of both the compressing and limiting actions — it all depends on the signal size you apply and the gains you set in the circuit. With the component values shown, the specification of this unit is very similar to devices currently in use in stereo radio broadcasting in the UK.

## On The Attack

In this circuit the attack has been made very fast indeed, the time constant being 220 microseconds: hence the time taken for the limiter to react fully to an

## HOW IT WORKS

The left and right channels of the unit are identical, so this description will be confined to the left-hand channel.

IC1 forms a buffer, and its gain is adjustable by PR1 so that it can be used to set the input sensitivity. The variable gain cell is made up from IC2 and IC7a and their associated components. The configuration used is slightly unusual: IC2 forms a conventional inverting amplifier, its gain being determined by  $R_{FB}/R_{IN}$  in the usual way. However, while  $R_{IN}$  is simply R2,  $R_{FB}$  is made up from R4 and IC7a which, as an operational transconductance amplifier, can be used as a current-controlled resistor. With the addition of a voltage-to-current converter to drive the control input of the LM13600, a complete VCA is formed which will produce a gain inversely proportional to the control voltage.

The first stage of the gain-control side chain is a full-wave rectifier made up from IC3a and IC6a. Q1 boosts the output current drive capability of the rectifier in order to produce a fast attack characteristic when charging C11.

From C11 onwards until the final voltage-to-current converters for the VCA, the two side chains are combined into one channel, the highest of the left or right input signals being registered on C11. In this way stereo ganging is achieved, and this prevents the stereo image from wandering from side to side during gain reduction (if the overload signal is

in one channel only). The adjustment of the decay time and limiting threshold for both left and right channels is achieved easily and equally by R32 and PR5. IC8b is used as a high impedance buffer for the control voltage held on C11, which is discharged by R31. The output of this buffer is fed to PR5, which controls the side chain gain and hence the limiting threshold.

The only problem with the particular VCA configuration chosen is that should the control voltage (and hence control current being fed to IC7a) fall to zero, the gain of the VCA will increase to the open-loop gain of IC2, probably resulting in the VCA output reaching one of the supply rails (as is usually the case when an IC amplifier loses its feedback). In order to prevent this from happening, the control voltage  $V_C$  is prevented from going below 0V5 by zener ZD1 and preset PR6. Thus the higher of either  $V_{MIN}$  or the output of PR5 is passed via D11 or D12 to the law-shaping amplifier IC8a.

The diode D13 and resistors R35, 36 are configured to make up for the voltage drop across D11 and D12, and maintain a tight compression ratio, typically 10:1. The output of the shaping amplifier provides a low source impedance to drive the voltage-to-current converter IC9a and Q3 (note that the left and right channels split again at this point).

TABLE 1

### Measured performance of the prototype.

Gain:	0 dB (adjustable)			
Bandwidth (3 dB points):	10 Hz and 30 kHz approximately			
Input impedance:	22k			
Output impedance:	100R			
Limiting threshold:	0 dB (adjustable)			
Compression ratio for signals exceeding the threshold:	10:1			
Crosstalk with non-speaking channel terminated with 600R (left-to-right or right-to-left):	100 Hz	1 kHz	10 kHz	20 kHz
	-70 dB	-70 dB	-68 dB	-65 dB
Noise with input terminated as above:	-70 dB			

(this is the gain required to make noise at the output peak to 0 dB on a standard broadcast peak program meter, ie this is the peak noise. Should a measurement be made with an RMS reading meter, this measurement may improve by as much as 6 dB).

Control voltage breakthrough onto non-speaking channel with 20 dB of gain reduction occurring on the other channel:	100 Hz	1 kHz
	-68 dB	-68 dB

### Tracking between channels during gain reduction:

better than 0.3 dB

### Distortion at 1 kHz:

Input	Output	Distortion
-8 dB	-8 dB	-66 dB
0 dB	-1 dB	-60 dB
+10 dB	0 dB	-58 dB

### Distortion at 100 Hz:

Input	Output	Distortion
-8 dB	-8 dB	-58 dB
0 dB	-1 dB	-45 dB
+10 dB	0 dB	-38 dB

NB. These figures for 100 Hz distortion were measured with a recovery time constant of 100 milliseconds (total recovery time approximately 220 milliseconds), hence a certain amount of distortion due to the compression of individual waveforms is to be expected. Increasing the recovery time constant as in the final design will improve the low frequency distortion measurements, until for long recovery times (greater than 3 seconds) they will approach the values obtained for 1 kHz.

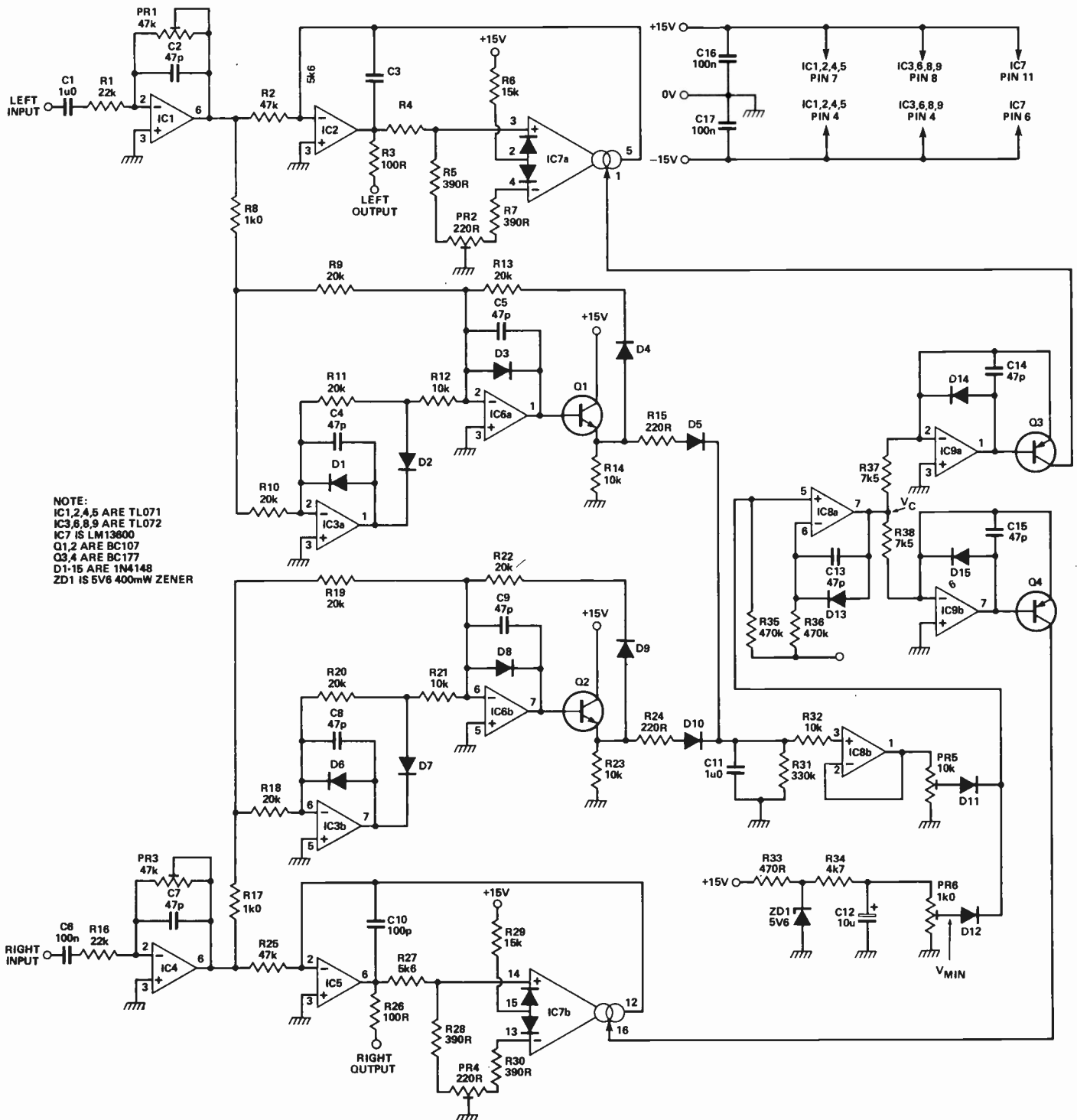


Fig. 1 Circuit diagram of the compressor/limiter.

overload above the limiting threshold is approximately 500 microseconds. The decay time was chosen to be 330 milliseconds; hence full recovery takes place approximately 700 milliseconds after the overload has been removed from the input. This recovery time was chosen after much subjective assessment, and is the fastest possible without undue distortion of low frequencies (this being a common problem in all

compressor/limiters). However, as this is a simple one-resistor adjustment it is easy to experiment and find the best compromise for different uses.

### Shaping Up

The need for the shaping amplifier built around IC8a arises because the side chain is, like most professional designs, an open loop system deriving its input from the incoming programme material and

not from the VCA output. This has the advantage that the limiting threshold and other dynamic characteristics may be altered easily and, if desired, other functions may be included. For example, de-essing could be implemented, where a treble boost in the side chain would lead to the gain reduction of high-energy, high-frequency sounds such as sibilants. It would also be possible to build a feedforward or overshoot limiter, by including a suitable delay



# PROJECT: Compressor/limiter

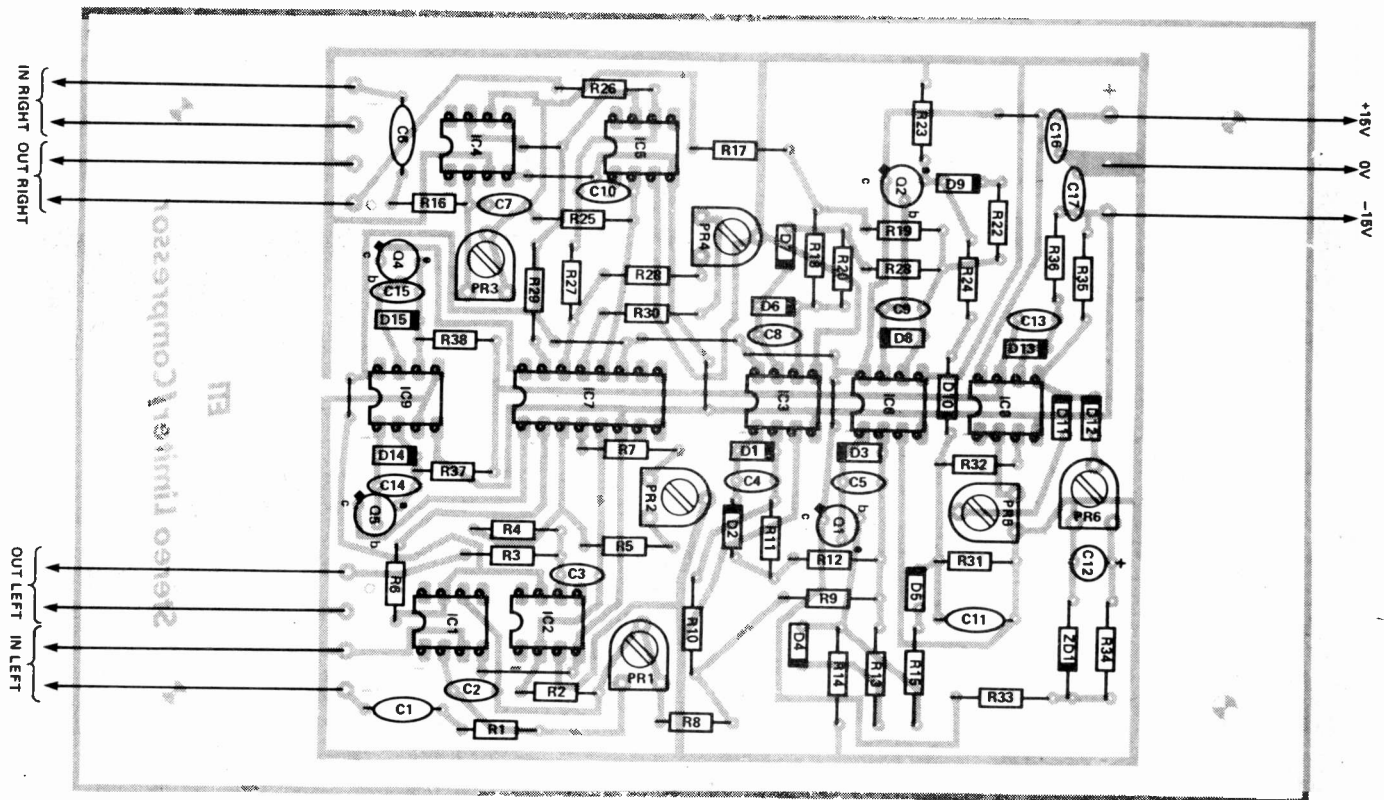


Fig. 2 Component overlay for the unit.

line in the main chain before the VCA. In this way gain reduction would take place before the programme material reached the VCA via the delay line and even the sharpest transient would be prevented from exceeding the limiting threshold at the output. However, in most applications this is not necessary, except in cases such as disc-cutting or radio broadcasting where an overload of even the shortest duration would have dire results.

The setting up procedure is very simple indeed. PR6 should be adjusted so that  $V_c$  is held at 0V5 with no input signal. PR1 and PR3 should then be adjusted to give the required gain from each channel (usually 0 dB). That concludes the static setting-up, except for PR2 and PR4 which should be adjusted for zero offset at the output of the VCA. This ensures minimal control voltage breakthrough onto the audio output during gain reduction. To set the compression

threshold, a high level signal (for example, +10 dB) should be applied to the input, and PR5 adjusted to give 0 dB at the limiter output.

If the above sequence is followed, the limiter will act as a normal unity-gain amplifier for all signals below 0 dB, and will reduce the gain of all signals above this threshold such that the output at no time exceeds 0 dB. Should the limiting threshold need to be reduced to, say, -10 dB to be more compatible with domestic equipment, then all that is required is an increase in the gain of the side channel by that amount. This is easily achieved by increasing R13 and R22 from 20k to, say, 47k. Should an indication of gain reduction be required, this is easily provided by buffering off  $V_c$ , the control voltage, by 1k0 or so to prevent any fault on the metering equipment affecting the operation of the limiter (for my own unit this metering equipment consists of a simple bargraph driver and LEDs).

## PARTS LIST

### Resistors (all $\frac{1}{4}$ W, 5%)

R1,16	22k
R2,25	47k
R3,26	100R
R4,27	5k6
R5,7,28,30	390R
R6,29	15k
R8,17	1k0
R9-11,13,	
18-20,22	20k
R12,14,21,	
23,32	10k
R15,24	220R
R31	330k
R33	470R
R34	4k7
R35,36	470k
R37,38	7k5

### Potentiometers

PR1,3	47k miniature horizontal preset
PR2,4	220R miniature horizontal preset

PR5	10k miniature horizontal preset
PR6	1k0 miniature horizontal preset

### Capacitors

C1,6,11	1u0 polycarbonate
C2,4,5,7-9,	
13-15	47pF ceramic
C3,10	100pF ceramic
C12	10uF 16 V tantalum
C16,17	100nF polycarbonate or ceramic

### Semiconductors

IC1,2,4,5	TL071
IC3,6,8,9	TL072
IC7	LM13600
Q1,2	BC107
Q3,4	BC177
D1-15	1N4148
ZD1	5V6 400 mW zener

### Miscellaneous

PCB (see Buylines); screened cable etc.

## BUYLINES

Although the design of this project results in top-notch performance, it uses components that are readily available and you should be able to find everything in the adverts in this issue. The PCB can be purchased from us using the order form on page 87.

# The Logic Probes

## Spend Less

## Test More



### LP-1 Logic Probe

The LP-1 has a minimum detachable pulse width of 50 nanoseconds and maximum input frequency of 10MHz. This 100 K ohm probe is an inexpensive workhorse for any shop, lab or field service tool kit. It detects high-speed pulse trains or one-shot events and stores pulse or level transistions, replacing separate level detectors, pulse detectors, pulse stretchers and pulse memory devices.

All for less than the price of a DVM

**£31.00\***

Model LP 3 illustrated



### LP-2 Logic Probe

The LP-2 performs the same basic functions as the LP-1, but, for slower-speed circuits and without pulse memory capability. Handling a minimum pulse width of 300 nanoseconds, this 300 K ohm probe is the economical way to test circuits up to 1.5 MHz. It detects pulse trains or single-shot events in TTL, DTL, HTL and CMOS circuits,


replacing separate pulse detectors, pulse stretchers and mode state analysers.

(Available in kit form LPK-1 £13.25)

**£18.00\***

Model LP 3 illustrated

\*price excluding P.&P and 15% VAT

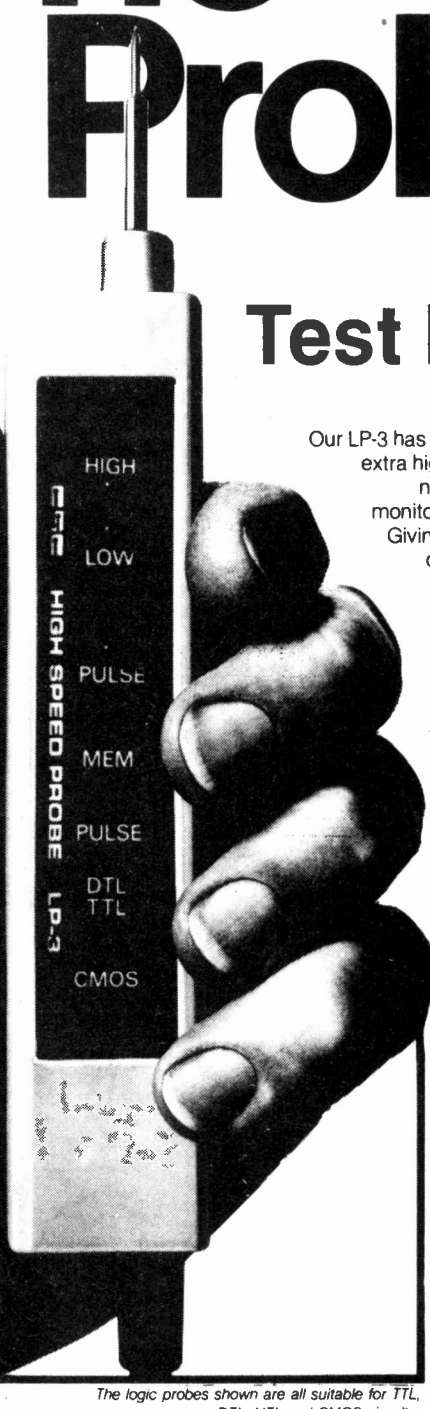

The logic probes shown are all suitable for TTL, DTL, HTL and CMOS circuits.

### LP-3 Logic Probe

Our LP-3 has all the features of the LP-1 plus extra high speed. It captures pulses as narrow as 10 nanoseconds, and monitors pulse trains to over 50 MHz. Giving you the essential capabilities of a high-quality memory scope at 1/1000th the cost.

LP-3 captures one shot or low-rep-events all-but-impossible to detect any other way.

All without the weight, bulk, inconvenience and power consumption of conventional methods.

**£49.00\***

Model LP 3 illustrated

### The New Pulser DP-1


The Digital Pulser: another new idea from G.S.C. The DP-1 registers the polarity of any pin, pad or component and then, when you touch the 'PULSE' button, delivers a single no-bounce pulse to swing the logic state the other way. Or if you hold the button down for more than a second, the DP-1 shoots out pulse after pulse at 1000 Hz.

The single LED blinks for each single pulse, or glows during a pulse train. If your circuit is a very fast one, you can open the clock line and take it through its function step by step, at single pulse rate or at 100 per second. Clever! And at a very reasonable price.

**£51.00\***

Model LP 3 illustrated

**GLOBAL SPECIALTIES CORPORATION**

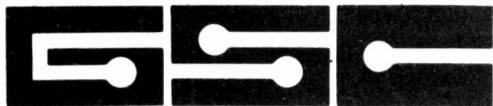

G.S.C. (UK) Limited, Dept. 9II  
Unit 1, Shire Hill Industrial Estate,  
Saffron Walden, Essex CB11 3AQ.  
Telephone: Saffron Walden (0799) 21682.  
Telex: 817477.

G.S.C. (UK) Limited, Dept. 9II, Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.

Prices include P.&P. and 15% VAT

LP-1	£37.38	Qty.	LP-2	£22.42	Qty.	LP-3	£58.08	Qty.	DP-1	£60.95	Qty.	LPK-1	£16.39	Qty.
------	--------	------	------	--------	------	------	--------	------	------	--------	------	-------	--------	------

Name \_\_\_\_\_ Address \_\_\_\_\_

I enclose Cheque/P.O. for £ \_\_\_\_\_ or debit my Barclaycard/Access/  
American Express card no. \_\_\_\_\_ exp. date \_\_\_\_\_

**FOR IMMEDIATE ACTION** — The G.S.C. 24 hour, 5 day a week service.


Telephone (0799) 21682 and give us your Barclaycard, Access, American Express  
number and your order will be in the post immediately.

For **FREE**  
catalogue  
tick box
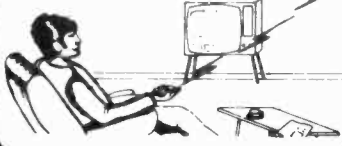
### HOME LIGHTING KITS

These kits contain all necessary components and full instructions & are designed to replace a standard wall switch and control up to 300w. of lighting.

- TDR300K Remote Control Dimmer **£14.30**
- MK6 Transmitter for above **£ 4.20**
- TD300K Touchdimmer **£ 7.00**
- TDE/K Extension kit for 2-way switching for TD300K **£ 2.00**
- LD300K Rotary Controlled Dimmer **£ 3.50**



### HOME CONTROL CENTRE

This New Remote Control Kit enables you to control up to 16 different appliances anywhere in the house from the comfort of your armchair. The transmitter injects coded pulses into the mains wiring which are received by receiver modules connected to the same mains supply and used to switch on the appliance addressed. Receivers are addressed by means of a 16-way keyboard, followed by an on or off command. Since pushing buttons can become rather boring, the transmitter also includes a computer interface so you can programme your favourite micro to switch lights, heating, electric blanket, make your coffee in the morning, etc., without rewiring your house. JUST THINK OF THE POSSIBILITIES. THE KIT includes all PCBs and components for one transmitter and two receivers, plus a drilled box for the transmitter. **£42.00**

Additional Receivers XK111 **£10.00**

### ELECTRONIC LOCK KIT XK101

This KIT contains a purpose designed lock IC, 10-way keyboard, PCBs and all components to construct a Digital Lock, requiring a 4-key sequence to open and providing over 5000 different combinations. The open sequence may be easily changed by means of a pre-wired plug. Size: 7 x 6 x 3 cms. Supply: 5V to 15 V d.c. at 40uA. Output: 750mA max. Hundreds of uses for doors and garages, car anti-theft device, electronic equipment, etc. Will drive most relays direct. Full instructions supplied. **ONLY £10.50**

Electric lock mechanism for use with latch locks and above kit **£13.50**

### THE MULTI-PURPOSE TIMER HAS ARRIVED

Now you can run your central heating, lighting, hi-fi system and lots more with just one programmable timer. At your selection it is designed to control four mains outputs independently, switching on and off at pre-set times over a 7 day cycle, e.g. to control your central heating (including different switching times for weekends), just connect it to your system programme and set it and forget it—the clock will do the rest.

#### FEATURES INCLUDE:-

- 0.5" LED 12 hour display.
- Day of week, am/pm and output status indicators.
- 4 zero voltage switched mains outputs.
- 50/60Hz mains operation.
- Battery backup saves stored programmes and continues time keeping during power failures. (Battery not supplied).
- Display blanking during power failure to conserve battery power.
- 18 programme time sets.
- Powerful "Everyday" function enabling output to switch every day but use only one time set.
- Useful "sleep" function—turns on output for one hour.
- Direct switch control enabling output to be turned on immediately or after a specified time interval.
- 20 function keypad for programme entry.
- Programme verification at the touch of a button.

(Kit includes all components, PCB, assembly and programming instructions). **ORDER AS CT5000**

Have you got our **FREE ORANGE CATALOGUE** yet?

**NO! Send S.A.E. 6" x 9" TODAY!!**

It's packed with details of all our **KITS** plus large range of **SEMICONDUCTORS** including CMOS, LS TTL, linear, microprocessors and memories; full range of LEDs, capacitors, resistors, hardware, relays, switches etc. We also stock VERO and Antex products as well as books from Texas Instruments, Babani and Elektor. **ALL AT VERY COMPETITIVE PRICES.**

**ORDERING IS EVEN EASIER — JUST RING THE NUMBER YOU CAN'T FORGET FOR PRICES YOU CAN'T RESIST.**

**5-6-7 8-9-10**

and give us your Access or Barclaycard No. or write enclosing cheque or postal order. Official orders accepted from schools, etc.

Answering service evngs & weekends

### MINI KITS

**MK1 TEMPERATURE CONTROLLER/THERMOSTAT**  
Uses LM3911 IC to sense temperature (80°C max.) and triac to switch heater. 1KW **£4.00**

**MK2 Solid State Relay**  
Ideal for switching motors, lights, heaters, etc. from logic. Opto-isolated with zero voltage switching. Supplied without triac. **£2.80**

**MK3 BAR/DOT DISPLAY**  
Displays an analogue voltage on a linear 10 element LED display as a bar or single dot. Ideal for thermometers, level indicators, etc. May be stacked to obtain 20 to 100 element displays. Requires 5-20V supply. **£4.50**

**MK4 PROPORTIONAL TEMPERATURE CONTROLLER**  
Based on the SL441 zero voltage switch, this kit may be wired to form a "burst fire" power controller, enabling the temperature of an enclosure to be maintained to within 0.5°C. Max. load 3KW. **£5.55**

**MK5 MAINS TIMER**  
Based on the ZN1034E Timer IC this kit will switch a mains load on (or off) for a preset time from 20 mins. to 35 hrs. Longer or shorter periods may be realised by minor component changes. Max. load 1KW. **£5.00**

### 3-NOTE DOOR CHIME

Based on the SAB0600 IC the kit is supplied with all components, including loudspeaker, printed circuit board, a pre-drilled box (95 x 71 x 35mm) and full instructions. Requires only a PP3 9V battery and push-switch to complete. **AN IDEAL PROJECT FOR BEGINNERS.** Order as XK102 **£5.00**

### XK113 MW RADIO KIT

Based on ZN414 IC, kit includes PCB, wound aerial and crystal earpiece and all components to make a sensitive miniature radio. Size: 5.5 x 2.7 x 2cms. Requires PP3 9V battery. **IDEAL FOR BEGINNERS.** **£5.00**

### COMPONENT PACKS

- PACK 1** 650 Resistors 47 ohm to 10 Mohm — 10 per value **£4.00**
- PACK 2** 40 x 16V Electrolytic Capacitors 10µF to 1000µF — 5 per value **£3.25**
- PACK 3** 60 Polyester Capacitors 0.01 to 1µF/250V — 5 per value **£5.55**
- PACK 4** 45 Sub-miniature Presets 100 ohm to 1 Mohm — 5 per value **£2.90**
- PACK 5** 30 Low Profile IC Sockets 8, 14 and 16 — pin — 10 of each **£2.40**
- PACK 6** 25 Red LEDs (5mm dia.) **£1.25**

## THE JUPITER ACE MICROCOMPUTER


**NOW available in stock**

uses FORTH which executes about 10 times faster and requires less program memory than a comparable program using basic. Features 8K ROM, 3K RAM, built in speaker, 40 key keyboard and a 32 x 24 line-flicker free display on TV. Comes supplied complete with leads, mains adaptor, a comprehensive easy-to-follow manual on Forth programming + **FREE** cassette containing 5 sample programs. **£75.00** (+ £2.00 carriage + VAT)

- JUPITER ACE SOFTWARE** **£5.00**
- J3 SPACE INVADERS** **£3.90**
- J7 ZAP 'EM (ASTEROIDS) DUCK** **£3.90**
- J4 SWAMP MONSTERS** **£3.90**
- SHOOT & MINEFIELD (3 programs)** **£5.20**
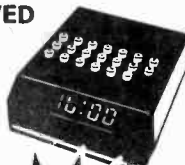
### LCD 3 1/2 DIGIT MULTIMETER

16 ranges including DC voltage (200 mv-1000v) and AC voltage, DC current (200 mA-10A) and resistance (0-2 M) + NPN & PNP transistor gain and diode check. Input impedance 10M. Size 155 x 88 x 31mm. Requires PP39V battery. **£29.00**  
Test leads included.



**NOW ONLY £39 WITH SO MANY EXTRA FEATURES. OPTIONAL BLACK PLASTIC CASE. READY DRILLED. £2.50**

### REMOTE CONTROL KITS

- MK6 SIMPLE INFRA RED TRANSMITTER**  
Pulsed infra red source complete with hand-held plastic box. Requires a 9V battery. **£4.20**
- MK7 INFRA RED RECEIVER**  
Single channel, range approx. 20ft. Mains powered with a triac output to switch loads up to 500W at 240V ac. **£9.00**
- MK8 CODED INFRA RED TRANSMITTER**  
Based on the SL490, the kit includes all components to make a coded transmitter and only requires a 9V (PP3) battery and keyboard. 8 x 2 x 1.3cms **£5.90**
- MK10 16-WAY KEYBOARD**  
For use with MK8 and MK18 to generate 16 different codes for decoding by the ML928 or ML926 receiver (MK12) kit. **£5.40**
- MK11 10-Channel + 3 Analogue a/p IR Receiver**  
Based on ML922 decoder IC. Functions include on/standby output, toggle, control of volume, tone and lamp brightness. Includes its own mains supply. **£12.00**
- MK12 16-CHANNEL IR RECEIVER**  
For use with MK8 kit with 16 on/off outputs, which with further interface circuitry, such as relays or triacs, will switch up to 16 items of equipment on or off remotely. Latched or momentary outputs — please specify when ordering. Includes its own mains supply. **£11.95**
- MK13 11-WAY KEYBOARD** For use with MK8, MK18 and MK11 kits. **£4.35**
- MK16 Mains Powered IR Transmitter**  
Mains powered for continuous operation — single channel, for applications such as burglar alarms, automatic door openers, etc. Range approx. 6 ft. **£2.50**
- MK17 12V d.c. IR RECEIVER**  
For use with MK6 or MK16. Relay output with DP 3 Amp change-over contacts, may be used as latched, momentary or "break beam" receiver. Operates from 6-13V d.c. **£9.50**
- MK18 HIGH POWER IR TRANSMITTER**  
Similar to MK8 but with range of approx. 60ft. **£6.20**
- Ancillary Kits:** MK2 Solid State Relay Opto-isolated with zero voltage switching. No. triac supplied. **£2.80**
- MK15 DUAL LATCHED SOLID STATE RELAY**  
Comprises 2 x solid state relays and latch for use with momentary version of the MK12. 2 output triacs required (not supplied). **£4.50**

### 24 HOUR CLOCK/APPLIANCE TIMER KIT

Switches any appliance up to 1kW on and off at present times once per day. Kit contains: AY-5-1230 IC, 0.5" LED display, mains supply, display drivers, switches, LEDs, triacs, PCBs and full instructions.



- CT1000K Basic Kit **£14.90**
- CT1000K with white box (56/131 x 71mm) **£17.40**
- (Ready Built) **£22.50**

Add 65p postage & packing + 15% VAT to total Overseas Customers; Add £2.50 (Europe), £6.00 (elsewhere) for p&p Send S.A.E. for further **STOCK DETAILS.** Goods by return subject to availability.

**OPEN** 9am to 5pm (Mon to Fri) 10am to 4pm (Sat)




For a detailed booklet on remote control — send us 30p and S.A.E. (6" x 9") today. **ALL PRICES EXCLUDE VAT**

## FAST SERVICE - TOP QUALITY - LOW LOW PRICES

No circuit is complete without a call to —

# ETI ELECTRONICS

11 Boston Road London W7 3SJ

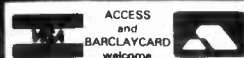


TEL: 01-567 8910 ORDERS 01-579 9794 ENQUIRIES 01-579 2842 TECHNICAL AFTER 3PM

Step-by-step fully illustrated assembly and fitting instructions are included together with circuit descriptions. Highest quality components are used throughout.

# Sparkrite


BRANDLEADING ELECTRONICS

## NOW AVAILABLE IN KIT FORM

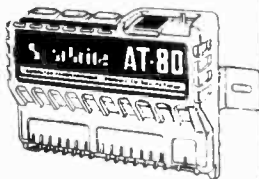

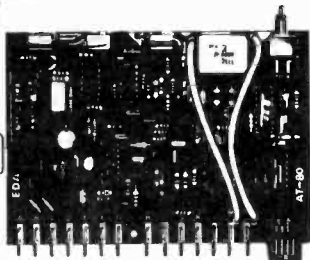
### AT-80 Electronic Car Security System

- Arms doors, boot, bonnet and has security loop to protect fog/spot lamps, radio/tape, CB equipment
- Programmable personal code entry system
- Armed and disarmed from outside vehicle using a special magnetic key fob against a windscreen sensor pad adhered to the inside of the screen
- Fits all 12V neg earth vehicles
- Over 250 components to assemble


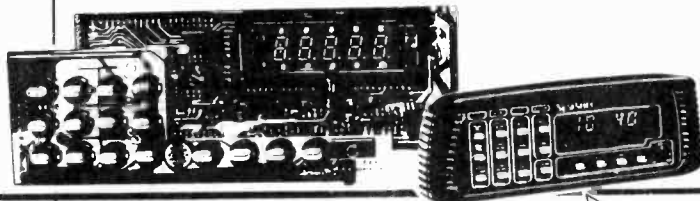
### VOYAGER Car Drive Computer

- A most sophisticated accessory
- Utilises a single chip mask programmed microprocessor incorporating a unique programme designed by EDA Sparkrite Ltd.
- Affords 12 functions centred on Fuel, Speed, Distance and Time
- Visual and Audible alarms warning of Excess Speed, Frost/Ice, Lights-left-on
- Facility to operate LOG and TRIP functions independently or synchronously
- Large 10mm high 400ft-L fluorescent display with auto intensity
- Unique speed and fuel transducers giving a programmed accuracy of + or - 1%
- Large LOG & TRIP memories 2,000 miles, 180 gallons, 100 hours
- Full Imperial and Metric calibrations
- Over 300 components to assemble
- A real challenge for the electronics enthusiast!





### SX1000 Electronic Ignition

- Inductive Discharge
- Extended coil energy storage circuit
- Contact breaker driven
- Three position changeover switch
- Over 65 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg. earth vehicles

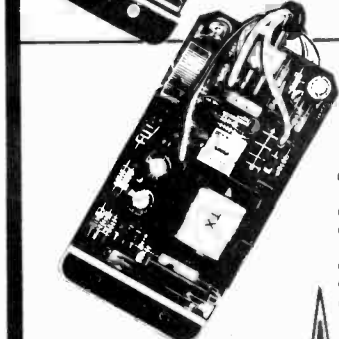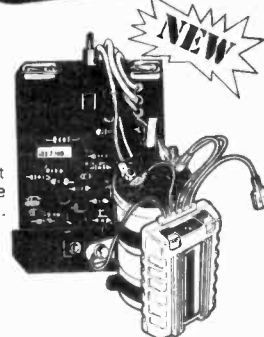
### TX1002 Electronic Ignition

- Contactless or contact triggered
- Extended coil energy storage circuit
- Inductive Discharge
- Three position changeover switch
- Distributor triggerhead adaptors included
- Die cast weatherproof case
- Clip-to-coil or remote mounting facility
- Fits majority of 4 & 6 cyl. 12V. neg. earth vehicles
- Over 145 components to assemble


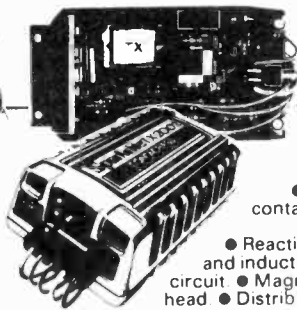
### SX2000 Electronic Ignition

- The brandleading system on the market today
- Unique Reactive Discharge
- Combined Inductive and Capacitive Discharge
- Contact breaker driven
- Three position changeover switch
- Over 130 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg. earth vehicles




### TX2002 Electronic Ignition

- The ultimate system
- Switchable contactless
- Three position switch with Auxiliary back-up inductive circuit
- Reactive Discharge. Combined capacitive and inductive
- Extended coil energy storage circuit
- Magnetic contactless distributor triggerhead
- Distributor triggerhead adaptors included
- Can also be triggered by existing contact breakers
- Die cast waterproof case with clip-to-coil fitting
- Fits majority of 4 and 6 cylinder 12v neg. earth vehicles
- Over 150 components to assemble

All SPARKRITE products and designs are fully covered by one or more World Patents

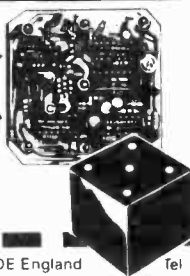**SPECIAL OFFER**  
 "FREE" MAGIDICE KIT WITH ALL ORDERS OVER £45.00



### MAGIDICE Electronic Dice

- Not an auto item but great fun for the family
- Total random selection
- Triggered by waving of hand over dice
- Bleeps and flashes during a 4 second tumble sequence
- Throw displayed for 10 seconds
- Auto display of last throw 1 second in 5
- Muting and Off switch on base
- Hours of continuous use from PP7 battery
- Over 100 components to assemble

SPARKRITE 82 Bath Street, Walsall, West Midlands, WS1 3DE England

tel (0922) 614791 Allow 28 days for delivery

	SELF ASSEMBLY KIT
SX 1000	£12.95
SX 2000	£19.95
TX 1002	£22.95
TX 2002	£32.95
AT 80	£32.95
VOYAGER	£64.95
MAGIDICE	£9.95

PRICES INC VAT. POSTAGE & PACKING

NAME \_\_\_\_\_ ETI/5/83  
 ADDRESS \_\_\_\_\_

I ENCLOSE CHEQUE(S)/POSTAL ORDERS FOR

£ \_\_\_\_\_ KIT REF \_\_\_\_\_

CHEQUE NO \_\_\_\_\_



BRANDLEADING BRITISH ELECTRONICS

CUT OUT THE COUPON NOW!



# BALANCED INPUT PREAMP

This versatile little preamp has a host of applications in the audio-and-beyond range, not the least of which would be as a balanced mike preamp. Design by David Tilbrook.

Many transducers require a balanced or differential preamplifier rather than the simpler single input unbalanced type. Balanced microphones, for example, require a balanced preamplifier to ensure minimal susceptibility to extraneous noise sources. The concept in the balanced approach is fairly simple: the microphone, for example, is connected to the balanced preamp using three wires instead of two. Two of these wires carry signals and the other is a ground connection. The balanced source, in this case a microphone, generates a signal voltage on the two signal wires such that one of the signals is 180 degrees out of phase with the other. The two active lines are twisted together with the earth line, or a two-wire shielded cable is used to connect the mike to the preamplifier.

In this way any external noise or hum source will affect both inputs equally, producing a signal that is in phase on both of the signal wires. Such a signal is called a *common mode* signal. The balanced preamplifier however, is configured in such a way as to amplify only a differential signal. The preamp produces an output signal that is proportional to the

difference between its two inputs. Since the signal is generated out of phase, it is amplified. The noise source, however, is a common signal and is the same in both input wires. The difference between the noise signals on each of the input wires is therefore zero, and is not amplified. With this technique small signals can be sent over long lines, an otherwise impossible task due to the susceptibility of these lines to mains hum in particular.

## A Transformation

In audio the most common method employed to implement a balanced line is with transformers. The basic approach is shown in Fig. 1. The source may be a microphone or a small preamplifier inside the microphone, or simply the output from a mixer or other electronic device. This is connected to the input of a balancing transformer that is wound to represent the correct load to the driving stage. The output of this transformer consists usually of a bifilar-wound secondary connected as shown in Fig. 1. A similar transformer is used at the other end of the line to convert the

differential signal back into one that can be amplified by the single input preamp.

This technique has the advantage that the signal earth of the source need not be connected to that of the preamplifier. This can be a very useful feature at times, particularly when large numbers of cables are connected together at a common point such as at a mixing console. The ability to isolate the input earths of the various inputs enables complete freedom from hum loops, which otherwise can become almost impossible to remove.

Transformers have disadvantages, however. First, good ones are expensive as they must be carefully wound and shielded from external hum fields. Since the transformer is a coil of wire, wound specifically for good response over the complete audio spectrum, they are particularly susceptible to magnetic fields produced by power transformers and so on. The problems associated with isolating the transformers from power supply hum fields can be very real, if not impossible in some instances.

## SPECIFICATIONS

Frequency response (10k load):	12 Hz — 60 kHz $\pm$ 0.1 dB
THD (at 5 V RMS output):	<0.007% at 100 Hz <0.006% at 1 kHz <0.012% at 10 kHz
Distortion figures can be expected to decrease further at more realistic signal levels but become difficult to measure.	
Total equivalent input noise: (20 kHz bandwidth)	-124 dB (approx)
Input impedance:	Nominally 560 ohms to ground from each input.
Output impedance:	Nominally 260 ohms.
Common mode rejection ratio:	Depends on calibration but easily adjusted to 80 dB.

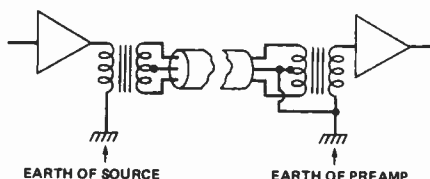


Fig. 1 Balanced line with transformer coupling.

It is often said that a transformer's ability to reject a common mode signal is inferior to that of a balanced preamplifier such as the one to be described in this project. Although this is true it is largely irrelevant, since the limit to common mode rejection is usually set by the shielded cable used to connect the input devices. Even the best quality cables seldom allow common mode rejections greatly in excess of 60 dB, a figure which is easily surpassed by most input transformers. The main advantage of differential preamps over transformers is cost and relative lack of susceptibility to hum fields. This makes it substantially easier to mount the preamp within the equipment to avoid degradation of

the signal-to-noise ratio by hum pickup. Another advantage of the preamp over transformers is that even the best transformers generate significant amounts of harmonic distortion in comparison to distortion figures easily obtained with an op-amp based balanced design.

## Construction

Construction of the unit is straightforward if the ETI PCB is used, since all components are mounted on the board. The usual precautions should be taken. The circuit employs several electrolytic capacitors so be certain these and the diodes and ICs are inserted with the correct orientation. The circuit is shown to run from a nominal  $\pm 20$  V supply. This ensures a clean

$\pm 15$  V supply to the op-amps giving the circuit good headroom. If this voltage is not available, however, the circuit will run perfectly well on a lower supply voltage. If the supply is clean regulated DC the on-board zeners can be eliminated. If not, replace them with a lower voltage type to suit the supply voltage.

Close tolerance resistors (1% or 2%) are specified for R6, 7, 8 and 9 so that any DC imbalance between the input stages, IC1 and IC2, can be balanced out by PR1.

It is a good idea to use low noise metal oxide resistors for the input resistors, R3 and R4, to get good noise performance. They cost little more than standard carbon deposition types. Indeed, metal oxide resistors could well be used

## DESIGN THEORY

The differential input needed is easy to implement with the help of operational amplifiers, since these have inverting and non-inverting inputs already. The simplest circuit that could be used and one that is adequate with microphones is shown in Fig. 2. This circuit is the standard differential op-amp circuit and offers good performance with most balanced sources. The resistor from the non-inverting input to ground is made the same value as the feedback resistor. In this way the gain of the stage is determined by the ratio of the resistors R2/R1. With the inverting input grounded, the gain of the op-amp is given by the standard formula

$$(R2 + R1)/R1.$$

In this case, however, the input resistor in series with the non-inverting input and the resistor from this input to ground form a potential divider and attenuate the signal by an amount given by:

$$V_i = V (R2/(R1 + R2))$$

So the total gain of the stage at the non-inverting input is

$$((R2 + R1)/R1)(R2/(R1 + R2))$$

or R2/R1, which is the same as the inverting input.

This circuit, however, has the disadvantage that the impedance to earth from each of the two inputs is very different. The impedance at the non-inverting input can usually be regarded as approximated by the series combination of the two resistors, ie R1 + R2. The impedance at the inverting input is simply that of the input resistor, since the inverting input is a virtual earth once feedback is applied in this way. This does not bother most balanced sources, since a true balanced source works independently of the ground connection.

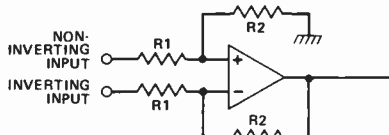


Fig. 2 Preamp stage with a simply-balanced input.

The impedance seen by the balanced source is a result of that due to both input resistors and the internal impedance from base to base of the input differential pair within the op-amp. In most circuits the resistance of the input resistors completely dominates and it is sufficiently accurate to quote the input impedance to balanced sources as  $2 \times R1$ .

A major disadvantage of this circuit is that the ability to reject common mode signals can be seriously degraded with some sources by differences in the source impedance to the two inputs. Remember that it is the matching of the two sets of resistors that determines the common mode rejection ratio. This is the ratio of the input signal to the output signal when a common mode signal is applied. It is usually quoted in dB. The value quoted earlier for shielded cables of around 60 dB is a relatively easy figure to obtain with the op-amp circuit so long as the driving source impedance is the same for both inputs. A mismatch of only one per cent will degrade the common mode rejection ratio (CMRR) of an otherwise well designed preamp by around 20 dB, and result in a figure that could easily be unsatisfactory.

Another disadvantage of this circuit is that it is not capable of delivering the full gain needed of the preamplifier and still give satisfactory distortion figures. If we take a nominal output signal level from a balanced microphone to be around 0.2 mV and the required output from the preamp to be around 100 mV, then a gain of 500 is required, or around 54 dB. The distortion figure obtained using the best op-amps available would be unsatisfactory. For example, an NE5534A at a gain of 500 would have a distortion figure around 0.15%, a poor figure by modern standards and well outside the capabilities of a good transformer. The solution is simply to decrease the gain of the stage and add a second stage to make up the difference. This, however, does not solve the problem of degradation of the CMRR on some sources. The real solution is to add a *third* op-amp to the design and implement a full instrumentation amplifier.

The basic circuit for an instrumentation amplifier is shown in Fig. 3. The second stage, formed by IC3, is the same

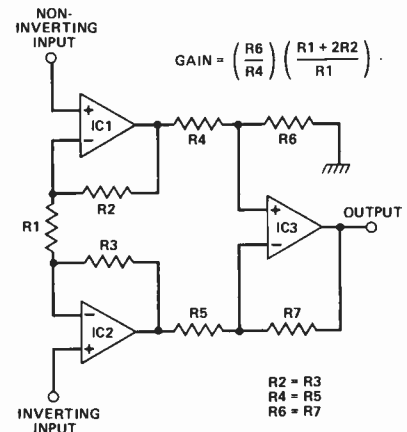


Fig. 3 The solution to the problem.

as the simple differential amplifier in Fig. 2, but its inputs are buffered by the input stages formed by ICs 1 and 2. Resistor pairs R2, R3 and R4, R5 and R6, R7 are made equal. The gain of the second stage is simply R6/R4 as derived above, but the gain of the first stage is given by the slightly more complex formula:

$$(R1 + 2R2)/R1$$


The overall gain is therefore

$$\frac{R6}{R4} \times \frac{R1 + 2R2}{R1}$$

If the value of R4 and R5 is made large in comparison to the estimated difference in the output impedances of the two input op-amps and if the gain of these two op-amps is the same then good CMRR will result.

A problem can occur on many instrumentation amplifiers in ensuring that the gains of the input op-amps are as close as possible to being the same. One feature of this circuit is that the CMRR is affected to a lesser extent by the matching of the resistors around the first stage. Furthermore, this will not be degraded by mismatch of the source impedance to the two inputs. The overall gain of the preamplifier is divided into two stages ensuring sufficient amounts of negative feedback to provide low distortion.

# PROJECT: Differential Preamp

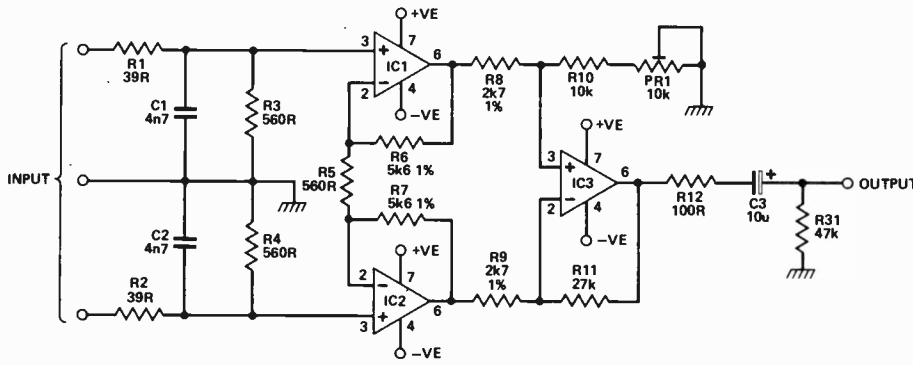

NOTE:  
IC1,2 ARE NE5534A  
IC3 IS TL071  
ZD1,2 ARE 15V  
1W ZENERS

NOTE: EXTERNAL CONNECTION MUST BE PROVIDED BETWEEN POWER SUPPLY 0V POINT AND THE SIGNAL GROUND. SEE TEXT.

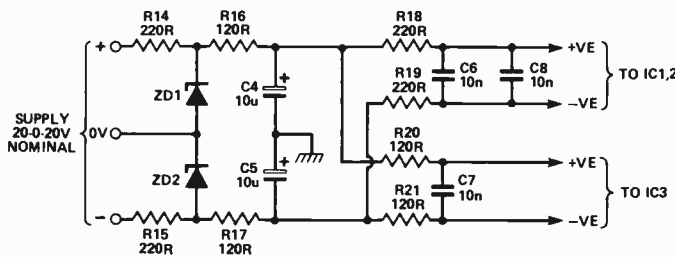


Fig. 4 Circuit diagram.

## HOW IT WORKS

The circuit is a relatively straightforward instrumentation amplifier. The main differential stage is formed by IC3, the TL071. This is a biFET op-amp with good common mode rejection ratio (CMRR) figures. This stage is buffered from the inputs by a pair of NE5534A op-amps that also provide additional gain and determine the overall noise performance of the preamp. As mentioned in the other box, the overall gain of the preamp is determined by the gain of the first and second stages. The gain of the second stage is determined by the ratio of R11 to R9, and is around 10. The gain of the first stage is approximately 20, giving an overall gain of about 200, or 46 dB. If you require a different gain to this, try to keep the ratios of gain in the first and second stages the same. The amount of gain provided here should be suitable for most microphones, providing around 100 mV output from a 0.5 mV input signal level.

The circuit is DC-coupled at the input. This assumes that the driving source will be transformer or capacitively coupled at the output, which should be a safe assumption. The input impedance of the stage is set by the two input resistors R3 and R4. To increase the input impedance, simply increase the value of these resistors.

The RC networks consisting of R1-C1 and R2-C2 are high frequency filters to reduce the circuit's susceptibility to RF interference. The split power supply is provided either from two zener regulators or from a well-regulated and filtered DC source. The supply pins to each IC are decoupled by 1kΩ resistors and 10n capacitors to prevent IC-to-IC interaction and possible feedback via the supply rails.

The split power supply is provided either from two zener regulators or from a well-regulated and filtered DC source. The supply pins to each IC are decoupled by 1kΩ resistors and 10n capacitors to prevent IC-to-IC interaction and possible feedback via the supply rails.

The split power supply is provided either from two zener regulators or from a well-regulated and filtered DC source. The supply pins to each IC are decoupled by 1kΩ resistors and 10n capacitors to prevent IC-to-IC interaction and possible feedback via the supply rails.

throughout, without a significant cost penalty.

The PCB has been designed so that an external connection must be provided between the 0 V point on the PCB and the signal earth. The correct place for this connection is at the input to the preamplifier, ie on the input socket. A separate wire is run from the 0 V point to the signal earth point of the input socket. The signal leads from the input socket to the PCB should be shielded cable with the earth braid connected at both ends. The signal earth should not be connected to the chassis directly. RF shielding can be accomplished by connecting a 100nF capacitor between the signal earth at the input socket and the chassis. This will eliminate any problems with hum loops that might otherwise be formed around the mains earth line.

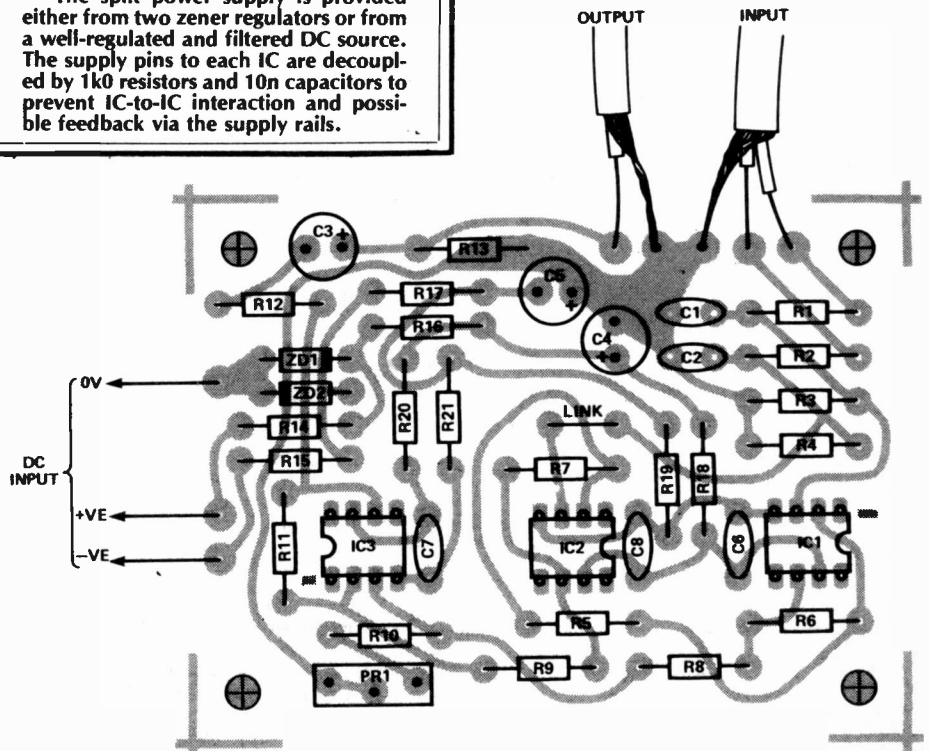


Fig. 5 Component overlay for the differential preamp.

## BUYLINES

We haven't used anything in this project that isn't commonplace in the advertisements of the mail order companies: even the NE5534A is becoming fairly well-stocked. The PCB can be ordered from our PCB Service on page 87.

## PARTS LIST

Resistors (all 1/4W, 5% except where stated)

R1,2	39R
R3-5	560R
R6,7	5k6 1%
R8,9	2k7 1%
R10	10k
R11	27k
R12	100R
R13	47k
R14,15, 18,19	220R
R16,17, 20,21	120R

Potentiometer

PR1	10k miniature vertical preset
-----	-------------------------------

Capacitors

C1,2	4n7 ceramic
C3	10u 35 V PCB electrolytic
C4,5	10u 16 V PCB electrolytic
C6-8	10n ceramic

Semiconductors

IC1,2	NE5534A (see text)
IC3	TL071
ZD1,2	15 V, 1 W zener

Miscellaneous

PCB (see Buylines)

ETI

ETI MAY 1983

# Play the AMBIT numbers game .....

The long awaited implementation of on-line order processing is with us at last, and whilst this means that orders for in-stock items can now be processed more efficiently, it also means that orders should be submitted using stock code results. Our current catalogue (75p) includes all order codes (watch out for the new expanded Spring edition), but here's an abstract from some of the more popular lines to use as a quick reference.

Remember that you can also access our catalogue via REWSHOP or REWTEL, which now includes on-line current price and delivery information. You need a 300 baud MODEM and RS232 terminal, (various suitable configurations based on popular micros have been published in recent past issues of Radio and Electronics World).

Prices shown here exclude VAT, and the P&P charge is currently 60p per order (unless otherwise indicated). Remember that our tele-sales service operates with human beings (not 'dumb' machines) from 8am to 7pm (and frequently later) Monday to Friday, and 9am to 6pm on Saturdays. REWSHOP operates 24 hours a day, 365 days a year with full price and delivery information.

## ALWAYS USE STOCK NUMBERS WHEN ORDERING PLEASE.

4000 CMOS			74HCXX			74LSXX			74CXX			LINEAR ICs			SMALL SIGNAL RF			SMALL SIGNAL FE			SMALL SIGNAL AUDIO			DIODES			VARICAPS			AUDIO POWER			ZENER DIODES			TRI COLOUR		
Type	Stock No.	Price	Type	Stock No.	Price	Type	Stock No.	Price	Type	Stock No.	Price	Type	Stock No.	Price	Type	Stock No.	Price	Type	Stock No.	Price	Type	Stock No.	Price	Type	Stock No.	Price	Type	Stock No.	Price	Type	Stock No.	Price	Type	Stock No.	Price			
4000B	23 04001	0.11	74C01	23 04073	4.28	74LS00	30 07400	0.11	LM1000	61 00010	3.88	74C02	29 07400	0.58	2SK134	60 00134	3.10	BA102	12 01025	0.30	2N2904	58 02904	0.25	2N2904	58 02904	0.25	2N2904	58 02904	0.25	2N2904	58 02904	0.25	2N2904	58 02904	0.25	2N2904	58 02904	0.25

**Ambit international**  
 200 North Service Road  
 Brentwood, Essex  
 CM14 4SG

Telecom directory:  
 Consumer 0277-230909  
 Industrial 0277-231616  
 Telex 995194 AMBIT G  
 DATEL 0277-232628






TELEPHONE SALES 8 am - 7 pm MON - FRI 9 am - 6 pm SAT



# COMPUTER WAREHOUSE

THE 'ALADDIN'S' CAVE OF COMPUTER AND ELECTRONIC EQUIPMENT

## HARD DISK DRIVES

Fully refurbished Diablo/DRE Series 30 2.5 mb hard disk drive for DEC RK05, NOVA, TEXAS etc.  
Front load £550.00 - Top load £295.00  
PSU type ME3029 for 2 drives £125.00  
DRE 44A/4000A/B 10 mb 5+5 all configurations from £995.00. Call sales office for details.

## 5 AMP MAINS FILTERS

Cure those unnerving hang ups and data glitches caused by mains interference. Matchbox size - Up to 5 amp 240 v load. As recommended by the ZX81 newsletter. Suppression Devices SD5A £5.95.

## COOLING FANS

Keep your hot parts COOL and RELIABLE with our range of BRAND NEW professional cooling fans.  
ETRI 99XU01 Dim. 92 x 92 x 25 mm. Miniature 240 v equipment fan complete with finger guard. £9.95.  
GOULD JB-3AR Dim. 3" x 3" x 2.5" compact very quiet running 240 v operation. NEW £6.95  
BUHLER 69.11.22. 8-16 v DC micro miniature reversible fan. Uses a brushless servo motor for extremely high air flow, almost silent running and guaranteed 10,000 hr life. Measures only 62 x 62 x 22 mm. Current cost £32.00. OUR PRICE ONLY £12.95 complete with data.  
MUFFIN-CENTAUR standard 4" x 4" x 1.25" fan supplied tested EX EQUIPMENT 240 v at £6.25 or 110 v at £4.95 or BRAND NEW 240 v at £10.50. 1000's of other fans Ex Stock. Call for Details. Post & Packing on all fans £1.60

## DISTEL ©

The UK's FIRST free of charge, 24 hr. public access data base. Get information on 1000's of stock items and order via your computer and credit card. On line now, 300 baud. CCITT tones, full duplex, fully interactive.

**DON'T MISS THOSE BARGAINS CALL NOW, IT'S FREE!**  
7 days per week 24 hrs per day  
**01-683 1133**

## COMPUTER 'CAB'

All in one quality computer cabinet with integral switched mode PSU, Mains filtering, and twin fan cooling. Originally made for the famous DEC PDP8 computer system costing thousands of pounds. Made to run 24 hours per day the PSU is fully screened and will deliver a massive +5v DC at 17 amps, +15v DC at 1 amp and -15v DC at 5 amps. The complete unit is fully enclosed with removable top lid, filtering, trip switch, 'Power' and 'Run' LEDs mounted on Ali front panel, rear cable entries, etc. Units are in good but used condition - supplied for 240v operation complete with full circuit and tech. man. Give your system that professional finish for only £49.95 + Carr. Dim. 19" wide 16" deep 10.5" high. Useable area 16" w 10.5" h 11.5" d. Also available LESS PSU with internal dim. 19" w, 16" d, 10.5" h, £19.95". Carriage & insurance £9.50.

## 8" FLOPPY DISK DRIVES



Unbelievable value the DRE 7100 8" floppy disk drives utilise the finest technology to give you 100% bus compatibility with most drives available today. The only difference being our PRICE and the superb manufacturing quality! The 7100 single sided and 7200 double sided drive accept hard or soft sectoring IBM or ANSI standard formats giving a massive 0.8 MB (7100) 1.6 MB (7200) of storage. Absolutely SHUGART, BASF, SIEMANS etc. compatible. Supplied BRAND NEW with user manual and full 90 day warranty. Carriage and insurance £9.75.  
**7100 Single sided £225.00 + Carr. 7200 Double sided £295.00 + Carr.**  
Optional accessories: Full technical manual £20.00 alone. £10.50 with drive. Refund of difference on drive purchase. DC and AC power connector and cable kit £8.45. 50 way IDC connector £5.50. 50 way ribbon cable £3.20 per metre.

## VIDEO MONITORS

**MOTOROLA 9"** open chassis monitor. Standard 240 v AC with composite 75 ohm video input, bandwidth in excess of 18 mhz. Monitors are ex equipment and although unguaranteed they are all tested prior to despatch, and have no visible burns on the screens. Dim approx. 9" x 9" x 9". Supplied complete with mains and input lead. Ideal ZX81 etc. or giving the tele back to the family! Black and white phosphor. £35.00 + £9.00 Carr.

**12" CASED.** Made by the British KGM Co. Designed for continuous use as a data display station, unit is totally housed in an attractive brushed aluminium case with ON-OFF, BRIGHTNESS and CONTRAST controls mounted to one side. Much attention was given to construction and reliability of this unit with features such as, internal transformer isolated regulated DC supply, all components mounted on two fibre glass PCB boards - which hinge out for ease of service, many internal controls for linearity etc. The monitor accepts standard 75 ohm composite video signal via SO239 socket on rear panel. Bandwidth of the unit is estimated around 20 Mhz and will display most high def graphics and 132 x 24 lines. Units are secondhand and may have screen burns. However where burns exist they are only apparent when monitor is switched off. Although unguaranteed all monitors are tested prior to despatch. Dimensions approx. 14" high x 14" wide by 11" deep. Supplied complete with circuit, 240 volt AC operation. **ONLY £45.00 PLUS £9.50 CARR.**

**14" COLOUR** superb chassis monitor made by a subsidiary of the HITACHI Co. Inputs are TTL RGB with separate sync. and will plug direct into the BBC micro etc. Exceptional bandwidth with good 80 col definition. Brand new and guaranteed. Complete with full data & circuit. 240 v AC working. Dim. 14" x 13" x 13". **ONLY £199.00 PLUS £9.50 CARR.**

## SUPER DEAL? NO - SUPER STEAL!!

The FABULOUS 25CPS TEC Starwriter Daisy wheel printer at a fraction of its original cost.

BRAND NEW AT ONLY £499+ VAT

Made to the very highest spec, the TEC Starwriter FP1 500-25 features a heavy duty die cast chassis and DIABLO type print mechanism giving superb registration and print quality. Micro-processor electronics offer full DIABLO/QUME compatibility plus Bi directional printing, 10 or 12 pitch, 136 or 183 chars per line, full width 381 mm friction or single sheet paper, - order now or call sales office for more information and print sample. Please specify RS232 or CENTRONICS interface. Supplied complete with FREE dust cover and daisy wheel. Optional extras: RS232 data cable £10.00 - Tech. manual £7.50. Carriage & Ins. (UK) £12.50. - Tractor feed option £120.00



## TELETYPE ASR33 I/O TERMINALS

FROM £195 + CAR + VAT  
Fully fledged industry standard ASR33 data terminal. Many features including ASCII keyboard and printer for data I/O auto data detect circuitry, RS232 serial interface, 110 baud, 8 bit paper tape punch and reader for off line data preparation and ridiculously cheap and reliable data storage. Supplied in good condition and in working order  
Options: Floor stand £12.50 + VAT  
KSR33 with 20ma loop interface £125.00 + Sound proof enclosure £25.00 + VAT

## SOFTY 2

The amazing SOFTY 2. The complete "toolkit" for the open heart software surgeon. Copies, Displays, Emulates ROM, RAM and EPROMS of the 2516, 2532 variety. Many other features include keyboard, UHF modulator, Cassette interface etc. Functions exceed capabilities of units costing 7 times the price! Only **£169.00** pp £1.95 Data sheet on request

## RECHARGEABLE BATTERIES

CYCLON type D001 sealed lead acid maintenance free 2v 2.5 ah. will deliver over 300 amps on short circuit!! Brand new at only £2.95  
SAFT VR2C size 'C' 1.2v 2 ah. nickel cadmium £1.50 each 10 for £11.50

## DATA MODEMS

Join the communications revolution with our range of EX TELECOM data modems. Made to most stringent spec and designed to operate for 24 hrs per day. Units are made to the CCITT tone spec. With RS232 I/O levels via a 25 way 'D' sct. Units are sold in a tested and working condition with data. Permission may be required for connection to PO lines.

**MODEM 13A** compact, async, same size as telephone base. Up to 300 baud, full duplex over 2 wires, but call mode only £75.00

**MODEM 2B/C** Fully fledged, up to 300 baud async, ANSWER & CALL modes, auto answer, auto switching, ideal networks etc. Just 2 wire connection to comms line. £85.00

**MODEM 20-1** Compact unit for use with PRESTEL or full duplex 2 wire link. 75 baud transmit - 1200 baud receive. Auto answer. £130.00

**MODEM 20-2** same as 20-1 but 75 baud receive 1200 baud transmit. £130.00

**MODEM 20-3** Made for data rates up to 1200 baud in full duplex mode over 4 wire circuit or half duplex mode over 2 wires. £130.00  
Carriage, 13A £4.50, 2B/C & 20 £9.50.  
For more details contact sales office.

## D.C. POWER SUPPLY SPECIALS

Experimentors PSU Ex-GPO unit all silicon electronics. Outputs give +5v @ 2 amps. +12v @ 800 ma. -12v @ 800 ma. +24v @ 350 ma. 5v @ 50 ma. floating. Dim 160 x 120 x 350 mm. All outputs fully regulated and short circuit proof. Removed from working equipment, but untested. Complete with circuit. Transformer guaranteed. Only **£14.50 + £2.50 pp.**

**CUSTOM POWER C055** 5v @ 3 amp. Very compact unit dim. approx 60 x 90 x 190 mm. Semi open chassis, full crowbar overvoltage protection. Tested Ex Equipment. **£11.95 + pp £1.25**

**MINI SYSTEM PSU** Ex equipment unit ideal for the small micro. Outputs give 5v @ 3 amps. +12v @ 1 amp and -12v @ 300 ma. Crowbar overvoltage protection and current limit. Fully tested. Dim 70 x 165 x 320 mm. Complete with Circuit only **£12.95 + £2.00 pp.**

**PERIPHERAL SYSTEM SUPPLY.** Fully cased unit supplied in a Brand new or little used condition. Outputs give 5v @ 11 amps. "+-" 15-17v @ 8 amps. "-" 15-17v @ 8 amps and "+-" 24v @ 4 amps. All outputs are crowbar protected and the 5 volt output is fully regulated. Fan cooled. Supplied tested, with circuit **£55.00 + £8.50 carr.**

**MAIN FRAME SUPPLY.** A real beefy unit designed for MINI or MAINFRAME use outputs give 5 volts @ 50 amps. +12v @ 5 amps. -12v @ 10 amps. All output are fully regulated with crowbar overvoltage protection on the 5v output. Supplied with circuit and tested. Ex-Equip. 110v AC input. Only **£49.95 + carr. £10.50.**

## 66% DISCOUNT ELECTRONIC COMPONENTS & EQUIPMENT

Due to our massive bulk purchasing programme which enables us to bring you the best possible bargains, we have thousands of I.C.'s, Transistors, Relays, Cap's, P.C.B.'s, Sub-assemblies, Switches, etc. etc surplus to our requirements. Because we don't have sufficient stocks of any one item to include in our ads, we are packing all these items into the "BARGAIN PARCEL OF A LIFETIME" Thousands of components at giveaway prices! Guaranteed to be worth at least 3 times what you play plus we always include something from our ads, for unbeatable value! Sold by weight.

2.5kls £4.25 + pp £1.25  
10kls £10.25 + pp £2.25  
5kls £5.90 + pp £1.80  
20kls £17.50 + pp £4.75

**ALL PRICES PLUS VAT**

DISPLAY  
-ELECTRONICS-

All prices quoted are for UK Mainland, paid cash with order in Pounds Sterling PLUS VAT. Minimum order value £2.00. Minimum Credit Card order £10.00. Minimum BONA FIDE account orders from Government depts., Schools, Universities and established companies £20.00. Where post and packing not indicated please ADD 90p + VAT. Warehouse open Mon-Fri 9.30 - 5.30. Sat. 10.15 - 5.30. We reserve the right to change prices and specifications without notice. Trade, Bulk and Export enquiries welcome.

64-66 Melfort Road, Thornton Heath, Near Croydon, Surrey  
01-689 7702 - 01-689 6800 Telex 27924



# BUYER'S GUIDE TO HI-FI SYSTEMS

And now we proudly present the Thinking Man's Guide to Buying Hi-fi. That is, ETI has done the thinking, now you go out and do the buying! Bring your own wallet (all sizes catered for).



**B**uying a hi-fi system is a harrowing experience, especially the first time out. After you've bought all the hi-fi mags for six months, thoroughly digested the conflicting and often lunatic advice given therein, listened to all your 'expert' friends disagreeing with each other and dared to cross the threshold of a shop . . . what then?

One word — LISTEN. It matters not a jot what anyone else tells you — us included — if you don't agree with the choice, don't buy it! You're going to have to live with it. However, it is a good idea to have a shortlist based upon reviews, price, but don't forget, most important of all are your own auditionings.

Reading the specialist audio press can be enlightening — but it can be mystifying too. At one time you could read through two or three different magazines and still be told that whether you were spending £500 or £5000 on a system, unless you bought a particular £300 turntable you were wasting your money! The field has to some extent sobered up of late, since crashing circulations and retreating advertisers have brought with them a certain measure of common sense. If you want a magazine reviewer's recommendation for 'which magazine' — mine would be *Hi-Fi For Pleasure*. It is a title that is not only a good read but has consistently demonstrated a sound technical understanding and displayed a commendable intelligence, when all around it were losing theirs!

(It's fun being an electronics-based magazine sometimes — we could never get away with saying things like that in the hi-fi press!)

In this supplement we're taking a different ap-

proach to the overall compatibility 'table' approach. Instead we have listed out eight full systems, from £350 to £8500 in price and which we have personally tried and tested (except one — and you'll see why . . .)

In this way each forms a perfectly good buy in itself — assuming you like the sound yourself, of course — or at the least will make a good starting point in the demonstration room when you're down to the final choice.


Each of the systems is for records only: no allowance is made in price for tape or tuner. Additions such as these we left until later. We have some advice to offer on those too, but in the form of a list of models which we have had through our hands at some point and have found to be good. A number of people have very expensive record playing systems but have tacked onto the end of them cassette decks of considerably lower-fi, to use as background music and so on. Because of this we have made no attempt to assign tape and tuner to the primary systems. You pick and choose as you like to fit your own individual needs.

A word of explanation about the system tables to be found overleaf. The first column contains details of our recommended system and the retail price (as far as we know — do shop around for bargains). The order of components is record deck, arm (if not included with the deck), cartridge, preamp/power amp combination, and speakers. Any alternatives are given in the second column with their prices bracketed.

We've also illustrated each of the systems to the best of our ability, but some companies were as compliant as concrete cantilevers, and the 'first class' post wasn't, so there are some unfortunate omissions. C'est la vie . . .


# SYSTEM 1

## £325


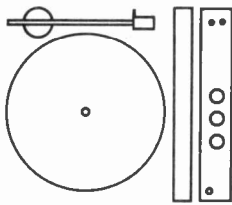


Dual CS505	80	There
Coral MC88E	25	Is
Sansui AU-D33	145	No
Videotone Minimax 2	75	Alternative!
<b>TOTAL</b>	<b>£325</b>	

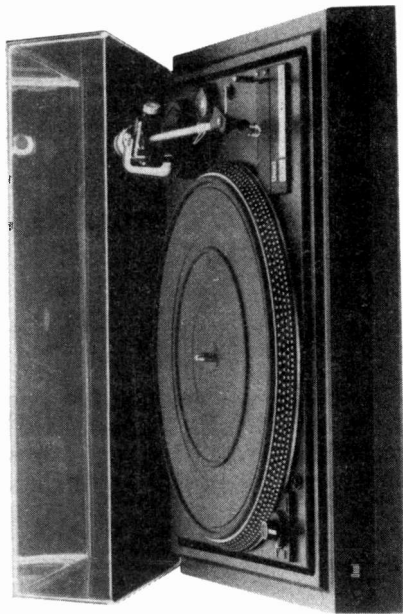With the rising costs of even the most basic system, the Dual CS505 is a godsend to the first time buyer. It offers very good performance for a reasonable cost. The Coral MC88E is a lively sounding moving coil unit, which needs a careful choice of speaker to make the most of its performance, and the new Minimax is an ideal match.




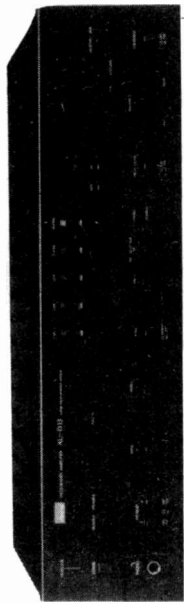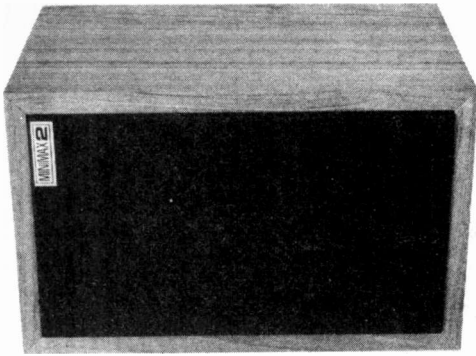Overall the system provides a clean and slightly forward sound, with a good bass performance for its size. The Sansui offers a sound technical performance allied to a good power delivery and is ideal as the centre of a sound system designed for a wide range of music but a narrow wallet.






# SYSTEM 2

## £504

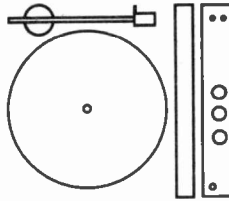


Systemdek II	115	Michell Focus 1 (105)
Linn Basik LV X	74	
A & R A60	195	NAD 3150 (98)
KEF Cantor 2	120	Mordaunt Short Festival 3 (150)
<b>TOTAL</b>	<b>£504</b>	

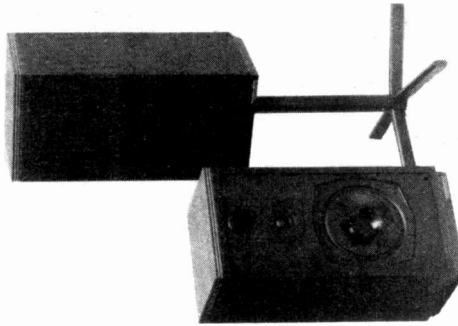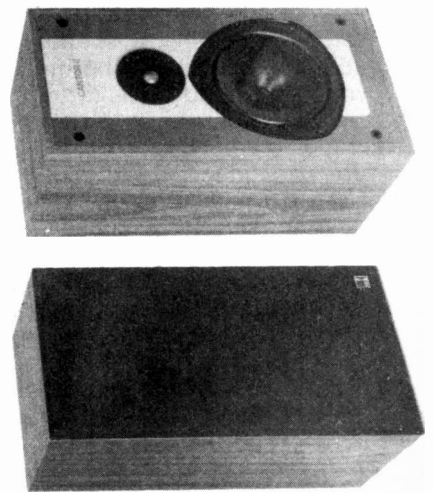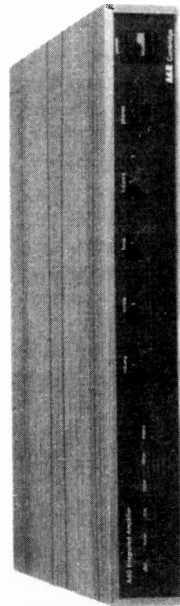


to provide as neutral result as can be obtained for this outlay. The A60 is a classic design and needs little introduction. It is probably the best of its kind for around £200 and you'll need to lay out a couple of hundred more to better this system for overall performance.

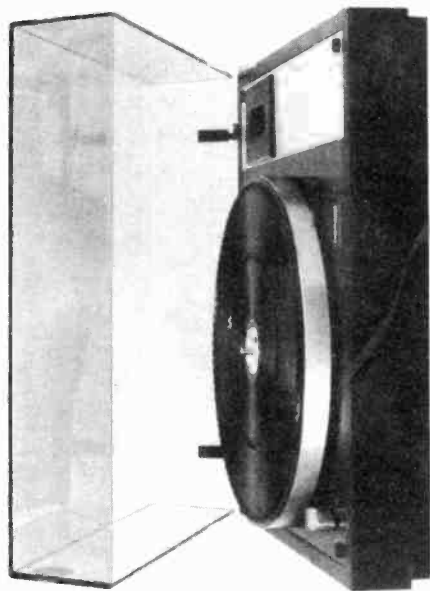The Systemdek II is an individual approach to design — you'll either love it or hate it! Either reaction is catered for here by the use of the Focus One as an alternative. The Basik is well established as a cheap way of obtaining a good pickup. It will work well with the Cantor loudspeakers



# SYSTEM 3




# £970

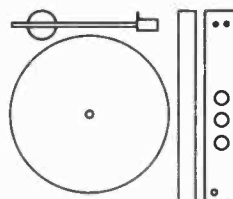

Thorens TD160S	175	
SME Series III	100	SME Series IIIS (80)
Shure V15V	105	Coral MC82 (120)
Trio KA-900	295	
Celestion SL6	295	Heybrook HB2 (185)
<b>TOTAL</b>		<b>£970</b>

The Thorens TD 160S is the basis for this system and although it does need very careful setting up — which any good dealer will carry out — it returns a performance which is far above that promised by the price of £175. It will consistently outperform decks costing £350 or more and as such is used in our next system upwards as well as in this one. The SME has become rather unfashionable of late, but is still THE best universal arm available. It matches high compliance designs particularly well and the V15V in particular.

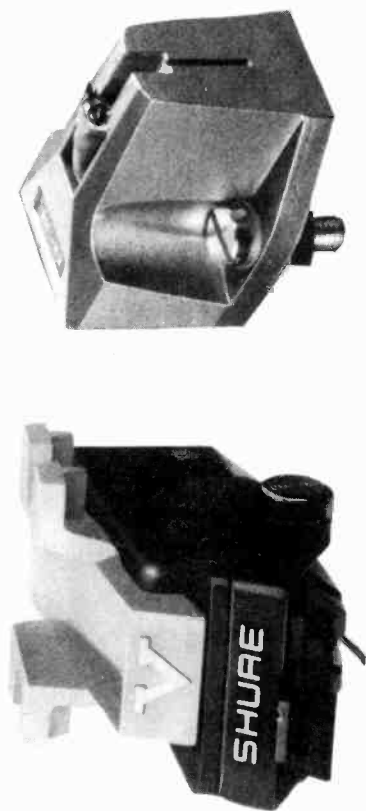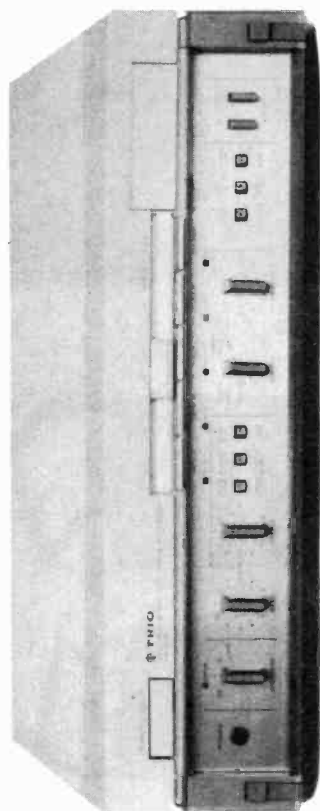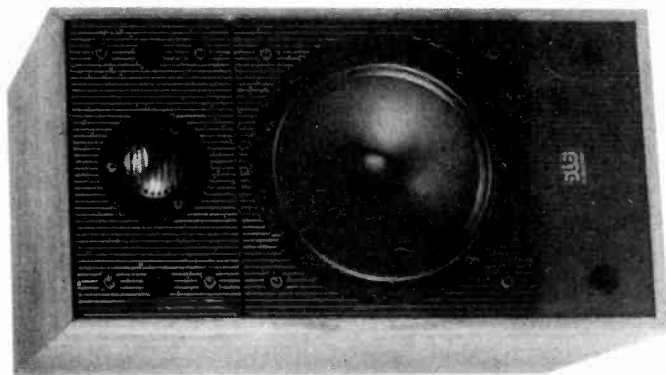With the Trio and the SL6, this adds up to a com-




pact system capable of very high sound quality indeed and with a staggering bass response for its size (a trait born of the combination of V15V and SL6s). The alternative system is perhaps slightly smoother and would suit classical orientated taste a little better, although you will not get quite the same dynamics from the HB2s as with the Celestions.

Using the 'S' version of the SME will save you £20 or so and with the MC82 it is a better match anyway. Don't use this cartridge with SL6's, however; they do not work well together. The V15V, on the other hand, is a perfect complement.




# SYSTEM 4

# £1368

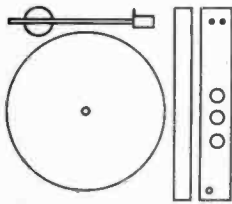




Thorens TD160S	175	
SME Series III	100	
Dynavector Karat Ruby	150	Shure V15V (105)
The Preamplifier/Carver M-400 (the Cube)	550	
Heybrook HB3	393	KEF 105 IV (500)
<b>TOTAL</b>	<b>£1368</b>	

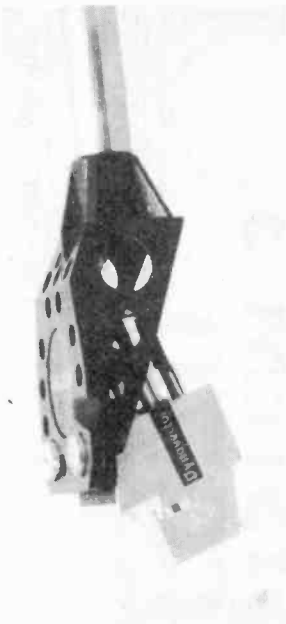

Using the 160S/SME III combination once more, it is possible to construct a more 'up market' system which will provide greater power delivery and a much-improved bass response. Changing the speakers to Heybrook HB3s allows the use of the Karat Ruby from Dynavector and this will open out the mid-range to provide greater detail than before.


The Carver M-400 or 'Cube' is well-known for its phenomenal power delivery and miniscule dimensions. Unfortunately Carver do not yet market a preamp which is its equal in sound quality. The unit from Musical Fidelity is very well-designed and provides a good match.

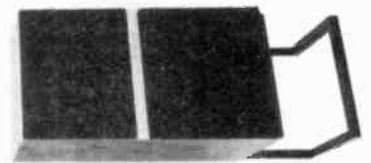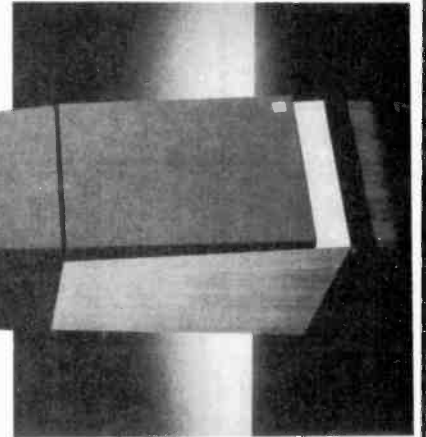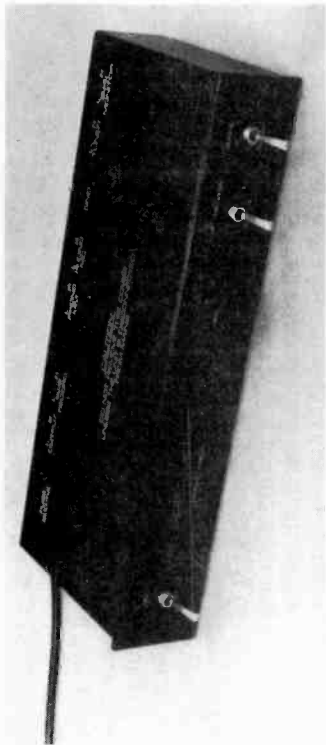If you have another £100 floating about spare, you could improve the system still further by substituting the excellent KEF 105 IV for the HB3. These are the smaller version of the illustrious 105 II and have many of that unit's admirable traits.



# SYSTEM 5

# £2840




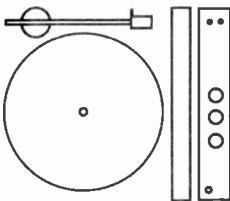


Oracle	600
SME Series III	100
Ortofon MC30/T-30	550
Elite 600/660	890
	NAC 32/NAP 20 (1100)
Gale 401	700
	KEF 105 II (900)
<b>TOTAL £2840</b>	

The Oracle is now accepted in many circles as the best-sounding turntable on the market. It is also one of the most expensive, at around £600. To obtain the absolute best from it, you need around £700 worth of cartridge and arm (see System 7) but the Oracle will still serve to improve less bank-breaking ambitions, provided care is exercised.


The Ortofon MC30 is a high compliance moving-coil unit of the highest quality. In our experience it does not work very well with the newer high-mass arms designed for moving-coil pickups. It does work superbly with the faithful SME Series III, however, with only the addition of the headshell weight. Use Ortofon's own step-up, the T-30, for optimum performance.

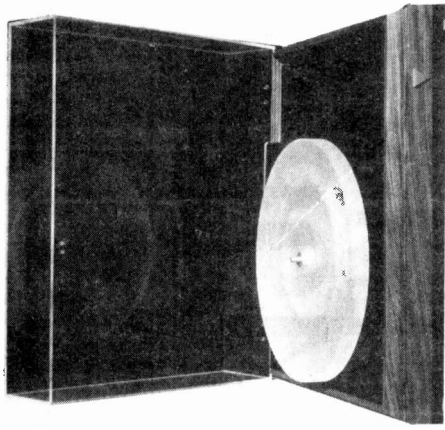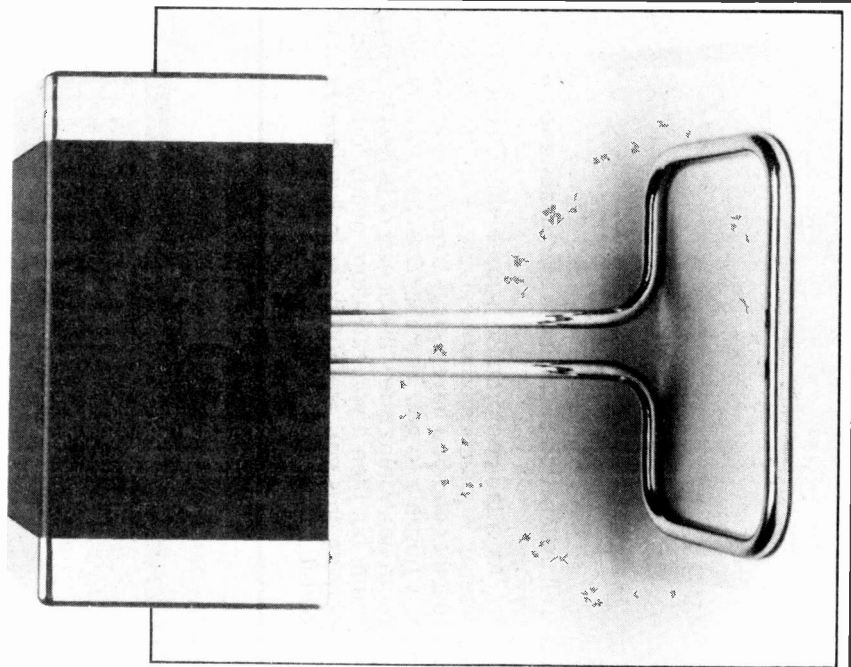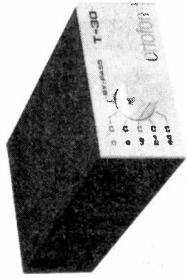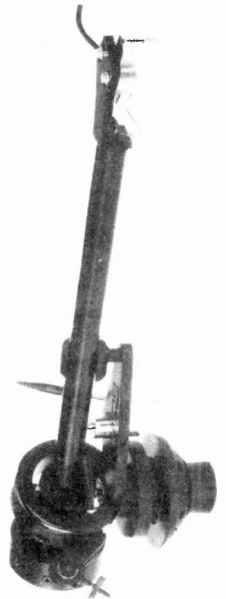The KEF 105 II will provide a more neutral rendition than the Gale, but at a cost of around £200 more. Either speaker soaks up power like a sponge, and you may find the extra punch of the Naim more to your tastes, especially with the KEF.



# SYSTEM 6


# £3071

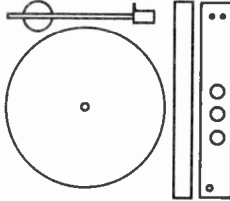

Pink Triangle	398
Mission 774SM	157
	Alphason HR100S (195)
Dynavector Karat	
Diamond	516
NAIM NAC 32/ NAP 20	1100
KEF 105 II	900
<b>TOTAL £3071</b>	


Based upon the Naim/105 combination this set-up brings you the benefits of the ultra-low compliance Dynavector Karat Diamond. This has a solid diamond cantilever and provides as good a way of extracting music from a disc as can be found anywhere. The Pink Triangle and Mission arm allow it to give of its best — no mean feat.

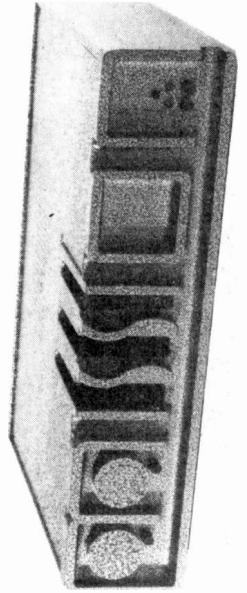As an alternative amplifier, consider the Mission 776/777 combination. This is fairly new, but has already acquired an enviable reputation. The power amp in particular is excellent for the price.



# SYSTEM 7



# £3393

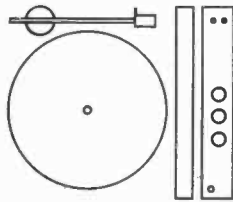


Oracle	600	
Fidelity Research FR 64	270	Linn Ittok (273)
Koetsu Silver	573	Linn Asak (207)
NAIM NAC 32/ Quad 405 II	750	NAC 32/Denon POA-3000 (2000)
Quad ELS-63	1200	
<b>TOTAL</b>	<b>£3393</b>	

**E**nter the Quad ELS-63 at £1200 the pair. If you want the best possible reproduction in the home, regardless of convenience or price then this is it. To drive them Quad's own 405 (now in Mk. 2 livery) takes some beating. It would appear that these two are designed to work together, since the 405 will lose units costing three or four times the price into the ELS-63's, and yet turn in a mediocre performance with some other speakers which are regarded as an easier load!

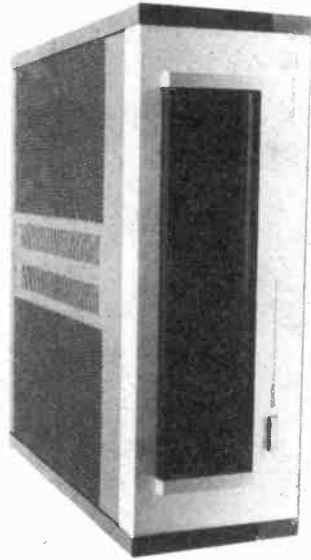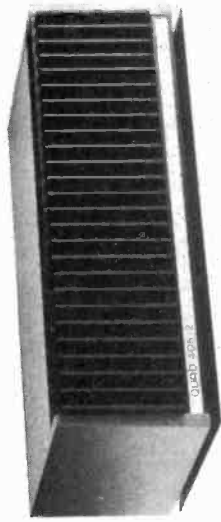As an alternative the Class A Denon POA-3000 is




well matched to ESL-63 both electrically and for quality. As a no-compromise source the Oracle/FR 64 Koetsu is practically unbeatable. Put this little lot together and you have as high a quality disc system as it is possible to get. The ESL-63 is very touchy about room positioning and will not give of its best in a small room, but then if you can afford nearly four grand to play records you are not likely to live in a 12 x 12 bedsit . . . are you?

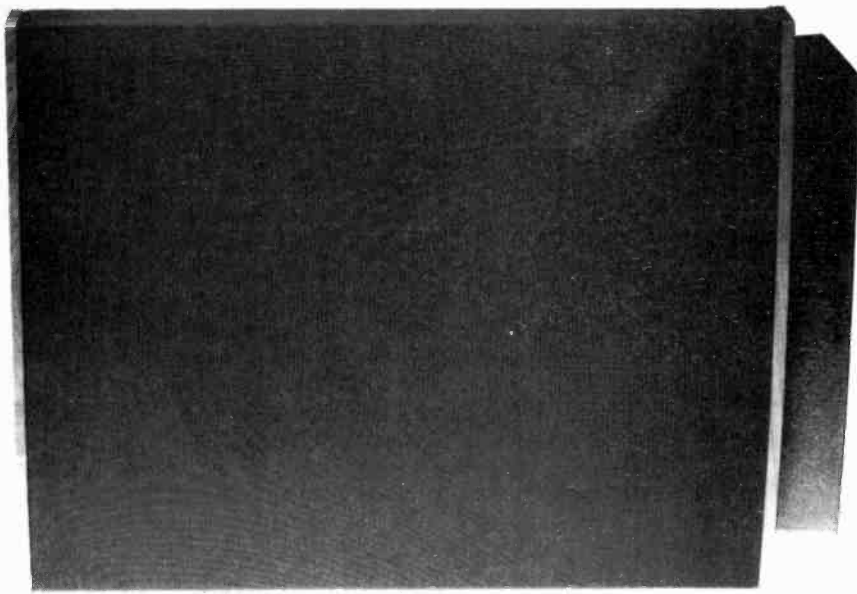


And just to be *really* silly . . .


# SYSTEM 8

# £8498

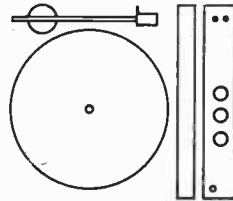

Marantz Esotec 1000	1000	
Sumiko The Arm	798	
Koetsu Gold	900	
Threshold		Denon PRA-2000
FET1/5500	4600	POA-3000 (3500)
Quad ELS-63	1200	
<b>TOTAL</b>	<b>£8498</b>	

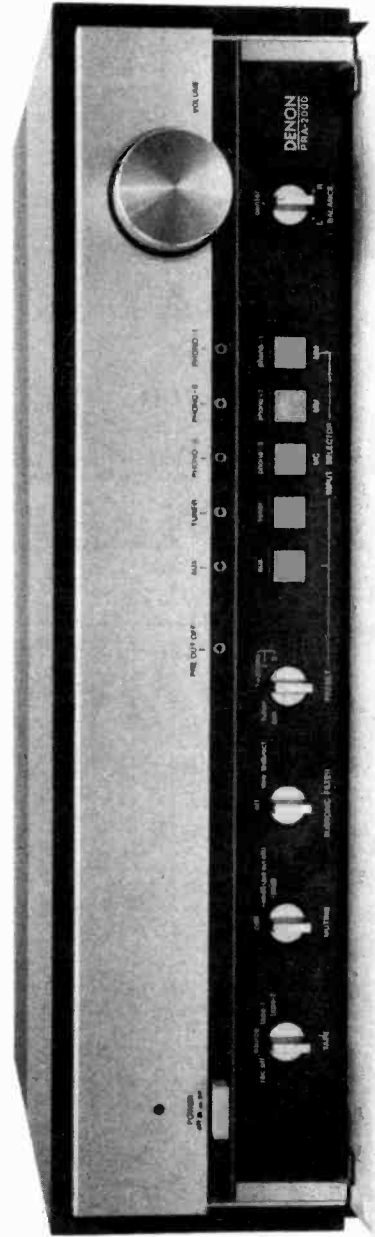


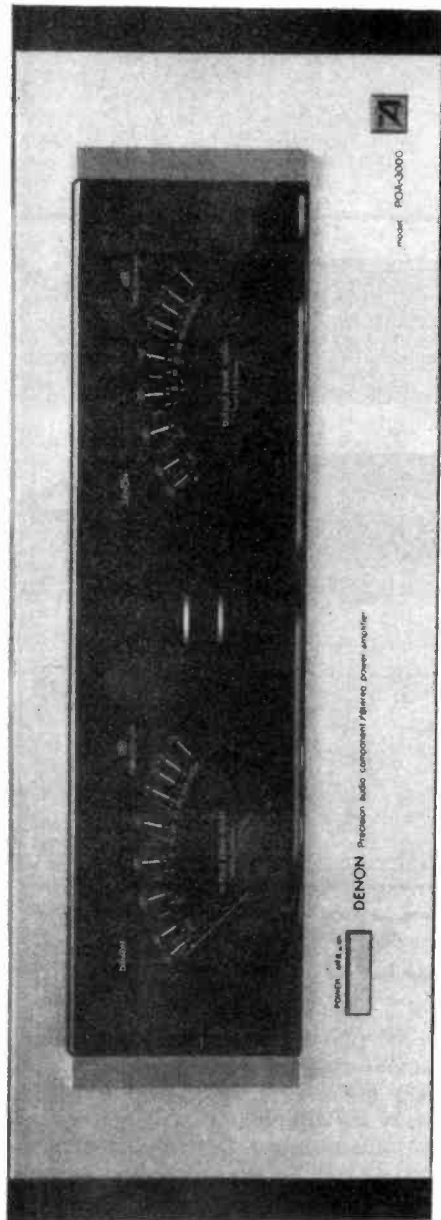

If you thought £3500 was expensive, try £8500! We must stress that we've never heard this precise arrangement of components and think it unlikely anyone else has either!

The Threshold amp is very highly regarded and on the occasions we've heard it, it is a very impressive piece of work indeed. Magnificent in all but generosity. £4600 is a lot of cash.

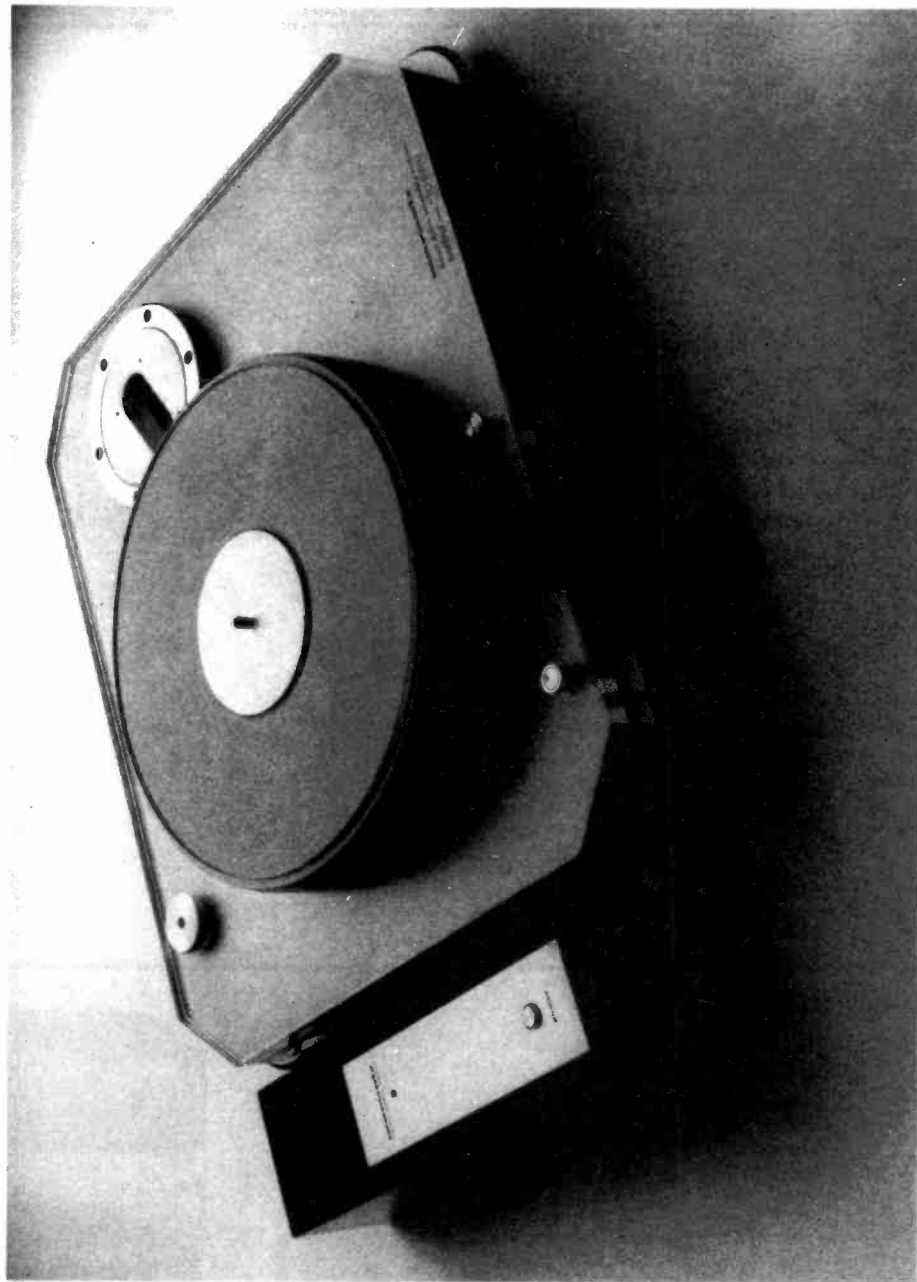The (Sumiko) Arm is another supreme example of 'That Which Is Possible' — given no constraints on price as a starting point. If you ever get this system together we'd be only too pleased to come and have a listen — we'll even bring the beer!



# CASSETTES AND TUNERS

Once you move away from the basic record playing system into tape and/or radio, then technical compatibility assumes a greater-than-ever importance. Without going through every amplifier input and every tape/tuner output, there is no real way to guarantee complete compatibility. The only useful advice is to check the model you want against the amplifier you're thinking of using it with.




Feeding a low impedance into a high(er) value is OK. Anything else is not. Look for approximately equal sensitivity and output levels, so that you are not flogging some poor little input stage to death somewhere to obtain the level you want.

Here we are presenting a list of ETI approved models — which is not to say that nothing else is approvable! These just happen to be components of which we have had experience and can thoroughly recommend as good performers and good value. Check them over if you're buying into this market. How much you need to pay is entirely dependent upon how much you value that particular source. The more you pay, the better they get.



# CASSETTE DECKS

MODEL	£
Sony TEF 44	110
Technics RSM230	155
Alpage AL-100	173
Akai GX-F51	200
Pioneer CT7R	260
Teac C3X	360
Alpage AL-300	372
Bang and Olufsen Beocord 8002	459
Revox B710 II	943
Nakamichi 1000 ZXL	1000

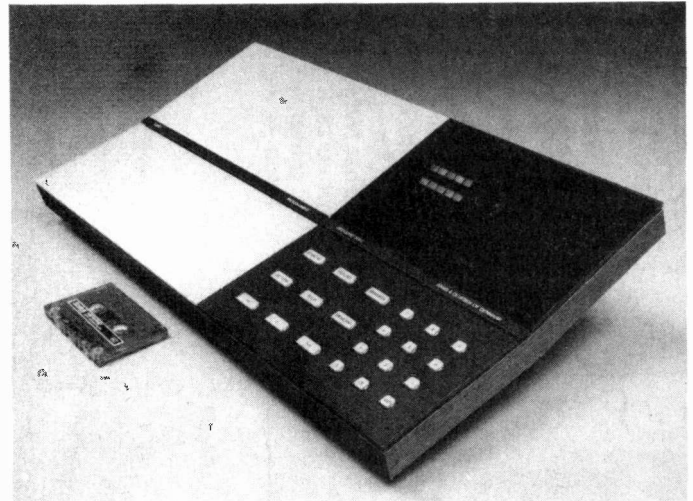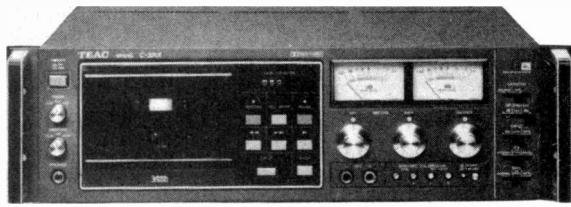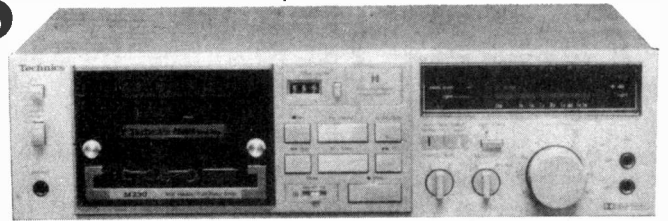

# TUNERS



MODEL	£
Yamaha 7760	143
NAD 4150	159
Sugden T48 II	161
Lux T115	170
A & R T21	190
Sony ST-J75	200
Pioneer F9	200

# COMPACT DISCS?

Perhaps the most relevant question at present is whether or not you should buy an analogue disc system now at all, or go straight for the incoming Compact Disc systems. Our advice would be to wait. While the Compact Disc is of undoubtedly higher quality than any vinyl spinner, the price is horrendous at present, and the records are expensive and very limited in choice.

In about a year the players will be cheaper by far, the choice much wider and the software library five times the size. If you like the music offered and love the gadgets — go buy it. Which one you get is probably irrelevant, as there should not be a whole lot of difference in performance between properly designed units, despite the ad claims.


ETI


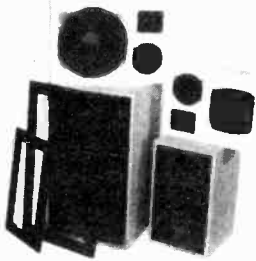
### MULLARD SPEAKER KITS

Purposefully designed 40 watt R.M.S. and 30 watt R.M.S. 8 ohm speaker systems recently developed by MULLARD'S specialist team in Belgium. Kits comprise Mullard woofer (8" or 5") with foam surround and aluminium voice coil. Mullard 3" high power domed tweeter. B.K.E. built and tested crossover based on Mullard circuit, combining low loss components, glass fibre board and recessed loudspeaker terminals. SUPERB SOUNDS AT LOW COST. Kits supplied in polystyrene packs complete with instructions. 8" 40W system — recommended cabinet size 240 x 216 x 445mm  
Price £14.90 each + £2.00 P & P.  
5" 30W system — recommended cabinet size 160 x 175 x 295mm  
Price £13.90 each + £1.50 P & P.


Designer approved flat pack cabinet kits, including grill fabric. Can be finished with iron on veneer or self adhesive vinyl etc.  
8" system cabinet kit £8.00 each + £2.50 P & P.  
5" system cabinet kit £7.00 each + £2.00 P & P.


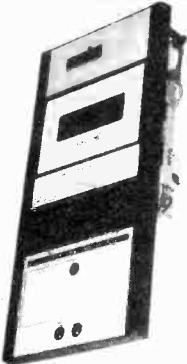
### STEREO CASSETTE TAPE DECK MODULE.

Comprising of a top panel and tape mechanism coupled to a record/play back printed board assembly. Supplied as one complete unit for horizontal installation into cabinet or console of own choice. These units are brand new, ready built and tested.

Features: Three digit tape counter. Autostop. Six piano type keys, record, rewind, fast forward, play, stop and eject. Automatic record level control. Main inputs plus secondary inputs for stereo microphones. Input Sensitivity: 100mV to 2V. Input Impedance: 68K. Output level: 400mV to both left and right hand channels. Output Impedance: 10K. Signal to noise ratio: 45dB. Wow and flutter: 0.1%. Power Supply requirements: 18V DC at 300mA. Connections: The left and right hand stereo inputs and outputs are via individual screened leads, all terminated with phono plugs (phono sockets provided). Dimensions: Top panel 5 1/2" x 11 1/2". Clearance required under top panel 2 1/2". Supplied complete with circuit diagram and connecting diagram. Attractive black and silver finish.  
Price £26.70 + £2.50 postage and packing.  
Supplementary parts for 18V D.C. power supply (transformer, bridge rectifier and smoothing capacitor) £3.50.



### LOUDSPEAKERS

**15" 100 watt R.M.S. (HI-FI, P.A., DISCO, BASS GUITAR)** Die cast chassis, 2" aluminium voice coil, white cone with aluminium centre dome. 8 ohm imp., Res. Freq. 20Hz., Freq. Resp. to 2.5KHz., Sens. 97dB (As photograph). Price: £32.00 + £3 carriage.



**12" 100 watt R.M.S. (HI-FI)** Die cast chassis. 2" aluminium voice coil. Black cone. 8 ohm imp., Res. Freq. 20Hz., Freq. Resp. to 4.5KHz. Sens. 95dB. (As photograph). Price: £23.50 + £3 carriage.

**8" 50 watt R.M.S. (HI-FI, P.A.)** 1 1/2" aluminium voice coil. White cone. 8 ohm imp. Res. Freq. 40Hz., Freq. Resp. to 6KHz. Sens. 92dB. Also available with black cone fitted with black metal protective grille. (As photograph). Price: White Cone £8.90, Black cone/grille £9.50 P&P £1.25.

**12" 85 watt R.M.S. McKENZIE C1285GP (LEAD GUITAR, KEYBOARD, DISCO)** 2" aluminium voice coil, aluminium centre dome, 8 ohm imp., Res. Freq. 45Hz., Freq. Resp. to 6.5KHz., Sens. 98dB. Price: £22.00 + £3 carriage.

**12" 85 watt R.M.S. McKENZIE C1285TC (P.A., DISCO)** 2" aluminium voice coil. Twin cone. 8 ohm imp., Res. Freq. 45Hz., Freq. Resp. to 14KHz. Price £22 + £3 carriage.

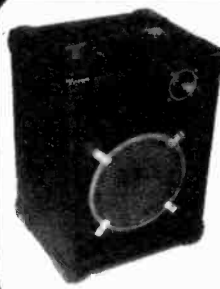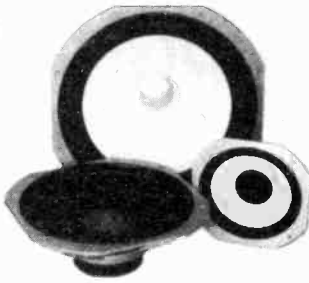**15" 150 watt R.M.S. McKENZIE C15 (BASS GUITAR, P.A.)** 3" aluminium voice coil. Die cast chassis. 8 ohm imp., Res. Freq. 40Hz., Freq. Resp. to 4KHz. Price: £47 + £4 carriage.



### OMP 80 LOUDSPEAKER

The very best in quality and value. Ported tuned cabinet in hardwearing black vinylite with protective corners and carry handle. Built and tested, employing 10in British driver and Piezo tweeter. Spec: 80 watts R.M.S. 8 ohms; 45Hz-20KHz; Size: 20in x 15in x 12in; Weight: 30 pounds.

Price: £89.00 each, £90 per pair  
Carriage: £5 each, £7 per pair

### 1K.WATT SLIDE DIMMER

- Controls loads up to 1KW
- Compact size



4 1/4" x 13" x 2 1/2"  
16

- Easy snap in fixing through panel/cabinet cut out
  - Insulated plastic case
  - Full wave control using 8amp triac
  - Conforms to BS800
  - Suitable for both resistance and inductive loads
- Innumerable applications in industry, the home, and discos/theatres etc.

Price: £11.70 each + 50p P&P (Any quantity)

### KEYBOARDS



**MEMBRANE KEYBOARDS** manufactured from a tough polycarbonate film mounted on 1mm glass fibre printed circuit board assembly incorporating silver plated contacts.

**16 way numeric keyboard** Standard keyboard providing 0-9 and A-F functions.

Size: 100mm x 100mm x 2mm. Price: £5.99 + 35p p&p  
**Alpha Numeric Keyboard** Full size 55 key non encoded keyboard with the commonly required functions in a Qwerty array. Matrix output via a 16 pin DIL socket.

Size: 350mm x 100mm x 2mm. Price: £13.99 + 50p p&p

### BSR P256 TURNTABLE


P256 turntable chassis ● S shaped tone arm

- Belt driven ● Aluminium platter
  - Precision calibrated counter balance ● Anti-skate (bias device) ● Damped cueing lever
  - 240 volt AC operation (Hz) ● Cut-out template supplied ● Completely manual arm.
- This deck has a completely manual arm and is designed primarily for disco and studio use where all the advantages of a manual arm are required.

Price £18.49 each + £3.00 P&P



### POWER AMPLIFIER MODULES

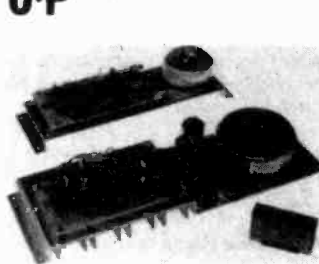

### 100 WATT R.M.S. AND 300 WATT R.M.S. MODULES

Power Amplifier Modules with integral toroidal transformer power supply, and heat sink. Supplied as one complete built and tested unit. Can be fitted in minutes. An LED Vu meter is available as an optional extra.

**SPECIFICATION:**  
Max Output Power: 110 watts R.M.S. (OMP 100) 310 watts R.M.S. (OMP 300)  
Loads: Open and short circuit proof. 4-16 ohms.  
Frequency Response: 20Hz — 25KHz ±3dB.  
Sensitivity for Max. Output: 500mV at 10K (OMP 100) 1V at 10K (OMP 300)  
T.H.D.: Less than 0.1%  
Supply: 240V 50Hz  
Sizes: OMP 100 360 x 115 x 72mm  
OMP 300 460 x 153 x 66mm  
Prices: OMP 100 £31.50 each + £2.00 P&P  
OMP 300 £89.00 each + £3.00 P&P  
Vu Meter £6.50 each + 50p P&P

### PIEZO ELECTRIC TWEETERS — MOTOROLA

Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.

TYPE 'A' (KSN2036A) 3" round with protective wire mesh, ideal for bookshelf and medium sized Hi-fi speakers. Price £4.29 each.

TYPE 'B' (KSN1005A) 3 1/2" super horn. For general purpose speakers, disco and P.A. systems etc. Price £4.99 each.


TYPE 'C' (KSN6016A) 2" x 5" wide dispersion horn. For quality Hi-fi systems and quality discos etc. Price £5.99 each.

TYPE 'D' (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-fi systems and quality discos. Price £7.99 each.

TYPE 'E' (KSN1038A) 3 1/2" horn tweeter with attractive silver finish trim. Suitable for Hi-fi monitor systems etc. Price £4.99 each.

TYPE 'F' (KSN1057A) Cased version of type 'E'. Free standing satellite tweeter. Perfect add on tweeter for conventional loudspeaker systems. Price £31.35 each.

P&P 20p ea. (or SAE for Piezo leaflets).

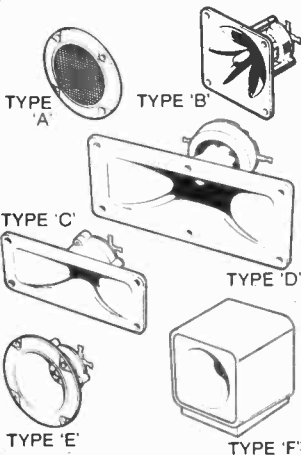

### Matching 3-way loudspeakers and crossover

Build a quality 60watt RMS system 8ohms

Build a quality 60 watt R.M.S. system.


- ★ 10" Woofer 35Hz-4.5KHz
- ★ 3" Tweeter 2.5KHz-19KHz
- ★ 5" Mid Range 600Hz-8KHz
- ★ 3-way crossover 6dB/oct 1.3 and 6KHz

Recommended Cab-size 26" x 13" x 13"  
Fitted with attractive cast aluminium fixing es-cutchions and mesh protective grills which are removable enabling a unique choice of cabinet styling. Can be mounted directly on to baffle with or without conventional speaker fabrics. All three units have aluminium centre domes and rolled foam surround. Crossover combines spring loaded loudspeaker terminals and recessed mounting panel.  
Price £22.00 per kit + £2.50 postage and packing. Available separately, prices on request.


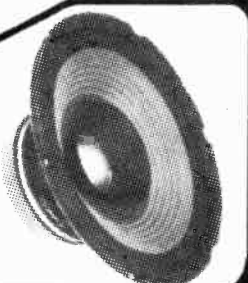
### 12" 80 watt R.M.S. loudspeaker.

A superb general purpose twin cone loudspeaker. 50 oz. magnet. 2" aluminium voice coil. Rolled surround. Resonant frequency 25Hz. Frequency response to 17KHz. Sensitivity 95dB. Impedance 8ohm. Attractive blue cone with aluminium centre dome.  
Price £17.99 each + £3.00 P&P.




# B.K. ELECTRONICS

37 Whitehouse Meadows, Eastwood, Leigh-on-Sea, Essex SS9 5TY

★ SAE for current lists ★ Official orders welcome. ★ All prices include VAT ★ Mail order only ★ All items packed (where applicable) in special energy absorbing PU foam. Callers welcome by prior appointment, please phone 0702-527572




# GET BIG POWER

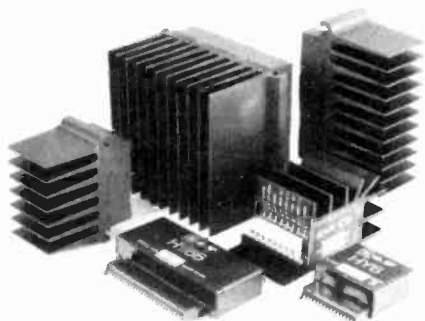
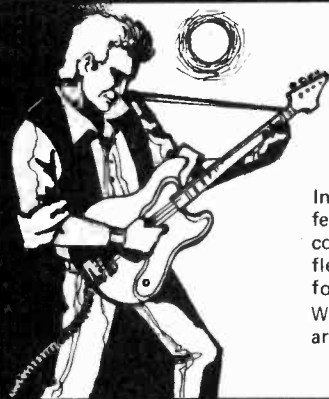
## Modular Amplifiers the third generation

Due to continuous improvements in components and design ILP now launch the largest and most advanced generation of modules ever.



### WE'RE INSTRUMENTAL IN MAKING A LOT OF POWER

In keeping with ILP's tradition of entirely self-contained modules featuring, integral heatsinks, no external components and only 5 connections required, the range has been optimized for efficiency, flexibility, reliability, easy usage, outstanding performance, value for money.

With over 10 years experience in audio amplifier technology ILP are recognised as world leaders.



#### BIPOLAR MODULES

Module Number	Output Power Watts rms	Load Impedance $\Omega$	DISTORTION		Supply Voltage Typ	Size mm	WT gms	Price inc. VAT
			T.H.D. Typ at 1KHz	I.M.D. 60Hz/7KHz 4:1				
HY30	15	4-8	0.015%	<0.006%	$\pm 18$	76 x 68 x 40	240	£8.40
HY60	30	4-8	0.015%	<0.006%	$\pm 25$	76 x 68 x 40	240	£9.55
HY6060	30 + 30	4-8	0.015%	<0.006%	$\pm 25$	120 x 78 x 40	420	£18.69
HY124	60	4	0.01%	<0.006%	$\pm 26$	120 x 78 x 40	410	£20.75
HY128	60	8	0.01%	<0.006%	$\pm 35$	120 x 78 x 40	410	£20.75
HY244	120	4	0.01%	<0.006%	$\pm 35$	120 x 78 x 50	520	£25.47
HY248	120	8	0.01%	<0.006%	$\pm 50$	120 x 78 x 50	520	£25.47
HY364	180	4	0.01%	<0.006%	$\pm 45$	120 x 78 x 100	1030	£38.41
HY368	180	8	0.01%	<0.006%	$\pm 60$	120 x 78 x 100	1030	£38.41

Protection: Full load line, Slew Rate: 15V/ $\mu$ s. Risettime: 5 $\mu$ s. S/N ratio: 100db. Frequency response (-3dB) 15Hz - 50KHz. Input sensitivity: 500mV rms. Input Impedance: 100K  $\Omega$ . Damping factor: 100Hz >400.

#### PRE-AMP SYSTEMS

Module Number	Module	Functions	Current Required	Price inc. VAT
HY6	Mono pre amp	Mic/Mag, Cartridge/Tuner/Tape/Aux + Vol/Bass/Treble	10mA	£7.60
HY66	Stereo pre amp	Mic/Mag, Cartridge/Tuner/Tape/Aux + Vol/Bass/Treble/Balance	20mA	£14.32
HY73	Guitar pre amp	Two Guitar (Bass, Lead) and Mic + separate Volume Bass Treble + Mix	20mA	£15.36
HY78	Stereo pre amp	As HY66 less tone controls	20mA	£14.20

Most pre-amp modules can be driven by the PSU driving the main power amp. A separate PSU 30 is available purely for pre amp modules if required for £5.47 (inc. VAT). Pre-amp and mixing modules in 18 different variations. Please send for details.

#### Mounting Boards

For ease of construction we recommend the B6 for modules HY6-HY13 £1.05 (inc. VAT) and the B66 for modules HY66-HY78 £1.29 (inc. VAT).

#### POWER SUPPLY UNITS (Incorporating our own toroidal transformers)

Model Number	For Use With	Price inc. VAT
PSU 21X	1 or 2 HY30	£11.93
PSU 41X	1 or 2 HY60, 1 x HY6060, 1 x HY124	£13.93
PSU 42X	1 x HY128	£15.90
PSU 43X	1 x MOS128	£16.70
PSU 51X	2 x HY128, 1 x HY244	£17.07

Please note: X in part no. indicates primary voltage. Please insert "0" in place of X for 110V, "1" in place of X for 220V, and "2" in place of X for 240V.

#### MOSFET MODULES

Module Number	Output Power Watts rms	Load Impedance $\Omega$	DISTORTION		Supply Voltage Typ	Size mm	WT gms	Price inc. VAT
			T.H.D. Typ at 1KHz	I.M.D. 60Hz/7KHz 4:1				
MOS 128	60	4-8	<0.005%	<0.006%	$\pm 45$	120 x 78 x 40	420	£30.41
MOS 248	120	4-8	<0.005%	<0.006%	$\pm 55$	120 x 78 x 80	850	£39.86
MOS 364	180	4	<0.005%	<0.006%	$\pm 55$	120 x 78 x 100	1025	£45.54

Protection: Able to cope with complex loads without the need for very special protection circuitry (fuses will suffice).

Slew rate: 20V/ $\mu$ s. Rise time: 3 $\mu$ s. S/N ratio: 100db

Frequency response (-3dB): 15Hz - 100KHz. Input sensitivity: 500mV rms

Input impedance: 100K  $\Omega$ . Damping factor: 100Hz >400.

#### 'NEW to ILP' In Car Entertainments

##### C15

Mono Power Booster Amplifier to increase the output of your existing car radio or cassette player to a nominal 15 watts rms.

Very easy to use.

Robust construction.

£9.14 (inc. VAT)

Mounts anywhere in car.

Automatic switch on.

Output power maximum 22w peak into 4 $\Omega$

Frequency response (-3dB) 15Hz to 30KHz, T.H.D. 0.1% at 10w 1KHz

S/N ratio (DIN AUDIO) 80dB, Load Impedance 3 $\Omega$

Input Sensitivity and Impedance (selectable) 700mV rms into 15K $\Omega$ . 3V rms into 8 $\Omega$

Size 95 x 48 x 50mm. Weight 256 gms.

##### C1515

Stereo version of C15.

£17.19 (inc. VAT)

Size 95 x 40 x 80. Weight 410 gms.

Model Number	For Use With	Price inc. VAT
PSU 52X	2 x HY124	£17.07
PSU 53X	2 x MOS128	£17.86
PSU 54X	1 x HY248	£17.86
PSU 55X	1 x MOS248	£19.52
PSU 71X	2 x HY244	£21.75

Model Number	For Use With	Price inc. VAT
PSU 72X	2 x HY248	£22.54
PSU 73X	1 x HY364	£22.54
PSU 74X	1 x HY368	£24.20
PSU 75X	2 x MOS248, 1 x MOS368	£24.20

# WITH A LOT OF HELP FROM




## PROFESSIONAL HI-FI THAT EVERY ENTHUSIAST CAN HANDLE...

### Unicase

Over the years ILP has been aware of the need for a complete packaging system for its products, it has now developed a unique system which meets all the requirements for ease of assembly, adaptability, ruggedness, modern styling and above all price.

Each Unicase kit contains all the hardware required down to the last nut and bolt to build a complete unit without the need for any special tools.

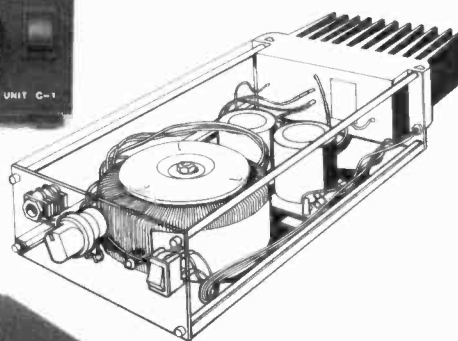Because of ILP's modular approach, "open plan" construction is used and final assembly of the unit parts forms a compact aesthetic unit. By this method construction can be achieved in under two hours with little experience of electronic wiring and mechanical assembly.



### Hi Fi Separates

**UC1 PRE AMP UNIT:** Incorporates the HY78 to provide a "no frills", low distortion, (<0.01%), stereo control unit, providing inputs for magnetic cartridge, tuner, and tape/monitor facilities. This unit provides the heart of the hi fi system and can be used in conjunction with any of the UP Unicase series of power amps. For ultimate hum rejection the UC1 draws its power from the power amp unit.

**POWER AMPS:** The UP series feature a clean line front panel incorporating on/off switch and concealed indicator. They are designed to compliment the style of the UC1 pre-amp. Performance for each unit which includes the appropriate power supply, is as specified on the facing page.

### Power Slaves

Our power slaves, which have numerous uses i.e. instrument, discotheque, sound reinforcement, feature in addition to the hi fi series, front panel input jack, level control, and a carrying handle. Providing the smallest, lowest cost, slave on the market in this format.

#### UNICASES

HiFi Separates					Price inc. VAT
UC1	Preamp				£29.95
UP1X	30 + 30W/4-8Ω	Bipolar	Stereo	HiFi	£54.95
UP2X	60W/4Ω	Bipolar	Mono	HiFi	£54.95
UP3X	60W/8Ω	Bipolar	Mono	HiFi	£54.95
UP4X	120W/4Ω	Bipolar	Mono	HiFi	£74.95
UP5X	120W/8Ω	Bipolar	Mono	HiFi	£74.95
UP6X	60W/4-8Ω	MOS	Mono	HiFi	£64.95
UP7X	120W/4-8Ω	MOS	Mono	HiFi	£84.95
Power Slaves					
US1X	60W/4Ω	Bipolar	Power	Slave	£59.95
US2X	120W/4Ω	Bipolar	Power	Slave	£79.95
US3X	60W/4-8Ω	MOS	Power	Slave	£69.95
US4X	120W/4-8Ω	MOS	Power	Slave	£89.95

Please note X in part number denotes mains voltage. Please insert 'O' in place of X for 110V, '1' in place of X for 220V (Europe), and '2' in place of X for 240V (U.K.) All units except UC1 incorporate our own toroidal transformers.

#### TO ORDER USING OUR FREEPOST FACILITY

Fill in the coupon as shown, or write details on a separate sheet of paper, quoting the name and date of this journal. By sending your order to our address as shown at the bottom of the page opposite, with FREEPOST clearly shown on the envelope, you need not stamp it. We pay postage for you. Cheques and money orders must be crossed and made payable to I.L.P. Electronics Ltd. if sending cash, it must be by registered post. To pay C.O.D. please add £1 to TOTAL value of order.

#### PAYMENT MAY BE MADE BY ACCESS OR BARCLAYCARD IF REQUIRED



Post to: ILP Electronics Ltd., Freepost 4, Graham Bell House, Roper Close, Canterbury CT2 7EP, Kent, England. Telephone: (0227) 54778. Technical: (0227) 64723. Telex: 965780.

Please send me the following \_\_\_\_\_

Total purchase price \_\_\_\_\_

I enclose Cheque  Postal Orders  Int. Money Order

Please debit my Access/Barclaycard No. \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

Signature \_\_\_\_\_



# ZX81 MUSIC BOARD

With the circuit and construction covered last month, we now turn to the software routines that enable you to use this project to the full. Design and development by M. P. Moore.

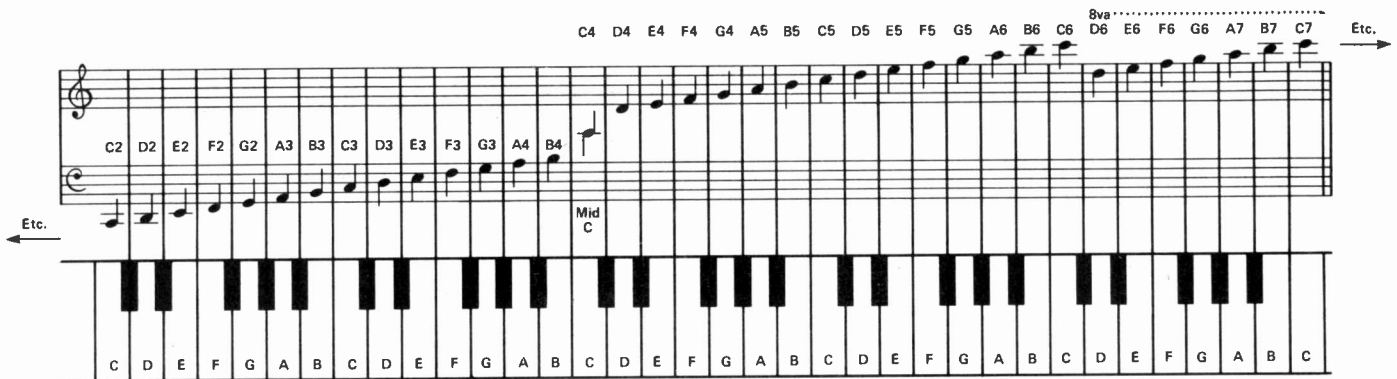


Fig. 1 Table of notes as used by the input routine.

## THE MUSIC

1	REM (our machine code)	158	IF N\$ < > "0" THEN GOTO	288	LET D = D + 1
2	CLS		163	289	POKE 16564, (PEEK D)
5	DIM H(7)	159	POKE D,0	290	LET D = D + 1
10	FOR N = 1 TO 7	160	POKE (D + 1),0	291	POKE 16565, (PEEK D)
15	LET H(N) = 76	161	PRINT "[6 SPC]";	292	LET D = D + 1
20	NEXT N	162	GOTO 170	293	POKE 16566, (PEEK D)
25	PRINT "CLEAR MUSIC SPACE	163	IF N\$ = "L" THEN GOTO	294	LET D = D + 1
	(Y OR N) OR PLAY (P) OR		350	295	RAND USR 16543
	LIST (L)?"	164	POKE D,N	296	PAUSE S
30	IF INKEY\$ = "N" THEN	165	POKE (D + 1),H	297	POKE 16437,22
	GOTO 55	170	GOSUB 2000	298	GOTO 282
31	IF INKEY\$ = "P" THEN	185	NEXT D	299	LET X = 16561
	GOTO 200	200	CLS	300	FOR D = 1 TO 6
33	IF INKEY\$ = "L" THEN	201	PRINT "SET VOLUMES (Y OR	305	POKE X,0
	GOTO 350		N), EDIT (E)", "OR LIST (L)?"	306	LET X = X + 1
35	IF INKEY\$ < > "Y" THEN	202	SLOW	307	NEXT D
	GOTO 30	205	IF INKEY\$ = "Y" THEN	308	SLOW
36	FAST		GOTO 215	310	RAND USR 16543
40	FOR N = 16670 TO 21670	206	IF INKEY\$ = "E" THEN	315	GOTO 200
45	POKE N,255		GOTO 136	350	CLS
50	NEXT N	207	IF INKEY\$ = "L" THEN	351	PRINT "LIST FROM LINE
51	SLOW		GOTO 350		NO.:";
55	PRINT "SHARPS?";	208	IF INKEY\$ = "N" THEN	355	INPUT Z
60	LET Z = 78		GOTO 265	360	PRINT Z
65	GOSUB 1150	210	GOTO 205	365	PRINT AT 21,0;Z;"[3 SPC]";
100	PRINT "FLATS?";	215	PRINT "A=";	366	FAST
105	LET Z = 74	220	INPUT S	370	LET X = 0
110	GOSUB 1150	225	POKE 16540,S	371	LET K = (Z - 1) * 6 + 16734
136	CLS	230	PRINT S;"B=";	372	FOR D = (Z - 1) * 6 +
137	PRINT "EDIT FROM LINE	235	INPUT S		16670 TO (Z - 1) * 6 +
	NO.:";	240	PRINT S;"C=";		16734 STEP 2
140	INPUT Z	245	POKE 16541,S	375	LET Y = 1
141	PRINT Z	250	INPUT S	380	LET L = PEEK D
142	PRINT AT 21,0;Z;"[3 SPC]";	255	POKE 16542,S	385	LET M = PEEK (D + 1)
143	LET X = 0	260	PRINT S	386	IF L = 255 AND M = 255
144	FOR D = (Z - 1)*6 + 16670	265	PRINT "SPEED?"		THEN PRINT " STOP "
	TO 21670 STEP 2	270	INPUT S	387	IF L = 255 AND M = 255
148	SLOW	271	PRINT "PLAY FROM LINE		THEN GOTO 491
149	COSUB 1000		NO.?"	388	IF L = 0 AND M = 0 THEN
150	IF N\$ < > "5" THEN GOTO	272	INPUT D	389	PRINT "[3 SPC]";
	155	275	LET D = (D - 1)*6 + 16670		IF L = 0 AND M = 0 THEN
151	LET Z = Z - 2	276	CLS	390	GOTO 470
152	LET D = D - 8	280	RAND USR 16514	395	LET L = L + M * 256
153	LET X = 2	281	FAST		IF L < 1966 THEN LET Y = Y
154	GOTO 170	282	IF PEEK D = 255 THEN		+ 1
155	IF N\$ = "R" THEN GOTO		GOTO 299	400	IF L < 1966 THEN LET L = L
	510	283	POKE 16561, (PEEK D)		* 2
156	IF N\$ = "E" THEN GOTO	284	LET D = D + 1	405	IF L < 1966 THEN GOTO 395
	136	285	POKE 16562, (PEEK D)	410	LET M = L/256
157	IF N\$ = "P" THEN GOTO	286	LET D = D + 1	415	LET M = INT M
	200	287	POKE 16563, (PEEK D)		

The music program allows the ZX81 to play up to three notes simultaneously. The range is from A octave 1 upwards, where middle C is C4 (see Fig. 1). There is sufficient memory space with a 16K expansion to enter 833 chords of music. Everything possible has been done to facilitate the entering of music. The key signature (sharps or flats) is set to begin with and remains set until changed; changes may be made during the entering of music; each of the three channels has an independently set volume; the same note repeated on one channel will give a continuous note, but if played on alternating channels, will give a repetitive note.

The symbols used are + (sharp), - (flat) and = (natural). The functions available are **EDIT**, which is used for entering and editing music already entered, and includes **BACKSPACE** and **REPEAT** functions;

**LIST**, which allows you to read the music entered, and **PLAY**.

Program "M" is very long and takes about five minutes to load. Having loaded the program the sequence of operations is as follows:-

Type **GOTO 2 NEWLINE**.

The computer will ask: **CLEAR MUSIC SPACE (Y OR N) OR PLAY (P) OR LIST (L)?**

The second and third functions don't interest us at the moment, and since the music space is clear to start with, type **N**.

The computer now asks **SHARPS?** if the key signature contains sharps, type them in (in any order) followed by **NEWLINE**.

If there are no sharps type **0 NEWLINE**.

The computer now asks **FLATS?**

Deal with the question as for sharps.

The computer asks **EDIT FROM**

## BUYLINES

Petron Electronics supply a full kit of parts for this project; we must apologise to them and any purchasers of the kit for the incorrect price given last month. The complete kit including PCB, all components, comprehensive user's manual and the software cassette containing this month's programs, costs £24.95 all inclusive. The board is also available ready-built together with manual and cassette, for £29.95, or in a smart ABS plastic case for only £34.90. Please state whether you require the board to be wired for mono or stereo. A demonstration cassette is available for 95p all inclusive, while the manual may be purchased separately for £1.25, refunded upon subsequent purchase of a kit. Petron Electronics may be found at 1 Courtlands Road, Newton Abbot, Devon.

## LINE NO.

Since you are starting from scratch enter **1 NEWLINE**.

The computer is now ready to accept up to 833 'lines' of music. A

## PROGRAM

420	IF L > = 256 THEN LET L = L - 256	561	LET D = (E - 2)	1100	LET H = INT H
425	IF L > = 256 THEN GOTO 420	562	SLOW	1105	IF N > = 256 THEN LET N = N - 256
430	POKE 16619,L	565	GOTO 185	1110	IF N > = 256 THEN GOTO 1105
435	POKE 16620,M	1000	INPUT N\$	1115	RETURN
440	LET L = USR 16608	1001	IF N\$ = "R" OR N\$ = "5" OR N\$ = "0" OR N\$ = "P" OR N\$ = "L" OR N\$ = "E" THEN RETURN	1150	INPUT H\$
445	LET L = L/4	1002	IF N\$(1) < "A" OR N\$(1) > "G" THEN GOTO 1000	1155	IF H\$ < "A" AND H\$ < > "0" OR H\$ > "G" THEN GOTO 1150
450	LET M = INT L - 19	1005	IF LEN N\$ < 2 THEN GOTO 1000	1160	IF H\$ = "0" THEN RETURN
454	LET M = INT M	1008	FAST	1165	FOR N = 1 TO LEN H\$
455	IF M = 37 AND INT L < > L THEN LET Y = Y - 1	1009	LET H = CODE N\$ - 37	1170	LET H = CODE H\$(N)
456	IF M = 37 THEN LET M = 44	1010	IF LEN N\$ 2 THEN GOTO 1030	1175	LET H = H - 37
460	PRINT CHR\$ M;	1015	IF N\$(2) = "-" THEN LET H(H) = 74	1180	LET H(H) = Z
465	IF INT L < L THEN PRINT "+";	1020	IF N\$(2) = "+" THEN LET H(H) = 78	1185	NEXT N
466	IF INT L = L THEN PRINT "=";	1025	IF N\$(2) = " " THEN LET H(H) = 76	1190	PRINT H\$
468	PRINT Y;	1030	LET N = CODE N\$	1195	RETURN
470	PRINT "[3 SPC]";	1035	LET N = N * 4	2000	LET X = X + 1
471	IF D = K THEN GOTO 491	1036	IF N = 160 AND H(H) = 74 OR N = 172 AND H(H) = 74 THEN LET N = N - 2	2005	IF X < 3 THEN RETURN
472	GOSUB 2000	1040	LET N = N + H(H)	2010	LET X = 0
490	NEXT D	1045	POKE 16581,N	2015	LET Z = Z + 1
491	SLOW	1050	LET N = USR 16567	2020	SCROLL
495	PRINT AT 0,0;	1055	PRINT N\$(1);	2025	SCROLL
496	IF INKEY\$ = "E" THEN GOTO 136	1057	IF H(H) = 78 THEN PRINT "+";	2030	PRINT Z; "[3 SPC]";
500	IF INKEY\$ = "P" THEN GOTO 200	1058	IF H(H) = 76 THEN PRINT "=";	2035	RETURN
501	IF INKEY\$ = "L" THEN GOTO 350	1059	IF H(H) = 74 THEN PRINT "-"		
505	GOTO 496	1060	IF LEN N\$ = 2 THEN LET H = CODE N\$(2)		
510	PRINT "REPEAT FROM LINE NO.?"	1065	IF LEN N\$ = 3 THEN LET H = CODE N\$(3)		
511	SCROLL	1066	PRINT CHR\$ H; "[3 SPC]";		
515	INPUT C	1067	LET H = H - 28		
516	LET E = D	1070	LET H = H - H - H		
517	FAST	1075	FOR H = H TO -1		
520	FOR C = C TO (Z - 1)	1080	LET N = N/2		
525	LET Q = (C-1) * 6 + 16670	1085	NEXT H		
530	FOR E = E TO E + 5	1086	LET N = N * 2		
531	IF E = 21670 THEN GOTO 200	1090	LET N = INT N		
535	POKE E,PEEK Q	1095	LET H = N/256		
540	LET Q = Q + 1				
545	NEXT E				
550	PRINT "DITTO";				
552	LET X = 2				
555	GOSUB 2000				
560	NEXT C				

Machine code at line 1:-

3E	07	D3	FF	3E	38	D3	F7
21	9C	40	01	08	03	79	D3
FF	0C	5E	7B	D3	F7	23	10
F5	C9	xx	xx	xx	21	B1	40
01	00	06	5E	79	D3	FF	7B
D3	F7	23	0C	10	F5	C9	xx
xx	xx	xx	xx	xx	3E	07	D3
FF	3E	78	D3	F7	3E	0E	D3
FF	01	FB	xx	78	04	D3	F7
3E	0F	D3	FF	ED	58	3E	0E
D3	FF	78	D3	F7	3E	0F	D3
FF	ED	50	D5	C1	C9	3E	07
D3	FF	3E	78	D3	F7	06	FE
21	xx	xx	7D	E6	80	6F	3E
0E	D3	FF	78	D3	F7	3E	0F
D3	FF	DB	FB	E6	80	BD	28
05	05	05	18	EA	00	3E	0E
D3	FF	04	78	D3	F7	3E	0F
D3	FF	DB	FB	BC	20	E9	05
48	06	00	C9				

Approximately 5,000 memory positions are reserved here for music.

## HOW IT WORKS — MUSIC PROGRAM

Array H is a one-dimensional seven-position array which is used to keep a record of whether each note A - G is natural, sharp or flat. Lines 5 to 20 load the value for natural (76) into each position of array H. Lines 25 to 35, depending on the answer typed in, make the computer jump accordingly or continue from line 36. Lines 36 to 51 clear the memory space set aside for music by POKING the stop code 255 to each memory location reserved. In conjunction with the BASIC subroutine at lines 1150 to 1195, lines 55 to 110 set the initial key signature by making the value of the appropriate position of H equal 78 for sharps and 74 for flats. Lines 137 to 142 make Z equal to the current line number for entering and editing music. Variable X is used to keep a record of which channel note you are currently entering. Line 144 sets up a loop using D where D starts with the address of the memory space corresponding to line number (Z) and ends with the value 21670, which is the last available music space. Line 149 calls the BASIC subroutine at line 1000. This subroutine inputs a key-press or series of key-presses which will either be note data, silence or one of the five available functions: REPEAT (R), BACKSPACE (S), PLAY (P), LIST (L) or EDIT (E). If silence or one of the functions is entered the computer returns to line 150.

If note data was entered the computer continues at line 1002 with a check that the data entered was in fact valid note data. Line 1009 makes variable H equal to the code of the note entered minus 37. If the data entered does not contain an appending sharp, flat or natural sign, line 1010 makes the computer jump to line 1030. Lines 1015 to 1025 adjust array H accordingly (sharp, flat or natural) depending on the second character of N\$ (ie N\$(2)). Lines 1030 to 1040 load the variable N with the code of the note entered (ie N\$(1)) and adjust this value together with corrective maths depending on the note (sharp, flat or natural) stored in array H to provide the address of the basic note data in the pre-programmed PROM. Lines 1045 to 1050 POKE this data to memory position 16581 and a machine code subroutine based at 16567 returns N with the basic tone period value of this note, ie the lowest octave. Lines 1055 to 1059 print the note and its sign on the screen. Lines 1060 to 1065 make variable H equal to the code of the octave number entered depending on whether N\$ is two or three characters long. Line 1066 prints the octave. Lines 1067 to 1075 correct the value of H and set up a loop using H where  $H = H - 1$ . This loop is used to divide the basic data in N by 2 (this has the effect of raising the note one octave each time N is divided by 2) until the correct tone period data is obtained. Line 1086 corrects the tone period value of N, otherwise it would be one octave too high. Lines 1095 to 1110 set H to equal the most significant byte of the note and N to equal the least significant byte.

Line 115 returns the computer from this subroutine at line 1001 because:-  
1) BACKSPACE function (S) was entered; it runs through lines 151 to 154 adjusting the values of Z, D and X to effect a backspace. Lines 155 to 157 check to see if the computer was returned with functions R, E or P and if so, it jumps

accordingly.

2) If 0 was entered, the computer runs through lines 159 to 162 entering silence in the current note position and printing spaces in that note position on the screen.

3) If L was entered, the computer jumps to line 350 to list data.

4) If P was entered, the computer jumps to line 200 to play the music.

5) If E was entered, the computer goes back to line 136 to restart the edit function.

6) If R was entered, the computer jumps to line 510.

7) If note data was entered, the computer runs through lines 164 and 165 which POKE the tone period data in the current memory position.

Line 170 calls a BASIC subroutine located at 2000. This subroutine simply checks whether or not the data just dealt with was the third note of a chord, and if so, scrolls the screen up two lines and prints a new line number before returning. Line 185 causes the computer to loop back to line 144 ready to enter the next string of music data. If all the available memory space were taken up, the computer would fall through line 185 and actuate the section of the program which plays music from line 200.

Had the R function returned the computer from the subroutine at 1002 the computer would have jumped to line 510 which puts the question FROM CHORD NO. ? Lines 511 to 565 perform a block copy of the lines specified and adjust the display accordingly. Lines 200 to 210 ask whether you want to set channel volumes, or edit or list. If the answer is E the computer jumps back to the EDIT program at line 136; if L is entered the computer jumps to the LIST program at line 350; if you didn't want to set the volumes so that the answer was N, the computer jumps to line 265. Lines 215 to 260 input volumes for the three channels A, B and C and POKE the volumes required to memory locations 16540, 16541 and 16542 respectively. Lines 265 to 270 input the value of the pause used in line 296 to regulate the speed at which music is played. Line 276 sets D to the address of the first memory position containing music data. Line 280 calls a machine code subroutine based at line 16514 which initialises the PSG for three channels of sound. This subroutine programs the PSG with the volumes held in memory locations 16540 to 16542. Line 282 checks the current music memory position for the STOP code (255) and if this position equals 255 it identifies this as the end of the music, and the computer jumps to 299. Lines 283 to 294 POKE to memory positions 16561 to 16566 the six bytes of tone period data for the next chord to be played.

It may be thought that memory space could have been saved by making lines 283 to 294 a loop. This proved, however, to have an unacceptable slowing effect on the maximum speed available (ie 0). Line 295 calls a machine code subroutine which relays the data in memory position 16561 to 16566 to the PSG, thus producing the next chord. Line 296 is the pause regulating the speed using the variable S and, since this program section is run in the FAST mode, line 297 POKES Sinclair's obligatory 255 to memory position 16437. Line 298 causes the computer to jump back to line 282 to

continue with the next chord. As we have seen, when the end of the music is reached, the computer jumps to line 299. Lines 299 to 307 load the silence value 0 to memory positions 16561 through 16566 and line 310 outputs this last set of data to the PSG using the above-mentioned machine code subroutine located at 16543. Line 315 then causes the computer to jump back to line 200.

The LIST (L) function starts at line 350. Lines 351 to 365 input and print the line number that is being listed which is held in variable Z. Variable X is used to keep a record of which channel data is being calculated. Line 371 sets the variable K to the memory address of the last note data to be listed in one full screen (providing a STOP code 255 is not encountered first). Line 372 sets variable D up in a loop, where D starts with the value of the first music location to be listed and thereafter holds the current memory position of data being calculated. Variable Y is used to keep a record of the octave as it is being calculated in lines 395 to 405. Lines 380 to 385 set variables L and M to the value of the data for the current note being listed. Lines 386 and 387 check for the STOP code 255 in variables L and M, and if it is detected the computer prints STOP and jumps to line 491. Lines 388 and 389 check for silence (0) and if detected the computer prints spaces and then jumps to line 470. Line 390 sets variable L to the value of the complete tone period. Lines 395 to 405 calculate the octave in Y by multiplying the value of L by 2 until it is within range of the basic octave values (ie greater than or equal to 1966).

Lines 410 to 425 reconstitute this new data into variables L and M. At this point the number held in L and M will be the same as a number in the basic octave of notes in the pre-programmed PROM. Lines 430 to 435 POKE this data to memory positions 16619 and 16620. Line 440 calls up a machine code subroutine which returns with L set to the memory position of the PROM where the note data POKED in lines 430 and 435 is to be found. Lines 445 to 455 reconstitute the value of L in variable M so that M contains the Sinclair code for the correct note A to G. Line 456 runs a check on variable M, so that if  $M = 37$  (ie G sharp) the computer, rather than printing 9, prints G (code 44). Line 460 prints the note thus calculated. Line 465 checks the value of L to see if it is a whole number. If it is not, due to the maths in lines 445 to 455, the note will be a sharp and line 465 prints + (sharp). Line 466 likewise checks to see if L is a whole number, and if it is, prints the sign for natural (=). Line 467 checks for the note being G sharp and corrects the octave value in Y accordingly. Lines 468 to 470 print the octave and the next three spaces. When a screen-full of data has been listed, D will equal K. Line 471 checks for this and if  $D = K$  the computer jumps to line 491. As with the EDIT function (E), the LIST function uses the subroutine at line 2000 to keep the VDU display correct. When it has finished listing music the computer continues at line 491. At lines 495 to 505 the computer waits for a further command EDIT (E), PLAY (P) or LIST (L), and jumps accordingly.

# PROJECT: ZX81 Music Board



THIS BAR SHOULD BE ENTERED AS FOLLOWS

LINE No.	Ch1	Ch2	Ch3
1	E4 NEWLINE	0 NEWLINE	0 NEWLINE
2	C5 NEWLINE	0 NEWLINE	0 NEWLINE
3	C5 NEWLINE	0 NEWLINE	0 NEWLINE
4	E4 NEWLINE	0 NEWLINE	0 NEWLINE
5	C5 NEWLINE	0 NEWLINE	0 NEWLINE
6	C5 NEWLINE	0 NEWLINE	0 NEWLINE
7	E4 NEWLINE	0 NEWLINE	0 NEWLINE
8	C5 NEWLINE	0 NEWLINE	0 NEWLINE

Fig. 2 Calculation of the number of lines in a bar.

'line' of computer music is a note (or silence) entered in each of the three channels A, B and C. Channels A and B are played through one audio output and C through the other if a stereo amplifier is used.

When copying music you must find the shortest note in the score: longer notes must be converted to the equivalent multiple of the shortest note to find the number of computer 'lines' in a bar (see Fig. 2). Notes 1, 3, 5 and 6 in the example are half the length of notes 2 and 4. The total number of computer 'lines' in the bar is therefore 8.

A note repeated on the same channel will sound as one continuous note. If the notes are to sound distinct, you must change from one channel to another (see Fig. 3).

Let us go back to our instruction **1 NEWLINE**.

The computer is now displaying 1 at the bottom left-hand corner of the screen. It is waiting for notes to be entered in channels A, B and C. Supposing you wish to enter A below middle C in channel A, silence in channel B, and E below middle C in channel C. Type:-

```
A4 NEWLINE
0 NEWLINE
E3 NEWLINE
```

The computer now displays on the screen:-

```
1 A = 4           E = 3
2
```

It is now waiting for the second 'line' of music.

Supposing the key signature has been set as 2 sharps (F and C) and the following is now entered:-

```
C4 NEWLINE
A3 NEWLINE
F3 NEWLINE
```

The computer now displays on the screen:-

```
1 A = 4           E = 3
2 C + 4         A = 3     F + 3
3
```

The computer has automatically made F and C into sharps, and is now waiting for 'line' 3 of music. If you now want to make C and F natural, type:-

```
C = 4 NEWLINE
A3 NEWLINE
F = 3 NEWLINE
```

The computer now displays on the screen:-

```
1 A = 4           E = 3
2 C + 4         A = 3     F + 3
3 C = 4         A = 3     F = 3
4
```

The computer is waiting for 'line' 4 of music. The same procedure applies, of course, for changing notes from flat to natural and vice-versa.

The **BACKSPACE** function enables you to backspace as required from any point in the music. The instruction is:- **5 NEWLINE**.

The **REPEAT** function allows the repetition of line(s) from the line specified to the line you have reached. Instruction:- **R NEWLINE**.

The computer will ask:- **FROM CHORD NO.**

Type in the line number from which you wish to repeat, followed by **NEWLINE**.

The computer will now repeat the line(s) requested.

**PLAYING** of music is effected through the instruction:- **P NEWLINE**

Wait for the screen to clear. The computer will now print:- **SET VOLUMES (Y OR N) OR EDIT (E) OR LIST (L)?**

If you want to play the music and have not already set the volumes, type **Y**.

The computer now prints:- **A =** Volumes range from 0 (silence) to 15 (loudest).

Type in the volume you require for channel A, followed by **NEWLINE**.

The computer repeats the question for channel B, and when dealt with, C. It will then print:- **SPEED?**

Speeds vary from 0 (fastest) upwards where 50 is approximately one second per computer 'line' or chord. Type in the speed you require, followed by **NEWLINE** and the computer will ask **PLAY FROM LINE NO. ?**

This question is answered by typing in the line number you wish the computer to start playing from. To start at the beginning type **1** followed by **NEWLINE**: the computer will now play the music you have entered.

When the music ends, the computer will ask:- **SET VOLUMES (Y OR N) OR EDIT (E) OR LIST (L)?**



LINE No.	Ch1	Ch2	Ch3
1	G4 NEWLINE	0 NEWLINE	0 NEWLINE
2	G4 NEWLINE	0 NEWLINE	0 NEWLINE
3	0 NEWLINE	G4 NEWLINE	0 NEWLINE
4	G4 NEWLINE	0 NEWLINE	0 NEWLINE
5	G4 NEWLINE	0 NEWLINE	0 NEWLINE
6	0 NEWLINE	G4 NEWLINE	0 NEWLINE
7	G4 NEWLINE	0 NEWLINE	0 NEWLINE
8	G4 NEWLINE	0 NEWLINE	0 NEWLINE
9	G4 NEWLINE	0 NEWLINE	0 NEWLINE

Fig. 3 Example of repetitive notes.

If you want to play the music again without changing the volumes, type **N** and the computer asks:- **SPEED?** Enter the speed as before and the music will be played again. If however you wish to change the volumes or one or more channels, type **Y** and proceed as before.

**LISTING** of music entered is effected by typing **L NEWLINE** and the computer will ask:- **LIST FROM LINE NO.** Type in the line you wish to start listing from, followed by **NEWLINE**.



The screen will go grey for about 20 seconds and then the computer will have printed 11 lines of music, starting from the line number you typed. You may now type **P** or **E** or **L** depending on which function you wish to use; to continue listing type **L** and give the line number that would carry on from where the first listing ended; to make alterations to the music or to enter more music, type **E**, and to play the music, type **P**.

## Devising Your Own Sound Effects

The third program on the software cassette effectively gives you direct access to the registers in the PSG. These registers are programmed with data to build up sound effects. The following is a short summary of the registers used and their functions.

Registers 0 to 5 determine the pitch (frequency) of the three notes on channels A, B and C. Registers 0, 2 and 4 are used to fine-tune the frequency of A, B and C respectively. Registers 1, 3 and 5 coarse-tune the frequencies. Data to the fine tune registers can vary from 0 to 255, and data to the coarse tune registers from 0 to 15. Register 6 can vary from 0 to 31. This sets the pitch of any white noise to be included. Register 7 is the enable register. Bits D0 to D5 enable noise and/or sound on channels A, B and C. 0 in a bit of



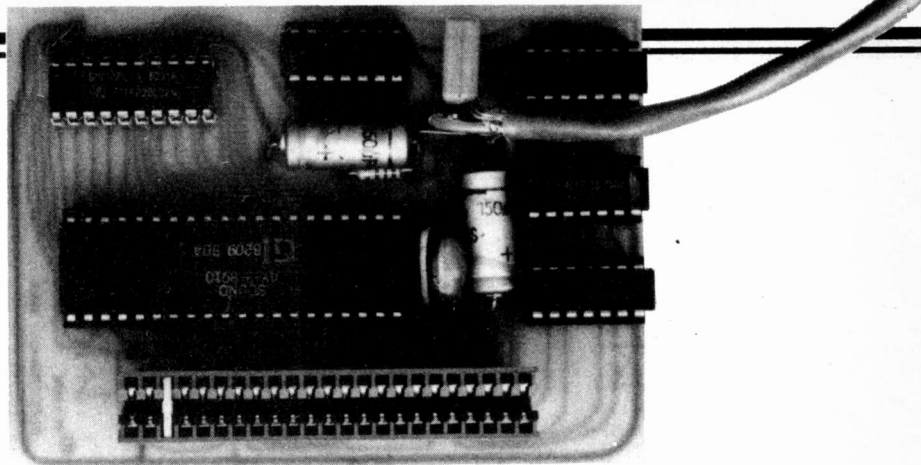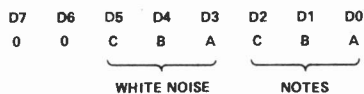

**Fig. 4** The functions of the bits in PSG register 7.

this register enables a function, 1 disables it (see Fig. 4). Registers 8, 9 and 10 set the volumes of channels A, B and C respectively. These can vary from 0 (off) to 15 (loudest). If you send the number 16 to any of these registers, the volume of channels thus set will be varied according to data in registers 11, 12 and 13, the envelope generator, as follows. Register 11 is used to fine-tune the envelope period; data sent to this register can vary from 0 to 255. Register 12 is used to coarse-tune the envelope period and data to this register can also vary from 0 to 255. Register 13 selects the shape of the envelope generator's waveform (Fig. 5).

Now, connect up your amplifier, keeping the volume fairly low, and load the third program ("D") from the software cassette. Type **GOTO 2 NEWLINE**. The computer will now print:-  
**YOU HAVE A CHOICE OF:**  
**A (TO HEAR THE SOUND AGAIN)**  
**R (TO ENTER ALL NEW DATA)**  
**C (TO CHANGE SPECIFIC DATA)**  
**L (TO LIST DATA)**  
**S (TO SILENCE THE PSG)**

Since you have not yet entered any data, type **R**. The screen will clear and the computer now prints:-

**REGISTER 0 DATA?**  
 Type in **0** as the data for register 0, followed by **NEWLINE**. The computer will respond:-  
**REGISTER 1 DATA?**  
 Type in **0** as the data for register 1, followed by **NEWLINE**. The computer will continue to request data for all registers in this manner. As an example, give it the following:-

Reg. 0 1 2 3 4 5 6 7 8 9 10 11-12 13

Data  
 0 0 0 0 0 31 7 16 16 16 255 40 9  
 If you examine the data you have just entered, you will see how the computer generated the sound of cannon fire. This data for cannon fire is contained in the PROM. The computer now repeats the question at the beginning of the program. If you type **A**, the computer will repeat the sound and will again ask the same question.

Now type **C**. The computer will respond with:- **REGISTER?**

**This little board does all the hard work.**

Type **6 NEWLINE**. The computer will now ask:- **DATA?**  
 Type **8 NEWLINE**. In response to the next question **REGISTER?** type **12 NEWLINE** and in response to **DATA?** type **5 NEWLINE**. Now type **99 NEWLINE**. You have just changed the data in the computer to generate a rifle shot. If you now type **L** the computer will list the data for you. You can silence a continuous sound by entering 0 into all register locations. Since doing this would wipe out your sound data, the function **S** for silence is included which will switch the sound off without altering your data. If you wish to start the sound again, type **A**.

When you have perfected your sound, use the **LIST** function and copy out the data. You can use your own sounds in your own programs using the fourth program ("G") on the software cassette.

**Mixing User And PROM Effects**

Having loaded program "G", type **GOTO 10 NEWLINE**. This runs a short program which simplifies the entering of your sound data. The computer asks **HOW MANY SOUNDS?** Type in the number of different sounds of your own that you wish to include in your program, followed by **NEWLINE**. The computer display will now look like this:-

**HOW MANY SOUNDS?**  
**SOUND No. 1**  
**REG.0 DATA?**

Type in the data for register 0 in your first sound followed by **NEWLINE**. The display will now read:-

**HOW MANY SOUNDS?**  
**SOUND No. 1**  
**REG.1 DATA?**

Type in the data for register 1, sound 1 as before. When you have entered data for all 14 registers, the display will read:-

**HOW MANY SOUNDS? SOUND No.2 REG.0 DATA?**


Continue entering data as before. When all the data for all your sounds has been entered the program will stop.

The user sound data is held in an array called **A**; in order not to lose this data do *not* use **CLEAR** or **RUN**. When you wish to run a program use the **GOTO** function. Do not use an array called **A** in your program and don't use variables **Y** and **Z**.

The fourth program consists of lines 1 to 9 and 10 through 21. **DO NOT ALTER LINES 1 through 9**, though if you wish, when you have entered your sound data, you can delete lines 10 through 21. When you wish to use your own sounds in your program simply insert the following two lines:-

**LET Z = x**  
 where x is the number of your sound,  
**GOSUB 2**

when your sound will be heard. You can of course mix your own sounds with the on-board sounds in your programs. Use the on-board sounds in the manner previously described — it is not necessary to load program "S" to do this if you have loaded program "G".

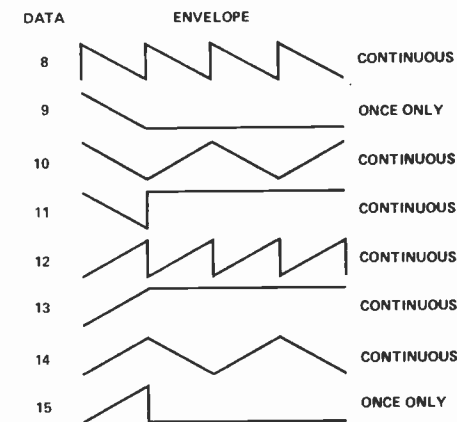

**Fig. 5** Envelope diagram for register 13.

# PROJECT: ZX81 Music Board

## HOW IT WORKS — USER EFFECTS

Line 2 dimensions a one dimensional array with 14 positions called A. This array is used to hold the data for the sound effects you are devising. Line 4 makes the computer jump to 200 where it is instructed to print the selection menu. Line 225 makes the computer jump to line 60. Lines 60 to 75 wait for an answer to this question and the computer jumps accordingly. If the function selected was R the computer jumps to line 5. Line 6 sets up a loop using variable D where D = 1 to 14. Line 10 prints the current register number which is held in D and asks what data you wish to go to that register. Lines 15 to 20 input and print the data. Line 25 causes the computer to loop back to line 6 until data for all 14 registers (0 to 13) has been entered. Line 35 again sets up a FOR NEXT loop using D where D equals from 1 to 14 (the PSG register numbers). Line 40 POKEs the register number to memory position 16515 and line 45 POKEs the data for that register to 16519. Line 46 calls a machine code subroutine based at 16514 which outputs to the PSG register (16515) data (16519). Line 50 causes a loop back to line 35 which continues until the data for all 14 registers (0 to 13) has been relayed to the PSG. Line 55 then causes a jump to 200 and a repeat of the initial question.

If the answer to the question at 200 is A, the computer again runs through lines 31 to 55 causing the PSG to repeat the sound. If the answer is C, the computer jumps to line 100. Lines 102 to 110 ask you the number of the register whose data you wish to alter. Line 110 inputs your answer in D and line 111 checks to see if your answer was 99, which would indicate that you had finished altering data for the time being and wished to hear the sound again — in which case the computer would jump to line 30. If your answer was not 99, the computer continues and lines 115 to 125 input and print your new data for the register you gave. Line 130 causes the computer to jump back to line 102 for you to change more data. If your answer

was L, you wished the computer to list register data and it would jump to line 150. At line 155 a loop is again set up using D. Line 160 prints the register number (D-1). Line 165 prints the data for that register. Line 170 causes the computer to loop back to line 160, which it continues to do until data for all 14 registers have been displayed. Line 180 makes the computer wait for you to type F, when it will jump to line 30 and your sound will again be heard. If your answer was S, ie the PSG was maintaining a continuous sound and you wished to silence it without losing your data, the computer would jump to 230. Lines 230 to 234 comprise yet another loop using D to output 0 to all PSG registers causing the PSG to become silent.

NOTE: (5 SPC) MEANS "5 SPACES"

```

1      REM (our machine code)
2      DIM A(14)
3      CLS
4      GOTO 200
5      CLS
6      FOR D = 1 TO 14
10     PRINT "REGISTER";
        D-1;"DATA?";
15     INPUT A(D)
20     PRINT A(D)
25     NEXT D
31     CLS
35     FOR D = 1 TO 14
40     POKE 16515,(D-1)
45     POKE 16519,A(D)
46     RAND USR 16514
50     NEXT D
55     GOTO 200
60     IF INKEY$ = "A" THEN
        GOTO 30
61     IF INKEY$ = "S" THEN
        GOTO 230
65     IF INKEY$ = "R" THEN
        GOTO 5
70     IF INKEY$ = "C" THEN
        GOTO 100
71     IF INKEY$ = "L" THEN
        GOTO 150
75     GOTO 60
100    CLS
101    PRINT "TYPE 99 AS A
    
```

```

REGISTER
NUMBER [5 SPC] WHEN
YOU WISH TO HEAR THE
SOUND."
102    PRINT "WHICH REGISTER?";
110    INPUT D
111    IF D = 99 THEN GOTO 30
112    LET D = D + 1
115    PRINT D - 1; " DATA? ";
120    INPUT A(D)
125    PRINT A(D)
130    GOTO 102
150    CLS
155    FOR D = 1 TO 14
160    PRINT "REGISTER";D - 1,
165    PRINT "DATA ";A(D)
170    NEXT D
175    SLOW
176    PRINT "PRESS ""F"" WHEN
        YOU HAVE FINISHED"
180    IF INKEY$ < >"F" THEN
        GOTO 180
190    GOTO 30
200    PRINT "YOU HAVE A
        CHOICE OF: "" A (TO HEAR
        THE SOUND AGAIN); "" R
        (TO ENTER ALL NEW
        DATA); "" C (TO CHANGE
        SPECIFIC DATA); "" L (TO
        LIST DATA); "" S (TO
        SILENCE THE P.S.G.)"
225    GOTO 60
230    FOR D = 1 TO 14
231    POKE 16515, (D-1)
232    POKE 16519,0
233    RAND USR 16514
234    NEXT D
235    CLS
236    GOTO 200
    
```

Machine code in line 1:

```

3E 07 D3 FF 3E 78 D3 F7
21 B4 40 E5 01 FB 0E C5
16 xx 3E 0E D3 FF 7A D3
F7 14 3E 0F D3 FF ED A2
20 F0 C1 E1 16 00 7A D3
FF 5E 7B D3 F7 23 14 10
F5 C9 xx xx xx xx xx
xx xx xx xx xx xx xx
3E xx D3 FF 3E xx D3 F7
C9
    
```

## HOW IT WORKS — USER/PROM SOUNDS PROGRAM

This program comprises a line of machine code, a subroutine at line 2 and a program to facilitate the entering of user sound data. This latter program is from line 10 to line 21. It sets up an array called A whose size depends on the number of different user sounds to be provided for. Lines 13 through 19 comprise a double loop which inputs the user's sound data into the appropriate position of array A.

The subroutine at line 2 is called when a sound, whose data is in array A, is to be heard. As has been explained, variable Z is set to the number of the user's sound. Line 2 sets up a loop using variable Y where Y = 1 to 14. Line 4 POKEs the register number (Y - 1) to memory position 16579 and line 5 POKEs the data for that PSG register which is already in array A(Z,Y) to memory position 16583. Line 6 calls a

machine code subroutine based at 16578. This subroutine outputs the number at memory location 16579 to the PSG to select a register and the number at memory location 16583 to the PSG as data for this register. Line 7 causes the computer to loop back to line 4 until data for all 14 PSG registers has been output. The user can insert instructions 3 FAST and 8 SLOW, but we recommend leaving these out since the operation of a program in FAST mode causes the computer to discontinue maintaining the video display. This would be annoying, especially in games programs.

```

1      REM our machine code
2      FOR Y = 1 to 14
3      POKE 16579, Y - 1
4      POKE 16583, A(Z,Y)
5      RAND USR 16578
6
    
```

```

7      NEXT Y
9      RETURN
10     PRINT "HOW MANY
        SOUNDS?"
11     INPUT S
12     DIM A (S,14)
13     FOR N = 1 TO S
14     FOR R = 1 TO 14
15     PRINT AT 1,0;"SOUND
        NO.":N
16     PRINT AT
        2,0;"REG.":"R-1;"" DATA? ""
17     INPUT A(N,R)
18     NEXT R
19     NEXT N
20     CLS
21     STOP
    
```

Machine code at line 1:

```

3E xx D3 FF 3E xx D3 F7
C9
    
```

# POWERFET AMPLIFIERS

## NEW DESIGNS

With the introduction of four new boards PANTECHNIC have pushed forward the performance and reliability of their powerfet amplifiers. Four key improvements have been incorporated in these second generation modules —

- 1.) The use of H-PAK powerfets, resulting in improved thermal efficiency and consequently enhanced power output capabilities.
- 2.) Low  $C_{OB}$  drivers now in power transistor packages, maintaining the superb HF performance and improving driver reliability.
- 3.) Separate driver and input supply rails allowing a 10% increase in available output power by increasing output stage efficiency.
- 4.) Bridge mode input pin allowing instant bridging between any two amplifiers without the need for extra circuitry.

## PFA100 Specification

Bandwidth 10Hz-100KHz  $\pm$  1dB  
 Output Power into 8 $\Omega$  100W ( $V_s = \pm$  55V)  
 THD (20Hz-20KHz) <0.008%  
 THD (1KHz at 100W) 0.004% typ.  
 SNR 120dB  
 Slew rate >30 V/ $\mu$ S  
 Gain x 23  
 Rin 30K  
 Vs max  $\pm$  70V




### Price

**£17.35 (Built & Tested)**  
**£15.17 (Kit)**

PFA100 120W into 8 $\Omega$  ( $V_s = \pm$  60V)
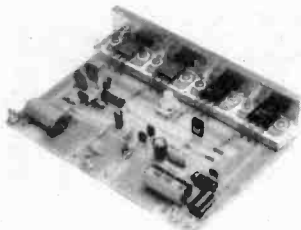
## PFA200 Specification

Bandwidth 10Hz-100KHz  $\pm$  1dB  
 Output power into 8 $\Omega$  150W ( $V_s = \pm$  60V)  
 THD (20Hz-20KHz) <0.005%  
 THD (1KHz at 150W) 0.002% typ  
 SNR 120dB  
 Slew rate >30 V/ $\mu$ S  
 Gain x 23  
 Rin 30K  
 Vs max  $\pm$  70V



### Price

**£23.87 (Built & Tested)**  
**£21.70 (Kit)**

PFA200 180W into 8 $\Omega$   
 300W into 4 $\Omega$  ( $V_s = \pm$  67V)

### And for those with a taste for power . . .

- **PFA500** Delivers 475W into 4 ohms and 600W into 2 ohms. These highly current capable units can deliver 25 amps continuous into a load, whilst maintaining the exemplary performance figures of the smaller units . . . . . **£42.00 (built & tested)**
- **PFA/HV** A very special module aimed at digital audio and wide dynamic range programme material. Delivers 300W into 4 ohms and 8 ohms on a continuous basis, it will peak for musically significant periods of time at up to 5dBs above this. The PFA/HV is the widest dynamic range power amplifier currently available . . . . . **£34.30 (built & tested)**
- **THE HEAT EXCHANGER.** Other people sell heatsinks. Pantechnic design, manufacture and sell heatexchangers. Re-examination of the heat transfer process has resulted in a radically new design possessing greatly improved efficiency. The unit 7" x 4" x 2" handles PFAs up to 300W or 1.2KW when blown . . . . . **£7.50**

## POWER SUPPLY COMPONENTS

### Toroidal Mains Transformers

Voltage	160VA	225 VA	300 VA	500 VA	625 VA
40-0-40	9.71	11.36	12.32	—	—
45-0-45	—	11.36	12.32	16.05	—
50-0-50	—	—	—	16.05	18.80

Special low flux windings. Carriage included

25A 400PIV Bridge rectifier	<b>£2.17</b>	For the PFA/HV 500VA	70-0-70
10,000 $\mu$ F 80V Electrolytics	<b>£4.13</b>		<b>£16.05</b>
30,000 $\mu$ F 75V Electrolytics	<b>£10.00</b>	10,000 $\mu$ F 100V Electrolytics	<b>£5.70</b>

Phone or write for advice on selecting the right components for your particular application.

All prices excl. VAT. Carriage 75p. Trade supplied

Ask about our preamps, protection boards and active crossovers

## THE POWERFET SPECIALISTS

# pantechnic

(incorporating J.W. Rimmer)

Dept ET1/5, 148 Quarry Street, Liverpool L25 6HQ

Telephone: 051 428 8485

Technical enquiries

Phil Rimmer 01-800 6667

HOBBY HERALD  
 HAS ALL THE  
 LATEST NEWS  
 FOR THE  
 ELECTRONICS  
 HOBBYIST


When you need to update yourself with all that is available in the "Do-it-yourself" market, then you need the Hobby Herald.

Packed with product information essential to the electronics enthusiast, this new electronics catalogue lists over 60 exciting products ranging from All Purpose Cutters to Verobloc, the solderless breadboard. All products are available throughout the U.K. from over 200 stockists.

# HOBBY HERALD

Alternatively ordering products through the Herald is simplicity itself, and you can pay by either cheque, Barclaycard or Access. So make sure you get your copy of Hobby Herald by ringing

**(04215) 62829.**

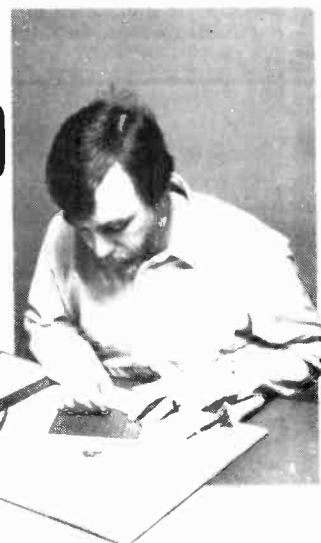

BICC-Vero Electronics Ltd.,  
 Industrial Estate,  
 Chandlers Ford, Hampshire,  
 SO5 3ZR.

**BICC**

**vero**

# Accurate Digital Multimeters at Exceptional Prices


NEW ANALOGUE METER WITH CONTINUITY BUZZER AND BATTERY SCALE

28 RANGES, EACH WITH FULL OVERLOAD PROTECTION

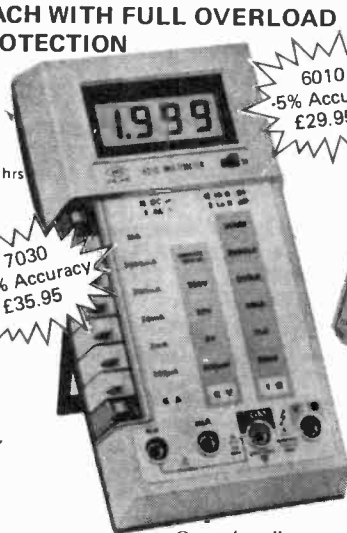**SPECIFICATION MODELS 6010 & 7030**

- 10 amp AC/DC
- Battery: Single 9V drycell. Life: 200 hrs
- Dimensions: 170 x 89 x 38mm.
- Weight: 400g inc. battery.
- Mode Select: Push Button.
- AC DC Current: 200µA to 10A
- AC Voltage: 200mV to 750V
- DC Voltage: 200mV to 1000V
- Resistance: 200Ω to 2MΩ
- Input Impedance: 10MΩ
- Display: 3 1/2 Digit 13mm LCD
- O/Load Protection: All ranges

**OTHER FEATURES:** Auto polarity, auto zero, battery low indicator, ABS plastic case with tilt stand, battery and test leads included, optional carrying case.



6010  
-5% Accuracy  
£29.95

7030  
-1% Accuracy  
£35.95



NEW  
HM102 BZ  
£13.00

**NEW HM 102 BZ SPECIFICATION**

- DC Voltage: 0-25, 1, 2.5, 10, 25, 100, 250, 1000 volts 20,000 ohms/volt.
- AC Voltage: 0-10, 25, 100, 250, 1000 volts 10,000 ohms/volt.
- Decibels: -20 to +22dB
- DC Current: 0-50, 500µA, 0-5, 50, 500mA
- Ohmmeter: 0-6 Megohms in 4 ranges. 30 ohms Centre Scale
- Power Supply: One 1.5V size 'A' battery (incl)
- Size & Weight: 135 x 91 x 39mm, 280gr.

**HM 101 POCKET SIZE MULTIMETER SPECIFICATION**


- DC & AC Voltage: 0-10, 50, 250, 1000 volts, 2000 ohms/volts
- Decibels: -10 to +22dB
- DC Current: 0-100mA
- Ohmmeter: 0-1 Megohm in 2 ranges, 60 ohms Centre Scale
- Power Supply: One 1.5V size 'A' battery (incl)
- Size & Weight: 90 x 60 x 29mm, 92gr. incl. battery
- Price: £5.50

Quantity discount for trade on application.

Add 15% to your order for VAT. P&P is free of charge. Payment by Cheque with Order.

**ARMON ELECTRONICS LTD.**

Access & Barclaycard accepted.

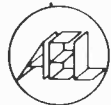


Cottrell House, 53-63 Wembley Hill Road, Wembley, Middlesex HA9 8BH, England

Telephone 01-902 4321 (3 lines)

TELEX No. 923985



# New Products

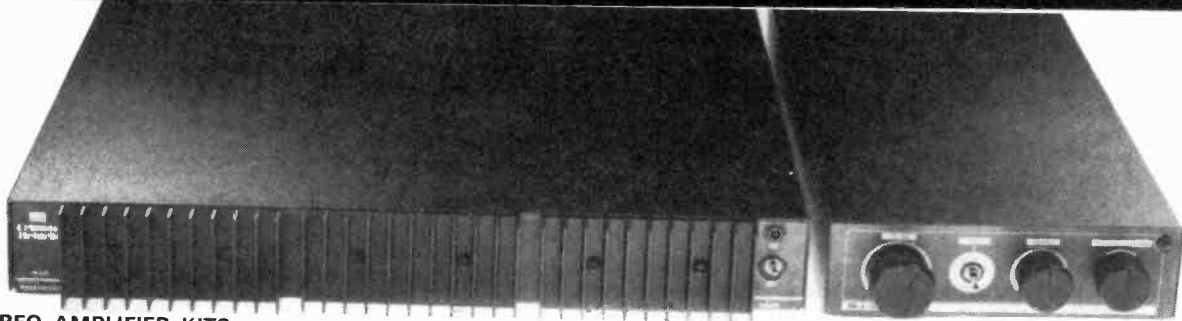

**HIFI STEREO AMPLIFIER KITS**

From one of Britain's leading esoteric amplifier manufacturers comes an exciting new package of stereo amplifier kits, designed to offer all the advantages of true high fidelity but without the usual price penalty.

These new kits offer the choice of moving magnet or moving coil inputs, 40 to 100 watts per channel, in fact, everything that made the previous models so popular is included but with added style, easier construction and a full two year warranty.

The new range consists of The CK 1010 Stereo Pre Amplifier, The CK 1040 WPC Power Amplifier, The CK 1100 WPC Power Amplifier.

**CK 1010**

This kit contains all the necessary parts to build a complete pre-amp. The main PCB is ready assembled and tested therefore construction is simply a matter of point to point wiring and mechanical assembly of the connections and controls to the pre punched chassis.

The CK 1010 takes its DC supply from the CK 1040, 1100 or, if using a different power amplifier a PSK power supply kit. Inputs for disc, tuner and tape are provided and an optional add-on moving coil input can be fitted to extend its versatility. (MC2K)

**CK 1040**

This is a nominal 40 watt per channel power amplifier kit which features our dual power supply and the DC output for the CK 1010. All components such as heatsinks, wire and connectors are included and protection is provided from short circuit outputs.

**CK 1100**

Similar to the CK 1040 this model provides a nominal 100 watts per channel with extra heatsinking and thermal cutouts are provided as standard. When correctly assembled these kits are guaranteed for two years.

"It would seem then that Crimson have maintained their position at the top of the commercial kit-build field. There is no oriental amplifier I know of that can better the sound of this combination overall at any price and only a few - such as the KA-1000 (£500+) - are of comparable standard. . . . I can say no more than that for £250 it (CK 1010/MC2K/1100) is a bargain and one that becomes the reference point for kit amplifiers from now on."

**PRICES** CK 1010 - RRP £92.00; CK 1040 - RRP £121.00; CK 1100 - RRP £151.00; MC2K - RRP £25.00; PSK - RRP £20.00

Barclaycard or Access accepted, otherwise send C.W.O. All prices include P&P to anywhere in the U.K. Export: Write for pro-forma

**SEND FOR FULL DETAILS ON OUR HIFI KIT PRODUCTS BY WRITING TO ADDRESS BELOW**



**Crimson Elektrik Stoke**

LONDON DISTRIBUTOR: BRADLEY MARSHALL LTD, 325 EDGWARE ROAD, LONDON W2 1BN

**PHOENIX WORK  
500 KINGS STREET  
STOKE-ON-TRENT  
TEL: 0782 330520**



electronize

# AUTO-ELECTRONIC PRODUCTS

## KITS OR READY BUILT

### ELECTRONIC IGNITION



### IS YOUR CAR AS GOOD AS IT COULD BE ?

- ★ Is it **EASY TO START** in the cold and the damp? Total Energy Discharge will give the most powerful spark and maintain full output even with a near flat battery.
- ★ Is it **ECONOMICAL** or does it "go off" between services as the ignition performance deteriorates? Total Energy Discharge gives much more output and maintains it from service to service.
- ★ Has it **PEAK PERFORMANCE** or is it flat at high and low revs. where the ignition output is marginal? Total Energy Discharge gives a more powerful spark from idle to the engines max. (even with 8 cylinders).
- ★ Do the **PLUGS and POINTS** always need changing to bring the engine back to its best. Total Energy Discharge eliminates contact arcing and erosion by removing the heavy electrical load. The timing stays "spot on" and the contact condition doesn't affect the performance either. Larger plug gaps can be used, even wet or badly fouled plugs can be fired with this system.

★ Is the **PERFORMANCE SMOOTH**. The more powerful spark of Total Energy Discharge eliminates the 'near misfires' whilst an electronic filter smooths out the effects of contact bounce etc.

Most **NEW CARS** already have **ELECTRONIC IGNITION**. Update **YOUR CAR** with the most powerful system on the market - 3 1/2 times more spark power than inductive systems - 3 1/2 times the spark energy of ordinary capacitive systems, 3 times the spark duration.

Total Energy Discharge also features: **EASY FITTING, STANDARD/ELECTRONIC CHANGEOVER SWITCH, LED STATIC TIMING LIGHT, LOW RADIO INTERFERENCE, CORRECT SPARK POLARITY and DESIGNED IN RELIABILITY.**

★ **IN KIT FORM** it provides a top performance system at less than half the price of competing ready built units. The kit includes: pre-drilled fibreglass PCB, pre-wound and varnished ferrite transformer, high quality 2µF discharge capacitor, case, easy to follow instructions, solder and everything needed to build and fit to your car. All you need is a soldering iron and a few basic tools.

**FITS ALL NEGATIVE EARTH VEHICLES**  
6 or 12 volt, with or without ballast.

**OPERATES ALL VOLTAGE IMPULSE TACHOMETERS:**  
(Older current impulse types need an adaptor).


**STANDARD CAR KIT £15-90**  
**Assembled and Tested £26-70**

PLUS  
P. & P.  
£1 (U.K.)

**TWIN OUTPUT KIT £24-55**  
For Motor Cycles and Cars with twin ignition systems  
**Assembled and Tested £36-45**

Prices  
include  
VAT
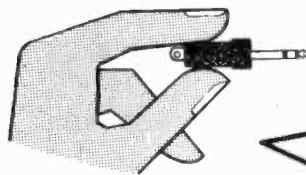
### PROTECT YOUR CAR WITH AN ELECTRONIZE ELECTRONIC ALARM



Don't Wait Until  
Its too Late ~  
Fit one NOW!

- ★ **2000 COMBINATIONS** provided by an electronic key - a miniature jack plug containing components which must match each individual alarm system. (Not limited to a few hundred keys or a four bit code).
- ★ **60 SECOND ALARM PERIOD** flashes headlights and sounds horn, then resets ready to operate again if needed.
- ★ **10 SECOND ENTRY DELAY** allows owner to dis-arm the system, by inserting the key plug into a dashboard mounted socket, before the alarm sounds. (No holes in external bodywork, fiddly code systems or hidden switches). Re-closing the door will not cancel the alarm, before or after it sounds, the key plug must be used.
- ★ **INSTANT ALARM OPERATION** triggered by accessories or bonnet/boot opening.
- ★ **30 SECOND DELAY** when system is armed allows owner to lock doors etc.

★ **DISABLES IGNITION SYSTEM** when alarm is armed.

★ **IN KIT FORM** it provides a high level of protection at a really low cost. The kit includes everything needed, the case, fibreglass PCB, CMOS IC's, random selection resistors to set the combination, in fact everything down to the last nut and washer plus easy to follow instructions.

**FITS ALL 12 VOLT NEGATIVE EARTH VEHICLES.**  
**SUPPLIED COMPLETE WITH ALL NECESSARY LEADS AND CONNECTORS PLUS TWO KEY PLUGS**

**CAR ALARM KIT £24-95**

**ASSEMBLED AND TESTED £37-95**

PLUS  
P. & P.  
£1 (U.K.)  
Prices  
include  
VAT



Access and Visa  
Welcome. Write or  
Phone Quoting Number

### ELECTRONIZE DESIGN

Dept. D · Magnus Rd · Wilnecote  
Tamworth · B77 5BY  
tel: 0827 281000

# CONFIGURATIONS

And so to solid state switches. In this month's Configurations Ian Sinclair looks at the basic techniques involving the thyristor and its close relatives.

As a component, the thyristor is so closely related to the diode that thyristor circuits just had to follow the treatment of power supplies last month. Technically, the thyristor is a four-layer diode, but as far as we are concerned, it's a silicon diode that is switched into conduction by a signal at a third electrode, the **gate**, as shown in Fig. 1. In many respects, however, the action is very much that of a normal silicon diode; for example, it will not conduct in the reverse direction (cathode positive), and it has about 0V6 forward drop across the anode-cathode terminal when it conducts. The distinguishing feature is that the start of forward conduction only occurs when a **trigger** pulse arrives at the gate and **fires** the thyristor. Whatever you subsequently do to the gate, the thyristor will continue to conduct until the forward current falls below a value known as the **holding current**, at which point the thyristor will turn off. However, while the thyristor is on, it is as fully conducting as a silicon diode would be.

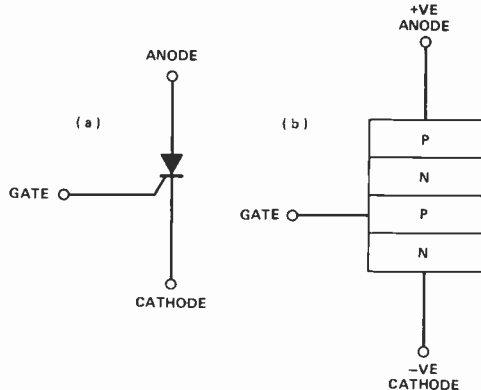


Fig. 1 The thyristor: (a) circuit symbol, (b) arrangement of semiconductor layers.

## Triggers Fingered

One point that is not always sufficiently understood is that the triggering requirements can vary enormously from one type of thyristor to another. A lot of small thyristors will trigger for a gate current of only a fraction of a microamp, so that interference signals will trigger the thyristor if the gate terminal is not 'earthed' to the cathode by a low-value resistor. A lot of false triggering of burglar alarms seems to be due to thyristor circuits in which the gate has too high a resistance to the cathode, making the gate circuit a very efficient aerial for any radiated energy! Even when quite low resistance values are used, thyristors can trigger in lightning storms or because of static discharges, so that some careful design of the gate circuit and extensive testing is needed if you are in the alarm business. The combination of low resistance and a suppressor ferrite bead placed at the gate terminal helps a lot! Large thyristors need rather more in the way of gate current, but even these can be triggered by a fraction of a milliamp.

Thyristors are most at home in circuits which use DC or unsmoothed (but rectified) AC. The use of rectified AC is particularly popular (Fig. 2) because the thyristor will

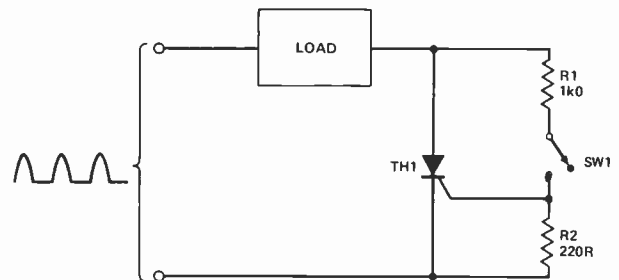


Fig. 2 Elementary switching circuit for use with rectified AC. When the switch is on, current will flow through the load.

switch off each time the supply voltage reaches zero, and all that we need to concentrate our attention on is the triggering which switches it on again. Where a thyristor is used in a DC circuit, there is the extra complication of reducing the voltage across the thyristor to zero in order to switch it off (Fig. 3).

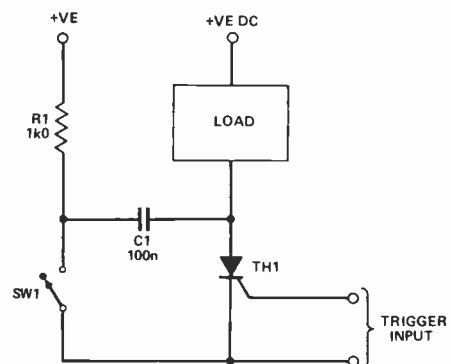


Fig. 3 Turning off a thyristor which is operated from DC. Pressing the switch will discharge the capacitor, pulsing the anode of the thyristor and so stopping the current. This is enough to prevent conduction until the gate is pulsed again.

## A Passing Phase

Down to configurations. The most useful basic triggering circuit is the phase-controlled thyristor fed with rectified AC as illustrated in Fig. 4. The load can be placed in the leads to the bridge rectifier, in which case the thyristor will control the average power dissipated in the load,


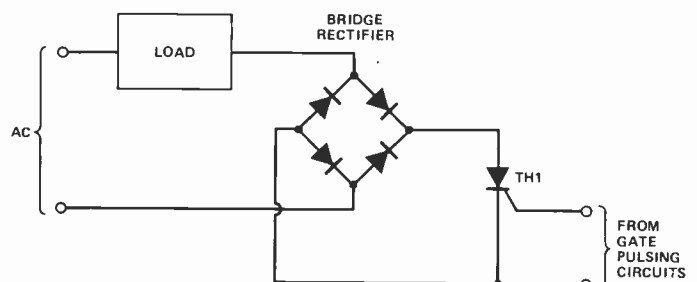
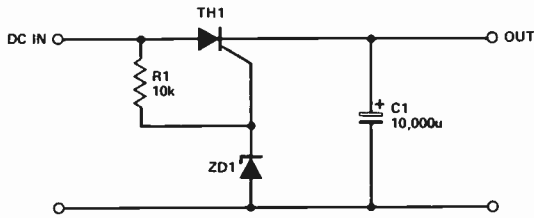


Fig. 4 Basic circuit for thyristor control of an AC circuit, using a bridge rectifier to supply the thyristor. The load, however, operates from AC.

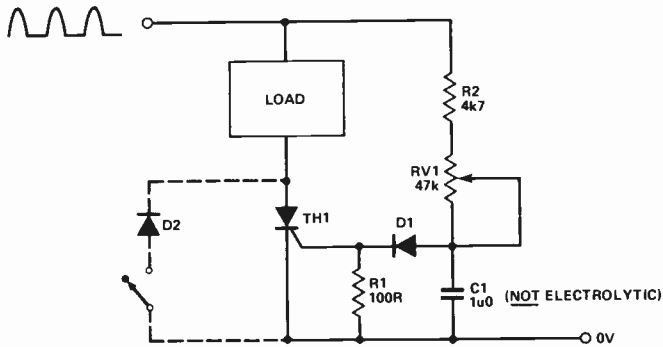

**Fig. 5** A thyristor regulator. This makes a very useful pre-stabiliser circuit, or can be used as a stabiliser in its own right where very precise stabilisation is not needed.

despite the fact that the load is working on AC and the thyristor is controlling a rectified supply. An interesting option is to place a reservoir capacitor on the cathode side of the thyristor, giving a low-cost and low-dissipation form of voltage regulation (Fig. 5). The gate control can be obtained from a charging capacitor, as demonstrated in Fig. 6, or from a zener diode as in Fig. 5 — remember that there is no triggering until the gate voltage is about 0V6 above the cathode voltage.

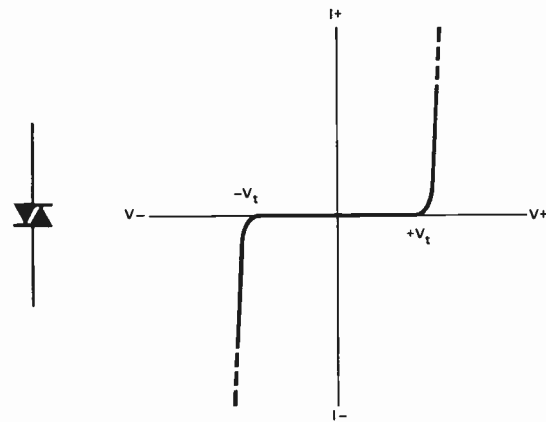


**Fig. 6** A typical phase control circuit for AC. The thyristor will conduct on only half of the input wave, so that a 'power-doubler' circuit, which switches a diode across the thyristor in the reverse conduction direction may be needed for a larger range of power control (shown dotted).

Simple triggering from a charging capacitor is never entirely satisfactory, because the thyristor cannot be relied upon to fire at exactly the same stage of charging in each cycle. To get round this, the simpler circuits make use of a trigger diode or diac which ensures more reliable triggering. The trigger diode has the curious characteristic that it will remain non-conducting while the voltage across it in either direction builds up, suddenly conduct at some voltage level which is determined by its construction, and remain fully conducting until the voltage across it has dropped almost to zero (Fig. 7). A diac wired between a charging capacitor and the gate of the thyristor, with a load of a few hundred ohms connected between the gate and the cathode to avoid unwanted triggering will serve nicely to make the triggering much more reliable. What you then have to be sure of is that you have enough voltage around to operate the diac — depending on type, you may need up to 15 V across it before it starts to conduct.

The very simple phase-control system operates well enough for a lot of applications, particularly for light dimming, but more care is needed where electric motors are being controlled, mainly because of the back-EMF that motors of the AC/DC type will generate. When any motor of this type is spinning, it will act as a generator of DC (even if the supply to the motor is AC), and the thyristor must be capable of withstanding a reverse voltage which consists of the peak reverse AC plus this additional voltage generated by the motor.


The methods that are used for thyristor control of the



**Fig. 7.** The diac, and its typical characteristic.

larger motors, larger than your domestic power drill/food mixer motor, are a lot more specialised. For these circuits, charging capacitors are simply not precise enough as a method of triggering the thyristor at the correct point in the waveform: more elaborate trigger circuits, synchronised to the mains frequency, have to be used. These pulse-generating circuits can be coupled to the thyristor circuitry by using small pulse transformers, so that the timing circuits need not be connected to the circuits that the thyristor controls. This is particularly important when thyristors are used in high-voltage three-phase circuits, because the thyristors may be operating at voltages well above or below earth, yet the control box needs to be earthed.

Radio interference is a continual problem for any thyristor circuit which makes use of phase control. Because the thyristor is being switched on when there is a substantial voltage across it, there are large current pulses which can be devastating for radio or TV receivers in the neighbourhood and which can also trigger other thyristors. It's essential, therefore, to design really effective pulse-transient suppression into the gate and anode circuits, and to ensure in the practical construction that the suppressors are placed as close as possible to the terminals of each thyristor. In general, small series inductors and

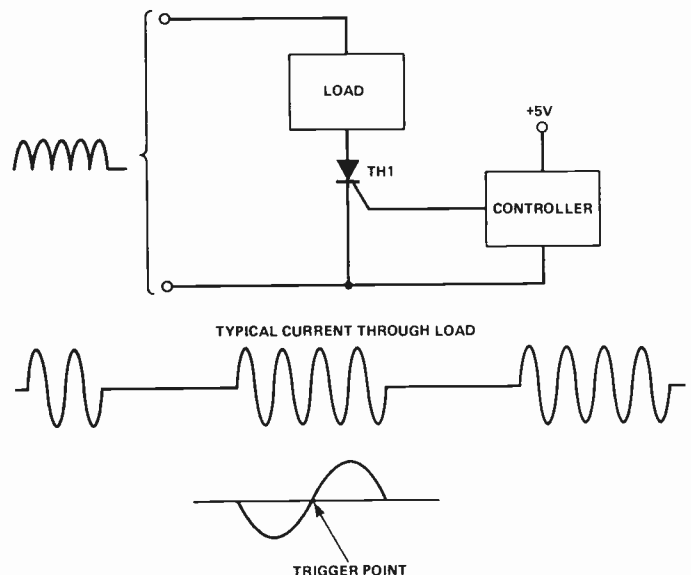

**Fig. 8** Principles of zero-voltage switching circuits. The controller (usually an IC) will switch the thyristor on at the point when the AC wave passes through zero. This ensures minimal RF interference, unlike the phase-control method.

parallel capacitors will do all that is needed, but they have to be capable of taking high peak currents, and must be wired close enough to prevent any wiring from acting as a radiating aerial.

## The Zero Option

The other way of controlling thyristors in energy-control circuits is seen much less in the small-scale circuits that we tend to be more familiar with. This alternative is zero-voltage switching, and it involves switching the thyristors on at the instant when the voltage between anode and cathode is zero. This has the advantage of generating no more interference than a silicon diode would, which is very much less than is generated by the phase-control circuit: but it can be used only with loads like water-heaters which have very long time constants. If you switch your electric drill motor on for 100 ms in each second, the speed will be rather erratic to say the least, but a water or room heater switched in this way does not cause noticeable fluctuations of temperature because the temperature does not shoot up rapidly when the heater is on, nor shoot down when the heater is off. Figure 8 shows an outline of a typical zero-voltage control circuit — there is an IC which can be used to govern the whole operation.

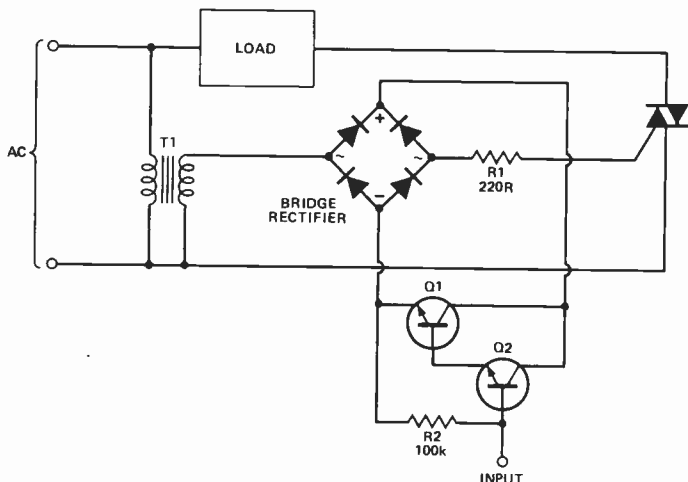


Fig. 9 Using a triac in a circuit where the switching signals are very small. Note that the whole circuit is live to mains.

## For My Next Triac . . .

The triac is a two-way equivalent of the thyristor, with the main circuit terminals labelled MT1 and MT2 rather than anode and cathode, since current can flow in either direction through the triac. Like the thyristor, the triac remains non-conducting until it has been triggered by a pulse at its gate terminal; the pulse can be of either polarity, but the minimum amplitude for firing is not the same for the two possible polarities. Again like the thyristor, the triac ceases to conduct when the current through it becomes too low to sustain conduction. Triacs are extensively used to switch raw AC because a triac circuit

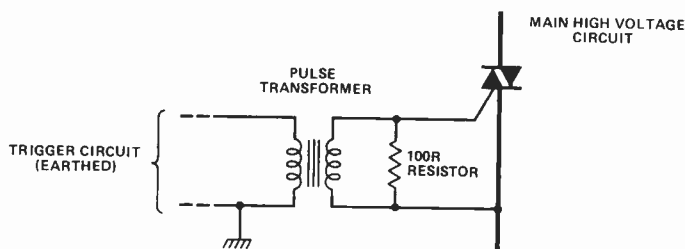


Fig. 10 Isolating the mains part of the circuit from the control part by using a pulse transformer.

represents a considerable saving on components as compared to a small thyristor circuit, even if the equivalent triac is more expensive than two thyristors. Figure 9 shows a typical triac circuit for AC use that can operate using a very small triggering input, such as from a microphone or photocell. The transformer supplies a low voltage for the gate circuit, and the rectifier bridge is arranged so that an unsmoothed full-wave rectified voltage is fed to the transistor amplifier circuit. When the transistor conducts, the current flowing in the bridge rectifier will also flow through the gate of the triac, triggering the triac on each half-cycle. The trigger current is AC because the gate is wired in the AC side of the transformer. Note that the whole circuit is connected to mains — if an isolated low-voltage circuit is needed, then the gate must be triggered by a circuit using a pulse transformer rather than directly as in this example, and the part-circuit shown in Fig. 10 is needed.

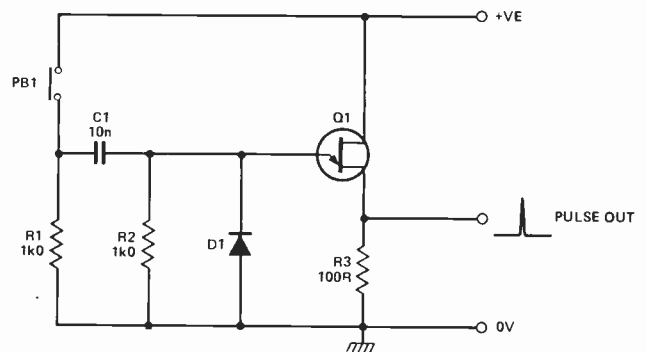


Fig. 11 The unijunction connected to provide a short pulse when a switch is pressed.

Triggering thyristors or triacs via a pulse transformer needs a fairly sharp spike waveform, and one of the devices that has traditionally been used to provide this type of waveform is the unijunction. As the name suggests, this uses one junction on an N-type silicon base whose doping normally ensures that the conductivity is low (resistance high). The junction is placed so as to provide an emitter terminal, and when the emitter voltage is raised to the conducting level, the injection of holes into the bar will make it highly conductive. This is the triggered state, which can be maintained only if a current continues to flow through the emitter. Unijunction circuits are arranged so as to prevent this continuous current, so ensuring a clean sharp pulse.

A unijunction 'one-shot' pulse generator is illustrated in Fig. 11. With the switch open, the emitter of the unijunction is earthed, and the device is non-conducting. Closing the switch contacts changes the voltage on one side of the capacitor from earth to the positive supply voltage, and the voltage on the other side will increase similarly, so triggering the unijunction. The conducting unijunction generates a positive-going spike at the earthy end of its circuit, and also charges the capacitor so that the end of the capacitor connected to the emitter is at about earth voltage. This process is very brief, and when the switch opens again, the emitter of the unijunction is protected from negative pulses by a diode.

The triggering voltage for a unijunction is a fixed fraction of the total voltage applied across the main terminals — the fraction is known as the 'intrinsic stand-off ratio', and is usually around 0.6, implying that the device will trigger when the emitter voltage is about 60 per cent of the supply voltage. Because this ratio is fixed, changes in the supply voltage do not make much difference to the frequency of the output.



# TOROIDALS


The toroidal transformer is now accepted as the standard in industry, overtaking the obsolete laminated type. Industry has been quick to recognise the advantages toroidals offer in size, weight, lower radiated field and, thanks to I.L.P., PRICE.

Our large standard range is complemented by our SPECIAL DESIGN section which can offer a prototype service within 7 DAYS together with a short lead time on quantity orders which can be programmed to your requirements with no price penalty.

\*Gold service available.  
21 days manufacture for urgent deliveries.

\*Orders despatched within 7 days of receipt for single or small quantity orders.

\*5 year no quibble guarantee.

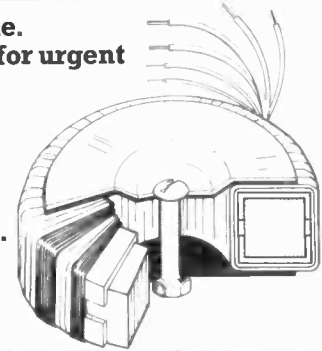

TYPE	SERIES No	SECONDARY Volts	RMS Current	PRICE	TYPE	SERIES No	SECONDARY Volts	RMS Current	PRICE	TYPE	SERIES No	SECONDARY Volts	RMS Current	PRICE																														
<p><b>NEW!</b> <b>NEW!</b> <b>NEW!</b></p> <p><b>15 VA</b> 0x010 6+6 1.25                  62 x 34mm 0x011 9+9 0.83                  0.35Kg 0x012 12+12 0.63                  Regulation 0x013 15+15 0.50                  19% 0x014 18+18 0.42                  0x015 22+22 0.34                  0x016 25+25 0.30                  0x017 30+30 0.25</p> <p><b>£5.12</b>                  + p &amp; p £0.78                  + VAT £0.89                  TOTAL £6.79</p> <p>(encased in ABS plastic)</p>					<p><b>120 VA</b> 4x010 6+6 10.00                  90 x 40mm 4x011 9+9 6.66                  1.2Kg 4x012 12+12 5.00                  Regulation 4x013 15+15 4.00                  11% 4x014 18+18 3.33                  4x015 22+22 2.72                  4x016 25+25 2.40                  4x017 30+30 2.00                  4x018 35+35 1.71                  4x028 110 1.09                  4x029 220 0.54                  4x030 240 0.50</p> <p><b>£7.42</b>                  + p &amp; p £1.72                  + VAT £1.37                  TOTAL £10.51</p>					<p><b>300 VA</b> 7x013 15+15 10.00                  110 x 50mm 7x014 18+18 8.33                  2.6Kg 7x015 22+22 6.82                  Regulation 7x016 25+25 6.00                  6% 7x017 30+30 5.00                  7x018 35+35 4.28                  7x026 40+40 3.75                  7x025 45+45 3.33                  7x033 50+50 3.00                  7x028 110 2.72                  7x029 220 1.36                  7x030 240 1.25</p> <p><b>£10.88</b>                  + p &amp; p £2.05                  + VAT £1.94                  TOTAL £14.87</p>					<p><b>30 VA</b> 1x010 6+6 2.50                  70 x 30mm 1x011 9+9 1.66                  0.45Kg 1x012 12+12 1.25                  Regulation 1x013 15+15 1.00                  18% 1x014 18+18 0.83                  1x015 22+22 0.68                  1x016 25+25 0.60                  1x017 30+30 0.50</p> <p><b>£5.49</b>                  + p &amp; p £1.10                  + VAT £0.99                  TOTAL £7.58</p>					<p><b>160 VA</b> 5x011 9+9 8.89                  110 x 40mm 5x012 12+12 6.66                  1.8Kg 5x013 15+15 5.33                  Regulation 5x014 18+18 4.44                  8% 5x015 22+22 3.63                  5x016 25+25 3.20                  5x017 30+30 2.66                  5x018 35+35 2.28                  5x026 40+40 2.00                  5x028 110 1.45                  5x029 220 0.72                  5x030 240 0.66</p> <p><b>£8.43</b>                  + p &amp; p £1.72                  + VAT £1.52                  TOTAL £11.67</p>					<p><b>500 VA</b> 8x016 25+25 10.00                  140 x 60mm 8x017 30+30 8.33                  4Kg 8x018 35+35 7.14                  Regulation 8x026 40+40 6.25                  4% 8x025 45+45 5.55                  8x033 50+50 5.00                  8x042 55+55 4.54                  8x028 110 4.54                  8x029 220 2.27                  8x030 240 2.08</p> <p><b>£14.38</b>                  + p &amp; p £2.40                  + VAT £2.52                  TOTAL £19.30</p>					<p><b>50 VA</b> 2x010 6+6 4.16                  80 x 35mm 2x011 9+9 2.77                  0.9Kg 2x012 12+12 2.08                  Regulation 2x013 15+15 1.66                  13% 2x014 18+18 1.38                  2x015 22+22 1.13                  2x016 25+25 1.00                  2x017 30+30 0.83                  2x028 110 0.45                  2x029 220 0.22                  2x030 240 0.20</p> <p><b>£6.13</b>                  + p &amp; p £1.35                  + VAT £1.12                  TOTAL £8.60</p>					<p><b>225 VA</b> 6x012 12+12 9.38                  110 x 45mm 6x013 15+15 7.50                  2.2Kg 6x014 18+18 6.25                  Regulation 6x015 22+22 5.11                  7% 6x016 25+25 4.50                  6x017 30+30 3.75                  6x018 35+35 3.21                  6x026 40+40 2.81                  6x025 45+45 2.50                  6x033 50+50 2.25                  6x028 110 2.04                  6x029 220 1.02                  6x030 240 0.93</p> <p><b>£9.81</b>                  + p &amp; p £2.05                  + VAT £1.78                  TOTAL £13.64</p>					<p><b>625 VA</b> 9x017 30+30 10.41                  140 x 75mm 9x018 35+35 8.92                  5Kg 9x026 40+40 7.81                  Regulation 9x025 45+45 6.94                  4% 9x033 50+50 6.25                  9x042 55+55 5.68                  9x028 110 5.68                  9x029 220 2.84                  9x030 240 2.60</p> <p><b>£17.12</b>                  + p &amp; p £2.55                  + VAT £2.95                  TOTAL £22.62</p>				
<p><b>30 VA</b> 1x010 6+6 2.50                  70 x 30mm 1x011 9+9 1.66                  0.45Kg 1x012 12+12 1.25                  Regulation 1x013 15+15 1.00                  18% 1x014 18+18 0.83                  1x015 22+22 0.68                  1x016 25+25 0.60                  1x017 30+30 0.50</p> <p><b>£5.49</b>                  + p &amp; p £1.10                  + VAT £0.99                  TOTAL £7.58</p>					<p><b>160 VA</b> 5x011 9+9 8.89                  110 x 40mm 5x012 12+12 6.66                  1.8Kg 5x013 15+15 5.33                  Regulation 5x014 18+18 4.44                  8% 5x015 22+22 3.63                  5x016 25+25 3.20                  5x017 30+30 2.66                  5x018 35+35 2.28                  5x026 40+40 2.00                  5x028 110 1.45                  5x029 220 0.72                  5x030 240 0.66</p> <p><b>£8.43</b>                  + p &amp; p £1.72                  + VAT £1.52                  TOTAL £11.67</p>					<p><b>500 VA</b> 8x016 25+25 10.00                  140 x 60mm 8x017 30+30 8.33                  4Kg 8x018 35+35 7.14                  Regulation 8x026 40+40 6.25                  4% 8x025 45+45 5.55                  8x033 50+50 5.00                  8x042 55+55 4.54                  8x028 110 4.54                  8x029 220 2.27                  8x030 240 2.08</p> <p><b>£14.38</b>                  + p &amp; p £2.40                  + VAT £2.52                  TOTAL £19.30</p>					<p><b>50 VA</b> 2x010 6+6 4.16                  80 x 35mm 2x011 9+9 2.77                  0.9Kg 2x012 12+12 2.08                  Regulation 2x013 15+15 1.66                  13% 2x014 18+18 1.38                  2x015 22+22 1.13                  2x016 25+25 1.00                  2x017 30+30 0.83                  2x028 110 0.45                  2x029 220 0.22                  2x030 240 0.20</p> <p><b>£6.13</b>                  + p &amp; p £1.35                  + VAT £1.12                  TOTAL £8.60</p>					<p><b>225 VA</b> 6x012 12+12 9.38                  110 x 45mm 6x013 15+15 7.50                  2.2Kg 6x014 18+18 6.25                  Regulation 6x015 22+22 5.11                  7% 6x016 25+25 4.50                  6x017 30+30 3.75                  6x018 35+35 3.21                  6x026 40+40 2.81                  6x025 45+45 2.50                  6x033 50+50 2.25                  6x028 110 2.04                  6x029 220 1.02                  6x030 240 0.93</p> <p><b>£9.81</b>                  + p &amp; p £2.05                  + VAT £1.78                  TOTAL £13.64</p>					<p><b>625 VA</b> 9x017 30+30 10.41                  140 x 75mm 9x018 35+35 8.92                  5Kg 9x026 40+40 7.81                  Regulation 9x025 45+45 6.94                  4% 9x033 50+50 6.25                  9x042 55+55 5.68                  9x028 110 5.68                  9x029 220 2.84                  9x030 240 2.60</p> <p><b>£17.12</b>                  + p &amp; p £2.55                  + VAT £2.95                  TOTAL £22.62</p>																			
<p><b>50 VA</b> 2x010 6+6 4.16                  80 x 35mm 2x011 9+9 2.77                  0.9Kg 2x012 12+12 2.08                  Regulation 2x013 15+15 1.66                  13% 2x014 18+18 1.38                  2x015 22+22 1.13                  2x016 25+25 1.00                  2x017 30+30 0.83                  2x028 110 0.45                  2x029 220 0.22                  2x030 240 0.20</p> <p><b>£6.13</b>                  + p &amp; p £1.35                  + VAT £1.12                  TOTAL £8.60</p>					<p><b>225 VA</b> 6x012 12+12 9.38                  110 x 45mm 6x013 15+15 7.50                  2.2Kg 6x014 18+18 6.25                  Regulation 6x015 22+22 5.11                  7% 6x016 25+25 4.50                  6x017 30+30 3.75                  6x018 35+35 3.21                  6x026 40+40 2.81                  6x025 45+45 2.50                  6x033 50+50 2.25                  6x028 110 2.04                  6x029 220 1.02                  6x030 240 0.93</p> <p><b>£9.81</b>                  + p &amp; p £2.05                  + VAT £1.78                  TOTAL £13.64</p>					<p><b>625 VA</b> 9x017 30+30 10.41                  140 x 75mm 9x018 35+35 8.92                  5Kg 9x026 40+40 7.81                  Regulation 9x025 45+45 6.94                  4% 9x033 50+50 6.25                  9x042 55+55 5.68                  9x028 110 5.68                  9x029 220 2.84                  9x030 240 2.60</p> <p><b>£17.12</b>                  + p &amp; p £2.55                  + VAT £2.95                  TOTAL £22.62</p>																																		

ALSO AVAILABLE  
 Sizes up to and including 5KVA are manufactured to order.

### The benefits of ILP toroidal transformers

ILP toroidal transformers are only half the weight and height of their laminated equivalents, and are available with 110V, 220V or 240V primaries coded as follows:

IMPORTANT: Regulation — All voltages quoted are FULL LOAD. Please add regulation figure to secondary voltage to obtain off load voltage.

For 110V primary insert "0" in place of "X" in type number.

For 220V primary (Europe) insert "1" in place of "X" in type number.

For 240V primary (UK) insert "2" in place of "X" in type number.

Also available at Electrovalue, Maplin, Technomatic and Barrie Electronics.

For mail order please make your crossed cheques or postal orders payable to ILP Electronics Ltd. Barclaycard/Access welcome. Trade orders standard terms.

Post to: ILP Electronics Ltd, Graham Bell House Roper Close  
 Canterbury C12 7EP, Kent, England  
 Telephone (0227) 54778 Telex 965780



**ILP**  
 TRANSFORMERS  
 (a division of  
 ILP Electronics Ltd)

## LOW COST PROFESSIONAL TEST INSTRUMENTS

**sabtronics**  
 FREQUENCY METERS  
 100MHz, 600MHz, and 1GHz Models  
 from £67

**Belemic**  
 Hand Held  
 Analogue and  
 Digital  
 Multimeters  
 16 Models  
 from £18.75

electro

- ★ FREQUENCY METERS
- ★ ANALOGUE MULTIMETERS
- ★ DIGITAL MULTIMETERS
- ★ FUNCTION GENERATOR
- ★ OSCILLOSCOPES
- ★ POWER SUPPLIES
- ★ LOGIC PROBE
- ★ SCOPE PROBES

Write or phone for illustrated test instrument catalogue and price list

**Black Star Ltd.**  
 9A, Crown Street  
 St. Ives, Huntingdon  
 Cambs. PE17 4EB  
 Tel: (0480) 62440 Telex 32339

# ORGAN PART 4

We conclude this excellent musical project with the constructional and setting up details, as well as the pricing for all the various bits and pieces. Design by Richard Watts.

**B**efore starting on the construction details for the organ, there is one section of circuitry remaining that needs to be explained — that of the swell pedal and glide control. Figure 2 in the February article contains the circuitry in question. The swell pedal performs the function of volume control for the whole organ and acts upon the signal which is output from the main mixer to the power amplifier. It operates by using an LDR (light dependent resistor), which is connected between ground and the signal line and which has a 12 V MES bulb mounted facing it. As the swell pedal is moved up and down, an optical filter is moved in the light path, allowing more or less light to reach the LDR and thus altering its resistance. This method of control is far superior to using potentiometers, which go noisy with age and wear and can produce fearful noises when connected to an amplifier input. The light operation ensures noise-free performance.

Attached to the side of the swell pedal is the glide switch. When operated, this switch causes the organ tuning to go flat by a semitone; when released, it allows it to slowly return to its original state. This effect is useful on all the voices and brings particular realism to those such as Hawaiian guitar and trombone.

When operated, the glide switch grounds the junction of D13 and D14: this discharges C18 through R34 (100R) and results in an immediate reduction in clock frequency, therefore flattening any audio currently being output. When released, the D13/D14 junction is again left open circuit, and C18 is allowed to return to its former state. The rate at which it returns is determined by the value of C18 and the amount by which the tuning is varied is determined by R33. The connection of D13 to the glide switch also causes the vibrato, if

selected, to be disabled by switching off IC8a for the duration of the glide switch operation. This adds to the effect of the glide.

## Construction

The main PCB is screen-printed with the component overlay and should present no constructional problems. A block diagram of the organ showing how all the remaining sections are interconnected to the main board is given in Fig. 1 as a guide to assembly.

The keyboard assembly comes as a complete unit, requiring only the contact assembly to be fitted. The keyboard chassis is fitted with end supports upon which both keyboards may be hinged up to facilitate access to the underside, where the contact assembly (the keyboard PCB) is fitted.

The keyboard is assembled as follows. First install and solder all the 1N4148 diodes with the cathodes (ringed) facing away from the bus bars. Next, with the board trackside up, install and solder all the track pins; one per diode and one per bus bar section. Ensure that the pins are pushed far enough into the PCB — the widest part of the

pin should be in contact with the track. Now, with the board 'diode side up', put a small solder blob on each of the pins just installed — this will help later. Next the Molex connector, through which all connections are made to the contacts and bus bars, is to be fitted and soldered. Install the connector from the component side, leaving the longest part of the pins uppermost, and solder the underside.

Now the bus bars can be fitted in turn as follows. Put two bus bar supports onto each bus bar section as shown in the diagrams and photograph. Use the upper of the two holes in the support. Align the bus bar supports with their locating holes in the PCB and mount the supports. A touch with a hot soldering iron to the protrusion below the board will secure the support; a spot of glue on the top side of the board is an alternative measure but take care not to get glue on the bus bars. Also keep your handling of the bus bars and contacts to a minimum as these are silver compounds and can get tarnished. Now slide the bus bar so that its left-hand end meets its associated pin and solder the bar to the pin. Take care not to use an excess of solder here since solder or flux running along to the contact area of the bus bar will impair the contact surface.

Insert the other 12-key bus bar sections and the 7-key section in the same way as described above. The top C key bus bar, since it handles one key only, has no bus bar support and is soldered directly to its pin at 90°. Check that no section of bus bar is touching any other section and check all joints on the underside of the board, as it is now to be mounted onto the keyboard chassis for insertion of the key contacts.

Insert the keyboard PCB spacers in the underside of the PCB as



The finished organ.

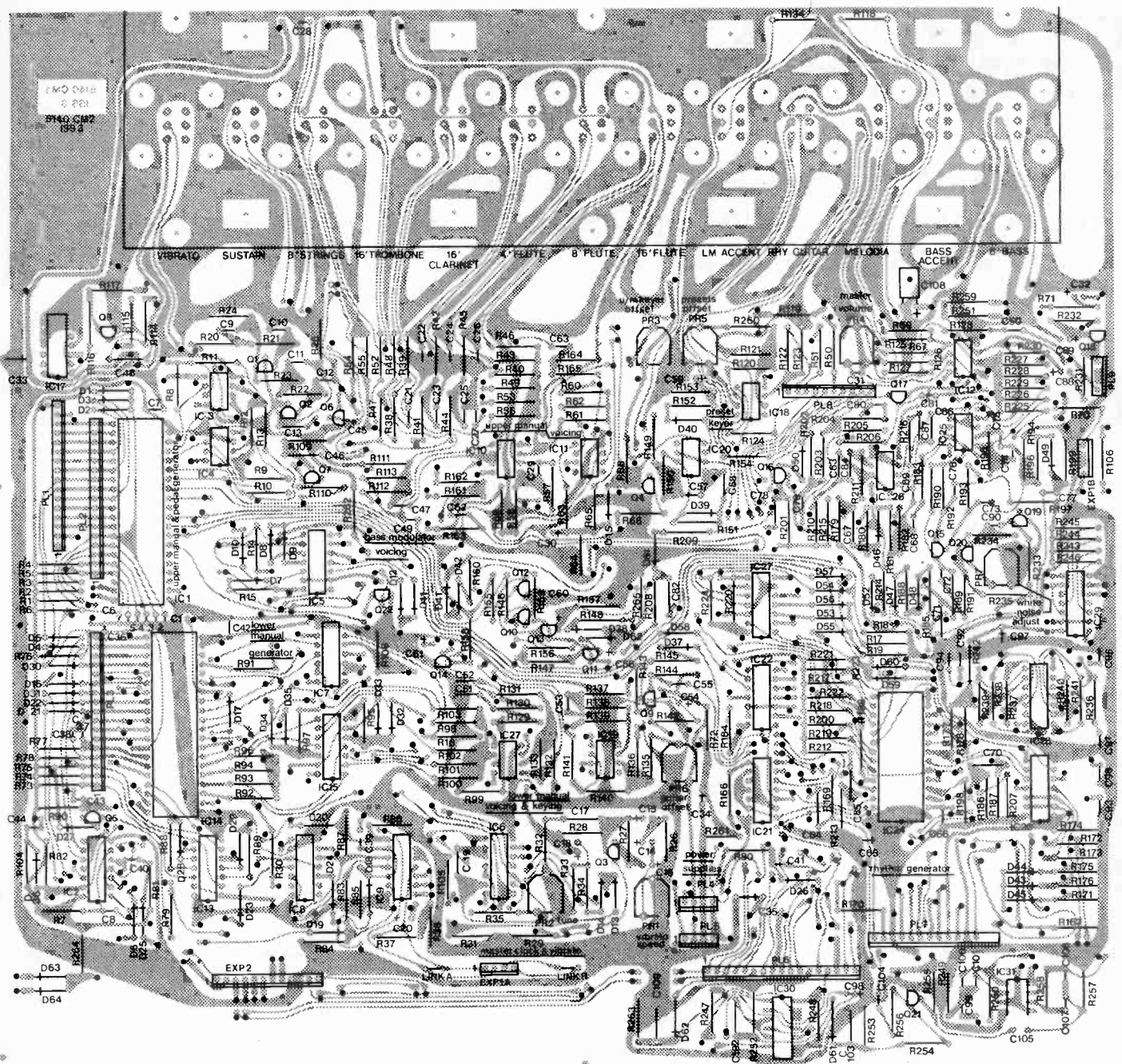


Fig. 2 (Above) The overlay for the main board. This is silk-screened on the finished item.


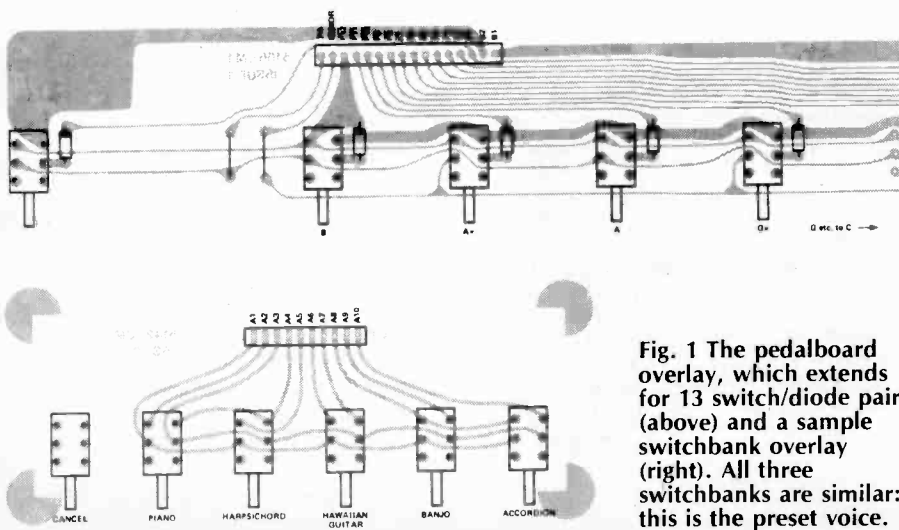


Fig. 1 The pedalboard overlay, which extends for 13 switch/diode pairs, (above) and a sample switchbank overlay (right). All three switchbanks are similar: this is the preset voice.

Fig. 3 (Below) The keyboard overlay.

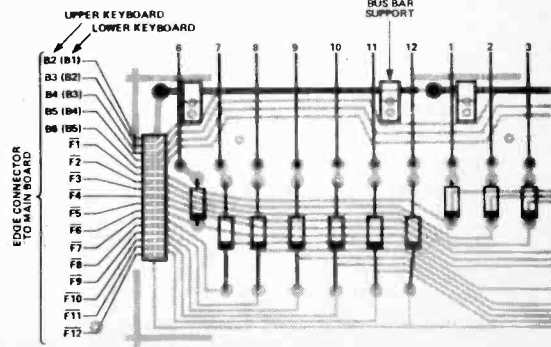

## PARTS LIST

Resistors (all 1/4W, 5%)  
 R1-6,71,73, 74,76,90, 148 6k8  
 R7,14,16,30,60,63, 67,85,95,97,108, 111-113,126,127 100k  
 135,159,167, 170-176,201, 260,265 15k  
 R8-10,69,164,262 47k  
 R11,28,32,40,50,57, 70,99,105,110,116, 141,180,199,204, 213,225,227,232, 235,243-246,256 22k  
 R12,20-25,36,38,39, 41-46,53,55,68,83, 87,109,115,124,138, 146,147,155,156, 158,162,168,177-179, 181,184,186-188,193, 194,198,200,207-209, 212,214,217-224,226, 228,230,247,264 10k  
 R13,17,19,26,47,49, 54,58,75,77-79,88, 122,129,131,137,161, 165,169 4k7  
 R15,72,206,255,261 1M0  
 R27,80-82,104,144, 151,185,203,205, 254,263 1k0  
 R29,66,91-94,96, 100-103,152,182, 215 2M2  
 R31,37,234 68k  
 R33,130,133,134, 145,153,197 100R  
 R34,210,242 12k  
 R35,89 150k  
 R48,52,62,114,120, 140,251 33k  
 R51,154,229 220k  
 R56,64,84,86,142, 150,157,189,211,233, 236,237,252,259 470R  
 R59,61,121,123, 136,139,166,196 2k2  
 R65,98,106,117,119, 160,192,202,231 27k  
 R118,125 18k  
 R128 1k5  
 R143,163,249,257 820R  
 R149 470k  
 R183,216,253,258 4M7  
 R190 330k  
 R191 270k  
 R238-241 39k  
 R248 820k  
 R250


Potentiometers (all miniature horizontal presets)  
 PR1,2 4k7

PR3,5,6 47k  
 PR4 220k  
 PR7 10k

Capacitors  
 C1-6,36-38,43,96 220pF  
 C7,23-26,40-42,44, 62,66,79 47nF  
 C8,28,53,68,69,76, 81,90,91,105 10nF  
 C9,11,21,22,27,39,47, 49,50,55,63,104 22nF  
 C10,12,29,72-75,99 2n2  
 C13,51,52,58,70,71, 78,83,84,86,87,103 100nF  
 C14-16,20,32,45,54, 59,88,89,98 1u0  
 C17,46,48,64,82,85 470nF  
 C18,30,56,60,61 10uF  
 C19 27pF  
 C31 100pF  
 C33,35 1000uF  
 C34,57,65,97 100uF  
 C67,102 220nF  
 C77,80,100,101,106, 107 4n7  
 C92 270pF  
 C93 1n8  
 C94 180pF  
 C95 3n3

Semiconductors  
 IC1 M208  
 IC2,7,8,15 4016B  
 IC3,4,10,12,16,25, 26,31 1458  
 IC5,22,27,30 4001B  
 IC6,21 4069UB  
 IC9 4081B  
 IC11,18,19 3080E  
 IC13 4071B  
 IC14 M108  
 IC17 4013B  
 IC20 555  
 IC23 4025B  
 IC24 M258EP2  
 IC28 40106B  
 IC29 4070B  
 Q1-5,7,8,10-14, 16-22 2N3704  
 Q6,9,15 2N3703  
 D1-61 1N4148  
 ZD1 6V2 400mW zener

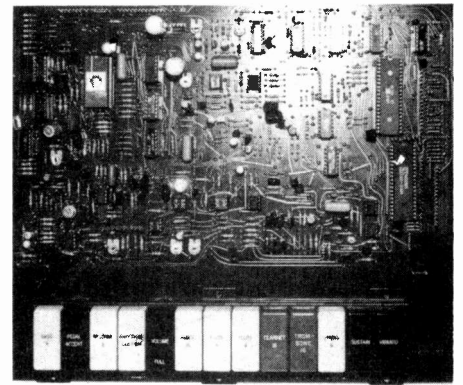Miscellaneous  
 PL1 16-way Molex  
 PL2,3,6 17-way Molex  
 PL4,5,9 4-way Molex  
 EXP1A,EXP1B 12-way Molex  
 PL7,EXP2 10-way Molex  
 PL8 PCB; 13-way rocker tab unit, PCB-mounting.



A picture of the assembled main board.


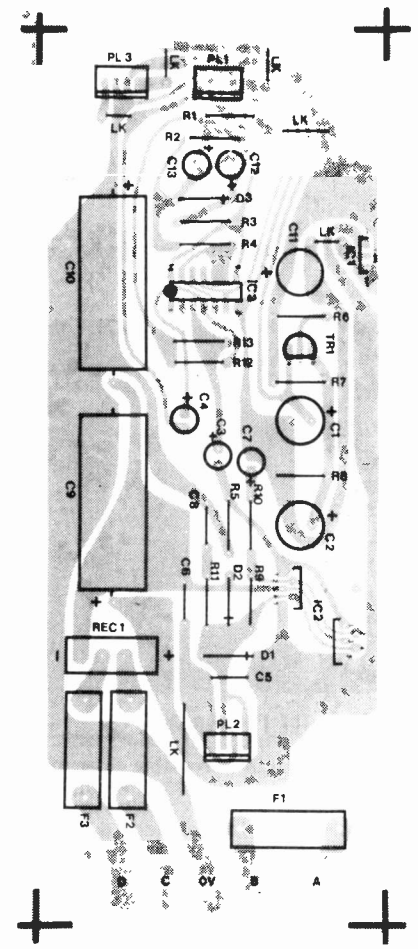


Fig. 4 (Above) The component overlay for the amplifier/power supply.

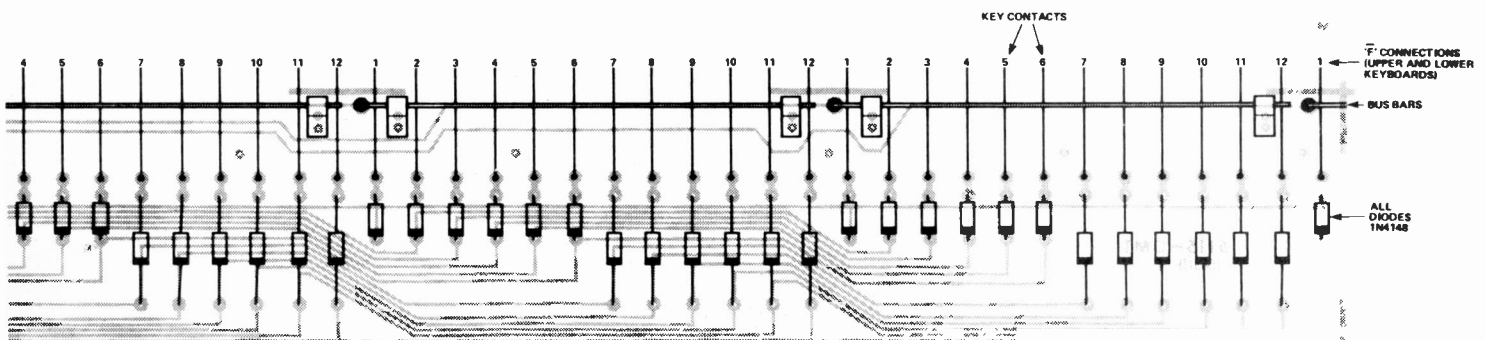





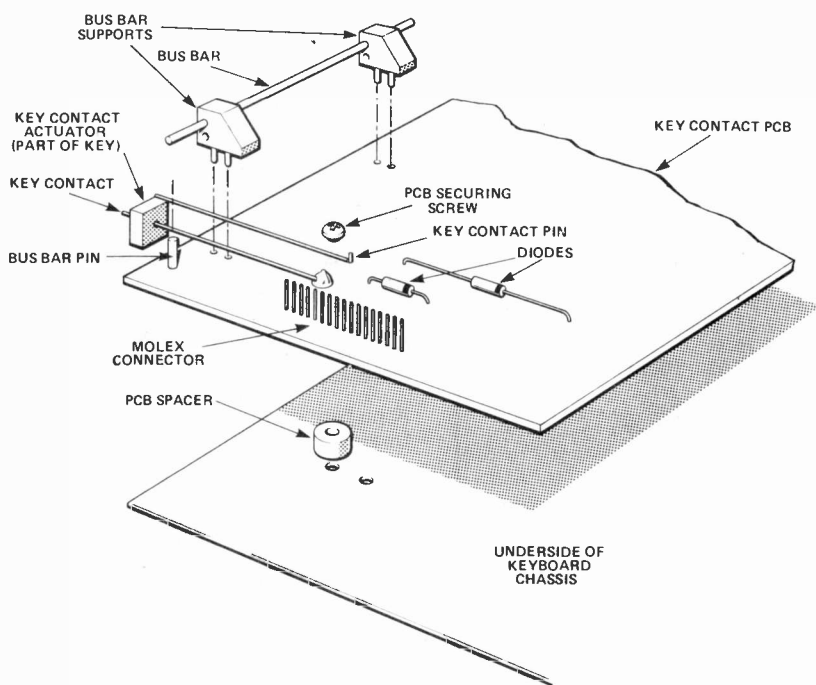


Fig. 5 Diagram showing the keyboard assembly. Compare with the photograph below.

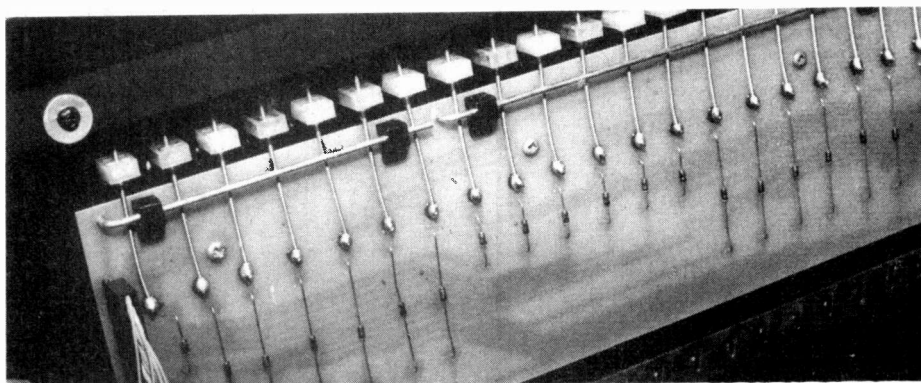
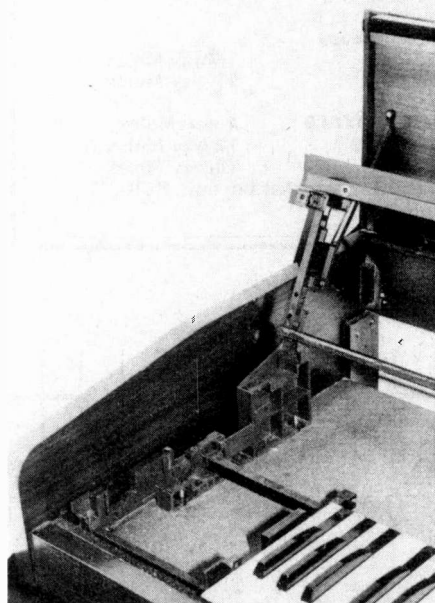
## BUYLINES

The Victory organ is available either as a complete kit or as sub-kits. The sub-kits are as follows: Starter kit (all parts for upper manual organ sounds); £98.80: Presets kit (upper manual preset voices); £14.54: Lower manual and bass kit (the lower manual and bass voices); £71.64: Pedal board kit; £30.84: Rhythm unit kit (includes ROM with programmed rhythm and bass patterns); £24.74: Amp and power supply unit; £36.96: Swell pedal and speakers; £34.54. VAT must be added to all prices. The total for all the sub-kits is £312.06 plus VAT but if the complete Victory kit is ordered at one time the price is reduced to £280.54 plus VAT. If you wish to build the organ in the cabinet shown in the photographs, it costs £143 and is supplied ready assembled with pre-drilled holes for the keyboard assemblies. A demonstration tape is available for £1.70 plus VAT. Carriage on all kits is extra, and individual components may also be ordered: a leaflet from the suppliers contains full details of the prices. Contact Leighton Electronic Services Ltd, 17 Bridge Street, Leighton Buzzard, Beds. LU7 7AH (telephone 0525 382504, telex 826717) for more information.



For easy construction, the keyboards hinge up and lift off.

shown. These will force-fit the holes in the PCB but may be glued or held against the board by using a small amount of Vaseline if the force fit proves difficult. Insert a spacer in each hole. Next, invert the keyboard and support it at the ends. This protects the surface of the keys and also ensures that the black keys are not depressed, as would be the case if the keyboard were just inverted and placed on a surface. It can now be seen that there are two rows of PCB securing holes in the keyboard chassis running along its length. Using the row nearest the front of the keys, lower the contact PCB onto the chassis and secure it with the screws supplied.


Finally the contacts can be fitted. Place a contact through the hole in the key contact actuator and move the wider end of the contact alongside its associated pin. Position the contact such that any excess length is through the contact's actuator and not at the pin end. Solder the contact to the pin. Repeat with all the contacts. Mechanical noise from the keyboard can be kept to a minimum by the insertion of a small amount of silicon grease or similar lubricant into the key contact actuator prior to the contact insertion.

## Cheeky Comments

The sidecheeks (the bits on the end of the keyboards) are injection mouldings supplied with the correct cut-outs, where required, for the mounting of the various switches and pots. The preset voices, rhythm and automatic function switchbanks are each mounted on a small PCB with a connector, and these assemblies are screwed onto mouldings on the underside of the sidecheek. The push-on button caps are secured to the switches with glue. It should be noted that the 'preset voices' switches have a slightly wider spacing than the other two switchbanks and have correspondingly larger push-buttons: be sure to have the correct ones before using the glue!

The voices/effects switchbank is mounted directly onto the main PCB; it comes complete with coloured and printed switch covers. The complete assembly of board and switchbank is then screwed to its sidecheek. The sidecheeks fit simply onto the keyboard chassis by clipping them in at the front and securing them at the back edge by two screws.

# PROJECT: Organ

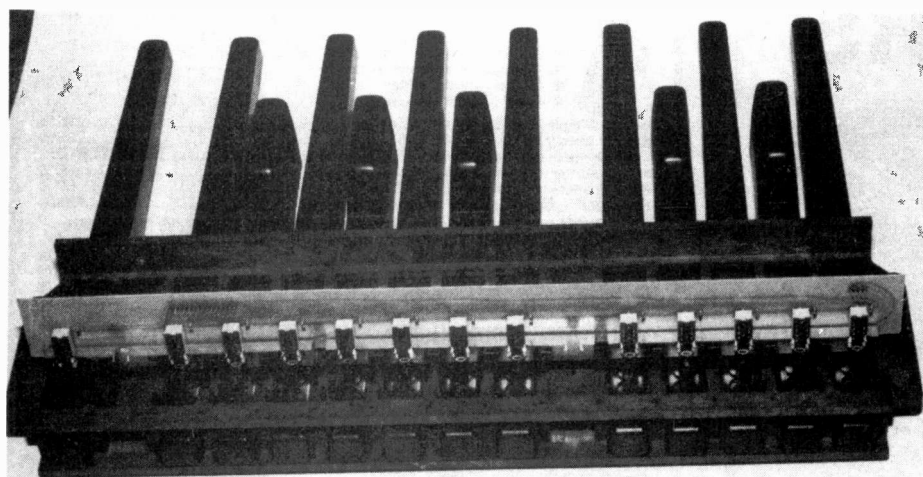


Here you can see the pedalboard PCB mounting arrangement.

All interboard connections are made using ribbon cable and insulation displacement connectors (IDC).

The pedalboard is a complete assembly requiring only the contacts to be fitted. These are in the form of two pole changeover switches (13 in all) which are mounted on a PCB with the associated pedal diodes and connector plug. The switches are then pedaled to the pedalboard and the pedalboard bolted into the cabinet using four bolts (see the photograph).

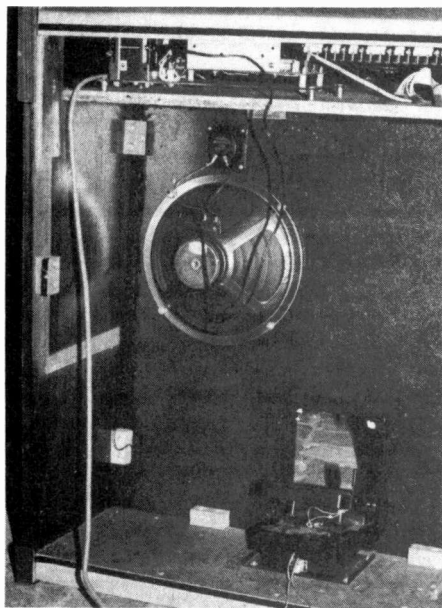The swell pedal assembly requires only the wiring of power (+12 V) to the bulb, and the coaxial signal lead from the preamp output to be connected across the LDR. This unit is then secured by four screws through its base plate: these need not be removed for access to the swell pedal as the pedal can be



A view inside the organ cabinet showing the tweeter, and speaker and swell pedal.

slid out from the front of the organ. The single pole glide switch is part of the swell pedal assembly and requires only ground to one contact and the glide circuitry to the other.

The amplifier assembly consists of the chassis, the PCB and the mains transformer. The latter two items are mounted on the former, which is also used as the heatsink for the +12 V regulator and the power amplifier IC. The regulator does not need to be electrically isolated from the chassis as its tab is at ground, but the amplifier IC must be electrically isolated using a mica washer.

The output signal from the amplifier is taken via the headphone socket to the speaker and piezo tweeter. No crossover is necessary with this type of tweeter.


The cabinet to be supplied needs no assembly and readily accepts all the subassemblies described above. It has integral mounting nuts for the bolts that secure the pedalboard assembly and speaker; a cut-out for mounting the tweeter is incorporated, as is a headphone socket mounting hole. The cabinet is finished in real wood veneer and has a removable back and lid for easy access.

## Setting Up

The simplest method of tuning the organ is to select A above middle C (that's the sixteenth note down from the top) on the upper keyboard with 8' flute selected. The frequency of this note should be 440 Hz. It may be adjustable either by using an A tuning fork and listening for beats, or by monitoring pin 1 of IC4a with a scope or frequency counter. The tuning control is PR2. Alternatively, IC6d pin 8 may be monitored for 1000.12 kHz.

The vibrato oscillator frequency is not critical and is usually about 6 Hz. Adjustment is made using PR1 and it may be monitored at the collector of Q3. Alternatively you can select, say, clarinet with vibrator and play individual notes, adjusting PR1 for the most pleasing effect.

The upper keyboard VCA, in common with the other two (preset voices and rhythm guitar), needs to be balanced as the control current envelope does not automatically centre around signal ground. The result of any imbalance on the upper keyboard VCA is to produce an undesirable thump when a key is depressed. So, with no upper keyboard voice selected, depress any upper key and adjust PR3 to one end of its travel. Then, while repeatedly depressing the key, move PR3 through its travel. It will be noted that at the extremes of the preset travel the thump will be

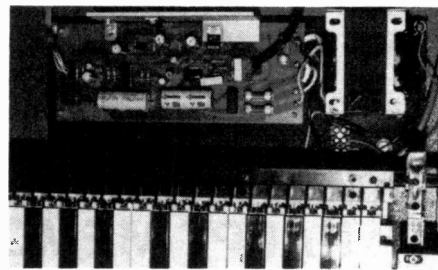

The amplifier/PSU board.

loudest and there will be a point on the preset where it is minimal. The VCA is balanced at this point.



The preset voices VCA is balanced by selecting the banjo voice and playing any upper key. Adjustment of PR5 will eliminate the thump which will occur with the voice at the banjo oscillator rate.

The rhythm guitar VCA can be balanced by using PR6 while the rhythm guitar voice is selected and any rhythm is selected. It is not necessary to play any keys and the task will be made easier by turning the rhythm volume right down and also having the lower manual accent on.

To adjust the noise volume preset (PR7), select swing on the rhythm unit and set the tempo to mid-range. Turn PR7 fully clockwise, then turn it anticlockwise until the white noise tends to sound continuous. Now turn it back slightly until the organ is making the normal sound of a snare drum. PR7 may be further adjusted clockwise to suit individual taste.

Finally, the overall volume of the organ can be adjusted by using PR4.

# MONITORS

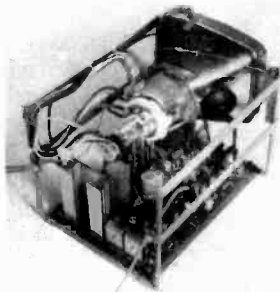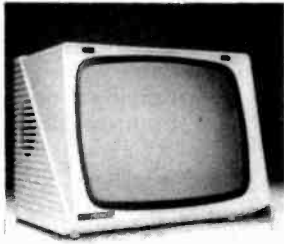

## HIGH RESOLUTION ~ AND LOW COST!

Either cased or open frames to OEM's. The specification is right, the price is even better.

Phone or write to our Sales Dept for immediate action and prices.

**CROFTON ELECTRONICS LTD**

35, Grosvenor Road, Twickenham, Middx, TW1 4AD.  
Telephone: 01-891 1923/1513 Telex: 295093 CROFTN G

## HAPPY MEMORIES

Part Type	1 off	25-99	100 up
4116 200ns	.90	.81	.78
4116 250ns	.70	.63	.60
4816 100ns For BBC comp	2.20	1.95	1.85
4164 200ns	3.99	3.56	3.42
2114 200ns Low power	1.15	1.00	.90
2114 450ns Low power	.95	.85	.80
4118 250ns	3.35	3.00	2.85
6116 150ns CMOS	3.35	3.00	2.85
2708 450ns	2.60	2.25	2.10
2716 450ns 5 volt	2.35	2.10	2.02
2716 450ns three rail	5.75	5.00	4.65
2732 450ns Intel type	3.50	3.15	3.00
2532 450ns Texas type	3.70	3.30	3.00
2764 250ns	4.90	4.35	4.20
Z80A-CPU £3.95	Z80A-PIO £2.99	Z90A-CTC £2.99	
6522 PIA £3.70	7002 A-D £4.60	3691 £2.75	
88LS120 £2.20	7805 reg .50	7812 reg .50	

Low profile IC sockets: Pins 8 14 16 18 20 22 23 28 40  
Pence 9 10 11 14 15 18 19 25 33

Soft-sectored floppy discs per 10 in plastic library case:  
5 inch SSSD £17.00 5 inch SSDD £19.25 5 inch DSDD £21.00  
5 inch DSQD £26.35  
8 inch SSSD £19.25 8 inch SSDD £23.65 8 inch DSDD £25.50

745LS series TTL, large stocks at low prices with DIY discounts starting at a mix of just 25 pieces. Write or 'phone for list.

Please add 50p post & packing to orders under £15 and VAT to total. Access & Visa welcome. 24hr service on (054 422) 618 Government & Educational orders welcome, £15 minimum. Trade accounts operated, 'phone or write for details.

### Happy Memories (ETI),

Gladestry, Kington, Herefordshire. HR5 3NY.  
Tel: (054 422) 618 or 628

## POWER DIMMER MODULES

A range of electronic modular dimmers designed to suit your custom channel and facility requirement


- Considerable saving over commercial equipment
- All the commercial facilities and more
- Compatible special effects
- Preset/remote/master
- Easily installed and wired

SPC - Simple but effective 1000W controller	£15.70
SPU - Used in conjunction with RS units for	£11.90
Remote desks in 1000 and 2000W versions	£23.90 (2K)
MC - Master dimmer for SPC/RS units	£7.90
RS - Remote controller for SPU/SPC Units	£9.40
SUP/REF - Supply/signals for up to 50 modules	£20.00

Discounts on above only (order £100 to £199 25% £200 to £299 £300 + 35%)	
<b>EFFECTS ACCESSORIES</b>	
MXSL - Four channel sound to light	£33.20
MXLS - Four Channel Sequencer	£21.40
MXLC-S Four Channel sound chaser	£24.00
MXECF - Dip/Dipless Electronic Crossfade	£28.70

### 3 CHANNEL SOUND/LIGHT CHASER £35.70

LB31000SLC

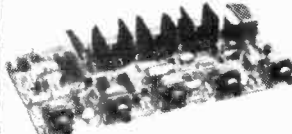

A high performance sound to light providing bass, mid and treble separation, employing active filters. Automatic switching to chase in the absence of a music signal 1000W/chan

### 3 CHANNEL SOUND/LIGHT LB31000SL



£22.70

All the advantages of the SLC without chase. Controls: bass/mid/treble/master sensitivity.

### STEREO DISCO MIXER/PREAMP

Main supply £7.20  
PFL supply £1.00

LBP3  
M - Magnetic  
C - Ceramic



£36.70

Magnetic or ceramic deck versions - please state  
All the requirements of a stereo disco preamp on one board, left and right deck mixers/controls/misc. mixer/tones/mic. auto fade over decks/and P.F.L. The unit can be used with virtually any power amp

### AND MORE!

- \* 4 CHAN SIL AUTO CHASER
- \* 4 CHAN MULTI SOUND CHASER
- \* 4 CHAN SEQUENCER
- \* 4 CHAN SOUND CHASER
- \* FASCIA PANELS

Active Crossovers £17.90 (supply £7.20)  
(3-way 300Hz/3kHz)

Don't hesitate to write or phone for immediate information. All prices include VAT. Please include 75p post except power dimmer (£2.75). Cheques/PO/COD/Access all welcome.

Tel: 01-640 6053 (Mon to Fri 9 to 4.30)

**L & B ELECTRONIC 34 Oakwood Ave, Mitcham, Surrey CR2 1AQ**

## PARNDON ELECTRONICS LTD.

Dept. No. 23, 44 Paddock Mead, Harlow, Essex CM18 7RR. Tel. 0279 32700

**RESISTORS:** 1/4 Watt Carbon Film E24 range ± 5% tolerance High quality resistors made under strictly controlled conditions by automatic machines. Banded/enclosed and colour coded.  
£1.00 per hundred mixed. (Min 10 per value)  
£8.50 per thousand mixed. (Min 50 per value)  
Special stock pack 60 values. 10 off each £5.50

**DIODES:** IN4148 3p each. Min order quantity 15 items  
£1.60 per hundred

**CAPACITORS, REGULATORS, SWITCHES, I.C. TRANSISTORS, DIODES, etc, etc.**  
FULL LIST AVAILABLE - SEND S.A.E.

**DIL SOCKETS:** High quality, low profile sockets  
8 pin - 10p. 14 pin - 11p. 16 pin - 12p. 18 pin - 19p. 20 pin - 21p.  
22 pin - 23p. 24 pin - 25p. 28 pin - 27p. 40 pin - 42p.

ALL PRICES INCLUDE V.A.T. & POST & PACKING - NO EXTRAS  
MIN ORDER - UK £1.00 OVERSEAS £5 CASH WITH ORDER PLEASE




### Visual Display Units

Burroughs MT686 VDUs  
These versatile micro controlled programmable terminals have 3 RCA 1802 CPUs and 64K of memory. 12" Green screen (80 x 25) RS232. 106 key detached keyboard. Can also be used as quality video monitor. £149 + £15 carr. WHILE STOCKS LAST.
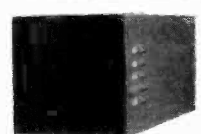
### CENTRONICS 306 LINE PRINTERS



professional fast compact line-printer. 80 columns, 120 char/sec. Parallel i/f. Quality at a silly price. Vertical format unit. To inc. operations manual. ONLY £149.00. Carriage (England) £17.50. Tech manual (230 pages) £10.00.



### FLOPPY DISC DRIVES

Fantastic MEMOREX 550 8" discs mounted in attractive case with power supply and fan. Shugart standard 50 way interface. Space for second drive. £199 (carr. £9.50).

## MAWSON ASSOCIATES

124 Lennard Rd, Beckenham, Kent BR3 1QP

WE ALSO BUY COMPUTERS AND COMPUTER PERIPHERALS

01-778 3600

Callers welcome by appointment s/h items sold working but not g'teed

# E.T.I. KITS

ALL KITS  
INCLUDE PCBs

Full kits include printed circuit boards, components, hardware, I.C. sockets, cases etc. unless stated (not batteries). If you do not have the issue of E.T.I. which

includes the project - you will need to order the instruction reprint at an extra 45p each. PCBs included. Reprints available separately 45p each + p&p 45p.

MAX/MIN THERMOMETER April 83	£43.78	SOUND BENDER Oct 81	£22.84
LOGIC PROBE March 83 less case	£8.98	WATCHDOG SECURITY ALARM Aug 81	£47.86
ALARM MODULE March 83	£24.57	RECHARGEABLE BATTERY extra	£19.98
ZX ADC Jan 83	£34.98	HANDCLAP SYNTHESIZER Aug 81	£22.98
SPECTRACOLUMN Dec 82. Less case and lights	£34.86	WAH PHASE June 81. Less pedal	£14.78
PLAYMATE Aug/Sept 82. less optional foot pedal + mains unit	£39.98	LED JEWELLERY June 81. Cross	£2.98
Case extra	£28.42	Star £9.91 Spiral £7.98	
DUAL LOGIC PROBE Sept 82	£14.98	GUITAR NOTE EXPANDER April 81	£17.98
AUTO VOLUME CONTROL Sept 82 £4.28 less case	£17.57	DRUM MACHINE April 81	£86.97
INSULATION TESTER May 82	£17.57	ENGINEERS STETHOSCOPE Mar 81	£20.98
AUTORANGING CAPACITANCE METER Mar/Apr 82	£71.99	SOUND PRESSURE LEVEL METER Feb 81	£443.98
HIGH QUALITY PHONO AMPLIFIERS Feb 82. Less case	£19.75	INFRA RED ALARM Feb 81	£59.98
MOVING COIL STAGE	£19.68	4 INPUT MIXER Dec 80	£21.74
MOVING MAGNET STAGE	£19.68	MUSICAL DOORBELL Dec 80	£12.77
PEST CONTROL Feb 82	£7.46	METRONOME Nov 80	£8.58
GUITAR TUNER Jan 82	£31.87	ULTRASONIC BURGLAR ALARM Aug 80	£28.50
COMPONENT TESTER Dec 81	£8.78	CAPACITANCE METER Aug 80	£22.28
CAR ALARM Nov 81	£19.77	CMOS LOGIC TESTER Aug 80	£11.98
		CLICK ELIMINATOR April 79 £87.70 Or Jess case	£49.98

## MORE KITS - SIMILAR STYLE TO ETI

Instructions included (separately 45p each)  
Please quote ref. no. when ordering

Q1 SEAT BELT REMINDER	£4.18	Q12 METRONOME	£12.98
Q2 ZX TAPE CONTROL	£8.93	Q13 ZX INTERFACE BOARD	£11.78
Q3 3 CHANNEL SOUND TO LIGHT	£21.44	Q14 DRUM SYNTHESIZER	£21.82
Q4 WEIRD SOUND EFFECTS GENERATOR	£5.98	Q15 TELEPHONE BELL REPEATER	£13.98
Q5 IN SITU TRANSISTOR TESTER	£8.98	Q16 ECHO REVERB	£34.43
Q6 ELECTRONIC DICE	£5.71	CASE extra	£3.78
Q7 DIGITAL CAPACITANCE METER	£21.82	Q17 MEMORY BANK - MINI SYNTH	£30.43
Q8 CABLE TRACER	£10.43	Q18 MASTHEAD AMPLIFIER	£14.98
Q9 SIGNAL TRACER	£4.31	Q19 GUITAR PRE AMP	£2.28
Q10 CONTINUITY CHECKER	£5.98	CASE extra	£2.28
Q11 FUZZBOX	£11.43	Q20 ULTRASONIC BURGLAR ALARM	£20.43

## MAGENTA ELECTRONICS LTD

EB26, 136 HUNTER ST., BURTON-ON-TRENT, STAFFS  
DE14 2ST 0283 65435. MON-FRI 9-5. MAIL ORDER ONLY

ADD 45p P&P  
TO ALL ORDERS

ACCESS AND BARCLAYCARD (VISA)  
ORDERS ACCEPTED BY PHONE OR POST.  
SAE ALL ENQUIRIES

Prices inc. VAT

OFFICIAL ORDERS WELCOME OVERSEAS  
Payment must be in sterling. IRISH REPUBLIC  
and BFO. UK PRICES + EUROPE. UK  
PRICES + 10%. ELSEWHERE - Write for Quote

# ALARMS MADE

## FREE CATALOGUE!

OUR GREAT NEW ILLUSTRATED CATALOGUE IS PACKED WITH INFORMATION ON SUPERB QUALITY, PROFESSIONAL BURGLAR ALARM EQUIPMENT

AT UNBEATABLE PRICES!

SEND S.A.E. OR PHONE NOW  
FOR YOUR COPY

THIEFCHECK BURGLAR  
ALARM D-I-Y SYSTEM

THIEFCHECK  
MAIN  
DISTRIBUTOR

A.D. ELECTRONICS  
DEPT. HE3  
217 WARBRECK MOOR  
AINTREE LIVERPOOL  
L9 0HU051 523 8440

## ELECTRONIC BARGAIN SUPPLIES

AMPLIVOX ULTRA LIGHTWEIGHT TRANSDUCER EARPHONES. Impedance 300 ohms. Made to fit inside Protective and crash helmets or can be used as pillow earphones. As new £4 per pair. P.P. £1.00. 2 pairs £8.00 post free. 4 pairs £15.00 post free.

NEW SURPLUS RELEASE VERSATILE BENCH POWER SUPPLY UNITS. Contains high quality transformer made to exacting specifications giving one 20v output and one 20-0-20v output. All outputs 3 amps. D.C. input 110/250v. 50c/s. Bridge rectification. contained on metal chassis with robust compact case size 7"x5 1/2"x4 1/2". Easily modified to give 40 or 60v outputs. Makes an ideal variable power supply. Normally cost around £60.00. OUR PRICE AS NEW with circuits £8.50. Carr. £3.00. 2 units for £20.00 Carr. free.

PLEASE ADD 15% VAT to all orders including carriage and P.P.

GENUINE TRANSFORMER BARGAIN. Brand new Westool 15v. 1 amp transformers. Mains input £2.75 each. P.P. 75p. Or 2 for £5.50. P.P. £1.00.

FOOT SWITCH. (Mains operation). Contains two micro switches and lead. Metal case. Good condition £3.50 each. Postage 50p. 2 for £7.50 post free.

HAVE YOU SEEN THE GREEN CAT. 1,000s of new components, radio, electronic, audio at unbelievably low prices. Send 50p for catalogue. (Refundable on purchases.)

TRY A JUMBO PACK. Contains transistors, resistors, caps, pots, switches, radio and electronic devices. OVER £50 WORTH for £11.00. Carriage and packing £2.50.

MINI JUMBO PACK (£20 worth) for £5.00 P.P. £1.50.

Depot: ET12 12/14, Harper Street, Leeds LS2 7EA  
Tel: (0532) 452045. Retail premises at above address (opposite Corals), 9 to 5. Mon to Sat. Sunday 10 to 1 by appointment. Govt. Surplus items always in stock

Myers Electronic  
Devices

## Constructor Series Speakers

KEF

IT'S  
SO  
EASY

Have fun, save money, building a Kef design with a Wilmslow Audio CS Total kit.


No electronic or woodworking knowledge necessary and the end result is a proven top-quality design that you'll be proud of.

Each kit contains all cabinet components, accurately machined for easy assembly, speaker drive units, crossovers, wadding, grille fabric, terminals, nuts, bolts, etc.

The cabinets can be painted or stained or finished with iron-on veneer or self adhesive woodgrain vinyl.

Easy foolproof assembly instructions supplied. Set of constructor leaflets sent free on receipt of large S.A.E.

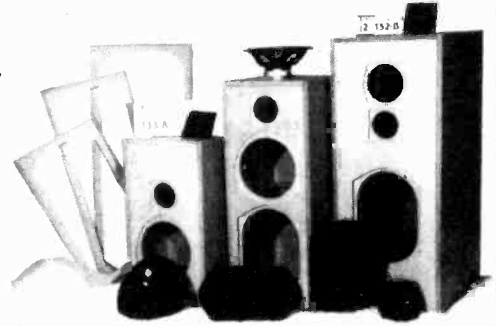Prices: CS1 (As 101) £110 pr. inc. VAT, plus carr./ins. £ 5.50  
CS1A (simplified LS3/5A) £103 pr. inc. VAT, plus carr./ins. £ 5.50  
CS3 (as 103.2) £129 pr. inc. VAT, plus carr./ins. £10.00  
CS5 (as Carlton II) £192 pr. inc. VAT, plus carr./ins. £15.00  
CS7 (as Cantata) £250 pr. inc. VAT, plus carr./ins. £18.00



0625 529599

35/39 Church Street, Wilmslow, Cheshire SK9 1AS

Catalogue - £1.50 post free



Lighting service on telephoned credit card orders!



### RECONDITIONED TELEPHONES

Push Button Trimphones £15 + £1.80 p&p. 2 for £28 + £2.50

Push Button 746 £13.50 + £1.80. 2 for £25 + £2.50

Recent Style Dial Phones £4.75 + £1.80. 2 for £9 + £2.50. 5 for £20 + £5

Seconds (in good working order)  
Class A (not too bad) £3.50 + £1.80. 5 for £15 + £5  
Class B (grotty) £2.25 + £1.80. 5 for £9 + £5

Desk-top Ten Way Manual Exchange (key & lamp unit) £8 + £1.80 P&P

Older style black telephones, £3. p&p as above. Our leaflet explains how to use G.P.O. phones in home intercom systems.

5 Digit Counters 48V coil. Non resettable 75p

UNISELECTORS. 50v, 4 Bank + Horning Bank, 25 way £3.50

P.O. TYPE 4 pole jack plug with moulded lead and panel socket. ONLY £1

Various stabilised power supplies available - Excellent prices send for details.

FREE on request - Leaflet "D.I.Y. Telephone Systems and Automatic Exchange Design".

### LOW-COST, RUGGED

### TEMPERATURE CONTROL

HIGH QUALITY



TEMP. GAUGE 0° - 120°C  
Remote sensor on 38" capillary, panel mounting dial 55mm. dia.

ONLY £2.50

### 16A 240V RANCO THERMOSTAT

Wide control range (low room temp. to over boiling point) Sensor on 22" capillary. £2.30, including control knob

### RANCO THERMAL CUT-OUT 100°C

15A 240V. Sensing coil on 41in. capillary panel mounting with reset button £1.20

BUY ONE EACH OF ABOVE FOR £5.50

LIGHT DEPENDENT RESISTORS in plastic housing with window, heavy-duty lead. Similar to ORP 61. You normally pay well over double for resistor alone. Only 30p or £2.35 for 10.

GEARED Synchronous motor, 8 r.p.m., 240V A.C. 3 Watt £2.

SOLENOID GAS VALVE. 240V A.C. 5 P.S.I. suitable for non-corrosive fluids. £2.20

BULGIN 3 pin free plug & panel socket, 2A 240V 50p

DIAL-OUT WITH YOUR COMPUTER. P.C.B. with custom chip, drive circuits and high-speed relays enables your computer to dial-out (with suitable interface). Ex-equipment. Tested. £12 with explanatory notes.



L.E.M. SERVICES  
22 Emcote Road,  
Warwick,  
Warwickshire

ADD 50p P&P  
ORDERS OVER  
£7.50 POST FREE  
unless stated otherwise

ALL ITEMS - MONEY BACK IF NOT DELIGHTED.




# TECH TIPS

## Simple Organ

J. P. Macaulay, Crawley

With the financial climate being what it is the following circuit may be of interest to harassed parents whose children want a stylophone. A simple oscillator is formed with two CMOS NAND gates (half a 4011B). Under quiescent conditions no sound is emitted. When the stylus is placed on the keyboard the circuit is made through the selected preset and the oscillator produces a square wave which is coupled to the output stage, an LM386. This IC is ideally suited to this application since its maximum output is limited to 200 mW and its quiescent current consumption is 3 mA. This, together with the fact that both ICs will work with battery voltages as low as 4 V, means that a fairly long battery life can be expected.

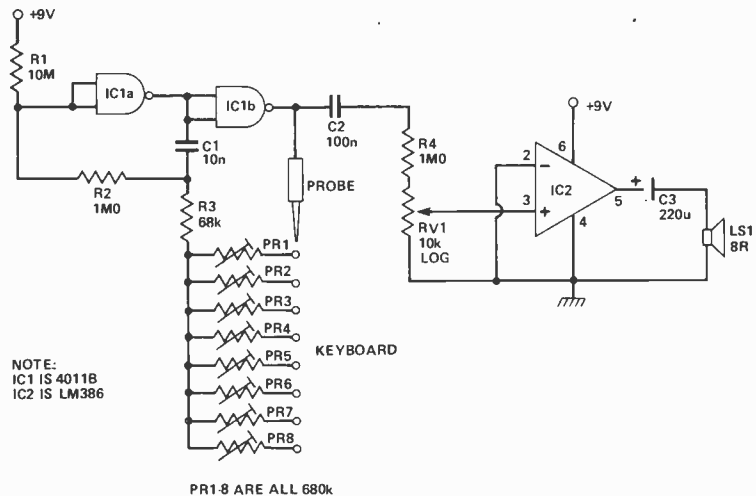
The organ will obviously require some form of keyboard. A simple one can be made from a piece of 0.15" matrix Veroboard with alternate tracks removed. Tuning is most easily done with the aid of a digital frequency meter; if all else fails the instrument can be tuned by ear against a piano.


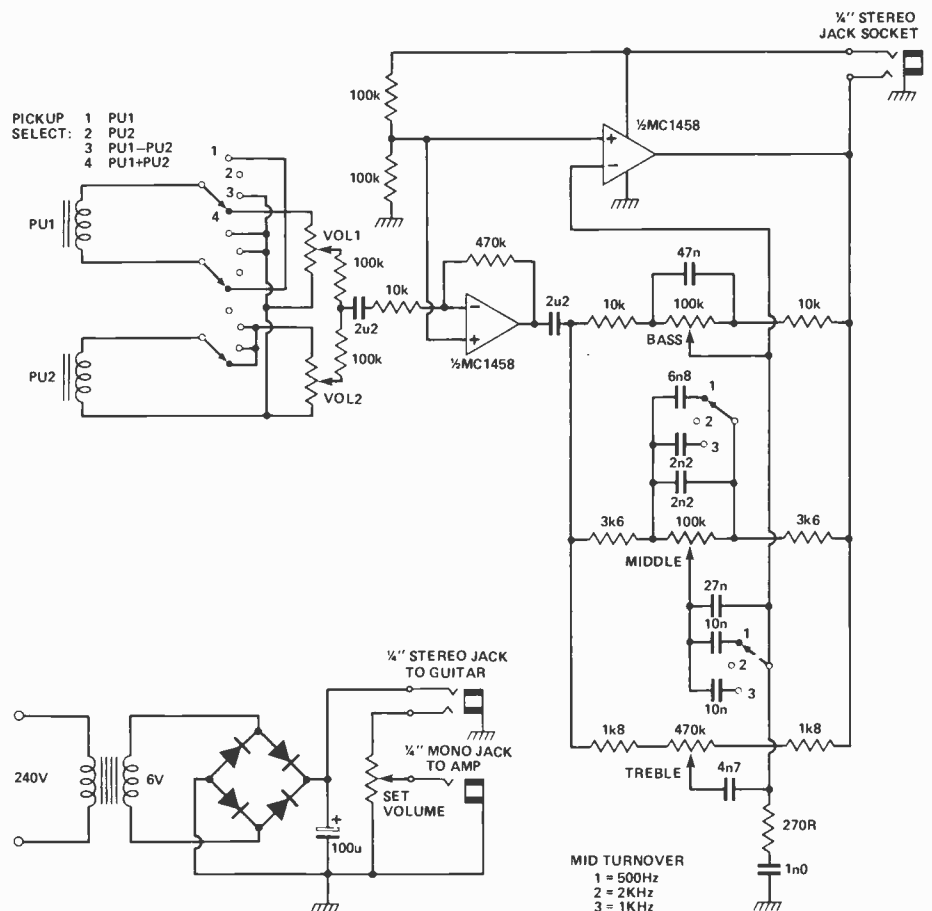
## Electronic Guitar

Quentin Rice, Mitcham

The circuit shown here was fitted inside a friend's Rickenbacker bass to increase the versatility of the guitar. Its controls are as follows: pickup/phase select, volume 1 and 2, bass, middle and treble tone controls and middle turnover frequency. It has low current consumption and can be used either with a battery, or with the 'phantom' power supply connected to the jack socket. It seems likely that most guitars will feature active circuitry in the future, giving musicians greater flexibility during a live performance.



Tech-Tips is an ideas forum and is not aimed at the beginner. We regret we cannot answer queries on these items. ITI is prepared to consider circuits or ideas submitted by readers for this page. All items used will be paid for at a competitive rate.

Drawings should be as clear as possible and the text should be typed. Text and drawings must be on separate sheets. Circuits must not be subject to copyright. Items for consideration should be sent to ETI TECH-TIPS, Electronics Today International, 145 Charing Cross Road, London WC2H 0EE.

# EUROPA ELECTRONICS

Mail Order to 160 High Road, Willesden, London NW10 2PB  
TEL: 01-459 7689

**SEND FOR A FREE LIST OF OUR LARGE RANGE OF ITEMS  
ALL DEVICES ARE NEW, FULL SPEC AND GUARANTEED**

Post & Packing: Add 30p to all orders under £5.

VAT: All UK orders add 15% to total cost including p. & p.

74LS SERIES	74LS148	75p	TTL	TRANSISTORS	4000 CMOS	LINEAR IC's
74LS01	74LS151	40p	7400	AD161	4000	741
74LS02	74LS153	40p	7401	AD162	4002	748
74LS03	74LS154	80p	7402	BC107	4006	(A3019
74LS05	74LS155	30p	7403	BC108B	4007	(A3046
74LS06	74LS156	36p	7404	BC109	4008	(A3048
74LS07	74LS157	25p	7405	BC109C	4009	(A3059
74LS08	74LS158	30p	7406	BC117	4010	(A3060
74LS09	74LS160	36p	7407	BC119	4011	CA3080E
74LS10	74LS161	36p	7408	BC121L	4012	CA3086
74LS11	74LS162	36p	7409	BC122L	4013	CA3130E
74LS12	74LS163	36p	7410	BC123L	4014	CA3130T
74LS13	74LS164	40p	7411	BC124L	4015	CA3140T
74LS14	74LS165	50p	7412	BC127	4016	CA3140E
74LS15	74LS166	60p	7413	BC128	4017	CA3160E
74LS16	74LS167	60p	7414	BC129	4018	CA3161E
74LS17	74LS168	85p	7415	BC131	4019	CA3182E
74LS18	74LS169	85p	7416	BC132	4020	CA3189E
74LS19	74LS170	70p	7417	BC133	4021	CA3240E
74LS20	74LS171	55p	7418	BC134	4022	CA3280G
74LS21	74LS172	40p	7419	BC135	4023	LF347
74LS22	74LS173	55p	7420	BC136	4024	LF351
74LS23	74LS174	40p	7421	BC137	4025	LF353
74LS24	74LS175	40p	7422	BC138	4026	LF355
74LS25	74LS176	40p	7423	BC139	4027	LF356
74LS26	74LS177	40p	7424	BC140	4028	LF357
74LS27	74LS178	40p	7425	BC141	4029	LM301A
74LS28	74LS179	40p	7426	BC142	4030	LM301
74LS29	74LS180	40p	7427	BC143	4031	LM311
74LS30	74LS181	90p	7428	BC144	4032	LM318
74LS31	74LS182	120p	7429	BC145	4033	LM319
74LS32	74LS183	120p	7430	BC146	4034	LM324
74LS33	74LS184	120p	7431	BC147	4035	LM332
74LS34	74LS185	120p	7432	BC148	4036	LM334Z
74LS35	74LS186	120p	7433	BC149	4037	LM335Z
74LS36	74LS187	120p	7434	BC150	4038	LM339
74LS37	74LS188	120p	7435	BC151	4039	LM348
74LS38	74LS189	120p	7436	BC152	4040	LM380
74LS39	74LS190	120p	7437	BC153	4041	LM381N
74LS40	74LS191	36p	7438	BC154	4042	LM382
74LS41	74LS192	36p	7439	BC155	4043	LM384
74LS42	74LS193	36p	7440	BC156	4044	LM386
74LS43	74LS194	36p	7441	BC157	4045	LM387
74LS44	74LS195	36p	7442	BC158	4046	LM388
74LS45	74LS196	45p	7443	BC159	4047	LM389
74LS46	74LS197	45p	7444	BC160	4048	LM393
74LS47	74LS198	45p	7445	BC161	4049	LM390
74LS48	74LS199	45p	7446	BC162	4050	LM3909N
74LS49	74LS200	45p	7447	BC163	4051	LM3911
74LS50	74LS201	45p	7448	BC164	4052	LM3914
74LS51	74LS202	45p	7449	BC165	4053	LM3915
74LS52	74LS203	45p	7450	BC166	4054	LM3916
74LS53	74LS204	45p	7451	BC167	4055	LM13600
74LS54	74LS205	45p	7452	BC168	4056	NE531
74LS55	74LS206	45p	7453	BC169	4057	NE544
74LS56	74LS207	45p	7454	BC170	4058	NE565
74LS57	74LS208	45p	7455	BC171	4059	NE566
74LS58	74LS209	45p	7456	BC172	4060	NE564
74LS59	74LS210	45p	7457	BC173	4061	NE565
74LS60	74LS211	45p	7458	BC174	4062	NE566
74LS61	74LS212	45p	7459	BC175	4063	NE567
74LS62	74LS213	45p	7460	BC176	4064	NE571
74LS63	74LS214	45p	7461	BC177	4065	NE592
74LS64	74LS215	45p	7462	BC178	4066	NE534P
74LS65	74LS216	45p	7463	BC179	4067	NE534F
74LS66	74LS217	45p	7464	BC180	4068	TB810
74LS67	74LS218	45p	7465	BC181	4069	TB820
74LS68	74LS219	45p	7466	BC182	4070	ZN423
74LS69	74LS220	45p	7467	BC183	4071	ZN425E
74LS70	74LS221	45p	7468	BC184	4072	
74LS71	74LS222	45p	7469	BC185	4073	
74LS72	74LS223	45p	7470	BC186	4074	
74LS73	74LS224	45p	7471	BC187	4075	
74LS74	74LS225	45p	7472	BC188	4076	
74LS75	74LS226	45p	7473	BC189	4077	
74LS76	74LS227	45p	7474	BC190	4078	
74LS77	74LS228	45p	7475	BC191	4079	
74LS78	74LS229	45p	7476	BC192	4080	
74LS79	74LS230	45p	7477	BC193	4081	
74LS80	74LS231	45p	7478	BC194	4082	
74LS81	74LS232	45p	7479	BC195	4083	
74LS82	74LS233	45p	7480	BC196	4084	
74LS83	74LS234	45p	7481	BC197	4085	
74LS84	74LS235	45p	7482	BC198	4086	
74LS85	74LS236	45p	7483	BC199	4087	
74LS86	74LS237	45p	7484	BC200	4088	
74LS87	74LS238	45p	7485	BC201	4089	
74LS88	74LS239	45p	7486	BC202	4090	
74LS89	74LS240	45p	7487	BC203	4091	
74LS90	74LS241	45p	7488	BC204	4092	
74LS91	74LS242	45p	7489	BC205	4093	
74LS92	74LS243	45p	7490	BC206	4094	
74LS93	74LS244	45p	7491	BC207	4095	
74LS94	74LS245	45p	7492	BC208	4096	
74LS95	74LS246	45p	7493	BC209	4097	
74LS96	74LS247	45p	7494	BC210	4098	
74LS97	74LS248	45p	7495	BC211	4099	
74LS98	74LS249	45p	7496	BC212	4100	
74LS99	74LS250	45p	7497	BC213	4101	
74LS100	74LS251	45p	7498	BC214	4102	
74LS101	74LS252	45p	7499	BC215	4103	
74LS102	74LS253	45p	7500	BC216	4104	
74LS103	74LS254	45p		BC217	4105	
74LS104	74LS255	45p		BC218	4106	
74LS105	74LS256	45p		BC219	4107	
74LS106	74LS257	45p		BC220	4108	
74LS107	74LS258	45p		BC221	4109	
74LS108	74LS259	45p		BC222	4110	
74LS109	74LS260	45p		BC223	4111	
74LS110	74LS261	45p		BC224	4112	
74LS111	74LS262	45p		BC225	4113	
74LS112	74LS263	45p		BC226	4114	
74LS113	74LS264	45p		BC227	4115	
74LS114	74LS265	45p		BC228	4116	
74LS115	74LS266	45p		BC229	4117	
74LS116	74LS267	45p		BC230	4118	
74LS117	74LS268	45p		BC231	4119	
74LS118	74LS269	45p		BC232	4120	
74LS119	74LS270	45p		BC233	4121	
74LS120	74LS271	45p		BC234	4122	
74LS121	74LS272	45p		BC235	4123	
74LS122	74LS273	45p		BC236	4124	
74LS123	74LS274	45p		BC237	4125	
74LS124	74LS275	45p		BC238	4126	
74LS125	74LS276	45p		BC239	4127	
74LS126	74LS277	45p		BC240	4128	
74LS127	74LS278	45p		BC241	4129	
74LS128	74LS279	45p		BC242	4130	
74LS129	74LS280	45p		BC243	4131	
74LS130	74LS281	45p		BC244	4132	
74LS131	74LS282	45p		BC245	4133	
74LS132	74LS283	45p		BC246	4134	
74LS133	74LS284	45p		BC247	4135	
74LS134	74LS285	45p		BC248	4136	
74LS135	74LS286	45p		BC249	4137	
74LS136	74LS287	45p		BC250	4138	
74LS137	74LS288	45p		BC251	4139	
74LS138	74LS289	45p		BC252	4140	
74LS139	74LS290	45p		BC253	4141	
74LS140	74LS291	45p		BC254	4142	
74LS141	74LS292	45p		BC255	4143	
74LS142	74LS293	45p		BC256	4144	
74LS143	74LS294	45p		BC257	4145	
74LS144	74LS295	45p		BC258	4146	
74LS145	74LS296	45p		BC259	4147	
74LS146	74LS297	45p		BC260	4148	
74LS147	74LS298	45p		BC261	4149	
74LS148	74LS299	45p		BC262	4150	
74LS149	74LS300	45p		BC263	4151	
74LS150	74LS301	45p		BC264	4152	
74LS151	74LS302	45p		BC265	4153	
74LS152	74LS303	45p		BC266	4154	
74LS153	74LS304	45p		BC267	4155	
74LS154	74LS305	45p		BC268	4156	
74LS155	74LS306	45p		BC269	4157	
74LS156	74LS307	45p		BC270	4158	
74LS157	74LS308	45p		BC271	4159	
74LS158	74LS309	45p		BC272	4160	
74LS159	74LS310	45p		BC273	4161	
74LS160	74LS311	45p		BC274	4162	
74LS161	74LS312	45p</				

# LB ELECTRONICS

## DISC DRIVE BONANZA

PERTEC FD650 DSDD 8"	£199 + VAT
TEAC FD-S5F $\frac{3}{4}$ Height DSDD 80 track Brand New	£228 + VAT
Cannon 5 $\frac{1}{4}$ " drive SSDD Shugart Compatible	£139 + VAT

The above drives are suitable for the BBC Micro, we can supply full documentation if requested with purchase of the drives only. Also available is a word processing package with is a tape to disc program (i.e. will not run without discdrives).

Offered with Full documentation at £9.80 p&p 50p.

### BRAND NEW AND BOXED PLUS DATA P&P AT COST

Apple controller card for two drives .....£40.00 + VAT p&p 50p  
ASC11 coded qwerty Keyboard manufactured by Alphanumeric (Woking UK). Model 60K brand new plus data .....£19.95 p&p £1.50  
SELLOUT used (Guaranteed replacement by us) 2716 (5v) 1.50 each p&p 30p. 12 for £15 p&p 75p.  
25 WAY 'D' Types, plugs £1.85, sockets £1.85 (solder tail) p&p 30p. Telephone for bulk prices.  
CASE model 430 Data modem, no information .....£30 each p&p £3.50

(Manuals available £5.00 each)

### INTERSCAN ACCOUSTIC COUPLER

10" x 4" x 5" WITH ELECTRONICS, SOUND TIGHT UNIT, FOR STANDARD GPO HAND SET. NO DATA — £10.00 (INC VAT) P&P £1.75

8" Drive Cabinets complete with power supply (LINEAR) to take two 8" Drives, Brand New £99.95p + VAT (carriage cost)  
Twin 5" Cabinets with power supply £85.00 + VAT (to arrive shortly)  
9" Green Phosphor Monitors Brand New and Cased Composite Video Input 18mhz band width £78 + VAT each (carriage cost)

## LB ELECTRONICS

11 HERCIES ROAD,  
HILLINGDON,  
MIDDLESEX UB10 9LS,  
ENGLAND  
TEL: UXBRIDGE 55399



## CIRCUIT BOARD ELECTRONICS

THE NEW EXCITING

NAME IN PCB'S

FOR THE HOME ENTHUSIAST

COMPARE OUR PRICES

FOR COMPLETE PRICE LIST

WRITE TO  
CIRCUIT BOARD COMPONENTS  
55 MURDOCK ROAD  
BEDFORD  
TEL. BEDFORD 214219

Interak 1

## HOME COMPUTERS DO NOT WORK!

You've already got a "home" computer — am I right? You may be anyone — a Hospital Electronics Workshop, a University Computer Dept., an Electronics Research Establishment, or you may be just plain Joe Soap.

Either way round — you're fed up with the boss, or your wife (may be the same thing), always asking you — "Very nice, but what does it do?" I know you can make it do things, so you must be pretty clever, but what a mess. What's that heap of junk plugged n the back — talk about spaghetti!

They look lovely, home computers, don't they — until you bolt on all the things round the back that the designer couldn't (or wouldn't) include.

I think we both know what is needed: A "rack and card" build it yourself system (Interak 1!). Something like Acorn's and Tangerine's original plug in systems, before they went on to more profitable things, but you don't want it 6502-based — Interak 1 uses the Z80A, (doesn't everybody who has any sense?).

If you use Interak 1, the Z80A CPU is on one card, the VDU Interface is on another, Dynamic RAM on another, and so on. Very tidy, and very modular because "any card fits in any slot". And that ugly expansion adaptor, and the special box of bits you've got sticking out of the back, can be neatly re-packaged and slid into the spare slots in Interak 1.

I've got no space to say more (this advert's cost a few hundred pounds already!), so send me a stamp (20p) and/or SAE, or neither, or 'phone if you prefer, and I'll send you the 38-page low-down.

David Parkins

P.S. Although this advert may sound a bit corny (we have to get your attention somehow) Interak 1 really is a serious, sensible system with thousands of cards sold, and in daily use. Cards, Manuals, all available separately, inc. circuit diagrams.

Greenbank

Greenbank Electronics (Dept. T3E), 92 New Chester Road,  
New Ferry, Wirral, merseyside L62 5AG  
Telephone: 051-645 3391 (Dept T5E)

## MARCO TRADING SPECIAL OFFERS

### Transistors

BC308A— PNP 30V, 0.2A, 0.3W, 130MHZ. (Similar to: BC178, 205, 213, 252, 513, 558)

Price: 10 for 50p; 100 for £3.00; 1000 for £20.00; Larger Qty prices on application)

BC170: NPN 20V, 0.1A, 0.3W, 100MHZ (Similar to: BC108, 183, 208, 238, 383, 548, 583)

Price: 10 for 50p; 100 for £3.00; 1000 for £20.00. Larger Qty prices on application)

BC250A— PNP 30v, 1.2A, 0.3W, 130MHZ. (similar to: BC178, 213, 252, 308, 513, 558)

Price: 10 for 75p; 100 for £6.00; 1000 for £50.00. Larger Qty prices on application)

AU110— PNP 160V, 10A, 30W, (Similar to AU107, 2N5324, 2N5325)

Price: 10 for £12.00; 100 for £85.00

### Capacitors

470u 16V Radial (25mm x 15mm-4mm lead length) 5p each: £3.00 per 100  
1000u 16V Radial (30mm x 15mm-4mm lead length) 8p each: £5.00 per 100  
3300u 16V Axial (50mm x 20mm) 25p each: 10 for £2.00; 100 for £15.00

### Boxes

Plastic boxes complete with removable lids (Fixing screws not supplied) Size: 3" x 3" x 1 $\frac{1}{2}$ " Deep. Available in black or red (Please state colour when ordering). Price: 50p each, 10 for £4.00.

### Transformers

Good quality transformers with independent secondaries:  
Primary: 240V Secondary 1: 15-0-15V at 1 $\frac{1}{2}$ A per side, Secondary 2: 9V at 4A (with a bridge gives 12V DC)  
Price: £2.50 each (P&P £1.20 in addition to 35p normal charge).

### Multibloc 4-Way Extension Socket

PVC body with internal cable grip fitted with 13A fuse and neon indicator. Max total load 13A 250V; Length 10 $\frac{1}{2}$ ; Width 2 $\frac{1}{2}$ .  
Price: £4.50 each (P&P 25p in addition to 35p normal charge).

Send 35p NOW for our latest Catalogue. Fantastic value it includes capacitors, diodes, resistors, transistors, LEDs, boxes, cable, prepaid envelopes and much, much more.

Please add 35p postage and packing and 15% VAT to all orders.

Send orders to:

### MARCO TRADING (Dept ET4)

The Maltings, High Street, Wem, Shropshire SY4 5EN  
Telephone: WEM (0939) 32763

Every order receives our latest special offer lists. Or send SAE.

All orders despatched by return of mail.

9" MONITOR in attractive case. With info £25 each. Carr E7. Matching Keyboard with Numeric Keypad. ASCII coded, £25 each. P&P £5. The Pair £40. Carr E7.  
 12" MONITOR cased, with info, £20 each, Carr E7. Together with matching Keyboard, £35. Carr E7.  
 POWER UNIT 240V Input. Outputs +5V/15A; +24V/1.5A; -24V/3A, £12 each. Carr E7.  
 INSTRUMENT CASE, standard 19" width x 16" depth x 10" high. £5 each. Carr. E7.  
 I.C.L. type 7181 VDU with Keyboard, upper & lower case, £40 each.  
 FACIT CASSETTE UNIT Model 4203 with internal electronics £60.  
**FOR MORE INFORMATION CONTACT DWAYNE STEWART**

GEARED MOTOR 117/234 Volt Input 50HZ. 4" dia x 5 1/2" deep, 1" shaft. New £5 each P&P £4  
 MOTOR 12V DC Input. 3" dia x 4 1/2" deep, 1" shaft. New £2.50 each P&P £3.  
 DC MOTOR 6-12 Volts. Mechanical Constant Speed Control 1 1/2" dia. £1 each.  
 MOTOR 12V DC with pulley & semi-conductor speed control. £1 each.  
 SYNCHRONOUS MOTOR 2 Phase 9 volt AC. 375 RPM. Good torque (needs 30-40 mfd capacitor. Suitable for Robotics/Plotters etc) £1 each.

**OTHER SYNCHRONOUS/STEPPING MOTORS AVAILABLE. PLEASE ENQUIRE**

GEARED MOTOR 12V 50HZ. 4 Watt 1 rpm, 2" dia x 1 1/2" deep. £1.50 each.  
 CENTAUR FANS 4 1/2". Brand new, 100V 20W, 2 speed. £2 each P&P £2.  
 CENTAUR FANS 4 1/2". 115V New, £4.50 each.  
 MUFFIN 115V 4 1/2". unused, £3 each P&P £2.  
 TRANSFORMERS - All brand new, all 240 volts input.  
 Sec 25.5V 2.5A. Size 3 1/2 x 2 1/2". £2.50 each.  
 Sec 115V1A (auto) £1.25 each. Sec 6V 1.66A £1.50 each.  
 Sec 12V 100MA 50p each.  
 TRANSFORMER 127/220 Volt Input. Sec 12V 1A RMS £1.50 each.  
 TRANSFORMER 120 Volt Input. Sec 10-0-10V 1A 75p each.  
 Sub Min TRANSFORMER 0-120-240V Input. Sec 12-0-12V 4VA 75p each 10 off £8.  
 TOROIDAL TRANSFORMER 0-115-230V Input. Sec 13.5-0-13.5V 8VA. £1.50 each 10 off £12.  
 TOROIDAL TRANSFORMER 0-120-240V Input. Sec 0-12V; 0-12V 10VA per winding. Encapsulated. £4 each. 10 off £35.  
 Sub Min PULSE TRANSFORMER. Sec centre tapped. Suitable for Thyristor triggering 20p each. 10 off £1.80.  
 RAPID DISCHARGE CAPACITOR 8 mfd 4KV £5 each P&P £2.


TELEPHONES. 706 style black, blue, green, grey, £5 each. 10 off £45.  
 Discoloured £4 each. 10 off £30. 746 style black or grey £7.50 each. P&P £2 each. 4-10 units E7. Over 10 by arrangements.  
 TOKIN NOISE FILTER YG215FU. 250VAC 15A 50/60HZ. With fixing bracket. New £2 each.  
 VU METER. Scaled 0-5, size 1 1/2 x 7/8". 50p each 10 off £4.  
 I.T.T. LOUD SPEAKER. 3 1/2" dia. 50 ohm 0.2 Watt. New. 75p each. 10 off £6.50.  
 E.H.T. CABLE. Overall dia 5mm, 10p per metre. 100 metre drum £7.50 P&P £4.  
 Multi Colour RIBBON CABLE 10 way, 50p per metre, 10 metres £4. 14 way 75p per metre, 10 metres £5. 100 metres £40.  
 ILLUMINATED ROCKER SWITCH. 2 pole 250V 8 Amp, orange, 50p each. 10 off £4.  
 JOYSTICK SWITCH 4 directions, £3 each. P&P £2.  
 CATHODE RAY TUBES. Brand new. D14-121GM & D14-12GH £40 each, SE5/2A/P31 £25 each. Many others available, please enquire.  
 PCB KEYBOARD PAD. 19 push contacts, 0-9; A-F plus 3 optional, £1.50 each. 10 off £12.  
 KEYBOARD PAD. 12 Alma Reed Switches, push to make, 0-9; \*; # Blank, size 3 x 2 1/2 x 2" high, £4 each. 10 off £15. P&P £3.  
 EPROM 2716 Single rail, £1.50 each, 2564 £4 each.  
 SPECTRAL RELIANCE TEN TURN POT. 100 ohm ± 1%. Brand new, 75p each 10 off £8.  
 SLIDER POTENTIOMETER. Twin Gang, 200K or 2M. 35p each 10 off £3.  
 PANEL MOUNTING FUSE HOLDER for 1 1/2" fuse. 20p each. 10 off £1.50.  
 BELLING LEE CHASSIS MOUNTING FUSE HOLDER for 1 1/2" fuse, 15p each. 10 off £1.  
 I.E.C. MAINS LEAD. 2 metre length, heavy duty, 80p each. 10 off £5.  
 4 CORE CURLY WIRE extending to 2 metres, 20p each. 10 off £1.80.  
 MICROPHONE/EARPIECE INSERTS. Brand new. 75p each. 10 off £8.

**EXECUTIVE TELEPHONE-PUSH BUTTON.** Functions include 10 number memory; repeat dialing; internal Microphone & Speaker and separate handset etc. Will connect direct to British Telecom System. BRAND NEW. ONLY £25 ea. P&P £4.  
**PUSH BUTTON TELEPHONES** for Internal Systems. BRAND NEW. P&P £2 ea. 746 style Two Tone Grey £8 each. KRONE type FeTAp 731. Beige. £6 ea. Quantity discount - Please Enquire

Minimum Order of Goods £3. Minimum P&P £1.50. VAT at 15%. MUST be added to TOTAL OF GOODS & PACKAGING.  
 Many more components and test equipment available. S.A.E. or telephone for lists.

**STEWART OF READING**  
 110 WYKHAM ROAD, READING, BERKS. RG6 1PL  
 Tel: (0734 68041)  
 Callers welcome 9 am-5.30 pm Monday to Saturday inclusive

**ROBOTICS FANS!!! LOOK!!**

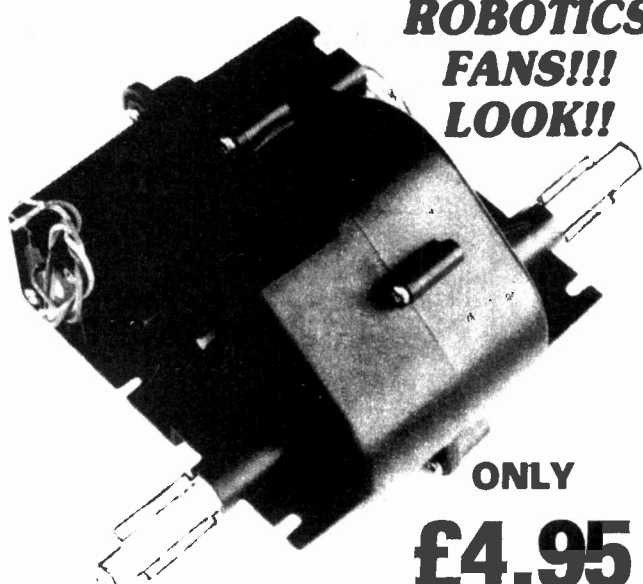

**ONLY £4.95**

**"BIG TRAK" MOTORIZED GEARBOX**  
 These units are as used in the "Big Trak" computerized vehicle, and offer the experimenter in robotics the opportunity to purchase the electro-mechanical parts required in building remote controlled vehicles. The unit comprises:  
 a) 2 x 3V motors, linked by a magnetic clutch, thus enabling turning of the vehicle;  
 b) A gearbox contained within the black ABS housing reducing the final drive speed to approx 50rpm.  
 Data is supplied with the unit showing various options on driving the motors, as well as a direction controller circuit, enabling the unit to turn right, left or go straight ahead.

**AA NI-CADS 10 for £9.95**  
 Brand new nickel cadmium batteries by GE, standard 1.2V at 450mA/H. Professional quality with solder tags both ends. Special price, £1.40 ea, 10 for £9.95; Box of 80 £65.  
 Nicad Charger: Charges up to 4Aa, C or D cells + P3C. Only £7.95.


**COMPUTER BATTLESHIPS**  
 Probably one of the most popular electronic games on the market. Unfortunately the design makes it impractical to test the PCB as a working model, although it may well function perfectly. Instead we have tested the sound chip, and sell the board for its component value only (PCB may be chipped or cracked). SN576477 sound IC; TMS1000 u-processor; batt clips. R's, C's etc. Size 160 x 140mm. Only £1.50. Instruction book and circuit 30p extra.

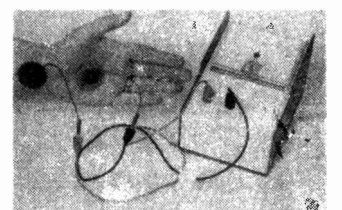**NOW REDUCED TO £3.95**



**SIMON GAME**  
 Simon is back again. Another supply of ready built PCB's for this flashing light/pulsating tone computerised game is now with us. Supplied tested and working with speaker and instructions. £4.95.

**ELECTRO DIAL**  
 Electrical combination lock-for maximum security-pick proof. One million combinations! Dial is turned to the right to one number, left to a second number, then right again to a third number. Only when this has been completed in the correct sequence will the electrical contacts close. These can be used to operate a relay or solenoid. Overall dia 65mm x 60mm deep. Only £3.95.



**FERRIC CHLORIDE**  
 New supplies just arrived - 250mg bags of granules, easily dissolved in 500ml of water. Only £1.15. Also abrasive polishing block 95p.

**STABILIZED PSU PANEL**  
 A199 A versatile stabilised power supply with both voltage (0-30V) and current (20mA-2A) fully variable. Many uses inc bench PSU, Ni-cad charger, gen. purpose testing. Panel ready built, tested and calibrated £7.75. Suitable transformer and pots £8.00. Full data supplied.

**LIE DETECTOR**  
 Not a toy, this precision instrument was originally part of an "Open University" course, used to measure a change in emotional balance, or as a lie detector. Full details of how to use it are given, and a circuit diagram. Supplied complete with probes, leads and conductive jelly. Needs 2 4 1/2 Vatts. Overall size 155x100x100mm. Only £9.95 - worth that for the case and meter alone!

**REED RELAYS**  
 Manufacturers rejects - DIL and other PCB mounting types. SP, DP and 4P - make, break and c/c contacts. Not tested, so may be only partially working or o/c etc; so very low price - pack of 10 assorted £1; 25 £2.00; 100 £7.00.

**TELESCOPIC AERIALS**  
 As used in Sinclair microvision, 9 section 100-610mm. Only 95p.

**IN4148 - BEST PRICE EVER**  
 Supplied in packs of 100, by Toshiba £2 per pack; 3 packs £5.50; 10 packs £15; 25 packs £32; 100 packs £115.

**2N3055 SCOOP!!**  
 Made by Texas - full spec devices. 60p each; 10 for £4; 25 for £9; 100 for £34; 250 for £75; 1000 for £265.


**COMPUTER SOFTWARE - EDUCATIONAL, UTILITY, GAMES**  
 We now sell a range of tapes and books for DRAGON 32, SPECTRUM, ZX81, BBC and VIC20. Send s.a.e. for list stating for which computer required, or call in our shop.

**WHOLESALE LIST**  
 We have in stock many millions of components - we supply shops, M/O companies, Schools, Industrial Users etc. Can we supply you, too? Our quantity (100+) prices for new full-spec components is very competitive. Ask for our free bulk-buyers list.

**COMING SOON . . . MORE COMPUTER GAMES PCB's - MICROVISIONS, ALPHIE, AVENGER, INTRUDER, AND STARBRD**

**GREENWELD**  
 443A MILLBROOK ROAD, SOUTHAMPTON SO1 0HX  
 All prices include VAT - just add 50p post. Tel 772501

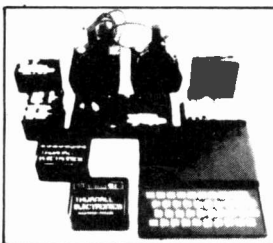**ZX81 OWNERS SPECIALISED PRODUCTS MODULAR EASY TO USE FOR HOME/INDUSTRY & EDUCATION**



**TE10 INPUT/OUTPUT PORT** - Easy to use. Fits between ZX & RAM PACK/PRINTER (if required). No skill required to connect. Can be used for such things as:- motor control; sound/music generators, connection to printers/floppy discs/light pens/other computers, temperature monitoring, square wave generating, control of rotating aerials, even train sets etc. Port has 16 programmable I/O lines and may be used without any electronics knowledge to connect other add-ons. Motherboard required ONLY when two or more add-ons are used at any one time.  
**FULLY ASSEMBLED KIT (WITHOUT CASE)** £17.95  
**TE12 4 CHANNEL RELAY BOX** - To suit Port Contact rating: - 240V AC/1.5A - 24V DC or 110V AC/3A. Up to 4 units i.e. 16 relays can be operated £14.95  
**TE15 8 WAY TRANSISTOR DRIVER** - £3.95  
**TE17 8 WAY SWITCH UNIT (EDUCATIONAL)** - £12.95  
**TE18 8 WAY INDICATOR UNIT (EDUCATIONAL)** - £12.95  
**TE20 JOYSTICK & FREE GAME** - (2 Joysticks may be connected via Motherboards.) £12.95  
**TE30 MOTHERBOARD** - Allows multiples combinations of add-ons - up to 16 I/O line may be used - £15.95  
**TE40 8 CHANNEL analogue to digital unit** £24.95  
**TE126 POWER SUPPLY** - 6/7.5/9V DC at 300 mA - Required for use with add-ons TE12/15 & 18 £4.95  
 23 + 23 WAY ZX Edge Con £2.85. Contact cleaner £2.30.  
 16 WAY SINGLE SIDED EDGE CON £1.95. EXTENDED PIO NOTES £1.  
 PRICES INCLUDE VAT

Receipts always provided: - Delivery normally ex-stock. ADD 50p towards p&p on all orders under £20.00, with the exception of accessories, e. g. Edge on. Full instructions and examples with all products.  
 SEND S.A.E. FOR CATALOGUE. TELEPHONE ORDERS ACCEPTED.

**THURNALL (ELECTRONICS) ENG.**  
 DEPT PCT. 95 LIVERPOOL ROAD,  
 CADISHEAD, MANCHESTER M30 5BG  
 TEL. 061-775 4461 (24 hour)




hi! performance hi! competitive hi!

hi! reliability hi! service hi! performance hi! competitive hi!
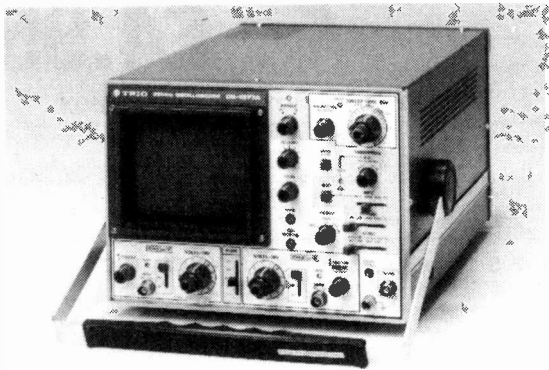
# OSCILLOSCOPES

with  
**PERFORMANCE,  
QUALITY & RELIABILITY**  
at the  
**RIGHT PRICE**



- CS 1577A - 35 MHz - Dual Trace - 2 mV/div
- CS 1566A - 20 MHz - Dual Trace - 5 mV/div
- CS 1560All - 15 MHz - Dual Trace - 10 mV/div
- CS 1562A - 10 MHz - Dual Trace - 10 mV/div

### Features include

- Large Bright Rectangular CRT - Graticule Illumination
- Sweep Times from 0.1  $\mu$ s/div plus  $\times 5$  MAG
- Auto Trigger - Single Sweep - Hold Off - Delay Line
- Excellent Video Sync - Line and Frame
- Single, Dual ADD, SUB, ALT, CHOP and X-Y modes
- TTL Intensity Mod - UNCAL. LED indicators
- Front panel control of Trace Rotation, Astig and DC Balance of Vert Amps
- FREE 2 YEAR Guarantee (inc pick up and return)
- Prices from just over £200

Also AVAILABLE a range of more than 20 Oscilloscopes from 1 to 100 MHz Real Time, Digital Storage, Battery Portable, X-Y and Programmable - DMMs - Frequency Meters - Electronic Voltmeters - Power and DIP meters - Variable Power Supplies - Noise meters - Signal Sources, AF, RF, Function, Sweep, TV Pattern and Stereo - Wow and Flutter etc etc. Ask for FREE Data and Prices.

House of Instruments  
Clifton Chambers, 62 High Street  
Saffron Walden, Essex CB10 1EE  
Tel: (0799) 24922 Telex: 818750



DEPT ETI

hi! competitive hi!



House of Instruments Ltd.

hi! reliability hi! service hi! performance hi! competitive hi!

★ ★ OPEN ALL HOURS ★ ★

The new **EMOS ELECTRONIC COMPONENT WAREHOUSE** is now open Monday to Saturday 9 a.m. to 4 p.m. You will easily find us opposite the John O'Gaunt Hotel on the A45. Even more Fantastic bargains to be found.

### LARGE ELECTROLYTICS:

- \* Computer Grade.
- \* Made by Sprague or General Electric.
- \* Following values available:
- 185,000 @ 15V
- 300,000 @ 7V
- 120,000 @ 15V
- 100,000 @ 30V
- 71,000 @ 40V
- 60,000 @ 40V
- 9,000 @ 50V

- \* Ideal for power supplies.
- \* Prices - fantastic value at only £3.50 each.
- \* Postage and packing: 1 or 2 capacitors - £1.00 3 or more - £1.50

CMOS	4019	71p	4038	89p	4066	39p	4096	83p	4528	47p	
4000	19p	4021	37p	4041	38p	4068	12p	4502	59p	4538	80p
4001	8p	4022	36p	4042	54p	4070	18p	4503	59p	4543	39p
4002	15p	4023	15p	4043	61p	4071	16p	4507	37p	4558	48p
4006	35p	4024	52p	4044	33p	4072	18p	4508	37p	4556	48p
4008	28p	4025	18p	4045	139p	4073	18p	4510	83p	4566	59p
4009	48p	4027	17p	4047	23p	4078	72p	4512	83p	4566	76p
4010	48p	4028	89p	4048	35p	4079	18p	4511	39p	4564	56p
4011	5p	4029	39p	4049	33p	4078	12p	4515	172p		
4012	13p	4030	12p	4051	41p	4081	12p	4516	89p		
4013	23p	4031	89p	4052	46p	4082	18p	4518	89p		
4014	87p	4032	95p	4053	48p	4086	59p	4519	25p		
4015	35p	4033	139p	4054	109p	4088	172p	4520	89p		
4016	34p	4034	125p	4055	113p	4083	18p	4521	89p		
4017	59p	4035	48p	4056	117p	4084	139p	4526	56p		
4018	81p	4036	239p	4083	39p	4095	93p	4527	89p		

### 25W-D Connectors - Male & Female - Solder Lug

£1.40

8255 P.I.A. £1.90

2N3055 £0.35

Regulators

7805 - 5V @ 1A £0.40

7905 - 5V @ 1A £0.55

CV 7644 (military BC107) Only £0.09

Fuseholders - 20mm - Panel £0.40

### BENCH POWER SUPPLY

See constitutional article in February '82 "Practical Electronics"

Available in kit form or built up.

Prices (inc VAT p+p):  
Kit £44.00  
Built £72.00

BC1088 10p	BC149 7p	BC171B 13p	BC182P 10p	BC212B 9p	BC302 40p	BC350A 17p	BC558A 14p
BC114 15p	BC154 23p	BC173 10p	BC183L 9p	BC212L 9p	BC307A 12p	BC351B 22p	BC612L 17p
BC115 17p	BC157 10p	BC173B 14p	BC205B 25p	BC213L 9p	BC308 13p	BC371A 20p	BC714L 30p
BC125B 33p	BC159 12p	BC178 13p	BC205 25p	BC237 12p	BC317 13p	BC446 27p	
BC137 35p	BC170C 16p	BC178B 20p	BC206 25p	BC238A 13p	BC320 22p	BC547 11p	
BC145 22p	BC171 10p	BC179 20p	BC207B 28p	BC239 13p	BC327 16p	BC556B 13p	
BC147 10p		BC182L 9p	BC212L 9p	BC300 42p	BC337 13p		

Dept 4E, High March, Daventry, Northants NN11 4HQ  
Tel: 03272 5523 Telex: 311245 GRENEL G.

Please add 50p per order post and packing - except where higher is indicated plus 15% VAT on total. No VAT on overseas orders - postage at cost cheques and P.O. payable to EMOS Ltd. Allow up to 14 days for delivery. Send large SAE for comprehensive catalogue.




## FOR HI-FI & ELECTRONICS ENTHUSIASTS!

We are the specialists of electronic kits. A catalogue with complete range of products including pre-amp modules, power amp modules, pre and power amplifier modules, complete kits of amplifiers, equalizers, reverbation amplifiers (with cases), alarm clocks, appliance timers, CB amplifiers, test equipment, control (electronic touch switch, sound activated switch, light activated switch, infra-red remote control), music generators, battery fluorescent light and high quality black anodised amplifier cases . . . etc. with illustrative pictures now available at the cost of 60p including P + P, together with a 10% discount voucher for your first order.

### EQUALIZER & REVERBERATION AMPLIFIER

Equaliser Built £73.50

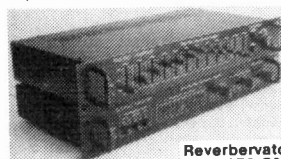

Reverbator Built £79.50


All prices include VAT

### HI-FI AMPLIFIER MODULES



- TA-323A 30W + 30W stereo amplifier £18.95 Kit £23.95 Ass.
- TA-280 60W + 60W stereo amplifier £27.50 Kit £32.50 Ass.
- TA-920 70W + 70W stereo amplifier £35.50 Kit £41.50 Ass.

### CONTROL MODULES

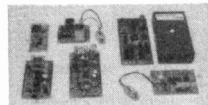

- TY-7 Electronic touch switch £2.90 Kit £3.70 Ass.
- TY-11 Light activated switch £2.20 Kit £2.70 Ass.
- TY-18 Sound activated switch (Clap-switch) £4.50 Kit £5.20 Ass.
- TY-38 Sound activated switch (voice-switch) £5.50 Kit £6.50 Ass.
- TY-41 Infra-red remote control (Receiver and transmitter) £17.20 Kit £18.90 Ass.

### PROFESSIONAL RACK MOUNTING CABINET



Available Soon  
● Wholly made of black anodised aluminium sheets ● Suitable for high quality amplifiers and many other purposes ● Top, bottom and rear cover removable for access ● Different sizes available ● Compatible price ● Front panel is of brushed aluminium finish

To: Concept Electronics Ltd., 51 Tollington Road, London N7 6PB

Mail orders only

Please send me the electronic kits catalogue & the 10% discount voucher for my first order. I enclose 60p in stamps/cheque/postal order. Make cheques payable to Concept Electronics Ltd.

Name .....


Address .....

Block caps please


# STAGE LIGHTING
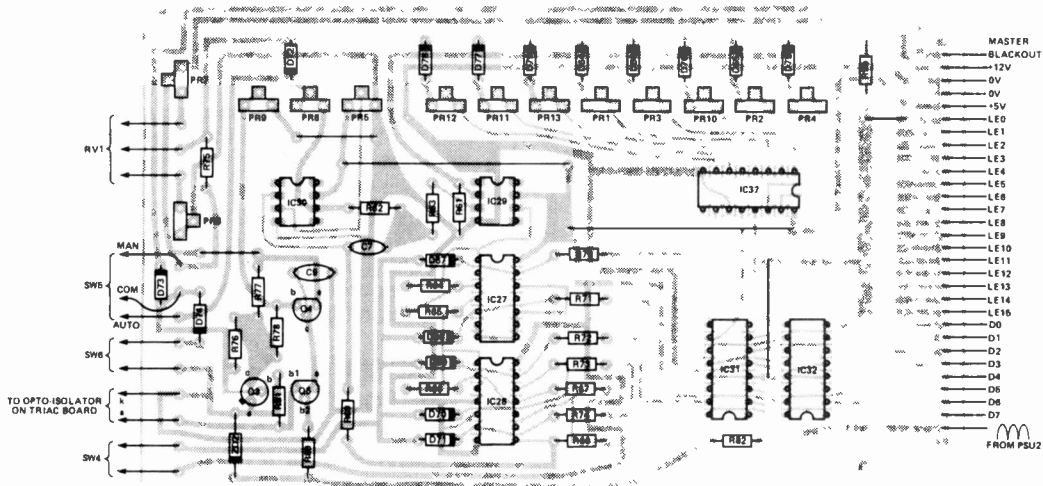
## PART 4

Design by David Colven and Ian Cleverley.



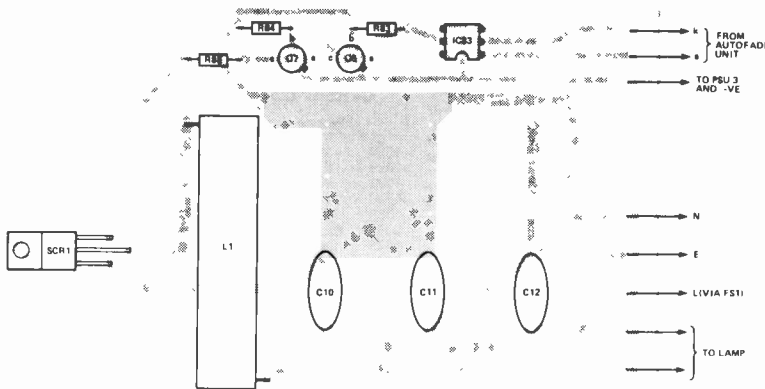\*LINK SELECTS CHANNEL NUMBER  
CHANNEL 0 SHOWN SELECTED



Above is the overlay for one autofade card and left, the overlay for one of the triac boards. No PCBs are given for the power supplies as these consist of little more than strings of capacitors in parallel and methods such as Veroboard are cheap and easy to employ.

### PARTS LIST

Resistors (all 1/4W, 5%)

- R61,84 4k7
- R62,77 470R
- R63,75 100k
- R64,76 10M
- R65 4M7
- R66,78 2M2
- R67 1M2
- R68 560k
- R69 270k
- R70-74 10k
- R79 47k
- R80 330R
- R81,85 100R
- R82 1k0
- R83 120k

Potentiometers

- RV1 10k linear
- PR1-4,10-13 2k2 miniature vertical preset

- PR5 470k miniature vertical preset
- PR6,7 1M0 miniature vertical preset
- PR8 10k miniature vertical preset
- PR9 47k miniature vertical preset

Capacitors

- C7 4u7 16 V tantalum
- C9 100nF polycarbonate or similar
- C10 100nF mains-rated capacitor (eg IS or mixed dielectric)
- C11,12 47nF mains-rated capacitor

Semiconductors

- IC27,28 4016B

- IC29,30 741
- IC31,32 74LS75
- IC33 opto-isolator eg CNY17
- IC37 4028B
- Q3,6,7 BC108
- Q4 BC214L
- Q5 TIS43
- SCR1 TIC246D
- D64-79 1N4148
- ZD2 12 V 400 mW zener

Miscellaneous

- SW4,6 SPST toggle switches
- SW5 SPDT toggle switch
- L1 14 turns of 15 A cable on a 3/8" ferrite rod lamp to suit
- LP1 10 A fuse and fuseholder
- FS1 (see page 87)
- PCBs sheet aluminium for heatsink

CALL IN AND SEE FOR YOURSELF

# AUDIO ELECTRONICS

ALL PRICES INCLUDE VAT

TEST EQUIPMENT CENTRES ALL MODELS ON DISPLAY OPEN SIX DAYS A WEEK

RETAIL • MAIL ORDER • EXPORT • INDUSTRIAL • EDUCATIONAL

## DIGITAL MULTIMETERS (UK C/P Free)



ALL MODELS 3-DIGIT UNLESS STATED



**HAND HELD** #With free carry case  
**KD25C** = 13 range 0.2A DC 2 meg ohm £24.95  
**KD30S** = 16 range 10A DC 2 meg ohm £29.95  
**KD30C** = 26 range 1A AC/DC 20 meg ohm £34.95  
**KD55C** = 28 range 10A AC/DC 20 meg ohm £39.95  
**6010+** = 22 range 10A AC/DC 20 meg ohm £34.40  
**7030+** As 6010 but 0.1% basic £41.30  
**KD615** = 16 range 10A DC 2 meg plus Hfe tester £39.95  
**189M** = 30 range 10A AC/DC 20 meg plus Hfe tester £69.95  
**HAND HELD AUTO RANGE**  
**DM2350** = 21 range 10A AC/DC 20 meg ohm (Miniature) £49.95  
**HD30** = 16 range 0.2A AC/DC 2 meg ohm £41.95  
**HD30/B** As above plus cont. buzzer £44.50  
**HD31** = 22 range 10A AC/DC 2 meg ohms plus cont. buzzer £58.95  
 +Optional carry case £2.95

**BENCH MODELS**  
**TM353+** = 27 range LCD 2A AC/DC £86.25  
**TM355+** = 29 range LED 10A AC/DC £86.25  
**TM351+** = 29 range LCD 10A AC/DC £113.85  
**2001** = 28 range LCD 10A AC/DC plus 5 range Cap. Meter with case £108.00  
**TM451** = 4% digit LCD every facility (0.02%) £171.00  
**1503a** = 4% digit LCD every facility (0.05%) £171.00  
**1503Ha** = 0.03% basic version of above £189.00  
 +Optional carry case £6.84

ALWAYS BARGAINS IN EQUIPMENT FOR CALLERS

## FREQUENCY COUNTERS



**PFM200A** = 200 MHz hand held pocket 8 digit LED £67.50  
**811DA** = 8 digit LED bench 2 ranges 100 MHz £77.00  
**8610B** = 9 digit LED bench 2 ranges 600 MHz £113.85  
**8000B** = 9 digit LED 3 ranges 1 GHz £178.00  
**TF400** = 8 digit LCD 40 MHz £126.50  
**TF200** = 8 digit LCD 200 MHz £166.75  
 #Optional carry case £6.84  
**Prescalers** - Extended range of most counters  
**TP600** = 600 MHz £43.00  
**TP1000** = 1 GHz £74.00

## SIGNAL GENERATORS (220/240V AC)



**FUNCTION** : All sine/square/triangle/TTL etc  
**TG100** = 1 Hz - 100 KHz £90.00  
**TG102** = 0.2 Hz - 2 MHz £166.75  
**PULSE**  
**TG105** = Various facilities 5 Hz - 5 MHz £97.75  
**AU010** = Multiband Sine/Square  
**LAG27** = 10 Hz to 1 MHz £90.85  
**AG202A** = 20 Hz to 200 KHz (List £94.50) £83.50  
**RF**  
**SG402** = 100 KHz to 30 MHz (Last few) £59.95  
**LSG17** = 100 KHz to 150 MHz £79.35

## ELECTRONIC INSULATION TESTER

**YF 501** = 500 V/0-100m with carry case £63.00

## MULTIMETERS (UK C/P 65p)

**C7081** = 50K/V 21 ranges. Range doubler 10A DC. SPECIAL PRICE £15.95  
**ETC5000/5001** = 21 ranges. 50K/V. Range doubler. 10A DC. £16.50  
**TMK500** = 23 ranges 30K/V. 12A DC plus cont. buzzer. £23.95  
**NH56R** = 20K/V. 22 range pocket £10.95  
**EU102** = 14 range 2K/V pocket £5.95  
**830A** = 26 range 30K/V. 10A AC/DC overload protection, etc. £23.95  
**360TR** = 23 range 100K/V. Large scale 10A AC/DC plus Hfe. £36.95  
**AT1020** = 18 range 20K/V. Deluxe plus Hfe tester £17.50  
**ST303TR** = 21 range 20K/V plus Hfe tester £16.95  
**YN 360TR** = 19 range 20K/V plus Hfe tester £13.95

## AUDIO • RF • FUNCTION • PULSE OSCILLOSCOPES



Full specification any model on request. SAE by post.  
**'HM' Series HAMEG: 'SC' THANDAR: 'CS' Series TRID: '3' Series CROTECH**  
**SINGLE TRACE**  
**3030** = 15 MHz 5mV. 95mm tube plus component tester C/P £3.00 £177.10  
**SC110A** = Miniature 10 MHz battery portable Post free £171.00  
**HM103** = 15 MHz 2mV. 6 x 7 display plus component tester C/P £3.00 £181.70  
 #Optional carry case £6.84 AC adaptor £6.69 Nicads £12.50  
**DUAL TRACE (UK C/P £4.00)**  
**HM203/4** = Dual 20 MHz plus component tester £303.60  
**CS1562A** = Dual 10 MHz (List £321.00) £268.50  
**3131** = Dual 15 MHz + component tester £276.00  
**CS1566A** = Dual 20 MHz. All facilities (List £401.35) £349.50  
**HM204** = Dual 20 MHz plus component tester sweep delay. £419.75  
**CS1820** = Dual 20 MHz with extra facilities (List £508.30) £485.00

## VARIABLE POWER SUPPLIES (UK C/P £1.00)

**PP241** = 0/12/24V. 0/1A £35.00  
**PP243** = 3 amp version £59.95  
**PS 1307S** = 8/15V 7 amp twin meter £24.95

## DIGITAL THERMOMETER

**TM301** = LCD -50°C to +75°C with thermocouple £68.43

## AC CLAMP METER

**ST300** = 0/300A. D/600 VAC. 0/1 Kohm 9 ranges With carry case (UK C/P 65p) £28.50

## LOGIC PROBES

**LP10** = 10 MHz £28.50  
**LPD076** = 50 MHz with carry case and accessories £71.30

## OPTIONAL PROBE KITS

**X1** £7.95 **X10** £9.45  
**X1-X10** £10.50 **X100** £16.95

## HIGH VOLTAGE METER

Direct reading 0/4g KV. 20K/Volt. (UK C/P 65p) £23.00

## DIGITAL CAPACITANCE METER

0.1 pF to 2000 mfd LCD 8 ranges **DMG013** £52.75 (Carry case £2.95)

## TRANSISTOR TESTER


Direct reading PNP: NPN, etc. **TC1** (UK C/P 65p) £21.95

FREE CATALOGUE! SEND LARGE SAE (UK 20p) ALL PRICES INCLUDE VAT

## AUDIO ELECTRONICS

301 EDGWARE ROAD, LONDON W2 1BN, TEL: 01-724 3564  
 ALSO AT HENRY'S RADII, 404/406 EDGWARE ROAD, LONDON W2, TEL: 01-723 1008

# SPEAKER BUILDERS!

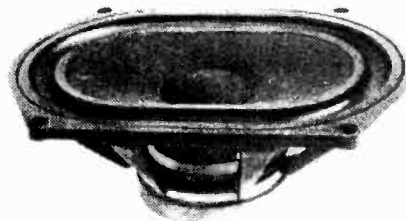

The IMF Electronics 128/20 is a 'new technology' bass driver of massive construction yet occupying the same baffle cutout as the widely-used KEF B139. By further development of the rigid piston concept, including the adoption of fibreglass and styrene cone materials, IMF Electronics' engineers have created a bass driver of advanced performance offering high power handling, low distortion, fast behaviour on transients and a free air resonance typically only 20Hz.

Information on the 128/20 and other fine drivers by IMF Electronics appears in our 1983 catalogue together with practical construction data including active operation. We would appreciate 4 x 16p stamps please (3 dollars overseas). Bona fide dealer enquiries welcome.

## BADGER SOUND SERVICES LTD

46 WOOD STREET, LYTHAM ST. ANNES, LANCS. FY8 4QG  
 Telephone: 0253 729247 (closed Mondays)



**C.M.O.S.**  
 4000 10p  
 4001 10p  
 4002 10p  
 4006 40p  
 4007 12p  
 4008 30p  
 4009 22p  
 4010 22p  
 4011 10p  
 4012 10p  
 4013 18p  
 4014 40p  
 4015 35p  
 4016 18p  
 4017 30p  
 4018 40p  
 4019 22p  
 4020 40p  
 4021 35p  
 4022 35p  
 4023 12p  
 4024 30p  
 4025 12p

**Rocar Electronics**  
 53 Edgeworth, Heron Garden, Yate, Avon  
**MAIL ORDER ONLY**  
**CHEAPEST COMPONENTS PRICES!**  
 Please add 50p P&P and 15% VAT

**SCRS**  
 C106D 40p  
 C116D 60p  
 C126D 65p

**Triacs**  
 TIC 206D 50p  
 TIC 225D 60p  
 TIC 226D 80p  
 TIC 236D 90p  
 TIC 246D £1.50

**Voltage Regulators**  
 7805 5V 1 amp T0220 30p  
 7812 12V 1 amp T0220 30p  
 7815 15V 1 amp T0220 30p

**I.C. Sockets**  
 8 pin - 6p 18 pin - 10p 24 pin - 15p  
 14 pin - 7p 20 pin - 12p 28 pin - 20p  
 16 pin - 7p 40 pin - 20p

**L.E.D.s**  
 3mm 5mm  
 Red 8p 8p  
 Yellow 8p 8p  
 Green 8p 8p

**4027 18p**  
**4048 35p**  
**4049 20p**  
**4050 20p**  
**4051 40p**  
**4052 45p**  
**4060 40p**  
**4066 20p**  
**4068 12p**  
**4069 12p**  
**4070 12p**  
**4071 12p**  
**4072 12p**  
**4073 12p**  
**4075 12p**  
**4076 40p**  
**4077 12p**  
**4078 12p**

All devices full spec Brand new and guaranteed

**VARIABLE VOLTAGE POWER SUPPLIES**  
 1 - 30v 1.5A £38.75 0 - 30v 1.5A £39.99  
 1 - 30v 3A £42.99 0 - 30v 3A £44.50  
 1 - 30v 5A £45.75 0 - 30v 5A £47.80  
 1 - 30v 10A £56.99 0 - 30v 10A £58.99

**MULTIRAIL POWER SUPPLIES FOR MICROS ETC.**  
 5v 5A, - 5v 1A, 12v 1A, 12 1A, 24v 1A £34.50  
 15v HAS CROWBAR OVERVOLTAGE PROTECTION!

**CONSTANT VOLTAGE/CONSTANT CURRENT SUPPLY**  
 1 - 32V/100mA - 5A £56.90

**OTHER SUPPLIES FOR MICROS**  
 5v 3A £25.99 5v 5A £28.99 5v 10A £35.99  
 12v 1A £12.45 12v 3A £27.95  
 (ALL THE ABOVE HAVE CROWBAR OVER VOLTAGE PROTECTION!)

**HIGH EFFICIENCY SWITCHING POWER SUPPLY**  
 1 - 15v 3A £27.99 1 - 15v 5A £34.99  
 2 - 15v 3A £29.99 2 - 15v 5A £35.99  
 SWITCHMODE P.S.U. 5v 5A £35.75

**C.B. RADIO E.T.C. POWER SUPPLIES**  
 12v/13.8v 3A £19.99 12v/13.8v 5A £25.99  
 12v/13.8v 10A £34.99  
 (ALL WITH CROWBAR OVERVOLTAGE PROTECTION!)

**NICAD CONSTANT CURRENT CHARGER FOR ALL DOMESTIC BATTERIES** £18.99

S.A.E. FOR LISTS

ALL POWER SUPPLIES ARE FULLY STABILISED AND OVERLOAD PROTECTED. ALL PRICES ARE INCLUSIVE AND INCLUDE CARRIAGE

**EDWARDS ELECTRIC**  
 UNIT 3, MILL LANE, CHURCH STREET, BRIDGWATER, SOMERSET TA6 5AT

# electronics today international BOOK SERVICE

How to order: indicate the books required by ticking the boxes and send this page, together with your payment, to ETI Book Service, Argus Specialist Publications Ltd, 145 Charing Cross Road, London WC20EE. Make cheques payable to ETI Book Service. Payment in sterling only please. Prices include postage and packing. Prices may be subject to change without notice.

## BEGINNERS GUIDES

- Beginner's Guide to Basic Programming Stephenson £4.95
- Beginner's Guide to Digital Electronics £4.95
- Beginner's Guide to Electronics £4.95
- Beginner's Guide to Integrated Circuits £4.95
- Beginner's Guide to Computers £4.95
- Beginner's Guide to Microprocessors £4.95

## COOKBOOKS

- Master IC Cookbook Hallmark £8.65
- Microprocessor Cookbook M. Hordeski £6.60
- IC Op Amp Cookbook Jung £13.15
- PLL Synthesiser Cookbook H. Kinley £6.60
- Active Filter Cookbook Lancaster £12.00
- TV Typewriter Cookbook Lancaster £9.95
- CMOS Cookbook Lancaster £10.85
- TTL Cookbook Lancaster £10.00
- Micro Cookbook Vol. 1 Lancaster £14.00
- BASIC Cookbook K. Tracton £5.20
- MC6809 Cookbook C. Warren £5.95

## ELECTRONICS

- Principles of Transistor Circuits Amos £8.50
- Design of Active Filters with experiments Berfin £10.40
- 49 Easy to Build Electronic Projects Brown £5.20
- Electronic Devices & Circuit Theory Boylestad £11.95
- How to build Electronic Kits Capel £3.55
- How to Design and build electronic instrumentation Carr £7.95
- Introduction to Microcomputers Daglecs £7.20
- Electronic Components and Systems Dennis £15.00
- Principles of Electronic Instrumentation De Sa £11.40
- Giant Handbook of Computer Software £11.00
- Giant Handbook of Electronic Circuits £14.75
- Giant Handbook of Electronic Projects £9.95
- Electronic Logic Circuits Gibson £5.55
- Analysis and Design of Analogue Integrated Circuits Gray £26.95
- Basic Electronics Grob £10.50
- Lasers - The Light Fantastic Hallmark £6.60
- Introduction to Digital Electronics & Logic Joynson £5.25
- Electronic Testing and Fault Diagnosis Loveday £6.60
- Electronic Fault Diagnosis Loveday £5.75
- Essential Electronics A-Z Guide Loveday £7.20
- Microelectronics Digital & Analogue circuits and systems Millman £11.80
- 103 Projects for Electronics Experimenters Minis £7.25
- VLSI System Design Muroga £30.00
- Power FETs and their application Oxner £23.00
- Practical Solid State Circuit Design Olesky £8.40
- Master Handbook of IC Circuits Powers £10.95
- Electronic Drafting and Design Raskhodoff £21.85
- VOM - VTVM Handbook Risse £7.25
- Video and Digital Electronic Displays Sherr £25.40
- Understanding Electronic Components Sinclair £7.50
- Electronic Fault Diagnosis Sinclair £4.50
- Physics of Semiconductor Devices Sze £14.50
- Digital Circuits and Microprocessors Taub £32.00
- Active Filter Handbook £6.50
- Designing with TTL Integrated Circuits Texas £14.00
- Transistor Circuit Design Texas £14.00
- Digital Systems: Principles and Applications Tocci £11.85
- Master Handbook of Telephones Traister £8.65
- How to build Metal/Treasure Locators Traister £5.20
- 99 Fun to Make Electronic Projects Tymony £7.25
- 33 Electronic Music Projects you can build Winston £5.95

## COMPUTERS & MICROCOMPUTERS

- BASIC Computer Games Ahl £6.35
- From BASIC to PASCAL Anderson £7.95
- Mastering Machine Code on your ZX81 T. Baker £6.95
- UNIX - The Book Banaham £7.80
- Z80 Microcomputer Handbook Barden £10.00
- Microcomputer Maths Barden £10.75
- Digital Computer Fundamentals Barter £9.20
- Viscalc Book. APPLE Edition Bell £14.50
- Viscalc Book. ATARI Edition Bell £14.50
- Introduction to Microprocessors Brunner £22.00
- Programming your APPLE II Computer Bryan £7.95
- Microprocessor Interfacing Carr £6.60
- Microcomputer Interfacing Handbook A/D & D/A Carr £8.10
- Musical Applications of Microprocessors Chamberlain £25.50
- 30 Computer Programs for the Home Owner in BASIC D. Chance £7.95
- Microcomputers Dirkson £7.95
- APPLE Personal Computer for Beginners Dunn £8.50
- Microcomputers/Microcomputers - An Intro Gioone £10.90
- Troubleshooting Microprocessors and Digital Logic Goodman £7.95

- Getting Acquainted with your VIC 20 Hartnell £8.50
- Getting Acquainted with your ZX81 Hartnell £5.95
- Let your BBC Micro Teach you to program Hartnell £7.90
- Programming your ZX Spectrum Hartnell £8.50
- The ZX Spectrum Explored Hartnell £6.95
- How to Design, Build and Program your own working Computer System Haviland £7.95
- BASIC Principles and Practice of Microprocessors Heffer £7.15
- Hints and Tips for the ZX81 Hewson £5.25
- What to do when you get your hand on a Microcomputer Holtzman £8.65
- 34 More Tested Ready to Run Game Programs in BASIC Horn £6.60
- Microcomputer Builders' Bible Johnson £10.75
- Digital Circuits and Microcomputers Johnson £13.00
- PASCAL for Students Kemp £7.20
- The C - Programming Language KERNIGHAN £17.20
- COBOL Jackson £7.95
- The ZX81 Companion Maunder £9.50
- Guide to good Programming Practice Meek £5.70
- Principles of Interactive Computer Graphics Newman £12.95
- Theory and Practice of Microprocessors Nichols £11.35
- Exploring the World of the Personal Computer Nilles £11.35
- Microprocessor Circuits Vol. 1. Fundamentals and Microcontrollers Noll £8.90
- Beginner's Guide to Microprocessors Parr £5.10
- Microcomputer Based Design Peatman £10.50
- Digital Hardware Design Peatman £9.10
- BBC Micro Revealed Ruston £9.45
- Handbook of Advanced Robotics Safford £12.15
- 1001 Things to do with your own personal computer Sawusch £7.50
- Easy Programming for the ZX Spectrum Stewart £7.15
- Microprocessor Applications Handbook Stout £34.40
- Handbook of Microprocessor Design and Applications Stout £37.60
- Programming the PET/CBM West £17.80
- An Introduction to Microcomputer Technology Williamson £6.20
- Computer Peripherals that you can build Wolfe £10.50
- Microprocessors and Microcomputers for Engineering Students and Technicians Wooland £6.60

## REFERENCE BOOKS

- Electronic Engineers' Handbook Fink £56.45
- Electronic Designers' Handbook Giacometto £59.55
- Illustrated Dictionary of Microcomputer Technology Hordeski £7.25
- Handbook for Electronic Engineering Technicians Kauffman £27.50
- Handbook of Electronic Calculators Kauffman £34.40
- Modern Electronic Circuit Reference Manual Marcus £40.70
- International Transistor Selector Towers £10.70
- International Microprocessor Selector Towers £16.00
- International Digital IC Selector Towers £10.95
- International Op Amp Linear IC Selector Towers £8.50
- Illustrated Dictionary of Electronics Turner £12.95

## VIDEO

- Servicing Home Video CAssette REcorders Hobbs £11.80
- Complete Handbook of Videocassette Recorders Kybett £7.95
- Theory and Servicing of Videocassette Recorders McGinty £11.95
- Beginner's Guide to Video Mathewson £5.20
- Video Recording: Theory and Practice Robinson £14.40
- Video Handbook Van Wezel £21.90
- Video Techniques White £12.95

Please send me the books indicated. I enclose cheque/postal order for £  
Prices include postage and packing.  
I wish to pay by Access/Barclaycard. Please debit my account.

5	2	2	4																
---	---	---	---	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

4	9	2	9																
---	---	---	---	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Signed .....

Name .....

Address .....

.....


.....



# YORK

New Electronics Store Opening Offers

## DIGITAL MULTIMETER

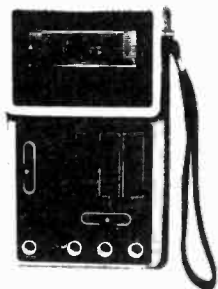

£29.95

## TMK 500



£22.50

C106D — 35p or ten for £3 —  
 LM317T — £1.80 or ten for £15 —  
 TRIAC 400V, 6A — 70p or ten for £6 —  
 60 Way Ribbon — £2.50 per metre.  
 0.1 µF 25V — 100 for £2.50.  
 Photo Board 6 x 4 Single Sided — £1.75  
 Photo Board 6 x 4 Double Sided — £1.99

Prices include VAT. Please add 50p p&p.

## GILLYGATE ELECTRICS

3 Gillygate  
 York YO3 7EA 0904-51012

# ELECTRONIC MUSIC

MODULAR SYNTHESIZER  
 (KIT OR READY BUILT);

MICRO-PROCESSOR CONTROL  
 SYSTEM;

INTEGRATED CIRCUITS FROM  
 CURTIS ELECTROMUSIC  
 SPECIALTIES (CEM SERIES);  
 ETC. ETC.

Write or telephone for latest price list  
 from:—



## DIGISOUND LIMITED

14/16 QUEEN STREET, BLACKPOOL,  
 LANCS FY1 1PQ  
 TEL: 0253 28900

**Branime**  
 TEACHING KITS  
 BUILD YOUR KNOWLEDGE

## TYPE 161B

# DUAL POWER SUPPLY KIT

INCORPORATES A POSITIVE & A NEGATIVE REGULATED SUPPLY


**BOTH ARE ISOLATED & ADJUSTABLE 1.3V TO 16V D.C.**

Interconnect to give 2.6V to 32V or  
 -1.3V/0/+1.3V to -16V/0/+16V

Output current 1A at 16V to 0.35A at 1.3V  
 Ripple is less than 1mV

**£25.99**

inc. P & P and VAT

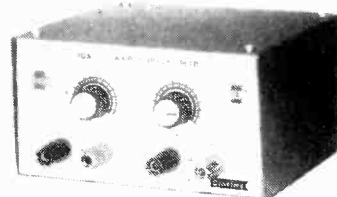

Built & Tested  
 £37.95 inc. P&P and VAT

Comprehensive design details with calculations are included so that the kit is an exercise in power supply design. The kit, which uses quality components, is complete with instructions. Case punched and stove enamelled in attractive blue and grey with a printed front panel to give a professional finish. Excellent for the beginner, the experienced amateur and as a tutorial for schools and colleges.

SEND CHEQUE OR P.O.

ALLOW 21 DAYS FOR DELIVERY

**BRANIME MARKETING LTD** DEPT. ETI  
 BALTHANE IND. EST., BALLASALLA, ISLE OF MAN

# CLEF ELECTRONIC MUSIC

## MICROSYNTH

2½ Octave Music Synthesizer with two Oscillators, two Sub-Occls. Switched Routing and Thumbwheel. A comprehensive instrument offering the full range of Synth. Music & effects.  
 FULL KIT £129 Also available in 3 parts.



## BAND-BOX PROGRAMMABLE BACKING TRIO

**THREE PIECE BACKING BAND**  
 Generates the sounds of three instrumentalists to back Soloists

**DRUMS + BASS + KEYBOARDS**  
 Over 3,000 chord changes (60 scores) on 132 different chords — extendable to 200 scores. Master Rhythm also required.  
 FULL KIT £235 EXTENSION £72

## 88/72 NOTE PIANOS SPECIALISTS SINCE 1972

Using Patented electronic technique to give advanced simulation of Piano Key Inertia.



### COMPONENT KITS

including Keyboard  
 88 NOTE £266  
 72 NOTE £234  
 The above may also be purchased in four parts.

### DOMESTIC KITS

inc. Cabinet, P.A. & Spkr.  
 88 NOTE £442  
 72 NOTE £398

### STAGE MODEL

inc. Cabinet & Stand  
 72 NOTE £383



## MASTER RHYTHM PROGRAMMABLE DRUMS

Twenty-Four Rhythm programmable Drum Machine with twelve instruments. Eight sections are extended to 24/32 measures for two bar programming. Sequence operation and instrument tone adjust.  
 COMPLETE KIT £79

STRING ENSEMBLE £197.50  
 ROTOR-CHORUS £98.00

**SQUARE FRONT KEYBOARDS**  
 88 NOTE £80 49 NOTE £29  
 73 NOTE £50 30 NOTE £19  
 KEYSWITCH ITEMS ALSO AVAILABLE

ALL PRICES INC. VAT, CARR. & TELEPHONE ADVICE  
 S.A.E. for full Specs & MANF. PRICES. VISA-ACGESS

CLEF PRODUCTS (ELECTRONICS) LIMITED (Dept ETI)  
 44A BRAMHALL LANE SOUTH BRAMHALL  
 STOCKPORT CHESHIRE SK7 1AH  
 TEL 061 539 3297

Universal NI-CAD, battery charger. All plastic case with lift up lid. Charge/Test switch. LED indicators at each of the five charging points.


Charges:- PP3 (9V), U12 (1.5V penlite), U11 (1.5V "C"), U2 (1.5V "D"). Power:- 220-240V AC, Dims:- 210 x 100 x 50mm. Knock down price only white stocks last.

Only £6.00  
Order No. MW 398

**Multitester & Transistor Tester**  
DC volts 0-1v-5v-2.5v-10v-50v-250v-1000v ±3%  
AC volts 0-10v-50v-250v-1000v ±3%  
DC current 0-50uA-2.5mA-25mA-0-25A ±3%  
Resistance:  
Minimum 0-2-2-200-200k ohms ±3%  
Midscale 20-200-20k-200k ohms  
Maximum 2k-20k-2m-20m ohms  
As a transistor tester  
Leakage current 0-150uA at Z1k range ±5%  
0-15mA at X10 range  
0-150mA at X1 range

PLEASE ADD 15% VAT & £1 P&P

Only £11.95  
Order No. HT 320



**ENFIELD ELECTRONICS**  
208 BAKER ST., ENFIELD, MIDDX. Tel: 01-366 1873

# THE "INSTANT" PC BOARD



E-Z CIRCUIT... "quick, easy & reliable... the best way to make one or two-of-a-kind PC boards". That's what "Doc" Savage (hobby editor, Radio Electronics magazine) says about E-Z CIRCUIT. Why all the excitement?

Simple. E-Z CIRCUIT's exclusive 1 oz. pressure-sensitive copper tapes & patterns apply directly to the PC board, creating an actual current carrying circuit. Simply apply E-Z CIRCUIT's Copper Mounting Configurations to the board, solder your components into place, and you have a professional, production quality PC board... *instantly*... without artwork, photography, screening or etching.

There's no need to worry about mistakes either. With E-Z CIRCUIT's special two-phase adhesive, you can make corrections, modifications or improvements quickly & easily... without damaging the performance or appearance of your PC board.

For building, prototyping or repairing PC boards instantly. E-Z CIRCUIT truly is the *quick, easy, reliable way!*

Prove it to yourself. send for your **FREE** copy of the E-Z CIRCUIT Copper Products Printed Circuit Technical Manual & Catalog EZ-3001. See why "Doc" Savage & thousands of other users recommend E-Z CIRCUIT for instant PC boards.

Send for your **FREE** E-Z CIRCUIT Printed Circuit Copper Products Technical Manual & Catalog EZ 3001




**Engineering & Electronic Design Services Ltd.**  
Unit 7, Enterprise Centre, Childers Road, Limerick. IRELAND  
Tel: (061) 49366

## OPTICAL FIBRES FOR COMMUNICATIONS AND LIGHTING

- ★ Silica fibre PTFE coated, 25 dB/km 0.05mm<sup>2</sup> active area. Xmits near UV
- ★ Glass fibre urethane coat, 60 dB/km 0.03mm<sup>2</sup> active area. Xmits near IR
- ★ Acrylic fibre, 0.75mm<sup>2</sup> active area 800 dB/km. Xmits visible light only
- ★ Glass Bundle, PVC sheath, 400 dB/km 1.0mm<sup>2</sup> active area, 440 fibres
- ★ Acrylic Bundle, sheathed, 800 dB/km 0.78mm<sup>2</sup> active area, 16 fibres

Type	Length in Metres		
	10	25	50
Silica Fibre	£6.26	£14.68	£27.57
Glass Fibre	£5.20	£12.40	£23.23
Acrylic Fibre	£3.03	£6.90	£13.55
Glass Bundle	£3.80	£8.75	£17.09
Acrylic Bundle	£8.10	£19.35	£37.07

**SAMPLE PACK:** contains six metres of Acrylic fibre plus one metre samples of the other fibres. In the Pack is a booklet that contains circuit diagrams, drawings, and practical tips. Its forty pages give details of fibre theory, manufacture, properties, and many uses. Send £5.45 + 50p P&P

**MARE'S TAIL:** A ferruled bundle of 5000 glass fibres that spread out into a 22" diameter dome shape. For use in a fibre optics lamp. Send £11.50 inclusive.

Quantum Jump Limited  
Dept ET1, 98 Queens Drive, Liverpool L18 1JN

Add 50p postage on orders under £10. No VAT. SAE for details. Mail order only.

## MULTIMETERS

(UK C/P 65p)

RANGE DOUBLER 10A DC1  
Special price.....£15.95

ETC 5000/5001 121 Ranges  
50K/V Range Doubler 10A DC  
.....£16.50

TMK 500 23 Ranges 30K/V 12A  
DC Plus cont. buzzer.....£23.95

NH56R 20K/V 22 Range Pocket  
.....£10.95

360TR 23 Range 100K/V. Large  
scale 10A AC/DC plus Hfe....£36.95

ATI 020 18 Range 20K/V. DeLuxe  
plus Hfe Tester.....£17.50

ST303TR 21 Range 20K/V plus Hfe  
Tester.....£16.95

## SPEAKERS

(Hi-Fi, P.A., Disco, Bass Guitar)

12" 50W .....£14.95

12" 100W .....£19.95

15" 100W .....£29.95

18" 100W .....£39.95

Postage and Packaging £3

**RETAIL • MAIL ORDER  
EXPORT • INDUSTRIAL  
EDUCATIONAL**

Order by Post with cheques, Access/Visa or you can telephone your orders.

ALL PRICES INCLUDE VAT

FREE CATALOGUE SEND LARGE SAE (UK 20p)

**MUSICRAFT 303 EDGWARE RD, LONDON W.2. TEL: 01-402 9729/2898**

## TALK TO THE WHOLE WORLD

Study now for the  
**RADIO AMATEUR'S EXAMINATION**

We have had 40 years successful experience in training men and women for the G.P.O. Transmitting licence.

FREE R.A.E. brochure without obligation from:-  
**British National Radio & Electronics School  
READING, BERKS. RG1 1BR**

Name .....

Address .....

ETI/5/817 BLOCK CAPS PLEASE

# EXPO DRILLS

## KITS TOOLS ACCESSORIES

### TITAN DRILL AND STAND

Engineering in miniature, the most powerful British, 12 Volt D.C. drill made, producing 10,000 R.P.M., 1740 C.M.P. comes complete with tommy bar, allen key, steel chuck + 4 collars, size zero, 1/16, 3/32, 1/8. Specially designed for drilling P.C. Board, mild steel, and many other uses in electronics, other crafts and hobbies.



Titan Drill, complete 4 collars, Cat No 0175  
**£10.28 Plus VAT**

Dual purpose Stand Cat No 0209  
**£12.00 Plus VAT**  
Hundreds of tools and kits to choose from

Transformer Rectifier also available

Also available specially designed Dura Life P.C.B. Drills, very hard and durable, but not brittle like Tungsten

**Price £1.10**





Available from your local stockists

**EXPO** EXPO Prices are approximately 40% cheaper than all other makes. Distributors, Wholesale, Retail and Export enquiries welcome


Many other Expo drills, tools, kits available  
Send for your copy of latest catalogue and price list today

**EXPO (DRILLS) LTD** Clock Tower Works, Brook Lane  
Warsash, Hants SO3 6FH Tel: Locks Heath 83966/7/8

# PCB FOIL PATTERNS

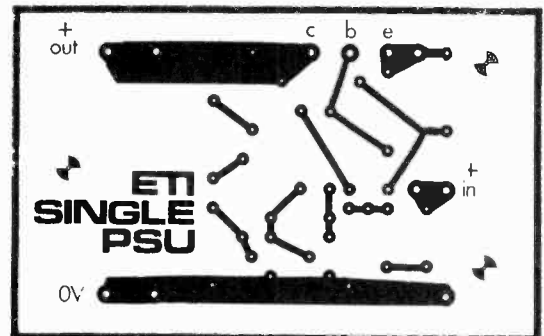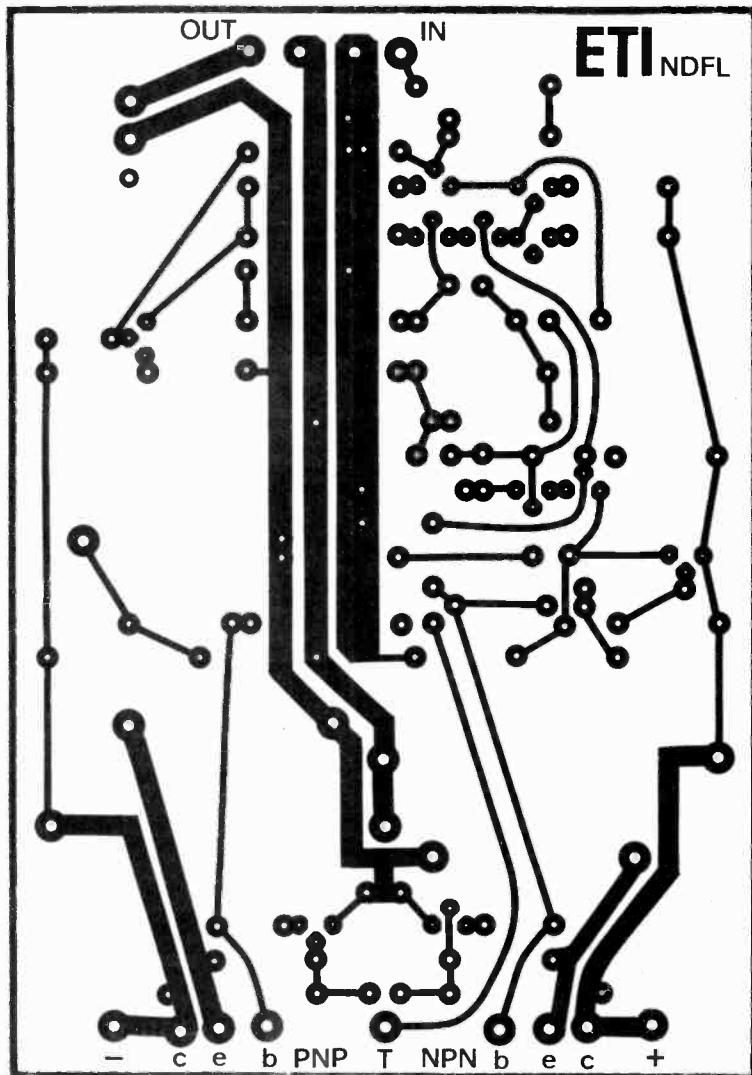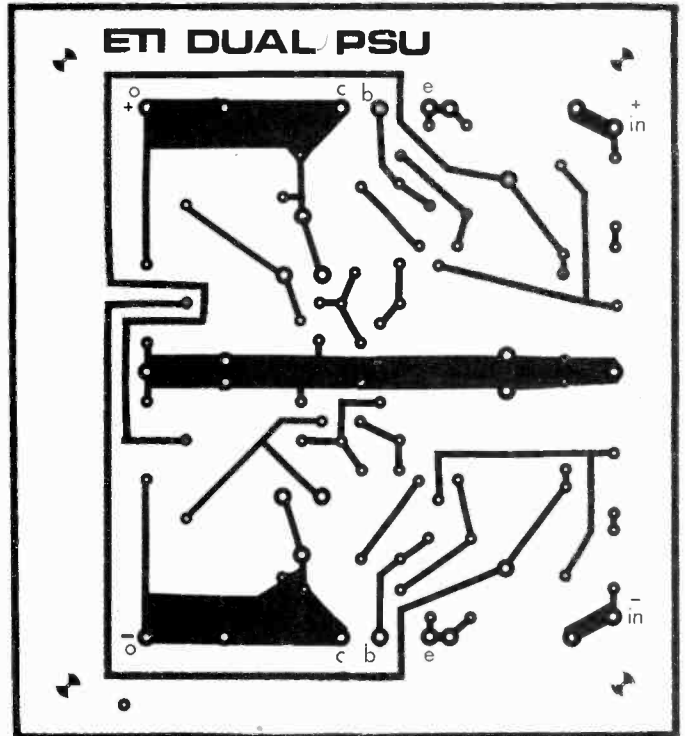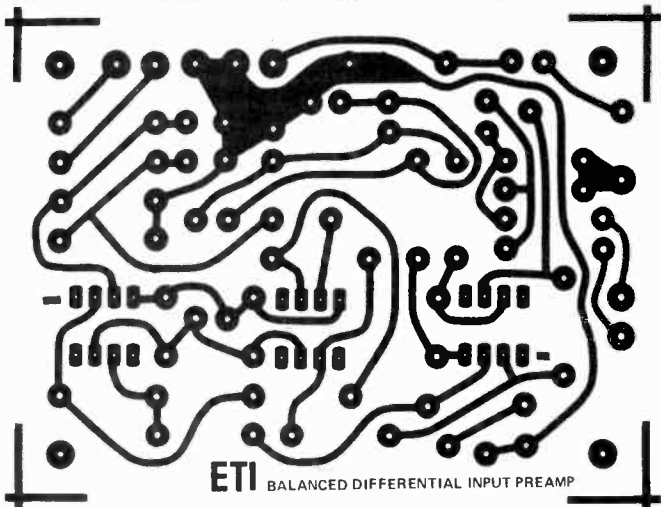

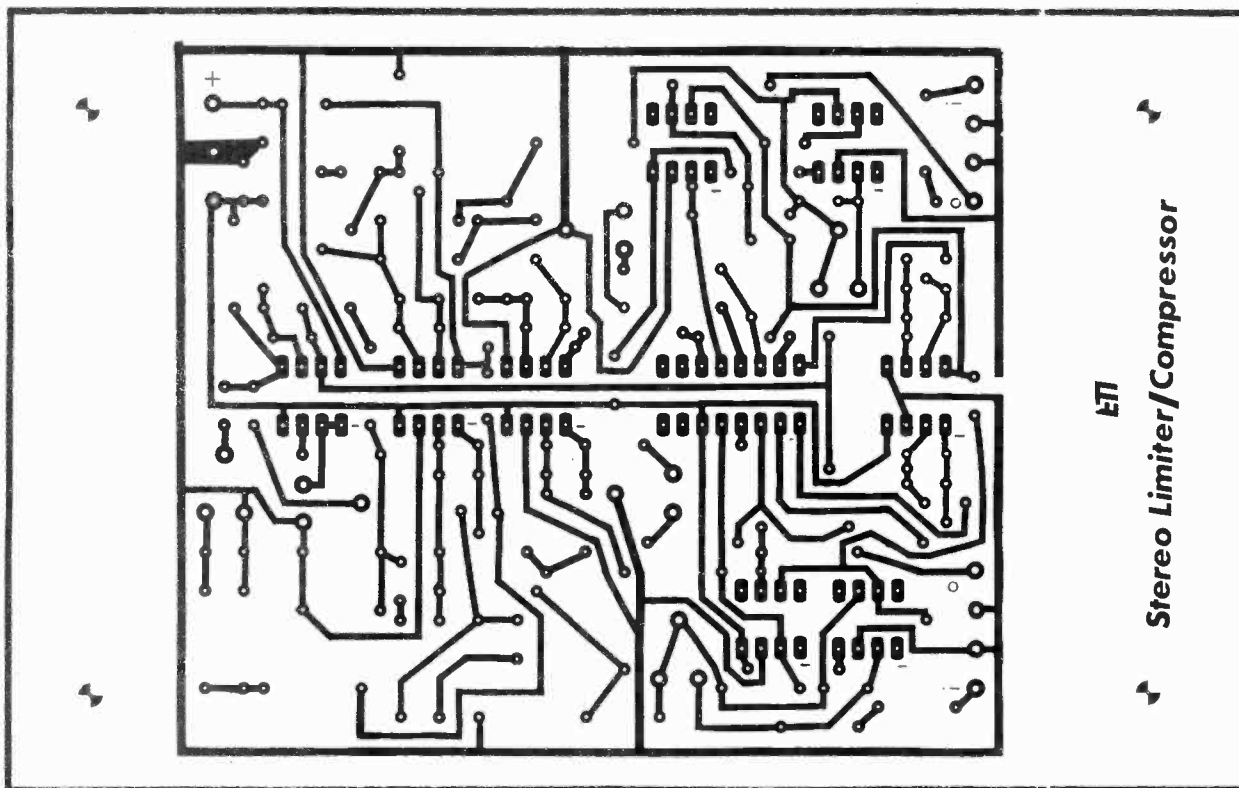Above: the elusive meter scale artwork for last month's Max/Min Thermemeter.



A complete set of foil patterns for the Stage Lighting Unit can be obtained by sending a large stamped addressed envelope to ETI, 145 Charing Cross Road, London WC2H 0EE. Mark your envelope 'FOIL PATTERNS'.

## MASTER ELECTRONICS NOW! The PRACTICAL way!

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to start or further a career in electronics or as a self-employed servicing engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write personally at any time, for advice or help during your work. A Certificate is given at the end of every course.

You will do the following:

- Build a modern oscilloscope
- Recognise and handle current electronic components
- Read, draw and understand circuit diagrams
- Carry out 40 experiments on basic electronic circuits used in modern equipment
- Build and use digital electronic circuits and current solid state 'chips'
- Learn how to test and service every type of electronic device used in industry and commerce today. Servicing of radio, T.V., Hi-Fi and microprocessor/computer equipment.



### New Job? New Career? New Hobby? Get into **Electronics** Now!

**FREE!**  
COLOUR BROCHURE

Please send your brochure without any obligation to

I am interested in:

ETI/5/821

NAME \_\_\_\_\_

COURSE IN ELECTRONICS  
as described above

RADIO AMATEUR LICENCE

MICROPROCESSORS

LOGIC COURSE

OTHER SUBJECTS \_\_\_\_\_

ADDRESS \_\_\_\_\_


BLOCK CAPS PLEASE

POST NOW TO:

**British National Radio & Electronics School** Reading, Berks. RG1 1BR



# MAKE YOUR OWN P.C.B's.

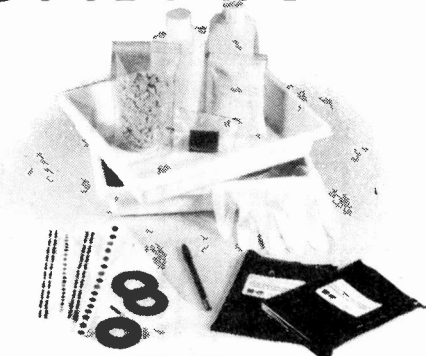

## PHOTO RESIST KIT

Complete kit containing artwork PCB, and all necessary process materials **£24.60**

## UV EXPOSURE UNIT

Perfect results everytime. Kit contains: Lamp, Holder & Shade together with full instructions for DIY Unit which offers PCB, Precision Photo, Label & Panel manufacture **£27.60**

Price inclusive of VAT & carriage. Please allow 21 days for delivery. Cheques, PO's or signed Access orders welcomed.



complete P.C.B. workshop

a division of  
**KELAN ENGINEERING Ltd**  
Hookstone Park  
Harrogate, N. Yorks

HB/PC2

## TECHNICAL TRAINING IN ELECTRONICS, TELEVISION AND AUDIO

IN YOUR OWN HOME - AT YOUR PACE

ICS can provide the technical knowledge that is so essential to your success, knowledge that will enable you to take advantage of the many opportunities open to the trained man. You study in your own home, in your own time and at your own pace and if you are studying for an examination ICS guarantee coaching until you are successful.

### City & Guilds Certificates

Radio Amateurs  
Basic Electronic Engineering (Joint C&G/ICS)

### Certificate Courses

TV and Audio Servicing  
Radio & Amplifier Construction  
Electronic Engineering\* and Maintenance  
Computer Engineering\* and Programming  
Microprocessor Engineering\*  
TV, Radio and Audio Engineering  
Electrical Engineering,\* Installation  
and Contracting \*Quality for IET Associate Membership



Approved by CACC



Member of ABCC

### POST OR PHONE TODAY FOR FREE BOOKLET

Please send me your FREE School of Electronics Prospectus.

Subject of Interest \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_



Post to: Dept G625  
ICS School of Electronics  
160 Stewarts Road,  
London SW8 4UJ



01-622 9911  
(All Hours)

## E.T.I. - MAY 83 ADVERTISERS INDEX

A.D.E. Electronics	73
Ambit International	41
Armon Electronics	61
Audio Electronics	80
Badger Sound Services	80
Bicc Vero	60
Bi-pak	16
BK Electronics	51
Black Star	66
BNRS	75,83
Bradley Marshall	10
Bramine Marketing	82
Circuit Board Components	76
Clef products	82
Comtech	17
Comquip	28
Concept Electronics	78
Cricklewood Electronics	8,9
Crimson Elektrik	61
Crofton Electronics	72
Delta Tech	17
Digisound	82
Display Electronics	42
Edwards Electronics	80
Electronize Design	62
Electrovalue	14
EMOS	78
Enfield Electronics	83
Engineering & Electrical	83
Europe Electronics	67
Expo Drills	83
Gillygate Electronics	82
Greenbank	76
Greenweld	77

G.S.C.	35
Happy Memories	72
House of Instruments	78
ICS	86
ILP	52,53,66
Kelan Engineering	86
LB Electronics	76
L & B Electronics	72
L.E.M. Services	73
Magenta Electronics	73
Maplin	OBC
Marco Trading	76
Mawson Associates	72
Midwich	29
Musicraft	83
Myers Electronics	73
Parndon Electronics	72
Powertran	IFC,IBC
Riscomp	23
Rocar	80
Quantum Jump	83
Rapid Electronics	6
J. W. Rimmer	60
R.T.V.C.	67
Sparkrite	68
Stuarts of Reading	77
Technomatic	30,31
Tempus (Micro Mail)	23
Thurnall Eng	77
T K Electronics	36
Velleman UK	12
Watford Electronics	4,5
Wilmslow	73

# ETI PCB SERVICE

Up until now PCBs were always the hardest component to obtain for a project. Of course you could make your own, but why bother anymore?

Now you can buy your boards straight from the designers — us! As of this issue all (non-copyright) PCBs will be available automatically from the ETI PCB Service. Each board is produced from the same master used to build our prototypes, so you can be sure it's accurate and will be finished to the high standard you would expect from ETI.

In addition to the PCBs for this month's projects, we are making available some of the more popular designs from our recent past. See the list below for details. Please note that **NO OTHER BOARDS ARE AVAILABLE**. If it's not listed, we don't have it!

<b>APRIL 79</b>		<b>JULY 80</b>		<input type="checkbox"/> Ion 'Blinker'	£2.47
<input type="checkbox"/> Guitar Effects Unit	£2.64	<input type="checkbox"/> System A A-MMA-MC	£2.65	<input type="checkbox"/> MOSFET Amp Module	£6.78
<input type="checkbox"/> Click Eliminator	£6.64	<input type="checkbox"/> System A A-PR	£5.17	<input type="checkbox"/> Logic Lock	£3.06
		<input type="checkbox"/> Smart Battery Charger	£1.97	<input type="checkbox"/> Digital PWM	£3.34
<b>JUNE 79</b>				<input type="checkbox"/> Optical Sensor	£1.74
<input type="checkbox"/> Accentuated Beat Metronome	£3.60			<input type="checkbox"/> Stylus Timer	£2.59
<b>FEBRUARY 80</b>		<b>AUGUST 81</b>		<input type="checkbox"/> Oscilloscope (four boards)	£11.60
<input type="checkbox"/> Tuning Fork	£2.64	<input type="checkbox"/> System A Power Amp(A-PA)	£4.77	<b>SEPTEMBER 82</b>	
		<input type="checkbox"/> Flash Sequencer	£3.44	<input type="checkbox"/> Auto Volume Control	£1.84
<b>MARCH 80</b>		<input type="checkbox"/> Hand-clap Synthesiser	£3.97	<input type="checkbox"/> Dual Logic Probe	£1.93
<input type="checkbox"/> Signal Tracer	£2.27	<input type="checkbox"/> Heartbeat Monitor	£1.83		
		<input type="checkbox"/> Watchdog Home Security (two boards)	£5.31	<b>OCTOBER 82</b>	
<b>AUGUST 80</b>				<input type="checkbox"/> Message Panel (one card)	£8.79
<input type="checkbox"/> CMOS Logic Tester	£2.64			<b>NOVEMBER 82</b>	
<input type="checkbox"/> Capacitance Meter	£2.93	<b>SEPTEMBER 81</b>		<input type="checkbox"/> Spectrum Analyst (3 boards)	£14.33
<input type="checkbox"/> Ultrasonic Burglar Alarm	£2.87	<input type="checkbox"/> Mains Audio Link (three boards)	£7.35	<input type="checkbox"/> Pulse generator	£5.29
		<input type="checkbox"/> Laboratory PSU	£4.53	<input type="checkbox"/> Message panel interface	£1.91
<b>OCTOBER 80</b>				<b>DECEMBER 82</b>	
<input type="checkbox"/> Cassette Interface	£2.93	<b>OCTOBER 81</b>		<input type="checkbox"/> ELCB	£2.41
<input type="checkbox"/> Fuzz/Sustain Box	£3.27	<input type="checkbox"/> Enlarger Timer	£3.40	<input type="checkbox"/> Servo Interface (two boards)	£5.87
<b>NOVEMBER 80</b>		<input type="checkbox"/> Sound Bender	£2.65	<input type="checkbox"/> Spectracolumn	£4.82
<input type="checkbox"/> Touch Buzzer	£1.93	<input type="checkbox"/> Thermal Alarm	£2.63	<input type="checkbox"/> Signal Line Tester	£1.25
<input type="checkbox"/> Light Switch	£1.93	<input type="checkbox"/> Micropower Pendulum	£2.21		
<input type="checkbox"/> Metronome	£1.93	<b>NOVEMBER 81</b>		<b>JANUARY 83</b>	
<input type="checkbox"/> 2W Power Amp	£1.93	<input type="checkbox"/> Voice-Over Unit	£3.97	<input type="checkbox"/> ETI/831/1 Fuel Gauge	£3.00
<input type="checkbox"/> RIAA Preamplifier	£1.93	<input type="checkbox"/> Car Alarm	£2.81	<input type="checkbox"/> ETI/831/2 ZX ADC	£2.25
<input type="checkbox"/> Audio Test Oscillator	£3.13	<input type="checkbox"/> Phone Bell Shifter	£2.96	<input type="checkbox"/> ETI/831/3 Programmable PSU	£3.00
<b>DECEMBER 80</b>		<b>DECEMBER 81</b>		<b>MARCH 83</b>	
<input type="checkbox"/> Musical Doorbell	£2.80	<input type="checkbox"/> Alcohometer (two boards)	£5.21	<input type="checkbox"/> ETI/833/1 6502 Sound/DAC	£11.16
<input type="checkbox"/> Bench Amplifier	£2.53	<input type="checkbox"/> Bodywork Checker	£1.75	<input type="checkbox"/> ETI/833/2 Alarm Module	£3.15
<input type="checkbox"/> Four Input Mixer	£2.64	<input type="checkbox"/> Component Tester	£1.40	<input type="checkbox"/> ETI/833/3 ZX81 Graphics	£0.93
<b>JANUARY 81</b>				<input type="checkbox"/> ETI/833/4 Logic Probe	£2.17
<input type="checkbox"/> LED Tacho	£4.13	<b>JANUARY 82</b>		<b>APRIL 83</b>	
<input type="checkbox"/> Multi-Option Siren	£3.20	<input type="checkbox"/> Parking Meter Timer	£2.20	<input type="checkbox"/> Real Time Clock	£7.60
<input type="checkbox"/> Universal Timer	£3.31	<input type="checkbox"/> Infant Guard	£1.56	<input type="checkbox"/> Thermemeter (main board)	£3.99
<b>FEBRUARY 81</b>		<input type="checkbox"/> Guitar Tuner (two boards)	£5.55	<input type="checkbox"/> Thermemeter (sensor)	£0.72
<input type="checkbox"/> Infra-red Alarm (four boards)	£6.64	<b>FEBRUARY 82</b>		<input type="checkbox"/> Stage Lighting (memory)	£11.97
<input type="checkbox"/> Pulse Generator	£3.57	<input type="checkbox"/> Ripple Monitor	£1.92	<input type="checkbox"/> Stage Lighting (display board)	£2.96
<b>MARCH 81</b>		<input type="checkbox"/> Pest Monitor	£1.68		
<input type="checkbox"/> Engineer's Stethoscope	£2.65	<input type="checkbox"/> I Ching Computer (two boards)	£5.15		
<b>APRIL 81</b>		<input type="checkbox"/> Moving-magnet stage	£3.49		
<input type="checkbox"/> Musical Box	£2.64	<input type="checkbox"/> Moving-coil stage	£3.49		
<input type="checkbox"/> Drum Machine (two boards)	£5.60	<b>MAY 82</b>			
<input type="checkbox"/> Guitar Note Expander	£3.20	<input type="checkbox"/> DV Meg	£2.72	<b>MAY 83</b>	
<b>JUNE 81</b>		<input type="checkbox"/> Analogue PWM	£3.06	<input type="checkbox"/> Compressor/Limiter	£5.38
<input type="checkbox"/> Mini-drill Speed Controller	£2.93	<input type="checkbox"/> Slot Car Controller	£4.51	<input type="checkbox"/> Single PSU	£2.75
<input type="checkbox"/> Antenna Extender	£3.20	<input type="checkbox"/> Wattmeter	£4.17	<input type="checkbox"/> Dual PSU	£3.49
<input type="checkbox"/> LED Jewellery: Cross	£1.47	<input type="checkbox"/> Sound Effects Board	£2.25	<input type="checkbox"/> 60 W NDFL Amp	£4.70
<input type="checkbox"/> Spiral (two boards)	£2.64			<input type="checkbox"/> Balanced Input Preamp	£2.81
<input type="checkbox"/> Star (two boards)	£2.65	<b>June 82</b>		<input type="checkbox"/> Stage Lighting (autofade)	£5.38
<input type="checkbox"/> Waa-phase	£1.53	<input type="checkbox"/> Ion Generator (two boards)	£5.53	<input type="checkbox"/> Stage Lighting (triac board)	£4.12

How to order: indicate the boards required by ticking the boxes and send this page, together with your payment, to: ETI PCB Service, Argus Specialist Publications Ltd, 145 Charing Cross Road, London WC2H 0EE. Make cheques payable to ETI PCB Service. Payment in sterling only please. Prices subject to change without notice.

Total for boards £.....  
Add 45p p & p 0.45  
Total enclosed £.....

PLEASE ALLOW  
28 DAYS FOR  
DELIVERY

Signed .....

Name .....

Address .....

# ELECTROMART

## AVON

### ANNLEY ELECTRO

190 Bedminster Down Road  
Bedminster Down, Bristol  
Tel: 0272 632622  
Open: Mon-Sat 9am-6.30 pm Wed 9am-2pm

## BEDFORDSHIRE

### BROADWAY ELECTRONICS

1 The Broadway, Bedford,  
Tel: 0234 213639

Open: 6 days 9-5.30 ½ day Thur.  
lunch 1.30-2.30.  
Specialists in electronic components and  
Acorn computers

## CHESHIRE



41 Winwick St., Warrington  
Tel. 54174  
Open: Mon-Fri 9.30-6  
(closed Tues) Sat 9.30-5  
Components, aerials & burglar alarm  
specialists

## DORSET

**D.J. ELECTRONICS**  
64 Ensbury Park Road,  
Bournemouth.  
Tel: (0202) 515073.

Open: Mon-Sat 9am-6pm.

## LANCASHIRE

### ETESON ELECTRONICS

**E.E.** 15B Lower Green,  
Poulton-le-Fylde, Blackpool  
Tel: (0253) 885107  
Open: 9.30am-12.30, 1.30-5.30 Closed Wed & Sun  
Electronic Component Specialists.

## MERSEYSIDE



WYMCA Building, College St.,  
St. Helens Tel. 50707  
Open: Mon-Fri 9.30-5.30  
(closed Thurs) Sat 9.30-5  
Components, aerials & burglar alarm  
specialists

### MYCA ELECTRONICS

2 VICTORIA PL, SEACOMBE FERRY,  
WALLASEY, L44 6NR.

Tel: 051 638 8647  
Open Mon-Sat 10am-5.30pm  
Mail Order price list 50p refundable

### PROGRESSIVE RADIO

93 Dale Street. Tel 051 236 0982  
47 Whitechapel, Tel 051 236 5489  
Liverpool 2

*THE ELECTRONICS SPECIALISTS'*  
Open: Tues-Sat 9.30-5.30

## W. MIDLANDS

### WAVEBANDS

103 Coventry St., Kidderminster  
Components, computers, car radios,  
C.B.'s, amateur radio  
and all electronic hobby equipment



Open: Mon-Sat 9-6, Sun 10-2

TEL: 0562 2179



### H. G. ELECTRONICS CO

1350 Stratford Rd., Hall Green  
Birmingham. Tel: 021-777 2369

Open: Mon-Sat 9-5.30 (Closed Weds)  
Electrical accessories, plugs, skts, leads,  
Electronic components, computers, audio,  
video, tape, disco, hi-fi . . .

## NORTHAMPTONSHIRE

- \* A new company selling electronic components.
- \* Mail order and walk-round supermarket.
- \* Vast stocks and very competitive prices.

**EMOS**

High March, Daventry. NN11 4WQ.  
Telephone 03272 5523. Telex 311245.  
(Off A45 opposite John O'Gaunt.)

## STAFFORDSHIRE



ELECTRONIC  
SUPPLIES

105 High St.,  
Wolstanton,  
Newcastle

Tel: 0782 636904

Open: Mon-Wed 9-6, Thurs 9-12 & 5-7,  
Fri & Sat 9-9, Sun 11-2

## S. WALES

### STEVE'S ELECTRONIC SUPPLY CO. LTD.


45 Castle Arcade, Cardiff

TEL: 0222 41905

Open: Mon-Sat 9-5.30

For components to computers

## WARWICKSHIRE

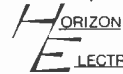

Charlotte St, Rugby. Tel: Rugby 78138

Open 5 Days 10-6 (closed Wed)

Wide range of components and R.S. stocks  
1983 Mail Order Catalogue 75p

## YORKSHIRE



ACE MAILTRONIX LTD.

3A Commercial Street,  
Batley. Tel: (0924) 441129

Open: Mon-Fri 9am-5.30pm. (Sat 1pm)  
Retail and wholesale.

Please include my business details in the next available issue of **ELECTRONICS TODAY INTERNATIONAL**:

BUSINESS NAME: .....

ADDRESS: .....

TEL. NO.: .....

OPENING HOURS: .....

RETAIL  WHOLESALE  MAIL ORDER  (Please tick)

CONTACT: (FOR OFFICE USE ONLY) .....



BARCLAYCARD  
VISA

**CLASSIFIED**

THE PATH TO  
SUCCESSFUL SALES!

01-437 1002  
Ext 213

## ADVERTISEMENT RATES

Semi-Display (min 2 cms)

1-3 insertions £10.00 per cm  
6-11 insertions £9.50 per cm  
12+ insertions £9.00 per cm.  
Lineage 35 p per word (min 15 words)  
Box Nos. £3.50

Closing date 1st Friday in the month preceding publication date.

All advertisements in this section must be prepaid. Advertisements are accepted subject to the terms and conditions printed on the advertisement rate card (available on request)

Send your requirements and cheque/P.O. to:

**E.T.I. CLASSIFIED ADVERTISING,**  
145 CHARING CROSS RD, LONDON  
WC2H 0EE

### COMPONENTS


#### BUMPER BOX OF BITS

WOW! We've got so many components in stock, we can't possibly list them all! — So buy a box. In it you'll find resistors, capacitors, displays, switches, panels with transistors, diodes, IC's etc., coils, pots... and so on. All modern parts — guaranteed at least 1000 items, minimum weight 10lbs. ONLY £8.50 inc.

**ELECTRONICS WORLD**  
1e Dewes Road, Salisbury,  
Wilts. SP2 7SN

NOW OPEN IN NEWCASTLE, Waterloo Street, "Marlborough Electronic Components" for the best in electronic components, test equipments etc. Tel 618-377.

### EQUIPMENT

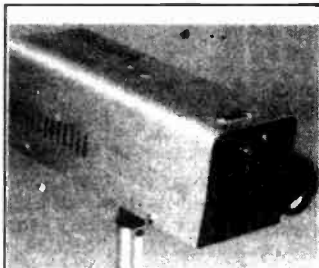

A really compact high performance CCTV camera for only £130.00 plus VAT plus p&p, TOTAL £152.95.  
Size 3" x 3" x 9"  
240v operation  
1v pp output.  
Lens extra

#### CROFTON ELECTRONICS LIMITED

35 GROSVENOR ROAD,  
TWICKENHAM,  
MIDDLESEX TW1 4AD  
Telephone: 01-891 1923/  
01-891 1513  
Telex 295093 CROFTN G

**TELEPHONE MONITOR KIT,** connects between telephone line and your cassette recorder and automatically records all phone usage. Complete kit including case and PCB only £9.95. Dept. ET5 UNITECH (Midlands). FREEPOST, Sutton Coldfield, West Midlands, B74 2BR. (Not British Telecom Approved).

**U.V. LIGHT EXPOSER UNIT** for use in prep. of photo-resist P.C.B's. Attractive wooden construction with exposer area of 250 x 150 mm. Case 350 x 250 x 95 mm. 240v operation. Only £37.00 p&p Send cheque to V.E.P. Ltd. 5 Hewens Rd. Uxbridge UB10 OFR.

### CENTURION ALARMS

We manufacture, you save £ £ £'s

Send s.a.e. or phone for our Free list of professional D.I.Y. Burglar Alarm Equipment and accessories. Discount up to 20% off list prices, eg. Control Equipment from £15.98, Decoy Bell Boxes from £5.95 inc.

TRADE ENQUIRIES WELCOME

0484-21000  
or 0484 35527 (24 hr. ans.)  
CENTURION ALARMS (ETI)  
265 Wakefield Road, Huddersfield  
HD5 9BE, W. Yorkshire  
Access by Visa  
Orders Welcomed

**BLEEPER ELECTRONIC SEAT BELT REMINDER,** flashers, full kits of parts, easy fitting, £6.95 plus 55p P&P. C.W.O. Microtech Industries, Brighouse, HD6 1RD.

**COPPER CLAD** Double Sided Fibreglass, 12" x 8". 10 sheets £6.5 sheets £4. Davron, Box No. E.T.I. 202, ASP Ltd., 145 Charing Cross Road, London WC2.

**BURGLAR Alarm Equipment.** Please visit our 2,000 sq. ft. showrooms or write or phone for your free catalogue. C.W.A.S. Ltd., 100 Rooley Avenue, Bradford BD6 1DB. Telephone 0274 308920.

### A1

051-228 3483  
INTRUDER ALARMS LTD  
WHOLESALE SUPPLIES  
MAIL ORDER DEPT


Bell Boxes	£6.00
Dummy Boxes	£4.50
Bell 6"	£7.50
<b>SIRENS</b>	
Minimite	£4.50
Electronic	£7.50
Cable (4 core)	£7.00
<b>PRESSURE MATS</b>	
Stair	£0.95
Standard	£1.50
<b>CONTROL PANELS</b>	
Battery T/E/E	£20.00
F.S.N. 20/40	£36.00
<b>CONTACTS</b>	
Aluminium	£1.85
Surface	£0.75
Flush	£0.65
Quickfits	£0.75
<b>BEAMS</b>	
Infra Red	£31.50
Ultrasonic comp.	£36.00
Rec Battery	£6.95

Discount on quantity — Please add 15% VAT

FOR ORDERS LESS THAN £30 P&P £2.00 OVER £30 P&P FREE

A1 ALARMS LTD  
86 Derby Lane, Old Swan, Liverpool 13

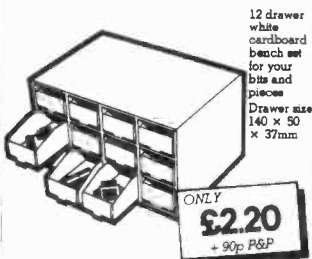Save money on drawer sets with the **BITSBBOX**



ONLY

£2.20

+ 90p P&P

Cheques/PO to: DMW Boxes  
81 Somerset Road London E17  
Prop. R.E. Davidson  
PERSONAL CALLERS & TRADE ENQUIRIES WELCOME

**DIGITAL WATCH REPLACE-**MENT parts, batteries, displays, backlights etc. Also reports publications, charts. S.a.e. for full list Profords Conersdrive, Holmergreen Bucks. HP15 6SGD

### NEW COMPONENTS CHEAPEST PRICES

New full spec parts ex stock. Same day despatch SAE or phone for full lists

Example prices: 10 uf. 35v radial capacitors 5p each. 100 1/4w resistors 75p (1K, 10K, 100K — other values available). BC308B 10p each 25IN 4148 for only 45p

**COLCHESTER COMPONENTS Unit A2**

Cowdry Centre, Colchester  
(0206) 66345

**AERIAL AMPLIFIERS** Improve weak television reception. Price £6.70, S.A.E. for leaflets. Electronic Mailorder, Ramsbottom, Lancashire BLO 9AGH.

**HIGH POWER MERCURY ION LASER,** emits green/red light. Easily built by the amateur constructor. Ideal school project, etc. Comprehensive kit of plans, including source of all materials, £5.25 + 25p P&P. Lasertech, 31 Mill Brow, Chadderton, Lancs.

### WANTED

**WANTED: ELECTRONIC COMPONENTS** and test equipment. Factories cleared. Good prices given. Q Services, 29 Lawford Crescent, Yateley, Camberley.

**WANTED** Trancedent DPX packs one to thirteen. Spy, 19 Queen Mary Ave., Queens Park, Glasgow.



**FOR SALE**

**STEREOPOWER 120 WATT**  
 £10.85 p.case & controls & sockets & instructions..KIA-8, Cunniffe Road, Ilkley..300 watt slaves £15 E/E.

**CABINET FITTINGS**  
 Freicloths, Coverings, Handles, Castors  
 Flight Case Locks & Parts, Jacks, XLRs,  
 Bulgins, Reverb Trays P & N mic Stands,  
 ABS Glasstire Horns,  
 CELESTION POWER  
 Speakers

**ADAM HALL SUPPLIES LTD**

Send  
 30p cheque,  
 P.O. for illustrated  
 catalogue Adam Hall (ET Supplies),  
 Unit B, Carlton Court, Grainger Road,  
 Southend-on-Sea.

**Anything to sell?**  
 Then sell it quickly  
 and cheaply  
 Phone **ASP** classified  
**01-437 1002 Ext 204**

**AVO 8 MODEL 8 MK5.** with leads in perfect condition £70  
 Phone Romford 21052 anytime.

**ELECTRONIC ORGAN** Two key-boards. Nice cabinet. Working but requires little work to complete £65. Dartford 20659.

**TAPE RECORDER LEADS** 7 pin Din to 2/3.5 1/2.5 jack plugs. Like AL 912p Intended for BBC computer £2 each post free A. Harvey, 38 St. Michaels Grove, Fareham, Hants, Mailorder only.

**SHEETMETAL FOLDERS** 18" x 18c steel, 16g aluminium Bench or vice held. Hobby or light industrial use. £38. 01-890-7838 day/evening.

**APPOINTMENTS**

**ASSISTANT  
 FILM RECORDISTS**

Assistant Film Recordists are required to undertake the operation of tape, disc and 16mm reproduction and recording equipment in Sound Transfer areas and Dubbing Theatre Record Rooms.

Candidates should have a knowledge and experience of film sound transfer and dubbing methods, together with an understanding of the use of sound in television film production. Normal hearing is essential.

These vacancies are offered on a contract basis of approximately three months duration. Salary £7314-£8859 according to qualifications and experience plus shift allowance when worked. Based West London.

Contact us immediately for application form (quote ref. 1153/ETI and enclose s.a.e.): **BBC Appointments, London, W1A 1AA. Tel. 01-580 4468 Ext. 4619.**

**We are an Equal Opportunities Employer**



**AUDIOPHILE FM TUNER ETI** Jan 81 with frequency readout (not LED's) and manor supplies TV tuner in Classic II case. £50 Tel 054 02677.

**PLANS 'N DESIGN**

**AMAZING ELECTRONICS PLANS.** Lasers, super-powered cutting rifle, pistol, light show, ultrasonic force fields, pocket defence weaponry, giant tesla, satellite TV pyrotechnics, 150 more projects. Catalogue £1 (refundable) from Plancentre, Bromyard Road Industrial Estate, Ledbury HR8.

**KITS**

**ELVIN ELECTRONIC ORGAN** Kit built. Needs minor repairs. Offers. All accessories mint condition Telephone (01) 947 6354.

**PRINTED CIRCUITS** Make your own simply, cheaply and quickly! Golden Fotolac light-sensitive laquer - now greatly improved and very much faster. Aerosol cans with full instructions, £2.50. Developer 35p. Ferric Chloride 60p. Clear acetate sheet for master 15p. Copper-clad fibreglass board, approx. 1mm thick £2.00 sq. ft. Post/packing 75p. White House Electronics, Castle Drive, Praa Sands, Penzance, Cornwall.

**PUSH BUTTON TELEPHONE,** 40 number memotry, build your own for around £16 using standard components. Full circuit, plans, and construction details, £3 (not BT approved). Ms M.J. Ellis, 1 Wells Drive, Heaton, Mersey, Stockport, Cheshire.

**AVOID  
 WASTED  
 RESPONSE**

Reach over 65,000 people in the electronics field and fill your vacancy cost effectively and quickly.  
 For details phone:  
**ASP** classified  
**01-437 1002  
 Ext 204**

**CLASSIFIED ADVERTISEMENT — ORDER FORM**

1.	2.	3.
4.	5.	6.
7.	8.	9.
10.	11.	12.
13.	14.	15.

Advertise nationally in these columns to over 100,000 readers for only 35p per word (minimum charge 15 words). Simply print your message in the coupon and send with your cheque or postal order made payable to Argus Specialist Publications Ltd to:

**CLASSIFIED DEPT., ELECTRONICS TODAY INTERNATIONAL**  
 145 Charing Cross Rd., London WC2H 0EE.

Tel: 01-437 1002

Please indicate classification required.

Name .....

Address .....

.....

.....

Tel.No.(Day) .....

We take Access and Barclaycard

Please place my advert in E.T.I. for  months. Please indicate number of insertions required.

# Get moving with these new developments in UK Robotics

— advanced electrohydraulic designs for education, industry and now available to the home constructor.

Hebot II is a turtle-type robot which takes programming out of the two dimensional world of the VDU into the real three dimensional world. Given a DC supply of 9-15V it can perform a bewildering number of moves under computer control — forwards, backwards, left and right — with each wheel independently controlled. It has blinking eyes, bleeps with a choice of two tones and has a solenoid operated pen to chart its progress. Touch sensors coupled to its shell return data, about its environment, to the computer for it to calculate evasive or exploratory action. Hebot II connects directly to an I/O port or alternatively with the universal interface board to the expansion bus of a ZX81 or other computer.



HEBOTT II

Up to the nano-second hard, firm and software developments embodied in a complete system. 1.2 Mega Hertz 16 bit CPU; 64K upwardly compatible DRAM; separate 16K video DRAM and 24K TI Power Basic with overwrite. Supports up to four Disc drives of mixed type with 16 serial I/O ports. Programmable Baud rate and comprehensive E Bus interface designed to support real world applications.

Very high resolution graphics gives 3D simulation in 16 colours on 36 prioritised planes of user definable characters. Software FORTH coming includes this trendy language along with NOS C/PM.

Hardware components available separately with details in Nov, Dec, and Jan issues of ETI. Software features include; Real time clock, full renumber command, buffered I/O to free machine whilst

Robotic experience is becoming as essential a subject as computing. MICROGRASP provides the lowest cost means of acquiring that experience but despite its ultra low price the robot has considerable versatility. There are 5 axes each using a servo motor and there is feedback from each of the arm movements. Control is by any computer with an expansion bus — the ZX81 being particularly suitable. Servoing is achieved with hardware on the interface board to keep programming simple and the robot is operated under BASIC commands with no computer specific software required. The interface board is memory mapped using only 64 bytes at any of 1024 switch selectable locations.

- MICROGRASP robot kit with power supply £145.00
- Universal computer interface board kit £48.50
- 23 way edge connector £2.50
- ZX81 peripheral/RAM Pack splitter board £3.00



MICROGRASP, INTERFACE BOARD AND ZX81

printing, call to machine code routines, hexadecimal support and user-friendly textual error trapping messages.

If computers interest you then the Cortex will expand your understanding infinitely more than off the shelf machines. Use it in business, education, research or just play with the incredible graphics capability. At Powertran we are using these machines in conventional roles, in product control and R & D. We shall co-ordinate the Cortex user group and distribute software for the TMS 9995 CPU. Complete 16 bit 64K computer kit £295.00 + VAT. Complete 16 bit 64K computer ready built £395.00 + VAT.



Top of the range is the Genesis P102 which has dual speed control, continuous servo operation and double acting cylinders for increased torque on the wrist and arm rotation joints. The microprocessor based control system has additional memory position interrogation via the RS232C interface increasing the versatility of computer control and inputs are provided for machine tool interfacing.

6 axis system READY BUILT £1950.00  
Powertran CORTEX 16 bit 64K computer kit £295.00; READY BUILT £395.00  
(Electronics Today International December issue on CORTEX)



GENESIS P102 PROCESSOR BOX, HAND HELD CONTROLLER AND CORTEX COMPUTER

### Example prices and specifications

**Genesis S101**  
Base: 19.5" x 11" x 7.5"  
Lifting capacity: 1500gm  
Arm lift: 6.6"  
Weight: 29Kg  
4 axis model in kit form £425  
5 axis model in kit form £475

**Genesis P101**  
Base: 19.5" x 11" x 7.5"  
Lifting capacity: 2000gm  
Arm lengths between axes: 14.0"  
Weight: 34Kg  
4 axis model in kit form £675  
6 axis model in kit form £595

### Complete Systems as shown in Photograph above

**Genesis S101**  
4 axis system in kit form £681.50  
5 axis system in kit form £737.50  
5 axis system Ready Built £1450  
**Genesis P101**  
6 axis system in kit form £945.00  
6 axis system Ready Built £1650

All prices exclusive of VAT

With prices starting below £1,000 the Genesis range of general purpose robots provide a first rate introduction to robotics for both education and industry. Each has a self-contained hydraulic power source, which enables loads of several pounds to be smoothly handled. The system operated from a single phase 240 or 120V AC supply or a 12V DC supply. The machine can be supplied with up to 5 axes each of which is fully independent but capable of simultaneous operation. Position control is achieved by means of a closed-loop feedback system based around a dedicated microprocessor. Movement sequences can be entered, stored and replayed by use of a hand held controller, alternatively the systems can also be interfaced to an external computer via a standard RS 232C link.



GENESIS S101 AND GENESIS P101 WITH PROCESSOR BOXES AND HAND-HELD CONTROLLERS

WORLD LEADERS IN ELECTRONIC KIT DESIGN AND SUPPLY

(CYBERNETIC DIVISION) PORTWAY INDUSTRIAL ESTATE  
ANDOVER HANTS SP10 3NM Phone Enquiries (0264) 64455  
Export Enquiries Powertran International  
Holm Down Farm Lopcombe Salisbury  
Wiltshire SP5 1BP  
Tel: 0264 781545 TLX: 477407 ZENMON



# SPEECH SYNTHESISER FOR ZX81 and VIC20

## THE MAPLIN TALK-BACK

Now your computer can talk!

- ★ Allophone (extended phoneme) system gives unlimited vocabulary.
- ★ Can be used with unexpanded VIC20 or ZX81 — does not require large areas of memory.
- ★ In VIC20 version, speech output is direct to TV speaker with no additional amplification needed.
- ★ Allows speech to be easily included in programs.


Complete kit only £24.95.

Order As LK00A (VIC20 Talk-Back).

LK01B (ZX81 Talk-Back).

Full construction details in Maplin Projects Book 6.

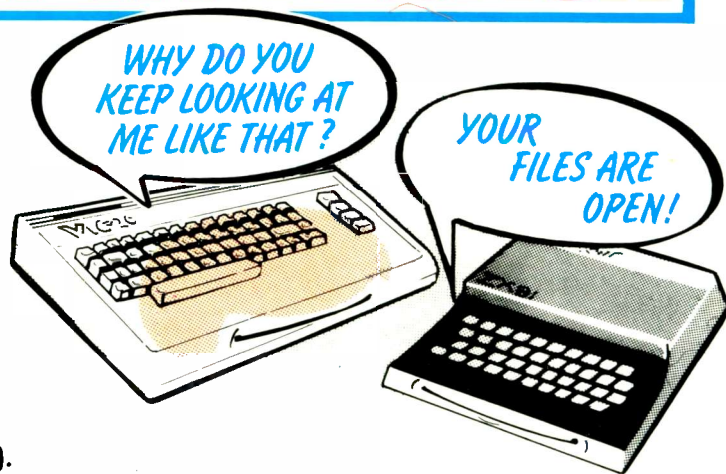Price 70p. Order As XA06G (Maplin Mag Vol. 2 No. 6).



### KEYBOARD WITH ELECTRONICS FOR ZX81



- ★ Full size, full travel keyboard that's simple to add to your ZX81 (no soldering in ZX81).
- ★ Complete with electronics to make "Shift Lock", "Function" and "Graphics 2" single key selections.
- ★ Powered (with adaptor supplied) from ZX81's own standard power supply.

Full details in Project Book 3 (XA03D) Price 60p.  
Complete kit (excl. case) £19.95. Order As LW72P.  
Case £4.95. Order As XG17T.  
Ready built-in case £29.95. Order As XG22Y.

### OTHER KITS FOR ZX81

3-Channel Sounds Generator (Details in Book 5).  
Order As LW96E. Price £10.95.

ZX81 Sound On Your TV Set (Details in Book 6).  
Order As LK02C. Price £19.95.

ZX81 I/O Port gives two bi-directional 8-bit ports  
(Details in Book 4).  
Order As LW76H. Price £9.25.

ZX81 Extendingboard will accept 16K RAM and 3 other  
plug-in modules.

PCB: Order As GB08J. Price £2.32.  
Edge Connectors (4 needed):  
Order As RK35Q. Price £2.39.

### HOME SECURITY SYSTEM

Six independent channels — 2  
or 4 wire operation. External  
horn. High degree of protec-  
tion and long term reliability.  
Full details in Projects Book 2.  
(XA02C) Price 60p



### MATINEE ORGAN

Easy-to-build, superb  
specification. Compar-  
able with organs selling  
for up to £1000. Full  
construction details in our  
book (XH55K). Price £2.50.  
Complete kits available.  
Electronics (XY91Y) £299.95\*  
Cabinet (XY93B) £99.50\*  
Demo cassette (XX43W) £1.99.



\* Carriage extra


### 25W STEREO MOSFET AMPLIFIER



- ★ Over 26W/channel into 8Ω at 1kHz both channels driven
  - ★ Frequency response 20Hz to 40kHz ± 1dB.
  - ★ Low distortion, low noise and high reliability power MOSFET output stage.
  - ★ Extremely easy to build. Almost everything fits on main pcb, cutting interwiring to just 7 wires (plus toroidal transformer and mains lead terminations).
  - ★ Complete kit contains everything you need including pre-drilled and printed chassis and wooden cabinet.
- Full details in Projects Book 3. Price 60p (XA03D).  
Complete kit only £55.20 incl. VAT and carriage (LW71N).
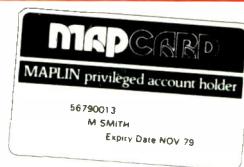
### BUY IT WITH MAPCARD

Send now for an  
application form — then  
buy it with MAPCARD.  
MAPCARD gives you  
real spending power —  
up to 24 times your  
monthly payments,  
instantly.



All prices include VAT & carriage. Please add 50p handling charge to orders under £5 total value.

### MAPLIN'S FANTASTIC PROJECTS

Full details in our project books. Issues 1 to 5: 60p each.  
Issue 6: 70p.

In Book 1 (XA01B) 120W rms MOSFET Combo-  
Amplifier ● Universal Timer with 18 program times and  
4 outputs ● Temperature Gauge ● Six Vero Projects.

In Book 2 (XA02C) Home Security System ● Train  
Controller for 14 trains on one circuit ● Stopwatch with  
multiple modes ● Miles-per-Gallon Meter.

In Book 3 (XA03D) ZX81 Keyboard with electronics ●  
Stereo 25W MOSFET Amplifier ● Doppler Radar Intruder  
Detector ● Remote Control for Train Controller.

In Book 4 (XA04E) Telephone Exchange for 16 exten-  
sions ● Frequency Counter 10Hz to 600MHz ● Ultrasonic  
Intruder Detector ● I/O Port for ZX81 ● Car Burglar  
Alarm ● Remote Control for 25W Stereo Amp.

In Book 5 (XA05F) Modem to European standard ●  
100W 240V AC Inverter ● Sounds Generator for ZX81  
● Central Heating Controller ● Panic Button for Home  
Security System ● Model Train Projects ● Timer for  
External Sounder.

In Book 6 (XA06G) Speech Synthesiser for ZX81 &  
VIC20 ● Module to Bridge two of our MOSFET Amps to  
make a 350W Amp ● ZX81 Sound on your TV  
● Scratch Filter ● Damp Meter

### MAPLIN'S NEW 1983 CATALOGUE

Over 390 pages packed  
with data and pictures  
and all completely  
revised and including  
over 1000 new items.  
On sale in all branches  
of WHSMITH  
Price £1.25.



### Post this coupon now!

Please send me a copy of your 1983 catalogue. I enclose £1.50 (inc p&p).  
If I am not completely satisfied I may return the catalogue to you and have  
my money refunded. If you live outside the U.K. send £1.90 or 10 International  
Reply Coupons.

Name

Address

ETI

# MAPLIN

MAPLIN ELECTRONIC SUPPLIES LTD.  
P.O. Box 3, Rayleigh, Essex SS6 8LR

Telephone: Sales (0702) 552911 General (0702) 554155

Shops at: Note: Shops closed Mondays  
159 King St., Hammersmith, London W6. Telephone: 01-748 0926  
284 London Rd., Westcliff-on-Sea, Essex. Telephone: (0702) 554000  
Lynton Square, Perry Barr, Birmingham. Telephone: (021) 356 7292