




electronics today

INTERNATIONAL

AUGUST 1983 85p

ANIMATE YOUR LIFE

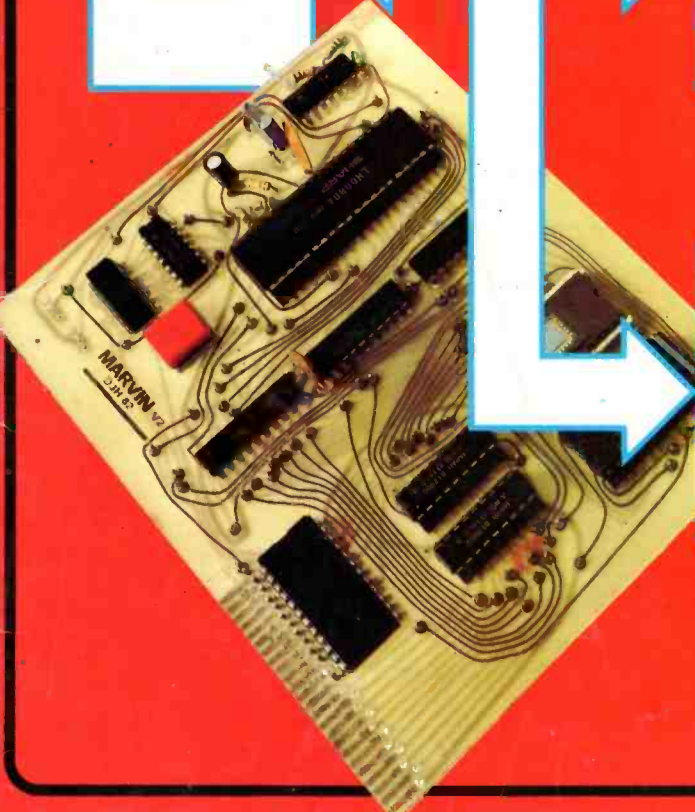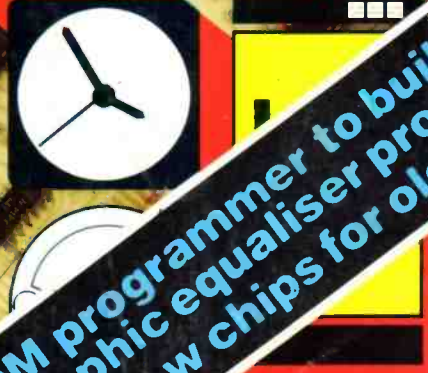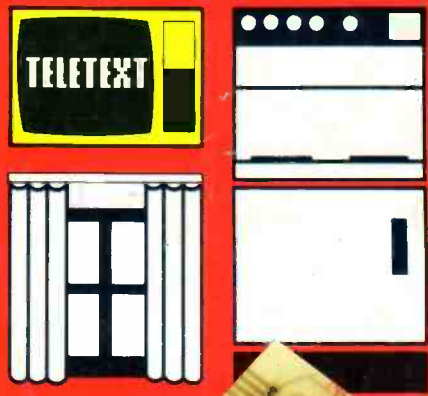Z80-based control computer for home, industrial and laboratory control
modular construction for maximum flexibility



PLUS EPROM programmer to build
High quality graphic equaliser project
IC update: new chips for old

Star sounds **

Star quality **

Star features **


BIG NEWS ABOUT OUR LATEST ADVANCES IN ROBOTICS SEE INSIDE BACK COVER

Free SECURICOR DELIVERY on all orders over £100 (UK mainland only) Add just £2.50 on lower price orders



DJ90 Stereo Mixer — this is a really versatile new mixer that enables the constructor DJ to produce a professional performance every time. There are two stereo inputs for magnetic cartridges, a stereo auxiliary input and mike input. Other 'plus' features are auto-panning for fast or slow slider controls, multi-mixing, ducking, interrupt, input modulation, in short everything... the whole works — AND — under £100 complete! Complete kit £97.50 + VAT

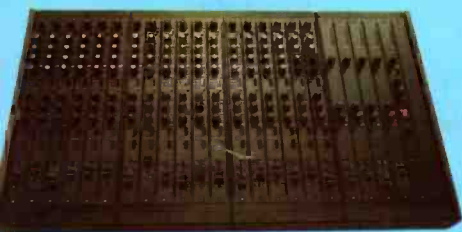TRANSCENDENT 2000 — Although only a 3 octave keyboard the '2000' features the same design ingenuity, careful engineering and quality components of its larger brethren. The kit is well within the scope of the first time builder — buy it, build it — play it! You will know you have made the right choice. Complete kit £165.00 + VAT



This versatile modular mixer, featured as a constructional article in Practical Electronics can be built up to a maximum of 24 inputs, 4 outputs and an auxiliary channel. Each input channel has Mic and Line inputs, variable gain, bass and treble controls and a parametric middle frequency equalizer. There are send and return jacks, auxiliary, pan and fader controls and output and group switching. The output channels have PPM displays and record and studio outputs. The auxiliary channel also has a PPM display and there is a headphone monitor jack and a built-in talk-back microphone. The mixer modules plug into base units each of which takes up to 6 channels. To eliminate hum, the power supply is in a separate cabinet.

SALES COUNTER Collect your order from the factory. Open 9-12/1-4.30 Mon-Thurs. Easy parking, no waiting

Digital Delay Line — With its ability to give delay times from 1.6 mSecs to up to 1.6 secs. Many powerful effects including phasing, flanging, A.D.T., chorus, echo &



vibrato are obtained. The basic kit is extended in 400 mS steps up to 1.6 secs. Simply by adding more parts to the PCB. Compare with units costing over £1,000! Complete kit (400 mS delay) £130 + VAT Parts for extra 400 mS delay £9.50 + VAT

KIT PRICES

Input channel	£19.90	Base unit and wooden front	£27.50
Output channel	£18.50	Pair of mahogany end cheeks	£12.50
Auxiliary channel	£22.50	Power Supply and cabinet	£19.50
Blank Panel	£3.00		

All prices are VAT exclusive

TRANSCENDENT POLYSYNTH — A four octave polyphonic synthesiser with outstanding design characteristics and versatility and performance to match. Complete kit £275.00 plus VAT (single voice) Extra voice (up to three-more) £42.00 plus VAT



Free Soldering Practise Kit on request with your first kit — useful tips, well illustrated.

MPA 200 — is a low price, high power 100W amplifier. Its smart styling, professional appearance and performance, make it one of our most popular designs. With adaptable inputs the mixer accepts a variety of sources yet straightforward construction makes it ideal for

the first time builder. Complete kit £49.90 + VAT. Chromatque 5000 — a 5 channel lighting system powerful enough for professional discos yet controllable for home-effects. Sound to light, strobe to music level, random or sequential effects — each channel can handle up to 500W yet minimal wiring is needed with our unique single board design. Complete kit £49.50 + VAT



Component packs for most kits are available See our great free catalogue, full details of all our range

ETI VOCODER — 14 channels, each with independent level control, for maximum versatility and intelligibility. Two input amplifiers — for speech/excitation — each with level control and tone control. The Vocoder is a powerful yet flexible machine that is interesting to build and thanks to our easy to follow construction manual, is within the capability of most enthusiasts. Complete kit £175.00 + VAT

SP2 200 twice the power with two of the reliable, durable and economic amps from the MPA 200, fed by separate power supplies from a common toroidal transformer. Superb finish and quality components throughout — up to (even over) the standard of high priced factory-built units! Complete kit £64.90 + VAT



WORLD LEADERS IN ELECTRONIC KIT DESIGN AND SUPPLY

PORTWAY INDUSTRIAL ESTATE ANDOVER, HANTS SA10 3NM. ORDER BY PHONE (0264) 64455



Simply request your chosen kit and quote your Access or Barclaycard Number.

electronics today

INTERNATIONAL AUGUST 1983 VOL 12 NO 8

AN ARGUS SPECIALIST PUBLICATION

electronics today

ANIMATE YOUR LIFE

Z80-based control computer for home, industrial and laboratory control modular construction for maximum flexibility

High quality gear available to build IC support for your chips for only

..AUDIO...COMPUTING... RADIO...ROBOTICS..

Dave Bradshaw: Editor
Phil Walker: Project Editor
Jerry Fowler: Technical Illustrator
David Kitchener: Advertisement Manager
Joanne James: Assistant Advertisement Manager
Ron Harris B.Sc: Managing Editor
T.J. Connell: Managing Director

PUBLISHED BY:
 Argus Specialist Publications Ltd.,
 145 Charing Cross Road, London WC2H 0EE.
DISTRIBUTED BY:
 Argus Press Sales & Distribution Ltd.,
 12-18 Paul Street, London EC2A 4JS
 (British Isles)
PRINTED BY:
 QB Limited, Colchester.
COVERS PRINTED BY:
 Alabaster Passmore.

OVERSEAS EDITIONS and their EDITORS

AUSTRALIA — Roger Harrison
 CANADA — Halvor Moorshead
 GERMANY — Udo Wittig
 HOLLAND — Anton Kriegsman



Member of the Audit Bureau of Circulation

Electronics Today is normally published on the first Friday in the month preceding cover date. □ The contents of this publication including all articles, designs, plans, drawings and programs and all copyright and other intellectual property rights therein belong to Argus Specialist Publications Limited. All rights conferred by the Law of Copyright and other intellectual property rights and by virtue of international copyright conventions are specifically reserved to Argus Specialist Publications Limited and any reproduction requires the prior written consent of the Company. © 1983 Argus Specialist Publications Ltd □ All reasonable care is taken in the preparation of the magazine contents, but the publishers cannot be held legally responsible for errors. Where mistakes do occur, a correction will normally be published as soon as possible afterwards. All prices and data contained in advertisements are accepted by us in good faith as correct at time of going to press. Neither the advertisers nor the publishers can be held responsible, however, for any variations affecting price or availability which may occur after the publication has closed for press.

□ Subscription Rates. UK £13.15 including postage. Airmail and other rates upon application to ETI Subscriptions Department, 513 London Road, Thornton Heath, Surrey CR4 6AR.

EDITORIAL AND ADVERTISEMENT OFFICE

145 Charing Cross Road, London WC2H 0EE. Telephone 01-437 1002/3/4/5. Telex 8811896.

FEATURES

- DIGEST**11
 What can we say? Irreverent irrelevancies, stupid stories, potty press releases, nefarious news . . .
- IC UPDATE**39
 New ICs for old — at least, one brand new IC and one replacement for a hoary old favourite.
- MOTOCAR**24
 When a leading manufacturer takes a bus to the car, it's time for big changes in the auto industry.



READ/WRITE54
 We have a controversy over the Hyconomiser and a criticism of our audio buying guide. We don't mind people being rude to us, honest.

TECH TIPS58
 Only room for a couple this month after last month's beano — these are for a traffic lights simulator and a keyboard alphanumeric lock.

PROJECTS

- GRAPHIC EQUALISER**18
 Not being a magazine for half measures, this a truly professional design with not one but three channels per octave.
- TV STORAGE SCOPE**30
 Second and concluding part of our state-of-the-art digital design can convert your TV into a 10 MHz storage scope.
- UNIVERSAL EPROM PROGRAMMER**45
 Now there's no excuse not to use EPROMs to hold your programs — this unit will program nearly all the devices that you can currently buy.
- RADIO CONTROL SERVO FAIL-SAFE**61
 A little gadget that sets servos in a 'safe' position if the radio link fails.



Z80 CONTROL COMPUTER65
 A simple microcomputer based on the well-known Z80 processor that has a multitude of uses in controlling all sorts of things.

FOIL PATTERNS72

INFORMATION

- THIS YEAR'S BREADBOARD EXHIBITION**35
ETI BOOKS SERVICE53
- READER SERVICES**70
ETI PCB SERVICE77
ADVERTISER'S INDEX82

MAKE YOUR OWN P.C.B's. & FRONT PANELS



AT LEAST
10% OFF
NORMAL REC. PRICE

PHOTO RESIST KIT (Ref: HB2)

Complete kit containing artwork PCB, and all necessary process materials
NORMAL REC. PRICE £24.60

UV EXPOSURE UNIT (Ref: UV1)

Perfect results everytime. Kit contains: Lamp, Holder & Shade together with full instructions for DIY Unit which offers PCB, Precision Photo, Label & Panel manufacture
NORMAL REC. PRICE £27.60

UV EXPOSURE UNIT AND ARTBOX (Ref: UV2)

A portable ready made unit containing two 8 watt UV tubes giving a 6" x 9" exposure area which may also be used as a light box with the UV filter supplied.
NORMAL REC. PRICE £64.60

FOTOTOOL KIT (Ref: HB3)

Containing artwork, film and all the necessary process materials required for professional quality labels and panels. CAN ALSO BE USED TO PRODUCE PRECISION PCB PHOTOMASTERS
NORMAL REC. PRICE £23.10

OFFERS VALID UNTIL AUGUST 31st 1983

Please send me the following as quickly as possible

QTY	DESCRIPTION	Price Ea.	TOTAL
	PHOTO RESIST KIT (HB2)	£21.50	£ :
	UV EXPOSURE UNIT (UV1)	£24.00	£ :
	UV ARTBOX (UV2)	£58.00	£ :
	FOTO TOOL KIT (HB3)	£20.00	£ :
	TOTAL	£ :	£ :
	Cheque/PO	£ :	£ :

(Cheques or Postal Orders only please for Special Offers).

Please send full catalogue Price includes VAT & Carriage.

Name

Address

hobbyboard

complete P.C.B. workshop

a division of
KELAN ENGINEERING LTD
Hookstone Park
Harrogate, N. Yorks

ETI/8/83

T.V. SOUND TUNER

BUILT AND TESTED

In the cut-throat world of consumer electronics, one of the questions designers apparently ponder over is "Will anyone notice if we save money by chopping this out?" In the domestic TV set, one of the first casualties seems to be the sound quality. Small speakers and no tone controls are common and all this is really quite sad, as the TV companies do their best to transmit the highest quality sound. Given this background a compact and independent TV tuner that connects direct to your Hi-Fi is a must for quality reproduction. The unit is mains-operated. This TV SOUND TUNER offers full UHF coverage with 5 pre-selected tuning controls. It can also be used in conjunction with your video recorder. Dimensions: 11 1/4" x 8 1/2" x 3 1/4"



£24.95 + £2.00p&p.


PRACTICAL ELECTRONICS STEREO CASSETTE RECORDER KIT COMPLETE WITH CASE

SPECIAL OFFER!

ONLY £31.00 plus £2.75 p&p.

• NOISE REDUCTION SYSTEM. • AUTO STOP. • TAPE COUNTER. • SWITCHABLE E.Q. • INDEPENDENT LEVEL CONTROLS. • TWIN V.U. METER. • WOW & FLUTTER 0.1%. • RECORD/PLAYBACK I.C. WITH ELECTRONIC SWITCHING. • FULLY VARIABLE RECORDING BIAS FOR ACCURATE MATCHING OF ALL TYPES.

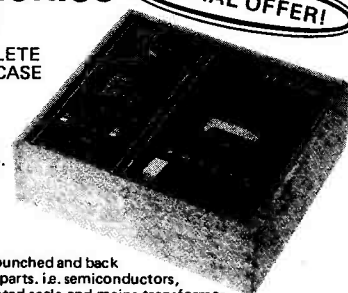Kit includes tape transport mechanism, ready punched and back printed quality circuit board and all electronic parts, i.e. semiconductors, resistors, capacitors, hardware, top cover, printed scale and mains transformer. You only supply solder & hook-up wire. Featured in April P.E. reprint 50p. Free with kit.



STEREO TUNER KIT

This easy to build 3 band stereo AM/FM tuner kit is designed in conjunction with P.E. (July '81). For ease of construction and alignment it incorporates three Mullard modules and an I.C. IF System. FEATURES: VHF, MW, LW Bands, interstation muting and AFC on VHF. Tuning meter. Two back printed PCB's. Ready made chassis and scale. Aerial: AM-ferrite rod, FM-75 or 300 ohms. Stabilised power supply with 'C' core mains transformer. All components supplied are to P.E. strict specification. Front scale size 10 1/2" x 2 1/2" approx. Complete with diagram and instructions.

SPECIAL OFFER! £13.95 + £2.50 p&p. Self assembly simulated wood cabinet sleeve to suit tuner only. Finish size: 11 1/4" x 8 1/2" x 3 1/4". £3.50 Plus £1.50 p&p.



STEREO CASSETTE DECK

Stereo cassette tape deck transport with electronics. Manufacturer's surplus -- brand new and operational -- sold without warranty.

£11.95 plus £2.50 p&p.

Just requires mains transformer and input/output sockets and a volume control to complete. Supplied with full connection details.



125W HIGH POWER AMP MODULES

The power amp kit is a module for high power applications - disco units, guitar amplifiers, public address systems and even high power domestic systems. The unit is protected against short circuiting of the load and is safe in an open circuit condition. A large safety margin exists by use of generously rated components, result, a high powered rugged unit. The PC board is back printed, etched and ready to drill for ease of construction and the aluminium chassis is preformed and ready to use. Supplied with all parts, circuit diagrams and instructions.

ACCESSORIES: Stereo/mono mains power supply kit with transformer: £10.50 plus £2.00 p&p.



SPECIFICATIONS: Max. output power (RMS): 125 W. Operating voltage (DC): 50 - 80 max. Loads: 4 - 16 ohm. Frequency response measured @ 100 watts: 25Hz - 20KHz. Sensitivity for 100w: 400mV @ 47K. Typical T.H.D. @ 50 watts, 4 ohms: 0.1%. Dimensions: 205x90 and 190x36mm.

KIT £10.50 +£1.15 p&p. BUILT £14.25 +£1.15 p&p.

AUDAX 8"

HIGH QUALITY 40 WATTS RMS BASS/MIDRANGE Ideal for either Hi-Fi or Disco use this speaker features an aluminium voice coil a heavy 70mm diameter magnet. Frequency res: 20Hz to 7KHz. Impedance: 8 ohms. £5.95 +£2.20 P&P.

AUDAX 40W Ferro-Fluid Hi-Fi Tweeter

X/over on 5kHz - 22kHz. 60mm square. 8 ohm. £5.50 +60p p&p.



SPEAKER BARGAINS

2 WAY 10 WATT SPEAKER KIT 8" bass/mid range and 3 1/4" tweeter. Complete with screws, wire, crossover components and cabinet. All wood pre-cut -- no cutting required. Finish - chipboard covered wood simulate. size 14 1/2" x 8 3/4" x 4". PAIR for ONLY £12.50 plus £1.75 p&p.



All mail to: 21E HIGH STREET, ACTON, W3 6NG.

Note: Goods despatched to U.K. postal addresses only. All items subject to availability. Prices correct at 31/5/83 and subject to change without notice. Please allow 14 working days from receipt of order for despatch. RTVC Limited reserve the right to update their products without notice. All enquiries send S.A.E. Telephone or mail orders by ACCESS welcome.

ALL CALLERS TO: 323 EDGWARE ROAD, LONDON W2. Telephone: 01-723 8432. (5 minutes walk from Edgware Road Tube Station) Now open 6 days a week 9 - 6. Prices include VAT.





MULLARD SPEAKER KITS

Purposely designed 40 watt R.M.S. and 30 watt R.M.S. 8 ohm speaker systems recently developed by MULLARD'S specialist team in Belgium. Kits comprise Mullard woofer (8" or 5") with foam surround and aluminium voice coil. Mullard 3" high power domed tweeter. Built and tested crossover based on Mullard circuit, combining low loss components, glass fibre board and recessed loudspeaker terminals. SUPERB SOUNDS AT LOW COST. Kits supplied in polystyrene packs complete with instructions.


8" 40W system — recommended cabinet size 240 x 216 x 445mm
Price £14.90 each + £2.00 P & P.

5" 30W system — recommended cabinet size 160 x 176 x 295mm
Price £13.90 each + £1.50 P & P.

Designer approved flat pack cabinet kits, including grill fabric. Can be finished with iron on veneer or self adhesive vinyl etc.

8" system cabinet kit £8.00 each + £2.50 P & P.

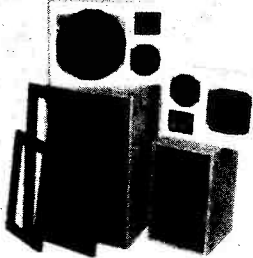5" system cabinet kit £7.00 each + £2.00 P & P.




STEREO CASSETTE TAPE DECK MODULE

Comprising of a top panel and tape mechanism coupled to a record/play back printed board assembly. Supplied as one complete unit for horizontal installation into cabinet or console of own choice. These units are brand new, ready built and tested.

Features: Three digit tape counter. Autostop. Six piano type keys, record, rewind, fast forward, play, stop and eject. Automatic record level control. Main inputs plus secondary inputs for stereo microphones. Input Sensitivity: 100mV to 2V. Input impedance: 68K. Output level: 400mV to both left and right hand channels. Output impedance: 10K. Signal to noise ratio: 45dB. Wow and flutter: 0.1%. Power Supply requirements: 18V DC at 300mA. Connections: The left and right hand stereo inputs and outputs are via individual screened leads, all terminated with phono plugs (phono sockets provided). Dimensions: Top panel 5 1/2" x 11 1/2". Clearance required under top panel 2 1/2". Supplied complete with circuit diagram and connecting diagram. Attractive black and silver finish.

Price £28.70 + £2.50 postage and packing.

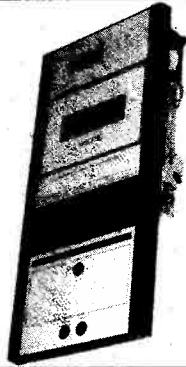Supplementary parts for 18V D.C. power supply (transformer, bridge rectifier and smoothing capacitor) £3.50.



LOUDSPEAKERS


THREE QUALITY POWER LOUD-SPEAKERS (15", 12" and 8" See Photo). Ideal for both Hi-Fi and Disco applications. All units have attractive cast aluminium (ground finish) fixing escutcheons.

Specification and Prices.

15" 100 watt R.M.S. Impedance 8 ohms. 50 oz. magnet. 2" aluminium voice coil. Res. Freq. 20 Hz. Freq. Resp. to 2.5KHz. Sens. 97dB. Price: £34.00 each + £3.00 P&P

12" 100 watt R.M.S. Impedance 8 ohms. 50 oz. magnet. 2" aluminium voice coil. Res. Freq. 25Hz. Freq. Resp. to 4 KHz. Sens. 95dB. Price: £24.50 each + £3.00 P&P

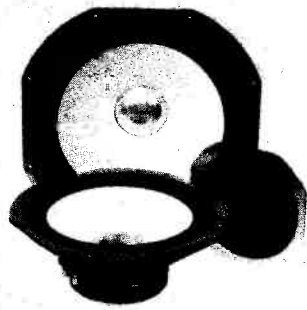8" 50 watt R.M.S. Impedance 8 ohms. 20 oz. magnet. 1 1/2" aluminium voice coil. Res. Freq. 40Hz. Freq. Resp. to 6 KHz. Sens. 92dB. Black Cone. Price: £9.50 each. Also available with black protective grille. Price: £9.99 each. P&P £1.50.



12" 85 watt R.M.S. McKENZIE C1286GP (LEAD GUITAR, KEYBOARD, DISCO) 2" aluminium voice coil, aluminium centre dome, 8 ohm imp., Res. Freq. 45Hz., Freq. Resp. to 6.5KHz., Sens. 98dB. Price: £22.00 + £3 carriage.

12" 85 watt R.M.S. McKENZIE C1286TC (P.A., DISCO) 2" aluminium voice coil. Twin cone. 8 ohm imp., Res. Freq. 45Hz., Freq. Resp. to 14KHz. Price £22 + £3 carriage.

15" 150 watt R.M.S. McKENZIE C15 (BASS GUITAR, P.A.) 3" aluminium voice coil. Die cast chassis. 8 ohm imp., Res. Freq. 40Hz., Freq. Resp. to 4KHz. Price: £47 + £4 carriage.

PIEZO ELECTRIC TWEETERS - MOTOROLA

Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.

TYPE 'A' (KSN2036A) 3" round with protective wire mesh, ideal for bookshelf and medium sized Hi-fi speakers. Price £4.29 each.

TYPE 'B' (KSN1005A) 3 1/2" super horn. For general purpose speakers, disco and P.A. systems etc. Price £4.99 each.



TYPE 'C' (KSN6016A) 2" x 5" wide dispersion horn. For quality Hi-fi systems and quality discos etc. Price £5.99 each.

TYPE 'D' (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-fi systems and quality discos. Price £7.99 each.

TYPE 'E' (KSN1038A) 3 3/4" horn tweeter with attractive silver finish trim. Suitable for Hi-fi monitor systems etc. Price £4.99 each.

TYPE 'F' (KSN1057A) Cased version of type 'E'. Free standing satellite tweeter. Perfect add on tweeter for conventional loudspeaker systems. Price £10.75 each

P&P 20p ea. (or SAE for Piezo leaflets).

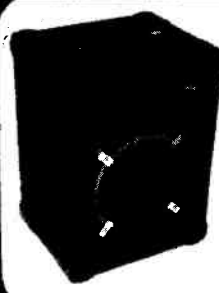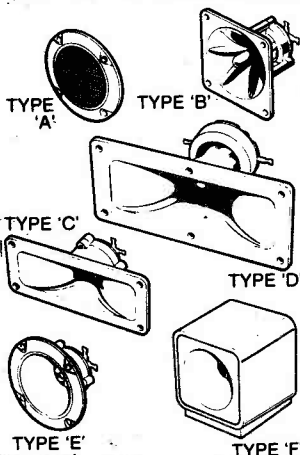

OMP 80 LOUDSPEAKER

The very best in quality and value.

Ported tuned cabinet in hard-wearing black vinylite with protective corners and carry handle. Built and tested, employing 10in British driver and Piezo tweeter. Spec: 80 watts RMS; 8 ohms; 45Hz-20KHz; Size: 20in x 15in x 12in; Weight: 30 pounds.

Price: £49.00 each
£90 per pair
Carriage: £5 each £7 per pair

BK ELECTRONICS

Prompt Deliveries
VAT inclusive prices
Audio Equipment
Test Equipment
by
Thandar
and
Leader



HOBBY KITS. Proven designs including glass fibre printed circuit board and high quality components complete with instructions.

FM MICROTRANSMITTER (BUG) 90/105MHz with very sensitive microphone. Range 100/300 metres. 5 x 46 x 14mm (9 volt)
Price: £7.99p

DIGITAL THERMOMETER -9.9°C to +99.9°C. LED display. Complete with sensor. 70 x 70 mm (9 volt) Price: £27.60p

3 WATT FM TRANSMITTER 3 WATT 85/115MHz varicap controlled, professional performance. Range up to 3 miles 35 x 84 x 12 mm (12 volt) Price: £12.49p

SINGLE CHANNEL RADIO CONTROLLED TRANSMITTER/RECEIVER 27MHz Range up to 500 metres. Double coded modulation. Receiver output operates relay with 2amp/240 volt contacts. Ideal for many applications. Receiver 90 x 70 x 22 mm 9/12 volt) Price: £16.49 Transmitter 80 x 50 x 15 mm (9/12 volt) Price £10.29 P&P All Kits +50p. S.A.E. for complete list.



3 watt FM Transmitter


BSR P256 TURNTABLE

P256 turntable chassis ● S shaped tone arm ● Belt driven ● Aluminium platter ● Precision calibrated counter balance ● Anti-skate (bias device) ● Damped cueing lever ● 240 volt AC operation (Hz) ● Cut-out template supplied ● Completely manual arm. This deck has a completely manual arm and is designed primarily for disco and studio use where all the advantages of a manual arm are required.

Price £31.35 each. £2.50 P&P



OMP POWER AMPLIFIER MODULE

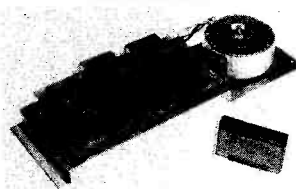

New model.
Improved specification

NEW OMP100 Mk.II POWER AMPLIFIER MODULE Power Amplifier Module complete with integral heat sink, toroidal transformer power supply and glass fibre p.c.b. assembly. Incorporates drive circuit to power a compatible LED Vu meter. New improved specification makes this amplifier ideal for P.A., instrumental and Hi-Fi applications.

SPECIFICATION
Output Power:— 110 watts R.M.S.
Loads:— Open and short circuit proof 4/16 ohms.
Frequency Response:— 15Hz - 30KHz -3dB. T.H.D.:— 0.01%
S.N.R. (Unweighted):— -118dB ±3.5dB
Sensitivity for Max Output:— 500mV @ 10K.
Size:— 360 x 115 x 72 mm
Price:— £31.99 + £2.00 P&P
Vu Meter Price:— £7.00 + 50p P&P.

HOME PROTECTION SYSTEM

Better to be 'Alarmed' than terrified. Thandar's famous 'Minder' Burglar Alarm System. Superior microwave principle. Supplied as three units, complete with interconnection cable. FULLY GUARANTEED.

Control Unit — Houses microwave radar unit, range up to 15 metres adjustable by sensitivity control. Three position, key operated fascia switch — off — test — armed. 30 second exit and entry delay.


Indoor alarm — Electronic swept freq. siren. 104dB output.

Outdoor Alarm — Electronic swept freq. siren. 98dB output. Housed in a tamper-proof heavy duty metal case.

Both the control unit and outdoor alarm contain rechargeable batteries which provide full protection during mains failure. Power requirement 200/260 Volt AC 50/60Hz. Expandable with door sensors, panic buttons etc. Complete with instructions. SAVE OVER £100 Usual price £228.85


— B.K.E.'s BARGAIN PRICE £128.00 + £5.00 P&P.

S.A.E. for colour brochure.

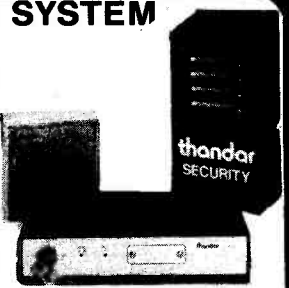

SAFGAN DT-520 DUAL TRACE OSCILLOSCOPE. New

British model. 12 month guarantee. 20 MHz Band Width.
Specification: ● CH1, CH2: 5mV/div-20V/div. ● Time Base: 1 Sec/div-100ns/div. ● XY Facility: Matched XY inputs. ● Trigger Level control ± slope selection. ● Auto, normal, TV Triggering. ● Z-Modulation. ● CAL output 1V 1KHz. ● Sweep output 0.9V. ● Graticule blue ruled 10 x 8 cm. (5" C.R.T.) Very sharp trace. ● Size: H235mm, W177mm, D360mm. ● Weight: 6.5 Kgs. ● Supply: 200-240 V. 40-60Hz. ● Price: £241.50 — FREE Securicor Delivery. Probes: X1 £8.05, X1/X10 Switched £10.93.

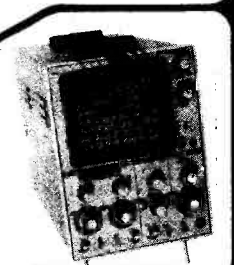

FREE SECURICOR DELIVERY

B.K. ELECTRONICS

UNIT 5, COMET WAY, SOUTHEND-ON-SEA, ESSEX, SS2 6TR



electronics today

INTERNATIONAL

NEXT
MONTH

64K DRAM

A little short on memory? ETI comes to the rescue with this project which is just the ticket for 6502 or 6800 based systems. Latching it into your system just couldn't be easier, because the DRAM board uses an EPROM to do the address decoding. No more lash-ups, just program the PROM to define where the memory goes in the micro's space. Why didn't we think of it before?

Smart NiCad Charger

Now there have been plenty of NiCad chargers that have graced these pages — but this one will automatically rejuvenate worn out cells. (Wonder if it would work on the cells in the Editor's brain?)

New Series: Audio Design


John Linsley Hood is one of the best known audio designers, and he'll be guest-writing this series for us. The emphasis will be on practicalities, with easy-to-follow explanations and simple but useful calculations. Although as little as possible be assumed about the level of expertise of the reader, there will be something here for even the most experienced of you.

Audiophile review

The Videotone Minimax speakers have provided a touch-stone in price-effective audio for many years. Now there's a Mark II version — can it be as good, or, possibly, even better? Our intrepid Audiophile investigates.

The Digger

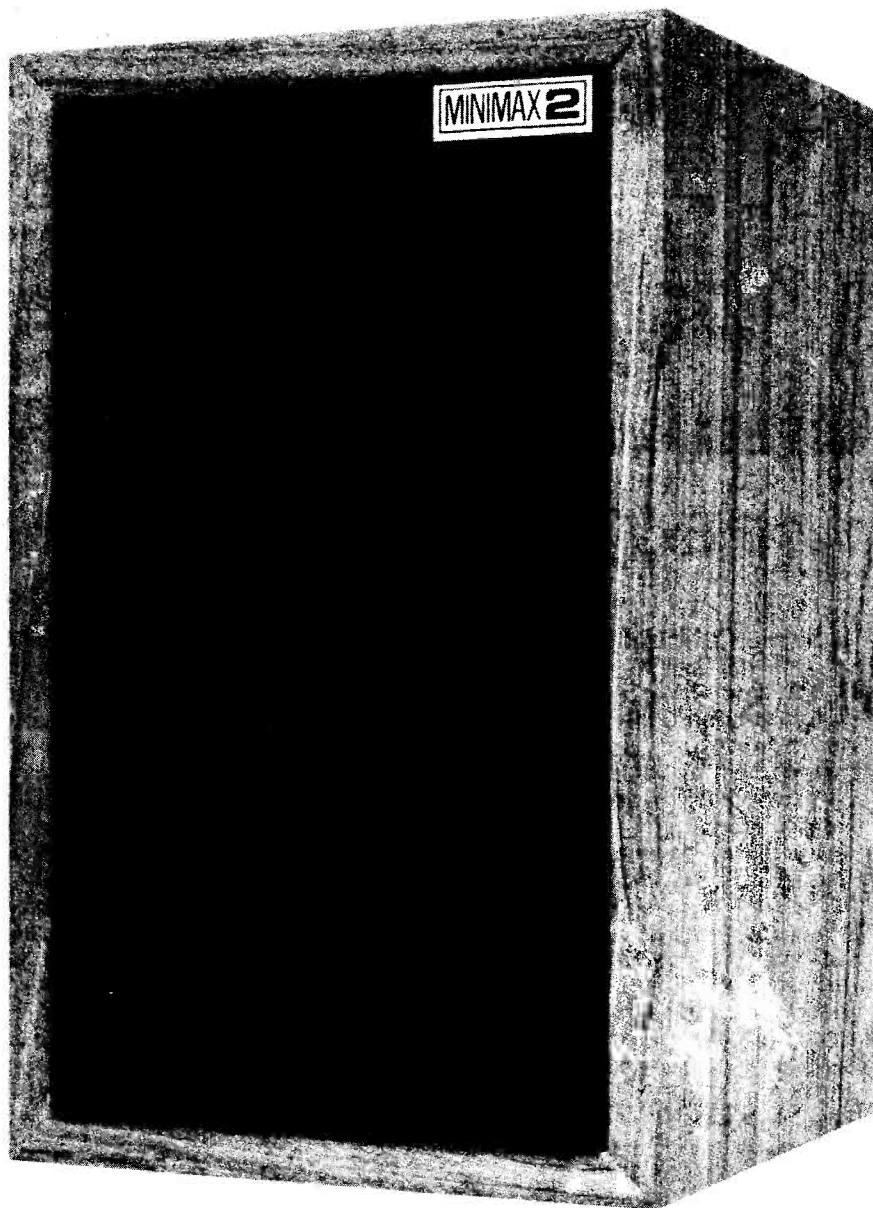No, nothing to do with our Australian colleagues, but a useful little device for digging around inside digital circuits — a logic oscilloscope trigger. The idea is very simple, really, all you do is . . . but if we told you that, you might not buy next month's mag, mightn't you?



ALL THIS AND MORE IN THE SEPTEMBER ISSUE OF ETI, ON SALE AUGUST THE 5th. PLACE YOUR ORDER NOW, OR RISK MISSING OUT!

Articles described here are in an advanced state of preparation. However, circumstances may dictate changes to the final contents.

**64K RAM
AS STANDARD!**

**POWERTRAN
COMPUTING TODAY
ELECTRONICS TODAY INTERNATIONAL**

COMBINE THEIR TALENTS TO BRING YOU

CORTEX

**SELF-
ASSEMBLY
KIT
£295
VAT
CARRIAGE FREE**



MASSES OF SOFTWARE
Pascal, Forth, Mdex, Nos, Meta
CP/M compatible QBasic, SPL,
Window, Spell + range of business
packages. Please contact:
Microprocessor Engineering Ltd,
21 Hanley Road, Southampton
SO1 5AP 0703 775482

**READY
BUILT
£395
+ VAT
CARRIAGE FREE**

CORTEX WITH OPTIONAL DISC DRIVES FITTED

16 BIT COLOUR COMPUTER

OPTIONAL EXTRAS
RS232C interface kit £9.20
Floppy disc interface £86.50
Pair of 5 1/4" disc drives & hardware kit .. £355.00
READY BUILT
CORTEX B - Basic machine + RS232C £410.00
CORTEX C - As above + disc drives £895.00
All items carriage free - prices exclusive of VAT

ALL THESE FEATURES PROVIDED AS STANDARD!

High speed 24K byte extended basic interpreter
Powerful TMS9995 16 bit microprocessor
48 bit floating point gives 11 digit accuracy
High resolution (256 x 192) colour graphics
Memory-mapped video controller for 3D simulation
Independent 16K video RAM
16 colours available on the screen together in
Graphic mode
Fast line drawing and point plotting basic commands
High speed colour shape manipulation from basic
Full textural error messages
String and Array size limited only by memory size
Real time clock included in basic
Interval timing with 10mS resolution via TIC function
Named load and save of basic or machine code programs
Auto-run available for any program
Powerful machine code monitor

Assembler & Disassembler
Auto line numbering facility
Full renumber command
Simple but powerful line editor
Buffered i/o allows you to continue executing the
program while still printing
Flexible CALL statement allows linkage to machine
code
routines with upto 12 parameters
Basic programs may contain spaces between keywords
to make programs readable without using more memory
64K RAM using latest technology 64K DRAMS
Over 34K bytes available for basic programs even when
extended basic includes IF-THEN-ELSE
Supports up to 16 output devices
Screen and cassette included as standard
Supports bit manipulation of variables from basic
Error trapping to a basic routine included
Basic supports Hexadecimal numbers

ULTRA POWERFUL 24K BASIC

COMMANDS	LOG	KEY	?	RANDOM	SGET
RUN	SOR	STATEMENTS	UNIT	ENTER	MAG
SIZE	SYS	IF	BAUD	LIST	TOF
CONT	TIC	ELSE	CALL	PURGE	TON
MON	SON	ON	DATA	NUMBER	DIM
	BIT	GOTO	READ	RENUM	DEF
FUNCTIONS	CRB	GOSUB	RESTOR	BOOT	NEW
ABS	CRF	POP	RETURN	GRAPH	END
ADR	MEM	REM	STOP	TEXT	BIT
ASC	MWD	FOR	TIME	PLOT	CRB
ATN	LEN	NEXT	WAIT	UNPLOT	CRF
SIN	MCH	ERROR	SAVE	COLOUR	MEM
COS	POS	INPUT	LOAD	CHAR	MWD
EXP	COL	PRINT	ESCAPE	SPRITE	BASE
FRA	MOD		NOESC	SHAPE	
INT	RND			SPOT	

Export enquiries to: Powertran International, Hollom Down Farm,
Lopcombe, Salisbury, Wilts SP5 1BP 0264 781545 Telex 477407 Zenmon

To: Powertran Cybernetics, Portway Industrial Estate,
Andover, Hants. SP10 3NM. 0264 64455

Please send me:

I enclose a cheque for

Please charge to my Access/Barclay Card no

Name

Address

DIGEST



Smart Cable

The SC817 SMART CABLE from KPG-Hardware House provides a simple, low cost method of interfacing 98% of RS232 equipment. Ideal for equipment salesmen and engineers the Smart Cable's unique logic senses the RS232 configuration at each end and automatically configures the

correct pin to pin connection. Providing male to male and male to female connection the Smart Cable totally eliminates the need for break out boxes, debugging cables and custom cables. KPG-Hardware House, 578-586 Chiswick High Road, London W4 5RP.

New Current Probe

The Model 711 Miniature Wide-band Current Probe manufactured by American Laser Systems, California, measures wideband current pulses without loading the circuit being tested. It induces no appreciable capacitive nor inductive effects on circuitry, therefore the signal under measurement does not change. The 711 exhibits only 0.02 ohm shunted by 4 μ H insertion impedance. The current is sensed by placing the conductor through the centre of the probe, which will accept a maximum lead diameter of No. 20 AWG. For general use as a test probe with oscilloscopes and test equipment,

Model 711 is available in a potted package with a 3ft co-ax cable and standard BNC connector. The UK agent is Dynamic Technology Limited, Zonal House, Alliance Road, Acton, London W3 0BA.

Whoops!


Stotron Ltd were just a little annoyed with us for saying that their latest catalogue was dated 1982 (Digest Shorts, June). In fact, they have now supplied us with their latest, 1983/4 catalogue, to prove that the other dropped through a worm-hole in

TOBIE Award For LCD Team

The TOBIE Award for Research Achievement has this year been won by the Physics Research team at the Royal Signals and Research Establishment, Malvern. For some years now this team has been working on the various uses of liquid crystals, including displays and addressing methods, this technology has made possible the 128 x 256 matrix liquid crystal cell developed in conjunction with Scopex Instruments Ltd., for use in the Voyager digital storage oscilloscope.

Many of the Voyager's ap-

plications are, apparently, linked to water or marine life. For instance, Water Boards find its lightness and ease of handling very useful on certain of their very remote pumping and control locations, and one of the strangest of applications to date has been for use on an expedition to the Amazon where it will be used for tests on a type of electric fish. Scopex ask: is this the dawn of a new era in ATE (Aquatic Test Equipment)? Scopex Instruments Limited, Pixmore House, Pixmore Avenue, Letchworth, Herts SG6 1HZ. Tel (04626) 72771.

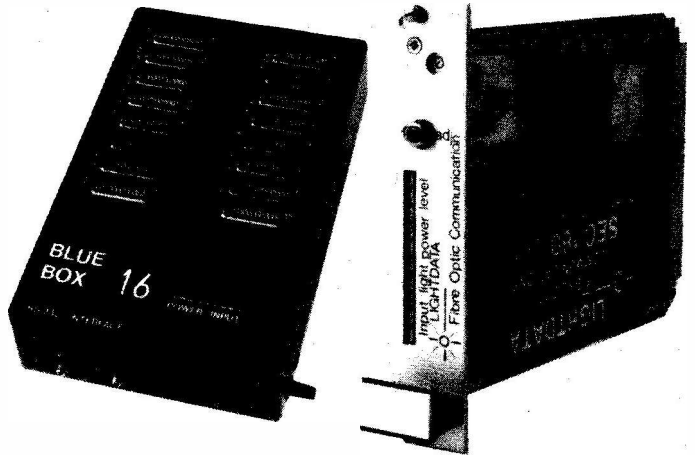

The Bead's Needs

A new range of ferrite beads manufactured by Stackpole are available exclusively to UK manufacturers from Walmore Electronics Ltd, 374 City Road, 11-15 Betterton Street, Drury Lane, London WC2H 9BS. Particularly interesting is a lead tape bead for use with automatic insertion equipment.

Ferrite beads are a simple, inexpensive, yet effective way to obtain RF decoupling, shielding and parasitic suppression without sacrificing low frequency power or signal level. Unlike conventional RF chokes, beads are compact, have no DC losses, and will not couple to stray capacity and introduce detuning or spurious oscillations. Installation of beads is easy. Simply slip over the appropriate conductor for the desired noise suppression or high frequency isolation.

Fibre Optic Links

Lightdata have two new L modules: on the left is the Blue Box 16-channel RS232 to fibre optic interface that is, apparently, simplicity itself to set up and use. It is intended to be mounted on a wall, and can provide a link over up to 1 km of optic cable. On the right is a Eurocard mounted version that requires a single 5 V supply. Lightdata, 4 Lias Road, Porthcawl, Mid Glamorgan, Wales CF36 3AH.

Energy In The Outback

A new \$250,000 Solar Energy Research Centre is to be built in Western Australia. It will be located next to the site earmarked for a proposed new technology park, which is to be established at the Western Australian Institute of Technology in Bentley.

The new centre will contain testing and monitoring equipment, computer facilities for automated data analysis, an information and display area, and office space for the staff of the Solar Energy Research Institute of Western Australia (SERIWA). Outside areas will be used to test various types of solar equipment.

the space-time continuum (that's our story, and we're sticking to it).

Stotron would also like us to point out that while they do continue to have offices in Hastings, readers should write to them at 72 Blackheath Road, Greenwich, London SE10 8DA, to obtain their copy of the catalogue.

COMPUTER WAREHOUSE

THE 'ALADDIN'S' CAVE OF COMPUTER AND ELECTRONIC EQUIPMENT

HARD DISK DRIVES

Fully refurbished Diablo/DRE Series 30 2.5 mb hard disk drive for DEC RK05, NOVA, TEXAS etc.
Front load £550.00 - Top load £295.00
PSU type ME3029 for 2 drives £125.00
DRE 44A/4000A/B 10 mb 5+5 all configurations from £995.00. Call sales office for details.

5 AMP MAINS FILTERS

Cure those unnerving hang ups and data glitches caused by mains interference. Matchbox size - Up to 5 amp 240 v load. As recommended by the ZX81 newsletter. Suppression Devices SD5A £5.95.

COOLING FANS

Keep your hot parts COOL and RELIABLE with our range of BRAND NEW professional cooling fans.
ETRI 99XU01 Dim. 92 x 92 x 25 mm. Miniature 240 v equipment fan complete with finger guard. £9.95
GOULD JB-3AR Dim. 3" x 3" x 2.5" compact very quiet running 240 v operation. NEW £6.95
BUHLER 69.11.22. 8-16 v DC micro miniature reversible fan. Uses a brushless servo motor for extremely high air flow, almost silent running and guaranteed 10,000 hr life. Measures only 62 x 62 x 22 mm. Current cost £32.00. OUR PRICE ONLY £12.95 complete with data.
MUFFIN-CENTAUR standard 4" x 4" x 1.25" fan supplied tested EX. EQUIPMENT 240 v at £8.25 or 110 v at £4.95 or BRAND NEW 240 v at £10.50. 1000's of other fans EX Stock. Call for Details. Post & Packing on all fans £1.60

DISTEL ©

The UK's FIRST free of charge, 24 hr. public access data base. Get information on 1000's of stock items and order via your computer and credit card. On line now, 300 baud. CCITT tones, full duplex, fully interactive.

DON'T MISS THOSE BARGAINS
CALL NOW, IT'S FREE

01-683 1133

8 BIT WORD - NO PARITY

7 days per week
24 hrs. per day

COMPUTER 'CAB'

All in one quality computer cabinet with integral switched mode PSU, Mains filtering, and twin fan cooling. Originally made for the famous DEC PDP8 computer system costing thousands of pounds. Made to run 24 hours per day the PSU is fully screened and will deliver a massive +5v DC at 17 amps, +15v DC at 1 amp and -15v DC at 5 amps. The complete unit is fully enclosed with removable top lid, filtering, trip switch, 'Power' and 'Run' LEDs mounted on Ali front panel, rear cable entries, etc. etc. Units are in good but used condition - supplied for 240v operation complete with full circuit and tech. man. Give your system that professional finish for only £49.95 + Carr. Dim. 19" wide 16" deep 10.5" high. Useable area 18" w 10.5" h 11.5" d. Also available LESS PSU with internal dim. 19" w, 16" d, 10.5" h, £19.95. Carriage & insurance £9.50.

8" FLOPPY DISK DRIVES

Unbelievable value the DRE 7100 8" floppy disk drives utilise the finest technology to give you 100% bus compatibility with most drives available today. The only difference being our PRICE and the superb manufacturing quality! The 7100 single sided and 7200 double sided drive accept hard or soft sectoring IBM or ANSI standard formats giving a massive 0.8 MB (7100) 1.6 MB (7200) of storage. Absolutely SHUGART, BASF, SIEMANS etc. compatible. Supplied BRAND NEW with user manual and full 90 day warranty. Carriage and insurance £9.75.
7100 Single sided £225.00 + Carr. 7200 Double sided £295 + Carr.
Optional accessories: Full technical manual £20.00 alone. £10.50 with drive. Refund of difference on drive purchase. DC and AC power connector and cable kit £8.45. 50 way IDC connector £5.50. 50 way ribbon cable £3.20 per metre.

RECHARGEABLE BATTERIES

CYCLON type D001 sealed lead acid maintenance free 2v2.5 ah, will deliver over 300 amps on short circuit!! Brand new at only £2.95

VIDEO MONITORS

12" CASED. Made by the British KGM Co. Designed for continuous use as a data display station, unit is totally housed in an attractive brushed aluminium case with ON/OFF, BRIGHTNESS and CONTRAST controls mounted to one side. Much attention was given to construction and reliability of this unit with features such as internal transformer isolated regulated DC supply, all components mounted on two fibre glass PCB boards - which hinge out for ease of service, many internal controls for linearity etc. The monitor accepts standard 75 ohm composite video signal via SO239 socket on rear panel. Bandwidth of the unit is estimated around 20 Mhz and will display most high def graphics and 132 x 24 lines. Units are secondhand and may have screen burns. However where burns exist they are only apparent when monitor is switched off. Although unguaranteed all monitors are tested prior to despatch. Dimensions approx. 14" high x 14" wide by 11" deep. Supplied complete with circuit. 240 volt AC operation. ONLY £45.00 PLUS £9.50 CARR.

24" CASED. Again made by the KGM Co with a similar spec as the 12" monitor. Originally used for large screen data display. Very compact unit in lightweight alloy case dim. 19" H x 17" D x 22" W. All silicon electronics and composite video input make an ideal unit for schools, clubs, shops etc. Supplied in a used but working condition. ONLY £55.00 PLUS £9.50 CARR. & INS.

14" COLOUR superb chassis monitor made by a subsidiary of the HITACHI Co. Inputs are TTL RGB with separate sync. and will plug direct into the BBC micro etc. Exceptional bandwidth with good 80 col. definition. Brand new and guaranteed. Complete with full data & circuit. 240 v AC working. Dim. 14" x 13" x 13". ONLY £199.00 PLUS £9.50 CARR.

SUPER DEAL? NO - SUPER STEAL!!

The FABULOUS 25CPS TEC Starwriter

Daisy wheel printer at a fraction of its original cost.

BRAND NEW AT ONLY £499+ VAT

Made to the very highest spec the TEC Starwriter, FP1500-25 features a heavy duty die cast chassis and DIABLO type print mechanism giving superb registration and print quality. Micro-processor electronics offer full DIABLO/QUME command compatibility and full control via CPM Wordstar etc. Many other features include bi directional printing, switchable 10 or 12 pitch, full width 381 mm paper handling with upto 163 characters per line, friction feed rollers for single sheet or continuous paper, internal buffer, standard RS232 serial interface with handshake. Supplied absolutely BRAND NEW with 90 day guarantee and FREE daisy wheel and dust cover. Order NOW or contact sales office for more information. Optional extras: RS232 data cable £10.00. Tech manual £7.50. Tractor feed £120.00. Spare daisy wheel £3.00. Carriage & Ins. (UK Mainland) £10.00.



Save over £400

TELETYPE ASR33 I/O TERMINALS

FROM £195 + CAR + VAT
Fully fledged industry standard ASR33 data terminal. Many features including ASCII keyboard and printer for data I/O auto data detect circuitry, RS232 serial interface, 110 baud, 8 bit paper tape punch and reader for off line data preparation and ridiculously cheap and reliable data storage. Supplied in good condition and in working order
Options: Floor stand £12.50 + VAT
KSR33 with 20ma loop interface £125.00 + Sound proof enclosure £25.00 + VAT

SOFTY 2

The amazing SOFTY2. The complete "toolkit" for the open hard software surgeon. Copies, Displays, Emulates ROM, RAM and EPROMS of the 2516, 2532 variety. Many other features include keyboard, UHF modulator. Cassette interface etc. Functions exceed capabilities of units costing 7 times the price! ONLY £169.00 pp £1.95 Data sheet on request

DATA MODEMS

Join the communications revolution with our range of EX TELECOM data modems. Made to most stringent spec and designed to operate for 24 hrs per day. Units are made to the CCITT tone spec. With RS232 i/o levels via a 25 way 'D' skt. Units are sold in a tested and working condition with data. Permission may be required for connection to PO lines.
MODEM 13A compact, async, same size as telephone base. Up to 300 baud, full duplex over 2 wires, but call mode only £75.00
MODEM 2B/C Fully fledged, up to 300 baud async, ANSWER & CALL modes, auto answer, auto switching, ideal networks etc. Just 2 wire connection to comms line. £85.00
MODEM 20-1 Compact unit for use with PRESTEL or full duplex 2 wire link 75 baud transmit - 1200 baud receive. Auto answer. £130.00
MODEM 20-2 same as 20-1 but 75 baud receive 1200 baud transmit. £130.00
MODEM 20-3 Made for data rates up to 1200 baud in full duplex mode over 4 wire circuit or half duplex mode over 2 wires. £130.00 Carriage. 13A £4.50. 2B/C & 20 £9.50.
DATA PUMP MODEM compact unit upto 1200 baud full duplex over 4 wires or half duplex over 2 wires. BELL specification with data i/o via RS232 25 way D socket, remote test etc. 240 v operation. Supplied complete with data £85.00 carr. £4.50.

For more information or details of other types of ex. stock modems contact sales office.

8" WINCHESTER price SLASH

Worldwide purchasing brings you two amazing Winchester SCOOPS at prices that will likely NEVER be repeated.
BASF 6172 8" 24 Mb. Complete unit consists of micro-processor controlled logic on 3 PCBs for all read/write and servo control functions. Fast data transfer is by the BASF 'Disk Bus' interface on a single 40 way multiplexed i/o bus. Units have been carefully removed from believed working equipment, but at the staggering price of ONLY £99.00 are sold without guarantee. Supplied complete with 200 page + tech. Manual. Dim 45 x 22 x 11 cm. DC requirements +5v, +12v, +24v. Carriage and ins. £10.00
£100 Bus 19 Mb. Subsystem. A cancelled order and change of policy by a major British disk drive manufacturer enables us to offer you 'last year's model' at a plug in and ready to go SUPER LOW PRICE. Our own custom controller plugs direct into the S100 bus and will control 2 disk drives, offering a total storage of OVER 36 Mbs! and at data transfer rates in excess of 7 Mb/sec seeing is believing!! Supplied complete with user configurable BIOS etc. Save a fortune, Limited quantity only.
3100 19 Mb. Disk drive £499.00 PSU unit £165.00
CD1100 controller & BIOS £345.00 PSU extension cable £9.95
Full tech Manual £20.00
Special SUBSYSTEM prices. 1 x 3100 disk + PSU + Controller £799.00
or 2 x 3100 disks + 2 PSU + Controller £1295.00
All prices + VAT and carriage. 90 day guarantee. Data on request.

ALL PRICES PLUS VAT

SEMICONDUCTOR 'GRAB BAGS'

Mixed Semis amazing value contents include transistors, digital, linear, I.C.'s triacs, diodes, bridge recs, etc. etc. All devices guaranteed brand new full spec, with manufacturer's markings, fully guaranteed, 50 + £2.95 100 + £5.15.
TTL 74 Series A gigantic purchase of an "across the board" range of 74 TTL series I.C.'s enables us to offer 100+ mixed "mostly TTL" grab bags at a price which two or three chips in the bag would normally cost to buy. Fully guaranteed all I.C.'s full spec. 100 + £6.90 200 + £12.30 300 + £19.90

CALLING DEC USERS

Brand new and boxed

RSX11M 3.2 Documentation kits, fill 3 feet of your bookshelf! Under half price only £120.00 carr. £6.50 0 vat on manuals.
We are always keen to buy all types of used or surplus DEC equipment.

Display
-ELECTRONICS-

All prices quoted are for U.K. Mainland, paid cash with order in Pounds Sterling PLUS VAT. Minimum order value £2.00. Minimum Credit Card order £10.00. Minimum BONA FIDE account orders from Government depts, Schools, Universities and established companies £20.00 Where post and packing not indicated please ADD 60p + VAT Warehouse open Mon-Fri 9.30 - 5.30. Sat. 10.15 - 5.30. We reserve the right to change prices and specifications without notice. Trade, Bulk and Export enquiries welcome.

64-66 Melfort Road, Thornton Heath, Near Croydon, Surrey
01-689 7702 - 01-689 6800 Telex 27924




The Phone That Thinks It's A Clock

The new Clock Radio Phone from Fidelity Radio, the CRP 100, is a compact unit incorporating the three facilities of radio, alarm clock and telephone. Operation is precisely the same as a conventional clock radio but with an automatic cut off when the telephone receiver is lifted. British Telecom approval is already applied for and the CRP 100 can be installed by connection to the mains and a standard British Telecom socket. The Clock Radio Phone is expected to retail at around £69, and should be in the shops by September.

Also from Fidelity is a new colour television chassis design, the ZX 3000. The chassis is smaller, more advanced with reduced component volume and covers eight programme channels. Advantages across the range include greater reliability, less weight and an even more economical price for high quality vision and sound reproduction.

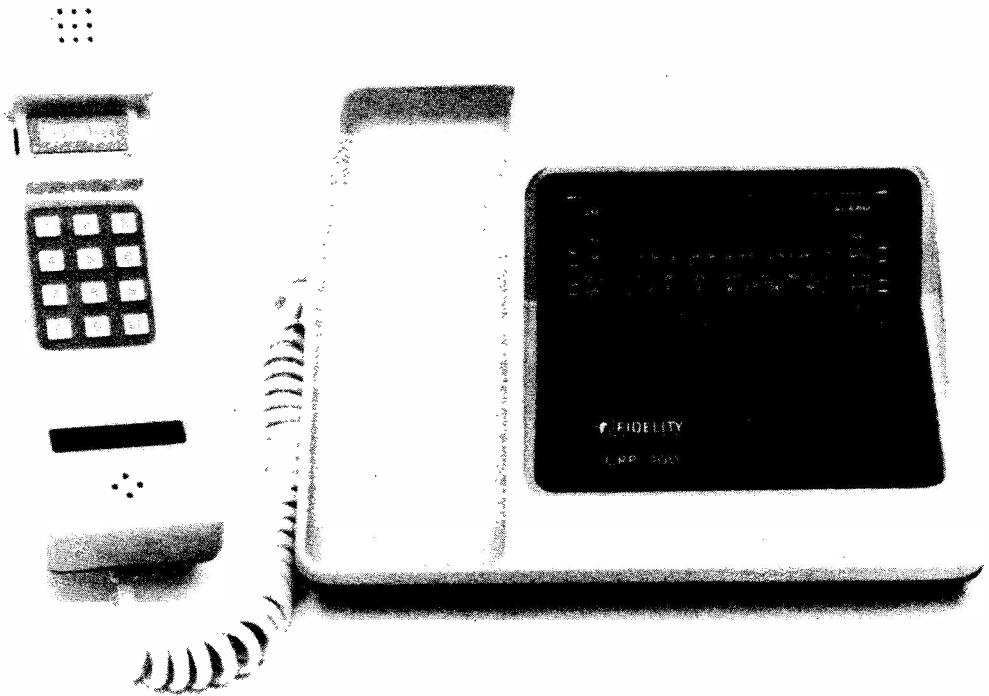You'll find the new chassis in some new models, the CTV 22T and CTV 20T Teletext models, the CTV 22R remote control model and a new 14 inch colour monitor. The existing CTV 20R and CTV 14S portable will continue in the range but with the new chassis.



Micros Go Down The Drain

Intel Corp has introduced its "Data Pipeline" hardware and software designed to link mainframe computer data bases with personal computers. The Data Pipeline is built around Intel's Data-Base Information System, iDIS 86/735, a microcomputer-based "traffic-manager" that interprets, stores and distributes mainframe data to and from terminals and personal computers. The Data Pipeline uses an enhanced version of Intel's System 2000 Data-Base Management System (DBMS). System 2000 currently handles data storage and retrieval in hundreds of large mainframe computer installations.

New Data Pipeline extensions to System 2000 provide a relational data-base capability, graphics and a fourth-generation software architecture, System 2000 On-Line Operation (SOLO).

Intel also has broadened its 700 family of Data-Base Information Systems with the iDIS 86/730, an iDIS version aimed at original equipment manufacturers and large-volume end users. Intel Corporation S.A., Rue du Moulin a Papier, 51, Boite 1, B-1160 Brussels, Belgium.

Speedy Prototypes

Computing Techniques (Mfg) Limited has introduced a fast and economic service on operational amplifiers designed and built to special requirements. Now, all but the most exacting orders can be met in two weeks or less. Many orders can be turned round in as little as seven days, and this British company is offering prices at up to 25% lower than those quoted by other major


manufacturers.

The service should prove of great interest to small and medium quantity users, who often experience difficulty in easily, or economically, meeting specifications when selecting standard linear integrated circuits from the major suppliers. Computing Techniques supplies a complete, packaged operational amplifier which it guarantees will

meet the customer's specification, however tight. Computing Techniques (Mfg) Ltd, Brookers Road, Billingshurst, West Sussex RH14 9RZ.

Please . . .

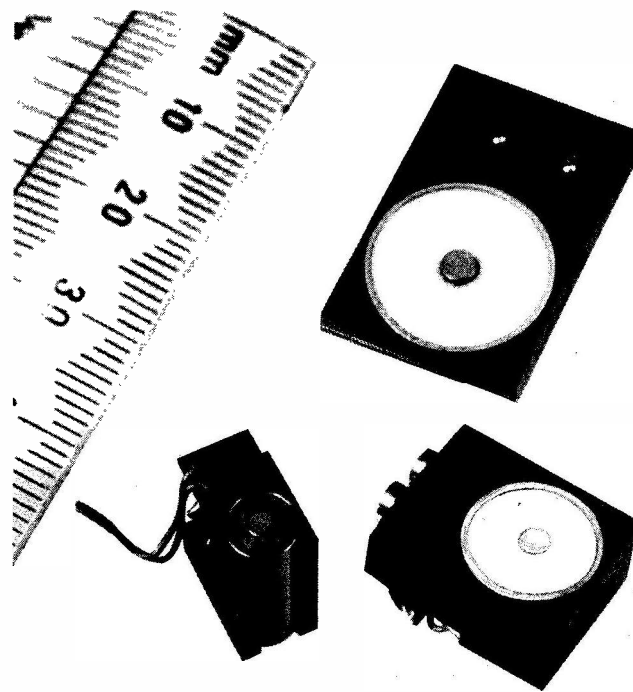At the time of writing, ETI is still without a replacement for Peter Green, our former deputy editor turned Computing Today. So please, keep your enquiries of us to a minimum, and follow the guidelines on page 70.



A Little Pull Helps

Miniature solenoids for use where space is at a premium have been introduced by Magnetic Components to augment its established recording head capability. Manufactured to meet manufacturers' specific requirements, the units are expected to have particular application to electronic security locks, access controls, low power system controllers, printer mechanisms, electronic camera shutters, etc.

Typical is one producing a latch pull force of 150 gms when 1.9 volts D.C. is applied to the 75 ohms coil. In addition to the solenoid component, MCL provides methods of controlling the unlatching force so as to give a higher level of release time repeatability; this is achieved by a specially developed keeper and/or the use of 'kick-off' electronic circuitry. Magnetic Components Limited, Bridge Wharf Industrial Estate, Chertsey, Surrey KT16 8LJ.

electronize

AUTO-ELECTRONIC PRODUCTS

KITS OR READY BUILT

TOTAL ENERGY DISCHARGE ELECTRONIC IGNITION



IS YOUR CAR

AS GOOD AS IT COULD BE ?

- ★ Is it **EASY TO START** in the cold and the damp? Total Energy Discharge will give the most powerful spark and maintain full output even with a near flat battery.
- ★ Is it **ECONOMICAL** or does it "go off" between services as the ignition performance deteriorates? Total Energy Discharge gives much more output and maintains its performance between services.
- ★ Has it **PEAK PERFORMANCE** - is it flat at high and low revs. where the inductive system is marginal? Total Energy Discharge gives a most powerful spark to ride the engines maximum even with low revs.
- ★ Is the **PERFORMANCE SMOOTH** - the more powerful spark of Total Energy Discharge eliminates the "misses" whilst an electronic filter smooths out the effects of contact bounce etc.
- ★ Do the **PLUGS and POINTS** always need changing to bring the engine back to life? Total Energy Discharge eliminates contact arcing and erosion, removing the heavy electrical load. The timing stays "spot on" and the contact condition doesn't affect the performance over. Larger plug gaps can be used, even wet or badly fouled plugs can be fired with this system.
- ★ **TOTAL ENERGY DISCHARGE** is a unique system and the most powerful on the market - 3 1/2 times the power of inductive systems - 3 1/2 times the energy and 3 times the duration of ordinary capacitive systems. These are the facts:
Performance at only 6 volts (max. supply 16 volts)
SPARK POWER — 140W, SPARK ENERGY — 36mJ
SPARK DURATION — 500µs, STORED ENERGY — 135mJ
LOADED OUTPUT VOLTAGE
50pF load — 38kV, 50pF + 500k — 26kV
We challenge any manufacturer to publish better performance figures. Before you buy any other make, ask for the facts, its probably only an inductive system. But if an inductive system is what you really want, we'll still give you a good deal.
- ★ **ALL ELECTRONIZE** electronic ignitions feature:
EASY FITTING, STANDARD/ELECTRONIC CHANGEOVER SWITCH, STATIC TIMING LIGHT and DESIGNED IN RELIABILITY (14 years experience and a 3 year guarantee).
- ★ **IN KIT FORM** it provides a top performance system at less than half the price of comparable ready built units. The kit includes: pre-drilled fibreglass PCB, pre-wound and varnished ferrite transformer, high quality 2µF discharge capacitor, case, easy to follow instructions, solder and everything needed to build and fit to your car. All you need is a soldering iron and a few basic tools.

Most **NEW CARS** already have electronic ignition. Update **YOUR CAR**

PROTECT YOUR CAR WITH AN ELECTRONIZE ELECTRONIC ALARM



- ★ **2000 COMBINATIONS** provided by an electronic key - a miniature jack plug containing components which must match each individual alarm system. (Not limited to a few hundred keys or a four bit code).
- ★ **60 SECOND ALARM PERIOD** flashes headlights and sounds horn, then resets ready to operate again if needed.
- ★ **10 SECOND ENTRY DELAY** allows owner to dis-arm the system, by inserting the key plug into a dashboard mounted socket, before the alarm sounds. (No holes in external bodywork, fiddly code systems or hidden switches). Re-closing the door will not cancel the alarm, before or after it sounds, the key plug must be used.
- ★ **INSTANT ALARM OPERATION** triggered by accessories or bonnet/boot opening.
- ★ **30 SECOND DELAY** when system is armed allows owner to lock doors etc.
- ★ **DISABLES IGNITION SYSTEM** when alarm is armed.
- ★ **IN KIT FORM** it provides a high level of protection at a really low cost. The kit includes everything needed, the case, fibreglass PCB, CMOS IC's, random selection resistors to set the combination, in fact everything down to the last nut and washer plus easy to follow instructions.

**FITS ALL 12 VOLT NEGATIVE EARTH VEHICLES.
SUPPLIED COMPLETE WITH ALL NECESSARY LEADS
AND CONNECTORS PLUS TWO KEY PLUGS**

**Don't Wait Until Its too Late ~
Fit one NOW!**

fill in the coupon and send to:

ELECTRONIZE DESIGN Dept D · Magnus Rd · Wilnecote · Tamworth · B77 5BY · tel 0827 281000

TOTAL ENERGY DISCHARGE (6 or 12 volt negative earth)

- Assembled ready to fit **£26.70 £19.95**
- D.I.Y. parts kit **£15.90 £14.95**

TWIN OUTPUT for cars and motor cycles with dual ignition

- Twin, Assembled ready to fit **£36.45 £29.95**
- Twin, D.I.Y. parts kit **£24.55 £22.95**

INDUCTIVE DISCHARGE (12 volt only)

- Assembled ready to fit **£15.95 £12.75**


Prices include VAT.

P+P £1-00 (UK)

CAR ALARM

- Assembled ready to fit **£37.95**
- D.I.Y. parts kit **£24.95**

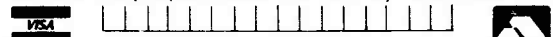I enclose cheque/postal order OR debit my Access/Visa card



Name _____

Address _____

Code _____

D

What Is It?

We know what it is — but do you? We get all sorts of obscure objects passing under our noses here at ETI, but this particular one seems to mark a new all-time height in enigma.

Actually, it's use is pretty boring, so we're not giving any prizes for the correct answer. However, the most ingenious incorrect answer will get some prize, though what it is, we haven't decided. It could be a guided tour of the ETI office, or it may even be one of these things — you'll have to wait and see.


Filters For CD

RIFA have introduced a new series of hybrid active filters, which have been designed for anti-aliasing applications in equipment such as digital audio systems. Constructed in RIFA's thick film process, the PBA 3167 and PBA 3179 hybrid active filters feature an extremely flat response over their operational passband. Included in their circuitry is a group-delay equalising network, which effects a constant group-delay response within $+10\mu\text{s}$ up to 19KHz in the case of the PBA 3167, and up to 13.5 KHz for the PBA 3179.

Cut off frequencies are specified as 20KHz (3167) and 15KHz (3179). Accordingly, the filters are ideally suited for applications in digital audio systems having sampling frequencies from 48 to 50KHz, or 32KHz. RIFA AB, Market Chambers, Shelton Square, Coventry.

Noisy Fault Locator

A new British manufactured and designed portable Audio/Visual faults locator is now available from Antron Electronics Ltd, Hamilton House, 39 Kings Road, Haslemere, Surrey GU27 2QA. Codenamed Toneohm 700, the instrument is used to locate short and partial short circuits caused by solder bridges, poor etching, partial device failure, i.e. substrate shorts, leaking capacitors etc., by tone or meter readout without removing com-

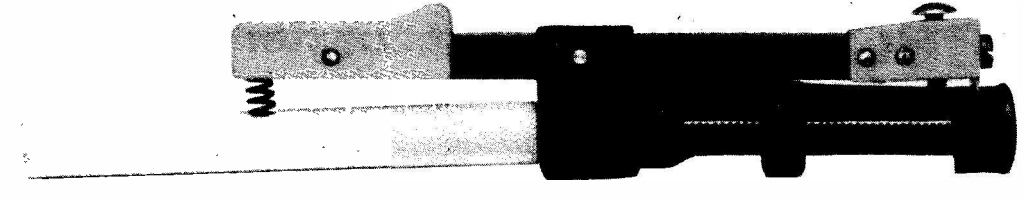

More Motorola Manuals

Motorola have been busy scribbling away, and the following new books bring the total number of Motorola technical publications up to 22: B012A — 8 bit Microprocessor Data Manual; B012B — 16 bit Microprocessor Data Manual; B001 — A/D and D/A Conversion Manual; B0015 — Switchmode and TMOS Power

Transistors; B038 — Linear/Switchmode Voltage.

These are available from Motorola Distributors, or write to

Motorola's European Literature Centre (at Milton Keynes) for the leaflet, describing each publication and detailing prices. Motorola Semiconductors, 88 tanners Drive, Blakelands, Milton Keynes.

Accurate Robot

Zehntel's Series 600 Robotic Board Handling System, the first fully operational robot aid for automatic testing equipment, is described in a 4 page brochure. The RBHS is easily programmed and has a unique 6 axis motion. Positioning accuracy is 0.022", believed to be the best available.

As well as loading and unloading boards at the test head, the RBHS can also be used for light mechanical tasks connected with testing, such as operating switches etc. It will also handle simple assembly tasks if required. Zehntel Limited, 62 Tanners Drive, Blakelands, Milton Keynes MK14 5BP.

Shorts

- United Components Ltd, Unit 5, Wye Estate, London Road, High Wycombe, Bucks HP11 1LH now carry stocks of Clare Reed and mercury wetted relays, as well as many other GI and related companies' products.

- Any manufacturer wishing to exhibit at the fourth Middle East Electricity and Electronics Exhibition in Kuwait in January 1984 should contact the British Electrical and Allied Manufacturers' Association (BEAMA) at 8 Leicester Street, London WC2H 7BN.

- Peripheral Hardware Ltd, Unit 13, Monkspath Industrial park, Highlands Road, Shirley, West Midlands B90 4NY have been appointed as an authorised dealer for Epson printers and personal computers.

- Apples have fallen. A new 256K Apple III will now cost a mere £2,395 (it was £2,869); the 128K Apple III is no longer available. Apple Computer (UK) Ltd, Eastman Way, Hemel Hempstead, Herts HP2 7QH.

- AKG are setting up a studio sound award, for professional and non-professional sound engineers. Details from AKG Acoustics Ltd, 191 The Vale, London W3 7QS.

- Instem Computer Systems Limited, formerly known as Kratos, has launched a new software programme for the Hewlett Packard HP-86 microcomputer to perform industrial monitoring and control functions using Instem's range of Link-On input/output stations. Instem Computer Systems Limited, Walton Industrial Estate, Ston, Staffordshire, ST15 0LT.

- One of the consequences of the general election being called at fairly short notice was the fall of a bill that would have made it illegal to sell "any machine capable of reproducing a sound recording . . . where the naute of the machine is such that the primary or substantial use to which it will be likely to be put is likely to result in the unauthorised making of any record embodying the recording . . .". Sounds like a cassette deck they were talking about, doesn't it?

- Thorn EMI have just released a leaflet describing a new range of rubidium caesium photocathode photomultiplier tubes. Contact the Sales Department, Thorn EMI Electron Tubes Limited, Bury Street, Ruislip, Middlesex HA4 7TA.

- Belling Lee have published a comprehensive 64 page catalogue of their range of RFI filters for up to 800 amps. Belling Lee, 540 Great Cambridge road, Enfield, EN1 3QU.

- Cotswold Electronics, Unit T1, Kingsville road, Kingsditch Trading Estate, Cheltenham GL51 9NX have issued a leaflet describing their "budget range" of toroidal mains transformers.

- Tasbian, the automated electronic assembly plant near Plymouth, have also issued a leaflet, describing their design, manufacturing and test facilities. Tasbian Ltd, 2/3 Burrington Way, Plymouth, Devon PL5 3LS.

- You'll no doubt be pleased to hear that the 20 companies involved in the development of magnetic disc stills cameras have reached agreement of standardisation of the disc. This should prevent the usual problem of a multiplicity of standards confusing the consumer, such as happened in video.


Twin Stripper

AB Engineering Company has developed a unique new cable stripper for the fast and safe removal of outer sheathing from twisted pair coaxial cables. Also suitable for other cables of irregular cross section, the new Coax-3 incorporates a spring loaded cutting head which when revolved accurately follows contours to produce a precise circumferential cut to a pre-determined depth. The operator then simply twists the cutting blade through 90 degrees and the outer sheathing is separated along the axis of the cable for ease of removal. AB Engineering Co., Timber Lane, Woburn, Milton Keynes MK17 9PL.

ponents or cutting tracks.

The instrument has four ranges to allow resistance measurement up to 20k and D.C. voltages between $\pm 20\text{V}$ to be made, so giving a complete range of diagnostic capability in one instrument. Kelvin needle probes are used for fault finding and are protected against accidental connection up to $\pm 30\text{V}$.

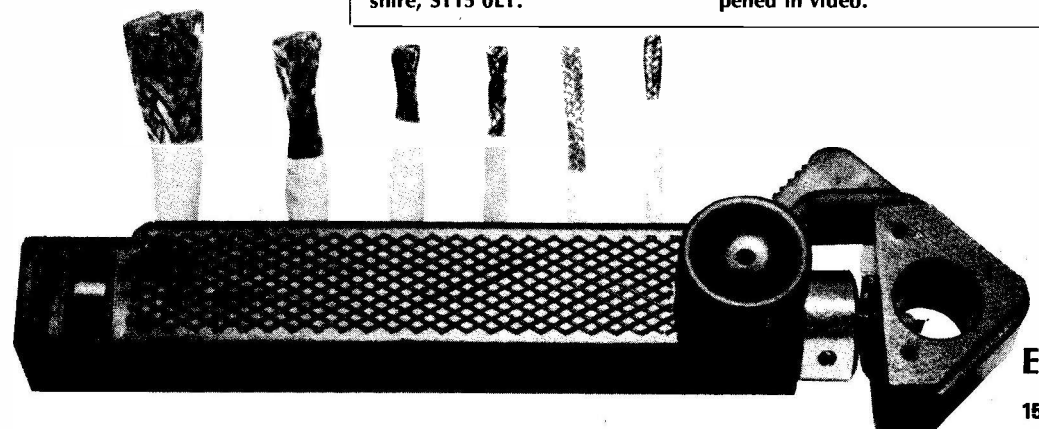
The instrument can also source a test voltage to stimulate circuit under test, with a maximum output voltage of 0.55V and maximum output current 150mA.



BBC
OFFICIAL
DEALER

Micro Computer System

Please phone for availability

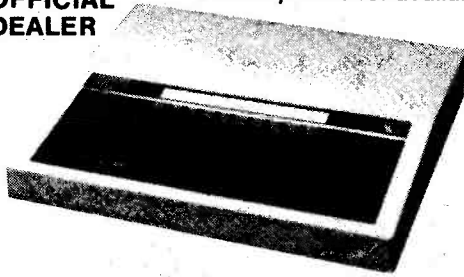

WORD PROCESSOR 'VIEW'
16K ROM £52

TELETEXT ADAPTOR
£195.00

BBC Model B £399
including VAT plus £8 carr.
Model A to Model B
Upgrade kit **£50**
Fitting charge **£15**
Individual upgrades
also available

WORDWISE
8K ROM **£39**
TORCH Z80
DISC PACK **£780**

FLOPPY DISC INTERFACE
Incl. 1.2 operating system
£95 + £20 installation

BBC FLOPPY DISC DRIVES
Single drive 5¼" 100K **£230 + £6 carr.**
Dual drive 5¼" 800K **£699 + £8 carr.**

BBC COMPATIBLE DRIVES
These drives are self powered and
supplied in BBC matching colour cases.
SINGLE 100K **£180**; 200K **£250**;
400K **£330**
DUAL 200K **£350**; 400K **£475**;
800K **£590**

Drive Cables: Single **£8** Dual **£12**
Disc Manual & Formatting Diskette **£17.50**

Phone or send for our BBC leaflet

BUSINESS, EDUCATION & FUN SOFTWARE IN STOCK

CASSETTE RECORDER

BBC Compatible Cassette Recorder
with Counter and Remote Control
£26.50 + £1.50 carr.
SANYO Data Recorder Model DR101
£39.50 + £1.50 carr.
Cassette Leads **£3.50**
Computer Grade Cassette
£0.50p each £4.50 for 10 + £1 carr.

MONITORS


MICROVITEC 1431 14" Colour Monitor.....**£249 + £8 carr.**
MICROVITEC 2031 20" Colour Monitor.....**£319 + £8 carr.**
KAGA 12" RGB Monitor..... **£255 + £8 carr.**
Lead for KAGA/SANYO RGB **£10**
SANYO 12" Hi Res Green Monitor ... **£99 + £6 carr.**
SANYO Hi Res RGB Monitor **£445 + £8 carr.**

BBC BOOKS

Basic on BBC **£5.95**
30 Hour Basic **£5.95**
Programming the BBC Micro **£6.50**
BBC Micro An Expert Guide **£6.95**
Assy. Lang. Prog for BBC **£8.95**
6502 Machine Codes for Beginners
£6.95 (No VAT)

NEC PC 8023 BE-C

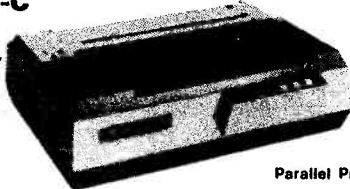Features include:
80 cols 100CPS,
Bi-Directional, Logic seeking,
Proportional Spacing,
Forward & Reverse Line
Feed, Hi-Res and Block
Graphics, International
and Greek characters,
Auto-Underline,
Friction & Tractor,
2K Buffer, Cartridge Ribbon.



£345 + £8 carr.

PRINTERS

SEIKOSHA GP 100A

80 Cols 30 CPS
Full ASCII e GRAPHICS
10" Wide paper

Now only **£180+ £6 carr.**
GP250A £235 plus £8 carr.

Parallel Printer lead for BBC/Atom to most printers **£13.50**
Variety of interfaces, ribbons in stock
2,000 fan fold sheets 9½" x 11" **£13.50 + £3 p & p**

EPSON RX80 and FX80

RX80 100CPS 80COL
Tractor Feed **£298**

FX80 160CPS 80COL
F&T Feed **£389**

MX100 F/T3 **£425**

(Carr./printer £8)
Full specification
on request

RUGBY ATOMIC CLOCK

This Z80 micro controlled clock/calendar
receives coded time data from NPL Rugby.
The clock never needs to be reset. The
facilities include 8 independent alarms and for
each alarm there is a choice of melody or
alternatively these can be used for electrical
switching. A separate timer allows recording
of up to 240 lap times without interrupting
the count. Expansion facilities provided.
See July/August ETI for details. Complete Kit
£145 + £2.00 p&p

ID CONNECTORS

Header	Recep-Plug	Edge	Conn
10 way	90	85	120p
20 way	145	125	195p
26 way	175	150	240
34 way	200	180	320
40 way	220	190	340
50 way	235	200	390

D-CONNECTORS

No of Ways	Male	Female
9	80p	105p
15	150p	210p
25	250p	365p
37	385p	500p

TEXTTOOL ZIF

Sockets	24 pin £5.75
	28 pin £8.00
	40 pin £9.75

DIL SWITCHES

4 way	70p
6 way	85p
8 way	90p
10 way	140p

CONNECTOR SYSTEMS

JUMP LEADS

4in Ribbon Cable with headers	14 pin	16 pin	24 pin	40 pin	
1 end	145p	165p	240p	390p	
2 ends	210p	230p	340p	540p	
24in Ribbon Cable with sockets	20 pin	26 pin	34 pin	40 pin	
1 end	160p	200p	280p	300p	
2 ends	290p	370p	480p	525p	
24in Ribbon Cable with D. Conn	25 way	Male	500p	Female	560p

AMPHENOL CONNECTORS

36 way plug Centronics Parallel	Solder £5.25	IDC £4.95
36 way socket Centronics Parallel	Solder £5.50	IDC £5.20
24 way plug IEEE	Solder £5.00	IDC £4.75
24 way socket IEEE	Solder £5.00	

RIBBON CABLE

Grey/meter	Price
10 way	40p
16 way	60p
20 way	85p
26 way	120p
34 way	160p
40 way	180p
50 way	200p
64 way	280p

TEST CLIPS

14 pin	275p
16 pin	£3
40 pin	£6

EURO CONNECTORS

DIN 41617	21 way	160p	165p
	31 way	170p	170p
DIN 41612	2x32 way St. Pin	220p	275p
	2x32 way Ang. Pin	275p	320p
	3x32 way St. Pin	260p	300p
	3x32 way Ang. Pin	375p	350p

EDGE CONNECTORS

0.1" 0.156"	Price
2x18 way	140p
2x22 way	190p
2x23 way	175p
2x25 way	225p
2x28 way	190p
1x43 way	260p
2x43 way	395p
1x77 way	600p
5100 Con n	600p

MICROTIMER

6502 Based Programmable clock timer with
★ 224 switching times/week cycle
★ 24 hour 7 day timer
★ 4 independent switch outputs directly interfacing to thyristor/triacs
★ 6 digit 7 seg. displays to indicate real time, ON/OFF and Reset times
★ Output to drive day of week switch and status LEDs.
Full details on request. Price for kit **£57.00**

DISC DRIVES FOR THE FORTH COMPUTER

5¼" Teac FD55 Slim Line Mechanisms
FD55A 40 track SDD 250kbytes unformatted bare: **£135** Cased: **£155**
2 x FD55A 40 track SSDD 500kbytes unformatted cased + psu **£350**
FD55E 80 track SSDD 500kbytes unformatted bare: **£180** Cased: **£205**
2 x FD55E 80 track SSDD 1 Mbyte unformatted cased + psu **£475**
5¼" Mitsubishi M4853 Slim Line mechanism
80 track DSDD 1 Mbyte unformatted bare: **£225** Cased: **£245**
2 x M4853 2 Mbytes Cased + psu **£590**
Single drive cable **£8** Dual Drive cable **£12**
Other parts for FORTH COMPUTER available send SAE for details.

SOFTY II INTELLIGENT PROGRAMMER

The complete micro processor development system for Engineers and Hobbyists. You can develop programs, debug, verify and commit to EPROMS or use in host computer by using softy as a romulator. Powerful editing facilities permit bytes, blocks of bytes changed, deleted or inserted and memory contents can be observed on ordinary TV. Accepts most +5v Eproms. Softy II complete with PSU, TV Lead and Romulator lead **£169**

SPECIAL OFFER

2532	350p
2732	350p
2764-25	450p
27128-25	£25
4116-2	80p
4164-2	450p
6116P	350p

BOOKS (No VAT p&p £1)

CRT Controller H/Book	£8.50
Programming the Z80	£11.50
Z80 Microcomp. handbook	£6.95
Programming the 6502	£10.25
6502 Assy. Lang.	£12.10
6502 Applications	£10.20
6502 Software Design	£9.05
6502 Games	£10.52
Large selection of databooks, inter-facing books, books on BBC, etc in stock. As for our list.	

UV ERASERS

UV1B up to 6 Eproms **£47.50**
UV1T with Timer **£80.00**
UV140 up to 14 Eproms **£61.50**
UV141 with Timer **£78.00**
(Carr £2/eraser)
All erasers are fitted with mains switches and safety interlocks

E.T.I. PROJECTS

Semiconductors inc. I.C., Transistors, Displays, Connectors and Sockets for most projects are stocked by us.

PLEASE SEND SAE FOR PRICE LIST

One of the ironies of life is that the largest single factor in determining how well any sound system performs has nothing to do with the system itself: it is the room.

Now you could adopt an all-or-nothing approach and take a pneumatic drill to your listening room, to get rid of all those resonances, throw out all the furniture, because it's too absorbent, and keep everyone else out of the listening area, because clothes absorb sound too (and bodies, so it's no good asking your friends to go naked). However this could lead to a certain amount of domestic unrest, and anyway, would be impractical at a large scale concert.

A less radical approach that has fewer disadvantages is to tailor the response of the electronics so that the overall response of the audio system plus the room is neutral. This is most usually done with a graphic equaliser.

While octave equalisers do have some use, most equalisers supplied for domestic use are pure gimmickry. If you're taking your equalisation seriously, the only real option is a $\frac{1}{3}$ -octave device, which, by pure coincidence, is what we're about to describe here.

The ETI $\frac{1}{3}$ -octave equaliser is of sufficient quality not to seriously degrade the sound of a high quality system. It should be noted however, that the use of any $\frac{1}{3}$ -octave equaliser will affect the performance of the system simply because it is in circuit. Each of the filters has a

$\frac{1}{3}$ OCTAVE EQUALISER

relatively high Q and will therefore cause significant modification to the overall phase linearity as well as the frequency response when cut or boost is applied. I have seen many otherwise high quality systems degraded significantly by the excessive use of $\frac{1}{3}$ -octave equalisers and we do not recommend the incorporation of these units into a high quality system unless a specific need is apparent. Nevertheless, when modification of the frequency response is required, no matter how drastic or how modest, a $\frac{1}{3}$ -octave graphic equaliser is an almost ideal way of doing this.

Each channel of the equaliser is controlled by a separate slider potentiometer so the array of pots gives an approximate indication of the response inserted.

Design

Each filter is formed by a series resonant network incorporated into the feedback loop of a high quality operational amplifier. In this case we have used the NE5534N.

'Gyrators' are used to simulate

In order to illustrate the principle of operation of the graphic equaliser we first need to consider the operation of a simplified version of a single stage, as illustrated in Figure 1. Here, the input signal is fed to the non-inverting input of an op-amp through a 10k resistor. A potentiometer is connected between the non-inverting inputs with its wiper going to signal common (ground) via a network represented by Z. Here, a series-resonant circuit is employed. Feedback is provided between the op-amp output and the inverting input.


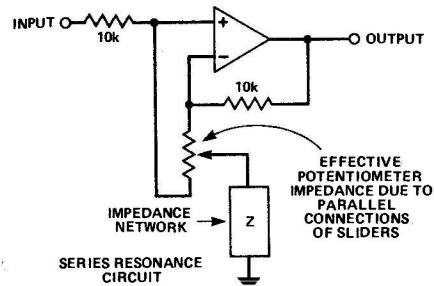


Fig. 1

The input resistor forms a potential divider with part of the potentiometer

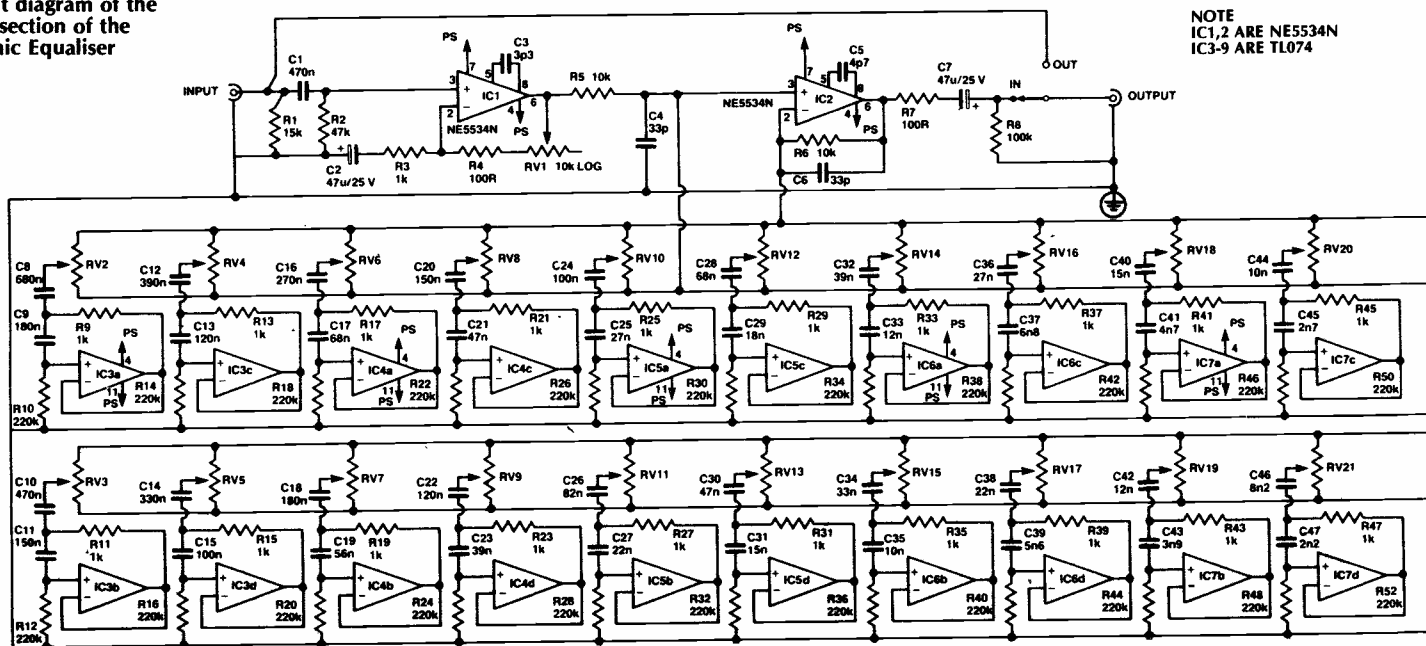Circuit diagram of the main section of the Graphic Equaliser



GRAPHIC

Is your listening room/concert hall dull and lifeless? Or does it echo and ring like the Whispering Gallery? David Tilbrook comes to the rescue with a project that will help get your response into shape.

HOW IT WORKS

(from the op-amp + input to the wiper) and the impedance Z to common. The feedback resistor also forms a potential divider with the end of the pot from the inverting input and the impedance Z to ground.

If the wiper of the pot is set to mid-travel, the attenuation of the input signal due to the potential divider is compensated by the gain of the op-amp and the overall gain from input to output is unity. If the pot wiper is now moved toward that end of the pot connected to the op-amp's inverting input, the gain of the stage is increased as the feedback ratio is reduced owing to a reduction of the impedance from the op-amp's inverting input to common. At the same time less attenuation of the input signal occurs as the impedance from the non-inverting input to common is decreased. The stage will have gain, maximum gain being determined by the impedance of the series resonant networks. If this is low, gain will be high. Series resonant networks exhibit very low impedance at resonance, rising either side of that frequency.

When the wiper of the pot is moved toward the non-inverting input of the op-amp, the attenuation due to the input potential divider is increased. The gain of the op-amp is decreased at the same time as the feedback ratio is increased because the impedance from the inverting input to common is increased. Once again, the overall gain of the circuit is a function of the impedance of the series resonant circuit, but this time the gain is at a minimum — in fact, attenuation occurs.

By choosing a suitable Q for the series resonant network, the bandwidth

can be set to cover a desired frequency range. The potentiometer then sets gain or attenuation of the stage at the centre of the chosen frequency band.

The technique just described above can be used whenever it is desired to incorporate a relatively large number of filters into the signal path as in graphic equalisers or tone controls. The filter networks need not be bandpass or notch filters, simpler bass and treble controls can also be used.

Once this basic configuration is set up, all that remains is to design the filter networks. As mentioned before, series resonant networks were used since these give the required characteristic of low impedance at the resonant frequency. In their simplest form these networks consist of an inductor, capacitor and resistor in series. At the resonant frequency, the impedance of the circuit is equal to that of the resistor assuming a perfect inductor and capacitor were used. To eliminate the inductor an op-amp circuit has been used to simulate the characteristics of an inductor. Such a circuit is called a 'gyrator'.

The gyrator circuit can provide both the inductance and the series resistance required in the network so this can simply be placed in series with the capacitor to form the required resonant circuit. This is shown in block diagram form in Fig. 2.

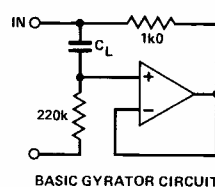
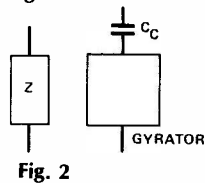


Fig. 3

Figure 3 shows the general circuit of the gyrator used in this project. The amount of inductance 'generated' by this circuit is given by the simple equation:

$$L = 1k \times 220k \times C_L \text{ in Henries}$$

where the value of C_L is in Farads

The equivalent circuit of the gyrator is shown in Fig. 4. The series resistance is equal to the 1k resistor while the 220k resistor becomes the parallel resistance of the coil. This value is high enough not to affect circuit operation drastically. The resonant frequency of this filter is given by the standard formula:

$$F = \frac{1}{2\pi\sqrt{LC}} \text{ in Hertz}$$

The general circuit, simplified, of the Third-Octave Graphic Equaliser is shown in Fig. 5. IC1 is simply a variable gain stage which also provides some input buffering. IC2 is the filter stage with a group of 28 gyrator circuits, all connected in parallel, in the feedback circuit. Commencing at a centre frequency of 31.5 Hz, each gyrator filter has a Q chosen such that its bandwidth covers one-third of an octave. Thus the upper and lower the 3 dB points of adjacent filters 'touch'. A total of 28 filters are required to cover the audio frequency band. Filters are not placed on the band limits of 20 Hz and 20 kHz as they are not really required. To reduce the IC count a set of seven quad op-amps (TL074s or uA774s) are used for the gyrators.

Slide pots are used to set the gain or attenuation inserted for each third-octave band as it is easy to see, at a glance, how much gain or attenuation has been set and, as all the pots are lined up in parallel across the front panel, one can instantly see the total modification made to the audio system's frequency response.

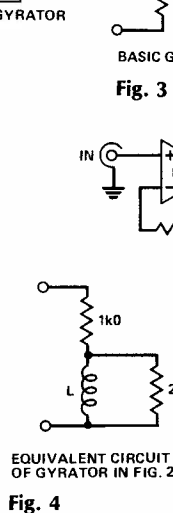
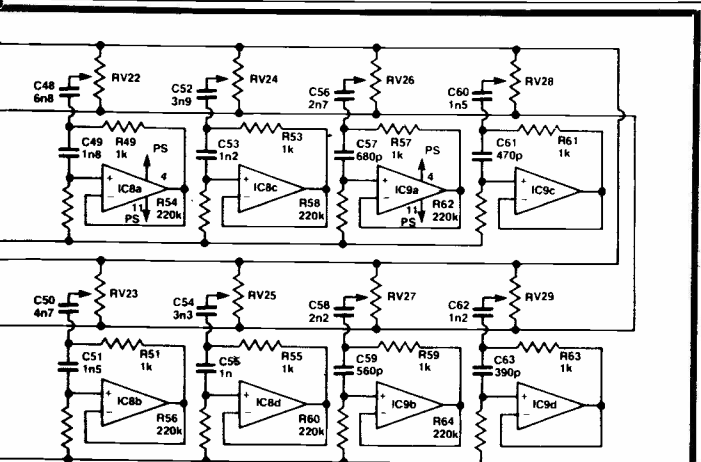


Fig. 4

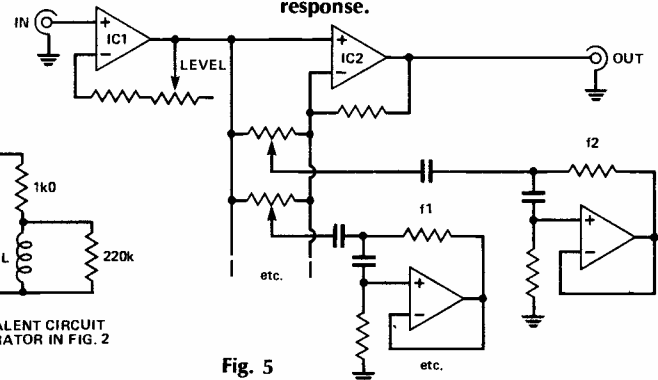


Fig. 5


PROJECT : Graphic Equaliser

the inductors necessary for the series of band-pass filters so there are no coils to wind. The gyrator is covered in more detail in the How it Works section, but the main problem associated with this approach is caused by phase shifts occurring in the op-amps used in the gyrators. The basic principle of a gyrator is to invert the phase response of a capacitor to simulate the characteristics of an inductor. The problem is that all amplifiers introduce a phase shift which increases towards the extremes of the frequency response. For this reason, care must be taken when choosing op-amps for use in gyrators at the top end of the frequency spectrum. This problem is accentuated when the Q of the filters concerned is increased. Since the Q of the filters must be higher in a $\frac{1}{3}$ -octave equaliser, an op-amp with greater phase linearity at high frequencies must be used. Fortunately, op-amps with the desired characteristics are not difficult to obtain and we are using the TL074 or uA774. These are both quad FET op-amps with almost identical performance and are capable of excellent results in the circuit, even in the top-most filter.

Earthing

In any large multi-component audio system, earthing is a continuous nightmare because of hum loops. The theory says that the entire audio circuit should be earthed at only one point. However, adding an extra earth connection can sometimes cure a hum that you've spent many hours chasing round the circuit — this is one of those occasions when the best approach is to leave it like that (but keep your fingers firmly crossed), hope it holds while the band is playing, and forget about it afterwards . . .

The other problem is deciding exactly where this one earth should be in the first place. Some people say the very start of the signal path — or, at least, as close as you can get to it. Others say that it should be at the power amp input. But everyone agrees — it's definitely never at the graphic equaliser. OK, then, what connection should there be between the mains earth and the graphic equaliser electronics? Some opt for a capacitor (100n is a reasonable value); others use a resistor (10 to 100R). We've left this up to you. However, all agree that there must also be a very low

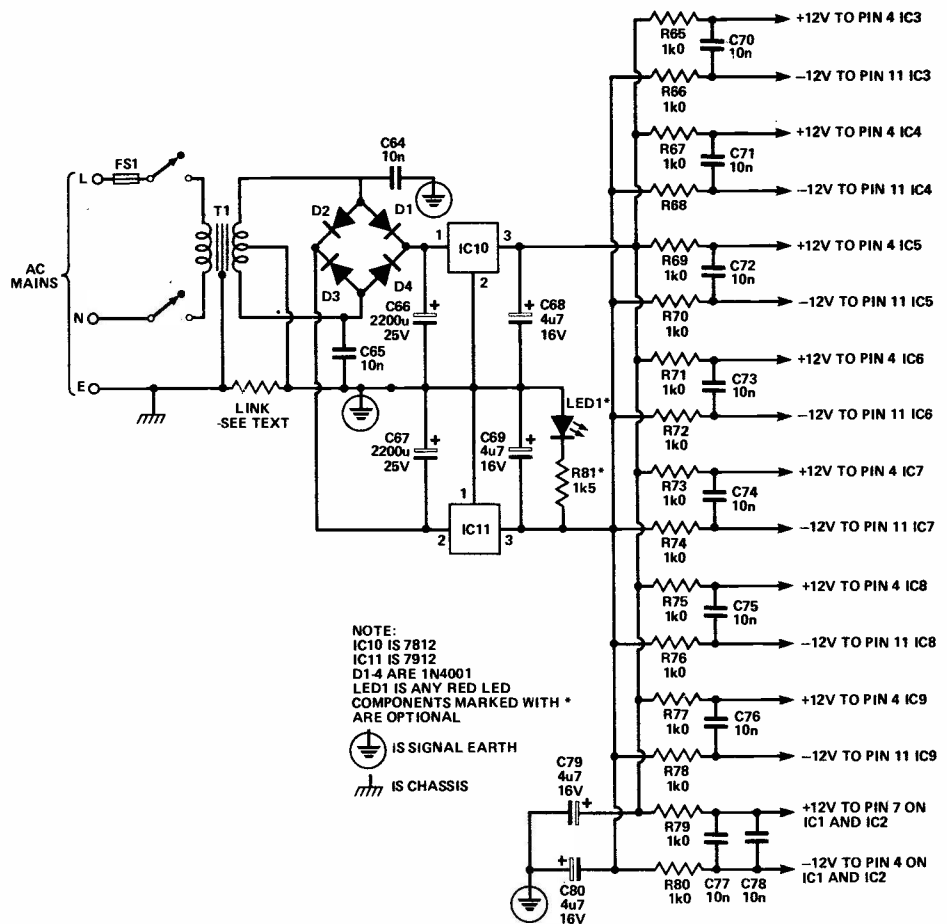

Circuit of the power supply for the Graphic Equaliser.

impedance path to earth through the rest of the equipment for safety reasons: if there isn't, you're asking for a nasty shock. Note also that you must use insulated audio input and output sockets, and be careful not to inadvertently connect the signal and mains earth in any other way — watch how you secure the PCB to the case, for example.


Capacitors

One possible area of trouble is in finding a supplier for the capacitors. If you look at the Parts List, you'll see that lots of the capacitors are in the E12 series: we hadn't realised how many suppliers had switched to supplying just the E6 series until we tried to locate a

supplier for a suitable type. In the end, we used Siemens polycarbonate layer types from Cricklewood for all the capacitors above 10n in value, and mixture of these and polystyrene for those under 1n0. Ours were all 5% types or better, and we'd strongly suggest that you use 5% tolerance or better for all the capacitors in the gyrators. We've designed the PCB so that it should accommodate most types you're likely to want to use.

Next month we will give constructional details of the Graphic Equaliser, including details of a super specially designed case from Newrad Instruments.

ETI

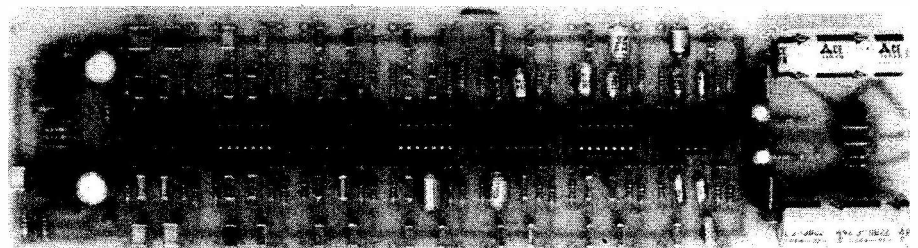

This is the completed PCB — more details next month.

CARBON FILM 5% H 182 100 20 10M 15W E24 2p 15W E27 2p 15W E27 3p 15W E27 4p 15W E27 5p 15W E27 6p	IDEAL AS MAINS SUPPRESSORS 1000V 15F 22h 15F 35p 15F 47p 15F 55p 15F 65p 15F 75p 15F 85p	100.0V 32p MANY MORE CARBON ORS IN STOCK P.L.S. PHONE 100mA 6.0-8V 9.0V, 12.0-12V 10-15V 95p	2.5 x 17 2.99 2.5 x 17 3.85 4.7V 17 4.93 Vj Board 1.92 Dig Board 3.90 Track Cutter 1.48 37 way 2.50 Pin Insertor 1.79 100 Pins 55p	CONDUCTORS R3 9x5x2 1.15 R4 11x6x3 3.85 R5 11x7x4 3.75 R6 13x8x4 4.75 R7 15x8x4 7.35	VEROBONES V1 3x2x1 1.15 V2 120x80 55p V3 180x110x55 V5 220x174x 100mm 10.40 15mm 10.40 16V 171x121x 75mm 5.65 REMOTE (Handheld) BOX 94x61x22.5mm White 89p	VEROBONES V1 3x2x1 1.15 V2 120x80 55p V3 180x110x55 V5 220x174x 100mm 10.40 15mm 10.40 16V 171x121x 75mm 5.65 REMOTE (Handheld) BOX 94x61x22.5mm White 89p	PCB RELAYS 24VAC 10 Rps C contacts SPDT 1x1/2 6v 72D 2.75 12V 285V 2.75 24V 1150V 2.95 48V 4600V 3.04	2N1102 35p 2N1127 35p 2N1218 25p 2N1218A 25p 2N1219 25p 2N2220 25p 2N2222 25p 2N2223 2.60 2N223A 4.15 2N2918 35p 2N2919 35p 2N2919A 35p 2N2920 35p 2N2921 3.47 2N2922 3.47 2N2923 2.5p 2N2924 1.5p 2N2925 1.5p 2N2926 1.0p 2N3010 75p 2N3011 65p 2N3012 65p 2N3013 27p 2N3014 1.85 2N3015 1.85 2N3055A 1.20 2N3056 1.85 2N3058 1.85 2N3059 1.85 2N3059A 1.85 2N3059B 1.85 2N3059C 1.85 2N3059D 1.85 2N3059E 1.85 2N3059F 1.85 2N3059G 1.85 2N3059H 1.85 2N3059I 1.85 2N3059J 1.85 2N3059K 1.85 2N3059L 1.85 2N3059M 1.85 2N3059N 1.85 2N3059O 1.85 2N3059P 1.85 2N3059Q 1.85 2N3059R 1.85 2N3059S 1.85 2N3059T 1.85 2N3059U 1.85 2N3059V 1.85 2N3059W 1.85 2N3059X 1.85 2N3059Y 1.85 2N3059Z 1.85	2N6126 75p 2N6127 75p 2N6130 75p 2N6131 75p 2N6132 75p 2N6199 75p 2N6200 75p	BC187A 10p BC187B 10p BC187C 10p BC187D 10p BC187E 10p BC187F 10p BC187G 10p BC187H 10p BC187I 10p BC187J 10p BC187K 10p BC187L 10p BC187M 10p BC187N 10p BC187O 10p BC187P 10p BC187Q 10p BC187R 10p BC187S 10p BC187T 10p BC187U 10p BC187V 10p BC187W 10p BC187X 10p BC187Y 10p BC187Z 10p	BC609 35p BC610 35p BC611 35p BC699 35p BC700 35p
---	---	---	---	--	---	---	---	--	---	---	---

BD 124 (Mullard)

THE MOTOCAR

Could this fairly ordinary looking Lancia car be the Car Of The Future? Motorola certainly think so. Read on and see if you agree.

At a press conference recently, Motorola revealed their Motocar (who says ETI has a monopoly on bad puns?). It's a Lancia Delta with a lot of electronics where there used to be switches and yards and yards of copper wire.

Even though they were very nice to us, impressing the press wasn't Motorola's reason for spending the equivalent of several Rolls Royces on building the car. Their main targets are the car and car component manufacturers. Not only are Motorola trying to persuade them that they need to bring car electrics up to date, but that they should use Motorola products to do this; and further, that they should work closely with Motorola to get the products they need. So, the car itself is by no means a finished design, it's a try out for a large number of different ideas.

Why Go Electronic?

Conventionally-wired cars have been around for quite a while now, so why should anyone want to change? Well, from the manufacturers' point of view, there are a number of good reasons.

Firstly, and always firstly in manufacturing, there's cost. At present, a wiring loom for a car costs around £35. Motorola's electronic system, with a great host of additional features that we'll be looking at in a moment, would cost around £100 to build after a tidy up of the prototype. Obviously, Motorola learned a few things during the building, and some newer components better suited to the project have since come on the market, so with a little optimisation, the cost could probably be halved to £50. However, once you start to use specially made components, a lot more cost saving can be carried out, and the price would easily go below that of the conventional loom, especially if the price of copper rises. And the electronic system will almost certainly be a lot easier to install.


Secondly, there's reliability. Well designed electronics should always be much more reliable than electro-mechanics. An electronic loom would considerably reduce the number of connectors in the system. Not only would this improve the car's reliability after sale, it would also cut down on manufacturing costs. Did you know that around 40% of all cars straight off the production line require some remedial work to be done on their electrical systems?

Thirdly, by using electronic control, the engine's performance can be much improved. Fuel efficiency is very important in Europe, but over in the States, tough anti-pollution legislation has led to emphasis on emission control. It was, in fact, this legislation that provoked the interest in electronic engine control in the first place — who says that conservation is always bad for industry?

Finally, an electronic control system can offer driver and servicing facilities very much more easily than the conventional system; for example, fault finding and fault monitoring can be automated.

Why The Rush?

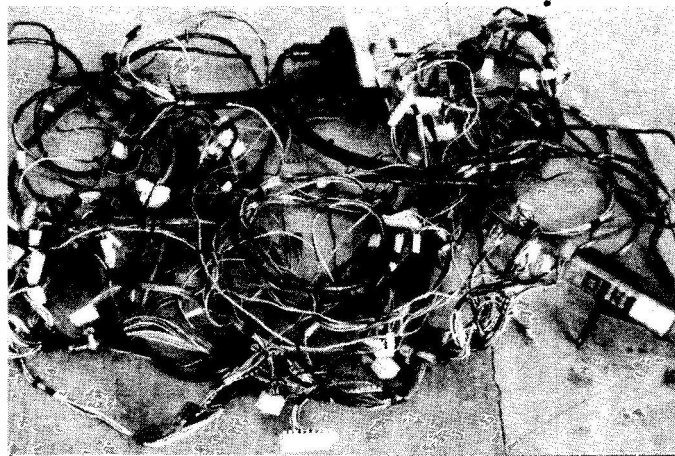
Motorola are keen to get into the market as soon as possible. They reckon that by 1987, 7% of the European semiconductor market will be for cars. Naturally, they're expecting a certain amount of competition, but they hope that their early start will catch their competitors napping.




This is what the Motocar no longer has — a conventional (messy) wiring loom containing about 500 metres of wire.

Take A Bus

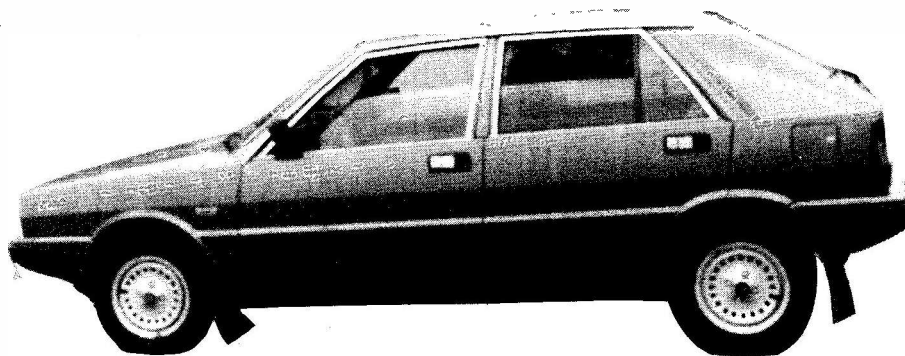At the heart of Motorola's electronics is a four-wire multiplexed bus. This links the master control unit to a number of outstations that are responsible for controlling



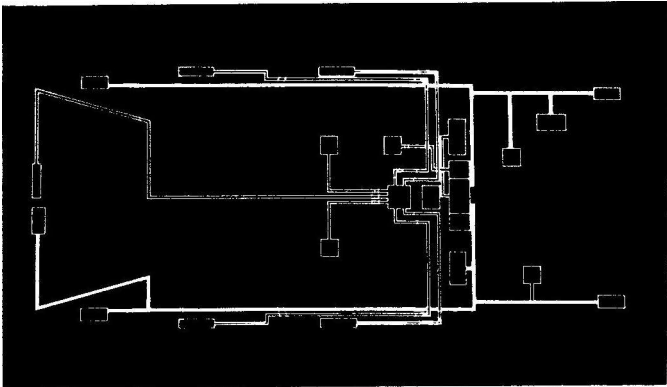

The layout of the main bus and the fibre-optic bus: the fibre optic bus radiates out from where you'd expect the gearshift to be. The main bus is in a H-shape and is drawn with a solid white line.

and monitoring the car's functions. The master control has a separate interface with the controls on the steering column, and there is also a completely separate fibre optic system that controls some 'luxury' items.


The four wires of the bus have the following functions: power (positive, negative return through chassis), signal earth, data, and bus control. Data transmission is sequential and bidirectional in half duplex mode with auto-clocking and RZ. The control line is used to sort out which unit is sending what to where. The power line is for the controlled devices as well as for the outstations themselves, so it has to be fairly meaty. All the other conductors can be light weight.

Outstations

All the outstations are based on the Motorola MC6805P2 microprocessor, as is the master control unit. Motorola now say that they would now use the cheaper and more appropriate MC6804P2, but it was not available when the design work was done.

The simplest of the outstations are the load-switching units, of which there are six, all identical. Each is capable of switching eight loads of up to 10 A, although in the present car, the most that is used in any one unit is seven (some units switch rather fewer). Because N-channel devices are cheaper to make than P-channel ones, N-channel T-MOS FETs are used to switch between the ground connection to the controlled devices and the car chassis; this means that the controlled load is always at positive supply potential with respect to the chassis, and this could lead to a corrosion problem.

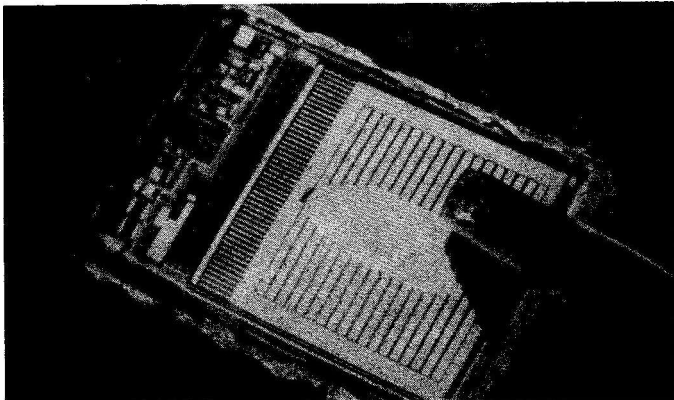Motorola's proposed solution is to use an on-board DC to DC converter to provide a higher voltage supply of 30 V. This will allow the N-channel FETs to switch reliably at the standard supply voltage (nominal 12 V) in common drain mode, even when the system is suffering from a



Motorola's smart power device — to be used for future load switching stations.

reduction in supply voltage (for instance, while the battery is turning over the engine on the starter motor). Surprising though this may seem, it is apparently cheaper to do this than to use P-channel FETs.

Each load switching unit has an A-to-D converter on board, so that it can measure, for example, the output from the petrol tank gauge. It also has a load-state monitor that can sense blown bulbs. This information is all transmitted back along the bus to the central control.

Further development of the load switching unit will almost certainly involve Motorola's smart power device, soon to enter production. These devices have a T-MOS power transistor with logic and drive components on the same chip (together with, perhaps, a DC to DC converter). These may make it feasible to use single load switching units, with each load on the bus having its own dedicated switching unit. In order to avoid increasing the number of connections by using these units, they may well be housed within the controlled load itself.

Condition Monitoring

Hard at work just gathering and transmitting data is the vehicle condition monitor, one of the four other types of outstation. It sits inside the engine compartment and monitors fluid levels and other information to be presented to the driver. A single A-to-D is used to monitor the alternator output, and, as well as being used to provide the system's equivalent of an ignition warning light, this also determines the control of the battery charging.

The other three outstations are semi-autonomous in that they are not under direct central control: for instance, you could not have the engine control unit having to deal with an interrupt when it was just about to fire a spark plug. Besides the engine control unit, there are the cruise control, so that you can take your foot off the accelerator and the car will maintain a steady (and legal) speed, and the climate control, a posh phrase for an air conditioner control unit.


The engine control has a pressure transducer in the inlet manifold; it also measures the position of the distributor arm in 0.35° increments (by using a phase locked loop to multiply up the output from a position sensor). Thus it can control the spark and fuel injection timing to a resolution of 0.35°; it can also control the amount of fuel injected. However, the opening and closing of the inlet and outlet valves is still done mechanically.

Alternative Bus

To avoid running lots of wires from the controls mounted on the steering column, Motorola engineered a much more simple multiplexed bus to link the steering column to the central control unit. It's a three wire bus, with unidirectional data flow; the encoding is done with standard CMOS, rather than a microprocessor (shame!).

Gone is the familiar needle and dial speedo — it's replaced by a fluorescent digital display, as in the latest Maestro. The display itself is an off the shelf Futaba plasma display, driven by (you've guessed it) a dedicated microprocessor, this time an MC6801. To be fair, the micro is kept busy displaying a range of messages (in a choice of several languages and imperial or metric units) on two separate LCD displays to tell the driver about the state of the car, distance travelled, etc. For instance, it is this that will tell you if one of bulbs has blown.

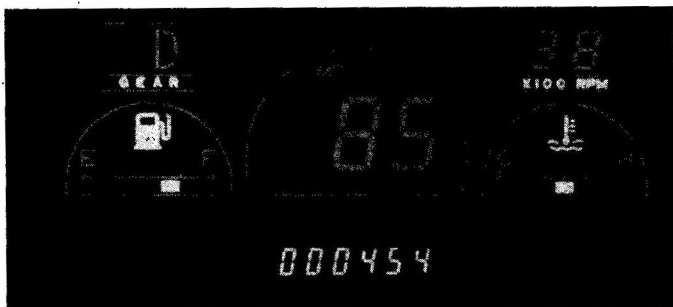One interesting feature is the use of an EEPROM to store the odometer reading. When the ignition is turned off, power is held on long enough to allow the old reading to be erased and the new one written into the EEPROM. Motorola have put quite a lot of thought into developing a system that is as secure as possible, to prevent




The Futaba display used, in full action. Unfortunately, you can't see that the figures are in a rather reassuring green, and the main beam indicator is in a baby blue . . .

unscrupulous dealers from being able to wind back the reading.

Multiplexed?

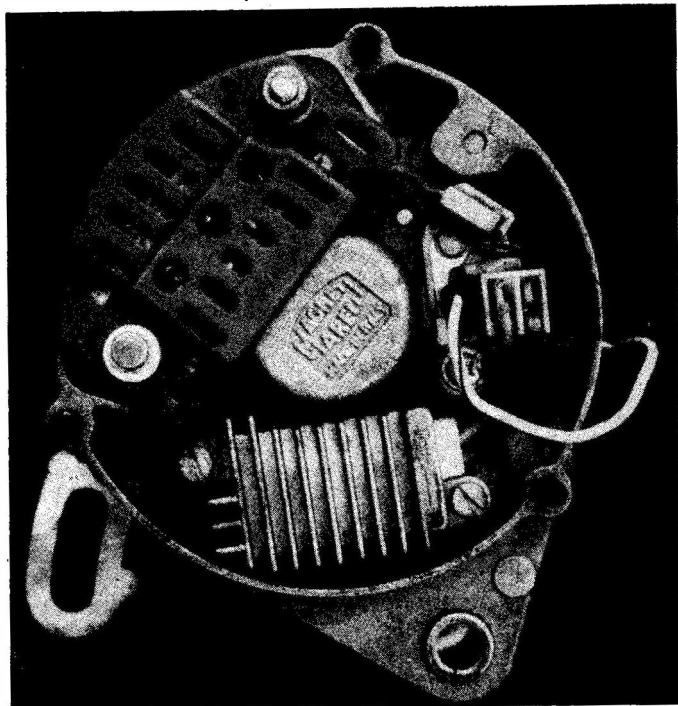Motorola claim that rather than confusing the poor mechanic, the multiplexed bus system should make ser-



Above: one nice touch not mentioned so far is that Motorola have tackled the problem of supply line transients at source, the alternator, by replacing three out of nine of the diodes with transient suppression types.

The present test unit (right) is just a little bigger than a hand-held calculator (though this does depend on how big your hands are . . .) Apparently the production model would need little more than a (yes, another) microprocessor, some ROM (possibly on board the micro) and a display.



vice and repair easier — but only provided that the garage buys a special adapter! This special unit would, when plugged into the car, take control of the bus and run the car through a test sequence, with a readout that tells the mechanic what needs attention. The special adaptor units should be around the size of a largish pocket calculator and cost about £150 (a special one will be needed for each car type).

Shine A Light

The other multiplex system uses optical fibres to control seat positioning servos, windows, door locking and window mirror positioning. This system is entirely separate from the other bus system, and it has its own control unit; it's also arranged in a different way, as a star network. Each unit has its own line running back to the control unit: this was necessary because of the lack of T-junctions for optical fibres.

Motorola's optical fibre system is unusual in two ways. Firstly, the same devices are used as transmitters and receivers, thus allowing two-way transmission along a single fibre. Because only short transmission distances are involved, signal strength is not a problem and a relatively inefficient detector can be tolerated.

Secondly, visible light is used because this will make it easier for a "mechanic" (perhaps Motorola had better invent a new term for this person while they're at it) to detect if a signal is present. The cost of the components needed for a visible light system is also considerably lower than those for an infra-red system.

Motorola say that fibre optic systems are used because they offer higher noise immunity and lower weight than copper wire systems. However, the fact that they've been confined to the luxury features of the car is probably evidence of a reliability problem — or is it just my cynicism?

Parting Shot

One last system that we haven't mentioned yet is the radio. It too (yes!) uses a dedicated microprocessor, and even though it's a Grundig radio, the micro is a Motorola MC6220. It's worth reflecting that Motorola started out by making car radios; having partially surrendered that market and gone on to greener pastures, they're now set to invade the rest of the car.

ETI

LB ELECTRONICS

LIMITED STOCKS

Brand new havard H452, power supply and Nickel charger, output 13 volts at 0.7A (max 1 amp) 7" x 3" x 3 1/2" appx. Fully cased and boxed only **£4.95p p/p £1.70p.**

SPECIAL OFFERS

(while stocks last)
Mullard .2" Red L.E.D.'s 0.06p, 7805 **38p**, 7805KC 5 Volt 1.5A **75p**, 78H05 5V 3 AMP **£3.50p**, 5K 3/4" multiturn trim pots 14 for **£2.50p**

DISC DRIVE BONANZA

PERTEC FD650 DSDD **£199 + VAT**
TEAC FD-55F 1/2 Height DSDD 80 track **£228 + VAT**
Cannon 2/3 drive SSDD Shugart Compatible 40 Track **£129 + VAT**

Apple controller card for two drives..... **£40.00 + VAT p&p 50p**
ASC11 coded qwerty Keyboard, manufactured by Alphanumeric (Woking UK). Model 60K brand new plus data..... **£19.95p p&p £1.50**

25 WAY 'D' Types, plugs **£1.85**, sockets **£1.85** (solder tail) p&p 30p. Telephone for bulk prices.

8" Drive Cabinets complete with power supply (LINEAR) to take two 8" Drives, Brand New **£99.95p + VAT** (carriage cost)

Twin 5" Cabinets with power supply **£30.00 + VAT** (providing a disc drive is purchased from us, if drives purchased elsewhere **£40.00 + VAT**)

9" Green Phosphor Monitors Brand New and Cased Composite Video Input 18mhz band width **£78 + VAT** each (carriage cost)

Textool 24 dil Zif Skt (used) **£3.95p p&p 30p**

Brand New 13" Colour monitor fully cased. Full warranty 540 x 236 pixel. RGB TTL Input plus apple Input **£220 + VAT** (carriage at cost).

BNC Lead Bonanza coax lead with BNC plug at one end, 2 metres plus **£1.00 p&p 30p** and 10 metres plus **£2.50 p&p 75p**



LB ELECTRONICS


11 HERCULES ROAD, HILLINGDON, MIDDLESEX UB10 9 LS, ENGLAND
TEL: UXBRIDGE 55399

American Express



ELECTROVALUE

FIRST FOR NASCOM 3

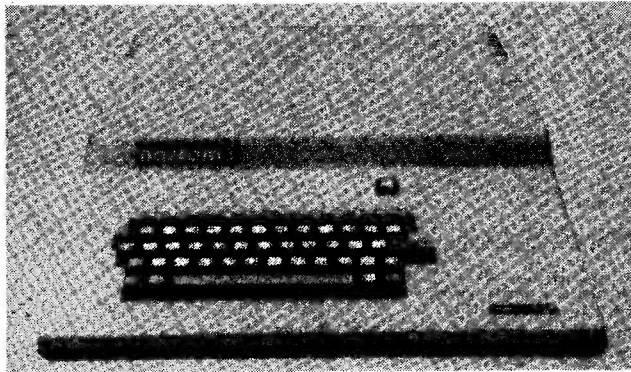

Highly recommended for its versatility, this latest Nascom microprocessor can be the foundation of a superb professionally styled system of excitingly useful applications and development... and of course, Electrovalue are accredited Nascom suppliers, ready to deliver your Nascom 3 (and ancillaries) NOW!

Nascom 3 Microprocessor **£549 + V.A.T.**

(to drive monitor or TV set) **£120 + V.A.T.**

Monitor for above **£685 + V.A.T.**

(takes standard 5 1/4") **£945 + V.A.T.**

Nascom High Capacity Dual Drive **£945 + V.A.T.**

Nascom 2 in kit form inc. keyboard but less power supply, case and RAM. Always available. **£225 + V.A.T.**

DID YOU KNOW that for almost 20 years Electrovalue have been foremost suppliers of components, etc, costing from pennies to hundreds of pounds? So why not send for our new Summer Price List and see why it pays to buy from us.

ELECTROVALUE LTD.

Head office, Mail Order and Shop: 28 St Judes Road, Englefield Green, Egham, Surrey TW20 0HB. Egham (STD 0784: London 87) 33603: Telex 264475. North - personal shoppers only. 680 Burnage Lane, Burnage, Manchester M19 1NA (061-432 4945).
EV Computing Shop, 700 Burnage Lane, Manchester (061-431 4866).
Electrovalue and EV Computing Shop are members of the Microvalue group.

CALL IN AND SEE FOR YOURSELF

AUDIO ELECTRONICS

ALL PRICES INCLUDE VAT

TEST EQUIPMENT CENTRES

ALL MODELS ON DISPLAY
OPEN SIX DAYS A WEEK

RETAIL • MAIL ORDER • EXPORT • INDUSTRIAL • EDUCATIONAL

DIGITAL MULTIMETERS (UK C/P Free)



ALL MODELS 3 1/2 DIGIT UNLESS STATED



HAND HELD	With free carry case	Beckman T110 As T100 plus Cont. test.	£67.85
K125C = 13 range 0.2A DC 2 meg ohm	£24.95	Sifam 2200B 21 range 2A AC/DC 20 meg ohm	£39.95
K130C = 16 range 10A DC 2 meg ohm	£29.95	+Optional carry case £2.95	
K135C = 26 range 1A AC/DC 20 meg ohm	£34.95	BENCH MODELS	
K155C = 28 range 10A AC/DC 20 meg ohm	£39.95	TM353 = 27 range LCO 2A AC/DC	£86.25
6010+ = 28 range 10A AC/DC 20 meg ohm	£34.40	TM355 = 29 range LED 10A AC/DC	£86.25
7030+ As 6010 but 0.1% basic.	£41.30	TM351 = 29 range LCO 10A AC/DC	£113.85
KD615 = 16 range 10A DC 2 meg plus Hfe tester	£39.95	+Optional carry case £8.84	
189M 30 range 10A AC/DC 20 meg plus Hfe tester	£69.95	2001 = 28 range LCO 10A AC/DC plus 5 range Cap. Meter with case	£109.00
HD30 16 range 0.2A AC/DC 2 meg ohm	£41.95	TM451 4 1/2 digit LCO every facility (0.02%)	£171.00
HD30/B As above plus cont. buzzer	£44.50	1503A 4 1/2 digit LCO every facility (0.05%)	£171.00
HD31 22 range 10A AC/DC 2 meg ohms plus cont. buzzer	£58.95	1503Ha 0.05% basic version of above	£189.00
DM2350 = 21 range 10A AC/DC 20 meg ohm miniature hand held auto range	£49.95	1504 true RMS version	£201.25
Beckman T100 34 range 10A AC/DC 20 meg ohm	£56.35	Sifam 2500 24 range LCO 2A AC/DC	£99.95
		Metrix (ITT) professional 3 1/2 + 4 1/2 digit	
		DMN's standard & true. RMS 4 models stocked	£77.00 - £201.25

FREQUENCY COUNTERS



PFM200A MHz hand held pocket 8 digit LED	£77.60
8110A 8 digit LED bench 2 ranges 100 MHz	£77.00
8110B 8 digit LED bench 2 ranges 600 MHz	£113.85
8000B 8 digit LED 3 ranges 1 GHz	£178.00
TF400 = 8 digit LCO 40 MHz	£126.50
TF200 = 8 digit LCO 200 MHz	£166.75
+Optional carry case £6.84	
Prescalers - Extended range of most counters	£43.00
TP900 600 MHz	£74.00
TP1000 1 GHz	£74.00

SIGNAL GENERATORS (220/240v AC)



FUNCTION : All sine/square/triangle/TTL etc	T6100 1 Hz - 100 KHZ	£30.00
	T6102 0.2 Hz - 2 MHz	£166.75
PULSE		
T6105 Various facilities 5 Hz - 5 MHz		£97.75
AUDIO : Multiband Sine/Square		
LA627 10 Hz to 1 MHz		£90.85
AG202A 20 Hz to 200 KHz (List £94.50)		£83.50
RF		
S6402 100 KHz to 30 MHz (List £79.50)		£69.50
LS617 100 KHz to 150 MHz		£79.35

ELECTRONIC INSULATION TESTER

YF 501 500 V/0-100m with carry case **£63.00**

MULTIMETERS (UK C/P 65p)

HM102Z 20K/V 10A DC 22 range & cont. buzzer	£13.50
HM102Z 20 K/V 22 range & cont buzzer	£14.95
ETC5000/5001 21 ranges 50K/V. Range doubler. 10A DC.	£18.95
TMK500 23 ranges 30K/V. 12A DC plus cont. buzzer.	£24.75
NH56R 20K/V. 22 range pocket	£10.95
ETU 102 14 range 2K/V pocket	£6.50
830A 26 range 30K/V. 10A AC/DC overload protection, etc.	£23.95
360TR 23 range 100K/V. Large scale 10A AC/DC plus Hfe	£39.95
AT1020 18 range 20K/V. Deluxe plus Hfe tester	£18.95
YN 360TR 19 range 20K/V plus Hfe tester	£15.95
Matrix Professional multimeters In stock 3 models from	£74.75

VARIABLE POWER SUPPLIES (UK C/P £1.00)

PP241 0/12/24V. 0/1A.	£35.00
PP243 3 amp version	£59.95
PS 1307S 8/15V 7 amp twin meter	£24.95

DIGITAL THERMOMETER

TH301 LCD -50°C to +750°C with thermocouple **£68.43**

AC CLAMP METER

ST300 0/300A 0/600 VAC. 0/1 KOhm 9 ranges With carry case (UK C/P 65p) **£28.50**

LOGIC PROBES

LP10 10 MHz **£28.50**
DLPS50 50 MHz with carry case and accessories **£52.33**

AUDIO ELECTRONICS

301 EDGWARE ROAD, LONDON W2 1BN. TEL: 01-724 3564
ALSO AT HENRY'S RADIO.
40A/406 EDGWARE ROAD, LONDON. W2. TEL: 01-724 0323
HENRY'S COMPONENT SHOP. TEL: 01-723 1008

HIGH VOLTAGE METER

Direct reading 0/40 KV. 20K/Volt. (UK C/P 65p) **£23.00**

DIGITAL CAPACITANCE METER

0.1 pf to 2000 mfd LCO 8 ranges **DM6013** **£52.75** (Carry case **£2.95**)

TRANSISTOR TESTER



Direct reading PNP. NPN, etc. TC1 (UK C/P 65p) **£21.95**

FREE CATALOGUES SEND LARGE SAE (UK 20p)

ALL PRICES INCLUDE VAT


Order by Post with CHEQUES/ACCESSES/ VISA or you can telephone your orders. All orders despatched within 9 days unless advised.

GET BIG POWER

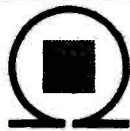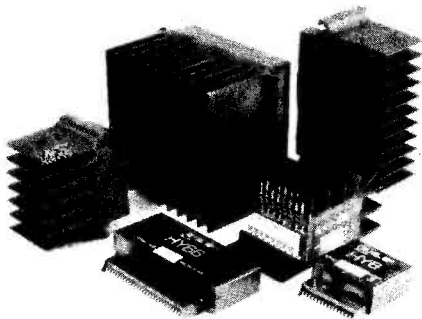

Modular Amplifiers the third generation

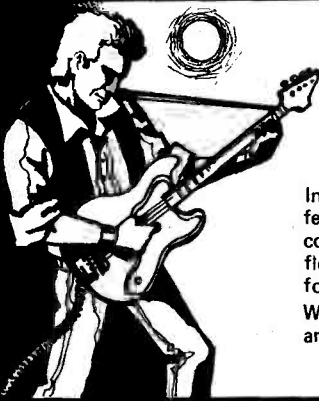Due to continuous improvements in components and design ILP now launch the largest and most advanced generation of modules ever.



WE'RE INSTRUMENTAL IN MAKING A LOT OF POWER

In keeping with ILP's tradition of entirely self-contained modules featuring, integral heatsinks, no external components and only 5 connections required, the range has been optimized for efficiency, flexibility, reliability, easy usage, outstanding performance, value for money.

With over 10 years experience in audio amplifier technology ILP are recognised as world leaders.



BIPOLAR MODULES

Module Number	Output Power Watts rms	Load Impedance Ω	DISTORTION		Supply Voltage Typ	Size mm	WT gms	Price inc. VAT
			T.H.D. Typ at 1KHz	I.M.D. 60Hz/7KHz 4:1				
HY30	15	4-8	0.015%	<0.006%	± 18	76 x 68 x 40	240	£8.40
HY60	30	4-8	0.015%	<0.006%	± 25	76 x 68 x 40	240	£9.55
HY6060	30 + 30	4-8	0.015%	<0.006%	± 25	120 x 78 x 40	420	£18.69
HY124	60	4	0.01%	<0.006%	± 26	120 x 78 x 40	410	£20.75
HY128	60	8	0.01%	<0.006%	± 35	120 x 78 x 40	410	£20.75
HY244	120	4	0.01%	<0.006%	± 35	120 x 78 x 50	520	£25.47
HY248	120	8	0.01%	<0.006%	± 50	120 x 78 x 50	520	£25.47
HY364	180	4	0.01%	<0.006%	± 45	120 x 78 x 100	1030	£38.41
HY368	180	8	0.01%	<0.006%	± 50	120 x 78 x 100	1030	£38.41

Protection: Full load line. Slew Rate: 15v/ μ s. Risetime: 5 μ s. S/N ratio: 100db. Frequency response (-3dB) 15Hz - 50KHz. Input sensitivity: 500mV rms. Input Impedance: 100K Ω . Damping factor: 100Hz >400.

PRE-AMP SYSTEMS

Module Number	Module	Functions	Current Required	Price inc. VAT
HY6	Mono pre amp	Mic/Mag. Cartridge/Tuner/Tape/Aux + Vol/Bass/Treble	10mA	£7.60
HY66	Stereo pre amp	Mic/Mag. Cartridge/Tuner/Tape/Aux + Vol/Bass/Treble/Balance	20mA	£14.32
HY73	Guitar pre amp	Two Guitar (Bass Lead) and Mic + separate Volume Bass Treble + Mix	20mA	£15.36
HY78	Stereo pre amp	As HY66 less tone controls	20mA	£14.20

Most pre-amp modules can be driven by the PSU driving the main power amp. A separate PSU 30 is available purely for pre amp modules if required for £5.47 (inc. VAT). Pre-amp and mixing modules in 18 different variations. Please send for details.

Mounting Boards

For ease of construction we recommend the B6 for modules HY6-HY13 £1.06 (inc. VAT) and the B66 for modules HY66-HY78 £1.29 (inc. VAT).

POWER SUPPLY UNITS (Incorporating our own toroidal transformers)

Model Number	For Use With	Price inc. VAT	Model Number	For Use With	Price inc. VAT	Model Number	For Use With	Price inc. VAT
PSU 21X	1 or 2 HY30	£11.93	PSU 52X	2 x HY124	£17.07	PSU 72X	2 x HY248	£22.54
PSU 41X	1 or 2 HY60, 1 x HY6060, 1 x HY124	£13.83	PSU 53X	2 x MOS128	£17.86	PSU 73X	1 x HY364	£22.54
PSU 42X	1 x HY128	£15.90	PSU 54X	1 x HY248	£17.86	PSU 74X	1 x HY368	£24.20
PSU 43X	1 x MOS128	£16.70	PSU 55X	1 x MOS248	£19.52	PSU 75X	2 x MOS248, 1 x MOS368	£24.20
PSU 51X	2 x HY128, 1 x HY244	£17.07	PSU 71X	2 x HY244	£21.75			

Please note: X in part no. indicates primary voltage. Please insert "0" in place of X for 110V, "1" in place of X for 220V, and "2" in place of X for 240V.

MOSFET MODULES

Module Number	Output Power Watts rms	Load Impedance Ω	DISTORTION		Supply Voltage Typ	Size mm	WT gms	Price inc. VAT
			T.H.D. Typ at 1KHz	I.M.D. 60Hz/7KHz 4:1				
MOS 128	60	4-8	<0.005%	<0.006%	± 45	120 x 78 x 40	420	£30.41
MOS 248	120	4-8	<0.005%	<0.006%	± 55	120 x 78 x 80	850	£39.86
MOS 364	180	4	<0.005%	<0.006%	± 55	120 x 78 x 100	1025	£45.54

Protection: Able to cope with complex loads without the need for very special protection circuitry (fuses will suffice).

Slew rate: 20v/ μ s. Rise time: 3 μ s. S/N ratio: 100db. Frequency response (-3dB): 15Hz - 100KHz. Input sensitivity: 500mV rms. Input impedance: 100K Ω . Damping factor: 100Hz >400.

'NEW to ILP' In Car Entertainments

C15

Mono Power Booster Amplifier to increase the output of your existing car radio or cassette player to a nominal 15 watts rms.

Very easy to use.

£9.14 (inc. VAT)

Robust construction.

Mounts anywhere in car.

Automatic switch on.

Output power maximum 22w peak into 4 Ω .

Frequency response (-3dB) 15Hz to 30KHz, T.H.D. 0.1% at 10w 1KHz

S/N ratio (DIN AUDIO) 80dB, Load Impedance 3 Ω

Input Sensitivity and impedance (selectable) 700mV rms into 15K Ω 3V rms into 8 Ω .

Size 95 x 48 x 50mm. Weight 256 gms.

C1515

Stereo version of C15.

£17.19 (inc. VAT)

Size 95 x 40 x 80. Weight 410 gms.

WITH A LOT OF HELP FROM



PROFESSIONAL HI-FI THAT EVERY ENTHUSIAST CAN HANDLE...

Unicase

Over the years ILP has been aware of the need for a complete packaging system for its products, it has now developed a unique system which meets all the requirements for ease of assembly, adaptability, ruggedness, modern styling and above all price.

Each Unicase kit contains all the hardware required down to the last nut and bolt to build a complete unit without the need for any special tools.

Because of ILP's modular approach, "open plan" construction is used and final assembly of the unit parts forms a compact aesthetic unit. By this method construction can be achieved in under two hours with little experience of electronic wiring and mechanical assembly.



Hi Fi Separates

UC1 PRE AMP UNIT: Incorporates the HY78 to provide a "no frills", low distortion, (<0.01%), stereo control unit, providing inputs for magnetic cartridge, tuner, and tape/monitor facilities. This unit provides the heart of the hi fi system and can be used in conjunction with any of the UP Unicase series of power amps. For ultimate hum rejection the UC1 draws its power from the power amp unit.

POWER AMPS: The UP series feature a clean line front panel incorporating on/off switch and concealed indicator. They are designed to compliment the style of the UC1 pre-amp. Performance for each unit which includes the appropriate power supply, is as specified on the facing page.

Power Slaves

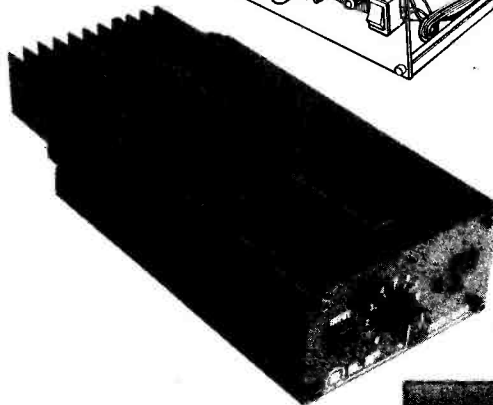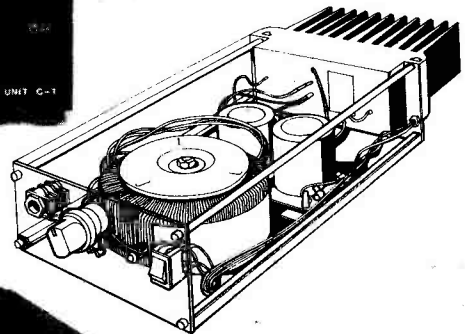Our power slaves, which have numerous uses i.e. instrument, discotheque, sound reinforcement, feature in addition to the hi fi series, front panel input jack, level control, and a carrying handle. Providing the smallest, lowest cost, slave on the market in this format.



TO ORDER USING OUR FREEPOST FACILITY

Fill in the coupon as shown, or write details on a separate sheet of paper, quoting the name and date of this journal. By sending your order to our address as shown at the bottom of the page opposite, with FREEPOST clearly shown on the envelope, you need not stamp it. We pay postage for you. Cheques and money orders must be crossed and made payable to I.L.P. Electronics Ltd, if sending cash, it must be by registered post. To pay C.O.D. please add £1 to TOTAL value of order.

PAYMENT MAY BE MADE BY ACCESS OR BARCLAYCARD IF REQUIRED

UNICASES

HIFI Separates					Price inc. VAT
UC1	Preamp				£29.95
UP1X	30 + 30W/4-8Ω	Bipolar	Stereo	HiFi	£54.95
UP2X	60W/4Ω	Bipolar	Mono	HiFi	£54.95
UP3X	60W/8Ω	Bipolar	Mono	HiFi	£54.95
UP4X	120W/4Ω	Bipolar	Mono	HiFi	£74.95
UP5X	120W/8Ω	Bipolar	Mono	HiFi	£74.95
UP6X	60W/4-8Ω	MOS	Mono	HiFi	£64.95
UP7X	120W/4-8Ω	MOS	Mono	HiFi	£84.95
Power Slaves					
US1X	60W/4Ω	Bipolar	Power	Slave	£59.95
US2X	120W/4Ω	Bipolar	Power	Slave	£79.95
US3X	60W/4-8Ω	MOS	Power	Slave	£69.95
US4X	120W/4-8Ω	MOS	Power	Slave	£89.95

Please note X in part number denotes mains voltage. Please insert '0' in place of X for 110V, '1' in place of X for 220V (Europe), and '2' in place of X for 240V (U.K.) All units except UC1 incorporate our own toroidal transformers.



Post to: ILP Electronics Ltd., Freepost 4, Graham Bell House, Roper Close, Canterbury CT2 7EP, Kent, England. Telephone: (0227) 54778. Technical: (0227) 64723. Telex: 965780.

Please send me the following _____

Total purchase price _____

I enclose Cheque Postal Orders Int. Money Order

Please debit my Access/Barclaycard No. _____

Name _____

Address _____

Signature _____

TV STORAGE SCOPE

The Tele-Scope 200S is a storage oscilloscope which utilises a number of electronic techniques to convert signals into a form suitable for display on a television screen. The unit is designed around the latest technology in analogue-to-digital conversion, using the Ferranti ZN441 flash converter to convert the input signal to a six-bit binary word at a point in time, which is determined by the sample rate. This sample rate can be selected to be up to 10 million samples per second (or one sample producing one word every 100 nS).

The resulting words are stored in one of two memories, which take it in turns to store the incoming

data and display the stored data. In manual trigger mode, the incoming signal controls the changeover of the two memories, so if the input signal only occurs once, or is removed, the last signal is displayed on the screen. When measuring DC levels, the auto trigger mode is used to give a continuous trigger, as the DC level has no recognisable transitions for the circuit to begin operation.

Functional Description

The analogue input is taken via the input coaxial socket to a switchable attenuator and is buffered with a source-coupled FET. A second FET in the source of this buffer puts a DC offset on the

buffer, which can be varied to produce a shift in the position of the display.

The resultant analogue signal is fed to the analogue-to-digital flash converter which produces a six-bit word for each sample. The sample rate can be up to 10 MHz (one sample every 100 nS), and is selected using the front panel switch marked 'width' in the same way that a conventional scope has a time base selector. The six-bit word will appear on the data bus and the input address clock, which is running at the sample rate, writes the data in to the selected memory.

When both the memory cycle and frame scan are completed, the memory is switched to read and the

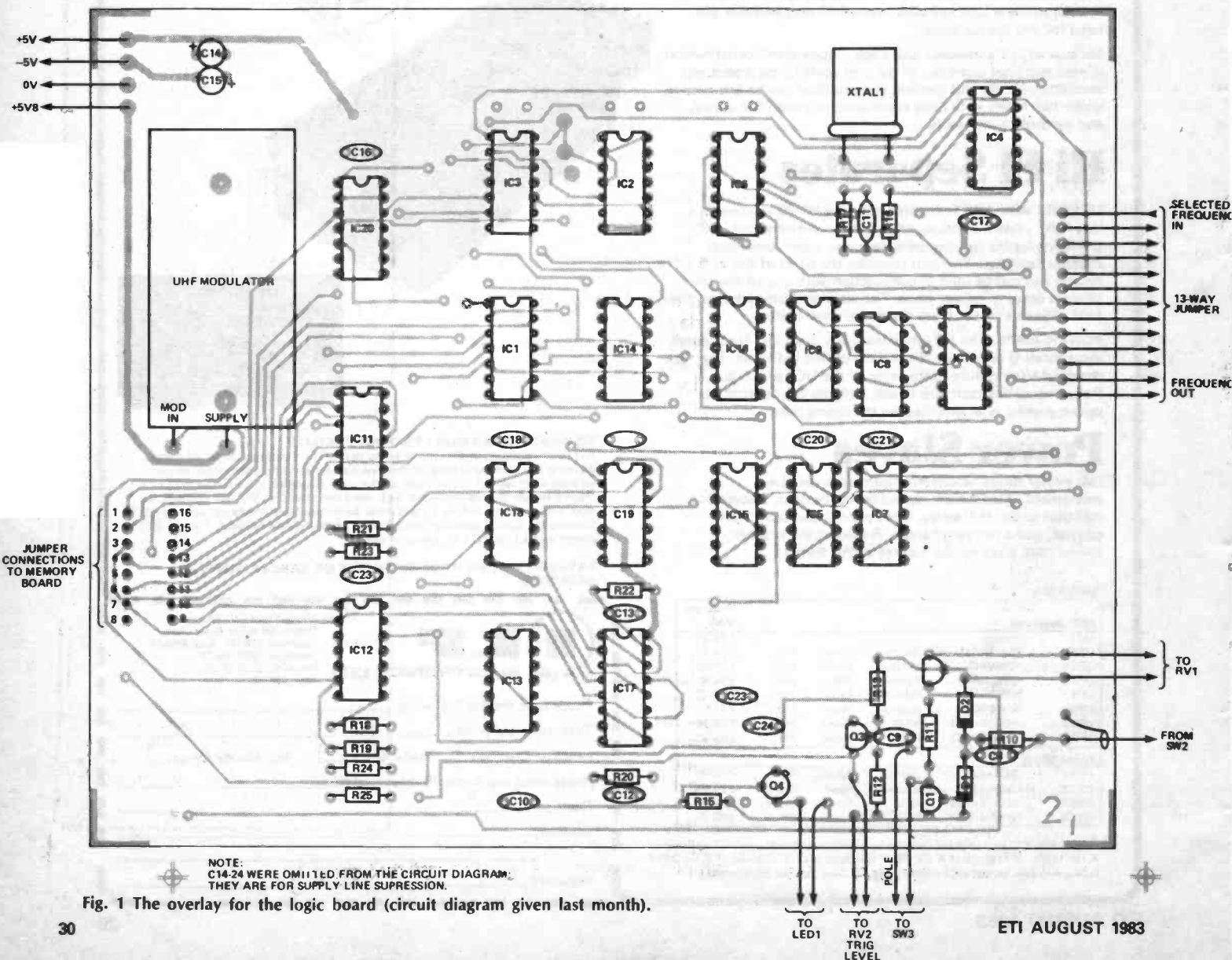


Fig. 1 The overlay for the logic board (circuit diagram given last month).

We conclude our description of this innovative piece of test gear with the circuit of the data processing board and full constructional details. Design and development by Ian Gooderson.

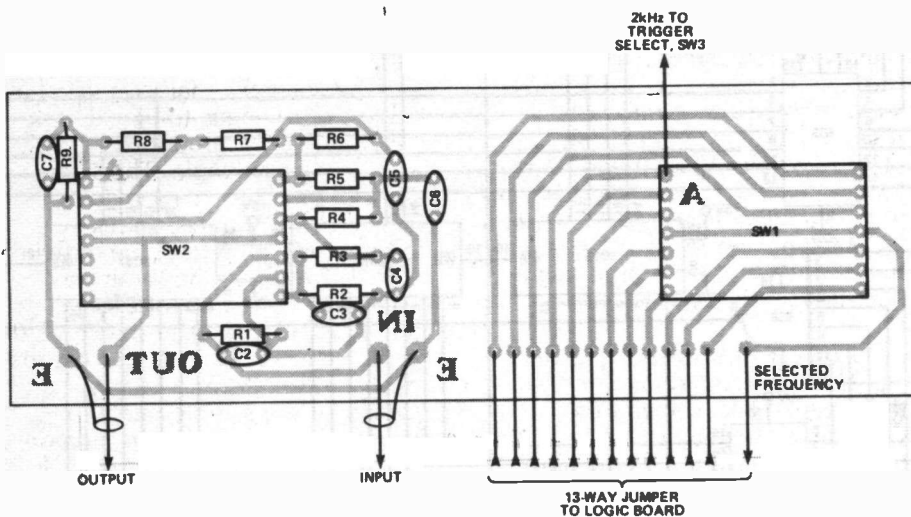


Fig. 2 Overlay for the front panel PCB, containing the input attenuator.

output address counter is routed to this memory for the output sequence to begin. The output address counter is cycled at 5 MHz and the six-bit words are output to a comparator, which compares the word to the video line number. If the six-bit word and the line number are equal, the comparator outputs a data bit to the video summing amplifier.

This data is then mixed with the line and frame sync pulses and output to the UHF modulator. The display has a memory map which is 247 pixels wide by 64 pixels high; each pixel is 200 nS wide and four lines high, utilising a screen area of 49.4 nS wide and 256 lines high. This data is repeated on the second field of the interlaced TV scan to prevent any flashing on the display, even at high input frequencies.

The memories are addressed by two counters and during the input cycle the input address counter is running at the same rate as the A-to-D, storing each data bit in a separate serial memory location. The output address counter is running at a constant 5 MHz as the display time is constant.

Construction

The Tele-Scope contains two double-sided, plated-through hole circuit boards, one for the data storage and routing, one for the control logic and analogue input buffering. The case cover has a

small PCB on the reverse, which holds some of the components associated with the input and trigger controls and the corresponding input sockets. The power supply board is mounted in the rear of the case, with the transformer to the left (viewed from the front).

First build the data storage and routing board (the circuitry for this board is described in this month's article). All the components are mounted on the circuit board (see the overlay in Fig. 5). All the connections to this board are made via a 16-way jumper lead to the control logic board (whose circuitry was described last month). All the ICs used are LS TTL series, with the exception of the memories and the ZN441. Although this latter chip is not static-sensitive, great care should be taken when handling it because it is the single most costly item in the equipment. For this reason it should be mounted in a 24-pin IC socket.

Next, build the control logic/input buffer board. All the chips on this board are LS TTL, with no special handling problems for them or any of the other discrete components used. A 16-way jumper lead connects this board to the data processing PCB. A 13-way length of ribbon cable should also be connected at the other end of the PCB at this point in the proceedings, for later connection to the sampling frequency selector

PARTS LIST — LOGIC BOARD

Resistors (all 1/4W, 5% except where stated)

R1	560k 2%
R2	270k 2%
R3	180k 2%
R4	56k 2%
R5	27k 2%
R6	18k 2%
R7	5k6 2%
R8, 9	2k7 2%
R10, 15	10k
R11	220R
R12	1M0
R13	470k
R14, 25	47R
R16, 17	330R
R18, 19	270R
R20	4k7
R21, 23	1k0
R22	56k
R24	470R

Potentiometers

RV1,2	10k linear
-------	------------

Capacitors (all ceramic except where stated)

C1,8-10,16-24	100nF
C2	100pF
C3, 5	20pF
C4	120pF
C6	68pF
C7	10pF
C11	27pF
C12, 13	2n2
C14,15	22uF 16 V PCB electrolytic

Semiconductors

IC1	74LS04
IC2, 6, 11	74LS74
IC3	74LS10
IC4	74LS00
IC5, 7-10	74LS90
IC12	74LS03
IC13-16, 19	74LS93
IC17	74LS123
IC18	74LS73
IC20	74LS08
Q1-3	2N3819
Q4	BC107
D1, 2	1N4148
LED1	red LED

Miscellaneous

SW1	SPDT slide switch
SW2	9-way PCB-mounting rotary switch
SW3	2-pole, 3-way slide switch (only one half used)
SW4	12-way PCB-mounting rotary switch
XTAL1	10 MHz
PCBs (see Buylines); UHF modulator type UM 1111E36; ribbon cable; sloping front case (see Buylines); screened cable for input; PCB pillars; power supply board (see Buylines).	


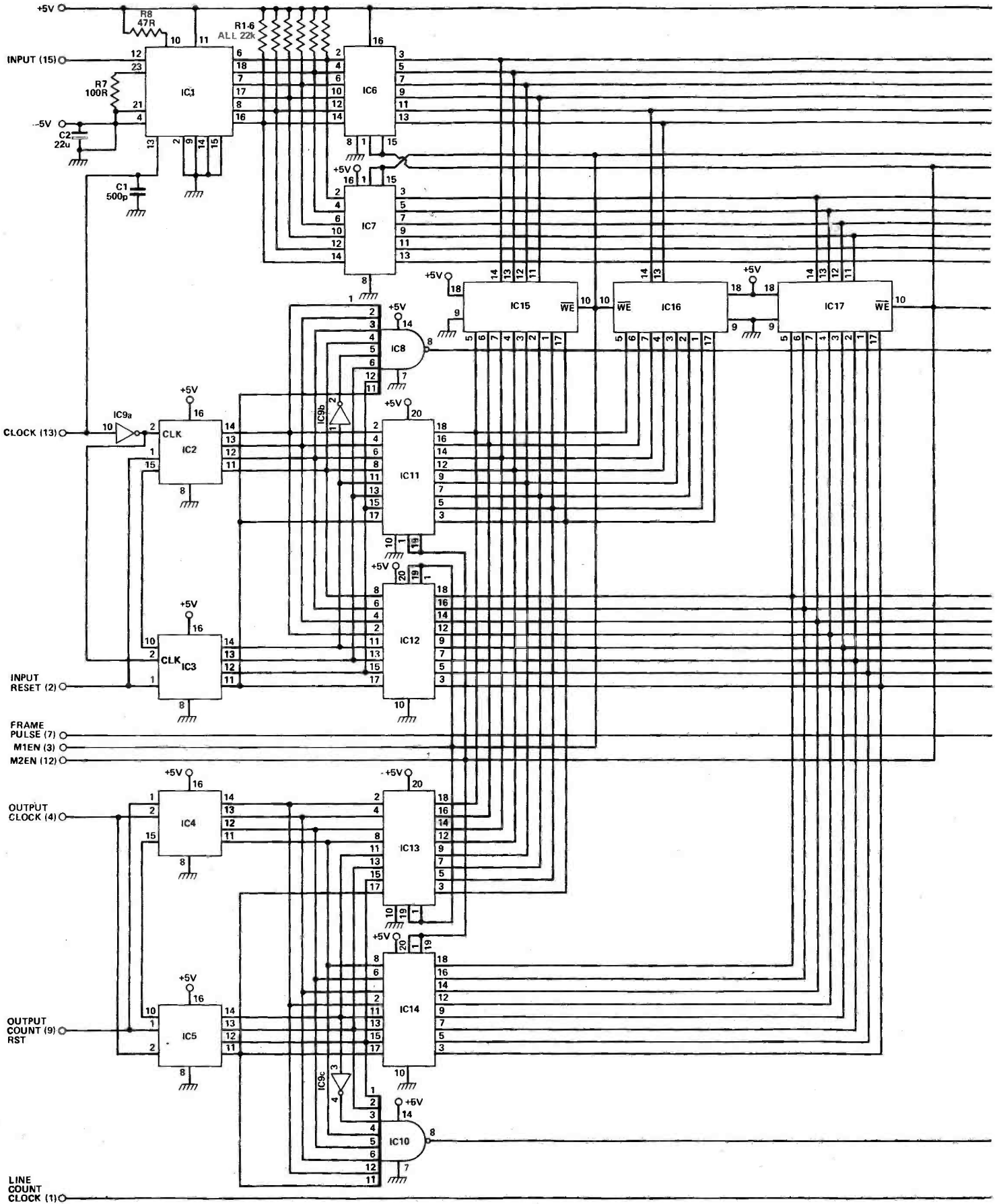


Fig. 3 Circuit diagram of the data storage and routing board.

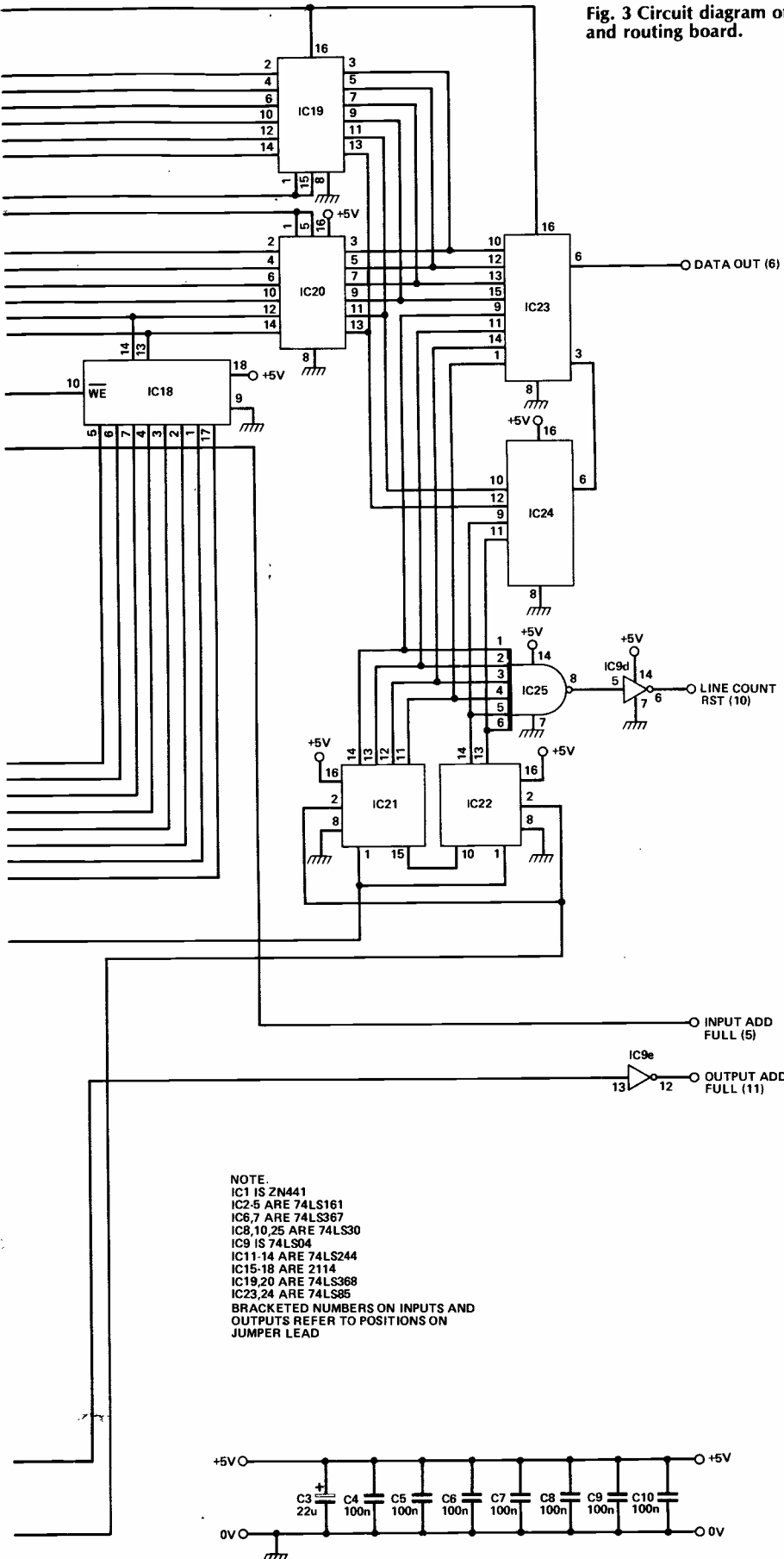

NOTE:
 IC1 IS ZN441
 IC2-5 ARE 74LS161
 IC6,7 ARE 74LS367
 IC8,10,25 ARE 74LS30
 IC9 IS 74LS04
 IC11-14 ARE 74LS244
 IC15-18 ARE 2114
 IC19,20 ARE 74LS368
 IC23,24 ARE 74LS85
 BRACKETED NUMBERS ON INPUTS AND
 OUTPUTS REFER TO POSITIONS ON
 JUMPER LEAD

HOW IT WORKS

IC1 is the ZN441 A-to-D converter. This converts the analogue input signal into a six-bit binary word at rates up to 10 million samples a second. The six-bit word from each sample is then passed to the memory buffers IC6 and IC7. If IC6 and IC20 are selected, then data is written to the memory block IC15, 16. In this case IC19 and IC7 are in the high impedance output mode, and IC20 enables data from the second memory block, IC17, 18, to be read to the comparator IC23, 24. The memory and buffer enables also select the address buffers, routing the input addressing to IC15, 16, and the output addressing to IC17, 18 in this example. In other words, in this phase of the operation IC11 is allowing the synchronous counters IC2 and IC3, which are acting as an eight-bit address counter, to cycle IC15, 16 synchronously with the sample rate, while IC14 is allowing the output address counter IC4, 5 to address IC17, 18. IC12, 13 are disabled to block the respective unwanted address lines. On the alternate phase, ICs 11 and 14 would be disabled, ICs 12 and 13 would be enabled, and the two memory blocks IC15, 16 and IC17, 18 would receive the opposite sets of address signals. The output of IC8 goes low when the input address cycle is completed, while the output of IC10 goes low when the output address cycle is complete.

IC21, 22 form the 256-line counter, which is advanced every four video lines for a total of 64 steps. This six-bit output is compared with the six-bit output from the memory by IC23, 24, and when these are equal, a data bit is output to the video summing circuit. The output of IC25 goes low when a count of 256 is completed.

When the input cycle is complete (the input memory block is full), the input clock is disabled. The output clock is only enabled for 256 lines of the scan and is therefore disabled during the first and last lines of the display and the frame flyback time. When the input address is completed and the frame scan is completed, the memories are switched over and the new data is output to the comparator. The video data is therefore refreshed every 50 mS unless the incoming data cycle is longer.

The power supply unit has regulated +5 V and -5 V rails at 650 mA and 160 mA respectively, with a separate 5V8 supply for the UHF modulator.

Oops

A couple of errors crept into the first part: IC6a pin 3 is connected to IC7 pin 12, etc, and not as shown; the supply line decoupling capacitors were not shown, and they are C15 (22u tant) and C16-24 (100n ceramic) on the +5 V line and C16 (22u tant) on the -5 V line. Additionally, R14 has now been omitted. (Note that all the above component numbering refers to the logic board circuit diagram, published last month).

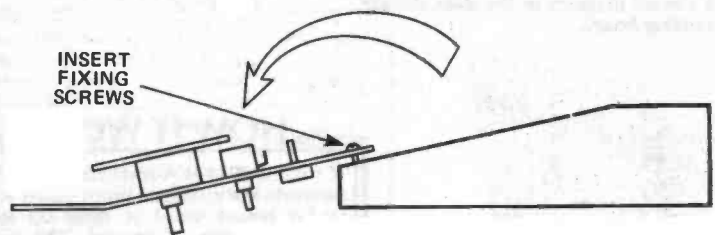


Fig. 4 This is how you attach the front panel to the box to make it easier to do the interconnecting

switch (see the overlay in Fig. 1). Incidentally, Q4 was incorrectly identified on the circuit diagram last month — it is actually a BC107.

The power supply is mounted on a single-sided PCB and is supplied ready-built with the kit. The front panel switches are also PCB-mounted as described earlier (see Figs. 2 and 6):

With the boards completed, the data processing board can be connected to the control logic


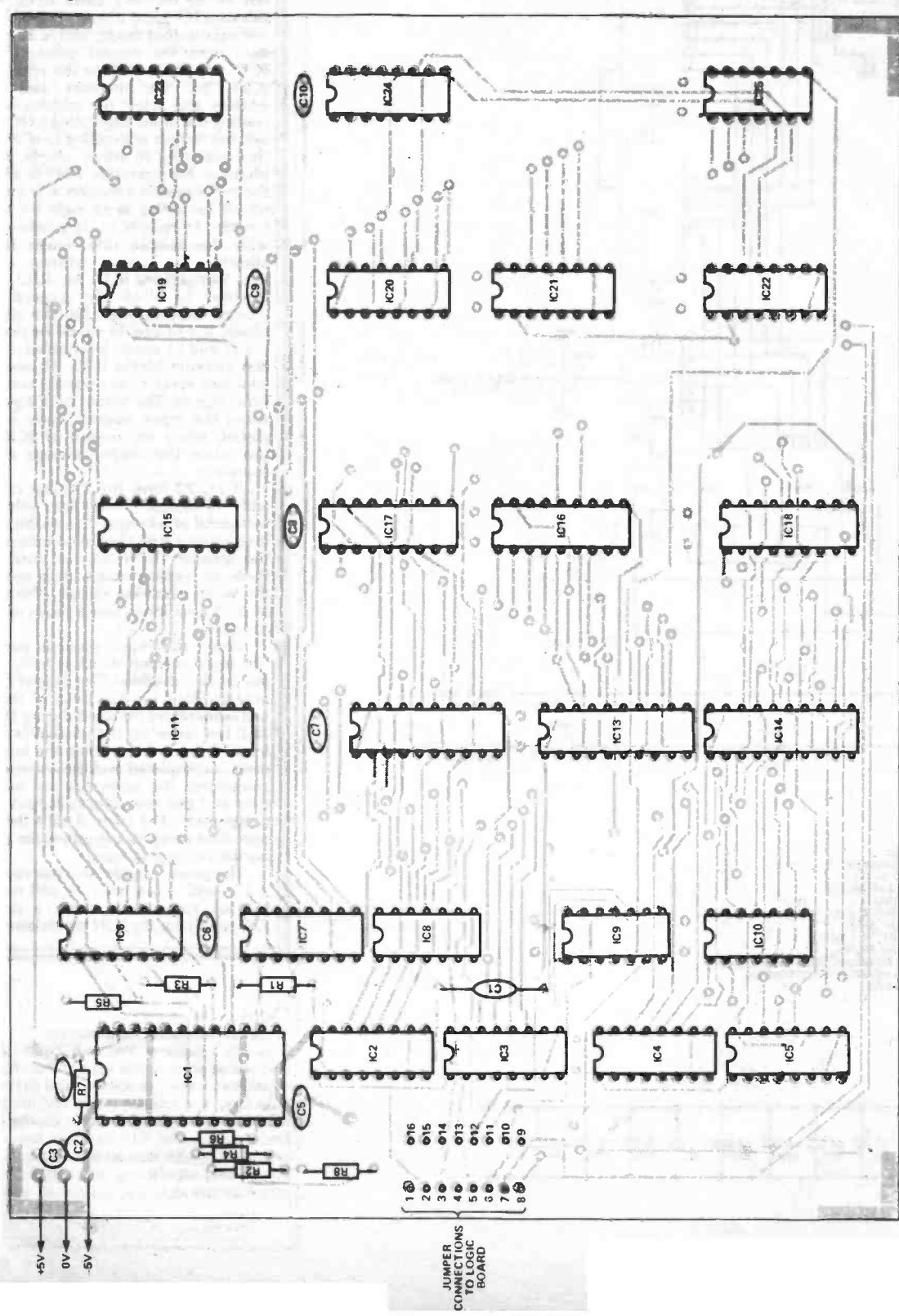


Fig. 5 Overlay of the data storage board

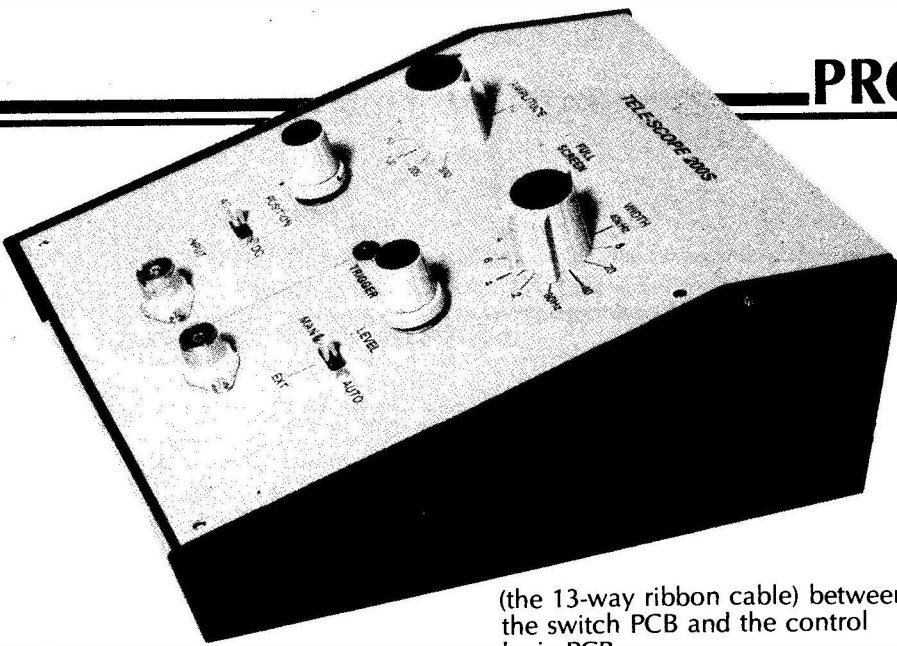

(the 13-way ribbon cable) between the switch PCB and the control logic PCB.

board using the 16-way jumper. The data processing board is then mounted on the base of the case with adhesive pillars, and the logic board is mounted on top of it, again using adhesive pillars. These special pillars are supplied with the kit and are required because there isn't enough space between tracks on either PCB to allow for fixing holes to be drilled. The power supply is fitted to the rear of the case, with the supply leads being soldered to the upper PCB. Don't forget to drill access holes in the rear of the case for the mains lead and UHF TV cable first, though!

Now mount the controls on the lid of the case. The lid should be screwed face down in the open position, using one pair of holes only, in order to make the front panel wiring easier. Figure 4 makes this clear.

First the input lines should be connected to the AC/DC input switch with C1 mounted directly across the switch terminals. Next wire the trigger switch (see Fig. 6) and the trigger LED, and finally connect the frequency selector lead

Operation

First switch on your television and tune in the Tele-Scope signal on an unused channel select button. Set the trigger switch to auto and locate the trace (a white line) using the position control. Set the voltage control to 10 V full screen and the full screen width control (the time base) to 80 Hz FSW. On touching the input socket with your finger, a 50 Hz sine wave will be displayed (due to mains pick-up).

By switching to manual trigger and adjusting the trigger level, it is possible to remove your finger and keep the sine wave display on the screen. This feature of the Tele-Scope allows you to do some interesting experiments — for instance, you can examine the EMF induced in a coil when a bar magnet is dropped through it.

Try using the Tele-Scope as a sampling scope on repetitive waveforms above 250 kHz (not calibrated, but it works). You can even capture one-shot events up to 250 kHz.

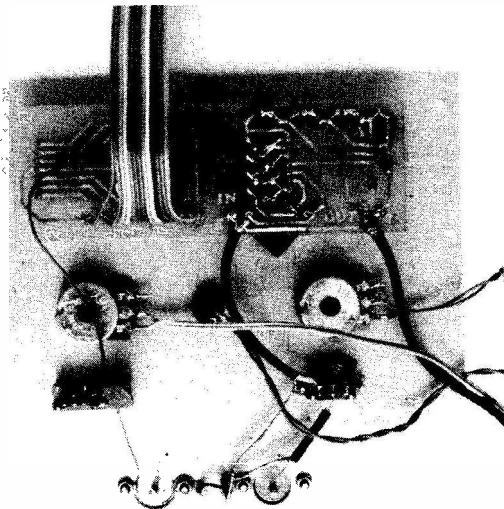


Fig. 6 Wiring the back of the front panel.

THE ZN441

The ZN441 is an ultra-high-speed parallel (flash) A-to-D converter comprising an array of 64 strobed comparators and encoding logic. A reference voltage applied across a tapped resistor chain defines 63 quantisation levels plus overrange and underrange, one input of each comparator being connected to the resistor string, while the other inputs are commoned and connected to the analogue input. When an analogue input is applied, all the comparators whose reference voltage is less than the analogue input will change state, ie if the input voltage is $V_{REF} \cdot n/64$ then n comparators will have tripped. The comparator outputs are decoded into a 1-of-64 format by NOR gates and then re-encoded into binary by a high-speed ROM.

Two or four ZN441s can be stacked to give a seven- or eight-bit converter with a minimum of external components. Applications include high-speed data acquisition, video an radar data conversion, digital signal storage and image processing.

PARTS LIST — DATA BOARD

Resistors (all $\frac{1}{4}W$, 5%)

R1-6 2k2
R7 100R

Capacitors

C1, 2 22uF 16 V PCB electrolytic
C3-9 100nF ceramic

Semiconductors

IC1 ZN441
IC2-5, 21, 22 74LS161
IC6, 7 74LS367
IC8, 10, 25 74LS30
IC9 74LS04
IC11-14 74LS244
IC15-18 2114
IC19, 20 74LS368
IC23, 24 74LS85

Miscellaneous

PCB (see Buylines); 24 pin IC socket for IC1.

ETI

BUYLINES

Hawk Electronics Test Equipment supply a full kit of parts for this project. All PCBs, the case (drilled and screen-printed), the ZN441 and all the other components are included, together with a comprehensive manual. The kit price is £89. The 'Tele-Scope' is also available built and tested for £109.

The manual may be purchased separately for £1.50 (no VAT required) refunded on the subsequent purchase of a kit or finished circuit.

Prices exclude 15% VAT, and postage and packing is £2.95 extra. The case, A-to-D converter, and the PCBs may all be purchased separately.

Hawk Electronic Test Equipment,
Unit 1,
Park Wood Industrial Estate,
Bircholt Road,
Maidstone,
Kent.
Telephone: 0622 686811.

BRADLEY MARSHALL LTD.

SPECIALIST ELECTRONIC COMPONENT DISTRIBUTORS

325 EDGWARE ROAD, LONDON W2 1BN Tel: 01-723-4242 Tlx: 295441

CRIMSON ELEKTRIK

No	Modules	Price
2580	CE 608 40W Mono	18.26
2581	CE1004 100W 4 Mono	21.30
2582	CE1008 100W 8 Mono	23.90
2583	CE1704 170W 4 Mono	30.43
2584	CE1708 170W 8 Mono	30.43
2585	CE3004 300W 4 Mono	42.60
2585a	FE 908 90W FET Mono	25.65
2585b	FE1704 170W FET Mono	33.48
2585c	BD1 Bridge Unit for Modules	7.13
2608	CPR 1X Pre-Amp Module	41.70

WE ALSO STOCK ALL THE POWER SUPPLIES TO DRIVE THESE MODULES

PS. THESE KITS AND MODULES ARE EXCLUSIVE OF VAT

JOIN THE PROFESSIONALS

No	Complete Pre-Amp Kit	CK1010	Price
2615	Complete Pre-Amp Kit	CK1010	£80.00
2616	Complete 40W Stereo Amp Kit	CK1040	£105.00
2616a	Complete 80W Stereo Amp Kit	CK1080	£116.00
2617	Complete 100W Stereo Amp Kit	CK1100	£131.00
2618	Add on Moving Coil Kit	MC12K	£21.74
2619	Pre-Amp Power Supply Kit	PSK	£17.39
	TS70 70° Thermal Switch		
	HS50 50mm Heatsink		
	HS100 100mm Heatsink		
	14.95 150mm Heatsink		

PLEASE NOTE ALL CRIMSON MODULES ARE GUARANTEED FOR 2 YEARS.

VELLEMAN KITS

No	Description	Price
K610	Mono UU using LEDES.	10.05
K1798	Stereo UU using LEDES	18.77
K1874	Running Light Kit	14.95
K2571	Light Computer with EPROM	36.23
K2569	Three Tone Chime	8.57
K2575	Microprocessor Doorbell 25 tunes	15.53
K2544	Complex Sound Generator	10.26
K2032	Digital Panel Meter	16.61
K2557	Digital Thermometer	26.57
K2545	50Hz Crystal Time Base	12.00
K615	High Precision Stopwatch	50.29

WE STOCK A WIDE RANGE OF BOXES TO HOUSE THESE KITS IN. FROM VERY SMALL TO VERY LARGE 19" MAXIMUM

PS. ALL KITS INCLUDE VAT

Some are easy some are hard

No	Transistor Ignition	11.16
K2543	Transistor Ignition	11.16
K2555	Digital Freq Counter for Receivers	45.40
K2566	3 Channel Coloured Light Organ	19.19
K2572	Universal Stereo Pre-Amplifier	6.56
K2574	Universal 4 Digit U/D counter with memory	44.72
K2577	Electric Motor Speed Control	11.17
K2579	Universal Start/Stop Timer	7.45
K2583	Heating Controller	81.45
K1682	Microprocessor Universal Timer (no case)	61.72
K2580	Electronic Power Switch Dimmer	12.37
K2551	Central Alarm Unit	15.48

TELETEXT KIT

This unit will make your TV fully remote control (infra-red) and bring you closer to the amazing world of teletext. The kit can also be updated to incorporate full Prestel, and with a keyboard this can give you full message facilities for ordering foods or sending and receiving messages (E.G.) Booking your Holidays!

With a microcomputer as an alternative keyboard the world is even greater adding bulk updating to viewdata computers and receiving telesoftware for implementation to any personal computer.

Even without the Prestel option, Telesoftware from the Teletext pages free!

The full features of Teletext, including subtitles are all included in the basic kit.

An attractive stylish case is available to complement the finished kit.

Basic Teletext Kit (no box) £130 + VAT P/P £2.50
with box £144.95 + VAT P/P £3.00
box by itself £14.95 + VAT P/P 75p

PRESTEL ADAPTOR

NEW

A Prestel micro computer adaptor to give full autodialling to your micro computer. All the usual Prestel facilities are added via this unit, plus many more, and can operate to any viewdata computer.

You can shop from home, bank transmitt messages and receive software, which means that the uses your micro can be put to are limitless.

The unit is not restricted to just the UK, for at least 28 countries use the Prestel viewdata format, so you can also mail-order from anywhere. The Prestel unit is suitable for most micro computers even the ZX-81, so at the push of a button, the technology of tomorrow is in your home today.

ANTEX

Soldering Irons

XS25	25W	5.46+
CX	17W	5.30+
C "iron"	15W	5.20+
CCN "ceramic"	15W	5.00+
Wide range of bits and elements in stock now.		
Soldering iron stand 2.40		
We stock multicore solder for normal use or fine.		

Iso-tip Cordless Iron	31.90+
Miniature low voltage soldering station	13.95+
Oryx50 50W temp controlled	15.50
Oryx super 30	5.90+
All irons are 240V mains. Earth Leakage current is less than 3 ua.	
The temperature controlled iron can be controlled within $\pm 2\%$ temperature range from 200°C to 400°C.	

ORYX

COMPONENTS

Device	Price
Z80A	3.20
Z80A PIO	3.20
Z80A CTC	3.20
6800	6.50
6810	3.00
6821	4.25
6502CPU	7.50
2114(200ns)	1.80
2708	3.00
2716	3.20
2732	7.50
2532	3.50
2764 (200ns)	11.00
ADC0816 (8 bit)	14.90

We also stock 74 series 74LS, C mos, transistors, capacitors, resistors, LED's, zeners, diodes, jack plugs, mains plugs XLR plugs, cannon plugs, arrow switches BNC connectors, reducers, photolok, developer, PC board, sensitive & normal, boxes, wire cutters, strip-pers, Edge connectors, pots, batteries, digital pulsers, logic probes, proto-boards, vero board.

This is just a small sample of what we stock, if you like to see more send £1.00 to us for our NEW 1983 CATALOGUE.

EDGE CONNECTORS

ZX81 E.C.	2.98
Spectrum E.C.	3.78
VIC 20 E.C.	3.78
50 Way E.C.	3.30
18 Way E.C.	2.80
64 Way E.C. Plug	2.50
64 Way E.C. Socket	4.80
31 Way E.C. Plug	2.00
31 Way E.C. Socket	2.10

We stock a very wide range of opto-devices, from Infra-Red to LED's to Opto-Couplers.

Check us out for competitive prices and helpful service.

BOOKS

*New Books

Please Note. Books are VAT exempt but add £1.00 to cover P/P

The 9900 Family Data Book	10.00
The Opto-Electronics Data Book	4.00
The Bipolar Microcomputer Databook	4.50
The Interface Circuits Data Book	7.00
The TTL Data Book	8.50
MDS Memory Data Book	3.95
The Linear Control Circuits Data Book	4.00
The Voltage Regulator Data Book	4.50
The Power-semiconductor Data Book	9.00
*TTI Data Book Volume I	9.00
*TTI Data Book Volume II	8.00
301 Circuits	5.00
Towers Transistor Equivalent	9.50
Towers Digital Selector	9.95
Towers Linear 10 Selector	7.50


Why not try our mail order service. It's fast and efficient. We take Barclay, Access, Am Exp, Diners or Cheque. Cheques made payable to Bradley Marshall Ltd.

PLEASE REMEMBER TO ADD VAT AT 15% + 70p P&P

NOW 'LIVE' THE AMBIT TOP TEN


* TOBIE DISTRIBUTOR OF THE YEAR *

AA NICADS



High quality Ever Ready nickel cadmium rechargeable batteries.
Size: 14.5x50mm; 1.2V; Capacity: 500mAh
Stock No. 01-12004 Price: 0.80


C NICADS



High quality Ever Ready nickel cadmium rechargeable batteries.
Size: 26 x 49mm; 1.2V; Capacity 2.2AH
Stock No. Price: 2.35

CRYSTAL FILTER

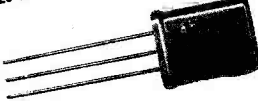A crystal filter for the first IF of CB receivers, in place of the usual ceramic filter can perform the single most significant improvement in blocking and cross mod in most circuits.
Model: 10M15A; Centre Freq: 10.7MHz; Band Width: 15kHz(3dB); Term Imp: 3kΩ
Stock No. 20-10152 Price: 1.99



MODEM KIT


A 300 baud full duplex originate only acoustically coupled modem. Use with any home computer with RS232 capability.
Not PO approved!!!



Electronics Stock No. 41-00201 Price: 19.94
Hardware Stock No. 41-00208 Price: 12.00


VEROBOARD

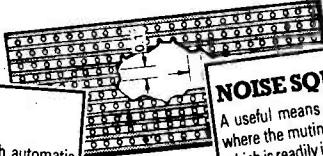0.1" pitch. No. holes: 36x50; Size("): 3.75x3.75.
Stock No. 21-09003 Price: 1.14




CH4/RX4

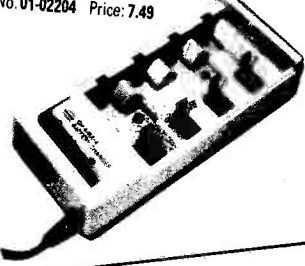Will recharge AA, C, D and PP3 size cells with automatic voltage selection.
Stock No. 01-02204 Price: 7.49



NOISE SQUELCH SYSTEM


A useful means of curing the deficiencies of NBFM sets where the muting control is derived from the signal level - which is readily influenced by ignition noise etc.
Kit Stock No. 40-44362 Price: 4.12
Built Stock No. 40-44363 Price: 8.45



FET DIP OSCILLATOR


Stock No. 40-16215 Price: 18.79

An essential piece of test equipment for the RF constructor. GDO or absorption wavemeter function covering 1.6-215MHz in five ranges.
Fibre-glass PCB, all components, all hardware, punch, painted and screen printed case, wire etc. for coils and printed scale.



Z8 TBPDS

Based on the Z8 basic/debug CPU is the most adaptable and understandable entry to this design on MPU based control systems.
Needs only to be connected to an RS232 terminal or a home computer configured as one, to provide complete program development/support.
Stock No. 40-00802 Price: 160.00



SCHOTTKY DIODE BALANCED MIXER

Hermetically sealed for receiver and modulator applications. SBL1, 1-500MHz premium type.
Stock No. 12-00003 Price: 4.68



Please add 60p postage & packing per order

AND LOTS, LOTS MORE IN THE CATALOGUE AVAILABLE FROM JULY
ALL PRICES EXCLUDING VAT

Ambit international
200 North Service Road
Brentwood, Essex
CM14 4SG

Telecom directory:
Consumer 0277-230909
Industrial 0277-231616
Telex 995194 AMBIT G
DATEL 0277-232628



TELEPHONE SALES 8 am - 7 pm MON - FRI 9 am - 6 pm SAT

IC UPDATE

Dear Reader,

What we've indulged in here is a slightly speculative venture, in that neither of the two ICs featured this month are actually available to the hobbyist, so far as we know (if you're in industry, then you'll be able to get the LM2877/8 from your Nat Semi supplier, and the RC4193 from Raytheon). However, we think that by bringing these to the light of day, we shall motivate someone, somewhere to stock them. And far be it from us to suggest our advertisers, but a word in their ear from you may not go amiss . . .

RC4193 Switched Mode PSU

What, not another switched mode PSU? Well, yes, but this one can keep your tranny going for longer, amongst many other applications.

The RC4193 is a monolithic switching regulator IC that, with very few external components is capable of stepping up or down, or inverting, with a typical efficiency of 80%.

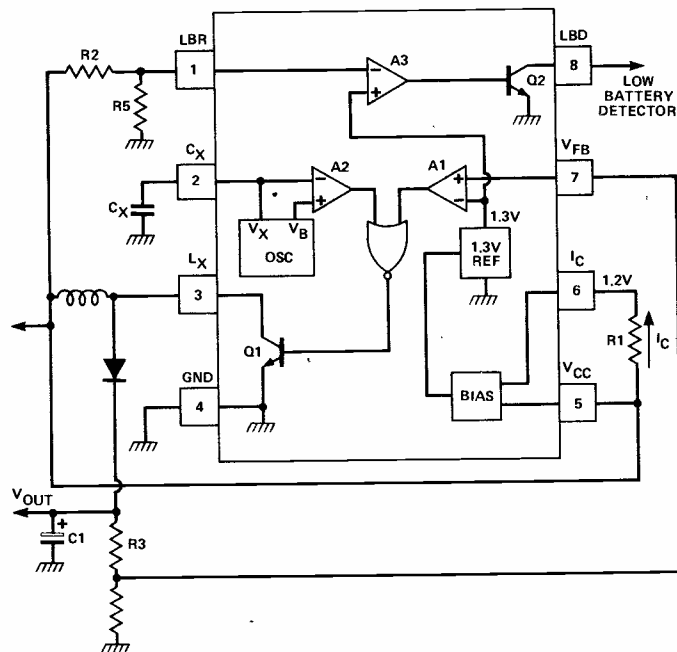


Fig. 1 RC4193 functional diagram.

Principles of Operation

The circuit has an on chip 1.31 V band gap reference with a typical TC of 50ppm. In addition to setting the bias currents in the 4193, this voltage is used as the reference at the input of comparators A1 and A3. The 1.31 V at the input of A1 is used as the threshold to compare to the feedback output voltage at pin 7 (V_{FB}). The output of A1 is fed to a NOR gate which is used to gate the output of the oscillator comparator (A2) which turns off Q1 whenever

V_{FB} is greater than 1.31V. Note when the output of A1 of A2 is high the switch transistor Q1 cannot turn on.

The oscillator has its frequency determined by a single capacitor C_x and outputs two waveforms, a square wave V_b and a saw tooth V_x (which appears at pin 2) both of which appear at the input of A2. The portions of the waveform where Q1 can be saturated as a result of the oscillator, are labelled T_c in Fig. 2, and the portion of the waveform where Q1 would be off is labelled T_o . Q1 can

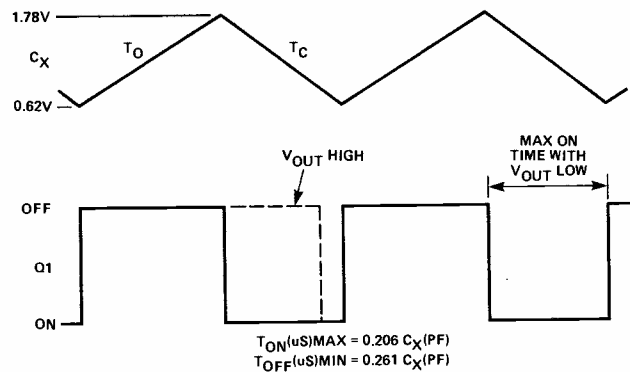


Fig. 2 Switching timing diagram.

be saturated only when V_{FB} is less than 1.31V. The voltage of the sense line from the R3/R4 voltage divider at the V_{FB} pin is directly proportional to the output voltage V_{OUT} , where $V_{OUT} = 1.31 (R3 + R4)/R4$. When V_{FB} is less than 1.31V, Q1 will saturate on every negative going oscillator cycle until V_{OUT} reaches the programmed value.

The 4193 also includes an uncommitted comparator and output transistor shown as A3 and Q2 in Fig. 1. The 1.31V internal reference is used as the threshold at the + input of A3. The voltage divider R2/R5 is used to determine the voltage at which Q2 switches. When the voltage at LBR (pin 1) falls below 1.31V then Q2 will saturate. A3 has about 0.7 μ A of hysteresis to produce a positive turn on/turn off at LBD (pin 8). The voltage at which Q2 switches is determined by $V = 1.31 (R2 + R5)/R5$.

Absolute Maximum Ratings

Internal Power Dissipation	500mW
Supply Voltage (without external series pass transistor)	24V
Operating Temperature Range	0°C to +70°C
Switch Current (I _{sw})	150mA
Reference Set Current (I _c)	1mA
V _{FB} , LBR, C _v Voltage	
L _v , LBD Voltage	24V

ed with any input between 9.3V and 2.4V.

If a lower supply voltage can be tolerated, the output of the 4193 can be set to start regulating at 7V (1.16V/Cell), effectively keeping the 4193 in its quiescent state (drawing only 150μA) until the battery voltage falls to 7.5V. Below 7.5V the 4193 will regulate the V_{OUT} at 7.0V until the battery falls below 2.4V. In this circuit R2 and R5 are used to indicate a low battery condition when the input voltage falls below 5.9V; any other voltage can be selected by changing the value of R2. If the Low Battery Detector circuitry is not going to be used, leave pin 1 and 8 unconnected. As mentioned previously, the top of R5 can also be connected to V_{OUT} when a low output indication is

PARAMETERS	CONDITIONS	MIN	TYP	MAX	UNITS
Supply Voltage, V _{CC}		2.4		24	V
Reference Voltage (internal), V _{REF}		1.24	1.31	1.38	V
Switch Current, I _{sw}	V ₃ = 400mV	75	100		mA
Quiescent Current, I _{CC}	Measure at Pin 5 I ₃ = 0		135	200	μA
Efficiency			80		%
Line Regulation	0.5V _O < V _{CC} < V _O		0.08	0.5	% V _{OUT}
Load Regulation	V _{CC} = 0.5V _O P _I = 150mW		0.2	0.5	% V _{OUT}
Operating Frequency, f _o		0.1	25	150	kHz
Reference Set Current, I _c		1	5	50	μA
Switch Voltage	I ₃ = 100mA		0.4	1	V
Switch Leakage Current	V ₃ = 24V		0.01	5	μA
Supply Current (Disabled)	I _c < 0.01μA		0.1	5	μA
Low Battery Bias Current	V ₁ = 1.2V		0.7		μA
Capacitor Charging Current			5.0		μA
Capacitor Threshold Voltage +			1.78		V
Capacitor Threshold Voltage -			0.62		V
Feedback Input Current	V ₇ = 1.3V		0.1		μA
Low Battery Output Current	V ₈ = 0.4V, V ₁ = 1.1V	100	600		μA

Table 1 Electrical characteristics

The 4193 series circuits contain an internal bias network which maintains the correct operating currents to the 4193 independent of temperature and input voltage variations. The internal bias network is turned on by supplying a current I_c between 1μA and 100μA into pin 1, and no change will result in the operating characteristics when I_c is varied over this range. To shut down the 4193, simply force pin 1 to less than 0.5V by using a mechanical switch or open collector transistor. The quiescent current in the 4193 will fall to less than 5μA (typically less than 0.1μA).

Design Equations

Table 2 is a set of design equations which can be used to determine resistor, capacitor and inductor values for step-down, step-up and voltage inverting applications. To use the equations, you determine the oscillator frequency (f_o), input voltage (V_{IN}), output voltage (V_{OUT}) and maximum output load current (I_L).

Basic Step-Up Switching Regulator

Figure 5 is the basic low current step-up configuration to be used for most battery powered applications requiring less than 150mW of load power (when V_{IN} > 0.5 V_{OUT}).

The output voltage V_{OUT} is determined by the expression 1.31 (R3 - R4)/R4; in this case V_{OUT} would be 9.0V. This configuration makes a good substitute for a 9V transistor battery, since a stable output voltage will be achieved

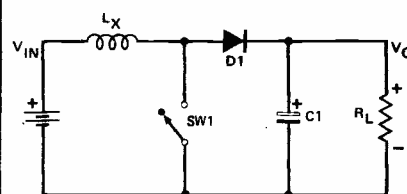


Fig. 3 Basic circuit for stepping up mode.

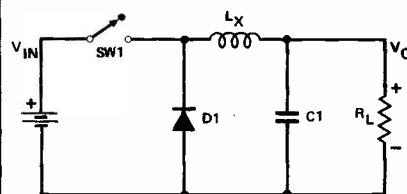


Fig. 4 Basic stepping down circuit.

	Step Up	Step Down	Inverting
R1(M)	$\frac{V_{IN} - 1.2}{5\mu A}$	$\frac{V_{IN} - 1.2}{5\mu A}$	$\frac{V_{IN} - 1.2}{5\mu A}$
R2(M)	$\frac{V_{IN} - 1.31}{5\mu A}$	$\frac{V_{IN} - 1.31}{5\mu A}$	$\frac{V_{IN} - 1.31}{5\mu A}$
R3*	$\frac{V_{OUT} - 1.31}{I_1}$	$\frac{V_{OUT} - 1.31}{I_1}$	$\frac{V_{OUT}}{I_1}$
R4*	$\frac{1.31}{I_1}$	$\frac{1.31}{I_1}$	$\frac{1.31}{I_1}$
R5	261kΩ	261kΩ	261kΩ
C _x (pF)	$\frac{2.14 \times 10^6}{f_o}$	$\frac{2.14 \times 10^6}{f_o}$	$\frac{2.14 \times 10^6}{f_o}$
L _x	$\frac{0.3V_8(V_{OUT} - V_{IN})}{f_o I_{LOAD} V_{IN}}$	$\frac{0.3V_{OUT}}{f_o I_{LOAD}}$	$\frac{0.3V_{IN} V_{OUT} }{f_o I_{LOAD}(V_{IN} + V_{OUT})}$
Cl	$\frac{2V_{OUT} - V_{IN}}{4f_o V_{OUT} V_R}$	$\frac{I_{LOAD}}{4f_o V_R}$	$\frac{0.15I_{LOAD}N + 2 V_{OUT} }{f_o V_{IN}(V_{IN} + V_{OUT})V_R}$
R6	$\frac{35V_{IN}}{I_{LOAD}V_{OUT}}$	$\frac{35}{I_{LOAD}}$	$\frac{35V}{I_{LOAD}(V_{IN} + V_{OUT})}$
R7	$\frac{R6}{7}$	$\frac{R6}{7}$	$\frac{R6}{7}$

Units are ohms, farads, henries, and hertz unless indicated otherwise.
I₁ = current into pin 1; recommended value 100μA.

Table 2 Design equations for the three modes.

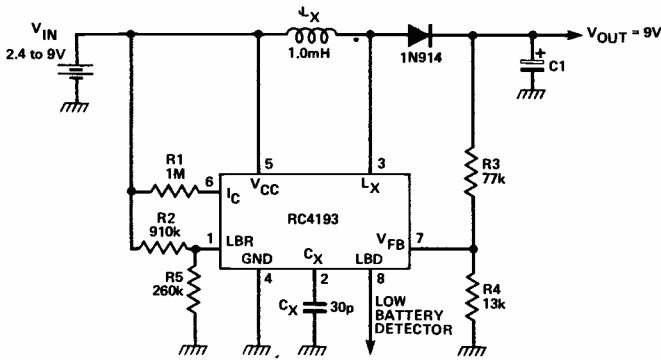


Fig. 5 RC4193 low current step-up mode.

desired.

A feature of the 4193 is the ability to shut off when pin 6 is forced below 0.5V. An example of this feature is shown in Fig. 6. In this circuit as long as V_c remains low the output will regulate to 5V. This type of circuit can be used to back up the main supply voltage when line interruptions occur, a particularly useful feature when using volatile memory systems.

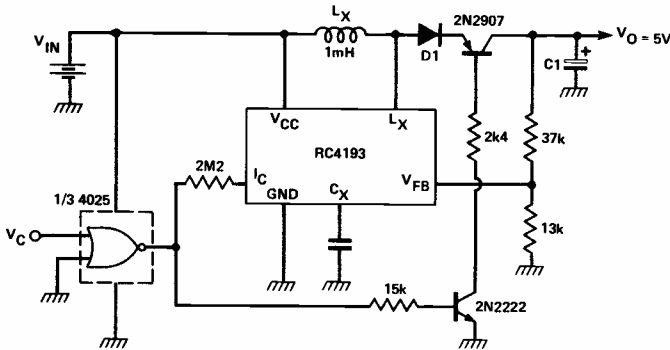


Fig. 6 RC4193 battery-back-up circuit.

In step-up application, power to the 4193 can be derived from the output voltage by connecting the V_{CC} pin and the top of R_1 to the output voltage (for example see Fig. 7). One requirement is that the battery voltage must be greater than 3.0V when the circuit is energized or else there is not enough voltage at the V_{CC} pin to operate the 4193. However, once running, the battery can decay to 1.0V before the circuit stops operating.

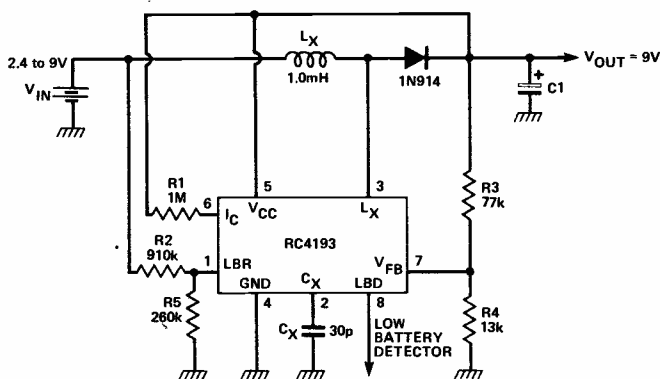


Fig. 7 Bootstrapping the supply to the RC4193.

Basic Step-Down Switching Regulator

Since the switch transistor in the 4193 is in parallel with the load a method must be used to convert it to a series connection; the circuit of Fig. 8 accomplishes this.

The 2N2907 replaces S1 of Figure 4, and R_6 and R_7 are added to provide the base drive to the 2N2907 in the correct polarity to operate the circuit properly; refer to Table 2 for equations for component values. Since the L_X pin is capable of sinking 100mA, high current switching transistors can be used in place of the 2N2907.

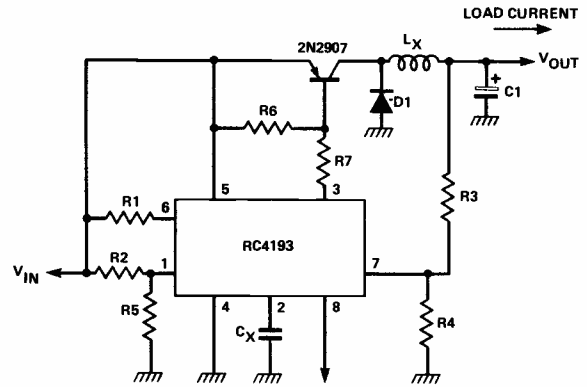


Fig. 8. RC4193 step-down mode.

Greater Than 30 Volt Application

Adding a zener diode in series with the base of the 2N2907 allows the input voltage to increase by the value of the zener, with only a slight decrease in efficiency. As an example, if a 24V zener is used, the maximum input voltage can go to 48V.

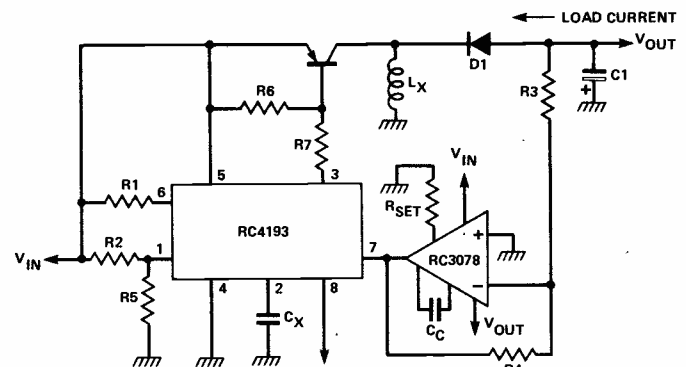


Fig. 9 RC4193 used as an inverter-regulator.

Inverting Switching Regulator

Many single-supply systems require an occasional negative voltage for a specific application; this circuit will meet those needs.

The circuit is similar to the type used in Fig. 8, except the location of L_X and the diode are reversed and a micropower op-amp RC3078 is added to provide inversion for the sense voltage. The output voltage is $1.31 R_3/R_4$.

The RC3078 operates at a closed-loop gain of close to one in most applications, therefore the value of C_c must be such to frequency compensate the RC3078 for unity gain conditions. The value for R_{SET} will determine the quiescent current in the 3078 and for micropower applications can be set to operate at approximately $10\mu A$. Where a larger amount of amplifier quiescent current can be tolerated, a ground sensing op-amp such as the LM324 or RC3403A can be used, eliminating the need for R_{SET} and C_c .

An important point is that pin 7 must be below 1.3V when $|V_{OUT}|$ is below the design output voltage or else the circuit will not start.

Due to their output stage design, op-amp types similar in design to the 741 may cause the circuit to not start properly since they fail to keep pin 7 below 1.3V when power is first applied.

LM2877/8 Audio Power Amps

The LM379 has had a good innings as linear ICs go, but it's now being replaced by the LM2877 and LM2878 in manufactured equipment.

The LM2877/8 are monolithic dual power amplifiers designed to deliver 4W (2877) or 5W (2878) continuous into eight ohm loads. Each power amplifier is biased from a common internal regulator to provide good power supply rejection and output centering. Both devices are internally compensated for gains greater than 10 and come in 11-lead single in-line packages.

Absolute maximum ratings

Supply voltage	26 V (35 V 2878)
Input voltage	+0.7 V
Operating temperature	0°C to +70°C
Junction temperature	150°C

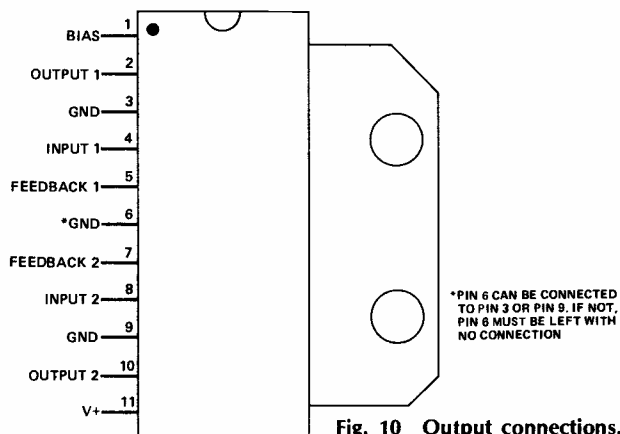


Fig. 10 Output connections.

Electrical Characteristics for LM2877: Where those of the LM2278 differ, they are given in brackets; otherwise the same figure applies.

$V_S = 20V$ (22V), $T_{TAB} = 25^\circ C$, $R_L = 8\Omega$, $A_v = 50$ (34 dB) unless otherwise specified

Note 1: For operation at ambient temperatures greater than 25°C, the LM2877 must be derated on a maximum 150°C junction temperature using a thermal resistance which depends upon device mounting techniques.

PARAMETER	CONDITIONS	MIN	TYP	MAX	UNITS
Total Supply Current	$P_O = 0W$		25(10)	50	mA
Operating Supply Voltage		6		24(35)	V
Output Power/Channel	$f = 1 \text{ kHz}$, THD = 10%, $T_{TAB} = 25^\circ C$ $V_S = 20V$ $V_S = 12V$, $R_L = 4\Omega$	4.0(5.0)	4.5(5.5)		W
Distortion, THD	$f = 1 \text{ kHz}$, $V_S = 20V$ $P_O = 50 \text{ mW/Channel}$ $P_O = 2W/Channel$		0.1(0.2)		%
			0.07(0.14)	1	%
Output Swing	$R_L = 8\Omega$		$V_S - 4$ ($V_S - 6$)		Vp-p
Channel Separation	$C_F = 50 \mu F$, $C_{IN} = 0.1 \mu F$, $f = 1 \text{ kHz}$ Output Referred $V_S = 20V$, $V_O = 4 \text{ Vrms}$	-50	-70		dB
PSRR Power Supply Rejection Ratio	$C_F = 50 \mu F$, $C_{IN} = 0.1 \mu F$, $f = 120 \text{ Hz}$, Output Referred $V_S = 20V$, $V_{RIPPLE} = 1 \text{ Vrms}$	-50	-68(-60)		dB
Noise	Equivalent Input Noise $R_S = 0$, $C_{IN} = 0.1 \mu F$, BW = 20 Hz-20 kHz		2.5		μV
Open Loop Gain	$R_S = 0$, $f = 1 \text{ kHz}$, $R_L = 8\Omega$		70		dB
Input Offset Voltage			15		mV
Input Bias Current			50(100)		nA
Input Impedance	Open Loop		4		M Ω
DC Output Level	$V_S = 20V$ (22V)	9(10)	10(11)	11(12)	V
Slew Rate			2.0		V/ μs
Power Bandwidth			65		kHz
Current Limit			1.0(1.5)		A

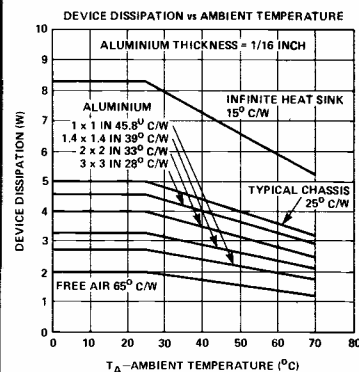


Fig. 11 Device dissipation vs. ambient temperature (LM2877).

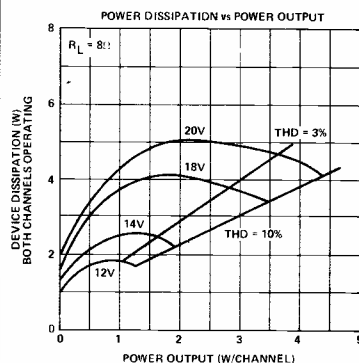


Fig. 12 Power dissipation vs. power output (LM2877).

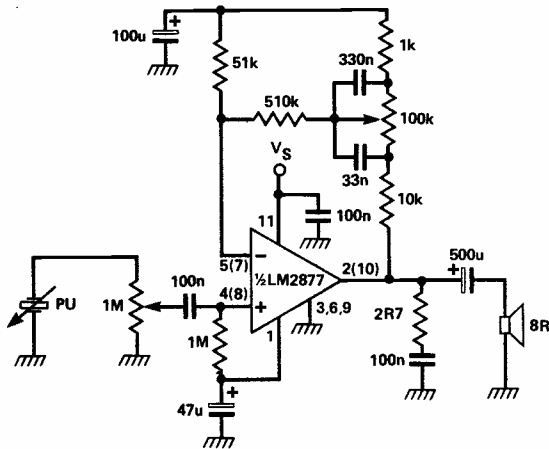


Fig. 13 Ceramic PU amplifier with bass control.

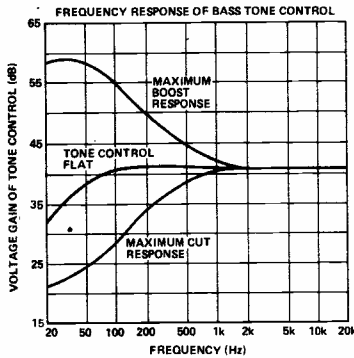


Fig. 14 Frequency response of bass control in Fig. 13.

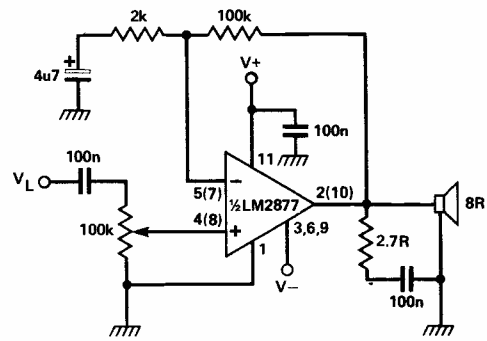


Fig. 15 Non-inverting amplifier using split supply.


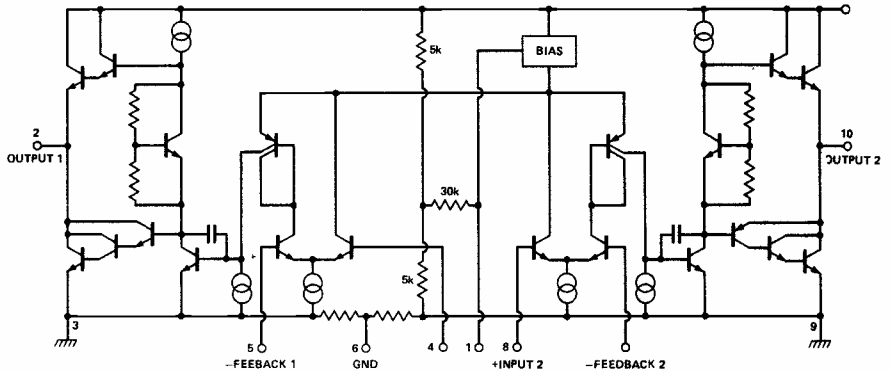


Fig. 16 Internal circuit.

Next month we'll take a look at a few more newcomer ICs.

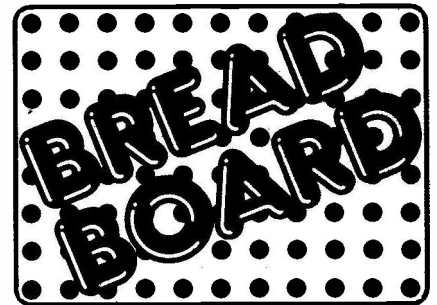**If you missed
out on Breadboard
'79, '80, '81 and '82.....
Now's the time to catch up
with BREADBOARD '83**



The premier electronics show for the enthusiast. Moved this year for your convenience and comfort to the Cunard International Hotel, Hammersmith, London W6

Friday November 25th 10am - 6pm
Saturday November 26th 10am - 6pm
Sunday November 27th 10am - 4pm

Why not bring the family to the show and enjoy a weekend in London? We have arranged a complete hotel package for our visitors to the exhibition. All inclusive rail tickets also available. Send now for details of what we, the organisers, can offer you.

Write to:
Breadboard '83
ASP Exhibitions
145 Charing Cross Road
London WC2H 0EE

This year's features include

- Computer controlled model railway competition. (send off for entry form now)
- Kits to build all sorts of projects.
- Magazines and books covering most aspects of electronics.
- Components and tools at bargain prices.
- Technical advice on electronics projects and Ham Radio technique.
- Clubs/User groups for amateur electronics and computing
- Lectures by professionals on a wide range of topics. eg. Basic Tuition For Beginners,
- Holography and Producing Printed Circuit Boards.

ORIC

SOFTWARE

from TANSOFT

ORIC CHESS



A superb chess game written in Basic with a Machine Code Move Search Routine. Features high resolution colour graphics, record of moves, allows Castling and En-Passant. 5 levels of play and computer can play black or white.

ONLY £9.99 inc VAT

48K only

ZODIAC



A 36K adventure game that will test your intelligence and patience for hours. Find the 12 hidden signs of the Zodiac to discover incredible treasures. Can you ward off the angry Yeti? What is the meaning of the radio that plays the 'Archers' over and over again (through your loudspeaker!)?

Only £9.99 inc VAT

48K only

ORIC FLIGHT



Can you fly your new 787 jet on to the runway without crashing, stalling or running out of fuel? Full digital instrument readout plus cockpit view of final runway approach. Superb graphics and sound.

Only £7.95 inc VAT

48K only

Please send me	Quantity	Total
Oric-Chess at £9.99		
Zodiac at £9.99		
Oric-Flight at £7.95		

TOTAL

Postage per cassette is 40p

Name _____
Address _____

Please send me latest price list _____

Please allow 28 days for delivery

All cheques payable to
TANSOFT LTD
3 CLUB MEWS
ELY
CAMBS
CB7 4NW

Tansoft is the software division of
Tangerine Computers.

UNIVERSAL EPROM PROGRAMMER

Get to grips with the bits using our Universal EPROM programmer. Design and development by Mike Bedford.

EPROMs provide a convenient means of storing commonly used software, but many micro-computer users are deterred from using this media due to the difficulties of erasure and programming. EPROM programmers are both commercially available and have been featured as constructional articles in some magazines, but the former are relatively expensive and the latter tend to be limited as regards types of EPROM supported. For these reasons, it was considered appropriate to develop a universal EPROM programmer which could be built by the amateur for a modest sum. The programmer presented here will support the following EPROMs: 2758, 2716, 2516, 2732, 2732A, 2532, 2764, 2564, 27128 and 27256. This list includes every single supply version of the 27-Series and 25-Series devices up to and including 256k bit capacity, which seems likely to be the largest EPROM which will be produced as further development will probably be of EAROMs and EEPROMs. The programmer is intended for use in conjunction with a 6502 computer system and appropriate software is presented. Although the hardware is designed to support the 27256, this one EPROM is not as yet supported by the software due to lack of preliminary data on this device, the chip itself having not been released by the manufacturer at the time of writing. To complete the requirements for programming EPROMs, some hints are given on building an erasure unit.

Hardware

The hardware has been designed for a Tangerine Microtan system, the physical dimensions of the circuit board being selected such that it will plug directly into the system rack. Non-Tangerine users should not be deterred,


however, as electronically it should be quite simple to interface this card to any computer using the 6502 or 6809 processors. No special power supplies are required as all voltages required for programming are derived from a single +5v supply.

Although the PCB has sufficient space for a zero insertion force socket to be mounted on board, it is probably more convenient, especially if the card is to be rack mounted, to mount this socket in a separate console, making a connection with a length of ribbon cable. Note that a switch should be provided on the console to isolate V_{pp} and V_{cc} on pins 1 and 28 respectively. This is necessary since inserting or removing an EPROM with these supplies present may result in its destruction.

If the console is not used, switch SW1 should be mounted on board to isolate these supplies. On EPROMs which have V_{pp} and V_{cc} on other pins, these supplies may be isolated under program control. It will also be noticed that only a single zero insertion force socket

has been provided on PCB. This decision was taken on grounds of economy and some constructors may prefer to add a 24-pin socket in addition. If a single 28-pin socket is used, 24-pin devices should be inserted into the bottom part of the socket, ie leaving pins 1, 2, 27 and 28 empty. Table 1 shows the pin outs of all EPROMs which are supported.

The programmer applies a TTL level to all pins with the exception of pin 1 which is connected to V_{pp} , pin 14 (0V) and pin 28 (+5v). V_{pp} is program selectable to +25 V, +21 V or +5 V and may also be applied to pins 22 and 23 as an alternative to a TTL level. To summarise this information, the programmer may be considered as a glorified 29-bit output port. This being the case, and since the circuitry required to implement the above would not completely fill a 8" x 4½" PCB, it seemed appropriate at the cost of only two more ICs to add four additional 8-bit output ports to make maximum use of the board space available. These ports are completely independent from the

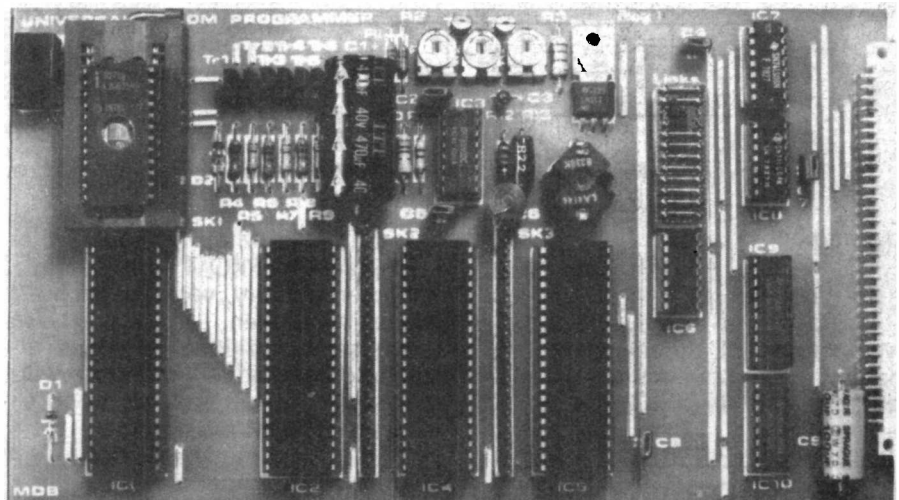

The Universal EPROM Programmer. Note that this prototype differs slightly from the final version — in particular, the component numbering is completely different!

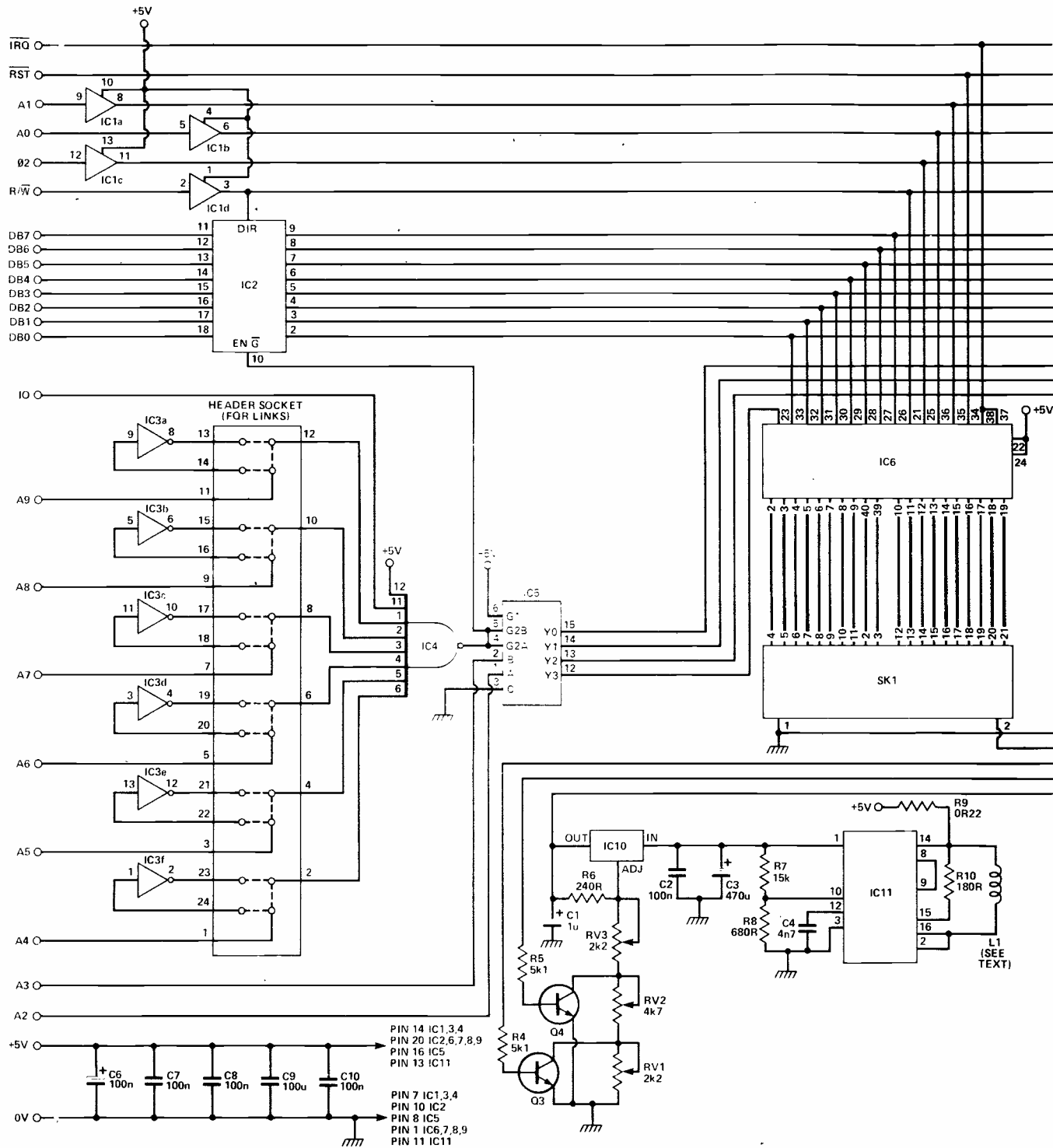


Fig. 1 Circuit diagram of the Universal EPROM Programmer.

programmer.

Software

In order to be a useful development tool, the following functions are the minimum requirements of an EPROM programmer:

1. Read data from an EPROM into computer memory;
2. Compare the contents of an EPROM with the contents of computer memory;


3. Test an EPROM for erasure;
4. Program an EPROM from data in computer memory, verifying each byte as it is written.

In fact, some additional functions have also been added and these will be described under the section on using the EPROM programmer.

Table 2 is a mode selection table for all supported devices, showing the read, program, verify and standby modes, these being the modes necessary to implement the

The design is based around four 6821 20-bit PIOs. The circuitry comprising IC3, IC4 and IC5 provides the interface to the Tangerine bus and, in conjunction with the links, allows the board to be configured to occupy a 16-byte block within the 1k I/O area. IC1 and IC2 are used to buffer various signals in order that no more than one TTL load is presented to any bussed input. Of the four 6821s, IC6 and IC7 provide the four independent I/O ports. These being connected to the outside world via SK1 and SK2, whereas IC8 and IC9 are used to drive the EPROM programmer. Most of the signals required to drive the pro-

PROJECT : EPROM Programmer

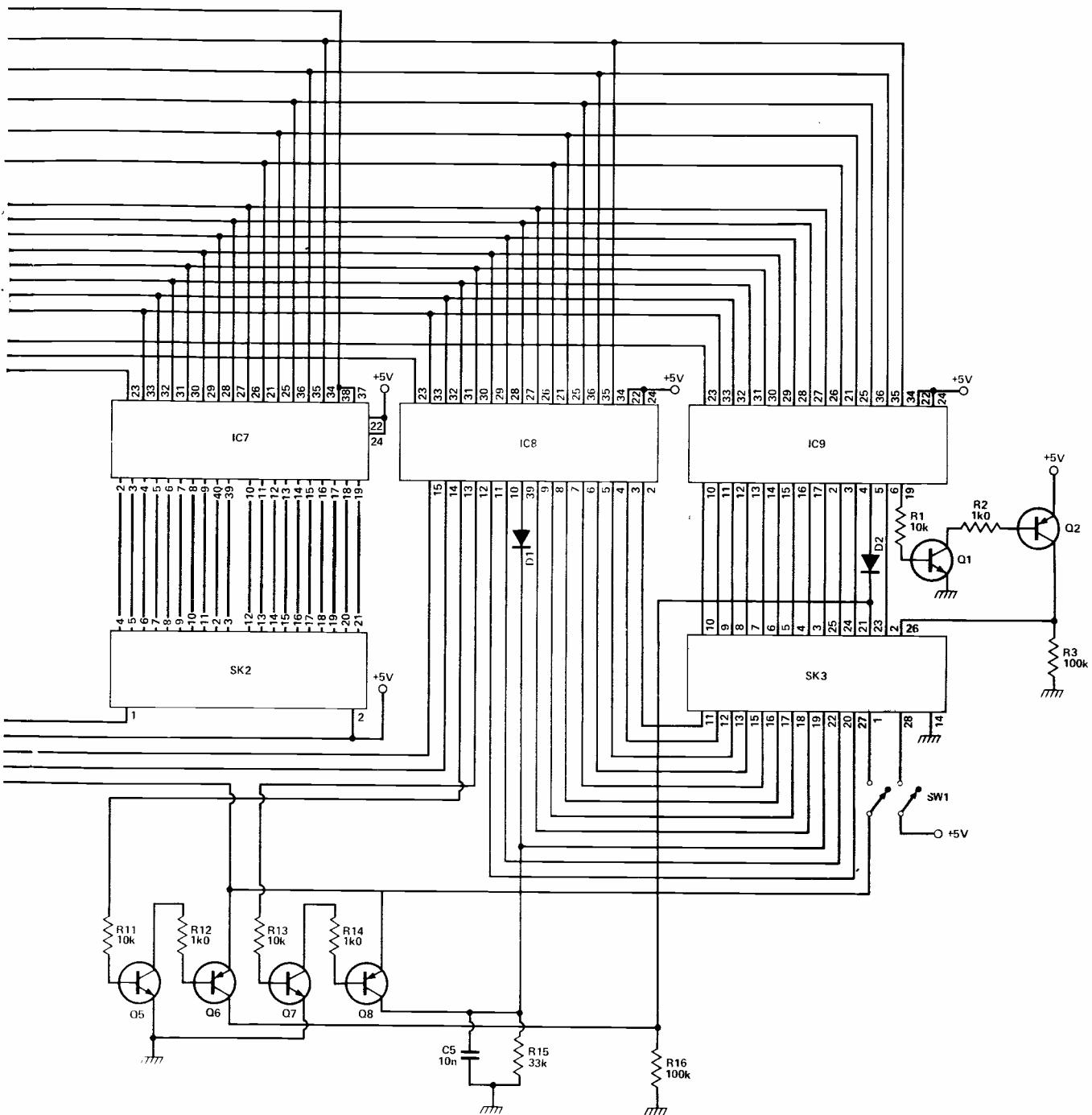

HOW IT WORKS


grammer are TTL levels and are taken directly from the two 6821s to the ZIF socket, SK3. Pin 26 on SK3 is slightly different in that although it is a pure TTL signal on all 28 pin devices, it is the V_{cc} supply on all EPROMs in 24-pin packages and hence requires a much greater current capacity than is available from a port on a 6821. Q1 and Q2 are therefore used to switch the +5 V supply to SK3 pin 26 under the control of IC9/CB2 (pin 19). A similar technique is used to switch V_{pp} onto SK3 pins 22 and 23 using transistor pairs Q5/Q6 and Q7/Q8 respectively. Since these two pins on SK3 are also required to present TTL

levels under different conditions, they are also connected to 6821 ports, isolating these signals by use of Germanium diodes D1 and D2 respectively.

It should be noted that when a 6821 is required to drive a transistor, a 'B' port is used, these having a greater current sourcing capacity than 'A' ports, and when a port needs to be isolated by a diode, an 'A' port is used as these give a full +5 V high signal so that, even allowing for the voltage drop across the diode, a good TTL high is presented. The V_{pp} supply is generated from the +5 V supply using IC11, a 78S40 switching regulator IC, in connection with timing

components L1 and C4. Although this component should be capable of regulating V_{pp} to within the required limits, experiments showed that it is advisable to select R7 and R8 such that IC11 would output about +30 V and use a separate LM317MP regulator to give the required voltage. Since V_{pp} may need to be +25 V, +21 V or +5 V, Q3 and Q4 are used, to switch out portions of the resistor chain between the regulator adjust terminal and 0 V hence altering the output voltage. These two transistors are connected to IC8 PB4 and PB5 (pins 14 and 15) hence allowing V_{pp} to be changed under program control.


27 256	27 128	25 64	27 64	25 32	27 32/ 32A	27/ 25 16	27 58	IC/ PIN
VPP	VPP	VPP	VPP					/1
A12	A12	$\overline{CS1}$	A12					/2
A7	A7	A7	A7	A7	A7	A7	A7	1/3
A6	A6	A6	A6	A6	A6	A6	A6	2/4
A5	A5	A5	A5	A5	A5	A5	A5	3/5
A4	A4	A4	A4	A4	A4	A4	A4	4/6
A3	A3	A3	A3	A3	A3	A3	A3	5/7
A2	A2	A2	A2	A2	A2	A2	A2	6/8
A1	A1	A1	A1	A1	A1	A1	A1	7/9
A0	A0	A0	A0	A0	A0	A0	A0	8/10
D0	D0	D0	D0	D0	D0	D0	D0	9/11
D1	D1	D1	D1	D1	D1	D1	D1	10/12
D2	D2	D2	D2	D2	D2	D2	D2	11/13
GND	GND	GND	GND	GND	GND	GND	GND	12/14

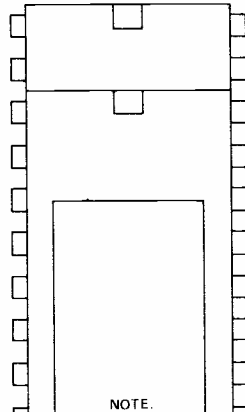

NOTE:
 1) PIN NUMBERS TO 28 PIN PACKAGES. SUBTRACT 2 FROM PINS 3-26 FOR 24 PIN PACKAGE PIN NUMBERS.
 2) OE (27 SERIES) IS EQUIVALENT TO CS (25 SERIES).
 3) CE/PGM (27 SERIES) IS EQUIVALENT TO PD/PGM (NOT PD/PGM) (25 SERIES).

IC PIN	27 58	27/ 25 16	27/ 32 32A	25 32	27 64	25 64	27 128	27 256
/28					VCC	VCC	VCC	VCC
/27					\overline{PGM}	$\overline{CS2}$	\overline{PGM}	A14
24/26	VCC	VCC	VCC	VCC	N/C	N/C	A13	A13
23/25	A8	A8	A8	A8	A8	A8	A8	A8
22/24	A9	A9	A9	A9	A9	A9	A9	A9
21/23	VPP	VPP	A11	VPP	A11	A12	A11	A11
20/22	\overline{OE}	\overline{OE}	$\overline{OE}/$ VPP	PD/ PGM	\overline{OE}	PD/ PGM	\overline{OE}	\overline{OE}
19/21	AR	A10	A10	A10	A10	A10	A10	A10
18/20	$\overline{CE}/$ PGM	$\overline{CE}/$ PGM	\overline{CE}	A11	\overline{CE}	A11	\overline{CE}	\overline{CE}
17/19	D7	D7	D7	D7	D7	D7	D7	D7
16/18	D6	D6	D6	D6	D6	D6	D6	D6
15/17	D5	D5	D5	D5	D5	D5	D5	D5
14/16	D4	D4	D4	D4	D4	D4	D4	D4
13/15	D3	D3	D3	D3	D3	D3	D3	D3

Table 1 Pin-outs of all the EPROMs our programmer will process.

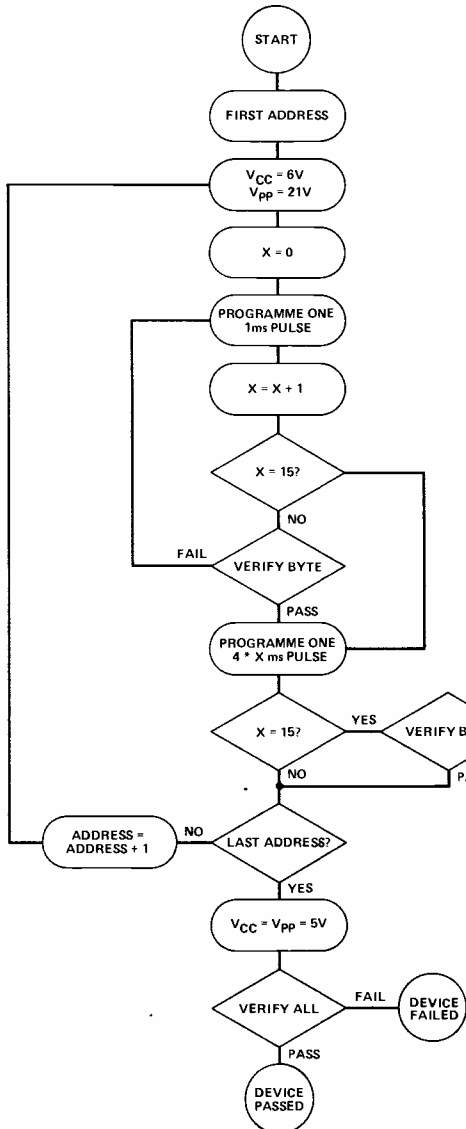

EPROM TYPE	FUNCTION	PIN	MODE				
			READ	STANDBY	PROGRAMME	VERIFY	
2758, 27/2516	*AR	19	VIL	VIL	VIL	VIL	
	$\overline{CE}/$ PGM	18	VIL	VIH	VIL → VIH	VIL	
	\overline{OE} VPP	20 21	VIL +5 V	X +5 V	VIH +25 V	VIL +25 V	
2732/32A	\overline{CE} $\overline{OE}/$ VPP	18 20	VIL VIL	VIH X	VIL **VPP	— —	
	2532	PD/PGM VPP	20 21	VIL +5 V	VIH +5 V	VIH → VIL +25 V	— —
2764, 27128	\overline{CE} \overline{OE} PGM VPP	20 22 27 1	VIL VIL VIH +5 V	VIH X X +5 V	VIL X VIH → VIL +21 V	VIL VIL VIH +21 V	
	2564	PD/PGM $\overline{CS1}$ $\overline{CS2}$ VPP	22 21 27 1	VIL VIL VIL +5 V	VIH X X +5 V	VIH → VIL VIL VIL +25 V	— — — —

NOTES:
 X = DON'T CARE
 * AR IS ONLY ON THE 2758
 ** VPP IS +25 V ON THE 2732, +21 V ON THE 2732A

Table 2 (above) Mode selection table.

Fig. 2 (left) Flowchart for intelligent programming mode.

functions mentioned. It may be noticed that some devices can perform both read and verify. Functionally, these modes are the same but verify is carried out with V_{pp} high, hence simplifying the program/verify process. From this table it may be seen that there is a great deal in common between the various EPROMs, hence simplifying the design of software.

PROJECT : EPROM Programmer

To get the full picture, the timing diagrams of each device should be scrutinised, but for the general user this information is probably not relevant. To summarise, however, EPROMs generally require about 50 ms to program each byte giving total programming times of from around 50 seconds for a 2758 to 13 minutes for a 27256. You may consider these times rather long, especially for the larger devices and although not implemented in the software presented here, there is an alternative programming method referred to as the *intelligent programming mode* which can reduce programming times by a factor of six for the 2764, 27128 and 27256. Figure 2 is a flow diagram of the functions which need to be performed in order to implement this method of programming. Notice that V_{cc} needs to be increased to +6V for this process to

be carried out and that there is no provision in the hardware to select this value of V_{cc} under program control. This need present no great problem, however, to the user wishing to implement this mode, as +6v may be switchable from the programming console, perhaps by deriving this voltage from the system +12v supply.

Any additions to, or modifications of the software will need to be made in the light of the information presented in Tables 3 and 4. These may be described as a programmer's view of the EPROM programmer, Table 3 showing the address of each register and Table 4 indicating which bits of the various 6821 ports connect to which EPROM pins or perform the various control functions required.

Construction And Alignment

Although the circuit of the programmer is of sufficient complexity that if it were to be produced commercially it would probably be double sided, it is not so complex that a single sided board would be impossible to design. It was considered that cost would be of prime importance to an amateur building a one-off project, and on these grounds it was artworked as a single-sided board. As a result of this, a number of insulated wire links need to be inserted prior to fitting the components. No special instructions are required on the fitting of components with the exception of socket SK3 and switch SW1. If a separate programming console is to be used, then an ordinary low profile DIL socket should be used as SK3, and two wire links should

Table 3 Register addresses.

FUNCTION	6821 NUMBER	REGISTER	OFFSET FROM BASE
	IC9	DDRA/ORA	00
	IC9	CRA	01
REGISTERS	IC9	DDRB/ORB	02
FOR	IC9	CRB	03
EPROM	IC8	DDRA/ORA	04
PROGRAMMER	IC8	CRA	05
	IC8	DDRB/ORB	06
	IC8	CRB	07
	IC7	DDRA/DRA	08
REGISTERS	IC7	CRA	09
FOR	IC7	DDRB/ORB	10
GENERAL	IC7	CRB	11
PURPOSE	IC6	DDRA/ORA	12
I/O	IC6	CRA	13
PORTS	IC6	DDRB/ORB	14
	IC6	CRB	15

Table 4 Port functions.

6821 NUMBER/PORT	SK3 PIN NO.	PROGRAMMER FUNCTION
IC9/PB0	10	A0
IC9/PB1	9	A1
IC9/PB2	8	A2
IC9/PB3	7	A3
IC9/PB4	6	A4
IC9/PB5	5	A5
IC9/PB6	4	A6
IC9/PB7	3	A7
IC9/PA0	25	A8
IC9/PA1	24	A9
IC9/PA2	21	A10 (EXCEPT 2758), AR (2758)
IC9/PA3	23	A11 (2732/32A/64/128/256), A12 (2564)
IC9/PA4	2	A12 (2764/128/256), $\overline{CS1}$ (2564)
IC9/CB2	26	A13 (27128/256), VCC (2758/16/32/32A, 2516/32)
IC8/PA0	11	D0
IC8/PA1	12	D1
IC8/PA2	13	D2
IC8/PA3	15	D3
IC8/PA4	16	D4
IC8/PA5	17	D5
IC8/PA6	18	D6
IC8/PA7	19	D7
IC8/CA2	22	\overline{OE} (2758/16/38/32A/64/128/256, 2516), PD/ \overline{PGM} (2532/64)
IC8/PB0	20	A11 (2532/64), $\overline{CE}/\overline{PGM}$ (2758/16, 2516), \overline{CE} (REMAINDER)
IC8/PB1	27	\overline{PGM} (2764/128), $\overline{CS2}$ (2564), A14 (27256)
IC8/PB2	22	VPP (2732/32A)
IC8/PB3	23	VPP (2758/16, 2516/32)
IC8/PB4	—	VPP + 5V SELECT*
IC8/PB5	—	VPP + 21V SELECT*

*NOT (VPP + 5) AND NOT (VPP + 21V) = + 25V SELECT

replace SW1. On the other hand, if the programmer is intended to be self contained on a single board, a zero insertion force DIL socket should be used as SK3 and switch SW1 is needed. Once the construction is complete, the links need to be configured to place the board at the desired address. The offset from the start of the I/O area is 16 times the binary number represented by the links. The best way to illustrate exactly how the links are used is probably graphically; Fig. 3 shows a few examples.

The other part of the circuit which requires setting up is associated with V_{pp} generation. This is very important as EPROMs will be destroyed if V_{pp} is more than 0V5 too high. The best way to check this

is with a voltmeter probe on the output of IC2, with IC8 removed from its socket. Apply +5 V to pin 14 of the IC8 socket and adjust RV3 until +5 V is recorded on the test meter. Now replace +5 V on pin 14 by +5 V on pin 13 of IC8 socket and adjust RV2 for +21 V on the meter. Finally, remove +5 V from pin 13 of IC8 socket and adjust RV1 for a potential of +25 V at IC2 output. Setting up is now complete.

Using The Programmer


The first stage in using the EPROM programmer is to load and run the support package software which is written in BASIC and assembly code. The user will first be prompted for EPROM type, valid responses being 2758, 2716, 2516, 2732, 2732A, 2532, 2764, 2564 and 27128. A request for a base address will then be made and the user should respond with a four-figure hexadecimal number. The base address is the address relative to which all references to computer internal memory are made and this means that the user does not need to be concerned with the actual absolute addresses in computer memory. The reasons for being able to select the base address are two fold. Firstly, to fit in with the memory map of any computer on which the software may be run and, secondly, to allow more than one set of data to be maintained at one time by using different base addresses. A table showing all the commands available will be printed before the *? prompt appears on the screen. When this prompt indicates that the program is waiting for input of a command, it is safe to insert or remove EPROMs from the ZIF socket, provided, of course, that the isolating switch is in the OFF position for 28 pin devices.

The following describes the function of the EPROM programmer support package commands. It should be noted that in each case, either the whole word or the initial letter may be used:-

(N)EW, (B)ASE These two commands cause the user to be prompted for a new EPROM type or a new base address respectively, hence allowing these two

parameters to be altered without exiting and re-running the program. **(T)EST** This performs a test on the EPROM, reporting whether or not it has been erased.

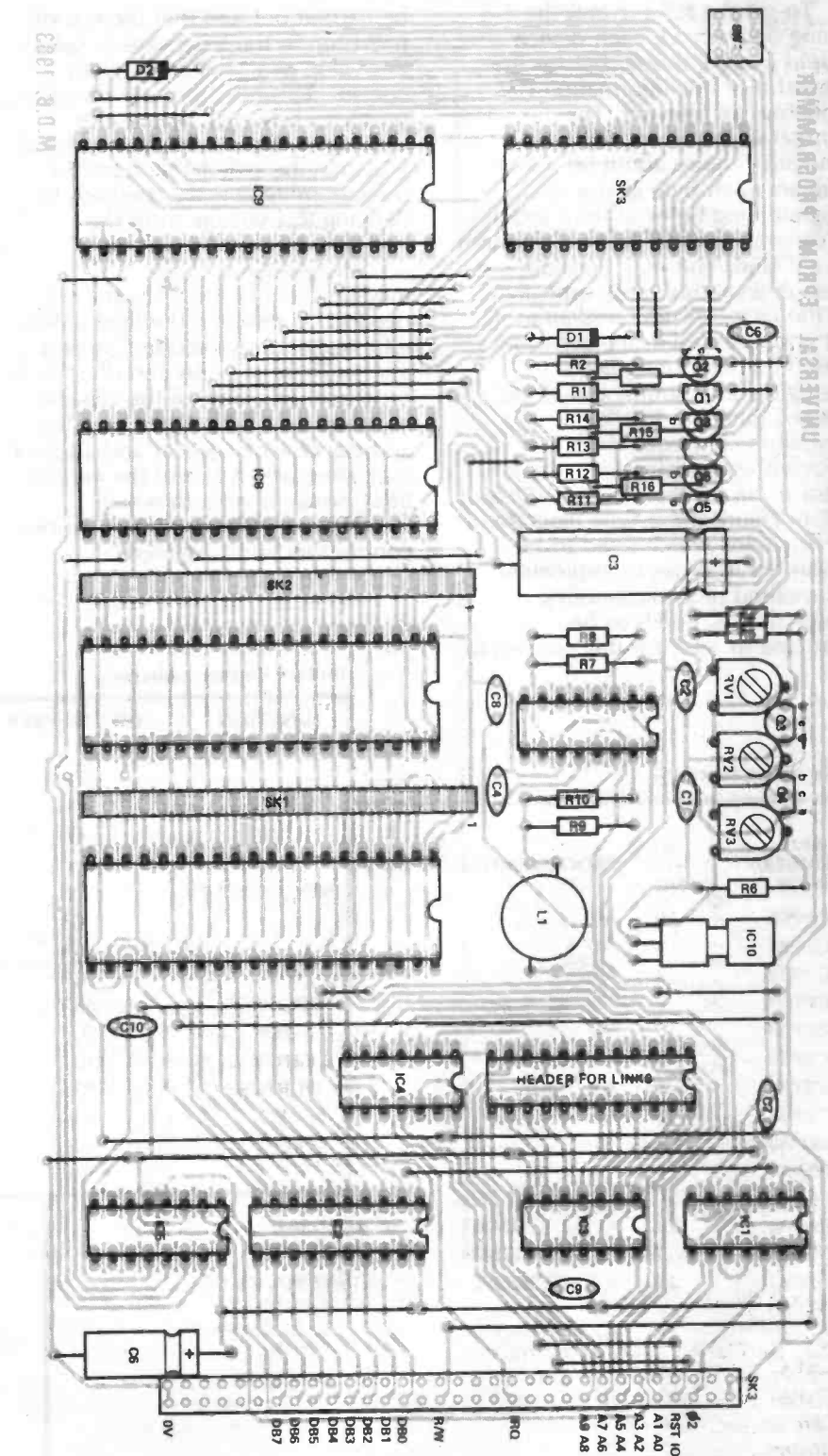(R)EAD, (P)ROGRAMME, (V)ERIFY These commands cause the user to be prompted for start and finish addresses which should be entered



Overlay diagram of the programmer.

as two four-figure hexadecimal numbers separated by a comma. These addresses define the portion of the EPROM to be used and also the portion of computer internal memory into which data will be written for a read operation or from which data will be read for program or verify operations. The computer

addresses are offset from the base address. In program and verify, any discrepancies between EPROM and computer memory will be reported. Such discrepancies will be printed, one per line, stopping after every 16 lines. Pressing return at this point will return to the *? prompt, whereas pressing any other key will

PROJECT : EPROM Programmer

PARTS LIST

RESISTORS (all $\frac{1}{4}$ W 5% unless stated)

R1, 11, 13	10k
R2, 12, 14	1k0
R3, 16	100k
R4, 5	5k1
R6	240R
R7	15k
R8	680R
R9	OR22 wire wound
R10	180R, 1W
R15	33k
RV1, 3	2k2 min horizontal preset
RV2	4k7 min horizontal preset

CAPACITORS

C1	1u 35 V axial electrolytic
C2, 7, 8, 9,	
10	100n ceramic
C3	470u 35 V axial electrolytic
C4	4n7 polyester
C5	10n ceramic
C6	100u 6V3 axial electrolytic
C10	10n ceramic

SEMICONDUCTORS

IC1	74LS126
IC2	74LS245
IC3	74LS04
IC4	74LS30
IC5	74LS138
IC6, 7, 8, 9	MC6821 (or similar)
IC10	LM317M
IC11	78S40
Q1, 3, 4, 5,	
7	BC184L
Q2, 6, 8	BC214L
D1, 2	OA91

MISCELLANEOUS

L1	34 turns 24 swg wire on RM6 pot core (AL = 250)
SK1, 2	0.1" pitch 22-way male molex connectors (or shorter ones made up to required length)
SK3	28 pin zero insertion force socket (or ordinary socket is console is used, see text)
SW1	two pole single throw switch (omit if using console)

One 16-way and one 80-way DIL headers and sockets; edge connector (2 x 32-way A+B DIN Euro connector, male angled pins, for Tangerine) PCB, wire, etc.

continue the programming or verification.

(L)IST, (M)ODIFY These commands probably duplicate facilities available in the computer monitor but are included here to allow minimum changes to be made to computer memory or data to be checked without the need to exit from this package. LIST will request start and finish addresses and will list on the screen the addresses and data of the portion of memory requested, offset from the base address. The listing will stop after every 16 lines at which point pressing return will exist to the *? prompt, whereas pressing any other key will continue with the listing.

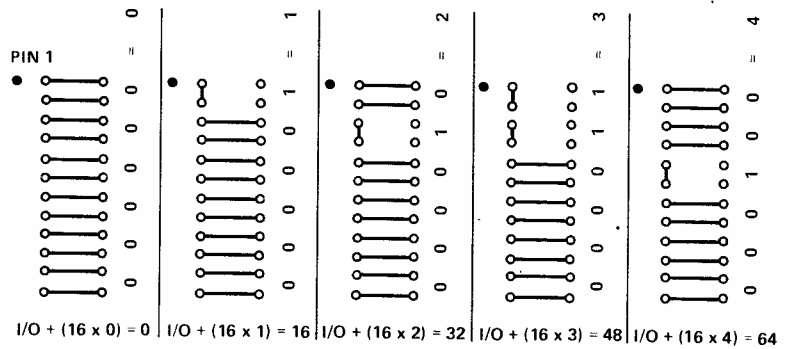


Fig. 3 Setting the address offset by wire links.

MODIFY will prompt for a single address, the contents of the base address offset by the value given being displayed on the screen. Entering an X at this point will return to the *? prompt leaving the data in that location unchanged, whereas entering a two-figure hexadecimal number will cause the relevant address to be updated with the data entered.

(H)ELP Lists all the commands available and reminds the user of the currently selected EPROM type and base address.

(E)XIT Causes the program to terminate.

In the above commands, any wrongly entered information will result in self-explanatory error messages. The one error message which, perhaps, requires a word of explanation is TYPE/RANGE INCOMPATIBLE. This error is a result of entering a start and finish address to any command which defines a range larger than the capacity of the selected EPROM type.

Erasing EPROMs

EPROMs are erased by exposure to ultra-violet light through the transparent window on the top of the package. Small commercially available erasing units with capacities of up to six chips cost typically in the £40-£50 region. If the requirements for erasing EPROMs are considered, it becomes obvious that an erasing unit can be constructed for considerably less than the price of commercial equipment. The requirements stated by EPROM manufacturers to erase such a device are a 20 to 30 minute exposure of 2357 Å (253.7 nm) wavelength ultra-violet light at an intensity of 12000 uW/cm². The Philips TUV 15 W tube emits UV at the required wavelength and at an intensity of 37 uW/cm² at about one inch from the tube, the distance metre from the tube, which

corresponds to about 12000 uW/cm² at a distance of one inch, as used in most EPROM erasers.

The tube costs in the region of £10 and will fit into an ordinary 15" fluorescent light fitting, it provides the basis for a relatively inexpensive unit which could accommodate about ten ICs.

A few words of caution are appropriate at this point. Ultra-violet radiation, and in particular shortwave UV as emitted by the TUV 15 W, is harmful to both the eyes and the skin. It is therefore essential to build the tube into a light-tight cabinet, ideally with a micro switch fitted under the lid to isolate the supply when opened, which will prevent UV light from coming into contact with skin or eyes.

EPROMs may also be erased by UV of longer wavelength (3000 Å - 4000 Å) although longer exposure times will probably be required. Since 'black light' tubes of the type used for disco lighting emit at about 3500 Å and are more easily available than short-wave UV tubes, it may be worthwhile experimenting with this type of light source.

One final point on the topic of erasing EPROMs is that both sunlight and ordinary fluorescent tubes emit some radiation in the 3000 Å - 4000 Å region with the result that prolonged exposure to these light sources will result in erasure. For this reason it is recommended that an opaque adhesive label is used to cover the windows of programmed EPROMs.

Next month, we'll describe the software for the unit.

ETI

BUYLINES



There should be relatively few problems in obtaining components for this project. The 0.22R resistor can be found in several suppliers' lists, including Watford's. The RM6 potcore is available from RS Components. our PCB service — see page 77 for details.

Step-by-step fully illustrated assembly and fitting instructions are included together with circuit descriptions. Highest quality components are used throughout.

Sparkrite

BRANDLEADING ELECTRONICS

NOW AVAILABLE IN KIT FORM

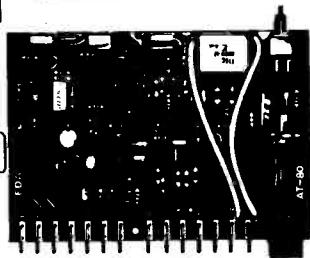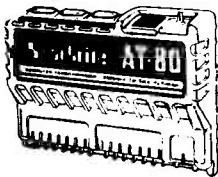


AT-80 Electronic Car Security System

- Arms doors, boot, bonnet and has security loop to protect fog/spot lamps, radio/tape, CB equipment
- Programmable personal code entry system
- Armed and disarmed from outside vehicle using a special magnetic key fob against a windscreen sensor pad adhered to the inside of the screen
- Fits all 12V neg earth vehicles
- Over 250 components to assemble


VOYAGER Car Drive Computer

- A most sophisticated accessory
- Utilises a single chip mask programmed microprocessor incorporating a unique programme designed by EDA Sparkrite Ltd.
- Affords 12 functions centred on Fuel, Speed, Distance and Time
- Visual and Audible alarms warning of Excess Speed, Frost/Ice, Lights-left-on
- Facility to operate LOG and TRIP functions independently or synchronously
- Large 10mm high 400ft-L fluorescent display with auto intensity
- Unique speed and fuel transducers giving a programmed accuracy of + or - 1%
- Large LOG & TRIP memories. 2,000 miles. 180 gallons. 100 hours
- Full Imperial and Metric calibrations
- Over 300 components to assemble
- A real challenge for the electronics enthusiast!

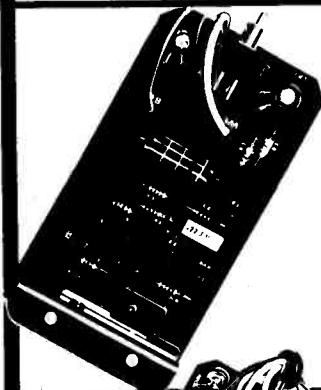

SX1000 Electronic Ignition

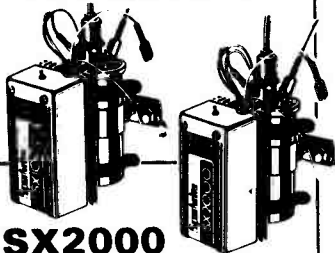- Inductive Discharge
- Extended coil energy storage circuit
- Contact breaker driven
- Three position changeover switch
- Over 65 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg. earth vehicles




TX1002 Electronic Ignition

- Contactless or contact triggered
- Extended coil energy storage circuit
- Inductive Discharge
- Three position changeover switch
- Distributor triggerhead adaptors included
- Die cast weatherproof case
- Clip-to-coil or remote mounting facility
- Fits majority of 4 & 6 cyl. 12V. neg. earth vehicles
- Over 145 components to assemble




NEW

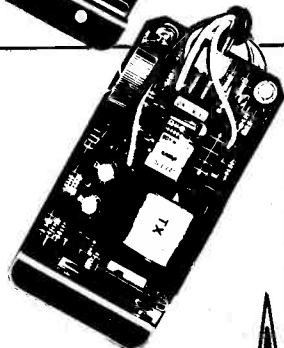

SX2000 Electronic Ignition

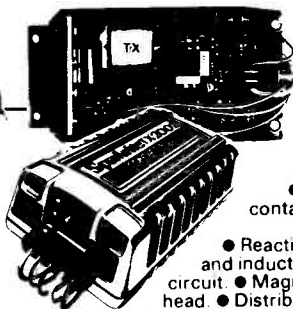- The brandleading system on the market today
- Unique Reactive Discharge
- Combined Inductive and Capacitive Discharge
- Contact breaker driven
- Three position changeover switch
- Over 130 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg. earth vehicles




TX2002 Electronic Ignition

- The ultimate system
- Switchable contactless
- Three position switch with Auxiliary back-up inductive circuit
- Reactive Discharge. Combined capacitive and inductive
- Extended coil energy storage circuit
- Magnetic contactless distributor triggerhead
- Distributor triggerhead adaptors included
- Can also be triggered by existing contact breakers
- Die cast waterproof case with clip-to-coil fitting
- Fits majority of 4 and 6 cylinder 12v neg. earth vehicles
- Over 150 components to assemble

All SPARKRITE products and designs are fully covered by one or more World Patents

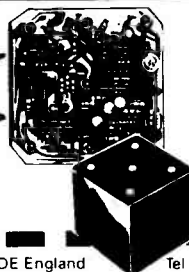SPECIAL OFFER
"FREE" MAGIDICE KIT WITH ALL ORDERS OVER £45.00



MAGIDICE Electronic Dice

- Not an auto-item but great fun for the family
- Total random selection
- Triggered by waving of hand over dice
- Bleeps and flashes during a 4 second tumble sequence
- Throw displayed for 10 seconds
- Auto display of last throw 1 second in 5
- Muting and Off switch on base
- Hours of continuous use from PP7 battery
- Over 100 components to assemble

SPARKRITE 82 Bath Street, Walsall, West Midlands, WS1 3DE England

Tel (0922) 614791 Allow 28 days for delivery

	SELF ASSEMBLY KIT
SX 1000	£12.95
SX 2000	£19.95
TX 1002	£22.95
TX 2002	£32.95
AT 80	£32.95
VOYAGER	£64.95
MAGIDICE	£9.95

PRICES INC. VAT, POSTAGE & PACKING

NAME _____ ETI/8
ADDRESS _____

I ENCLOSE CHEQUE(S)/POSTAL ORDERS FOR

£ _____ KIT REF _____
CHEQUE NO _____



BRANDLEADING BRITISH ELECTRONICS

CUT OUT THE COUPON NOW!

electronics today international BOOK SERVICE

How to order: indicate the books required by ticking the boxes and send this page, together with your payment, to: ETI Book Service, Argus Specialist Publications Ltd, 145 Charing Cross Road, London WC2 0EE. Make cheques payable to ETI Book Service. Payment in sterling only please. All prices include P & P. Prices may be subject to change without notice.

BEGINNERS GUIDE

<input type="checkbox"/>	Beginner's Guide to Basic Programming Stephenson	£5.35
<input type="checkbox"/>	Beginner's Guide to Digital Electronics	£5.35
<input type="checkbox"/>	Beginner's Guide to Electronics	£5.35
<input type="checkbox"/>	Beginner's Guide to Integrated Circuits	£5.35
<input type="checkbox"/>	Beginner's Guide to Computers	£5.35
<input type="checkbox"/>	Beginner's Guide to Microprocessors	£5.35

COOKBOOKS

<input type="checkbox"/>	Master IC Cookbook Hallmark	£10.15
<input type="checkbox"/>	Microprocessor Cookbook M. Hordeski	£7.70
<input type="checkbox"/>	IC Op Amp Cookbook Jung	£14.25
<input type="checkbox"/>	PLL Synthesiser Cookbook H. Kinley	£7.70
<input type="checkbox"/>	Active Filter Cookbook Lancaster	£13.40
<input type="checkbox"/>	TV Typewriter Cookbook Lancaster	£11.15
<input type="checkbox"/>	CMOS Cookbook Lancaster	£11.85
<input type="checkbox"/>	TTL Cookbook Lancaster	£10.95
<input type="checkbox"/>	Micro Cookbook Vol. 1 Lancaster	£15.30
<input type="checkbox"/>	BASIC Cookbook K. Tracton	£6.00
<input type="checkbox"/>	MC6809 Cookbook C. Warren	£7.25

ELECTRONICS

<input type="checkbox"/>	Principles of Transistor Circuits Amos	£8.50
<input type="checkbox"/>	Design of Active Filters with experiments Berlin	£11.30
<input type="checkbox"/>	49 Easy to Build Electronic Projects Brown	£6.00
<input type="checkbox"/>	Electronic Devices & Circuit Theory Boylestad	£13.20
<input type="checkbox"/>	How to build Electronic Kits Capel	£3.55
<input type="checkbox"/>	How to Design and build electronic instrumentation Carr	£9.35
<input type="checkbox"/>	Introduction to Microcomputers Daglees	£7.20
<input type="checkbox"/>	Electronic Components and Systems Dennis	£15.00
<input type="checkbox"/>	Principles of Electronic Instrumentation De Sa	£11.40
<input type="checkbox"/>	Giant Handbook of Computer Software	£12.95
<input type="checkbox"/>	Giant Handbook of Electronic Circuits	£17.35
<input type="checkbox"/>	Giant Handbook of Electronic Projects	£11.75
<input type="checkbox"/>	Electronic Logic Circuits Gibson	£5.55
<input type="checkbox"/>	Analysis and Design of Analogue Integrated Circuits Gray	£30.25
<input type="checkbox"/>	Basic Electronics Grob	£11.30
<input type="checkbox"/>	Lasers - The Light Fantastic Hallmark	£7.70
<input type="checkbox"/>	Introduction to Digital Electronics & Logic Joynson	£5.25
<input type="checkbox"/>	Electronic Testing and Fault Diagnosis Loveday	£7.85
<input type="checkbox"/>	Electronic Fault Diagnosis Loveday	£6.25
<input type="checkbox"/>	Essential Electronics A-Z Guide Loveday	£7.50
<input type="checkbox"/>	Microelectronics Digital & Analogue circuits and systems Millman	£12.70
<input type="checkbox"/>	103 Projects for Electronics Experimenters Minis	£8.30
<input type="checkbox"/>	VLSI System Design Muroga	£34.10
<input type="checkbox"/>	Power FETs and their application Oxner	£9.40
<input type="checkbox"/>	Practical Solid State Circuit Design Olesky	£25.00
<input type="checkbox"/>	Master Handbook of IC Circuits Powers	£12.85
<input type="checkbox"/>	Electronic Drafting and Design Raskhodoff	£22.15
<input type="checkbox"/>	VOM - VTVM Handbook Risse	£8.50
<input type="checkbox"/>	Video and Digital Electronic Displays Sherr	£28.85
<input type="checkbox"/>	Understanding Electronic Components Sinclair	£7.50
<input type="checkbox"/>	Electronic Fault Diagnosis Sinclair	£4.50
<input type="checkbox"/>	Physics of Semiconductor Devices Sze	£17.35
<input type="checkbox"/>	Digital Circuits and Microprocessors Taub	£32.00
<input type="checkbox"/>	Active Filter Handbook	£7.60
<input type="checkbox"/>	Designing with TTL Integrated Circuits Texas	£15.20
<input type="checkbox"/>	Transistor Circuit Design Texas	£15.20
<input type="checkbox"/>	Digital Systems: Principles and Applications Tocco	£12.95
<input type="checkbox"/>	Master Handbook of Telephones Traister	£10.00
<input type="checkbox"/>	How to build Metal/Treasure Locators Traister	£6.00
<input type="checkbox"/>	99 Fun to Make Electronic Projects Tymony	£8.50
<input type="checkbox"/>	33 Electronic Music Projects you can build Winston	£6.95

COMPUTERS & MICROCOMPUTERS

<input type="checkbox"/>	BASIC Computer Games Ahl	£6.35
<input type="checkbox"/>	From BASIC to PASCAL Anderson	£9.95
<input type="checkbox"/>	Mastering Machine Code on your ZX81 T. Baker	£7.25
<input type="checkbox"/>	UNIX - The Book Banaham	£8.75
<input type="checkbox"/>	Z80 Microcomputer Handbook Barden	£10.95
<input type="checkbox"/>	Microcomputer Maths Barden	£11.90
<input type="checkbox"/>	Digital Computer Fundamentals Barter	£9.90
<input type="checkbox"/>	Visicalc Book. APPLE Edition Bell	£15.55
<input type="checkbox"/>	Visicalc Book. ATARI Edition Bell	£15.55
<input type="checkbox"/>	Introduction to Microprocessors Brunner	£23.00
<input type="checkbox"/>	Programming your APPLE II Computer Bryan	£9.25
<input type="checkbox"/>	Microprocessor Interfacing Carr	£7.70
<input type="checkbox"/>	Microcomputer Interfacing Handbook A/D & D/A Carr	£9.50
<input type="checkbox"/>	Musical Applications of Microprocessors Chamberlain	£28.85
<input type="checkbox"/>	30 Computer Programs for the Home Owner in BASIC D. Chance	£9.25
<input type="checkbox"/>	Microcomputers Dirkson	£9.30
<input type="checkbox"/>	APPLE Personal Computer for Beginners Dunn	£9.50
<input type="checkbox"/>	Microcomputers/Microcomputers - An Intro Gioone	£11.80

<input type="checkbox"/>	Troubleshooting Microprocessors and Digital Logic Goodman	£9.25
<input type="checkbox"/>	Getting Acquainted with your VIC 20 Hartnell	£8.50
<input type="checkbox"/>	Getting Acquainted with your ZX81 Hartnell	£5.95
<input type="checkbox"/>	Let your BBC Micro Teach you to program Hartnell	£7.90
<input type="checkbox"/>	Programming your ZX Spectrum Hartnell	£8.50
<input type="checkbox"/>	The ZX Spectrum Explored Hartnell	£6.95
<input type="checkbox"/>	How to Design, Build and Program your own working Computer System Haviland	£9.30
<input type="checkbox"/>	BASIC Principles and Practice of Microprocessors Heffer	£7.15
<input type="checkbox"/>	Hints and Tips for the ZX81 Hewson	£5.25
<input type="checkbox"/>	What to do when you get your hand on a Microcomputer Holtzman	£9.95
<input type="checkbox"/>	34 More Tested Ready to Run Game Programs in BASIC Horn	£7.70
<input type="checkbox"/>	Microcomputer Builders' Bible Johnson	£12.40
<input type="checkbox"/>	Digital Circuits and Microcomputers Johnson	£14.55
<input type="checkbox"/>	PASCAL for Students Kemp	£7.20
<input type="checkbox"/>	The C - Programming Language Kernighan	£18.20
<input type="checkbox"/>	COBOL Jackson	£9.25
<input type="checkbox"/>	The ZX81 Companion Maunder	£9.50
<input type="checkbox"/>	Guide to Good Programming Practice Meek	£6.40
<input type="checkbox"/>	Principles of Interactive Computer Graphics Newman	£13.95
<input type="checkbox"/>	Theory and Practice of Microprocessors Nicholas	£11.35
<input type="checkbox"/>	Exploring the World of the Personal Computer Nilles	£12.95
<input type="checkbox"/>	Microprocessor Circuits Vol. 1. Fundamentals and Microcontrollers Noll	£9.80

<input type="checkbox"/>	Beginner's Guide to Microprocessors Parr	£5.35
<input type="checkbox"/>	Microcomputer Based Design Peatman	£11.30
<input type="checkbox"/>	Digital Hardware Design Peatman	£9.80
<input type="checkbox"/>	BBC Micro Revealed Ruston	£9.45
<input type="checkbox"/>	Handbook of Advanced Robotics Safford	£14.45
<input type="checkbox"/>	1001 Things to do with your own personal computer Sawusch	£8.50
<input type="checkbox"/>	Easy Programming for the ZX Spectrum Stewart	£7.15
<input type="checkbox"/>	Microprocessor Applications Handbook Stout	£34.40
<input type="checkbox"/>	Handbook of Microprocessor Design and Applications Stout	£37.60
<input type="checkbox"/>	Programming the PET/CBM West	£17.80
<input type="checkbox"/>	An Introduction to Microcomputer Technology Williamson	£8.20
<input type="checkbox"/>	Computer Peripherals that you can build Wolfe	£12.40
<input type="checkbox"/>	Microprocessors and Microcomputers for Engineering Students and Technicians Wooland	£7.10

REFERENCE BOOKS

<input type="checkbox"/>	Electronic Engineers' Handbook Fink	£56.45
<input type="checkbox"/>	Electronic Designers' Handbook Giacoletto	£59.55
<input type="checkbox"/>	Illustrated Dictionary of Microcomputer Technology Hordeski	£8.45
<input type="checkbox"/>	Handbook for Electronic Engineering Technicians Kauffman	£27.50
<input type="checkbox"/>	Handbook of Electronic Calculators Kauffman	£35.00
<input type="checkbox"/>	Modern Electronic Circuit Reference Manual Marcus	£44.00
<input type="checkbox"/>	International Transistor Selector Towers	£10.70
<input type="checkbox"/>	International Microprocessor Selector Towers	£16.00
<input type="checkbox"/>	International Digital IC Selector Towers	£10.95
<input type="checkbox"/>	International Op Amp Linear IC Selector Towers	£8.50
<input type="checkbox"/>	Illustrated Dictionary of Electronics Turner	£12.95

VIDEO

<input type="checkbox"/>	Servicing Home Video Cassette Recorders Hobbs	£12.95
<input type="checkbox"/>	Complete Handbook of Videocassette Recorders Kybett	£9.25
<input type="checkbox"/>	Theory and Servicing of Videocassette Recorders McGinty	£12.95
<input type="checkbox"/>	Beginner's Guide to Video Matthewson	£5.35
<input type="checkbox"/>	Video Recording: Theory and Practice Robinson	£14.40
<input type="checkbox"/>	Video Handbook Van Wezel	£21.90
<input type="checkbox"/>	Video Techniques White	£12.95

Please send me the books indicated. I enclose cheque/postal order for £..... Prices include postage and packing. I wish to pay by Access/Barclaycard. Please debit my account.

5 2 2 4

4 9 2 9

Signed.....

Name.....

Address.....

READ/WRITE

Hyconomiser

Dear Sir,

I have been a more or less regular reader of ETI since its inception and I think generally you do a pretty good job; however, you have now made a serious error by recommending a product which you are not really qualified to pronounce upon. I refer to the feature on the Hyconomiser in your June issue.

If, instead of questioning the garages involved in selling the device, who you must admit have a vested interest, you had spoken to a recognised authority on the subject, I am sure you would have been told not to waste your time on it, and certainly not to give any recommendation. Talking to garage mechanics about engine fuelling and exhaust emission technology (a subject not far behind aerospace and electronics for expenditure and complexity) is rather like asking an electrician to comment on the latest microprocessor.

For many years, including a number as a senior development engineer at Jaguar Cars, fuel economy had been a specialist subject of mine and devices such as the Hyconomiser invariably come my way for appraisal. In fact, two or three years ago this device was being marketed as the PED with a rather different story behind it. I enclose a copy of the advertising material relevant to that incarnation which you will see employs the same diagram you reproduced. In an attempt to win me over I was visited by the alleged inventor of the device, a certain Canadian called Andrew MacGuire, and was presented with an impressively thick report, produced in the USA, purporting to show how effective it was. To the uninitiated it was most convincing but on close examination most of the tests were based on unrealistic baseline figures, in one case an exhaust CO level of 8% (a vastly over-rich condition) was used as a basis for comparison. I still have a copy of the report if you should wish to see it.

Whilst it may be that your reviewer obtained a measurable improvement after fitting the device, any air bleed into the inlet manifold (which in essence is what the Hyconomiser is) will have a mixture

weakening effect more or less compensating for wear of the carburettor metering orifice. For the car in question a new carburettor, or even simply replacing the metering needle costing about £3, would undoubtedly have shown similar, if not better gains. In any event the only way to test a device such as this is under carefully controlled conditions and even then so many variables can be involved that results are likely to have a spread of 10% or so.

As for the claim that fuel droplets are broken up with sonic waves generated by three pulsating balls, if you believe that I would also expect you to look for fairies at the bottom of your garden. For sonic waves to pulverise fuel droplets it is necessary for a large amount of energy to be expended in shearing the mixture and even then economy gains are unlikely to exceed 10%.

The claim that the device maintains the air/fuel ratio close to stoichiometric is quite unfounded. If you can find out how this is achieved pleased let me know — nobody has been able to explain to me how it can happen.

Finally, if a device such as this was able to offer the improvements claimed, the motor manufacturers would be already using it rather than running multi-million pound retooling programmes to obtain relatively modest gains, and electronic engine management systems (surely a more appropriate subject for you to become involved in) would be unnecessary.

If you wish to maintain the high reputation of your magazine I think you would be well advised to print a retraction on the subject as soon as possible.

Yours faithfully

Roger Bywater

Roger Bywater Engineering Ltd
Stockport
Cheshire

The author replies:

Much more about the Hyconomiser, its inventor and history was known to me before undertaking the review, but my brief from the editor was to confine the report to 1,000 words so much had to be omitted. The device reduces pollution as well as effects fuel economy. In Canada where it was first produced, pollution control

is of greater interest than economy because of government controls, hence it was called the PED., (Pollution Elimination Device). Out of 400 devices tested by the American Environmental Protection Agency, the PED came out first. To the British motorist economy is the more important factor, hence the change of name. There is nothing sinister in that.

Mr Bywater scorns the idea that sonic waves produced by plastic balls can break up fuel droplets. Perhaps he would likewise scorn the suggestion that a piece of flapping paper could permanently damage scores of human eardrums at a range of many yards, yet if he would visit his nearest disco he will find loudspeaker cones doing just that. It is the power actuating the medium, not the medium itself that is important. Here, the power is provided by the vacuum generated by the engine intake or induction stroke. If this has sufficient power to atomise fuel from the carburettor in the first place why should it be insufficient to complete the job by means of the Hyconomiser?

The balls are in fact tuned to resonance, and when resonating any physical object is capable of high amplitude oscillation which can even be destructive, as any student of mechanical stress engineering would know. The effect has in fact been observed in tests carried out by a motor manufacturer. An intake manifold with transparent quartz window was assembled to a production engine. With normal running, drops of fuel could be seen coursing the over the inside surfaces to be ejected with the exhaust, but when Hyconomiser was switched in by a control valve, the drops instantly vaporised into a mist. Special rapid-exposure photographic techniques and precision measurements revealed the particle size to be in the region of eight microns.

The motor manufacturer, (a well-known name that I cannot reveal at present) will in fact be using the Hyconomiser in future production models. It has not been used before because car design and planning is usually at least three years ahead of current production. Other manufacturers are actively considering it.

Mr Bywater's assertion that my economy figures were due to a leaner mixture produced by bleeding air past the carburettor can be refuted on two counts. First, the carburettor mixture setting must be made slightly richer before fitting the Hyconomiser to compensate for the extra air thus restoring the correct air/fuel ratio. Se-

cond, when the device went off tune for reasons described in my review, the consumption climbed to its former figure. On re-tuning, the economy returned. According to Mr Bywater tuning should have made no difference as air was still passing through. He alleges that the air bleed merely neutralizes wear in the fuel needle and orifice of the carburettor, and that a replacement would have the same result. However, the device has been fitted to brand new cars with notable economy improvements.

The 8% CO emission figure he complains of does indeed represent an abnormally rich mixture, some 9:1 air/fuel ratio. However, this was merely the starting point of a graph plot which shows the comparative CO emissions with and without the Hyconomiser, over a wide range of mixtures from 9:1 to 20:1. You have to start a plot somewhere, usually it is best to do so outside of the area of interest so that a complete picture is presented.

As to the question as to how the stoichiometric (optimum) 14.6:1 ratio is maintained by the device, this is done firstly by improved atomisation and distribution of fuel. Thus the anomalies of lean and rich areas in different cylinders and parts thereof are avoided. Secondly, the lowest ball in the Hyconomiser seats against its exit orifice. This expands and contracts according to the vacuum in the inlet manifold and so controls the airflow. Thereby the amount of air, hence mixture ratio, varies in response to engine speed and throttle setting, so compensating for the mixture vagaries produced by the carburettor under differing conditions.

Garages who fit the Hyconomiser may indeed, as Mr Bywater says, have a vested interest, but not of the sort he insinuates. All those I contacted were reputable main-agent establishments with large factory-trained staffs and the latest in electronic tuning and diagnostic equipment. Their vested interest is in their reputation which would soon be in tatters if they fitted rubbish that didn't work. As the proprietor of a fuel injection and economy development company, may I suggest that HE is the one that has a vested interest in knocking the Hyconomiser!

Vivian Capel.

We doubt whether we have heard the last of this topic. For those of you still sending us missives by various means, the Hyconomiser is now made under licence by: Atwell Construction Ltd, Station Road, Wrington, Avon, Tel: Bristol 719441.

Compact Disc

Dear Sir,

The article in your May '83 issue concerning recommended high-quality turntable systems was punctuated by a small section on the new Compact Disc format. As the author observes, 'in about a year' CD players will be altogether affordable, probably considerably cheaper than specialist analogue turntables and therefore likely to oust them on grounds of both performance and value. At that time, second hand (one year old), once-expensive analogue players would presumably be demoted to duties such as door-stopping or pot-throwing in view of their likely marketability. I would therefore query the advisability of any recommendation to buy high quality analogue disc equipment.

Of course, my premis in such a sweeping statement is that CD will be a vastly superior format, bringing me onto my second beef; why so little space for such an important breakthrough, about which plentiful information has been distributed in advance certainly to many Hi-Fi magazines who have seen fit to publish reports on the subject? Now I would not expect you to give a high priority to reporting on Hi-Fi matters normally, though surely the presence of an audio article anyway might have been used to better advantage.

I would certainly be interested to know what levels of fidelity are claimed for the pressing and then optimal reading of vinyl discs so that these could be compared with the plentiful information available for digital format.

The world of audio performance assessment has become altogether cluttered with highly subjective judgement. Hi-Fi magazines persist in, what seems to me, the odious convention of allowing poets with 'golden ears' to subjectively assess nebulous qualities, transferring little hard information to the reader. For reference, it would be interesting to see, published alongside a reviewer's observations, the results of a thorough hearing test performed on him at a relevant time. Could controlled levels of distortion, on identical pieces of recorded music, be used to test a 'golden auditor's' true calibration?

Personally, I find it difficult to give more credence to the doubtless limited-bandwidth response of ageing reviewers than laboratory test equipment. Admittedly, standards of distortion measurement are confusing, and it is not sufficiently relevant

to music reproduction to be testing pure tones, but why not simply compare 'scope photos of microphone signals at the recording studio with the ultimate, played-back signal from analogue and digital discs? Could such a test be arranged or would vested interests prevent it?

An article devoted to bringing more rigour into Hi-Fi assessment along these lines would certainly have my fullest attention, and should not be irrelevant to the aims of your magazine, since it would not labour the subject of the Hi-Fi market or the present state of the manufactured art, but would deal rather with 'transduction'.

Yet more relevant, of general interest and, as yet, unreported (to my knowledge) would be an investigation of the digital disc format and its protocol; how are the discs manufactured, what is this error correction business? Would it be at all possible to produce an alternative erasable and programmable, ideally compatible, optical recording system, perhaps by populating a disc fully with reflective logic cells but positioning an optically switchable window in front of each?

Presumably it is the variability in performance of D-to-A convertors that accounts for the present variability in CD player performance. Would it be conceivably possible to delay the mapping to as late a stage as possible, having a (perhaps integral) D-to-A power output stage, or is the process of amplification (and transduction) best left to conventional analogue techniques? An acquaintance has described to me his attempts to make a digital switching amplifier. (A-to-D-to-A), but, presumably digital speakers could not successfully operate composed of an array of switching drivers, (one twice the size of the next) whilst the idea of linear stepper motors attached to conventional diaphragm(s) would seem unrealistic.

Any ideas?

Yours faithfully

Mr P.E. Cox

Derby

Mr Cox raises far too many points for us to answer in the space available! Suffice to say that CD will not make analogue players obsolete because there will still be a lot of analogue discs around for many years to come. We'll obviously be reporting further on CD in the future.

MASTER ELECTRONICS NOW!

The PRACTICAL way!

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to start or further a career in electronics or as a self-employed servicing engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write personally at any time, for advice or help during your work. A Certificate is given at the end of every course.

You will do the following:

- Build a modern oscilloscope
- Recognise and handle current electronic components
- Read, draw and understand circuit diagrams
- Carry out 40 experiments on basic electronic circuits used in modern equipment
- Build and use digital electronic circuits and current solid state 'chips'
- Learn how to test and service every type of electronic device used in industry and commerce today. Servicing of radio, T.V., Hi-Fi and microprocessor/computer equipment.



New Job? New Career? New Hobby? Get into **Electronics** Now!

FREE!
COLOUR BROCHURE

Please send your brochure without any obligation to

I am interested in:

ETI/8/83

NAME _____

COURSE IN ELECTRONICS

as described above

RADIO AMATEUR LICENCE

MICROPROCESSORS

LOGIC COURSE

OTHER SUBJECTS _____

ADDRESS _____

BLOCK CAPS PLEASE

POST NOW TO:

British National Radio & Electronics School Reading, Berks. RG1 1BR

BUILD A BETTER AMPLIFIER!



How can you own a top class HiFi amplifier, of comparable standard to Naims, Meridians, Quads etc., for an outlay of less than £250? — Simple! Built it yourself — with a Crimson kit.

It is not necessary to spend a small fortune to obtain true Hifi performance. Crimson Kits offer all the features and sound quality of the most esoteric amplifiers available and their ease of assembly ensures that they work first time and continue to do so. Not only do Crimson Kits offer outstanding value, but they also have the flexibility to adapt to any users needs. All the P.C.B.'s are ready assembled and tested (they are *not* "potted" as we believe disposable modules are rather extravagant!) therefore constructing a kit is pleasurable in itself and, once built, will give years of untroubled service. So, whether you use a simple record player or a compact disc, you can be sure to get the most from your system. E.T.I. said, in their review of the CK1010/1100: "I can say no more than that for £250 it is a bargain and one that will become the reference point for kit amplifiers from now on." Need we say more?

PRICES ★ **Summer Special Offer: Buy a CK1010 and any CK power amplifier and get an MC2K board free!!** ★

CK1010 — STEREO PRE-AMPLIFIER (moving magnet, tape, tuner input) takes power from any CK power amp or separate p.s.u. type P.S.K. **£92.00**

CK1040 — STEREO POWER-AMPLIFIER 40 watts R.M.S./Chanel **£121.00**

CK1080 — STEREO POWER-AMPLIFIER 80 watts R.M.S./Chanel **£134.00**

CK1100 — STEREO POWER-AMPLIFIER 100 watts R.M.S./Chanel **£151.00**

MC2K — Moving coil add on kit for CK1010 **£25.00**

P.S.K. — power supply for CK1010 (if not used with a CK power amp) **£20.00**

CRIMSON also supply power amp, pre amp and electronic crossover modules, power supplies and hardware — too much to list here — but on receipt of an S.A.E. we will be happy to supply full details.

TO ORDER Send C.W.O. or quote your access card no (phone orders accepted) Crimson Products are also available from Bradley Marshall Ltd, 325 Edgware Road, London.

* Offer closes 31st July 1983 (Return this ad with your order)



CRIMSON ELEKTRIK STOKE

MANUFACTURERS OF PROFESSIONAL, DOMESTIC & INDUSTRIAL AMPLIFICATION

PHOENIX WORKS, 500 KING STREET, LONGTON, STOKE-ON-TRENT, STAFFORDSHIRE. ST2 1EZ ☎ 0782 330520

TOROIDALS


The toroidal transformer is now accepted as the standard in industry, overtaking the obsolete laminated type. Industry has been quick to recognise the advantages toroidals offer in size, weight, lower radiated field and, thanks to I.L.P., PRICE.

Our large standard range is complemented by our SPECIAL DESIGN section which can offer a prototype service within 7 DAYS together with a short lead time on quantity orders which can be programmed to your requirements with no price penalty.

***Gold service available.**
21 days manufacture for urgent deliveries.

***Orders despatched within 7 days of receipt for single or small quantity orders.**

***5 year no quibble guarantee.**

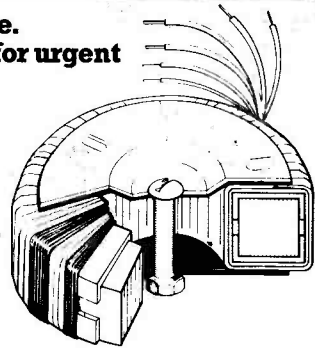

TYPE	SERIES No	SECONDARY Volts	RMS Current	PRICE	TYPE	SERIES No	SECONDARY Volts	RMS Current	PRICE	TYPE	SERIES No	SECONDARY Volts	RMS Current	PRICE				
NEW! NEW! NEW!																		
15 VA 62 x 34mm 0.35Kg Regulation 19%	0x010	6+6	1.25	£5.12 + p & p £0.78 + VAT £0.89 TOTAL £6.79	120 VA 90 x 40mm 1.2Kg Regulation 11%	4x010	6+6	10.00	£7.42 + p & p £1.72 + VAT £1.37 TOTAL £10.51	300 VA 110 x 50mm 2.6Kg Regulation 6%	7x013	15+15	10.00	£10.88 + p & p £2.05 + VAT £1.94 TOTAL £14.87				
	0x011	9+9	0.83			4x011	9+9	6.66			7x014	18+18	8.33					
	0x012	12+12	0.63			4x012	12+12	5.00			7x015	22+22	6.82					
	0x013	15+15	0.50			4x013	15+15	4.00			7x016	25+25	6.00					
	0x014	18+18	0.42			4x014	18+18	3.33			7x017	30+30	5.00					
	0x015	22+22	0.34			4x015	22+22	2.72			7x018	35+35	4.28					
	0x016	25+25	0.30			4x016	25+25	2.40			7x026	40+40	3.75					
	0x017	30+30	0.25			4x017	30+30	2.00			7x025	45+45	3.33					
						4x018	35+35	1.71			7x033	50+50	3.00					
			4x028	110		1.09	7x028	110			2.72							
			4x029	220	0.54	7x029	220	1.36										
			4x030	240	0.50	7x030	240	1.25										
30 VA 70 x 30mm 0.45Kg Regulation 18%	1x010	6+6	2.50	£5.49 + p & p £1.10 + VAT £0.99 TOTAL £7.58	160 VA 110 x 40mm 1.8Kg Regulation 8%	5x011	9+9	8.89	£8.43 + p & p £1.72 + VAT £1.52 TOTAL £11.67	500 VA 140 x 60mm 4Kg Regulation 4%	8x016	25+25	10.00	£14.38 + p & p £2.40 + VAT £2.52 TOTAL £19.30				
	1x011	9+9	1.66			5x012	12+12	6.66			8x017	30+30	8.33					
	1x012	12+12	1.25			5x013	15+15	5.33			8x018	35+35	7.14					
	1x013	15+15	1.00			5x014	18+18	4.44			8x026	40+40	6.25					
	1x014	18+18	0.83			5x015	22+22	3.63			8x025	45+45	5.55					
	1x015	22+22	0.68			5x016	25+25	3.20			8x033	50+50	5.00					
	1x016	25+25	0.60			5x017	30+30	2.66			8x042	55+55	4.54					
1x017	30+30	0.50	5x018	35+35		2.28	8x028	110			4.54							
50 VA 80 x 35mm 0.9Kg Regulation 13%	2x010	6+6	4.16	£6.13 + p & p £1.35 + VAT £1.12 TOTAL £8.60		225 VA 110 x 45mm 2.2Kg Regulation 7%	6x012	12+12			9.38	£9.81 + p & p £2.05 + VAT £1.78 TOTAL £13.64	625 VA 140 x 75mm 5Kg Regulation 4%		9x017	30+30	10.41	£17.12 + p & p £2.55 + VAT £2.95 TOTAL £22.62
	2x011	9+9	2.77				6x013	15+15			7.50				9x018	35+35	8.92	
	2x012	12+12	2.08		6x014		18+18	6.25	9x026	40+40	7.81							
	2x013	15+15	1.66		6x015		22+22	5.11	9x025	45+45	6.94							
	2x014	18+18	1.38		6x016		25+25	4.50	9x033	50+50	6.25							
	2x015	22+22	1.13		6x017		30+30	3.75	9x042	55+55	5.68							
	2x016	25+25	1.00		6x018		35+35	3.21	9x028	110	5.68							
2x017	30+30	0.83	6x026	40+40	2.81		9x029	220	2.84									
80 VA 90 x 30mm 1Kg Regulation 12%	3x010	6+6	6.64	£6.66 + p & p £1.72 + VAT £1.26 TOTAL £9.64	6x019		25+25	4.50	9x030	240	2.60							
	3x011	9+9	4.44		6x017		30+30	3.75										
	3x012	12+12	3.33		6x018	35+35	3.21											
	3x013	15+15	2.66		6x026	40+40	2.81											
	3x014	18+18	2.22		6x025	45+45	2.50											
	3x015	22+22	1.81		6x033	50+50	2.25											
	3x016	25+25	1.60		6x028	110	2.04											
3x017	30+30	1.33	6x029	220	1.02													
3x028	110	0.72	6x030	240	0.93													
3x029	220	0.36																
3x030	240	0.33																

The benefits of ILP toroidal transformers

ILP toroidal transformers are only half the weight and height of their laminated equivalents, and are available with 110V, 220V or 240V primaries coded as follows:

IMPORTANT: Regulation — All voltages quoted are FULL LOAD. Please add regulation figure to secondary voltage to obtain off load voltage.

For 110V primary insert "0" in place of "X" in type number.

For 220V primary (Europe) insert "1" in place of "X" in type number.

For 240V primary (UK) insert "2" in place of "X" in type number.

Also available at Electrovalve, Maplin, Technomatic and Barrie Electronics.

For mail order please make your crossed cheques or postal orders payable to ILP Electronics Ltd. Barclaycard/Access welcome. Trade orders standard terms.

Post to: ILP Electronics Ltd, Graham Bell House, Roper Close, Canterbury CT2 7EP, Kent, England. Telephone (0227) 54778 Telex 965780



ILP TRANSFORMERS
(a division of ILP Electronics Ltd)

LOW COST PROFESSIONAL TEST INSTRUMENTS

sabtronics
FREQUENCY METERS
100MHz, 600MHz, and 1GHz Models
from £67

Belemic
Hand Held
Analogue and
Digital
Multimeters
16 Models
from £18.75

electro RSI

- ★ FREQUENCY METERS
- ★ ANALOGUE MULTIMETERS
- ★ DIGITAL MULTIMETERS
- ★ FUNCTION GENERATOR
- ★ OSCILLOSCOPES
- ★ POWER SUPPLIES
- ★ LOGIC PROBE
- ★ SCOPE PROBES

Write or phone for illustrated test instrument catalogue and price list

Black Star Ltd.
9A, Crown Street
St. Ives, Huntingdon



Cambs. PE17 4EB
Tel: (0480) 62440 Telex 32339

TECH TIPS


Keyboard Alphanumeric Lock Switch

G. Franklin, Mid Glamorgan

If your ASCII keyboard is like mine, then you too will have become tired of having to press 'SHIFT' for capital letters. SHIFT lock is useless because you have to 'unlock' to use the numbers. This circuit does away with this problem by providing you with yet another key to press. This is the 'ALPHA LOCK' switch.

If you study the ASCII codes you will find that to change 'a' into 'A' requires only the removal of the logic '1' on the data bit 5 line (of the 8 bit bus from the keyboard to your computer).

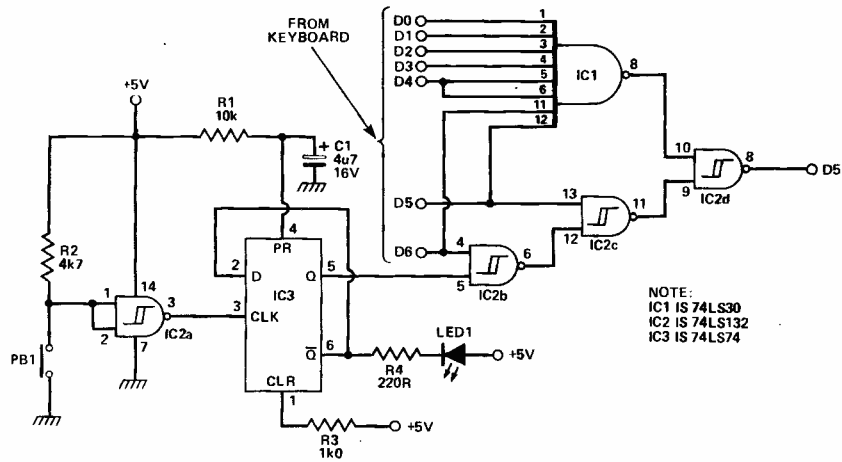e.g.:-
 ASCII code a A
 in binary:- 0110 0001 0100 0001
 We require to alter the complete alphabet, this stretches from a (\$61)



NOTE:
 IC1 IS 74LS30
 IC2 IS 74LS132
 IC3 IS 74LS74

to z (\$7A). The circuit cheats slightly, by altering codes \$60 to \$7F inclusive, the only problem with this is that \$7F is the ASCII code for 'DELETE'. IC1 deals with this, by detecting the \$7F code and making sure D5 stays at a logic 1 via the NAND gate at the end of the circuit.

One quarter of the 74LS132 is used to give a degree of switch bounce to S1. Every time S1 is pressed, the Q output of the latch (IC 3) will change, R1 and C1 ensure that on power-up the output is at a logic 1. This, along

with data bit 6 being 'HIGH' will make D5' a 'LOW', thus shifting a \$60 code down to \$40 (unless of course it was the 'DELETE' key that was pressed). The LED will come on to show when the ALPHA mode is selected. To insert this circuit into your keyboard, it is only necessary for D5' to come via this circuit, D5' then continuing in its place to the computer, the other data lines just connect to the circuit. The only other requirement is that you insert a switch somewhere.


Controller For Model Traffic Lights

P. Bailey, Glasgow

The circuit shown was devised to control LED traffic lights at a road junction in a model railway layout, for added realism. IC2, a decade counter, together with IC3a and IC3b, generates the normal traffic light sequence continuously at a rate determined by the oscillator formed around IC1a and IC1b. A monostable formed by IC1c and IC1d is triggered by a '1' on the 'GREEN' output, and inhibits IC2 for a period set by C_T and R_T, thus causing the green light to be on for a longer period than the others.

IC4 selects either LIGHT 1 or LIGHT 2 to display the sequence, these being selected alternately. When one light is changing or at green, the other is held at red.

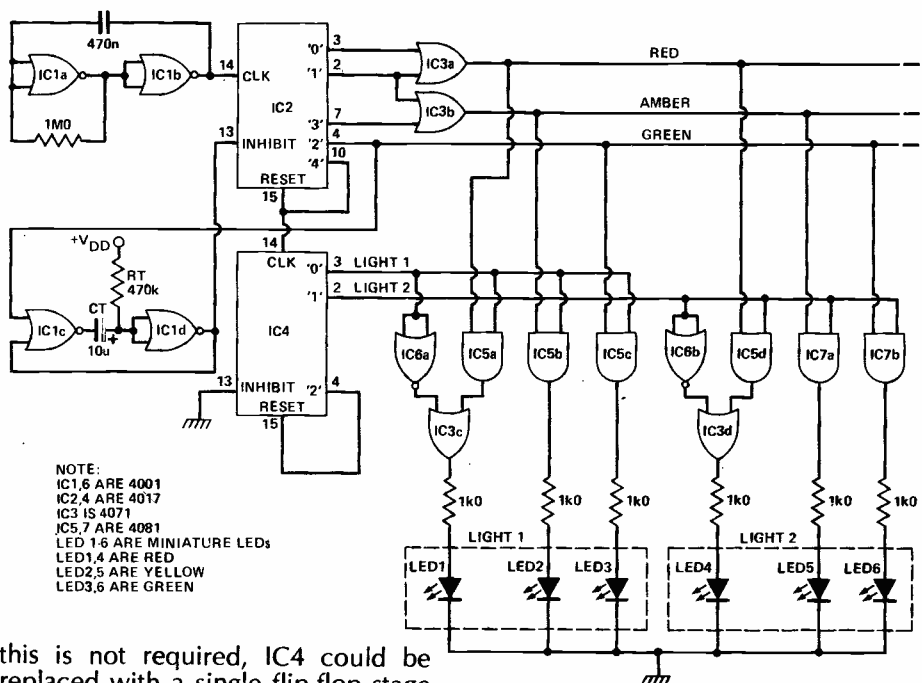The controller is easily expanded to operate more than two lights by using further outputs from IC4, but if



NOTE:
 IC1,6 ARE 4001
 IC2,4 ARE 4017
 IC3 IS 4071
 IC5,7 ARE 4081
 LED 1,6 ARE RED
 LED2,5 ARE YELLOW
 LED3,6 ARE GREEN

this is not required, IC4 could be replaced with a single flip-flop stage (eg a 4013), set to toggle, LIGHT 1 and LIGHT 2 being connected to the Q and Q' outputs respectively. With a little ingenuity, realistic-looking traffic

lights can be constructed from miniature LEDs and empty pen refill tubes.

ETI

AITKEN BROS.

ELECTRONIC COMPONENTS AND TEST EQUIPMENT
35, HIGH BRIDGE, NEWCASTLE
UPON TYNE NE1 1EW TEL: 0632 326729



MULTIMETERS

THANDAR TM351

● Bench/portable ● 3½-digit 0.5" LCD ● 0.1% basic accuracy ● 29 ranges ● Battery life typically 2000 hrs ● Complete with batteries & test leads. £113.85.
Accessories: Carrying case £6.84. Universal test lead set £12.65. Service Manual £3.00.



THANDAR TM353

● Bench/portable ● 3½-digit 0.5" LCD ● 0.25% basic accuracy ● 26 ranges ● Battery life typically 3000 hrs ● Complete with batteries & test leads £86.25. Accessories as TM351.



THANDAR TM354

● Pocket size ● 3½-digit 0.5" LCD. ● 0.75% basic accuracy. ● 14 ranges ● Battery life 200 hrs £45.94. Carrying case £3.45. Universal test lead set £12.65. Service Manual £3.00.



THANDAR TM451

● Bench/portable ● 4½-digit 0.4" LCD ● 0.03% basic accuracy ● Full auto-ranging or manual ● Sample hold ● Audible continuity test ● Complete with battery and leads £171.35. AC Adaptor £7.99. Universal test leads £12.65. Service Manual £3.00.



OSCILLOSCOPE

THANDAR SC110A

● Bench/portable ● Low power ● 10 MHz bandwidth ● 10mV sensitivity £171.35. Carrying case £6.34. AC Adaptor £7.99. Rechargeable battery pack £12.65. X1 probe £8.05. X10 probe £8.20. X1 X10 Switched probe £10.93. Sprung hook trimmer pack £2.88. Manual £3.00.

GENERATORS

THANDAR TG100 Function 1 Hz to 100 KHZ

£90.85

TG102 Function 0.2 Hz to 2 MHz £166.75

TG105 Pulse 5 Hz to 5 MHz £97.75



FREQUENCY COUNTERS

THANDAR TF200 10 Hz to 200 MHz

● Bench/portable ● 8-digit Liquid Crystal Display. ● Frequency range 10 Hz - 200 MHz ● Resolution better than 1 ppm ● Sensitivity typically 10mVrms ● Time base accuracy 0.3 ppm. ● Battery life 200 hours ● Frequency, time average period, totalize & reset; 2 ranges, 5 gate times; external clock facility ● Complete with batteries. £166.75.



THANDAR TF040 10 Hz to 40 MHz

● Bench/portable ● 8-digit Liquid Crystal Display. ● Frequency range 10 Hz - 40 MHz ● Resolution 1 Hz. ● Sensitivity 40 mV rms. ● Timebase accuracy 0.5 ppm ● Battery life 80 hours. ● Frequency, totalize & reset; 2 gate times ● Complete with batteries. £126.50.

ACCESSORIES FOR TF200 & TF040 AC adaptor £7.99, Carrying case £6.48, X1 Probe £8.05, X10 Probe £8.20, Service manual £3.00. TP600 prescaler £51.75. TP1000 prescaler £74.75.



THANDAR PFM200A 20 Hz to 200 MHz

● Pocket size ● 8-digit LED display ● Frequency range 20 Hz - 200 MHz. ● Resolution 0.1 Hz. Sensitivity typically 10 mV rms. Timebase accuracy 2 ppm ● Battery life 10 hours. ● Frequency; 2 ranges, 4 gate times ● BNC input sockets £77.62. Accessories: Carrying case £3.45, AC adaptor £7.99, X1 probe £8.05, X10 probe £9.20, Service Manual £3.00.

Full spec available on all instruments, just phone or write:



Schools, colleges, universities supplied on official orders. Prices include VAT. Please add £1.00 postage to orders under £20.00.

Accurate Digital Multimeters at Exceptional Prices


NEW ANALOGUE METER WITH CONTINUITY BUZZER AND BATTERY SCALE

28 RANGES, EACH WITH FULL OVERLOAD PROTECTION

SPECIFICATION MODELS 6010 & 7030

- 10 amp AC/DC
- Battery: Single 9V drycell. Life: 200 hrs
- Dimensions: 170 x 89 x 38mm.
- Weight: 400g inc. battery.
- Mode Select: Push Button.
- AC DC Current: 200µA to 10A
- AC Voltage: 200mV to 750V
- DC Voltage: 200mV to 1000V
- Resistance: 200Ω to 20MΩ
- Input Impedance: 10MΩ
- Display: 3½ Digit 13mm LCD
- O/Load Protection: All ranges

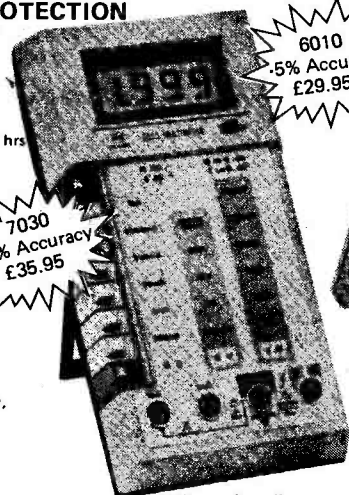OTHER FEATURES: Auto polarity, auto zero, battery low indicator, ABS plastic case with tilt stand, battery and test leads included, optional carrying case.



6010
±.5% Accuracy
£29.95

7030
±.1% Accuracy
£35.95



NEW
HM102 BZ
£13.00

NEW HM 102 BZ SPECIFICATION

- DC Voltage: 0-25, 1, 2.5, 10, 25, 100, 250, 1000 volts 20,000 ohms/volt.
- AC Voltage: 0-10, 25, 100, 250, 1000 volts 10,000 ohms/volt.
- Decibels: -20 to +22dB
- DC Current: 0-50, 500µA, 0-5, 50, 500mA
- Ohmmeter: 0-6 Megohms in 4 ranges. 30 ohms Centre Scale
- Power Supply: One 1.5V size 'A' battery (incl)
- Size & Weight: 135 x 91 x 39mm, 280gr.

HM 101 POCKET SIZE MULTIMETER SPECIFICATION


- DC & AC Voltage: 0-10, 50, 250, 1000 volts, 2000 ohms/volts
- Decibels: -10 to +22dB
- DC Current: 0-100mA
- Ohmmeter: 0-1 Megohm in 2 ranges, 60 ohms Centre Scale
- Power Supply: One 1.5V size 'A' battery (incl)
- Size & Weight: 90 x 60 x 29mm, 92gr. incl. battery
- Price £5.50

Quantity discount for trade on application.

Add 15% to your order for VAT. P&P is free of charge. Payment by Cheque with Order.

ARMON ELECTRONICS LTD.

Access & Barclaycard accepted.

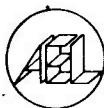

Cottrell House, 53-63 Wembley Hill Road, Wembley, Middlesex HA9 8BH, England

Telephone 01-9024321 (3 lines)

TELEX No 923985




hi! performance hi! competitive hi!

FULL HOUSE OF MULTIMETERS

TRIO

Bench Models DL 705, 706, 720 and DF 760

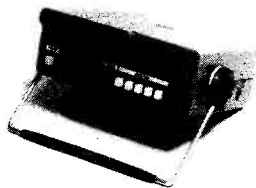
- 3½ and 4½ digit LED
- Rugged and Reliable
- 2 YEAR GUARANTEE
- Simple Operation – Auto Ranging
- Mains or Battery
- 7 Digit Frequency Counter
- Resolutions 1 and 0.1 mV
- DCV, ACV, DCA, ACA and Ohms
- Basic accuracy 0.8, 0.25, 0.1 and 0.05%
- Prices from just over £100 includes FREE Batteries, Hand Book and Test Leads



HC

Hand Held Models HM101 and 102 Series, HC 601, 703, 6010 and 7030.

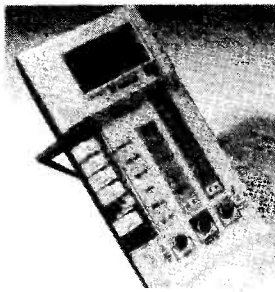- 3½ digit LCD and Analogue
- Colour coded front panel and edge switches
- High impact ABS with Tilt stand
- Safety features meets UL 1244
- Basic accuracy 0.6 and 0.2%
- Full Range of DCV, ACV, DCmA, ACmA and Ohms
- Audio Continuity Tone Plus 10A capability.
- Switched HI and LO ohms
- FREE Battery, Manual and Test Leads
- Analogue from approx £6 – Digital from approx £34



BBC GOERZ METRAWATT

MA1H, 2H, 3E and 5D. M2011, 2012, 2030, 2031 and 2032. Unigor 3N.


- Digital and Analog – Hand Held and Bench
- Huge LCDs – Many Safety Features
- Black, Rugged and Reliable
- 1 Year Guarantee
- 3½ and 4½ Digits
- Variable Viewing Angle – Hand free operation
- 20 Amp capability
- DCV, ACV, DCA, ACA, Ohms, Capacitance, Temp and Level in dBs
- Meet DIN 40050, 43780, 57410 or 57411 Requirements
- Prices from approx £27 includes FREE Batteries, manual and Test Leads



MIC

Hand Held Models 6000Z and 3300A

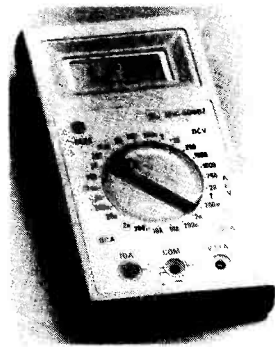- 3½ digit LCD with easy single rotary control.
- 10 Amp., 1000V and 20M ohm capability.
- TRANSISTOR hFE measurement.
- Audible Continuity check and Diode Test.
- Optional accessories incl. Carry Case and Battery Eliminator.
- Fully Guaranteed for 12 months.
- Prices from approx £39 include Free Battery, Manual and Test Leads.



Prices do not include VAT or P + D.

House of Instruments
Clifton Chambers, 62 High Street
Saffron Walden, Essex CB10 1EE
Tel: (0799) 24922 Telex: 818750



hi!

House of Instruments Ltd.

pantechnic

THE POWERFET SPECIALISTS

OEM USERS

Pantechnic present the most adaptable high powered amplifier ever.

FET SYSTEM AMP

Features:

- HIGH POWER. 1.2KW (single ended).
 - LOW VOLUME. 1/15 Cubic foot inc. Heat Sink.
 - VERSATILE. Delivers more than 1KW into ½ to 8 ohms.
- OR 2 x 600W into 2 to 8Ω
OR 4 x 300W into 2 to 4Ω (200W into Ω)
1 x 600W into 2 to 8Ω
OR 1 x 300W into 2 to 4Ω
1 x 150W into 4 to 8Ω
- Etc. Etc.

Having been closely involved in a wide variety of OEM applications of their amp boards, Pantechnic became aware of numerous implementation problems often left untackled by other amp board manufacturers. These problems specifically of size and thermal efficiency became particularly aggravated at high powers and considerably lengthened OEM product development time.

By including thermal design in the totality of board design it has been possible to reduce the size of the electronics, and increase the efficiency of the transistor to heatsink thermal circuit. The combined effect of this has been to dramatically increase the volumetric efficiency of the amplifier/heatsink assembly. The SYSTEM Amp offers 1.2KW of power in a space of 102mm x 102mm x 77mm, excluding PSU and Fan.

The basis of this considerable advance is the PANTECH 74 Heat Exchanger, newly designed and manufactured by us. By eliminating the laminar air flow found in conventional, extruded heat sinks, heat transfer to the environment is greatly enhanced.

The flexibility of the 1.2KW amp stems from its division into 4 potentially separate amplifiers of 300W each (downrateable with cost savings to 150W.) These can be paralleled, increasing current capability or seriesed (bridged in pairs) doubling voltage capability. In consequence a large variety of amplifier/load strategies can be implemented.

As ever Pantechnic offer a full range of customising options including DC coupling, ultra high slew etc. Contact Phil Rimmer on 01-800 6667 with your particular application problem. P.S. Specs, as ever, are exemplary.

OTHER POWERFET AMPLIFIER MODULES

Model	Price	Range (Rms)	Dyn-loads	Notes
*PFA100	20.65	50-150W	4Ω, 8Ω	Physically small (32 x 78 x 108mm)
*PFA200	27.35	100-300W	4Ω, 8Ω	High watts/C ratio
PFA/HV	36.04	200-300W	4Ω, 8Ω, 16Ω	5dB dynamic headroom Drives 70V line direct.
*PFA500	42.00	250-600W	2Ω, 4Ω, 8Ω	25A cont. output current.

mounted on type 74 Heat Exchanger (see below).

*The power output of these amplifiers can be increased by approx 15% with no diminution in quality by adding PSU102 (£7.61) to your existing power supply.

Some Other Products & Components

Type 74 Heat Exchanger. Dissipates 300 W (1.2KW fan cooled) £7.50

25A 400PIV Bridge Rect. £2.17

10,000uF 80V electrolytic with clip £4.75

PAN20 Pre-amplifier module. Very low noise and distortion £7.61

PAX2/24 2 Way active crossover (specify frequency) £10.10

PSU103 Powers 2 x PAN20 + 2 x PAX2/24 £6.91

PAN1397 20W power amp. (LOW THD) £5.04

PSU101 Powers 2 x PAN1397 £3.43

Transformer for above £4.30 (inc. postage)

TOROIDAL TRANSFORMERS

with special low flux windings

Nom. VAC	160VA	225VA	300VA	500VA	625VA	750VA
40-0-40	10.43	12.00	13.04	—	—	—
45-0-45	—	12.00	13.04	16.96	—	—
50-0-50	—	—	—	16.96	19.84	22.00
70-0-70	—	—	—	16.96	—	—

(for PFA/HV)

Transformer prices include postage. Ask for leaflet "Choosing a Transformer."

Carriage 75p. Add VAT at 15% to all prices.

THE POWERFET SPECIALISTS

pantechnic

Mail order only to

Dept ET1/8 148 Quarry Street, Liverpool L25 6HQ.

Telephone 051-428 8485

Technical enquiries

Phil Rimmer 01 800 6667

hi! reliability hi! service hi! performance hi! competitive hi!

hi! reliability hi! service hi! performance hi! competitive hi!

hi! competitive hi!

RADIO CONTROL SERVO FAIL-SAFE

Up, up and away? Bring your model aircraft down to earth *without* a bump using the ETI Conservo. Phil Walker shows you how to make your servos fail safe.

No-one who has spent many hours and pounds constructing their radio-controlled boat, plane or animated aardvark would want it to sail, fly or crawl out of range of their transmitter. However, there is always the remote possibility that some nasty little gremlin will creep in and throw the spanner in the works. When that happens all your controls may well be stuck in the last position you used; and by a well-known Law of Nature (Lex Divoti*), the position will make it as hard as possible to retrieve your model.

Help is at hand! This project will set your servos to any position you require (if you fit it beforehand) and if set up correctly your precious model should sail, fly or waddle home safely.

Use

The ETI Conservo is simply connected into the servo leads (get the polarity right) and the variable resistor can then be set to make the servo take up what you hope is a safe position. This setting is best done with slightly used batteries, to get a true position. Do not have the radio link operating while doing this or you won't be able to make the setting.

If your system uses low voltage (ie, around 3.6 volts) don't forget to increase the size of C2 to its higher value.

The Circuit

The circuit of this project is designed around a 4093 CMOS quad Schmitt trigger. This device will operate down to quite low supply voltages while still providing reliable switching performance.

One section of the device (IC1a) is used to detect the possibility that the input signal has stuck at a high

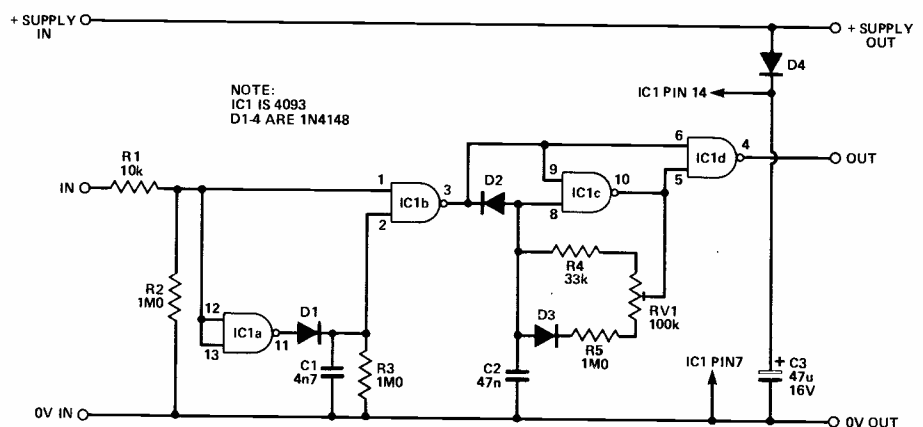


Fig. 1 Circuit diagram of the Conservo.

HOW IT WORKS

R1 and R2 protect the inputs of the CMOS devices from overload or static damage. The normal input to the device is a series of 1 to 2 ms positive pulses repeated at about 20 ms period. When the input is low, IC1a holds C1 high via D1 thus maintaining IC1b pin 2 at a high level.


When a pulse arrives, the output of IC1b goes low, discharges C2 and forces the output of IC1d high for the duration of the pulse. When the input pulse goes low again, C2 starts to charge via RV1 and R4 but will be discharged again by another input pulse before its voltage reaches the trigger threshold of IC1c. This means that the output of IC1c will stay high permanently in normal operation.

If another pulse does not arrive and the input stays low, the output of IC1b will stay high and C2 will charge up until its voltage reaches the threshold of IC1c

whose output will then go low and discharge C2 via RV1, R5 and D3 until the lower threshold of IC1c is reached. IC1c's output will then go high again and the cycle will repeat. When the output of IC1c is low, the output of IC1d will be forced high. The component values used in the circuit are such that this cycle approximates to the normal servo control signal with RV1 controlling the pulse width.

If for any reason the input sticks at a high level, C1 which is normally kept charged up by IC1d will have time to discharge effectively putting a low level on the input to IC1b. This will cause the same sequence of events to occur as when the input stuck low but after a short delay.

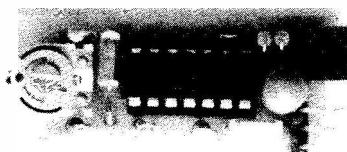Finally, D4 and C3 form a reserve power supply to ensure that the circuit is not affected by supply line transients.



A small project (this is actual size) but a long name — and a large degree of usefulness.

level. Since normally the input only goes high for relatively short periods at a time, the output from IC1d spends most of the time at a high level. This fact is used to charge a capacitor to near the supply potential. This capacitor can only be discharged by a resistor connected in parallel with it and then only if it has enough time to do so. In normal operation this will not be the case.

The second part of IC1 (IC1b) combines the original input signal with the 'stuck at high' signal and its output goes high when either is low. Note that this output only usually goes low when normal control pulses are being received. The low periods of the output from IC1b are used to discharge the timing capacitor of the oscillator formed around IC1c. The output from this oscillator would normally be a series of low going pulses of approximately the same frequency as the usual control pulses. The width of these pulses can be set by the variable resistor to simulate any servo position required. However these pulses will only be generated if the normal input fails to discharge the timing capacitor within a reasonable time.

The output from the gated oscillator described above and the output from IC1b are combined in IC1d to give the final output from the unit.

In normal operation the output will follow the input with no alteration as C1 will not discharge enough and C2 will not charge enough to have any effect. In a fault condition, however, the output from IC1b will stay at a high level (driven either by the input being low or by IC1a detecting the input high) and enable the gated oscillator (IC1c) whose output will be passed on to the servo being controlled. This will send the controlled servo to its preset position.

Construction

This should pose no real problems provided that care is taken to put the diodes, IC1 and C3 the right way round. This is a little more awkward than usual since some components must be mounted vertically to conserve PCB area.

A socket is recommended for IC1 — at least the first time you build it. Take care when handling IC1 to discharge yourself of any static charge. This also applies to your soldering iron which must be earthed. CMOS devices are still

delicate things.

RV1 can be either vertical or horizontal mounting and the PCB is laid out for both. If you want to save space and weight use a vertical mounting device and cut off the end of the PCB as shown by the dotted line. Inputs and outputs can be soldered directly to the board or alternatively, there are some 0.1 in. pitch PCB connectors available from Maplin in 3 way versions which would do the job.

The whole unit could be mounted in a box or possibly just varnished to keep out moisture (but not if the device is likely to be immersed!). For use on low voltages, ie less than 5 V, it may be necessary to increase the value of C2 up to 100nF in order to maintain the required output timing.

PARTS LIST

RESISTORS (¼W 5% carbon film)

R1	10k
R2,3,5	1M0
R4	47k
RV1	100k min. preset horizontal or vertical mounting

CAPACITORS


C1	4n7F min. layer polycarbonate
C2	47nF min. layer polycarbonate (100nF for 3.6 volt operation)
C3	47uF 16 V min electrolytic

SEMICONDUCTORS

D1,2,3,4	1N4148
IC1	4093


MISCELLANEOUS

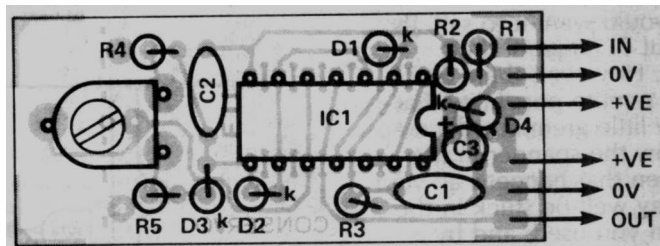PCB: see Buylines. 2 off 3 way 0.1 in. connectors (if required).



k = CATHODE

Fig. 2 Overlay diagram of the Conservo. Here we show a horizontal preset, but a vertical one could be used to save space — just cut the PCB along the marked line.

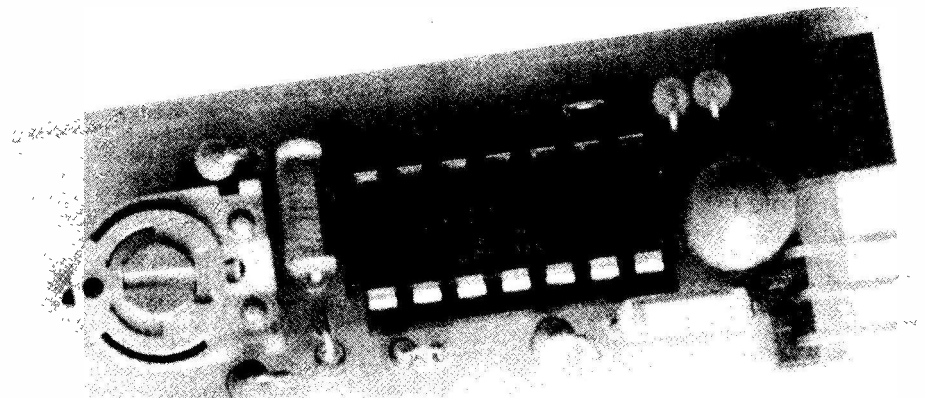

FOOTNOTE

*For those of you who are not scholars of Latin, Lex Divoti is a Law of Nature known by a number of names, most of them not printable, but can be summed up as: "If something can possibly go wrong, it will, at the most inconvenient moment and in the way that causes maximum damage."

BUYLINES

None of the components in this project should be at all difficult to obtain. The PCB is available through our PCB service — see page 77 for details.

All devices guaranteed Brand New and to full spec. Items ex stock despatched same day. Prices are EXCLUSIVE of VAT. Please add 60p to order to cover P&P BEFORE calculating VAT. Payment by cheque, Postal Order, Bankers Draft or Cash (PLEASE register) with order. Official orders from Govt. Depts and Educational Institutes Welcome. Trade Accounts opened subject to satisfactory status — send for details. We are pleased to receive overseas orders (please allow adequate postage — surplus refunded) which, unless accompanied by Bankers Draft in UK Currency may be subject to Bankers Commission and slight delay in despatch. Overseas trade enquiries welcome — send for full details. VAT not applicable to export orders. Price List detailing full range of components available — 30p refundable with first order. Please send SAE.

COMMQUIP

LTD
HAMILTON HOUSE 11 WALKERN ROAD
STEVENAGE HERTS SG1 3QD
Telephone (0438) 729771 Telex 8253378 G

COMPARE OUR PRICES

LINEAR				CMOS				74LS				TANTALUM					
555CMOS	80	LM3909	70	ZN459	285	4000	11	4518	39	LS00	11	LS153	38	BEADS	1N5408	19	
556CMOS	140	LM3911	120	ZN1034E	200	4001	11	4520	48	LS01	11	LS155	29	0.1/35	12	ZENER DIODES	
709	25	LM3915	175	LOGIC ICs				4521	90	LS02	11	LS156	33	0.22/35	12	2V7-33V500MW	7
741	14	LM3915	195	AY5-2376	590	4008	11	4522	105	LS03	11	LS157	25	0.33/35	12	5V1-75V 1.3W	14
748	35	LM13600	105	MC1488	55	4009	34	4526	55	LS04	12	LS158	27	0.47/35	12	BRIDGE RECTIFIERS	
9400CJ	345	MC1498	68	MC1489	55	4011	11	4527	65	LS05	12	LS160	30	0.68/35	12	1A/100V	20
AY-3-1270	710	MC3340	120	MM5303	625	4012	14	4528	45	LS08	12	LS161	35	1.0/35	12	1A/400V	23
AY-3-8910	370	MF10CN	350	MMS307	1250	4013	20	4531	65	LS09	12	LS162	35	1.5/35	14	1A/800V	25
AY-3-8912	540	ML924	195	MMS507	700	4015	39	4532	60	LS10	12	LS163	35	2.2/35	16	2A/100V	36
CA3046	60	NE529	225	MMS507	700	4016	20	4533	60	LS11	12	LS164	35	3.3/35	17	2A/200V	40
CA3080	65	NE531	135	MMS6114	365	4017	32	4538	80	LS12	12	LS165	40	10/25	18	2A/400V	40
CA3089	190	NE544	180	TMS6011	75	4020	42	4543	60	LS14	22	LS168	80	15/25	24	2A/800V	52
CA3080AQ	370	NE555	18	ULN2003	75	4021	39	4545	35	LS15	12	LS170	70	22/16	14	25/100V	36
CA3130E	85	NE556	45	8T26	99	4022	49	4555	35	LS20	12	LS171	47	33/16	14	25/200V	27
CA3140E	38	NE565	110	8T28	120	4023	39	4556	35	LS21	12	LS173	47	33/16	14	25/400V	27
CA3161E	100	NE566	140	8T95	90	4024	32	4558	100	LS22	12	LS174	36	4.7/16	16	25/400V	40
CA3189	200	NE567	100	8T97	90	4025	12	4584	40	LS22	12	LS175	36	6.8/16	16	25/600V	52
CA3240E	110	NE570	370	81LS95	80	4027	20	4585	50	LS27	12	LS181	87	10/16	18	REGULATORS	
ICL7106	680	NE571	370	81LS96	80	4028	47	COMPUTER ICs				LS183	105	15/16	27	78L05	30
ICL7611	95	RC4136	55	81LS97	80	4029	37	1802	650	LS32	13	LS190	35	22/16	27	78L12	30
ICL7621	180	RC4558	45	81LS98	85	4029	43	2650A	1175	LS33	14	LS191	35	33/16	40	78L15	60
ICL7622	180	SL490	250	6522	310	4035	45	6502	320	LS37	14	LS193	35	47/16	40	78L24	30
ICL8038	290	SL76477	380	6532	675	4040	40	6800	220	LS38	14	LS194	36	100/16	75	78L25	30
ICL8211A	150	SP8629	250	6821	110	4042	38	6802	250	LS40	12	LS195	32	15/10	22	78L26	30
ICM7224	775	TBA120S	70	6845	650	4043	40	6809	615	LS47	35	LS196	43	22/10	22	78L27	30
ICM7555	80	TBA800	75	6847	650	4044	41	8035	345	LS48	40	LS197	45	47/10	35	78L30	30
LF353	85	TBA810	95	6850	110	4049	21	8035	345	LS49	50	LS221	50	100/10	55	78L31	36
LF358	90	TBA820	70	6852	250	4050	42	8060	1090	LS51	14	LS240	55	100/6.3	42	78L32	36
LM10	325	TBA950	220	6875	485	4052	48	8080A	345	LS54	14	LS241	55	63V MINI MONOLYTHIC CERAMIC		78L35	36
LM301A	24	TDA1008	310	8155	350	4052	48	8085A	345	LS55	14	LS242	55	10nF	10	78L36	36
LM311	70	TDA1022	480	8212	110	4053	48	Z80A	315	LS56	16	LS243	55	22nF	10	78L37	36
LM318	120	TDA1024	115	8216	100	4066	22	MEMORIES				LS244	55	47nF	10	78L39	36
LM324	30	TL061	40	8224	110	4068	14	2101	395	LS75	16	LS245	55	68nF	10	78L40	36
LM334Z	90	TL062	60	8226	250	4069	13	2114(200ns)	85	LS76	16	LS251	28	100nF	14	78H05-5A/5V	550
LM335Z	120	TL064	95	8228	220	4071	13	2532	295	LS78	17	LS253	28			RESISTORS	
LM339	45	TL071	25	8243	270	4072	13	2708	225	LS83	33	LS257	29	1N4001	4	Carbon Film,	
LM348	60	TL072	45	8250	865	4073	13	2764	225	LS85	39	LS258	32	1N4002	4	High Stab 5%	
LM358	55	TL074	95	8251	250	4075	13	2764	225	LS86	15	LS259	53	1N4003	5	1/4W 10Ω-1M	
LM377	165	TL081	24	8253	400	4076	44	2764	225	LS88	39	LS266	18	1N4004	6	1/4W 10Ω-10M	
LM380	65	TL082	45	8255	400	4078	13	2764	225	LS89	22	LS267	30	1N4005	5	Metal Oxide/Film	
LM381	120	TL084	90	8257	400	4081	12	2716(5V)	210	LS90	22	LS279	53	1N4006	7	2% Met. Film E24	
LM382	110	TL170	49	8259	395	4082	12	2764	210	LS92	25	LS283	38	1N4007	4	1% Met. Film E24	
LM384	130	UA2240	115	8279	385	4093	23	2764	210	LS93	36	LS283	38	1N4148	2		
LM386	65	ULN2003	75	8832	250	4099	70	4116(200ns)	80	LS95	21	LS290	40	1N5401	12		
LM387	120	ULN2004	75	9602	220	4502	50	4118-3	325	LS109	21	LS293	40	1N5404	14		
LM393	95	XR2206	285	Z80ACTC	260	4508	110	4164	420	LS112	20	LS366	27	1N5407	12		
LM711	60	ZN414	79	Z80ADART	775	4510	45	5101(450ns)	150	LS113	20	LS367	27	1N5408	14		
LM725	325	ZN423	130	Z80ADMA	975	4511	45	5204	725	LS114	21	LS368	27	1N5409	14		
LM733	69	ZN424	130	Z80AP10	270	4512	42	6116(150ns)	375	LS123	34	LS368	27	1N5410	12		
LM747	60	ZN425E	340	Z80AEB	320	4514	110	6514	330	LS126	25	LS368	27	1N5411	12		
LM1458	40	ZN426E	290	Z80AEB	320	4514	110	6810	115	LS132	29	MICRO-MINI 100V CERAM PLATE CAPS					
LM2917	185	ZN427E	575	Z80AEB	320	4515	110			LS136	23	1pF 10nF	7	BEADS			
LM3900	45	ZN428E	395	Z80AEB	320	4516	50			LS138	24			ZENER DIODES			
										LS139	27			BRIDGE RECTIFIERS			
										LS151	30			REGULATORS			

RECRUITING? SELLING A PRODUCT? OR A SERVICE?

GET MAXIMUM BENEFIT FOR
YOUR MONEY

FIND OUT ABOUT OUR WHOLE
RANGE OF PUBLICATIONS IN:

COMPUTING VIDEO RADIO ELECTRONICS

Simply telephone

ASP CLASSIFIED

01-437 1002

(We take Access and Barclaycard)

It's easy
to complain
about
advertisements.

The Advertising Standards Authority. ✓
If an advertisement is wrong, we're here to put it right.
A.S.A. Ltd., Brook House, Torrington Place, London WC1E 7HN.

Z80 CONTROLLER COMPUTER

This article describes the design and construction of a simple microcomputer control unit. (We called it MARVIN for reasons that would take too long to explain.) The unit is designed specifically for control functions which usually require complex purpose-built hardware. Consisting of a microprocessor and support chips, the unit is cheap enough to be used as an alternative to hard-wired logic with the advantage that its function is determined by easily-changed software.

The system can be used in conjunction with analogue devices, heavy duty switching, light dimmers, remote controllers, etc, to control anything from a Stirling Moss style computer controlled futuristic home to a morse code tutor.

Since there are so many possible uses, the construction of only the central computer parts (CPU, I/O, interrupt board) will be described; you will be left to chose external circuits according to your needs. Some additional interfaces will be available from the kit suppliers (see Buylines for details).

Split Personality

For maximum flexibility, MARVIN is divided into a CPU

board and two other types of board. The CPU board houses the microprocessor, a 2K EPROM containing the operating system, a second 2K of EPROM for the user's programs, 1K of RAM accessible to both the operating system and the users, and the selection circuitry for the various types of external port

details of programming will be given in a further article.

Since the I/O ports are on individual boards, you can add as many or as few as you need. MARVIN's I/O board provides 16 latched output lines and 16 input lines, which are TTL compatible. You can use up to five of these

boards.

The other type of board we shall describe provides up to eight individual lines which can interrupt the CPU. These are useful for allowing external devices to force the CPU to carry out a pre-designated routine. A typical use might be for controlling devices that need servicing at regular intervals, using an external clock to provide the timing.

This first part describes the functioning and construction of the CPU

board. This will be followed by a description of MARVIN's I/O and interrupt board and of MARVIN's operating system.

EPROMs

A Z80A running at 4 MHz theoretically needs memory capable of 375 nS access time. Most 2716s have an access time of 450 nS and although some may work adequately, it is strongly recommended that for reliable operation you make sure that you buy 350 nS EPROMs. If you decide

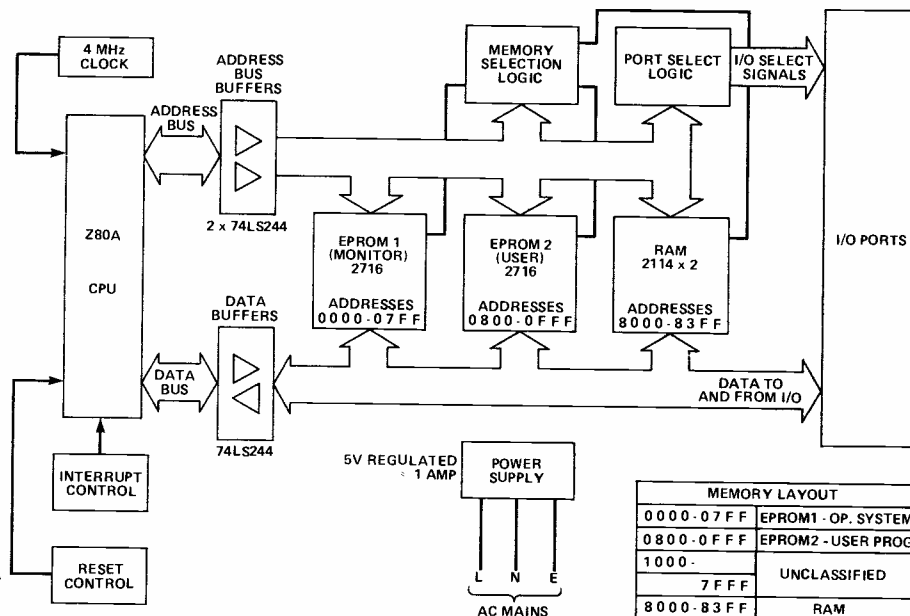


Fig. 1 Block diagram of Marvin.

MEMORY LAYOUT	
0 0 0 0 - 0 7 F F	EPROM1 - OP. SYSTEM
0 8 0 0 - 0 F F F	EPROM2 - USER PROG
1 0 0 0 -	
7 F F F	UNCLASSIFIED
8 0 0 0 - 8 3 F F	RAM

board.

Although 2K of program may seem small in comparison with the memory capacity of a personal computer, it will hold a surprisingly complex machine code program, of up to nearly 1000 instructions.

Several of the routines that you are likely to need are built into the operating system, and are directly accessible to the user by simple two-byte instructions. Your program must be inserted into the EPROM before use by a suitable PROM programming unit. Some further

Computer projects are usually complex affairs, as anyone who saw the Cortex will testify. This one isn't. Design and development by Peter Grigson and David Harris.

to make do with 450 nS types, then the crystal should be changed to 3.2768 MHz.

Also, we suggest that you should use a zero insertion force socket for the user EPROM, as

you'll probably be taking it in and out quite a lot.


Construction

The component layout of the PCB is shown in Fig. 4. The PCB is

double sided, but as PCBs with plated through holes are expensive, pins have been used to make connections between the two sides. The PCB is difficult to make unless you have access to suitable

equipment: see Buylines for the source of the PCB. If you do make it yourself, you must be very careful to align the two sides accurately. All the holes are cut using a 0.8 mm (or approx) drill.

Fig. 2. Circuit diagram of Marvin's main board.

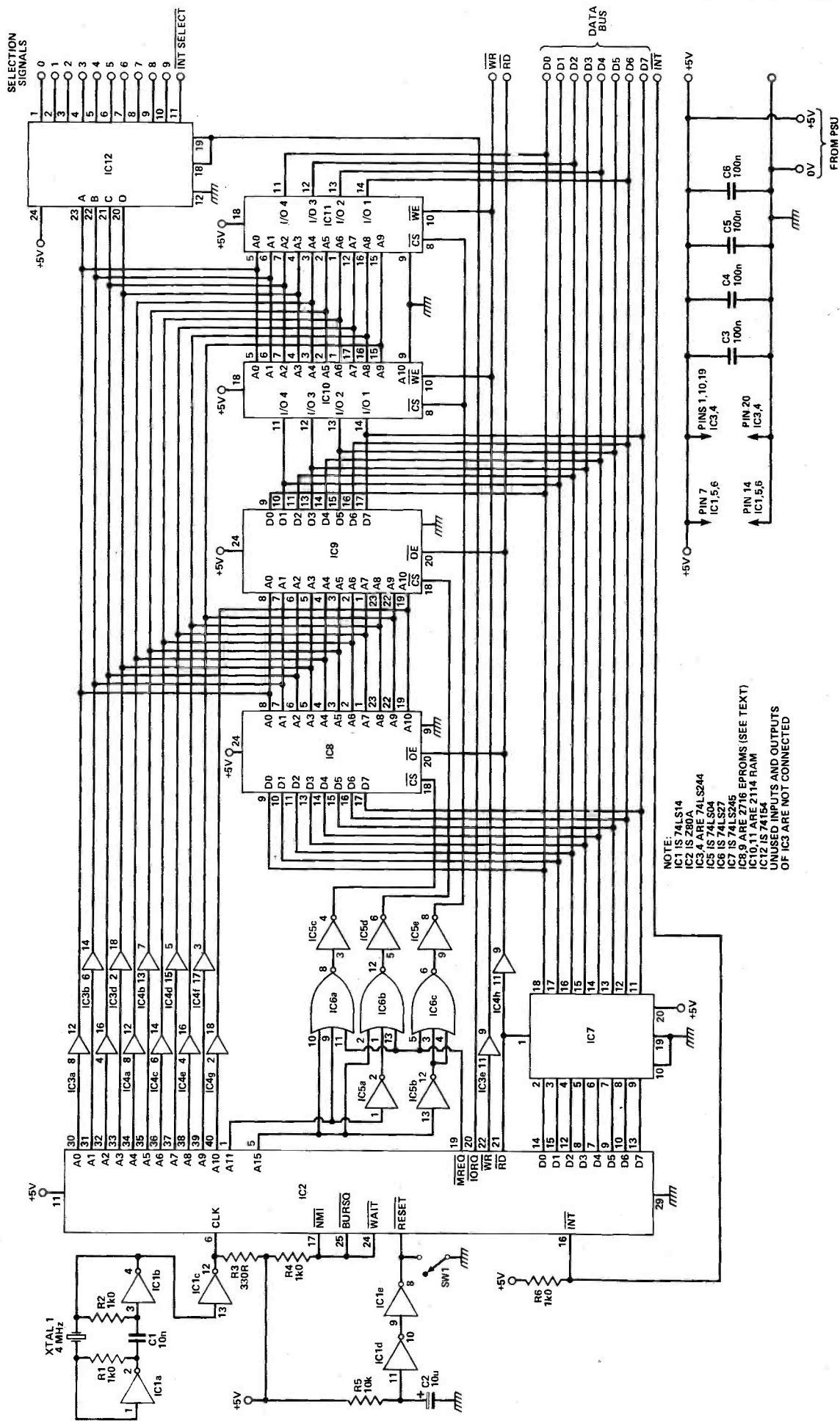

NOTE:
 IC1 IS 74LS14
 IC2 IS Z80A
 IC3,4 ARE 74LS244
 IC5 IS 74LS04
 IC6 IS 74LS27
 IC7 IS 74LS246
 IC8,9 ARE 2716 EPROMS (SEE TEXT)
 IC10,11 ARE 2114 RAM
 IC12 IS 74LS123
 UNUSED INPUTS AND OUTPUTS
 OF IC3 ARE NOT CONNECTED

HOW IT WORKS

Schmitt triggers IC1a and b form a standard oscillator circuit whose frequency is stabilised at 4 MHz by XTAL1; the output from this oscillator is buffered by IC1c and fed into the clock input of the Z80 CPU, IC2 (R3 is necessary to fulfil the Z80's input requirements as it has no internal pull-up resistor). NMI, BUSRQ, and WAIT inputs are not used in this design, so they are tied high by resistor R4.

At switch-on, execution would begin at a random location in the memory but for C2 (via IC1d and e) holding RESET low until voltages and internal CPU register contents stabilise. The CPU may be reset at any future time by momentarily closing SW1 (note that debouncing is unnecessary). After being

reset, the Z80 will begin by fetching an instruction from memory location 0000 hexadecimal, and executing it. Therefore, it places this address on the address bus and then takes MREQ and then RD low.

The memory selection logic, ICs 5 and 6, detects that this address is less than 07FFH and enables IC8, the EPROM containing the operating system. MARVIN then proceeds with the initialisation program in the operating system.

The address bus is buffered by most of two 74LS244s, ICs 3 and 4, and the data bus by a single 74LS245, IC7. As data can pass to and from the CPU, IC7 has to be a bidirectional device. ICs EPROMs, ICs 8 and 9, and the RAM, ICs

10 and 11 have their address and data lines permanently wired to the buses, but each has an individual selection line (CS) that takes its bus connections to a high impedance state until the selection line is pulled low by the memory selection logic.

The output enable inputs (OE) on the EPROMs are connected to RD (read) from the Z80, and the RAMs' WE (write enable) inputs are connected to WR (write).

If the MPU wants to perform an output or input operation it takes IORQ low; address lines A0 and A3 will contain (in binary, of course) the number of the port to be selected. Either RD or WR can be low, depending on whether the port is to be read from or written to.

IC12 is a four to 16 line decoder, and it's used to provide an individual selection line for each port. IC12 is active only when IORQ is low, so port boards may be selected by one of these lines and either RD and WR. Only one interrupt board is usable, so there is only one interrupt selection line, INT SELECT.

The interrupt line itself, INT, is normally held high by R3; however, it may be pulled low by a suitable external device. Because we have chosen to use INT rather than NMI (non maskable interrupt), it is possible to program MARVIN to ignore interrupts. If this has not been done, the result of pulling INT low will be to make the CPU service the interrupt according to your predesignated routine.

PARTS LIST

RESISTORS (all 1/4 W 5%)	
R1, 2, 4, 6	1k0
R3	330R
R5	10k
CAPACITORS	
C1	10n ceramic
C2	10u axial electrolytic
C3, 4, 5, 6	100n ceramic or polyester
SEMICONDUCTORS	
IC1	74LS14 or 7414
IC2	Z80A
IC3, 4	74LS244
IC5	74LS04 or 7404
IC6	74LS27 or 7427
IC7	74LS245
IC8, 9	2716 EPROM (see text)
IC10, 11	2114 RAM (300nS or less)
IC12	74154
MISCELLANEOUS	
SW1	push to make single pole switch as required
XTAL1	4 MHz crystal (see text)
IC sockets: one 40 pin, two 24 pin, two 18 pin; Veropins (about 130); PCB; edge connector if required; ribbon cable.	

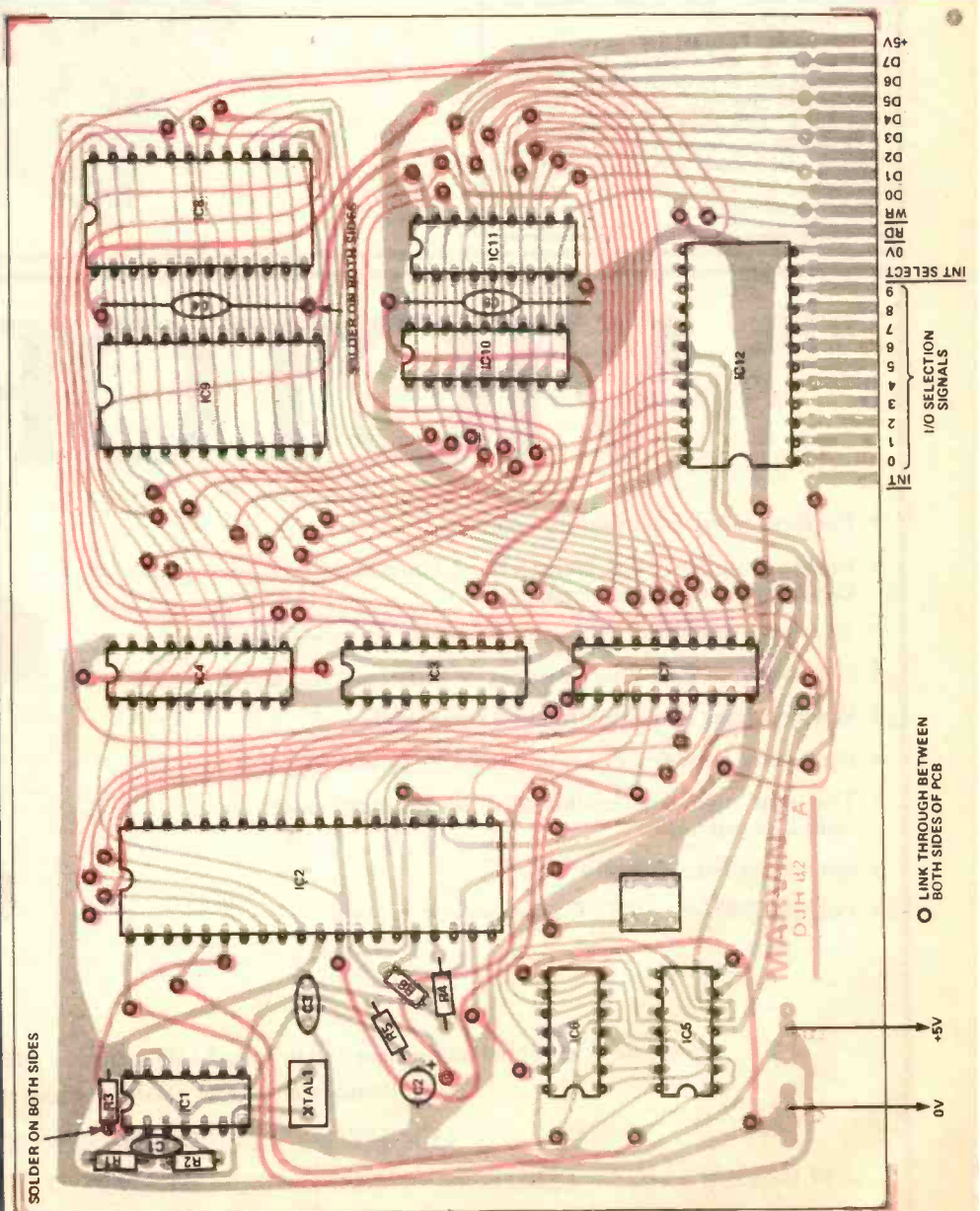


Fig. 3 Overlay diagram.

ICs 2,8,9,10,11 should be socketed as they are NMOS devices; Sockets are optional for the remaining TTL ICs, and there should be no problems in soldering them directly provided the usual precautions are observed.

To proceed with the construction, first insert and solder, on the underside only, all the TTL ICs, and the sockets for the NMOS. It is a good idea to use a fine-tipped soldering iron and to be careful to check that you do not make any bridges between tracks, especially where they pass between IC pins.

Next insert and solder the crystal, resistors and capacitors

(noting the polarity of C1). Where there are pads on both sides of the board the components' leads should be soldered to both. There will remain a large number of unused holes, and many of these are used for the pins that link tracks on both sides of the board. You can tell these holes by looking to see if there are pads on both sides of the hole: if this is the case, then you should insert a pin and solder on **both** sides.


You can use a 24-way 0.1 in. pitch edge connector to connect the

board to the others; we recommend that power connections to all the boards be hard-wired to the positions provided and not taken through the connector. If you're very cost-conscious, you could hard-wire direct; holes have been provided for you to insert pins for this purpose next to the edge connector strips.

Finally, solder SW1 (reset) into position, or, if you prefer, take off wires to a control panel.

BUYLINES

The following will be available from ARK Electronics, Ashes Lane, Wentworth, Rotherham, S. Yorks S62 7TY:
EPROM containing the monitor program, 4 MHz clock, £6.00; 3 MHz (or lower) clock £4.00;
Double sided PCB, £6.00;
Complete 4 MHz kit excluding the operating system EPROM £26.00.
Please add 50p p&p and make cheques payable to ARK Electronics. Sending an SAE to ARK will secure further details of D-to-A and A-to-D converters, lighting dimmers, remote controllers and a speech synthesiser.

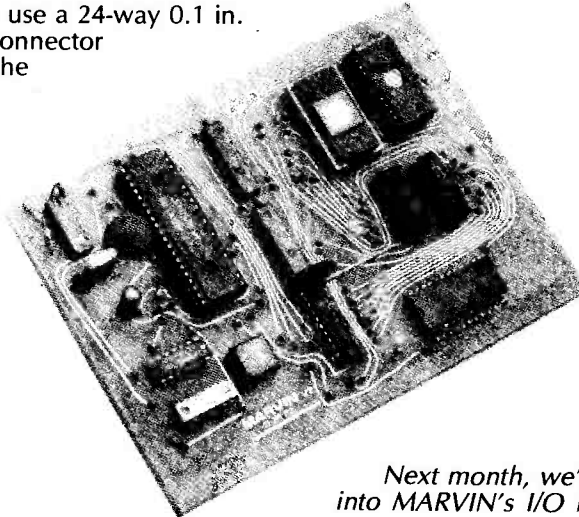


Next month, we'll be delving into MARVIN's I/O boards.

ETI

THE VICTORY ORGAN

- ★ Exciting range of authentic voices
- ★ Preset sounds—Piano, Harpsichord, Hawaiian Guitar (with glide), Banjo (with repeat), Accordion
- ★ 16 modern rhythms with superb sounds including handclap
- ★ Full range of 'Easi-Play' features ★ Custom Programmed ROM
- ★ Walking Bass on Lower Manual and Pedals
- ★ Real wood veneer cabinet with American walnut finish
- ★ The only organ with update facilities for synthesizer and "add-a-chord" unit
- ★ Starter kit from £98.80 + VAT
- ★ Full kit £280.54 + VAT Carriage extra on kits

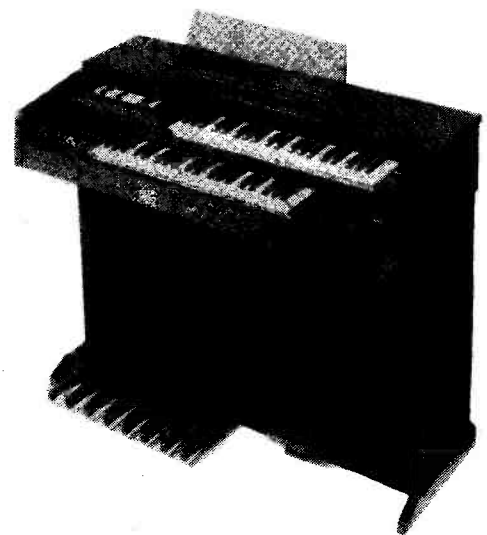

Send for a demonstration tape today only £1.95 inclusive. Hear the difference yourself.

Full details & specification on request

LEIGHTON ELECTRONIC SERVICES

17 BRIDGE STREET, LEIGHTON BUZZARD, BEDFORDSHIRE LU7 7AH · TELEPHONE (0525) 382504

Interak 1

THERE'S NO LIMIT TO WHAT A COMPUTER WITH NO CARDS CAN DO!

It's the oldest trick in the book to grab your attention with a stupid title, but in this case there's a grain of truth in the statement above.

The Interak 1 Computer System is a 4MHz Z80A development system, one which you build yourself, perhaps for enthusiastic home use, or more often for industrial or educational purposes.

The fundamental structure is a 3U 19" rack which has space for 13 cards ("International" size, i.e. 4.5" x 8") on 1" pitch, with space for a power supply at one end of the rack. International size — rack mounting: Inter-rak Interak!

13 cards 4.5" by 8" gives a total potential board area of over 400 square inches, enough for a couple of hundred chips or more; there's no real limit on what that could do is there? (It would leave a few of today's marvels a bit in the shade eh?)

But don't be scared, you don't have to build a Frankenstein's monster until you're ready. The first few cards are pretty straightforward: First the VDU-K, which can be connected to your own T.V. (or monitor), then the Z80A-CPU card, the brains; then dynamic RAM, and finally the Keyboard interface (to any standard parallel ASCII keyboard), and you've got a computer — with the ultimate resource: 9 empty slots for the future. (Perhaps use one of them for a 2400 baud tape interface or later floppy disks.)

Example prices (excluding VAT), everything is available separately and full after sales service in case you make a mistake: Z80A CPU card £10.95, Manual £1.50, Main Parts £13.41.

40 type-written pages of description, specification, price lists etc. are yours for the asking (a 25p stamp and/or SAE is a help, but not essential), or telephone if you prefer. You'll have to live with your computer for a long time, so make the effort and find out all about Interak now; a couple of minutes is all it takes to ask for a leaflet!

Greenbank

Greenbank Electronics (Dept. T8E), 92 New Chester Road, New Ferry, Wirral, Merseyside L62 5AG
Telephone: 051-645 3391

circuit board components

Castle House, 1 Castle Lane, Bedford MK40 3QE
Telephone 0234 214219

Please note our new address

All components brand new — Please add 35p P&P plus 15% VAT. Please send cheque or P.O. with your order. Official orders are welcome from educational establishments, Government bodies and public companies. Credit accounts are available. Please ask for details.

LOW PROFILE SOCKETS
8 Pin 8p 14 Pin 10p 16 Pin 11p
18 Pin 16p 20 Pin 18p 22 Pin 22p
24 Pin 24p 28 Pin 28p 40 Pin 30p
ORDER 12 OF ANY ONE TYPE AND WE WILL SUPPLY 13.
"A BAKERS DOZEN"
SPECIAL FOR JUNE-JULY '83

MEMBRANE KEYPADS. By F.S.T.
Multi-choice Graphics Keyboard. 57 standard characters to choose from. Blue or white as standard graphic options keyboard complete with flexible backing with Berg connector.

PANEL DIMENSIONS
3 x 4 — 79 x 98 mm £5.98
4 x 4 — 97 x 98 mm £6.69
5 x 4 — 114 x 98 mm £7.41

TTL			
7400	11p	7427	18p
7401	11p	7428	25p
7402	11p	7430	13p
7403	12p	7432	20p
7404	12p	7433	20p
7405	14p	7437	23p
7406	19p	7438	24p
7407	19p	7440	14p
7408	13p	7442	30p
7409	13p	7444	85p
7410	13p	7446	56p
7411	15p	7447	36p
7412	17p	7448	43p
7413	17p	7450	14p
7414	23p	7451	14p
7416	19p	7453	14p
7417	19p	7454	14p
7420	14p	7460	14p
7421	19p	7472	22p
7422	19p	7473	24p
		7474	19p
		7475	26p
		7476	25p
		7480	45p
		7482	86p
		7483	30p
		7485	80p
		7486	19p
		7489	180p
		7491	19p
		7491	34p
		7491	24p
		7493	24p
		7497	33p
		7495	33p
		7496	38p
		7497	86p
		74100	78p
		74107	22p
		74108	24p

CMOS			
4000	10p	4020	42p
4001	10p	4021	40p
4002	12p	4022	45p
4006	50p	4023	18p
4007	14p	4024	33p
4008	36p	4025	12p
4009	24p	4026	75p
4010	24p	4027	20p
4011	10p	4028	49p
4012	15p	4029	45p
4013	20p	4030	14p
4014	48p	4031	125p
4015	40p	4034	140p
4016	20p	4035	249p
4017	30p	4039	280p
4018	45p	4040	40p
4019	25p	4041	40p
		4042	38p
		4043	40p
		4044	40p
		4046	40p
		4047	35p
		4048	38p
		4049	21p
		4050	21p
		4051	42p
		4052	48p
		4053	48p
		4054	78p
		4055	80p
		4059	430p
		4060	42p
		4063	80p
		4066	22p

Free — Satin Gold Biro
With all orders over £3.00 in "June and July" '83

TRAIN FOR SUCCESS

in Television, Radio & Electronics

ICS have helped thousands of ambitious people to move up into higher paid more secure jobs in the field of electronics—now it can be your turn. Whether you are a newcomer to the field or already working in the industry, ICS can provide you with the specialised training so essential to success.

Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful, is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

Basic Electronic Engineering (C & G/ICS)
Radio Amateurs

Certificate Courses

TV & Audio Servicing
TV, Radio and Audio Engineering
Radio & Amplifier Construction
Electronic Engineering*
Computer Electronics*
Industrial Electronics*
Radio Frequency Electronics*
Electrical Engineering*
Qualifical Contracting & Installation

*Quality for IET Associate Membership



Approved by CACC



Div. National Education Corporation



Member of ABCC

FREE BOOK

Please send me your FREE School of Electronics Prospectus

Subject of interest _____

Name _____

Address _____



Dept K265
ICS School of Electronics
160 Stewarts Road
London SW8 4UJ



01 622 9911
(All Hours)

SERVICE SHEET

Enquiries

We receive a very large number of enquiries. Would prospective enquirers please note the following points:

- We undertake to do our best to answer enquiries relating to difficulties with ETI projects, in particular non-working projects, difficulties in obtaining components, and errors that you think we may have made. We do not have the resources to adapt or design projects for readers (other than for publication), nor can we predict the outcome if our projects are used beyond their specifications;

- Where a project has apparently been constructed correctly but does not work, we will need a description of its behaviour and some sensible test readings and drawings of oscillograms if appropriate. With a bit of luck, by taking these measurements you'll discover what's wrong yourself. Please do not send us any hardware (except as a gift!);

- Other than through our letters page, Read/Write, we will not reply to enquiries relating to other types of article in ETI. We may make some exceptions where the enquiry is very straightforward or where it is important to electronics as a whole;

- **We will not reply to queries that are not accompanied by an SAE** (or international reply coupon). **We are not able to answer enquiries over the telephone.** We try to answer promptly, but we receive so many enquiries that this cannot be guaranteed.

- Be brief and to the point in your enquiries. Much as we enjoy reading your opinions on world affairs, the state of the electronics industry, and so on, it doesn't help our already overloaded enquiries service to have to plough through several pages to find exactly what information you want.

Subscriptions

The prices of ETI subscriptions are as follows:

UK: £13.15
Overseas: £16.95 Surface Mail
£36.95 Air Mail

Send your order and money to: ETI Subscriptions Department, 513 London Road, Thornton Heath, Surrey CR4 6AR (cheques should be made payable to ASP Ltd). Note that we run special offers on subscriptions from time to time (though usually only for UK subscriptions, sorry).

ETI should be available through newsagents, and if readers have difficulty in obtaining issues, we'd like to hear about it.

Backnumbers

Below we list the backnumbers that are available from our backnumbers department. Please note that this list will be out of date if you use an old copy of the magazine. Backnumbers cost £1.50 (UK or overseas by surface mail) and are available from: ETI Backnumbers Department, 513 London Road, Thornton Heath, Surrey CR4 6AR (cheques should be made payable to ASP Ltd).

Even if the copy of ETI you need is not listed, all may not be lost, because we run a photocopying service. For £1.50 (UK and overseas) we will photocopy an entire article (note that parts of a series of articles count as separate articles). Your request should clearly state what article you require and the month and year in which it appeared (the index for 1980 and 1981 was published in January 1982, and the index for

1982 appeared in December 1982). Send your request to ETI Photocopies, Argus Specialist Publications Ltd, 145 Charing Cross Road, London WC2H 0EE (cheques should be made out to ASP Ltd).

November 78
November 79
April 80
September 80
October 80
November 80
December 80
January 81
February 81
March 81
April 81
May 81

June 81
November 81
December 81
March 82
May 82
June 82
July 82
August 82
September 82
October 82
December 82
February 83

Write For ETI

We are always looking for new contributors to the magazine, and we pay a competitive page rate. If you have built a project or you would like to write a feature on a topic that would interest ETI readers, let us have a description of your proposal, and we'll get back to you to say whether or not we're interested and give you you all the boring details.

We don't bother with the bureaucracy for Tech Tips — all you do is to send in your idea, stating clearly if you want an acknowledgement of receipt. If possible, please type your explanation of why the circuit is different, what it does and how it works, on a separate sheet from the circuit diagram; both sheets should carry your name, address and the circuit title. We'll let you know (within a month or so) if we want to use your Tech Tip.

Trouble With Advertisers

So far as we know, all our advertisers work hard to provide a good service to our readers. However, problems can occur, and in this event you should:

1. Write to the supplier, stating your complaint and asking for a reply. Quote any reference number you may have (in the case of unsatisfactory or incomplete fulfilment of an order) and give full details of the order you sent and when you sent it.
2. Keep a copy of all correspondence.
3. Check your bank statement to see if the cheque you sent has been cashed.
4. If you don't receive a satisfactory reply from the supplier within, say, two weeks, write again, sending your letter recorded delivery, or telephone, and ask what they are doing about your complaint.

If you exhaust the above procedure and still do not obtain a satisfactory response from the supplier, then please drop us a line. We are not able to help directly, because basically the dispute is between you and the supplier, but a letter from us can sometimes help to get the matter sorted out. But please, don't write to us until you have taken all reasonable steps yourself to sort out the problem.

We are a member of the mail order protection scheme, and this means that, subject to certain conditions, if a supplier goes bankrupt or into liquidation between cashing your cheque and supplying the goods for which you have paid, then it may be possible for you to obtain compensation. From time to time, we publish details of the scheme near our classified ads, and you should look there for further details.

OOPS!

We have in the past published small corrections to projects on the letters page, and major corrections separately. From now on corrections will appear on this page, and will be repeated for several months (just to increase our embarrassment). If a correction is too large to fit on here, we will publish it just once, but will note the fact that a correction does exist, and that copies of it can be obtained from us provided you send in an SAE. But please — request copies only if you really do need them; if this service is abused, we may be forced to withdraw it.

ZX A to D (Jan '83)

D2 is shown the wrong way round on the overlay; wires on the RH side of the switch SW1 should go to top contacts. Some of the early PCBs had an error: pins 2 & 4 of IC1 should go to pin 16 (top) of edge connector (published foil pattern is OK).

.Stage Lighting Unit (Jan, Feb, April, May '83)

Transformer specs are as follows: Primaries all 250 V; secondaries T1: 0-6, 0-6 V, 12 VA tot; T2: 0-12, 0-12 V, 12 VA tot; T3: 0-6 V, 3 VA. ICs 34, 35, 36 are 7805 5V regulators.

ZX Sound Board Design Comp. results, Feb '83)

The first line of the program has to be entered in reverse order to get it to go in (COS, GOSUB, COPY, ASN and RND are functions). The line should read:

```
10 REM : "Y - =?COS GOSUB 5 COP  
Y ??ASN ?RND??RND
```

Alarm Module (MARCH '83)

R21 is 220k (parts list OK, circuit diagram wrong) Q5 is BC182L (left off parts list).

Max Min Thermometer (April '83)

A revised foil pattern was published in July ETI. To get original PCB to work, replace D4 and D5 with wire links, cut tracks from pins 7 and 8 on IC6, and solder 15k resistor across cut — remove ICs while doing this! (It's messy but it works.)

Real Time Clock (April '83)

Frequency of XTAL1 is 32.768 kHz.



NDFL Power Amplifier (May '83)

C13 is 33p (parts list correct, circuit diagram wrong). Table 1: lengths of wire quoted do not allow for lead lengths — add 40 mm or so to them. This is particularly important for L3. Resistors R29 and R30 can be wire-wound types, it isn't necessary to use carbon types (their inductance will be small).

Flash Sequencer (July '83)


Q1 should be BC184L; Q2-5 should be BC182L.

PCB FOIL PATTERNS

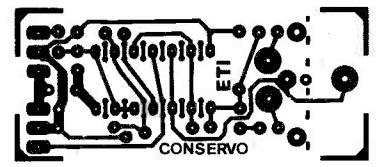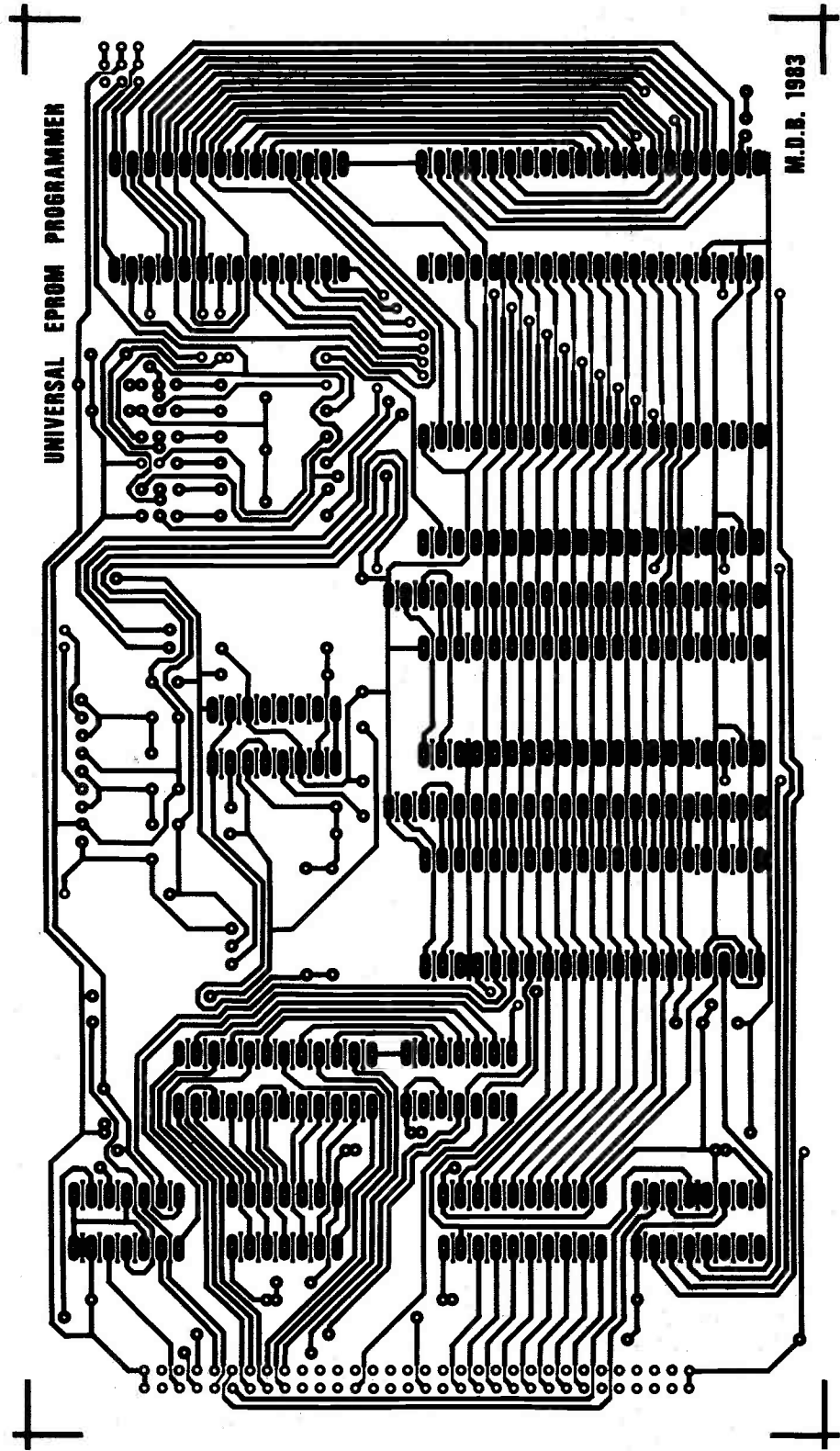


The Servo Fail-Safe

Universal EPROM Programmer

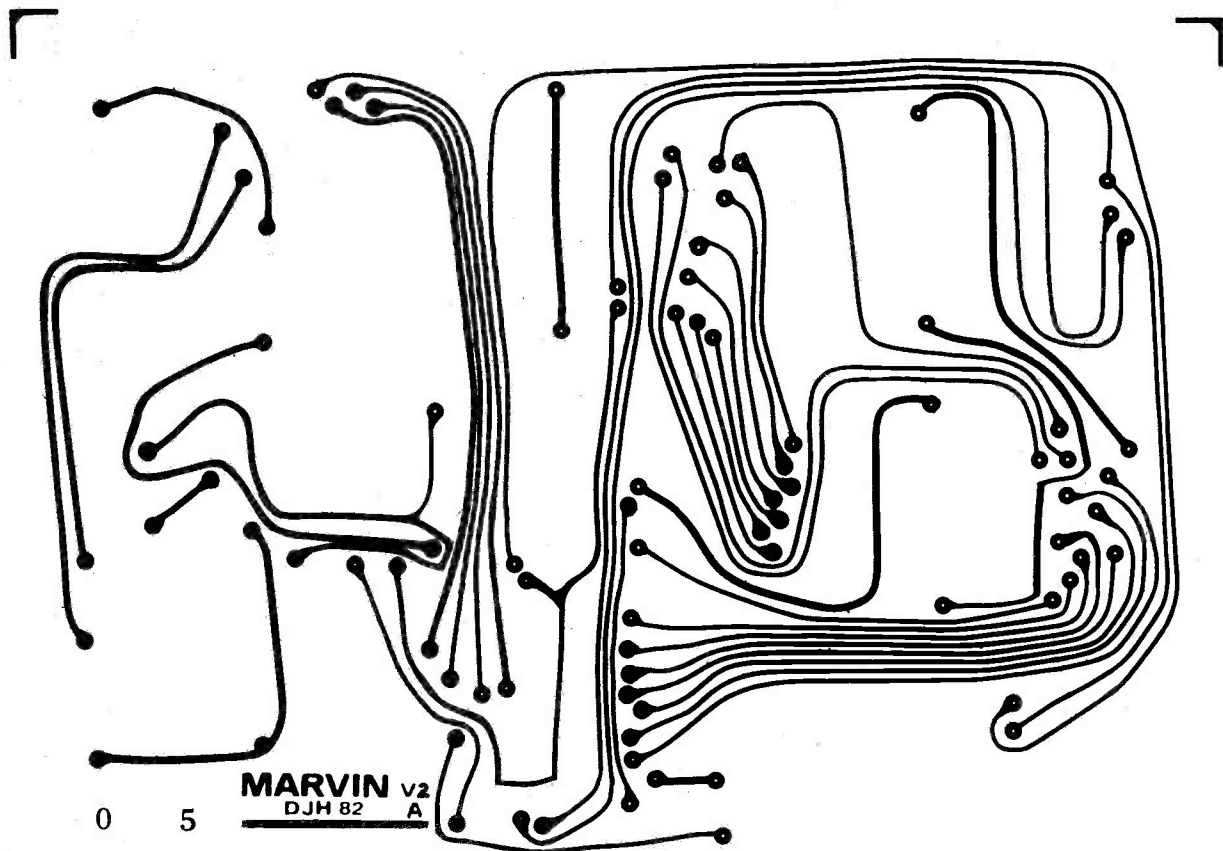

Marvin (component side)

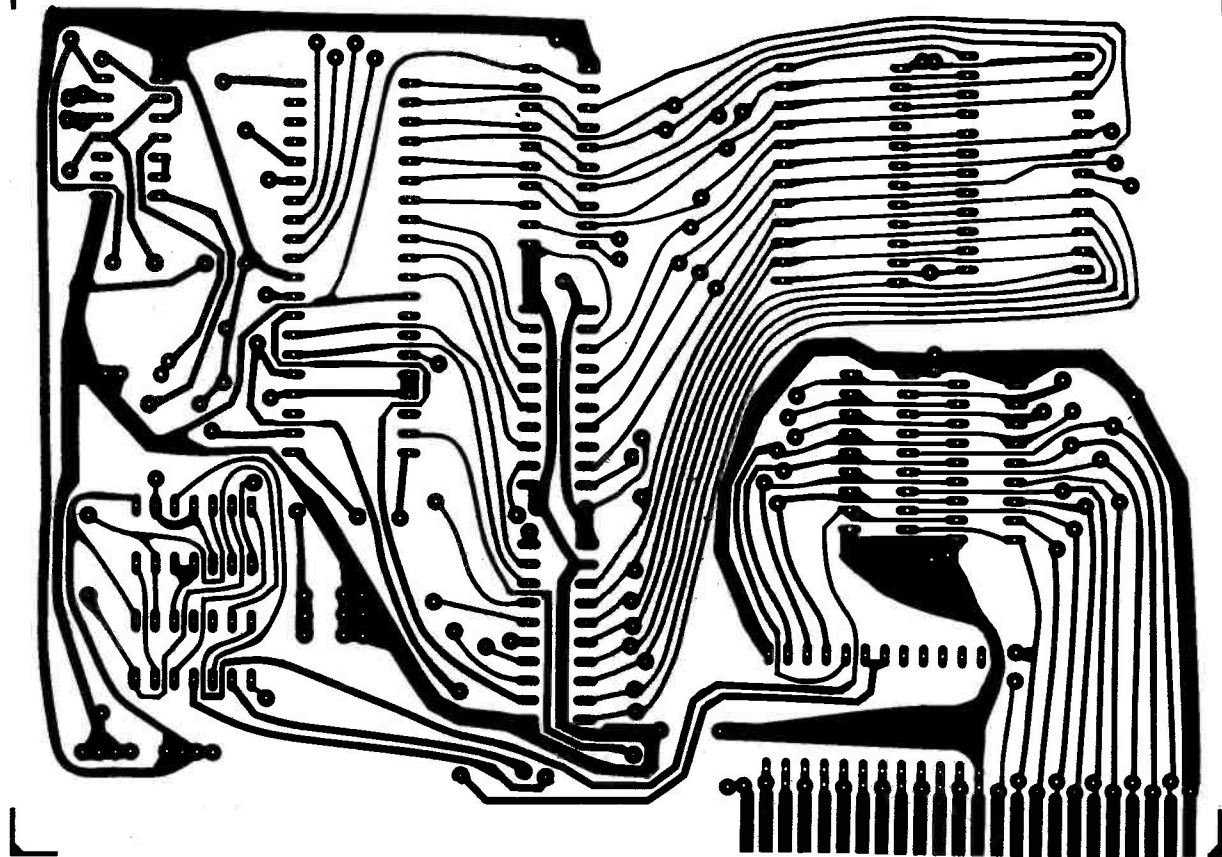

Marvin (solder side)

HOME COMPUTERS

AQUARIUS



AQUARIUS: The brand new Aquarius Personal Computer is part of Mattel Electronics latest developments in advanced technology and offers full home computing facilities, as well as extensive game play, using a very wide range of plug in cartridges. Since Aquarius is a Mattel Electronics product, it benefits by the company's wide experience of producing high

technology equipment, as well as their game programming expertise which is evident from the advanced games which have been produced for the Intellivision. Aquarius costs £79 and comes with microsoft basic built in. It is so simple to use that you'll be writing your first programs within minutes of taking the machine out of its box. You can even record the programs on your own cassette recorder at home, so you can use them again at a later date. Most available domestic tape recorders are compatible with the Aquarius.

A POWERFUL MACHINE: For all its simplicity, it is also very sophisticated. It has a 280A processor and 8K of built in ROM as well as 4K of RAM, which is user expandable to 52K. It has a display of 40x24 characters, and a graphic resolution of 320x192 with a total character set of 256 (including the complete ASCII set with upper and lower case letters, numbers and additional graphic symbols). The keyboard has 49 full stroke moving keys, unlike some of the cheaper machines which have membrane keyboards. The size of the machine (excluding any of the additional peripherals), is 13"x6"x2".

PERIPHERALS: It is very easy to increase the capabilities of your Aquarius as all the peripherals plug straight into one another. You can add a Printer, a Modem, a Data Recorder, Mini Expander and other items. All of the peripherals are very easy to install and what is more, they're easy to use. But the best news of all is, they're easy to afford.

CPM OPERATING CAPABILITY: The Aquarius is capable of being expanded to 52K RAM and later in 1983 a disk drive will be available for it, with the commercial CPM business operating system. This will allow you access to one of the largest software libraries in the world, with literally hundreds of programs available for you to use.

CARTRIDGES: Various sophisticated programs will be launched on plug in cartridges such as a Visicalc type spreadsheet and a word processor. In addition there will be dozens of games and utilities and alternative languages such as Logo, which combined with the built in microsoft basic gives an unbeatable combination of high quality programming ability.

MATTEL AQUARIUS - £68.70 + VAT = £79

£79

ATARI 400/800



NEW LOW PRICES

ATARI 400/800: With the Atari Personal Computers, you can play the ultimate in T.V. games, teach yourself new subjects or skills, balance budgets, and even write your own computer programs in Basic.

SPECIFICATIONS: Both the Atari 400 and 800 can display in up to 16 colours, each with 16 intensities. They have four independent sound synthesizers for music tunes/game sounds, giving four octaves with variable volume and tone control on your T.V.'s speaker. The display graphics

are of amazing quality, having a detailed resolution of 320 x 192, comprising 24 lines of 40 characters. Atari personal computers have a standard 10K ROM operating system. In addition the standard Atari 400 (£149) comes with 16K of RAM, and the expanded version with 48K (£198). The Atari 800 (£299) comes with 48K as standard. Both the 400 and 800 are now supplied with a FREE £40 Basic Programming Kit, which includes the Basic Programming Cartridge, as well as a 120 page Basic Reference Manual and the 184 page Self Teaching Manual by Bill Carris called 'Inside Atari Basic', so you can begin programming straight away, without buying any 'extras'. Even a mains plug is supplied!

OVER 500 PROGRAMS AVAILABLE: The Atari computers are supported by well over 500 programs available for your use, a larger selection than you will find on any other television game or home computer! The wide selection puts Atari way ahead of the competition. Just fill in the coupon and we will be pleased to send you a full price list which gives details of our range of software available for entertainment, home education, programming and home office use. We think you'll agree when we say it's quite impressive.

100 FREE PROGRAMS FROM SILICA SHOP: If you buy your Atari Home Computer from Silica Shop, you will receive a FREE presentation pack of 6 cassettes, containing 100 programs including games, utilities and demonstrations. A 16 page booklet giving full details of all of these programs is available on request. If you have already purchased your computer elsewhere you can buy the set of 6 cassettes for £30. What's more, Silica Shop offer a two year guarantee on all computers as well as a FREE joystick. This adds up to a great offer that we believe can't be beaten or matched by any of our competitors.

ATARI 400 16K - £129.57+VAT=£149

ATARI 400 48K - £172.17+VAT=£198

ATARI 800 48K - £260.00+VAT=£299

£149

COLECOVISION



THE SYSTEM: The CBS Colecovision offers new standards in video game play. The excellent graphics are well implemented with arcade titles such as Zaxxon, Lady Bug, Gorf, Wizard of Wor, Carnival, Mouse Trap and the lovable Smurfs. The console comes supplied with a three screen arcade quality version of DONKEY KONG. Parker and other companies have also announced ranges of cartridges for Colecovision, to further enhance the wide range of quality titles available for this new television games machine.

THE CONSOLE: The CBS Colecovision video games system has advanced technology which produces superlative graphics resolution and excellent sound effects. The styling of the console and hand controllers has been carefully researched; the console is designed to complement modern hi-tech equipment, and has clear features for easy operation. The hand controllers allow fingertip control via the 8 direction joystick, and feature 2 independent fire buttons. The push button keyboard is used for game selection and for game control with some cartridges. The hand controllers are detachable and are connected to six feet of telephone coil cable, storing neatly away in the console when not in use.

ATARI EXPANSION MODULE: The Atari converter module allows Atari VCS software cartridges to be played on the Colecovision console, allowing owners the freedom to purchase from the extensive range of Atari compatible cartridges. It also means that existing Atari owners can buy the CBS Colecovision games system without discarding their software library. Silica Shop offer part exchange facilities if you wish to upgrade.

TURBO EXPANSION MODULE: The Turbo Driver Expansion Module allows you to actually drive the vehicle that appears on your T.V. screen. The module consists of a steering wheel, dashboard and accelerator pedal. One hand controller is mounted on the dashboard to provide a gear change unit. The module comes complete with a Turbo Driver cartridge, the first of several cartridges to make use of the module, which provides all the action of sitting in the driving seat. This facility is unique to CBS Colecovision.

HOME COMPUTER EXPANSION MODULE: The Home Computer Module scheduled for late 1983, allows conversion of the games unit into a sophisticated Home Computer. This flexibility of design is an important feature of the CBS Colecovision System.

COLECOVISION - £127.82 + VAT = £147

£147

VECTREX



THE SYSTEM: Vectrex is a totally unique Home Arcade System, which has been exclusively designed and engineered to duplicate real arcade game play. Complete with its own monitor display, Vectrex won't cause any arguments over the use of the family's television because it has its own built in screen.

THE SCREEN: Vectrex does not use ordinary display techniques, instead it uses vector scanning to control the images on the screen. With this scanning method, the gun only updates the area of the screen that has changed, whereas a normal T.V. re-transmits the ENTIRE screen 50 times a minute. It is this that gives Vectrex its speed, and means that very little computer power is required for screen control, and the results provide very fast responding and clear images. These 'Vector Graphics' are used in several arcade games such as Asteroids and Battlezone, to give you incredibly high resolution and quality. Vectrex brings all of this from the arcade right into your living room. The Vectrex screen is capable of displaying 80 columns by 40 lines, which is significant to the extensive developments planned for the system.

EXCITING SOUNDS AND ELECTRONICS: Vectrex has an advanced microprocessor with more speed and power and exciting effects than many home video games systems.

REAL ARCADE CONTROLS: Vectrex has a unique control panel, similar to those used in many real arcade games, with 4 concave action buttons and a full 360° self centering joystick. This control panel has a 4 foot detachable cord for maximum player freedom.

REAL ARCADE GRAPHICS: Vectrex has its own 9 inch vertical screen and unlike a conventional T.V. screen, uses advanced display technology to achieve brilliant, high resolution imagery and superb game play never before possible. The Vectrex display provides special effects too, such as 3-D rotation and zooming in and out, which a regular T.V. cannot match. Using a black and white monitor, each Vectrex game comes supplied with its own coloured plastic screen overlay to add to the excitement of game play. The range of Vectrex cartridges (£21.95 each), gives a good selection of arcade games such as Berzerk, Scramble, Rip-Off and Bomber Attack. Vectrex comes complete with a fast paced 'Minestorm' game built into memory.

VECTREX: Vectrex has an advanced state-of-the-art microprocessor with more speed than other T.V. games

VECTREX - £129.57 + VAT = £149.00

£149

WHO ARE SILICA SHOP?

Silica Shop are one of the leading specialist suppliers of Video Games & Personal Computers. We consider that our service, to those who already own or to those who are interested in any products in our range, cannot be matched by any other supplier. Just look at what we have to offer:

- * **SHOP DEMONSTRATION FACILITIES** - we provide full demonstration facilities at our shop in Sidcup, so that you can get hands on experience of our range.
- * **SHOP OPENING HOURS** - we are open from Monday to Saturday 9 am - 5.30 pm, but close at 1 pm on Thursday's and 8 am on Friday's.
- * **MAIL ORDER** - we are a specialist mail order company and are able to supply goods direct to your door at no extra cost.
- * **FREE FIRST CLASS DELIVERY** - all orders are sent Post and Packing FREE, most of them being despatched by FIRST CLASS POST within 24 hours of an order being placed. If you require overnight delivery, this can be arranged at a charge of £3 for items under £50, or alternatively £5 for items over £50.
- * **MONEY BACK UNDERTAKING** - if you are totally dissatisfied with your purchase, you may return it to us (in good condition) within 18 days for a full refund, no questions asked.
- * **PART EXCHANGE** - we will offer you up to one third of our current selling price in part exchange on your old Mattel Intellivision or Atari console (and related cartridges), if you decide to buy a new video game or personal computer from us.
- * **SECONDHAND GOODS** - we sell secondhand Mattel & Atari consoles/cartridges (with a full 1 year guarantee), at two thirds of our normal retail price.
- * **COMPETITIVE PRICES** - both our prices and services are very competitive. We are never knowingly undercut and will normally match any bona fide price quoted by our competitors, providing they actually have the goods in stock. We will also send the order to you post and packing free!
- * **HELPFUL ADVICE** - our specialist staff are always available to give you advice on the suitability of various consoles or T.V. games.
- * **SERVICE/REPAIRS** - are available on all machines in our range, often utilising our in house service facilities. We will support your machine long after you buy it, even if you did not originally purchase it from Silica Shop. All repairs during the manufacturers 12 month guarantee, including Atari Personal Computers.
- * **2 YEAR GUARANTEE** - we offer a 2 year extension on some manufacturers 12 month guarantee, including Atari Personal Computers.
- * **VIDEO GAMES AND COMPUTER CLUBS** - we offer a full information service on all video games and computers in our range. Advanced information on many new developments is often included, so you are always kept informed. We now issue regular newsletters on software releases so make sure that you join our club.
- * **OVERSEAS ORDERS** - we regularly send goods overseas and use various dispatch services. Please let us know your requirements and we will give you a quotation.
- * **PAYMENT** - we accept Access/Businesscard/Visa/American Express/Diners Club credit cards, as well as cash, cheques, postal orders, COD or Post Office Transacash.
- * **CREDIT FACILITIES** - we also offer credit facilities with varying payment over 12, 24 or 36 months. Please send for our FREE literature and a written quotation.



01-309 1111

SILICA SHOP

**SILICA SHOP LIMITED, Dept ZET1 0883,
1-4 The Mews, Hatherley Road, Sidcup, Kent, DA14 4DX
Telephone: 01-309 1111 or 01-301 1111**

VIDEO GAMES

ACCESS Atari
Aerial Splitter
Joysticks
Keypads
Main Adaptor
Paddles

ACCESS 3rd P
Extra Lead
Joysticks
Le Stick
Puzzlemaster
Quick Shot
Redball
Starfighter
Straight Stick
Trackball
Triga Command
Vic Command
Wico
Zircon

ACCESS Misc
Video Storage
Units

ACTIVISION
Barnstorming
Boxing
Bridg
Chopper Cmd
Dolphin
Oragrar
Enduro
Fishing Drby
Freeway
Grand Prix
Ice Hockey
Kaboom
Keystn Capers
Laser Blast
Megamania
Onk
Pitfall
Pique Attack
River Raid
Robotank
Seaquest
Skiing
Sky Jinks
Soldier Fighter
Stampede
Starstrmer
Tennis

APOLLO
Lost Luggage
Racquetball
Shark Attack
Street Shoot
Space Cavern
Space Chase



ATARI

ATARI VCS (2600) - THE NO 1 BRAND LEADER IN THE U.K.

ATARI: The Atari Video Computer System known as the Atari VCS or the 2600 has now become the T.V. game brand leader. In the U.K. there are over 700,000 owners of the VCS with access to a range of over 200 different plug in cartridges, each having a multitude of different variations and difficulty levels. Every system comes complete with the main console, two individual joystick controllers, a pair of paddle controllers, aerial splitter, mains adaptor and a 27 game Combat cartridge. It gives you bright crisp graphics, realistic sound effects and even specially designed circuits for the protection of your Television Set.

SECONDHAND GAMES: We currently have several secondhand Atari VCS units in stock which we are selling for only £49 (inc VAT). This price includes the Console, with Combat Cartridge and all the accessories, as well as a 12 month guarantee. **£49**
We also have stocks of several secondhand cartridges many at half price (all with 12 months guarantee). We will normally buy back secondhand units and cartridges at one third of our standard price.

EXTENSIVE CARTRIDGE RANGE: The Atari VCS is so popular that in addition to Atari's own cartridges, there are over 150 compatible cartridges, produced by at least a dozen different third party manufacturers. Silica Shop has one of the largest cartridge selections available in the U.K. Our range of over 200 titles (printed either side of this column), includes items in stock now, as well as many of the new releases for later in 1983.

SILICA ATARI CLUB: Silica Shop has over 20,000 Atari VCS club members registered on our computer. As a specialist company we are able to obtain advance information about new developments and send detailed catalogues to all of our club members, enabling them to evaluate new products before they buy. This is a totally FREE service, to receive your copies complete the coupon below.

SERVICE CENTRE: Atari International (UK) Inc has recently appointed Silica Shop as an authorised Atari Service Centre. This means that we can now service your Atari VCS or 400/800 (under guarantee if applicable), whether or not you purchased it from us.

VCS COMPUTER KEYBOARD: A keyboard will soon be launched to convert the VCS into a fully programmable home computer. For further details, join our club by completing the coupon below. We will then let you know when further information is available.

STARPATH SUPERCHARGER: The supercharger plugs into the cartridge socket of your VCS and expands its RAM almost 50 fold, from 128 to 6,272 bytes. This increased memory adds vivid high resolution graphics capabilities and significantly lengthens the game playing time. Supercharger has a range of multi-load games (at £19.45 each), these offer the facility to play a game in several distinct parts (great for adventures), the next section being loaded when you have completed the previous one, thus enhancing the game play. For further information please complete the coupon below. **£79**

ATARI VCS CONSOLE- With Combat Cart & Accessories £68.70+VAT = £79.00

ATARI/Conto
Super Bkout
Surround
Swordquest E
Swordquest F
Tennis (1p/2p)
Vanguard
Volleyball (r/s)
Warlords
Yars Revenge

BOMB
Assault
Great Escape
Splendour
Wall Defender
Z-Tack

CBS (Coles)
Blue Print
Carnival
Donkey Kong
Gorf
Mousetrap
Smurf
Solar Fox
Turbo
Venture
Wizard of War
Zaxxon

IMAGIC
Atlantis
Cosmic Ark
Demon Attack
Dem. Attack II
Dragonfire
Fire Fighter
No Escape
Riddle of Spz
Scuba
Sterioram
Star Voyager
Trick Shot
Zone

M.NETWORK
Aldo of Tron
Air Raiders
Burger Time
Come Revenge
Frog & Fish
Intnl Soccer
Lock 'n' Chase
Space Attack
Tron Dddy Dcd
Winter Olymp

PARKER
Action Force
Amidar

PARKER/Con
Emp Strls Bk
Frogger
Incredible Hulk
James Bond 007
Jedi Arena
Lord of Rings
Popeye
Q-Bert
Reactor
Rtn of Jedi 1
Rtn of Jedi 2

SPECTRIVISION
Chall of Nexar
China Syndrome
Cross Force
Gangster Alley
Galactic Tactic
Mangle
Master Builder
Planet Patrol
Tape Worm

SUPERCHARGER
Communist Mut
Galactic Tactic
Mangle
Master Builder
Planet Patrol
Tape Worm

TELESY
Chall of Nexar
China Syndrome
Cross Force
Gangster Alley
Galactic Tactic
Mangle
Master Builder
Planet Patrol
Tape Worm

TIGREVISION
Jawbreaker
King Kong
Marauder
Miner 2049er
Polaris
Phaser Patrol
Threshold
Thrasher

ZIMAG
Cosmic Corridor
Dishester
Implosion & Agg
I want my Mom
Pizza Chef
Quest for Gold
Tally Ho
Tanks no Tanks

ACCESSORIES

We stock a wide range of accessories for the Atari VCS and 400/800 personal computers. The same accessories can be used on the Commodore VIC range of computers. The Wico range can also be used with the Texas Instruments computers on purchasing a special adaptor. To give you an idea of the range available, just take a look at the following list:



LE STICK: A mercury filled joystick specially made for one handed operation, with thumb fire button.

WICO RED-BALL: An arcade type joystick with a red ball handle, it features 2 fire button locations, one at the base and one on the stick. It comes supplied with 4 grip pads for easier table top use.

WICO STRAIGHT - STICK: The main feature of this joystick is its arcade style, bat handle grip. It also has 2 fire buttons. Four grip pads included for table top use.

WICO TRACKBALL: A true arcade style trackball for use with your Atari or Commodore VIC. This product is designed to give arcade control in your living room.

12" EXTENSION LEAD: A 12" extension for Atari and Atari compatible joysticks for greater player freedom.



Wico
Straight
Stick
with
Stick
Fire
Button

MATTEL INTELLIVISION



MATTEL INTELLIVISION: The Mattel games unit is a most versatile T.V. game which offers 3-D graphics quality for only £98. Each cartridge comes with 2 overlays which fit over the unique hand controller giving easy directions for game play. Using the handset's control disc, objects

can be moved accurately in 16 directions giving a realistic simulation of lifelike movement.

VOICE SYNTHESIS: The Intellivoice unit, price £49, is used with special cartridges where high quality synthesised male and female voices feature as part of the game play.

NEW MATTEL CARTRIDGE RELEASES: Why not complete the coupon below and join the Silica Mattel Owners Club and receive our FREE news bulletins and 16 page catalogues detailing new Mattel releases. There will soon be over ninety cartridges available for the Mattel, and a small selection from these is listed below:

MATTEL: Arctic Squares, Burger Time, Buzz Bombers, Chess, Cloudy Mountain, Loco Motion, Mission X, Mystic Castle, Sharp Shot, Solar Sailor, Space Shuttle, Vectron, Winter Olympics.

ACTIVISION: Happy Trails, Pitfall, Stampede.

CBS: Blue Print, Carnival, Donkey Kong, Gorf, Mousetrap, Smurf, Solar Fox, Turbo, Venture, Wizard of War, Zaxxon.

IMAGIC: Bezer, Dracula, Ice Trek, Nova Blast, Satecracker, Swords & Serpents, Tropical Trouble, White Water.

PARKER: James Bond 007, Lord of the Rings, Popeye, Q-Bert, Spiderman, Star Wars, Super Cobra, Tutankham.

COMPUTER KEYBOARD: In July/August 1983, Mattel will be launching their new £89, 49-key computer keyboard attachment called "Lucky" which is fully programmable and has microsoft basic built in. It will transform your Master Component into a home computer. The adaptor also accepts a 6 note polyphonic music synthesiser and full size 49-key piano keyboard that will make learning music as easy as playing games. **£98**

MATTEL CONSOLE £85.22 + VAT = £98.00

VIDEO GAME CLUB

In a fast moving market like video games, it is difficult to keep up to date with all the developments that take place. With new programmes and accessories being introduced at a fast rate by several different manufacturers, it is impossible to get all the information you require from one manufacturer alone. It is for this reason, that we have set up owners clubs for the more popular video games and home computers, to keep you fully up to date with what is going on with your particular machine. As far as we know, Silica Shop are the only company to offer such clubs, but that is not surprising since we are the specialists. We currently have FREE clubs for the Atari VCS, Atari 400/800 home computers, and Mattel Intellivision. Soon we will have clubs for Colecovision, Aquarius and Vectrex. So if you own one of these machines, fill in the coupon opposite, and we will enrol you FREE OF CHARGE in the club relevant to your computer or video game.

FREE LITERATURE

FREE LITERATURE - Please send me your FREE LITERATURE and catalogues on the following items:

OWNERS CLUB - I already own the following products, please enrol me in your FREE club:

Mr/Mrs/Miss: Initials: Surname:

Address:

Postcode: ZET1 0883


FREE LITERATURE

01-309 1111

SILICA SHOP

SILICA SHOP LIMITED, Dept ZET1 0883,
1-4 The Mews, Hatherley Road, Sidcup, Kent, DA14 4DX
Telephone: 01-309 1111 or 01-301 1111

EDUCATIONAL ELECTRONIC KITS

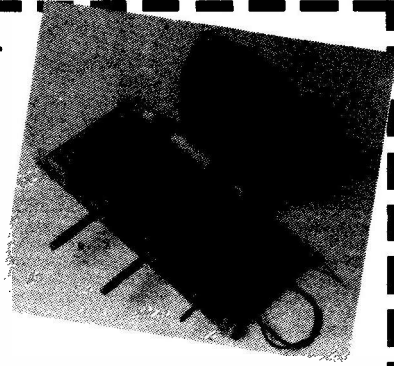

RADIO KIT

This AM radio is supplied with building instructions plus comprehensive electronic theory, exercises and test procedure. A complete learning package, requiring only a 9V battery.

The large fibreglass printed circuit board has been designed in 3 sections — a TRF radio, a bass treble control and an amplifier push-pull output circuit. Each section can be built and tested as a separate project.

This comprehensive radio circuit shows an application of tuned circuits, I.C.'s, field effect and bipolar transistors, common emitter and collector configurations, stabilizer circuits, feedback circuits, complementary output stages, etc.

The radio project kit should give entertainment and interest to the novice, yet provide valuable learning material for the electrical student. Particularly relevant to current T.E.C. electronic courses.

The price is only **£16.70** inc. VAT + £1.50 p&p. (Allow 28 days delivery).

Educational and quantity enquiries welcome.

Send cheque or postal order to:-

HAZZLEWOOD ELECTRONICS LTD.,
Sales Department,
149 Main Street,
Grenoside,
Sheffield, S30 3PN.
Tel: 0742 463585


Send an S.A.E. to receive a list of our current electronic project kits.

For Hi-Fi & Electronics Enthusiasts! Concept Electronics Ltd.

51 Tollington Road, London N7 6PB

We are the specialist of electronic kits and rack mounting cabinets. A catalogue with complete range of products including pre-amp modules, power amp modules, pre and power amplifier modules, complete kits of amplifiers, equalizers, reverbation amplifiers (with cases), alarm clocks, appliance timers, CB amplifiers, test equipment, control modules, music generator, battery fluorescent light and high quality rack mounting cabinets etc. with illustrative pictures now available at the cost of 35p + 25p p&p.

Professional rack mounting cabinet

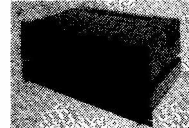

Panel Size W H (inch)	Rear Box W H D	Inc VAT £
19x5	17x4.5x10	23.54
19x4	17.3.5x10	21.24
19x3.5	17x3x10	20.09
19x2.5	17x2x10	18.94
19x6	17x5.5x12	24.69
19x5	17x4.5x12	23.54
18x4	17x3.5x12	21.24
19x3.5	17x3x12	20.09
17x3.5	15.5x3x9	17.79
17x2.5	15.5x2x9	16.64
17x4	15.5x3.5x12	21.24
17x3	15.5x2.5x12	20.09

● Suitable for high quality amplifiers and many other purposes ● Top, bottom and rear cover removable for access ● Separate front mounting plate ● Front panel is made of black anodised aluminium, the rear box is manufactured from steel painted in black ● With ventilation slits and plastic feet ● Heavy gauge front panel is of brushed aluminium finish

The above sizes are also available in black anodised aluminium. Front panel & rear box are both wholly made of black anodised aluminium sheets at only £4.00 extra per item.

Second Generation Class A Amplifiers

Mail order only



TA-1020A DC CLASS A PROFESSIONAL PRE-AMPLIFIER
TA-1000A 100W DYNAMIC BIAS CLASS A POWER AMPLIFIER
TY-25A SUPER SPEAKER PROTECTOR
TA-1020Ax1 £25.50 (kit)
TA-1000Ax2 £55.00 (kit)
TY-25Ax1 £6.75 (kit)

TA-1000Ax2 £55.00 (kit)
TY-25Ax1 £6.75 (kit)

Total £87.25

Total £61.75

Special offer kit £69.99 + £2.50 p/p
Ass £66.99 + £2.50 p/p
Note: discount voucher not valid

Special offer kit £49.99 + £2.00 p/p
Ass £60.99 + £2.00 p/p
Price inc. VAT

E.T.I. KITS

Full Kits inc. PCBs, hardware, electronics, cases (unless stated). Less batteries.

ZX ADC Jan 83	£34.98
BALANCED INPUT PREAMP May 83 less case	£10.99
COMPRESSOR/LIMITER May 83 less case	£19.43
MAX/MIN THERMOMETER Apr 83	£43.78
LOGIC PROBE Mar 83 less case	£8.95
ALARM MODULE Mar 83	£24.57
DUAL LOGIC PROBE Sept 82	£14.99
AUTO VOLUME CONTROL Sept 82 £4.28 less case	£19.69
INSULATION TESTER May 82	£17.57
HIGH QUALITY PHONE AMPLIFIER Feb 82	£19.75
MOVING COIL STAGE less case	£19.69
MOVING MAGNET STAGE less case	£19.69
PEST CONTROL Feb 82	£7.45
GUITAR TUNER Jan 82	£21.87
COMPONENT TESTER Dec 81	£8.78
CAR ALARM Nov 81	£19.77

SOUND BENDER Oct 81	£22.84
WATCHDOG SECURITY ALARM Aug 81	£47.98
RECHARGEABLE BATTERY extra	£19.98
HANDCLAP SYNTHESIZER Aug 81	£32.98
WASH PHASE June 81. Less pedal	£14.78
LED JEWELLERY June 81. Cross	£2.98
Star £9.91 Spiral £7.98	
GUITAR NOTE EXPANDER April 81	£17.99
DRUM MACHINE April 81	£85.97
ENGINEERS STETHOSCOPE Mar 81	£20.98
SOUND PRESSURE LEVEL METER Feb 81	£43.98
INFRA RED ALARM Feb 81	£59.99
4 INPUT MIXER Dec 80	£21.74
MUSICAL DOORBELL Dec 80	£12.77
METRONOME Nov 80	£8.58
ULTRASONIC BURGLAR ALARM Aug 80	£28.50
CAPACITANCE METER Aug 80	£22.28
CMOS LOGIC TESTER Aug 80	£11.98
CLICK ELEMINATOR April 79 £87.70 Or less case	£49.98

MAGENTA ELECTRONICS LTD
EG31, 135 Hunter St., Burton-on-Trent
Staffs., DE14 2ST. Mail Order Only
Add 45p p&p to all orders. Prices include VAT. Access & Visa phone/post

Official school orders welcome.
OVERSEAS: Payment must be in sterling.
IRISH REPUBLIC + BFPO — UK PRICES.
EUROPE: UK PRICES + 10%.
ELSEWHERE: WRITE FOR QUOTE.

HORIZON ELECTRONICS

(Midlands)
Dept H/E Charlotte St. Rugby Tel: 7B13B
Prime quality. TERRIFIC PRICES. Mail order only

REGULATORS (5/12/15V) 100mA +ve 28p 500mA +ve 45p 723 var 28p	TRIACS (plastic) 4 amp 400v 50p 8 amp 400v 75p 25 amp 400v 168p	LINEAR IC's 747 50p 748 50p ICM 7555 130p ICM 5558 130p LM 311 40p LM 312 40p LM 313A 24p LM 314 27p LM 318 60p LM 330 60p LM 339 60p NE 557 28p TDA 2020 285p TDA 2022 185p
ZENERS (3.3 to 30V) 500mW 8p 1.3 watt 12p IN 5401 50p 5402 46p 5404/6 60p 5405 12p 5408 14p	TOGGLE SWITCHES Mn DP ST 57p S. Mn DP ST 48p S. Mn DP DT 62p	SOLDERING IRONS Antex C 15w 445p Antex C 25w 450p K25 25w 470p All bits 60p
BRIDGES 1 amp 50v 20p 2 amp 100v 30p 2 amp 200v 35p 2 amp 400v 38p 6 amp 200v 45p 6 amp 400v 75p 10 amp 50v 170p 10 amp 100v 180p 10 amp 200v 195p	TRANSISTORS BC107B 8p BC107C 8p BC107D 8p BC108 8p BC108B 10p BC140 25p BC142 25p BC171 15p BC182 7p BC212 7p BC237 8p BD139 32p BD139 32p BD148 32p	IC (Mini) connectors 16 way plug 88p 16 way socket 120p Cover 98p 20 way plug 120p 20 way socket 150p Cover 98p

ABOVE: Just a few examples Send S.A.E./List
ADD: 65p p&p to all orders under £5.00
VAT: add 15% VAT to total order value

THE "INSTANT" PC BOARD



E-Z CIRCUIT... quick, easy & reliable... the best way to make one or two-of-a-kind PC boards! That's what "Doc" Savage (hobby editor, Radio Electronics magazine) says about E-Z CIRCUIT.

Why all the excitement?

Simple, E-Z CIRCUIT's exclusive 1 oz., pressure-sensitive copper tapes & patterns apply directly to the PC board, creating an actual current carrying circuit. Simply apply E-Z CIRCUIT's Copper Mounting Configurations to the board, solder your components into place, and you have a professional, production quality PC board... instantly... without artwork, photography, screening or etching.

There's no need to worry about mistakes either. With E-Z CIRCUIT's special two-phase adhesive, you can make corrections, modifications or improvements quickly & easily... without damaging the performance or appearance of your PC board.

For building, prototyping or repairing PC boards instantly, E-Z CIRCUIT truly is the quick, easy, reliable way!

Prove it to yourself, send for your FREE copy of the E-Z CIRCUIT Copper Products Printed Circuit Technical Manual & Catalog EZ-3001. See why "Doc" Savage & thousands of other users recommend E-Z CIRCUIT for instant PC boards.

Send for your FREE E-Z CIRCUIT Printed Circuit Copper Products Technical Manual & Catalog EZ 3001

Engineering & Electronic Design Services Ltd.

Unit 7, Enterprise Centre, Childers Road, Limerick.

IRELAND

Tel: (061) 49366

ETI PCB SERVICE

Up until now PCBs were always the hardest component to obtain for a project. Of course you could make your own, but why bother anymore?

Now you can buy your boards straight from the designers — us! As of this issue all (non-copyright) PCBs will be available automatically from the ETI PCB Service. Each board is produced from the same master used to build our prototypes, so you can be sure it's accurate and will be finished to the high standard you would expect from ETI.

In addition to the PCBs for this month's projects, we are making available some of the more popular designs from our recent past. See the list below for details. Please note that **NO OTHER BOARDS ARE AVAILABLE**. If it's not listed, we don't have it!



ALWAYS QUOTE THE PCB CODE WHEN ORDERING PLEASE

- | | | |
|---|--|---|
| <p>1979</p> <ul style="list-style-type: none"> <input type="checkbox"/> E/794-1 Guitar Effects Unit 2.64 <input type="checkbox"/> E/794-2 Click Eliminator 6.64 <input type="checkbox"/> E/796-1 Accented Beat Metronome 3.60 <p>1980</p> <ul style="list-style-type: none"> <input type="checkbox"/> E/803-1 Signal Tracer 2.27 <input type="checkbox"/> E/808-1 CMOS Logic Tester 2.64 <input type="checkbox"/> E/808-3 Ultrasound Burglar Alarm . 2.87 <input type="checkbox"/> E/8010-1 Cassette Interface 2.93 <input type="checkbox"/> E/8010-2 Fuzz/Sustain Box 3.27 <input type="checkbox"/> E/8011-5 RIAA Preamp 1.93 <input type="checkbox"/> E/8011-6 Audio Test Oscillator . . . 3.13 <input type="checkbox"/> E/8012-1 Musical Doorbell 2.80 <input type="checkbox"/> E/8012-3 Four Input Mixer 2.64 <p>1981</p> <ul style="list-style-type: none"> <input type="checkbox"/> E/811-1 LED Tacho 4.13 <input type="checkbox"/> E/811-2 Multi-Option Siren 3.20 <input type="checkbox"/> E/813-1 Universal Timer 3.31 <input type="checkbox"/> E/812-1 IR Alarm (4 boards) 6.64 <input type="checkbox"/> E/812-5 Pulse Generator 3.57 <input type="checkbox"/> E/813-1 Engineer's Stethoscope . . . 2.66 <input type="checkbox"/> E/814-2 Drum Machine (2 boards) . 5.60 <input type="checkbox"/> E/814-4 Guitar Note Expander . . . 3.20 <input type="checkbox"/> E/816-8 Waa-Phase 1.53 <input type="checkbox"/> E/816-9 Alien Attack 3.48 <input type="checkbox"/> E/817-1 System AS- Input (MM or MC) 2.66 <input type="checkbox"/> E/817-2 System A - Preamp 5.17 <input type="checkbox"/> E/817-3 Smart Battery Charger . . . 1.97 <input type="checkbox"/> E/818-3 Hand Clap Synth 3.97 <input type="checkbox"/> E/818-5 Watchdog Home Security (2 boards) 5.31 <input type="checkbox"/> E/819-1 Mains Audio Link (3 boards) 7.35 | <ul style="list-style-type: none"> <input type="checkbox"/> E/819-4 Laboratory PSU 4.53 <input type="checkbox"/> E/8110-1 Enlarger Timer 3.40 <input type="checkbox"/> E/8110-2 Sound Bender 2.65 <input type="checkbox"/> E/8111-1 Voice Over Unit 3.97 <input type="checkbox"/> E/8111-2 Car Alarm 2.81 <input type="checkbox"/> E/8111-3 Phone Bell Shifter 2.96 <input type="checkbox"/> E/8112-1 Alcohometer (2 boards) . 5.21 <input type="checkbox"/> E/8112-3 Bodywork Checker 1.75 <input type="checkbox"/> E/8112-4 Component Tester 1.49 <p>1982</p> <ul style="list-style-type: none"> <input type="checkbox"/> E/821-1 Parking Timer 2.20 <input type="checkbox"/> E/821-3 Guitar Tuner (2 boards) . . 5.55 <input type="checkbox"/> E/822-1 Ripple Monitor 1.92 <input type="checkbox"/> E/822-2 Allez Cat Pest Repeller . . 1.68 <input type="checkbox"/> E/822-5 Moving Magnet Stage 3.49 <input type="checkbox"/> E/822-6 Moving Coil Stage 3.49 <input type="checkbox"/> E/823-4 Capacitance Meter (2 Bd) 10.14 <input type="checkbox"/> E/824-5 Voltage Monitor 1.86 <input type="checkbox"/> E/825-1 DV Meg 2.72 <input type="checkbox"/> E/825-2 Analogue PWM 3.06 <input type="checkbox"/> E/825-3 Slot Car Controller 4.51 <input type="checkbox"/> E/826-1 Ion Generator (3 Bds) . . . 8.00 <input type="checkbox"/> E/826-4 MOSFET Amp Module 6.78 <input type="checkbox"/> E/826-5 Logic Lock 3.06 <input type="checkbox"/> E/826-6 Digital PWM 3.34 <input type="checkbox"/> E/826-7 Optical Sensor 1.74 <input type="checkbox"/> E/826-9 Oscilloscope (4 Boards) . . 11.60 <input type="checkbox"/> E/827-7 TV Bargraph Main 4.56 <input type="checkbox"/> E/827-3 TV Bargraph Channel 2.28 <input type="checkbox"/> E/827-4 Hotwire 2.63 <input type="checkbox"/> E/827-5 Bridging Adaptor 2.38 <input type="checkbox"/> E/828-1 Playmate (3 Boards) 7.20 <input type="checkbox"/> E/828-4 Kitchen Scales 1.84 <input type="checkbox"/> E/828-5 Sound Track 4.25 <input type="checkbox"/> E/829-1 Auto Volume Control 1.84 | <ul style="list-style-type: none"> <input type="checkbox"/> E/829-2 Dual Logic Probe 1.93 <input type="checkbox"/> E/8210-1 Message Panel (2 Boards) 10.70 <input type="checkbox"/> E/8211-4 Pulse Generator 5.29 <input type="checkbox"/> E/8212-1 ELCB 2.41 <input type="checkbox"/> E/8212-2 Servo Interface (2 Boards) 5.87 <input type="checkbox"/> E/8212-4 Spectracolumn 4.82 <p>1983</p> <ul style="list-style-type: none"> <input type="checkbox"/> E/831-1 Fuel Gauge 3.00 <input type="checkbox"/> E/831-2 ZX ADC 2.25 <input type="checkbox"/> E/831-3 Programmable PSU 3.00 <input type="checkbox"/> E/833-1 Sound Board 11.16 <input type="checkbox"/> E/833-2 Alarm Module 3.15 <input type="checkbox"/> E/833-3 ZX81 User Graphics 0.93 <input type="checkbox"/> E/833-4 Logic Probe 2.17 <input type="checkbox"/> E/834-1 Real Time Clock 7.60 <input type="checkbox"/> E/834-2 Thermometer (2 Boards) . . 8.47 <input type="checkbox"/> E/834-4 Stage Lighting - Main . . . 11.94 <input type="checkbox"/> E/834-5 Stage Lighting - Display . . 3.00 <input type="checkbox"/> E/835-1 Compressor/Limiter 5.38 <input type="checkbox"/> E/835-2 Single PSU 2.75 <input type="checkbox"/> E/835-3 Dual PSU 3.49 <input type="checkbox"/> E/835-4 60 W NDFL Amp 4.70 <input type="checkbox"/> E/835-5 Balanced Input Preamp . . . 2.81 <input type="checkbox"/> E/835-6 Stage Lighting - Autofade 5.38 <input type="checkbox"/> E/835-7 Stage Lighting - Triac Board 4.12 <input type="checkbox"/> E/836-1 to 3 PseudoROM (3 Bds) . 3.15 <input type="checkbox"/> E/836-4 Immersible Heater 2.00 <input type="checkbox"/> E/836-5 Atom Keypad 4.50 <input type="checkbox"/> E/837-1 Flash Sequencer 2.32 <input type="checkbox"/> E/837-2 Trigger Unit Main Board . . 2.32 <input type="checkbox"/> E/837-3 Trigger Unit Transmitter . . 1.44 <input type="checkbox"/> E/837-4 Switched Mode PSU 14.00 <input type="checkbox"/> E/838-1 Graphic Equaliser 7.91 <input type="checkbox"/> E/838-2 Servo Fail-Safe (four off) . 2.55 <input type="checkbox"/> E/838-3 Universal EPROM prog. . . . 8.38 |
|---|--|---|

STRICTLY CASH WITH ORDER — OFFICIAL ORDERS ARE NOT ACCEPTED

Prices Quoted are valid until 1st November 1983

How to order: indicate the boards required by ticking the boxes and send this page, together with your payment, to: ETI PCB Service, Argus Specialist Publications Ltd, 145 Charing Cross Road, London WC2H 0EE. Make cheques payable to ETI PCB Service. Payment in sterling only please. Prices subject to change without notice.

Total for boards £
 Add 45p p & p 0.45
 Total enclosed £

**PLEASE ALLOW
28 DAYS FOR
DELIVERY**

Signed
 Name
 Address

What The PCB Code Means

The first two numerals indicate the year in which the project was published; the third the year. The numeral after the dash uniquely identifies the board within those boards published that month.



Bigger and Better

the colourful Wilmslow Audio brochure
— the definitive loudspeaker catalogue!

Everything for the speaker constructor — kits, drive units, components for HiFi and PA.

50 DIY HiFi speaker designs including the exciting new dB Total Concept speaker kits, the Kef Constructor range, Wharfedale Speakercraft, etc.

Flatpack cabinet kits for Kef, Wharfedale and many others.

- ★ Lowest prices — Largest stocks ★
- ★ Expert staff — Sound advice ★

- ★ Choose your DIY HiFi Speakers in the comfort of our ★
two listening lounges
(Customer operated demonstration facilities)
- ★ Ample parking ★

Send £1.50 for catalogue

(cheque, M.O. or stamps — or phone with your credit card number)

- ★ Access — Visa — American Express accepted ★
also HiFi Markets Budget Card.



0625 529599

35/39 Church Street, Wilmslow, Cheshire SK9 1AS



Lightning service on telephoned credit card orders!



TALK TO THE WHOLE WORLD

Study now for the RADIO AMATEUR'S EXAMINATION

We have had 40 years successful experience
in training men and women for the
G.P.O. Transmitting licence.



FREE R.A.E. brochure without obligation from:—

British National Radio & Electronics School
READING, BERKS. RG1 1BR

Name

Address

ET1/8/817

BLOCK CAPS PLEASE

MULTIMETERS

(UK C/P 65p)

RANGE DOUBLER 10A DC1

Special price.....£15.95

ETC 5000/5001 121 Ranges

50K/V Range Doubler 10A DC

.....£16.50

TMK 500 23 Ranges 30K/V 12A

DC Plus cont. buzzer.....£23.95

NH56R 20K/V 22 Range Pocket

.....£10.95

360TR 23 Range 100K/V. Large

scale 10A AC/DC plus Hfe.....£36.95

ATI 020 18 Range 20K/V. DeLuxe

plus Hfe Tester.....£17.50

ST303TR 21 Range 20K/V plus Hfe

Tester.....£16.95

SPEAKERS

(Hi-Fi, P.A., Disco, Bass Guitar)

8" 60W... £11.95

10" 50W... £12.95

12" 100W... £26.95

18" 100W... £39.95

**MOTOROLA PIEZO
TWEETERS IN STOCK
RETAIL • MAIL ORDER
EXPORT • INDUSTRIAL
EDUCATIONAL**

Order by Post
with cheques,
Access/Visa or
you can
telephone your
orders.

ALL PRICES
INCLUDE
VAT

FREE
CATALOGUE
SEND LARGE
SAE
(UK 20p)

MUSICRAFT 303 EDGWARE RD, LONDON W.2. TEL: 01-402 9729/2898

PARNDON ELECTRONICS LTD.

Dept. 23, 44 Paddock Mead, Harlow, Essex. CM18 7RR. Tel: 0279 32700

RESISTORS: ¼ Watt Carbon Film E24 range ± 5% tolerance
Bandoliered and colour coded. Full Range 1R0-10M.

£1.00 per hundred mixed (Min 10 per value) **£8.50** per thousand mixed (Min 50 per value)
Special stock pack 60 values. 10 of each **£5.50**

**1 AMP
VOLT REG**
+ve 5v, 12v,
15v, 24v — **£0.40**
—ve 5v, 12v
15v — **£0.43**

3½ Digit LCD Display: 1 colon, 3 decimal points
plus/minus sign and lo bat indicator.
Complete with low power 7106 A/D converter display driver.
Driver set **£8.95**
Display **£3.50** Driver **£6.50**

DIODES: IN4148 **£1.60** per hundred

**DIL
SOCKETS** 8 pin — **10p.** 14 pin — **11p.** 16p pin — **12p.** 18p pin — **19p.** 20p pin — **21p**
22 pin — **23p.** 24 pin — **25p.** 28 pin — **27p** 40 pin — **42p.**

Full List Available — Send SAE
ALL PRICES INCLUDE V.A.T. & POST & PACKING — NO EXTRAS
MIN ORDER — UK £1.00 OVERSEAS £5 CASH WITH ORDER PLEASE
Same Day Despatch

NEW! MODULAR AUTOMATIC TELEPHONE SYSTEM

£24.50
+ £1 p&p

Each ready built module is a complete exchange
providing up to ten extension lines

- ★ Simply connect 'phones and power supply
- ★ Only two wires to each telephone
- ★ Uses ordinary dial or push-button 'phones
- ★ Complete privacy for conversations
- ★ Range of several miles
- ★ Fully expandable system

Each module allows two 'phones to be used at one time,
two modules allows four, etc.

RECONDITIONED TELEPHONES

Push Button Trimphones **£15**

+ £1.80 p&p. 2 for **£28** +

£2.50

Push Button 746 **£9.75** +

£1.80. 2 for **£18** + **£2.50**

Recent Style Dial Phones

£4.75 + **£1.80.** 2 for **£9** +

£2.50. 5 for **£20** + **£5**

Seconds (in good working

order)

Class 1 **£3.50** + **£1.80.** 5 for

£15 + **£5**

Class 2 (discoloured) **£2.25** +

£1.80. 5 for **£9** + **£5**

TEMPERATURE GAUGE 0-120°C

Remote sensor on 38" capillary, panel mounting dial
55mm. dia. Only **£2.50**

16A 240V RANCO THERMOSTAT

Wide control range (low room temp. to over boiling point).
Sensor on 22" capillary. 2.30, including control knob

BUY ONE EACH OF ABOVE FOR £5.50

GEARED Synchronous motor, 8r.p.m. 240V A.C. 3 Watt
£2.

SOLENOID GAS VALVE. 240V A.C. 5 P.S.I. suitable for
non-corrosive fluids. **£2.20**

BULGIN 3 pin free plug & panel socket. 2A 240V
50p

DIAL-OUT WITH YOUR COMPUTER. PCB's convert
binary to dialing pulses and enable your computer to
dial-out (with suitable interface). Ex-equipment.
Tested. **£12** with explanatory notes.

Desk-top Ten Way Manual Ex-
change (key & lamp unit)
with instructions
£8 + **£1.80 P&P**

Send SAE for free leaflet on
telephone systems.



L.E.M. SERVICES
22 Emscote Road,
Warwick,
Warwickshire
Tel: 0926 490740

**ADD 50p P&P
ORDERS OVER
£7.50 POST FREE**
unless stated otherwise

ALL ITEMS — MONEY BACK IF NOT DELIGHTED



Visual Display Units
Burrhoughs MT686 VDUs
These versatile micro
controlled programmable
terminals have 3 RCA
1802 CPUs and 64K of
memory. 12" Green
screen (80 x 25) RS232.
106 key detached key-
board. Can also be used
as quality video monitor.
£149 + **£15 carr.** WHILE
STOCKS LAST.

CENTRONICS 306 LINE PRINTERS



professional fast
compact line-printer. 80
columns, 120 char/sec.
Parallel i/f. Quality at a
silly price. Vertical format
unit. To inc. operations
manual. **ONLY £149.00.**
Carriage (England)
£17.50. Tech manual
(230 pages) **£10.00.**



FLOPPY DISC DRIVES

Fantastic MEMOREX
550 8" discs mounted in
attractive case with
power supply and fan.
Shugart standard 50 way
interface. Space for
second drive. **£199** (carr.
£9.50).

MAWSON ASSOCIATES

124 Lennard Rd, Beckenham, Kent BR3 1QP

WE ALSO BUY COMPUTERS
AND COMPUTER PERIPHERALS

01-778 3600

Callers welcome by appointment
s/h items sold working but not g'teed

ELECTROMART

AVON


ANNLEY ELECTRO

190 Bedminster Down Road
Bedminster Down, Bristol
Tel: 0272 632622
Open: Mon-Sat 9am-6.30 pm Wed 9am-2pm

PROGRESSIVE RADIO

93 Dale Street. Tel 051 236 0982
47 Whitechapel, Tel 051 236 5489
Liverpool 2
THE ELECTRONICS SPECIALISTS
Open: Tues-Sat 9.30-5.30

WARWICKSHIRE

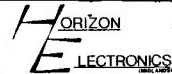

Charlotte St, Rugby. Tel: Rugby 78138
Open 5 Days 10-6 (closed Wed)
Wide range of components and R.S. stockists
1983 Mail Order Catalogue 75p

LANCASHIRE

ETESON ELECTRONICS

15B Lower Green,
E.E. Poulton-le-Fylde, Blackpool
Tel: (0253) 885107
Open: 9.30am-12.30, 1.30-5.30. Closed Wed & Sun.
Electronic Component Specialists.

NORTHAMPTONSHIRE

- * A new company selling electronic components.
- * Mail order and walk-round supermarket.
- * Vast stocks and very competitive prices.

EMOS

High March, Daventry, NN11 4NQ.
Telephone 03272 5523. Telex 311245.
(Off A45 opposite John O'Gaunt.)

WORCS/W. MIDLANDS

WAVEBANDS

103 Coventry St., Kidderminster
Components, computers, car radios,
C.B.'s, amateur radio
Spares & Repairs
Open: Mon-Sat 9-6,
TEL: 0562 2179

MERSEYSIDE

MYCA ELECTRONICS

2 VICTORIA PL, SEACOMBE FERRY,
WALLASEY, L44 6NR.
Tel: 051 638 8847
Open Mon-Sat 10am-5.30pm
Mail Order price list 50p refundable

S. WALES

STEVE'S ELECTRONIC SUPPLY CO. LTD.

45 Castle Arcade, Cardiff
TEL: 0222 41905
Open: Mon-Sat 9-5.30
For components to computers

YORKSHIRE



ACE MAILTRONIX LTD.
3A Commercial Street,
Batley. Tel: (0924) 441129

Open: Mon-Fri 9am-5.30pm. (Sat 1pm)
Retail and wholesale.

JUST OUT

OUR NEW CATALOGUE

Presented with a Professional Approach and Appeal to ALL who require Quality Electronic Components, Semiconductors and other Accessories ALL at realistic prices.

There are no wasted pages of useless information so often included in Catalogues published nowadays. Just solid facts i.e. price, description and individual features of what we have available. But remember, BI-PAK's policy has always been to sell quality components at competitive prices and THAT WE STILL DO.



We hold vast Stocks "in stock" for fast immediate delivery, all items in our Catalogue are available ex stock.

The Catalogue is designed for use with our 24 hours "ansaphone" service and the Visa/Access credit cards, which we accept over the telephone.

To receive your NEW 1983 BI-PAK Catalogue, send 75p PLUS 25p p&p to:-

BI-PAK

ET1/8



Access & VISA accepted

Ring 0920 3182 for immediate despatch

WHY WRITE TO LONDON

When you can walk to the Midlands largest selection of DIY.

Plugs, sockets, connectors, cable, flex, leads, boxes, Aerials, styli, components, elements, semi-conductors, meters.


In fact the lot!

Spares and repairs for all electronic, electrical and audio.

H. G. Electronics Co.

1350 Stratford Road, Hall Green,
Birmingham B28 9EH

Telephone: 021-777 2369

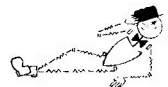

ALARMS



FREE BOOKLET

on

BURGLAR ALARMS

with

LOWEST U.K. DIY PUBLISHED PRICES

PHONE OR WRITE FOR YOUR COPY

051-523 8440

AD ELECTRONICS

217 WARBRECK MOOR
AINTREE, LIVERPOOL L9 0HU



Lineage:

35p per word (minimum 15 words)
Semi Display: (minimum 2 cms)
 £10.00 per single column centimetre
 Ring for information on series bookings/discounts
 All advertisements in this section must be prepaid.
 Advertisements are accepted subject to the terms and conditions printed on the advertisement rate card (available on request)



01-437 1002

EXT 282

Send your requirements to:
 Julie Bates,
 ASP Ltd.,
 145 Charing Cross Road,
 London WC2H 0EF

FOR SALE

CABINET FITTINGS

ADAM HALL SUPPLIES LTD.

Adam Hall (E.I. Supplies)
 Unit B, Carlton Court, Grainger Road,
 Southend-on-Sea

ELECTRONIC ORGAN KEY-BOARDS and other parts being cleared out as special offer. Elvins Electronic Musical Instruments, 40A Dalston Lane, London E8. 01-986 8455.

SHEETMETAL FOLDERS 18" x 18c Steel, 16G Aluminium bench or vice held. Hobby or Light industrial use. £38. 01-890-7838. Day/evening.

1000 16 PIN WIREWRAP SOCKETS, gold plated £3 for 10, £25 for 100. 75 ITT lever switches, gold contacts eg. 4 c/o + 4 c/o 3 way 60p, 2 c/o 1 way 40p. Miniature DP centre off 40p. Some TTL eg. 7400 8p, 7474 14p, 74121 20p. Phone: 0477 32754 evenings.

A LASER for £125. Complete in cabinet with power supply. Send 50p for details, plus information regarding other Lasers, Holograms available new and exhibit. D.H.S. Developments, 21 Grosvenor Road, Scarborough.

PERSONAL STEREO FM/AM radio + headphones. Superb tone. Fully guaranteed. Only £12.95. Taits Mail Order, 31 Lime Grove, Adlestone, Surrey.

300 WATT SLAVES £15 E/£11 ... Illustrated leaflet. S.A.E. KIA-8, Cunliffe Road, Ilkley. 120 Watt, case + sliders £10.85.

TEKTRONIX SCOPES £110, Teletypes £80. Free leaflet: James Sinclair, 82 Plumstead Common Rd., SE18. 01-316 1779.

MAPLIN 3800 SYNTH. Fully completed and tuned, plus internal speaker and manual. £250. Tel: Christchurch 478935 evenings.

FOUR OLIVETTI TE. 300 input/output terminals. Integral 8 hole paper tape punch and reader. 110 Baud Standard ASC11 serial input/output. 120 columns untested, unguaranteed. Buyer to collect, £40 each. Mr. A. J. Stichtman, Chesterfield College of Technology, Infirmary Road, Chesterfield (0246) 201011, extension 337.

PLANS 'N DESIGN

AMAZING ELECTRONICS PLANS. Lasers, super-powered cutting rifle, pistol, light show, ultrasonic force fields, pocket defence weaponry, giant tesla, satellite TV pyrotechnics, 150 more projects. Catalogue £1 (refundable) from Plancentre, Bromyard Road Industrial Estate, Ledbury HR8.

CONVERT any TV into large screen oscilloscope. External unit plugs into aerial socket of TV. Circuit & plans £3 or S.A.E details. J. Bobker, 29 Chadderton Drive, Unsworth, Bury, Lancs.

HARDWARE

COMPUTER SPARES

POWER SUPPLIES
 BBC MICROCOMPUTER PSU MOD D1597
 240V ac 30W. Outputs—5V dc 100 ma, + 5V dc 2.25A. Conform to BS415. **£10.00** + £2.00 p&p + VAT.
 RACAL MILGO EX EQUIP POWER MODULE MOD 001
 240V ac Input. Outputs—2 x +5V dc, 1 x -12V dc, 1 x +12V dc. **£25.00** + £2.95 p&p + VAT.

MAINS ADAPTORS
 INGERSOLL MOD XK2598
 Output 9V dc 500ma, 4 metres twin lead to 2.5mm jack. Conforms to BS415. **£3.00** + 75p p&p + VAT.
 (Other types available S.A.E. for list).
 VULCAN NL CAD CHARGER MOD V92
 Charges 8aa cells and 4aa cells. **£5.00** + 75p p&p + VAT.

IMP PRINTER KITS
 To enable building of complete printer (no main board components or top cover included). Kit consists of: Imp main drive, base plate, transformer, ribbon cable, capacitor, switch assembly, printer PCB (unpopulated) plus circuit diagrams and connection instructions. Free Nascom 1 PCB & 8 amp PSU PCB with each order received before end of August. **£55.00** + £5 p&p + VAT. Some discrete components available for printer PCB. S.A.E. for details.
 LONDEX TIMER STP-NR SUB MINY 110V ac 0-215 secs **£10.00** + £1.00 p&p + VAT.
 OMRON MIN PCB RELAY. LCIN-E 48V dc SPCD 50p + 25p p&p + VAT.
 4WAY POWER Plug—Consists 2.5mm or 3.5mm jacks. Plus 2.1mm x 2.5mm power-in plugs on 2 metre lead. **£1.25** + 25p + VAT.
 4WAY DIN SOCKET on 1.5 metre 4 core lead. **£1.00** + 25p + VAT.

Trade enquiries on all above welcome.

Dionics, 17 Hawkesworth Drive,
 Kenilworth, Warks.
 Tel. 0926 59658 Tx. 312440

VALVES

EX-GOVT VALVE and Semiconductor Equivalents Guide. Contains an up to date fully comprehensive cross referenced guide to British and American Service valves and semiconductors. £2.50 plus pp 30p. Valve List. Valves from 1925 to 1980. Many obsolete types. Modern TV, radio and transmitting valves. Send 60p (refundable on purchase). Or free with Ex-Govt., Valve Guide. We sell valves of all types. Please send SAE for your requirements. Dept. ETI Myers Electronic Devices. 12/14 Harper Street, Leeds LS2 7EA. Tel: (0532) 452045.

AERIALS

AERIAL BOOSTERS

NEXT TO THE SET FITTING.
B45H/G-UHF TV. Gain about 20dbs. Tunable over the complete UHF TV band. **Price £8.70.**
BII-VHF/FM RADO. Gain about 14dbs. When on the off position connects the aerial direct to the radio. **Price £7.70.**
 All boosters we make use a PP3/006p/6F22 type battery or 8v to 18v DC. P&P 30p per order.
Electronic Mailorder Ltd
 62 Bridge St., Ramsbottom,
 Lancs. BL0 9AG.
 Tel: (070682) 3036
 Access/Visa Cards Welcome, see leaflets

EXHIBITIONS

SUSSEX MOBILE RALLY. A day by the sea with the family for £1. Brighton Raceground. 17th July. 10.30 am - 5.00 pm. Free car parking. Good catering under cover.

COMPUTERS

CORTEX COMPUTER with RS232 working fast and powerful. £310. Phone Mr Hill, Midhurst 3632 after 7pm.

For All ETI Classifieds
 Tel: 01-437 1002
 ext 282

WIRES 'N CABLES

THE SCIENTIFIC WIRE COMPANY

811 Forest Road, London E17
 01-531-1568

ENAMELLED COPPER WIRE			
SWG	1lb	6oz	4oz
8-34	3.63	2.09	1.10
35-39	3.82	2.30	1.26
42-43	5.20	2.91	2.25
44-47	8.56	5.80	3.49
48	15.96	9.58	6.38
SILVER-PLATED COPPER WIRE			
14-30	9.09	5.20	2.93
TINNED COPPER WIRE			
14-30	3.97	2.41	1.39

Prices include P&P and VAT. Orders under £2 add 20p. Dealer inquiries welcome.

EQUIPMENT

ROB'S

Printed Circuit Boards
to your specification
from artwork through to
finished board.

**QUICK DELIVERY -
COMPETITIVE PRICES**

BROXTON ELECTRONICS LIMITED

35 Grosvenor Road,
Twickenham, Middlesex
TEL: 01-891 1923/1513 Telex: 295093

COPPER CLAD double sided fibreglass, 12" x 18". 10 sheets £6.50, - 5 sheets £4.50, - 20 sheets £10.50. Davron, 1 Industrial Unit, Parker Road, Chelmsford, Essex.

BURGLAR Alarm Equipment. Please visit our 2,000 sq. ft. showrooms or write or phone for your free catalogue. C.W.A.S. Ltd., 100 Rooley Avenue, Bradford BD6 1DB. Telephone 0274 308920.

FOR SALE. Acorn Atom 12K Rom. 12K Ram. Sony Cassette Recorder and games programs £110. Telephone 01-568 4254.

RS232 CABLES and D-type connectors at competitive prices. 25-way D connector plate/wallbox for only £5.25. Write or phone for details. VEP Limited, 5 Hewens Road, Uxbridge UB10. Tel: 01-848 7207.

WANTED

WANTED: ELECTRONIC COMPONENTS and test equipment. Factories cleared. Good prices given. Q Services, 29 Lawford Crescent, Yateley, Camberley.

TURN YOUR SURPLUS transistors, IC's etc into cash. Contact Coles Harding & Co., 103 South Brink, Wisbech, Cambs. Tel: 0945 584188. Immediate settlement.


COMPONENTS

DO YOU WISH TO LEGALLY TRANSMIT AUDIO SIGNALS OVER BRITISH TELECOM CIRCUITS?

We manufacture approved Interface Equipment for NARROW or WIDE BAND PRIVATE WIRE and PUBLIC SWITCHED TELEPHONE NETWORK circuits. Also TELECOM LINE CIRCUIT SAFETY BARRIERS.

PARTRIDGE ELECTRONICS
The Mixer People
56 Fleet Road, Benfleet, Essex, SS7 5JN, England.
(Telephone 03745 3256)

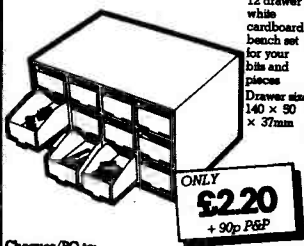Save money on drawer sets with the **BITSABOX**



Cheques/PO to: **DMW Boxes**, 81 Somerset Road London E17
Prop. R.E. Davidson
PERSONAL CALLERS & TRADE ENQUIRIES WELCOME

256K BUBBLE MEMORIES. Interface details included. Only £7.50 each. Speech synthesis boards. Very high quality. £45 each. Farrell, 78 Glenfield Road, Paisley. SAE. Tel: 041 884 6240.

BURGLAR ALARM EQUIPMENT: As used in the trade. JN Security Centre, 176 Sydenham Road, London SE26 5JZ. 01-778-1111. Showrooms open six days.

MAIDSTONE ELECTRONIC COMPONENTS shop. Thyronics. Control Systems 8, Sandling Road, Maidstone, Kent, Maidstone 675354.

KITS

DIGITAL WATCH REPLACEMENT parts, batteries, displays, backlights etc. Also reports publications, charts. S.a.e. for full list Profords Conersdrive, Holmergreen Bucks. HP15 6SGD

PRINTED CIRCUITS Make your own simply, cheaply and quickly! Golden Fotolac light-sensitive laquer - now greatly improved and very much faster. Aerosol cans with full instructions, £2.50.

ALARMS

A1

051 228 3483
INTRUDER ALARMS LTD
WHOLESALE SUPPLIES
MAIL ORDER DEPT

Bell Boxes.....	£6.00
Dummy Boxes.....	£4.50
Bell 6".....	£7.50
SIRENS	
Minimite.....	£4.50
Electronic.....	£7.50
Cable (4 core).....	£7.00
PRESSURE MATS	
Stair.....	£0.95
Standard.....	£1.50
CONTROL PANELS	
Battery T/E/E.....	£20.00
F.S.N. 20/40.....	£36.00
CONTACTS	
Aluminium.....	£1.85
Surface.....	£0.75
Flush.....	£0.65
Quickfits.....	£0.75
BEAMS	
Infra Red.....	£31.50
Ultrasonic comp.....	£36.00
Rec Battery.....	£6.95

Discount on quantity - Please add 15% VAT
FOR ORDERS LESS THAN £20 P&P £2.00 OVER £20 P&P FREE
A1 ALARMS LTD
86 Derby Lane, Old Swan, Liverpool 13

CENTURION ALARMS

We manufacture, you save £ £ £'s

Send s.a.e. or phone for our Free list of professional D.I.Y. Burglar Alarm Equipment and accessories. Discount up to 20% off list prices, eg. Control Equipment from £15.98, Decoy Bell Boxes from £5.95 inc.

TRADE ENQUIRIES WELCOME



BOOKS & PUBLICATIONS

PARAPHYSICS JOURNAL (Russian translation); psychotronics, kirlianography, heli-phonics music, telekinetics. Computer software. S.A.E. 4 x 9", Paralab, Downton, Wiltshire.

MANUALS for test and communications equipment. Send S.A.E. for list. P. Mack, 14 Court Eight, Hemingway Road, Witham, Essex CM8 2QU.

BOUND E.T.I.'s Jan. 1977 to Dec. 1982. £13 each complete year plus p&p. Phone (0252) 511048 after 6pm. No splits.

Developer 35p. Ferric Chloride 60p. Clear acetate sheet for master 15p. Copper-clad fibreglass board, approx. 1mm thick £2.00 sq. ft. Post/packing 75p. White House Electronics, Castle Drive, Praa Sands, Penzance, Cornwall.

Phone **ASP Classified**
01-437-1002

CLASSIFIED ADVERTISEMENT — ORDER FORM

Advertise nationally in these columns to over 100,000 readers for only 35p per word (minimum charge 15 words). Simply print your message in the coupon and send with your cheque or postal order made payable to


Argus Specialist Publications Ltd to:
CLASSIFIED DEPT., ELECTRONICS TODAY INTERNATIONAL
145 Charing Cross Rd., London WC2H 0EE. Telephone: 01-437 1002
Please indicate classification required.

Name.....
Address.....
.....
Tel. No. (Day)

WE TAKE ACCESS AND BARCLAYCARD

Please place my advert in E.T.I. for months. Please indicate number of insertions required.

WHAT USE A MICRO WITHOUT A PRINTER?

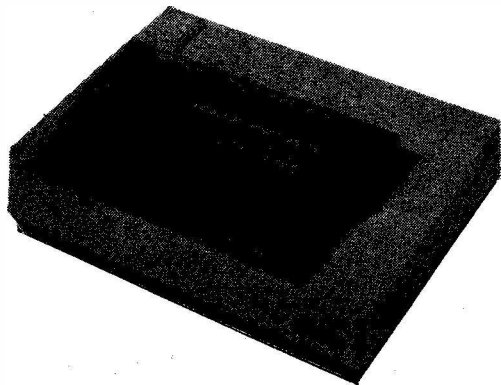

NEW A.D.M. 80 COL. DOT MATRIX WITH TRACTOR FEED. BACKED BY ONE OF BRITAIN'S LARGEST MANUFACTURERS, IT IS NOW STOCKED BY US.

SPECIAL LAUNCH PRICE

£311.00 + VAT. Carriage £7.50 or collect from our warehouse.

CROFTON ELECTRONICS LTD.


35 GROSVENOR ROAD, TWICKENHAM, MIDDX 01-891 1923/1513 Telex 295093

E.T.I. AUGUST 1983 ADVERTISERS INDEX

A.D. Electronics	79
Aitken Bros	59
Ambit International	37
Armon Electronics	59
Audio Electronics	27
Bi-pak	79
BK Electronics	8
Black Star	57
BNRS	56, 78
Bradley Marshall	36
Clef Products	6
Comtech Electronics	6
Comquip Electronics	64
Concept Electronics	76
Cricklewood Electronics	22, 23
Crimson Elektrik	56
Crofton Electronics	82
Display Electronics	12
Electronize Design	14
Electrovalue	27
Engineering & Electrical Design	76
Greenbank	69
Hawk Electronics	64
Hazzlewood Electronics	76
H.G. Electronics	79
Horizon Electronics	76
House of Instruments	60
ICS	69
ILP	28, 29, 57
Kelan Engineering	7
Kempston Electronics	82
L.B. Electronics	27
L.E.M. Services	78
L. & M. Services	52
Magenta Electronics	76
Maplin	OBC
Mawson Assocs.	78
Midwich Electronics	63
Musicraft	78
Pantechnic	60
Parnden	78
Powertran	IFC, 10, IBC
Rapid Electronics	21
R.T.V.C.	7
Sparkrite	75
Stewarts of Reading	6
Tangerine Computers	44
Technomatic	16, 17
T K Electronics	38
Watford Electronics	4, 5
Wilmslow Audio	78

SIMPLE PLUG-IN

CENTRONICS INTERFACE

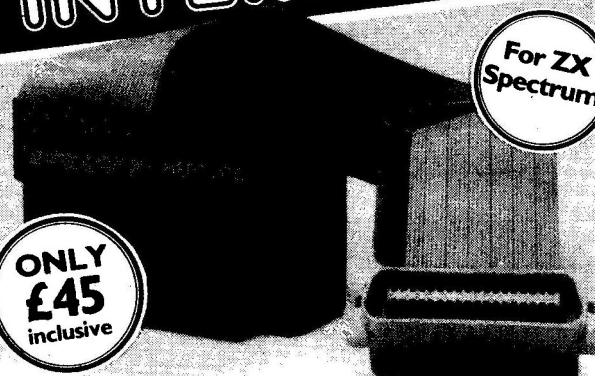

For ZX
Spectrum

ONLY
£45
inclusive

- Recognises LLIST and LPRINT which allows programs to be listed directly from your Spectrum
- Also allows printout direct from BASIC listings without the need for special user calls
- Completely self contained with 1 metre of ribbon cable and connectors
- Works with any Centronics Interface including all Epsoms, Seikosha 100A, OKI Microline 80 etc
- Includes driving software which allows up to 128 characters per line
- Full range of business software available
- Fully tested and guaranteed for 12 months

Trade Enquiries
Welcome

Plus £1.00 P + P

KEMPSTON

MICRO ELECTRONICS

Dept ET1 8, 180a Bedford Road, Kempston, Bedford MK42 8BL

Get moving with these new developments in UK Robotics

— advanced electrohydraulic designs for education, industry and now available to the home constructor.

Hebot II is a turtle-type robot which takes programming out of the two dimensional world of the VDU into the real three dimensional world. Given a DC supply of 9-15V it can perform a bewildering number of moves under computer control — forwards, backwards, left and right — with each wheel independently controlled. It has blinking eyes, beeps with a choice of two tones and has a solenoid operated pen to chart its progress. Touch sensors coupled to its shell return data, about its environment, to the computer for it to calculate evasive or exploratory action. Hebot II connects directly to an I/O port or alternatively with the universal interface board to the expansion bus of a ZX81 or other computer.



HEBOTT II

Up to the nano-second hard, firm and software developments embodied in a complete system. 12 Mega Hertz 16 bit CPU; 64K upwardly compatible DRAM; separate 16K video DRAM and 24K TI Power Basic with overwrite. Supports up to four Disc drives of mixed type with 16 serial I/O ports. Programmable Baud rate and comprehensive E Bus interface designed to support real world applications.

Very high resolution graphics gives 3D simulation in 16 colours on 36 prioritised planes of user definable characters. Software FORTH coming includes this trendy language along with NOS C/PM.

Hardware components available separately with details in Nov, Dec, and Jan issues of ETI. Software features include; Real time clock, full renumber command, buffered I/O to free machine whilst

Robotic experience is becoming as essential a subject as computing. MICROGRASP provides the lowest cost means of acquiring that experience but despite its ultra low price the robot has considerable versatility. There are 5 axes each using a servo motor and there is feedback from each of the arm movements. Control is by any computer with an expansion bus — the ZX81 being particularly suitable. Servoing is achieved with hardware on the interface board to keep programming simple and the robot is operated under BASIC commands with no computer specific software required. The interface board is memory mapped using only 64 bytes at any of 1024 switch selectable locations.

MICROGRASP robot kit with power supply £145.00
 Universal computer interface board kit £48.50
 23 way edge connector £2.50
 ZX81 peripheral/RAM Pack splitter board £3.00



MICROGRASP, INTERFACE BOARD AND ZX81

printing, call to machine code routines, hexadecimal support and user-friendly textual error trapping messages.

If computers interest you then the Cortex will expand your understanding infinitely more than off the shelf machines. Use it in business, education, research or just play with the incredible graphics capability. At Powertran we are using these machines in conventional roles, in product control and R & D. We shall co-ordinate the Cortex user group and distribute software for the TMS 9995 CPU. Complete 16 bit 64K computer kit £295.00 + VAT. Complete 16 bit 64K computer ready built £395.00 + VAT.



Top of the range is the Genesis P102 which has dual speed control, continuous servo operation and double acting cylinders for increased torque on the wrist and arm rotation joints. The microprocessor based control system has additional memory, position interrogation via the RS232C interface increasing the versatility of computer control and inputs are provided for machine tool interfacing.

6 axis system READY BUILT £1950.00
 Powertran CORTEX 16 bit 64K computer kit £295.00; READY BUILT £395.00
 (Electronics Today International December issue on CORTEX)



GENESIS P102 PROCESSOR BOX, HAND HELD CONTROLLER AND CORTEX COMPUTER

Example prices and specifications

Genesis S101
 Base: 19.5" x 11" x 7.5"
 Lifting capacity: 1500gm
 Arm lift: 66"
 Weight: 29Kg
 4 axis model in kit form £425
 5 axis model in kit form £475

Genesis P101
 Base: 19.5" x 11" x 7.5"
 Lifting capacity: 2000gm
 Arm lengths between axes: 14.0"
 Weight: 34Kg
 4 axis model in kit form £675
 6 axis model in kit form £595


Complete Systems as shown in Photograph above

Genesis S101
 4 axis system in kit form £681.50
 5 axis system in kit form £737.50
 5 axis system Ready Built £1450

Genesis P101
 6 axis system in kit form £945.00
 6 axis system Ready Built £1650

All prices exclusive of VAT

With prices starting below £1,000 the Genesis range of general purpose robots provide a first rate introduction to robotics for both education and industry. Each has a self-contained hydraulic power source, which enables loads of several pounds to be smoothly handled. The system operated from a single phase 240 or 120V AC supply or a 12V DC supply. The machine can be supplied with up to 6 axes each of which is fully independent but capable of simultaneous operation. Position control is achieved by means of a closed-loop feedback system based around a dedicated microprocessor. Movement sequences can be entered, stored and replayed by use of a hand held controller, alternatively the systems can also be interfaced to an external computer via a standard RS 232C link.

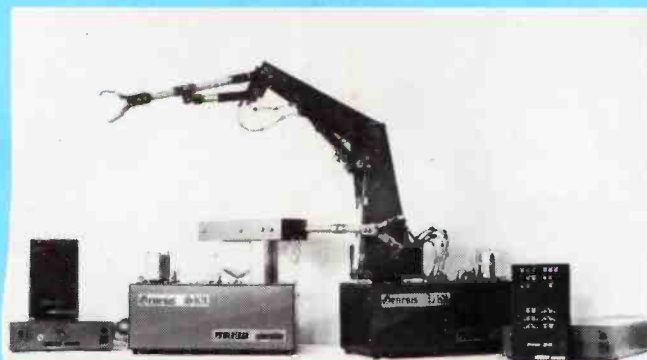

GENESIS S101 AND GENESIS P101 WITH PROCESSOR BOXES AND HAND-HELD CONTROLLERS




WORLD LEADERS IN ELECTRONIC KIT DESIGN AND SUPPLY

(CYBERNETIC DIVISION) PORTWAY INDUSTRIAL ESTATE
 ANOOVER HANTS SP10 3NM Phone Enquiries (0284) 84455
 Export Enquiries Powertran International
 Hollom Down Farm Lopcombe Salisbury
 Wiltshire SP5 1BP
 Tel: 0264 781545 TLX: 477407 ZENMON

Send now for an application form — then buy it with MAPCARD.

MAPCARD gives you real spending power — up to 24 times your monthly payments — instantly!

Maplin News

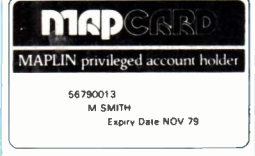

Sole UK Agents for Heathkit

NOW THE world-famous Heathkit range of superb electronic kits is available from Maplin — the newly appointed exclusive UK distributor. Kits range from a simple clock for beginners to a unique Robot (see pic) with which you can learn about robotics.

There is a range of training courses covering electronics and computing topics, many containing constructional projects. For full details, pick up a copy of the latest Maplin magazine or write for a free copy of our Heathkit catalogue. Order As XH62S.



GREAT PROJECTS FROM E&MM



OUR NEW book "Best of E&MM Projects Vol. 1" brings together 21 fascinating and novel projects from E&MM's first year.

Projects include Harmony Generator, Guitar Tuner, Hexadrum, Syntom, Auto Swell, Partylite, Car Aerial Booster, MOS-FET Amp and other musical, hi-fi and car projects. ORDER AS XH61R. PRICE £1.

Computer Shopping Arrives

AS FROM June 1st you can place orders directly with our computer from your personal computer. The computer shopping revolution has arrived! To communicate, you'll need a modem (our RS232 compatible modem kit is LW99H price £39.95) and an interface (our ZX81 interface LK08J price £24.95 is available already with many more for most popular micros coming soon).

Just dial us up on 0702 552941 and you'll be able to interrogate our stock file then place your order, type in your credit card number and a few minutes after you hang up your order will print out in our warehouse ready for packing. And all without saying a word.

Try out the future way of shopping now! You'll see immediately what stock we've got available and you'll discover how easy it is to ensure your order is exactly right. And you'll see precisely what the current price is for each item and what total amount will be charged to your credit card. It all helps to make buying easier. So give us a ring now!

Maplin's Fantastic Projects

FULL DETAILS in our project books. Price 70p each.

In Book 1 (XA01B) 120W rms MOSFET Combo-Amplifier • Universal Timer with 18 program times and 4 outputs • Temperature Gauge • Six Vero Projects.

In Book 2 (XA02C) Home Security System • Train Controller for 14 trains on one circuit • Stopwatch with multiple modes • Miles-per-Gallon Meter.

In Book 3 (XA03D) ZX81 Keyboard with electronics • Stereo 25W MOSFET Amplifier • Doppler Radar Intruder Detector • Remote Control for Train Controller.

In Book 4 (XA04E) Telephone Exchange for 16 extensions • Frequency Counter 10Hz to



600MHz • Ultrasonic Intruder Detector • I/O Port for ZX81 • Car Burglar Alarm • Remote Control for 25W Stereo Amp.

In Book 5 (XA05F) Modem to European standard • 100W 240V AC Inverter • Sounds Generator for ZX81 • Central Heating

Controller • Panic Button for Home Security System • Model Train Projects • Timer for External Sounder.

In Book 6 (XA06G) Speech Synthesiser for ZX81 & VIC 20 • Module to Bridge two of our MOSFET Amps to make a 350W Amp • ZX81 Sound on your TV • Scratch Filter • Damp Meter • Four Simple Projects.

In Book 7 (XA07H) Modem Interface for ZX81/VIC20 • Digital Enlarger Timer/Controller • DXers Audio Processor • Sweep Oscillator • CMOS Crystal Calibrator.

25W Stereo MOSFET Amplifier



- Over 26W/channel into 8Ω at 1kHz both channels driven.
- Frequency response 20Hz to 40kHz ± 1dB.
- Low distortion, low noise and high reliability power MOSFET output stage.
- Extremely easy to build. Almost everything fits on main pcb, cutting interwiring to just 7

wires (plus toroidal transformer and mains lead terminations). • Complete kit contains everything you need including pre-drilled and printed chassis and wooden cabinet.

Full details in Projects Book 3. Price 70p (XA03D). Complete kit only £55.20 incl. VAT and carriage (LW71N).

MATINEE ORGAN

EASY-TO-BUILD, superb specification. Comparable with organs selling for up to £1000.

Full construction details in our book (XH55K). Price £2.50. Complete kits available. Electronics (XY91Y) £299.95*. Cabinet (XY93B) £99.50*. Demo cassette (XX43W) £1.99. *Carriage extra



Maplin's New 1983 Catalogue

Over 390 pages packed with data art pictures and all completely revised and including over 1000 new items. On sale in all branches of WH SMITH. Price £1.25.



MAPLIN ELECTRONIC SUPPLIES LIMITED, P.O. Box 3, Rayleigh, Essex SS6 8LR. Telephone: Sales (0702) 552911 General (0702) 554155.

Shops at: 159 King St., Hamersmith, London W6. Tel: 01-748 0926. 284 London Rd., Westcliff-on-Sea, Essex. Tel: (0702) 554000. Lynton Square, Perry Barr, Birmingham. Tel: (021) 356 7292.

Shops closed Mondays.

All prices include VAT & carriage. Please add 50p handling charge to orders under £5 total value.

POST THIS COUPON NOW!

Please send me a copy of your 1983 catalogue. I enclose £1.50 (inc. P&P). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the UK send £1.90 or 10 International Reply Coupons.

Name

Address

.....

.....

Post Code