

# Hobby

AN ARGUS SPECIALIST PUBLICATION

# Electronics

Project Electronics For Everyone

85p

## ZX81/Spectrum Programmable Joystick Controller



**Protect Your  
Car Aerial  
With The...**



**HE  
Auto-Winder!**

**Novel Remote-Control Mains Power Switch**  
**RAM Pack and Interface Board for the Jupiter ACE**

# NOW 'LIVE' THE AMBIT TOP TEN

\* TOBIE DISTRIBUTOR OF THE YEAR \*

## AA NICADS



High quality Ever Ready nickel cadmium rechargeable batteries.  
Size: 14.5x50mm; 1.2V; Capacity: 500MAH  
Stock No. 01-12004 Price: 0.80

## CNICADS

High quality Ever Ready nickel cadmium rechargeable batteries.  
Size: 26 x 49mm; 1.2V; Capacity 2.2AH  
Stock No. Price: 2.35

## CRYSTAL FILTER

A crystal filter for the first IF of CB receivers, in place of the usual ceramic filter can perform the single most significant improvement in blocking and cross mod in most circuits.  
Model: 10M15A; Centre Freq: 10.7MHz; Band Width: 15kHz(3dB); Term Imp: 3kΩ  
Stock No. 20-10152 Price: 1.99



## MODEM KIT


A 300 baud full duplex originate only acoustically coupled modem. Use with any home computer with RS232 capability.  
Not PO approved!!!



Electronics Stock No. 41-00201 Price: 19.94  
Hardware Stock No. 41-00208 Price: 12.00


## VEROBOARD

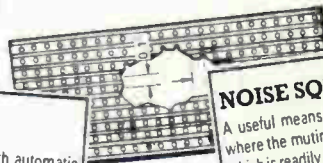0.1" pitch. No. holes: 36x50; Size("): 3.75x3.75  
Stock No. 21-09003 Price: 1.14


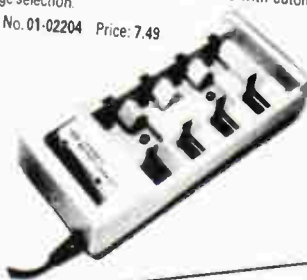
## CH4/RX4

Will recharge AA, C, D and PP3 size cells with automatic voltage selection.  
Stock No. 01-02204 Price: 7.49



## NOISE SQUELCH SYSTEM

A useful means of curing the deficiencies of NBFM sets where the muting control is derived from the signal level which is readily influenced by ignition noise etc.  
Kit Stock No. 40-44362 Price: 4.12  
Built Stock No. 40-44363 Price: 8.45



## FET DIP OSCILLATOR


Stock No. 40-16215 Price: 18.79

An essential piece of test equipment for the RF constructor. GDO or absorption wavemeter function covering 1.6-215MHz in five ranges.  
Fibre-glass PCB, all components, all hardware, punch, painted and screen printed case, wire etc. for coils and printed scale.


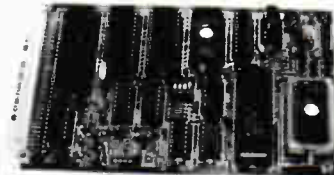
## Z8 TBPDS

Based on the Z8 basic/debug CPU is the most adaptable and understandable entry to this design on MPU based control systems.  
Needs only to be connected to an RS232 terminal or a home computer configured as one, to provide complete program development/support.  
Stock No. 40-00802 Price: 160.00



## SCHOTTKY DIODE BALANCED MIXER

Hermetically sealed for receiver and modulator applications. SBL1, 1-500MHz premium type.  
Stock No. 12-00003 Price: 4.68




Please add 60p postage & packing per order

AND LOTS, LOTS MORE IN THE CATALOGUE AVAILABLE FROM JULY  
ALL PRICES EXCLUDING VAT

**Ambit international**  
200 North Service Road  
Brentwood, Essex  
CM14 4SG

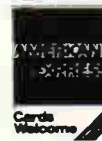Telecom directory:  
Consumer 0277-230909  
Industrial 0277-231616  
Telex 995194 AMBIT G  
DATEL 0277-232628



TELEPHONE SALES 8 am - 7 pm MON - FRI 9 am - 6 pm SAT



# Hobby Electronics

AUGUST 1983  
VOL 5 No 8

## PROJECTS

- ★ PROGRAMMABLE JOYSTICK CONTROLLER ..... 11  
*Fun and games for the Spectrum, ZX81 and ACE.*
- ★ WHISTLE SWITCH ..... 36  
*Whistling in the dark?*
- ★ EXPANDING THE ACE ..... 42  
*Get this ACE RAM pack and I/O up your sleeve.*
- ★ AUTO-WINDER ..... 56  
*Retract your car radio aerial.*
- ★ READER'S PROJECT: ENLARGER TIMER ..... 60  
*Photographic Developments.*



Programmable Joystick — page 11

## FEATURES

- ★ ALL ABOUT ELECTRONICS PART 2 ..... 20  
*Electromagnets and Ohm's Law.*
- FAMOUS NAMES ..... 52  
*Concluding our longest-running series with Alexander Graham Bell.*
- ★ CAREERS IN ELECTRONICS PART 4 ..... 47  
*Transmitting radio and television.*



Ace Expansion Project — page 42

## REGULARS

- Monitor ..... 6
- What's On Next ..... 18
- HE Bookshelf ..... 26
- Points Of View ..... 28
- Forward Bias ..... 31
- Buylines ..... 34
- HE Subscriptions ..... 40
- Clever Dick ..... 41
- Reader Services ..... 55
- HE Backnumbers ..... 62
- PCB Service ..... 63
- PCB Printout ..... 64




Whistle Switch — page 36

*The Hobby 'Scope: Once more we extend our apologies to readers awaiting the second part of this project. Due to unexpected technical and component supply problems beyond our control, it has had to be withdrawn again.*

*The final instalment of Components For Computing has also had to be held over for a future issue.*

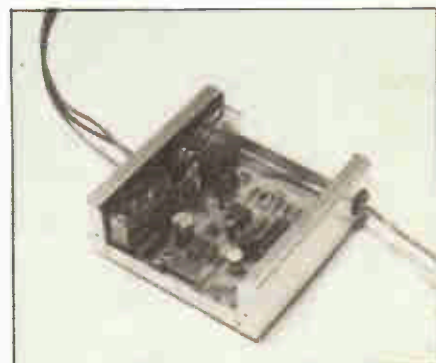Editor: Ron Keeley  
 Assistant Editor: Helen Armstrong BA  
 Technical Illustrator: Jerry Fowler  
 Advertisement Manager: David Kitchener  
 Assistant Advertisement Manager: Joanne James  
 Managing Editor: Ron Harris BSc  
 Managing Director: T.J. Connell



Auto-Winder for car radio aerials — page 56

Hobby Electronics is normally published on the second Friday of the month prior to the cover date.  
 Hobby Electronics, 145 Charing Cross Road, London WC2H 0EE, 01-437 1002. Telex No 8811896. Published by Argus Specialist Publications Ltd.  
 Origination by Ebony Typesetting, Trion House, 13 Dean Street, Liskeard, Cornwall PL14 4AB.  
 Distributed by S. M. Distribution Ltd, 16/18 Trinity Gardens, London SW9 8DX.  
 Printed by QB Ltd, Colchester. Covers printed by Alabaster Passmore.

Notice: The contents of this publication including all articles, designs, plans, drawings and programs and all copyright and other intellectual property rights therein belong to Argus Specialist Publications Limited. All rights conferred by the Law of Copyright and other intellectual property rights and by virtue of international copyright conventions are specifically reserved to Argus Specialist Publications Limited and any reproduction requires the prior written consent of the Company. All reasonable care is taken in the preparation of the magazine to ensure accuracy, but Argus Specialist Publications Ltd cannot be held responsible legally. ©Copyright 1982 Argus Specialist Publications Ltd. Member of Audit Bureau of Circulation.

# Hobby Electronics

AUGUST 1983  
VOL 5 No 8

## PROJECTS

- ★ PROGRAMMABLE JOYSTICK CONTROLLER ..... 11  
*Fun and games for the Spectrum, ZX81 and ACE.*
- ★ WHISTLE SWITCH ..... 36  
*Whistling in the dark?*
- ★ EXPANDING THE ACE ..... 42  
*Get this ACE RAM pack and I/O up your sleeve.*
- ★ AUTO-WINDER ..... 56  
*Retract your car radio aerial.*
- ★ READER'S PROJECT: ENLARGER TIMER ..... 60  
*Photographic Developments.*

## FEATURES

- ★ ALL ABOUT ELECTRONICS PART 2 ..... 20  
*Electromagnets and Ohm's Law.*
- FAMOUS NAMES ..... 52  
*Concluding our longest-running series with Alexander Graham Bell.*
- ★ CAREERS IN ELECTRONICS PART 4 ..... 47  
*Transmitting radio and television.*

## REGULARS

- Monitor ..... 6
- What's On Next ..... 18
- HE Bookshelf ..... 26
- Points Of View ..... 28
- Forward Bias ..... 31
- Buylines ..... 34
- HE Subscriptions ..... 40
- Clever Dick ..... 41
- Reader Services ..... 55
- HE Backnumbers ..... 62
- PCB Service ..... 63
- PCB Printout ..... 64

*The Hobby 'Scope: Once more we extend our apologies to readers awaiting the second part of this project. Due to unexpected technical and component supply problems beyond our control, it has had to be withdrawn again.*

*The final instalment of Components For Computing has also had to be held over for a future issue.*


Editor: Ron Keeley  
 Assistant Editor: Helen Armstrong BA  
 Technical Illustrator: Jerry Fowler  
 Advertisement Manager: David Kitchener  
 Assistant Advertisement Manager: Joanne James  
 Managing Editor: Ron Harris BSc  
 Managing Director: T.J. Connell




Programmable Joystick — page 11



Ace Expansion Project — page 42

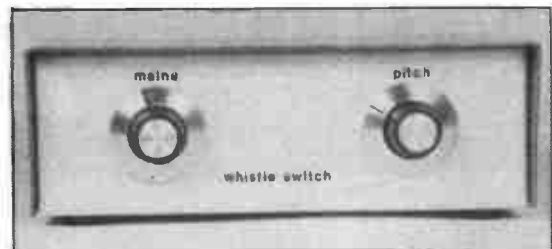

Whistle Switch — page 36

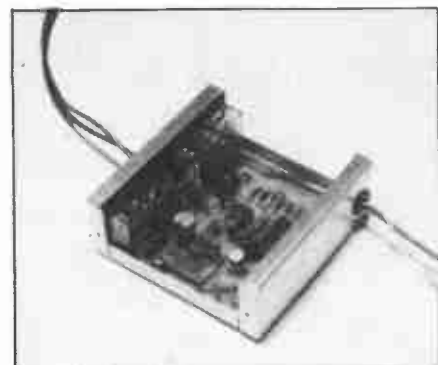

Auto-Winder for car radio aerials — page 56


Hobby Electronics is normally published on the second Friday of the month prior to the cover date.  
 Hobby Electronics, 145 Charing Cross Road, London WC2H 0EE, 01-437 1002. Telex No 8811896. Published by Argus Specialist Publications Ltd.  
 Origination by Ebony Typesetting, Trion House, 13 Dean Street, Liskeard, Cornwall PL14 4AB.  
 Distributed by S. M. Distribution Ltd, 16/18 Trinity Gardens, London SW9 8DX.  
 Printed by QB Ltd, Colchester. Covers printed by Alabaster Passmore.

Notice: The contents of this publication including all articles, designs, plans, drawings and programs and all copyright and other intellectual property rights therein belong to Argus Specialist Publications Limited. All rights conferred by the Law of Copyright and other intellectual property rights and by virtue of international copyright conventions are specifically reserved to Argus Specialist Publications Limited and any reproduction requires the prior written consent of the Company. All reasonable care is taken in the preparation of the magazine to ensure accuracy, but Argus Specialist Publications Ltd cannot be held responsible legally. ©Copyright 1982 Argus Specialist Publications Ltd. Member of Audit Bureau of Circulation.

Step-by-step fully illustrated assembly and fitting instructions are included together with circuit descriptions. Highest quality components are used throughout.

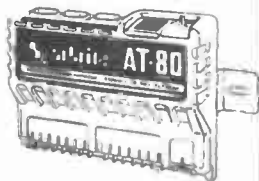
# Sparkrite

BRANDEADING ELECTRONICS  
NOW AVAILABLE IN KIT FORM



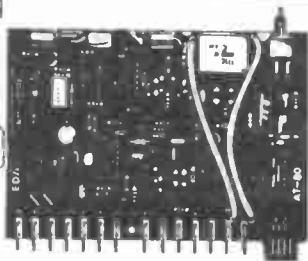
## AT-80 Electronic Car Security System

- Arms doors, boot, bonnet and has security loop to protect fog/spot lamps, radio/tape, CB equipment
- Programmable personal code entry system
- Armed and disarmed from outside vehicle using a special magnetic key fob against a windscreen sensor pad adhered to the inside of the screen
- Fits all 12V neg earth vehicles
- Over 250 components to assemble


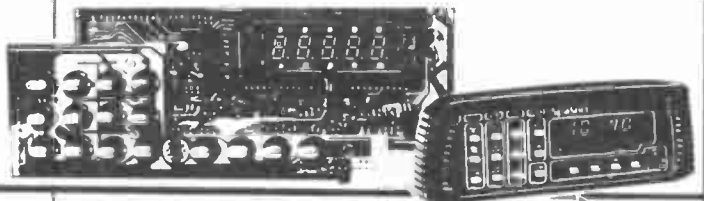
## VOYAGER Car Drive Computer

- A most sophisticated accessory
- Utilises a single chip mask programmed microprocessor incorporating a unique programme designed by EDA Sparkrite Ltd
- Affords 12 functions centred on Fuel, Speed, Distance and Time
- Visual and Audible alarms warning of Excess Speed, Frost/Ice, Lights-left-on
- Facility to operate LOG and TRIP functions independently or synchronously
- Large 10mm high 400ft-L fluorescent display with auto intensity
- Unique speed and fuel transducers giving a programmed accuracy of + or - 1%
- Large LOG & TRIP memories: 2,000 miles 180 gallons 100 hours
- Full Imperial and Metric calibrations
- Over 300 components to assemble
- A real challenge for the electronics enthusiast!




## SX1000 Electronic Ignition

- Inductive Discharge
- Extended coil energy storage circuit
- Contact breaker driven
- Three position changeover switch
- Over 65 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg. earth vehicles

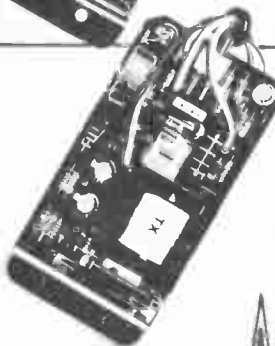
## TX1002 Electronic Ignition

- Contactless or contact triggered
- Extended coil energy storage circuit
- Inductive Discharge
- Three position changeover switch
- Distributor triggerhead adaptors included
- Die cast weatherproof case
- Clip-to-coil or remote mounting facility
- Fits majority of 4 & 6 cyl. 12V. neg. earth vehicles
- Over 145 components to assemble


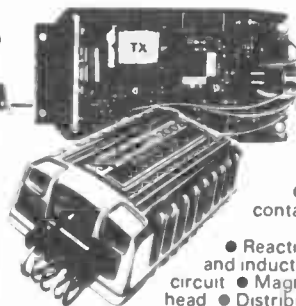
## SX2000 Electronic Ignition

- The brandleading system on the market today
- Unique Reactive Discharge
- Combined Inductive and Capacitive Discharge
- Contact breaker driven
- Three position changeover switch
- Over 130 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg. earth vehicles




## TX2002 Electronic Ignition

- The ultimate system
- Switchable contactless
- Three position switch with Auxiliary back-up inductive circuit
- Reactive Discharge Combined capacitive and inductive
- Extended coil energy storage circuit
- Magnetic contactless distributor triggerhead
- Distributor triggerhead adaptors included
- Can also be triggered by existing contact breakers
- Die cast waterproof case with clip-to-coil fitting
- Fits majority of 4 and 6 cylinder 12v neg. earth vehicles
- Over 150 components to assemble

All SPARKRITE products and designs are fully covered by one or more World Patents

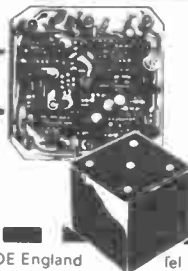**SPECIAL OFFER**  
"FREE" MAGIDICE KIT WITH ALL ORDERS OVER £45.00



## MAGIDICE Electronic Dice

- Not an auto item but great fun for the family
- Total random selection
- Triggered by waving of hand over dice
- Bleeps and flashes during a 4 second tumble sequence
- Throw displayed for 10 seconds
- Auto display of last throw 1 second in 5
- Muting and Off switch on base
- Hours of continuous use from PP7 battery
- Over 100 components to assemble

SPARKRITE 82 Bath Street Walsall West Midlands WS1 3DE England

tel (0922) 614791 Allow 28 days for delivery

	SELF ASSEMBLY KIT
SX 1000	£12.95
SX 2000	£19.95
TX 1002	£22.95
TX 2002	£32.95
AT 80	£32.95
VOYAGER	£64.95
MAGIDICE	£9.95

PRICES INC VAT POSTAGE & PACKING

NAME \_\_\_\_\_ HE8

ADDRESS \_\_\_\_\_

I ENCLOSE CHEQUE(S) POSTAL ORDERS FOR

£ \_\_\_\_\_ KIT REF \_\_\_\_\_

CHEQUE NO \_\_\_\_\_



BRANDEADING BRITISH ELECTRONICS

CUT OUT THE COUPON NOW!

# MONITOR

## Computer Data

A survey conducted by the British Market Research Bureau earlier this year, and published by Gowling Marketing Services of Liverpool, has produced some facts and figures which may be of interest to readers, although they are aimed primarily at companies marketing micros. The survey was conducted over 2000 households, which doesn't sound like a lot, but let's trust to the experience of the BMRB and see what they have come up with.

The picture that emerges is very much one of "A Portrait of the Micro Owner as a Young Man" and seems to be putting across the message that your proverbial 'computer society' is one which will grow up with the younger generation of users, rather than emerging fully fledged from the work done by industry and scientists — leaving aside that the one has only been made possible by the other.

The report shows that 4.9% of households, or about one in twenty, have a microcomputer — slightly under one million households in the UK. The most likely buyers are social groupings "AB, and C1", or, to put it another way, not only people with a certain amount of spending money to spare, but also people who have to ration 'non-essentials' (if you'll pardon the heresy!) fairly carefully.

"Males, *more particularly sons*" (our italics) "are the most likely users of the family home computer . . . Females appear to have little interest in computers." states the survey. (Significantly, the gels I know who actually like computing for its own sake work with mainframes, and think that micros are a waste of time!) The picture of earnestly struggling Dad being upstaged by Lad while Mum and Lass take no interest whatever rings true, doesn't it? Or does it? Any opinions?

"People living in modern "middle price" owner occupied housing with young families, and those living in traditional high status suburbia" are also identified as outstanding users of micros.

Unsurprisingly, the Sinclair ZX81 emerged as market leader with 43%, the Spectrum with 14% and the VIC20 with 12%. Also not totally surprising is that 40% of all micro sales were made in December, and 40% of all micros during the year were known to have been bought as gifts. These were mostly at the lower end of the price range.


Is it just a fad, like the Christmas puppy, which will soon be discarded, or is it a determined trend towards a micro in every home? Well, the marketing people certainly see it as a trend upwards. It looks as though Dad, not to mention Mum, had better start buttering up their BASIC before they come home one day and find they don't speak the same language as the electric cooker!

Another sign of the March of the Micros is the establishment, for the first



time in the UK, of a Computer Trade Association to represent the retailers, distributors, software houses, manufacturers, consultants, and all who operate on the commercial side of computing. As with the Video Trade Association, their main reason for forming is to fight software piracy and the unauthorised lending and copying of copyright software. They also hope to establish a professional code of conduct to govern dealings both within the trade and between the trade and the public.

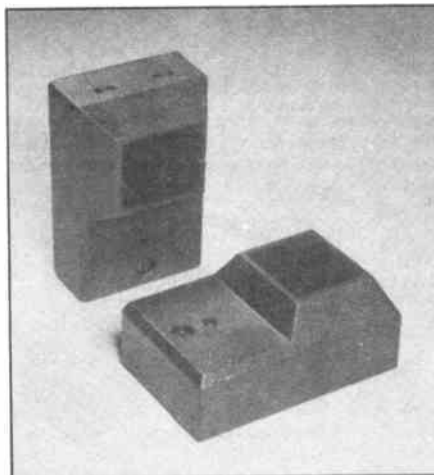Among the members are Atari, Bug-Byte, Buffer, Micro Shop, Computers, Grundy, Silversoft, Tandy and Virgin Games (who are handling the press side). Any enquiries about the CTA to The Computer Trade Association, The Secretary, Nigel Buckhurst, 108 Margaret St., Coalville, Leicester LE6 2LX. Tel: (0530) 35566.



## Infra-Red Alert

Riscomp have announced an addition to their range of security modules and accessories: an infra-red system known as the IR 1470. The unit, which operates from a conventional supply, consists of a separate infra-red transmitter and receiver, and provides a modulated beam of infra-red light over distances of up to 50ft. In the event of the beam

being interrupted, a relay in the receiver unit is energised. If this is connected to an appropriate warning device, it will sound an alarm. Both transmitter and receiver are housed in compact moulded enclosures and are easily mountable on most surfaces. An LED incorporated in the receiver indicates when the beam is lined up properly.

The system is British made and fully guaranteed, and is supplied with comprehensive data. It costs £25.60. Riscomp do a range of professional security modules, many of which are installable by anyone with adequate electrical and electronics knowledge. For further information contact Riscomp Ltd., 21 Duke St., Princes Risborough, Bucks HP17 0AT. Tel: (08444) 6326.



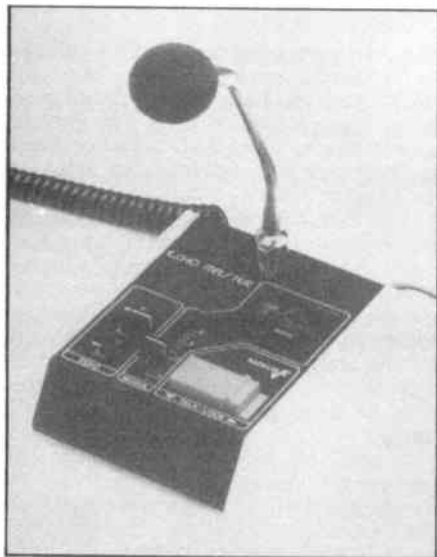
## A Word In Your VIC

SPT Electronics are marketing a versatile and low-priced software package for the VIC-20 and 64, by the highly descriptive name of Quick Brown Fox.

SPT boast that QBS offers more features than "industry standard" programs costing many times as much. Features include full editing, automatic reformatting of whole texts, single-key command operations, compatibility with a wide variety of printers without complicated installation procedures, takes comparatively little memory space (and will run on the VIC-20's 5K without need for expansion) and — a unique feature — is apparently able to send and receive information from one computer





to another via built-in telecommunication facilities. This allows Fox systems to converse, and can work between QBS and some other systems as well.

The package costs £60 and, apart from converting the VICs into word processors, SPT see the system as the basis of a full professional letter-quality workstation for under £1000, a considerable reduction.

For more information contact **SPT Electronics Ltd., Tollesbury, Essex CM98SE. Tel: (0621) 868484.**

## Get Miked Up

**Sadelta Microphones**, of Spain, have appointed **Telecomms**, of Portsmouth, as their sole UK distributors. To coincide with this, Sadelta have announced several new mikes in their range.

The **Bravo O** is a preamplifier compressor base microphone in a 'de-luxe' style housing with a normal/vox switch for amateur radio use. The maximum compression is 20dB. The **Bravo 2** version has two VU meters for monitoring compression and preamp gain. The **Bravo O** is £29.95, the **Bravo 2** is £39.95.

The **HM-20** is a mobile hand-mike, designed for maximum comfort and ease of use. Sadelta claim that it can improve transmission in all frequency bands and modulation modes — mentioning DX and CB as good examples of 'worst conditions, perturbations and interference!' The **HM-20** has four switching circuits and is adaptable to electronic and relay switch equipment, with a four wire cable which makes it compatible with all transceivers with three to seven pins. It has output level control on a revolving control switch in the thumb position.

The **Sadelta Echo Master** is a preamp desk mic with a built-in reverb 'echo chamber', for use with both radio and discos. Powered by an external 12V power supply, the **Echo Master** includes a VU meter for monitoring the modulation output, adjusted by a sliding pot. The price is £57.56.

Lastly, and most unusually, the **LM-20** is a voice-operated microphone in two parts: a necklet with the actual mic on it, and a control box, connected to the necklet by a thin wire which can easily be connected or disconnected. The microphone is triggered by the sound of the operator's voice (with a slight delay in switching off — to allow the speaker to draw breath or pause!) — and its sensitivity is controlled by a setting on the control box. The control box also has red and green LEDs which light when the rig is transmitting or receiving, and a switch to deactivate the mic for normal conversation.

We don't have a price for this one or for the **HM-20**, but information can be had from the distributors, **Telecomms, 189 London Rd., North End, Portsmouth. Tel: (0705) 660036 and 882145.**

## Breadboard Sighted!

The time draws near when a hobbyist's fancy lightly turns to thoughts of **BREADBOARD '83**. You have extra planning time this year, as the dates have (by popular demand) been moved nearer to Christmas; the 25th, 26th and 27th of November, to be precise.

This year's venue will be the plush, carpeted **Cunard International Hotel** at Hammersmith, right on the doorstep of the tube and bus services, and with easy access to the prime shopping areas of Kensington, Knightsbridge and Central London.

Features so far planned will include an extended programme of lectures, a bigger, better **Computer Corner**, **Ham Radio Today's Action Centre**, and a special package deal that will include rail travel, **Breadboard ticket**, bed and breakfast at a first class hotel, discount vouchers, etc. More details of this will follow.

Specially for model railway enthusiasts is the **Computer Controlled**

**Railway Layout competition** for a control system based on any microcomputer on a layout of not more than 6ft x 2ft x 6in. Get you entry forms by writing to **Peter Freebrey, Argus Specialist Publications, 145 Charing Cross Rd., London WC2H 0EE**, sending a small SAE.

## Cassette Cleaner

**Nu-Way Stylis** have produced a cleaning cassette for recorders. The difference between this cassette and many other 'cleaning cassettes' is that this one uses moving felt pads to clean the tape heads, and not an abrasive moving tape, and therefore causes far less wear and tear on the (expensive and troublesome to replace) tape heads.

The pack includes a cleaning lubricant, which is used to damp the two felt pads lightly. The cassette is then placed in the recorder and the recorder switched to 'play'. The pads move back and forth, cleaning the dirt and oxide not only from the record and playback heads but also the pinch and capstan rollers (dirty rollers can cause mistracking, which leads swiftly to the dreaded **Magnetic Spaghetti** which cheap or neglected cassette players love to feed on...) Once done, a pause of half a minute to let the cleaning fluid evaporate, and you're ready to roll again.

Regular cleaning like this (according to the instructions, of course) not only improves the sound quality but protects the player and the cassettes from damage. 90% of cassette player aggro is caused by dirt on the moving parts! So, if you can't clean the heads and whirly bits by hand, a cassette of this kind is the best option. It's especially useful for car players and other portables where the heads and rollers are hard to reach. The only recorders it may not do the job on are three-head machines — if you're lucky enough to have one!



# MONITOR

The 3 Point Cassette Cleaner is made by Nu-Way Styli Components Ltd., of 15 Haywood Ind. Park, Tameside Drive, Castle Bromwich B35 7BJ. Tel: 021 749 2240. It costs £2.99 and is available from hifi retailers.



## Mini Multitrack

Bandive Ltd. reckon that the cost of multitrack recording has been dramatically cut by the introduction of their Fostex X15 Tracker, which they call their 'musical sketch box'. This creature gives the impression, from the picture, of being a fairly meaty machine, but they claim that you can 'hold it in the palm of your hand', and at 3 x 11½ x 9in and 2.1kg, you could, too, if you happen to have fairly substantial hands.

The X15 is designed to run from an external AC adaptor (which is an optional extra) or a clip on battery pack (ditto), car battery or other battery.

All the essential features for taping and mixing for multitrack recording are in the X15, and all you need to add are microphones and headphones.

Tracks may be recorded individually, and monitoring for overdub is switched automatically. A built-in mixer, and tone control during record and playback allow skillful recordings to be made. Battery operation, remote punch-in, powerful headphone monitoring are among the features included.

Noise reduction is Dolby B; there are three positions on the input selector for mike, line or tape out signals going to the level control, equaliser facilities for input and output, gain and pan controls for each channel at overdub and mixdown, and plus or minus 15% pitch control for tuning and special effects.

For more information contact Bandive Ltd., Brent View Rd., London NW9 7EL. Tel: 01 202 4155.

## New Spectrum Software

Oxford Computing Publishing have some new programs available for the ZX Spectrum.

Those currently available are a Machine Code Test Tool (with a version for the ZX81), including a character generator for the Spectrum version (£9.95), and Address Manager which will handle up to 1500 names or 400 full addresses on the 48K Spectrum (less on the 16K, obviously) and boasts the qualities of very high speed, super friendliness, multiple indexing and full-screen editing (£8.95) and "The Turk"

chess program with six levels of difficulty and chess against the clock amongst its features (£8.95).

Later in the year other programs including Edit/Assembler, Financial Manager, VAT Manager and a Bridge Program will be released.

Having resolved certain problems with their GPO Box number, mail order turnaround at OCP is now usually 48 hours.

Information from Oxford Computer Publishing Ltd., "Brimrod", 48 High St., Chalfont St. Peter, Buckinghamshire SL9 9QB. Tel: (0753) 888866.

## New Electronics Club

Newly formed is the National Electronics Correspondence Club — newly, that is, back at the end of April when first we heard of them just in time to miss the deadline for our July issue! According to their letter, the club has been set up with the express purpose of providing a communications link for all hobbyists who are remote from local electronics clubs — an excellent idea, and I'm sure they won't be turning away members of other electronics clubs who want to join, either.

Club features such as a bi-monthly newsletter with hints on project construction, topical features, circuit ideas, views and advertisements, plus special offers on equipment, are planned, and members will be free to correspond with the club and with other members for help and encouragement.

Membership will be £4.50 a year, and anyone interested should write to Mr. E. Foley (Secretary), N.E.C.C., 95 Albert Rd., Levenshulme, Manchester M19 2FU, enclosing 25p for information and application form (which will be refundable on membership). It would be nice to see this club flourish, as active hobby clubs are a benefit to everyone.

## Sinclair Sound

Timedata are expanding their business to include add-ons for Sinclair computers, and the first product they have come up with is a tidy-looking sound box for use either with the ZX81 or the Spectrum, without the need for an adaptor.

The XZM Sound Box is based on the 9812 three channel sound chip to give a wide range of programmable effects. The unit has a nine pin I/O socket which can be used with Atari and Commodore joysticks, and other Sinclair add-ons can be plugged into the back of the box. The built in amp and loudspeaker can also be used to boost the Spectrum's 'beep'.

The XZM retails at £29.95 all inclusive. Order and enquiries to Timedata Ltd., 16 Hemmells, High Rd., Laindon, Basildon, Essex SS15 6ED. Tel: (0268) 418121.



## Teach Yourself The Lot

Electroni-Kit, already well known for their popular Chip Shop kits, straightforward construction kits with all the parts (even solder!) included, and simple no-prior-knowledge instructions





which even include a recommendation of which books to go on and read if you want to know more about electronics) are going about to make a whole new name for themselves distributing a new line in building-block, teach-yourself electronics and computing kits by **Denshi Block Mnfg. Co** and the **Gakken Co.**, of Japan.


The **FX-Computer** is a contraption about the size of a substantial transistor radio. Within this battery-operated unit (no messing about with mains) is a series of interchangeable component blocks which enables scores of circuits to be built up without soldering or waste. The **FX** has two manuals, one for the electronic circuits, the second and longer containing 100 computer programs aimed at youngsters and complete beginners. The whole unit costs £69.95 plus £3.00 p&p, and the manuals are said to be excellent. A longer look at the **FX-Computer** will be appearing in **HE** in due course.

Along the same lines but somewhat smaller and less ambitious are the **EX-System** electronics construction kits, basically the same principle but with a lesser range of experiments. The kits range from the **EX-15**, with 15 projects to build, up to the **EX-150**, plus additional add-on sets. Prices range from £22 to £55.

For price lists and brochures, contact **Electroni-Kit Ltd.**, 388 John St., London EC1V 4NN. Tel: 01 278 0109.
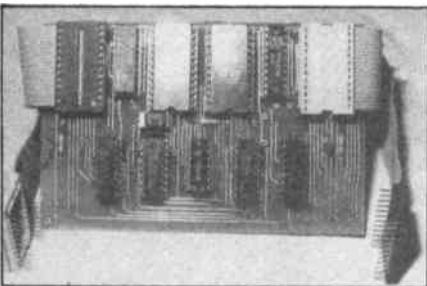
## Shorts

From **J P Designs** comes a multiplexed RAM card, **Interface 84**, which allows different microsystems to 'speak' to each other. **Interface 85** plugs directly into 24 pin RAM or EPROM




sockets, via ribbon cable headers. A select switch allows onboard memory to be mapped on either microsystem. This feature gives the card the ability to alter the memory contents from the master microsystem, whilst acting as an EPROM on the developing system. This is particularly useful when software debugging 'dumb' controllers.

The internal static CMOS memory has a fast access time of less than 250ns, making the card usable with nearly all microsystems. **Interface 84** comes fully tested complete with user notes at £49.95 plus VAT. Enquiries to **J P Designs**, 37 Oyster Row, Cambridge, CB5 8LJ. Tel (0223) 522234.

Possibly the world's lowest profile DIL

IC sockets, the new **EMC 21,000** series, available in 6 to 64 pin, 0.3, 0.4, or 0.6 in pitch options, allows the IC to sit only 2.92mm (0.115in) from the board. With the new funnel entry, short four finger style, Mini-Tulipe contact with bored out, closed-end, anti-wicking tail, this new range of sockets is suitable for manual or automatic IC loading and readily accepts both short and long IC legs.

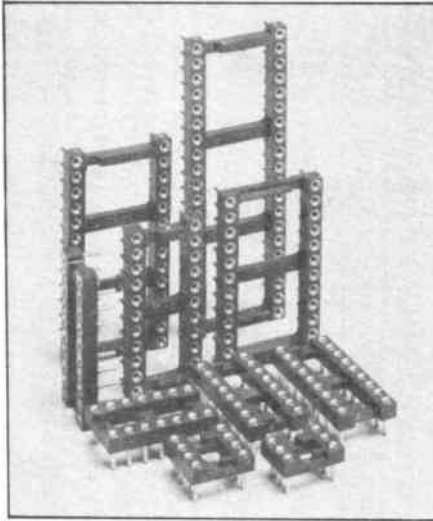

Needing only standard layout 0.813mm (0.032in) PCB piercings and available in various gold/tin plating options, this new beryllium copper contact is rated for 1A but offers typical contact resistance of only 4.3mR. Capable of operating over a temperature range of -65°C to +175°C and utilising 94-VO rated glass reinforced polyester, the socket body is of an open frame design that will not twist, bend or soften during installation but still allows maximum cooling air flow plus easy cleaning and inspection and if you can follow that lot — ! — and want to know more, contact **EMC Interconnection Specialists**, 50 London Rd., Sevenoaks, Kent. Tel: (0732) 460525.

Made-to-measure dustcovers for video recorders can be ordered for £3.95 from **Helbri Products Ltd.**, 51 Birstwith Rd., Harrogate HG1 4QT Tel: (0423) 889704. Please supply all dimensions (and make sure you leave room for switches sticking out beyond the line of the casing) including dimensions and location of the front panel clock so that a transparent window can be incorporated. Protection from dust prolongs videorecorder life in general, especially the expensive and fragile heads. **Helbri** do not say whether they make dust covers for other similar bits of equipment, but it is probably worth enquiring.

**Elkan Electronics** have announced their **EASI-CALC 1251** program for the **Sharp PC1251** pocket computer. Coupled with the **CE125** printer-recorder this gives a "spreadsheet" with as many as 26 lines across and up to 100 rows deep, with over 200 "cells" or co-ordinates on the sheet. As

well as being a problem-solving tool answering "What if . . . ?"-type questions, **EASI-CALC 1251** can be a portable mini data base storing up to 100 names and phone numbers. The package consists of a data-quality micro-cassette tape and a twenty-page user's manual. No programming knowledge is needed.

**EASI-CALC** costs £14.95 from **Elkan Electronics**, 11 Bury New Road, Prestwich, Manchester M25 8JZ. Tel: 061 798 7613.

Robotic arms producers **Colne Robotics** have produced a computer vision system costing only £395. Aimed at the educational market, the **COLVIS** system consists of a solid-state camera connected to a powerful microcomputer, which can extract and learn information from the image received from the camera. It can use parameters such as area, perimeter and centre of gravity to recognise the object in view, and deduce its position and orientation. It can be used with any microcomputer which has or can be fitted with an 8-bit bi-directional port.

Enquiries to **Colne Robotics Co. Ltd.**, Beaufort Rd., Off Richmond Rd., East Twickenham, Middx. TW1 2PQ. Tel: 01 892 8197.

**Namal Electronics** have announced their **ROMBLO 1248** EPROM blower for the Apple microcomputer. This device will program all common 24- and 28-pin EPROMs of type 2508, 2516, 2564, 2716, 2732 and 2764 or any pin compatible 5V EPROMS. The software is on-board, eliminating the need for disk drives.

The price is £95. Enquire to **Namal Associates Ltd.**, "Gatehouse", 25 Gwydir St., Cambridge CB1 2LG. Tel: (0223) 355404.

Anybody wanting to sell or buy leisure goods in the south-east can contact **Leisure Line**. They are a telephone sales company who keep a register of goods on computer. They have expanded to include a listing of clubs, schools, organisations and private teachers involved in leisure pursuits. The service is free to those seeking information, charged to those advertising. Contact **Leisure Line Data Ltd.**, 238-246 King St., Hammersmith, London W6 0RF or phone 01 741 8301 9am to 9pm Monday to Friday.

**Dawne Instruments** have also added a high standard multimeter, the **Unigor 3n**, to their range. It features 62 measuring ranges, costs £100, and is said to be the standard multimeter used by many professional European organisations. Special points mentioned by **Dawne** include single rotary switch for thirty-two measurement ranges, nearly 32k ohms/volt sensitivity, better than 0.5% accuracy, 0 to 500Rohms on the low range and 50MR on the highest, and a number of others.

More information from **Dawne Instruments and Electronics**, Shields Rd., Bill Quay, Gateshead NE10 0RS. Tel: (0632) 695117.





# ZX81:Jupiter Ace:Spectrum Programmable Joystick Controller

Paul Moody and Chris Lloyd

**Set your fingers free! Banish keyboard cramp! Play action games as they were always meant to be played, with the HE Joystick Controller!**

**This project is a completely new idea in Joystick design because it is fully programmable and can be used with *any* games software for the ZX81, Spectrum or Jupiter Ace.**

THE ZX81, Spectrum and Jupiter Ace keyboards are excellent for entering programs, but they are very difficult to use for playing any fast moving games. This is a great pity because there is a wide range of excellent games software written for the ZX81 and Spectrum. The Ace has perhaps been a little slower to catch on, but now that its versatility and speed are being appreciated, a number of good games have appeared for it.

The Joystick Controller described here can transform your computer

from a toy into a true arcade style machine, and its unique design allows its use on *all* software. You won't need to buy software especially written for a joystick, because *all* your existing programs will work with it.


## Basic Ideas

The way most joysticks work is to mimic the action of the keyboard, so that when the joystick is moved, the computer is fooled into believing that a key has been pressed. The problem that arises is simply this: which keys


should the joystick mimic? One convention is to use the "arrow" keys — 5, 6, 7 and 8 for left, down, up and right, and 9 for fire. But unfortunately only a limited amount of software uses these keys — mainly because it is very awkward to use keys so close together. The result is that many people buy a joystick and then find that they can't use it on any of their old software, or that many programs that they would like to buy won't work with the joystick.

This article describes a completely



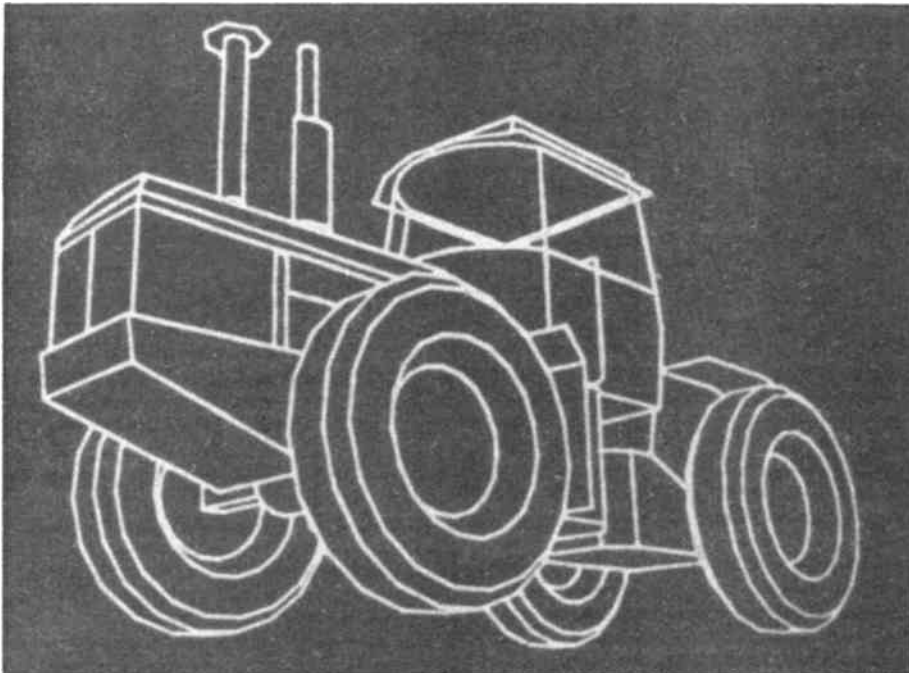

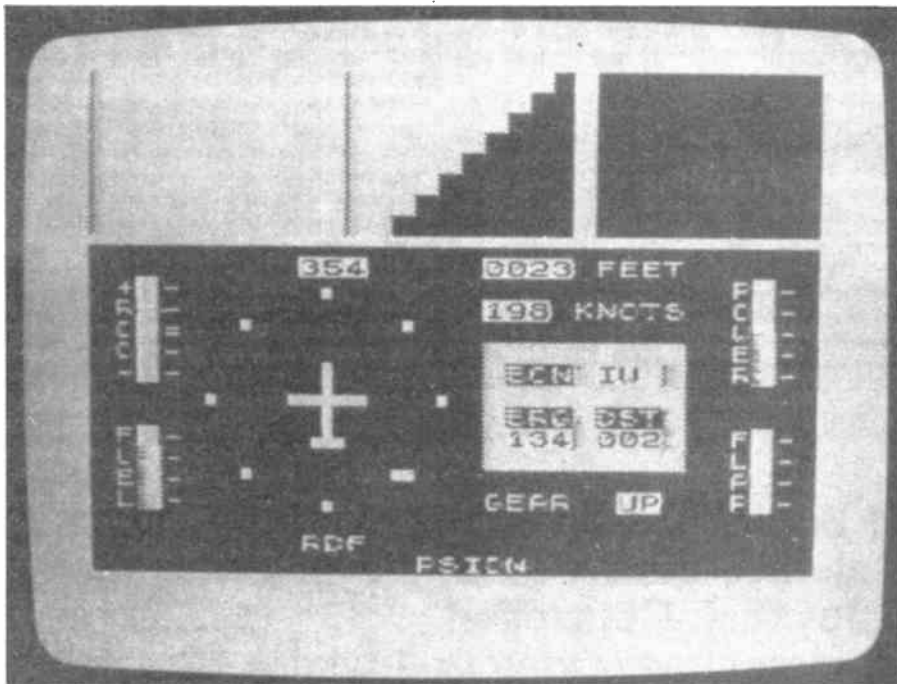Although this drawing was produced by a Computer Aided Design package, similar 'sketches' could easily be made using the joystick and a simple drawing programme. The 'fire' buttons could also be used, for example to delete points back along the plotted track and, on the Spectrum, to change the foreground colour.



Some games, such as the flight simulator shown, use more than the six functions available on the joystick. However the keyboard can still be used for flaps, undercarriage etc provided the joystick controls are not operated simultaneously.

A new idea in joystick design — the joystick is actually programmable and can mimic the action of *any* keys. To make things even easier for you, a program is included which remembers which games use which keys, so if you want to play a game that you've played before then you don't need to reprogram the joystick — simply give it the name of the program and it will do the rest.

To understand how the joystick works let's first take a look at the Sinclair keyboard.

## The Keyboard

The keyboard consists of a five by eight grid of wires, with a key over each crossing point (Figure 1). When a key is pressed, it connects together the two wires passing beneath it. The keyboard is read, one row at a time, by taking each of the eight address lines low, in turn, leaving the other seven high. Say, for instance, that the computer wishes to read the row containing the letters "QWERT", then

it sends A10 low with A8, 9, 11, 12, 13, 14, 15 all high. Now if none of the keys on that row are pressed, the outputs labeled KBDO-4 will all be at logic 1 — because they are all tied via resistors to +5 volts. But now consider what happens when key "W" is pressed: it connects A10 to KBD1, pulling KBD1 low and sending a logic 0 to the ULA (or to a tristate buffer in the case of the Ace, which has no ULA). So, by scanning through each row in turn the computer is able to build up a complete picture of the keyboard, and it does this every 1/50th of a second.

If you are wondering what those diodes are doing in the address lines, consider what would happen if they were not there and two keys in the same column were pressed at the same time; address lines would be shorted together and the computer would crash instantly!

## Input/Output

But how does the CPU distinguish between reading the keyboard and reading memory? In both cases it puts out an address, but for reading the keyboard it sends out a low on  $\overline{IORQ}$  instead of on  $\overline{MREQ}$ . This signal, combined with a low on A0, tells the ULA (or tristate buffer, in the case of the Ace) that it is reading the keyboard, and it transfers the values of KBDO-4 to the lower data lines, DO-4.

## In A Nutshell . . .

To explain the operation of the Joystick Controller, we'll use the very simplified (and highly schematic) circuit diagram of Figure 2. It consists of five basic blocks, plus a certain amount of control circuitry, represented here by a single two-input or gate.

The joystick itself is a simple array of six microswitches operated by the control lever; the output lines are connected to a +5V when one or more switches are closed.

An 8-into-3 line encoder operates on the CPU's address lines, A8 - A15, that are consecutively taken low during a Keyboard Read operation. The encoder simply reduces the number of address lines required for the memory by utilising the fact that only one of A8 to A15 will be low at any one time during a keyboard read. Since there are only eight possible states for A8-A15 at these times, only three lines ( $2^3 = 8$ ) are needed to contain this information.

These three lines become the top three address lines to the Controller's Random Access Memory. The lower order address lines are derived from one of two sources, depending on whether the Controller is being programmed for use, or is in use. The address lines are selected by an electronic switch, operated by the CPU's Write Enable line,  $\overline{WE}$ .

When the controller is being programmed (this is further explained, later),  $\overline{WE}$  is taken to logic 0 and the


'switches' are in the position shown, connecting the RAM's low-order address lines to the CPU's address lines. At the same time WE enables the RAM so that data can be written to it, and simultaneously connects the RAM's data lines to accept information from the CPU's data lines (this is actually done not by a switch as shown in Figure 2 — but this will be explained in a moment!).

Now the keyboard is not actually located at a single address; in fact any time A0 is low and an IN instruction has been issued (either by the CPU's Monitor program or by a user program — the Sinclair ULA can't tell the difference) the computer is performing a keyboard read operation. So, when programming the Controller, the keyboard is read by the program written for the purpose and the CPU will return, on data lines D0 - D4, a five-bit 'word' corresponding to whichever key has been pressed, if any. This data now has to be stored in the Controller RAM, and the location in RAM at which it is stored is determined by the CPU's address lines A1 - A7. This address is set up by a single number, entered as part of the set-up routine, which corresponds to a particular joystick position. What happens, in effect, is that the data corresponding to a particular key — 'Q', say, — is stored in the Controller RAM at a location which corresponds to a certain joystick position.

Now when a game is being played, the joystick output lines are connected to the RAM via the electronic switch (because WE is kept high).

Normally the ZX81 monitor performs a keyboard read about 50 times per second, and during these times both IORQ and A0 will be low, so the Controller RAM Chip Select pin will

Figure 1. The keyboard circuit shown is typical of the ZX81, Spectrum and Ace, with minor variations between them. Each square over a pair of crossed wires represents a switch which, when closed, pulls a KBD line to logic 0 when the corresponding address line is at 0. The Monitor programme performs a keyboard scan about once every 20 milliseconds by consecutively pulling each address line to 0. The diodes prevent two address lines being shorted if two keys are pressed together. The keyboard is also scanned by an INKEY instruction in a user-programme.

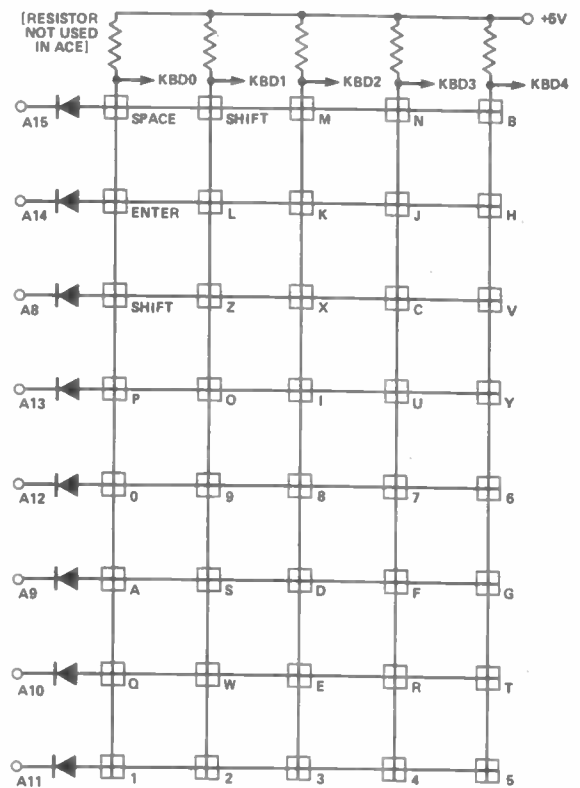

be enabled and data will be read from it, as well as from the keyboard. The RAM address, now depends on the physical joystick position, rather than a number representing it, and at that location will be found data corresponding to a particular keyboard letter!

As mentioned before, the RAM data lines are connected to the CPU's data lines by a 'switch' that is not really a switch. In fact 'it' is five high-power tri-state buffers, each bypassed by a

resistor. When the buffer outputs are in a high impedance condition ('off') the resistors allow data to be written to the Controller RAM. However when the WE input is high the buffers are active (the 'switches' are then in the opposite position to that shown in Figure 2) and they have sufficient 'muscle' to override the CPU data. Thus the computer receives data corresponding to the joystick position, rather than the actual keyboard data, whatever it may be. And, since the joystick position


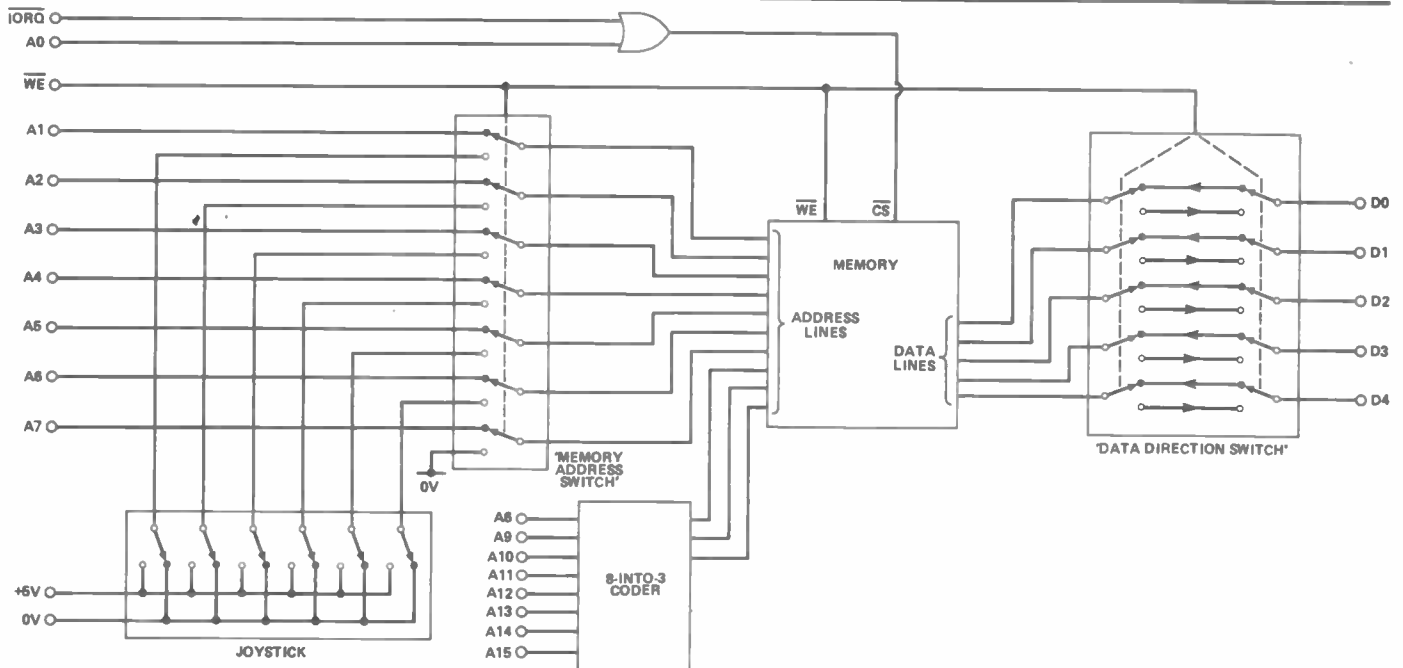


Figure 2. A highly representational block diagram of the Controller. When it is being programmed, the memory address lines are connected to the computer's address bus and data is accepted from the data bus, as shown. In use the "switches" are reversed; the joystick provides the addresses and previously programmed information is forced onto the data bus, overwriting information from the keyboard.

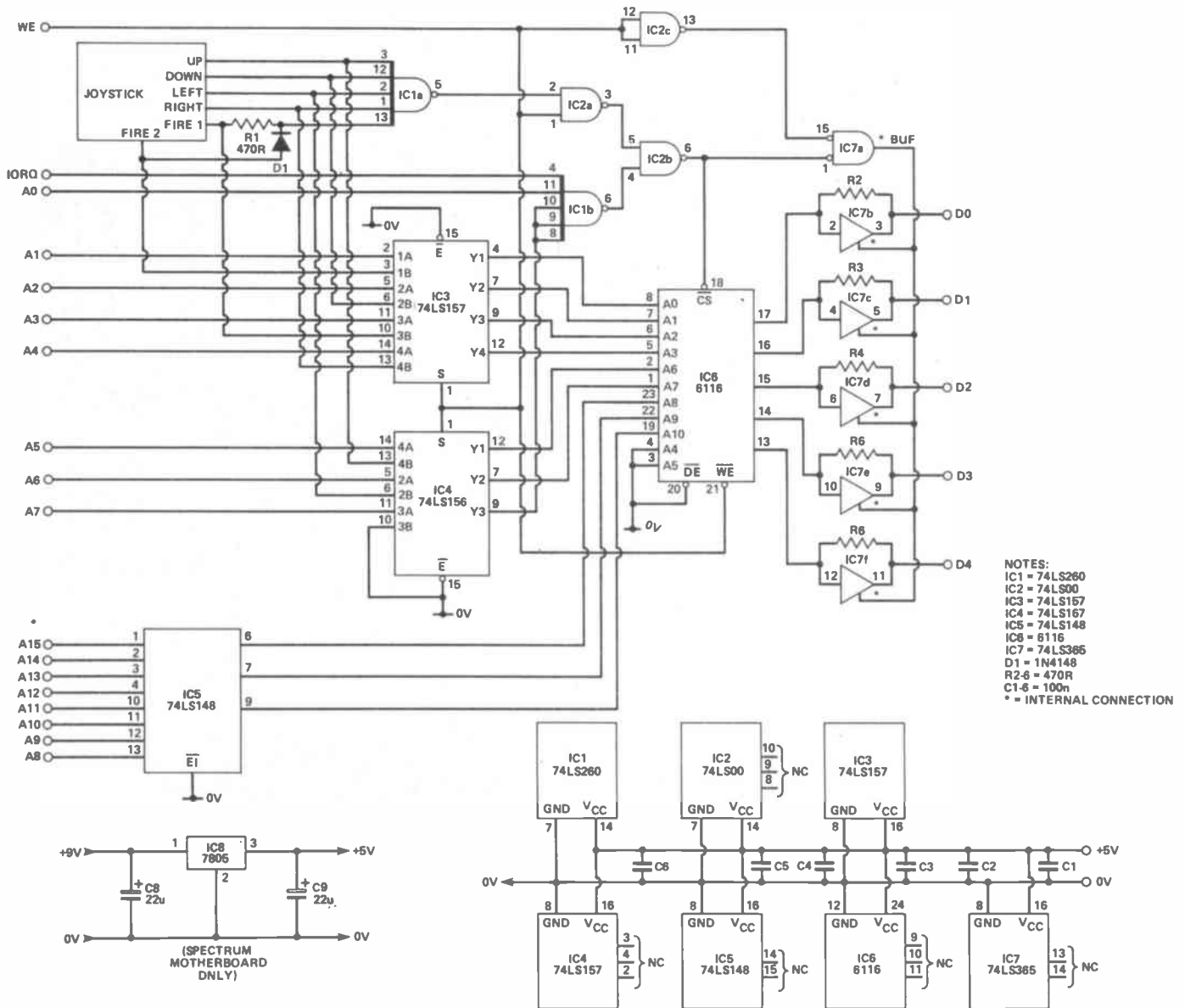

- NOTES:  
 IC1 = 74LS260  
 IC2 = 74LS00  
 IC3 = 74LS157  
 IC4 = 74LS157  
 IC5 = 74LS148  
 IC6 = 6116  
 IC7 = 74LS385  
 D1 = 1N4148  
 R2-6 = 470R  
 C1-6 = 100n  
 \* = INTERNAL CONNECTION

Figure 3. The full circuit of the Controller. ICs 3 and 4 are the "memory address switch" while IC7 controls the data direction.

has been set-up to correspond to a particular key, the computer receives the appropriate command — unless the Invaders have just bombed you out of the game!

## The Complete Circuit

Figure 3 gives the complete circuit for the joystick interface. As before, A8 to A15 are encoded by IC5 to give three address lines for the memory, IC6, a 6116 2K by 8-bit static CMOS RAM. IC3 and IC4 are 2-into-1 multiplexers connected as electronic switches — when SELECT (S) is at logic 0 the A inputs are connected to the outputs, and when at logic 1 the B inputs are selected.

First consider how the memory is programmed. To do this, an OUT command is given along with an address (on the ZX81 this command can only be given in machine code — there is no OUT command in ZX81 BASIC). The address must have both A0 and A7 low; A0 is always low for a keyboard read while A7 must be held low to avoid the Joystick memory

being accidentally written to by the CPU when it gives control signals to the logic circuitry.

The OUT command sends both  $\overline{\text{IORQ}}$  and WE low. Since WE is connected to the select line on the multiplexers IC3 and 4, the A inputs are selected, and in particular Y1 is connected to A7 and is thus at logic 0. This means that IC1a has all zero inputs and so gives out a logic 1. Then, since one of the inputs to IC2a is WE, at logic 0, its output is at logic 1; therefore IC2b has both inputs at logic 1 and so it gives a 0 output. Thus IC6's CS pin is taken low, enabling the RAM. And, since the output of IC2c is a 1, BUF is 0 and the buffer outputs are open circuit, this allows data to be read into the memory from the data lines via R2 - R6.

Now consider what happens when the computer tries to read the keyboard. When the joystick is not being used it is important that the keyboard functions normally, and it is the function of IC1b to detect whether

or not the joystick is being used. When the joystick is not being used, IC1b has all zero inputs and so gives a 1 output. D1 and R1 are included because IC1b has only five inputs while the joystick has six outputs; D1 and R1 form a hardware OR gate, thereby reducing the number of inputs to the IC1b. So, when the CPU tried to read the keyboard  $\overline{\text{IORQ}}$  is 0 and WE is at 1; this, combined with the 1 from IC1b, gives a 0 on IC2a which gives a 1 at the output of IC2b. This takes the BUF line to 0 and the buffers are not selected, allowing the keyboard to be read normally.

When the joystick is being used, at least one of the inputs to IC1b is high and so its output is low, and this gives a 1 at the output of IC2a. Now, because WE is 1 during a keyboard read Y1 is connected to 1B and hence is at logic 0. Thus all the inputs to IC1a are 0 and so its output is at logic 1. Then the two 1 inputs at IC2b give a 0 output, selecting the memory, IC6. And, since IC2c is outputting a 0, BUF is at logic 1 and the output from the



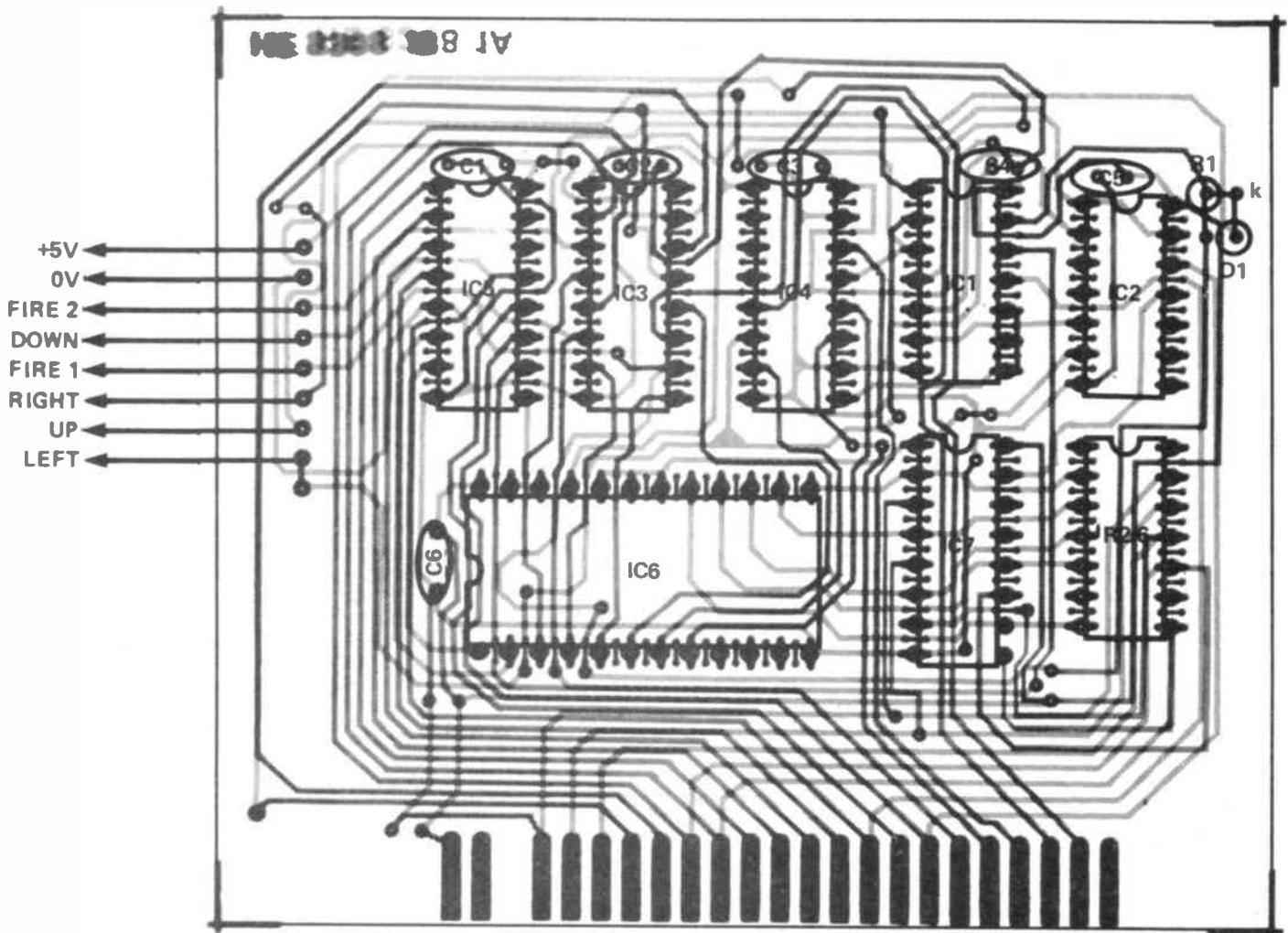


Figure 4. The component layout shown over the double-sided PCB patterns (the component-side tracks are in red). The Controller PCB plugs into a motherboard which carries the correct edge connector for whichever computer is being used. The Spectrum motherboard (not shown) also carries a 5V regulator circuit.

## Parts List

### RESISTORS

R1 - R6 ..... 470R

### CAPACITORS

C1 - C7 ..... 100n  
disc ceramic  
C8, C9 ..... 22u 16V  
radial electro

### SEMICONDUCTORS

IC1 ..... 74LS260  
dual 5-in NOR  
IC2 ..... 74LS00  
quad 2-in NAND  
IC3, 4 ..... 74LS157  
quad 2-in selector  
IC5 ..... 74LS148  
8-into-3 decoder  
IC6 ..... 6116  
2K x 8-bit CMOS static RAM  
IC7 ..... 74LS365  
hex tri-state buffer  
IC8 ..... 7805  
+5V regulator

### MISCELLANEOUS

PCB; motherboard, wire, solder etc.

BUYLINES ..... page 34

memory is buffered onto the data lines, overwriting the keyboard data.

## Construction

The interface is built on two double sided PCBs. The main board plugs vertically into a smaller motherboard, which plugs into the edge connector; the main board is the same for the ZX81, Spectrum and Jupiter Ace, while the three motherboards are different. The ZX81 and Ace motherboards provide their own edge connectors so that rampacks may be plugged on, while the Spectrum motherboard has its own power supply — this is needed because the 48K Spectrum cannot supply enough current for the joystick interface. The interface actually needs very little power, but even the little that it does draw would be enough to make the Spectrum unreliable if the extra supply were not provided.

Construction of the main board is relatively easy — but take care with the 6116 memory. Since it is a CMOS IC it can be damaged quite easily by static charges. It has internal protection diodes which are effective up to about 4,000V, but since you can quite easily generate over 10,000V simply by walking on a nylon carpet

you can destroy it simply by touching the pins! To avoid damage make sure that you don't remove the chip from its protective conductive foam until you are ready to use it, and earth yourself (eg by touching a water tap) before handling it.

## Testing

When you have finished building the main board, plug it into the motherboard, plug the joystick onto the computer edge connector and plug the joystick into the DIN socket in the main board. Now switch on the computer — it should behave normally. Now move the joystick into the UP position and try the keyboard. The keyboard should be completely inoperative, since it is being overruled by the joystick. Test the other joystick positions to make sure that the keyboard remains inoperative.

## Software

Consider the BASIC program given in Program 1 written for the Spectrum. It is a much simplified version of the complete joystick program, but it clearly demonstrates the ideas involved.

The program first accepts an input,

J, a number between 1 and 6, corresponding to the joystick position which is to be programmed — 1 corresponds to UP, 2 to DOWN, 3 to LEFT, 4 to RIGHT, 5 to FIRE 1, and 6 to FIRE 2. It then asks you to press a key, so that when the joystick is moved into the appropriate position *it will be as though that key has been pressed*. Say, for instance, that you enter 1 for the joystick position and then press "Q" for the key. Then, whenever the joystick is moved into the up position, the computer will believe that "Q" has been pressed.

Line 40 simply waits for you to press the key before entering the next section, a FOR/NEXT loop which reads the keyboard and then transfers the data to the joystick memory. The variable N counts through each row of the keyboard in turn; let's consider the case where J = 1 and it is the first time through the loop, when N = 8. Then the address, A in line 60 is equal to  $65280 - 2\uparrow J + 2$ , which in binary is 1,111 1110 0000 0010. This address has A0 = 0, which it must have for a keyboard read, and in addition the higher address lines (A8 to A15) are set to read the row SHIFT to V on the keyboard (see Figure 1 again!). So, in line 70, "IN A" reads this line on the keyboard and "OUT A" transfers this to the joystick memory — and puts it into the memory location which has A1 = 1. So later,

## PROGRAM 1

```

10 INPUT "Which joystick position?",
J
20 PAUSE 50
30 PRINT "Press the key
corresponding to this position — and
keep your finger on the key"
40 IF INKEY$ = "" THEN GOTO 40
50 FOR N = 8 TO 15
60 LET A = 65280 - 2↑N + 2↑J
70 OUT A, IN A
80 NEXT N
90 CLS
100 PRINT "Now take your finger off
the key"
110 IF INKEY$ <> "" THEN GOTO 100
120 CLS
130 GOTO 10
    
```

when the computer tries to read this line of the keyboard and the joystick is in the up position, A1 will again be 1 (since it is coming from the joystick) and the joystick memory will output the data that had been transferred to it during the OUT operation. The counter N scans through the entire keyboard, making each of the address lines A8 to A15 low in turn, and transferring the keyboard data to the joystick. The overall result is that the joystick saves a copy of the keyboard which it will later output when the joystick is moved into the appropriate position.

This program seems to do

everything we require, but it does suffer from two faults. The first problem is simply that it won't work with the BREAK key; as soon as this key is pressed the Sinclair BASIC monitor breaks out of the program and data is not transferred to the joystick. The only solution is to write the program in machine code, where it is safe from the BASIC monitor. The second problem is more difficult to cure. It arises whenever two or more functions are used on the joystick at the same time, for example when the joystick is moved into the UP position and FIRE button 1 is pressed. This sends both A1 and A5 high at the same time, but since the memory location this corresponds to has not been programmed, the joystick will not work. The answer is to rewrite the simple program, making it into two parts; the first part reads the keyboard, line by line, and saves the data for the second part which transfers the data to the joystick, filling up every memory location with the appropriate data. The software tape which is being supplied with the Joystick kit (see Buylines for details) actually contains three complete programs, one each for the ZX81, Spectrum and Ace. They are all very easy to use and are able to remember which keys are used by which programs, so you need only program the Joystick once for each game.

HE

## WHY WRITE TO LONDON

When you can walk to the Midlands largest selection of DIY.

Plugs, sockets, connectors, cable, flex, leads, boxes, Aerials, styli, components, elements, semi-conductors, meters.

**In fact the lot!**

Spares and repairs for all electronic, electrical and audio.

**H. G. Electronics Co.**  
1350 Stratford Road, Hall Green,  
Birmingham B28 9EH  
Telephone: 021-777 2369



## Modem Kit Only £39.95

- \* CCITT standard
- \* 300 baud full duplex
- \* Direct connection:- greatly reduces data loss associated with acoustic couplers
- \* Powered from phone lines therefore no power supply required
- \* Opto coupled data in and data out for intrinsically safe operation

Build it yourself for £39.95 including VAT and postage (note — case not included).

Racom Ltd, Dept. A.  
81 Cholmeley Road, Reading, Berks RG1 3LY  
Tel: 0734 87027

# ALARMS

A  
D  
E

**FREE BOOKLET**  
on  
**BURGLAR ALARMS**  
with  
**LOWEST U.K. DIY PUBLISHED PRICES**  
PHONE OR WRITE FOR YOUR COPY  
**051-523 8440**  
**AD ELECTRONICS**  
217 WARBRECK MOOR  
AINTREE, LIVERPOOL L9 0HU

# RECHARGEABLE BATTERIES

## AND CHARGERS

PRIVATE OR TRADE ENQUIRIES WELCOME  
FULL RANGE AVAILABLE  
SEND SAE FOR LISTS

£1.45 for booklet "Nickel Cadmium Power"

● TRADE PRICES FOR SCHOOLS & COLLEGES ●

**SANDWELL PLANT LTD**  
2 Union Drive, Boldmers, Sutton Coldfield,  
West Midlands 021-354 9764  
After Hours: Lichfield 57977  
Now open Saturday mornings

74 SERIES		74LS11		74LS12		74LS13		74LS98		74LS99																																				
7400	11p	74136	28p	74LS11	13p	74LS244	50p	4041	40p	CA3096	40p	MB3717	25p	ZN419C	190p	MJ4502	£4	2N3702/3	10p	<b>BRIDGE RECTIFIERS</b>	TIL321/2	130p	TIL330	140p	7750/60	200p	<b>DISPLAYS</b>	31015F	200p	DL104	140p	DL707 Red	100p	FND357	120p	FND500	80p	FND507	90p	MAN3640	175p	MAN4640	200p	250p	<b>DRIVERS</b>	9368	250p	9370	300p	UDN6118	320p	UDN6184	320p	<b>PCB MOUNTING RELAYS</b>	6 or 12V DC	8 pin	8p	Col SPDT 2A	180p	14 pin	10p	6 or 12V DC	16 pin	11p	Col DPDT 5A	18 pin	16p	24V DC	20 pin	18p	24V AC	200p	22 pin	22p	6 or 12V DC	24 pin	24p	Col SPDT 10A	28 pin	28p	24V DC	40 pin	30p	<b>WIRE WRAP SOCKETS BY ITI</b>	8 pin	25p	14 pin	35p	16 pin	40p	18 pin	50p	DRP60	120p	20 pin	60p	DRP61	120p	22 pin	65p	24 pin	70p	28 pin	90p	40 pin	100p	<b>OPTO ELECTRONICS</b>	2N577	40p	OC71	10p	DRP12	120p	DRP60	120p	DRP61	120p	TIL78	55p	32 pin	110p	32 pin	110p	40381/2	75p	40408	90p	40410	100p	40411	110p	40594	120p	40595	120p	40673	75p	40871/2	100p	<b>DIODES</b>	8Y127	12p	8YX36300	20p	DA47	9p	DA50/91	9p	DA95	9p	DA200	9p	OA202	10p	1N914	4p	1N916	4p	1N148	4p	1N4001/2	5p	1N4003/4	5p	1N4006/7	7p	1N5401/3	14p	1N5404/7	18p	5920	9p	<b>LEDs</b>	0 125"	55p	TIL209 Red	9p	TIL211	12p	TIL212 Ye	14p	TIL216 Red	18p	0 -	TIL200 Red	10p	TIL222 Gr	12p	TIL228 Ye	14p	Rectangular LEDs (R, G, Y)	NS58581	570p	TIL311	800p	TIL312/3	110p	<b>SWITCHES</b>	TOGGLE SWITCHES	Sub-miniature	SPT 000p	SPDT 60p	DPDT 70p	Rotary Switches	IP120w, 2P6w, 3P4w, 4P3w 55p	DIGITAL SWITCHES 1xP	Push to make	J.R.G.B.75p	Slide to break (Black)	10p	Push Switch DPDT	10p	Square PCB Switch	85p

**RUGBY ATOMIC CLOCK**  
This Z80 micro controlled clock/calender receives coded time data from NPL Rugby. The clock never needs to be reset. The facilities include 8 independent alarms and for each alarm there is a choice of melody or alternatively these can be used for electrical switching. A separate timer allows recording of up to 240 lap times without interrupting the count. Expansion facilities provided.

Ready Built Unit £145 + £5.00 carr.  
Reprint of ETI articles at £1.00 + s.a.e.

**AS DESCRIBED IN JUNE/JULY/AUGUST ISSUE**

**MICROTRAINER**

Complete Kit £64.00 + £1.00 p&p  
8V 1.8A PSU £7.00 + 70p p&p  
1802 Ref £7.00  
IDEAL for HOBBYISTS - learn and explore the workings of microprocessors and unravel the mystical field of computers. INVALUABLE for training centres, schools and industries - gives effective insight into micros to engineers, electricians etc not directly involved in the computer field. INEXPENSIVE - a truly low cost teaching aid - in fact a short step towards developing new ideas and systems.

**BBC MICRO COMPUTER**  
OFFICIAL DEALER  
Please phone for availability

**BBC Model B £399** (incl VAT) Carr £8/unit  
**Model A to Model B upgrade kit £50**  
**Fitting charge £15**  
Individual upgrades also available  
**WORD PROCESSOR 'VIEW' 16k ROM £52**  
**TELETEXT ADAPTOR £195**  
**WORLDWIDE 8K ROM £39**  
**TORCH Z80 DISC PACK £780**  
Business, Education and Fun Software in stock

**FLOPPY DISC INTERFACE**  
inc. 1.2 O.S. £95 + £20 Installation  
**BBC FLOPPY DISC DRIVES**  
Single drive 5 1/4" 100K £230 + £6 carr.  
Dual drive 5 1/4" 800K £699 + £8 carr.  
**BBC COMPATIBLE DRIVES**  
These are drives with TEACFD50 mechanism and are complete with power supply  
**SINGLE: 100K £180; 200K £250; 400K £330**  
**DUAL: 200K £350; 400K £475; 800K £590**  
**Drive Cables: Single £8 Dual £12**  
**Disc Manual & Formatting Diskette £17.50**

**MICRO TIMER**  
The programmable clock timer is a 6502 based dedicated micro computer with memory and 4 digit 7 segment displays to form an extremely versatile timing device with following features:  
• 24 hour 7 day timer  
• 4 completely independent switch outputs  
• 6 digit 7 segment display output to indicate real time turn off times and reset times  
• Individual outputs to day of week, switch and status LEDs  
• Data entry through a simple matrix pad  
Further details on request  
Complete Kit £56.00 + £1.00 p&p  
PSU £7.00 + 70p p&p  
Construction details supplied

**TECHNOMATIC LTD**  
MAIL ORDERS TO: 17 BURNLEY ROAD, LONDON NW10 1ED  
SHOPS AT: 17 BURNLEY ROAD, LONDON NW10  
(Tel: 01-452 1500, 01-450 6597. Telex: 922800)  
305 EDGWARE ROAD, LONDON W2  
**PLEASE ADD 40p p&p & 15% VAT**  
(Ex.port: no VAT, p&p at Cost)  
Orders from Government Departments & Colleges etc welcome  
Detailed Price List on request  
Stock items are normally by return of post



# COMING SOON TO . . .

# Hobby Electronics

## CABLE AND SATELLITE TELEVISION

Going Up! Coming Down! All Change? Find out about the new directions in communications technology before they appear on the horizon — or under your feet!

## TREMOLEKO GUITAR EFFECT

A small impressive unit, costing little but producing a truly amazing sound effect combining elements of tremolo and echo. This unique new effect for guitarists is exclusive to Hobby Electronics!

## VARIABLE POWER SUPPLY

No matter how great your interest in electronics, two items of equipment are essential: one is a good multimeter, the other is a bench power supply. This one is of the "cheap and cheerful" variety, but it provides a variable voltage between 3 and 30V, with current limiting at 1A1 less than 10mV ripple on the output. For the price, could you ask for more?

## GRIPOMETER

Amaze your friends, astound yourself . . . test the strength of your grip with the HE Gripometer. Can you light up the last LED, and make the tone climb to the top of the scale? Find out when you build this novel project!

## NO-FUSS SOUND PRESSURE LEVEL METER

Calibrating this useful instrument for accurate sound pressure level readings is simplicity itself. The only test equipment needed is an audio signal generator and a voltmeter capable of measurements at frequencies of around 1kHz, say. And if you don't already have them . . . you can build those too!

Please reserve \_\_\_\_\_ copies of the September issue of

Hobby  
Electronics

for

Name .....

Address .....



Hobby  
Electronics

September issue on sale  
at you newsagent  
from 12th August  
Place your order now!

Although these articles are being prepared for the next issue, circumstances may alter the final content.

# H.E. PROJECT KITS

I.C.s  
TRANSISTORS  
CAPACITORS

TOOLS  
RESISTORS  
HARDWARE

CASES  
KITS  
PCBs

# MAGENTA

Make us your No. 1 SUPPLIER OF KITS and COMPONENTS for E.E. Projects. We supply carefully selected sets of parts to enable you to construct E.E. projects. Kits include ALL THE ELECTRONICS and HARDWARE NEEDED. Printed circuit boards (fully etched, drilled and roller tinned) or Veroboard are, of course, included as specified in the original article, we even include nuts, screws and I.C. sockets. PRICES INCLUDE CASES unless otherwise stated. BATTERIES ARE NOT INCLUDED. COMPONENT SHEET INCLUDED. If you do not have the issue of E.E. which includes the project — you will need to order the instruction reprint at an extra 45p each.

Reprints available separately 45p each + p. & p. 45p.

BINCLAIR SOUND BOARD Jun 83 less case	£18.98	LEO VU METER Nov 81 less case	£4.87
TRAFFIC LIGHT TOY June 83 less case	£6.23	MED LINKING WIRE EXTRA	£13.67
BTL LIGHT (car battery indicator) June 83 less case	4.99	REACTOR TESTER GAME Sept 81	£4.96
TACTIC LOGIC PROBE June 83	£7.98	SIMPLE STYLUS ORGAN Nov 81 less case	£12.81
AUTO TESTER May 83	£5.98	METRONOME Nov 81	£12.71
STALL THIEF May 83 (inc relay)	£11.72	TELEPHONE BELL REPEATER Oct 81	£13.67
STEREO VOICE OVER UNIT April 83	£17.82	Mid linking wire extra	14p metre
OPTIONAL MIC PRE AMP April 83 (no case)	£4.28	COMBINATION LOCK Oct 81 less solenoid	£19.65
AUTO POWER DOWN April 83 no case	£6.98	BBY ALARM Oct 82	£8.70
LINEAR OHMMETER Mar 83	£13.55	Fig 8 linking wire	7p metre
LOW RANGE OHMMETER Mar 83	£10.37	'DIANA' METAL LOCATOR Sept 82	£24.90
PHASE FOUR Dec 82	£18.71	REACTOR TESTER GAME Sept 81	£13.67
STEREO NOISE GATE Dec 82	£18.98	VARIABLE BENCH POWER SUPPLY Aug 81	£19.98
TAPE/BLUETOOTH SYNCHRONIZER Dec 82	£21.73	ULTRASONIC BURGLAR ALARM July 81	£5.98
BIG EAR Dec 82	£6.21	ELECTRONIC METRONOME July 81	£4.99
MICROMMETER ADAPTOR Dec 82	£4.98	CONTINUITY CHECKER June 81	£17.96
ODOMETER Nov 82	£14.98	ENVELOPE GENERATOR June 81	£5.33
DIANA V.C.D. Nov 82	£4.99	AUDIO MIXER June 81	£19.48
CS SQUELCH UNIT Oct 82	£9.19	PUBLIC ADDRESS AMPLIFIER March 81	£8.53 each
'JUNIOR' BLOT CAR CONTROLLER Sept 82	£8.60 (less case)	Extra — horn speakers	£4.40
ZX INTERFACE BOARD Sept 82 inc edge con	£11.33	PUZZBOX March 81	£10.96
T.V. 1. FILTER July 82	£5.33	WINDSCREEN WIPER CONTROLLER March 81	£8.20
AUTO WAH June 82 £18.98 inc case or £12.28 less case		TEAM LOCO WHISTLE March 81	£12.98
OR AUTO GREENHOUSE SPRINKLER June 82	£14.38	PHOTOGRAPHIC TIMER March 81	£3.50
less pump and power supply		HEATBEAT MONITOR Feb 81	£2.98
£33.42 less power supply		TWO-TONE TRAIN HORN Feb 81	£5.60 less case
(suitable type below)		MEDIUM WAVE RADIO Feb 81	£8.20
POWER SUPPLY DESIGN 12V 500MA June 82	£9.98	BENCH AMP Jan 81	£10.80
ECHO REVERSE UNIT May 82 Less case	£33.98	NICAD CHARGER Jan 81	£9.71
Economy case WB3		CHUFFER Jan 81, less case	£7.83
DIGITAL THERMOMETER May 82 excluding case + bezel	£19.98	BATTERY CHARGE MONITOR Dec 82	£5.77
AUDIO SIGNAL GENERATOR May 82	£20.98	MEMORY BANK — MINI SYNTHESISER Nov & Dec 80	£29.98
CABLE TRACKER May 82	£9.98	TRANSISTOR TESTER Nov 81	£6.84 inc test leads
DIGITAL CAPACITANCE METER Apr 82	£21.37	GUITAR AMP Nov 80	£2.29
SIGNAL TRACKER Apr 82	£3.98	case (diecast) extra	£2.29
BIKE ALARM Apr 82	£11.74	INTRUDER ALARM Oct 80	£20.98
DIGITAL DICE Mar 82	£7.29	TOUCH SWITCH Sept 80	£2.75 less case & contacts
BI-CYCLE BIREN Mar 82	£10.89	GUITAR PHASER Sept 80	£16.28
NOISE FREE FUZZ Feb 82	£10.45	BOUND OPERATED FLASH TRIGGER July 80 no aht	£6.33
MASHHEAD AMPLIFIER Feb 82	£14.74	POG HORN June 80	£6.64
ORUM SYNTHESIZER Dec 81, Full kit	£21.37	SPEED CONTROLLER FOR R/C April 80	£17.56 (less case)
GUITAR HEADPHONE AMPLIFIER Dec 81	£3.72	DIGITAL FREQUENCY METER April 80	£39.98
IN CAR CASSETTE POWER SUPPLY Dec 81	£4.77	GUITAR TUNER Nov 79	£12.82
SCRATCH FILTER Nov 81 Mono	£8.98	CAR ALARM Feb 79	£12.91
Stereo	£8.98		

## BOOKS: ELECTRONICS & COMPUTING

205 First Book of Hi-Fi Loudspeaker Enclosures	£0.95	Semiconductor Data Book Newnes	£6.95
221 28 Tested Transistor Projects	£1.25	Basic Electronics Theory and Practice	£7.98
223 50 Projects Using IC CA3139	£1.25	Microprocessor for Hobbyist	£4.75
225 A Practical Introduction to Digital IC's	£2.28	Burglar Alarm Systems	£3.90
226 How to Build Advanced Short Wave Receivers	£1.95	Electronics: Build and Learn	£3.90
228 Essential Theory for the Electronic Hobbyist	£1.95	Electronic Projects in Music	£3.90
BP39 50 (FET) Field Effect Transistor Projects	£1.75	Electronic Projects in Photography	£3.90
BP40 Digital IC Equivalents and Pin Connections	£3.50	Electronic Projects in Home Security	£2.70
BP41 Least IC Equivalents and Pin Connections	£3.50	Electronic Projects in the Car	£3.90
BP42 50 Simple L.E.D. Circuits	£1.90	20 Solid State Projects Car and Garage	£4.80
BP43 How to Make Walkie-Talkies	£1.95	110 Electronic Alarm Projects	£8.98
BP45 Projects in Opto-Electronics	£1.95	Computing is Easy	£4.25
BP47 Mobile Diacophone Handbook	£1.35	81 Users Handbook	£5.75
BP48 Electronic Projects for Beginners	£1.95	ZX81 Basic Book	£5.45
BP49 Popular Electronics Projects	£1.95	Byteing Deeper into Your ZX81	£6.48
BP56 Electronic Security Devices	£1.95	The ZX Spectrum Explored	£6.48
BP58 50 Circuits Using 7400 Series IC's	£1.75	24 50 CMOS J.C. Projects	£1.35
BP59 Second Book of CMOS IC Projects	£1.50	BP24 52 Projects Using IC 741	£1.25
BP61 Beginners Guide to Digital Techniques	£0.25	BP44 IC555 Projects	£1.35
BP70 Transistor Radio Fault Finding Chart	£0.50	BP50 IC LM3900 Projects	£1.35
BP71 Electronic Household Projects	£1.75	BP65 Single IC Projects	£1.50
BP75 Electronic Test Equipment Construction	£1.78	BP69 Electronic Games	£1.78
BP78 Practical Computer Experiments	£1.75	BP72 A Microprocessor Primer	£1.78
BP79 Radio Control for Beginners	£1.75	BP73 Remote Control Projects	£1.95
BP80 Popular Electronic Circuits — Book 1	£1.75	BP74 Electronic Music Projects	£1.78
BP81 Electronic Synthesiser Projects	£1.75	BP76 Power Supply Projects	£1.75
BP82 Electronic Projects Using Solar Cells	£1.95	BP83 VMOS Projects	£1.95
BP85 International Transistor Equivalents Guide	£2.98	BP84 Digital IC Projects	£1.95
BP87 Simple L.E.D. Circuits — Book 2	£1.35	BP86 How to Use OP-Amps	£1.95
BP92 Easy Electronics — Crystal Set Construction	£1.95	BP90 Audio Projects	£1.95
BP94 Electronic Projects for Cars and Boats	£1.95	BP93 Electronic Timer Projects	£1.95
BP98 Popular Electronic Circuits — Book 2	£2.25	BP95 Model Railway Projects	£1.95
BP101 How to Identify Unmarked IC's	£0.65	BP97 IC Projects for Beginners	£1.95
BP103 Multi-Circuit Board Projects	£1.95	BP98 Mini Matrix Board Projects	£1.95
BP105 International Diode and Transistor Projects	£2.28	BP105 Aerial Projects	£1.95
BP109 The Art of Programming the 1K ZX81	£1.95	BP106 Modern OP-AMP Projects	£1.95
BP114 The Art of Programming the 16K ZX81	£2.50	BP115 The Pre-Computer Book	£1.95
BP119 The Art of Programming the ZX Spectrum	£2.50		

292 Handbook of Integrated Circuits (IC's) Equiv. & Substitutes	£1.95	AY3-8912 I.C. £5.95	
222 Solid State Short Wave Receivers for Beginners	£1.25	ZX81 edge connector	£2.25
227 Beginners Guide to Building Electronics Projects	£1.95	ZX81 edge plug	£1.50
BP1 First Book of Transistor Equivalents and Substitutes	£1.50	ZX Spectrum edge connector	£2.55
BP14 Second Book of Transistor Equivalents and Substitutes	£1.75	SINCLAIR SOUND BOARD KIT A5	June 83 H.E. complete (less case) £18.98.
BP27 Chart of Radio, Electronic, Semi-conductor and Logic Symbols	£0.50	Reprint extra 45p	
BP32 How to Build Your Own Metal and Treasure Locations	£1.95		
BP36 50 Circuits Using Germanium, Silicon and Zener Diodes	£1.50		
BP37 50 Projects Using Relays SCRs and TRIACS	£1.95		
BP51 Electronic Music and Creative Tape Recordings	£2.28		
BP53 Practical Electronics Calculations and Formulae	£2.95		
BP57 How to Build Your Own Solid State Oscilloscope	£1.95		
BP60 Practical Construction of Pre-amp, Tone Controls, Filters & Attr	£1.45		
BP66 Beginners Guide to Microprocessors and Computing	£1.78		
BP67 Counter Drive and Nueral Display Projects	£1.95		
BP68 An Introduction to BASIC Programming Techniques	£1.95		
BP107 30 Solderless breadboard Projects — Book 1	£2.28		
BP110 How to Get Your Electronic Projects Working	£1.95		
BP117 Practical Electronic Building Blocks — Book 1	£2.28		
Elementary Electronics: Siaddin, Excellent theory and 35 constructional projects. Uses S-Dec. First steps to CSE level interfacing to microprocessors and microcomputers	£3.95		
	£6.75		

### ZX SPECTRUM AMPLIFIER

250mW output. Volume control. Internal speaker. Very simply connected using load/save lead. Puts real power even into the simplest "Beep" commands. Adds a real "zing" to musical programs and games. Requires PP3 battery — not supplied. Very low current drain. Supplied ready built complete with demo software and instructions.

ORDER AS: ZX SPECTRUM AMPLIFIER (SAHE) £6.98

### ZX SPECTRUM SUPER AMPLIFIER

250mW output. Now add synthesizer quality to those "Beep" commands. Supercircuit with adjustable ATTACK, SUSTAIN and DECAY envelope controls. Plus variable ECHO. Generates a wide range of special effects. Five graduated controls. Internal speaker. Very smart case. Requires batteries — not supplied. Very low current drain. Ready built complete with demo software and instructions.

ORDER AS: ZX SPECTRUM SUPER AMPLIFIER (SSAHE) £17.98

## SOLDERING/TOOLS

ANTEX X5 SOLDERING IRON 25W	£5.48
SOLDERING IRON STAND	£1.98
SPARE BITS. Small standard, large.	65p each
For X5 + X25	
SOLDER Handy size	99p
SOLDER CARTRON	£1.84
DESOLDER BRAID	£1.99
HEAT SINK TWEEZERS	29p
DESOLDER PUMP	£6.48
HOW TO SOLDER LEAFLET	12p
LOW COST CUTTERS	£1.69
LOW COST LONG NOSE PLIERS	£1.68
WIRE STRIPPERS & CUTTERS	£2.69
PRECISION PETITE	
12V P.C.B. DRILL	£11.67
DRILL STAND	£7.98
GRINDING STONE	50p
GRINDING WHEEL	50p
SAW BLADE	85p
BRASS WIRE BRUSH	50p
8URR	50p
VERO SPOT FACE CUTTER	£1.49
pin insertion tool	£1.98
VEROPINS (pk of 100) 0.1"	52p
MULTIMETER TYPE 1 (1.00 dpp)	£5.48
CROCODILE CLIP TEST LEAD SET.	
10 leads with 20 clips	99p
REPRODUCTION COLOUR CODE CALCULATOR	21p
CONNECTING WIRE PACK TYPE ED.	
11 colours	48p
ILLUMINATED MAGNIFIERS	
Small 2" dia. (5 x mag)	£1.14
Large 3" dia. (4 x mag)	£2.40
CAST IRON VICE	£2.98
SCREWDRIVER SET	£1.98
POCKET TOOL SET	£3.98
DENTIST INSPECTION MIRROR	£2.85
JEWELLERS EYEGLASS	£1.50
PLASTIC TWEEZERS	77p
PAIR OF PROBES WITH LEADS (cc)	69p
Q MAX PUNCHES	
¼" £2.98; ½" £3.06; ¾" £3.17; 1" £3.24	



MULTIMETER TYPE 2 (VNS807) PK of p.v. with transistor tester. £14.75 AC & DC volts DC current 4 very useful resistance ranges. We've used it and we like it!



HELPING HANDS JIG £6.30 Heavy base. Six ball and socket joints allow infinite variation of clips through 360°. Has 2 1/2" diameter (2.5 magnifier attached), used and recommended by our staff.

Speakers min 8 ohm 87p; 64 ohm 89p; 80 ohm 95p	Brimboard breadboard	£6.98
Crystal earpiece	Verobloc breadboard	£4.20
Magnetic earpiece	PCB etching kit	£2.98
Stethoscope attachment	ZX81 edge connector	£2.25
Mono headphones	Ferrite rod 5 inch	59p
Stereo headphones	PP3 clips	10p
Min buzzer pick up coil	PP9 clips	11p
Euro breadboard	2 station Intercom	£6.75
S Dec breadboard	IC sockets 8 pin 16p; 14 pin 17p	16 pin 18p

### ADVENTURES WITH MICROELECTRONICS

Similar to 'Electronics' below. Uses I.C.s. Includes dice, electronic organ, doorbell, reaction timer, radio etc. Based on Bimboard 1 bread board. Adventures with Microelectronics £2.98. Component pack £29.64 less battery.

### ADVENTURES WITH DIGITAL ELECTRONICS

Entertaining and instructive. Includes details of some digital ICs and 8 projects: shooting gallery, 2 way traffic lights, electronic adder, computer space invaders game etc. No soldering. Adventures with Digital Electronics book £3.25. Component pack including breadboards £42.50 less batteries.

### ADVENTURES WITH ELECTRONICS by Tom Duncan

An easy to follow book suitable for all ages. Ideal for beginners. No soldering, uses an S-Dec breadboard. Gives clear instructions with lots of pictures. 16 projects — including three radios, siren, metronome, organ, intercom, timer, etc. Helps you learn about electronic components and how circuits work. Component pack includes an S-Dec breadboard and all the components for the projects. Adventures with Electronics £2.85. Component pack £18.98 less battery.

### 30 SOLDERLESS BREADBOARD PROJECTS

Book 1 by R.A. Penfold. Clear verobloc layouts and circuit diagrams. Includes fuzz box, radio, metronomes, timers, transistor checker, switches etc. Introduction gives basic information on components including resistors, capacitors, I.C.s, transistors, photocells etc. Ideal for beginners as well as those with some experience. Complete kit including verobloc, book and components (less batteries) £24.75. Less book £22.50, less verobloc £20.25. Book only £2.25.

### MORE KITS AND COMPONENTS IN OUR LISTS

FREE PRICE LIST Price list included with orders or send sae (9 x 4) CONTAINS LOTS MORE KITS, PCBs & COMPONENTS

### ELECTRONICS CATALOGUE

Illustrations, product descriptions, circuits all included. Up-to-date price list enclosed. All products are stock lines for fast delivery. Send 80p in stamps or add 80p to order. FREE to Schools/Colleges requested on official letterhead.

MAGENTA gives you FAST DELIVERY OF QUALITY COMPONENTS & KITS. All products are stock lines and are new & full specification. We give personal service & quality products to all our customers — HAVE YOU TRIED US?

### MAGENTA ELECTRONICS LTD.

Magenta Electronics Ltd, HA39, 135 Hunter St., Burton on Trent, Staffs, DE14 2ST. MAIL ORDER ONLY. 0283 65435. Mon-Fri 9-5. Access/Barclaycard (visa) by phone or post. Add 45p P&P to all orders. Prices include VAT. SAE all enquiries. Official orders welcome. OVERSEAS. Payment must be in sterling. IRISH REPUBLIC and BFPO UK PRICES. EUROPE: UK Prices plus 10%. ELSEWHERE: write for quote.

# ALL ABOUT ELECTRONICS

Our new Beginner's Series tells you all you'd like to know about electronics. From start to finish, all about components and circuits, all the theory you need to get started in the world of electronics.

Keith Brindley

## The Story So Far

Last month, we looked at electricity itself: what it is (a flow of electrons) and its three fundamental quantities (potential difference, current, resistance) which are tied together in a physical way defined by Ohm's Law. Put into mathematical formulae, Ohm's Law can be expressed by:

$$V = IR$$

$$I = V/R$$

$$R = V/I$$

So, if two of the quantities in any electronic circuit are known, the third can easily be calculated.

There are two main types of electricity: DC (direct current), where the potential difference, or voltage, remains constant — this is the sort of electricity which is obtained from a dry-cell battery — and AC (alternating current), where the potential difference alternates between two extremes. House electric systems are AC and here the voltage alternates between equal positive and negative amounts to give an overall voltage of 240V.

We saw that electricity need not always consist of large currents and large voltages, hence the need to divide the units of current (the ampere) and voltage (the volt) up into smaller parts, such as a microamp:

$$\text{ie, } 1 \times 10^{-6} = \text{A}$$

or, say, a millivolt:

$$\text{ie, } 1 \times 10^{-3} = \text{V}$$

Voltages and currents such as these are the sorts which we may find from such a device as a microphone which converts sound waves into electricity. We tend to call such voltages and currents *signals*

— they represent the sound in an electrical way, just a traffic signals represent what to do next in a way which the motorist can understand. Now that we have seen exactly what electricity is, we're going to turn our attention to what electricity does. In other words, we are going to study the main effects of electricity.

## Let There Be . . . Heat!

The first effect, observed every day when a light bulb is turned on is the creation of heat. Any conductor, if a high enough potential difference is applied across it, will conduct enough electricity to get warm. The thinner the conductor, the lower the potential difference it takes to heat it. What happens in a light bulb is that the conductor (known as the filament) is so thin that it doesn't take much electricity to heat it up. And it gets hot! So hot that it radiates enough energy to glow white hot — in other words, it gives off light.

Heat is also dissipated from the bar of a bar fire or a ring of an electric cooker, but here the electricity used only makes the bar or ring glow red hot — *even though more electricity is used and more heat is given off than with a light bulb filament.*

The reason for this generation of heat is connected with the very reason why electricity flows at all, ie, because the atoms of conductors allow their electrons reasonably free movement. The key phrase here is "reasonably free movement". No atom gives up its electrons without a struggle, however good a conductor it is and force (or energy) is always required to take the electron away from the atom. The potential difference applied across the conductor provides this energy by literally pulling the electrons out of orbit towards the positive side of the voltage source. When the electron jumps along to the next atom to take its place in

'orbit', some of that energy is then given off and is released as heat (Figure 1).

## Thick And Thin

In a large mass of conducting material the effect of these small heat releases is to raise the temperature only by a small amount. In a thin conductor, however, the temperature obviously rises more dramatically with the same potential difference, even though the actual power released is identical. So, light bulbs are manufactured with a very thin filament so that only a small amount of power is used up or dissipated for the amount of light emitted.

Naturally, there is a mathematical relationship between the amount of electricity and the power dissipated as heat. It is summarised by a formula which can be used to calculate the power dissipated by any conductor with a voltage across it:

$$P = IV \text{ (measured in watts)}$$

So, for example, a potential difference of 100V across a conductor, with a current of 10A through it, would mean that the conductor will dissipate a power of:

$$100 \times 10 = 1000 \text{ watts} = 1\text{kW} \\ \text{(ie, one kilowatt)}$$

But, from Ohm's Law we know that  $V = IR$  and  $I = V/R$ . So also:  $P = I^2R = V^2/R$ .

This means power is also dissipated by a resistor in a circuit, not just a conductor, and we can calculate the power dissipated by that resistor if we know its value and the value of the current through it, or the voltage across it. Enough said for now, but next month when the whole topic of resistance is discussed in depth, you'll see how the question of power plays an important rôle in our choice of resistor in a given electronic circuit.



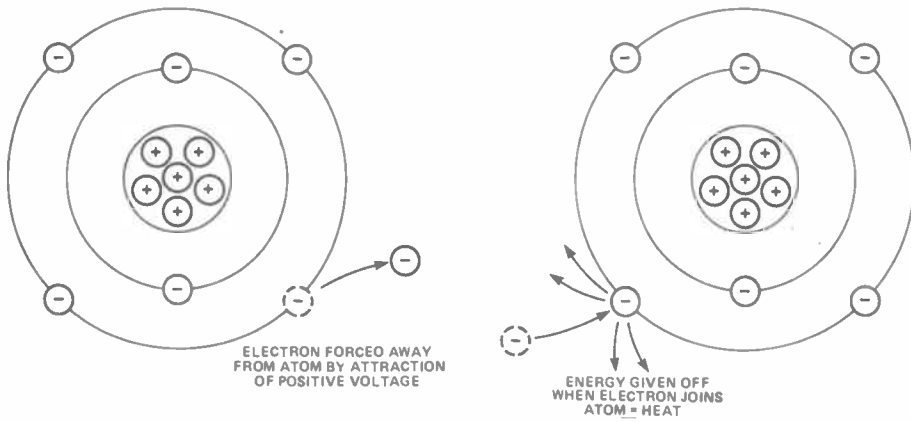


Figure 1. An electron can be forced away from its atom with the application of a voltage, but the energy used to force it away is released when the electron finds another atom with a missing electron.

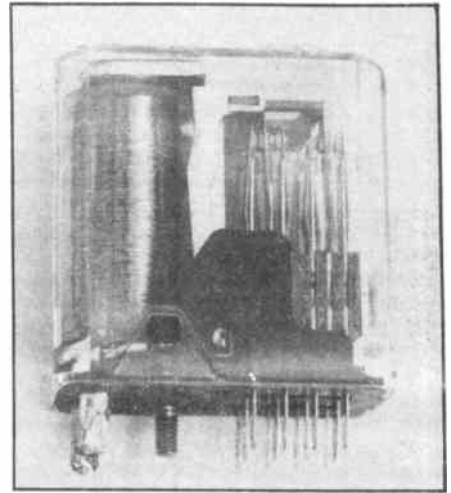


Figure 6. A relay can be used to switch currents (some relays have as many as 10 sets of switch contacts) upon application of a small current to pass through the coil.



Figure 2. When the circuit is completed the needle of the compass will jump to a new position. As the circuit is disconnected the compass needle will once again point north.

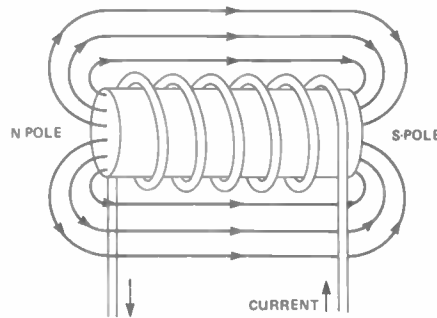


Figure 5. Reversing the direction of the electric current reverses the magnetic field.

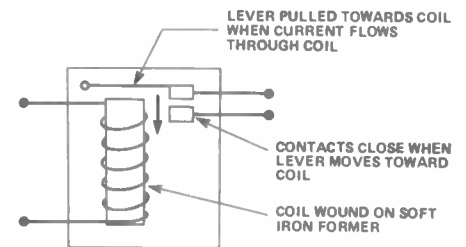


Figure 7. Inside a typical relay.

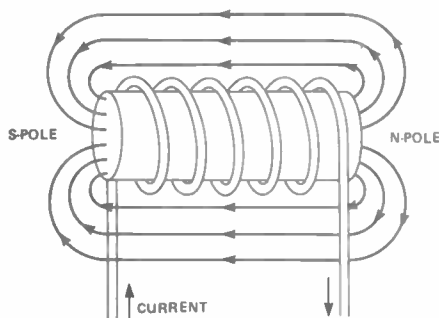


Figure 3. When current passes through a coil of wire, the electromagnetic field is stronger than that from a single length of wire. A north- and south-pole are generated.

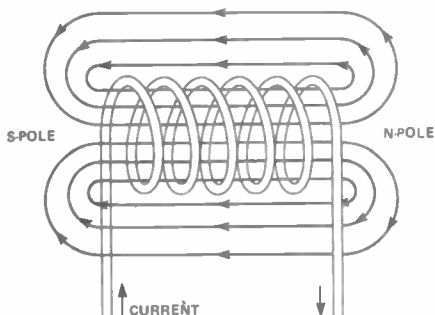


Figure 4. Winding the coil around a soft iron former concentrates the electromagnetic field.

### Electromagnetism

The second effect of electricity we shall now look at is the magnetic field which is formed whenever a current is passed through a conductor. You can 'see' this magnetic field if you have a magnetic compass, a battery, a bulb and connecting wire. Simply position the compass close to the middle of the length of wire (Figure 2) and then connect the two ends of the wire to the battery. As you connect the circuit the compass needle will jump, then steady. Similarly, when you disconnect the wire, the needle of the compass will once again jump, then steady and point north.

This magnetic field is caused, like heat, by the energy electrons give off when jumping back to an atom. It is termed *electromagnetic* radiation to distinguish it from magnetic radiation from a permanent magnet (eg, bar-magnet, horseshoe-magnet) — electromagnetic radiation only occurs in a conductor when an electric current is flowing.

If you do the experiment in Figure 2 you will see that the field generated is not a very powerful one. It might have caused the compass needle to move but it certainly would not have been strong enough to pick up a piece of metal, a pin for example. One way to increase the field should be obvious: increase the current. But there is a limit to how much current is available from a power source

such as a battery. A better way to increase the magnetic field is to loop the wire into a coil, as in Figure 3. Each turn of the wire radiates its own field and the total effect is to create a magnet which is *n* times as strong as the single wire, where *n* is the number of loops in the coil.

### Loop The Loop

Another way to create a stronger magnetic field is to form this loop around a metal core (soft iron is best). The soft iron core (Figure 4) concentrates the field, producing a stronger electromagnet. Figure 4 shows how the coil is now effectively a single magnet with the usual north (N) and south (S) poles. When the current flows as shown, ie, anti clockwise, the north pole is at the right hand end of the electromagnet. However, if the current flows clockwise as in Figure 5 the poles reverse ends!

We have now seen the magnetic field which is generated around a conductor with a current flowing and the next question must be to ask, how can we use this effect? After all, an electromagnet is an electromagnet and by itself it must have only limited use. The most important use in the form is probably in a relay, an example of which is shown in Figure 6. Such a relay has an electromagnetic coil inside, which is operated by a specific voltage and

current. When current flows through the coil it creates a field which pulls a lever towards it (Figure 7) activating switch mechanisms. The current to activate the coil is small but the current which is switched by the switch mechanism can be large and at a high voltage. So, for example a relay can be used to turn on and off a 240V mains-powered heater with only a 9V battery as in the circuit in Figure 8.

Undeniably though, electromagnetism doesn't seem to offer much until we consider the electromagnet in use alongside another, say a permanent magnet. If we remember the statement "like poles repel, opposites attract", then we can begin to understand the real usefulness of being able to switch magnetism, the force that pulls opposite poles together and pushes like poles apart, on and off at will.

## Testing, Testing

The single conductor and compass experiment of Figure 2 shows such a force making the needle of the compass (a permanent magnet) jump. Obviously, if we take our coil of wire formed around a soft iron core and pass a current through it, then put it beside a strong permanent magnet, the force between the two magnets will be a lot stronger. And, more important, because the strength of the electromagnetic field depends on the current through the coil, the force between the two magnets depends on the current passed through the coil.

This principle is used in the common test meters used everyday in electronics. Figure 9 shows the basic part of a meter. The main items include a permanent magnet, a coil wound on a former, and a pointer attached to the coil. The coil is mounted on bearings so that it can rotate. The magnet's poles are shaped so that the field produced is radial and equal at all points on the coil. A coil-spring ensures the coil always returns to the same position when no current is passed.

When a current is passed through the coil, the electromagnetic field, interacting with the permanent magnetic field, forces the coil to rotate. When the force produced equals the force which the spring exerts against it an equilibrium is set up — in other words, the coil stops turning. The pointer therefore indicates on a scale the strength of the magnetic field produced by the coil and, because the field depends on the current through the coil, the position of the pointer on the scale is an indication of the size of this current.

For accurate measurements, all parts of a meter obviously need to be carefully designed and manufactured, but modern day meters can exhibit full-scale deflection (FSD), ie, the pointer goes from zero to maximum, when currents of only 1 uA or so are passed through the coil. A modern multimeter suitable for a selection of general-purpose test measurements in electronics is shown in Figure 10. This multimeter has a switch in order that

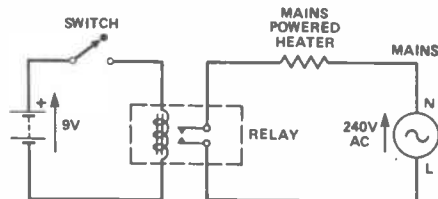


Figure 8. Showing how a relay and a 9V battery can turn a mains-powered heater on and off.

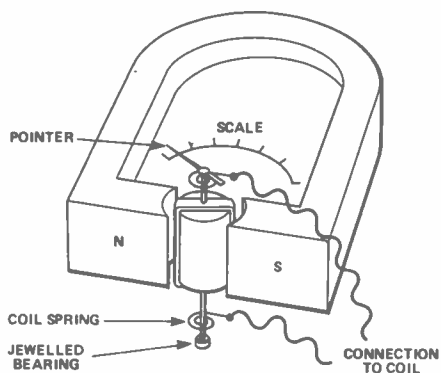


Figure 9. Inside a moving-coil meter.

the measurement range can be changed, so that larger currents can be measured. Also on the switch dial are locations so that voltage and resistance measurements can be taken, all with the same meter!

Now, how can this be done? How can we use the same meter to measure current, voltage and resistance at the flick of a switch? For the answer we must look at some circuits to understand exactly what we are measuring. Then we will see how to measure them.

## Current

Figure 11a shows a circuit of a battery and a resistor. Battery voltage is 10V and the resistor has a value of 10k (ie, 10,000 ohms). So we can calculate, using one of the formulae associated with Ohm's Law, the current in the circuit:

$$I = \frac{V}{R} = \frac{10}{10,000} = 1 \cdot 10^{-3} \text{A} = 1 \text{mA}$$

Figure 11b shows how we measure current. The meter must be part of the circuit — in this way the current actually passes through the meter coil. If the meter has FSD of 1mA then the pointer of the meter will be at its maximum position. If the meter had FSD of 10mA the pointer will be only 1/10th of the way across the scale.

But what happens if the meter has FSD of only 1uA? The pointer will try to go off the scale! The current going through the coil (1mA) is one thousand times greater than the current the coil was designed to withstand and it may "burn-out" ie, the heat generated by the current may actually be great enough to melt one or more of the loops of the coil. Once this occurs a break in the circuit

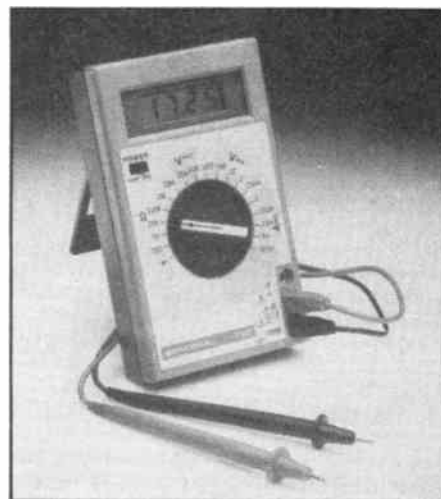


Figure 10. A typical digital multimeter with test probes.

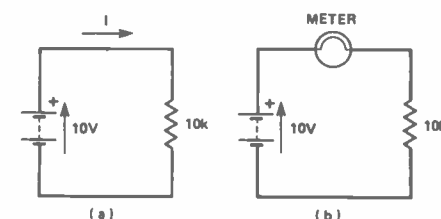


Figure 11a) Current flows when a resistor is connected to a battery b) measuring the current using a meter.

will be made and the meter is ruined. For this reason you must be very careful when using a test meter not to attempt to measure greater currents and voltages than the meter is switched to read at FSD. It is easy to adapt a meter with a very low FSD to measure currents of much greater value as shown in Figure 12a.

The meter can only be used to measure a maximum current of 1uA but the current in the circuit is 1mA (as Figure 11a). So to use this meter we need to sample only 1uA of the 1mA circuit current and bypass the meter with the other 999uA. We do this as in Figure 12b by putting a resistor, R2, in parallel with (ie, across) the meter. The resistance is calculated to allow 999uA through for every 1uA which the meter allows through.

Now the voltage across the meter is the same as the voltage across the meter resistor (because they are joined at both ends — they are in parallel) whatever happens. So from Ohm's Law

$$IR (\text{meter}) = V = IR (\text{resistor})$$

That is, the current through the meter coil multiplied by the coil resistance must equal the current through the resistor multiplied by its own resistance. We know that the current through the meter has to be 1/999 of the current through the resistor so

$$\frac{1}{999} \times R (\text{coil}) = I \times R2$$

So,  $R2 = R/999$  (coil). If the coil resistor

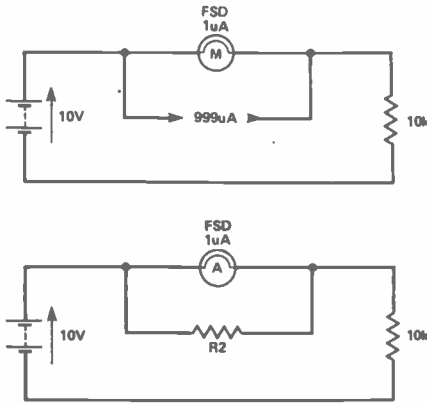


Figure 12 a) measuring a current which is larger than the FSD current of the meter — some of the current has to bypass the meter coil b) a shunt resistor (ie, in parallel) allows some current to bypass the coil

Figure 13 a) The voltage across a resistor b) measuring the voltage using a meter with a series resistor.


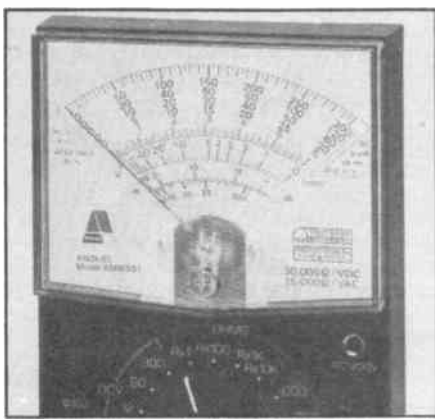


Figure 14. A typical analog multi-meter scale. Note the reverse-reading resistance scale.

Figure 15. A typical use of a meter to measure an unknown resistance value.

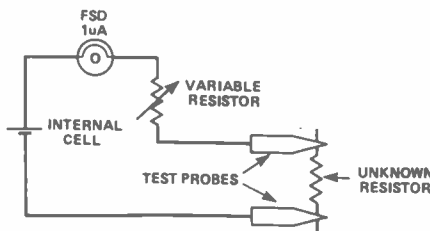

is say 1k, then  $R2 = 1000/999 = IR$ . In this example we must put a resistance (which is 1/999 of the meter coil resistance) in parallel with the meter to let the meter which has FSD of 1uA measure up to 1mA. Other current values can be measured simply by putting another value of resistor, calculated as above, in parallel with the meter. All the switch does in a multimeter such as that of Figure 10 is to connect in a different value resistor for every range of current to be measured.

### Voltage

Voltage measurement is slightly different. The circuits in Figure 13 show why. Say we went to find out the voltage across R2 in Figure 13a. We can calculate the voltage using Ohm's Law if we want, but in such a simple example it is possible to calculate the voltage by introspection. Look at the circuit: there are two equal resistors in the series (ie, in a line) across a source of 10V. So the mid-point of the resistor will have a voltage at the mid-point of the source voltage: 5V.

If we use the same meter as above, ie, with FSD of 1uA and a coil resistance of 1k, then we can calculate from Ohm's Law the current which will pass through the coil if the meter is simply

placed across the resistor to measure 5V:

$$I = \frac{V}{R} = \frac{5}{1,000} = 5\text{mA}$$

(ie, 5000 times the FSD current!)

Obviously such a current will damage the meter, so we need to restrict the amount of current to be no greater than the meter's FSD current (1uA). When we measured large currents using the meter we connected a resistor in parallel to restrict the current flow through the coil. Things are different, however, when we want to measure a large voltage — we add a resistor in series (Figure 13b).

To calculate the value of this resistor we must remember that the aim is to restrict current flow through the meter to 1 A. So the total resistance of the meter coil to the added resistor must only pass 1 A of current. From Ohm's Law therefore,

$$R(\text{total}) = \frac{V}{I} = \frac{5}{1 \times 10^{-6}} = 5 \times 10^6 \text{ ohm} = 5\text{M} (5 \text{ Megohm})$$

The meter coil resistance is 1k so the added resistor should have a value of 4999000 ohms. It is not possible to manufacture a resistor to this sort of accuracy so in fact a resistor of 5M would be used. In a multimeter such as that in Figure 10 different values of

series resistors are switched in to measure different voltage ranges in the same way that different values of parallel resistors are switched in to measure current.

### Resistance

Measurement of resistance is a lot different! A resistor is a passive device: unless a current is passed through it no voltage occurs to be measured and unless a voltage is applied across it no current can be measured, so a meter by itself will not be able to measure resistance. Any multimeter therefore has an internal battery cell to provide voltage and current. The current which passes through the resistor is given by Ohm's Law:

$$I = \frac{V}{R}$$

and the voltage is fixed by the voltage of the cell. So the current which flows is determined by the value of the resistor being measured. If we measure this current, using the meter as we've already seen, the position of the pointer will therefore indicate the value of the resistor.

An important point to note with a multimeter switched to measure resistance is that the current (therefore the pointer position) is inversely proportional to the resistance of the resistor being measured. In other words the meter appears to read backwards — the higher up the scale the pointer is, the lower the value of resistance. This also means that the scale is non-linear, ie, equal amounts of resistance are not equally spaced. An example of a typical multimeter scale is shown in Figure 14. You can see the linear scales of voltage and current and also the non-linear reverse scale of resistance. A typical resistance measuring circuit is shown in Figure 15. The main component to note is the variable resistor in the circuit which allows for varying voltages due to the cell discharging with time and use.

Using a resistance meter (or ohmmeter) is a little bit different to a voltage meter (voltmeter) or current meter (ammeter) in that you first have to set the meter to read zero resistance on the scale, by adjusting the variable resistance when the ohmmeter probes are in good contact. This makes sure that at every resistance reading the varying voltage from the internal cell has been allowed for.

### Safety First

An important characteristic of any meter is its sensitivity, ie, how far the pointer moves for a given current. It is normally expressed in ohms-per-volt (R/V). The more sensitive a meter is, the higher the R/V ratio will be. Any meter can be given such a rating by dividing its FSD current into one volt. For example a 1uA FSD gives:

$$\text{sensitivity} = 1\text{V}/1\mu\text{A} = 1 \times 10^6 \text{ R/V}$$

If you are going to purchase a multimeter for use in electronic











Table 1. Circuits symbols for this month's new components.

Table 2. Standard abbreviations for measurements and values used universally in electronics. It is important to distinguish between capital and lower case abbreviations, as they can mean different things.

Table 2

DC	direct current
AC	alternating current
V	voltage/volts
I	current
R	resistance/ohms
A	amperes/amps
m	$1 \times 10^{-3}$ eg, one milliamp = 1mA
u	$1 \times 10^{-6}$ eg, one microvolt = 1uV
n	$1 \times 10^{-9}$ eg, one nanovolt = 1nV
p	$1 \times 10^{-12}$ eg, one picofarad = 1pF
k	$1 \times 10^3$ eg, one kilovolt = 1kV
M	$1 \times 10^6$ eg, one megohm = 1MR
P	power
W	watts

	bulb		coil
	meter		relay (with 100R coil and one switch contact)
	ammeter		variable resistor
	voltmeter		
	ohmmeter		

measurements, make sure you get one with as high a sensitivity as you can afford. Buy one with a sensitivity of at least 50,000 ohms/volts, preferably 100,000 ohms/volts.

The last thing to remember about multimeters is that there are a few rules you must follow which ensure the meter isn't damaged in any way:


- When you measure a current, voltage, or resistance which is unknown always measure it first on the highest range and step down range by range until you obtain a good measurement. This will make sure that the meter coil is not burned out by too large a current.
- The meter has to be polarised when taking DC voltage and current measurements ie, the negative terminal of the multimeter goes to the more negative side of the circuit and the positive terminal to the more positive side of the circuit. This

prevents the meter pointer going in the reverse direction and being bent or damaged. AC measurements are different, however. A small circuit inside the multimeter converts AC to DC and always makes sure the coil turns in the right direction.

- Resistance measurements must not be taken with the resistor in circuit. A voltage may be present across the resistor when in circuit and too much current may flow through the coil due to this voltage and the coil may be damaged.

Finally, Table 1 gives a list of the new circuit symbols we've met this month and Table 2 lists some common abbreviations in electronics. Learn them well, you will see them time and time again. Next month, we will go deeper into the bits and pieces used in electronics — the components which go together into circuits — and show you how they work.

HE

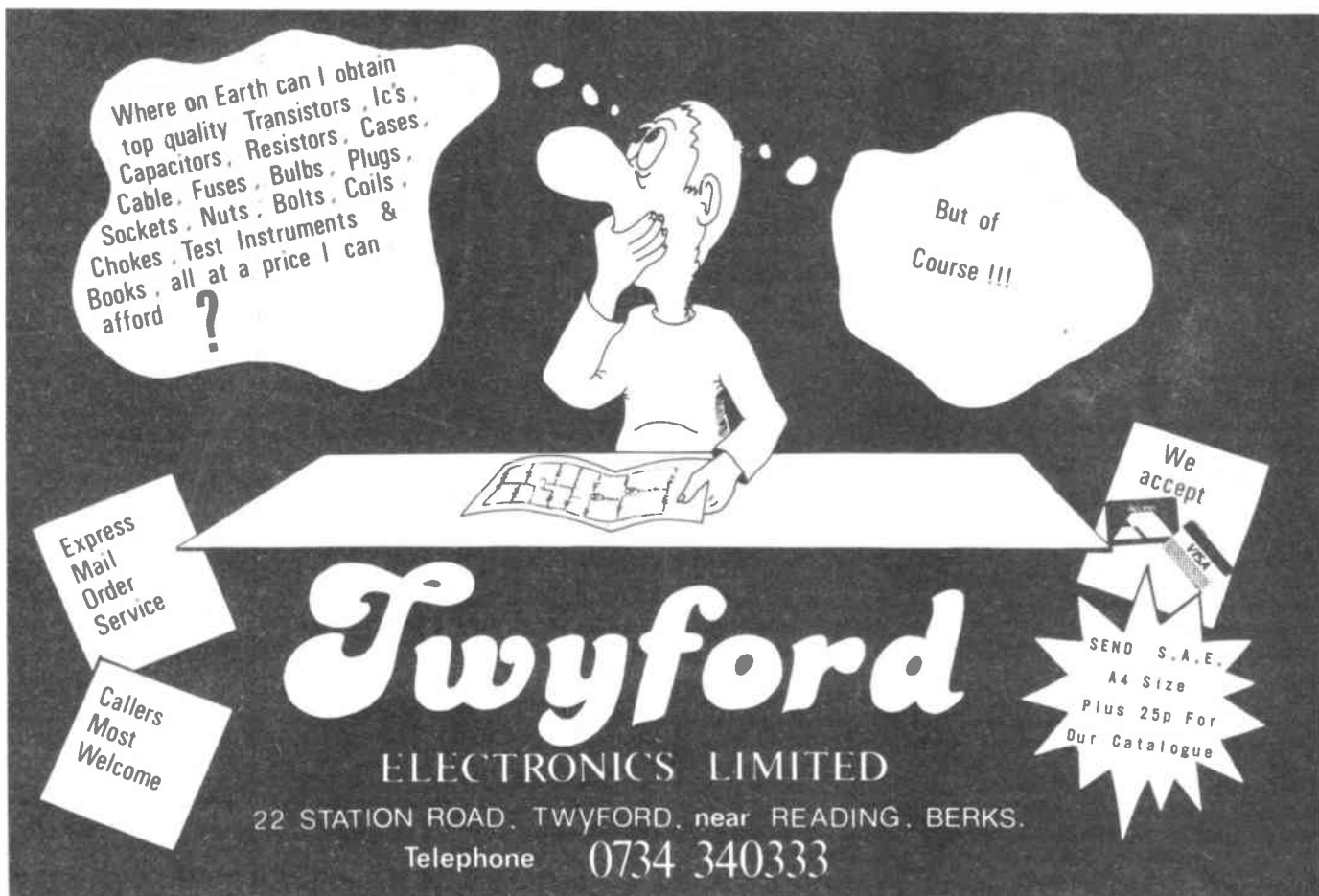

Where on Earth can I obtain top quality Transistors, Ic's, Capacitors, Resistors, Cases, Cable, Fuses, Bulbs, Plugs, Sockets, Nuts, Bolts, Coils, Chokes, Test Instruments & Books, all at a price I can afford?

But of Course !!!

Express Mail Order Service

Callers Most Welcome

**Twyford**  
ELECTRONICS LIMITED

22 STATION ROAD, TWYFORD, near READING, BERKS.  
Telephone 0734 340333

We accept VISA

SEND S.A.E. A4 Size Plus 25p For Our Catalogue

**XK113 MW RADIO KIT**  
Based on ZN414 IC, kit includes PCB, wound aerial and crystal earpiece and all components to make a sensitive miniature radio. Size: 5.5 x 2.7 x 2cms. Requires PP3 9V battery. IDEAL FOR BEGINNERS. **£5.00**

**HOME LIGHTING KITS**  
These kits contain all necessary components and full instructions & are designed to replace a standard wall switch and control up to 300w of lighting.

**TD300K Remote Control £14.30**  
Dimmer Transmitter for above **£ 4.20**

**TD300K Touchdimmer £ 7.00**

**TS300K Touchswitch £ 7.00**

**TDE/K Extension kit for 2-way switching for TD300K £ 2.50**


**LD300K Rotary Controlled Dimmer £ 3.50**



**DVM/ULTRA SENSITIVE THERMOMETER KIT**

This new design is based on the ICL7126 (a lower power version of the ICL7106 chip) and a 3 1/2 digit liquid crystal display. This kit will form the basis of a digital thermometer (only a few additional resistors and switches are required—details supplied), or a sensitive digital thermometer (-50°C to +150°C) reading to 0.1°C. The basic kit has a sensitivity of 200mV for a full scale reading, automatic polarity indication and an ultra low power requirement—giving a 2 year typical battery life from a standard 9V PP3 when used 8 hours a day, 7 days a week

**Price £15.50**



**THE JUPITER ACE MICROCOMPUTER**

**NOW available in stock**

uses FORTH which executes about 10 times faster and requires less program memory than a comparable program using basic. Features 8K ROM, 3K RAM, built in speaker, 40 key keyboard and a 32 x 24 line-flicker free display on TV. Comes supplied complete with leads, mains adaptor, a comprehensive easy-to-follow manual on Forth programming + FREE cassette containing 5 sample programs. **ONLY £75.00** (+ £2.00 carriage + VAT)

**JUPITER ACE SOFTWARE**

**J3 SPACE INVADERS £3.90**  
**J4 SWAMP MONSTERS £3.90**  
**J5 DOT MAN £3.90**

**DRAGON 32 £143 + £7 carriage**  
**ORIC 1 £143 + £2.50 carriage (48K RAM)**

**COMPONENT PACKS**

**PACK 1 650 Resistors 47 ohm to 10 Mohm - 10 per value £4.00**  
**PACK 2 40 x 16V Electrolytic Capacitors 10µF to 1000µF - 5 per value £3.25**  
**PACK 3 60 Polyester Capacitors 0.01 to 1µF/250V - 5 per value £5.55**  
**PACK 4 45 Sub-miniature Presets 100 ohm to 1 Mohm - 5 per value £2.90**  
**PACK 5 30 Low Profile IC Sockets 8, 14 and 16 - pin - 10 of each £2.40**  
**PACK 6 25 Red LEDs (5mm dia) £1.26**

**3-NOTE DOOR CHIME**

Based on the SAB0600 IC the kit is supplied with all components, including loudspeaker, printed circuit board, a pre-drilled box (95 x 71 x 35mm) and full instructions. Requires only a PP3 9V battery and push-switch to complete. AN IDEAL PROJECT FOR BEGINNERS. Order as XK 102.

**£5.00**

**LCD 3 1/2 DIGIT MULTIMETER**  
16 ranges including DC voltage (200 mv-1000 v) and AC voltage, DC current (200 mA-10 A) and resistance (0-2 M) + NPN & PNP transistor gain and diode check. Input impedance 10M. Size 155x88x31 mm. Requires PP3 9V battery. Test leads included **ONLY £29.00**

**ELECTRONIC LOCK KIT XK101**  
This KIT contains a purpose designed lock IC, 10-way keyboard, PCBs and all components to construct a Digital Lock, requiring a 4-key sequence to open and providing over 5000 different combinations. The open sequence may be easily changed by means of a pre-wired plug. Size: 7 x 6 x 3 cms. Supply: 5V to 15V d.c. at 40µA. Output: 750mA max. Hundreds of uses for doors and garages, car anti-theft device, electronic equipment, etc. Will drive most relays direct. Full instructions supplied. **ONLY £10.50**

Electric lock mechanisms for use with latch locks and above kit **£13.50**

**DISCO LIGHTING KITS**

**DL 1000K**  
This value-for-money kit features a bi-directional sequence, speed of sequence and frequency of direction change, being variable by means of potentiometers and incorporates a master dimming control. **£14.60**

**DL2100K**  
A lower cost version of the above, featuring unidirectional channel sequence with speed variable by means of a pre-set pot. Outputs switched only at mains zero crossing points to reduce radio interference to a minimum. **Only £8.00**

Optional opto input DLA1  
Allowing audio ("beat")  
—light response. **60p**

**DL3000K**  
This 3 channel sound to light kit features zero voltage switching, automatic level control & built in mic. No connections to speaker or amp required. No knobs to adjust - simply connect to mains supply & lamps. (1Kw/Channel) **Only £11.95**

Have you got our **FREE GREEN CATALOGUE** yet?  
**NO?! Send S.A.E. 6" x 9" TODAY!!**

It's packed with details of all our KITS plus large range of SEMICONDUCTORS including CMOS, LS TTL, linear, microprocessors and memories; full range of LEDs, capacitors, resistors, hardware, relays, switches etc. We also stock VERO and Antex products as well as books from Texas Instruments, Babani and Elektor.

**ALL AT VERY COMPETITIVE PRICES.**

**ORDERING IS EVEN EASIER - JUST RING THE NUMBER YOU CAN'T FORGET FOR PRICES YOU CAN'T RESIST.**

**5-6-7 8-9-10**

Answering service evngs & weekends

**FAST SERVICE · TOP QUALITY · LOW LOW PRICES**

**TK ELECTRONICS**  
11 Boston Road  
London W7 3SJ

Add 65p postage & packing +15% VAT to total Overseas Customers.  
Add £2.50 (Europe), £3.00 (elsewhere) for p&g  
Send S.A.E. for further STOCK DETAILS.  
Goods by return subject to availability

**OPEN** 9am to 5pm (Mon to Fri)  
10am to 4pm (Sat)

**ALL PRICES EXCLUDE VAT**

**HE**

TEL: 01-567 8910 ORDERS  
01-579 9794 ENQUIRIES  
01-579 2842 TECHNICAL AFTER 3PM



**The MIGHTY MIDGETS SOLDERING IRON 18 WATT SUMMER**

**SPECIAL OFFER**

**£4 inc v.a.t & post**

**12 MONTH GUARANTEE**

usual price £5.46 + 35p post

**S&R BREWSTER LIMITED**  
86-88 UNION ST. PLYMOUTH PL1 3HG

PLEASE QUOTE YOUR NUMBER WHEN ORDERING

**EDUCATIONAL ELECTRONIC KITS**

**RADIO KIT**

This AM radio is supplied with building instructions plus comprehensive electronic theory, exercises and test procedure. A complete learning package, requiring only a 9V battery.

The large fibreglass printed circuit board has been designed in 3 sections — a TRF radio, a bass treble control and an amplifier push-pull output circuit. Each section can be built and tested as a separate project.

This comprehensive radio circuit shows an application of tuned circuits, I.C.'s, field effect and bipolar transistors, common emitter and collector configurations, stabilizer circuits, feedback circuits, complementary output stages, etc.

The radio project kit should give entertainment and interest to the novice, yet provide valuable learning material for the electrical student. Particularly relevant to current T.E.C. electronic courses.

The price is only **£11.99 inc. VAT + £1.50 p.p.**

Educational and quantity enquiries welcome.

Send cheque or postal order to:-

**HAZZLEWOOD ELECTRONICS**  
Sales Department,  
149 Main Street,  
Grenoside,  
Sheffield, S30 3PN.  
Tel: 0742 463585

Send an S.A.E. to receive a list of our current electronic project kits.

# Bookshelf

THE HE BOOKSHELF is the easiest way to build up your library of electronics books. Order today to have these top titles delivered **DIRECT TO YOUR DOOR.**

**52 Projects Using IC 741**  
£1.25  
More than 50 ways of using the ubiquitous IC 741.

**BEGINNERS GUIDE TO MICROPROCESSORS AND COMPUTING**  
£1.75  
Basic introduction to binary arithmetic, micro-processor operation and machine language programming.

**REMOTE CONTROL PROJECTS**  
£1.95  
Practical information about many applications of remote control.

**ELECTRONIC PROJECTS USING SOLAR CELLS**  
£1.95  
A range of practical applications using silicon solar cells.

**50 (FET) FIELD EFFECT TRANSISTOR PROJECTS**  
£1.75  
Contains a wide range of projects, all based on Field Effect Transistors.

**IC 555 PROJECTS**  
£1.95  
The 555 timer users 'Bible'

**ELECTRONIC MUSIC PROJECTS**  
£1.75  
Many practical circuits for less complex items of electronic music equipment.

**VMOS PROJECTS**  
£1.95  
Contains a number of varied and interesting projects using VMOS power FETs.

**COUNTER DRIVER AND NUMERAL DISPLAY PROJECTS**  
£1.75  
Features many varied projects using numeral displays, counter and driver ICs.

**CHOOSING AND USING YOUR HI-FI**  
£1.65  
Concise information for all hi-fi enthusiasts.

**ELECTRONIC TEST EQUIPMENT CONSTRUCTION**  
£1.75  
How to build and use a wide range of test equipment for the hobbyist.

**DIGITAL IC PROJECTS**  
£1.95  
Simple and advanced projects based on digital ICs.

**RADIO CIRCUITS USING ICs**  
£1.35  
All you need to know about using IC's for AM or FM reception.

**ELECTRONIC GAMES**  
£1.75  
Amusing electronic games which can easily and inexpensively be constructed by the enthusiast.

**POWER SUPPLY PROJECTS**  
£1.75  
Packed with circuits for building various kinds of power supply.

**INTERNATIONAL TRANSISTOR EQUIVALENTS GUIDE**  
£2.95  
Find possible equivalents for a popular user-orientated selection of modern transistors.

**IC LM3900 PROJECTS**  
£1.35  
Provides the ground work for simple and more advanced uses of IC LM3900.

**ELECTRONIC HOUSEHOLD PROJECTS**  
£1.75  
Packed with circuits for projects that can be used in or around the home.

**SINGLE IC PROJECTS**  
£1.60  
Easy to construct projects based around a single IC.

**HOW TO USE OP-AMPS**  
£2.25  
All you need to know about Op-Amps, a source book of circuits and design calculations.

**PRACTICAL CONSTRUCTION OF PRE-AMPS, TONE CONTROLS, FILTERS AND ATTENUATORS**  
£1.45  
Contains practical designs for use with home constructed equipment or commercial modules.

**A MICROPROCESSOR PRIMER**  
£1.75  
A painless approach to understanding computers and computing

**PRACTICAL COMPUTER EXPERIMENTS**  
£1.75  
Build and examine a number of basic computer circuit elements

**AUDIO PROJECTS**  
£1.95  
Clear information on how to build pre-amps, mixers, power amps, tone controls etc

To receive your books you have only to fill in the form below and send it, together with your payment, to the address stated. Please allow up to 21 days for delivery. This offer applies only within the U.K. Prices may be subject to change without notice.

SEND TO: HE BOOKSHELF, 513 London Road, Thornton Heath, Surrey CR4 6AR.

I am enclosing my Cheque/Postal Order/for: (delete as necessary)

£..... (Made payable to A.S.P. Ltd)



OR Debit my Access/Barclaycard (delete as necessary)



--	--	--	--	--	--	--	--	--	--

Please use BLOCK CAPITALS and include post codes.

Name (Mr/Mrs/Miss) .....

Address .....

.....

.....

.....

Signature ..... Date .....

Books Required	Price
Add 75p p&p	0.75
Total Payment	£

CALL IN AND SEE FOR YOURSELF


# AUDIO ELECTRONICS

ALL PRICES INCLUDE VAT

TEST EQUIPMENT CENTRES ALL MODELS ON DISPLAY OPEN SIX DAYS A WEEK

RETAIL • MAIL ORDER • EXPORT • INDUSTRIAL • EDUCATIONAL

## DIGITAL MULTIMETERS (UK C/P Free)

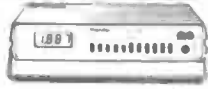

ALL MODELS 3 1/2 DIGIT UNLESS STATED



<b>HAND HELD</b>	With free carry case	Beckman T110 As T100 plus Cont. test etc.	£67.85
K025C=13 range 0.2A DC 2 meg ohm	£24.95	Sifam 2200B 21 range 2A AC/DC 20 meg ohm	£39.95
K030S=16 range 10A DC 2 meg ohm	£34.95	+Optional carry case £2.95	
K030C=26 range 1A AC/DC 20 meg ohm	£34.95	<b>BENCH MODELS</b>	
K055C=28 range 10A AC/DC 20 meg ohm	£39.95	TM353=27 range LCD 2A AC/DC	£86.25
6010+ 28 range 10A AC/DC 20 meg ohm	£34.40	TM355=29 range LCD 10A AC/DC	£86.25
7030+ As 6010 but 0.1% basic.	£41.30	TM351=29 range LCD 10A AC/DC	£113.85
K0615=16 range 10A DC 2 meg plus Hfe tester	£39.95	+Optional carry case £6.84	
189M 30 range 10A AC/DC 20 meg plus Hfe tester	£69.95	2001 28 range LCD 10A AC/DC plus 5 range Cap Meter with case	£108.00
HD30 16 range 0.2A AC/DC 2 meg ohm	£41.95	TM451 4 1/2 digit LCD every facility (0.02%)	£171.00
HD30/B As above plus cont. buzzer	£44.50	1503a 4 1/2 digit LCD every facility (0.05%)	£171.00
HD31 22 range 10 AC/DC 2 meg ohms plus cont. buzzer	£58.95	1503Ha 0.03% basic version of above	£189.00
<b>DM2350</b> = 21 range 10A AC/DC 20 meg ohm miniature hand held auto range	£49.95	1504 true RMS version	£201.25
Beckman T100 34 range 10A AC/DC 20 meg ohm	£56.35	Sifam 2500 24 range LCD 2A AC/DC	£99.95
		Metrix (ITT) professional 3 1/2 + 4 1/2 digit	
		DMM's standard & true RMS 4 models stocked	£77.00 - £201.25

## FREQUENCY COUNTERS

PFM200A MHz hand held pocket 8 digit LED	£77.60
811DA 8 digit LED bench 2 ranges 100 MHz	£77.00
86100 9 digit LED bench 2 ranges 600 MHz	£113.85
8000B 9 digit LED 3 ranges 1 GHz	£178.00
TF040 = 8 digit LCD 40 MHz	£126.50
TF200 = 8 digit LCD 200 MHz	£166.75
+Optional carry case £6.84	
Prescaler - Extended range of most counters	
TP600 600 MHz	£43.00
TP1000 1 GHz	£74.00

## SIGNAL GENERATORS (220/240v AC)

<b>FUNCTION</b> : All sine/square triangle/TTL etc	CG100 1 HZ 100 KHZ	£90.00
	TG102 0.2 HZ - 2 MHz	£166.75
<b>PULSE</b>		
TG105 Various facilities 5 Hz - 5 MHz		£97.75
<b>AUDIO</b> : Multiband Sine/Square		
LAG27 10 Hz to 1 MHz		£90.85
AG202A 20 Hz to 200 KHz (List £94.50)		£83.50
<b>RF</b>		
SG402 100 KHz to 30 MHz (List £79.50)		£69.50
LSG17 100 KHz to 150 MHz		£79.35

## OSCILLOSCOPES

Full specification any model on request, SAE by post	
<b>MM</b> Series NAMEG: 'SC' THANDAR:	
<b>CS</b> 'TRIO': '3' CROTECH 'DT' Salfan	
<b>SINGLE TRACE</b> UK C/P £3.00	
3D30 15 MHz 5mV 95mm tube plus component tester C/P £3.00	£177.10
SC11DA = Miniature 10 MHz battery portable	£171.00
Post free	
HM103 15 MHz 2mV 6 x 7 display plus component tester C/P £3.00	£181.70
+Optional carry case £6.84 AC adaptor £6.69	
Wecads £12.50	
<b>DUAL TRACE</b> (UK C/P £4.00)	
DT 520 Dual 20 MHz	£241.50
NM203/4 Dual 20 MHz plus component tester	£287.50
CS1562A Dual 10 MHz (List £321.00)	£269.50
3131 Dual 15 MHz - component tester	£276.00
CS1566A Dual 20 MHz All facilities (List £401.35)	£349.50
NM204 Dual 20 MHz plus component tester sweep delay	£419.75
CS1820 Dual 20 MHz with extra facilities (List £508.30)	£485.00
DX710 Metrix dual 15 MHz - component tester	£304.75
<b>OPTIONAL PROBE KITS</b>	
X1 £7.95 X10 £10.50 X100 £9.45 X1000 £16.95	

## ELECTRONIC INSULATION TESTER

YF 501 500 V/O 100m with carry case £83.00

## MULTIMETERS (UK C/P 65p)

HM102 220K/V 10A DC 22 range & cont. buzzer	£13.50
HM102Z 20 K/V 22 range & cont buzzer	£14.95
ETC5000/5001 21 ranges, 50K/V, Range doubler, 10A DC.	£18.95
<b>TMK500</b> 23 ranges 30K/V 12A DC plus cont. buzzer	£24.75
NH56R 20K/V, 22 range pocket	£10.95
ETU102 14 range 2K/V pocket	£6.50
830A 26 range 30K/V, 10A AC/DC overload protection, etc.	£23.95
360TR 23 range 100K/V, Large scale 10A AC/DC plus Hfe	£39.95
AT102D 18 range 20K/V, Deluxe plus Hfe tester	£18.95
YN 360TR 19 range 20K/V plus Hfe tester	£15.95
Metrix Professional multimeters In stock 3 models from	£74.75

## VARIABLE POWER SUPPLIES (UK C/P £1.00)

PP241 0/12/24V 0/1A	£35.00
PP243 3 amp version	£59.95
PS 1307S 8/15V 7 amp twin motor	£24.95

## DIGITAL THERMOMETER

TH3D1 LCD -50°C to +750°C with thermocouple £88.43

## AC CLAMPMETER

ST300 0/300A: 0/600 VAC, 0/1 Kohm 9 ranges With carry case (UK C/P 65p) £28.50

## LOGIC PROBES

LP1D 10 MHz £28.50  
DLP50 50 MHz with carry case and accessories £25.33

## TRANSISTOR TESTER

Direct reading PNP NPN, etc. TC1 £21.95 (UK C/P 65p)

**AUDIO ELECTRONICS** Cubegate Limited  
301 EDGWARE ROAD, LONDON W2 1BN, TEL: 01-724 3564  
ALSO AT HENRYS RADIO, 404/406 EDGWARE ROAD, LONDON, W2, TEL: 01-724 0323  
HENRY'S COMPONENT SHOP, TEL: 01-723 1008

Order by Post with CHEQUES/ACCBES  
VISA or you can telephone your order  
All orders despatched within 8 days  
unless advised

FREE CATALOGUE! SEND LARGE SAE (UK 20p)

ALL PRICES INCLUDE VAT

# MAKING YOUR OWN P.C.B's ?

Have you tried "Hobbyboard" Etch Resist Kit?



**INTRODUCTORY OFFER**

2-Sheets Resist transfers each containing over 500 Pads - 14 DIL Packs - connectors - and many other useful aids

- 1 - Transfer Spatula
- 1 - Etch Resist Pen
- 2 - Rolls Track Tape - 18 yds long (.031" and .039")
- 3 - Copper Clad Sheets - 6" x 4" single sided

**SPECIAL OFFER PRICE** (until Oct 31st 1983)  
**£6.50 Inclusive of VAT & Postage**

please send full Hobbyboard Catalogue please send me

off ETCH RESIST KIT, HB/SOER @ £6.50 ea. Cheque/P.O. enclosed. £.....

Name .....

Address .....

**hobbyboard**  
complete P.C.B. workshop

a division of  
**KELAN ENGINEERING Ltd**  
Hookstone Park  
Harrogate, N. Yorks

HE/883



# POINTS OF VIEW

Feel like sounding off?  
Then write to the Editor stating your Point of View!

## Calling Mr. Giggs

If there is a Mr. Giggs out there, who wanted a Heathkit manual for a C-3U R-C Bridge, please could he get in touch? We know somebody who has one.

## Atari In The Islands

Dear Sirs,

I receive your very helpful magazine a little later than some of your readers but it is better than gold. In February's issue which has just arrived you comment about the hobbyists in remote corners of the country - well we here in the middle of the South Pacific are in a rather remote part of the world, so all we can get hold of in the way of news and information is even more valuable than to those who can buy magazines off the bookstall and whose public libraries are stacked with the latest books.

I teach Physics here - and computing, and when I was visiting Britain last year I bought myself an Atari 400. I explained to the supplier that I was going to a rather remote part of the world and would value keeping in touch. He promised all sorts of help - including the VAT back on my machine after I'd left the country. That is the last I've heard from him.

I am delighted with the capabilities of the 400, but had problems with the program recorder; I wrote to the supplier, and also Atari in the States. I heard back from the States saying I'd be having a reply to my problem - that was February 3rd, and I'm still stuck.

I have regular classes that I teach - imagine my frustration setting up programs the night before and finding that when the engineers at the power station have changed over from one generator to the other there has been a break in the power and I've lost everything - my hair which is already thin is going even faster!

My idea in teaching computing is to give a chance to young men and women to get "hands-on" experience which they would not, and do not get otherwise. I'm also experimenting with the use of the 400 as a multi-purpose piece of physics equipment which I hope will lead the way to teachers in other third-world countries 'discovering' the micro as a means of doing much more with little capital outlay. However I am very limited with no means of storing programs.

Just after I came back I encouraged a local electronic music shop owner to become an Atari stockist, he is all enthusiastic and has gone ahead, but

*we need outside help and advice beyond our own capabilities. I hope this letter may stir some.*

*Much as we enjoy the sunshine here we are also keen on keeping up with the latest technology.*

*Yours sincerely,  
Rob Pattison,  
Physics Dept.,  
Lelean Memorial School,  
Box 66,  
Nausori,  
Fiji.*

*PS. Our school is one of the only three with a computer in Fiji.*

You seem to be doing a lot with a little, and good luck to you. It's a pity about dealers who take the 'out of sight, out of mind' line but I hope Atari either in the UK or the States (or both) will help you out with your problems. You may have to nag them.

I am ignoring our usual custom and printing Mr. Pattison's school address so that readers and teachers in similar situations can write to him and exchange ideas.

Mr. Pattison would also like to know whether there are any broadcast satellites that he could tune into with the right receiver in his part of the world (the Pacific Islands, for non-geographers!) In between coping with cyclones and hurricanes, that is. . .

## In Search Of A Job

Dear Sirs,

I am a regular reader of HE and was very interested in your article on Careers in Electronics in May '83.

I am about to start the last term of a full-time TEC Higher Certificate in Electronics course I am taking at Liverpool Polytechnic, which I am advised I should successfully pass, so I am beginning to look around for appropriate employment. The few approaches I have so far made to local firms have been unsuccessful, some so strange to electronics as to assume I was looking for employment as an electrician's mate!

Anyway, I am writing to ask if you could advise me where I might obtain names and addresses of the major firms in the Electronics field, anywhere in the country, so that I can contact them regarding employment prospects. Any help you could give me would be very much appreciated.

*Yours faithfully,  
J. A. Richardson,  
Middlesborough,  
Cleveland.*

Yes. Random approaches to firms, while they can turn up an unexpected gem of opportunity, very often result in blank stares and puzzlement.

To get the names and addresses of electronics firms, you need to consult professional magazines and trade papers advertising for posts (this is not to say you can only apply for the posts being advertised). Find the largest reference library you can and try to get hold of papers like *Electronics News* and *Electronics Weekly*. Ask the librarian for assistance in tracing electronics journals and also any trade directories which lists electronics firms. Also, don't forget the Yellow Pages phone directories.

This is the long, laborious, individual way of looking for an employer. The other one is to contact your local Educational Authority and ask to be put in touch with their Careers Office. Go and talk to them.

Doesn't your polytechnic have a technical library and/or a careers office.

## In Search Of Electronics

Dear Editor,  
HELP!!

*I've spent many years in the software side of the computer industry, however, I've caught the BUG to know and learn more about the hardware element.*

*I want to be able to read and understand circuit diagrams upwards, because I want to build my own microcomputer. The principle application will be the knowledge I would have gained in actually building it.*

*The snag is, I don't want to go back to college, so I would like to know of home/correspondence courses and books available, no matter what the cost.*

*Can you PLEASE, PLEASE inform me of those bodies etc. that can help.*

*Yours in much need,  
Richard Lanyon-Hogg,  
Husbourne Crawley,  
Beds.*

Now there is an encouraging noise! Someone who wants to know how the things work. Stick with it - people who know about the innards as well as the outards (is there such a word as outards?? There is now . . .) of microcomputers are going to be in demand.

Bodies: Well first of all, there is HOBBY ELECTRONICS. We have just started a new series for beginners, All

*About Electronics*; going back a bit, Hobby has run *Into Electronics* (Nov '78 to June '79), *Into Digital Electronics* (Sept '80 to Jan '81), *Into Electronics Components* (Aug '81 to July '82) and *Into Electronics Construction* Feb '80 to July '80). All these articles are available from our Backnumbers service, £1.50 an issue.

Then there is the *British Amateur Electronics Club*. Contact The Secretary, Mr. J. G. Margetts, 113 South Rd., Horndean, Hants PO8 0ER for information.

Check out your local main library for information about part-time courses in electronics run by your local education authority.

For information on books, check out some of the publishers mentioned in *Look In The Book* (HE February '83) and write for their technical catalogues.

You could also try *Electronics, Its Easy*, the popular collection of reprints on basic electronics compiled by our sister magazine ETI and available for £4.95 from the same address as HE Bookshelf, viz. 513 London Rd., Thornton Heath, Croydon, Surrey CR4 6AR, which has just been reprinted for the third time.

And you could always contact The Open University, Milton Keynes (right up your street — literally!) — and write to the Courses Information Department and ask what they have. You don't have to commit yourself to doing a degree, and can work entirely at home.

Correspondence courses are a bit outside our frame of reference, but you will find them advertising in many semi-pro electronics magazines, including ETI. One address plucked at random is the *British National Radio and Electronics School*, Reading, Berks RG1 1BR.

Keep an eye on MONITOR which sometimes features self-teaching kits, and electronics and computing clubs.

Build something! But start with a kit, if in doubt — you will have fewer variables to cope with. It's not as complicated as it looks.

Self-education is a convoluted process, full of mysteries. Get a decent multimeter, cultivate an elegant soldering technique, double-check for dry joints, have patience and keep reading *Hobby Electronics* — and you can't go far wrong . . .

## Sine Errato

Dear Sir,

In the HE June '82, Ian Sinclair lets his poetic license run away with him: the sine wave is not so called because it is snake-like but because it is the plot of an actual sine wrt time. The Romans used 'sinus' to describe anything in the curvaceous department. Our 'sinusoid' is the plotting of another curve but just happens to be a curve in itself.

The curve in question is the arc, TQ, of a circle. TQ comes from drawing a tangent TS, a radius OT and a secant OS cutting the circumference at Q. P

is the vertical projection (shadow) of Q on OT. To be fair, we don't measure TQ but its height, PQ — because its always harder to measure a curve, even with bits of string. Although 'sine' means a curve (like the sinus in your head), we already have another Latin word, 'arc'. In this context we have corrupted the translation of 'sine' to mean not the curve TQ but its straight height.


As you know, in engineering, navigation etc, useful ratios are:

$$\begin{aligned} \text{sine unit}^{-1} \text{ radius} &= \frac{PQ}{OQ} \\ \text{secant unit}^{-1} \text{ radius} &= \frac{OS}{OT} = \frac{OQ}{OP} \end{aligned}$$

(by alternate angles) and

$$\text{tangent unit}^{-1} \text{ radius} = \frac{TS}{OT} = \frac{PQ}{OP}$$

(by alternate angles).

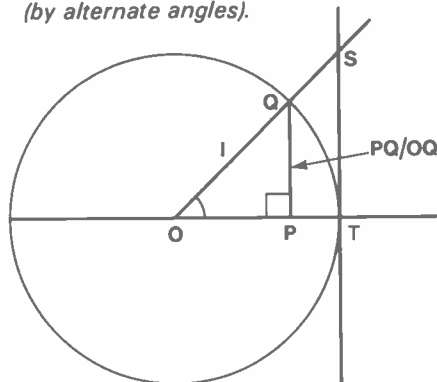

The unit circle as described in our letter.

The basis for simplifying these long names is to assume a unit circle to begin with. For any such right angled triangle POQ, you can always invent a unit circle with sine PQ/OQ and a radius of one unit (one yard, French loaf, yard per minute, etc.) Now 'sine per unit radius' equals numerically 'sine', since the radius is a unit. I.e. PQ/OQ over 1 equals PQ/OQ, which is why we say simply that the sine of POQ is PQ/OQ. Similarly secants, tangents and the co-functions. I'll leave you to work out the hyperbolics!!!  
Yours faithfully,  
Kathy Louise Saint-John Crostorry,  
Machen,  
Gwent.

Ian Sinclair replies:

"Thanks for the letter. Methinks the lady doth protest too much. The point I was making is that there has to be some reason for calling a ratio of two straight lines a sine, and the shape of the graph of sine (angle) plotted against angle is a good reason, just as the name of the tangent, (from tangere, to touch) must come from the appearance of a graph of tan(angle) plotted against angle."

Well, if you will take advice from a nation which tried to build circles out of straight lines, what can you expect? They spoke Latin too, and where are they now? And now we've got typesetters quoting ancient Greek

at us. It's getting "out of hand" (ex digitas), if you ask me . . .

## Meet Your Match

Dear Sir,

I have written to three of your advertisers, but none has been able to help me. Would it be possible for you to give me the name of a manufacturer or supplier for the following information?

I would like to obtain five matched pairs of 47uF capacitors or a pair of matched capacitors of the values of 47, 94, 141, 188 and 235 which must be 10-volt working.

Yours faithfully,  
R Head.

Heanor,  
Derbyshire.

Capacitors are not sold as matched pairs, nor are they available in any of the values you require except 47uF.

To match capacitors, you must have a reasonably large number of the nominal value and then measure the exact value, choosing the closest pair. You'll find our Digital Capacitance Meter, a project published in HE April '82, quite suitable for the job.

As for the odd values, you'll have to make them up by selecting the appropriate values and then correcting them in series or parallel as required.

Capacitor networks are the opposite of resistor networks. Two capacitors in series have the total value of:

$$C_t = \frac{C_1 C_2}{C_1 + C_2}$$

while capacitors in parallel are simply added together, re:

$$C_t = C_1 + C_2$$

So, to make up a capacitor of 95uF, you need 47 = 47uF. A 141uF capacitor is three 47uF in parallel and so on.

## Microlog Transformer

Dear Sir or Madam,  
After reading HE December '82, I am building (or trying to build!) an HE Microlog computer.

However, I have had considerable difficulties (apart from postage problems to Dubai) in obtaining a suitable transformer (3VA, 240V, 20-0-20). Please could you send me some information on possible buylines for the transformer (no reference to it was given in the Buylines section of HE) as my only other alternative is a multi-purpose transformer costing over £10.00.

Thank you.  
Yours faithfully,  
D. Horton-Szar,  
Dubai,  
UAE.

This is a fairly standard transformer, stocked by many companies who advertise in HE. Try Cricklewood Electronics.

HE

**HOBBY HERALD  
HAS ALL THE  
LATEST NEWS  
FOR THE  
ELECTRONICS  
HOBBYIST**

When you need to update yourself with all that is available in the "Do-it-yourself" market, then you need the Hobby Herald.

Packed with product information essential to the electronics enthusiast, this new electronics catalogue lists over 60 exciting products ranging from All Purpose Cutters to Verobloc, the solderless breadboard. All products are available throughout the U.K. from over 200 stockists.

# HOBBY HERALD

Alternatively ordering products through the Herald is simplicity itself, and you can pay by either cheque, Barclaycard or Access. So make sure you get your copy of Hobby Herald by ringing **(04215) 62829.**



BICC-Vero Electronics Ltd.,  
Industrial Estate,  
Chandlers Ford, Hampshire,  
SO5 3ZR.



## JUST OUT OUR NEW CATALOGUE

Presented with a Professional Approach and Appeal to ALL who require Quality Electronic Components, Semiconductors and other Accessories ALL at realistic prices.

There are no wasted pages of useless information so often included in Catalogues published nowadays. Just solid facts i.e. price, description and individual features of what we have available. But remember, BI-PAK's policy has always been to sell quality components at competitive prices and THAT WE STILL DO.



We hold vast Stocks "in stock" for fast immediate delivery, all items in our Catalogue are available ex stock.

The Catalogue is designed for use with our 24 hours "ansaphone" service and the Visa/Access credit cards, which we accept over the telephone.

To receive your NEW 1983 BI-PAK Catalogue, send 75p PLUS 25p p&p to:—

**BI-PAK**

Dept HE/8  
Catalogues! PO Box 6  
WARE, Herts SG12 9AD



Access & VISA accepted  
Ring 0920 3182 for  
immediate despatch

# circuit board components

Castle House, 1 Castle Lane, Bedford MK40 3QE  
Telephone 0234 214219  
Please note our new address

All components brand new — Please add 35p P&P plus 15% VAT. Please send cheque or P.O. with your order. Official orders are welcome from educational establishments, Government bodies and public companies. Credit accounts are available. Please ask for details.

### LOW PROFILE SOCKETS

8 Pin 8p 14 Pin 10p 16 Pin 11p  
18 Pin 16p 20 Pin 18p 22 Pin 22p  
24 Pin 25p 28 Pin 20p 40 Pin 30p

ORDER 12 OF ANY ONE TYPE AND WE WILL SUPPLY 13.  
\*8 BAKERS DOZEN  
SPECIAL FOR JUNE-JULY 83

### MEMBRANE KEYPADS By F.S.T.

Multi-choice Graphics Keypads, 57 standard characters to choose from. Blue or white as standard graphic options keypad complete with flexible backing with Berg connector.

### PANEL DIMENSIONS

3 x 4 — 70 x 98 mm £5.88  
4 x 4 — 97 x 98 mm £6.89  
5 x 4 — 116 x 98 mm £7.41

TTL			
7400	11p	7427	18p
7401	11p	7428	25p
7402	11p	7430	13p
7403	13p	7432	20p
7404	13p	7433	20p
7405	14p	7437	23p
7406	19p	7438	24p
7407	19p	7440	14p
7408	13p	7442	30p
7409	13p	7444	85p
7410	13p	7446	58p
7411	15p	7447	38p
7412	17p	7448	43p
7413	17p	7450	14p
7414	23p	7451	14p
7415	19p	7453	14p
7417	14p	7454	14p
7418	19p	7459	14p
7419	19p	7472	22p
7420	14p	7473	24p
7421	19p		
7422	19p		
		7474	18p
		7475	28p
		7476	28p
		7480	45p
		7482	85p
		7483	30p
		7485	80p
		7486	18p
		7489	18p
		7490	18p
		7491	34p
		7492	24p
		7493	24p
		7494	32p
		7495	38p
		7496	32p
		7497	38p
		74100	72p
		74107	22p
		74109	24p

CMOS			
4000	10p	4020	43p
4001	10p	4021	40p
4002	12p	4022	45p
4006	60p	4023	78p
4057	14p	4024	33p
4008	36p	4025	12p
4009	24p	4026	75p
4010	24p	4027	30p
4011	15p	4028	45p
4012	15p	4029	45p
4013	20p	4030	14p
4014	45p	4031	125p
4015	40p	4034	140p
4016	30p	4035	249p
4017	30p	4039	280p
4018	45p	4040	40p
4019	25p	4041	40p
		4042	38p
		4043	40p
		4044	40p
		4046	40p
		4047	35p
		4048	38p
		4049	21p
		4050	21p
		4051	42p
		4052	48p
		4053	48p
		4054	78p
		4055	80p
		4059	430p
		4060	42p
		4063	60p
		4066	22p

Free — Satin Gold Biro  
With all orders over £3.00 in "June and July" 83



# FORWARD BIAS

## Questions, answers and errata from readers and writers.

The **Soft Fuzz** project, published in *Hobby Electronics* last month, was originally designed as a two-step unit to which extra steps could be added at the constructor's whim, to experiment with different effects. The author has a few words (and numbers!) to add on the subject:

"From the explanations given in the **Soft Fuzz** article, it is a small step to design a feedback network to produce any required type of compression. First of all, you should draw a graph of the required characteristics. When you are satisfied with the shape of the graph, read from it the slopes (hence the gains needed), and the output voltages at which the slope of the graph changes.

Taking a two-step circuit as an example, suppose that you wanted the gain to be 1 for large signals. For smaller signals let us say that we want a gain of  $1\frac{1}{2}$  for outputs up to 1V2 and a gain of 5.2 from 1V2 to 2V.

First of all, since the final gain is to be 1, R13 must be the same value as R3 (3k3) — simple. Next, calculate for the gain of 5.2. For this,  $R11 + R12 + R13$  must be equal to  $5.2 \times R3$ .

Therefore, since  $R13 = 1 \times R3$ ,  $R11 + R12 = 4.2 \times R3 = 13k86$ .

Similarly, for the gain of 13.5,  $R1 + R2 + R11 + R12 + R13$  must be equal to  $13.5 \times R3$ . Since  $R11 + R12 + R13 = 5.2 \times R3$ ,  $R1 + R2 = (13.2 - 5.2) \times R3 = 27k39$ .

The next step is to calculate the ratios of the resistors. Since we know the total resistance of each pair, it is simple (with a calculator) to multiply the total value by the appropriate fraction, and then pick the nearest preferred value to the answer.

The best way to find the required ratios is to start with the lowest voltage breakpoint, 1V2. This is the charge from the highest gain to the intermediate gain, so resistors R1 and R2 are the ones concerned.

In order to switch to TR1 or TR2, a voltage of OV6 must be developed across R1. For a 1V2 breakpoint, this allows OV6 across all other resistors together. This means that R1 is half of the total resistance value, which is  $13.5 \times 3k3 = 44.55k \Rightarrow R1 = 22k275$  equals about 22k. Since  $R1 + R2 = 27k39$ , R2 should be 5k39, so pick the nearest preferred value: 5k6.

In order to make it simple to calculate R11 and R12, you can remove TR1, TR2, R1 and R2 from the calculation.

Once TR1 or TR2 has switched on, R1 and R2 have no further resistive effect on the feedback. The effect of the network is to subtract a voltage from that appearing across the rest of the feedback network. This voltage is:

$$\frac{(R1 + R2) \times OV6}{R1}$$

$$\frac{(22 + 5.6) \times OV6}{22} = OV753$$

Therefore when the output reaches 2V, there will be 1V247 across the rest of the feedback network. The calculation is now carried out much as above: for OV6 across R11,  $R11 = OV6 \times R11 + R12 + R13$  (ie  $17k16 \Rightarrow R11 = 8k256$  — so choose the preferred value of 8k2).

To find the final resistor,  $R11 + R12 + R13 + 17k16$  and  $R11 + R13 = 313 + 8.2 = 11.5 \Rightarrow R12 = 17.16 - 11.5 = 5k66$ , so choose the preferred value of 5k6.

That's it! All calculated!

With enough patience for tedious sums, this can be extended to many more stages.

Incidentally, if you happen to possess a 'scope and a triangle wave generator, and if you dislike sums, you could make up the circuit with resistor values chosen by "finger in the air" methods, display the performance on the scope, and modify the values until the performance pleases you."

Or — we suppose — you could attach it to an electric guitar and see what happens! Just remember to disconnect the power before you change any components, that's all . . .

## COLLECTED BOOBS

Starting right here, *Forward Bias* is going to reprint all the official *Hobby Electronics* Errata Cards, going back to January 1979, for the benefit of those readers who are either struggling with a project which has some nameless disease, or who are thinking of embarking on an old *Hobby* project.

Photocopies of Errata Cards are still available on request with an SAE or International Reply Coupons, but regular readers will now have the chance to build up their own file.

Let's get started:

### Flash Trigger (HE January '79)

Figure 3: 'RV1' label on the right hand side of the board should read 'RV1 Wiper'.bng.

The Parts List should read:

R1, 2	33k
R3-5	330k
R6	100k
R7	470R


Also:

RV1	50k linear
-----	------------

Some switch details were omitted. They are:

- SW1 ..... SPST On/Off
- SW2 ..... 2 pole 6 way rotary (only 1 pole 4 ways used)

SW2 should be connected as follows:

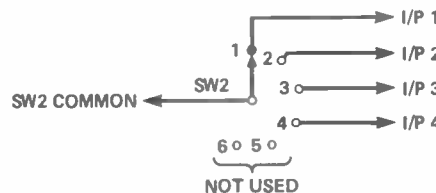

### Drill Speed Controller (HE June '79)

Figure 1: On the Circuit Diagram, the link shown shorting Q1 base and collector, and Q2 base and collector together is incorrect. The PCB and overlay give the correct version.

### Starburst (HE September '79)

PCB Overlay: the OV and +9V notation should be swapped over. Also, reduce R7 - R11 to 15 - 18k for reliable switching.

## Recent Errata

HE Starburst (HE September '79) see *Projects From The Past*, Points of View HE May '83.

Big Ear (HE December '82) see *Ear Errata*, Points of View HE March '83.

Microlog (HE December '82) see *Microlog Mistake*, Points of View HE March '83, and *Microlog Errata*, Monitor and PCB Printout HE January '83.


HE Echo-Reverb (HE May '82) see *Designer On The Dole*, Points of View, HE December '82.

## Past Project Progress

There is now a PCB available from our PCB service for the **Low Cost Alarm** (HE December '82) — see the PCB Printout, HE June '83.


The troublesome **Telephone Timer** (HE June/July '82) is being re-examined from the bottom up by our technical team (all of him), but the solution is not yet on schedule for publication and probably won't be for some time. The **Echo Reverb** (HE May '82) may also be coming in for scrutiny shortly.

# GET BIG POWER

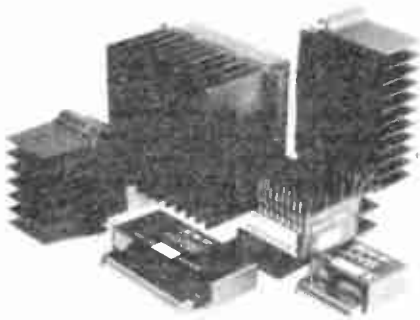
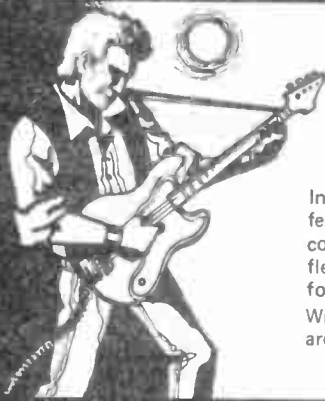
## Modular Amplifiers the third generation

Due to continuous improvements in components and design ILP now launch the largest and most advanced generation of modules ever.



### WE'RE INSTRUMENTAL IN MAKING A LOT OF POWER

In keeping with ILP's tradition of entirely self-contained modules featuring, integral heatsinks, no external components and only 5 connections required, the range has been optimized for efficiency, flexibility, reliability, easy usage, outstanding performance, value for money.

With over 10 years experience in audio amplifier technology ILP are recognised as world leaders.



#### BIPOLAR MODULES

Module Number	Output Power Watts rms	Load Impedance $\Omega$	DISTORTION		Supply Voltage Typ	Size mm	WT gms	Price inc. VAT
			T.H.D. Typ at 1KHz	I.M.D 7KHz 4:1				
PSU 21X	15	4 $\Omega$	<0.005%	<0.005%	1.5V	86 x 49 x 40	300	£10.90
PSU 22X	15	4 $\Omega$	<0.005%	<0.005%	1.5V	86 x 49 x 40	300	£10.90
PSU 23X	15	4 $\Omega$	<0.005%	<0.005%	1.5V	86 x 49 x 40	300	£10.90
PSU 24X	15	4 $\Omega$	<0.005%	<0.005%	1.5V	86 x 49 x 40	300	£10.90
PSU 25X	15	4 $\Omega$	<0.005%	<0.005%	1.5V	86 x 49 x 40	300	£10.90
PSU 26X	15	4 $\Omega$	<0.005%	<0.005%	1.5V	86 x 49 x 40	300	£10.90
PSU 27X	15	4 $\Omega$	<0.005%	<0.005%	1.5V	86 x 49 x 40	300	£10.90
PSU 28X	15	4 $\Omega$	<0.005%	<0.005%	1.5V	86 x 49 x 40	300	£10.90
PSU 29X	15	4 $\Omega$	<0.005%	<0.005%	1.5V	86 x 49 x 40	300	£10.90
PSU 30X	15	4 $\Omega$	<0.005%	<0.005%	1.5V	86 x 49 x 40	300	£10.90

Protection: Full load line. Slew Rate: 15V/ $\mu$ s. Rise time: 5 $\mu$ s. S/N ratio: 100dB. Frequency response (-3dB): 15Hz - 50KHz. Input sensitivity: 500mV rms. Input Impedance: 100K  $\Omega$ . Damping factor: 100Hz > 400.

#### PRE AMP SYSTEMS

Module Number	Module	Functions	Current Required	Price inc. VAT
PSU 31X	Monopre-amp	Mixing, Compressor, Tuner, Equalizer, Auto Gain Control	10mA	£15.60
PSU 32X	Stereo pre-amp	Mixing, Compressor, Tuner, Equalizer, Auto Gain Control	20mA	£21.20
PSU 33X	Source pre-amp	Equalizer, Volume, Bass, Treble, Mix, Auto Gain Control	50mA	£15.60
PSU 34X	Stereo pre-amp	Equalizer, Volume, Bass, Treble, Mix, Auto Gain Control	20mA	£21.20

Most pre-amp modules can be driven by the PSU driving the main power amp. A separate PSU 30 is available purely for pre-amp modules if required for £5.47 (inc. VAT). Pre-amp and mixing modules in 18 different variations. Please send for details.

#### Mounting Boards

For ease of construction we recommend the BB for modules HY6-HY13 £1.05 (inc. VAT) and the B66 for modules HY66-HY78 £1.29 (inc. VAT).

#### POWER SUPPLY UNITS

Model Number	For Use With	Price inc. VAT
PSU 21X	1 x HY30	£11.93
PSU 41X	1 x HY30, 1 x HY60, 1 x HY60S0, 1 x HY124	£13.83
PSU 42X	1 x HY30	£15.90
PSU 43X	1 x HY30, 1 x HY248	£16.70
PSU 51X	2 x HY128, 1 x HY248	£17.07

Please note: X in part no. indicates primary voltage. Please insert "0" in place of X for 110V, "1" in place of X for 220V and "2" in place of X for 240V.

#### MOSFET MODULES

Module Number	Output Power Watts rms	Load Impedance $\Omega$	DISTORTION		Supply Voltage Typ	Size mm	WT gms	Price inc. VAT
			T.H.D. Typ at 1KHz	I.M.D 7KHz 4:1				
PSU 35X	15	4 $\Omega$	<0.005%	<0.005%	1.5V	86 x 49 x 40	300	£10.90
PSU 36X	15	4 $\Omega$	<0.005%	<0.005%	1.5V	86 x 49 x 40	300	£10.90
PSU 37X	15	4 $\Omega$	<0.005%	<0.005%	1.5V	86 x 49 x 40	300	£10.90
PSU 38X	15	4 $\Omega$	<0.005%	<0.005%	1.5V	86 x 49 x 40	300	£10.90
PSU 39X	15	4 $\Omega$	<0.005%	<0.005%	1.5V	86 x 49 x 40	300	£10.90
PSU 40X	15	4 $\Omega$	<0.005%	<0.005%	1.5V	86 x 49 x 40	300	£10.90

Protection: Able to cope with complex loads as fitted for many systems. protection (protects) if used with a fan.

Slew rate: 20V/ $\mu$ s. Rise time: 3 $\mu$ s. S/N ratio: 100dB.

Frequency response (-3dB): 15Hz - 100KHz. Input sensitivity: 500mV rms.

Input impedance: 100K  $\Omega$ . Damping factor: 100Hz > 400.

#### 'NEW to ILP' In Car Entertainments

##### C15

Mini Power Booster Amplifier to increase the output of your existing car radio to enable it to drive a maximum 15 speakers.

Very easy to use.

Robust construction.

£9.14 (inc. VAT)

Available anywhere in the

Republic of Ireland.

Maximum 15W RMS.

Output power maximum 20W into 8 $\Omega$ .

Frequency response (-3dB): 10Hz to 20KHz. T.H.D.: 0.1% at 10W RMS.

S/N ratio (DIN AUDIO) 80dB. Load Impedance 1 $\Omega$ .

Input sensitivity and modulation (maximum 500mV rms into 10K $\Omega$ ) 240mV into 8 $\Omega$ .

Size 95 x 46 x 50mm. Weight 200 gms.

##### C1515

Stereo version of C15.

£17.19 (inc. VAT)

Size 95 x 40 x 90. Weight 410 gms.

Model Number	For Use With	Price inc. VAT
PSU 44X	1 x HY248	£22.54
PSU 45X	1 x HY306	£22.54
PSU 46X	1 x HY306	£24.20
PSU 47X	2 x HY306, 1 x HY306	£24.20

# WITH A LOT OF HELP FROM



# ILP ELECTRONICS LTD



## PROFESSIONAL HI-FI THAT EVERY ENTHUSIAST CAN HANDLE...

### Unicase

Over the years ILP has been aware of the need for a complete packaging system for its products, it has now developed a unique system which meets all the requirements for ease of assembly, adaptability, ruggedness, modern styling and above all price.

Each Unicase kit contains all the hardware required down to the last nut and bolt to build a complete unit without the need for any special tools.

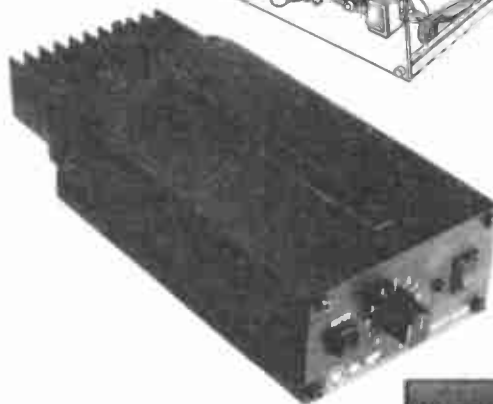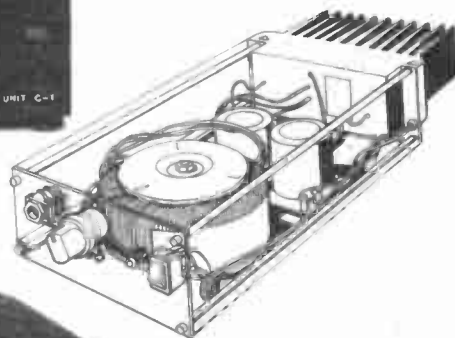Because of ILP's modular approach, "open plan" construction is used and final assembly of the unit parts forms a compact aesthetic unit. By this method construction can be achieved in under two hours with little experience of electronic wiring and mechanical assembly.



### Hi Fi Separates

**UC1 PRE AMP UNIT:** Incorporates the HY78 to provide a "no frills", low distortion, (<0.01%), stereo control unit, providing inputs for magnetic cartridge, tuner, and tape/monitor facilities. This unit provides the heart of the hi fi system and can be used in conjunction with any of the UP Unicase series of power amps. For ultimate hum rejection the UC1 draws its power from the power amp unit.

**POWER AMPS:** The UP series feature a clean line front panel incorporating on/off switch and concealed indicator. They are designed to compliment the style of the UC1 pre-amp. Performance for each unit which includes the appropriate power supply, is as specified on the facing page.

### Power Slaves

Our power slaves, which have numerous uses i.e. instrument, discotheque, sound reinforcement, feature in addition to the hi fi series, front panel input jack, level control, and a carrying handle. Providing the smallest, lowest cost, slave on the market in this format.

#### TO ORDER USING OUR FREEPOST FACILITY

Fill in the coupon as shown, or write details on a separate sheet of paper, quoting the name and date of this journal. By sending your order to our address as shown at the bottom of the page opposite, with FREEPOST clearly shown on the envelope, you need not stamp it. We pay postage for you. Cheques and money orders must be crossed and made payable to I.L.P. Electronics Ltd. if sending cash, it must be by registered post. To pay C.O.D. please add £1 to TOTAL value of order.

**PAYMENT MAY BE MADE BY ACCESS OR BARCLAYCARD IF REQUIRED**

#### UNICASES

HI FI Separates					Price inc. VAT
UC1	Preamp				£29.95
UP1X	30 + 30W/4-8Ω	Bipolar	Stereo	HiFi	£54.95
UP2X	60W/4Ω	Bipolar	Mono	HiFi	£54.95
UP3X	60W/8Ω	Bipolar	Mono	HiFi	£54.95
UP4X	120W/4Ω	Bipolar	Mono	HiFi	£74.95
UP5X	120W/8Ω	Bipolar	Mono	HiFi	£74.95
UP6X	60W/4-8Ω	MOS	Mono	HiFi	£64.95
UP7X	120W/4-8Ω	MOS	Mono	HiFi	£84.95
Power Slaves					
US1X	60W/4Ω	Bipolar	Power	Slave	£59.95
US2X	120W/4Ω	Bipolar	Power	Slave	£79.95
US3X	60W/4-8Ω	MOS	Power	Slave	£69.96
US4X	120W/4-8Ω	MOS	Power	Slave	£89.95

Please note X in part number denotes mains voltage. Please insert 'O' in place of X for 110V, '1' in place of X for 220V (Europe), and '2' in place of X for 240V (U.K.) All units except UC1 incorporate our own toroidal transformers.



Post to: ILP Electronics Ltd., Freepost 4,  
Graham Bell House, Roper Close,  
Canterbury CT2 7EP, Kent, England.  
Telephone: (0227) 54778.  
Technical: (0227) 64723.  
Telex: 965780.

Please send me the following \_\_\_\_\_

Total purchase price \_\_\_\_\_

I enclose Cheque  Postal Orders  Int. Money Order

Please debit my Access/Barclaycard No. \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

Signature \_\_\_\_\_



# BUYLINES

## Joystick Controller

A full set of parts and components for this project, including the PCB and a two-button joystick, is being supplied by Cambridge Computing, 1 Benson Street, Cambridge CB4 3QJ. A motherboard is provided as part of the package so don't forget to specify which computer (ZX81, Spectrum or Ace) you intend to use with it. An instruction sheet for assembling the Spectrum motherboard, which carries a 5V regulator, will be included where appropriate.

The cost of the kit is £26.00, including VAT, packaging and postage, and a cassette of joystick operating software for all three computers.

## Expanding The Ace

Usually it's easy enough to locate a single supplier for all the components of a Hobby Electronics project, but not always! For this project you'll need to go to at least two suppliers for all the requisite bits and pieces.

For the semiconductors, try Technomatic, who stock a very large range of digital components. They can also supply the IC sockets which, while not essential, provide some flexibility when first completing the project.

The interface section of the project is connected to the real world via two 12-way inter-PCB plugs, and one of the few sources for these gadgets is Ambit International. Order them using Ambit's stock code numbers: 10-03012 for the plugs, 10-03003 for the cable shells and 10-03030 for the crimp terminals (don't forget that you need 24 of them). Ambit can also provide the ICs and the passive components, if you don't already have them.

Finally there is the PCB edge connector socket that plugs onto the Ace expansion port. Like the ZX81, the Ace uses a 23+23-way (double-

sided) edge connector, but differs in that the polarising key is in position 23, at the extreme left of the expansion port as viewed from the rear (our numbering of the Ace port pins thus follows the convention established in the many volumes of literature on the ZX81 and Spectrum, where the pins are numbered from right to left as viewed from the rear).

Again, there are alternative sources of supply for the socket; Technomatic can supply a 25+25 way unpolarised socket which can easily be modified to place the polarising key in the correct position (if you state that the component is for this project and ask them nicely, Technomatic will do the modification for you).

Alternatively a 23+23-way socket with the key in position 23 is available from Innovonics, 147 Uplands Road, East Dulwich, London SE22 0DF.

## Whistle Switch

A novel project, this, but one for which the imaginative constructor will find many uses!

The standard components — resistors, capacitors, most of the semiconductors — are all easily obtainable. Where there might be some problem is in finding the transformer, and the relay.

T1 is a sub-miniature 12-0-12V type, rated at 50mA per winding (1.2VA total) and, somewhat unusually, is not intended for printed circuit board mounting. The required type should measure about 30 x 27 x 25mm, and the fixing centres should be at 36mm to fit the holes marked out on the PCB. However if the exact type can't be had, it should be easy enough to drill the PCB to accept slightly wider fixing centres.

Alternatively the transformer could be mounted off the board and wired into the appropriate PCB points (this will mean a bigger case, too).

The specified relay is an ultra-miniature mains contact relay with a single changeover contact rated at 10A; it is an unusual device, with unusual pin-outs and so it will be hard to find a substitute unless you're prepared to re-design the PCB tracks!

The alternative to modifying the project (a course we do not recommend, as it happens), is to contact Magenta Electronics, who have kindly arranged to stock exactly the type of relay and transformer required for the project.

The most important IC to find is the 567 tone decoder/PLL; it may be either an NE567 or an LM567 — they're equivalent, so it doesn't matter. Similarly a TL071 could be substituted for the specified 081, with some improvement in the noise performance, and any of the standard general purpose silicon PNP transistor types could be used in place of the BC109 — BC149, 319, 549 and so on.

All these other bits and pieces are also available from Magenta, of course, and the cost of the project excluding case and PCB should be around £10.00. A Vero type GP3 case, which measures 180 x 110 x 55mm, is £2.28 and the price of the PCB can be found by looking at our PCB Service page.

## Auto-Winder



No problems with this project — all the components are stock-standard and available from regular mail order companies such as Rapid Electronics in Colchester.

The relays are both 12VDC/160-240R coil types with contacts rated at 5 amps or better. If the relays and PCB are mounted in one case, it should measure approximately 4" x 4" x 1 1/2" (101 x 101 x 64mm); if the relays are mounted separately the case for the PCB alone will need to be at least 4" x 2" x 1 1/2" (101 x 50 x 64mm). Either way, use a metal case — folded or diecast aluminium — not plastic!

The cost of the Auto-Winder project ought to be under £10 including the relays but not the PCB or the metal box.

# BEASTIES

BY AH

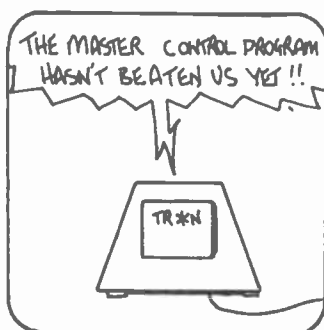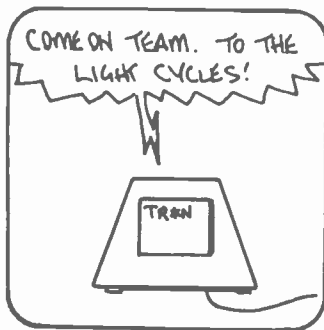



# Just Whistle

R. A. Penfold

The Whistle Switch unit is a novel form of remote control which enables an item of mains powered equipment to be switched on and off at will, simply by whistling the appropriate note! Although the system was designed originally for its novelty value, it is in fact a practical form of remote control and has the advantage over most other systems of not requiring a transmitter of some kind to activate the receiver. The unit could also be very useful to a disabled person, so it is not purely frivolous.

The maximum range that can be obtained depends on a number of factors such as the sensitivity of the microphone used, but a range of about 6 meters or so can be readily achieved using the prototype equipment, and this is more than adequate since the unit is only intended for the control of equipment in the same room as the user (like the popular infra-red and ultrasonic remote control systems). Using the specified relay the unit can control mains equipment having a power rating of up to 2400 watts.

## Tone Decoder

The device at the heart of the Whistle Switch is an NE567 phase locked loop tone decoder. The block diagram of Figure 1 shows the internal arrangement of this device plus the discrete components required in order to make it function correctly.

A fairly conventional phase locked loop circuit is formed by the phase comparator, amplifier, and current controlled oscillator (CCO). Most phase locked loops use a voltage controlled oscillator (VCO) rather than a CCO, but the basic method of operation is the same using either type. With no input signal the CCO receives a control current that sets its operating frequency at roughly the centre of its operating range. The values of R2 and C1 set this free running frequency.

If an input signal is applied to the circuit, and is at the same frequency and in phase with the signal from the CCO (in other words the two signals rise and fall in amplitude precisely in unison and with the same polarity) there is no change in the output signal from the phase comparator and the following amplifier stage. If the

It won't fetch you a private taxi, fix you a long, cool cocktail or come running up with your tennis ball when you call it, but it *will* turn you household gadgets off and on, and doesn't require tactful handling or regular feeding!

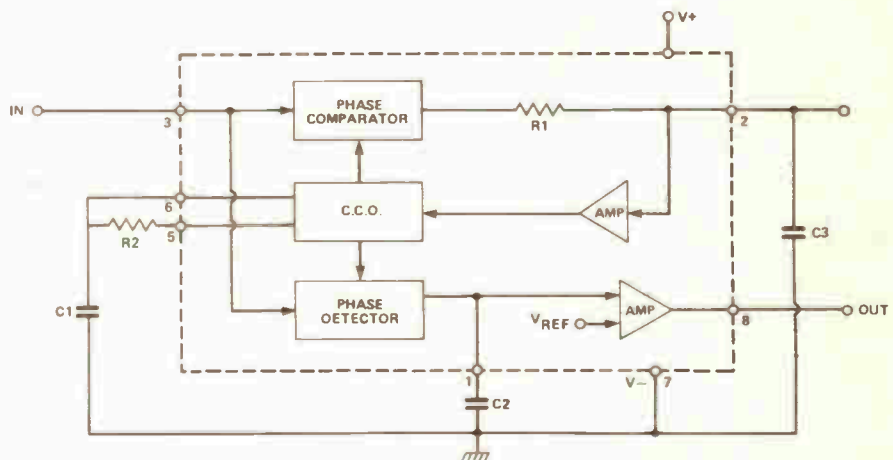


Figure 1. The block diagram, with internal units and components.

## How It Works

Basically the unit is very straightforward, as can be seen from the block diagram. The output signal from the microphone is extremely small and is first amplified by a high gain preamplifier to produce a usable signal level. The signal is then fed to a phase locked loop (PLL) tone decoder, and this activates a switch if the input signal is within a fairly narrow band of frequencies. A trigger circuit plus some simple filtering are used to give a clean switching action as the input tone commences and finishes, so that multiple operation of the circuit

and unreliable results are avoided.

If the trigger circuit was to be used to directly drive a relay or relay driver stage the relay would only be switched on while the input tone was present and this would be of limited practical use. A flip-flop is therefore used between the trigger and relay driver circuits so that each time a burst of tone is received at the input the relay changes state (ie if it is on, it switches off; or if it is off, it switches on). A set of relay contacts are used to control the load.



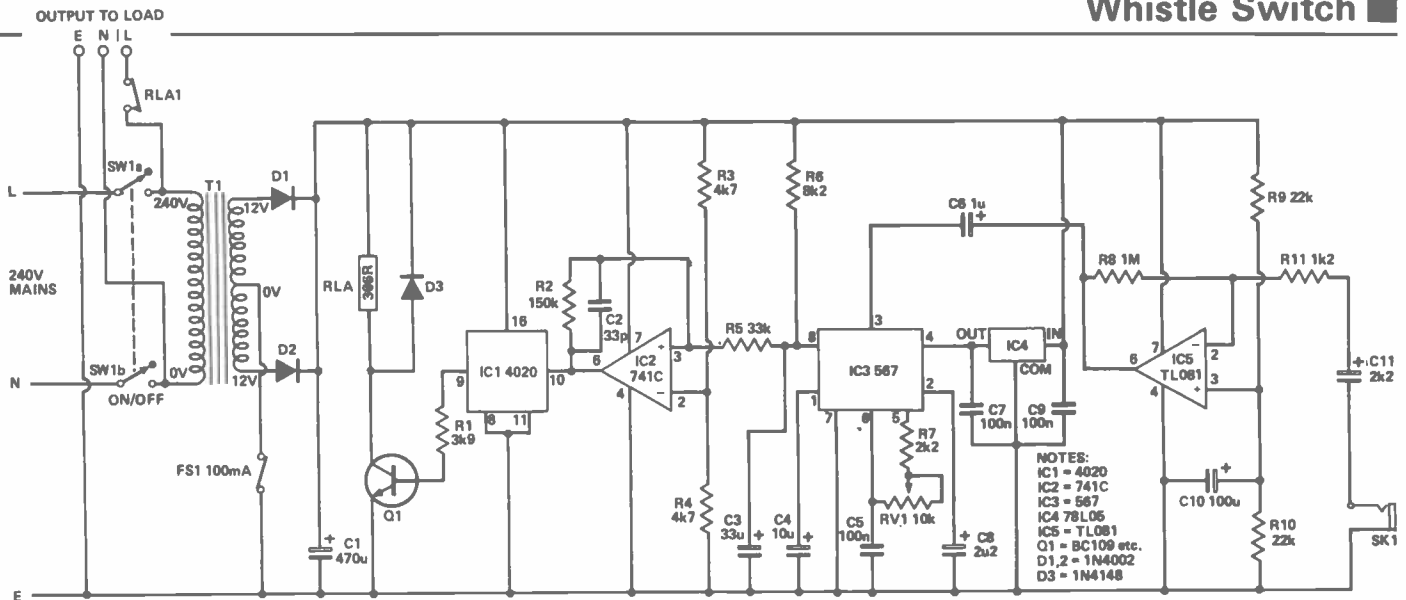


Figure 2. The circuit. SW1 disconnects the unit from the mains.

input signal is at a higher frequency than the CCO or leading it in phase, then the output voltage from the phase comparator increases slightly, and the amplified signal is fed to the CCO as an increased control current. This raises the operating frequency of the CCO so that it locks onto the frequency of the input signal and keeps in phase with it. Of course, this only happens if the input signal is reasonably close to the free running frequency of the CCO ie, within the locking range.

A similar thing happens if the input signal is at a slightly lower frequency than the CCO, but the output voltage from the phase comparator reduces as does the control current from the amplifier so that the operating frequency of the CCO reduces to match that of the input signal, and the CCO is locked in-phase with the input signal. The output from the phase comparator is actually a series of pulses, and the required control voltage for the amplifier is obtained by feeding these pulses to a lowpass filter which is comprised of R1 and C3. This simply gives an output voltage which is an average of the output potential from the phase comparator.

The CCO is used to operate an electronic switch, and it closes the switch on positive output half cycles and opens it on negative half cycles. The input signal is fed via this switch to a capacitor (C2), and if then the phase locked loop has achieved lock the input signal will only be connected to the capacitor during positive half cycles. This gives a strong positive charge on C2, producing a sufficiently large potential to activate the voltage comparator and switch on a transistor at the output of this circuit. If the input signal and CCO are not phased locked, the switch will sometimes conduct while the input is positive going, but it will conduct while the input is negative going as well, and just as often. This gives only a low charge on C2 since the positive and negative input signal tend to cancel out one another. The output transistor of the voltage

comparator does not therefore switch on.

This may seem a rather complex way of doing things when compared to a filtering and level detection arrangement, which it is, but the complexity is in the NE567 integrated circuit and only four discrete components are needed (R1 is within the IC), R2 and the three capacitors are discrete components). Also, using conventional filtering it would be difficult to obtain a similar level of performance. This arrangement has good sensitivity to any signal within the locking range of the PLL, but signals outside the locking range cannot activate the circuit. This gives the circuit what is effectively an ideal frequency response for tone decoding applications, and provides virtually complete immunity against spurious operation.

## The Circuit


The full circuit diagram of the Whistle Switch appears in Figure 2. As the unit will be left running continuously and has a significant current consumption even when the relay is not switched on, it would be impractical to power the unit from batteries, and a simple unregulated mains power supply is therefore used. This uses push-pull fullwave rectification, and smoothing is provided by C1.

The preamplifier stage uses a BIFET

operational amplifier, IC5, as a simple inverting amplifier having a voltage gain of nearly 60dB (1000 times). An output level of around 20 millivolts RMS is sufficient to drive the next stage of the circuit, and this obviously gives the unit a high degree of sensitivity. However, the preamplifier is designed for use with a low impedance dynamic (cassette type) microphone and the output level from one of these is usually no more than a few hundred microvolts even if the microphone is in quite close proximity to a loud sound. This high sensitivity is therefore essential in order to give the unit a good maximum operating range.

IC3 is the NE567 PLL tone decoder, and this is powered from the main supply lines via a 5 volt monolithic voltage regulator. This prevents the device from receiving an excessive supply voltage and also helps to avoid problems with the lock frequency range drifting. C5, R7, and RV1 control the centre frequency of the PLL, and using RV1 the centre frequency can be adjusted from about 700HZ to approximately 4KHZ. C8 is the lowpass filter capacitor and C4 is the charge storage capacitor in the output switching section of IC3.

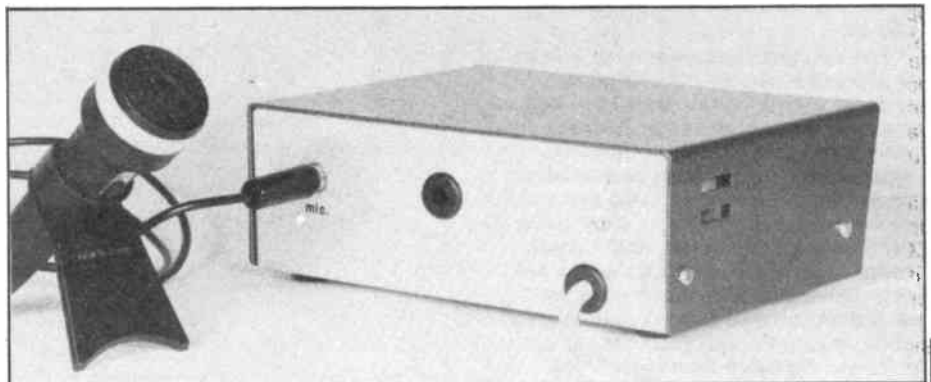Getting a system of this type to operate reliably is more difficult than it might at first appear, due to the fact that the input signal does not consist of perfectly gated tone bursts, and is likely to be contaminated with a





## Whistle Switch

substantial amount of noise. The NE567 gives excellent noise immunity, and an R-C filter at the output (R6 plus C3) largely overcomes problems with the input signal starting and finishing less than instantly. IC2 is used as a trigger circuit having a substantial amount of hysteresis, and the 4020BE divide by two circuit also has a trigger circuit at its input. A combination of all these measures give the unit excellent reliability.

Q1 is the relay driver and this is fed from the output of the first binary counter stage of IC1 via current limiting resistor R1 (IC1 is a 14 stage binary counter, incidentally). A set of normally closed relay contacts are used to switch the "live" supply lead to the piece of (mains powered) controlled equipment. An on/off switch is included, and this can be used to disconnect both the Whistle Switch and the controlled equipment from both sides of the mains supply.

### Construction

With the exception only of the controls and input sockets, the components are all mounted on a printed circuit board, as detailed in Figure 3. FS1 is mounted in a chassis mounting fuseholder which is bolted to the board. Similarly, T1 is not a printed circuit mounting component and must be bolted in place. It is advisable to use the specified relay since any other type would almost certainly necessitate a drastic redesign of the board before it could be used, and it might even be necessary to mount it off-board. Note that IC1 is a CMOS device and it should therefore be mounted in a (16 pin) DIL IC socket, and it should not be fitted into the socket until all the of the components have been mounted on the board. Handle this device as little as possible.

A case measuring about 150 by 100 by 50mm is suitable, but this represents about the smallest size that is capable of accommodating all the parts. SW1 and RV1 are mounted at opposite ends of the front panel (SW1 on the left — RV1 on the right), while SK1 is fitted at the left hand end of the rear panel (as viewed from the rear). The entrance hole for the mains lead is drilled low down at the opposite end of the rear panel and the exit hole for the mains output lead is drilled at roughly the centre of the panel. Both these holes should be fitted with grommets to protect the cables.

The printed circuit board is bolted to the base panel of the case and spacers about 12mm long are used so that the underside of the board is held well away from the metal casing. The final wiring-up is then completed. A short screened lead is used to connect SK1 to the printed circuit board. Be careful not to make an error when connecting the mains lead and SW1, and check this wiring carefully before switching on and testing the finished unit!

A low impedance dynamic


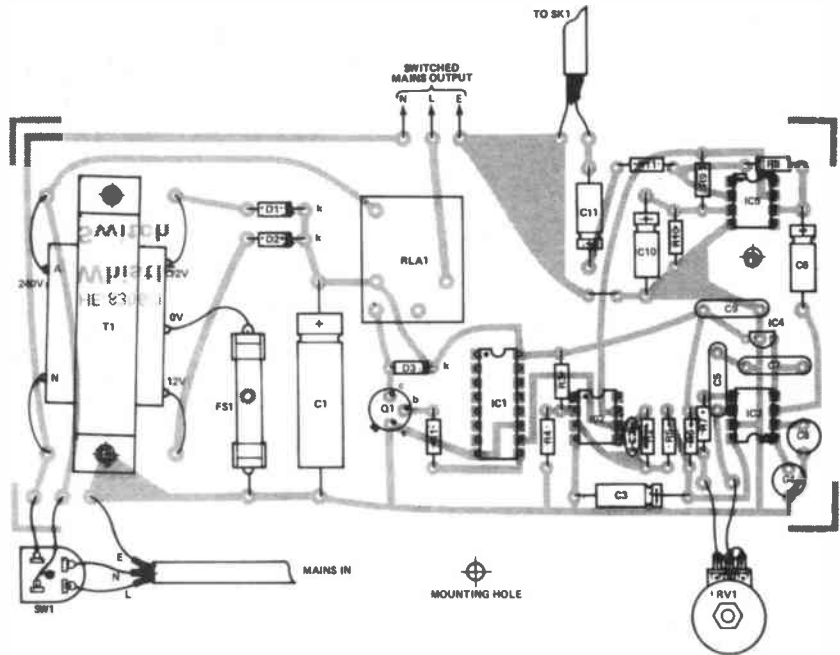


Figure 3. The PCB and components. T1 must be bolted down.

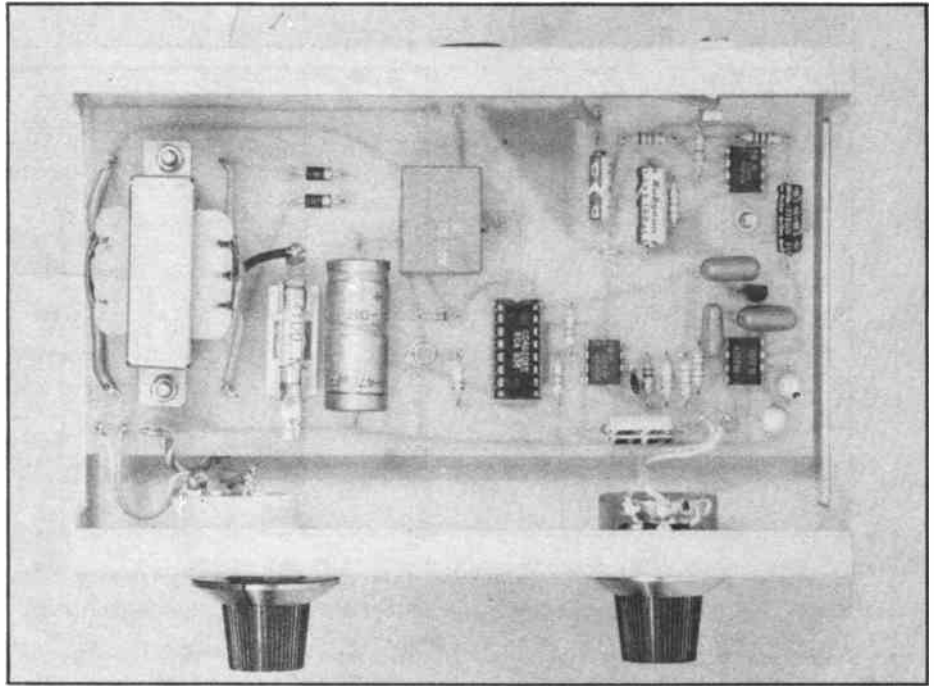

# Parts List

## RESISTORS

(All 1/4 watt 5% carbon)

R1	3k9
R2	150k
R3, 4	4k7
R5	33k
R6	8k2
R7	2k2
R8	1M
R9, 10	22k
R11	1k2

## POTENTIOMETERS

RV1	10k linear carbon
-----	----------------------

## CAPACITORS

(All axial electrolytic except as noted)

C1	470u 25V
C2	33p ceramic plate
C3	33u 16V
C4	10u 25V radial electro
C5, 7, 9	100n polyester
C6	1u 63V
C8	2u2 63V radial electro
C10	100u 10V
C11	2u2 63V

## SEMICONDUCTORS

IC1	4020BE 14-stage counter
IC2	741C op-amp
IC3	NE567N tone decoder/PLL
IC4	78L05 5V regulator
IC5	TL081 BIFET op-amp
Q1	BC109 etc.
D1, 2	1N4002 rectifier diodes
D3	1n4148 signal diode

## MISCELLANEOUS

T1	12-0-12 100mA secondary
FS1	20mm 100mA quick-blow
SW1	two-pole rotary mains switch
RL1	12V/400R coil see Buylines
SK1	3.5mm socket PCB; case, 150 x 100 x 50mm (see Buylines); 20mm chassis mount fuseholder; 2 x control knobs; 1 x 16-pin DIL socket; 6BA fixings, wire, solder etc.

BUYLINES .....page 34

microphone is connected to SK1 (inexpensive microphones of this type are readily available as replacements for cassette recorders). These often have a remote control switch and a moulded twin 2.5 plus 3.5mm jack plug (the 2.5mm plug connecting to the remote control switch). In this case it will either be necessary to change the plug for an ordinary 3.5mm type, or a "dummy" 2.5mm socket must be fitted at a suitable position on the rear panel.

RV1 can be adjusted to give operation at any practical frequency desired, and the correct setting can be found simply by whistling the desired operating note and adjusting RV1 from maximum to minimum resistance, but stopping when the relay switches on or off (it can assume either state at switch-on). It takes the unit a fraction of a second to operate, and RV1 should therefore be adjusted reasonably slowly so that it is not taken beyond the correct setting before the relay is activated.

The locking range of the phase locked loop is only plus and minus about 7%, and this gives excellent immunity to spurious triggering by general noise and household sounds, but it is also necessary to hit the right note with reasonable accuracy in order to operate the unit. However, this should not be difficult for anyone with a reasonable sense of pitch.

**PARNDON ELECTRONICS LTD.**  
Dept. 22, 44 Paddock Mead, Harlow, Essex. CM18 7RR. Tel: 0279 32700

**RESISTORS:** 1/4 Watt Carbon Film E24 range ± 5% tolerance  
Bandolered and colour coded. Full Range 1R0-10M.  
£1.00 per hundred mixed (Min 10 per value) **£8.50** per thousand mixed (Min 50 per value)  
Special stock pack 60 values. 10 of each **£5.50**

<b>1 AMP VOLT REG</b> +ve 5v, 12v, 15v, 24v — <b>£0.40</b> —ve 5v, 12v, 15v — <b>£0.43</b>	<b>3 1/2 Digit LCD Display:</b> 1 colon, 3 decimal points plus/minus sign and lo bat indicator. Complete with low power 7106 A/D converter display driver. Driver set <b>£8.95</b> Display <b>£3.50</b> Driver <b>£6.50</b>
--	--

**DIODES:** 1N4148 **£1.60** per hundred

**DIL SOCKETS** 8 pin — 10p. 14 pin — 11p. 16p pin — 12p. 18p pin — 19p. 20p pin — 21p. 22 pin — 23p. 24 pin — 25p. 28 pin — 27p. 40 pin — 42p.

**Full List Available — Send SAE**  
**ALL PRICES INCLUDE V.A.T. & POST & PACKING — NO EXTRAS**  
MIN ORDER — UK £1.00 OVERSEAS £5 CASH WITH ORDER PLEASE  
Same Day Despatch

**HORIZON ELECTRONICS**  
(Midlands)  
Dept H/H Charlotte St. Rugby Tel: 781338  
Prime quality. TERRIFIC PRICES. Mail order only

<b>REGULATORS (5/12/15V)</b> 100mA +ve 29p 1 amp +ve 33p 723 var 28p	<b>ZENERS (1.3 to 30V)</b> 500mW 13p 1.3 watt 13p	<b>DIODES</b> IN 4001 2p 4002 2p 4004 8p 4005 13p 4006 13p 4007 13p	<b>TRANSISTORS</b> BC107 8p BC108 8p BC109 8p BC177 15p BC178 15p BC179 15p BC182 7p BC183 7p BC184 7p BC185 7p BC186 7p BC187 7p BC188 7p BC189 7p BC190 7p BC237 8p BC238 8p BC239 8p BC240 8p BC1000 8p	<b>TOGGLE SWITCHES</b> 870 700 450 650	<b>LINEAR IC'S</b> 411 8p 412 8p 413 8p 729 8p 730 8p
---	---	---	--	--	--

## DURRANTS (ELECTRONIC COMPONENTS)

9 ST MARYS STREET, SHREWSBURY, SHROPSHIRE  
TELEPHONE 61239


ALL PRICES INCLUDE V.A.T. add 40p P&P

Resistors 1/4w 5% c/film all values 1p each (min 10); Resistors 1/2w 5% c/film all values 2p each (min 10); Capacitors (polyester) .001 MFD to .1 MFD 8p each; Capacitors (ceramic) 1pf to .047 MFD 6p each; Capacitor packs 100 polyester/ceramic £1.50; Resistor Packs 100 1/4w c/film 60p; Resistor/Capacitor Packs 100 mixed 90p; Bush Stereo Cassette Panel (new with diagram) £1.00; T.C.E. Stereo Decoder Panel (new) £1.00; Copper Clad Board 8 1/2" x 5 1/2" 75p; Copper Clad Board 4" x 5 1/2" 39p; Slide Switch D.P.D.T. (min type) 12p each 10 for £1.00; Reed Switch N/o contacts 15p each 10 for £1.20; M.E.S. Lampholders (screw down type) 10p each; Relays 24v coil 2 pole c/over 30p each; Holder for above 10p each; Connecting Wire Assorted Colours 50 mtrs 60p; Micro switch 10a contacts, lever type 35p; Micro Switch Burgess (Min Type) 20p; Bridge Rectifier 30v 350ma 25p each 5 for £1.00; Transistors BFR50 — BFY51 15p; ORP12 Light Dependant Resistor £1.20; Cassette Tape Counter Units 45p; Mains Filter 240v 15A £1.50; Terminal Blocks 12 way 25p; Stranded Connecting Wire: orange, brown or black 10 yds 20p; Heat Sink Compound 95p per tube; Soldering Irons 240v 25w £4.99; 100 mfd 63v Radial Capacitors 8p each 10 for 80p; 2.2 MFD 63v Axial Capacitors 5p each 10 for 40p; 100 Assorted Nuts and Bolts (S.A. & Metric) 25p

This is a sample of the many thousands of items in stock  
Price lists 15p & 25p P&P
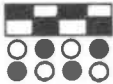
## Elen Electronics — DISCO

Tired of boring 3 & 4 channel lighting controllers.  
Then try our new 8 CHANNEL PATTERNMAKER  
for spotlights or lighting screens.



16 different sequential patterns including  
Catherine Wheel, Screen Writer, Checker & Light Train.

Kit comprises PCB & all components including 2K PROM &  
Monitor LEDs. Only £27.00 + VAT.

Hardware kit including case, 12 way socket & matching plug, mains  
lead etc. Only £9.50 + VAT.

Please add 60p P&P to order.

**ELEN ELECTRONICS**  
Unit 9, Telford OP. Centre,  
Halesfield 14, Telford, Shropshire  
Tel: 0952 585897

Further details on request

# MINIATURE TOOL SETS



## AT MINIATURE PRICES

Ideal for work on optical and electronic equipment, instruments and models. Japanese made, top quality metric tools in hardened and tempered steel, with fitted plastic cases. Swivel-top, chromium-plated brass handles. Not to be confused with similar cheap non-Japanese sets.

**SCREWDRIVER SET 113.** 6 plain screwdrivers, blades 0.9, 1.2, 1.8, 2.3, 3.0 and 3.5mm. Price £2.70.

**SOCKET SET 227.** 5 socket spanners, 3.0, 3.5, 4.0, 4.5 and 5.0mm. Price £2.80.

**CROSSPOINT/HEXAGON SET 305.** 2 Japanese crosspoint screwdrivers, sizes 0 and 1.3 Hex. key wrenches 1.5, 2.0 and 2.5mm. Price £2.70.

**COMBINATION SET 228.** 5 open spanners 4.0, 4.5, 5.0, 5.5 and 6.0mm. 5 socket spanners 3.0, 3.5, 4.0, 4.5 and 5.0mm. 2 crosspoint screwdrivers bit sizes 0 and 1.3 screwdriver bits 1.5, 2.5 and 3.5mm. 3 Hex. keys 1.5, 2.0 and 2.5mm. 1 scriber. 1 swivel-top driver/holder. Price £4.83. All prices include postage and 15% VAT

Ring for Access/Barclaycard  
Sales or send remittance to:



Light Soldering Developments Limited, 97-99 Gloucester Road,  
Croydon, Surrey CR0 2DN. Tel: 01-689 0574.

## Do you think that designing and understanding electronic circuits is beyond you?

The summer edition of Electronics Digest, *Gateway To Circuit Design*, provides a step-by-step introduction for the newcomer to the art of circuit design. Firstly, you'll be introduced to the commoner electronic components — but not in a passive way. Electronics is a practical subject, so *Gateway To Circuit Design* will enable you to build simple circuits for yourself, and take measurements on them (along the way learning how to use a multimeter). Once these introductions are over, *Gateway To Circuit Design* shows you what goes into the design of a wide range of electronic equipment — for audio, computing and electronic music, for instance.

*Gateway To Electronics* is an occasional popular series in Electronics Digest, published by Argus Specialist Publications. Previous issues in the series have concentrated on projects; now we'd like you to design your own!

At all good newsagents now or available by post from Electronics Digest, 513 London Road, Thornton Heath, Surrey.

## We'd like to show you that you're wrong



£1.85

# CLEVER DICK

Poor CD's in trouble, his brain all befuddled,  
Put him out of his muddle, by solving this puzzle.

Now here's a challenge for all crossword and puzzle fanatics. Let's have your answers then! All genuine and logical replies will be placed in a box and an answer selected by the fair hand of HE's editorial assistant. The reward? Oh, a binder . . . of course! The competition closes with the last entries received at the HE editorial office on 30th July 1983, and if no reasonable solution is submitted, the binder goes to the author, by default.

O Clever Dick!

*My first belongs to us all, slave or free  
My second concludes what is to be.  
My third is initially placed by you second.  
My fourth of all men is the end.  
With my fifth may the answer be seen,  
While my sixth lives and dies for its queen.  
Solve this riddle and justice be done,  
For my whole must be backed to be won.  
Guy Inchbald,  
Manchester.*

*PS Now at the last one further surprise:  
I have no desire for your glittering prize!  
A Spectrum cassette of the Hobbit would do,  
But I doubt such a reward may be granted by you.*

As for the Hobbit, you'd be amazed what the Wee Folk of the HE office can get up to. They'll be in touch.

Meanwhile, some people have strange ideas about what's witty and what's not . . .

Dear CD,  
*You wrote in the February issue of HE that you would award a Binder to the writer of the most witty letter: well, try this one.*

*I don't normally buy anything at Tandy (£1.19 for a 4011 IC is bad news), but I needed a piece of Veroboard like yesterday, so I risked it.*

*I went to the counter and asked if they had any Veroboard: "What board?" the man said, "I don't understand". So I pointed to a piece of perforated board and said "Like that but with copper strips across it". "Oh", he said, "If you can't see any we don't have any".*

*Tandy? Who needs them?  
M. Bronze,  
Corringham,  
Essex.*

OK. I tried it, but I don't see what's so funny. I can't believe you left the store in fits of laughter . . . did you? Prices like that are no joke!

It's not true, by the way, that I complain about hand-written letters. Of course I sometimes have to guess at words, which can be awkward!

Dear Clever Dick,  
*I think that it is appalling that a Hobby Electronics Binder costs £4.95. I'd rather spend the money on components and I'm probably not the only one! (Hint, hint).  
PS I'm only 13.  
PPS Sorry about the spelling.  
M. Myers,  
Cheltenham,  
Glos.  
PPPS ACE mag.  
PPPPS Please print this.*

A request I cannot refuse (to print the letter that is — free binders are another matter entirely).

I agree that £4.95 is a lot of money, but if you only knew what it costs to produce them, the time and effort, the painstaking craftsmanship . . . oh alright, you win, you can have one. But if it doesn't arrive you can blame it on your handwriting!

Dear CD,  
*I have just made the Stall Thief project (May issue) but don't know how to connect it to the points in the car, which is a Renault 4. I have tried a few likely spots, with the engine running, on the outside of the distributor but only saw sparks and received a healthy shock. Please explain how and where they are connected.  
Yours etc,  
SC,  
Hampstead.*

First of all, I can't imagine why you bought a Renault — don't you know it's French? — and second, I find it difficult to believe that anyone would actually want to steal one. As for your problem (the Stall Thief, not the car) Figure 2 in the article shows that the device is connected across the distributor

contact breaker. Not being a French Mechanic I can't do better than that. And since you regard a jolt from the ignition system as "healthy" you may as well continue to experiment with the engine running.

Personally, I prefer jogging.

In a recent issue, I referred a reader to HE's Book Service but apparently forgot to mention the price.

Dear Sirs,  
*In the May 1983 issue of Hobby Electronics magazine, in the Clever Dick feature, you make reference to a book on Long Distance Television Reception. Unfortunately no price was quoted.*

*I am interested in receiving two (2) copies of this book. Please advise price and delivery charge.*

*The most convenient way for me to make payment is by certified cheque in pesetas. I trust this is acceptable.  
S. L. Watkins,  
Malaga,  
Spain.*

Hmmmm. Long Distance Magazine Reception, eh? Not bad, not bad. My apologies to Mr. Watkins; the price is £1.95, and the order should refer to publication BP52. You should add £1 to the post and packaging charge and, if possible, make out the cheque in pounds, not pesetas.

As ever, I'm happy to try and answer any reasonable enquiry . . . but some questions simply leave me feeling blanche.

Dear Mr. Dicks,  
*I have only been interested in electronics for two months, now, so all this grovelling is quite new to me. Why do they do it? I would be inclined to send a cheque for £5 and ask for a binder.*

*P. Roberts,  
Yeovil,*

*Somerset.*

*PS HE is the best mag out (I've only just realised what HE stands for).  
PPS What are those cute cuddly looking balls that sometimes appear in your pages?*

I'm inclined to agree — especially since my binders are being purveyed to the public (that's you) for only £4.25, including postage and packaging! I'll leave it to another reader to try to describe our 'Beastie' cartoon characters; words fail me!

HE



# Extending the ACE

HE's Input/  
Output board  
supplies the  
extra RAM the  
ACE needs to  
control HEBOT or  
similar useful  
devices.

**Mike Lord**

If you are the proud owner of a Jupiter ACE then you will know that although it has 3K bytes of RAM fitted most of this is taken up by the screen and character set areas, leaving not a lot for your 'programs'. And you will probably know that FORTH was originally developed for control applications — like steering a telescope or guiding a robot — and may be interested in experimenting along these lines.

This project has been developed to help in both of these areas; by giving you an additional 2 or 4 bytes of RAM space, plus 8-bit input and output ports to control devices such as the HEBOT computer controlled robot.

Everything is on one printed circuit board which plugs onto the ACE's rear bus connector. If you don't want the I/O ports, then you can just build the RAM extension, or you could even leave out the RAM parts for the time being and just make the I/O ports.

**The Credit**

Figure 1 gives the complete circuit diagram of the add-on board. Looking at the RAM part first, this is provided by ICs 1, 2 and 3, ICs 1 and 2 are 6116 2K bytes CMOS static RAM chips, chosen because they are very easy to use — having no particular vices — and take very little power. These chips deal with a complete 8-bit byte at a time, the data being transferred into or out of the IC on the ACE's data bus lines D0-D7. Since each IC holds 2K (2048) bytes, eleven address inputs are needed to select a particular byte, and these come from the ACE's address bus lines A0-A10. To read data out of the chip, or to write new data in a 'low' pulse must be applied to the 'Output Enable' or 'Write Enable' inputs; these pulses are easily obtained from the ACE's

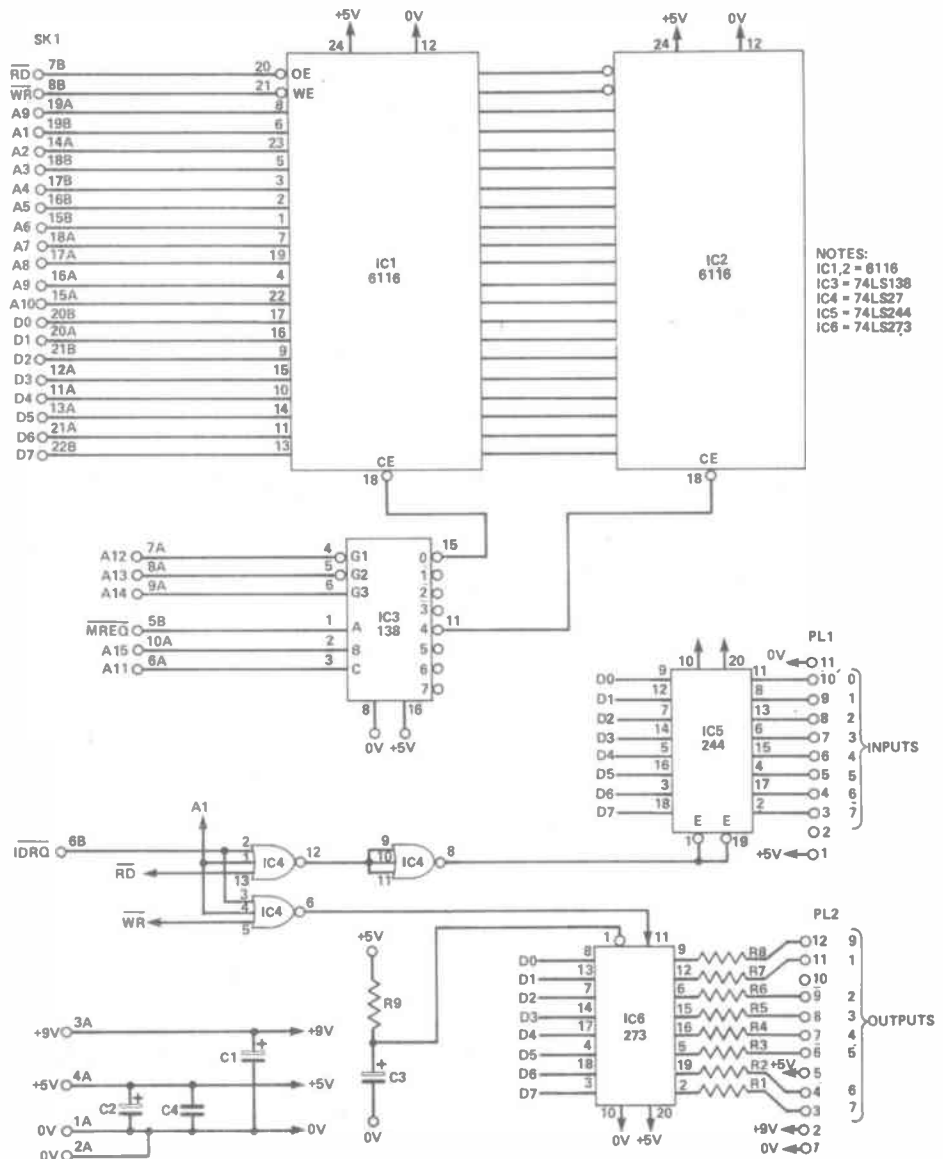


Figure 1. The complete circuit.

bus  $\overline{RD}$  and  $\overline{WR}$  lines. The other connections to the RAM chips are the  $\overline{OV}$  and +5V supplies, and the  $\overline{CE}$  (Chip Enable) input on pin 18, which must be low when data is being written to or read from the IC.

The  $\overline{CE}$  inputs to the two RAM chips are provided by IC3, which ensures that ICs 1 and 2 are only enabled when the ACE wants to access memory at the appropriate addresses. IC3 is a 'one out of eight decoder' having eight outputs which normally give out a 'high' logic level. When the chip is enabled by low level signals on its G1 and G2 inputs and high level signal on its G3 input, then one of the eight outputs will go to a low level, which output depending on the signal applied to the chip's A, B & C select inputs.

These A, B, C and G inputs are connected to the five most significant address lines from the ACE and to the  $\overline{MREQ}$  line, which goes low when the ACE wants to read from or write to a memory location (as opposed to an I/O location). The way they are connected results in IC1 being enabled whenever the address is in the range 4000-47FF (hex) and IC2 being enabled when the address is in the range 4800-4FFF. These addresses follow immediately after the addresses used by the RAM in the ACE itself, so that the new memory adds directly onto the existing directory and stack area.

The I/O ports are provided by ICs 4, 5 and 6. IC5 is a simple 8-bit tri-state buffer which, whenever it is enabled by a low level signal on pins 1 and 19, transfers whatever signals are present on PL1 directly to the system data bus lines D0-D7. At other times the outputs of IC5 are in a high impedance state, so as to not affect the data bus.

IC6 is an 8-bit latch which, when clocked by a pulse on pin 11, grabs whatever information is on the data bus lines at that time and holds it until the next time it is clocked. The eight outputs are fed through the protective resistors R1-R8 to the board output plug PL2. These resistors have been put in to prevent damage to IC6, in case any of the board outputs are accidentally connected together or to +5V, but they do limit the available output signals and so their values should really be chosen to give as much protection as possible depending on exactly what the board is driving. If it is driving TTL loads, then R1-R8 should be between 100 to 330 ohms each, but higher values (around 1kR) can be used when the board is driving light loads such as those presented by the HEBOT control circuitry.

R9 and C3 reset IC6 so that all of its outputs are at low level when power is switched on.

IC4 is a triple 'positive NOR' gate which is used here to provide the enable and clock pulses to ICs 5 and 6. It gives a low level 'enable' pulse to IC5 whenever the ACE reads from an I/O location with address line A1 to '0', and gives a clock pulse to IC6 whenever the ACE writes to an I/O location with address line A1 at '0'.

The I/O connectors PL1 and 2 carry +5V as well as the input/output signals; this comes from the regulator inside the ACE and not more than about 100mA should be drawn. PL2 carries the +9V unregulated line from the ACE's mains adaptor; again, not more than about 100mA should be drawn. If you look at Figure 2, you will see that the two holes on the board are labelled 'OV' and '+9V'. These let you connect an external higher-powered unregulated '9V'

## Parts List

### RESISTORS

(All 1/4 watt 5% carbon)

R1-8 .....	1kR
	(see text)
R9 .....	4k7

### CAPACITOR

C1, 2, 3 .....	4u7 25V
	radial electro
C4 .....	100n
	ceramic

### SEMICONDUCTORS

IC1, 2 .....	6116
	2K static RAM
IC3 .....	74LS138
	1-of-8 decoder
IC4 .....	74LS27
	triple 3-input NOR
IC5 .....	75LS244
	octal tri-state buffer
IC6 .....	74LS273
	octal latch

### MISCELLANEOUS

SK1 .....	edge connector
	see Buylines
PL1, 2 .....	12-way PCB plugs
	see Buylines
	1 x 14-way, 1 x 16 way, 2 x 20 way,
	2 x 24 way IC sockets; PCB; wire,
	sleeving, solder etc.

BUYLINES ..... page 34

supply if the devices you are controlling need more power than can be provided by the ACE's mains adaptor, but note that if you do connect such an external supply then it will also be powering the ACE, and so the ACE's own mains adaptor should not then be connected.

## Construction

The component layout is shown in Figure 2. A single sided printed circuit board has been used to keep the cost of the project down, but this has meant that 14 wire links have to be added, as shown, to complete all of the connections. These should be sleeved where there is a danger of accidental short circuits.

After fitting the links, the resistors R1-R9 should be soldered in place, followed by the IC sockets and then the capacitors. Note that the sockets used for ICs 3 and 4 *must* be low profile types.

The input and output connectors, PL1 and PL2, should be fitted so that their plastic mouldings are on the component side of the board with the short ends of the pins going through the board to be soldered on the track side. Two pins will have to be removed from PL1 and one from PL2, as only 10 and 11 holes respectively have been drilled in the board. The missing pins provide a polarising facility to reduce the chance of putting the mating sockets on wrongly.

The sockets to be used with the input/output plugs are purchased as empty 'shells', with loose contacts which are soldered onto the



## ■ Extending The ACE

connecting wires then pushed into the shell so that they latch home.

SK1 is a 25+25 way, 0.1in pitch double sided edge connector with wire-wrap pins. If you can't get exactly the right type then buy a longer one and cut it down to the correct length. The pins should be removed from the third position from one end and a polarising key fitted in their place (if you can't find a suitable key in the shops, then one can easily be cut from a piece of thick plastic). This polarising key is most important, as it is the only thing that will prevent you from plugging the board in wrongly, with possibly disastrous consequences. SK1 should be fitted so that it is square onto the PCB, and spaced so that the body of the connector is about 1/4in from the PCB.

If you want to build up the RAM part of the board then ICs 4, 5, 6 and R1-9 and also C1 & C3 and PL1, 2 need not be fitted. If you are starting small, then IC2 can be left out, resulting in only 2K extra bytes of RAM. On the other hand, if you are only interested in the I/O circuits then leave out ICs 1, 2 & 3.

### Testing It

Before plugging the board into the ACE, check it very carefully to make sure that the right components have been fitted the right way round — most important — that solder splashes or excess solder on joints have not caused any short circuits between adjacent tracks. The areas that this type of fault is most likely to have occurred are where tracks pass between the pins of ICs 1, 2, 5 & 6.

Once you are certain that it won't damage anything, you can then try the ACE with the new board plugged in. Remember to switch off the power before plugging anything in or out! It should behave exactly as before except that if you had added RAM then entering:

15384 @

should print 18432, if you have added 2K, or 20480 if you have added 4K bytes, and you will now be able to enter much longer dictionaries.

If you have equipped the board with the I/O circuits then you can test these with a voltmeter and a wire link. First, check that the outputs on pins 3, 4, 6-11 of PL2 are all at less than 0V4. Then set them all to the high level by:

255 253 OUT

and they should then be between 3 and 5 volts. To check the input circuits, use:

253 IN

which will print 255 if all of the inputs on pins 3-10 of PL1 are open, and lesser values if any or all of these pins are connected to 0V.

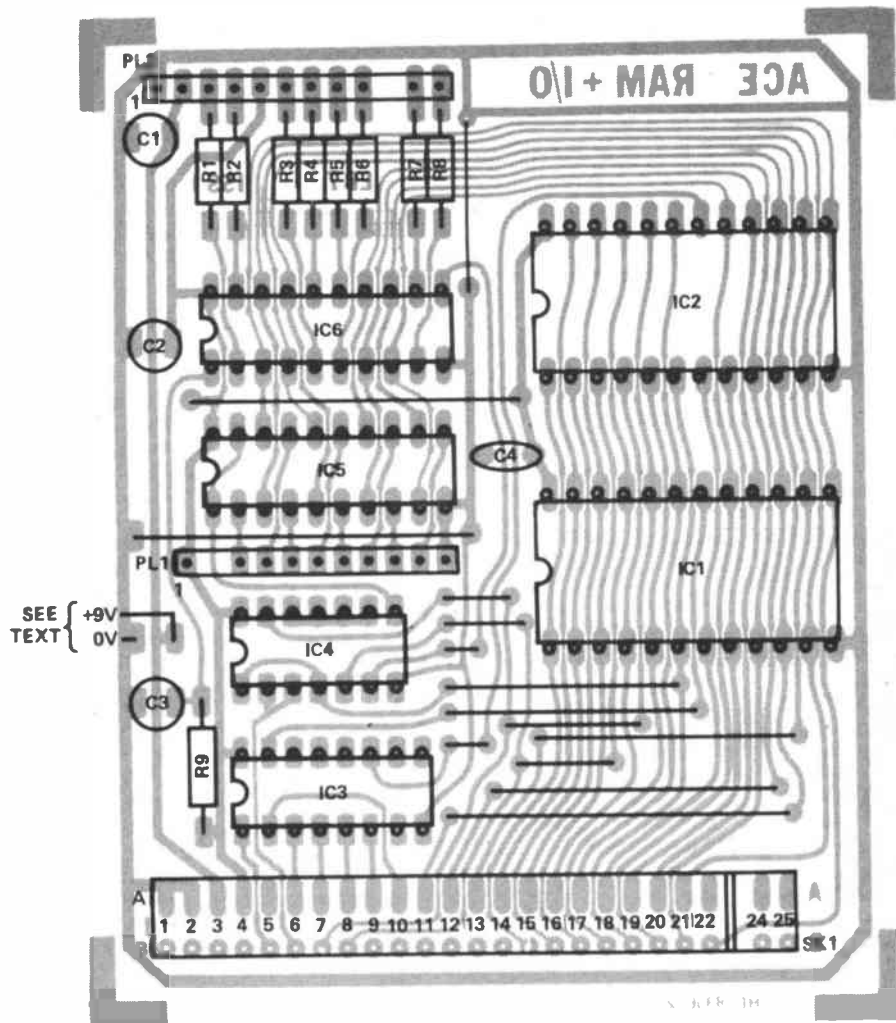


Figure 2. The PCB and components. Wire links are used to keep the board one-sided.

### Using The I/O

Both the input and the output ports are at I/O address 253 (actually they will appear at many addresses because only address line A1 is looked at, but 253 is a convenient value to remember) and are accessed by using the ACE FORTH words IN and OUT. For example,

253 IN

will put on the stack a value corresponding to the logic levels on the eight input pins, while

253 OUT

will set the eight output pins according to the value on the top of the stack.

Both the input and the output are 8-bit binary values which you can translate to and from decimal with the aid of Table 1, so that — for example — to set bits 1 and 3 of the output port to the 'high' level (1) and the rest to 'low' (0) you could use:

10 253 OUT

It is worth noting that FORTH's OR word works on a bit by bit basis, so

that we could have set output bits 1 and 3 to '1' by:

2 8 OR 253 OUT

And so does the AND word, which is very convenient when we want to examine the state of a particular input line;

253 IN 8 AND

leaves a value onto the stack which is zero only when input bit 3 is zero (bit 3 corresponding to decimal value 8).

TABLE 1

I/O Bit	Decimal Value
0	1
1	2
2	4
3	8
4	16
5	32
6	64
7	128

Table 2

PL1		PL2	
1	+5V	1	0V
2	***	2	+9V
3	IP 7	3	OP 7
4	IP 6	4	OP 6
5	IP 5	5	+5V
6	IP 4	6	OP 5
7	IP 3	7	OP 4
8	IP 2	8	OP 3
9	IP 1	9	OP 2
10	IP 0	10	***
11	OV	11	OP 1
12	***	12	OP 0


\*\*\* = pin removed for polarising

Table 3

HEBOT PCB	ACE I/O BOARD
RM1	PL2-11
RM2	PL2-10
RT	PL1-9
FT	PL1-8
LT	PL1-10
BT	PL1-7
P	PL2-6
OV	PL2-1
OV	PL1-11
+10V	PL2-2
H	PL2-4
T	PL2-3
LM2	PL2-8
LM1	PL2-9
L	PL2-7

Table 4

OUTPUT VALUE	CONTROL FUNCTION
0	HEBOT stopped, lights & beeper off.
5	Move forward.
6	Turn clockwise.
9	Turn anti-clockwise.
10	Move backwards.
16	Lamps on.
32	Pen solenoid on.
64	Low frequency beep.
192	High frequency beep.

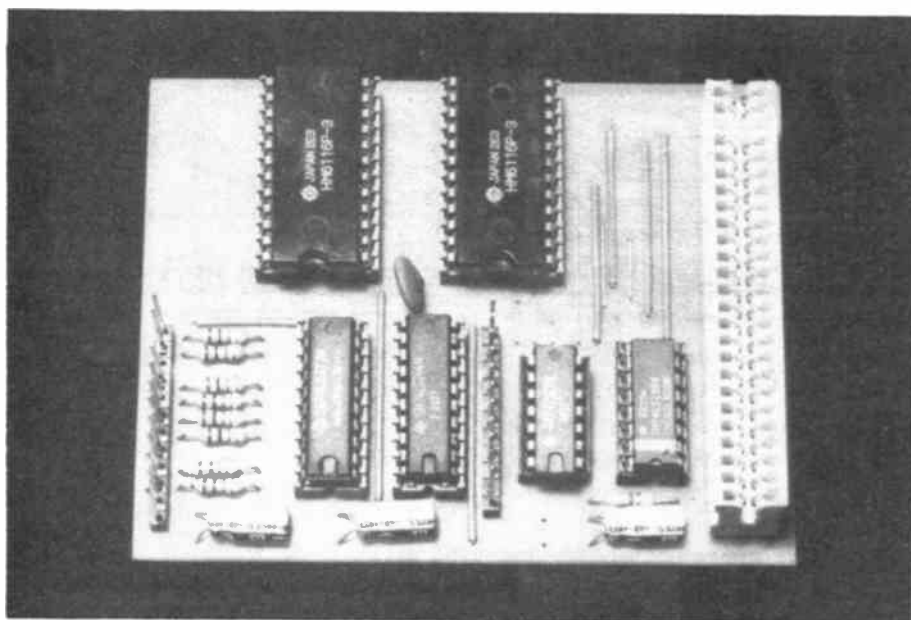

### Driving HEBOT

HEBOT (HE's computer controlled robot project published in the November 1982 issue) is an ideal vehicle for experimenting with the use of FORTH as a control language, using the input/output capabilities of this board.

Eight output lines are needed to control the motors, speakers, lights

and pen of HEBOT, and four input lines are used to monitor the touch sensors. These can be connected to PL1 and 2 as shown in Table 2. The ACE's mains adaptor will give just about enough power to drive HEBOT, as well as the ACE, as long as you don't want to operate the pen solenoid and avoid switching instantaneously from full forward to

full reverse. If you want to operate the pen or thrash about at high speed then a more powerful supply should be connected as described earlier.

Table 3 shows the decimal values to be output to get HEBOT to perform as discussed earlier these can be combined by adding the values or by making use of the OR word. Program 1 gives a simple program to make HEBOT move, beep and flash using keys W, E, S and 3 to control direction L to light the lamps and B OR H to beep. Pressing key Q will turn off HEBOT and end the program.

#### Program 1



```

: MATCH 3 PICK = IF
  ROT DROP SWAP
  ELSE DROP
  THEN;

: GO BEGIN
  0 INKEY
  6 ASCII E MATCH
  9 ASCII W MATCH
  10 ASCII S MATCH
  5 ASCII 3 MATCH
  16 ASCII L MATCH
  64 ASCII B MATCH
  192 ASCII H MATCH
  SWAP 253 OUT
  ASCII 0 =
  UNTIL ;
    
```

## BEASTIES

BY RH

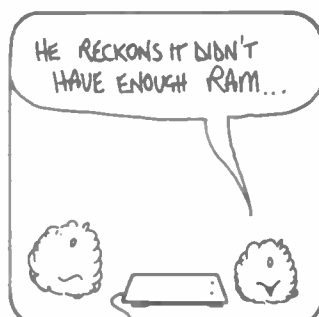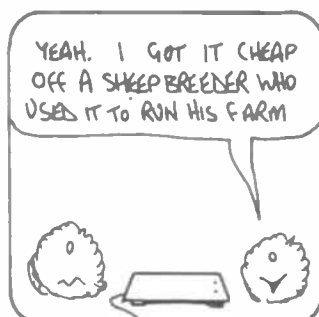



# MASTER ELECTRONICS NOW!

## The PRACTICAL way!

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to start or further a career in electronics or as a self-employed servicing engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write personally at any time, for advice or help during your work. A Certificate is given at the end of every course.

You will do the following:

- Build a modern oscilloscope
- Recognise and handle current electronic components
- Read, draw and understand circuit diagrams
- Carry out 40 experiments on basic electronic circuits used in modern equipment
- Build and use digital electronic circuits and current solid state 'chips'
- Learn how to test and service every type of electronic device used in industry and commerce today. Servicing of radio, T.V., Hi-Fi and microprocessor/computer equipment.



**New Job? New Career? New Hobby? Get into Electronics Now!**

**FREE!** COLOUR BROCHURE

Please send your brochure without any obligation to

I am interested in:

HE/8/821

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

COURSE IN ELECTRONICS as described above

RADIO AMATEUR LICENCE


MICROPROCESSORS OTHER SUBJECTS

LOGIC COURSE

POST NOW TO: BLOCK CAPS PLEASE

**British National Radio & Electronics School** Reading, Berks. RG1 1BR

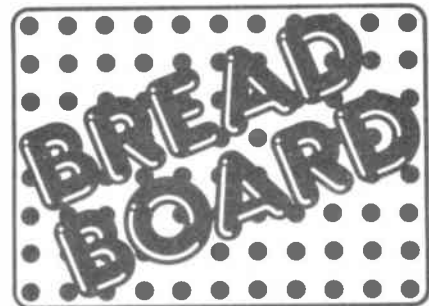**If you missed out on Breadboard '79, '80, '81 and '82..... Now's the time to catch up with BREADBOARD '83**



The premier electronics show for the enthusiast. Moved this year for your convenience and comfort to the Cunard International Hotel, Hammersmith, London W6

Friday November 25th 10am - 6pm  
 Saturday November 26th 10am - 6pm  
 Sunday November 27th 10am - 4pm

Why not bring the family to the show and enjoy a weekend in London? We have arranged a complete hotel package for our visitors to the exhibition. All inclusive rail tickets also available. Send now for details of what we, the organisers, can offer you.

Write to:  
 Breadboard '83  
 ASP Exhibitions  
 145 Charing Cross Road  
 London WC2H 0EE

**This year's features include**

- Computer controlled model railway competition. (send off for entry form now)
- Kits to build all sorts of projects.
- Magazines and books covering most aspects of electronics.
- Components and tools at bargain prices.
- Technical advice on electronics projects and Ham Radio technique.
- Clubs/User groups for amateur electronics and computing
- Lectures by professionals on a wide range of topics. eg. Basic Tuition For Beginners,
- Holography and Producing Printed Circuit Boards.


# CAREERS IN ELECTRONICS '83

**Steady nerves, high standards of engineering achievement and no illusions about glamour are the basic requirements for getting into the broadcasting business.**
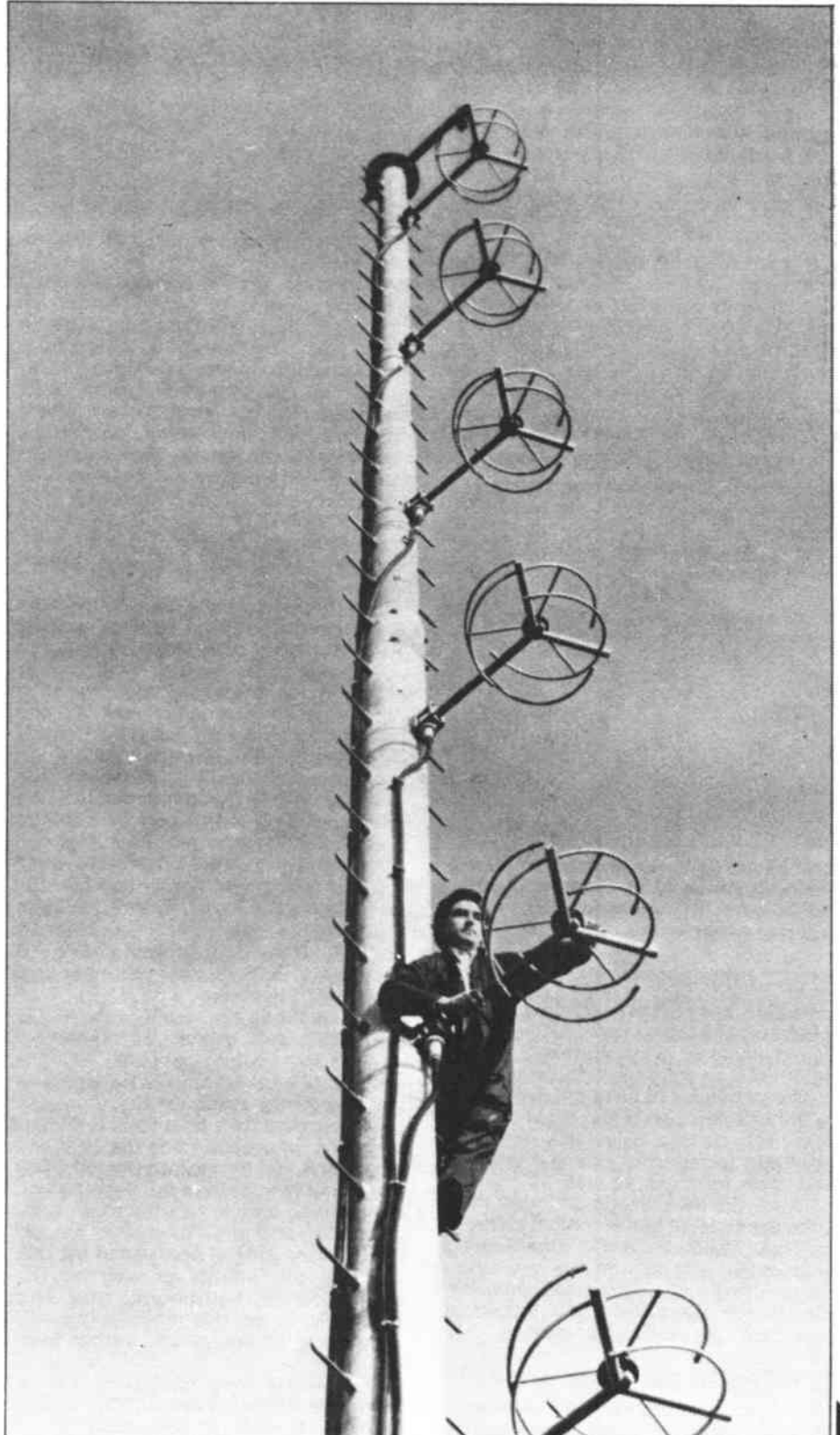
#### **Helen Armstrong**

MANY CAREERS in electronics make highly specialised, even rarified, demands on the engineer, enabling him or her to work safely within a narrow field. In the world of broadcasting, this is far less likely to be true. Broadcasting is one of the most competitive of all industries. On the one hand, it feeds the constant public demand for new ideas and entertainment, calling for continual experimentation, even innovation, with new effects and equipment and, on the other hand, the media is enormously self-publicising by its very existence, attracting talent from many fields from all over the country. So competition to get in is fierce. To compensate for this possibly discouraging picture, broadcasting companies are less likely to be looking for the brilliant theoretician who cannot wire up a plug, and more likely to take the self-motivated enthusiast with reasonable qualifications and a proven personal interest in a relevant activity: amateur radio, sound recording or film-making, to take some obvious examples. The vivid — and possibly apocryphal — description of the ideal trainee engineer: "A third class degree who can get an outside broadcast truck out of a bog" may not tell the whole story, but it illustrates the kind of practical problem which a broadcast engineer may be faced with.

With the expansion of the telecommunications industry during the past decade, the need for a supply of able engineers and technicians has grown in fits and starts. The arrival of the video boom and new television companies like Channel 4 is currently opening up, by direct and indirect means, more opportunities in broadcasting in general than for some time, providing some of the most varied careers in engineering.



### IBA And BBC

There are, as you might expect, a number of categories of technician and engineer employed in the industry. The two big transmitting organisations in the UK, the BBC (British Broadcasting Corporation) and the IBA (Independent Broadcasting Authority) have very similar structures where engineers are concerned, except that with the BBC the studio and transmitter operations are contained in the same organisation, whereas with independent TV and radio, the IBA operates the transmission networks, while various private companies operate the studios.

In this month's issue, we are going to by-pass the studio side — which would partially tend to attract engineers perhaps with more creative yearnings, who want to work with cameras, sound and video equipment — and look at the engineering jobs on the transmission networks in the two broadcasting companies.

It is worth noting that the IBA, having a smaller number of jobs on offer, advertises its posts less widely than the BBC. While the BBC may advertise in specialist magazines, and also (naturally) in *The Listener*, as well as advertising for trainees through college and local authority careers offices, the IBA restricts its advertising, which therefore reaches the press more rarely.



Part of the IBA's Harman Engineering Training College, in Seaton, Devon, the centre of operations for their training programme.

In both cases however, if you know what sort of a job you are looking for, or would like to train for, and what kind of qualifications you have or hope to have, it can be helpful to send an application to the relevant part of the organisation. Don't rely on this, however — keep an eye open for specific jobs and courses and apply for these as well.

When the IBA needs trainees they circulate schools and technical colleges on the "Milk Round", interviewing prospective candidates on the spot. When they do advertise, amateur electronics magazines and the local press are two media they choose.

### Getting In Training

The BBC puts its trainee engineers through a course which starts with a



Taking test measurements on a transmitter during on-the-job training.

twelve week stint at their Engineering Training Centre at Wood Norton in Worcestershire and then continues on the job, depending on their specialisation. Training includes further stints at the training centre and, particularly in transmitter work, trainees will be moved round the country to some extent. Their specialist training for engineers is registered with the IEE and counts towards the qualification of Chartered Engineer and membership of the IEE. Trainees work towards attaining Engineer status within three years.

The IBA recruits one group of trainees every year, and to fill jobs as needed. Their training programme begins in June and takes in four stages over eighteen months. This begins with a nine-week induction course at the Harman Engineering Training College in Devon, and concentrates on broadcast engineering, especially the systems used by Independent television and radio. This is followed by a stay at one of their transmitting stations, and after that a full-time two-term polytechnic course. The last six months concentrates on Transmission Technology, again at the Harman college. The course concludes, if successful, with your appointment as a Broadcast Engineer.

Non-qualified engineers beginning at the BBC are known as Technical Assistants. Young people — this effectively includes anyone from college leaver age up to about thirty — can begin a career as a broadcast engineer by acting as assistants to the qualified engineers, and training on the job. They work chiefly at setting up, aligning and maintaining broadcast equipment, both in London and at various sites around the country. This of course can include work in the studio as well as the transmission equipment, but the emphasis is on the maintaining and developing of equipment, rather than operating it.

The basic requirements for a Technical Assistant are GCE 'O' levels, grade A, B or C, or CSE grade 1s, in

English, Maths and Physics, as well as "A" level study (or the equivalent) in Maths and Physics. English, plus a TEC Certificate or Diploma, or a City and Guilds Part 1 in Telecommunications, or an ONC/OND in Electrical or Electronic Engineering can be considered. As well as this, a keen amateur interest in and knowledge of an electronic-based subject is effectively vital. The minimum age for appointment is 18, and normal hearing and colour vision are essential. For the Transmitter Department, especially, a driving license is an asset.

### Qualified Opportunities

The BBC also takes on qualified engineers for a wide range of jobs. Transmitter Engineers are needed for the maintenance and operation of complete transmission stations around the country, including SHF link equipment, receivers, RF standards converters, stereo encoders, digital equipment for synchronisations and pulse code modulation signals, low and high voltage switching gear, generators, aerials, cooling systems, test equipment and the transmitters



An important factor in all broadcast work is learning to work as a team, as well as using individual initiative.



Constant monitoring of signals is the basis of transmission work.

themselves. There are opportunities to work on both analogue and digital, valve and transistor equipment. The work is usually based at transmitting stations often in isolated areas around the country and needs a fair amount of mobility from day to day.

There is a Research Department where new techniques and systems are developed for use by the whole organisation. The Radio Frequency Group deals with the business of transmitting from the stations to home receivers. The Transmission Group deals with long-distance transmission and signal coding of all sorts. In the Design Department the Transmission Group designs new equipment for transmitting, monitoring and controlling, and the Transmitter Capital Projects Department commissions and sets up new transmission links.

Communications engineers based in London or other main regional centres maintain the radio and TV links between studio and transmitters, and also international links, including satellite links at short notice — very demanding work.

As a qualified engineer, you will need to have at least a degree, an HND or HNC



One field of transmission engineering is experimental work with satellite transmissions. This is an outside broadcast transmitter/receiver.

in electronics or electrical engineering, or physics or a City and Guilds Full Tech Certificate in Telecommunications or a TEC Higher Certificate or Diploma in Electronics or Telecommunications. For work on R&D or Capital Projects a first or good second class degree is needed.

## An Expanding Business

The IBA's requirements for both trainees and engineers are very similar. They specify City and Guilds Full Tech, HNC or HTC or CNAA degree in Electrical or Electronic engineering as basic qualifications for trainee Broadcast Engineers, and recruit qualified engineers on an ad hoc basis.

Broadcast Engineers operate and maintain the IBA's 750-and-growing transmission stations; some are based at their four Regional Operations Centres, and are concerned with monitoring and operating transmission. The majority of Broadcast Engineers are based at one of the twenty-two maintenance bases and work as part of a Mobile Maintenance Team, visiting transmitters within a certain range. As well as signal measuring, repairs, maintenance and trouble-shooting, Broadcast Engineers are involved in setting up new transmitters at the rate of about one a week, countrywide; and the expansions brought about by Channel 4 and increasing local radio stations are both widening the scope of the services provided and bringing in new engineering techniques.

The central planning and control centre is at the Engineering Headquarters, Crawley Court, Winchester, where there are also sections dealing with new developments and experimental electronics, including digital work.

## Getting In Touch

If you are interested in a career in broadcasting, then the first step is to write to the Personnel Officer of the

organisation (or organisations!) that you would like to work for, stating your qualifications (or potential qualifications, if studying) and interests. The demand for engineers of the right calibre is high at the moment, and likely to remain so for a long while, so now is a good time to be planning towards a broadcasting career. All the broadcast companies, both those we have looked at here, and the television companies and independent video companies, can afford to choose candidates of the highest calibre and posts are usually filled by people holding more than the basic qualifications are kept to a level which any bright student of engineering can fulfil, to encourage enthusiastic people to apply, since the broadcasting organisations are looking for the right people, rather than for a sheaf of paper qualifications.

Both the BBC and the IBA produce booklets laying out the requirements — and rewards — for engineers which you should look at before making a speculative application, or if planning a course of study. The two addresses you need to know are:



Inside IBA's Television Transmission Laboratory, students learn how to operate equipment used at the transmitting stations.

The Personnel Officer,  
The IBA,  
Crawley Court,  
Winchester,  
Hants.

The Engineering Recruitment Officer,  
BBC,  
Broadcasting House,  
London W1A 1AA


You can also look in the engineering and audio press, and consult your college careers office and local Education Authority careers office, where vacancies will be on file.

Our thanks to the BBC, IBA and Central London Careers Office for assistance with this feature. Pictures reproduced by kind permission of the BBC and IBA.



# HOME COMPUTERS

## AQUARIUS

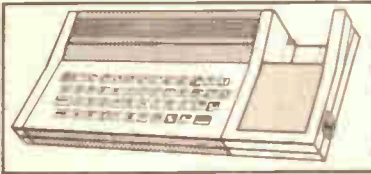

**AQUARIUS:** The brand new Aquarius Personal Computer is part of Mattel Electronics latest developments in advanced technology and offers full home computing facilities, as well as extensive game play, using a very wide range of plug in cartridges. Since Aquarius is a Mattel Electronics product, it benefits by the company's wide experience of producing high technology equipment, as well as their game programming expertise which is evident from the advanced games which have been produced for the Intellivision. Aquarius costs £79 and comes with microsoft basic built in. It is so simple to use that you'll be writing your first programs within minutes of taking the machine out of its box. You can even record the programs on your own cassette recorder at home, so you can use them again at a later date. Most available domestic tape recorders are compatible with the Aquarius.

**A POWERFUL MACHINE:** For all its simplicity, it is also very sophisticated. It has a Z80A processor and 8K of built in ROM as well as 4K of RAM, which is user expandable to 52K. It has a display of 40x24 characters, and a graphic resolution of 320x192 with a total character set of 256 (including the complete ASCII set with upper and lower case letters, numbers and additional graphic symbols). The keyboard has 49 full stroke moving keys, unlike some of the cheaper machines which have membrane keyboards. The size of the machine (excluding any of the additional peripherals), is 13"x6"x2".

**PERIPHERALS:** It is very easy to increase the capabilities of your Aquarius as all the peripherals plug straight into one another. You can add a Printer, a Modem, a Data Recorder, Mini Expander and other items. All of the peripherals are very easy to install and what is more, they're easy to use. But the best news of all is, they're easy to afford.

**CPM OPERATING CAPABILITY:** The Aquarius is capable of being expanded to 52K RAM and later in 1983 a disk drive will be available for it, with the commercial CPM business operating system. This will allow you access to one of the largest software libraries in the world, with literally hundreds of programs available for you to use.

**CARTRIDGES:** Various sophisticated programs will be launched on plug in cartridges such as a Visicalc type spreadsheet and a word processor. In addition there will be dozens of games and utilities and alternative languages such as Logo, which combined with the built in microsoft basic gives an unbeatable combination of high quality programming ability.

**MATTEL AQUARIUS - £68.70 + VAT = £79**

**£79**

## ATARI 400/800



### NEW LOW PRICES

**ATARI 400/800:** With the Atari Personal Computers, you can play the ultimate in T.V. games, teach yourself new subjects or skills, balance budgets, and even write your own computer programs in Basic.

**SPECIFICATIONS:** Both the Atari 400 and 800 can display in up to 16 colours, each with 16 intensities. They have four independent sound synthesizers for music tunes/game sounds, giving four octaves with variable volume and tone control on your T.V.'s speaker. The display graphics

are of amazing quality, having a detailed resolution of 320 x 192, comprising 24 lines of 40 characters. Atari personal computers have a standard 10K ROM operating system. In addition the standard Atari 400 (£149) comes with 16K of RAM, and the expanded version with 48K (£198). The Atari 800 (£299) comes with 48K as standard. Both the 400 and 800 are now supplied with a FREE £40 Basic Programming Kit, which includes the Basic Programming Cartridge, as well as a 120 page Basic Reference Manual and the 184 page Self Teaching Manual by Bill Carris called 'Inside Atari Basic', so you can begin programming straight away, without buying any 'extras'. Even a mains plug is supplied!

**OVER 500 PROGRAMS AVAILABLE:** The Atari computers are supported by well over 500 programs available for your use, a larger selection than you will find on any other television game or home computer! The wide selection puts Atari way ahead of the competition. Just fill in the coupon and we will be pleased to send you a full price list which gives details of our range of software available for entertainment, home education, programming and home office use. We think you'll agree when we say it's quite impressive.

**100 FREE PROGRAMS FROM SILICA SHOP:** If you buy your Atari Home Computer from Silica Shop, you will receive a FREE presentation pack of 6 cassettes, containing 100 programs including games, utilities and demonstrations. A 16 page booklet giving full details of all of these programs is available on request. If you have already purchased your computer elsewhere you can buy the set of 6 cassettes for £30. What's more, Silica Shop offer a two year guarantee on all computers as well as a FREE joystick. This adds up to a great offer that we believe can't be beaten or matched by any of our competitors.

**ATARI 400 16K - £129.57+VAT=£149**  
**ATARI 400 48K - £172.17+VAT=£198**  
**ATARI 800 48K - £260.00+VAT=£299**

**£149**

## COLECOVISION



**THE SYSTEM:** The CBS Colecovision offers new standards in video game play. The excellent graphics are well implemented with arcade titles such as Zaxxon, Lady Bug, Gorf, Wizard of Wor, Carnival, Mouse Trap and the lovable Smurfs. The console comes supplied with a three screen arcade quality version of DONKEY KONG. Parker and other companies have also announced ranges of cartridges for Colecovision, to further enhance the wide range of quality titles available for this new television games machine.

**THE CONSOLE:** The CBS Colecovision video games system has advanced technology which produces superlative graphics resolution and excellent sound effects. The styling of the console and hand controllers has been carefully researched; the console is designed to complement modern hi-tech equipment, and has clear features for easy operation. The hand controllers allow fingertip control via the 8 direction joystick, and feature 2 independent fire buttons. The push button keyboard is used for game selection and for game control with some cartridges. The hand controllers are detachable and are connected to six feet of telephone coil cable, storing neatly away in the console when not in use.

**ATARI EXPANSION MODULE:** The Atari converter module allows Atari VCS software cartridges to be played on the Colecovision console, allowing owners the freedom to purchase from the extensive range of Atari compatible cartridges. It also means that existing Atari owners can buy the CBS Colecovision games system without discarding their software library. Silica Shop offer part exchange facilities if you wish to upgrade.

**TURBO EXPANSION MODULE:** The Turbo Driver Expansion Module allows you to actually drive the vehicle that appears on your T.V. screen. The module consists of a steering wheel, dashboard and accelerator pedal. One hand controller is mounted on the dashboard to provide a gear change unit. The module comes complete with a Turbo Driver cartridge, the first of several cartridges to make use of the module, which provides all the action of sitting in the driving seat. This facility is unique to CBS Colecovision.

**HOME COMPUTER EXPANSION MODULE:** The Home Computer Module scheduled for late 1983, allows conversion of the games unit into a sophisticated Home Computer. This flexibility of design is an important feature of the CBS Colecovision System.

**COLECOVISION - £127.82 + VAT = £147**

**£147**

# VIDEO GAMES

## VECTREX



**THE SYSTEM:** Vectrex is a totally unique Home Arcade System, which has been exclusively designed and engineered to duplicate real arcade game play. Complete with its own monitor display, Vectrex won't cause any arguments over the use of the family's television because it has its own built in screen.

**THE SCREEN:** Vectrex does not use ordinary display techniques, instead it uses vector scanning to control the images on the screen. With this scanning method, the gun only updates the area of the screen that has changed, whereas a normal T.V. re-transmits the ENTIRE screen 50 times a minute. It is this that gives Vectrex its speed, and means that very little computer power is required for screen control, and the results provide very fast responding and clear images. These 'Vector Graphics' are used in several arcade games such as Asteroids and Battlezone, to give you incredibly high resolution and quality. Vectrex brings all of this from the arcade right into your living room. The Vectrex screen is capable of displaying 80 columns by 40 lines, which is significant to the extensive developments planned for the system.

**EXCITING SOUNDS AND ELECTRONICS:** Vectrex has an advanced microprocessor with more speed and power and exciting effects than many home video games systems.

**REAL ARCADE CONTROLS:** Vectrex has a unique control panel, similar to those used in many real arcade games, with 4 concave action buttons and a full 360° self centering joystick. This control panel has a 4 foot detachable cord for maximum player freedom.

**REAL ARCADE GRAPHICS:** Vectrex has its own 9 inch vertical screen and unlike a conventional T.V. screen, uses advanced display technology to achieve brilliant, high resolution imagery and superb game play never before possible. The Vectrex display provides special effects too, such as 3-D rotation and zooming in and out, which a regular T.V. cannot match. Using a black and white monitor, each Vectrex game comes supplied with its own coloured plastic screen overlay to add to the excitement of game play. The range of Vectrex cartridges (£21.95 each), gives a good selection of arcade games such as Berzerk, Scramble, Rip-Off and Bomber Attack. Vectrex comes complete with a fast paced 'Minestorm' game built into memory.

**VECTREX:** Vectrex has an advanced state-of-the-art microprocessor with more speed than other T.V. games.

**VECTREX - £129.57 + VAT = £149.00**

**£149**

### WHO ARE SILICA SHOP?

Silica Shop are one of the leading specialist suppliers of Video Games & Personal Computers. We consider first our service, to those who already own or to those who are interested in any products in our range, cannot be matched by any other supplier. Just look at what we have to offer:

- **SHOP PROMOTIONS FROM FACILITIES:** we offer a 10% discount on all purchases over £50.00.
- **SHOP OPENING HOURS:** we are open 10.00 am to 6.00 pm, 7 days a week, but closed at 1.00 pm on Thursdays and 1.00 pm on Fridays.
- **MAIL ORDER:** we are a specialist mail order company and are able to supply goods direct to your door at the lowest price.
- **FREE FIRST CLASS DELIVERY:** all orders are sent Free and Postage FREE, most of them being dispatched by FIRST CLASS POST within 24 hours of your order.
- **MONEY BACK GUARANTEE:** we offer a 1 year guarantee on all our products, with the exception of our video games and software.
- **PART EXCHANGE:** we will offer you up to one third of our current selling price in part exchange on your old equipment, including our Atari computers.
- **BEHIND THE SCENES:** we offer a 1 year guarantee on all our products, with the exception of our video games and software.
- **COMPETITIVE PRICES:** both our prices and service are very competitive. We will meet and beat the price of any other supplier who sells the same product.
- **HELPFUL ADVICE:** our staff are always available to give you advice on the suitability of various products for your requirements.
- **SERVICE PARTS:** we maintain an extensive stock of service parts for all our products, including our Atari computers.
- **ATARI SERVICE CENTRE:** we are now an authorised Atari service centre and can therefore assist you with all your Atari computer problems.
- **2 YEAR WARRANTY:** we offer a 2 year warranty on some manufacturers' 12 month guarantee.
- **VIDEO GAMES AND COMPUTER CLUBS:** we offer a full membership service to all our video game and software users. This includes access to our extensive stock of software, a monthly newsletter, a free home visit to help you with your equipment, and a free home visit to help you with your equipment.
- **OVERSEAS ORDERS:** we regularly send goods overseas and use a reliable despatch service. Please note that we do not accept orders from outside the UK.
- **PAYMENT:** we accept Advance Bank Orders, Cheques, Personal Cheques, Credit Cards, as well as cash. However, please note that we do not accept orders from outside the UK.
- **CREDIT FACILITIES:** we also offer credit facilities with varying periods up to 12, 24 or 36 months. Please send for our FREE brochure and a credit application form.



**SILICA SHOP LIMITED, Dept ZHE 0883,  
 1-4 The Mews, Hatherley Road, Sidcup, Kent, DA14 4DX  
 Telephone: 01-309 1111 or 01-301 1111**



# VIDEO GAMES

# ATARI

ATARI VCS (2600) - THE NO 1 BRAND LEADER IN THE U.K.

**ATARI:** The Atari Video Computer System known as the Atari VCS or the 2600 has now become the T.V. game brand leader. In the U.K. there are over 700,000 owners of the VCS with access to a range of over 200 different plug in cartridges, each having a multitude of different variations and difficulty levels. Every system comes complete with the main console, two individual joystick controllers, a pair of paddle controllers, aerial splitter, sound adaptor and a 27 game Combat cartridge. It gives you bright crisp graphics, realistic sound effects and even specially designed circuits for the protection of your Television Set.

**SECONDHAND GAMES:** We currently have several secondhand Atari VCS units in stock which we are selling for only £49 (inc VAT). This price includes the Console, with Combat Cartridge and all the accessories, as well as a 12 month guarantee. We also have stocks of several secondhand cartridges many at half price (all with 12 months guarantee). We will normally buy back secondhand units and cartridges at one third of our standard price. **£49**

**EXTENSIVE CARTRIDGE RANGE:** The Atari VCS is so popular that in addition to Atari's own cartridges, there are over 150 compatible cartridges, produced by at least a dozen different third party manufacturers. Silica Shop has one of the largest cartridge selections available in the U.K. Our range of over 200 titles (printed either side of this column), includes items in stock now, as well as many of the new releases for later in 1983.



dozen different third party manufacturers. Silica Shop has one of the largest cartridge selections available in the U.K. Our range of over 200 titles (printed either side of this column), includes items in stock now, as well as many of the new releases for later in 1983.

**SILICA ATARI CLUB:** Silica Shop has over 20,000 Atari VCS club members registered on our computer. As a specialist company we are able to obtain advance information about new developments and send detailed catalogues to all of our club members, enabling them to evaluate new products before they buy. This is a totally FREE service, to receive your copies complete the coupon below.

**SERVICE CENTRE:** Atari International (UK) Inc has recently appointed Silica Shop as an authorised Atari Service Centre. This means that we can now service your Atari VCS or 400/800 (under guarantee if applicable), whether or not you purchased it from us.

**VCS COMPUTER KEYBOARD:** A keyboard will soon be launched to convert the VCS into a fully programmable home computer. For further details, join our club by completing the coupon below. We will then let you know when further information is available.

**STARPATH SUPERCHARGER:** The supercharger plugs into the cartridge socket of your VCS and expands its RAM almost 50 fold, from 128 to 6,272 bytes. This increased memory adds vivid high resolution graphics capabilities and significantly lengthens the game playing time. Supercharger has a range of multi-load games (at £19.45 each), these offer the facility to play a game in several distinct parts (great for adventures), the next section being loaded when you have completed the previous one, thus enhancing the game play. For further information please complete the coupon below. **£79**

**ATARI VCS CONSOLE - With Combat Cart & Accessories £68.70+VAT = £79.00**

- ACCESSORY:** Atari Splitter, Joysticks, Keyboards, Maine Adaptor, Paddles.
- ACBIM 3rd P:** Erin Lead, Joysticks, Le Brick, Poinmaster, Quick Shot, Redball, Starfighter, Straight Brick, Tractor, Trips Command, Video Command, Whoo, Zaxxon.
- ACCESSORY:** Video Storage Units.
- ACTIVISION:** Barnstorming, Boxing, Bridge, Chopper Cmd, Delphin, Grappler, Enduro, Fishing Drty, Freeway, Grand Prix, Ice Hockey, Kaboom, Keystr Capers, Laser Blast, Megamania, Onk, Pirat, Plaque Attack, River Raid, Robotank, Seaquest, Soling, Sky Jinks, Spider Fighter, Stampede, Starmaster, Tennis.
- APOLLO:** Cat Luggage, Racquetball, Shark Attack, Star Shoot, Space Cavern, Space Chase.
- ATARI:** J-O tic tac toe, Adventure, Air/Sea Battle, Asteroids, Backgammon, Basic Math, Basic Program, Basketball, Basketball (r/s), Berzerk, Bowling, Brain Games, Breakout, Casino, Centipede, Checkers, Chess, Circus, Codebreaker, Combat, Concentration, Defender, Demons/Diame, Dig Dug, Dodge 'em, E.T., Football/Facer, Fun with Nuts, Galaxian, Gopher, Cmd, Gravitar, Hangman, Haunted Hse, Jungle Hunt, Human Cann, Hunt & Score, Indy 500, Jumpin' Beans, Keyhole, Krull, Meth G Prix, Megamania, Golf, Min Golf, Missile Command, Ms Pac Man, Night Driver, Olympics, Othello, Outlaw, Pac-Man, Phoenix, Pinball, Pole Position, Raiders of LJA, Sky Diver, Slot Racers, Soccer, Space Invaders, Space War, Star Raiders, Street Racer, Superman.

- ATARI/Cont'd:** Super Brkout, Surround, Swordsquest E, Swordsquest F, Tennis Int'l, Vanguard, Volleyball (r/s), Werfords, Yarn Revenge.
- ATARI/Cont'd:** Emp Strike Bk, Froggible Mult, James Bond 007, Jack Arena, Lord of Rings, Popeye, O-Bert, Reactor, Rtn of Jedi 1, Rtn of Jedi 2, Sky Slapper, Spideyman, Super Cobra, Tutankham.
- ACTIVISION:** Chial of Nesar, China Syndrome, Cross Force, Galactic Aster, Galactic Tactic, Menes, Master Builder, Planet Patrol, Tape Worm.
- SUPERCHARGER:** Communist Mut, Dragonstomper, Escape from M, Fire Ball, Kiler Satellite, Patrol Patrol, Succes Mission.
- TELEVE:** Commodore, Cosmic Cruise, Demotn Herby, Fast Food, Ram - it.
- INTERVISION:** Jeweller, King Kong, Mercader, Miner 2048r, Palera, River Patrol, Threshold.
- M-NETWORK:** Ads of Iron, Air raiders, Burger Time, Camp Revenge, Frog & Pile, Invtl Soccer, Lock 'n' Chase, Space Attack, Tron Dnly Dec, Winter Olymp.
- ZIMAG:** Cosmic Corridor, DnMaster, Immies & App, Iwenty My Mom, Pizza Chef, Quert for Gold, Tally Ho, Tanks no Tanks.
- PARKER/Con:** Emp Strike Bk, Froggible Mult, James Bond 007, Jack Arena, Lord of Rings, Popeye, O-Bert, Reactor, Rtn of Jedi 1, Rtn of Jedi 2, Sky Slapper, Spideyman, Super Cobra, Tutankham.

## ACCESSORIES

We stock a wide range of accessories for the Atari VCS and 400/800 personal computers. The same accessories can be used on the Commodore VIC range of computers. The Wico range can also be used with the Texas Instruments computers on purchasing a special adaptor. To give you an idea of the range available, just take a look at the following list:



**TRACKBALL:** Trackball by Wico.

**WICO RED-BALL:** An arcade type joystick with a red ball handle, it features 2 fire button locations, one at the base and one on the stick. It comes supplied with 4 grip pads for easier table top use.

**WICO STRAIGHT - STICK:** The main feature of this joystick is its arcade style, bat handle grip. It also has 2 fire buttons. Four grip pads included for table top use.

**WICO TRACKBALL:** A true arcade style trackball for use with your Atari or Commodore VIC. This product is designed to give arcade control in your living room.

**12' EXTENSION LEAD:** A 12' extension for Atari and Atari compatible joysticks for greater player freedom.

**LE STICK:** A mercury filled joystick specially made for one handed operation, with thumb fire button.

**QUICK - SHOT:** This joystick features a contoured handle grip, thumb trigger and optional base fire button. It is supplied with 4 sure foot suction grips.

**STARFIGHTER:** Neat and compact with a small direction stick. Metal interior for added strength.



**VIDEO COMMAND:** With a tapered handle, this joystick is for one handed use. It has a directional control which is similar to a jet fighter joystick.

**Wico Straight Stick with Stick Fire Button**

## VIDEO GAME CLUB

In a fast moving market like video games, it is difficult to keep up to date with all the developments that take place. With new programmes and accessories being introduced at a fast rate by several different manufacturers, it is impossible to get all the information you require from one manufacturer alone. It is for this reason, that we have set up owners clubs for the more popular video games and home computers, to keep you fully up to date with what is going on with your particular machine. As far as we know, Silica Shop are the only company to offer such clubs, but that is not surprising since we are the specialists. We currently have FREE clubs for the Atari VCS, Atari 400/800 home computers, and Mattel Intellivision. Soon we will have clubs for Colecovision, Aquarius and Vectrex. So if you own one of these machines, fill in the coupon opposite, and we will enrol you FREE OF CHARGE in the club relevant to your computer or video game.

**01-309 1111**

**SILICA SHOP**

SILICA SHOP LIMITED, Dept ZHE 0883,  
1-4 The Mews, Hatherley Road, Sidcup, Kent, DA14 4DX  
Telephone: 01-309 1111 or 01-301 1111

## MATTEL INTELLIVISION



**MATTEL INTELLIVISION:** The Mattel games unit is a most versatile T.V. game which offers 3-D graphics quality for only £98. Each cartridge comes with 2 overlays which fit over the unique hand controller giving easy directions for game play. Using the handset's control disc, objects can be moved accurately in 16 directions giving a realistic simulation of lifelike movement.

**VOICE SYNTHESIS:** The Intellivoice unit, price £49, is used with special cartridges where high quality synthesised male and female voices feature as part of the game play.

**NEW MATTEL CARTRIDGE RELEASES:** Why not complete the coupon below and join the Silica Mattel Owners Club and receive our FREE news bulletin and 16 page catalogue detailing new Mattel releases. There will soon be over ninety cartridges available for the Mattel, and a small selection from these is listed below:

- MATTEL:** Arctic Squares, Burger Time, Buzz Bombers, Chess, Cloudy Mountain, Loco Motion, Million X, Mystic Castle, Sharp Shot, Solar Sailor, Space Shuttle, Vectron, Winter Olympics.
- ACTIVISION:** Happy Trails, Pitfall, Stampede.
- C&S:** Blue Print, Carnival, Donkey Kong, Gorf, Mousetrap, Smurf, Solar Fox, Turbo, Venture, Wizard of Wor, Zaxxon.
- IMAGIC:** Bezer, Dracula, Ice Trek, Nova Blast, Satecracker, Swords & Serpents, Tropical Trouble, White Water.
- PARKER:** James Bond 007, Lord of the Rings, Popeye, O-Bert, Spideyman, Star Wars, Super Cobra, Tutankham.

**COMPUTER KEYBOARD:** In July/August 1983, Mattel will be launching their new £89, 49-key computer keyboard attachment called 'Lucky' which is fully programmable and has microsoft basic built in. It will transform your Master Component into a home computer. The adaptor also accepts a 6 note polyphonic music synthesiser and full size 49-key piano keyboard that will make learning music as easy as playing games.

**MATTEL CONSOLE £85.22 + VAT = £98.00** **£98**

## FREE LITERATURE

**FREE LITERATURE** - Please send me your FREE LITERATURE and catalogues on the following items:

**OWNERS CLUB** - I already own the following products, please enrol me in your FREE club:

Mr/Mrs/Miss: ..... Initials: ..... Surname: .....

Address: .....

Postcode: ..... ZHE 0883

## FREE LITERATURE

# Alexander Graham Bell

Ian Sinclair

## Dooby Doo Doo Wop! Time to ring off with the most Famous Name of them all . . .

YES, of course you've heard of *him*, Bell of telephone fame and founder of the Bell Telephone Co., "Ma Bell" to millions of US citizens who take for granted a standard of telephone service that makes us as sick as a Buzby to think about. But did you know that the decibel is named after him, or that he invented the telephone as a deaf aid? Read on, and discover more about the life of this remarkable pioneer.

Alexander Graham Bell was born in Edinburgh in 1847, to a family who had dedicated their lives to the service of the deaf and dumb — his father was the inventor of the hand signals which are still used to this day. His parents were established authorities in elocution and speech correction (what would they have made of CB?), and they did not send Alexander to school, preferring to draw on the considerable talents of the family for his education. The success of this education, unhindered by local authorities or social workers (not yet invented), gained Alexander his first job in 1864, as resident master at Weston House Academy, a small boarding school in Elgin, a cold grey town in the Highlands.

### Devoted To The Deaf

In 1870, however, the whole Bell family decided to emigrate, like so many Scots before and since, in search of a better living in Canada, and they moved to Brentford, Ontario. Alexander found nothing to his taste there, and shifted again to Boston, Mass. in the USA, to open a small school, in 1872, for training teachers of the deaf, a topic in which he took a passionate interest.

He had very considerable success, and in a remarkably short time established a nationwide reputation for his methods of training teachers, particularly in the "hand alphabet" which his father had devised. This, incidentally, is a subject of controversy at the moment because it is no longer being taught, and the change is bitterly resented by many deaf people who feel that a valuable method of communication may be lost to future generations.

As a result of Bell's success, he was asked to incorporate his school into Boston University, and he became Boston's first Professor of Vocal


Physiology in 1873. It was as a result of this achievement that he was able to find time for research, with all the facilities of a University now available to him.

### Telegraphy Progress

He was fascinated by the development of Telegraphy, because it was a method of communication which was open to people with severe hearing or speech defects — in fact many deaf people were trained as telegraph operators in those days, just as the tradition of training blind people as piano tuners grew up. Bell's interest in the electric telegraph led to the invention, along with his excellent but lesser known assistant Thomas Watson, of many improvements in telegraph design, and to Bell's increasing involvement in, and knowledge of, electrical circuits. Gradually he conceived a system which would convert the sound waves of speech into electrical signals, and back again, with the purpose of allowing the deaf to hear what was being said some distance away. Curiously enough, another emigré, David Hughes, was working in Virginia along similar lines.

Bell's telephone system, after a few false starts, took the simple form of a carbon microphone, a battery, and an earpiece. The carbon microphone was until very recently still being used in telephones, particularly in this country; it is now being replaced by the electret microphone, the only device sufficiently sensitive, and with a large enough signal output, to take its place.

The carbon microphone principle (which is attributed to Hughes) goes thus: a thin flexible membrane or diaphragm of metal is held in an insulating cylinder which has a metal backplate, and the space between the diaphragm and the backplate is packed with granules of carbon. Carbon is a resistive material, and the resistance depends very much on how tightly the carbon particles are packed together. With this arrangement, pressing the diaphragm inwards considerably reduces the resistance between the diaphragm and the backplate; pulling the diaphragm outwards considerably increases the resistance. With a battery connected, the device becomes a

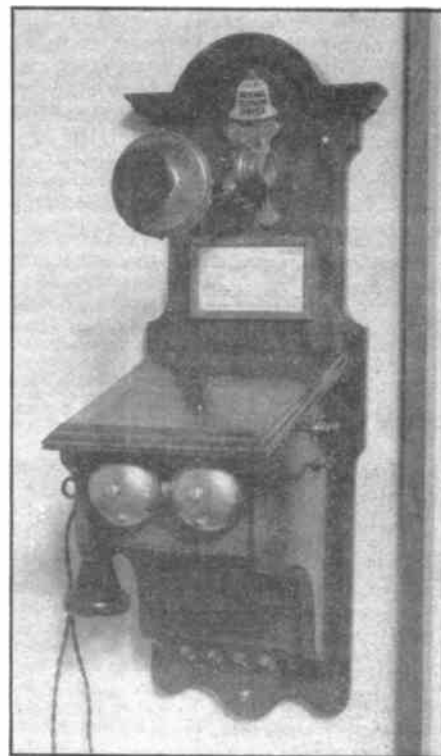

variable current generator, with the amount of current depending on the movement of the diaphragm.

### A Toast To Carbon

When a sound wave hits the diaphragm, it causes the diaphragm to vibrate at the same frequency as the sound wave, and with an amplitude (amount of movement) which depends on the loudness of the sound. In this way, sound waves hitting the diaphragm cause waves of electric current in the circuit connected to the carbon microphone. The useful and remarkable thing about the carbon microphone is the size of the electrical signal that it generates, putting several volts across a load with several milliamps flowing. Until the development of electrets there was nothing that came anywhere near such an output, and the defects of the carbon microphone, such as its narrow bandwidth and the resonances which



it caused, were not of great significance in telephone use.

Bell's receiver was electromagnetic, using the arrangement which, once again, has survived more than a hundred years. This uses a magnetised metal diaphragm held close to an electromagnet, usually of horseshoe shape. The varying currents transmitted by the microphone are sent through the electromagnet of the earpiece, and they cause the diaphragm to be magnetically attracted to an extent that depends on the amount of current. In this way, the current waves that flow in the circuit when someone speaks into the microphone are converted back to a sound by the action of the earpiece.

According to the notes that Bell made at the time, the first words spoken over a telephone circuit were "Come here, Watson, I want you . . .". The fact that Watson heard them and rushed through to Bell's room was the start of something big. They took out a patent on their telephone system in 1876, and the invention was recognised by the confederation of the Volta Medal on Bell in 1880 by the French Government. By this time, the Bell Corporation was being set up to exploit the invention which in a few years was to change the habits of the whole world.

### Enter The Decibel

Bell, at this stage, could have simply retired from active life, content to amass

a fortune as President of one of the most important and rapidly-growing corporations in the US. It is typical of him that he did not, preferring to devote more time to research and to the twin ideals of developing his invention and of helping the deaf. His work on sound transmission soon highlighted a short-coming of measurement, that there was no scale of comparative loudness of sound.

From a large number of careful measurements, Bell found that the apparent loudness of a fixed frequency from a telephone receiver was proportional not to the electrical power but to the *logarithm* of the power, and so he proposed a unit for comparative loudness, the logarithm of the power ratio of two signals. This was widely adopted, and named the Bel in his honour, dropping the final "l" to avoid any confusion between unit and name.

The Bel, however, is a larger unit, and just as we use microfarads instead of farads for measuring capacitance, it's more convenient to use tenths of a Bel, or "decibels", in place of Bels. Unfortunately the decibel is the most abused and least understood of all the units encountered in electronics.

### Photos On The Phone . . .

Bell also worked on developments of the telephone system, as always, with a view to helping the deaf to communicate. One notable develop-

ment, well ahead of its time, was the Photophone of 1880. This was a device to transmit photographic images over a telephone, a forerunner in many ways of the Photofax process and of slow-scan TV.

The principle was simple and ingenious. A transparency is fastened to a glass cylinder so that a light can be shone through transparency and glass on to a photocell (using selenium), which is inside the hollow cylinder. The cylinder is spun round, and the photocell is slowly moved from one end to the other, so that varying currents are generated in a circuit connected to the cell as varying amounts of light reach it through the transparency.

These currents could be transmitted over telephone lines, and at the receiver a photographic method was used to re-create the image. A piece of moist sensitised paper (the original sensitising chemical was potassium iodide) was then wrapped round a metal drum, which was the earth connection of the receiver. The signals from the transmitter were connected to a brush contact, which touched the moist paper as it revolved with the drum. The current flowing through the paper caused the chemical to decompose, leaving a stain (iodine, when potassium iodide is used), and the amount of staining depends on the amount of current. Provided that the receiver drum is synchronised with the transmitter drum, the received image is a reasonably good reproduction of the transmitted one. An incidental advantage is that the picture size can be scaled up or down by making the receiving drum a different size from the transmitting drum.


### . . . Letters Down The Line

The Photophone principle was developed into Photofax, and its descendants are still used. Bell followed it up with the Graphophone of 1887, designed to allow writing to be transmitted along telephone lines — and a large part of his receiver principle for this device can now be seen in the form of XY plotters for computers.

Bell died in 1922, the Grand Old Man of the telephone, and to the end a benefactor of the deaf, to whom he left much of the vast fortune he had accumulated. His other monument was the founding of the American Association to Promote Teaching of Speech to the Deaf, now known as the Alexander Graham Bell Association for the Deaf. This institute sponsors a great deal of research, much of it nowadays into electronics, resulting in a constantly improving service to the deaf. In many ways, I think that Bell would be more interested in this than in the whole telephone service if he could return to see it all.

*Many, many thanks to Ian Sinclair for our longest-running series, and we hope our readers have enjoyed reading Famous Names as much as we have enjoyed running it.*

HE

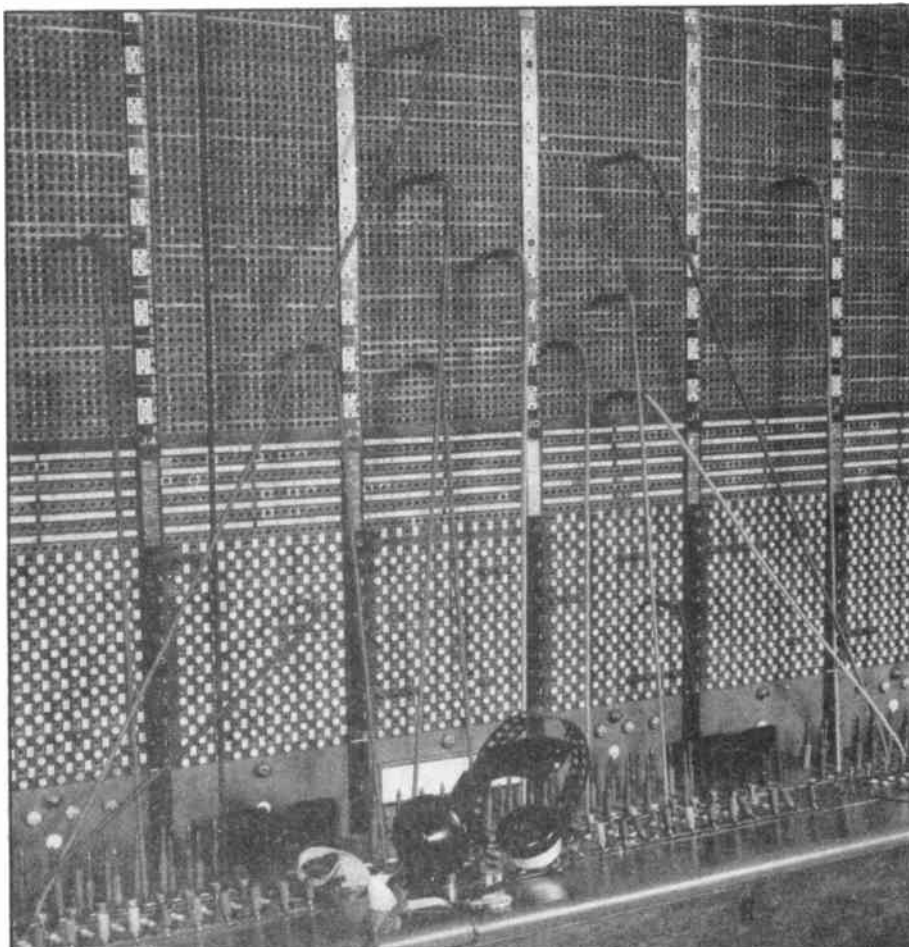



# It's easy to complain about advertisements.

The Advertising Standards Authority. If an advertisement is wrong, we're here to put it right.  
A.S.A. Ltd., Brook House, Tomington Place, London WC1E 7HN

## TALK TO THE WHOLE WORLD

Study now for the **RADIO AMATEUR'S EXAMINATION**

We have had 40 years successful experience in training men and women for the G.P.O. Transmitting licence.



FREE R.A.E. brochure without obligation from:-

**British National Radio & Electronics School**  
READING, BERKS. RG1 1BR

Name .....

Address .....

HE/8/817

BLOCK CAPS PLEASE

## TYPE 161B DUAL POWER SUPPLY KIT


INCORPORATES A POSITIVE & A NEGATIVE REGULATED SUPPLY

**BOTH ARE ISOLATED & ADJUSTABLE 1.3V TO 16V D.C.**

Interconnect to give 2.6V to 32V or -1.3V/0/+1.3V to -16V/0/+16V  
Output current 1A at 16V to 0.35A at 1.3V  
Ripple is less than 1mV

**£25.99**

inc. P & P and VAT

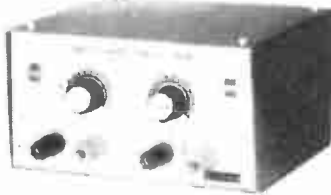

Built & Tested  
**£37.95** inc. P&P and VAT

Comprehensive design details with calculations are included so that the kit is an exercise in power supply design. The kit, which uses quality components, is complete with instructions. Case punched and stove enamelled in attractive blue and grey with a printed front panel to give a professional finish  
Excellent for the beginner, the experienced amateur and as a tutorial for schools and colleges.

SEND CHEQUE OR P.O. ALLOW 21 DAYS FOR DELIVERY

**BRANIME MARKETING LTD DEPT. HE/8**  
BALTHANE IND. EST., BALLASALLA, ISLE OF MAN

# EUROPA ELECTRONICS

Mail Order to 160 High Road, Willesden, London NW10 2PB  
TEL: 01-907 1659


SEND FOR A FREE LIST OF OUR LARGE RANGE OF ITEMS  
ALL DEVICES ARE NEW, FULL SPEC AND GUARANTEED

Post & Packing: Add 30p to all orders under £5.  
VAT: All UK orders add 15% to total cost including p&p.

VALS SERIES	75p	TRANSISTORS	COMPUTER CHIPS	LINEAR ICs	4000 CMOS
74LS00 11p	74LS141 40p	AD181 42p	280A 320p	746 14p	400 100p
74LS01 11p	74LS153 40p	AD182 42p	280C 280p	746 38p	4001 12p
74LS02 12p	74LS154 80p	BC107 10p	280CACT 280p	CA3018 70p	4002 10p
74LS03 12p	74LS155 30p	BC108 10p	280DART 700p	CA3046 70p	4008 90p
74LS05 12p	74LS156 38p	BC109 10p	280AP10 280p	CA3048 270p	4007 14p
74LS06 12p	74LS157 25p	BC109C 12p	280H10 810p	CA3058 285p	4008 38p
74LS07 12p	74LS158 30p	BC109C 12p	280H10 810p	CA3059 285p	4008 38p
74LS08 12p	74LS159 38p	BC117 18p	6801 225p	CA3059 285p	4008 38p
74LS09 12p	74LS160 38p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS10 12p	74LS161 38p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS11 13p	74LS162 38p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS12 12p	74LS163 38p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS13 13p	74LS164 40p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS14 25p	74LS165 80p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS15 12p	74LS166 85p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS16 12p	74LS167 85p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS17 12p	74LS168 85p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS18 12p	74LS169 85p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS19 12p	74LS170 70p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS20 12p	74LS171 70p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS21 12p	74LS172 70p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS22 12p	74LS173 70p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS23 12p	74LS174 40p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS24 12p	74LS175 40p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS25 14p	74LS176 40p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS26 14p	74LS177 40p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS27 13p	74LS178 40p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS28 14p	74LS179 40p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS29 13p	74LS180 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS30 13p	74LS181 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS31 14p	74LS182 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS32 14p	74LS183 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS33 14p	74LS184 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS34 14p	74LS185 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS35 14p	74LS186 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS36 14p	74LS187 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS37 14p	74LS188 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS38 14p	74LS189 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS39 14p	74LS190 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS40 14p	74LS191 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS41 14p	74LS192 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS42 30p	74LS193 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS43 30p	74LS194 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS44 30p	74LS195 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS45 30p	74LS196 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS46 30p	74LS197 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS47 30p	74LS198 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS48 48p	74LS199 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS49 14p	74LS200 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS50 14p	74LS201 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS51 14p	74LS202 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS52 14p	74LS203 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS53 14p	74LS204 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS54 14p	74LS205 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS55 14p	74LS206 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS56 14p	74LS207 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS57 14p	74LS208 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS58 14p	74LS209 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS59 14p	74LS210 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS60 14p	74LS211 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS61 14p	74LS212 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS62 14p	74LS213 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS63 14p	74LS214 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS64 14p	74LS215 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS65 14p	74LS216 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS66 14p	74LS217 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS67 14p	74LS218 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS68 14p	74LS219 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS69 14p	74LS220 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS70 14p	74LS221 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS71 14p	74LS222 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS72 14p	74LS223 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS73 14p	74LS224 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS74 14p	74LS225 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS75 14p	74LS226 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS76 14p	74LS227 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS77 14p	74LS228 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS78 14p	74LS229 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS79 14p	74LS230 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS80 14p	74LS231 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS81 14p	74LS232 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS82 14p	74LS233 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS83 14p	74LS234 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS84 14p	74LS235 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS85 14p	74LS236 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS86 14p	74LS237 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS87 14p	74LS238 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS88 14p	74LS239 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS89 14p	74LS240 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS90 14p	74LS241 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS91 14p	74LS242 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS92 14p	74LS243 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS93 14p	74LS244 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS94 14p	74LS245 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS95 14p	74LS246 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS96 14p	74LS247 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS97 14p	74LS248 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS98 14p	74LS249 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS99 14p	74LS250 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS100 14p	74LS251 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS101 14p	74LS252 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS102 14p	74LS253 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS103 14p	74LS254 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS104 14p	74LS255 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS105 14p	74LS256 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS106 14p	74LS257 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS107 14p	74LS258 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS108 14p	74LS259 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS109 14p	74LS260 120p	BC117 18p	6821 100p	CA3059 285p	4008 38p
74LS110 14p	74LS261 120p	BC117 18p	6821 100p	CA3059	
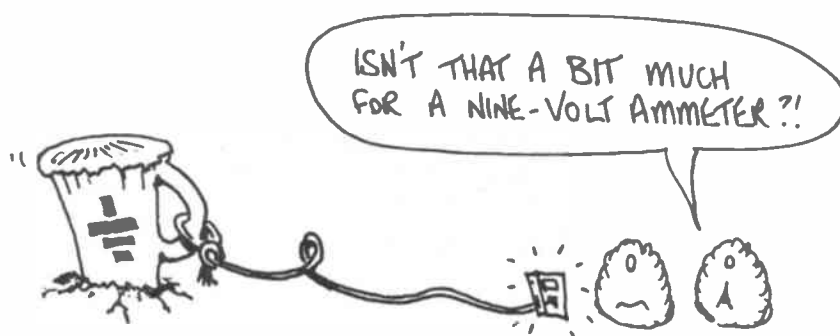
# READERS' SERVICES

Feeling stumped?  
Looking for the  
right connection?  
It must be time to  
reach for HOBBY  
ELECTRONICS!  
Here's how . . .



## Letters

While we are always happy to receive correspondence from readers, it is simply not possible for the editorial staff to reply to every letter. Because of staff limitations and the fact that producing the monthly editions of HE must take precedence, *we cannot even guarantee to answer letters accompanied by an SAE*. Hopefully this situation will prove temporary and we can shortly resume a full service to readers.

In the meantime, to reduce the amount of mail to which we attempt a reply, certain guidelines have had to be imposed:

- Letters from readers who have been unable to successfully build a Hobby project will receive first claim on our attention. But we urge readers to first make sure they understand the problem, and to read all parts of the article thoroughly: it is wasting our time (which is better spent ensuring that current projects are error free) to reply (to pick a common case) that the supplier of certain components is given in Buylines, on page 34.

- Many enquiries are concerned with drafting errors in circuit diagrams or component overlays; corrections for most errors have been published in subsequent issues, so please check your back numbers before writing to us — the information may already be in your hands.

- Where there is a definite problem, we ask that readers first try to solve the problem themselves; again, reading the article carefully will often resolve what appears to be a contradiction between, say a Veroboard layout and the circuit diagram.

- If it is necessary to write, please try to supply useful information: it is impossible to give constructive advice to the reader who says "My project doesn't work. Can you help?". The short answer, and the only one possible, is *no*!

- We would like to hear from any reader who has had difficulty with a Hobby project and who has come up with a solution, but we cannot advise when a project has been modified and fails to work: if you decide to make

changes you will have to live with the consequences. Similarly, we are pleased to take readers suggestions for projects they would like to see in the magazine, or for modifications to improve a published project, but we cannot design circuits on request or re-design a project to suit the requirements of a single reader.

- We will try to answer any readers' questions on electronics in general, to suggest sources for components for old projects or to offer whatever advice we can when circumstances permit; however, we cannot advise on the purchase, use or modification of commercial equipment.

- We are unable to advise on the purchase of components in foreign countries; overseas readers are advised to read carefully the advertisements placed in HE by mail-order component suppliers and to write to them directly (this advice also applies to many UK readers wishing to obtain components for projects!).

- Unless specifically requested to the contrary, any letter to Hobby Electronics may be selected for publication in the magazine, including letters with an SAE if they are sufficiently interesting; in such a case a copy of the editorial comment will be returned to the reader prior to publication.

- Letters not accompanied by a stamped, self-addressed envelope may be selected for publication but will not receive a personal reply. We will attempt to reply to all enquiries backed by an SAE (if writing from outside the UK please include the correct number of International Reply Coupons, available from Post Offices) but we cannot guarantee a reply, nor can the publishers, Argus Specialist Publications, be held legally responsible for the accuracy of the information supplied.

## Writing For HE

- Hobby Electronics' editor is continually looking for good projects, ideas for projects and designers to

develop an idea into working project.

However unless you are already a seasoned contributor, it is unlikely that your first effort will reach the standard required for publication in the magazine. So if you have an idea or a design and you personally think it would be suitable as a Hobby project, write and tell us about it — and please include a telephone number (night or day, we're open all hours here) where you can be contacted.

Similarly if you are a designer, perhaps with time to develop someone else's ideas, please write or phone the editor!

## Any Old Rope?

We will also undertake to publish any suitable but undeveloped ideas as experimental "Reader's Projects". The article will generally fill one page when published and should include a circuit diagram and description, parts list, component overlay (the projects should generally be on Veroboard) and some brief suggestions as to how the device might be constructed by the adventurous reader! A working prototype will not be needed, and the flat rate for Reader's Projects will be £20.

Simple circuits are also needed for publication as "Short Circuits"; no constructional information is needed, and contributors of "Shorts" will be rewarded with £10 per idea.

## The Back-Log

The above guidelines for writing to Hobby Electronics have had to be drawn up in response to the growing pile of yet un-answered letters from readers.

We apologise to all those still awaiting a reply; we are doing everything possible to clear the jam, but to enable us to do so in reasonable time we are retrospectively imposing the above restrictions on the type of enquiry with which we will deal. Therefore, any letter or question not relating to a Hobby Electronics project or a general electronics enquiry will be returned, with the SAE, to the reader.

The Automatic Car Wash has just eaten your Car Radio Aerial for the third time in six months. It's time you got wise to the

Barry Foster

# Auto Winder

LIKE MOST THINGS, car aerials are not intended to last forever. Far from it, you'd be lucky if one stayed in its appointed place for 12 months, because as well as the perils of rust and accidental damage, car aerials seem to provide an irresistible attraction for some . . . people. So, a car aerial that can be wound up and down by an electric motor is worth those few extra pounds — unless you like the battered chic of the coat-hanger look, of course.

The problem with motorised aerials, though, is that you have to remember to wind the thing down when you leave the car. No problem, you'd say — but the one time you forget will be the night you'll lose it, won't you! The solution to all these problems, then, is to install an automatic car aerial motor, one that winds the aerial up when you turn the radio on and winds it down when the radio is switched off. You can buy such an item outright, of course, but why spend more than you have to? The HE Auto-Winder will do the trick, and impress your friends as well!

## Up And Down Circuits

Since the Auto-Winder has to automatically wind the aerial either up or down, it has to respond to two different conditions in different ways. First, when the radio is switched on, it must wind the aerial up; then when the radio is turned off the aerial has to be retracted. All this is accomplished by a circuit which controls two relays to drive the motor in one direction or the other; a gating network turns on the appropriate relay while an adjustable timer sets the period for which the motor is driven.

The Auto-Winder circuit is permanently connected to the car's battery (the current consumption of the control circuitry is a matter of around eight milliamps and is hardly significant, especially when compared to the current drawn from the battery by the starter motor, say) and therefore will instantly respond when the radio is turned on or off.

The control input is taken from the on/off switch of the radio; when power is applied capacitor C1 rapidly charges up through the isolating diode D1, and when the voltage reaches the Schmitt trigger threshold of IC1a, its pin 11 will go low. Now C2 begins to charge through R4 and D4, pulling the trigger input of IC2 (a 555 timer) below 1/3 supply voltage and thus starting the

timing period. C2 charges fairly rapidly, producing a low-going pulse approximately 120 microseconds wide, after which it charges up to the supply voltage; this leaves the trigger input at V+ so that it can respond to another low-going pulse.

IC2 is connected in a standard monostable configuration. Initially the Q output is low and the Discharge input, pin 7, is in a low impedance state,


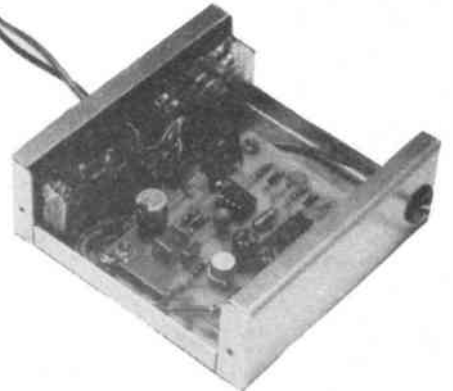


Figure 1. The circuit, using a 555 timer and 4093B Schmitt trigger.

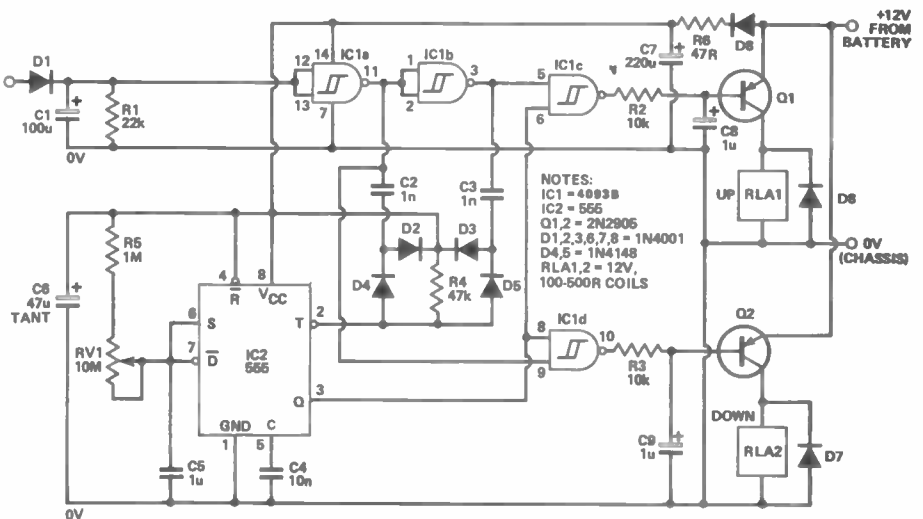

## How It Works

The input to the unit comes from the car radio power supply, which provides a positive voltage on the input gate when the radio is switched on. The gate output is a negative pulse to the trigger generator; this produces trigger pulses to start the timer in two different situations: first, when the radio is switched on and then

when the radio is switched off. The timer sets the period for which the aerial motor is on, so that the aerial may be either completely extended or totally retracted. The timer output is gated to either the Up or Down relay by another output from the trigger generator.


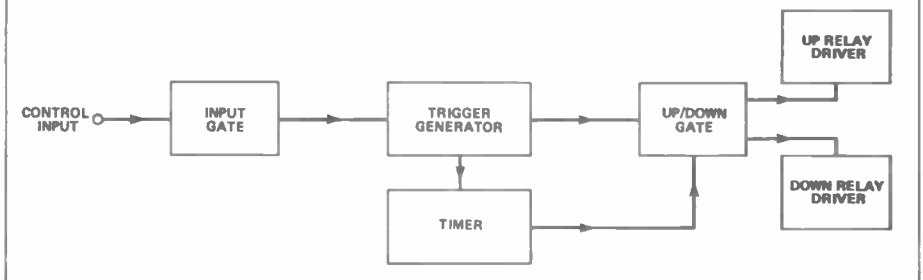
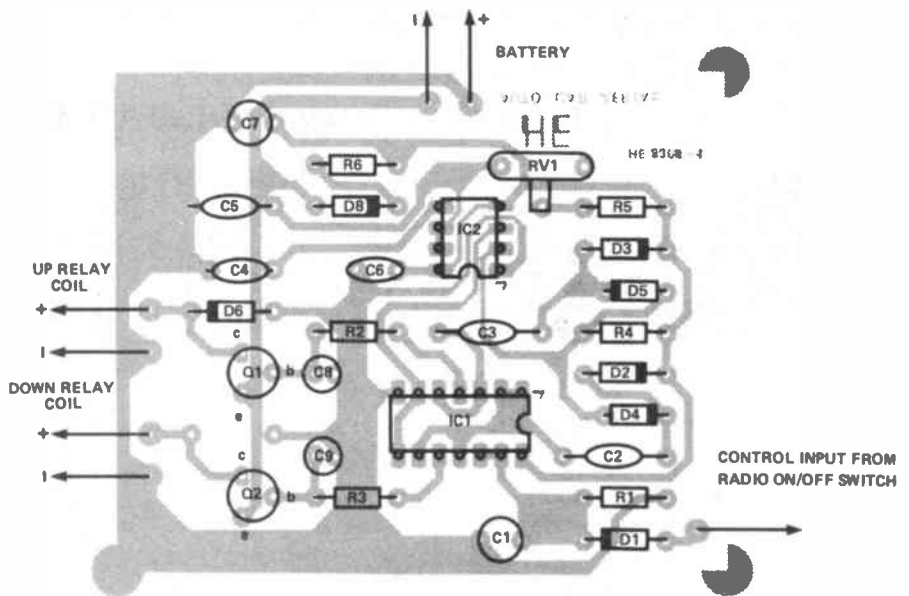


Figure 2. The PCB and components. Note that the relays are designed to be mounted away from the board.

Figure 3. Wiring for the relays. See over the page for suggestions on how to install the relay with the Auto Winder.

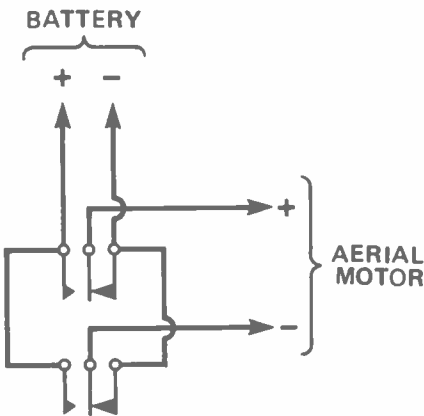

## Parts List

### RESISTORS

(All 1/4 watt 5% carbon)

R1	22k
R2,3	10k
R4	47k
R5	1MR
R6	47R

### POTENTIOMETERS

RV1	10M	vert. preset
-----	-----	--------------

### CAPACITORS

C1	100u 16V	radial electro
C2,3	1n	polyester
C4	10n	metallised polyester
C5	1u	metallised polyester
C6	47u 16V	tantalum bead
C7	220u 16V	radial electro
C8,9	1u 16V	radial electro

### SEMICONDUCTORS

IC1	4093B	quad 2-in Schmitt trigger NAND
IC2	555	timer
Q1,2	2N2905	PNP transistors
D1,2,3,6,7,8	1N4001	
D4,5	1N4148	

### MISCELLANEOUS

RLA1,2 ..... see Buylines  
Case (see buylines); PCB; wire, solder, nuts and bolts etc.

BUYLINES .....page 34

shorting out the timing capacitor C5. When the IC is triggered, Q goes high and pin 7 goes to a high impedance state. C5 then begins to charge via R5 and RV1 until the voltage on it reaches 2/3 of the supply; this is detected by the Sample or 'threshold' input, pin 6, and the output promptly changes to low. At the same time pin 7 switches to low impedance and C5 discharges to ground through the IC, in readiness for the next timing period. The charge rate of C5, and hence the monostable on-time, can be varied by adjusting RV1.

The Q output of IC1 is applied to gates IC1c and d; since the output from IC1a is low when the radio is switched on, the pin 9 output of IC1d is low, and so its output is high. However C9 was charged to near the supply voltage through the emitter-base junction of Q2 when the unit was first connected to the battery, so this high just ensures that the charge on C9 is maintained, keeping Q2 turned off.

However with a low on pin 11 of IC1a, the output of IC1b will be high, thus both inputs to IC1c are high and its output will go low. Now C8 will discharge into pin 4 and as soon as the voltage on the base drops to more than 0V7 below the battery voltage, Q1 will turn on, activating RLA1 and driving the motor to wind the aerial up. The sequence of events when the radio is switched off is similar; the unit will not operate immediately however, because C1 will take some time to discharge through R1, thus maintaining a high on IC1a's inputs for about two seconds. This is to prevent the aerial shuttling up and down if it takes two or three attempts to start the motor! Eventually, though, C1 will discharge below the threshold voltage of the Schmitt trigger and the output of IC1a will go high, IC1b output goes low and IC1c output goes high. However C2 was previously charged through R4, D4, so now the voltage at the junction of C2, D2 and D4 goes rapidly to 2V+ but then discharges via D2 and R4.

Meanwhile C3 is charging up through R4 and D5, pulling the trigger input of IC1 below 1/3 V+ and so commencing another timing period. This time, though, IC1c has a low input and so its output is high, keeping Q1 and the up relay turned off. But IC1d has both inputs high, and therefore a low output, so C9 will now discharge into pin 10 of IC1d; when the voltage on the base drops more than 0V7 below the battery voltage Q2 turns on RLA2, driving the aerial motor to wind the stick down.

## Construction

The Auto-Winder is easily built on a single-sided PCB (see PCB Service page for a ready-made board or build your own using the pattern printed on page 64), following the overlay diagram Figure 2. No special precautions are needed beyond the usual handling restrictions applicable to CMOS integrated circuits and the correct orientation of polarised components such as electrolytic capacitors.

When the PCB has been assembled, temporarily connect the relays to the points indicated on the component overlay. The relays have not been mounted on the PCB to allow a wider selection of relay types and to allow more flexibility when it comes to installing the unit in the car. However, the relay contacts should be rated at at least 5A, preferably 10A, since the aerial motor will draw quite a lot of current when it starts up. Then connect a lead to the control input on the PCB and temporarily connect the power supply lines to a 12V battery or power supply (do not connect the aerial motor, yet) and test the unit by touching the control input lead to the positive terminal of the supply. Hold it there, and the Up relay should click on for a moment, then turn off. Remove the control lead from the positive terminal and after a short delay the Down relay should turn on, then release. You can now adjust RV1 to hold the relays on for





electronize

# AUTO-ELECTRONIC PRODUCTS

## KITS OR READY BUILT

### TOTAL ENERGY DISCHARGE ELECTRONIC IGNITION



IS  
YOUR CAR

### AS GOOD AS IT COULD BE ?

- ★ Is it **EASY TO START** in the cold and the damp? Total Energy Discharge will give the most powerful spark and maintain full output even with a near flat battery.
- ★ Is it **ECONOMICAL** or does it "go off" between services as the ignition performance deteriorates? Total Energy Discharge gives much more output and maintains it from service to service.
- ★ Has it **PEAK PERFORMANCE** or is it flat at high and low revs. where the ignition output is marginal? Total Energy Discharge gives a more powerful spark from idle to the engines maximum (even with 8 cylinders).
- ★ Is the **PERFORMANCE SMOOTH**. The more powerful spark of Total Energy Discharge eliminates the "near misfires" whilst an electronic filter smoothes out the effects of contact bounce etc.
- ★ Do the **PLUGS and POINTS** always need changing to bring the engine back to its best? Total Energy Discharge eliminates contact arcing and erosion by removing the heavy electrical load. The timing stays "spot on" and the contact condition doesn't affect the performance either. Larger plug gaps can be used, even wet or badly fouled plugs can be fired with this system.
- ★ **TOTAL ENERGY DISCHARGE** is a unique system and the most powerful on the market - 3½ times the power of inductive systems - 3½ times the energy and 3 times the duration of ordinary capacitive systems. These are the facts:  
**Performance at only 6 volts (max. supply 16 volts)**  
 SPARK POWER — 140W, SPARK ENERGY — 36mJ  
 SPARK DURATION — 500µs, STORED ENERGY — 135mJ  
 LOADED OUTPUT VOLTAGE  
 50pF load — 38kV, 50pF + 500k — 26kV  
 We challenge any manufacturer to publish better performance figures. Before you buy any other make, ask for the facts, its probably only an inductive system. But if an inductive system is what you really want, we'll still give you a good deal.
- ★ All **ELECTRONIZE** electronic ignitions feature:  
**EASY FITTING, STANDARD/ELECTRONIC CHANGEOVER SWITCH, STATIC TIMING LIGHT and DESIGNED IN RELIABILITY (14 years experience and a 3 year guarantee).**
- ★ **IN KIT FORM** it provides a top performance system at less than half the price of comparable ready built units. The kit includes: pre-drilled fibreglass PCB, pre-wound and varnished ferrite transformer, high quality 2µF discharge capacitor, case, easy to follow instructions, solder and everything needed to build and fit to your car. All you need is a soldering iron and a few basic tools.

Most **NEW CARS** already have electronic ignition. Update **YOUR CAR**

### PROTECT YOUR CAR WITH AN ELECTRONIZE ELECTRONIC ALARM



- ★ **2000 COMBINATIONS** provided by an electronic key - a miniature jack plug containing components which must match each individual alarm system. (Not limited to a few hundred keys or a four bit code).
- ★ **60 SECOND ALARM PERIOD** flashes headlights and sounds horn, then resets ready to operate again if needed.
- ★ **10 SECOND ENTRY DELAY** allows owner to dis-arm the system, by inserting the key plug into a dashboard mounted socket, before the alarm sounds. (No holes in external bodywork, fiddly code systems or hidden switches). Re-closing the door will not cancel the alarm, before or after it sounds, the key plug must be used.
- ★ **INSTANT ALARM OPERATION** triggered by accessories or bonnet/boot opening.
- ★ **30 SECOND DELAY** when system is armed allows owner to lock doors etc.
- ★ **DISABLES IGNITION SYSTEM** when alarm is armed.
- ★ **IN KIT FORM** it provides a high level of protection at a really low cost. The kit includes everything needed, the case, fibreglass PCB, CMOS IC's, random selection resistors to set the combination, in fact everything down to the last nut and washer plus easy to follow instructions.

**FITS ALL 12 VOLT NEGATIVE EARTH VEHICLES.  
SUPPLIED COMPLETE WITH ALL NECESSARY LEADS  
AND CONNECTORS PLUS TWO KEY PLUGS**

**Don't Wait Until Its too Late ~  
Fit one NOW!**

fill in the coupon and send to:

**ELECTRONIZE DESIGN** Dept E · Magnus Rd · Wilnecote · Tamworth · B77 5BY · tel 0827 281000

**TOTAL ENERGY DISCHARGE** (6 or 12 volt negative earth)

- Assembled ready to fit      £26.70 £19.95  
 D.I.Y. parts kit      £15.90 £14.95

**TWIN OUTPUT** for cars and motor cycles with dual ignition

- Twin, Assembled ready to fit      £36.45 £29.95  
 Twin, D.I.Y. parts kit      £24.55 £22.95

**INDUCTIVE DISCHARGE** (12 volt only)

- Assembled ready to fit      £15.95 £12.75

Prices Include VAT.      P+P £1.00 (UK)

**CAR ALARM**

- Assembled ready to fit      £37.95  
 D.I.Y. parts kit      £24.95

I enclose cheque/postal order OR debit my Access/Visa card



Name \_\_\_\_\_

Address \_\_\_\_\_

Code \_\_\_\_\_

# READER'S PROJECT

Simple, untested circuits straight from Hobby readers.

## Enlarger Timer

A. Clegg

THIS CIRCUIT differs from most of those published in recent years inasmuch as neither a transformer nor a relay are employed. The preference here is for a lighter, more compact mains switching device — one that can be built for a fifth of the price asked in photographic shops — with an acceptable degree of accuracy and repeatability of the timing period.



### The Circuit

The unit is powered from the mains, via a 13A plug fused at 3A, with the mains rectified directly by BR1; thyristor SCR1 provides the load switching and both these components can easily accommodate a 100W bulb.

The remainder of the circuit is powered from a 10V rail provided by dropping resistor R1, Zener diode ZD1 and smoothing capacitor C1. The dropping resistor should be rated at least 3W for the value shown; it can be reduced, but to no lower than 10k, in which case it should be a 5W type, and the values of R3 and R6 should be decreased to 1kR.

The timing is provided by IC1, a 555. The timing period commences when SW2, a push-to-make momentary action switch, is operated. Then, pin 3 goes high and feeds the potential divider formed by R4, R5; the voltage from the divider switches on the SCR and thus the load. C4 and R7 are included as a precaution against self-latching of the SCR when a high wattage bulb is used but they may be omitted for a normal 60W bulb.

When pin 3 goes high at the start of the timing period, it also drives LED 2 to indicate 'time on', and commences to charge C2 via RV1, which therefore sets the timing period. When C2 charges up to 2/3 of the supply voltage, the timer pin 3 output will go low, causing the SCR to switch off and extinguish LED 2. C2 now discharges into pin 7 of IC1 and the green LED 1 comes on to indicate the timer is in the standby condition. The indicator LEDs are arranged to switch alternately to maintain a reasonably constant current through R1.

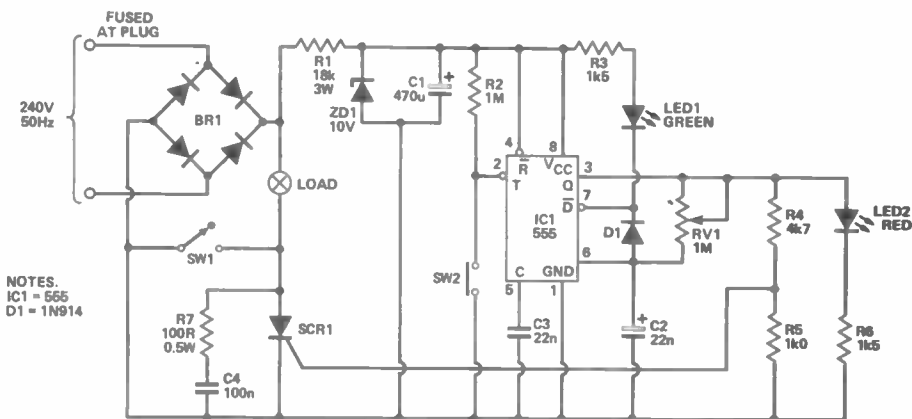


Figure 1. The circuit.

### Parts List

#### RESISTORS

(All 1/4 5% carbon except as noted)  
 R1 ..... 18k 3W  
 (see text)  
 R2 ..... 1M  
 R3, 6 ..... 1k5  
 R4 ..... 4k7  
 R5 ..... 1k  
 R7 ..... 100R 0.5W

#### POTENTIOMETERS

RV1 ..... 1M  
 OW5 linear

#### CAPACITORS

C1 ..... 470u 16V  
 radial electro  
 C2 ..... 22u 16V  
 tantalum  
 C3 ..... 22n  
 radial polyester  
 C4 ..... 100n  
 400V axial polyester


#### SEMICONDUCTORS

IC1 ..... 555  
 SCR1 ..... C106  
 400V/4A SCR  
 BR1 ..... WO-04  
 400V/1A diode  
 ZD1 ..... BZX61C10V  
 10V 1W3 Zener  
 D1 ..... 1N914  
 LED1 ..... 0.2" green  
 LED2 ..... 0.2" red

#### MISCELLANEOUS

SW1 ..... 240V/1A  
 mains rated slide or toggle  
 SWS2 ..... push-to-make  
 momentary action  
 Case (see text); PCB; mains flex or  
 'Figure 8'; control knob, wire solder  
 etc.

BUYLINES ..... page 34

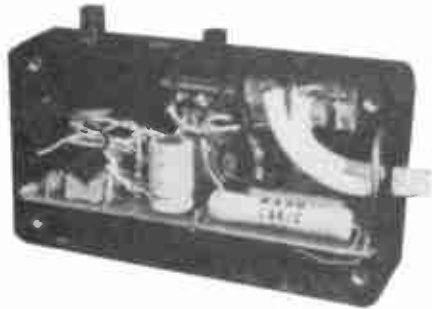

### Construction

The circuit can be built on a PCB and housed in an ABS plastic case measuring 112 x 62 x 31mm. As the circuit is powered directly from the mains, without the isolation afforded by a transformer, *every care should be taken with all connections, soldered or otherwise*; a plastic enclosure should be used and the timing capacitor RV1 should have a plastic shaft and a plastic covered control knob. The input and output leads should be securely clamped inside the box to prevent the connections from being pulled apart. If light 'Figure 8' flex is used, tie a knot in the cables inside the box, beside the outlet holes.

An over-ride switch, SW1, is included for setting up the enlarger

*Hobby Electronics cannot undertake to answer queries on Reader's Projects.*

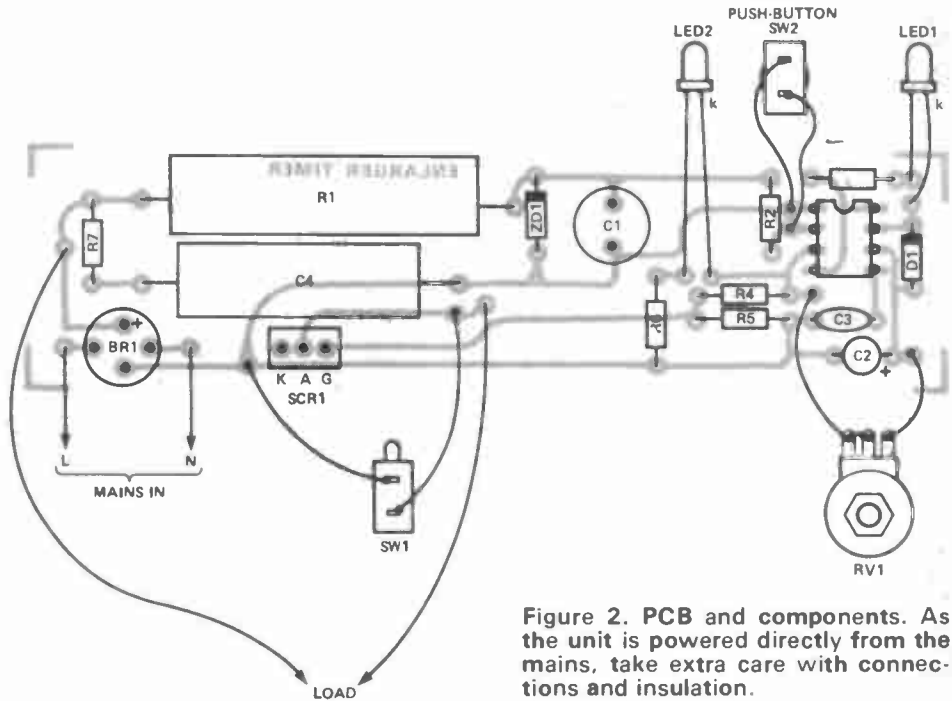


Figure 2. PCB and components. As the unit is powered directly from the mains, take extra care with connections and insulation.

and a graduated scale can be drawn around the timing control knob. First sketch out the timing positions (0 to 30 seconds) on white card, then use rub-down lettering to mark the

positions for 0, 10, 20 and 30 seconds. Finally, cover the card with a piece of thin clear plastic and secure it under the potentiometer with the hex locking nut.

HE

## FREE CAREER BOOKLET

### Train for success, for a better job, better pay

Enjoy all the advantages of an ICS Diploma Course, training you ready for a new, higher paid, more exciting career.

Learn in your own home, in your own time, at your own pace, through ICS home study, used by over 8 million already!

Look at the wide range of opportunities awaiting you. Whatever your interest or skill, there's an ICS Diploma Course there for you to use.

Send for your FREE CAREER BOOKLET today—at no cost or obligation at all.

TICK THE FREE BOOKLET YOU WANT AND POST TODAY

<b>ELECTRONICS ENGINEERING</b> <input type="checkbox"/>	<b>TV &amp; AUDIO SERVICING</b> <input type="checkbox"/>
<b>ELECTRICAL ENGINEERING</b> <input type="checkbox"/>	<b>RUNNING YOUR OWN BUSINESS</b> <input type="checkbox"/>

Name .....

Address .....




ICS  
Dept K626  
160 Stewarts Road  
London SW8 4UJ



01 622 9911  
(all hours)
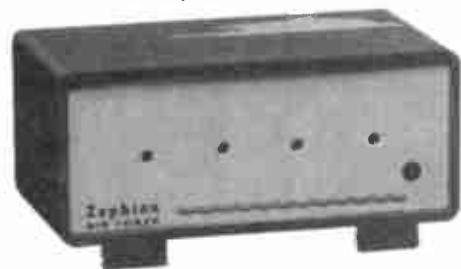
## FEEL HEALTHIER WITH ZEPHION

Bring fresh clean air into your home with the Zephion Air Ioniser.



Airfree smoke, dust and other pollutants of modern day living can bring to many the relief of breathing comfortably once again.

We are confident that you will be delighted with the Zephion Air Ioniser, but if you are not entirely satisfied a full money back guarantee is available if items are returned in good condition within 28 days.

### BUILD IT YOURSELF!

TO:- Dataplus Developments  
81, Cholmeley road  
Reading, Berks.  
RG1 3LY TEL:- 0734 67027

NAME:- .....

ADDRESS:- .....

ZEPHION KITS • £24.15p  
(Kits include all parts)

ZEPHION AIR TONERS  
BUILT AND TESTED. • £34.50p

Money immediately refunded if items returned in good condition.

Prices include VAT & postage; allow 14 days for delivery.

DATAPLUS HE



# BACKNUMBERS



**February 1980**  
Passion Meter, Win Indicator, Short Circuit Special, Kit Review Special, Into Electronics Construction Part 1.

**September 1980**  
MicroMixer, Reaction Tester, Guitar Phaser, Development Timer, Teletext Explained, Into Digital Electronics Part 1.

**April 1981**  
Pre-Amplifier Part 1, Super Siren, Guitar Tremolo, Russian Roulette Game, Doorbell Monitor, Anatomy of a Space Shuttle.

**May 1980**  
MiniClocks, 5080 Preamp, Model Railway Track Cleaner, 5080 Loudspeakers, Loudspeaker Crossover Design, Radio Controlled Model Survey.

**October 1980**  
Kitchen Timer, Tug 'o' War Game, Light Dimmer, Freezer Alarm, Intruder Alarm, Temperature-Controlled Soldering Iron.

**May 1981**  
Electronic Organ, Voice-Operated Switch, Infra-Red Controller, Pre-Amplifier Part 2, Audio Millivoltmeter.

**June 1980**  
Microbe Radio Control System, Egg Timer, Two Watt Amplifier, Fog Horn, Short Circuits, LEDs and LED Displays.

**January 1981**  
Car Rev-Counter, Bench Amplifier, Sound-Into-Light Converter, Chuffer, Electronic Games reviewed.

**June 1981**  
Power Amplifier Part 1, Continuity Checker, Envelope Generator, Early Radio, Gadgets, Games and Kits Supplement.

**July 1980**  
Sound-Operated Flash Trigger, 18+18 Car Stereo Booster, Hazard Flasher, Electronics in Photography, Electronic Espionage, Piezo Electricity.

**February 1981**  
Heartbeat Monitor, High-Impedance Voltmeter, Medium Wave Radio, Two-Tone Train Horn, Audio Signal Generator.

**July 1981**  
Burglar Alarm, Doorbuzzer, Treble Booster, Electronic Aids for the Disabled, Power Amplifier Part 2.

**August 1980**  
EquiTone Car Equaliser, Pass-The-Loop Game, Gaztec Gas Detector, OP-Amp Checker, In-Car Entertainment Survey, Introducing Microprocessors.

**March 1981**  
Public Address Amplifier, Windscreen Wiper Controller, Bicycle Speedometer, Photographic Timer, Microcassettes.

**August 1981**  
Electronic Ignition, Thermometer, Electronic Organ (final part), RPM Meter, Bench Power Supply, Radio Control Survey, Into Electronic Components Part 1.

All of the 1980 issues, except January and April, are still available together with the remaining issues from 1981.

All backnumbers cost £1.50 each. For those of you who only want copies of articles, we do offer a photocopying service. Each copy costs £1.50 and information as to its title and publication date should be given. Ordering backnumbers and photocopies could hardly be easier, just fill in the coupon, cut it out and send it to the appropriate address.

**HOBBY ELECTRONICS  
BACKNUMBER ORDER FORM TO:**



513, London Road,  
Thornton Heath,  
Surrey, CR4 6AR  
England.

Please send me the following items:

NAME .....

ADDRESS .....

.....

.....

.....

Back issues ..... at £1.50 each

I enclose £.....

Cheques and Postal Orders should be made payable to ASP Ltd.

**HOBBY ELECTRONICS  
PHOTOCOPY ORDER FORM TO:**



145 Charing Cross Road,  
London,  
WC2H 0EE

Please send me the following items:

NAME .....

ADDRESS .....

.....

.....

Photocopies of ..... in the

..... issue at £1.50 each


I enclose £.....

Cheques and Postal Orders should be made payable to ASP Ltd.






# PCB FOIL PATTERNS

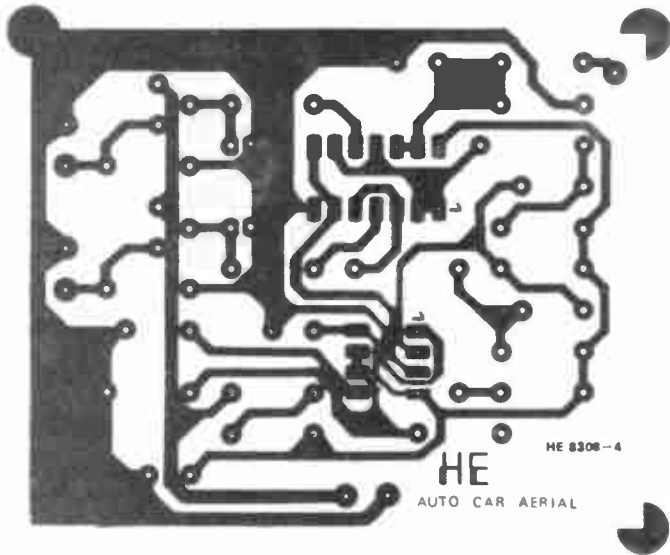


Above. The Auto Winder PCB foil.

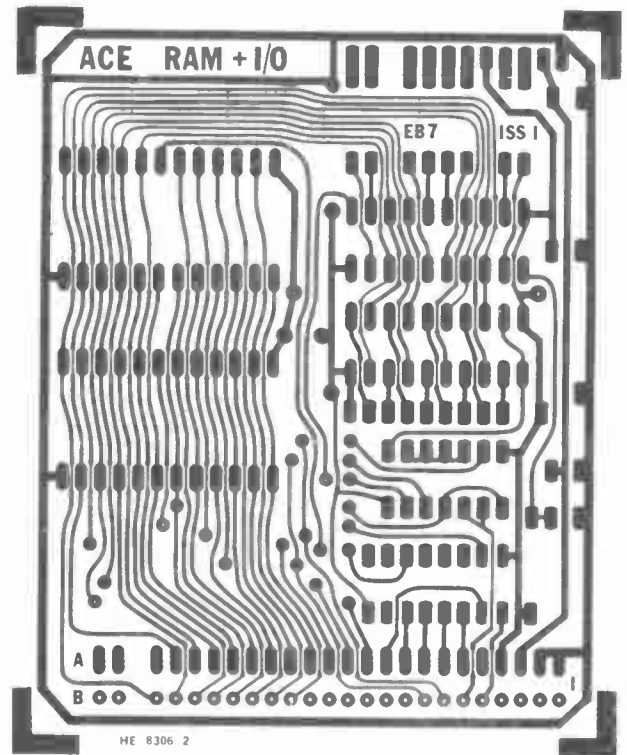


Above.  
The ACE I/O board. Take care, before soldering in components, that the fine tracks have not fused together at any point, and that you have drilled out all the connection pads.

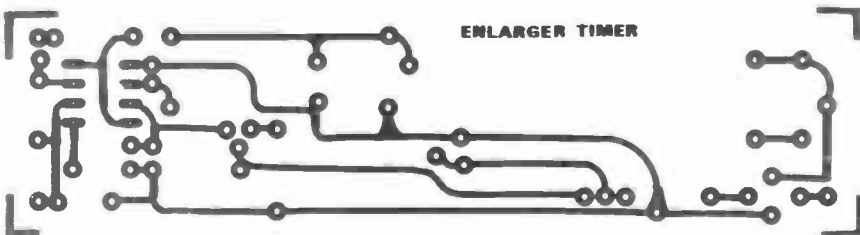Below. The Photographic Enlarger/Timer PCB.



Below. The HE Whistle Switch.

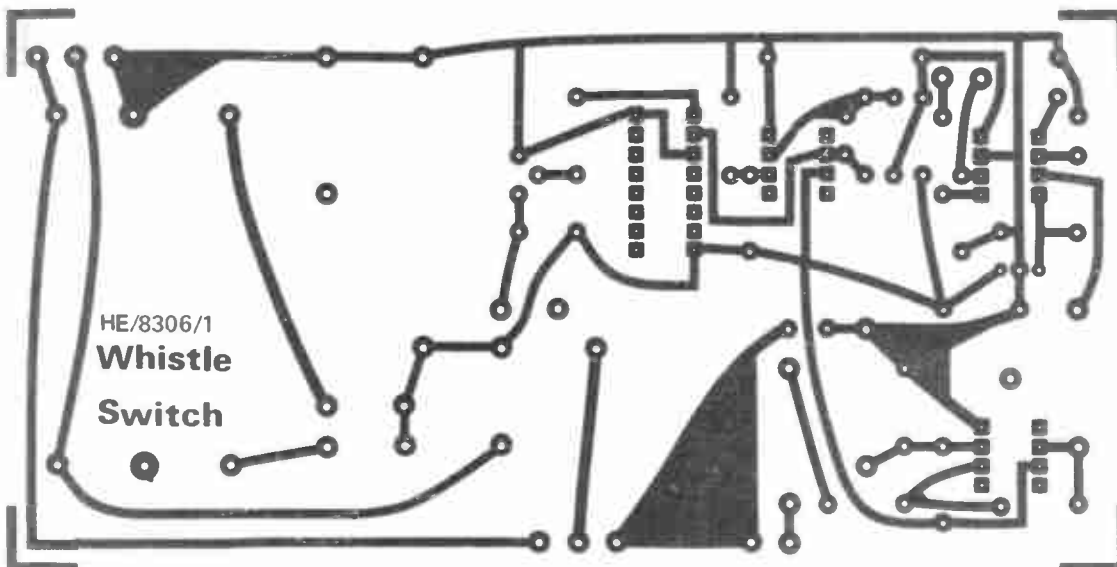

### Lineage:

30p per word (minimum 15 words)  
Semi-display £7.50 per single column centimetre  
Ring for information on series bookings/discounts



01-437 1002  
EXT 282

Send your requirements to:  
Julie Bates,  
ASP Ltd.,  
145 Charing Cross Road,  
London WC2H 0EF

All advertisements in this section must be prepaid.  
Advertisements are accepted subject to the terms and conditions printed on the advertisement rate card (available on request)

## PLANS 'N DESIGN

**AMAZING ELECTRONIC PLANS.** Lasers, Super-powered Cutting Rifle, Pistol, Light Show, Ultrasonic Force Fields, Pocket Defence Weaponry, Giant Tesla, Satellite TV Pyrotechnics, 150 more projects. Catalogue £1 (refundable) — from Plancentre, Bromyard Road Industrial Estate, Ledbury HR8.

## BOOKS & PUBLICATIONS

**PARAPHYSICS JOURNAL** (Russian translations). Psychotronics, Kirlianography, heliphonic music telekinetics. Computer software. SAE 4 x 9"—Paralab, Downton Wilts.

**MACHINE CODE.** If you are at all interested in learning more about this invaluable tool, then join the ZX machine code users club. Send £1.00 for trial issue of club magazine "Micro Arts" to: Toni Baker, 5 Dumergue Avenue, Queenborough, Kent ME11 5BT. Cheques payable to Micro Arts.

## ALARMS

### CENTURION ALARMS

We manufacture, you save £ £ £'s

Send s.a.e. or phone for our Free list of professional D.I.Y. Burglar Alarm Equipment and accessories. Discount up to 20% off list prices, eg. Control Equipment from £15.98, Decoy Bell Boxes from £5.95 inc.

TRADE ENQUIRIES WELCOME

0484-21000  
or 0484 35627 (24 hr. ans.)

CENTURION ALARMS (ETI)

285 Wakefield Road, Huddersfield  
HD6 9BE, W. Yorkshire  
Access & Visa  
Orders Welcomed

**BURGLAR ALARM EQUIPMENT.** Please visit our 2,000 sq. ft. showrooms or write or phone for your free catalogue. C.W.A.S. Ltd. 100 Rooley Avenue, Bradford BD6 1DB. Telephone 0274-308920.

## COMPONENTS

**MAIDSTONE ELECTRONIC** components shop. Thyronics Control System, 8 Sandling Road, Maidstone, Kent. Maidstone 675354.

## WAVEBANDS

Auto Electronics,  
103 Coventry Street,  
Kidderminster  
Tel: (0562) 2179

Brand new components by return post or ring with Access/Barclaycard number for same day despatch.

All manufacturers guaranteed new stock. All at most competitive prices. Catalogue available only 50p. All prices inclusive of VAT.

**IN STOCK** New telephone plugs and sockets also ZX81 plugs and spectrum plugs and wide range of burglar alarm equipment and all accessories for same plus large range of components. Shudehill Supply Co. Ltd., 53 Shudehill, Manchester 4. 061-834 1449.

## KITS

**ELECTRONIC** kits for sale: Morse Practice £4.10, Dice £8.10. SAE for details. Bee Micro, 33 Bevendene Crescent, Brighton, E Sussex.

**PRINTED CIRCUITS.** Make your own simply, cheaply and quickly! Golden Fotolac light-sensitive lacquer — now greatly improved and very much faster. Aerosol cans with full instructions, £2.25. Developer 35p. Ferric chloride 55p. Clear acetate sheet for master 14p. Copper-clad fibreglass board, approx. 1mm thick £1.75 sq. ft. Post/packing 75p. White House Electronics, Castle Drive, Praa Sands, Penzance, Cornwall.

**DIGITAL WATCH** replacement parts, batteries, displays, backlights, etc. Also reports publications charts. S.A.E. for full list: Profords Copners Drive, Holmer Green, Bucks HP15 6SGE.

## SOFTWARE GAMES

**FANTASTIC 16K ZX81.** Adventure £3. Fight monsters and collect as many treasures as possible. Only from Softbus, 6 Aston Mead, Salisbury, Wilts.

## SOFTWARE APPLICATIONS

**SPY CASSETTE.** Amazing cassette will allow you to stop, list or copy any previously un-stoppable tape. Includes two free utilities. State if for ZX81 or Spectrum. Send just £3. Bobber, 29 Chadderton Drive, Unsworth, Bury, Lancs.

## EQUIPMENT

**AERIAL AMPLIFIERS** improve weak television reception. Price £6.70. S.A.E. for leaflets. Electronic Mailorder, Ramsbottom, Lancashire BLO 9AGH.

**U.V. Light exposer** unit for use in prep. of Photo-resist P.C.B's. Attractive wooden construction with exposer area of 250x150mm. Case 350x250x95mm 240V operation. Only £37.00 p&p. Send cheque to V.E.P. Ltd., 5 Hewens Road, Uxbridge, UB10 0FR.

**BURGLAR ALARM EQUIPMENT.** Please visit our 2,000 sq. ft. showrooms or write or phone for your free catalogue. C.W.A.S. Ltd. 100 Rooley Avenue, Bradford BD6 1DB. Telephone 0274-308920.

**ELECTRONIC** AN ALTERNATIVE NOT AN ADD ON  
**klik keyboard**  
FOR ZX81  
£24.95 INC VAT P+P £1.00  
**KEMPSTON** MICRO ELECTRONICS  
Dept 180, Bedford Road, Kempston, Bedford MK42 8BL

## FOR SALE

**QUARTZ L.C.D. CLOCK.** Only 1½" diameter. Sticks anywhere. Only £2.80. p&p 30p. Tait's Mail Order, 31 Lime Grove, Addlestone, Surrey.

**KIA RETURN AN AD No. 9...** Quality 120 Watt Fibreglass. TO3 Poweramp Modules + Heatsinking, ... £7.95 + Advert 9... 8 Cunliffe Road, Ilkley.

## WANTED

**WANTED.** Source of burglar alarm PCB's. Please send details of cost and type to Steve Lawton, Midland Works, Filey Ave, Royston, Barnsley, S. Yorks.

For all your classified needs contact Julie on 01-437-1002 Ext 282

## PROJECTS

### BOXES

To House Your Project  
Plastic 80mm x 82mm x 40mm 95p  
100mm x 75mm x 40mm £1.15  
120mm x 100mm x 45mm £1.30  
Many other sizes in Aluminium and Plastic.

S.A.E. for lists. Price includes VAT. Add 30p p&p.

**ELECTRONICS CENTRE**  
28 Station Road,  
Dovercourt, Essex.

## SERVICES

**T-SHIRTS FOR SUMMER!** "I'm user friendly", "Have you seen my peripherals?" And many more. £3.25. White or blue. S. M. L. One Per Cent Screens 12 Star Lane, Great Wakering, Essex.

## TRANSISTORS

**SPECIAL OFFER** of unmarked transistors (each type of transistor supplied in separate, marked bag). BC338, BC237B, BC239B, BC115, BC173B, BC182B, BC238B. Only 50p for 10 (excluding VAT). Add 25p p&p. Access/Barclaycard accepted. Van Gelder Ltd, P.O. Box 10, Southend-on-Sea, SS2 6Q6.



# CLASSIFIED ADVERTISEMENT — ORDER FORM

Advertise nationally in these columns to over 100,000 readers for only 30p per word (minimum charge 15 words).

Simply print your message in the coupon and send with your cheque or postal order made payable to

Argus Specialist Publications Ltd to:

**CLASSIFIED DEPT., HOBBY ELECTRONICS**

145 Charing Cross Rd., London WC2H 0EE. Telephone: 01-437 1002

Please indicate classification required.


Name .....

Address .....

Tel. No. (Day) .....

## WE TAKE ACCESS AND BARCLAYCARD

Please place my advert in H.E. for  months. Please indicate number of insertions required.

**It's easy  
to complain  
about  
advertisements.**

**The Advertising Standards Authority** ✓  
**If an advertisement is wrong, we're here to put it right.**  
 ASA Ltd, Brook House, Torrington Place, London WC1E 7HN.

## THE ADVERTISERS INDEX AUGUST 1983


A.D. Electronics	18
Ambit International	IFC
Audio Electronics	27
Bicc Vero	30
Bi-pak	30
B K Electronics	IBC
B.N.R.S	46,54
Branime Marketing	54
Circuit Board Components	30
Cricklewood	10
Dataplus Developments	61
Durrant Radio	45
Electronize Design	59
Elen Electronics	45
Europa Electronics	54
Hazzlewood Electronics	25
Hemmings Electronics	58
H.G Electronics	18
Horizon Electronics	39
ICS	61
ILP	32,33
Kelan Engineering	27
Litesold	45
Magenta Electronics	19
Parndon Electronics	39
Racom	18
Rapid Electronics	35
Brian J Reed	39
Sandwell Plant	18
Silica Shop	4,5, OBC
Sparkrite	51
S&R Brewster	25
Technomatic	17
T K Electronics	25
Thandar Electronics	50
Twyford Electronics	24


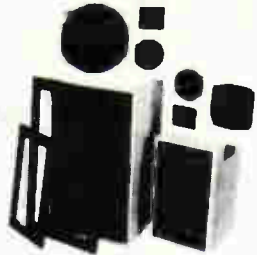
### MULLARD SPEAKER KITS

Purposefully designed 40 watt R.M.S. and 30 watt R.M.S. 8 ohm speaker systems recently developed by MULLARD'S specialist team in Belgium. Kits comprise Mullard woofer (8" or 5") with foam surround and aluminium voice coil. Mullard 3" high power domed tweeter. B.K.E. built and tested crossover based on Mullard circuit, containing low loss components, glass fibre board and recessed loudspeaker terminals. **SUPERB SOUNDS AT LOW COST.** Kits supplied in polystyrene packs complete with instructions. 8" 40W system — recommended cabinet size 240 x 216 x 445mm Price £14.90 each + £2.00 P & P. 5" 30W system — recommended cabinet size 160 x 175 x 295mm Price £13.90 each + £1.50 P & P.


Designer approved flat pack cabinet kits, including grill fabric. Can be finished with iron on veneer or self adhesive vinyl etc. 8" system cabinet kit £8.00 each + £2.50 P & P. 5" system cabinet kit £7.00 each + £2.00 P & P.


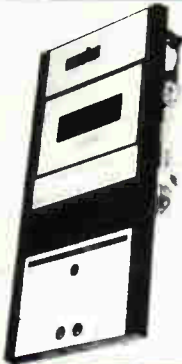
### STEREO CASSETTE TAPE DECK MODULE

Comprising of a top panel and tape mechanism coupled to a record/play back printed board assembly. Supplied as one complete unit for horizontal installation into cabinet or console of own choice. These units are brand new, ready built and tested.

**Features:** Three digit tape counter. Autostop. Six piano type keys, record, rewind, fast forward, play, stop and eject. Automatic record level control. Main inputs plus secondary inputs for stereo microphones. Input Sensitivity: 100mV to 2V. Input Impedance: 68K. Output level: 400mV to both left and right hand channels. Output Impedance: 10K. Signal to noise ratio: 45dB. Wow and flutter: 0.1%. Power Supply requirements: 18V DC at 300mA. Connections: The left and right hand stereo inputs and outputs are via individual screened leads, all terminated with phono plugs (phono sockets provided). Dimensions: Top panel 5 1/2" x 11 1/2". Clearance required under top panel 2 1/2". Supplied complete with circuit diagram and connecting diagram. Attractive black and silver finish. Price £26.70 + £2.50 postage and packing. Supplementary parts for 18V D.C. power supply (transformer, bridge rectifier and smoothing capacitor) £3.50.



### LOUDSPEAKERS

**THREE QUALITY POWER LOUD-SPEAKERS (15", 12" and 8" See Photo)** Ideal for both Hi-Fi and Disco applications. All units have attractive cast aluminium (ground finish) fixing escutcheons. **Specification and Prices.**

15" 100 watt R.M.S. Impedance 8 ohms 50 oz magnet 2" aluminium voice coil. Res. Freq. 20 Hz. Freq. Resp. to 2.5KHz. Sens. 97dB. Price: £34.00 each + £3.00 P&P  
12" 100 watt R.M.S. Impedance 8 ohms 50 oz magnet 2" aluminium voice coil. Res. Freq. 25Hz. Freq. Resp. to 4 KHz. Sens. 95dB. Price: £24.50 each + £3.00 P&P  
8" 50 watt R.M.S. Impedance 8 ohms. 20 oz magnet 1 1/2" aluminium voice coil. Res. Freq. 40Hz. Freq. Resp. to 6 KHz. Sens. 92dB Black Cone. Price: £9.50 each. Also available with black protective grille. Price: £9.99 each P&P £1.50

12" 85 watt R.M.S. MCKENZIE C1285GP (LEAD GUITAR, KEYBOARD, DISCO) 2" aluminium voice coil, aluminium centre dome, 8 ohm imp., Res. Freq. 45Hz., Freq. Resp. to 6.5KHz., Sens. 98dB. Price: £22.00 + £3 carriage.

12" 85 watt R.M.S. MCKENZIE C1285TC (P.A., DISCO) 2" aluminium voice coil. Twin cone, 8 ohm imp., Res. Freq. 45Hz., Freq. Resp. to 14KHz. Price £22 + £3 carriage.

15" 150 watt R.M.S. MCKENZIE C15 (BASS GUITAR, P.A.) 3" aluminium voice coil. Die cast chassis. 8 ohm imp., Res. Freq. 40Hz., Freq. Resp. to 4KHz. Price: £47 + £4 carriage.



### PIEZO ELECTRIC TWEETERS MOTOROLA

Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series) **FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.**

**TYPE 'A' (KSN2036A)** 3" round with protective wire mesh, ideal for bookshelf and medium sized Hi-Fi speakers. Price £4.29 each.


**TYPE 'B' (KSN1005A)** 3 1/2" super horn. For general purpose speakers, disco and P.A. systems etc. Price £4.99 each.

**TYPE 'C' (KSN6016A)** 2" x 5" wide dispersion horn. For quality Hi-Fi systems and quality discos etc. Price £5.99 each.

**TYPE 'D' (KSN1025A)** 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz) Suitable for high quality Hi-Fi systems and quality discos. Price £7.99 each.

**TYPE 'E' (KSN1038A)** 3 1/2" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems etc. Price £4.99 each.

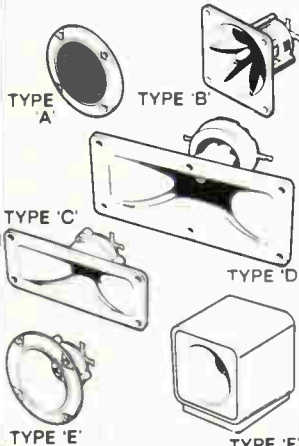**TYPE 'F' (KSN1057A)** Cased version of type 'E'. Free standing satellite tweeter. Perfect add on tweeter for conventional loudspeaker systems. Price £10.75 each. P&P 20p ea. (or SAE for Piezo leaflets).



### OMP 80 LOUDSPEAKER

The very best in quality and value. Ported tuned cabinet in hard-wearing black vinylite with protective corners and carry handle. Built and tested, employing 10in British driver and Piezo tweeter. Spec: 80 watts RMS; 8 ohms; 45Hz-20KHz; Size: 20in x 15in x 12in; Weight: 30 pounds.

Price: £49.00 each  
£90 per pair  
Carriage: £5 each £7 per pair

### BK ELECTRONICS

Prompt Deliveries  
VAT inclusive  
prices  
Audio Equipment  
Test Equipment  
by  
Thandar  
and  
Leader



### HOBBY KITS. Proven designs including glass fibre printed circuit board and high quality components complete with instructions.

**FM MICROTRANSMITTER (BUG)** 90/105MHz with very sensitive microphone. Range 100/300 metres. 5 x 46 x 14mm (9 volt) Price: £7.99p

**DIGITAL THERMOMETER** -9.9°C to +99.9°C. LED display. Complete with sensor. 70 x 70 mm (9 volt) Price: £27.80p

**3 WATT FM TRANSMITTER** 3 WATT 85/115MHz varicap controlled, professional performance. Range up to 3 miles 35 x 84 x 12 mm (12 volt) Price: £12.49p

**SINGLE CHANNEL RADIO CONTROLLED TRANSMITTER/RECEIVER** 27MHz Range up to 500 metres. Double coded modulation. Receiver output operates relay with 2amp/240 volt contacts. Ideal for many applications. Receiver 90 x 70 x 22 mm (9/12 volt) Price: £18.49 Transmitter 80 x 50 x 15 mm (9/12 volt) Price £10.29 P&P All Kits +50p. S.A.E. for complete list.



### BSR P256 TURNTABLE

P256 turntable chassis ● S shaped tone arm ● Belt driven ● Aluminium platter ● Precision calibrated counter balance ● Anti-skate (bias device) ● Damped cueing lever ● 240 volt AC operation (Hz) ● Cut-out template supplied ● Completely manual arm. This deck has a completely manual arm and is designed primarily for disco and studio use where all the advantages of a manual arm are required.

Price £31.35 each, £2 50 P&P



### OMP POWER AMPLIFIER MODULE



**NEW OMP100 Mk.II POWER AMPLIFIER MODULE** Power Amplifier Module complete with integral heat sink toroidal transformer power supply and glass fibre p.c.b. assembly. Incorporates drive circuit to power a compatible LED Vu meter. New Improved specification makes this amplifier ideal for P.A., Instrumental and Hi-Fi applications.

**SPECIFICATION**  
Output Power:— 110 watts R.M.S.  
Loads:— Open and short circuit proof 4/16 ohms.  
Frequency Response:— 15Hz - 30KHz - 3dB.  
T.H.D.:— 0.01%  
S.N.R. (Unweighted):— -118dB ±3.5dB  
Sensitivity for Max Output:— 500mV @ 10K.  
Size:— 360 x 115 x 72mm  
Price:— £31.99 + £2.00 P&P  
Vu Meter Price:— £7.00 + 50p P&P.

New model.  
Improved specification

### HOME PROTECTION SYSTEM

Better to be 'Alarmed' than terrified. Thandar's famous 'Minder' Burglar Alarm System. Superior microwave principle. Supplied as three units, complete with interconnection cable. **FULLY GUARANTEED.**

**Control Unit** — Houses microwave radar unit, range up to 15 metres adjustable by sensitivity control. Three position, key operated fascia switch — off — test — armed. 30 second exit and entry delay.

**Indoor alarm** — Electronic swept freq. siren. 104dB output.

**Outdoor Alarm** — Electronic swept freq. siren. 98dB output. Housed in a tamper-proof heavy duty metal case.

Both the control unit and outdoor alarm contain rechargeable batteries which provide full protection during mains failure. Power requirement 200/260 Volt AC 50/60Hz. Expandable with door sensors, panic buttons etc. Complete with instructions. **SAVE OVER £100 Usual price £228.85 — B.K.E.'s BARGAIN PRICE £128.00 + £5.00 P&P.**

S.A.E. for colour brochure.



**SAFGAN DT-520 DUAL TRACE OSCILLOSCOPE.** New British model. 12 month guarantee. 20 MHz Band Width. Specification: ● CH1, CH2. 5mV/div-20V/div. ● Time Base: 1 Sec/div-100ns/div ● XY Facility. Matched XY inputs. ● Trigger. Level control ± slope selection. ● Auto. normal, TV Triggering ● Z-Modulation ● CAL output 1V 1KHz ● Sweep output 0-9V ● Graticule blue ruled 10 x 8 cm (5" C.R.T.) Very sharp trace. ● Size. H235mm, W177mm, D360mm ● Weight: 6.5 Kgs ● Supply: 200-240 V. 40-60Hz ● Price. £241.50 — FREE Securicor Delivery Probes. X1 £8.05, X1/X10 Switched £10.93.

FREE SECURICOR DELIVERY

## B.K. ELECTRONICS

UNIT 5, COMET WAY, SOUTHEND-ON-SEA, ESSEX, SS2 6TR

★ SAE for current lists ★ Official orders welcome ★ All prices include VAT ★ Mail order only ★ All items packed (where applicable) in special energy absorbing PU foam. Callers welcome by prior appointment, please phone 0702 527572

