

Electronics

THE MAPLIN MAGAZINE

**NAVIGATION SYSTEM
USES ZX81 TO PROVIDE A
COMPLETE SELF-STEERING
SYSTEM FOR YOUR BOAT AT
AN INCREDIBLY LOW PRICE**



**RTTY TERMINAL TU1000 HAS RS232
PORT, FIXED & VARIABLE TONE SHIFTS,
VISUAL TUNING AID, DIRECT CONNECTION
TO RECEIVER OR TRANSCEIVER.**



PLUS


◆ COMPUTADRUM ◆ LIGHT PEN ◆ PROJECT FAULT FINDING ◆ MANY MORE ◆

DID YOU MISS THESE ISSUES?

Project Book 1

Universal Timer. A programmable controller with 18 program times for up to 4 mains appliances.
Combo Amplifier. Superb 120W MOSFET power amp with low-noise BI-FET pre-amp having built-in flanger, inputs for guitars, keyboards or microphones, and five-step equaliser.
Temperature Gauge. Coloured LED indication of 10°C to 100°C.
Pass The Bomb! Low-cost easy-to-build electronic version of pass-the-parcel – keeps kids amused for hours!
Six easy to build projects on Veroboard. Car Battery Monitor – Colour Snap Game – CMOS Logic Probe – Peak Level Indicator – Games Timer – Multi-Colour Pendant.

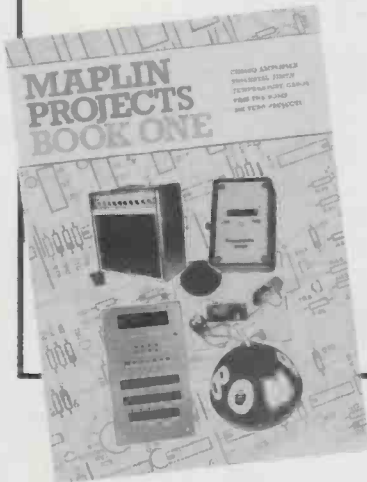
All this for only 70p.
Order As XA01B (Maplin Project Book No. 1)
Price 70p NV.



Project Book 2

Digital Multi-Train Controller. Controls up to 14 loco's with up to 4 simultaneously. Features automatic short-circuit protection and DC supply present all the time for carriage lights etc. Modules will fit in most modern 00-scale engines.
Home Security System. With six independent channels and 2 or 4-wire operation, main and external tamper-proof cabinets, and detection of open or short circuits or just resistance change, the unit offers a high degree of protection with excellent long-term reliability.
Digital MPG Meter. Easy to build with large LED display, makes motoring more economical.


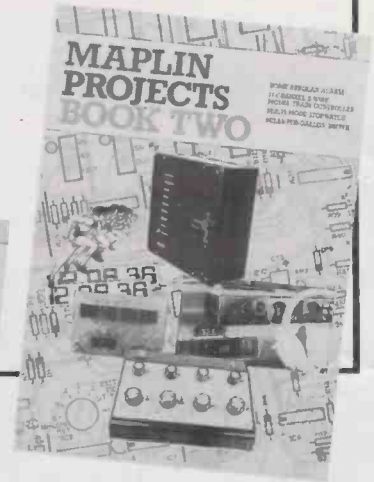
All this for only 70p.
Order As XA02C (Maplin Project Book No. 2)
Price 70p NV.



Project Book 3

ZX81 Keyboard. Full-size full-travel 43-key keyboard with electronics makes graphics, functions and shift lock, single key selections. Keyboard plugs directly into sockets inside ZX81 and there is no soldering in ZX81. Gives fast, reliable entry.
Stereo 25W MOSFET Amp. Kit includes wooden cabinet and printed and punched chassis. This superb 25W rms per channel amp has inputs for magnetic pick-up, tape tuner and aux. Very easy to build, no setting up, superb frequency response, low noise low distortion and the grandeur of MOSFET sound.
Radar Intruder Detector. Home Office type-approved detector gives coverage up to 20m. May be used with our Burglar Alarm.
Remote Control for Train Controller. Infra-red, radio, or wired remote control units for our Multi-Train Controller.

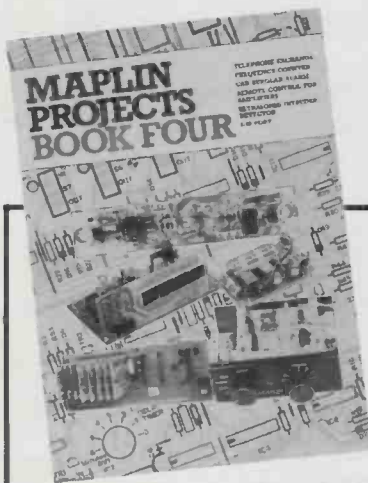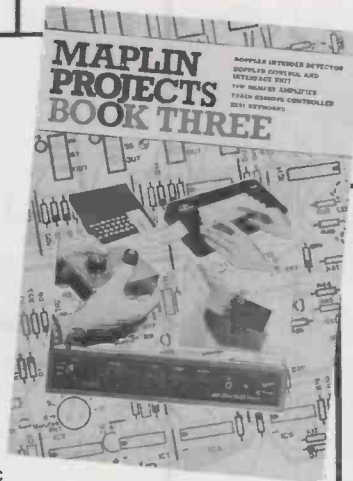All this for only 70p. Order As XA03D (Maplin Project Book 3) Price 70p NV.



Project Book 4

Telephone Exchange. Up to 32 extensions on 2-wire lines for home, office or factory. Save £££'s on rental charges. Details for up to 16 lines in this book.
Remote Control for Amplifier. Adjust volume, balance and tone whilst you sit back and relax with our infra-red remote control. For use with our 25W MOSFET stereo amp or almost any amp.
Frequency Counter. Superb easy-to-build low-cost 8-digit counter with superior specification covers 10Hz to 600MHz range. Incorporates full push-button control, electronic switching, and one input for the whole range.
Ultrasonic Intruder Detector. This easy-to-build ultrasonic transceiver covers up to 400 square feet; though more than one unit can be used for larger areas. The unit automatically adjusts itself to transmit at the frequency where the transducers give their maximum output. Up to three of these units may be connected to our Home Security System.

All this for only 70p. Order As XA04E (Maplin Project Book No. 4) Price 70p NV.

Project Book 5


Modem. A low-cost high quality unit capable of 300 baud transmission speed over normal telephone lines. Send data to your friends anywhere in Europe or talk to our computer.
Inverter. Reliable MOSFET design is ideal for camping, caravanning or standby use during power cuts.
ZX81 Sound Generator. This unit plugs into the Maplin ZX81 extension board and gives full control from BASIC of 3 tone generators, with single address access.
Central Heating Controller. Optimise performance of your heating system with this advanced unit.
External Horn Timer. To comply with latest legal requirements.
Panic Button. Add on to our Home Security System.
Model Train Projects. Additions for our Multi-Train Controller.
Interfacing Microprocessors. Describes the use of parallel input/output ports. Complete with circuits.

All this for only 70p. Order As XA05F (Maplin Project Book No. 5) Price 70p NV.



PROJECTS

RTTY Unit 6

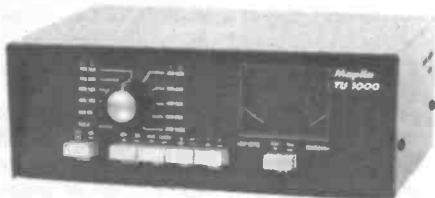


Easily as good as units selling for well over 4 or 5 times the price of this unit, the TU1000 features fixed or variable tone shifts, VCO controlled filters, receive and transmit capability and RS232 port for direct connection to your computer.

Computadrum 20



Turn your home computer into a drum synthesiser! This unit has six tunable drums and resonance control to enable the timbre of the drums to be varied. May be used with many different home computers.

Light Pen 38

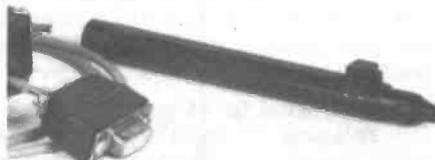

Draw pictures on your TV set or select menu options just by pointing, with our Light Pen all this is possible and much more. And its cheaper and better than most ready-built models as well!

PWM Motor Driver 44

A high performance model motor driver for 6V and 12V motors. The unit gives smooth control from off to full speed and is ideal for use in model boats and cars and in robotics.

Five Easy Pieces 50

Five fascinating circuits including a personal medium wave radio using a new IC, a telephone amplifier, an opto-coupled rpm meter, a tremolo unit and a model train chuffer controlled from the train speed controller on your layout.

FEATURES

The ZX81 & Your Boat 2

A complete navigation system for your boat. The unit compares tides, wind speed and direction, and water speed and distance and can steer the boat for you. In a yacht the unit will tell you when to tack and the best course to sail allowing for the prevailing wind.



Electronic Chronicles 16

Another dip into the past to look at the late 19th century geniuses who were largely responsible for making the 20th century the electronics age.

Machine Code Programming with the 6502 25

More on the wide range of facilities offered by the 6522 and how to get the most out of this incredible chip.

First Base 41

Part seven looks at the CMOS digital integrated circuit family and features circuits for a timer and a piezo-electric timer.

Project Fault Finding 47

The start of a brand new series that will prove invaluable to all home constructors. In part one we look at some of the most common problems encountered when building at home.

All About Telephones 54



To complement our range of phone connectors featured in our last issue, this article describes how to use them and how your telephone works.

Measurements in Electronics 58

This month we look at the specialised test equipment available for use in fault-finding in digital circuits.

Dwell Angle Measurements 62

Shows how to measure dwell angle on your car using your multimeter. The method is far more accurate than using feeler gauges.

Connections Made Easy .. 63

How to connect up the new range of space-saving and time-saving IDC connectors.

NEWS

Catalogue for 1985	64
Classified Advertisements	61
Corrigenda	36
New Books	28
Price Change List	31
Price List of Items Since Catalogue	29
Readership Survey Results	37
Shop Addresses	30
Subscriptions	64
Top Twenty Books	36
Top Twenty Kits	36

Mail Order

P.O. Box 3, Rayleigh, Essex SS6 8LR.
Telephone: Retail Sales: (0702) 552911.
Trade Sales: (0702) 552961.
General: (0702) 554155.

Shops: See page 30.

All shops closed Mondays.

Cover

Cover photograph by Ian James.

Seawolf 26 supplied by:
J. & J. Yachting,
Essex Yacht Marina,
Wallasea Island,
Essex.

Editorial & Production

Editor Doug Simmons
Production Manager Hugh Moir
Technical Editors Robert Kirsch
Dave Goodman
Peter Blackmore
Art Editor Roy Smith
Technical Artists John Dudley

Published by Maplin Electronic Supplies Limited.

Typesetting Essex Process Engraving, Stock Rd, Southend

Printed by Edén Fisher (Southend) Ltd, Stock Rd, Southend

Distributed by Spotlight Distribution, Benwell Rd, London N7

Copyright. All material is subject to world wide copyright protection, and reproduction or imitation in whole or part is expressly forbidden. All reasonable care is taken to ensure accuracy in preparation of the magazine, but Maplin Electronic Supplies Ltd. cannot be held legally responsible for its contents. Where errors occur corrections will be published as soon as possible afterwards. Permission to reproduce printed circuit board layouts commercially or marketing of kits must be sought from the publisher.
© Copyright 1984 Maplin Electronic Supplies Limited.

The ZX81 computer is robust, relatively powerful and has no moving parts. It is compact, uses 9 volts D.C. and is very cheap. A kit cost me £25. A boat is a joy to possess and sometimes a delight to sail. However there are two things which make sailing difficult - bad weather and having to navigate during bad weather. It is much easier in a rough sea to punch a few keys than to use a parallel rule and mental arithmetic. A computer can ask you all the right questions and unerringly give you the correct answers. It is not affected by sea sickness or exhaustion.

The following article describes how your ZX81 will aid your navigation and, in average seas, steer your boat. In bad weather, it at least removes the need for mental arithmetic. When sailing into the wind, it can calculate the best course and

constantly available data from the wind speed and direction finder and that from the water log to enable the computer to adjust the course continually. This would ensure the most economical passage. As you can see there is scope for you to combine your computer and handyman skills to produce either an aid to navigating or a complete self-steering system which will compete with most on the market, but at a fraction of the price.

The Programs

These have been written as a menu of five parts entered as one program. All the parts display a brief description of their function and ask for input when needed. When the program has been entered (loading sign 'IN'), press RUN followed by NEWLINE and the television will display a menu with 5 options. Type in the number of the option required followed by NEWLINE and new information screens will be displayed. To return to the menu, press R.

Option 1. Tides.

This program calculates the average strength and angle of the tides over the estimated duration of the voyage. An estimate is made of the time it will take, and the strengths and angles of the tides are entered into the program for every hour. The output gives the averages for the journey which can be used in program 2. It also gives the Eastings and Northings of the accumulated tides which can be of great help if you decide to do some plotting.

Option 2. Navigation.

If motoring, this program calculates the course and distance through the water allowing for the tides. If sailing, it will also take into account the wind and properties of your boat. It will tell you if it will be necessary to tack, the courses to sail and distances through the water on each leg of the tack.

Option 3. Wind Speed and Direction.

This program displays on the TV the wind speed and direction. It uses a purpose-built anemometer and wind direction finder, and an I/O port. Wind speed is measured electronically by counting the rate that two small magnets pass a sensor. Wind direction is measured by four sets of Infra Red (IR) emitters and sensors. The signals are sent to the computer which decodes them and displays them on the TV screen.

Option 4. Water Speed and Distance.

This program displays the water speed and distance travelled through the water. It uses an I/O port and a trailed log. The rotation of the propeller on the log is measured by magnets and a small magnetic switch. The on/off signals are counted by two binary counters. A four-bit counter cycles from 0 to 15 and is sampled every cycle of the computer. It then calculates the speed of the boat and displays the result on the TV. An eight-bit counter continually counts the on/off

The ZX81 and Your Boat

by D.I. Heaps Part One

tell you when to tack. The program with this article contains five parts combined into a menu. It is written for use on a 16k extended ZX81 and is entered as one program. Each part can be used separately on a simple ZX81 with a little rewriting of the program.

The sections are:-

- (1) Tides: Averages the tides.
- (2) Navigation: Allows for tides and how close the boat will sail into the wind. It will tell you when to tack.
- (3) Wind speed and direction: Uses an Input/Output port (I/O port) and simple hardware to tell the wind speed and direction.
- (4) Water speed and distance: Uses an I/O port and a towed log to tell the speed of the boat and the distance travelled through the water.
- (5) Steering: Uses an I/O port and purpose-built compass and servos to steer the boat.

By using the Navigation program several times it is possible to optimise your navigation. It removes the guesswork in choosing between a slower, shorter journey close hauled, or a faster but longer one off the wind. A further development would be to use the


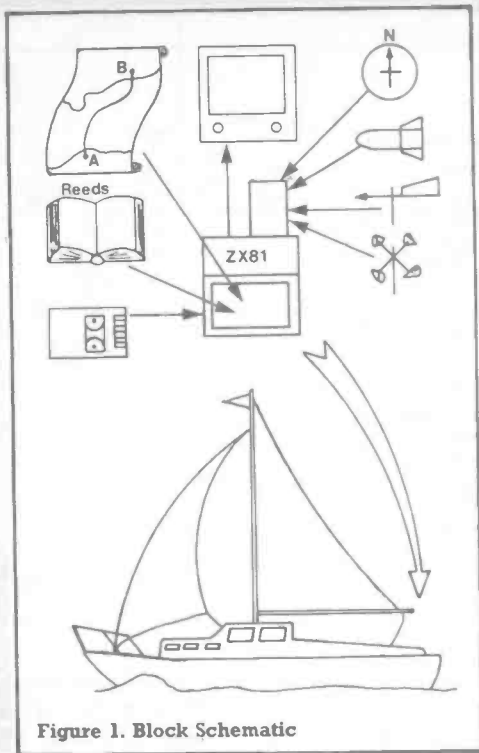


Figure 1. Block Schematic

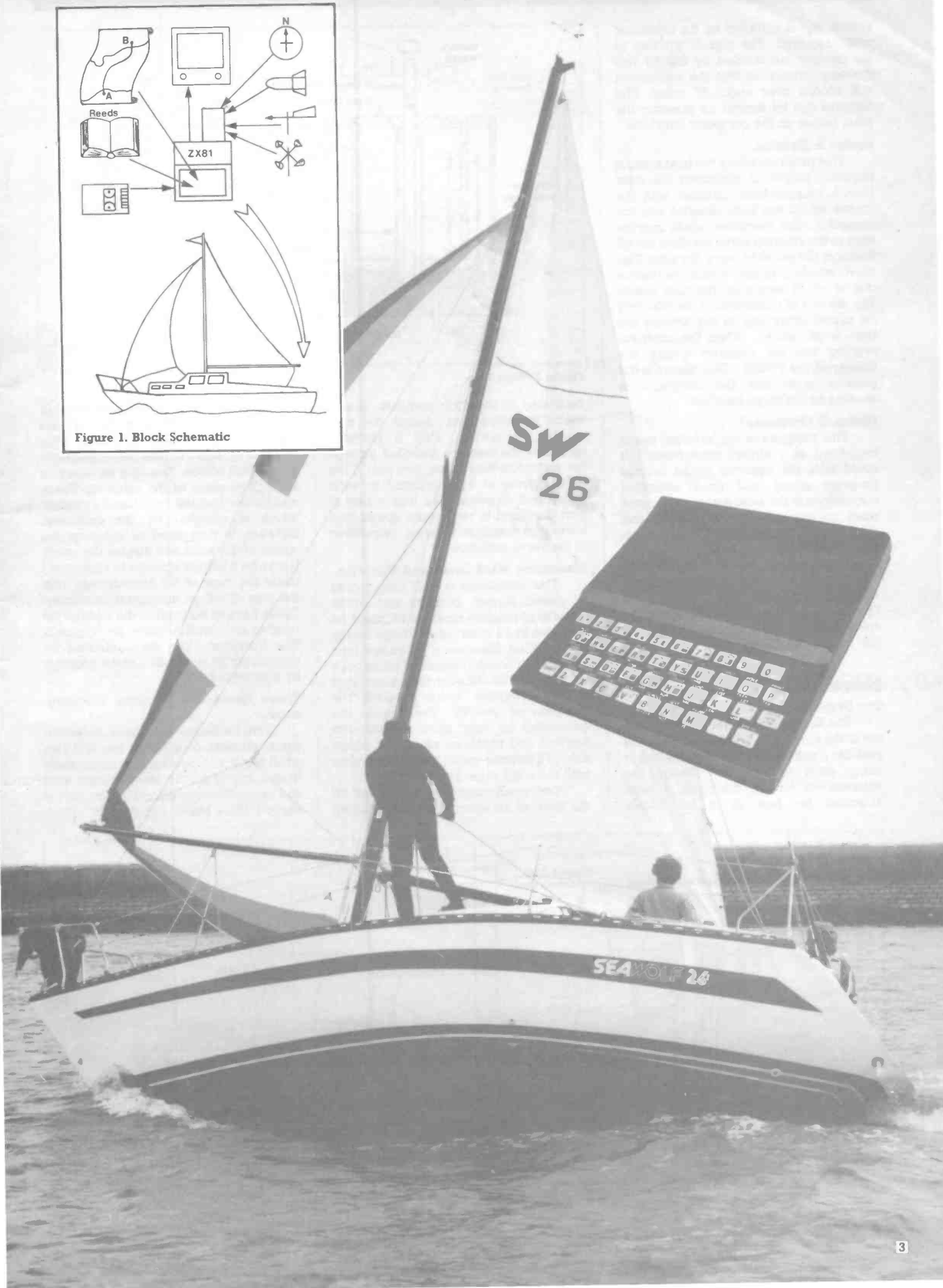

signals and is sampled by the computer when required. The signals arriving at the counter are divided by 256 by two dividing circuits so that the equipment will record over about 30 miles. The displays can be zeroed by pressing the reset button on the computer interface.

Option 5. Steering.

This program steers the boat along a required course. It compares the data from a purpose-built compass with the course which has been entered into the computer. The computer sends instructions to the steering servo interface which instructs the servo to move the tiller. The servo interface knows where the tiller is due to an IR sensor on the tiller servo. The amount of movement of the tiller will be varied according to the amount the boat is off course. When the compass reading and the required course are displayed, the STEER CODE shown is the position code that the computer is sending to the servo interface.

Option 6. Optimiser?

This program is not included but is suggested as a further improvement. It could take the contents of the various program stores and issue amended instructions to the steering servo. It could react to changes in wind speed and direction and adjust the course in much the same way as would a skilled helmsman. It could measure the distance travelled along the first leg of a tack, and when at the tacking point, tack the boat. Of course, most boats would have to be specially fitted with a tacking jib to make this happen properly.

Hardware

The Maplin I/O Port.

The first step is to get data into and out of the computer. The Maplin ZX81 I/O port has 3 ports which can be adjusted in many ways to read or change the environment for the computer. I have arranged for port A to be mainly

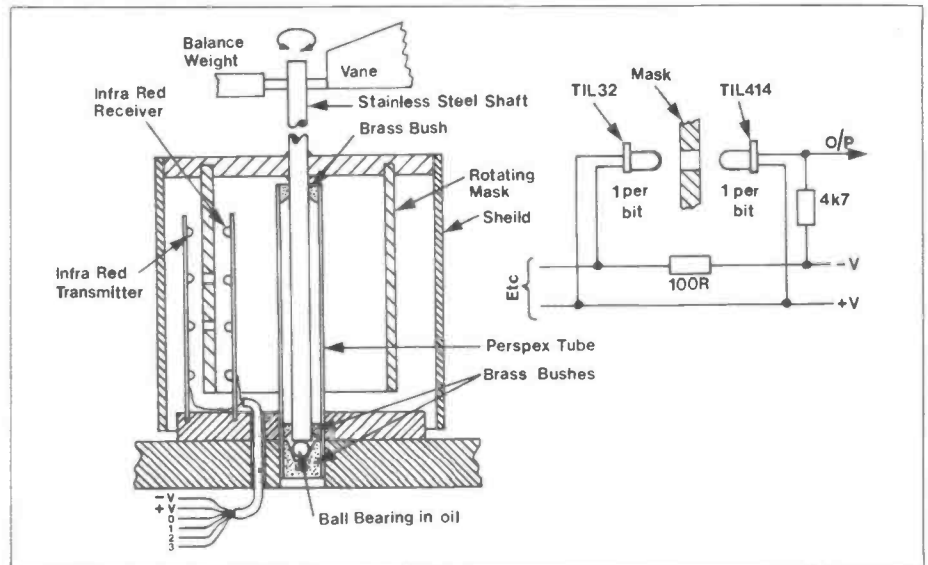


Figure 2. Wind Vane

dedicated to the 6 bit compass. It also sends instructions to change the data arriving at port B. Port B normally measures the distance travelled through the water. On instruction from port A the data arriving at it is changed to wind speed and direction. The higher part of port C is used to read water speed. The lower part issues the steering instructions to the servo interface.

Measuring Wind Speed and Direction.

This instrument is built from pieces of plastic piping, perspex and brass. Lengths of stainless steel are required for the axles and I used ball bearings for the pivots. Wind Direction is measured by a Wind Vane which is mounted on top of a circular four-bit encoder. Signals are sent to the computer which displays the direction on the TV. The signals are generated by four pairs of infra-red emitters and receivers placed on either side of a circular mask. The mask rotates with the wind vane. See Figure 2.

Two small magnets are mounted on the shaft of an anemometer to measure

Wind Speed. As the anemometer rotates with the speed of the wind, the magnets pass close to a small electronic chip which is sensitive to changes in magnetic fields (Hall effect). The chip switches on at each passage of the magnets. These signals are counted by a four-bit counter which is sampled by the computer. Software is then used to calculate the speed of the wind and display the result. It may be a help to builders to know that I made the cups of the anemometer from the tops of roll-on deodorant containers. These have to be fixed to the ends of the rotating arms with Araldite. See Figure 3. The instrument can be calibrated by multiplying 'N' in line 3055 of the program by a suitable factor.

Water Speed and Distance Measurement.

The hardware for these measurements consists of a towed log and two small electronic circuits. The log is made from a rod of plastic about 100mm long and about 25mm in diameter. One end is shaped like a bullet. 25mm is cut off the

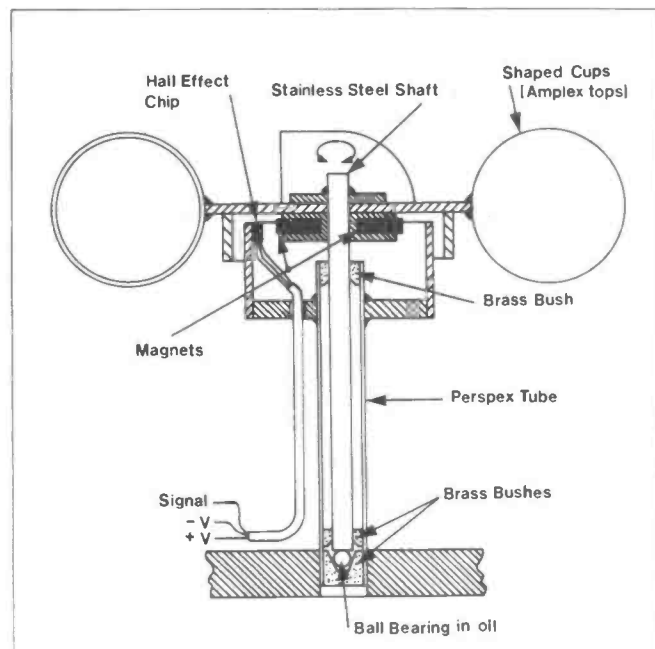


Figure 3. Anemometer

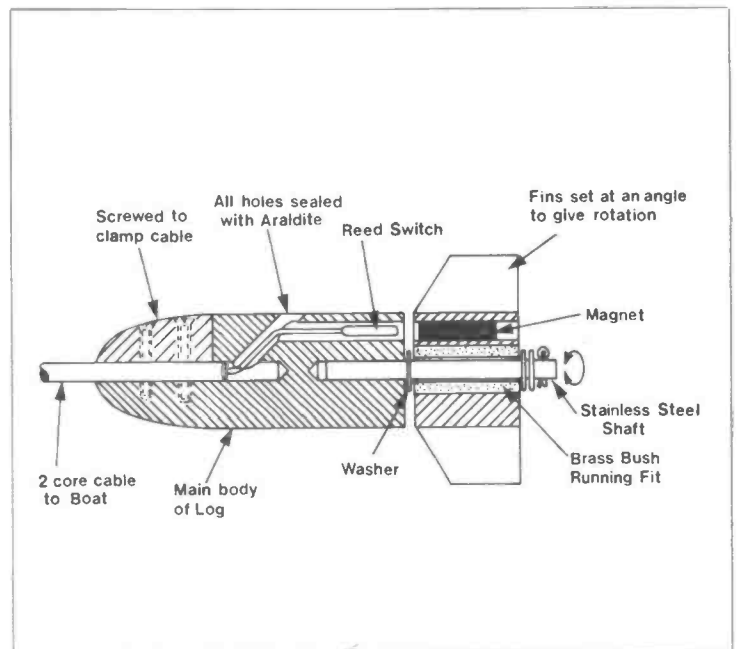


Figure 4. Log

other end to make the rotating part. The static bullet shaped part is drilled out to take the towing/signal wire and the shaft for the rotating part. A magnetic switch is located close to the flat end of the static part (Reed switch) and a magnet inserted in the rotating part. The Reed switch is wired through the body of the log to the towing wire. The bullet end of the log is split in two and then bolted around the towing wire to act as a clamp. All holes are then filled with Araldite. Two vanes are fitted to the rotating part and a small bush is pressed into its centre to aid free rotation. Care must be taken to see that the magnet passes close to the Reed switch when the spinner rotates. See Figure 4. The on/off signals from the log are counted by a four-bit counter as with the wind speed measurer. The computer samples the counter each cycle of the program and displays the speed through the water on the TV. Again the instrument can be calibrated by introducing a multiplier into the software. The on/off signals from the log are also fed through a signal divider and then to an eight-bit counter. The eight-bit counter is then sampled on demand and the distance from the start of the journey displayed. The software can be used to calibrate the instrument.

Steering.

This part of the project compares the required course with that actually happening and adjusts the tiller accordingly. It requires a compass that the computer can read, a servo to move the tiller and a sensor to tell the computer where the tiller is. The required course can be calculated using program 2. Any allowance for lee-way should be made at this point.

The Compass is a purpose built compass which converts the direction being sailed into six-bit binary numbers. The computer then decodes these numbers, compares them with the required course and issues coded instructions to the steering servo. The construction of the coding part of the compass is similar to that of the wind direction finder. It consists of six pairs of infra red emitters and sensors separated by a mask. The mask is rotated by a compass magnet and has holes in it coded to give compass bearings. See Figure 5.

The tiller is moved by a servo made from a modified windscreen wiper motor. The one I used came from a D registered Mini and has served me well for three years so far. The motor drives a slider in a length of steel channel which in turn moves the tiller through a push rod. The motor moves the slider by a system of pulleys and ropes. See Figure 6. To make the motor rotate in either direction, it was necessary to modify it so that the field winding could be connected to the servo control box separately.

The Tiller Sensor consists of a four-bit infra red emitter and sensor which reads a coded mask to find out where the tiller is. The sensor is moved up and down the mask by the movements of the tiller slider. The mask is fixed so

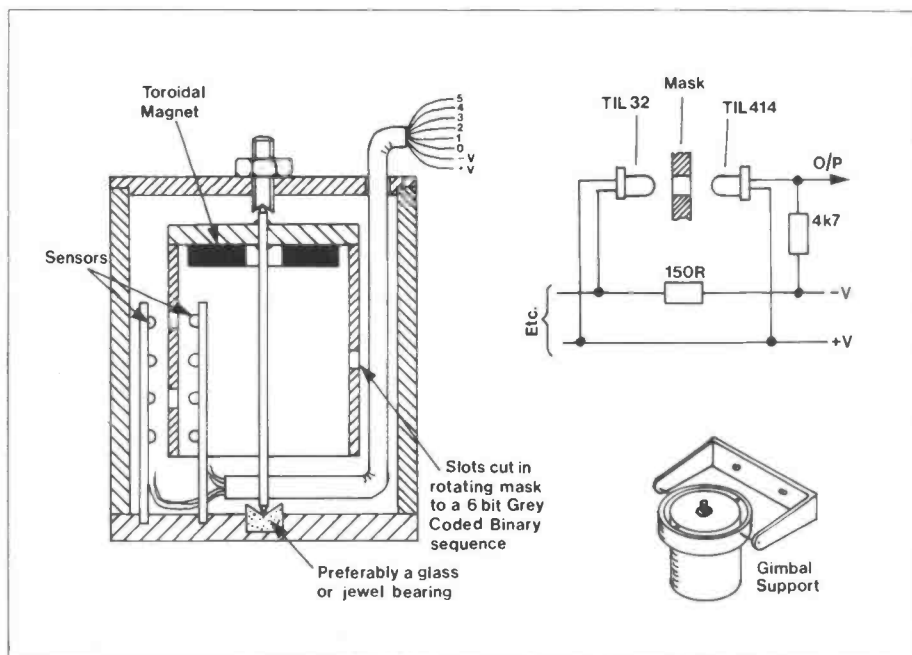


Figure 5. Compass



that it can be adjusted to allow for bias in the set of the sails or boat steering. The readings from the sensor are fed to a four-bit comparator chip which compares the position of the tiller with that instructed by the computer. If there is a difference between the two then the servo is made to move the tiller to the required position. The movement of the tiller will then change the heading of the boat, which will be noted by the compass and the computer. The computer will then give new instructions to the comparator chip which then goes through the process again. See Figure 7.

Installing the System

The ideal would be to have a television and a keyboard in the cockpit. However, as we are building an 'economy' system, we will have to put up with mounting our £50 black and white portable TV in the corner of the cabin. A good arrangement would be to build two

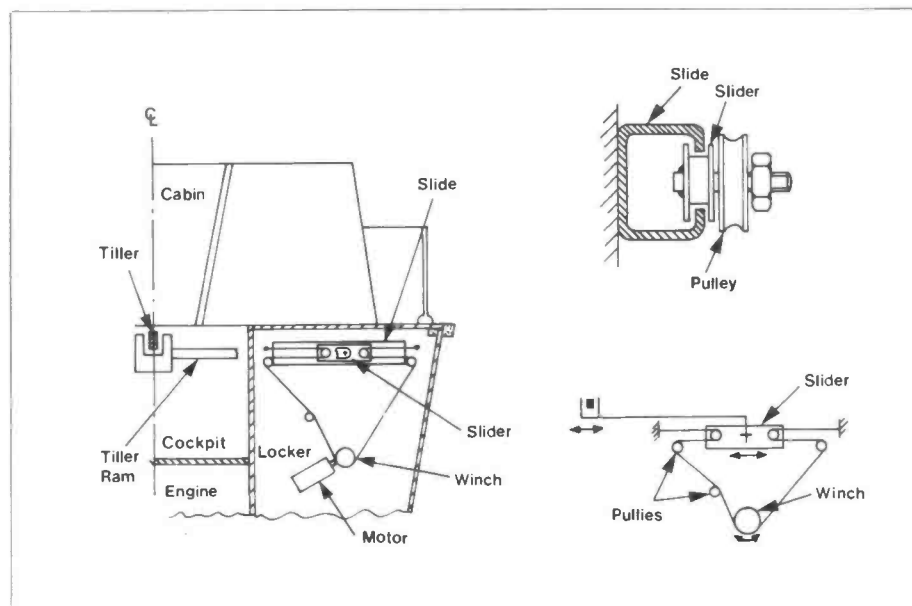


Figure 6. Tiller Servo

Continued on page 19.

RECEIVED RTTY

RECEIVED RTTY

CAIAS FURTHER
DOWN AT THE WEEKEND. SINCE SATURDAY, THE BIGGEST GOR CONDOLENCES ON TRAIN ACCIDENT IN YUGOSLAVIA
ELIXSTONE, HAS BEEN CLOSED, BRINGING THE NUMBER B E R L I N , JULY 15 ADN - ERICH HONECKER, GENERAL SECRETARY OF THE
ORTS TO AT LEAST SIXTY. A SPOKESMAN FOR THE DOCSOCIALIST UNITY PARTY OF GERMANY (SED) AND GERMAN DEMOCRATIC
ANNOUNCED THE CLOSURE ON MONDAY OF THE PORT OF D I R E P U B L I C STATE COUNCIL CHAIRMAN, HAS CABLED CONDOLENCES TO THE
IMPORTANT PASSENGER PORT TO THE EUROPEAN MAINLAND. PRESIDENT OF THE PRESIDENCY OF YUGOSLAVIA, VESELIN DJURANOVIC, ON
PRIME MINISTER MARGRET THATCHER HAS THREATE DEEP-FELT SYMPATHY OF THE PARTY AND STATE LEADERSHIP AND OF THE GOR. DELEGATION ARRIVES IN ETHIOPIA
MEASURES.

E 27
FIGHTING IN NORTH LEBANON TAILS OFF
B E I R U T , JULY 15 ADN - THE BATTLES BE
NORTHERN LEBANON HAVE LARGELY SUBSIS
BEIRUT RADIO REPORTS.
THE BATTLES IN THE ARE
COMMUNITIES, BROKE OUT AT
27 (27) LIVES, NEWSPAPERS

E 1
SEVERE EARTHQUAKE IN MEXICO
M E X I C O C I T Y ,
REGIONS IN CENTRAL MEXICO
OPEN-ENDED RICHTER SCALE,
TACUBAYA, THE EPICENTRE WA
OF HERE IN OAXACA STATE. T
CASUALTIES OR DAMAGE.

E 2
PLANE CRASH IN CALIFORNIA
W A S H I N G T O N , JULY
TWIN-ENGINE SPORT PLANE
IN THE CALIFORNIAN TOWN O


E 3
NICARAGUAN WOMEN FIRMLY LINKED
M A N A G U A , JULY 15 ADN - THOUSANDS OF
SATURDAY REAFFIRMED THEIR FIRM CONFIDENCE IN THE 25
REVOLUTION AND PROTESTED AGAINST THE AGGRESSIVE TEMPESTS IN CHILE TAKE 54 LIVES
STATES, DURING A MARCH THROUGH THE CITY AND AN S A N T J A G O D E C H I L E , JULY 14 ADN - VIOLENT TEMPESTS IN TRAIN DISASTER RISES
MEMBERS OF THE NICARAGUAN WOMEN'S ORGANIZATION 46 (46) PERSONS ARE MISSING. OVER ONE HUNDRED THOUSAND PEOPLE HAVE
COUNTRY'S LEADERSHIP THAT, JUST AS THEIR HUSBAN TISSUFFERED LOSSES BY THE TORRENTIAL RAINS, STDRMS AND LANDSLIDES.
AT THE FRONT, THEY WOULD DO ALL THEY CAN FOR TISUFFERED LOSSES BY THE TORRENTIAL RAINS, STDRMS AND LANDSLIDES.
REVOLUTIONARY ACHIEVEMENTS.

L 20
CARNIVAL SEASON BEGINS IN HAVANA
H A V A N A , JULY 15 ADN - THE CARNIVAL SEASON HAS OPENED IN TH
CURAN CARNE , JULY 15 ADN - A FIRST HIGHLIGHT WAS ON SL
CHILDREN. THE TRADITIONAL CARNIVAL PROCESSIONS ST

ARRIVED HERE ON SATURDAY ON AN OFFICIAL VISIT TO ETHIOPIA. IT IS
BY THE MARSHAL OF THE SOVIET UNION, VASIL PETROV, DEPUTY OFFENCE
THE GROUND FORCES.

IA PLANS TO EXPAND ITS RAILWAY
METRES BY THE END OF NEXT YEAR.
ND THE RAILWAYS TO LATAKIA AND
860) KILOMETRES AT

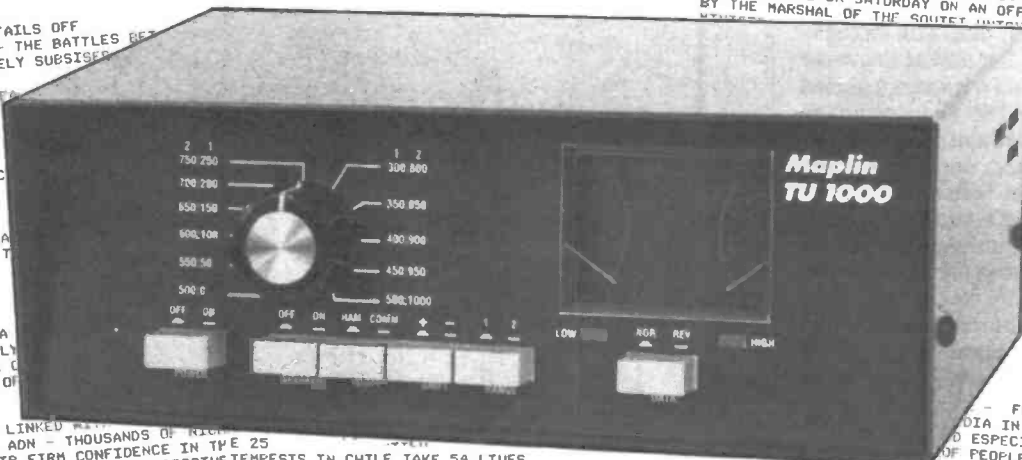NEW ZEALAND
U.S. SECRETARY OF STATE GEORGE
DAY TO ATTEND A TWO-DAY
AUSTRALIA, NEW ZEALAND AND TH
NG, MALAYSIA, SINGAPORE,



The prototype RTTY unit

The Maplin TU1000

Introduction


Home computers are mostly used for games and educational applications, but if you are looking for more than this, computer communications may be the answer. Many of you have probably heard of computers 'talking to each other', using a telephone modem. The major drawback to this system is the expense of running it. Telephone charges can run into pounds, for just a few minutes usage, though obviously this will depend on the distance and the time of the day. Transatlantic hook-ups are, therefore, prohibitively expensive and unless you are very wealthy, out of the question.

An alternative is not to use the telephone network, but use radio communications instead. The advantages are that there are no charges for hooking-up and no distance limitations. There is one slight problem: to use the system for sending data, you must have a licence to use a radio transmitter. However, no licence is required to receive data! This in itself is an interesting and absorbing pastime.

With a modest communications receiver it is possible to receive data transmitted by radio amateurs from all over the world. The short wave bands also abound with commercial stations sending news, weather reports and many other services, 24 hours a day. This system of typed data by radio, referred to as 'radio teletype' or abbreviated to RTTY, has been in use for many years.

by Chris Barlow

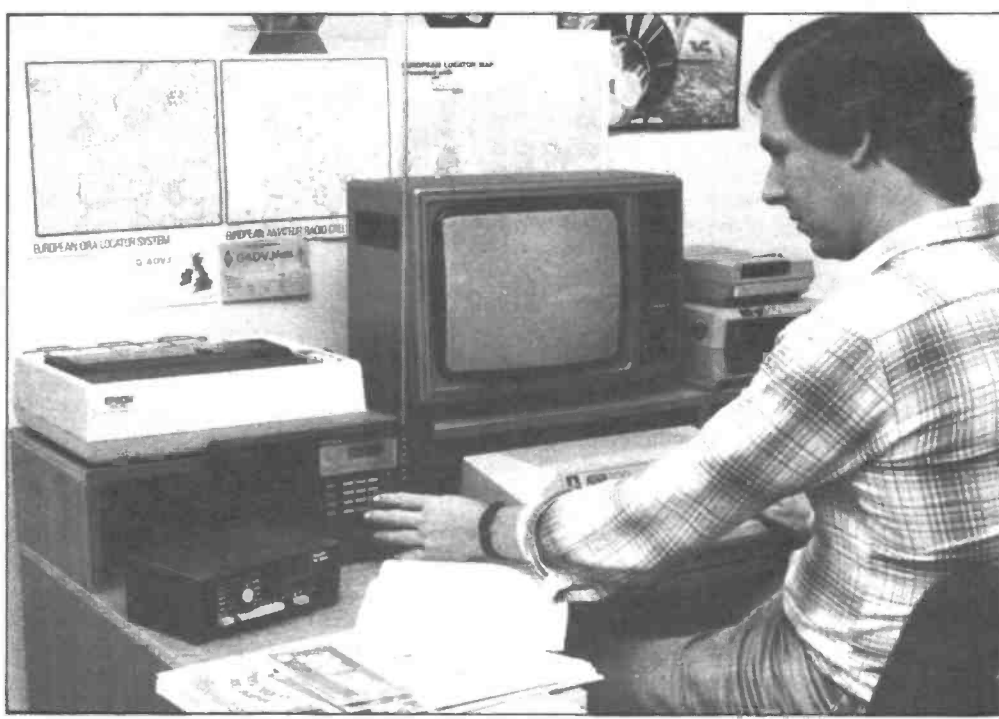- ★ RS232 Compatible
- ★ Fixed or Variable Tone Shifts
- ★ Receive and Transmit
- ★ Visual Tuning Aid
- ★ VCO Controlled Filters



The system uses two audio tones which represent the two logic conditions, high or low, to control a mechanical teleprinter, or an ever increasing number of computer-based VDU systems.

The TU1000 has been developed for the purpose of demodulating the received audio tones into RS232 logic signals that a home computer, with the necessary software, can display. The TU1000 also offers audio output tones controlled by your computer for transmitting RTTY data.

The History of RTTY

As previously mentioned, RTTY dates back to the beginning of the 20th century and the code used goes back even further. In 1874 a Frenchman, Emile Baudot, formulated a five-unit code to control an electro-mechanical system. In 1903, Donald Murray modified Baudot's code to run his time division multiplex system which was used by the British Post Office. This code, although modified slightly over the years, is still referred to as the Baudot Code under the auspices of the International Telecommunication Union.

The earliest recorded use of radio teletype was in 1904 during the Russo-Japanese war, for military and civilian purposes. The first use of encrypted radio teletype signals was in the two world wars for communicating secret messages between military positions. Encryption, or 'scrambling' of the message, is still in use today for confidential and restricted information by various factions world-wide, although the majority of stations send messages in plain language.

The Baudot Code


The code has five data bits, or elements, so there are only thirty-two possible characters to be interpreted. The alphabet takes twenty-six of the code values, which leaves six for control functions, null or no data, return, line-feed, space, letters and figures. The last two speak for themselves. 'Letters' puts the printer, or VDU into upper case A to Z and 'Figures' gives numbers 0 to 9, fifteen punctuation marks, and the 'bell' command.

If the 'bell' code were sent, on the receiving teleprinter a bell would sound to alert the operator to an incoming message. As you can see, the system does *not* support lower case as well as numbers and punctuation marks, unlike the majority of home computer displays.

A complete list of the Baudot Code, showing letters and figures, plus their decimal and hexadecimal values, is shown in Figure 1. Apart from the five data bits, the system uses 1 start bit and 1½ stop bits, although, in practice, you can set your RS232 port to 1 or 2 bits, if 1½ is not available.

The Two-Tone System

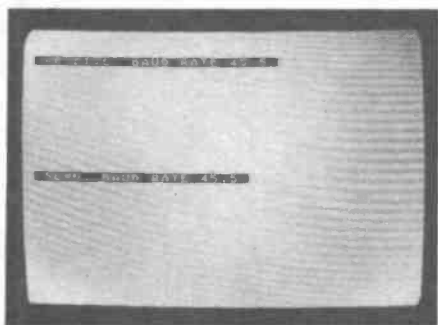As stated in the introduction, RTTY uses two audio tones to represent the logic conditions high or low, commonly September 1984 Maplin Magazine



referred to as mark and space tones. The mark produces the negative RS232 output and the standing tone when no data is being sent. The space tone gives the positive RS232 output and is generated when the RS232 input is taken positive.

The frequency difference of the tones can vary considerably but, in practice, three are used; 170Hz, 425Hz and 850Hz. The TU1000 has these three shifts, plus the ability to be tuned continuously up to a difference of 1000Hz between tones.

The space tone recognised by the TU1000 is 1275Hz. The mark is higher in frequency at 1445Hz for a 170Hz shift, 1700Hz for 425Hz, and 2125Hz for 850Hz shift.

The rate of change between the tones, or baud rate, has to be configured on your computer's RS232 port to resolve the incoming data correctly. Radio amateurs use baud rates of 45.45 or 50. Commercial stations tend to use 50, or 75 bauds, upwards.

		HEXA-	
LETTERS	FIGURES	DECIMAL	DECIMAL
A	-	3	03
B	?	25	19
C	:	14	0E
D	\$	9	09
E	3	1	01
F	! or %	13	0D
G	& or +	26	1A
H	£ or #	20	14
I	8	6	06
J	' or bell	11	0B
K	(15	0F
L)	18	12
M	.	28	1C
N	,	12	0C
O	9	24	18
P	0	22	16
Q	1	23	17
R	4	10	0A
S	bell or '	5	05
T	5	16	10
U	7	7	07
V	:	30	1E
W	2	19	13
X	/	29	1D
Y	6	21	15
Z	"	17	11
return	return	8	08
line feed	line feed	2	02
space	space	4	04
letters	letters	31	1F
figures	figures	27	1B
not used	not used	0	00

Figure 1. The Baudot Code

Circuit Description


The audio tones from the speaker or earphone socket are fed into the TU1000 via a two pin speaker DIN socket. The signal passes through choke CH1 and capacitor C1, to S1, the speaker on/off switch. The switch, when in the off position, connects the output of the receiver to an 8 ohm resistor to simulate a loudspeaker load. This facility is provided to mute the sound while maintaining the signal to the TU1000. When S1 is pressed in, the signal is fed, via CH2 and C2, to another two pin speaker DIN socket connecting your loudspeaker or earphone. The reason the incoming and outgoing signals go via the two chokes and capacitors, is to prevent any stray radio frequencies from entering the TU1000, if you use an amateur radio transmitter.

The audio signals passing through the system are tapped off S1 via the passive filter components R2, R3, C3 and C4 into IC1. IC1, with diodes D1 and D2, amplify the audio signal and limit the output to approximately 1 volt. This stage will provide limiting for an input as low as 10 millivolts. The limiting action is provided in order that the volume setting of the receiver and the fading radio signal are maintained to a constant level within the range of the circuit. At this stage, the frequencies are not separated for mark and space. The splitting of mark and space tones is achieved by feeding the output of the limiter to IC2 (MF10).


The MF10 is a dual switched capacitor filter. It offers two independent filter blocks controlled by a clock generator and, in the mode I have selected, the frequency passed by the filters is 100 times less than the clock frequency. That is, for a filter frequency of 1275Hz, the clock must run at 127.5kHz. The passband, or width of the filter, is very narrow because the difference between tones can be as little as 170Hz. There are two clock frequencies required to drive each filter. These clocks are generated by IC3 and IC4, which are voltage controlled oscillators. IC4's frequency is set by RV5, which is 127.5kHz. IC3 produces the clock frequencies for the mark filter, by switching in RV1 to RV4, setting the voltage controlled oscillator to 144.5kHz, 170kHz and 212.5kHz. These are the necessary shifts for 170Hz, 425Hz and 850Hz. RV1, 2 and 3 are preset potentiometers, while RV4 is a front panel potentiometer for the variable shift whose range is from almost 0 up to 1000Hz. IC's 3 and 4 also provide clock outputs which are required for generating the audio tones needed for transmitting data.

The mark and space tones leaving IC2, on pins 2 and 19, are buffered by IC5, a quad op-amp (3403). The remaining two stages of IC5 perform the task of driving the dual meter M1 that shows the mark and space tone levels. It is necessary to convert the mark and space tones to a DC voltage in order that the meters can display a *relative level*. This is achieved by D4 and D5 and the voltage produced here is fed to C13 and C14. The effect of

Figure 2. Circuit Diagram

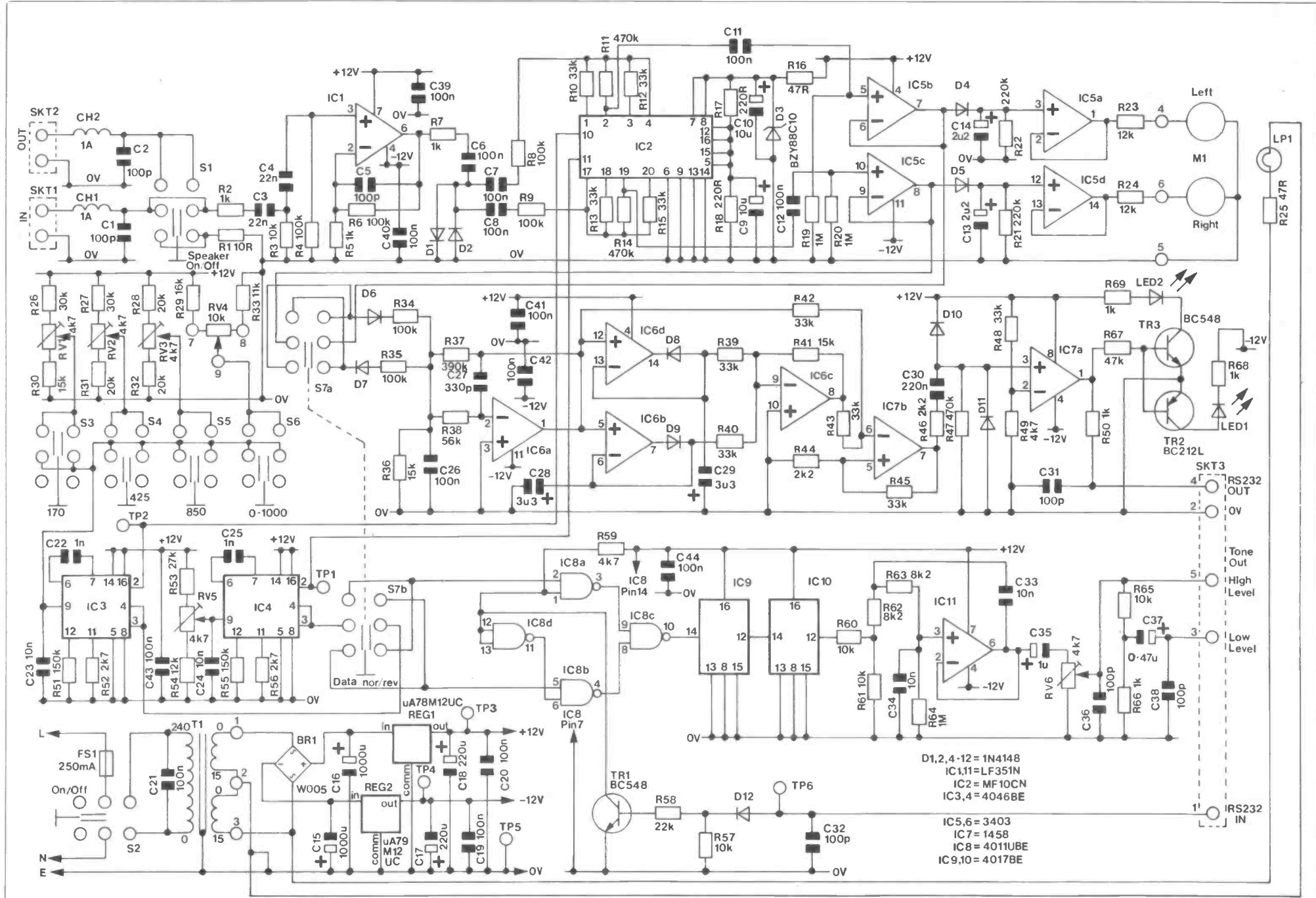

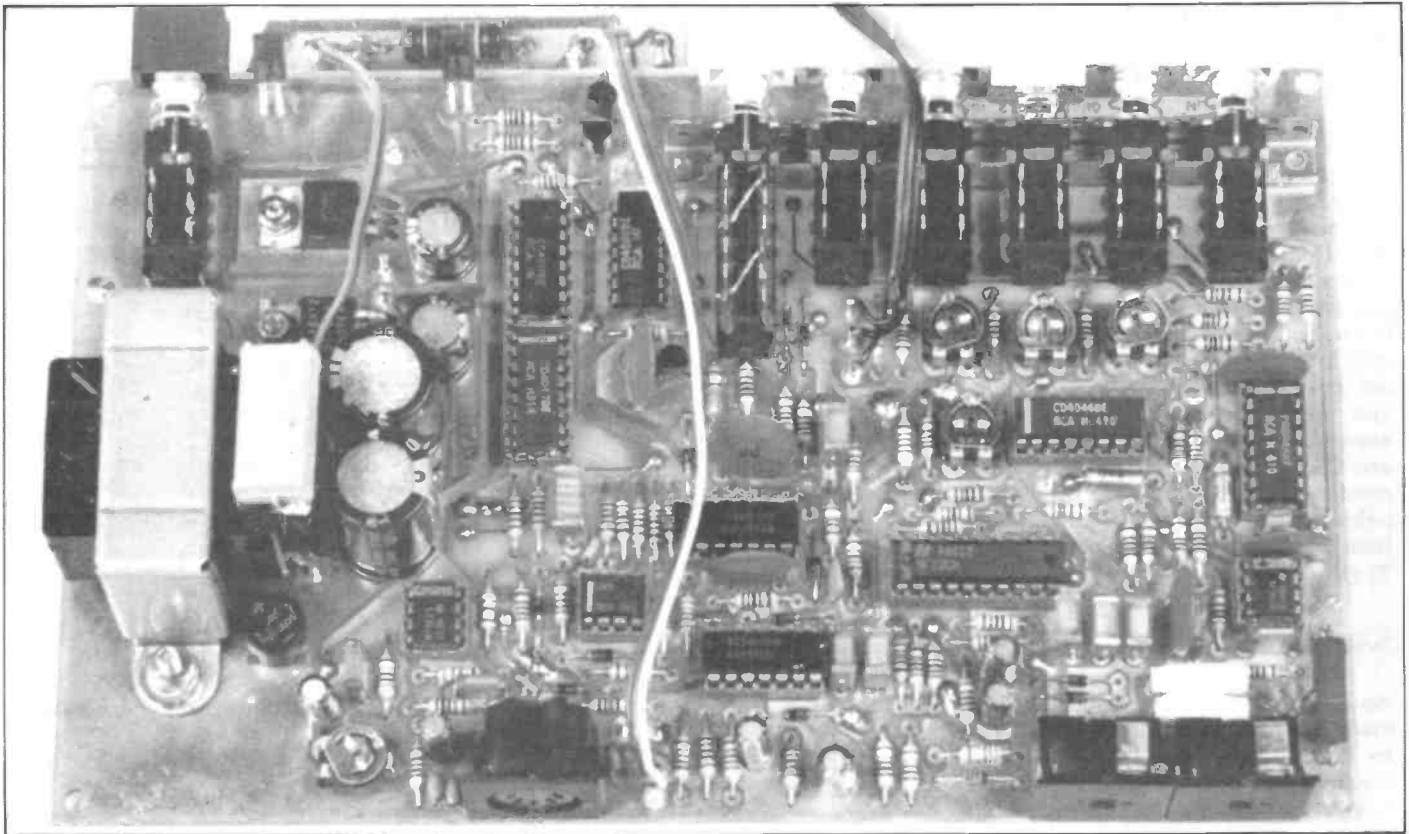- D1,2,4-12 = 1N4148
- IC1,11 = LF351N
- IC2 = MF10CN
- IC3,4 = 4046BE
- IC5,6 = 3403
- IC7 = 1458
- IC8 = 4011UBE
- IC9,10 = 4017BE



this is to slow down the changes in level over a short period of time to maintain a more stable reading on the meters which are back-illuminated by LP1.

As previously mentioned, the mark and space tones are buffered by two sections of IC5, and are then fed, via S7 (section A), to the discriminator diodes D6 and D7. The function of S7 (A) is to accommodate normal or reversed tones. The discriminator circuit produces DC pulses, positive or negative, depending upon the dominant signal from either filter. The output from the discriminator is connected to IC6 (3403), which forms the active part of a low-pass filter. The signal is then fed to the remaining three sections of IC6, forming the signal balancing circuit. The output from this circuit provides a bias voltage which centres the output level of the low-pass filter to the input of the first part of IC7, a dual op-amp (1458). This section is referred to as the 'Slicer', the function of which is to allow only its output state to change when its input exceeds the pre-set threshold, set by the values of R44 and R45. This circuit prevents low level signals from producing spurious outputs.

The second half of IC7 forms the 'mark hold circuit' which returns the RS232's output negative if a space signal is longer than 150 milliseconds. Normally, this condition will not arise, because even at 45.45 bauds, the maximum space timing element is shorter in duration than 150 milliseconds, ensuring that if a prolonged tone is received, it will not hold the RS232 output high. The output from this stage is monitored by TR2 and TR3, which switch LED 1, or LED 2, on. These LED's indicate the logic state of the RS232 output. LED 1 indicates the mark, or negative output, while LED 2 indicates the space, or positive output. Before the

RS232 output of IC7 is fed to pin 4 of the 5-pin DIN socket, it passes through R50 to limit the current should a short circuit accidentally appear on the RS232 line. Between pin 4 and ground, capacitor C31 has been placed to prevent any RF signals, that may be picked up on the leads connected to the 5-pin DIN socket, from entering the TU1000. This completes the description of the receiving part of the circuit and we now proceed to the audio tone generator used for transmitting.

If you recall, IC's 3 and 4 provide high frequency clock signal outputs which are now utilised in this part of the circuit to provide audio tones. S7, (section B), has the same function as section A, but allows normal or reversed tones to be transmitted. IC8 performs the function of selecting either the mark or the space high frequency clock when TR1 is turned on by the RS232 input on pin 1 of the 5-pin DIN socket. Normally, IC8 passes the mark clock frequency, however, when the RS232 input goes 'high', turning on TR1, IC8 gates the space clock frequen-

cy. The gated output of IC8 is fed to IC9 and IC10. These two IC's form a frequency 'divide by one hundred' stage which result in frequencies at the two audio tones required for transmitting. The audio tones will be directly related to the tones passed by IC2, the filter, because the same division ratio is used, which makes alignment of the transmit tones automatic, since they must be the same as the receive filter pass tones. In other words, once the receive tones are aligned, the transmit tones will also be aligned.

Before these tones can be fed to a transmitter, it is necessary to convert the square wave output of IC10 into a filtered signal, as a square wave is very rich in harmonics and can lead to a very wide transmitted signal. This is achieved by passing the square wave signal through a low pass filter, IC11. The cut-off frequency is set slightly higher than the maximum audio tone to be generated, and is set by the filter network, C33 and C34, R63 and R64. Although not a pure sine wave, the output is clean enough for transmitting

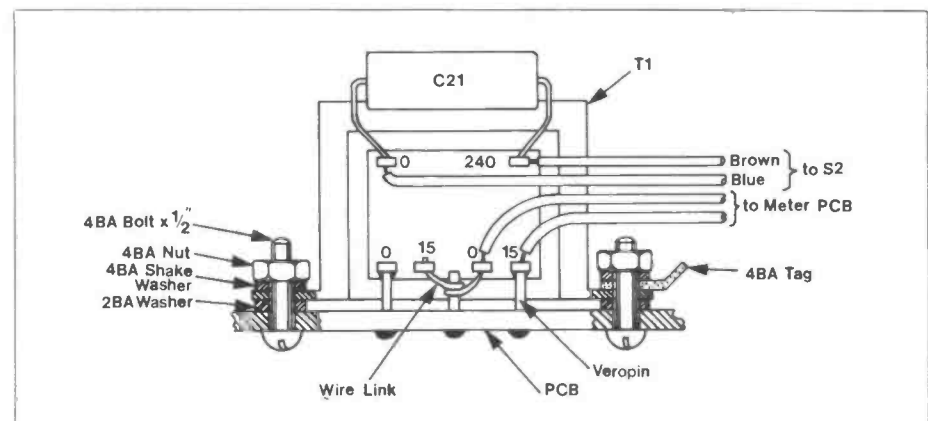


Figure 3. Transformer mounting

At switch position 6, install the leaf spring as shown in Figure 5. Using wire off-cuts from C21, solder two links onto S7. The switch assembly should not be mounted on the board at this stage.

Install the Veropins on the meter PCB in the same manner as the main PCB. As you will see from Figure 6, the pins protrude through side one of the board. The lamp is mounted on side two. This board is now fitted to the back of the dual meter by carefully bending the lugs of the meter over the board and soldering in position on one side. The meter assembly is also fitted at a later stage.

Returning to the main PCB, fit the resistors in their respective positions according to the legend and remove any excess wire after they have been soldered into position. The five preset potentiometers are fitted next. They are all of the same value and should be set at the halfway point of travel. The tantalum and the electrolytic capacitors are installed next. Make sure that they are correctly positioned according to their polarity. The remaining capacitors can be installed either way round and are fitted next.

Fit D3, a 10V zener according to its polarity marking. The remaining diodes are all of the same type (1N4148), and are fitted with the same consideration to polarity. The three transistors can then be fitted by matching the flat on the transistor with the flat on the board and soldering in place. The two RF chokes are mounted immediately behind the two 2-pin DIN sockets. The two LED's have to be mounted so that they will fit neatly through the holes in the front panel, see Figure 7.

Fit the mains switch, S2, pushing the switch leads into the board as far as they will go. Fit the switch assembly, S1, S3 to S7 in the same manner. Check that each of these switches is operating smoothly. Using Figure 8 as a guide, wire RV4, the 10k linear pot, using three lengths of wire from the ribbon cable to the three Veropins immediately behind S6.

The dual meter assembly is also wired according to Figure 8, using wire from the ribbon cable. Three connections are made from the meter to the three Veropins close to the 5-pin DIN socket and the remaining two 15V wires from the

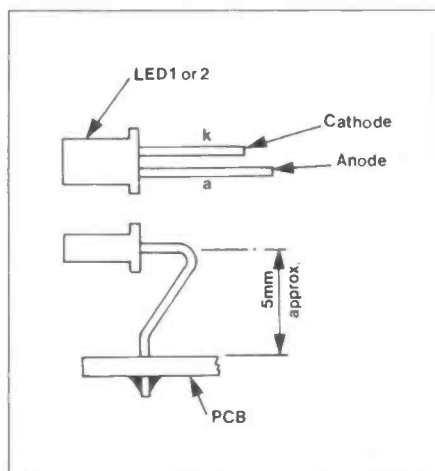


Figure 7. Fitting the LED's
September 1984 Maplin Magazine

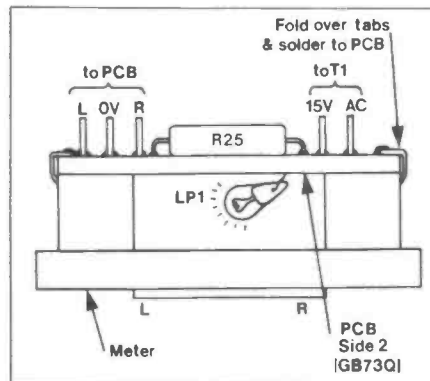
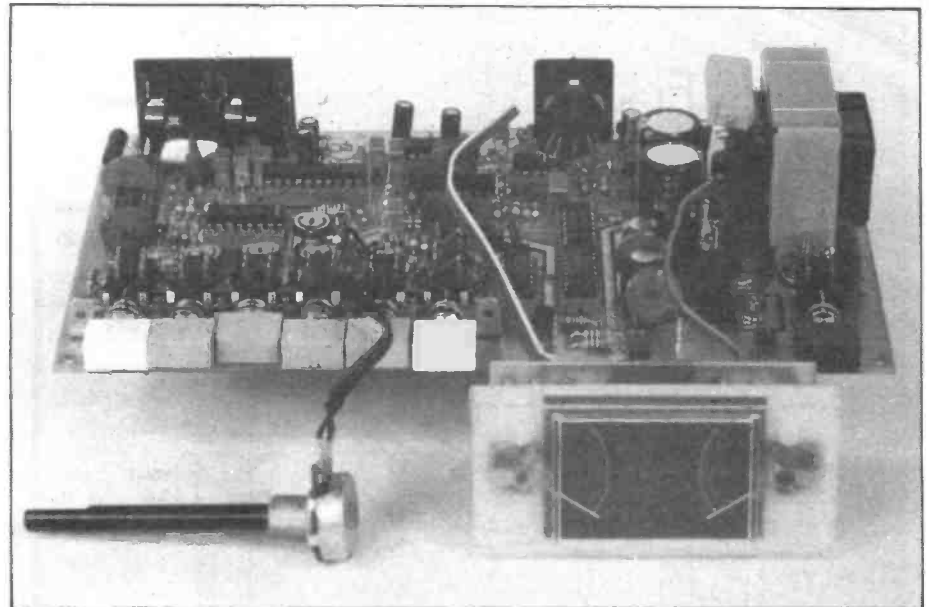


Figure 6. Meter illumination

mains transformer are connected to the meter board at the points shown in the diagram. This completes the construction of the main PCB, but note that the IC's are not to be inserted yet.

Initial Tests

Visually check the circuit board for the correct installation of the components, unsoldered joints, solder bridges, dry joints, capacitor and diode polarisation, and transistor orientation. Place the PCB on a clean non-conductive surface, with the meter assembly and RV4 clear of the board. Temporarily solder the mains

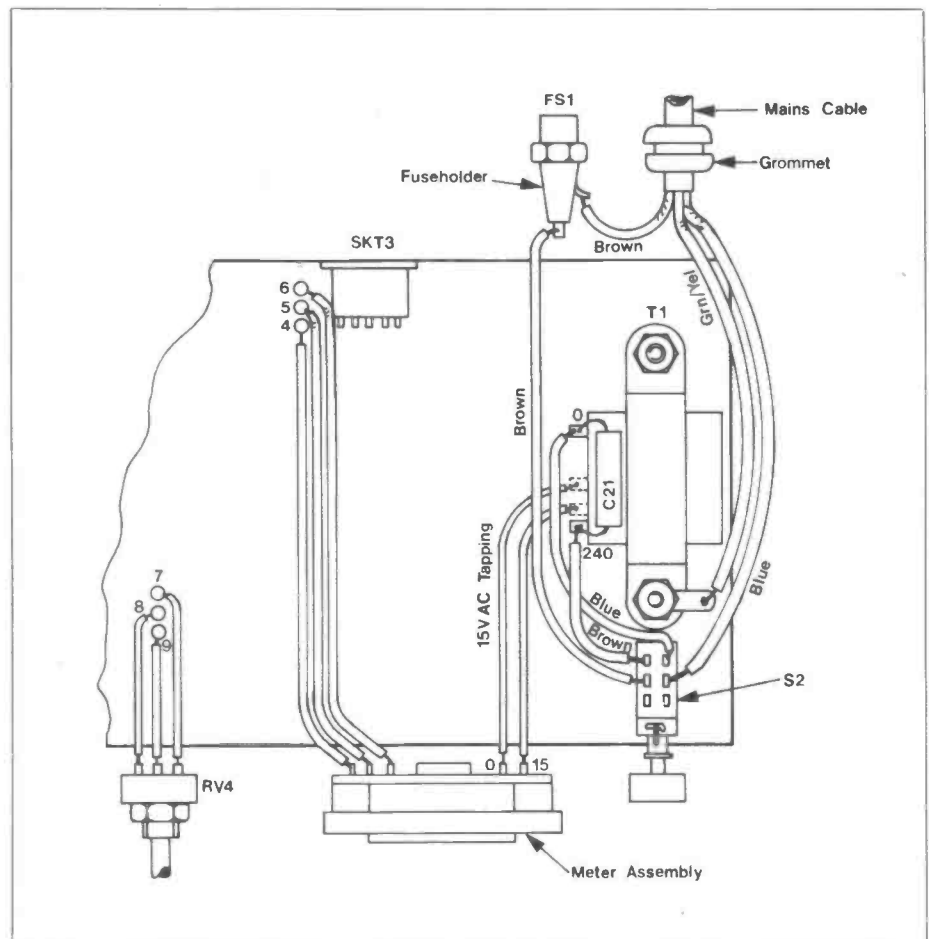


Figure 8. Wiring

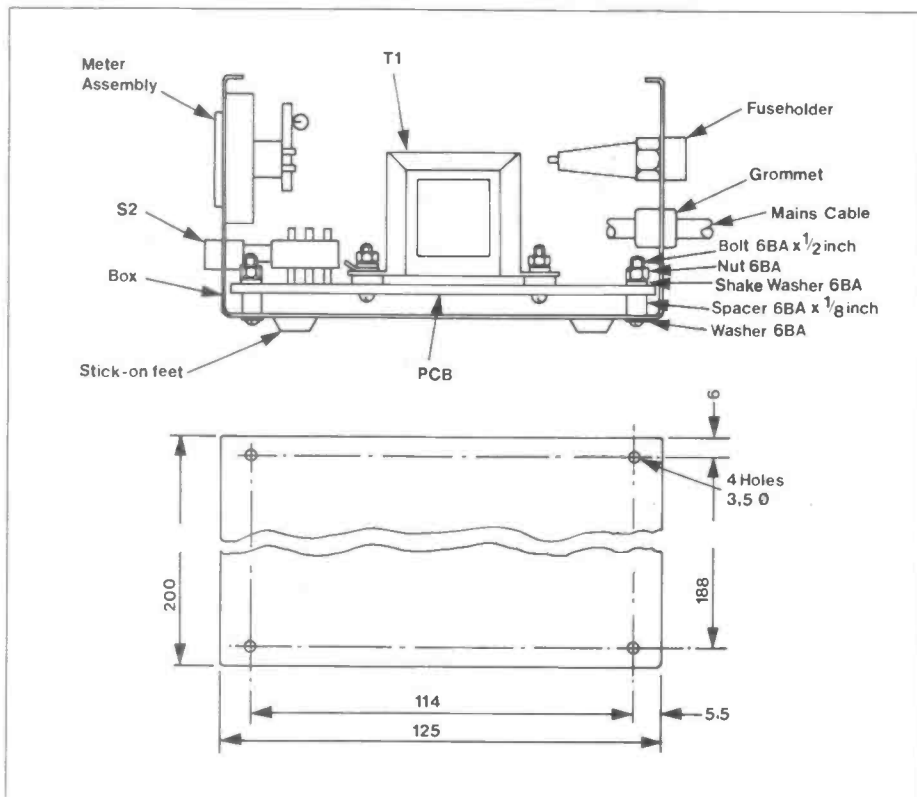


Figure 9. Case layout

cable to the transformer 0 and 240V tags and the mains earth lead to the solder tag installed on the transformer fixings. Insert a 3A fuse into a mains plug. **WARNING!! There will be live mains on the transformer, so please use extreme care.**

A voltmeter will be required in the following stages to check the power supplies to the various parts of the circuit. Plug the unit into the mains. At this stage LED1 and 2 will not light, but the meter bulb should. Set the voltmeter to cover a range suitable for 12V DC, connect the -V lead to Test Point 5 and the +V lead of the meter to Test Point 3, when a reading of between 11.5V and 12.5V should be seen. Reconnect the +V lead to Test Point 5 and the -V lead to Test Point 4, when a similar reading should be seen. Connect the -V lead to Test Point 5 and the +V lead to the cathode or banded end of D3. An approximate reading of 10V should be seen. If the readings you have obtained are within this range, the initial voltage tests are complete.

Disconnect the mains supply from the unit and insert all the IC's. You must be careful to insert these devices according to the notches on the IC and with the markings on the PCB. Check that all the pins are fitted into their respective holes, because they are easily bent under the IC. Reconnect the mains supply and LED1 should light, but not LED2. Repeat the voltage tests from the initial checks once more when you should obtain the same readings for each test as before.

These voltage tests allow us to proceed to the function tests. Set the following controls: S1 on (in), S3 on (in), RV4 set half way, and S7 off (out). Connect a piece of insulated wire between pin 5 of the 5-pin DIN socket and the round pin marked S on SKT1, one

of the 2-pin DIN sockets. The left-hand meter should indicate a full scale deflection and LED1 should remain on. Connect another piece of wire between Test Point 6 and Test Point 3. LED1 and 2 should momentarily change state and the left-hand meter should go from full scale deflection to low, and the right-hand meter should go to full scale. If S7 is switched on (in), the meter conditions will be reversed. Repeat this test for S4, S5 and S6. Remove the wire from Test Points 3 and 6. This completes all the function tests. Disconnect the unit from the mains supply, desolder and remove the mains connections from the transformer and earth tag.

Final Assembly

Referring to Figure 9, drill the holes for the PCB mounting pillars, drill the front and rear holes and cut the window for the meter using the decorative front and rear labels as templates. Thoroughly clean any swarf from the holes, clean the case with detergent and warm water and give all surfaces a thorough going over with methylated spirit. Remove the backing from the decorative front and rear labels and carefully stick them in position.

Stick the rubber feet supplied with the case in place on the base of the case. Carefully scrape away the paint from around the holes in the bottom inside surface of the case. This will provide an earth connection between the PCB and the case via the pillars. The PCB is mounted as shown in Figure 9, using the 6BA hardware from the kit. Strip approximately 5 inches of the outer sleeving from the mains cable provided, and cut off a 3 inch length from the brown wire and discard it. Strip a 1/4 inch length from all of the wires and twist and tin the ends

with solder. Pass the prepared lead through the mains inlet hole and fit the strain relief grommet. Solder the green/yellow earth lead to the solder tag on the transformer, and the blue 'neutral' wire to S2 (Figure 8). Fit the fuseholder, and solder the brown 'live' wire to the terminal as shown in Figure 8. Locate the 6 inch length of blue and brown mains wire from the kit and complete the wiring according to the diagram. Because all of these connections are directly associated with mains voltages check all of them very carefully before connecting the unit to the mains. Bolt RV4 into position and cut the plastic shaft to fit the knob. Carefully put a coat of impact adhesive to the recessed portion of the meter (M1) and also a suitable area around the inside of the cut-out in the case, following the adhesive maker's instructions. If not already fitted, put the control buttons onto the switches. With the completion of this stage, we can now proceed to the alignment of the unit.

Alignment

There are two basic methods of alignment: with test gear, or tuning around on a radio and adjusting the presets until you can resolve the incoming data. Tuning around is the least accurate method of the two, but you can, in time, obtain quite good results.

Using test gear is much more accurate, and this method is to be preferred if the unit is to be used for transmitting. The only test gear required is a digital frequency counter, the resolution of which must be capable of reading down to at least 100Hz. Because the frequencies involved are below 1MHz, even a modest counter is more than adequate.

Connect the test lead of the counter to Test Point 5, ground. The signal input lead of the counter should be connected to Test Point 1 and RV5 adjusted to give a reading of 127.5kHz. This sets the frequency of the space filter and the space tone output for transmit. Now connect the test lead to Test Point 2 and push in S3, adjusting RV1 to produce a reading of 144.5kHz. Leaving the leads in this position, press S4 and adjust RV2 for a reading of 170.0kHz. The last preset shift is set by RV3 and with S5 pushed in, adjust this preset to give a reading of 212.5kHz. This completes the fixed shifts and if S6 is pressed, the front panel control, RV4, will produce a reading of about 127.5kHz in the fully anti-clockwise position and about 227.5kHz in the fully clockwise position. The alignment of the TU1000 is now complete and you may connect it up to a computer and a suitable receiver.

RTTY Software

The software necessary to receive and transmit RTTY data can be as complex as you care to write. Not many RTTY or communication programs have been published in the computer magazines, but the program included in this article is for use with an Atari home computer and the Atari 850 RS232 interface. Due to the large number of

microcomputers used in the home, it is not possible, at the moment, to produce a program listing which will run satisfactorily on all machines. This is due to the various BASIC dialects and differing internal structures, such as port addressing and PEEK's and POKE's. It is hoped that sufficient interest will be generated in this article so that more computer systems might run RTTY software. If there is any feedback from this article, programs for other processors may be published in future editions of 'Electronics'. But note that Scarab Systems, 39 Stafford Street, Gillingham, Kent produce a range of suitable software for most of the popular home computers.

In order to help you write your own programs, here are a few guidelines. The program, if intended to be used for transmitting as well as receiving data, must have the ability to select either mode. If you intend to receive only, virtually half of the program may be discarded. As you can see from Figure 1. the decimal value allocated to each character is not the same as the ASCII value. For this reason, the value of one must be translated to the other for received codes as well as transmitted codes. A simple method for achieving this is to set up an array of sixty-four ASCII values, their positions in the array relating to the decimal value of the incoming or outgoing data. For example if the third value in the array was 65, this would represent the letter 'A'. When the 'figures shift' code is received, an additional offset must be added to select the correct position in the array to return the ASCII character codes for numbers and punctuation marks. If the program is written to support transmit facilities, an additional array of 128 values must be set up to convert ASCII values to the correct decimal value representing the outgoing data. The reason for the size of the ASCII array is due to the large number of possible values returned by a typical computer keyboard. Any non-valid key should be converted by the array, to a value of 0. This will inhibit values outside the range of the five-bit code.

This would be the minimal requirement for an RTTY program, but should really be used as the basis for additional refinements. Such refinements could be a split-screen to enable one, if transmitting, to compose your reply while the incoming message is being displayed on the other half of the screen, or it may be useful, if a printer is available, to add a hard copy option to the program. If you do not possess a printer, another manner of storage is to create a file on cassette, or preferably disc. Another very useful option is to be able to select the baud rate, if your system allows software control of the RS232 parameters. Pre-recorded messages and tests (RYR) could be retrieved from cassette or disc - another useful feature if you are transmitting. It is also possible that you may require other features to be built into your program. The possibilities are quite large and limited only by one's imagination.



The TU1000 In Use

A receiver that is capable of resolving RTTY signals must have a BFO (beat frequency oscillator), although most communications receivers have a built-in CW or SSB position, and of course an antenna to pick up the signals. The frequencies covered by a modern receiver are typically between 1 and 30MHz. It is within this range of frequencies that there are literally thousands of RTTY signals. Probably the best antenna to use for simple monitoring is a long wire, as long as possible and as high as possible. If you can orientate it South-West - North-East, so much the better. It is advisable to tune the receiver against a good external ground system, such as a buried bare copper wire, or a ground rod.

The connection to the TU1000 is made through the headphone or loudspeaker socket. Provision has been made

on the TU1000 for muting the sound output by pressing S1. This switches off the loudspeaker and introduces a 10Ω resistor which acts as a dummy load for the receiver audio circuit. The initial tuning is done by identifying the characteristic sound produced by RTTY transmissions and once this is done the data will be presented on the VDU avoiding the need to sit for hours listening to the tones.

I would recommend that initially you tune into one of the amateur RTTY portions of the band. A good start would be to set the receiver to 14.090MHz. It is around this frequency that RTTY signals will be found 24 hours a day, except in the winter when they will tend to disappear around sunset or shortly after. RTTY is easy to identify from the other signals most likely to be found in this portion of the band, namely morse code. RTTY signals have a pronounced warble as one tone is transmitted and then the next. Amateur RTTY transmissions are set at 170Hz shift between mark and space tones. Using the main tuning control of the receiver, tune across the RTTY transmission and you will notice that the sound of the pitch of the signal will change, the S-meter on the receiver will peak and the twin meters on the TU1000 should also peak together, usually at full scale. At the same time the LED's on the front panel should flash.

RECEIVED RTTY

E 9
 PRAVA ON INDIAN WHITE BOOK
 M O S C O W , JULY 15 ADN - AN IMPORTANT DOCUMENT - THIS IS HOW THE LEADING SOVIET PAPER PRAVA ON SUNDAY CALLS THE WHITE BOOK PUBLISHED BY THE INDIAN GOVERNMENT ON THE EVENTS IN THE COUNTRY IN THE PAST THREE YEARS. THE CORRESPONDENT'S REPORT SAYS THE DOCUMENT POINTS TO A GRAVE DANGER WHICH HAS ARISEN FOR INDIA FROM CONSPIRACIES OF RELIGIOUS FANATICS AND OTHER DIVISIONIST FORCES RECEIVING SUPPORT FROM ABROAD.

E 10
 TUNISIAN PRESIDENT RECEIVES SPANISH PREMIER
 T U N I S , JULY 15 ADN - PRESIDENT HABIB BOURGUIBA OF TUNISIA RECEIVED THE SPANISH PRIME MINISTER, FELIPE GONZALEZ, ON SATURDAY. THEY CONFERRED ON BILATERAL RELATIONS, THE SITUATION IN THE MIDDLE EAST AND ON QUESTIONS OF MUTUAL INTEREST.
 THE PREMIER IS ON A PRIVATE VISIT IN TUNISIA.

E 11
 FOUR TONS OF FALSE MONEY SEIZED
 P A R I S , JULY 15 ADN - FRENCH CUSTOMS OFFICERS HAVE SEIZED A LORRY AND TRAILER WITH 500,000 (500,000) FALSE TEN-FRANC COINS, WEIGHING FOUR TONS, ON THE ITALIAN BORDER.

E 12
 CHILEAN POLICE DENY ENTRY TO DAUGHTER OF LUIS CORVALAN
 U E N O S A I R E S , JULY 15 ADN - THE CHILEAN POLICE HAS REFUSED MARIA VICTORIA CORVALAN ENTRY INTO HER HOME COUNTRY, PRENSA LATINA REPORTS.
 THE DAUGHTER OF THE GENERAL SECRETARY OF THE COMMUNIST PARTY OF CHILE WAS PREVENTED FROM ENTERING THE COUNTRY AT SANTIAGO DE CHILE'S INTERNATIONAL PUDAHUEL AIRPORT AND PUT BY POLICE ON A PLANE TO ARGENTINA ALTHOUGH SHE HELD A VALID PASSPORT. MARIA VICTORIA CORVALAN WANTED TO VISIT FAMILY MEMBERS IN CHILE.

E 16
 TALKS BETWEEN CUBA AND UNITED STATES IN NEW YORK
 H A V A N A , JULY 15 ADN - CUBAN AND UNITED STATES GOVERNMENT OFFICIALS HELD TALKS IN NEW YORK ON JULY 12 AND 13, ACCORDING TO A STATEMENT RELEASED BY THE CUBAN FOREIGN MINISTRY AT THE WEEKEND. ACCORDING TO PRENSA LATINA, THE TALKS CENTRED ON ENTRY REGULATIONS BETWEEN THE TWO COUNTRIES AND ON WAYS OF CUBANS WHO HAD COMMITTED CRIMES RETURNING FROM THE U.S. TO CUBA. PREPAREDNESS FOR NEGOTIATING THESE QUESTIONS WAS STATED BY FIDEL CASTRO DURING HIS MEETING WITH U.S. PRESIDENTIAL CONTENDER JESSE JACKSON WHEN THE LATTER VISITED CUBA AT THE END OF JUNE.
 THE CUBAN DELEGATION WAS LED BY DEPUTY FOREIGN MINISTER RICARDO ALARCON.

E 17
 SOLIDARITY WEEK IN PUERTO RICO
 S A N J U A N , JULY 15 ADN - A WEEK OF PEACE AND SOVEREIGNTY BEGAN IN THE PUERTO RICAN CAPITAL SAN JUAN ON SUNDAY. IT HAS BEEN SPONSORED BY THE PUERTO RICAN CENTRE FOR COORDINATING SOLIDARITY WITH CENTRAL AMERICA AND THE CARIBBEAN AND BY THE NATIONAL COMMITTEE FOR SOLIDARITY WITH CENTRAL AMERICA. THE EVENTS ARE BEING MARKED BY SOLIDARITY WITH THE PEOPLES OF NICARAGUA AND CUBA.

E 18
 OPERATIONS OF SALVADOREAN LIBERATION FIGHTERS
 S A N S A L V A D O R JULY 15 ADN - MEMBERS OF EL SALVADOR'S NATIONAL LIBERATION FRONT FARABUNDO MARTI HAVE LAUNCHED FRESH ACTIONS AGAINST LINES OF SUPPLY OF THE DUARTE REGIME. FORTY KILOMETRES NORTH OF HERE THEY STOPPED A TRAIN DURING WHICH THEY PUT FORTY SOLDIERS OUT OF ACTION IN A SEVERAL-HOUR BATTLE.

Connect the TU1000's RS232 I/O port to your computer system. The normal rate of an amateur RTTY transmission is either 45.45 or 50 bauds. The majority of them are at 45.45 bauds. With this rate set by your system and the software set to receive, the data should now be displayed on the screen. S7 will have to be pressed if the signal is garbled, because the tones may be reversed. If the transmission is idling, the mark tone will cause the meter to peak. Therefore if the right-hand meter is peaked, then the reverse tones are being transmitted and if it is the left-hand needle that is peaked



then the tones are being transmitted in the normal manner. If, after trying these settings, the data is not being resolved, it is likely that the transmission is at 50 baud and again could be normal or reversed. When it is not possible to peak both

meters, it is likely that a shift other than 170Hz is being used, so try pressing the other fixed tone shift switches, or the variable control RV4.

If you would like to learn more about the subject, I would recommend contacting John Perkins, The British Amateur Radio Teleprinter Group, 5 Ash Keys, Southgate, Crawley, W. Sussex, who would be best able to assist. There are numerous books on the subject and again the secretary of BARTG can supply a list. I can personally recommend 'Guide to RTTY Frequencies' by Oliver P. Ferrell and published by Gilfer Associates Inc.

RTTY UNIT TU1000 PARTS LIST

RESISTORS: All 0.4W 1% Metal Film unless specified

R1	10Ω 3W Wirewound	1	(W10R)
R2,5,7,80,66,68,69	1k	7	(M1K)
R3,57,60,61,65	10k	5	(M10K)
R4,6,8,9,34,35	100k	6	(M100K)
R10,12,13,15,39, 40,42,43,45,48	33k	10	(M33K)
R11,14,47	470k	3	(M470K)
R16	47Ω	1	(M47R)
R17,18	220Ω	2	(M220R)
R19,20,64	1M	3	(M1M)
R21,22	220k	2	(M220K)
R23,24,54	12k	3	(M12K)
R25	47Ω 1W Carbon Film	1	(C47R)
R26,27	30k	2	(M30K)
R28,31,32	20k	3	(M20K)
R29	16k	1	(M16K)
R30,36,41	15k	3	(M15K)
R33	11k	1	(M11K)
R37	390k	1	(M390K)
R38	56k	1	(M56K)
R44,46	2k2	2	(M2K2)
R49,59	4k7	2	(M4K7)
R51,55	150k	2	(M150K)
R52,56	2k7	2	(M2K7)
R53	27k	1	(M27K)
R58	22k	1	(M22K)
R62,63	8k2	2	(M8K2)
R67	47k	1	(M47K)
RV1,2,3,5,6	4k7 Hor S-Min Preset	5	(WR57M)
RV4	10k Pot Lin	1	(FW02C)

CAPACITORS

C1,2,5,31,32,36, 38	100pF Ceramic	7	(WX56L)
C3,4	22nF Polycarbonate	2	(WW33L)
C6,7,8,11,12,26	100nF Polycarbonate	6	(WW41U)
C9,10	10μF 35V PC Electrolytic	2	(FF04E)
C13,14	2μ2F 63V PC Electrolytic	2	(FF02C)
C15,16	1000μF 25V PC Electrolytic	2	(FF18U)
C17,18	220μF 16V PC Electrolytic	2	(FF13P)
C19,20,39-44	100nF Disc Ceramic	8	(BX03D)
C21	100nF IS Cap	1	(FF56L)
C22,28	1nF Polystyrene 1%	2	(BX56L)
C23,24	10nF Ceramic	2	(WX77J)
C27	330pF Ceramic	1	(WX62X)
C28,29	3μ3F 35V Tantalum	2	(WW63T)
C30	220nF Polycarbonate	1	(WW45Y)
C33,34	10nF Polycarbonate	2	(WW29G)
C35	1μF 100V PC Electrolytic	1	(FF01B)
C37	0.47μF 100V PC Electrolytic	1	(FF00A)

SEMICONDUCTORS

D1,2,4-12	1N4148	11	(QL80B)
D3	BZY88C10	1	(QH14Q)
LED1,2	Red LED Shape R1	2	(YY45Y)
TR1,3	BC548	2	(QB73Q)
TR2	BC212L	1	(QB60Q)
BR1	W005	1	(QL37S)
REG1	μA78M12UC	1	(QL29G)
REG2	μA79M12UC	1	(WQ89W)
CH1,2	RF Supp Choke 1A	2	(HW04E)
IC1,11	LF381	2	(WQ30H)

IC2	MF10C	1	(QY35Q)
IC3,4	4046BE	2	(QW32K)
IC5,6	3403	2	(QH51F)
IC7	1458C	1	(QH46A)
IC8	4011UBE	1	(QL04E)
IC9,10	4017BE	2	(QX09K)

MISCELLANEOUS

T1	Min Tr 15V	1	(WB16R)
M1	Dual VU Meter	1	(YQ47B)
LP1	Wire Bulb 12V	1	(WQ13P)
S1-6	Latchswitch 2-pole	6	(FH67X)
S7	Latchswitch 4-pole	1	(FH68Y)
FS1	250mA Fuse 20mm	1	(WR01B)
SKT1,2	2-pin DIN Skt	2	(YX90X)
SKT3	5-pin DIN Skt	1	(YX91Y)
	Latchbracket 6-way	1	(FH80B)
	Rct Latchbutton Grey	4	(FH62S)
	Rct Latchbutton Red	1	(FH63T)
	Rct Latchbutton White	2	(FH64U)
	Safuseholder 20mm	1	(RX96E)
	DIL Skt 8-pin	3	(BL17T)
	DIL Skt 14-pin	3	(BL18U)
	DIL Skt 16-pin	4	(BL19V)
	DIL Skt 20-pin	1	(HQ77J)
	SR Grommet 6W-1	1	(LR49D)
	Knob K7B	1	(YX02C)
	Veropin 2141	1 pkt	(FL21X)
	Track Pin	1 pkt	(FL82D)
	C6A Mains Cable Black	2m	(XR03D)
	10-way Ribbon Cable	1m	(XR06G)
	Wire 3202 Blue	1m	(XR33L)
	Wire 3202 Brown	1m	(XR34M)
	6BA Bolt 1/4"	1 pkt	(BF05F)
	6BA Nut	1 pkt	(BF18U)
	6BA Shakeproof Washer	1 pkt	(BF26D)
	4BA Bolt 1/2"	1 pkt	(BF03D)
	4BA Nut	1 pkt	(BF17T)
	4BA Shakeproof Washer	1 pkt	(BF25C)
	2BA Washer	1 pkt	(BF20W)
	4BA Tag	1 pkt	(BF28F)
	4BA Spacer 1/8"	1 pkt	(FW30H)
	TU1000 PCB	1	(GB67X)
	Meter PCB	1	(GB73Q)
	Front Panel	1	(FJ53H)
	Rear Panel	1	(FJ54J)

OPTIONAL

Blue Case 222	1	(XY45Y)
DIN Plug L/S	2	(HH24B)
DIN Plug 5-pin	1	(HH27E)
13 Amp Plug	1	(RW67X)
3 Amp Fuse	1	(HQ32K)

A complete kit of parts (excluding Optional items) is available.
Order As LK53H (TU1000 RTTY Kit) Price £49.95

The following parts used in this project are also available separately, but are not included in our current catalogue.

FJ53H	Front Panel	Price £1.65
FJ54J	Rear Panel	Price £1.45
GB67X	Main PCB	Price £7.50
GB73Q	Meter PCB	Price £1.75

ELECTRONIC CHRONICLES

A Brief History of Electronics

by Mike Wharton Part 3

In this issue we shall continue following the infant subject of electronics as it developed during the last half of the 19th century. The foundations had been laid down by the earlier pioneers, but from this point the rate of development was to increase dramatically as the general tide of scientific advancement pushed forward. During the previous centuries the work had been carried out by a few individuals who had contributed single, but vital, pieces to the emerging 'jig-saw' puzzle of electricity. From now on the modern subject of electronics can be seen to take shape, supported by the many discoveries in the connected areas of physics and chemistry. It was during this period that some of the land-marks were pointed out by the leaders in their field, although it was not until 1897 that J. J. Thomson was able to prove the existence of the electron.

In 1868 Georges Leclanché invented a cell which bears his name, and which was the fore-runner of the modern dry battery. The availability of such a convenient current source made it possible to investigate the effect of passing an electric current through almost anything the scientists could lay their hands on. Passing a current along a wire gives rise to the heating and magnetic effects; passing a current through a solution produces effects which have led to the whole subject of electro-chemistry; and passing a current through a gas at low pressure eventually led to the production of the modern cathode ray tube, or CRT, something which we all look at every day!

HENRY

Up until this time, nearly all the work had been done by people living in Europe; the only notable exception being the American Benjamin Franklin. However, the name of another American, Joseph Henry, cannot go unmentioned here, since if history had been played a little differently it might have been his name we remember rather than Michael Far-



Joseph Henry 1797-1878

day's. Henry was born in Albany, the state capital of New York in 1797. He had only the barest of educations, but he was an avid reader. Like his contemporary, Faraday, a chance encounter with a book on science led to him studying seriously for entry to the Albany Academy, where he studied chemistry, anatomy and physiology with the intention of becoming a doctor of medicine. However, in 1825 he gave up the idea of becoming a doctor in favour of a career in engineering. After qualifying, he worked at the Academy for some years as a teacher and was appointed Professor of Mathematics. Six years after this he was made Professor of Natural Philosophy at the University of Princeton, where he taught a range of subjects, from mathematics and physics to astronomy and architecture.

From 1846, and for the remainder of his long life, Henry was the first director of the Smithsonian Institute in Washington. This well-known organisation was

founded by James Smithson, the wealthy son of the Duke of Northumberland. From the Smithsonian many other scientific bodies were to emerge, such as the Meteorological Bureau and the National Museum. Henry was also a founder member of the National Academy of Science and, during the American Civil War, was a technical adviser to Abraham Lincoln.

From his early days Henry was interested in electro-magnetism, and he greatly improved the power of his electro-magnets by using insulated wire, rather than just insulating the core. By this means he was able to use many layers of overlapping turns. He made a large electro-magnet for Yale College which was able to raise a load of one ton, a record at that time.

One of his major contributions to the subject of electronics was the discovery of self-inductance. He showed that when a current in a coil of wire changes in strength with time, a weaker current flowing in the opposite direction is produced, which retards the change in the original current. Another important discovery was that a varying current flowing in a coil produced a current in an adjacent coil, which is the basis of the transformer.

The American inventor was mortified when Faraday, who published his work on similar lines in 1831, received all the credit. Henry's other duties of teaching, together with his involvement on numerous committees, had delayed the publication of his own work. He was later given some recognition, and of course his name is remembered in the SI unit of inductance, an honour which was bestowed in 1893, after his death.

Henry also paralleled Faraday by constructing one of the first electric motors, which he regarded simply as a toy! He also designed and operated the first electric telegraph over a distance of a mile, and later used it to collect data for weather forecasts from a number of volunteers scattered around the country. With the help of his brother-in-law he

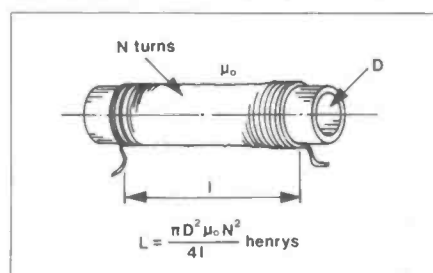


Figure 1. Inductance of Air-cored Solenoid.

carried out investigations into sunspots and solar radiation. By using a sensitive thermo-galvanometer he was able to show that sunspots are cooler than the normal surface of the sun. A potentially more significant discovery to the study of electronics was that the discharge from a Leyden jar, which was a primitive form of capacitor, was of an oscillatory nature. Moreover, the oscillations were of a very high frequency, and this was to be of great value to Hertz in his later work on electro-magnetic radiation.

Joseph Henry died in 1878 in Washington DC, and is considered by Americans to be one of their greatest scientists. Many claim that he actually beat Faraday by at least one year in discovering electro-magnetic induction, but that his other work delayed publication of the results. It is quite possible that had he devoted more time to his scientific pursuits and less to committee work he would have been of greater service to American science.



Ernst Werner Von Siemens 1816-1892

SIEMENS

Ernst Werner von Siemens was the eldest of four gifted brothers who were all engineers and inventors. Werner was born in 1816 at Lenthe in Hanover, Germany. His father was a patriot who believed in the unification of Germany, and so the family moved from the 'Royal British' province of Hanover to Meuzendorf in Mecklenburg-Strelitz. The young Siemens went to school in Lubeck and then decided to study engineering. His father thought that the Berlin Academy would be too expensive and decided that the Army could provide just as good an education for free! After some difficulty he managed to gain entry to the Prussian Army Engineer Corps, for special permission was needed from the King of Prussia for a 'foreigner' to join the army. He enjoyed the strict discipline of the army, and studied maths, physics and chemistry with great enthusiasm. However, he still managed to get involved in a duel, for which he served a short term in prison.

After a period spent at the Engineers and Artillery School in Berlin he moved to Wittenburg, where he produced his first invention. This was the plating of metal articles with gold and silver. He sold the rights to the process, and then used the money to finance further projects. As he began to make money from his inventions

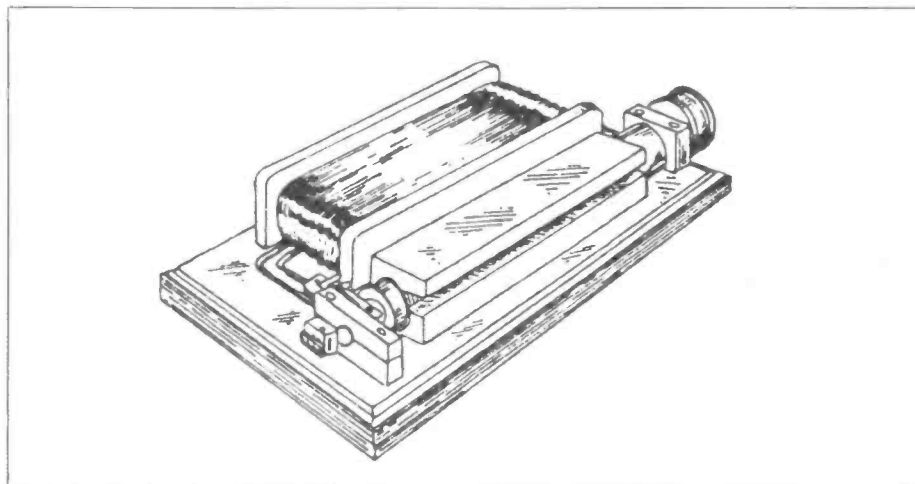


Figure 2. Siemens' self-exciting Dynamo, 1867.

he paid for one of his brothers, Karl Wilhelm, to travel to England to develop the market for his electro-plating and other inventions related to electricity. His brother eventually returned to Germany, but soon made his way back to England, which became his second home. Here he became involved with the manufacturers of iron and steel, and invented the Siemens Open Hearth Furnace. Meanwhile, back in Germany, Werner was busy developing other electrical inventions, such as the Wheatstone dial telegraph in which he introduced automatic make and break circuits, and which was adopted by the German and Russian railways in 1846. In 1847 the world famous firm of Siemens and Halske was founded in Berlin; J.G. Halske was Werner's brilliant mechanic. The factory made needle telegraphs, sounders for railways and insulated wire. Siemens also turned his attention to the generation of electric power. He developed a generator in which the usual permanent field magnets were replaced by electro-magnets, and invented the 'H' armature. He and his brothers were responsible for a great many inventions. Between them they were involved in the design of the trans-Atlantic cable laying ship 'Faraday', building an electric railway at Portrush in Ireland and the introduction of a telegraphy system throughout Russia; the news from the Crimean War reached St. Petersburg on the longest land-line of the day.

Ernst Werner von Siemens died in 1892 at the age of 76 at Charlottenburg in Germany. He had experienced the satisfaction of seeing his inventions come to fruition and attaining public acclaim worthy of his great creativeness. Besides other honours bestowed on him and his brothers, Werner also has the honour to have an SI unit named after him. The 'siemen' (S) is the unit of conductance, the inverse of the ohm.

KIRCHHOFF

Gustav Robert Kirchhoff was born at Königsburg, Prussia, now part of the Soviet Union, in 1824. On leaving school he entered Königsburg University where he studied theoretical physics. After getting his doctorate in 1848, he moved to a teaching post at Berlin University,

where he met the famous Bunsen. Both men then moved to Heidelberg, where they teamed up with Helmholtz. They were so successful that students flocked from all over Germany and abroad to hear their lectures and attend the laboratories. Kirchhoff was particularly interested in the field of spectrum analysis, and with Bunsen, discovered the metals Caesium and Rubidium. It was the almost non-luminous flame of Bunsen's famous burner that made such work possible, and it was originally designed for this purpose rather than the one it is usually put to these days in school laboratories.



Gustav Robert Kirchhoff 1824-1887

It is Kirchhoff's early work on electricity for which he is remembered in the form of 'Kirchhoff's Laws'. These describe in a formal manner the fact that the sum of any currents flowing into a junction is zero, and that in a closed circuit the e.m.f. applied is equal to the sum of the products of current and resistance.

An interesting story concerns Kirchhoff's bank manager who, when told by Kirchhoff of the discovery of terrestrial metals on the sun remarked "what use is gold on the sun if I can't get it down to earth?". Later, after Queen Victoria had presented him with a medal and a prize in gold sovereigns for his work on the sun's spectrum, he took it to the bank manager and said, "Look, gold from the sun!"

In 1868 he seriously injured his leg and this affected his general health. He returned to Berlin to the Chair of Physics, which was a less arduous job. His health continued to deteriorate and he was forced to retire in 1884. He died in Berlin in 1887 at the age of 63.



William Thomson, Lord Kelvin 1824-1907

LORD KELVIN

Lord Kelvin was born William Thomson in Belfast in 1824. His father was Professor of Mathematics, first at Belfast and then at Glasgow University when the family moved to Scotland. His mother died when he was only six, and his father took on the job of educating both him and his brother, James. He must have made a good job of it judging by the results, for William managed to pass the entrance exam to Glasgow University at the incredibly early age of ten. He was a very gifted student, and had produced no less than twelve research papers before he had even graduated. At the age of twenty-two he became Professor of Natural Philosophy at Glasgow and his work was soon known throughout Europe. He produced a flood of research works and, unlike many other scientists, kept his finances in strict order. During his life-time he amassed the sum of £160,000, a fortune in those days. The success of the Atlantic Telegraph Cable was due largely to his engineering genius. He determined the most suitable method for transmitting the signals, and invented instruments of the highest standard for sending and receiving them. For example he was responsible for the Kelvin bridge, which was used for measuring very low resistance, the Kelvin sounder and the Kelvin compass. He also discovered the 'Kelvin effect', also called the skin effect, where high frequency currents tend to concentrate at the surface of a conductor, a phenomenon which has been of great importance in

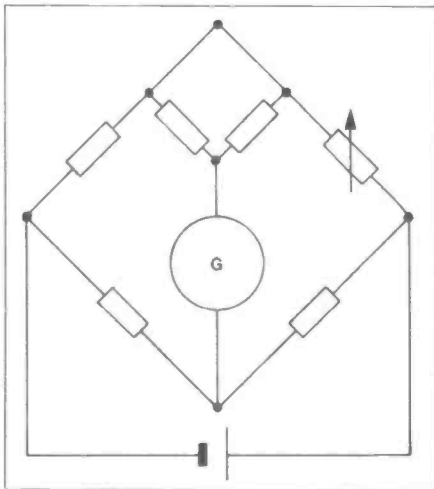


Figure 3. Kelvin Bridge (Thomson Double Bridge).

radio and high frequency heating. He also devised Kelvin's Law, which determines the most economical size of conductor for carrying electrical power, taking into account the cost of the cable used and the resistive losses incurred.

Kelvin was also greatly interested in the theory of conservation of energy, and developed the idea of an absolute scale of temperature. Thus he is remembered for the work which he did in this area, rather than that of electricity, and thermodynamic temperature is now expressed in the SI unit of kelvins, (K).

Thomson was knighted in 1866 for his many contributions to science and engineering, and took the title Lord Kelvin of Largs. He died at Netherhall, near Largs in Ayrshire in 1907 at the ripe old age of 83. During his life he had produced 600 scientific papers, taken out 70 patents, received honours from 250 academies and societies around the world, and made a considerable fortune.



James Clerk Maxwell 1831-1879

MAXWELL

James Clerk Maxwell is universally accepted as the greatest theoretical physicist of the nineteenth century. He possessed a wonderful mathematical ability and a complete grasp of physical reality together with a brilliant imagination. Thus he was able to make great advances in science without recourse to any preconceived ideas about the working of nature. Maxwell is mainly remembered in the study of electricity for his mathematical interpretation of Faraday's concept of the electro-magnetic field which had been deduced by his laboratory experiments. In carrying out this task he gave the world the electro-magnetic theory of light which paved the way for the discoveries of Rudolf Hertz 23 years later.

Maxwell was born in Edinburgh in 1831, but spent most of his early life on his parents estate at Middlebie. His mother died when he was eight years old and, like Kelvin, he was brought up by his father. At the age of ten he was sent to Edinburgh Academy where his broad Galloway accent and rather fancy clothes, in which his father had unfortunately dressed him, earned him the nick-name 'Dafty'. The other boys bullied him and he arrived home at the end of his first day bleeding and his clothes in tatters.

He showed no particular ability until he was put onto a course in maths at the

age of thirteen. He then made such swift progress that by the age of fourteen he had won a gold medal in the subject. At sixteen he entered Edinburgh University, where he made such an impression that he was allowed the run of the physics and chemistry labs, and was able to carry out any research in which he was interested. He then entered Trinity College, Cambridge in 1850 and was appointed Professor of Natural Philosophy at Aberdeen in 1856. In 1860 he was appointed Professor of Natural History at King's College, London.

During his time at King's College he carried out a great deal of research work on a variety of subjects, including the kinetic theory of gases and statistical mechanics. His work on electricity yielded the Maxwell bridge for measuring capacitance and inductance and his famous field equations. These formalized the ideas of Gauss, Faraday and Ampère and may be used to derive the theory of electro-magnetic radiation. He was able to predict the possibility of radio waves many years before their existence was shown by Hertz, and thus led the way to all the inventions which were to come in the field of electro-magnetic radiation.

On the death of his father in 1865 he retired from academic life and returned to the family estate in Scotland, where he devoted himself to research and writing his great treatise on electro-magnetism. In 1871 he was persuaded to accept the Cavendish Professorship at Cambridge, where he designed the new Cavendish Laboratories. He continued to work with unabated enthusiasm until the time of his death, which occurred after some stomach trouble, ignored because of the pressure of work. He suddenly became seriously ill and died on November 5th 1879 at the age of 48.



Heinrich Rudolf Hertz 1857-1894

HERTZ

Heinrich Rudolf Hertz was the son of a successful lawyer, born in the city of Hamburg in Germany in 1857. At school he was particularly fascinated by experiments in optics and mechanics, and attended additional evening classes on engineering and the use of measuring instruments. On leaving school young Rudolf decided to become an engineer and attended the Polytechnic Institute at Munich. After one year, though, he realized that his interest lay in the field of pure science and so moved to Berlin

Maplin Magazine September 1984

University to study under the famous trio, Kirchhoff, Bunsen and Helmholtz. Later on he went to Kiel for further study and was then appointed Professor of Physics at Karlsruhe, where he carried out his famous experiments on radio waves. It had been some years previously that Maxwell had put forward his theory that electrical oscillations could produce electro-magnetic waves, and that they would travel at the speed of light. Hertz used a spark coil to generate the electro-magnetic radiation, with large plates attached to each side of the spark gap. When the receiver was positioned close to this 'transmitter' a feeble spark could be observed in the receiver gap. Hertz then went on to show that the radiation had a wavelength of only 24cm, the same frequency used nowadays for microwave communication and radar. Moreover, he showed that the radiation behaved in the same manner as light, and could be reflected, refracted and polarised, and that its velocity was the same as that of light, 30,000,000 metres per second.

The name of Rudolf Hertz has become more prominent since the introduction of the Systeme International d'Unites (SI). Previously the term for the frequency of a periodic vibration was not connected with anyone's name, simply being described as 'cycles per second' or possibly 'vibrations per minute'. However, it is now named in honour of the German physicist who first demonstrated

$$\begin{aligned} \text{curl } H &= \partial D / \partial t + j \\ \text{div } B &= 0 \\ \text{curl } E &= -\partial B / \partial t \\ \text{div } D &= p \end{aligned}$$

Where:
 H is the magnetic field strength
 D is the electric displacement
 t is time
 j is the current density
 B is the magnetic flux density
 E is the electric field strength
 p is the volume charge density

Figure 4. Maxwell's Field Equations.

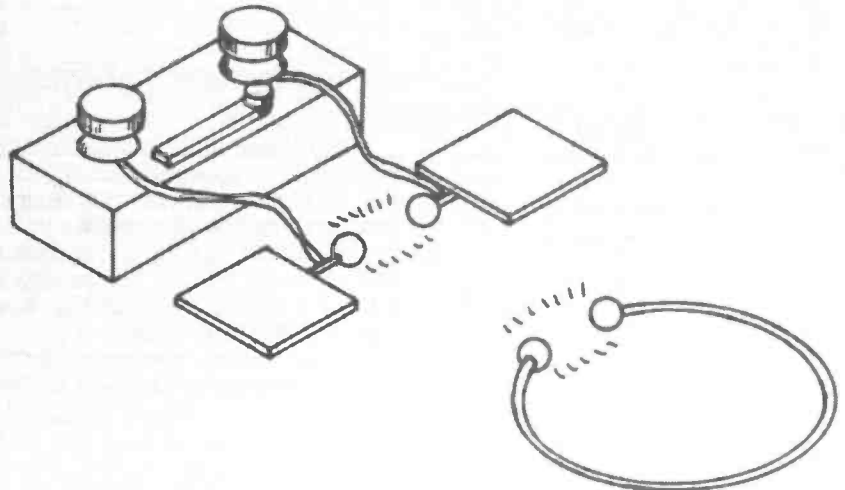


Figure 5. Hertz' Experiment.

ZX81 & YOUR BOAT *Continued from page 5.*

shelves in the corner, one above the other. The top one would carry the TV whilst the lower one would carry the ZX81 and the interface box. If the shelves were mounted over the chart table, so much the better. Of course, the shelves will have to be strong enough to hold the instruments in a rough sea. The best place for the wind instrument is on top of the mast. However, this will need long leads and make any maintenance very difficult. A 3 metre long pole fixed to the push pit would make life much easier. The instrument could be fixed to the top of this and the leads would be short and access would be easier. The trailer log can be fixed to the push pit by a length of rope in much the normal way. You may need to use a length of shielded wire through the cockpit or past any engine. On a previous model of the log, I found that I was counting the revs. of the engine as well! The positioning and securing of the compass should be considered very carefully. The device does not have a very high resolution but you do want it to give you the best service it can. It must be able to swing freely on its gimbles in all directions. It must not be close to any engines, metal or electronics. This compass doesn't have to be 'read' so it can be mounted safely in a locker out of sight and out of harms way. The tiller servo and follower can be mounted in a cockpit locker. The moving parts must be clear of obstructions. It would be useful if the tiller

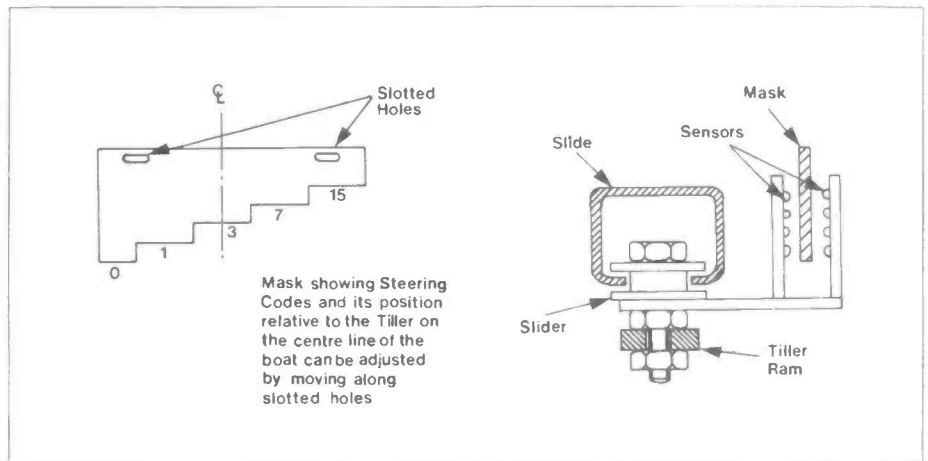


Figure 7. Tiller Follower



the transmission of radio waves and thus paved the way for the invention of wireless telegraphy.


In 1889 Hertz succeeded Clausius (of thermodynamics fame) as Professor at Bonn, but his career here was short-lived. Five years later, at the age of only 37, he died as a result of blood-poisoning on New Years Day, 1894. Seven years later the Italian engineer Guglielmo Marconi was successfully to transmit a wireless signal across the Atlantic.

This latter event heralded the enormous advances which were to be made in the 20th century, and next time we shall have a look at those famous names involved during this period.

follower mask was accessible so that it can be adjusted easily.

Power for the servo and the TV can be taken straight from the boats 12 volt DC supply. (Of course, the TV can be switched off if a display is not required, say during automatic steering.) It is necessary to use a separate power supply for the electronics. The ZX81 and the other circuits can be affected by the 'spikes' in voltage caused by the switching of the relays and the servo motor. The power needed is quite small and an old, but not dead, car battery will give many months of power. In part 2 of this article, I will give the circuitry and the program listing plus some hints on navigation.

COMPUTADRUM

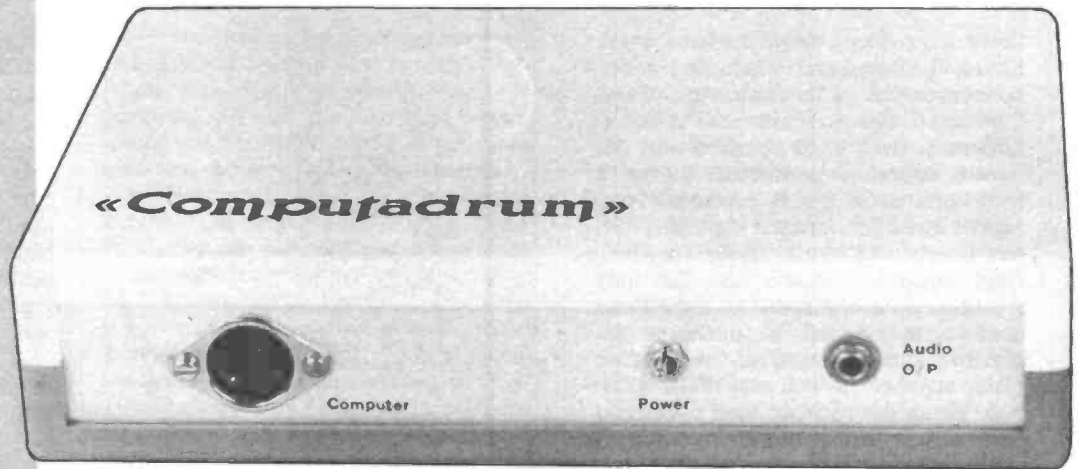

by Robert Penfold

This is a six channel drum synthesiser which is designed specifically for use with a home computer. The computer acts as a sophisticated sequencer, and the unit can be directly driven from the BBC model B, VIC-20, Commodore 64, Atari 400/600XL/800/800XL, and Memotech MTX500/512 machines.

It can also be used with machines such as the ZX81 and ZX Spectrum if they are fitted with an external input/output port that provides at least six digital outputs. For example, a ZX81 plus the Maplin ZX81 I/O Port would be perfectly suitable. The Computadrum only requires brief trigger pulses from the controller, and it could even be used with a non-computer based control circuit.

The sound generated by the unit is a simple fixed pitch drum sound rather than a falling pitch disco drum sound, but the pitch of each channel is tunable over a reasonably wide range using a preset control. Also, each channel has a resonance control which enables the output sound to be varied from a dull, short duration signal to a rich and resonant sound lasting a few seconds. Each drum has a different central pitch, and together they provide a very wide pitch range. The unit is battery powered and has an output for use with an external amplifier and loudspeaker.

Filters

Figure 1 shows the unit in block diagram form, and the circuit consists basically of six filters with their outputs combined by an active mixer stage. The output signal from the computer is a short

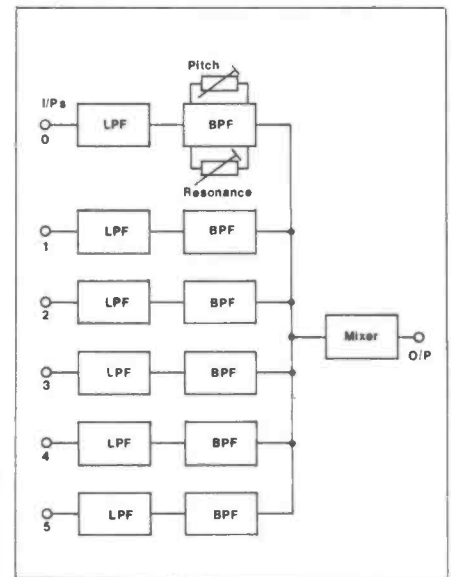


Figure 1. Block diagram

pulse which gives a 'click' sound, and each filter is fed from a digital output of the computer. A lowpass filter is used to remove most of the high frequency content on each input pulse to give a lower pitched 'thud' sound, like the initial sound when a drum is struck. A bandpass filter close to oscillation is fed with this signal, which excites the filter giving a short burst of sinewave signal at the output. The signal has a fast attack and slower decay, with the latter being controlled by means of the resonance control.

This gives a straightforward but quite realistic drum sound. The pitch and decay times can be controlled using the preset pitch and resonance controls, and the attack time is controlled by the cut-off

- ★ Complete Electronic Drum Kit for Your Home Computer
- ★ Six Variable Pitch Drums
- ★ Resonance Control Varies Drum Timbre
- ★ Works With Many Makes of Home Computer

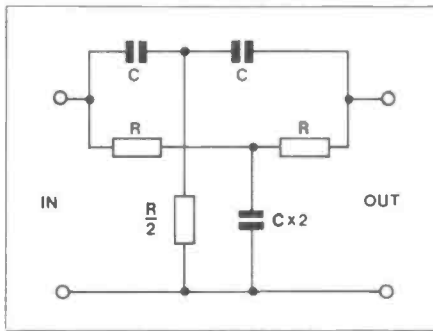


Figure 2. Twin T Filter

frequency of the lowpass filter. The operating frequency of each lowpass filter is not adjustable, but if desired the attack times can be altered by changing the value of the filter capacitor used in each lowpass filter. Thus, although this is an extremely simple way of generating a drum sound, it does give good control over the sound produced.

The bandpass filters are all based on the twin T arrangement shown in Figure 2, and the way in which this filter configuration obtained its name will probably be obvious. This passive filter circuit gives a notch of (theoretically) infinite attenuation at a certain frequency (the frequency at which the impedance of C is equal to that of R). This type of filter provides quite a narrow notch of attenuation, with losses of only a few dB being produced slightly 'off-tune'.

Of course, what we require in this application is a sharp bandpass response, which is the exact opposite of what the twin T configuration provides. However, by using a twin T filter in the negative feedback circuit of a reasonably high gain amplifier the required high Q bandpass response is obtained. All that

happens here is that the twin T filter provides a low impedance path at frequencies outside the notch, giving a large amount of negative feedback and little voltage gain. At the notch frequency (and very close to it) the impedance through the twin T network is so high that there is no significant negative feedback, and the amplifier has its open loop voltage gain.

The Circuit

Figure 3 shows the circuit diagram of the Computadrum. The filters are each built around one section of a CMOS 4069BE hex inverter. Although not really intended for use in linear applications, a CMOS inverter will operate as a linear amplifier having a voltage gain of about 34dB (50 times) if a bias resistor is connected between its input and output terminals. In this case the bias resistance is provided by two resistors in the twin T circuit. The six filters are essentially the same, the only difference being the use of different values in each one so that a different pitch range is covered.

If we consider the filter based on IC1a, C1 provides DC blocking at the input while R1 and C2 form the lowpass filter circuit. C4, C5 and RV2 are one of the T networks, and RV2 acts as the resonance control. Using the theoretically correct value in the RV2 position the circuit oscillates at its resonant frequency. This is due to the phase changes that occur through the twin T circuit, giving positive rather than negative feedback at the resonant frequency. RV2 is therefore used to give a somewhat higher resistance which prevents continuous oscillation from being produced. If RV2 is set just below the threshold of oscillation the

input pulse will still produce strong oscillations that take several seconds to decay, giving a very resonant drum sound. If, on the other hand, RV2 is well backed off from this point, the filter will have a low Q and the oscillations will rapidly die away, giving a short, well damped drum sound.

The other T network is formed by RV1, R3, R4 and C3. RV1 enables the resonant frequency of the filter to be adjusted, but as only one resistive element of the T network is being varied this inevitably means that adjustment of RV1 has some effect on the resonance setting of the filter. Similarly, adjustment of RV2 has a small effect on the operating frequency of the filter. In practice this interaction is too slight to be a major drawback, and it does not result in the unit being difficult to set up ready for use.

IC2 is used in the mixer circuit which is a standard operational amplifier summing mode type. The output from each filter circuit is quite high at a few volts peak to peak, and the mixer circuit has therefore been given less than unity voltage gain to prevent overloading if more than one drum is activated at any one time. The input resistors of the mixer have been given high values so that a high input impedance (about 220k) is provided at each input. This is essential as an input impedance of several kilohms or less is sufficient to damp the filters to the point where a resonant drum sound cannot be achieved.

Power for the circuit is provided by a 9 volt battery, and the current consumption of the circuit is only about 7 milliamps. IC3 is used to provide a well stabilised supply to the filter circuits, and this is necessary because changes in supply voltage affect the gain of the amplifiers, and therefore the resonance setting. The use of a stabilised supply for the filters ensures that consistent results are obtained, as the battery voltage drops due to ageing.

Construction

Details of the printed circuit board are provided in Figure 4. IC1 is a CMOS device, and it should be fitted in a 14 pin DIL IC socket. Leave it in the antistatic packaging and do not fit it into the socket until the board is in other respects finished. Handle the device as little as possible. The only other point to watch when building the board is to make sure that components are inserted in the right positions in the board. There are numerous resistors and physically similar capacitors, which makes it all too easy to produce mistakes. It is advisable to work through the components methodically and carefully, rather than just taking them at random and fitting them onto the board. Use Veropins at points on the board where connections to SK1, JK1, and S1 will eventually be made.

A Verocase measuring about 180 by 120 by 40 millimetres will comfortably accommodate all the components. SK1, JK1, and S1 are mounted on the front panel, as can be seen by referring to the photographs of the prototype. A 7 way DIN

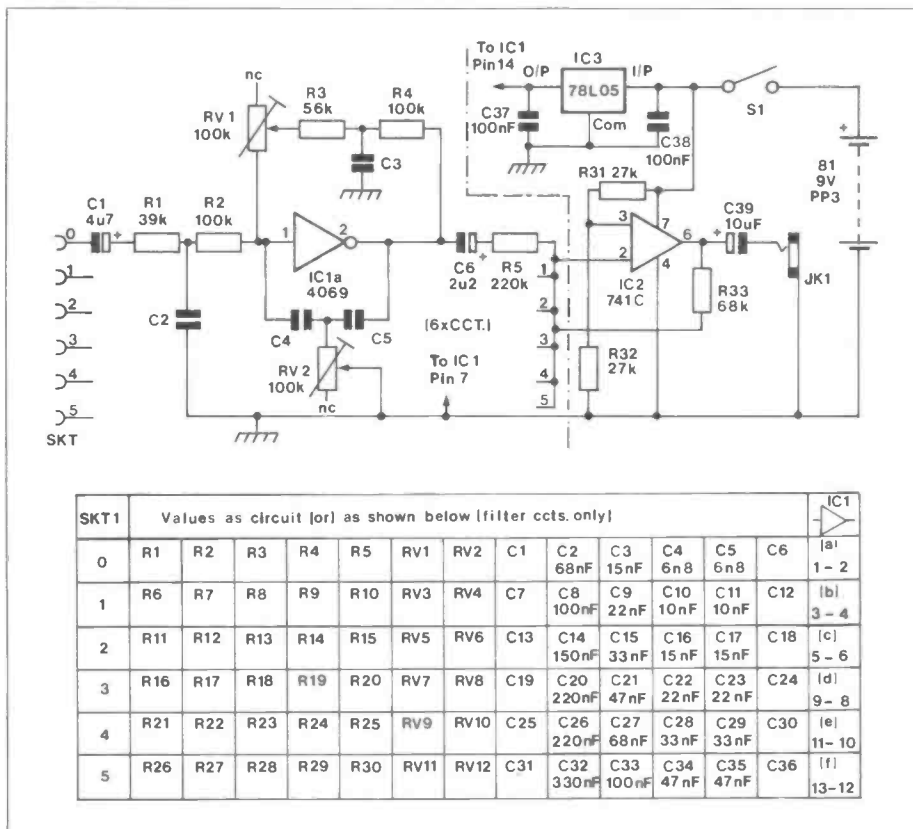


Figure 3. Circuit Diagram

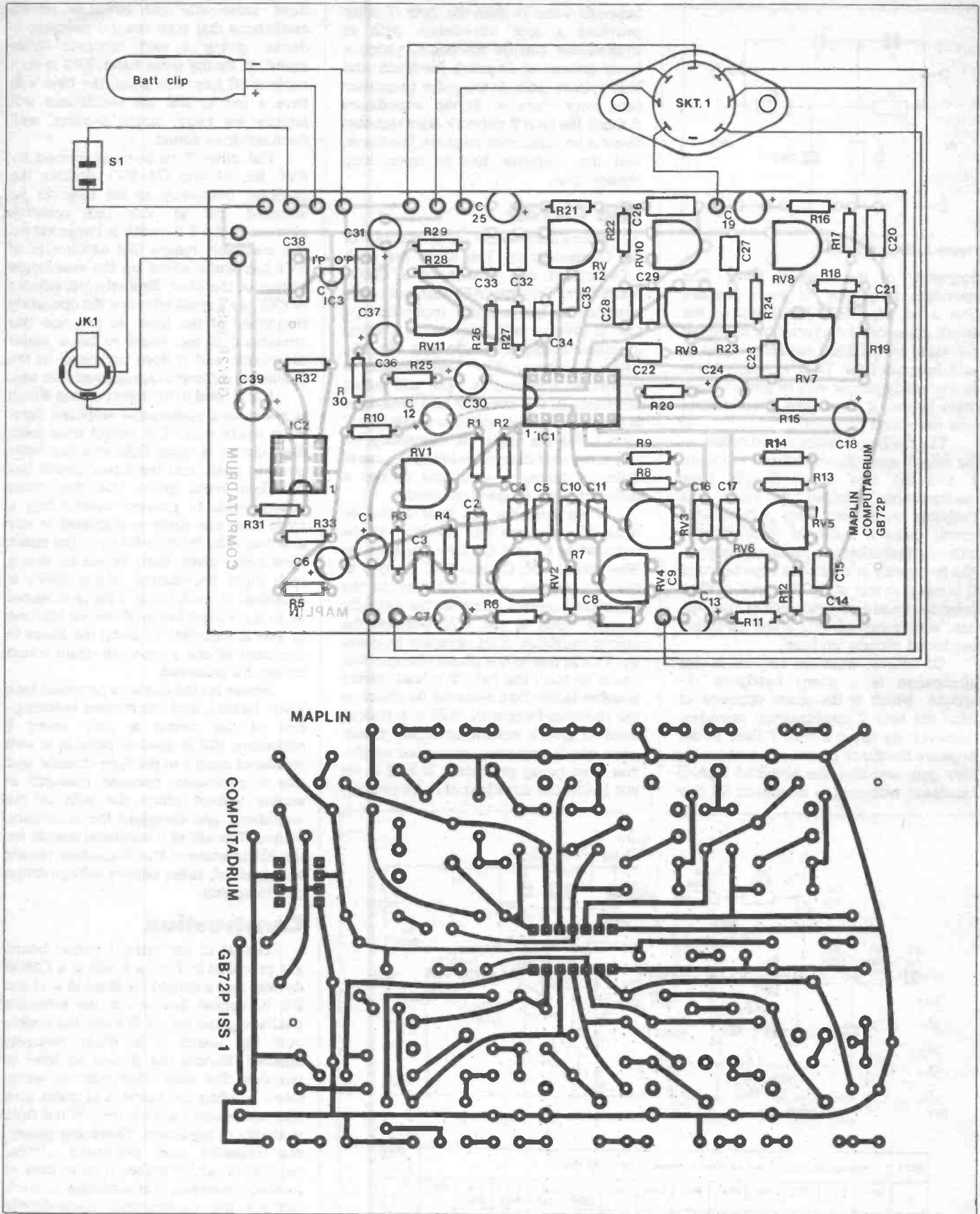


Figure 4. Artwork and wiring

socket is specified for SK1, and this is likely to be the most convenient type to use in practice, but obviously any socket having 7 or more ways will do. Assuming a DIN connector is used, two 6BA 1/4 inch mounting screws plus nuts are required.

Mount the completed printed circuit board on the base panel of the case using 6BA or M3 mounting bolts about 12

millimetres long. There are four mounting pillars moulded into the lower section of the case, but these serve no useful purpose in this case, and may in fact get in the way. They can easily be drilled out using a bit of about 8 to 10 millimetres in diameter. Finally, the hard wiring is added using ordinary multistrand insulated hook-up wire.

Connection

The audio output of the unit is coupled to the amplifier (or whatever) using an ordinary screened audio cable fitted with a 3.5mm jack plug which connects to JK1. Connection to the computer is via a piece of 7 way ribbon cable about 1 metre long, and fitted with a 7 way DIN plug at the end, which

connects to SK1. The connector used at the other end of the lead must obviously be varied to suit the computer used as the sequencer. For a VIC-20 or Commodore 64, a 2 by 12 way 0.156 inch edge connector is required; a 20 way IDC header socket is required for the BBC model B; the Atari machines need two 9 way D sockets; and for the Memotech machines a 14 pin DIL header plug is needed. Figure 5 gives connection details for all these computers. Note that the Memotech computers require a shorting lead from the output strobe terminal (pin 5) to ground (pin 16), to enable the outputs.

With any of the computers, an output pulse to trigger the unit is generated by setting an output line high and then immediately setting it low again. The speed of BASIC is such that a pulse of a few milliseconds in duration will be generated, and this is ideal. With machine code programs the output pulse generated will be too short unless a delay loop is used to suitably extend the pulse.

With the Memotech machine there is no setting up procedure required, and the Computadrum is controlled by writing data to the user port using the OUT 7,X instruction, where X is the value written to the port (e.g. OUT 7,2: OUT 7,0 would trigger channel 1).

With the VIC20, Commodore 64, and BBC model B computers the six lines of the user port that are used to control the unit must be set up as outputs. This is done by writing 63 to the data direction register which is at 37138, 56579, and &FE62 for the VIC20, Commodore 64, and BBC model B respectively. The Computadrum is then controlled by writing data to the user port which is at 37136, 56577, and &FE60 respectively. Joystick ports 1 and 2 of the Atari machines are set

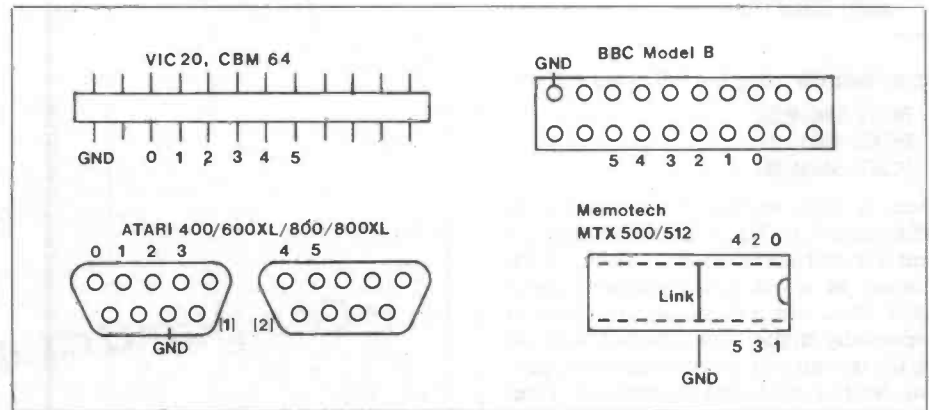
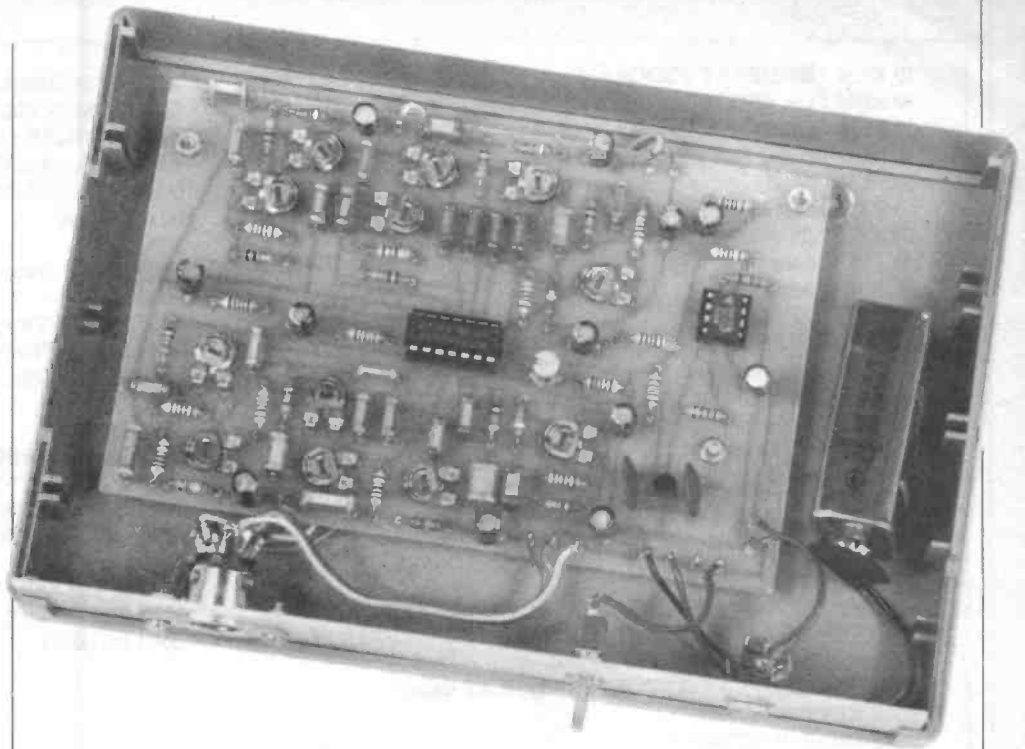


Figure 5. Connections to various computers

```

10 REM DRUMBEAT PROGRAM
20 REM FOR VIC20
30 REM SETUP
40 DIM ST(20)
50 POKE 37138,63
60 REM MAIN PROGRAM
70 GOSUB 1000:REM INPUT
80 GOSUB 2000:REM PLAYLOOP
90 GOTO 70
1000 PRINT "":REM CLEAR SCREEN
1010 INPUT "NUMBER OF DRUMBEATS":N
1020 FOR P=1 TO N*2 STEP 2
1030 INPUT "DRUM NO.":ST(P)
1040 INPUT "TIME INTERVAL":D
1050 ST(P+1)=D*50
1060 NEXT P
1070 RETURN
2000 PRINT:PRINT"PRESS ANY KEY TO STOP"
2010 FOR P=1 TO N*2 STEP 2
2020 POKE 37136,ST(P):POKE 37136,0
2030 FOR DE=0 TO ST(P+1):NEXT DE
2040 NEXT P
2050 GET A$:IF A$="" THEN 2010
2060 RETURN

```

For Commodore 64, change to:-

```

50 POKE 56579,63
2020 POKE 56577,ST(P):POKE 56577,0

```

```

10 REM DRUM CONTROLLER PROGRAM
20 REM FOR ATARI COMPUTERS
30 REM SETUP
40 DIM STORE(20)
50 POKE 54018,56
60 POKE 54016,63
70 GOSUB 1000:REM INPUT ROUTINE
80 GOSUB 2000:REM PLAY ROUTINE
90 GOTO 70
1000 ?CHR$(125):REM CLEAR SCREEN
1010 PRINT "NUMBER OF DRUMBEATS IN LOOP"
1020 INPUT N
1030 FOR P=1 TO N*2 STEP 2
1040 PRINT "DRUM ";
1050 INPUT DRUM:STORE(P)=DRUM
1060 PRINT "TIME INTERVAL ";
1070 INPUT DELAY:STORE (P+1)=DELAY*50
1080 NEXT P
1090 RETURN
2000 PRINT: PRINT "PRESS SELECT TO STOP"
2010 FOR P=1 TO N*2 STEP 2
2020 POKE 54016, STORE (P):POKE 54016,0
2030 FOR D=0 TO STORE (P+1):NEXT D
2040 NEXT P
2050 POKE 53279,8:IF PEEK (53279)..5 THEN GOTO 2010
2060 RETURN

```

```

10 REM DRUMBEAT PROGRAM
20 REM FOR BBC MODEL B.
30 REM SETUP
40 DIM STORE (20)
50 ?&FE62=63
60 REM MAIN PROGRAM
70 REPEAT
80 PROCinput
90 PROCloop
100 UNTIL FALSE
1000 DEF PROCinput
1010 CLS
1020 INPUT "Number of drumbeats", N%
1030 FOR P=1 TO N% *2 STEP 2
1040 INPUT "Drum No.",STORE (P)
1050 INPUT "Time interval", D
1060 STORE (P+1)=D*100
1070 NEXT P
1080 ENDPROC
2000 DEF PROCloop
2005 PRINT"PRESS ANY KEY TO STOP":REPEAT
2010 FOR P=1 TO N% *2 STEP 2
2020 ?&FE60=STORE(P):?&FE60=0
2030 FOR delay=0 TO STORE (P+1):NEXT delay
2040 NEXT P
2045 UNTIL INKEY$(1)=""
2050 ENDPROC

```

```

10 REM DRUMBEAT PROGRAM
20 REM MTX 500/512 VERSION
30 DIM STORE (20)
40 GOSUB 1000:REM INPUT
50 GOSUB 2000:REM PLAY LOOP
60 GOTO 40
1000 CLS
1010 INPUT "Number of drumbeats?";N
1020 FOR P=1 TO N*2 STEP 2
1030 INPUT "Drum No.?";STORE (P)
1040 INPUT "Time interval?";DELAY
1050 LET STORE (P+1)=DELAY*50
1060 NEXT P
1070 RETURN
2000 PRINT: PRINT "PRESS ANY KEY TO STOP"
2010 FOR P=1 TO N*2
2020 OUT 7,STORE(P): OUT 7,0
2030 FOR D=0 TO STORE (P+1): NEXT D
2040 NEXT P
2050 IF INKEY$="" THEN GOTO 2010
2055 PRINT "OUT OF LOOP"
2060 RETURN

```


up as outputs using the following routine:

```

POKE 54018,56
POKE 54016,63
POKE 54018,60

```

Data is then written to the outputs at address 54016. When initially testing the unit it is probably best to start with all the presets at about half maximum resistance. Then use a short loop program to repeatedly trigger one channel, and set up the two presets for that channel to give the desired pitch and resonance. Then repeat this procedure for the other five channels. For those who do not wish to devise their own software the accompanying listings give suggested software for each of the machines mentioned here, and these programs are self explanatory in use.

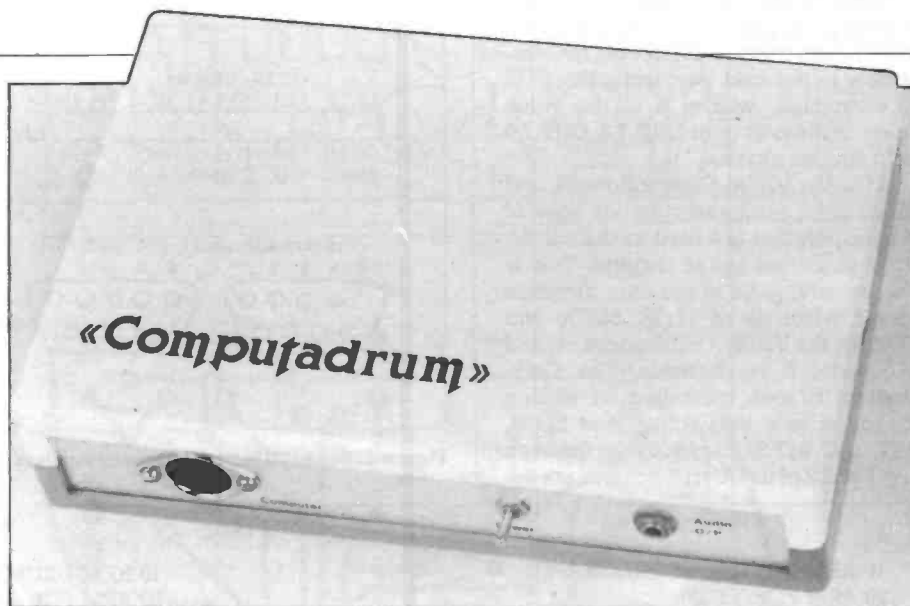

COMPUTADRUM PARTS LIST

RESISTORS: All 0.4W 1% Metal Film			
R1,6,11,16,21,26	39k	6	(M39K)
R2,4,7,9,12,14,17,	100k	12	(M100K)
19,22,24,27,29		6	(M56K)
R3,8,13,18,23,28	56k	6	(M220K)
R5,10,15,20,25,30	220k	2	(M27K)
R31,32	27k	1	(M68K)
R33	68k	12	(WR61R)
RV1-12	100k Hor Sub-Min Preset		
CAPACITORS			
C1,7,13,19,25,31	4µ7 63V PC Electrolytic	6	(FF03D)
C2,27	68nF Polycarbonate	2	(WW39N)
C3,16,17	15nF Polycarbonate	3	(WW31J)
C4,5	6n8 Polycarbonate	2	(WW27E)
C6,12,18,24,30,36	2µ2 63V PC Electrolytic	6	(FF02C)
C8,33	100nF Polycarbonate	2	(WW41U)
C9,22,23	22nF Polycarbonate	3	(WW33L)
C10,11	10nF Polycarbonate	2	(WW29C)
C14	150nF Polycarbonate	1	(WW43W)
C15,28,29	33nF Polycarbonate	3	(WW35Q)
C20,26	220nF Polycarbonate	2	(WW45Y)
C21,34,35	47nF Polycarbonate	3	(WW37S)
C37,38	100nF Minidisc	2	(YR75S)
C39	10µF 35V PC Electrolytic	1	(FF04E)
C32	330nF Polycarbonate	1	(WW47B)

SEMICONDUCTORS

IC1	4069BE	1	(QX25C)
IC2	µA741C (8 pin)	1	(QL23Y)
IC3	µA78L05AWC	1	(QL26D)

MISCELLANEOUS

SKT1	DIN Socket 7 Pin	1	(HH37S)
JK1	Jack Socket 3.5mm	1	(HF82D)
S1	SPST Ultra-Min Toggle	1	(FH97F)
	Printed Circuit Board	1	(GB72P)
	Veropin 2145	1 pkt	(FL24B)
	PP3 Clip	1	(HF28F)
	DIL Socket 14-pin	1	(BL18U)
	DIL Socket 8-pin	1	(BL17T)
	Hook-up Wire	2m	(BL00A)

OPTIONAL

Case Verobox 214	1	(LQ07H)
Bolt 6BA ½inch	1 pkt	(BF06G)
Nut 6BA	1 pkt	(BF18U)
Spacer 6BA ½inch	1 pkt	(FW33L)
Plug Scr. 3.5mm	1	(HF81C)
DIN Plug 7-pin	1	(HH30H)

A complete kit of parts (excluding Optional items) is available.
Order As LK52G (Computadrum Kit) Price £9.95

The Printed Circuit Board used in this project is available separately.
Order As GB72P Computadrum PCB Price £2.95


MAPLIN

FOR

THE

FOR

THE

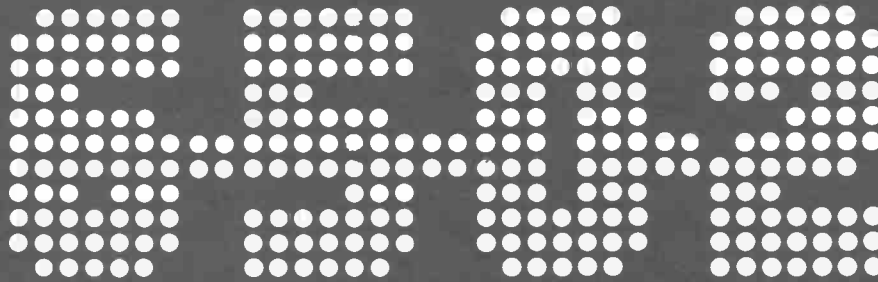

by Graham Dixey C.Eng., M.I.E.R.E. Part Six

Introduction

The 6522 VLA, which is often associated with the 6502, offers 16 parallel input/output lines plus several control lines which can oversee the transfer of data between the micro and certain peripherals. A basic discussion of this was undertaken in the last article and it is now time to look at further facilities offered by this extremely versatile support chip. We shall start with the 6522's timer facilities.

The 6522 Timers

The 6522 has two timers, designated logically as Timer 1 and Timer 2. They are able to perform either input or output functions. When used on output, a timer will generate a specified single pulse or train of pulses. The duration of the pulse or the number of pulses will be specified by the contents of the timer register. When used on input, a timer will either measure the length of a pulse or count the number of input pulses. The register mentioned above is first cleared in this mode. Whether used as input or output, when dealing with single pulses the timer is said to be in the 'one-shot' mode. However, when handling trains of pulses, the timer is in the 'free-running' mode.

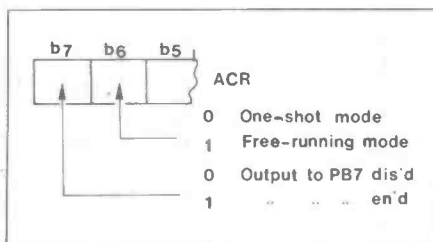


Figure 1. Use of the ACR to control Timer 1 modes.

Timer 1 has four operating modes which are determined by bits 6 and 7 of the Auxiliary Control Register (ACR). This is shown in Figure 1. Bit 6 determines whether the timer is in single-shot or free-running mode, while bit 7 enables or disables an output on PB7 of Port B. This latter can be used to signal the end of a

timed period when timing out for example. The easiest way to assimilate this is by an application example, which will now be described.

Performing Two Simultaneous Tasks

This is an apt heading in more senses than one since, not only can one show how to make the micro perform two (or more) unrelated tasks but, at the same time, the use of the timer facility can be demonstrated. Let us start by specifying the two tasks:

- (i) the micro will generate a square-wave of a specified frequency and mark/space ratio, for outputting to some external device.

- (ii) the micro will also continuously monitor data input at a port and process this data.

Taking item (i) first, it was shown in Part Four of this series that square-waves could be generated by successively taking an output line to logical 1, logical 0, logical 1, etc. while interposing a delay loop between these transitions in order to specify the frequency and mark/space ratio. This method does work but has the disadvantage that the micro is 'twiddling its thumbs', so to speak, between said transitions. Why not make it fill in the time with some useful employment? This is exactly what will be done by passing the responsibility for generating the time intervals over to one of the 6522 timers, say Timer 1. This allows the micro to get

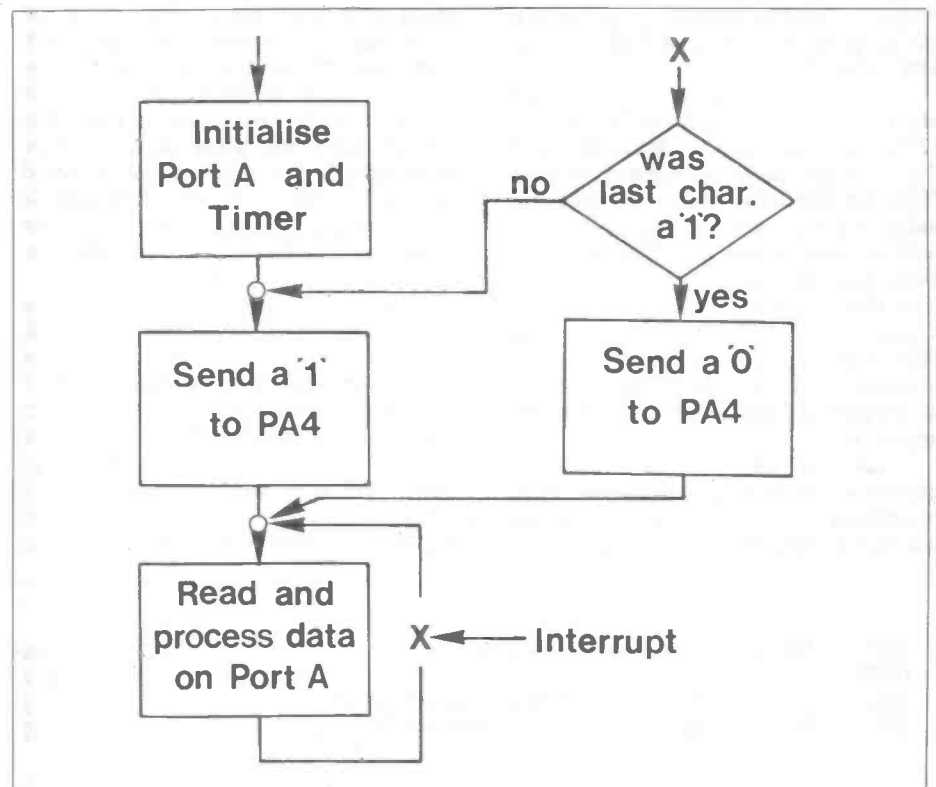


Figure 2. Flow-chart for timer application example.

LDA	#F0	Initialise Port A: PA0 - 3 as inputs;
STA	DDRA	PA4 - 7 as outputs (square-wave on PA4).
SEI		Disables \overline{IRQ} .
LDA	#C0	Initialise timer: output to PB7 enabled;
STA	ACR	free-running mode selected.
LDA	#00	Set timer count i.e. establish frequency
STA	T1L	of square-wave (mark/space ratio is 1:1).
LDA	#02	
STA	T1H	

Table A.

on with some other job while the timer ticks happily away. This 'other job' is, of course, the task specified in (ii) above i.e. data handling at Port A. When the timer 'times out' we just 'interrupt' the data handling program momentarily while the next transition of the square-wave is generated and then return, hardly knowing that we have been away. If the timer has been put into the free-running mode it will go straight into another timing sequence exactly as before. The result will be a continuous square-wave output and a data-handling program that appears continuous so short are the breaks in it. Bearing all the foregoing in mind, the problem should be formally stated now, in the form of a flow-chart (Figure 2).

The Flow Chart

A flow-chart is not just a pretty picture. It really does help to clarify one's thought processes, get the procedure sorted out, break the program down into separate blocks and, finally, test the likelihood of the program's success by means of a dry run. In this case, there are five blocks, the first of which is concerned with initialising the ports and timers i.e. establishing their exact roles in the program. In Assembly Code it looks like Table A.

The Timer 1 register is sixteen bits wide, each byte being loaded separately (T1L = low byte; T1H = high byte). So in this example the initial register value is 0200 and the timer will decrement this value down to zero, at which point it is said to have 'timed out'. Obviously any value from 0000 to FFFF could be loaded into this register, giving a range, in decimal, from 0 to 65535. The value of 0200 in decimal is 512 and is an arbitrary choice in this case; it gives a square-wave of frequency 500Hz with a unity mark/space ratio.

The next block on the flow-chart generates the leading (positive) edge of the square-wave. This it does by loading the Port A Data Register (DRA) with the

LDA	MEM0	Tests last transition at PA4.
CMP	#01	
BEQ	SEND0	Branches to SEND0; makes PA4 logic 0.
BMI	SEND1	Branches to SEND1; makes PA4 logic 1.

Table D.

SEND1	LDA	#10	Send '1' to PA4.
	STA	DRA	
	STA	MEM0	Notes that PA4 is at logic 1.

Table B.

INDATA	LDA	DRA	Get four lowest bits only (PA0 - 3)
	AND	#0F	of Port A.
	JMP	SUB1	Jumps to data handling routine (actual routine not specified); returns to INDATA, forming a continuous loop.

Table C.

HEX value 10. Write out this number in binary (00010000) to see that it puts a '1' into the fifth bit position from the right which corresponds to PA4. This is a very short program segment which, in Assembly Code is shown in Table B.

One little trick in the program is to generate the alternate positive and negative edges of the square-wave. This means taking PA4 alternately to the logic 1 and logic 0 levels. It is necessary to note the direction of the last transition in order to know which way it has to go next time. To this end, MEM0 is a memory location that holds a '1' or a '0' according to the direction of the last transition. This is then consulted before each new transition and updated after it.

At this point, on the first pass through the program, the leading edge of the square-wave would have been generated and the timer would be counting down. It is possible to put the 6502 to work on the main program of data handling while leaving the 6522 to look after the first half-cycle of the square-wave.

Table C shows a program segment using a 'masking' operation (AND#0F) to get the data input on lines PA0 - 3. This is then handled by a sub-routine which keeps returning for more data. This it does until 'interrupted'. And that is the important point. It should be appreciated that it doesn't really matter what task the main program is performing. What is being demonstrated is that the micro can occupy itself with some job but can be diverted, momentarily, at the required instant in order to do something else. In this example it is the cessation of the timing period that initiates the interrupt procedure.

Assuming that an interrupt occurs during the main program then this will bring us to the decision diamond on the flow-chart. Was the last character a 1? This question is answered in the program segment that follows, (Table D), by the CMP#01 instruction and the two branches BEQ and BMI. It will be remembered that the CMP#01 instruction subtracts 01 from the Accumulator con-

tents (without actually affecting these contents) and conditions flags in the Processor Status Register according to the result. If the Accumulator is first loaded with the contents of MEM0 then, if MEM0 holds a '1', the result is zero (BEQ branch taken to SEND0), since last transition was positive, this one must be negative. But, if MEM0 holds a '0', this will give a negative result and the BMI branch to SEND1 will be taken. Thus MEM0 is consulted, as stated previously, in order to determine the sign of the last transition. See Table D.

We come now to the final program in which PA4 is taken to logic 0 when required and MEM0 is updated to record this fact. This loops back to the main program to continue handling data input as before. See Table E.

Now count the number of lines in the

PC	OPCODE	BYTE 2	BYTE 3
0020	A9	F0	
0022	8D	03	09
0025	78		
0026	A9	C0	
0028	8D	0B	09
002B	A9	00	
002D	8D	04	09
0030	A9	02	
0032	8D	05	09
0035	A9	10	
0037	8D	01	09
003A	85	60	
003C	AD	01	09
003F	29	0F	
0041	4C	00	03
0044	A5	60	
0046	C9	01	
0048	F0	02	
004A	30	E9	
004C	A9	00	
004E	8D	01	09
0051	85	60	
0053	4C	3C	00

Table F.

SEND0	LDA	#00	Send a '0' to PA4.
	STA	DRA	
	STA	MEM0	Notes that PA4 is at logic 0.
	JMP	INDATA	Returns to main program.

Table E.

complete Assembly Code program i.e. Tables A to E inclusive: there are 23 all told. Thus, there will be the same number of lines in the Machine Code program. A line by line comparison should present no problems and there are no tricks in encoding into machine code. Only four addressing modes are used (all non-indexed): Implied (Inherent); Zero-page; Absolute and Relative. Assigning addresses is a matter for the programmer according to the specific machine in use. Those given in Table F are mainly on zero page, the exceptions being the 6522, which is on page 9 as previously agreed, and the sub-routine for the data handling, which has been located on page 3. The complete machine-code program is shown in Table F.

The data for the branches is computed in the usual way. Just as a reminder, the branch length is always taken from the address 'immediately after' the program line for the branch. Thus for the BEQ instruction, the branch starts at 004A and ends at 004C (2 steps FORWARD), while for the BMI instruction, the branch starts at 004C and ends at 0035 (23 steps BACKWARDS). Converting these two distances to signed HEX gives: +2 = 02 and -23 = E9.

Interrupts NMI and IRQ

It will be remembered that programming bit 7 of the ACR enabled or disabled an output on PB7 (bit 7 on Port B) and, since this occurs at the end of the timer period, it effectively signals its conclusion. The question is - how can we make use of this facility?

What we want to do is to interrupt the 6502 processor at the end of each timed period in order to generate either the leading or the trailing edge of the square-wave. The 6502 has two interrupt lines, one of which has a lower priority than the other.

The lower priority line is $\overline{\text{IRQ}}$ - INTERRUPT REQUEST in full. This line, when taken low, will stop the execution of the program, allowing the processor to complete its current instruction only before initiating an interrupt sequence which diverts it from the main program to do something else; that 'something else' is called INTERRUPT SERVICE ROUTINE (ISR). In the example that we are dealing with the ISR is merely a short piece of program that produces the square-wave transitions at PA4. However, the 6502 will

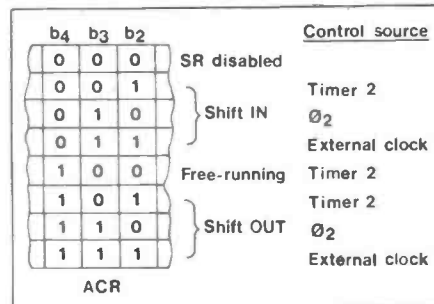


Figure 3. Role of the ACR in shift register control.

only respond to $\overline{\text{IRQ}}$ going low if the 'interrupt flag' in the Processor Status Register is 'clear'. This is achieved with a CLI (Clear Interrupt Mask) instruction. If, however, the SEI (Set Interrupt Mask) instruction has been used then the interrupt flag will be 'set' and the $\overline{\text{IRQ}}$ going low will be ignored. It has been 'masked out', giving priority to calls on the other interrupt line $\overline{\text{NMI}}$ (Non-Maskable Interrupt). It is this procedure that assigns the priority in a case where both interrupt lines are in use. In the specific program that we are dealing with we could equally well have used $\overline{\text{IRQ}}$. However, $\overline{\text{NMI}}$ was chosen in order to introduce the SEI instruction just as if there were another device connected to $\overline{\text{IRQ}}$.

Now to return to the 'end of timing' signal on PB7. To make use of this we must do two things:

- (i) Make an electrical connection from PB7 on Port B of the 6522 to the $\overline{\text{NMI}}$ pin of the 6502
- (ii) Tell the 6502 where to find the start address of the Interrupt Service Routine. This is known as the 'interrupt vector'. This interrupt vector is contained in two specific,

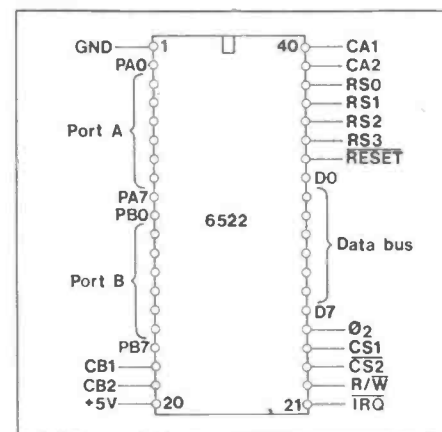


Figure 4. 6522 VIA pin-out diagram.

consecutive memory locations (which are machine dependent - see user manual). The programmer must remember to load this vector into these two locations at the time that he enters the rest of the program into RAM. For this particular program the ISR starts at location 0044; this is therefore the interrupt vector for this program.

The subject of interrupts will be dealt with in detail in the next article together with the topic of 'stack' operations.

The Shift Register (SR)

This section of the 6522 chip operates as either a parallel - serial (output) or serial - parallel (input) converter. It can be programmed to shift data at a rate determined by one of a number of sources e.g. Timer 2, 02 of the system clock, or an external clock. It is also able to output data continuously (free-running mode) under the control of Timer 2. These modes are selected by programming the appropriate pattern of bits into bit positions 2, 3 and 4 of the ACR, as shown in Figure 3. The Shift Register is actually connected to pin CB2 of the 6522.

To use this register on output the user first loads it with data, which operation initiates the shifting process. At the end of an 8-bit shift, bit 2 of the Interrupt Flag Register is set, a fact which can be tested by the program. An example of a parallel - serial 'shift out' is given in the Assembly Code segment - shown in Table G.

To shift data in serially and then fetch it as an 8-bit word (parallel input) is similar. The ACR is cleared and initialised to select the mode, which also starts the shifting. A loop is set up to keep testing bit 2 of the IFR to establish when the whole 8-bit word is in. When bit 2 is set the data word can be stored in memory via the accumulator.

In Assembly Code, a typical serial - parallel 'shift-in' program is shown in Table H.

This completes what is, necessarily, a fairly brief survey of the facilities of the 6522. It is evident that it offers a lot of potential in the handling of input and output data, whether in parallel or serial form. Further, the timers allow functions to be performed while the processor is otherwise occupied. Interrupts allow this task to be suspended momentarily. The pin-out for the 6522 is shown in Figure 4.


LDA	#00	Clear ACR.
STA	ACR	
LDA	#18	Program bits 3 and 4 of the ACR to be '1's, - shift out under 02 control.
STA	ACR	
LDA	MEM1	Fetch data from a memory location.
STA	SR	Send data to shift register.

Table G.

LDA	#00	Clear ACR.
STA	ACR	
LDA	#08	Program bit 3 of the ACR to be 1,
STA	ACR	shift in under 02 control.
AGAIN	LDA	IFR
		Done for 8 bits? [Tests bit 2 of
	AND	#04
		IFR (SR interrupt flag)].
	BEQ	AGAIN
		Keep testing.
	LDA	SR
		Get data from shift register.
	STA	MEM2
		Store data in memory.

Table H.

New Books

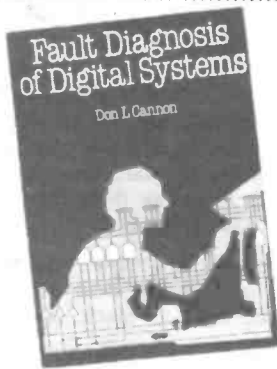

Fault Diagnosis of Digital Systems

by Don L. Cannon
Although modern semiconductor technology and integrated circuits have improved the reliability of digital systems to the point where one rarely thinks about it anymore, what do you do if the system does develop a fault, or to use the jargon, develops a 'bug' or is said to have 'a failure'? This book helps the reader to understand the workings of digital systems and digital system component operation, so that he may go on to tackle fault-finding ('trouble-shooting' or 'de-bugging'), and the book covers this in detail. A must for anyone who has any concern for the welfare and maintenance of their home computer, and is also of use to those wanting to take up the servicing of digital systems as a career.

210x147mm, 270 pages, illustrated.
Order As WM88V (Fault Diag Dig Syst) Price £10.65NV

25 Simple Indoor and Window Aerials

by E.M. Noll
For the short wave listening enthusiast who may be living in a flat or similar accommodation where the use of external aerials is impossible, this book describes how one can install aerials in or around the room, attic, windows, ceiling etc - twenty five different permutations are shown in detail. The book also shows how simple variations can be improved for the best optimum performance. Much information is given on the short wave bands, aerial directivity, time zones, working dimensions etc.

178x110mm, 70 pages, illustrated.
Order As WM81C (25 Simple Ind Aerial) Price £1.90NV

25 Simple Indoor and Window Aerials




Micro Interfacing Circuits - Book 1

by R.A. Penfold

It is now perfectly feasible for the average amateur electronics enthusiast to build reasonably simple add-ons for a microcomputer, and transform it into a versatile and sophisticated piece of equipment for measurement or control. This book will help those who, although having some previous knowledge of electronics, are unfamiliar with the 'interfacing jargon'. It describes the basic principles of interfacing circuits to microprocessor equipment, but not just in a purely theoretical manner. The circuits are all practical ones using real devices. Subjects covered include address decoding, parallel and serial interfacing, A to D and D to A converters etc.

178x110mm, 98 pages, illustrated.

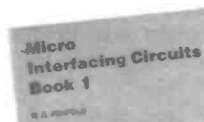Order As WM79L (Micro I/Face Ccts) Price £2.35NV



An Introduction to Programming the ATARI 600/800 XL

by R.A. and J.W. Penfold



An Introduction to Programming the Atari 600/800XL

by R.A. and J.W. Penfold

Learning to program in BASIC might at first appear to be a daunting task, but it can be made much easier if tackled in a sensible way. This book takes the reader, step by step, from the fundamentals of BASIC, on to more advanced topics such as animated graphics, allowing the reader to exploit the Atari's exceptional graphics and sound capabilities. Although it is impossible to cover every aspect of a micro as versatile as the Atari fully, the authors have attempted to complement the manufacturers' information rather than just copy it. Hopefully the reader will be able to write their own programs and progress on to more advanced programming. Chapters include variables and arrays, strings and codes, INPUT, PRINT and DATA, sound generator, animation etc.

178x110mm, 116 pages, illustrated.
Order As WM80B (Intro Prog Atari XL) Price £2.10NV

An Introduction to Semiconductor Microtechnology

by D.V. Morgan and K. Board

Containing everything you ever wanted to know about how a transistor is manufactured. The book provides an introduction to the technology of semiconductors and integrated circuits. The emphasis is on principles, but a real-life design sequence is included, in order to give an insight into real technology. The book is aimed at readers who have no specialist knowledge beforehand, and contains a minimum of mathematics. Should appeal to students of electronic engineering, computer science, physics, and materials science. Contents include the development of semiconductor technology, materials used, photolithography, fabrication, future developments and a host of informative appendices.

227x152mm, 167 pages, illustrated.

Order As WM90X (Intro Semi Microtech) Price £9.55NV



An Introduction to Simulation Techniques on the Sinclair QL

by John Cochrane

You too can make your computer think it's a dog, fly a Jumbo Jet in your living room, find out what the Stock Exchange is going to do tomorrow, or anything else that takes your fancy, with the aid of computer simulation. The author is an experienced consultant engineer and an expert in computer simulations. He shows how you can make the most of the considerable potential of the Sinclair QL, working within its limitations as far as simulation is concerned. The book takes the reader logically through the world of computer simulations, building up knowledge of the techniques used by professionals to produce useful programs to create working electronic models which may, for example, be used to solve a practical problem.

235x155mm, 125 pages, illustrated.

Order As WM87U (Intro Sim Sinclair) Price £7.65NV



Microchip Technology

by Charles Kerridge

Basically a history of the silicon microchip, this rather jovial book goes into the design, construction and manufacture of 'chips', touching on such aspects as their chemical structure, and their enormous variety of applications. The author takes us from electricity as a natural phenomenon, to transistors, integrated circuits and their manufacture; and computer peripherals and software. Includes some amusing analogies to illustrate a few basic principles. There is also some speculation on what the silicon chip holds in store for the future!

229x152mm, 176 pages, illustrated.
Order As WM89V (Microchip Technology) Price £9.62NV

Electronics Servicing

by Rhys Lewis

Part of a series covering the Part II Core Studies syllabus in the City and Guilds Institute course 224, it could nevertheless be a useful reference book of basic electronic principles. The book follows a logical teaching order, components and devices being described in themselves prior to the presentation of actual circuits. The topics covered are LCR circuits, transformers, semiconductor diodes, transistors and other devices, voltage amplifiers, waveform generation and shaping, the cathode ray tube and power supplies. A minimum of the essential basic mathematics is included, although physical explanations are used throughout.

234x156mm, 142 pages, illustrated.
Order As WM86T (Elect Servicing) Price £7.65NV



Continued on page 36.

NEW ITEMS PRICE LIST

The following is a list of all items introduced since our 1984 catalogue, excluding new items in this issue.

BOOKS

- WK05F** Mastering Visicalc by Douglas Hergert. Price £10.98NV
WK06G Hart's Dictionary of BASIC by W.A. Hart. Price £7.25NV
WK07H The Spectrum Pocketbook by Trevor Toms. Price £7.95NV
WK08J The Spectrum Games Companion by Bob Maunder. Price £5.95NV
WK09K Mastering CP/M by Alan Miller. Price £13.52NV
WK10L Adventures with Digital Electronics by Tom Duncan. Price £4.25NV
WK11M Assembly Language Programming for the BBC Micro by Ian Birnbaum. Price £9.65NV
WK12N VIC Innovative Computing by Clifford Ramshaw. Price £7.10NV
WK13P Understanding Your Spectrum by Dr Ian Logan. Price £7.95NV
WK14Q Practical Design of Digital Circuits by Ian Kampel. Price £12.20NV
WK15R Programming the BBC Micro by P. Williams. Price £7.55NV
WK16S Programming Languages for Micros by G. Marshall. Price £7.49NV
WK17T Programming Microcomputers with Pascal by M. Beer. Price £7.70NV
WK18U Over the Spectrum. Price £6.95NV
WK19V Introducing Spectrum Machine Code by Ian Sinclair. Price £8.95NV
WK20W Programming with Graphics by G. Marshall. Price £6.75NV
WK21X Machine Intelligent Programs for the 16K ZX81 by Charlton, Harrison & Jones. Price £5.25NV
WK22Y Games ZX Computers Play by Tim Hartnell. Price £3.25NV
WM31J Audio Amplifier Construction by Robert Penfold. Price £2.25NV
WM34M An Introduction to Programming the Dragon 32 by R.A. & J.W. Penfold. Price £1.95NV
WM38R The Atari Book of Games by James, Gee & Ewbank. Price £5.95NV
WM39N Spectrum Adventures by Bridge & Carnell. Price £7.39NV
WM40T Master your ZX Microdrive by Andrew Pennell. Price £8.20NV
WM41U Commodore 64 Adventures by Mike Grace. Price £7.53NV
WM42V The Commodore 64 Games Book by Owen Bishop. Price £6.88NV
WM43W Programming for Education on the BBC Computer by Scotiden & Hall. Price £7.49NV
WM44X Putting Your BBC Micro to Work by Chris Callender. Price £5.30NV
WM46A Advanced Programming Techniques for the BBC Micro by McGregor & Watt. Price £10.20NV
WM47B The Oric 1 Companion by Bob Maunder. Price £7.66NV
WM48C 40 Educational Games for the Spectrum by Vince Apps. Price £6.45NV
WM49D 21 Games for the Electron by James, Gee & Ewbank. Price £6.35NV

- WM50E** The Aquarius and How to Get Most From It by Ian Sinclair. Price £6.20NV
WM51F Software 64 (Commodore) by Owen Bishop. Price £6.30NV
WM52G Spectrum Interfacing & Projects by Graham Bishop. Price £7.63NV
WM53H DIY Robotics and Sensors with the BBC Computer by John Billingsley. Price £7.79NV
WM54J Advanced Sound and Graphics for the Dragon Computer by Keith and Steven Brain. Price £10.96NV
WM55K Writing Strategy Games on the Atari Computer by John White. Price £6.95NV
WM56L Advanced Programming Techniques on the Commodore 64 by David Lawrence. Price £10.63NV
WM57M Graphic Art on the Commodore 64 by Boris Allan. Price £6.85NV
WM59P Linear Electronic Circuits and Systems by Graham Bishop. Price £8.95NV
WM60Q Mastering Electronics by John Watson. Price £4.35NV
WM62S Introducing Dragon Machine Code by Ian Sinclair. Price £8.95NV
WM63T The Electron Programmer by S.M. Gee & M. James. Price £6.95NV
WM64U The Electron Book by J. McGregor & A. Watts. Price £9.98NV
WM65V Assembly Language Programming on the Electron by John Ferguson & Tony Shaw. Price £9.48NV
WM66W Basic & Fortran in Parallel by S.J. Wainwright & A. Grant. Price £2.10NV
WM67X How To Design Electronic Projects by R.A. Penfold. Price £2.40NV
WM68Y An Introduction to Programming the Acorn Electron by R.A. & J.W. Penfold. Price £2.10NV
WM69A An Introduction to Programming the BBC Model B by R.A. & J.W. Penfold. Price £2.15NV
WM70M Secrets of the Commodore 64 by P. Cornes & A. Cross. Price £2.15NV
WM71N The Atari 600XL Program Book by Peter Goode. Price £6.95NV
WM72P Electronically Speaking: Computer Speech Creation by John P. Cater. Price £13.62NV
WM73Q Language of the Dragon by Mike James. Price £8.45NV
WM74R Interfacing Projects for the BBC Micro by Bruce Smith. Price £7.95NV
WM75S Master Memory Map for Commodore 64 by Paul Pavelko & Tim Kelly. Price £14.45NV
WM76H Programming the M68000 by Tim King & Brian Knight. Price £10.15NV
WM77J Working with dBase II by M. de Page. Price £8.95NV
WM78K Memotech Computing by Ian Sinclair. Price £7.95NV
- BOXES**
XR78K PVC Beading Section. Price 25p per metre
- CABLE**
XR73Q IDC Cable 16-way. Price 29p per 30cm
XR74R IDC Cable 20-way. Price 35p per 30cm

- XR75S** IDC Cable 26-way. Price 45p per 30cm
XR76H IDC Cable 34-way. Price 58p per 30cm
XR77J IDC Cable 40-way. Price 68p per 30cm
- CAPACITORS**
FG75S AM/FM Varitone Capacitor. Price £1.72
- COMPUTERS**
YK76H Floppy Disk Album. Price £5.95
YK82D Computer Disk Cleaner Kit. Price £13.95
YK83E Computer Cassette Cleaner Kit. Price £11.20
YK87U Flip 'n' File Minibox 15. Price £6.78
YK88V Flip 'n' File Keyboard 25. Price £22.95
YK89W Tape & Disk Cleaning Fluid. Price £4.99
YK90X Anti-Static Foam Cleaner. Price £3.25
YK91Y Anti-Static Screen Cleaner. Price £3.99
YK92A Anti-Static Spray. Price £4.49
YK93B Safesolve Cleaning Solvent. Price £5.75
YK94C Pressurised Air Duster. Price £4.25
YK95D Anti-Static Polish. Price £3.75
YK96E Flip 'n' File Standardbox 50. Price £16.95
YK97F Flip 'n' File Minibox 10. Price £4.49
YK98G Data Buds 100. Price £2.75
YK99H Data Wipes 150. Price £9.60
- CONNECTORS**
BK79L 0.156 inch 2 x 22 Way P.C. Edgecon. Price £3.50
BK84F 18 Way R.A. Minicon Plug. Price 92p
BK85G 18 Way Latch Minicon Plug. Price 84p
BK86T 18 Way Jumper Cable. Price £4.82
BK96E 34 Way IDC Socket & Cable. Price £3.85
BK97F 2 x 20 Way P.C. Edgecon. Price £1.60
BK98G Budget 3-pin XLR Line Plug. Price £1.54
BK99H Budget 3-pin XLR Line Socket. Price £1.68
FG76H Budget 3-pin XLR Chassis Plug. Price 95p
FG77J Budget 3-pin XLR Chassis Socket. Price £95p
FG78K XLR Type PCB Connector. Price 49p
FJ00A PCB Mono Jack Socket. Price 25p
FJ01B IDC Skt & ¼m Cable 16-way. Price £2.45
FJ02C IDC Skt & ¼m Cable 20-way. Price £2.65
FJ03D IDC Skt & ¼m Cable 26-way. Price £2.98
FJ04E IDC Skt & ¼m Cable 40-way. Price £3.95
FJ05F PCB Stereo Jack Socket. Price 35p
FJ13P IDC PCB Header 16-way. Price £1.40
FJ14Q IDC PCB Header 20-way. Price £1.60
FJ15R IDC PCB Header 26-way. Price £1.80
FJ16S IDC PCB Header 34-way. Price £2.30
FJ17T IDC PCB Header 40-way. Price £2.60
FJ24B BBC Analog Port Cable. Price £5.85

- FJ25C** BBC 1MHz Port Cable. Price £4.99
FJ26D BBC I/O Port Cable. Price £3.30
FJ27E Flush Master Line Jack Unit 3/4A. Price £3.99
FJ28F Jack Plug 420. Price £1.65
FJ29G 5m Line Cord 4/504. Price £3.45
FJ30H Dual Adaptor 10/3A. Price £5.30
FJ31J Line Plug Screw Terminal Adaptor. Price £4.15
FJ32K Line Plug/US Socket Adaptor. Price £4.20
FJ33L Line Plug 4-way 431A. Price 50p
FJ34M Flush Secondary Line Jack 3/6A. Price £2.85
HF99H PCB Phono Socket. Price 28p
- HARDWARE**
BK83E Loudspeaker Clamp Kit. Price £1.79
BK87U Snap Rivet (Pack of 10). Price 20p
FG79L Flexible Nylon Handle. Price 79p
- HEATHKIT**
HC46A Regulated High Voltage Power Supply IP-2717A. Price £239.95
HP03D Microcomputing Course EC-1000. Price £39.95NV
For Passive Circuit Design Course EE-1001:
HS23A Classroom Text EB-6001. Price £18.95NV
HS24B Workbook EB-6001-40. Price £12.95NV
HS25C Instructors Guide EB-6001-50. Price £10.75
HS26D Parts Kit EB-6001-30. Price £15.95
For Transistor Circuit Design Course EE-1002:
HS27E Classroom Text EB-6002. Price £20.95NV
HS28F Workbook EB-6002-40. Price £12.95NV
HS29G Instructors Guide EB-6002-50. Price £10.75NV
HS30H Parts Kit EB-6002-30. Price £25.95
HS58N Robot Applications Course EE-1812. Price £114.95
HS59P Microprocessor Applications Course EE-3405. Price £114.95
HS60Q Battery Life Tester GD-1703. Price £21.95
HS63T HW-9 QRP Transceiver. Price £299.95
HS64U HWA-9 Accessory Band Pk. Price £49.95
HS65V EC-1121 MS-DOS Course. Price £109.95
HS67X Automatic Mode ROM. Price £39.95
For Robot Applications Course EE-1812:
HS69A Classroom Text EB-1812. Price £25.95NV
HS70M Workbook EB-1812-40. Price £15.95NV
HS71N Instructors Guide EB-1812-50. Price £13.95NV
HS72P Parts Kit EB-1812-30. Price £64.95
For Microprocessor Applications Course EE-3405:
HS73Q Classroom Text EB-6405. Price £23.95NV
HS74R Workbook EB-6405-40. Price £14.95NV
HS75S Instructors Guide EB-6405-50. Price £13.95NV
HS76H Parts Kit EB-6405-30. Price £64.95
HS77J Herol Body Only ET-18. Price £899.95

HS78K Herol Arm Only ET-18-1.
Price £399.95
HS79L Herol Voice Only ET-18-2.
Price £119.95
HS80B Hero 1 Assembled ETW-18.
Price £2199.95

PROJECTS & MODULES

FJ35Q Front Panel Noise Reduction Unit Mk. II. Price £2.25
FJ36P Mapmix Front Panel. Price £3.85
GB26D TTL/RS232 Converter P.C.B. Price £1.62
GB27E ZX81 1K Extendi-RAM P.C.B. Price £3.20
GB32K Latchcard P.C.B. Price £2.20
GB33L Spectrum ADC P.C.B. Price £2.80
GB34M Spectrum DAC P.C.B. Price £2.84
GB35Q Digi-Tel Expansion P.C.B. Price £25.95
GB36P Logic Pulser P.C.B. Price £1.32
GB39N Motherboard for BBC P.C.B. Price £5.40
GB40T Frequency Mtr Adaptor PCB Price £1.42
GB41U VIC 20 Extendi-board P.C.B. Price £5.75
GB43W ZX81 Hi-Res Graphics PCB. Price £11.99
GB44X Personal Stereo DNL PCB. Price £1.96
GB45Y Oric Talkback P.C.B. Price £3.62
GB47B Spectrum Keyboard P.C.B. Price £10.72
GB48C Spectrum Kbd Conn PCB Price £1.96
GB50E TDA 7000 Radio P.C.B. Price £1.82
GB51F 2.8kW Power Controller P.C.B. Price £2.38
GB52G Fluorescent Tube Driver P.C.B. Price £1.96

GB54J Auto-Waa P.C.B. Price £1.99
GB55K Oric Maplin Modem Interface P.C.B. Price £3.25
GB56L Dragon Extendiport P.C.B. Price £3.25
GB57M Spectrum Easyload P.C.B. Price £3.62
GB59P 80 Metre Receiver P.C.B. Price £2.75
GB60Q Mapmix P.C.B. Price £5.35
GB61R Xenon Tube Driver P.C.B. Price £2.45
GB64U Enlarger Exposure Meter P.C.B. Price 99p
GB65V Ni-Cad Charger P.C.B. Price £2.55
GB66W 8-Channel Fluid Detector P.C.B. Price £3.10
GB68Y Servodriver P.C.B. Price £1.35
LK16S ZX81 1K Extendi-RAM Kit. Price £8.95
LK17T TTL/RS232 Converter Kit. Price £11.95
LK19V Logic Pulser Kit. Price £5.95
LK20W Frequency Mtr Adaptor Kit. Price £7.95
LK22Y VIC 20 Extendi-board Kit. Price £29.95
LK23A ZX81 High Res Graphics Kit. Price £27.50
LK24B Latchcard Kit. Price £6.95
LK25C Spectrum DAC Kit. Price £17.95
LK26D Spectrum ADC Kit. Price £32.95
LK27E Personal Stereo DNL Kit. Price £8.95
LK28F Oric Talkback Kit. Price £23.95
LK29G Spectrum Keyboard Kit. Price £28.50
LK30H Spectrum Kb Adaptor Kit. Price £6.50
LK32K TDA 7000 Radio Kit. Price £10.95

LK33L Infra-Red Movement Detector Kit. Price £34.95
LK34M 2.8kW Power Controller Kit. Price £18.95
LK35Q Fluorescent Tube Driver Kit. Price £8.45
LK36P Auto-Waa Kit. Price £11.95
LK37S Digi-Tel Expansion Kit. Price £129.95
LK38R Mk II Noise Reduction Kit. Price £39.95
LK39N Spectrum Easyload Kit. Price £9.95
LK40T Oric Maplin Modem Interface Kit. Price £13.95
LK41U 80 Metre Receiver Kit. Price £15.95
LK42V Car Battery Monitor Kit. Price £6.95
LK43W Noise Gate Kit. Price £9.95
LK44X Enlarger Exposure Meter Kit. Price £7.95
LK45Y Servodriver Kit. Price £9.75
LK46A Xenon Tube Driver Kit. Price £11.75
LK47B BBC Motherboard Kit. Price £27.95
LK48C 8-Channel Fluid Detector Kit. Price £12.95
LK49D Mapmix Kit. Price £29.95
LK50E Ni-Cad Charger Kit. Price £19.95
QY58N 2716/M8. Price £8.50
QY60Q 2716/M5. Price £10.50
XG35Q Spectrum Case. Price £4.95
XG36P Spectrum Ready-built Keyboard (including adaptor & case). Price £44.95
XG37S Mk. II Noise Reduction Unit Case. Price £8.95
XG38R Mapmix Case. Price £8.95
YK77J Spectrum Keypop Print. Price 68p

RECORD, TAPE & VIDEO
FJ06G Video Belts VSK9707. Price £6.95

FJ07H Video Belts VSK9806. Price £7.95
FJ08J Video Belts VSK9876. Price £7.95
FJ09K Video Belts VSK9708. Price £6.95
FJ10L Video Belts VSK9794. Price £6.95
FJ11M Video Belts VSK9605. Price £7.95
FJ12N Video Belts VSK9635. Price £7.95
FJ18U Drive Belt Nat/Pan AS8187. Price £2.85
FJ19V Drive Belt Pioneer AS8189. Price £2.45
FJ20W Drive Belt Sony AS8195. Price £2.45
FJ21X Drive Belt Trio AS8201. Price £2.45
FJ22Y Drive Belt Sansui AS8205. Price £2.45
FJ23A Drive Belt Hitachi AS8210. Price £2.45

SEMICONDUCTORS

QQ64U BFY90. Price 95p
QY56L 7581 ADC. Price £26.95
QY59P 74LS260. Price 84p

SOUNDERS & SPEAKERS

YK84F VDU/Speaker Stand. Price £15.95
YK85G 12V DC 6 inch Dome Bell. Price £9.95

TEST GEAR

BK78K Carrying Case MC20. Price £3.32

WOUND COMPONENTS

HX17J Trans Coil 3T Blue. Price £2.20
HX78K Trans Coil 3T Red. Price £2.20
YK86T Toroidal Transformer 24V/24V. Price £13.95

Before you send your next order to us by post, take a look and see if there's a Maplin shop near you. In our shops you'll find that personal service that even the best mail-order operations cannot match. And you can look at the products before you buy. If you're coming for a particular item, a quick phone call will enable you to be certain the shop has everything you want in stock.

Our shops are pleased to accept Access, Barclaycard, American Express and Mapcard, and also cheques up to £50 with a cheque guarantee card. We'll even accept ordinary money as well!

All our shops are close to excellent parking facilities, meters in London and Manchester, and free elsewhere.

The South

In the South our Southampton store is conveniently placed for easy access from all parts of Hampshire and surrounding counties and is just 15 minutes from Portsmouth (from the M27 junction 6, turn left onto the A335).

London

Our London store situated just to the west of the pedestrian shopping centre in Hammersmith, is just 5 minutes from the end of the M4 and only a short walk from the



MAPLIN'S 5 REGIONAL SHOPS

HELP SERVE YOU BETTER!

Birmingham: Lynton Square, Perry Barr. Tel: 021 356 7292.

London: 159-161 King Street, Hammersmith W6. Tel: 01 748 0926.

Manchester: 8 Oxford Road. Tel: 061 236 0281.

Southampton: 46-48 Bevois Valley Road. Tel: 0703 25831.

Southend-on-Sea: 282-284 London Road, Westcliff-on-Sea, Essex.
Tel: Southend-on-Sea (0702) 954000.

District, Piccadilly and Metropolitan lines' Hammersmith station.

The Midlands

In the Midlands our Birmingham store is just 5 minutes from the M6 on the A34, and only a little farther from the M5 (junction 1) on the A4040.

The North

Our self-service store in Manchester serves the North and is just off the Mancunian Way, opposite the BBC, about 5 minutes from the end of the M602 or junction 10 on the M63.

South-East

Essex and Kent are served by our Southend shop which is right on the A13, just 2 minutes before you reach the centre of Southend. And we're only 30 minutes from the M25 (junction 29) as well.

All our shops are open from 9 a.m. to 5.30 p.m. Tuesday to Saturday (closed all day Sunday and Monday) and do not close for lunch.

There's a friendly welcome in store for you at any Maplin shop. Our helpful staff may often be able to help with a technical problem or a constructional difficulty.

Call in at a Maplin store and get what you want today. We look forward to serving you.

1984 CATALOGUE PRICE CHANGES

The price changes shown in this list are valid from 13th August 1984 to 10th November 1984. Prices charged will be those ruling on the day of despatch.

For further details please see 'Prices' on catalogue page 12. The letter in brackets after the price on some items, indicates the minimum trade quantity thus: A = 5; B = 10; C = 25; D = 50; E = 100; F = 250; G = 500; H = 1000. For further details see 'Trade Prices' on catalogue page 13.

Price Changes

All items whose prices have changed since the publication of the 1984 catalogue are shown in the list below. Those where the price has changed since the last Price Change Leaflet (dated 14th May 1984) are marked '*' after the price. A complete Price List is also available free of charge - order XF08J.

Key

- NYA Not yet available.
- DIS Discontinued.
- TEMP Temporarily unobtainable.
- FEB Out of stock; new stock expected in month shown.
- ↑ To be discontinued when stocks are exhausted.
- NV Indicates that item is zero rated for VAT purposes.
- ★ See 'Amendments To Catalogue'. Note that not all items that require amendments are shown in this list.
- \$ Please add £6 carriage if your order contains one or more items marked thus.

1984 Catalogue Page No.	VAT Inclusive Price	1984 Catalogue Page No.	VAT Inclusive Price	1984 Catalogue Page No.	VAT Inclusive Price	1984 Catalogue Page No.	VAT Inclusive Price	1984 Catalogue Page No.	VAT Inclusive Price		
AERIALS											
Page 24											
*X023A	Mushkiller FM1083	£13.96 (A)	*X023C	Mushkiller FM1085	£19.80 (A)	*X027E	Mushkiller FM1087	£23.60 (A)	X029G	Trucolour TC10 Grp A	£11.20 (A)
X030H	Trucolour TC10 Grp B	£10.38 (A)	X031J	Trucolour TC10 Grp C/D	£10.95 (A)	X032K	Trucolour TC13 Grp A	£12.95 (A)	X034M	Trucolour TC13 Grp C/D	£12.50 (A)
X036P	Trucolour TC18 Grp B	£14.95 (A)	X037S	Trucolour TC18 Grp C/D	£14.20 (A)	*X038R	Extragain XG5	£17.95 (A)			
Page 25											
*X039N	Extragain XG8 Group A	£23.95 (A)	*X040T	Extragain XG8 Group B	£23.50 (A)	*X041U	Extragain XG8 Grp C/D	£22.50 (A)	*X042V	Extragain XG8 Wdbnd	£24.95 (A)
*X043W	Extragain XG14 Group A	£39.95 (A)	*X045Y	Extragain XG14 Grp C/D	£12.50 (A)	*X046A	Extragain XG14 Wdbnd	£38.95 (A)	*X050E	Extragain XG21 Wdbnd	£37.95 (A)
XY30H	Topenna	£3.98 (B)									
Page 26											
X057M	Lashing Kit Type 7	£16.95 (A)	X060Q	Mast D	£4.25 (C)	X061R	Mast E	£11.99 (B)	X062S	Mast G	£18.95 (A)
X063T	Mast M	£8.62 (B)	XY30J	Amp XG1U	£16.95 (A)	BK06G	Amp VX18	£19.95 (A)			
Page 27											
BK75S	Xtra Set 3 Amp.	£23.15 (A)	*BW51F	Diplexer UF20	£8.72 (B)	BW52G	Splitter CS1000	£8.25 (B)	YQ23A	Splitter CS200	£5.95 (C)
Page 28											
*LB09K	75-300 Balun	£1.30 (D)	BK470	3dB Attenuator	£1.98 (D)	BW59P	Attenuator 6dB	£1.95 (D)	BK068	Attenuator 12dB	£1.98 (D)
YG20V	Ferrite Rod 810	95p (F)	TYG21X	Ferrite Rod 814	95p (F)	TYG22Y	Ferrite Rod 101	95p (F)	TYG23A	Ferrite Rod 102	£1.95 (E)
Page 29											
LB12N	MW1/LW Aerial	£2.34 (C)	RK48C	8-Section Antenna	£1.36 (D)	RL10L	Telescop Aerial 1.22m	£4.95 (C)			
BATTERIES											
Page 30											
YG02C	Ni Cad C	£3.48 (C)	RK48A	PCB Recharge 3.5V Bat	£7.95 (B)	WY22Y	Ni-Cad Charger	£7.95 (B)			
Page 31											
*HW32K	PP3 NiCad Charger	£7.95 (B)	*X098K	AC Adaptor BR300	£5.95 (C)	WR59P	1.5V Batt Box	45p (F)	YF61R	4.5V Batt Box	45p (F)
YF29G	6V Batt Box	36p (F)	HQ01B	9V Batt Holder	45p (F)	RK45J	12V NiCad Battery Box	79p (F)	YF97F	HPZ Batt Box	95p (E)
Page 32											
HY32K	Large Batt Hldr	£2.22 (D)	XY32A	Dummy Battery	24p (G)						
BOOKS											
Page 33											
WA27E	Basic Elec & DC Ccts	£13.60 NV	WA28F	Basic AC Ccts	£12.25 NV	RL27E	Book NB147	£8.96 NV	XW31J	Book MM639	DIS
Page 34											
WG71N	Book BP94	DIS	WA44X	Undrstndg Auto Elec	£5.79 NV	RL13P	Book NB099	£3.52 NV	RH04E	Book BP6	DIS
Page 35											
RH53H	Book BP160	£1.95 NV	XW53H	Book NB454	£4.90 NV	XW80T	Book JM471	£3.08 NV (C)	RL19V	Book NB126	£5.62 NV
WA20V	Undrstndg Electrnics	£5.74 NV	WM23A	Digital Electronics	£12.99 NV	WA21X	Undrstndg Dig Elec.	£5.72 NV			
Page 36											
RH63T	Book NB041	£3.46 NV	RH13L	Book NB188	£11.30 NV	XW87U	Book AG530	£4.95 NV	WA24B	Undrstndg Communctns	£5.79 NV
RG68Y	Book FT938	£10.58 NV									
Page 37											
RO69A	Book FT986	£9.54 NV	RF11M	Book BP401	DIS	WA19V	TI Linear IC Guide	DIS	WG58N	Book FT1199	£13.46 NV
Page 38											
RO54J	280 Data	£3.95	WG23A	Book JW568	£32.75 NV	RL07H	Book NB076	DIS	RO26D	Book NB319	DIS
WA29G	Book BP89	£2.45 NV	RB25C	Book BP225	£1.69 NV						
Page 39											
RR37S	Photocell Apps Book	DIS	WA08J	TI Dpno Data	£6.55 NV	RR27E	Book NB2026	£4.72 NV	RR04E	Book NB203	£4.67 NV
Page 40											
WG01B	Book NB447	£8.42 NV	WG44X	Book AG600	£5.44 NV	RR09K	Book NB229	£4.94 NV	RQ28F	Book BP48	£1.78 NV
Page 41											
WG57M	Book FT1300	£19.95 NV	WG28F	Book BP83	DIS						
Page 42											
WG35Q	Book HD093	£8.20 NV	WK45Y	Undrstn Phone Electrn	£5.84 NV	WG94C	Book FT1349	£12.95 NV	WG91Y	Book FT1261	£8.95 NV
RH18U	Book BP24	£1.88 NV									
Page 43											
RL01B	Book NB058	DIS	RO66V	Book BP59	£1.95 NV	RR07H	Book NB216	DIS	WA62S	Book NB769	£5.95 NV
RL07H	Book NB269	£6.75 NV									
Page 44											
RF20V	Book HD734	£8.20 NV	RD05W	Book MM700	DIS	XW06J	Book BP60	£1.95 NV	XW46A	Book MM513	DIS
XW47B	Book MM398	£4.53 NV									
Page 45											
WK61R	Electrnics For Techns.	£6.88 NV	HQ00B	Book FT926	DIS	TYG00A	Book FT1021	£6.84 NV	WG61R	Book HD192	£11.20 NV
Page 46											
WG72F	Book FT841	£7.95 NV	XW73Q	Book FT1241	£9.99 NV	WG92A	Book FT1341	£13.36 NV	WG47B	Book FT1191	DIS
WA56P	Book FT1076	£8.20 NV	WA69Q	Book FT1391	£10.95 NV	RR00A	Book NB195	DIS	WA90X	Book NB112	£5.60 NV
WA90X	Book NB112	£5.60 NV	XW54J	Book NB349	£3.64 NV						
Page 47											
XW99H	Book FT1054	DIS	RB22V	Book BP222	£1.98 NV	WG95D	Book FT1305	£10.90 NV	WG93B	Book FT1235	DIS
WG95D	Book FT1305	£10.90 NV	WG93B	Book FT1235	DIS	WG80B	Book FT1185	£7.95 NV			
Page 48											
WA97B	Book NB156	£8.20 NV	WA97B	Book FT1409	£10.27 NV	WG20W	Book AG652	£5.76 NV	WG97F	Book KN035	DIS
WG97F	Book KN035	DIS	WG97M	Book KN400	DIS	XW60E	Book FT933	DIS	WG16S	Book NB016	£5.65 NV
RH57M	Book NB001	DIS									
Page 49											
WG69W	Book NB132	£3.30 NV	WG52V	Book AC569	£5.95 (C)	RO59P	Book NB367	£3.45 NV	XW84F	Book AG353	DIS
XW84F	Book AG353	DIS	RL10L	Book NB084	£5.56 NV	RL14Q	Book NB101	£5.54 NV	RR24D	Book NB970	£6.96 NV
WG95D	Book FT1305	£10.90 NV	WG93B	Book FT1235	DIS	XW29G	Book NB378	DIS	RH62S	Book NB033	DIS
Page 50											
RF17T	Book NB240	£14.88 NV	RL23A	Book NB137	£13.74 NV	WA94C	Book NB577	£5.69 NV	WA95D	Book NB506	£9.96 NV
WA95D	Book NB506	£9.96 NV	WG68A	Book AG602	£5.95 NV	XW85G	Book AG510	DIS			
Page 51											
TRF13P	Book NB2441	£5.70 NV	TRF15R	Book NB252	£13.61 NV	RF16S	Book NB253	£14.56 NV	WK80B	Music and the Micro	£5.84 NV
WK80B	Music and the Micro	£5.84 NV	WG09K	Book JW266	DIS	WG40T	Book HD752	£21.76 NV	TXW50T	Book AG695	£5.15 NV
Page 52											
RR01B	Book NB196	DIS	RQ34M	Book NB369	£5.99 NV						
Page 53											
RO38R	Book NB359	DIS	WA22Y	Undrstndg Micros	DIS	RD01B	Book Sybx C201	£15.45 NV	WA87U	Book NB579	£5.59 NV
RQ13P	Book Sybx M11	£10.69 NV	WG79L	Book NB580	DIS	WK66V	Complete Programmer	£5.85 NV			
Page 54											
WK95H	Micro Facs	NOV84	TKW70M	Chosing A Micro	£5.02 NV	WM08J	Using The New Brain	DIS	WG78K	Book NB496	£7.53 NV
WG78K	Book NB496	£7.53 NV	WG17T	Book HD857	DIS						
Page 55											
WG24B	Book HD165	£16.20 NV	XW15R	Book HD813	£5.38 NV	WA58N	Book FT1200	£10.38 NV	WG10T	Book FT1070	£11.56 NV
RQ02C	Book Sybx C207	£15.45 NV	WA92A	Book NB129	£6.98 NV	WK29G	Simple Interface Bk	£7.94 NV	XW57M	Book HD177	DIS
WG51C	Book FT1330	£8.95 NV									
Page 56											
XW19V	Book HD166	DIS	XW80F	Book C202	£13.59 NV	XW81B	Book C302	£12.56 NV	WA05F	5502 Assembly Subs.	£15.72 NV
WM17T	5502 Machine Code	DIS	WG63T	Book HD183	DIS	XW70M	Book M3	£14.81 NV	RD05W	Book MM700	DIS
WK30H	Programming 5809	£14.20 NV	WA04E	58000 Assembly Prog.	£16.59 NV						
Page 57											
XW69A	Book M2	£14.87 NV	WG66W	Book JW009	£11.72 NV	WG21X	Book HD167	£11.95 NV	XW71N	Book M4	£16.61 NV
WG21X	Book HD167	£11.95 NV	XW71N	Book M4	£16.61 NV	WK030	20 ZX Programs	£9.90 NV	TKW78K	Instant Programme	£5.78 NV
TKW78K	Instant Programme	£5.78 NV	TKW79L	Deeper Spectrum Book	£8.50 NV	WM22Y	Programmes For ZX	£7.23 NV			
Page 58											
TKW50E	Book MM286	£6.66 NV	RL04Z	Book HD585	£14.25 NV	WA89A	Microsoft Basic Book	£13.99 NV	TKW42V	Book HD115	£5.46 NV
TKW42V	Book HD115	£5.46 NV	TKW47A	Instant Basic Book	£11.99 NV	TKW43B	Book NB184	£5.95 NV			
Page 59											
WA72P	Book JW932	£11.35 NV	WA45U	Learn Pascal Frm Bsc	£5.47 NV	WG26D	Book JW180	DIS	WG26K	Book P320	£17.70 NV
WG26K	Book P320	£17.70 NV	TRQ43W	Book HD682	£11.20 NV	WA58Y	Discover FORTH	£13.95 NV	WG29S	Book JW415	DIS
WG29S	Book JW415	DIS	WK97L	Book C300	£13.46 NV	WK98G	Exploring Forth	£6.24 NV			
Page 60											
WK93A	Book Basic Adventure	DIS	TKW69X	Book FT1369	£14.43 NV	TKW69X	Book JW410	£8.21 NV	TKW71N	BASIC For Scientists	£13.54 NV
TKW69X	Book JW410	£8.21 NV	TKW71N	BASIC For Scientists	£13.54 NV	XW60E	Book HD762	£13.26 NV	XW48C	Book FT1095	£5.45 NV
XW48C	Book FT1095	£5.45 NV	WK78H	Giant Games Book	DIS	XW23A	Book HD155	£16.40 NV			
Page 61											
TKW71J	Visicalc Companion	£15.41 NV	WA67X	Word Processing	£12.95 NV	WG41U	Book M46	£15.62 NV	WA65V	Book FT1394	DIS
WA65V	Book FT1394	DIS	WG45F	Book FT1275	£9.23 NV	TKW71Q	Book JW466	£10.50 NV	TKW73Q	Book JW644	£8.98 NV
TKW73Q	Book JW644	£8.98 NV	WG05F	Book JW496	DIS						
Page 62											
WA47B	Games For The Atari	£5.77 NV	WA39N	Book JW593	£10.90 NV	WA40T	Your Atari Computer	£14.93 NV	XH57M	Master Memory Map	DIS
XH57M	Master Memory Map	DIS	WA46A	Op-Sys Users Manual	£20.84 NV	WG56L	De Re Atari	£20.75 NV	WK33L	Atari BASIC 6502	£8.40 NV
WK33L	Atari BASIC 6502	£8.40 NV	WK44X	Atari BASIC Exercise	£13.64 NV	WK85G	More From The Atari	£6.61 NV			
Page 63											
*WK19V	Atari Gms (WMO4E7)	DIS	WA43W	Book JW414	DIS	WK04E	BBC Micro Book	£7.78 NV	WK41U	Burns BBC Compts Ply.	£8.85 NV
WK41U	Burns BBC Compts Ply.	£8.85 NV	WK43W	BBC Creative Graphics	£8.85 NV	WK46A	BBC Machine Code Bk	£5.62 NV	WK65V	BBC Assembly Lang	£9.20 NV
Page 64											
WK71N	21 BBC Micro Games	£6.61 NV	WK85V	Machine Code BBC	£7.42 NV	WK21X	BC Micro Book	£9.50 NV	WK90X	Advncd Prog BBC Elocn	£6.25 NV
WA31J	Learn Prog VIC	£3.20 NV	WA32K	VIC Revealed	£13.20 NV	WA33L	VIC Prog Ref Guide	£13.17 NV	TKW37S	VIC20 for Children	£7.45 NV
TKW37S	VIC20 for Children	£7.45 NV	TKW39H	VIC Acq wth VIC 20	£6.44 NV						
Page 65											
1WA47S	VIC20 Symphony	£8.44 NV	WA48C	VIC Graphics	£7.20 NV	WK72P	More From The VIC 20	£5.85 NV	WK46A	The Working CBM 64	£8.95 NV
WK62S	CBM64 Prgrmmers Ref	£12.40 NV	WM18U	Commodore							

1984 Catalogue Page No.	VAT Inclusive Price	1984 Catalogue Page No.	VAT Inclusive Price	1984 Catalogue Page No.	VAT Inclusive Price	1984 Catalogue Page No.	VAT Inclusive Price	1984 Catalogue Page No.	VAT Inclusive Price		
CAPACITORS				CAR ACCESSORIES				CONNECTORS			
Page 92				Page 100				Page 169			
WX35U Ceramic 1.8 7p (H)		FF40T DG Verh. £8.68 (B)*		FK20W Zaxxon Cass. DIS		FK90X Geography Cass (64) DIS		HF23A Alligator Clip Black 19p (G)		WF57M 1mm Plug Black 24p (G)	
WX36P Ceramic 2.2 7p (H)		FF41U Twin OD £7.86 (B)		FK38R Diaper Normandy Cass. DIS		FK91Y History Cass (64) DIS		WF620 Charger Clip 28p (F)		WF58N 2mm Socket Green 19p (G)	
WX38R Ceramic 3.3 7p (H)		FF46A SW Trim 50pF £9.30 (B)		FK38R Diaper Normandy Cass. DIS		FK92A Home Man Cass + Dak(64) DIS		WF620 Terminal Post Black 45p (F)		WF59K 2mm Socket Yellow 24p (G)	
WX39N Ceramic 3.3 7p (H)				FK38R Diaper Normandy Cass. DIS		FK93B Labyrinth Cass (64) DIS		WF620 Terminal Post Black 45p (F)		WF600 2mm Socket Yellow 24p (G)	
WX40T Ceramic 4.7 7p (H)				FK38R Diaper Normandy Cass. DIS		FK95D Maths 1 Cass (64) DIS		WF620 Terminal Post Blue 45p (F)		WF600 2mm Socket Yellow 24p (G)	
WX42V Ceramic 5.6 7p (H)				FK38R Diaper Normandy Cass. DIS		FK96E Maths 2 Cass (64) DIS		WF620 Terminal Post Green 45p (F)		WF600 2mm Socket Yellow 24p (G)	
WX43W Ceramic 8.2 7p (H)				FK38R Diaper Normandy Cass. DIS		FK97F Maze Mast Cart (64) DIS		WF620 Terminal Post Brown 45p (F)		WF600 2mm Socket Yellow 24p (G)	
WX44X Ceramic 10 7p (H)				FK38R Diaper Normandy Cass. DIS		FK98G Paint Brush Cart(64) DIS		WF620 Terminal Post Green 45p (F)		WF600 2mm Socket Yellow 24p (G)	
WX45Y Ceramic 12 7p (H)				FK38R Diaper Normandy Cass. DIS		FK99A Physics Cass (64) DIS		WF620 Terminal Post Green 45p (F)		WF600 2mm Socket Yellow 24p (G)	
WX46A Ceramic 15 7p (H)				FK38R Diaper Normandy Cass. DIS		FK1000 Rat Race Cass (64) DIS		WF620 Terminal Post Green 45p (F)		WF600 2mm Socket Yellow 24p (G)	
WX47B Ceramic 18 7p (H)				FK38R Diaper Normandy Cass. DIS		FK101B Sea Wolf Cass (64) DIS		WF620 Terminal Post Green 45p (F)		WF600 2mm Socket Yellow 24p (G)	
WX48C Ceramic 22 7p (H)				FK38R Diaper Normandy Cass. DIS		FK102C Simons Bas Cart (64) DIS		WF620 Terminal Post Green 45p (F)		WF600 2mm Socket Yellow 24p (G)	
WX49D Ceramic 27 7p (H)				FK38R Diaper Normandy Cass. DIS		FK103D Snowman Cass (64) DIS		WF620 Terminal Post Green 45p (F)		WF600 2mm Socket Yellow 24p (G)	
WX50E Ceramic 33 7p (H)				FK38R Diaper Normandy Cass. DIS		FK104E Stellar Wars Cass(64) DIS		WF620 Terminal Post Green 45p (F)		WF600 2mm Socket Yellow 24p (G)	
WX51F Ceramic 39 7p (H)				FK38R Diaper Normandy Cass. DIS		FK105F SuperBlitz Cass (64) DIS		WF620 Terminal Post Green 45p (F)		WF600 2mm Socket Yellow 24p (G)	
WX52G Ceramic 47 7p (H)				FK38R Diaper Normandy Cass. DIS		FK106G Super Fruit Cass. DIS		WF620 Terminal Post Green 45p (F)		WF600 2mm Socket Yellow 24p (G)	
WX57M Ceramic 120 9p (H)				FK38R Diaper Normandy Cass. DIS		FK107H Swordpoint Disk (64) DIS		WF620 Terminal Post Green 45p (F)		WF600 2mm Socket Yellow 24p (G)	
WX58N Ceramic 150 9p (H)				FK38R Diaper Normandy Cass. DIS		FK108J Synthesound Cart (64) DIS		WF620 Terminal Post Green 45p (F)		WF600 2mm Socket Yellow 24p (G)	
WX61R Ceramic 270 9p (H)				FK38R Diaper Normandy Cass. DIS		FK109K Turtle Train Cart 64. DIS		WF620 Terminal Post Green 45p (F)		WF600 2mm Socket Yellow 24p (G)	
WX62S Ceramic 330 9p (H)				FK38R Diaper Normandy Cass. DIS		FK110L Turtle Tutor Cart 64. DIS		WF620 Terminal Post Green 45p (F)		WF600 2mm Socket Yellow 24p (G)	
WX63P Ceramic 390 9p (H)				FK38R Diaper Normandy Cass. DIS				WF620 Terminal Post Green 45p (F)		WF600 2mm Socket Yellow 24p (G)	
WX64U Ceramic 470 9p (H)				FK38R Diaper Normandy Cass. DIS				WF620 Terminal Post Green 45p (F)		WF600 2mm Socket Yellow 24p (G)	
WX65V Ceramic 560 9p (H)				FK38R Diaper Normandy Cass. DIS				WF620 Terminal Post Green 45p (F)		WF600 2mm Socket Yellow 24p (G)	
WX66W Ceramic 680 9p (H)				FK38R Diaper Normandy Cass. DIS				WF620 Terminal Post Green 45p (F)		WF600 2mm Socket Yellow 24p (G)	
WX67X Ceramic 820 9p (H)				FK38R Diaper Normandy Cass. DIS				WF620 Terminal Post Green 45p (F)		WF600 2mm Socket Yellow 24p (G)	
WX68T Ceramic 1000 9p (H)				FK38R Diaper Normandy Cass. DIS				WF620 Terminal Post Green 45p (F)		WF600 2mm Socket Yellow 24p (G)	
WX69A Ceramic 1200 9p (H)				FK38R Diaper Normandy Cass. DIS				WF620 Terminal Post Green 45p (F)		WF600 2mm Socket Yellow 24p (G)	
WX70M Ceramic 1500 6p (H)				FK38R Diaper Normandy Cass. DIS				WF620 Terminal Post Green 45p (F)		WF600 2mm Socket Yellow 24p (G)	
WX71N Ceramic 1800 6p (H)				FK38R Diaper Normandy Cass. DIS				WF620 Terminal Post Green 45p (F)		WF600 2mm Socket Yellow 24p (G)	
WX72P Ceramic 2200 6p (H)				FK38R Diaper Normandy Cass. DIS				WF620 Terminal Post Green 45p (F)		WF600 2mm Socket Yellow 24p (G)	
WX73D Ceramic 2700 6p (H)				FK38R Diaper Normandy Cass. DIS				WF620 Terminal Post Green 45p (F)		WF600 2mm Socket Yellow 24p (G)	
WX74R Ceramic 3300 4p (H)				FK38R Diaper Normandy Cass. DIS				WF620 Terminal Post Green 45p (F)		WF600 2mm Socket Yellow 24p (G)	
WX75S Ceramic 3900 7p (H)				FK38R Diaper Normandy Cass. DIS				WF620 Terminal Post Green 45p (F)		WF600 2mm Socket Yellow 24p (G)	
WX77J Ceramic 10,000 8p (H)				FK38R Diaper Normandy Cass. DIS				WF620 Terminal Post Green 45p (F)		WF600 2mm Socket Yellow 24p (G)	
WX78K Ceramic 22,000 9p (H)				FK38R Diaper Normandy Cass. DIS				WF620 Terminal Post Green 45p (F)		WF600 2mm Socket Yellow 24p (G)	
Y24B Monocap 0.001uF 32p (F)				FK38R Diaper Normandy Cass. DIS				WF620 Terminal Post Green 45p (F)		WF600 2mm Socket Yellow 24p (G)	
Y25C Monocap 0.0022uF 32p (F)				FK38R Diaper Normandy Cass. DIS				WF620 Terminal Post Green 45p (F)		WF600 2mm Socket Yellow 24p (G)	
Y27H Monocap 0.0047uF 32p (F)				FK38R Diaper Normandy Cass. DIS				WF620 Terminal Post Green 45p (F)		WF600 2mm Socket Yellow 24p (G)	
Y28J Monocap 0.01uF 32p (F)				FK38R Diaper Normandy Cass. DIS				WF620 Terminal Post Green 45p (F)		WF600 2mm Socket Yellow 24p (G)	
Y29K Monocap 0.022uF 38p (F)				FK38R Diaper Normandy Cass. DIS				WF620 Terminal Post Green 45p (F)		WF600 2mm Socket Yellow 24p (G)	
Y30L Monocap 0.047uF 59p (F)				FK38R Diaper Normandy Cass. DIS				WF620 Terminal Post Green 45p (F)		WF600 2mm Socket Yellow 24p (G)	
Y31M Monocap 0.1uF 53p (F)				FK38R Diaper Normandy Cass. DIS				WF620 Terminal Post Green 45p (F)		WF600 2mm Socket Yellow 24p (G)	
Page 93				Page 102				Page 152			
HY18U 1000V Disc 4700pF 55p (G)				FK38R Diaper Normandy Cass. DIS		FK117T Ant Ester Cart. DIS		WH45Y Word Proc Cass (SP) DIS		WH45Y Word Proc Cass (SP) DIS	
WX02C Mica 5pF 24p (G)				FK38R Diaper Normandy Cass. DIS		FK118U Atari Writer Cart. DIS		WH45Y Word Proc Cass (SP) DIS		WH45Y Word Proc Cass (SP) DIS	
WX03D Mica 10pF 24p (G)				FK38R Diaper Normandy Cass. DIS		FK119V Financial Manager. DIS		WH45Y Word Proc Cass (SP) DIS		WH45Y Word Proc Cass (SP) DIS	
WX05F Mica 22pF 24p (G)				FK38R Diaper Normandy Cass. DIS				WH45Y Word Proc Cass (SP) DIS		WH45Y Word Proc Cass (SP) DIS	
WX07H Mica 33pF 24p (G)				FK38R Diaper Normandy Cass. DIS				WH45Y Word Proc Cass (SP) DIS		WH45Y Word Proc Cass (SP) DIS	
WX09K Mica 47pF 26p (G)				FK38R Diaper Normandy Cass. DIS				WH45Y Word Proc Cass (SP) DIS		WH45Y Word Proc Cass (SP) DIS	
WX11M Mica 68pF 26p (G)				FK38R Diaper Normandy Cass. DIS				WH45Y Word Proc Cass (SP) DIS		WH45Y Word Proc Cass (SP) DIS	
WX13P Mica 100pF 26p (G)				FK38R Diaper Normandy Cass. DIS				WH45Y Word Proc Cass (SP) DIS		WH45Y Word Proc Cass (SP) DIS	
WX14D Mica 120pF 26p (G)				FK38R Diaper Normandy Cass. DIS				WH45Y Word Proc Cass (SP) DIS		WH45Y Word Proc Cass (SP) DIS	
WX15R Mica 150pF 26p (G)				FK38R Diaper Normandy Cass. DIS				WH45Y Word Proc Cass (SP) DIS		WH45Y Word Proc Cass (SP) DIS	
WX16S Mica 180pF 26p (G)				FK38R Diaper Normandy Cass. DIS				WH45Y Word Proc Cass (SP) DIS		WH45Y Word Proc Cass (SP) DIS	
WX17T Mica 220pF 26p (F)				FK38R Diaper Normandy Cass. DIS				WH45Y Word Proc Cass (SP) DIS		WH45Y Word Proc Cass (SP) DIS	
WX19V Mica 330pF 32p (F)				FK38R Diaper Normandy Cass. DIS				WH45Y Word Proc Cass (SP) DIS		WH45Y Word Proc Cass (SP) DIS	
WX21X Mica 470pF 45p (F)				FK38R Diaper Normandy Cass. DIS				WH45Y Word Proc Cass (SP) DIS		WH45Y Word Proc Cass (SP) DIS	
WX22A Mica 560pF 45p (F)				FK38R Diaper Normandy Cass. DIS				WH45Y Word Proc Cass (SP) DIS		WH45Y Word Proc Cass (SP) DIS	
WX25C Mica 1000pF 49p (F)				FK38R Diaper Normandy Cass. DIS				WH45Y Word Proc Cass (SP) DIS		WH45Y Word Proc Cass (SP) DIS	
WX31J Mica 4700pF £1.20 (D)				FK38R Diaper Normandy Cass. DIS				WH45Y Word Proc Cass (SP) DIS		WH45Y Word Proc Cass (SP) DIS	
Page 94				Page 103				Page 153			
BX25C Polystyrene 33 15p (H)				FK38R Diaper Normandy Cass. DIS		FK120V Atari Writer Cart. DIS		WH45Y Word Proc Cass (SP) DIS		WH45Y Word Proc Cass (SP) DIS	
BX57M 1% Poly 1200 22p (F)				FK38R Diaper Normandy Cass. DIS		FK121V Atari Writer Cart. DIS		WH45Y Word Proc Cass (SP) DIS		WH45Y Word Proc Cass (SP) DIS	
BX58G 1% Poly 5200 39p (F)				FK38R Diaper Normandy Cass. DIS		FK122V Atari Writer Cart. DIS		WH45Y Word Proc Cass (SP) DIS		WH45Y Word Proc Cass (SP) DIS	
Page 95				Page 104				Page 154			
WW36P Carbonate 0.039 15p (G)				FK38R Diaper Normandy Cass. DIS		FK123V Atari Writer Cart. DIS		WH45Y Word Proc Cass (SP) DIS		WH45Y Word Proc Cass (SP) DIS	
WW38R Carbonate 0.056 DIS (G)				FK38R Diaper Normandy Cass. DIS		FK124V Atari Writer Cart. DIS		WH45Y Word Proc Cass (SP) DIS		WH45Y Word Proc Cass (SP) DIS	
WW48C Carbonate 0.33 27p (G)				FK38R Diaper Normandy Cass. DIS		FK125V Atari Writer Cart. DIS		WH45Y Word Proc Cass (SP) DIS		WH45Y Word Proc Cass (SP) DIS	
WX02F Carbonate 0.12 9p (F)				FK38R Diaper Normandy Cass. DIS		FK126V Atari Writer Cart. DIS		WH45Y Word Proc Cass (SP) DIS		WH45Y Word Proc Cass (SP) DIS	
BX70M Polyester 0.01uF 9p (H)				FK38R Diaper Normandy Cass. DIS		FK127V Atari Writer Cart. DIS		WH45Y Word Proc Cass (SP) DIS		WH45Y Word Proc Cass (SP) DIS	
BX71N Polyester 0.015uF 9p (H)				FK38R Diaper Normandy Cass. DIS		FK128V Atari Writer Cart. DIS		WH45Y Word Proc Cass (SP) DIS		WH45Y Word Proc Cass (SP) DIS	
BX72P Polyester 0.022uF 10p (H)				FK38R Diaper Normandy Cass. DIS		FK129V Atari Writer Cart. DIS		WH45Y Word Proc Cass (SP) DIS		WH45Y Word Proc Cass (SP) DIS	
BX75H Polyester 0.1uF 10p (H)				FK38R Diaper Normandy Cass. DIS		FK130V Atari Writer Cart. DIS		WH45Y Word Proc Cass (SP) DIS		WH45Y Word Proc Cass (SP) DIS	
BX77J Polyester 0.15uF 14p (G)				FK38R Diaper Normandy Cass. DIS		FK131V Atari Writer Cart. DIS		WH45Y Word Proc Cass (SP) DIS		WH45Y Word Proc Cass (SP) DIS	
BX78K Polyester 0.22uF 14p (G)				FK38R Diaper Normandy Cass. DIS		FK132V Atari Writer Cart. DIS		WH45Y Word Proc Cass (SP) DIS		WH45Y Word Proc Cass (SP) DIS	
BX80B Polyester 0.47uF 22p (G)				FK38R Diaper Normandy Cass. DIS		FK133V Atari Writer Cart. DIS		WH45Y Word Proc Cass (SP) DIS		WH45Y Word Proc Cass (SP) DIS	
BX81C Polyester 0.58uF 25p (F)				FK38R Diaper Normandy Cass. DIS		FK134V Atari Writer Cart. DIS		WH45Y Word Proc Cass (SP) DIS		WH45Y Word Proc Cass (SP) DIS	
BX82D Polyester 1uF 32p (F)				FK38R Diaper Normandy Cass. DIS		FK135V Atari Writer Cart. DIS		WH45Y Word Proc Cass (SP) DIS		WH45Y Word Proc Cass (SP) DIS	
BX84F Polyester 2.2uF 42p (F)				FK38R Diaper Normandy Cass. DIS		FK136V Atari Writer Cart. DIS		WH45Y Word Proc Cass (SP) DIS		WH45Y Word Proc Cass (SP) DIS	
Page 96				Page 105				Page 155			
FF53H IS Cap 0.01uF 7p (F)				FK38R Diaper Normandy Cass. DIS		FK137V Atari Writer Cart. DIS		WH45Y Word Proc Cass (SP) DIS		WH45Y Word Proc Cass (SP) DIS	
FF55K IS Cap 0.047uF 36p (F)				FK38R Diaper Normandy Cass. DIS		FK138V Atari Writer Cart. DIS		WH45Y Word Proc Cass (SP) DIS		WH45Y Word Proc Cass (SP) DIS	
FF57M IS Cap 0.22uF 58p (F)				FK38R Diaper Normandy Cass. DIS		FK139V Atari Writer Cart. DIS		WH45Y Word Proc Cass (SP) DIS		WH45Y Word Proc Cass (SP) DIS	
WW73Q Tam 22uF 25V 95p (E)				FK38R Diaper Normandy Cass. DIS		FK140V Atari Writer Cart. DIS		WH45Y Word Proc Cass (SP) DIS		WH45Y Word Proc Cass (SP) DIS	
Page 97				Page 106				Page 156			
FF60D PC Elect 2200uF 16V 33p (F)				FK38R Diaper Normandy Cass. DIS		FK141V Atari Writer Cart. DIS		WH45Y Word Proc Cass (SP) DIS		WH45Y Word Proc Cass (SP) DIS	
FB14U Axial 1.5uF 63V 9p (G)				FK38R Diaper Normandy Cass. DIS		FK142V Atari Writer Cart. DIS		WH45Y Word Proc Cass (SP) DIS		WH45Y Word Proc Cass (SP) DIS	
FB19V Axial 4.7uF 650V 30p (F)				FK38R Diaper Normandy Cass. DIS		FK143V Atari Writer Cart. DIS		WH45Y Word Proc Cass (SP) DIS		WH45Y Word Proc Cass (SP) DIS	
FB22A Axial 10uF 450V 12p (G)				FK38R Diaper Normandy Cass. DIS		FK144V Atari Writer Cart. DIS		WH45Y Word Proc Cass (SP) DIS		WH45Y Word Proc Cass (SP) DIS	
FB24B Axial 10uF 100V 12p (G)				FK38R Diaper Normandy Cass. DIS		FK145V Atari Writer Cart. DIS		WH45Y Word Proc Cass (SP) DIS		WH45Y Word Proc Cass (SP) DIS	
FB25C Axial 10uF 450V 15p (F)				FK38R Diaper Normandy Cass. DIS		FK146V Atari Writer Cart. DIS		WH45Y Word Proc Cass (SP) DIS		WH45Y Word Proc Cass (SP) DIS	
Page 98				Page 107				Page 157			
FB26D Axial 15uF 16V 12p (H)				FK38R Diaper Normandy Cass. DIS		FK147V Atari Writer Cart. DIS		WH45Y Word Proc Cass (SP) DIS		WH45Y Word Proc Cass (SP) DIS	
FB27E Axial 15uF 40V 10p (G)				FK38R Diaper Normandy Cass. DIS		FK148V Atari Writer Cart. DIS		WH45Y Word Proc Cass (SP) DIS		WH45Y Word Proc Cass (SP) DIS	
FB28F Axial 15uF 63V 11p (G)				FK38R Diaper Normandy Cass. DIS		FK149V Atari Writer Cart. DIS		WH45Y Word Proc Cass (SP) DIS		WH45Y Word Proc Cass (SP) DIS	
FB30H Axial 22uF 25V 10p (G)											

1984 Catalogue Page No.	Inclusive Price	1984 Catalogue Page No.	Inclusive Price
RK69A Minch Lich Hng 17way	29p (F)	LR63T Isotag M4	33p (G)
YW28F Mincon Skt 6-way	39p (E)	LR64T Isotag M3	33p (G)
YW30H Mincon Skt 12-way	69p (E)	LR65V Isotag M2.5	17p (G)
YW96E IDC Con 4-way	35p (F)	BF72P Nyl 4BA 1/2in	57p (F)
YW98G IDC Con 8-way	79p (E)	BF74R Nyl 4BA 1/2in	57p (F)
YW99H IDC Con 12-way	120p (E)	BF77J Nyl 8BA 1/2in	119p (E)
YK49D IDC Insertion Tool	£2.95 (C)	BF81C Nyl Nut 8BA	85p (E)
FG44X 2x8 dill IDC socket	£1.75 (D)	WH19V Nylon Nut M3	33p (H)

1984 Catalogue Page No.	Inclusive Price
FG84F 2x10 dill IDC Socket	£1.49 (D)
FG85G 2x13 dill IDC Socket	£1.62 (D)
FG85T 2x17 dill IDC Socket	£2.96 (E)
FG87U 2x20 dill IDC Socket	£3.45 (C)

1984 Catalogue Page No.	Inclusive Price
HL06G Watercon Plug 6-pin	22p (G)
HL07H Watercon Plug 8-pin	22p (G)
HL08J Watercon Plug 12-pin	34p (F)
HL13P Watercon Skt 12-way	32p (F)
RK38R 8-Way PC Terminal	65p (E)
YY22V CB Pin Blue	44p (F)
YY22Z CT Pin White	£1.62 (D)
YB08J Large Patchboard	£174.95 (A)
WL10L Large Patch Plug	38p (F)

1984 Catalogue Page No.	Inclusive Price
HH38R Universal Plug	95p (E)
HH60Q Std Power Plug 2.1	16p (G)
HH63T Low Power Plug 2.5	18p (G)

1984 Catalogue Page No.	Inclusive Price
RW64U Car Lead Sharp	D1S (E)
RW65V Car Lead Sonly	D1S (E)
HL43W Euro Facility Plug	£1.15 (E)
WY16S Euroboard 6-way	£3.95 (E)
WY17T Euroboard 8-way	£5.95 (E)
HL23A Mains Socket P430SE	£1.52 (D)

1984 Catalogue Page No.	Inclusive Price
ML27E Mains Plug SA2190	£1.15 (F)
HL30H Mains Plug SA2019A	£1.64 (D)
HL34M Mains Socket SA2368	98p (E)
HL36P Mains Plug P635	£1.36 (D)

1984 Catalogue Page No.	Inclusive Price
HL39N Mains Plug P551	£3.40 (C)
HL40T Mains Socket P552	£1.20 (E)
HL50E Steeve 8037	14p (G)
FG29F Line Jack Unit	£9.95 (E)
FG29G PTC Line Cord	£1.95 (E)
RK71N Video Copy Kit	£3.95 (A)
RK84F Video Lead 1	£2.65 (C)

1984 Catalogue Page No.	Inclusive Price
FG18U Computer Lead 1	£2.22 (D)
FG20H Printer Cable 1	£3.10 (D)
RK87U Video Lead 5	£2.32 (C)
FG13J Printer Cable 2	£8.45 (D)

1984 Catalogue Page No.	Inclusive Price
RW01B Adaptor B	45p (F)
RW03R Adaptor W	D1S (E)
RW07H Adaptor H	D1S (E)
RW03D Adaptor D	D1S (E)
RW08J Adaptor J	39p (F)
YW35D Adaptor T	95p (D)
RW05F Adaptor F	45p (F)
RW09K Adaptor K	D1S (E)
RK55K Adaptor Y	45p (F)
RW26D Dinpak N	D1S (D)
RW15R Dinpak B	D1S (D)

1984 Catalogue Page No.	Inclusive Price
RW22A Dinpak J	95p (E)
RW23A Dinpak K	95p (E)
RW18U Dinpak E	86p (E)
RW17T Dinpak D	£1.86 (D)
RK20W Dinpak G	£1.86 (D)
RW49D Dinpak 280	D1S (D)
RK58N Plugpak Y	£1.84 (D)

1984 Catalogue Page No.	Inclusive Price
HL83E Switched Flex Outlet	£4.75 (C)
HL86T Blanking Plate	92p (E)
HL87U 20A Plug Switch	£2 (C)
HL88V 20A Water Htr Switch	£5.26 (E)
HL89W Light Swch 2 Single	£1.38 (D)
HL91Y Light Swch Dual	£2.94 (C)
FL15R Security Dimmer	D1S (A)
FQ16S Auto Security Switch	£1.98 (A)
YB09K FI Patress 16mm Sgl	98p (E)
YB10L FI Patress 25mm Sgl	79p (E)

1984 Catalogue Page No.	Inclusive Price
YB14Q Sur Part 20mm Sngl	84p (E)
YB16S Sur Part 20mm Dble	£1.84 (D)
YB17T Sur Part 47mm Dble	£2.98 (C)
YB18U Conversion Patress	£2.82 (C)
FQ00A Ceiling Switch 1-way	£2.94 (C)
FQ02C Lampholder 702	92p (E)
FQ05F Ceiling Rose	£1.39 (D)
YB19V Time Switch	£18.95 (A)

1984 Catalogue Page No.	Inclusive Price
WY23A Timetouch	£34.95 (A)
YB20W Room Thermostat	£12.15 (B)
YX08J Extn Lead 5A	£15.25 (A)

1984 Catalogue Page No.	Inclusive Price
BF00A Bolt 2BA 1/2in	62p (F)
BF05F Bolt 6BA 1/4in Sgl	18p (G)
BF06G Bolt 8BA 1/2in	21p (G)
BF08J Bolt 8BA 1/4in	55p (F)
BF09K Bolt 8BA 1/2in	59p (F)
LR56L C/S Screw 6BA 1/4in	18p (H)
LR00A C/S Screw 8BA 1/2in	39p (F)
BF14D Panel Screw	5p (H)
LR75S C/S Panel Screw	8p (H)
BF16S Nut 2BA	22p (G)
BF31J Pozi Screw M5 12mm	29p (F)
BF35H Pozi Screw M3 40mm	65p (F)
BF39N Pozi Screw M2.5 6mm	26p (G)
BF40T Pozi Screw M2.5 12mm	21p (G)

1984 Catalogue Page No.	Inclusive Price
BF46A Isobolt M5 12mm	72p (E)
BF48B Isobolt M6 6mm	38p (F)
BF49D Isobolt M4 12mm	38p (F)
BF53H Isobolt M3 25mm	42p (F)
BF55K Isobolt M2.5 12mm	28p (F)
BF61R Isowasher M4	12p (H)

1984 Catalogue Page No.	Inclusive Price
FW13P Sudding 2BA	35p (F)
FW30H 4BA Spacer 1/8in	68p (F)
FW31J 4BA Spacer 1/4in	68p (F)
FW32K 4BA Spacer 1/2in	68p (F)
FW33L 6BA Spacer 1/8in	42p (F)
FW34M 6BA Spacer 1/4in	45p (F)
LR70M 8BA Spacer 1/4in	42p (F)
FR37S M4 Spacer 1/2	86p (E)
LR72P Threded Spcr 6BA	86p (E)
FW18U Standoff Long	3p (H)

1984 Catalogue Page No.	Inclusive Price
LI12N Sealing Strip	94p (E)
LI13P Aly Sheet 16 swg	£4.42 (C)
XG31J PCB Guides	29p (F)

1984 Catalogue Page No.	Inclusive Price
PK81R HW-5400 Syn HF Xcvr	£549.95
PK62S HVA-5400-1 PSU/Ck	£229.95
MK62T HVA-5400-3 Keypad	£69.95
HK65W HVA-5400-2 Filter	£149.95
HK73Q HW-1418 Active Filt	£189.95

1984 Catalogue Page No.	Inclusive Price
NK43W HW-8 QRP Xcvr	D1S
TK44X HVA-7-1 Power Supply	£39.95
HK24B HW-31A Centenna Load	£24.95
HK25C HW-1224 Antenna Sw	£25.95
HK74R HW-9 HF/VHF Watmate	£59.95
HK75S HFT-9 SWF Tuner	£64.95

1984 Catalogue Page No.	Inclusive Price
HK22Y HD-1416 Morse Cd Osc	£34.95
HK77H HM-2140A Dtd Watmt	£109.95
HK77V PS-2450 Power Unit	£22.95
HK23A HD-1250 Dip Meter	£94.95

1984 Catalogue Page No.	Inclusive Price
HK78K HD-8999 Pro CW Keybd	£229.95
HK41U SA-5010 U/Matic Keyer	£103.95
HK01B GC-1107 Dig Alarm Cl	£22.95
HK02G CO-2600 Igm Analyser	£89.95

1984 Catalogue Page No.	Inclusive Price
HK29J CI-1080 Exhat Anlysr	£139.95
HK29G CI-2065 Charging Trns	£29.95
HK01B GC-1107 Dig Alarm Cl	£22.95
HK40T GC-1720 Wall Clock	£59.95

1984 Catalogue Page No.	Inclusive Price
HK39N IM-248AE Firact Lmp	D1S
HK08B NE-2112 Heat Smfltr	£34.95
HK07H GC-1091 Heat Smfltr	£84.95
HK71N GC-1701 Flood Alarm	£34.95

1984 Catalogue Page No.	Inclusive Price
HK33L EI-3133 Soldering Crs	£25.95
HK42V EI-3106 Etc Crs	£18.95
HK04E EI-3140 Hobby Etc Crs	£79.95
HK32K EI-3100 Basic Etc Crs	£34.95
HK05F EI-3101A Dc Etc Crs	£64.95

1984 Catalogue Page No.	Inclusive Price
HK06G EI-3102A AC Etc Crs	£69.95
HK07H EI-3103A Semi Dv Crs	£89.95
HK08J EI-3104A Etc Crs	£79.95

1984 Catalogue Page No.	Inclusive Price
HK09K EI-3105A Tat Eqp Crs	£79.95
HK42V EI-3106 Etc Crs	£18.95
HK10L ET-3100B Eng Trainer	£104.95
HK11M ETW-3100B Assembled	£189.95

1984 Catalogue Page No.	Inclusive Price
HK81C EI-1001 Passive Crs	£64.95
HK82D EI-1002 Tran Crs	£74.95
HK83E ET-1000 Eng Trainer	£229.95
HK84F ETW-1000 Assembled	£429.95

1984 Catalogue Page No.	Inclusive Price
HK85G EH-701 Linear Course	£59.95
HK49D EH-702 TTL/CMOS Crs	£74.95
HK92A EH-4201 Fibre Op Crs	£109.95
HK12N EH-3201 Dig Tech Crs	£109.95
HK64U EH-3202 CMOS Tech Crs	£99.95

1984 Catalogue Page No.	Inclusive Price
HK13P ET-3200B Dig Trainer	£109.95
HK14Q ETW-3200B Assembled	£219.95
HK15R ETW-3200B Course	£119.95

1984 Catalogue Page No.	Inclusive Price
HM34M EB-6104 Eic Clr Text	£20.95
HM35D EB-6104-40 Eic Wbkk	£12.95
HM36P EB-6104-50 Eic Part	£10.75
HM37S EB-6104-30 Eic Part	£7.95
HM40T EB-6105 Test Eq Text	£20.95
HM41U EB-6105-40 Test Wbkk	£12.95
HM42V EB-6105-50 Test Inst	£10.75
HM43W EB-6105-30 Test Part	£7.95
HM48A EB-6106 Commn Text	£18.95

1984 Catalogue Page No.	Inclusive Price
HM47B EB-6106-40 Comm Wbkk	£11.95
HM48C EB-6106-50 Comm Inst	£9.95
HM49D EB-6106-30 Comm Part	£7.95
HM52G EB-6201 Digital Text	£24.95
HM53H EB-6201-40 Digi Wbkk	£13.95
HM54J EB-6201-50 Digi Inst	£10.75
HM55K EB-6201-30 Digi Part	£7.95
HM56M EB-6401 Micro Text	£24.95
HM57M EB-6401-40 Micro Wbkk	£12.95
HM58N EB-6401-50 Micro Inst	£10.75

1984 Catalogue Page No.	Inclusive Price
HM59P EB-6401-30 Micro Part	£9.95
HM61R EB-6402 Infract Text	£24.95
HM62S EB-6402-40 Inf Wbkk	£11.95
HM63T EB-6402-50 Inf Part	£10.75
HM64U EB-6402-30 Inf Part	£8.95
HM66W EB-6404 Adv MP Text	£23.95
HM68Y EB-6404-50 Adv Inst	£10.75
HM69Z EB-6404-40 Adv Part	£7.95
HM67X EB-8088 16-Bit Text	£75.95
HM77J EB-8088-40 16-Bit Wbkk	£13.95
HM78K EB-8088-50 16-Bit Ins	£10.95
HM79L EB-8088-30 16-Bit Pt	£84.95

1984 Catalogue Page No.	Inclusive Price
HM82D EB-1801-40 Robot Wbkk	£18.95
HM83E EB-1801-50 Robot Inst	£10.95
HM84F EB-1801-30 Robot Pt	£59.95
HM71N EB-6100 BASIC Text	£20.95
HM72P EB-6100-40 BASIC Wbkk	£12.95
HM73Q EB-6100-50 BASIC Inst	£10.75
HM74R EB-6108 Ass Lan Text	D1S
HM75S EB-6108-40 Lnguage Wbkk	D1S
HM76H EB-6108-50 Ass Inst	D1S

1984 Catalogue Page No.	Inclusive Price
HK96E 2-207-3 Disk Drive	£594.95
HK98D 2-18 Colour RAM	£159.95
HM00A 2-205 256K RAM	£899.95

1984 Catalogue Page No.	Inclusive Price
HM01B HS-207-41 One Drive	£1249.95
HM02C HS-207-42 Two Drive	£1799.95
HM03D HS-207-6 Adv On Disk	£799.95
HM04E HS-217 Winchester Dr	£219.95
HM87U HSS-100-1 Soft Pack	£369.95

1984 Catalogue Page No.	Inclusive Price
IG-5218 Audio Genrr	£159.95
IG-3117 Resisic Box	£89.95
HK50E IM-5288 Distrn Anly	£299.95
HK26D IM-5288 RF Oscilltr	£59.95

1984 Catalogue Page No.	Inclusive Price
IT-2251 RCL Bridge	£59.95
IT-2250 Capacitc Mtr	£179.95
IMA-100-10 Dc Probe	£19.95
IM-2410 Freq Counter	£149.95

1984 Catalogue Page No.	Inclusive Price
IM-2400 Hand-Freq Cl	£159.95
PS2405 Hand-Freq PSU	£17.95
SMA-2400-1 Antenna	£14.95
IP-2718 Trn-Opt PSU	£129.95

1984 Catalogue Page No.	Inclusive Price
IG-4244 Osc Calibrtr	£169.95
IP-2728 Low-Volt PSU	£54.95

1984 Catalogue Page No.	Inclusive Price
ID-4001 Weather Cndr	£449.95
ID-1500E Wind Spd In	D1S
ID-1500E Wind Dir	£129.95
ID-2090C Digi-Barom	£159.95

1984 Catalogue Page No.	Inclusive Price
KN28F Knob BK12	22p (G)
RX28H Knob RN82	34p (F)
HB24B Knob K2	45p (F)
RW88W Knob M1	35p (F)

1984 Catalogue Page No.	VAT Inclusive Price
-------------------------	---------------------

Page 292	
GA30W Command PCB	£3.35 (C)
GA43W Noise Gate PCB	£1.42 (D)
GB13P Tbl Scrch Fltr PCB	£2.32 (C)

Page 293	
XY280 Heatsink Mtg Plate	£4.20 (C)
AB721 Disco Cabinet	£55.45 (A)
BB19C Diaco Pot Amp Tn PCB	£2.10 (D)
BB19V Diaco PSU PCB	£2.10 (D)
BB20W 150W Amp Board	£2.42 (C)
BB26D Motor Switch PCB	£1.26 (D)
BB27E Light Mod Board	£3.98 (B)
BB24S Diaco Fader Bd	£2.32 (C)
KB37S Switch To Light Case	£14.20 (A)

Page 294	
LW93B Perylite Kit	£3.95 (B)
LW65V Stopwatch Kit	£39.50 (A)
YQ21X Snd/Lght Conv PCB	£2.38 (C)

Page 295	
GA62S Timer Switch Board	£3.95 (C)
LW94C Universal Timer Kit	£47.95 (A)

Page 296	
GB04E E L C Board	£5.45 (C)
GB07H T/E PSU PCB	£5.98 (C)
LW82D Digi-Tel Main Kit	£9.95 (A)
GA45Y Burgl Alarm Main PCB	£7.45 (B)
GA46A Break Contact PCB	£1.95 (D)
LW57M Burglar Alarm Kit	£48.95 (A)
LW59P Break Contact Kit	£2.85 (C)
LW58N Ext Horn Kit	£37.50 (A)

Page 297	
LW73Q RTX Doppler Kit	£48.95 (A)
LW74R Radar Ch/PSU Module	£15.95 (A)
LW83E Usonic Xceiver Kit	£10.95 (A)
LW84F Usonic Interface Kit	£2.95 (C)

Page 298	
LW97F Panic Button Kit	£3.95 (C)
LW98G Progible Timer Kit	£8.95 (B)

Page 299	
XF44X Magnum Booklet	78p NV (E)
YQ45Y Magnum 2 PCB	£3.32 (C)

Page 300	
LW61R Train Common/PSU Kit	£29.35 (A)
GB18U X81 Talkback PCB	£7.50 (B)
LW99H Modem Kit	£44.95 (A)

Page 301	
LK12N Drgn/R5232 Infr. Kit	£18.95 (A)
LK18U Dragon I/O Port	£14.95 (A)

Page 302	
LK00A VIC 20 Talkback Kit	£22.95 (A)

Page 303	
LW72P X81 Keyboard Kit	£23.95 (A)
YG22Y X81 Keyboard	£25.50 (A)
GA80X I/O Port PCB	£2.25 (D)
LW76H X81 I/O Port Kit	£2.48 (B)
GB08J X81 Extendable Board	£2.40 (C)

Page 304	
LW96E Sound Generator Kit	£13.49 (A)
GB18U X81 Talkback PCB	£7.50 (B)
LK01B X81 Talkback Kit	£19.95 (A)

Page 305	
LK08J X81 Modem Intfce Kit	£29.95 (A)
LK21X Sptm/R5232 Infr. Kit	£19.95 (A)
1F330 M5235	£1.28 NV (E)
1B828 RC Decoder PCB	£2.32 (D)
1B829 RC Xmitter PCB	£2.35 (C)
1B830H RC Receiver PCB	£1.96 (D)
1B831J RC Interface PCB	£1.69 (D)
1B832K RC Decoder PCB	£1.95 (D)
1B833L RC Relay Drive PCB	£1.30 (E)
1B834M RC Servo Drive PCB	£1.32 (D)
1B835Q RC Servo Amp PCB	£1.08 (E)
1B836P RC Tone Gen PCB	£3.96 (E)
1B837S RC Tone Decoder PCB	£1.10 (E)
YQ03D McM Encoder PCB	£2.95 (D)
YQ05F McM Rcvr Dcdr PCB	£2.20 (D)
YQ07H McM Transmitter PCB	£3.22 (C)

Page 306	
LK05F D'Kers Processor Kit	£8.95 (A)
LW95D Inverter Kit	£55.95 (A)
LK07H Enlarger Timer Kit	£7.95 (A)

Page 307	
LW78K Car Burgl Alarm Kit	£7.49 (B)
LW76X MPG Meter Kit	£54.95 (A)

Page 309	
GB02C Frequency Counter PCB	£5.95 (A)
GB04D Freq Chr Display PCB	£23.00 (D)
BB72P Sine/Square Gen PCB	£3.62 (C)

Page 310	
LK10L CMOS Xcl Cbrtr Kit	£19.95 (A)
LK06G Sweep Osc Kit	£1.95 (A)
GB31J Probe Lower PCB	£1.25 (E)
YQ54J Low Current Disc	£3.45 (C)
LK13P Logic Probe Kit	£10.95 (B)

Page 311	
LK09K Minilab Kit	£35.95 (A)

Page 312	
XF58L E&MM February 1982	DISC
XF58N E&MM April 1982	DISC
XF59P E&MM May 1982	DISC
1XF60D E&MM June '82	£1.10 NV
XF61R E&MM July 1982	DISC
XF62S E&MM August 1982	DISC
XF63T E&MM September 1982	DISC
1XF65V E&MM November 1982	£1.10 NV
1XF66W E&MM December 1982	£1.10 NV
XF67X E&MM January 1983	£1.10 NV

PROTECTION	
LK10L CMOS Xcl Cbrtr Kit	£19.95 (A)
LK06G Sweep Osc Kit	£1.95 (A)
GB31J Probe Lower PCB	£1.25 (E)
YQ54J Low Current Disc	£3.45 (C)
LK13P Logic Probe Kit	£10.95 (B)

Page 314	
RX93F Safesholder 1.1/4in	£1.98 (D)
RX49D Chassis F/H 20mm	14p (G)
RX50E Chassis F/H 1.1/4in	75p (G)
RX51F F/H Car 1 1/2in	11p (G)
WR19V Fuse A/S 1A	13p (G)
WR20W Fuse A/S 2A	13p (G)
HQ33L Plug Fuse 5A	13p (G)

Page 315	
BK22Y Thermal Breaker 3A	£2.25 (D)
BK23A Thermal Breaker 5A	£2.10 (D)
BK20W Thermal Breaker 15A	£1.95 (D)
HB51F Fuse Wire	33p (F)
HW06G RF Supp Choke 3A	44p (F)
HW07H Delta Cap	£1.20 (E)
*YW47B Surface Ba Reed	£1.95 (D)

Page 316	
XY33L Smoke Detectr Type 1	DIS (A)

1984 Catalogue Page No.	VAT Inclusive Price
-------------------------	---------------------

RECORD & TAPE

Page 317	
XQ00A Autochanger	DIS (A)
GB25S Belt Drive Turntable	£42.95 (A)
LB75S Drive Wheel BSR	£2.20 (D)

Page 318	
FQ36P Garrard Drive Belt	£3.48 (C)
HR09K Crdg BSR SC12M	£4.95 (C)
HR17T Crdg Sone V100	£7.95 (B)

Page 319	
HR16S Crdg Goldring 8000	£9.95 (B)
FQ34R Crdg Goldring 8000H	£9.95 (B)
FQ41U Crdg Tenoret T2001ED	£9.62 (A)

Page 322	
BK07H Stylus ATN3400	£7.45 (C)
HR66W Stylus Acos SM6	£5.95 (C)
BK09K Re-enterer As F68U	£6.30 (C)
HR39A Stylus BSR T8	£5.15 (D)
HR74R Stylus BSR ST21	£9.50 (D)
HR75H Stylus D10E	£5.95 (B)
YX20W Styl Philips GP401MK2	£5.95 (B)
HR95D Stylus Sansul SN28	£5.95 (C)
FQ38G Sanyo ST28 Stylus	DIS
YK2C Sanyo ST123 Stylus	£7.32 (C)
YK26D Stylus Sonotone V101	£5.95 (B)
HR53H Stylus KS40A DD	£1.45 (D)
FQ69E Sony ND250 Stylus	DIS
TK18U Stylus ND200	£7.25 (B)
YK2C Stylus Sony XL15	£4.95 (C)
YK28F Stylus Sony ND125	DIS (C)
YK47B Hi-Fi Care Kit C72	£7.95 (C)
LX06G Cleaning Arm C100	£3.45 (E)
FR46A Stylus Cleaner C50	DIS (E)

Page 323	
FG71N Rollaclean	£5.42
LX10L Anti-Stat Mat C119	£2.95 (C)

Page 324	
FG74R Head + Capstan Kit	£1.64
FR62S Straight Demagnetizer	DIS (C)
LK17R Splicing Tape	78p (E)
RB01B Cassette Fast Winder	£3.45 (E)
YG25C Cassette Tape C60	65p (E)

Page 325	
FQ63T GF Cassette Head	£9.62 (A)
FQ65E Cassette Grip Head	£1.96 (C)
FQ65W Stereo Cassette Head	£3.95 (C)

Page 327	
W W/W Min 0.22R to 1R	37p (F)
W W/W Min 2R2 to 22K	22p (G)

Page 328	
L 7W W/W	33p (F)
H 10W W/W	42p (F)
W/R 15W 1M-33M	15p (G)
V H/R Res 47M	29p (F)
YI12N Resnet 100R	9p (E)
YI15R Resnet 1k	85p (E)
YI20W Resnet 47k	79p (E)

Page 329	
WR81C Hor Skeleton 1k	28p (F)
WR82D Hor Skeleton 2k2	33p (F)
WR83E Hor Skeleton 4k7	28p (F)
WR84F Hor Skeleton 10k	28p (F)
WR85G Hor Skeleton 22k	28p (F)
WR87T Hor Skeleton 47k	28p (F)
WR87U Hor Skeleton 100k	32p (F)
WR88A Hor Skeleton 220k	32p (F)
WR89X Hor Skeleton 470k	31p (F)
WR90W Hor Skeleton 1M	31p (F)
WR91Y Hor Skeleton 2M2	28p (F)
WR92A Hor Skeleton 4M7	31p (F)
WV00A Vrt Skeleton 100k	31p (F)
WV01B Vrt Skeleton 200k	31p (F)
WV02C Vrt Skeleton 470k	33p (F)
WV03D Vrt Skeleton 1k	31p (F)
WV04E Vrt Skeleton 2k	31p (F)
WV05F Vrt Skeleton 4k7	31p (F)
WV06G Vrt Skeleton 10k	31p (F)
WV07H Vrt Skeleton 22k	33p (F)
WV08J Vrt Skeleton 47k	31p (F)
WV09K Vrt Skeleton 100k	31p (F)
WV10L Vrt Skeleton 220k	31p (F)
WV11M Vrt Skeleton 470k	31p (F)
WV12N Vrt Skeleton 1M	31p (F)
WV13P Vrt Skeleton 2M2	31p (F)
WV14Q Vrt Skeleton 4M7	31p (F)
WR92A 15-Turn Cermet 10k	£1.20 (E)
WR50E 15-Turn Cermet 50k	£1.20 (E)
WR51F 15-Turn Cermet 50k	£1.20 (E)
BV06DE Edge Control Pot	DIS (E)
BV07H Edge Knob Small Blk	DIS (H)
BV08E Edge Knob Large Blk	DIS (H)
BV10L Edge Knob Large Gray	DIS (H)

RESISTORS

Page 327	
W W/W Min 0.22R to 1R	37p (F)
W W/W Min 2R2 to 22K	22p (G)

Page 328	
L 7W W/W	33p (F)
H 10W W/W	42p (F)
W/R 15W 1M-33M	15p (G)
V H/R Res 47M	29p (F)
YI12N Resnet 100R	9p (E)
YI15R Resnet 1k	85p (E)
YI20W Resnet 47k	79p (E)

Page 329	
WR81C Hor Skeleton 1k	28p (F)
WR82D Hor Skeleton 2k2	33p (F)
WR83E Hor Skeleton 4k7	28p (F)
WR84F Hor Skeleton 10k	28p (F)
WR85G Hor Skeleton 22k	28p (F)
WR87T Hor Skeleton 47k	28p (F)
WR87U Hor Skeleton 100k	32p (F)
WR88A Hor Skeleton 220k	32p (F)
WR89X Hor Skeleton 470k	31p (F)
WR90W Hor Skeleton 1M	31p (F)
WR91Y Hor Skeleton 2M2	28p (F)
WR92A Hor Skeleton 4M7	31p (F)
WV00A Vrt Skeleton 100k	31p (F)
WV01B Vrt Skeleton 200k	31p (F)
WV02C Vrt Skeleton 470k	33p (F)
WV03D Vrt Skeleton 1k	31p (F)
WV04E Vrt Skeleton 2k	31p (F)
WV05F Vrt Skeleton 4k7	31p (F)
WV06G Vrt Skeleton 10k	31p (F)
WV07H Vrt Skeleton 22k	33p (F)
WV08J Vrt Skeleton 47k	31p (F)
WV09K Vrt Skeleton 100k	31p (F)
WV10L Vrt Skeleton 220k	31p (F)
WV11M Vrt Skeleton 470k	31p (F)
WV12N Vrt Skeleton 1M	31p (F)
WV13P Vrt Skeleton 2M2	31p (F)
WV14Q Vrt Skeleton 4M7	31p (F)
WR92A 15-Turn Cermet 10k	£1.20 (E)
WR50E 15-Turn Cermet 50k	£1.20 (E)
WR51F 15-Turn Cermet 50k	£1.20 (E)
BV06DE Edge Control Pot	DIS (E)
BV07H Edge Knob Small Blk	DIS (H)
BV08E Edge Knob Large Blk	DIS (H)
BV10L Edge Knob Large Gray	DIS (H)

Page 330	
FW84F Dual Pot Lin 4k7	£1.42 (D)
FW85G Dual Pot Lin 10k	£1.42 (D)
FW86U Dual Pot Lin 22k	£1.42 (D)
FW87A Dual Pot Lin 47k	£1.42 (D)
FW88V Dual Pot Lin 100k	£1.42 (D)
FW89W Dual Pot Lin 220k	£1.42 (D)
FW90X Dual Pot Lin 470k	£1.42 (D)
FW91Y Dual Pot Lin 1M	£1.42 (D)
FW92A Dual Pot Lin 2M2	£1.42 (D)
FX08J Dual Pot Log 4k7	£1.42 (D)
FX09K Dual Pot Log 10k	£1.42 (D)
FX10L Dual Pot Log 22k	£1.42 (D)
FX11M Dual Pot Log 47k	£1.42 (D)
FX12N Dual Pot Log 100k	£1.42 (D)
FX13P Dual Pot Log 220k	£1.42 (D)
FX14Q Dual Pot Log 470k	£1.42 (D)
FX15R Dual Pot Log 1M	£1.42 (D)
FX16S Dual Pot Log 2M2	£1.42 (D)

Page 331	
FW50E W/W Pot 10R	DIS (C)
FW51F W/W Pot 25R	DIS (C)
FW73D W/W Pot 500R	£2.48 (D)
FX08J Slide Pot Lin 5k	82p (E)
FX09K Slide Pot Lin 10k	82p (E)
FX30M Slide Pot Lin 25k	82p (E)
FX35Q Slide Pot Lin 50k	82p (E)
FX36P Slide Pot Lin 100k	82p (E)
FX37S Slide Pot Lin 250k	82p (E)
FX38T Slide Pot Lin 500k	82p (E)
FX53H Slide Pot Log 5k	82p (E)
FX54J Slide Pot Log 10k	82p (E)
FX55K Slide Pot Log 25k	82p (E)
FX56L Slide Pot Log 50k	82p (E)
FX57M Slide Pot Log 100k	82p (E)
FX58N Slide Pot Log 250k	82p (E)
FX59P Slide Pot Log 500k	82p (E)
FX76H Dual Slide Lin 5k	£1.48 (D)
FX77J Dual Slide Lin 10k	£1.48 (D)
FX78K Dual Slide Lin 25k	£1.48 (D)
FX79L Dual Slide Lin 50k	£1.48 (D)
FX80M Dual Slide Lin 100k	£1.48 (D)
FX8	

1984 Catalogue Page No.	VAT Inclusive Price	1984 Catalogue Page No.	VAT Inclusive Price
YF61R 74LS157	95p (F)	Page 388	
YF62S 74LS158	95p (F)	WQ76H TL172C	£1.24 (E)
WH05K 74160	£1.95 (E)	WQ75S TL170C	95p (E)
YF63T 74LS160	£1.22 (F)	QR55K 64S452	£6.95 (C)
YF64U 74LS161	£1.22 (F)		
YF65W 74LS163	£1.22 (F)	Page 389	
WH10L 74164	£2.32 (E)	YY99H LM1830	£2.95 (C)
YF67X 74LS164	£1.58 (E)	YY73Q LM3252	£1.32 (D)
YF68Y 74LS165	£1.95 (D)	YG37S CL960	£39.95 (A)
YF69A 74LS166	£2.95 (D)	YY98G AY-3-1270	DIS (B)
YF71N 74LS169	£1.84 (E)		
YF72P 74LS170	£3.40 (D)	Page 390	
YF73Q 74LS173	£1.82 (E)	WQ41U LM3914	£3.95 (C)
WH11M 74174	£1.95 (E)	YY96E LM3915	£2.98 (C)
YF74R 74LS174	£1.95 (F)	YY97F LM3916	£2.98 (C)
YF75S 74LS175	£1.42 (F)		
YF76H 74LS181	£3.38 (C)	Page 391	
YF78K 74LS190	£1.52 (E)	QY14Q UAA170L	£3.95 (C)
YF79L 74LS191	£1.48 (E)	YH30H 74C317	£9.60 (B)
YF80B 74LS192	£1.62 (E)	YY93B ICM7045PI	£17.98 (A)
QD30X 74193	£2.22 (D)		
YF81C 74LS193	£1.62 (E)	Page 393	
WH13P 74194	£1.68 (E)	YH88V TMS1121	£11.95 (B)
YF82D 74LS194	£1.22 (E)	QY08J 74C925	£6.95 (B)
YF83E 74LS195	£1.19 (F)		
YF84F 74LS196	£1.62 (E)	Page 394	
YF85M 74LS197	£1.10 (E)	YY94C ICM72160PI	£21.95 (A)
YF86T 74LS221	£1.62 (E)		
YF87U 74LS240	£2.26 (E)	Page 395	
YF88V 74LS241	£2.24 (E)	QH66W NE 555	39p (G)
YF89W 74LS242	DIS (D)	QH67X NE 556	78p (E)
YF90X 74LS243	£1.95 (E)		
QD56L 74LS244	£2.32 (E)	Page 396	
YF91Y 74LS245	£3.42 (D)	YH63T ICM 7555	£1.95 (D)
YF92A 74LS251	£1.18 (E)		
YF93B 74LS253	£1.54 (E)	Page 397	
YF95D 74LS257	£1.19 (E)	WQ39N LM3909	95p (E)
YF97F 74LS259	£2.62 (E)	YY76H TDA1024	£1.95 (D)
YF99H 74LS266	49p (F)		
YH00A 74LS273	£1.19 (F)	Page 398	
YH01B 74LS279	£1.19 (F)	QY36P LM1851N	£2.70 (D)
YH02C 74LS283	£1.45 (E)	YH45W 8211 CPA	£2.95 (C)
YH03D 74LS290	DIS (D)	YH39N 8069 DCQ	£2.95 (C)
QY39N 74LS292	DIS (D)	YH78K TL497A	£2.20 (D)
YH04E 74LS293	DIS (E)	YY77J TL430C	£1.22 (E)
YH06G 74LS298	£14.48 (A)		
YH11M 74LS365	79p (F)	Page 399	
YH12N 74LS366	89p (F)	YY75S ICL7660CPA	£6.98 (C)
YH13P 74LS367	78p (E)	YH74R L300	£1.82 (C)
YH14Q 74LS368	79p (F)		
YH15R 74LS373	£2.38 (E)	Page 401	
YH16S 74LS374	£2.42 (E)	YQ39N 0.1A Reg PSU PCB	£1.45 (D)
YH18U 74LS377	£2.42 (E)	YH22Y 74LS393	£1.82 (D)
YH19V 74LS378	79p (D)	Page 403	
YH20W 74LS379	DIS (C)	QV00A 780-CPU	£3.98 (B)
YH22Y 74LS393	£1.82 (D)	QV03D 780-PIO	£3.30 (C)
YH23A 74LS395	£1.15 (D)	YH40T 8080A	£6.45 (C)
WH02C 74LS629-74LS124	£1.98 (D)		
YH30H 74C917	£9.60 (B)	Page 405	
YH08J 74C925	£6.95 (B)	YH41U 8085A	£8.20 (B)
YH32K 76477	£5.95 (B)	YH46A 8224	£3.98 (C)
YH34M 8728	£2.74 (D)	YH47B 8228	£8.25 (C)
YH35Q 8729	70p (C)	YH49D 8238	£8.25 (C)
YH38R 8038 CCPD	£4.98 (C)	YH48C 8250	£13.25 (B)
YH39N 8069 DCQ	£2.95 (C)	YH51F 8279	£6.95 (B)
YH40T 8080A	£8.45 (C)		
YH41U 8085A	£8.20 (B)	Page 406	
YH42W 8211 CPA	£2.95 (C)	YH44X 8212	£2.26 (D)
YH44X 8212	£2.25 (D)	YH34M 8728	£2.74 (D)
YH46A 8224	£3.98 (C)	YH35Q 8729	70p (C)
YH47B 8228	£8.25 (C)	YH89W MC1488N	£1.38 (E)
YH48C 8250	£13.25 (B)	YH90X MC1489N	£1.38 (E)
YH49D 8238	£8.25 (C)		
YH51F 8279	£6.95 (B)	Page 407	
		WQ19V AY-5-2378	DIS (A)
Page 363		QD04E 6402	£7.74 (B)
YH58Y NE5534A	£2.48 (C)	QD03D MC6845	£13.95 (B)
QH51F 3403	95p (E)	YH31J 5011-L1	£3.48 (C)
QH42V LM3900	£1.36 (E)		
		Page 408	
Page 364		QW11M 2102 450ns	£2.85 (C)
QH28F CA3130E	£1.38 (D)	WQ45Y MC6810AP 450ns	£3.36 (D)
WQ21X CA3240E	£1.55 (D)	QW12N 2114 450ns	£1.99 (D)
YH98A LF13741	95p (E)	WQ42V MCM4027 250ns	£2.48 (D)
WQ30M L535	85p (E)	QW93B 4118 250ns	£2.46 (D)
WQ29G LF347	£1.62 (D)	QD06E 184 250ns	£8.95 (C)
QV27E LF411CN	£1.22 (E)	QW13P 2708 450ns	£5.95 (C)
QV28F LF412CN	£2.48 (D)		
QV29G LF441CN	96p (E)	Page 409	
QY30H LF442CN	£1.88 (D)	QD07H 2716 450ns	£5.75 (C)
QY31J LF444CN	£2.98 (D)	QD08J 2732 450ns	£7.95 (B)
		QD09K 2764 450ns	£12.85 (B)
Page 365			
YH58N CA3080E	£1.48 (E)	Page 410	
YH48U LM13700N	£1.95 (D)	QW11M 2102 450ns	£2.85 (C)
QV09K LM1311N	£1.62 (E)	WQ45Y MC6810AP 450ns	£3.36 (D)
YH84C MC3302P	95p (E)	QW12N 2114 450ns	£1.99 (D)
		WQ42V MCM4027 250ns	£2.48 (D)
Page 367		QW93B 4118 250ns	£2.46 (D)
QH40T LM380	£1.82 (E)	QD06E 184 250ns	£8.95 (C)
WQ34M LM384	£1.72 (D)	QW13P 2708 450ns	£5.95 (C)
Page 370		Page 411	
QH41U LM381	£1.80 (C)	QW90B 4151	£1.15 (E)
WQ35Q LM387	£1.95 (D)	YH93B AM7910	£49.95 (A)
Page 371		Page 412	
QY19V LM1035	£3.95 (C)	QY43W XR2211CP	£3.84 (C)
		QD01B DAC0801LCN	£4.45 (C)
Page 372			
YK33L LM1037N	£2.30 (C)	Page 413	
QY34M LM1038N	£4.65 (D)	QD00A ADC0804LCN	£5.95 (C)
YK55G LM1081N	£1.98 (D)	WQ38R LM2917	£2.20 (C)
Page 373		Page 415	
QH49D MC3304P	£3.62 (C)	WR29G Transist 3-Lead T018	22p (F)
		WR30H Transist 4-Lead T018	42p (F)
Page 374			
QY35Q MF10CN	£4.95 (C)	Page 416	
QD52G AY-1-1320	£6.45 (C)	QH77J Oil Socket 20-pin	18p (G)
QD51F AY-1-5050	£3.15 (D)	BL20W Oil Socket 24-pin	20p (G)
QH71N M251	£15.95 (A)	HQ38R Oil Socket 40-pin	30p (F)
		YQ29G Header 24-pin	£1.45 (D)
Page 377		YK50E ZIF Socket 24-Way	£4.95 (C)
YH79L TCA350Z	£3.85 (C)		
		Page 417	
Page 378		FG52G Clip on T0220	31p (F)
YH32K 76477	£5.95 (B)	FG55K Powerfin plastic	59p (F)
Page 380		Page 418	
QY50E SP0256	£9.95 (A)	FG60Q Heatsink T0220HP	88p (E)
		FG63T Dip Smtk 40-pin	82p (E)
Page 381		FL41U Heatsink 4Y	£2.30 (C)
BL35Q TBA 651	DIS (C)	*FG64U Coverplate 4Y	38p (B)
WQ64U TCA4500A	£3.95 (C)		
		Page 419	
Page 383		FL42V Heat Sink	£4.36 (C)
QY23A MC10116P	£1.32 (E)	FL54J Heatsink 100N	£2.48 (C)
QH47B MC1496	£1.95 (E)	FL57J Heatsink 6W-1	£7.98 (D)
		*FG65V Coverplate 6W	38p (D)
Page 384			
QD07H SG3402	£4.98 (C)		
QD26D CA3046	£1.22 (E)		
QD11M VQ1000CJ	£7.74 (D)		
*YH66W SL490	£3.95 (C)		
Page 386			
BK66W UM1286 Modulator	£11.90 (A)		
YF71N LM1817	£1.95 (D)		
YQ69A LM1871 Xmitter PCB	£1.25 (D)		

1984 Catalogue Page No.	VAT Inclusive Price	1984 Catalogue Page No.	VAT Inclusive Price
YF61R 74LS157	95p (F)	Page 388	
YF62S 74LS158	95p (F)	WQ76H TL172C	£1.24 (E)
WH05K 74160	£1.95 (E)	WQ75S TL170C	95p (E)
YF63T 74LS160	£1.22 (F)	QR55K 64S452	£6.95 (C)
YF64U 74LS161	£1.22 (F)		
YF65W 74LS163	£1.22 (F)	Page 389	
WH10L 74164	£2.32 (E)	YY99H LM1830	£2.95 (C)
YF67X 74LS164	£1.58 (E)	YY73Q LM3252	£1.32 (D)
YF68Y 74LS165	£1.95 (D)	YG37S CL960	£39.95 (A)
YF69A 74LS166	£2.95 (D)	YY98G AY-3-1270	DIS (B)
YF71N 74LS169	£1.84 (E)		
YF72P 74LS170	£3.40 (D)	Page 390	
YF73Q 74LS173	£1.82 (E)	WQ41U LM3914	£3.95 (C)
WH11M 74174	£1.95 (E)	YY96E LM3915	£2.98 (C)
YF74R 74LS174	£1.95 (F)	YY97F LM3916	£2.98 (C)
YF75S 74LS175	£1.42 (F)		
YF76H 74LS181	£3.38 (C)	Page 391	
YF78K 74LS190	£1.52 (E)	QY14Q UAA170L	£3.95 (C)
YF79L 74LS191	£1.48 (E)	YH30H 74C317	£9.60 (B)
YF80B 74LS192	£1.62 (E)	YY93B ICM7045PI	£17.98 (A)
QD30X 74193	£2.22 (D)		
YF81C 74LS193	£1.62 (E)	Page 393	
WH13P 74194	£1.68 (E)	YH88V TMS1121	£11.95 (B)
YF82D 74LS194	£1.22 (E)	QY08J 74C925	£6.95 (B)
YF83E 74LS195	£1.19 (F)		
YF84F 74LS196	£1.62 (E)	Page 394	
YF85M 74LS197	£1.10 (E)	YY94C ICM72160PI	£21.95 (A)
YF86T 74LS221	£1.62 (E)		
YF87U 74LS240	£2.26 (E)	Page 395	
YF88V 74LS241	£2.24 (E)	QH66W NE 555	39p (G)
YF89W 74LS242	DIS (D)	QH67X NE 556	78p (E)
YF90X 74LS243	£1.95 (E)		
QD56L 74LS244	£2.32 (E)	Page 396	
YF91Y 74LS245	£3.42 (D)	YH63T ICM 7555	£1.95 (D)
YF92A 74LS251	£1.18 (E)		
YF93B 74LS253	£1.54 (E)	Page 397	
YF95D 74LS257	£1.19 (E)	WQ39N LM3909	95p (E)
YF97F 74LS259	£2.62 (E)	YY76H TDA1024	£1.95 (D)
YF99H 74LS266	49p (F)		
YH00A 74LS273	£1.19 (F)	Page 398	
YH01B 74LS279	£1.19 (F)	QY36P LM1851N	£2.70 (D)
YH02C 74LS283	£1.45 (E)	YH45W 8211 CPA	£2.95 (C)
YH03D 74LS290	DIS (D)	YH39N 8069 DCQ	£2.95 (C)
QY39N 74LS292	DIS (D)	YH78K TL497A	£2.20 (D)
YH04E 74LS293	DIS (E)	YY77J TL430C	£1.22 (E)
YH06G 74LS298	£14.48 (A)		
YH11M 74LS365	79p (F)	Page 399	
YH12N 74LS366	89p (F)	YY75S ICL7660CPA	£6.98 (C)
YH13P 74LS367	78p (E)	YH74R L300	£1.82 (C)
YH14Q 74LS368	79p (F)		
YH15R 74LS373	£2.38 (E)	Page 401	
YH16S 74LS374	£2.42 (E)	YQ39N 0.1A Reg PSU PCB	£1.45 (D)
YH18U 74LS377	£2.42 (E)	YH22Y 74LS393	£1.82 (D)
YH19V 74LS378	79p (D)	Page 403	
YH20W 74LS379	DIS (C)	QV00A 780-CPU	£3.98 (B)
YH22Y 74LS393	£1.82 (D)	QV03D 780-PIO	£3.30 (C)
YH23A 74LS395	£1.15 (D)	YH40T 8080A	£6.45 (C)
WH02C 74LS629-74LS124	£1.98 (D)		
YH30H 74C917	£9.60 (B)	Page 405	
YH08J 74C925	£6.95 (B)	YH41U 8085A	£8.20 (B)
YH32K 76477	£5.95 (B)	YH46A 8224	£3.98 (C)
YH34M 8728	£2.74 (D)	YH47B 8228	£8.25 (C)
YH35Q 8729	70p (C)	YH49D 8238	£8.25 (C)
YH38R 8038 CCPD	£4.98 (C)	YH48C 8250	£13.25 (B)
YH39N 8069 DCQ	£2.95 (C)	YH51F 8279	£6.95 (B)
YH40T 8080A	£8.45 (C)		
YH41U 8085A	£8.20 (B)	Page 406	
YH42W 8211 CPA	£2.95 (C)	YH44X 8212	£2.26 (D)
YH44X 8212	£2.25 (D)	YH34M 8728	£2.74 (D)
YH46A 8224	£3.98 (C)	YH35Q 8729	70p (C)
YH47B 8228	£8.25 (C)	YH89W MC1488N	£1.38 (E)
YH48C 8250	£13.25 (B)	YH90X MC1489N	£1.38 (E)
YH49D 8238	£8.25 (C)		
YH51F 8279	£6.95 (B)	Page 407	
		WQ19V AY-5-2378	DIS (A)
Page 363		QD04E 6402	£7.74 (B)
YH58Y NE5534A	£2.48 (C)	QD03D MC6845	£13.95 (B)
QH51F 3403	95p (E)	YH31J 5011-L1	£3.48 (C)
QH42V LM3900	£1.36 (E)		
		Page 408	
Page 364		QW11M 2102 450ns	£2.85 (C)
QH28F CA3130E	£1.38 (D)	WQ45Y MC6810AP 450ns	£3.36 (D)
WQ21X CA3240E	£1.55 (D)	QW12N 2114 450ns	£1.99 (D)
YH98A LF13741	95p (E)	WQ42V MCM4027 250ns	£2.48 (D)
WQ30M L535	85p (E)	QW93B 4118 250ns	£2.46 (D)
WQ29G LF347	£1.62 (D)	QD06E 184 250ns	£8.95 (C)
QV27E LF411CN	£1.22 (E)	Q	

TOP TWENTY KITS

THIS LAST MONTH	DESCRIPTION OF KIT	ORDER CODE	KIT PRICE	DETAILS IN PROJECT BOOK
1. (1)	◆ 75W Mosfet Amp Module	LW51F	£15.95	Best of E&MM
2. (2)	◆ Modem	LW99H	£44.95	5 XA05F
<i>Case also available: YK62S Price £9.95.</i>				
3. (3)	◆ Car Burglar Alarm	LW78K	£7.49	4 XA04E
4. (5)	◆ Partylite	LW93B	£9.95	Best of E&MM
5. (4)	◆ Spectrum Easyload	LK39N	£9.95	10 XA10L
6. (8)	◆ 8W Amp Module	LW36P	£4.45	Catalogue
7. (10)	◆ VIC20/64 RS232 Interface	LK11M	£9.45	7 XA07H
8. (-)	◆ Cautious Ni-Cad Charger	LK50E	£19.95	11 XA11M
9. (6)	◆ Syntom Drum Synthesiser	LW86T	£12.95	Best of E&MM
10. (12)	◆ Spectrum RS232 Interface	LK21X	£19.95	8 XA08J
11. (7)	◆ Ultrasonic Intruder Detector	LW83E	£10.95	4 XA04E
12. (9)	◆ Logic Probe	LK13P	£10.95	8 XA08J
13. (13)	◆ ZX81 I/O Port	LW76H	£10.49	4 XA04E
14. (16)	◆ Harmony Generator	LW91Y	£17.95	Best of E&MM
15. (17)	◆ Guitar Tuner	LW90X	£12.95	Best of E&MM
16. (20)	◆ Burglar Alarm	LW57M	£49.95	2 XA02C
17. (-)	◆ Keyboard for ZX81	LW72P	£23.95	3 XA03D
<i>Case also available: XG17T £4.95. Complete ready-built: XG22Y £32.50</i>				
18. (19)	◆ 80m Amateur Receiver	LK41U	£15.95	10 XA10L
19. (-)	◆ ZX81 Sounds Generator	LW96E	£13.49	5 XA05F
20. (-)	◆ ZX81 Talkback	LK01B	£19.95	6 XA06G E&MM

Over 80 other kits also available. All kits supplied with instructions. The descriptions above are necessarily short. Please ensure you know exactly what the kit is and what it comprises before ordering, by checking the appropriate Project Book mentioned in the list above.

CORRIGENDA

Vol. 1 No. 3

The specification of the 25W MOSFET Amplifier should read: Magnetic pick-up input 2mV at 68k; Tape input 50mV at 1k2; Tuner input 50mV at 1k2; and Auxiliary input 50mV at 1k2. Also note that if you check the +15V rails on D5 and D6 you should obtain a reading below 30mV DC between the cases of the four MOSFETs and the chassis.

Vol. 2 No. 6

ZX81 Talkback: If you have a talkback module that suffers from 'slurred speech' when POKing data from a string or REM line, then two simple component value changes can be made. Change R8 to 47Ω from 1k and C7 to 10μF 16V tantalum from a 0.1μF Disc ceramic. The +V lead of C7 must connect to pins 2 and 25 of IC5.

Vol. 2 No. 7

ZX81 Modem Interface: Some kits are being supplied with IC3 as

an NEC D8255AC-5 type, in which case a small modification is required to improve access timing. Remove the track pin adjacent to IC1 pin 9 (which connects to MREQ). Re-connect IC1 pin 9 to IC1 pin 7 (0V). The MREQ line is left disconnected.

Digital Enlarger Timer/Controller: In the circuit diagram pin 10 of IC2b should go to +12V and not 0V.

Vol. 3 No. 9

TDA 7000 Radio: Improved reception can sometimes be obtained by decreasing the number of turns in L1 to 5.

Vol. 3 No. 10

Spectrum Easyload: In the circuit diagram, note that R5 and R15 are reversed. R5 is the resistor from the base of TR1 to -V, and R15 is the resistor from the base of TR1 to D1/IC3. Note the PCB layout is correct.

TOP TWENTY BOOKS

- (3) How to Design & Make Your Own PCB'S, by R.A. Penfold (WK63T) cat. P40.
- (2) Power Supply Projects, by R.A. Penfold (XW52G) cat. P41.
- (10) IC555 Projects, by E.A.Parr (LY04E) cat. P42.
- (11) International Transistor Equivalents Guide, by Adrian Michaels (WG30H) cat. P36.
- (7) Understanding Telephone Electronics, by J. Fike and G. Friend (WK45Y) cat. P42.
- (-) Audio Projects, by F.G. Rayer (WG46A) cat. P44.
- (9) How to Build Your Own Solid State Oscilloscope, by F.G. Rayer (XW07H) cat. P45.
- (20) Electronic Synthesiser Projects, by M.K. Berry (XW68Y) cat. P51.
- (-) Atari Op-sys Users Manual (Technical Notes), (WA46A) cat. P62.
- (8) Electronic Security Devices, by R.A. Penfold (RL43W) cat. P43.
- (1) Remote Control Projects, by Owen Bishop (XW39N) cat. P45.
- (14) How to Use Op-amps, by E.A. Parr (WA29G) cat. P38.
- (-) Z80 IC's Data Sheets (4th Edition) (RQ54J) cat. P38.



- (6) A Z80 Workshop Manual, by E.A. Parr (WA54J) cat. P57.
- (16) Radio & Electronics Colour Codes & Data Chart (RH05F) cat. P34.
- (-) How to Make Walkie-Talkies, by F.G. Rayer (RF18U) cat. P47.
- (-) 68000 Assembly Language Programming, by Kane, Hawkins and Leventhal (WA04E) cat. P56.
- (-) 30 Solderless Breadboard Projects Book 1, by R.A. Penfold (WA51F) cat. P35.
- (-) Towers' International Transistor Selector Update 2, by T.D. Towers (RR39N) cat. P36.
- (19) How to Build Advanced Shortwave Receivers, by R.A. Penfold (RB26D) cat. P47.

These are our top twenty best selling books based on mail order and shop sales during March, April and May 1984. Our own publications and magazines are not included. We stock nearly 700 different books, covering a wide range of electronics and computing topics. The full selection is shown on pages 33 to 70 of the 1984 catalogue, plus the new books sections in 'Electronics' Volume 3 issues 9, 10 and 11, and the new books in this issue.

Continued from page 28.

NEW BOOKS

ZX Spectrum Astronomy by Maurice Gavin

A book aimed at Spectrum owners who wish to expand their computing knowledge to include astronomy. All aspects of the subject are introduced, including star charts, star systems, tracking the orbit of a planet, satellites etc, plus much more. Great emphasis is placed on the high quality graphics that can be achieved, to display such things as the simulated movement of stars. 234x153mm, 229 pages, illustrated. Order As WM84F (Spectrum Astronomy) Price £7.95NV

Artificial Intelligence on the Commodore 64 by Keith and Steven Brain

An interesting new book which explains Artificial Intelligence from first principles; all the important aspects of the subject are covered and fully illustrated with programs. The book will show you how to implement A.I. routines on the Commodore 64 and turn it into an 'intelligent' machine which can converse rationally. 233x155mm, 144 pages, illustrated. Order As WM85G (A.I. Commodore 64) Price £7.65NV

The Commodore 64 Puzzle Book by Brian Boyde-Shaw

The book is not about how to make up crossword puzzles or play games of snakes and ladders on the 64, rather it is a teaching system to help the reader learn how to write and enter programs and eventually be able to use the machine with confidence. Ideal for beginners, the 'puzzles' take the form of writing programs to solve problems for which solutions are also provided in case of difficulty or to double-check your progress. By the time you have solved the first few problems you will be

confident that you can write programs that will for example, display text on the screen, just as YOU want it to look, carry out calculations, or play simple games. You will solve these problems and learn BASIC at the same time, and also learn to approach each problem in a logical fashion. Your success in solving a problem is used to reinforce what you already know, so that the next problem is solved more easily. 214x135mm, 130 pages, illustrated.

Order As WM91Y (64 Puzzle Book) Price £8.20NV



READERSHIP SURVEY

RESULTS RESULTS RESULTS RESULTS RESULTS

Most opinion polls rely on interviews with a minute cross-section of the population and assume that their responses can be extrapolated to the population as a whole. Usually about one to two thousand people are questioned and the response of twenty to thirty million people predicted from the result. Even with such a small percentage poll, the results can be extraordinarily accurate.


The results of our survey should be even more accurate, since we received 1657 replies, yet wish to use this as a guide to what only a little over 200,000 people (our customers) think about us. Before we begin though, let me tell you the winners of our Prize Draw. First out of the hat was Mr. R. Murphy, a student from Bourne in Lincolnshire who wins £50. The second and third prizes of £10 each went to Mr. A. Raja, a printer from London, and Mr. B. Harrington, an electronics engineer from South Ascot in Berkshire. Now to the actual results.

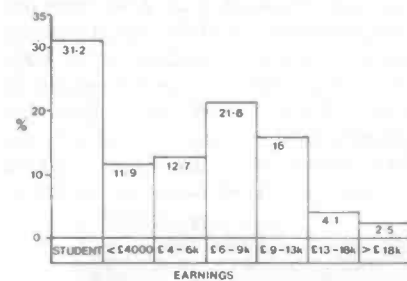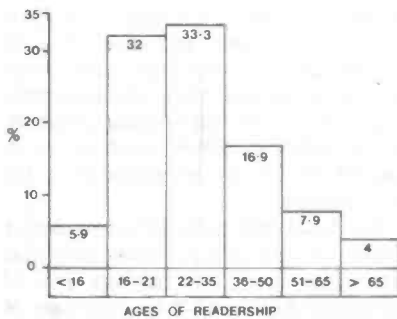Nearly two-thirds of our readers are in the age-group 16 to 35 and well over a



third are under 21. I would have thought that electronics would be a fascinating hobby for those who have retired, so it was disappointing to see such a low audience amongst the over 50's. Perhaps the content of the magazine doesn't appeal to them, (or as is much more likely, all the most enthusiastic, constructors have long since died, welded between the cathode and anode of an 807). Ah, those were the days, when men were men and the power rail would melt the end of your screwdriver if you weren't careful. Nowadays it's all 5V and CMOS. These youngsters can't remember the excitement of turning on a new project with its lethal voltages buzzing before you; the hairs on the back of the neck tingling and the smell of ozone rising from a bad joint.







September 1984 Maplin Magazine

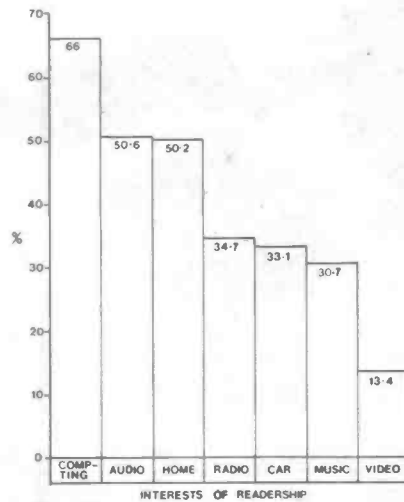

We were pretty certain that computing would be one of the main interests of our readers, so we were not surprised to see such a large figure here: nearly two-thirds of our readers. Lots of you mentioned security as another interest, but we really meant this area to be covered by "Home", so we've added these together, and still "Audio" just scraped in as second favourite. Fortunately, many people were interested in a wide range of subjects, which means we can please most of the people most of the time with our average content.

The only really sizeable vote for more coverage was for non-computer projects whilst over a third of you also wanted more educational articles and equipment reviews. However, since there was no really large vote for less of anything, this could be a problem.

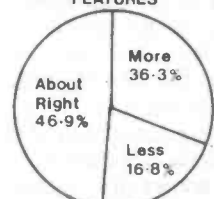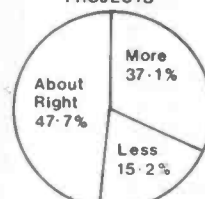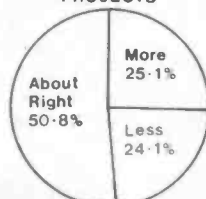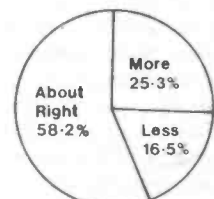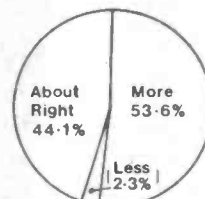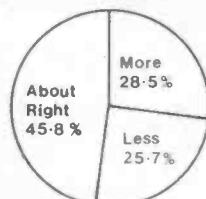A massive 91% of our readers, regularly build projects and the average project builder builds an astonishing 5.8 projects per year. (We must have been out of stock of something for the sixth one). Only a third of the projects you built were Maplin's, but we were pleased to see that 99% of them worked; 64.6% first time as well. Less than 8 in a thousand of our readers were unsuccessful.





MAGAZINE CONTENTS

Of those who had built Maplin projects over 98% thought they were at least as good as other magazines' etc. and a very gratifying 64% of you thought they were better.

Another very pleasing result was that over 70% of you read the magazine very thoroughly, and over 97% keep the magazine for future reference.

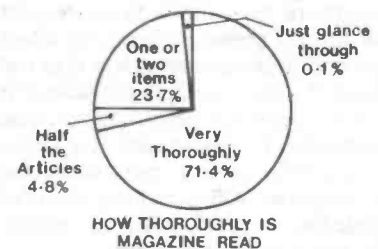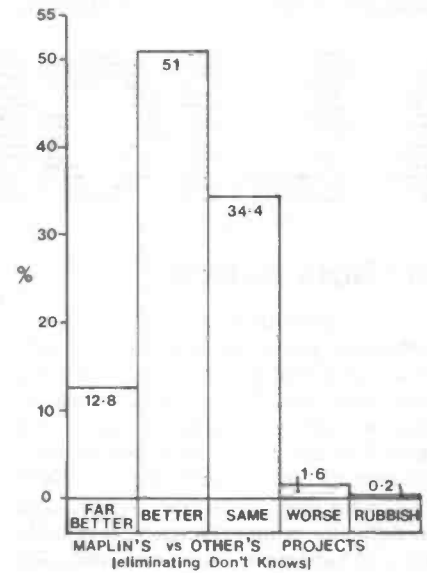We haven't yet finished analysing what you thought of the monthly magazines, so we'll tell you about that in our next issue. And we'll answer some of the more interesting comments (good and bad) then as well.





by Chris Barlow

If you own an Atari, VIC20, or Commodore 64, you possess a computer with the ability to accept a light pen input. But if you have ever tried to obtain a ready-built unit, you will probably have been amazed at the cost even if you found a source at all. This is partly due to the lack of software that the device requires, and the difficulty in manufacturing a reliable piece of hardware. Some manufacturers have attempted to produce such a device, but due to marketing considerations (i.e. cost and potential sales), the resulting hardware leaves a lot to be desired. In this article I present a Light Pen which should cost in components, less than half the price of a commercially available unit, with, in my opinion, a considerably better performance. I have written the article with reference to my own computer, which is an Atari 800, but I have also tried the Light Pen on a VIC20 and a Commodore 64 and it works perfectly.

Method

To explain how a light pen works, you must first have an idea of how the television picture system is generated. A TV picture is basically constructed from a number of lines produced on the phosphor coating on the inside of the screen. The original TV system in this country used 405 lines, but today 625 lines is used. The phosphor on the screen glows when struck by the high speed electrons given off by the hot cathode wire (gun) in the tube. This is focussed by a magnetic field around the tube to produce a single spot of light on the TV screen. A set of electro-magnets called horizontal deflection coils are used to move the spot of light across the screen to produce a horizontal line (X axis). When the spot reaches the right-hand side of the screen, it is deflected back to the left-hand side


for the Atari, VIC20, and Commodore 64



at high speed and during this period the gun is blanked to prevent spurious fly-back lines being generated. A vertical deflection coil is slowly moving the spot down the screen as well so that by the time the spot gets back to the left-hand side again it is slightly below its previous

start position and thus ready to draw a new line. The downward scan (Y axis) continues until all 625 lines have been drawn, at which point the beam is made to return to its top left starting position. This is a highly simplified description; in a real TV set the actual procedure is far more complex.

The Light Pen is designed to detect the spot of light which moves over the screen. The computer has the job of determining the X and Y co-ordinates of the spot as it passes the pen. These values are obtained in an Atari from the internal register set of the 'Antic' display processor. Since the position of the light spot on the screen is directly related to the time it took to get there from the beginning of the first scan position, the hardware can determine X and Y values and store them in two hardware registers.

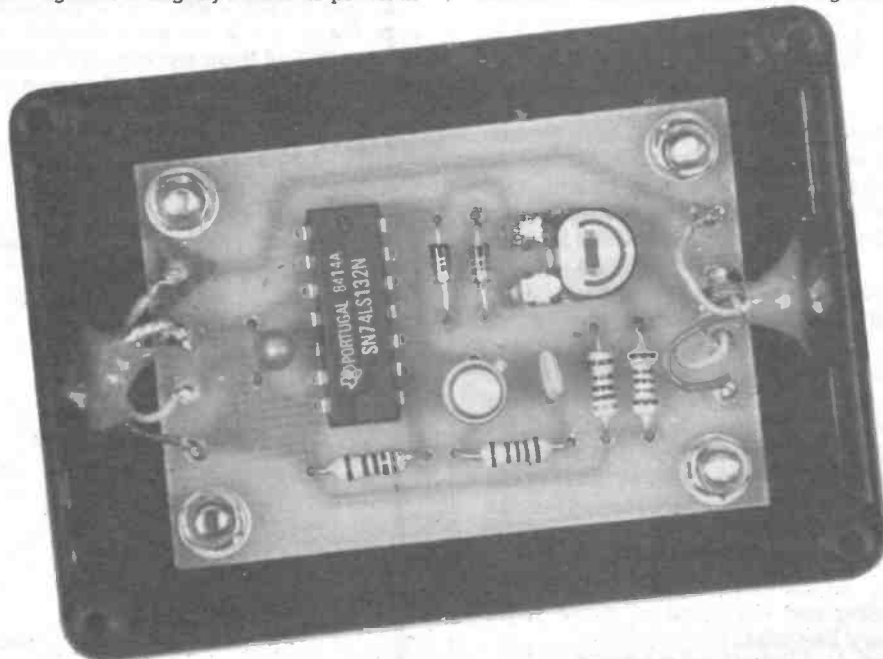

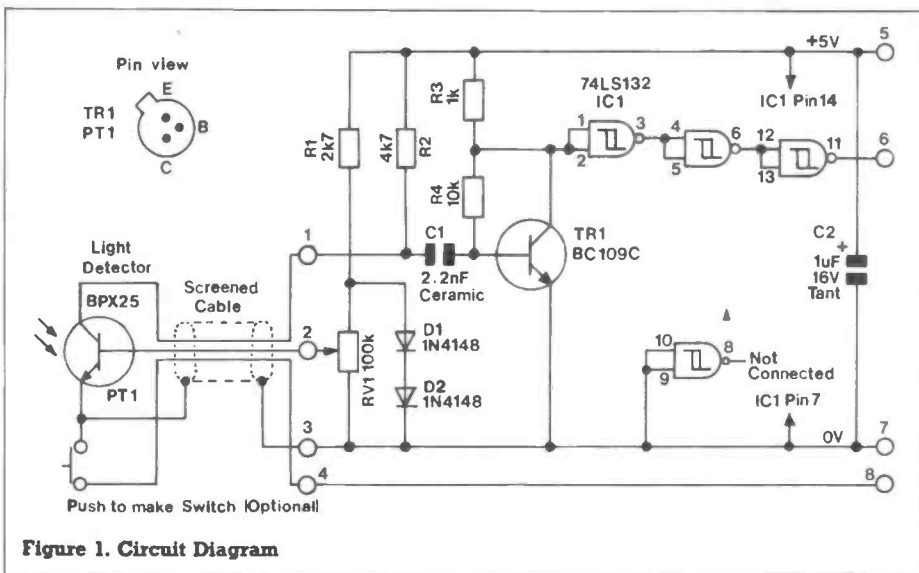


Figure 1. Circuit Diagram

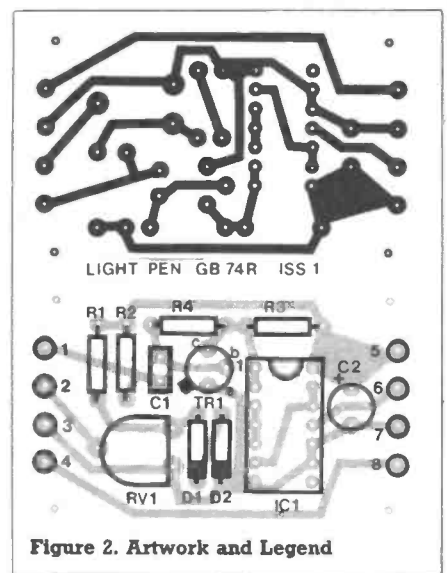


Figure 2. Artwork and Legend

When programming in BASIC, the X and Y values are obtained by PEEKing locations 564 for X and 565 for Y.

The user's software then has to interpret these values in order to obtain screen position related values. The horizontal or X location (564) will return a value of 78 for the extreme left-hand side of the screen, increasing by 1 up to a value of 227. Then something rather strange happens; the value jumps to 0 and then increments to a final value of 8 for the extreme right-hand side. Although this is a problem, it can be allowed for in the software. The vertical or Y location (565) will return a value of 16 for the extreme top of the display, incrementing by 1 to a value of 111 at the extreme bottom of the display. The values stored at these two locations are updated when any of the four joystick trigger inputs are used.

Circuit

As can be seen in the circuit diagram (Figure 1), there are very few components necessary to obtain a working Light Pen. The most important is the light detector. It must have good sensitivity and fast reaction characteristics. The BPX25 phototransistor meets both requirements at a modest cost. This device is equipped with its own built-in optical lens which is made of glass. This point is worth noting, since, if direct contact is made with the glass of the TV screen, scoring may occur. To prevent this, the BPX25 should be recessed into a plastic tube of some description. To obtain maximum sensitivity and operating speed, it is necessary to bias the base of the transistor. The voltage required is quite small, about 0.5V. This voltage is adjustable with the 100k preset (RV1) from 1.2V down to 0V. In practice the

preset wiper position comes out at about half way round its travel. The 1.2V at the top end of the preset is generated by two silicon diodes in series, and forward biased. The current through the diodes is limited by R1 connected to the +5V supply taken from pin 7 of the joystick port (PCB pin 5).


When the phototransistor detects a light pulse, the amount of current flowing through it changes. The current through the device is limited by R2 in the collector. These changes in current cause a voltage change at the collector of the phototransistor. The voltage pulses are then coupled by C1 into the base of a BC109C, TR1. This device performs the necessary voltage amplification to obtain TTL logic levels. The final stage of shaping the pulse is left to IC1, a quad 2-input NAND Schmitt trigger, 74LS132. As can be seen, only three of the four gates are used. The final component in the circuit is C2, a tantalum bead capacitor across the supply rails to remove any spurious noise on the rails. The output of the final gate is fed to pin 6 of the joystick

port. The ground connection is made from PCB pin 7 to pin 8 on the joystick port.

In the prototype, a push-to-make switch was used as the trigger for the Light Pen. The switch was simply connected between pin 1 and pin 8 of the joystick port. The final construction and choice of housing is left to you, but an old Biro or felt-tip pen case is ideal for the pen itself, and the electronics can be housed in a small plastic box. The cable linking the phototransistor to the circuit board must be screened to prevent stray interference pick-up. The prototype used 4-core overall screened cable. Connection to the joystick port is via a standard D-type 9-way connector. Please note that if you have one of the Atari XL range of computers, due to the case moulding around the joystick ports, the standard D-range connector supplied in the kit will not fit and will either have to be modified or a suitable substitute found.

Programs

Included in this article are three very

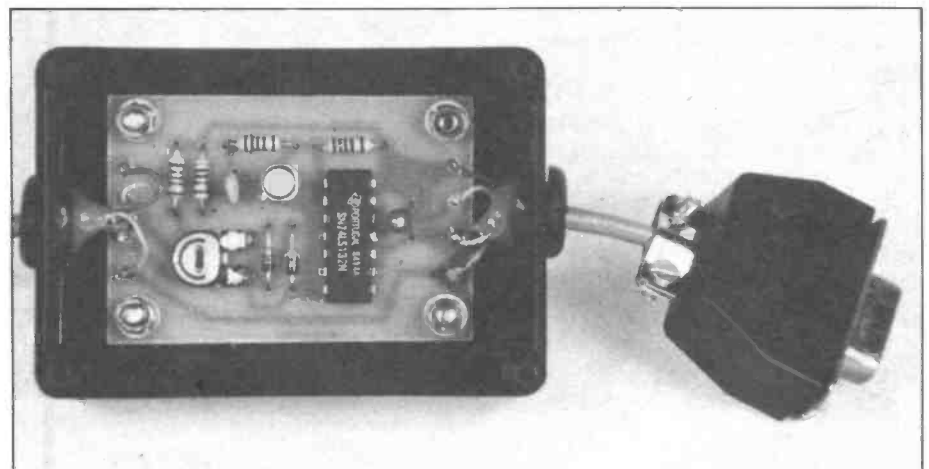

simple programs for the Atari, the first of which is used to set up RV1 in the circuit. In all three programs we have used joystick port 1, because the Light Pen's switch controls the value of STICK (0). However, the Light Pen will work in any of the four joystick ports, except on the 400 where it will only work on port 4, so STICK(3) should be used in the programs in this instance. Program 1 is a simple drawing utility which will produce lines or dots depending on the state of the function keys. Holding Select down will put the drawing program into dot mode and the Option key will clear the screen and reset the starting position to the current pen position. Pressing the Light Pen's own button will produce continuous line drawing. To set a new starting point,

simply place the pen on the screen and press the Select key. To adjust the preset to obtain the correct results simply hold the Light Pen against the screen, press the switch on the Light Pen and move the pen slowly. If the line does not trace the movement, adjust the preset until it does. If you cannot obtain a satisfactory result, try increasing the brightness and contrast controls on your TV. If there is still no response, recheck your soldering and construction.

Program 2 is an example of how a Light Pen can be used for menu-driven software. Position the pen over the number you wish to choose and press the Light Pen switch. If all is well, a tone will be heard and your selection will be shown at the bottom of the screen.

The final program (3) is a very simple musical instrument, in which you can select both volume and pitch. The sound will only be present whilst pressing the Light Pen switch. The display on the screen is a matrix of square dots with volume increasing down the screen and pitch increasing across the screen, right to left.

In conclusion I must point out that the programs shown are by no means good examples of what can be achieved, but are adequate for testing purposes and demonstrating the principles behind Light Pen Software implementation. When writing your own software, you must bear in mind where the screen is dark, no information can be detected by the Light Pen.

Atari Program 1

```
10 GRAPHICS 24:COLOR 1
20 X=PEEK(564):X=X-155+X:IF X<1 THEN X=1
30 Y=PEEK(565):Y=Y-30+Y:IF Y>190 THEN Y=190
40 IF PEEK(53279)=3 THEN GOSUB 80
50 IF PEEK(53279)=5 THEN PLOT X,Y
60 IF STICK(0)<>15 THEN DRAWTO X,Y
70 GOTO 20
80 GRAPHICS 24:COLOR 1
90 PLOT X,Y:RETURN
```

Atari Program 2

```
10 REM MENU
20 GRAPHICS 2+16:SETCOLOR 0,0,12:SETCOLOR 4,4,1
30 PRINT #6;" atari 1"
40 PRINT #6;" atari 2"
50 PRINT #6;" ATARI 3"
60 PRINT #6;" ATARI 4"
70 PRINT #6;" atari 5"
80 PRINT #6;" atari 6"
90 PRINT #6;" ATARI 7"
100 PRINT #6;" ATARI 8"
110 PRINT #6;" atari 9"
120 PRINT #6;" atari 10"
130 IF STICK(0)<>15 THEN 150
140 GOTO 130
150 LET I=PEEK(565)
160 IF I<18 OR I>94 THEN 150
170 IF I=18 OR I=19 OR I=20 OR I=21 OR I=22 THEN
M=1:GOSUB 280
180 IF I=26 OR I=27 OR I=28 OR I=29 OR I=30 THEN
M=2:GOSUB 280
190 IF I=34 OR I=35 OR I=36 OR I=37 OR I=38 THEN
M=3:GOSUB 280
```

```
200 IF I=42 OR I=43 OR I=44 OR I=45 OR I=46 THEN
M=4:GOSUB 280
210 IF I=50 OR I=51 OR I=52 OR I=53 OR I=54 THEN
M=5:GOSUB 280
220 IF I=57 OR I=58 OR I=59 OR I=60 OR I=61 THEN
M=6:GOSUB 280
230 IF I=65 OR I=66 OR I=67 OR I=68 OR I=69 THEN
M=7:GOSUB 280
240 IF I=74 OR I=75 OR I=76 OR I=77 OR I=78 THEN
M=8:GOSUB 280
250 IF I=82 OR I=83 OR I=84 OR I=85 OR I=86 THEN
M=9:GOSUB 280
260 IF I=90 OR I=91 OR I=92 OR I=93 OR I=94 THEN
M=10:GOSUB 280
270 GOTO 130
280 IF MM=M THEN RETURN
290 POSITION 4,11:PRINT #6;" ATARI=";M;" "
300 FOR V=15 TO 0 STEP -1:SOUND 0,M*10,10,V:NEXT
V:LET MM=M:RETURN
```

Atari Program 3

```
10 GRAPHICS 4+16:COLOR 1
20 SETCOLOR 4,2,3:SETCOLOR 0,0,15
30 FOR Y=0 TO 47 STEP 4
40 FOR X=0 TO 70 STEP 4
50 PLOT X,Y
60 NEXT X:NEXT Y
70 IF STICK(0)<>15 THEN 90
80 SOUND 0,0,0,0:GOTO 70
90 SOUND 0,PEEK(564)/3,10,PEEK(565)/10
100 GOTO 70
```

PARTS LIST FOR LIGHT PEN

RESISTORS: All 0.4W 1% Metal Film

R1	2k7	1	(M2K7)
R2	4k7	1	(M4K7)
R3	1k	1	(M1K)
R4	10k	1	(M10K)
RV1	100k Hor Sub-Min Preset	1	(WR61R)

CAPACITORS

C1	2n2 Ceramic	1	(WX72P)
C2	1µF 35V Tantalum	1	(WW60Q)

SEMICONDUCTORS

TR1	BC109C	1	(QB33L)
D1,2	1N4148	2	(QL80B)
IC1	74LS132	1	(YF51P)
PT1	BPX28 Phototransistor	1	(QF30H)

MISCELLANEOUS

Printed Circuit Board	1	(GB74R)
Veropin 2145	1 pkt	(FL24B)
Cable Multi-Core 4-Way	2m	(XR25C)
Verobox 301	1	(LL12N)
D-Range Socket 9-way	1	(RK61R)
D-Range Cover 9-way	1	(RK62S)
Bolt 6BA 1/4inch	1 pkt	(BF08C)
Nut 6BA	1 pkt	(BF18U)
Shakeproof Washer 6BA	1 pkt	(BF26D)
Spacer 6BA 1/4inch	1 pkt	(FW33L)
Grommet Small	2	(FW59P)

A complete kit of parts is available.

Order As **LK51F (Light Pen Kit) Price £10.95**

The Printed Circuit Board in this project is also available separately.
Order As **GB74R Light Pen PCB Price £1.25**

FIRST BASE



by Mike Wharton

A Beginner's Guide To Logic Design.

Part Seven

CMOS Devices

As mentioned in the last article, there is available a range of logic devices based on a different type of technology from that of TTL devices. TTL chips have resulted from developments in bipolar transistors, that is the common or garden type like the ubiquitous BC109 and its ilk. The term bipolar is used to describe the manner in which the electrical current is carried through the transistor, which is by two charge carriers called electrons and 'holes'. The electron we are all familiar with, in a manner of speaking, being the basic particle carrying a unit negative charge; a 'hole', on the other hand, is simply the absence of an electron within the crystal structure of the semi-conductor material. It is really beyond the scope of this series of articles to delve further into the theory of semi-conductor action, but suffice to say that this type of device has certain electrical features which have been used to advantage in TTL devices.

Many readers will be quite aware that besides bipolar transistors there are the so-called FET's or Field Effect Transistors. In these devices the charge is carried only by electrons, there being no involvement with 'holes'. FET's have been developed along different lines to give several families, from Junction Gate FET's, (JUGFET's) to Insulated Gate FET's, (IGFET's). A widely used member of this last family is the MOSFET, or Metal Oxide Semi-conductor FET, and it is distantly related cousins of these that form the basis of the Complementary Metal Oxide Semi-conductor, or CMOS, logic devices. Figure 1 shows how CMOS transistors are fabricated on the surface of a silicon chip, whilst Figures 2a and 2b give an indication of the internal circuitry of typical CMOS and TTL devices.

As mentioned last time, there are a variety of advantages and disadvantages associated with both kinds of device, but it seems that many of the disadvantages with the CMOS variety are rapidly being overcome and they are poised to become

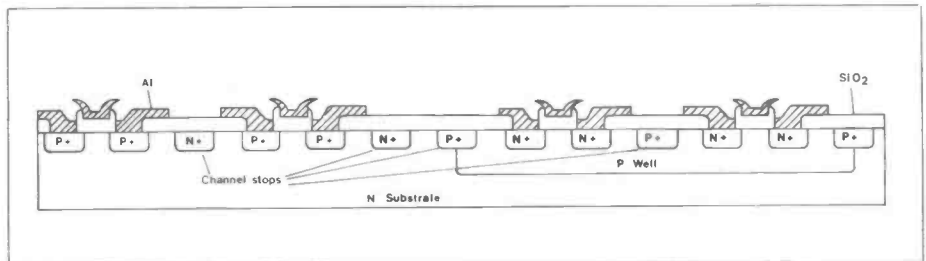


Figure 1. Conventional Metal Gate CMOS Structure.

the major type of logic element. Briefly, their most serious problem has been the low speed of operation as compared with TTL devices, but this may be off-set by their much reduced power consumption and wider operating voltage. For CMOS devices the supply positive is connected to V_{DD} (drain voltage), and supply negative to V_{SS} (source voltage). The negative is connected to source since it can be regarded as the 'source' of negatively charged electrons. Practically all CMOS devices will tolerate a range of supply voltages from 3 to 15 volts, and hence may be operated quite happily from a standard TTL supply of 5 volts. If any difficulties are experienced, though, then it may be necessary to increase the supply to 9 volts or so.

Many of the logic elements available in TTL have direct equivalents in CMOS, indeed, some are even pin compatible replacements. A glance through the appropriate pages of the Maplin catalogue will give a very good idea of the range of devices commonly available along with their respective pinouts. Pretty well all of the circuits given so far in this series can be implemented using CMOS devices, and Figure 3 shows one of the earlier ideas but using a CMOS chip, the 4520. Because of the larger scales of integration possible with CMOS, this actually contains two four-bit binary counters within the 16-pin package, and the internal arrangement is a little different from the 7493 which was used in the original design.

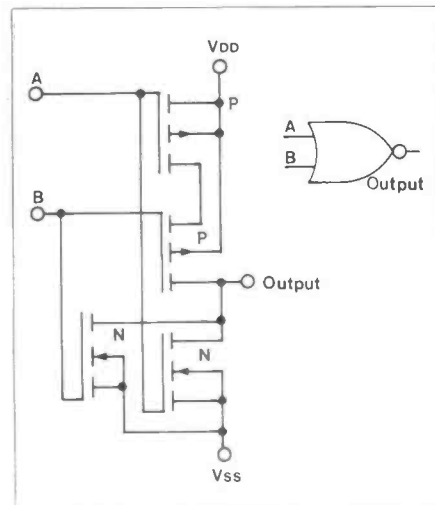


Figure 2a. CMOS 2-input NOR Gate.

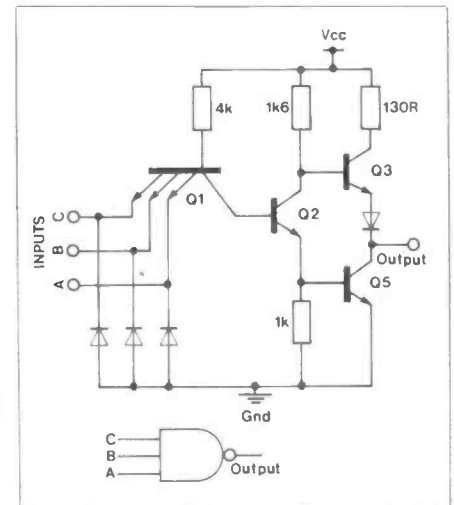


Figure 2b. TTL 3-input NAND Gate.

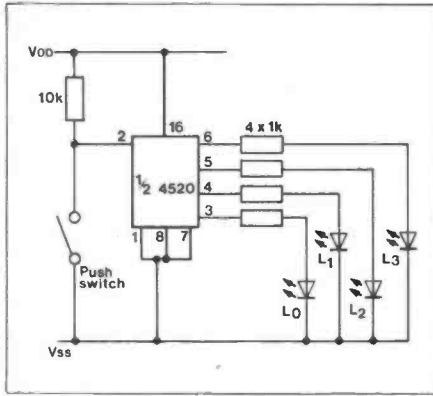


Figure 3. 4520 Dual 4-bit Binary Counter.

Beware of Static!

This point is perhaps a convenient one at which to mention one of the problems of using CMOS devices which is never encountered with TTL, that of sensitivity to static discharges. One may inadvertently destroy a CMOS device by careless handling even before it is put into the circuit. The reason for this is due to the nature of the input to this type of device; the layer of insulating silicon dioxide, shown in Figure 1, is extremely thin, typically only a few microns thick. It is very easy to generate high static charges due to friction; for example by walking across a synthetic fibre carpet in rubber-soled shoes it is possible to produce a charge of 10,000 volts. Normally this would quickly leak away, but if applied to a CMOS chip then the thin oxide layer will break down and the device is effectively destroyed. Most of the devices produced nowadays have some form of protection against static discharge, usually in the form of internal zener diodes. However, the protection is not completely effective, and some care needs to be taken. The usual advice is to work on an earthed metal tray with all manner of other anti-static precautions, but for the common logic devices this is not really necessary. Provided you avoid touching the pins when handling them and resist the temptation to polish them up on your woolly jumper, no 'dead' chips should be produced. Also, it is a good idea to store them in their anti-static tubes or with the pins pushed into polystyrene foam which has been covered with aluminium cooking foil, so that the pins are all effectively shorted together.

One word of caution, don't adopt too much of a cavalier attitude to them or you might be tempted to treat a microprocessor in the same way, with expensive results!

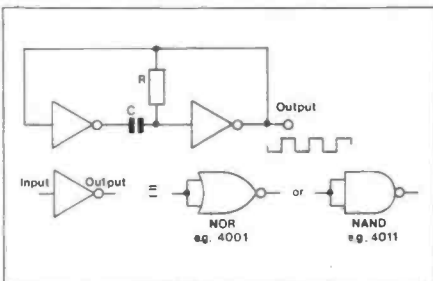


Figure 4. CMOS Astable Formed by 2 Inverters.

CMOS Logic Gates

One very useful effect of the insulated gate construction of these devices and its associated high input resistance is that some 'tricks' are feasible which would be difficult or impossible with TTL gates. For example, Figure 4 shows how a simple square wave oscillator, or astable flip-flop, may be obtained from just two gates. The frequency of operation is set by the values of capacitor and resistor chosen, but the exact frequency will be determined to some extent by the gate input characteristics, which will vary slightly from device to device. The approximate frequency of operation is found from the empirical formula:—

$$f = 0.6 / C \times R$$

where frequency, f , is in Hertz, capacitance is in Farads and resistance is in ohms and with an upper frequency set by the natural limitations of these devices. Similarly, Figure 5 shows a monostable flip-flop made up from two gates; due to the high input resistance long time constants can be achieved by the use of relatively small value capacitors in conjunction with large resistors. The period of this type of monostable is given by another form of the above expression:—

$$t = 0.6 \times C \times R$$

where C and R are as before and t is the period in seconds.

A third type of flip-flop is shown in Figure 6. This is the bistable flip-flop, which is so called because it can adopt either of two stable states, and a suitable trigger pulse can flip it from one state to the other, where it remains until it is triggered to flop back.

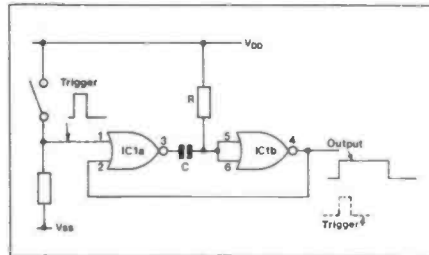


Figure 5. Monostable Formed by Two 2-input NOR Gates.

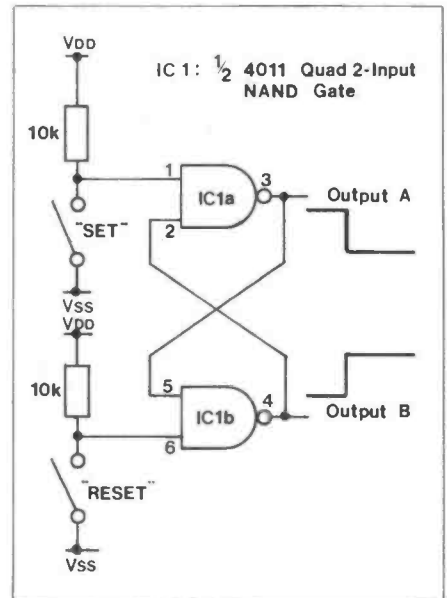


Figure 6. Bistable Formed by Two 2-input NAND Gates.

CMOS Counters

Some of the above ideas are brought together in Figure 7. If you have been following the series you should have some idea as to the function of the circuit, which is a simple timer to count up to 59 seconds and then reset to 00. The clock pulses are obtained from an astable flip-flop which has a period of about one second. Because of the simple nature of this part of the design the overall accuracy of the timer will not be very good; a much more accurate method of generating clock pulses will be discussed in a future article. The clock pulses are fed into one half of a 4518 binary coded decimal (BCD) counter. The outputs from this counter are then used to operate a 4511 BCD to seven segment decoder/driver for the 'units' LED display. The output from the most significant bit (MSB) of the first half of the 4518 is then used as the clock input to the second half of the counter, which produces the required output for the 'tens', via the second 4511 and LED display. The extra

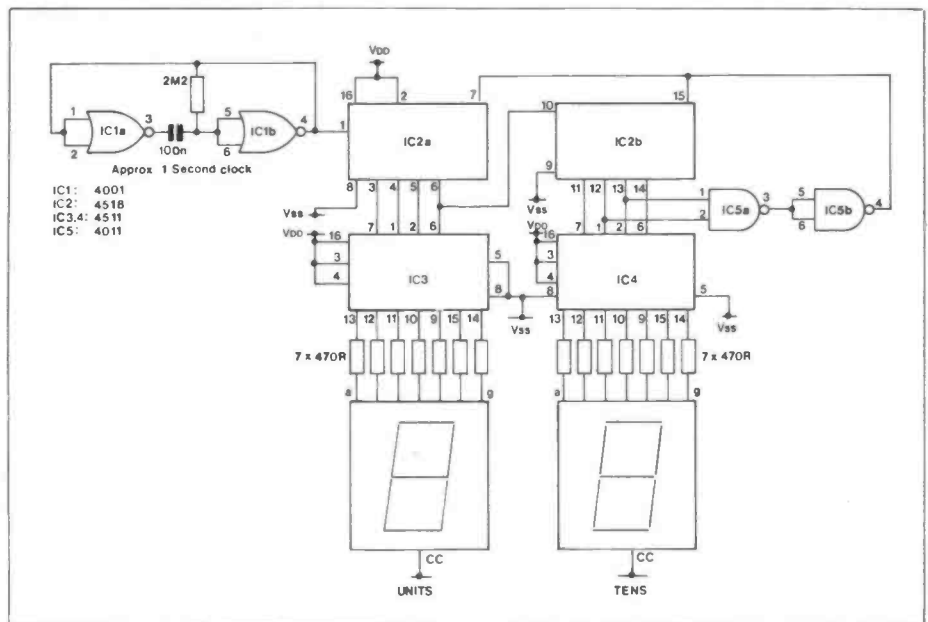


Figure 7. Simple Seconds Timer.

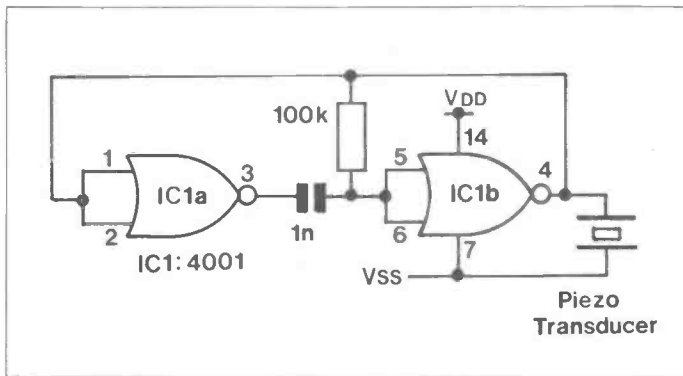


Figure 8. Astable used to operate a Piezo-Electric Sounder.

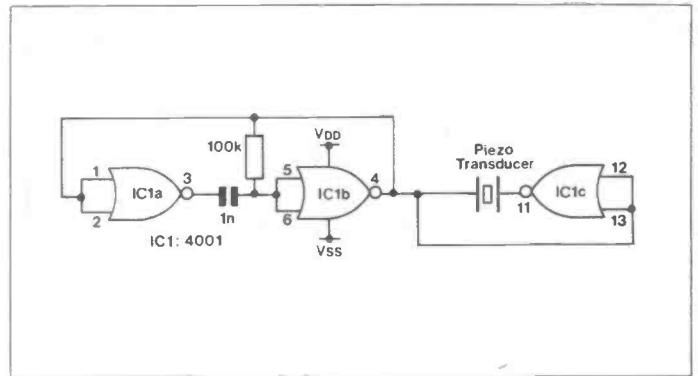


Figure 9. Circuit for Increased Output.

gating of IC5a and IC5b is to detect the presence of the value '6' on the output from the second counter, since it is desired only to count up to 59 and then reset to zero. The method of achieving this is to connect both the '4' and the '2' output lines to the inputs of a two-input AND gate, since the value of '6' is present when '4' AND '2' are both at logic 1. You may well be wondering, then, why two NAND gates are shown in the diagram. This is simply to avoid purchasing a chip containing AND gates when the job can be done with the more versatile NAND gates. The two NAND gates connected as shown, of course, produce an AND gate, as reference to previous Truth Tables will reveal.

The output from the AND gate is then fed to the Reset pins on both counters, so that counting is forced to re-commence from zero. Actually, a figure 6 will appear on the display, but only for the time it takes for the reset signal to be gated through the decoder and counter, which is of the order of a few nano-seconds, so you are unlikely to see it! Of course, it is possible to detect other values, so that instead of counting minutes some other number is counted. Without any reset logic, i.e. with the Reset pins connected permanently to Ground (or Vss), the circuit will count up to 99 before cycling round to zero again. The reader is left to experiment for himself, the only requirement being to AND all the unique values of the next highest count together to the Reset pins. For example, if it were desired to display the value '60', then 61 would need to be detected by ANDing '4' and '2' from the tens counter, along with '1' from the units counter. This could be achieved with a three-input AND gate or more conveniently with an equivalent array composed of two-input NAND gates. This kind of decoding can be done with this counter since it is of the synchronous type, described in the last article.

Jeepers Bleepers!

Returning to the simple oscillators made up from a couple of CMOS gates, and incorporating some of the ideas outlined above, brings us to the final portion of this issue's logic feast.

Although the output stages of CMOS gates are unable to drive even a small loudspeaker directly, they are ideal for operating the small piezo-electric sounders for producing an audible note. The

type shown on page 421 of the current Maplin catalogue, order code QY13P, is the kind to use. It requires some care in soldering on a couple of connecting wires, but has the advantage of being cheap. Figure 8 shows a circuit which has an output of around 1kHz, which may be used to test the transducer. The audio output can be increased by the use of an extra gate, as indicated in Figure 9, but even then it will not be rock-crushing! By employing another set of gates operating at a much lower frequency it is possible to control the audio oscillator to produce a pulsating tone, as shown in Figure 10. Developing this idea further, it is then possible to control this circuit with yet another one, this time a monostable with a period of, say, 5 seconds. When initiated, the circuit of Figure 11 will produce a pulsed tone for this duration, and could be used as an audible warning device. Finally, Figure 12 shows how this last idea can be added to the simple timer outlined above, so that a warning note is sounded when a particular time is reached on the counters, in this case at every minute mark.

If you have a requirement for a simple timer of this nature, then the design could well be made up into a more permanent form, rather than being left as a breadboard experiment. In such a case it would be better if the features of the design were more versatile; for example, if the 'alarm time' could be set to any value over a wider range of times, to produce a high technology egg-timer! You may have some idea as to how this might be achieved, but the next article will include a suitable design, as well as probing deeper into the use of other interesting CMOS devices.

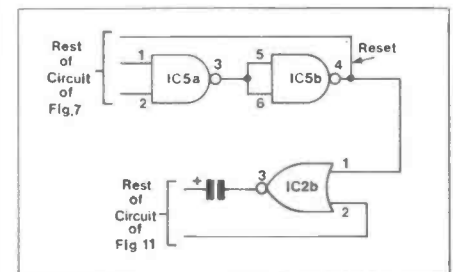


Figure 12. Reset Pulse used to Trigger Monostable for Audible Warning Device.

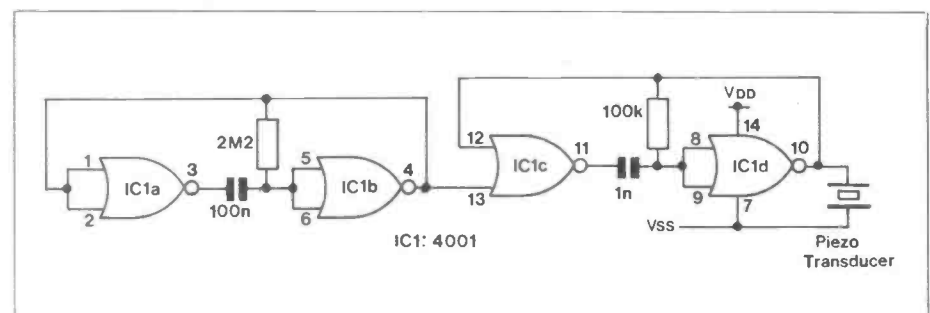


Figure 10. Gated Astable to produce Pulsating Tone.


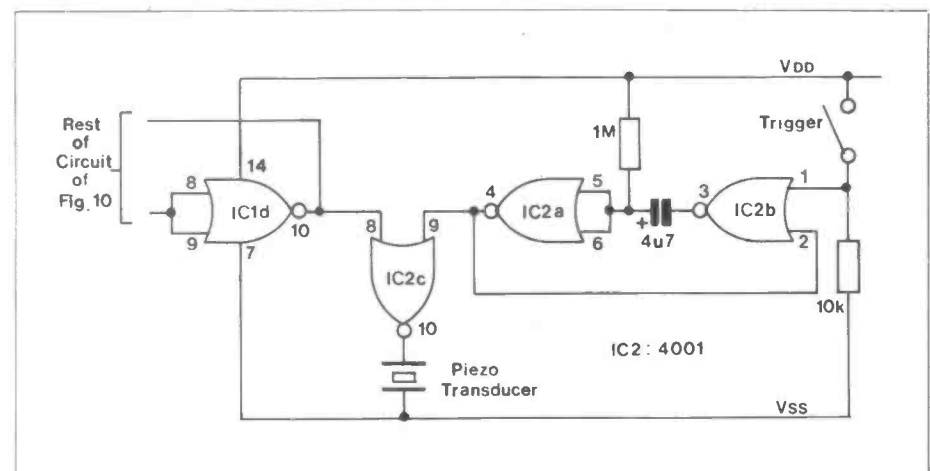


Figure 11. Monostable used to Gate Pulsed Astable.

PWM MOTOR DRIVE MODULE

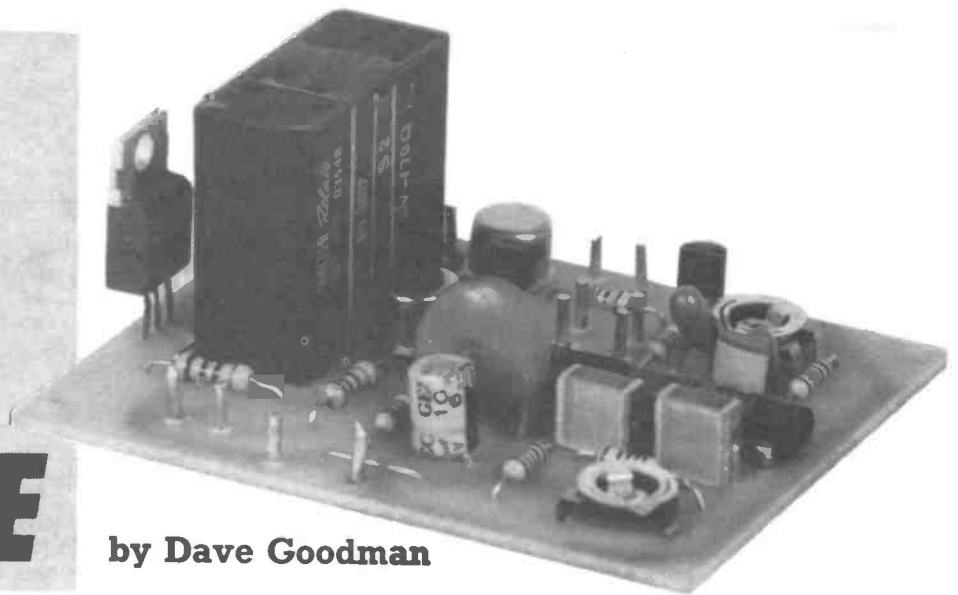

by Dave Goodman

- ★ 6 - 12V Forward and Reverse Model Motor Driver
- ★ Proportional Control Offers Smooth Transition from Off to Full Speed
- ★ Ideal for Model Boats, Cars and Robotics

Following on from the previous issues PWM Servo Driver, this model speed controller will drive low voltage electric motors from a suitably encoded pulse width modulated signal. Both 6V and 12V systems are catered for by the output drive circuitry which will handle motor stall currents up to 5 amps, while the front end decoding section connects separately to a low voltage 4.8 - 6V supply obtainable from radio control Rx battery packs for instance. Although primarily intended for Radio Control model use, the project also finds application in Robotics projects where computer control of movement and direction is required.

Proportional Control

Unlike servo's, the speed controller does not require positional feedback information. Essentially all that is required to start and stop an electric motor is to apply then disconnect power via a switch, and toggling the switch will alternately increase then decrease the speed at which the motor is running. If the switch could be held closed for a set time period and then held open for the same time, so that its MARK (closed) to SPACE (open) ratio becomes even, then the motor would be expected to run at approximately half power allowing for over-run and starting losses.

Lengthening the switch make time and reducing the switch break time repeatedly will therefore mean that power is applied for longer periods and the motor will increase its speed accordingly. Conversely, reducing the switch make time and lengthening the break time will slow the motor. This principle is applied in PWM systems as shown in Figure 7.

The repetition rate, or switch on and switch off cycle, is standardised at 20ms and each complete cycle is called a Frame. The reciprocal value from this ($1 \div 0.02$) produces the Frame Rate and is

50 frames per second. During each 20ms frame cycle the positive going pulse can be increased from a minimum width of 0.2/0.5ms, up to a maximum width of 2.0/2.5ms, the latter corresponding to maximum speed and the former to minimum. Obviously, manually operating a switch in the motor supply line at 50 times a second is slightly impractical and use of electronic switching IC's becomes desirable.

Circuit Description

In Figure 1, IC1 is a linear pulse width amplifier and expands the incoming signal at pin 14 into a pulse train whose MARK/SPACE ratio can be varied between zero (0V) and one (+V). Preset RV2 and C4 set the internal monostable timing period and input pulses less than or greater than this period determine motor speed. Because both forward and reverse drive are necessary, a 'no drive' or zero position is required and RV2 can be adjusted to determine this. RV1 sets the 'dead band' area, or the relationship between motor speed and control 'stick' movement. Along with the pulse expansion component, C3, this preset can be

adjusted for maximum speed and zero positions. IC1 pin 4 output determines motor direction and has a high (+V) output in one direction and a low (0V) output in the other.

One of two links A or B are inserted for operating RLA via TR1, TR2, and IC2b or IC2c, and are fitted according to the required direction of rotation of the motor armature. Pins 5 and 9 are NANDed by IC2a and produce a positive pulse train which switches TR3, TR4 and TR5. Either pin 5 or pin 9 is active, but not both together, and each signal is complementary to the other depending on forward or reverse direction signals. TR5 must be capable of switching high currents to the motor and R10 will supply drive signals to external NPN transistors if larger current handling becomes necessary (pin 10). Pin 4 output is either high or low with a selected direction and could be buffered for reversing-lights on a model car for example. Both relay contacts reverse connections to the motor when operated by RLA from IC1 pin 4, so that the same drive signal at TR5

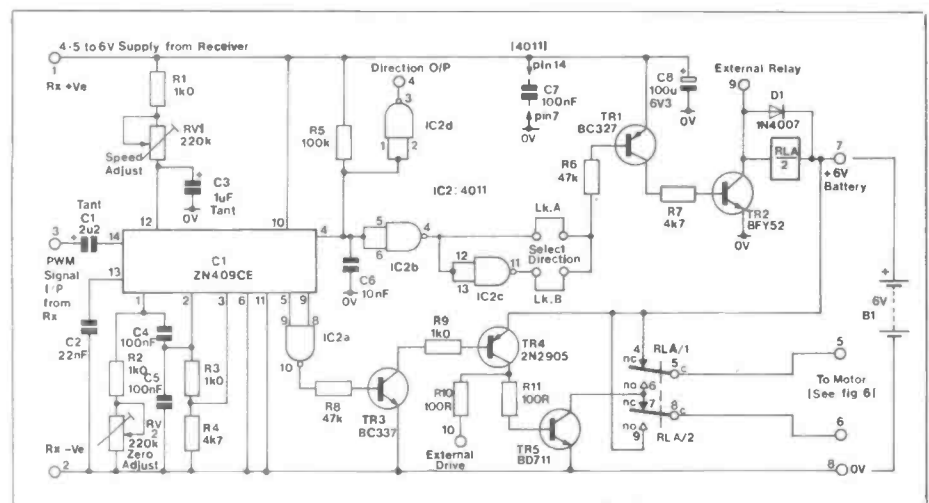


Figure 1. Circuit Diagram

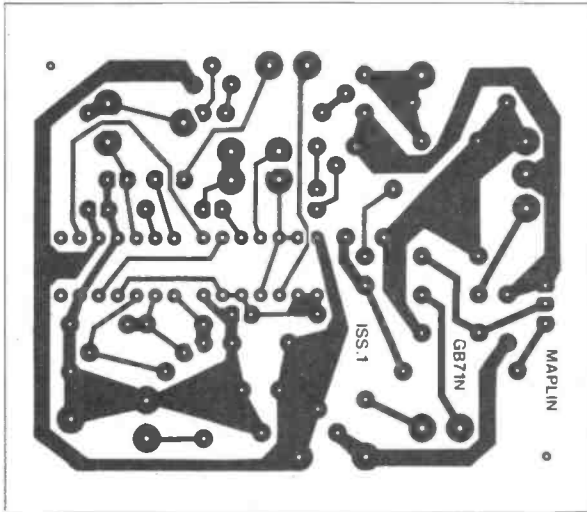


Figure 2. Artwork

collector is available for both forward and reverse modes. Output pin 9 may be connected to an externally mounted relay if larger current switching is required.

Construction

Two links are initially required to be inserted directly into the PCB and are best formed from 24swg tinned copper wire. Excess lengths removed from resistor leads could be utilised for this. Next fit R1 to R9 and standard resistors R10 and R11 followed by D1, which must be correctly aligned as per the PCB legend. It may be convenient at this stage to solder these components and cut off excess leads, thus avoiding the inevitable jungle that would otherwise result.

Fit the fourteen Veropins from the track side and push the heads down to the respective pads with a soldering iron and apply solder. Fit both presets RV1, RV2 and IC1, IC2. Be sure to fit IC's correctly by aligning the end notch with the legend otherwise they will be damaged in use and are not easy to remove after soldering! Fit all capacitors and note that C1 and C3 are polarised and must be fitted correctly with the +V markings in line. Polycarbonate capacitors C4 and C5 can have their terminals broken quite easily, so exercise care when fitting both to the PCB. Again, solder all components in place, remove surplus wires and fit RLA, which can only be inserted in one position.

The parts list offers both 6 volt and 12 volt versions for the relay and is a matter of choice to suit individual requirements, but note that only the 6V version is supplied in the kit. Next, mount the five transistors. TR5 is positioned with its mounting bracket facing outwards, away from the PCB and the plastic body facing inward towards RLA. Later on, it may be necessary to heatsink TR5, so ensure reasonable length leads between the PCB and bottom of TR5. This will allow it to be manoeuvred over the edge of the PCB for easier mounting.

Finally, solder all remaining components, clean the track surface with solvent, to remove flux and solder splashes, and inspect the work. When satisfied that all is correct, proceed with testing the module. It is worth pointing

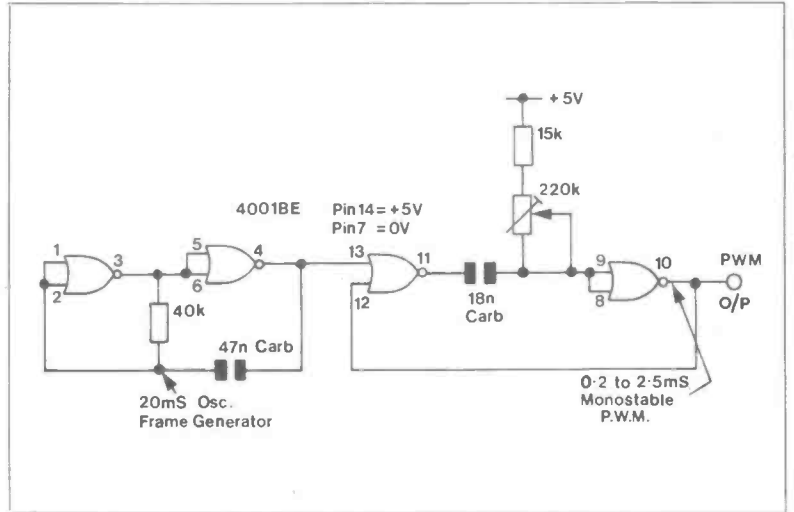


Figure 3. Test Circuit

out that many problems develop from incorrect component recognition, poor soldering and messy track surfaces. Always carefully inspect and re-check parts for mistakes before applying power and this will ensure that any problems can be rectified before damage occurs.

Testing

Initial checks concern voltage and current measurements, and a multimeter is the minimum item of test equipment that should be available. Refer to Figure 4 connections diagram. Connect a 5V supply with -V to Pin 2 on the PCB, and +V to the + lead of a multimeter. Set the meter to measure DC current (100mA), connect its negative lead to Pin 1, and turn on the power. Set RV1 wiper to approx. 7 o'clock and RV2 wiper to approx. 11 o'clock as depicted by the arrows in Figure 4. A current reading of 5 - 6mA should be seen on the meter.

Remove power and meter, reconnect the supply +V to Pin 1 on the PCB and connect the meter with +V lead to Pin 1 and -V lead to Pin 7. Re-apply power and check the meter for a zero reading. Temporarily connect Link A and listen for a click in the relay. The meter should read approx. 10mA when using the 12V relay, or 55 - 60mA when using the 6V relay. Remove Link A. The meter should drop to zero and the relay should click as it releases. These checks should give an indication that the module is basically functioning, providing the above figures correspond to within a few percent.

With the absence of a suitable +V pulse PWM system, such as a radio control Tx and Rx, a simple CMOS test circuit is shown in Figure 3. This too requires a 5V supply and serves as a 20ms frame generator and variable monostable. Please note that the Figure 3

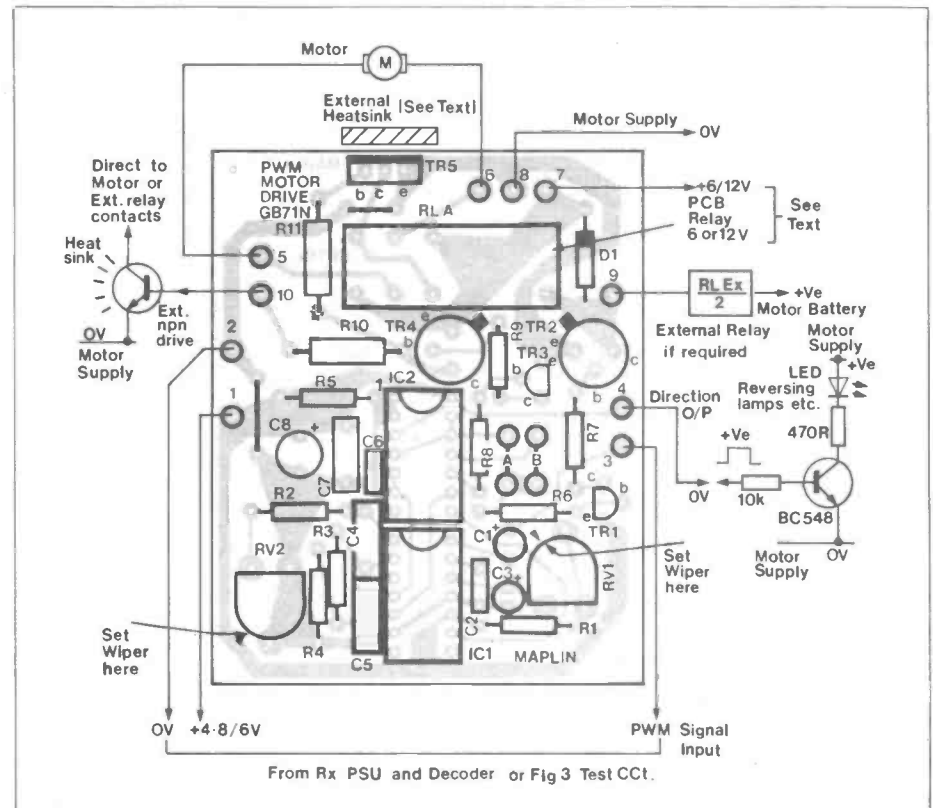


Figure 4. PCB Wiring & Legend

circuit is not a project or kit and exists solely as a guide to assist with testing the module. Whatever system is used, connect the PWM O/P to Pin 3 on the module, and ensure a signal return path exists along Pin 2 (0V) connection. Figure 8 can be used for reference. Fit Link B only onto the module and apply both low and high power supplies as shown.

It is certainly not advisable to take the motor supply +V from module input or receiver supplies, as large current surges will affect both, causing glitching at least, or battery failure at worst. In use, low power Nicads (4.8 - 6V) are perfectly adequate for the input supply, but larger battery packs (if used) will need to be either high power Nicads or Lead Acid/Cadmium varieties for driving the motor. Remember to choose the motor supply voltage to suit both relay and motor ratings (6 - 12V). Do not connect the motor just yet, but switch on all supplies. Adjust either the appropriate transmitter stick, or preset (in the case of Figure 3) from centre zero, which should correspond to an approximate 1.5ms frame pulse down to 0.5ms, whereupon the relay should operate with a click. Reverse stick or preset back through zero in the opposite direction, and the relay will release. When using Link A instead of Link B the relay will normally be in the operated state at first, and release during the test; this being the opposite condition. So Link A holds the relay operated for release mode and Link B holds the relay released for operate mode. In either case, connect a voltmeter adjusted to read 10 - 20V between 0V and PCB pin 4. The reading should be normal at 0V and +5V when moving the stick (pot!).

Connect a motor to PCB pins 5 and 6, and again with all supplies connected ensure full forward, zero and full reverse conditions can be established by varying the control stick or pot. It may be found necessary to re-adjust RV1 and RV2 on the module to ensure these conditions are met with a wide zero or motor off position, therefore trial and error settings will indicate optimum performance for your particular system.

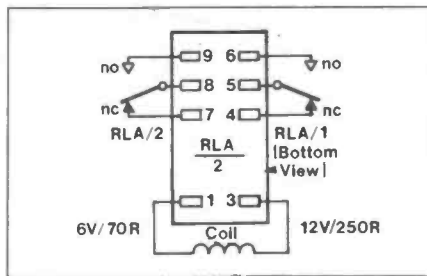


Figure 5. Relay Pinouts

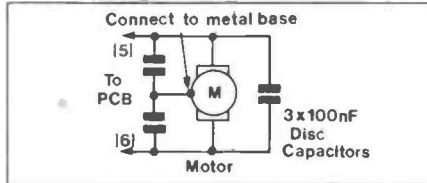


Figure 6. Motor Suppression

Motors

Owing to the wide variety of motors and applications that could be used, it would be best to examine the limitations of the module rather than discuss individual requirements. For instance, Bullet type motors used with large model aircraft can draw 30 Amps or more and relays, drive transistors and PCB tracks must be capable of handling this for long periods. On the module, RLA can comfortably switch 5 Amps although TR5 will dissipate large amounts of power, especially under low speed or stall conditions, so without extra relays and drive transistors fitted, smaller motors of 1 to 2 Amps only should be used. As explained previously, Pin 10 can supply a further three or four NPN power transistors, and Pin 9 a second relay, should it be required to drive larger motors. Simply connect the transistor's emitter to Pin 8, base to Pin 10, and collector to

collector of TR5: in other words in parallel with TR5. Figure 6 offers a simple suppression circuit which should prove adequate for most motors without adversely affecting performance too much. Excessive capacitive loading will affect the pulse waveform at low speeds, so bear this in mind when using suppression.

Heatsinks

TR5 may tend to run hot under heavy load conditions and heatsinking will have to be used to prevent damage or loss of power. Any method used will depend entirely on the space available, and the weight allowance within the model. Model boats generally have plenty of space and buoyancy, and a large heatsink may add ballast for stability. One eighth and half scale cars often have a metal chassis and this could be utilised for heatsinking, but plastic kits may melt around TR5 or its heatsink, so allow plenty of airflow to keep temperatures down.

In conclusion, always keep batteries for the motor drive supply and logic drive separate; only use low power 1 - 2 Amp motors unless adding further power transistors; ensure adequate heatsinking and ensure all supplies are switched off after use.

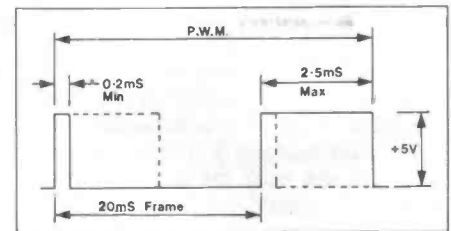


Figure 7. Control Waveform

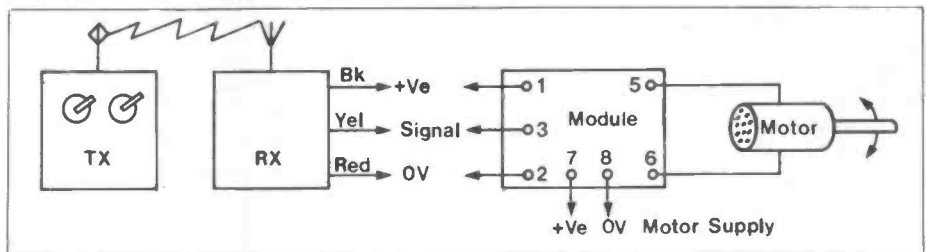


Figure 8. Block Diagram

PWM MOTOR DRIVE PARTS LIST

RESISTORS: All 0.4W 1% Metal Film unless stated.

R1-3,9	1k	4	(M1K)
R4,7	4k7	2	(M4K7)
R8	100k	1	(M100K)
R6,8	47k	2	(M47K)
R10,11	100Ω ½W 5% Carbon Film	2	(S100R)
RV1,2	220k Hor Sub-Min Preset	2	(WR62S)

CAPACITORS

C1	2μF 35V Tantalum	1	(WW62S)
C2	22nF Ceramic	1	(WX78K)
C3	1μF 35V Tantalum	1	(WW60Q)
C4,5	100nF Polycarbonate	2	(WW41U)
C6	10nF Ceramic	1	(WX77J)
C7	100nF Disc	1	(BX03D)
C8	100μF 6.3V Minelect	1	(RK50E)

SEMICONDUCTORS

D1	1N4007	1	(QL79L)
TR1	BC327	1	(QB66W)
TR2	BFY52	1	(QF29G)
TR3	BC337	1	(QB68Y)

TR4	2N2905	1	(QR17T)
TR5	BD711	1	(WH15R)
IC1	ZN419CE	1	(YH92A)
IC2	4011BE	1	(QX05F)

MISCELLANEOUS


RLA	Min DPDT 6A 6V Relay	1	(FJ42V)
	Printed Circuit Board	1	(GB71N)
	Veropin 2141	1 pkt	(FL21X)

OPTIONAL

Ca,b,c	100nF Disc	3	(BX03D)
	Min DPDT 6A 12V Relay	1	(FJ43W)

A complete kit of parts (excluding Optional Items) is available.
Order As **LK54J (PWM Motor Drive Kit) Price £9.50**

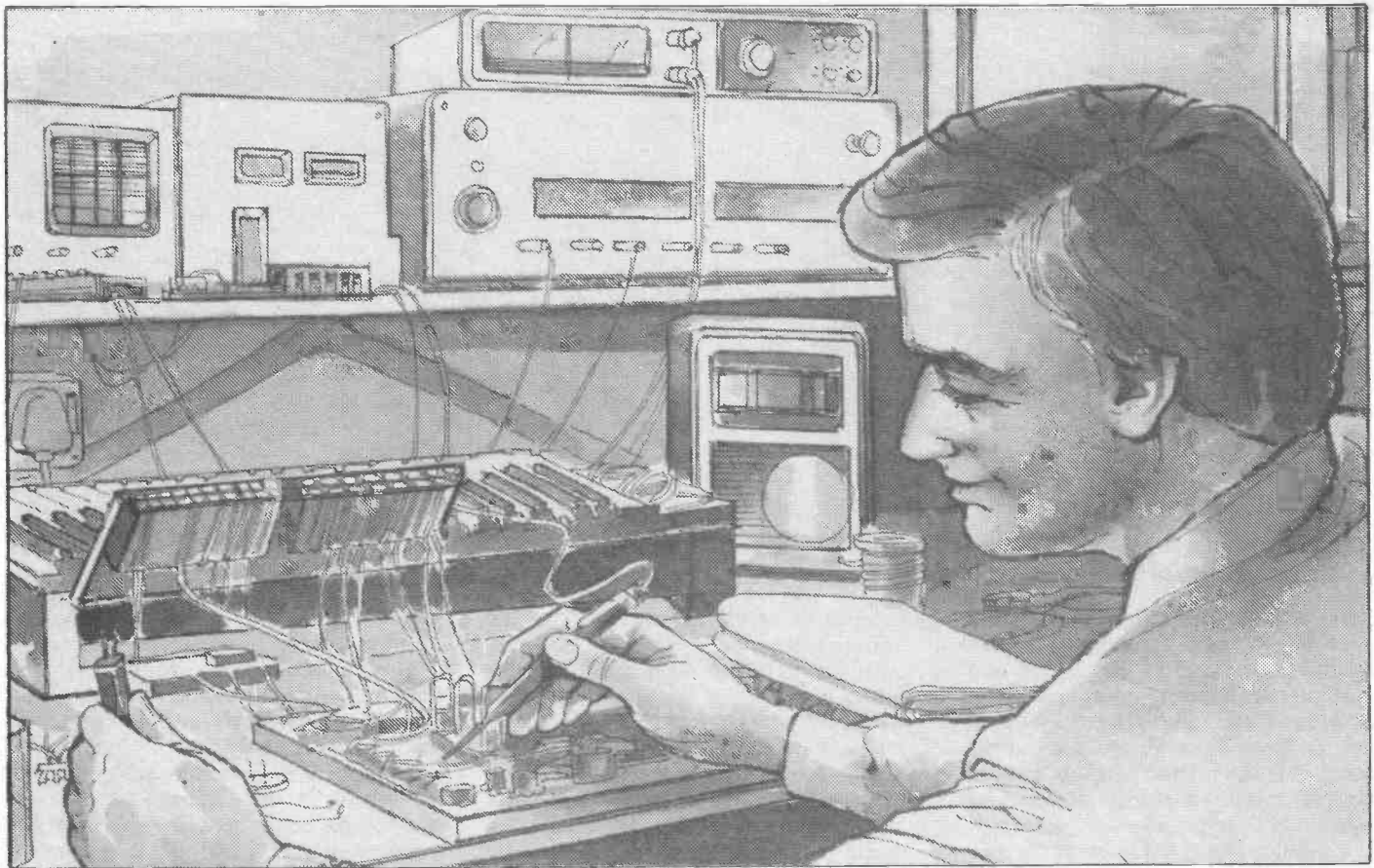The following parts used in this project are also available separately but are not included in our current catalogue.
FJ42V Min DPDT 6A 6V Relay Price £2.98
FJ43W Min DPDT 6A 12V Relay Price £2.98
GB71N Printed Circuit Board Price £1.75



PROJECT FAULT FINDING

by Robert Penfold Part One

Although the constructional information provided in electronics magazines and books is generally very concise and easy to follow, probably every electronics constructor is sooner or later faced with the problem of a newly constructed project that fails to work properly. Most projects these days (including virtually all the Maplin projects) are based on a custom printed circuit board, and these certainly help to greatly reduce the likelihood of a new project failing. However, they are not as 'foolproof' as many people seem to imagine, and do not eliminate the problem.

Ideally when fault-finding on a project one should understand the precise way in which each stage operates, and should have the necessary test equipment to methodically check each stage until the fault is located. Looking at things realistically, probably few constructors are in a position to undertake fault-finding in this way. However, even with the aid of little or no test equipment it should in most cases be possible to locate the fault. This is due to the fact that

the majority of newly constructed projects that fail to operate do so because of an error in construction rather than a design error or a faulty component. At one time there was no shortage of genuine 'duds' in circulation, but at present it is very rare indeed for faulty components to slip through the battery of tests at the factory, or for unscrupulous dealers to sell faulty components as tested and operational components. Of course, it is not advisable to use untested components obtained cheaply unless you have the facilities to test them for yourself and discard any that fail to reach a suitable standard. All Maplin supplied components are of good quality and from reputable manufacturers.


With modern semiconductors it is possible to design repeatable projects that do not require a lot of experimentation with component values before they will operate properly. If a project fails to work properly first time it is only human nature to think that it is due to someone else's mistake, but this really is unlikely to be the case. Those who have checked

faulty projects invariably find that more than nine times out of ten the problem is due to something like a component not fitted correctly, or a badly soldered joint.


Checking

The inference of this is clear: if you construct a project and it does not work, the chances are very much in favour of it being possible to discover the error and rectify the fault without resorting to any test equipment at all. The first job is to read the description of the project thoroughly to make quite sure that you are using the unit correctly, and have not misunderstood something. This may seem a silly point, but as projects become increasingly complex and difficult to understand, the faulty project that isn't becomes less rare. Pay particular attention to any setting up or adjustment instructions, as this is where difficulties and misunderstandings are most likely to occur.

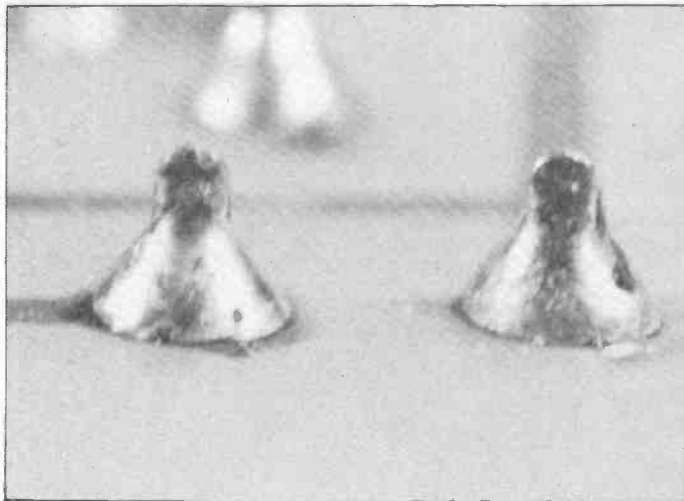The next step is simply to check the unit against the construction diagrams to ascertain that there are no discrepancies



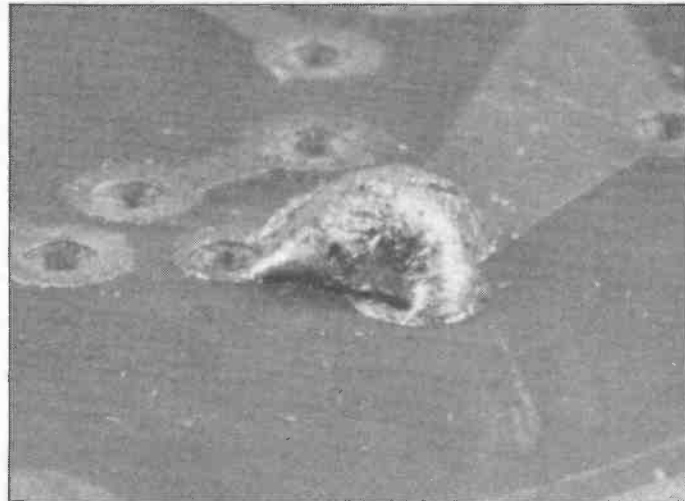The correct appearance for soldered joints.



A joint of dubious quality.

here. In particular check that components which must fit onto the printed circuit board the right way round (e.g. most semiconductors, and polarised capacitors) are indeed fitted correctly. Few projects have all the components mounted on the printed circuit board, and it is easy to make a mistake in the wiring to off-board components such as switches, potentiometers, and sockets. There is a lot to be said in favour of using connecting wires of different colours or multicoloured ribbon cable when wiring up projects, since errors are then less likely, and any that do occur are easily spotted.

If a thorough check of the wiring etc. fails to show up the cause of the problem it is still quite likely that the fault is due to a mechanical problem of some kind, rather than a faulty component or design fault. With a project constructed on stripboard a common problem is that of minute blobs of excess solder producing short circuits between adjacent copper strips. With printed circuit boards the copper tracks are mostly much more spaced out, and this is a less common problem. It is not one that can be totally ignored though, and with most printed circuit boards there are areas of the board where the track spacing is minimal. This occurs principally around DIL integrated circuits.

The offending pieces of solder might be easy to spot with the naked eye, but often they are very small and difficult to spot. They can also be hidden under excess flux, of which there is usually no shortage on a completed printed circuit board. It is advisable to use a de-greasing solvent to remove any excess flux from the board prior to making a careful inspection of the underside of the board. Alternatively, a continuity tester can be used to check for short circuits between closely spaced printed circuit tracks, and this is the only certain way of finding any accidental short circuits.

With modern components and solders there is usually no difficulty in producing neat and effective soldered joints. Even so, 'dry' joints are not totally a thing of the past, and these inevitably occur from time to time. It can easily happen, for example, if a lot of flux is

allowed to build up on the bit of the soldering iron, or if joints are made by using the bit to transfer solder to the joint rather than adding the bit and then the solder to the joint. It is often possible to find a 'dry' joint simply by looking at the board. A good connection should look like the illustration of Figure 1(a), but a 'dry' joint usually looks more like the shape in Figure 1(b). There is often a lot of excess flux around the joint as well. In fact the flux is often all that holds the board, solder, and leadout wire together.

With a fresh soldered joint the solder should have a shiny surface. A dark and dull surface to the solder is another tell-tale sign of a 'dry' joint. There can be two causes of this, one of which is movement in the joint as it solidifies. This causes the solder to crack and craze, producing an electrically poor connection as well as a mechanically weak one. The other main cause of this type of thing is having the iron applied to the solder for too long so that the flux burns away. This is also something that is likely to happen if soldered joints are made using the soldering iron bit to transfer molten solder to the joint.

To check for a 'dry' joint, a continuity tester (a multimeter set to a low resistance range will do) is used to check for a low resistance between the component's leadout wire and the appropriate

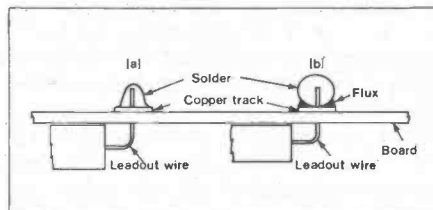


Figure 1(a) A good joint (b) A solder blob printed circuit track. When a 'dry' joint is discovered the solder should be removed from the joint using a desoldering tool or solder wick. Clean the printed circuit track and the end of the leadout wire using something like fine sandpaper or a miniature file, and then solder the connection again. Do not simply try re-applying the soldering iron and some more solder to the joint as this is unlikely to produce a reliable connection.

'Dry' joints do not only occur on the


printed circuit board, and can also be produced when making connections to off-board components. In fact this is probably when they are most likely to be produced. Prevention is better than cure, and provided the tags of the components and the ends of the connecting wires are generously tinned with solder prior to making the connections, there should be no problems of this type. A continuity tester can be used to test for these 'dry' joints, and the tell-tale signs are again a dull surface to the solder and probably a lot of excess flux as well. Also as much as before, to remedy the situation the solder should be removed from the joint, and the component tag plus the end of the lead then cleaned and tinned with solder before remaking the connection.

Component Testing

If a thorough check for mechanical faults fails to bring results, then a check for faulty components is the next step. A visual inspection of the components may show up a possible fault. For instance, a resistor or capacitor that has gone rather dark in colour might be indicative of overheating when it was soldered into circuit, with a consequent change in value.

Assuming that there is no clue of this type, it is then a matter of going through the components and testing them one by one. This task can obviously only be undertaken with the aid of some test equipment, but an ordinary analogue multimeter (which is something no electronics constructor should be without) is probably a little more versatile in this respect than most people realise.

Any multimeter should be equipped with a few resistance ranges, and should be capable of testing any resistance value within reason. An important point to bear in mind if you try measuring resistances with the component in-circuit is that other resistances in the circuit could shunt the component you are testing, and give a low resistance reading. If the reading obtained is higher than the marked value of the component then it is certainly faulty. If the reading obtained is much lower than the marked value try reversing the test prods. If a semiconductor junction was shunting the

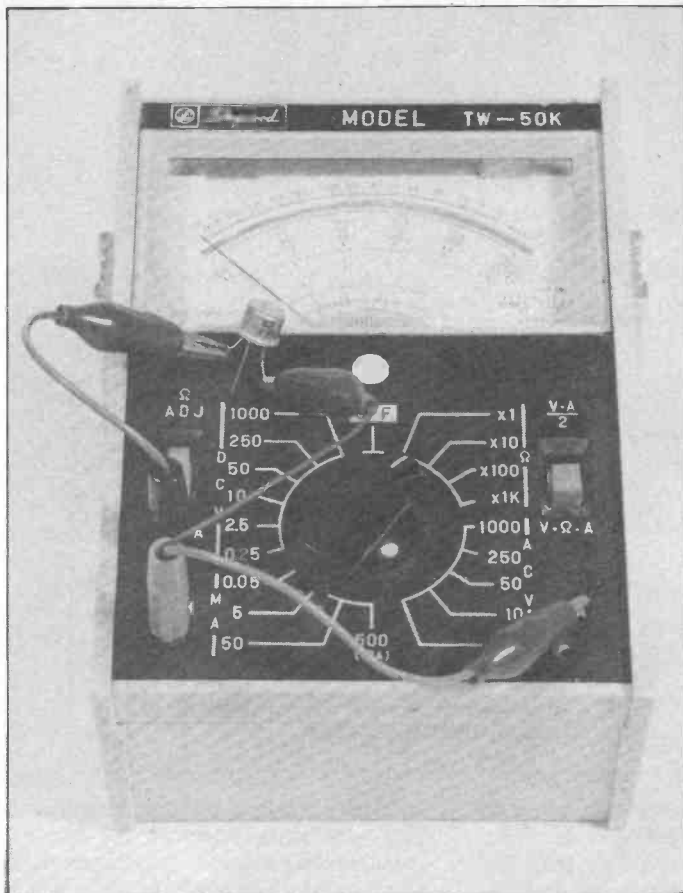


Testing for Leakage.

resistor and giving a low reading, reversing the test prods will reverse bias the junction so that it has a much higher resistance and does not significantly shunt the resistor. Of course, there could still be resistances in parallel with the resistor under test, but if the expected value is obtained with the test prods one way round or the other then the component is probably alright. If in any doubt, simply desolder one leadout wire so that the resistance can be measured in isolation from the rest of the circuit.

Potentiometers and preset resistors are also easily tested with a multimeter, but check that the resistance from the wiper terminal to each track connection varies properly, and do not merely check for a suitable track resistance. Bear in mind that the tolerances of potentiometers are quite high, being typically about plus and minus 20%, and that the track resistance may therefore be substantially different to the marked value.

Capacitors

Capacitors are difficult to test using just a multimeter, and low values cannot be checked properly. A check that can be made on any capacitor is a leakage test. Simply set the multimeter to a high resistance range and connect it across the capacitor. Apart possibly, from an initial 'kick' from the meter, a very high resistance reading should be obtained. In fact an infinite resistance reading should be obtained when testing non-polarised types. This test almost invariably has to be carried out with one leadout wire disconnected from the printed circuit as stray resistances in the circuit otherwise

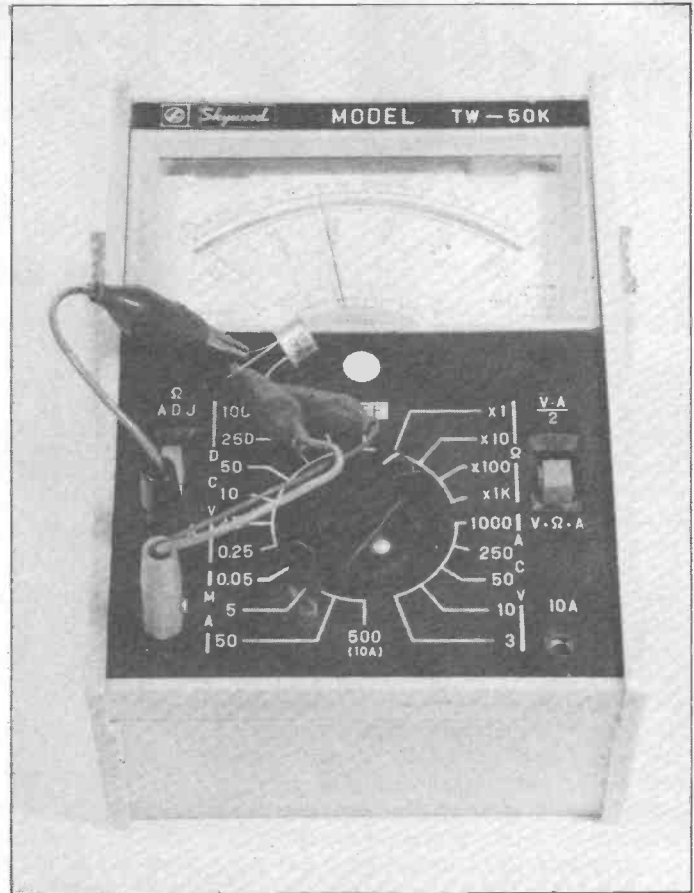

Testing for Gain.

prevent a suitably high reading from being obtained.

With electrolytic and tantalum capacitors the test prods must be connected to the test capacitor with the correct polarity. Although one might expect the positive test prod to connect to the positive terminal of the multimeter's battery, it actually connects to the negative terminal. Therefore, connect the negative test prod to the positive leadout of the capacitor, and the positive test prod to the negative leadout of the capacitor. Due to the relatively high values of electrolytic and tantalum capacitors it may take some time for the capacitor to fully charge, and for the meter reading to reach a very high value.

Electrolytic types generally have small but significant leakage currents, and for low value types a reading of several megohms or more is satisfactory. For high value types a reading of about a hundred kilohms or more is satisfactory as these should never be used in a part of a circuit where low leakage is important. In order to give a reasonably short charge time when measuring high value capacitors it might be necessary to switch to a lower resistance range.

The 'kick' of the needle when a capacitor is connected to the multimeter can be used as a rough test of a capacitor's value. It is just a matter of first short-circuiting the capacitor to ensure it is fully discharged, and then connecting it to the multimeter (being careful to use the correct polarity where appropriate). Make a note of the peak reading obtained. You can gauge whether or not the component has roughly the correct

value by subjecting capacitors of the same value to this test and comparing the peak readings obtained. This is admittedly only a very rough and ready check, and it will only work for capacitors of about 10nF or more in value, but it is better than nothing.

Semiconductors

Diodes and rectifiers are easily checked using a multimeter set to any resistance range. With an analogue type there should be a high resistance reading with the positive test prod connected to the anode and the negative test prod connected to the cathode (the leadout which comes from the end of the component having the coloured band). The reading should be infinity with silicon devices, but with germanium types a reading of a few hundred kilohms or more is acceptable. With the test prods reversed a much lower reading should be obtained, and the precise reading produced is of no importance.

The procedure is much the same with a digital multimeter, but initially a low resistance reading should be obtained, followed by a high resistance reading when the test prods are reversed. A few digital multimeters use an inadequate voltage for this test to work properly with silicon devices, but it will operate properly with the vast majority of digital multimeters.

Transistors

Some multimeters have a built-in transistor checker facility, but most transistors can be tested satisfactorily using an analogue multimeter that does not

Five Easy Pieces

from Robert Penfold

Personal MW Radio


The ZN414 radio integrated circuit has been popular with the home-constructor for a number of years now, but recently two improved versions of the device have been released. One of these is the ZN415, which is basically just the familiar ZN414, but in an 8 pin DIL encapsulation, and including a built-in bias resistor, a load resistor, and a two transistor output stage. In the circuit diagram the area within the broken lines represents the ZN415.

VC1 and L1 are the medium wave ferrite aerial plus tuning capacitor, and the input of the device is biased through the aerial coil in order to minimise loading on the aerial (and give good selectivity). C3 is the RF filter capacitor at the output of the detector. Like the ZN414, a supply potential of about 1.2 to 1.6 volts is needed. This is provided from a small 9 volt battery via a simple voltage regulator which consists of D1, D2, and R1. Alternatively, a single 1.5 volt cell can be used as the power source, in which case D1 and D2 are omitted, while R1 is replaced with a shorting link. The current consumption of the circuit is only about 4 milliamps incidentally.

The output stage of the unit may seem a little strange, consisting of a very low gain common emitter amplifier followed by an emitter follower stage which provides only a modest maximum output current. It is in fact designed specifically to drive medium impedance headphones of the type used with personal stereo cassette players and radios. The maximum drive available is rather limited, and the very high volume levels that can be achieved using this type of headphone cannot be obtained from this circuit. However, the volume from any reasonably strong station is sufficiently loud for most requirements, and the audio quality is surprisingly good provided headphones of adequate quality are used. For best results the headphones should be connected in series and not in parallel.

C5 is an RF filter capacitor and is needed to prevent instability. The bandwidth of the receiver is quite wide, which helps to give good treble response and audio quality. On the other hand, this can often result in a quite high level of interference. Closing S1 shunts C6 across the headphones and gives a reduction in the treble response.

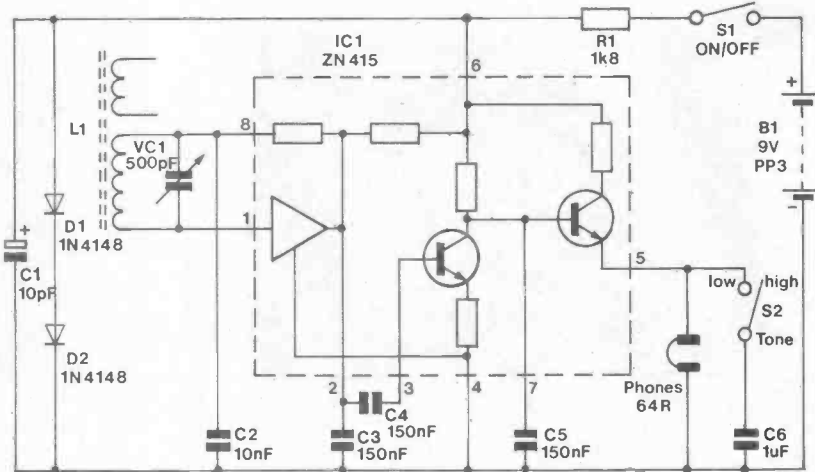L1 can be any medium wave ferrite aerial. The position of the coil on the rod is adjusted to give full coverage of the medium waveband. Most aerials of this type have a low impedance coupling



winding, but in this case the coupling winding is not needed and is either removed or just ignored. The specified aerial includes a longwave winding which is removed from the rod. It would be perfectly feasible to have a changeover switch to select either the medium or


longwave winding, and thus provide dual band operation. However, the ZN415 is not at its most sensitive at the frequencies involved in longwave reception, and as reception conditions on this band are very poor in many areas anyway, this is probably not a worthwhile modification.

Telephone Amplifier

A telephone amplifier is simply a device which boosts the audio output of a telephone to a sufficient level to drive a small loudspeaker at reasonable volume to enable several people to follow a telephone conversation. The normal method of connection to the telephone is via a special pick-up coil which receives the signal radiated by an inductive component inside the telephone. Apart from avoiding possible legal problems associated with direct connections to the telephone system, this is a very convenient

way of doing things since the telephone amplifier can be set up ready for use in a matter of a few seconds. One slight problem with this system is the need for a high gain amplifier to boost the minute output signal of the pick-up coil to a sufficient level to drive a loudspeaker.

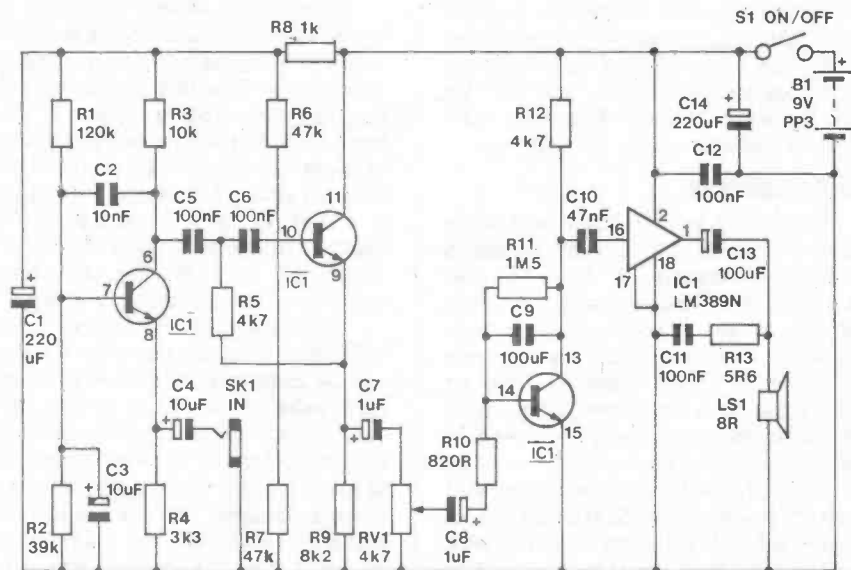This telephone amplifier is based on the very useful LM389N audio amplifier device. This is very similar to the well-known LM380N integrated circuit, but it has three transistors in addition to the audio power amplifier section. This gives great versatility and the LM389N is



well-suited to an application such as this. To make the operation of the unit clearer the three transistors have been shown as if they were discrete components in the circuit diagram, but the pin numbers have been included alongside each one.

TR1 is used as a common base input stage. This effectively acts as a step-up transformer which takes the low level, low impedance output from the pick-up and provides a higher voltage, higher impedance output signal. This is coupled to the next stage of the unit which is a 12dB per octave highpass filter. There is little point in having a good low frequency response as these frequencies do not contribute to the intelligibility of a

voice signal, and are unlikely to be present on the input signal anyway. The use of highpass filtering helps to give an improved signal to noise ratio, and in particular it helps to reduce any mains 'hum' that is picked up by the unit. The cut off frequency of the filter is about 300Hz.

The output of TR2 is coupled to volume control RV1, and then the signal is taken to the input of a high gain common emitter amplifier based on TR3. C9 provides a certain amount of low-pass filtering, as does C2 at the input stage, and this helps to give an improved signal to noise ratio with reduced background 'hiss'. The output from TR3 is coupled by

C10 to the input of the power amplifier, which is a conventional class B type. An output power of about 200 to 300 milliwatts RMS into an 8 ohm impedance loudspeaker is available.

The pick-up coil is mounted on the base section of the telephone by means of the built-in suction cup. A little experimentation will soon determine the position that gives optimum signal pick-up, but for the current (standard style) telephones this will be roughly at the centre of the right hand side. Keep the loudspeaker reasonably well away from the handset and do not advance the volume control too far or there may be problems with acoustic feedback.


Opto-Coupled RPM Meter

Most RPM meters are designed for use in cars and obtain the input pulses from the ignition circuit of the car. This is obviously a technique which cannot be applied to most other applications where an RPM meter would be of use. There are two common ways of obtaining suitable timing pulses where none are produced by the machine being monitored. One is to use an optical circuit and the other is to use a system based on magnetic sensors (with suitable activating magnets positioned on the rotating shaft). The optical method is generally the more simple and inexpensive, and one that can be applied to virtually any set up.

The pulse counting section of this circuit is a conventional type based on the LM2917N frequency to voltage converter chip. With the specified values the circuit has a nominal full scale frequency of 333.33Hz. This corresponds to 20000 RPM with one pulse per revolution, or more realistically, 10000 RPM with two pulses and 5000 RPM with four pulses per revolution. However, the full scale frequency/RPM value can easily be modified by changing the value of C6 (reduced value giving a proportional increase in full scale frequency).

The sensor circuit consists of photo transistor TR1 and load resistor R2. The base terminal of TR1 is left unconnected, and the collector to emitter terminals are connected to form a sort of light dependent resistor. The BPX25 phototransistor has a built-in lens which makes the device highly directional and helps to avoid spurious trigger pulses from being generated. The Maplin 'Low Cost Phototransistor'(YY66W) also seems to work quite well in the circuit, and is a useful low cost alternative to the BPX25.

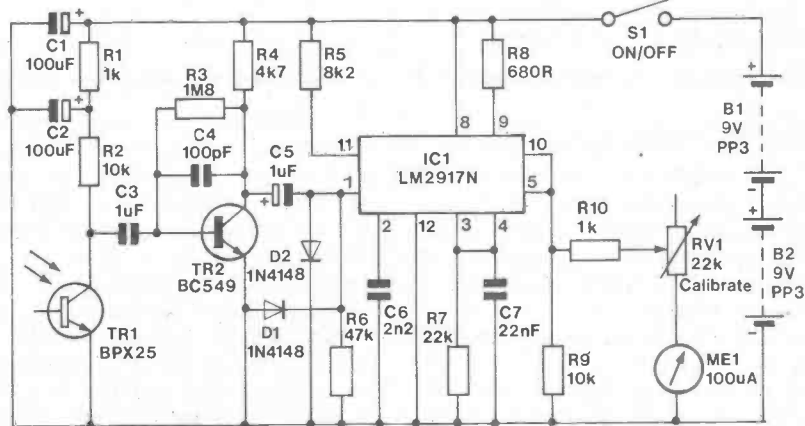The output from the sensor circuit is likely to be far too small to directly drive IC1, and TR2 is therefore used as a high gain common emitter amplifier which boosts the signal to a suitably high amplitude. D1 prevents the input of IC1 from being taken strongly negative, which would cause a malfunction in the device.



The circuit is very sensitive, and in order to produce usable results it is merely necessary to have patches on the monitored shaft that contrast with the shaft itself. For instance, with a highly reflective metallic shaft, spots of matt black paint would be used. The reduction in the light level received by TR1 as these spots pass in front of it would then generate the required timing pulses. The circuit does not require a high light level

in order to produce proper operation, but it obviously cannot operate in total darkness.

If the circuit proves to be over-sensitive, connecting a resistor of about 470Ω in series with the emitter of TR2 should cure the problem. An easy way of obtaining a calibration signal for the unit is to simply aim TR1 at a mains powered tungsten light. This gives a 100Hz calibration frequency.

Tremolo Unit

A tremolo unit is one of the most simple types of musical effects unit, although one would probably not guess this from the prices of ready-made units. The design featured here can be built at low cost but it nevertheless has a high level of performance.


The function of a tremolo unit is to amplitude modulate an input signal, with the modulation frequency being variable from typically about 0.5 to 5Hz or so. The modulation waveform must be one that has a low harmonic content, such as a sine or triangular type, so that a smooth and pleasant effect is produced. In this circuit the modulation signal is generated by IC2 which is a dual operational amplifier used as a conventional triangular waveform generator. This is a form of relaxation oscillator which uses IC2a as a Miller Integrator, and IC2b as a Schmitt Trigger. This gives a squarewave output from IC2b, and the required triangular

waveform from IC2a. Timing capacitor C3 charges and discharges via R6 and RV2, and the operating frequency of the oscillator can therefore be controlled using RV2. This gives an approximate frequency range of 0.5Hz to 10Hz.

The modulator uses MOSFET IC1 as a simple voltage controlled resistor. IC1 is a CMOS 4007UBE device, which contains two complementary pairs and an inverter. In this design, only one (N channel) transistor of one complementary pair is used and the other parts of the device are totally ignored. The drain to source resistance of IC1 forms an attenuator in conjunction with R1. However, R2 is connected in parallel with IC1, and this ensures that there is always a loss of 20dB or more through the attenuator. This is to keep the signal voltage across IC1 at a low level so that good distortion performance is obtained. The losses through the attenuator reach a maximum of about 50dB with IC1 biased

into saturation. The gate of IC1 is driven from the output of the modulation oscillator via RV1. The latter is adjusted to give an input voltage range to IC1 that gives good symmetrical modulation, and this is really just a matter of adjusting RV1 to obtain what is judged to be the best effect, unless suitable test gear (an AF signal generator and an oscilloscope) is to hand.

IC3 is used as an amplifier and buffer stage which compensates for the losses through the attenuator and provides the unit with a low output impedance. S1 is a bypass switch, and in practice this is a heavy duty (latching) push button switch mounted on the top panel of the case so that it can be foot operated. The case must be a strong type, such as a diecast aluminium box. The current consumption of the circuit is very low at only about 4 milliamps.

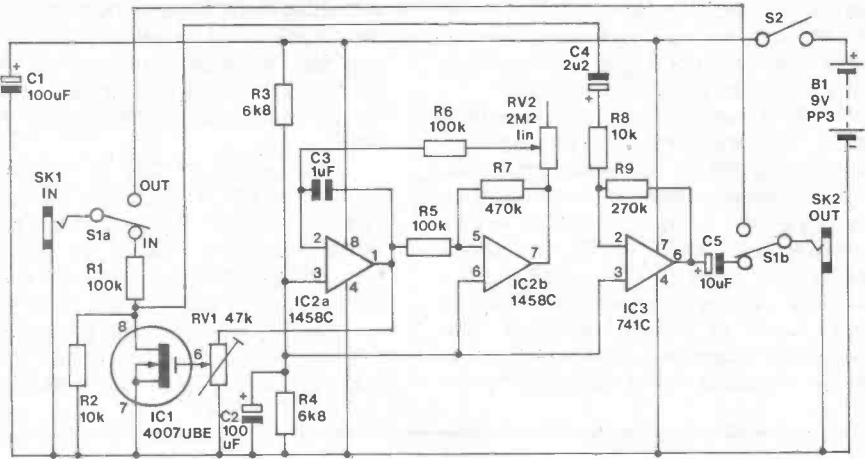


Model Train Chuffer

Sound effects can greatly enhance the realism of a model railway layout, and one of the most popular of these is the 'chuffer' effect. As its name suggests, it simply makes a 'chuffing' sound like a steam locomotive, but ideally a unit of this type should be designed so that the 'chuff' rate approximately matches the speed of the train. This is done by monitoring the track voltage and varying the 'chuff' rate in sympathy with this.

The 'chuffer' circuit shown here is based on the popular SN76477 sounds generator device, and this contains a number of stages including a VCO, super low frequency oscillator, noise source and filter, a mixer, a modulator and an envelope generator. In this case it is mainly the VCO, the noise source, and the modulator that are of interest. The noise generator gives the basic 'hissing' steam sound, while the VCO, in conjunction with the modulator, is used to amplitude modulate the noise signal to give the 'chuffing' effect.

The noise generator is a high quality digital type using a clock oscillator and shift register arrangement. R7 is part of the clock oscillator circuit, while R8 and C3 are discrete components in the noise filter. These give a small amount of low-pass filtering which gives a slightly lower pitched sound that is better for this application. R9 and C4 are the timing components for the VCO, and these have quite high values in order to provide a suitably low output frequency range. R10 controls the amplitude of the output signal while R5 and R6 control the timbre (the on to off ratio of the noise signal). The SN76477 has a built-in driver stage, but an external complementary output stage (TR2 and TR3) is required. R12 is the load resistor for the driver stage and R11 is a bias resistor. An output of around two or three hundred milliwatts RMS is provided into an 8 ohm impedance loudspeaker. The SN76477 has numerous control inputs, and these are either tied to earth or the stabilised 5 volt supply output at pin 15 in order to program the correct operating mode for this application.

The frequency of the VCO is controlled by the voltage fed to pin 16 of IC1. This voltage must be in the range 0 to 2.4 volts, with maximum voltage corresponding to minimum frequency. The track voltage, which may well be a pulsed DC signal, is smoothed by R1 and C1. D1 to D4 form a bridge rectifier which ensures that the voltage applied to the next stage is of the correct polarity. This stage is an inverter which uses TR1 in the common emitter mode. This converts the track voltage, which will be in the range 0 to about 15 volts, into a (roughly) 2.4 to 0 volt control voltage for the VCO. RV1 is adjusted so that the VCO switches on at the same track voltage that causes the train to start. Incidentally, there is a steady 'hissing' steam sound when the train is stationary and the VCO is cut off. RV2 is adjusted so that the VCO only just achieves maximum frequency with the train at full speed. After repeating adjustment of RV1 and RV2 two or three times the 'chuff' rate should vary realistically in sympathy with the speed of the train.

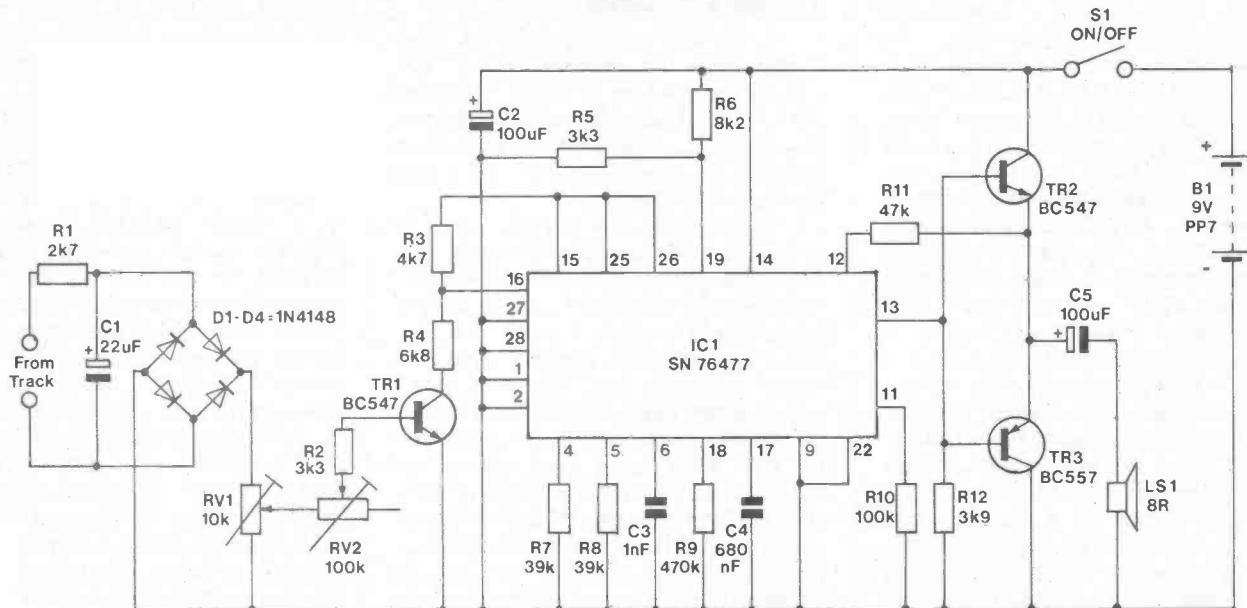

MODEL TRAIN CHUFFER PARTS LIST

RESISTORS: All 0.4W 1% Metal Film

R1	2k7	1	(M2K7)
R2,5	3k3	2	(M3k3)
R3	4k7	1	(M4K7)
R4	6k8	1	(M6K8)
R6	8k2	1	(M8K2)
R7,8	39k	2	(M39K)
R9	470k	1	(M470K)
R10	100k	1	(M100K)
R11	47k	1	(M47K)
R12	3k9	1	(M3K9)
RV1	10k Sub-Min Hor Preset	1	(WR58N)
RV2	100k Sub-Min Hor Preset	1	(WR61R)

CAPACITORS

C1	22 μ F Reversolytic	1	(FB08J)
C2,5	100 μ F 10V Axial Electrolytic	2	(FB48C)
C3	1nF Polystyrene	1	(BX35Q)
C4	680nF Polycarbonate	1	(WW51F)

SEMICONDUCTORS

IC1	SN76477	1	(YH32K)
TR1,2	BC547	2	(OO14Q)
TR3	BC857	1	(OO16S)
D1,2,3,4	1N4148	4	(QL80B)

MISCELLANEOUS

B1	9 Volt (PP7) Battery	1	
S1	Min SPST Toggle	1	(FH97F)
	Battery Clips	1 pr	(HF27E)
	28-pin DIL IC Socket	1	(BL21X)

TREMOLO UNIT PARTS LIST

RESISTORS: All 0.4W 1% Metal Film

R1,5,6	100k	3	(M100K)
R2,8	10k	2	(M10K)
R3,4	6k8	2	(M6K8)
R7	470k	1	(M470K)
R9	270k	1	(M270K)
RV1	47k Sub-Min Hor Preset	1	(WR60Q)
RV2	2M2 Lin Pot	1	(FW09K)

CAPACITORS

C1,2	100 μ F 10V Axial Electrolytic	2	(FB48C)
C3	1 μ F Polycarbonate	1	(WW53H)
C4	2 μ 2 63V Axial Electrolytic	1	(FB15R)
C5	10 μ F 25V Axial Electrolytic	1	(FB22Y)

SEMICONDUCTORS

IC1	4007UBE	1	(QX04E)
IC2	1458C	1	(QH46A)
IC3	μ A741C	1	(QL22Y)

MISCELLANEOUS

S1	DPDT Push Button	1	(FH93B)
S2	SPST Min Toggle	1	(FH97F)
B1	9 Volt (PP3) Battery	1	
SK1,2	Standard Jack	2	(HF90X)
	14-pin DIL IC Socket	1	(BL18U)

OPTO-COUPLED RPM METER PARTS LIST

RESISTORS: All 0.4W 1% Metal Film

R1,10	1k	2	(M1K)
R2,9	10k	2	(M10K)
R3	1M8	1	(M1M8)
R4	4k7	1	(M4K7)
R5	8k2	1	(M8K2)
R6	47k	1	(M47K)
R7	22k	1	(M22K)
R8	680 Ω	1	(M680R)
RV1	22k Sub-Min Hor Preset	1	(WR59P)

CAPACITORS

C1,2	100 μ F Axial Electrolytic	2	(FB49D)
C3	1 μ F Polycarbonate	1	(WW53H)
C4	100pF Ceramic	1	(WX56L)

TELEPHONE AMPLIFIER PARTS LIST

RESISTORS: All 0.4W 1% Metal Film

R1	120k	1	(M120K)
R2	39k	1	(M39K)
R3	10k	1	(M10K)
R4	3k3	1	(M3K3)
R5,12	4k7	2	(M4K7)
R6,7	47k	2	(M47K)
R8	1k	1	(M1K)
R9	8k2	1	(M8K2)
R10	820 Ω	1	(M820R)
R11	1M5	1	(M1M5)
R13	5.6 Ω	1	(M5R6)
RV1	4k7 Log Pot	1	(FW21X)

CAPACITORS

C1,14	220 μ F 10V Axial Electrolytic	2	(FB60Q)
C2	10nF Polycarbonate	1	(WW29G)
C3,4	10 μ F 25V Axial Electrolytic	2	(FB22Y)
C5,6	100nF Polycarbonate	2	(WW41U)
C7,8	1 μ F 63V Axial Electrolytic	2	(FB12N)
C9	100pF Ceramic	1	(WX56L)
C10	47nF Polycarbonate	1	(WW37S)
C11,12	100nF Ceramic	2	(BX03D)
C13	100 μ F Axial Electrolytic	1	(FB48C)

SEMICONDUCTORS

IC1	LM389N	1	(WQ36P)
-----	--------	---	---------

MISCELLANEOUS

LS1	76mm dia 8 Ω Speaker	1	(YW53H)
SK1	3.5mm Jack	1	(HF82D)
S1	SPST Sub-Min Toggle	1	(FH97F)
B1	9 Volt (PP3) Battery	1	
	Telephone Pick-up Coil	1	(LB92A)
	18-pin DIL IC Socket	1	(HQ76H)
	Battery Connector	1	(HF28F)

PERSONAL MW RADIO PARTS LIST

RESISTOR: 0.4W 1% Metal Film

R1	1k8	1	(MIK8)
----	-----	---	--------

CAPACITORS

C1	10 μ F 25V Axial Electrolytic	1	(FB22Y)
C2,5	10nF Polycarbonate	2	(WW29G)
C3,4	180nF Polycarbonate	2	(WW43W)
C6	1 μ F Polycarbonate	1	(WW53H)

SEMICONDUCTORS

IC1	ZN415E	1	(QY61R)
D1,2	1N4148	2	(QL80B)

MISCELLANEOUS

L1	Ferrite Aerial	1	(LB12N)
S1,2	SPST Sub-Min Toggle	2	(FH97F)
B1	9 Volt (PP3) Battery	1	
	Battery Connector	1	(HF28F)
	Headphones	1	(YK56L)
	8-pin DIL IC Socket	1	(BL17T)

The IC used in the MW Radio is not shown in our current catalogue.
Order As QY61R ZN415E Price £1.95

C5	1 μ F 63V Axial Electrolytic	1	(FB12N)
C6	2n2 Polycarbonate	1	(WW24B)
C7	22nF Polycarbonate	1	(WW33L)

SEMICONDUCTORS

IC1	LM2917N	1	(WQ38R)
TR1	BFX25	1	(QF30H)
TR2	BC549	1	(OO15R)
D1,2	1N4148	2	(QL80B)

MISCELLANEOUS

S1	SPST Sub-Min Toggle	1	(FH97F)
B1,2	9 Volt (PP3) Battery	2	
ME1	100 μ A Panel Meter	1	(RW92A)
	14-pin DIL IC Socket	1	(BL18U)



The telephone has for many years been something most people have taken for granted both at home and in the office. The recent loss of monopoly by British Telecom, (formally the Post Office) has generated a new interest in telephony by the general public as they may now buy and install their own approved telephone equipment.

This article describes briefly the history and operation of the telephone as we know it today. Information about the use of the new Line Jack units is also included although it must be noted that only British Telecom may install the Master Line Jack unit and no connections may be made to the P.S.T.N. (Public Switched Telephone Network) without British Telecom approval.

History

The origins of the telephone can be traced as far back as 1854 when a Frenchman called Charles Bourseul suggested that it was possible to transmit speech "by electricity". Phillip Reis, a German physicist, produced the first transmitter (microphone) in 1861 but it

by Robert Kirsch

was not until 1875 that the first practical telephone was developed by Alexander Graham Bell. The principle of Bell's first instrument was that when sound waves vibrate a magnetic diaphragm in the field of an electro magnet, the current flowing through the coils of the electro magnet would vary in sympathy with the sound. The principle is still used today in the receiver (telephone earpiece). This device, although making a good receiver, was not very sensitive as a microphone. The problem was overcome by the invention, in about 1880 by the Reverend Hunnings, of the variable resistance microphone using carbon granules. This type of transmitter is still in use in many of the older telephones although the electret and dynamic microphone are now being used as their relatively low output can be amplified in the telephone by semiconductor devices powered from the line current.

How the Telephone Works

Figure 1. shows a basic telephone circuit using carbon microphones and electromagnetic receivers. This system will work, but there are several disadvantages. One problem is that direct current flows through the receiver which is undesirable. Another is that speech from one transmitter will be received at the same volume by both receivers, giving an unacceptable sound level at the sending end. This effect is called 'sidetone' and all telephones are fitted with an anti-sidetone circuit to reduce the level.

Figure 2 shows the block diagram of


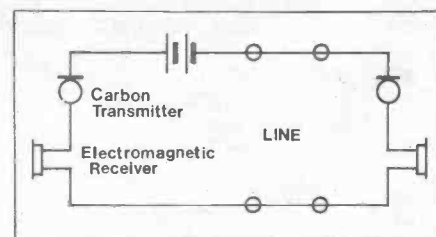


Figure 1. Simple Telephone Circuit

ALL ABOUT THE TELEPHONE

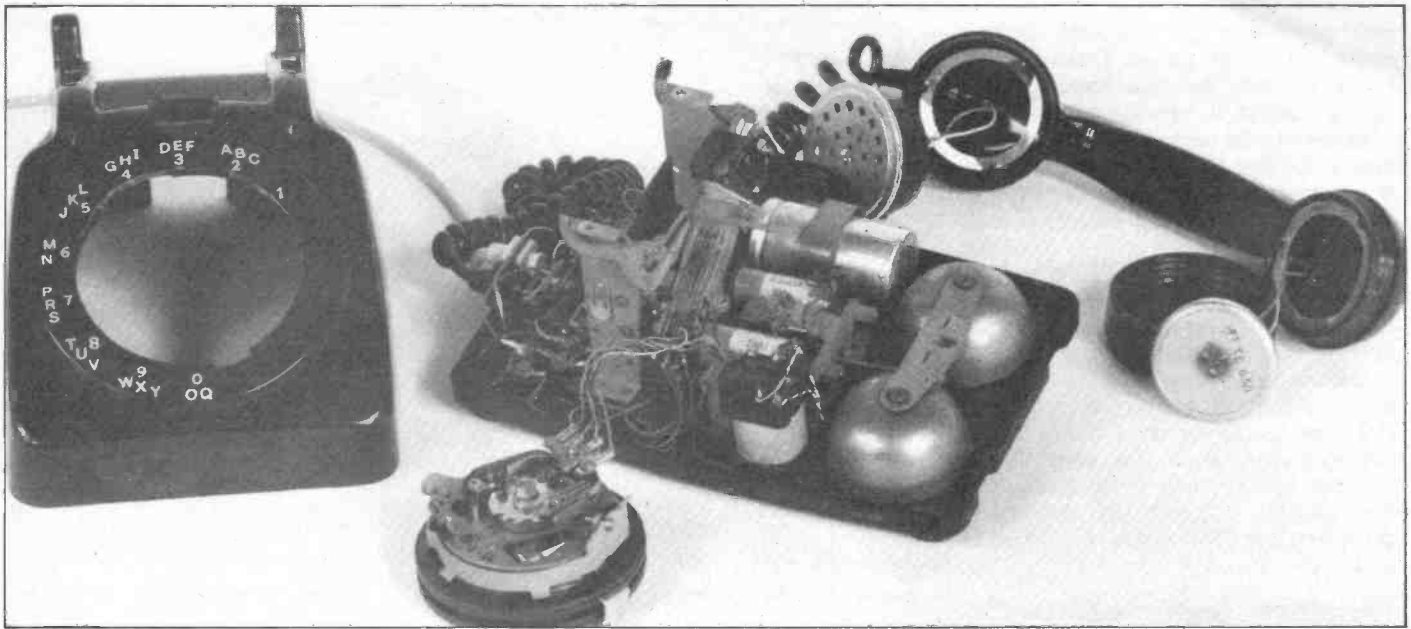

a practical telephone including transmitter, receiver and anti-sidetone circuit as well as the contacts, called the 'switch hook springs' operated by the handset when in its cradle. Figure 3 is the circuit of an actual telephone of older design.

Dialling is accomplished by discon-

necting the loop through the telephone (when the handset is raised) for a short duration (67ms), for a number of times depending upon the number dialled. The telephone dial is a clockwork device that is wound by the clockwise rotation of the finger plate and is returned by the action

of a spring, its speed being controlled by a governor. The dial, in its return direction, breaks a set of contacts a number of times, corresponding to the number dialled. Note that when 0 is dialled the circuit is interrupted 10 times. The dial also has contacts to short out the receiver,

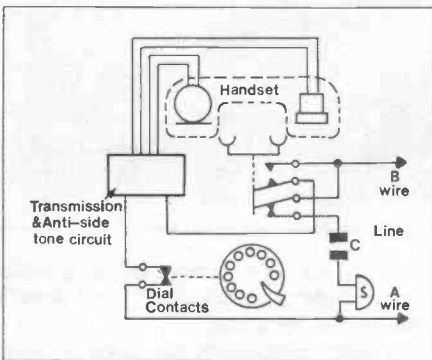


Figure 2. Simplified schematic of standard telephone

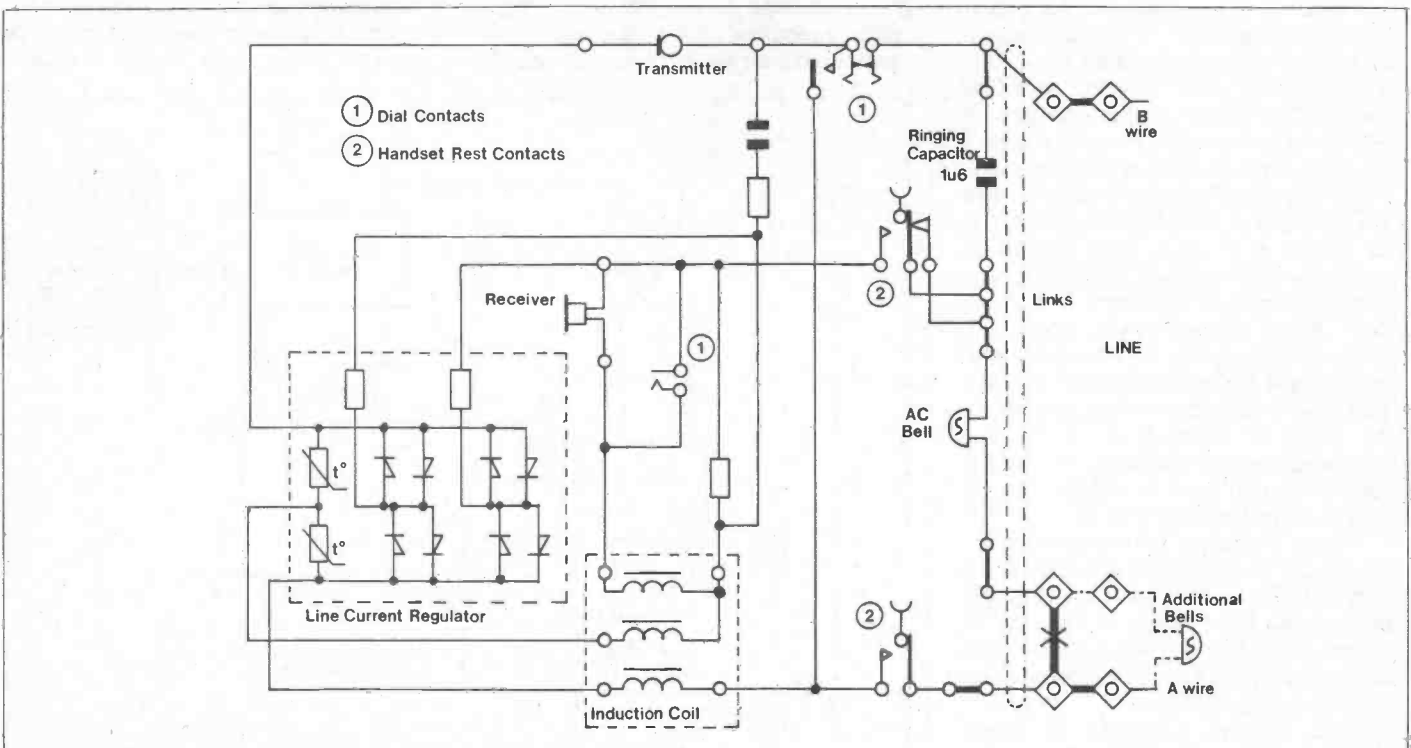


Figure 3. Circuit of telephone type 706
September 1984 Maplin Magazine

thus preventing an annoying clicking caused by the dial pulses. There are also contacts to short the transmission circuits during pulsing, to provide a lower loop resistance to the exchange during the 'on' time of the dial. The standard dial rate in this country is 10 pulses per second.

The telephone bell is rung by an A.C. signal of about 90 volts sent from the exchange. This relatively high voltage was used to provide sufficient energy to ring bells over long distances. The capacitor provided in the bell circuit presents a low impedance to A.C. ringing but prevents the bell causing a permanent D.C. loop across the line and thus calling the exchange, as in the case of the handset being lifted. When more than one telephone is used, one capacitor is provided and all the bells are wired in series.

Modern Developments


A telephone system designed today, would be very different from the present one, due to advances in technology. The existing system is so large that it would be impossible to change all the equipment at one time, although work has already begun on upgrading the system in some parts of the country. This means that modern telephones, used on the old system, use new technology to produce improved results, but must be compatible with techniques in use at the beginning of the century. There follows a brief description of areas in which new techniques have benefitted the performance of the telephone. Figure 4 shows a typical block diagram of a modern telephone.

The transmission system has been greatly improved by the use of dynamic or electret microphones with solid state amplification and sidetone suppression within the telephone, powered by line current. This results in a better quality and level of speech even over long lines.

Most modern telephones have push button dialling. This is usually accomplished by using a dedicated IC (e.g. the AY-5-9158 or the Mullard PCD3320 series). This device converts the keypad information into loop disconnect pulses of the same form as those of the rotary dial. These IC's often have the facility to store the last number dialled and to re-dial it at the press of a single key. The actual pulsing is accomplished by a reed relay or a transistor in series with the telephone loop. When a transistor is used it is connected across the DC side of a bridge rectifier and the loop across the AC side. This is to ensure the correct polarity for the transistor irrespective of the line connection to the telephone. The bridge rectifier is also used to provide the DC supply for the internal circuits.

Tone Dialling is now slowly replacing the old loop disconnect system and it is called DTMF (dual tone multi-frequency) and has been in use in America for many years. This system enables rapid dialling and is particularly suited to microprocessor applications.

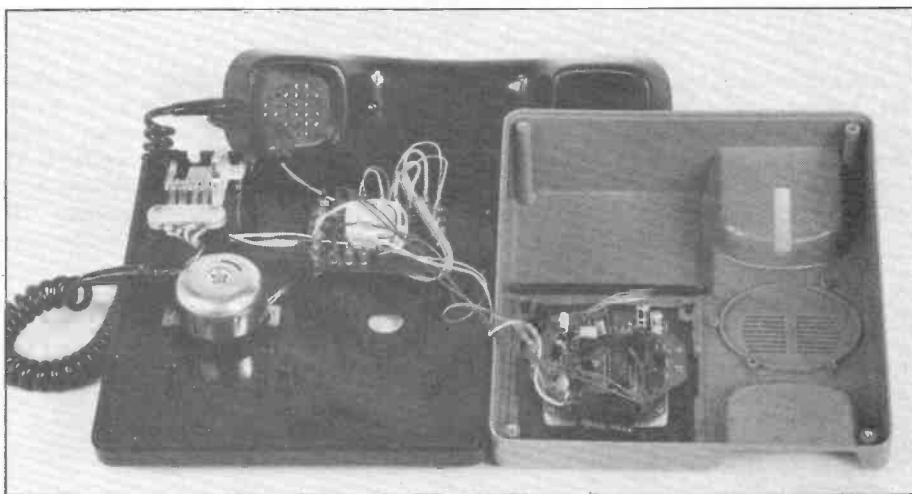The modern telephone no longer uses a bell; instead another IC is commonly used to provide indication of an



incoming call. This IC also is usually fed from a bridge rectifier, but in this case the AC ringing is fed to it via a capacitor. The rectified output is then used to supply the ringer IC whose output is connected to a small loudspeaker or piezo sounder. Due to the relatively low current required for the electronic ringer compared with the conventional bell, the

ringers are now connected in parallel, but a single capacitor is still used, fitted in the master jack unit.

Microprocessors are used in many modern telephones and these can provide many new features including multi-number storage and call metering; allowing the customer to know the cost of a call as it is being made. Figure 5 shows a

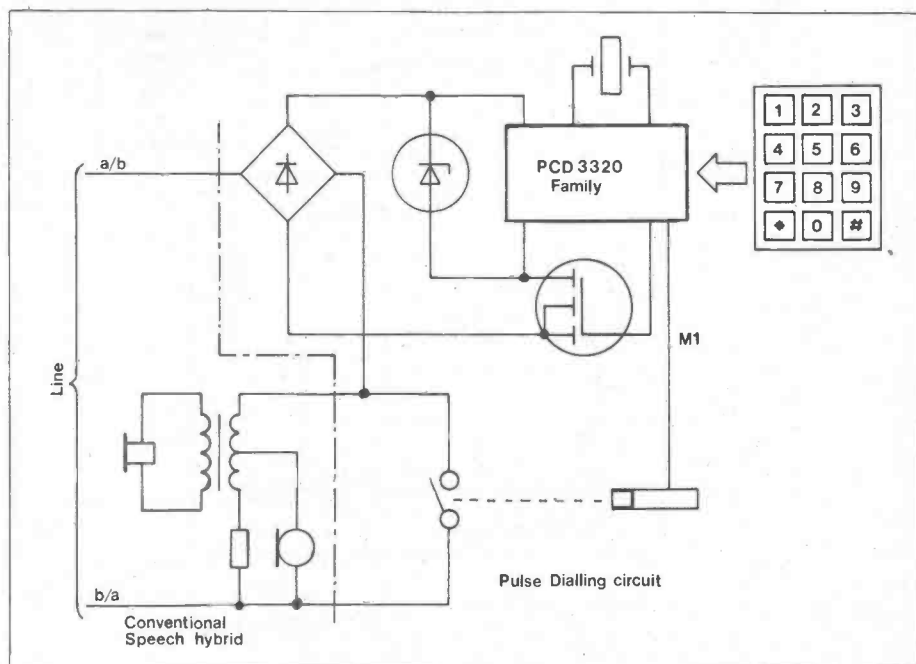


Figure 4. Block diagram of modern telephone

typical state of the art telephone using Mullard IC's.

Line Jack Units

Modern telephone installations use Line Jack sockets. This system has several advantages as customers may now buy and install their own (approved) telephone apparatus and simply plug it in. Also if several sockets are fitted, the customer can move the telephone from room to room or have as many instruments as he requires. This system also helps in the tracing of faults on an installation as customers equipment can be easily disconnected.

The Master Jack Unit is fitted by B.T. and contains the ringing capacitor and a discharge tube (for line and equipment protection against high voltages), see Figure 6. The two wires from the exchange are referred to as the A and B wires and it will be seen that all telephones are connected between A and B wire but all ringers are connected between the shunt wire (via the capacitor) and the A wire.

Several accessories are now available to plug into the line jack sockets including adaptors for various types of telephone and a dual outlet adaptor which is particularly suited for the use of direct connect modems where it is desirable to have the telephone and the modem in parallel.

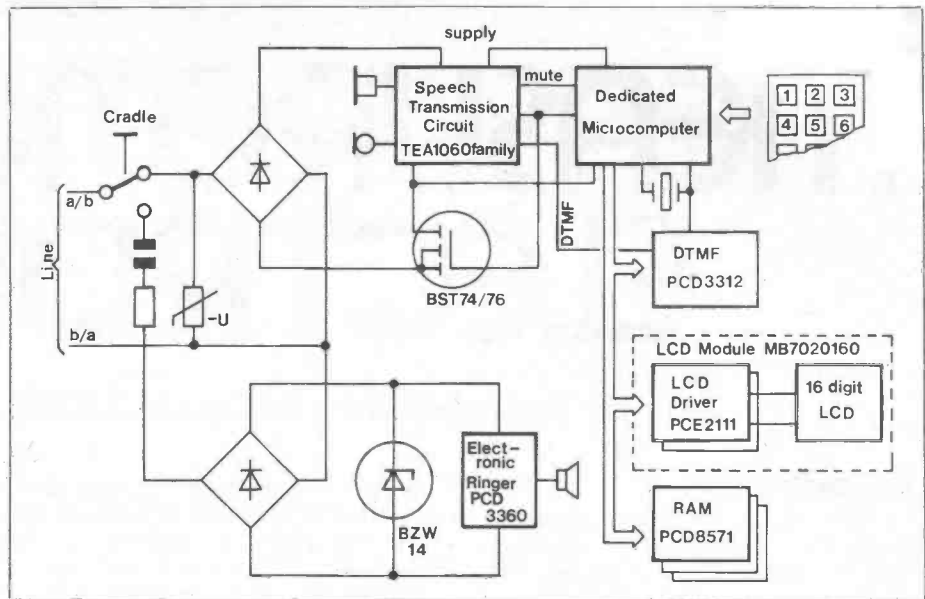


Figure 5. Microprocessor controlled telephone

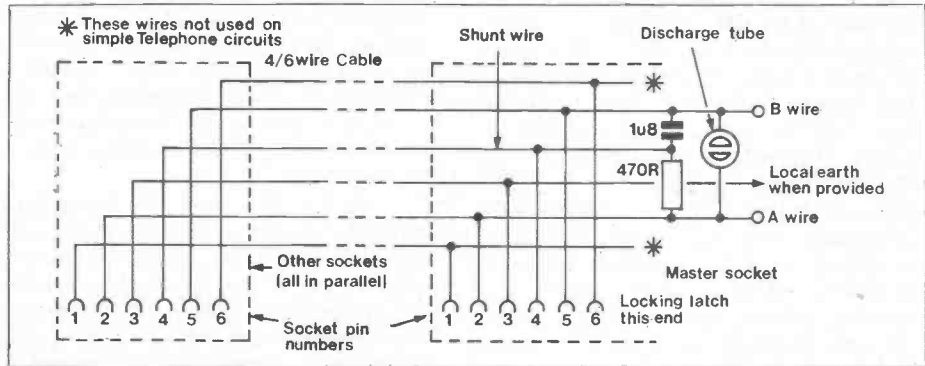


Figure 6. Line jack wiring

PROJECT FAULT FINDING *Continued from page 49.*

have this facility. To test npn transistors for leakage, set the multimeter to its highest resistance range, and then connect the emitter and collector terminals to the positive and negative test prods respectively. The test is basically the same for pnp transistors. The only difference is that the test prods are connected around the other way (positive to the collector, negative to the emitter). Silicon transistors should give an extremely high resistance reading, probably with no noticeable deflection of the meter at all, but be careful not to touch the base leadout wire when making this test or erroneous results could be produced. Germanium transistors often have significant leakage currents, and this test is of little worth with these devices.

It is easy to make a rough check to see if a transistor has a reasonable level of current gain, and the basic set-up is similar to that used for leakage tests. It is better to use a lower resistance range though, so that the transistor is tested at a reasonable collector current. A resistance range having a half scale value of around 100Ω to 1k should suffice. A resistor of about 100k in value is connected between the collector and base terminals of the transistor under test, and there should be no difficulty in making up a set of test leads which include this resistor. If the test device is serviceable the resistance reading obtained should

be much lower than the 100k resistance of the base feed resistor. The lower the resistance reading obtained, the higher the gain of the device under test. A high reading of about 30k or more indicates that the transistor under test has little or no current gain, and is unusable. This test may not be effective with some germanium devices due to their high leakage currents, and it may not be effective with some power transistors as these are designed to operate at much higher currents than the test currents used with this set-up. This simple method of testing will work well with the vast majority of transistors though.

Most other semiconductor devices cannot be checked easily, and must be tested using in-circuit voltage checks or by building a simple test circuit. Assuming that you are unable to undertake this type of check, there is little alternative to replacing a semiconductor such as an integrated circuit, which is a suspected 'dud'.

Switches can easily be tested using a continuity tester or a multimeter set to a low resistance range. Due to their mechanical nature switches are amongst the components that are most likely to fail. Apart from checking for a fault, using a continuity tester also enables you to check whether or not you have correctly identified the tags of the component.

A multimeter set to a low resistance

range can also be used to give transformers and inductors a rough check. With small inductors there should be no significant resistance through the components. Similarly, with RF coils there should be no significant resistance through each winding, but there should, of course, be an extremely high resistance between one winding and another. Things are much the same with large inductors and low frequency transformers, but a resistance of a few tens of ohms (or even a few hundred ohms) may be present across the windings. The most common fault in transformers and inductors is a break in the winding, and this should be readily shown up by a continuity check (and the lack of continuity). More complex faults such as shorted turns are not likely to be brought to light by a continuity check, unless a large winding has a suspiciously low resistance.

The methods of checking described here have the advantage of needing little or no test equipment, and a similar degree of technical knowledge. These methods are rather 'hit and miss' though, and if the fault is traced rapidly this is achieved by sheer luck. In the next article we will look at logical methods of fault finding which require slightly more equipment and technical know-how, but should give much speedier fault diagnosis.

MEASUREMENTS IN ELECTRONICS

By Graham Dixey C.Eng., M.I.E.R.E. Part Four

Introduction

The testing of digital equipment requires a slightly different approach from the testing of linear circuits. The approach still has to be a logical one, of course, and disciplined but there is unlikely to be the multiplicity of instruments to choose from. Therefore, it is not so much the correct choice of instrument that matters as knowing how to use the basic few that are normally accepted as being required. A real advantage of digital testing is that quite useful pieces of test equipment can be assembled at little cost; nonetheless they can be used to test a variety of circuits such as counters, registers, microcomputer inputs and outputs, indeed quite complex digital systems. Naturally, there are other more sophisticated items of test equipment such as logic analysers that can be very useful at times but most work can be done very simply. For this reason this article will include a number of circuits that can be made up cheaply but which will allow a variety of digital circuits to be examined for correct functioning.

Digital versus Analogue Signals

The clue to the differing degrees of complexity in digital and analogue test equipment lies in the 'signals' themselves. An analogue signal may occupy a wide range of amplitudes from a few micro-

volts to many volts; its frequency may lie between a fraction of 1Hz and many MHz. For this reason a voltmeter of high sensitivity and wide bandwidth may be needed in order to measure it. Its waveform, if it is not a pure sine wave, may also be a complicating factor. Digital signals, on the other hand, occupy only one of two possible levels - in theory anyway. These levels may be continuous i.e. d.c. or may consist of pulses varying in length from a few seconds down to nanoseconds.

On the face of it the digital input signals to a system may be synthesised by either a switched level (to give either logic 0 or logic 1) or by a pulse generator. An output indicator has only to differentiate between these two levels and can be a simple two-state device such as an LED, rather than the costly moving-coil meter of the analogue system.

Inputs and Outputs

A desirable characteristic of any indicator is that it does not load the test point, a requirement met, in the case of an LED, by driving it from a high-gain transistor (Figure 1(b)). The input resistance is, in this case, 33k, sufficiently high to avoid loading the test point. The two input levels, logic 0 and logic 1, can be developed using the circuit of Figure 1(a), consisting of no more than an SPST toggle switch and a pull-up resistor. This is about as simple as you can get so

naturally there are limitations to what can be done with it. The switch, being a mechanical device with spring contacts, suffers from 'contact bounce' i.e. when the contacts close a short series of pulses is generated. These occupy only a very short period of time. Nonetheless, when the response times of TTL devices are measured in nanoseconds, the test circuit may well 'catch' all of the pulses. In the case of a counter the indication will be a false one. What is needed is a bounce-free switch and this is provided by the circuit of Figure 2. Half of a 7400 chip is wired as a simple latch. The SPCO switch 'sets' or 'resets' the latch giving either logic 1 or logic 0 levels at Q. The latch operates as soon as the switch closes either way and having flipped over into its new state then ignores the spurious pulses that follow. If the switch is a push-button type then regular operation generates a series of slow pulses, useful for studying counter operation, etc.

The indicator can also be improved. A simple logic probe can be made in which a positive indication of logic 0 or logic 1 is made on one or other of two separate LED's. Actually the design of logic probes is not as simple as may seem at first sight. The problem is that it actually has to recognise THREE separate conditions:

- (i) probe connected to logic 1 (one LED lit).

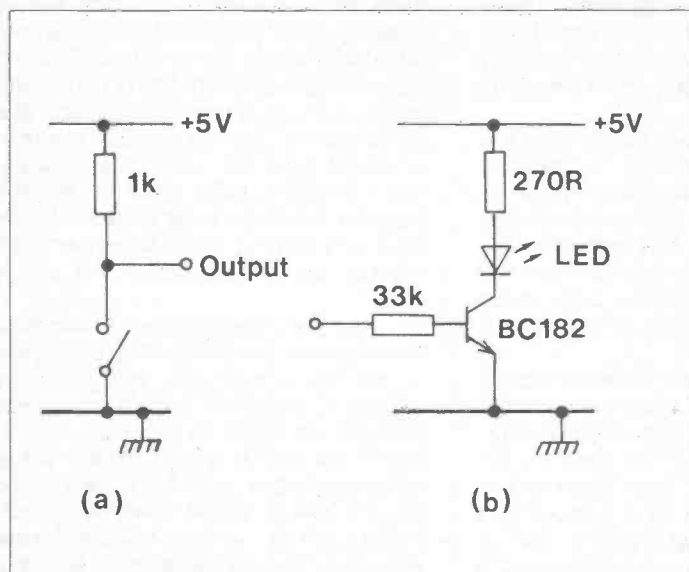


Figure 1. Simple input/output devices (a) switched logic levels (b) logic level indicators.

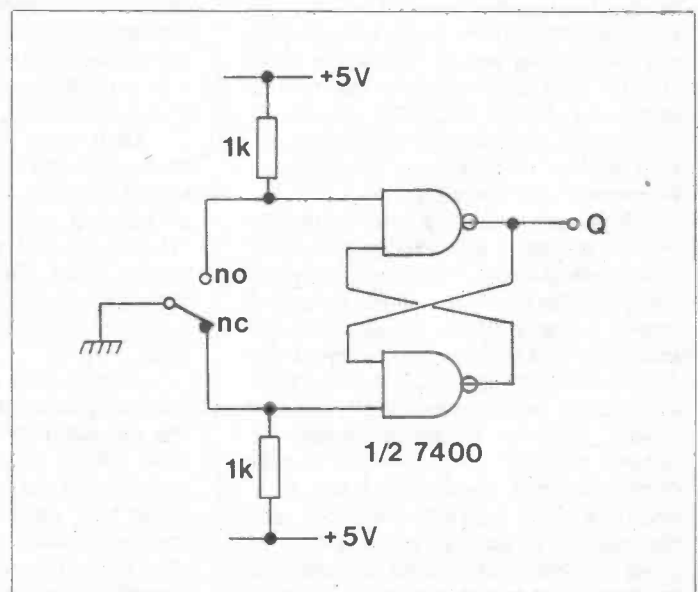


Figure 2. A de-bounced TTL switch.

- (ii) probe connected to logic 0 (other LED lit).
- (iii) probe not connected at all (neither LED lit).

The design of Figure 3 shows a simple circuit that meets all three of these conditions, which it does by a bit of honest cheating. Each of the NAND gates, G1 and G2, has an input held at logic 0 by the normally-closed push-button switch. Therefore, the outputs of both G1 and G2 are at logic 1, ensuring that both latches G5/G6 and G7/G8 are re-set i.e. neither LED is lit.

However, when the switch is pressed the above mentioned inputs to G1 and G2 rise to logic 1 level and either G1 or G2 will then have a logic 0 output, depending upon the logic level at the probe input. The appropriate latch will then be set, lighting one LED or the other. It is a simple three chip design with obvious limitations but justified by its extremely low cost.

A more useful probe would perform the following functions:

- (i) indicate logic 0 and logic 1 levels within recognised thresholds e.g. logic 0 between 0V and 0.8V, logic 1 between 2.5V and 5V.
- (ii) indicate the presence of a pulse train by flashing LED's at a constant rate, irrespective of the frequency of the pulse train.
- (iii) incorporate a 'memory' LED to signify that a level transition has occurred; this is useful when the speed of the level change is too great to be detected with the human eye.

A probe incorporating all of these features can become quite sophisticated in design. There are a number of kits available for less than £20, that go some way towards meeting these requirements. In fact, a kit is available from Maplin (order no. LK13P) that at the moment sells for £10.95. It has the following features:

Detects HI, LO and Open Circuit (Floating Input) states and Pulse trains from 1Hz up. The display is novel in that a seven-segment display is used to indicate the states by the letters H, L, F or P, corresponding to those listed above.

Testing a System

Suppose that the items of Figures 1, 2 and 3 have all been constructed. How can they be used in practice? Figure 4 shows a circuit for a code converter; in fact it converts 2421 BCD numbers into their 8421 BCD equivalents. In this system the 2421 BCD number 1101 (ABCD) is equivalent to the 8421 BCD number 0111 (WXYZ), both equalling decimal 7. It is possible to check the logic of the unit by wiring in the switch units of Figure 1 (a) as inputs and the LED units of Figure 1 (b) as outputs. It is well worth making up two boxes - one with eight switches and one with eight LED's. This will cover the checking of almost any logic circuit including the input/output functions of

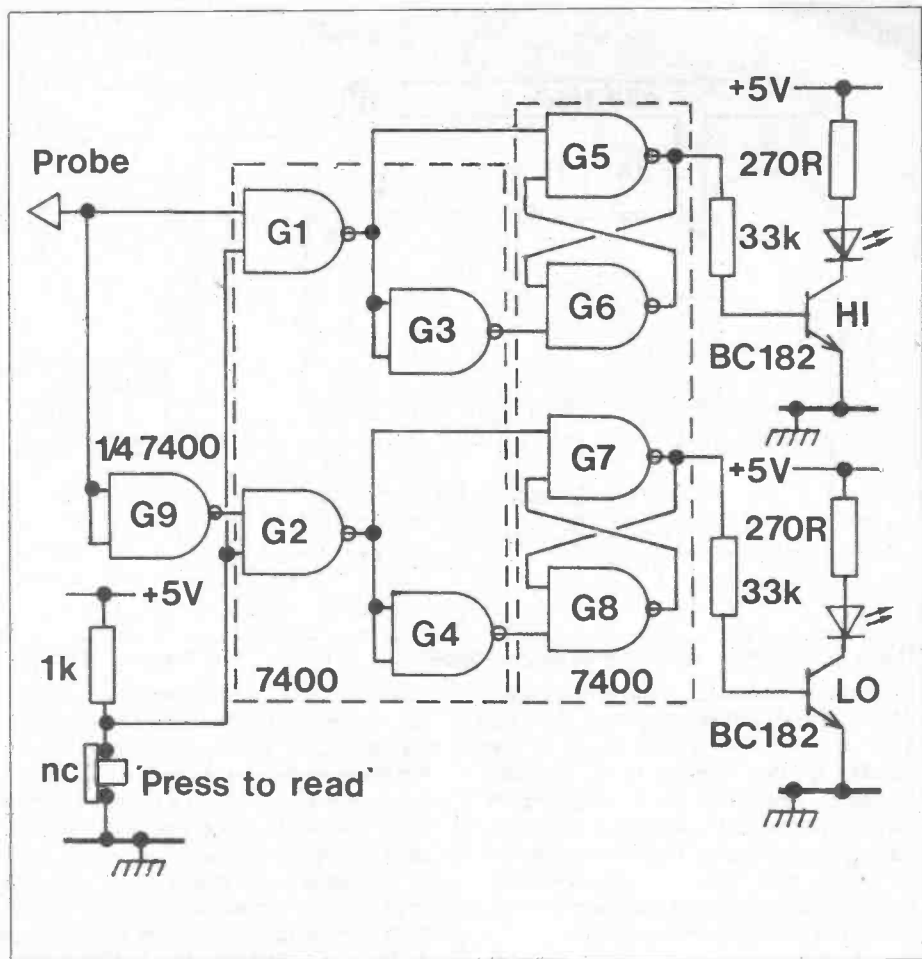


Figure 3. A simple HI-LO logic probe.

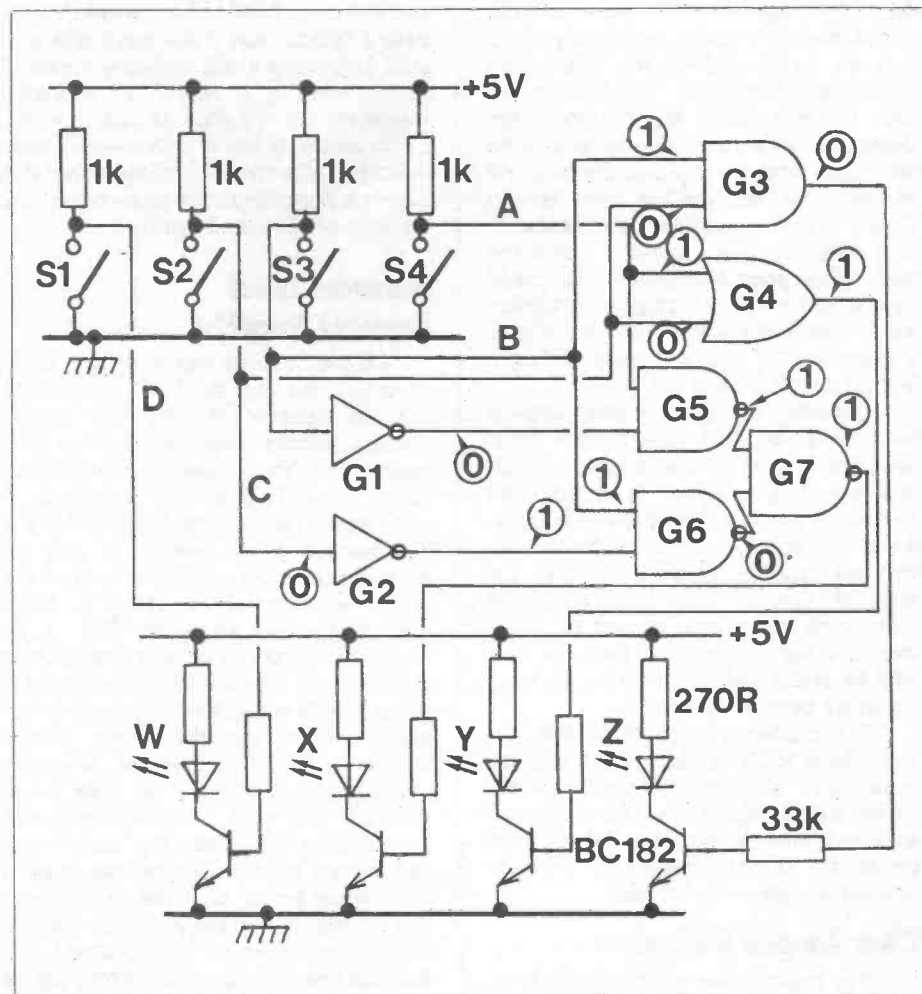


Figure 4. Checking the logic of a code converter.

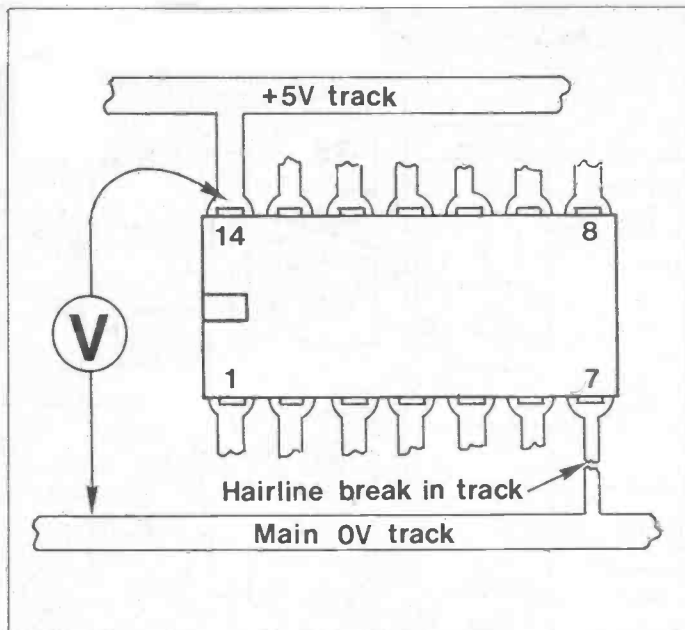


Figure 5. The wrong way of checking chip supplies.

8-bit microcomputers. The switches S1, S3 and S4 are closed to set up the 2421 BCD number 1101 as the input to the circuit. If the converter is working correctly then the LEDs will light up to give WXYZ = 0111. All other combinations in the set can be input in this way on S1 - S4 and the outputs checked. However, these will not be given here as this is just an illustrative example.

Suppose that the circuit doesn't work. There are several possibilities. The original design may be incorrect; the circuit may be wired up incorrectly; there may be a chip fault or the board may have a fault. Assuming that the first two can be eliminated by checking the design procedure and visually examining the circuit layout, this leaves the question of a physical fault. The test items used in Figure 4 have established the existence of a fault but do not actually locate the fault. At this point diagnostic testing takes over from functional testing. This implies some degree of knowledge - in this case a knowledge of the logic levels throughout the circuit for a given input.

Consider the input number already mentioned i.e. 1101. The correct logic levels at the inputs and output of each gate are shown circled. Enter the logic probe! By placing the probe at each of these test points in turn, the faulty area can be quickly found. Suppose, for example, that the input to gate G2 was found to be logic 0 (correct) and its output was also logic 0 (wrong), then G2 may well be faulty, possibly shorted, or have an errant earth at its output.

But another possibility is that the lower input to G6 is faulty. If the IC's are in sockets a quick substitution check will reveal which chip is faulty but if IC's are soldered straight into the board, this procedure is not convenient. What is needed is another instrument.

The Logic Pulser

The logic pulser may be thought of as the digital equivalent of the analogue signal injector. When it is applied to a test

point in a circuit and a push-button switch depressed, it sends a very short, high-current pulse into the test point. This is sufficient to change the state of a working gate even when held in a given state by a fault. Thus, in Figure 4, the pulser will test gate G2 by sending a pulse into its input at the same time that a logic probe is applied to its output. If the probe's LED's flash momentarily, the gate is alright. A kit for a logic pulser is also available from Maplin (order no. LK19V) which at present costs £5.95. This design has the added feature that if the push-button is held depressed it will deliver a stream of pulses, making it useful for checking sequential circuits such as counters, etc. Furthermore, it has a built-in logic level indicator (effectively a simple probe) that makes a separate probe unnecessary for the type of test just described.

Power and Board Faults

Digital circuits tend to be fairly complex, leading to PCB's that have intricate patterns of very fine tracks, perhaps double-sided. In the event of a board failure the temptation to pull out all the IC's and 'twiddle with every pot' in sight should be resisted. The first thing to be checked is the power. It may be present at its entry point on the board but disappear somewhere along a track leading to one or more IC's. It is, therefore, necessary to check the power at every chip separately. On the face of it, this is simple enough to do; however, it is quite easy to get the wrong results without realising it. Imagine how you might proceed to carry out such a test yourself. You take your voltmeter, clip the negative lead onto the earth track and, in turn, put the positive lead on each plus supply pin on all of the chips. Every one shows a correct reading, yet the circuit doesn't work. You conclude that the fault lies elsewhere. Yet it may not be so at all. To see why not, look at Figure 5.

This particular chip has a minute

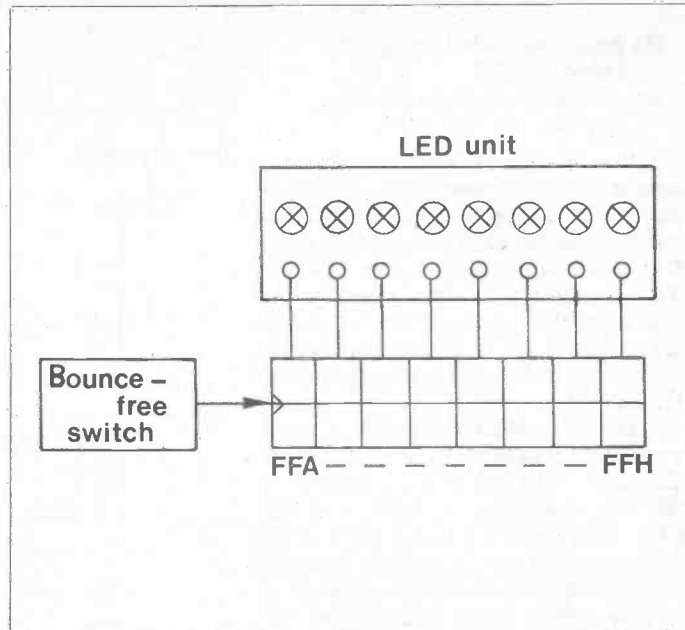


Figure 6. Testing the sequence of a counter manually.

break in the earth track right near the pin. By placing the negative lead on the main earth track, this break has been effectively 'bridged', thus allowing the voltmeter to read the supply voltage even though the chip actually lacks an earth return. If, however, the supply is checked directly between the IC pins (usually 14 and 7 on a 14-pin DIL TTL chip), any break like this soon shows up. Or at least the lack of supply to the chip is soon found, which should mean the same thing to the keen-eyed! The moral is - always check the supplies right at the chip pins. And that really means the pins of the chip themselves, not the track adjacent to the pins because another sort of break that can easily occur is a badly fitting pin in an IC socket. This also applies to the checking of logic levels at gate inputs and outputs.

Counters and Registers

These are examples of 'sequential' circuits i.e. those in which the current state of the circuit is dependent upon the number of inputs (pulses) received. After the design of a counter to a specified sequence, this sequence can be checked by noting the states that the Q outputs assume in turn, by using LED indicators of the type of Figure 1(b), while the input is being pulsed repeatedly by either the bounce-free switch of Figure 2 or the 1Hz TTL oscillator of Figure 7. This latter uses the well-known 555 chip and actually has two speeds. The 1Hz speed is used where the operation has to be slow enough to allow observation of the changing states of the LED's and the 1kHz speed is used when a CRO is used to look at the waveform at any stage in the counter.

Synchronous counters using extra gating can be more difficult to fault-find than simple 'ripple-through' counters because there is both sequential logic and combinational logic to deal with. If they seem to 'stick' or avoid some states completely, chip changes should be tried if at all feasible. If a JK flip-flop has both of

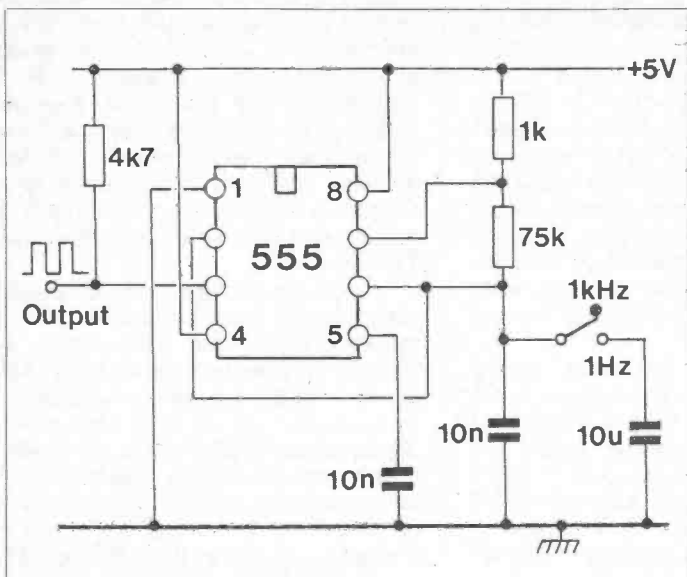


Figure 7. A two-speed TTL oscillator.

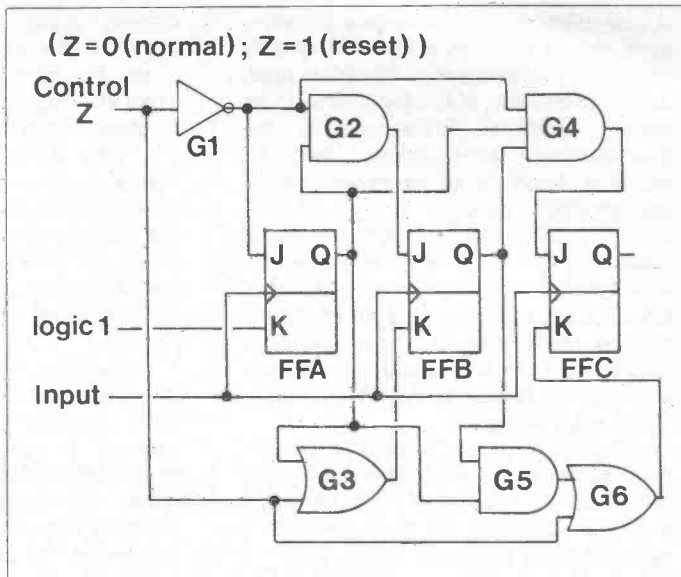


Figure 8. A divide-by-eight resettable counter.

its J and K inputs connected to logic 1, it should toggle whenever clocked. If it doesn't, try the logic pulser on the clock input to see if it responds; if it does, look for a missing clock pulse. An example of a gated synchronous counter is shown in Figure 8. A logic pulser, together with the LED indicators on the flip-flop Q outputs, will test the counter for correct sequencing. The pulser will provide the pulses to be counted at the input, and can also be used for checking the logic of the gates if

the sequence is wrong.

Suppose that the counter gets to a state where flip-flop FFC is 'set', but taking the control input Z up to logic 1 fails to reset it. The question is whether gate G6 is receiving this transition or, if it is, whether it is responding to it. The logic pulser is applied to the input of G6, the logic probe is placed on G6's output and the integrity of this gate is thus checked.

It is possible to give numerous examples of digital circuits which can be

analysed with the test items described in this article. However, what it usually comes down to is that one proceeds logically through the system testing power, checking logic levels with the logic probe and eliminating chips by substitution or by means of the logic pulser. Many quite complex digital circuits are nothing more than large-scale repeats of smaller ones. If you can trouble-shoot the latter, you can deal with the former. It just takes a little longer!

CLASSIFIED

VARIOUS FOR SALE

MAPLIN STEREO Disco Console, with built in amplifiers and sound to light unit. £200. Tel. St. Helens (0744) 811490.

FIVE-BAND STEREO Frequency Equaliser, good condition, boxed, etc. Only £25. Also Stereo Bass Enhancer, very good condition and boxed. Only £15. Tel. Bristol (0272) 772965.

S.W.L. REPORT Forms designed for maximum information from your listening post. Give real meaning to your D.X. reports. Details to: IRC, Rout, 3-137 Champion St., Christchurch, New Zealand.

150W STEREO DISCO, Case, all printed circuit boards, both transformers, one gooseneck lamp and all discrete components. Value approx. £170, offers around £100 inc. carriage. Tel. 061-773-5237.

CLUBS

ATARI OWNERS issue 6 of the U.K. Atari Computer Owners Club newsletter is now available. It contains tutorials on High-res Graphics dumps to a printer, 80 column text display, Adventure column, a review of 'Fun with Art' from EPYX, reviews of new software including BOULDER DASH, BRUCE LEE and JAVA JIM, and much more. Send for your copy to P.O. Box 3, Rayleigh, Essex at only £1.00 plus 30p postage.

COMPUTERS FOR SALE

ATARI 400, data recorder, joysticks, manuals, etc. £95 o.n.o. Sony Betamax VCR, 10 blank tapes, unused £280 o.n.o. Phone: Mrs. Grayson, Canterbury 65066 (evenings) or 65367 (daytime).

If you would like to place an advertisement in this section, here's your chance to tell Maplin's 200,000 customers what you want to buy or sell, or tell them about your club's activities - absolutely free of charge. We will publish as many advertisements as we have space for. To give a fair share of the limited space, we will print 30 words free of charge. Thereafter the charge is 10p per word. Please note that only private individuals will be permitted to advertise.

DRAGON 32 Computer with joysticks, £95. Many games and peripherals also for sale. D.Kavanagh Tel: Tiptree 817124.

ZX81 + 16K RAM with Maplin full-size Keyboard with a Modified socket. Hardly used, good condition, £45's worth of software, PSU, leads and manual, cost over £150. Sell for £75 o.n.o. Sae to Ian Williams, Maescraiu, Llanwrin, Machynlleth, Powys, SY20 8NB.

SECONDHAND ZX Spectrum tapes for sale, all originals, packs of four tapes for £10. Send sae for lists to: M. Graham, 1 The Cottages, Dovenby, Cockermouth, Cumbria, CB13 0PN.

COLOUR GENIE 16K Computer + 16K RAM chips, upgraded BASIC, circuit diagrams for micro and interfaces, still in box £150 o.n.o. Phone (02273) 69108 after 5pm weekdays or any time weekends.

Commercial or trade advertising is strictly prohibited in the Maplin Magazine.

Please print all advertisements in bold capital letters. Box numbers are available at £1.50 each. Please send replies to Box Numbers to the address below. Please send your advertisement with any payment necessary to: Classifieds, Maplin Mag., P.O. Box 3, Rayleigh, Essex SS6 8LR.

For the next issue your advertisement must be in our hands by 5th October 1984.

MUSICAL FOR SALE

RARE OPPORTUNITY due to unforeseen infirmity new 'Wersi' Cosmos electronic organ, normally retails at £4000+, bargain £2,300. Tel: 0222-766414 (Cardiff). Will consider good video in part exchange.

MAPLIN MESS3 Organ, partially assembled to good standard. All circuit boards, DMO2T master oscillator and instruction leaflets MES 51-55. Component value over £300. Detailed list available. Offers? Chippenham (0249) 650926.

MAPLIN MATINEE Organ, good working order, hardly used, £475, Archer, Felixstowe 283452.

CRUMAR COMPOSER Polysynth, mono, poly, organ and strings + 4 octave keyboard. Touch and breath modulation etc. Home use only, 1 yr old, cost £800 sell £350. Tel: Bradford (0274) 685926 evenings/weekends.

SYNTHESISER, based on 4600. Mostly working but not completely finished. Large wooden case with internal amps and speakers. Plug in PCBs, huge patchboard. £220 o.n.o. Cambridge (0223) 893593.

MAPLIN 5600S Stereo Synthesiser, fully tuned, perfect condition, plus demonstration cassette, books, pedals etc. offers around £500. Tel: Birmingham (021)-523-7240.

MAPLIN 5600S, save £200 on the kit price and get a superbly built example - £495, Alphadac complete, cased, power supplies for all the modules you will ever want - £250, RSD Studiomaster Studio 4, the ultimate cassette multitrack - £595, Synctrack - £35, Roland TB-303 - £155, Roland TR-606 - £135, E&MM 1.6 second DDL - £225, Clef master rhythm - £60. Comber, Tel: Ramsey (0487) 813961 - offers/package deals, genuine reason for reluctant sale.

WANTED

WANTED: MAPLIN touch sensitive electronic piano, complete and working. V.Hulme, 26 Lincoln Green, Chichester, Sussex PO19 4DN.

WANTED: COPY of circuit diagram and/or PCB layout of a FM-transmitter 88-108MHz approx. 3 watt output. Please write to: Kristiansson, Kastrupgatan 9, S-16342 Spånga, Sweden.

ALI REZA MAHABADI of 121 Emam Mousasadr Street, Rey Avenue, Tehran 11797, Iran, would very much like the gift of any of the following: TMS1000, AY-3-8710, TMS1601NLL, HM6147P, 7555.

With the increased price of petrol, it is now essential that the engine performance should be kept at its peak to give economical consumption. To obtain maximum combustion of the fuel, the ignition system must be maintained to the manufacturer's specification, the most important factor being the correct gap of the contact breaker points on the distributor. The most common method of measuring this gap is by a feeler gauge, which is not very accurate, because it does not allow for any wear or back lash on the distributor and can only give approximate results, which can be detrimental to engine performance, especially at higher speeds.

A more accurate method of measuring the gap is by using a dwell meter and measuring the number of degrees during which the contacts are closed, which is referred to as the dwell angle. Figure 1

closed. This angle can be increased by closing the gap, or decreased by opening the gap. See Figure 1. A Dwell Meter could be purchased at a cost of £12 upwards, but the dwell angle can be measured using a multimeter in conjunction with the simple circuit shown in Figure 2. The principle on which the dwell angle is measured, is by observing the duty cycle of the voltage waveform across the points. When points are open, the multimeter will read zero and when the points are closed, the multimeter will read 90.

Therefore, with the engine running the needle will take up a position on the scale proportional to the number of degrees in which contact points are closed, which is the dwell angle. Figure 3 shows the multimeter adjusted to 90 divisions and an indication of the reading with the engine running (as for a Vauxhall

contact points are closed. With the contact points closed and a reading on the multimeter, switch on the ignition and adjust (R1) until a reading of 90 is obtained on the multimeter. Start the engine at a normal tick over speed and you will note that the needle will drop back to a position on the scale proportional to the number of degrees in which the contact points were closed. i.e. The dwell angle.

If the dwell angle is not in accordance with the dwell angle stated in your repair manual, the points must be adjusted to give the correct dwell angle by closing the points to increase the dwell angle and opening the gap to decrease the dwell angle. If the reading is unsteady, you may be able to improve the condition by putting in a capacitor of about $0.047\mu\text{F}$ to smooth the circuit as shown by dotted lines (C) in Figure 2. The

DWELL ANGLE MEASUREMENTS

illustrates the contact breaker points, cams, lobes and angles for points opened and closed as given for a Vauxhall Viva. This measurement is taken with the engine running which will compensate for any wear on the distributor components such as the spindle and cam lobes, thus averaging the error and obtaining the maximum results. The dwell angle varies with different ignition systems, but they are all designed with a dwell angle which will allow the ignition coil sufficient time to give maximum build up of the magnetic field, to produce the strongest spark at the plug points. The correct dwell angle for a particular make of car can be obtained by referring to the maker's Workshop Manual. For example:— Vauxhall Viva 1256 cc Engine number 1639738 onwards, the Cam Dwell Angle is 49 to 51 degrees.

In brief, the dwell meter measures the angle in degrees through which the cam rotates whilst the contacts are

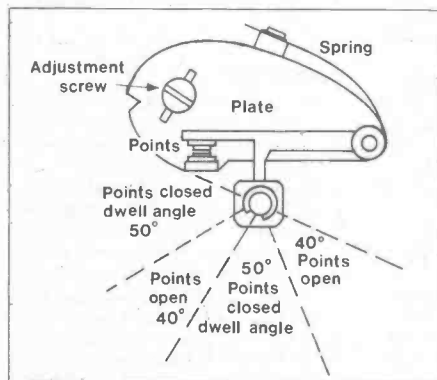


Figure 1.

by R. Richards

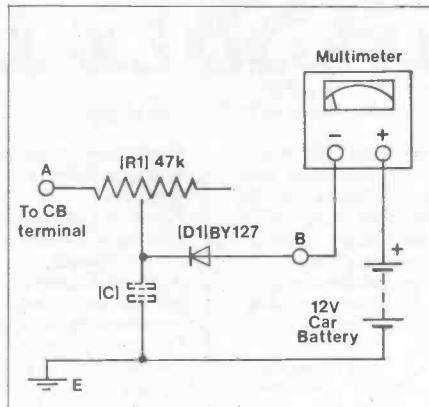


Figure 2.

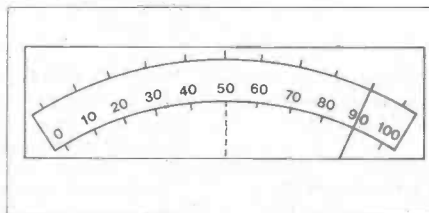


Figure 3.

Viva). The circuit consists of a 47k pot or preset connected in series with a diode BY127. Point (A) is connected to the C.B. terminal of the ignition coil and point (B) to the negative terminal of the multimeter. The multimeter is switched to 5 or 10 volts, and the positive lead of the multimeter is connected to the positive pole of the car battery. If the contacts are closed a reading will be obtained on the multimeter. If no reading is obtained the engine should be turned over until the

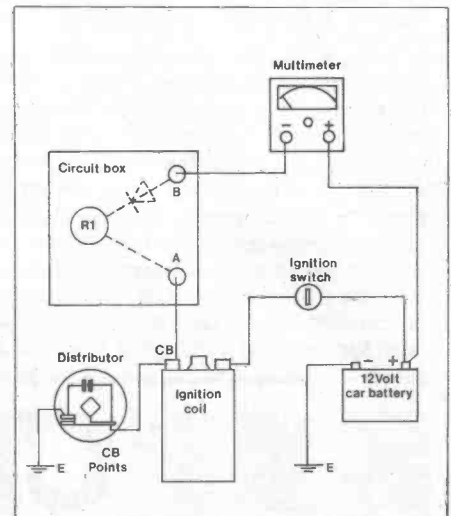


Figure 4.

diode BY127 prevents any current from feeding back from the ignition coil, so it is essential that it is fitted the correct way round with the cathode to the 47k pot.

The above circuit can be accommodated in a small box as shown in Figure 4. A knob is fitted to the 47k pot, and points (A) and (B) brought out on two terminals. The multimeter could also be used to carry out the following tests: Continuity Test, Circuit Tracing, Current Leakage, Battery Voltage and condition, together with testing for high resistance of any leads, switches or contacts. All of the examples shown applied to four cylinder engines. To measure the dwell angle on engines with more than four cylinders, the multimeter adjustment should equal the number of degrees between the lobes, which are as follows:

- 4 cylinder: $360 \text{ divided by } 4 = 90$
(adjusted reading on meter)
- 6 cylinder: $360 \text{ divided by } 6 = 60$
(adjusted reading on meter)
- 8 cylinder: $360 \text{ divided by } 8 = 45$
(adjusted reading on meter)

To complete the engine tune, the checking of the dwell angle is followed by checking the timing with a timing light, adjusting the valves, cleaning and adjusting the plugs and setting the carburettor with a Colortune, or similar appliance.

CONNECTIONS MADE EASY

by D. H. Jennings

Marketing Director, H&T Components

ID Connector/Flat Cable, Design and Use

The development of flat cable technology in the early 1970's created problems of wire termination which remained largely unsolved until the introduction of insulation displacement termination techniques.


The requirement was to achieve simultaneous termination of a number of wires simply, quickly, cheaply and reliably. Insulation displacement connector technology or IDC as it is termed, has met all these requirements. This article attempts to help the reader to understand what it is, how it works and where and when it can be used. More ambitious readers can perform their own cable harness construction with relatively low cost tools but for the majority the quickest and simplest way is to purchase a ready made harness with the knowledge that it is easy to specify, well constructed and very reliable in use.

What is IDC?

To understand the what we need to consider the why; the evolution of IDC stems from the need to join together printed circuit boards and/or sub assemblies as well as peripheral equipment, with anything from five to sixty wires. The cables had to be compact and lightweight and to some extent replace co-axial and twisted pair as well as round harnesses. The superior mechanical and electrical performance of flat cable (Figure 1) as well as its improved flexibility made it ideal for use in interconnections in hitherto unattempted areas, including home computers, video

games, hi-fi equipment, apart from the traditional commercial and military electronics applications.

Having established the cable suitable for these applications the need arose to terminate the ends with some form of connector. To strip and solder up to sixty wires at either end of a short cable is extremely time consuming and fraught with problems of quality. Likewise, stripping and crimping wires, or stripping and wire-wrapping is equally time consuming, added to which there is the further need to provide some form of strain relief to prevent the connector and cable termination interface being compromised during use.

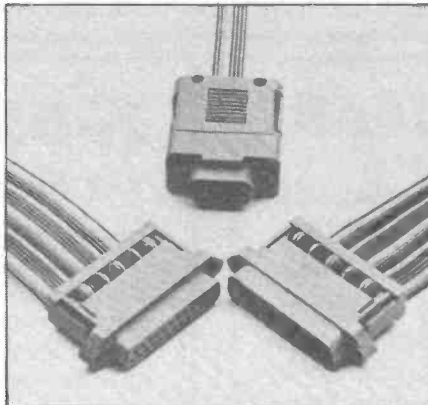

The solution when it came seemed so obvious that many users questioned its originality. In fact the concept used a combination of many ideas including crimping, wire wrapping, and clamping wires onto terminals. What was significantly different was that the technique enabled reliable connections to be made between the wire and connector *without* pre-stripping the insulation. It also enabled all of the wires in the cable to be connected at the same time.

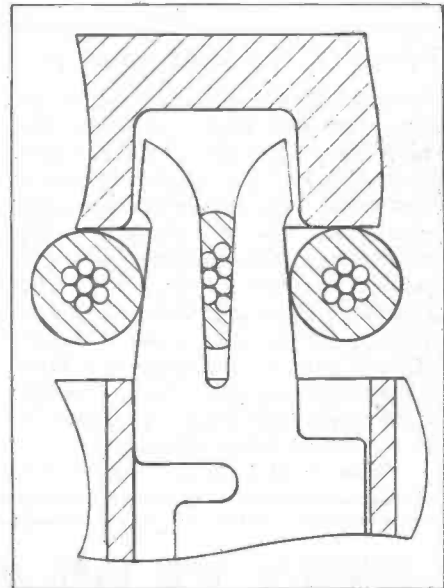


Figure 2. Contact point between forks and wire

The principle of the contact termination is a 'V' shaped slot into which the plastic coated stranded wire is forced. The insulation is displaced (hence the name) and the wire core is compressed between the forks of the contact, thus creating a number of contact points with the wire. The joint is similar in conception to a wire wrap termination, except in this case the contact surrounds the wire rather than the reverse (Figure 2).

In practical terms a connector, be it plug, socket, PCB transition, dip, card edge or input/output is identical in terms of termination and consists of a number of forks, a plastic cover, and in some cases a strain relief member. The flat cable is laid onto the back of the connector after which the cover is assembled. This sandwich is then placed in a press which is closed thus forcing the wires down into the forks and making an instant and complete termination.

Lest anyone think this technology low level; examination of the components will show precisely manufactured plastic and metal parts, which in themselves have to displace the insulation without shorting the wires together or creating open circuits (Figure 2).

Types of Connector

Differing needs inside and outside electronic equipment have generated a

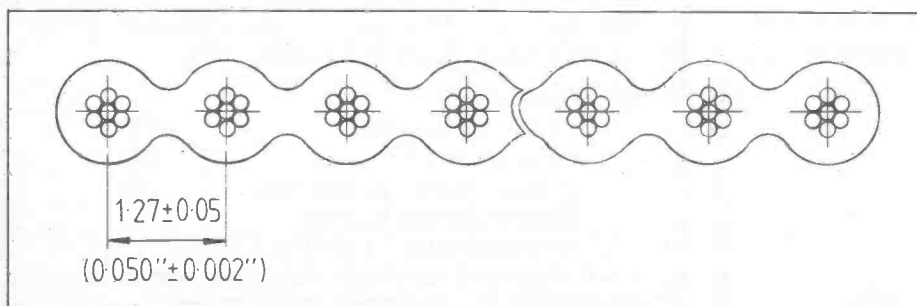


Figure 1. Cross section through flat cable
September 1984 Maplin Magazine

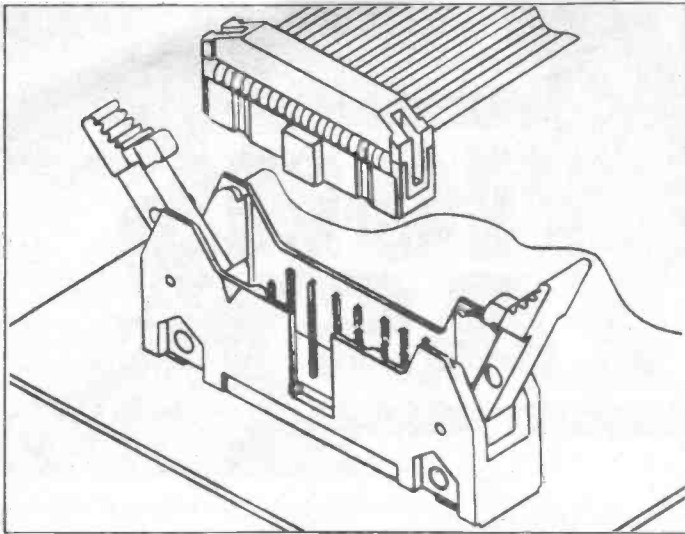


Figure 3. P.C. Board header/socket

whole family of connector shapes and sizes. The two most commonly used connectors are the header and its mating socket (Figures 3 & 4). The header is mounted on the end of the printed circuit board and has conventional solder terminations which connect with the tracks on the board. The mating end of the header consists of pins to which the socket is plugged and secured with end latches (Figure 3). The header and socket are polarised to prevent reversed mating which could have disastrous effects on the equipment being connected.

Other members of the family include

PCB transition connectors which enable permanent connection to be made between flat cable and boards, dual in line plugs which provide a connection to the ubiquitous DIL socket (Figure 5), flat cable card edge connectors and the ever popular 'D' miniature complete the family.

IDC Benefits

In conclusion, ID connectors and flat cable harnesses provide a reliable means of interconnecting electronic equipment and sub assemblies whilst eliminating time consuming cable preparation and

potentially unreliable connection points. The result is gas tight high speed termination interconnections, that can be relied upon to continue to give problem free service throughout their installed life. Furthermore they can be of particular help to the home constructor in providing a simple and reliable method of connecting flat multi-way cable to his PC board.

Maplin stock a wide range of IDC's, flat IDC cable and accessories (in 0.1 & 0.05 inch spacing), for full details please see pages 82, 179 and 185 of the 1984 Catalogue and the new products in the last issue of this magazine.

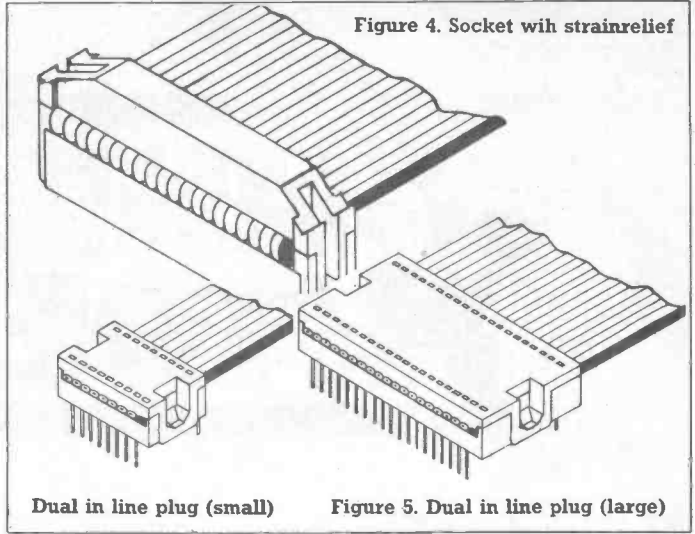


Figure 4. Socket with strainrelief

Dual in line plug (small)

Figure 5. Dual in line plug (large)

ONLY £2.80 A YEAR

The best way to buy a quarterly magazine is by subscription, because it's hard to remember when new editions are due.

And it's just as hard for newsagents to remember, which is why you may find our magazine hard to get. So make sure you get every issue of 'Electronics' by sending a subscription now. Clip the coupon below and we'll ensure that you get every issue of Britain's 'biggest selling electronics magazine in the UK', as soon as it's published.

P.S. Don't forget to renew your subscription, either!

Don't delay, send your cheque or postal order now to:

**Maplin Magazine Subscriptions Dept.,
Maplin Electronic Supplies Ltd.,
P.O. Box 3, Rayleigh, Essex SS6 8LR.**

I enclose £2.80 (Overseas: surface £3.24, air £6.84) for 1 year's subscription to the Maplin Magazine.

Please start from Issue No.

Customer No. (if known)

Name

Address


..... Post Code

Issue 13 on sale 9th November 1984.

1985 CATALOGUE

On Sale 10th November 1984

The amazing Maplin Catalogue is here again! The new edition is packed with hundreds and hundreds of new electronic components to bring you right up to date with all the latest developments. As all home constructors agree (and a good many professionals too) the Maplin Catalogue is the one essential piece of equipment they need for their hobby. And now with all our **prices on the page** the Maplin Catalogue is better value than ever.

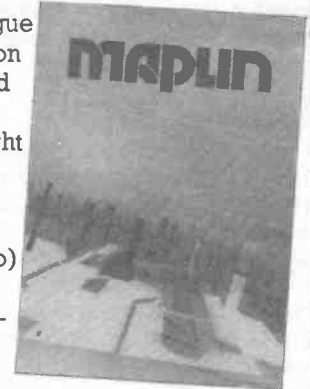

Pick up a copy as soon as it's published at any branch of W.H. Smith or in one of our shops. The price is still just £1.35. Alternatively, you can order a copy by post by sending £1.75 (including postage) to our Rayleigh address and quoting CA02C.

Overseas Prices

Europe surface mail	£2.40
Europe air mail	£3.70
Outside Europe surface mail	£2.40
Outside Europe air mail	
(depending on distance) £5.25/£6.85/£7.95	

For surface mail anywhere in the world you may send eleven International Reply Coupons.

DID YOU MISS THESE ISSUES?

Project Book 6

VIC20 and ZX81 Talkbacks. Projects to enable these micro's to speak! Allophone based system gives unlimited vocabulary. Plus a fascinating article on speech synthesis techniques using allophones.

Scratch Filter. This tunable design will make those old scratched records playable again.

Bridging Module. Use this kit and two Maplin 75W MOSFET amplifier modules to make a superb 400W amp. — with loudspeaker protection.

Moisture Meter. A low cost project which enables you to check walls and floors for damp.

ZX81 TV Sound and Normal/Inverse Video. Your ZX81 can now give you sound directly on a TV, plus inverted video display facility.

Four Simple Veroboard Projects: — Portable Stereo Amplifier, Sinewave Generator, Headphone Enhancer and Stylus Organ.

All this for only 70p. Order As XA06G (Maplin Project Book No. 6) Price 70p NV.



Electronics Issue 7

Copies of issue 7 are still available, contents include:

CMOS Crystal Calibrator. A device which enables Radio Amateurs to check receiver calibration & Amateur Band positioning.

DX'ers Audio Processor. Improve the performance of your communications receiver — no modifications needed.

Enlarger Timer. An accurate timer with a display that allows it to be used for colour enlarging.

Sweep Oscillator. A useful easy-to-build item of test equipment.

VIC20 & ZX81 Interfaces. Connect either of these computers to modems, printers, VDU's or any other RS232 compatible device.

All this for only 70p. Order As XA07H (Maplin Magazine Volume 2 Issue 7) Price 70p NV.



Electronics Issue 8

Copies of issue 8 are still available, contents include:

Modem/RS232 Interface for Spectrum computers, operates up to 2400 Baud, has self contained operating system.

Synchime. Simulate bells, gongs, etc., with this interesting project.

Dragon 32 RS232/Modem Interface. Plugs directly into ROM expansion port, has programmable word format.

CodeLock. A programmable electronic lock which has many applications.


Logic Probe. Digital display instantly shows CMOS logic states

Minilab Power Supply. A versatile unit for your test bench.

Dragon 32 I/O Ports. Two 8 bit ports; plugs into cartridge socket.

Doorbell for the Deaf. Flashes a bulb to attract attention.

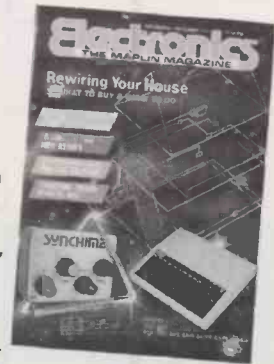All this for only 70p. Order As XA08J (Maplin Magazine Volume 2 Issue 8) Price 70p NV.



Electronics Issue 9

Copies of issue 9 are still available, contents include:

Spectrum Keyboard. 47 full size, full travel, keys; including single key Graphics, Shift lock, Delete, etc. Plugs directly into expansion port,

VIC Extendiboard. Provides three expansion ports — one switchable.

Oric Talkback. A speech synthesiser for the Oric 1 with vast vocabulary.

Infra-Red Movement Detector. Fitted outside can detect people 30m away.

TDA7000 FM Radio. Easily built radio — requires no alignment.

ZX81 High Resolution Graphics. Full 256 x 192 fine pixel display, draw patterns, textures, etc. Operates from extended BASIC.

Ten More Projects! including; Dynamic Noise Limiter for personal stereo, Logic Pulser, 1K Extendi-RAM for ZX81, TTL/RS232 Converter, Pseudo Stereo AM Radio, plus lots more.

All this for only 70p. Order As XA09K (Maplin Magazine Volume 3 Issue 9) Price 70p NV.



Electronics Issue 10

Copies of issue 10 are still available, contents include:

Spectrum Easyload. Novel battery powered unit will enhance cassette loading with the Spectrum.

80m Receiver. Single-sideband, direct conversion, easy to build and align.

Fluorescent Tube Driver. An 8 Watt 12 Volt unit; ideal for camping, etc.

2.8kW Power Controller. A versatile device which will handle up to 2.8kW.


Auto-Waa. Automatically produces Waa-Waa type effects.

Digi-Tel Expansion. Enables the Maplin Digi-Tel telephone exchange to be expanded to accommodate 32 extensions.

Oric 1 Modem Interface. Connect the Maplin Modem to an Oric.

Dragon Extendiport. This project enables the cartridge socket on the Dragon 32 to be brought to a more accessible position.

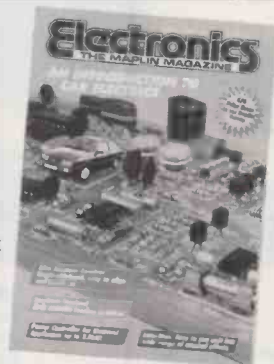All this for only 70p. Order As XA10L (Maplin Magazine Volume 3 Issue 10). Price 70p NV.



Electronics Issue 11

Copies of issue 11 are still available, contents include:

Mapmix. Six channel mono/stereo, battery operated audio mixer.

Xenon Tube Driver. Compact driver, module with internal strobe oscillator.

Enlarger Exposure Meter. A simple & inexpensive meter with a wide range.

8 Channel Fluid Detector. Monitor fluid level with 8 LED display or check for fluid level in up to 8 containers.

Servo & Driver Module. Complete servo mechanics & driver module kit.

Mark II Noise Reduction Unit. An enhanced design of the Noise Reduction Unit, improves signal-to-noise ratio by 30dB.

Cautious Ni-Cad Charger. This advanced design features; multiple cell charging, auto discharge, fast charge & much more

Motherboard for the BBC Micro. Gives easy access to ports.

All this for only 70p. Order As XA11M (Maplin Magazine Volume 3 Issue 11) Price 70p NV.



ANTEX a world of soldering



Professional Precision for the Amateur Enthusiast.

ANTEX has a worldwide reputation for quality & service & for many years has been one of the best known & most popular names in soldering. Always at the forefront of technology, ANTEX is continually researching new and better ways of achieving more accurate, reliable, and cost effective soldering. On ANTEX Soldering Irons, the advanced design of the interface between the element & the bit allows more efficient heat transfer to the bit and improved stability of the temperature at the point of contact with the work. Indeed, experiments have shown that an X525 watt iron can be used for tasks where a 40 watt iron would normally have been required.

ANTEX Soldering Irons exhibit exceptionally low leakage currents & hence are suitable for use on Static Sensitive Devices. Sophisticated temperature controlled soldering units have recently been added to the ANTEX range.



SK5 Soldering Kit

Model XS

Model CS

Model C

TCSU-D
Temperature-Controlled
Soldering Unit

ST4 Stand

TCSU1 Soldering Unit

Model C
15 Watts 240V miniature soldering iron.
Order As FJ44X Price £6.75

Model CS
17 Watts 240V miniature soldering iron
Order As FY62S Price £6.95

Model XS
25 Watts 240V general purpose soldering iron
of an exceptionally high standard.
Order As FR12N Price £7.25

ST4 Stand
Suits all irons.
Order As FR20W Price £2.75

SK5 Soldering Kit
Contains model CS 240V soldering iron, an ST4
stand, solder and a booklet of hints on soldering.
Order As FY68Y Price £9.95

Model TCSU1
A very robust 240V soldering unit with a choice of
30W (CSTC) or 40W (XSTC) temperature controlled
irons. Temperature range 65°C to 420°C. Accuracy 2%.
Order As XG55K (CSTC) Price £68.95
XG56L (XSTC) Price £68.95

All prices include VAT and postage and packing.

SK6 Soldering Kit
Contains model XS 240V soldering iron, an ST4
stand, solder and a booklet of hints on soldering.
Order As FY69A Price £10.15

Model TCSU-D
An elegantly designed, moderately priced,
240V temperature controlled soldering unit giving an
accurate and continuous display of soldering
temperature. The unit is built around a unique ULA;
custom-built by Ferranti especially for Antex.
Temperature range ambient to 450°C. Accuracy $\pm 5^\circ\text{C}$.
Supplied with 50W iron (XSD). Other features include
zero-crossing switching and detachable sponge tray.
Order As XG57M Price £79.95